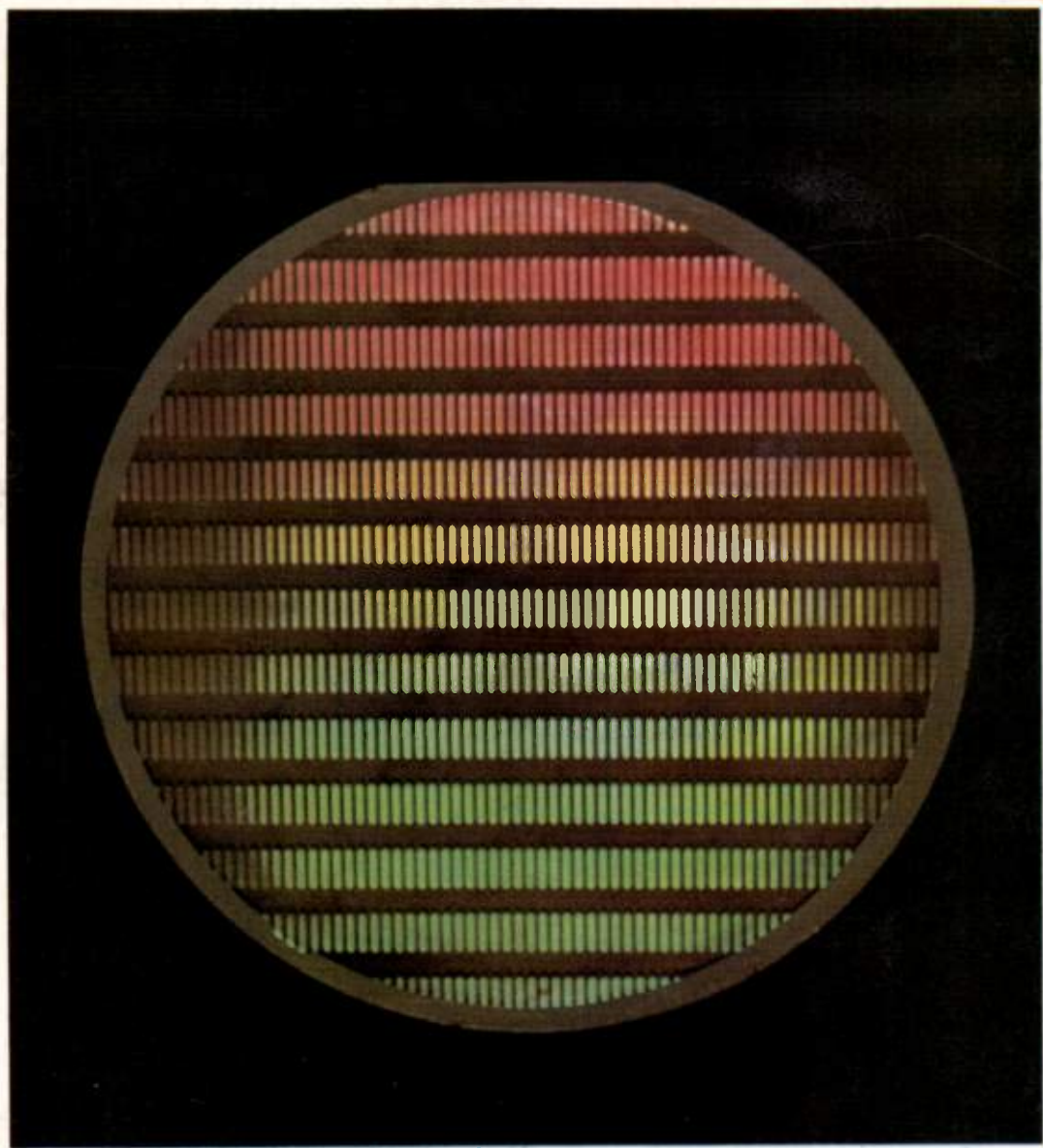


rad design




VICTABOOSU2 RFL101902MCJAG091
ALAN M VICTOR/SIF ENG SAM/AI782608106
MOTOROLA COMM DIV
8000 W SUNRISE RM 2332
SUNRISE FL 33322

**SAWS Cut Away Circuit Complexity
Chebyshev Filter Selection . . . Again
“L” Matching Hybrid**

MILESTONES IN TECHNOLOGY

ONE OF A SERIES

High Volume Schottky and PIN Diodes

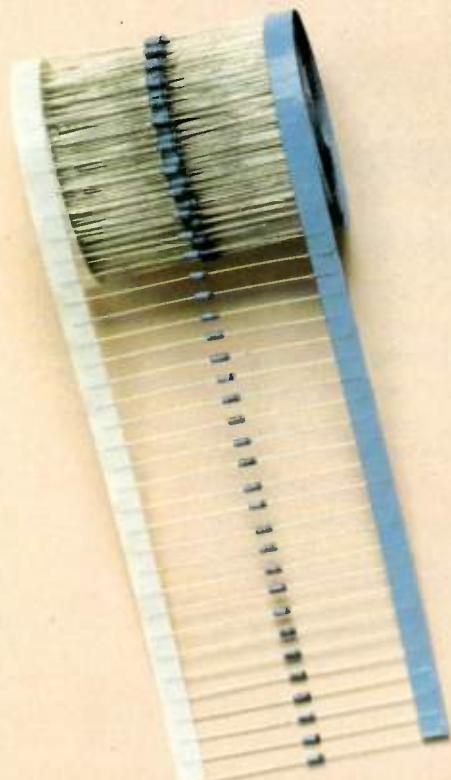


MOBILE COMMUNICATIONS •
CATV • DIGITAL SWITCHING

These *low cost* axial-lead glass diodes are ideal for use as attenuators, switches, mixers, or detectors in commercial applications. Representative of today's microwave technology, these diodes exhibit performance characteristics far superior to UHF devices. Key typical characteristics for a few typical models are shown in the table.

TYPICAL CHARACTERISTICS

Application	Type	Model MA-	V_B (Min.)	V_F (Max. @ 1 mA)	C_T (pF-Max.)	R_S (Ohms @ 100 mA)	R_S (Ohms @ 1 mA)	R_S (Ohms @ 0.01 mA)	T_L (μ s)	Max. T_L (ps @ 5 mA)
Switch	PIN	4P205	100	—	1.0 @ 50V	0.4	4	250	1.0	—
Attenuator	PIN	4P208	100	—	0.4 @ 50V	5	90	5000	4.5	—
Detector/ Switch	Schottky	4E2800 (1N5711)	70	0.410	2.0 @ 0V	—	—	—	—	100
Mixer	Schottky	4E2810 (1N5712)	20	0.550	1.2 @ 0V	—	—	—	—	100
Detector	Schottky	4E2835	5	0.340	1.0 @ 0V	—	—	—	—	100

HIGH VOLUME PINS

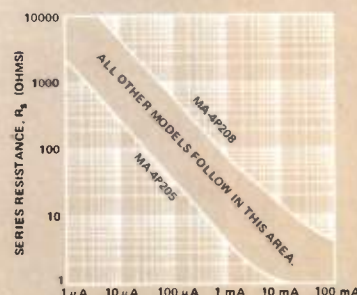

SEND FOR YOUR COPY of
Digital Communications from our
Milestones in Technology series
along with specifications of *High
Volume Schottky and PIN Diodes* —
all packaged in a handy file folder.

M/A-COM



M/A-COM SILICON PRODUCTS, INC.

BURLINGTON, MASSACHUSETTS 01803 • (617) 272-3000

INFO/CARD 24



© 1982

HP Introduces Spectral Excellence!



HP's 8662A Synthesized Signal Generator delivers outstanding spectral purity.

Here's the very best spectral purity you can get for testing systems that depend on a low noise synthesized reference signal in the 10 kHz to 1280 MHz range. Ideal for the most demanding applications like these:

Satellite Applications. Use the 8662A's close-in SSB phase noise (see chart) for communication multiplier chains and up/down converters. 0.1/0.2 Hz steps and excellent long-term phase stability give better ranging and tracking accuracy.

Doppler Radar. Low phase jitter cuts velocity ambiguity. Automate testing with HP-IB.

Out-of-channel Receiver Tests. Uses low SSB noise and spurious. ± 1 dB level accuracy. Programmable.


Automated SSB Noise Measurements. A quiet reference local oscillator.

Frequency Agile Communications. 420 μ s switching speed and very low spurious during switching meets demanding applications like cellular telephone.

New Application Note Available. To find out how HP achieved this spectral excellence and more information

on the 8662A, write for AN 283-1, "Applications and Measurements of Low Phase Noise Signals Using the 8662A" Hewlett-Packard Company, 1820 Embarcadero Rd., Palo Alto, CA 94303.

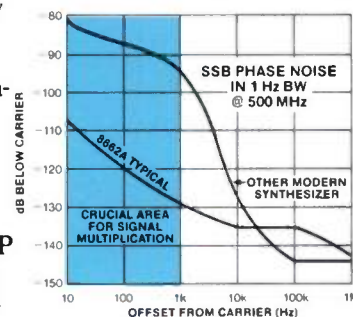8662A, \$32,500*
*U.S. domestic price only.



DESIGNED FOR
HP-IB
SYSTEMS


04103A




**HEWLETT
PACKARD**

INFO/CARD 2

W01

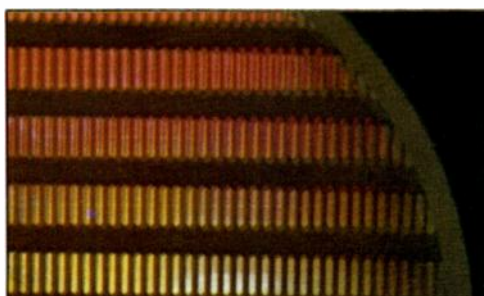

SAWS!

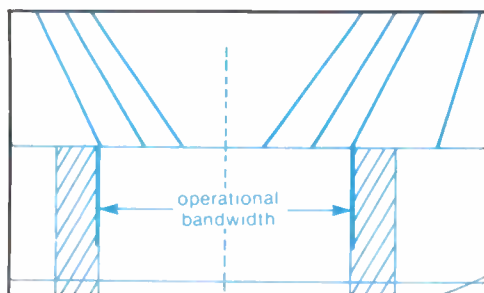

Programmable Calculator Method



Improved Lumped Constant Hybrids

March/April Cover — This a completed three-inch wafer of 680 megahertz resonators prior to cutting. The colors are due to light diffraction by the one micron lines deposited on the substrate.

1

SAWS! Powerful Passives — Second generation SAW filters are providing powerful new alternatives in circuit design.

12

Design RF Amplifiers, Part 1: Using Potentially Unstable Devices — Dealing with the "Catch 22" of conjugating matching both the input and output of a potentially unstable device.

20


A Programmable Calculator Method for Chebyshev Filter Selection — The author is not suggesting discarding your Chebyshev filter tables or curves (he's keeping his!), but rather an alternative procedure for selecting a filter based on an exact solution of the Chebyshev loss equation using a programmable calculator.

26

An Improved Lumped-Constant Hybrid — Here is a lumped-constant "L" matching hybrid which performs better than the conventional lumped-constant Wilkinson Hybrid and is readily constructed at 175 MHz and below. It also readily transforms impedance at the same time as splitting or combining power.

34

Editorial	8	Products	40
Subscription Card	9	INFO/CARD	43
Letters	11	Advertiser Index	50

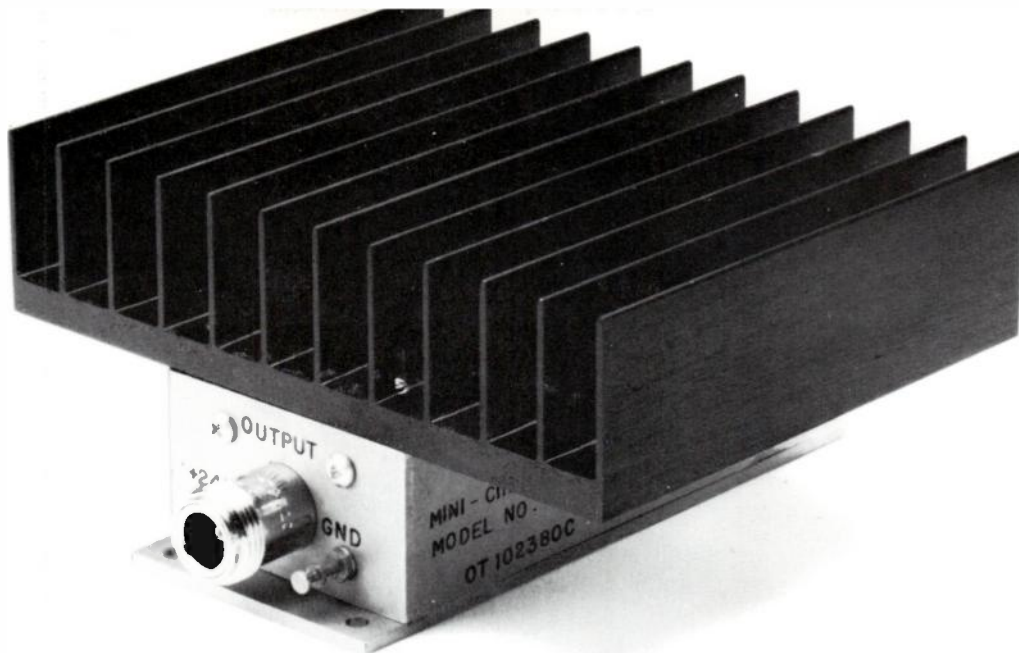

power amplifiers


**1 Watt and now... 2 Watts linear output
from 50KHz to 1200 MHz from \$199**

If your application requires up to 2 watts for intermodulation testing of components... broadband isolation... flat gain over a wide bandwidth... or much higher output from your frequency synthesizer or signal/sweep generator... Mini-Circuits' ZHL power amplifiers will meet your needs, at surprisingly low prices. Seven models are available, offering a selection of bandwidth and gain.

Using an ultra-linear Class A design, the ZHL is unconditionally stable and can be connected to any load impedance without amplifier damage or oscillation. The ZHL is housed in a rugged 1/8 inch thick aluminum case, with a self-contained hefty heat sink.

Of course, our one-year guarantee applies to each amplifier.

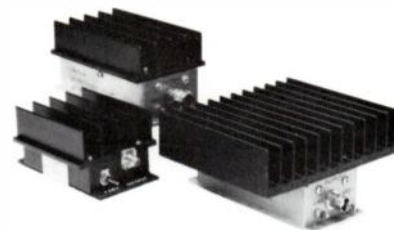So from the table below, select the ZHL model for your particular application... we'll ship within one week!



* Model No.	Freq. MHz	Gain dB	Gain Flatness dB	Max. Power Output dBm 1-dB Compression	Noise Figure dB	Intercept Point 3rd Order dBm	DC Power		Price	
							Voltage	Current	\$ Ea.	Qty.
ZHL-32A	0.05-130	25 Min.	± 1.0 Max	+29 Min.	10 Typ	+38 Typ.	+24V	0.6A	199 00	(1-9)
ZHL-3A	0.4-150	24 Min.	± 1.0 Max	+29.5 Min.	11 Typ.	+38 Typ.	+24V	0.6A	199 00	(1-9)
ZHL-1A	2-500	16 Min.	± 1.0 Max	+28 Min.	11 Typ.	+38 Typ.	+24V	0.6A	199 00	(1-9)
ZHL-2	10-1000	15 Min.	± 1.0 Max	+29 Min.	18 Typ.	+38 Typ.	+24V	0.6A	349 00	(1-9)
ZHL-2-8	10-1000	27 Min.	± 1.0 Max	+29 Min.	10 Typ.	+38 Typ.	+24V	0.65A	449 00	(1-9)
ZHL-2-12	10-1200	24 Min.	± 1.0 Max	+29 Min.	10 Typ.	+38 Typ.	+24V	0.75A	524 00	(1-9)
ZHL-1-2W	5-500	29 Min.	± 1.0 Max	+33 Min.	12 Typ.	+44 Typ.	+24V	0.9A	495 00	(1-9)

Total safe input power +20 dBm, operating temperature 0° C to +60° C, storage temperature -55° C to +100° C. 50 ohm impedance, input and output VSWR 2:1 max. +28.5 dBm from 1000-1200 MHz

For detailed specs and curves, refer to 1980/81 MicroWaves Product Data Directory, Gold Book, or EEM

* BNC connectors are supplied; however, SMA, TNC and Type N connectors are also available.

Mini-Circuits

A Division of Scientific Components Corporation
World's largest manufacturer of Double Balanced Mixers
2625 East 14th Street, Brooklyn, New York 11235 (212)769-0200
Domestic and International Telex 125460 International Telex 620156

INFO/CARD 3

6

Solutions VHF




12
TO-72



32
TO-92



33
SOT-23

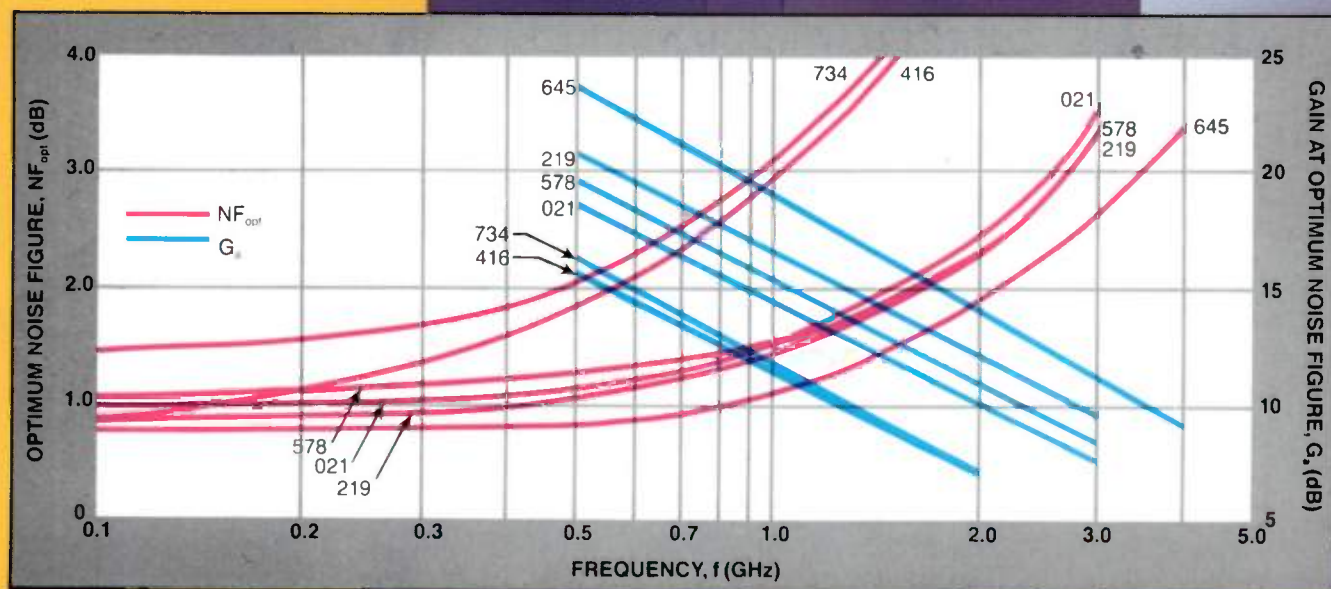

NEC microwave semiconductors

...to your low cost UHF & MW problems

NE021 — NE219 — NE416 — NE578 — NE645 — NE734

These famous high performance small signal NPN transistors from NEC are now available in one or more low cost packages and at prices you can afford for virtually all your VHF, UHF, and MW applications.


They feature the NEC highly reliable metallization system of platinum-silicide, titanium, platinum and gold which provides consistent high temperature operation at rated dissipation.

The highest degree of performance, uniformity and reliability are assured by NEC's famous quality control and test procedures patterned after MIL-S-19500.

Devices in the famous "MICRO-X" package (#35) are available with either JANTX or JANTXV equivalent screening and are highly recommended for high performance military and communications applications.

Step up to quality and performance at the right price.
SPECIFY NEC.

INFO/CARD 4

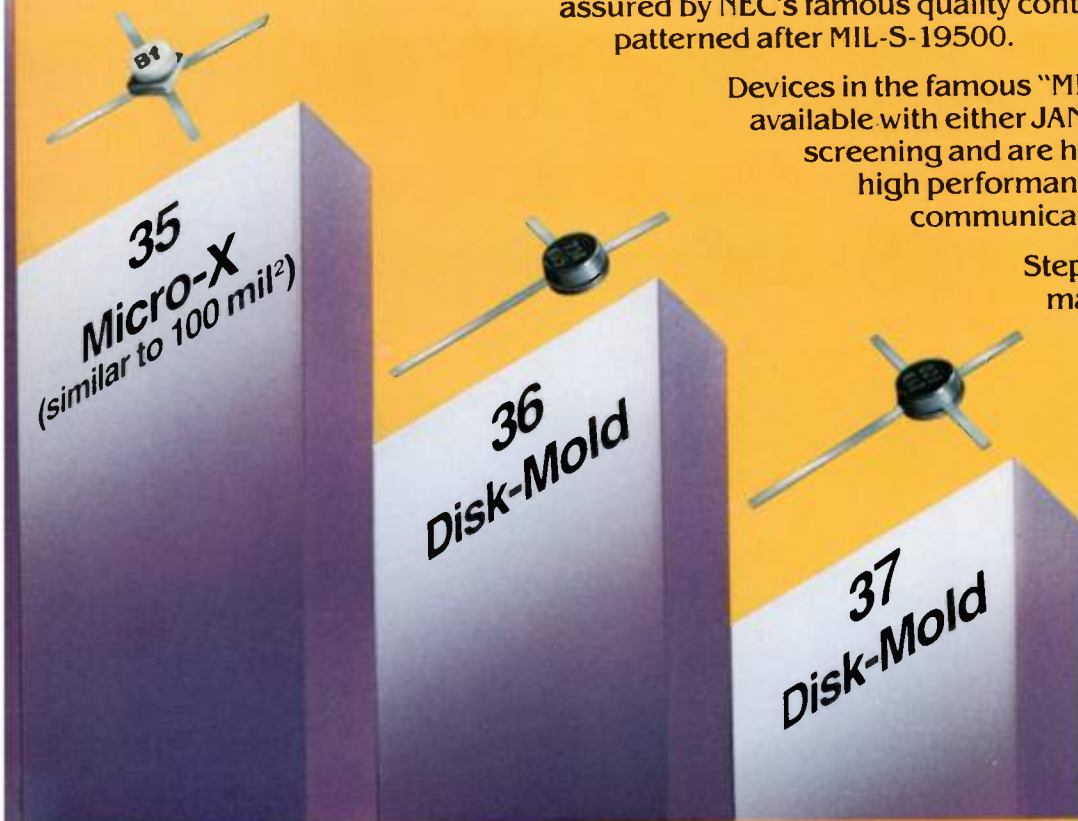

CALIFORNIA EASTERN LABORATORIES, INC. — U.S. and Canada
Exclusive sales agent for **Nippon Electric Co., Ltd.** Microwave Semiconductor Products.



3005 Democracy Way, Santa Clara, California 95050 • Tel. (408)988-3500 • Tlx. 346393 or 171197



Publisher
Bill W. Childs

Editor
Larry Brewster

Consulting Editor
E. Patrick Wiesner

Sales Manager
Ruth Breashears

Account Executives
Blair S. Meador
Suzan Myers
Dianne Oveson

Editorial Review Board
Alex Burwasser
Rob Coe
Doug DeMaw
Hank Keen
Dave Krautheimer
Ed Oxner
Andy Przedpelski
Jeff Schoenwald
Raymond Sicotte

Advertising Services
Doug Lumdsden

Production Manager
Dara Hinshaw

Group Art Director
Mike Morris

Artist
Tim Gabor

Composition
Daniel P. Jones
Dana Harris

Published by



Cardiff Publishing Company
Subsidiary of Cardiff Communications, Inc.
6430 S. Yosemite St.
Englewood, Colo. 80111
(303) 694-1522

For subscription inquiries please contact
Cardiff Publishing Circulation Service
Center, P.O. Box 1077, Skokie, IL 60077

Chairman
Stanley M. Searle


President
Robert A. Searle

Treasurer
Patrick T. Pogue

Vice President
Phil D. Cook

Circulation Manager
Sandra Gill

Circulation Assistant
Joyce Yates

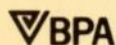

Looking Ahead

Each year, most of us look forward to another year; and some of us initiate plans that will bring us toward certain year-end goals. This year, we have been a few months late in getting our 1982 plans off to a timely start. I am, however, now in the position to share with you some 1982 planning that I am very pleased with.

First of all, with the last issue of the magazine and in all future issues, you will begin to see pleasing changes in the magazine. More color and larger issues are just two of the many goals established for *R.F. Design* magazine. Naturally, we plan to maintain the high quality you have come to expect in the articles throughout the year.


The last three issues of 1982 will be especially interesting. In addition to the usual menu of good RF technical articles, each issue will provide an opportunity for you to win a \$1000 U.S. Savings Bond by understanding what makes your fellow engineers read advertisements and technical articles.

- In July/August, a contest to rank the ads in order of readership
- In September/October, a contest ranking technical articles in order of helpfulness
- In November/December, a "super contest" to design a circuit or system using items advertised.

In 1982, I am going to look forward to bringing you better issues of *R.F. Design* magazine. Also, if you are in Boston for Electro 82, please stop by our booth, pick up a fresh issue of the May/June magazine, and meet our new and expanding staff.

Thank you.

Bill W. Childs
Publisher

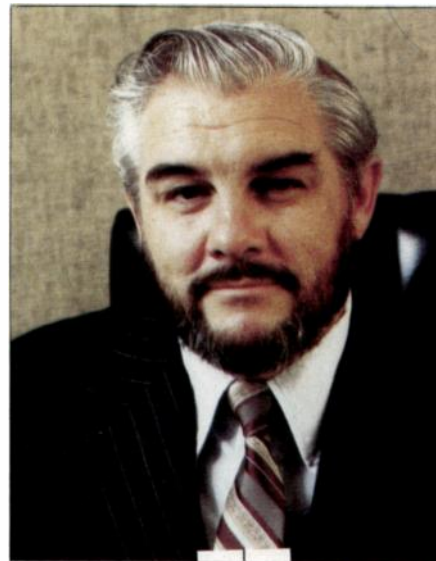

Interesting Problem

Dear Sir:

Is there any way we can appeal to your readers for assistance in the following problem?

Motorola has discontinued manufacturing the MPS-H83 transistor, a UHF pnp AGC-able device having no second source or equal alternative. Motorola's stock and all distributor stocks are used up. We received no notice of this, and badly need about 500 pieces quickly to tide us over until a redesign can be completed.

Perhaps somewhere on a shelf are 500 such transistors no longer needed by the owner. Do you know of any route through which we might contact such a surplus stock, if it exists? Motorola has not been able to help us.

J.W. Streater
Chief Engineer
Mentor Radio Company
1561 Lost Nation Road
Willoughby, Ohio 44094
(216) 942-2025

Stability Circles

Dear Editor:

In Marty Jones' recent article, "High Frequency Transistor Amplifier Design," Nov./Dec. 81 issue, the author discusses stability circles and states that "an individual impedance point must be evaluated to determine whether the interior of the circle is the unstable region." Actually, the origin of the Smith Chart serves this purpose ideally. Since the stability circles describe a boundary condition, all points inside are stable (unstable) if any point inside is stable (unstable). From the non-unilateral port reflection equations:

$$S'_{11} = S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L} \quad \left| \Gamma_L = 0 \text{ (50}\Omega \text{ load)} \right. = S_{11}$$

$$S'_{22} = S_{22} + \frac{S_{12} S_{21} \Gamma_s}{1 - S_{11} \Gamma_s} \quad \left| \Gamma_s = 0 \text{ (50}\Omega \text{ source)} \right. = S_{22}$$

Assuming the transistor (or two-port) was stable when characterized in a 50 Ω system, $|S_{11}| < 1$ and $|S_{22}| < 1$. In other words, the origin represents a stable termination. It is then safe to say that, for such a two-port, if the stability circle encompasses the origin, all points within the circle represent a stable termination. If the circle does not enclose the origin, all points inside are unstable.

Hal Hamilton
Sr. Staff Engineer
Motorola Government Electronics Division

r.f. design

EAS


ELECTROLINE'S ADDRESSABLE SYSTEM

**A cost-effective system
offering maximum security
with ease of control for
multi-unit buildings.**

EAS

Designed to control access or premium service to subscribers in multidrop buildings. The system is modular in design. Security is maintained by means of continuous scanning. EAS is ideal for apartments, hotels, hospitals or other such location where constant control is needed and to provide visual audit of each subscriber's status.

ADDRESSABLE SYSTEM

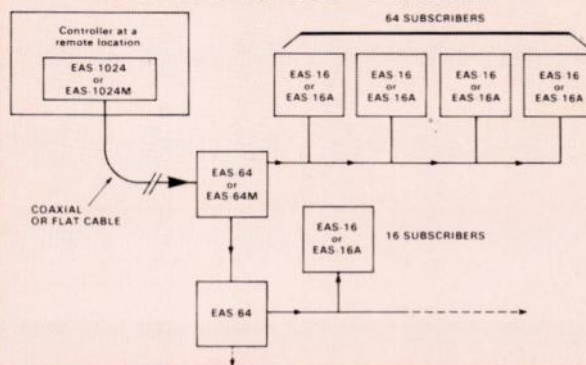

EAS

The above system is composed of 3 units — a microprocessor control (EAS-1024); a decoder (EAS-64); and a wide-band, multitap switch assembly (EAS-16). The system can be installed in 2 alternative configurations and is most compatible with other systems.

Illustrated folder with specifications upon request.



ELECTROLINE Television Equipment Inc.

8750, 8th Avenue . St-Michel
Montreal, Que. H1Z 2W4

or phone **collect**
(514) 725-2471

Representatives across
Canada and the U.S.A.

- ☐ TAPS
- ☐ FILTERS
- ☐ COUPLERS
- ☐ SPLITTERS
- ☐ SPECIAL AMPLIFIERS
- ☐ SWITCH-TRANSFORMERS

INFO/CARD 5

SAWS!

By Darrel L. Ash
Vice President Engineering
and Richard H. McLean
Vice President Sales
RF Monolith
Dallas, Texas

When Surface Acoustic Wave devices entered the marketplace some 15 years ago, first applications were found in certain government-related programs where the initial high cost could be justified by the size/performance advantages they offered.

Tediously fabricated and produced in small quantities, outstanding performance was achieved in applications such as radar signal processing and high resolution counter-measures receivers. Further applications have been successful in major U.S. Defense Programs, making use of SAW delay line oscillators and SAW correlators for spread-spectrum communications.

During this period, low-frequency SAW filters found use in television receivers in large quantities and at very low cost.

These "First-Generation" series of designs generally resulted in size-efficient filters, generally below 100 MHz

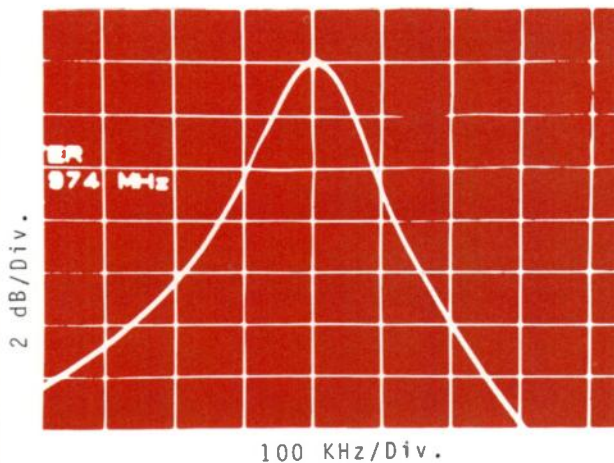


Figure 1A. SAW Resonator Frequency Response.

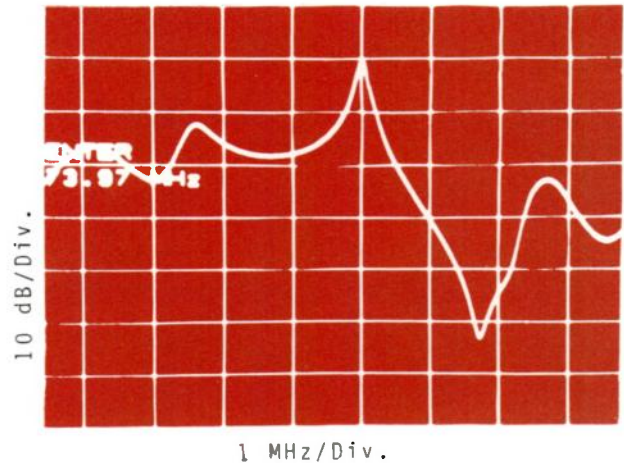


Figure 1B. SAW Resonator Frequency Response.

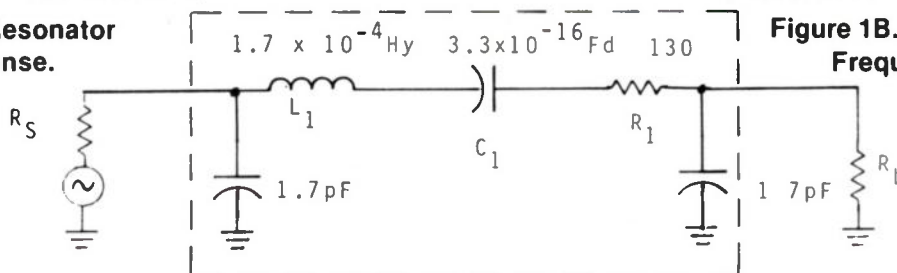


Figure 1C. SAW Resonator Equivalent Circuit.

POWERFUL PASSIVES

Second generation SAW filters are providing powerful new alternatives in circuit design.

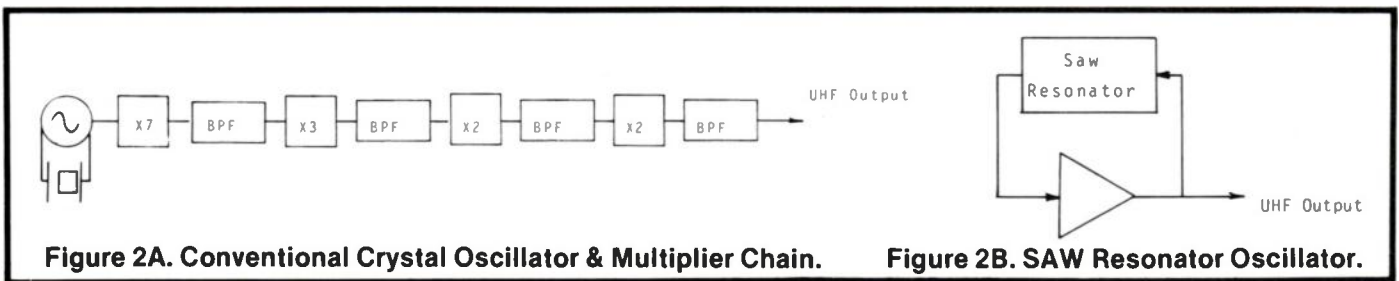


Figure 2A. Conventional Crystal Oscillator & Multiplier Chain.

Figure 2B. SAW Resonator Oscillator.

and usually exhibiting insertion loss figures in the 25 dB area. Given this background, a new awareness began among communications engineers of the benefits in using the technology, requiring less than the exotic designs necessary for reflective array correlators but more powerful devices than the mass-produced video IF TV filters.

This discussion, then, will address the fastest growing segment of SAW applications, generally defined by the frequency boundaries of 40 MHz to 1000 MHz which are being placed into use by the commercial communications industry.

These newer designs may be termed "Second-Generation," in that filters may be produced in the mid-100's frequency range, smaller in size and with much reduced signal loss than their first generation counterparts. Also defined by the second generation label are SAW resonators for use as the frequency-control element for size-and-cost-efficient oscillators, operating directly at frequencies to 1 GHz, while at the same time eliminating crystals, multiplier chains and amplifier stages.

SAW Resonator Applications

A SAW Resonator consists of two reflective gratings forming a resonant cavity with transducer coupling of energy into and out of the cavity. The typical unloaded Q range is from 50,000 to 5,000 depending on center frequency, reflector array size, and other factors. Center frequencies up to 1000 MHz are attainable within that Q range. Figure 1 includes photographs of the frequency responses of a two port 674 MHz resonator, presently being mass produced, as well as its equivalent circuit. The equivalent circuit (within the dash lines) consists of a series resonant

circuit with a series Q-determining resistor and shunt capacitances to ground at each port.

The high Q and low spurious modes exhibited by SAW resonators make them ideal frequency references for oscillator circuits. Figure 2A is a block diagram of a crystal oscillator and frequency multiplier chain which is typical of the approach presently used to obtain a stable, fixed UHF output for local oscillator or transmitter applications. Figure 2B is a block diagram of a SAW resonator oscillator with the same UHF output. Figure 3 is a schematic diagram of a SAW oscillator circuit presently in mass production

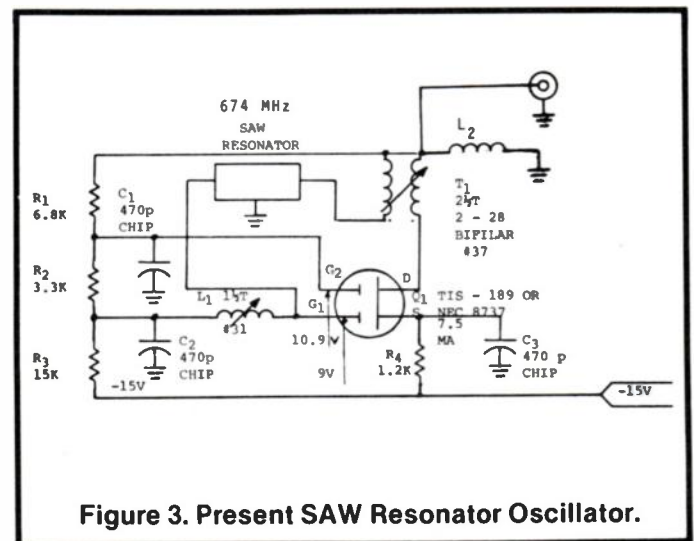


Figure 3. Present SAW Resonator Oscillator.

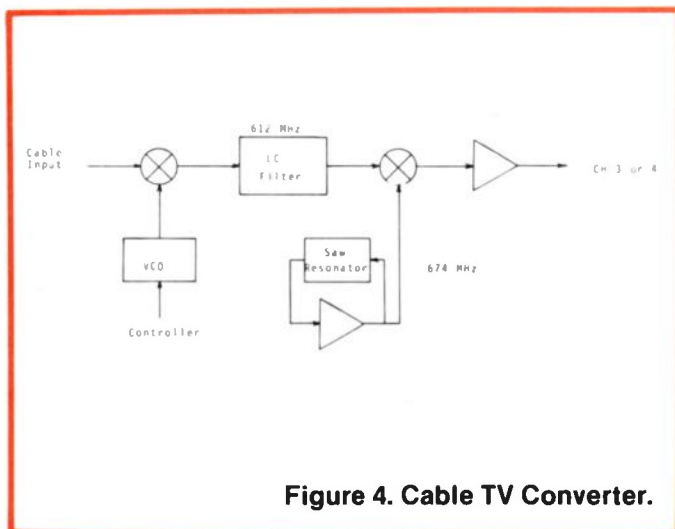


Figure 4. Cable TV Converter.

which accepts resonators with center frequencies from 674 MHz to 680 MHz. The simplicity of the SAW resonator oscillator compared to the crystal oscillator and multiplier chain is obvious. A single transistor amplifier with simple tuned input and output circuits is all that is required in addition to the SAW device to realize a stable UHF oscillator.

Use in Cable TV

The circuit of Figure 3 is presently being used to provide a stable second local oscillator for cable TV converters as illustrated in the block diagram of Figure 4. A stable second local oscillator is needed in cable converters to maintain an output within the AFC pull-range of television receivers using frequency synthesizers and also to interface with descrambler circuits. A 674 MHz L.O. at the second mixer produces a converter output on Channel 3.

Referring to Figure 3 again, the SAW resonator used in this circuit has a phase shift of 0° at the resonator center frequency. The transformer, T1, and inductor, L1, are adjusted to yield a 0° phase shift around the oscillator loop. T1 con-

sists of an air core bifilar-wound coil which couples a portion of the output power back to the amplifier input through the SAW device. A dual gate FET device is used for the amplifier to present a large Q-reducing impedance to the resonator. This particular circuit can be pulled more than 200 kHz by adjusting T1. One disadvantage of this circuit is that it will oscillate only on the high side of the resonator response. Excess phase shift in the transistor (approximately 240° rather than 180°) must be compensated for by using part of the phase slope of the resonator device on the high side of resonance to obtain 0° phase shift around the oscillator loop, since the external tuning elements have too much attenuation at the required phase shift.

The more recent oscillator circuit of Figure 5 can be pulled through the resonator center frequency to either side of resonance. This oscillator uses a resonator device which exhibits a 180° phase shift at its center frequency. The series inductors, L1, and L2, in conjunction with the transistor input and output capacitances and the input and output capacitances of the resonator yield the necessary phase shift around the oscillator loop to compensate for the excess phase shift in the transistor. This oscillator can also be pulled more than 200 kHz by adjusting L2.

Other Uses for the Resonator

The block diagram of Figure 6 illustrates another use for such a SAW stabilized oscillator. A very low cost, single transistor, low power (>0 dBm), stable, FSK transmitter can be realized by adding a varactor diode to pull the oscillator in response to a modulation source.

SAW resonators can also be used as narrow band pass-filters. The block diagram of Figure 7 illustrates how a narrow band receiver can be greatly simplified by using a SAW resonator filter. Most narrow band receivers cannot take advantage of low cost 455 kHz IF filters for the first IF because the resulting image frequency at 910 kHz is too close to the desired frequency to be filtered out in the RF filter in front of the first mixer. Thus, double conversion is usually used in such receivers (10.7 MHz for the first IF and 455 kHz for the second IF). Referring to Figure 1B, the notch on the high side of the resonator response can

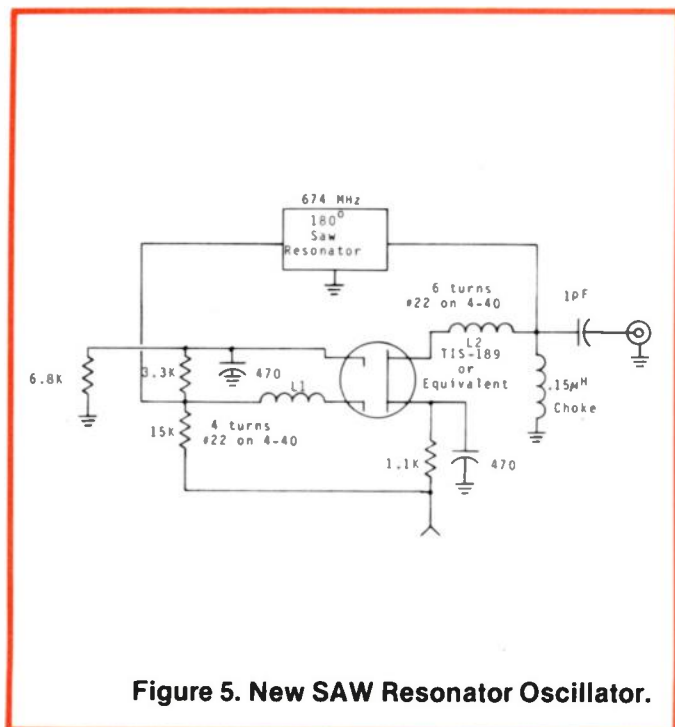


Figure 5. New SAW Resonator Oscillator.


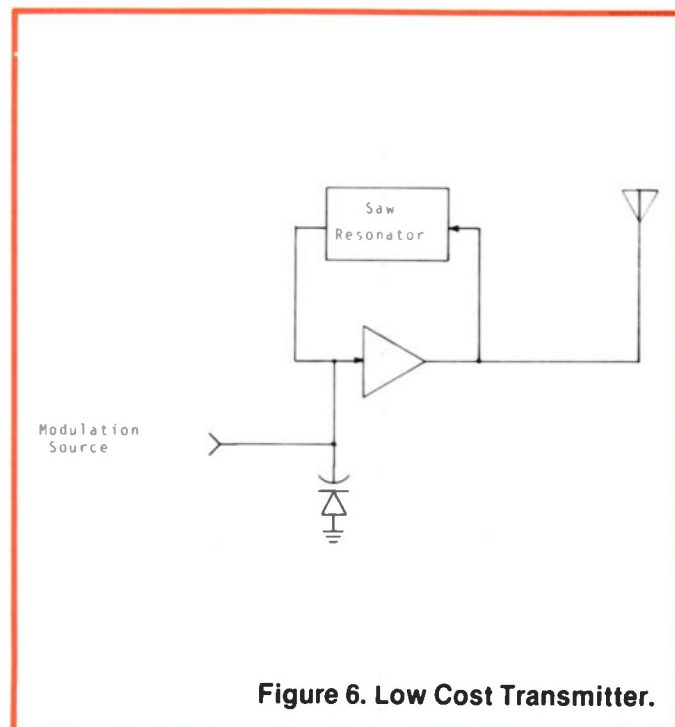



Figure 6. Low Cost Transmitter.

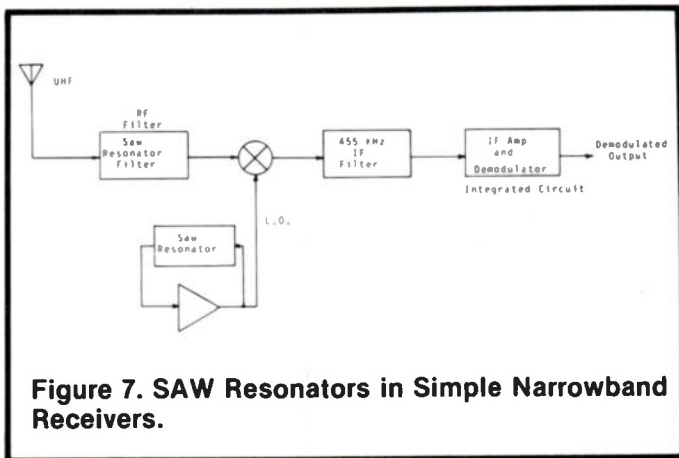

be placed 910 kHz above the response by a simple design change. Thus, an image rejection of ~ 50 dB would be obtained at RF with a single resonator filter. Of course, a SAW resonator could also be used for the local oscillator rather than a crystal oscillator and multiplier chain which would further simplify the receiver. The result is a very low cost, high performance, narrow band receiver.

Notch Filter

Figure 8 schematically illustrates how a SAW resonator with 180° phase shift at center frequency can be used in a narrow notch filter configuration. A feedback resistor is added whose resistance is equal to the internal resistance of the resonator. This produces a null at the resonator center frequency. The pass-band insertion loss is the loss of the feedback resistor. A lowpass filter network making use of the resonator shunt input and output capacitance can be added to the simple circuit of Figure 8 to further decrease the passband insertion loss. The response of such a notch filter at 674 MHz is shown in the photographs of Figure 9. The notch depth was 65 dB and the pass-band insertion loss was 3 dB.

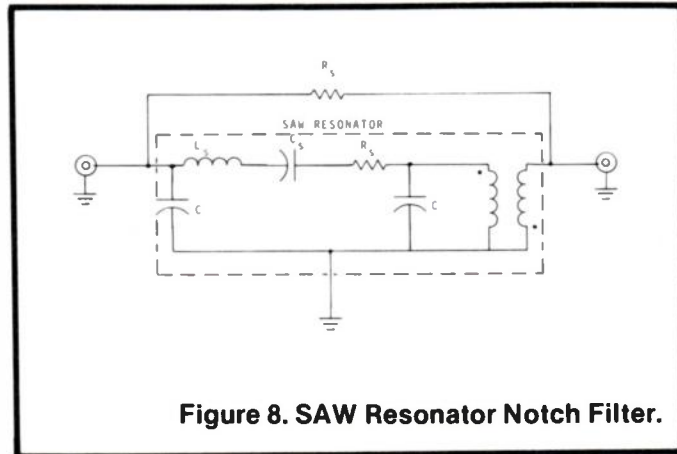

Determining Resonator Bandwidth

Roughly stated, loaded Q (Q_L) will be approximately equal to resonant frequency divided by bandwidth, and can be calculated from the RLC relationship shown in Figure 1C. Since the equivalent circuit for the resonator is a series resonant circuit, the bandwidth can be increased by increasing the source and/or load resistance, R_s and R_L in Figure 1C.

$$Q_u = \mu L / R_1 \text{ where } \mu = 2\pi f_0$$

Loaded Q (Q_L) appears as:

$$Q_L = \mu L / (R_1 + R_s + R_L)$$

Saw Filters

The SAW filters presently in use in TV IF's are simple transducer based filters with high insertion loss (20 dB typical). Such a high loss requires that additional gain blocks be added in front of the filter to avoid noise figure degradation. However, gain blocks in front of the IF filter are not protected from large interfering signals and are potential sources of cross modulation and intermodulation distortion.

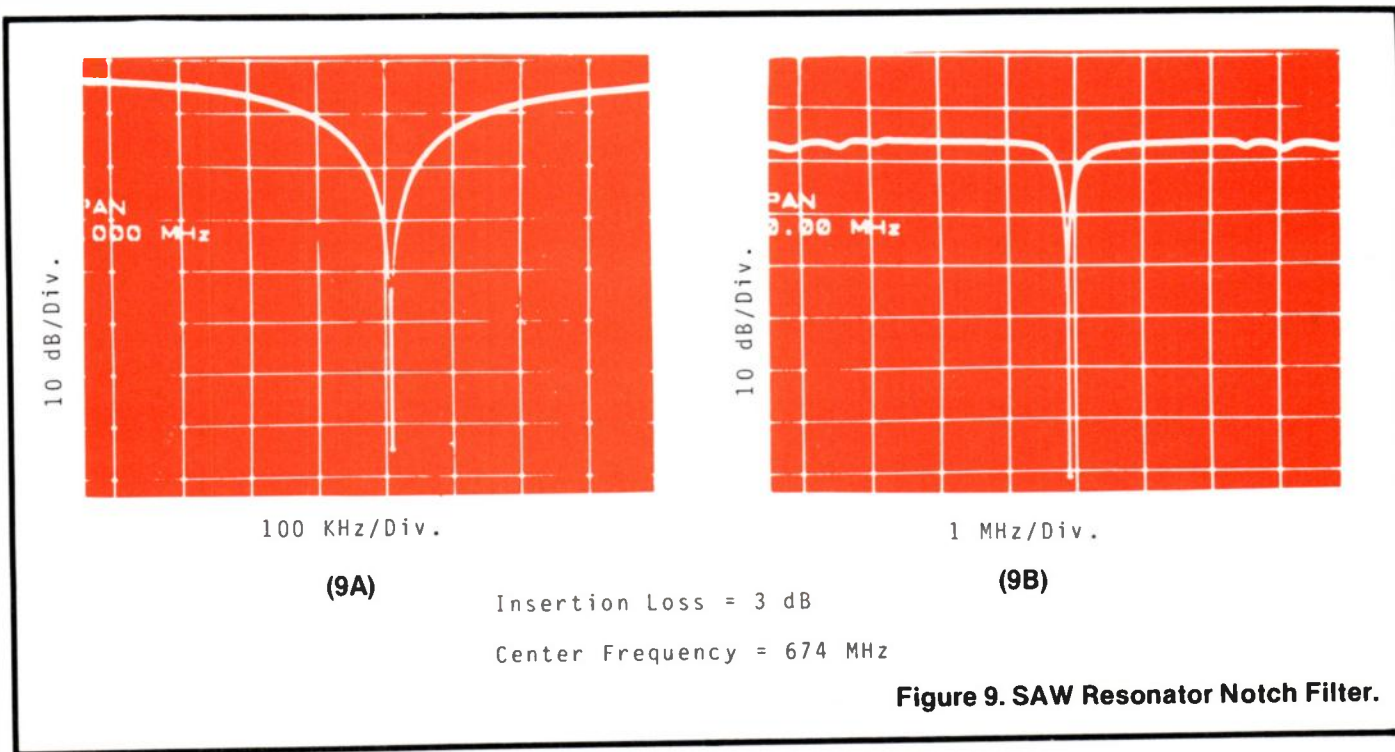


Table I
Broadband Band Pass Filters

	Demonstrated	Production	Projected Practical Limits
Center Frequency	1.0 MHz-2.75 GHz	10 MHz-1.0 GHz	10 MHz-2.0 GHz
Minimum Insertion Loss	0.65 dB	2.0 dB	1.0 dB
Maximum Fractional Bandwidth	100%	50%	100%
Sidelobe Rejection	70 dB	60 dB	90 dB
Minimum Bandwidth	100 kHz	100 kHz	50 kHz
Minimum Transition Bandwidth	100 kHz	100 kHz	50 kHz
Minimum Shape Factor	1.15	1.2	1.1
Triple Transit Suppression	55 dB	45 dB	60 dB
Amplitude Ripple	± 0.02 dB	± 0.05 dB	± 0.01 dB
Phase Deviation from Linear	$\pm 0.1^\circ$	$\pm 2^\circ$	$\pm 0.1^\circ$

New Designs — New Applications


A second generation of mass producible SAW filters is now available. These filters offer low insertion loss, low triple transit distortion, independent tailoring of magnitude and phase response, excellent out-of-band rejection, and center frequencies approaching 1 GHz. Table I is a summary of absolute minimums and maximums both demonstrated and projected for this second generation of filters.

These devices are three-phase transducer based filters with three electrodes per wavelength on the substrate driven 120° out of phase. As a result, the matching network is more complex than that for first generation high loss filters, but the resulting improvement in system performance and the elimination of gain blocks is more than a fair trade-off. Figure 10B includes a schematic diagram of the equivalent circuit of a three-phase unidirectional transducer within the dashed lines. The necessary transformation

from a single phase driving source to a three phase driving source is accomplished using a 60° Pi phase shifting network schematically illustrated in Figure 10A. The design of the network is straight-forward, as shown in Figure 10. An L-network is used to obtain the desired impedance match. The resulting matching network consists of three coils and one capacitor for each of the two three-phase transducers.

Wide-band Receivers

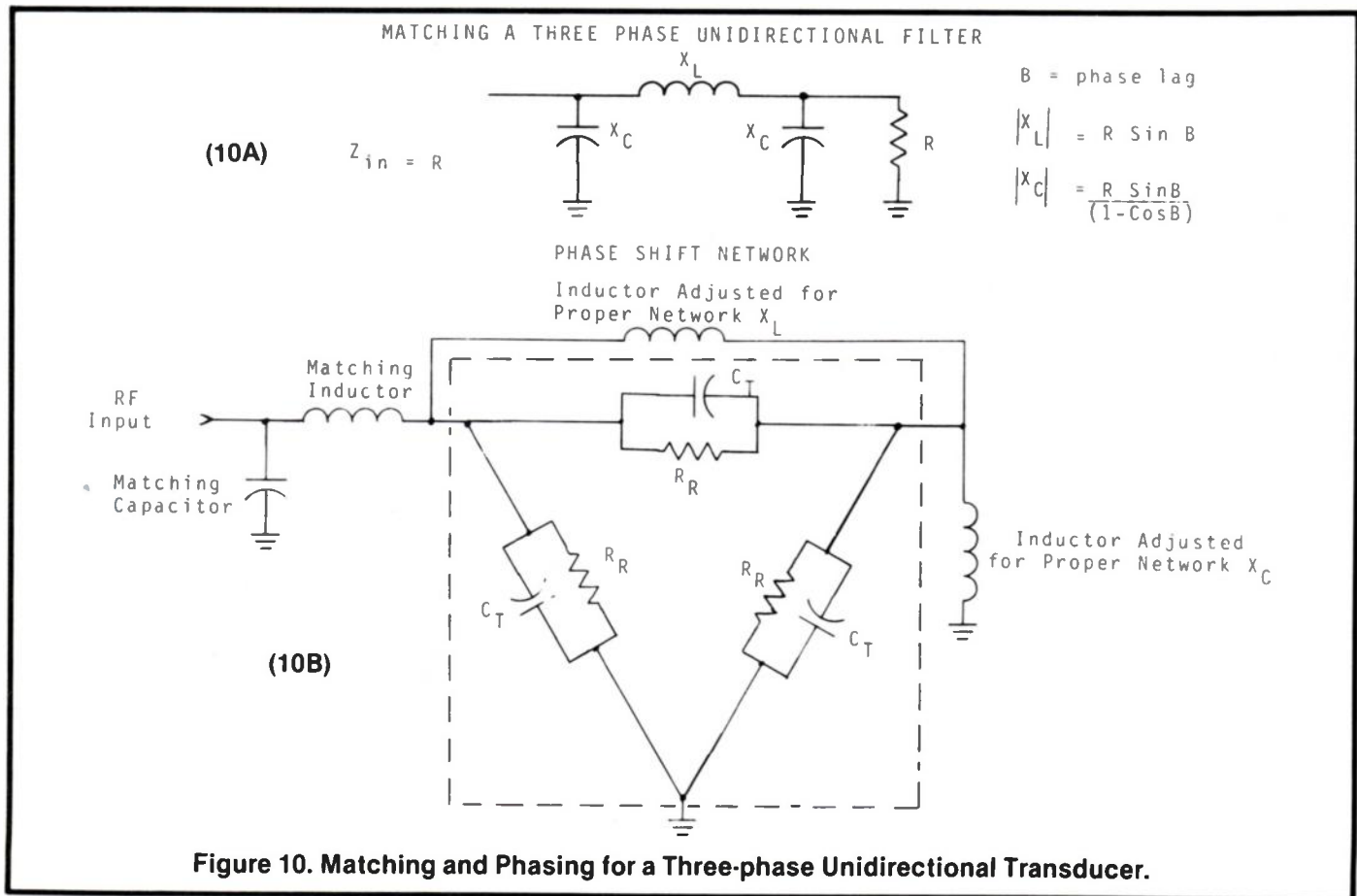Given the low loss, excellent out-of-band rejection, and independent magnitude and phase response exhibited by the unidirectional low-loss filter, as well as a center frequency in the UHF band, a means of simplifying wide band receivers becomes evident. A common problem in broadband systems such as television receivers is spurious



Some modulation meters are really slow and cumbersome to use, which can easily lead to profanity. That's why we designed the Model 4101 to set up fast—on the bench or in the field—and to make many different AM and FM measurements quickly, accurately, and automatically.

Simple pushbutton controls select function, meter range, filter, and

de-emphasis. A single input gives you sensitivity from 3 mV to 1 V, with a frequency range of 1.5 MHz to 2.0 GHz.

You'll be able to balance transmitter modulation much faster using the Model 4101 "DIFFERENCE" mode. It directly measures the difference between peak and trough.

Besides being fast, accurate,

and easy to use, the Model 4101 is inexpensive—only \$1095. So call us for a demonstration right away. We swear you'll find it worth your time.

Wavetek Indiana, Inc.,
5808 Churchman, P.O. Box 190,
Beech Grove, Indiana 46107. Phone
(317) 787-3332. TWX 810/341-3226.




WAVETEK[®]

Demonstration INFO/CARD 6

Literature INFO/CARD 7

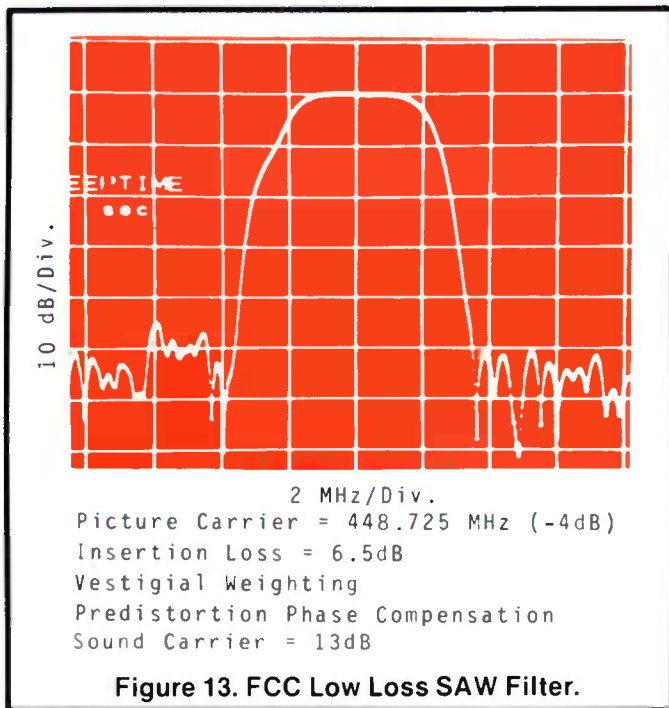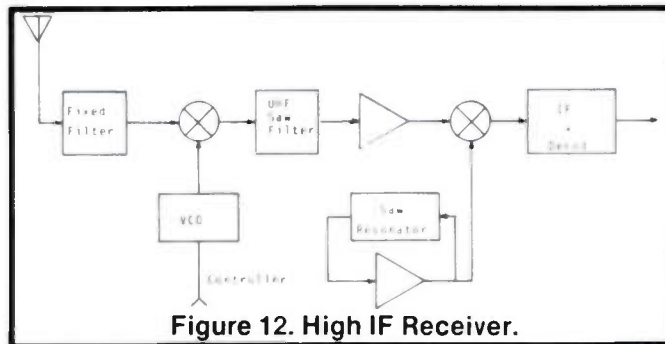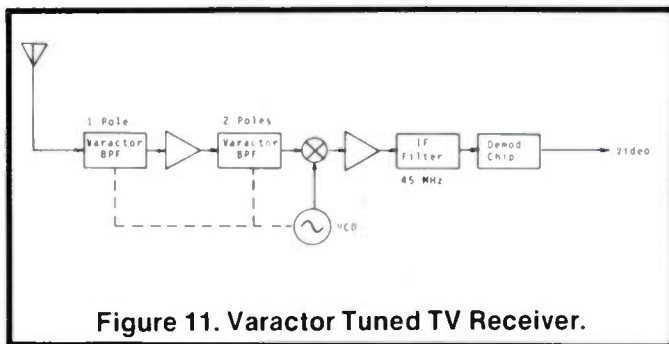You'll swear by our new modulation meter, not at it.






receiver responses to IF related signals. Examples are IF beat, half-IF beat, image response, and local oscillator radiation. This problem is presently addressed using tunable RF filters such as the three pole varactor filters in TV front ends illustrated in Figure 11. However, UHF varactor filters are necessarily broad and have insufficient rejection to eliminate these responses in a system with a 45 MHz IF.

The low loss SAW filter makes it feasible to use a high first IF such as 450 MHz or higher to move the IF related spurious responses out of the desired frequency band. This makes it possible to use a fixed broadband RF filter to eliminate these responses. For example, a 450 MHz IF would have an image response at 900 MHz above the desired RF signal and an IF beat response at 450 MHz above the desired signal. Figure 12 is a block diagram of such a high first IF system. The low loss, UHF SAW filter is capable of rejecting adjacent channels in excess of 50 dB in a TV receiver with an IF of 450 MHz.

As shown in Figure 12, the high IF system would probably make use of double conversion to take advantage of IF gain and demodulator integrated circuits at IF frequencies such as 45 MHz. A SAW resonator oscillator would provide a low cost, stable second L.O. for such a system. The use of a high dynamic range mixer in conjunction with low RF gain minimizes cross modulation and intermodulation in the front end while providing a low system noise figure due to the low loss of the SAW filter. The SAW filter provides the

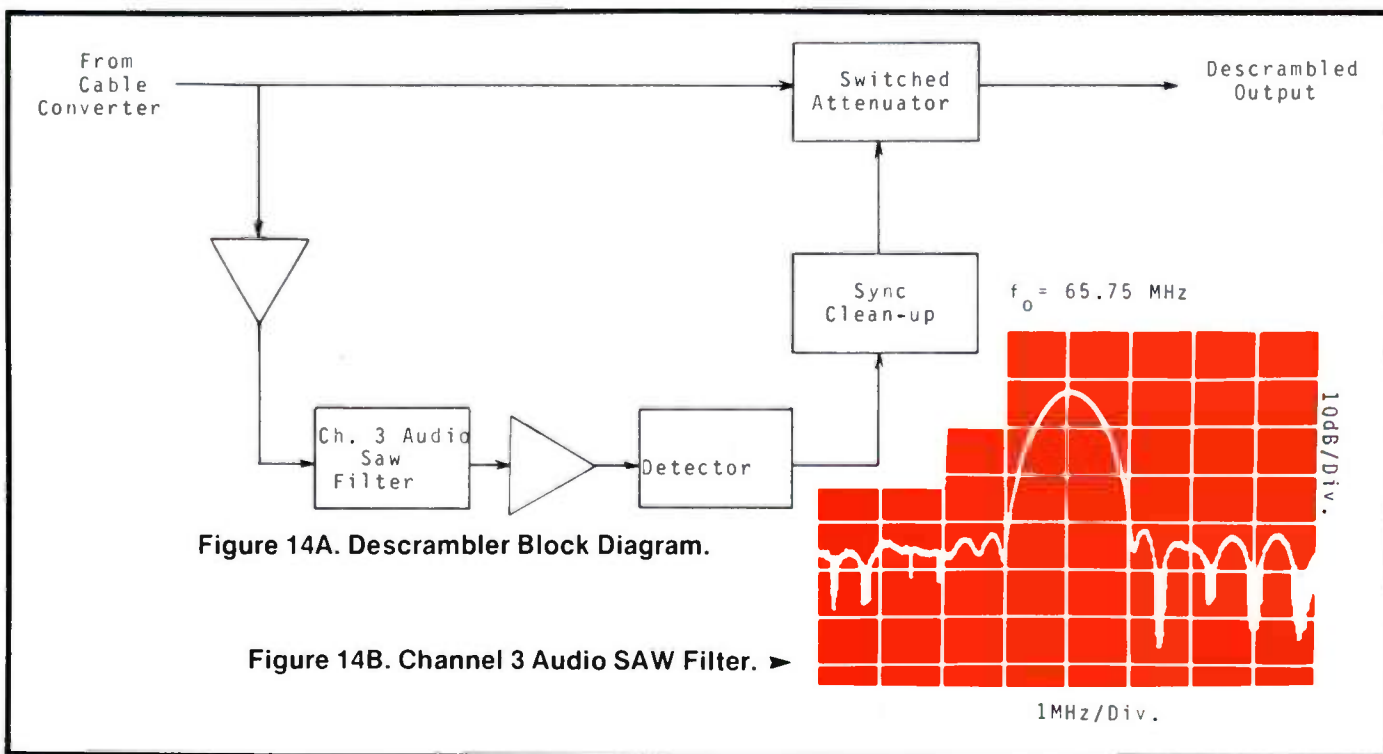

total filtering function as well as any needed phase compensation for predistortion and the like.

FCC Sponsored Receiver

Under a contract with the Federal Communications Commission, this author developed a high IF receiver to show that the UHF interfering signal handling capability of a TV receiver could be greatly improved with a simultaneous improvement in sensitivity or noise figure. The picture carrier frequency in the first IF was 448.725 MHz and a 402.975 MHz SAW resonator second L.O. converted the picture carrier to 45.75 MHz in the second IF.

The frequency response of the low loss SAW filter used in the first IF is included in Figure 13. The filter was vestigially weighted on the picture carrier side (upper side), phase compensation was included for transmitter phase pre-distortion, and adjacent channel rejection was in excess of 50 dB. The magnitude and phase weighting used for this filter also took into consideration other tuned element responses in the system. For example, the picture carrier is 4 dB down on the upper filter skirt, rather than the standard 6 dB, to compensate for a 2 dB roll off in the tuned circuit on the output of the second mixer. This new system exhibits a large improvement in performance over that obtained with present receivers. The performance parameters for this system will be released by the FCC at a later date.

The Low-loss Filter in Cable TV

Referring to Figure 14, another potential application for a low loss unidirectional filter is in the first IF of a cable TV converter to replace the four pole 612 MHz LC filters presently used. Such a filter would greatly reduce potential intermodulation and cross modulation distortion in the converter's second mixer and the TV receiver by rejecting adjacent channels. Alternatively, a low loss Channel 3 SAW filter can be used to reject adjacent channels on the cable converter output if distortion in the converter second mixer is not a problem but TV receiver distortion is a problem.


Other potential applications for such low loss SAW filters and/or resonator filters include satellite links and RF data modems.

"Standard" SAW Filters Still Working


First generation high loss filters, due to their simplicity, will probably continue to be used for applications where high loss does not adversely affect system performance. One example of this is the 45 MHz head end modulator filter which is used to carefully shape the spectral characteristics of cable TV signals. Another function which can be satisfied using a high loss SAW filter is that of a Channel 3 sound carrier filter in a TV descrambler circuit as illustrated in Figure 14A. In such a sync suppression system, the horizontal sync information is derived from the sound carrier. The filter is necessary to avoid interference from the video components of the TV signal which are too close to reliably filter out in mass production with LC filter techniques. Figure 14B is a photograph of the frequency response of a SAW filter designed for this purpose.

Many of these new uses for SAW devices were not even under consideration just a short time ago. As the technology matures, designers feel more secure in specifying them and gaining the improvements offered. No longer laboratory curiosities, SAW components have come of age and can be put to work in all of the above applications as well as many yet to be determined. □

BROADBAND SP2T SWITCHES 20-2000 MHz

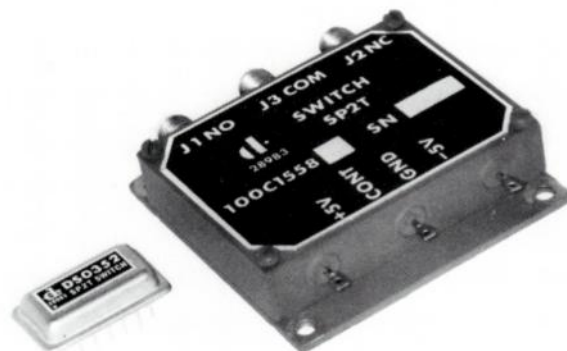

MIC & CONNECTORIZED

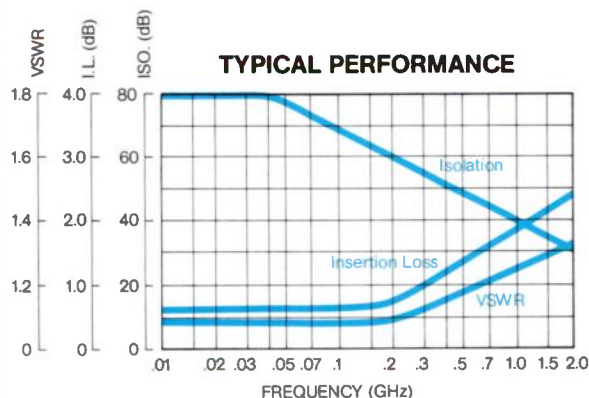

Key Specifications: P/N DS0352 | P/N 100C1558

Size	14 PIN DIP	1-1/2" x 2" x 7/16"
Control	1 line TTL	
Switching Speed	2 microsec. max.	
D.C. Power	+5 volts at 25 mA -5 volts at 25 mA	
R.F. Power	+10 dBm max.	
Impedance	50 ohms	
Unused port terminated in	50 ohms	

ALSO AVAILABLE IN MULTI-THROW CONFIGURATIONS.



**Industry Leader in
Microwave Integrated
Circuit & Connectorized
Switches, Step
Attenuators, Voltage
Control Attenuators**

DAICO INDUSTRIES, INC.

2351 East Del Amo Blvd., Compton, Calif. 90220
Telephone: (213) 631-1143 · TWX 910-346-6741

© 1982 Daico Industries, Inc.

mp82410

INFO/CARD 8

Design Of RF Amplifiers

Part I: Using Potentially Unstable Devices

Dealing with the “Catch 22” of conjugately
matching both the input and output
of a potentially unstable device.

*By D.R. Hertling and R.K. Feeney
School of Electrical Engineering
Georgia Institute of Technology
Atlanta, Georgia 30332*

RF designers must often design an amplifier with a potentially unstable device. It is impossible to conjugately match both the input and output of a potentially unstable device.¹ The designer must therefore, calculate Y_S and Y_L for the device, as shown in Figure 1, which insure stability and yield high gain. For an active device whose Y parameters are known, the stability of the device under worst case conditions (both input and output ports open circuited) can be investigated by calculating the Linvill stability factor C .

$$C = \frac{|y_r y_o|}{2g_i g_o - \text{Re}(y_i y_o)} \quad \text{Eq. (1)}$$

$$y = \begin{bmatrix} y_i & y_r \\ y_i & y_o \end{bmatrix} = \frac{\begin{bmatrix} g_i + jb_i & g_r + jb_r \\ g_i + jb_i & g_o + jb_o \end{bmatrix}}{\begin{bmatrix} g_i + jb_i & g_o + jb_o \end{bmatrix}}$$

where $\|$ and $\text{Re}()$ denote the magnitude and the real part of the complex quantity respectively. If $0 \leq C < 1$, the device is inherently stable and optimum terminations which yield maximum gain can be directly calculated from formulas.² Often, however, C is not between 0 and 1 and the device is potentially unstable.

Stern developed a procedure by which an amplifier can be designed which

TI 59 programs are provided which calculate device terminations and transducer power gain for an RF amplifier with specified stability. The programs use a modified Stern's procedure which can be used with either Y or S parameters.

delivers maximum power gain for a given degree of stability.³ Stern's procedure was derived using Y parameters, but can easily be adapted for S parameters by performing an S to Y parameter conversion. The Stern stability factor, K is given by

$$K = \frac{2(g_i + G_s)(g_o + G_L)}{|y_{12}| + \text{Re}(y_{12})} \quad \text{Eq. (2)}$$

For K greater than 1, the amplifier is stable. The circuit is potentially unstable for K less than 1.* Design with potentially unstable devices by Stern's procedure basically involves a tradeoff of gain for a higher degree of stability with K generally chosen between 4 and 10.

The values for the real parts of the source and load admittance, G_s and G_L for a specified K can be calculated using the following formulas.

$$G_s = \frac{K[|y_{12}| + \text{Re}(y_{12})]g_o^{1/2}}{2g_o} - g_i \quad \text{Eq. (3)}$$

$$G_L = \frac{K[|y_{12}| + \text{Re}(y_{12})]g_o^{1/2}}{2g_i} - g_o \quad \text{Eq. (4)}$$

*Note: By setting $G_s = G_L = 0$, one can use Stern's rather than the Linvill stability factor to investigate the stability of the device under worst case conditions.

Solution for the imaginary parts of the source and load admittance B_s and B_L by Stern's procedure requires the solution of a cubic equation and is tedious.

The given program employs an alternative approach which uses an iterative method of successive approximations.² B_L is first chosen as $-b_o$ (b_o is the imaginary part of y_o). Next, using the value of G_L calculated from (4) and the first guess for B_L , the input admittance of the amplifier is calculated.

B_s is then chosen to be the negative of the imaginary part of the input admittance. Using the value of G_s calculated from (3) and the first guess for B_s , the output admittance of the ampli-

fier is calculated. The second guess for B_L is then taken to be the negative of the output admittance. This procedure is continued until the new value of B_L is within .1 percent of its value from the previous iteration. The program is very simple to use and yields excellent agreement with the exact Stern's procedure.

If the Y parameters of a potentially unstable device are known, the designer need only enter these parameters and the desired K. The program will then calculate G_s , B_s , G_L , B_L , and the transducer gain in dB. If a printout is desired, label A' should be pressed before execution. The execution time is a function of K becoming longer as K approaches unity.

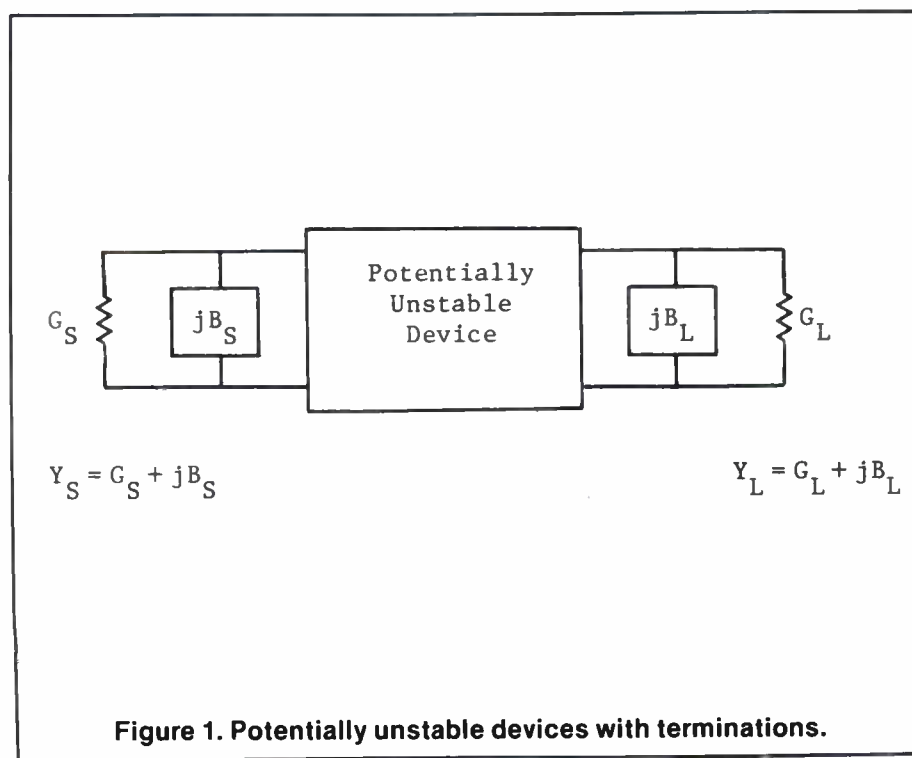


Figure 1. Potentially unstable devices with terminations.

Program Listing

RF Amp with Specified K

```

000 91 R/S 075 42 STD 150 10 10 225 32 X:T 300 13 13 375 43 RCL
001 76 LBL 076 25 25 151 42 STD 226 93 . 301 42 STD 376 26 26
002 11 R 077 61 GTD 152 03 03 227 00 0 302 02 02 377 91 R/S
003 72 ST* 078 23 LNX 153 43 RCL 228 00 0 303 43 RCL 378 43 RCL
004 09 09 079 76 LBL 154 11 11 229 01 1 304 14 14 379 32 32
005 99 PRT 080 33 X² 155 42 STD 230 22 INV 305 42 STD 380 91 R/S
006 69 DP 081 53 ( 156 04 04 231 77 GE 306 03 03 381 76 LBL
007 29 29 082 53 ( 157 36 PGM 232 34 FX 307 43 RCL 382 24 CE
008 91 R/S 083 43 RCL 158 04 04 233 43 RCL 308 15 15 383 02 2
009 76 LBL 084 20 20 159 10 E* 234 30 30 309 42 STD 384 06 6
010 16 R* 085 65 x 160 36 PGM 235 94 +/- 310 04 04 385 69 DP
011 86 STF 086 53 ( 161 04 04 236 42 STD 311 36 PGM 386 04 04
012 01 01 087 43 RCL 162 17 B* 237 26 26 312 04 04 387 43 RCL
013 91 R/S 088 19 19 163 32 X:T 238 61 GTD 313 13 C 388 20 20
014 76 LBL 089 85 + 164 94 +/- 239 35 1/X 314 94 +/- 389 69 DP
015 12 B 090 43 RCL 165 42 STD 240 76 LBL 315 44 SUM 390 06 06
016 98 ADV 091 18 18 166 24 24 241 34 FX 316 27 27 391 02 2
017 98 ADV 092 54 ) 167 43 RCL 242 43 RCL 317 32 X:T 392 02 2
018 42 STD 093 65 x 168 18 18 243 30 30 318 94 +/- 393 03 3
019 20 20 094 43 RCL 169 42 STD 244 94 +/- 319 44 SUM 394 06 6
020 43 RCL 095 21 21 170 01 01 245 42 STD 320 28 28 395 69 DP
021 12 12 096 54 ) 171 43 RCL 246 26 26 321 53 ( 396 04 04
022 42 STD 097 55 ÷ 172 29 29 247 61 GTD 322 53 ( 397 43 RCL
023 01 01 098 53 ( 173 42 STD 248 42 STD 323 43 RCL 398 23 23
024 43 RCL 099 02 2 174 02 02 249 76 LBL 324 27 27 399 69 DP
025 13 13 100 65 x 175 53 ( 250 35 1/X 325 33 X² 400 06 06
026 42 STD 101 43 RCL 176 43 RCL 251 53 ( 326 85 + 401 01 1
027 02 02 102 22 22 177 10 10 252 43 RCL 327 43 RCL 402 04 4
028 43 RCL 103 54 ) 178 85 + 253 10 10 328 28 28 403 03 3
029 14 14 104 54 ) 179 43 RCL 254 85 + 329 33 X² 404 06 6
030 42 STD 105 34 FX 180 23 23 255 43 RCL 330 54 ) 405 69 DP
031 03 03 106 75 - 181 54 ) 256 23 23 331 35 1/X 406 04 04
032 43 RCL 107 43 RCL 182 42 STD 257 54 ) 332 65 x 407 43 RCL
033 15 15 108 21 21 183 03 03 258 42 STD 333 04 4 408 24 24
034 42 STD 109 54 ) 184 53 ( 259 01 01 334 65 x 409 69 DP
035 04 04 110 92 RTN 185 43 RCL 260 53 ( 335 43 RCL 410 06 06
036 36 PGM 111 76 LBL 186 11 11 261 43 RCL 336 23 23 411 02 2
037 04 04 112 23 LNX 187 85 + 262 11 11 337 65 x 412 02 2
038 13 C 113 43 RCL 188 43 RCL 263 85 + 338 43 RCL 413 02 2
039 42 STD 114 17 17 189 24 24 264 43 RCL 339 25 25 414 07 7
040 18 18 115 94 +/- 190 54 ) 265 24 24 340 65 x 415 69 DP
041 53 ( 116 42 STD 191 42 STD 266 54 ) 341 53 ( 416 04 04
042 24 CE 117 26 26 192 04 04 267 42 STD 342 43 RCL 417 43 RCL
043 33 X² 118 76 LBL 193 36 PGM 268 02 02 343 14 14 418 25 25
044 85 + 119 42 STD 194 04 04 269 53 ( 344 33 X² 419 69 DP
045 32 X:T 120 43 RCL 195 18 C* 270 43 RCL 345 85 + 420 06 06
046 42 STD 121 18 18 196 43 RCL 271 16 16 346 43 RCL 421 01 1
047 29 29 122 42 STD 197 16 16 272 85 + 347 15 15 422 04 4
048 33 X² 123 01 01 198 42 STD 273 43 RCL 348 33 X² 423 02 2
049 54 ) 124 43 RCL 199 03 03 274 25 25 349 54 ) 424 07 7
050 34 FX 125 29 29 200 43 RCL 275 54 ) 350 54 ) 425 69 DP
051 42 STD 126 42 STD 201 17 17 276 42 STD 351 53 ( 426 04 04
052 19 19 127 02 02 202 42 STD 277 03 03 352 24 CE 427 43 RCL
053 43 RCL 128 53 ( 203 04 04 278 53 ( 353 28 LDG 428 26 26
054 10 10 129 43 RCL 204 36 PGM 279 43 RCL 354 65 x 429 69 DP
055 42 STD 130 16 16 205 04 04 280 17 17 355 01 1 430 06 06
056 21 21 131 85 + 206 10 E* 281 85 + 356 00 0 431 02 2
057 43 RCL 132 43 RCL 207 36 PGM 282 43 RCL 357 54 ) 432 02 2
058 16 16 133 25 25 208 04 04 283 26 26 358 42 STD 433 03 3
059 42 STD 134 54 ) 209 17 B* 284 54 ) 359 32 32 434 07 7
060 22 22 135 42 STD 210 32 X:T 285 42 STD 360 87 IFF 435 69 DP
061 71 SBR 136 03 03 211 42 STD 286 04 04 361 01 01 436 04 04
062 33 X² 137 53 ( 212 30 30 287 36 PGM 362 24 CE 437 43 RCL
063 42 STD 138 43 RCL 213 53 ( 288 04 04 363 43 RCL 438 32 32
064 23 23 139 17 17 214 53 ( 289 13 C 364 20 20 439 69 DP
065 43 RCL 140 85 + 215 24 CE 290 42 STD 365 91 R/S 440 06 06
066 10 10 141 43 RCL 216 85 + 291 27 27 366 43 RCL 441 91 R/S
067 42 STD 142 26 26 217 43 RCL 292 32 X:T 367 23 23 442 76 LBL
068 22 22 143 54 ) 218 26 26 293 42 STD 368 91 R/S 443 15 E
069 43 RCL 144 42 STD 219 54 ) 294 28 28 369 43 RCL 444 01 1
070 16 16 145 04 04 220 55 ÷ 295 43 RCL 370 24 24 445 00 0
071 42 STD 146 36 PGM 221 43 RCL 296 12 12 371 91 R/S 446 42 STD
072 21 21 147 04 04 222 26 26 297 42 STD 372 43 RCL 447 09 09
073 71 SBR 148 18 C* 223 54 ) 298 01 01 373 25 25 448 81 RST
074 33 X² 149 43 RCL 224 50 I×I 299 43 RCL 374 91 R/S

```


Example #1

Calculate the terminations which yield maximum gain for a device with the following Y parameters and for K = 10. (C = 4.76)

$$\begin{bmatrix} y_1 & y_r \\ y_l & y_o \end{bmatrix} = \begin{bmatrix} 1.5 + j3.5 & 0 - j.3 \\ 56 - j11 & .1 + j.75 \end{bmatrix}$$

all in mmhos

Procedure:

1. Read side 1 and side 2 of the "RF Amp with Specified K" program.
2. Press E to initialize the program.
3. Enter y_1 , y_r , y_l , and y_o in order using the following procedure.
Enter y_1
Press A (Note: g_1 , b_1 , ..., g_o , b_o are automatically printed as they are entered.)
Enter y_r
Press A
.
.
.
Enter y_l
Press A
.
.
.
Enter y_o
Press A
4. Press A' if a printout of the output is desired.
5. Enter K
Press B

This is the resulting printout:

```

1.5-03
3.5-03
0. 00
-3. -04
5.6-02
-1.1-02
1. -04
7.5-04

```

```

1. 01      K
3.0695931-02 GS
-1.1248646-02 BS
2.0463954-03 GL
-1.2665531-03 BL
2.2183488 01 GT

```

If the printer is not used, the calculator will stop with K displayed. Successive pressings of R/S will display G_s , B_s , G_L , B_L , and G_T in that order. To repeat the calculation for say K = 4, simply enter 4 and press B. The Y

r.f. design

parameters need not be reentered. For K = 4, the following printout is obtained.

```

4. 00      K
1.8862495-02 GS
-1.4201746-02 BS
1.2574996-03 GL
-1.4632185-03 BL
2.6489989 01 GT

```

Execution time for this example is approximately 45 seconds for K = 10 and approximately 70 seconds for K = 4.


Execution time will vary for different Y parameters.

If S parameters are to be used the second program which converts S to Y parameters must be executed first. This program uses the same procedure for entering the device parameters and automatically places the calculated Y parameters in the proper registers for execution of the first program. The S parameters must be entered in polar form.

RF Telemetry Links with state-of-the-art performance and reliability

Communitronics new family of low cost receivers and transmitters is available in high or low band VHF and UHF models. They're designed to telemeter voice, low speed digital information and tone signals for such applications as Data Links, Status Control, Supervisory Control, Alarm Systems, Monitoring Systems, Pipeline Control and Low Power Repeaters, to name a few. Besides our standard models, which are available with optional RF connectors, we can also design and produce custom units to meet your exact requirements.

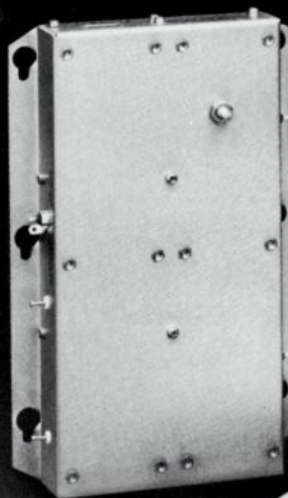So, if you want the latest in RF telemetry links, write or call Communitronics for detailed specifications and pricing.




TRANSMITTER

- 1½ and 4 watt powers
- Rated continuous duty
- Compact size

RECEIVER

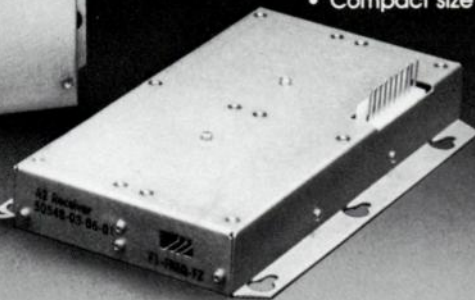- Dual Conversion
- Low standby current for battery operation
- Compact size



COMMUNITRONICS LTD.

160 Wilbur Place, Bohemia, N.Y. 11716 • (516) 567-8320
INFO/CARD 9

Program Listing S→Y

000	91	R/S	052	32	X↑T	104	36	36	156	38	38	207	43	RCL	258	43	RCL
001	76	LBL	053	94	+/-	105	43	RCL	157	22	INV	208	14	14	259	37	37
002	11	A	054	44	SUM	106	35	35	158	37	P/R	209	55	÷	260	32	X↑T
003	72	ST*	055	27	27	107	32	X↑T	159	32	X↑T	210	43	RCL	261	43	RCL
004	09	09	056	43	RCL	108	43	RCL	160	53	(211	35	35	262	38	38
005	99	PRT	057	27	27	109	36	36	161	24	CE	212	54)	263	22	INV
006	69	DP	058	42	STD	110	22	INV	162	55	÷	213	32	X↑T	264	37	P/R
007	29	29	059	35	35	111	37	P/R	163	43	RCL	214	53	(265	32	X↑T
008	91	R/S	060	43	RCL	112	42	STD	164	35	35	215	43	RCL	266	53	(
009	76	LBL	061	28	28	113	36	36	165	54)	216	15	15	267	24	CE
010	12	B	062	42	STD	114	32	X↑T	166	32	X↑T	217	75	-	268	55	÷
011	60	DEG	063	36	36	115	42	STD	167	53	(218	43	RCL	269	43	RCL
012	53	(064	43	RCL	116	35	35	168	24	CE	219	36	36	270	35	35
013	43	RCL	065	10	10	117	01	1	169	75	-	220	54)	271	54)
014	10	10	066	32	X↑T	118	42	STD	170	43	RCL	221	37	P/R	272	32	X↑T
015	65	x	067	43	RCL	119	37	37	171	36	36	222	42	STD	273	53	(
016	43	RCL	068	11	11	120	43	RCL	172	54)	223	15	15	274	24	CE
017	16	16	069	37	P/R	121	10	10	173	37	P/R	224	32	X↑T	275	75	-
018	54)	070	42	STD	122	42	STD	174	42	STD	225	42	STD	276	43	RCL
019	32	X↑T	071	11	11	123	39	39	175	11	11	226	14	14	277	36	36
020	53	(072	32	X↑T	124	94	+/-	176	32	X↑T	227	01	1	278	54)
021	43	RCL	073	42	STD	125	44	SUM	177	42	STD	228	42	STD	279	37	P/R
022	11	11	074	10	10	126	37	37	178	10	10	229	37	37	280	42	STD
023	85	+	075	43	RCL	127	43	RCL	179	53	(230	43	RCL	281	17	17
024	43	RCL	076	16	16	128	11	11	180	02	2	231	39	39	282	32	X↑T
025	17	17	077	32	X↑T	129	42	STD	181	94	+/-	232	44	SUM	283	42	STD
026	54)	078	43	RCL	130	40	40	182	65	x	233	37	37	284	16	16
027	37	P/R	079	17	17	131	94	+/-	183	43	RCL	234	43	RCL	285	01	1
028	42	STD	080	37	P/R	132	42	STD	184	12	12	235	40	40	286	00	0
029	28	28	081	42	STD	133	38	38	185	55	÷	236	42	STD	287	32	X↑T
030	32	X↑T	082	17	17	134	43	RCL	186	43	RCL	237	38	38	288	76	LBL
031	42	STD	083	32	X↑T	135	16	16	187	35	35	238	43	RCL	289	22	INV
032	27	27	084	42	STD	136	44	SUM	188	54)	239	16	16	290	05	5
033	53	(085	16	16	137	37	37	189	32	X↑T	240	94	+/-	291	00	0
034	43	RCL	086	01	1	138	43	RCL	190	53	(241	44	SUM	292	22	INV
035	14	14	087	44	SUM	139	17	17	191	43	RCL	242	37	37	293	64	PD*
036	65	x	088	35	35	140	44	SUM	192	13	13	243	43	RCL	294	09	09
037	43	RCL	089	43	RCL	141	38	38	193	75	-	244	17	17	295	69	DP
038	12	12	090	10	10	142	43	RCL	194	43	RCL	245	94	+/-	296	39	39
039	54)	091	44	SUM	143	27	27	195	36	36	246	44	SUM	297	43	RCL
040	32	X↑T	092	35	35	144	94	+/-	196	54)	247	38	38	298	09	09
041	53	(093	43	RCL	145	44	SUM	197	37	P/R	248	43	RCL	299	77	GF
042	43	RCL	094	16	16	146	37	37	198	42	STD	249	27	27	300	22	INV
043	15	15	095	44	SUM	147	43	RCL	199	13	13	250	94	+/-	301	91	R/S
044	85	+	096	35	35	148	28	28	200	32	X↑T	251	44	SUM	302	76	LBL
045	43	RCL	097	43	RCL	149	94	+/-	201	42	STD	252	37	37	303	15	E
046	13	13	098	11	11	150	44	SUM	202	12	12	253	43	RCL	304	01	1
047	54)	099	44	SUM	151	38	38	203	53	(254	28	28	305	00	0
048	37	P/R	100	36	36	152	43	RCL	204	02	2	255	94	+/-	306	42	STD
049	94	+/-	101	43	RCL	153	37	37	205	94	+/-	256	44	SUM	307	09	09
050	44	SUM	102	17	17	154	32	X↑T	206	65	x	257	38	38	308	81	RST
051	28	28	103	44	SUM	155	43	RCL									

Example #2

Calculate the terminations which yield maximum gain for a device with the following S parameters and for $K = 10$. ($C = 1.56$)

$$\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} = \begin{bmatrix} .691 \angle -141.3^\circ & .043 \angle 29.1^\circ \\ 3.406 \angle 92.5^\circ & .781 \angle -20.7^\circ \end{bmatrix}$$

Procedure:

1. Read side 1 and 2 of the S→Y program.
2. Enter S_{11} , S_{12} , S_{21} , S_{22} in order.

S_{11}

Press A

$\angle S_{11}$

Press A

.

.

$\angle S_{22}$

Press A

3. Press B

4. Read side 1 and 2 of the "Amp with Specified K" program.

5. Press A' if a printout of the output is desired.

6. Enter the desired K.

Press B

Note: Neither program uses direct addressing which allows easy additions to the programs should the user desire to add to or modify the program.

0.691
-141.3
0.043
29.1
3.406
92.5
0.781
-20.7

10.	K
0.179353366	GS
-.1441593196	BS
.0013361587	GL
-.0040675364	BL
20.67207998	GT

References

1. Carson, R.S., *High-Frequency Amplifiers*, Wiley Interscience, 1975.
2. Kraus, H.L., *Solid State Radio Engineering*, Wiley, 1980.
3. Stern, A.P., "Stability and Power Gain of Tuned Transistor Amplifiers," *Proc. IRE*, Vol. 45, March 1957. ☐

r.f. design

JOHANSON ENGINEERING ECLIPSES THE INDUSTRY



For over 35 years Johanson engineering has set the standard of quality for the variable capacitor industry. The Giga-Trim® (gigahertz trimmers) are tiny variable capacitors that are a cost effective means of fine tuning RF hybrid and microwave circuits. Now, a new improved series provides an increased Q factor of >3000 to >5000 and a zero temperature coefficient. *Electronic Accuracy through Mechanical Precision.*


Johanson

Manufacturing Corporation
400 Rockaway Valley Road
Boonton, New Jersey 07005
201-334-2676 TWX 710-987-8367

U.S. Patent No. 3,469,160

INFO/CARD 10

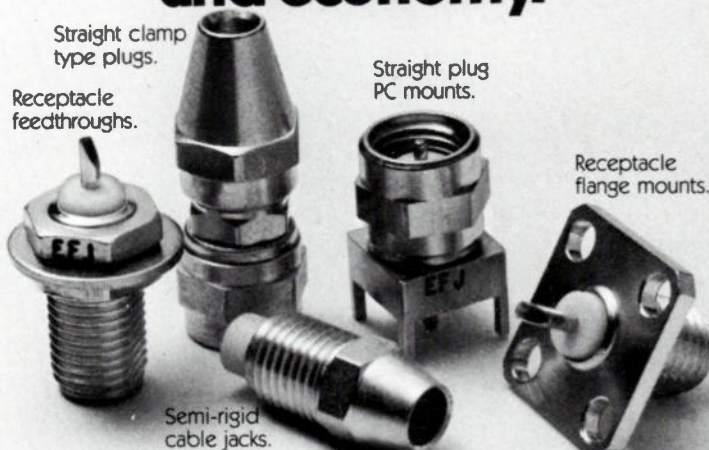We've found a connection between reliability and economy.



Johnson makes coaxial connectors for all types of applications. For a free catalog, phone (507) 835-6222 or write E.F. Johnson Co., 299 10th Avenue Southwest, Waseca, Minnesota 56093.



JOHNSON

TWX 910-565-2161

E. F. JOHNSON COMPANY, WASECA, MINN. 56093

TLX 290470

INFO/CARD 11

A Programmable Calculator Method for Chebyshev Filter Selection

By Marvin Kefer
Hazeltine Corp.
Greenlawn, N.Y.

This article presents a fundamental method of choosing a bandpass filter based on the solution of the Chebyshev Loss Equation. The advantages of this approach are:

- Extension of accuracy
- Selection of *any* integer number of poles
- Selection of *any* bandpass ripple
- Extension of frequency and skirt rejection ranges
- Simplification of computation and rapid results (with no manual normalization required).

Selecting a Chebyshev Filter

An ideal filter provides transparent processing of signals, in the passband, and infinite attenuation of signals outside of the passband. A Chebyshev response is often chosen to

approximate the ideal filter. Matched filters, Cauer filters and Bessel function filters are superior filters for many receiver applications, but because of realization and fabrication difficulty the designer often selects a Chebyshev filter instead and accepts a small degradation of performance.

Two approaches, for selection of Chebyshev filter parameters, will be illustrated by two examples. In the first example an IF filter is selected by fixing the passband and solving for the required rejection. In the second example an RF filter is selected by fixing the rejection and solving for the required passband.

Example 1 — The passband of an IF filter determines the noise bandwidth of the receiver, defined as the operational bandwidth of Figure 1. To provide adjacent channel rejection the filter must provide an insertion loss (rejection) of A dB at frequency f_1 . Figure 1 illustrates that a six pole filter provides the required rejection with Δ dB rejection margin. The five pole filter provides ϵ dB less than the required rejection.

Because fewest poles is the most practical solution from a cost/alignment viewpoint, the 10 pole solution is rejected in favor of the six pole solution.

Example 2 — The rejection of an RF filter which provides rejection to image, spurious and out of band signals, is set at A dB in Figure 2. The minimum operational bandwidth is the product of the number of channels plus 1 and the channel spacing however, a wider bandwidth may be used to:

1. Allow for filter passband variations for manufacturing tolerances, for non-infinite unloaded " Q_u " and for temperature changes.

2. Move the channels away from the 3 dB bandedge, to where the phase-frequency characteristic is more linear.


In Figure 2 all the filter responses provide the required rejection, but only filters having six or more poles have sufficient operational bandwidth.

The six pole filter solution in example 2 provides bandwidth margin while the example 1 solution provided rejection margin. In each example the solution is not unique. The designer has the option to trade some rejection margin for bandwidth margin.

Numerical Examples

Classically bandpass filter selection involves:

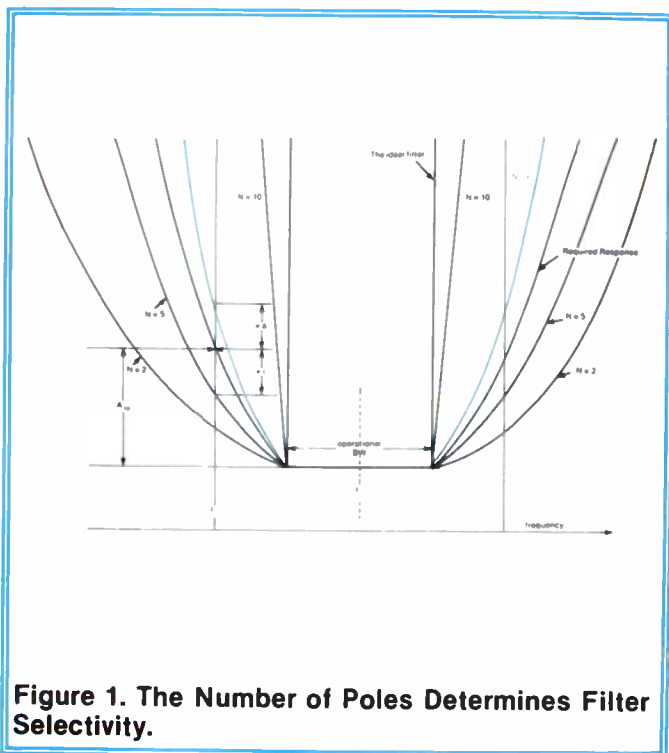1. Scaling the filter requirements to an equivalent normalized low pass filter.
2. Comparing the scaled low pass response to normalized Chebyshev curve.



The author is not suggesting discarding your Chebyshev filter tables or curves (he's keeping his!), but rather an alternative procedure for selecting a filter based on an exact solution of the Chebyshev loss equation using a programmable calculator.

Our approach solves the Chebyshev loss equation directly, without manual frequency normalization. We use the number crunching ability of the calculator, instead of normalized curves, for precise solution of the loss equation.

The Chebyshev loss equation is:

$$A \text{ dB} = 10 \log \{ 1 + (10^{AM/10} - 1) \cosh^2 (N \cosh^{-1} W) \} \text{ Eq. (1)}$$

The parameters are defined for $W \geq 1$ in figure 2A.

In the following numerical examples the loss equation solutions will be illustrated by the calculator printout. These solutions will also serve as a program check for the calculator program, which will be explained in the following section.



The examples are intended to demonstrate procedure as well as the insight and benefit achieved by tracking the ripple bandwidth. The numerical examples add numerical values to the previous examples.

Example 1 — How many poles are needed for the following IF bandpass filter requirements?

Characteristic	Requirement
Passband ripple (AM)	0.5 dB
Center frequency (f0)	1780 MHz
Operational bandwidth, equals the ripple bandwidth, (BW/A)	140 MHz
Operational bandwidth bandedge rejection (A/DF)	0.5 dB
32 dB rejection bandwidth (BW)	210 MHz

The operational bandwidth was selected as the ripple bandwidth however, the operational bandwidth can be selected as the 3 dB bandwidth or any rejection bandwidth greater than or equal to the ripple bandwidth.

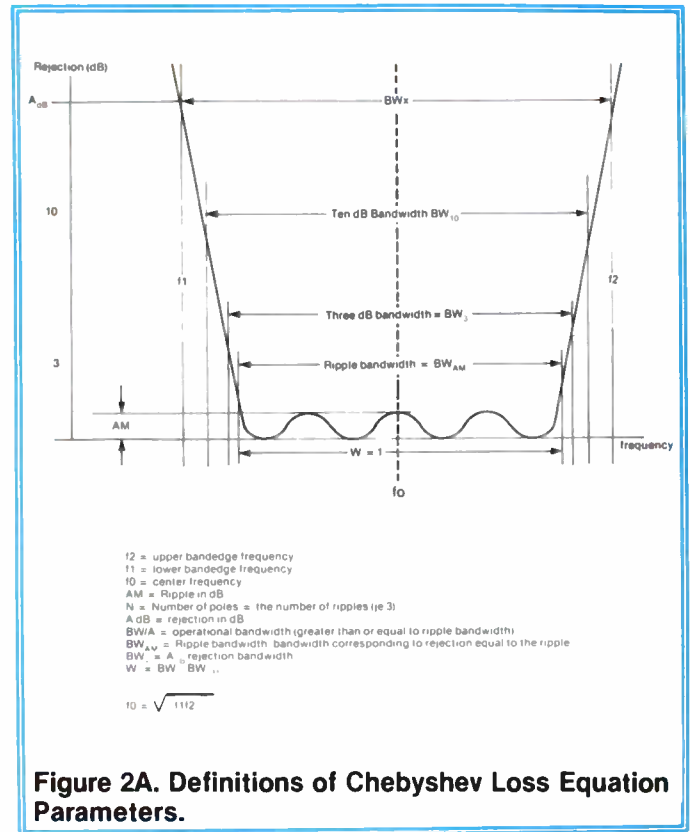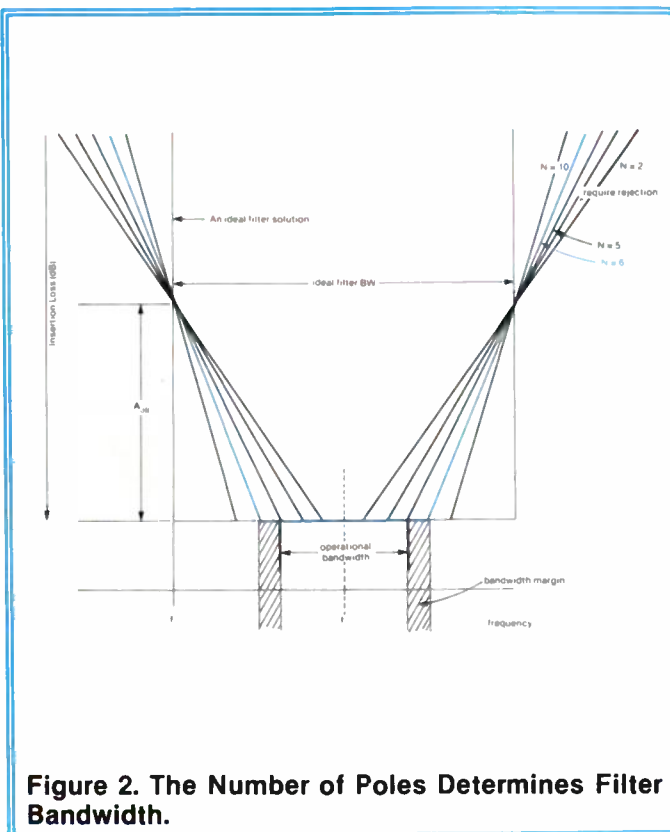Equation (1) is solved for $N=2,3,4,5,6,8$ the results, annotated and printed by the program, are listed in Figure 3.



FILTER SKIRTS				FILTER SKIRTS				FILTER SKIRTS			
1780.	FD	1780.	FD	1780.	FD	1780.	FD	1780.	FD	1780.	FD
0.5	A/DF	0.5	A/DF	0.5	A/DF	0.5	A/DF	0.5	A/DF	0.5	A/DF
140.	BW/A	140.	BW/A	140.	BW/A	140.	BW/A	140.	BW/A	140.	BW/A
0.5	AM	0.5	AM	0.5	AM	0.5	AM	0.5	AM	0.5	AM
2.	N	3.	N	4.	N						
210.	BW	210.	BW	210.	BW						
3.970218646	IL	10.36768374	IL	18.34458891	IL						
1678.094221	F1	1678.094221	F1	1678.094221	F1						
1888.094221	F2	1888.094221	F2	1888.094221	F2						

FILTER SKIRTS				FILTER SKIRTS				FILTER SKIRTS			
1780.	FD	1780.	FD	1780.	FD	1780.	FD	1780.	FD	1780.	FD
0.5	A/DF	0.5	A/DF	0.5	A/DF	0.5	A/DF	0.5	A/DF	0.5	A/DF
140.	BW/A	140.	BW/A	140.	BW/A	140.	BW/A	140.	BW/A	140.	BW/A
0.5	AM	0.5	AM	0.5	AM	0.5	AM	0.5	AM	0.5	AM
5.	N	6.	N	8.	N						
210.	BW	209.9935538	BW	210.	BW						
26.65115774	IL	35.	IL	51.71973117	IL						
1678.094221	F1	1678.097254	F1	1678.094221	F1						
1888.094221	F2	1888.090808	F2	1888.094221	F2						

Figure 3. Increasing the Number of Poles Linearly Increases the 210 MHz Bandwidth Rejection.

FILTER SKIRTS				FILTER SKIRTS				FILTER SKIRTS			
1780.	FD	1780.	FD	1780.	FD	1780.	FD	1780.	FD	1780.	FD
0.5	A/DF	0.5	A/DF	0.5	A/DF	0.5	A/DF	0.5	A/DF	0.5	A/DF
140.	BW/A	140.	BW/A	140.	BW/A	140.	BW/A	140.	BW/A	140.	BW/A
0.125	AM	0.25	AM	0.5	AM	1.	AM	0.5	AM	0.5	AM
6.	N	6.	N	6.	N	6.	N				
210.	BW	210.	BW	210.	BW	210.	BW				
30.51243032	IL	32.64945431	IL	35.00214561	IL						
1678.094221	F1	1678.094221	F1	1678.094221	F1						
1888.094221	F2	1888.094221	F2	1888.094221	F2						

FILTER SKIRTS				FILTER SKIRTS			
1780.	FD	1780.	FD	1780.	FD	1780.	FD
0.5	A/DF	0.5	A/DF	0.5	A/DF	0.5	A/DF
140.	BW/A	140.	BW/A	140.	BW/A	140.	BW/A
1.	AM	2.	AM	2.	AM	2.	AM
6.	N	6.	N	6.	N	6.	N
210.	BW	210.	BW	210.	BW		
38.3651153	IL	41.89337226	IL				
1678.094221	F1	1678.094221	F1				
1888.094221	F2	1888.094221	F2				

Figure 4. Filter Rejection Increases When Ripple is Increased.

FILTER SKIRTS				FILTER SKIRTS				FILTER SKIRTS			
1780.	FD	1780.	FD	1780.	FD	1780.	FD	1780.	FD	1780.	FD
32.	A/DF	32.	A/DF	32.	A/DF	32.	A/DF	32.	A/DF	32.	A/DF
210.	BW/A	210.	BW/A	210.	BW/A	210.	BW/A	210.	BW/A	210.	BW/A
0.5	AM	0.5	AM	0.5	AM	0.5	AM	0.5	AM	0.5	AM
2.	N	3.	N	4.	N						
27.70203013	BW	66.96350933	BW	101.384986	BW						
0.5	IL	0.5	IL	0.5	IL						
1766.202875	F1	1746.83066	F1	1730.029195	F1						
1793.904905	F2	1813.799169	F2	1831.414181	F2						

FILTER SKIRTS				FILTER SKIRTS				FILTER SKIRTS			
1780.	FD	1780.	FD	1780.	FD	1780.	FD	1780.	FD	1780.	FD
32.	A/DF	32.	A/DF	32.	A/DF	32.	A/DF	32.	A/DF	32.	A/DF
210.	BW/A	210.	BW/A	210.	BW/A	210.	BW/A	210.	BW/A	210.	BW/A
0.5	AM	0.5	AM	0.5	AM	0.5	AM	0.5	AM	0.5	AM
5.	N	6.	N	8.	N						
127.299596	BW	146.0341448	BW	169.4619819	BW						
0.5	IL	0.5	IL	0.5	IL						
1717.487842	F1	1708.479908	F1	1697.284537	F1						
1844.78744	F2	1854.514093	F2	1866.746519	F2						

Figure 5. Operational Bandwidth Dependency on the Number of Filter Poles.

Comparing the IL (insertion loss or rejection) in Figure 3 observe that from N = 3 to 8 the increase in IL is approximately 8 dB/Pole. This relationship is a specific example of a general rule which is mathematically proven in Appendix A.

Given constant ripple (AM) and constant bandwidth to ripple bandwidth ratio ($W' = \text{constant}$), rejection will increase linearly for each additional pole added to the Chebyshev loss equation expressed mathematically.

Equation (2) (From Appendix A)

$$\Delta A \text{ dB} \cong 8.68 \phi$$

Where

$\Delta A \text{ dB} = \text{increase in rejection per additional pole}$

$$\phi = \text{Cosh}^{-1} W'$$

given

$A \text{ dB} \geq 10 \text{ dB}$

AM = fixed

$W' = \text{fixed}$

$N > 2$

Using this relationship reduces the number of trials needed to solve for the required number of poles (see Appendix C).

To gain further insight, about the Chebyshev loss equation parameters, we have varied only the ripple (AM), by doubling it each step, from AM = .125 dB to AM = 2 dB.

As the ripple doubles (In Figure 4) the rejection, at 210 MHz bandwidth increases approximately 3 dB. Another specific case of a general rule proven in Appendix B.

The increase in rejection, caused only by an increase in the passband ripple is approximately 3 dB for each doubling of the ripple. Expressed Mathematically by Equation (3) (From Appendix C).

$$\Delta A \text{ dB} = 10 \log \frac{AM2}{AM1}$$

for AM2 = Ripple Value 2 in dB

AM1 = Ripple Value 1 in dB

BW_{AM} (BW/A) fixed and W' fixed

N fixed

then $A \text{ dB} \geq 10 \text{ dB}$

Example 2 — A second solution to Example 1 is approached by fixing the rejection bandwidth and solving for the operational bandwidth. This approach corresponds to Figure 2.

Characteristic	Requirement
Passband Ripple (AM)	0.5 dB
Center frequency	1780 MHz
Rejection bandwidth (BW/A)	210 MHz
Rejection bandwidth bandedge rejection (A/DF)	32 dB
1/2 (IL) bandwidth (BW)	140 MHz

Figure 5 shows the dependency of operational bandwidths on the number of filter poles. We meet the 140 MHz requirement with a 6 MHz bandwidth margin, for N = 6.

This approach, while it does not reduce to a linear relationship of bandwidth and poles, can be useful for trading bandpass margin once an approximate solution is known.

Using the Program

The program requires a TI 59 calculator and may be used with or without a PC 100 printer.

The program is divided into four parts sharing common subroutines as follows: (see Figures 6 and 7).

Part 1 — scales the loss equation to the desired frequency and bandwidth

Part 2 — solves for rejection corresponding to the inputted bandwidth

Electronics By Land...

Hynes Veterans Auditorium
and the Sheraton-Boston Hotel



Electronics By Sea...

Commonwealth Pier
Exhibition Hall

...all needed to accommodate the largest *Electro* in history!


- **1260 Exhibit Booths** featuring a full-range of products in four distinct product categories: Components & microelectronics; instrumentation, test equipment & control systems; mini/microcomputers & EDP peripherals; and production & packaging equipment.
- **150 Professional Program Presentations** • Special tutorials and workshops
 - Business Communications Conference • Keynote Luncheon
 - Film Theater • Plus Special Exhibits on Robotics and Office Automation

 **Electro/82**
Boston
May 25, 26, 27, 1982

For complete information, request an Electro/82 Preview Program. Telephone: 617 / 232-4193
or (tollfree) 800 / 421-6816;
in California 800 / 262-4208

Electro is sponsored by Central New England Council, Region 1 and METSAC Sections, IEEE; and New England and New York Chapters of ERA
Produced by Electronic Conventions, Inc., a nonprofit corporation

INFO/CARD 12

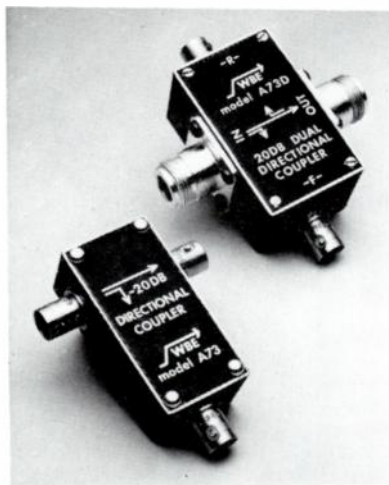


**BROADBAND EQUIPMENT
FOR INSTRUMENTATION
AND COMMUNICATIONS**

Directional Couplers

Model	Freq Range MHz	Coupler Type	In Line Power	Minimum Directivity (dB)		In Line Loss (dB)	Response Flatness of -20 dB part (dB)	VSWR
				1-500 MHz	5-300 MHz			
A73-20	1-500	single	5W cw (10W cw 5-300 MHz)	20	30	.4 max .2 typical	-1	1.1:1
A73-20GA				30	40		5-500	1.5:1
A73-20GB				40	45		1-500	1.5:1
A73-20P	1-100	single	50W cw (75 ohm limited to 10W cw)	35 dB min		.15		1.1:1 max
A73D-20P		dual		40 dB min typical				
A73-20PX		single		45 dB min				
A73D-20PX	10-200	dual				.3		1.04:1 typical
A73-20PA		single		35 dB min				
A73D-20PA		dual		40 dB min typical				
A73-20PAX		single				.15		
A73D-20PAX		dual		45 dB min				

WIDE BAND ENGINEERING COMPANY, INC.

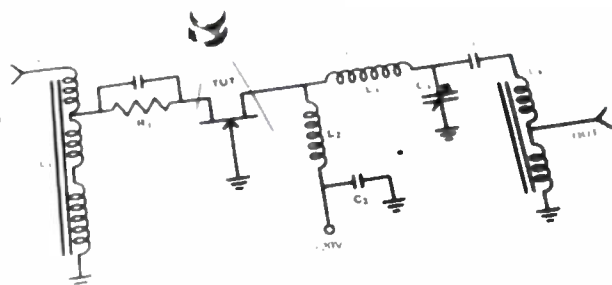P O BOX 21652, PHOENIX, ARIZONA 85036, U S A • TELEPHONE (602) 254 1570
INFO/CARD 13



High Voltage Broadband RF FET

High dynamic range RF FET now available up to 50V BVDGO for use with 24 & 32V supplies, and where higher drain voltage improves dynamic range. The CP664 (30V), CP665 (40V), and CP666 (50V) have third order intermodulation intercept <+40 dBm, and 50 Ohm VSWR > 1.5 to 1 over 0.5 to 50 MHz range.

**TELEDYNE
CRYSTALONICS**

147 Sherman Street, Cambridge, MA 02140
Tel: (617) 491-1670 • TWX 710-320-1196

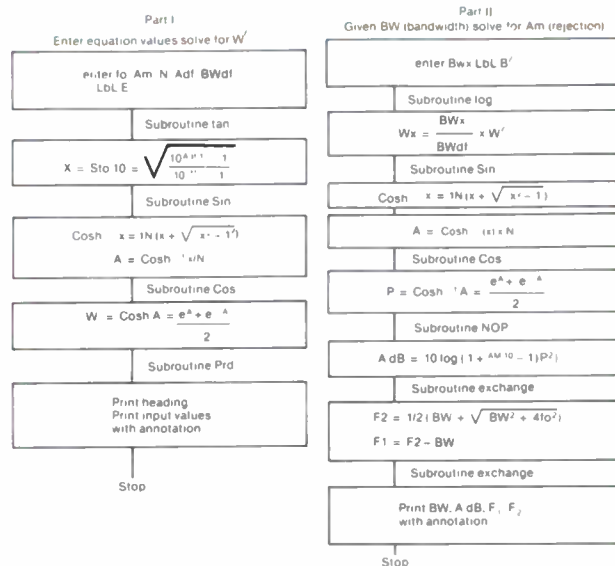


Figure 6. Flow Charts of Parts I and II of Calculator Program.

Part 3 — solves for bandwidth corresponding to the inputted rejection

Part 4 — solves for the bandwidth corresponding to the inputted bandedge frequency

The program is described in Figure 8, with memory locations indicated and is listed in Figure 9.

Comments:

- Care must be exercised when entering a rejection bandwidth (BWx), if the bandwidth entered is smaller than the ripple bandwidth the answer will be incorrect. The $W' \geq 1$ requirement will have been violated and the program has no failsafe solution.

- To use the program for low pass filter selection set $f_0 = 0$ and enter frequency as if it was bandwidth. Band reject and highpass filter responses require program modifications or working with inverse entries.

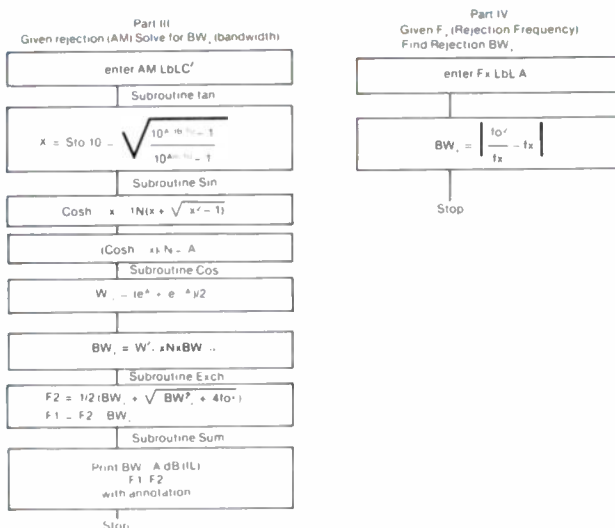


Figure 7. Flow Charts of Parts 3 and 4 of Calculator Program.

TI PROGRAM RECORD

PROGRAM DESCRIPTION

Normalizes the loss equation for center frequency, ripple, number of poles and a particular rejection bandwidth. Solves the normalized equation for bandwidth given rejection or rejection given bandwidth, for low pass and band pass filters. For low pass set $F0 = 0$ and $Bw = \text{frequency}$.

USER INSTRUCTIONS

STEP	PROCEDURE	ENTER	PRESS			DISPLAY
1	Enter center frequency	FO	A			FO
2	Enter ripple in dB	AM	B			AM
3	Enter number of poles	N	C			N
4	Enter desired rejection	A/DF	D			A/DF
5	Enter corresponding bandwidth Printer lists annotated inputs and calculates w' (normalizes to input)	BW/A	E			N
6	Enter f_x , for calculation of associated rejection bandwidth BW_x	f_x	A			BW_x
7	Enter BW_x , for calculation of associated rejection Printer lists annotate outputs BW, IL (rejection) F1 (lower band edge) F2 (upper band edge)	BW_x	B			F2
8	Enter IL for calculation of associated BW. Printer lists annotated outputs of BW, IL, F1, F2	IL	C			IL

USER DEFINED KEYS			DATA REGISTERS (INV)			LABELS (Op 08)								
A	FO (center freq)		0	Constant		10	Cosh ϕ		INV	Ing	CE	CLR	π	π^2
B	AM (dB ripple)		1	Work register		11	ϕ		$\sqrt{}$	1/x	STO	RCL	SUM	γ^2
C	N (# poles)		2	A/DF (input)		12			EE	()	+	GTO	X
D	A/DF (BW reject.)		3	AM (input)		13	F2 (upper freq.)		SBR	-	RST	\div	R/S	*
E	BW/A (reject. BW)		4	F0 (input)		14	F1 (lower freq.)		+/-	=	CLR	INV	$\frac{1}{\sqrt{}}$	$\frac{1}{\gamma}$
A	f_x (reject. freq.)		5	BW/A (input)		15	F input				P \rightarrow			\rightarrow
B	BWx (reject. BW)		6	N (poles input)		16	A/DF		$\frac{1}{x}$		x	$\frac{1}{x}$	$\frac{1}{x}$	
C	ILx (BW reject.)		7	W' ripple BW ratio		17			$\frac{1}{x^2}$	$\frac{1}{x^2}$	$\frac{1}{x^2}$	$\frac{1}{x^2}$	$\frac{1}{x^2}$	$\frac{1}{x^2}$
D			8	BWx (input or cal.)		18			$\frac{1}{x^3}$	DMS	π		π	
E			9	ILx (A/DF or Cal.)		19			$\frac{1}{x^4}$					
FLAGS			0	1	2	3	4	5	6	7	8	9		

149	76	LBL	202	01	01	254	06	06	306	04	04	358	06	06	410	42	STD
150	30	TAN	203	02	2	255	01	1	307	43	RCL	359	02	2	411	11	11
151	43	RCL	204	07	7	256	03	3	308	06	06	360	01	1	412	71	SBR
152	02	02	205	03	3	257	06	6	309	69	DP	1	00	0	413	39	CDS
153	55	+	206	07	7	258	03	3	310	06	06	362	03	3	414	71	SBR
154	01	1	207	01	1	259	01	1	311	98	ADV	363	00	0	415	68	NOP
155	00	0	208	07	7	260	06	6	312	92	RTN	364	00	0	416	71	SBR
156	95	=	209	03	3	261	02	2	313	76	LBL	365	00	0	417	48	EXC
157	22	INV	210	05	5	262	01	1	314	44	SUM	366	00	0	418	71	SBR
158	28	LOG	211	00	0	263	69	DP	315	25	CLR	367	69	DP	419	44	SUM
159	75	-	212	00	0	264	04	04	316	98	ADV	368	04	04	420	92	RTN
160	01	1	213	69	DP	265	43	RCL	317	01	1	369	43	RCL	421	76	LBL
161	95	=	214	02	02	266	02	02	318	04	4	370	13	13	422	18	C'
162	42	STD	215	00	0	267	69	DP	319	04	4	371	69	DP	423	42	STD
163	12	12	216	00	0	268	06	06	320	03	3	372	06	06	424	09	09
164	43	RCL	217	03	3	269	01	1	321	00	0	373	98	ADV	425	48	EXC
165	03	03	218	06	6	270	04	4	322	00	0	374	92	RTN	426	02	02
166	55	+	219	02	2	271	04	4	323	00	0	375	76	LBL	427	48	EXC
167	01	1	220	06	6	272	03	3	324	00	0	376	15	E	428	16	16
168	00	0	221	02	2	273	06	6	325	69	DP	377	42	STD	429	71	SBR
169	95	=	222	04	4	274	03	3	326	04	04	378	05	05	430	30	TAN
170	22	INV	223	03	3	275	01	1	327	43	RCL	379	71	SBR	431	71	SBR
171	28	LOG	224	05	5	276	03	3	328	08	08	380	30	TAN	432	38	SIN
172	75	-	225	69	DP	277	69	DP	329	69	DP	381	43	RCL	433	55	+
173	01	1	226	03	03	278	04	04	330	06	06	382	10	10	434	43	RCL
174	95	=	227	03	3	279	43	RCL	331	02	2	383	71	SBR	435	06	06
175	35	1/X	228	07	7	280	05	05	332	04	4	384	38	SIN	436	95	=
176	65	x	229	03	3	281	69	DP	333	02	2	385	55	+	437	42	STD
177	43	RCL	230	06	6	282	06	06	334	07	7	386	43	RCL	438	11	11
178	12	12	231	00	0	283	01	1	335	00	0	387	06	06	439	71	SBR
179	95	=	232	00	0	284	03	3	336	00	0	388	95	=	440	39	CDS
180	34	FX	233	00	0	285	03	3	337	00	0	389	42	STD	441	65	x
181	42	STD	234	00	0	286	00	0	338	00	0	390	11	11	442	43	RCL
182	10	10	235	00	0	287	00	0	339	69	DP	391	71	SBR	443	05	05
183	92	RTN	236	00	0	288	00	0	340	04	04	392	39	CDS	444	55	+
184	76	LBL	237	69	DP	289	00	0	341	43	RCL	393	42	STD	445	43	RCL
185	49	PRD	238	04	04	290	00	0	342	09	09	394	07	07	446	07	07
186	25	CLR	239	69	DP	291	69	DP	343	69	DP	395	71	SBR	447	95	=
187	69	DP	240	05	05	292	04	04	344	06	06	396	49	PRD	448	42	STD
188	00	00	241	02	2	293	43	RCL	345	02	2	397	92	RTN	449	08	08
189	69	DP	242	01	1	294	03	03	346	01	1	398	76	LBL	450	71	SBR
190	01	01	243	03	3	295	69	DP	347	00	0	399	17	B'	451	48	EXC
191	00	0	244	02	2	296	06	06	348	02	2	400	42	STD	452	71	SBR
192	00	0	245	00	0	297	03	3	349	00	0	401	08	08	453	44	SUM
193	00	0	246	00	0	298	01	1	350	00	0	402	71	SBR	454	25	CLR
194	00	0	247	00	0	299	00	0	351	00	0	403	28	LOG	455	43	RCL
195	00	0	248	00	0	300	00	0	352	00	0	404	71	SBR	456	16	16
196	00	0	249	69	DP	301	00	0	353	69	DP	405	38	SIN	457	42	STD
197	02	2	250	04	04	302	00	0	354	04	04	406	65	x	458	09	09
198	01	1	251	43	RCL	303	00	0	355	43	RCL	407	43	RCL	459	48	EXC
199	02	2	252	04	04	304	00	0	356	14	14	408	06	06	460	02	02
200	04	4	253	69	DP	305	69	DP	357	69	DP	409	95	=	461	92	RTN
201	69	DP															

Figure 9. A Listing of the Loss Equation Program.

● The TI 59 calculator does not have an inverse Cosh function

The relationship:

$\text{Cosh}^{-1} x = \ln(x + \sqrt{x^2 - 1})$ for $x \geq 1$ was used in the program

Conclusion: A procedure to select the design parameters for a filter using a programmable calculator has been described. The method provides accurate solutions to the

Chebyshev loss equation to provide design specifications for:

- center frequency
- operational bandwidth
- bandwidth ripple
- rejection for out of band signals

The procedure also provides an accurate tool for trading rejection margin, ripple and passband margin.

Appendix A

Given constant rejection, ripple bandwidth, ripple and large rejection (≥ 10 dB). Rejection will increase linearly, for a given rejection bandwidth, for each pole added to the Chebyshev equation.

$$A \text{ dB} = 10 \log \{1 + (10^{AM/10} - 1) \text{Cosh}^2(N \text{Cosh}^{-1} W')\} \quad \text{Eq. (1)}$$

For $\phi = \text{Cosh}^{-1} W'$ for AM and W'

Then $A \text{ dB} \approx 10 \log(1 + K \text{Cosh}^2 N\phi)$

For $K \text{Cosh}^2 N\phi \gg 1$ or $A \text{ dB} \geq 10$ dB

$$A \text{ dB} \approx 10 \log K \text{Cosh}^2 N\phi$$

$$\approx 10 \log K + 20 \times .434 \ln \text{Cosh } N\phi$$

$$A \text{ dB} \approx 10 \log K + 8.68 \left(N\phi + \frac{1}{N\phi} \right)$$

$\Delta A \text{ dB}$ = increase of attenuation for an additional pole

$$\Delta A \text{ dB} \approx A \text{ dB}|_{(N+1)} - A \text{ dB}|_N$$

$$= 8.68 \left[(N+1)\phi + \frac{1}{(N+1)\phi} + N\phi \frac{-1}{N\phi} \right]$$

$$\approx 8.68 \left[\phi + \left(\frac{1}{N+1} - \frac{1}{N} \right) \frac{1}{\phi} \right]$$

$$= 8.68 \left[\phi - \frac{1}{N(N+1)\phi} \right]$$

For $N > 2$

Then $A \text{ dB} \approx 8.68 \phi$ Equation (2)

Appendix B

Changing only the ripple (AM) (the number of poles (N) and the ratio of bandwidth to ripple bandwidth (W') remaining constant). The attenuation will increase as the log of the ratio of the ripple for large rejection (≥ 10 dB) and small ripple ($\approx 3/4$ dB).

$$A \text{ dB} = 10 \log \{1 + (10^{AM/10} - 1) \text{Cosh}^2(N \text{Cosh}^{-1} W')\}$$

Eq. (1)

for N & W' constant

$$A \text{ dB} = 10 \log \{1 + (10^{AM/10} - 1) K\}$$

rearranging terms

$$10^{A \text{ dB}/10} - 1 = (10^{AM/10} - 1) K$$

for $10^{A \text{ dB}/10} \gg 1$ large rejection ($A \text{ dB} \geq 10$)

$$10^{A \text{ dB}/10} \approx 1 + 10^{AM/10} \text{ small ripple } (\approx 3/4 \text{ dB})$$

$$\text{then } 10^{A \text{ dB}/10} \approx (AM/10) K$$

$$\text{or } A \text{ dB} \approx 10 \log \frac{K}{10} + 10 \log AM$$

$$\text{So } \Delta A \text{ dB} = A \text{ dB}|_{AM2} - A \text{ dB}|_{AM1}$$

$$\approx 10 \log AM2 - 10 \log AM1$$

$$\text{Then } \Delta A \text{ dB} \approx 10 \log \frac{AM2}{AM1} \quad \text{Equation (3)}$$

Appendix C

Using the linear relationship, Equation (2), to solve numerical Example 1.

$$\Delta A \text{ dB} \approx 8.68 \text{Cosh}^{-1} W' = \text{Constant}$$

where

$\Delta A \text{ dB}$ = increase in attenuation per added pole

and $A \text{ dB} \geq 10$ dB

Instead of trial and error two samples, $N = 3$ (IL = 10.4) and $N = 4$ (IL = 18.4), could have been used to solve for the needed number of poles.

For example:

From figure 3

for

N	BW	IL	$\Delta A \text{ dB}$
3	210	10.37	
4	210	18.35	7.98 \approx 8

for 32 dB rejection how many additional poles are required?

$18.35 + 8x = 32$ where $x = 1.7$ additional poles so that $4 + 1.7 = 5.7$ poles are needed. Again six poles are selected, and there is rejection margin. ☐



AN IMPROVED LUMPED-CONSTANT HYBRID

Here is a lumped-constant "L" matching hybrid which performs better than the conventional lumped-constant Wilkinson Hybrid and is readily constructed at 175 MHz and below. It also readily transforms impedance at the same time as splitting or combining power.

*By Ernie Franke and Wayne Faulkenberry
General Electric Company
Mountain View Road
Lynchburg, Virginia 24502*

Designers of medium power RF amplifiers use hybrids to achieve output powers greater than about 75 watts. The power density in a single transistor is so large that two transistors or two modules must be combined to achieve this power. Power combining is accomplished by using a hybrid. Hybrid junctions may be used to combine or to split power. This makes the device reciprocal. An example of using the hybrid in a mobile radio power amplifier for splitting and combining power is shown in Figure 1.

The hybrid must present the proper impedance at all ports. It must also provide isolation between the side ports. Maintaining spectral purity in a mobile radio power amplifier under the conditions of variations in supply voltage, RF drive power, operating temperature and load impedance is difficult enough with a single output transistor. If two transistors are connected in parallel at the output to achieve higher power, the interaction of dynamic impedances makes the job even more difficult. Thus we need the hybrid which offers high isolation between the side ports.

At frequencies below 175 MHz the hybrid is typically formed using lumped-constants. The familiar Wilkinson¹ Hybrid is formed with quarter-wave transmission lines synthesized with two pi sections. A typical example of this lumped-constant Wilkinson Hybrid used in an RF amplifier is given by Ken Dufour.² It is suggested that the performance of this amplifier can be improved by replacing the Wilkinson with an "L" network hybrid. This hybrid is based on the familiar "L" matching network. Both of these hybrids are shown in Figure 2 for comparison. The Wilkinson uses quarter-wave or 90° phase-shift lines. The improvement uses "L" matching networks with a phase-shift dependent on any impedance transformation.

Wilkinson Lumped Constant

The Wilkinson Hybrid is composed of two quarter-wave (90° phase shift) lines connected together at the summation port. The artificial transmission line can be synthesized using a pi section as shown in Figure 3a. We could just as easily have used the "T" section.³ The combined pi sections are also shown forming the Wilkinson Hybrid. Power applied at the sum port 1 will be split equally (3.01 dB) between side port 2 and side port 3. The impedance looking into any port will be 50 ohms, provided that the other ports are properly terminated.

The beauty of the Wilkinson Hybrid is that side port 2 is isolated from port 3. This isolation is achieved by using the balance resistor R1. The transmission path from side port 2 to side port 3 is shown re-drawn as two paths in Figure 3b. Power from a signal generator injected at side port 2 traveling through the two pi sections undergoes a 6 dB loss and a 180° phase shift before exiting at the termination placed at side port 3. The alternate path from side port 2 to port 3 is through the balance resistor R1. This path also introduces a 6 dB loss but zero phase shift. The re-combined signal at port 3 is thus cancelled out as two equal amplitude, 180° out-of-phase signals. This isolation is needed to prevent interaction when combining the power from two transistors or from two modules. A value of 20 dB of isolation is considered adequate. Any reflected power at port 2 will then be reduced by a factor of 100 before appearing at port 3.

The theoretical performance of a 50 ohm Wilkinson Hybrid is shown in Figure 4. The results are plotted on a normalized frequency scale so that the designer can merely multiply by the design center frequency to predict the response at any particular frequency. The input return loss at the sum port is better than 15 dB ($SWR \leq 1.4$), insertion loss less 3.15 dB, and side port isolation greater than 20 dB over a 24 percent bandwidth. (Percent bandwidth is deter-

mined by dividing the measured bandwidth by the center frequency.) This in itself is good but the L network lumped-constant hybrid is better.

“L” Network Hybrid

The L network hybrid is shown dissected into two L matching networks in Figure 5a. We can accomplish this dissection because any components placed between the side ports such as C5 and R2 do not affect equal power splitting. Because the voltage and phase at side port 2 is the same as that at side port 3, no current will flow through any component connected between them. The hybrid is composed of two “L” matching networks connected together at the sum port. Because these two matching networks are in parallel at the sum port, they must individually have a 100 ohm input impedance (R4). The output impedance

(R3) is made equal to the side port impedance of 50 ohms. The design of an “L” network⁴ indicates that:

$$L = \frac{R3 \sqrt{(R4/R3) - 1}}{2\pi f}$$

$$C = \frac{\sqrt{(R4/R3) - 1}}{2\pi f R4}$$

where $R4 > R3$

L = inductor in henries

C = capacitance in farads

f = frequency in hertz

π = pi, 3.14159

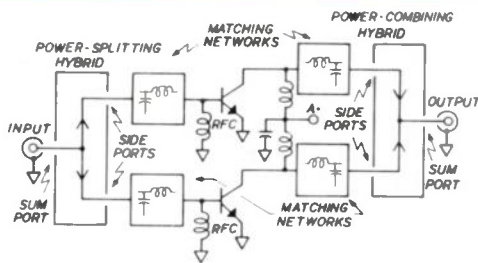


Figure 1. The reciprocity of the hybrid is demonstrated by its use as a power splitter at the input and a combiner at the output.

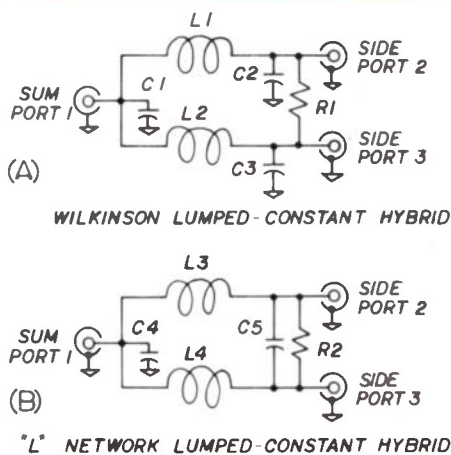


Figure 2. The schematic for the Wilkinson hybrid (a) differs from the “L” Network hybrid (b) only in the capacitors across or in shunt with the side ports.

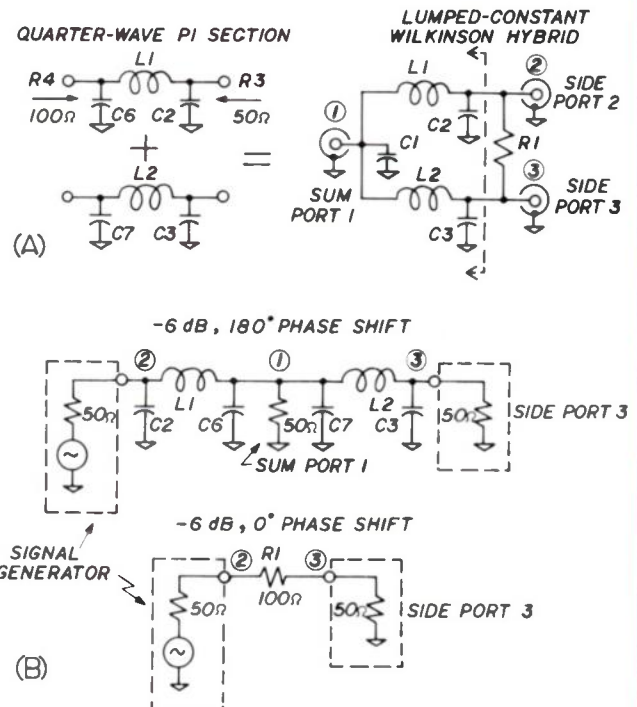


Figure 3. The Wilkinson hybrid uses two 90° artificial line sections (a). The isolation is achieved by two equal loss, 180° out-of-phase paths (b).

Wilkinson Hybrid		Low-pass "L" Network Hybrid		High-pass "L" Network Hybrid	
Component	Formula	Component	Formula	Component	Formula
C1	$1/(\pi f \sqrt{R4R3})$	C4	$[\sqrt{(R4/R3) - 1}]/\pi f R4$	C10, C11	$1/[2\pi f R3 \sqrt{(R4/R3) - 1}]$
C2, C	$1/(2\pi f \sqrt{R4R3})$	C5	$1/[4\pi f R3 \sqrt{(R4/R3) - 1}]$	L5	$R4/[4\pi f \sqrt{(R4/R3) - 1}]$
L1, L2	$(\sqrt{R4R3})/2\pi f$	L3, L4	$[R3 \sqrt{(R4/R3) - 1}]/2\pi f$	L6	$[R3 \sqrt{(R4/R3) - 1}]/\pi f$
R1	2R3	R2	2R3	R5	2R3

where $\pi = 3.14159$

f = frequency in Hertz

R3 = impedance of side port termination

R4 = twice the sum port termination

Table 1. Calculation for the components of a lumped-constant hybrid.

Let's consider the design of a 52 MHz hybrid for example. We substitute $R4 = 100\Omega$, $R3 = 50\Omega$, and $f = 52$ MHz into the above equations.

$$L3, L4 = \frac{50 \sqrt{(100/50) - 1}}{(2 \times 3.14) (52 \times 10^6)} = 153 \text{ nH}$$

$$C8, C9 = \frac{\sqrt{(100/50) - 1}}{(2 \times 3.14) (52 \times 10^6) (100)} = 30.6 \text{ pF}$$

When the two L networks are combined into a hybrid we find that the shunt capacitor C4 at the sum port is equal to the sum of C8 and C9. This forms the "L" network power splitter/combiner. The performance is predicted in Figure 4. The sum port return loss is improved while the insertion loss is reduced as compared to the Wilkinson Hybrid. The isolation for either hybrid is practically equal. The return loss at each side port is not shown because it is always quite good (≥ 20 dB over a 40 percent bandwidth).

The phase shift of an L matching network at the center frequency is defined by the equation:

$$\cos B = \sqrt{R3/R4}$$

where B = phase shift in degrees

The L matching network needed for this lumped constant network must match the 100 ohm impedance connected to the sum port down to a 50 ohm impedance at either side port, $R4 = 100$ ohms and $R3 = 50$ ohms.

$$\cos B = \sqrt{50/100} = 0.707$$

$$B = 45^\circ$$

The phase shift for a wave travelling between the sum port and either side port is 45° . For a Wilkinson Hybrid this value is always 90° .

The isolation between side ports is only 6 dB at the center frequency if we only use the two L networks to form the hybrid. This means that one-fourth of any mismatched energy at one side port appears at the other side port. The balance network (Figure 2b) consisting of resistor R2 and capacitor C5 increases the isolation to greater than 20 dB over a 20 percent bandwidth. These balance components do not even enter into the power splitting portion of the circuit because they are placed between equal amplitude/phase points. As long as the power divides equally and the phase shift in each leg is equal, there will be no current flow in any device placed between side port 2 and side port 3.

The balance network used to increase isolation consists of two paths. One path is through the "bridged-tee" network as shown in Figure 5b. The 6 dB loss, 180° phase shift in this path must again be cancelled out by the

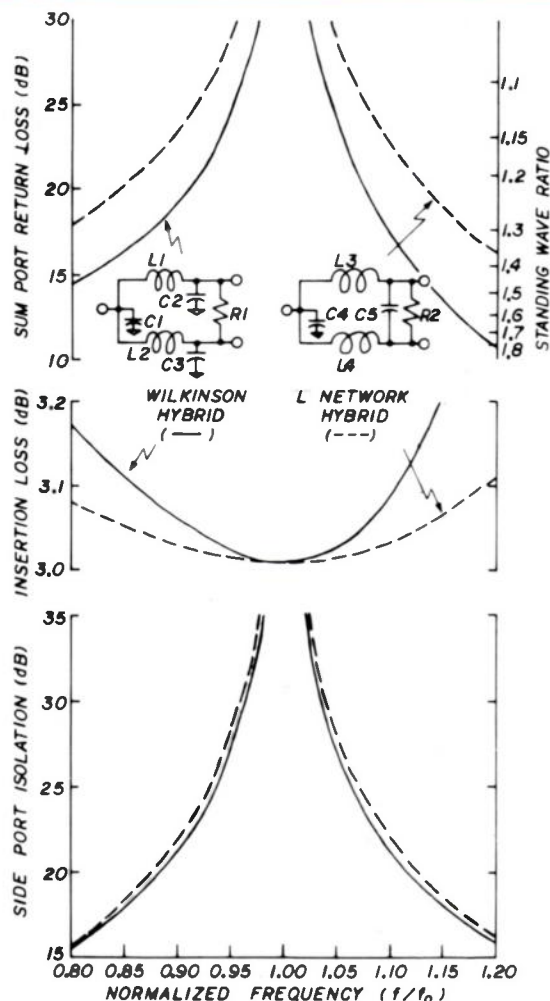


Figure 4. The theoretical response of the Wilkinson (solid line) is less than the response of the "L" Network hybrid (dotted line).

Frequency (MHz)	C1 (pF)	C2 (pF)	L1, 2 (nH)	Number Turns	ID (Inch)	Wire Size AWG
29	110	55	274	10	0.30	14
52	62	30	153	6	0.30	16
146	22	10	54	4	0.22	16

Table 2. Experimental Models.

6 dB loss, 0° phase shift resistive path through R2. The value of the balance capacitor C5 is set so that its capacitive reactance exactly equals the inductive reactance of L3 plus L4. The value of the balance resistor R2 is still twice the side port impedance.

$$C5 = \frac{1}{2(2\pi f \times R3 \times \sqrt{[R4/R3 - 1]})}$$

$$R2 = 2R3$$

The calculations for constructing either a Wilkinson or an "L" network hybrid are summarized in Table 1.

Experimental Models

Several "L" network lumped-constant models were constructed according to the values shown in Table 2 for 29, 52, and 146 MHz. The measured results are shown in Figure 6, along with a photograph of one of the models. The experimental results agree quite well with the predicted performance. The capacitors were formed by tacking several values together to achieve the calculated values.

The input shunt capacitor should be as close to the calculated values as possible for a good starting point. The value should be selected using a bridge or a digital

capacitance meter. The inductors are then adjusted by injecting a signal at the sum port and minimizing the reflected signal into the sum port at the center frequency with the side ports properly terminated. The inductors are optimized by using "diddle" sticks with a core of ferrite on one end and a brass slug on the other end. The presence of brass lowers the inductance of the coils. The isolation is next maximized by injecting a signal into one side port and minimizing the detected energy at the other side port. The balance capacitor C5 is adjusted for maximum attenuation. The coils must be sufficiently spaced from each other so that there is minimal coupling. The largest manageable wire size is used to make self-supporting coils. Figure 7 shows the worse-case theoretical response when all of the components are varied by ± 10 percent. Even if all of the parts

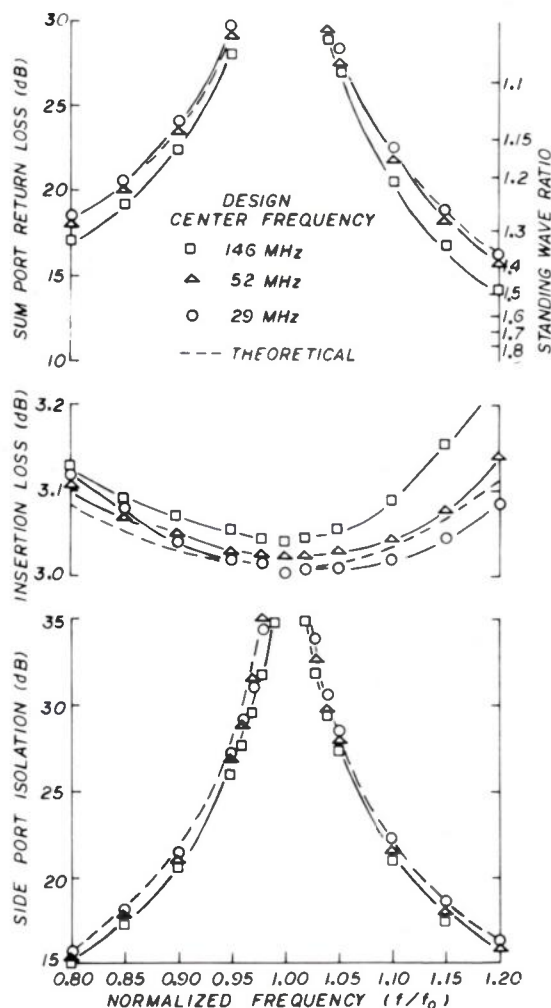
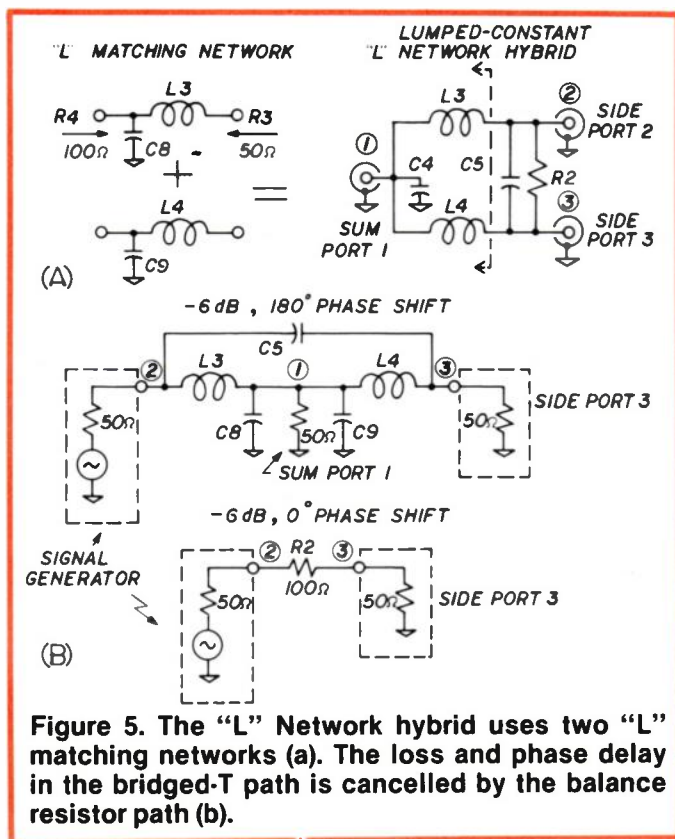


Figure 6. The experimental results for a 10 meter, 6 meter, and 2 meter "L" Network hybrid.

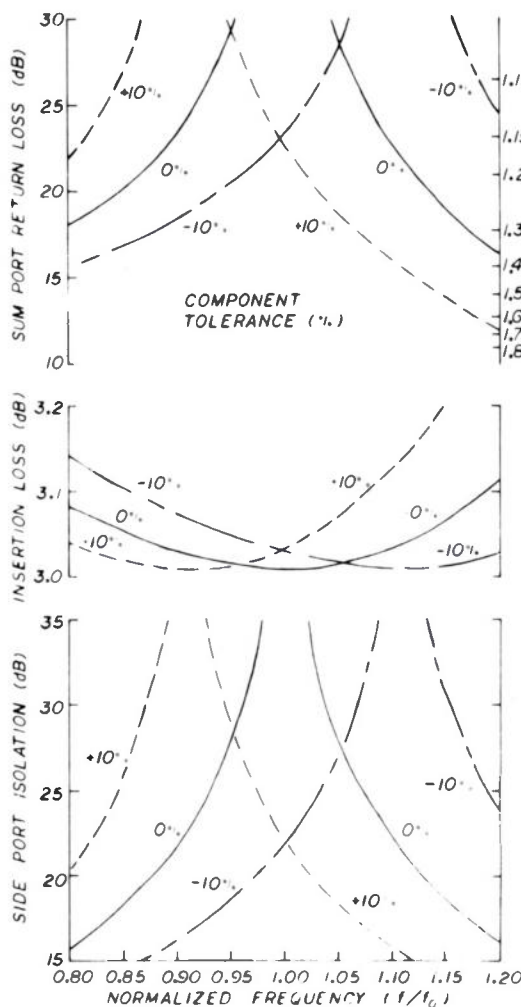


Figure 7. Theoretical response of the "L" Network hybrid when all of the components are varied by ± 10 percent.

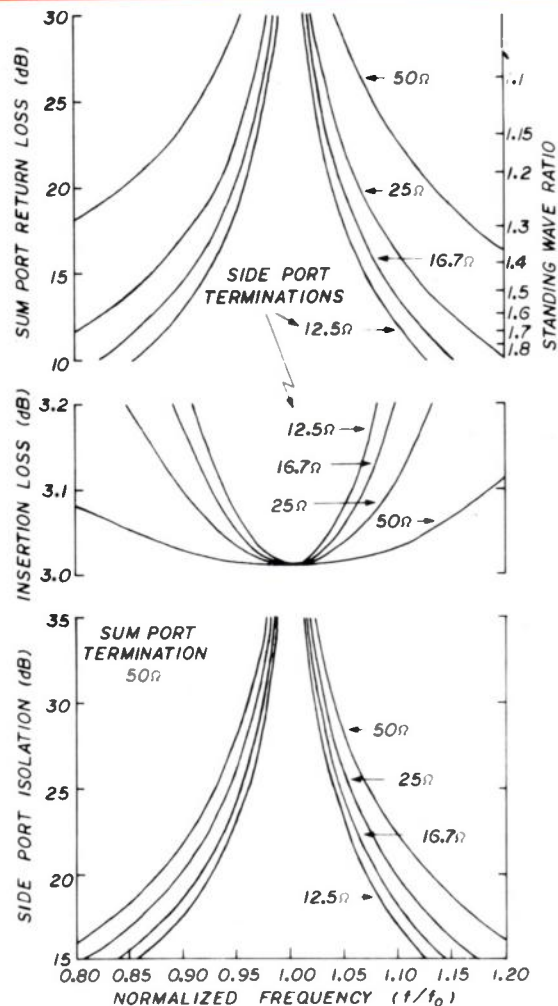


Figure 8. Theoretical response of the "L" network hybrid when used as a hybrid and as an impedance transformer for side port impedances of 50, 25, 16.7, and 12.5 ohms.

vary by 10 percent the sum port return loss is greater than 15 dB, the insertion loss less than 3.15 dB, and the side port isolation is better than 15 dB over a 24 percent bandwidth.

Impedance Transformation

Until now we have only considered hybrids which presented 50 ohms impedance at each port. In practice it is usually desirable to transform impedances at the same time we are combining or splitting power. A good example of this is the hybrid used to combine the power from the collector circuits of two transistors. Instead of using a multi-section network to raise the extremely low transistor output impedance up to 50 ohms we might design a hybrid with a side port of 25 or maybe 12.5 ohms input impedance. A penalty is paid in bandwidth anytime the Q or the impedance transformation ratio is increased, but that penalty must be paid somewhere. As an example, consider two cases for transforming a collector resistance of 2 ohms up to an antenna impedance of 50 ohms where the design is limited to only two "L" matching sections plus the hybrid. The Q of an "L" network is given as

$$Q = \sqrt{Z_{\text{Ratio}} - 1}$$

where Z_{Ratio} is the ratio of the input to output resistive component of impedance.

For the first case two "L" sections are placed before the 50 ohm hybrid. The impedance transformation ratio is

$$Z_{\text{ratio}} = \frac{\left(\frac{50 \text{ ohms}}{2 \text{ ohms}} \right)^{\frac{1}{\text{Number of sections}}}}{2} = 5$$

$$Q = \sqrt{5 - 1} = 2$$

Thus, the Q of two for each of the first two sections would do most of the band-limiting. The "L" network within the 50 ohm hybrid has a Q of 1.

For the second case let us still be limited to two "L" matching sections but consider the "L" section within the hybrid as a variable. Thus, effectively there are three sections of matching. The final impedance will be the 100 ohms presented by one-half the hybrid at the sum port.

$$Z_{\text{ratio}} = \frac{100^{\frac{1}{3}}}{2} = 3.68$$

$$Q = \sqrt{3.68 - 1} = 1.64$$

Now each matching section is band-limiting equally with individual Q's of 1.64. This yields a wider bandwidth amplifier for the same number of parts. The theoretical results when using the hybrids to transform impedances are shown in Figure 8 using the same equations as before where R4 is always equal to 100 ohms and R3 is equal to the side port impedance. It appears that a ratio of 50 ohms to 25 ohms is the limit for wideband amplifiers. Just as the experimental results matched quite well with the predicted results for the equal impedance case, similar results for the case of impedance transformations can be expected.

The phase shift through each arm of the L network hybrid is no longer 45° as in the 50 ohm hybrid but equal to the arcsine of the square root of the impedance ratio. For the case of a 4:1 impedance transformation, where the sum port is 50 ohms and the side port is 12.5 ohms $R4 = 100$, $R3 = 12.5$.

$$\cos B = \sqrt{R3/R4} = \sqrt{12.5/100}$$

$$B = 82.8^\circ$$

High-pass Version

When forming the "L" matching network in the lumped-constant hybrid the low-pass version was naturally chosen. Alternatively, the high-pass version as shown in Figure 9 could have been chosen. The individual "L" sections are combined with the junction shunt inductance L5 equal to the electrical paralleling of L7 and L8. The balance network used for isolation consists of L6 and R5. As before, consider the two possible paths between side ports. The path through the matching networks is made to equal 6 dB loss and 180° phase shift by resonating the inductance L6 with the series sum of the capacitors C10 and C11. The alternate

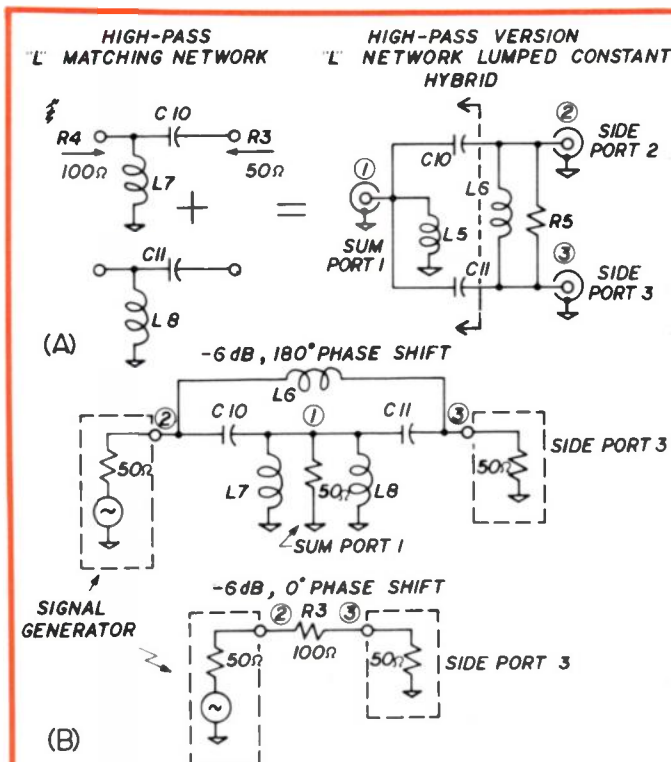


Figure 9. The High-Pass "L" Network hybrid uses two high-pass "L" matching networks (a). The loss and phase delay in the bridged-tee path are cancelled by the balance resistor path (b).

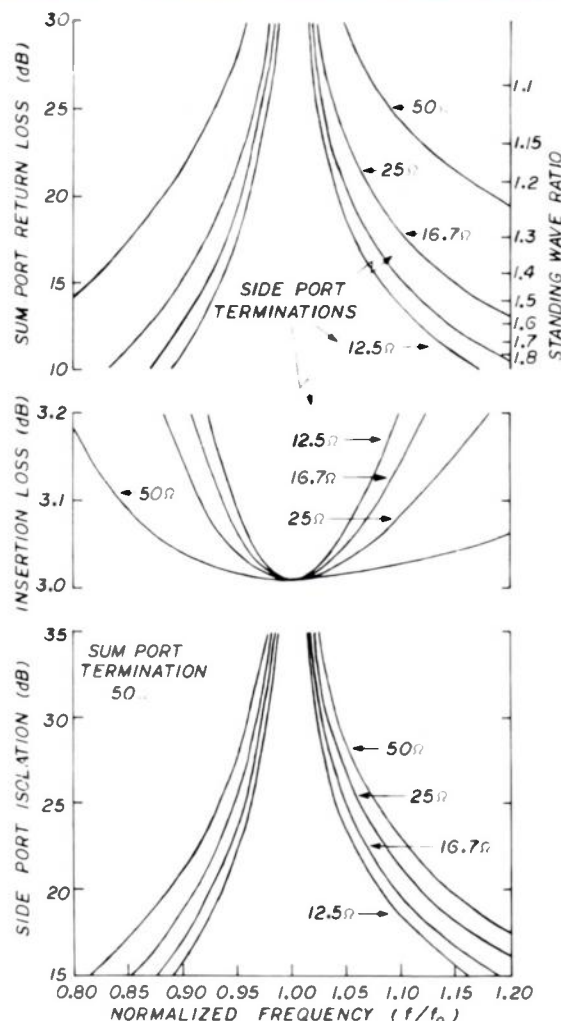


Figure 10. Theoretical response of the High-Pass "L" Network Hybrid for side port impedances of 50, 25, 16.7 and 12.5 ohms.

path through R3 is again made equal to twice the side port impedance to achieve the necessary 6 dB loss, zero degree phase shift.

Normally, the low-pass version of the lumped-constant combiner is preferred because it does offer additional harmonic attenuation. The high-pass version does offer the advantage of having built-in coupling capacitors. It also offers space advantages if the balance inductor L6 is wound around R5.

The theoretical results for the high-pass version are shown in Figure 10. They differ from the low-pass curves in that they are skewed toward the higher frequencies.


References

1. E.J. Wilkinson, "An N-Way Hybrid Power Divider," *IRE Trans. on Microwave Theory and Techniques*, Vol. MTT-8, January 1960, pp. 116-118.
2. Ken Dufour, "60 Watt VHF Amplifier Using Splitting/Combining Techniques," *r.f. design*, September/October 1981, pp. 18-23. Motorola Engineering Bulletin EB-93.
3. F.E. Terman, *Electronic and Radio Engineering*, McGraw-Hill, 1955, pp. 112-115.
4. Ernie Franke, WA2EWT, "Appreciating the L Matching Network," *Ham Radio*, September, 1980, pp. 26-30.

Hi-heat Pumping Thermoelectric Modules

A new series of Cambion "Cool and Heat" TE devices for low cost cooling and close temperature control uses are realized because the new TE modules are supplied *without metalized pads* with no sacrifice in performance. Thermal performance is at least as high as conventional TE devices having metal plates on the module surfaces.

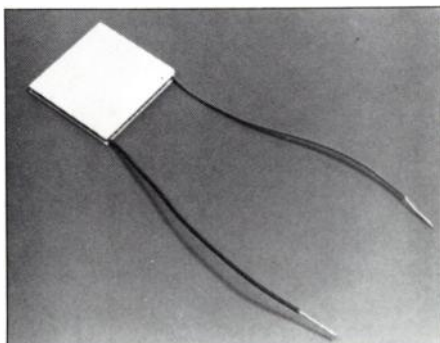Available in "off-the-shelf" production quantities, the new economical TE




modules provide a range of 20 watts through 45 watts heat-pumping capacity at current ratings from 7 through 14 amperes.

Contact Cambion Customer Service at 445 Concord Avenue, Cambridge, MA 02238. (617) 491-5400. Please circle INFO/CARD #140.

Microwave Power Meters Measure Peak Power Directly

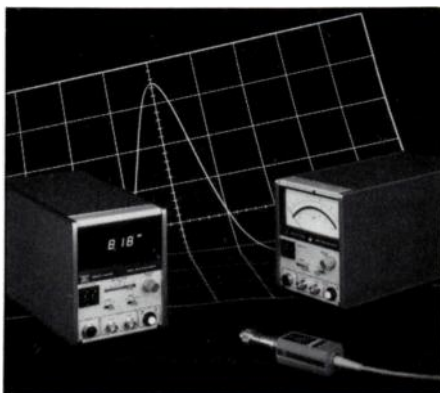Two new microwave power meters — one digital, the other analog — have been announced by Hewlett-Packard Company. The meters will measure



peak power output of pulsed microwave systems from 1 to 100 mW, and from 100 MHz to 18 GHz.

The HP 8900C has an analog meter for easy peaking of pulsed power while the HP 8900D uses a digital display with range annunciators for unambiguous readings.

Both measure peak power directly instead of the old method of using an average power meter and a duty cycle computation. This new technique reduces the chance for both instrument and computation error.

In conjunction with the HP 84811A peak power sensor, the new method covers most RF and microwave applications of pulsed power systems.

Each meter has two operating modes:

- *Direct mode* senses and displays peak power with no adjustments.
- *Compare mode* drives an external oscilloscope to provide a video reproduction of the pulse envelope along with an adjustable reference line. The operator then positions the line to correspond to various points of a pulse — overshoot, for example — and reads out the power level of the reference line.

The HP 84811A peak power sensor responds accurately to peak power from 1 mW to 100 mW, pulse widths from 1 microsecond to CW and repetition rates from 100 Hz to 100 kHz. Each sensor also is furnished with a correction factor table vs. frequency that can be set into the meter to correct the reading for sensor frequency response.

SWR is less than 1.5 from 10 MHz to 12 GHz and less than 2.0 from 12 GHz to 18 GHz. Maximum power overload is 250 mW.

As an additional convenience for system measurements that sample power with a directional coupler, the HP 8900D digital meter features 0-60 dB power offset in 10 dB steps. By setting in the coupling value, the meter thus displays up to 100 kilowatts directly.

Overall measuring uncertainty depends on frequency but is approximately ± 1.5 dB at 12 GHz, exclusive of mismatch effects. Recorder output allows leveling of peak power sources, and the video output permits digitizing of the waveform with external equipment. INFO/CARD #139.

1400 MHz Prescaler

Phasetec Corporation of West Peabody, Mass., a growing electronics manufacturer, has introduced its new model PHT 1300 Divide by 1000 Prescaler, which can extend the range of your existing counter to 1400 MHz, thus providing a high performance, low cost alternative for microwave frequency measurement.

An ideal addition to any lab bench or test station, this easy-to-use AC operated Prescaler divides input frequency by 1000. The PHT 1300 Prescaler features low input VSWR, high sensitivity, and wide dynamic range over the 10-1400 MHz spectrum. Internal threshold circuitry provides output



gating plus a clear visual indication of minimum input operating level.

The PHT 1300 Prescaler is now available from stock for \$239. For additional information contact Jeff Schiffer, president, Phasetec Corporation, P.O. Box 2086, West Peabody, MA 01960. (617) 535-4833. INFO/CARD #138.

Planar Capacitor Array

Viclan, Inc. introduces a new Planar Capacitor Array (PCA) that provides a combination of multi-line EMI filtering with mass termination at the connector interface. One Viclan PCA may be used to replace as many as 128 single-line filtering devices — allowing significant reductions in weight, space, and cost.

The Viclan PCA consists of a monolithic ceramic package with a customer-specified number and pattern of capacitors to fit connector pin arrangements.

Viclan PCA's are available in circular, subminiature D, dual-in-line, and



other custom shapes. Planars may be used in the design of "C," "L," "T," and "Pi" style filters. Capacitance values up to 10,000 pF. Voltage ratings up to 600 VDC or 230 VAC.

Engineering samples of your custom requirements available in four weeks. Pricing per line as low as 25 cents, depending on quantity and complexity of design.

For more information contact your local Viclan representative, or call Maurice Westbury, Viclan, Inc., (714) 292-1411. Write 7373A Engineer Road, San Diego, CA 92111. INFO/CARD #137.

Automatic/Manual Transceiver Test Set

A new transceiver test set that provides fully automatic or manual operation by combining general-purpose instruments into one test system has been announced by Hewlett-Packard Company.

Performing both automatic and manual in-channel tests of AM, FM and ϕ M communications receivers and transmitters, the new test set meets transceiver testing needs at the lowest prices ever set for an HP product with this capability.

Modular in structure, the HP 8953A combines the measurement power of the HP 8901A modulation analyzer, HP 8903A audio analyzer and HP 8656A synthesized signal generator with the HP 8954A transceiver interface, all necessary cables and accessories, and a choice of instrument controllers. As a combination of standard HP instruments, it can be assembled from on-hand components and purchased items or obtained as a complete test set.

Both the HP-85F instrument controller and the recently introduced HP 9826A desktop computer are available as controller options. Together these instruments and controllers per-



PTS SYNTHESIZER FLEXIBILITY



**RANGE, INTERFACE
CABINET, ATTR
EXTRA OUTPUTS**



PTS 160

PTS 200

**More basic performance per dollar...
and more options to meet your specifications**

	PTS 160/200	FLUKE 6160B	WAVETEK ROCKLAND 5600
160 MHz or 200 MHz	✓	NO	NO
Built-in GPIB or par. program	✓	NO	NO
Optional Resolution 0.1 Hz — 100 KHz	✓	NO	✓
Metered Output	✓	NO	NO
20 μ s Switching	✓	NO	✓
99 dB programmable Attenuator	✓	NO	NO

Price: PTS160, 1 Hz Res, Rem. only, TCXO, \$4,625.00 — (Sample)

PTS
FREQUENCY SYNTHESIZERS

PROGRAMMED TEST SOURCES, INC.
BEAVERBROOK RD., LITTLETON, MA 01460
(617) 486-3008
INFO/CARD 15

form simple tests such as frequency and distortion as well as complex measurements such as receiver-usable sensitivity and audio flatness in just a few seconds.

For those requiring additional measurement capabilities such as out-of-channel or SSB testing, the test set's HP 8954A transceiver interface provides additional instrument connections.

A second RF signal generator such as an HP 8662A synthesized signal generator may be added for out-of-channel receiver testing and a second RF monitor such as the HP 8568A spectrum analyzer or the HP 3586C

selective-level meter is available for out-of-channel transmitter and SSB testing.

The HP 8953A transceiver test set's three key instruments — the HP 8901A, HP 8903A and HP 8656A — are general-purpose, fully programmable instruments with HB-IB (IEEE-488) interface for remote control. Both manually and under remote control, these instruments perform complex measurements quickly and accurately.

Front-panel annunciators continuously indicate the filter, detector, measurement keys, modulation and display formats in use. The techni-

cian can monitor the state of the instruments at all times, even when they are being controlled remotely.

The HP 8656A signal generator has calibrated AM, FM and simultaneous internal and external modulation, which can generate simultaneous squelch and test tones.

For tests such as transmitter distortion, the HP 8903A audio analyzer's selectable high-pass and low-pass input filters remove unwanted signals such as noise or squelch tones. Circle INFO/CARD #136.

Flange Attenuators

New 3mm/SMA flange attenuators from EMC Technology, Inc., Cherry Hill, N.J. function as coax connectors for MIC packages while providing precise attenuation values. Series 7400 flange attenuators eliminate connector pairs to permit smaller, lower cost and more reliable packages.

These and other advantages of the new attenuators make them ideal for applications including channel amplitude balancing in receiver circuits for RF or IF packages. They are available in 1 dB increments up to 20 dB for highest flexibility, and are only 3/4" long to accommodate a package without creating design problems.

GET 10 TIMES MORE RFI PROTECTION WITH A LINDGREN "DEI" SCREEN ROOM


Lindgren's double-electrically-isolated (DEI) screen rooms offer 120 dB RF attenuation of electric and plane waves from 14 KHz to 1 GHz... up to 10 times more shielding than any other type of screen room.

This patented design keeps your design/test area interference-free despite rising ambient RFI levels. You get shielding equal to conventional solid-sheet-metal enclosures without sacrificing the see-through, hear-through and lighter-weight advantages of screen.

DEI design is superior because inner and outer screens of 0.011" dia. 22 x 22 bronze mesh are electrically separated, except for a single grounding point. Doors feature separate inside and outside RF seals on all four edges, with a single handle that assures an RF-tight closure by applying cam pressure at three points.

Built of panel modules, Lindgren RF enclosures can be moved, expanded or reshaped easily. Our patented overlapping pressure joints maintain full shielding integrity no matter how many times they're reassembled.

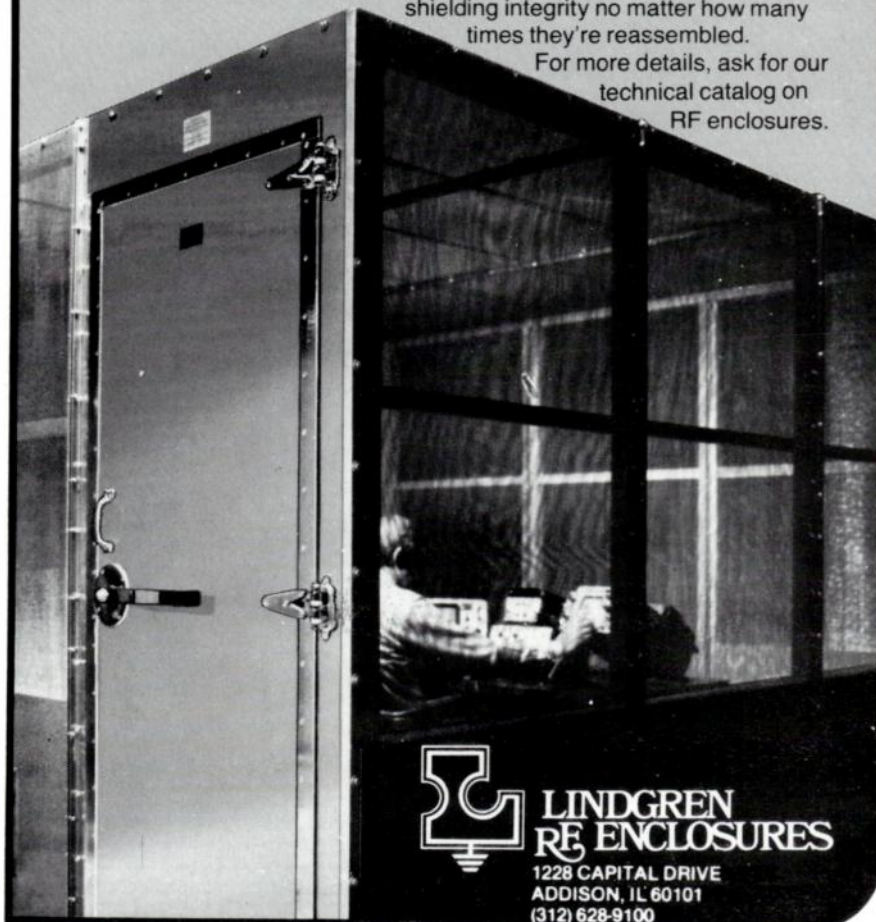For more details, ask for our technical catalog on RF enclosures.



**LINDGREN
RF ENCLOSURES**

1228 CAPITAL DRIVE
ADDISON, IL 60101
(312) 628-9100

INFO/CARD 16

rf millivoltmeter by HELPER INSTRUMENTS



Model RF-801

**An RF Voltmeter with
the traditional HELPER quality
at a realistic price.**

- **FULL VOLTAGE RANGE**
300 Microvolts to 100 Volts
- **FULL FREQUENCY RANGE**
Beyond 1 Gigahertz
- **UNIQUE PROBE DESIGN**
Permits low inductance ground connection for repeatable accurate measurements. New Teflon® tip extender.
- **LESS THAN 2 PICO FARADS**
Circuit loading in any measurement mode

AVAILABLE FROM STOCK AT:

HELPER INSTRUMENTS COMPANY

305/777-1440

P. O. BOX 3628

INDIALANTIC, FLORIDA 32903

INFO/CARD 18

A re-designed version of the company's model 4400 attenuator, series 7400 models incorporate EMC's unique interchangeable transition pins which provide precise matches between the circuit and the transmission line. The pins are available in four different configurations to meet specific requirements. Configurations include slotted, tab, standard SMA pins and machinable blank pins.

The attenuators operate from DC to 18 GHz. To assure highest electrical and mechanical performance, attenuators are constructed with passivated stainless steel bodies and gold-plated beryllium copper pins. Operating temperature ranges from -55°C to 125°C . Power rating is 1 watt at 25°C . Full calibration is also offered as an option.

Cost for the new series 7400 four-hole flange termination is \$24.64 each in 100 lot quantities; delivery is from stock to six weeks depending upon attenuation value.

Contact EMC Technology, Inc., 1971 Old Cuthbert Road, Cherry Hill, NJ 08034. (609) 429-7800. INFO/CARD #135.

Solid State Modulator

EDCO model PS103048 Modulator is designed to control 40 Watt mini-TWTs in parallel providing a 400 Volt pulse with operating frequency of CW to 2 MHz. Rise and fall delays are less than 40 nanoseconds, with a RF rise time of 5 ns. The modulator input accepts a 10 kHz square wave, 40 V peak-to-peak, and operates on 15 Watts



of standby power. Trigger pulse is 10 Volts into a 50 ohm impedance. The unit is ruggedized and designed to operate under military airborne environments. Volume is less than 34 cubic inches.

Contact Edco Engineering Corporation, 3255 Scott Blvd., Bldg. 6A, Santa Clara, CA 95050. (408) 241-7226. Telex: 171-598. INFO/CARD #133.

High Power RF Gated Amplifier Generates Pulses Up to 3 KW

A high power rf gated amplifier for use with the manufacturer's main frame

r.f. design

gating modulator and an external cw source in studies of ultrasonics and nuclear resonance is being introduced by Matec, Inc. of Warwick, R.I.

The Matec model 515A-HP R.F. Gated Amplifier features an rms pulse power output rated at 3 KW from 0.5 to 8 MHz and 1.75 KW from 8 to 20 MHz. Plugged into the firm's model 5100 Gating Modulator (Main Frame) and an external cw source, it produces sequences of coherent, high power rf pulses with pulse width and separation variable continuously or in steps of one or 10 cycles of the cw frequency.

The Matec model 515A-HP R.F. Gated Amplifier accepts cw input levels from less than 10 mV to more than 100 mV with no change in output. The unit also accepts externally generated rf pulses: i.e. a multiple rf pulse program for NMR studies, or a single rf pulse from a low level pulsed oscillator in ultrasonic applications.



The Matec model 515A-HP R.F. Gated Amplifier is priced at \$4595 (domestic); model 5100 Gating Modulator (Main Frame) at \$4450. Literature is available on request. For more information contact Matec, Inc., Bruce B. Chick, 60 Montebello Road, Warwick, RI 02886, (401) 739-9030. INFO/CARD #118.

New Testing Services

Retlif, Inc. announces the addition of two new testing services. The laboratory is now equipped to perform 200 V/M susceptibility testing over the frequency range of 10 kHz to 40 GHz. Retlif, Inc., a leader in the field of FCC compliance testing, has recently completed an expansion program in regards to its FCC test division. This program included the addition of another shielded enclosure along with automated CISPR test instrumentation in order to provide rapid testing in line with FCC Subpart J type testing. For additional information please contact our sales department at (516) 751-4600 or write Retlif, Inc., Flowerfield Bldg. 25, St. James, NY 11780. Please circle INFO/CARD #131.

Automated Scaler Network Analyzer

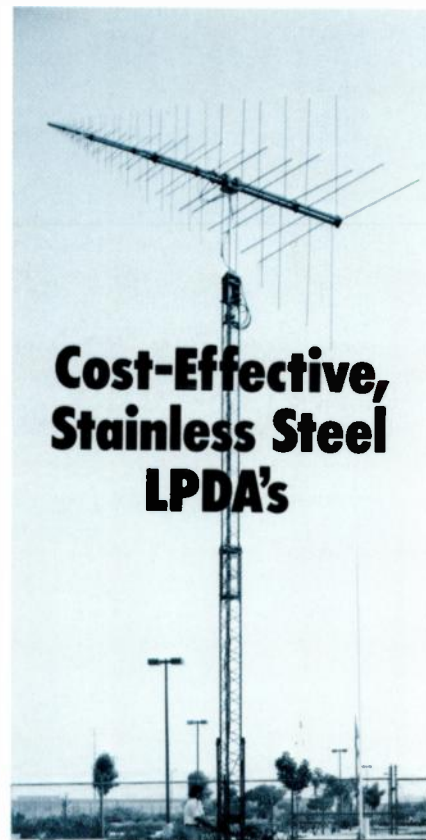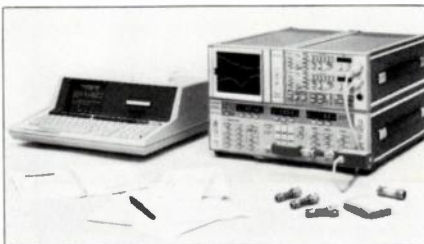The Wiltron 5609/75 Automated Scaler Network Analyzer measures return



Cost-Effective, Stainless Steel LPDA's

from 30 to 4000 MHz Linear or Dual Linear

Watkins-Johnson Company offers log-periodic dipole arrays in long-lived, corrosion-resistant, stainless-steel configurations for structural reliability. The life-cycle cost of these antennas is far less than similar antennas constructed of aluminum. Several antenna models operate between 30 MHz and 1100 MHz. One model operates from 90 to 4000 MHz.

For further details or information regarding our complete line of antennas, circle the reader service number below or phone Applications Engineering in San Jose, California, at (408) 262-1411, ext 247.



WATKINS-JOHNSON

2525 North First Street
San Jose, California 95131
Telephone: (408) 262-1411

INFO/CARD 17

loss (SWR), transmission loss or gain, and power of 75 ohm impedance devices over the 10 to 2000 MHz range.

The accuracy with which return loss can be measured is the best available because of the unmatched 40 dB directivity of the type N SWR Autotester included in the system. Accuracy is also enhanced as the system automatically subtracts residual system errors stored in memory during calibration. Errors that would otherwise be introduced by reflections from measurement components are minimized by the low 1.17 SWR of the detector used for transmission and

power measurements and by a new adapter that converts the source impedance of the 6609 Sweep Generator to 75 ohms.

Measurements begin by inserting the preprogrammed cartridge supplied in the model 85 Controller. The operator is then guided step-by-step through the straightforward test procedure. Return loss and transmission characteristics are displayed, permitting the operator to adjust the test device before a hard-copy graph or tabulation of test data is made.


Model 5609/75 is priced at \$27,490 with 90 day delivery. Contact Walt

Baxter, Wiltron Company, 805 East Middlefield Road, P.O. Box 7290, Mountain View, CA 94042-7290. (415) 969-6500. TWX: 910-379-6578. Please circle INFO/CARD #132.

CATV Hybrid Return Amplifiers

CATV hybrid return amplifiers in the 5 to 200 MHz frequency range offer high dynamic range to eliminate critical fine tuning problems. The CA 4400 series, from TRW Semiconductors, are designed for mid-split and high-split systems. They achieve a substantial improvement in dynamic range (typically 5 dB), compared with earlier models, due to the incorporation of a new-generation transistor.

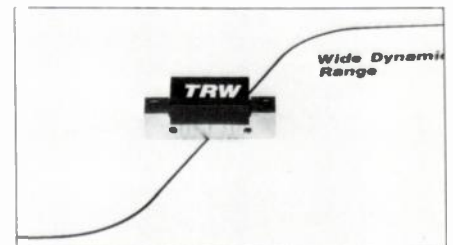Three versions are available. The CA 4412 has 13 dB of gain. And... the CA 4418 and the CA 4422 have 18.5 dB




and 22 dB of gain respectively. CA 4400 series amplifiers are available immediately from TRW Semiconductors' worldwide sales and distribution network.

For further information, contact TRW Semiconductors, 14520 Aviation Blvd., Lawndale, CA 90260. (213) 679-4561. TWX: 910-325-6206. Telex: 67-7148. INFO/CARD #130.

Log-periodic Antenna


Watkins-Johnson Company has introduced the WJ-8344 Log-Periodic Antenna featuring extremely broadband operation. This antenna covers the full 1.0 to 18.0 GHz range and is designed for use in applications where size, weight and cost are factors.

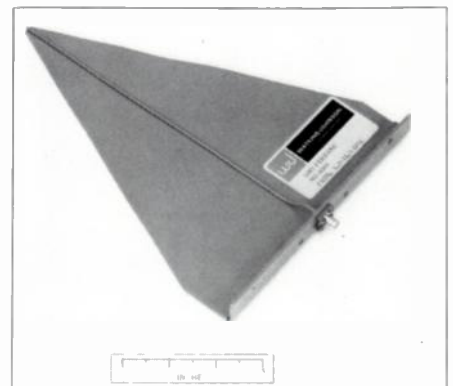The WJ-8344 features excellent VSWR (2.5:1 over the band) and a gain which ranges from 5 to 8 dB with



March/April 1982

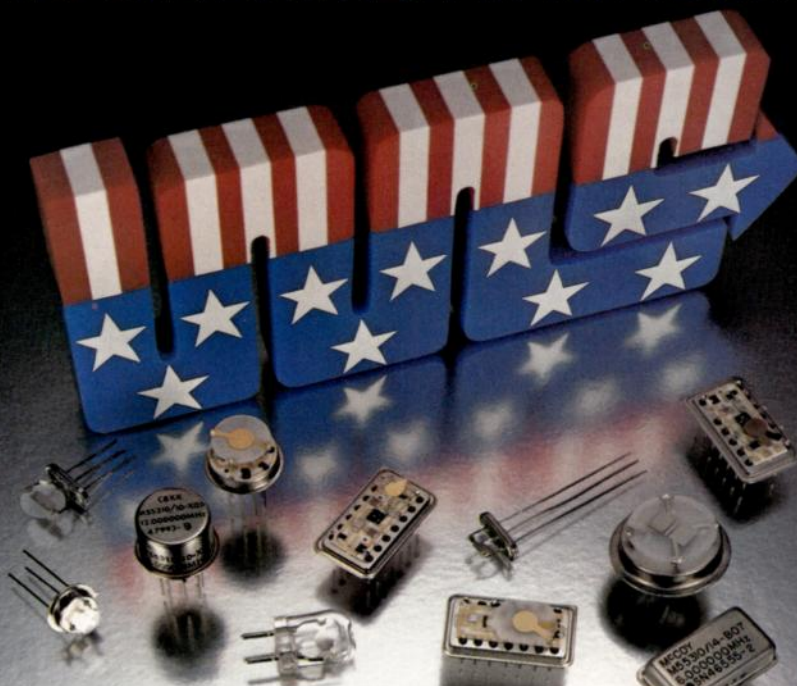AMERICAN TECHNOLOGY ... IT'S STILL THE BEST IN THE WORLD



MCCOY IS ADVANCING AMERICAN TECHNOLOGY IN QUARTZ CRYSTALS, FILTERS AND OSCILLATORS

For over three decades McCoy Electronics Company has pioneered the custom frequency control industry, and has established leadership in its field.

To assure the market place the finest performance available, McCoy manufactures all of its crystals, filters, and oscillators within the United States. The competitive challenge is being met technologically, economically, and with care to maintain the highest standards of quality.

For your next frequency control application consider McCoy. Write for free catalog.

MCCOY
ELECTRONICS COMPANY

a subsidiary of **SAE** Technology Inc.

MT. HOLLY SPRINGS, PA 17065 • 717-486-3411 - TWX: 510-650-3548

INFO/CARD 23

frequency. This unique antenna is lightweight, (less than four ounces) and is easily adapted to various mounting configurations.

Applications for the WJ-8344 include surveillance, RFI, EMC, TEMPEST, point-to-point communication and detection.

Complete details, including price and delivery, are available from Watkins-Johnson Company, Antenna Applications Engineering, 2525 North First Street, San Jose, CA 95131. (408) 262-1411, ext. 247. Please circle INFO/CARD #127.

0.5 μ m Gallium Arsenide FET

The ALF 3000 series is a high performance 0.5 μ m gate GaAs Field Effect Transistor designed for use in oscillators and low noise amplifiers up to, and above, X-band frequencies.

As with Alpha's other high performance GaAs FET products, this device



Professional Program Order Form

Please send me the following *Electro/82* Professional Program Session Records. Each Session Record is \$5.

Session No. & Title

- ☐ 1. Logic Designs for Interfacing Systems in the 1980s
- ☐ 2. Career Enrichment for Maturing Engineers
- ☐ 3. Human Interfacing with Instruments
- ☐ 4. Computer-Aided Microwave Network and Device Characterization
- ☐ 5. Managing New Design Processes in the Changing Design Environment of the 80s
- ☐ 6. CMOS Fulltime Designer's Requirements for Low Power A/D Conversion
- ☐ 7. Display Devices and Systems
- ☐ 8. Radar Systems and Techniques
- ☐ 9. The Gate Array Approach to Circuit Design
- ☐ 10. Linear in the '80s
- ☐ 11. Speech Recognition, Generation and Synthesis
- ☐ 12. Applications of, and Design Requirements for, EMV/RFI Test Equipment
- ☐ 13. IC Solutions for Data Communications Applications
- ☐ 14. Master/Slave Distributed Processing Systems
- ☐ 15. Biomedical Engineering
- ☐ 16. Manufacturing Offshore in the 1980s
- ☐ 17. Token Access Protocols
- ☐ 18. New Microcomputer Numerics Solutions
- ☐ 19. Integrated Sensors
- ☐ 20. Quality Circles: Myth or Milestones?
- ☐ 21. CSM/ACD Protocols
- ☐ 22. Emerging Architectures for Digital Signal Processing
- ☐ 23. Progress in Robotics and Automated Manufacturing
- ☐ 24. Environmental Risk Assessment For the Hazards of Electrical Energy
- ☐ 25. Programming Single-Chip Microcomputers
- ☐ 26. Redundancy Considerations in High Density Memory Devices
- ☐ 27. Component Considerations for Low-Cost Fiber Optics Links
- ☐ 28. The Use of Fans and Blowers in Electronics
- ☐ 29. More Single-Chip Microcomputer Advancements
- ☐ 30. New Non-Volatile Memory Features
- ☐ 31. New Desktop Computers Invite Expansion, Engineering Development and Innovation
- ☐ 32. Object Oriented Systems and Languages
- ☐ 33. CMOS Microprocessor Systems
- ☐ 34. LBI Memory Controllers: System Design Trends and Architectures

TOTAL Session Records @ \$5 ea. = \$

(in USA) - Plus \$2 Mailing Charge = \$ 2.00

(Outside USA) - Plus \$4 Mailing Charge = \$ 4.00

Total Cost = \$

Make check payable to *Electro* and mail with this form to:

Electro
P.O. Box 92275
Los Angeles, CA 90009

Date


Name

Firm

Street Address

City, State, Zip Code

SOME THINGS YOU LEARN TO DEPEND ON

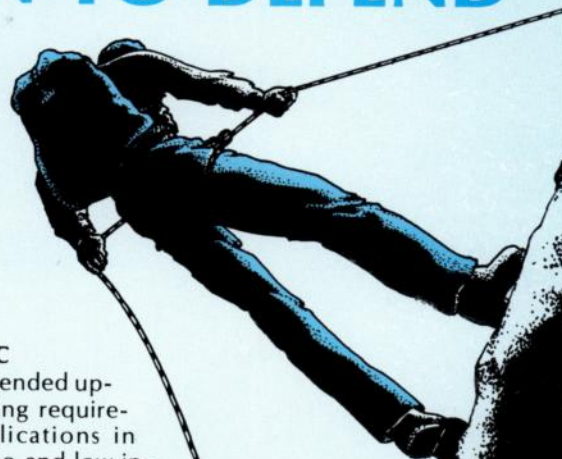

SUMMIT ELECTRONIC

SWITCHES can be depended upon to meet the exacting requirements of those applications in which high on-off ratio and low insertion loss are necessary. Insertion losses of 2 db, on-off ratios of 100 db, and switching signal isolation in excess of 60 db are typical of the performance of Summit switches. Models are available to cover frequencies up to 700 MHz, with switching speeds of 2 nanoseconds.

PCB 8-LEAD METAL CASE

relay can header, .4" x .8" hermetically sealed package, .5 MHz to 700 MHz.

PCB 6-LEAD METAL CASE

designed for the replacement market, .5" x 1.0" hermetically sealed package, .5 MHz to 400 MHz.

PCB 6-LEAD PLASTIC CASE

economy model, .5" x 1.0" package, .5 MHz to 500 MHz.

COAXIAL 1300 SERIES

BNC or SMA connectors, .5 MHz to 500 MHz, isolation to 100 db.

SPST and SPDT MODELS available in all series.

SUMMIT RF COMPONENTS set industry standards for switches, mixers, matched diodes and assemblies, frequency doublers, transformers, and hybrids. Fully warranted for two years.

YOU CAN DEPEND ON

SUMMIT RF COMPONENTS



SUMMIT ENGINEERING

P O Box 1906
Bozeman MT 59715
Phone (406) 587 4511
TWX (910) 975 1950



INFO/CARD 19

MEMORY PHONE™ III

The telephone
that's an
automatic
dialer, too.

Reliable Electronic Components. Micro-processor chip design for dependable, trouble-free performance.

Battery Backup supplies power in the event of electrical failure or if you move Memory Phone III to another location. No need to reprogram numbers.

Memory Phone™ III combines a compact telephone with an automatic dialer. Stores up to 24 phone numbers. Saves monthly phone rental charges.

Dial Mode Switch. Memory Phone III gives you push-button convenience with either rotary or tone dialing system.

Last-number-dialed Memory. One-button redial of a busy phone number.

13-24 Button. Use to program or retrieve stored numbers 13-24.

LED Hold Indicator. Lights when the Hold button is engaged.

Wall Mountable. Keeps Memory Phone III out of the way and convenient.

Magic Touch™ Dialing Pad. Push-button convenience for dialing, programming, and recalling numbers.

Save Button. Press and store any number for later retrieval.

Hold Button disconnects mouthpiece mike so caller can't hear you. Gives you privacy without covering mouthpiece with your hand.

On/Off Switch. To hang up, just place Memory Phone III face down on any flat surface.

Line Powered. Coiled cord plugs directly into any phone outlet. No additional cords or power packs necessary.

Dial Button. Press to retrieve and automatically dial stored numbers.

Electronic Tone Ringer. Pleasant sounding.

To order, please send check or money order for \$79.95 to:
Mountain Region Associates
3560 S. Lincoln
Englewood, CO 80110

Name _____

Address _____

City, State, Zip _____

Colorado Residents add sales tax.

features a recessed-gate structure and is available in both chip and package form. Typical performance of the ALF 3000 chip is 0.9 dB noise figure, 13.5 dB associated gain at 4.0 GHz, and 1.5 dB noise figure, 11.0 dB associated gain at 8.0 GHz. This low noise figure and high gain combination, coupled with a device geometry that facilitates bonding, makes the ALF 3000 series an obvious choice for all oscillator and LNA applications.

The price is \$62.50 each in quantities of 100 and availability is from stock. For further information contact Alpha Industries, Inc., 20 Sylvan Road, Woburn, MA 01801, (617) 935-5150, TWX: 710-393-1236, Telex: 949436. INFO/CARD #128.

Synthesized Signal Generator

Eaton Corporation's Electronic Instrumentation Division has introduced the AILTECH model 384, an advanced direct synthesized signal generator capable of providing signals to 4 GHz. The instrument features fast switching — 25 μ s across its entire range of 1 MHz to 4 GHz.

The 384 is the latest in the AILTECH 360/380 family of signal generators. A microprocessor controlled frequency synthesized instrument, it features keyboard entry and IEEE Standard 488 interface BUS.

The unit has a wide range of laboratory and field applications for frequency agile systems including production ATE, EW target simulators, secure communications systems and avionics ground support consoles.

Contact Eaton Corporation, Electronic Instrumentation Division, 2070 Fifth Avenue, Ronkonkoma, NY 11779. (516) 588-3600. INFO/CARD #129.

Modulation Meter

Boonton's new 8210 Modulation Meter is the first low-cost instrument that automatically calibrates both AM and FM channels each time power is applied. As a result of this self-calibration, AM accuracy is one percent of reading, from 10 percent to 90 percent AM, for carrier frequencies from 2 MHz to 520 MHz and modulation frequencies of 50 Hz to 5 kHz. FM accuracy is also one percent of reading for deviations up to 150 kHz, carrier frequencies of 2 MHz to 1.5 GHz, and modulation rates of 50 Hz to 5 kHz. Modulation frequencies from 30 Hz to 15 kHz are accepted on both AM and FM channels with degraded accuracy.

Tuning and leveling are fully automatic with the 8210. The instrument acquires the largest signal present at




the input connector and adjusts its local oscillator and measurement channel gain to indicate the fully calibrated AM or FM on a 3-1/2 digit display. Selectable 3 kHz and 15 kHz loss-pass filters are standard, as is a 750 μ s de-emphasis switch. Residual FM of less than 150 Hz at 1.5 GHz, decreasing linearly to a floor of less than 5 Hz with 3 kHz bandwidth, and residual AM of less than 0.15 percent AM allow the measurement of unmodulated carriers. FM rejection is less than one percent AM at 100 kHz peak deviation; AM rejection is less than 100 Hz deviation at 50 percent AM.

The meter is priced at \$1,795 with 90 day delivery. Contact Scott Elkins, VP Marketing, Boonton Electronics Corp., P.O. Box 122, Parsippany, NJ 07054. (201) 887-5110. INFO/CARD #126.

Compact 150 Watt Amplifier

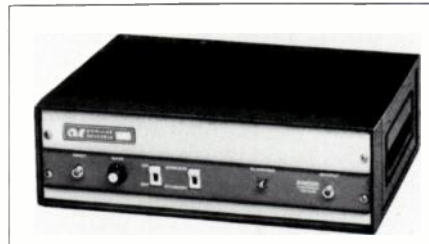Considerably smaller and lighter than other RF amplifiers in its class, the new model 150LA from Amplifier Research is rated at 150 Watts minimum power, 1-110 MHz (60 watts minimum to 150 MHz). It will continue





to operate regardless of the magnitude or phase of source and load impedances, without oscillation, shutdown, or damage.

Model 150LA combines solid-state low power stages with a vacuum tube final amplifier, providing instantaneous bandwidth (full power at any frequency in its operating spectrum, without tuning or bandswitching) and exceptional pulse and blanking characteristics. A typical RF envelope exhibits pulse droop of less than one percent.

At only 23 kg (50 lb), the new unit measures 50 cm wide, 16 cm high, and 45 cm deep (19.8" x 6.3" x 18.0") and is priced at \$4,900. Contact Amplifier Research, 160 School House Road, Souderton, PA 18964. (215) 723-8181. TWX: 510-661-6094. INFO/CARD #125.

Low Noise Crystal Oscillators

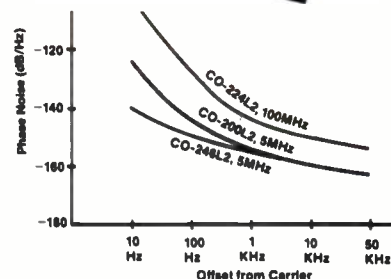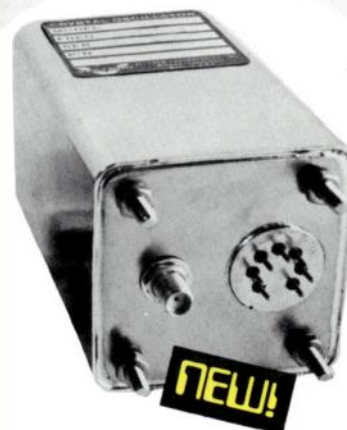

HF MODELS

Series:	CO-200L2	CO-246L2
Frequency:	4-25 MHz	5 MHz (opt. to 100 MHz)
Aging:	1x10 ⁻⁹ /day 3x10 ⁻⁷ /year	1x10 ⁻¹⁰ /day 3x10 ⁻⁸ /year
Phase noise:	at 5 MHz	
@ 100 Hz:	-145 dB/Hz	-150 dB/Hz
@ 1 KHz:	-155 dB/Hz	-155 dB/Hz
@ 50 KHz:	-163 dB/Hz	-163 dB/Hz

VHF MODELS

Series:	CO-224L2	CO-220L2
Frequency:	25-300 MHz	25-125 MHz
Aging:	1x10 ⁻⁸ /day 2x10 ⁻⁶ /year	1x10 ⁻⁹ /day 3x10 ⁻⁷ /year
Phase noise:	at 100 MHz	
@ 100 Hz:	-130 dB/Hz	-120 dB/Hz
@ 1 KHz:	-145 dB/Hz	-130 dB/Hz
@ 50 KHz:	-155 dB/Hz	-140 dB/Hz

Write, phone or TWX today for complete details...

From the world's largest and most respected full line manufacturer of crystal oscillators...



VECTRON LABORATORIES, INC.
The Crystal Oscillator Company
166 Glover Avenue, Norwalk, Connecticut 06850
Telephone: 203/853-4433 TWX: 710/468-3796

Advertiser Index

Andersen Laboratories, Inc	51
California Eastern Labs	6-7
Communitronics, Ltd.	23
Daico Industries, Inc	19
Electroline	11
Electronic Conventions, Inc	29, 47
Helper Instruments	42
Hewlett Packard Co	3
Johanson Mfg. Corp.	25
E.F. Johnson Co	25
Lindgren RF Enclosures	42
McCoy Electronics	46
M/A-COM Silicon Products, Inc	2
Mini-Circuits	5, 52
Mountain Region Assoc	48
Programmed Test Sources, Inc	41
Summit Engineering/ Dana Industrial	47
Teledyne Crystalonics	30
Vectron Laboratories	49
Watkins-Johnson	45
Wavetek Indiana, Inc	17
Wide Band Engineering	30

SECTION MANAGER R.F. PRODUCTS

Lead a creative group of R.F. Design Engineers through the development of a new line of innovative Broadcast Products. This position requires a strong background in the design of AM and FM transmitting equipment along with proven skills in project management. B.S.E.E. or M.S.E.E. with at least 3-5 years of R.F. Design experience and some supervisory skills are desired. This position is an excellent opportunity for a successful project engineer to move into engineering management.

The Company

Broadcast Electronics is known for high quality broadcast audio, automated programming, and FM transmitting equipment.

We are located on the Mississippi river in a friendly, medium sized community with good schools, recreational opportunities, and pleasant life style.

We have an excellent benefit package including group insurance and profit sharing. Our facilities are consolidated into a single modern 70,000 square foot plant. The working environment is informal, friendly, and individually oriented with excellent opportunity for advancement.

For additional information call or send resume in complete confidence to: Vice President, Engineering.



a PUBLERT company

BROADCAST ELECTRONICS INC.

4100 N. 24th ST., P.O. BOX 3606
QUINCY, IL 62305, (217)224-9800, TELEX: 25-0142

Programmable Broadband Solid State Noise Generators

Replacing conventional sweep generators, Micronetics' model PNG 5100 through 5110 series of Noise Generators feature full noise source capability from 10 Hz to 1 GHz in a compact instrument or rack-mounted panel, only seven inches high. Output is greater than +10 dBm (10 mW) across the given frequency range.

IEEE-488 Interface Bus Remote Programming includes on and off standby, external pulse and attenuation control, as well as local and remote capability.

Standard frequency bands are: 10 Hz-20 kHz, 10 Hz-100 kHz, 10 Hz-500 kHz, 100 Hz-3 MHz, 100 Hz-10 MHz, 100 Hz-25 MHz, 100 Hz-100 MHz, 1 MHz-200 MHz, 1 MHz-500 MHz, 10 MHz-1 GHz.



Optional frequency bands are available up to 40 GHz.

For complete details on these new Programmable Solid State Noise Sources, contact Micronetics, Inc., 36 Oak Street, Norwood, NJ 07648. (201) 767-1320. TWX: 710-991-9603. INFO/CARD #123.

Manual A-B Data Switch For Coax, Twinax Introduced

A manual A-B Coax or Twinax switch with several housing and connector options, for switching between two data, video or digital sources, has been announced by MarLee Switch Company.

The single pole, double throw switch, model 981, covers the DC to 100 MHz frequency range. Isolation is better than -100 dB, insertion loss less than 1/2 dB. Characteristic impedances are 50 or 75 ohms, with other impedances and terminated versions available. The unit can allow, for instance, manual switching of two CRT terminals to one controller, or, switching of one display between two controllers.

The model 981-0001 desk model Coax A-B manual switch is \$140.00 in single piece quantity. Delivery is typically 60 days after receipt of order. Normal quantity discounts are offered.

MarLee Switch Company, 933-D North Central Ave., Upland, CA 91786, designs and manufactures switches, matrices, controls and displays for RF, video, data and audio switching and interconnecting. INFO/CARD #124.

New Literature

Inductive Components Catalog

CAMBION, a leading manufacturer and supplier of components to the electronics industry, has just published its *Inductive Components Catalog 111*. This new and completely updated 34-page catalog features comprehensive listings of Cambion's Variable Coils (shielded and unshielded), RF Chokes (including military types), Coil Forms (both PC board and panel mount), Micro-inductors (see section below), Testing Fixtures, and selected Capacitors.

The new Catalog 111 contains full documentation for all Inductive Components with accompanying dimensioned line drawings and tabulated specifications. Also included in this compact, information-filled 34-page engineering design literature is a "tear-out" MIL Standard/Cambion RF Choke Cross Reference for convenient wall-mounting or other fast reference. And, the new catalog contains an Index by part sequence to simplify ordering, plus a Table of Contents for easy reader reference.

Response to the new Catalog 111 offering is expected to be very high so Cambion anticipates 4-6 weeks delivery of this useful data after receipt of request. Letterhead inquiries will receive more prompt attention, and all requests should be directed to Cambion Customer Service at 445 Concord Avenue, Cambridge, MA 02238. (617) 491-5400. Telex: 92-1480. TWX: (710) 320-6399. INFO/CARD #118.

Ceramic Disc Capacitor Brochure

The Passive Components Division of Thomson-CSF Components is offering free a new eight-page, two-color brochure on its ceramic disc capacitor line.

The brochure describes the three types of ceramic disc capacitors presently available from Thomson-CSF: temperature compensating, general purpose, and barrier layer capacitors. For each of these three types, the brochure provides full technical data including capacitance ranges, technical characteristics, and performance graphs. In addition, details of capacitor markings and coatings, and full ordering information is included.

Contact Thomson-CSF Components Corp., 6660 Variel Avenue, Canoga Park, CA 91303. (213) 887-1010. Please circle INFO/CARD #113. □




Our SAW Filters give you less for your money.

Less cost.

Today, Andersen SAW filters are priced competitively with other filter technologies. We have hundreds of standard designs suitable for thousands of applications. So you save on design charges. And if you need something tailor-made, our fast, computerized design capabilities and large production volume can reduce your costs far below what you'd expect.

Less bulk.

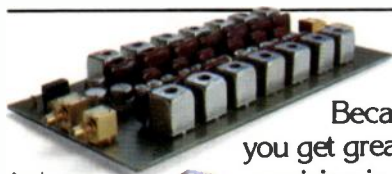

Andersen SAW filter vs. equivalent LC network.


Because you get greater precision in a smaller package.

See for yourself how Andersen SAW filters stack up in size against LC filters.

Less tuning.

Because there's nothing to tune. Our filters are passive analog solid-state devices. They have

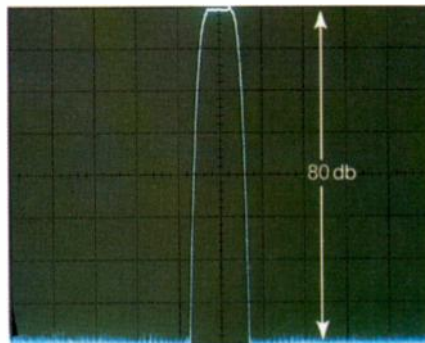permanently fixed performance characteristics. Once that design is checked by our computers, it never has to be checked again. Unlike LC filters, our SAW filters need no tuning, assembly, checking, retuning, and rechecking. So you save time, labor and capital equipment costs.



Typical frequency response of Andersen BPP70-1300-3-133A of 1.5MHz bandwidth.

Less maintenance.

Because there's nothing that can ever get out of tune. Our SAW filters not only cost less than you'd think to begin with. They won't nickel and dime you to death after you buy them.

Less rejects.

Because SAW filters of the same design are virtually identical. That helps you produce a more consistent end product. And our proven designs assure top performance. You get a superior shape factor. Improved close-in rejection. Inherent linear phase. And less distortion than with conventional filter designs.

Less confusion.

Because if there's one thing we give you more of, it's information. Volume I of our Handbook of Acoustical Signal Processing will tell you everything you need to know about the right SAW filter for your application. Plus, for a limited time, the Handbook is free. So send for your copy now.



Andersen SAW filters. We think you'll agree they're everything you've always wanted in a filter.



ANDERSEN LABORATORIES

Andersen Laboratories, Inc., 1280 Blue Hills Avenue, Bloomfield, CT 06002 Telephone (203) 242-0761 TWX: 710-425-2390


Andersen SAW products are available in the United Kingdom and Europe through our sister company, Signal Technology Ltd., Swindon, Wiltshire, UK.

INFO/CARD 1



RF transformers

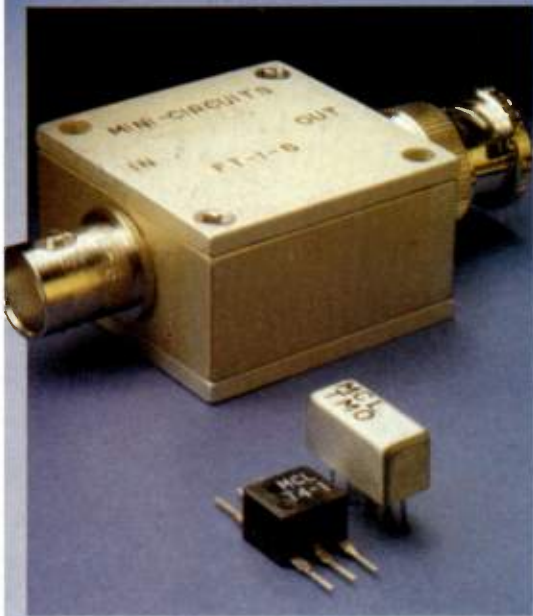the world's widest selection of matching ratios
10KHz-800MHz... balanced, DC isolated, center-tapped
 46 off-the-shelf models from Mini-Circuits from \$2.95



Select from the economical, microminiature T-series (plastic case) or TMO series (hermetically-sealed metal case) covering 10 KHz to 800 MHz. These models operate from 12.5 to 800 ohms with insertion loss typically less than 0.5 dB.

For large dynamic range applications, specify the T-H series which can handle up to 100 mA primary current without saturation or distortion.

Need a connector version? Select from the FT or FTB series, available with unbalanced or balanced outputs. Connector choices are female (BNC, Isolated BNC, and Type N) and male (BNC and Type N). These units operate from 10 KHz to 500 MHz with impedances of 50 and 75 ohms.

Of course, Mini-Circuits' one-year guarantee is included.

DC ISOLATED PRIMARY & SECONDARY



	T1-1	T1-1H	T1.5-1	T2.5-6	T4-6	T9-1	T9-1H	T16-1	T16-1H
Model No.	TMO1-1		TMO1.5-1	TMO2.5-6	TMO4-6	TMO9-1		TMO16-1	
Imped. Ratio	1	1	1.5	2.5	4	9	9	16	16
Freq. (MHz)	15-400	8-300	1-300	0.1-100	0.2-200	15-200	2-90	3-120	7-85
T Model (10-49)	\$2.95	\$4.95	\$3.95	\$3.95	\$3.95	\$3.45	\$5.45	\$3.95	\$5.95
TMO model (10-49)	\$4.95		\$6.75	\$6.45	\$6.45	\$6.45		\$6.45	

CENTER-TAPPED DC ISOLATED PRIMARY & SECONDARY




	T1-1T	T2-1T	T2.5-6T	T3-1T	T4-1	T4-1H	T5-1T	T13-1T
Model No.	TMO1-1T	TMO2-1T	TMO2.5-6T	TMO3-1T	TMO4-1		TMO5-1T	TMO13-1T
Imped. Ratio	1	2	2.5	3	4	4	5	13
Freq. (MHz)	0.5-200	0.7-200	0.1-100	0.5-250	2-350	8-350	3-300	3-120
T Model (10-49)	\$3.95	\$4.25	\$4.25	\$3.95	\$2.95	\$4.95	\$4.25	\$4.25
TMO model (10-49)	\$6.45	\$6.75	\$6.75	\$6.45	\$4.95		\$6.75	\$6.75

UNBALANCED PRIMARY & SECONDARY



	T2-1	T3-1	T4-2	T8-1	T14-1
Model No.	TMO2-1	TMO3-1	TMO4-2	TMO8-1	TMO14-1
Imped. Ratio	2	3	4	8	14
Freq. (MHz)	0.25-600	5-800	2-600	15-250	2-150
T model (10-49)	\$3.45	\$4.25	\$3.45	\$3.45	\$4.25
TMO Model (10-49)	\$5.95	\$6.95	\$5.95	\$5.95	\$6.75

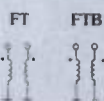

	FT1.5-1	FTB1-1	FTB1-6	FTB1-1-75
Model No.				
Imped. Ratio	1.5	1	1	1
Freq. (MHz)	1-400	2-500	0.1-200	5-500
(1-4)	\$29.95	\$29.95	\$29.95	\$29.95

Mini-Circuits

A Division of Scientific Components Corp.

World's largest manufacturer of Double Balanced Mixers

2625 East 14th Street, Brooklyn, New York 11235 (212)769-0200

Domestic and International Telex 125460 International Telex 620156