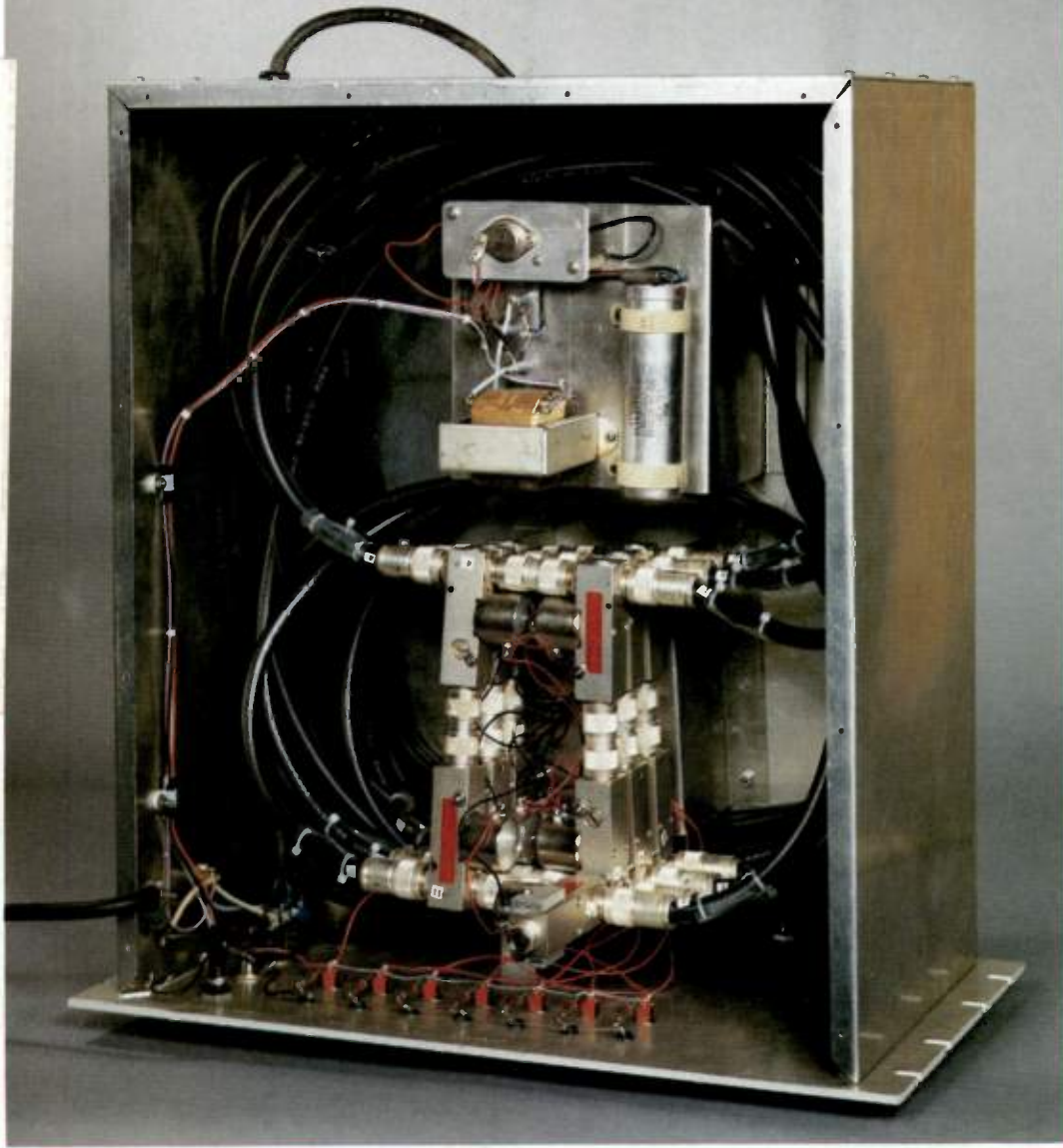





VICTA800S02 RF1101902MCJA0091
ALAN M VICTOR/STF SAJ/AI782608106
MOTOROLA COMM DIV ENG
8000 W SUNRISE RM 2332
SUNRISE FL 32322



**PCB Crosstalk • EMI Filters
Binary Stepped Transmission Line
Bandpass Filter Design
Triple Tuned Circuits**

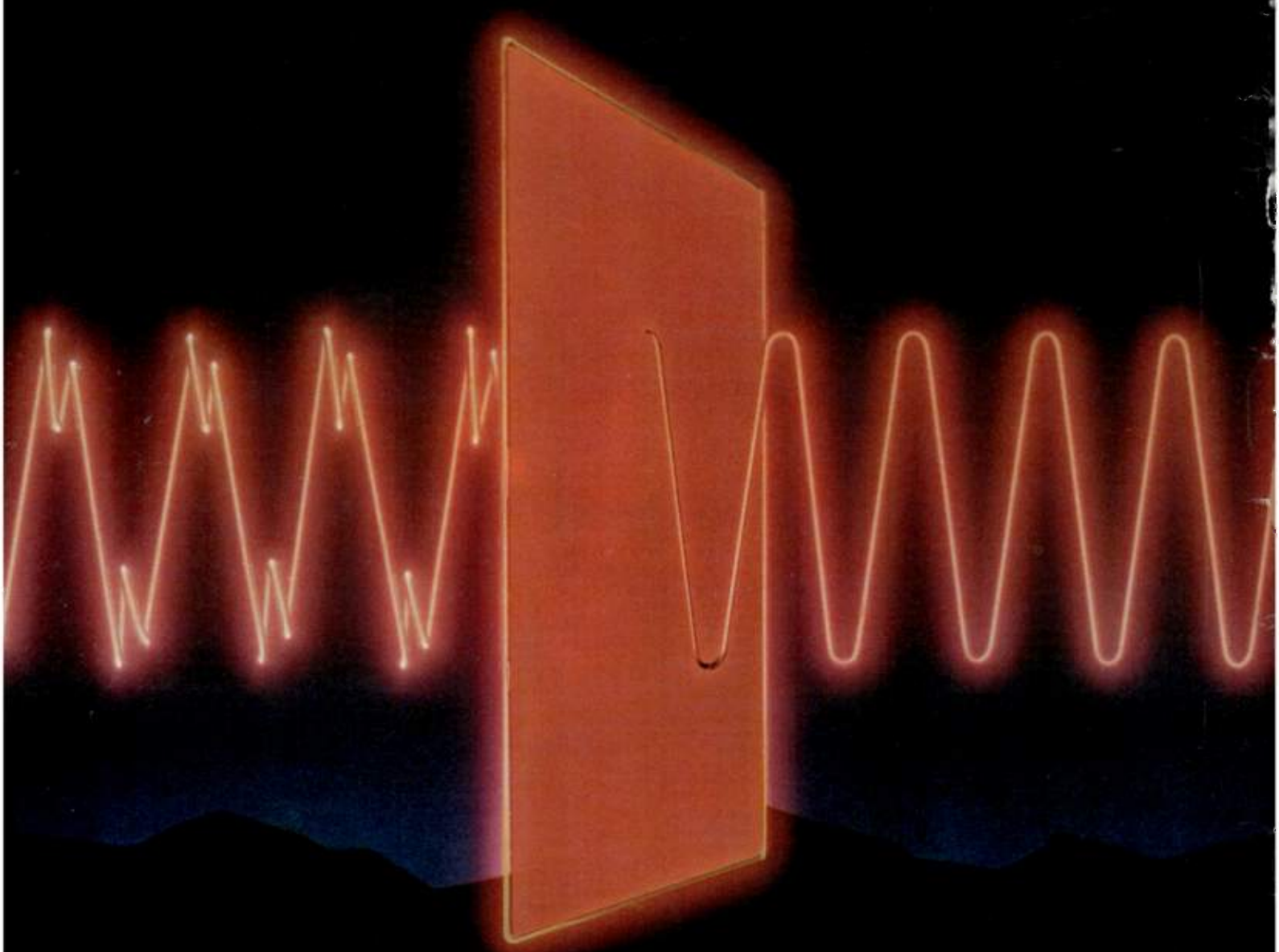DWCI. STILL THE BEST AGAINST INTERFERENCE.



We're swimming in a sea of EMI. No way to escape it.
You design around it. Beat it before it beats you. Or retrofit
to solve interference problems in existing designs. That takes special skills.
Skills they didn't teach you back in school.

DWCI teaches Electromagnetic Compatibility courses all over the world.
Offers computer programs, handbooks, and engineering/consulting services
anywhere in the world.

DWCI is the benchmark for the fast-growing EMC industry. We were
the first; we're still the best. Practical, hands-on experience sets us apart
from Ivory-tower theorists.

If it's electronic, DWCI knows how to protect it from electromagnetic
interference. Check us out. Write or call today for our free catalog.

INFO/CARD 31

DWCI

DON WHITE CONSULTANTS INC.

The Interference Control Experts.

P.O. Box D, Gainesville, Virginia 22065
703/347-0030

**TECKNIT
solves the
toughest design
and packaging EMI
noise problems.**

**EFFECTIVELY.
ECONOMICALLY.**

#1 in EMI Shielding

- Knitted Wire Mesh • Oriented Wire Gaskets • Conductive Elastomers
- Shielding Optical Windows • Shielding Air-Vent Panels
- Conductive Adhesives and Sealants • Switch and Connector Seals


Write or Call for
the TECKNIT Data Guide
or
to discuss an
EMI shielding problem.




TECKNIT®

EMI Shielding Products
129 Dermody Street, Cranford, NJ 07016
(201) 272-5500

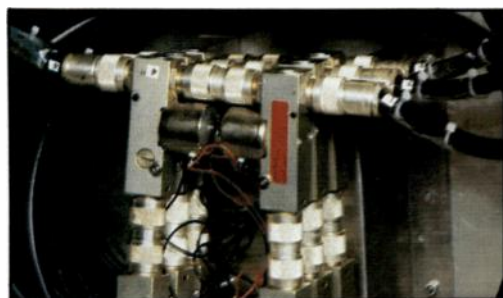
TWX (710) 996-5951
TELEX 685 3079TCKNT
INFO/CARD 2



Binary Stepped

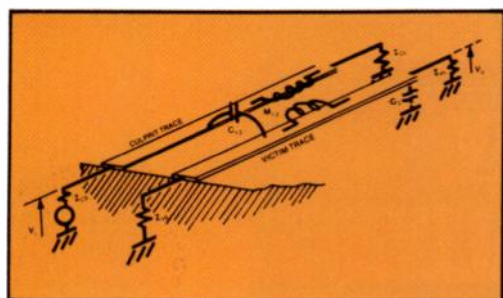

Prediction & Control

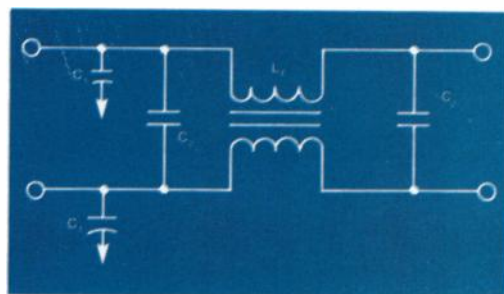

Insertion Loss Testing

July/August Cover—The cover photo is a device to simplify the testing of high frequency linear power amplifiers. This photo shows the implementation of the design described in the article "A Binary Stepped Transmission Line".

1

Prediction and Control of Crosstalk in Printed Circuit Boards—A discussion of crosstalk as it relates to printed circuit boards. Clarification on the parameters that influence crosstalk, plus layout rules to reduce its effects without adding appreciable cost.

12

Insertion Loss Testing of Common Core Filters—Described in this article is a discussion of the testing specifications for EMI filters.

20

A Binary Stepped Transmission Line—Details for designing a means of rapidly changing load impedances for power amplifier testing.

22

Bandpass Filters with Self-Equalized Group Delay: Part II—The second part of a comprehensive article dealing with the design of bandpass filters. Part II continues the theoretical discussion and gives an example filter design.

30

Triple Tuned Circuits—Previous articles described double tuned coupling circuits; now a wide band triple tuned coupling circuit offering.

36

Editorial	6	INFO/CARD	44
Subscription Card	9	Classifieds	50
Products	38	Advertiser Index	50



tough attenuators

from **\$11.95**
(1-49)

the world's lowest-priced coax attenuators
3, 6, 10 or 20 dB... from DC to 1500 MHz
one-piece design defies rough handling

Check these features:

- ✓ Solid one-piece tubular construction
- ✓ Available with BNC, N, SMA, TNC connectors
- ✓ Male/female connectors standard
- ✓ Connector series intermixing available
- ✓ 2 watts max. power (except 0.5W for SMA)
- ✓ Excellent temperature stability, .002 dB/°C
- ✓ Low-cost, only \$11.95 BNC (1-49 qty.)
attenuation values may be combined
- ✓ Delivery, from stock
- ✓ Exclusive one-year guarantee

Model	Attenuation, dB	Attenuation Tolerance	Frequency MHz	Attention Change over Frequency Range, MHz		VSWR Max. (50 ohms)	
				DC-1000	1000-1500	DC-1000	1000-1500
—AT—3	3	± 0.2dB	DC-1500	0.6dB	1.0dB	1.3:1	1.5:1
—AT—6	6	± 0.3dB	DC-1500	0.6dB	0.8dB	1.3:1	1.5:1
—AT—10	10	± 0.3dB	DC-1500	0.6dB	0.8dB	1.3:1	1.5:1
—AT—20	20	± 0.3dB	DC-1500	0.6dB	0.8dB	1.3:1	1.5:1

— Add prefix **C** for BNC (\$11.95), **T** for TNC (\$12.95),
N for Type N (\$15.95), **S** for SMA (\$14.95)

finding new ways...
setting higher standards

 **Mini-Circuits**

A Division of Scientific Components Corporation
World's largest manufacturer of Double Balanced Mixers
2625 East 14th Street, Brooklyn, New York 11235 (212)769-0200
Domestic and International Telex 125460 International Telex 620156

"For Mini Circuits sales and distributors listing see page 93."

Publisher
Bill W. Childs

Editor
Larry Brewster

Consulting Editor
E. Patrick Wiesner

Sales Manager
Ruth Breashears

Account Executives
Blair S. Meador
Suzan Myers
Dianne Oveson

Editorial Review Board
Alex Burwasser
Rob Coe
Doug DeMaw
Hank Keen
Dave Krauthheimer
Ed Oxner
Andy Przedpelski
Jeff Schoenwald
Raymond Sicotte

Advertising Services
Betsy Loeff

Production Manager
Dara Hinshaw

Group Art Director
Mike Morris

Artist
Tim Gabor

Composition
Melody Benner
Sandy Bennett

Published by



Cardiff Publishing Company
Subsidiary of Cardiff Communications, Inc.
6430 S. Yosemite St.
Englewood, Colo. 80111
(303) 694-1522

For subscription inquiries please contact
Cardiff Publishing Circulation Service
Center, P.O. Box 1077, Skokie, IL 60077

Chairman
Stanley M. Searle

President
Robert A. Searle

Treasurer
Patrick T. Pogue

Vice President
Phil D. Cook

Circulation Manager
Chris Woodbury



EMC/EMI

This issue is focused on a subject which is on the minds of much of the electronics industry at the present time: EMC/EMI. There seems to be concern over the requirements, new regulations, and the best methods for compliance. We attempt to answer a few of these questions in this issue.

Also in this issue, we are kicking off a contest to help our advertisers determine which advertisements are best remembered. For you, it is a chance to end up with a \$1,000 savings bond. So look for more details on page 42.

In the next few weeks we will be setting the direction for issues of next year. This publication strives to bring you the types of articles you want to see. It is very important that we get feedback as to the type of material you want to read. Let me know what subjects you are interested in so you can get the information you need.

Readers write most of the articles published in *R.F. Design*. Think about it for yourself. It is good for your career, prestige and recognition to place articles in trade magazines such as ours. It is good for your company to have your articles published. If you have an idea for an article, please contact me to supply whatever help is necessary to bring into print the information you want to convey to other designers.

Larry Brewster
Editor



GILBERT ENGINEERING

ANNOUNCES



G900™



G874™

Gilbert Engineering has acquired the GenRad (General Radio) product line of R.F. coaxial connectors, attenuators, adaptors, terminations and cable assemblies. Gilbert, a manufacturer of coaxial connectors will now produce the GR874 and GR900 series connectors.

For pricing and delivery, please write or call:

**GILBERT
ENGINEERING**

P.O. Box 23189, Phoenix, Arizona 85063-3189
5310 West Camelback, Glendale, Arizona 85301-7597
(602) 245-1050 • (800) 528-5567 • TWX 910-951-1380



Join the premier tactical missile team

Let your talents reach into the 21st Century

You will earn lasting rewards if you can help Hughes meet the challenges of AMRAAM, Maverick, Tank Breaker, Wasp, Phoenix, and TOW.

These long-term programs have created genuine career opportunities for ambitious individuals with BS or higher degrees in Electrical Engineering and experience in these areas of Microwave Engineering:

Stripline & Microwave Integrated Circuit Design — Experience in active or passive microwave circuit design using stripline and microstrip transmission lines. Requires expertise in L-, X-, and Ka-band mixer, amplifier and multiplier design, microwave noise characterization and measurement, and use of CAD software.

Radome Analysis & Design — Knowledge of electromagnetic theory. Experience in design or analysis of narrowband and broadband radomes for transmitting and receiving microwave and millimeter-wave signals. Competent in radome error-slope calculations, corrections, and contour synthesis.

Antenna Analysis & Design — Experience in narrowband and multi-octave antenna design for active and anti-radiation homing radar missile applications.

High-Power Transmitter Design — Knowledge of high-power TWT or Klystron transmitters for military airborne applications. Familiarity with HV switching, modulation test, and analysis techniques plus understanding of tube characteristics.

Exciter Design—Experience in design of VCO's, multipliers, filters, PIN diode switches, bi-phase modulators, and bi-polar and FET power amplifiers. 0.1 to 10 GHz frequency bandwidth.

Millimeter-Wave Subsystem Design — Experience in design of millimeter-wave components, preferably for Ka- and W-band applications.

IF & RF Circuit Design — Experience with phase-locked loops, crystal oscillators, and receivers, preferably in military applications. Worst-case circuit analysis highly desirable.

You'll work at our campus-like R&D facility in Southern California's San Fernando Valley, as part of a company with 1,500 varied projects in progress.

Hughes salaries are highly competitive. Benefits are outstanding. California climate and unmatched recreation will be yours all year round.

For prompt and confidential consideration, please mail your resume to: Hughes Missile Systems, Engineering Employment, Dept. FR-7, Fallbrook at Roscoe, Canoga Park, CA 91304.

Creating a new world with electronics


HUGHES

HUGHES AIRCRAFT COMPANY

MISSILE SYSTEMS

Proof of U.S. Citizenship Required
Equal Opportunity Employer

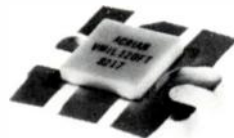
"POWER TO SUCCEED" When you need solid state RF...



Power to Communicate

120 Watts • 175 MHz ISOFET

Gain	13 dB
Efficiency	65 %
V _{DD}	28 Volts
C _{oss}	240 Pf
C _{iss}	210 Pf
C _{rss}	12 Pf
g _m	3.0 mhos
Model	VMIL 120FT

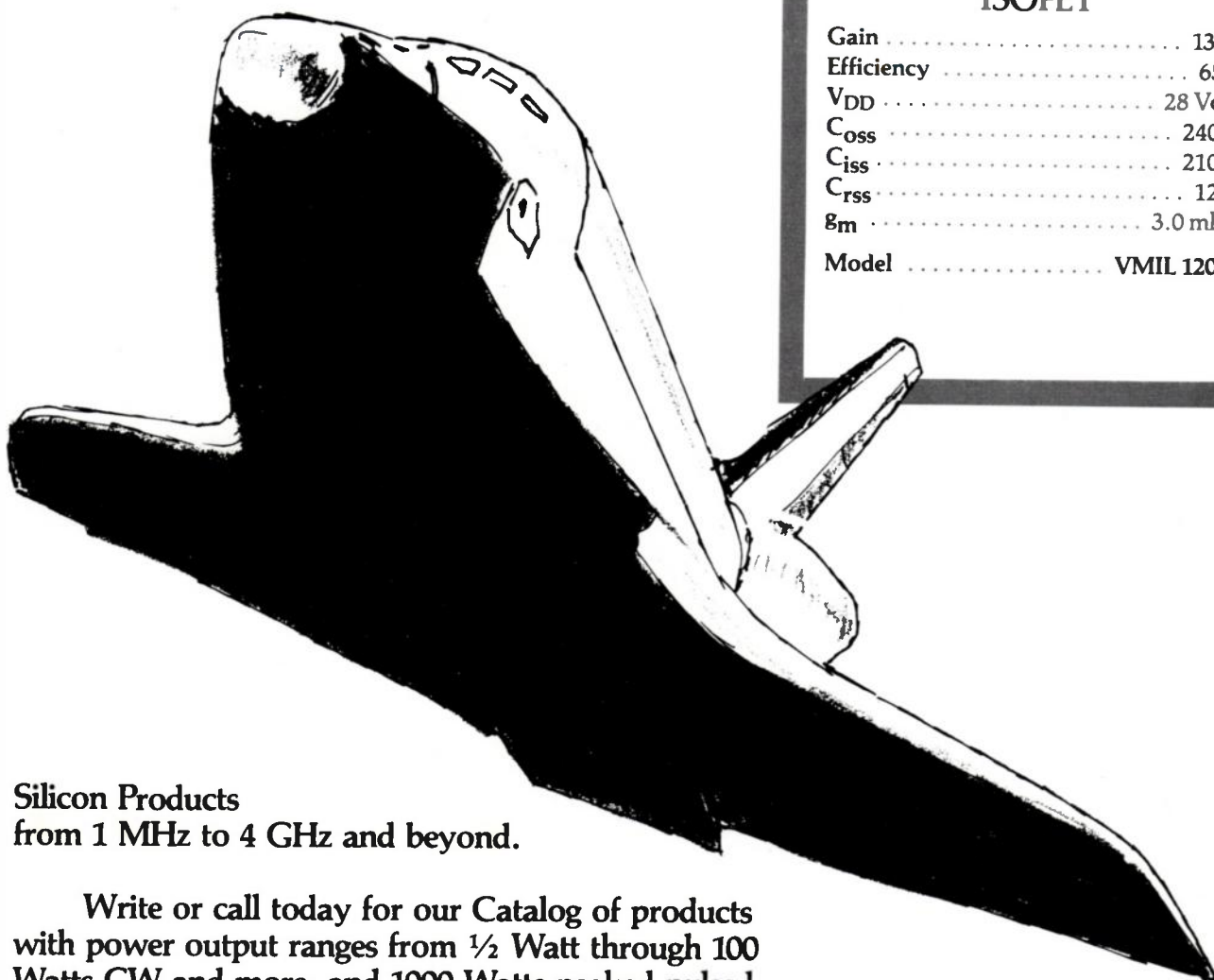

Silicon Products
from 1 MHz to 4 GHz and beyond.

Write or call today for our Catalog of products with power output ranges from 1/2 Watt through 100 Watts CW and more, and 1000 Watts peaked pulsed and more. ACRIAN, 10131 Bubb Road, Cupertino CA 95010. Or For Quick response, call (408) 996-8522; TWX (910) 338-2172.

ACRIAN

Prediction and Control of Cross

Crosstalk: A Somewhat Misused Term.

By Michel Mardiguian
Director of Training
Don White Consultants, Inc.
Gainesville, VA 22065

Inherited from telephony, where it addresses the parasitic coupling from one voice channel to an adjacent one, the term **CROSSTALK** is employed to characterize, more generally, the percentage of a signal which is coupled from a circuit #1 to a nearby circuit #2 by wire-to-wire influence. Sometimes its meaning has degenerated and, outside the EMC community, some authors use it to cover any kind of undesired noise generation within a limited area, whether it is real wire-to-wire coupling, common impedance coupling or mismatch reflections.

In this article, we will discuss the crosstalk in printed circuit boards strictly in the significance of this term, i.e., the capacitive or inductive transfer between adjacent printed traces.

A Simple Model Permits Quick but Satisfactory Approximations

At the risk of oversimplifying, the PCB crosstalk problem can be represented by Figure 1. Two circuits that we identify as *culprit* and *victim* are using parallel printed traces of some length. As long as the trace is electrically short, i.e., the trace length is $\ll \lambda/4$ of the culprit frequency or, more precisely, the *rise time* τ_r of the culprit signal is longer than the line propagation delay τ_d , the distributed trace-to-trace capacitance and mutual inductance can be replaced by a localized capacitance $C_{1,2}$ and a localized mutual inductance $M_{1,2}$.

Then it appears that the parasitic voltage V_v transferred to the victim by culprit line voltage V_c has two contributors:

- (1) The capacitive coupling
 - (2) The mutual inductance coupling
- If we define the crosstalk as being the ratio of $V_{\text{victim}}/V_{\text{culprit}}$, we have a *figure of merit of any given configuration*, i.e., *how much voltage appears on victim load per volt on the culprit line*. Since telephony and the EMC community uses the decibel extensively, the Xtalk will then be:

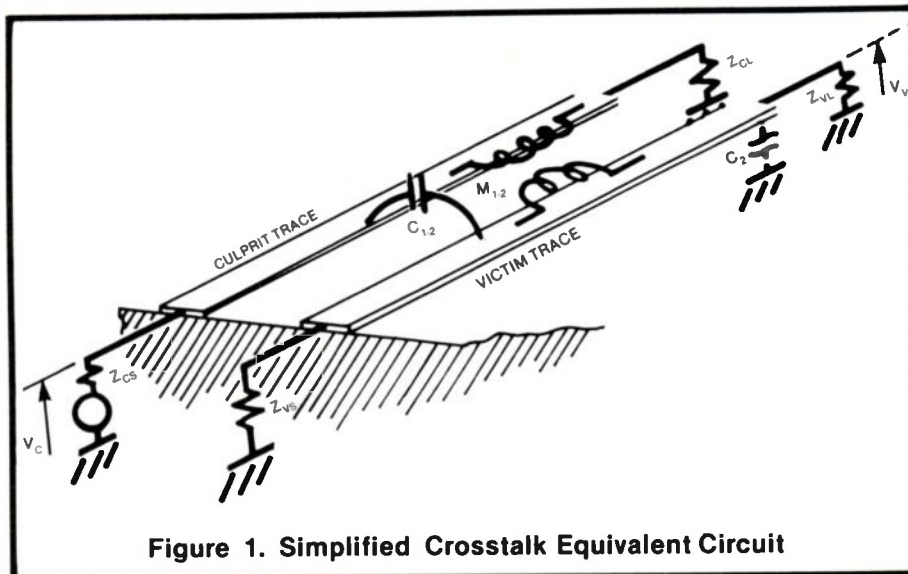


Figure 1. Simplified Crosstalk Equivalent Circuit


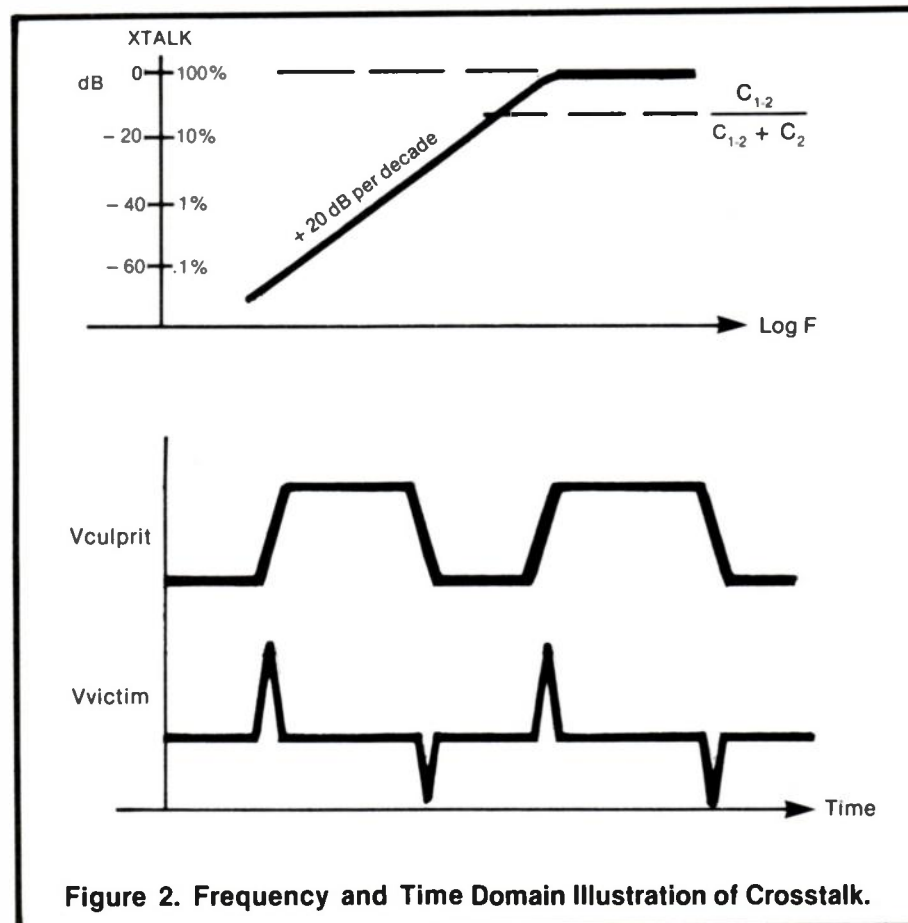


Figure 2. Frequency and Time Domain Illustration of Crosstalk.

talk in Printed Circuit Boards

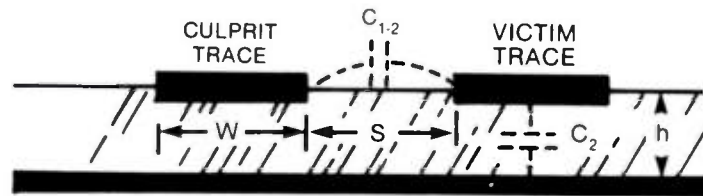

		W/h = 10 (Cvg = 3.5pF/cm)			W/h = 3 (Cvg = 1pF/cm)			W/h = 1 (Cvg = .35pF/cm)			W/h ≤ .3 or no gnd return below traces			
W/S (Ccv, pF/cm)		.3 (.10)	1 (.20)	3 (.27)	.3 (.10)	1 (.20)	3 (.27)	.3 (.10)	1 (.20)	3 (.27)	.3 (.10)	1 (.20)	3 (.27)	
FREQ.	1 kHz	-144	-138	-136	-144	-138	-136	-144	-138	-136	-144	-138	-136	Culprit Pulse Rise Time
	3kHz	-134	-128	-126	-134	-128	-126	-134	-128	-126	-134	-128	-126	
	10kHz	-124	-118	-116	-124	-118	-116	-124	-118	-116	-124	-118	-116	
	30kHz	-114	-108	-106	-114	-108	-106	-114	-108	-106	-114	-108	-106	10μs
	100kHz	-104	-98	-96	-104	-98	-96	-104	-98	-96	-104	-98	-96	3μs
	300kHz	-94	-88	-86	-94	-88	-86	-94	-88	-86	-94	-88	-86	1μs
	1MHz	-84	-78	-76	-84	-78	-76	-84	-78	-76	-84	-78	-76	300ns
	3MHz	-74	-68	-66	-74	-68	-66	-74	-68	-66	-74	-68	-66	100ns
	10MHz	-64	-58	-56	-64	-58	-56	-64	-58	-56	-64	-58	-56	30ns
	30MHz	-55	-49	-47	-54	-48	-46	-54	-48	-46	-54	-48	-46	10ns
	100MHz	-46	-40	-38	-44	-38	-36	-44	-38	-36	-44	-38	-36	3ns
	300MHz	-39	-33	-31	-36	-30	-28	-35	-30	-28	-34	-30	-26	1ns
	1GHz	-34	-28	-26	-28	-22	-20	-26	-20	-18	-24	-18	-16	.3ns
	3GHz	-32	-26	-24	-23	-17	-16	-15	-12	-11	-14	-8	-6	.1ns
	10GHz	-31	-25	-23	-21	-15	-14	-13	-10	-8	-4	0	0	.03ns

NOTES

- Epoxy glass assumed ($\epsilon_r \cong 4$)
- Xtalk given as $20 \log_{10} \frac{V_{victim}}{V_{culprit}}$ per cm of parallel run. For other lengths, add $20 \log_{10} l_{cm}$
- For $Z_{victim} \neq 100\Omega$ (10 to 300Ω), add $20 \log_{10} \frac{Z_{victim}}{100}$
- Clamp to 0dB, Xtalk cannot be positive
- Example of some typical values $W = 20$ mils (.5mm), $S = 30$ mils (.75 mm), for single layer $h = 30 - 40$ mils (.7 to 1mm), for Multilayer $h = 5$ mils (.12mm).

Figure 3. Capacitive XTalk Table for 100Ω Total Victim Impedance.

YOUR MAGNETIC SHIELDING PROBLEMS END HERE

Save tooling costs—Ad-Vance already owns tooling for most standard shields. Our problem solving magnetic shielding specialists will adapt or custom design exactly what you need.


- Magnetic shields for 324 types of PM tubes
- AD-MU sheet stock
- AD-MU protective cases assure full fidelity of valuable taped data
- Helpful engineering & design service
- Painsaking in-house quality control.

Now—4 decades of magnetic shielding leadership. Your magnetic shielding problems end here at Ad-Vance.



Completely modern mfg. facilities

AD-MU foils cut, wrap easily, quickly

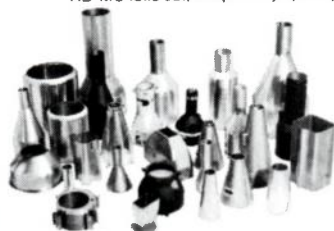

Typical fabricated shields for components and systems



Gives major designing/procuring guidelines. 2/3 of 64-page book contains valuable technical/engineering information about the entire magnetic shielding field; 1/3 is catalog data. Yours for the asking

AD-VANCE MAGNETICS, INC.

AD-Vance Shielding: The "Nickel's" Worth
625 Monroe Street, Rochester, Indiana 46975
(219) 223-3158 TWX 810-290-0294

INFO/CARD 7

★ATTENTION★



Your QPL Source For MIL-C-85049 Connector Accessories Is Glenair.

Glenair is now a qualified source for over three dozen MIL-C-85049 connector backshells. This new document includes backshells previously contained within the following connector specifications:
MIL-C-26482 Series II
MIL-C-38999 Series I-II-III-IV
MIL-C-5015 (MS3400 Series)
MIL-C-83723 Series III
MIL-C-83733. And, additional backshells are being qualified.

From simple wire bundle strain reliefs to advanced devices for EMI/RFI shielding, Glenair continues to design and develop new connector accessories and backshells to meet industry's demands. Glenair offers the widest choice of backshells within the scope of MIL-C-85049, and continues to be the leader in developing new products to satisfy the diversity of wiring system requirements. Call or write for more information.

GLENAIR, INC.

1211 Air Way • Glendale, California 91201 • (213) 247-6000

INFO/CARD 8

$$X_{\text{talk}} = 20 \log_{10} \frac{V_{\text{victim}}}{V_{\text{culprit}}} \quad (1)$$

For the capacitive contributor, a crude expression of the coupling is:

$$X_{\text{talk}}(\text{cap}) = 20 \log \frac{Z_v}{Z_v + \frac{1}{jC_{1-2}\omega}} \quad (2)$$

Z_v , the victim circuit impedance, includes the trace-to-ground capacitance C_2 . At frequencies such as $1/C_2\omega \gg R_{\text{victim}}$, the X_{talk} simplifies as:

$$X_{\text{talk}}(\text{cap}) = 20 \log R_{\text{victim}} \times C_{1-2}\omega \quad (3)$$

$$\text{or } X_{\text{talk}}(\text{cap}) = 20 \log 2\pi f \times R_{\text{vict}} \times C_{1-2}$$

If one prefers time domain to frequency domain, the voltage induced in the victim trace can also be expressed as:

$$V_{\text{victim}} = R_{\text{vict}} \times C_{1-2} \times \frac{\Delta V}{\tau_r} \quad (4)$$

where ΔV is the culprit voltage swing and τ_r its rise time — with C_{1-2} in Farads, τ_r in sec of C_{1-2} in nanofd and τ_r in nanosec.

From Eq. (3), it is obvious that crosstalk is a phenomena which monotonically increase with frequency. At the worst, crosstalk could reach 0dB, i.e., the peak voltage in victim equals the peak culprit voltage (Figure 2). If the frequency where $R_{\text{vict}} \times C_{2w} = 1$ occurs before the 0dB asymptote, the crosstalk remains *clamped* to a value equal to the capacitive divider $C_{1-2}/(C_{1-2} + C_2)$.

For the mutual inductance contributor, the voltage induced *longitudinally* in the victim is

$$V_v = M_{1-2}\omega I_{\text{culprit}} = M_{1-2}\omega \frac{V_c}{Z_{c1}} \quad (5)$$

So the inductive contributor expresses as:

$$X_{\text{talk}}(\text{ind}) = \frac{M_{1-2}\omega}{Z_{c1}} \quad (6)$$

Here again it is a coupling increasing with frequency. In theory, there is no reason why the inductive crosstalk should not become greater than 0dB, i.e., the victim induced voltage being larger than the culprit line voltage, like in a step-up transformer. However, in PCB configurations, the two circuits are sufficiently similar and, being *one-turn* coupled loops, the coupling factor never exceeds unity.

Although Inductive Coupling Exists, Capacitive Coupling Generally Predominates

Since we know that 2 contributors participate to crosstalk, it seems necessary to compute them separately, then retain the larger of the two, or their combination. Hopefully in PCB's, a rough estimate can be made without this complexity.

A look at equations (3) and (6) shows that for a given geometry, *capacitive crosstalk increases with large victim impedances, and inductive crosstalk increases with low culprit impedances*. The take-over of capacitive coupling over the inductive one occurs for circuit loads $\approx 100\Omega$ (very exactly when loading equals Z_0 of the line). Also the wire-to-wire capacitance is aggravated by ϵ_r of the epoxy glass while mutual inductance stays equal to its free-air value.

For these reasons, unless the culprit circuit is a very low impedance ($< 30 \text{ Ohms}$), a *quick crosstalk estimate can use the capacitance coupling only*.

The table of Figure 3 gives this crosstalk per centimeter length of parallel runs on epoxy glass, for victim impedances of 100Ω and several printed traces dimensions (1 oz base material assumed, i.e., trace ≈ 20 micrometers thick). The left vertical entry is scaled in frequencies of the culprit signal while the right entry is scaled in corresponding rise times using the relation $F = 1/\pi\tau_r$ (if fall time is faster than rise time, the shortest of the two should be used).

The procedure to apply the table is the following:

- Select the geometry corresponding to the culprit-victim cross section
- Define culprit critical frequency or rise time
- Find the corresponding crosstalk per unit length (cm)
- Apply length correction
- Apply impedance correction if $Z_{\text{victim}} \neq 100\Omega$ by computing


$$20 \text{ Log}_{10} l_{\text{cm}}$$

$$20 \text{ Log}_{10} \frac{Z_{\text{victim}}}{100\Omega}$$

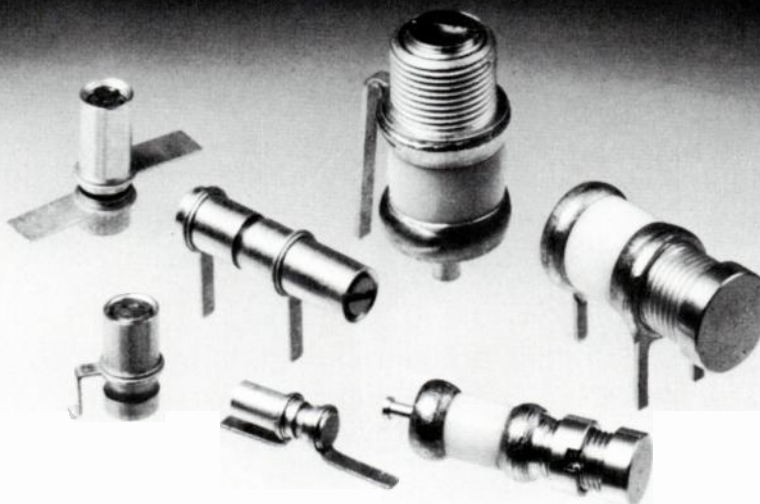Example

Two traces have a 10cm parallel trip.
Trace width $W = 20 \text{ mils}$
Trace separation $S = 20 \text{ mils}$
No ground plane
Culprit = Schottky Logic, 4 volts swing, 3 nanosec rise time

MIL-C-14409 and Johanson Variable Capacitors...



TWO TIMES ACTUAL SIZE

Now qualified to MIL-C-14409 are Johanson high performance Giga-Trim® Capacitors, military styles PC21, PC22, PC23, and PC24. Air dielectric capacitors are available in military styles PC25 through PC32. These rugged sapphire and air dielectric trimmer capacitors meet the highest standards of quality and reliability. From the early space programs to today's sophisticated military electronic circuitry, Johanson Variable Capacitors continue their record of outstanding service.

Electronic Accuracy through Mechanical Precision

Johanson

Manufacturing Corporation

Rockaway Valley Road Boonton, New Jersey 07005
201-334-2676 TWX 710-987-8367

U. S. Patent No. Re30,406

INFO/CARD 9

For FCC & VDE Compliance

10 GOOD REASONS TO USE

A.H. SYSTEMS

EMI TEST EQUIPMENT



SPECTRUM ANALYSIS EMI TESTING


**FCC, VDE, CISPR, TEMPEST
& MIL-STD-461**

The SAS-210 EMI Spectrum Analysis Set is the newest most economical method of performing RFI/EMI tests. The SAS-210 is a complete set of antennas, current probes, cables, preselectors and switches which converts a standard spectrum analyzer into a RFI/EMI receiver system. The SAS-210 provides the user the convenience and flexibility of a spectrum analyzer while affording all of the capabilities of a wide range receiver in performing the following tests:

E-Field — 1KHz to 1.8GHz
H-Field — 20Hz to 50KHz
Conducted — 20Hz to 100MHz

The IEEE 488 GPIB option when used with the latest spectrum analyzers, provides computer controlled EMI testing with automatic preselector/antenna selection.

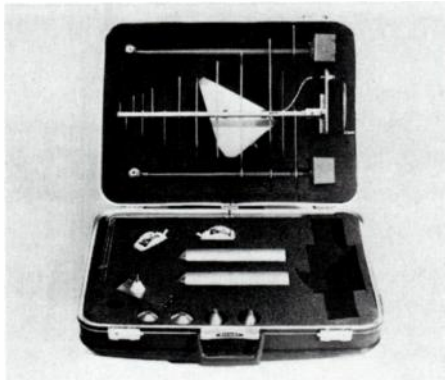The complete SAS-210 EMI Set is contained in 3 foam-lined carrying cases (each 27" x 21" x 9") for transportability and storage.



EMC ANTENNAS & CURRENT PROBES


A.H. Systems manufactures a full line of broadband antennas to cover the frequency range from 20Hz to 18GHz. Each antenna is tested and supplied with an Antenna Factor Calibration Curve. One foam-lined carrying case (27" x 21" x 9") contains all the antennas/probes/cables to perform the following measurements.

E-Field — 1KHz to 18GHz
H-Field — 20Hz to 50KHz
Conducted — 20Hz to 100MHz

Antenna factor calibrations at 1, 3, 5, 10 & 30 meter distances are available for all E-Field antennas to satisfy FCC, VDE & MIL-STD-461 specifications.

MODEL #	FREQ. RESP.	DESCRIPTION
SAS-200/510	300 - 1800 MHz	Log Periodic
SAS-200/511	1000 - 12000 MHz	Log Periodic
SAS-200/518	1000 - 18000 MHz	Log Periodic
SAS-200/530	150 - 550 MHz	Broadband Dipole
SAS-200/540	20 - 280 MHz	Biconical
SAS-200/541	20 - 280 MHz	Bicon'l, Collapsible
SAS-200/542	20 - 280 MHz	Biconical, Folding
SAS-200/550	.001 - 60 MHz	Active Monopole
SAS-200/560	per MIL-STD-461	Loop - Emission
SAS-200/561	per MIL-STD-461	Loop - Radiating
BCP-200/510	20 Hz - 1 MHz	LF Current Probe
BCP-200/511	100 KHz-100 MHz	HF/VHF Crnt. Probe

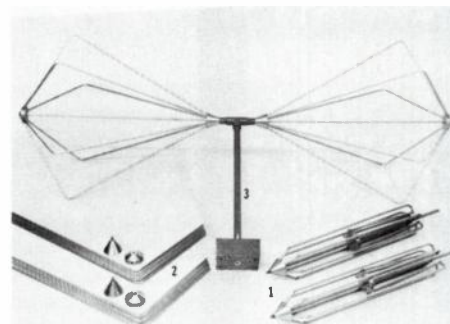All antennas are stocked for immediate delivery. VDE Loops and FCC Dipoles available in Spring 1981.



FOLDING BICONICAL ANTENNA

3 different biconical antenna element configurations are available. They are electrically equivalent over the frequency range of 20 to 280MHz.

1. Folding Biconical. Elements can be folded similar to an umbrella to a 3½ inch diameter cylindrical package. For use where rapid operate/travel conditions are desired with the mobility of a small package. Antenna assembly takes less than one minute.

2. Collapsible Antenna. Elements can be disassembled to reduce volume of antenna for travel or storage. For use where travel is often enough to require a small antenna package. Antenna assembly takes from 8 to 10 minutes.

3. Standard Biconical. Is a rigid element assembly as shown in MIL-STD-461.



A.H. Systems

For further information
and Catalog, write:

A.H. Systems
9710 Cozycroft Ave.
Chatsworth, CA 91311

INFO/CARD 10



FOR SAME DAY DELIVERY
CALL: (213) 998-0223

Victim = Schottky Logic, Noise margin typical 1 volt, wst case 0.4 volts (input *low*)

Victim impedances = one gate *low* output impedance (about 50Ω) on driving side, parallel with one gate *low* input impedance (about 200Ω) on load side so total victim impedance = 40Ω

$$\begin{aligned} X_{\text{talk}} &= -38 \text{ dB (table value)} \\ &+ 20 \text{ Log } 10_{\text{cm}} \\ &\quad \text{(length correction)} \\ &+ 20 \text{ Log } \frac{40}{100} \\ &\quad \text{(imp. correction)} \end{aligned}$$

$$\begin{aligned} X_{\text{talk}} &= -38 \text{ dB} + 20 \text{ dB} + \\ &(-8 \text{ dB}) = -26 \text{ dB} \cong 5\%. \end{aligned}$$

$$V_{\text{victim}} = 4 \text{ volts} \times .05 = 200 \text{ mV}$$

This is about one half of the worst case signal line noise margin, so normally no problem can be expected. However, if several adjacent culprit lines, or a fan-out of several devices are running close to the victim trace, capacitive crosstalks may add up to upset the threshold of the receiving gate.

Apply Stop Band Rejection For Crosstalk Between Different IC Technologies

When different technologies are involved between the crosstalk source and victim, for instance ECL and TTL, or TTL and CMOS, or even analog devices, bandwidth limitation has to be checked. If the frequency F_{EMI} of the culprit is larger than the cut-off frequency F_{co} of the victim, a relaxation equal to $20 \text{ Log}_{10} F_{\text{co}} / F_{\text{EMI}}$ should be applied to the computed crosstalk. In time domain terms, one should compute the same relaxation per 20 Log_{10} Victim rise time/Culprit rise time. This accounts for the fact that noise immunity of the victim device improves when the pulse width of the noise stimuli becomes shorter than the minimum turn-out time of this IC family. The slope of this stop-band is generally given by the gate input capacitance, i.e., 6 dB octave or 20 dB per decade.

How Geometry and Impedances Influence Crosstalk

There is an enormous amount of parameters which influence crosstalk, like trace thickness, trace self inductance, fringing capacitance in the air, mismatch factor in culprit and victim circuits.

Figure 4, summarizes the circuit parameter's dependency for crosstalk.

Simple Layout Rules Can Reduce Crosstalk at No, or Moderate, Added Cost

Several simple and easy-to-remember design guidelines can end up with a trouble-free PC board layout, rather than the *wait and see if it works* strategy:

(A) Control the ratio length/separation of parallel traces. One centimeter of parallel runs spaced by 10 mils (0.25mm) can be more fatal than 10 cm runs with 1 cm separation.

(B) Preferably run the signals *above* their ground plane or return trace,

rather than co-planar layout.

(C) Strictly ban parallel runs of high speed Logic (TTL, LS, ECL) with low level analog circuits.

(D) When (B) and (C) cannot be achieved, consider a grounded *guard* trace between culprit and victim wiring.


(E) When long parallel runs are unavoidable, (example: motherboards), consider a grounded *guard ring*: a double trace surrounding the culprit (or victim) trace. This has proven very useful with long clock runs.

(F) Multilayers do include, by design,

RF Telemetry Links with state-of-the-art performance and reliability


Communitronics new family of low cost receivers and transmitters is available in high or low band VHF and UHF models. They're designed to telemeter voice, low speed digital information and tone signals for such applications as Data Links, Status Control, Supervisory Control, Alarm Systems, Monitoring Systems, Pipeline Control and Low Power Repeaters, to name a few. Besides our standard models, which are available with optional RF connectors, we can also design and produce custom units to meet your exact requirements.

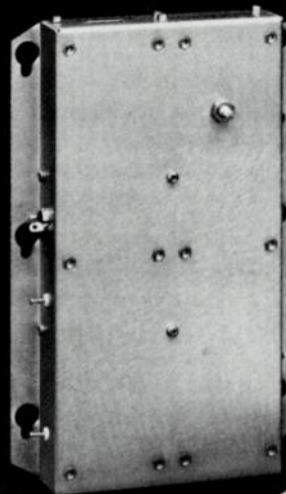So, if you want the latest in RF telemetry links, write or call Communitronics for detailed specifications and pricing.



TRANSMITTER

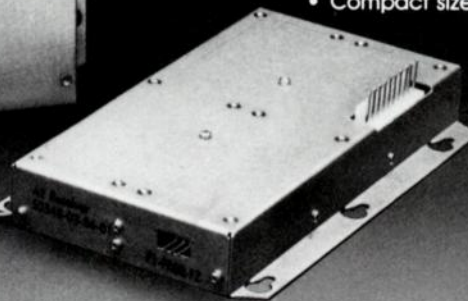- 1½ and 4 watt powers
- Rated continuous duty
- Compact size



RECEIVER


- Dual Conversion
- Low standby current for battery operation
- Compact size

COMMUNITRONICS

LTD.

160 Wilbur Place, Bohemia, N.Y. 11716 • (516) 567-8320
INFO/CARD 11

HIGH POWER MICROSTRIP ATTENUATOR

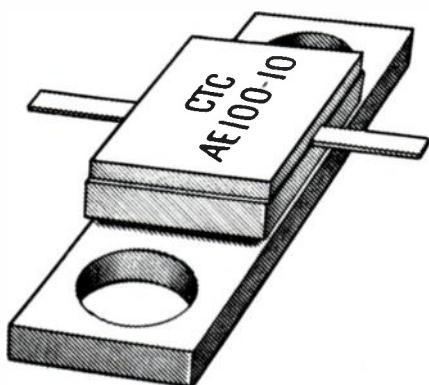

You won't find more power per square inch in a high frequency, fixed ratio attenuator. Developed especially for microstrip applications, our new attenuator uses state-of-the-art thermal design to deliver maximum performance from 25 to 250 watts, from .5 to 30 dB. And the microstrip construction offers VSWR of 1.25:1 up to 2 GHz with no resonant loops.

High Reliability

Instead of soft solder interfacing, we used a high temperature brazed package and a thin film, high-stability resistor to ensure dependability and long life. What's more, every attenuator is thoroughly tested as it comes off the line—and guaranteed to your specification.

Fast Delivery

You don't have to wait months for this kind of performance, either. We'll get them to you in as little as four to six weeks.



Need more information?
Just give us a call:
Communications Transistor
Corporation, 301 Industrial
Way, San Carlos, California
94070 (415) 592-9390.

INFO/CARD 12

Parameter	Crosstalk
Trace Spacing Increase	→
Trace-To-GND (or return trace) Spacing Increase	→
Larger ϵ_r	→
Z victim LARGER	→
Z culprit SMALLER	No influence on capacitive coupling. But may cause inductive coupling to show up.
Length of Parallel Run Increase*	→

Note* When applying length correction add-on, be sure to clamp to $l \leq \lambda/4$ of EMI frequency.

Figure 4. Geometry and Impedance vs. Crosstalk

the advantage of rule (B). But when 2 signal layers are sandwiched together without an intermediate ground layer, for cost saving, the crosstalk can be even worse than with a single layer, double sided PCB because victim and culprit traces are coupled like parallel plates, embedded in a high ϵ_r media.

And once you have checked your layout, do not overlook these two outsiders: the IC socket and the PCB connector. About the socket, there is not much you can do: it introduces an in situ parasitic coupling of 3pF or more, pin-to-pin. Hopefully, IC devices are generally characterized using some socket anyway and they are deemed to tolerate this coupling. The PCB connector can ruin the efforts of a sound PCB layout if care is not taken for pin assignment. Avoid assigning fast signal pins next to susceptible ones, and at least alternate signal-ground-signal-ground—this will preserve the characteristic impedance, too, if needed.

Conclusion

This short description does not pretend to encompass the whole subject. Tons of papers have been written on this specific matter. The Bibliography on the calculation of the trace edge capacitance only would occupy a full shelf in a respectable library, notwithstanding that they give often different results, depending on the degree of sophistication of their mathematical or empirical derived nature.

But the user can rely on the Table of Figure 3 for rough prediction within 6 dB confidence, which is more than adequate in usual EMI calculations.

A good practice is to *allocate, at the beginning of a design*, a certain budget for crosstalk. For instance, no more than -20 dB (10% max) of the

logic immunity threshold, for each culprit-victim team.

References

- R.K. Southard, "High Speed Signal Pathways," Electronic Engineering, Sept., 81.
- C.R. Paul, "Prediction of Crosstalk in Ribbon Cables," IEEE EMC Transactions, Nov., 76.
- R.J. Mohr, "Interference Coupling, Attack It Early," EDN, July, 69.
- J.A. DeFalco, "Predicting Crosstalk in Digital System," Computer Design, June, 73.
- D.R.J. White, "EMI Methodology & Procedure," published by DWCI, Gainesville, VA 20065.
- D.R.J. White, "EMI Control in PCB," published by DWCI, Gainesville, VA 20065.
- H.W. Ott, "Noise Reduction Techniques," John Wiley & Son.

Author's Background

Michel Mardigian, is a Graduate Electro-Mechanical Engineer. He started in Electronic Packaging of Aircrafts, then in Computers Packaging at IBM R & D Laboratory. He entered the EMC area in 1974 and enjoys design and field experience of problems in the computer/telecommunications area. For four years he has been an active member of the CISPR (EMC studying body of the IEC) group on computer interference. He is Director of Training at Don White Consultants, Inc., a well-known firm which conducts seminars and consulting on Electro Magnetic Compatibility.

ELECTRO-METRICS

A PENRIL COMPANY

Let Electro-Metrics Satisfy All Your EMC Measurement Requirements...



**... With Quality Instrumentation Known Worldwide
For Performance and Reliability.**

Featuring:

- Complete frequency coverage from 20Hz to 40GHz
- Choice of single-unit, automated or calculator-controlled testing
- Testing per FCC/VDE/CISPR and MIL-STD 461/462 EMC specifications
- Complete range of options and accessories available

100 CHURCH ST. • AMSTERDAM, NY 12010 • (518) 843-2600 • TWX 710-446-4798

ELECTRO-METRICS

Insertion Loss Testing Of Common Core Filters

Filters are an important element in controlling EMC/EMI. This article describes the specification and testing of these devices.

by Kenneth Sanders
Genisco Technology Corp.
Electronics Division
Rancho Dominguez, CA

Introduction

The last several years have seen a dramatic change in the composition of the EMI (Electromagnetic Interference) filter marketplace. Increased understanding of EMI (separating interference into common mode and differential mode signals) coupled with changes from regulatory safety agencies and revisions to Mil-Std 461 limiting ground currents, have led to the development of a new configuration in filters, the common core or common mode filter. Also testing specifications have not kept pace with advances in technology, specifically and most notably Mil-Std 220, the specification for insertion loss testing.

Common Mode and Differential Mode Noise

To gain an understanding of what is required for common core filter insertion loss testing, a simple explanation of common mode and differential mode noise, as well as, the functioning of a common core filter is presented. The discussion that follows is stated for a two phase three wire system, but is easily extended to three phase, three and four wire systems.

Common mode noise is any noise signal that is in phase on each of the two above ground lines with respect to ground. Differential mode noise is a noise signal that is out of phase on the two above ground lines. If the 60Hz line voltage were noise, it would be differential mode. Screen room tests have demonstrated that the majority of noise below 1MHz is common mode and above 1MHz is differential mode noise.

Filter Testing

A simple common core filter is illustrated in Figure 1. The

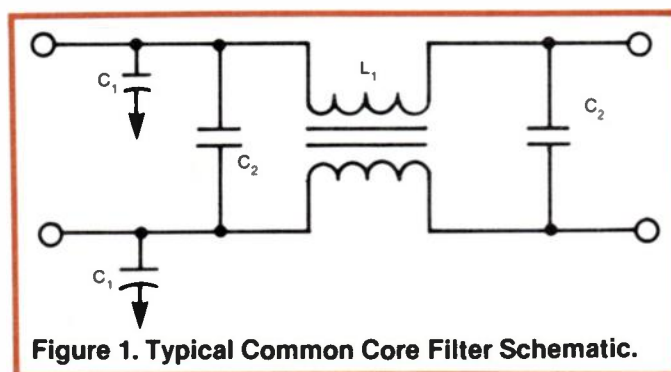


Figure 1. Typical Common Core Filter Schematic.

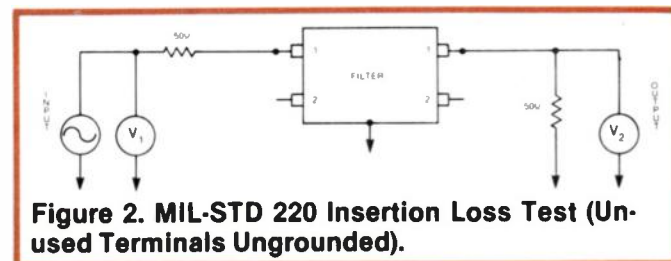


Figure 2. MIL-STD 220 Insertion Loss Test (Unused Terminals Ungrounded).

two C_1 capacitors are small in value to limit ground current and, as frequencies increase, become effective in shunting both common mode and differential mode noise to ground. The two C_2 capacitors are generally one to two magnitudes larger in value than the C_1 capacitors. They are effective only for differential mode noise as common mode noise signals would be, by definition, in phase across C_2 and thereby present no potential difference. The L_1 inductor, also called common core, is two windings on a single core. The windings are connected in a manner that the power line currents which tend to saturate a core, cancel each other and the net effective saturating current is zero. The L_1 inductor offers a high impedance to common mode signals up to a frequency where the coupling between windings falls off and leakage inductance becomes a factor. Above this frequency, L_1 becomes effective against

differential mode signals and less effective against common mode signals.

Mil-Std 220 insertion loss testing is not adequate to test a common core filter. The test configurations of Figure 2 and Figure 3 only inject a differential mode signal and therefore do not test for common mode signals at all. Mil-Std 220 allows for testing with unused terminals grounded or ungrounded and using the worst case. In Figure 2 only one C_1 capacitor and L_1 are effective in filtering. In Figure 3 one C_1 and both C_2 capacitors are doing filtering, but L_1 is shorted out thru terminal 2 being shorted to ground. At frequencies above L_1 winding coupling failure, L_1 becomes effective, but at only a fraction of it's original inductance.

The test circuit depicted in Figure 4 is being specified by one user of common core filters. It has most of the same disadvantages of Mil-Std 220. This method only partially shorts L_1 with 100 ohms limiting the maximum impedance of L_1 to 100 ohms. This method almost totally negates any value of the C_2 capacitors.

Insertion loss testing as depicted in Figure 5 can be accurately utilized for differential mode testing as shown. Common mode noise testing can be achieved by clamping the injection and current probes around two or three lines simultaneously. Load and source impedances are reasonably simulated, eliminating the classic argument against Mil-Std 220 testing utilizing 50 ohms. While this method is undoubtedly the most accurate, there are significant cost safety considerations for the filter manufacturer. There is the potential for operator hazard working with line voltages and currents. Test set-up time is extensive. Test time per frequency is extensive. Test readings in the 5 to 50MHz range may be difficult to obtain and above 50MHz, impossible due to line impedances and frequency/power limitations of the injection probe.

Figures 6 and 7 represent an extension of Mil-Std 220 test methods to completely test common core filters for both common mode and differential mode signals. The classic arguments against Mil-Std 220 testing in that 50 ohms does not accurately represent real world performance of a filter are still applicable. This can be easily overcome by writing filter specifications that contain both schematics and nominal element values of the filter. Elements values that are derived from testing to meet a specified conducted radiation or susceptibility requirement.

Conclusion

Wide bandwidth balun transformers shown in Figure 7 are readily commercially obtainable. The test method proposed in Figure 6 and 7 can be readily adapted for full load testing by insertion of buffer networks, etc. Standardization in insertion loss test methods for common core filters is necessary to realize both cost effective and repeatable test results. □

Author's Background

Kenneth Sanders received his formal education in engineering at the University of California at Los Angeles. He has been with Genisco Technology Corporation for eighteen years as a design engineer, quality manager, and production manager. He currently is product manager for the filter product line of Genisco.

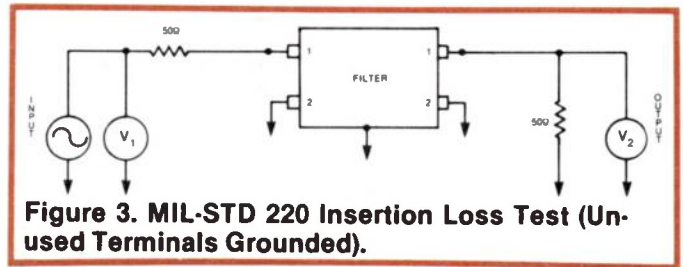


Figure 3. MIL-STD 220 Insertion Loss Test (Unused Terminals Grounded).

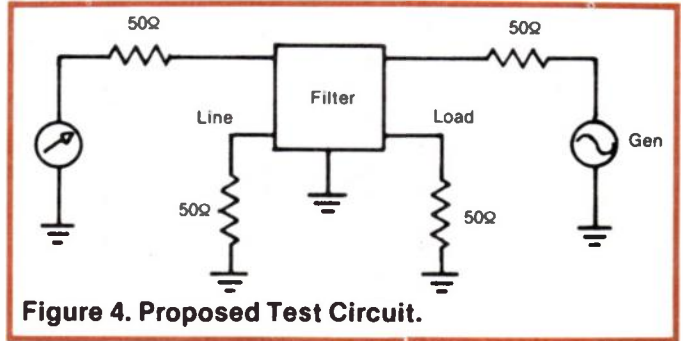


Figure 4. Proposed Test Circuit.

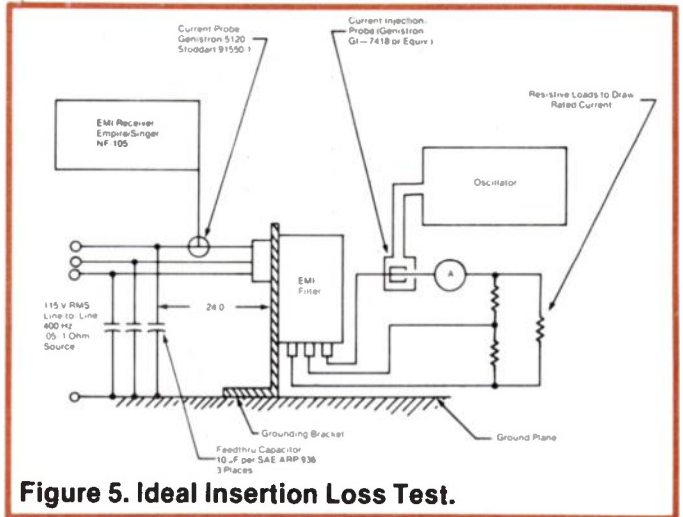


Figure 5. Ideal Insertion Loss Test.

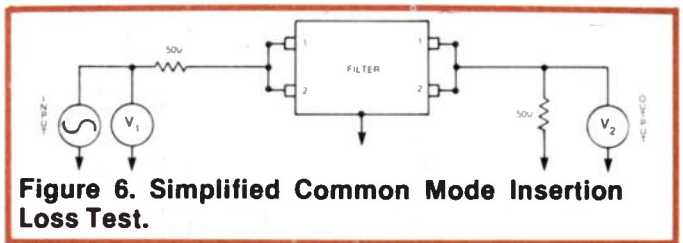


Figure 6. Simplified Common Mode Insertion Loss Test.

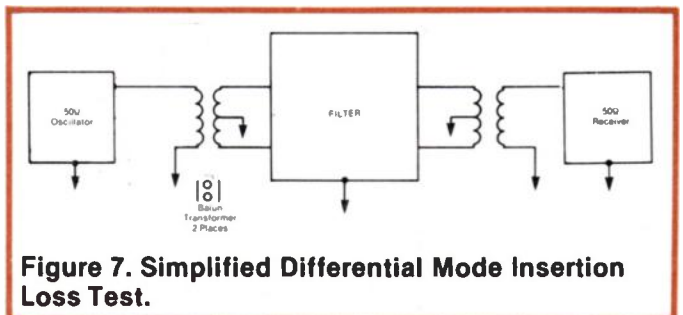


Figure 7. Simplified Differential Mode Insertion Loss Test.

A Binary Stepped Transmission Line

Binary related line lengths simplify testing procedure for high powered linear amplifiers.

By Roderick K. Blocksome
Rockwell International
Collins Telecommunications Product Division
Cedar Rapids, Iowa

The Problem

The design and development of high frequency linear power amplifiers involve specifications which describe the amplifier performance at various VSWR's referenced to a nominal output load. For example, the output tank circuit may be specified to match a 3:1 (or less) VSWR relative to 50 ohms. A broadband solid state PA may specify rated output power into loads presenting a VSWR of 1.3:1 or less. Additionally, the amplifier stability must be insured at higher VSWR's. How does one test to such specifications over the wide range of impedances of a given VSWR circle and over the frequency range of the PA? A common method used at HF (1.6 to 30 MHz) requires an adjustable matching network and a 50Ω dummy load. A reversible L-network, with sufficient tuning range, connected to a standard 50 ohm resistive load will transform the load to the desired complex impedance on the VSWR circle at the frequency of interest.

Amplifier testing at a moderate number of impedance points at selected frequencies and VSWR's can become a very time consuming task. Each point must be calculated, then with the aid of an impedance measuring instrument, the L-network adjusted, then connected to the amplifier under test and the measurement made. The time required by this method can be reduced somewhat by making up several lengths of transmission line which can be inserted between a desired VSWR load and the unit under test. Since the line electrical lengths are different at different fre-

quencies, data taking at a constant complex impedance for different frequencies becomes a problem.

Microwave engineers use a very handy device commonly called a "sliding load" or "trombone line section". It is a low loss transmission line whose length may be quite easily changed by sliding the line in telescoping fashion. Such lines, whose length may be changed over a half wavelength, are quite manageable in the laboratory. But for testing at 1.6 MHz we would have a "trombone line section" several hundred feet long! A HF "trombone line section" could be approximated by a large number of small discrete lengths of line and a switching arrangement to connect as many lengths in series as desired. The line length would not be continuously variable, but if each elemental line length were short compared to a half wavelength line at the highest test frequency, then several impedance points could be obtained at a given VSWR. For example, if the elemental line lengths were 20 electrical degrees long at 30 MHz, then 9 different impedance points on a Smith Chart VSWR circle could be transformed from a given VSWR load. At lower frequencies, more points correspondingly closer could be realized since the elemental line lengths become electrically shorter. However, the total number of elemental line sections required to achieve $\frac{1}{2} \lambda$ (180° electrical degrees) becomes quite large with a corresponding increase in switching complexity. How can we then build a switched variable transmission line with reasonable size, cost, and complexity?

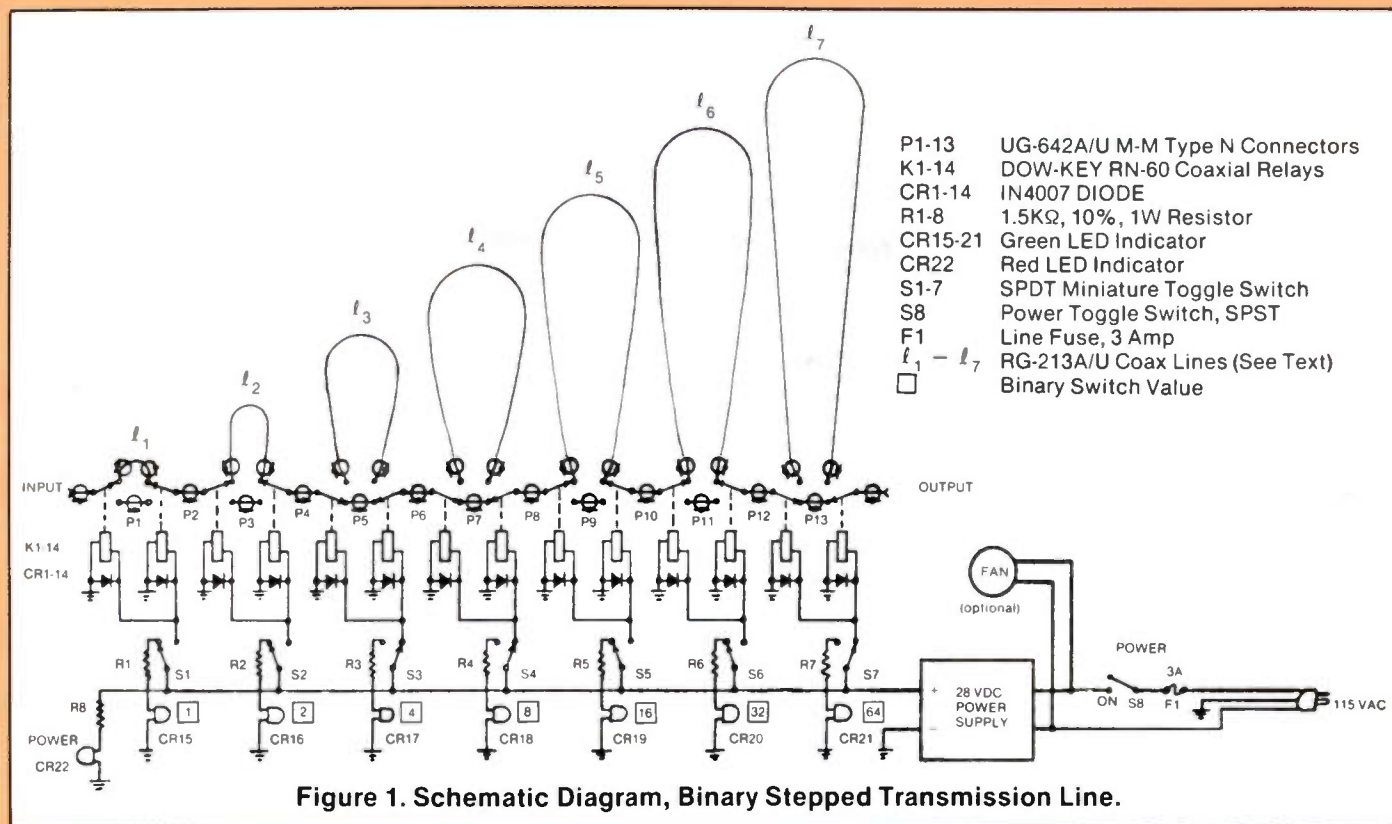


Figure 1. Schematic Diagram, Binary Stepped Transmission Line.

The Solution

The answer lies in making the "elemental" line lengths binarily related. Thus any desired total line length can be achieved in length increments equal to the smallest line length that can physically be implemented. I have designed such a device for use between 1.6 and 30 MHz. There are many ways of implementing a binary stepped transmission line within desired frequency and power requirements. A brief description of a 1 KW HF unit which was designed and built may prove helpful to others wishing to build similar units.

Circuit Description

A schematic of a Binary Stepped Transmission Line is shown in Figure 1. The unit was designed to operate up to 1000 watts, on a 50 ohm system and at frequencies between 1.6 and 30 MHz. The coaxial relay selected was the Dow-Key RN-60 SPDT with type N connectors. It was selected because of good reliability, low cost, and adequate impedance characteristics. RG 213 A/U coaxial cable was selected for the transmission lines. The velocity factor of RG-213A/U is given as 0.66 which means approximately 202 feet of cable is required to achieve $\frac{1}{2} \lambda$ at 1.6 MHz. The smallest length of line used was 1.59 feet. This was about the shortest length that could be physically connected between the relay connectors, and was arrived at by calculating back from the maximum desired line length. The calculated lengths are

- $l_1 = 1.59$ ft.
- $l_2 = 3.17$ ft.
- $l_3 = 6.34$ ft.
- $l_4 = 12.68$ ft.
- $l_5 = 25.37$ ft.
- $l_6 = 50.74$ ft.
- $l_7 = 101.48$ ft.

Packaging 14 coaxial relays and 200 feet of RG-213A/U cable into a convenient size for general purpose lab use is

not difficult if the relays are connected and stacked in a vertical zig-zag manner. The coaxial cables are dressed around the perimeter of a chassis box measuring 17-in wide \times 9.75-in high \times 20-in deep. Type N double male coaxial fittings are used to interconnect all relays to minimize line length through the relays. Each pair of relays at a switch point are controlled by toggle switches on the front panel. Each switch is labeled with its binary bit weight. This requires the user to do some mental addition to find the actual step number. One could readily design a relay control circuit using digital IC's and seven segment displays if the toggle switch system is too inconvenient. The first relay, K1, is mounted with its common terminal exposed at the front panel providing the input connection. The last relay, K14, is mounted in a vertical manner such that its common terminal is exposed through the top cover of the chassis to provide the output connection. This somewhat unusual arrangement precludes having internal relay interconnecting cables which would add to the inherent line length of the relays and allows the connection of loads other than 50 ohms directly and allows the connector. A fan mounted in the chassis provides cooling air to these loads. A 28 volt DC power supply was incorporated in the unit to power the relays. The cover picture shows the interior of the completed unit.

VSWR Loads

The load impedance required to produce various VSWR's may easily be obtained either of two ways. The easiest is to connect two, three, or four commercial 50-ohm dummy loads in parallel using "Tee" connectors to produce 25, 16.67, and 12.5 ohm loads for tests at 2:1, 3:1, and 4:1 VSWR. If other intermediate VSWR's are desired, large wattage carborundum type resistors are available to construct a load suitable for operation up to 30 MHz. Experiment with resistors and an impedance measuring instrument to obtain the desired resistive load with negligible reactance at

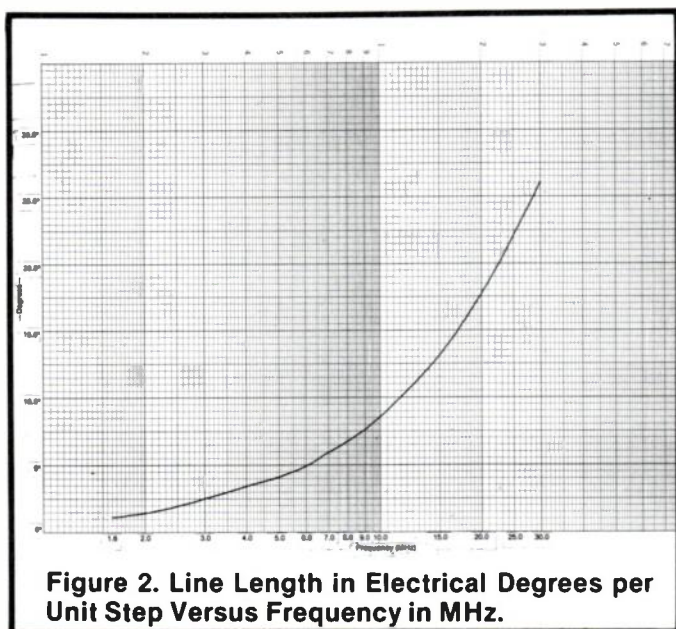


Figure 2. Line Length in Electrical Degrees per Unit Step Versus Frequency in MHz.

30 MHz. Another possible source would be custom load impedances from manufacturers of dummy loads. Perhaps one could purchase otherwise rejected resistor elements in the range of 40 to 60 ohms for low VSWR testing.

An alternative method of obtaining low VSWR resistive loads is to use attenuators terminated into either an open circuit or short circuit. Such attenuators are commonly available in lower power ratings. Table 1 lists VSWR which may be obtained from common attenuator values. The formula for calculating the values in Table 1 is provided for those desiring other values.

Using the Binary Stepped Line

When using the binary stepped transmission line, it is convenient to know the number of electrical degrees of line produced, per unit step, at the frequency of interest. The graph shown in Figure 2, kept with the equipment, will aid the user. Line losses will introduce an error in actual VSWR (VSWR reduction with increasing line length and line loss). For this reason it is a good practice to always use line lengths of $\frac{1}{2} \lambda$ or less even though longer lines are possible at higher frequencies. Remember, impedance transformation on lines up to a $\frac{1}{2} \lambda$ cover a full VSWR circle on the

Table 1. VSWR of Various Attenuators

Attenuator Value	VSWR	Formula for calculating VSWR of an attenuator terminated in either an open or short circuit.
1 dB	8.72:1	
2 dB	4.42:1	
3 dB	3.01:1	
4 dB	2.33:1	
5 dB	1.93:1	
6 dB	1.67:1	
7 dB	1.50:1	
8 dB	1.38:1	$\text{VSWR} = \frac{10^{-A/10} + 1}{10^{-A/10} - 1}$ where A = Attenuation in dB
9 dB	1.29:1	
10 dB	1.22:1	
20 dB	1.02:1	

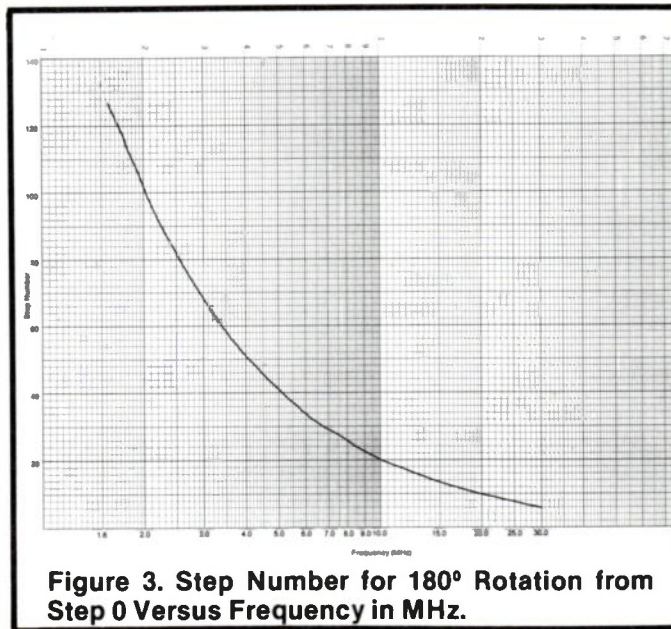


Figure 3. Step Number for 180° Rotation from Step 0 Versus Frequency in MHz.

Smith Chart. A second graph shown in Figure 3 gives the step number versus frequency to produce $\frac{1}{2} \lambda$ of line. As mentioned previously, VSWR will decrease slightly as one inserts longer and longer line lengths between the load and the device under test. This loss is also a function of the VSWR on the line. This should not be a problem for most applications if the maximum VSWR is held to 5:1. In tests which require greater impedance or VSWR accuracy, it is a simple matter to set up the test with the binary stepped transmission line and an HP-4815A RF Vector Impedance meter to read the impedance. The VSWR for that impedance can readily be found by solving the following equation on a handheld calculator. An HP-25 program is given in Table 2.

$$\text{VSWR} = \frac{1 + |\Gamma|}{1 - |\Gamma|} \quad \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

where: $Z_L = R_L + jX_L$ load impedance

$Z_0 =$ characteristic line impedance

assuming Z_0 is real, solving for $|\Gamma|$:

$$|\Gamma| = \left[\left(\frac{\left(\frac{R_L}{Z_0} - 1 \right) \left(\frac{R_L}{Z_0} + 1 \right) + \left(\frac{X_L}{Z_0} \right)^2}{\left(\frac{R_L}{Z_0} + 1 \right)^2 + \left(\frac{X_L}{Z_0} \right)^2} \right)^2 + \left(\frac{2 \frac{X_L}{Z_0}}{\left(\frac{R_L}{Z_0} + 1 \right)^2 + \left(\frac{X_L}{Z_0} \right)^2} \right)^2 \right]^{1/2}$$

Increasing electrical line length per step with increasing frequency permits fewer impedance points to be accessible around the VSWR circle. A "trombone line" borrowed from the UHF lab and inserted in series with the binary stepped line will allow access to these intermediate impedance points.

Applications

Applications of the binary stepped transmission line in HF department work are numerous. Some uses that it has been put to in our HF lab are:

1) Tuning range evaluation of transmitter output networks and antenna couplers.

(Continued on page 29.)

Texscan's XR-1500...A sweep generator with a difference.

Compare the XR-1500 with other sweep generators in its class. We think you'll come to the conclusion that the XR-1500 stands alone in performance at a competitive price.

The XR-1500 offers excellent stability with low residual FM. Its' unique phase lock feature allows for sweep testing of devices with less than 10 KHz bandwidth with ease and accuracy.

An internal crystal marker system provides $\pm 0.005\%$ frequency accuracy.

Exceptional flatness and precision built-in RF attenuation provide relative amplitude measurement accuracy of ± 0.1 db over narrow frequency ranges and ± 0.5 db over the full 1500 MHz range.

The XR-1500 also performs all the conventional sweep generator functions, such as transmission and reflection response of wide band components, amplifiers, filters and other devices.



phase locked

Call us today and ask
about our fast delivery.

Texscan

Texscan Corporation
2446 N Shadeland Ave
Indpls IN 46219
(317) 357-8781
TWX #810-341-3184
TELEX #272110-01

Texscan Instruments Limited
1 Northbridge Rd
Berkhamsted
Hertfordshire, England
UK
04427 71138
TELEX #851-82258

GMBH
Peschelanger II
D 8000 Munchen 83
West Germany
089-67010-48
TELEX #841 522915

6

Solutions VHF




12
TO-72



32
TO-92



33
SOT-23

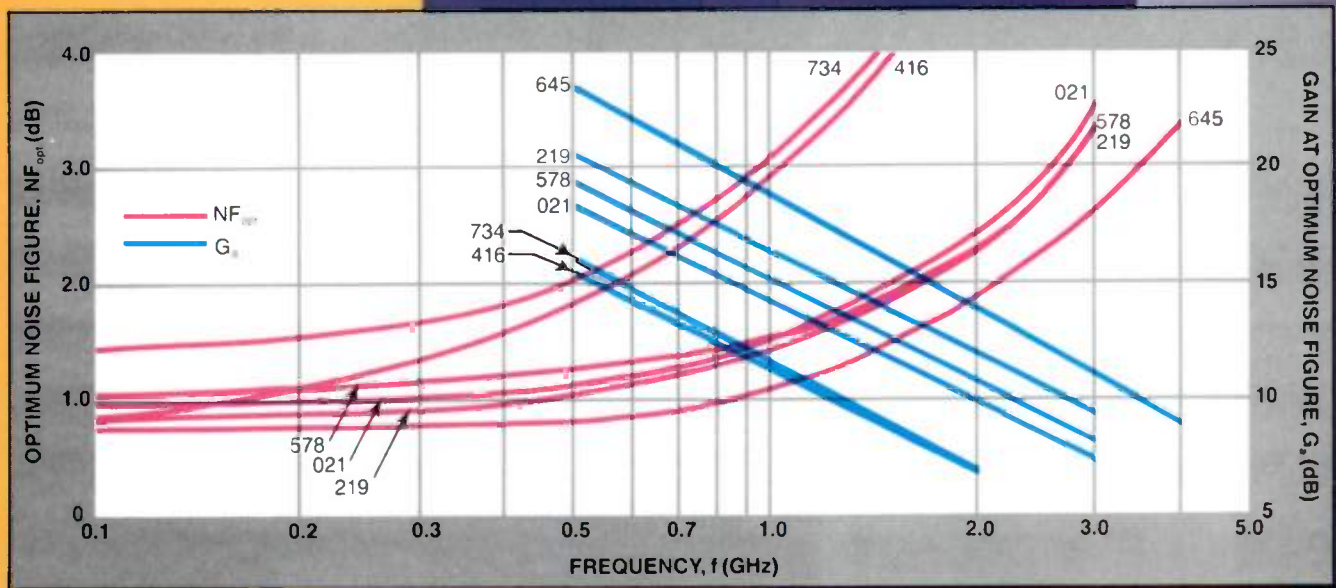

NEC microwave semiconductors

...to your low cost UHF & MW problems

NE021 — NE219 — NE416 — NE578 — NE645 — NE734

These famous high performance small signal NPN transistors from NEC are now available in one or more low cost packages and at prices you can afford for virtually all your VHF, UHF, and MW applications.

They feature the NEC highly reliable metallization system of platinum-silicide, titanium, platinum and gold which provides consistent high temperature operation at rated dissipation.


The highest degree of performance, uniformity and reliability are assured by NEC's famous quality control and test procedures patterned after MIL-S-19500.

Devices in the famous "MICRO-X" package (#35) are available with either JANTX or JANTXV equivalent screening and are highly recommended for high performance military and communications applications.

Step up to quality and performance at the right price.

SPECIFY NEC.

INFO/CARD 15

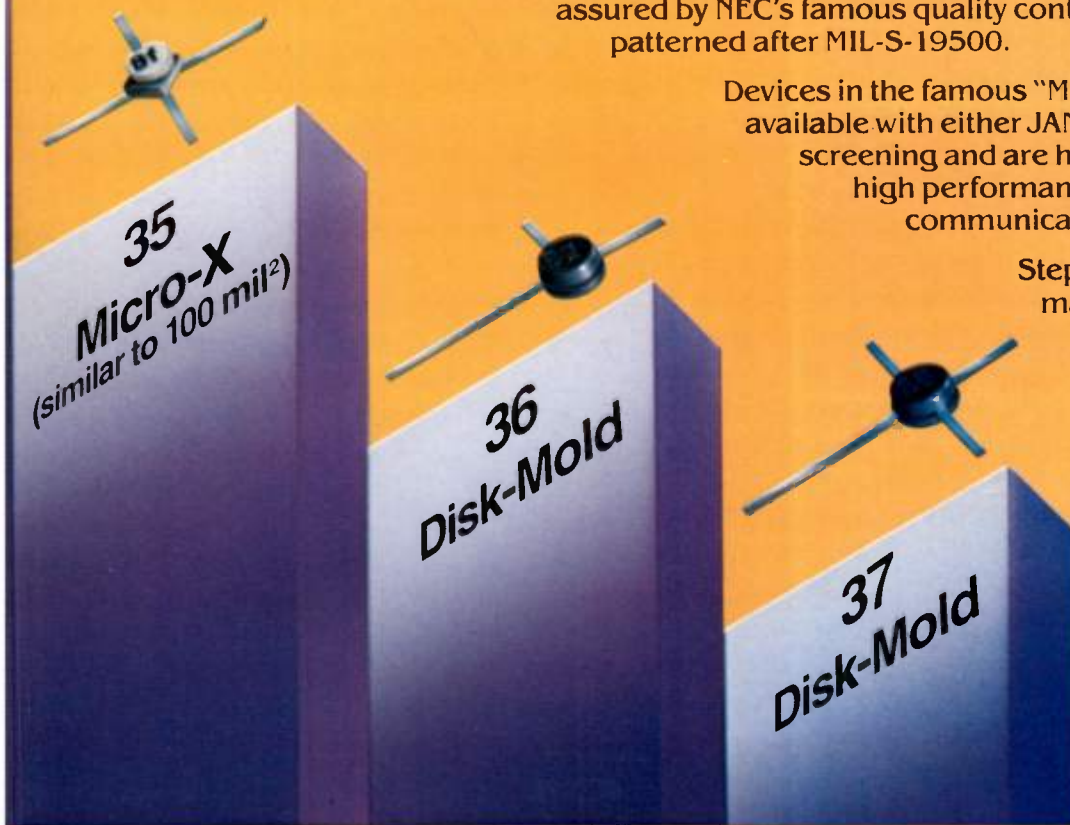

CALIFORNIA EASTERN LABORATORIES, INC. — U.S. and Canada
Exclusive sales agent for **Nippon Electric Co., Ltd.** Microwave Semiconductor Products.



3005 Democracy Way, Santa Clara, California 95050 • Tel. (408)988-3500 • Tlx. 346393 or 171197

September 14, 15, 16

1400+ Product Exhibits • 38 Professional Program sessions with more than 160 presentations • Special Exhibits on *Robotics* and *Office Automation* • Continuous shuttle bus service between *Mini/Micro* and *Wescon* • Technical Forecasting and Business seminars • Purchasing Conference • Film Theater

For a Preview Program, write: Wescon/82, P.O. Box 92275 Worldway P.C., Los Angeles, CA 90009

INFO/CARD 16

Table 2.
HP-25 Program to Solve for VSWR,
Given Impedance.

STEP	PROGRAM	STEP	PROGRAM
1	RCL 0	23	+
2	÷	24	X ↔ Y
3	STO 1	25	÷
4	STO 2	26	g X ²
5	1	27	STO 5
6	STO - 1	28	RCL 3
7	STO + 2	29	2
8	R↓	30	X
9	R↓	31	RCL 4
10	RCL 0	32	÷
11	+	33	g X ²
12	STO 3	34	RCL 5
13	g X ²	35	+
14	RCL 2	36	f √ X
15	g X ²	37	STO 6
16	+	38	1
17	STO 4	39	+
18	RCL 1	40	RCL 6
19	RCL 2	41	CHS
20	X	42	1
21	RCL 3	43	+
22	g X ²	44	÷

STORE Z₀ in Register 0

a) Input Data for Z_L in Rectangular form:

key in X_L
ENTER
key in R_L
ENTER
R/S

b) Input Data for Z_L in Polar form:

key in angle θ (degrees)
ENTER
key in magnitude |Z| (ohms)
f → R
R/S

(Continued from page 24.)

- 2) Evaluation of solid state PA dissipation protection controls under VSWR conditions.
- 3) Evaluation of filter input harmonic impedances and their relationship to solid state power amplifier performance.
- 4) Solid State PA stability tests under VSWR conditions.

Within the limitations of the impedance transformation accuracy described above, the binary stepped transmission line provides a means of rapidly transforming any known or given impedance to any other desired impedance on essentially the same VSWR circle. Changes in test frequencies are likewise handled rapidly and efficiently.

Acknowledgment

The author wishes to acknowledge the contribution of Forrest Arnold in packaging design and construction of a working model. □

DIGITAL ATTENUATORS

63.5 dB
30-500 MHz
7 Bits: 0.5 dB least significant

internal driver
TTL or CMOS compatible



Specification	TTL	CMOS
Part Number	DA0295	DA0285
Control	7 line TTL	7 line CMOS
D.C. Power	+5 VDC at 50 mA	+5 to +15 VDC 25 mA
Frequency	30 to 500 MHz	
Range	63.5 dB Above Insertion Loss	
Sections	0.5, 1, 2, 4, 8, 16, 32 dB	
Switching Speed	5 Microseconds Nominal	
R.F. Power	+13 dBm CW Maximum	
Insertion Loss	6 dB Maximum	
VSWR	1.35 Maximum	
Impedance	50 Ohms	



**Industry Leader in
Microwave Integrated
Circuit & Connectorized
Switches, Step
Attenuators, Voltage
Control Attenuators**

DAICO INDUSTRIES, INC.

2351 East Del Amo Blvd., Compton, Calif. 90220
Telephone: (213) 631-1143 • TWX 910-346-6741

© 1980 Daico Industries, Inc.

mp8408

INFO/CARD 17

Bandpass Filters With Self-Equalized Group Delay: Part 2

Part I dealt with the background, practical and theoretical considerations dealing with this design method. Part II gives the details of the filter design.

*By Robert W. Sellers
Harris Corp., GESD
Melbourne, Florida*

Filter Design Method

The procedure to be described is admittedly not mathematically exact, but it is sufficient to calculate correct capacitor values to within a fraction of 1%. The calculated values may be easily adjusted via either the computer program or in the case of actual circuit construction, obtained by measurement on a well calibrated capacitance bridge, and trimmed slightly in final alignment of the network.

As mentioned previously, the procedure to be described is based on a design with four inband resonators and two correction poles. For bandwidths less than about 25% of center frequency, a pair of series tuned compensator circuits are used to improve the group delay even further in the transition regions. These compensator circuits are due to Lerner and comprise the means by which the reactive residual components of the network are effectively included as a part of the filter loads. For the wider bandwidth (36 MHz) filters, the low Q necessary in these compensators produce excessive non-symmetry in the amplitude response. For the 36 MHz filter, the group delay ears are produced by the pair of out-of-band zeros which are used to adjust the out of band attenuation.

It should be realized that there are two basic choices for implementation of the filter to be described shortly. For example, the filter may be designed using linear frequency spacing across the passband; in this case, exponential component sizing is necessary for the networks. The design is equally valid for the case where each inband resonator uses the same magnitude of capacitance and the frequency spacing is made exponential across the passband. The case of linear frequency spacing is selected for the design example.

Example

The example will now be presented via a 14 step design procedure of a filter with the following characteristics, schematically represented by Figure 6.

Center frequency (f_0) = 70 MHz
Bandwidth (3 dB) = 10 MHz
Inband resonators = 4

(1) Determine the frequency spacing necessary between parallel resonances:

$$\frac{10 \text{ MHz BW}}{4 \text{ resonances}} = 2.5 \text{ MHz} = 2 \Delta f$$

(2) Calculate the actual center frequency of the resonances:

Since there is an even number of networks in the total filter (both arms), there is no single network resonance at exactly 70 MHz. The two closest (f_3 and f_4) will therefore be

located at $\pm \frac{2\Delta f}{2} = \Delta f \pm 1.25 \text{ MHz}$ away from 70 MHz. Following Lerner, we will choose to use the linear frequency spacing. However, because we choose to do this, we must abandon the use of the same capacitor value for each of the resonators, we therefore arrive at the frequencies of the resonances as follows:

$$\begin{aligned} f_2 (L_2 - C_2) &= 66.25 \text{ MHz} \\ f_3 (L_3 - C_3) &= 68.75 \text{ MHz} \\ f_4 (L_4 - C_4) &= 71.25 \text{ MHz} \\ f_5 (L_5 - C_5) &= 73.75 \text{ MHz} \end{aligned}$$

f_1 and f_6 are the corrector poles and will be nominally adjusted to be at the upper and lower band edges of the filter. The calculated frequency for these resonances would be

65 and 75 MHz respectively in the Lerner design. The Lerner method requires that the inband capacitors each be the same magnitude and the corrector capacitances twice that value. We will later arrive at a nominal value for these corrector capacitances which are $\approx \pi/2$ rather than 2 times the inband capacitor values. This in turn requires that the frequencies for the corrector resonances be placed $\approx 20\%$ (of $2 \Delta f$) out of band. The correctors will be determined in the final steps of this procedure.

(3) Place the resonances from the lowest inband frequency (f_2) to the highest inband frequency (f_3) in alternate arms of the lattice. At this point, f_2 and f_4 are in say, arm B, while f_3 and f_5 reside in arm A. A space, f_1 , is reserved for the low frequency corrector pole in arm A, and likewise, a space for corrector f_6 is reserved in arm B.

(4) Determine the desired impedance level for the filter. Remember that as in Figure 3, the filter sees a total external resistance of R , which is the sum of the source and load resistance. This step allows the freedom to choose the ap-

range to resonate the 100 pf capacitors near 70 MHz.

The Q of the inductors should be measured and a good average (practical value) employed for the calculations which follow. Say the average of this unloaded Q is $Q_u = 100$, evaluated at 70 MHz.


$$X_c(\text{nom}) \text{ at } 70 \text{ MHz} = 22.7\Omega.$$

$$\therefore R_p = 2.27K = (Q)(X_c);$$

$$(7) \text{ Calculate } \alpha_{\text{nom}} = \frac{1}{2RC} \text{ for the nominal values.}$$

$$\alpha_{\text{nom}} = \frac{1}{2RC} = \frac{1}{2(2.27K)(100\text{pf})} = 2.2026 \times 10^6$$

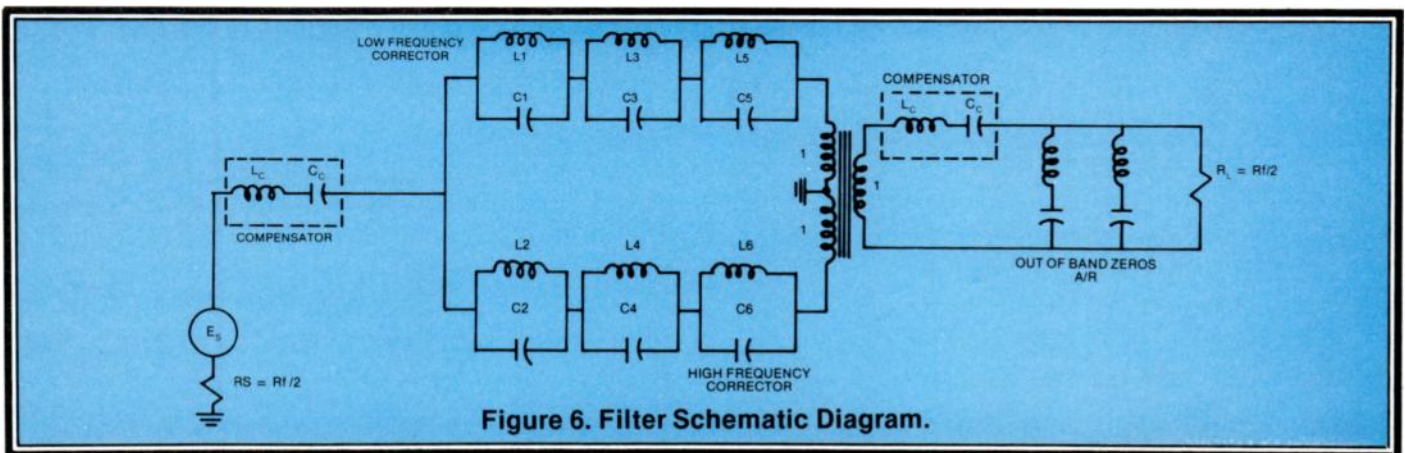(8) The results of step 7 is the Neper frequency we wish to scale as a constant across the band of the filter. Since the filter is symmetrical about f_o , we need only to calculate α at the resonance above, (f_4) and below, (f_2) f_o . Both these resonances appear in arm B. Arm A will then use the same capacitor values but in reverse order.



proximate magnitude of the capacitors to be used in the filter implementation.

$$R(\text{Filter}) = (4/\pi)(X_c) | f = 2 \Delta f$$

where X_c is the reactance of the selected capacitor evaluated at a frequency of $2 \Delta f$. (2.5 MHz in this example) Say the desired total load resistance is 500 ohms; then $C = 100$ pF.

The capacitor value thus calculated is the "nominal" value to be used in the implementation. It is important to realize that a capacitor of exactly 100 pF will not actually be used. Likewise the filter source and load resistance will not be exactly 250 ohms each; herein lies the root of some of the mathematical inexactness. It will later be found, however that the effective performance of the filter will be well within predicted tolerances in implementation.

The significance of the 100 pF value which was calculated may be explained by realizing that with an even number of resonators, no network is required at the filter center frequency. If an odd number was selected for the inband resonators, it would use such a capacitor value. Further, it is customary to assume that any practical filter will only exhibit the calculated resistive component at precisely f_o . Small mismatches at inband frequencies other than f_o are tolerated in this design as well.

(5) Select an unloaded Q for the resonators. This is an important step as all the Q 's should be the same. The choice of inductor style as well as capacitor type and frequency range to be covered (B W of filter) will have an impact on this selection. As with any filter, we wish to have the greatest unloaded Q possible, to minimize the filter insertion loss.

For the example filter, we need inductors in the 50 nH

$$\alpha(f_2) = 2.2026 \times 10^6 \left(\frac{66.25 \text{ MHz}}{70 \text{ MHz}} \right) = 2.0846 \times 10^6$$

$$\alpha(f_4) = 2.2026 \times 10^6 \left(\frac{71.25 \text{ MHz}}{70 \text{ MHz}} \right) = 2.2419 \times 10^6$$

(9) Arm B contains individual parallel resonances at f_2 and f_4 representing finite attenuation poles. It is necessary, however, that a frequency f_3 , arm B contain a transmission zero. In order for arm B to be series resonant at f_3 , it is necessary to employ the capacitance residual from f_2 (above resonance) and obtain the proper magnitude of inductance from f_4 (below resonance). These solutions must be simultaneously achieved while maintaining the correct α and parallel resonances.

$$\alpha(f_3) = 2.2026 \times 10^6 \left(\frac{68.75}{70} \right) = 2.163 \times 10^6$$

Note that $\alpha(f_3)$ must be obtained from a series resonant circuit where $\alpha = \frac{R'}{2L}$


$$\text{where } R' = \frac{R_p}{1 + Q^2} = 0.227\Omega$$

we now calculate:

$$\frac{R'}{2L} = 2.163 \times 10^6; \quad \frac{1}{L} = \frac{(2)(2.163 \times 10^6)}{(0.227)}$$

$$L = 52.47 \text{ nH}$$

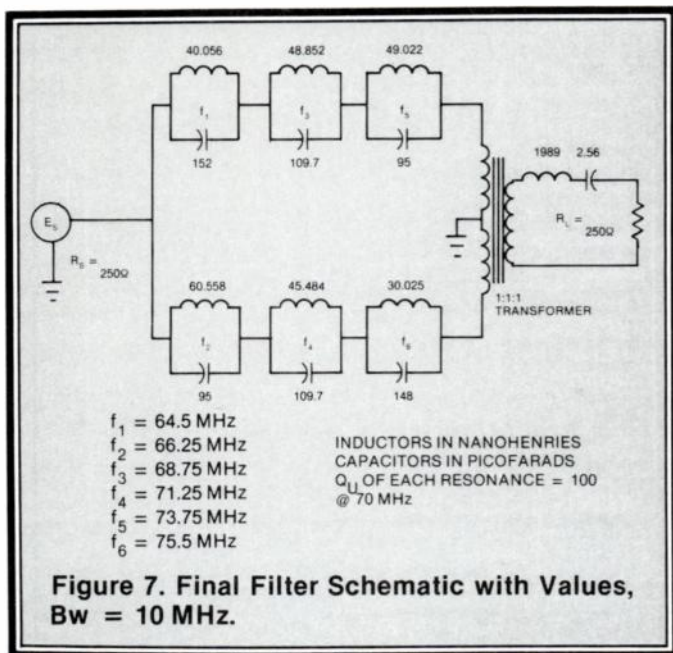
This is a mythical inductance. It will be used to calculate the final capacitor values necessary at f_2 and f_4 to provide the proper α . The same comment regarding mathematical



exactness as discussed in step 4 for the nominal capacitor applies here.

The capacitor values are calculated using the standard approximation for resonances, $\omega_0 = \frac{1}{\sqrt{LC}}$ ($R \gg \omega L$)
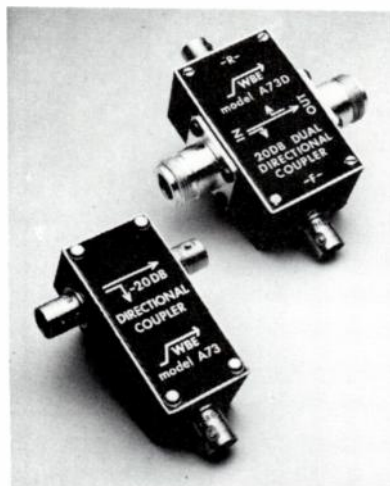
$$66.25 \text{ MHz} = \frac{1}{(2\pi) \sqrt{52.47 \times 10^{-9} C_2}}$$



**BROADBAND EQUIPMENT
FOR INSTRUMENTATION
AND COMMUNICATIONS**

Directional Couplers

Model	Freq Range MHz	Coupler Type	In Line Power	Minimum Directivity (dB)		In Line Loss (dB)	Response Flatness of -20 dB part (dB)	VSWR
				1-500 MHz	5-300 MHz			
A73-20	1-500	single	5W cw (10W cw 5-300 MHz)	20	30	.4 max	-1 5-300 MHz +.25 1-500 MHz	1.1:1
A73-20GA				30	40	.2 typical		1.5:1
A73-20GB				40	45			1-500
A73-20P	1-100	single	50W cw (75 ohm limited to 10W cw)	35 dB min		.15	1.1	1.1:1 max
A73D-20P		dual		40 dB min typical		.3		
A73-20PX		single		45 dB min		.15		
A73D-20PX		dual				.3		
A73-20PA	10-200	single		35 dB min		.15		1.04:1 typical
A73D-20PA		dual		40 dB min typical		.3		
A73-20PAX		single		45 dB min		.15		
A73D-20PAX		dual				.3		

WIDE BAND ENGINEERING COMPANY, INC.

P O BOX 21652, PHOENIX, ARIZONA 85036, U S A • TELEPHONE (602) 254 1570

INFO/CARD 18

$$C_2 = 109.99 \text{ pf}; (f_2 = 68.75 \text{ MHz})$$

Likewise, C_4 is found to be 95.1 pf. ($f_4 = 71.25 \text{ MHz}$)

(10) The simple calculations above must now succumb to some logical reasoning. C_2 and C_4 were calculated based upon the α we wish to be simultaneously exhibited by the *other* arm—the one containing f_3 and f_5 . Since the value for α should be scaled across the entire filter, and not just in one arm, the capacitors calculated to be used as C_2 and C_4 must be actually used for C_3 and C_5 respectively! This requires that the values for C_2 and C_4 be reversed to provide the exponential value symmetry for each lattice arm *and* for the filter simultaneously. With this realization, the capacitor values calculated may be placed in the filter as follows:

$$\begin{aligned} \text{Arm "B"} \left\{ \begin{array}{ll} f_2(66.25 \text{ MHz}) & C_2 \text{ value} = 95.1 \text{ pf} \\ f_4(71.25 \text{ MHz}) & C_4 \text{ value} = 110 \text{ pf} \end{array} \right. \\ \text{Arm "A"} \left\{ \begin{array}{ll} f_3(68.75 \text{ MHz}) & C_3 \text{ value} = 110 \text{ pf} \\ f_5(73.75 \text{ MHz}) & C_5 \text{ value} = 95.1 \text{ pf} \end{array} \right. \end{aligned}$$

The corrector resonators, f_1 and f_6 , are yet to be determined.

(11) With the capacitor values thus selected, it is a simple matter to parallel each value with an inductor to provide the proper center frequency using the resonance approximation, $\omega_0 = \frac{1}{\sqrt{LC}}$

100	PLC	AA	SE	40.056892	152	100	70
110	CAP	BB	PA	.0000001	1000	70	
120	PLC	CC	SE	48.852662	109.7	100	70
130	CAP	DD	PA	.0000001	1000	70	
140	PLC	EE	SE	49.022179	95	100	70
150	CAP	FF	PA	.0000001	1000	70	
160	TRF	GG	TR	1			
170	CAX	AA	GG				
180	PLC	HH	SE	60.558568	95.3	100	70
190	CAP	II	PA	.0000001	1000	70	
200	PLC	JJ	SE	45.48455	109.7	100	70
210	CAP	KK	PA	.0000001	1000	70	
220	PLC	LL	SE	30.025113	148	100	70
230	CAP	MM	PA	.0000001	1000	70	
240	CAX	HH	MM				
250	TRF	XX	TR	1			
260	CAS	HH	XX				
270	PAR	HH	AA				
280	EQU	QQ	HH				
290	SLC	NN	SE	1989 2.56	100	70	
300	RES	OO	SE	.01			
310	CAP	PP	PA	.0000001	1000	70	
320	RES	RR	SE	.01			
330	SLC	SS	SE	.001	1000000	1000000	70
340	CAX	NN	SS				
350	PLO	NN	S7	250			
360	PRI	NN	S7	250			
370	END						
380	60	70	1				
390	71	80	1				
400	END						
READY.							

Figure 8a. Compact Program for 10 MHz Bw Filter.

Polar S-Parameters in 250.0 Ohm System

Freq.	S11			S21		S12		S22		
	Magnitude	Angle	dB	Angle	Magnitude	Angle	Magnitude	Angle	Delay	
60.00	.92	- 111	- 28.33	- 89.2	.038	- 89.2	.96	131	32.909	
61.00	.89	- 128	- 24.38	- 103.1	.060	- 103.1	.94	123	44.651	
62.00	.83	- 152	- 19.76	- 122.7	.103	- 122.7	.91	113	64.729	
63.00	.72	172	- 14.36	- 152.3	.191	- 152.3	.85	97	101.694	
64.00	.49	109	- 8.76	160.0	.365	160.0	.69	74	161.872	
65.00	.23	4	- 5.06	92.7	.558	92.7	.38	46	200.003	
66.00	.10	- 76	- 3.93	20.3	.636	20.3	.08	38	200.288	
67.00	.11	- 76	- 3.88	- 51.3	.640	- 51.3	.11	129	198.008	
68.00	.10	- 115	- 3.89	- 122.9	.639	- 122.9	.08	100	200.592	
69.00	.07	- 104	- 3.85	164.7	.642	164.7	.06	- 159	200.221	
70.00	.07	- 142	- 3.83	93.2	.643	93.2	.08	- 178	198.155	
71.00	.03	- 122	- 3.83	21.5	.643	21.5	.05	- 131	200.052	
72.00	.06	- 174	- 3.88	- 50.7	.640	- 50.7	.11	- 112	200.576	
73.00	.04	52	- 3.85	- 122.7	.642	- 122.7	.11	- 107	199.314	
74.00	.01	6	- 3.91	165.5	.637	165.5	.11	- 62	200.972	
75.00	.25	- 17	- 5.15	92.2	.553	92.2	.39	- 42	201.621	
76.00	.58	- 92	- 9.19	28.1	.347	28.1	.72	- 70	150.397	
77.00	.75	- 144	- 14.36	- 14.5	.191	- 14.5	.87	- 93	95.157	
78.00	.83	- 178	- 19.04	- 42.1	.112	- 42.1	.93	- 108	63.492	
79.00	.88	158	- 23.02	- 61.2	.071	- 61.2	.95	- 118	45.486	
80.00	.90	139	- 26.42	- 75.2	.048	- 75.2	.96	- 125	34.359	

Figure 8b. Computer Calculated Values for S-Parameters and Delay for Figure 8a.

The resulting values for the example are:

$$\begin{aligned} \text{Arm A} \left\{ \begin{aligned} C_3 &= 110 \text{ pf}, L_3 = 48.719 \text{ nH}, Q_u = 100, f = 68.75 \text{ MHz} \\ C_5 &= 95.1 \text{ pf}, L_5 = 49.022 \text{ nH}, Q_u = 100, f = 73.75 \text{ MHz} \end{aligned} \right. \\ \text{Arm B} \left\{ \begin{aligned} C_2 &= 95.1 \text{ pf}, L_2 = 60.749 \text{ nH}, Q_u = 100, f = 66.25 \text{ MHz} \\ C_4 &= 110 \text{ pf}, L_4 = 45.360 \text{ nH}, Q_u = 100, f = 71.25 \text{ MHz} \end{aligned} \right. \end{aligned}$$

(12) The values of the corrector capacitors must be selected to achieve two simultaneous results.

- The magnitude of the resonator must have the desired effect of cancelling the closed inband pole in the opposite lattice arm, and
- The effect must exponentially vanish out of band with a damping coefficient such that it provides no overshoot and maintains the proper α to insure a (resistance) transition to a low value. The termination of the filter for the transition out of band is extremely important, however at frequencies as far as $2 \Delta f$ out of band, the termination of the filter is relatively unimportant allowing the use of zeros as mentioned earlier.

Continuing with the idea of exponential sizing for the filter capacitor values (since we have used a linear frequency spacing), we may estimate the corrector capacitor values as follows:

$$C_c(\text{nominal}) = \frac{1}{1 - e^{-1}} (95.1 \text{ pf}) = 150.3 \text{ pf}$$

The value 95.1 pf will be recognized as the smallest value in each arm. Since the "nominal" capacitor value which was originally calculated in step 4 was 100 pf and not 95 pf, a closer estimate for the two corrector capacitors may be found by allowing for the average difference between these values.

$$\text{We have } C_c = 150.3 \text{ pF} \pm 2.5 \text{ pF}$$

The larger value $\approx 152 \text{ pF}$ would be associated with f_1 , while the smaller value of 148 pF would be used with f_6 .

(13) The inductances to be used are calculated as in step 11, and the final corrector values are found to be:

$$\begin{aligned} \text{ARM A; } f_1 &= 65 \text{ MHz}, C_1 = 152 \text{ pF}, L_1 = 39.44 \text{ nH}, Q_u = 100 \\ \text{ARM B; } f_6 &= 75 \text{ MHz}, C_6 = 148 \text{ pF}, L_6 = 30.426 \text{ nH}, Q_u = 100 \end{aligned}$$

At this point it should be noted that since the corrector capacitors are not twice the value of the inband capacitors, the transmission zero formed by the corrector and its closest inband neighbor in each arm will not fall precisely on top of the pole to be cancelled in the opposite arm. This dilemma is solved by purposely tuning the correctors out of band by 20% of the $2 \Delta f$ value, in the case of the example, this amounts to 500 kHz. The values of L_1 and L_6 are adjusted to do this, resulting in the new values for L_1 and L_6 of 40.057 and 30.025 nH, respectively.

(14) The final step is to calculate a compensation circuit which will be placed in series with the entire filter. The use of this circuit is completely due to Lerner, and is found to consist of a series LC circuit resonant as f_0 . This circuit is useful to absorb the reactive components of both the filter and the source/load. Since the network is in series with the filter, rather than in parallel as it would be in the y-style Lerner filter, it is necessary that its bandwidth be greater than that of the filter. For the z-transformed filter using the capacitor values of 2X for the corrector poles, the Lerner theory reveals that the Q required of this network be 3/5 that of the filter.

The use of the exponential methods described in this recipe results in non-existent or very minimal group delay ears; therefore the effect of this network on the filter is much less.

It has been found experimentally that such a network is


EAS ELECTROLINE'S ADDRESSABLE SYSTEM

A cost-effective system offering maximum security with ease of control for multi-unit buildings.



Designed to control access or premium service to subscribers in multidrop buildings. The system is modular in design. Security is maintained by means of continuous scanning. EAS is ideal for apartments, hotels, hospitals or other such location where constant control is needed and to provide visual audit of each subscriber's status.

ADDRESSABLE SYSTEM

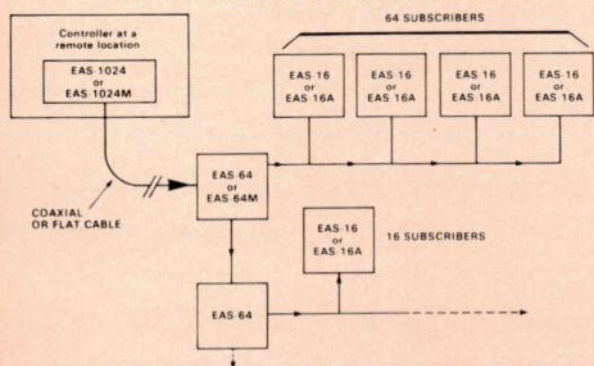

The above system is composed of 3 units — a microprocessor control (EAS-1024); a decoder (EAS-64); and a wide-band, multitap switch assembly (EAS-16). The system can be installed in 2 alternative configurations and is most compatible with other systems. Illustrated folder with specifications upon request.



ELECTROLINE Television Equipment Inc.

8750, 8th Avenue, St-Michel
Montreal, Que. H1Z 2W4

or phone **collect**
(514) 725-2471

Representatives across
Canada and the U.S.A.

- ☐ TAPS
- ☐ FILTERS
- ☐ COUPLERS
- ☐ SPLITTERS
- ☐ SPECIAL AMPLIFIERS
- ☐ SWITCH-TRANSFORMERS

INFO/CARD 19

useful indeed for "tuning" the source and load reactances. Via use of a computer program we have determined the correct value range for these components to be non-critical and reasonably close to an inductive reactance that is 5/3 of the *total* loop resistance of the filter. For the example, when the losses due to the finite Q's of the networks is included, X_L is found to be 874 ohms corresponding to an inductor of about 2 μ H. The capacitance required for 70 MHz resonance is then found to be 2.5 pF.

The Final Schematic for the filter is given in Figure 7. This schematic is used for the computer analysis shown in Figures 8 a-c. The performance of the filter as constructed is shown in Figure 9. The slight change in the values of C_3 and C_4 to 109.7 pF from the calculated values of 110 pF was a result of changing the corrector resonator center frequency slightly out of band as mentioned in Step 13.

Other Analysis

Additional analysis and work was done on 70 MHz filters with 5 MHz, 17 MHz and 36 MHz BW filters of this type. The effect of out-of-band zeros was noticed on the implementations of the 36 MHz filter. These components were not included in the 36 MHz computer program. Their addition enabled much better symmetry for the near skirts at the expense of some group delay ears. In particular, the filter implementation for the 36 MHz filter contains a total of only 8 individual LC circuits including the out-of-band zeros, resulting in the elimination of considerable circuitry over the present means of fitting this particular Intelsat mask.

The Computer Program

The analysis program will be recognized as written in COMPACT*, a very useful R.F. analysis tool for both active and passive networks. It is available under this name via G.E. timeshare, or from C.D.C. Corporation, where it is termed RFOPT. It is also available directly from Compact Engineering.

The actual programs contain lines which were used during development of the filters to experiment with the effects of non-perfect layout and components. Their effect


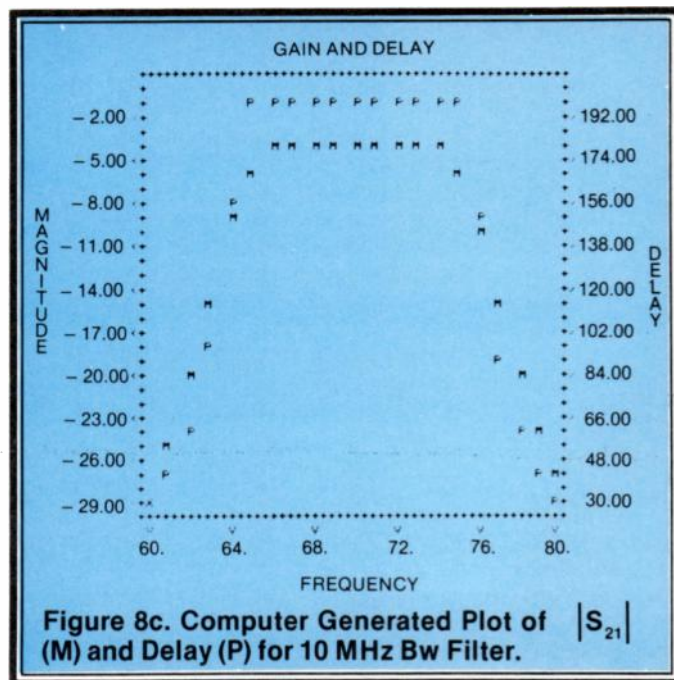
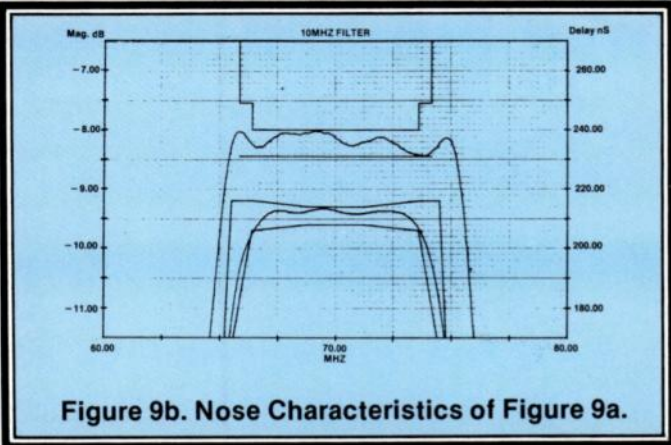


Figure 8c. Computer Generated Plot of $|S_{21}|$ (M) and Delay (P) for 10 MHz Bw Filter.

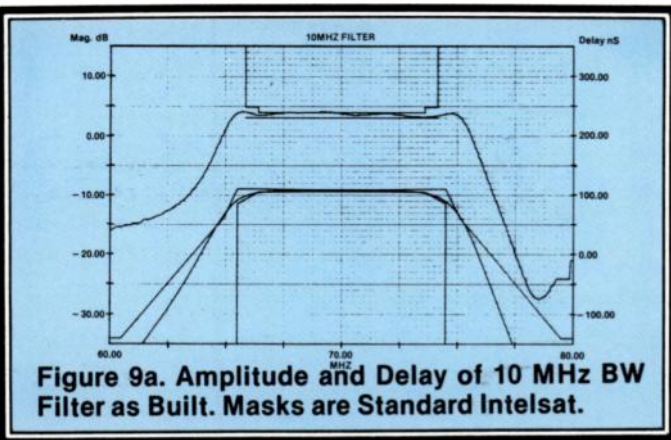

on the analysis presented is nil because the values set into them as shown for example in Figure 8a, lines 110, 130, 140, 190, 210, 230, and 300 thru 330, have no effect at the evaluation frequencies.

Breadboard Photograph

The cover of May/June issue of *R.F. Design* is a photograph of a 36 MHz BW filter. The 180° transformer is mounted beneath the p.c. card. The Motorola MWA series amplifiers, together with S.A.T. resistor networks are used to set the module gain that was needed for a particular application. All filter components are shown in the photo (with the exception of the transformer). □

*COMPACT information is available from: Compact Engineering, Inc., 1088 Valley View Court, Los Altos, California 94022.

Errata

In part 1 in the last issue, the following errors were noticed.

The corrected equations should be:

$$AN(\omega) = \left(1 + \frac{\omega^2 \ln 2}{N}\right)^{-N/2} \quad (6)$$

$$\phi N(\omega) = N \tan^{-1} \left(\frac{\omega \sqrt{\ln 2}}{\sqrt{N}} \right) \quad (7)$$

$$A = e^{-\left(\omega^2 \frac{\ln 2}{2}\right)} \quad (8)$$

Also the caption under figure 2b should read "nose response" rather than "noise response".

ENGINEERING PROFESSIONALS

Jerrold Division Offers Direct Involvement In New Developmental Projects For Satellite & Cable TV.

If you want to work on long-term, state-of-the-art projects and be involved in their development from concept through completion, look at what we have to offer. Jerrold is the nation's leading manufacturer of CATV equipment/systems and has pioneered many of today's most advanced products in communications. Explosive, on-going growth has created the following openings:

RF DESIGN ENGINEERS Subscriber Systems

Multiple positions, Junior through Project level, are available, requiring 3 to 5 years of experience in the design/development of RF circuitry. Familiarity with tuners, oscillators, video & RF amplifiers and phase-locked loops, a must. Distinguished background in digital design is highly desirable.

RF DESIGN ENGINEERS CATV Distribution Systems

Multiple positions, Junior through Project level, are available, requiring involvement in the design of broadband linear amplifiers; AGC/ALC RF amplifiers, hybrid splitters/couplers, filters and equalizers. Requires 3 to 5 years of solid experience in the field and/or an interest in CATV electronic systems development plus a BSEE or equivalent.

SENIOR CIRCUIT DESIGN ENGINEERS Advanced R&D Group

Multiple positions, Junior through Project level, with hands-on R&D applications, focusing on encoding analog signals and encrypting digital signals. Frequency range-video and RF to 1 Ghz. Requires a minimum of 3 years of experience in building breadboards of analog and/or digital circuits from discrete components & standard integrated circuits & standard integrated circuits. BSEE or equivalent mandatory.

All positions are located at our Divisional HQ in Hatboro, PA, a suburb of Philadelphia. You'll have the benefits of living in a lovely suburb with fine schools and a very affordable standard of living. Yet you'll be close to a historical city experiencing a renaissance in beauty, culture, entertainment, sports and development.

We offer excellent salaries, commensurate with experience, full benefits including paid relocation, superior career opportunities and an exciting environment for working and living. Qualified applicants should contact: **Rich Keyser, Jerrold Div., GENERAL INSTRUMENT CORPORATION, Dept. RF1, 2200 Byberry Rd., Hatboro, PA 19040, (215) 874-4800.** An Equal Opportunity Employer, M/F.

Jerrold Division

GENERAL INSTRUMENT

Triple Tuned Circuits

Previous articles described double tuned coupling circuits, now a wide band triple tuned coupling circuit offering.

By Andrzej B. Przedpelski
A.R.F. Products, Inc.
Boulder, Colorado

While the previously described double tuned circuits^(1, 2) offer simplicity, sometimes a wide band coupling circuit with more stop band attenuation is needed. The triple tuned circuit may be the answer. It has 18 dB/octave ultimate attenuation versus 12 dB/octave for the double tuned version and is very easily implemented. The described technique has been used successfully, using standard fixed military RF chokes and ceramic capacitors, for applications requiring up to 3:1 bandwidths.

The basic technique is described by Terman⁽³⁾. It can be modified to include finite Q values of inductors. The circuit is shown in Figure 1 and equations for the modified component values are:

$$L_1 = \frac{R'}{\pi(f_2 - f_1)} \quad (1)$$

$$C_1 = \frac{f_2 - f_1}{4\pi f_1 f_2 R'} \quad (2)$$

$$L_2 = \frac{R_0 [Q_L(f_2 - f_1) - \sqrt{f_1 f_2}]}{2\pi Q_L f_1 f_2} \quad (3)$$

$$C_2 = \frac{1}{2\pi(f_2 - f_1)R'} \quad (4)$$

where
 f_1 and f_2 are the passband limits
and
 R is R_0 and $Q_L \omega L_2$ in parallel

$$\omega = (f_1 + f_2)/2$$

$$R' = R_0 \parallel Q_L \omega L_2$$

Terman implies that $R_0 = R'$, but it will be shown that good performance can be obtained when that is not the case.

The HP-41C program of Table I calculates the values of L_1 , C_1 , L_2 and C_2 using equations (1), (2), (3), and (4).

The program of Table II calculates the frequency response in dB ($20 \log e_o/e_i$).

The following may serve as an example:

$R_0 = 75$ ohms
 $R_1 = 25$ ohms
 $f_1 = 20$ KHz
 $f_2 = 60$ KHz
 $Q_L = 50$

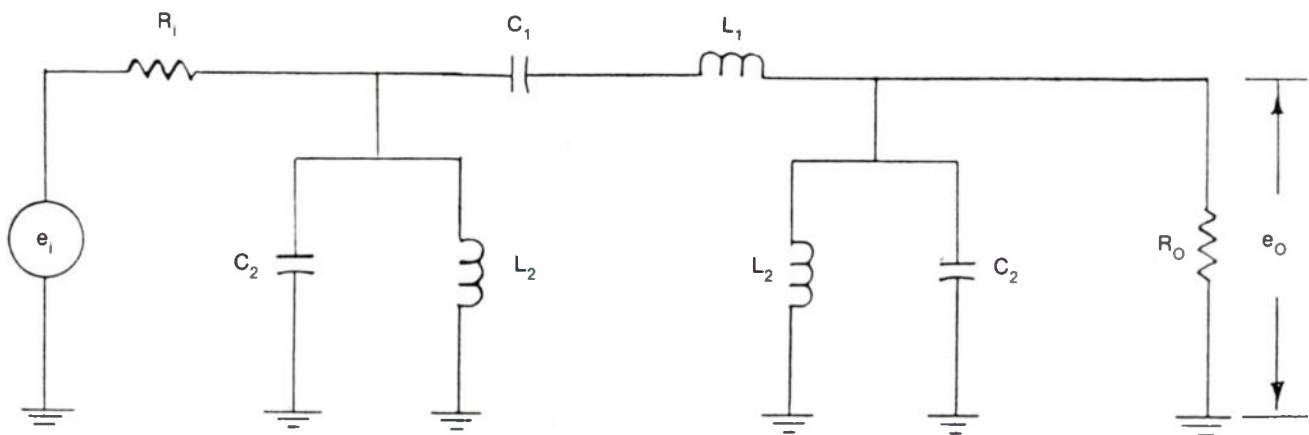


Figure 1. Triple Tuned Circuit

The calculated circuit values are:

$$\begin{aligned} L_2 &= 3.91 \times 10^{-4} \text{ H} \\ L_1 &= 5.88 \times 10^{-4} \text{ H} \\ C_2 &= 5.39 \times 10^{-8} \text{ F} \\ C_1 &= 3.59 \times 10^{-8} \text{ F} \end{aligned}$$

The frequency response can then be calculated and the plot is shown in Figure 2. (Use SF 00 for the PRPLOT routine).

The 3 dB points are at 22 KHz and 56 KHz. This can be compensated for, if necessary, by changing f_1 and f_2 accordingly and recalculating the values of L_1 , L_2 , C_1 and C_2 . The calculated response at geometric center is -2.8 dB. The actual value, using lossless inductors should be -2.5 dB (20 log 75/100); thus about 0.3 dB is lost in the inductors due to their finite Q. □

References

1. A.B. Przepelski, "Double Tuned Circuits", r.f. design, Jan/Feb 82.
2. A.B. Przepelski, "Low Impedance Double Tuned Circuit", r.f. design, May/June 82.
3. F.E. Terman, "Radio Engineers' Handbook", McGraw-Hill Book Co., NY, 1943, p. 231.

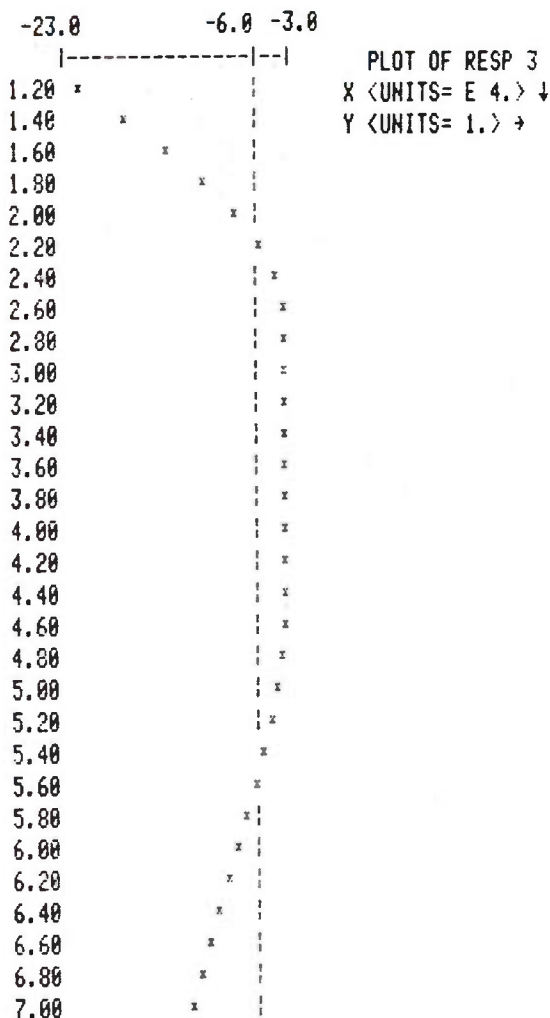


Figure 2. Frequency Response.

```

01*LBL "CIRAT 3"
02 RCL 02
03 RCL 01
04 -
05 STO 03
06 RCL 17
07 *
08 RCL 01
09 RCL 02
10 *
11 SORT
12 -
13 RCL 16
14 *
15 2
16 /
17 PI
18 /
19 RCL 17
20 /
21 RCL 01
22 /
23 RCL 02
24 /
25 *L2= "
26 ARCL X
27 AVIEW
28 STO 12
29 STOP
30 2
31 *
32 PI
33 *
34 RCL 02
35 RCL 01
36 +
37 2
38 /
39 *
40 RCL 17
41 *
42 STO 08
43 RCL 16
44 *
45 RCL 08
46 RCL 16
47 +
48 /
49 STO 09
50 PI
51 /
52 RCL 03
53 /
54 *L1= "
55 ARCL X
56 AVIEW
57 STO 14
58 STOP
59 RCL 09
60 RCL 03
61 *
62 2
63 *
64 PI
65 *
66 1/X
67 *C2= "
68 ARCL X
69 AVIEW
70 STO 13
71 STOP
72 RCL 03
73 4
74 /
75 PI
76 /
77 RCL 01
78 /
79 RCL 02
80 /
81 RCL 09
82 /
83 *C1= "
84 ARCL X
85 AVIEW
86 STO 15
87 END

```

Table I.

```

01*LBL "RESP 3"
02 FS? 00
03 GTO 00
04 *F=? "
05 PROMPT
06 ARCL X
07 AVIEW
08*LBL 00
09 2
10 *
11 PI
12 *
13 STO 19
14 RCL 13
15 *
16 CHS
17 RCL 19
18 RCL 12
19 *
20 STO 21
21 1/X
22 +
23 STO 20
24 1/X
25 RCL 16
26 1/X
27 RCL 21
28 RCL 17
29 *
30 STO 21
31 XEQ 03
32 STO 24
33 X<Y
34 STO 25
35 RCL 16
36 /
37 STO 23
38 X<Y
39 RCL 16
40 /
41 STO 22
42 RCL 25
43 RCL 15
44 RCL 19
45 *
46 1/X
47 -
48 RCL 14
49 RCL 19
50 *
51 STO 25
52 +
53 RCL 24
54 RCL 25
55 RCL 17
56 /
57 +
58 STO 26
59 X<Y
60 STO 27
61 X<Y
62 R-P
63 1/X
64 P-R
65 1/X
66 X<Y
67 RCL 20
68 +
69 1/X
70 X<Y
71 1/X
72 RCL 21
73 XEQ 03
74 STO 24
75 X<Y
76 STO 25
77 X<Y
78 RCL 27
79 RCL 26
80 XEQ 01
81 RCL 23
82 RCL 22
83 R-P
84 X<Y
85 XEQ 02
86 RCL 24
87 RCL 18
88 +
89 RCL 25
90 X<Y
91 XEQ 01
92 R-P
93 RCL 16
94 *
95 LOG
96 20
97 *
98 FS? 00
99 RTN
100 *RESP= "
101 ARCL X
102 *F DB= "
103 AVIEW
104 ADV
105 RTN
106*LBL 01
107 R-P
108 1/X
109 X<Y
110 CHS
111*LBL 02
112 RDN
113 RDN
114 R-P
115 RT
116 *
117 RDN
118 +
119 RT
120 P-R
121 RTN
122*LBL 03
123 1/X
124 +
125 1/X
126 X<Y
127 1/X
128 X<Y
129 1/X
130 P-P
131 1/X
132 P-R
133 RTN
134 .END.

```

Table II.

REGISTERS

R01
R02
R16
R17

SIZE 018

REGISTERS

R12
R13
R14
R15
R16
R17
R18

SIZE 028

Note: Set flag 00 for PRPLOT



Portable DC Magnetometer

The Electro-Mechanics Company is introducing their 6701 DC Magnetometer to fulfill a renewed interest in the EMI/RFI industry for a convenient and versatile magnetic field testing instrument.

Battery powered with rechargeable batteries, the 6701 is lightweight (7 lbs.) enough to be used in the field. It also performs with such high precision and reliability that the 6701 is ideal for the test lab.

The Application

Increasing applications of micro-electronic technology is compounding the problems in electromagnetic interference (EMI). A great many of these difficulties are caused entirely by magnetic field radiation. The interference problems are compounding due to several factors: the increasing use of semiconductor devices in power switching applications, the trend toward miniature high density circuitry, high susceptibility of solid state components, and the general increase in sensitivity of new electronic systems. Many of the interfering fields are of an impulse nature and therefore contain a wide band of frequencies. Other problems may originate from low frequency magnetic phenomena by either inducing a current for circuit perturbation or by Hall effect perturbations within semiconductor junctions. A solution to these problems involves identifying the levels and sources of the interfering magnetic fields. This requires the use of an instrument which can measure a broad frequency range of low level magnetic fields.

Magnetometers are normally thought of as being very low frequency devices whose greatest use is to measure small variations in the earth's magnetic field. Although several types of magnetometers are available, rarely have they been developed for directional broadband low intensity pulse measurements and consequently, most instruments are not suitable for this type measurement. Many of the available instruments are incapable of being extended to broad frequency usage due to both theoretical and practical limitations.



The Instrument

The variable- μ magnetometer developed by the Electro-Mechanics Co. is based upon a principle significantly different from other magnetometers. Many of the desirable characteristics for a new approach to low frequency EMI are exhibited by the variable- μ technique.

The variable- μ magnetic sensor and receiver system called a Magnetic Field Intensity Meter or by its acronym MFIM is an instrument capable of measuring time varying magnetic fields from 1 Hz to 50 KHz. The sensor portion of the instrument is reasonably compact so that it may be placed close to small electrical components. The characteristics of being directionally sensitive (a cosine pattern about the sensor's axis) plus its compactness makes the instrument quite useful for identifying a source of a magnetic field.

Unlike most magnetic field sensor systems which can measure directional, time varying fields, the MFIM has a flat output independent of frequency. The instrument is a broadband receiver whose output is flat from the low to high frequency cut-

off points. Broadband sensitivity of the instrument is approximately 300 picoteslas. Narrowband operation can be accomplished through the use of external filtering at the analog output of the receiver. Such filtering makes possible narrowband sensitivities of less than 100 picoteslas and with a dynamic range greater than 80 dB.

EMI Effects

Practically any electronic circuit subjected to time varying magnetic fields will have its operation influenced by the field. The influence which causes interference of the normal operation of the circuit may vary from a slight modulation of the output of the circuit to a complete degradation of the circuit operation. In the case of a very strong field, large voltages and currents may be induced into the circuitry and cause damage or destruction of the more sensitive components in the circuit. Current surges can cause thermal damage at points of high thermal inertia (poor heat dissipative characteristics), but the current path must have low resistance for the development of this type of damage. The greatest danger likely to affect a

solid state device is a semiconductor junction puncture produced from induced voltages which exceed the peak voltage rating of the junction. A damaging high voltage induction is more often produced by a high intensity magnetic field, but it can also be generated by relatively low level fields which change intensity rapidly.

Consideration has been given to damage and destruction of components brought about by high intensity magnetic fields or fields of rapidly changing levels; however, low level audio frequency fields are often all that is needed to disrupt proper operation of a solid state electronic circuit. Errant triggering of a digital microcircuit may cause a computer to malfunction or cause failure of a microcircuit control system. Failures caused by low level magnetic signals are, by far, the most prevalent and most overlooked problem sources in high density microelectronics. The proper architecture of component layout becomes as much of an art as an engineering task in high density electronics. The methods of reducing magnetic coupling, a spatial configuration, or the proper use of shielding materials can become as important as the intricacies of circuit design and function.

Integrated circuits can be affected by magnetic fields in several ways. Most IC semiconductors contain several types of components which are influenced by magnetic fields. These include Hall effect properties and magnetoresistive properties although the most prominent mode is loop coupling as developed in Faraday's law.

Although the level of induced voltage is proportional to the frequency of the interfering signal, it is fortunate that with nearly any shielding material, the shielding effectiveness of the shield increases with the increase in frequency.

Magnetic Field Measurement

It can be seen that miniature, high density electronic circuitry is susceptible to failure of operation or damage through the action of exposure to magnetic fields. The source of these fields needs to be found and measured in order that engineers can avoid problems in design before the problem surfaces.

The variable- μ magnetic field intensity meter is an instrument, developed by the Electro-Mechanics Co., which can detect levels and direction of the source of an interfering magnetic field in the ELF band from 1 Hz to 50 KHz.

Contact Mike Hart, Electro-Me-

PTS SYNTHESIZER FLEXIBILITY



**RANGE, INTERFACE
CABINET, ATT'R
EXTRA OUTPUTS**



PTS 160

PTS 200

**More basic performance per dollar . . .
and more options to meet your specifications**

	PTS 160/200	FLUKE 6160B	WAVETEK ROCKLAND 5600
160 MHz or 200 MHz	✓	NO	NO
Built-in GPIB or par. program	✓	NO	NO
Optional Resolution 0.1 Hz — 100 KHz	✓	NO	✓
Metered Output	✓	NO	NO
20 μ s Switching	✓	NO	✓
99 dB programmable Attenuator	✓	NO	NO

Price: PTS160, 1 Hz Res, Rem. only, TCXO, \$4,625.00 — (Sample)

PTS
FREQUENCY SYNTHESIZERS

PROGRAMMED TEST SOURCES, INC.
BEAVERBROOK RD., LITTLETON, MA 01460
(617) 486-3008
INFO/CARD 20

chanics Company, P.O. Box 1546, Austin, Texas 78767, (512) 835-4684, or INFO/CARD #140.


EMI Broadband Filters

U.S. Capacitor Corporation has introduced a comprehensive line of sub-miniature broadband EMI filters which are designed to meet or exceed applicable sections of MIL-F-28861 and MIL-F-15733 for high reliability.

Available in both solder-in and screw body filter styles, the line includes the most commonly used sizes and configurations and introduces a new high temperature series. Contact Donald F. Hosmer, 11144 Penrose Street, Sun Valley, CA 91352. (213) 767-6770, or circle INFO/CARD #139.

Silicone Elastomer For EMI Shielding

TECKNIT, recently announced the addition of a new silicone elastomer to its EMI Shielding product line. The new product, CONSIL-C, is a conductive elastomer filled with silver-plated copper particles, which achieves high-performance electrical conductivity and provides high-broadband shielding effectiveness. The product additionally provides moisture sealing for enclosure joints and seams. TECKNIT will manufacture its new CONSIL-C in the forms of sheets and die-cut flat gaskets as well as standard rectangular, round and cross-sectional strips. Strips and strip formed gaskets can also be provided with vulcanized joints to provide effectively continuous strip

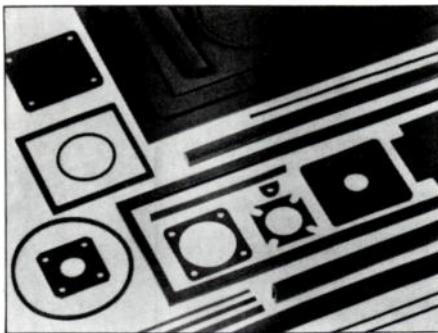

lengths and finished gasket shapes. Contact Peter Grant, EMI Shielding Products Manager, TECKNIT, 129 Dermody Street, Cranford, NJ, (201) 272-5500, or circle INFO/CARD #138.

EMI Testing Service

Stanford Applied Engineering announces that full EMI testing services are now available to equipment manufacturers. The new testing laboratory offers certification testing to FCC Docket 20780 regulations, thus assuring the equipment manufacturer of complete FCC compliance. Documented FCC compliance is guaranteed. Stanford Applied Engineering, 3520 De La Cruz Blvd., Santa Clara, CA 95050, (408) 988-0700, or please circle INFO/CARD #135.

EMI And RFI Enclosures

EMI and RFI Shielding to satisfy new FCC and MIL-STD requirements is available, as a standard option, on plastic electronics enclosures from PAC-TEC Corp. Subsidiary of LaFrance

Corp. Anticipating increased regulation of EMI and RFI, particularly in light of the economies offered by Plastics over metals in enclosure costs, PAC-TEC has thoroughly studied various shielding methods and now employs conductive coating applied to enclosure interiors. The coatings include applications of nickel, silver and graphite in various thicknesses. PAC-TEC Corp., Enterprise and Executive Avenues, Philadelphia, PA 19153 U.S.A.: (215) 365-8400, or circle INFO/CARD #137.

Conductive Epoxies For EMI Shielding

Key Polymer Corporation, has announced that its Marpoxy™ copper-filled conductive epoxy resins have passed Military Standard MIL-STD-461B for EMI (electromagnetic interference) shielding. The epoxies offer excellent shielding effectiveness over the frequency range from 150 KHz to 100 GHz, with attenuations from 65 dB to 76 dB. Key Polymer Corp., Jacob's Way, Lawrence Industrial Park, Lawrence, MA 01842, (617) 683-9411, or circle INFO/CARD #134.

Thermally Conductive Copper Filled Adhesive Film

A glass supported, copper filled epoxy adhesive film has been developed as a less expensive alternative to silver filled adhesive systems by Ablestik Laboratories. Ablefilm® ECF550C provides the highest thermal conductivity of all the ABLESTIK adhesive films,


LOW COST, Multi-Stage IF/RF Modular Amplifiers, Satisfy MIL-STD-883B.

MODEL	TM-7201	TM-7202	TM-7203
Frequency:	5-250 MHz	5-250 MHz	5-250 MHz
Gain, Min:	28 dB	26 dB	28 dB
Gain Flatness:	± 0.7 dB	± 0.7 dB	± 0.7 dB
Noise Fig., Max:	5 dB	6 dB	3.5 dB
1 dB CP min:	+ 7 dBm	+ 15 dBm	+ 7 dBm
VSWR:	2:1	2:1	2:1
DC @ + 15VDC	35	85	35
Price: 1-9	\$22	\$30	\$25

• Guaranteed specifications • Other amplifiers to 1 GHz • High Reliability • TO-8 package

Amplifonix

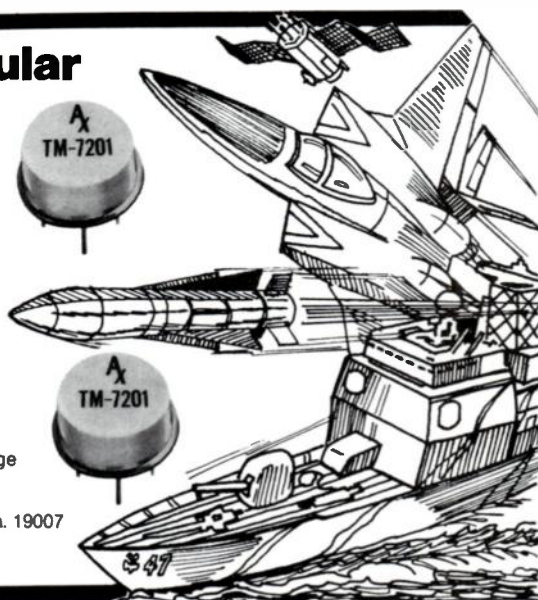220 Route 13, Bristol, Pa. 19007
(215) 788-2350



INFO/CARD 21


making it ideal for substrate attach and heat sink bonding. In shielding applications, ECF550C provides electrical conductivity equal to silver at a significant cost savings. **Ablestik Laboratories, 833 West 182 Street, Gardena, CA, 90248 or circle INFO/CARD #136.**

TEM Cell

Two models of transverse-electromagnetic-mode (TEM) cells are now available from Amplifier Research. Models TC0250 and TC0500 are designed for rf testing of smaller objects within the frequency ranges of dc-250 MHz and dc-500 MHz respectively. Price for the TC0250 is \$6600. For the TC0500, \$5500. Delivery: 90 days ARO. **Amplifier Research, 160 School House Road, Souderton, PA 18694. 215-723-8181, or circle INFO/CARD #133.**

High Power 900 MHz Transistors

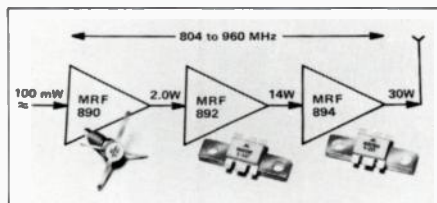Motorola has introduced a new 24 Vdc, 900 MHz power transistor series. The new line includes the MRF 890, a 2.0 watt, 9.0 dB minimum gain pre-driver, the MRF 892, a 14 watt, 8.5 dB driver, and the MRF 894, a 30 watt, 7.0 dB final amplifier. The new RF transistors are fully characterized across




the 804 to 960 MHz frequency range and are intended for large-signal, common-base amplifier applications in industrial and commercial cellular FM radio-telephone equipment, which was recently approved by the FCC. All devices have guaranteed gain performance at 900 MHz, collector efficiencies of 55% minimum, and will withstand 30:1 VSWR load mismatch at rated output power and voltage supply. Sampling is now taking place with approximately 8 to 12 weeks delivery. Prices in 100-499 pc. qty., MRF 890-\$10.00, MRF 892-\$19.55, MRF 894-\$30.60. **Contact Tom Bishop, Motorola Semiconductor Products Inc., P.O. Box 20912, Phoenix, Arizona 85036, (602) 244-6394 or circle INFO/CARD #132.**

Miniature RF Coaxial Connector Kit

E.F. Johnson Company, Waseca, MN announced the introduction of its
(Continued on page 46.)

TUNEABLE MOLDED COILS

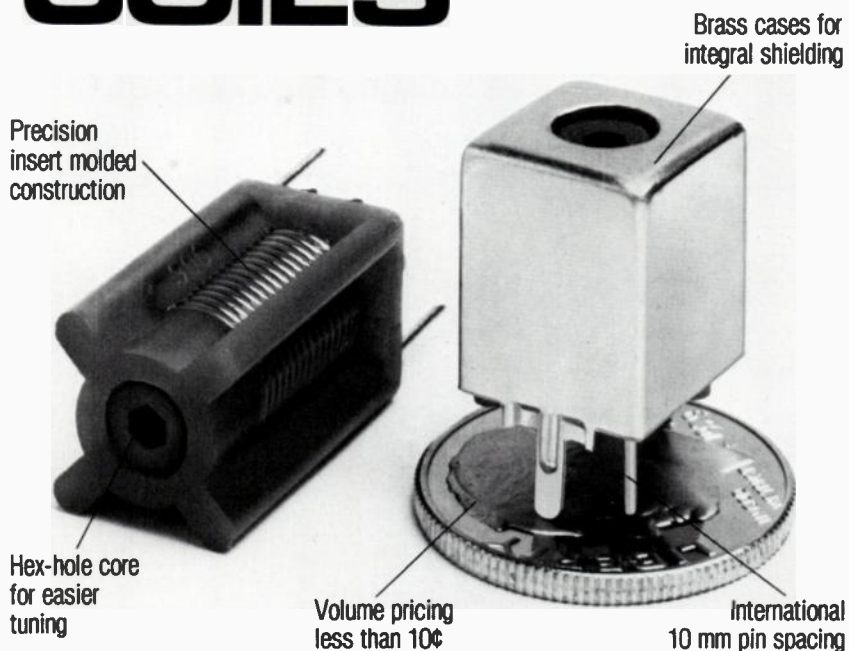

Our new Uni-10 coils give you the compactness of a 10 mm coil with the low drift reliability of an insert molded coil.

Windings are precision molded into a single piece of polypropylene for mechanical and electrical stability.

The Uni-10's hex-hole tuning core is easier to tune than slotted cores.

And optional brass shield cans give you integral shielding and additional mounting stability.

Typical Uni-10 applications include IF coils, RF coils, oscillators and chokes.


SPECIFICATIONS:

Inductance 0.060-0.915 μ H
Typical Q 90 @ 40 mHz
Frequency typically used at 25 mHz and up

Coilcraft

Cary, Illinois 60013 • 312/639-2361

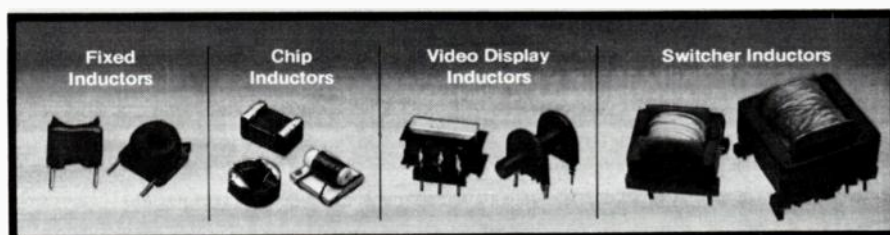MAKERS OF A FULL LINE OF INDUCTIVE DEVICES



INFO/CARD 22



Win a
\$1,000

U.S. Savings Bond

Pick the top 5 full page or larger advertisements and the top 5 fractional page advertisements in this issue.

Reader Contest Rules

- Examine this issue of *r.f. design* carefully. Pick the ten advertisements you think your fellow engineers-subscribers will best remember.
- List them on the entry form in this issue. Every entry form must be filled in completely or it will not be considered.
- To enter, readers must be engaged in or supervising design activities or involved in component specification/selection for design activities.
- Contest void where prohibited or taxed by law. Liability for any taxes is the sole responsibility of the winner.
- In case of a tie, the earliest postmark will determine the winner. Decisions of the reader contest judges will be final.

MEMORY PHONE™ III

The telephone
that's an
automatic
dialer, too.

Reliable Electronic Components. Micro-processor chip design for dependable, trouble-free performance.

Battery Backup supplies power in the event of electrical failure or if you move Memory Phone III to another location. No need to reprogram numbers.

Memory Phone™ III combines a compact telephone with an automatic dialer. Stores up to 24 phone numbers. Saves monthly phone rental charges.

Dial Mode Switch. Memory Phone III gives you push-button convenience with either rotary or tone dialing system.

Last-number-dialed Memory. One-button redial of a busy phone number.

13-24 Button. Use to program or retrieve stored numbers 13-24.

LED Hold Indicator. Lights when the Hold button is engaged.

On/Off Switch. To hang up, just place Memory Phone III face down on any flat surface.

Line Powered. Coiled cord plugs directly into any phone outlet. No additional cords or power packs necessary.

Wall Mountable. Keeps Memory Phone III out of the way and convenient.

Magic Touch™ Dialing Pad. Push-button convenience for dialing, programming, and recalling numbers.

Save Button. Press and store any number for later retrieval.

Hold Button disconnects mouthpiece mike so caller can't hear you. Gives you privacy without covering mouthpiece with your hand.

Dial Button. Press to retrieve and automatically dial stored numbers.

Electronic Tone Ringer. Pleasant sounding.

To order, please send check or money order for \$79.95 to:
Mountain Region Associates
3560 S. Lincoln
Englewood, CO 80110

Name _____

Address _____

City, State, Zip _____


Colorado Residents add sales tax.

(Continued from page 41.)

JCM Miniature RF Coaxial Kit. The kit contains 5 pieces each of 9 popular styles of Gold Plated Miniature RF Coaxial Connectors. All 45 pieces are housed in a handy 9 drawer plastic cabinet. Complete assembly instructions are enclosed in each drawer. All connectors are 50 ohm type and the Plug and Jack assortment covers the major cable group sizes—RG-178, RG 196, RG-174, RG-188, RG-316, RG-55, RG-58, RG-141, RG-142, RG-233. The complete kit is OEM priced at \$98.40 and is available through the nearest Johnson Distributor. **E.F. Johnson Company, 299 10th Ave., S.W., Waseca, MN 56093, (507) 835-6222, or circle INFO/CARD #131.**

Wideband Current Probe

The Model 711 Miniature Wideband Current Probe measures wideband current or pulses without loading the circuit being tested. It induces no appreciable capacitive nor inductive effects on circuitry, therefore the signal under measurement does not change. Being 20 times smaller than other commercially available devices, it requires no additional lead length for insertion and, therefore it does not alter circuit performance. The 711

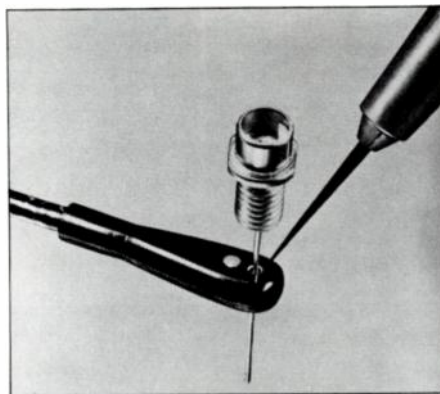

exhibits only .02Ω shunted by 4μh insertion impedance. The current is sensed by placing the conductor through the center of the probe, which will accept a maximum lead diameter of #20 AWG. Typical applications include: current measurement in high frequency amplifiers, drive circuits for LEDs and lasers, electro-magnetic devices (deflection coils), energy storage devices, and SCR gate drivers. The 711 is used in any field requiring the accurate measurement of current up to 100 amps with Ampere-Sec. products of less than 6A-μs. **American Laser Systems Inc., 106 James Fowler Rd., Santa Barbara Airport, Goleta, CA 93117, (805) 967-0423 or circle INFO/CARD #130.**


S Parameter Design Program

Gamma Electronics Inc., announces that it will market several of its' design and analysis computer programs. The first program to be offered is called SPAMO (S Parameter Analysis and Manual Optimization). The program runs on a low cost computer requiring only 32 K of memory and a single disk drive. The program contains several unique features: direct or computed S parameter data entry, easy topology entry (R/L/C, node #, node #, value), add additional elements and nodes at any time as well as changing component types and values, execution time of approximately 20 seconds per frequency. The manual that is supplied with the program provides several step by step examples. One example starts with a "bare" transistor then adds and modifies components to obtain a final design which has a gain of 11 dB minimum from 50 to 1000 Mhz, a flatness of ±0.05 dB and an input/output VSWR of 1.6:1 maximum. **Gamma Electronics Inc., 6223 Edgewater Dr., Falls Church, VA 22041, (703) 820-7741 or INFO/CARD #129.**

Solid State Dip Meter

A solid state dip meter for testing radio frequencies, antennas, oscil-

HF/VHF JFET RF AMPLIFIER

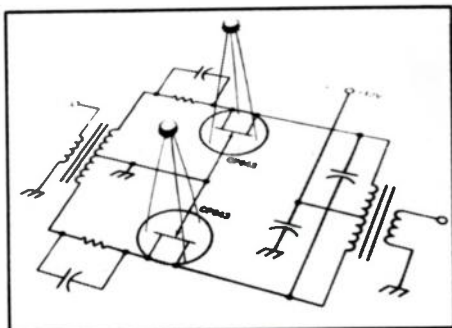

Use the low noise, wide dynamic range CP643 in applications through 500 MHz. The versatile device has a g_m of 25,000 μmhos @ 25 mA IDS, and makes an ideal IF preamp, presenting a constant 50 Ohm input impedance over 1 to 108 MHz range, a near-perfect termination for diode double-balanced mixers. Other applications are: receiving multicouplers, high purity oscillators, active mixers, RF and IF amplifiers.

**TELEDYNE
CRYSTALONICS**

147 Sherman St. Cambridge, MA 02140
Tel. (617) 491-1670 • TWX: 710-320-1196

INFO/CARD 24

LMI shielded rooms. Your best investment.

"See us,
EMC Int'l. Sym.
Sept. 8, 9, 10."



Clamp-together Shielded Rooms

- Prefab. modular, demountable.
- Excellent RF attenuation.
- Unequalled structure rigidity and electrical circuit integrity.
- Easy to assemble and relocate.


All-welded Shielded Rooms

- Super RF attenuation.
- Supplied for NSA 65-5 and other secure specs where 100 to 120 db shielding is required from 1.0 to 10 KHz, to 10 GHz and higher.
- Meet storage and vault needs.
- Ask for catalog LSR-1000.

RF Shielded Anechoic Chambers

Plus these LMI benefits

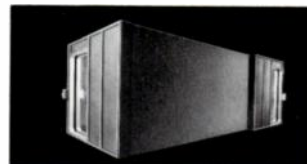
- Complete turnkey facilities by nationally known EMI engineers.
- Specifications design and engineering services.
- Registered professional engineers; licensed contractors.
- After-sale service; long-term upgrading.
- Ask for catalog LDC-500.




To discuss your needs call or write Fred Nichols, LectroMagnetics, Inc. 6056 West Jefferson Blvd. Los Angeles, CA 90016 (213) 870-9383

LMI  **LectroMagnetics, Inc.**


INFO/CARD 25

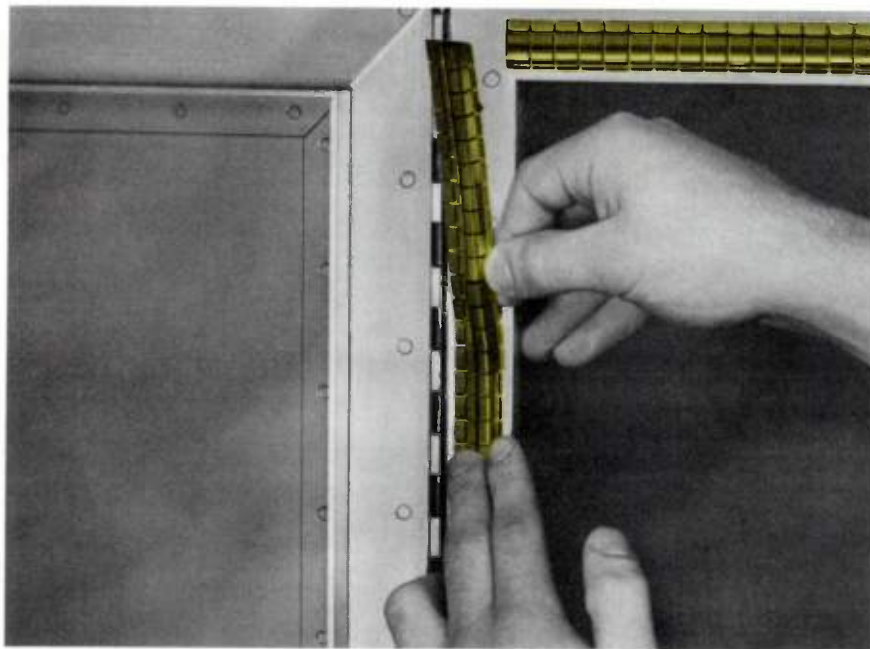


Series 541
.380" wide

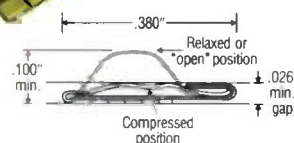

Series 521
.512" wide

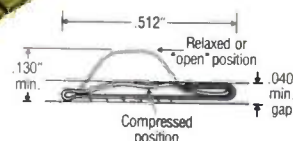

Series 515
.760" wide

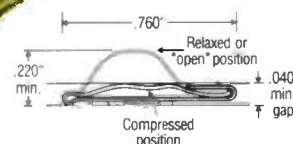

New *stickn fingers*® design resists damage, provides superior RFI/EMI shielding!

Now! Sticky-Fingers beryllium copper shielding gaskets have been made even better! A special, U-shaped end permits the upper part of the strip to slide when enclosure doors are closed, protecting against accidental damage to the strip's fingers.

Three models provide you a choice of widths to suit your application. As with all Instrument Specialties Sticky-Fingers shielding strips, they attach quickly and securely with a *really* sticky self-adhesive strip. You simply peel off the backing, press the strip to the surface selected, and it's there to stay!

At the same time, you get the same high shielding effectiveness offered by all Sticky-Fingers...
attenuation of more than 102 dB at 10 GHz plane wave,
and 71 dB at 14 kHz magnetic.

Complete information on these new strips, as well as the complete line of Sticky-Fingers shielding strips is available free. Write today to Dept. RF-4.



INSTRUMENT SPECIALTIES COMPANY, INC.

Delaware Water Gap, PA. 18327

Phone: 717-424-8510 • TWX: 510-671-4526

Specialists in beryllium copper since 1938

INFO/CARD 26



lators, RF chokes, and etc., formerly manufactured by Millen, is available from Caywood Electronics, Inc. The Millen Solid State Dipper is a portable oscillating frequency meter that determines the resonant frequency of de-energized resonant circuits with an accuracy of $\pm 2\%$. Covering a range from 1.65 to 310 MHz with 7 plug-in coils, it also features an absorption-type wavemeter with the oscillator circuit acting as a Q multiplier amplifier to enhance tuning response and dip sensitivity. The Millen Solid State Dipper is priced at \$210 each, complete with 7 coils and case. **Contact Wade Caywood Electronics, Inc., P.O. Drawer U, Malden, MA 02148-0921, (617) 322-4455, or INFO/CARD #127.**

SAW Filter

RF Monolithics, Inc., has announced a new clean-up filter to eliminate the adjacent channel interference which results from certain combination of TV receivers and cable converters. Called the CTVF-3, the filter is fully matched, SAW stabilized and carries an insertion loss of less than 5 dB. It is priced at \$16.25 in quantity. **RF Monolithics, Inc., 4441 Sigma Rd., Dallas, Texas 75234, (214) 233-2903 or circle INFO/CARD #126.**

New Literature

EMI Consultant Service Brochure

R & B Enterprises, long a leader in EMI testing, consulting, publications, and related training, announces a new brochure which details its comprehensive services. **R & B Enterprises, 1050 Colwell Lane, Conshohocken, PA 19428. (215) 828-6236 or circle INFO/CARD #107.**

EMI Shielding Design Guide

TECKNIT, announces the availability of a complete reference source that provides design engineers with up-to-date, state-of-the-art information for dealing with the increasing demands of EMI shielding problems. The 75-page TECKNIT publication systematically addresses the design criteria involved in the area of EMI shielding. A detailed tutorial reference for those unfamiliar with the selection and application of EMI shielding materials, the guide is organized into ten (10) convenient sections. Each section covers a specific topic in sufficient detail to provide readers with information on

subjects ranging from "Metal Shielding Barriers" to "Shielding Performance Testing" and "Procurement." The TECKNIT Design Guide is available for \$10.00. To obtain your copy, **contact Robert E. Bilby, Manager Corporate Communications, TECKNIT, 129 Dermody Street, Cranford, NJ (201) 272-5500.**

55-85 MHz 75 Ohm Amplifier Application Note

California Eastern Laboratories, Inc., offers new Application Note AN82302 titled "A 55-85 MHz 75 OHM AMPLIFIER USING TWO NE74114 BIPOLAR MICROWAVE TRANSISTORS." This 70 MHz IF amplifier can be used in many different systems applications, including a TVRO front end. **California Eastern Laboratories, Inc., 3005 Democracy Way, Santa Clara, CA, 95050, (408) 988-3500, or circle INFO/CARD #105.**

Microwave Transistor Selection Guide

A new microwave transistor selection guide is now available. **Motorola Semiconductor Products Inc., P.O. Box**

QUALITY ISN'T A MIRACLE.

And it shouldn't be. At Sentry, quality is a daily commitment—not an occasional miracle. Which is why Sentry consistently produces the highest quality crystals available.

Each crystal is hand-crafted of flawless materials to exceed MIL-Spec standards. To insure quality, the crystals are X-rayed, lapped, plated with precious metals, sealed in an inert atmosphere and pre-aged to prevent drifting.

Reliability isn't a miracle, either. It's Sentry's usual way of business. We stand behind the quality of every crystal.

Call us TOLL FREE, 1-800-654-8850 for quality service. We deliver in five working days to two weeks, plus 48-hour emergency service.

Sentry

Crystal Park, Chickasha, Oklahoma 73018

* Please allow for extra time for precision, UHF and special frequencies.

INFO/CARD 27


PROBLEM: EMI SUPPRESSION

SOLUTION: CAPCON 'LOSSYLINE' FLEXIBLE FILTER WIRE

The Capcon "LossyLine" FLEXIBLE FILTER is an absorptive/dissipative low-pass microwave filter. It eliminates undesired harmonics, EMI, and other types of spurious microwave energy. Provides over 100db attenuation in the microwave ranges from 10 MHz to over 45 GHz.

- 1 mA to 50 A
- 10 to 100,000 volts
- -67° to $+250^{\circ}\text{C}$
- 0.5" minimum bend, radius

Send For Full Information

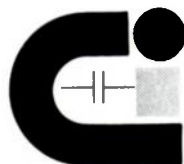

CAPCON® INC.

147 West 25th Street
New York, N.Y. 10001
Phone: (212) 243-6275

INFO/CARD 28

20912, Phoenix, AZ 85036, (602) 244-6900, or circle INFO/CARD #104.

Automatic Power Meter Calibrator Brochure

A new 12 page brochure describing the unique System II Automatic Power Meter Calibrator has just been released by Weinschel Engineering. It demonstrates how System II can complete power meter calibration tasks in minutes providing accurate, cost effective calibration of terminating power meters (even by semi-skilled

personnel) at a rate of 1.5 seconds per point with typical accuracies of less than 1% above those available directly from the National Bureau of Standards including mismatch uncertainties. **Weinschel Engineering, One (1) Weinschel Lane, Gaithersburg, MD 20877. (301) 948-3434 or INFO/CARD #106.**

Eimac Cavity Amplifiers

Eimac, a division of Varian Associates, describes its complete line of cavity amplifiers designed for FM, TV and UHF broadcast service in a new 14-page brochure. **Varian Associates,**

EIMAC Division, 301 Industrial Way, San Carlos, CA 94070, (415) 592-1221, or circle INFO/CARD #102.

Instrument Catalog

The latest full-line instrumentation catalog from Marconi is now available. This 176 page book is of particular interest to signal generator users, as it includes complete details of both the new cavity tuned 2017 generator and the 2018/2019 synthesizers. **Marconi Instruments, 100 Stonehurst Court, Northvale, N.J. 07647, (201) 767-7250, or INFO/CARD #101.** □



Professional Program Order Form

Please send me the following *Wescon/82* Professional Program Session Records. Each Session Record is \$5.
No. Title

- ☐ 1. Servicing Microprocessor Equipment
- ☐ 2. UNIX-Based Systems for Process and Laboratory Control
- ☐ 3. Development Systems for Custom and Semi-Custom Circuits
- ☐ 4. Microcomputer Controlled Robots
- ☐ 5a. Single-Chip Microcomputer Programming
- ☐ 5b. CMOS Single-Chip Microcomputers
- ☐ 5c. Single-Chip Microcomputer Hardware
- ☐ 6. Equipment Cooling Considerations
- ☐ 7. Digital Gate Arrays - Part I
- ☐ 8. Effective Logic Analysis Techniques for Increased Design Productivity
- ☐ 9. Implementing an ECL Design - Devices and Circuit Board Alternatives
- ☐ 10. Digital Gate Arrays - Part II
- ☐ 11. Designing Plastic Packages for Optimal Electromagnetic Compatibility
- ☐ 12. 16-Bit Microprocessor Systems: The Third Generation
- ☐ 13. Microelectronics Education - The U.K. Experience
- ☐ 14. Semi-Custom Analog Capabilities
- ☐ 15. The Engineering Workstation: The Third Generation CAD Tool
- ☐ 16. Advanced System Architecture Concepts For 16-Bit Microprocessors
- ☐ 17a. Standard Programming Languages and the Portability Problem
- ☐ 17b. High Level Languages in Single-Chip Computers
- ☐ 17c. Systems Software in FORTH
- ☐ 18. Alternatives to Gate Arrays in Custom Design
- ☐ 19. Human Engineering in Electronic Design
- ☐ 20. Advanced Peripherals for the New Generation of 16/32-Bit Systems
- ☐ 21. New Developments in Programmable Logic
- ☐ 22. Built-In Test (BIT) and Fault-Tolerance for Military Computers
- ☐ 23. Modern Components Design for the '80s
- ☐ 24. (To be determined)
- ☐ 25. Components for Digital Audio Applications
- ☐ 26. Real-Time Signal Processing Using Integrated Optics Technology
- ☐ 27. IC Solutions for Data Communications Applications
- ☐ 28. Microprocessor Software: Make or Buy?
- ☐ 29. Design Process for an Automatic Speech Recognition (ASR) Based Solution
- ☐ 30. High Speed A/D Conversion
- ☐ 31. Electronics Media Public Relations: The Hows and Whys
- ☐ 32. Computing Without Programming
- ☐ 33. Developments in Video Display Controllers
- ☐ 34. Trends in the Design and Application of Digital Signal Processors

TOTAL Session Records @ \$5 ea. = \$

(In USA) - Plus \$2 Mailing Charge = \$ 2.00

(Outside USA) - Plus \$4 Mailing Charge = \$ 4.00

Total Cost = \$

Make check payable to **Wescon**
and mail with this form to:

**Wescon
P.O. Box 92275
Los Angeles, CA 90009**

Date _____

Name _____

Firm _____

Street Address _____

City, State, Zip Code _____

GET 10 TIMES MORE RFI PROTECTION WITH A LINDGREN "DEI" SCREEN ROOM

Lindgren's double-electrically-isolated (DEI) screen rooms offer 120 dB RF attenuation of electric and plane waves from 14 KHz to 1 GHz... up to 10 times more shielding than any other type of screen room.

This patented design keeps your design/test area interference-free despite rising ambient RFI levels. You get shielding equal to conventional solid-sheet-metal enclosures without sacrificing the see-through, hear-through and lighter-weight advantages of screen.

DEI design is superior because inner and outer screens of 0.011" dia. 22 x 22 bronze mesh are electrically separated, except for a single grounding point. Doors feature separate inside and outside RF seals on all four edges, with a single handle that assures an RF-tight closure by applying cam pressure at three points.

Built of panel modules, Lindgren RF enclosures can be moved, expanded or reshaped easily. Our patented overlapping pressure joints maintain full shielding integrity no matter how many times they're reassembled.

For more details, ask for our technical catalog on RF enclosures.

**LINDGREN
RF ENCLOSURES**
1228 CAPITAL DRIVE
ADDISON, IL 60101
(312) 628-9100

INFO/CARD 29

Classifieds

CLASSIFIED ADVERTISING RATES

(priced by column inch; earned rates available)

ONE TIME RATE: \$90/in. • THREE TIME RATE: \$80/in.

SIX TIME RATE: \$70/in.

Confidential box numbers are available with any ad for \$5.00.

Mail inquiries to *RF Design Magazine*, 6430 S. Yosemite, Englewood, CO 80111, or call Betsy Loeff at (303) 694-1522.

SAN DIEGO CALLING!

Enjoy world-famous attractions, sunny beaches, year' round shirt-sleeves weather. All free with career opportunities at Loral!

RF ENGINEER: Your transmitter and/or Receiver experience with L, S, C bands (plus, hopefully, transponders, digital logic, analog) is your passport to beautiful San Diego!

TECHNICAL WRITER: If you're an Engineer, or Senior Technician, who loves to write—and have a flair for it—we'd like to hear from you. You'll need strong theory in RF (VHF, UHF bands), digital, or video. Supervisory capability desirable. Two years' writing military—level test or EMC procedures gets you top consideration!

Loral Data Systems (Conic) offers an excellent salary/benefits package. Send resume/salary history to Clinton Myer, Personnel. LORAL DATA SYSTEMS, 9020 Balboa; San Diego 92123.

R.F. ENGINEERS

HF Mgr. 70K
Supervise engr design team in 2-30 MHz range

Sr. EE 40K
BSEE - Design receiver systems

Sr. ME 40K
BSME - Package airborne & ground radios

Systems EE 38K
BSEE - Integrate telephone circuits with HF, VHF, etc.

These are a few of many national openings. Please send resume including salary and location preference to Dale Mayhall, Vice President - Engineering.

licensed employment agency since 1952

(219) 424-4466

BONE PERSONNEL, INC.

2008 Fort Wayne Bank Bldg.
Fort Wayne, IN 46802

RF Analog Design Engineer—to \$70K with base salary and performance bonuses. Must have experience in low-power miniature VHF (30-450 mHz) transmitter and receiver design. San Francisco Bay Area based company manufactures wireless microphone, wireless musical instrument, and wireless headset intercom systems. A golden opportunity for an ambitious designer with a rapidly growing young firm.



Nady Systems, Inc.
1145—65th St.
Oakland, CA 94608
(415) 652-2411.

R.F. DESIGN ENGINEERS

Cubic Communications, a leader in HF and VHF communications systems with equipment installed worldwide, is expanding its commercial product line to include a new generation of high performance radio communications products. We are looking for several talented R.F. design engineers to participate in our growth. If you are experienced in the design of one or more of the following areas, we will have an interest in you.

- Receiver and Exciter Circuits
- Frequency Synthesizer Circuits
- Processor Controlled Transceivers
- Solid State Power Amplifiers
- HF Antenna Couplers

We are located in sunny Southern California but away from the smog and congestion of the big cities. We are a small company with the backing of our much larger parent corporation. We offer the usual assortment of fringe benefit packages plus an opportunity to share in our success through our profit sharing plan.

If you are interested, please send your resume and salary history to our Director of Engineering at:



CUBIC COMMUNICATIONS

A Member of the Cubic Corporation
Family of Companies
305 Airport Road, Oceanside CA 92054
An Equal Opportunity Employer

We've found a connection between reliability and economy.



Johnson makes coaxial connectors for all types of applications. For a free catalog, phone (507) 835-6222 or write E.F. Johnson Co., 299 10th Avenue Southwest, Waseca, Minnesota 56093.



JOHNSON

TXW 910-565-2161

E. F. JOHNSON COMPANY, WASECA, MINN. 56093

TLX 290470

Advertiser Index

A.H. Systems	16
Acrian, Inc.	11
Ad-Vance Magnetics, Inc.	14
Amplifonix	40
California Eastern Labs.	26-27
Capcon, Inc.	48
Coilcraft	41
Communications Transistor Corp. ..	18
Communitronics, Ltd.	17
Daico Industries, Inc.	29
Electroline	34
Electro-Metrics	19
Electronic Conventions, Inc.	28
Electronic Navigation Industries ..	52
Gilbert Engineering Co.	7
Glenair Corp.	14
Hughes Aircraft Co.	8
Instrument Specialties Co., Inc.	47
Jerrold Division of General Instruments	35
Johanson Mfg. Corp.	15
E.F. Johnson Co.	50
LectroMagnetics, Inc.	46
Lindgren RF Enclosures	49
Mini Circuits	5
Mountain Region Associates	45
Programmed Test Sources, Inc.	39
R.F. Design	42-43
Sentry Manufacturing	48
Tecknit	3
Teledyne Crystalonics	46
Texscan	25
Wescon	49
Don White Consultants	2, 51
Wide Band Engineering	32

EMC Technology Magazine.

The way we handle interference makes us Number One.

As of January, 1982, EMC TECHNOLOGY MAGAZINE became the top trade journal...world wide...in the fast-growing field of electromagnetic compatibility.

How does a quarterly journal vault from the drawing board to Number One...65,000 readership...even before the first issue is published?

The content is right on target. It meets the *real* needs of people with EMC problems, not the needs of publishers, advertisers (except in the truest sense), or dilettantes.

EMC Technology Magazine is packed with technical articles and papers on EMC problems and solutions; editorial news and views; New Product information; Hands-On reports; even book reviews.

Published by the world's leading experts on EMC. 25 handbooks and thousands of EMC courses and seminars have formed the foundation for EMC TECHNOLOGY MAGAZINE. The editorial staff lists some of the most distinguished educators and technicians in the field.



96 pages of practical technology. The emphasis is on the practical rather than the theoretical, with detailed analyses of EMC design problems and solutions; compliance with FCC, CISPR, MIL-STD-462, etc.; measurements; case histories; components; and on and on.

Each issue will be loaded with usable information. Coming up: special issues on FCC, VDE, and CISPR regs and test procedures; cables and cable connectors; diagnostic testing and field retrofit. Each issue will carry 8 to 12 articles dealing specifically with EMC problems and solutions.

Don't put up with interference. EMC TECHNOLOGY is must reading for every designer, user, or troubleshooter of virtually any type of electronics equipment. Don't miss a single issue of the Number One magazine in the field of electromagnetic compatibility...the magazine that won't sit still for interference! Subscribe today.

INFO/CARD 1

GET THE MOST . . . to solve your EMC needs . . .
Subscribe now to **EMC Technology**

North American Subscribers

- ☐ \$20 for 1 year (4 issues)
- ☐ \$36 for 2 years (8 issues)
- ☐ \$50 for 3 years (12 issues)

All Other Subscribers

- ☐ \$30 for 1 year
- ☐ \$54 for 2 years
- ☐ \$75 for 3 years

- ☐ Payment Enclosed
- ☐ Bill Me
- ☐ Bill My Company

NAME/TITLE _____

COMPANY _____

ADDRESS _____


CITY/STATE/ZIP _____

What is your end product? _____

What products do you purchase? _____

Number of employees in your company? _____

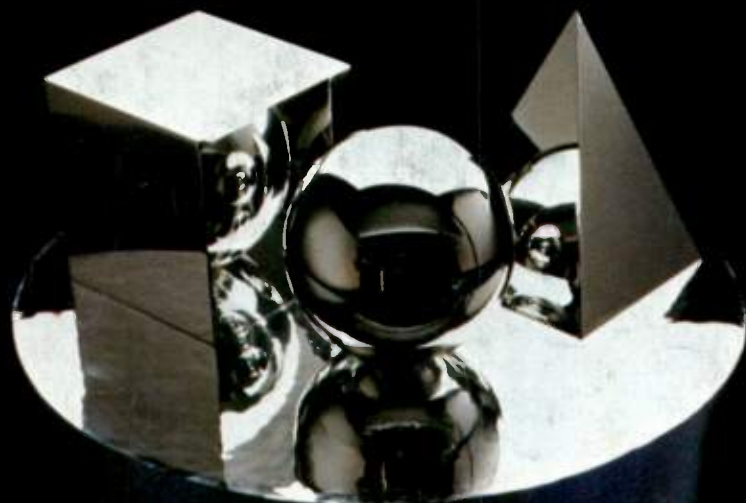EMC TECHNOLOGY State Route 625, P.O. Box D, Gainesville, Virginia 22065 U.S.A. (703) 347-0030



**Wherever you need
100 Watts of RF power
from 10kHz to 400MHz...**



ENI has it covered.

Imagine the tremendous versatility you could enjoy with the extremely wide coverage of just these two broadband power amplifiers.

The ENI 5100L spans the frequency range of 1.5 to 400 MHz with a Class A linear output rating of 100 Watts and a flat 50 dB gain. And it will deliver 200 Watts from 1.5 to 200 MHz.

The ENI 2100L covers the range from 10 kHz to 12 MHz with a Class A linear output of more than 100 Watts. And it, too, can deliver 200 Watts over much of its useful frequency range.



Both units are solid state. Both units are unbelievably rugged. Unconditionally stable. Will not oscillate for any conditions of load or source imped-

ance. And will withstand all mismatched loads including short and open circuits.

Now there's no need to buy a whole expensive spread of individual units. With just these two portable amplifiers, you can work on an almost infinite range of applications. If it's 100 Watts... ENI has it covered!

For more information, a demonstration, or a full line catalog, please contact us at ENI, 3000 Winton Road South, Rochester, NY 14623. Call 716/473-6900, or telex 97-8283 ENI ROC.

ENI

The advanced design line of RF power amplifiers