
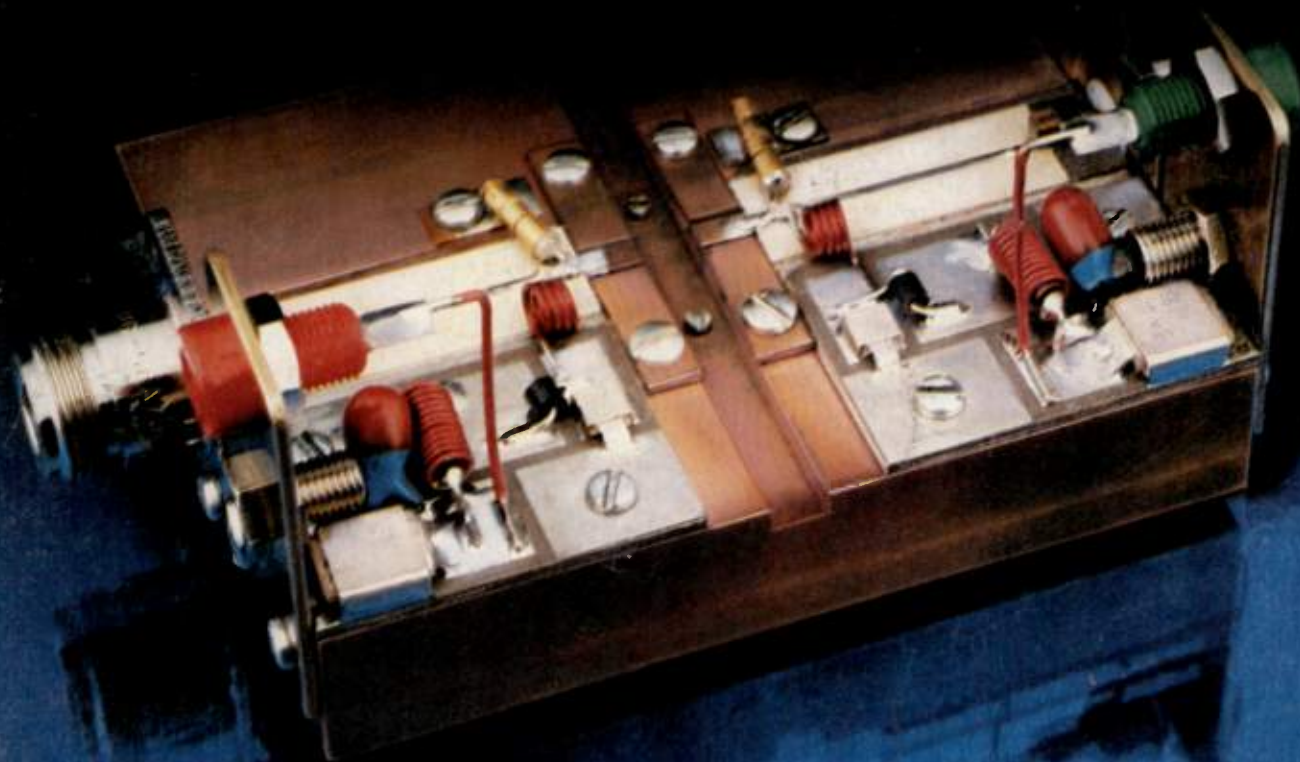


March/April 1984

A Cardiff Publication

inf design

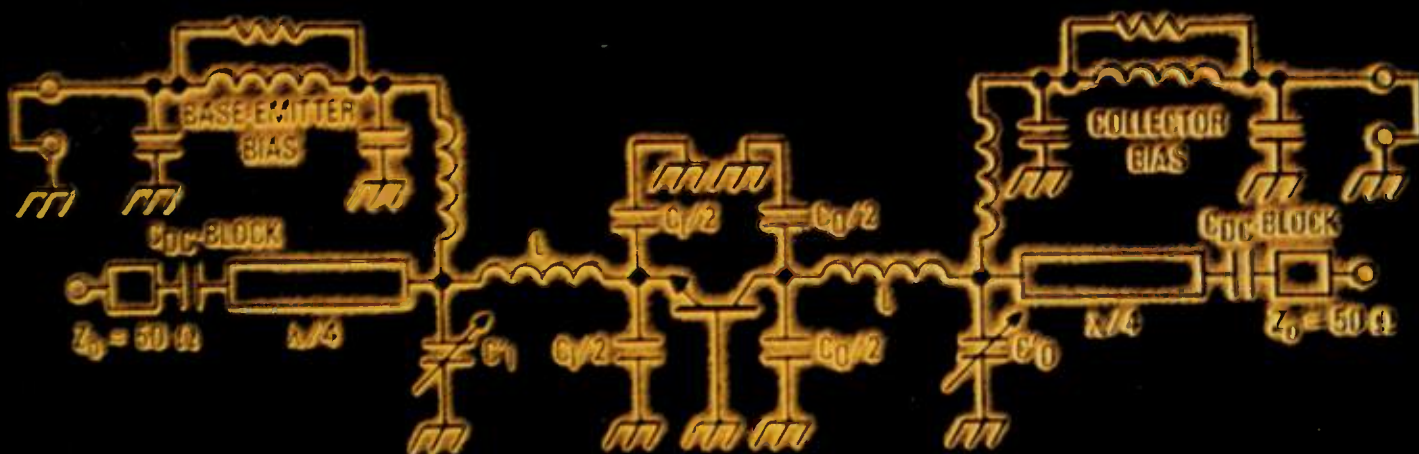

When your message means business



Amperex

A NORTH AMERICAN PHILIPS COMPANY

Now —reliable RF Transistors from 900 MHz down to 1 MHz for Mobile Communications.



900 MHz	MOBILE APPLICATIONS				
Type	Power (W)	Freq. (MHz)	Gain (db) min.	VCC (V)	Package
BLU98	0.5	900	9.0	12.5	SOT-103/E1
BLV90	1	900	7.5	12.5	SOT-172
BLV91	2	900	6.5	12.5	SOT-172
BLU99	4	900	7.3	12.5	SOT-122
BLV92	4	900	8.0	12.5	SOT-171
BLV93	8	900	6.0	12.5	SOT-171
BLV94	15	900	6.0	12.5	SOT-171

400 to 512 MHz	MOBILE APPLICATIONS				
Type	Power (W)	Freq. (MHz)	Gain (db) min.	VCC (V)	Package
BLU60/12	60	470	4.8	12.5	SOT-119
BLU45/12	45	470	5.1	12.5	SOT-119
BLU30/12	30	470	6.0	12.5	SOT-119
BLU20/12	20	470	6.5	12.5	SOT-119
BLW82	30	470	5.0	12.5	SOT-119
BLW81	10	470	6.0	12.5	SOT-122
BLU99	5	470	10.5	12.5	SOT-122
BLW80	4	470	8.0	12.5	SOT-122
BLW79	2	470	9.0	12.5	SOT-122
BLX65	2	470	6.0	12.5	TO-39

175 MHz	MOBILE APPLICATIONS				
Type	Power (W)	Freq. (MHz)	Gain (db) min.	VCC (V)	Package
BLV75/12	75	175	7.0	12.5	SOT-119
BLV45/12	45	175	6.5	12.5	SOT-119
BLV30/12	30	175	8.2	12.5	SOT-119
BLW60C	45	175	5.0	12.5	SOT-120
BLW31	28	175	9.5	12.5	SOT-120
BLY89C	25	175	6.0	12.5	SOT-120
BFQ43	4	175	12.0	12.5	TO-39E
BFQ42	2	175	10.5	12.5	TO-39

30 to 900 MHz	BASE STATIONS				
Type	Power (W)	Freq. (MHz)	Gain (db) min.	VCC (V)	Package
BLW96	200	30	13.5	50	SOT-121
BLV25	175	108	10.5	28	SOT-119
BLV80/28	80	175	6.5	28	SOT-119
BLV33F	85	225	10.5	28	SOT-119
BLV36	120	225	10.0	28	SOT-161
BLU53	100	400	6.5	28	SOT-161
BLV97	30	860	6.5	24	SOT-171
BLV57	38	860	6.5	25	SOT-161

66 to 870 MHz	AMPLIFIER MODULES FOR LAND MOBILE				
Type	Freq (MHz)	P In (MW)	P Out (W)	VCC	Package
BGY32	68-88	100	20	12.5	SOT-132
BGY33	80-108	100	20	12.5	SOT-132
BGY35	132-156	150	20	12.5	SOT-132
BGY36	148-174	150	20	12.5	SOT-132
BGY43	148-174	150	13	12.5	SOT-132B
BGY40A	400-440	100	7.5	12.5	SOT-132C
BGY41A	400-440	150	13	12.5	SOT-132C
BGY40B	440-470	100	7.5	12.5	SOT-132C
BGY41B	440-470	150	13	12.5	SOT-132C
BGY40A	470-512	100	7.5	12.5	SOT-132C
BGY41C	470-512	150	13	12.5	SOT-132C
BGY45A	68-88	150	30	12.5	SOT-301-A-03
BGY45B	144-175	150	30	12.5	SOT-301-A-03
BGY46A	400-440	30	1.5	9.6	SOT-26NC
BGY47A	400-440	45	2.2	9.6	SOT-26NC
BGY47B	430-470	45	2.2	9.6	SOT-26NC
BGY47C	460-512	45	2.2	9.6	SOT-26NC
BGY22	380-512	50	2.9	12.5	SOT-75A
BGY23	380-480	2.5 WATTS	7	12.5	SOT-75A

One of the purest signals your radios will ever receive.



The Fluke 6071A Signal Generator

Leading mobile radio manufacturers worldwide have selected the Fluke 6071A as their preferred synthesized signal generator.

Why?

As a critical element in RF tests systems, the 6071A meets their demands for receiver testing to 1040 MHz.

How?

Its -140 dBm to $+13$ dBm output is strong enough to reach the upper limits required for distortion tests, and pure and quiet enough to easily make multi-order intermodulation, adjacent

channel rejection, and other off-channel measurements. Spurious output levels are on the order of -90 dBc to -100 dBc, while the typical broadband noise floor is -150 dBc/Hz. Plus the 6071A offers built-in AM, FM, ϕ M, and IEEE-488 compatibility!

The 6071A is backed by Fluke's 20 years of experience in RF technology. And it's available at a price that's half of what you might expect to pay for equivalent performance. Only \$18,100.

Picture the 6071A in your RF test system. Then to find out how to get it there give us a call at 1-800-426-0361

or contact your local Fluke Sales Engineer or Representative. You'll prefer the 6071A too. Pure and simple.

IN THE U.S. AND NON-EUROPEAN COUNTRIES:

John Fluke Mfg. Co., Inc.
P.O. C9090, M/S 250C
Everett, WA 98206
(206) 356-5400, Tlx: 152662

IN EUROPE:

Fluke (Holland) B.V.
P.O. Box 5053, 5004 EB
Tilburg, The Netherlands
(013) 673973, Tlx: 52237





March/April 1984

Cover

- 1** **March/April Cover** — The front cover for this issue shows a schematic and test fixture described in the article "Designing Transistor Test Fixtures for the 800 MHz Frequency Spectrum." This month's cover photo is courtesy of Motorola Inc., Semiconductor Products Sector.

Features

- 14A** **Designing Transistor Test Fixtures For The 800 MHz Frequency Spectrum** — Test fixtures tend to be the last consideration for most RF power amplifier development programs, yet they are the most valuable tool available for measuring and maintaining device consistency.
- 25A** **High Performance VSWR Measurements** — This article describes the operation and use of the Return Loss Bridge for making low power precision VSWR measurements.
- 38A** **Reference-Level Control in Spectrum Analyzers: Simplification Through Internal Intelligence** — Modern spectrum analyzers are including more sophisticated circuits to simplify instrument operation. This article explains the approach used by Tektronix in their 490 series.
- 46A** **"Near Field" Communication** — The "Near Field" low frequency communication applications have been neglected for quite some time. However, suitable applications still exist and should be more closely explained.
- 58A** **Divider Delay: The Missing PLL Analysis Ingredient** — This article will analyze PLL divider delay using control systems models and demonstrates the impact of delay on loop stability.

Departments

- 6A Letters
68A r.f. designer's notebook
69A Application Note
72A New Products/Literature
79A Info Card
79A Subscription Card
96A Advertisers Index

Publisher
Keith Aldrich
Editor
Larry Brewster
Account Executive
Mike Morong
Editorial Review Board
Alex Burwasser
Rob Coe
Doug DeMaw
Dave Krauthelmer
Ed Oxner
Andy Przedpelski
Jeff Schoenwald
Raymond Sicotte

Advertising Services
Tami Baird

Circulation Director
Patti Wilbourn

Circulation Assistant
Sharon Rierson

Production Manager
Madeline Price

Assistant Production Manager
Mary Barr

Production Coordinator
Craig Ebel

Artists
Laura Alexander
Blair Hamill
Maurice Lydick
Dawn Jelinek

Composition
Cheryl Snow
Kristi Kehres

Published by

CARDIFF

PUBLISHING COMPANY, INC.

6530 S. Yosemite St.
Englewood, CO 80111
(303) 694-1522

Please address subscription inquiries to:
r.f. design, Cardiff Publishing Company,
P.O. Box 6317, Duluth, MN 55806
Postmaster: send form 3579 to the above address.

President
Robert A. Searle

Vice President:
Judy L. Rudrud

Controller
Mike Drake

Operations Manager
Cherry Greenman

BPA

R.F. DESIGN (ISSN: 0163-321X) is published bi-monthly. This issue March/April 1984, Volume 7, No. 2. Copyright 1984 by Cardiff Publishing Company, a subsidiary of Argus Press Holdings, Inc., 6530 S. Yosemite Street, Englewood, CO 80111 (303) 694-1522. Contents may not be reproduced in any form without written permission. Second-Class Postage paid at Englewood, CO and at additional mailing offices. Subscription office: 1 East First Street, Duluth, MN 55802, (1-800-346-0085). Subscriptions are sent free to qualified individuals responsible for the design and development of communications equipment. Other subscriptions are: \$15 per year in the United States; \$25 per year in Canada and Mexico; \$25 per year for foreign countries. Additional cost for first class mailing. Payment must be made in U.S. funds and accompany request. If available, single copies and back issues are \$5.00 each (in the U.S.). This publication is available on microfilm/fiche from University Microfilms International, 300 N. Zeeb Road, Ann Arbor, MI 48106 USA (313) 761-4700. POSTMASTER & SUBSCRIBERS: Please send address changes to: R.F. Design, P.O. Box 6317, Duluth, MN 55806.

RF switches



10 to 2500 MHz
from \$19⁹⁵ PSW 1211 (500 qty.)

Now, for your wideband systems design, under —\$20.00 SPST and SPDT pin diode switches that operate over the 10 to 2500 MHz range with less than 1 dB (typ.) insertion loss at 1000 MHz, 1.5 dB at 2500 MHz.

No waiting, immediate delivery . . . with one year guarantee.
Call or write for 64-page, catalog or see our catalog in the Gold Book, EBG, EEM or Microwaves Product Data Directory.

SPECIFICATIONS for PSW 1111 (SPST) and PSW 1211 (SPDT)

FREQUENCY RANGE	10-2500 MHz
INSERTION LOSS	
10-2000 MHz	1.7 dB max.
2000-2500 MHz	2.7 dB max.
ISOLATION	
10-500 MHz	40 dB min.
500-1000 MHz	30 dB min.
1000-2000 MHz	25 dB min.
2000-2500 MHz	20 dB min.
SWR	1.5 max. ("on" state)
SWITCHING SPEED	1 μ sec. (max.)
MAXIMUM RF INPUT	+20 dBm
CONTROL	+5 V (5 mA max.)
OPERATING TEMPERATURE	-54°C to +100°C
STORAGE TEMPERATURE	-54°C to +100°C

PRICE (6-24)

PSW 1111	\$29.95
PSW 1211	\$29.95



finding new ways . . .
setting higher standards

Mini-Circuits

A Division of Scientific Components Corporation
World's largest manufacturer of Double Balanced Mixers
P.O. Box 166, Brooklyn, New York 11235 (212) 934-4500
Domestic and International Telex 125460 International Telex 620156

C80 REV. ORIG.

"Basic, The Universal Language?" Part III

Dear Editor:

Mr. O'Neil (Sept./Oct. 1983) has indeed sparked a controversy! Sides are forming as loyal defenders of the faith are rushing to the battlements to defend the Holy Grail; in this case either the programmable calculator or the personal computer. As one who has walked down both paths the last 16 years, I would like to share a few comparative thoughts.

The programmable calculator and the personal computer are as alike, and as different, as the tack hammer and the sledge; each is a tool and each has its uses.

I have some 44 programs that I regularly use on my HP-41CV programmable system. In terms of size, the average program takes up 57 storage registers. One is only 10 registers long while another is 296; the short one returns physical line length as a function of frequency and dielectric constant, while the long one will tell you almost everything you could want to know about all types of microwave bandpass and bandstop filters and exactly how to fabricate each one. In between, almost every conceivable eventuality is covered: one determines the Fano bandwidth limits, another fully implements the Smith Chart in both lumped and distributed form, still others cover all forms of single and coupled line calculations.

I can use my programmable at my desk, on the bench, in a car, or on business trips all thanks to its portability and battery power source. And, because of the extensive built-in math functions, I can quickly program a solution to most any design problem. I do not have to write a subroutine to make a simple polar to rectangular conversion! I can even use it at the supermarket to add up the groceries.

On the other hand, my personal computer is faster and has a good deal more memory. However, these are relative terms in actuality since my average program is so short. Who cares if I can shave off a few tenths of a second in calculating a line length? And who really runs programs requiring 5 to 64K of memory everyday? I use my PC for what it is best at, word processing, spread sheet, and generating reams of data on microstrip, stripline, and coupler characteristics;

I have 5 programs that do all of that. I also run one program employing a gradient search adaptive algorithm for wide band amplifier design. It needs the speed of my PC and runs for hours; it is so big it takes up 40 feet of printer paper!

I only use my personal computer in my office. I don't like to carry it around. I use it for big things. On occasion I even take command of the Enterprise and go out to fight off the Klingons!

I think the point has been made? The majority of the calculations made by the average RF/Microwave Engineer are relatively short and can be handled quite well on a little handheld that you can slip into your shirt pocket. We mostly deal with "tack hammer" type tasks. On the other hand, the generation of tabular data, the optimization of large networks, or the creation of ones own in-house version of COMPACT are all "sledge hammer" tasks and make good use of the speed and memory of a personal computer.

Perhaps something that would make everyone happy would be for a young and knowledgeable engineer with time on his/her hands to just sit down and write an article detailing a translator program? Translator routines exist in the larger PC world, why not a routine that could simply and quickly turn an HP or TI program into Apple, Commodore, IBM, or Radio Shack Basic? Is anyone out there listening? If you have been waiting for an idea, something that many would appreciate and use, something that r.f. design would snap up and publish in an instant, get off the dime and GO FOR IT!

Sincerely,

James J. Lev
Mgr. RF/Microwave Design
Cartwright Engineering Inc.

Dear Editor,

Should "Basic" be the universal language. I do not think it should. I am presently converting a Fortran 4 program published in the April 1980 r.f. design, page 28, Design of a Miniature Quadrature coupler to use on my TI59. I feel you have published interesting solutions in the past and programs that I can use on calculators I can carry in and out of the plant. We do have the large circuit design systems here at Hughes but they are not always available to the working circuit designer, when he needs them. Most circuit

men I know like their handheld programmable calculators, and I have yet to see the personal computer run a Fortran 4 program with complex calculations.

Sincerely,

Robert Gunderson
Hughes Aircraft Co.

Dear Editor:

I have been reading with some amusement the BASIC versus Calculator "controversy." It seems to me that any well written article would not have this problem because it would include the kind of complete documentation one would expect of an engineer, namely: all formulas used, definition of all variables, and an example or two for reference.

Perhaps proponents of each tool (for computer and calculators are merely tools for an RF Engineer) could provide an article on "Translating BASIC to Calculators" and "BASIC Translations of Calculator Subroutines and RPN," especially in the Rectangular to Polar, Radians to Degrees, and Stack usage areas. There are differences in Labeling and use of subroutine calling, etc. as well.

I use both an HP-25 and Timex 1000 in my work . . . the Timex for formatted calculations with hard copy, the HP calculator for general simple calculations. Each has its strengths and its weaknesses. Both are equally useful depending on application.

Sincerely,

James Eagleson
R.F. Engineer
Identronix, Inc.

Dear Editor,

I would like to congratulate you on the improvement in the quality of the articles in RF Design in the last year. Many of them have been very useful for some of my recent projects.

The recent letters on the usefulness of calculator programs versus Basic programs for home computers were interesting. As an unbiased observer, I find it hard to beat the usefulness of a programmable calculator for engineering applications. Besides that, most of the programs for the calculator are free while the computer programs are over priced in many instances. Also, most computer programs are not well documented be-



**When the margin is slim,
our Attenuator Diodes help stretch the odds.**

**Alpha's new
attenuator diode
series combines
flexibility with
wide dynamic range
and a variety of
packaging options
to satisfy your most
pressing design needs.**

When it comes to designing transportable radios, dependable performance *must* be taken for granted. An entire mission may depend on it.


Alpha helps you meet the challenge with a new line of current-controlled attenuator diodes that are ideal for applications involving attenuators, modulators, electronically tuned filters, phase shifters, limiters, switches, and AGC applications.

Offering a broad selection of features, these devices operate over the entire RF range, with their low capacitance permitting attenuation well into the microwave spectrum. Furthermore, their thick intrinsic region permits their use at frequencies as low as 1 MHz with low distortion. And they are capable of generating a 50-ohm impedance at many different current loads, ranging from 200 μ A to 2 mA.

Other distinguishing characteristics include a low level of harmonic distortion and a wide selection of glass packaging configurations. In addition, when our standard curves don't match your design requirements precisely, we'll go back to the drawing board and come up with a set that will.

Features and Specifications

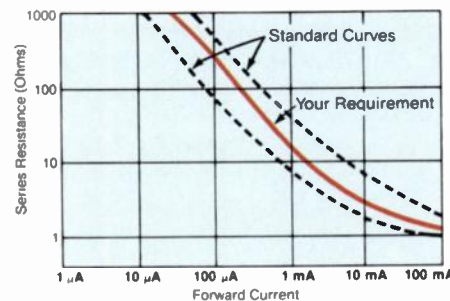- Wide Resistance Variation
- Low Harmonic Distortion
- Low Capacitance
- Low Series Resistance
- Long Operating Life and Thick Intrinsic Region



When your design requirements fall in between two of our standard curves, our design engineers will come up with the curve to meet them.



The Microwave People

Alpha Industries, Inc.
20 Sylvan Road
Woburn, Massachusetts 01801
Telephone: 617-935-5150
Twx: 710-393-1236
Telex: 949436

Part Numbers	Typical Resistance 1.0 mA 100 MHz ohms	High Resistance 10.0 μ A 100 MHz ohms (min.)	Low Resistance 20.0 mA 100 MHz ohms (max.)	T_L $I_L = 10$ mA $I_R = 6$ mA ns (min.)	C_T - 50 V 1.0 MHz pf (max.)	V_B $I_R = 10$ μ A — volts (min.)	Series Resistance 100 mA — ohms (max.)
DSB 6419-52	15	800	—	800	0.3	100	1.5
DSB 6419-53	20	1100	—	800	0.3	100	1.5
DSB 6419-55	25	1200	—	800	0.3	100	1.5
DSB 6419-59	40	1500	8.0	1000	0.4	100	2.5
DSB 6419-61	60	1500	—	1300	0.4	100	3.5
IN5767	40	1000	8.0	1000	0.4	100	2.5

Alpha Semiconductors. Our built-in flexibility lets you come as close as possible to meeting your design requirements...so that you don't have to compromise! Send for more information today.

INFO/CARD 4

Now, HP packs more value into its economical RF spectrum analyzers with digital display and rugged portability.



Measuring RF signals? HP's economy RF spectrum analyzers now give you even more value for your money. We've added digital display, versatile data I/O and rugged portability to the excellent performance and operating simplicity of these popular spectrum analyzers. The new HP 853A digital display spectrum analyzer mainframe with the HP 8557A (10 kHz-350 MHz) or 8558B (100 kHz-1500 MHz) spectrum analyzer plug-in combines accurate performance and simple three-knob operation to meet a wide range of RF measurement applications.

Digital display adds clarity and convenience.

The HP 853A provides two independent 480-by-800-point resolution traces for flexibility in storing trace data and monitoring signal changes. You get a crisp, flicker-free, easy-to-read display. And the microprocessor-managed display system includes maximum hold for storing peak signal values, digital averaging over successive sweeps to reduce noise effects, and trace normalization to help detect signal changes in a crowded spectrum.

Rugged portability lets you take it almost anywhere.

The 853A is designed for transportable use in rigorous environments. Weighing less than 48 lbs., the analyzers can be taken outdoors for field test use, or easily moved around lab and production sites. The 853A comes with a tilt-bail handle, rubber bumpers, and a drip-proof front panel cover. What's more, the HP 853A with plug-in installed is type-tested to meet shock, vibration and driptest

levels specified under MIL-T-28800 C Type III, Class 3, Style C performance tests. **A choice of RF plug-ins covers your applications.**

Notable performance specifications of the 8557A and 8558B plug-ins include 70 dB dynamic measurement range, 1 kHz to 3 MHz variable resolution, full range frequency response of ± 1 dB and 70 dB IF substitution amplitude accuracy of ± 1 dB. Basic measurements require only a three-knob sequence: TUNE to a signal and read frequency from the LED display, narrow the FREQUENCY SPAN for closer analysis and adjust REFERENCE LEVEL to read amplitude directly. Resolution and sweep speed are automatically adjusted.

U.S.A. list prices for the plug-ins are: HP 8557A (350 MHz) \$6,520; HP 8558B (1500 MHz) \$7,925. The new 853A display mainframe is listed at \$5,550*



For a permanent record or comparison of many displays, the 853A push-button controls can directly operate an HP-IB plotter for hard copy data recording. Or connect the 853A to a computer (like the HP-85) via HP-IB and get trace I/O as well as operator prompts on the CRT.

To add portability and digital display convenience to your RF spectrum analysis applications, call your nearest HP sales office and ask for "Instruments." For the same simplicity and performance in microwave applications, ask about HP's economical microwave plug-in for the 853A. For more information about these instruments, write Hewlett-Packard, 1820 Embarcadero Road, Palo Alto, CA 94303.

5301201

*U.S.A. list prices only



**HEWLETT
PACKARD**

cause of the excessive secrecy desired by most programmers, so the engineer in using them, must rely on the competence of the person writing them and sometimes the assumptions used. As a professional engineer, I prefer to know how a program was developed before paying a lot of money for it.

Perhaps some manufacturer would be interested in developing a combination machine with a calculator and computer keyboard together. It is certainly faster to press the button $1/x$ than to perform the operation in BASIC.

Yours truly,
Jon GrosJean

"Divider Time Delay"

The "divider time delay" discussed by Mr. Przedpelski in your July/August 1983 issue is an important effect in phase-locked frequency synthesizer design but it is not as simple as is suggested there.

It is true that information cannot be passed from frequency divider to phase detector except at divider output transitions. This happens, at most, twice per reference period and, with some types of phase detectors (phase/frequency, sample-and-hold), only once per reference period. However, this does not necessarily cause a delay equal to the reference period (or to $(N-1)/(F_R N)$ as shown below your Eq. (11)). For example, a sudden phase change at the VCO output could be seen at the phase detector almost immediately if it happened to occur just before the divider's output transition, or it could be delayed as much as a reference period if it occurred slightly later.

What is operating here is a sampling process. If a sine wave of phase modulation should exist at the input to the frequency divider, the width of the narrow pulses from a phase/fre-


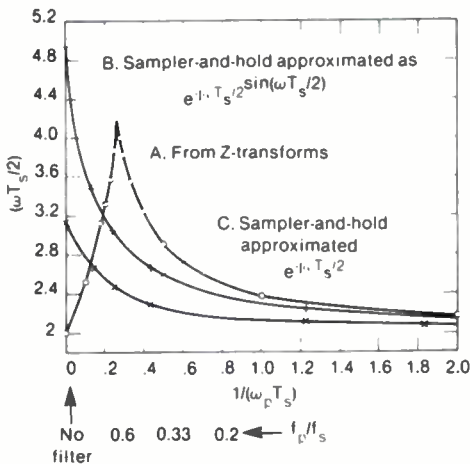


Figure 5.40 Maximum loop gain ω_0 for stable operation versus low-pass corner frequency ω_p , both normalized to sampling period T_s . From *Frequency Synthesis by Phase Lock*, p. 135. Copyright 1981, John Wiley & Sons, Inc. Reprinted by permission.

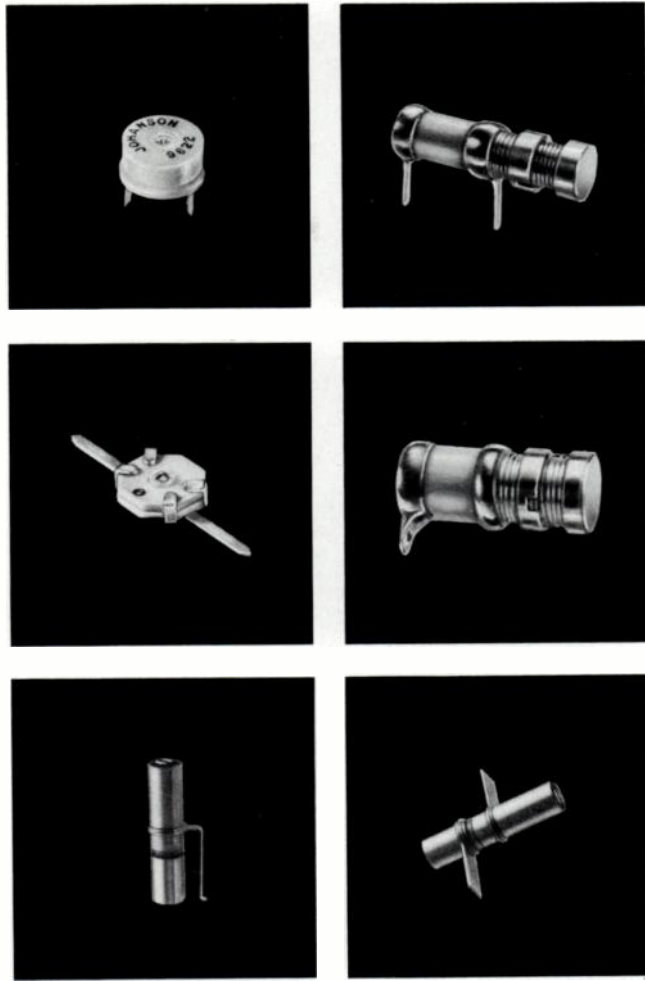

Variable Capacitors

Johanson air and sapphire dielectric variable capacitors are designed for RF applications from HF through microwave frequencies. They incorporate a patented self-locking constant torque drive mechanism which insures uniform torque and low dynamic noise. Johanson Thin-Trim® and Seal-Trim® capacitors are an advanced development in micro-miniaturized variable capacitors. They feature low drift rates and high Q and are ideal for high frequency applications. Thin-Trim® and Seal-Trim® incorporate the Johanson square drive tuning mechanism to assure non-slip tamper proof adjustments.

Electronic Accuracy through Mechanical Precision

Johanson

Manufacturing Corporation

Rockaway Valley Road Boonton, New Jersey 07005
201-334-2676 TWX 710-987-8367

Johanson products are covered by
U.S. Patent No. Re. 30,406; U.S. Patent No. 3,701,932; U.S. Patent No. 4,179,722

INFO/CARD 6

quency detector (e.g. MC4044) would represent the divided and sampled sine wave and the "fundamental" component of that pulse train would not be delayed relative to the input phase modulation. Of course other newly-created frequencies would also exist at the phase-detector output.¹

The sampling rate is signal dependent but for small percentage frequency changes it is approximately equal to the reference frequency into the phase detector. Constant-sampling-rate systems can be analyzed exactly

using Z-transforms. One approximation sometimes employed where there is a sample-and-hold circuit, such as with a sample-and-hold phase detector, is to ignore all but the lowest (input) frequency generated by the sampling process. The sampled system is then replaced by an approximately equivalent continuous system. In this case the zero-order hold has a transfer function of

$$e^{-j(\omega T_s/2)} \frac{\sin(\omega T_s/2)}{(\omega T_s/2)}$$

where T_s is the sample period equal to the reciprocal of the reference frequency. A further simplification retains only the phase term. This gives a time delay of approximately half the value indicated by Mr. Przepielski but it is actually associated with the hold circuit rather than the divider. Figure 5.40 (reference 1) shows how these approximations compare to the exact analysis of a simple phase-locked loop with a sample-and-hold phase detector and a loop filter consisting of a single-pole low-pass at ω_p .² The vertical scale gives maximum allowed gain ω_o (at $\omega = 1$) for stability. The approximations are seen to be good if the low-pass corner frequency (ω_p) is low compared to the sampling frequency ($1/T_s$).

Other important effects due to this inherent sampling process are the translation of noise frequencies^{1, 4} and the existence, under some circumstances, of loop oscillations of finite magnitude — that is, they neither grow nor die out.³

On a different topic in Mr. Przepielski's article, the transfer function shown in Fig. 18(b) is for a zero-impedance source. When a charge pump (such as is included in the Motorola MC4044 1C) is used, however, the source is an open circuit at times, usually most of the time, which surely complicates the generation of a transfer function for this filter.

Sincerely,

William F. Egan
Sylvania Systems Group —
Western Division
GTE Communications Products Corp.

1. W.F. Egan, "Frequency Synthesis by Phase Lock," (New York, N.Y.: John Wiley, 1981), pp. 75-81.

2. Ibid, pp. 131-135.

3. Ibid, pp. 209-211.

4. W.F. Egan, "The Effects of Small Contaminating Signals in Nonlinear Elements Used in Frequency Synthesis and Conversion," Proceedings of the IEEE, July 1981, pp. 797-811.

Dear Editor:

I appreciate Dr. Egan's comments. The point of the PLL articles was to provide the designer with some degree of assurance that the circuit he was designing would perform more-or-less as expected. We found that using the standard references this was almost impossible in most instances without deriving the presented formulae, which were not available in literature. It is difficult to put all the information into an article that is not available even in textbooks, but it has been our exper-

"Our Coaxial Switching Systems are Computer Compatible."



Another Reason Why MATRIX is the Leader in Coax Switching Systems.

MATRIX programmable switching systems are designed to operate directly off your minicomputer or microprocessor 16-bit parallel output.

Using reliable, hermetically sealed reed relays, a computer-controlled MATRIX switching system can handle any format. Apply your control input to your MATRIX and the system will route your signal to as many points as you wish — and in one millisecond!

MATRIX systems can be controlled manually as well. And now, with our new IEEE-488 Interface, any MATRIX switching system can be tied into the general purpose interface bus.

So when a coaxial or audio switching requirement comes up, be sure to contact MATRIX first. Most likely, we've got the solution sitting on our shelf.

Phone or write for details.



MATRIX

SYSTEMS CORPORATION

5177 NORTH DOUGLAS FIR ROAD • CALABASAS, CALIFORNIA 91302
(213) 992-6776 • TWX 910-494-4975

GOING THE DISTANCE



The date: February 1, 1925—Togo, a 10-year-old Siberian husky, led his team in the desperate drive to carry diphtheria anti-toxin to the children of Nome Alaska—going the distance for an incredible 340 miles, non-stop, in the face of 80 mph winds and 50-below-zero temperatures.

ACRIAN GOES THE DISTANCE IN BROADBAND COMMUNICATIONS TECHNOLOGY

Acrian is a world leader in high power, high-reliability RF and microwave broadband power devices. We got there by going the distance—meeting a diversity of telecommunications needs with a non-stop commitment to engineering and manufacturing teamwork, no matter how tough the challenge, or how basic.

Take a hard look at the 0105-100, an internally input-matched balanced NPN power transistor, with 100 watts output for 100-500 MHz broadband applications.

Gold thin-film metalization and surface passivation deliver proven high MTTF,


making the 0105-100 an outstanding example of the Acrian communication transistor series.

Call us for complete specifications on the 0105-100, or any of more than 500 Acrian products that go the distance in communications, radar, and avionics. Call or Telex: (408) 996-8522 TWX (910) 338-2172.

Acrian Inc. 10060 Bubb Road
Cupertino, California 95014

ACRIAN

POWER WITH A PURPOSE

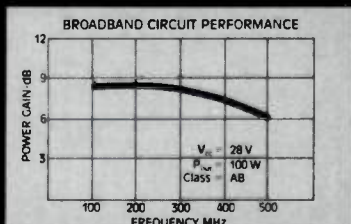

ience that, using the material presented, predictable PLL circuits can be built. To comment on Dr. Egan's comments:

- Delay in frequency dividers is seldom mentioned in PLL references. Even Dr. Egan in his book (which I consider as one of the basic reference texts on the subject) talks about divider delay as the propagation delay, which is a function of the logic used and the divider configuration. This is not the delay in question (and usually is small enough, in comparison, to be neglected). Westenkamp seems to be the first

to try to reduce this delay to some manageable form. The inclusion of this delay in the overall PLL equation seems to have removed the last discrepancies between paper design and actual hardware in the more complex PLL designs. This delay would be independent of the type of phase detector used.

- Yes, it is, of course, true that equation of Fig. 18(b) assumes a zero source impedance. Any source resistance has to be included in the first R_s resistor. This is common practice and works well with phase detectors such as Motorola MC12040

and MC4044 (without the charge pump — Motorola does not recommend the charge pump for critical applications).

Again, I would like to thank Dr. Egan for taking the time to send his comments.


Yours very truly,

Andrzej B. Przedpelski

Diagram Error

Dear Editor,

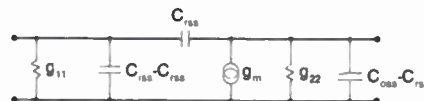In the article November/December (1983) Issue "How The Isofet Enhances Stability in Broadband High Gain Amplifiers" some errors were found in Figure 1. More specifically,



Please publish this in the letters or corrections section so that this oversight on my part can be corrected.



I would like to thank Nathan O. Sokal, President of Design Automation, Inc., for informing me of this error.

Larry Leighton

Edison didn't need Modpak™

But modern electronics involves more than a bulb, a vacuum, and a filament.

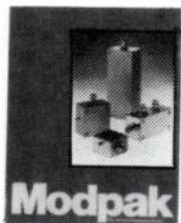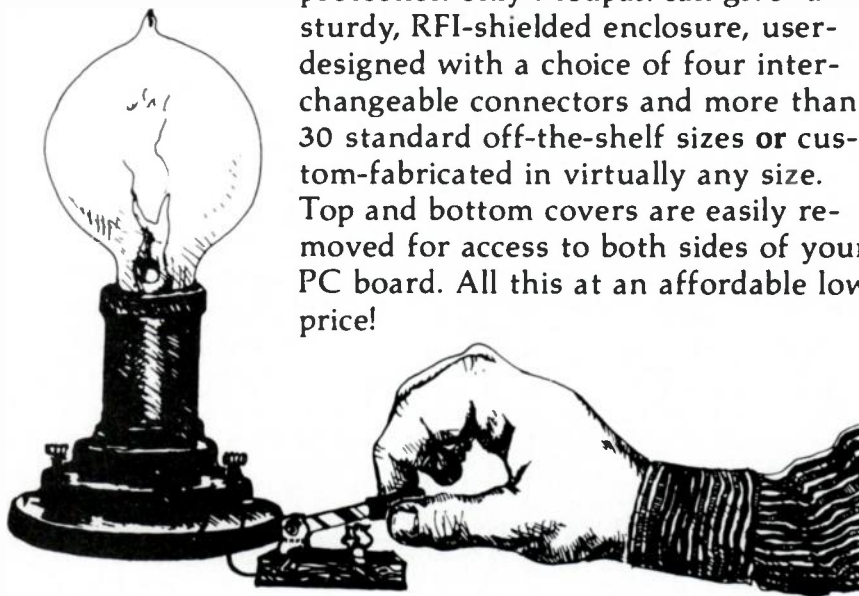Your vulnerable RF circuit needs the protection only Modpak can give: a sturdy, RFI-shielded enclosure, user-designed with a choice of four interchangeable connectors and more than 30 standard off-the-shelf sizes or custom-fabricated in virtually any size. Top and bottom covers are easily removed for access to both sides of your PC board. All this at an affordable low price!




Find out why you need Modpak, send for our complete catalog.

Adams Russell
MODPAK DIVISION

80 Cambridge St., Burlington, MA 01803
(617) 273-3330

ACCURACY

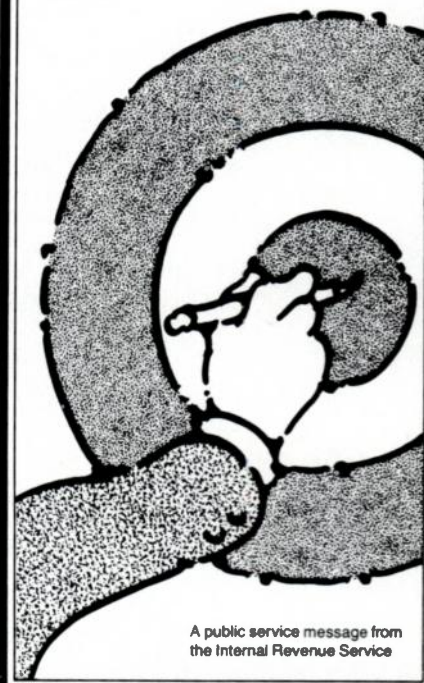An accurate return means a faster refund!



A public service message from the Internal Revenue Service

ANNOUNCING THE END OF THE GaAs CRISIS.



Feel like you're waiting in line every time you order gallium arsenide devices?

Maybe it's bad enough when they're standard products you're after. And just plain intoler-

able when you need something made to your specs.

Well, here's relief.

Announcing a full line of high performance gallium arsenide diodes for C Band to millimeter applications, made the way you need them, available when you need them.

And they're all from Frequency Sources. So you know they've been measured, tested, retested and optimized in some of the most advanced microwave circuits anywhere.

We have a sales and engineering support staff eager to help you find exactly the right gallium arsenide diode solution for your special problem. Why not call today?


PACKAGED GUNN DIODES
The rugged, reliable, MIL-SPEC standard for signal generation up to 24 GHz. Available to your exact specifications. Feature low noise and power to 500mW.



PLATED HEATSINK GUNN CHIPS
The ideal "chip form" Gunns for hybrid circuits. Feature power up to 500mW and 6% efficiency. Wide band widths up to 18 GHz.



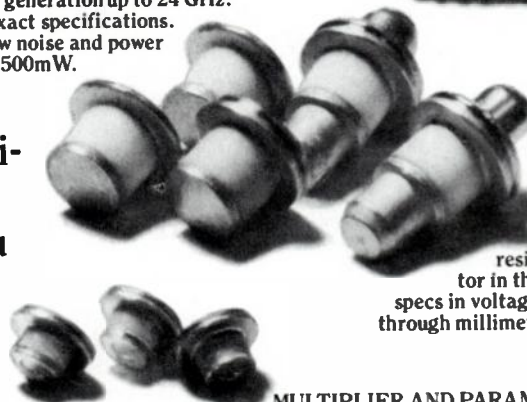HIGH Q TUNING VARACTORS
The highest Q (up to 16,000) and lowest series resistance of any tuning varactor in the industry. Made to your specs in voltages from 15 to 60 volts. RF through millimeter tuning.



MULTIPLIER AND PARAMP VARACTORS
Extremely sensitive for paramps, extraordinarily efficient for multipliers. Available in a wide range of hermetic packages to match your exact application — from S Band through millimeter.

**FREQUENCY
SOURCES**
SEMICONDUCTOR DIVISION

A SUBSIDIARY OF LORAL CORPORATION

16 Maple Road
Chelmsford, MA 01824
(617) 256-8101
TWX (710) 343-0404



Designing Transistor Test Fixtures For The 800 MHz Frequency Spectrum

Test fixtures tend to be the last consideration for most RF power amplifier development programs, yet they are the most valuable tool available for measuring and maintaining device consistency.

By Dan Moline
Motorola Inc.
Semiconductor Products Sector
Phoenix, AZ 85008

Minimum power gain, collector efficiency and broadband performance requirements, though they are always detailed in some form of written specification, are meaningless unless they are demonstrated and controlled by a test fixture. A good test fixture will assure correlation between the customer and vendor while functioning as a trouble shooting tool in the event of radio problems. When alternate sources are pursued for a stage, test fixtures can shorten qualification cycles. But the prevention of gradual shifts in RF performance over the lifetime of a product is the major purpose of a test fixture. Although this article presents techniques for the general case of UHF-800 MHz circuit design, the emphasis is placed specifically on test fixture design for 800 MHz.

Motorola has recognized the importance for good test fixtures and has established general guidelines for their implementation.

All the hi-tech products are tied to a well defined test fixture, which have the following general specifications:

Broadband performance, demonstrating typical characteristics throughout the band. (Ex.: UHF; 450-512 MHz, 800; 800-870 MHz)

A 3" x 5" mechanical format, which is rugged for large quantity test applications.

Simple RF match construction to represent realistic radio performance.

Devices will meet all minimum test requirements at the specified test frequency. UHF: 470 MHz, 800: 870 MHz.

The repeatability, mechanical ruggedness and broadband performance are all very important factors needing consideration in the design of test fixtures. The remainder of this article goes into detail, using the MRF846 as an example.

The schematic representation of the fixture outlined in this article is shown in Figure 1.

C_i and C_o represent the shunt capacitors at the input and output (respectively) which cancel most of the inductive reactance associated with the transistor's input and output impedance. Mini clamped-mica capacitors are used for these components and are physically located beneath the common lead wear blocks. Inductance "L" is introduced by the input (and output) wear blocks. Because of this parasitic inductance, L, trimmer capacitors (C_i or C_o) are required to transform the now reactive impedance back to real before launching off into the $\lambda/4$ transmission lines.

The transistor's input and output impedance can be represented as a combined series resistor and inductor as shown in Figure 2.

This series combination can be transformed into a parallel equivalent by using the equations shown in Figure 3. The capacitors C_i and C_o are selected by calculating the value necessary to form a parallel resonance with X_p . Since all capacitors have a finite, series lead inductance, the capacitor is actually considered as a simple series resonant circuit. The resulting effect is the capacitance is al-

ways higher than the marked value and goes through resonance at some frequency. Mini clamped-mica capacitors are recommended for test fixture design due to the very low parasitic inductance associated with them; which increases the usable range of capacitances. (They are also extremely high "Q"). A typical measured series inductance for clamped-mica capacitors is about 0.5 nH. The equivalent capacitance is calculated by subtracting the series lead inductance from the capacitive reactance, or $X_{c(equiv)} = X_c - X_{L(0.5nH)}$.

Since two capacitors are used in parallel, the total capacitance is derived as shown in Figure 4.

A value of $2X_c$ is used in the example since each capacitor will contribute only $1/2$ to the total capacitance. By setting $X_{c(equiv)}$ equal to the parallel equivalent reactance calculated in Figure 3, the exact capacitor values may be determined.

$$X_p = \frac{2X_c - X_{L(0.5nH)}}{2}$$

$$X_c = \frac{2X_p + X_{L(0.5nH)}}{2}$$

$$(X_c = 1/2 fC)$$

$$C = \frac{1}{\pi f (2X_p + X_{L(0.5nH)})}$$

Introducing an actual example at this time should help in explaining the remaining steps involved in a test fix-

AUTOMATIC PEAK POWER MEASUREMENTS

AT YOUR FINGERTIPS



MODEL 478

No other peak power meter can give you all this...

Now you can measure:

- Peak power automatically
- Instantaneous power at any point on a waveform
- From 0.1 to 26.5 GHz
- -30 dBm to +15 dBm
- 10 nsec rise and fall times
- Pulse widths from 15 nsec to CW

Built-in features include:

- High-contrast 7" CRT display
- IEEE Bus
- Power head self correction

POWER HEADS AVAILABLE		
Model Number	Freq. Range (GHz)	Pwr. Range (dBm)
N436	0.75-18	-30 to +15
M438*	0.75-26.5	-24 to +15

*For delivery fall 1984

Note: Low frequency limits extendable with moderate decrease in video bandwidth. Option 02: 100 MHz; Option 03: 500 MHz

World's most powerful, most flexible, most accurate Peak Power Meter

This fully programmable, microprocessor-based instrument automatically selects the optimum time base and power range to fully characterize a microwave pulse. The instrument self-corrects for linearity and frequency response of the power head, enabling measurement accuracy to within ± 0.3 dB.

The pulse waveform is presented on a calibrated CRT, displaying a graph in linear or logarithmic units. Peak and instantaneous powers as well as rise/fall times and pulse widths are also digitally displayed.

An offset feature automatically scales the readout to compensate for external gain and loss with 0.01 dB resolution.


Other features include: Keyboard Programmability
 • Manual/Automatic Operation • Optional CIIL Compatibility • Trigger Delay • X-Y Recorder and Video Outputs
 • Digital Averaging

For complete details, write or call

**General
Microwave**



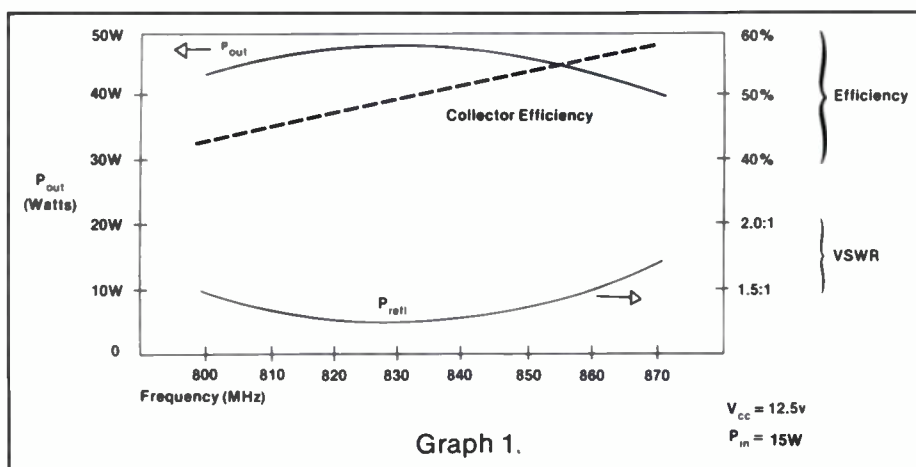155 Marine Street, Farmingdale, New York 11735, Tel: (516) 694-3600



ture design. The MRF846 is a 40 W, 12.5 V, 800 MHz device whose input and output impedances are:

TABLE 1.

Freq.	Z_{in}	Z_{out}
800 MHz	$1.1 - j4.8$	$1.20 + j2.4$
836 MHz	$1.0 - j4.9$	$1.15 + j2.5$
870 MHz	$1.0 + j5.0$	$1.10 + j2.7$
900 MHz	$0.9 + j5.1$	$1.10 + j2.8$

Since X_p will vary as a function of frequency, C_i and C_o need only be calculated for one point within the frequency band. Typically, the input response of an RF power transistor is optimized about the center of the band. Hence, the input R_p and X_p are generally calculated at this frequency $[(f_H + f_L)/2]$

The output response is different. If C_o were selected for a resonance to occur with X_p , at band-center, an unacceptable performance roll-off would be seen at the upper end of the frequency band. Overall performance is best when C_o is calculated at a frequency within 20% of the upper end of the band. Since device gain increases as frequency decreases, the performance at lower frequencies is generally no problem.

Using the MRF846 as an example, input and output capacitor values may be determined as follows:

INPUT: Freq. = 836 MHz

$$Z_{in} = 1 + j4.9 \quad Q = 4.9/1 = 4.9$$

$$X_p = 4.9(1 + 1/(4.9)^2) = 5.1 \text{ ohms}$$

$$X_{L(0.5nH)} = 2\pi(836 \times 10^6) (.5 \times 10^{-9}) = 2.63 \text{ ohms}$$

$$C = 1/[\pi(836 \times 10^6) (2 \times 5.1 + 2.63)] = 29.7 \text{ pF}$$

2-15 pF Capacitors would be the best choice.

OUTPUT: Freq. = 870 MHz

$$Z_o = 1.1 + j2.7 \quad Q = 2.7/1.1 = 2.45$$

$$X_p = 2.7(1 + 1/(2.45)^2) = 3.15 \text{ ohms}$$

$$X_{L(0.5nH)} = 2\pi(870 \times 10^6) (.5 \times 10^{-9}) = 2.7 \text{ ohms}$$

$$C = 1/[\pi(870 \times 10^6) (2 \times 3.15 + 2.7)] = 40.7 \text{ pF}$$


2-20 pF Capacitors would be the best choice.

(20 pF Capacitors were not available, so an 18 pF & a 24 pF capacitor were chosen instead. The total C = 42 pF).

Though the MRF846 test fixture used at Motorola does use these capacitor values, the above calculations may act only as a good starting point. Imperical measurements and more precise impedance measurements for a given applications may

THE SIGNAL PROCESSING SPECIALISTS

IMAGE REJECT MIXER

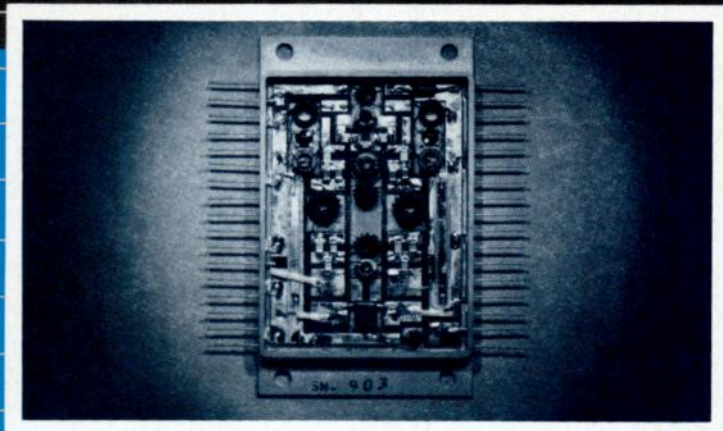

Typical Specifications

- RF Operating Bands Up to 4 GHz
Octave to 10:1 Bandwidths
- Image Rejection 20/25 dB
- IF Output Frequencies 0.5 to 500 MHz
Octave to 5:1 Bandwidths
- Conversion Loss 9 dB
- LO Power Input +10 to +13 dBm
- Input/Output Impedances 50 Ohms, Nominal
All Ports

Typical Features

- Hi-Rel Versions Available
- Hermetically Sealed
- Operating Temperature: -35° to +85°C
- Lightweight: ≤ 2 oz.
- Compact Packaging: 1.3" x 1.75" for Sample Pictured
- Low Profile: ≤ 0.2" High
- SSB Generators Available in Same Package Outline

Send for complete specifications or contact factory for your specific needs.

Merrimac
INDUSTRIES, INCORPORATED

P.O. BOX 986, 41 FAIRFIELD PLACE, WEST CALDWELL, N.J. 07007
201-575-1300 • TWX 710-4314 • TELEX 6853128

How to avoid Capitol Punishment.



Now there's a code of silence in Washington. It's called FCC Docket 20780. And the Cannon® Shielded/Shrouded D Series of subminiature connectors helps manufacturers meet all its stringent EMI/RFI requirements, while helping to maintain the integrity of the entire shielded system.


Our shield is crimped to the cable to maximize shielding effectiveness and provide a low-impedance path to the ground.

The shroud/plastic backshell protects the equipment from ESD (Electro Static Discharge) and isolates the user from ground potentials that may exist on the shield. Plastic strain-relief members are provided to prevent cable pullout. The center-latched version is available in configurations of 9, 15, 25 and 37 contacts.

Cannon's quality D Subminiature Transverse Monolith Filter connectors reduce EMI/RFI noise.

The addition of the transverse monolith filter expands the overall shielding versatility of the D Subminiature without adding to the overall dimensions of the connectors.

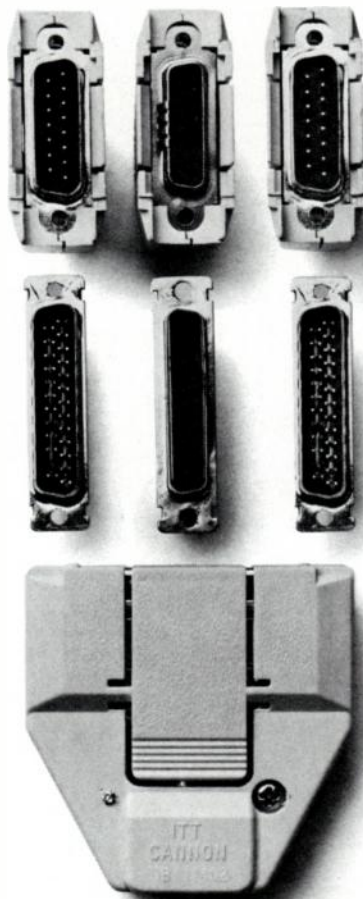Silence FCC Docket 20780 with D Series subminiature connectors.



And these Cannon connectors are available in contact arrangements of 9, 15, 25 and 37, with a wide range of capacitances and cutoff frequencies offered.


The Shielded/Shrouded D and Transverse Monolith Filter Series connectors from ITT Cannon. The best way to give FCC Docket 20780 the silent treatment.

For more information on Transverse Monolith Filter Connectors, contact Phoenix Division, ITT Cannon, 2801 Air Lane, Phoenix, AZ 85034. Telephone: (602) 275-4792.

Or for more information on the D Subminiature Shielded/Shrouded D Series, contact Commercial/Industrial products, ITT Cannon, a Division of ITT Corporation, 10550 Talbert Avenue, Fountain Valley, CA 92708. Telephone: (714) 964-7400. For the local sales office nearest you, call toll-free: (800) 845-7000.

CANNON ITT
The Global Connection

plug-in attenuators

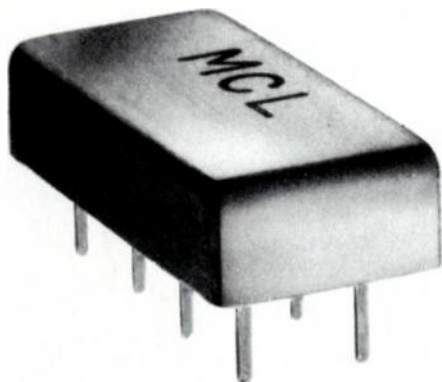

DC to 1500 MHz
only \$1⁹⁵ (1,000 qty.)
\$3.95 (10-49)

IN STOCK...IMMEDIATE DELIVERY

- rugged...meets MIL-STD-202
- hi-stability, thick-film construction
- miniature 0.4 x 0.8 x 0.4 in.
- flat frequency response...
±0.3dB (typ.)
- VSWR less than 1.2:1 (typ.)
- 1W maximum power
- designer's kit available,
4 of each type (12 units) \$39.95

SPECIFICATIONS

MODEL	ATTEN.	ATTEN. TOL.
AT-3	3 dB	±0.2 dB
AT-6	6 dB	±0.3 dB
AT-10	10 dB	±0.3 dB
AT-20	20 dB	±0.3 dB

For complete specifications and performance curves refer to the Microwaves Product Data Director, the Goldbook, EEM, or Mini-Circuits catalog

finding new ways...
setting higher standards

Mini-Circuits
A Division of Scientific Components Corporation
World's largest manufacturer of Double Balanced Mixers
2625E, 14th St. B'klyn, N.Y. 11235 (212) 769-0200

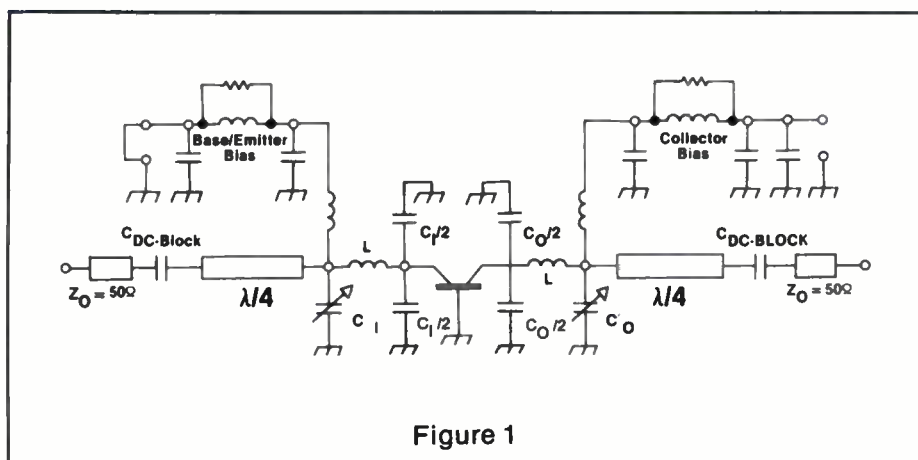


Figure 1

result in minor deviations from these values.

Assuming no additional circuit parasitics had to be accounted for, the quarter wave transmission line sections could now be determined. The input (and output) fixture wear blocks do, however, contribute additional series lead inductance to the impedances. These inductances are counteracted by the trim capacitors C_1 and C_0 . The wear block inductance could be calculated and then used to determine the proper capacitance values. However, since there are other, less obvious frequency and grounding effects which may influence the impedance transformation, it is a more practical (and generally a more accurate) procedure to measure the impedance which will be transformed by the transmission line to 50 ohms.

The capacitors C_1 and C_0 should be mounted into the test fixture and a known characteristic impedance transmission line soldered into place as shown in Figure 5.

Triple stub tuners are used on the input and output to tune for maximum output power and minimum reflected power at various frequencies throughout the band. Band edges and band center are generally adequate for a good circuit design. Due to higher impedance levels produced by adding C_1 and C_0 , $[Z_{in}]$ and $[Z_{out}]$ are measured instead of the real transistor impedances, Z_{in} and Z_{out} . Also, by measuring impedances in the actual applications fixture, the design can be optimized for that particular fixture. Perhaps a maximum gain tuning point is not desired. Obtaining impedances for an efficiency/gain compromise may

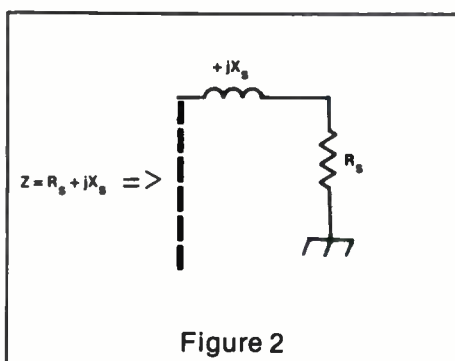


Figure 2

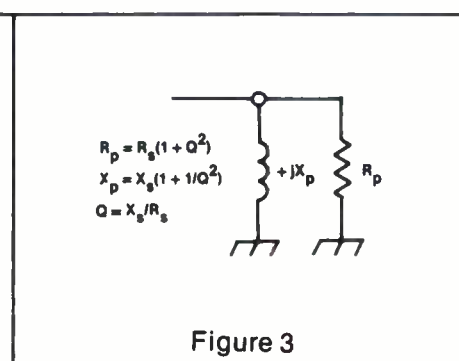


Figure 3



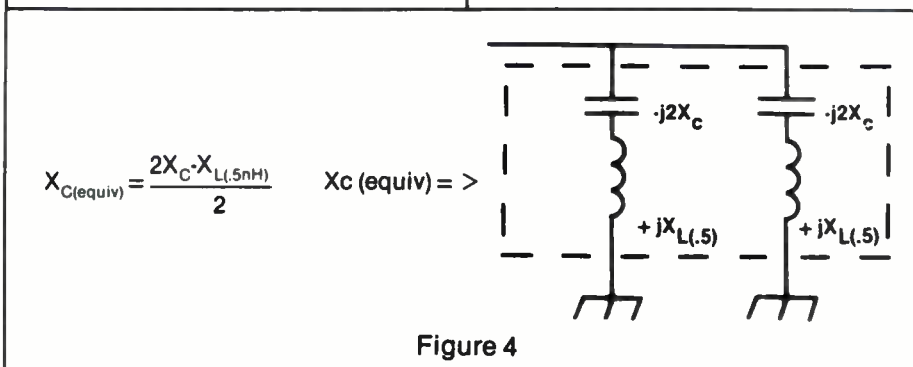


Figure 4

Looking into an Anechoic Chamber?

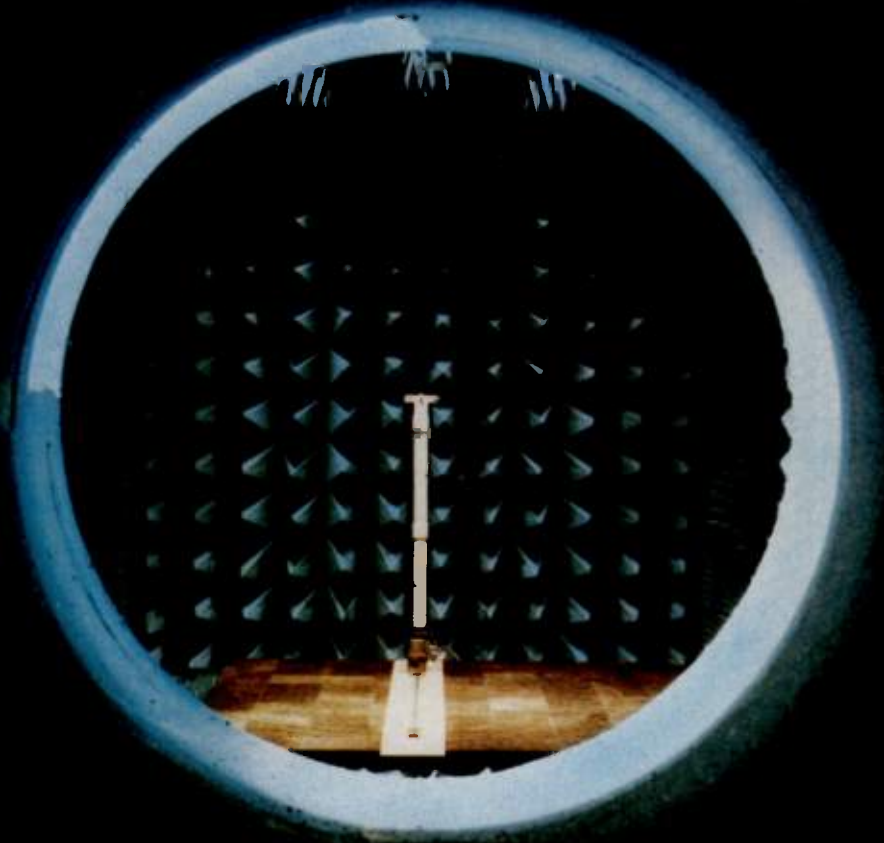

Look into Ray Proof.

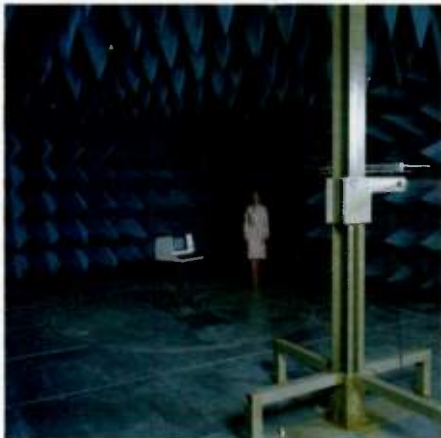

And you'll find the performance that has made us the leading source of RF shielded anechoic test systems — including microwave absorbers produced in our Advanced Absorber Products facility.

Customers like IBM, DEC, GE, TI and Bell Labs have selected Ray Proof. And Ray Proof provides **performance** — a quality product, on-time delivery and a commitment to service backed by over 50 years of experience.

Take a look at Ray Proof today!

KEENE
CORPORATION

RAY PROOF DIVISION

50 KEELER AVENUE, NORWALK, CONNECTICUT 06856-5060 TELEPHONE (203) 838-4555 TELEX #96-5812
EUROPEAN OFFICE: KEENE INTERNATIONAL LTD., RAY PROOF DIVISION, UNIT 23, MITCHAM IND. ESTATE,
STREATHAM ROAD, MITCHAM, SURREY CR42AP ENGLAND, TELEPHONE 01-640-9214, TELEX #25635

INTERNATIONAL REPRESENTATIVES:

AUSTRALIA: Epping N.S.W., 477-5494 • BELGIUM: Brussels, 02-7352135 • DENMARK: Copenhagen, 02-804200 • ENGLAND: Hitchin, 0462-57181
GERMANY: Frankfurt, 06194-2788 • HONG KONG: 5-220964 • INDIA: Bangalore, 567443 • ISRAEL: Tel Aviv, 49-19-22
ITALY: Milan, 02-4982451; Rome, 06-5139455 • JAPAN: Tokyo, 3-270-5921; Osaka, 6-231-5051; Nagoya, 52-935-7486 • NETHERLANDS: Rijswijk, 070-99-63-60
NORWAY: Oslo, 02-282624 • PORTUGAL: Lisbon, 19-682185 • SINGAPORE: Sembawang, 65-2570211 • SOUTH AFRICA: Brixton, 8391824
SPAIN: Madrid, 01-6194108 • SWEDEN: Stockholm, 08-820400 • SWITZERLAND: Zurich, 01-7105566 • TAIWAN: Taipei, 2-7077111

INFO/CARD 16

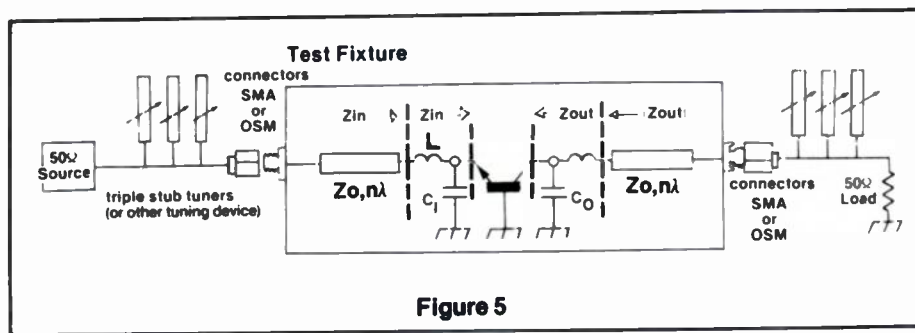


Figure 5

be more desirable. If this is the case, an impedance table for the appropriate conditions may be obtained. It is then for these impedances that C_1 , C_0 and Z_0 will be calculated.

The procedure for obtaining the impedances is simple and requires a vector voltmeter (VVM) or a network analyzer. Both are used at Motorola, but a vector voltmeter is less expensive and if used with a high directivity directional coupler, (>40 db), is very accurate. The set-up is constructed as shown in Figure 5. With the frequency set, stub tuners are adjusted for the desired performance. Again, using the MRF846 as an example, the following numbers were measured:

Pin = 12.0 watts, Vcc = 12.5 volts
 806 MHz 838 MHz 870 MHz
 $P_{out} = 50.0W$ $P_{out} = 48.3W$ $P_{out} = 44W$
 Eff. = 53.3% Eff. = 55.2% Eff. = 58%
 $P_{refl.} = 0W$ $P_{refl.} = 0W$ $P_{refl.} = 0W$

The output stub tuners were adjusted for maximum gain at each frequency and the input stub tuners were adjusted for 0 watts reflected power. After each measurement, the impedance presented to the fixture by the triple stub tuner and load (or source) combination is measured by the vector voltmeter. The impedance is then translated by the transmission line used in the test fixture to obtain $[Z_{in}]$ and $[Z_{out}]$. In the above example, a 26 ohm, .309λ (@836 MHz) transmission line was arbitrarily chosen to be in the MRF846 measurements. By using the equation: $Z/\theta = R_0[(1 + \Gamma/\theta)/(1 - \Gamma/\theta)]$ or various computer or calculator programs, the transformation is easily calculated. The most important part of the whole procedure is obtaining an accurate measurement from the stub tuners. Prior to making any measurements, the vector voltmeter must be referenced to a short (180° on a Smith Chart). As a means of accounting for the errors introduced by the connectors at the fixture's input and output, that same connector is used for a referencing short as shown in Figure 6.

The measurement reference plane is now the edge of the connector used on the test fixture, which is also the

beginning of the transmission line. Assuming the same reference plane is maintained during the measurements, an accurate impedance value will be produced. A good technique for maintaining the appropriate reference plane is accomplished by creating a new connector to measure the triple stub tuners. Two connectors are attached as shown in Figure 7.

The triple stub tuner, load combination may now be measured with an adequate degree of accuracy, as demonstrated in Figure 8.

Repeat the process for the input stub tuner combination. Two numbers are obtained for each frequency from which $[Z_{in}]$ and $[Z_{out}]$ can be calculated from, as shown in the MRF846 example below:

Freq.	Measured Γ/θ	Γ/θ converted to Impedance	Impedance Transformed over 26Ω line
806 MHz	Input 0.35/-155	24.97 + j8.42	20.72-j5.64 $[Z_{in}]^*$
	Output 0.37/-144	24.86 + j12.53	17.72-j6.66 $[Z_{out}]^*$
838 MHz	Input 0.26/-166	29.78 + j3.98	21.35 + j0 $[Z_{in}]^*$
	Output 0.22/-154	33.30 + j6.58	18.68 + j.74 $[Z_{out}]^*$
870 MHz	Input 0.14/-169	38.25-j1.99	20.21 + j6.92 $[Z_{in}]^*$
	Output 0.07/-158	44.10-j2.24	17.90 + j8.3 $[Z_{out}]^*$

Table 3
 Note: $[Z_{out}]^*$ is conjugate of $[Z_{out}]$ $[Z_{in}]^*$ is conjugate of $[Z_{in}]$

The new impedances can be obtained by using a Smith Chart or using the equation $Z/\theta = R_0[(1 + \Gamma/\theta)/(1 - \Gamma/\theta)]$. These impedances (shown in the last column of Table 3) are the impedances around which the test fixture will be optimized. Once again, it is convenient to convert these numbers into parallel equivalents. By doing so, the values of C_1 and C_0 become more obvious. Table 4 shows this process.

From Table 4, notice the calculated values of C_1 and C_0 come close to giving the desired frequency response. C_1 is zero at the band center, indicating the capacitors selected for the input is optimum. The values for C_0 produce a slight skew in performance toward the high end of the band. Capacitor values for the output could be reduced slightly, but they will remain the same until final fixture performance is determined.

Since C_1 and C_0 are very small capacitor values, little or no capacitance is actually needed for C_1 and C_0 . However, to allow minor tuning adjustments, a small trimmer capacitor is included at the wear block/transmission line interface.

The final calculation which needs to be performed is that of finding the optimum characteristic impedance for the transmission line. The recommended approach for doing this is to use a computer optimization program which will iterate any number of variables for a desired frequency response. The variables available to be optimized at this point are Z_0 , C_1 and C_0 and even nλ (transmission line length). Z_0 , C_1 and C_0 are the very minimum variables.

In the example of the MRF846,

where input R_p varies from 22.3 ohms to 21.6 ohms over the frequency band, a close approximation can be had by using a mean value of 21.9 ohms. This results in a Z_0 of $\sqrt{50 \times 21.9} = 33$ ohms. The output R_p starts at 20.2 ohms, dips to 19.7 ohms and goes back up to 21.75 ohms. Using the same method as before, Z_0 is calculated as $\sqrt{50 \times 20.2} = 31.7$ ohms where 20.2 ohms is the mean value of 18.7 and 21.75. Using

Series Impedance $[Z_{in}]$ & $[Z_{out}]$	R_p	X_p	Capacitance Required
20.72 + j5.64	22.26	j81.8	2.42 pF C_1
17.72 + j6.66	20.2	j53.8	3.67 pF C_1
21.35 + j0	21.35	∞	0 pF C_1
18.68-j.74	18.7	j472	.40 pF C_0
20.21-j6.92	21.6	-j68.3	-2.68 pF C_1
17.90-j8.3	21.75	-j46.9	-3.90 pF C_0

Table 4

NEC

Silicon Monolithic IC's

Small Package and Low Cost


Cascadable RF Amplifiers

NEC's Silicon Monolithic IC series, now available in small "can" packages, is the ultimate choice for your narrow or broadband applications up to 1300 MHz. Available in chip form or metal hermetic packages, the series assures uniform performance and reliability at a low cost.


The MM765 and MM766 series, both matched to 50Ω, are cascadable for multistage applications. The MM765 features excellent linearity with over +10 dBm output power at 1 dB compression. The MM766, with an output power of over +3 dBm, is an excellent driver for the MM765.

NEC's Silicon Monolithic IC's are now ready for delivery to meet all your production needs. For immediate information, circle #150 on the reader service card.

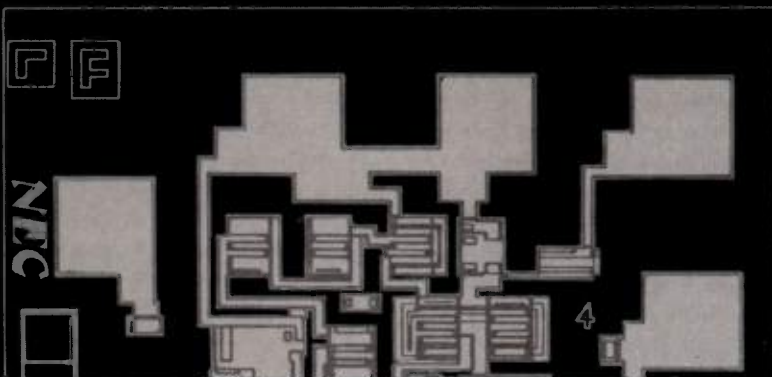- Broadband performance
- Matched to 50Ω
- Chip or hermetic packages
- High reliability
- Cascadable



MM PART NUMBER Package Code			MM76515 15 (TO-33)			MM76612 12(TO-72)		
SYMBOLS	PARAMETERS AND CONDITIONS	UNITS	MIN	TYP	MAX	MIN	TYP	MAX
I _{cc}	Operating Current at V _{cc} = 10V V _{cc} = 5V	mA mA	38	43	48	15	20	25
S ₂₁	Power Gain at f = 500 MHz, V _{cc} = 10V V _{cc} = 5V	dB dB	17	19	21	16	18	20
NF	Noise Figure at f = 500 MHz, V _{cc} = 10V V _{cc} = 5V	dB dB		5.5	6.5		5.5	6.5
BW	Bandwidth at V _{cc} = 10V, (3 dB BW) V _{cc} = 5V, (3 dB BW)	MHz MHz	950	1100		1100	1300	
P _{1dB}	Output Power (1dBc) at f = 500 MHz, V _{cc} = 10V V _{cc} = 5V	dBm dBm	9	10.5		3	5	
IM ₃	3rd Order Intermodulation at f ₁ = 500 MHz, f ₂ = 510 MHz f = 2f ₁ - f ₂ , V _{cc} = 10V, P _{out} = 0dBm V _{cc} = 5V, P _{out} = -7dBm	dB dB		-40			-40	
S ₁₁	Input Return Loss at f = 500 MHz, V _{cc} = 10V V _{cc} = 5V	dB dB	-15	-18		-20	-23	
S ₂₂	Output Return Loss at f = 500 MHz, V _{cc} = 10V V _{cc} = 5V	dB dB	-9	-12		-13	-16	
S ₁₂	Isolation at f = 500 MHz, V _{cc} = 10V V _{cc} = 5V	dB dB	-24	-27		-25	-28	

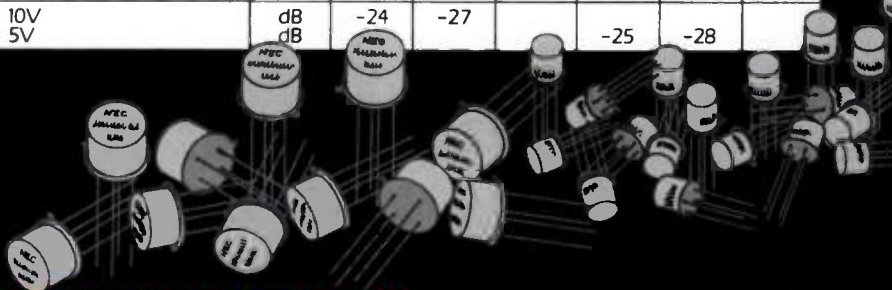

CALIFORNIA EASTERN LABORATORIES, INC.—U.S. and Canada
Exclusive sales agents for **NEC Corporation**, Microwave Semiconductor Products.

Headquarters, Santa Clara, CA 95050 • 3260 Jay Street • (408)988-3500 • Tlx. 34-6393 or 171197

In Europe Contact: **NEC Electronics (Europe) GmbH** • Oberrather Strasse 4 • 4000 Düsseldorf 30 • West Germany
Tel. 0211/50301 • Telex 841/9581252 or 8574410

a computer optimization program, a 32 ohm, quarter wave transmission line is optimum for the input and a 30 ohm quarter wave line is optimum for the output. These are the values used in the MRF846 test fixture.

After constructing the MRF846 test fixture and tuning the small trimmer capacitors for best overall gain and input reflected response, the average data shown in Graph 1 was obtained.

The goal was to demonstrate 12/40 W across the band with better than 2.0:1 input VSWR and better than 45% collector efficiency. Further optimization could be done by performing impedance measurements on additional transistors or characterizing the test fixture more accurately. However, the above performance is very satisfactory to the required performance. The best compromise for a second pass fixture would be to tradeoff gain at 806 and 838 MHz for efficiency, and redesign input and output matching networks for the new impedance tables. This, of course, is only one of the many procedures which may be followed in developing an 800 MHz test fixture.

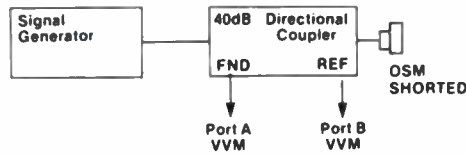


FIG. 6


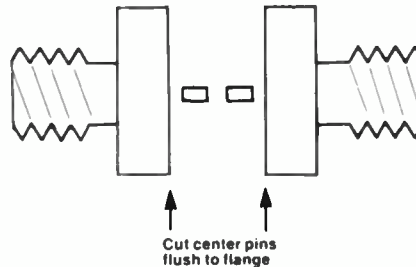
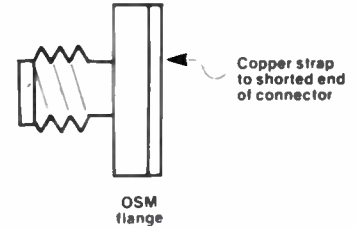


FIG. 7

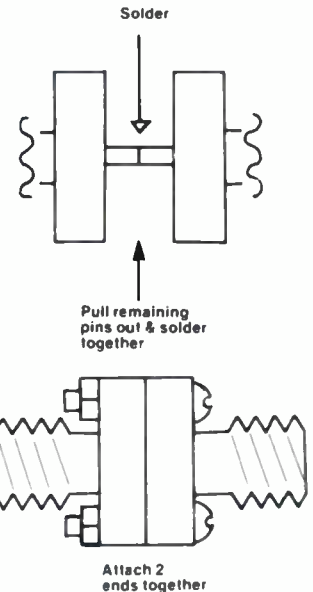

PIEZO's Little Wonder.

Superb performance in a plug-in compatible replacement for HP 10544A/B/C or HP 10811A/B oscillators.

- | | | |
|--|--|--|
| <input type="checkbox"/> High short term stability | <input type="checkbox"/> Low power consumption | <input type="checkbox"/> Rugged construction for extra shock and vibration control |
| <input type="checkbox"/> Low phase noise | <input type="checkbox"/> DRAT* SC cut crystal | |
| <input type="checkbox"/> Fast warm up | <input type="checkbox"/> Fast delivery | |

PIEZO's new Model Number 2810007 Series oscillators are designed for equipment requiring a compact, rugged, precision frequency source. The DRAT (*doubly rotated AT) stress compensated (SC cut) crystal offers the advantages of a longer life and a lower operating cost. This makes the 2810007 an ideal, cost effective oscillator for precision time keeping, instruments, communication and navigation equipment.


The PIEZO standard of quality guarantees you this kind of performance:

- Aging rates: < 5 parts in 10^{10} /day
- Phase noise: Better than 160 dbc at 10 kHz offset
- Warm up: Within 5 parts in 10^9 of

final frequency in 10 minutes

- Time domain stability: Better than 5 parts in 10^{12} for a 1 second averaging time
- Power consumption: Approximately 2 watts after warm up
- Output frequency: 10 MHz or 10.23 MHz standard

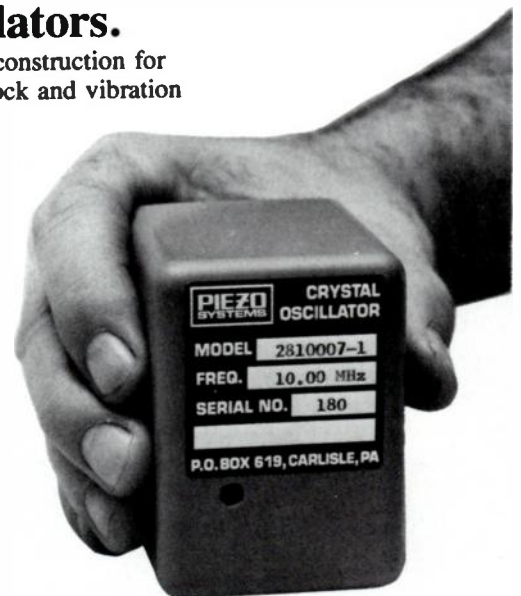We offer *fast* delivery, with limited orders shipped directly from stock. PIEZO Systems is an affiliate of PIEZO Crystal Company, a leader in the production of piezo-electric crystals since 1936. For more information call your nearby PIEZO representative, or write to PIEZO SYSTEMS, P.O. Box 619, Carlisle, PA 17013. Telephone (717) 249-2151.



*** Best aging available to date: parts in 10^{12} /day!**





These signal generators from Marconi will change your way of thinking.

Think about testing receivers quickly. Wouldn't it speed your operations if all your signal generators gave the same answers and if your operators could recall complete test settings at the touch of a button even after the instrument had been switched off. Or when setting up a GPIB system, wouldn't you like your controller to be able to learn the settings of the generator.

Think about maintaining your signal generator easily. How much down time could microprocessor assisted fault diagnosis and recalibration from the GPIB or front panel save you? Wouldn't you like the reliability of a cool-running instrument, with no noisy fan to maintain.

Think about cost . . . would a quality signal generator giving all this with wide

frequency coverage and 10Hz resolution really cost more than you can afford? Marconi have a pleasant surprise for you!

2018 and 2019 Well Worth Thinking About

80kHz to 520MHz or 80kHz to 1040MHz frequency coverage

Non-volatile memory

Save operator time – recall up to 50 settings at any time – even after switch off

RF Level offset

Save arguments – standardise your microvolt and compensate for cable losses

GPIB Talker facility

Save program preparation time – let the GPIB controller learn the instrument settings

Reverse Power Protection

Save maintenance costs – no more burnt out attenuators to repair

Recalibration via Keyboard or GPIB

Save recalibration costs – adjust r.f. level and f.m. deviation calibration without removing the covers

Fully programmable

Save measurement time – automate your testing

Contact Marconi today – they will change your way of thinking.

marconi
instruments 

U.S.: 100 Stonehurst Court, Northvale, NJ 07647
(201) 767-7250 (East) (714) 857-2326 (West)
U.K.: Longacres, St. Albans, Herts. AL4 0JN
Country Code 44 (0727) 59292 TELEX 23350
FRANCE: (1) 687-36-25 **GERMANY** (089) 845085

INFO/CARD 19

Some Questions You Should Ask Your EMI/RFI Test Equipment Supplier

How long has your company been in the EMI/RFI Testing Equipment business?


The Electro-Mechanics Company has been designing and manufacturing EMI/RFI Test Accessories for over 25 years.

We began with Magnetic Field Instruments and Radio Frequency Antennas for the military. Since the mid-sixties we have been working closely with the military and industry standard setting groups, and EMCO now has one of the broadest lines of Test Antennas and EMI/RFI Test Accessories in the World.

What exactly is your major product line?

EMCO's primary business is Test Antennas for use in Emissions and Immunity (Susceptibility) Testing as required for MIL Standard, FCC, VDE, and CISPR Test Procedures.

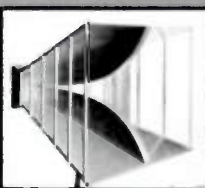Typical Military Antennas for Radiated Immunity (RS) and Emissions (RE) Testing cover the frequency ranges from 30 Hz to 18 GHz, and are noted in MIL STD 462, Notice 3, Table 1. EMCO currently manufactures Magnetic Field Loops, the 41" Rod Antenna, Parallel Strip Line, both



Biconical Antennas, the **Conical Log Spirals** and the **Double Ridged Guide Antennas** shown on this table.

Antennas which are currently acceptable for use in FCC Volume II, Part 15 Emissions Testing include, **Adjustable Element Dipole Sets**, **Broadband Biconical Antennas** and **Broadband Log Periodic Antennas**. EMCO manufactures all of these separately or can include them as part of an FCC "Class A" and "Class B" Antenna Test System.

What differentiates your antennas from your competitors?

One major difference is Calibration. Each Antenna is calibrated using NBS Traceable Testing Equipment, on our own FCC open field test site. Calibration data includes Antenna Factor, Numeric Power Gain, and dBi Gain for each individual Antenna. For Immunity Testing Antennas we include Field Strength measurements in Volts Per Meter, and Radiation Patterns where applicable.

Another difference is Design and Construction. Each Antenna is designed to be durable and long-lasting, yet functional in varied applications, such as in Anechoic Chambers or Outside Test Sites. Antennas and accessories are machined and constructed "in-house" for Optimum Quality Control.



improvement thru Research and Development. For example, our **Dipole** and **Biconical Balun** design is much improved from the old DM-105 and military designs . . . and we are continually researching and redesigning to make EMI/RFI Testing simpler and more accurate.


What other Test Equipment and Accessories do you offer?

EMCO adds efficiency to EMI Testing with an **Antenna Positioning Tower** (1-6 meters) and an **Equipment Testing Turntable**. Both are suitable for outside or indoor use, come with a standard Digital Readout Controller and are available with **IEEE-488 Bus Option**.



For Conducted Emissions Testing, EMCO manufactures **Line Impedance Stabilization Networks** to satisfy FCC and VDE requirements. Our unique design allows production of as many as 4 separate lines (three phase) in one unit.

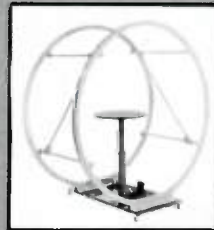Other Related Equipment include: **Signal Rejection Networks**, **Acceptance Networks**, **Magnetic Field Intensity Meters**, **Magnetometers** and **Helmholtz Coil Systems**.



Why should my company buy your EMI/RFI Test Equipment?

The Electro-Mechanics Company is more than just another manufacturer. We realize that in order to grow and help improve EMI/RFI Testing we must constantly forge ahead . . . not live in the past.

As the FCC moves toward better and more Standardized Test Procedures, EMCO is staying close to ANSI (American National Standards Institute), NBS (National Bureau of Standards) and other standards groups so we can keep improving our equipment. Involvement with current and future industry needs also helps us plan for design of new equipment . . . an ongoing process at EMCO.

EMCO is committed to offering Technical Assistance, as well as Test Accessories, to help solve EMI Testing Problems. Part of that Technical Assistance is advice on purchasing only the equipment needed, not kits or systems with unnecessary items. We can also advise on various manufacturers of other complimentary test equipment.

If you have more questions and are looking for Helpful Answers, Call us at (512) 835-4684.

The Electro-Mechanics Company

P.O. Box 1546/Austin, Texas 78767/Telex 767187
INFO/CARD 20

High Performance VSWR Measurements

The Return Loss Bridge is a useful device for making low power precision VSWR measurements. This article describes the operation and use of this instrument.

By James S. Beck
Eagle Consultants
Fallbrook, CA 92028

This article describes the operation and use of the Return Loss Bridge. This includes a basic definition of terms, outlines of test and other background information. Although there are many methods available to perform VSWR measurements, ranging from sliding lamps down a transmission line to highly precise slotted lines, only directional bridges will be addressed in this article.

Background

What is VSWR, rho, and return loss?

When reading specifications describing various equipment one often see references to VSWR, or possibly rho or return loss. These are all expressions for the same quantity and if one is known the others can be determined by simple mathematics.

These quantities are defined as follows:

VSWR: This is the maximum amplitude on a transmission line to the

minimum amplitude on the transmission line; this is expressed mathematically as:

$$VSWR = \frac{V(MAX)}{V(MIN)}$$

ρ : Is the Greek letter "rho" and expresses reflection coefficient; this is described mathematically as:

$$\rho = \frac{VSWR-1}{VSWR+1}$$

It can be seen when VSWR is infinite $\rho = 1$ and when the VSWR = 1 then $\rho = 0$. By multiplying ρ times 100 and squaring the percentage of power reflected into the source is found.

Return Loss: This is simply the logarithmic expression of rho. This is defined as return loss (dB) = $-20 \log_{10} \rho$. This quantity is the amount of power returned to the source relative to the amount of power delivered.

Return Loss Conversion Chart

Return Loss	Rho	SWR
1.0	0.89	17.4
3.0	0.71	3.0
5.0	.56	3.6
10.0	.32	1.9
15.0	.18	1.4
20.0	.10	1.2
25.0	.056	1.12
30.0	.032	1.07
35.0	.018	1.04
40.0	.010	1.02
50.0	.003	1.006
60.0	.001	1.002

Table 1

Measurements


The measurement equipment will determine the type of data that will be presented. Use of a VSWR meter will provide a scale that presents the data in terms of VSWR. If directional

couplers are used then the absolute reflected power will be known and calculations will put this data into any desired form. A directional bridge will present either rho or return loss depending on the ancillary equipment. It should be noted that directional bridges appear under many names which can be confusing. A directional bridge may be referred to as a rho bridge, return loss bridge, directional bridge or impedance bridge. Generally speaking a bridge that has an internal detector is called a rho bridge while bridges with an RF output use the other terms.

Directional Bridges

Directional Bridges are available in all form and fashion, frequencies range from audio to microwave, some contain internal references while others do not. Bridges may contain internal detectors at the MEASUREMENT PORT or the port may be of the RF variety; finally the price range of these bridges is from \$100 to \$2000.

Figure 1 is illustrative of a typical return loss bridge. The arrows and lines indicate the direction and gain of the power flows through the bridge. For VSWR measurements the source (stimulus or generator) is connected

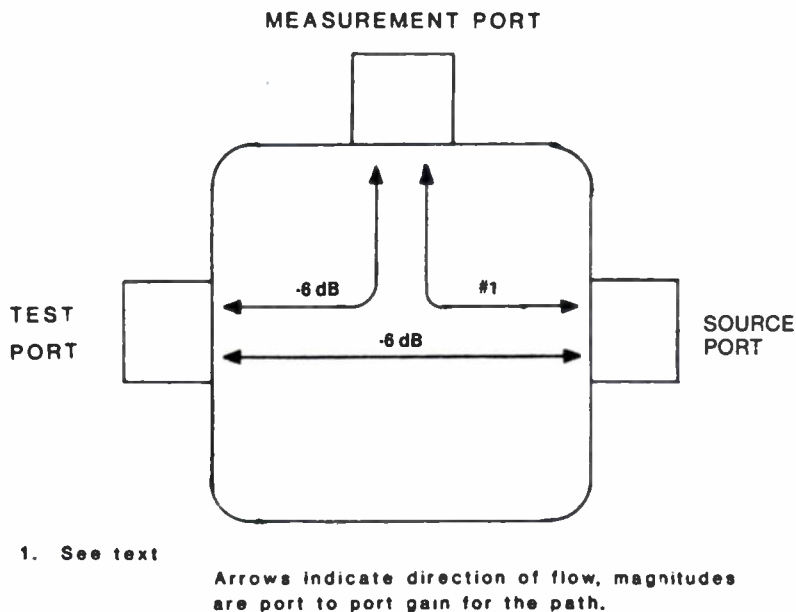

RETURN LOSS BRIDGE PORT CONFIGURATION


Figure 1

HP's Small Wonders


Reliable switches for repeat performance.

- 33311B, SPDT, DC—18 GHz, \$570
- 33311C, SPDT, DC—26.5 GHz, \$750
- 33311B-CO4, 4 Port, Matrix, DC—18 GHz, \$735
- 33311B-CO5, 5 Port, Transfer, DC—18 GHz, \$735



If you need switches that perform with typical 0.03 dB repeatability after 1,000,000 switching operations—and give you features like a momentary 24 VDC (5 VDC optional) magnetic latch that automatically de-energizes coils—just call your local HP Sales Office listed in the telephone white pages. Ask for the Components Department. Or write: Hewlett-Packard Co., 1820 Embarcadero Road, Palo Alto, CA 94303.

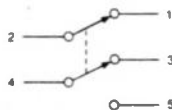

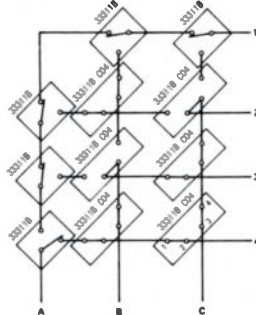33311B-CO5
Use as a two SPDT switches with a common terminal



Build a microwave matrix

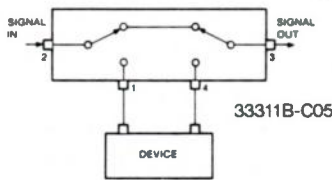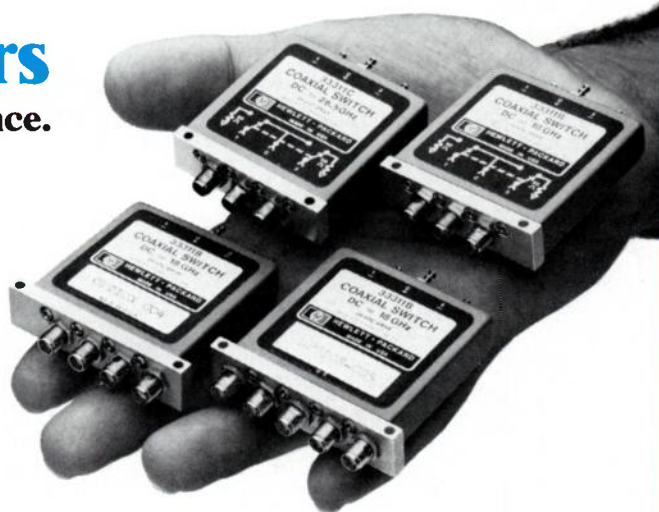

Use for signal transfer



Program on HP-IB using 11713A Switch Driver

USA list prices only. QTY 1-9

0408305B



HEWLETT
PACKARD

TM8 autoranging millivoltmeter

The Texscan TM8 is an autoranging, true r.m.s. millivoltmeter with a specified operating range of 10kHz to 1GHz with useful indications to 1500MHz. It measures r.f. voltages from 1mV to 3V full scale in eight ranges and may be operated automatically (in the autoranging mode), manually or remotely. The maximum voltage measured can be increased to 300V r.m.s. using the 100:1 divider provided and readings on any range can be held for at least three minutes by momentary depression of the probe switch.

Measurements are true r.m.s. but average responding can also be selected with a front panel switch. The meter reads 100 μ V-3V and also features a corresponding dB scale from -60 to +23dBm. A

single logarithmic range is also provided and covers four decades scaled -30 to +10dBm. Fast or slow meter response may be selected to permit the observation or removal of rapid signal amplitude changes.

Remote programming is a standard feature and the socket is located on the rear panel. An output to drive a pen recorder is also provided from this socket and this can be used with an interface module, OB2, to connect to IEEE-488 bus systems.


The TM8 is supplied complete with probe (integral with input lead), probe to BNC adapter, "T" connector, and a 100:1 high impedance divider.



Texscan Instruments
2446 North Shadeland Avenue
Indianapolis, Indiana 46219
Phone: (317) 357-8781
TWX: (810) 341-3184

Texscan

MINIATURE WIDEBAND PIN DIODE SWITCHES

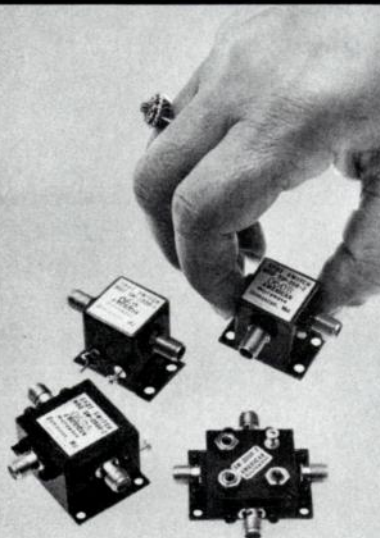

Now you can select the state-of-the-art miniature wideband pin diode switch you need from our stock. AMC Series SW-2000 pin switches (SPST and SPDT) measure only 1" H x 1.2" W x 0.75" L. And, hundreds of these units have already been used to solve solid state switching design problems in communication, aerospace, microprocessor and surveillance applications.

Check these specifications:


- SPST through SP5T Configurations Available
- Frequency: 2-2000 MHz (usable to 4000 MHz)
- Switching Time: 5 μ sec Typical
- Insertion Loss: 1.5 dB, maximum (SPDT)
- Isolation: 40 dB, minimum
- SMA Connectors
- RFI Control Terminals
- RF Power 1 watt CW
- Available with **one load** TTL Drivers

Standard models and quantities available from stock. Special switches designed to your specifications.

For solutions in solid state switching contact:

**AMERICAN
MICROWAVE CORP.**

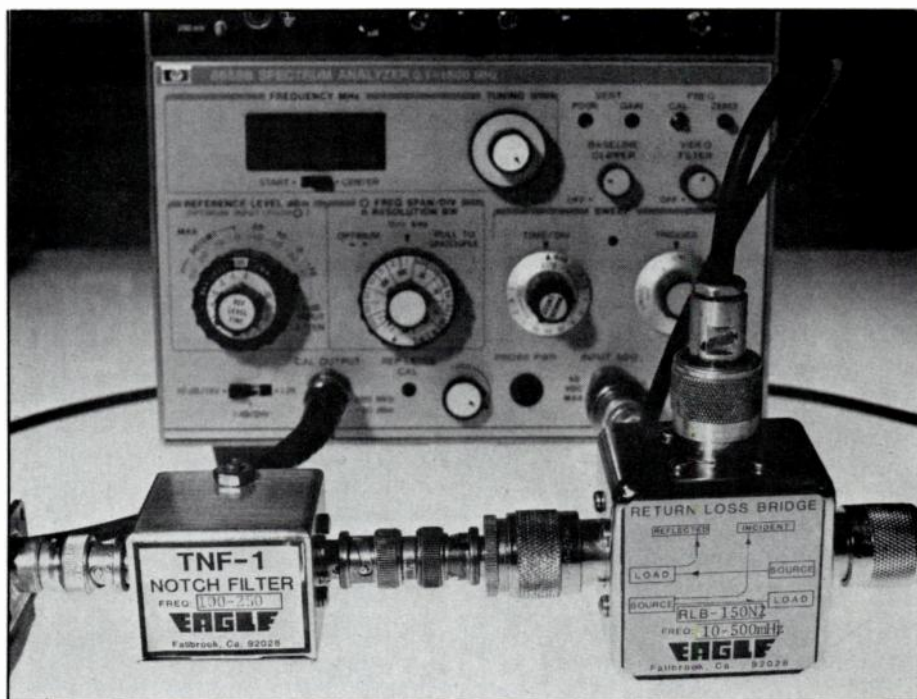6835 Olney-Laytonville Road
Gaithersburg, Maryland 20879
(301) 948-6800



to the right hand port, SOURCE PORT, while the device to be measured (load) is connected to the left hand port, TEST PORT. When the power is applied it flows from the right to left hand port losing 6 dB through the internal resistors in the bridge. If the left hand port is terminated perfectly no power will be reflected from the left hand port. Since no power is reflected there will be no power appearing at the MEASUREMENT PORT, at least theoretically.

Some power will be present at the MEASUREMENT PORT, however, this is due to imperfections in the bridge. This is illustrated by the path from the right hand port, SOURCE PORT, to the top port, MEASUREMENT PORT. The gain of this path will be -52 dB if the bridge has a directivity of -40 dB. The directivity of a bridge is measured by terminating it in a perfect, or near perfect, load and measuring the residual power at the MEASUREMENT PORT. The residual power is then referenced to the amount of power appearing with the TEST PORT terminated in an open or short; the result is converted to dB and becomes the directivity of the bridge. This parameter is very difficult to measure because of the difficulty in finding "perfect" terminations.

Above 500 MHz or so the connector VSWR becomes significant in precision bridges; thus even if a perfect load is presented to the connector interface there is the possibility that the bridge itself is seeing reflections from its own connector. Bridges operating above 500 MHz with specified direct-

ivities of 40 dB or better should use an external reference termination so that the interface connectors at the TEST PORT and REFERENCE PORT are identical. If this is the case then the connector VSWR will factor out.

If the TEST PORT is shorted or opened then all of the power is reflected back to the MEASUREMENT PORT again losing 6 dB due to internal losses in the bridge. Because of the internal losses the infinite VSWR (open or short) will be 12 dB below the amount of power that is present at the SOURCE PORT.

Power may also be applied to the MEASUREMENT PORT. If this is the case it will be transferred to the TEST PORT again losing 6 dB. Thus if a generator is connected to the MEASUREMENT PORT and another generator is connected to the SOURCE PORT the signals from these generators will be combined by the bridge. This combined power will appear at the TEST PORT. If the TEST PORT is terminated in a reasonable load no power will be reflected back from the TEST PORT; thus the generators will be well isolated from each other. This technique is useful in making intermodulation distortion tests and other measurements requiring two generators.

It should be remembered that the losses through the paths in the bridge are theoretical 6 dB. In actual practice these losses will be somewhat greater than 6 dB. In a good bridge 7 to 7.5 dB is not unreasonable at higher frequencies.

Clean sweep to 1 GHz.

50 watts minimum is a lot of rf power throughout a bandwidth of 1 to 1000 MHz. But that's what our new Model 50W1000 delivers for all your broadband test needs.

As your hunger for power plus bandwidth grows, this year and next, our all-solid-state "W" series

of 100-kHz-to-1000-MHz linear amplifiers should become more and more important in your plans. Today you may need only 1 watt (the little portable on the top of the pile), or 5, or 10—all with that fantastic bandwidth instantly available without tuning or bandswitching—the kind

of bandwidth that lets you sweep clean through with no pausing for adjustment.


And next year?

But chances are good that next year you'll be moving up into higher-power work in the same bandwidth. Then you'll be glad you have a 50W, the *only* rf power amplifier in its power-to-bandwidth class. At that point, your smaller "W" series amplifiers can be freed for lower-power work around your lab.

What you can't see in the performance curves shown below is the unconditional *stability* of all Amplifier Research amplifiers—immunity to even the worst-case load mismatch or shorted or open cable with no fear of damage or system shutdown.

The "W" series is part of a complete line of amplifiers offering rf power up to 10,000 watts cw, for such diverse applications as plasma/fusion research, NMR, RFI susceptibility testing, and a host of other test situations that demand the very finest in broadband rf power.

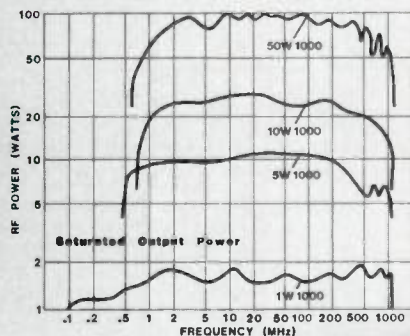Send for our free booklet, "Your guide to broadband power amplifiers."




**AMPLIFIER
RESEARCH**

160 School House Road, Souderton, PA 18964 USA
Phone 215-723-8181 • TWX 510-661-6094

INFO/CARD 24

HIGH POWER EPSCO

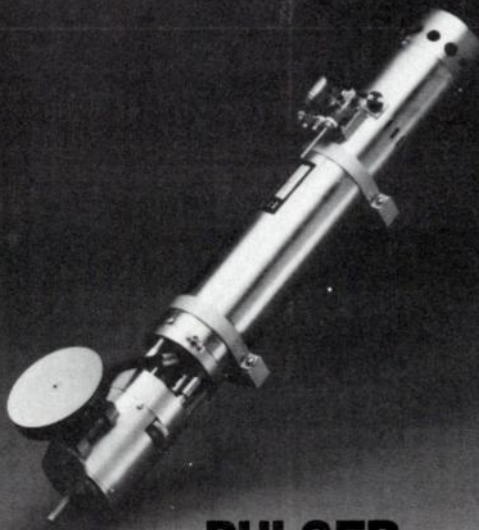

PULSED CAVITY OSCILLATORS

EPSCO designs and manufactures high power cavity oscillators to customer specification as well as for use in our own signal sources. Precision-engineered for accurate, trouble-free tuning, each is capable of long life and reliability in even the most demanding military environments.

Featuring:

- Broad frequency range
- High stability at all frequencies
- Wide power output range
- Pulse width/duty cycle variability
- Silver-plated and rhodium finished

TO MEET YOUR SPECS

For more information or discussion of your specific needs, give us a call today.



411 Providence Highway
Westwood, MA 02090
(617) 329-1500.
TWX: (710) 348-0484.

INFO/CARD 25

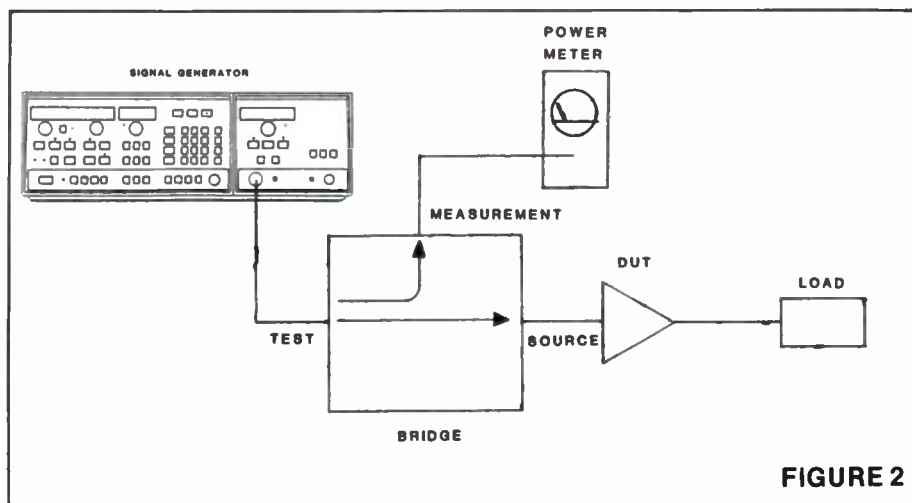


FIGURE 2

Bridges that provide an RF signal at the MEASUREMENT PORT tend to be more expensive because of the increased complexity of manufacture. These bridges are much more versatile. By using a spectrum analyzer several signals can be measured at one time. With an internal diode detector, this would be impossible and the signals would have to be removed in order to get an accurate measurement. With an RF MEASUREMENT PORT, phase information is present which can be very useful. Also, power can be fed into the MEASUREMENT PORT thus allowing the bridge to be used for power combining purposes.

Depending on the application an external or internal reference might be desirable. In most applications an internal reference is preferred because it simplifies the measurement and the requirement to maintain precision terminations. High precision measurements require the connector VSWR to be factored out by using identical connectors on the reference and test ports. On bridges equipped with the "F" type connector this is a must to obtain any reasonable reading at all.

Applications

In addition to the standard function of making return loss measurements, return loss bridges may also be used for other tests that are very common in the RF laboratory. The following uses are just some of the many applications of an instrument equipped with an RF MEASUREMENT PORT.

Drive Power Measurement

In this circuit (Figure 2.) the power meter will read the amount of power being delivered to the DUT, assuming the DUT has the same impedance as the bridge. In this case the power rating of the bridge will determine the amount of drive power that can be applied

to the input port. Remember that since the power is split there will be a 6 dB power reduction. Bridges are available with up to a five watt power rating which would allow 1.25 watts drive to the DUT.

Power Combining for TWO-TONE Tests.

In this case (Figure 3.) the output to the TEST PORT will be the combination of signals produced by the two generators. The generator port to port isolation will be approximately the same as the specified directivity of the bridge at the two test frequencies. This feature will aid in preventing intermodulation distortion because the signal generators will be well isolated from each other. The above test set can be used for measuring the IM performance of a DUT. If intermods are present, set the spectrum analyzer to 10 dB of RF attenuation to check that the intermods are not coming from the spectrum analyzer.

Amplifier Input Return Loss

A signal generator (Figure 4.) is connected to the SOURCE PORT of the return loss bridge and the amplifier (DUT) is connected to the TEST PORT. A power meter connected to the MEASUREMENT PORT will now indicate the amount of power reflected by the DUT. Be sure to add six dB to the power meter's reading because of the six dB loss in the arm between the TEST and MEASUREMENT port.


There is also a power loss of six dB between the SOURCE and TEST port; this means that the amount of drive available to the DUT will be reduced by six dB. The maximum amount of drive that can be applied will depend on the power rating of the bridge. A one watt rated bridge will deliver .25 watts while a bridged rated at 5 watts can safely deliver

March/April

Complete Systems for EMI/EMC Testing from Electro-Metrics

Electro-Metrics offers a broad range of instrumentation and total systems to test both emissions and susceptibility.

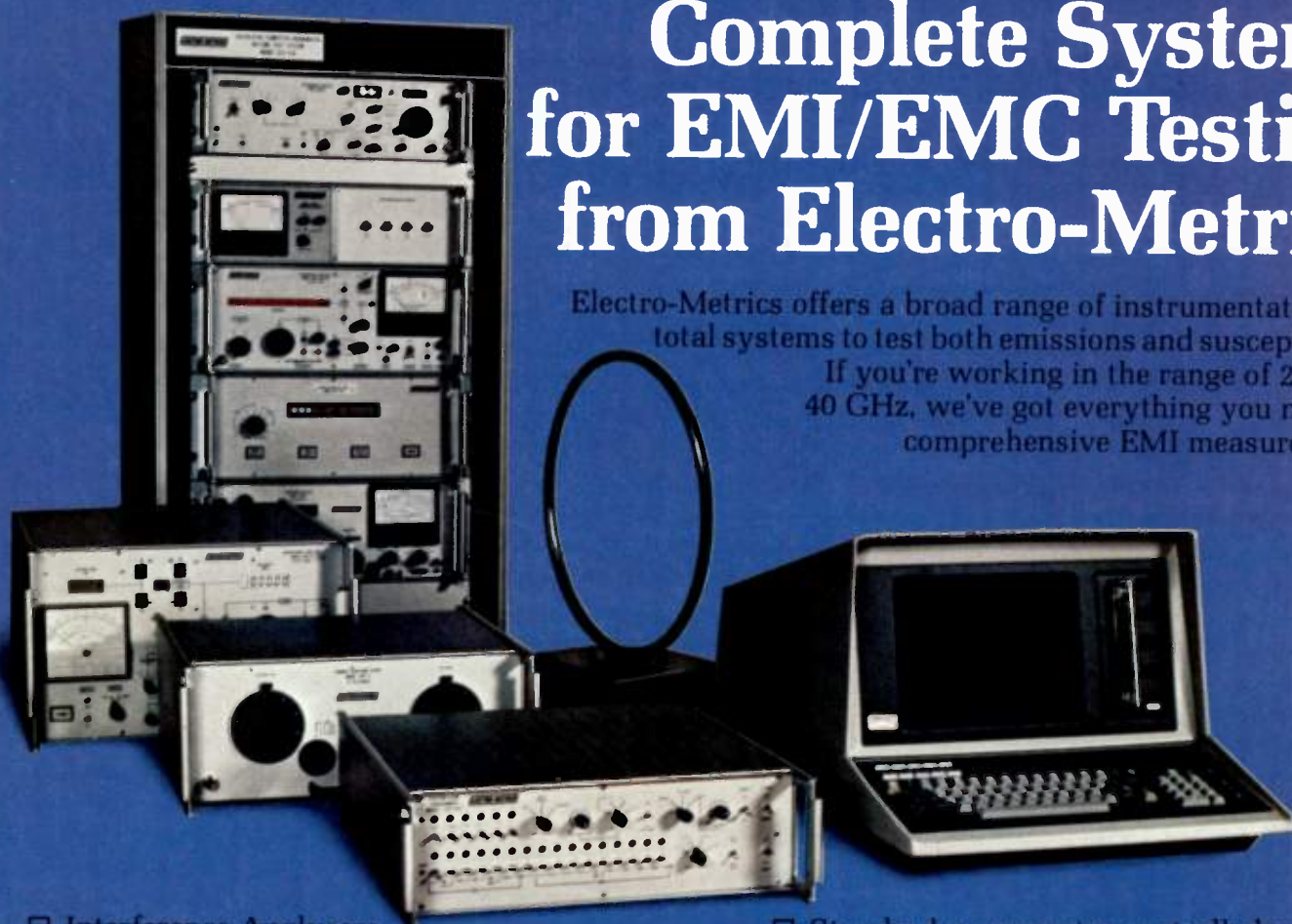If you're working in the range of 20 Hz to 40 GHz, we've got everything you need for comprehensive EMI measurements.



- ☐ Interference Analyzers
- ☐ Spectrum Analyzers
- ☐ Emissions and susceptibility testing

INFO/CARD 91

- ☐ Standard or computer-controlled systems for automated testing
- ☐ 20 Hz to 40 GHz



**NTR-51
TEMPEST Test
Receiver**

Can your emanations pass the special tests of NACSIM 5100A? The NTR-51 TEMPEST Test Receiver will let you know. Its unmatched performance permits the operator to select nearly any combination of low-noise amplification and filtering characteristics.

- ☐ 100 Hz to 1 GHz @ 50 ohms
- ☐ Up to 80 dB gain
- ☐ Bandwidths from 45 Hz to 995 MHz

INFO/CARD 90

For more information, call or write:



**NEW!
Electrostatic
Discharge (ESD)
Simulators**

For testing ESD susceptibility of electronic equipment as well as IC's and discrete components.

- ☐ Generates repeatable, fast rise-time high-voltage waveform (up to 30 kV)
- ☐ Simulates human and inanimate object ESD waveforms
- ☐ Compact and portable
- ☐ Developed by Experimental Physics Corporation

INFO/CARD 26

100 Church Street
Amsterdam, New York 12010

ELECTRO-METRICS

A PENRIL COMPANY

Tel.: (518) 843-2600
TWX: 710-446-4798

or not the exact power can be calculated by the following formula:

$$P_r = P_t G_t G_r \lambda^2 / (4\pi R)^2$$

Where:

λ = wavelength in meters
 G_r = gain of receiving ant.
 G_t = gain of transmit ant.
 P_t = transmit power
 R = distance in meters
 P_r = received power

After making the calculation if there is still any doubt than connect a power meter such as a Bird thru-line to the antenna system; and measure the power level present. Remember if there is more than one transmitter, the power levels are cumulative.

CAUTION: Insure that the colocated transmitters are on while making antenna power measurement.

As long as the incoming power level is below the rated power level of the bridge the measurement can be safely made. A bridge rated at five watts can normally be used with no problem. The Figure 6 illustrates a typical measurement system for antennas:

The power meter is indicating 1.25 watts at the MEASUREMENT PORT of the return loss bridge; and the signal generator isn't even turned on yet. The power meter is reading the power from the FM station which is being received by antenna at KTV. It was anticipated that the generator would supply a signal of +12 dBm and the directivity of the antenna would be 35 dB. Since 12 dB is lost through the arms of the bridge, the signal returned would be -35 dBm. This is 66 dB below the signal being received from KFM which is +31 dBm. No way can the measurement be made while KFM is on.

If the return loss bridge has a DC MEASUREMENT PORT you are out of luck. Your reflected signal and KFM's are combined by the detection diode; internal in the return loss bridge. The only hope is to shut KFM off while the measurements are being made. If the return loss bridge has an RF MEASUREMENT PORT then simply replace the power meter with a spectrum analyzer.

The Figure 7 illustrates the test system with a spectrum analyzer substituted for the power meter. A notch filter is also installed and is adjusted to suppress KFM an additional 25 dB, this insures that the analyzer front end is not overloaded. Note that the dynamic range is narrowed to approximately 40 dB; well within the 60 dB limit of an economical spectrum analyzer.

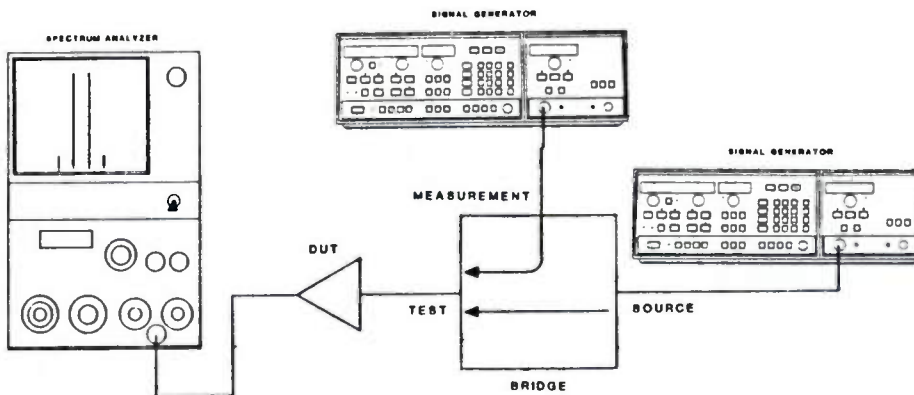


Figure 3

1.25 watts. If more than 1.25 watts is required a different technique will have to be utilized.

Amplifier Output Return Loss

In this test (Figure 5) the amplifier (DUT) is connected to the TEST PORT while an attenuator is connected to the SOURCE PORT. A signal generator is then connected to the other side of the attenuator. A second attenuator is connected to the MEASUREMENT port of the return loss bridge. The attenuators are to protect the spectrum analyzer and signal generator from damage.

The test procedure is as follows:

1. Adjust the signal generator (#2) to the amplifier carrier frequency plus or minus the narrowest separation required by the spectrum analyzer to discriminate between the two signals.
 2. Apply enough power from generator 2 so that the power level at SOURCE PORT is approximately 10 dB below output level of amplifier under test.
 3. Apply drive to amplifier and adjust for maximum or test output power.
- CAUTION!** Bridges can handle no more than rated power!!

Antenna System Return Loss

Antenna measurements can be readily made using return loss bridges.

Before covering the actual measurements it will be beneficial to discuss some of the considerations involving real world antenna measurements. Antenna measurements present a unique and sometimes hazardous situation due to congestion and collocation of equipments. Antennas that are connected to high power transmitters may be located within several hundred feet of each other. Thus, there may be considerable energy present at the terminals of the antenna to be tested.

Before commencing any measurement, study the location to determine if any other system could radiate enough power into the antenna under test to cause equipment damage. The chart below will aid in making this determination:

Power Level	Minimum Safe Distance	Power Received
1000 watts	100 feet	.24 watt
10000 watts	500 feet	.10 watt
100000 watts	1000 feet	.24 watt

The above chart is based on both stations using unity gain antennas on an operating frequency of 50 MHz. If frequency is lower gain will be higher and vice versa.

If there is some doubt as to whether the measurement can safely be made

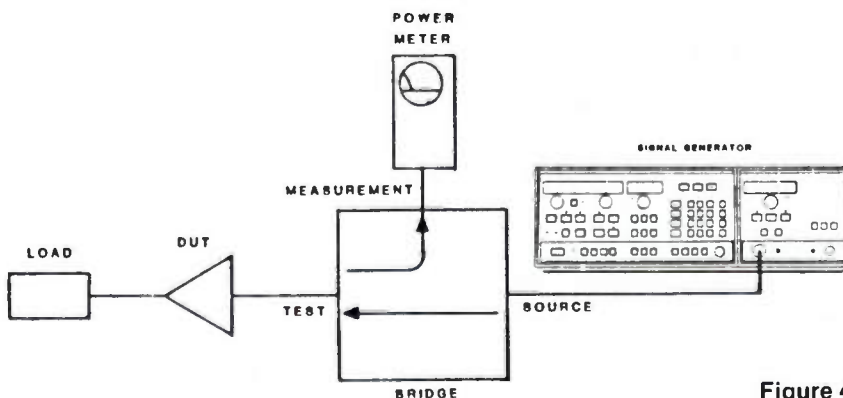


Figure 4

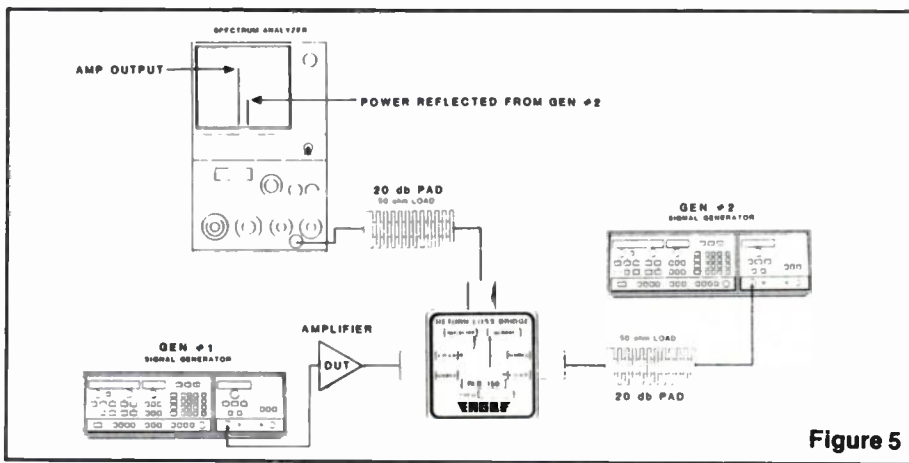


Figure 5

Mixer Port Return Loss and Isolation

The advent of high level diode mixers has brought with it associated problems in testing these devices. Parameter measurement is a time consuming and elaborate process that requires much care. The test system shown below will measure all important mixer parameters simultaneously, this includes port return loss, port to port isolation and intermodulation distortion. If sweep generators are used, this can be a swept test that covers the frequency range of the return loss bridge. Using this setup mixer can easily be tested in less than five minutes.

The test procedure is as follows:

1. Apply drive and RF power at desired levels. Read LO port return loss on SA 1. Since the return loss bridge incident (MEASUREMENT PORT) port is sourced by the mixer read RF feed through on SA 1. If desired LO power can be varied while return loss and feed through are monitored.

2. On SA 2 observe the RF port reflected power and feed through from the LO and IF ports of the DUT. To run intermodulation select generator

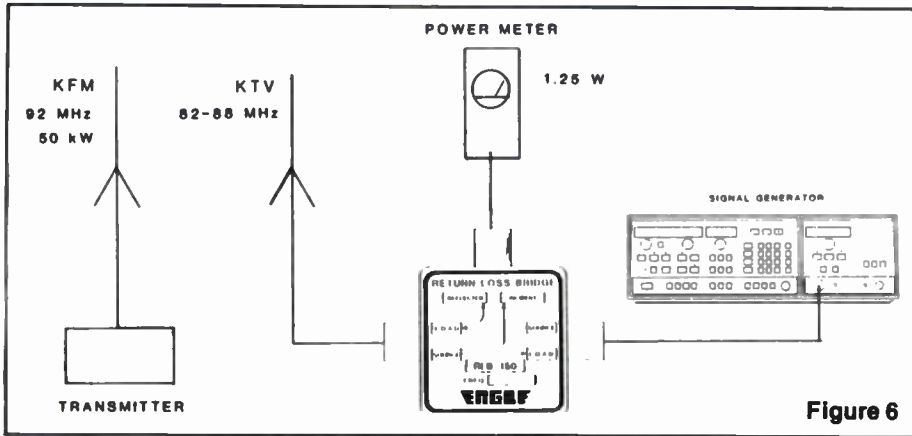


Figure 6

THE PROBLEM: THE SOLUTION: THE FACTS:


Design and build a distribution Amplifier with noise immunity and drive capability to interface a localized frequency standard to other equipment at distances up to 1000 feet.

The Austron Model 1295C, which receives any one of four (4) standard frequencies (10 MHz, 5 MHz, 1 MHz and 0.1 MHz) and distributes up to 40 individual outputs of the input frequency. Frequencies different than the input can be created and distributed in groups of four.

1. The harmonic distortion is down more than 40 dB from the 1 Vrms output.
2. The non-harmonic related distortion is down more than 60 dB from the rated output.
3. Channel isolation is greater than 50 dB.
4. Reversible mounting (all outputs on back or front of chassis).
5. Modular design for expandability (up to 40 outputs) and reconfiguration.
6. Built-in test equipment with fault isolation to card.

40/100 kHz — 10 MHz
Outputs

Fault Lights
Input Module

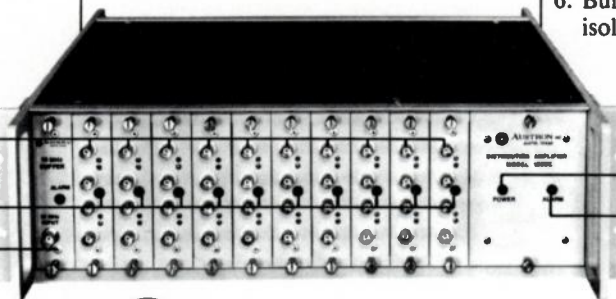

Power On
Fault Alarm



AUSTRON INC.
P.O. Box 14766, Austin, Texas 78761
(512) 251-2313 TWX 910/874-1356

For additional information, contact Austron
Time and Frequency Division.

One Antenna Kit with everything, to go please.

A complete line of kits with upper limits to 18GHz that satisfy FCC, VDE, and MIL-STD 461 specifications, and more.



Available now from your source for the finest EMI test equipment and accessories.

Antenna kits that meet your specifications of high quality and frequency response, and that are also responsive to your demands of portability and easy use. A.H. Systems offers nine different kits that fill the bill. Each comes in a single, lightweight case. Just one kit can contain all the antennas, probes and cables to perform E-Field 1KHz-18GHz, H-Field 20Hz-50KHz and conducted 20Hz-100MHz testing. Antenna factor calibrations are provided with each antenna.

So order one to go, with everything, or one of our other tantalizing specials.

MODEL #	FREQ. RESP.	DESCRIPTION	MODEL #	FREQ. RESP.	DESCRIPTION
SAS-200/510	300 - 1800 MHz	Log Periodic	SAS-200/542	20 - 300 MHz	Biconical, Folding
SAS-200/511	1000 - 12000 MHz	Log Periodic	SAS-200/550	001 - 60 MHz	Active Monopole
SAS-200/512	200 - 1800 MHz	Log Periodic	SAS-200/560	per MIL-STD-461	Loop - Emission
SAS-200/518	1000 - 18000 MHz	Log Periodic	SAS-200/561	per MIL-STD-461	Loop - Radiating
SAS-200/530	150 - 550 MHz	Broadband Dipole	BCP-200/510	20 Hz - 1 MHz	LF Current Probe
SAS-200/540	20 - 300 MHz	Biconical	BCP-200/511	100 KHz - 100 MHz	HF VHF Crnt. Probe
SAS-200/541	20 - 300 MHz	Biconical Collapsible			

A.H. Systems
9710 Cozycroft Avenue
Chatsworth, CA 91311
(213) 998-0223

A.H. SYSTEMS

INFO/CARD 28

WJH

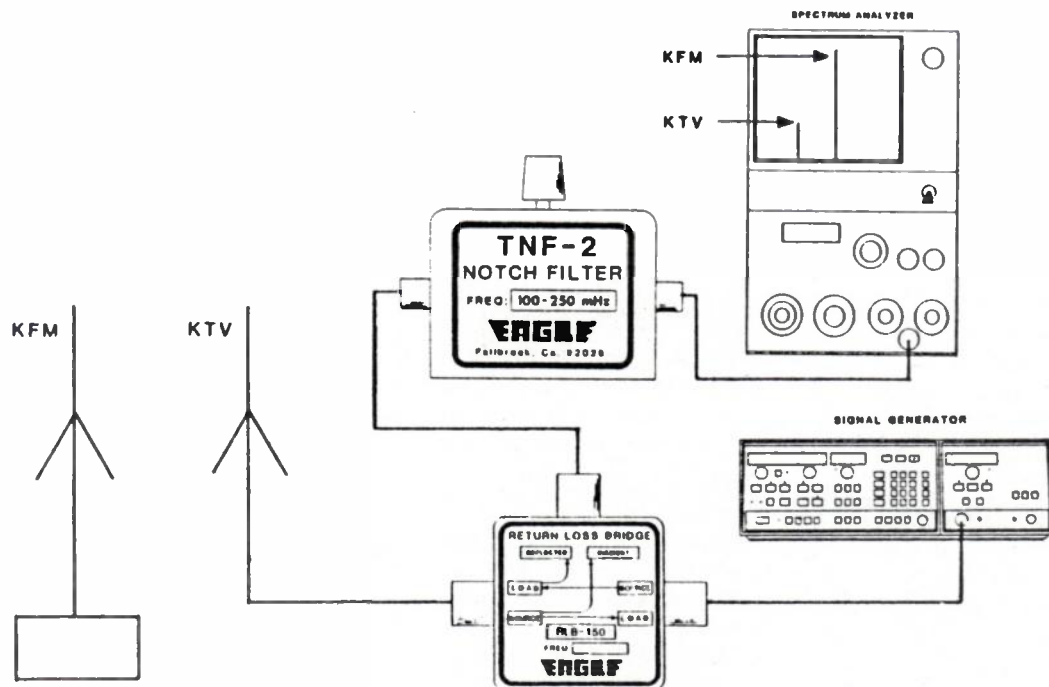


Figure 7

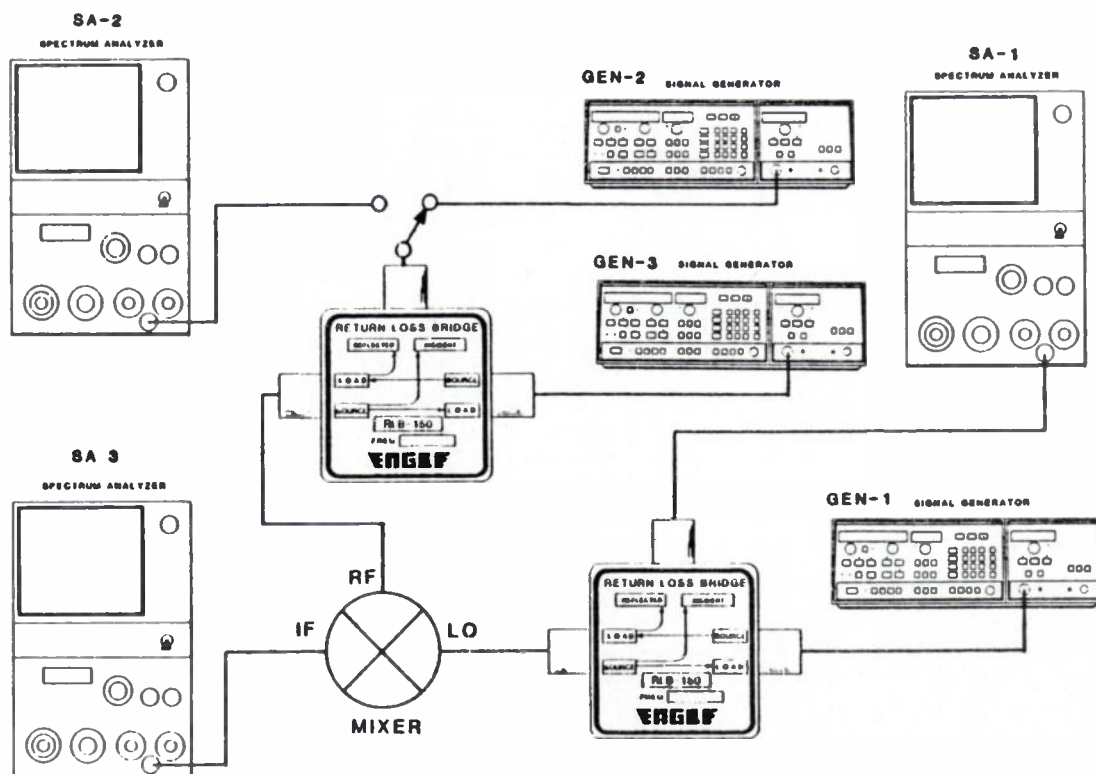


Figure 8

**Last year
more people had cancer
of the colon-rectum
than any other cancer.**

**And you
haven't had
a procto
lately?**

Procto: an everyday way
of saying proctoscopic
examination.

It's a simple diagnostic
test for cancer of the colon
and rectum.

And it helps save more
lives than any other step in the
checkup.

So, if you're over 40, you
should have a procto as part of
your health examination.

Just think of it as a
regular part of living.

American Cancer Society

THIS SPACE CONTRIBUTED BY THE PUBLISHER AS A PUBLIC SERVICE

2 on RF port, the return loss bridge now becomes a power combiner thus supplying a two tone signal to the RF port of the DUT.

3. On spectrum analyzer 3 observe IF output, intermodulation distortion as well as feedthrough from the RF and LO ports of the mixer.

Naturally the bridges used for this system must have an RF MEASUREMENT PORT. A bridge with a five watt rating can easily supply the required drive levels to any diode type mixer.

Impedance Using a Vector Network Analyzer

A vector network analyzer may be connected directly to the MEASUREMENT port of a return loss bridge provided that it has an RF type port. Both magnitude and phase of the reflection are present at this port. A reference signal can be derived by using an isolating power divider at the

SOURCE PORT. The second output is then fed into the network analyzer as a reference signal. It is recommended that a resistive divider be used because of the excellent phase balance inherent in this device.


Summary

The Return Loss Bridge is a useful device for making low power precision VSWR measurements. Most of these devices will be able to yield a -40 dB directivity which is equivalent to a 1.02 VSWR. Performance in excess of this is only possible using slotted line techniques. Return loss bridges can be used for characterizing passive networks, antennas and low power RF amplifiers.

Because of the size, price, high performance and ease of use the return loss bridge is, or should be, a standard piece of test equipment in the RF laboratory or service center.

EMI PROBLEMS?

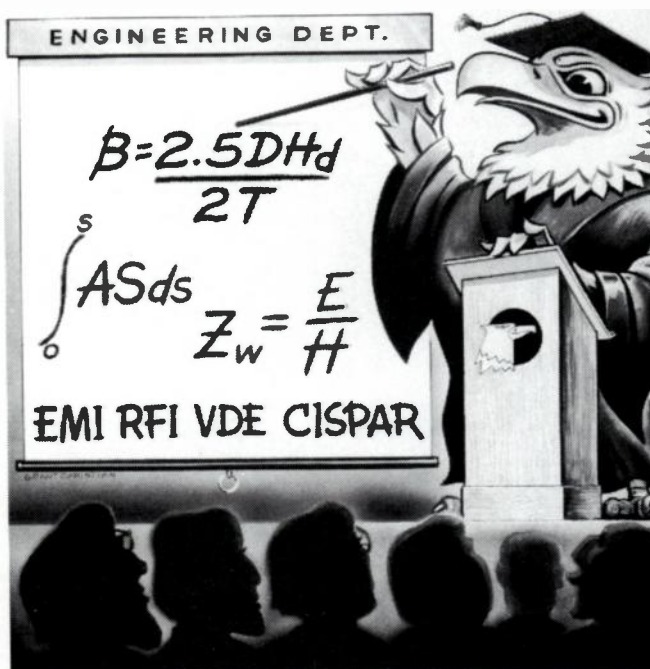**Let Eagle Magnetic solve your
magnetic shielding problems!**



For more information write or call:
P.O. Box 24283 • Indianapolis, Ind. 46224
Phone (317) 297-1030



**CONSULTING,
DESIGN,
and FABRICATION**

★ EM SENSORS


Current Probes
Antennas
FCC & CISPR LISNs

★ NANOSECOND TRANSIENT SUPPRESSORS

Coaxial Lines
Power Lines
Telephone Circuits
I/O Semiconductor Circuits

Fischer Custom Communications, Inc.

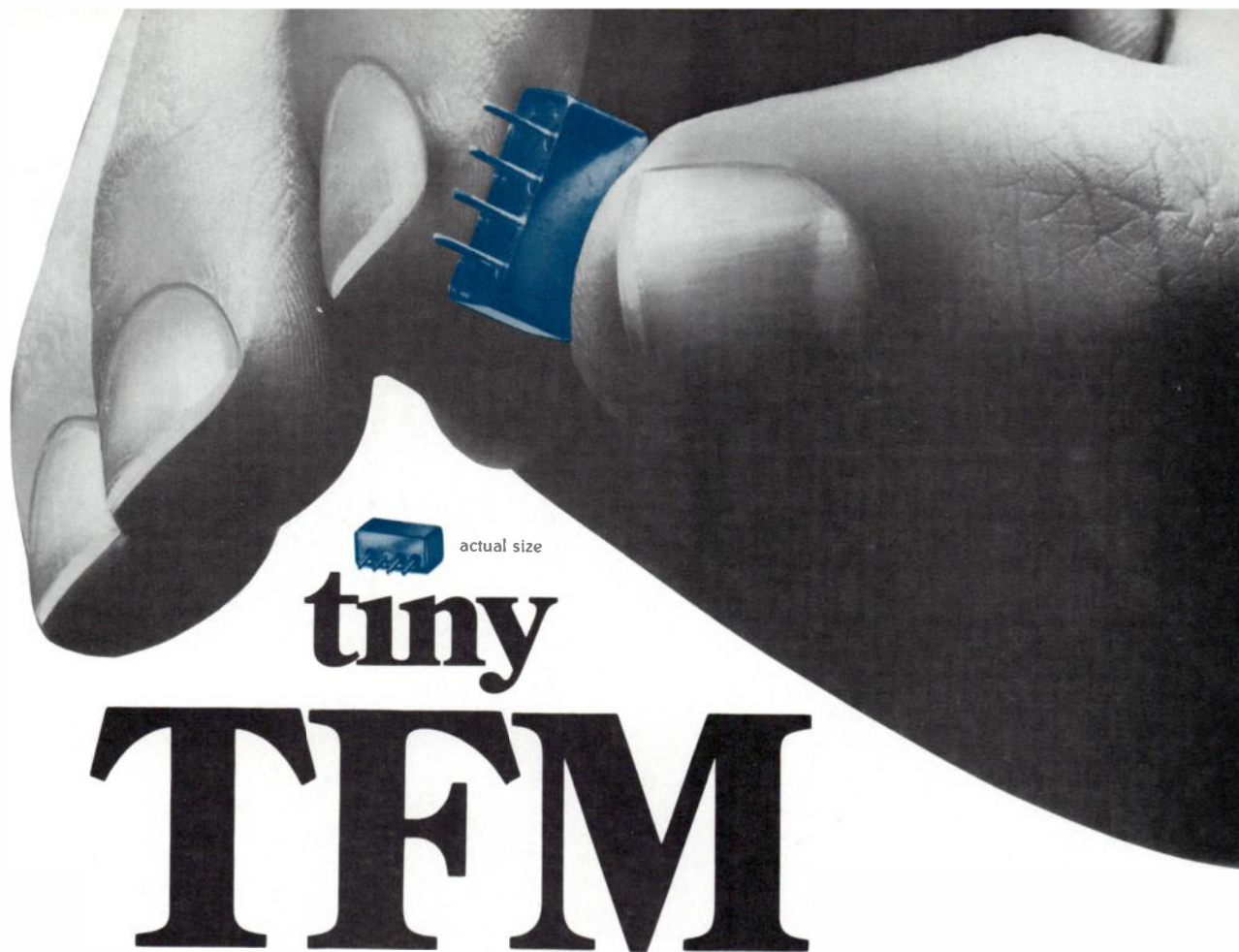P.O. Box 581 Dept. J
Manhattan Beach, Ca. 90266
(213) 545-4617




the world's smallest hermetically-sealed mixers from \$11⁹⁵ 40 KHz to 3 GHz, MIL-M-28837 performance*

Increase your packaging density, and lower your costs... specify Mini-Circuits miniature TFM Series. These tiny units 0.5" x 0.21" x 0.25" are the smallest, off-the-shelf Double Balanced Mixers available today.

Requiring less PC board area than a flat-pack or TO-5 case, the TFM Series offer greater than 45 dB isolation, and only 6 dB conversion loss.

Manufactured to meet the requirements of MIL-M-28837*, the tiny but rugged TFM units have become the preferred unit in new designs for military equipment.

PLUG-IN FLAT MOUNT EDGE MOUNT

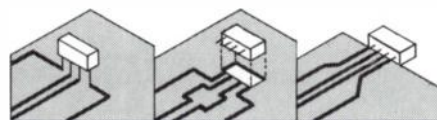

E-Z Mounting for circuit layouts

Use the TFM series to solve your tight space problems. Take advantage of the mounting versatility—plug it upright on a PC board or mount it sideways as a flatpack.

MODEL	FREQUENCY, MHz		CONVERSION LOSS dB, TYPICAL		ISOLATION dB, TYPICAL						PRICE	
	LO/RF	IF	1 Octave from Band Edge	Total Range	Lower Band Edge LO-RF	Mid Range LO-IF	Upper Band Edge LO-RF	Mid Range LO-IF	Upper Band Edge LO-RF	Mid Range LO-IF	\$ EA.	QTY.
TFM-2	1-1000	DC-1000	6.0	7.0	50	45	40	35	30	25	11.95	(1-49)
TFM-3	.04-400	DC-400	5.3	6.0	60	55	50	45	35	35	19.95	(5-49)
TFM-4	5-1250	DC-1250	6.0	7.5	50	45	40	35	30	25	21.95	(5-49)
***TFM-11	1-2000	5-600	7.0	7.5	50	45	35	27	25	25	39.95	(1-24)
***TFM-12	800-1250	50-90	—	6.0	35	30	35	30	35	30	39.95	(1-24)
***TFM-15	10-3000	10-800	6.3	6.5	35	30	35	30	35	30	49.95	(1-9)
***TFM-150	10-2000	DC-1000	6.0	6.5	32	33	35	30	35	30	39.95	(1-9)

***If Port is not DC coupled

==+10 dBm LO, +5 dBm RF at 1dB compression

*Units are not QPL listed

For complete specifications and performance curves refer to the Goldbook, EEM, EBG, or Mini-Circuits catalog



finding new ways...
setting higher standards

Mini-Circuits
A Division of Scientific Components Corporation

World's largest manufacturer of Double Balanced Mixers
P.O. Box 166, Brooklyn, New York 11235 (212) 934-4500
Domestic and International Telex 125460 International Telex 620156

INFO/CARD 22



Reference-Level Control In Spectrum Analyzers: Simplification Through Internal Intelligence

By Morris Engelson
Tektronix, Inc.
Beaverton, Oregon

Both users and designers of spectrum analyzers are constantly seeking ways to simplify instrument operation. While a modern spectrum analyzer includes many control functions, three are essential: frequency tuning, frequency span across the screen, and amplitude level. Unfortunately, each of these functions involves several circuit operations, so that more than one control is usually required for each function.

Inclusion of increasingly more sophisticated circuits, coupled with microprocessor intelligence, has moved the spectrum analyzer closer and closer to a true three-knob-control instrument. For example, microprocessor monitoring of which local oscillator is to be tuned, depending on phaselock condition, has resulted in just a single center-frequency control, with internal switching among oscillators transparent to the user.

Changing the amplitude function into a single control is much more complicated. The solution chosen for the Tektronix 492, 494, and 496 Spectrum Analyzers departs from previous practice, although the control operation is quite similar to that used in the popular 7L5. The arrangement may seem strange to those not used to it, but once understood, it saves the user much extra control manipulation.

The Reference-Level Function

Amplitude-calibrated spectrum analyzers provide a logarithmic vertical display in dB/div, in addition to a linear volts/div scale. Because dB (decibels) is a relative amplitude measure, dB differences must be compared to a


"reference level" to obtain an absolute measure of amplitude. Theoretically, the reference level could be anywhere on screen, although by convention it is the top graticule position. The reference level is defined as the absolute input signal level, in dBm, that produces full screen display.

The reference level is changed whenever instrument transmission gain is increased or decreased (attenuation). An increase in gain permits a smaller input signal to produce a full screen display; thus, the reference level is decreased (e.g., from -30 dBm to -40 dBm). A decrease in gain, or an increase in signal attenuation prior to the gain stages, means that the input signal level has to increase to produce a full screen display; thus, the reference level is increased (e.g., from -30 dBm to -20 dBm).

Clearly, there are two separate instrument areas that affect reference level — gain and signal attenuation. Ideally, it would be desirable to influence both of these areas with one control. Gain change or input signal attenuation can also reduce the signal level and create different instrument behavior for noise level and distortion. The user then needs to choose between these parameters. Furthermore, input impedance characteristics and mixer protection against large (especially pulsed) signals depend on the choice of input attenuation.


A Model

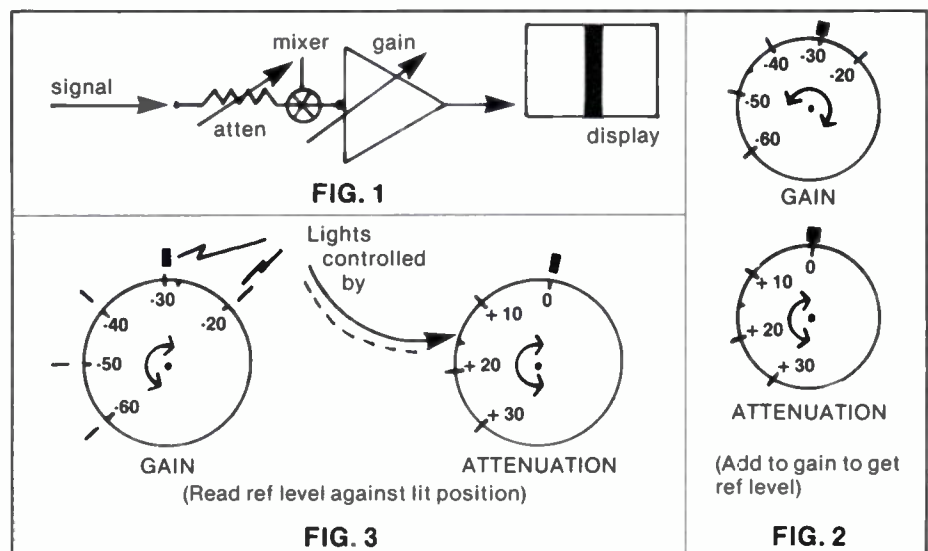Circuitry for controlling the reference level in spectrum analyzers can be represented by the model shown in Figure 1. At some particular level of input attenuation (call it 0 dB), and



Don't you wish someone could show you a cost-effective, flexible, efficient way to transmit data and handle your monitor and control needs? Someone can. Repco.

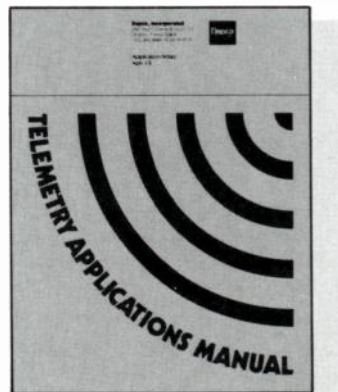Our RF communications link products and design services can meet your telemetry needs. Economically. Efficiently.



Send for our new applications manual. It's unique in the industry. A far-reaching exploration of the possibilities for RF links.

You'll see why businesses and industry from oil to security to nuclear plants depend on Repco for imaginative solutions to tough problems.

We'll help you design an entire system, or provide one small piece of equipment or anything in between.

Someone *can* show you a cost-effective, flexible, efficient way to transmit data and handle your monitor and control needs. Repco.

Repco, Incorporated

2421 North Orange Blossom Trail
Orlando, Florida 32804
(305) 843-8484, TELEX 56-6536



Distributed in Canada by
Repco Radio Canada, Ltd.
1750 Plummer St. • Unit 20
Pickering, Ontario, Canada
L1W3L7 • (416) 839-5911

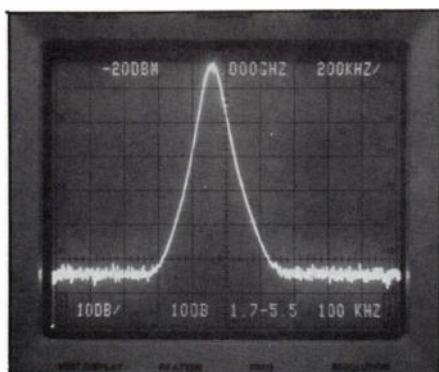


Figure 4

amplifier gain (call it 0 dB), the zero-reference input signal produces a full-screen reference-level display. The zero-reference signal is defined as the input level which, on the whole, provides the best dynamic measurement range as noise, distortion products, and on-screen display capability are balanced against each other. High amplifier gain increases internal noise and thus reduces the measurement range, while very low gain requires high input signal levels into the mixer and results in measurement-limiting distortion products. There is no one absolutely best zero level under all measurement conditions. The range runs from about -20 dBm to -40 dBm, with most spectrum analyzers designed around a -30 dBm level. A zero level of -30 dBm is used in the 490 Series.

How It Was Done Before

In the earlier years of calibrated spectrum analyzers, reference levels were set by two independent controls: one for gain (or IF gain), and another for input (or RF) attenuation. Both controls were calibrated in dB, with zero corresponding to the zero-reference input signal level. Knowing the zero level (e.g., -30 dBm), the user could add or subtract gain or attenuation to compute the reference level. In a more sophisticated variation of this method, the zero-reference gain position was labeled at -30 dBm, as shown in Figure 2. Gain changes would then indicate the reference level directly, so long as attenuation was not changed.

A later improvement provided a moving reference indicator around the gain control, as shown in Figure 3. The indicator was either mechanically or electrically (lights) coupled to the attenuator control. This method eliminated the need for the mental arithmetic of the previous approach.

Another version provided for a mechanical interlock between the two controls so that an indicator window

or other mechanism would move to provide for direct readout of reference level.

Whatever the arrangement, the user had to manipulate two controls to get the desired reference level because gain and attenuation were independent variables, with reference level dependent. In the 490 Series, however, reference level is set directly, while gain and attenuation change as needed to accommodate the desired reference level. This solution results in a single control arrangement.

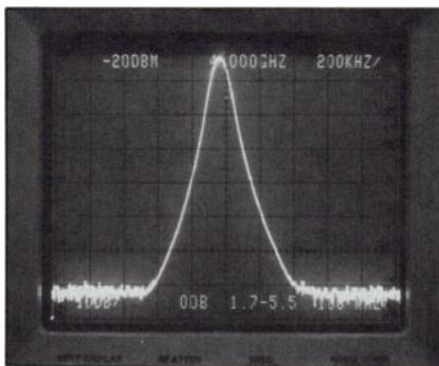


Figure 5

The Tektronix Arrangement

Reference level (R in dBm), gain (G in dB), and attenuation (A in dB) are related through the following simple equation: $R = G + A + C$, where C is a normalization constant. Clearly, the same value of R can be obtained through more than one combination of G and A. Therefore, it is necessary to have independent access to either gain or attenuation even when the reference level can be manipulated directly. In the 490 Series, such access is provided by providing a "minimum attenuation" control that sets the minimum level of attenuation below which the instrument will not go. (This control should not be confused with the attenuation setting control in previous arrangements.) Once the "min-atten" control is set, the reference

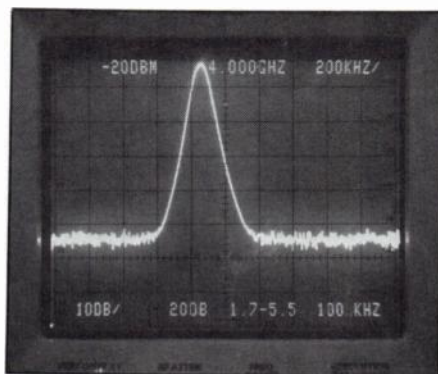


Figure 6

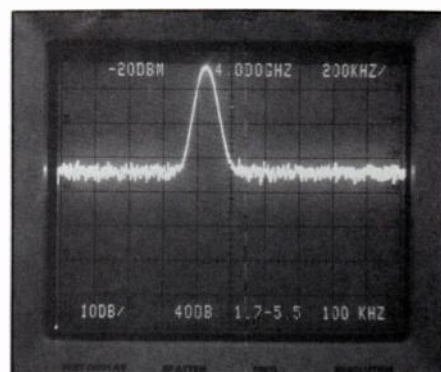


Figure 7

level is actuated by a single control that switches in gain or attenuation as needed to provide the desired reference level. The choice of gain and attenuation is determined by two restrictions: attenuation cannot go below the minimum chosen, and gain will not be reduced below the point that provides a good dynamic range.

Trading Dynamic Range For Noise Reduction


A signal with an amplitude greater than the reference level will produce an off-screen display. The spectrum can be brought on-screen by reducing the apparent signal level in either of two ways, front-end attenuation or gain reduction. Gain reduction reduces the displayed noise level and thus permits more of the screen to be used for signal display. However, the front-end spectrum analyzer circuits are then subjected to greater signal levels and produce more distortion (compared to the attenuation technique of signal-level reduction). In the 490 Series, the choice of operating conditions is provided by a min-distortion/min-noise control. The minimum noise setting provides 10 dB of noise reduction instead of 10 dB front-end attenuation (although attenuation will still not go below the minimum setting).

Although other spectrum analyzers provide 20 dB, 30 dB, or even as much as 40 dB of gain reduction, a limit of 10 dB is used in the 490 Series to assure that the on-screen display reflects real signals rather than spurious responses. This choice (of how much gain reduction to provide) is not related to how the gain attenuation and reference level are controlled, but rather to the fact that the intermodulation dynamic range drops by at least twice the rate of gain reduction. For example, a 40-dB gain reduction cuts an 80-dB dynamic range to zero — not a particularly useful measurement arrangement. Reductions of 10 dB or 20 dB do provide a reasonable intermod-

Plan to be in SAN FRANCISCO MAY 30 - JUNE 1, 1984



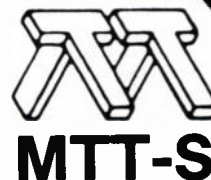To Attend The 1984 IEEE/MTT-S MICROWAVE SYMPOSIUM/EXHIBITION and Take Full Advantage of ...



AN OUTSTANDING TECHNICAL PROGRAM — the traditional forum for announcing significant microwave technology and application developments will feature sessions on:

Field Theory • Acoustic and Magnetic Devices • Biomedical Aspects of Microwaves • FET Amplifiers • Filter Systems • FET Oscillator Stabilization • Communications Filters • Semiconductor Control and Frequency Conversion • mm-wave Applications • MIC Techniques • FET Modeling • mm-wave Techniques • Planar Transmission Line Structures • IMPATT and Bipolar Oscillators • Dielectric Waveguides • Microwave and mm-wave Measurements • Optical and Submillimeter-wave Technology • mm-wave Mixers • Six-port Measurement Techniques

SPECIAL WORKSHOPS AND PANEL SESSIONS — provide unique opportunities for dialogue with recognized specialists from all over the world on these subjects:

mm-wave Measurements • MMICs • Japan/USA Competition in Technology • Testing and Trimming of Miniature Batch Processed MICs • 40 GHz+ Coaxial Connectors • Clinical Hyperthermia
• Suspended Stripline Filters • Field-Theoretical Methods for Microwave Problems • Industrial Applications of Microwaves

THE LARGEST MICROWAVE EXHIBITION OF THE YEAR — more than 200 microwave component, device, instrumentation, material and subsystem suppliers will display their latest products and be prepared to discuss your needs at production or engineering levels.

A FULL SOCIAL PROGRAM — spouses tours, an exhibitor reception and the MTT-S award banquet complement the program and exhibition activities.

Complete the coupon below and return it to Microwave Journal to receive the Advance Program, advance registration form and hotel reservation forms.

MICROWAVE JOURNAL • 610 Washington Street • Dedham, Massachusetts 02026

Send me additional information on attending MTT-S '84

Name _____ Title _____

Organization _____

Address _____

City, State, Zip Code _____

Country _____ Phone _____

MTT-S Member? ☐ Yes ☐ No

The 490 Series Arrangement Compared To Others

Advantages

- Permits presetting the minimum attenuation desired. Set it, then forget it.
- True single knob reference level control. No need to manipulate two controls to get the desired ref. level.
- Choice of minimum distortion or minimum gain algorithms. The user knows what he is getting. Comes up the same way (minimum distortion) every time the instrument is turned on.
- Does not provide too much gain reduction to avoid mistaking spurious responses for real signals. Additional

gain reduction can be simulated by going off screen.

Disadvantages

- New scheme, people are not used to it.
- Noise level will be high and stay high if the min-atten is set at a high level (e.g. 40 dB), and the user does not realize it.
- Not obvious how to get a desired gain and attenuation setting as opposed to a reference level.
- Only 10 dB of gain reduction means that for some rare applications one needs to drive the signal off screen.

ulation measurement range. Each has its merits and disadvantages, and the choice is pretty subjective. In any event, it is always possible to drive the signal off screen, thus simulating a larger gain reduction.

Advantages and disadvantages of the arrangement used in the 490 series are listed in the table above.

Photographic Examples

The vertical calibration arrangement provided by the 490 series permits

setting all combinations of gain, attenuation, and reference level. Figure 4 shows the normal setting intended for best dynamic range, which occurs at -30 dBm for 0 dB front-end attenuation. The microprocessor sets 10 dB of attenuation to reach -20 dBm reference, although the minimum attenuation was preset at 0 dB.

Figure 5 shows what happens when the minimum noise position is chosen. The 10 dB of rf attenuation is removed, and gain (also on-screen noise) drops by 10 dB. The reference level is un-

changed, and the full-screen signal display remains full-screen.

Figure 6 shows what happens when the minimum attenuation is preset to 20 dB. Gain and noise increase, attenuation is up to 20 dB, and the reference level and signal display amplitude are unchanged.

Figure 7 shows a similar situation at 40 dB minimum attenuation. As stated earlier, all possible combinations of gain (normal, -10 dB, and increase by over 100 dB in 1-dB steps), attenuation (zero to 60 dB in 10-dB steps), and reference level can be set with the control system in the 492, 494, and 496.

Although the 490 Series provide a maximum 10 dB of gain (noise) reduction, the equivalent of greater reduction can be achieved by driving the signal off-screen. This approach has the advantage that most on-screen displays are real; thus, there is no possibility of erroneously identifying a spurious response as a real signal. The disadvantage is that on-screen displays cannot be achieved on those occasions when noise reduction greater than 10 dB is desired.

Figure 8 shows a normal two-signal display. Intermodulation products are below noise level.

Figure 9 shows the same two 0-dBm

For a power resistor that stays non-X up to vhf, there's only one choice.

The Carborundum® Type SP. Only Carborundum has a ceramic power resistor that behaves like a pure resistance rather than an inductor and/or capacitor. It operates from low audio frequencies up into the vhf range. Each unit is a solid body of resistive material. No windings, no film. Ideal for frequency-sensitive rf applications like feedback loops.

And it gives you extremely high power density, with great surge-handling capability because it's solid.


Our Type 234SP, for example, is about the size of a 2-watt carbon comp, but dissipates a full 10 watts in 40°C ambient air. Moreover, it can consistently absorb surges of over 10X rated power for several seconds and come back for more with very little ΔR . Forced-air-cooled, water-cooled or

immersed in oil, it will handle even greater power overloads.

Other Carborundum Type SP resistors—including high-power, water-cooled configurations—are rated from 2.5 to 1000 watts. For further details, call or write E. B. (Woody) Hausler at (716) 278-2143.

The Carborundum Company
Electric Products Division
P.O. Box 339
Niagara Falls, New York 14302

CARBORUNDUM
A Sohio Company

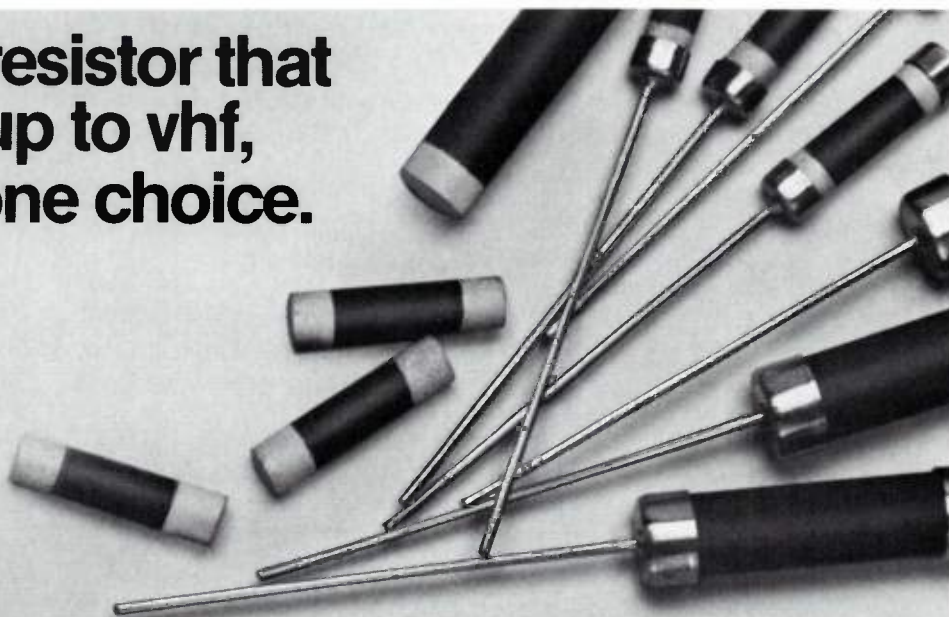

When looking for a Synthesizer for frequency agile systems (such as FSK, secure communications or radar), our new Model 5135A is the fastest now on the market. Latest in our series of 160 MHz units, it completes frequency changes as large as 10 MHz in less than 1 μ sec (5 μ sec for larger ones). For low-noise, phase-coherent radar systems, switching is also **phase-continuous** with frequency

changes of 100 kHz or less.

Its .001 Hz resolution over the full 160 MHz range makes it ideal as a local oscillator, where small frequency changes are reflected as large ones in a transmitted signal. Adjacent channel interference for high resolution systems is kept to a minimum by our very low SSB phase noise of -95 dBc/Hz, as close as 10 Hz from the carrier.


To find out how this unique synthesizer can fit your application, contact us or your local Wavetek representative.

Wavetek Rockland Scientific, Inc.
10 Volvo Drive
Rockleigh, NJ 07647
(201) 767-7900

WAVETEK®

**1 μ sec switching
makes it hard
to eavesdrop
or interrupt...**

**...and our NEW Synthesizer
has 1 μ sec switching,
the fastest you can buy**

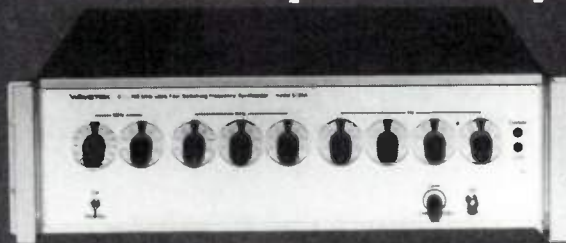

Model 5135A

Literature Info/Card 85
Demonstration Info/Card 34

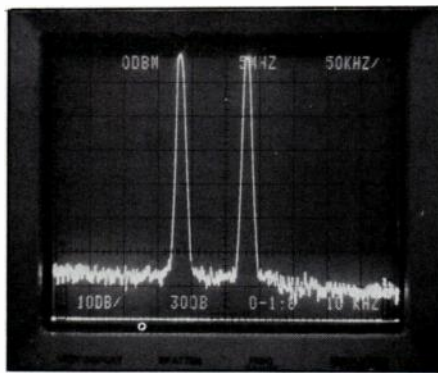


Figure 8

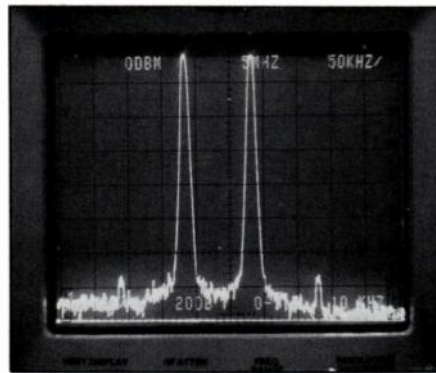


Figure 9

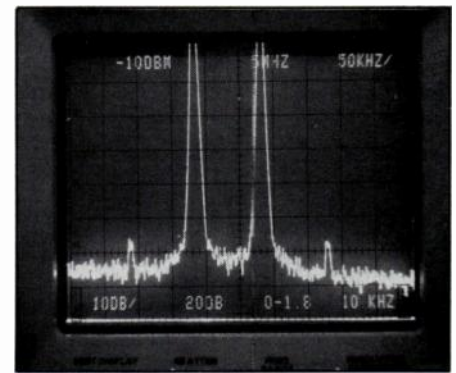


Figure 10

signals in the minimum noise mode. The noise level has dropped by 10 dB, and the input circuits are subjected to 10 dB greater signal level as the front-end attenuator is down from 30 dB to 20 dB. Third-order intermodulation products can now be observed on the screen. The information provided by Figure 9 can also be obtained by changing the reference level by 10 dB and driving the signal 10 dB off-screen, as shown in Figure 10.

Going another 10 dB off-screen brings the third-order products up to only 50 dB below the input signals, as shown in Figure 11, a composite of two photos. Finally, Figure 12 shows the display on a competitive instrument, where gain reduction greater than 10 dB is possible. Although the signal spectrum is all on-screen, the intermodulation products are not real. Figure 8 shows that these products are significantly more than 50 dB down.

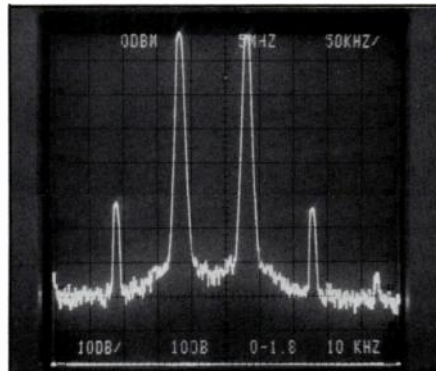


Figure 11

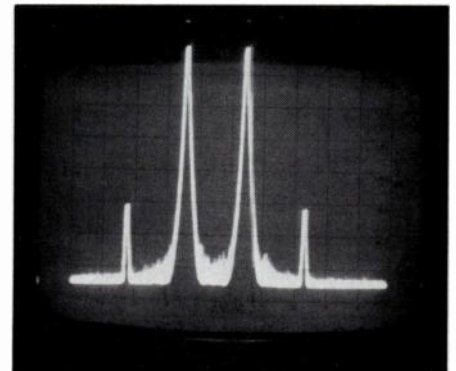


Figure 12

Conclusion

Perhaps one day, artificial intelligence will reach a level where human judgment will be replaced by machines. We are certainly not there now. Therefore, we continue to have some degree of ambiguity in applications involving complicated interactions or relationships. The vertical display level of the

spectrum analyzer is no exception.

Current efforts are in the direction of assuring that the more common measurements can be done more or less automatically; that the control arrangement is as simple to use and learn as possible and that the human operator knows when to, and is able to, override the computer.



You Demand Precision . . . We Build It!

High precision ovenized crystal oscillators for use in counters, synthesizers and communications systems.

- Up to 1×10^{-10} /24 hr. aging
- Single side band phase noise (BW-1Hz) at 1 KHz-160dB
- Frequencies from 1 to 120 MHz
- MIL-SPEC, JANTX Radiation-hardened capability
- $\pm 5 \times 10^{-10}$ from 0 to 50°C
- MIL-SPEC temperature ranges
- Fast warm-up options available
- Various mechanical configurations

Call or write with your oscillator requirements!




P.O. Box 14766 • Austin, Texas 78761 • (512) 251-2313 • TWX 910-874-1356

If you checked any or all of the items below, then you must order from Wavetek. Because Wavetek specializes in small, lightweight, high-performance programmable attenuators for OEM systems.

They're available in 50- or 75-ohm versions covering a frequency range up to DC to 2000 MHz. They have a switching life of 10 million operations and a switching speed of less than 8 milliseconds with a typical 12 VDC address.

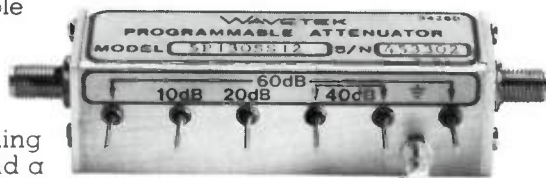In addition to three standard configurations, Wavetek programmable attenuators can be



World's smallest
DC-2 GHz programmable attenuator.

custom-designed for your specific applications. And we can produce them in volume quantities at surprisingly low prices.

For complete information, contact: Wavetek Indiana, Inc., 5808 Churchman, P.O. Box 190, Beech Grove, IN 46107. Or call TOLL-FREE 1-800-428-4424. In Indiana, call (317) 787-3332. TWX 810-341-3226.

WAVETEK

Programmable Attenuator Checklist:

- ☒ Must be small and lightweight.
- ☒ Must deliver high performance at low cost.
- ☒ Must be available in volume and in custom configurations.
- ☒ Must be DC-2 GHz.

“Near Field” Communication

The “Near Field” low frequency communication applications have been neglected for quite some time. However, suitable applications still exist and should be more closely examined.

By Andrzej B. Przedpelski
R & D Laboratory
A.R.F. Products, Inc.
Boulder, CO 80301

Despite the fact that “microwaves” became quite a buzzword in the last few decades, there are still some applications for the lowly low frequencies. In the thirties, high power low frequency broadcasting stations were quite de rigueur practically everywhere but in the United States. I remember, as a child, putting together my first crystal set to listen to Warsaw I at about 200 kHz. Thanks to the high power output and a good ground wave, reliable reception could be had with the simplest equipment. In those days all you needed was a crystal (not a JANTX diode, but a hunk of galena with a “sensitive spot”), some wire, a cold pipe for ground and the power line for an antenna (if you were very careful - I almost burned the house down when my “antenna” shorted to my “ground”) and you were in business. During World War II, when amateur transmissions were restricted, low frequencies enjoyed a short revival in the United States. Some hams, not willing to give up their hobby, switched to carrier current as means of communicating. This meant operation below 100 kHz, using the power lines as transmission lines. Theoretically, the radiation was supposed to be negligible, but it was possible to “jump” from one power line to another. This was handy in places like Boston, where some of the power was AC and some DC therefore line jumping was necessary to obtain reasonable distances.

Long range (high power) applications for low frequencies always existed, such as: communicating with submarines at sea, navigation (Omega, Loran-C, Decca), and timing (WWVB and US Navy standard frequency and time stations such as NAA, NSS NLK).

For a while things were quiet on the low frequency front, until garage door openers first became popular in the late forties. To provide “license-less” operation (it is doubtful if the average motorist could pass any kind of FCC exam), a very low power operation was required by the FCC. This is where “near field” operation comes in [Reference 1]. To meet the low maximum allowable field strength permitted, the fact that the field varies as the inverse cube of the antenna separation for distances considerably less than a wavelength, was utilized. At distances over one wavelength,

the usual inverse law applies. Thus, using very low frequencies (long wavelengths), a usable signal level could be obtained while still satisfying the FCC requirements.

It may be desirable, at this point, to define what is meant by “near field.” An RF current in a transmitter loop antenna produces an oscillatory magnetic field. This field, in turn, induces a proportional current in a receiver loop antenna placed in it. Thus, the transmitter loop — receiver loop system can be thought of as a very loosely coupled (“leaky”) transformer (see Figure 1).

The formula for mutual inductance of two parallel coils, as shown in Figure 1, is [Reference 2]:

$$M = \frac{\mu \cdot \pi}{16} \sqrt{r_R r_T} \left[\frac{4 r_R r_T}{(r_R + r_T)^2 + d^2} \right] \quad (1)$$

which, for $r_R + r_T \ll d$ (the usual case), can be simplified to:

$$M = 0.2\pi^2 \frac{r_T^2 r_R^2}{d^3} \quad (2)$$

Using the formula for induced voltage:

$$e = -j\omega M i \quad (3)$$

and taking into account the fact that multiturn coils are used, the overall system formula for induced voltage in the receiver loop antenna becomes:

$$e_R = 0.4\pi^3 \frac{r_T^2 r_R^2 n_T n_R}{d^3} f i_T \quad (4)$$

Basically, the same results can be obtained using Henney's formula for radial near field [Reference 3]:

$$e_n = \frac{18.85 n_T r_T^2}{d^3} i_T \times 10^7 \quad (5)$$


Weinschel's 3100 Variable Attenuator Chosen by IFR for their FM/AM 1500



IFR, Inc. Model FM/AM 1500 Communications Services Monitor uses Weinschel Model 3100-127 to achieve a high degree of accuracy and dependability

IFR, the leading designer and manufacturer of precision test equipment for the Avionics Electronics and Communications industry, chose Weinschel's 3100-127 variable attenuator for use in their FM/AM 1500 Communications Services Monitor. A member of the National Conference of Standards Laboratories, IFR demands a high quality and dependable OEM product.

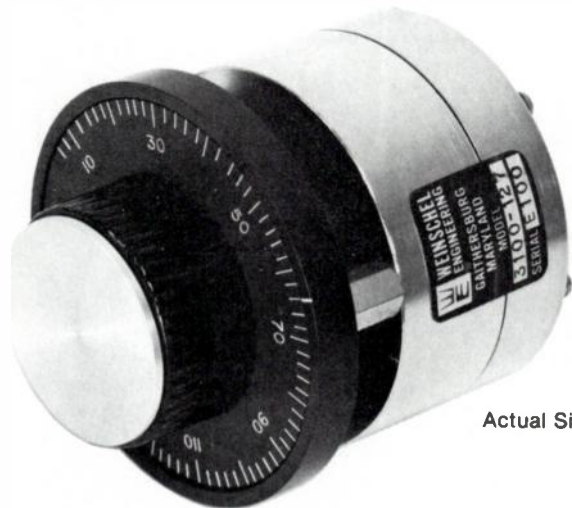The 3100-127 is the smallest available precision variable attenuator with an incremental range of 127 dB. Designers appreciate the small front panel dimensions and flat frequency response which enhance broadband OEM instrumentation designs.



Actual Size

Here's why. . .

Continuously Variable

127 dB incremental range between minimum insertion loss (6 dB) and 133 dB

Broadband

DC to 2 GHz

Low Frequency Sensitivity

$\pm 0.015 \frac{\text{dB}}{\text{dB} \times \text{GHz}}$ to 133 dB absolute

Calibration Frequency Accuracy (at 1 GHz)

0.5 dB or 1% (whichever is greater) to 120 dB,
2% to 133 dB (including resetability)

Environmentalized

Against humidity, salt, shock, and vibration; 0 to 85°C operating temperature range


Long Life

Rated for and tested successfully to 50,000 operations

CALL

800-638-2048


to receive literature next week

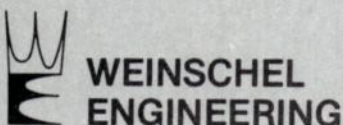

One Weinschel Lane
Gaithersburg, MD 20877
(301) 948-3434
Telex: ITT440702
or WU89-8352

C-49

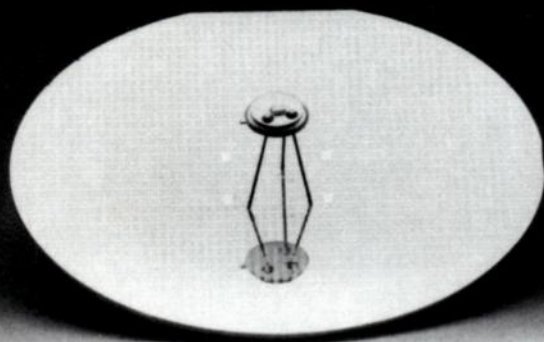A quartz resonator for UHF oscillators has surfaced...



Introducing the surface acoustic wave (SAW) resonator. This fundamental-mode UHF resonator is manufactured with semiconductor processing techniques using quartz as a substrate. The high-Q resonance of the SAW resonator arises from phased reflections across the surface of the device — similar mathematically to the resonance of a laser. The quartz SAW resonator makes an excellent frequency control device for UHF oscillators from 300 to over 1000 MHz. SAW resonators are used in RF applications from precision instrumentation to high-volume consumer electronics.

For more information on the characteristics and applications of the quartz SAW resonator please contact:



RFMonolithics, Inc.
4441 Sigma Road
Dallas, Texas 75234
(214) 233-2903
TWX: 910-860-5474

and Terman's for induced receiver loop voltage [Reference 4]:

$$e_R = 2\pi e N \frac{A}{\lambda} \quad \text{where } e \text{ can be } e_n \text{ or } e_r. \quad (6)$$

The induced receiver antenna voltage thus becomes:

$$e_R = 3.9585\pi \frac{r_T^2 r_R^2 n_T n_R}{d^3} f i_T \quad (7)$$

For comparison, the "far" field transfer function was derived:

$$e_R = 8.89\pi^5 \frac{r_T^2 r_R^2 n_T n_R}{d} f^3 i_T \times 10^{-18} \quad (8)$$

using [Reference 5]:

$$e_f = \frac{120\pi^3 n_T r_T^2}{d\lambda^2} i_T \quad (9)$$

and Equation (6).

The inverse and inverse cube relationships are clearly visible in Equations (8) and (7). Figure 2 shows them for normalized conditions ($r_R = r_T = n_R = n_T = i_T = 1$) for an RF frequency of 100 kHz. It can be seen that at a distance of just under $\frac{1}{4}$ wavelength the performance of the two approaches is equal. At shorter distances, the "near field" is clearly superior. At longer distances, the more common "far field" performance is better.

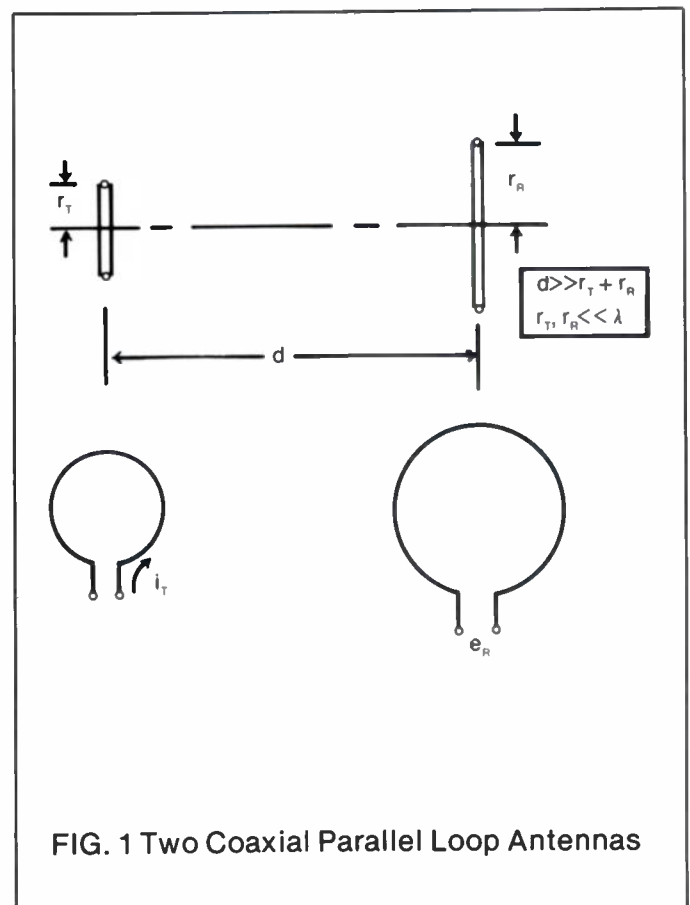


FIG. 1 Two Coaxial Parallel Loop Antennas

3rd ANNUAL Test & Measurement World EXPO

APRIL
3-5,
1984

BROOKS
HALL,
SAN
FRANCISCO

INTERNATIONAL TECHNICAL CONFERENCE & TECHNOLOGY EXHIBIT

Areas of test, measurement & inspection technology covered by technical program & exhibit:

Robotics & Machine Vision
Test Data Analysis
CAM/CAD/CAT
Electro-Optics Test
Image Analysis for Test & Inspection
Factory of the Future-Test, Measurement & Inspection
Subassembly/System ATE
Test Software
VLSI Test
Component Test
Test Instruments
Communication Test
Microwave Test
Economics of Testing
Process Monitoring
Test/Analysis/Services
Optical Inspection
Failure Analysis
Microelectronics Measurement
Fiber Optics Test
EMI/RFI Test & Evaluation
Precision Instruments
Production/QA/ATE
Test Hardware

Test & Measurement World Expo,
215 Brighton Avenue
Boston, MA 02134 617/254-1445

For more
information,
fill out
and send
coupon below.

YES, I'M INTERESTED.

- ☐ Please send me detailed information on the 1984 Test & Measurement World Expo technical program as soon as it is available.
☐ I want to show my products as an exhibitor at Test & Measurement World Expo.
☐ Please have a Representative phone me.

NAME _____

TITLE _____

COMPANY _____

MS/DEPT. _____

ADDRESS _____


CITY/STATE/ZIP _____

() _____

TELEPHONE _____

Return coupon to: Test & Measurement World Expo,
215 Brighton Avenue, Boston, MA 02134
INFO/CARD 39

DALE MEASURES UP to your TCXO NEEDS.

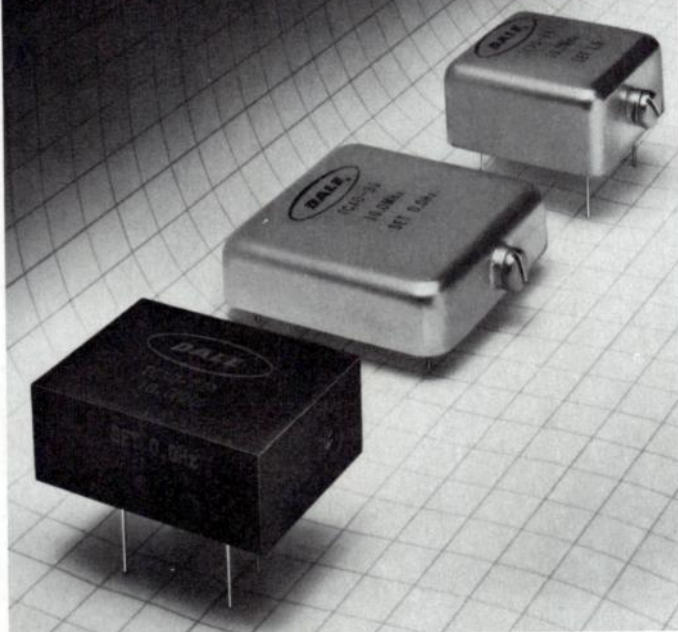

Check our expanded line of temperature compensated crystal oscillators. It includes both military and commercial models in frequently specified styles — with stock frequencies available fast! Here's a quick look at our lineup, including the new hermetically sealed TCXO-30 and TCXO-32 now in production.

Model No.	TCXO-22	TCXO-24	TCXO-26	TCXO-30	TCXO-32
Freq. Range	3 MHz to 15 MHz				
Stock Freq.	4, 5, 10 MHz				
Stability vs Temp. (PPM°C)	±1, ±5 (0 to +55°C)		±1 (0 to +70°C)	±3 (-40° to +85°C)	±1 (-40° to +85°C)
Case Style	Epoxy	Metal with Hermetic Seal			

Contact Dale today for complete price and delivery information, plus assistance with custom models.
Phone 602-967-7874



Dale Electronics, Inc., 1155 West 23rd Street, Tempe, AZ 85282

Table 1
Definitions

f = frequency, hertz
 d = loop antenna separation, meters
 n_T = number of turns in transmitter loop antenna
 n_R = number of turns in receiver loop antenna
 r_T = radius of transmitter and antenna loop, meters
 r_R = radius of receiver antenna loop, meters
 i_T = transmitter RF loop current, amperes
 e_n = near-field strength, microvolts per meter
 e_f = far-field strength, microvolts per meter
 e_R = voltage induced in receiver loop antenna, microvolts
 M = mutual inductance, microhenries
 μ_o = permeability of free space, $4\pi \times 10^{-7}$ henries per meter
 λ = wavelength, meters
 A = loop antenna area, square meters

Table 2
FCC Regulations - Part 15

Maximum allowable field strength for nonlicensed operation:

Frequency - kHz	Distance - meters	Field Strength
10-490	300	2400/frequency
510-1600	30	24,000/frequency
Frequency - MHz		
70-130	30	50
130-174	30	50-150 (linear interpolation)
174	30	150
260-470	30	150-500 (linear interpolation)
470 and above	30	500

There are many applications where the "near field" approach provides important advantages. They are basically low power short range systems which can be divided into two main categories:

-systems which cannot exceed a certain field strength at a specified distance, and

-systems where partial security of transmission is desired.

A typical example of the first is the FCC low power requirement mentioned before in connection with the garage openers. To operate without a license, the low power FCC requirements have to be satisfied, as shown in Table 2. Figure 3 shows a comparison of operation at two frequencies: 100 kHz and 200 MHz. The maximum FCC allowable signal strengths are indicated. At distances of over about 400 meters the 200 MHz system will provide higher field strength, but at very short distances over 40 dB higher field strengths are provided using the low frequency approach. A free bonus is the reduced interference with other receivers located nearby, since the inverse cube relation applies to a distance of about 670 meters.

In addition to the above advantages, the lower frequency usually provides better propagation characteristics. It penetrates solid objects better and does not exhibit the usual nulls encountered in VHF operation.

The other application is in partially secure (or non-interfering) short distance communication systems. Let's assume



CRYSTAL OSCILLATORS

Clock Oscillators



TTL: 1 Hz - 100 MHz
CMOS: 1 Hz - 15 MHz
ECL: 5 MHz - 500 MHz
SINE: 50 Hz - 1000 MHz
Standard: 0/+ 70°C: $\pm 0.025\%$
Option 1: -55/+ 85°C: $\pm 0.05\%$
Option 2: -55/+ 125°C: $\pm 0.05\%$
Option 3: 0/+ 50°C: $\pm 0.003\%$

Oven Controlled



Aging: 1×10^{-8} /day to
 1×10^{-10} /day
Frequency: 1, 5, 10 or 100 MHz std.
<1 to 400 MHz available
Temperature: $2 \times 10^{-9}/^{\circ}\text{C}$ to
 $2 \times 10^{-11}/^{\circ}\text{C}$
Noise: as low as -160dBc/Hz
at 10 KHz

TCXOs



0/+ 50°C: $\pm 1 \times 10^{-6}$ to $\pm 1 \times 10^{-7}$
-20/+ 70°C: $\pm 5 \times 10^{-6}$ to $\pm 5 \times 10^{-7}$
-55/+ 85°C: $\pm 5 \times 10^{-6}$ to $\pm 1 \times 10^{-6}$
Aging: 1×10^{-8} /day, 1×10^{-6} /yr
Input: 5-30 VDC, 4-30 ma
Output: Sine: 1 MHz - 400 MHz
TTL: 50 Hz - 100 MHz
CMOS: 50 Hz - 10 MHz
ECL: 1 MHz - 280 MHz

Name _____
Mail Stop _____ Title _____
Firm _____
Address _____
City _____ State _____ Zip _____
Phone _____ Ext. _____

PLEASE QUOTE:

☐ Clock ☐ TCXO ☐ VCXO ☐ Oven Type
Freq _____ Output _____
Temp _____ Stab _____
Other (e.g. aging) _____
Quantity _____
☐ Immediate Need ☐ Send your Catalog
☐ Have Sales Engineer contact me

You can reach us at 203/853-4433



BUSINESS REPLY CARD

FIRST CLASS PERMIT No. 431 Norwalk, CT

POSTAGE WILL BE PAID BY ADDRESSEE

VECTRON LABORATORIES, INC.

The Crystal Oscillator Company

166 Glover Avenue

Norwalk, CT 06856-9979

NO POSTAGE
NECESSARY
IF MAILED
IN THE
UNITED STATES



REF LEVEL

INPUT ATTEN

LOG SCALE

10 dBm

10 dB ATTEN

10 dB

Many of today's complex instrumentation systems depend on programmable frequency synthesizers. Varian Instrument Division, Palo Alto, is using PTS 160 and PTS 200 low noise sources in their state-of-the-art-products.

The reliability record established by these synthesizers over the years has been outstanding. If you need VHF-UHF Synthesizers for precision frequency control in your system or lab, follow the leaders, specify PTS with confidence.



FREQUENCY SYNTHESIZER MODELS
40 MHz, 160 MHz, 200 MHz, 500 MHz



PTS
PROGRAMMED TEST SOURCES, INC.

Littleton, MA, 617-486-3008



PRECISION CRYSTAL OSCILLATORS SERIES 8000

STANDARD FREQUENCY	5.0 MHz
AGING RATE	MODEL ER8001 1×10^{-9} /day MODEL ER8003 1×10^{-10} /day MODEL ER8005 5×10^{-11} /day
PHASE NOISE	SSB 1 Hz BW at 10 Hz offset MODEL ER8001 . . . 124 db MODEL ER8003 . . . 135 db
INPUT VOLTAGE	12 VDC \pm 10% STANDARD
OUTPUT	SINE-WAVE 1VRMS INTO 50 ohm LOAD
SIZE	MODEL ER8001 and MODEL ER8003 2" \times 2" \times 4" H MODEL ER8005 2.25" \times 2.25" \times 4.25" H
OPTIONS	MANY OPTIONS ARE AVAILABLE TO INTERFACE WITH YOUR REQUIREMENTS

ELECTRONIC RESEARCH COMPANY SERIES 8000 PRECISION OVENIZED CRYSTAL OSCILLATORS ARE THE ULTIMATE CHOICE WHERE PROVEN RELIABILITY AND FREQUENCY STABILITY IS REQUIRED. THESE OSCILLATORS ARE IDEAL FOR APPLICATIONS WHERE A PRECISION TIME BASE IS TO BE MULTIPLIED OR SYNTHESIZED REQUIRING A LOW PHASE NOISE SOURCE. ALL ELECTRONIC RESEARCH COMPANY'S OSCILLATORS UTILIZE QUARTZ CRYSTALS MANUFACTURED BY ERC FOR MAXIMUM CONTROL ON ALL PARAMETERS TO INSURE PERFORMANCE SPECIFICATIONS. IF YOUR APPLICATION REQUIRES SUPERIOR OSCILLATOR PERFORMANCE CALL US OR WRITE FOR OUR COMPLIMENTARY CATALOGUE.

For information and prices, send your specifications to:



FREQUENCY CONTROL PRODUCTS
electronic research company

7618 Wedd, Overland Park, Kansas 66204
TWX: (910) 749-6477
Telephone: (913) 631-6700

that a system is needed having a minimum signal-to-noise ratio of 40 dB at transmitter/receiver separation of 100 meters. The intelligence bandwidth is 10 kHz. Two systems will be compared: one at 400 MHz and one at 50 kHz. Assuming a receiver noise level equivalent to a field strength of one microvolt per meter [Reference 6], a field strength of 100 microvolts per meter at 100 meters is needed, as shown in Figure 4. At a distance of 10,000 meters the system will have a 0 dB S/N.

On the other hand, the 50 kHz system, while requiring considerably higher field strength to provide the required S/N, will be lost in the atmospheric noise [Reference 6] (S/N of 0 dB) at a distance of only about 460 meters, as shown in Figure 5. Thus, security is considerably enhanced compared to the VHF system.

The necessity of using loop antennas is sometimes considered a disadvantage of the low frequency, near field systems. While modern loop design data is somewhat scarce, it is possible to design efficient structures [Reference 7] with minimal effort.

The above analysis is not meant to be all-inclusive, but it shows that the long neglected low frequencies still have some modern applications. Each individual short-range system requirements have to be considered before a final decision can be made, but in many cases the low frequency approach may have considerable advantages. In addition, after working at VHF and UHF it is quite a revelation to find out that capacitors really behave like the book says and an inductor is $+j$ and not $-j$.

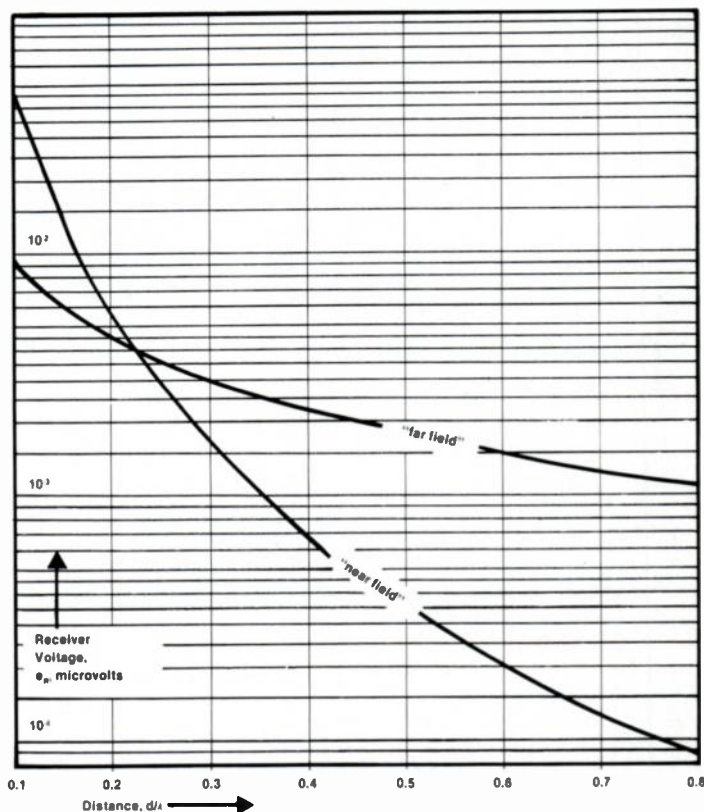


FIG. 2 Induced Receiver Voltage, e_r (Normalized)

The high performance requirements of your

RECEIVING SYSTEM

can be realized with Reaction Instruments' standard or customized Receiving Equipment.


**Your Choice
For High Quality
Communications
Equipment**

DISTRIBUTION AMPLIFIERS

The Model 7298 Video Line Driver Amplifier is a general purpose, dc to 8 MHz amplifier, with up to 15 plug-in 6 output distribution amplifiers, each with output rated at +20 dBm.

The Model 7292A FDM Distribution Amplifier System, with up to 15 plug-in 6 output amplifier channels, features low noise ($\text{BINR} > 70 \text{ dB}$) and intermodulation ($\text{npr} > 65 \text{ dB}$) for distributing CCITT FDM demodulator outputs.

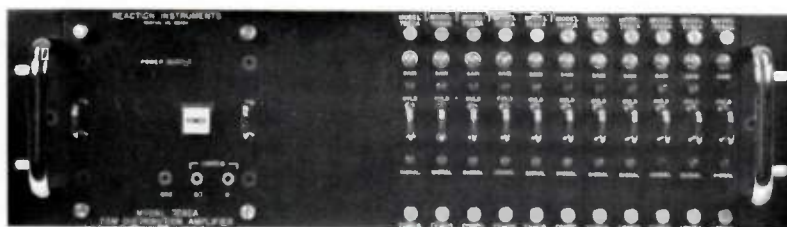The Model 7291 Distribution Amplifier is a general purpose, wideband (dc to 32 MHz), low distortion video distribution amplifier with dual 6 output channels.



Please Write or Call



**REACTION
INSTRUMENTS**

1916 Isaac Newton Square West
Reston, Virginia 22090
Phone: (703) 471-6060


icouplers • Receivers • Signal Distribution • Frequency Converters • Processors

INFO/CARD 44

NEW

Ultra Q Crystals for Your Most Demanding Applications

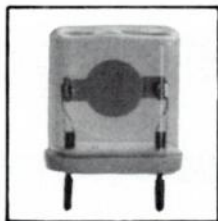Better resolution, improved stability—greater performance all the way around—are yours. This new generation of **10 MHz, 5th-overtone, AT- and SC-cut** quartz resonators processed in Colorado Crystal's new precision clean room, can make the difference in your design. Use Ultra-Q crystals wherever you need more reliable signal information or improved accuracy in frequency or timing standards.



**Better Crystals
Mean
Better Products**

For typical specifications and information
on custom ultra-precision crystals,
call or write:

**COLORADO
CRYSTAL
CORP.**

(303) 667-9248

2303 W. 8th St. • Loveland, Colorado 80537

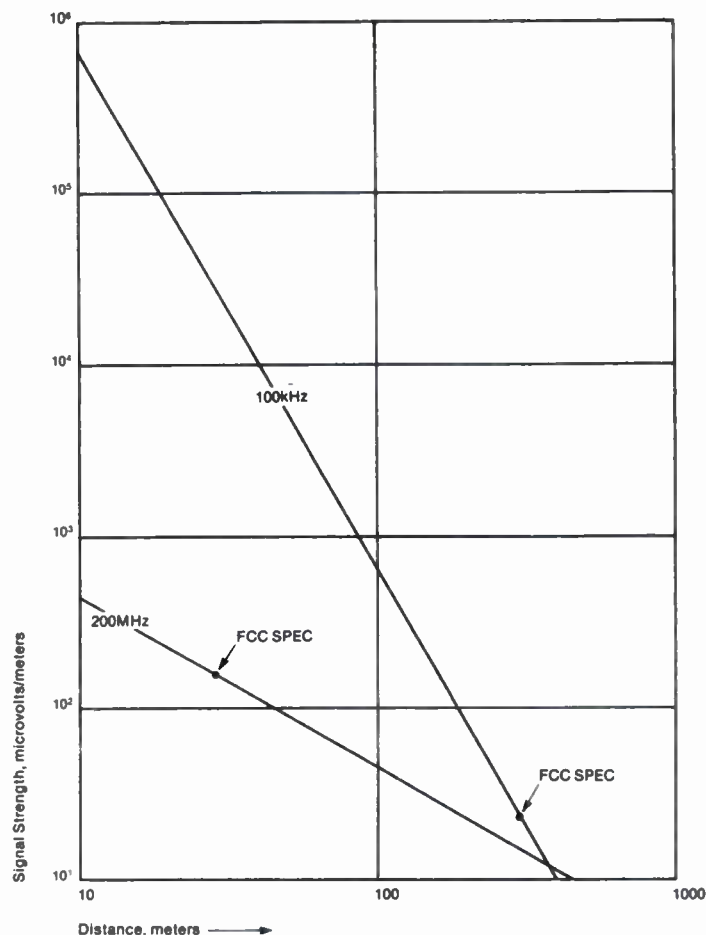


Fig. 3 Operation Under FCC "Low Power" Rules.

References

1. J.J. Hupert, "Remote Control by 'Near' Magnetic Field," *Electronic Industries*, July 1959.
2. Gaylord P. Hamwell, *Principles of Electricity and Electromagnetism*, McGraw-Hill Book Co., Inc., N.Y., NY, 1949, p.329.
3. Keith Henney, *Radio Engineering Handbook*, McGraw-Hill Book Co., Inc., N.Y., NY, 1959, p.19-7.
4. Frederick Emmons Terman, *Radio Engineers' Handbook*, McGraw-Hill Book Co., Inc., N.Y., NY, 1943, p.813.
5. John D Kraus, *Antennas*, McGraw-Hill Book Co., Inc., N.Y., NY, 1950, p.161.
6. "Reference Data for Radio Engineers," 4th ed., *International Telephone and Telegraph Corporation*, N.Y. NY, 1956, p.763.
7. Andrzej B. Przedpelski, "Loop antenna Design," *r.f. design*, November/December 1982.

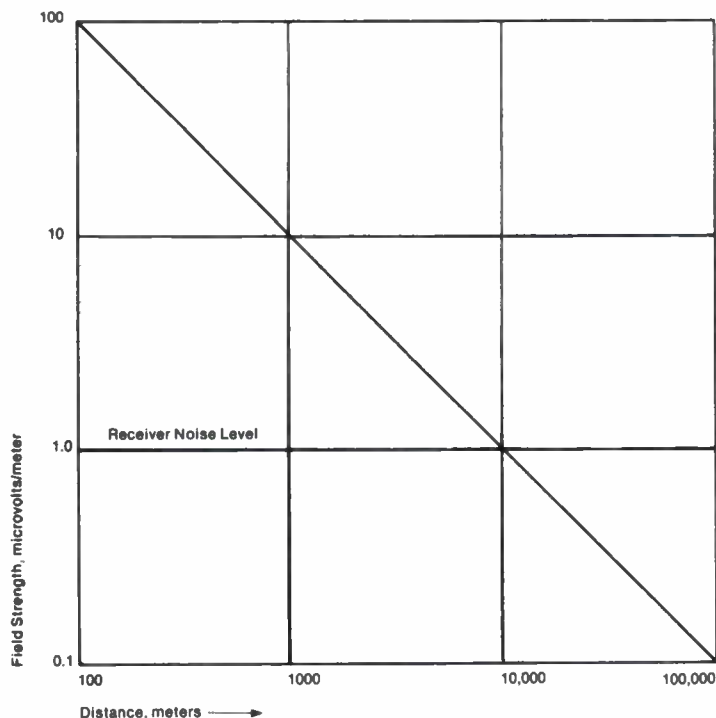


Fig. 4 Signal Levels Using 400 MHz.

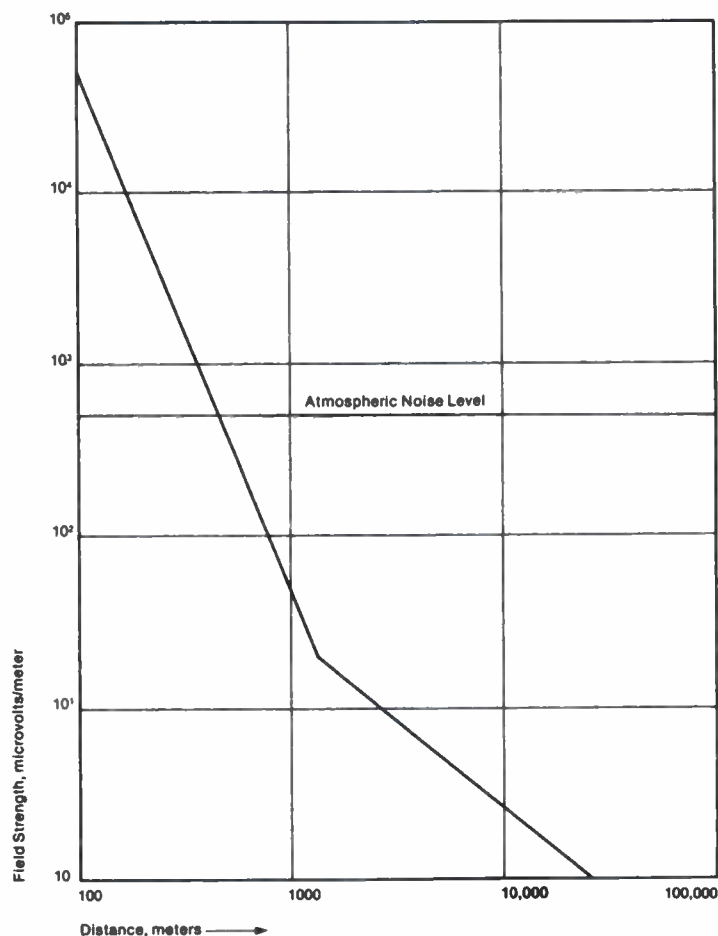



Fig. 5 Signal Levels Using 50 kHz.

VCA



VOLTAGE CONTROLLED ATTENUATORS

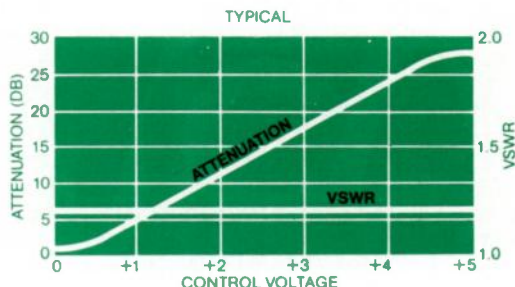- ✓ 50 to 1250 MHz
Frequency Range
- ✓ 20 or 40 dB Attenuation



- ✓ ± 0.5 dB Linearity
- ✓ 1.25 VSWR Max.

SPECIFICATION	P/N DA0244	P/N DA0243
Frequency	50-200 MHz	50-1250 MHz
VSWR	1.25 max.	1.5 max.
Linearity	± 0.5 dB	± 2.0 dB
Insertion Loss	1 dB max.	3.5 dB max.
RF Power	10 dBm	
Impedance	50 ohms	
Attenuation Range	20 dB min.	
Control	0 to +5 volts	
DC Power	15 volts at 60 mA -15 volts at 80 mA	



**Industry Leader in
Hybrid Switches,
Delay Lines, Step
Attenuators, Voltage
Control Attenuators**

DAICO INDUSTRIES, INC.

2351 East Del Amo Blvd., Compton, Calif. 90220
Telephone: (213) 631-1143 • TWX 910-346-6741

© 1980 Daico Industries, Inc. INFO/CARD 54 mp79411

Divider Delay: The Missing PLL Analysis Ingredient

This article will analyze PLL divider delay using control systems models and demonstrates the impact of delay on loop stability.

By Stan Goldman
Texas Instruments
Dallas, Texas 75230

Phase Lock Loops are used in many applications, but frequency generation is the most common. As design requirements for Phase Lock Loops (PLL) become more stringent, so does the importance of accurate analysis for loop performance. Most of the demanding PLL design decisions are related to increasing loop bandwidth to reduce noise and improve loop switching speed. The component values calculated using classical loop analysis equations have been used in circuits where the measured electrical response was not always in agreement with the calculated electrical response.

The discrepancy between theory and experiment was found to be attributed to divider delay which caused a decrease in phase margin significant enough in many cases to cause unstable loop performance. Divider Delay is one of the most significant parameters which limits larger Phase Lock Loop bandwidths. It is defined as the time delay from a changing frequency input to the dividers until the detection of the changing frequency by the phase detector. The time delay results from the many clock pulses required to change the divider's output state which is sampled by the phase detector's input reference clock frequency rising or falling edge. This article will analyze

Divider Delay using control systems models and demonstrate the impact of delay on loop stability.

To begin the analysis, Control Systems Theory will be reviewed, followed by the derivation of a PLL control system model. Next, through several algebraic rearrangements, equations will be derived to solve for circuit elements from which Bode plots of magnitude and phase of the Open Loop Transfer Function can be made. Finally, an example will be used to show the effects of Divider Delay.

The generalized Phase Lock Loop Function can be expressed in terms of Control Systems Theory as follows:

$$\frac{\theta_o(s)}{\theta_i(s)} = \frac{G(s)}{1 + G(s)H(s)} \quad (1)$$

Stability is determined by the $G(s)H(s)$ function, which is referred to as the Open Loop Gain Function. If $G(s)H(s)$ ever becomes equal to -1, then equation 1 becomes unstable. Naturally, the parameters that define the $G(s)H(s)$ function must be carefully scrutinized.

A type 2 second order loop is used to illustrate the analysis technique as shown in Figure 1. This circuit con-

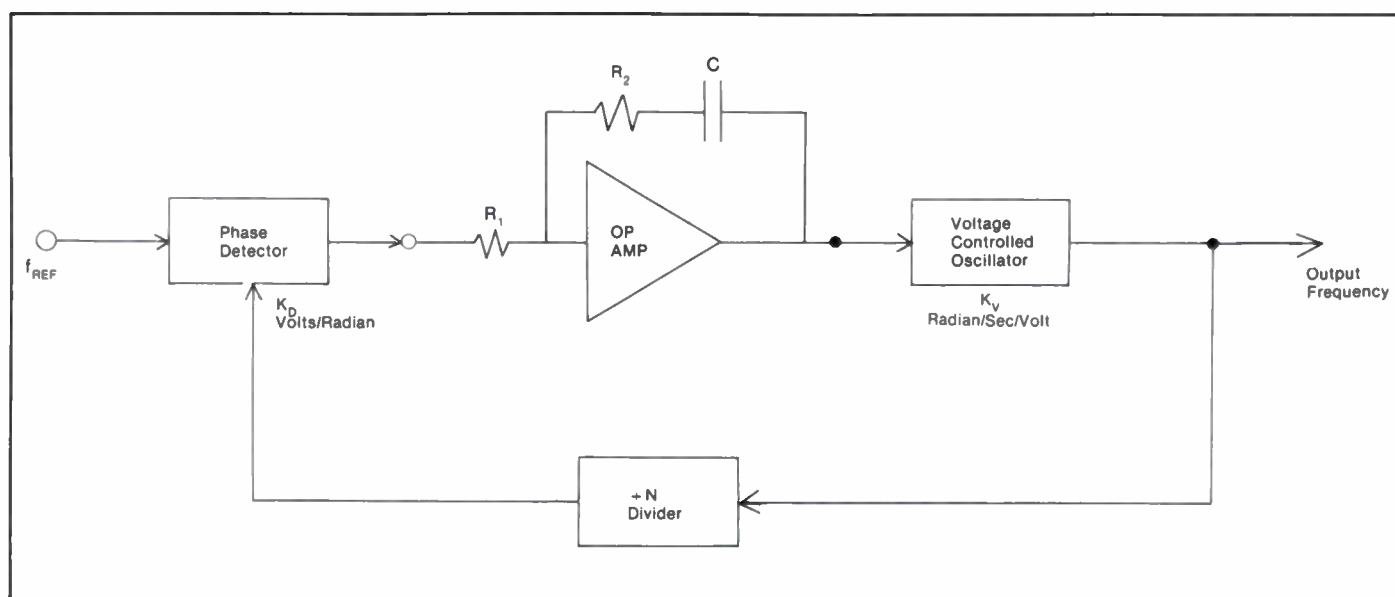


Figure 1. A Type 2 Second Order Loop.

NOW! In one manual— all you need to know about EMC design and products— and it's **FREE!**



If you're involved in designing for EMC—if you're involved in testing and measuring electromagnetic interference—you *need* this manual. For the first time, in one place, you'll find all the data, all the formulas, and all the products you need to meet your interference control problems!

Included are charts, tables, graphs, dimensional drawings, and technical data ranging from a discussion of theoretical design requirements to how to select a specific shielding material.

For your free copy, use the Reader Service Card or write us directly at Dept. RF-9.



INSTRUMENT SPECIALTIES COMPANY, INC.
Delaware Water Gap, PA. 18327
Phone: 717-424-8510 • TWX: 510-671-4526
Specialists in beryllium copper since 1938

INFO/CARD 32

figuration is generally used in frequency generation applications. From Figure 1 the Open Loop Gain Function can be mathematically described as follows:

$GH(s) = (\text{Phase Detector Gain}) (\text{Filter Transfer Function}) \times (\text{VCO Transfer Function}) (\text{Divider Transfer Function})$ (2)

$$= (K_D) \left(\frac{sCR_2 + 1}{sCR_1} \right) \left(\frac{K_V}{s} \right) \left(\frac{1}{N} \right) (e^{-sT}) \quad (3)$$

$$= \left(\frac{K_D K_V}{NCR_1} \right) \left(\frac{1}{s^2} \right) (sCR_2 + 1) (e^{-sT}) \quad (4)$$

where:

$T = 1/\text{Reference Frequency}$ $K_V = \text{VCO Transfer Function}$
 $K_D = \text{Phase Detector Gain}$ $N = \text{Integer divider value}$

Equation 4, the Open Loop Transfer Function, is organized into terms which can be expressed easily using Bode Plot graphic techniques. The first term represents a gain constant; the other terms represent Bode Plot functions of frequency. Notice the two poles at the origin. This term represents two integrators which will force the error function closer to zero with decreasing frequency. The last term is the mathematical representation of delay. Equation 4 was derived using references 2 and 3.

When designing a Phase Lock Loop, the loop requirements are generally specified by loop bandwidth, output frequency ($N \times \text{Reference Frequency}$), and stability (Damping Factor) parameters. Using these parameters and equation 4 one can determine circuit elements necessary to meet the loop performance requirements.

To calculate circuit elements for the PLL requires several operations. First, an equation for phase variations versus frequency must be developed and used to solve for the frequency location of the Zero ($1/2\pi R_2 C$). Next, a magnitude versus frequency equation must be calculated and used to solve for the value of the Gain Constant term ($K_D K_V / NCR_1$).

Stability requirements are determined by the phase of $GH(s)$. If the phase equals 180° and the magnitude equals unity, then oscillations will occur. The loop bandwidth is the frequency where the Open Loop Transfer Function equals unity. The last term of equation 4, $((sCR_2 + 1)e^{-sT})$ contains phase variations versus frequency, while the other terms have a constant phase. Therefore, the other terms can be put aside. Now, solving the last term in equation 4 for phase:

$$\text{Phase} = \text{ARCTAN} \left[\frac{(\sin(-\omega T) + (\omega R_2 C)(\cos(-\omega T)))}{\cos(-\omega T) - (\omega R_2 C)(\sin(-\omega T))} \right] \quad (5)$$

Where:

$\omega = 2\pi f$

$f = \text{Frequency variable}$

Equation 5 can be used to plot the Open Loop Transfer Function's phase variation as a function of frequency. To find the frequency location of the Zero and thereby insure the required loop stability, equation 5 has to be rearranged, and values substituted. The stability requirement can be expressed by Damping Factor values and then expressed in terms of phase by the following formula:


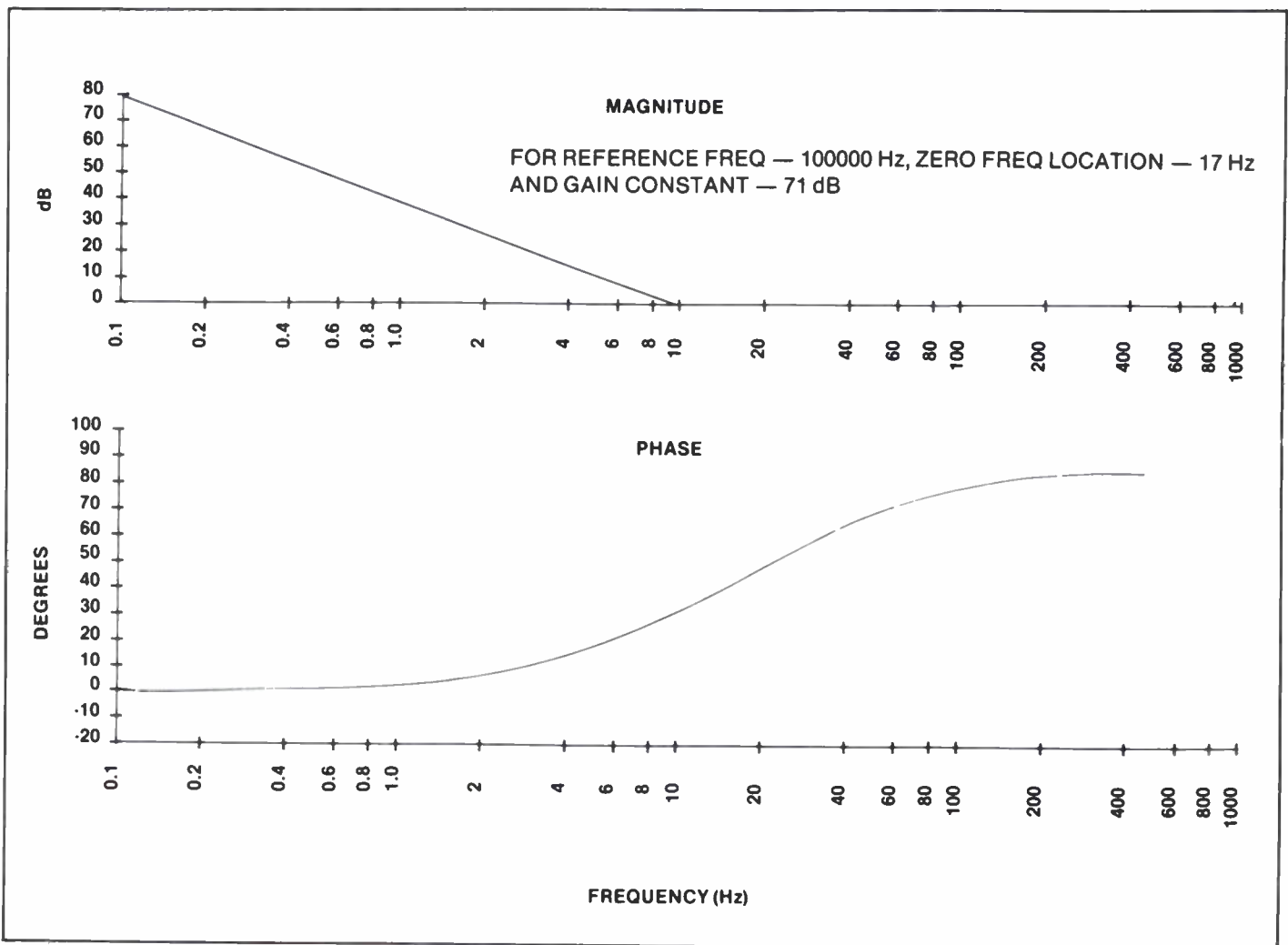


Figure 2. Classic PLL Solution

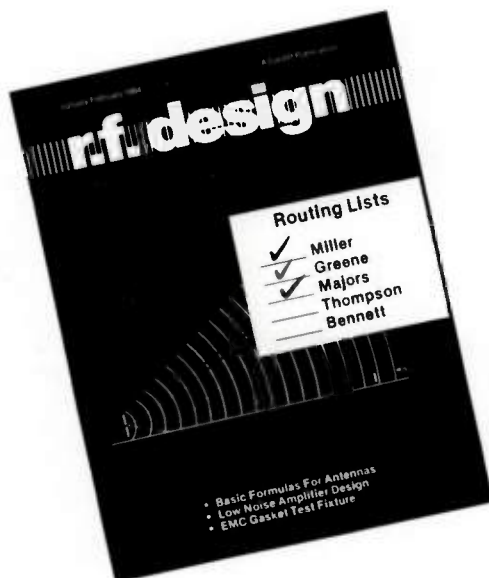ARE YOU WAITING IN LINE FOR YOUR INFORMATION?



Order your own **FREE** subscription to R.F. Design Magazine Today, and get off the routing list.

You'll get the information you want, when you want it; no waiting. No copies with articles already cut out or pages missing.

By Subscribing before April 1, 1984 you will also receive the 1st Annual R.F. Design Directory. This directory zeroes in on products used in R.F. systems and equipment . . . the "bits and pieces" which go into them, the instruments used to develop and test them and the subsystems incorporated into them.

Order your FREE subscription to R.F. Design Magazine today. Fill out the enclosed subscription card and send it in.

LMI shielded rooms. Your best investment.



Clamp-together Shielded Rooms

- Prefab, modular, demountable.
- Excellent RF attenuation.
- Unequalled structure rigidity and electrical circuit integrity.
- Easy to assemble and relocate.


All-welded Shielded Rooms

- Super RF attenuation.
- Supplied for NSA 65-5 and other secure specs where 100 to 120 db shielding is required from 1.0 to 10 KHz, to 10 GHz and higher.
- Meet storage and vault needs.
- Ask for catalog LSR-1000.

RF Shielded Anechoic Chambers

Plus these LMI benefits

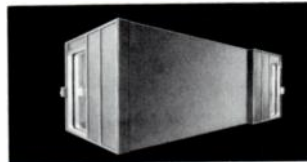
- Complete turnkey facilities by nationally known EMI engineers.
- Specifications design and engineering services.
- Registered professional engineers; licensed contractors.
- After-sale service; long-term upgrading.
- Ask for catalog LDC-500.



To discuss your needs call or write Fred Nichols, LectroMagnetics, Inc. 6056 West Jefferson Blvd. Los Angeles, CA 90016 (213) 870-9383



INFO/CARD 50

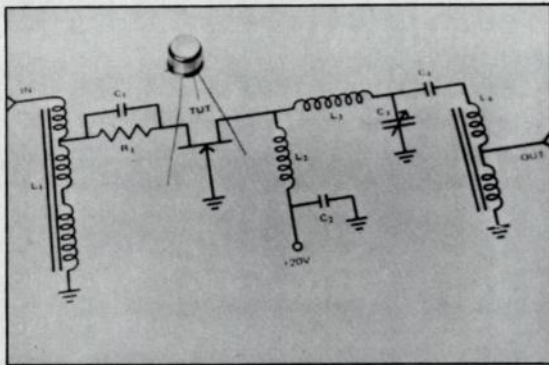

HIGH VOLTAGE BROADBAND RF FET

High dynamic range RF FET now available up to 50V BVDGO, for use with 24 & 32V supplies, and where higher drain voltage improves dynamic range. The CP664 (30V), CP665 (40V), and CP666 (50V) have third order intermodulation intercept >+40 dBm, and 50 Ohm VSWR <1.5 to 1 over 0.5 to 50 MHz range.

HIGH VOLTAGE RF FET



147 Sherman Street, Cambridge, MA 02140
Tel: (617) 491-1670 • TWX 710-320-1196

Phase Angle = $2DX$

where:

D = Damping Factor

$$X = (2D^2 + (4D^4 + 1)^{0.5})^{0.5} = \frac{\omega_{BW}}{\omega_N}$$

ω_N = natural frequency

$$\frac{f_{BW}}{f_{BW(3dB)}} = \frac{X}{(1 + 2D^2 + ((1 + 2D^2)^2 + 1)^{0.5})^{0.5}} \approx 1$$

EXAMPLE

Optimum Solution of Figure 4

Given:	Detector	= .4V/Radian (Fairchild 11C44)
	K_V	= 125,000 (XR 2207)
	N	= 64
	D	= .27
	BW	= 10 Hz
	Ref. Freq.	= 100 Hz
Choose:	C	= 1 ufd
Solution:	R_1	= 489K
	R_2	= 35.9K
	BW (3dB)	= 15 Hz
	Freq. Crossing	= 10 Hz
	R_2/R_1	= .0735

Now, the phase angle value where the magnitude of the Open Loop Transfer Function equals unity determines phase stability. The number of phase angle degrees greater than -180 degrees (ie. instability) is called the Phase Margin. The frequency where the Open Loop Transfer Function equals unity is defined as the Loop Bandwidth. Therefore, equation 5 can be solved for the Zero Frequency Location:

$$f_{zero} = \frac{(-\omega_{BW} \sin(\omega_{BW}T)) (\tan(\text{phase angle}) + \omega_{BW} \cos(\omega_{BW}T))}{(\tan(\text{phase angle})) (\cos(\omega_{BW}T) + \sin(\omega_{BW}T))} 2\pi$$

where:

$$f_{zero} = \frac{1}{2\pi R_2 C}$$

$$\omega_{BW} = 2\pi f_{BW(3dB)} \left(\frac{f_{BW}}{f_{BW(3dB)}} \right) = \text{zero magnitude crossing of GH}$$

T = 1/Reference Frequency = $N/\text{Output Frequency}$

N = Loop Frequency Multiplication Factor

f_{BW} = Loop Bandwidth (Zero Crossing)

$f_{BW(3dB)}$ = 3dB Bandwidth

Now that the frequency location of the Zero is determined, more circuit parameters can be calculated. The magnitude response of equation 4 can now be solved:

$$|GH(f)| = \left(\frac{K_D K_V}{NCR_1} \right) \left(\frac{1}{\omega^2} \right) \left[\left(1 + \left(\frac{f}{f_{zero}} \right)^2 \right) \right]^{0.5} \quad (8)$$

where:

$$\omega = 2\pi f$$

Equation (8) can be used to plot the Open-Loop Transfer Function magnitude versus frequency. However, since the Zero frequency is located by solving equation 7 and the bandwidth is a known requirement, then equation 8 can also be used to solve for the Gain Constant after being set equal to unity at the Loop Bandwidth frequency:

$$\text{Gain Constant} = \frac{K_D K_V}{NCR_1} = \frac{(2\pi f_{BW})^2}{\left[1 + \left(\frac{f_{BW}}{f_{zero}}\right)^2\right]^{0.5}} \quad (9)$$

This leaves the parameters K_D , K_V , N , C , R_1 , and R_2 to be determined. The parameters K_D and K_V are determined by component selection. N is determined by the frequency multiplication requirement. Thus, C , R_1 and R_2 remain to be calculated. From equation 7.

$$C = \frac{1}{2\pi R_2 f_{zero}} \quad (10)$$

Substitution of equation 10 into equation 9 results in the following resistance ratio:

$$\frac{R_2}{R_1} = \frac{N(\text{Gain Constant})}{K_D K_V 2\pi f_{zero}} \quad (11)$$

Unfortunately, there are two equations and three unknown variables. Therefore, engineering experience can be used to select component values. First select a reasonable capacitor value which will make the circuit component non-electrolytic or one with excellent frequency response characteristics. Now, equation 10 can be solved for R_2 and then R_1 can be calculated from equation 11. Check the resistance values calculated and compare these values to the range of resistances that the Phase Detector data sheet specifies. Also check the Op Amp specification sheet for gain (R_2/R_1) for frequencies less than the loop bandwidth and resistance ranges. If these criteria are not met then recalculate until they are achieved or find other devices which can accommodate the design calculations.

Examples


The effects of delay can be shown through examples. The PLL example design requires a 10 Hz Loop Bandwidth, a Damping Factor of 0.27, and a Reference Frequency of 100 KHz. Figure 2 shows a Bode Plot with the results of a Zero Frequency Location of 17 Hz and a Gain Constant of 71 dB. Note the Phase Margin is ≈ 30 degrees at 10 Hz and the magnitude is at 0 dB to give a 10 Hz Loop Bandwidth. These results are the common classic solutions seen in several references. Many references suggest no Loop Bandwidth limitations; however, unexplained bandwidth limitations were encountered in circuit applications. Note the reference frequency is a factor of 10,000 greater than the Loop Bandwidth.

A new plot can be calculated with the Reference Frequency at 100 Hz or 10 times greater than the Loop Bandwidth. The new plot is shown in Figure 3. One notices that the Phase Margin has gone negative and that results in an unstable loop. This demonstrates the dramatic effect of delay on loop performance.

A new solution for the example with reference frequency at 100 Hz can be calculated. Using the derived equations which include Divider Delay effects, results in Figure 4 which shows a 4 Hz Zero Frequency Location and a 64 dB Gain Constant and has a 30 degree Phase Margin (0.27 Damping Factor). Also notice the magnitude of 0 dB at 10 Hz (3dB BW = 15Hz from Equation 7.) results in a Loop Bandwidth of 10 Hz. Thus an unstable loop in Figure 3 can be adjusted to meet loop requirements as shown in Figure 4.

With the establishment of these equations, a few tables can be used to aid PLL design. The first table in Figure 5 shows Damping Factor versus Loop Bandwidth to

r.f. design

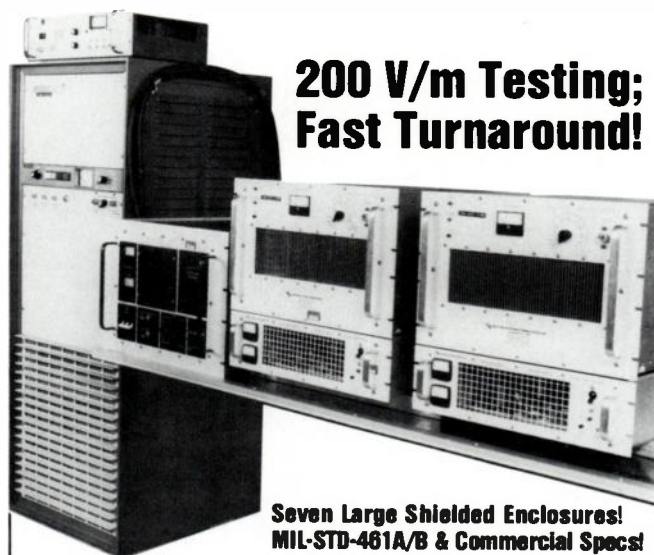

200 V/m Testing; Fast Turnaround!

**Seven Large Shielded Enclosures!
MIL-STD-461A/B & Commercial Specs!**

- Radiated Susceptibility Testing 10 kHz - 18 GHz
- Enclosure Treated with R.F. Anechoic Material
- Emissions Testing: 20 Hz to 18 GHz
- Modern Semi-Automatic Swept EMI Receivers
- Mobile EMI Vans for Remote Site Testing
- 25 Years of EMI/EMC Experience
- EMC Consulting; Custom EMI Filter Designs

Call or Write For Capabilities Brochure!



GENISCO
TECHNOLOGY CORPORATION
EMC Engineering Services Division

18435 Susana Rd., Rancho Dominguez, CA 90221, (213) 537-4750, TWX: 910-346-6773

INFO/CARD 52

HIGH PERFORMANCE

POWER DIVIDERS



Janel offers a wide variety of standard power dividers. The chart below shows a sampling of what's available. All feature high *guaranteed* performance and yet are competitively priced. Many models are available from stock.

Model	Outputs	Frequency	Isolation	VSWR
PD7724	2	20-512MHz	25dB	1.35
PD7725	4	20-512	25	1.35
PD7726	8	20-512	25	1.35
PD7852	12	2-512	25	1.5
PD7905	4	2-50	30	1.2
PD7848	8	800-960	25	1.35

In addition to Power Dividers, Janel manufactures a wide range of standard Amplifiers and other rf components. Custom designs can be provided for unusual applications. For detailed information, call or write Janel Laboratories, Inc., 33890 Eastgate Circle, Corvallis, OR 97333. Telephone (503) 757-1134.



JANEL LABORATORIES

INFO/CARD 53

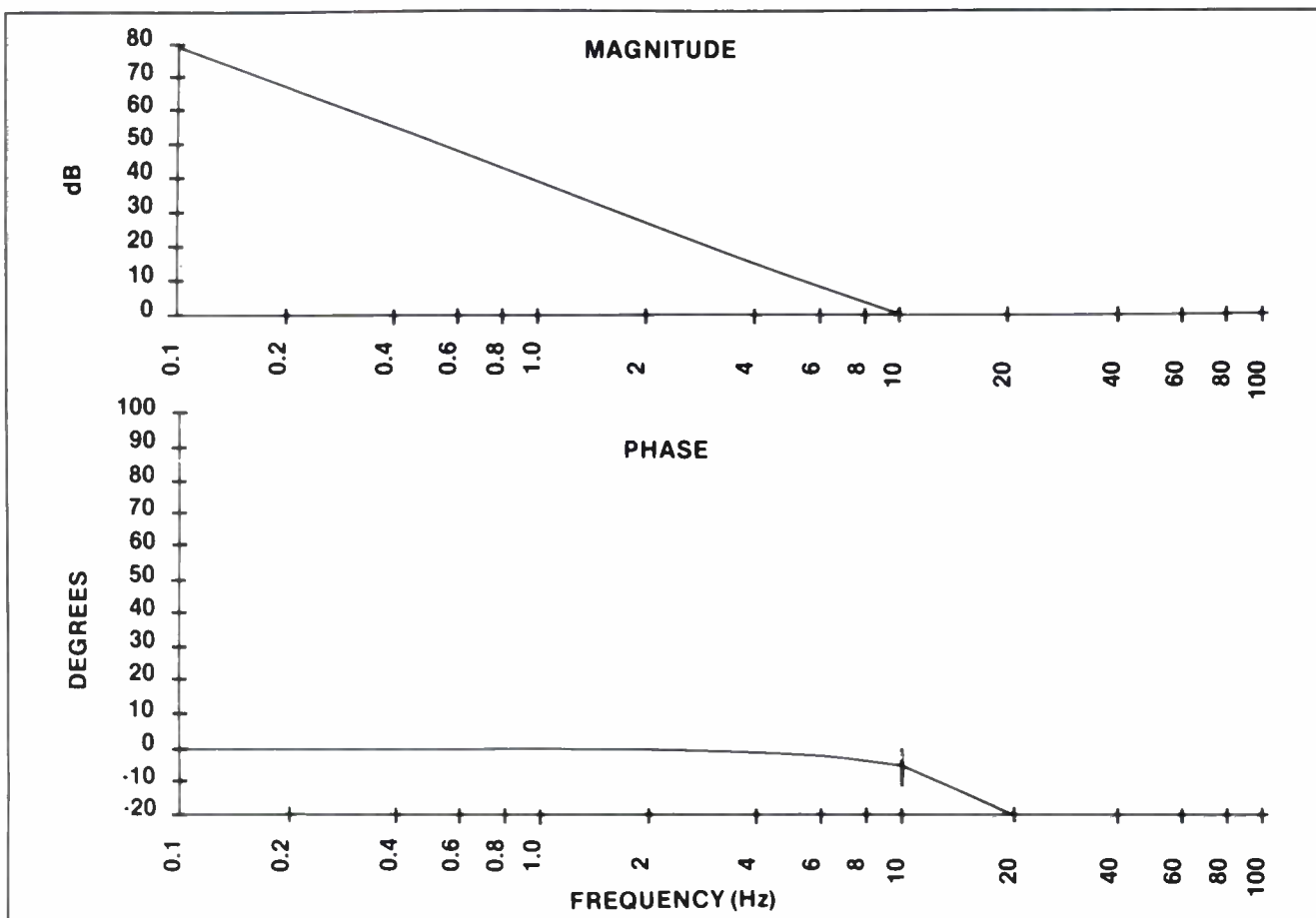


Figure 3. PLL open-loop transfer plot for reference freq- 100Hz. Zero freq location- 17Hz and gain constant- 71dB

NEW! No-Snag Fingers for RFI/EMI Shielding

Beryllium copper shielding gaskets engineered for computer applications which must comply with the FCC RFI Interference requirements. NO SNAG FINGERS feature pressure sensitive adhesive mounting or the Tech-Etch "Clip-On" design for fast, reliable assembly.

- Eliminates broken fingers
- Self cleaning contact surfaces
- Special plating available
- Finger width from 3/32"
- Bright standard finish
- Gaps up to 3/16"

Series M

For a free sample, please forward your request on your company letterhead

For more than 35 years, the Braun Division of Tech-Etch has been supplying standard and custom designed shielding gaskets to companies in this country and abroad. Always abreast of the latest requirements, Tech-Etch engineers can solve your shielding problems.

Tech-Etch
Braun Division

Tech-Etch, Inc. / 45 Aldrin Road, Plymouth, MA 02360 / (617) 747-0300

DAMPING	BW/REF RATIO
0.10	0.22
0.20	0.19
0.30	0.16
0.40	0.13
0.50	0.11
0.60	0.09
0.70	0.07
0.80	0.06
0.90	0.05

Figure 5. Bandwidth to reference frequency ratio for a zero location at 0Hz.

DAMPING	ZERO/BW RATIO	GAIN CONST (dB 1Hz BW)
0.05	1.12	29.38
0.1	0.92	28.53
0.15	0.75	26.26
0.2	0.61	24.75
0.25	0.49	22.9
0.3	0.38	20.56
0.35	0.28	17.45
0.4	0.19	12.84
0.45	0.11	3.57
0.5	0.04	
0.55	negative	

Figure 6. Calculation of damping factor versus normalized zero location for BW/REF ratio of 0.1

Reference Frequency ratios. This table show ideally how close the Reference Frequency can be to achieve the Damping Factor shown. System choices in determining Loop Bandwidth, Reference Frequencies and stability can be aided with this table.

Figure 6 shows another table which locates the Zero Frequency Location relative to Loop Bandwidth for different Damping Factors at a 0.1 Loop Bandwidth to Reference Frequency ratio. Notice to achieve higher Damping Factor (greater stability), the Zero Frequency Location approaches 0 Hz, while the Gain Constant decreases to compensate for the Zero Frequency Location. This table gives insight into the Zero Frequency Locations effect on stability.

Conclusion


The results of this paper will allow more analysis of Phase Lock Loops before they are built and modifies the classic PLL approach to solve an increased number of PLL problems. It has been shown that for wide bandwidths the delay term is a dominating factor in determining bandwidth. Thus, an aid to System Designers has been developed so that the feasibility of proposed Phase Lock Loops can be determined.

References

- Przedpelski, Andrzej B., "Analyze Don't Estimate Phase Lock Loop Performance," *Electronic Design*, Vol. 26, No. 10 (May 10, 1978).
- Gardner, Floyd Martin, *Phaselock Techniques*, John Wiley & Sons, New York 1966.
- Hutchinson, "Contemporary Frequency Synthesis Techniques," Gorshi-Popiel, J, *Frequency Synthesis: Techniques and Applications*, IEEE Press, New York (1975).

r.f. design

CINOX

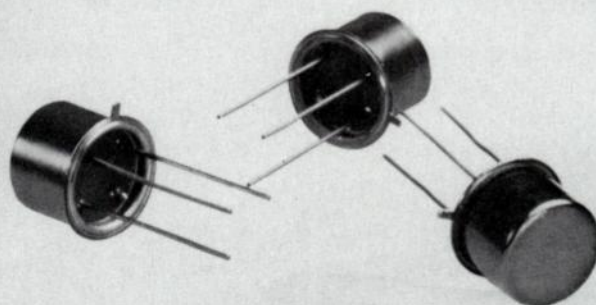

MICROWAVE FREQUENCY CONTROL

Low Phase Noise. CINOX offers a complete line of TO-5 and other coldweld crystals for microwave applications.

Available frequencies range up to 250 MHz. Frequency tolerances as tight as $\pm 0.0005\%$ at operating temperature, with stabilities of $\pm 0.0005\%$ from -10°C to $+60^{\circ}\text{C}$, or $\pm 0.0001\%$ from 73°C to 77°C , are available. Typical crystal aging is within $\pm 0.0001\%$ per year under normal ambient conditions.

CINOX is the industry leader in low phase noise crystals, currently supplying crystals for applications requiring -170 dbc @ 1 KHz . When aerospace and defense engineers need performance under the stress of high shock and vibration, CINOX is the preferred source.

Call today to discuss your precise application with a crystal sales engineer. Or, write for a copy of our complete, up-to-date product catalog.

- OCXO's
- TCXO's
- VCXO's
- PRECISION CRYSTALS
- CHANNEL CRYSTALS

CINOX CORPORATION

4914 GRAY RD., CINCINNATI, OH 45232
PHONE 523/542-5555 TWX 810-461-2749

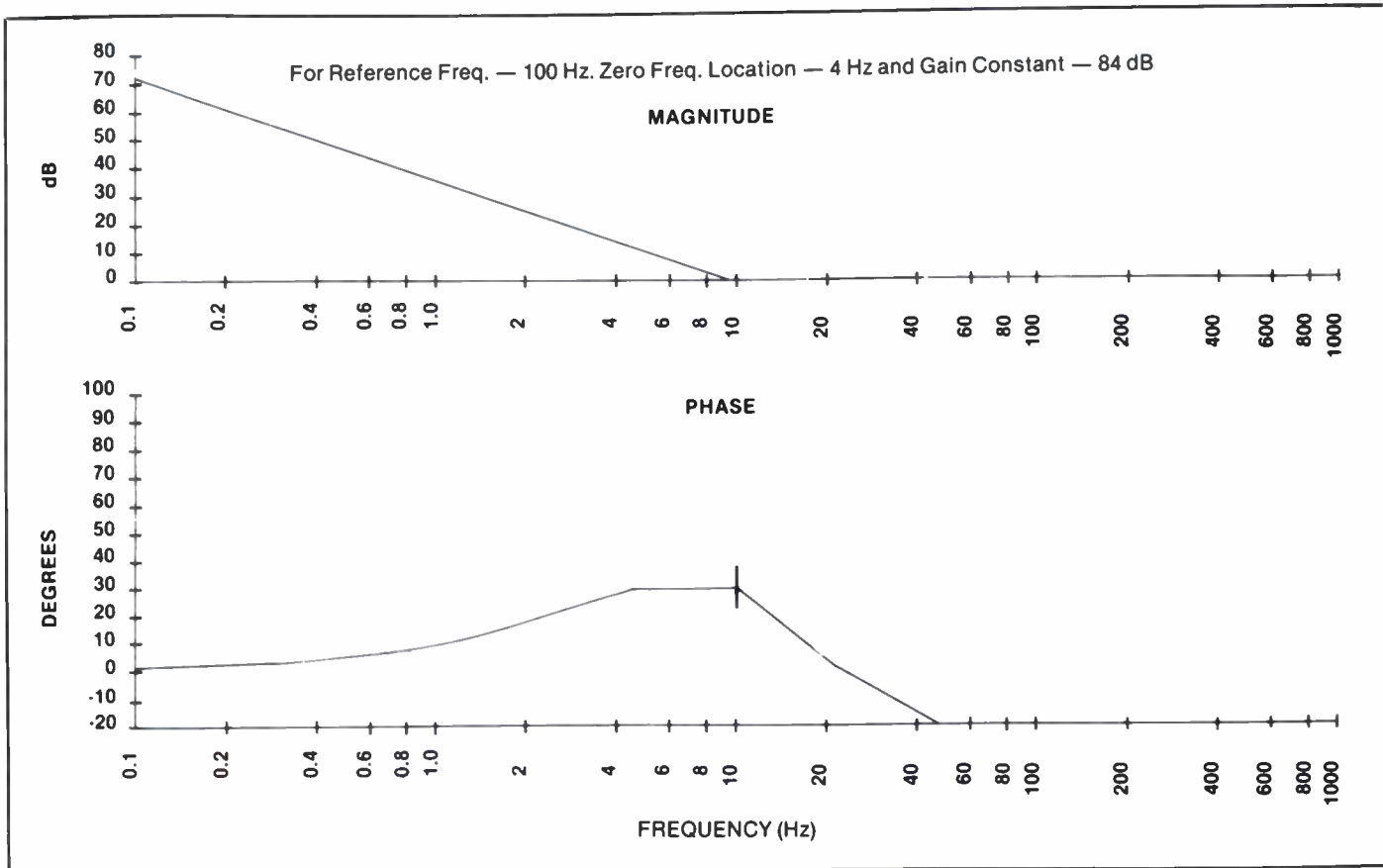


Figure 4. Modified PLL Solution.

June 1984

r.f. design directory

AMPLIFIERS CAPACITORS CONVERTERS
CRYSTALS ENCODERS DIODES SWITCHES
INDUCTORS RESISTORS TRANSFORMERS
TRANSISTORS HOUSINGS SUBSTRATES
ANTENNAS VARACTORS ATTENUATORS
DIVIDERS COUPLERS CABLES DOUBLERS
DETECTORS OSCILLOSCOPES BRIDGES
DISCRIMINATORS FILTERS RECEIVERS
LIMITERS METERS RELAYS OSCILLATORS
MODULATORS WATTMETERS COUNTERS
SWEEPERS GENERATORS SYNTHESIZERS
VOLTMETERS COMBINERS CIRCULATORS

r.f. design plans a designer's directory to be published in June 1984.

If you manufacture products in this market and would like to be listed in the directory, please contact Grace Brewster, 6530 So. Yosemite, Englewood, CO 80111, 303/694-1522.

Now! EMC testing services from Instrument Specialties— the company that knows shielding inside and out!

If you're involved with keeping RFI/EMI in or out, you already know about Instrument Specialties. You've probably used our beryllium copper shielding strips...received our engineering help...even used our new line of ESD devices.

And *now*—the superb EMC testing facilities we use to assure performance of our products is *available to you for the first time*. You now can access the sophisticated equipment you don't have—but *must* have—to secure the test results you need!

State-of-the-art computer-controlled emission and susceptibility measurements from 10 kHz to 1 GHz...RF gasket evaluation...FCC/VDE/CISPR and MIL-STD-461A/B Tests...networks for power line conducted RF emission tests...semi-anechoic shielded enclosure...confirming open field test site...computer-produced hard copy readout of test results—all are yours at Instrument Specialties.

Following testing, you'll leave our facility with the precise documentation you need. In the event you need help to meet required interference specifications, we can supply that as well. All this, from one qualified source!

For more information, rates, and schedule availability, phone us and ask for EMC Customer Service. Or, write us at Dept. RFD-10.







INSTRUMENT SPECIALTIES COMPANY, INC.

Delaware Water Gap, PA. 18327

Phone: 717-424-8510 • TWX: 510-671-4526

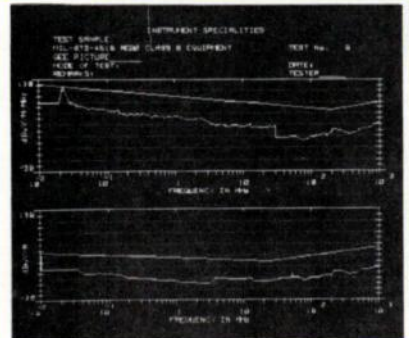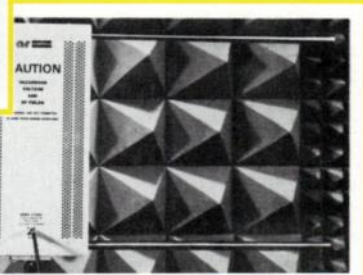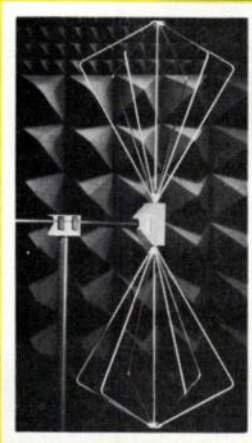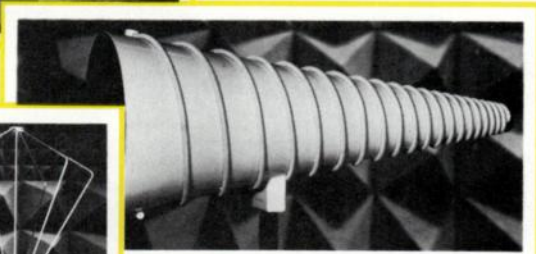
Specialists in beryllium copper since 1938




r.f. designers notebook

A Wideband, Low Intermodulation Electronic Attenuator Using PIN Attenuator Diodes

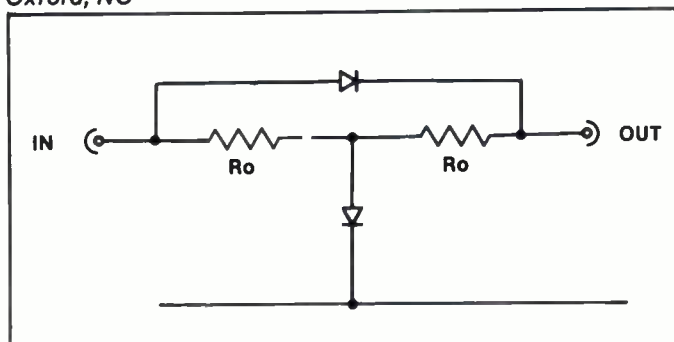By Robert Dennison
Channel Master Satellite Systems
Oxford, NC



Bridged T Network

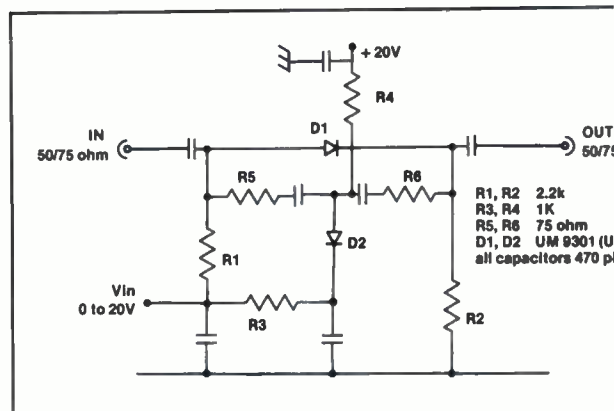

Actual Circuit Developed

Application

Broadband systems such as cable television a.g.c. circuits where intermodulation is of prime concern.

Circuit Description

Based on the well known bridged - T network shown above:

At high input voltage and low attenuation, D1 tends to conduct the signal.

R1 and R2 set the current and isolate the DC. D2 tends to be off.

At low input voltage and high attenuation, D1 tends to be off. D2 tends to bypass the signal to ground. R3 and R4 set the current and isolate the DC. R5 and R6 maintain the characteristic impedance.

Performance -

This is largely dependent on construction techniques. The following results were obtained using standard components with ultra short lead a printed circuit board. Chip components would greatly enhance performance.

When fed by every cable T.V. channel up to 400 MHz at levels up to -3 per carrier, intermod products lower than -65 dB.

The following summarizes attenuation, flatness and return - loss:

One Section		100 MHz		200 MHz		400 MHz	
INPUT VOLTS		LOSS dB, R-LOSS dB		LOSS dB, R-LOSS dB		LOSS dB, R-LOSS dB	
20		2	18	2	24	3	1
16		4	26	4	20	5	1
12		6	23	6	17	6	1
8		8	28	8	18	8	1
4		10	24	10	20	10	1
2		14	18	14	18	13	
1		18	15	18	15	18	
0		22	14	21	14	18	

Two Series Sections -		100 MHz		200 MHz		400 MHz	
INPUT VOLTS		LOSS dB, R-LOSS dB		LOSS dB, R-LOSS dB		LOSS dB, R-LOSS dB	
20		4	15	4	16	5	
18		7	23	7	18	8	
14		10	16	10	14	10	
8		15	20	15	15	14	
5		19	30	18	18	16	
3		24	25	23	19	20	
2		29	20	28	18	24	
1		38	15	35	15	28	
0		46	13	40	14	31	

application note

A 50-350 MHz, 50 OHM Amplifier With 24dB Gain

By Gary McCollum
California Eastern Laboratories, Inc.

Introduction

This two stage amplifier is designed to operate over the 50-350 MHz communication band. Using NEC's NE99532 transistor in a 50 ohm system, the design achieves noise figures at the band edges of 3.1 dB and 3.0 dB with a typical gain of +24 dB. P_{1dB} at the band edges is 11.6 dBm and 20.4 dBm. Construction is on a single sided copper clad G10 circuit board material.

Specifications

The electrical parameters of the NE99532 amplifier are shown below:

$$V_{CC} = 18V, I_{CC} = 55mA$$

Frequency (MHz)	NF (dB)	Gain (dB)	Input Return Loss (dB)	P_{1dB} (dBm)
50	3.1	+24.2	-20.0	11.6
100	2.6	+24.0	-17.0	13.6
150	2.2	+24.1	-22.0	16.5
200	2.3	+24.4	-13.5	19.7
250	2.4	+24.0	-24.0	21.0
300	2.6	+24.0	-21.5	21.8
350	3.0	+24.6	-20.0	20.4

Circuit Description

Figure 1 shows the amplifier's circuit design. The input circuit is a 50 ohm low pass/high pass network followed by a transformer for matching to the first NE99532 transistor. In the interstage matching network, inductor L_5 series tunes the output of the first stage transistor and is followed by a high pass filter to flatten the gain. The output circuit

uses L_8 to series tune the output of the second stage transistor; the two-section high pass filter matches the output to 50 ohms. Any out-of-band response is stabilized by placing a 68 ohms resistor in parallel with an RF choke connected to the collector of each transistor. Figure 2 shows the printed circuit board's actual size and component layout.

Tuning And Performance

Tuning of the input, interstage and output circuits is accomplished by spreading the turns of the inductors to obtain the best matching conditions and frequency responses. Figures 3 and 4 show the performance of the prototype amplifier.

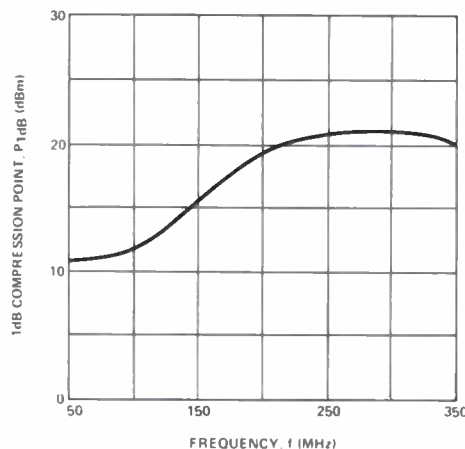


Figure 3. P_{1dB} vs. Frequency.

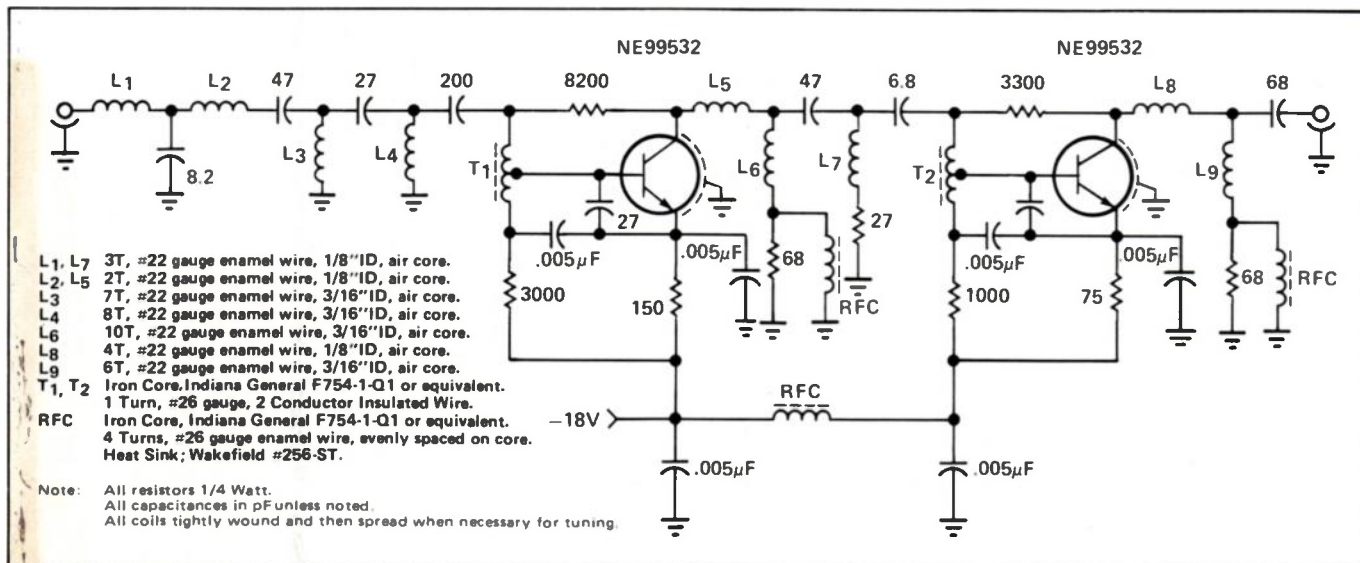


Figure 1. Amplifier Schematic.

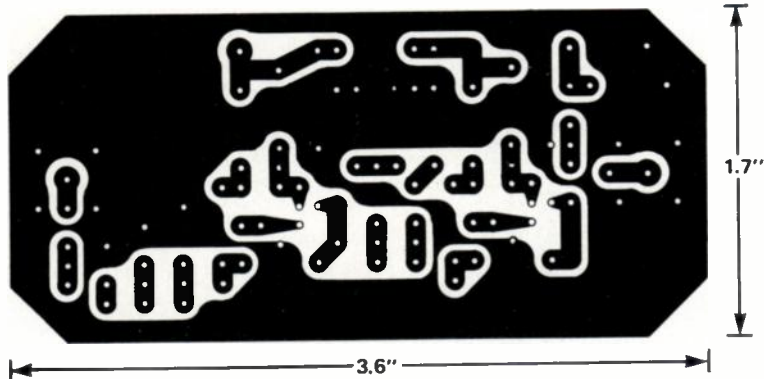


Figure 2. Printed Circuit Board and Layout; Actual Size.


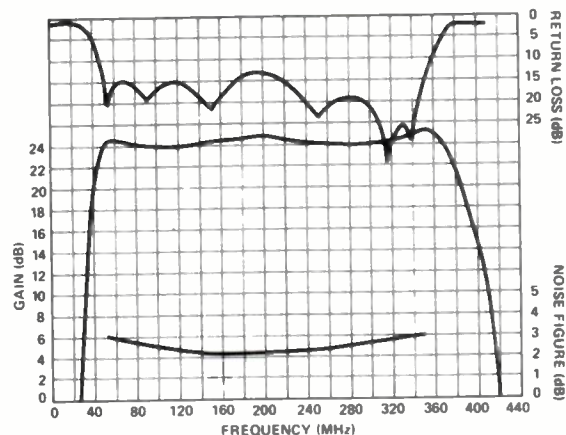



Figure 4. Gain/Return Loss/Noise Figure vs. Frequency.

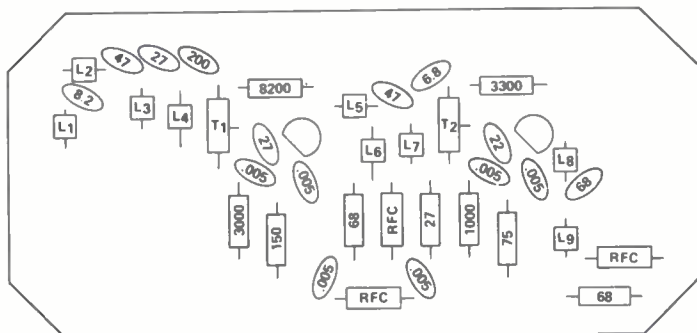

Based on an application note,
(AN83301) from California
tern Laboratories, Inc.

HYBRID SOURCES

With Integral Bandpass Filter

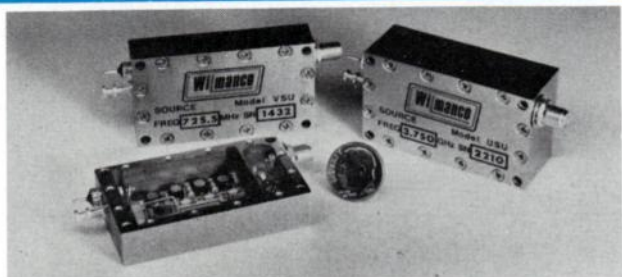

Model VSC & VSU

- 1-750 MHz
- 35 mA @ +15-32V
- 2.22" x 1.3" x 0.5"

Model USC & USU

- 750 MHz - 4 GHz
- 150 mA @ +15-32V
- 2.22" x 1.3" x 0.8"

Stability:

VSC & USC: $\pm 0.005\%$ +10°C to +45°C

VSU & USU: $\pm 0.03\%$ -25°C to +85°C

RF Power Output: +10 dbm min. Harmonics: > -50 dbc

Delivery: 45-60 days

Wilmanco

MANUFACTURERS OF MICROWAVE PRODUCTS

19529 Business Center Drive, Northridge, CA 91324

(818) 993-1662

Our Reader Service Card
brings you more information
about products, companies,
and services advertised in
the pages of

rf. design

Be sure to use this valuable
free service to help you
make better informed
management decisions.

Consider the source.

HP's 8656A programmable signal generator



Consider the value.

Versatility.

The HP 8656A synthesized RF signal generator is fully HP-IB programmable. Even your most time-consuming tests can be readily automated, increasing productivity in the laboratory and throughput on the production test floor.

Performance.

With a frequency range of 100kHz to 990MHz, the 8656A's signals are accurate and stable with good spectral purity. You get 100 or 250Hz resolution, an output range of +13 to -127dBm with microprocessor-controlled unit conversion, ± 1.5 dB absolute accuracy and 0.1dB resolution. Low RFI leakage provides confidence in micro-volt

level signals. AM and FM are available from both internal and external sources and simultaneous modulation modes are easily generated. All this and reverse power protection and HP-IB are standard.

Quality.

The 8656A incorporates HP's 30 years of experience in designing and manufacturing high performance signal generators. Our reputation for designed-in quality and reliability is backed world-wide by a responsive sales and service network.

Economy.

At \$7150*, the 8656A is HP's lowest-priced programmable signal generator. It's a price-performance value that makes good economic sense for both laboratory and production environments in a broad range of applications.

Consider the exceptional value of the 8656A. You may find that it's just the right source for you. To put the 8656A to work in your particular application, or for help in choosing from our broad line of signal generators, contact your nearby HP sales office. Or write, Hewlett-Packard, 1820 Embarcadero Road, Palo Alto, CA 94303.

*U.S. domestic prices only.

Consider HP

10202



**HEWLETT
PACKARD**

Microwave Circuit Analysis Program

NODAL® runs on a standard IBM PC® with 128K memory.

This program will analyze a circuit with up to 50 elements and 15-nodes. 19 different element types are available including resistor, inductor, transformer, current source, transmission lines, microstrip, stripline, 2 port models and data files. 9 unique graphic outputs with plot times typ < 4 sec. give fast design information. Abundant print options with up to 50 frequency points.

Other features include:

- Operating manual
- Step-by-step procedure
- Program on 5-1/4 disk plus file disk including demo
- Large element library
- Low cost design tool
- Simple node connection system
- Verified, high accuracy
- Easy editing
- Multiple plots
- Eliminates main frame time
- Store element & data files for future use

This is an engineering program... Ready to generate parameters on products.

You can do all this for \$695.00. Ready now!

IBM is a registered trademark of International Business Machines Corporation.

order

- ☐ I want to order _____ programs now! (10% off second order)
- ☐ Please have salesperson call.

Name _____

Company _____

Address _____

City _____

State _____ Zip _____

Telephone (____) _____


IR&D

ELECTRONICS

2218 Old Middlefield Way, Suite M
Mountain View, CA 94043
Phone: 415/969-5484

Wideband Microwave Network Analyzer

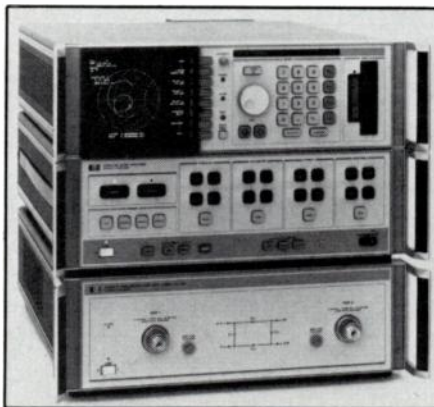Hewlett-Packard Company's new HP 8510 network analyzer system brings to the microwave-design engineer what HP officials believe are truly profound microwave-measurement capabilities. Foremost among these are:



- Error-corrected measurement of vector transmission and reflection parameters in real time, permitting real-time operator adjustments on the test device.

- Measurement accuracies that are 10 to 100 times more precise than previously attainable with commercially available instrumentation.

- 45-MHz to 26.5-GHz vector testing in a single setup with no change of connections.

- Optional transformation (using fast-Fourier-transform techniques) of error-corrected data between frequency and time domains at speeds permitting real-time adjustments.

The HP 8510 system can measure forward and reverse transmission and reflection characteristics (i.e., a network's scattering parameters) — measurements that have been vector-error corrected for systematic errors at 401 frequency points — in less than one second.

HP engineers believe that the HP 8510 system is the first commercial instrument able to measure magnitude and phase of transmission and reflection characteristics from 45 MHz to 26.5 GHz with a single test set. Furthermore, the measurement accuracies and resolution are believed to be 10 to 100 times better than is currently achievable in commercial practice.

List prices and current delivery estimates for the units comprising the new analyzer system are:

8510A, Network analyzer Option

010: Time-domain capability, \$33,500 add \$9,500, 12 weeks ARO; 8511A Frequency converter (45 MHz to 26.5 GHz), \$17,300, 20 weeks ARO; 8512A Reflection/transmission test set (500 MHz to 18 GHz), \$17,300, 12 weeks ARO; 8513A, Reflection/transmission test set (45 MHz to 26.5 GHz), \$25,000, 20 weeks ARO; 8514A, S-parameter test set (500 MHz to 18 GHz), \$28,000, 12 weeks ARO; and 8515A, S-parameter test set (45 MHz to 26.5 GHz), \$37,200, 20 weeks ARO.

Hewlett-Packard Company, Palo Alto, CA 94304, Info/Card #110.

Spectrum Analyzer

As a leading supplier of portable and rugged spectrum analyzers, Tektronix, Inc. is adding a new set of "twins" to its 490 Series spectrum analyzer family. The two major new products — the 494 and its programmable compatible counterpart, the 494P — offer many features never before available in a spectrum analyzer. The new spectrum analyzers cover the frequency range from 10 KHz to 325 GHz and offer an exclusive "HELP" mode which provides explanations of controls and functions, on the CRT itself, at the push of a button. Fitting a competitive niche in the marketplace, the 494 and 494P will sell for \$40,950 and \$45,950 respectively. Delivery at introduction is eight weeks after receipt of customer orders. **Tektronix, Inc., Beaverton, OR 97077, Info/Card #109.**

L/C Meter

The Model 522 digital L/C meter and test fixture combination is being offered by Cambridge Technology, Inc at a new low price. This instrument combination allows measurement and sorting of inductances and capacitances at a basic accuracy of 0.25%, with dual measurement frequencies, and 0 to 10 VDC internal capacitor bias, for less than \$1000; and industry first. A built-in comparator allows simultaneous sorting for high and low tolerances, and dissipation limits. Measurement frequencies of 120 Hz or 1 KHz are automatically selected. The instrument is autoranging and a range-hold feature permits fast repetitive measurements. The electrical contacts of the test fixture provide four terminal measurement capability. A push button allows both electrical contacts to be held open simultaneously so that components with very fine leads can be inserted conveniently. A second

Global security depends on every component.



Medium Power Class A * > 200 Milliwatts
PA2/PA3/PA3.1/PA5/PA6/PA7/PA10/PA10.1/PA12/PA12.1/PA15/PA37 Series

Low Noise * High Dynamic Range * High Efficiency
A70 A70.1 A70.2 A70.3 Series

High Efficiency * Transformer Coupled
A81/A81.1/A81.2/A81.1/A86 Series

High Gain * Two Stages * Full Performance
A73A/A74.1/A76/A84/A85/A85.1/A87

High Output Level * Low Intermod Series
A78/A79/A80/A81/A82/A83/A84/A85/A86/A87/A88/A89/A90/A91/A92/A93/A94/A95/A96/A97/A98/A99/A100 Series

Low Noise * High Efficiency * High Reverse Isolation
A81/A81.1/A81.2/A81.3/A82/A82.1 Series

Watkins-Johnson Cascadable Amplifiers

Watkins-Johnson has the optimum cascadable amplifier for your application. W-J cascadable amplifiers are designed for maximum performance and manufactured to the highest standards of quality.

W-J's extensive product line provides the utmost in system design flexibility. The amplifiers are grouped by families where there is commonality of design to ease the selection process.

Choose Watkins-Johnson, where top performance and quality leadership are the norm — not the exception.



The reliability goes in before the component goes out.



WATKINS-JOHNSON

Watkins-Johnson—U.S.A.: • California, San Jose (408) 262-1411; El Segundo (213) 640-1980 • Florida, Fort Walton Beach (904) 863-4191 • Georgia, Atlanta (404) 458-9907 • Illinois, Palatine (312) 991-0291 • Maryland, Gaithersburg (301) 948-7550 • Massachusetts, Lexington (617) 861-1580 • Texas, Dallas (214) 234-5386 • United Kingdom: Dedworth Rd., Oakley Green, Windsor, Berkshire SL4 4LH • Tel: (07535) 69241 • Cable: WJUKW-WINDSOR • Telex: 847578 • Germany, Federal Republic of: Kefelroher Strasse 90, 8000 Muenchen 40 • Tel: (089) 35 23 46 • Cable: WJDBM-MUENCHEN • Telex: 509401; Deutschherrenstrasse 46, 5300 Bonn 2 • Tel: (228) 33 20 91 • Telex: (886) 9522 • Cable: WJBN BONN • Italy: Piazza G. Marconi 25, 00144 Roma-EUR • Tel: 592 45 54 or 591 25 15 • Cable: WJ ROM I • Telex: 612278

HIGH POWER EPSCO



SOLID STATE POWER AMPLIFIERS

EPSCO'S family of GaAs FET power amplifiers features low distortion and high efficiency for telecommunications and other applications.

Computer-aided design flexibility and modular construction provide quick turnaround and a broad range of customer-specified characteristics, including these available options:

- Gain
- Output power to 10 watts
- Wide operating temperature range
- Output monitor
- Custom packaging if required
- Broad supply voltage range

TO MEET YOUR SPECS

For more information and discussion of your high power amplifier needs, give us a call today.



411 Providence Highway
Westwood, MA 02090
(617) 329-1500.
TWX: (710) 348-0484.
INFO/CARD 60



push button allows each set of contacts to be individually opened for components with flying leads such as coils or transformers. Other features include rugged all-metal enclosure, tilt stand, and lead capacitance null. The instrument is protected against damage from charged capacitors and comes with a one year warranty on materials and workmanship. A full refund within 30 days is available if the instrument is found unsatisfactory for any reason. The Model 522 is available from stock to 4 weeks and is priced at \$875. **Cambridge Technology, Inc., Cambridge, MA 02140, Info/Card #107.**

Magnetic Field Strength Meter

Holaday Industries' new Isotropic Broadband Magnetic Field Strength Meter, Model HI-3006, measures magnetic fields from 300 KHz to 300 MHz.

Our standard magnetic field probe covers the range from 5 MHz to 300 MHz and our new low frequency magnetic field probe covers the range from 300 KHz to 10 MHz. With this instrument, one can easily make accurate measurements of potentially hazardous fields in the vicinity of RF induction heaters, as well as near RF heat sealers, broadcast antennas, and other industrial and communications RF sources. The HI-3006 has all the features of the HI-3000 series including fully automatic zero adjust, audio output and peak reading memory. The HI-3006 comes complete with both probes, batteries and instruction manual in an attractive and protective carrying case. It is an ideal companion to the HI-3001 which, when configured with the optional high-sensitivity probe, can measure electric fields from 0.3 V/M to well over 3000 V/M. **Holaday Industries, Inc., Eden Prairie, MN 55344, Info/Card #106.**

Frequency Synthesizer

With the introduction of two new synthesizers, PTS has created the most complete selection of cost-effective direct synthesizers. The PTS 500 now in production delivers low phase-noise and 0.1 Hz resolution at \$7,300 while the PTS 040 has even

Bliley



Frequency control.
We can fine tune
it for virtuoso
performance
and critical
reliability in your circuit.

Why fiddle around with anything less?

Quartz Crystals • Crystal Oscillators • Free Catalog

We're The First Name In Frequency Control

BLILEY ELECTRIC COMPANY

2545 West Grandview Blvd.
P.O. Box 3428 Erie, PA 16508
(814) 838-3571 TWX 510-696-6886


INFO/CARD 61

PRECISION. PROTECTION. CALIBRATION. SUPERIOR CONSTRUCTION.

INSTRUMENTS FOR INDUSTRY

State-of-the-Art E-Field Testing and Monitoring. Radiation Hazard Monitors, TEM Cells and E-Field Sensors. All from IFI.

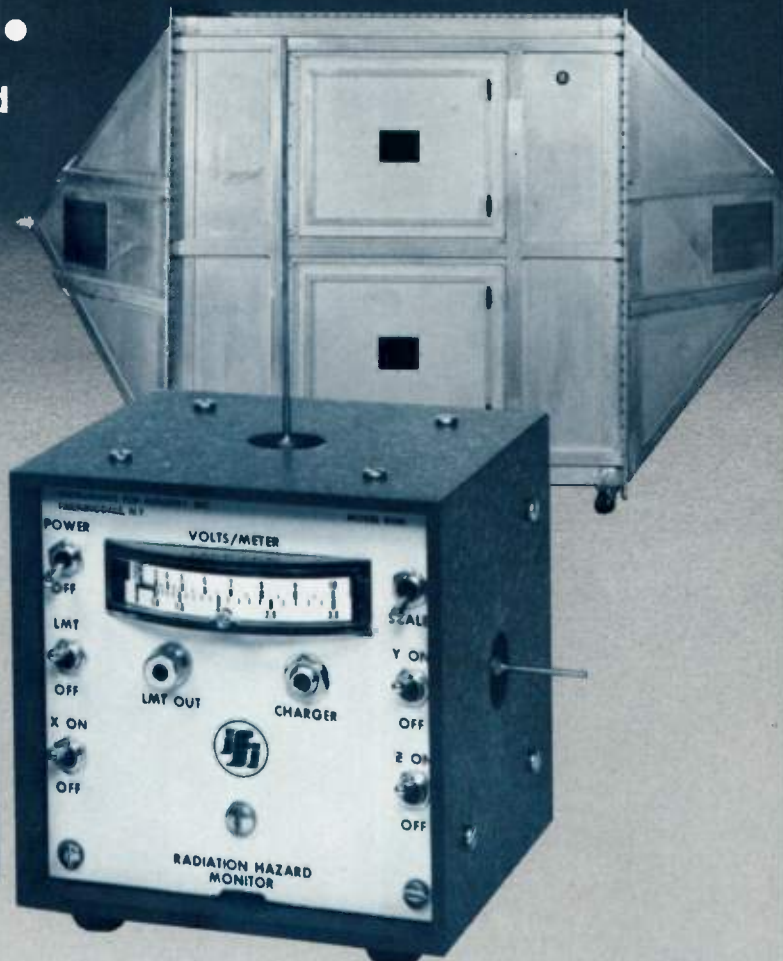The EFS and FHM series of E-Field Sensors provide direct readout in the near and far field for accurate measurements, both in and out of the laboratory environment. IFI TEM Cells, when used for RF susceptibility testing, permit safe generation of extremely high E-Field levels with a moderate amount of RF power.



RADIATION HAZARD MONITORS

E-FIELD SENSORS

TEM CELLS

FEATURES

APPLICATIONS

- No tuning or bandswitching
- Broadband coverage
- Negligible Field Distortion
- Direct reading between 1-300 volts per meter
- Isotropic response
- Individual vector selection

For measurement of strong electric fields in the VLF through VHF regions of the spectrum. An optional dielectric handle will permit it to be used as a probing device for sources of radiation.

- No tuning or bandswitching
- Compact, battery operated
- System compatible
- No calibration curves or tables
- Five meter ranges for easy reading
- Fiber optic remote readout available

Ideal for radiated susceptibility testing. A versatile, cost-effective instrument, the EFS-1 monitors electromagnetic environments, measures field strength, and more.

- Available in 10 different size models
- Rugged, commercial construction
- Easy access of cables and connections to test sample
- Side door allows for safe product insertion

Suitable for various test applications ranging from dc to 1 GHz, IFI has produced the first commercial TEM Cell for lab and RF susceptibility testing. The IFI TEM Cell offers an efficient means of accurate and broadband E-Field testing.



Instruments for Industry, Inc.


151 Toledo St., Farmingdale, N.Y. 11735 (516) 694-1414

"Depend on IFI"

INFO/CARD 62

flat pack mixers

(+7 dBm LO)

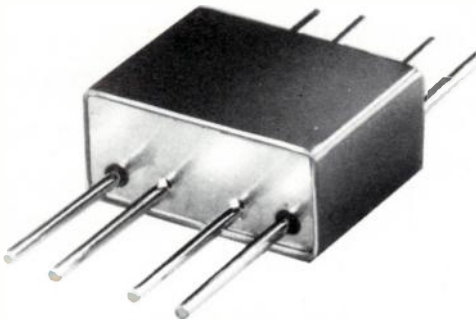

5 to 1000 MHz
only \$14⁹⁵ (6-24)

IN STOCK...IMMEDIATE DELIVERY

- pin-for-pin replacement of competitive models
- **MIL-M-28837/1A performance***
- extra-rugged construction
- hermetically-sealed
- every unit thermal shock tested, 5 cycles, -54°C to +100°C
- low conversion loss, 6.2dB
- hi isolation, 40dB
- 1 year guarantee

*units are not QPL listed

LMX-113 SPECIFICATIONS

FREQUENCY RANGE, (MHz)
LO, RF 5-1000
IF DC-1000

CONVERSION LOSS, dB	TYP.	MAX.
one octave from band edge	6.2	7.0
total range	7.0	8.0

ISOLATION, dB	TYP.	MIN.
5-50 MHz LO-RF	50	45
LO-IF	45	40

50-500 MHz LO-RF	40	30
LO-IF	35	25

500-1000 MHz LO-RF	30	20
LO-IF	25	17

SIGNAL 1dB Compression Level 0dBm min

finding new ways...
setting higher standards

Mini-Circuits

A Division of Scientific Components Corporation
World's largest manufacturer of Double Balanced Mixers
2625 E. 14th St. B'klyn, N.Y. 11235 (212) 769-0200

INFO/CARD 63 C91-3 REV. ORIG.




lower noise and equal resolution at \$4,400. It addresses the ATE, Laboratory, and communications markets. Features common to all models of the line are: 200u sec switching, remote-only (OEM) models, choice of resolution, choice of integral interface BCD or GPIB. **Programmed Test Sources**, Littleton, MA 01460, Info/Card #105.

FFT Analyzer

Wavetek Rockland Scientific, Inc., has announced the introduction of their Model 5810A real-time spectrum analyzer, which incorporates extensive built-in data reduction to simplify the solution of typical measurement problems in vibration, acoustics, and electronics. The 400 line single channel analyzer also processes and displays new data at a high rate of 17 spectra per second, even while averaging as

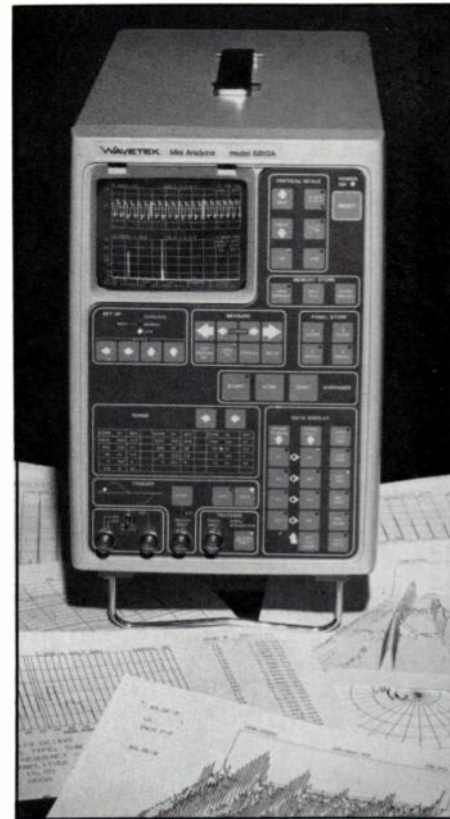
many as five spectra simultaneously (4 zoom and on baseband). Using a real time bandwidth of 7.2 KHz, the Model 5810A covers frequencies from 0.0025



AEP THE FIELD REPLACEABLE CONNECTION FOR HERMETICALLY SEALED MIC'S

- 16 quality models for sealed, modular MIC use.
- In 2 or 4 hole mounts • Any quantity, any size run.
- Accepts leads from .011 to .021". • Designs available for special bead sizes.
- Freq Range: DC to 18GHz/18 to 24GHz. • VSWR (Max): 1.05 + .005 fGHz/1.05 + .010fGHz. • Insertion Loss (Max): .03dB x \sqrt{fGHz} .
- Captivation (Center): 6lb. min. Axial force.

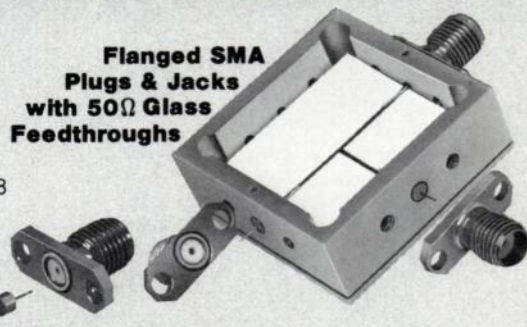**Flanged SMA
Plugs & Jacks
with 50Ω Glass
Feedthroughs**



Write for details and specs.



APPLIED ENGINEERING PRODUCTS

1475 Whalley Ave., P.O. Box A-D, Amity Station, New Haven, CT 06525
(203) 387-5282 TWX 710 465 1173

INFO/CARD 89

Hz to 100,000 Hz. A built-in non volatile memory can store 200 spectra together with all information for later reconstruction of test conditions, including set-up, calibration, date, and time. Automatic storage at preset time intervals allows unattended logging of long term events such as drift or machine coastdown, or of short term data collection for stack ("waterfall") plots. Built-in data reduction routines permit data analysis in any of 11 different formats. These include stack plots of spectra at time or RPM increments, plots with the highest peak amplitudes and frequencies listed, time histories of four selected frequencies or orders of machine rotation, polar plots of phase vs. amplitude for balancing, and optional 1/2 octave and full octave conversions of live and stored narrow band spectra. Portable with on-line data storage, the Model 5810A is designed for use on-site. It also provides high sensitivity and wide coverage for laboratory testing. Simple set up, using any of 3 stored panels and 12 stored measurement cursor positions, insures repeatability in production or other high volume usage. In addition, the Model 5810A is GPIB compatible for fully automatic data collection and testing. Computational capabilities of the analyzer include single or double integration in time or frequency do-

main, PDS calculation, RMS overall or in spectrum regions, and consistent calibration in English or Metric units. Price of the Model 5810A is \$12,400. Delivery is within 60 days after receipt of order. **Wavetek Rockland Scientific, Inc., Rockleigh, NJ 07647, Info/Card #103.**


Waveform/Vector Monitor Combination With SCH Capability

A rackmountable, single unit waveform/vector monitor combination from Tektronix, Inc., is now available for use by television personnel in all NTSC and PAL system countries. Similar in appearance and identical in mechanical configuration to the recently introduced 1740 Series, the new 1750 Series Waveform/Vector Monitor instruments offer a unique SCH phase (subcarrier to horizontal sync) monitoring and measurement capability, and full function vertical interval line



tiny power splitters

2 way 0°

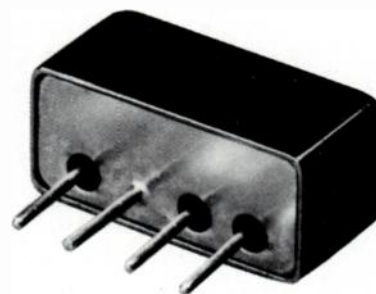

1 to 400 MHz
only \$13⁹⁵ (5-24)

IN STOCK...IMMEDIATE DELIVERY

- tiny...only 0.23 x 0.5 x 0.25 in.
- **can be mounted upright or as a flatpack**
- low insertion loss, 0.8dB (typ.)
- hi isolation, 25dB (typ.)
- hermetically-sealed
- excellent phase/amplitude balance
- 1 year guarantee

TSC-2-1 SPECIFICATIONS

FREQUENCY (MHz) 1-400	
INSERTION LOSS, dB (above 3 dB)	TYP.
1-10 MHz	0.25
10-200 MHz	0.4
200-400 MHz	0.8
ISOLATION, dB	25
AMPLITUDE UNBAL.	0.2
PHASE UNBAL.	2°
IMPEDANCE	50 ohms

finding new ways...
setting higher standards


Mini-Circuits

A Division of Scientific Components Corporation
World's largest manufacturer of Double Balanced Mixers
2625 E. 14th St. B'klyn, N.Y. 11235 (212) 769-0200

INFO/CARD 66

81A

3 SHORT WAYS to simplify design

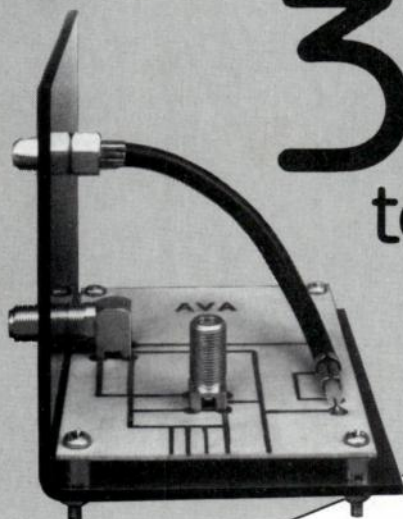

Ava provides a variety of "F" connectors for OEM chassis or printed circuit applications. You can select any connector configuration which fits the space limitations of your PC board and chassis design. Ease of installation reduces your assembly costs. Direct interface between PC board and chassis lowers RF loss and VSWR. Our "F" connectors are engineered to meet today's stringent demands limiting RFI under new FCC regulations. Ava connectors are available in all the most wanted standards and our custom designs are as unlimited as your imagination. Take the shortest distance to a good connection. Contact Ava today.



Ava Electronics Corp.

4000 Bridge Street, Drexel Hill, PA 19026 (215) 284-2500

A-101

INFO/CARD 65

HIGH POWER EPSCO



250W CW SIGNAL SOURCE

The EP250C is a versatile, self-contained, CW generator. One of many EPSCO high power signal sources, both CW (as high as 500W) and pulsed (as high as 100KW). For years, these quality instruments have been performing reliably in such applications as Metrology, EMC, Medical Research, Plasma Research, Component Testing, and Simulation.

The EP250C features:

- 50-2000 MHz tuning range
- Solid State mainframe
- Wide range power adjustment
- Digital readout forward and reflected power
- Plug-in RF heads
- Frequency stability
- Remote control option

TO MEET YOUR SPECS

For more information and discussion of your high power amplifier needs, give us a call today.



411 Providence Highway
Westwood, MA 02090
(617) 329-1500.
TWX: (710) 348-0484.
INFO/CARD 67

and field selection capabilities. The new 1750 (NTSC), 1751 (PAL), and 1752 (PAL-M) Series is intended to extend and complement the line of television products offered by Tektronix. This new instrument provides unique SCH display capability, line and field select with LED readout, and the features of both the widely used 528A Waveform Monitor and 1420 Vectorscope Series. It requires the space of only one of the earlier units (5.25 inch, half rack) and costs just slightly more than a 528A/1420 combination. The 1750 (NTSC) and 1751 (PAL) will each cost about \$5,600. The 1752 (PAL-M) will cost about \$6,160. The 1750 Series can be serviced at designated Tektronix facilities in the U.S.; and the company's service centers in Canada, Mexico, Japan, and Europe. Product availability is six weeks after the 1750's first public showing at the National Association of Broadcasters (NAB) 62nd Annual Convention and International Exposition, April 29-May 2, in Las Vegas, Nevada. **Tektronix, Inc., Beaverton, OR 97077, Info/Card #102.**

Hybrid Amplifier Module For Cellular Radio

A new series of three-stage common emitter hybrid amplifiers modules, designed and fully characterized for


800 MHz cellular mobile radio applications, has been introduced by Motorola. The new series (MHW808A1, MHW808A2 and MHW808A3) has a typical power output of 7.5 watts and a typical power gain up to 25 dB. Its class A input stage allows automatic gain control over 35 dB in output power range. The automatic gain control capability is necessary for cellular operation. The series employs three gain stages with transistors connected in a common-emitter configuration. The devices are specified at 12.5 volt, UHF characteristics. Included in the series are the following devices: MHW808A1, 806-870 MHz, 25 dB 7.5 W, \$68.20; MHW808A2, 806-890 MHz, 25 dB, 7.5 W, \$74.80; and MHW808A3, 870-960 MHz, 23.2 dB, 7.5 W, \$79.20. Availability is approximately 12 weeks from the factory and through authorized Motorola distributors. **Motorola Semiconductor Products Inc., Phoenix, AZ 85036, Info/Card #101.**

Air Variable Capacitors

Trim-Tronics, Inc., has introduced a line of air variable capacitors designed with a self resonant frequency greater than 5 GHz. The new multi-turn concentric ring capacitors complement Trim-Tronics tubular capacitor and air plate trimmer lines. They are suitable

AMPLIFIERS, 5MHz-1GHz

- MIL-STD-883B Screening

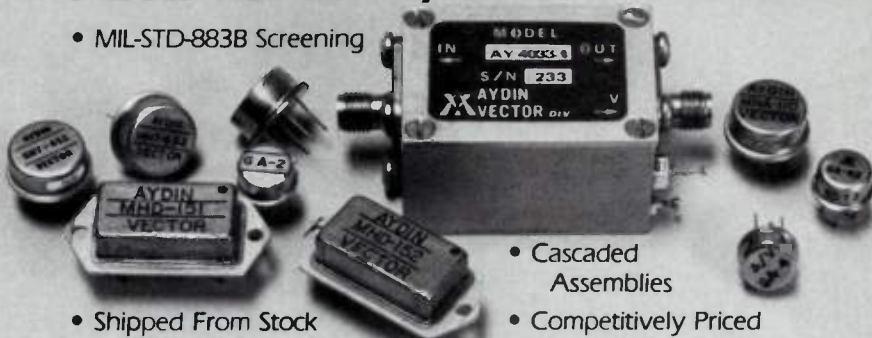

- Shipped From Stock

- Cascaded Assemblies

- Competitively Priced

Series	Freq Range (MHz)	Typ. Gain (dB)	Noise Figure Range (dBm)	Power Output Range (dBm)	VSWR		Input Power		Package Style
					In	Out	Vdc	I _{ma}	
GA Single-Stage	kHz-400	13	4.5-6.0	5-15	2.0	2.0	+15 typ.	17-70 (range)	TO-12
MHT Single-or Multi-Stage	5-1000	14	2.5-7.0	-2 to +23	2.0	2.0	+15 typ.	10-105 (range)	TO-8
GHT Single-or Multi-Stage	5-400	13	4.0-7.0	5-15	2.0	2.0	+15 typ.	17-70 (range)	TO-8
MHD Multi-Stage	1-500	21	2.5-6.5	5-20	1.6 (typ.)	1.6 (typ.)	+15 typ.	50-115 (range)	4-pin DIP


Aydin Vector

P.O. Box 328, Newtown, PA 18940 • TEL 215-968-4271 TWX 510-667-2320

INFO/CARD 68

AVX Single-Layer Ceramic Capacitor Chip

A new single-layer ceramic and porcelain capacitor chip uniquely suited for stripline width matching in microwave integrated circuitry is now available from AVX. This new SLC is designed specifically for low-noise amplifiers, GaAs FET amplifiers, voltage-controlled oscillators, and other EW/ECM components. The new capacitor chip, called Pathguard™, employs sputtered electrodes with pure gold metallization and a leach-proof intermediate layer. The dielectric is fine-grained high-density ceramic with NPO, P090, X7R, or X7V temperature characteristics. Six different chip sizes are available depending on the capacitance required. The smallest chip measures nominally 0.015" x 0.015" x 0.006"; the largest measure nominally 0.090" x 0.090" x 0.010". These dimensions are precisely controlled for high repeatability. The capacitance range of the chips is from 0.5 pF to 2700 pF, with tolerances of ± 0.1 pF to ± 20 percent. Working voltage rating is at least 50 Vdc. Mechanical and environmental specifications are in accordance with applicable Mil Standards (883B and 202). Price of the chips ranges from \$0.50 to \$2.00 each in 1000-unit quantities. Delivery time is from stock to eight weeks. **AVX Corp., Myrtle Beach, SC 29577, Info/Card #99.**

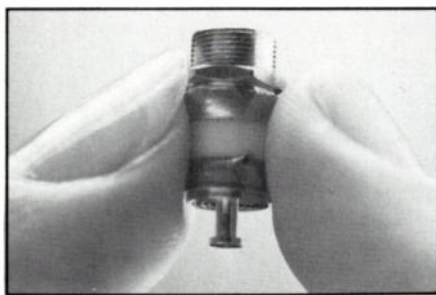

for sensitive telecommunications applications such as satellite, microwave, two-way radio and test instrumentation, where very precise tolerances are required. Typical functions include RF amplifiers, oscillators, crystal trimming, coupling, impedance matching and filter tuning. A unique component design produces a high Q-factor (greater than 5000 at 200 MHz), allowing the capacitor to operate at microwave frequencies. The capacitor's vertical slotted rotor mechanism results in complete surface area contact, producing uniform torque and contact resistance less than 1 milliohm. Available in several mounting styles, the Trim-Tronics air variable capacitor has a temperature coefficient of 0 ± 15 ppm over a temperature range from -55 to +125 degrees C. it is rated to 250 V DC. **Trim-Tronics, Inc., Cazenovia, NY 13035, Info/Card #100.**



1000 MHz PULSE GENERATOR

PRINCIPLE FEATURES OF THE PG 1000A PULSE GENERATOR:
 High-speed ECL/TTL Pulse Generator
 Risettime: 200 ps ECL, 750 ps TTL
 Transition times (20-80%):
 150 ps for ECL, 500 ps for TTL
 Frequency range: 1 MHz to 1000 MHz
 ECL (350 MHz TTL), extendible to dc in EXT MODE. Frequency indicated by 4½ digit LED display.
 Low transient aberration.
 Time-domain Reflectometry through separate DRIVER AMPLIFIER.
 Precision duty cycle control.
 Min. pulse width: 500ps ECL, 2 ns TTL.
 Short pulse width also producible independent of frequency.
 Variable rise/fall time possible.
 All outputs are truly differential and are available simultaneously.
 250 ps GATE on/off capability.
 Output amplitude and offset can be set independently for ECL.
 Price: \$4950



HIGH-SPEED PULSE DRIVERS

The high-speed driver amplifiers of the PG 1000A 1000 MHz Pulse Generator are available as separate modules. These modules exhibit features and performance rather similar as stated above. Additionally, the outputs are available as voltage or currents or both. Output amplitude and offset are programmable.

Four models are available: 1 V (40 mA) per side at \$795; 2 V (80 mA) per side at \$995; 5 V per side at \$1250; TDR unit (40 mA) with reverse termination brought out at \$950.

We now offer leasing on all of our equipment.

For further details please call or write:

Colby Instruments, Inc.
 P.O. Box 84379
 Los Angeles, CA 90073-0379
 Phone: (213) 450-0261

Also available with TNC connectors.



Model 4410 Mini-Specs:

Power & Frequency Range: 1/3/10/30/100/300/1000 watts or 10/30/100/400/1000/3000/10,000 watts, in frequency bands from 0.200 to 1000 MHz, CW or FM signals. Accuracy $\pm 5\%$ OF READING from 200 milliwatts up (2-1000 MHz) over a compensated temperature range of 0°C-50°C. Price \$495.


7-in-1 Elements \$125 to \$175.

Ask for Bulletin No. 4410-83

BIRD
 Electronic Corporation

30303 Aurora Rd., Cleveland (Solon), Ohio 44139
 216 • 248-1200 TLX: 98-5298 Cable: BIRDELEC

11.5dB directional couplers

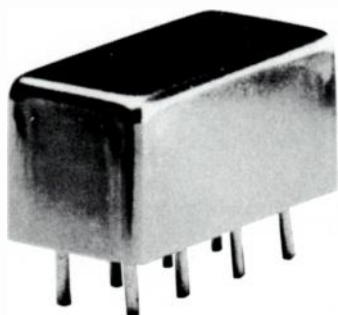

**0.5 to 500 MHz
only \$11⁹⁵ (5-49)**

IN STOCK... IMMEDIATE DELIVERY

• MIL-C-15370/18-002 performance*

- low insertion loss, 0.85dB
- high directivity, 25dB
- flat coupling, ± 0.5 dB
- miniature, 0.4 x 0.8 x 0.4 in.
- hermetically-sealed
- 1 year guarantee

*Units are not QPL listed

PDC 10-1 SPECIFICATIONS

FREQUENCY (MHz) 0.5-500
COUPLING, dB 11.5

INSERTION LOSS, dB	TYP.	MAX.
one octave band edge	0.65	1.0
total range	0.85	1.3

DIRECTIVITY, dB	TYP.	MIN.
low range	32	25
mid range	32	25
upper range	22	15

IMPEDANCE 50 ohms.

For complete specifications and performance curves refer to the Microwaves Product Data Director, the Goldbook, EEM, or Mini-Circuits catalog

finding new ways...
setting higher standards

Mini-Circuits


A Division of Scientific Components Corporation
World's largest manufacturer of Double Balanced Mixers
2625 E. 14th St. B'klyn, N.Y. 11235 (212) 769-0200

INFO/CARD 71

C 79-3 REV. B

Minature Chip Attenuators

New miniature thin film chip attenuators from EMC Technology, Inc., are designed for high density circuit applications which also require stable, predictable performance. Model TS0500 chip attenuators are available in 1 to 20 dB values, with 3, 6 and 10 dB as standard, and for the frequency range from DC to 18 GHz. Attenuation accuracy is $\pm .25$ dB. Measuring only .075" x .060" with .025" terminals, the new automatically trimmed attenuators require one-fourth the space used by similar attenuators. As a result, they are suitable for hybrid cir-

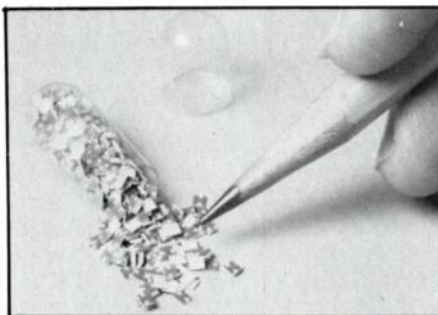

cuits of all kinds where packaging density of add-on devices as well as improved high frequency performance are important considerations. Attenuators may be solder mounted by all

commonly used methods. EMC's new chip attenuators meet or exceed all applicable requirements of MIL-E-5400 and MIL-R-55342, and are fully RF tested through the X-band. For enhanced electrical performance, VSWR is 1.25 from DC through 4 GHz, 1.35 from 4-8 GHz, and 1.50 up to 18 GHz. Power dissipation is .1 watt, and impedance is 50 ohms. Attenuators operate from -55° to 150°C. Prices of the new Model TS0500 attenuators are based upon quantity and bandwidth desired; delivery is stock to 4 weeks A.R.O. **EMC Technology, Inc., Cherry Hill, NJ 08034, Info/Card #98.**

Crystal Oscillator

Piezo Systems has developed a crystal oscillator with improved SSB phase noise characteristics. The P/N 1830025 offered in the range of 50 to 110 MHz will provide SSB phase noise levels of -120 dbc/Hz at 100 Hz, -150 dbc/Hz at 1 kHz and -158 dbc/Hz at 10 kHz and beyond from the carrier, with a typical noise floor of -165 dbc/Hz (100 MHz measurements) the output power is 0 dbm into 50 ohms. (higher power available). The frequency stability is ± 10 ppm over an operating temperature range of 0°C to +55°C. A volume of 3.3 cubic inches makes it attractive for compact systems where



Johnson delivers variable capacitors when you want them.

Air variable, tubular, ceramic or teflon dielectric, no matter what variable capacitor type you need, Johnson can meet your specifications—for both design and delivery.

Our engineering and manufacturing staffs produce innovative, cost-effective products. Our national network of 200

distributors helps with your prototypes.

Write for your free catalog or call 1-507-835-6307. Telex: 290470. TWX: 910-565-2161.



JOHNSON
Components Division

E. F. JOHNSON COMPANY, WASECA, MINN. 56093

INFO/CARD 72

March/April



low phase noise is desired, such as synthesizers. The input voltage is +15 VDC (others available). **Piezo Systems, Carlisle, PA 17013, Info/Card #96.**

20 GHz GaAs FET

Harris Microwave Semiconductor, a subsidiary of Harris Corporation, has announced the product release of its newest Gallium Arsenide Field Effect Transistor (GaAs FET), the HMf-0310. The HMf-0310 addresses the needs of broadband and narrow-band amplifier manufacturers for a high yield gain stage device which offers high gain and wide dynamic range at a reasonable cost. An extremely versatile GaAs


FET, the HMf-0310 provides 15 dB gain at 8GHz, 8 dB at 18 GHz. Power bias and tuning conditions produces a typical linear power level of 100 mW (20 dBm) at 18 GHz. Low noise matching conditions typically result in a 1.2 dB Noise Figure at 8 GHz. Priced at \$16.25 (US) each at 1000 pieces and designed for consistent performance and high yield through assembly, the HMf-0310 represents a cost-effective solution to a wide array of high frequency, high gain amplifier requirements. **Harris Microwave Semiconductor, Milpitas, CA 95035, Info/Card #95.**

Passive Delay Line

A new economy series of 14 pin DIP (Dual Inline Package) passive delay lines manufactured by Automatic Coil Corp. are compatible with various logic systems including TTL and video. These 180 standardized units, identified as the CD300 Series, have extensive applications in telecommunication, computer and instrumentation areas. These units are produced at the firms off-shore Caribbean facilities to ensure extremely competitive pricing. They feature reliable hybrid construction and precise, stable delays in accordance with the specification of MIL-D-23859. Operating temperatures range from -55° to +125°C. Mounted dimensions of the units

power splitter/ combiners

4 way 0°

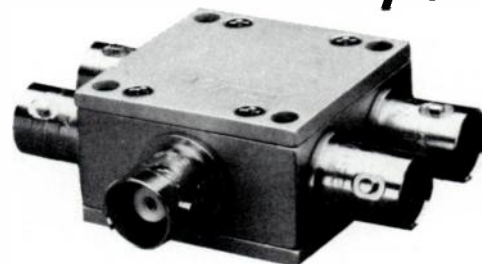

10 to 500 MHz
only \$74⁹⁵ (1-4)

AVAILABLE IN STOCK FOR
IMMEDIATE DELIVERY

- rugged 1 1/4 in. sq. case
- BNC, TNC, or SMA connectors
- low insertion loss, 0.6 dB
- hi isolation, 23 dB

ZFSC 4-1W SPECIFICATIONS

FREQUENCY (MHz) 10-500			
INSERTION LOSS, dB (above 6 dB) 10-500 MHz	TYP. 0.6	MAX. 1.5	
AMPLITUDE UNBAL., dB	0.1	0.2	
PHASE UNBAL. (degrees)	1.0	4.0	
ISOLATION, dB (adjacent ports)	TYP. 23	MIN. 20	
ISOLATION, dB (opposite ports)	23	20	
IMPEDANCE	50 ohms.		

For complete specifications and performance curves refer to the 1980-1981 Microwaves Product Data Directory, the Goldbook or EEM.

finding new ways...
setting higher standards

Mini-Circuits

A Division of Scientific Components Corporation
World's largest manufacturer of Double Balanced Mixers
2625 E. 14th St. B'klyn, N.Y. 11235 (212) 769-0200

83-3 REV. ORIG.

INFO/CARD 74

85A


Give us .24 Cubic Inch

And we'll take miles off your oscillator design problems... and put the crystal in the same package! International's new MTE oscillators are packaged in a standard 14 pin DIP for design convenience. A complete oscillator and our FM-1 crystal are included in a package measuring .630"x.5"x.86" excluding pins. Convenient top trimmer access hole. Frequencies from 7 MHz to 60 MHz are available now.

Specifications:

DC Input	+9V dc @ 10ma max.
RF Output	+5 DBm
Output Impedance	50 Ohms
Freq. Stability	.002 to .0002%*
Temp Range	-30°C to +60°C


*Depending on crystal supplied

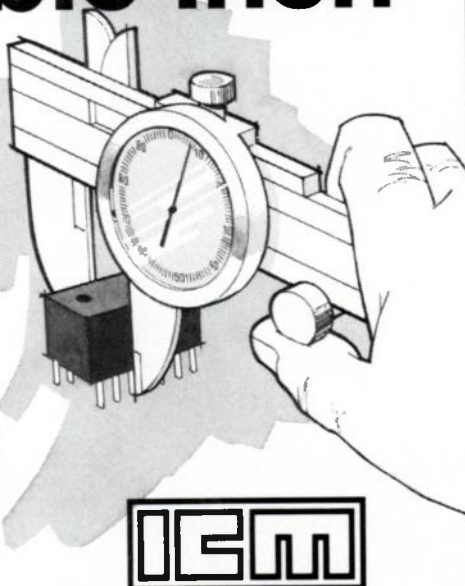

International Crystal Manufacturing Company, Inc.

10 N. Lee, P.O. Box 26330, Oklahoma City, OK 73126

measure .800" long by .300" wide by .300" high. The solder coated phosphor bronze leads are .15" long and are evenly spaced at a center distance of .100". They are offered with overall delays ranging from 5 to 300 NS and with rise times ranging from 2.5 to 60.0 NS. Three basic styles are offered. One without taps and two styles with 10 taps each in different configurations. All units are available with standard impedances of 50, 100 or 200 ohms. Total delay tolerances are ± 2 NS or 5% whichever is greater. Impedance tolerance is $\pm 10\%$ and the attenuation standards are 10%

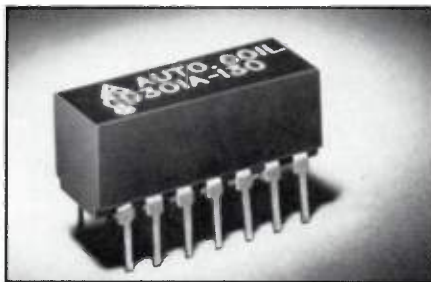


max. These units are also available to meet custom specifications which could include: intermediate delays, special taps or electrical parameters; tighter tolerances, lower profiles, inde-

pendent delay increments or internal terminations. **Automatic Coil Corp.**, Hialeah, FL 33010, Info/Card #93.

Matched Power GaAs FETS


A series of internally-matched power GaAs FETs for operation at C-band has been introduced by Raytheon Company's Special Microwave Devices Operation. The RIM series consists of four devices that deliver 3 watts power at 3.7-4.2 GHz, 5.9-6.4 GHz, 6.4-7.1 GHz or 7.1-7.8 GHz. Each device contains a single 10 mm periphery pellet mounted between double-section matching networks. A hermetically-sealed, metal-ceramic package is utilized.

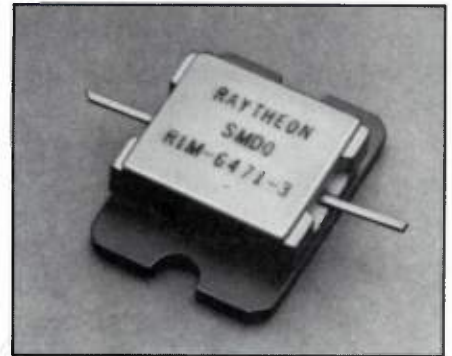

Raytheon's exclusive "via-hole" source connections makes possible low common-lead inductance. This results in highly-stable operation as well as virtual elimination of spurious oscillations. Other features include thinned chips with integral-plated heat sink for low thermal resistance, thick bonding pad metallization for bond strength, and dielectric passivation for environmental protection. RIM series internally-matched power GaAs FETs are priced at \$300 each (1-9 quantity). Deliveries are 2-4 weeks after receipt of order. **Raytheon Co.**, Northborough, MA 02254, Info/Card #92.

50-Watt Microwave Power Transistor

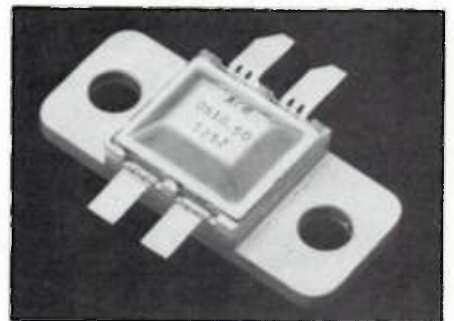Acrian, Inc., has announced a 50-watt microwave power transistor for broadband amplifiers for military and commercial markets. The new transistor, called the Acrian 0510-50, is a Class AB part capable of supplying 50 watts (28 volts) of instantaneous and continuous power broadband across



GET 10 TIMES MORE RFI PROTECTION WITH A LINDGREN "DEI" SCREEN ROOM


Lindgren's double-electrically-isolated (DEI) screen rooms offer 120 dB RF attenuation of electric and plane waves from 14 KHz to 1 GHz... up to 10 times more shielding than any other type of screen room.

This patented design keeps your design/test area interference-free despite rising ambient RFI levels. You get shielding equal to conventional solid-sheet-metal enclosures without sacrificing the see-through, hear-through and lighter-weight advantages of screen.

DEI design is superior because inner and outer screens of 0.011" dia. 22 x 22 bronze mesh are electrically separated, except for a single grounding point. Doors feature separate inside and outside RF seals on all four edges, with a single handle that assures an RF-tight closure by applying cam pressure at three points.

Built of panel modules, Lindgren RF enclosures can be moved, expanded or reshaped easily. Our patented overlapping pressure joints maintain full shielding integrity no matter how many times they're reassembled.

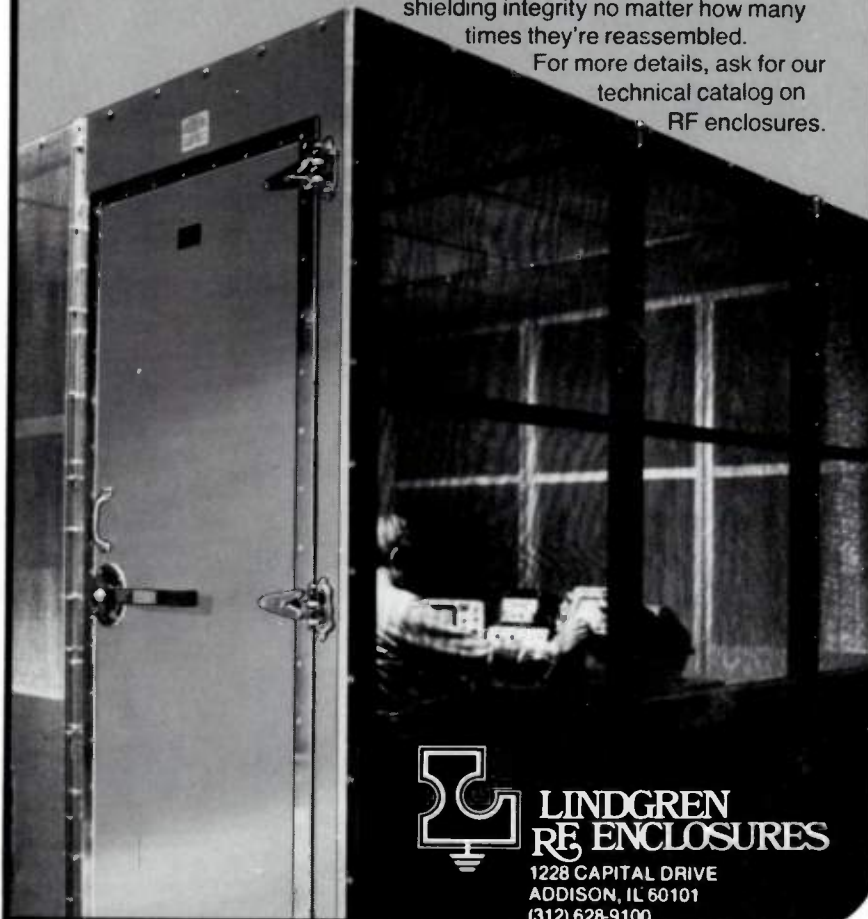For more details, ask for our technical catalog on RF enclosures.



**LINDGREN
RF ENCLOSURES**

1228 CAPITAL DRIVE
ADDISON, IL 60101
(312) 628-9100


the 500-1000 MHz frequency range. The 0510-50 has high efficiency and good linearity. The 0510-50 has 50 percent collector efficiency and can withstand 5:1 VSWR. Maximum power dissipation is 125 watts, rated at 25 degrees centigrade case temperature. The 0510-50 is currently in full production and available for immediate shipment, at a cost of \$210.80 in quantities of 1-99. **Acrian, Inc., Cupertino, CA 95014, Info/Card #141.**

VHF RF Amplifier

RF Gain, Ltd. introduces the RF6140V RF Power Amplifier in the 450-470 MHz band. With an input of 2-6 watts and output of 120-150 watts this 8 MHz spread amplifier features and anodized aluminum case heat sink. This makes the eighth model in their line of VHF amplifiers, including two repeater models. **RF Gain, Ltd, Rockville Centre, NY 11570, Info/Card #142.**

FA-2000 Filter Amplifier

HDS announces the availability of the FA-2000 Filter Amplifier. The FA-2000 is a dual channel, low-noise, wide dynamic range video amplifier for use with low impedance sources. Remote control of gain, low frequency cutoff, and high frequency cutoff are provided. Connections for first stage output and external offset trimming are also provided. A nickel-iron enclosure shields against electric and magnetic fields. Voltage gain control ranges

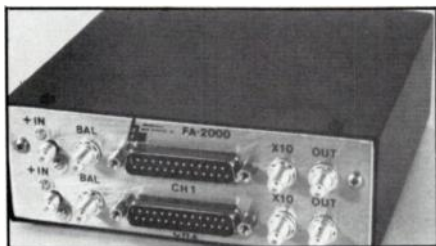

from 10 to 10K; high pass filter control ranges from DC to 1 kHz; and low pass filter control ranges from 0.3 to 300 kHz. Features include 6 dB noise figure, 100 μ V DC offset referenced to input, 50 μ A input bias current, and distortion less than 0.1%. The FA-2000 is packaged in a 5.5 x 5.5 x 2.0 inch nickel-iron enclosure. Signal input and output connections are SMA. Control input is via a DB-25 connector. The FA-2000C Controller/Power Supply is available for remote operation. Single channel, fixed gain, and differential input versions are available. Delivery: Stock to 90 days. **HDS, Inc., Reston, VA 22091, Info/Card #143.**

Broadband Power Amplifier

A new generation of RF Amplifier, designed to replace those bulkier,

less efficient and more costly the amplifiers. The new 3100LA is compact, lightweight (60 pounds) and capable of producing more power, over a wider frequency range than its predecessors. The 3100LA will operate from any ordinary single phase power receptable. The 3100LA will produce more than 100 Watts of linear Class A power and up to 180 watts of pulse and saturated CW power, with a useable operating range from 100 kHz to 180 MHz. The unit is unconditionally stable and will not oscillate for any condition of load and source impedance. Any signal generator, synthesizer or sweeper will supply adequate signal level to drive the 3100LA. The unit offers 55 dB of

gain and will amplify AM, FM, SSB, TV and Pulse as well as other complex modulation with minimum distortion. Output RF Voltage level as well as power output into 50 ohms is monitored by a front panel meter. Both the integral power supply and forced air cooling system are conservatively designed to permit operations over a wide range of temperatures and AC line conditions. **Electronic Navigation Industries, Inc., Rochester, NY 14623-2881, Info/Card #144.**

Microwave Power Source

Antennas, waveguides and electronic components can now be tested and evaluated under microwave power

Dedicated to Quality.

PROGRAMMABLE ATTENUATORS

50P-136
Single Supply Programmable
TTL Control Logic
20-400 MHz
0-127 dB in 1 dB steps
\$ 450.00 (1-9 qty.)

50P-076
Wideband Programmable
DC-1000 MHz
0-127 dB in 1 dB steps
\$ 360.00 (1-9 qty.)


50AP-002
Analog Programmable
10-500 MHz
0-30 DB Continuously Variable
\$ 90.00 (1-9 qty.)

50AP-008
PCB Mount
Analog Programmable
50-500 MHz
0-40 DB Continuously Variable
\$ 135.00 (1-9 qty.)

JFW Industries, Inc.
2719 E. Troy Avenue
Indianapolis, Indiana 46203
(317) 783-9875

low distortion mixers

hi level (+17 dBm LO)

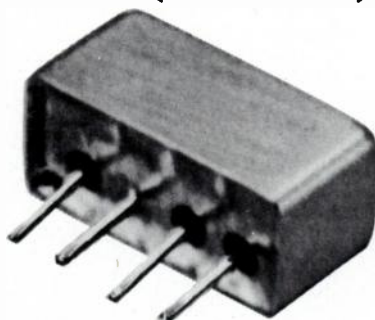

5 to 1000 MHz

only \$31⁹⁵ (5-24)

IN STOCK... IMMEDIATE DELIVERY

- micro-miniature, pc area only
0.5 x 0.23 inches
- RF input up to +14dBm
- guaranteed 2 tone, 3rd order
intermod 55 dB down
at each RF tone 0dBm
- flat-pack or plug-in mounting
- low conversion loss, 6.2dB
- hi isolation, 40 dB
- MIL-M-28837/1A performance*
- one year guarantee

*Units are not QPL listed

TFM-2H SPECIFICATIONS

FREQUENCY RANGE, (MHz)			
LO, RF	5-1000		
IF	DC-1000		
CONVERSION LOSS, dB			
One octave from band edge	TYP.	MAX.	
	6.2	7.0	
Total range	7.0	10.0	
ISOLATION, dB			
	TYP.	MIN.	
LO-RF	50	45	
LO-IF	45	40	
LO-RF	40	30	
LO-IF	35	25	
LO-RF	30	20	
LO-IF	25	17	

SIGNAL 1 dB Compression level +14 dBm min

finding new ways...
setting higher standards

Mini-Circuits

A Division of Scientific Components Corporation
World's largest manufacturer of Double Balanced Mixers
2625 E. 14th St. B'klyn, N.Y. 11235 (212) 769-0200

INFO/CARD 77

C82-3 REV. A

using Cober's new Model 4169 Power Generator. Employing commercially available klystrons, the Model 4169 will deliver 2 kW of continuous power and can also be used in a pulse mode with duty factors to 100%. Power output and frequency of the Model 4169 is determined by the klystron selected. Typical tubes provide 2 kW at a tunable frequency in S band (1.7 to 2.4 GHz), C band (4.4 to 5.0 GHz) and X band (10.0 to 12.4 GHz). The Model 4169 will power other klystrons requiring beam supplies up to 10 kV at 1.25 A and 10V/10A floated filament supplies. Connecting a conventional PIN diode RF modulator to the unit's input, enables pulse mode operation. Pulse widths are narrow as 50 ns or repetition frequencies to 10 MHz are achievable. Under typical test conditions, 10 ms pulse widths at 10 KHz produce 200 W of average power. The Model 4169 is available as a single or dual tube configuration. In the latter, two klystrons are included in the cabinet permitting operator selection of aperticular output of interest. A fully integrated and instrumented test console, the Model 4169 monitors key parameters with analog meters with overload relay protection. Safety interlocks are provided and equipment functions are displayed with clearly identified status lights. The Model 4169 is

priced at \$44,900 in the single tube configuration and \$49,500 as a dual tube model. Klystrons are selected and provided by the customer. Delivery is 6 months. **Cober Electronics, Inc., Stamford, CT 06904, Info/Card #87.**

Yagi Antennas

Childs Corp has introduced two new control station Yagi antennas that are heavy-duty and yet are low in cost. The 6 element 806 to 870 MHz Yagi and the 3 element 144-174 MHz Yagi feature a square boom for rugged accurate element alignment together with heavy-duty 3/8 inch and/or 1/2 inch elements. The 800-Yagi comes factory tuned and covers the entire 806-870 MHz frequency range with low VSWR. The Yagi-150 is field tuneable over the 144-174 MHz range for optimum low VSWR. All 3 models feature an extra large L-bracket mount that allows horizontal or vertical mounting to the tower, mast or wall mounting. The antennas are completely preassembled and tested at the factory for easy installation. **Childs Corp., Janesville, MN 56048, Info/Card #86.**

Dual Directional Coupler

Sage Laboratories, Inc., is now offering a compact, low-loss, dual directional coupler operating from 1-18 GHz.

HI-POWER RF

AMPLIFIERS, TRANSMITTERS, POWER GENERATORS

10-10,000 WATTS! — 2-500 MHz Frequency Range!

HENRY RADIO HAS THE PRODUCT YOU NEED.

(If we don't have it, we'll make it.)

APPLICATIONS:

NMR, Nuclear Magnetic Resonance
PLASMA Generation
MEDICAL Applications
NUCLEAR Magnetic Imaging
COMMUNICATIONS Applications



The new, dynamic

HENRY RADIO


2050 S. Bundy Drive, Los Angeles, CA 90025

TOLL FREE: 1-800-421-6631 • In California call (213) 820-1234



INFO/CARD 78

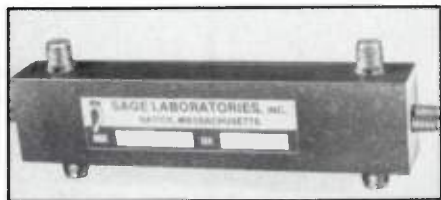Dimensions of this broadband coupler, model FC3428, are 3.70 x 8.50 x 0.6 inches. The unit has both a 10 dB coupler and a 15 dB coupler. Main-line insertion loss is 1.5 dB maximum, including coupling loss. Directivity is



15 dB minimum and the VSWR is 1.5/1 maximum. The coupler has a 1 dB roll off with frequency to compensate for system insertion loss-increase frequency. Delivery is 60 days. **Sage Laboratories, Inc., Natick, MA 01760, Info/Card #147.**

New Literature

Microwave Products Catalog

A new 44 page catalog covering attenuators and accessories for microwave applications has been published by Alan Industries, Inc. This edition updates electrical specifications for the company's programmable, cam actuated, rotary, manual switch and fixed attenuators as well as their ac-

cessories of loads, dividers, terminations, RF fuses and bridges. Among new attenuators in the catalog are a continuously variable series and additions to the programmable and manual switch series. New accessories include high frequency terminations and directional couplers. Product details are complete with photographs and line drawings. **Alan Industries, Columbus, IN 47202, Info/card #140.**

EMI/EMC Equipment Catalog

Tucker Electronics Company announces publication of a 52-page catalog featuring a full range of EMI and EMC equipment. This catalog, available now, contains descriptions and specifications on over 500 items. Included in the catalog are such items as: receivers — ELF, LF, VHF, microwave and surveillance; spectrum analyzers, antennas and probes, transient detectors and recorders, impulse and special purpose generators, power oscillators, signal sources, sweep generators, and power amplifiers. This equipment is manufactured by companies like Electro-Metrics, Singer-Stoddart, Empire, Collins, Honeywell, Hewlett-Packard and Tektronix. All equipment is expertly reconditioned and calibrated in Tucker's extensive lab facilities. A new feature of this

Sprague-Goodman. Nobody Offers a Broader Selection of Trimmer Capacitors.

When it comes to high-quality trimmer capacitors, nobody comes close to Sprague-Goodman.

We have the world's largest selection of models, styles and dielectrics: sub-miniature glass, quartz and sapphire Pistoncaps® plastic Filmtrims® or Ceramic single turn, Mica compression, Airtrim® air dielectric, multi-turn plastic and miniature LC tuners and Strab-L® metalized inductors.

So whether you

need standard or custom products, you can count on Sprague-Goodman. The first and last name in trimmer capacitors.

Sprague-Goodman Electronics, Inc.



(An affiliate of the Sprague Electric Company)

134 Fulton Avenue,
Garden City Park, NY 11040
516-746-1385
TLX 14-4533



THE MISSING LINK

If high rel crystals and filters are the weak links in your space, military, and commercial systems, you've been missing out on SCP.

Our ruggedized (Swept Quartz; high G's; shock; and h.f. vibration to 3000 Hz) problem solvers tough it out for you.

Monolithics, time delays, and matched filter sets (smallest in the industry) from 1-200 MHz. Quality and Inspection to MIL-I-45208.

When you need high rel and tight specs in small packages, call us.

We're the missing link you're looking for.

Never the weak one.



**Sokol
Crystal Products, Inc.**

Where the Impossible Becomes the Ordinary

121 Water St., Box 249, Mineral Point, WI 53565
Phone 608-987-3363, Telex 467581

catalog is the Technical Book Store. This section contains a full selection of handbooks on EMC/EMI technology, including the six-volume library from Donald R.J. White. Another section is devoted to items new to Tucker's inventory. These include amplifiers, analyzers, bridges, frequency measuring, meters, microwave, scopes and probes, phase/synchro/resolver, recorders, and sweep and signal generators. All of these items are also reconditioned and calibrated. All reconditioned and calibrated equipment purchased from Tucker Electronics carries a 90-day warranty on parts and labor. In addition

Tucker offers a 10-day return privilege, with full refund, if the buyer is not completely satisfied. **Tucker Electronics Co., Garland, TX 75046, Please circle Info/card #138.**

Communications Catalog Cross-Reference Guide

RF Gain releases new first edition communications catalog/cross-reference guide. This new catalog contains never before published cross-references. In addition to expanded cross-references for Motorola, G.E., Johnson, RCA/TACTEC, Quintron, Regency,

Wilson and Aerotron, and pricing at 20%-50% below the manufacturers dealer prices, the new catalog now includes cross-references for Standard, Repco and a comprehensive list of Japanese transistors for Midland, Yeasu, Force, Icom., etc. **Richardson Electronics, Ltd., Rockville Centre, NY 11570, Info/Card #139.**

Antenna Catalog

Watkins-Johnson Company has released a new 112-page catalog describing the company's entire line of antennas and antenna systems. The fully illustrated catalog details W-J's directional, omnidirectional, aerospace, direction-finding, search and surveillance, high-power and special-purpose antenna products. Compatible pedestals and controllers are also described in the catalog. **Watkins-Johnson Co., San Jose, CA 95131, Info/Card #137.**

Multi-Turn Capacitors Brochure


A new six-page brochure highlights the Trim-Tronics, Inc., line of air variable capacitors including the company's recently introduced multi-turn tubular capacitor. The 19 trimmers discussed are suitable for sensitive telecommunications applications such as satellite, microwave, two-way radio and test instrumentation where very precise tolerances are required. Capacitance of the line ranges from 3pF to 16pF, with four mounting styles to meet almost any application. The brochure includes photographs of each product, along with detailed dimensional diagrams, specifications and ordering information. **Trim-Tronics, Inc., Cazenovia, NY 13035, Info/Card #136.**

Military and Commercial Coil Catalog

A new 28-page catalog from Automatic Coil Corp. includes 655 military and commercial coils plus RF chokes. A highlight of the catalog, identified as AC-36, is a detailed 15-page coil specification guide for 5 popular military radios. These include the AN/PRC 104, AN/PRC 77, AN/VRC-12, AN/GRC-106 and WRC-1 radios. In addition to the Signal Corps module numbers used in each radio the catalog identifies all coils, toroids and filters used by Signal Corps part number and by Automatic Coil cross reference number. In addition, photographs of each radio plus all coil types are shown. The catalog will make it easier than ever for U.S. and overseas contractors to formulate their military radio component requirements. The commercial section of the catalog is devoted to standardized toroidal inductors and encapsulated toroidal RF chokes. Toroidal inductors are used in a myriad

Analyze the Universe for Under \$10,000.

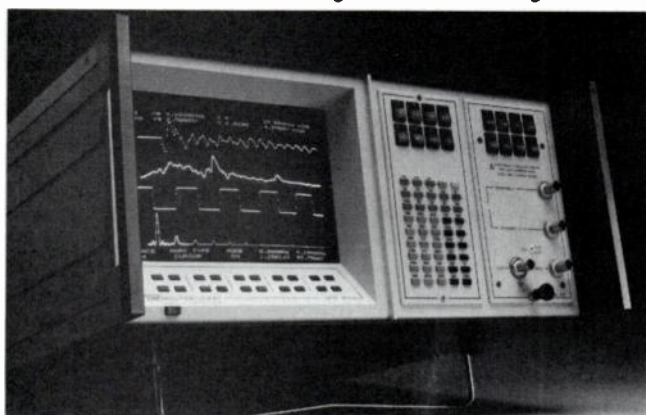The Data 6000 *Universal Waveform Analyzer*



The Data 6000 Universal Waveform Analyzer is modestly priced at under \$10,000. But that's where the modesty ends. No other instrument offers so much power to observe, analyze, and display the waveforms of the physical universe in a single benchtop system. No matter what your application — from high-energy physics to audio signal processing, from automatic testing to ballistics — the Data 6000 offers more versatility, accuracy and computational power than you'll find in any other instrument.

Built around a powerful M68000 microprocessor and armed with real-time operating system, a super-fast Fast Fourier Transform algorithm, a convenient user-interface and easily readable graphics, the Data 6000 is the superior choice for waveform analysis.

Delivery in 30 days or less.

For further information, call: 800-343-8150 or in Massachusetts, 800-892-0528



ANALOGIC ■

DATA PRECISION®

Data Precision Division of Analogic Corporation,
Electronics Avenue, Danvers, MA 01923. Telephone: 617-246-1600. Telex: 6817144

of applications including: EMI and RFI filters, power supplies, switching regulators, triac and SCR controls, transformers and loading coils. The catalog emphasizes that Automatic Coil has specialized in custom toroidal coil production for over 33 years because they represent a nearly perfect inductor. This is because their magnetic field is almost wholly confined within the core and the flux density is essentially uniform over the entire magnetic path. **Automatic Coil Corp., Hialeah, FL, 33010, Info/Card #135.**

Crystal Filter Catalog

Piezo Filters has introduced its new Crystal Filter catalog. Contained are technical specifications and data on standard crystal filters in the range of 2 to 155 MHz. A detailed description of the Engineering and Manufacturing capabilities of Piezo Filters is also included. Piezo Filters offers crystal filters in the range of 1 to 175 MHz with bandwidths of .01 to 3% of center frequency. **Piezo Filters, Carlisle, PA 17013, Info/Card #134.**

Power Inductors Data Sheet

The Inductive Products Division of TRW offers engineering specifications for its SR and LL lines of power inductors. The data sheet includes application, packaging, performance and military specifications. Included are charts listing inductance at 0 DC, maximum DCR, and current for each military part number and product type. Additionally, photographs, outline drawings and a chart provide size and construction information. SR and LL power inductors are recommended for

switching regulator and AC filter choke applications. **Inductive Products Division TRW Electronic Components Group, New York, NY 10013, Info/Card #131.**

Cadec Software Package Brochure

Communications Consulting Corp. has just released a new brochure describing CADEC a computer aided design of electronic circuits software package. Available in standard and microwave versions, this software package is used for analysis and optimizations of any kind of electronic circuit on desk top computers in both the time and frequency domain. This 8-page brochure describes the features of CADEC, a program description, hardware requirements, technical data, and some typical circuit responses as analyzed by CADEC. **Communications Consulting Corp., Upper Saddle River, NJ 07458, Info/Card #130.**

Rectifier Bridges And Diodes Catalog

Electronic Devices, Inc.'s new catalog provides information on its line of standard, fast, and superfast recovery silicon rectifiers that includes silicon bridge rectifiers, high voltage axial lead rectifiers, high voltage packs and cartridges, and other rectifier devices. Extensive electrical and mechanical specifications are included, as well as information on new, state-of-the-art, 50ns. recovery rectifiers, 100 ampere rectifier bridges, and integral heat sink designs. **Electronic Devices, Inc., Yonkers, NY 10710, Info/Card #119.**



RF BRIDGES

Fixed or Variable
Directivity (balance) 40 or
50 dB options.

1-900 MHz RF Instruments

- RF Amplifiers
- RF Analyzers
- RF Comparators
- RF Switches
- Hybrid Divider/Combiners
- RF Detectors
- Impedance Transformers
- Precision Terminations
- Precision DC Block
- Filters
- Available 50 or 75 Ohms

WIDE BAND ENGINEERING COMPANY, INC.

P.O. Box 21652, Phoenix, Arizona 85036, U.S.A. Telephone (602) 254-1570

INFO/CARD 15

MINIATURE BANDPASS FILTERS



We hold the state-of-the-art filter technology inside the palm of our hand.

State-of-the-art filter technology at its best. Only .325" H x .25" W and as short as 1.25", FBC Cavity filters are setting the standard in communications, aerospace, EW, surveillance and ECM applications.

- 6 GHz—17 GHz
- 3 to 10 Poles
- Typical Butterworth amplitude, phase and group delay responses
- 1 dB BW of 1 to 70% of F_0
- 1.5:1 or less VSWR
- As low as < 0.5 dB insertion loss
- Up to 10 watts CW
- 50 Ω impedance
- SMA female/male connectors

*Length depends on number of poles and frequency

FBC cavity filters designed to your specifications within 6 to 8 weeks. Small quantities as soon as 2 weeks.



Call (301) 946-1800. Let CIRQTEL, a leader in filter technology for 21 years, solve your filter problems.

Superior Products by Design

CIRQTEL
INCORPORATED

10504 Wheatley Street
Kensington, Maryland 20895
Telephone: (301) 946-1800
TWX: 710-828-0521

SIGNATURE TECHNOLOGY SPECIALISTS

GENERAL DYNAMICS CONVAIR DIVISION, an acknowledged leader in defense and aerospace systems, offers you professionalism and career enhancement in a stimulating environment. We are expanding our team of talented engineers to accommodate the needs of our exciting high technology programs in ground, air and sea launched missiles; vehicles for launch, orbital insertion and station keeping; aircraft subsystems; energy development.

We are currently seeking qualified Signature Technology Specialists experienced in the following areas:

- **RCS Prediction & Analysis**
- **Radar Absorbing Materials & Structures**
- **RCS Control Techniques**
- **Data Reduction & Display**
- **RCS Measurement Instrumentation**
- **Specialized Radars (High Resolution & Bistatic)**
- **Infra red, Acoustic & Visual Measurements & Analysis**

We offer challenging assignments that will let you grow technically and professionally. These positions require a BS, MS or PhD in Engineering, Physics or Mathematics.

We can provide one of the best benefit packages in the industry. In addition to the San Diego environment, we offer competitive salaries, a stock/savings plan, company paid insurances, retirement plan, tuition reimbursement, liberal relocation allowances including temporary company funded housing and exceptional recreational facilities.

Please send your resume to: Division Vice President — Research & Engineering, GENERAL DYNAMICS CONVAIR DIVISION, P. O. Box 85357, MZ 11-1342-I361, San Diego, CA 92138. An Equal Opportunity Employer/U.S. Citizenship Required/Principals Only.

LAUNCH A PROMISING FUTURE WITH *Convair*

GENERAL DYNAMICS
Convair Division

ECM: The Core of America's Defense

Northrop DSD Electronic Countermeasures Technology is the heartbeat of today's national defense. It quickens to the challenge and represents our ability to out-think . . . out-maneuver . . . and out-calculate rapidly.

Experienced professionals can join our opportunities and work along with an outstanding corps of R&D engineers in an exciting, technologically progressive and advanced product design and development environment.

Northrop DSD. The Core of advanced ECM technology. The place for a new career.

ELECTRICAL DESIGN/ DEVELOPMENT ENGINEERS

Positions require BSEE or equivalent, and design and development experience in one of the following specialized areas:

POWER SUPPLIES: Develop high/low voltage linear/switching power systems and modulators: magnetics and feedback theory analysis.

MICROWAVE: Active/passive microwave integrated circuit design (2-26 GHz); familiarity with filter detectors, wave guides, high frequency solid state amplifiers and S-parameters.

NORTHROP
MAKING ADVANCED
TECHNOLOGY WORK.

RECEIVERS: Conceptual design, fabrication, and test of state-of-the-art receiver systems for ECM/Elint applications. Familiarity with system architecture, signal processing (26GHz frequency range), and channelized, set-on, and micro-scan techniques is desirable.

ANALOG: Specialist in videoamplifiers, filters, A/D and D/A conversion; background should include feedback theory analysis and computer-aided circuit analysis.

PROJECT ENGINEERS

BSEE, or equivalent; experience in one of the following areas:

- High efficiency broad band solid state RF power amplifiers having precision linearity. Strong documentation skills required.
- Military receiver HW design for precision phase track receivers to DOA requirements using ultra-precision internal phase/amplitude alignment.

MANUFACTURING TEST EQUIPMENT DESIGN ENGINEERS

Individuals with BSEE, BSCE, BSCS or equivalent, and related experience. Projects will involve design of automated/semi-automated test equipment systems.

- **HARDWARE:** Microprocessor/MSI, LSI, analog and RF circuits.
- **SOFTWARE:** Real-time microprocessor controlled software programming in Assembly, PASCAL and Fortran.

Northrop offers an outstanding salary and comprehensive benefits package including complete medical and dental coverage, company supported savings program, profit sharing and more. For immediate consideration, please forward resume with salary requirements to: **Manager, Professional Employment.**

NORTHROP CORPORATION DEFENSE SYSTEMS DIVISION

600 Hicks Road,
Rolling Meadows, IL 60008

We are an equal opportunity employer and encourage minorities, females, veterans and the handicapped to apply. U.S. CITIZENSHIP REQUIRED.

At Raytheon Electromagnetic Systems Division, we take Hide-and-Seek seriously.



We create the ECM systems that hide even the most massive friendly ships and aircraft from the prying "eyes" of enemy radars; make missiles miss, identify enemy platforms, and gather vital intelligence — all with uncanny speed and accuracy.

For more than twenty years, Raytheon professionals have defined the leading edge in state-of-the-art countermeasure technology. Help us stay out in front.

If you have an inquisitive mind and strong technical skills, you can discover exciting new dimensions in the challenge of sophisticated defense electronics.

Raytheon offers you opportunity for involvement — and for enjoyment — like nowhere else. Join us and become a vital part of our growing Electromagnetic Systems Division. We offer challenging, yet stable work environment for:

Component Engineers

Will select parts, determine proper applications, prepare procurement

specs, select/evaluate vendors and be responsible for technical coordination and control.

BSEE preferred and six + years applicable experience required.

Experience in any of the following areas highly desirable: RF/Microwave or Power Supply components and sub-assemblies, multi-pin connectors or wire and cable components.

Microwave Design Engineers

- active microwave component design
- MIC/MMIC-microwave/ Millimeter wave integrated circuit design
- microstrip and stripline design

BSEE preferred and five + years experience required.

Advanced Receiver Development Engineers

- conceptual design fabrication and test of advanced receiver systems
- signal processing
- system architecture

- background in channelized, set-on and micro-scan techniques design

BSEE and five + years experience required.

DRFM Engineers

- digital RF memory experience
- ECL design
- RF experience desirable

BSEE and five + years experience required.

We have opportunities at our California facility. Call COLLECT or send resume including present salary and/or requirements to **Professional Employment:**

RAYTHEON
Dept. RFD 384
6380 Hollister Ave.
Goleta, CA 93117
(805) 967-5511, Ext. 2500



Electromagnetic Systems Division
Equal Opportunity Employer
U.S. Citizenship Required

MANAGER, TRANSMITTER DESIGN RADAR SYSTEMS

Our client has an immediate need for a radar transmitter design engineer to manage a group involved in the design of microwave amplifier systems.

If interested, you should have a BSEE with three to ten years experience in the various aspects of radar transmitter design; vis a vis: application of microwave power amplifiers including travelling wave tubes, Klystrons, and crossed field amplifiers; as well as the design of pulse modulator tube type and solid state circuits; and related high voltage power supply equipment.


The company is located in a highly desirable

suburban area close to a major city with its attendant cultural and educational advantages. Salary and benefits are more than competitive and relocation can be made relatively painless.

If you are interested in this position, or in any of our other engineering and management opportunities, call A.J. Walsh COLLECT or send your resume to:

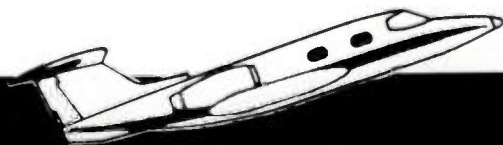(215) 968-0707

WALSH
Engineering Placement
Service
The Commons West
638 Newtown-
Yardley Road
Newtown, PA 18940
Equal Opportunity
Employer



RF DESIGN ENGINEERS

Wulfsberg, a leading manufacturer of aviation-related communication equipment including airborne radio telephone, FM air mobile communications and AM air/ground communications equipment, has engineering openings now.

COME GROW WITH US

A growing market and new expanded lab facilities cause us to look for engineers with the following qualifications:

- BSEE
- At least 3 years experience in RF circuit and radio design techniques

Outstanding employee benefits including year-end profit sharing.

Enjoy an unexcelled "quality of life" in this attractive Kansas City metropolitan location. Let us tell you about it.


If qualified, please forward your resume to Jerry Henson, Director of Personnel.



WULFSBERG
ELECTRONICS, INC.

11300 West 89th Street • Overland Park, Kansas 66214

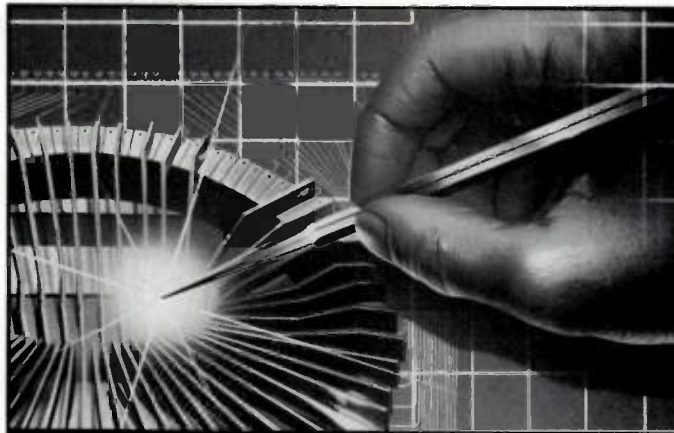We Are An Equal Opportunity Employer, M/F



Bring Technology To Life At General Dynamics.

Over 30 years ago, General Dynamics Pomona Division brought Terrier, the nation's first tactical guided missile system, to life. Since then, we've continued to design, develop and manufacture state-of-the-art tactical weapons systems for America's Armed Forces. We're constantly exploring new realms of technology that will keep our reputation for quality second to none. And we're always searching for innovative engineers and scientists who can add new dimensions to our efforts.

That's where you fit in. By bringing your talents to Pomona Division, you can bring our technology, as well as your career, to life in one of the following positions:

MICROELECTRONICS

We have numerous opportunities for Custom Microelectronics Specialists with a minimum of 3 years of experience as well as a BSEE Degree. The areas in which we're seeking microelectronics designers include: large scale hybrid assembly, custom CMOS process development, custom high speed circuit design and IR detector development. Knowledge in one or more of the following areas is desired: assembly processes, semi-conductor device modeling, thermal processing, and analog, digital & RF circuit design. Some positions require an MS/PhD Degree.

RADAR

We currently have a variety of positions available for Radar Design Engineers with a BSEE and a minimum of 3 years of experience. Desired areas of experience include: signal processor design (digital & RF), transmitter design (high voltage, switching power supplies design, high power RF), radar analysis (system performance, clutter analysis, ECCM) and radar systems (DMTI techniques, radar design).

MICROWAVE/ANTENNA

We're looking for engineers experienced in microwave systems, component and antenna design. A minimum of 3 years of experience is desired as well as a BSEE or BSME Degree. You will be designing microwave circuitry for missile and radar systems. Knowledge of one or more of the following functions is preferred: microwave circuit design, computer-aided design, antenna design, microwave component design and production support of microwave hardware for missile systems.

Our long range contracts can offer you a promising future with diverse opportunities for personal growth and advancement. We'll also enhance your life with a competitive salary, excellent benefits and extensive recreational facilities.

For more information and immediate consideration, please contact: General Dynamics Pomona Division, Director, Design Engineering, P.O. Box 3011, Drawer B-783, Pomona, CA 91769.

GENERAL DYNAMICS

Pomona Division

Equal Opportunity Employer / U.S. Citizenship Required

ENGINEER

PRODUCT MANAGER RF/EMI

Come join a growing progressive firm where you will have complete responsibilities for testing, development, applications & marketing of our current & future shielding products. A BSEE with RF/EMI experience is required.

We provide an excellent salary & benefits package, together with a working environment most conducive to both personal & professional growth.

For immediate consideration, send resume including salary history to our Personnel Manager.

INSTRUMENT SPECIALTIES

BOX A

DELAWARE WATER GAP, PA 18327

Equal Opportunity Employer

GROWTH POSITIONS:

\$25-65,000 + .

30+ years National coverage. Ground/mobile/aircraft communications related equipment. Design, Devel. Quality/Reliability, Test, Mfg. All Fees Paid. Longberry Employment, 930 Main Place, P.O. Box 471, Niles, Ohio 44446. (216) 652-5871.

ELECTRONIC ENGINEER (R.F.)

— Michigan —

Fast growing CATV manufacturing company is seeking an individual to assume responsibilities for design and application engineering. This position requires BSEE and experience with R.F. circuits. Salary commensurate with experience. Send resume to:

Ron DeVries
C&D Electronics
P.O. Box 177
Gennison, MI 49428
(616) 669-2440

RF/MICROWAVE ENGINEERS

Representing companies (in New England and Nationally) with hundreds of opportunities for RF and Microwave Engineers means we are the one contact necessary for that right position, whether it be a new challenge or career advancement.

ENTRY LEVEL (0-3 YRS. EXP) 22-35K
MID LEVEL (5-10 YRS. EXP) 30-45K
SENIOR AND MANAGEMENT 40-70K

Professional, confidential, free resume preparation service.

*Nationwide
Business Service*

PERSONNEL CONSULTANTS
ESTABLISHED 1937

145 STATE STREET,
SPRINGFIELD, MASSACHUSETTS 01103

Advertiser Index

A.H. Systems 34A
Acrian, Inc. 11A
Adams Russell-Modpak
Division 12A
Alpha Industries, Inc 7A
American Microwave Corp. 28A
Amperex Electronics Corp. 2A
Amplifier Research 29A
Applied Engineering
Products 76A
Astron, Inc. 33A, 44A
Ava Electronics Corp. 81A
Aydin Vector 82A
Bird Electronics 83A
Bliley Electric Company ... 74A
C&D Electronics 96A
California Eastern
Laboratories 21A
The Carborundum
Company 42A
Cinox Corp. 65A
Cir-Q-Tel 91A
Colby Instruments 83A
Colorado Crystal 56A
Daico Industries, Inc. 57A
Dale Electronics 50A
Data Precision 90A
Eagle Magnetic Co., Inc. ... 56A
Electro-Metrics 31A
Electronic Research
Company 54A
Epso Microwave. . 30A, 74A, 82A
John Fluke Manufacturing
Company, Inc. 3A
Frequency Sources, Inc.,
Semiconductor Division. 13A
Fischer Custom
Communications, Inc. ... 56A
General Dynamics - Convair
Division 92A
General Dynamics - Pamora
Division 95A
General Microwave 15A
Genisco Technology Corp. 63A
Henry Radio 88A
Hewlett-Packard
Company 8A, 26A, 71A
IR&D 72A
ITT Cannon 17A
Instrument Specialties
Co., Inc. 59A, 67A, 96A

Instruments for Industry... 75A
International Crystal
Manufacturing Co., Inc. . 85A
JFW Industries Inc. 87A
Janel Laboratories, Inc. ... 63A
Johanson Manufacturing
Corp 9A
E.F. Johnson Company. . . 84A
Keene Corp. 19A
LectroMagnetics, Inc. 62A
Lindgren RF Enclosures... 86A
Longberry Employment
Service, Inc 96A
MTT-S 41A
Marconi Instruments 23A
Matrix Systems 10A
Merrimac Industries. 16A
Mini-Circuits . 1-64, 5A, 18A, 37A
..... 76A, 81A, 84A, 85A, 88A, 98A
Nationwide Business
Services 96A
Northrop Corporation 93A
Piezo Systems 22A
Programmed Test
Sources, Inc. 53A
RF Monolithics, Inc. 48A
Raytheon Co. 94A
Reaction Instruments 55A
Repco, Inc. 39A
Sprague-Goodman
Electronics 89A
Sokol Crystal Products, Inc. 89A
Tech-Etch, Inc. 64A
Teledyne Crystalonics 62A
Teledyne Microwave 97A
Test & Measurement World. 49A
Texscan Corp. 27A
US Communications 96A
Vectron Laboratories . 51A-52A
Voltronics Corporation. 77A-78A
Walsh Engineering
Placement 95A
Watkins-Johnson Company. 73A
Wavetek-Indiana, Inc. 45A
Wavetek Rockland, Inc. ... 43A
Weinschel Engineering. ... 47A
Wide Band Engineering
Company 18A
Wilmanco 70A
Wulfsburg Electronics 95A



ELECTRONIC ENGINEER (RF) wanting Southern IDAHO sports and recreation, state-of-the-art mobile communication challenges and professional growth should consider **US COMMUNICATIONS CORPORATION**.


Junior and Senior grade professional RF electrical engineers with BS or MS degrees for assignments in new product development programs for exciting new mobile communications hardware/software.

RF TECHNICIANS - Two year AA or equivalent education with proven record in RF Engineering Laboratory work are encouraged to apply.

Please reply with resume and salary history to:

US COMMUNICATIONS CORPORATION
A SUBSIDIARY OF
JOHNSON
SECTION M
P.O. Box 268 • Twin Falls, ID 83303-0268
AN EQUAL OPPORTUNITY EMPLOYER M/F

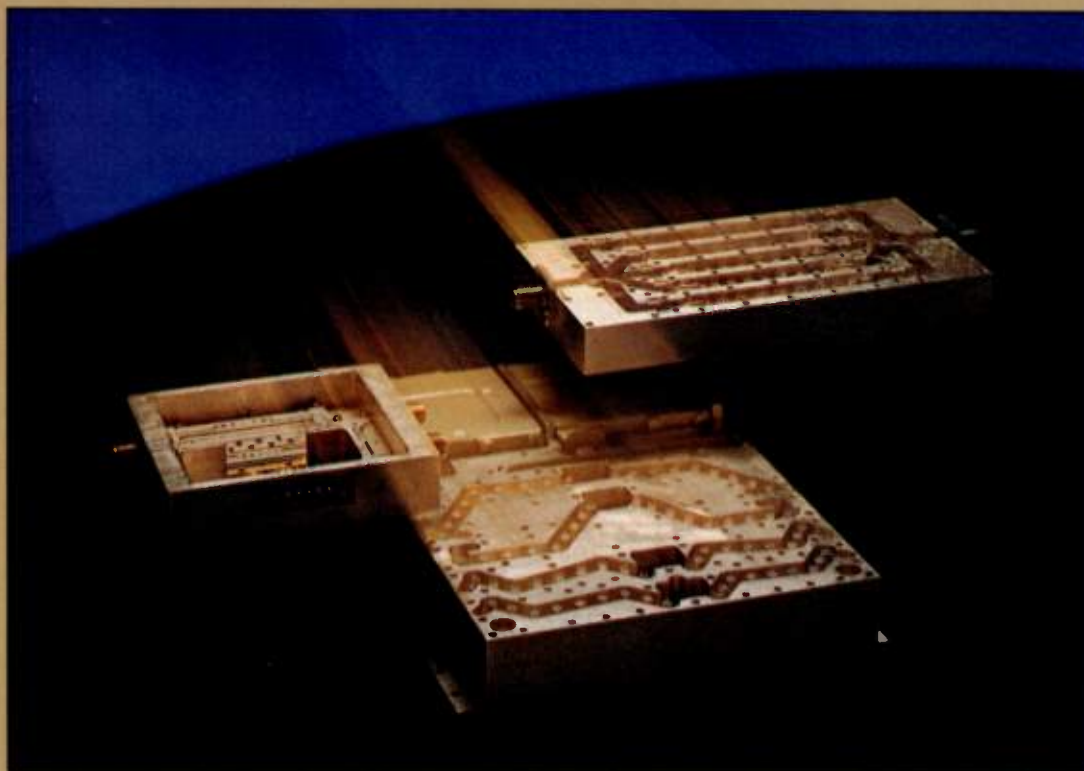Teledyne Microwave Has Something to Offer In Switch/Filter Combinations



Everything.

Combining diode switches and filters in a single package makes a lot of sense. And Teledyne Microwave is more qualified and experienced in designing and building switch/filters and switch/multiplexers than anyone else. We use this experience in filters, switches, multiplexers and MIC technology to offer the system designer a variety of switch/filter approaches specially configured for his application.

Type	Insertion Loss	Switching Speed	Band Overlap
Switch/Filter/Switch	Highest	Fast	Yes
Switch/Multiplexer	Moderate	Fast	Possible
Multiplexer (comparison) ¹	Lowest²	Instantaneous	No

1) Requires parallel signal processing.

2) Except at band edge.

To meet a system designer's requirement for band channelization, we can choose between MIC thin film, cavity, or combine filters. We can then select a switching or multiplexing configuration for best selectivity, isolation, and lowest loss. Many customers find it cost effective to have us integrate TTL compatible drivers and decoders as well.

Design excellence is important to Teledyne Microwave. But so is our commitment to build and deliver reliable microwave components when we promised—on time. Quality is designed into our products and then we screen each unit just to be sure.

You can be confident that Teledyne Microwave will have a switch/filter combination to suit your needs, and you can rely on our proven record of production quantity deliveries. Call us.


TELEDYNE MICROWAVE

"Pride in Performance"

Teledyne Microwave
1290 Terra Bella Avenue
Mountain View, CA 94043

Phone: (415) 968-2211
TWX: 910-379-6939

© Teledyne Microwave 1983

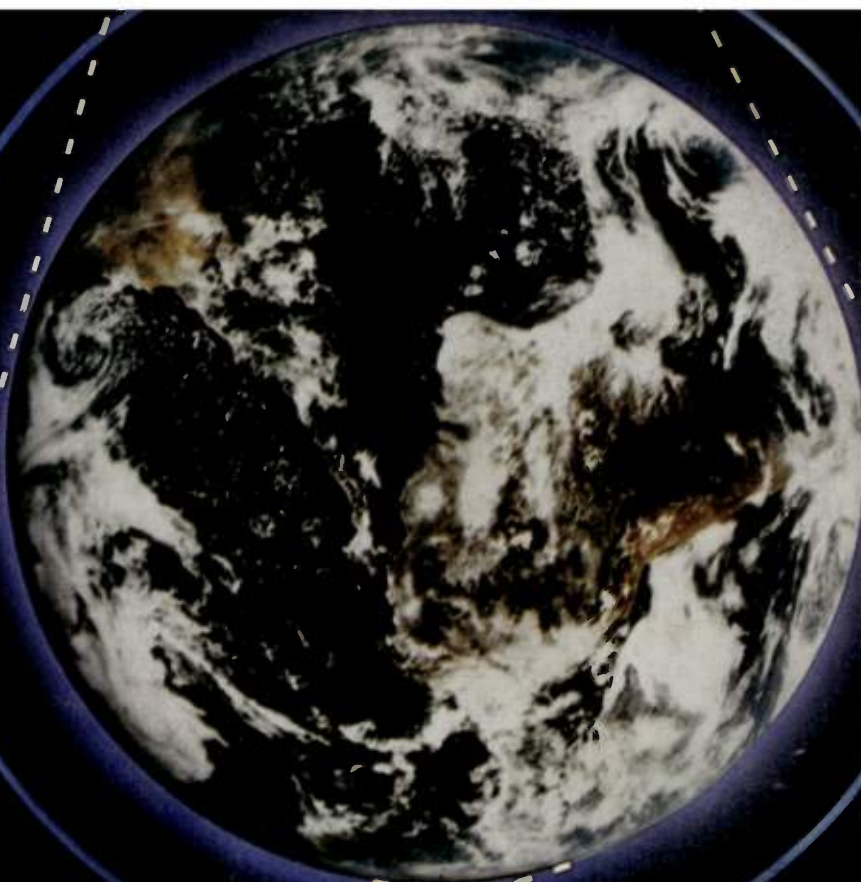

The Earth from 22,300 miles in space. (Photo: Courtesy of NASA)



Clarke's proposed 3-satellite system.

FINDING NEW WAYS...

In 1945, Arthur C. Clarke—a British mathematician, wireless operator and creative science fiction writer found a better way to beam communications signals around the world. He theorized that an artificial satellite, carried by a rocket to an orbit 22,300 miles above the earth's equator and traveling at 6879 mph (the speed at which the earth rotates on its axis), would appear motionless to an observer on earth. From that height, Clarke reasoned, a radio relay station could cover one-third of the earth's surface; three such satellites, placed in geosynchronous orbit around the equator could provide worldwide communications. In 20 years, advances in electronics, miniaturization and rocketry made Clarke's dream a reality and gave the world improved communications capability.

Likewise, in 1969, Mini-Circuits made its total commitment to serve the emerging communications market . . . by replacing expensive, custom RF signal-processing components with low-cost, catalog units with unparalleled reliability.

Our dream, like Clarke's, has come true. Over 1,000 catalog items available with such Mini-Circuits innovations as our exclusive HTRB burn-in testing, the world's only 3-year guaranteed mixers, computer-automated performance data (CAPD) to eliminate design guesswork . . . just to name a few.

Mini-Circuits' products have become the industry standard. We are actively dedicated to the pursuit of further improvements in product cost/performance, quality and reliability for more effective worldwide communications.

finding new ways . . .
setting higher standards

Mini-Circuits

A Division of Scientific Components Corporation
World's largest manufacturer of Double Balanced Mixers
P.O. Box 166, Brooklyn, New York 11235 (212) 934-4500
Domestic and International Telex 125460 International Telex 620156



INFO/CARD 84