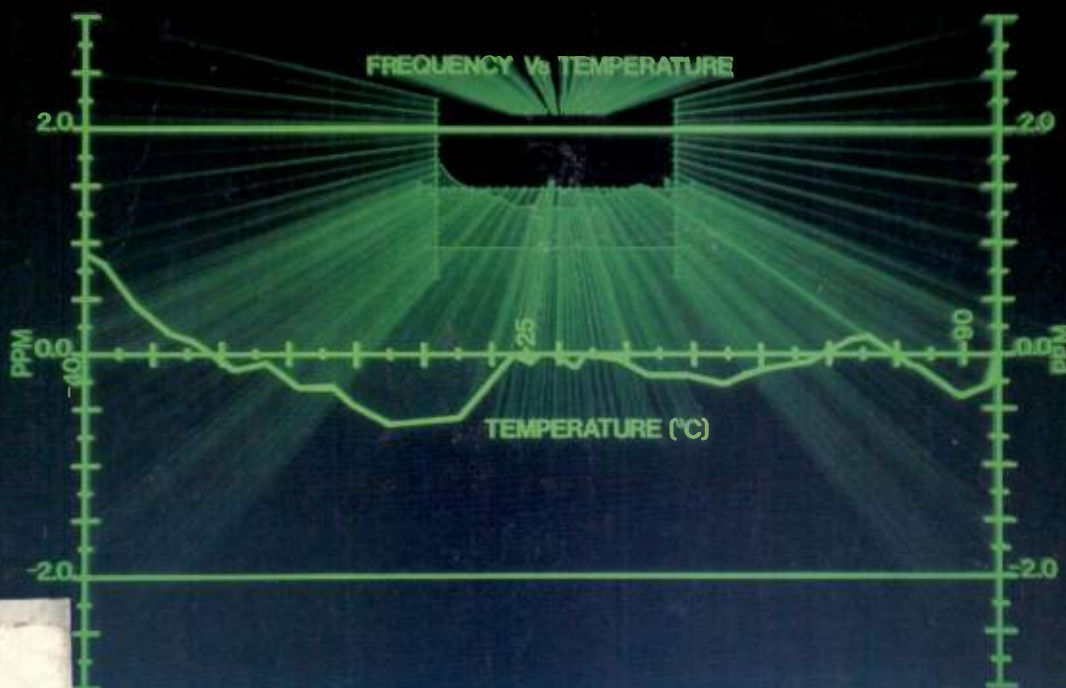


rfdesign

ideas for engineers

March 1985



736 00123358 41 31
0040 0010 1 071084 00 1
ALAN M VICTOR
SP STE ENG COMM DIV
MOTOROLA CORP
8000 W SUNRISE PM 1174
SUNRISE FL 33322



Special Report:
New Waves in Oscillator Design

A collection of various electronic components, including integrated circuits, transistors, diodes, and connectors, arranged on a light-colored surface. Some components are labeled with text like "SMALL SIGNAL RF SEMI'S", "CUSTOM RF HYBRIDS", "LINEAR WIDEBAND AMPS", and "CATV AMPS".

INFO/CARD 1


AT-STRIP QUARTZ CRYSTALS SET NEW SIZE AND PERFORMANCE STANDARDS.



**90% SMALLER THAN HC-18
WITH GREATER SHOCK
RESISTANCE AND A WIDE
FREQUENCY RANGE**

Motorola introduces the latest technology in crystal miniaturization. This success is part of our ongoing commitment to reliability and smaller size.

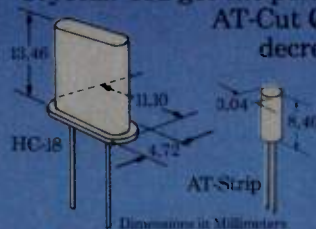It is the 3.0 mm x 8.4 mm AT-Strip Quartz Crystal. You get the performance of conventional AT-Cut Quartz in a significantly decreased package volume.



Both new and existing applications benefit from this development — pocket pagers, disk drives, modems, commercial communi-


cations devices, and driving microprocessor-based systems.

WITHSTANDS 8,000 g SHOCK FORCE

The new Motorola AT-Strip Crystals offer a shock survival level two and three times higher than traditional crystals.

These and other environmental characteristics are documented in tests performed in accordance with MIL STD 202.

TYPICAL CRYSTAL SHOCK PERFORMANCE

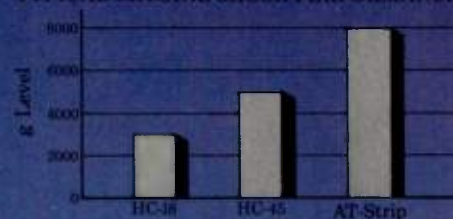

Our advanced manufacturing and quality assurance capabilities provide unsurpassed reliability in the field.

EXPANDING AVAILABILITY OF FREQUENCIES


Motorola AT-Strip Crystals are currently available in popular fundamental frequency ranges. And our engineers are adding frequencies daily — with the shortest lead times in the industry — to meet your needs.

That means you can start incorporating a new AT-Strip Crystal in your applications now. Give your new products an edge. And improve your current product's performance. Contact us for complete literature on the full line of Motorola Devices.


Motorola, Inc. Components Division,
2553 N. Edgington Street, Franklin Park, IL
60131. Phone (312) 451-1000, Ext. 4414
TWX 910-255-4619, Telex 4990104.



MOTOROLA INC.
Components Division

© 1985 Motorola, Inc. Motorola and  are registered trademarks of Motorola, Inc.

GOING THE DISTANCE



*O*n May 11, 1926—a 16-man team of international explorers, led by South Pole discoverer Roald Amundsen, sailed the dirigible Norge from Spitzbergen, Norway to the "top of the world." The flags of the United States, Norway, and Italy were released as the 348-foot airship crossed the North Pole. Then the weary crew pressed on, fighting ice and high winds. After 46 bone-numbing hours, the Norge reached Alaska, setting down in an Eskimo village 3,200 miles from the starting point.

NOW ACRIAN IS GOING THE DISTANCE TO INTEGRATED POWER MODULES

Acrian has already earned an industry-wide reputation as the leader in high reliability microwave and RF power transistors.

Today Acrian is going

cally to provide our customers with single-stage and integrated hybrid modules, both custom and standard, for military, commercial, and industrial RF power applications.

Acrian's Module Division is fully staffed with RF engineering, manufacturing and quality control experts. And our new design and production facilities utilize the latest in state-of-the-art technologies.

With our resources, we have the in-house capability to compress your design cycle and reduce your engineering time, while assuring

result: a higher quality product that saves you time and money.

Ask us today for details on the new lineup of Acrian integrated power modules and hybrid assemblies. We'll be glad to send you data on these or any of more than 500 Acrian products designed to go the distance in communications, radar and avionics. Call (408) 294-4200. Or TWX (910) 338-2172.

Acrian, Inc., 490 Race Street
San Jose, California 95126

 **ACRIAN**



Cover

This month's cover features Motorola's MDO-2 (left) and the new MDO-3 (right) temperature-compensated crystal oscillators. Motorola considers these MDO products to be the best in TCXO performance in their cost range. The MDO-3 is described in this month's Special Report, along with other recently announced oscillator products. Many of the considerations mentioned in Dennis Marvin's article on frequency-temperature performance determination in crystal oscillators were incorporated in the MDO-2 series. (Photo courtesy of Motorola, Inc.)



Features

20 Special Report: New Waves in Oscillator Design

This month's Special Report covers common oscillators designed to operate primarily at frequencies below 2 GHz. Examples of the kinds of improvements being made in crystal and SAW resonator oscillators are described, along with indications of probable trends in oscillator design — James N. MacDonald.

26 The SAW Resonator: How It Works — Part 2

The author continues his explanation of the surface acoustic wave resonator and his program to model device responses. He describes how to use the program to examine the properties of reflective arrays and single and multiple cavities. A BASIC version of the program is given for microcomputer users. — Jeffrey S. Schoenwald, Ph.D.

53 Frequency-Temperature Performance Determination in High Stability TCXOs

High stability temperature-compensated crystal oscillators are subject to many instabilities not normally considered in the design of lower stability products. The design engineer must carefully consider the system requirements in dynamic environments and as a function of time. The author reviews several second order effects and attempts to quantify the amount of performance debasement that can result. — Dennis Marvin.




Scenes from RF Technology Expo 85 — Anaheim, Calif.

Departments

- 6 Editorial
- 8 Publisher's Notes
- 14 Letters
- 16 News
- 24 RFI/EMI Corner
- 34 Calendar
- 45 Info Card
- 60 The Digital Connection
- 63 New Products
- 72 New Literature
- 76 Advertisers Index

R.F. DESIGN (ISSN: 0163-321X USPS: 453-490) is published monthly plus one extra issue in June, March 1985, Volume 8, No. 3. Copyright 1985 by Cardiff Publishing Company, a subsidiary of Argus Press Holdings, Inc., 6530 S. Yosemite Street, Englewood, CO 80111 (303) 694-1522. Contents may not be reproduced in any form without written permission. Second-Class Postage paid at Englewood, CO and at additional mailing offices. Subscription office: 1 East First Street, Duluth, MN 55802, (1-800-346-0085). Subscriptions are sent free to qualified individuals responsible for the design and development of communications equipment. Other subscriptions are: \$15 per year in the United States; \$25 per year in Canada and Mexico; \$25 per year for foreign countries. Additional cost for first class mailing. Payment must be made in U.S. funds and accompany request. If available, single copies and back issues are \$5.00 each (in the U.S.). This publication is available on microfilm/fiche from University Microfilms International, 300 N. Zeeb Road, Ann Arbor, MI 48106 USA (313) 761-4700. POSTMASTER & SUBSCRIBERS: Please send address changes to: R.F. Design, P.O. Box 6317, Duluth, MN 55806.

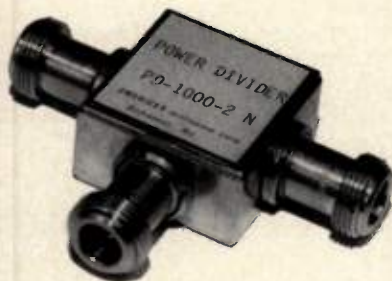**Broadband Power Divider
10-1000 MHz**

PD-1000 Series Power Dividers are broadband, low loss, high isolation units available with BNC, TNC, SMA and N connectors and usable to 1300 MHz.

Check these specifications:

Frequency Range: 10 MHz-1 Ghz

Isolation(output):

10-20 MHz	25dB Min
20-500 MHz	35dB Min
500-1000 MHz	30dB Min

Insertion Loss:

10-500 MHz	0.4dB Max
500-1000 MHz	0.6dB Max

Return Loss:

10-20 MHz	14dB Min (1.50:1)
20-1000 MHz	20dB Min (1.22:1)

Impedance: 50 Ohms

Amplitude Balance: 0.2dB Max

Phase Balance: 2° Max

Input Power: 2.5 Watts

Temperature Range: -50°C to +85°C

Other UHF/VHF products available are directional couplers and impedance transformers. Send for catalog.

AMERICAN microwave corp

7311-G GROVE ROAD
FREDERICK, MARYLAND 20701
(301) 662-4700

INFO/CARD 4

Where Do You Learn About RF Circuits?



James MacDonald
Editor

The biggest surprise at the RF TECHNOLOGY EXPO was the response to the Fundamentals of RF Design course. Based on pre-registrations, the room was set up for a maximum of 350. By starting time the first day the room was filled and more than 100 conference attendees were in the hall hoping to register. We were able to add some chairs, but many who had not pre-registered had to be turned away.

The situation was similar when the course was repeated the next day. By then the room had been expanded to seat 500, anticipating the overflow from the first day. All seats were filled and remained filled throughout the day.

On one hand, this overwhelming response reflected the response to the EXPO as a whole. Attendance exceeded our expectations, if not our hopes. On the other hand, it provided dramatic proof of a serious lack of educational opportunities for RF engineers. The audience composition ranged from young recent graduates to university professors with well-established reputations in electrical engineering.

As I talked with attendees the same fact was mentioned over and over; electrical engineering students have little opportunity or incentive to study RF circuit principles. In many universities the courses simply are not available. Where they are available advisors do not encourage such courses.

Current employment opportunities apparently are greater and salaries higher in the digital and power fields, but this not-very-widely promoted course in RF design fundamentals attracted more than 800 engineers and others involved in designing RF equipment, some from foreign countries. Clearly there is a significant lack of educational opportunities in RF circuit theory and design. We think engineering colleges should take a look at this educational need.

Proceedings of the sessions, including the Fundamentals of RF Design course, will be published soon. RF designers who could not attend the EXPO may want to order a copy. Each session was tape recorded, as well. Tapes may be ordered from Meyer Communications Corp., 13791 E. Rice Place, Aurora, CO 80015.

During World War II many amateur radio operators were hired by defense contractors to build communications gear. Even fewer engineers were trained in RF principles at that time. Amateurs knew how to build equipment, even if they did not thoroughly understand how it worked. Many of them eventually became engineers.

This is one reason so many RF designers are amateur radio enthusiasts. Most of those who worked during WWII are retired, but they passed their enthusiasm on to the younger generation. During EXPO 85 quite a few hams were seen with handheld 2-meter gear and others were heard on the band with mobile and base station rigs.

Carl Lodstrom, SM6MOM/W6, has suggested that we select a frequency for simplex operation during the next EXPO and publicize it. Carl said such a frequency seemed to be chosen by chance at EXPO 85, perhaps because people heard others talking on it and joined the net. He said it was a great way for hams to get together for dinner or meetings.

What do *RF Design* readers think of this idea?

James H. MacDonald



ATTENUATORS TERMINATIONS MATCHING PADS DETECTORS

FIXED ATTENUATORS

DC-2 GHz BNC, TNC, SMA or Type N
DC-18 GHz SMA or Type N

TERMINATIONS

DC-2 GHz BNC or SMA
DC-8 GHz Type N
DC-18 GHz SMA

PUSHBUTTON ATTENUATORS

DC-750 MHz BNC, TNC, SMA or Type F

DETECTORS

100 KHz - 1000 MHz

Units available 50 or 75 Ohm



JFW Industries, Inc.
5134 Commerce Square Dr.
Indianapolis, IN 46237
317-887-1340

That Old Black Magic — Losing Its Old Spell



Keith Aldrich
Publisher

Something happened at the RF TECHNOLOGY EXPO 85 in January: something which spells the end for that old myth about RF technology being a "black art" which practitioners exercise by instinct, or by "the seat of the pants."

Call it a new generation. Call it the light of rational analysis breaking like a dawn to dispel the blackness. Whatever you call it, it became obvious at the EXPO that "weakling" and "tuning" approaches to RF design are giving way to analytic approaches, in which the vagaries of RF propagation are not regarded as unexplainable mysteries, but phenomena which can be characterized, predicted, and harnessed with precision. The end result is designs which take days instead of weeks and which are proved in the lab instead of the field.

The new generation factor was evident in viewing the 800-plus attendees who listened with such close attention to Les Besser and other instructors at the "RF Fundamentals" course. While there was a liberal sprinkling of gray heads... more, perhaps, than the title of the course would lead you to expect... the studiously attentive faces were mainly young, young, young. Not college young. The badges read "Hughes" and "Rockwell" and "General Dynamics," and the exhibitors who encountered them later in their booths exclaimed over their knowledgeable questions and their purchasing power (one instrument manufacturer an-

nounced sales of \$250,000 worth of equipment the first day). No, these were real engineers... just young — and *eager to learn*. Les Besser was up there talking about constant gain circles, and S-parameters, and computer-aided design, and they were eating it up.

Just a couple of years ago, RF engineers were characterized as being hostile to such innovations, on the average, preferring to "do it their way." And, on the average, they have successfully resisted the innovations. Instructor Besser asked for a show of hands, toward the end of his lecture, to see how many attendees commonly applied tolerance analysis to check out their designs. Only a small fraction raised their hands. "About three percent," Les computed; "about the national average." He went on to preach the gospel: how his listeners could cut down their failures in the field by applying some of the methods he was espousing.

It had the ring of one of those futile lectures about littering or something. Except for one thing. These young people were listening carefully, not yawning and fidgeting. And you realized, if you thought about it, that these people were not *inherently* antagonistic to computers, and modeling and simulation. They grew up with computers. They are already competent EEs, for the most part. It is only RF that is new to them. They are listening so carefully to Les because they are going to *practice* what he is preaching.

That is good news for their employers, and for the RF boom that was so apparent in the mood of RF TECHNOLOGY EXPO 85. While much of the electronics industry is faltering, and while digital engineers in many parts of the country are being thrown out of work, manufacturers of RF equipment can hardly keep up with the demand. To keep up with what is needed from them RF engineers must be as productive as modern technology can make them. We are pleased to have been of service in helping bring them up to speed.

Keith Aldrich

Publisher
Keith Aldrich

Editor
James MacDonald

Consulting Editor
Andy Przedpelski

Editorial Review Board
Alex Burwasser
Doug DeMaw
Dave Krauthelmer
James W. Mize, Jr.
Ed Oxner
Andy Przedpelski
Jeff Schoenwald
Raymond Slocote

Account Executives
Eric Nieman
Kathryn L. Walsh

Sales Service Administrator
Lisa Fontana

Advertising Services
Andrea Wendelin

Circulation Director
Ron Kinnes

Circulation Manager
Trish Shapiro

Circulation Assistant
Sharron Rierson

Production Manager
Madeline Price

Assistant Production Manager
Mary Barr Felker

Artists
Carol Bates
David Hauschild
Maurice Lydick
Matt Park
Bill Schmitt

Composition
Jay Jarrett
Kristi Kalb

President
Robert A. Searle

Vice President
Judy L. Rudrud

Controller
Mike Drake

Operations Manager
Cheryl Greenman

Published by

CARDIFF
PUBLISHING COMPANY, INC.

6530 S. Yosemite St.
Englewood, CO 80111
(303) 694-1522

VBPA

Member of Business Publications Audit of Circulations, Inc.

Please address subscription inquiries to:
RF Design, Cardiff Publishing Company,
P.O. Box 6317, Duluth, MN 55806
Postmaster: send form 3579 to the above address.

**50% smaller
than you'd expect
...available now!**

CTS Hybrid VCXO



Actual size:
.860" x .830" x .350"

**End the trouble of designing your oscillator—
now you can specify this highly reliable CTS component!**

Solve your space limitations and put an end to specifying a crystal and designing your own oscillator. This CTS hybrid VCXO comes in a package that is 50% smaller than usual—and you can simply specify and order the oscillator as you do any other component. Because CTS Knights Division *specializes* in precision crystal products, we have the largest staff of engineers in the industry. We even make our own crystals to assure precise uniformity.

This subminiature JKVXO-100 voltage

controlled crystal oscillator is available today, with the specs listed here. Or, if you have a special application, we will customize a design to meet your requirements. Either way, you'll get traditional CTS reliability at very competitive prices.

WRITE TODAY for full specifications on this CTS subminiature crystal oscillator. Contact: CTS Corporation, Knights Division, 400 Reimann Ave., Sandwich, IL 60548. Phone: (815) 786-8411.



Specifications JKVXO-100, Crystal Oscillator

Small Size	.860" x .830" x .350"
Wide Pullability	± 200 PPM minimum
Temperature Stability	0°C to +60°C ± 40 PPM
Center Frequency @ Room Temperature	+ 10 PPM when shipped

CTS® MEANS RELIABILITY


CTS CORPORATION • ELKHART, INDIANA



Series CCXO-140 Leadless Chip Carrier Crystal Oscillator for surface mounting. Phone: (815) 786-8411



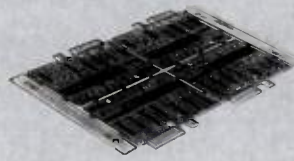
DIP Attenuator Switchable attenuator in standard DIP package. Phone: (317) 463-2565



Printed Circuit Boards Complex double-sided and multilayer styles. Phone: (415) 964-5000



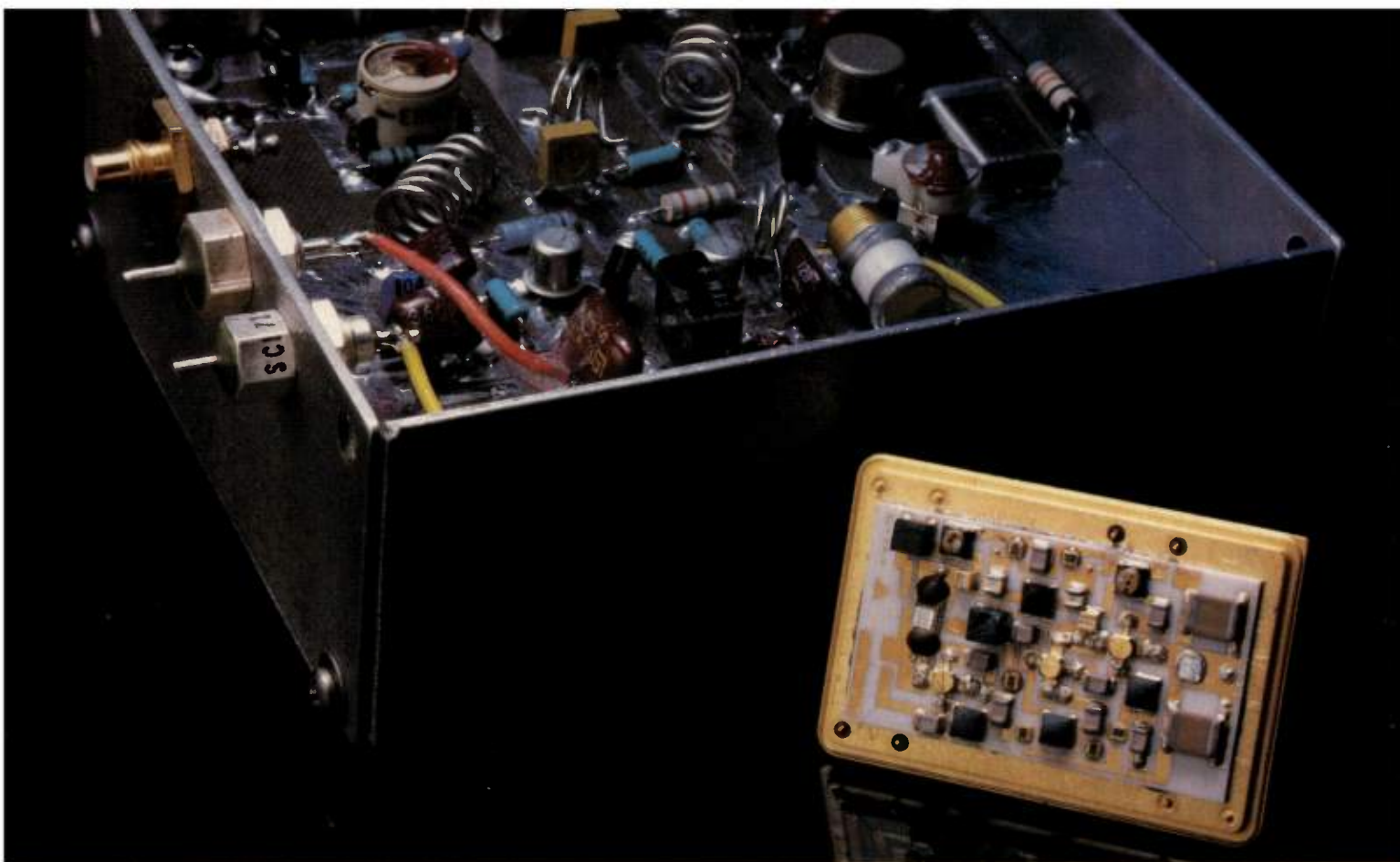Custom Crystal Oscillator with multiple integrated functions. Phone: (815) 786-8411



Until now, you had to go to great lengths to produce an oscillator this good.

Now you can simply buy a source-on-a-chip.

That's what an Andersen SAW oscillator is: a compact fundamental-mode device that operates from 100 MHz to 1.1 GHz without the need for multiplier chains. As a result you get superior performance in a fraction of the space, often at a lower overall cost.


Fundamentally Better

Since Andersen SAW oscillators are fundamental-mode devices, they produce a spurious-free signal. They are also alignment-free. No tuning or optimization is required.

These compact devices are also more rugged than any

comparable source. Just plug them into your system. They're available in standard industry packaging for PC mounting.

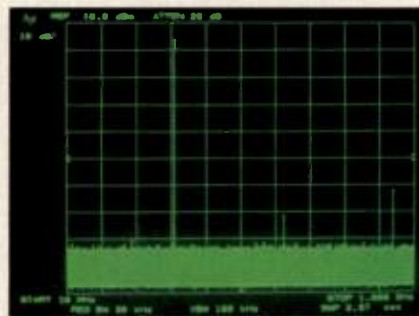Andersen SAW oscillators are the perfect source for hundreds of applications. They're



Frequency spectrum of Andersen Model SO-314-600-V Oscillator over 0 to 1 GHz range. Fundamental frequency is 314 MHz. Second harmonic is -65dBc, third harmonic is -55dBc. Spurious responses are essentially nonexistent.

also capable of functioning as VCO's. The output frequency can be modulated or locked to another reference for applications such as a PLL.

Make It Easy On Yourself

We'll supply oscillators to your specific frequency requirements without a tooling charge. We can do that because of our unique CAD SAW design facility—and the versatility of our oscillator design.

Save money, save time, simplify your circuit design. Incorporate an Andersen SAW oscillator in your system today. Send for more information right now. Or give us a call at (203) 242-0761.




ANDERSEN LABORATORIES

Andersen Laboratories, Inc., 1280 Blue Hills Avenue, Bloomfield, CT 06002 Telephone (203) 242-0761/TWX 710-425-2390
Andersen SAW products are available in the United Kingdom and Europe through our sister company, Signal Technology Ltd., Swindon, Wiltshire, UK.

INFO/CARD 7

MORE EMI/RF PROTECTION

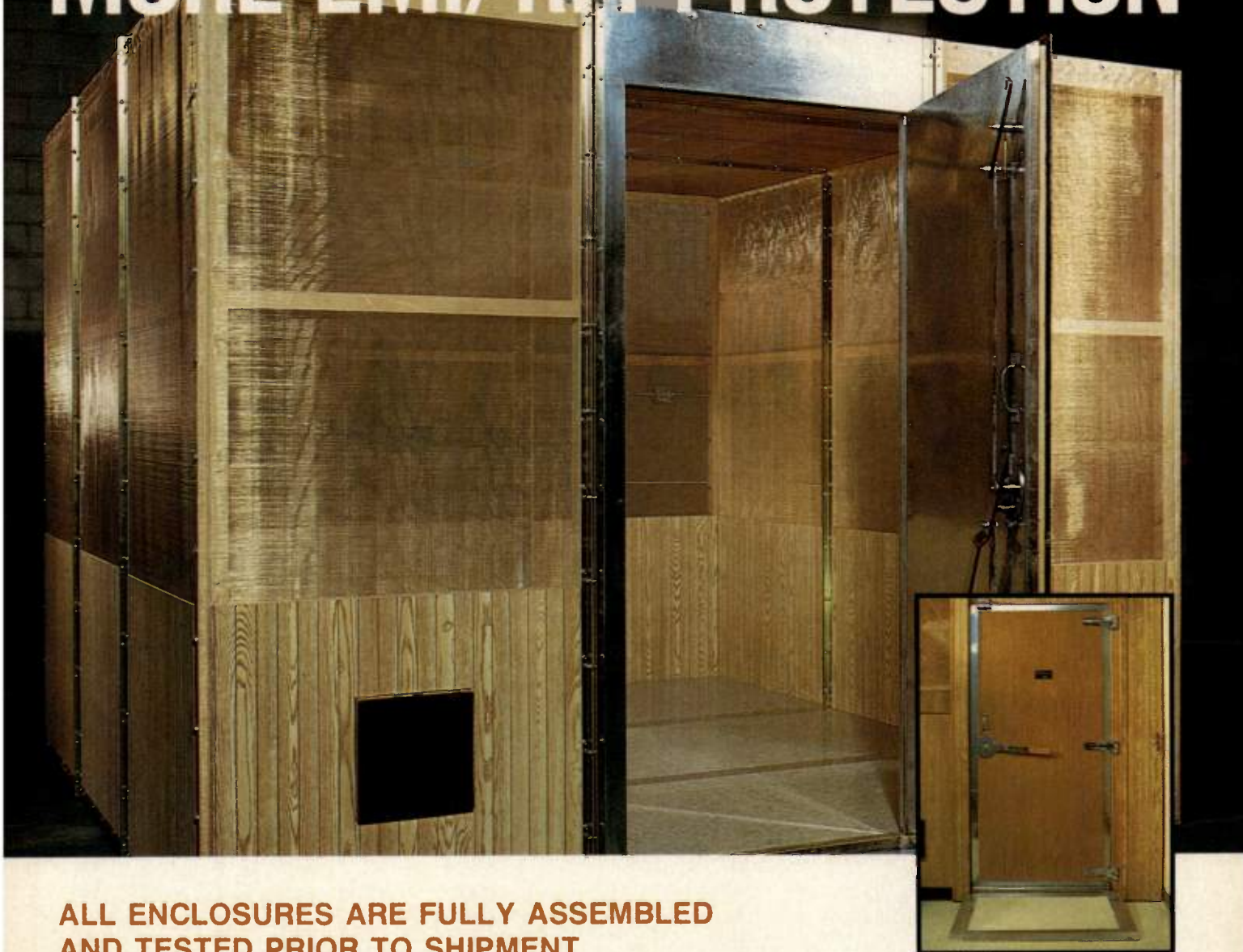

ALL ENCLOSURES ARE FULLY ASSEMBLED AND TESTED PRIOR TO SHIPMENT

Only Lindgren combines the proven superior performance of double-electrically-isolated (DEI) shielding with the benefits of modular room construction. Independent tests demonstrate that Lindgren's DEI design gives highest shielding efficiency in both low-frequency magnetic and high-frequency microwave fields.

Lindgren offers a complete line of modular enclosures, equipment cabinets, and custom RF rooms. Lindgren enclosures are offered in virtually all shielding materials, in all typical shielding thicknesses, in solid-sheet or screen, to cover all shielding requirements. Each enclosure is fully assembled at our plant before shipment, tested to verify RF integrity, and guaranteed to meet its attenuation specifications.

Patented overlapping pressure joints allow Lindgren enclosures to be easily assembled, rearranged, moved, expanded, partitioned, and reassembled again and again with no need for specially trained personnel.

To coordinate with your specific environment, Lindgren can also provide special interior/exterior finishing... soundproofing... suspended ceilings... recessed lighting... raised computer floors.

A wide range of options lets you custom-design your

enclosure with windows, access panels, manual or automatic sliding doors, wave guide feedthru, lights. RF connectors, fiber-optics, filters for power, signal and communication lines, emergency (panic bars) doors, permanent in place threshold ramps, and more.

The diversity of Lindgren enclosures has satisfied the needs of more than 5000 customers we've served over the last 30 years.

Next time you need a specialized shielded enclosure, make sure you get the superior performance of double-electrically-isolated design plus all the other Lindgren advantages.

Write or call today for full information or applications assistance.



**LINDGREN
RF ENCLOSURES**

1228 Capitol Drive—Addison, IL, 60101
(312) 628-9100



EIMAC cavities cover 54 to 970 MHz at power levels to 30 kW —our design or yours

Varian EIMAC has complete cavity design and production capability. We make sure that tube and cavity are compatible. If it isn't an off-the-shelf-item, we have the designers and engineers for any specific job.

EIMAC has expertise in all disciplines including pulse, CW, FM, and TV. We match tube, power,

bandwidth and operating mode to achieve optimum performance.

More information on EIMAC cavities and tubes is available in our Cavity Capability brochure from Varian EIMAC. Or for prompt consideration of your special design requirements, contact Product Manager, Var-

ian EIMAC, or the nearest Varian Electron Device Group sales office. Call or write today.

Electron Device Group
Varian EIMAC
301 Industrial Way
San Carlos, California 94070
415-592-1221

Varian A.G.
Steinhauserstrasse
CH-6300 Zug, Switzerland
Tel: (042) 23 25 75
Telex: 868-841

EIMAC Cavity	Matching EIMAC Tube	Tuning Range (MHz)	Power Output
CV-2200	4CX20,000A	86-108	30 kW
CV-2220	3CX1500A7	86-108	1.5 kW
CV-2225	4CX3500A	86-108	5 kW
CV-2240	3CX10,000U7	54-88	10 kW†
CV-2250	3CX10,000U7	170-227	10 kW†
CV-2400	8874	420-450	300/1250 W*
CV-2800	3CX400U7	850-970	225 W
CV-2810	3CX400U7	910-970	190 W

*pulsed power

†peak sync. or 2.5 kW combined in translator service





QUALITY & RELIABILITY **that stand the test of time**

AROUND THE GLOBE...

Along with offering the best performance/price in the industry, our goal at PTS has always been reliability. We believe, that with a yearly failure rate of 4%, we do indeed produce the most reliable synthesizer line.

It's easy to talk about a commitment to quality; at PTS we are actually doing something about it. We are backing that commitment by extending our warranty . . . **NOW TWO YEARS!**

Models covering 40MHz, 160MHz, 250MHz, 500MHz
Choice of resolution; low phase noise, fast switching,
fully programmable, BCD or IEEE BUS



NEW: Choice of table-look-up resolution with steady-phase switching.

PTS 500 shown with 0.1 Hz resolution,
frequency standard, 3×10^{-9} /day: \$7,750

Editor:

I enjoyed the "Frequency Synthesized Signal Generators" article in the November/December 1984 issue of *RF Design*.


I was dismayed, however, to find that Eaton Electronic Instrumentation Division's signal generator products were not included in the story, or the product briefs which followed, although I responded to your request for information.

I am sure the oversight was unintentional but, in the event you are planning future coverage of this product line, I have included data sheets descriptive of both the Model 460 AM/FM Φ M Signal Generator and the 360, 380 Series of Direct Synthesized Signal Generators for your future reference. The 380 Series is particularly exciting offering 20 microsecond switching to 4 GHz.

If I can ever provide additional information on Eaton's broad line of test and measurement instrumentation, please call me without hesitation.

Sincerely,
Patricia W. Ullrich
Marketing Communications Manager

Because of the large response from manufacturers to our call for new product information we must set limiting guidelines for our special reports. We attempt to keep our readers informed of the most recent product developments. A number of products were not included in the special report on "Frequency Synthesized Signal Generators" because they had been on the market long enough for most RF engineers to know of them. We welcome comments from manufacturers and readers on this subject. Readers wanting information about the products mentioned in Patricia Ullrich's letter may circle info/card #177. — editor

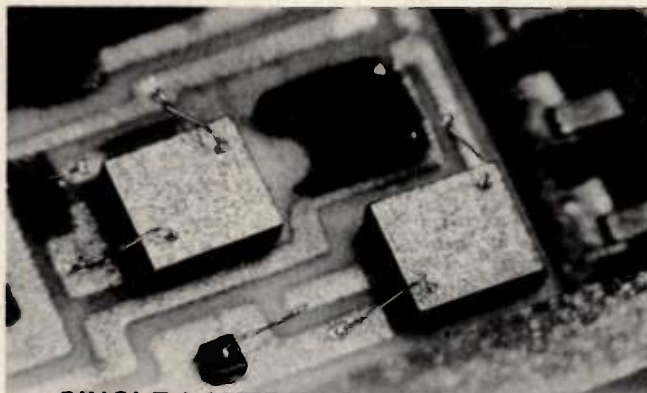

SINGLE LAYER PARALLEL PLATE CERAMIC CAPACITOR CHIPS

Featuring a single layer dielectric construction with associated low series inductance, this family of capacitor chips are ideal for applications ranging from DC to microwave frequencies.


Available in capacitance ranges from 0.25 pf to 15,000pf voltage ratings to 15KV, their high dielectric strength makes them resistant to damage from static discharge. Precious metal terminations are compatible with epoxy, solder or wire bonding assembly techniques.

**JOHANSON
DIELECTRICS** 

2220 SCREENLAND DRIVE, BURBANK, CALIFORNIA 91505
(818) 848-4465 TWX 910-498-2735

INFO/CARD 18

DALE MEASURES UP to your TCXO NEEDS.

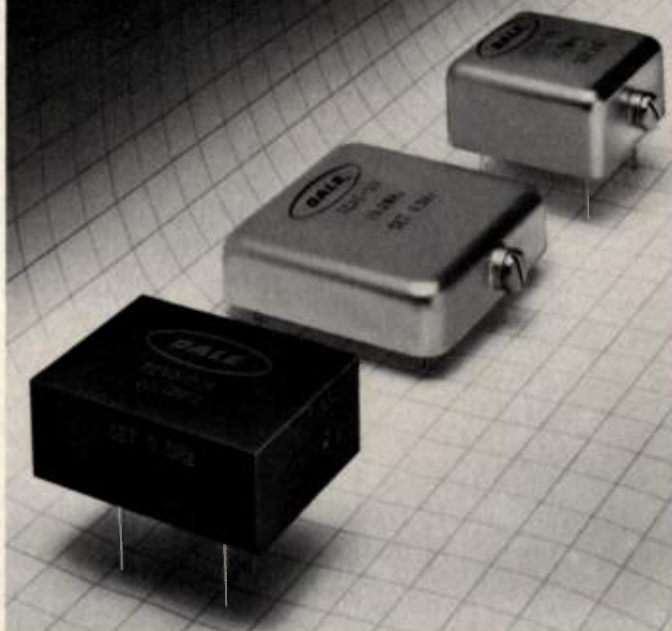

Check our expanded line of temperature compensated crystal oscillators. It includes both military and commercial models in frequently specified styles — with stock frequencies available fast! Here's a quick look at our lineup, including the new hermetically sealed TCXO-30 and TCXO-32 now in production.

Model No.	TCXO-22	TCXO-24	TCXO-26	TCXO-30	TCXO-32
Freq. Range	3 MHz to 15 MHz				
Stock Freq.	4, 5, 10 MHz				
Stability vs Temp. (PPM°C)	$\pm 1, \pm 5$ (0 to +55°C)		± 1 (0 to +70°C)	± 3 (-40° to +85°C)	± 1 (-40° to +85°C)
Case Style	Epoxy		Metal with Hermetic Seal		

Contact Dale today for complete price and delivery information, plus assistance with custom models.
Phone 602-967-7874



Dale Electronics, Inc., 1155 West 23rd Street, Tempe, AZ 85282

INFO/CARD 11

HIGH PERFORMANCE AM/FM DEMODULATOR

- Choice of IF
- High Intercept Point
- IEEE-488 Control
- Compact—1 $\frac{3}{4}$ " high

REACTION INSTRUMENTS
RESTON, VA

MODEL 701 AM/FM DEMODULATOR

Reaction Instruments' Model 701 AM/FM Demodulator accepts an IF input which is demodulated in high performance FM and AM demodulators. Front panel controls allow selection of AM/FM demodulator, IF/Video/Audio gain, IF/Video bandwidth, and AGC/MGC. Filter bandwidths regularly available range from 0.5 to 36 MHz, and up to 4 IF filter bandwidths are optionally available. All functions are under IEEE-488 control.

The Model 701 AM/FM Demodulator is housed in a standard 1 $\frac{3}{4}$ inch high rack-mount chassis.

IF	160 MHz (Std.)	BW	0.5 to 36 MHz
IP3	+30 dBm	Disc. Linearity	+/-2.5%

For further information, please call or write to:
Marketing Department, Reaction Instruments,
1930 Isaac Newton Square, Reston, VA 22090
PHONE (703) 471-8060, TWX 710 833 9031

**REACTION
INSTRUMENTS**

INFOCARD 12

Sweet Smell of Success at RF Technology Expo 85



Even the night before it opened, at a crowded VIP reception in one of the Disneyland Hotel's posh ballrooms, exhibitors and speakers were congratulating executives of sponsoring Cardiff Publishing Company, *RF Design* magazine staff members and each other. Cardiff president Robert A. Searle, veteran of many such shows, said late that night, "They're declaring it a success before it happens. When they do that it's a good sign."

The stage was set. In the exhibit hall 60 exhibits were poised in 75 booth spaces. Elsewhere in the complex five large rooms were set up for the concurrent technical sessions accommodating the 71 papers to be given at the first RF TECHNOLOGY EXPO.

Shortly after dawn the next day, long before registration desks opened, the line of attendees began to form. The hundreds who already had registered by mail were there just to pick up their badge and program, but they were joined by hundreds starting from scratch.

The final attendance figure was 1,300, plus 400 exhibit personnel and speakers, and as Convention Manager Kathy Kriner said, "Nobody expected them show up all at once!"

The opening day jam-up was alleviated by dispatching those who were there for the Fundamentals of RF Design course directly to the classroom sans admission, to return for registration at the noon break.

In the hotel's huge Embassy Room, classroom for the fundamentals course, instructor Les Besser was staggered as an overflow crowd topping 400 poured into a space set up for 350. Adapting admirably, the president of Microwave Educational Programs held the jammed-in crowd spellbound through a four-hour lecture on Small Signal Amplifier Design.

In mute testimony to the value of the material they were receiving, the crowded participants sat silently and seemingly motionless as instructor Besser revealed the mysteries of what others have called the "Black Art." The art became a science.

In other rooms, some almost as crowded, three papers were being given concurrently, truly offering something for everyone. Attendees could go from room to room, from topic to topic, picking up the particular knowledge needed for the job back home. Four papers were delivered in each room.

Registration continued through the morning, as exhibitors prepared for the noon opening. Many of them later said they were not prepared for the number and caliber of people who crowded their booth constantly until the exhibits closed at 6:00 p.m.

"Every person I talked to was a qualified customer," was a common remark from exhibitors.

Many discovered they had brought too few people to talk to the visitors and too little printed material to hand out. Frantic calls went out for help and literature. Business cards became unexpectedly scarce items.

While attendees enjoyed lunch at the variety of famous restaurants in the hotel complex, hotel employees expanded the Embassy Room to provide comfortable seating for the extra 100 in the Fundamentals class. University of Colorado Professor K.C. Gupta started the afternoon session with a detailed explanation of striplines and microstriplines. He was followed by Joe Johnson, president of Microwave Modules and Devices, explaining high power amplifier design: John Morton, engineering manager for Microsonics, Inc., who gave an overview of oscillators; and Carl Erickson Jr., with a complete description of surface acoustic wave devices.

From the silence that prevailed all day the intensely concentrating crowd of 400 could have been a group of six. Very few had left by the end of the session, and those who left may have gone to catch a particularly interesting presentation in one of the other sessions.

When all papers had been presented most attendees gathered at the exhibit hall for free refreshments and relaxed conversation. Even now the exhibit booths were crowded, although the pace was slower. Some exhibitors had made thousands of dollars worth of unexpected sales that afternoon. They were pleasantly tired, not just from the constant flow of visitors to their booths but also from the depth of the questions they had to answer.

"You were smart to only open the exhibits from noon to 6:00," one exhibitor told *RF Design* publisher Keith Aldrich. "I don't think we could have taken this all day."

Attendance at the RF Fundamentals course was even larger the second day. Once again the room was expanded as


NEC

SOLUTION SOURCEBOOK #2: Small Signal Bipolars


Too often, design engineers are forced to use several device suppliers, juggling cost, performance, reliability, and availability.

Here is the single source solution from NEC: a wide range of small signal bipolars that offer better reliability at a lower cost, high gain with low noise, and the confidence of designing with NEC.

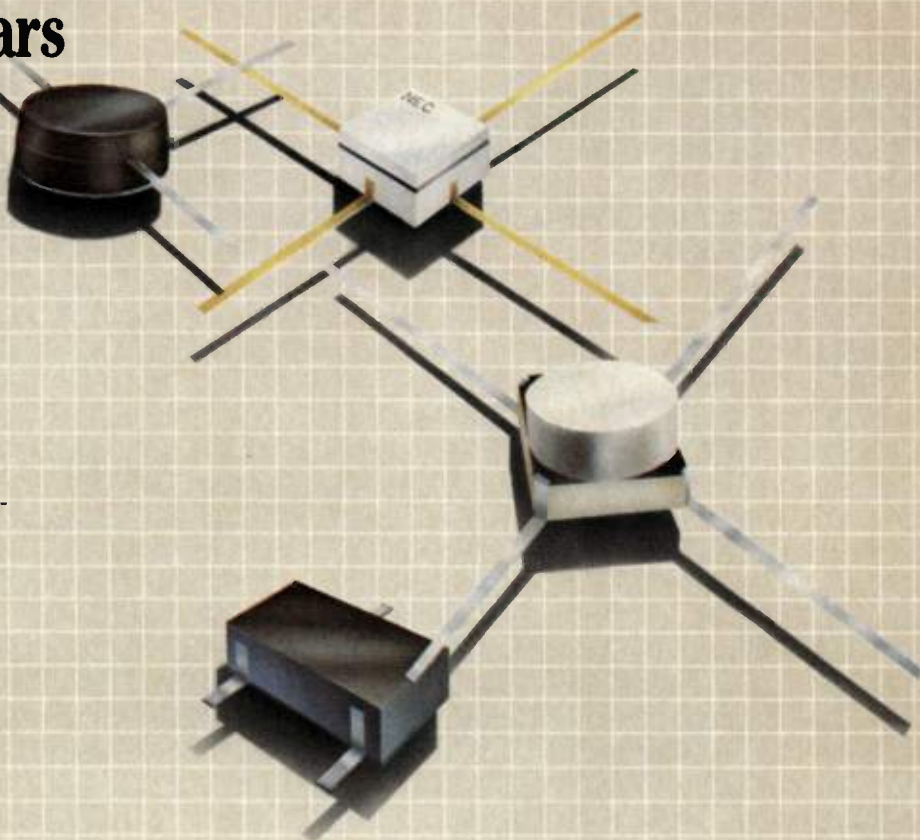Call your nearest regional sales office listed below for detailed information. NEC, the reliable source for complete solutions.



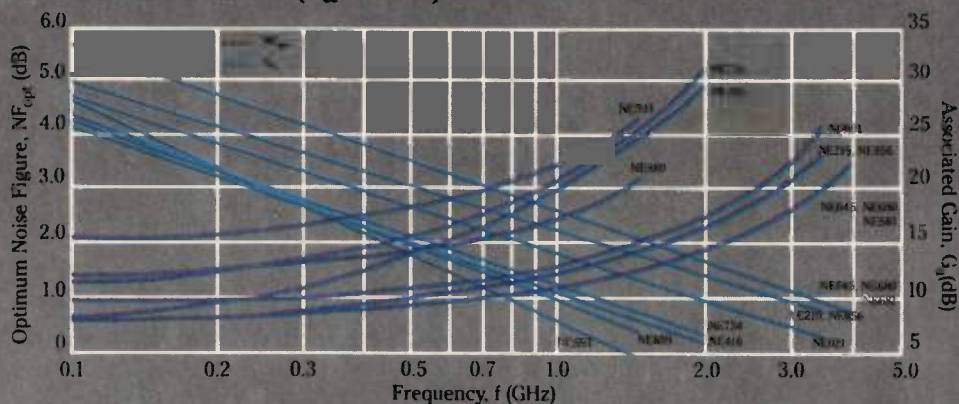Performance Curves ($T_a = 25^\circ\text{C}$)



CALIFORNIA EASTERN LABORATORIES, INC.—U.S. and Canada

Exclusive sales agents for **NEC Corporation**, Microwave Semiconductor Products.

Western Regional Office • 3260 Jay Street • Santa Clara, CA 95054 • Tel: (408) 988-3500 • Tlx: 346-393 or 171-197

Eastern Regional Office • 12 Galloway Avenue • Cockeysville, MD 21030 • Tel: (301) 667-1310

Midwestern Regional Office • 1101 E. Arapaho, Suite 145 • Richardson, TX 75081 • Tel: (214) 437-5487

In Eastern Canada Contact: Ballinger Microwave Canada Inc. • 301 Moodie Drive, Suite 108 • Nepean, Ontario, Canada K2H 9C4 • Tel: (613) 726-0626

In Europe Contact: NEC Electronics (Europe) GmbH • Oberrather Strasse 4 • 4000 Düsseldorf 30 • West Germany
Tel: 0211/650301 • Tlx: 841/8581353 or 8587419



hotel employees removed walls and brought in chairs. When they had finished, nearly 500 chairs were occupied.

It was remarkable that in spite of the last minute rearrangement of the room, leaving about 100 without tables to write on, there were no complaints. Those who were there considered themselves lucky to receive the information, regardless of the circumstances.

As many as 200 attended some of the

other sessions, covering the general topics of circuits, transmitters, computer-aided design, antennas, techniques and components. Sessions were arranged both days so conference attendees could go from room to room and hear papers on each topic. RF TECHNOLOGY EXPO registration badges could be seen everywhere in the hotel complex as attendees went from session to session or to the exhibit hall.

His work was over, but program chairman Andy Przedpelski could be seen many places during the EXPO, going to sessions or touring the exhibits or just joining one of the many spontaneous discussion groups that seemed to develop wherever attendees came together. He had put together a valuable program, and now he could enjoy and benefit from it along with those he had done it for — the RF designers who came from as far away as China and Israel to attend.

It was no surprise to the staff that 360 copies of the proceedings had been ordered by those in attendance, or that 67 percent of the exhibitors said they definitely would be back for EXPO 86. Another 30 percent said they probably would be back. One who said he probably would not return said his products were "too microwave" for the attending engineers. He said most of those he talked to worked in frequencies "from 2 GHz down."


Of course, that was the idea of the RF TECHNOLOGY EXPO. It was the first show held specifically for engineers working from 2 GHz down. But Cardiff officials say it won't be the last one.

Keith Aldrich said, as the show was closing Friday morning, "This phenomenon confirms the premise of the show — that there is a desperate need for RF engineering information that is not being met, among engineers who have been pressed into service without adequate training in RF."

Dates and site of the RF TECHNOLOGY EXPO 86 will be announced in next month's issue of *RF Design*.

Dow-Key Becomes Subsidiary of Kilovac

Dow-Key Microwave Corp. was incorporated Jan. 2, as a wholly owned subsidiary of Kilovac Corp., Carpinteria, Calif. Sales manager Jack Dysart announced the company's new status at a news conference at RF TECHNOLOGY EXPO 85. The company previously had been a division of Kilovac involved in the design and manufacture of coaxial relays and switches for the RF and microwave communications, radar, electronic warfare and test equipment markets. The company recently moved into a large facility in Carpinteria with class 100,000 clean room facilities and MIC capability.

Dysart said the company is introducing the concept of intelligent relays which integrate higher levels of digital, analog and microwave integrated circuits into their existing line of electromechanical switches designed to meet Mil-S-3928. 

Bliley



**We grow the quartz.
We process the crystal.
We design, build and
test to the toughest
MIL standards.**

**And this integration yields consistent
and reliable frequency control.**

• Quartz Crystals • Crystal Oscillators • Free Catalog

The First Name in Frequency Control for Your Circuit.

BLILEY ELECTRIC COMPANY

2545 West Grandview Blvd.

P.O. Box 3428, Erie, PA 16508

(814) 838-3571

TWX 510-696-6886

LOOK AGAIN.



**You're missing plenty if
"rubber duckies" are all you see
when you look at Centurion.**


Our Tuf-Duck™ flexible antennas ("rubber duckies") have enjoyed such success over the last few years that we're beginning to wonder if people might not forget about the other things we do.

In addition to manufacturing a very popular line of replacement antennas and batteries for portable radios, we've worked hard to establish ourselves as a supplier of components and services to OEM's. In many cases Centurion has been called on to provide expertise in several areas, from design and development through final production.

If your firm is involved in the design or manufacture of portable radio equipment or similar products, chances are good that we can be a positive asset to your efforts. We hope you'll look our way for dependable components and services delivered on a timely basis at very competitive rates, including:

- Design, development and manufacturing of radio accessories
- Tuning correlations for special antenna applications
- Cellular radio accessories Miniaturized antennas (UHF & VHF)
- Design, development and manufacturing of battery packs
- Injection molding and vacuum forming Sonic Welding
- Tool & die manufacturing and design (plastics)
- Secondary assembly operations
- Technical and manufacturing consultation

 **CENTURION**
INTERNATIONAL, INC.

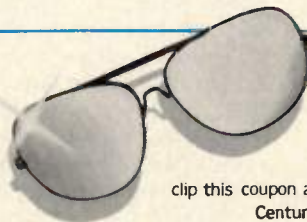

**Maybe new glasses
would help?**

Radio design and manufacturing engineers are invited to clip this coupon and send it to us along with their business card. In return, Centurion will send you a **free** pair of great-looking sunglasses!

Name _____

Job Responsibilities _____

P.O. Box 82846 • Lincoln, NE 68501 • Toll Free 800/228-4563

Centurion International reserves the right to verify eligibility. Please allow 4-6 weeks for delivery.

INFO/CARD 15

New Waves In Oscillator Design

By James N. MacDonald

It starts with an amplifying device, usually a semiconductor. Part of the current is tapped from the amplifier output and fed back into the input. This feedback current is passed through a circuit designed to be resonant at a specific frequency. The resonant frequency within the band of frequencies in that current is again boosted by the amplifier and the process is repeated. If the amplifier provides sufficient gain and the current remains in phase, the circuit oscillates continuously at that frequency. This is the common oscillator circuit.

There are three types of oscillator circuits in general use by RF engineers, and nearly all receiving and transmitting systems as well as many other devices use one or more of each type. The types are based on inductor-capacitor (LC) circuits, crystals and surface acoustic wave resonators (SAWs). All types are widely used and new designs are being developed regularly from each type.

When first developed each type of circuit represented a new wave in oscillator design. The next new wave, described later in this report, will probably combine microprocessors with analog oscillator circuits. Between these major developments improvements have tended to involve better manufacturing methods, resulting in smaller and more stable devices to meet increasingly rigorous military and commercial requirements. Engineering design improvements have made the better manufacturing methods possible.

This report will discuss some of the latest developments in oscillators designed to operate primarily in the lower RF frequencies (through UHF). The distinction is difficult to make since design and manufacturing improvements are steadily extending the operating ranges of crystal and SAW oscillators. In general, we will not discuss atomic standards and oscillators designed to operate primarily above 2 GHz.

LC Circuits

The LC circuit is the first oscillator circuit learned by an RF designer. A coil and a capacitor connected in an AC circuit will resonate at a certain frequency determined by the reactance of each component. The resonant frequency is reinforced by the coil and capacitor, while other frequencies meet impedance. It is a simple circuit and relatively easy to

design. The many improvements that have been made in this type of oscillator have depended mostly on the creativity of circuit designers. The LC circuit, sometimes called the tank circuit, can be used at any frequency, but in and above the UHF frequency range the electrical characteristics of inductors and capacitors begin to change and circuit design becomes more complex. At higher frequencies discrete components are replaced by thin-film deposited on small circuit boards or by cavity resonators.

The LC circuit with discrete coils and capacitors often is the only practical oscillator for low-priced, low frequency equipment where size is not a major consideration. A problem with this circuit is frequency instability in environments of wide temperature variation and physical shock. However, the LC circuit is still the choice of many RF designers in applications where these disadvantages are not significant or can be compensated for.

Quartz Crystals

For many years the quartz crystal oscillator has been the workhorse of the industry. A piece of quartz crystal will vibrate when AC voltage is applied across it. The frequency of vibration depends on the dimensions of the crystal piece, a slice from a naturally formed crystal. Current alternating at the natural vibrating frequency of the crystal will be in resonance with the crystal. The crystal functions like an LC circuit in a single element.

Held between metal electrodes the quartz crystal acts like a capacitor. It has very high Q and, consequently, good frequency selectivity.

Quartz crystal oscillators are also highly stable, holding on frequency under physical shock that might change the resonating frequency of an LC circuit. However, the resonant frequency of a crystal changes as its temperature changes. Since electronic equipment often is subjected to wide temperature variations, this tendency must be compensated for.

Frequency-temperature changes can be reduced by controlling the oscillator temperature, varying oscillator tuning voltage or using a phase lock loop. The PLL has been discussed in several previous articles, so it will not be discussed here. Oscillator temperature can be controlled by containing the oscillator in an "oven," a metal chamber kept at a con-

stant temperature. Tuning voltage can be varied by a thermistor network reacting to oscillator temperature changes.

This issue's cover features Motorola's new line of temperature-controlled crystal oscillators. As the latest addition to their line of hermetically sealed oscillators, the MDO-3 offers ± 5 ppm frequency stability over a -30 to $+70^\circ$ temperature range, company officials say. This stability is said to be inclusive of variations in temperature, voltage, load and humidity. Measuring 0.82 in. x 0.52 in. x 0.32 in. with DIP compatible pin out, this oscillator is said to be ideal for those applications in which low cost and small size are required. Motorola claims aging rates for this oscillator of ± 1 pp.m

The MDO-3 operates from a 5 volt power supply over a frequency range of 10 to 20 MHz. It uses the AT-Strip crystal to achieve reductions in size and improvements in mechanical shock survivability over previously offered designs. The all-metal welded package provides a full hermetic seal which minimizes RF radiation while keeping the oscillator on frequency in environmental extremes of temperature and humidity.

The MDO-3 can be adjusted through the use of an external potentiometer, or it can be electronically tuned, providing AFC capability. Motorola says the automated manufacturing, proprietary thick film hybrid design and use of the AT-Strip quartz crystals have resulted in reduced parts count for cost savings with improved field reliability.

These are the kinds of improvements crystal oscillator manufacturers are making.

Often the designer wants the oscillator circuit frequency to be variable. This can be done by changing the capacitance of the circuit, either mechanically, with a variable capacitor, or electronically, with a varactor.

At the higher frequencies the crystal is so small and thin it is subject to breakage from its own vibrations. To avoid this problem crystal manufacturers obtain higher frequencies from a harmonic overtone of a crystal that resonates at a lower frequency. A frequency multiplier is used to select and amplify this harmonic overtone.

An analysis of new products recently announced shows that crystal oscillator manufacturers generally are striving for high stability, low power consumption,

small size and fast warm-up.

Greenray Industries' new digitally compensated crystal oscillator is said to offer frequency-temperature stabilities approaching those of ovenized oscillators while consuming only a small fraction of the input power required to operate an oven. The advantage, Greenray says, is that the oscillator is on frequency instantly, eliminating the wait for an oven to stabilize.

The angle at which a slice is cut from a crystal is one of the factors determining its frequency-temperature stability, and many different cuts are used. CTS Corp., Knights Division, says their relatively new doubly-rotated S-C cut crystal resonator provides fast warm-up and excellent temperature and long-term stability in an ovenized oscillator. They say their TCXO design can consistently be produced to less than $\pm 4 \times 10^{-7}$ over a -55 to $+85^\circ$ temperature range for the life of the oscillator, even after the center frequency has been adjusted to account for aging.

As a custom manufacturer, CTS/Knights reports receiving more than a few inquiries for such devices as:

A small, low power, fast warm-up ovenized oscillator that can withstand the severe environments encountered in tactical jet fighters;

An oscillator packaged and mounted to permit mechanical shock operation of 3000 Gs;

A synthesized multiple-output device using monolithic VCOs to lock to a stable ovenized reference;

A leadless chip-carrier crystal oscillator — a complete quartz crystal oscillator in a ceramic chip carrier package.

CTS/Knights considers the requirements described above to be among the factors determining the future of the quartz crystal oscillator market.

Seiko Instruments has developed a series of oscillators using a GT-cut crystal, which company officials say provides good frequency-temperature characteristics. Seiko says it has developed a photolithographic fabrication process that permits the high-accuracy dimensioning required to mass produce the GT-cut.

Wenzel Associates has developed a small, low power ovenized oscillator they call the Small Fry. Officials say the Small Fry uses a 3rd overtone crystal which provides aging of 5×10^{-10} per day, with close in phase noise that can be specified to -135 dB at 10 Hz for 10 MHz oscillators. They attribute the performance to a tiny vacuum flask that insulates the oven and provides a five-fold improvement in thermal conductance over conventional foam and to a low flicker crystal exciter design.

The Vari-L Company has just announced a new line of voltage controlled oscillators covering frequencies as low as 25-50 MHz. The company says the low power dissipation, less than 200 mW, helps them meet rigid military specifications of -55 to $+100^\circ$.

These are a few of the new developments announced recently. They are examples of the kinds of improvements many quartz crystal oscillator manufacturers are making in their products. Designers are urged to contact all manufacturers for information before specifying a product.

Designers specifying crystal oscillators should be familiar with a recent study by V. Rosati, S. Schodowski and R. Filler of the Electronics Technology & Devices Laboratory, Fort Monmouth, New Jersey. Oscillator vendors were asked to identify two temperature-compensated crystal oscillators for testing, one to meet certain specifications and the other to be their best available TCXO. A total of 105 oscillators were tested for frequency-voltage, frequency-load, frequency-temperature and aging. The researchers asked for moderate (5.0 ppm) or high (0.5 ppm) stability oscillators.

Oscillators in the 1-5 ppm stability range were found to conform to manufacturers' specifications, but long-term aging characteristics were widely variable. A significant percentage of those between 0.5 ppm and 1 ppm were found to be out of specification. No correlation between price and performance was found. The researchers concluded that system designers should carefully specify and test TCXOs before designing them into systems and supporting data should be requested for each oscillator being considered in the 0.5 ppm class.

Reporting the study results, the laboratory's Frequency Control branch chief, J.R. Vig, said "historically the accuracy of quartz oscillators has improved by an order of magnitude approximately every seven to 10 years." He said he expects the rate of improvement to continue.¹

Vig said he expects revolutionary improvements in TCXOs from the use of microcomputers and "dual-mode" techniques. He said a dual-mode device measures crystal temperature without using an external sensor. The temperature-frequency profile of a crystal is stored in a dedicated microcomputer chip that controls compensation as a function of crystal temperature. Vig predicted frequency-temperature stability of 5×10^{-9} by 1990, with designs that are one-third smaller and use one-third as much power as current TCXOs.

SAW Devices

At frequencies above 100 MHz Surface Acoustic Wave (SAW) devices have a cost and a size advantage over quartz crystal oscillators, which need frequency multipliers, and a frequency stability advantage over LC circuit oscillators.

A typical SAW resonator consists of thin metal strips laid or deposited on a thin substrate, usually of quartz or lithium niobate. High frequency AC voltage across the strips creates surface waves along the face of the crystal. Because of the piezoelectric effect of the crystal the surface waves are detected by other strips on its surface. The principal feature of the SAW resonator is that the surface waves travel many times slower than the electromagnetic waves causing them. This frequency reduction feature allows SAW resonators to handle frequencies up to 1 GHz. Because they can work directly in higher frequencies, SAW oscillators avoid non-harmonic spurious outputs that are a problem with crystals and frequency multipliers.

SAW devices can be designed with taps at any point for multiple use of the oscillating signal. They are often used in hybrid modules and components because they are so small.

The major problems with SAW devices are frequency drift as the crystal substrate ages and contaminants introduced in the manufacturing process. Aging can be compensated for as quartz crystal resonator aging is compensated for. The amount of contamination depends on the care taken when the SAW device is made. SAW devices must be hermetically encased. Water vapor condensing on the surface of the substrate could slow the surface wave and might mix with contaminants to form acids that could etch the surface, changing its wave propagation characteristics.

Trends in SAW oscillator design are toward higher frequencies and better temperature stability. The higher frequencies (mass production above 400 MHz) are aimed at the cellular radio and microwave link markets. Better temperature stability will probably be achieved by using different materials.

Andersen Laboratories uses a SAW delay line as the frequency controlling element in their standard hybrid oscillator. They say their oscillators are capable of operating at fundamental frequencies in the VHF and UHF ranges and beyond, reducing the need for frequency multipliers and post multiplier filtering. The oscillator signal is coupled out of the loop by a power divider and further isolated from the load by the output amplifier, which minimizes load pulling.

THE NEW WAVE IN AC POWER SOURCES



BEHLMAN KB SERIES OF INTELLIGENT AC POWER SOURCES...

NEW... because the KB Series offers more than just programmability — they're INTELLIGENT. You can perform a wider range of tests and do them faster, while eliminating costly test equipment, and simplifying ATE systems.

BETTER... because KB Series AC power sources let you throw away costly voltmeters, ammeters, and frequency counters. They're all built-in, measuring outputs independent of programmed values. We tossed in self-diagnostics and now you have a combination guaranteed to make your job easier, simpler and more productive.

BEST... because you never have to worry about load power factors, borderline power ratings or overloads. All Behlman AC power sources will operate into zero power factor loads at rated voltamperes, or into unity power factor loads at 50% over their rated power — all day long. Automatic overload and short circuit protection removes the bother of overload concerns.

COMPLETE MEASUREMENTS & DIAGNOSTICS

- Measurements of outputs independent of programmed values
- Self-diagnostics
- Stand-alone or computer controlled
- IEEE-488 (Listener/Talker) and others

WIDE RANGE OF MODELS

- 45 Hz to 10,000 Hz
- 100 VA to 54 KVA power ratings
- One, two, and three phase outputs

BEHLMAN QUALITY PRODUCTS SINCE 1968

- Intelligent KB Series AC power sources
- Programmable AC power sources
- Standard AC power sources
- Uninterruptible Power Systems

Call or write for KB Series information and our complete AC power catalog.



BEHLMAN
Engineering Corporation

Electronic Energy Conversion Sources & Systems

(805) 684-8311

1142 Mark Avenue
Carpinteria, CA 93013

Avantek, Inc., is working on development of integrated subassemblies at the substrate level, combining thin-film oscillators, switches and monolithic amplifiers into an oscillating unit that can be tuned over several octaves. They expect to be in production by the end of the year.

Only a few of the many reputable oscillator manufacturers have been mentioned in this report. It was not our intention to present a complete report on all available manufacturers or devices. Such a report would be incomplete the day it was published because new designs or improved devices are being announced almost weekly. Only by reading new product announcements and literature from manufacturers can the designer keep well informed.

Designers may obtain specific information about currently manufactured oscillators by circling the following Info/Card numbers.

Crystal Oscillators

- Austron — Info/Card #130
- Aydin Vector — Info/Card #129
- Bliley Electric — Info/Card #128
- Cinox — Info/Card #127
- CTS/Knights Div. — Info/Card #126
- Dale Electronics — Info/Card #125
- Frequency Control Products — Info/Card #124
- Frequency Sources — Info/Card #123
- Greenray Industries — Info/Card #122
- Hewlett-Packard — Info/Card #121
- K&L Quartztek — Info/Card #120
- McCoy Electronics — Info/Card #119
- Merrimac Industries — Info/Card #118
- Microsonics — Info/Card #117
- Motorola, Inc. — Info/Card #116
- Piezo Crystal — Info/Card #115
- Piezo Technology — Info/Card #114
- Seiko — Info/Card #113
- Signetics — Info/Card #112
- Sokol — Info/Card #111
- Vectron Laboratories — Info/Card #110
- Wenzel — Info/Card #109

SAW and Other Types

- Alpha Industries — Info/Card #108
- Andersen Laboratories — Info/Card #107
- Avantek — Info/Card #106
- Crystal Technology — Info/Card #105
- Phonon — Info/Card #104
- RF Monolithics — Info/Card #103
- Sawtek — Info/Card #102
- Teledyne — Info/Card #101

Footnotes

1. Phillip J. Klass, "Advances Forecast in Crystal Oscillators," Aviation Week and Space Technology, Nov. 28, 1983, pp 148-149.



March 1985




SAW Oscillators

Sawtek's Surface Acoustic Wave oscillators for military and commercial applications simplify design and improve noise performance. High-Q SAW resonators offer quartz stability at fundamental frequencies from 100 MHz to 1250 MHz. Hybrid oscillators in hermetic packages are available for reduced size and increased reliability. FM or pulse code modulation capability is optional.

Sawtek maintains a large selection of frequencies from an inventory of pre-tooled resonator crystals and new designs can be tooled rapidly. Our engineers also offer assistance in oscillator design for specific applications and are prepared to help evaluate the

suitability of SAW oscillators for your requirements.

In addition to oscillators and resonator products, Sawtek produces other high performance SAW components including bandpass filters, delay lines, and pulse compressors for cable television, satellite communications, modems, radar, EW, and many other signal processing applications. And, if what you need is not among our hundreds of standard products, we can provide technical assistance and rapid response to new design and production requirements. Quality and performance have made Sawtek the industry leader in SAW technology; you can rely on us for the total engineering support you need.

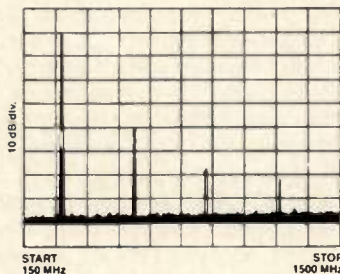

***When your system demands the advantages of
SAW Technology. . . Demand SAWTEK.***

SAWTEK
INCORPORATED

P.O. BOX 18000, DEPT. MRF, ORLANDO, FL 32860. (305) 886-8860
TLX: 514083 TWX: 810-862-0835

INFO/CARD 17

Controlling Radiated EMI From Digital Systems

By W. Scott Bennett
Hewlett-Packard Company
Ft. Collins, Colo.

Radiated electromagnetic interference (EMI) from digital systems results from the poor design — or lack of design — of current-path geometries in digital systems. In digital circuits, if the path followed by each return current is not effectively the same as the path followed by its associated forward current and the current has RF Fourier components, unacceptable levels of radiated EMI will almost certainly result. This can be predicted from the expressions for the electric and magnetic fields of a small loop antenna⁽¹⁾, both of which are directly proportional to the area bounded by the loop. Current loops in a digital system are not all necessarily "small;" however, the fields of any large current loop can be equivalently represented as the superposition of the fields from a number of smaller current loops having the same perimeter as the large loop. Thus, to effectively control radiated EMI from digital systems one must effectively reduce the areas bounded by the current loops in such systems.

A coaxial cable, for example, can make the effective area enclosed by its current loop equal to zero. At every point external to the cable there are two components which make up the electric field and two components which make up the magnetic field. In each case, one component is due to the (forward) current in the inner conductor and one component is due to the (return) current in the outer conductor. However, because the conductors are coaxial the field components result from currents which are coaxial as well. The forward and return currents appear to be following the same path but they are oppositely directed. If, at each point on the path the currents are equal and oppositely directed, at each point outside the cable the net fields due to the currents are zero.

A simple method for reducing current loop areas on a printed circuit (PC) board is to make one full layer of the board a

ground plane. Return currents will then tend to follow the same paths in the ground plane as their associated forward currents follow in adjacent layers. The distance between each forward current path and its return current path will then be the distance between the layer of the forward current trace and the layer of the ground plane. Thus, all current loop areas on the board will tend toward zero and radiated EMI due to those loop areas will tend toward zero as well. This same technique can be applied to flat multi-conductor cables which connect one PC board to another.

To obtain a quantitative understanding of the importance of minimizing current loop areas, consider the following equation:

$$A = 58.9 \frac{E_d}{f^2}$$

in which A represents current loop area in square inches, E represents electric field strength in microvolts/meter, d represents distance from the loop in meters, f represents the frequency of a current component in Megahertz and I represents the amplitude of a current component in milliamperes. This equation was derived from the expression for the maximum electric field of a small current loop, assuming the loop is positioned over a large conductive ground plane. It provides a good worst-case approximation of the electric field that would be observed from such a loop when measured according to FCC specifications⁽²⁾.

Now, suppose one wishes to know the loop areas which are associated with the FCC Class A and Class B radiated EMI limits for digital devices at 200 MHz. At that frequency the Class A limit is an electric field strength of 50 $\mu\text{V/m}$ measured over a ground plane at a distance of 30 meters and the Class B limit is an electric field strength of 150 $\mu\text{V/m}$ measured over a ground plane at a distance of 3

meters⁽²⁾, (3). From the above equation, the loop area associated with the Class A limit for a 1 mA current component at 200 MHz is 2.2 in² and the loop area associated with the Class B limit for the same current and frequency is 0.66 in². It should be clear from the small sizes of these areas that current loop areas *must* be minimized by digital designers if the FCC regulations are to be met.

Finally, since the current loop areas associated with the FCC radiated EMI limits for digital systems are so small, it should be clear that long cables between major components of digital systems must be designed very carefully. For example, any common mode currents measured on a multiconductor cable of more than a few inches in length will more than likely be a problem because the associated return current paths must lie elsewhere. Although current components in I/O cables, for example, are generally lower in frequency than current components on PC boards, current loop areas established by I/O cables are generally much larger than those of PC boards because the cables are generally long and the PC boards are relatively small. Thus, from long intrasystem cables one generally has radiated EMI problems at frequencies lower than those of PC board radiation.

In summary, the importance of RF current-path geometries cannot be overlooked if one is to design marketable digital systems.

1. J.D. Kraus, *Antennas*. New York: McGraw-Hill, 1950, p.157.
2. U.S. Federal Communications Commission, "Methods of measurement of radio noise emissions from computing devices," in *Rules and Regulations*, pt. 5, subpt. J. Appendix A, pp. 163-171, July, 1981.
3. R.K. Keenan, *Digital Design for Interference Specifications*. Vienna, VA.: The Keenan Corp., 1983, p. A1-5.

One Antenna Kit with everything, to go please.

A complete line of kits
with upper limits to
18GHz that satisfy FCC,
VDE, and MIL-STD 461
specifications, and more.



Antenna kits that meet your specifications of high quality and frequency response, and that are also responsive to your demands of portability and easy use. A.H. Systems offers nine different kits that fill the bill. Each comes in a single, lightweight case. Just one kit can contain all the antennas, probes and cables to perform E-Field 1KHz-18GHz, H-Field 20Hz-50KHz and conducted 20Hz-100MHz testing. Antenna factor calibrations are provided with each antenna.

So order one to go, with everything, or one of our other tantalizing specials.

Available now from your
source for the finest
EMI test equipment and
accessories.

AH Systems
9710 Cozycroft Ave
Chatsworth, CA 91311
Tel: 818 998-0223
Telex: 182 640 WKVG

MODEL #	FREQ. RESP	DESCRIPTION	MODEL #	FREQ. RESP	DESCRIPTION
SAS-200-510	300 - 1800 MHz	Log Periodic	SAS-200-542	20 - 300 MHz	Biconical, Folding
SAS-200-511	1000 - 12000 MHz	Log Periodic	SAS-200-550	.001 - 60 MHz	Active Monopole
SAS-200-512	200 - 1800 MHz	Log Periodic	SAS-200-560	per MIL-STD-461	Loop - Emission
SAS-200-518	1000 - 18000 MHz	Log Periodic	SAS-200-561	per MIL-STD-461	Loop - Radiating
SAS-200-530	150 - 550 MHz	Broadband Dipole	BCP-200-510	20 Hz - 1 MHz	LF Current Probe
SAS-200-540	20 - 300 MHz	Biconical	BCP-200-511	100 KHz-100 MHz	HF VHF Crnt. Probe
SAS-200-541	20 - 300 MHz	Bicon I Collapsible			

INFOCARD 19

A.H.
SYSTEMS

The SAW Resonator Filter: How It Works. Part II

By Jeff Schoenwald
Contributing Editor

Last month, SAW resonator theory and a program for the TI-59 calculator and printer were described. This month, we use the program to learn about SAW resonators. Of special value is the definition and order of parameter entry.

Unless otherwise indicated, certain initial parameters that must be entered will always be the same:

$$\begin{aligned} l_1 &= l_2 = 0.25 \\ n_2 &= 1 \\ f_0 &= 100 \end{aligned}$$

As a first example, consider the characteristics of a single reflector array as a function of changing strip/gap impedance ratio Z at a fixed number of segments $N = 200$. Figures 1a and 1b show the reflection loss and transmission power loss respectively for $Z = 1.005$, 1.01 and 1.015. At frequencies above or below f_c the reflectors are transparent to traveling waves, so the transmission loss is small and the reflected wave loss is quite large. Closer to center frequency, the reflection efficiency of the gratings improves and the transmission loss increases relative to the impedance mismatch Z or number of segments in the array.

In the next example, shown in Figure 2, two reflectors are cascaded. $Z = 1.01$, $N = 100$ in each reflector, and the cavity is 5 wavelengths long (i.e., $l_g = 4.75$). Away from the center frequency, the results are similar to that of the previous examples. Near center frequency, the Fabry Perot cavity becomes resonant and the structure is "transparent," and at f_c the reflected energy is negligible.

While we have assumed no losses due to absorption in the transmission line, we

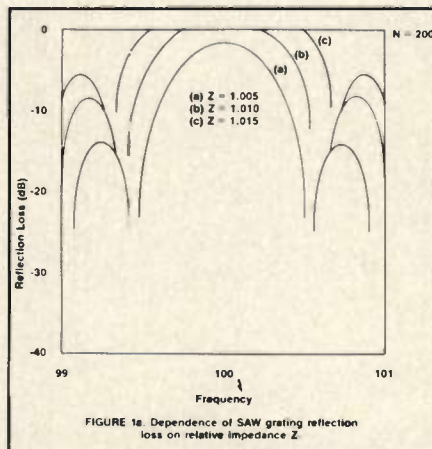


FIGURE 1a. Dependence of SAW grating reflection loss on relative impedance Z .

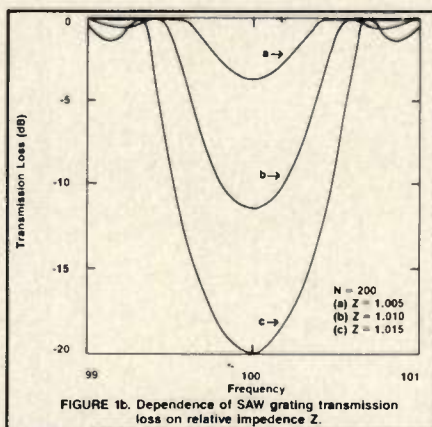


FIGURE 1b. Dependence of SAW grating transmission loss on relative impedance Z .

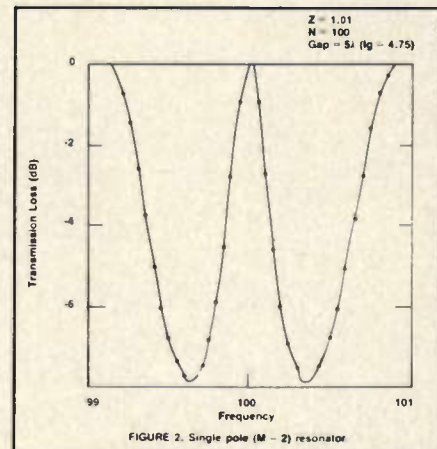


FIGURE 2. Single pole ($M = 2$) resonator

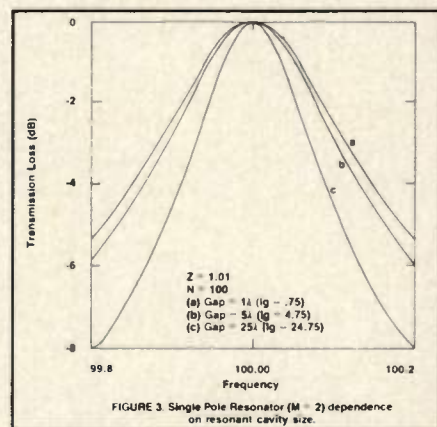


FIGURE 3. Single Pole Resonator ($M = 2$) dependence on resonant cavity size.

will still never obtain an infinite Q factor in a lossless device because a reflective array can never be 100% efficient unless Z or N go to infinity. What we do observe is a resonant peak at the center frequency with the 3 dB fractional bandwidth that determines the unloaded Q ($= f_c \Delta f_{3\text{ dB}}$) of the resonator. Figure 3 shows the

power transmission characteristics near $f_0 = f_c$ for a single cavity resonator ($M = 2$), with 100 sections/reflector, $Z = 1.01$, with the cavity size as the variable. It is apparent that the 3 dB bandwidth of the resonance decreases and Q increases as the cavity length increases. Figure 4 shows how the Q varies with

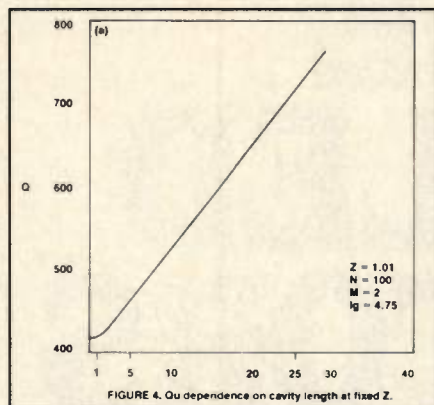


FIGURE 4. Q_u dependence on cavity length at fixed Z.

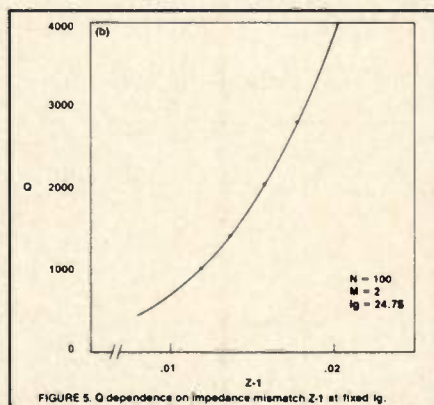


FIGURE 5. Q dependence on impedance mismatch Z-1 at fixed lg.

cavity length while N and Z are held constant. Similar sets of curves can be obtained to determine the dependence of Q or N or Z, which I encourage you to do. Figure 5 shows how Q varies with Z at fixed cavity size.

Cavity Dimension Is Critical

The resonant Fabry-Perot cavity formed by the two reflective arrays will act as an interference filter that efficiently transmits energy at wavelengths which satisfy the cavity relationship:

$$L = \frac{n\lambda_c}{2} \quad (1)$$

where $L = (l_1 + l_g) \cdot \lambda_c$. λ_c is the normalized wavelength at the peak of reflectivity of the grating. If the wavelength is different from λ_c , narrow band transmission through the structure will not occur at the center of the reflection stop-band of the grating. Another way of saying this is, if we let $L = l_1 + l_g$ be equal to some non-integer multiple of $\lambda_c/2$, the transmission spectrum appears non-symmetric. Figure 6 illustrates the effect of advancing the cavity dimension successively by $\lambda_c/8$. If resonance is not precisely

centered at the stop band center of the reflectors the Q, selectivity and efficiency of the resonator suffer.

Another interesting case is worth mentioning before we move on to more complicated structures. If we obey the Fabry-Perot condition of Eq. (1), but make n very large, we encounter a regime in which several longitudinal modes of the cavity can exist, all at slightly different wavelengths (frequencies). This is precisely the case for lasers. A simple laser with two mirrors will have many possible longitudinal cavity modes because the cavity is orders of magnitude larger than wavelength. Special techniques are used to lock the laser into a single mode for added spectral purity. Figure 7 shows some examples of multiple resonances due to oversized cavities.

Designing Multi-Pole Filters

The program is capable of synthesizing device designs that exhibit the essential features of multi-pole SAW resonator filtering behavior. There is no limit to the number of poles one may wish to model, nor does this affect the speed at which the frequency response is synthesized. A design consisting of M grating reflectors will result in an M-1 cavity structure with an M-1 pole response. This assumes, of course that the cavities are kept small enough to avoid more than a single longitudinal mode in each one. The resonances in each cavity will begin to couple and we shall begin to see how this coupling through the grating reflectors that separate each cavity give rise to the very narrow bandpass filtering which has made the SAW resonator popular in the RF and signal processing community.

With this program, all cavities will be the same size and all reflectors will have the same number of strip/gap segments for any one example run. How much can you expect from the TI-59? *C'est la vie*. We will, however, squeeze a bit more out of it.

Figures 8a, b, c and d show the transmission characteristics of 1-, 2-, 3-, and 4-pole resonators. All reflectors have 200 sections, with $Z = 1.01$, and all cavities are $5\lambda_c$ long (i.e., $l_g = 4.75$). The valleys between resonant peaks are very characteristic of the SAW resonator multi-pole filter. Typically, interdigital transducers (idts) are placed within the two outermost cavities of such a structure. This has the property of enhancing the resonance behavior over the broadband response of the idts, since by themselves they have an insertion loss that is often 20 or 30 dB,

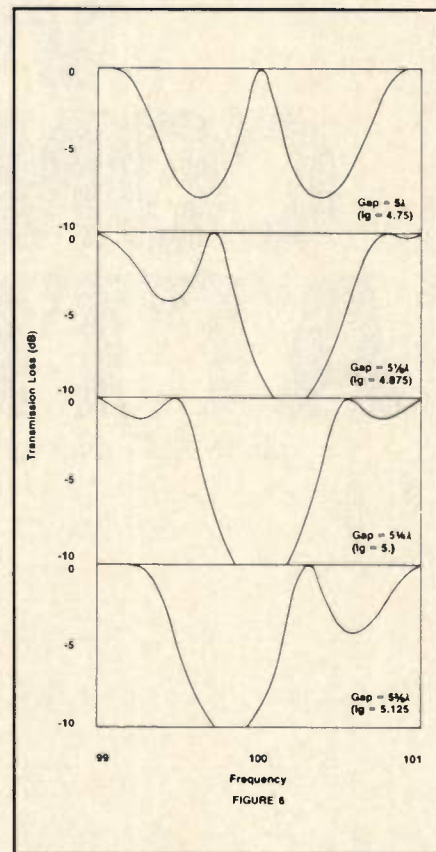


FIGURE 6

whereas the resonances are much stronger because the device impedance drops markedly at those frequencies. Before the idt is properly matched electrically, the resonator response is essentially that of the "unloaded" device and is quite well reproduced by the TI-59 program model. Impedance matching the electrical equivalent circuit of the idt to the cavity impedance will flatten the transmission response over the multipole pass-band.

The Phase of the Reflected and Transmitted Waves



Once the transmission matrix for the entire structure has been calculated, we may easily determine the phase of the reflected and transmitted wave from the transmission factor and reflection factor, T_F and R_F , using equations 2a and 2b.

$$\Phi(\text{refl}) = \arctan \frac{\text{Imag}(R_F)}{\text{Real}(R_F)} \quad (2a)$$

$$\Phi(\text{trans}) = \arctan \frac{\text{Imag}(T_F)}{\text{Real}(T_F)} \quad (2b)$$

VOLTAGE CONTROLLED ATTENUATORS

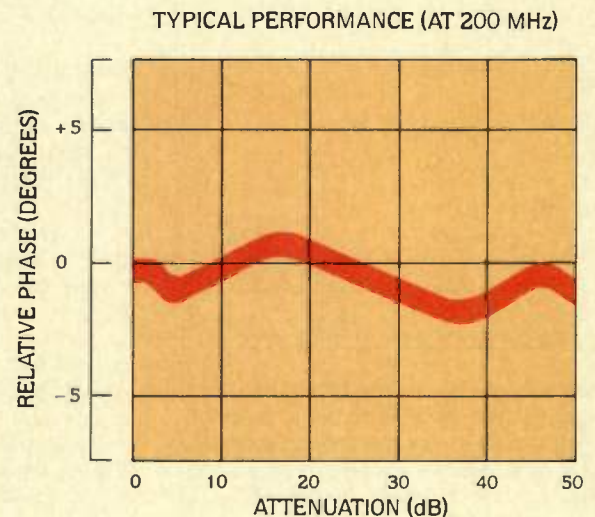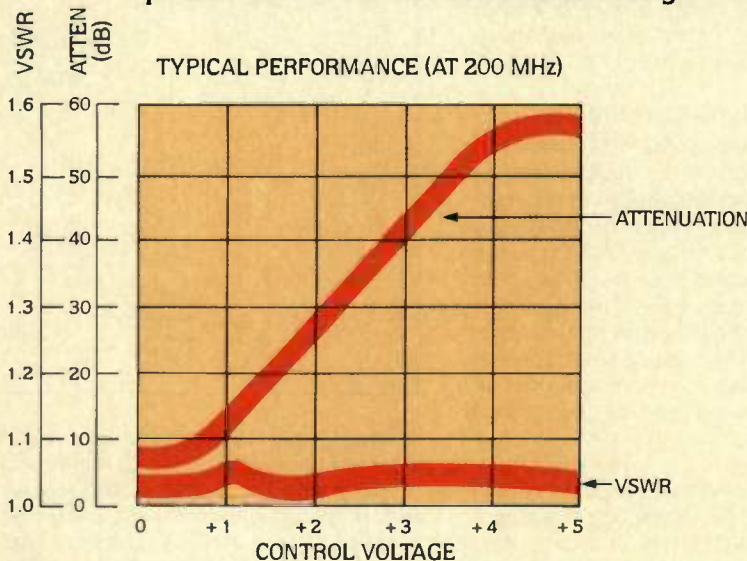
☐ phase stable over full attenuation range ☐ internal linearizer ☐ internal driver



DAICO DESIGN BRIEFS:

The phase compensated voltage controlled attenuator provides a linear 40dB analog attenuation with a maximum VSWR of 1.25 over the full range. The phase variation is typically less than $\pm 3^\circ$ at 200MHz. Daico phase compensated VCAs are designed and fabricated utilizing in house thin-film technology in accordance with MIL-STD-883B. They are offered in frequency ranges through 500MHz and in connectorized packages or MIC configurations for P.C. mounting.

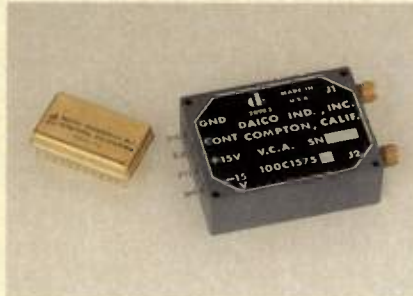Also offered are 2300 varieties of MIC & Connectorized Solid-State Switches, RF Relays, Delay Lines & Step Attenuators from DC to 6GHz.



TYPICAL SPECIFICATIONS

frequency	150-250MHz
phase stability	10° max over specified attenuation
attenuation range	40 dB min
linearity	± 2 dB
insertion loss	4 dB max
VSWR	1.25 max
control	0 to +5 volts
RF power	+ 15 dBm max
DC power	+ 15 volts @ 40 mA - 15 volts @ 40 mA
impedance	50 ohms
size	1.5 x 2.0 x .6 in
connectors	SMA
part number	100C1575



DAICO INDUSTRIES, INC.

2351 East Del Amo Blvd., Compton, CA 90220
Telephone 213/631-1143 • TWX 910-346-6741

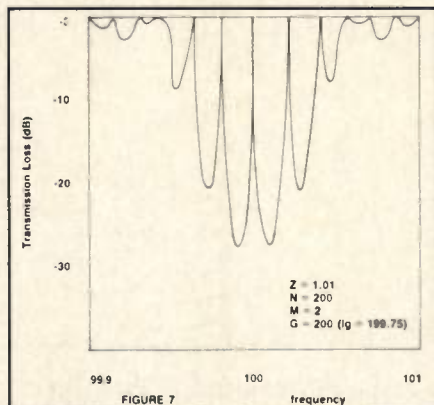


FIGURE 7

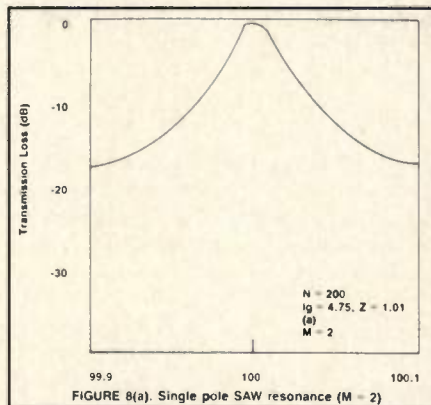


FIGURE 8(a). Single pole SAW resonance (M = 2)

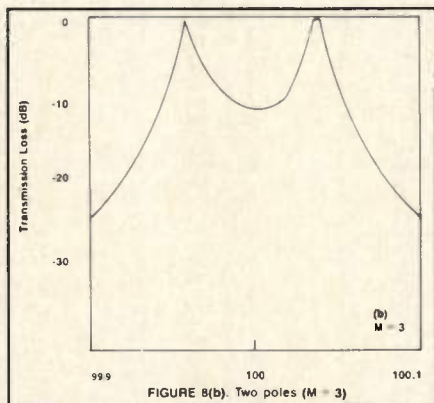


FIGURE 8(b). Two poles (M = 3)

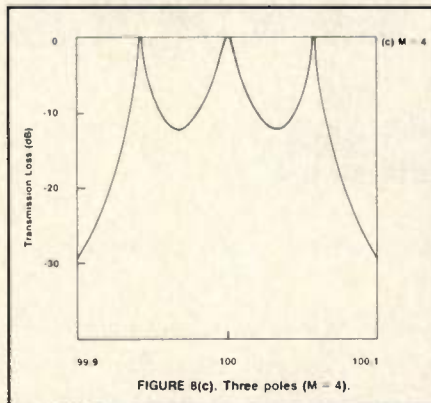


FIGURE 8(c). Three poles (M = 4).

In order to implement this calculation, the listing shown in Table I may be substituted for the last portion of the program, starting at step 638. This may be stored in a simple way. Since the calculator is partitioned for 720 steps, the entire program can be stored in three data banks. The modification occurs only in bank 3. The modified version can be stored on the second edge of the second card (normally used for bank 4). Be sure the calculator is in floating point mode (exit the learn mode and press INV 2nd FIX). Press 3 2nd WRITE but feed in the second magnetic card upside down. Later, when loading the program for phase analysis, the calculator will recognize this as a bank 3 read.

Using this method, power magnitude calculations can be done first, then the third bank replaced with phase calculation, the input parameters re-entered and the calculation repeated, yielding the phase response. Not all registers containing the input parameters are re-used. Look at Table II to determine at which label you must re-enter data. Practically speaking, however, it is easier and safer to re-enter all the data from scratch.

Figures 9 and 10 are examples of the phase response for a single pole resonator. They have identical structures but different values of Z . Rather than short-change the phase computational ability of this program, I will spend a few moments to explain some of the things you can learn from it about SAW resonators. For a plane wave incident on a reflecting surface, the general form of the reflected wave, relative to an incident wave of unit amplitude and zero phase at the front of the reflector, is

$$R_r = re^{2ik \cdot D} \quad (3)$$

where r is the coefficient of reflection magnitude and D is the distance from the point at which the observation is made to the plane of the reflecting surface. If we imagine that the observation point is the front edge of the distributed grating reflector and D is the distance to a fictitious point at which we may assume a single reflecting mirror is placed, then we are constructing a simple model that represents the distance to the "effective center of reflection."

GOING STRONG ON TERMINATIONS



STRONG ON RELIABILITY.

Acrian is the market leader because we offer you the broadest range of high reliability terminations and other passive components for power amplifier applications.

We've applied the latest thin-film technology for increased power dissipation (30-300W) and reliable high temperature operation. At 250° C, Acrian terminations have the highest temperature derating in the industry. Our microwave package construction yields VSWR's of 1.25:1 up to 4 GHz with no resonant loops. 100% tested and guaranteed to specifications.

STRONG ON DELIVERY.

Look to Acrian for off-the-shelf delivery when you need it, through the nationwide distribution services of Richardson Electronics.

Call toll-free: 800-645-2322.
Locally 516-536-8868.

GOING THE DISTANCE



490 Race Street
San Jose, Ca 95126
408/294-4200

The phase of the reflected wave is given by the argument of the exponential. If we take the first derivative of this phase with respect to the frequency and convert from radians to degrees, we obtain

$$\Phi_{\text{rad}} = 2 \frac{2\pi}{\lambda} D = \frac{4\pi D f}{v}$$

$$\frac{d\Phi_{\text{rad}}}{df} = 4\pi \frac{D}{v} = \frac{4\pi D}{f\lambda} \quad (4)$$

Therefore,


$$D = \frac{\lambda f}{4\pi} \cdot \frac{d\Phi}{df} = \frac{\lambda f}{4\pi} \frac{\pi}{180} \frac{d\Phi_{\text{deg}}}{df}$$

$$\frac{D}{\lambda} = \frac{f}{720} \frac{\Delta\Phi}{\Delta} \quad (5)$$

Thus, by measuring the slope of phase data we obtain for the reflected wave we are able to compute the distance to the

Bell didn't need Modpak™

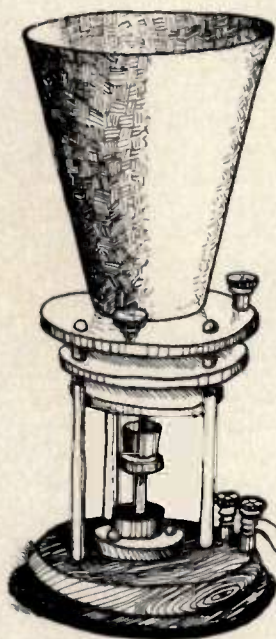But modern electronics involves more than a transmitter, a receiver, and a wire.



Your vulnerable RF circuit needs the protection only Modpak can give: a sturdy, RFI-shielded enclosure, user-designed with a choice of four interchangeable connectors and more than 30 standard off-the-shelf sizes or custom-fabricated in virtually any size. Top and bottom covers are easily removed for access to both sides of your PC board. All this at an affordable low price!

Adams & Russell

MODPAK DIVISION

80 Cambridge St., Burlington, MA 01803
(617) 273-3330



Find out why
you need Modpak,
send for our
complete catalog.

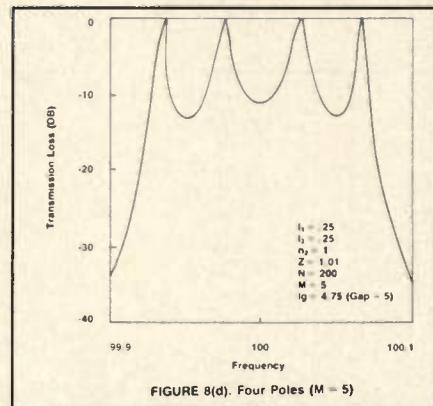


FIGURE 8(d). Four Poles (M = 5)

TABLE I Phase Calculation

638	60	DEG	678	53	(
639	53		679	43	RCL
640	02	2	680	06	06
641	65	x	681	85	+
642	53		682	43	RCL
643	43	RCL	683	07	07
644	08	08	684	54)
645	65	x	685	55	+
646	43	RCL	686	53	(
647	06	06	687	43	RCL
648	75	-	688	05	05
649	43	RCL	689	85	+
650	05	05	690	43	RCL
651	65	x	691	08	08
652	43	RCL	692	54)
653	07	07	693	94	+/-
654	54)	694	22	INV
655	55	+	695	30	TAN
656	53		696	95	=
657	43	RCL	697	99	PRT
658	05	05	698	98	ADV
659	33	x²	699	43	RCL
660	85	+	700	13	13
661	43	RCL	701	32	X-T
662	06	06	702	43	RCL
663	33	x²	703	26	26
664	75	-	704	67	EQ
665	43	RCL	705	19	D'
666	07	07	706	43	RCL
667	33	x²	707	29	29
668	75	-	708	42	STO
669	43	RCL	709	11	11
670	08	08	710	61	GTO
671	33	x²	711	14	D
672	54)	712	76	LBL
673	54		713	19	D'
674	22	INV	714	43	RCL
675	30	TAN	715	26	26
676	95	=	716	91	R/S
677	99	PRT			

"effective center of reflection." At the peak in reflectivity the center of reflection appears to move toward the front of the reflective array, as evidenced by a decrease in the magnitude of the phase slope. Away from resonance, where the array ultimately looks transparent, the center of reflection moves to the geometric center of the array.

For the cases shown in Figures 10a and 10b, the reflection centers are located, at resonance, a distance of 22 and 17 wavelengths, respectively, inside the array, as viewed from the direction of incidence. Now consider two identical reflectors separated by a distance necessary to produce a single pole resonance. The total length of the cavity is then given by

$$L = (l_g + 1/4) \cdot c + 2D \quad (6)$$

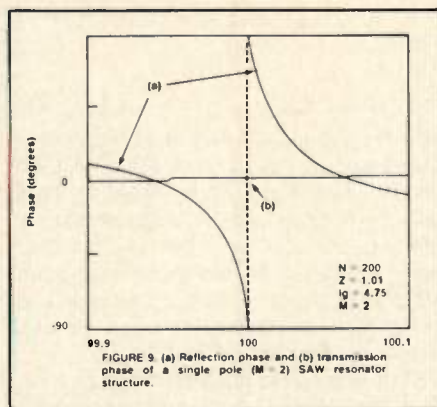


FIGURE 9 (a) Reflection phase and (b) transmission phase of a single pole ($M=2$) SAW resonator structure.

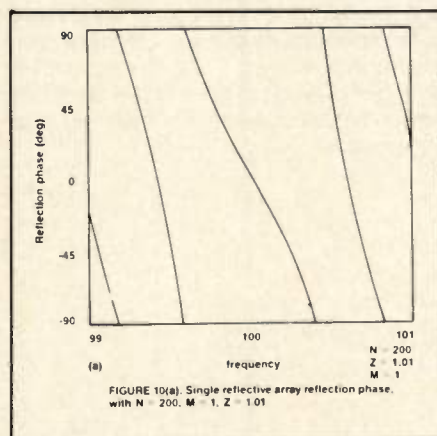


FIGURE 10(a). Single reflective array reflection phase, with $N=200$, $M=1$, $Z=1.01$.

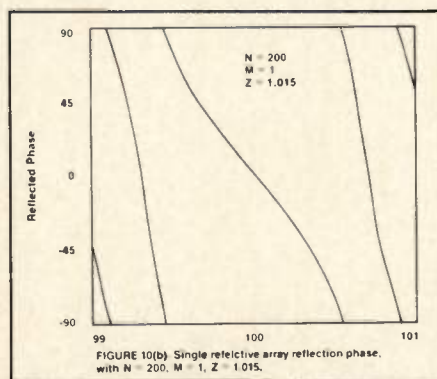


FIGURE 10(b). Single reflective array reflection phase, with $N=200$, $M=1$, $Z=1.015$.

Knowing the value of D is important for determining the frequency spacing between longitudinal modes in the resonant cavity formed by the two arrays. Now we can see that mode spacing is a function of both cavity size and reflective properties of the array, as represented by the distance D . It is possible to derive frequency spacing dependence on effective length of the cavity L , and such derivations abound in books on lasers. The reader is encouraged to do this for the specific case shown in Figure 7. You will indeed find that the mode spacing observed in large SAW resonator cavities,

or in SAW resonators with Z so close to unity that D is sizable, is properly described by taking this reflection distance into account properly. More than once, ignorance of this fact has bitten SAW resonator designers when they least expected it.


Conclusion

I have tried to give the reader a tool for modeling and exploring the behavior of the SAW resonator, a very interesting tool in RF technology. Even if you have no plans for designing such devices you may very likely wish to specify one from a number of vendors that supply them. In that case, you will be better off for having become familiar with the properties of these devices and being an educated customer.

TABLE II

Register	Variable
0	$N, N-1, M, M-1$
1	λ_1, λ_2
2	M
3	lg
4	$\Theta, \lambda_1 \uparrow N, \lambda_3 \uparrow N$
5	$I_1, A(N), A(N+9)$
6	$I_2, B(N), B(N+9)$
7	$n_2, C(N), C(N+9)$
8	$f_0, D(N), D(N+9)$
9	fc
10	Z
11	N
12	$t, \cos \Theta = (A + D)/2$
13	f_1
14	df
15	$\alpha = \pi \cdot f_1/f_c$
16	$Z + 1$
17	$Z - 1$
18	$1 - 2t$
19	$A(1), A(N)$
20	$B(1), B(N)$
21	$C(1), C(N)$
22	$D(1), D(N)$
23	$[(A + D)/2]^{1/2} - 1$
24	λ_1
25	λ_2
26	$f_2 + df$
27	$\sin N\Theta$ or $(\lambda_1 \uparrow N - \lambda_2 \uparrow N)/(\lambda_1 - \lambda_2)$
28	$\sin (N-1)\Theta$ or $(\lambda_1 \uparrow (n-1) - \lambda_2 \uparrow (n-1))/(\lambda_1 - \lambda_2)$
29	N

GOING STRONG ON RESISTORS

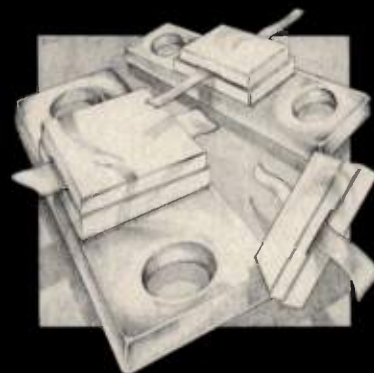

STRONG ON DEPENDABILITY.

If you're involved in power amplifier design, you can depend on Acrian for the most complete line of hi-rel power microstrip resistors and other passive components.

We've applied the latest thin-film technology for highest power dissipation (30-300W) and dependable high temperature operation. (Acrian resistors have the highest derating temperature in the industry to 250° C).

Our microwave package construction yields VSWR's of 1.25:1 up to 4 GHz with no resonant loops. 100% tested and guaranteed to specifications.

STRONG ON DELIVERY.

Look to Acrian for off-the-shelf delivery when you need it, through the nationwide distribution services of Richardson Electronics.

Call toll-free: 800-645-2322. Locally 516-536-8868.

GOING THE DISTANCE



490 Race Street
San Jose, CA 95126
408/294-4200

**Johnson
delivers
variable
capacitors
when you want
them.**

Air variable, ceramic or teflon dielectric, no matter what variable capacitor type you need, Johnson can meet your specifications—for both design and delivery.

Our engineering and manufacturing staffs produce innovative, cost-effective products. Our national network of 250 distributors helps with your prototypes.

Write for your free catalog or call
1-507-835-6307. Telex: 290470.
TWX: 910-565-2161.



JOHNSON

Components Division
F. F. JOHNSON COMPANY WASECA MINN 56093

INFO/CARD 24

BONUS!:
A *BASIC* Version

For readers who own or work with a computer, here is a BASIC version of the TI-59 calculator program to model the transmission and reflection power and phase of a SAW resonator type of structure. This program was written on a Commodore 64, which uses a version of BASIC and an ASCII character set that is slightly different from standard ones. I have taken pains to write the program to be as transportable as possible, indicating, when necessary, what lines are not transportable and require change or deletion. The POKes only pertain to screen or letter color. There are no PEEKs. The printer commands are usable "as is" only on Commodore printers and serve as an example which must be tailored for other brands.

Because memory is not as tight for most micros, power and phase are computed and provisions are made for screen display and hard copy. Disk or tape storage of data files and high resolution plotting are routines that the devoted hacker should add, but these have been left out because of differences between computers in storage procedures and screen addressing.

Data entry is simple and screen prompted. If the velocity in a strip segment is different from the gap velocity the center frequency will be different from the designated reference frequency. I suggest you start with a ratio of 1 and then try small changes to observe the trend. The same advice holds for the impedance ratio and cavity size.

```

10 REM *****
20 REM * CERTAIN LINES ARE *
30 REM * SPECIFIC TO THE *
40 REM * COMMODORE 64. *
50 REM * DELETE OR ALTER AS DESIRED. *
60 REM *****
70 PI = 3.14159265 REM * C-64 RECOGNIZES SYMBOL FOR PI. USE IT IF YOU CAN. *
80 POKE 53281,0:POKE 53280,0:REM *SET BACKGROUND TO BLACK FOR C-64*
90 PRINT CHR$(145);REM *SET SCREEN LETTERS TO YELLOW ON C-64*
100 PRINT CHR$(147)
110 PRINT"SAW RESONATOR TRANSMISSION"
120 PRINT" LINE SIMULATION"
130 PRINT"
140 PRINT" *OF RIGHT JEFF SCHENWALD*
150 PRINT" 1984"
160 FOR I = 1 TO 2000
170 NEXT I
180 PRINT CHR$(147)
190 INPUT" *GAP SEGMENT LENGTH, L1*L2"
200 INPUT" *LINE SEGMENT LENGTH, L3*L4"
210 INPUT" *RELATIVE VELOCITY INDEX OF L3 AND L4"
220 INPUT" *REFERENCE FREQUENCY F0*F0
230 INPUT" *STRIP GAP IMPEDANCE RATIO, Z0/Z
240 INPUT" *OF SEGMENT PAIRS PER REFLECTOR, N*N
250 REM
260 INPUT" *START FREQUENCY, F1*F1
270 INPUT" *FREQUENCY INCREMENT, DF*DF
280 INPUT" *STOP FREQUENCY, F2*F2
290 INPUT" *OF REFLECTOR ARRAY SECTIONS, M*M
300 INPUT" *CAPACITY SIZE, LG*LG
310 F0=F0/2*(L1+L2+L3+L4)
320 PRINT CHR$(147)
330 PRINT" *CENTER FREQUENCY = *F0
340 T=LN(LG)/LN(2)
350 K1=INT (F2-F1)/DF
360 DIM AN*(K1+BN+KN),CN*(K1+DN+KN),TP*(K1+PN+KN),TF*(K1+RN+KN)
370 FOR K = 0 TO K1
380 F = F1 + DF*K
390 LET GAMMA = F1-F0
400 A1 = (Z-1)/(Z+1)*COS(GAMMA) - (Z-1)/(Z+1)*COS(GAMMA*(1-D+T))
410 B1 = (Z-1)/(Z+1)*SIN(GAMMA) - (Z-1)/(Z+1)*SIN(GAMMA*(1-D+T))
420 C1 = (Z-1)/(Z+1)*SIN(GAMMA) - (Z-1)/(Z+1)*SIN(GAMMA*(1-D+T))
430 D1 = (Z-1)/(Z+1)*COS(GAMMA) - (Z-1)/(Z+1)*COS(GAMMA*(1-D+T))
440 NB=N
450 GOSUB 600 REM *COMPUTE EIGENVALUES FOR ONE ARRAY AND COMPUTE T MATRIX*
460 GOSUB 700 REM *COMPUTE CAPACITANCE MATRIX*
470 GOSUB 1000 REM *MULTIPLY MATRICES*
480 GOSUB 1090 REM *REDEFINE NEW T MATRIX*
490 NB=M
500 GOSUB 640
510 REM
520 REM *COMPUTE EIGENVALUES AND MATRIX FOR *
530 REM *M CASCADED REFLECTORS AND CAPACITIES*
540 AN(K1)=AN
550 BN(K1)=BN
560 CN(K1)=CN
570 DN(K1)=DN
580 PRINT CHR$(147)
590 PRINT" *FREQUENCY PT. M*(K1) = *F
590 GOSUB 1160 REM *COMPUTE POWER & PHASE*
600 NEXT K:REM *NEXT FREQUENCY POINT*
610 REM *GOTO OUTPUT MENU*
620 GOTO 470
630 REM
640 REM**REAL OR COMPLEX EIGENVALUES**
650 TRIG = A1/D1/2
660 IF TRIG(2-1)=0 THEN 690
670 IF TRIG(2-1) THEN 870

```




```

600 RETURN
610 REM * MATRIX FOR COMPLEX EIGENVALUE READY.
620 AGL = -2*TRIG/SQR(-TRIG*TRIG+1)+PI/2
630 IF AGL=0 THEN 780
640 N1=N0-1
650 AN=A1/SIN(N0*AGL)/SIN(AGL)-SIN(N1*AGL)/SIN(AGL)
660 BN=B1/SIN(N0*AGL)/SIN(AGL)
670 CN=C1/SIN(N0*AGL)/SIN(AGL)
680 DN=D1/SIN(N0*AGL)/SIN(AGL)-SIN(N1*AGL)/SIN(AGL)
690 GOTO 720
700 GOSUB 1010
710 RETURN
800 REM * WHEN EIGENVALUES ARE *
810 REM * DEGENERATE *
820 AN=A1-1
830 BN=B1
840 CN=C1
850 DN=D1-1
860 RETURN
870 REM * MATRIX FOR REAL EIGENVALUES *
880 K1=TRIG+SQR(1-TRIG*2-1)
890 K2=1-K1
900 N1=N0-1
910 AN=A1*(K1*N0-K2*N0)/(K1-K2)-(K1*N1-K2*N1)/(K1-K2)
920 BN=B1*(K1*N0-K2*N0)/(K1-K2)
930 CN=C1*(K1*N0-K2*N0)/(K1-K2)
940 DN=D1*(K1*N0-K2*N0)/(K1-K2)-(K1*N1-K2*N1)/(K1-K2)
950 RETURN
960 REM ***GENERATE CAVITY MATRIX***
970 REM
980 A=COS(2+GAMMA*LG)
990 B=SIN(2+GAMMA*LG)
1000 C=SIN(2+GAMMA*LG)
1010 D=COS(2+GAMMA*LG)
1020 RETURN
1030 REM ***MATRIX MULTIPLICATION***
1040 AP=AN*A-BN*B
1050 BP=AN*B+BN*B
1060 CP=CN*A+DN*B
1070 DP=DN*A-CN*B
1080 RETURN
1090 REM
1100 A1=AP
1110 B1=BP
1120 C1=CP
1130 D1=DP
1140 RETURN
1150 REM ***COMPUTE REFLECTED AND***
1160 REM ***TRANSMITTED POWER AND***
1170 REM ***PHASE***
1180 Q = (AN(K)-DN(K))*2*(BN(K)+CN(K))*2
1190 TP=4*Q
1200 TPX = 10*LOG(TP)/LOG(10)
1210 RP=1-TP
1220 IF RP = 0 THEN 1280
1230 RPK = 10*LOG(RP)/LOG(10)
1240 TPK = -10*LOG(1-TP)/LOG(10)
1250 RF=2*(BN(K)+DN(K)+AN(K)-CN(K))*2-DN(K)*2-CN(K)*2
1260 RFX = 10*LOG(RF)/LOG(10)
1270 RETURN
1280 RPK = -99.0
1290 GOTO 1010
1300 W=20:REM *STOP SCREEN PRINT EVERY 20 LINES*
1310 PRINT CHR$(147)
1320 PRINT "FREQ. R-PWR T-PWR(DB) R-PHA T-PHA"
1330 PRINT " (DB) (DB) (DEG) (DEG)"
1340 FOR K=0 TO K1
1350 F = F1+DF*K + .000001
1360 B1=STR$(F):GOSUB 1690:F1=B1
1370 R1=STR$(RPK)
1380 B1=R1:GOSUB 1590:R1=B1
1390 T1=STR$(TPK)
1400 B1=T1:GOSUB 1590:GOSUB 1670:T1=B1
1410 R2=STR$(RFX)
1420 B1=R2:GOSUB 1590:R2=B1
1430 T2=STR$(TFK)
1440 B1=T2:GOSUB 1590:T2=B1
1450 IF W*W<2 THEN 2000
1460 PRINT F;TAB(14-LEN(R1));R1;TAB(20-LEN(T1));T1;TAB(30-LEN(R2));R2;TAB(40-LEN(T2));T2
1470 PRINT R1;TAB(39-LEN(T1));T1
1480 IF K=0 THEN 1510
1490 IF K<K2 THEN 1520
1500 IF K/W=INT(K/W) THEN 1920
1510 NEXT K
1520 IF W<K2 THEN 2000
1530 PRINT "END OF LISTING. PRESS C FOR MENU"
1540 GET #1
1550 IF A#="" THEN 1540
1560 IF A#="C" THEN 1700
1570 IF A#="Q" THEN 1540
1580 RETURN
1590 REM *MANIPULATE STRINGS TO LINE UP COLUMNS*
1600 FOR U = 1 TO LEN(B1)
1610 IF MID$(B1,U,1)="" THEN 1640
1620 NEXT U
1630 RETURN
1640 B1=LEFT$(B1,U-1)
1650 IF LEN(RIGHT$(B1,U-1))<2 THEN B1=B1+" "
1660 RETURN
1670 IF ABS(TPK)/100 THEN B1=""-0.00"
1680 RETURN
1690 FOR U = 1 TO LEN(B1)

```

CONNOR-WINFIELD OSCILLATORS

SHORT-ORDER SPECIALISTS

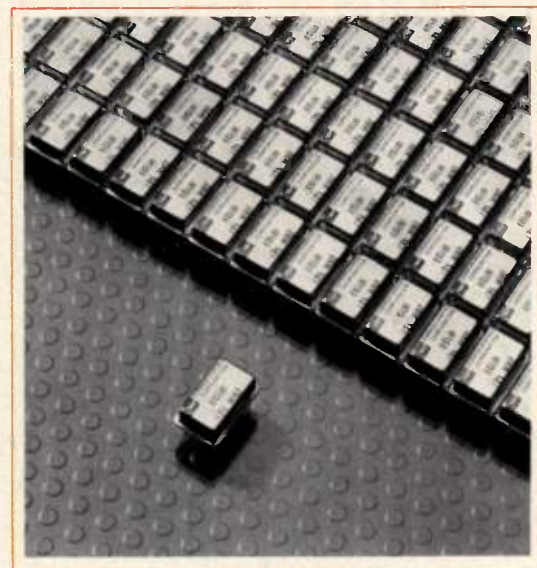

But we can cook up a big batch, too!

Connor-Winfield is ready to serve. Whether the oscillators you need are in stock or custom designed or whether you need 1 or 10,000, our special of the day—everyday—is meeting your needs with the right combination of quality and low cost. Are you ready to order? Call or write us today for more information.

ECL DIP High Frequency

Models: ECLA, ECLB
Frequency: 8MHz—200MHz, $\pm .01\%$
Supply: $-5.2\text{Vdc} \pm 5\%$ or $-4.5\text{Vdc} \pm 5\%$
Output: 10K ECL or 100K ECL
Package: All metal, hermetically sealed

DIP SINEWAVE Low Frequency

Models:	DPS1	DPS2
Frequency:	1KHz—75KHz	100Hz—100KHz
Tolerance:	$\pm .01\%$, THD $\leq 5\%$	$\pm .01\%$, THD $\leq 5\%$
Supply:	5Vdc $\pm 10\%$	8Vdc—15Vdc
Package:	All metal, hermetically sealed	

TTL CLOCKS Tight Tolerance

Models:	S10C	S10D	S10E
Frequency:	31KHz—25MHz		
Tolerance:	$\pm .001\%$	$\pm .0025\%$	$\pm .005\%$
Temp. Range:	0°—50°C	0°—70°C	-25°—75°C
Package:	All metal, hermetically sealed 14 pin DIP		

TTL CLOCKS Stock Frequencies/ Low Cost

Models:	S14R8	S15R8
Tolerance:	$\pm .005\%$	$\pm .01\%$
Supply:	+5Vdc $\pm 10\%$, 60mA max	
Frequencies:	1,2,4,5,6,8,10,12,16,20,24,40,70MHz	
Package:	All metal, hermetically sealed 14 pin DIP	



CONNOR-WINFIELD CORPORATION
West Chicago, IL 60185 USA
Phone: 1-312-231-5270
TWX No. 910-230-3231
Cable: CONWINWCGO


```

1700 IF MID$(B$,0,1)="" THEN 1730
1710 NEXT U
1720 RETURN
1730 B$=LEFT$(B$,U-3)
1740 IF LEN(RIGHT$(B$,U-3))=3 THEN B$=B$+"00"
1750 RETURN
1760 PRINT CHR$(147)
1770 PRINT "CHOOSE AN OPTION. PLEASE"
1780 PRINT""
1790 PRINT "1 - REPEAT CALCULATION" CHR$(13)
1800 PRINT "2 - PRINT DATA TO PRINTER" CHR$(13)
1810 PRINT "3 - PRINT DATA TO SCREEN" CHR$(13)
1820 PRINT "4 - QUIT PROGRAM" CHR$(13)
1830 GET A$
1840 IF A$="1" THEN 1850
1850 IF A$="2" THEN 2000
1860 IF A$="3" THEN 1300
1870 IF A$="4" THEN END
1880 IF A$="" THEN 1830

```

```

1890 CLR
1900 GOTO 190
1910 PRINT CHR$(147)
1920 PRINT "PRESS CTR TO CONTINUE"
1930 GET A$
1940 IF A$="C" THEN 1950
1950 IF A$="" THEN 1930
1960 PRINT "FREQ. R-PWR T-PWR E-PHA T-PHA"
1970 PRINT "DB DB DEG DEG"
1980 GOTO 1300
1990 PRINT CHR$(147)
2000 W=1/2
2010 OPEN "4.4 CMD" REM * C-44 COMMAND TO OPEN CHANNEL TO COMMODORE PRINTER *
2020 REM * TO SUIT YOUR PRINTER PLEASE ALTER THE FOLLOWING *
2030 REM * LINES 2010, 2030, 2100 AND 2110
2040 GOTO 1310
2050 PRINT "CLOSE"

```

```

2060 PRINT CHR$(147)
2070 PRINT "END OF HARD COPY LISTING"
2080 GOTO 1770
2090 REM
2100 PRINT "1" CHR$(13) CHR$(13) CHR$(13) CHR$(13) CHR$(13)
2110 PRINT "2" CHR$(13) CHR$(13) CHR$(13) CHR$(13) CHR$(13)
2120 GOTO 1450

```



Why do it yourself when we've done it for you?



The Schaffner FN 380.

We've put it all together for you.

Schaffner's FN 380 universal power entry module is a complete package. . . in fact, it's fast becoming the standard of the industry.

The FN 380 features an on/off power switch along with an IEC connector and international fusing (one or two fuses, either 3 AG or IEC size). It also has a field-proven connector filter already mounted.

And of course, it's all agency approved.

The all-in-one component.

Why do it yourself when Schaffner has done it for you? Get the universal power entry module series that includes fuse holders, voltage selector switch, power switch, IEC connector. . . plus standard filter!

Available in current ratings of 2, 4 and 6 amps with interchangeable fuse holders and 1 or 2 pole switch.

For more information about the universal power entry module series (FN 370/380), and all three dimensions of Schaffner EMC, call or write today.



Series 380
RFI Filter

SCHAFFNER

approved

• RFI Suppression Filters • EMC Test Equipment • Test and Application Services
USA: Schaffner EMC, Inc., 825 Lehigh Ave., Union NJ 07083/(201) 851-0644
Switzerland: Schaffner Elektronik AG, CH-4708 Luterbach, Switzerland/Telefon 065 4231 31

Erratum:

There was an error in equation (13) as printed in Part I. It should have read:

$$[Tg] = \begin{vmatrix} \cos y & jZ_1 \sin y \\ j\sin y & \cos y \end{vmatrix} \begin{vmatrix} \\ Z_1 \end{vmatrix}$$

rf calendar

March 11-15

Electromagnetic Interference and Control

A Five-day Short Course

Washington, DC

Information: Shirley Forlenzo, George Washington University; Tel: (202) 676-8530 or toll-free (800) 424-9773.

March 18-20

Dielectric Resonators

A Three-day Short Course

University of Mississippi, Oxford Campus
Oxford, MS

Information: Dr. Darko Kajfez, Department of Electrical Engineering, University, MS 38677; Tel: (601) 232-7231.

March 19-22

Componentes Electronicos '85

Guadalajara, Mexico

Information: Ms. Raquel Polo, Deputy Project Manager, United States Trade Center, P.O. Box 3087, Laredo, TX 78044; Tel: (905) 591-0155.

MODULAR INSERT INFO/CARD #64 ►

MICROWAVE MODULES & DEVICES



**HIGH
TECHNOLOGY**

SOLID STATE AMPLIFIER MODULES




• COMMUNICATIONS • RADAR • BROADCAST • TV •
• JAMMERS • AVIONICS • IFF • EW • ECM • TELEMETRY •



The Company

Microwave Modules & Devices is uniquely dedicated to integrating device and circuit technology to break through current technological barriers to achieve a new level of pricing and performance in the RF/Microwave field.

The professionals who head the company have been engaged in the design, development and production of high power, solid-state microwave modules and devices for over 15 years. Today, MMD's expanding line of products includes amplifiers employing both hybrid micro-circuitry and modular printed circuit technology. The company's high performance amplifiers are targeted for use in military and industrial applications worldwide. In addition, MMD is deeply involved in the design, development and manufacture of a wide variety of RF and microwave functions for high technology applications both for military and industrial markets. MMD's markets include communications, counter-measures, radar, space, broadcast, avionics, industrial, scientific and medical. Reduction in size is one of MMD's on-going goals while constantly striving to improve both performance and product reliability. This brochure highlights MMD's current capabilities and its technological direction in the future.

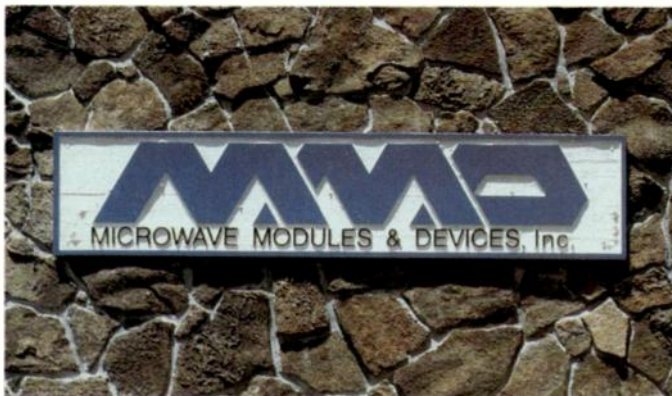


Fast Response Time

Fast response to customer amplifier needs is assured by a complete in-house design, prototyping and manufacturing capability. This is due totally or in part to:

- Complete engineering model shop.
- Computer-aided design.
- Automated die attach.
- Automated test capabilities.
- Engineering staff with more than 125 years combined experience.
- Computerized manufacturing/accounting systems.

Soft Board Amplifiers

State-of-the-art performance, high reliability, small size and fast development time are among the challenges that MMD is accepting every day. If these sound like your particular problems, MMD can provide the solutions you have been looking for. For example, complete solid-state amplifiers with power outputs to more than 1 KW can be designed and manufactured to your specifications. If you have a new design requirement for TV, radar, communications, avionics, EW, or need a solid state replacement for a vacuum tube, MMD is in business to solve your problems **fast!!** If improvements in efficiency or linearity are important in your application, MMD can help. In fact, MMD is providing an order of performance previously unachievable in RF power amplifier modules. MMD can **demonstrate** how to reach such goals as wide bandwidth, high efficiency, power outputs to

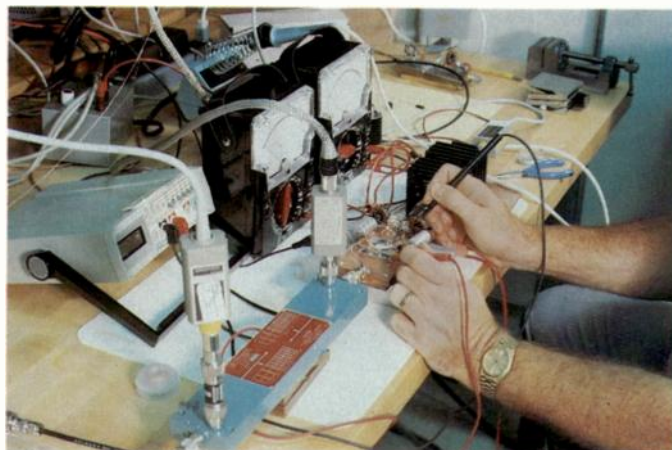

Custom Modules

MMD specializes in developing and manufacturing modules to your specifications. What do you need to maintain your competitive edge?

- Higher power?
- Wider bandwidth?
- Better efficiency?
- Smaller size?
- Improved reliability?

MMD can solve these design problems to meet your performance requirements.


The Plant

Microwave Modules & Devices (MMD) is located in Mountain View, California, in the heart of the high technology area known internationally as "Silicon Valley." The modern 10,000 square foot plant is fully equipped with the most advanced test, process and assembly equipment. It has clean room and assembly capabilities for delivering softboard and hybrid modules to the demanding requirements of military programs and sophisticated industrial applications. MMD's quality assurance procedures are designed to incorporate the latest military standards.



Hybrid Power Amplifiers

MMD hybrid power amplifier modules using chip transistors and either thick or thin film construction offer improved performance and ease of use compared to discrete designs. Hybrid power amplifier modules can provide guaranteed performance with no additional tuning or impedance matching headaches and the "Drop-in" configuration simplifies the user's mechanical design. In addition, smaller size offers a real advantage in systems where space is at a premium. MMD specializes in custom designs requiring BeO substrates or chip carriers to achieve performance not possible with discrete designs.

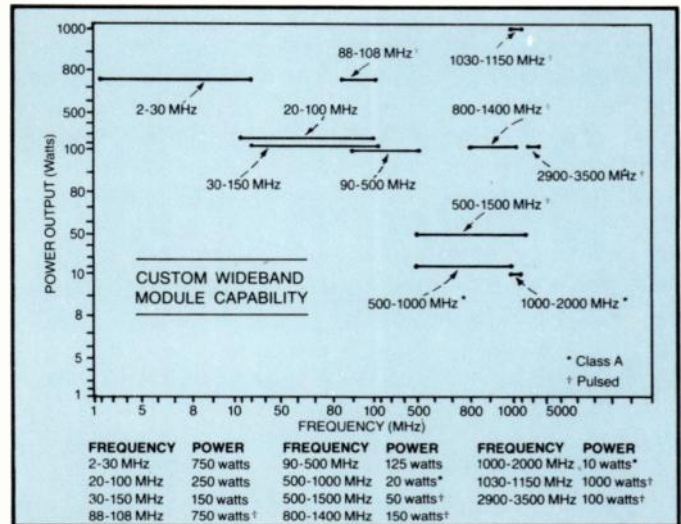


more than 1 KW Class C or Linear, Pulse or CW. All of this can be achieved by several unique MMD capabilities including:

- Custom die designs for optimized performance.
- Custom BeO ceramic chip carriers for best die/circuit interfaces.
- In-house custom ceramic/metal device packaging for lower thermal resistance; lower parasitics; hermetic seal.
- Device assembly.

For example, these unique capabilities come together to create MMD's "POWER QUAD" concept which combines with new wideband matching components to offer power/bandwidth capability far superior to that of conventional designs. So, if **performance** is an important consideration, call and find out how Microwave Modules & Devices can provide you with a **cost effective** alternative to in-house design, development and manufacturing of your critical power amplifier modules.

RF Functions

MMD can provide all the RF functions you need for your particular system requirements. Active mixers, AGC amplifiers, high speed modulators, wideband amplifiers and IF amplifiers are just some of the products under development. MMD functions use transistors with F_t up to 8GHz and power capability up to 1 watt, making them ideal for low distortion, wide dynamic range EW applications. A variety of packages are available for your custom requirements such as welded hermetic enclosures or small microstrip styles.

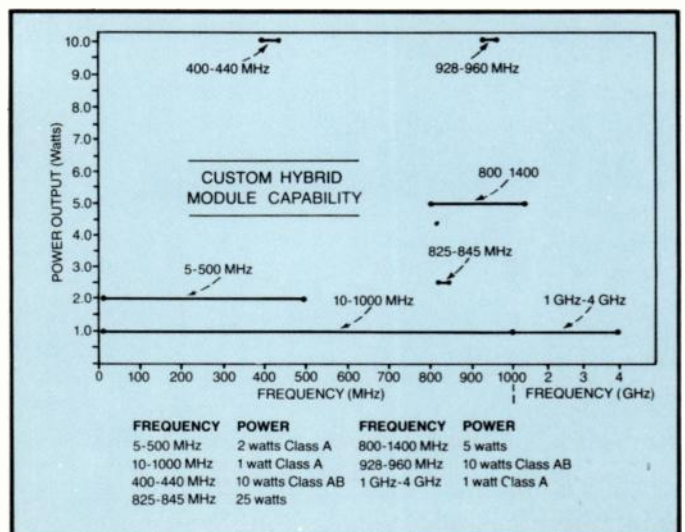



MICROWAVE MODULES & DEVICES, Inc.

**OFFERS THE
RF/MICROWAVE COMMUNITY
A NEW HIGH ORDER OF
PERFORMANCE IN SOLID STATE
SYSTEMS, MODULES AND
CIRCUITS IN COMBINATION
WITH UNIQUE APPROACHES
TO DEVICES AND
PACKAGING
DESIGN**



MICROWAVE MODULES & DEVICES, Inc.



AC-0003-500W

500 WATT SOLID STATE AMPLIFIER MODULE

The AC-0003-500W is a modular wideband HF Class AB Linear Power Amplifier that provides 500 watts of output power at an intermodulation distortion level of better than -35dB (IMD₃). The module incorporates wideband 90° quadrature combiners resulting in predictable 50 ohm system interfaces and superior performance into imperfect loads. The unit also contains internal voltage regulation and reverse voltage protection.

A single AC-0003-500W can be used as the final stage in a 500 watt system or modules can be combined to construct multi-kilowatt transmitters.

The MMD AC-0003-500W module is a reliably rugged building block designed for a wide variety of uses in Military and Industrial HF applications.

MODULE SPECIFICATIONS

PARAMETER	LIMITS		UNITS	CONDITIONS
	MIN.	MAX.		
GAIN	13.0		dB	P _{OUT} = 500 WATTS PEP FREQ. = 2 TO 30 MHz V ₁ = 5.0 VOLTS V ₂ = 45 VOLTS
GAIN FLATNESS		±1.5	dB	
EFFICIENCY	30		%	
INPUT VSWR		1.5:1		
OPERATING LOAD VSWR		2.0:1		
NON-DESTRUCTIVE LOAD VSWR		5.0:1		
IMD ₃		-35	dB	FREQ. = 2 TO 30 MHz V ₁ = 5.0 VOLTS V ₂ = 45 VOLTS
P _{SAT}	700		W	
OUTPUT SOURCE VSWR		1.5:1		
WEIGHT		7	LBS.	


All specifications are at a 30° C baseplate unless otherwise stated.

PRIME POWER REQUIRED: V₁ = 5.0 ±0.1 VOLTS @ 2.5 AMPS.
 V₂ = 45.0 ±1.0 VOLTS @ 40 AMPS.

OPERATING BASEPLATE TEMPERATURE: -25°C TO +85°C.

CONNECTORS: TYPE "N" FEMALE (RF). SOLDER PIN (DC).

2 to 30MHz
HF MODULE

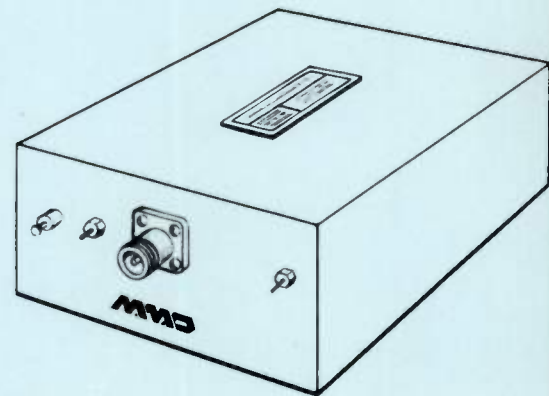



FEATURES:

- HIGH POWER HF BUILDING BLOCK MODULE
- 500 WATT LINEAR OUTPUT
- 50 OHMS IN AND OUT
- WIDEBAND 2 to 30MHz
- 14dB GAIN
- FLAT GAIN VS FREQUENCY
- INTERNAL VOLTAGE REGULATION AND REVERSE VOLTAGE PROTECTION






AC-0003-500W

500 WATT SOLID STATE AMPLIFIER MODULE

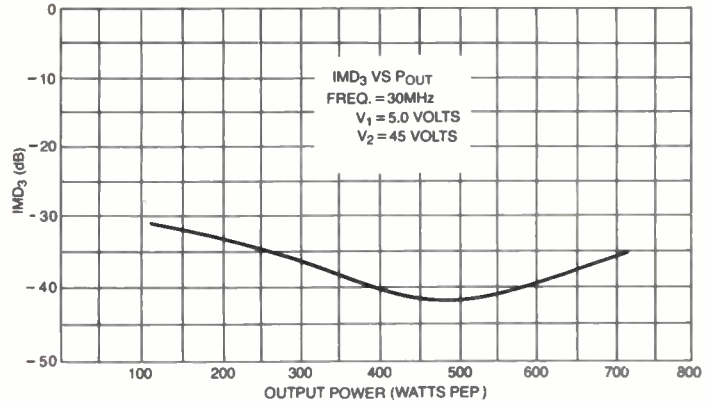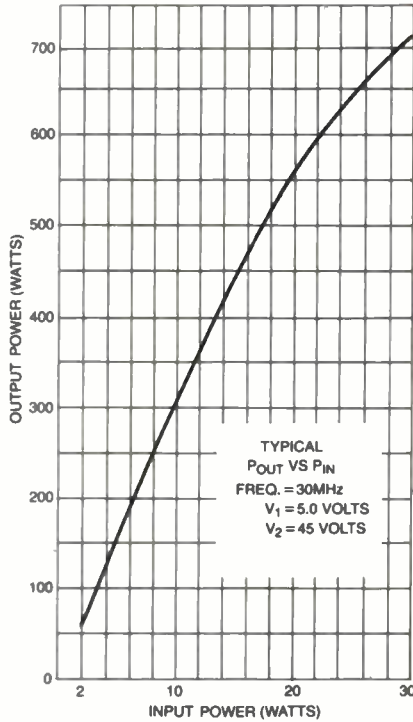

MICROWAVE MODULES & DEVICES, Inc.

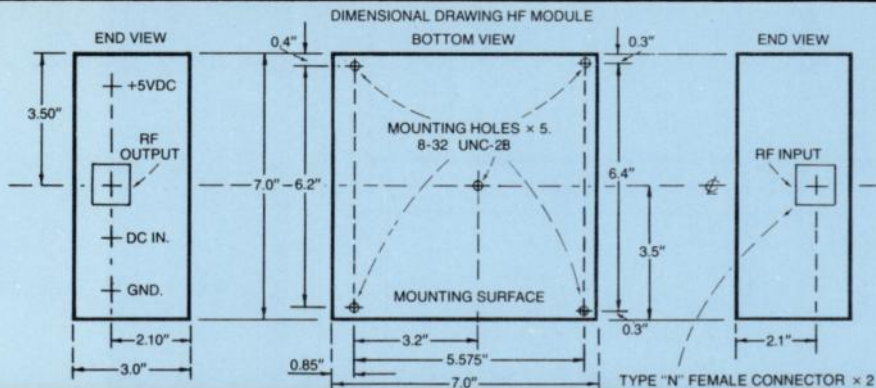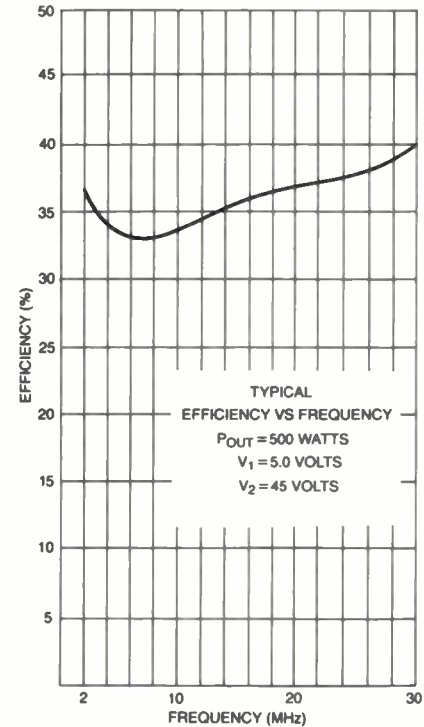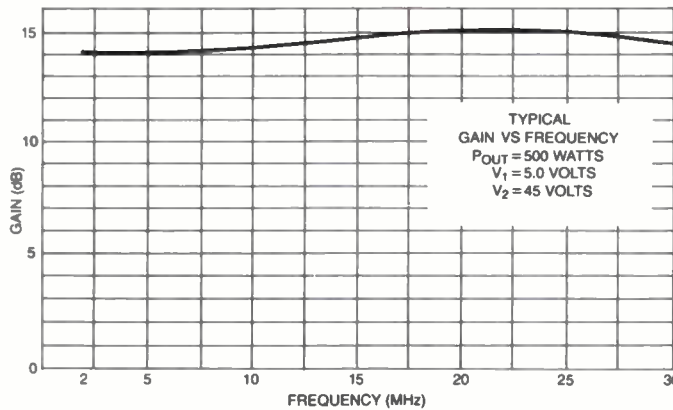

550 Ellis St., Mountain View, CA 94043 (415) 961-1473 TWX 508746



MICROWAVE MODULES & DEVICES, Inc.

FA-501

WIDEBAND RF FUNCTION AMPLIFIER

FREQUENCY RANGE: 5-500 MHz.

The FA-501 is an RF function amplifier that offers the circuit designer the versatility of an operational amplifier in both transmitter and receiver applications. With more than 20dB of reverse isolation and unconditional stability, a wide variety of systems problems can be solved. Features include 5.5dB noise figure, 10dB gain, 25dB AGC and a bandwidth that exceeds 500 MHz. In some applications the FA-501 is useful to 750 MHz. The compact unit is housed in a hermetically sealed package.

AMPLIFIER SPECIFICATIONS @ 25°C, $V_{CC} = +5V$.

Frequency Range:	5-500MHz.
Gain ($I_0 = 110$ ma)	10dB min.
Gain Flatness:	(G = 0 to 10dB) ± 1 dB (G = -15 to 10dB) ± 3 dB
Power Output @ 1dB Gain	
Compression ($I_0 = 110$ ma)	+10dBm min.
Noise Figure ($I_0 = 110$ ma)	5.5dB max.
VSWR (50 ohms)	Input: 2.5:1 max. Output: 2.5:1 max.
3rd Order Intercept Point ($I_0 = 110$ ma)	+20dBm typ.
2nd Harmonic	-25 dBc @ P_{1dB}
Suppression:	-40 dBc @ $P_{1dB} - 10$ dB.
Reverse Isolation:	20dB min.

AGC RELATED:

Control Range:	5-500 MHz: 25dB min. 5-100MHz: 30dB min.
Control Input Range:	+1 to +4 V 2 to 18 ma.
Response Time for 25dB Δ :	1 μ sec max.
Gain Stability: -30 to +50°C	4dB p-p max. (For Any Setting Within Specified Control Range)

ENVIRONMENTAL:

Operating Case Temp.	-55° to +85°C.
Storage Temp.	-62° to +125°C.


ABSOLUTE MAXIMUM RATINGS:

V_{CC}	+8 volts.
$V_{CONTROL}$ (Without External Resistor)	+5 volts.
Current (I_0):	150 ma.
RF Input Power At Any Port:	+13dBm.



MIXER CHARACTERISTICS:

Frequency Range:	LO: 5-500MHz. RF: 5-500MHz. IF: 5-500MHz.	Isolation:	LO-RF: 25dB min. LO-IF: 10dB min. RF-IF: 0dB min.*	Two Tone IM_3 : 35dBc at -10 dBm RF Port Power
Conversion Loss/Gain:	Minimum: -4dB. Typical: 0dB. Maximum: +2dB.	Noise Figure:	10MHz: 17dB 200MHz: 17dB 500MHz: 17dB	VSWR at R Port: 2.0:1 max. VSWR at L Port: 1.8:1 max. VSWR at I Port: 2.0:1 max. (5-500 MHz)

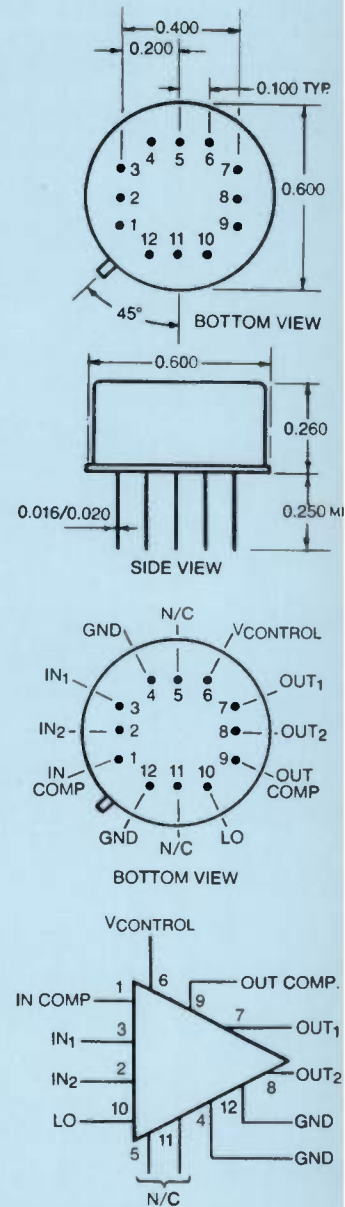
NOTES: 1. V_{cont} Set for $I_0 = 40$ ma.
2. LO Level: -5 dBm typical.
* Measured At 10MHz



TYPICAL APPLICATIONS

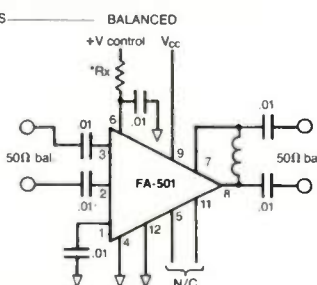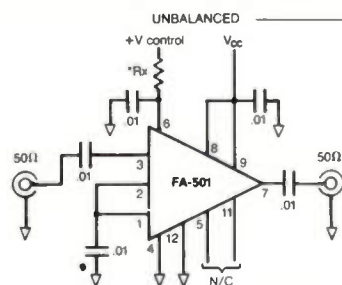

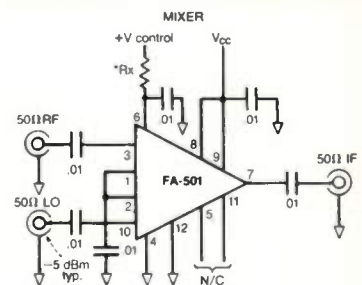* R_x required for control voltages higher than +5 volts:
 $R_x = 560\Omega$ for $V_{CONTROL} = +15V$.



* Set $V_{CONTROL}/R_x$ for $I_0 (V_{CC}) = 40$ ma.



MICROWAVE MODULES & DEVICES, Inc.









550 Ellis St., Mountain View, CA 94043 (415) 961-1473 TWX 508746



FA-501

WIDEBAND RF FUNCTION AMPLIFIER

FREQUENCY RANGE: 5-500 MHz.

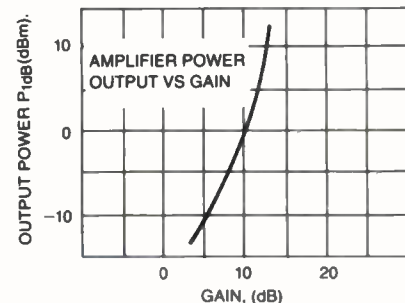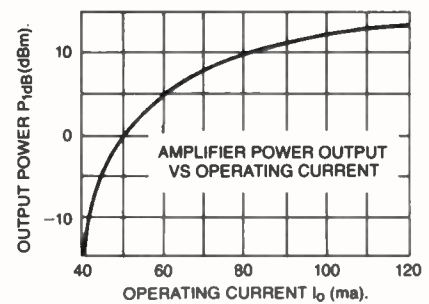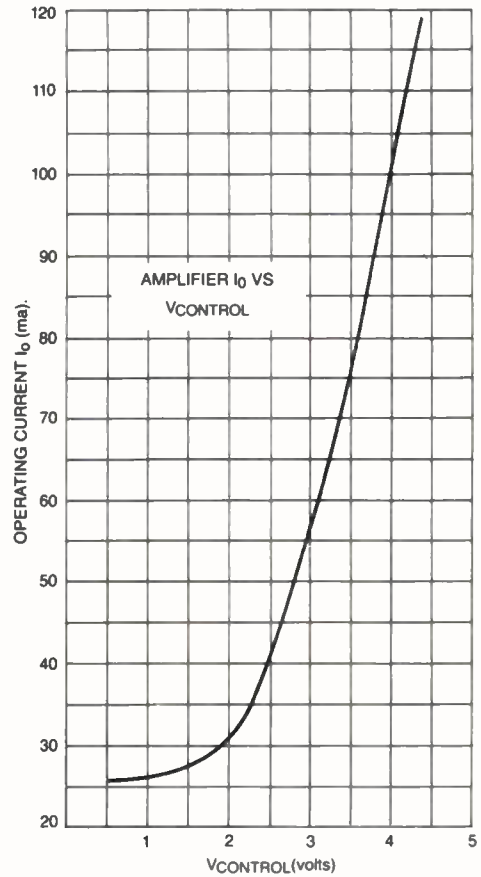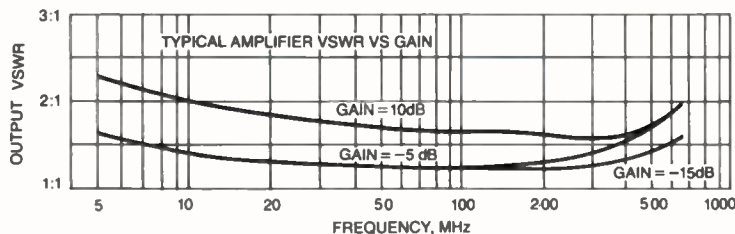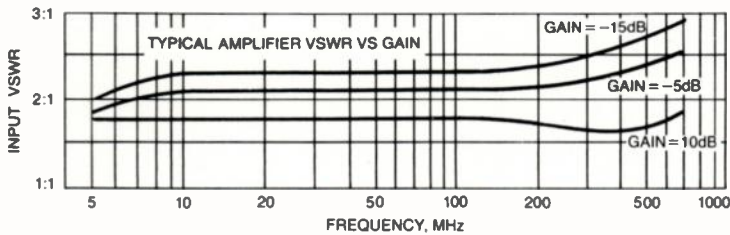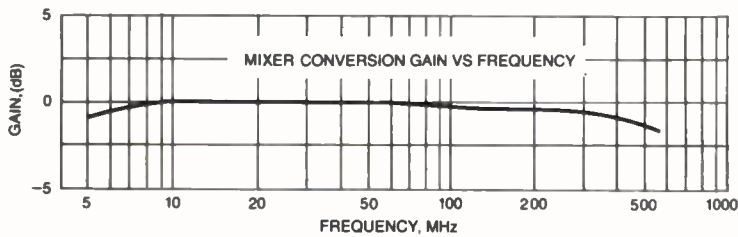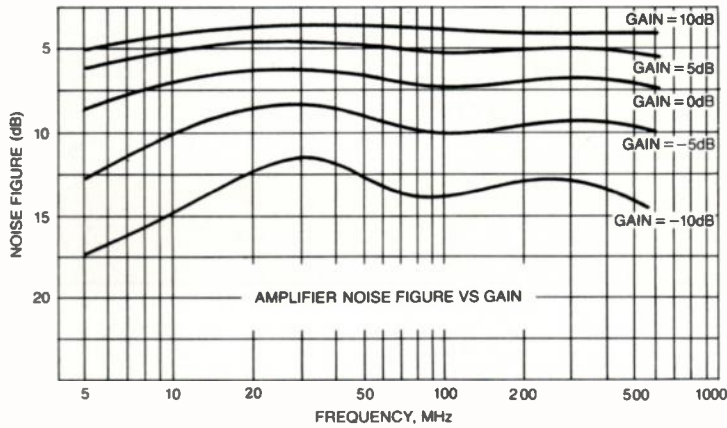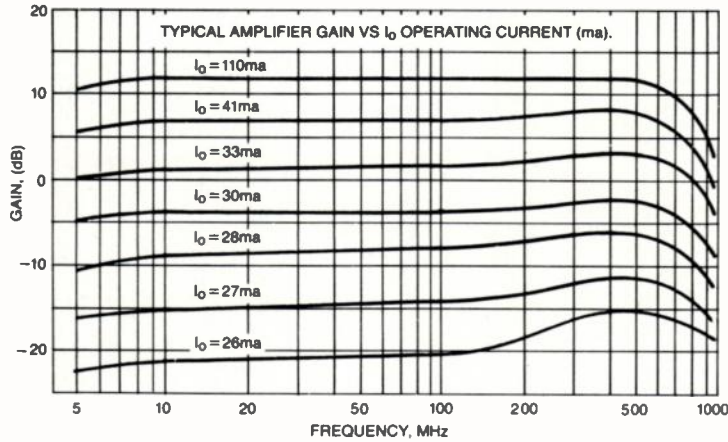

AT
\$3950
IT'S
A
GIANT.



IT'S THE NEW 2022 • 1GHz SIGNAL GENERATOR





Main Function Keys

For entry of carrier frequency, modulation depth or deviation, and r.f. level. The associated l.e.d. is lit when a function is selected.



Numeric Keypad

Provides rapid and accurate setting of parameters.

Δ Key

Allows step values of any size to be entered for the main functions.




Store/Recall

Up to 100 settings may be stored, and recalled instantly. When Recall l.e.d. is lit the increment keys are used to step through memory locations in sequence, giving fast semi-automatic selection of settings.



The model 2022 weighs only 16

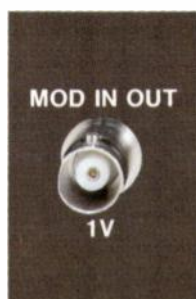

Mod. IN-OUT

Provides wideband modulation input for external a.m., f.m. or ϕ .m. with selectable a.l.c. and out-of-limits indicators to ensure high accuracy. Also provides output of internal modulation.



Unit Keys

Terminate parameter entry. They also provide single-key conversion of r.f. level settings, e.g. μ V to dBm.

Sets New Price/Performance Standards


Int/Ext

Selects internal or external frequency standard, or toggles between internal and external modulation source.




Second Function

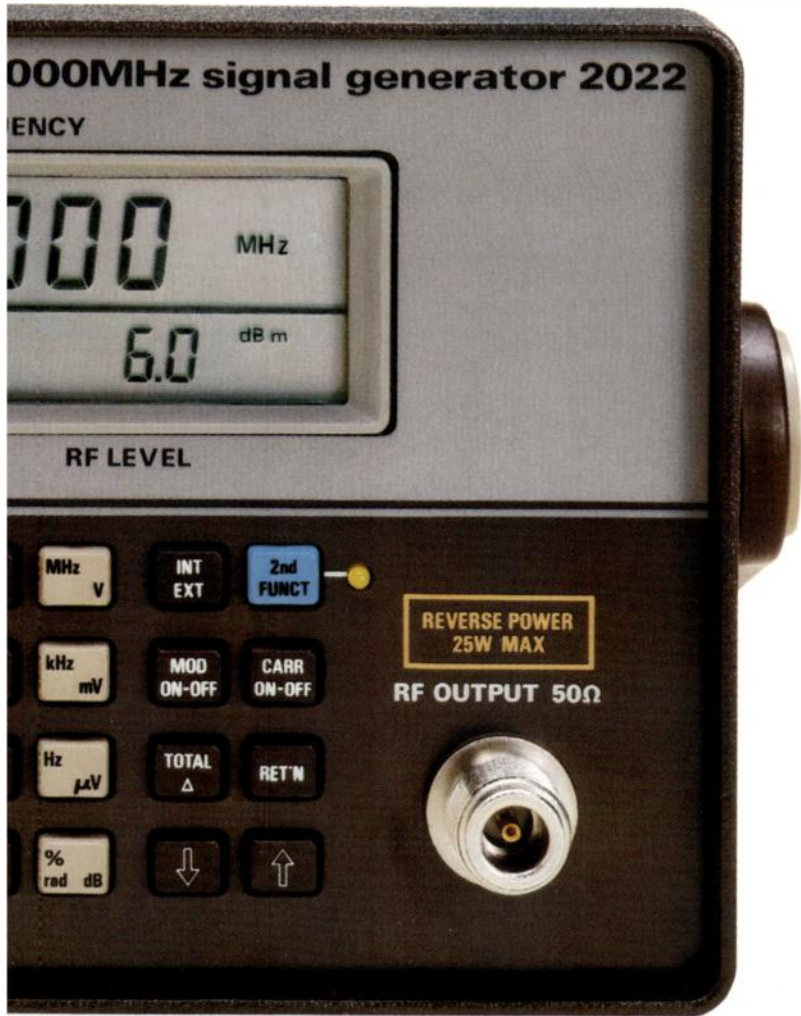Gives access to many extra and innovative facilities. Sensitive Second Functions are protected by a secure key sequence.



Mod. ON-OFF

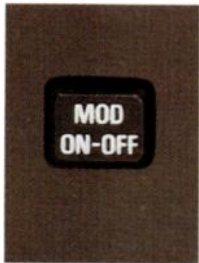Removes modulation, for speedy simple signal-to-noise measurements.



Carr. ON-OFF

Toggles r.f. output on and off. For fast measurements of quieting sensitivity, etc.



Illustrated precisely full size!

Incrementing Facilities

Allows any parameter to be incremented or decremented in pre-defined steps. TOTAL Δ plays the shift from initial settings. RET'N key restores initial setting.



RF Output

Delivers -127 to +6 dBm in c.w. and f.m. modes. Reverse power protection up to 25 W saves accidental damage to output circuits. Protection fail-safe — acts even with unit turned off.



Check Out These Unique Features And Benefits- Use The Reply Card For Full Specifications

Wide frequency range

10 kHz to 1000 MHz, enables 2022 to cover all bands from v.l.f. to u.h.f., including i.f. stages.

FM, ϕ M and AM output

Allows tests on a wide variety of receivers. 2022 gives peak f.m. deviations up to 99.9 kHz for all carrier frequencies, while phase modulation up to 9.99 radians peak deviation caters for the most up-to-date f.m. radios. And a.m. is available up to 99.5% depth.

Small and lightweight

All this performance in a package only 6" high by 10¼" wide. Weighing just 16½ lb, it's easy to carry for remote measurements or where access is difficult.

True non-volatile memory

Stores up to 100 measurement settings. This makes for rapid testing in routine measurements, especially when memories are stepped through using the increment facility. One set of measurement conditions can be recalled automatically at switch-on. A memory lock can safeguard settings and prevent accidental overwriting.

Fully programmable

With the optional GPIB module. The instrument acts as a talker and listener over the General Purpose Interface Bus, and this facility includes all front panel functions—including calibration settings—giving fast automated testing in maintenance and production.

Single easy-to-read l.c.d. indicator

Gives a clear simultaneous readout of carrier frequency, modulation and r.f. output level, with units annunciators and other information. The display can be disabled using a secure key sequence, preventing stored settings being shown, for example when they contain classified data.

10 Hz resolution

Provided to 100 MHz, for tests on narrow-band receivers such as SSB equipment.

Accurate output level

Ensures precise and consistent sensitivity measurements. Errors are less than ± 1 dB for r.f. levels above -10 dBm. Resolution is 0.1 dB.

Offset calibration

Enables allowance to be made for cable losses, or to ensure that all instruments in a particular area give identical results. Output level may be offset by up to ± 2 dB, in 0.1 dB steps.

Wide choice of RF calibration units

Lets users work with the units they choose to, and units may be converted by a single keypress.

External modulation

Is readily usable, with wideband input for a.m., f.m. or ϕ .m. HI or LO messages in the display together with the instrument's a.l.c., simplify the use of external sources.

Reverse power protection

Up to 25 W, prevents damage to the generator when power is accidentally applied while testing transceivers. Protection is provided even with generator off. Gives longer unit life and lower cost-of-ownership.

Rapid keyboard entry

Is provided by front panel keys with a logical layout. Parameters can be incremented with variable step sizes, simplifying operation even further. Manual measurements of bandwidth, sensitivity and modulation linearity could hardly be easier.

Easy to maintain

With powerful diagnostic aids. Available from the front panel or via GPIB, fault localization is fast. Careful mechanical design brings fast access to internal circuitry — for low M.T.T.R.

Elapsed time

And total operating time indications are available from the front panel, enabling calibration intervals to be recorded or fault and usage statistics to be compiled.

Choice of external standard frequencies

Universally compatible with 1, 5 or 10 MHz references.

All This For *3,950—Act Now!



3 Pearl Court,
Allendale, New Jersey 07401
East (201) 934-9050 • West (714) 895-7182




Frequency-Temperature Performance Determination In High Stability TCXOs

By Dennis Marvin
Motorola, Inc.
Communications Systems Division

The temperature compensated crystal oscillator (TCXO) has been with us for over thirty years and is quite often taken for granted. However, as frequency vs. temperature (f-T) stability requirements continue to tighten, many of the previously ignored second order effects will have a significant impact. TCXO stability requirements of 0.5PPM or 2PPM over temperature ranges as wide as -55 to $+95^{\circ}\text{C}$ are becoming commonplace. This article will review several of these second order effects and attempt to quantify the amount of performance debasement that can result.

AT-cut crystals are commonly assumed to have an f-T characteristic that can be represented by a third order polynomial. While this fit is quite adequate for most current applications, it can be inadequate for tight f-T requirements over wide temperature ranges. Figure 1 shows the difference between actual data and the least squares third order curve fit for a typical fundamental crystal. There is a decided, consistent fourth order component. Oscillators with f-T stabilities approaching 1PPM must incorporate a compensation scheme capable of correcting for the fourth order term and crystal evaluation algorithms must do a fourth order fit to insure that good crystals are not discarded.

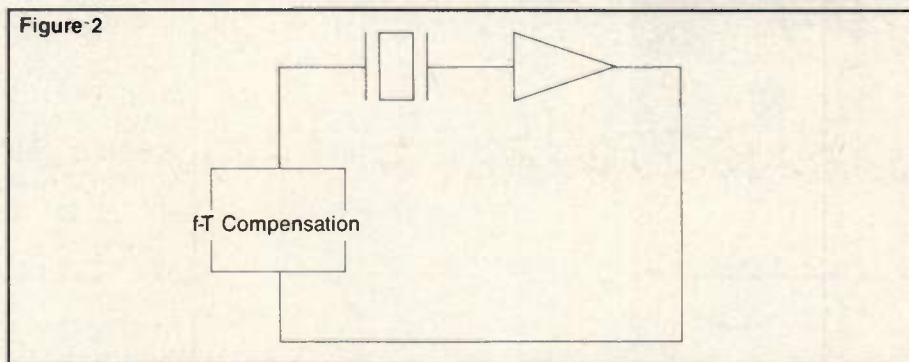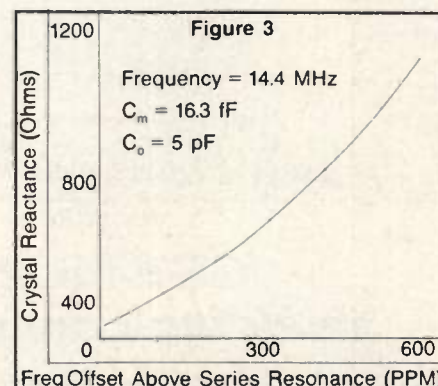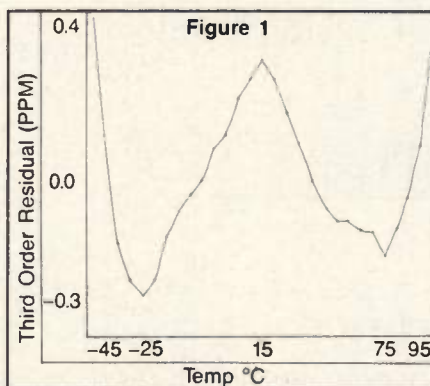Tight tolerance TCXO designs are further complicated by component TC and non-linear transfer characteristics. Even though the frequency stability of an AT-cut crystal is almost always less than 1PPM/ $^{\circ}\text{C}$, work at Motorola and by Holbeche and Morley(1) has determined that the motional capacitance, C_m , of a



fundamental crystal varies approximately 230PPM/ $^{\circ}\text{C}$. This variability must be addressed during the oscillator design. The varactor and its operating voltage must be carefully selected. If a varactor with a non-linear V-X characteristic is used, the compensation network will have to generate a more complex V-T function to compensate for the distorted varactor transfer function. Similarly, if a nonlinear varactor is used for both temperature compensation and aging adjust, the amount of compensation will change as the aging is corrected.

Background

A fundamental AT-cut (3-20 MHz) TCXO can be simply represented by the block diagram of Figure 2, where the feedback scheme is incorporated into the amplifier block. This block can represent any of the common configurations: Colpitts, Pierce or Clapp. The oscillator operates by meeting Barkhausen's criterion; the sum of the reactances around the loop must equal zero, with the crystal operating at whatever frequency meets this requirement. Figure 3 shows that the crystal reactance is a function of fre-

NEMP—Tester for EMP-Tests

The portable PEMI 12 tester simulates the fast impulses generated by high altitude nuclear explosions. Test your instruments and electronic assemblies with this tester delivering a $<10/400$ ns impulse with an adjustable peak voltage of 0.5 - >10 kV! The bus bar connector allows fitting a 150Ω parallel strip line antenna accommodating a standard 19" EUT and subjecting it to an



E-field of 50 kV/m. Separate current injection output for peak current up to 150 Amps!

If you care whether your equipment is NEMP-proof you should call us or send us the bingo card. We have a lot of experience with NEMP testers with extremely fast rise times, charging voltages up to 1.5 MV and we manufacture them also to NATO specs.


AMERICAN

HV TEST SYSTEMS, INC.

Telephone (301) 826-8651 Telex 86223
Central Garrett Industrial Park, Accident, MD 21520


INFO/CARD 27

GST-MC2 Shielding Laminates

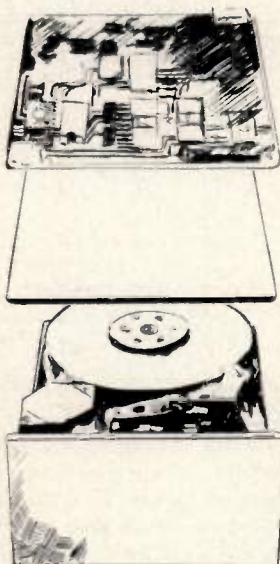

When it comes to direct shielding of printed circuit boards, Glasteel Industrial Laminates will help keep you covered with GST-MC2 shielding laminates.

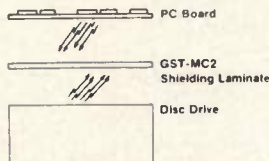Applications include die cut forms to reduce RFI in disc drives, card cage PC board radiated interference, or aesthetic coverings for walls to effect shielding to E fields of greater than 120 dB at 1 MHz to 70 dB at 500 MHz.



Features:

Excellent fabricating qualities
May be die-cut to almost any size and shape



Inquire for your special requirements

Glasteel Industrial Laminates

A DIVISION OF THE ALPHA CORPORATION
P.O. BOX 217 • 1727 BUENA VISTA • DUARTE, CA 91010
(213) 357-3321



INFO/CARD 28



PRECISION CRYSTAL OSCILLATORS SERIES 8000

STANDARD FREQUENCY 5.0 MHz

AGING RATE _____ MODEL ER8001 1×10^{-9} /day
MODEL ER8003 1×10^{-10} /day
MODEL ER8005 5×10^{-11} /day

PHASE NOISE _____ SSB 1 Hz BW at 10 Hz offset
MODEL ER8001 . . . 124 db
MODEL ER8003 . . . 135 db

INPUT VOLTAGE _____ 12 VDC $\pm 10\%$ STANDARD
OUTPUT _____ SINE-WAVE 1VRMS INTO 50 ohm LOAD

SIZE _____ MODEL ER8001 and
MODEL ER8003
2" x 2" x 4" H
MODEL ER8005
2.25" x 2.25" x 4.25" H

OPTIONS _____ MANY OPTIONS ARE AVAILABLE TO INTERFACE WITH YOUR REQUIREMENTS

ELECTRONIC RESEARCH COMPANY SERIES 8000 PRECISION OVENIZED CRYSTAL OSCILLATORS ARE THE ULTIMATE CHOICE WHERE PROVEN RELIABILITY AND FREQUENCY STABILITY IS REQUIRED. THESE OSCILLATORS ARE IDEAL FOR APPLICATIONS WHERE A PRECISION TIME BASE IS TO BE MULTIPLIED OR SYNTHESIZED REQUIRING A LOW PHASE NOISE SOURCE. ALL ELECTRONIC RESEARCH COMPANY'S OSCILLATORS UTILIZE QUARTZ CRYSTALS MANUFACTURED BY ERC FOR MAXIMUM CONTROL ON ALL PARAMETERS TO INSURE PERFORMANCE SPECIFICATIONS. IF YOUR APPLICATION REQUIRES SUPERIOR OSCILLATOR PERFORMANCE CALL US OR WRITE FOR OUR COMPLIMENTARY CATALOGUE.

For information and prices, send your specifications to:




FREQUENCY CONTROL PRODUCTS
electronic research company

7618 Wedd Overland Park Kansas 66204
TWX: (910) 749-6477
Telephone: (913) 631-6700

INFO/CARD 29

This narrow strip...

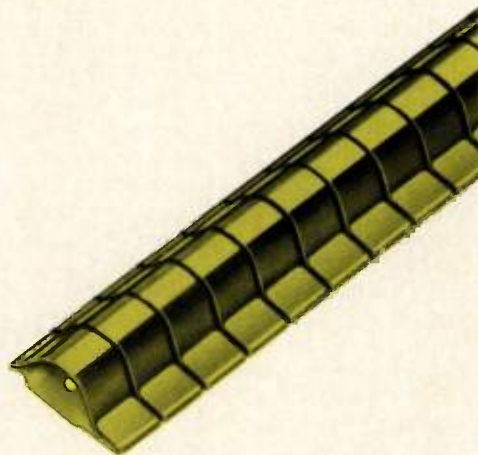

quency by following the nonlinear relationship:

$$X = 1 / ((C_m / 2 \Delta f / f - C_o) w)$$

Where: C_m is the motional capacitance of the crystal model;
 C_o is the capacitance of the crystal plate, the holder and any associated stray circuit capacitance;
 $\Delta f / f$ is the fractional frequency change of the crystal from series resonance.

Such a circuit can be temperature compensated by having a compensation block that generates a reactance characteristic as a function of temperature such that it causes the crystal to change the operating point on its reactance curve. By carefully designing this block the crystal can be operated so as to cause a net "zero" frequency change over temperature.

There are several networks that are used for the compensation block, both direct and indirect. The preferred circuits are indirect, i.e., a DC voltage is generated external to the oscillator loop and is used to vary the loop reactance via a varactor. Direct compensation, where the compensation is inserted directly in the oscillator loop, has fallen on disfavor, as its use lowers circuit Q. Of the several methods of indirect compensation used, including custom integrated circuits and digital compensa-

tion, the most common and the most easily understood is thermistor-resistor compensation. One embodiment of this is shown in Figure 4(2). Other designs can be similarly analyzed.

If we assume that the varactor has a $\partial = 1$ (not bad for hyperabrupt varactors over a limited voltage range) and that all other parts in the oscillator are constant over temperature ms. characteristic of the crystal. This is a good approximation for initial analysis purposes, with corrections necessary for an exact compensation.

In any case, this thermistor-resistor network has the following transfer function:

$$V_{out} = V_{in} \frac{RT_3(R_1 + RT_1)(R_2 + RT_2)}{(R_1 + RT_1)(R_2 + RT_2)(R_3 + RT_3) + R_2 RT_2(R_1 + RT_1 + R_3 + RT_3)}$$

where RT_1 , RT_2 and RT_3 are the resistances of the three thermistors at a particular temperature.

R_1 and RT_1 affect performance over the entire temperature range, while R_2 and RT_2 primarily affect the cold end and R_3 and RT_3 primarily affect the hot end. Care must be taken to obtain suitable parts values so the appropriate transfer function can be obtained while still maintaining a high degree of independence among the temperature ranges. The use of a personal computer to gather f-T data and process it reduces the need for in-

dependence among the compensation sections.

Parts Aging

When oscillators are being temperature compensated one is normally concerned with passing the specification at a half-dozen or so temperatures with a little margin for measurement error. This is quite adequate for oscillator stabilities of 5PPM or looser, but if a tighter system stability is required parts aging can become very important.

Parts aging can have two effects on the oscillator stability. The first is a positive or negative frequency shift over the entire temperature range, i.e., the oscillator will have the same f-T characteristic after aging has occurred as it did before, but the whole response has a new room tem-

TYPE	AGING
Resistors	
Carbon Comp	>10%
Carbon Film	3 to 5%
Thick Film	1 to 5%
Metal Film	1.5 to 2%
High Precision Metal	
Film Thermistors	0.1 to 0.5%
Non-hermetically sealed	1 to 5%

TABLE 1

perature reference frequency. A more insidious result of parts aging is the distortion done to the f-T response.

Over the life of a product, the resistors and thermistors can age as shown in Table 1.

The effects of parts aging on frequency drift and the f-T characteristic can be determined by inserting a small resistor or thermistor change (e.g., 1%) into the transfer function and analyzing the results. Parts changes of + and - 1% for all of the resistors and thermistors in Figure 4 were inserted and the resulting errors maximized by proper selection of sign. The maximum offset was 36mV or 0.61PPM given a sensitivity of 17PPM/V. Figure 5 is a plot of the maximum f-T distortion. Changes in f-T performance as poor as 0.80PPM/% change are possible. Allowing the 1% aging to occur in a random direction among the resistors and thermistors, there is on average a 0.27PPM/% offset and a 0.41PPM/% f-T distortion to the T.C. curve.

Of these figures the f-T distortion is by far the more serious problem, since a means of frequency adjust can usually be provided to compensate for the frequency drift. With these results now available, the

appropriate resistors and thermistors can be specified and the initial f-T specification appropriately tightened so that system stability can be maintained to allow for compensation aging.

Frequency Adjust Aging

Compensation aging isn't the whole story, unfortunately. The major source of frequency drift is almost always the crystal. This drift is normally corrected by adjusting a capacitor or inductor in the oscillator loop to shift the operating point in the crystal curve and thus return the oscillator to nominal frequency. This shift in operating point also distorts the f-T characteristic and is known as trim effect. Galla and McVey(3) have developed equations to quantify this distortion for both series and parallel adjust circuits (see Figure 6). The values shown are typical for a fundamental frequency equivalent circuit. These equations are:

f-T distortion (PPM)

$$\frac{\text{SERIES}}{4\pi C_o(C_o+C_1)X_{10}-3} \frac{C_1 C_m}{C_1 C_m}$$

$$\frac{\text{PARALLEL}}{4\pi(C_o+C_1)X_{10}-3} \frac{C_m}{C_m}$$

where a is the amount of aging to be corrected (PPM)

p is the amount of temperature compensation (PPM)

C_o is the crystal and holder capacitance (pF)

C₁ is the load capacitance seen by the crystal (pF)

C_m is the motional capacitance of the crystal (fF).

As the distortion in the series adjust configuration is equal to that of the parallel adjust multiplied by C_o/C₁, and this term is significantly less than 1, the series performance far surpasses that of the parallel. The parallel adjust should never be used in a high stability design if the use of a series is possible. Even if a series adjust is used, an additional 0.17PPM distortion will be generated. Figure 7 shows the f-T characteristic for a series adjust oscillator and its trim effect.

There are several ways that this problem could be alleviated. If C_m were increased, the distortion would decrease. However, all things being equal, C_o would increase in proportion to C_m. Additionally, the larger C_m becomes, the more the variations in the oscillator components affect performance.

The easiest way to reduce this distortion is to reduce p, the amount of temperature compensation, by carefully selecting the crystal angle. It can be further reduced by not overspecifying the temperature range. The smaller the temperature range, the smaller p will be.

Reducing a, the amount of aging to be corrected, is also possible. This can be done by using a better aging design, preaging the crystals or by sorting them for aging. Remember that a reasonably well made crystal will age approximately as much in the first year as it will age in the next ten years combined.

Voltage Regulator Contributing

In addition to the compensation circuitry and the crystal aging, one must also consider the voltage regulator circuit driving the compensation. The regulator is very important, as any voltage variations in it are directly coupled to the varactor and will create drift and distortion problems.

Using the compensation network of Figure 4 and allowing the regulator to vary +1mV/° (a fairly typical value for a fixed commercial regulator) results in an f-T distortion of about 0.4PPM, as shown in

DATUM's Model 9390 GPS Time and Frequency Monitor

DATUM's 9390 provides a cost-effective means of synchronizing precision clocks and timing instruments to within better than 100 nanoseconds of GPS time. The unit employs C/A code transmissions from the GPS satellite constellation and produces corrected 1-pps and 1-ppm reference outputs.

Scheduled satellites are automatically acquired and tracked for time and frequency determination. Only one satellite is required when geographical coordinates of the antenna are known. Otherwise, positioning is performed by tracking four satellites.



Front panel controls are provided for manual control. Remote control and data transfer are accommodated by an RS232C I/O port.

Entirely self contained, the 9390 is supplied complete with antenna/preamp and cable. Several optional features are available.

DATUM also manufactures a comprehensive line of timing instrumentation, from individual displays to complete range timing systems.

For complete information or applications assistance, call or write today.

Datum inc
TIMING DIVISION

1363 S. State College Blvd.
Anaheim, California 92806
(714) 533-6333

...or this narrower strip...

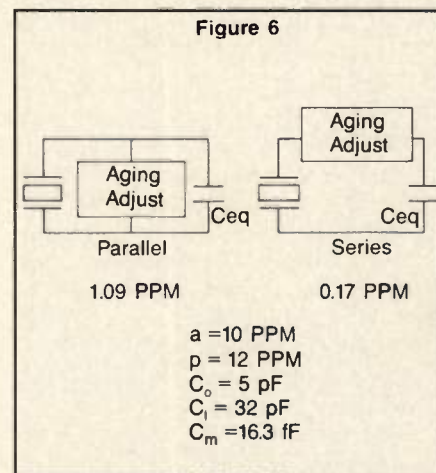
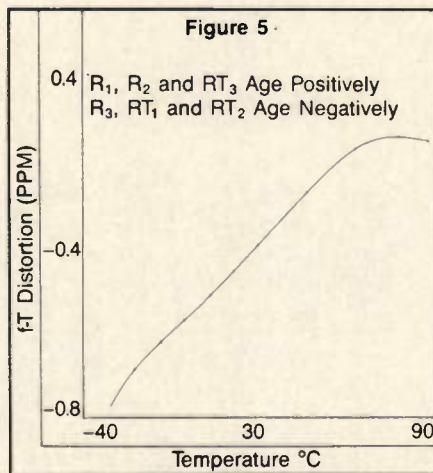
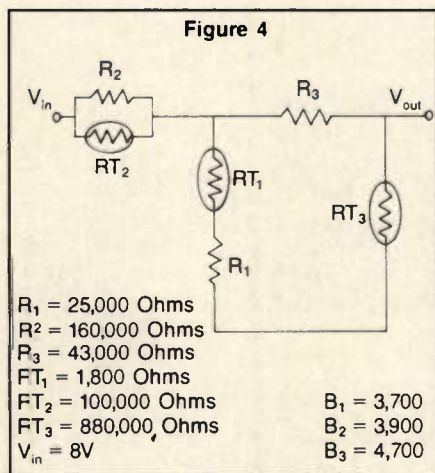
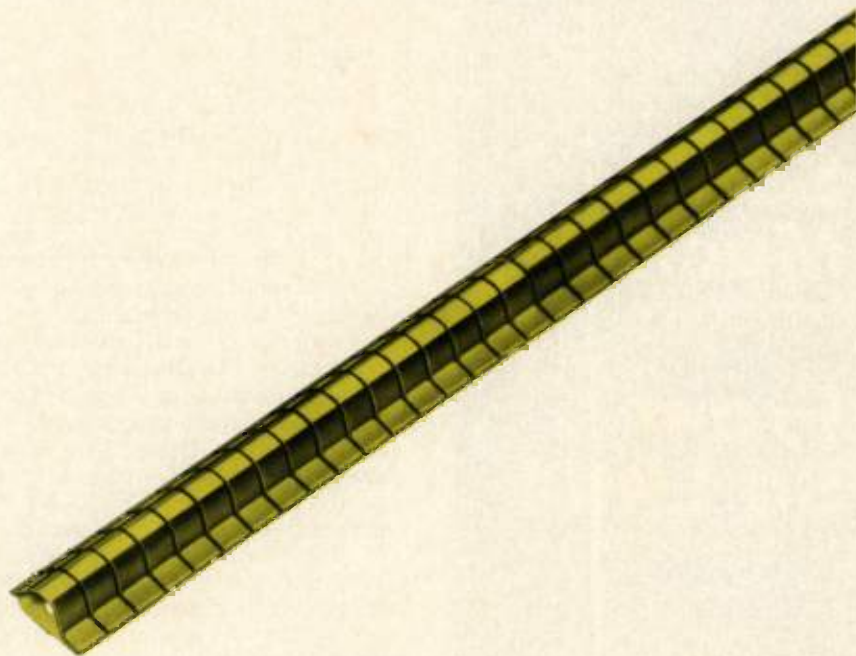


Figure 8. The only way to alleviate the problem of regulator voltage variation with temperature is to temperature compensate the oscillator with an internal regulator so that the temperature variations are compensated out.

Even with a built-in regulator, there is still the potential for aging. Figure 9 shows the distortion for a +1% change in regulator voltage.

Hysteresis

Crystal oscillator frequency performance can be very dependent on environmental dynamics. The designer must consider what dynamic frequency

stability is required and what maximum rate of change of temperature the oscillator will see. The temperature of the oscillator does not normally change nearly as fast as the ambient, as it is generally well isolated inside the system.

There are two major contributors to the hysteresis problem. The most easily visualized is the imbalance in thermal time constants among the several thermistors and the crystal. Time constants for thermistors in still air range from less than 0.1 sec. for small chips to over 10 sec. for 0.1 inch diameter beads, while typical HC-18 crystals have time constants of from 1 to 2 minutes. There is a

lot of variability in the crystal time constant. Important parameters causing this variability include package, lead and mount material and size, crystal blank size, crystal mounting technique and the type and density of gas sealed in the package.

There are so many variables present that the best way to determine the magnitude of the frequency shift is to measure it for the particular application. Tests performed on a hand-held 2-way radio subjected to a -30 to $+90^\circ$ temperature shock have given shifts as large as 0.3PPM.

If a product will be subjected to severe



Actual Size

So Much

Frequency range 17-250 MHz

From So Little

.12" diameter x .32" high

Or how about an HC45 package that meets or beats performance specs of similar fundamental crystal filters three times its size? The industry's smallest matched filter sets? They're all ours.

Our crystals, monolithics, discretes, and time delay filters come in sizes tough to imagine. With specs tough to match. At prices tough to beat. And as for durability, they're just plain tough.


At Sokol, we help you conquer space. By saving it.



Sokol
Crystal Products, Inc.

Where the Impossible Becomes the Ordinary
121 Water St., Box 249, Mineral Point, WI 53565
Phone 608-987-3363, Telex 467581

Figure 7

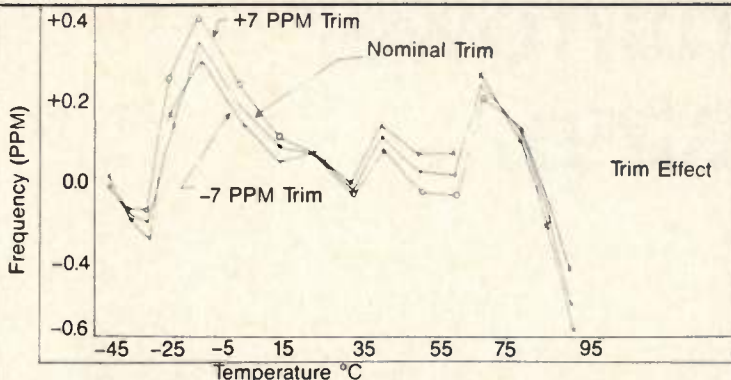

swings, this effect can be reduced by better matching time constants through thermally coupling the compensation temperature sensors to the crystal or by increasing the shorter time constant.

The second hysteresis problem lies within the crystal. If an AT-cut crystal undergoes a temperature change, stresses will be set up within it. As the temperature of the crystal is swept back and forth an f-T characteristic is generated that traces a loop about the familiar static characteristic. The direction and magnitude of this offset is dependent upon the particular crystal design, the

temperature range and the speed with which the temperature is changed.

Ballato(4) has modified this effect by changing the familiar crystal model from

$$f/f = a_0 \Delta T + b_0 \Delta T^2 + c_0 \Delta T^3$$

to


$$f(t)/f = a(t) \Delta T(t) + b_0 \Delta T^2(t) + c_0 \Delta T^3(t)$$

where $a(t) = a_0 + \hat{a}T(t)$ with \hat{a} being evaluated separately for each crystal design.

For a particular design where the

AMPLIFIERS, 5MHz-1GHz

- MIL-STD-883B Screening

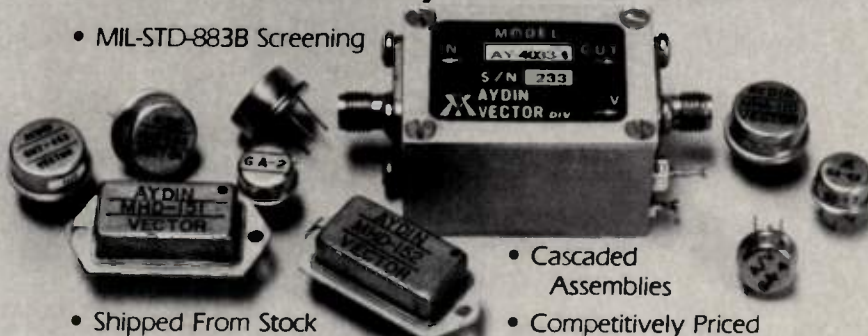

- Shipped From Stock




- Cascaded Assemblies
- Competitively Priced

Series	Freq Range (MHz)	Typ. Gain (dB)	Noise Figure Range (dBm)	Power Output Range (dBm)	VSWR		Input Power		Package Style
					In	Out	Vdc	I _{ma}	
GA Single-Stage	kHz-400	13	4.5-6.0	5-15	2.0	2.0	+15 typ.	17-70 (range)	TO-12
MHT Single-or Multi-Stage	5-1000	14	2.5-7.0	-2 to +23	2.0	2.0	+15 typ.	10-105 (range)	TO-8
GHT Single-or Multi-Stage	5-400	13	4.0-7.0	5-15	2.0	2.0	+15 typ.	17-70 (range)	TO-8
MHD Multi-Stage	1-500	21	2.5-6.5	5-20	1.6 (typ.)	1.6 (typ.)	+15 typ.	50-115 (range)	4-pin DIP

Aydin X Vector

P.O. Box 328, Newtown, PA 18940 • TEL 215-968-4271 TWX 510-667-2320

...or these even narrower strips...

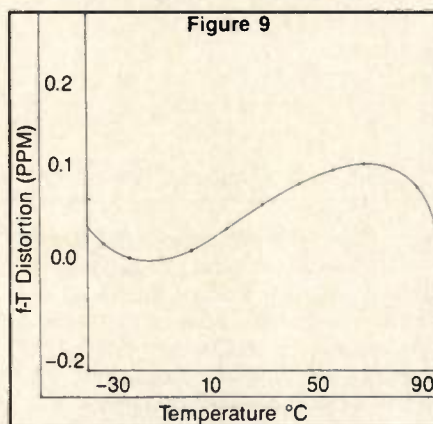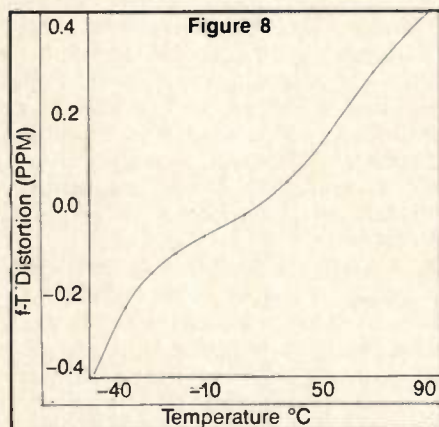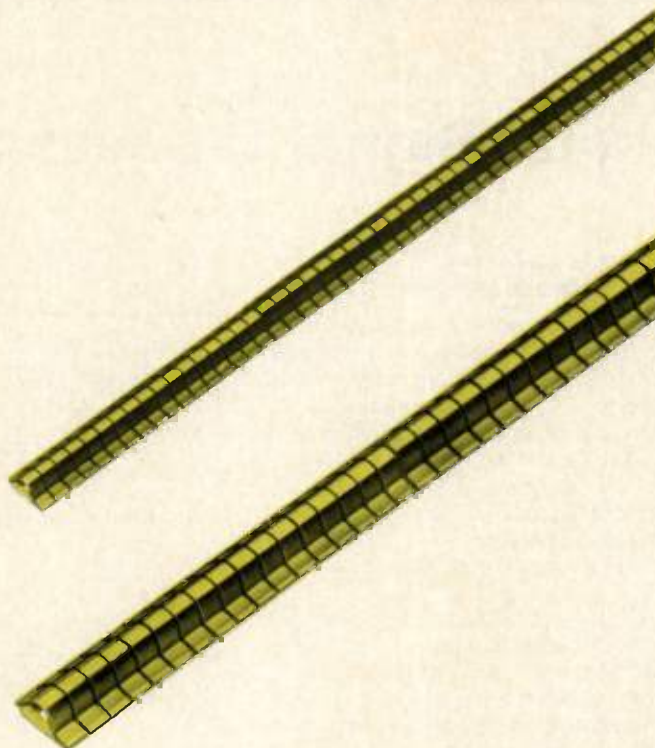


temperature is varied in a sinusoidal manner + and - 60° about 30° at a frequency of 0.01Hz (an orbital time of 628 sec.) the peak deviation from the static curve was 7.2PPM. As the deviation is linearly related to the frequency of the temperature change for this model, the maximum orbital time to keep the peak deviation below 0.1PPM for this crystal is 12.6 hours. Hence, fast temperature changed can and do affect the desired stability. It should be stressed that the magnitude and direction of this deviation is quite crystal dependent, with this example tending to be worst case, and that this is the peak error over the entire temperature loop.

Conclusion

High stability TCXOs are subject to many instabilities not normally considered in the design of lower stability products. Several of these have been reviewed. The design engineer must carefully consider the system requirements in dynamic environments and as a function of time.

For example, the design Motorola has chosen to use is shown in Figure 10. The as shipped f-T stability requirement is as tight as 1PPM from -40 to +95° with a total system stability of better than 2PPM. In order to accomplish these specification and still maintain a small package size (< 0.3 cu.in.) while minimizing costs, a

 custom integrated circuit in a hermetic chip carrier was used (5). The chip consists of a three segment non-linear compensation ms, but has improved isolation between the stages for ease of production. Compensation is achieved with four trimmable resistors. Hermetic sealing of the IC minimizes regulator drift. Parts drift is minimized by utilizing the matched TC characteristics in the IC design while good crystal aging is maintained by pre-aging and then sorting crystals with a curve fit routine using data obtained by actively aging the crystals. Hysteresis is also minimized through crystal sorting and with attention to thermal design. Overall hysteresis and aging are further controlled by hermetically sealing the entire oscillator. 

References

1. Holbeche, R.J. and Morley, P.E., "Investigation into Temperature Variation of Equivalent-circuit Parameters of AT-cut Quartz Crystal Resonators," IEEE Proc., vol 128, pt. A, no. 7, October 1981, pp.507-510.
2. Frerking, M.E., *Crystal Oscillator Design and Temperature Compensation*, Van Nostrand Reinhold Co., 1976.
3. Galla, W.D. and McVey, E.S., "TCXO Error Due to Aging Adjustment," PROCEEDINGS OF THE 34th ANNUAL SYMPOSIUM ON FREQUENCY CONTROL, pp.504-508.
4. Ballato, A., "Static and Dynamic Behavior of Quartz Resonators," IEEE TRANSACTIONS ON SONICS AND ULTRASONICS, vol. SU-26, No. 4, July 1979, pp.299-306.
5. Keller, T., Marvin, D. and Steele, R., "Integrated Circuit Compensation of AT Cut Crystal Oscillators," PROCEEDINGS OF THE 34th ANNUAL SYMPOSIUM ON FREQUENCY CONTROL, pp. 498-503.

Digital Signal Processing

By Thomas Callaghan
Watkins-Johnson Company

Digital signal processing is not an easy topic to comprehend. It combines theories of both the analog and the digital disciplines. To ease this understanding, one should remember that all aspects of DSP can be divided into three areas:

- 1) Input Signal
- 2) Digital Processor
- 3) Information Extraction

The input signal must be sampled and quantized before it can be fed to the digital processor. The digital processor can only perform the operations of addition, multiplication and delay (storage) on the signal data. The end result of the digital processor is to extract information from the signal or modify it in some way. This article will explain the input signal.

The input signal, which is analog in nature, can be classified as a continuous time, continuous amplitude signal. To be of a form useful to a digital processor the signal must be converted to a discrete time, discrete amplitude signal.

Sampling

Sampling is the process by which the continuous time, continuous amplitude signal is converted to a discrete time, continuous amplitude signal. This is done by periodically taking minute time chunks out of the analog signal. The output of a sampler is a series of pulses whose envelope approximates the original signal. The process can be represented by multiplying the input signal by a pulse train of uniform amplitude and equal spacing, (Figure 1).

The pulse spacing, T , that is the sampling frequency, $1/T$, cannot be arbitrarily chosen. According to the Sampling Theorem, "If a continuous time function contains only frequency components below F cycles per second, $2F$ samples per second suffice to represent it perfectly and permit perfect recovery." The reason for this is more readily seen in the frequency domain. Referring to Figure 2, one can see that one of the byproducts of sampling is the duplication of the signal every F_s , the sample frequency. If the sample frequency is kept above or equal to $2F$, (Figure 2b), the sampled frequen-

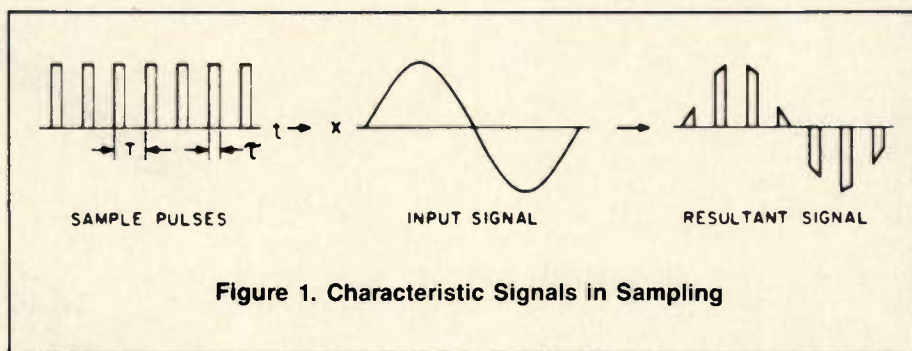


Figure 1. Characteristic Signals in Sampling

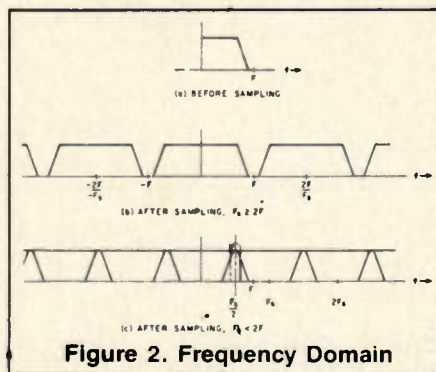


Figure 2. Frequency Domain

cy spectrum produces no overlap and the original signal can be retrieved. If the sample frequency drops below $2F$, the sample frequency spectrum starts to overlap. Any of the frequencies whose spectra are contained in this overlap tend to fold over about $F_s/2$ and into the actual frequency band, as indicated in Figure 2C. This foldover of frequency is called aliasing.

Examples of frequency aliasing are witnessed daily by many unknowing observers. For example, in the old "Westerns," the stage coach rides out of town and its wheels appear to speed up, stop and then go backwards. The backwards revolution is caused by the movie camera not taking sufficient frames per second to dependably capture the wheel's revolution. Another example is when a television or computer terminal is shown in a movie with black bars across the screen. Again, the movie camera is not updating the screen fast enough. In this case, the camera moves at 24 frames per second while the television scans a new frame at

60 times per second.

The sampling theory is all well and good on paper, but in reality it is difficult to remove all unwanted frequencies above the frequency of interest. The most common solution is to place a filter ahead of the sampler to remove unwanted frequencies. The filter, however, has two disadvantages; it alters the signal of interest and unless it has very steep skirts certain unwanted frequencies are passed. A second solution is to sample at a faster rate than $2F$. How much faster is open to debate. Sample too fast and one puts an undue burden on the digital processor.

Another consideration in determining sampling frequency is interpolation errors. Since one is dealing in discrete time, what has happened to the input signal between samples is not known. Naturally, the faster the sample rate the more information known about the signal. When processing is finished, it may be desired to convert back to an analog signal. The conversion is usually done with a D/A converter and some type of low-pass filter to smooth, or interpolate, the discrete points.

So how does one select the sample rate? Gardenhire in [1] presents a good approach to the problem. In his work, the sampling rate is based upon the amount of interpolation error tolerable from the output filter given a specified input filter roll-off characteristic. The input filter roll-off determines the order of the system. Given a certain roll-off, m , the sample rate can be determined from the acceptable interpolation error. The rate is given for a 5% error in Table 1.

...can solve your interference control problems!

Are you involved with FCC Class A and/or Class B Computing Devices—or any other equipment requiring shielding? Instrument Specialties' new, patented* beryllium copper Sticky-Fingers® shielding strips can help you solve your problems!

They offer the attenuation you need, of course. And to attach, you need only peel off the self-adhesive backing strip and press into place. It's there to stay!

What's more, unlike other shielding strips, Sticky-Fingers will not take a set which would reduce performance *after you felt it was satisfactory*. Sticky-Fingers *can't* absorb moisture, are not affected by air, ozone solvents, UV light, or radiation. They can't burn, support combustion, outgas; they can't stretch or tear, flake or break into small conductive particles to short out electronics.

For more information, write today to Dept. RF-7.

INSTRUMENT SPECIALTIES COMPANY, INC.

Delaware Water Gap, PA. 18327

Phone: 717-424-8510 • TWX: 510-671-4526


Specialists in beryllium copper since 1938



INFO/CARD 34

97-515
.760" wide

*Pat. No. 3504095

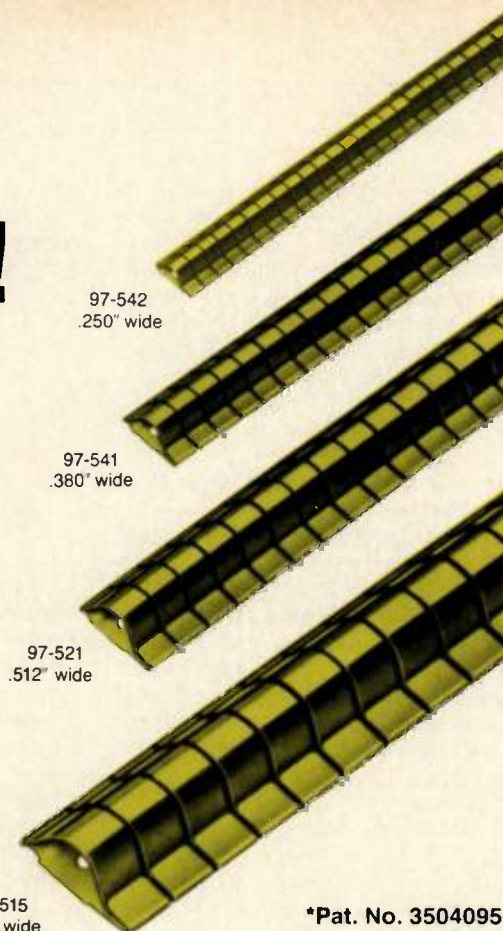

The filter method employs analog interpolation after D/A conversion. The 2, 3, or 4 point linear interpolation method is done via a computer and the output is still in a digital format. It is interesting to note how the sample rate approaches the theoretical rate of $2F$ as the order of the filter increases. It is also worth noting how the sample rate increases drastically as one tries to follow the input signal more closely with a minimum of error.

For communications applications, however, one is dealing primarily with input filters whose order does approach infinity. The output filters are also optimized, or of Butterworth types. For these reasons a sample rate in the range of 2 to 5 times F should prove satisfactory.

Another error that appears during sampling is known as aperture error. This error is caused by the sample pulses taking a small amount of time to capture the analog signal. During this time, the input voltage can change drastically as the signal goes through zero. This is indicated in Figure 1 by the triangular shapes of some of the sampled data pulses. The aperture error can be expressed mathematically [2] for a sinusoidal input by:

$$\epsilon = \frac{\Delta V}{V_{FS}} = 2\pi\tau$$

Table 1. Systems Resulting in a 5% Interpolation Error [1]

Normalized sample frequency (F_s/f_1)

Interpolation Method	m = 1	m = 2	m = 3	m = 4	m = 5	m = 6
Wiener Optimum Filter	640	11	5.1	3.8	2.6	2.0
Butterworth n = 4	—	16	8.3	5.5	5.5	5.5
n = 3	—	18	9.2	6.7	6.7	6.7
n = 2	1.2×10^3	29	17.0	11	11	11
RC Filter n = 1	1.2×10^4	220	130	91	91	91
2 Point and Linear Interpolation	640	13	8.3	5.9	5.9	5.9
3 Point Linear Interp.	640	12	6.2	5.2	—	4.0
4 Point Linear Interp.	640	12	5.7	4.3	—	3.3

where V_{FS} is the full scale voltage and τ is the duration of the pulse.

Expressed another way, the acceptable pulse duration can be calculated as

$$\tau = (2\pi \times F \times 2^n)^{-1}$$

where n is the number of bits of resolution of the A/D converter for an A/D converter with a 1LSB error. For instance, if the input frequency is 10 kHz and eight bits or resolution are used, the allowable pulse duration = 63.5 ns.

To alleviate aperture error, a track and hold amplifier can be inserted before the

A/D converter. This device's output will follow the input signal while its track digital level is active. When the track input switches, the output is held at its current level and will not vary over the duration of the pulse.

Quantization

After the discrete time, continuous amplitude signal is obtained, it must then be converted to a discrete time, discrete amplitude signal for the digital processor. This process is formally called quantization, but it is more commonly known as analog to digital (A/D) conversion. A quantizer takes a specific amplitude

range and divides it into a series of discrete steps, Q . A digital number is then assigned to each Q .

The number of bits in the digital word determines the number of steps that can be achieved. For n bits, the number of steps would be 2^n . Each step Q , or each change of 1LSB, would be

$$Q = V_{FS}/2^n$$

where V_{FS} is the full scale magnitude of the allowable input voltage.

If the input signal falls between steps then the digital number assigned to it depends on whether the quantizer rounds the samples or truncates them.

As its name implies, the quantizer rounds off the analog input to the nearest quantizer level, Q . In truncation, (Figure 3), the signal is represented by the highest Q level that is not greater than the signal. Thus, for each LSB (least significant bit) step of the digital output word, the error from the original signal would be $\pm 1/2$ LSB for rounding and a 0 or +1LSB for truncation. An error of $\pm 1/2$ LSB yields a mean error of zero, whereas a 1LSB error yields a mean error of $+1/2$ LSB. For

this reason, rounding is preferred in most practical considerations.

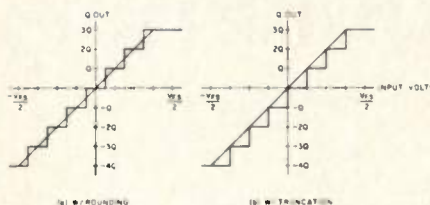



Figure 3. Quantizer Characteristics

How the digital word is represented is another area of consideration. Binary representation varies widely for positive and negative numbers. Again, for most practical considerations, two's complement representation is chosen because most processors use this type of representation. Also, for other applications only positive numbers are expected. Many A/D converters allow either; that is, a range of 0 to V_{FS} or $-V_{FS}/2$ to $+V_{FS}/2$, as well as other representations.

Finally, once the quantizer or A/D converter is chosen the number of bits of

resolution must be decided. While a large number of bits will represent an analog signal more accurately, they will not represent a cleaner analog signal. In every analog signal, there exists some inherent noise that is some small portion of that signal. The more bits of resolution, the smaller the step size in the quantizer. The smaller the step, the more the digital word is affected by noise, so that the lower significant bits only serve to give a good representation of this noise. 

References

1. L.W. Gardenhire, *Selecting Sampling Rates*, Instrumentation Society of America, April 1964.
2. Willard Bucklen, Dr. John Eldon, Louis Schirm, and Fred Williams, "Designers Guide to DSP," *EDN*, Magazine.
- Part 1, "Understanding the Fundamentals Eases Signal Processing Task," March 18, 1981.
- Part 2, "Single Chip Digital Multipliers Form Basic DSP Building Blocks," April 1, 1981.
- Part 3, "Digital Processing Facilitates Signal Analysis," April 15, 1981.
- Part 4, "DAC's and Multifunction Chips Enhance Your DSP Options," April 29, 1981.
- Part 5, "Digital Correlators Illustrate DSP Trends," May 13, 1981.
3. L.R. Rabiner and B. Gold, *Theory and Application of Digital Signal Processing*, Prentice Hall, 1975.
4. A.V. Oppenheim and R. Schaffer, *Digital Signal Processing*, Prentice Hall, 1975.

PIEZO's Quiet Wonder

Improve system performance using Piezo's low noise reference oscillator with vibrational sensitivity of $5 \times 10^{-10}/g$.

- ☐ Stress Compensated (SC) cut crystal
- ☐ Low vibrational sensitivity
- ☐ High short term stability
- ☐ Rugged Construction
- ☐ Low Phase Noise


PIEZO's new Model 1830025 Series oscillators are specifically designed for applications requiring low phase noise for multiplication to microwave frequencies. The internal ruggedized construction and the use of a PIEZO stress compensated SC cut crystal results in typical vibrational sensitivities of $5 \times 10^{-10}/g$. These characteristics make the Model 1830025 ideal for use in communication, radar and instrumentation applications.

PIEZO Systems is a manufacturer of custom oscillators engineered to your requirements, including TCXOs, VCXOs, OCXOs, and XOs. PIEZO Systems is an affiliate of PIEZO Crystal Company, an



Available from 80 to 110 MHz.

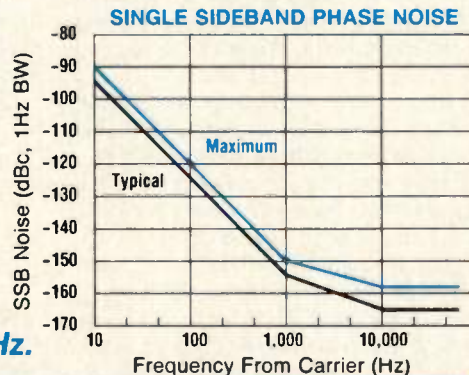innovator in the production of piezoelectric crystals since 1936. For more information and a free catalog describing our capabilities, contact your nearby PIEZO representative. Or contact PIEZO Systems, P.O. Box 619, Carlisle, PA 17013, (717) 249-2151.



**PIEZO
SYSTEMS**

MiCAD, Plotter And MicKnife

RF and microwave engineers can now produce prototype artwork right in their own offices using EEsof's Computer-Aided Design program, MiCAD; an HP plotter; and MicKnife, EEsof's latest product for RF/microwave computer-aided design. MicKnife is a sharp diamond stylus specially configured to replace a pen on an HP 7470/75 or 7580/85 plotter and cuts the rubylith, which replaces the plotter paper.

MiCAD automatically processes and displays an RF/microwave circuit designed with Touchstone (EEsof's computer-aided engineering program). MiCAD, used to prepare drawings, documentation, and camera-ready artwork, supports not only MicKnife and HP plotters, but also established artwork generators such as Aristomat and Wild Heerbrugg Aviotab. **EEsof, Westlake Village, Calif., INFO/CARD #134.**


RF Amplifier Controller

The Erbtec RF amplifier controller incorporates the intelligence and all the necessary electronics to monitor, control and properly drive external high power vacuum tube amplifiers. It also includes an interface which enables all of its functions to be completely controlled and monitored by a remote host computer system. Very modular, it is comprised of 8 plug-in modules installed in a rack-mountable frame. Nylon card guides and knurled screws hold each card securely into a mother board mounted on the back of the frame. Each module can be quickly and easily removed and replaced from the front if servicing is necessary. The printed circuit mother board is designed with a ground plane on one side, which assures a low impedance grounding system between modules and shields against external RF fields and reduces any radiation of internally generated noise. **Erbtec Engineering, Boulder, Colo. INFO/CARD #133.**

Function Generator

The Model 625 5 MHz Function Generator offers sine, square, triangle, havel waveforms, inverted waveforms, variable symmetry waveforms and DC. Frequencies from 100 microhertz to 5 MHz may be selected using 9 overlapping ranges. Within each range except 5 MHz the frequency may be varied over a ratio of 1300:1 remotely, from the front panel or using an external VCF voltage. In the 5 MHz range the frequency may be varied over a ratio of 500:1. Operating modes include: Run (continuous waveform), Gate

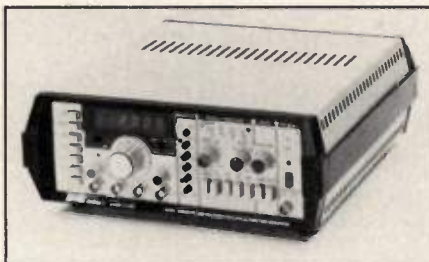(continuous only while gated), Trigger (single cycle waveform with each trigger) and Inhibit (no waveform at output except during GPIB trigger commands. i.e., external and manual triggers are inhibited).




All numerical parameter values are selected and displayed on a 3½ digit LED display. These parameters are: frequency, amplitude, offset, symmetry and calibration sequence number. A decimal point and range LEDs determine the multiplier. Amplitude range is 10 millivolts p-p to 10 volts p-p into 50 ohms, offset range is zero volts to ±5 volts peak into 50 ohms, and symmetry range is 5%:95% to 95%:5% with 1% resolution. Additional front panel LEDs annunciate the non-numerical parameters which are selected. **Exact Electronics, Carson City, Nev., INFO/CARD #176.**

Hyperabrupt Tuning Varactors


DKV4105 A, B & G and DKV4109 A, B & G hyperabrupt tuning diodes are packaged in glass rather than plastic to offer hermetically sealed devices for all applications. The high reproducibility of C vs. V characteristics guarantees long-term availability of devices with uniform electrical properties. The diodes are ideal for straight line frequency vs. voltage applications in crystal or LC-tuned circuits as well as for frequency or phase modulators. **Alpha Industries, Woburn, Mass., INFO/CARD #175.**

Isolated Power MOSFET Driver

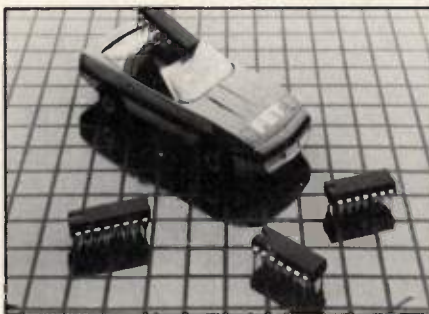A 16-pin DIP, power MOSFET driver, the FDA100 provides 2500 volt input/output isolation. Now you can drive power MOSFETs in 10 to 500 microseconds with full optical isolation. In recent years,



MOS FET POWER From INTECH

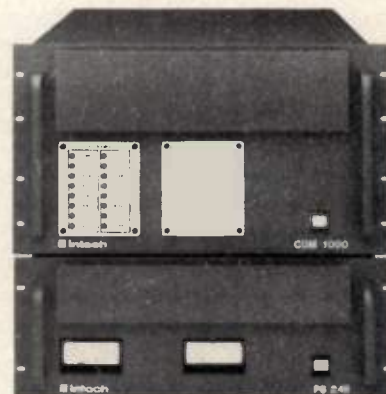

COM 1000: 1000W. Av. Power 1.6-30 MHz with PS 248 Dual Switching AC Power Supply.

Introducing the next generation of unconditionally stable POWER MOS FET Linear Amplifiers from Intech.

Combining the low order distortion of Class "A" with the high efficiency of "AB" & "C"

Designs, they can withstand severe load mismatch conditions without spurious oscillation or failure.

They are capable of high speed on-off switching and are Frequency Agile over their 1.6-30 MHz range.

They are ideal for: RFI/EMI Testing, H.F. Transmitters, Linear Accelerators, N.M.R. CATSCAN, plasma equipment and diathermy.

Power levels — 500 W, 1Kw and up.

Please contact Ted Stevenson Phone: 408-727-0500, TWX: (910) 338-0254) to discuss your State-of-the-Art amplifier requirements or write him at

intech

**282 Brokaw Rd.
Santa Clara, CA 95050**

power MOSFETs have gained increasing acceptance, especially in switching power supply applications. In addition to expected major use in programmable controllers, it can just as easily be used in high speed driving of smaller MOSFETs. Linked, for example, to a small signal FET, it can result in a speed/gain product for high speed datacom circuits much greater than that achievable with opto-coupler circuits. **Theta-J Corp., Wakefield, Mass., INFO/CARD #174.**

Tunable Bandpass Filters

A full line of $n=2 > 12$ pole (easy cavity adjust) bandpass filters, in convenient low cost tubular configuration, with up to 5:1



tuning range (example: $0.2 > 1$ GHz) is now available. **Cir-Q-Tel, Kensington, Maryland, INFO/CARD #173.**

MATE Interfaces

MATE Interfaces for the 50 MHz Pulse

Generator Model 859 and the 50 MHz Synthesizer Model 178 have proven records in systems based on GPIB (IEEE-488) interface. The new MATE interface allows GPIB programming in user friendly CIIL (Control Interface Immediate Language) which standardizes instrument command syntax. In both models, a full MATE confidence test capability is implemented which assures the user that the unit functions properly. In addition to the MATE interface both models also feature the standard GPIB interface. **Wavetek, San Diego, Calif., please circle INFO/CARD #172.**

PX Connectors

Printed circuit board connectors, featuring low insertion force and superior operation in rigorous environments of temperature, vibration and moisture are intermountable with and designed to meet or exceed MIL-C-55302 function requirements. The PX connectors provide an 80% reduction in connector mating force — 1½ ounces per contact. High performance thermoplastic insulators provide high strength at a service temperature range of -55°C to $+125^{\circ}\text{C}$.



PX connector pins are shrouded to guard against field damage, and a polarized insulator housing prevents 180° mismatching of the connectors. The connector design deals against moisture that can contribute to circuit or system malfunction. **ITT Cannon, Fountain Valley, Calif., please circle INFO/CARD #171.**

IMB PC Based Multichannel Digital Oscilloscope

WAVEFORM-CATALYST is a multichannel digital oscilloscope software package with powerful capabilities for acquisition, display, archiving and analysis of high-speed waveforms. It is an integrated system consisting of LeCroy's series of modular waveform digitizers, any of the IBM personal computers (PC,

eighth dimension enterprises

Software for Apple(*) II Computers.

"FILE IT ALL"

with Personal Inventory

Keep track of everything!
100% user friendly
Fully menu driven.
Search any record.
Sort any record.
No codes, keywords,
fields or formats.

Can be used ANY subject.
REAL ESTATE RECORDS
TECHNICAL LIBRARY
CALENDER
INSURANCE RECORDS
BANK RECORDS
INVENTORY
DESIGN YOUR OWN!

\$59.95

RF FILTERS

1. Low Pass Filters
DC to 1200 Mhz
 2. High Pass Filters
1 Khz to 1200 Mhz
 3. Band Pass Filters
10 Khz to 1000 Mhz
 4. Band Reject Filters
10 Khz to 1200 Mhz
- Tablized Filter Response
over range you request.
Each program **\$99.95**
ALL 4 PROGRAMS
\$349.95
Micro-Strip Low Pass
Filter **\$399.95**

INCOME TAX DATA RECORDER

Don't lose a deduction!

Organizes your receipts
& sub-totals the
sections in forms 1040,
1040A, 2441, 4562,
Schedules A,B,C,D, & E.
Use as a guide to fill
out tax forms. Sorts &
searches per form and
category. **\$29.50**

Send check/money order
to P.O. BOX 62366,
Sunnyvale, Ca. 94088
Calif. res. add 6.0%
Sales tax.

(*) Apple is the registered trademark of APPLE Computer, Inc.

portable, XT or AT) and system software. Digitizer plug-ins offer bandwidths to 100 MHz and maximum sampling rates of 200 MHz or 5 nsec between points. CATALYST operates like an instrument, not a computer. Single keystroke operating commands and familiar scope terminology make knowledge of computers or programming language unnecessary. The high resolution graphics permit simultaneous viewing of up to four



“live” or previously stored traces, each with its own timebase and grid. Dual cursors control zoom, positioning, and the absolute and differential measurement of time and voltage, while on-screen markers identify the trigger point, zero baseline, off-scale conditions, etc. **LeCroy Research Systems Corporation, Spring Valley, New York, please circle INFO/CARD #170.**

HP Oscilloscope

The HP 54200A/D is a fully programmable, 200-megasample-per-second digitizing oscilloscope, ideal for capturing high-speed single-shot events. It is particularly useful to designers of digital and analog systems who must deal with transient fault conditions. Transients as narrow as 10 nanoseconds can be captured easily. The HP 54200A/D's 200-megasample-per-second digitizing rate enables it to capture high speed events in a single-shot manner. Pre-trigger viewing allows the user to see what happened before the trigger event. With built-in automatic pulse-parameter measurements, the HP 54200A/D provides fast, repeatable




answers. Automatic answers relieve the designer of having to write programs to cover these functions. The HP 54200 A/D's average mode extracts the signal from uncorrelated noise, allowing the

user the probe in noisy environments. The HP 54300A/D's infinite persistence eliminates the trial-and-error fine-tuning inherent in analog storage controls. With two proprietary analog-to-digital converters, the HP 54200A/D provides two-channel simultaneous acquisition without sacrificing sample rate. The HP 54200A/D provides four memory locations in which a waveform, averaged waveform or waveform envelope can be

stored for later analysis, allowing the user to make before and after comparisons. **Hewlett-Packard, Palo Alto, Calif., INFO/CARD #169.**

Coax Dual Line Strippers

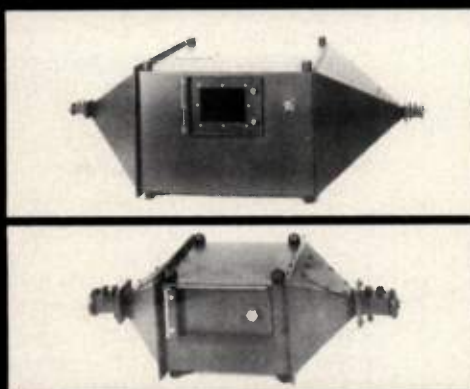The TOR-1C Coaxial Cable Stripper and the TOR-1F Dual Line Stripper are an ideal complement to the electrical and electronic technicians tool kit. Each tool comes with a spare set of blades. **Davle**



depend on ifi: Precision design TEM test chambers for accurate and broadband EMC testing

IFI's precision design and construction allows accurate E-Field generation within ± 1 db.

Each cell is equipped with a hinged access door that provides clearance for insertion of test objects, and transition panels for easy cable entry.

Larger cells can be supplied with integral E-Field Sensors, for direct readout in volts per meter.

Model CC-108—This test cell, with an operating range of DC to 800 MHz, offers an efficient means of obtaining broadband E-Field measurements in a compact, bench top application.

Model BC-100—This portable cell, specifically designed for medical and biological testing, provides a means of generating extremely high E-Fields up to 1GHz.

Model CC-103—The TEM Cell that has set industry standards, permits fully controlled testing at high E-Field levels with a moderate amount of input power.

Applications

- EMC/Susceptibility Testing
- Calibration of Field Intensity Meters
- Research & Development Applications
- Testing & Calibration of Power Density Probes

Benefits


- Cost Effective Alternative to a Full Size Screen Room
- Portable Shielded Enclosure for Lab Testing
- Protection from Hazardous Radiation During High E-Field Tests
- Useful for both Susceptibility and Emissions Measurements

“Also Depend on IFI for Broadband Amplifiers, E-Field Sensors and EMC Test Equipment”



INSTRUMENTS FOR INDUSTRY, INC.
151 Toledo Street
Farmingdale, N.Y. 11735
(516) 694-1414

Wilmanco

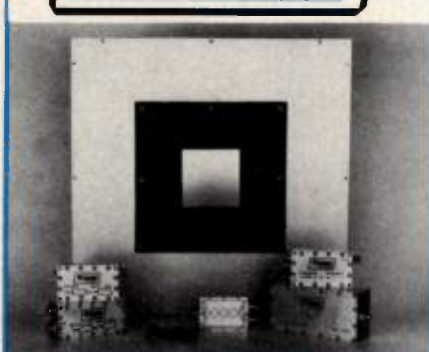

HYBRID SOURCES

Crystal Oscillator/Multiplier
10 MHz to 6GHz
Commercial or Military Quality
Digital Temperature
Comp Option

HYBRID FREQUENCY MULTIPLIERS

5 or 10 MHz In/100 MHz Out
100 MHz In/1400 MHz Out
Custom Multipliers

NAVSTAR GPS CLOCK MULTIPLIERS

10.23 MHz In/
1432.2 MHz Out

FM and PM MODULATORS

10 MHz to 6 GHz RF Output
DC-6 MHz Baseband Input
Digital Temperature
Comp Option

NAVSTAR GPS ANTENNAS

RCP Microstrip Patch
Antennas
Dual Patch Antenna for
L1 & L2
Other Frequencies and
Polarizations

GaAs FET LNA FOR NAVSTAR DOWNLINK

Effective Noise Temperature
< 65°K

PASSIVE DEVICES ON DROP-IN SUBSTRATES

Power Dividers, Mixers
& Directional Couplers
.5 to 12.4 GHz
Connectorized Housings
Optional

CUSTOM THICK FILM HYBRIDS

Your Designs Hybridized

Wilmanco

MANUFACTURERS OF
MICROWAVE PRODUCTS
19529 Business Center Dr.
Northridge, CA 91324
(818) 993-1662

INFO/CARD 39

rf products Continued

Tech Inc., Fair Lawn, New Jersey,
INFO/CARD #168.


PIN Diode Drivers

Model 254's small 1/4 wide x 3/8 long size makes it easy to fit into any circuit. This inverting driver with typical output current of 20 mA is fully TTL compatible, including low power Schottky logics. It operates from ± 5 VDC and dissipates less than 1/2 watt under switching conditions of 35 ns max. In house screenings per MIL-STD-883C, Method of 5008.2, Class B, Table VIII is available for a minimal charge of \$10 each. New England Microwave Corporation, Hudson, New Hampshire, INFO/CARD #167.

Miniature Optocouplers

The SFH 610/611 series of miniature optocouplers in a 4-lead dual in-line package is being offered in four high current transfer ratio groups: SFH 610/611-1: 40-80%; SFH 610/611-2: 63-125%; SFH 610/611-3: 100-200%; and SFH 610/611-4: 160-320%. The difference in the SFH 610 and SFH 611 is only in the pin connections. Package dimensions for

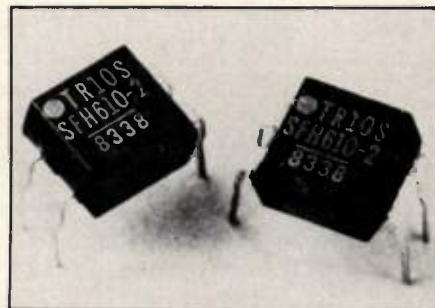this handy 4-pin single-channel coupler are significantly scaled down in length to only .2" — compared to a standard 6-pin DIP length of .34" — and make it especially suitable for applications where board space is at a premium. It is designed for use in electronic test equipment, medical instrumentation, computer



peripherals and communications equipment. The devices are optically coupled isolators employing a gallium arsenide (GaAs) infrared emitter and a silicon phototransistor detector. They feature a 2800 volt isolation and are awaiting VDE approval. Siemens Components, Inc., Cupertino, Calif., INFO/CARD #165.

LOWEST PRICED, HIGHEST QUALITY ATTENUATORS - BNC \$11.00 1-9EA, SMA \$8.90 10EA, AND TERMINATIONS - BNC \$5.60 10EA, SMA \$5.60 10EA, MIL. HI-REL. NETWORKS

Model Number (2)	Impedance Ohms (Power W)	Frequency Range	BNC	UNIT PRICE (4) EFFECTIVE 1-18-85	SMA	PC
Fixed Attenuators, 1 to 20 dB						
AT-50(3)	50 (1 SW)	DC-1.5GHz	14.00	20.00	18.00	—
AT-51	50 (1 SW)	DC-1.5GHz	11.00	18.00	15.00	12.00
AT-52	50 (1 SW)	DC-1.5GHz	14.50	20.50	18.50	—
AT-53	50 (2 SW)	DC-3.0GHz	14.00	17.00	15.00	—
AT-54	50 (2 SW)	DC-4.2GHz	—	—	18.00	—
AT-55	50 (2 SW)	DC-4.2GHz	—	—	8.90 (10EA)	—
AT-75 or AT-90	75 or 93 (1 SW)	DC-1.5GHz (750MHz)	14.00	20.00	18.00	—
Detector, Mixer, Zero Bias Schottky						
CD-51	50	01-4.2GHz	84.00	—	54.00	—
DM-51	50	01-4.2GHz	—	—	64.00	—
Resistive Impedance Transformers, Minimum Loss Pads						
RT-50/75	50 to 75	DC-1.5GHz	10.50	19.50	17.50	—
RT-50/93	50 to 93	DC-1.5GHz	13.00	19.50	17.50	—
Terminations						
CT-50 (3)	50 (1 SW)	DC-4.2GHz	11.80	15.00	17.50	—
CT-51	50 (1 SW)	DC-4.2GHz	9.50	12.00	9.50	—
CT-52	50 (1 SW)	DC-2.5GHz	10.50	15.00	13.00	15.50
CT-53M	50 (1 SW)	DC-4.2GHz	5.60 (10EA)	—	5.60 (10EA)	—
CT-54	50 (2 SW)	DC-2.0GHz	14.00	15.00	17.50	—
CT-75	75 (2 SW)	DC-2.5GHz	10.50	15.00	13.00	15.50
CT-93	93 (2 SW)	DC-2.5GHz	13.00	15.00	—	15.50
Mismatched Terminations, 1:05:1 to 3:1, Open Circuit, Short Circuit						
MT-51	50	DC-3.0GHz	45.50	45.50	45.50	—
MT-75	75	DC-1.0GHz	—	45.50	—	—
Feed thru Terminations, shunt resistor						
FT-50	50	DC-1.0GHz	10.50	19.50	18.00	17.50
FT-75	75	DC-500MHz	10.50	19.50	19.50	17.50
FT-90	93	DC-150MHz	13.00	19.50	19.50	17.50
Directional Coupler, 30 dB						
DC-500	50	250-500MHz	90.00	—	—	—
Resistive Decoupler, series resistor or Capacitive Coupler, series capacitor						
RD or CC-1000	1000 (1000PF)	DC-1.5GHz	12.00	18.00	18.00	17.00
Adapters						
CA-50 (N to SMA)	50	DC-4.2GHz	—	—	13.00	13.00
Inductive Decouplers, series inductor						
LD-R15	0.15uH	DC-500MHz	12.00	18.00	18.00	17.00
LD-R6	6.5uH	DC-55MHz	12.00	18.00	18.00	17.00
Fixed Attenuator Sets, 3, 6, 10, and 20 dB, in plastic case						
AT-50-SET (3)	50	DC-1.5GHz	60.00	84.00	84.00	78.00
AT-51-SET	50	DC-1.5GHz	48.00	64.00	64.00	60.00
Reciprocal Multipliers, 2 and 4 output ports						
TC-125-2	50	1.5-125MHz	64.00	—	67.00	67.00
TC-125-4	50	1.5-125MHz	67.00	—	81.50	81.50
Resistive Power Dividers, 3, 4 and 8 ports						
RC-3-30	30	DC-2.0GHz	84.00	—	—	84.00
RC-3-30	30	DC-500MHz	64.00	—	—	84.00
RC-8-30	30	DC-500MHz	—	—	—	84.50
RC-3-75, 4-75	75	DC-500MHz	64.00	—	—	84.00
Double Balanced Mixers						
DBM-1000	50	5-1000MHz	81.00	—	71.00	81.00
DBM-500PC	50	2-500MHz	—	—	—	34.00
RF Fuse, 1/8 Amp and 1/16 Amp						
FL-50	50	DC-1.5GHz	12.00	18.00	—	17.00
FL-75	75	DC-1.5GHz	12.00	18.00	—	17.00

NOTE: 1) Critical parameters fully tested and guaranteed. Fabricated from Mil. Spec. High-Rel. materials. Schottky diodes. Mil. Spec. plated parts and connectors (in nickel, silver, and gold). 2) See catalog for complete Model Number, Specify connector series. Specials available. 3) Calibration marked on label of unit. 4) Price subject to change 1985-A without notice. Shipping \$5.00 Domestic or \$15.00 Foreign on Prepaid Orders. Delivery by stock to 30 days ARO.

Send for Free Catalog on your Letterhead.
Elcom SYSTEMS INC. 305-994-1774
4032 CLINT MOORE ROAD, BOCA RATON, FL 33431

INFO/CARD 40

TWT Power Supply

A MODULAR INTEGRATED TWT POWER SUPPLY, Model No. 10755 coupled to a 50-125w (C-Band) or 50-125w (Ku-Band) TWT tube will reduce waveguide losses for Ku-Band and C-Band antenna pedestal installation. Highly efficient with state of the art current driven VFET circuitry, the power supply is easily adaptable to particular customer specifications and unique requirements. Fully encapsulated high voltage components are included in this easy to operate unit with capacity up to 125 watt TWTs. The power supply has a modular concept, extreme wide operating temperature range and is conduction cooled. **MCL, Inc., LaGrange, Ill., INFO/CARD #163.**


Circuit Simulator

The SIMON circuit simulator is a full circuit simulation software package created specifically for MOS and CMOS circuits. Using an entirely new algorithm (not a SPICE derivative) SIMON offers unmatched speed (10 to 50 times faster than SPICE), guaranteed convergence, simulation of circuits far larger than

previously possible and state of the art user friendly features. SIMON is available for a variety of host computers with price depending on the individual installation and CPU unit. Ongoing support, maintenance and updates are available via a maintenance agreement. **Simon Software, Inc., San Jose, Calif., INFO/CARD #162.**

Ruggedized EMI Filter Pins

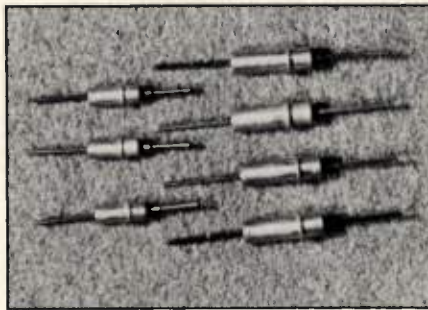EMI Filter Pins are improved and updated versions of the traditional tubular ceramic-bodied filter pin. Features include: metal shell construction providing a rugged housing to withstand assembly and environmental rigors; round or



square cross section pins for solder or wire-wrap applications; expanded capacitance range. 100 pf to .07 μ f available; voltage ratings of 50-300 VDC and 115 VAC; current rating 10 AMPS; available in C, L, π and T circuit configurations; typical insertion loss values of 4 dB at 100 kHz, 20 dB at 1 MHz, 50 dB at 10 MHz and 70 dB at 100 MHz and up for the 50 volt rated π section filter. **Ceramic Devices, San Diego, Calif., INFO/CARD #161.**

Digital Potentiometer

The HEDS-7500 digital potentiometer produces digital output directly from manual rotary input. The new device



IMS CHIP RESISTORS

Surface Mounted Devices
STOCK 24 HOUR DELIVERY
Others 2 Weeks MAX.

- **STANDARD**
10 Ohm to 25 Meg
- **LOW OHM**
1 to 10 Ohm
- **HI MEG**
Up to 100 GigOhm
- **POWER**
Up to 10 W
- **Any Value/Tolerance**
- **18 Standard Sizes**
Smallest .025" x .030"
- **Hi Quality - Low Cost**
- **Microwave Applications**

ENGINEERING KITS
10 to 100 pcs / Value
SMD 1206 (IMS 10-2) IN STOCK

401-683-9700

International Manufacturing Serv.
50 Schoolhouse Lane, Portsmouth, RI 02871


QPL CLOCK OSCILLATORS

MIL-0-55310 / 8 THRU / 19

Q-TECH provides quality QPL oscillators at competitive prices with short lead times from our expanded production facilities. See us for your standard or custom requirements.

CONTACT US FOR ALL YOUR CLOCK OSCILLATOR REQUIREMENTS

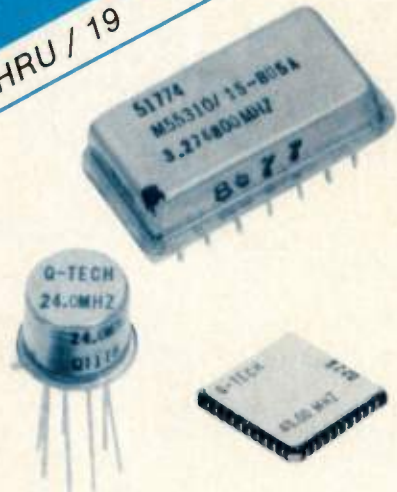- Standard Oscillators (TO 5, 8, DIP LCC and Flatpack)
- Baud Rate Generators
- 6875 Type Microprocessor Drivers
- ECL Clocks
- VCXO In Hybrid
- Z8000 Drivers
- Precision Ovenized Crystal Oscillators



Q-Tech Corporation

2201 Carmelina Avenue
Los Angeles, CA 90064
(213) 820-4921

THE LONG-TERM STABILITY OF A CESIUM. THE SHORT-TERM STABILITY OF A RUBIDIUM.



AUSTRON MODEL 2110 DISCIPLINED FREQUENCY STANDARD

Announcing

THE FIRST MICROPROCESSOR CONTROLLED DISCIPLINED FREQUENCY STANDARD.

Austron's Model 2110 is the first microprocessor controlled Disciplined Frequency Standard. It offers an economical solution to the most difficult and demanding applications.

The Model 2110 automatically locks the frequency of its internal oscillator to an external reference that has superior long-term stability. Through the use of a third-order servo oscillator control technique, the instrument corrects the frequency offset and aging of the internal oscillator. Should the reference fail, the Austron 2110 can limit the frequency offset to parts in 10^{12} for several days.

A SOLUTION FOR DEMANDING APPLICATIONS

- in communications systems where spectral purity and redundancy are of paramount importance
- in metrology where stable frequencies to parts in 10^{12} accuracy are required
- in clock systems where a stable clock with accuracies to ± 100 ns is necessary

- in frequency measurement where there is a need to quickly set oscillators to very high accuracies

OFFERING STATE-OF-THE-ART FEATURES

- microprocessor controlled
- high-stability internal oscillator
- third-order servo oscillator control system
- frequency measurement to parts in 10^{-12} with 100 sec averaging times
- 1 PPS clock output (externally synchronizable)
- spectrally pure output signals
- optional IEEE-488 interface
- optional dual reference frequency input allowing a choice of external references

The Austron Model 2110 microprocessor controlled Disciplined Frequency Standard is a first and it's from Austron. The 2110 can solve your most difficult timing and frequency application problems.

CALL OR WRITE FOR MORE
DETAILED INFORMATION.

LEADERS IN TIMING AND FREQUENCY MANAGEMENT



AUSTRON INC.

P.O. BOX 14766 AUSTIN, TEXAS 78761 • (512) 251-2313 • TWX 910/874-1356

rf products *Continued*

enables bi-directional counting by decoding two digital-pulse trains, which are out of phase by 90 electrical degrees. Available with a standard 256 pulses per revolution, the device commonly is used as a knob on the front panel of equipment where a digital display may be used to indicate the position of the knob. Hewlett-Packard, Palo Alto, Calif., please circle INFO/CARD #160.

Snap Lock Connectors

An environmentally sealed series of quick connect/disconnect connectors that provides a labor-saving alternative to traditional environmental PC board connectors, called Snap Lock Environmental (SLE), is specifically designed for computer/controlled applications that must



withstand severe environments. The SLE design does away with expensive slide latches, spring latches or even center jack screws by integrally molding snap locks to the receptacle body on the mating side. This side also offers a heavy duty interfacial gasket and multiple labyrinth seals in the rear to protect against severe conditions. ITT Cannon, Fountain Valley, Calif., INFO/CARD #159.


Insulated Ground Straps

CHO-STRAP™ Grounding Straps are flexible, double-insulated laminates of copper (inside) and Mylar (outside), with pre-punched tinned ends to facilitate termination. They provide low-impedance ground paths at RF frequencies, thereby reducing radiated EMI problems caused by ordinary wire grounds. CHO-STRAPS are generally more cost-effective than braided ground straps. CHO-STRAP ground straps are supplied in a variety of standard widths and lengths. Standard construction is 5-oz. rolled annealed copper, laminated on both sides to 2-mil Mylar with flame retardant polyester adhesive. CHO-STRAPS are UL rated and pass all requirements of UL specification 94VO. Chomerics, Woburn, Mass., please circle INFO/CARD #158.

March 1985

800 Volt Hi-Rel Power MOSFETs

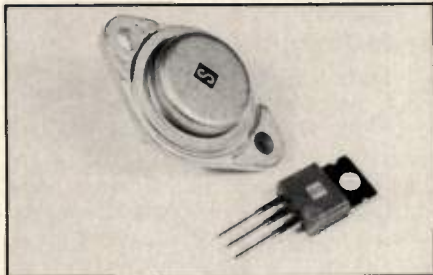A new series of high reliability, fast switching power MOSFETs meet high temperature requirements and feature hexagonal geometry, voltage (drain to source) to 800 volts and drain currents to 456 amps. Identified as SWITCHMOS,



these units offer eutectic mounted packaging for military and industrial applications in TO-220 and TO-3 cases. Solitron Devices, Inc., Riviera Beach, Fla., INFO/CARD #157.

Miniature Pin Switch

This miniature pin switch has a frequency range of 10-1000 MHz at a 50 ohm impedance with an environmental temperature range of -55°C to +85°C. It

These words are worth a thousand pictures.

That's how many individual photos it would take to show you the entire Sprague-Goodman trimmer capacitor line. If you'd like to see them, just write for our catalog to

134 Fulton Ave., Garden City Park, NY 11040. Or call 516-746-1385. Or telex: 14-4533. Sprague-Goodman Electronics, Inc. is an affiliate of the Sprague Electric Company.



The world's broadest line of trimmer capacitors.

INFO/CARD 44

K-W Manufacturing, Inc.

Post Office Box 508
Prague, Oklahoma 74864
Phone (405) 567-2285

QUALITY CRYSTALS


- Delivery — 10 working days
- Custom made to your specifications or to the original equipment manufacturer's specifications
- Medium frequency range 6,000 kHz to 24,000 kHz
- Hi frequency overtone range 10,000 MHz to 135,000 MHz
- No minimum quantity requirement
- OEM volume capability
- Competitive prices
- Highest quality available
- K-W Crystals are guaranteed against defective workmanship and materials when used in specified oscillator or equipment for which they were ordered.

For a catalog, fill out the coupon and return it. Write or call Dave Randall or Freda Pickard to order your CRYSTALS today.

K-W Manufacturing, Inc.
P.O. Box 508
Prague, Oklahoma 74864
Phone: 405-567-2285

Name _____
Address _____
City _____ State _____ Zip _____

INFO/CARD 45

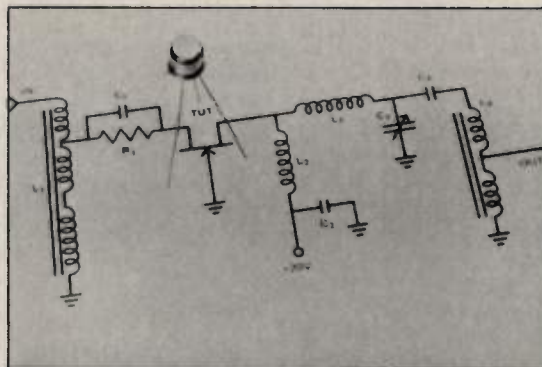

HIGH VOLTAGE BROADBAND RF FET

High dynamic range RF FET now available up to 50V BVDGO, for use with 24 & 32V supplies, and where higher drain voltage improves dynamic range. The CP664 (30V), CP665 (40V), and CP666 (50V) have third order intermodulation intercept >+40 dBm, and 50 Ohm VSWR <1.5 to 1 over 0.5 to 50 MHz range.

HIGH VOLTAGE RF FET

TELEDYNE CRYSTALONICS

147 Sherman Street, Cambridge, MA 02140
Tel: (617) 491-1670 • TWX 710-320-1196

INFO/CARD 46

IMAGINE!

Everything you'll ever want— or need—in circular connector accessories.

Glenair has the widest choice available in the industry.

Every feature. Every design option. Every application. Glenair, the leader in connector accessories for over 25 years, has developed and tooled thousands of accessory designs—from simple wire bundle strain reliefs, backshells, dummy stowage receptacles and protective covers to advanced devices for EMI/RFI shielding, and more:

- MIL-C 85049 backshells
- Shrink boot adapters, w/wo EMI/RFI shield termination
- Extender backshells
- Pipe thread adapters



- Shorting cap backshells
- Non-environmental backshells w/wo EMI/RFI shield termination
- Cable sealing backshells with immersion capability, w/wo EMI/RFI shield termination
- TAG Ring® backshells for shield termination
- Conduit backshells
- Crimp ring backshells
- Qwik Ty® strain reliefs
- EMI/RFI G-spring backshells

If you're having trouble making an existing accessory fit your needs, Glenair will design and produce a solution. Call or write:

®Registered trademark of Glenair, Inc.

GLENAIR, INC.

1211 Air Way • Glendale, California 91201-2497 • (818) 247-6000


INFO/CARD 47

rf products *Continued*

is available in the TO-5 housing. Power requirement is ± 15 volts at 10 mA, and a maximum RF input at 20 dBm. This SPST configuration has an insertion loss of less than 1.75 dB at 1000 MHz and isolation greater than 30 dB at 1000 MHz. Wavetek Indiana, Inc., Beech Grove, Ind., INFO/CARD #156.

Modular Probe Family

A unique high voltage RF detector probe, Model 10851A, features an optional "Tee" connector for direct 50-ohm measurements and a 100:1 divider to handle very high RF input voltages; the first multimeter probe capable of this performance. The new probes are designed to mate with virtually any brand of laboratory-grade oscilloscope. An adjustable wideband probe cable terminator network is provided so that correct high frequency compensation can be obtained for any scope. There is no compromise in risetime or bandwidth relative to comparable original equipment probes. Switch-selectable X1/X10 attenuation is also available on several models.

Ballantine Laboratories, Inc., Boonton, New Jersey, INFO/CARD #155. 



"America's Shielding Source"

- Magnetic Shielding of all types
- Shielding grade alloys
- Total in-house design, testing and manufacturing capabilities.
- Send for our latest product literature.

Magnetic **RADIATION
LABORATORIES, INC.**

92-A North Lively Boulevard • Elk Grove Village, Illinois 60007
Phone: 1-312-437-5200 • TWX 910-222-0225

INFO/CARD 48

CAE for
Analog Circuit Designers


50 TIMES FASTER

than your HP AC Circuit Analysis
for your 9836, 9816, 9920, 9845 and 9020

PLUS:

- OPTIMIZATION
- 98 NODES
- TIME DOMAIN
- GROUP DELAY
- RELATIVE PHASE
- NEGATIVE COMPONENTS

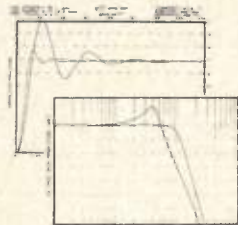- COMPONENT SENSITIVITY
- OUTPUT WAVEFORM for any INPUT
- IMPROVED ALGORITHMS
- COMPATIBLE with HP DATA FILES
- INTEGRATED with FFT and MEASUREMENTS with HP1B
- 6 YEAR TRACK RECORD
- 30 DAY TRIAL



ALSO: FFT WAVEFORM ANALYSIS

- 4 TIMES FASTER than HP
- INTEGRATED into ONE FILE

THREE INTEGRATED MODULES:

AC-CAP	
AC Circuit Analysis with OPTIMIZATION	\$750.00
S-WAVE	
FFT Waveform Analysis for Time Domain	\$750.00
PLOTFT	
Time Domain Data Acquisition	\$750.00

Double all prices for 9020 Computer version.

DEMO DISK AVAILABLE

COMTRAN INTEGRATED SOFTWARE
FROM

jensen transformers
INCORPORATED

10735 Burbank Boulevard • North Hollywood, California 91601
Contact Deane Jensen (213) 876-0059 • Closed Fridays


INFO/CARD 49

NACSIM 5100A — can your emanations pass the test?

The NTR-51 will let you know.

The NTR-51 TEMPEST Test Receiver offers unmatched performance — surpassing even the rigorous NACSIM 5100A requirements. Independently-adjustable upper and lower passband edges yield bandwidths from 45 Hz to 995 MHz, and permit the operator to select nearly any combination of low-noise amplification and filtering characteristics.

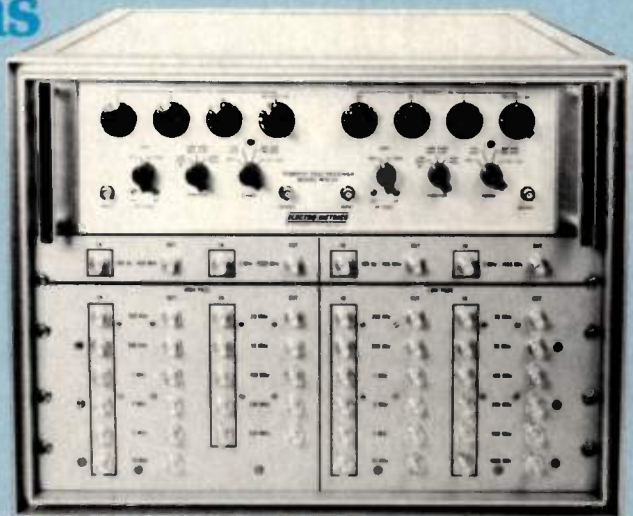Complete detection system certification data is furnished with each unit to facilitate quick system approval. And because the unit is compatible with any of the usual TEMPEST test accessories, you can put it into service right away. For more information about the NTR-51, call or write today.



- ☐ 100 Hz to 1 GHz at 50 ohms
- ☐ Up to 80 dB gain
- ☐ Extremely low noise figure
- ☐ Bandwidths from 45 Hz to 995 MHz
- ☐ Surpasses NACSIM 5100A requirements

INFO/CARD 65

New all-purpose interference analyzer for audio range testing

Electro-Metrics EMC-11 Interference Analyzer combines high sensitivity with adjustable bandwidth for the versatility you need in sophisticated measurement processes.

The new EMC-11 is ideal for tests and measurements for compliance to all standards including MIL, ANSI, CISPR, IEEE, SAE, RTCA, SAMA, FCC and other military and government standards. For more information about the EMC-11, call or write today.



- ☐ 20 Hz to 50 kHz
- ☐ Nine selectable bandwidths
- ☐ Improved sensitivity for all uses
- ☐ Selectable low and high pass filters
- ☐ Spectrum analyzer mode using oscilloscope
- ☐ Front panel functions remotely controllable
- ☐ Balanced and unbalanced input

INFO/CARD 50

100 Church Street
Amsterdam, New York 12010

ELECTRO-METRICS
A PENRIL COMPANY

Tel.: (518) 843-2600
TWX: 710-446-4798

A quartz resonator for UHF oscillators has surfaced...



Introducing the surface acoustic wave (SAW) resonator. This fundamental-mode UHF resonator is manufactured with semiconductor processing techniques using quartz as a substrate. The high-Q resonance of the SAW resonator arises from phased reflections across the surface of the device — similar mathematically to the resonance of a laser. The quartz SAW resonator makes an excellent frequency control device for UHF oscillators from 300 to over 1000 MHz. SAW resonators are used in RF applications from precision instrumentation to high-volume consumer electronics.

For more information on the characteristics and applications of the quartz SAW resonator please contact:



RF Monolithics, Inc.
4441 Sigma Road
Dallas, Texas 75244
(214) 233-2903
TWX: 910-860-5474

rf literature

Electrolytic Capacitor Catalog

Included in a new 33-page Electrolytic Capacitor Catalog are complete electronic and mechanical specifications for high voltage and extended temperature range versions; miniature, subminiature, and super subminiature sizes; low leakage, low noise and bi-polar versions; low ESR and low impedance types. **Paccorn Electronics, Redmond, Wash., INFO/CARD #142.**

Semiconductor Catalog

The comprehensive 400-page catalog from Alpha Industries contains technical data sheets and application notes for mixer and detection diodes, including Schottky barrier and point contact diodes; control diodes, including PIN switching, attenuator, and limiter diodes, and Silicon/GaAs tuning diodes; power generation devices, including Gunn diodes/modules, and Silicon GaAs parametric amplifier diodes; Silicon/GaAs multiplier and step recovery diodes. **Alpha Industries, Inc., Woburn, Mass., INFO/CARD #138.**

Triple Output Power Supply Comparison Chart

A free triple output power supply comparison chart covers Electronic Measurements, Lambda, Kepco, Hewlett Packard, Dynascan and Systron Donner models. Parameters needed to select the proper triple output supply for your specific needs are detailed, including outputs for 1, 2, 3, max. output power outputs isolated, series operation, parallel operation, output modes, voltage current set, panel meter, simulation read volts and amps, regulation, ripple, isolation, output/case, frequency at output, size, bench area sq. ft., warranty and price. **Electronic Measuring, Inc., Neptune, New Jersey, INFO/CARD #137.**

DESIGN ENGINEERS HAVE LEARNED

"When you buy a crystal from Sentry, you never have to buy it again."

Continuing advances in the design and development of analytical instrumentation have tremendous impact on all aspects of scientific research. And that means enhanced sensitivity; faster, more efficient procedures; and - perhaps most critical for the designer - a demand for reliability.

Your reputation is on the line every time you provide a new set of specs. And our reputation is on the line every time you specify Sentry crystals. That's why we make high quality crystals and back them with a lifetime warranty.

Next time you specify crystals, put Sentry to the test. We'll measure up. You have our promise.




SENTRY MANUFACTURING COMPANY
CRYSTAL PARK
CHICKASHA OK 73018
405-224-6780

PRECISION QUARTZ CRYSTALS AND ELECTRONICS
FOR THE COMMUNICATIONS INDUSTRY

© SENTRY MFG CO. 1983

Largest Independent Lab In The West

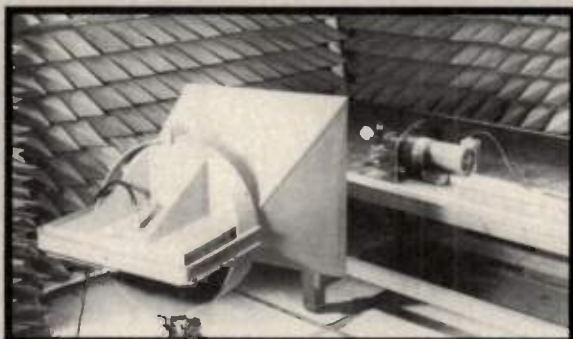Faster Turnaround EMI/EMC Testing Two Weeks or Less!



200 V/m Testing to 18 GHz Receiving Capability to 40 GHz

With seven large shielded enclosures, 25 years of EMI/EMC experience, and a highly trained staff, Genisco has the "right stuff" to solve all of your susceptibility and emissions testing problems. Talk to us about much-shorter lead times before you schedule your next test. We can even set up a two-or-three shift operation for you to meet urgent scheduling requirements!

- MIL-STD 461A/B, medical and commercial specs
- Radiated susceptibility testing: 10kHz-18 GHz
- Enclosure treated with RF anechoic material
- Emissions testing: 20 Hz to 40 GHz
- Modern semi-automatic swept EMI receivers
- Automated analysis; x-y plots to 40 GHz
- Mobile EMI vans for remote-site testing
- EMC consulting and custom EMI filter designs

Current Capabilities Include:

Frequency	Field Intensity	Modulation	Antennas
10 kHz - 30 MHz	200 V/m	CW, AM, FM or β M	IFI EFG-3, AR AT3000, parallel plate
30 MHz - 150 MHz	200 V/m	CW, AM, FM, β M or pulse mod	IFI EFG-3
150 MHz - 375 MHz	200 V/m	CW, AM, FM, β M or pulse mod	IFI EFG-3, AR AT1000
375 MHz - 1 GHz	200 V/m	CW, AM, FM, β M or pulse mod	AR AT1000, Stoddart 92270-1 Horn
1 GHz - 18 GHz	200 V/m	CW, AM or pulse mod	Standard gain horns, and ridged-guide horns
18 GHz - 40 GHz	200 V/m	CW, AM or pulse mod	(Available by August 1985)

Call Bill Parker at (213) 537-4750



GENISCO

TECHNOLOGY CORPORATION

EMC Engineering Services Division

18435 Susana Rd., Rancho Dominguez, CA 90221
(213) 537-4750, TWX: 910-346-6773

INFO/CARD 53

LOW POWER ATTENUATORS

NOW FROM BIRD



50 ohms nominal

Use two or more in tandem for odd values, or use with Bird High Power Attenuators (to 4000 watts) for additional attenuation.

Input Power Watts	dB Attenuation	Frequency GHz	Connectors	VSWR Max.
2	1, 2, 3, 6, 8, 10, 14, 20	DC-2	BNC-M/F	1.2
5	3, 6, 10, 20, 30	DC-4	N-M/F	1.25
10	3, 6, 10, 20, 30	DC-4	N-M/F	1.25
15	3, 6, 10, 20, 30	DC-4	N-M/F	1.25
25	3, 6, 10, 20, 30	DC-4	N-M/F	1.25
75	3, 6, 10, 20, 30	DC-2	N-M/F	1.25

BIRD

30303 Aurora Rd., Cleveland (Solon), Ohio 44139

216-248-1200 TLX: 706898 Bird Elec UD

WEST: Ojai, CA 805-646-7255

For Low Power Bulletin
circle INFO/CARD 54

For High Power Bulletin
circle INFO/CARD 55

HIGH DYNAMIC RANGE

RF AMPLIFIERS



Janel offers a wide variety of high dynamic range RF Amplifiers. The chart below shows a sampling of what's available. All feature high *guaranteed* performance and yet are competitively priced. Many models are available from stock.

Model	Frequency	Gain	N.F.	3rd I.P.
PF811A	1-32 MHz	16.5dB	4.5dB	+42dBm
PF841	2-32	16.5	5.0	+46
PF804	215-320	27.0	4.0	+32
PF829	406-512	16.5	4.5	+38
PF833	800-920	26.5	2.8	+34
PF845	800-915	18.0	2.0	+35

In addition to RF Amplifiers, Janel manufactures a wide range of standard Power Dividers and other rf components. Custom designs can be provided for unusual applications. For detailed information, call or write Janel Laboratories, Inc., 33890 Eastgate Circle, Corvallis, OR 97333. Telephone (503) 757-1134.



JANEL LABORATORIES

INFO/CARD 56



How to get fast delivery on step attenuators

Select from the wide range of precision step attenuators in our catalog and get fast delivery. Of course, if you require a custom design we will build it for you but this increases lead time and your cost. Consider modifying your requirements to our catalog specifications. This will get you fast delivery and save you money. It is to your advantage to compare your needs with our specs below.

Alan Step Attenuator Condensed Catalog List

All products manufactured per MIL-Q-9858A and MIL-STD-45662

Series Description	Attenuation Range/Steps	Frequency Max.	Connectors
SV, Subminiature	0-10dB/1dB 0-100dB/10dB	DC-1.5GHz	SMA, SMB, SMC
V, Low Attenuation	0-1dB/0.1dB 0-70dB/10dB	DC-2GHz	TNC, BNC, N, SMA, F
V, Medium Attenuation	0-80dB/10dB 0-100dB/10dB	DC-1GHz	TNC, BNC, N, SMA, F
V, High Power	0-10dB/1dB	DC-500MHz	BNC, TNC, SMA, N
B, Low Cost	0-10dB/1dB 0-50dB/10dB	DC-300MHz	BNC, TNC, SMA, F
SDV, Miniature Dual Concentric	0-29dB/1dB 0-109dB/1dB	DC-1GHz	BNC, TNC, N, SMA
DV, Standard Dual Concentric	0-10.9dB/0.1dB 0-109dB/1dB	DC-1.5GHz	BNC, TNC, N, SMA, F

Whether you use a catalog or custom built unit we want to be of service to you. Call us for price and delivery on the attenuator you require.

Alan

Alan Industries, Inc.
P.O. Box 1203
Columbus, Indiana 47202
Phone: (812) 372-8869

INFO/CARD 57

OSCILLATEK CORPORATION

620 N. Lindenwood Dr. • Olathe, Kansas 66062
Tel: (913) 829-1777 • TELEX: 437045

stabilized controlled thick film hybrid oscillators (TCXO's)

- Baud rate generators and microprocessor drivers
- Screening per MIL-Q-55310 and MIL-STD-883B is available
- QPLD to MIL-Q-55310/883B

temperature compensated crystal oscillators (TCXO's)

Cu30m designed oscillators to meet your specifications

Standard frequencies are available from 1

DIP M80	T05	T08	BAUD RATE GENERATOR	FLAT PACK
<p>Pin 14 = VCC</p> <p>Pin 8 = GND</p> <p>Pin 7 = GND</p> <p>REST = NC/TTP</p> <p>M80 = 80 "length"</p>	<p>Pin 4 = GND</p> <p>Pin 5 = OUT</p> <p>Pin 8 = VCC</p> <p>REST = NC/TTP</p> <p>TTP = INTERNAL TIE POINT</p>	<p>Pin 4 = GND</p> <p>Pin 5 = OUT</p> <p>Pin 8 = VCC</p> <p>REST = NC/TTP</p>	<p>Pin 1 = GND</p> <p>Pin 11 = GND</p> <p>Pin 12 = GND</p> <p>Pin 13 = GND</p> <p>Pin 14 = GND</p> <p>Pin 15 = GND</p> <p>Pin 16 = GND</p> <p>Pin 17 = GND</p> <p>Pin 18 = GND</p> <p>Pin 19 = GND</p> <p>Pin 20 = GND</p> <p>REST = NC/TTP</p>	

NOTE 1: Very low current CMOS analog logic requires an input frequency of up to 20 MHz and 5V is available

NOTE 2: Non standard custom designing with multiple outputs, 20MHz outputs, ECL, 8 pin package available

NOTE 3: Low or high impedance outputs available with custom designing

TCXO's	VCXO's	XO's
<p>STABILITY:</p> <p>1 $\pm 1 \times 10^{-4}$ (0°C to 50°C)</p> <p>2 $\pm 2 \times 10^{-4}$ (-20°C to 70°C)</p> <p>3 $\pm 5 \times 10^{-4}$ (-40°C to 85°C)</p> <p>4 $\pm 1 \times 10^{-3}$ (-55°C to 105°C)</p>	<p>STABILITY: $\pm 0.001\%$ to $\pm 0.01\%$</p> <p>LINEARITY: $\pm 1\%$ to $\pm 10\%$</p> <p>DEVIATION: $\pm 0.001\%$ to $\pm 1\%$</p>	<p>STABILITY:</p> <p>1 $\pm 5 \times 10^{-4}$ (0°C to 50°C)</p> <p>2 $\pm 10 \times 10^{-4}$ (-20°C to 70°C)</p> <p>3 $\pm 20 \times 10^{-4}$ (-40°C to 85°C)</p> <p>4 $\pm 45 \times 10^{-4}$ (-55°C to 125°C)</p>


FREQUENCY RANGE: TTL = 1 Hz to 100 MHz, CMOS = 01 Hz to 10 MHz, ECL = 1 MHz to 100 MHz, SINEWAVE = 100 kHz to 100 MHz

SUPPLY: 5V to 30V (Current as low as 1.5 mA available)

STANDARD SIZES: 1" x 1" x .25", 1.5" x 1.5" x .5", 2" x 1" x .5", 2" x 2" x .5"

IN ADDITION TO OUR STANDARD PRODUCT LINE WE OFFER CUSTOM DESIGN CAPABILITY

INFO/CARD 58

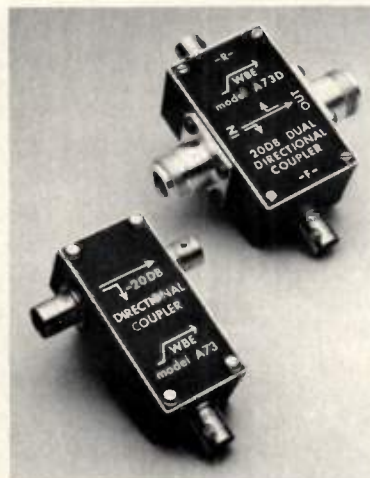

WBE

**BROADBAND EQUIPMENT
FOR INSTRUMENTATION
AND COMMUNICATIONS**

Directional Couplers

Model	Freq Range MHz	Coupler Type	In Line Power	Minimum Directivity (dB)		In Line Loss (dB)	Response Flatness of -20 dB port (dB)	VSWR
				1-500 MHz	5-300 MHz			
A73-20	1-500	single	5W cw (10W cw 5-300 MHz)	20	30	.4 max .2 typical	±.1 5-300 MHz ±.25 1-500 MHz	1.5:1
A73-20GA				30	40			
A73-20GB				40	45			
A73-20P	1-100	single	50W cw (75 ohm limited to 10W cw)	35 dB min		.15	±.1	1.1:1 max
A73D-20P		dual		40 dB min typical		.3		
A73-20PX		single		45 dB min		.15		
A73D-20PX		dual		35 dB min		.15		
A73D-20PA		dual		40 dB min typical		.3		
A73-20PAX	10-200	single		45 dB min		.15		1.04:1 typical
A73D-20PAX		dual				.3		

WIDE BAND ENGINEERING COMPANY, INC.

P. O. BOX 21652 PHOENIX, ARIZONA 85036 U.S.A.


TELEPHONE (602) 254-1570

INFO/CARD 59

Plan to be in ST. LOUIS
JUNE 4-6, 1985



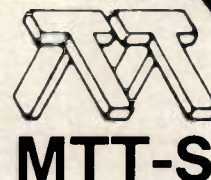To Attend The
1985 IEEE/MTT-S MICROWAVE
SYMPOSIUM/EXHIBITION
and Take Full Advantage of ...



AN OUTSTANDING TECHNICAL PROGRAM — the traditional forum for announcing significant microwave technology and application developments will feature sessions on:

Biomedical • Guided Waves • Communication Systems • Integrated Microwave Systems
• Acoustics and Ferrites • FET Oscillators • Solid State Sources and Amplifiers • FET Amplifiers • Filter Networks • Nonlinear Computer Aided Design • Optical and Submillimeter Wavelengths
• Millimeter Wave Component Technology • Advanced Millimeter Wave Technology • Solid State Device Topics • Active Components • Passive Components

SPECIAL WORKSHOPS AND PANEL SESSIONS — provide unique opportunities for dialogue with recognized specialists from all over the world on these subjects:

Phased Arrays for Hyperthermia Treatment of Cancer • Modern Microwave Oscillator Design Techniques • Advances in Millimeter Wave Subsystems • Historical Perspective of Microwaves
• Future of Microwave Engineers • Microwave Procurement Strategies for the late 80's and 90's

THE LARGEST MICROWAVE EXHIBITION OF THE YEAR — more than 200 microwave component, device, instrumentation, material and subsystem suppliers will display their latest products and be prepared to discuss your needs at production or engineering levels.

A FULL SOCIAL PROGRAM — spouses tours, an exhibitor reception and the MTT-S award banquet complement the program and exhibition activities.

Complete the coupon below and return it to Microwave Journal to receive the Advance Program, advance registration form and hotel reservation forms.

MICROWAVE JOURNAL • 610 Washington Street • Dedham, Massachusetts 02026

Send me additional information on attending MTT-S '85

Name _____ Title _____

Organization _____

Address _____

City, State, Zip Code _____

Country _____ Phone _____

MTT-S Member? ☐ Yes ☐ No

R

INFO/CARD 60

WRH

B-D CRYSTAL

Precision Quality
Fast Delivery



Quartz Crystal Products For:

- COMMUNICATION
- MICROPROCESSORS
- CRYSTAL OSCILLATORS
- TEST INSTRUMENTS
- CATV
- PROTOTYPES

"Any Quantity. . .
Made to Your Specifications"

**48 HR. SERVICE
AVAILABLE
513-522-3300**

1727 W. Galbraith Road
Cincinnati, Ohio 45239
TELEX 21-4545

RF/MICROWAVE ENGINEERS

Representing companies (in New England and National-ly) with hundreds of opportunities for RF and Microwave Engineers means we are the one contact necessary for that right position, whether it be a new challenge or career advancement.

ENTRY TO 3 YRS. EXP 22-35K
MID LEVEL 30-45K
SENIOR AND MANAGEMENT 40-70K

Professional, confidential, free resume preparation service. Client companies assume all interviewing, employment and relocation costs.

Nationwide Business Service

PERSONNEL CONSULTANTS
ESTABLISHED 1937
145 STATE STREET,
SPRINGFIELD, MASSACHUSETTS 01103

AUTOMATIC TEST ENGINEERS:

BSEE/BSCS BACKGROUND IN ATE/SEMI-AUTOMATED TEST EQUIPMENT
HARDWARE: ANALOG & RF CIRCUITS
SOFTWARE: REAL TIME PASCAL/
FORTRAN ASSEMBLY
POSITIONS AS UNIT MANAGERS & SR
PROJECT ENGINEERS
LOCATION SOUTHWEST

PROJECT ENGINEER & SR. PROJECT
ENGINEERS:
BSEE/MS BROAD BAND SOLID STATE
RF POWER AMPLIFIERS

TWT & SWITCHING POWER SUPPLY
DESIGN ENGINEERS
BSEE OR PHYSICS PRODUCT LINE
DESIGN BACKGROUND
SOUTHWEST/SOUTHEAST/ROCKY MNT.


Send resume in confidence to:
Terry Ryder, Sr.

**International
Technical
Services**

P.O. Box 56037
Phoenix, AZ 85079
602/246-6951

INFO/CARD 61

RF ENGINEER Colorado

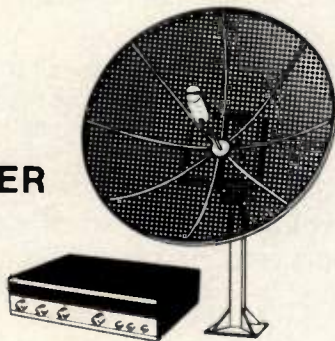

Manufacturer of RF products for TV broadcast, CATV and satellite TVRO needs EE's to design new products. Experience in RF/microwave circuit design required.

Based in Burlington, Iowa and recognized as an industry leader for 30 years, Winegard Company develops new products at its engineering and research division located in a scenic Colorado mountain community within commuting distance of Denver.

Our medium-sized, stable, independent company offers multiple benefits for its professional employees.

Phone or send resume to Jim Kluge, Winegard
R&D Lab, P.O. Box 940, Evergreen, CO 80439.
(303) 674-5576

WINEGARD



Advertiser Index

Acrian, Inc. 4, 29, 31	International Manufacturing Services . . . 67
Adams-Russell — Modpak 30	JFW 7
A.H. Systems 25	Janel Labs, Inc. 73
Alan Industries 74	Jensen Transformers . . . 70
American HV Test Systems 54	E.F. Johnson 32
American Microwave 6	Johanson Dielectrics . . . 14
Amperex-Slatersville 2	D-W Manufacturing 69
Andersen Laboratories, . . 10	Lindgren RF Enclosures . 11
Austron, Inc. 68	MTT-S 75
Aydin Vector 58	Magnetic Radiation Labs . 70
Behlman Engineering . . . 22	Marconi 47-52
Bird Electronics 73	Modular Microwave Devices 35-42
Bliley Electric 18	Motorola Components . . . 3
CTS Knights 9	Oscillatek 74
California Eastern Labs . . 17	Piezo Crystal 62
Centurion International . . 19	Programmed Test Sources 13
Conner-Winfield 33	Q-Tech 67
Daico Industries 28	RF Monolithics 72
Dale Electronics 14	Reaction Instruments . . . 15
Datum 56	Sawtek 23
Eighth Dimension 64	Schaffner EMC, Inc. 34
Elcom Systems 66	Sentry Manufacturing . . . 72
Electro-Metrics 71	Sokol Crystal Products . . 58
Electronic Research 54	Sprague-Goodman Electric 69
Frequency Sources 77	Teledyne Crystalonics . . . 69
Genisco 73	Texscan 78
Glaeste Industrial 54	Varian 12
Glenair, Inc. 70	Vectron 43, 44
Instruments for Industry . . 65	Wide Band Engineering . . 74
Instrument Specialties . . . 55, 57, 59, 61	Wilmanco 66
Intech, Inc. 63	


THE "CAN DO" COMPONENT COMPANY

Semiconductors for Defense, Communication and Instrumentation

You can select with complete confidence from our full line of semiconductors for your UHF to millimeter applications. Whether they be in chip form, glass or ceramic configuration, they have one thing in common — operating reliability. Each has been designed, processed, measured, tested and re-tested to provide optimal performance in some of the most advanced RF and microwave circuits. We produce them by the dozens or thousands to match strict specification requirements, as well as the equally important parameters of price and delivery.

Many of our high performance products are available as standard products, or call to discuss your special design 617-256-8101.

- Silicon Abrupt Junction Tuning Varactors, 30V to 90 Volts
- FLTVAR — Frequency Linear Tuning Varactors
- VHF/UHF Hyperabrupt Tuning Varactors
- GaAs Tuning Varactors 15V to 60 Volts
- Power Generation — Multiplier Varactors
- Step Recovery Diodes
- Harmonic Generator Varactors
- Multi-Chip High Power Generator Varactors
- Noise Diodes
- Gunn Diodes
- Parametric Amplifier Varactors
- Control Devices — PIN and NIP Diodes
- UHF/VHF PIN Diodes
- Power RF Switching
- Small Signal RF Diodes
- HF Power PIN Diodes
- Limiter Diodes
- Chip Capacitors

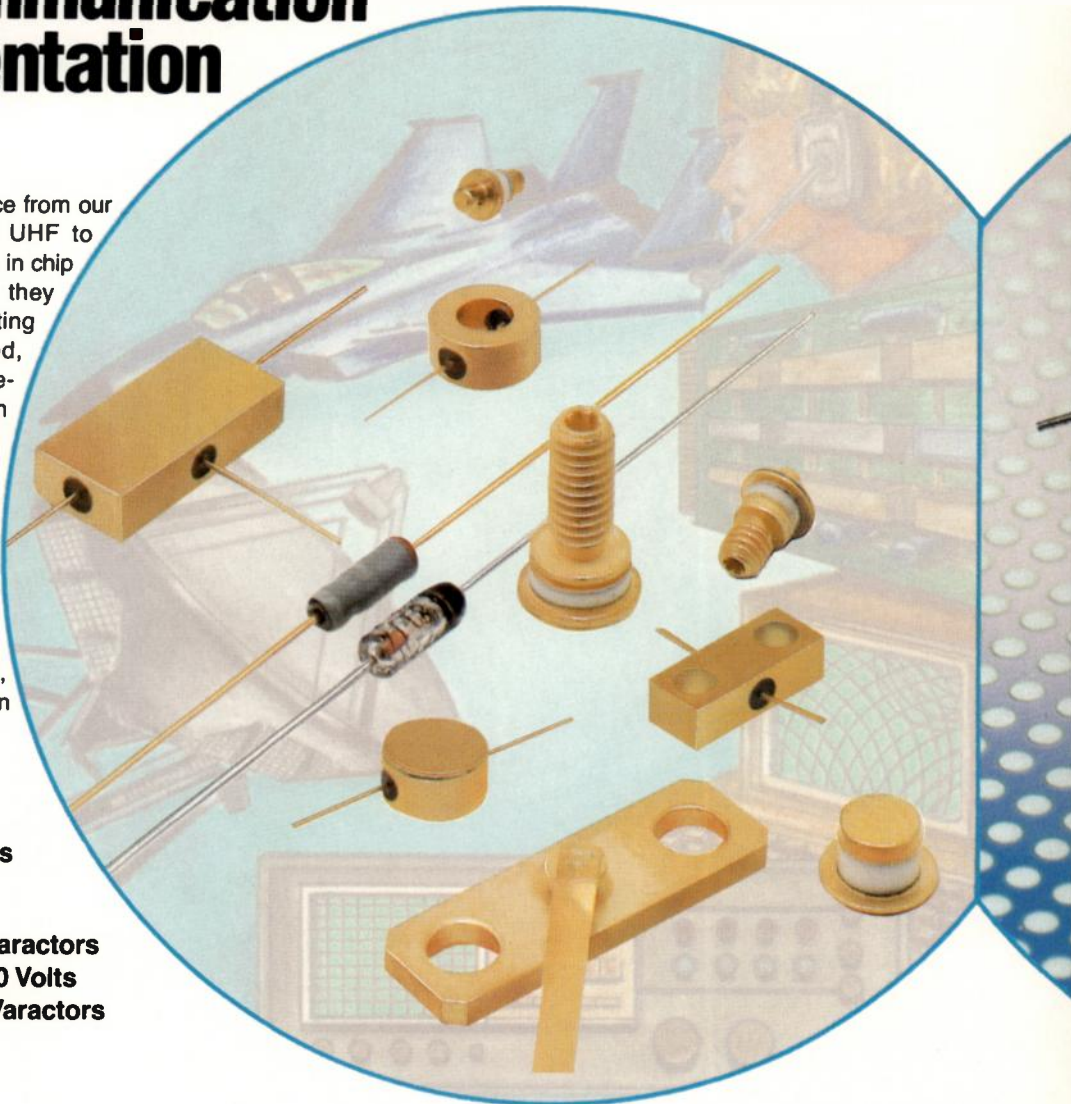

FREQUENCY SOURCES

SEMICONDUCTOR DIVISION

A SUBSIDIARY OF LORAL CORPORATION

16 Maple Road
Chelmsford, MA 01824
(617) 256-8101
TWX (710) 343-0404

ATTENUATORS



The Difference Isn't Always Obvious

At Texscan, we don't believe that you can judge an attenuator by its cover. The point is, all of them look pretty much the same. But, differences lie just below the surface.

Our customers have made it a habit to buy from Texscan because they know we're not just a surface company. Quality construction, reliable performance and customer service are just a few of the underlying reasons to buy Texscan attenuators. And selection is another good reason. Choose from a wide variety of Rotary, Programmable, Fixed, Continuously Variable and Microwave attenuators, all with a choice of connectors in 50 or 75 ohm.

Call Texscan Instruments today. We'll change the way you look at attenuators.

And with features like these:

ROTARY ATTENUATORS

.1, 1 and 10 dB steps
DC to 2 and 4 GHz
Miniature and STD sizes

PROGRAMMABLE ATTENUATORS

.1, 1 and 10 dB steps
DC-2GHz
5V, 12V and 26V control

FIXED PADS

1 to 60 dB
DC-2 GHz
Individual calibration

Texscan
INSTRUMENTS

Texscan Instruments
3169 North Shadeland Ave
Indianapolis, Indiana 46226
(317) 545-4196

INFO/CARD 63