RF Technologies Announces Open-

ing — A new company has opened who will provide high power and super high power waveguide and coax networks, as well as transmission systems and components. The company, RF Technologies Corporation, will also offer a line of RF instrumentation and control equipment. Their address is 482 Congress Street, Suite 101, Portland, Maine 04101. Tel: (207) 773-7778 or (800) 634-4075.

Motorola and Northern Telecom to Develop Open Cellular System Standards — Motorola and Northern Telecom recently announced an agreement to develop major enhancements to their existing cellular products for global markets, based on new open system standards. The two companies intend to jointly specify, develop and implement, in connection with the appropriate standards bodies, open cellular system interface standards which will permit operators to purchase cellular system components from a number of vendors. The standards will be based on existing international switching and cellular standards, such as CCS7, GSM, ISO and ISDN.

New Cellular Network Antenna — CAL Corporation and Bell Cellular recently introduced a new cellular antenna to improve network performance for cellular users. The low profile sectorbeam cellular antenna was developed through a joint venture. The antenna tilt, used to adjust antenna frequency and scope, can be controlled remotely and adjustments no longer need to be done manually.

Antenna Specialists Relocates — Antenna Specialists Company have announced the moving of its Site Management Products Research and Development Group to new facilities in Reno, Nevada. The new facility, with 50 percent more space, will include additional test equipment and environmental test chambers.

Varian Completes Restructuring — Varian Associates recently completed the initial phase of its financial turnaround with the sale of its last remaining non-core business, a broadcast transmitter operation in England, to the Harris Corporation. The sale of this unit and four other non-core businesses and six product lines have generated combined proceeds in excess of \$60 million. The funds will be used for various purposes, including the second phase of Varian's turnaround which involves achieving operational excellence in each of its core businesses - electron devices, analytical instruments, medical equipment and semiconductor equipment

S.T. Research Receives HPI Receiver System Contract — S.T. research has been awarded a contract for the development and product of the High Probability of Intercept (HPI) Receiver System from the Naval Sea Systems Command. The contract, depending upon options exercised and ancillary system and support, will exceed \$50 million.



Celebrating Our 20th Anniversary Year 1971 - 1991

HYBRID POWER DIVIDER/COMBINERS

Models A66 and A67 are hybrid splitter/combiners with exceptional bandwidth and performance for instrumentation and communications. Applications include signal splitting, combining, mixing, and phasing. Due to the high port-to-port isolation, effects of impedance changes, shunts, or disconnections at one or more ports have a minimum effect on the insertion loss or impedance match through the other ports. This high isolation also minimizes intermodulation problems caused by mixing between signal sources.

Each Model A66 or A67 is individually tuned for optimum performance.

Connector options are available. 3-Way, N-Way, and Special Couplers are available. Quantity and O.E.M. pricing.



Model	N-Way	Freq. Range MHz	VSWR (max)	Loss (max) back-back dB	Isolation (with matched input termination) dB	Response Flatness dB	Max Power to Input	Max Power to Output
		1-500	1.5:1	.7	20	±.25		22.5
A00	2	2.5-300	1.1:1	.30	35	±.1		
	2	1-500	1.5:1	.7	20	1.25	5	25
A66GA		2.5-400	1.1:1	.5	40	1.15	Watte	Watte
	2	.3-100	1.5:1	.5	35	1.2	watts	Walls
ADOL		1-50	1.1:1	2	40	±.06		
A66U	2	5-1000	1.2:1	1.0	30	±.3		
		1-500	1.5:1	1.0	20	±.25		1 march
A0/	4	2.5-300	1.2:1	.5	30	1.1	1201100	12 28

WIDE BAND ENGINEERING COMPANY, INC. P.O. BOX 21652, PHOENIX, AZ 85036 TELEPHONE; (602) 254-1570

RF industry insight

HDTV: The World is Waiting

By Gary A. Breed Editor

High definition television (HDTV) has clearly reached critical mass in its development. Regular developmental broadcasts are taking place in Europe and Japan, studio video equipment is readily available (although expensive), and component manufacturers are actively developing products for HDTV receivers and monitors.

The components industry is nearly ready for high-volume HDTV manufacturing, although production will wait until the market requires it. Thomson-ICS, Sawtek, and other SAW device houses have announced HDTV IF bandpass filters. Video amplifier and switching components from Maxim, National Semiconductor, Comlinear, Elantec, Burr-Brown and Analog Devices are capable of handling the required bandwidths. Direct satellite broadcast of HDTV is attractive to GaAs front-end suppliers such as Pacific Monolithics, Triquint and Anadigics.

Also required are high performance analog and digital signal processing components. A-to-D and D-to-A converters with at least 10-bit resolution must accurately handle greater than 25 MHz video bandwidth. Digital signal processing circuits have the same constraints. To put the required performance in perspective, current NTSC studio video requires 6 to 10 MHz bandwidths, depending on the ultimate quality level desired, while HDTV requires 25 to 50 MHz.

Studio equipment is already in place, and manufacturers are clamoring to supply networks, stations and video production houses with new systems. Test equipment, cameras, recorders, graphics and special effects, signal routing equipment, signal processing systems, and monitor makers are waiting for the doors to open on a huge market. However, the list of current suppliers is a Who's Who of Japanese electronics. NHK, the Japanese broadcasting agency, sponsored an HDTV "open house" at the recent National Association of Broadcasters convention, and the list of participating companies included 20 major firms such as Sony, Canon, NEC, Panasonic, and Toshiba.



Nikon offers HDTV imaging for microscopic observation.

Non-broadcast applications are helping keep enthusiasm high while broadcast standards evolve. Medical imaging, industrial monitoring and inspection, photo archives, and military display systems are but a few of the more promising applications. For example, Nikon is promoting high resolution imaging systems for microscopy in medical, metallurgical and microelectronic applications. Although alternative high resolution display technologies are available now, many potential applications will not become widespread until the large guantity manufacturing for consumer HDTV receivers brings prices down.

Terrestrial Broadcast

The selection of a method to bring HDTV to homes in the U.S. is the single major problem area at this time. FCC testing of the five applicants for consideration as the broadcast standard has been delayed again, this time due to delivery problems with a standards converter being built by Tektronix. Final development of this complex unit has required hand-picked A to D converters because standard components cause visible defects in the picture.

The goal of the FCC is to complete on-the-air testing by Spring 1992, in order to have evaluation ready for Commission consideration by September of that year. Selection of a standard is currently planned for early 1993. Many industry and government observers believe that this is the latest possible date that is acceptable, and any further delay will certainly jeopardize the U.S. market position in the world HDTV market.

One industry participant, choosing to remain anonymous, muses, "Why are terrestrial standards holding things up when DBS and fiber are perfectly capable of delivering HDTV?" The strength of the broadcast lobby is one part of the answer to his question, but the situation is not quite that simple. First, neither fiber nor DBS is in widespread use in North America, and the time required to bring those technologies to "universal" status is unknown, perhaps longer than that required for a changeover to a broadcast system that at least approaches the quality available with HDTV.

With HDTV VCRs already developed, and given the current popularity of rented video programming, it will be extremely interesting to see how the average consumer reacts to broadcast television that has somewhat lesser picture quality than taped programming. Currently, the opposite is true.

Which leads us to the biggest question — will the consumer accept HDTV at all? The quality difference is analogous to that of the compact audio disc versus vinyl records, and CDs are enormously successful. However, the improvement offered by stereo AM broadcasting and quadraphonic FM has been generally ignored. Even stereo television sound has been under-utilized.

Will reruns of Gilligan's Island become more interesting on HDTV, or will program producers react to the quality of the medium and produce higher quality programs? The answer to this question is probably the key to HDTV's future, not the technical standards or hardware capabilities. **RF**

For reprints of this report, contact Cardiff Publishing Company at (303) 220-0600; ask for the Circulation Department.

Coilcraft Designer's Kits

First they save you time. Then they save you money.

These kits make it easier than ever to pick the right coils, chokes and other magnetics for your project.

Why waste hours calling around

"Unicoil" 7/10 mm Tuneable Inductors .0435 μΗ - 1.5 μΗ 49 shielded, 49 unshielded (2 of each) Kit M102 \$60

"Slot Ten" 10 mm Tuneable Inductors 0.7 μH - 1143 μH 18 shielded, 18 unshielded (3 of each) Kit M100 \$60

Surface Mount Inductors 4 nH - 33 µH 48 values (10 of each) Kit C100 \$125

Axial Lead Chokes 0.1 μΗ - 1000 μΗ 25 values (5 of each) Kit F101 \$50

Horizontal Mount Inductors Tuneable and fixed Inductance: 31.5 - 720nH 33 Values (6 of each) Kit M104 \$60

Common Mode Data Line Filters Attenuation bandwidth: 15 dBm,1.5-30 mHz DC current capacity: 100 mA 2, 3, 4 and 8 line styles (4 of each) Kit D101 \$65

Common Mode Line Chokes Current: .25 - 9 amps RMS Inductance: 508 µH - 10.5 mH 8 styles (2 of each) Kit P202 \$100

Current Sensors Sensing range: 0.5-35 amps Freq. resp.: 1 - 100 kHz, 50 - 400 Hz Transformer and sensor-only versions 8 styles (15 total pieces) Kit P203 \$50

Base/Gate Driver Transformers Inductance: 1.5 mH Min. Frequency: 10 - 250 kHz 2 single, 2 double section (2 of each) Kit P204 \$50

Mag Amp Toroids Current: 1, 5 amps Volt-time product: 42 - 372 V-µsec 6 styles (2 of each) Kit P206 \$100

Power Filter Chokes Current: 3, 5, 10 amps Inductance: 5 - 300 µH 18 styles (48 total pieces) Kit P205 \$75

Axial Lead Power Chokes Current: .03-4.3 amps Inductance: 3.9 µH - 100 mH 60 styles (2 of each) Kit P209 \$150

Coilcraft

for samples or trying to wind them yourself. Coilcraft's low-cost kits put dozens of values right at your fingertips!

You not only save time on engineering. You also save money when you go into production

Coilcra

Coilcra

because we stock just about all the parts in our kits at low off-the-shelf prices.

Call in today, and you can have your kit tomorrow!

TUNEABLE RF COILS

AXIAL LEAD CHOKES

MAG AMP TOROID

To order, phone 800/322-COIL.

CCIM/electronic engineers master See our catalog in Vol. A, Section 1800

DATA UNE FILTERS

1102 Silver Lake Rd., Cary IL 60013 800/322-COIL Fax 708/639-1469

RF featured technology

A Channel Sounder For Indoor Communications Systems

By Fernando Casadevall and Xavier Barba Department of Signal Theory and Communications Catalunya Polytechnic University

From the beginning of the 80s the possibility of giving total mobility to the increasing number of communications terminal equipment in large buildings like factories, hospitals, warehouses, commercial centers etc., has emerged strongly due to the important advantages it brings. Even though an infrared optical system could be considered for achieving such an objective, it becomes inoperative when obstructed. For this reason, radio systems must be considered.

n radio communication systems, the multiple reflections of the transmitted signal from the structure of the building and surrounding inventory create multipath interference. Multipath has historically been identified as the most important factor limiting mobile and portable radio communication systems. For narrow-band systems (where the baseband digital symbol duration is several times greater than the extent of multipathinduced propagation delays, that is, flat fading conditions), multipath causes large fluctuations (fading) In the received signal voltage due to the changing phasor sum of the signal components arriving at the receiver antenna via different paths. Temporal variations of the channel as well as changing multipath geometry seen by a mobile user are the mechanisms for the fading. Therefore, an accurate characterization of the operating channel is a mandatory prerequisite for the development of reliable indoor radio systems.

Usually we could distinguish between a large scale model, used in determining coverage areas and co-channel interference levels, and a small scale model that describes the fading due to temporal variations of the received signal and used in determining the bit error rate and outage probability.

The expression that characterizes the large scale model is the Path Loss (L) given by L=Kdⁿ where K is an appropriate constant, d is the distance between

transmitter and receiver in meters and n is the mean path loss exponent. For stationary transmitters and receivers, the small scale model is usually characterized by a Rician distribution. In this case the most relevant parameter is the ratio of the received power of the specular radio signal to the average power of the scattered signal.

Measurements reported in References 1 and 2, indicate that n usually ranges between 2 to 6 and K between 1 to 16 dB depending on the building structure. So, there is a great value dispersion and it could be convenient to characterize the operating channel in each case.

In this paper we present a simple channel sounder appropriate for characterizing narrow-band indoor communications channels. The first part is devoted to analyzing the transmitter structure, the second studies the receiver system and the last presents some practical results and conclusions.



Figure 1. Schematic drawing of the CW transmitter.

Transmitter

The schematic drawing of the CW transmitter is shown in Figure 1. We can distinguish five parts. The synthesizer produces a sine signal whose carrier frequency ranges between 800-850 MHz. The frequency doubler changes the carrier frequency up to the 1.6-1.7 GHz band. This signal is not synthesized directly in the 1.6-1.7 GHz area because the voltage controlled oscillator (VCO) and counters (Prescalers) are cheaper and more readily available in the 800 MHz band than in the 1.6 GHz band. The high pass filter eliminates the



Figure 2. Schematic diagram of the synthesizer.

Now <u>we</u> should be your <u>1st</u> source!

Amplifonix is one of the industry's most trusted 2nd sources. With over 10 years of experience in producing high-quality components and thousands of high-performance amplifiers, Amplifonix can deliver a full spectrum of standard and custom products designed to meet your exact specifications.



Frequency	DC to 2000 MHz	
Ins. Loss	0.6 to 2.5 dB	
Isolation	3.5* to 70 dB ⁽¹⁾	
Sw. Spd. (Typ.)	7 to 50 µ sec	
*1500 MHz to 3,000 GHz (1) DC to 1500 MHz		

STEP

Frequency	10 to 500 MHz	
Attenuation Steps	0.1 to 32 dB	
Switching Characteristics	1 μsec to 10 μsec	
Sections	1 to 8 bits	

Write or call for complete information.



2707 Black Lake Place • Philadelphia, PA 19154 PHONE: 215-464-4000 • FAX: 215-464-4001

AMPLIFIERS BIPolar/GaAs FET

Frequency	5-2500 MHz	
Gain	8 to 40 dB	
Noise	1.2 to 9.5 dB	
Pwr Out	Up to +27 dBm	

VCOs

Frequency	70 to 2500 MHz
Output Power	+7 to +20 dBm
Phase Noise 10 kHz to to 100 kHz	-85 to -125 dBc/Hz
Tuning Voltage Sensitivity	2.25 to 12.0 mHz/V
Supply Voltage	+8 to +20



Stanford Telecom... continues to lead the way in providing the highest performance at the lowest cost.

These are but a few of the many outstanding products and prices available today and offered by Stanford Telecom for frequency synthesis and digital communications. For the highest performance and most cost effective solutions in integrated digital communications products, Stanford Telecom continues to stand out as the industry leader.

Call today to discuss how Stanford Telecom might become a member of your team. New prices also available for Stanford Telecom's entire line of Digital Communication ASICs.



Dual 50MHz NCO Only \$25* STEL-1178 (Check for compatibilityand price savings over other dual NCO's available!) 750 MHz GaAs Synthesizer Single Package STEL-2373 (NCO, DAC, converters, etc. all within a single 70-pin package!) 50 MHz NCO Less Than \$20* STEL-1174 (Cost, area, power & spurs are all held to a minimum with this outstanding, low cost performer) 80 MHz BCD NCO Only \$50* STEL-1176 (For BCD interface & resolution characteristics, this NCO is not only distinguished, but unmatched in architecture, performance & cost effectiveness) *1,000 piece quantity

2421 Mission College Boulevard Santa Clara, California 95056-0968 TEL: (408) 980-5684 FAX: (408) 727-1482



Figure 3. Frequency doubler.

spurious signals around 800 MHz that appear at the frequency doubler output. The output amplifier increases the useful signal level up to 20 dBm. Finally, the low pass filter attenuates the level of the harmonics present in the output signal.

In the paragraphs below we describe the most relevant aspects of each part.

Synthesizer - The synthesizer is built around the integrated circuit NJ8820 from Plessey. This circuit contains a reference oscillator, an 11 bit programmable reference divider, two phase comparators: one digital and one sample and hold type, two programmable dividers: one, called A, that counts down to zero from the programmed input, with a 7 bit length, and the other, called M, that counts up from zero to the programmed input and with a 10 bit length, and finally the necessary control and latch circuitry for accepting and latching the input data. By means of an external dual modulus counter (N/N+1), the synthesizer is able to program a total division ratio given by NM+A, where A is between 0 and 127. M is always greater than or equal to A and the minimum division ratio is N2-N. However, the value of N must also be large



```
Figure 4. High pass filter.
```

enough to guarantee that the output frequency from the dual modulus counter not exceed the maximum input frequency of the integrated circuit.

The frequency synthesizer is completed by an active loop filter and a VCO, as shown in Figure 2.

For each synthesized frequency, the NJ8820 circuit reads eight 4 bit words from an external memory. The timing signals needed are provided by the same integrated circuit. With this structure the synthesizer can produce a carrier frequency that ranges from 800 MHz to 850 MHz, with a frequency step of 25 KHz and whose level is around -5 dBm.

Frequency Doubler - The schematic of the frequency doubler is shown in Figure 3. It uses an HXTR3615 transistor as active device. The input matching network is composed of an open circuit microstrip stub and a transmission line, whereas the output matching network uses two open circuit microstrip stubs with two sections of transmission line between them (3). In this case the stub lengths are designed in order to present a 1/4 length at the second and the third harmonic of the output signal, respectively. In this way the network not only matches the output impedance but also introduces a selective effect to the undesired signals. A band stop filter, tuned at 800 MHz, is placed behind the output matching network. This filter is built using two open circuit microstrip stubs and three transmission line sections. Obviously this filter also eliminates the undesired signals placed around the third, fifth and seventh harmonics of the input signal.

It is important to emphasize that this circuit, and everything described below, have been designed using computer aided design (CAD) techniques. In particular, we used the SuperCompact



INFO/CARD 25

29

Do Birds Fly?



They do at Henry Radio.

Because when we receive your order for any *Bird* product it flies out of our warehouse in just 24 hours.

And don't expect us to say we're out of stock on the products you need, because Henry Radio is one of the nation's largest distributors of *Bird* equipment.

Our large inventory includes a vast selection of the most popular *Bird* equipment, including wattmeters, elements, loads and accessories. So if you're looking for a hard-to-find *Bird* product, call Henry Radio.

HENRY RADIO

Over a half-century of reliability in communications.

2050 S. Bundy Drive, Los Angeles, CA 90025; TOLL FREE: 1-800-877-7979; FAX: 1-213-826-7790

INFO/CARD 26

RF Design Software Service

Computer programs from *RF Design*, provided on disk for your convenience. All disks are MS-DOS/PC-DOS compatible, unless otherwise noted

Disk RFD-0591: May 1991

"CAD of Single and Tandem Lange Couplers," by T. O'Connell and P. Murphy. Computes design parameters of Lange couplers, with output in tabular form or in a Touchstone" file format. (Fortran, compiled version and source code listing.

Disk RFD-0391: March 1991

This disk contains "NOVA" by Robert Stanton, a nodal circuit analysis program for AC, time domain, and S-parameter analysis. Numerous models are included, and operating instructions are included in a READ ME file. This is offered by the author as shareware; a co-processor version, additional documentation, and future updates are provided to users who wish to pay for registration

Disk RFD-0291: February 1991

"Cable Equalizer Design," by Frederick Radler of Trilithic. For the design of equalizers to flatten frequency response of cable runs. (Compiled, executable)

Send for a complete listing of available programs, or circle Info/Card below.

Disks are \$9.00 each (5¼ in.) or \$10.00 (3½ in.). Outside U.S. and Canada, add \$8.00 per order. Foreign checks must be in U.S. funds, and must be payable through the U.S. banking system. Prices include postage and handling.

Annual subscriptions are available, providing 13 disks for \$90.00 (51/4 in.) or \$100.00 (31/2 in.). Specify starting date. For subscribers outside the U.S. and Canada: add \$50.00

Payment must accompany order...specify disks wanted...send check or money order to:

RF Design Software Service

PO Box 3702 Littleton, Colorado 80161-3702

Questions and comments should be directed to RF Design magazine

INFO/CARD 100

program for this purpose.

High Pass Filter - In order to attenuate the 800 MHz spurious signal present at the output of the frequency doubler, we have placed a high pass filter before the amplifier. This filter has been designed using a fifth order Butterworth structure (4) and made using transmission lines and short-circuit stubs as shown in Figure 4. The 3 dB cut-off frequency is 1.56 GHz and the insertion loss is 1.34 dB. This structure has a theoretical attenuation value of 50 dB at the 800 MHz band and it guarantees sufficient attenuation of the spurious signals.

Amplifier - The signal level at the output of the frequency doubler is -5 dBm. Therefore, in order to obtain an useful signal of 20 dBm at the transmitter output, the amplifier gain must be approximately 25 dB. This amplifier has three stages with power gains of 10, 10 and 5 dB respectively. The first two stages make use of a HXTR3102 transistor as an active device whereas the output stage uses a BFG34 transistor able to produce the required output level. The matching network between stages is built by means of transmission lines and microstrip stubs in open and short circuit.

In Figure 5 we show the schematic diagram the amplifier. The last two microstrip stubs, placed at the output of the amplifier, are designed in order to attenuate the second and third harmonic respectively. It is important to emphasize that we have chosen for the second stage a short-circuit microstrip stub to diminish the low frequency gain of the amplifier and consequently to increase its stability.

Low Pass Filter - The low pass filter is devoted to attenuation, as much as possible, of the harmonics and other spurious signals present at the output of the amplifier. For this purpose we have chosen a seventh order Butterworth filter, built again using transmission lines and open-circuit microstrip stubs. In Figure 6 shows a schematic diagram of the filter. The 3 dB cut-off frequency is 1.9 GHz and the insertion loss is 0.7 dB. This structure guarantees a theoretical attenuation value of 46 dB at 3.2 GHz (second harmonic of the output signal) and more than 70 dB at 4.8 GHz (third harmonic). These values are sufficient to obtain an output rejection to harmonics and spurious signals greater than 60 dB with respect to the

Trilithic Family Album

From our industry leading surface mount filters to our time-proven rotary and fixed pad attenuators, Trilithic is your source for a complete family of RF and microwave components. Our strict quality assurance standards apply to all product lines, whether your application is for high reliability military or fieldtough commercial items. In addition, Trilithic's high stock volume ensures competitive pricing and availability, so call us toll-free at 800-344-2412, and get acquainted with our family.



Miniature filters



Maveguide filters



Surface mount filters



Cavity filters



Jubular filters



Junable filters



Coarial attenuators



Programmable step attenuators



Pushbutton attenuators



Switch attenuators

Rotary step attenuators



Microwave coasial attenuators

9202 East 33rd Street • Indianapolis, IN 46236 Phone: 317-895-3600 1-800-344-2412 FAX: 317-895-3613



NEW, ALL SOLID STATE AMPLIFIER WORKS INTO ANY LOAD IMPEDANCE.

The 525LA is an extraordinarily versatile source of power that will find wide application in virtually all RF labs. Covering the frequency range of 1 to 500 MHz, with a flat 50 dB of gain, the 525LA is driven to its full Class A linear output by any signal or sweep generator.

Like all ENI amplifiers, the 525LA features unconditional stability, absolute protection from overloads, and it will work into any load impedance. So if you need a rugged source of RF power for RFI/EMI, RF transmission, component testing, NMR or transmitter design, the 525LA amplifier could just be the most useful tool in your laboratory.

For more information, or a full-line catalog, contact us at:

ENI

A Division of Astec America, Inc. 100 Highpower Road, Rochester, NY 14623-3498 (716) 427-8300 Telefax: (716) 427-7839





Figure 5. RF amplifier.

useful signal.

Transmitter Performance - Once the transmitter was made, a complete set of measurements was taken for its characterization. The most relevant features are described below:

-Output level: 18.5 dBm - 0.5 dB -Frequency Range: 1.6 GHz to 1.7 GHz, with 50 kHz steps -Spurious and harmonic rejection: Greater than 60 dBC -SWR: 1.5 at 1.65 GHz, <1.85 between 1.6-1.7 GHz

Receiver

The schematic drawing of the CW receiver is shown in Figure 7. We can distinguish six different parts: an RF amplifier that increases the level of the weak signal present at the antenna output; an RF attenuator that generates an appropriate level at the input of the mixer; the mentioned mixer that produces a frequency translation of the received signal to a new carrier frequency of 70 MH₂; the local oscillator associated with the mixer; an IF amplifier, and finally a logarithmic amplifier that produces an output signal proportional to the received power at the



Figure 6. Low pass filter.

antenna port. This signal is delivered to a data acquisition card, controlled by a personal computer (PC), in order to be processed properly.

As with the transmitter, all the above mentioned subsets of the receiver have been designed using CAD techniques.

RF Amplifier - The schematic of the RF amplifier is shown in Figure 8. It is composed of two amplifier stages and a high pass filter. The first amplifier stage is designed to optimize the noise figure whereas the linearity aspects are emphasized in the second amplifier. Both use common emitter structure with transmission lines and open circuit microstrip stubs for the matching circuits. The transistor HXTR3615 from Hewlett-Packard is used as an active device. The power gains are 12.5 dB for the first stage and 13.5 dB for the second, and the 3 dB bands are 1.5-2 GHz and 1.5-1.9 GHz respectively. A high pass filter is placed between both stages which eliminates the noise and all the spurious signals below 1 GHz that could appear in the antenna port. The cut-off frequency is 1.3 GHz and the insertion loss is 0.3 dB. This high pass filter is placed after the first amplifier in order to optimize the noise figure of the receiver.

RF Attenuator - A simple attenuator can be made using a resistive pi structure. If the resistor values are controlled properly this circuit is capable of giving variable attenuation over a wide bandwidth and provide matched impedances in both ports. On the other hand, for



Figure 7. Schematic drawing of the CW receiver.

When Selecting a Spectrum Analyzer, Go by the Numbers. CATV • EMC/EMI • Mobile Radio • Satellite Communications • Radar • Production test • Broadcast • R&D

from \$12,900



R3261/3361 Series

- 9kHz to 2.6GHz frequency range for R3261A/3361A
- 9kHz to 3.6GHz frequency range for R3261B/3361B
- IHz resolution setting and measurements with synthesis technique
- Also featured are a built-in tracking generator, IC memory card, controller function, preselector and GPIB

from \$5,995

R4131C/4131D Series

- 10kHz to 3.5GHz frequency range
- 22lb(10kg) weight for portability
- -80dBc skirt characteristics
- Also featured are built-in guasi-peak measurement and saving/recalling measurement conditions, including waveforms and GPIB

New visions in test instrumentation



300 Knightsbridge Parkway, Lincolnshire, IL 60069, U.S.A. (708)634-2552 FAX (708)634-2872

AVANTEK MMICs NATURE, AT A NATURAL PRICE

High Performance RF/ Microwave Circuits in Tiny SMD Packages

Fresh idea. A growing family of DC to 5.0 GHz amplifiers, active mixers, and other high performance monolithic microwave ICs (MMICs), at design conscious prices as low as \$0.95 each in 10,000 piece quantities. Avantek's new ISOSAT[™] process yields a harvest of silicon MMICs in plastic SMD packages for portable, handheld, and low-power high-volume designs, where size and cost are as critical as RF performance.

Cellular, Spread Spectrum, Fiber Optics, GPS—Any RF/ Microwave Application

Avantek, the pioneer of commercial and defense RF/microwave solid-state, offers the ISOSAT family of plastic MMICs in bulk, tape and reel. High-volume, low-cost circuits that meet your highest requirements for low power consumption, bandwidth, low noise (as low as 1.7dB), high gain, stability and cascadeability. ISOSAT products make your linear design goals easy and efficient.

Get a Little Help from Your Friends

Avantek has over 50 field specialists around the world to assist in developing your RF/ microwave designs. And, Avantek ISOSAT amplifier product data is available for use in all major CAE libraries, such as EEsof Touchstone.[™]



With over 20 major stocking locations, and a worldwide trans-shipment operation, Avantek has the largest RF/microwave semiconductor distribution network in the world. We meet the demands of the most demanding JIT programs, or supply critical prototypes with the same matchless service and support.



Call Your Local Distributor or 1-(800) AVANTEK for Fast Delivery



Putting Microwave Technology to Work for You



NO WAITING AVANTEK DELIVERS TODAY

Penstock, Inc.

(800) PENSTOCK

Insight Electronics

(800) 677-7716

(800) 334-7127

(800) 548-0409

International

Distributors

BFI-Ibexsa SpA

(49) 89-3195135

(33) 1-69-41-8282

(46-8) 626-99-00

(44) 62-288-2467

Asia and Far East

(81) 03-3475-1121

Yamada Corporation

BFI-Ibexsa Nordic AB

BFI-Ibexsa Electronics LTD.

(39) 2-331-005-35 Milan

BFI-Ibexsa Electronik GmbH

(39) 6-8088191 Rome

Europe

Germany

France

Sweden

II K

Japan

Scie Dimes

Italy

Sertek, Inc.

Canada

Sertek, Inc.

(206) 454-2371 WA

Southwest/Rocky Mountain

North America Distributors Northeast Nu Horizons (617) 246-4442 MA Sickles Distribution Sales (617) 862-5100 MA

East Central Applied Specialties, Inc. (301) 595-5395 MD Nu Horizons (301) 995-6330 MD (201) 882-8300 NJ (516) 226-6000 NY (716) 248-5980 NY (215) 557-6450 PA Penstock East (800) 842-4035 NJ (516) 368-2773 NY (215) 383-9536 PA

Southeast Component Distributors, Inc. (800) 558-2351 FL Nu Horizons (305) 735-2555 FL

North Central Penstock Midwest (708) 934-3700 IL (317) 784-3870 IN

South Central Insight Electronics, Inc. (800) 677-7716 TX Thorson Distributing Co. (214) 233-5744 TX

Northwest Insight Electronics, Inc. (800) 677-7716



Putting Microwave Technology to Work for You



INFO/CARD 50



Figure 8. Receiver part: RF amplifier.

small signals at RF frequencies, the PIN diode, when it is conducting, appears essentially as a pure resistor whose value is roughly inversely proportional to the bias current. Moreover, the quality of this resistor, i.e. its linearity and lack of distortion products, can be very good if the diode is used under the right conditions. So, for these reasons the RF attenuator has been made using a PIN diode attenuator, as shown in Figure 9, where the series and parallel bias currents are properly controlled by means of a single control voltage (5). The insertion losses are 1.5 dB, the attenuation reaches up to 18 dB and the SWR ratio is lower than 2 dB in the full range of the attenuation values.

Mixer - This circuit is built around the SRA-2000 double balanced mixer from Mini-Circuits. In order to guarantee that the RF port and the IF port have 50 ohms at any frequency, special matching networks have been used (6), as shown in Figure 10. The input network is composed of an impedance transformer, made by means of a transmission line, and a short circuit microstrip stub in series with a 50 ohm resistor. At



Figure 9. Receiver part: RF attenuator.

the working frequency the stub appears as an open circuit. Then, the impedance transformer changes the output impedance of the RF amplifier (50 ohms) to the nominal mixer impedance of 200 ohms. At lower frequencies the stub appears as a very small inductive impedance. A 50 ohm resistor is placed at the input of the impedance transformer regardless of the source impedance value. Really, at these frequencies, the 10 pF capaci-



Figure 10. Receiver part: mixer.

When connections are critical, depend on Omni Spectra

When you need subminiature connectors, depend on the company who makes more of them than anyone else. More people buy SMA's from Omni Spectra because we don't compromise on quality.

Our totally integrated capabilities, coupled with state-of-the-art SPC, assure the highest degree of quality. We control the critical processes of machining, plating, brazing and glass sealing in-house. When you really need to get small, think big. Depend on Omni Spectra.

For more information, call or write: M/A-COM Omni Spectra, Inc. 140 Fourth Avenue. Waltham, MA 02254 Tel: USA (617)890-4750 UK (0734)580833 Japan 03(226)1671

See M/A-COM's Latest Technology at MTT-S #1005





Figure 11. Local oscillator chain of the receiver part.

tor guarantees a joint impedance (source plus capacitor) greater than 50 ohms. The output network acts as a low pass filter with a cut-off frequency around 400 MHz. The insertion losses of the mixer and matching networks are approximately 9 dB.

A bandpass filter is placed at the output of the above mentioned circuit in order to reduce the noise bandwidth of the receiver. This filter is a third order Butterworth structure with 10 MHz bandwidth.

Local Oscillator - The schematic drawing of the local oscillator chain is shown in Figure 11. We can distinguish three parts. The synthesizer that produces a sine signal whose carrier frequency ranges between 765-815 MHz and has the schematic shown in Figure 2, but with different words recorded in the memory; the frequency doubler that changes the carrier frequency up to the 1530-1630 MHz band (its schematic is shown in Figure 3) and the amplifier that increases the useful signal level to 7 dBm and whose schematic corresponds to the first two amplifier stages shown in Figure 5.

IF Amplifier - The IF amplifier provides the additional gain necessary to guarantee that, even with a signal level equal



Figure 12. Receiver part: IF amplifier.

to the receiver sensitivity, the IF signal delivered to the input of the logarithmic amplifier has an appropriate level. The schematic is shown in Figure 12, where we can see that the amplifier uses a common emitter structure with an AC feedback between the collector and the base. This feedback permits us to provide the appropriate 50 ohm value to the input and output impedance. The power gain at 70 MHz is 24 dB and the amplifier band ranges between 20 to 140 MHz.

Logarithmic Amplifier - The logarithmic amplifier is a device that produces a video output which is proportional to the logarithmic value of the IF input amplitude (7). It uses a cascade of logarithmic video amplifiers which permits almost 70 dB of the dynamic range. This amplifier whose schematic diagram is shown in Figure 13 is basically built using three SL623B and one SL621B integrated circuits from Plessey. These integrated circuits are intended primarily for use in successive detection logarithmic IF strips, operating at center frequencies between 10 and 140 MHz. For the SL621B the mid-band gain voltage





RF Design



Filmtrim® Single Turn Plastic Trimmer Capacitors

- Cap ranges: 1.0-5.0 pF to 25-500 pF
 Q to 5000 at 1 MHz
- Operating temp: PTFE, Polycarbonate, Polyimide: -40° to +85°C Polypropylene: -40° to +70°C High temp PTFE: -40° to +125°C
- 6 sizes from 5 mm to 16 mm
- More stable with temperature than other single turn trimmers

Phone, fax or write today for Engineering Bulletin SG-402E.



134 Fulton Ave Garden City Park, NY 11040 Phone: 516-746-1385 • Fax: 516-746-1396

INFO/CARD 32



Airtrim® Single Turn Air Dielectric Trimmer Capacitors

- Cap ranges: 1.0-3.7 pF to 2.9-24.0 pF
- Q typically 8000 at 1 MHz;
- 4000 at 100 MHz; 1500 at 200 MHz • Operating temp: -55° to 85°C
- Temp coeffcient as low as 10 ± 10 ppm/°C
- 2 sizes and 10 mounting configurations for printed circuit and panel mounting
 Machined from solid brass

- Machined from Solid Drass

Phone, fax or write today for Engineering Bulletin SG-600A.



134 Fulton Ave Garden City Park, NY 11040 Phone: 516-746 1385 • Fax 516-746-1396



Figure 14. Photograph of the antenna.

is around 12 dB whereas for the SL623B it is 24 dB. The former provides a logarithmic characteristic over a 10 dB range and the later over 20 dB. As the integrated circuits provide a current whose level is proportional to the logarithm of input signal (with maximum level equal to 2.1 mA), the common base transistor and the operational amplifier act as a current-voltage transformer with appropriate gain and DC offset.

The input signal must range between 0.2 mV_{RMS} and 1 V_{RMS} for an accurate behavior of the logarithmic amplifier, but it could withstand input voltages up to 1.8 V_{RMS} without damage. Within the input range, the dynamic error of the logarithmic characteristic is lower than 0.5 dB and the DC output signal ranges between 0 to 5 Volts.

Receiver Performance - Once the receiver was built, we obtained a complete set of measured characteristics, whose most relevant aspects are described below:

- Sensitivity: -97 dBm
- Maximum input level: 0 dBm
- IF Bandwidth: 10 MHz
- Logarithmic amplifier output: 0-5 Volts
- CAG: 18 dB manually controlled
- SWR: 1.9 at 1.65 GHz, <2.2
- between 1.6-1.7 GHz

Antennas

In order to complete the channel sounder, two monopole antennas with ground planes were constructed. We used a 1/4 monopole with four bars inclined 45 degrees to simulate the ground plane. The measured SWR at the antenna port is lower than 1.2 in the 1.6-1.7 GHz working band. A photograph of the antenna is shown in Figure 14.

Preliminary Measurements and Conclusion

Using the above described channel sounder, some preliminary measurements of the propagation conditions inside buildings were done. We recorded the received signal during 20 minute periods and using 20 samples/ sec. In Figure 15 a typical example of the recorded measurements of the received signal amplitude in two standard cases is shown. The first case is line of sight between the transmitter and receiver and the second when obstructed. In both cases we can see large fluctuations (fading) in the received signal voltage. As was explained in the introduction, these fluctuations are due to the changing phasor sum of the signal components arriving at the receiver antenna via different paths. Presently a complete set of measurements is in process in order to characterize the transition channel in different buildings constructed using different materials.

In conclusion, a simple narrow-band channel sounder, appropriate for characterizing narrow band indoor communications channels, has been described.



Acknowledgements

This work has been supported by CICYT (Spain) under Grant TIC880543. RF

References

1. R. Bultitude, "Measurement, Characterization and Modeling of Indoor 800/ 900 MHz Radio Channels for Digital Communications," IEEE Communications Magazine, Vol.25, pp.5-12, June 1987.

2. T. Rappaport, "Indoor Radio Communications for Factories of the Future", IEEE Communications Magazine, Vol.27, pp.15-24, May 1989.

3. K.C. Gupta and alt., Microstrip Lines

and Slotline, Artech House, New-York, 1970.

4. A. Zverev, Handbook of Filter Synthesis, John Wiley and Sons Inc. New York, 1970.

5. Hewlett-Packard, "An Attenuator Design Using PIN Diodes," Application Note 912.

6. J. Kestler, "Matching Circuits for Schottky Ring Mixers," VHF Communications, Vol.1, pp. 13-18, 1976. 7. M. Birch, "Logarithmic Receivers,"

Advanced Signal Processing (edited by D.J. Creasey), IEE Telecommunications Series. Peter Peregrinus Ltd. London 1985.

About the Authors

Fernando Casadevall received his Engineer of Telecommunications and PhD degrees from the Catalunya Polytechnic University in Spain. He has been an Associate Professor there since 1983. Xavier Barba received his Engineer of Telecommunications degree from Catalunya Polytechnic University in 1990. He is currently doing research on mobile communications. They may be reached at Dpto. Teoria del Senval i Comunicacions, Universitat Politecnica de Catalunya, Apdo. 30.002, 08080-Barcelona, Spain. Tel: 34-3-4016781. Fax: 34-3-4016901



Figure 15. Signal level at the antenna port versus the time, (a) line of sight, (b) obstructed.

Your Design Deserves It.

You work hard to design a quiet synthesizer. Shouldn't you have a PLL to match?

With QUALCOMM's new Q3036 single-chip PLL, you can have a PLL noise floor of <-150dBc at 100 Hz.

You can input VCO frequencies from DC to 1.6 GHz using the built-in prescaler while selecting division ratios as wide as 2 to 1295.

Choose reference input frequencies from DC to 100 MHz with division ratios of 1-16.

The quiet Q3036 PLL, named a Top New Product of 1990 by the editors of Microwaves & RF magazine.

Now it's your turn to give what you and your synthesizer deserve. Peace and Quiet.

To learn more, please call or FAX:



VLSI Products Division 10555 Sorrento Valley Road San Diego, CA 92121 USA TEL: 619-597-5005 • FAX: 619-452-9096

INFO/CARD 34 Please see us at the MTT-S Show, Booth #721.

RF featured technology

High Power Bi-Directional Coupler For Space Applications

By Pascal R. Goux Ancom Electromagnetics Ltd.

Satellites requiring their transmitted RF power to be amplified in a linear fashion, such as M-SAT and INMAR-SAT, need carefully controlled amplifiers in order to maintain optimum operating conditions.

his paper describes the RF portion of the control circuitry associated with the L-Band High Power Amplifier designed for such service by Spar Aerospace of Montreal.

Each amplifier has a 27 dB bidirectional coupler at its output to allow measurement of transmitted and reflected signal power levels. The resulting detector signals are used to limit output power, hence power consump-







tion without degrading linearity, and to protect the amplifier against output mismatch. In order to obtain sufficient accuracy, high directivity in the coupler is essential. A block diagram is shown in Figure 1.

The design of the coupler is presented together with a description of the method by which high directivity is obtained. Artwork and measured results are presented including results from high power testing in vacuum. The objective is to design, build and test a coupler with the specifications of Table 1.

Choice of Configuration

In order to be compatible with the rest of the circuitry making up the amplifier, the coupler must be fabricated using microstrip techniques on metallized alu-

 Operating Frequency	1 to 2 GHz
Low Insertion Loss (to minimize impact on amplifier efficiency)	≤0.15 dB
Low Coupling Value (to minimize insertion loss)	<mark>≼−25</mark> dB
High Directivity (to differentiate forward & reflected signals)	≥25 dB
High Isolation (to achieve high direc- tivity with low coupling)	≥50 dB
Return Loss (to guarantee the direc- tivity)	≥25 dB
Must sustain high CW power and be tempera- ture insensitive	≥100W −60°C +120°C

NOTE: Must also be bi-directional, symmetrical and easy to fabricate (preferably not to require tuning)

Table 1. Design specifications.

Figure 2, Artwork.



Testing for rf susceptibility to 200 volts/meter? You need the power to do it.

If you're lining your shielded room with anechoic material to avoid mutipath reflections, you already know you need an amplifier with infinite-VSWR tolerance. But you also



need an amplifier/antenna marriage made in heaven. Here is one of our many matched systems specifically designed to assure you reliable field levels as high as 1.000 V/m.

Our new Model 400HB power amplifier delivers a *minimum* of 400 watts through a bandwidth of 400 to 1,000 MHz. And our Model AT4001 horn antenna dis-

plays the happy faculty of putting out more V/m as the frequencies rise.

Other matched systems of AR amplifiers and antennas cover the frequency spectrum from 10 kHz to 1 GHz with reliable power from one to 2,000 watts. Systems that give you the reserve power you're bound to need sooner than you may think. Systems that let you sweep clean through the band of interest without the headache and delay of changing antennas.

Why not chat—on our nickel—with one of our applications engineers about *your* rf susceptibility-testing situation? He'll answer the phone himself when you dial



160 School House Road, Souderton, PA 18964-9990 USA 215-723-8181 • TWX 510-661-6094 • FAX 215-723-5688

mina substrate (0.050'' thick, $\varepsilon_r = 9.9$).

The problem of designing a high directivity coupler in this medium, (compared to an ideal TEM design), is due to the inhomogeneity of the dielectric structure. The isolation of the coupler is the most difficult characteristic to control, requiring wave cancellation and equal phase velocities for the even and odd modes of propagation. The quarter-wave edge coupled design approach is chosen for its symmetry and simplicity, however the non-TEM propagation must be compensated.

Design Details

In order to solve the problem of non-TEM propagation, various techniques have been proposed. References 1 and 2 describe the Wiggly

NEW MULTIPORT SWITCH MULTIPORT N303 SERIES SMA SWITCHES Excellent insertion loss repeatability Epoxy sealed cases Low power actuator DC - 18 GHz operation Convenient packaging Competitive pricing • 12 & 28 volt actuator; 6,5,4 & 3 ports are options **BURNE, INC.** COMPANY A 2085 SHELBURNE ROAD, SHELBURNE, VERMONT 05482 TEL 802-985-8621 FAX 802-985-2070 INFO/CARD 36

coupled line but the available design information and mathematical relationships are not well suited for loose coupling. The electromagnetic field analysis is quite complex and none of the known CAD tools are helpful in this regard. References 3-5 describe the dielectric overlay coupler, but show poor repeatability due to the overlay boundary's position affecting matching, coupling and isolation. This solution is also somewhat cumbersome to produce and may be sensitive to high temperatures and high power levels. A configuration that is simple, repeatable and requires no tuning would be preferable.

References 6-10 present the design of an edge coupler with lumped capacitors at each end to compensate for the unequal phase velocities of even and odd modes at the isolated port. In the even mode, the capacitors have no effect, but they increase the odd mode phase length (transit time, ε_{reff} odd), thus equalizing the waves.

Due to the small value of the capacitance required, it can be realized as an interdigital structure (ICAP) formed on the same microstrip substrate as the coupler. From a mathematical approach, a capacitor at each end of the coupled



Figure 3. Predicted vs. experimental return loss (S₁₁).



Figure 4. Predicted vs. experimental insertion loss (S_{21}) .

Because you're thinking fast... Quads compress space and cost.

Multi-channel designs have you in a corner? Want to cut cost and space? Then take a look at Comlinear's four new high-speed quad amplifiers.



Fast op amps for multi-channels.

For high-speed designs such as multistage active filters and video, consider these quads. The 90MHz CLC414 offers high speed and low power with a 1000V/µs slew rate at just 2mA per channel. And our 160MHz CLC415 combines excellent video specs with a fast 1500V/µs slew rate at only 5mA per channel. INFO/CARD 37

Buffers for video and more.

For multi-channel buffering, the 200MHz CLC114 features a 450V/ μ s slew rate at 3mA per channel. It's ideal for driving high density crosspoint switches. And our 350MHz (5V_{pp}) CLC115 delivers a 2700V/ μ s slew rate for large-signal designs. Plus 0.03%/0.03° diff. gain/phase with the ability to drive up to six video loads per channel.

Call today for details. And start cutting down on space and cost. INFO/CARD 38



Solutions with speed

4800 Wheaton Drive Fort Collins, CO 80525 (303) 226-0500 1-800-776-0500 (USA)



At last: A complete GPS station clock under \$10,000

Everything you want in a GPS station clock, in one neat box:

- GPS receiver
- Disciplined standard
- Multiple output timing signal generator, and much, much more.

What do you expect from a company with more than 30 years of production and field experience in the timing business? You'd expect a one-unit master timing station, capable of tracking six satellites simultaneously — even while moving at 1,000 miles per hour — all inside a $3\frac{1}{2}$ inch rack-mount chassis.

That's the **Model 8810** — a mature product, valueengineered and time-tested, just like the ones we've been providing to NASA and DoD for decades. And there's so much built into this unit, it's hard to describe. Just review the features listed below:

- Automatically determines geographical coordinates no need to enter position anywhere on earth
- · Automatic multi-satellite acquisition
- Time accuracy maintained with platform velocities to over 1,000 mph
- · Outputs position data whether stationary or moving
- Multiple time code and rate output options
- · User friendly, menu-prompted setup
- 20-key keypad and 4-line, 40 character display allows complete operation, checkout, and status acquisition without ancillary equipment
- · Nonvolatile memory stores setup and data indefinitely
- · Accurate to within 100 ns worldwide, 24 hours a day

- RS-232 remote control and time output (optional IEEE-488 output)
- RS-232 printer port
- · Displays time, position, and REF-UTC/GPS
- Time display is keypad-selectable to UTC, GPS, or local time
- 115/230 VAC with optional 24 VDC backup
- Antenna with 50' coax cable included
- · Built-in test routines
- · Fully modularized
- · GPS receiver is drop-in replaceable
- Workmanship standards to MIL-STD-454
- Three-year limited warranty
- Plus, a host of desirable options

That's the **Model 8810**, from TRAK Systems. And at this price, there's nothing else like it on the market. So why pay more, and install boxes of equipment, when you can have it all in one neat unit?

For free literature, or more information, contact us at:

TRAK SYSTEMS DIVISION 4726 Eisenhower Blvd. Tampa, Florida 33634-6391 Phone: (813) 884-1411, extension 248 TLX: 52-827 FAX: (813) 886-2794



line is used, (they must be separated by a quarter-wave length in order not to generate scattered waves to all ports). As mentioned in Reference 11, the capacitor at either end is satisfactory, but in order to have a good return loss, the capacitor should be located in the middle of the coupler to preserve the double symmetry of the circuit. The possibility of using just one capacitor located in the middle of the coupler was then investigated.

With this configuration, some characteristics tend to conflict and it is theoretically impossible to obtain both coupling flatness and optimum isolation. The selection of the capacitor requires evaluating the major performance parameters in terms of the intended service. In our case, the slope in frequency response of the coupled port can be conveniently equalized with a capacitor in the middle of the double-pi attenuator. Note that if the ICAP varies, the slope does not change, only the level changes. The design therefore is made for maximum isolation and the capacitor value is calculated to be 0.11 pF. The model of the ICAP was derived from Reference 12. It is important to note that the ICAP has a significant shunt component that can affect the even mode. In order to reduce this undesired shunt capacitance, the ground plane below the ICAP is removed. Figure 2 details the artwork and layout of the coupler, attenuators and detectors. Note the ICAP and compensating capacitors (C1) in the attenuators (AT1 and AT2).

The coupling value was chosen for the best tradeoff between low insertion loss (loose coupling) and high directivity (tight coupling because of fixed isolation). Optimum power levels and slope for the Schottky diode detectors (D2) is then adjusted with the appropriate attenuator. The computed prediction and experimental results are shown in Figures 3-6.

Results

Due to the double symmetry of the coupler (verified experimentally), only four parameters are shown: the return loss (S_{11}) in Figure 3, the insertion loss (S_{21}) in Figure 4, the coupling (S_{31}) in Figure 5 and the isolation (S_{41}) in Figure 6. Comparing these experimental results and computer predictions, we can see some small explainable differences.

In Figure 3, we see that the predicted return loss is better than the one obtained experimentally. This is attributed to the connector-to-microstrip discontinuities.

In Figure 4, we see that the experimental insertion loss is more than expected. This is due to the coaxmicrostrip transition which was not included in the simulation.

In Figure 5, we see a small difference in the slope and level of the coupling. The slope difference is due to the presence of the capacitor between the two coupled lines in the coupled region resulting in an incomplete confining of the fringing field through the dielectric. The level difference is due to the ICAP stray capacitance to ground.

In Figure 6, we see that the isolation is as expected, the small difference being due to a 0.1 pF over-etching of the ICAP. This could be fixed with a dielectric slab to increase the serial ICAP



Kay Dependable Attenuators

Kay Elemetrics Corp. offers a complete line of **Programmable, In-Line and Continuously Variable Attenuators.** We can supply you with the right model to fit your application. We have both 50Ω and 75Ω models from DC-3GHz.

Model	Imped	- Freq.	Atten.	Steps
No.	ance	Range	Range	
839 1/839 847 870	50Ω 50Ω 75Ω 75Ω	DC-3GHz DC-1GHz DC-1GHz DC-1GHz DC-1GHz	0-101dB 0-22.1dB 0-102.5dB 0-132dB	1dB 1dB 1dB 1dB
4440	50Ω	DC-1.5GHz	0-130dB	10dB
4450	50Ω	DC-1.5GHz	0-127dB	1dB
1/4450	50Ω	DC-1GHz	0-16.5dB	.1dB
4467	75Ω	DC-1GHz	0-31dB	1dB
0/400	50Ω	DC-500MHz	1-13dB	Ξ
0/410	75Ω	DC-400-MHz	2-14dB	

For more information or to place an order call Kay's **Product Specialist at (201) 227-2000**.

KAY

Kay Elemetrics Corp.

12 Maple Avenue • Pine Brook, NJ 07058 USA Tel. (201) 227-2000 • TWX: 710-734-4347 FAX: (201) 227-7760



Figure 5. Predicted vs. experimental coupling (S₃₁).

value (note that all results are without RF tuning).

Acknowledgement

This paper was written while the author was employed by Spar Aerospace as an RF/Microwave engineer.

References

1. A. Podell, "A High Directivity Microstrip Coupler Technique," International Microwave Symposium, IEEE MTT 1970, pp. 33-36 2. F.C. de Ronde, "Wideband High Directivity



WHEN IT COMES TO OSCILLATORS, ONLY RALTRON HAS IT AL

RALTRON manufactures one of the industry's most complete lines of high quality oscillators. Call us for all your oscillator needs from clock to temperature compensated, oven or voltage controlled. Or call us for our 28 page catalogue.

WORLD'S SMALLEST OCXO - ROXO 210A

- Frequency Range: 1.0 MHz-20.0 MHz
- Temperature Stability: ±2 x 10⁻⁷ (-20°C to +65°C)
 Long Term Stability: ±2 x 10⁻⁷ per year
- Phase Noise: 145 dbc (10 KHz offset)
- Power consumption (stabilized): 2.0 W • Size: 35.3 x 27 x 25.4 mm (1.40" x 1.06" x 1.0")

MINIATURE TCXO – RTXO-065-X

- Frequency Range: 1.0 MHz-20.0 MHz
- Frequency Stability: ± 1.0 ppm (-40°C to +85°C)
- Aging: ±1.0 ppm per year Size: DIL 16 Pin (.980" x .520" x 0.4")
- MIL 0-55310 if required

The Products. The Prices. The People. Only RALTRON has it all.

FRON ELECTRONICS CORP. 2315 NW 107th Avenue, Miami, Florida 33172

FAX (305) 594-3973 TELEX 441588 RALSENUI (305) 593-6033



Figure 6. Predicted vs. experimental isolation (S₄₁).

in MIC Proximity Couplers by Planar Means," International Microwave Symposium, IEEE MTT 1980, pp. 480-482.

3. B. Sheleg and B.E. Speilman, "Broadband Directional Couplers Using Microstrip With Dielectric Overlays," IEEE MTT 1974, pp. 1216-1220

4. D.D. Paolino, "MIC Overlay Coupler Design Using Spectral Domain Techniques," IEEE MTT 1978, pp. 646-649.

5. B. Majkic and C.E. Smith, "Analysis of Two-Conductor Microstrip Transmission Lines With Dielectric Overlay," IEEE Southeastcon '82 Conference Proceedings, April 1982, Paper 4.2, pp. 84-87.

6. G. Schaller, "Directivity Improvement of Microstrip #/4 Directional Couplers," AEU 26, 1972, pp. 508-509.

G. Schaller, "Optimization of Microstrip Directional Couplers With Lumped Capacitors,

AEU 31, 1977, pp. 301-307. 8. H.J. Herzog, "Microstrip Couplers With Improved Directivity," Electronic Letters, Vol. 14, Feb. 1978, pp. 50-51

9. D. Kajfez, "Raise Coupler Directivity With Lumped Compensation," Microwaves, Vol. 17, March 1978, pp. 64-70.

10. S.L. March, "Phase Velocity Compensation in Parallel-Coupled Microstrip," IEEE MTT Symposium Digest, 1982, pp. 107.1-107.3. 11. L.F. Franti and G.M. Paganuzzi, "Wideband

High Directivity Microstrip Couplers for Micro-wave Integrated Circuits," European Microwave Conference, 1980, pp. 377-381. 12. J.I. Smith, "The Even- and Odd-Mode

Capacitance Parameters for Coupled Lines in Suspended Substrate," IEEE MTT 1971, pp. 32-38

About the Author

Pascal Goux is currently an EMI/ EMC engineer working as a consultant for Ancom Electromagnetics Ltd. He may be reached at 9665 Cote de Liesse, Dorval, Quebec, H9P 1A3. Tel: (514) 633-9679. Fax: (514) 633-9681

Meet our new division.

Frequency Divide	ers			NEC
÷ 2	÷ 4	÷ 8	÷ 2/4/8 ÷ 8/9	÷ 10/11
		4	Time	
UPG502 UPB565 UPG504 UPB581 UPB558 UPB584	UPG501 UPB565 UPG503 UPB582 UPB585	UPG506 UPB565 UPB567	UPB555 UPB587	UP B551 UPB552 UPB554
÷ 16/17	÷ 20/21	÷ 20/22	÷ 32/33	÷ 40/41
UPB553 UPB556 UPB555 UPB571	UPB572	U PB551 UPB552 UPB554	UPB555 UPG569 UPB571	UPB572
÷ 40/44	÷ 64	÷ 64/65	÷ 64/68	÷ 80/81
ALL				
UPB551 UPB552 UPB554	UPB564 UPB565	UPB566 UP B569 UPB571	UPB562 UPB568	UPB572
÷128 ÷ 128/129	÷ 128/64	÷ 128/136	÷ 256	÷ 256/512
	٠	•	٠	(in
UPB564 UPB566	UPB588	UPB562 UPB568	UPB564	UPB586

Our low cost prescalers help you divide and conquer just about any design problem you face, including delivery.

Need wide band-width? Low power dissipation? Performance to 14 GHz? Start here and save money. We have both Silicon and GaAs ICs—in chips and a variety of packages from auto-insertable to MIL screened.

And the price is right.

So if frequency division has been multiplying your design costs, give us a call. We'll send you a *Product Summary and Selection Guide*, and arrange for samples and applications assistance. NEC quality and CEL support. It's a combination that'll work for you.



California Eastern Laboratories

CEL Headquarters, 4590 Patrick Henry Drive, Santa Clara, CA 95056-0964; (408) 988-3500 FAX (408) 988-0279 Santa Clara, CA (408) 988-7846 🗆 Los Angeles, CA (213) 645-0985 Bellevue, WA (206) 455-101 🗆 Scottsdale, AZ (602) 945-1381 🗆 Richardson, TX (214) 437-5487 🗀 Shawnee, KS (913) 962-2161 🗆 Woodridge, IL (708) 241-3040 🗠 Cockeysville, MD (301) 667-1310 Peabody, MA (508) 535-2885 🗆 Hackensack, NJ (201) 487-1155 or 487-1160 🗆 Palm Bay, FL (407) 727-8045 🗀 Nepean, Ontario, Canada (613) 726-0626

© 1991, California Eastern Laboratories

RF products

20 MHz General Purpose/Arbitrary Function Generator

John Fluke Mfg. Co. introduces the PM 5139 from Philips Test and Measurement, a 0.1 mHz to 20 MHz function generator combining ten general purpose test waveforms with arbitrary function capability. Sonar, mechanical testing, brain and heart waves, and baseband video or RF signals are just a few examples of arbitrary waveform applications. Using WaveCAD, a waveform generator and editing software package available from Fluke, the PM 5139's memory can be loaded with up to six arbitrary waveforms. Also, a real signal can be captured with a Philips digital storage oscilloscope, edited in software, and downloaded to the PM 5139.

Standard waveforms include sine, triangular and square waves, positive and negative rectangular pulses, positive and negative sawtooth waves, haversine, half-period sine, and triangular pulses. Modulation modes available are: AM, FM, gating, bursts, PSK, and linear or logarithmic sweeps. Frequency accuracy is within ± 2 ppm over the entire range, with low jitter and phase noise, and very flat amplitude response. In the low frequency range, five of the standard waveforms can be varied in duty cycle from 1 to 99 percent with 0.1 percent accuracy. All manual settings can be performed remotely using an IEEE-488 bus interface.

The panel has a single rotary knob for numerical setting of parameters, with a logical array of parameter selection and control keys. Each key activates the rotary knob for dialing in the desired setting. A large central backlit LCD display shows all instrument settings at a glance.

The price of the PM 5139 is \$4190, or \$4690 with the IEEE-488/GPIB interface. John Fluke Mfg. Co., Inc. INFO/CARD #230



Six-Octave Bandpass Filter

Optolectronics announces a new receiver bandpass filter that separates closely space radio signals. The Model APS-204 has a constant 4 MHz bandwidth, tunable over a 20 MHz to 1000 MHz frequency range.

The unit is an active circuit with no loss and very small size (4×1) $1/2 \times 7$ inches). At the heart of the circuit is a 4 MHz bandwidth, 4-pole resonant cavity filter with a Q of 325. A unique doublehetrodyne technique currently being patented routes the signal to the filter and back to the operating frequency.

Noise figure is specified at 10 dB, and the third-order intercept is 15 dBm, typical. Power requirements are 12 VDC with 6 watts consumption. Price of the APS-204 is \$995.

Optoelectronics Inc. INFO/CARD #229



RF Modem for Wireless Networking

The RF Modem, using unlicensed spread spectrum tech-



niques defined by FCC Part 15, has been introduced by Proxim. Applications include hospital bedside monitors, point-of-sale devices, portable data recorders, traffic management, and security systems.

Usable for distances up to 500 feet, the RF Modem interfaces to a computer using a standard RS-232 or RS-485 port. Packages and unpackaged versions are available.

Two unpackaged version are available for designing into OEM products. One operates at 121 kbps, while the other operates at 242 kbps. **Proxim, Inc.**

INFO/CARD #228

Farnell Instruments Now Available in U.S.

Wayne Kerr announces the introduction of the Farnell line of RF test instruments to the U.S. and Canadian markets. Farnell equipment has previously been marketed in the U.K. and the rest of Europe.

The product line includes the following signal generator products: The PSG1000 Synthesized Signal Generator (pictured below) covering 10 kHz to 1 GHz, the ESG Signal Generator which also covers 10 kHz to 1 GHz, the 100 kHz to 2 GHz SSG2000 Signal Generator. Other current product models include the 352C Spectrum Analyzer, covering 300 kHz to 1 GHz, and the AMM2000 Modulation Meter with 250 kHz to 2.4 GHz coverage.

Wayne Kerr Inc. INFO/CARD #227



Lightning Protector for Cellular Radios

Huber+Suhner has introduced a 1/4-wave shorted stub specifically designed for cellular radio base stations, with an operating frequency range of 797-1016 MHz. Features include lower residual pulse than other protection methods and no intermodulation effects. The unit is offered with either type N or 7/16 connectors.

Mechanically, the lightning protector features zinc diecast construction, waterproof design for outdoor installation, and easy mounting with standard plumbing brackets or clamps. Huber+Suhner AG

INFO/CARD #224



Common Problem: SPECS CALL FOR CUSTOM DESIGN – DEADLINES CALL FOR OFF-THE-SHELF

Simple Solution: CALL MERRIMAC (201)575-1300

Our Stock is Anything but Common!

Double Balanced Mixers Image Reject Mixers Biphase Modulators Frequency Doublers Quadraphase Modulators Vector Modulators Single Sideband Modulators Phase Modulators I & Q Phase Detectors Frequency Discriminators Phase Comparators Analog Phase Shifters Digital Phase Shifters Precision Phase Resolvers 0° Power Dividers 2, 3, 4, 5, 6, 8 & 12 ways 90° Power Dividers Quadrature Hybrids

Merrimac

41 Fairfield Place, West Caldwell, NJ 07006 Tel: (201) 575-1300 / Fax: (201) 575-0531 180° Power Dividers Hybrid Junctions Quadrature Couplers Filmbrid Couplers Directional Couplers Bidirectional Couplers Complex Phasing Networks Digital Attenuators Analog Attenuators Balanced Switches Amplifiers & Isolators

Formerly Circuit Busters

Eagleware

Eagleware software integrates network synthesis for the initial design with the flexibility and power of high-speed simulation, tuning and optimization.



The Leader in Quality

We offer a full array of

designs and in-depth

subsystem experience

Smaller SMT DIP Package

Signetics announces the first two integrated circuit products in their new SSOP small-footprint SMT package. The package is small enough to replace chip-andwire assembly in some applications. The NE/SA575DK Compandor and the NE/SA605DK FM IF System are available in the 1.5 × 4.5 × 6.75 mm SSOP. In 100s, these device are priced at \$2.04 and \$3.54, respectively. Signetics Company INFO/CARD #226

GPS Precise Positioning Module

Stanford Telecommunications has received National Security Agency endorsement of its STEL-9300 Precise Positioning Service - Security Module (PPS-SM), allowing authorized users to realize the most accurate capabilities of GPS. Anti-Spoof and Selective Availability techniques deny access to the Precise Positioning Service (PPS) to unauthorized users. With this capability, GPS equipment can provide access to PPS for authorized users without making the equipment classified.

Stanford Telecommunications INFO/CARD #225

Standard Power Amplifier Line

Alpha Industries announces the new CMA Series of Standard Power Amplifiers for terrestrial and satellite microwave communications systems. Models cover 5.9-6.4 GHz with 60 dB linear gain (minimum) and power outputs ranging from 40 to 44 dBm (minimum), utilizing +12 or +15 volt power supplies.

Alpha Industries, Inc. INFO/CARD #224

Power Measurement Upgrade

High speed CW power measurement capabilities have been added to the 8003 Precision Scalar Analyzer from Wavetek Microwave. These new measurement modes provide power readings at greater than 100 per second over GPIB. The upgrade provides a 10 to 100 times improvement in speed over thermocouple CW power meters. This speed is particularly attractive in automated measurement systems.

Wavetek Microwave, Inc. INFO/CARD #223

1000 Watt Amplifier

Model BHE4819-1000 from Power Systems Technology offers 1000 watts CW power output in AB linear service over 400-1000 MHz. RF input is 0 dBm, in CW, AM, Pulse, FM, or phase modulation. Protective circuits prevent damage from excessive VSWR, and the unit offers graceful degradation in the event of transistor failure. Applications include EMI testing, EW and ECM, troposcatter, television broadcasting, and laboratory amplification. Power Systems Technology Inc.

INFO/CARD #222

Video Brickwall Filters

Miniature filters for NTSC and PAL video systems are available from Allen Avionics, offering cut-



off frequencies from 2 to 8.4 MHz. P.C. board or packaged versions are available. The typical ABW-4P20-P has passband flatness of 0.15 dB to 4.2 MHz, less than \pm 10 nsec delay distortion, and 1.066 stopband ratio. These filters reduce interference from high frequency subcarriers and other out-of-band signals. Allen Avionics, Inc. INFO/CARD #221

ECL Oscillators With Enable/Disable

MF Electronics announces the M1900 ECL oscillators for graphics and other high speed circuits requiring clocks of 10 to 225 MHz. A unique feature is a "tristate" enable/disable feature which effectively disconnect the output. System test, selectable clock frequencies, and noise reduction by shutoff of unused sources are all benefits of this feature. MF Electronics Corp.

INFO/CARD #220

Locus Converter and Modulator/ Demodulator Subsystems

Unique solutions for unique requirements

P.O. Box 740

State College, PA 16804 Ultra-High Dynamic Range IF to Baseband Converters and Tuners

custom capabilities based on

extensive library of existing

- Single and Independent-Sideband Modulators
- FSK Modulators
- Coherent and Non-Coherent Demodulators
- Modulation Recognizers
- I-Q Detectors

We're problem solvers. CALL for information or with your questions. (814) 466-6275

See the Locus Difference

LOCUS, Inc.

KAMAN

814-466-6275

FAX 814-466-3341

INFO/CARD 47

Are You Designing for the Following Applications?

- GPS
- Wireless LAN
- Spread Spectrum
- Wireless Key
- Wireless ID
- Wireless P.O.S.

Penstock has the largest inventory of RF/Microwave Semiconductors & Components. Application Assistance is just a phone call away

- Datasheets/Technical Assistance
- Overnight Delivery/No minimums
- FREE Product Selection Guide

CALL 1-800 PENSTOCK

Multipath and Fading Simulator

The new HP 11757B multipath-fading simulator/signature test set features an internal printer, firmware and error counters to produce permanent records of M-curves. These signatures are used in installation and maintenance of digital radio systems. The HP 11757B is \$19,000. and an upgrade to the earlier HP 11757A is \$4000. Hewlett-Packard Co. INFO/CARD #219

MIL-STD-2000 Capability

Bliley Electric announces that it is qualified and certified to design and manufacture soldered electrical and electronic assemblies to meet all requirements of MIL-STD-2000. This capability is used in custom-designed crystal oscillators, and is also available for contract assembly. Bliley Electric Co. INFO/CARD #218

Feedthrough Terminations

tions designed to terminate inputs to oscilloscopes, frequency counters, RF voltmeters, etc., have been introduced by Elcom Systems. They are available in 50, 75 and 93 ohms, with BNC, TNC, type N or SMA connectors. Prices start at \$17.50 in small quantities. Elcom Systems, Inc. INFO/CARD #217



Hybrid Amplifiers

Two new 10 MHz - 1.2 GHz high linearity amplifiers have been introduced by Motorola RF Devices. Models CA5900 and CA5915 are designed for operation in 50 ohm linear systems, offering 28 or 15 volt supply, 15 dB gain, and 1 watt power output at 1 dB compression. Packaging is in the CATV style case 714P-01, and they are also available with a low profile heat sink package. Pricing is \$91.30 (U.S. delivery, 100s).

Motorola RF Devices INFO/CARD #216

3-Way Divider

New three-way power dividers/ combiners are available from RLC Electronics. Featuring 5 watt dissipation and either pin or SMA connector configurations, standard units are offered in octave or narrow band ranges from 500 MHz to 12 GHz. Amplitude balance is ±0.5 dB, phase balance is ±3 degrees, and isolation is 18 dB minimum. Prices start at \$225. RLC Electronics, Inc. INFO/CARD #215

EMI Measuring System

The Vianello PMM-8030 from IBEX Group is a complete emission measuring and monitoring system in the 30 to 1000 MHz band, meeting CISPR, VDE, FCC and EN specifications. External PC control offers ease of use and



flexibility. A complete package is available, including receiver, antennas, computer and software. IBEX Group Inc. INFO/CARD #214

SMT RF Chokes

Vanguard Electronics is offering surface-mount RF chokes designed and built to MIL-C-15305 or MIL-T-27. The chokes are fully encapsulated; suitable for various soldering techniques. Products are available for the 1 to 500 MHz frequency range with impedances up to 10 kohms. 1000piece pricing ranges from \$3.50 to \$4.50 each. Vanguard Electronics Co. INFO/CARD #213

EMC/TEMPEST Antennas

Two new models from Antenna Research Associates are designed for shield room testing requirements of MIL-STD 285 and NSA 65-6. Each antenna is a 12-inch tuned loop operating from 1 kHz to 30 MHz. The PLA-130/A is a two-band transmit/ receive antenna capable of handling 1 kW input power, and the Model ALA-130/A is a receive antenna containing a low noise preamplifier. Each is individually calibrated.

Antenna Research Assoc., Inc. INFO/CARD #212

New SMT Filters

Trilithic has introduced two new surface mount filter packages, which extend center frequencies to the 10-2000 MHz range and increase ultimate rejection to 70 dB. Designs available include Chebyshev, Butterworth, Linear Phase, Bessell, Gaussian and Elliptic with -3 dB bandwidths from 2 to 150 percent.

Trilithic, Inc. INFO/CARD #211

Crystal Products

New products from KS Electronics include a 70.0 MHz VCXO with pullability of over ± 1500 ppm and +10 dBm output. Higher frequencies are also available. Also announced are 70.0 MHz crystal filters with 1.0 MHz bandwidth, with other frequencies available. The company has the capability of manufacturing crystal filters with third order intercept of +30 dBm.

KS Electronics INFO/CARD #210

Matrix Switch

Watkins-Johnson introduces a series of Matrix Switch Distribution Systems offering high performance and reliability. Technology used varies with the frequency range, and may be reed relay, FET or PIN switching. Designs are available for audio (DC-20 kHz), video (DC-20 MHz), HF (1-30 MHz), VHF (20-500 MHz), V/UHF (20-1000 MHz) and IF (narrow bands 80-200 MHz). Control is via front panel, RS-232

RF SHIELD PROTOTYPE KIT!

No tooling costs with standard shields!

27 prototype rf shields to choose from (range: .5" x .5" to 2.5" x 5.0"). Selectable side-wall heights (.25"; .50"; .75"). 54 potential combinations in all. All on two flat 12" x 17" sheets. Shields fold into boxes easily by hand. You get 90° corners every time. All shields are made from .016 brass. They're tin-plated for solderability.





Immediate Delivery!

For your production, you can order any *one* of the 54 sizes in our kit by-the-sheet in large or small quantities. We supply $12^{"} \times 18^{"}$ sheets of .016 thick brass shields with tin plating.

Introductory price only \$14500

Just call, fax or mail your purchase order to:



INFO/CARD 30



THOMSON-CSF

interface, or IEEE-488 bus. Watkins-Johnson Co. INFO/CARD #210

+17 dBm Amplifier

Model TM5150 from Amplifonix offers 19 dB gain, +17 dBm power output at 1 dB compression, and 3.5 dB noise figure over the -55C to +85C temperature range. Package options include 4-pin TO-8, surface mount, and connectorized housings. Amplifonix

INFO/CARD #209

SPDT Switches

Teledyne Microwave announces type CS-53 coaxial switches with faster switching times; 20 msec for failsafe and 10 msec for latching designs. DC to 6 GHz performance specifications include: 1.25:1 maximum VSWR, 0.4 dB maximum insertion loss and minimum 70 dB isolation. To 18 GHz, these specifications are 1.5:1, 0.5 dB and 60 dB, respectively, and from 18-26.5 GHz, they are 1.8:1, 0.7 dB and 50 dB

Teledyne Microwave INFO/CARD #208

Grounding Contacts

The Omni Grounding Series provides a simple means of mounting grounding contacts individually or in series, using pressure sensitive tape or mechanical fasteners. Made from beryl-



lium copper, they compress to 80 percent of their height and allow sliding contact from either end

Tech-Etch, Inc. INFO/CARD #207

ESM Antenna

RF Microsystems has added

the model 216 antenna to their line, a shaped biconical design with a very broad bandwidth, omnidirectional azimuth coverage and vertical polarization. The antenna operates over 0.5 to 18 GHz with a maximum VSWR of 2.5:1 in a 50 ohm system. Weight is one pound, and the size is approximately 5 inch diameter by 5.25 inch height, plus mounting flange.

RF Microsystems Inc. INFO/CARD #206

2 GHz Power FETs

ST5000 and ST5001 from Semetex provide 0.5 and 1.0 watts of class A power with 11.5 and 10 dB gain, respectively, at 2 GHz. Applications include broadband multi carrier, low noise, high intercept amplifiers, medium gain power amplifiers, high level VCOs and high performance receiver front ends. 1-99 unit pricing is \$45.00 for the ST5000 and \$52.00 for the ST5001.

Semetex Corp. INFO/CARD #205

SMT Connectors

Surface mount connectors in SMA and SMB types are available from Applied Engineering Products. Accurate solder seating with no-hole mounting shortens assembly time. Parts tested withstood straight pull of 24 lb., side loads to 40 lb., and radial torque to 16 in -lb.

Applied Engineering Products INFO/CARD #204

Switched Filter Modules

Integrated Microwave offers two, three and four channel modules for frequencies up to 3 GHz. GaAs switching offers 150 ns speed and typical switch loss of 4 dB. Highpass, lowpass, bandpass and band-reject responses are available.

Integrated Microwave INFO/CARD #203

GSM/PCN SAWs

Sawtek has applied low-loss filter techniques for IF filtering requirements of GSM/PCN equip-





Ceramic fixed value capacitors are ideal for communication applications requiring high quality, low values at competitive prices.

For over 40 years Quality Components Inc. has been a major supplier of high quality fixed value capacitors to the OEM electronic communication industry.

Engineers prefer the broad range of low values, close tolerances (± 5%) and values ranging from .1pf to 4.7 pf with increments of .1 pf between each value.

Quality Components' capacitors are ideal for applications such as RF filters, coupling capacitors, bypasses, wave shapers and tuned circuits, requiring high reliability at a competitive price. For detailed information or sample kit contact:



Quality Components Inc.

P.O. Box 113, St. Mary's, PA 15857 TEL. (814) 834-2817 · FAX (814) 834-9141

INFO/CARD 77

54

ment. Center frequencies between 70 and 250 MHz have been demonstrated, with insertion loss of approx. 6 dB. Group delay variation is an excellent 150 nsec. A simple fabrication technique reduces manufacturing costs. Sawtek, Inc. INFO/CARD #202

Multitone Generator

Systematix offers a multitone generator for intermodulation testing, with up to four carriers available, tuned as close as 100 kHz at frequencies of 800-900 MHz or higher. Internal intermod spurs are better than -80 dBc at 45 dBm output. All four tones are independent and front-panel tunable. Modulation and automatic control are optional. Price of the unit is \$19,500

Systematix INFO/CARD #201

BNC Crimp Connectors

Alpha Wire announces their new BNC Crimp Connector, a nickel plated connector with Delrin dielectric and gold-plated center pin. Rapid assembly time and reliable electrical and mechanical contact are major features. The connector is provided in standard 50 ohm impedance. Alpha Wire Corp. INFO/CARD #200

Cell Site Antenna

Model ASP-2892 is a 13 dB gain log periodic array for 60degree sectorized cell sites. The design covers a bandwidth of 800-960 MHz with only a 15 degree vertical beamwidth. Five degrees of beam tilt is built in, with additional tilt available by adjustment of the mounting clamp. Power rating is 500 W and wind velocity rating is 130 MPH. The Antenna Specialists Co. INFO/CARD #199

Solderable Flexible Laminates

Foil-film laminates are offered by Chomerics, to serve as flexible circuits in commercial and military equipment. The laminates can be copper or solder-coated copper, bonded to a variety of dielectric films in continuous rolls



or die-cut pieces. These products are also suitable for grounding and shielding applications. Chomerics, Inc. INFO/CARD #198

Package Seam Welder

The Venus II Parallel Seam Sealer from Polaris adjusts to variations in carrier configurations in electronic packages and package placement. Square or rectangular package sup to 6 inches are sealed by resistance welding or solder reflow. Polaris Electronics Corp. INFO/CARD #197

Coaxial Resonator Oscillators

T and M Microwave offers the CR 1000 series of coaxial resonator oscillators covering the frequency range of 300 MHz to 4.5 GHz. Nominal power output is +13 dBm, harmonics and spurious are specified at -20 dBc and -80 dBc, respectively, and phase noise at 10 kHz offset is -115 dBc. Size for a typical 840 MHz unit is .475 × 1.0 × 1.5 inches. T and M Microwave, Inc. INFO/CARD #196

Arbitrary Waveform Generator

The HI-2009A by Hitronetic has been introduced in the U.S. by Kersaint Associates. The unit synthesizes analog signals with a time resolution of 2.2 nsec per point, two megabytes of signal memory, programming flexibility, and a 450 Mpts/sec sample rate. The price starts at \$40,000. Kersaint Associates

INFO/CARD #195



RFemc corner

Surge and Transient Considerations

By Gary A. Breed Editor

Surges and transients on power and signal lines are major EMC problems in electronic equipment of all types. It is common to see these events occur at magnitudes of thousands of volts, with a considerable amount of total energy. The problem is a particular nuisance at radio frequencies, where even small amounts of energy can interfere with the reception of desired signals. Eliminating, or at least limiting the effects of this unwanted energy usually requires a combination of several standard protection components and circuits.

Surges

Surges are by common definition a low frequency phenomenon, whether they occur on power distribution circuits or signal lines. Intuitively, they can be considered as low frequency modulation of the desired electric or electronic energy normally found on the line. Most signal line surges can be traced to lightning, while power lines are also subject to the inductive kick of machinery or sudden changes in load.

Lightning surges (not direct hits) are usually the result of the discharge path being inductively coupled to a power or telecommunications line. Rural locations are particularly susceptible, since there are long, uninterrupted stretches of distribution lines available for coupling. This type of surge can be very substantial, but is largely dissipated by a combination of spark-gap discharge units and metal-oxide varistors (MOVs). However, equipment must be designed to withstand surges that are below the protection threshold of these devices.

Inductive kick and distribution circuit load changes are somewhat more predictable. Unless they are accompanied by switching transients, they tend to be smooth changes in voltage, with a damped swing of voltage on the line. Their effects are almost always limited to power supply variations. Linear power supplies must be designed to have an adequate raw DC voltage and capacitive storage to remain above the regulator's dropout threshold. Switching supplies



react much like they would to a change in load. If the supply is near its maximum current output capability, the voltage swing of the surge can modulate the regulated output.

Transients and Noise

Variations with very short time duration or with repetitive spikes are called transients, and they come from a large number of sources. In power distribution, they occur when circuits are switched in and out of the power grid, or when nearby lightning results in energy from close coupling or by direct contact of charged ions to the lines. Physical damage causing arcing or shorts contribute to the problem, as well. On signal lines, the potential effects due to lightning are the same as on power lines. AC line filters will remove most of the RF noise conducted by the lines, but

Metallic Surge (across wires): Longitudinal Surge (common mode): Surge Protection Devices: B Leakage Current (tip or ring to ground): On-Hook Impedance (tip or ring to ground): Signal-to-Noise Ratio (voice grade): Signal-to-Noise Ratio (digital loops): Longitudinal-to-Metallic Balance:

radiation from nearby wiring will still be present, unless shielded by conduit.

AC or DC potentials on signal lines can be another source of trouble. DC and ringing voltages are present on telephone circuits, and DC power is present on CATV distribution coaxial cable, as well the RF signals. If a leakage path is present, or if balanced lines become unbalanced with respect to ground, the resulting currents can cause problems with hum pickup from longitudinal currents coupled from AC power distribution circuits. These currents are normally suppressed by the balanced nature of the signal lines.

Outside sources of trouble are common on signal lines. Failed distribution equipment, faulty customer equipment and physical damage are relatively common. The result may not be restricted to disturbances in the desired signals

100 A, 800 V, 10 x 560 msec rise/fall 200A, 1500 V, 10 x 160 msec Breakdown voltage greater than 250 V 10 mA, 1000 VRMS): 100 kohms greater than 30 dB, typical depends on data rate 60 dB minimum

Table 1. Some telephone circuit performance specifications.

and voltages. A broken shield on a coaxial line or unbalance due to inadvertent grounding of one side of a telephone line increases susceptibility to RFI from nearby transmitters. Illegal telephone and CATV connections are notorious culprits for increased RFI because they create mismatch, unbalance or compromise shielding integrity.

Noise in the user's equipment is the result of all the above effects, and more. Other sources of impairment on signal lines include crosstalk, distortion and excess attenuation. Line balance, its physical condition, and the status of transmission equipment all affect overall signal transmission performance. Table 1 shows some key performance specifications for telephone line performance, including surge and overvoltage protection standards, as well as signal path performance.

Protection and Prevention

Transients and noise are insidious problems. They often result in intermittent problems that are extremely difficult to diagnose. Methods of dealing with voltage-current surges and transients include filtering techniques to minimize high-frequency components of the disturbances, along with fuses, spark gap, varistor and zener protection against more dramatic spikes.

Standard practices in the construction of these facilities include separation of signal and power distribution conductors whenever possible, metallic sheathing on telephone trunk lines, periodic grounding to minimize the accumulation of a potential on the shield, and static discharge wires on certain power lines. CATV systems, with a completely shielded system, usually include a ground block with a spark-gap arrestor at the entrance to the customer's location. Telephone lines have fuses in both tip and ring circuits, which may be at a distribution pedestal or at the customer service entrance.

Noise, hum, distortion and interference that appear along with the desired signal require different techniques. Most areas of noise performance are dependent on the condition of the transmission equipment and the transmission medium. Designers of user equipment must be certain that they are compatible with the wire or coax system they utilize, and must allow sufficient design margin to be sure that the transmission medium is the weakest link in the system. Minimizing noise and distortion requires control of signal levels to maintain exactly what is specified for the system used.

Above all, familiarity with system requirements, and the nature of surges, transients and noise helps make a good relationship with the power, telephone and CATV companies. The best service always seems to be given to knowledgeable customers. RF

See the RF Design Awards winners in the July issue!



FILTERS THAT DELIVER WHEN YOU NEED THEM



Custom designs, Fast prototypes, Quantities in stock, Specifications guaranteed.

Lowpass Highpass Bandpass Band reject ■ NTSC & PAL video ■ Medium cut-off ■ Sharp cut-off Delay equalized Delay equalized, sharp cut-off Linear phase Tempest Anti-Aliasing ■ Tubular ■ TO-8 ■ Low profile ■ Subminiature

Call or write for Application Brochures from Allen Avionics and BAL.

224 East Second Street, Mineola, NY 11501



57

Tel: 516-248-8080 Fax: 516-747-6724 INFO/CARD 54 Please see us at the NAB Show, Booth #5751.

RF Design

RF design awards

A Simple Clock and PSK Carrier Recovery Circuit

By Francois Methot RadioSysteme, Inc.

Today, analog designers have to interface with the digital world by recovering the clock from their modem (electric or optic) for high speed data transmission.

The interface between analog and digital is critical, especially when it must be done at a low cost. I propose a different approach to obtain PSK demodulator and clock recovery with the same kind of circuit.

The circuit is based on a PLL with a "D" flip-flop as the phase comparator, coupled with a VCXO to avoid locking on undesired frequencies.

The carrier and/or clock is recovered by using the positive edge of the incoming PSK signal or data stream to sample the carrier or clock and create a DC voltage to control the VCXO. Figure 1 depicts the interconnection between the "D" flip-flop and the VCXO.

However, there is a compromise to be made in using this design. The phase detector does not have a linear transfer



Figure 1. Interconnection between "D" flip-flop and VCXO.



Figure 2. Transfer function from design in Figure 1.

function versus phase error. The gain of the phase detector (K ϕ) in frequency is low but K ϕ for the phase is very high. Figure 2 shows an example of the transfer function of this design.

In the absence of data, the output of the "D" flip-flop can be at a logical "O" or "1" depending where the data did the last sampling in the clock, so the VCXO can be at the maximum or the minimum frequency. When the PLL begins the search for the frequency, it requires many samples to converge on the correct frequency, but the search for the phase is very fast.

For a low bit rate, I recommend the use of a CMOS "D" flip-flop because it has the same threshold for a logical "1" or logical "0". Most of the time a passive filter will do, when it is connected on the Q or Q output, depending if it is the positive edge or negative edge that is required at the center of the data bit.

For a high bit rate, an ECL "D" flip-flop must be used because it has only 1 nsec of propagation delay. However, an active filter (integrator) must be implemented to increase the range on the diode varicap in the VCXO circuit.

This circuit can be implemented to demodulate a PSK signal with some compromise. The carrier must be an exact multiple of the bit rate. Moreover, the phase transition of the carrier must be synchronized with the data. These requirements are cost efficient and easily implemented on the demodulator.

When feasible or when given the choice of IF frequency, the carrier to be modulated must be an exact multiple of



Figure 3. A simple PSK modulator.

the data clock to be transmitted. A simple PLL can multiply the clock synchronously and form the carrier to be modulated. Figure 3 shows an example of a simple PSK modulator. Now the PSK carrier can be seen as a data stream of "1", "0", "1" ..., with one extra "0" or one extra "1" at each transition of the data. Refer to Figure 4 for the timing diagram.

A carrier can be regenerated at twice the PSK carrier frequency with the same circuit for the clock recovery and later, by dividing the carrier by two. A simple exclusive "or" can demodulate the PSK signal. Because of the use of the divider, there exists a phase ambiguity of 180 degrees. By using a differential code or NRZI encoding, the demodulated data will always be the same polarity.

In Figure 5, one ECL IC is used for limiting the PSK signal, another IC has the phase comparator and the frequency divider, and a final IC to demodulate the PSK signal and produce the VCXO. An NRZI to NRZ must be added after the low pass filter. This technique, compared to the conventional approach, requires no treatment on the signal (X^2) to rebuild the carrier information.

The component values of the integrator were calculated using Communica-



Figure 4. Timing diagram (a) the PSK signal can be seen as a data stream of 1, 0, 1, ... with one extra 0 or 1 at each transition of the data, (b) a carrier can be regenerated at twice the PSK carrier with a simple clock recovery and when it is divided by two, can demodulate the PSK signal.



Figure 5. PSK demodulator circuit.

tions Consultion Corporation's (now Compact Software) PLL Design Kit.

Figure 6 shows my RF Design Contest entry: clock recovery based on "D" flip-flop phase detector. Figures 7 and 8 show the performance of the circuit's clock and data recovery.

Conclusion

The circuit shown in Figure 6 uses only one IC to both perform the phase comparator and sample the data. The VCXO was made with a crystal in fundamental at 139.264 MHz to eliminate frequency multiplication and achieve a larger range. A Δ F of 50 kHz was obtained with ±15 kHz of capture range. The data stream comes from the optical detector from a source at -25



Figure 7. Spectrum analyzer display of the recovered clock signal. dBm. The clock recover still locks up to -31 dBm even if the data is at 10^{-2} of error rate. For the PLL, the parameters are: $W_n = 10$ kHz, $K_{vco} = 1$ kHz/volt, $K_o = 10$ volts/radian, $\xi = 0.7$.

About the Author





Figure 8. Digital oscilloscope display of clock and recovered data.



Figure 6. Clock recovery based on "D" flip-flop phase detector.

At last, an affordable PIN DIODE TUNED HOPPING FILTER!

Useful whenever you need a tunable narrowband filter..... Or when you just need a filter you can set to a particular frequency... For testing, breadboards, or as a system component.

OUTSTANDING FEATURES

- 2 MHz to 1 GHz
- 10 μS tune time
- 1 Watt power handling
- +40 dBm IP₃ great for wide dynamic range receiver preselection
- 251 tune positions with internal decoding and drivers
- Less than 2 in³ world's smallest digitally tuned RF filters



4480 LAKE FOREST DRIVE CINCINNATI, OHIO 45242 PHONE / 513 563-1133 INFO/GARD 55

EPSON THE CRYSTAL MASTER*

leads new crystal oscillator technologies into the 90's with...

the most cost effective hi-temp SMD crystals and oscillators and low cost plastic thru-hole crystal oscillators.

EPSON SURFACE MOUNT CRYSTALS AND OSCILLATORS

Epson has pioneered the first truly heat resistant crystal for

use in its surface mount crystals and crystal oscillators. Capable of withstanding 260°C for 20 seconds...far above the demands of standard IR and vapor phase reflow processing systems...these laborsaving high-temp SMD crystals have become the accepted standard for surface mount crystal and oscillator components.

 MODEL SG-615 OSCILLATOR

 Frequency:
 1.5 to 66.7 MHz

 Symmetry:
 45/55 (TYP)

 Rise/Fail Time:
 5 nsec (TYP)

 Tristate:
 Available

 Compatible

 Technology:
 CMOS and TTL

 Op. Temp. Range:
 -40°C to 85°C

MODEL MA 505/506 CRYSTAL Frequency: 4.00 to 66.7 MHz MODEL MC-405 CRYSTAL Frequency: 32.768 KHz

actual size



EPSON THRU-HOLE OSCILLATORS REPLACE METAL CAN OSCILLATORS



MODEL SG-51/SG-531 Si OSCILLATOR Ri

 Frequency:
 1.5 to 66.7 MHz

 Symmetry:
 45/55 (TYP)

 Rise/Fall Time:
 5 nsec (TYP)

 Tristate:
 Available

 Compatible Technology:
 CMOS and TTL

EPSON EPSON AMERICA, INC. Composent Sales Department Tellephone: 213/787-87

CALL YOUR SALES REP TODAY

SON Sales Representatives: AL-GA-TN Concord Components 205/772-8883 · AZ-NM Fred Board Assoc. 602/994-9388 · CA-No. Costar 408/446-9339 · CA-So. Bager Electronics 714/957-338 - UT Wn. Region Mktg. 303/428-8088 · FL Dyne-A-Mark 407/831-2822 · IL-WI LTD Technologies 708/773-2900 · IN-KY C C Electro 317/921-5000 · KS-MO-IA Microtronics 913/262-1444 · MA-NH sen Assoc. 617/449-4700 · MD-YA Tech Sales Assoc. 301/461-7802 · MN Electro Mark 612/944-5850 · NC-SC WLA Assoc. 919/231-9939 ·NJ JMR Sales 201/525-8000 · NY Elcom Sales 716/385-1 Hetro, NY Niktronix 516/929-4671 · DH-MI J. D. Babb Assoc. 216/934-4454 · OR-WA Matrex 503/245-8080 · PA Omega Sales 215/244-4000 · TX-OK Component Tech. 214/783-8831

RF oscillators

WHF and UHF Crystal Oscillators — Part II

By Andrzej B. Przedpelski A.R.F. Products, Inc.

This note contains some theory, more circuits, some suggestions and further considerations of 5th, 7th, and 9th overtone crystal oscillators (up to 630 MHz) using simple easy to build circuits.

should have started Part I, July of 1990 (1), with some applicable theory, but I got carried away by the ease of constructing and adjusting these high frequency crystal oscillators and their reliable performance. To rectify this omission let's consider the requirements for an oscillator. Barkhausen tells us that for a circuit to oscillate, two conditions have to exist.

- the open loop gain (A() x () of Figure
- 2) has to be more than unity, and

• the phase of this gain has to be 360n, where n is an integer (including 0).

In the circuits described, the gain, A() is supplied by the MMIC amplifier and the feedback, () consists of the crystal, in series with a length of transmission line, and the capacitor(s). Using an ideal non-inverting amplifier (such as Figure 1a) (1), the feedback can have 0 degrees phase shift and no phase shifting network is thus necessary. The crystal can, theoretically, operate in series resonance (presenting only a resistance in the feedback path) and becomes an attenuator in conjunction with the 50 ohm input impedance of the MMIC amplifier. If this attenuation is lower than the gain of the amplifier, the circuit will oscillate. The oscillations start slowly (relatively speaking) by amplifying circuit noise at the resonant frequency until the amplifier saturates (gain of the amplifier becomes equal to the feedback attenuation).

In the inverting amplifier configuration (such as Figure 1b) (1), the feedback has to provide the (theoretically) required 180 degree phase shift to allow oscillations to take place.

In practice, of course, the non-inverting amplifier has some phase shift at the operating frequency, and the inverting amplifier phase shift is usually somewhat less than 180 degrees. Thus, the feedback circuit has to compensate for these small phase shift discrepancies.

The inverting amplifier oscillator configurations are generally preferred, since they have less tendency to oscillate at undesired frequencies. Any "simple" undesired feedback usually does not have the required 180 degree phase shift.

To provide the needed feedback phase shift, different methods can be used. The crystal itself can provide some phase shift. However, it is better to use it in a series resonance mode to reduce losses through the crystal. Thus, a phase shifting network providing almost 180 degree phase shift has to be used. At lower frequencies, a pi or tee phase shifter can be used. However, at the higher frequencies, accurate inductors



Figure 1. Figures from Part I: (a) third overtone circuit, (b) 350 MHz fifth overtone, (c) overtone oscillator with L/C phase shift, (d) approximate crystal equivalent circuit at fifth overtone.

are difficult to construct, and spurious reactances cause additional uncontrolled phase shifts. To overcome this, and to provide very simple implementation of reliable circuits, a transmission line can be used to provide the main required feedback phase shift. This approach is feasible at the higher frequencies and provides easily reproducible phase shifts. To demonstrate this, the circuit shown in Figure 3 was built. While feasible and very simple it was not considered very practical since the length of the transmission line was difficult to optimize. A more feasible method using variable capacitors to fine-adjust the feedback phase shift was used in the more practical circuits. This method had the additional advantage of allowing some "pulling" of the oscillator frequency.

Now back to some more circuits

Circuit # 1 (350 MHz fifth overtone)

The circuits presented in Part I used hybrid type RF amplifiers. To reduce size still more and allow the use of surface mounted components, monolithic RF amplifiers were then tried. A typical inverting type was used (Avantek MSA-0735). Two possible circuit configurations were tried (Figures 4 and 5). Both gave an output of 6-8 dBm with either a 3.6 inch or 6 inch length of transmission line. The capacitors had to be retuned, of course. The circuit of Figure 5 seemed to have lower harmonic content (35-40 dB below fundamental for second and third harmonics). While monolithic amplifiers usually have the disadvantage of requiring input and output capacitors, one capacitor can be omitted, since the crystal provides DC isolation. These amplifiers also require a biasing resistor. In the case of the circuits shown, this was actually taken advantage of to provide a circuit which worked reliably directly from an airborne power source of 22-30 VDC. This was accomplished by the use of the high value (1000 ohm) biasing resistor.

Circuit # 2 (490 MHz seventh overtone)

The basic circuit of Figure 5 could be easily modified to provide reliable operation on the seventh overtone of the crystal. The same crystal was used with an 8.2 or 7.2 inch length of transmission line, as shown in Figure 6. An output of 6-8 dBm was obtained, but the harmonic content was high (-10 to -15 dB). Otherwise, the circuit performed reliably.

Comments

Output was always observed on a spectrum analyzer to ensure that the proper overtone operation was obtained. Power output was measured at the desired output frequency.

All circuits were checked to ensure



Precision quartz crystals in solder seal, resistance weld, and coldweld configurations and oscillators with low aging and low phase noise characteristics.

and oscillators that will perform in such critical applications.

EG&G's high reliability standards include compliance with WS6536E. Our continuous quality assurance from raw quartz to finished product



helps maintain that level of excellence. Computerized production control enables us to provide you with shortened lead time delivery. EG&G also supplies custom-designed high per-

formance crystal and LC filters, discriminators, modules and atomic frequency standards making us a single qualified source for all your frequency control needs. Call or write today for more information on precision products that perform under pressure.

In-house experts working in state-of-the-art facilities broduce highly stable TCXOs, VCXOs and OCXOs for precise control of frequency.



A(w) BCu

Figure 2. Oscillator equivalent circuit.

that no mode switching could be induced. DC power was turned on instantaneously or was brought up gradually while output was observed on the spectrum analyzer. The oscillators always started at the desired frequency.

50 ohm coaxial transmission lines were used, since they are readily available and easily changed. Once the circuit is finalized, the transmission line can be part of the PC board. There is no apparent reason why other impedances cannot be used. However, only 50 ohm coax cables were used.

An amplifier gain of about 12 dB at the desired frequency seems adequate. Higher gain amplifiers would allow a higher loss in the feedback circuit. This could reduce the crystal drive and improve stability. However, too much gain may make the circuit more susceptible to oscillations at undesired frequencies.

The phase shift in the amplifier changes with frequency. The typical inverting amplifier actually becomes noninverting at higher frequencies. This occurs at about 4.5 GHz for the MSA-0735 used in the tests. The amplifier still has gain at this frequency, however, and this should be considered.

The crystal resistance does not seem to be critical. The crystal used had a resistance of about 140 ohms at the fifth harmonic (Figure 10). Higher resistance crystals can be used, if the amplifier gain is adequate.

The feedback path loss has to be less than the amplifier gain to sustain oscillations. The input impedance to the feedback path should be higher than 50 ohms to allow most of the amplifier power output to appear as useful power in the load. This is not unreasonable, since the feedback path can have appreciable insertion loss.

A quick temperature check was made using the circuit of Figure 5. The frequency vs. temperature curve was smooth and no mode jumping was observed.

The circuits were very reproducible.

EG&G Frequency Products, Inc. 4914 Gray Road, Cincinnati, Ohio 45232 FAX 513-542-5146, PHONE 513-542-5555

INFO/CARD 57

EGEG FREQUENCY PRODUCTS, INC.

Imagine A Single Source For Every Frequency Control Need...

Now Imagine What That Source Can Do For You.

With CTS, you can specify from one of the broadest lines of frequency control products available anywhere—crystals, clock oscillators, VCXO's, TCXO's and ovenized oscillators. If a standard product won't do, our engineers will design one that meets the requirements of your application. But there are more reasons for making CTS your single source for frequency control products.

Our cutting-edge technology assures you of the most advanced frequency control products. The in-house production of crystals, precision designs and strict quality control give you an added margin of reliability. Additionally, our technical support teams provide a problem solving capability that can be a real asset for your design and engineering teams.

Get the product your application requires, plus technical services and reliability proven in the most demanding military, instrumentation, telecommunication and data processing applications. All from a single source. Call now for the name of your CTS Sales Representative.



Around The World, Your Single Source For Excellence[™]

CTS Frequency Control Division, 400 Reimann Ave., Sandwich, IL 60548, Tel: 815/786-8411, Fax: 815/786-9743

THE INDUSTRY'S

MOST WANTED

TCXO

The latest TCXO from STC

DESCRIPTION:

- 0.2 cubic inches 1" × 1" × 0.2" high
- Mil grade available
- Surface mountable
- Custom configurable leads

MODE OF OPERATION:

- Low phase noise
- Frequencies up to 350 mhz
- Low power consumption
- Highly stable, precision performance

Analog Chip Temperature Compensation Technology

Buy one or borrow one.

Call us for technical literature and complete details on our unique offer.

STC COMPONENTS, INC., 636 REMINGTON ROAD, SCHAUMBURG, IL 60173 1.800.624.6491 • 708.490.7150 • FAX 708.490.9707 • CANADA: 1.800.624.6494 UK: 0279.626626





Figure 3. The simplest circuit.

The same circuit was built using direct interconnections (no chassis), using a ground plane or a PC board with all surface mount components. The performance was essentially the same.

Increasing feedback loss (reducing drive to the amplifier) reduces harmonic content (as expected). This reduces power output somewhat. For a power output reduction of 1-2 dB, the harmonic content can be reduced by 15-25 dB.

The initial tuning procedure is quite simple. Using a spectrum analyzer (to make sure that the right overtone operation is achieved) set one capacitor and tune the other (if two are used). If proper operation is not obtained, retune the first capacitor and repeat tuning with the other. Once the proper frequency is obtained, the output can be maximized using both capacitors.

The crystal can oscillate at the fundamental or an odd overtone. Circuit #10 (Figure 1c) (1), for instance could be made to oscillate at the third, fifth and seventh overtone by retuning the two capacitors. At these different frequen-



Figure 4. 350 MHz fifth overtone oscillator.

cies, the phase shift through the amplifier is different. While at very low frequencies it is the theoretical 180 degrees, it decreases with frequency. The crystal also looks different at these frequencies. Mr. David Smith of Innovative Frequency Control Products, Inc. kindly supplied typical equivalent circuit values for the crystal used (see Figure 1d) (1). Series R is about the same for the overtones, but is about 1/6 this value for the fundamental operation. The motional inductance (series L) is about the same for the fundamental and overtones. The motional capacitance varies to provide the proper series resonance.

While operation only up to the 9th overtone (630 MHz) was confirmed, there were indications that the 11th overtone was also feasible. The transmission line length became very short and was difficult to optimize. However sporadic operation at 730 MHz was obtained using the Figure 3 circuit and a transmission length of about 0.5 inch. As results of Figure 3 indicate, there is some spurious phase shift caused by



Figure 5. 350 MHz fifth overtone oscillator.

NEW NAME! The Block Diagram Simulator you knew as TESS is now:



TESLA has all of the great features that classic TESS had like:

- Fast RF Time Simulation
- Mixed Analog & Digital
- Spectrum Analysis
- Input with OrCAD & PCAD

• Free support & BBS (1yr) <u>Plus</u> TESLA has the powerful new goodies added in version 1.1:

- 24 new filters
- Amp and mixer models with intercept specs
- Hi-res graphics output to lasers, plotters, printers and wordprocessors
- Quantizer, Integ&Dump, Laplace and resp models
- Lots more space for useradded models—fill it up from the free BBS.
- Run OrCAD and PCAD without leaving TESLA
- Many new power-features

STILL ONLY \$695!

30-day Moneyback Guarantee! CALL FOR DEMO DISK

T E S O F T PO Box 305 Roswell GA 30077 404-751-9785 FAX404-664-5817

INFO/CARD 60

RF Design

1111	5-		ITEM NUMBER EDITION		DOMESTIC PRICE	OUTSIDE USA AIRMAIL
	1	RF EXPO PROCE	EDINGS		22	
	62		1986W RF Techn 1986E RF Expo 1987W RF Techn 1987E RF Expo 1988W RF Techn 1988W RF Techn 1989W RF Techn 1989W RF Techn 1989W RF Techn 1989E RF Techn 1989E RF Expo 1990W RF Techn 1990E RF Expo	ology Expo 86 East 86 ology Expo 87 East 87 ology Expo 88 ology Expo 89 East 89 ology Expo 90 East 90	\$ 145.00 145.00 145.00 145.00 145.00 145.00 145.00 145.00 145.00	• Add \$30.00 to total order for shipping.
			1991 Set - 10		. 145.00 .	• •
	- /	OSCILLATOR HA	NDBOOKS			
Q			3190 1990 Oso	cillator Design	. \$ 28.00 .	\$31.00
5		FILTER HANDBOO	OKS			
R	>		3211 1991 Filte 3212 1991 Filte 3200 Set - 2	er Applications Vol. 1 er Design Vol. 2 volume	. \$ 28.00 . 28.00 . 50.00 .	\$31.00 31.00 55.00
00	10C		TO ORDER: Fill out of desired PAYM	order form; indicating and price. Shipping IENT MUST ACCOMPA	item numb charges are NY ORDER.	er, quantity e included.
5			ITEM	QUANTITY	PRICE	
					\$	
A	$\neq \vee$	A CONTRACTOR			ED 0	
X	100	and the second		IOTAL ENGLOS	S	5 2 3 3
×.		1	Payment enclose Charge my orde	ed (check or money o er to: Visa Mast	order) erCard 🗆 A	merican Exp
	A LANGER BERNELL	ELT INLAS	Account Number			
			Signature	at Planetaria	104	
M		A AVIENCE	Expiration date		/	******
	A Sel March		Name	C. C		
	A THE REAL PROPERTY AND		Title	1 11 1 1 1		
			Company			
			Address	Mail Sto	op q	
		is and the s	Coupt	7. m th 4 "	Code	-
			My check or mor	ey order is made po Cardiff Publishin 5300 S Syracuse Way Englewood, CO 80	g (; #650 111	dollars to RFD 5/91
				6300 S Syracuse Way Englewood, CO 80	7, #650 0111	RFD 5/



Figure 6. 490 MHz seventh overtone oscillator.

the stray inductances and capacitances in the circuit. With the breadboard used it was also somewhat difficult to accommodate the very short transmission line lengths. A better layout may make the 11th overtone operation quite feasible.

Another problem at the higher overtones is the stray pin-to-pin crystal capacity. While small (about 2 pF) its reactance at the higher frequencies becomes comparable or smaller than the crystal resistance. It may then provide the necessary feedback path to sustain oscillation at the wrong frequency. No effort was made to "tuneout" this reactance, as is sometimes done at lower frequencies to obtain true series resonant operation and to reduce the risk of spurious oscillations.

While the above treatment of UHF crystal oscillators is by no means complete, the main effort was directed toward the simplest low cost reproducible designs using non-critical components. It was also meant as a starting point for further investigations using this general overall approach. The noninverting amplifier circuits were also not adequately explored. One reason was that only one device was available at the time of the test; several manufacturers make suitable low cost inverting types.

References

1. Andrej B. Przedpelski, "VHF and UHF Crystal Oscillators," *RF Design*, July 1990, pp. 63-65.

About the Author

Andrej B. Przedpelski is the consulting editor for *RF Design* and vice president of development for A.R.F. Products, Inc., 7260 Terrace Place, Boulder, CO 80303. Tel: (303) 443-4844.



HIGH ENERGY CORP



BLILEY ELECTRIC COMPANY IS CERTIFIED FOR MIL-STD-2000 ON SOLDERED ELECTRICAL AND ELECTRONIC ASSEMBLIES

RF featured technology

Design of Quadrature Detectors

by Edward A. Richley Xerox Palo Alto Research Center

The quadrature detector is a very common circuit used for the demodulation of both wide band and narrowband FM. However, there is a general misconception about its method of operation, and little information on its proper design. After careful analysis, it can be seen that the engineering trade-offs involved in the design of a quadrature network are easy to understand and very interesting. This article will describe such an analysis, and will show the important considerations for proper design.

The basic single-tuned quadrature detector network is shown in Figure 1. This network is typically used with FM receiver ICs such as the Motorola MC3357 (and related parts), Signetics NE604, or the RCA CA3189. The network has one input and one output. The input generally comes from the output of a limiting IF strip. This input, V_{IN} and the output of the network, V_{OUT} , are connected to the inputs of an analog multiplier. The basic purpose of the quadrature network is to produce

The basic purpose of the quadrature network is to produce two signals which have a nominal phase difference of 90 degrees (hence the term "quadrature detector"), but with a variation in phase which depends on instantaneous frequency. The multiplier then serves as a phase detector, and can detect the lead or lag in phase caused by the interaction of the frequency modulated signal with the network.

In some versions of the circuit, the coupling capacitor, C_1 of Figure 1, is replaced by an inductor. The operation of the circuit is conceptually the same in both cases. Many texts give an explanation for the operation of this circuit which is based on the following assumption (1,2):

$$X_{1}(\omega_{0}) >> R_{L}$$
⁽¹⁾

where X₁ is the magnitude of the reactance of the coupling component, either a capacitor or an inductor, and ω_0 is the center frequency of the frequency modulated signal. ω_0 is also the resonant frequency of the network formed by L_L and C_L. With the assumption of equation 1, the nominal 90 degree phase shift is provided by the reactance of X₁ in series with a much smaller resistance, R_L. The subsequent phase lag or lead about the nominal will result from changes in the received signal frequency which cause the reactance of the R-L-C circuit to swing inductive or capacitive.

A quick look at some application notes, however, shows that the condition of equation 1 is often not met in practice. In fact, it is often strongly violated (3,4). Thus, the question arises as to how the nominal 90 degree phase shift is provided, and how the phase shift varies with frequency. In order to address this point of confusion, the network of Figure 1 must be examined more closely.

It is instructive to look at the network of Figure 1 in an alternate form. The dashed portion of Figure 2 can be transformed into a Norton equivalent, as shown in Figure 3. The resultant parallel capacitors combine as a single element of value ($C_1 + C_L$). From Figure 3, it is evident that the nominal 90 degree phase shift can be guaranteed at the frequency ω_0 by simply making the combination of L_L and $C_L + C_1$ resonant

at ω_0 . Thus, the condition of equation 1 is not necessary. The size of C₁ relative to C_L does not affect the phase characteristics of the circuit at all, since the two capacitors are effectively in parallel. Their relative sizes only affect the amplitude of the output, and, as shall be seen later, the input impedance of the network. Thus, the condition of equation 1 is not necessary at all.

The Transfer Function

The circuit of Figure 1 has a transfer function, $H(j\omega)$, defined as the ratio of the output voltage to the input voltage, when both are expressed in phasor notation:

$$H(j\omega) = \frac{V_{OUT}(j\omega)}{V_{IN}(j\omega)}$$
(2)

From the equivalent circuit of Figure 3, it is easy to show that $H(j\omega)$ is determined by the impedance of the R-L-C circuit, and is given by:

$$H(j\omega) = -\frac{\omega^2 C_1 L_L R_L}{R_1 (1 - \omega^2 L_1 (C_1 + C_1)) + j\omega L_1}$$

There are four main concerns regarding the design of the quadrature network. These are as follows:

1. $|H(j\omega_0)|$ should be as large as possible.

2. The variation in $|H(j\omega)|$ over the desired range of frequency deviation should be as low as possible.

3. The phase variation in $H(j\omega)$ over the desired range of frequency deviation should be as linear as possible.

4. The input impedance of the network must be sufficient so as to not load the driving circuit.

In order to simplify the investigation of each of these requirements, it is useful to define some quantities. The first of these is the loaded Q of the network:

$$Q = \frac{H_L}{\omega_0 L_1}$$
(4)

In this analysis, any load resistance due to the phase detector input is lumped into the resistance R_L .



Figure 1. Basic single tuned quadrature detector network.

(3)

Another useful quantity is the center frequency, ω_0 . As described earlier, component values are chosen for resonance at ω_0 , so that:

$$\omega_0^2 = \frac{1}{L_L(C_1 + C_L)}$$
(5)

Finally, the frequency, ω , can be normalized to ω_0 by defining a new quantity, γ , as follows:

$$\gamma = \frac{\omega}{\omega_0} \tag{6}$$

In terms of these quantities, the transfer function is given by:

$$H(j\omega) = -\frac{C_1}{C_1 + C_L} \frac{\gamma^2 Q}{(1 - \gamma^2)Q + j\gamma}$$
(7)

From equation 7 it follows that the magnitude of the transfer function at the center frequency ($\gamma = 1$) is given by:

$$|H(j\omega_{0})| = \frac{C_{1}Q}{C_{1} + C_{L}}$$
(8)

From equation 8 it is clear that for greatest magnitude of $H(j\omega_0)$, both Q and C₁ should be as large as possible. However, once C₁ is made comparable to C_L there is not much to be gained from increasing it further.

It is also useful to define the normalized frequency, γ , in terms of the deviation, ξ :

$$y = 1 + \xi \tag{9}$$

In terms of ξ , the transfer function is :

$$H(j\omega) = -\frac{C_1}{C_1 + C_L} Q \frac{(1 + \xi)^2}{(-\xi(2 + \xi))Q + j(1 + \xi)}$$
(10)

The Amplitude Response

In order to examine the flatness of the amplitude response with frequency, it is helpful to look at the magnitude squared of the transfer function:

$$|\mathbf{H}(\mathbf{j}\omega)|^2 = \left(\frac{C_1}{C_1 + C_L}\right)^2 \mathbf{Q}^2 \frac{(1+\xi)^4}{\mathbf{Q}^2 \xi^2 (2+\xi)^2 + (1+\xi)^2}$$
(11)

This expression can be expanded in terms of ξ about the center frequency, $\xi = 0$:

$$|H(j\omega)|^{2} = \left(\frac{C_{1}}{C_{1} + C_{L}}\right)^{2} Q^{2}(1 + 2\xi + (1 - 4Q^{2})\xi^{2} + ...)$$
(12)



Figure 2. The quadrature network redrawn.

From equation 12 it is clear that in order to prevent AM distortion from becoming induced on the detector, it is necessary that:

$$|\xi| << \frac{1}{2} \tag{13}$$

and that:

$$4Q^2|\xi|^2 << 1 \tag{14}$$

In general, $|\gamma|$ is quite small (0.01 is typical) so that both of these requirements will be met for modest values of Q.

The Phase Response

The phase response can be examined in a similar manner. Equation 10 leads to the following expression for ϕ , the phase of the transfer function, $H(j\omega)$:

$$\phi = \arctan\left(\frac{(1+\xi)}{\xi(2+\xi)Q}\right) \tag{15}$$

Since the nominal value of ϕ is known to be 90 degrees ($\pi/2$), it is most useful to look at the deviation in ϕ about this mean. This deviation, θ , is given by:

$$\theta = \phi - \frac{\pi}{2} = -\arctan\left(\frac{\xi(2+\xi)Q}{(1+\xi)}\right)$$
(16)

The linearity of the phase response of the network can be evaluated by looking at the quantity $\partial \theta / \partial \xi$. From equation 16, it follows that:

$$\frac{\partial \theta}{\partial \xi} = -Q \frac{2 + 2\xi + \xi^2}{1 + 2\xi + (4Q^2 + 1)\xi^2 + 4Q^2\xi^3 + Q^2\xi^4}$$
(17)

This expression can be expanded in terms of ξ to give:

$$\frac{\partial \theta}{\partial \xi} = -2Q(1 - \xi + \frac{1}{2}(3 - 8Q^2)\xi^2 + \dots)$$
(18)

In order to maintain a linear phase response, it is important for the constant term in equation 18 to be the dominant term. Thus, the requirement for phase linearity can be expressed as follows:

and

$$4Q^2|\xi|^2 << 1$$
 (20)

These requirements can be seen to be almost identical to the requirements of equations 13 and 14.



Figure 3. Norton equivalent of the quadrature network.

RF Design

The Input Impedance

The remaining requirement has to do with the input impedance of the network. The magnitude of the impedance of the network of Figure 1, at the center frequency, ω_0 , as seen by V_{IN} , is:

$$|Z_{\rm IN}(\omega_0)| = \omega_0 L_{\rm L} \frac{\sqrt{Q^2 + \left(\frac{C_1 + C_{\rm L}}{C_1}\right)^2}}{1 + Q^2 \left(\frac{C_1}{C_1 + C_{\rm L}}\right)^2}$$
(21)

For even modest values of Q, and for values of C, which approach C_{L} (which is encouraged from equation 8), $|Z_{IN}(\omega_{0})|$ approaches the following form:

$$|\mathsf{Z}_{\mathsf{IN}}(\omega_0)| \to \frac{\omega_0 \mathsf{L}_{\mathsf{L}}}{\mathsf{Q}}$$
(22)

Clearly, a large enough value of Q and a small enough value of L_{L} could lead to an input impedance which is too low to be driven from the IF output. This consideration places a limit on the size of Q or the size of C, relative to C_L.

Design Procedure

Consideration of all of these constraints leads to a reasonable approach to the design of these single tuned quadrature networks. As with most engineering problems, there are trade-offs to be made. In general, the following procedure should suffice:

1. Choose frequency deviation or center frequency such that $|\xi| << 1/2$.

2. Choose Q as large as possible, without violating the requirement: $4Q^2 |\xi|^2 << 1$.

3. Choose the largest value for L_L which can be obtained within the limits of physical size, self-resonance, and the effects of its unloaded quality factor on Q.

4. If $(\omega_0 L_L/Q)$ is an acceptable value for input impedance, choose a value for C₁ which about is half the capacitance needed for resonance with L_L at ω_0 . Let C_L be the remaining capacitance needed for resonance.

5. If $(\omega_0 L_L/Q)$ is not acceptable, choose a value for C_1 which provides an acceptable value for $|Z_{1N}(\omega_0)|$, from equation 21. Choose a value for C_L which completes the requirement for resonance with L_L at ω_0 (equation 5).

This procedure should work well for most designs. It will provide the largest possible output level without sacrificing other parameters. Equations 8, 9, 12, 18, and 21 provide some quantitative insight into the behavior of signal tuned quadrature detectors. Although this analysis has been carried out for



Figure 4. The double tuned quadrature network.

capacitive coupling, it must be emphasized that a similar exercise could be performed for a circuit using an inductor in place of C_1 .

The Double Tuned Quadrature Detector

There is a higher performance version of the quadrature network which is often described in application notes (4,5). This is the double-tuned network which is shown in Figure 4. Much better linearity is claimed for this network.

This network uses a weakly coupled transformer having a tuned primary and a tuned secondary. In most implementations, both windings are identical. In Figure 4, both windings are shown to have an inductance, L. The amount of mutual inductance, M, is always a fraction of L. Thus:

$$M = kL, \qquad k < 1 \tag{23}$$

where k is known as the coupling coefficient.

Instructions in various application notes indicate that the coupling coefficient, k, should be at least 70 percent of critical coupling, k_{cr} , where k_{cr} is defined in terms of the primary Q, Q_p , and the secondary Q, Q_s , as follows:

$$k_{\rm cr} = \frac{1}{\sqrt{-Q_{\rm p}Q_{\rm s}}}$$
(24)

Instructions also indicate that the primary is to be tuned for maximum signal, while the secondary is to be tuned for maximum linearity.

An analysis of the double tuned network will now be presented. This analysis will focus on the phase response of the network, as that is the important advantage of a double tuned network when compared with the single tuned network. An analysis of the amplitude response and the input impedance can be derived easily from this phase response analysis, and so will not be presented.

Some Approximations

| | <<

The double tuned network is significantly more complicated and difficult to analyze than the single tuned network. Consequently, some assumptions and approximations will be used. These approximations are extremely plausible and serve to greatly enhance the understanding of the analysis. In fact, the analysis of the single tuned network would be greatly simplified by these approximations and would yield exactly the same result as equation 20.

The first assumption is simply that the maximum frequency deviation is very small. Thus, it is assumed that:

In comparison with terms of order 1, ξ can be ignored. Of course, one must be very careful to not ignore ξ when subtraction of large numbers will result in a term of the order ξ .



Figure 5. Equivalent of the double tuned quadrature network.

(25)

70



Figure 6. Approximation of the double tuned quadrature network.

Furthermore, it is assumed that the Q of both primary and secondary are large:

$$Q_s >> 1$$
, $Q_p >> 1$ (26)

From these assumptions, and the definition of $\mathbf{k}_{\rm cr}$, it is clear that:

Equivalent Circuit

An equivalent circuit can be made for the double tuned network of Figure 4. This is shown in Figure 5. This equivalent will yield exactly the same output as the original circuit. The transfer function is determined once again by the input impedance of this network.

Only an analysis of the phase response of the double tuned network will be given here. Clearly the variation in the phase of the transfer function, about the 90 degree point, is given by the phase of the input impedance of the network. Just as with the single tuned network, the coupling element provides the initial 90 degrees of phase shift while the tuned network provides the deviation. Thus, the phase of interest is simply the phase of the input impedance.

Figure 6 shows this input impedance as Z, with the impedance of all elements normalized to $\omega_0 L$. Simplification is provided by the use of equation 27. This simplified approximate network clearly consists of two networks in parallel. Figure 7 shows these two networks distinctly. Clearly, the admittance of the combined network Y, is simply the sum of the two admittances, Y₁ and Y₂. The admittance, Y, is just as useful for determining the phase response of the network as the impedance, Z, because Y and Z are reciprocals of each other. Thus, the variation component of phase response is simply the negative of the phase of Y.

Using equation 25, it is easy to show that, to a very good approximation sufficiently close to the center frequency, the admittance, Y_1 , is given by:

$$Y_1 = \frac{1}{Q_p} + 2j\xi$$
 (28)

Similarly, the admittance, Y₂, can be well approximated by:

$$Y_{2} = k \frac{1 + 2jQ_{s}\xi}{Q_{c}(k - 2\xi) + j}$$
(29)

These forms for the admittances, Y_1 and Y_2 , assume that the tuned circuits of Figure 7 are tuned for resonance at $\xi = 0$. This is not necessarily the case. In fact, some degree of mistuning will yield the desired results. This mistuning can be represented by replacing ξ with $(\xi - \xi_1)$ in equation 28 and $(\xi - \xi_2)$ in equation 29. Thus, the total admittance, Y, is given by:

$$Y = \frac{1}{Q_{p}} + 2j(\xi - \xi_{1}) + k \frac{1 + 2jQ_{s}(\xi - \xi_{2})}{Q_{s}(k - 2(\xi - \xi_{2})) + j}$$
(30)

This detuning accounts for several effects. Slight differences in winding inductance, the loading effects of the coupling



Figure 7. Simplified double tuned quadrature network.

element, L₁, and the approximation made by replacing L(1 + k) if Figure 5 with L in Figure 6 are a few of these effects. In general, the quantities ξ_1 and ξ_2 allow two more degrees of freedom for optimizing the transfer function.

The Phase Response

The trouble with the single tuned network is that once it has been tuned for nominal 90 degree phase shift, the transfer function is completely determined. Basically, the phase shift in a single tuned network is determined to be $\arctan(2Q\xi)$. There is no such limitation in the double tuned network. If the argument of the $\arctan()$ function could be made to more closely resemble the tan() function, a more linear phase relationship would be possible. This is exactly what the double tuned circuit allows. In order to see this more clearly, it is important to look at the Taylor expansion of the function tan(ax):

$$\tan(ax) = ax + \frac{a^3x^3}{3} + \frac{2a^5x^5}{15} + \dots$$
(31)

where a is some constant. For the purpose of this analysis, it is clearly desirable to have:

$$\frac{\text{Im}(Y)}{\text{Re}(Y)} = \tan(a\xi) \tag{32}$$

In practice, the best that can be obtained is an approximation to equation 32 for some range of ξ . If this relation can be approximated, the arctan function performed by the phase detector would more closely reflect a linear relation with input frequency. Several requirements on Y are immediately clear:

Im(Y) must vanish as ξ goes to zero. The ratio Im(Y)/Re(Y) must have no even order terms. The coefficients of (a ξ) should match those in the expansion of equation 31 through as many terms as possible.

The first two of the above requirements can be met by proper choice of ξ_1 and ξ_2 . Although not easy to derive, it is easy to verify that the choice of $\xi_1 = \xi_2 = -k/2$ satisfies both. Inserting this condition into equation 30 leads to:

$$\frac{\text{Im}(Y)}{\text{Re}(Y)} = 2\xi Q_{p} \left(\frac{(1 - k^{2}Q_{s}^{2})}{(1 + k^{2}Q_{s}Q_{p})} \right) \left(\frac{(1 + \frac{4Q_{s}^{2}}{1 - k^{2}Q_{s}^{2}}\xi^{2})}{(1 + \frac{4Q_{s}^{2}}{1 + k^{2}Q_{s}Q_{p}}\xi^{2})} \right)^{(33)}$$

This expression clearly has no terms in even powers of ξ . It also goes to zero as $\xi \rightarrow 0$. The polynomial quotient can be expanded to give the complete power series:

$$\frac{\text{Im}(Y)}{\text{Re}(Y)} = 2\xi Q_{p} \frac{(1 - k^{2}Q_{s}^{2})}{(1 + k^{2}Q_{s}Q_{p})}$$
(34)
$$\left[1 + 4Q_{s}^{2} \frac{k^{2}Q_{s}(Q_{s} + Q_{p})}{1 + k^{2}Q_{s}(Q_{p} - Q_{s}) - k^{4}Q_{s}^{3}Q_{p}} \xi^{2} + \dots\right]$$

The coefficient of the third order term in the Taylor expansion of tan(ax) can be matched by making:

$$\frac{1}{3} 4Q_{p}^{2} \frac{(1 - k^{2}Q_{s}^{2})^{2}}{(1 + k^{2}Q_{s}Q_{p})^{2}}$$

$$= 4Q_{s}^{2} \frac{k^{2}Q_{s}(Q_{s} + Q_{p})}{1 + k^{2}Q_{s}(Q_{p} - Q_{s}) - k^{4}Q_{s}^{3}Q_{p}}$$
(35)

This defines a relation between k, Q_s , and Q_p . For example, if $Q_s = Q_p = Q$, the requirement of equation 35 can be found to be simply that kQ = 0.327. For $Q_s \neq Q_p$, the opportunity to make more terms in the expansion coincide, at least approximately, is available.

The data sheet for the RCA CA3189 (4) indicates that a preferred circuit uses $Q_{p} = 20$, $Q_{p} = 55$, and k is at least 70 percent of k_{cr} . Application of equation 35 leads to a value of 0.0229 for k. This is roughly 76 percent of k_{cr} , precisely as indicated by the data sheet. Although this choice does not give a good match for the term in ξ^5 , it gives a much better coefficient for that term than could be obtained from the choice of $Q_{c} = Q_{p} = Q$.

In general, for quadrature network design, the phase response, amplitude response, and input impedance are the important considerations. Of these quantities, the one most often overlooked is input impedance. It is clear from this analysis that as the output impedance of the limiting IF is lowered, its drive capability is increased. With proper design, a greater output signal from the quadrature network can be provided. Finally, the double tuned network can be used to greatly improve the linearity of the demodulator. Proper design of the double tuned network can be a bit tedious, as several



terms in the power expansion of equation 34 should be carefully evaluated. However, it is fairly easy to get a good match through the third order term.

Although the quadrature detector is a very popular device for the demodulation of FM, the literature contains very little information on its operation or design. This analysis provides the fundamental relations needed for the proper design of quadrature networks. The relations derived here provide the RF engineer with a means for optimizing the design of quadrature detectors.

References

1. Henry Stark and Franz B. Tuteur, *Modern Electrical Communications*, Prentice-Hall, 1979.

2. William Gosling, *Radio Receivers*, Peter Peregrinus, Ltd., 1986.

Motorola, Inc., Motorola Linear/Interface Devices, 1988.
 RCA Corporation, RCA Integrated Circuits for Linear

Applications, 1986.
5. Sprague Electric Company, Semiconductor Division, Integrated Circuits Data Book, 1982.

About the Author

Edward Richley works in the Computer Science Laboratory at Xerox Corporation. He may be reached at Xerox Corp., Palo Alto Research Center, 3333 Coyote Hill Road, Palo Alto, CA 94304. Tel: (415) 494-4410.

Why engineers have relied on T T E filters for over 35 years

- Over 1,239,580 standard filters
- Custom designs at stock filter prices
- 10 day shipment guaranteed
- 72 hour prototype service is available
- Unconditional factory guarantee

Got a problem? Call our Engineering Hotline.

(213) 445-2796



America's Filter Specialist

T T E, Inc. West Los Angeles, CA (213) 478-8224 FAX: 1-800-473-2791 or (213) 445-2791

INFO/CARD 64

May 1991



RF transmission lines

CAD of Single and Tandem Lange Couplers

Timothy O'Connell and Patrick Murphy University College Cork, Ireland

In recent times the 90 degree hybrid has become one of the most important passive elements to be used in microwave integrated circuits (MICs), because of its important function in balanced mixers, balanced amplifiers, and other circuits. Although there are many types of hybrids available that provide equal power division with 90 degree phase shift, the Lange coupler has been the most widely used because of its superior broadband performance. This article describes a CAD program which calculates the design parameters of Lange couplers. Since the main disadvantage of Lange couplers is their difficulty in fabrication due to the very small dimensions of the interdigitated fingers, the concept of combining couplers in tandem is presented, and this option is incorporated into the CAD program.

Since its introduction by Julius Lange in 1966 the Lange coupler (1) has been the most widely used 90 degree hybrid at microwave frequencies because of its very wideband -3 dB coupling over octave bandwidths. The structure of the device, shown in Figure 1 is relatively simple, with alternate interdigitated fingers coupled together using bond wires. For this structure:

S is the spacing between interdigitated fingers.

W is the width of the interdigitated fingers.

L is the width of the coupler; 1/4 wavelength at the center frequency.

h is the substrate thickness of the microstrip.

To date, the accepted design approaches are those reported by Presser (2) and Osmani (3), which are similar in nature and are suitable for CAD implementation. Their design approach may be summarized as follows:

The interdigitated directional coupler may be viewed as a multiconductor transmission line of K (K even) elements, not including the ground plane. However, coupling between non-adjacent sections may be neglected with little error. Using



Figure 1. Diagram of a Lange coupler.

this simplification, Ou (4) derived the following set of equations for the even and odd mode impedances for such an array of parallel coupled lines.

$$Z_{oo} = Z_{o} \left(\frac{1-C}{1+C}\right)^{1/2} \frac{(K-1)(1+q)}{(C+q)+(K-1)(1-C)}$$
(1)

$$Z_{oe} = Z_{oo} \frac{C + q}{(K - 1)(1 - C)}$$
 (2)

where,

K = even number of strips

 $Z_0 =$ terminating impedance (usually 50 ohms)

C = voltage coupling coefficient

$$q = [C^2 + (1 - C^2)(K - 1)^2]^{1/2}$$

Next, the shape ratios are calculated from the synthesis equations of Akhtarzadm et al (5):

$$S/h = \frac{2}{\pi} \cosh^{-1}\left[\frac{\cosh\left(\frac{\pi}{2}(W/h)_{se}\right) + \cosh\left(\frac{\pi}{2}(W/h)_{so}'\right) - 2}{\cosh\left(\frac{\pi}{2}(W/h)_{so}'\right) - \cosh\left(\frac{\pi}{2}(W/h)_{se}\right)}\right] (3)$$

W/h =
$$\frac{1}{\pi} \cosh^{-1} \left[\frac{g+1}{2} \cosh \left((W/h)_{se} \frac{\pi}{2} \right) + \frac{g-1}{2} \right] - \frac{S}{2h}$$
 (4)

where,

$$(W/h)'_{so} = 0.78(W/h)_{so} + 0.1(W/h)_{se}$$
 (5)

and $(W/h)_{se,so}$ are given by Wheeler's equations for wide and narrow microstrip lines:





$$(W/h)_{se,so} = \frac{8}{p} \left[\frac{p(7 + 4/\epsilon_r)}{11.0} + \frac{11/\epsilon_r}{0.81} \right]^{1/2}$$
(6)
where,
$$p = \left[e^{\left(\frac{Z_{waso}}{84.8} \sqrt{\epsilon_r + 1} \right)_{-1}} \right]$$
(7)

Tandem Lange Couplers

Although the design of Lange couplers is relatively straightforward using the above equations, their main disadvantage lies in the fact that the dimensions of the finger width (W) and spacing (S) are often so small that fabrication of the circuit is difficult. Typical dimensions for Lange couplers are of the order of 10 µm, and this can pose difficulties unless the fabrication process has very good tolerances. A novel solution is to combine two Lange couplers in tandem, so that the overall coupling coefficient is higher than the individual coupling coefficients. Therefore, since the dimensions are inversely related to the value of the coupling coefficients, the etching constraints are greatly reduced.

Consider two couplers connected in tandem as shown in Figure 2. Assuming the signal level at input A is 1, and is 0 and A', and that the coupling coefficient of each section is k, the signal level at the other ports are:

$$\mathsf{B} = \mathsf{k} \tag{8}$$

$$B' = j \sqrt{1 - k^2}$$
(9)

$$C = k^2 - (1 - k^2)$$
(10)

$$C' = j2k \sqrt{1 - k^2}$$
 (11)

Here we can see that the 90 degree phase shift between C and C' is still preserved. Now for -3 dB power division, signals at C and C' must be equal. Therefore,

$$K^{2} - (1 - k^{2}) = 2k \sqrt{1 - k^{2}}$$
(12)

Defining $I = k^2$ yields:

$$8l^2 - 8l + 1 = 0 \tag{13}$$

By solving this equation and discarding one of the solutions, we get k = -8.34 dB. Thus, to achieve an overall coupling factor of -3 dB, each of the two couplers connected in tandem



Figure 3. Tandem Lange coupler arrangement.

must have a coupling factor of -8.34 dB.

Therefore, two Lange couplers with coupling factors of -8.34 dB can be combined to make a -3 dB coupler with the same overall characteristics as a single coupler. The more loosely coupled individual sections will relax the etching constraints by increasing the dimensions of the coupled fingers. Figure 3 shows two Lange couplers connected in tandem.

The CAD Program

(7)

A FORTRAN CAD program has been written which enables the user to design Lange couplers using the equations above. Single or tandem configurations can be selected, depending on the dimensions obtained and the quality of the etching process available. Figure 4 shows the simulated Touchstone* response of the single and tandem couplers. While the response of the single coupler is marginally better, in some applications this slight deviation is much less than the discrepancy in results (with a single coupler) due to the etching tolerances of the process available.

Finally, the CAD program gives the user the option of producing an output file directly in the format of a Touchstone input file. This allows great flexibility in incorporating the Lange coupler into a larger circuit, or allows the mask of the circuit to be generated directly from software such as MICAD® or **GAS-STATION**[®]

The operation of the program TLANGE is described by the flowchart in Figure 5. First, the design parameters are entered; substrate dielectric constant, substrate thickness, center frequency, and overall coupling coefficient. If a tandem arrangement is selected, the program then calculates the coupling coefficient of each section. Next, the dimensions of the Lange coupler are calculated using the Osmani/Presser method, and finally, the results are produced either directly to the screen, or in the format of a Touchstone input file. Figure 6 shows a typical output of the TLANGE program. Here a six finger tandem Lange coupler with a center frequency of 4 GHz has been designed on 5880 RT-Duroid* (0.79 mm substrate thickness).

The program is available from the RF Design Software Service, including a compiled version and source code listing. See page 30 for more information. RF



Figure 4. Simulated results of a single and tandem Lange coupler.

References

1. J. Lange, "Interdigitated Stripline Quadrature Hybrid," *IEEE Trans. on MTT*, December 1969, pp. 1150-1151.

2. A. Presser, "Interdigitated Microstrip Coupler Design," IEEE Trans. on MTT, October 1978, pp. 801-805.

3. R.M. Osmani, "Synthesis of Lange Couplers," *IEEE Trans.* on MTT, February 1981, pp. 168-170.

4. W.P. Ou, "Design Equations for an Interdigitated Directional Coupler," *IEEE Trans. on MTT*, February 1975, pp. 253-255.
5. S. Akhtarzed, et al, "The Design of Coupled Microstrip Lines," *IEEE Trans. on MTT*, June 1975, pp. 486-492.

About the Authors

Timothy O'Connell is currently working towards a Ph.D. in the area of "Microwave Components for Digital/Cellular Radio" at The Microwave Laboratory, University College Cork, Ireland. He completed his M.Eng.Sc. in 1989 and a B.E. with first class Honours in 1987. Dr. Patrick J. Murphy is Director of the Microwave Laboratory, University College Cork, Ireland. Both authors can be reached at telephone no. +353 21 276871 ext. 2214.



Figure 5. Flowchart of the TLANGE program.

DIM FREQ GHZ RES OH IND NH CAP PF LNG MM TIME PS COND /OH ANG DEG
CKT MSUB ER= 2.20 H=0.79 T=.005 RHO=1 RGH=0 MLANG6 1 2 3 4 W=.253 S=.406 L=13.500 MLANG6 2 6 4 7 W=.253 S=.406 L=13.500 DEF4P 1 6 3 7 LNGE
OUT LNGE DB[S21] GR1 LNGE DB[S41] GR1
FREQ SWEEP 2.5 4.0 5.5
GRID RANGE 2.5 4.0 5.5 GR1 0 -20 2

Figure 6. Touchstone file output from the TLANGE program.



WRI

Tunable Filters



BANDPASS & BANDREJECT FILTERS:

With K&L's bandpass filters you can tune any center frequency over the 3-3,000MHz frequency range (1 octave per filter). These filters are available in either 3 or 5 sections, a VSWR of 1.5:1, and a low insertion loss of < 1 dB in the 5% 3dB bandwidth model.

Bandreject or "notch" filters have a 25-1,000MHz (1 octave per filter) frequency range, VSWR of < 1.2:1 and is capable of eliminating undesirable signals by greater than 50dB rejection.

MULTICOUPLERS:

Standard units cover the 225-400MHz UHF and 100-160MHz VHF frequency ranges. Both manually and digitally tuned models are available. Ground based or airborne modules of up to four units each.



DIGITAL TRACKING FILTER NETWORKS: K&L's digitally controlled tunable bandpass network has a 20-1500MHz frequency range, using a single controller. The network has a tuning accuracy of \pm .25% of tuned center frequency, a 5 section Chebychev response with 3 to 30dB shape factor of 2.2:1 and 3 to 50dB shape factor of 3.5:1 and RFI/EMI moisture-sealed racks with 100dB isolation.

HIGH Q BANDPASS FILTERS:

Provides the answer to noise and interference signals found on co-located communication links. These filters feature 225-400MHz UHF or 100-163 MHz VHF frequency range capability. High selectivity of > 70dB, narrow 3dB bandwidth <600KHz, VSWR < 1.5:1 and a typical tuning speed of 10 seconds.



TUNABLE DIPLEXERS:

K&L's 30 to 88MHz tunable diplexer allows simultaneous receiver and transmitter operation from a single antenna over the entire frequency range. Nominal insertion loss of 2.5dB with nominal VSWR of 1.75:1. The filter is capable of handling 50 watts C.W.

DIGITALLY CONTROLLED BANDPASS FILTERS:

K&L's digitally controlled bandpass filters are high Q devices covering the frequency spectrum from 24MHz to 18GHz, 1 octave per filter. Each model has its own built-in microprocessor which controls a precision stepping motor. This filter series gives the system designer the options of control logic, drive voltages and packages.

For A Partner...



A DOVER TECHNOLOGIES COMPANY

408 Coles Circle Salisbury, Md. 21801 • PHONE: 301-749-2424 • FAX: 301-749-5725 • TWX: 710-864-9683

RF product report

A Clear Signal for RF Filters

By Liane G. Pomfret Associate Editor

The market for RF filters is stable and growing with minor variations that can be linked to the current recession. As usual, the commercial market is enjoying greater success than the military market. Despite a worldwide economic slump, some of the best business is being generated internationally and has buoyed relatively flat domestic sales. Surface mount technology is also contributing to continued profits. With a host of new applications and new technology, there's little to stand in the way of a successful future for RF filters.

It comes as no great surprise that the military market for RF filters has suffered because of congressional cutbacks. While the cutbacks have not been disastrous, they have been noticeable and companies involved in military have felt the pinch. For companies who focus on the commercial market, business is much better. The recent explosion of commercial RF applications has opened up new business opportunities. The list of applications - wireless communications, PCNs, mobile and land mobile, data transfer, medical systems, and satellites - continues to grow. While much of this technology was developed for the military, it has found success within the commercial arena, making it doubly profitable for the manufacturers.

Not all of the technology evolved from military contracts. Some developments came from the commercial sector. Surface mount and miniaturization of RF filters are the results of requests for smaller commercial devices - the 2 pound cellular phone as opposed to the 7 pound cellular phone. Like much of the RF industry, surface mount technology is now working its way into the filter industry. Yet the military still lags behind. Arie Verhagen, Vice President of Marketing for Murata-Erie comments, "The industry as a whole, has to do their homework to bring surface mount to the military's attention." Qualifying new technology for military specifications is a long, expensive process and the industry is reluctant to invest time and money without assurances that the technology will be accepted.

In the commercial sector, suppliers



A switched filter module from Integrated Microwave.

have been reducing their prices while maintaining or improving quality. As a result, manufacturers have more latitude to experiment with manufacturing techniques and materials. Steve Sodaro, Vice President of Marketing and Sales at TTE notes, "Components now are not as costly. It affords us the opportunity to do miniaturization. We're always trying to miniaturize without sacrificing performance." However, while a large firm has the resources to experiment with technologies such as surface mount, smaller companies are often restricted because of the lack of available packaging technology within their company. Packaging technology is available from outside vendors but cost and availability are a stumbling block to in-house development.

The communications industry offers a large number of uses for filters. Voice communications, data transfer and acquisition, LANs, and voice over data are all demanding more sophisticated filtering techniques. "The applications for filters in general are increasing, mainly due to enhancements in telecommunications, LANs, and various radio systems including cellular and land mobile beyond the classic military market,' says Dave Distler, Director of Sales and Marketing for Trilithic. Manufacturers are demanding extremely sophisticated filters capable of high reliability, high performance filtering.

Every company has its own area of specialty and responses will vary regarding the active areas for filter products. However, the general consensus is that communications equipment is the hot area right now. Randy Rhea, President of Eagleware notes, "We see a definite

increase in interest in filters for data communications systems and that often results in a greater emphasis in the delay characteristics of filters." AI Lowenstein, National Sales Manager, for Motorola's RF filter products components division, sees interest for their products in other areas as well. "The new activity is in the 915 MHz range, especially spread spectrum, new generation portable telephones, and remote data acquisition, meter reading and things along that line." He adds, "The other thing that is taking off is GPS and the satellite industry in general." Wavetek's focus has been high reliability communications such as those found in avionics communications systems. Even with the slowdown in the domestic military market, Sara Mussman, Components Business Unit Manager for Wavetek comments, "I see a significant amount of business out there.

A lot of this business is coming from the international sector. Mussman notes, "Any country that is aggressively pursuing an upgrade will be a good source of business." For George Szentirmai, President of DGS, business has been fairly flat. "The only thing is that our international sales are pretty strong especially in Europe." His company has had a great deal of interest from eastern european countries, but since there's no money available, there's been no sales. Werner Mueller, Vice President of KVG, North America comments, "I would hope that due to the reunification of Europe and due to the communication lack in eastern Europe, that there will be an increase in the European market." Toyocom's market situation is different. They currently hold less than 10 percent of the U.S. market and are looking to expand within the United States according to Dennis Reifel, Marketing Manager at Toyocom.

With the majority of the RF filter business on the upswing, the outlook for the future is optimistic. The advent of surface mount technology and constant improvements in price and performance make filters an excellent prospect for profit in the coming year. RF

For reprints of this report, contact Cardiff Publishing Company at (303) 220-0600; ask for the Circulation Department.

RF software

SPICE Transistor Library

A comprehensive library of RF transistor SPICE models is available from Intusoft. Models include 36 popular bipolar and JFET transistors, usable with any Berkeley SPICE compatible simulator. The models use a subcircuit approach that accounts for package parasitics, and matches published Sparameter magnitude and phase data up to 5 GHz. The library is priced at \$99, and is available in PC and Macintosh formats Intusoft

INFO/CARD #233

Dielectric Resonators

Two programs with easy data input are available for analyzing dielectric resonators. The program DRESV3 computes the resonant frequency and the Q factor of the TE01d mode. Program FOAM3 estimates the resonant frequencies of sixteen higher-order modes. Diskettes for the IBM PC or compatibles are priced at \$25.

Kajfez Consulting INFO/CARD #235

Version 3.0 Introduced

EEsof announces the new Version 3.0 product suite, upgrading their line of highfrequency software tools. Version 3.0 links all of EEsof's simulators under a single design environment; linear and nonlinear frequency domain, nonlinear transient SPICE analysis, and system/subsystem analysis. Its graphical design environment provides block diagram and schematic entry, multi-simulator control, documentation, and optional IC and board layout capability. Version 3.0 runs on UNIXbased workstations and PCs using the OS/2 operating system. EEsof, Inc.

INFO/CARD #234

Software Catalog

A new eight page catalog presents simulation and synthesis CAE tools from Webb Laboratories. Included are the SysCad and Receiver Advantage system simulators, FilSolv and TransCad for filter and transmission line structure synthesis, and SANA for microwave network signal and noise analysis and optimization.

Webb Laboratories INFO/CARD #232

Graphics-Based Analysis

DADiSP is a visually-oriented graphics software package designed for scientific and technical applications. Among the 200 data processing functions are signal arithmetic and editing, waveform generation, FFTs, and peak-finding. Extended memory support is an option, as is an IEEE-488 bus driver and an software module to interface with popular data acquisition boards. Versions are available for a wide range of PCs, workstations and larger computers.

DSP Development Corp. INFO/CARD #231

SPICE Library for Linear ICs SPICE macromodels are now available for

nearly every Burr-Brown op amp, difference amp, and instrumentation amplifier. Two levels are offered: PSpice® Parts™ and Enhance Parts[™] macromodels. A 5 1/4 inch diskette with more than 75 models is free from Burr-Brown.

Burr-Brown INFO/CARD #230

Thermal Analysis

Version 1.33 of SAUNA, a 3-D thermal annalysis package has been released by Tatum Labs. Larger models are possible; up to 700 nodes and 2750 thermal resistors. Reduced air density due to altitude is also accoutned for. SAUNA runs on IBM PC compatible and Macintosh II and SE/30 computers.

Tatum Labs, Inc. INFO/CARD #229



Mask Software CAD Translators

Reduce turnaround time and cut mask costs when you use our software postprocessors to directly photoplot board artwork. Stop cutting and peeling Rubylith . Our postprocessors convert AutoCAD, EGS, Generic CADD, or Calma drawings into Gerber photoplotter code.

РНОТО	PLOTTERS			
ACS 500	DXF to Gerber			
ACS 600	GDSII to Gerber			
ACS 700	HP EGS to Gerber			
TRANSLATORS				
ACS 800	EGS to AutoCAD DXF			
ACS 1000	MiCAD to AutoCAD			
ACS 3500	AutoCAD to GDSII			
ACS 3600	EGS to GDSII			
l or write for our ap	plication notes describing			

Ca how to photoplot hybrid circuits directly from your CAD database.

ARTWORK CONVERSION SOFTWARE, INC. 1320 Mission St. #5, Santa Cruz, CA 95060 408/ 426-6163 Fax: 408/ 426-2824

INFO/CARD 67

kr'desi REPRINTS

RF Design reprints are available for printing in quantities of 500 or more.

For further information contact:

REPRINTS REPRINTS REPRINTS REPRINTS

REPRINTS

Reprint Department RF Design 6300 S. Syracuse Way, Ste. 650 Englewood, CO 80111 (303) 220-0600

CRYSTAL FILTERS

MONOLITHIC • DISCRETE •

TEMEX ELECTRONICS is a manufacturer of Crystal Filters, Discriminators, L/C Filters and Crystals. TEMEX designs to custom specifications as well as the 10.7 MHz and 21.4 MHz standards. We take pride in fast response and the support of our customers. • PHONE • FAX • MAIL •

TEMEX ELEC	FRONICS, INC.
5021 N. 55th Ave. #1	0 Glendale, Az. 85301
el) 602-842-0159	(Fax) 602-939-6830

RF literature

RF/Microwave Product Guide

Avantek offers a 48-page Product Selection Guide to give engineers a guick overview of the company's standard products. Summary specifications are provided for transistors, integrated circuits, amplifiers, signal processing and control products, LNAs, uplink amplifiers, cellular base amplifiers, and YIG oscillators. Most items are in stock at Avantek distributors. Avantek, Inc.

INFO/CARD #250

Ceramic Filter Catalog

Murata Erie announces a design manual and catalog for their line of ceramic filters for communications. Single and multiple ele-ment filters are listed, covering standard frequencies such as 455 kHz, 3.58 MHz, 4.5 MHz and 10.7 MHz. Ceramic discriminators and signal detectors are also included, as are surface mount filters. Application information includes theory of operation and circuit design considerations.

Murata Erie North America INFO/CARD #249

Frequency Control Products

Comprehensive data on products available from Piezo Technology, Inc. is included in a new 96-page handbook. Monolithic and dis-crete crystal filters, LC filters, cavity bandpass filters, combline filters, interdigital filters, crystal and non-crystal oscillators, precision crystal resonators, RF subassemblies, and custom hybrid circuits are listed. Piezo Technology, Inc. INFO/CARD #248

RF Data Book

Motorola's RF Products Division has released their new RF Data Book, DL110/D Rev. 4, a two-volume edition covering power FETs, power bipolar and small-signal transistors, plus RF power modules. 84 new products have been included since the previous version, along with new applications information Motorola, Inc.

INFO/CARD #247

Coaxial Switches

A new Standard Products Brochure is available from Dow-Key Microwave, listing standard electromechanical coaxial switches and relays in configurations from SPDT to SP12T. Transfer switches, bypass switches and low cost RF relays are also included. Photographs, specifications and schematic diagrams are provided for these products. Dow-Key Microwave Corp. INFO/CARD #246

1991 Test Instruments

Tektronix' 1991 customer catalog is now available, highlighting more than 3000 products in three broad areas: electronic test and

measurement instruments, professional broadcast equipment, and computer peripherals. New products include communication signal analyzers, VXIbus products, high resolution display monitors, HDTV test equipment and low cost broadcast spectrum analyzers. Tektronix, Inc. INFO/CARD #245

Coatings Brochure

A line of coating and ink systems is described in a new brochure from Emerson & Cuming. One and two-component systems are presented, used in making membrane switches, molded and flexible circuits, polymer thick film circuitry, and for modifying circuit boards. The coatings provide protection against electrical contact during component assembly.

Emerson & Cuming, Inc. INFO/CARD #244

Frequency Chart Update The RF Products and Linear Integrated

Circuits Divisions of Motorola have published a new U.S. frequency allocation chart covering the RF spectrum up to 4000 MHz. Added to the previous version's allocation categories is a segment for Part 15 unlicensed devices. The chart is free, and is suitable for convenient wall mounting.

Motorola, Inc INFO/CARD #243

SAW Filter Note

A new Application Note discussing SAW coupled-resonator (CR) filters is available from RF Monolithics. SAW CR filters are suitable for many narrow-band applications from 70 MHz to 1500 MHz, and can be built with fractional bandwidths from 0.03 to 0.5 percent. The filters exhibit low loss (3 dB typical) under matched conditions. The note covers theory, operational performance limits, and a comparison with other filter technologies

RF Monolithics, Inc. INFO/CARD #242

Reconditioned Equipment

A catalog featuring reconditioned Philips/ Fluke test and measurement equipment is announced by Rubytron. Oscilloscopes, synthesizers, frequency counters/timers, sweepers, function generators and pulse generators are among the equipment types available. All instruments are calibrated and warranted. **Rubytron Instruments** INFO/CARD #241

Distributor Catalog

Tektronix 1991 Distributor Products Catalog contains data on analog and digital oscilloscopes, frequency counters, digital multimeters and function generators. These products are offered through authorized distributors.

RAG Electronics, Inc. INFO/CARD #240

No matter how you look at it...we've got the right GPS time and frequency receiver for you Power line Voltage Phase Angle Module provides precise time-tagged 60-cycle phase 2

Integrated antenna/downconverter supports long cable feeds Contact us today for complete literature and information. Find out how you can benefit rom GPS and get with the leading edge of todays most sophisticated technology FTS/(0) AUSTRON angle measurement Event Time Logging Module provides precise time-tagging for power line fault locating systems Network synchronization configurations support telecommunications master clock applications 2

Datum companies working together to meet yor needs... O. BOX 14766 AUSTIN, TX 78761 - TEL (512) 251-2313 - FAX (512) 251-3685



JFW Rotary Attenuators



50R-002 Frequency Range: DC-1000 MHz Attenuation Range: 0-130 in 10 dB steps Connectors: BNC, N, TNC or SMA

50BR-008 Frequency Range: DC-2000 MHz Attenuation Range: 0-80 dB in 1 dB steps Connectors: BNC female (standard) SMA and N available upon request



50R-029 (left)

Frequency Range: DC-2000 MHz Attenuation Range: 0-70 dB in 10 dB steps Connectors: SMA female (standard) BNC available upon request

50R-019 (right)

Frequency Range: DC-2000 MHz Attenuation Range: 0-10 dB in 1 dB steps Connectors: SMA female (standard) BNC available upon request



50R-079 (left) Frequency Range: DC-1000 MHz Attenuation Range: 0-120 dB Connectors: BNC female or "N" female

50R-080 (right) Frequency Range: DC-1000 MHz Attenuation Range: 0-12 dB Connectors: BNC female or "N" female



JFW Industries, Inc. 5134 Commerce Square Dr. Indianapolis, Indiana 46237 (317) 887-1340

Advertising Index

	•
A&A Engineering	Kay Elemetrics Corp
Adams Russell Electronics-	KVG
Anzac Division	Locus, Inc
Advantest America, Inc	Loral Microwave—Wavecom
Alan Industries, Inc	M/A-Com Control
Allen Avionics, Inc	Components Division
American Technical Ceramics Corp. 19	M/A-Com Omni Spectra, Inc
Amplifier Research	Maxim
Amplifonix	Merrimac
Andersen Laboratories	Noise/Com, Inc
Applied Specialties, Inc	Oscillatek
Arrowsmith Shelburne, Inc	Penstock Engineering, Inc
Artwork Conversion Software, Inc	Pole Zero Corporation
Avantek	Programmed Test Sources
Axonn Corporation	QUALCOMM, Inc
Bliley Electric Company	Quality Components, Inc
Cal Crystal Lab, Inc	Ramsey Electronics
California Eastern Laboratories	RF Design Software Service
CIR-Q-TEL Microwave	RF Neulink
Coilcraft	RF Prototype Systems
Comlinear Corporation	Somersoft
CTS Corp	Spraque-Goodman 37
DAICO Industries, Inc	Stanford Telecommunications 28
Dale Electronics	STC Components
Eagleware	Surcom Associates, Inc
E.F. Johnson, Inc	Teledyne Microwave 29
EG&G Frequency Products, Inc	Temex Electronics, Inc. 78
Elcom Systems	Tesoft
ENI	Thomson—CSF 53
Epson America, Inc. 60	Time & Frequency, Ltd. 46
Fotofabrication Corp	Trak Microwave Corporation
Frequency & Time Systems/Austron 79	Trilithic
Henry Radio	TTE. Inc
Hewlett-Packard	Viewlogic Systems, Inc. 9
IFR Systems, Inc	Voltronics Corporation 83-84
JFW Industries, Inc. 80	Wavecom 2
Johanson Manufacturing Corp. 57	Werlatone, Inc.
K&L Microwave 76	Wide Band Engineering
Kalmus Engineering International, Ltd. 10-11	Company, Inc. 23
5 5	

RF engineering opportunities

RF ENGINEERS

GEO-CENTERS, INC., a high technology, growthoriented research and development company specializing in engineering and high-tech services for the U.S. Department of Defense, has the following immediate, full-time openings at our central New Jersey location:

Senior RF Engineer — to perform R&D on high stability frequency standards and clocks, including oscillator design and specifications; and resonator and oscillator testing. A PhD in EE or a related field and CAD/ATE experience are desirable. Must be a self-starter who is capable of independent and creative work in an R&D environment.

RF Engineer — to perform R&D on high stability frequency standards and clocks, including oscillator design, fabrication and specification; and resonator and oscillator testing. A BS in EE or a related field and CAD/ATE experience are desirable. Experience in data analysis, modern computational methods and good oral and written communication skills are necessary.

GEO-CENTERS, INC. offers competitive salaries, an outstanding benefits package and unlimited growth potential. To explore these positions, please forward your resume with salary requirements to: GEO-CENTERS, INC., Human Resources Dept. - RF, 762 Rt. 15 South, Lake Hopatcong, NJ 07849. An Equal Opportunity/ Affirmative Action Employer. U.S. citizenship or permanent residency required.

YOU HAVE AS MUCH POTENTIAL AS WE DO-UNLIMITED.

RADIO FREQUENCY ENGINEERS

W

hen you're creating the world's most advanced cellular network, you need the most advanced Radio Frequency Engineers.

Among your varying responsibilities, you will evaluate subscriber traffic, present and future RF coverage and growth data to forecast system expansion and to provide optimal service for our customers. You will design the frequency plan, conduct testing on potential installation areas, assist the real estate group on potential cell and enhancer locations, and remain current on new technology and industry advancements.

The individuals we're seeking will have a Bachelor's degree in Electrical Engineering and two or more years of experience in the cellular or radio design industry.

Located in the Southern California community of Irvine, near recreational parks and the ocean, you'll enjoy many of the benefits that come from a progressive company, including a competitive salary, company wide bonus plan and an extensive benefits package. For immediate, confidential consideration, please send your resume with salary history to: PacTel Cellular, Dept. CR-RF/D, P.O. Box 19707, Irvine, CA 92713-9707. An Equal Opportunity Employer. Principals only, please.



A Pacific Telesis Company

WR



- 900 MHz/2.4 GHz
- Complete RF Lab Facilities
- Patented, FCC Approved Designs

AXONN CORPORATION 101 W. Robert E. Lee Blvd., 2nd Floor New Orleans, Louisiana 70124 (504) 282-8119

INFO/CARD 73

175/mo.

303-220-0600

allows you to randomly tune, cut, copy or paste any component. This makes it very easy to experiment with many different kinds of circuit topologies in order to achieve the best design. This also makes the software very educational for those who are just learning the Smith chart.

... PARTIAL LIST OF FEATURES ...

Network Analyzer Z-Theta Chart H, S, Y, Z, ABCD Conversions Common B - Common E - Common C Simultaneous Multiple File Analysis Operating and Available Power Gain Circles Unilateral Power Gain Circles Noise Circles Stability Circles S-Parameter Stack for Recursive Operations Data Tables on Screen or Dump to Printer Internal Graphic Screen Dump

\$259.00, Somersoft, (707)829-0164