

engineering principles and practices

March 1995



000000-40

0617

ANSI

100 100 100 *Cover Story* New ASIC Targets Interactive Cable

Featured Technology Test Methods



- less than 1dB insertion loss greater than 40dB stopband rejection surface mount BNC, Type N, SMA available
- 5-section, 30dB/octave rolloff
 VSWR less than 1.7(typ.)
 rugged hermetically sealed pin models
 constant phase
 meets MIL-STD-202 tests
 over 100 off-the-shelf models
 immediate delivery



Mini-Circuits RF/IF Surface Mount Designer's Guide features 48 pages of the most up-to-date and complete product and specification information about Mini-Circuits surface mount components. The RF/IF Microwave Handbook is packed with 740 pages of articles, selection guides and detailed specifications for Mini-Circuits components.

Call, write or fax for your free Surface Mount Designer's Guide and Handbook today!





low bass. Plug-in. dc to 155MHz dc to 1200MHz

LOW PASS attenuation, dB 80

frequency



HIGH PASS



frequency

BANDPASS



frequency

Passband No. Stopband, MHz boss MHz boss Passband boss Stopband, MHz boss Stopband, MHz boss Model Model MHz MHz Stopband, MHz boss Ioss boss Stopband, MHz Ioss boss Stopband, MHz Ioss boss Stopband, MHz Ioss boss Ioss Ioss									
★LP-1.9 DC-1.9 3.4-4.7 4.7-200 ★LP-200 DC-190 290-390 390-800 ★LP-2.5 DC-2.5 3.8-6.0 5.0-200 ★LP-300 DC-225 320-400 400-1200 ★LP-5 DC-5 8-10 10-200 ★LP-300 DC-225 320-400 400-1200 ★LP-50 DC-211 19-24 24-200 ★LP-450 DC-470 580-750 750-760-1800 ★LP-300 DC-120 ★LP-450 DC-400 580-750 750-980 920-2000 ★LP-30 DC-32 47-61 61-200 ★LP-800 DC-680 840-1120 1120-2000 ★LP-50 DC-48 70-90 90-2000 ★LP-800 DC-700 1000-1300 1300-2000 ★LP-30 DC-48 70-90 90-2000 ★LP-760 DC-700 1000-1300 1300-2000 ★LP-70 DC-680 90-117 117-300 ★LP-800 DC-780 1100-1400 1400-2000 ★LP-90 DC-81 121-157 157-400 ★	Model No.	Passband MHz loss < 1dB	Stopban loss > 20dB	id, MHz ioss > 40dB		Model No.	Passband MHz loss < 1dB	Stopban loss > 20dB	id, MHz loss > 40dB
*LP-150 DC-140 210-300 300-800 *LP-1200 DC-1000 1820-2100 2100-2500	★LP-1.9 ★LP-2.5 ★LP-5 ★LP-21.4 ★LP-30 ★LP-30 ★LP-70 ★LP-90 ★LP-100 ★LP-150	DC-1.9 DC-2.5 DC-5 DC-11 DC-22 DC-32 DC-48 DC-60 DC-81 DC-98 DC-140	3.4-4.7 3.8-5.0 8-10 19-24 32-41 47-61 70-90 90-117 121-157 146-189 210-300	4.7-200 5.0-200 10-200 41-200 61-200 90-200 117-300 157-400 189-400 300-600	_	*LP-200 *LP-250 *LP-300 *LP-450 *LP-450 *LP-650 *LP-600 *LP-800 *LP-800 *LP-1000 *LP-1000	DC-190 DC-225 DC-270 DC-400 DC-520 DC-520 DC-780 DC-720 DC-780 DC-780 DC-780 DC-1000	290-390 320-400 410-550 580-750 750-920 840-1120 1000-1300 1080-1400 1100-1400 1340-1750 1620-2100	390-800 400-1200 550-1200 750-1800 920-2000 1120-2000 1400-2000 1400-2000 1750-2000 2100-2500

All models priced qty, 1-9 (\$ee.), Conn. Type P = 11.45, B = 32.95, S = 34. • Exceptions: *LP-1.9 P = 13.95, B = 34.95, *LP-2.5 P = 14.95, B = 35.95 __On both models, add following to B price: \$3.00 for N, \$2.00 for S 34.95, N = 35.95

75 ohm versions available

70-90

146-189

Surface-mount dc to 1200MHz dc to 108MHz DC-5.0 DC-8.0 DC-11 DC-22 DC-25 DC-30 DC-45 DC-95 DC-135 DC-190 DC-225 DC-380 DC-420 DC-550 DC-700 DC-1000 SCLF-5 SCLF-8 SCLF-10.7 SCLF-21.4 SCLF-25 SCLF-30 SCLF-45 SCLF-135 SCLF-190 SCLF-225 SCLF-380 8-10 12.5-16.5 19-24 32-41 10-200 210-300 16.5-200 24-200 41-200 290-390 340-440 580-750 36-47 47-61 47-200 61-200 SCLF-420 SCLF-550 750-920 800-1050

90-200

189-400

Price: SCLF 21.4-SCLF 420 \$11.45 ea. SCLF-8, 10.7, 550, 700, 1000 \$12.95 ea. SCLF-5 \$14.95 Qty. (1-9)

SCLF-700

SCI F-1000

Elat Time Delay, dc to 1870MHz

Model	Passband MHz	Sto N loss	pband /IHz loss	Freq. Rang 0.2fco	WR je, DC thru 0.6fco	Group I Freq. fco	Delay Variati Range, DC 21co	ions, ns thru 2.67fco
INO.	1055 < 1.200	>1008	>2000	L	~	^	~	~
*BLP-39 *BLP-117 *BLP-156 *BLP-200 *BLP-300 *BLP-467 ▲BLP-933 ▲BLP-1870	DC-23 DC-65 DC-94 DC-120 DC-180 DC-280 DC-560 DC-850	78-117 234-312 312-416 400-534 600-801 934-1246 1866-2490 3740-5000	117 312 416 534 801 1246 2490 5000	1.3:1 1.3:1 1.6:1 1.25:1 1.25:1 1.3:1 1.3:1 1.45:1	2.3:1 2.4:1 1.1:1 2.2:1 2.2:1 2.2:1 2.9:1	0.70 0.35 0.30 0.40 0.20 0.15 0.09 0.05	4.0 1.4 1.1 0.6 0.4 0.2 0.1	5.00 1.90 1.50 0.80 0.55 0.28 0.15
Price (1-0 oh/	all modele: pl	unio \$10.05	RMC \$38.05	SMA \$29.05	Turne N \$20.05			

I YDE N NOTE:

-933 and -1870 only with N and SMA connectors.

high pass, Plug-in, 13 to 1200MHz

SCLF-95

210 to 2200MHz

Model No.	Stopl Mł loss > 40dB	band Hz loss > 20dB	Passband, MHz loss < 1dB	VSWR Pass- band Typ.	Model No.	Stopi Mi loss >40dB	band Hz loss > 20dB	Passband, MHz loss < 1dB	VSWR Pass- band Typ.
*HP-25 *HP-50 *HP-100 *HP-150 *HP-175 *HP-200 *HP-250 *HP-300	DC-13 DC-20 DC-40 DC-70 DC-70 DC-70 DC-90 DC-100 DC-145	13-19 20-26 40-55 70-95 70-105 90-116 100-150 145-190	27.5-200 41-200 90-400 133-600 160-800 185-800 225-1200 †290-1200	1.7:1 1.5:1 1.5:1 1.8:1 1.5:1 1.6:1 1.3:1 1.7:1	*HP-400 *HP-500 *HP-600 *HP-700 *HP-800 *HP-900 *HP-1000	DC-210 DC-280 DC-350 DC-400 DC-445 DC-520 DC-550	210-290 280-365 350-440 400-520 445-570 520-660 550-720	395-1600 500-1600 600-1600 700-1800 780-2000 910-2100 1000-2200	1.7:1 1.9:1 2.0:1 1.6:1 2.1:1 1.8:1 1.9:1

Price, (1-9 qty), all models: plug-in \$14.95, BNC \$36.95, SMA \$38.95, Type N \$39.95. For *HP-25, Add \$2 ea. 1Loss 1.5 dB max.

bandpass, Elliptic Response, 10.7 to 70MHz

Model No.	Center Freq. (MHz)	Passband I.L. 1.5 dB Max. (MHz)	3 dB Bandwidth Typ. (MHz)	I.L. > 20dB at MHz	pbands I.L. > 35dB at MHz	
*BP-10.7 *BP-21.4 *BP-30 *BP-60 *BP-70	10.7 21.4 30.0 60.0 70.0	9.5-11.5 19.2-23.6 27.0-33.0 55.0-67.0 63.0-77.0	8.9-12.7 17.9-25.3 25-35 49.8-70.5 58.0-82.0	7.5 & 15 15.5 & 29 22 & 40 44 & 79 51 & 94	0.6 & 50-1000 3.0 & 80-1000 3.2 & 99-1000 4.6 & 190-100 6.0 & 193-100	
Price. (1-9 atv). all models: plug-in \$18.95.						

BNC \$40.95, SMA \$42.95, Type N \$43.95

Passhand I

MHz

loss

< 1dB

18-25 25-35 35-49

Stophand

loss 20dB

at MHz

1.3 & 150 1.9 & 210 2.6 & 300 3.1 & 350 3.8 & 400 4.4 & 490

VSWR

1:3:1 Total Band

MHz

DC-220 DC-330 DC-400 DC-440 DC-500 DC-550

Constant Impedance,

21.4 to 70MHz

Center

Freq.

MHz

21.4 30.0 42.0 50.0 60.0 70.0

Model

No.

*IF-21.4 *IF-30 *IF-40

*IF-50 *IF-60 *IF-70

NOTE: *Add Prefix P, B, N, or S for Pin, BNC, N, or SMA connector requirement.



INFO/CARD 1

P.O Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718)332-4661 For detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER • MICROWAVE PRODUCT DATA DIRECTORY • EEM • MINI-CIRCUITS' 740- pg. HANDBOOK. CUSTOM PRODUCT NEEDS...Let Our Experience Work For You. F 200 Rev Orig

300-600

390-800 440-1200 750-1800

920-2000 1050-2000 1300-2000

2100-2500

1000-1300

1620-2100

⁴¹⁻⁵⁸ 50-70 58-82 Price, (1-9 qty), all models: plug-in \$14.95, BNC \$38.95, SMA \$38.95, Type N \$39.95

THE WORLD'S LARGEST SELECTION



2kHz-10GHz from \$295

Choose from over 480 standard off-the-shelf models from 2-way to 48-way; 0°, 90° and 180°; 50 and 75 ohms; covering 2kHz to 10GHz. Mini-Circuits will also supply your special needs such as wider bandwidths, higher isolation, lower insertion loss, and phase matched ports…all at catalog prices with rapid turnaround time. Models include surface mount, plug-in, flat-pack and standard connectorized designs such as SMA, N, TNC, C, and F connectors as well as custom designs. Ultra-miniature surface mount units provide excellent solutions in cellular communications, cable systems and countless wireless applications. All units come with a 1year guarantee and "skinny" 4.5 sigma repeatability unit-to-unit and production run to production run. Catalog models are guaranteed to ship within one week.

Mini-Circuits...we're redefining what VALUE is all about!

Mini-Circuits RF/IF Surface Mount Designer's Guide features 48 pages of the most up-to-date and complete product and specification information about Mini-Circuits surface mount components. The RF/IF Microwave Handbook is packed with 740 pages of articles, selection guides and detailed specifications for Mini-Circuits components.

Call, write or fax for your free Surface Mount Designer's Guide and Handbook today!

INFO/CARD 3



P.O Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718)332-4661

r detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER • MICROWAVE PRODUCT DATA DIRECTORY • EEM • MINI-CIRCUITS' 740- pg. HANDBOOK. CUSTOM PRODUCT NEEDS...Let Our Experience Work For You.

1052

F 194 Rev Orig

2.5KHz-8GHz AMPLIFIERS (3 Piece Set)

10MHLA.2GHL

2.5KHZ-500MHZ



\$1095 (Set of 3 1-9 qty.) +20dBm Power Output, 20dB Gain

Model :	Freq. (MHz)	Gain (dB)	Power Output, dBm @ 1dB Compression	DC Volt V	Power Current mA	Conn. Type	Indiv. Price (\$) (1-9 qty.)
ZHL-6A	.0025-500	21	+23	+24	350	BNC	199
ZHL-1042J	10-4200	25	+20	+15	330	SMA	495
ZRON-8G	2000-8000	20	+20	+15	310	SMA	495

Set of 3 Amplifiers # KZHL-318: \$1095 (1-9 aty.)

Expand laboratory capabilities and put a full spectrum of power at your fingertips with Mini-Circuits 2.5KHz to 8GHz medium power amplifier set. Each ultra-wideband set contains three individual heat sinked RF amplifiers with at least +20dBm output and overlapping frequency response range capabilities; 2.5KHz to 500MHz, 10MHz to 4.2GHz and 2GHz to 8GHz. Applications for these amplifiers include increasing the signal levels to power meters, spectrum analyzers, frequency counters and network analyzers as well as boosting signal generator outputs.

ZHL-1042,

You can buy these amplifiers individually at Mini-Circuits already low prices, or own the full spectrum set for the money saving price of only \$1095 (1-9 qty.) ! To order from stock with a guarantee to ship within one week, call Mini-Circuits today !

Mini-Circuits...we're redefining what VALUE is all about!



P.O Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718)332-4661 For detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER • MICROWAVE PRODUCT DATA DIRECTORY • EEM • MINI-CIRCUITS' 740- pg. HANDBOOK. CUSTOM PRODUCT NEEDS...Let Our Experience Work For You.

INFO/CARD 4

RFdesign

contents

March 1995

featured technology

30 Bridge Method for Measuring Amplitude Intermodulation Distortion

This article describes a distortion measurement method that greatly reduces contributions from the signal source and the spectrum analyzer. —*Nina Krikorian*

38 Distortion Measurements Using the Spectrum Analyzer

This overview of several types of distortion is meant to provide an introduction to these unwanted signal components, and to give a brief description of how the spectrum analyzer is used to measure them. — Morris Engelson

cover story

46 A Low-Cost Return Path CATV Transmitter ASIC The application specific IC (ASIC) described in this article provides BPSK or QPSK signals to be transmitted "upstream" in interactive cable television applications. The chip produces bursts of spectrally-shaped signals centered at 40 MHz to prevent interference. — Bill Xenakis

tutorial

58 Nonlinear Analysis in RF Design The strengths and weaknesses of time-domain, harmonic balance, and

The strengths and weaknesses of time-domain, harmonic balance, and Volterra-series analysis of nonlinear circuits are reviewed. Some of the pitfalls of each of the methods are pointed out, along with ways to avoid them. — Steve Maas, Ph.D.

design awards

64 CircleX Program Analyzes S Parameter Data This high placer in the 1994 RF Design Awards Contest accepts a

This high placer in the 1994 RF Design Awards Contest accepts a device's two-port data in S, y, or h formats and then displays gain and stability circles for the device. — Chris Buckingham

70 Analysis and Optimization of Oscillators for Low Phase Noise and Low Power Consumption

This article presents investigations into the design, analysis and performance of practical voltage-controlled or tunable LC oscillators. Modeled versus measured performance of several common oscillator designs are compared, and the steps taken to obtain more accurate models for CAD analysis are noted. —*Ulrich L. Rohde and Chao-Ren Chang*



departments

- 8 Editorial
- 14 Calendar
- 19 Courses 20 News
- 28 Industry Insight
- 52 New Products
- 69 New Literature
- 69 New Software
- 80 Product Forum
- 82 Marketplace
- 92 Advertiser Index
- 92 Company Index
- 93 Info/Čarď

RF DESIGN (ISSN:0163-321X USPS: 453-490) is published monthly and semi-monthly in August. March 1995. Vol.18, No. 3. RF Design is a registered trademark of Argus Inc. Copyright 1995 by Argus Business, a division of Argus Inc., 6151 Powers Ferry Road, NW, Atlanta, GA 30339, (404) 955-2500. Editorial and advertising offices at 6300 S. Syracuse Way, Suite 650, Englewood, CO 80111, (303) 220-0600. Printed in USA. Second-Class Postage paid at Atlanta, GA and at additional mailing offices. Subscription office: RF Design, P.O. Box 1077, Skokle, IL 60076. Sub-scriptions are \$39 per year (\$67 for two years) in the United States; \$50 (surface mail) or \$99 (Air Mail) per year for foreign countries. Payment must be made in U.S. funds and accompany request. If available, single copies and back issues are \$8.00 each (in the U.S.). This publication is available on microfilm/fiche from University Microfilms Internation-al, 300 Zeeb Road, Ann Arbor, MI 48106 USA (313) 761-4700. Authorization to photocopy items for internal, personal or educational classroom use is granted by RF Design, pro-vided the appropriate fee is paid directly to Copyright Clear-ance Center, 222 Rosewood Drive, Danvers, MA 01923 and provided the number of copies is fewer than 100. For autho-rization, contact the Copyright Clearance Center at (508) 750-8400. The Transactional Reporting Service fee code is: 0163-321X/95/\$3.00. For those seeking 100 or more more copies, please contact the magazine at (303) 220-0600.

SUBSCRIPTION INQUIRIES: (708) 647-0756.

HIGH POWER QUADRATURE HYBRIDS



FREQ. RANGE 100-1000 MHz POWER 250 WATTS CW

TYPICAL SPECIFICATIONS

MODEL QH3198	100-300	MHZ
MODEL QH3199	300-1000	MHZ
LOSS	0.5db.	max.

AMP.BAL	± 0.3db max.
ISOLATION	20db typ.
PHASE	
VSWR	1.3:1 max.
CONNECTORS	N

WERLATONE offers a full line of quadrature hybrids covering the 2-1000MHz frequency range at power levels to 1000 watts.

BROADBAND HIGH POWER

- DIRECTIONAL COUPLERS
- POWER COMBINERS
- HYBRID JUNCTIONS

WERLATONE INC. DECADES AHEAD

P.O. Box 47 Brewster, NY 10509 Tel. (914) 279 6187 FAX. (914) 279 7404

RF editorial

The Changing Role of the RF Engineer



By Gary A. Breed Editor

At the recent RF Expo West conference in San Diego, our keynote speaker, Dr. Ted Rappaport, gave us a look at the future of wireless. Ted is the founder of the Mobile and Portable Radio Research Group at Virginia Tech. The MPRG is a model of industry/university cooperation, matching research and student education with the present and future needs of the communications industry. His remarks were fascinating, and I'd like to note some of his views in this month's editorial column.

Public demand for wireless services are higher than for any other telecommunications services — As evidence for this, television sets are in nearly every household in the nation, a penetration that was achieved in very few years after its widespread introduction in the late 1940s. More households have televisions than have telephones, and cable TV only reaches about 60 percent of households. Wireless wins!

Cellular growth rate matches that of television's early years — Once cellular service was firmly in place, it really took off. The current growth of cellular is 50 percent a year, an astounding number in any business. New Personal Communications Services (PCS) will simply add new, lower cost choices to fuel further growth in mobile telecommunications.

The challenges of such growth involve a lot more than circuits — Acquiring locations for base stations, connection agreements to the wired telephone infrastructure, and management of spectrum allocations are among the top concerns of the communications industry. These are at least as important as building a new, cheaper handsets. The equipment is essential, of course, but it can't be used if there is no place to put it, physically or in channel space.

The engineer's role is changing dramatically — Low cost, high volume, rapid development and complex technical specifications require new engineering approaches. Today's wireless engineers need to merge design criteria based on propagation, digital signal processing, power management, physical design, reliability, and manufacturability. RF circuit design is but one element of wireless product development.

To add my own comment on this last item: does every engineer need to be a Renaissance Man? No, but those who can achieve this wide range of capabilities will be the most sought after, especially in small-to-mid-size companies. The best alternative (presently used by most companies) is to have close-knit teams whose participants represent all the necessary specialties. Even in a team, each member will be expected to have a familiarity with areas outside his or her area of primary expertise — more than has been expected of engineers in the past. Then we must add an emphasis on cost that makes the personal computer price battles look tame!

New markets bring new opportunities, but they also bring changes. The wireless marketplace is intensely competitive, and that competition extends to the engineers who design wireless products.

ULTRA-BROADBAND RF POWER AMPLIFIER SYSTEMS



MODEL 7100LC WITH IEEE 488

EMI-EMC-RFI

- AC Operation
- Fully Protected
- Drive Mismatched Loads
- No VSWR Shutdown
- ALC Flat Gain Response
- Remote Functions
- Lowest Prices
- IEEE Interface Capability



1-800-344-3341 (206) 485-9000 fax(206) 486-9657 21820-87th S.E. Woodinville, WA 98072 USA

DUNTRY	REPRESENTATIVE	TELEPHONE NO.	FACSIMILE NO.
RANCE	KMP ELECTRONICS	1464 50945	146452403
RMANY	EMCO ELEKTRONIK	898562071	898597785
WEDEN	MAT & TEST TEK.	87926100	87923190

ALL S	SOLID-STATE I	MOS-FET RF AMPI	LIFIER SY	YSTEMS
MODEL	RF OUTPUT	FREQUENCY RANGE	GAIN	SPECIAL USA PRICE
700LC	1.5W CW	.003-1000 MHz	33dB	\$ 1,795
704FC	4W CW	.5-1000 MHz	33dB	\$ 2,095
210LC	10W CW	.008-225 MHz	40dB	\$ 2,495
710FC	10W CW	1-1000 MHz	40dB	\$ 6,695
*727LC	10W CW	.006-1000 MHz	44dB	\$ 7,950
713FC	15W CW	20-1000 MHz	42dB	\$ 5,680
225LC	25W CW	.01-225 MHz	40dB	\$ 3,295
*737LC	25W CW	.01-1000 MHz	45dB	\$ 9,995
712FC	25W CW	200-1000 MHz	45dB	\$ 6,950
714FC	30W CW	20-1000 MHz	45dB	\$ 9,350
250LC	50W CW	.01-225 MHz	47dB	\$ 5,550
715FC	50W CW	200-1000 MHz	47dB	\$ 14,990
707FC	50W CW	400-1000 MHz	50dB	\$ 10,990
716FC	50W CW	20-1000MHz	47dB	\$ 17,950
*747LC	50W CW	.01-1000 MHz	47dB	\$ 18,550
116FC	100W CW	.01-225 MHz	50dB	\$ 9,500
709FC	100W CW	500-1000 MHz	50dB	\$ 16,990
717FC	100W CW	200-1000 MHz	50dB	\$ 19,500
718FC	100W CW	20-1000 MHz	50dB	\$ 29,800
7100LC	100W CW	80-1000 MHz	50dB	\$ 19,500
*757LC	100W CW	.01-1000 MHz	50dB	\$ 29,950
122FC	250W CW	.01-225 MHz	55dB	\$ 19,950
723FC	300W CW	500-1000 MHz	55d3	\$ 29,995
LA500V	500W CW	10-100 MHz	56dB	\$ 12,900
LA500UF	500W CW	100-500 MHz	57dB	\$ 46,000
LA500G	500W CW	500-1000 MHz	57dB	\$ 55,000
LA1000V	1000W CW	10-100 MHz	60dB	\$ 22,500
LA1000UF	1000W CW	100-500 MHz	60dB	\$75,000
LA1000G	1000W CW	500-1000 MHz	60dB	\$ 99,000
LS-1000	1000W CW	.01-1000 MHz	60dB	\$230,000
RUGG	ED VACUUM	TUBE DISTRIBUTE	D AMPL	FIERS
116C	100W CW	.01-220 MHz	50dB	\$ 9,995
122C	200W CW	.01-220 MHz	53dB	\$ 12,950
134C	500W CW	.01-220 MHz	57dB	\$ 20,500
137C	1000W CW	.01-220 MHz	60dB	\$ 28,950

 140C
 2000W CW
 .01-220 MHz
 64dB
 \$ 46,500

 Warranty: Full 18 months all parts. Vacuum tubes 90 days.

 * = Indicates Dual-Band System (coaxial band switching)

The World's Most Complete Line of RF Power Amplifiers

> More Than 200 Standard Models to Choose From

> > INFO/CARD 6

Giga-tronics Synthesized RF Signal Generators

Giga-tronics May Not Be The First Name You Think Of For RF Synthesizers, But It Should Be.

Yes, Giga-tronics is a new name in RF synthesizers.

But this new choice may be your best choice.

Because an RF synthesizer from Giga-tronics is an incredible value. You get proven performance and reliability at a low price, backed by an experienced service organization.

Here are the specifics. Performance.

Check the charts. Giga-tronics offers four instruments, each with its own unique combination of performance and capability.

The 6061A is ideal for accurate and affordable general purpose RF testing.

The 6062A adds the modulation capability you need to generate complex

170

TIL

signals for communications and radar testing.

And the 6080A and 6082A give you the performance and capability to test sophisticated systems accurately and quickly.

It's easy to command the power and capability of each instrument from the front panel. And the low profile, standard rack size and IEEE-488 interface make each instrument ideal for ATE applications.

1056 000 00

500-

٦N

6



Reliability.

1

E1-

The John Fluke Manufacturing Company initially developed and introduced this line of synthesized RF signal generators. To date, thousands have performed

flawlessly in the field. The instruments incorporate selftesting,

5.00

-

-

100

-

-

20

-

Giga-tronics offers you a full line of RF synthesizers with proven performance and reliability at low prices.

2 100 000 001

internal diagnostics and modular design for easy fault isolation. **Service.**

If a problem occurs, our technical support staff can often help you find and fix it over the phone.

If you need to return an instrument for service, we can take care of it at our factory in California, or at one of our worldwide service centers. **Experience.**

Countrad Circ

Granted, Giga-tronics may be a new name for RF synthesizers, but it's a trusted name to microwave test professionals.

Giga-tronics has a 14-year history of building test and measurement gear for the most demanding requirements. We've shipped thousands of instruments for use

Specifications	Giga-tronics 6061A	Giga-tronics 6062A	Giga-tronics 6080A	Giga-tronics 6082A
Frequency Range Switching speed	.01 to 1050 MHz <100 ms	.1 to 2100 MHz <100 ms	.01 to 1056 MHz <100 ms	.1 to 2112 MHz <100 ms
Spectral Purity* Spurious Subharmoni cs	<-60 dBc None	<-54 dBc <-45 dBc	<-100 dBc None	<-94 dBc <-45 dBc
Phase Noise* @ 20 kHz offset	<-117 dBc/Hz	<-110 dBc/Hz	<-131 dBc/Hz	<-125 dBc/Hz
Residual FM* (Bandwidth)	<12 Hz (.5 to 3 kHz)	<24 Hz (.5 to 3 kHz)	<1.5 Hz (.3 to 3 kHz)	<3 Hz (.3 to 3 kHz)
Output Range* Accuracy Reverse Power Protection	+13 to -147 dBm ±1 dB >127 dBm 50 Watts/50 Vdc	+13 to -147 dBm ±1.5 dB >-127 dBm 25 Watts/25 Vdc	+17 to -140 dBm ±1 dB >127 dBm 50 Watts/50 Vdc	+13 to -140 dBm ±1 dB >-127 dBm 25 Watts/25 Vdc
Amplitude Modulation Depth Distortion @ 30%	0–99.9% <3%	0–9 9.9% <3%	0-99.9% <1.5%	099.9% <1.5%
Frequency Modulation Max. Deviation* Distortion	100 kHz <1%	400 kHz <1%	4 MHz <1% @ 50% Dev.	8 MHz <1% @ 50% Dev.
Phase Modulation Max. Deviation*	NA	40 Rad.	40/400 Rad.	80/800 Rad.
Pulse Modulation On/off Rise/fall time Minimum Pulse Width	NA	>80 dB <15 ns <2 µs	>40/60 dB <15 ns (Typ 7.5 ns) <30 ns	>80 dB <15 ns (Typ 7.5 ns) <30 ns
Internal Modulation Source Level Range Waveforms Programmable	400, 1000 Hz NA Sine Yes	100, 1000 Hz NA Sine Yes	0.1 Hz to 200 kHz 0 to 4 Vpk Sine/Sq/Tri/Pulse Yes	0.1 Hz to 200 kHz 0 to 4 Vpk Sine/Sq/Tri/Pulse Yes
Memory Locations (NVM)	50 Full Function	50 Full Function	50 Full Function	50 Full Function

*Specifications for the 6061A and 6080A are at 1 GHz, and specifications for the 6062A and 6082A are at 2 GHz. Phase noise is typical for the 6061A and 6062A.

in testing communications, radar and EW systems.

Value.

What makes a Giga-tronics RF Signal Generator such an incredible value is its blend of proven performance and reliability at a low price.

Take a closer look at Giga-tronics. The new choice for RF synthesizers may be your best choice.

Call us toll free at 800 726 GIGA (4442). We'll send you more information and arrange for a demonstration.

Giga·tronics

Giga-tronics Incorporated 4650 Norris Canyon Road San Ramon, California 94583 Telephone: 800 726 4442 or 510 328 4650 Telefax: 510 328 4700 INFO/CARD 7





The Ultimate Field Sensing Probe System exclusively from Electro-Metrics

The new EM-4420 Isotropic Field Sensing Probe System from Electro-Metrics offers innovative and improved features for electric field measurement.

The EM-4420 has exceptional dynamic range of 0.5 V/m to 300 V/m, which can be obtained without a probe or range change. This wide measurement capability makes it ideal for high level field tests found in military and automotive test applications, or low level fields as found in consumer electronics and medical instrumentation test applications.

Features include interference free fiber optic data transmission direct to an ISA-BUS plug-in card, PC/AT and DOS/Windows compatibility with a DOS linkable object module and Windows dynamic link library, removable and rechargeable battery, all at a lower cost.

For a prompt response and more information regarding this and other Electro-Metrics products, call us today at 518-843-2600 or Fax 518-843-2812.



100 Church Street Amsterdam, New York 12010 TEL: (518)843-2600 FAX: (518)843-2812 TWX: 710-446-4798

INFO/CARD 8



Established 1978

President — Argus Business Jerrold France

Editorial and Advertising Offices 6300 S. Syracuse Way, Suite 650 Englewood, CO 80111 (303) 220-0600 Fax: (303) 267-0234

Vice President and Group Publisher David Premo

Editor and Associate Publisher Gary A. Breed

Technical Editor Andrew M. Kellett

Associate Editor Jennifer A. Collins

Consulting Editor Andy Przedpelski, The Shedd Group

Editorial Review Board Madjid A. Belkerdid, Univ. of Central Florida Alex Burwasser, RF Products Dave Krautheimer, MITEQ, Inc. Ed Oxner, InterFET Corporation Jeff Schoenwald, Rockwell International Raymond Sicotte, American Microwave Corp. Robert J. Zavrel, Jr., Metricom

Corporate Editorial Director Robin Sherman

Account Executives Jessica Caid Jeff Gordon Henderson Mik Tisha Hill Cin

Jeff Peck Mike Henry Cindy Solomonson

Vice President — Special Advertising Drew DeSarle

Vice President — Production and Promotion Cherryl Greenman

Production Manager Jenny Tague

Reprints Manager Vivian Peterson

Vice President — Marketing Research Director Tina D'Aversa-Williams

Vice President — Circulation Doug Florenzie

Creative Director Brian Buxton

Art Director Pamela Bobe

Staff Artist Susumu Komatsu

List Rental Manager Etta Davis

Argus Business Corporate Offices 6151 Powers Ferry Rd., N.W. Atlanta, GA 30339-2941 Tel: (404) 955-2500



BPA

President — Argus Inc. Scott Smith Vice President, Finance — Argus Inc. Wayne Otterbourg, C.P.A. Senior Vice President — Argus Inc. Arthur E. Sweum

sident — Argus Trade Shows nnis Corcoran

New RF Amplifier New Performance Features Traditional ENI Reliability



ENI's 6100 Amplifier offers new performance features and solid state reliability for EMC and broadband component testing, communications transmission, ATE, and general laboratory use:

- □ 51 dB Class AB Linear Gain.
- Automatic Level Control maintains power output over a 30dB range with ±0.3dB flatness.
- Internal Microprocessor Control provides forward and reflected power readouts with 1W resolution.
- Standard IEEE and RS232 / 422 Interfaces for easy link-up to your system components.

ASK FOR OUR NEW CATALOG! For complete technical information on the 6100/630L,* contact the ENI office nearest you.



World Headquarters

ENI, A Division of Astec America, Inc. 100 Highpower Road, Rochester, NY 14623 USA Tel: (716) 427-8300, FAX: (716) 427-7839 *Also Available Model 630L: 30W Class A output, 400 to 1000MHz

Sales & Service Offices Santa Clara, CA Welwyn Garden City, UK Gerlingen, Germany Tokyo, Japan Osaka, Japan

Subscription inquiries: (708) 647-0756

INFO/CARD 9



April

RF calendar

March 20-24 The 11th Annual Review of Progress in Applied **Computational Electromagnetics** Monterev, CA Information: Ray Luebbers, Department of Electrical Engineering, Pennsylvania State University, University Park, PA 16802. Tel: (814) 865-2362. Fax: (814) 865-7065. 21-23 **Nepcon Electronics** Birmingham, England Information: Reed Exhibition Companies, 383 Main Avenue, Norwalk, CT 06851, Tel: (203) 840-5398. Fax: (203) 840-9398. 26-29 **Fifth IEE Conference on Telecommunications** London, UK Information: ICT 95 Secretariat, IEE Conference Services, Savoy Place, London WC2R 0BL, UK. Tel: 44-071-344 5478/5477. Fax: 44-071-497 3633. 28-31 Internepcon/Microelectronics Indonesia Jakarta, Indonesia Information: Reed Exhibition Companies, 383 Main Avenue, Norwalk, CT 06851. Tel: (203) 840-5398. Fax: (203) 840-9398. 28 - 2995 Mid-Lantic Electronics Show and Conference King of Prussia, PA Information: Judith Ginsberg, Show Manager. Tel: (610) 828-2271. 3-8 Hannover Fair 95 Hannover, Germany Information: Hannover Fairs USA, Inc. 103 Carnegie Center, Princeton, NJ 08540, Tel: (609) 987-1202. Fax: (609) 987-0092. 11-14 Internepcon/Semiconductor Korea Seoul, Korea Information: Reed Exhibition Companies, 383 Main

Avenue, Norwalk, CT 06851. Tel: (203) 840-5398. Fax: (203) 840-9398.

19-21 4th International Conference & Exhibition on **Multichip Modules** Denver, CO

Information: International Symposium on Multichip Modules 95, Conference Management, ISHM-The Microelectronics Society, 1850 Centennial Park Drive, Suite 105, Reston, VA 22091. Tel: (800) 535-ISHM or (703) 758-1060. Fax: (703) 758-1066.

23 - 26**IEEE Instrumentation/Measurement Technology** Conference Waltham, MA

Information: Robert Myers, 3685 Motor Ave., Suite 240, Los Angeles, CA 90034. Tel: (310) 287-1463. Fax: (310) 287-1851. or Dan Sheingold, Analog Devices, P.O. Box 280, Norwood, MA 02062. Tel: (617) 461-3294. Fax: (617) 329-1241.

14

Don't fade away



Rely on **Marconi 2050** digital and vector signal generator: the first with built-in Rayleigh and Rician fading simulation.

High buildings, cars, trees...they all cause fading problems for communications systems. The problem is that realistic testing means replicating real-world conditions: and that's always needed expensive, specialist equipment.

Now there's the new Marconi 2050 series. It's the first-ever generator with a built-in Rayleigh and Rician fading simulator, allowing receivers to be tested under realistically adverse conditions.



The 2050 series is highly versatile, with comprehensive IQ modulation facilities plus the ability to test new digital systems including TETRA and APCO 25. Covering an exceptionally wide carrier frequency range from 10 kHz to 5.4 GHz with the 2052 - it maintains a high standard of accuracy and stability. The flexible operator interface and large clear back-lit display, ensure simplicity of control and ease of use.

Choose a one-box solution for testing receivers: get the Marconi 2050 in focus.

Call your local office for more information.



Marconi Instruments Ltd, Longacres, St Albans, Herts AL4 OJN, England. Telephone: 01727 859292 or (UK only) free on 0800 282388 Fax: 01727 857481

Marconi Instruments worldwide: Australia Tel (02) 638-0800 Fax (02) 638-3131 Benelux Tel (013) 63-95-40 Fax (013) 63-96-63 France Tel (1) 60-77-90-66 Fax (1) 60-77-69-22 Germany Tel (089) 84936-0 Fax (089) 841-9142 Hong Kong Tel (852) 2-832-7988 Fax (852) 2-834-5364 Latin America (Florida) Tel (305) 491-4188 Fax (305) 928-2801 Singapore Tel (65) 381-1470 Fax (65) 281-0113 Spain Tel (91) 372-98-75 Fax (91) 307-69-39 USA Tel (201) 934 9050 Fax (201) 934 9229 RUGGED CONSTRUCTION passes MIL-M-28837 shock and vibration tests. AUTOMATED ASSEMBLY for low-cost and 1 week shipment guaranteed!

4.5 SIGMA REPEATABILITY

ALL-WELDED INTERNAL CONSTRUCTION withstands up to 240°C for 5 min.

ALL CERAMIC PACKAGE cover pull strength in excess of 20 lbs.

SURFACE MOUNT .28"x.31" board area. Available in tape and reel.

> ULTRA-REL™ MIXERS 5 YEAR GUARANTEE

J-LEAD

improves reliability of the solder connection. Leaching and thermal stress is significantly reduced.



Mini-Circuits RF/IF Surface Mount Designer's Guide features 48 pages of the most up-to-date and complete product and specification information about Mini Circuits surface mount components. The RF/IF Microwave Handbook is packed with 740 pages of articles, selection guides and detailed specifications for Mini-Circuits components.

Call, write or fax for your free Surface Mount Designer's Guide and Handbook today!

J-LEAD MIXERS UNPRECEDENTED IN VALUE.



Mini-Circuits JMS mixers are at the forefront of the industry for performance, reliability and value! With all-welded construction, these low cost ceramic mixers feature the functional J lead designed for strain relief...and set the pace for ruggedness required to go through surface mount reflow soldering and aqueous wash.

From cellular to satellite applications, this is the tough, reliable surface mount mixer you demand! JMS...from Mini-Circuits!

Mini-Circuits...we're redefining what VALUE is all about!

SPECIFICATIO	NS			Midban	d (dB, '	Гур.)		
	LO	Freq.	(MHz)	Conv.	Isc	si.	\$ea.	
Model	(dBm)	LO/RF	IF	Loss	L-R	L-I	(qty. 1-9)	
JMS-1	+7	2-500	DC-500	5.75	45	45	4.95	
JMS-1LH	+10	2-500	DC-500	5.75	55	45	8.45	
JMS-1MH	+13	2-500	DC-500	5.75	60	45	9.45	
JMS-1H	+17	2-500	DC-500	5.90	50	50	11.45	
JMS-2L	+3	800-1000	DC-200	7.0	24	20	7.45	
JMS-2	+7	20-1000	DC-1000	7.0	50	47	7.45	
JMS-2LH	+10	20-1000	DC-1000	6.5	48	35	9.45	
JMS-2MH	+13	20-1000	DC-1000	7.0	50	47	10.45	
JMS-2H	+17	20-1000	DC-1000	7.0	50	47	12.45	
JMS-2W	+7	5-1200	DC-500	6.8	60	48	7.95	
JMS-11X	+7	5-1900	5-1000	6.7	35	37	4.25*	

Note: *10-49 qty.



P.O Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718)332-4661

or detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER • MICROWAVE PRODUCT DATA DIRECTORY • EEM • MINI-CIRCUITS' 740- pg. HANDBOOK.

CUSTOM PRODUCT NEEDS...Let Our Experience Work For You. INFO/CARD 12

Quality Crafted сизтом & sтоск

Crystals Crystal filters L/C filters Monolithics 12 years manufacturing



MONOLITHIC CRYSTAL FILTER KITS

<u>10.7 MHz</u> <u>21.4 MHz</u> <u>45 MHz</u> Prototyping kits worth their weight in gold to the RF designer.

10.7 MHz & 21.4 MHz kits contain: 3 dB BW (kHz)

2 pole	qty.	4 pole	qty
7.5	2	7.5	2
13	2	13	2
15	2	15	2
30	2	30	2

45 MHz kit contains:

3 dB BW (kHz) 2 pole qty. 7.5 2 15 2 30 2

4 pole	qīy.
7.5	2
15	2
30	2

 Call or FAX now for

 delivery from stock!

 MCFPK-10.7
 \$ 85.00

 MCFPK-21.4
 \$ 95.00

 MCFPK-45
 \$ 125.00

refills available prices subject to change

Temex Electronics, Inc. 3030 W. Deer Valley Rd. Phoenix, AZ 85027



INFO/CARD 13

RF courses

Power Hybrids April 3-5, 1995, Los Angeles, CA Advanced Communication Systems Using Digital Signal Processing April 3-7, 1995, Los Angeles, CA Hybrid Microcircuit and Multichip Module Packaging Technologies April 10-13, 1995, Los Angeles, CA Multichip Module Design April 24-26, 1995, Los Angeles, CA Information: UCLA Extension, Engineering Short Courses, 10995 LeConte Ave., Ste. 542, Los Angeles, CA 90024. Tel: (310) 825–1047. Fax: (310) 206–2815.

Error Correcting Codes/Digital Storage Systems March 27-30, 1995, Palo Alto, CA Plasma Etching: Processes & Technologies April 24-26, 1995, Monterey, CA Information: University Consortium for Continuing Education, 16161 Ventura Boulevard, M/S C-752, Encino, CA 91436. Tel: (818) 995–6335. Fax: (818) 995–2932.

Wireless Digital Communications March 20-24, 1995, Switzerland Information: CEI-Europe/Elsevier, Mrs. Tina Persson. Tel: (46) 122-175-70. Fax: (46) 122-143-47.

Optical Systems Fundamentals March 20-21, 1995, Washington, DC **Modern Optical Systems Design** March 22-24, 1995, Washington, DC The Cellular Telephone System March 27-29, 1995, Washington, DC **Spread Spectrum Communications Systems: Commercial and Government Applications** March 27-31, 1995, Washington, DC **Global Positioning System: Principles and Practice** April 3-6, 1995, London, UK Video Communications: An Introduction April 3-6, 1995, Washington, DC **Communication Satellite Systems:** The Earth Station-A Practical Approach to Implementation April 10-13, 1995, Washington, DC **Satellite Communication Engineering Principles** April 18-21, 1995, Washington, DC Information: The George Washington University, Continuing Engineering Education, Academic Center, Room T-308, 801 22nd Street, N.W., Washington, DC 20052. Tel: (202) 994-6106 or (800) 424-9773. Fax: (202) 872-0645.

Wireless and Mobile Networks: From Theory to Practical Implementation March 27-28, 1995, Denver, CO

Information: Lori Milhaven, Project Leader, International Institute for Learning, 110 East 59th St., Sixth Floor, New York, NY 10022-1380. Tel: (800) 325–1533 or (212) 758–0103. Fax: (212) 909–0558.

DSP Without Tears

April 5-7, 1995, San Jose, CA April 24-26, 1995, Chicago, IL Information: Z Domain Technologies, Inc., 325 Pine Isle Court, Alpharetta, GA 30202. Tel: (800) 967–5034, (404) 587–4812. Fax: (404) 518–8368.

FACTORY DIRECT!



INFO/CARD 40

P.O. BOX 60017 • FORT MYERS, FLORIDA 33906

1-800-JAN-XTAL

New Research Center to Enliven US Share of **Electronics Market**

Partners in a new \$40 million engineering research center expect to help rebuild the US share of the world electronics market by making dramatic breakthroughs in ultra lowcost, smaller and more powerful electronics. Established at the Georgia Institute of Technology and supported by the National Science Foundation, the Low-Cost Electronics Packaging Research Center will also blaze a trail for enhanced collaboration between industry and universities. Thirty-five companies from all segments of the U.S. electronics industry have expressed interest in participating in the research and education efforts.

The United States leads the world in developing new technologies, but companies in other nations often turn these developments into profitable consumer products and dominate the resulting markets. To maintain or expand their business, US manufacturers will have to compete in the low-cost electronics product market, now dominated by other nations. Development of new products and the restoration of lost markets should mean more jobs in the United States. If US companies can increase their market share from 33 to 40 percent by the year 2004, two million new jobs could be added in electronics manufacturing and another two million in support industries.

Companies participating in the center's work will pay to share the knowledge generated in some or all of the technology areas. Support for the center will come over the next ten years in matching amounts from the National Science Foundation, the State of Georgia, the industry partners, the Department of Defense and Sematech.



- · Covers octave + bands from 1.5MHz to 1GHz.
- 50Ω building block.
- · Frequencies are digitally tuned from the front panel or RS232.
- · High reliability, solid state design - no servo-mechanical part.



5530 UNION CENTRE DR. / WEST CHESTER, OH PHONE (513) 870-9060 / FAX (513) 870-9064

INFO/CARD 16

С 0 R

1994 US Electronics Factory Sales Total \$342.7 Billion

Factory shipments of electronics equipment, components, and related products totaled \$342.7 billion for year-end 1994, representing an increase of more than 13 percent over 1993's sales of \$303.2 billion, according to preliminary data released by the **Electronic Insdustries Association** (EIA). Telecommunications manufacturing led industry growth in 1994 with \$53.4 billion in sales, up 29 percent over 1993. The electronics components sector totaled \$87 billion, up 19.3 percent. Computers and peripherals showed healthy improvement, hitting \$70.7 billion for year-end 1994, up 17 percent from year-end 1993. Consumer electronics grew by 7.8 percent, electromedical equipment by 2 percent, and other related products improved slightly, with a growth of 2.9 percent over 1993. Only one sector fell during the reporting period. The defense communications area had total sales of \$28.9 billion, a loss of 6.9 percent from the 1993 sales of \$31 billion.

Call for Papers

The Advanced Technology Acquisition, Qualification, and Reliability workshop is calling for papers for the August 15-17, 1995 workshop in Newport Beach. Topics of interest include advanced packaging concepts, multichip modules, generic qualification, chip/system reliability, radiation effects, fabrication line certification, testability and self test (BIT/BIST). GaAs space qualification, acquisition changes, known good die, and plastic packaging. Authors should submit five copies of a one-page abstract to the workshop coordinator by May 31, 1995 for review by the program committee. Abstracts should include author's name, complete address, and telephone number. Abstracts will be selected based on technical merit, supporting test results, and overall suitability to advanced silicon and GaAs technology issues. Abstracts should be sent to Dorothy Connor, Workshop Coordinator, General Technical Services, Inc., 3100 Route 138, Wall Township, NJ 07719, tel: (908) 544-3231, fax: (908) 389-3992.

NIST Seeks Improved Semiconductor Competitiveness

NIST's Manufacturing Extension Partnership, in cooperation with the

PORATI

0 N

troducing the PLLatinum™ family of PLLs—the world's quietest frequency synthesizers.

ather than make a lot of noise about our new single and dual PLLs, we're reping it quiet—as low as -169dBc/Hz to be exact. What does come through ud and clear is their meager power consumption, 2.7V—5.5V V_{cc} range, htning-fast lock times, and 16- and 20-pin packaging options. They're ideal r everything from analog and digital cellular to advanced cordless to CATV arigns. If you think all this sounds good, check out the offer. It's golden. Ir a free sample and product selection guide, call **1-800-NAT-SEMI, Ext. 361**.



Ultra-low phase noise floor says it all.

	LMX1501A	LMX1511	LMX2314/15	LMX2320	LMX2325	LMX2330	LMX2331	LMX2332
Input-Main PLL	1.1GHz	1.1GHz	1.2GHz	2.0GHz	2.5GHz	2.5GHz	2.0GHz	1.2GHz
Input-Aux PLL						510MHz	510MHz	510MHz
(typ) @3V	6mA	6mA	6mA	12mA	14mA	15mA	14mA	8mA
werdown (typ)	N/A	N/A	30µA	30µA	30µA	1µA	1µA	1μΑ

995 National Semiconductor Corporation. PLLatinum is a trademark of National Semiconductor Corporation. All rights reserved

In Germany call 49-81-411-030, Hong Kong 852-737-1600, Japan 043-299-2300.



RF news continued

Department of Commerce's Bureau of Export Administration and the Department of Energy's National Laboratories System, has established a consortium to reduce manufacturing costs and improve the worldwide marketability of I/O pins. The pilot effort hopes to strengthen the competitive position of the US semiconductor industry. The new NIST-led consortium will seek ways to improve energy efficiency; pin cleaning and finishing methods; manufacturing processes; sources of long-term financing; technical training; cooperative buying methods; and supplier relations. Companies who join the consortium are also asked to sign cooperative research and development agreements with NIST.



Call for Papers

The International Conference on **Electromagnetics for Advanced Appli**cations now invites submissions of papers addressing all kinds of advanced applications. Suggested topics are electromagnetic measurements; electromagnetic modeling of devices and circuits; electromagnetic packaging; electromagnetic properties of materials; EMC/EMP; frequency selective surfaces; inverse scattering; mathematical models and simulation; microwave antennas; phased and adaptive arrays; printed and conformal antennas; radar cross section and asymptotic techniques; radar imaging; radomes; and random and non-linear electromagnetics. Authors should send four copies of a 1-2 page summary for consideration by March 31, 1995. Abstracts should be sent to Professor Mario Orefice, Dipartimento di Elettronica, Politecnico di Torino, Corso Duca degli Abruzzi 24, 10129 TORI-NO, Italy.

CDMA Group Begins International Expansion

The CDMA Development Group has created a new international working group within the organization to address CDMA development issues outside the US. Through this new working group, manufacturers, carriers, and government entities can participate in the CDG efforts. As part of the new international group, the CDG has already formed a Korean working group and is currently discussing membership with carriers and manufacturers in other areas, including countries in Southeast Asia, South America, the Middle East, North America, and Europe. The CDG group will also publish specifications, requirements, documents, and testplans that the group has developed over the last year. The CDG recently completed a specification for higher data rate 13 kbps voice coding.

Business Execs Lead the Pack in Cellular Use

Business leaders under the age of 35 have embraced the power of cellular communications faster than their elders, according to a recent survey by Ameritech. Seven out of ten business executives under 35 own or use cellular phones, compared with six out of ten executives aged 35-54, and four of ten executives aged 55 and older.

MARCH 1995

1-800-366-2266



Low Cost Surface Mount Transformers

Broad product offering of impedance matching devices. 10 MHz -2.5 GHz. Small size (0.15 in. / 3.81 mm sq.) ETC Series transformers are designed for communication applications. Balun transformer steps up or down impedances or transitions from balanced to unbalanced systems. ETC Series

M/A-COM, Inc. 1-800-366-2266 CIRCLE READER SERVICE NO.60



New 3-Piece SMA Connectors Fewer component piece parts and crimpable center contacts reduce installation costs up to 70%. Stainless steel construction ensures reliable, consistent performance. These connectors are available for flexible RG/U and double braided RD-316 cables .They can be crimped using industry standard tooling.

CIRCLE READER SERVICE NO.59

M/A-COM, Inc.



Nomex Braided Test Cables with Interchangeable Connectors

DC - 18 GHz cables with VSWR 1.15:1, 7mm connectors and 1.25:1 N, SMA, ETNC or 35 mm connectors (male / female). Field replaceable interfaces allow variable connector combinations. Tapered boot design provides strong junction without decreasing flexibility. Standard and custom length assemblies available.

M/A-COM, Inc. 1-800-366-2266

CIRCLE READER SERVICE NO.61



Square Outline Surface Mount PIN Diode

Square surface mountable PIN diode in a non-rollable, metal electrode leadless faced (MELF) package. Designed for lower loss and lower distortion in moderate power 2-100 watt TR switches used in VHF through L-band radios and cellular systems. The MA4P1250 has $R_S > 0.5$ ohms and harmonic distortion -90 dBc typ. @ 30 watts. P/N MA4P1250 series

M/A-COM, Inc. 1-800-366-2266

CIRCLE READER SERVICE NO.62

Perhaps Trying To Put Our Entire Line Of Base Station Components Into One Ad Wasn't Such A Good Idea.

No one gives you more design choices than M/A-COM when it comes to building the wireless infrastructure that today's marketplace domands. We're talking about hundreds of different. proven products, already hard at work in base stations around the world.

However, these days you're looking for more than a supplier. You want a strategic

partner who is already working on solutions for the microcell- and picocellbased systems of tomorrow.

That's exactly what you'll find at M/A-COM. We're

investing millions of dollars annually to develop the next generation of sophisticated base station components.

From discretes to integrated

nodules and r

transistors, power nulti-channel linear power amplifiers.

Our unique combination of talent, drive and experience has helped make M/A-COM the world's largest independent designer and manufacturer of RF, microwave and millimeter wave semiconductors, components and subsystems.

M/A-COM products range from discretes to ICs; from connectors to cable assemblies; from isolators and circulators to filters and attenuators. And, as you can see above, much, much more.

Of course, this is proof that a single ad just can't handle everything

we could tell you about our base station components. Which is why we also make lots of big, thick, sturdy catalogs. To get yours, or simply to learn more about us, call M/A-COM today at 1-800-366-2266, or contact the distributor nearest you. For information in Europe, call +44 (0344) 869 595. In Asia, +81 (03) 3226-1671.



INFO/CARD 19



Components for traditional base stations, plus microcells and picocells

Business Briefs

MacNeal-Schwendler and NASA Langley Sign Cooperative Technology Transfer Agreement – The MacNeal-Schwendler Corporation has signed a cooperative agreement with NASA-Langley Research Center for the inclusion of NASA's Finite Element Interface Technology into MSC/NASTRAN. The agreement will lead to the implementation of the technology in MSC/NASTRAN.

Vari-L Announces Results of 1994 Customer Order Analysis – Vari-L Company has published its analysis of 1994 customer orders. Total commer-



cial orders increased 59 percent, while military orders declined 2 percent. 1994 commercial orders represented 63 percent of the total, up from 51 percent from 1993. Domestic orders dropped from \$6.66 million to \$6.1 million. The overall decrease in domestic orders is attributable to a 24 percent decrease in military orders that was offset by a 14 percent increase in commercial orders.

Jay-El Products Acquires Dynatech Microwave Technology – Jay-El Products, Inc. has acquired the assets of Dynatech Microwave Technology, Inc., a manufacturer of electromechanical switches and microwave/ RF components. The company will now be the DMT division of Jay-El Products, and will move its manufacturing operations to Carson, CA.

World's First High Temp Superconductor Transformer to be Built by American Superconductor and ABB – The world's first transformer to use high temperature superconductors will be designed and built by ABB, with technology developed by American Superconductor Corporation. The development is a significant step toward HTS transformers that are expected to constitute a worldwide market of several billion dollars per year.

AEG and Andrew Join Forces to Develop Radar-Based Automatic Train Controls – AEG Transportation systems, Inc, and Andrew Corporation have teamed up to develop a communications-based advanced automatic train control system. When completed, the spread spectrum radio-based system could replace the traditional track circuit approach which employs electrical track shorting for vehicle detection, positioning, and speed code transmission.

Ericsson Unveils Smallest Digital Cellular Phone – The world's smallest digital cellular telephone was introduced by Ericsson, Inc. at the Winter Consumer Electronics Show in Las Vegas, January 6-9. Called the DH338, the digital phone weighs 6.9 ounces and is completely menu-driven. The DH338 takes advantage of TDMA, and operates in both digital and analog modes so that it can be used by all cellular phone customers.

ENGINEERING SUPPORT ...WHEN YOU NEED IT!

Merrimac Design Engineers Are Always Available To Answer Your Questions. So Call 1-800-575-1301

...And Talk To Somebody Who Speaks Your Language (not somebody's voicemail)





INFO/CARD 21



HIGH RELIABILITY, COMMERCIAL QUALITY

♦ 1.8 to 30 MHz ♦ 1500 to 10,000 Watts

HENRY HF Power Amplifiers have been the reliability standard for 30 years. Thousands are in use at commercial, government, and military installations around the world.

If you require trouble-free, 24-hour-per-day, year-round operation, call or write today for prices and specifications.



RF news continued

Contracts

Xircom and NEC Announce Technology Agreement – Xircom, Inc. and NEC Corp. have signed a joint licensing agreement providing Xircom Netwave wireless networking technology to NEC to develop and manufacture wireless LAN chipsets. Xircom grants NEC rights to develop and market wireless LAN chipsets for customers developing wireless LAN products.

Rohde & Schwarz Sells Trunked Radio System to Fire Brigade of Damascus – The Fire Brigade of Damascus will take delivery of a modern trunked radio system, the first of its kind to be installed in the region. The system will be supplied and installed by R&S BICK Mobilfunk, a German daughter company of Rohde & Schwarz.

Motorola Wins \$23 Million Contract for Malaysia's First Digital Cellular System – Motorola's International Cellular Infrastructure Division has been awarded a \$23 million contract to install the base station system for Malaysia's nationwide Global System for Mobile Communications Network. It will be the first fully digital cellular network in Malaysia.

Conductus Awarded Navy Contract for Superconductive Geophysical System – Conductus Inc. has been awarded a contract by the Navy to develop a geophysical surveying system based on high-temperature superconducting magnetic sensors. The project spans two years with a total funding of about \$.75 million.

PCS Group Signs Agreement with Ericsson for PCS Equipment – The PCS Group has signed an agreement with Ericsson Radio Systems to supply Personal Communications Services network equipment for its clients. The agreement enables the PCS group's clients to obtain timely delivery of Ericsson Equipment.

Northern Telecom Orders \$1.4 Million in Test Equipment from Tektronix – Northern Telecom has ordered \$1.4 million in test equipment from Tektronix, Inc. Northern Telecom will use the equipment to produce its new comprehensive PCS system.

INFO/CARD 23



Specify NEC Power FETs — You'll see the difference overnight

Lead times giving you ulcers? Get relief overnight. CEL stocks Power FETs, including those for your 5.9 to 6.4 GHz C-Band VSAT designs, and we're ready to ship *now*. Available in 4 1/2, 9 and 18 Watt versions, these NEC devices are package compatible with other suppliers' parts — and more: They'll give you more power out, better linearity, higher efficiency, *or all three*. So when you need Power FETs, spec the parts with better specs, and get on-time delivery from onshore stock.

For data sheets, call your nearest CEL Sales Office, or circle the number below.



IN STOCK, AVAILABLE, AND MORE THAN EQUAL TO THE JOB



CEL California Eastern Laboratories

CEL Headquarters 4590 Patrick Henry Drive, Santa Clara, CA 95054-1817; (408) 988-3500 FAX (408) 988-0279 Santa Clara, (408) 988-7846 Los Angeles, CA (310) 645-0985 San Diego, CA (619) 450-4395 Bellevue, WA (206) 644-3307 Richardson, TX (214) 437-5487 Olathe, KS (913) 780-1380 Woodridge, IL (708) 241-3040 Cockeysville, MD (410) 667-1310 Middleton, MA (508) 762-7400 Hackensack, NJ (201) 487-1155 Palm Bay, FL (407) 727-8045 Clearwater, FL (813) 538-0706 Snellville, GA (404) 978-4443

RF industry insight

Market Demanding Real Usefulness of RF-Linked Data Devices

By Andy Kellett Technical Editor

Ten years ago fax machines and cellular phones were technological exotica used only by people who could really see a monetary benefit from using them. Will RF-linked data devices follow the history and fax machines and cellular phones and become ubiquitous, or will they remain the tools of a few specialized users?

According to Brian Button, Vice President of Marketing for RF modem maker Proxim, the markets into which his company sells, "... are all markets where there is a large payback in being mobile and networked." Button cites wireless patient record keeping as an example, "you can measure the time and money saved by not having to reenter patient information." Wireless meter reading is another area where RF-linking makes economic sense. "They get more data, more accuracy, and it's cheaper than a meter reader, says Morris Engelson, an RF Engineer for American Meter Co. Button notes that wireless technology can even increase revenues by bringing the point of sale to customers. For instance, "You can move the beer cart out to the pool," says Button.

Market Potential

Will more broad markets emerge for wireless data links? "That really is the \$64,000 question in our industry," says Proxim's Button.

The key to acceptance of wireless data links, according to Earl McCune Jr, a consultant in the RF communications field, is, "Cost, cost, cost." McCune says that while the price of RF devices is coming down as compared to RF devices in the past, the most important comparison is between RF devices and the wired devices with which they compete.

The expansion of wireless data transmission out of niche markets depends not only on bringing down price, but also on changing user behavior says Proxim's Button. An application often predicted for wireless LANs is networking during meetings. "Right now you really don't see too many people going to meetings and taking notes on their notebook PCs," says Button, "that may be different in two or three years."

Technological Issues

A protocol for wireless data transmission is currently being developed by the IEEE's 802.11 committee. While not yet complete, it is known that the standard covers transmission by infrared, direct-sequence spread spectrum, and frequency-hopping spread spectrum. The protocol also specifies two data rates, 1 Mbps and 2 Mbps. "People are really going to have to stretch to reach that 2 Mbps," says McCune. According to McCune data rates are currently being constrained by the spreading required to get the processing gain required by FCC regulations. "To get the processing gain requires spreading the signal all the way to the band edges," says McCune.

Range versus power consumption is another characteristic that manufacturers are working to improve. Reduction of intermodulation products by increasing the intercept points of the analog portions of data radios, "is happening very nicely," says McCune, "unfortunately most of that comes at the expense of power consumption."

Meet the PC Card

As more RF engineers help design devices to be used with portable computing devices, more come into contact with the PCMCIA (Personal Computer Memory Card International Association) standard. Recently renamed PC Card, this standard specifies an interface whose function is analogous to that of ISA or EISA bus standards. Mechanically, cards come in three sizes, type I (3.3 mm thick), type II (5.0 mm thick), and type III (10.5 mm thick). Most wireless PC Card devices use "extended" cards, which use a Many of the wireless applications for use with personal computers will take the form of PC Cards (see sidebar). Wireless LAN cards, pagers and other RF devices are being designed to fit in the slim form of a PC Card. The problem some of these manufacturers have is segregating the digital and RF signals. "Interference is a real problem," says Tom Parrish, editor of *IC Card Systems & Design*, "These guys are all trying to figure out how to control all the signals being transmitted inside the computer."

To help the many non-RF engineers designing RF functions into their products, some RF companies are selling transmitting and receiving modules that are almost "plug and play". "That was the main focus for the development of the ASH receiver and HX transmitters," says Frank Perkins, Vice President of Marketing for RF Monolithics. "These have all the RF guts in them, you put data in and get modulated RF out for the HX transmitters, and for the ASH receiver you put RF in and get data out." says Perkins.

RF-linked data devices have yet to break out of niche applications, but the demand for mobile computing, and the increasing ease with which system designers can incorporate RF functions, may change that soon. *RF*

"bubble" attached to the end of the card. The "bubble" contains some of the bulkier RF components which will not fit in the actual thin card. The standard also specifies pin assignments for the PC Card's 68-pin connector. Electrically, the PC Card standard allows both 5 V and 3.3 V operation, with a mechanical key to prevent placing a low-voltage card in a high voltage slot. In the past, PC Cards used eight- and sixteen-bit busses, limiting their speed, but the latest revision of the standard features a 32-bit bus called CardBus.

FINALLY! 3VOLT BADDEN BADDELESS FOR HANDHELD WIRELESS PRODUCTS

NEC'S NEW LOW CURRENT SILICON ICS not only reduce power consumption in your 3 Volt designs, they reduce the parts count, improve the reliability, and simplify the assembly. NEC is committed to 3 Volt Silicon technology; these parts are just an introduction.

There are more on the way — soon! If 5 Volt ICs are the solution, NEC has a wide

selection of them as well, all available right now.

And don't forget NEC's huge family of discrete devices. Many are characterized at 2.5 Volts and they're available in a variety of packages, including a new ultra-small SMD that's a third the size of a SOT 23!

For a *FREE Product Selection Guide*, call your nearest CEL Sales Office. Or circle the number below.

New 3 Volt NEC Silicon ICs

UPC2745 Ultra Broad Band Amplifier DC to 2.7 GHz 12 dB Gain -1 dBm Psat 7.5 mA lcc

UPC2746 High Gain Amplifier DC to 1500 MHz 19 dB Gain 0 dBm Psat 7.5 mA Icc

UPB1502 Frequency Divider 0.5 to 2.0 GHz Divide by 64/65, 128/129 6 mA Icc UPC2747 Broad Band Low Noise Amplifier 100 to 1800 MHz 12 dB Gain 3.3 dB NF, 5 mA Icc

UPC2748 High Gain Low Noise Amplifier 200 to 1500 MHz 19 dB Gain 2.8 dB NF 6 mA Icc

UPB587 Frequency Divider 50 to 1000 MHz Divide by 2/4/8 5.5 mA lcc

...plus dozens of Bipolar Transistors characterized at 2.5 Volts, including:

f = 1500 MHz NE68519	f = 2.5 GHz NE68030	f = 1000 MHz NE68039
1.3 dB NF	1.90 dB NF	1.0 dB NF
10.0 dB GA	7.2 dB GA	11.6 dB GA
@ only 3 mA Ic	@ only 3 mA Ic	@ only 1 mA lc

Surface Mount packages shown actual size

...and a variety of 5 Volt RF ICs including:

UPC2708	UPC2710	UPC2713	
Wide Band	Wide Band Amplifier	Wide Band	
Amplifier	DC to 1000 MHz	Amplifier	
DC to 2.9 GHz 15 dB Gain 10 dBm Psat	33 dB Gain 3.5 dB NF	DC to 1200 MHz 29 dB Gain 3.2 dB NF	
UPC2723	UPC2721	UPC2726	
AGC Amplifier	Down Converter	Differential	
100 to 1100 MHz	RF = 0.4 to 3.0 GHz	Amplifier	
38 dB AGC	IF = 50 to 600 MHz	400 to 1400 MHz	
13 dB Gain	15 dB Conversion Gain	15 dB Gain	
	NEC		

Typical Performance at 25°C, Frequency Range is 3 dB Bandwidth

CEL California Eastern Laboratories

CEL Headquarters 4590 Patrick Henry Drive, Santa Clara, CA 95054-1817; (408) 988-3500 FAX (408) 988-0279 Santa Clara, (408) 988-7846 Los Angeles, CA (310) 645-0985 San Diego, CA (619) 450-4395 Bellevue, WA (206) 644-3307 Richardson, TX (214) 437-5487 Olathe, KS (913) 780-1380 Woodridge, IL (708) 241-3040 Cockeysville, MD (410) 667-1310 Middleton, MA (508) 762-7400 Hackensack, NJ (201) 487-1155 Palm Bay, FL (407) 727-8045 Clearwater, FL (813) 538-0706 Snellville, GA (404) 978-4443

RF featured technology

Bridge Method for Measuring Amplitude Intermodulation Distortion

By Nina Krikorian Matrix Test Equipment Inc.

This article describes a distortion measurement method that greatly reduces contributions from the signal source and the spectrum analyzer. This method utilizes a bridge technique to cancel the test signals, leaving the distortion products of the device under test (DUT).

For designing and manufacturing multi-channel communication networks, the distortion products of the components must be measured. Distortion in an RF amplifier can be measured with no more than a signal source and a spectrum analyzer. One or more signals are fed into an amplifier and the amplifier output is displayed on the spectrum analyzer. Those signals not present at the input of the amplifier, but which are a result of the signals, are distortions.

There are two critical limitations that make these measurements difficult. The signal sources may not be completely distortion-free. It is often necessary to design separate combining networks with amplifiers and pads to minimize these products. Second, it is often necessary to amplify the signal source before applying it to the DUT, and amplifying a signal inevitably raises the noise level and degrades the signalto-noise ratio.

The spectrum analyzer may generate its own distortion. In many applications the distortion from the spectrum analyzer may be overcome by the use of a bandpass filter that passes only the distortion product of interest. This causes some problems in calibration and is impractical in the case of closely-spaced multiple signals.

The bridge method for making distortion measurements solves these problems. This method is similar to that used in the first part of a feedforward amplifier. The circuitry of both the bridge method and feedforward amplifiers extract only the distortion products. The feedforward amplifier design uses these products to effect distortion cancellation at the output,



Figure 1. Block diagram of bridge setup to cancel source noise.

while the bridge method cancels the test signals at the amplifier output, allowing measurements of only the distortion products.

Implementation

Referring to Figure 1, the input signal (X) is divided by using a 3 dB power splitter. One half of the signal is fed through path A that contains a continuously variable attenuator (L_B) and a line stretcher (Φ_A). The line stretcher is used as a phase shifter. The second half of the signal is fed through path B, which contains a fixed attenuator (L_B) and the amplifier under test (G). The value of the attenuation should be such that the gain in path B is nominally -5 dB, that is 5 dB loss. Although it may not be immediately apparent, the signal-to-noise ratio of the measurement is better when the attenuation is on the input side of the amplifier rather than the output. When measuring high power amplifiers it may be necessary to add attenuation at the amplifier output. The variable attenuator and phase

shifter are now adjusted until the input signals from the source are nulled at the output.

In order to null the signals, a 180° phase shift is required in one path. When testing a non-inverting amplifier, a 180° combiner must be used. Typical nulls of -40 dB can be achieved over 20 percent bandwidth in spite of the fact that the splitters and combiners are not specified to this performance. This is because the variable phase shifter and attenuator compensate for the inherent inaccuracies of the two paths. Actually, a -25 dB null can be attained over decade bandwidths with comparative ease. This suppression not only suppresses the signal, but any other extraneous signals and distortions along with any noise produced by the source.

Although nulls exist whenever the signals are out of phase at the output, the broadest null occurs when the time delays in both paths are equal to each other. It may be necessary to add lengths of cable to one of the paths

Split Personality

To ENGINEERS, we are the performance-price leader

> To OEMs, we are the ultimate in reliability.

The Standard for Performance

For over fifteen years engineers and OEMs alike have relied on PTS frequency synthesizers for unmatched stability, speed and spectral purity. These direct analog and direct digital synthesizers meet the most challenging systems development requirements... ATE systems, satcom, wireless, medical imaging, secure communications, and more. You'll also find them in production environments, where they play a key role in quality assurance.

Our synthesizer models cover the 100 KHz to 1 GHz band with 0.1 Hz



FREE OFFER

resolution. They are available with switching times from 1µsec, spurious outputs as low as -75 dBc and outstanding phase noise characteristics (SSB phase noise at 1GHz, 1 KHz offset, -110 dBc/Hz).

The Standard for Reliability

9999994

PTS synthesizers were designed from the outset to deliver the best reliability in the business. We adhere to conservative derating practices, keep power consumption and internal heat buildup to an absolute minimum and subject finished systems to rigorous temperature cycling and electrical testing. The result: a field-proven 25,000 hr MTBF. Since 1985 we've offered a full 2 year warranty and a flat-rate repair fee of just \$350 for wears 3 through 10.

It's time you had the best of both worlds. The best performance-price and the best reliability. Call today for more information and we'll also send you a free copy of the RF Design Frequency Synthesis Handbook.

Features and Options

- BCD or GPIB remote control
- •DDS with phase-continuous switching
- OCXO, TCXO or external frequency standard
- Resolution to 0.1 Hz
- •Digital phase rotation
- •Output power to +13dBm
- •Proven 25,000 hr MTBF
- •2 yr warranty
- •\$350 repair fee, yrs 3 10 (\$500, Model PTS 1000)



PROGRAMMED TEST SOURCES, INC. 9 Beaver Brook Road, Littleton, MA 01460 Tel: 508 486-3008 Fax: 508 486-4495

Does Your Work Involve Wireless Technologies & Commercial Applications?

IEEE MTT-S International Microwave Symposium/Exhibition May 14-18 1995 in Orlando, FL

Featuring Technical Sessions and Workshops on:

ICs for Wireless Communications

REGISTER

NOW FOR

- Field Theoretical Problems for Wireless Technology
- Microwave Vehicular Technology
- CAD Design Methology for Commercial Applications
- Power Devices and MMICs for Wireless and Military Applications
- EDA Requirements for Wireless Telcom System Design
- Wireless Communication Systems and Technologies
- · Power Amplifiers for Wireless Applications
- Subsystems for Commercial Communications and Auto Applications

In addition, visit the World's Largest Microwave Exhibition, featuring more than 300 industry innovators displaying their newest wireless and commercial products and services.



For more information fill out coupon below and return it to Kelly Fleming Microwave Journal, 685 Canton St., Norwood, MA 02062

Name	Title
Organization	
Address	
City	State Zip
Country	Telephone
Are you an MTT-S member? Yes 🗌 No 🗌	
Have you ever attended MTT-S before? Yes No	How many times?



Figure 2. 20 input signals with their inherent distortion.

because the phase shifter range is limited. It may also be difficult to find the null that produces equal time delay in both paths. To simplify the process of adjusting the circuit for equal time delay and hence produce a broadband null, a sweep signal generator or amplified noise source may be substituted for the signal source. This allows the user to adjust the L_A to equal L_BG and therefore, the resulting equation from Figure 1 will be the difference of the two paths:



Figure 3. The two innermost signals, with the distortion signal between them.

output = path A – path B
output D_A = L_A
$$\left[\frac{\sqrt{2}}{2}\sin(\omega t + \Phi)\right]$$
 (1)
 $-\left[L_BG\left[\frac{\sqrt{2}}{2}\sin(\omega t + \Phi_{Amp})\right] + D_A\right]$

where:

 $X = input signal = sin(\omega t)$ $L_A = loss of variable attenuator$



Figure 4. Spectrum of signal through path B.

 $\Phi_A =$ variable phase shift $L_{B} = fixed attenuator$ G = amplifier gain Φ_{Amp} = amplifier phase shift; and $D_A =$ amplifier distortion

Example

Figure 2 shows the 20 input signals from the signal generator along with its residual distortion. Figure 3 is expanded around the center to show only the two innermost signals and the distortion present in the input signal.

• 25, 50 and 100 WVDC

Commercial Line Capacitors

Low Cost, General Purpose **Multilayer Ceramic Capacitors** For Surface Mount Applications, Manufactured for ATC



0603	NPO	1.0 pF to 470 pF	1210	NPO	220 pF to .010 MFd		
	X7R	470 pF to .022 MFd		X7R	.010 MFd to .33 MFd	NPO X7R and 75U Dielectrics	• Six popular EIA S
	250	.010 MFd to .068 MFd		250	.033 MFd to T.U MFd	• Toleronces: C. D. G. I. K. M. 7	• 25 50 and 100 V
0805	NPO X7R	1.0 pF to 1000 pF	1812	NPO X7R	470 pF to .018 MFd 022 MEd to 1.0 MEd	OUIK PICK 48 Hour Shipment® av	ailable on selected items
	Z5U	.010 MFd to .22 MFd		Z5U	.15 MFd to 1.5 MFd		
1206	NPO	1.0 pF to 4700 pF	2225	NPO	1200 pF to .047 MFd	CALL AIL S COMMERC	ETAL LINE NUMBER
	X7R	1000 pF to .22 MFd		X7R	.033 MFd to 1.5 MFd	(210) 247	-3700
	Z5U	.022 MFd to .47 MFd		Z5U	1.0 MFd to 4.7 MFd	-	

Size

American Technical Ceramics One Norden Lane, Huntington Station, N.Y. 11746 Fax: (516) 547-5748

Dielectric Cap. Value Range

American Technical Ceramics

Size



Figure 5. Spectrum of signal after passage through paths A and B and combination.

This distortion is about 60 dB below the signal level.

Figure 4 is a representation of the signals when the transfer switch position is at 1 (referring to Figure 1). The reference level reading of the signal is taken at this point, and is -33.2 dBm. The insertion loss from the amplifier output to the input of the spectrum analyzer is 3.2 dB. This makes the amplifier output level -30 dBm.

Figure 5 is a representation of the signals after a 40 dB suppression with

the transfer switch at position 2 (referring to Figure 1). The input signals and their distortions, along with any noise present in the input, have been nulled at this point. This has allowed a 20 dB decrease in the RF attenuation of the spectrum analyzer, therefore improving the noise floor. The amplifier distortion is now visible and is 74 dB below the reference signal level.

The distortion products of the signal generator and the spectrum analyzer are no longer a factor in our measurements because the 40 dB suppression of the input signals and the input distortion level of -60 dB is the equivalent of -100 dB distortion levels at the input. At this particular signal level, the spectrum analyzer is not contributing any significant distortion. This is verified by adding attenuation to the input of the spectrum analyzer and observing that no change occurs in the carrier to distortion ratio.

Conclusion

By using this technique, we have alleviated many of the problems encountered while using other distortion measurement methods, such as signal source distortion and noise from the spectrum analyzer. Although the example chosen was for a low level amplifier, the technique is also useful for high level amplifiers and other active devices. Our experience indicates that the bridge method of distortion measurement eliminates the need for bandpass filters. RF

References

 RF/IF Designer's Handbook, Mini-Circuits, 1992.
 Multiple Frequency Comb Generator Handbook, Matrix Test Equipment Inc.

 HP 8560 E Spectrum Analyzer Operating and Programming Manual, Hewlett Packard, 1992.
 C. Rice, "Techniques to Achieve Linear Amplification at HF", *RF Design*, December 1993, pp. 46-49.

About the Author

Nina Krikorian is employed at Matrix Test Equipment Inc. and presently attends Polytechnic University in New York. She can be reached at Matrix Test Equipment Inc., 90-11 Colin Dr., Holbrook, NY 11741, tel: (516) 472–0153, fax: (516) 472–0624.



Noise Com. Broadband Noise Sources for Wireless, Space, Military and Commercial Applications.

Noise Com noise sources and noise subsystems are being used throughout the world to evaluate the performance of commercial and military, radar, satellite communications, and data transmission systems.

Noise Com has established a solid reputation for quality, performance, and product support that is among the most highly regarded in the industry. We have recently enhanced our facilities and equipment to increase the precision of our calibration, measurement, and testing capabilities and we hope that you will benefit from this.

Every Noise Com product is based on the generation of true white Gaussian noise, a result of years of research and testing to produce devices with outstanding stability and quality.

Noise Com routinely designs and manufactures custom components, subsystems, and turnkey systems with on-time deliveries. If you don't see a product here that meets your requirements, just ask for it—call a Noise Com representative for a prompt response.

A Noise Product For Every Application.

For more information and quick response, call NOISE COM, the experts in testing, at 201-261-8797.



IF YOU'RE LOOKING FOR NOISE COMPONENTS,



OR TEST EQUIPMENT,



ALL ROADS LEAD TO...




Chips and Diodes

All Noise Com diodes deliver symmetrical white Gaussian noise and flat output power versus frequency. Noise Com diodes are available in a wide variety of package styles, and in special configurations on request.

TYPICAL STANDARD MODELS

MODEL	FREQUENCY RANGE	
NC 204	0.1 Hz – 500 MHz	
NC 302	10 Hz - 3 GHz	
NC 401	100 MHz – 18 GHz	
NC 406	18 GHz - 110 GHz	



Drop in Modules for BITE

The NC 500 series drop-in noise modules in TO-8 cans are an economical solution for built-in test requirements. These devices contain complete biasing networks and need no external components. Also available are TO-39 and surface mount packages.

TYPICAL STANDARD MODELS		
MODEL	FREQUENCY RANGE	OUTPUT ENR
NC 501/15	0.2 MHz - 500 MHz	31 dB
NC 506/15	0.2 MHz – 5 GHz	31 dB
NC 511/15	0.2 MHz - 500 MHz	51 dB
NC 513/15	0.2 MHz – 2 GHz	51 dB



Broadband Amplified Modules

The NC 2000 series amplified noise modules are an excellent choice when a high level noise output is desired and the noise source is to be mounted on a circuit board. 24 pin packages are standard, 14 pins are available.

TYPIC	AL S	TAND	ARD	MO	DELS
-------	------	------	-----	----	------

MODEL	FREQUENCY RANGE	OUTPUT
NC 2101	100 Hz - 20 kHz	0.15 Vrms
NC 2105	500 Hz - 10 MHz	0.15 Vrms
NC 2201	1 MHz – 100 MHz	+5 dBm
NC 2601	1 MHz – 2 GHz	-5 dBm



The NC 1000 series amplified noise modules produce white Gaussian noise from -14 dBm to +13 dBm at frequencies up to 6 GHz. They are designed for coaxial test systems, and are available with several bias voltages and connector options.

TYPICAL	STANDARD	MODELS
---------	----------	--------

MODEL	FREQUENCY RANGE	OUTPUT
NC 1101A	10 Hz - 20 kHz	+13 dBm
NC 1107A	100 Hz- 100 MHz	+13 dBm
NC 1112B	20 MHz - 2 GHz	0 dBm
NC 1126A	2 GHz – 6 GHz	-14 dBm
		1



Broadband Precision, Calibrated Coaxial

Noise Com's NC 346 series is designed for precision noise figure measurement applications. These products are available with coaxial or waveguide outputs. For OEM applications, the NC 3200 series provides high performance in a small ruggedized package.

TYPICAL STANDARD MODELS

MODEL	FREQUENCY RANGE	OUTPUT ENR
NC 346A	0.01 GHz - 18 GHz	6 dB
NC 346B	0.01 GHz - 18 GHz	15 dB
NC 346D	0.01 GHz - 18 GHz	25 dB
NC 346Ka	0.1 GHz - 40 GHz	15 dB



Broadband Calibrated Millimeter-wave

The NC 5000 series noise sources feature outstanding stability and convenience in waveguide bands up to 110 GHz.

TYPICAL STANDAR	DI	МС	D	EL	S
-----------------	----	----	---	----	---

MODEL	FREQUENCY RANGE	WAVEGUIDE
NC 5142	18 GHz - 26.5 GHz	WR-42
NC 5128	26 GHz - 40 GHz	WR-28
NC 5115	50 GHz – 75 GHz	WR-15
NC 5110	75 GHz – 110 GHz	WR-10



Coaxial with Built-in Isolators

The NC 3400 series are precision calibrated noise sources for extreme accuracy and flatness enhanced by their low VSWR 1.25:1.

TYPICAL STANDARD MODELS

MODEL	FREQUENCY RANGE	OUTPUT ENR
NC 3404	2 - 4 GHz	30-36
NC 3405	4 – 8 GHz	30-35
NC 3406	8 – 12 GHz	28-33
NC 3407	12 – 18 GHz	26-32



BER Testing Equipment

The UFX-BER accurately sets and displays Eb/No, C/N, C/No, or C/I between a user supplied signal and internally generated white Gaussian noise. The UFX-BER can be used for back to back or IF loop-back testing with extreme precision over a broad range of input or output power. Eb/No values can be entered directly from the front panel or by IEEE-488 bus.

TYPICAL STANDARD MODELS			
FREQUENCY RANGE	APPLICATION		
50 MHz - 90 MHz	General		
50 - 90; 100 - 180 MHz	IBS/IDR		
824 MHz - 849 MHz	CDMA		
1800 MHz-1900 MHz	DCS-1800		
	L STANDARD M FREQUENCY RANGE 50 MHz - 90 MHz 50 - 90; 100 - 180 MHz 824 MHz - 849 MHz 1800 MHz - 1900 MHz		



Amplifier Test Station

The UFX-NPR series instruments perform automatic distortion measurements in mobile telephone (CDMA and FDM) base stations, satellite communications systems, CATV, and other equipment operating in multi-signal environments. Some models are available with tunable measurement frequency or with multiple measurement frequencies.

MODEL	FREQUENCY RANGE
UFX-NPR-70	50 MHz - 90 MHz
UFX-NPR-CATV	50 MHz – 1.0 GHz
UFX-NPR-1700	1.6 GHz – 1.9 GHz
UFX-NPR-2400	2.2 GHz - 2.6 GHz
UFX-NPR-11900	10.95 GHz - 12.8 GHz



Broadband Noise Generators

The NC 60%0 and NC 8000 series noise generating instruments are designed for applications on the test bench or incorporated with other equipment to provide a wide variety of functions. Each instrument contains a precision noise source, amplification, and step attenuators to provide repeatable symmetrical white Gaussian noise with variable output power.



The new UFX-7000 series noise generating instruments are extremely easy to use, combining dedicated keys for control of operations and programming, with a large 4 x 20 character LCD display. Control of output power, filter settings, and attenuator step size for both the noise and the signal (for units with internal combiners) is performed from the front panel or remotely using the IEEE-488 interface.

MODEL	FREQUENCY RANGE	OUTPUT POWER
NC 6107	100 Hz - 100 MHz	+13 dBm
NC 6110	100 Hz - 1500 MHz	+10 dBm
NC 6124	2 GHz – 4 GHz	-10 dBm
NC 8107	250 kHz - 100 MHz	+30 dBm

TVPICAL STANDARD MODELS

TYPICAL STANDARD MODELS				
MODEL	FREQUENCY RANGE	OUTPUT POWER		
UFX-7107	10 Hz - 100 MHz	+13 dBm		
UFX-7108	100 Hz - 500 MHz	+10 dBm		
UFX-7110	100 Hz - 1500 MHz	+10 dBm		
UFX-7218	2 GHz - 18 GHz	-20 dBm		
UFX-7909	1 MHz – 300 MHz	+30 dBm		



Noise Com Inc. E. 49 Midland Ave., Paramus, NJ 07652 Tel: 201-261-8797 • Fax: 201-261-8339

Small talk.

Size is everything in today's wireless product market. Ever since the first cellular phone was designed, the big challenges have been how to make them more portable; how to reduce power consumption while extending talk time; and how to add more features.

How do you do it? Simple. With ITT RFIC power amplifiers. Based on our MSAG®-Lite technology, our line of RFIC power amplifiers can help you reduce total system size while adding more features in the same space. Cell phone talk time can be extended by as much as 30% compared to using discretes or modules. In addition, you can lighten up the entire system by reducing the battery weight required to power the phone.

And all this at an *extremely* competitive price.

Small wonder that designers of all kinds of wireless products are talking to us first.

ACTUAL SIZE What about you? Call us at 703-563-3949.



INFO/CARD 30

WR

RF featured technology

Distortion Measurements Using the Spectrum Analyzer

By Morris Engelson Tektronix, Inc.

The instrument most frequently used to measure, display, adjust or test for distortion, especially at RF and microwave frequencies, is the spectrum analyzer. Much published material is available on the use of the spectrum analyzer in distortion measurements. The reader will find some of this material cited in the references. Usually, an article will deal in some depth with one aspect of distortion, such as intermodulation or circuit gain compression. The intent here is to provide a summary overview of many varieties of distortion items associated with spectrum analysis.

The sinewave is usually considered an ideal signal, and any deviation from a perfect sinewave is called distortion. Usually distortion is not wanted. Sometimes, though, the intent is to create distortion in the sense of having a non-sinusoidal signal, such as a pulse or square wave. While the idea of distortion is usually associated with a signal, it need not always be so. Frequently, distortion is used to determine circuit behavior rather than signal content. Any circuit can cause distortion, and that includes the circuits in the measuring instrument. Therefore, accurate distortion measurement should include consideration, or tests, to establish the validity of the result.

Baseband or RF?

Distortion of a modulated signal, or waveform, can occur at audio or baseband prior to modulation, or at RF after modulation. Usually, the measurement is made at the lower frequency either before modulation or after demodulation. But this does not fully show what happens during the modulation process, for example, what level of distortion the modulator introduces. Today, there is no technical reason for not making the measurement at whatever frequency is of interest, with the availability of high frequency resolu-



Figure 1. Modulating signal, fundamental and harmonics spectrum.

tion spectrum analyzers such as the Tektronix 2794 (which was used for the measurements in this paper).

Various items related to signal distortion measurements with the spectrum analyzer, in general, and differences between pre-modulation and post-modulation, in particular, are illustrated below.

Figure 1 shows the spectrum of a 50 kHz sinewave and its harmonics. The 2794 vertical setting is 10 dB/division for an 80 dB screen. Only two harmonics, the second and third, at about 60 dB down are observed. The 50 kHz signal exhibits about 0.1 percent distortion.

Figure 2 shows the spectrum of a 10 GHz carrier amplitude modulated with the 50 kHz signal discussed in Figure 1. The 50 kHz sideband is 14.8 dB below the 10 GHz carrier amplitude, representative of 36.4 percent AM. We also have spectral lines at the second and third harmonics of the 50 kHz modulating signal. These however, are much greater in amplitude than shown in Figure 1. Here the 100 kHz term is only 20 dB below the 50 kHz line rather than 60 dB as in Figure 1. Clearly, the modulating process has changed the relative harmonic levels.

Not only 50 kHz sidebands, but closein spectral terms are easily observed and measured at the 10 GHz carrier frequency. Figure 3 shows a 234 Hz



Figure 2. Modulated signal spectrum at 10 GHz.

tone at 12 dB down, representing 50 percent AM. A closer look using a 10 Hz resolution setting in Figure 4 shows additional modulation terms of 80 Hz.

Harmonic Distortion

Signal harmonics observed on a spectrum analyzer can come from three sources: the original signal, an outside circuit through which the signal passes (such as an amplifier), and the measuring spectrum analyzer. Harmonic distortion caused by a circuit, such as an outside amplifier or the spectrum analyzer input mixer, will be signal-level dependent, while the harmonic content of the original signal will not be amplitude-level dependent. A check for change of harmonic level as a function of signal level is the principal method for distinguishing between circuitcaused versus original-signal harmonic content.

Figure 5 is a dual trace display of the spectrum of a 200 kHz signal (actually 196.6 kHz as measured with the markers). The full screen spectrum analyzer reference level is -20 dBm for both traces. With 10 dB of input RF attenuation, the mixer input level is -20-10 = -30 dBm, and the second harmonic is measured at 68 dB down. With zero dB of input attenuation and a mixer input level of -20 dBm, the upper trace shows a second harmonic almost 10 dB larger. The increase is due to spectrum

MRF166W - Class A, 40 W, 500 MHz, Broadband Power MOSFET



Motorola's rugged 40 watt RF Power MOSFET is designed primarily for wideband large-signal output and driver stages to 500 MHz. The MRF166W's excellent thermal stability makes it ideal for Class A operation. Its push-pull configuration reduces even numbered harmonics. Other features include a 13 dB minimum gain and 50% efficiency at 40 watts. **Richardson Electronics, Ltd.** 400W267 Keslinger Road, LaFox, IL 60147. **1-800-348-5580**.

MRF861 - Class A, 800-960 MHz, 27 W (CW) RF Power Transistor



Motorola's 27 watt (CW) RF power transistor is designed for 24-volt UHF largesignal common emitter, class A linear amplifier applications in industrial and commercial equipment operating in the 800-960 MHz range. Features include a 9.5 dB minimum gain, an output capacitance of 45 pF at 24'Vdc, a minimum ITO of +53.5 dBm and typical noise figure of 6.5 dB. The MRF861 will withstand RF input overdrive of 8 W CW. It is in a push-pull flange package (case 375A).

Richardson Electronics, Ltd.

40W267 Keslinger Road, LaFox, IL 60147 1-800-348-5580.

MRF862 - Class A, 800-960 MHz, 36 W (CW) RF Power Transistor



Motorola's 36 watt (CW) RF power transistor is designed for 24-volt UHF largesignal common emitter, class A linear amplifier applications in industrial and commercial equipment operating in the 800-960 MHz range. Features include a 9 dB minimum gain, an output capacitance of 75 pF at 24 Vdc, a minimum ITO of +55 dBm and typical noise figure of 6.5 dB. The MRF862 will withstand RF input overdrive of 13.6 W CW. It is in a push-pull flange package (case 375A).

Richardson Electronics, Ltd.

40W267 Keslinger Road, LaFox, IL 60147 1-800-348-5580. MRF858 - Class A, 800-960 MHz, 3.6 W (CW) RF Power Transistor



Motorola's 3.6 watt (CW) RF power transistor is designed for 24-volt UHF largesignal common emitter, class A linear amplifier applications in industrial and commercial equipment operating in the 800-960 MHz range. Features include an 11 dB minimum gain, an output capacitance of 6.5 pF (typ) at 24 Vdc, a minimum ITO of +44.5 dBm and typical noise figure of 6 dB. The MRF858 will withstand RF input overdrive of 0.85 W CW. It is in an SOE flange package (case 319).

Richardson Electronics, Ltd. 40W267 Keslinger Road, LaFox, IL 60147 1-800-348-5580.

Depend on Motorola. Count on Richardson. Motorola's Largest RF Distributor

Reliable. Dependable. Knowledgeable. Motorola recognizes the traits of its largest North American RF distributor, Richardson Electronics. For these same reasons, you too can rely on Richardson Electronics for Motorola RF Devices.

Maybe you didn't realize Richardson Electronics has been distributing electronic components for nearly 50 years. As a design engineer we're certain you'll be impressed by our portfolio of RF, microwave and power semiconductors and related components.

RF & Microwave Focus

Because of our specialization on niche markets and products, Richardson has become the world's largest RF transistor distributor. We're Motorola's largest North American RF distributor and the largest worldwide distributor for many other component manufacturers.

Just how have we grown into a \$200 million distributor and reliable resource for design engineers like you?

Inventory

Currently a \$10 million RF semiconductor inventory housed in 14 worldwide stocking locations. In most cases, Richardson can ship the RF, microwave or power semiconductors you need the same day. This extensive inventory also enables us to handle your midstream production increases.

Technical Sales Support

We've brought together sales and marketing people from leading manufacturers in the RF and microwave industry. We're capable of assisting OEMs with new designs as easily as suggesting the proper replacement to service dealers and end users.

Value-added Services

Stocking programs, electronic data interchange, special testing, selecting, matching and bar coding are available. Richardson routinely provides the extra services you demand.



Bichardson Electronics, Ltd.

Motorola's Largest RF Distributor

Call 1-800-RF Power (in the U.S.A.) 1-800-348-5580 (in Canada)

MRF860 - Class A, 800-960 MHz, 13.7 W (CW) RF Power Transistor



Motorola's 13.7 watt (CW) RF power transistor is designed for 24-volt UHF large-signal common emitter, class A linear amplifier applications in industrial and commercial equipment operating in the 800-960 MHz range. Features include an 11 dB minimum gain, an output capacitance of 21 pF (typ) at 24 Vdc, a minimum ITO of +51.5 dBm and typical noise figure of 6.5 dB. The MRF860 will withstand RF input overdrive of 3.25 W CW. It is in a push-pull flange package (case 395B).

Richardson Electronics, Ltd. 40W267 Keslinger Road, LaFox, IL 60147 1-800-348-5580.





Figure 3. Higher resolution look at 10 GHz signal.



Figure 4. Close-up observation of 10 GHz signal spectrum using 10 Hz resolution bandwidth.

High Stability Ovenized Oscillator

The SC10 10 MHz quartz oscillator uses an SC cut crystal to provide an extremely low aging rate, high thermal stability and very low phase noise. For the most critical frequency and timing applications, the SC10 is the ultimate solution.

Grade Aging Thermal Stability (0-50° C) Phase Noise: 10 Hz 100 Hz 1 kHz Operating Range Allan Variance (1 second)	J <1x10 ⁻⁹ /day <±2x10 ⁻⁹ <-120 dBc/Hz <-150 dBc/Hz <-155 dBc/Hz 0° to 50°C <1x10 ⁻¹¹	K <5x10 ⁻¹⁰ /day <±1x10 ⁻⁹ <-125 dBc/Hz <-150 dBc/Hz <-155 dBc/Hz -10° to +60°C <5x10 ⁻¹²	A <2x10 ⁻¹⁰ /day <±5x10 ⁻¹⁰ <-130 dBc/Hz <-150 dBc/Hz <-155 dBc/Hz -20° to +70°C <2x10 ⁻¹²
 SMD construction Electronic and mechani frequency tuning +15 or +24 VDC operati 	• P cal ca • S on • \$; (d	in, SMA, SMB o prinectors ize: 2" x 2" x 4" 250 base price quantity of 100	r SMC for J grade)
	Anteroperature Particular of Particular of Parti		
SRS STANFORD 1290-D Rea TEL: (408)	RESEARCH S mwood Avenu 744-9040	GYSTEMS Je, Sunnyvale, FAX: (408) 74	CA 94089 14-9049



Figure 5. Testing for harmonic distortion caused by the spectrum analyzer.

analyzer generated distortion and the measurement is not correct.

It is not safe to assume that the observed distortion is part of the signal without additional information. Either the user needs to check spectrum analyzer specifications for appropriate safe settings, or the signal input level needs to be changed to check for impact on distortion. Figure 6 shows the spectrum of a 1 GHz carrier amplitude modulated with a 58 kHz tone. The intent is to determine the total harmonic distortion, THD, of the signal. THD is the rms sum, that is, the square root of the sum of the squares, of individual distortion terms.

First we determine the distortion content on a term-by-term basis, then the THD is easily computed. We have the following for Figure 6.

Harmonic	2nd	3rd	4th	5th
dBc	21.6	43.6	59.6	62.0
% Ratio	8.32	0.66	0.10	0.08

The square root of the sum of the squares yields a THD of 8.35 percent.

A distortion meter usually shows THD while a spectrum analyzer usually determines distortion on a term-byterm basis and THD is calculated. However, many spectrum analyzers, including the Tektronix 2794, have macro software available where the dis-



Figure 6. Harmonic distortion measurement for THD computation.



Figure 7. Low harmonic level, test for valid measurement.

tortion measurement and THD calculation is obtained automatically by executing a single measurement command.

Figure 7 shows an attempt to measure the second harmonic of a very clean 250 kHz signal. A change of 10 dB in the spectrum analyzer input attenuator shows an almost 10 dB (9.2 dB as seen in the upper left corner of the readout) change in harmonic level. This is too close for comfort. Some of the displayed harmonic content is likely due to the spectrum analyzer. Therefore, we need to reduce the spectrum analyzer input level by an additional 10 dB to make certain. The result of inserting 20 dB of RF attenuation is shown in Figure 8. The second harmonic is very small now, and we need to improve the signalto-noise ratio to measure it. This is accomplished by reducing the 10 kHz resolution bandwidth used in Figure 7 to 100 Hz used in Figure 8. Such a narrow resolution setting makes it difficult to span enough spectrum to observe the fundamental and harmonic in one sweep. Hence, Figure 8 shows two traces, obtained in two sweeps, one for the fundamental, and one for the harmonic. The 2794 has "intelligent" markers that will make measurements between different traces. A delta marker measurement shows a second harmonic level at 73.2 dB below the fundamental, or 0.02 percent distortion. A modern spectrum analyzer can measure harmonic distortion down to about 0.01 percent.

Intermodulation

Intermodulation, IM, is a form of distortion where multiple sinewave signals interact to create additional signal components. The simplest and most usual intermodulation tests involve two signals. Thus, if the two signals are at frequencies f_1 and f_2 , we can get new signals at frequencies: f_1+f_2 , f_2-f_1 , $2f_1-f_2$, $2f_2-f_1$, etc. The usual test is for the so called, third order terms consisting of $2f_1-f_2$ and $2f_2-f_1$.

Intermodulation testing is a complicated and extensive topic. This paper



Figure 8. Measuring relative amplitude of low level 2nd harmonic.

does not deal with it in depth. Here are

some examples of the factors that need to be considered. These are discussed in more detail in the references.

Test signal spacing – Some circuits are sensitive to test signal frequency spacing. The closer the two signal frequencies at f_1 and f_2 , the larger the IM products at $2f_1-f_2$ and $2f_2-f_1$. Be sure to vary the signal frequency spacing if you suspect that you have such a circuit.

Generating the two tone signal – Special two-tone signal sources can be pur-





The LPKF Protomat 91S System provides faster turnaround and better throughput of circuit board prototypes than other methods. There is NO better value in prototype PCB fabrication systems-here's why:

- Takes your Gerber or HPGL files and produces Analog, Digital, RF or Microwave circuit board prototypes.
- Windows software with programmable insulation width, multiple tool rub out, and full tool management.
- Small footprint from a fully integrated system package.
- Environmentally safe uses NO chemicals.

- Fast payback typically 3-12 mos.
- Full 1 year warranty

FREE PCB INFO PACK

CALL TODAY 1-800-345-LPKF (800) 345-5753 FAX request to: (503) 297-2820



6840 SW Canyon Dr. Portland, OR 97225

GO THE DISTANCE in baltimore



E A S T GOES THE DISTANCE

Sponsoring magazine: **RF**design

August 21-23, 1995 Baltimore Convention Center Baltimore, MD

HIGHLIGHTS INCLUDE:

- Full-Day Special Courses
- 30+ Educational Sessions
- Expansive Exhibit Area Showcasing the Latest Advances In Products and Services
- Unlimited Networking Opportunities
- Exhibitor/Attendee Receptions

RF Expo East `95 features both intensive tutorials and technical paper presentations exploring the challenges of the RF industry today—and in the future.

CALL FOR PAPERS

For more information on submitting technical papers, contact:

Gary Breed, Editor RF Design magazine 6300 S. Syracuse Way Suite 650 Englewood, CO 80111 (303) 220-0600 Fax (303) 773-9716









FOR INFORMATION ABOUT EXHIBITING AT RF EXPO EAST `95 CONTACT:

Jessica Cook West Coast/Southwest (404) **61**8-0422 Jon Lehl North Atlantic Region (404) 618-0423

Scott Moskowitz Midwest/Southeast (404) 618-0433

DED 3/05

FOR INFORMATION ON ATTENDING, PLEASE COMPLETE THE COUPON AND MAIL OR

FAX TO:

RF Expo East 6151 Powers Ferry Road, NW Atlanta, GA 30339 or call (800) 828-0420 or (404) 618-0393 Fax (404) 618-0441

Please send me m	ore information o	n RF Expo East 1995.
	LAST	
Title:		
Company:		
Address:		
City:	State:	Zip:
Phone: ()	Fax: ()



Figure 9. Third order intermodulation spectrum, testing for distortion from spectrum analyzer.

chased. Most people, however, combine the outputs from two independent signal generators to create a two-tone signal. It is very important that the two sources be well isolated from each other. Otherwise the interaction between the test sources will introduce IM terms which can be mistaken for legitimate test results. Isolators, directional couplers or filters and attenuators are primary means for maintaining independence between the test sources. Crosstalk by radiation from cables is also a potential problem when looking for very low levels of IM.

Most circuits are "well behaved" over a large range of signal frequency and amplitude levels. This means that equations involving the intercept point, as discussed later, are applicable. Using such equations makes IM testing much easier, as it means that testing can be performed at one set of conditions and results can be determined by computation for another set of conditions. However, not all circuits are well behaved, and not all well behaved circuits are well behaved all times. Make sure that you are not going beyond the range of your circuit when getting results by computation rather than direct measurement.

Figure 9 shows a typical IM test spectrum. The two signals have a 55 kHz separation (marker shows 54.9 kHz) centered at 1.5 GHz. The display shows two traces, one with 0 dB of input attenuation and one with 10 dB of attenuation. As with harmonic distortion. IM distortion products are circuit input level sensitive. A change in input level to the spectrum analyzer will show whether the IM products are real or being generated by the test instrument. We note in Figure 9 that a change of RF attenuation does change the IM level. Hence, the result at 0 dB attenuation setting is not correct. Measurement of the smaller IM (at 10 dB attenuation) shows 73.2 dBc.

If the test specification were 70 dB, for example, then a 73.2 dB result



Figure 10. Third order IMD test with main signal off screen.

would be sufficient to show compliance. It would not be important to determine whether the real number is better than that. If, however, we need to know the true result, then it becomes necessary to see what happens at a 20 dB attenuator setting. Possibly, some of the IM at 73.2 dBc is still due to the spectrum analyzer. Figure 10 shows such a measurement. As was the case with Figure 8, the result was obtained in two traces, once for a input test signal and once for an IM component. Here the spectrum analyzer gain setting needed to properly display the IM component is such that the main signal goes off screen. Nevertheless, the "intelligent" marker of the 2794 is able to make the measurement at 78.4 dBc. Indeed, some of the result shown in Figure 9 was due to IM from the spectrum analyzer.

Figure 10 may be acceptable for getting a result, but it is deficient in showing all the information. Most people prefer that all signal parts be on screen. Such a measurement is shown in Figure 11. Here the gain was reduced for the upper trace so as to bring the signal top on screen. The "intelligent" markers keep track of this change and the measurement using the markers again shows 78.4 dBc. However, one must be careful to do this only while making a measurement with the markers. Had the result been determined manually from the traces, with-



Figure 11. Third order IMD test with main signal fully displayed on screen.

Accessories for rf testing

PCB emissions scanner • Locates low-to-high emissions, displays color image, stores data for design corrections at development stage.

Dual-directional couplers • Seven models up to 15 kW, matched to AR amplifiers and antennas.

Ultra-broadband E-field monitor • Four-channel capability, 1 to 300 V/m, isotropic probes cover 10 kHz to 1000 MHz or 80 MHz to 40 GHz.

Broadband fiberoptic data links • Modular plug-in analog systems for acquiring and measuring interference data, stimulating EUT, displaying results in color or monochrome, 10 kHz to 1 GHz.

Fiberoptic CCTV systems • Watch performance of EUT under hostile EMI and/or EMP shielded-room conditions, in color or monochrome.

TEM cells • Half again the bandwidth of comparable-size chambers: To 750 MHz for 15-cm EUT, 375 MHz for 30-cm EUT.

Computer bus interfaces • Two models, for isolated GPIB connection or isolated TTL connection, permit remote operation of amplifiers.

RF connection kit • Things you'd search for around the lab: Cables, coax adapters, connectors, fuses, lamps, fabricated cables.

Power combiner/dividers • Combine signals from four amplifiers, or divide one signal into four outputs.

High-power rf matching transformers • Match 50-ohm input to 12.5- or 200-ohm output. Up to 2 kW cw.

Call toll-free (1-800-933-8181), and one of our applications engineers will answer the phone.



160 School House Road, Souderton, PA 18964-9990 USA • Fax 215-723-5688 In Europe, call EMV: Munich, 89-612-8054; London, 908-566-556; Paris, 1-64-61-63-29. 6312



Figure 12. Two tone IMD spectrum.

out the markers, the result would show 70 dB with a seven-division display difference at 10dB/div.

The intermodulation distortion level generated by a well behaved circuit depends on the test signal input level (S in dBm) and the circuit intercept point (I in dBm). The reader will find extensive discussion on the intercept point concept in the references. For now it is sufficient to note that the intercept point is a measure of circuit linearity. The higher the intercept, the more linear the circuit and the lower the distortion products. The relationship is given by I = (dBc/n-l)+S. The quantity dBc is the IM product level compared to the carrier and n is the IM order number. The order number is the sum of the test signal harmonics involved and is equal to three for the $2f_1-f_2$ and $2f_2-f_1$ products previously discussed.

Using the intercept point concept it is possible to make measurements at whatever signal level is convenient and the desired result is computed. Thus, if the IM level is measured at dBc = 70 dB, when each of the test signals is at S = -30 dBm, then: I = (70/3-1)-30 = +5dBm. From this we can determine that dBc is 110 dB when S = -50 dBm, even though our spectrum analyzer may not be able to make this measurement.

Multi-Tone IM

Multi-tone intermodulation is much more complicated than the two-tone variety. This is because the number of possible distortion terms increases geometrically as the number of tones increases. Some systems, such as baseband telephony, use three tones, while CATV applications can involve hundreds of tones. Choice of tone frequencies will have an impact on results depending upon whether multiple IM terms will fall on top of each other or not. For example, three tones at 200 kHz, 600 kHz and 1000 kHz will have IM clusters at: 2x200=400, 1000-600 = $400,\ 600-200 = 400;\ 200,\ 600-2x200 =$ 200, 2x600-1000 = 200; etc.

A two tone arrangement has two IM



Figure 13. Three tone IMD spectrum.

products in the frequency vicinity of the test tones at $2f_1-f_2$ and $2f_2-f_1$. A three tone arrangement with f_1 , f_2 and f_3 near each other can produce nine IM products near the test tones at: $2f_1-f_2$, $2f_2-f_1$, $2f_2-f_3$, $2f_3-f_2$, $2f_1-f_3$, $2f_3-f_1$, $f_2+f_3-f_1$, $f_1+f_2-f_3$, $f_1+f_3-f_2$. In other words, multi-tone IM can get messy. Here is an example of a threetone IM test.

Figure 12 shows a familiar two-tone IM test. Signal separation is 59.3 kHz. Two intermodulation components are observed, one on each side of the spectrum at a 59.3 kHz offset. Figure 13 shows the same spectrum as before but with a third test signal inserted between the first two. The left side test signals are spaced at 25.7 kHz, the right side at 33.6 kHz and the outer signals are spaced at 59.3 kHz as in Figure 12. We now have several new IM components in addition to the two observed in Figure 12. Some are very obvious, and easy to identify as to cause. Thus, the left most IM component is the same as in Figure 12 and spaced at 59.3 kHz from the nearest test tone. The IM component next in line, at two divisions from the left, is spaced 33.6 kHz below the left test signal. It comes from $f_1+f_2-f_3$. Some of the IM products are very difficult to recognize unless you know where to look. The little bump at the right side base of the middle test signal is the $f_2+f_3-f_1$ component, spaced at 33.6-25.7=7.9 kHz above the middle test tone.



Figure 15. Harmonic level measurement using a preselector.



Figure 14. Checking for validity of harmonic test result using a preselected spectrum analyzer.

The Preselector

A preselector is a signal tracking filter at the input of the spectrum analyzer used primarily at microwave frequencies. Signals must be simultaneously present in a circuit to cause distortion. Therefore, signals whose frequency spacing is greater than the preselector bandwidth will not cause distortion in the spectrum analyzer.

Figure 14 shows the sixteenth harmonic of a 500 MHz signal. A change in input attenuation does not change the harmonic amplitude level. This is because the spectrum analyzer is protected from generating harmonic components by an input preselector. Figure 15 shows the same harmonic at 8 GHz as shown in Figure 13, along with the 500 MHz fundamental on a second trace. Gain and attenuation settings have been changed between traces to permit both signals to show on screen. But the spectrum analyzer markers take these changes into account as discussed for Figure 11. The harmonic amplitude level measures at 87.6 dB below fundamental.

Preselected measurements can easily exceed 100 dB, even though the normal display range on screen is only 80 dB. This is illustrated in Figure 16. Here we determine the relative amplitude of the eighteenth harmonic at 9 GHz. The result shows 119.2 dB.



Figure 16. Measuring a very low level harmonic at 119.2 dBc using a preselector.



Figure 17. Spectrum of fundamental at 500 MHz and two harmonics.

Deliberate Distortion

Not all distortion need be avoided. Some signals are intended to be nonsinusoidal and hence, "distorted".

Figure 17 shows the lower frequency spectrum of the 500 MHz signal whose sixteenth and eighteenth harmonic was previously measured. The second harmonic at 1 GHz is 54.4 dB below the 500 MHz fundamental. To provide a stable higher frequency test signal it is desired to enhance the harmonic level at higher frequencies. This is accomplished by means of a snap diode multi-



Figure 18. Spectrum of 17 after snap diode multiplier.

plier. Connecting the multiplier results in the spectrum shown in Figure 18. This results in a substantially flat spectrum. The fundamental level has dropped and the second harmonic level increased to 2.8 dB above fundamental. The spectrum analyzer is an excellent tool for testing the performance of the multiplier. *RF*

References

1. Large Dynamic Range Spectrum Analyzer Measurements. Tektronix 2EW-8417-0

2. Large Signal Impact on Spectrum Analysis. Tektronix 2EW-8961-0

3. Spurious Free Signal Range in Spectrum

Analysis. Tektronix 2EW-8696-0

4. Engelson, M., "Measuring IMD By Properly Using The Spectrum Analyzer," *Microwaves & RF*, February, 1988.

5. Engelson, M., "Skills Improve Spectrum Analysis With Preselectors," *Microwaves & RF*, December, 1988.

6. Perlow, "Basic Facts About Distortion And Gain Saturation," *Applied Microwave*, May, 1989. 7. Engelson, M., *Modern Spectrum Analyzer*

7. Engelson, M., Modern Spectrum Analyzer Theory and Applications, ISBN 0-89006-150-5. JMS, Portland, OR.

8. Engelson, M., Modern Spectrum Analyzer Measurements. LIC 91-90030. JMS, Portland, OR.

About the Author

Morris Engelson is the former chief engineer at Tektronix and is currently associated with Tektronix on a consulting basis. He is a Fellow of the IEEE for contributions to spectrum analysis and is the author of several books on the topic. He is a NARTE-certified EMC engineer. He is currently director at the Portland, Oregon-based consulting firm of JMS. He can be reached at Tektronix at (503) 627-4823, and at JMS at (503) 292-7035.



INFO/CARD 34



NFO/CARD 35

RF cover story

A Low Cost Return Path CATV Transmitter ASIC

Bill Xenakis Stanford Telecommunications, Inc.

Cable television's coaxial cable distribution network has traditionally been used for one-way video broadcast only. This high-bandwidth medium. however, provides the clear possibility of 2-way interactivity, enabling such services as video-on-demand, data communications, and telephony. Transmission on the cable return path can be accomplished using a new chip developed by Stanford Telecom, the STEL-1103 Digital PSK Modulator. This chip's novel architecture (patent pending) is ideally suited to the unique challenges associated with upstream cable transmission, and has been selected by several major companies for inclusion in their high volume products. It is specifically designed to perform burst data transmission of bandwidth-efficient signals while meeting cable operator requirements for out-ofband interference. Requiring only the addition of a digital to analog converter and a lowpass filter, the chip produces BPSK or QPSK modulated, spectrally-shaped RF signals at center frequencies of up to 40 MHz. Based on its low cost and unique performance characteristics, the STEL-1103 represents a major breakthrough for the interactive communications market.

A complete transmission system based on the STEL-1103 is shown in Figure 1. Note that 12 bits of output data are provided; however, fewer bits may be used, depending on the performance requirements or cost goals of the particular systems. It has been found that 10 bit DACs are economical and provide very high performance.

The key features of the STEL-1103 PSK modulator chip are:

- Programmable FIR filters providing:
 Spectral shaping to minimize occu-
- pied bandwidth - Excess bandwidths as low as 20
- percent - Pulse shaping to minimize inter-
- symbol interference
- Stop band rejection greater than



Figure 1. A complete transmitter based on the STEL-1103.

50 dB

- Precise tuning (24 bit NCO provides 6 Hz steps with a 100 MHz master clock)
- Fast tuning (less than 1 microsecond, compared to many milliseconds for analog PLLs)
- Very low phase noise (equivalent to that of the crystal oscillator time base being used)
- Multi-octave tuning (DC to 40 MHz)
- Programmable bit rates up to 10 Mbps in QPSK, 5 Mbps in BPSK mode
- Burst operation control interface
- Differential encoding option, permitting simple I/Q ambiguity resolution
- Variable-rate interpolation filters eliminating unwanted alias energy
- All-digital modulator design resulting in:
 - Zero phase and amplitude error (the constellation is perfectly centered)
 - Performance constant over entire output frequency range
 - Immunity to process-related performance variations (very high repeatability)
 - No need for factory or field adjustments
- Possible integration with other digital system functions to save cost
- Lowest possible overall system parts-count
- Low cost 80 pin PQFP package

CATV Advantages

A number of the characteristics listed above result in the STEL-1103 being suited for upstream transmission of voice and data over CATV cable (or for any application having a direct RF output of under 40 MHz). Note the following advantages:

1) Since the STEL-1103 covers the entire upstream path frequency range, no analog frequency conversion is required. This eliminates: a) nonlinearities associated with mixers, b) phase noise associated with analog PLL-based synthesizers, and c) unnecessary complexity.

2) The output signal can be spectrally shaped to occupy minimum bandwidth, thereby allowing many signals to be closely spaced.

3) The stop band rejection is greater than 50 dB, thereby preventing interference with other upstream digital signals. The required lowpass filter will eliminate spurious energy occurring above 40 MHz.

4) The built-in burst control interface allows short bursts to be transmitted without splatter, i.e. the start up and shut down of the bursts are precision controlled to prevent stray high frequency energy from being sent onto the cable. This can eliminate the need for RF switches.

Applications Details

The STEL-1103 can transmit in either continuous or burst mode. The most common use of this chip in a cable system is as a TDMA transmitter. Each subscriber sends bursts of data upstream during assigned time slots. These bursts are demodulated at the cable head end by a single receiver.

Some Standard Features On The 2050 Aren't Even Available * As Options Elsewhere *

The feature rich Marconi 2050 series of digital and vector signal generators will test most of the world's emerging digital radio system standards with complex modulation formats. Some of the features of the 2050 include:

- Emulates most digital cellular systems NADC, PDC, TETRA and APCO 25.
- Error injection for testing receivers at system limits.
- Adjustable I & Q offset and I & Q gain imbalance.
- Rician and Rayleigh fading simulation.
- I & Q modulation bandwidths to 10MHz suitable for spread spectrum and high speed systems.
- SSB and TTIB signal generation.

SETTING NEW S

172 UEV ()

LA SWEEP 305 019

Marconi Instruments

ARCONI INSTRUMENTS

3 Pearl Court, Allendale, NJ 07401 Tel: (201) 934-9050 / 1-800-888-4114 Fax: (201) 934-9229 INFO/CARD 36



In Canada contact Canadian Marconi at 514-341-7630 X4695

1000

RAKON TCXO'S OUTSTANDING QUALITY & PERFORMANCE





- Miniature size
- SMD Low profile package available
- Excellent temperature stability performance ±1 to 2.5 ppm from -40 to 85°C
- No frequency perturbations
- Low power consumption of only 1.5mA

- Very low Hysteresis
- Low parts in 10⁻¹⁰ Alan Variance
- G sensitivity of 2x10⁻¹⁰ typical
- Excellent vibration performance
- Clipped sinewave output
- Frequency range of 9.6 to 20 Mhz

RAKON

RAKON LIMITED

Private Bag 99943, New Market, One Pacific Rise, Mt. Wellington, Auckland, New Zealand. Fax: 64-9-573-5559, Phone: 64-9-573 5554. FAX YOUR ENQUIRY NOW. 64 IS THE COUNTRY CODE, 9 IS THE AREA CODE.



Figure 2. STEL-1103 digital PSK modulator block diagram.

One goal of the network controller is to maximize the system throughput by assigning time slots as close together as possible. The STEL-1103 supports the precision burst timing control required for TDMA systems.

In CATV applications, frequency division multiplexing (FDM) is also used in the 5 to 40 MHz return channel. Data rates in the range of 128 kbps up to 4 Mbps, with excess bandwidths of 20 to 50 percent are common. A one megabaud signal with 20 percent excess bandwidth will occupy 1.2 MHz of the return spectrum, allowing signals to be spaced 1.2 MHz apart. The STEL-1103 provides precise center frequency control and bandwidth shaping to support FDM systems.

Operation

A simplified block diagram of the chip is shown in Figure 2. Data is clocked into the STEL-1103 at the bit rate, which can be as high as 10 Mbps for QPSK modulation, or 5 Mbps for BPSK. The data may then be differentially encoded (optional). Differential encoding provides a simple way for a receiver to determine the correct reference phase (four phases are possible for QPSK) for reassembling the data in the right sequence. The data is next passed to dual I and Q 32 tap FIR filters operating at four times the symbol rate. These are symmetrical filters each having 16 programmable 10-bit coefficients. These filters permit precise spectral shaping to obtain excess bandwidths as low as 20 percent of the symbol rate and can be programmed for any desired shape such as squareroot-raised-cosine.

If the filtered baseband data were to be digitally modulated at this point the results would not be desirable. The signal spectrum would fold about the sample rate which is now at four times the symbol rate (See Figure 3). This effect is eliminated by first passing the data through a multi-stage interpolation filter, which interpolates multiple points between those generated by the FIR filter. The effect of this process is to suppress the unwanted alias energy associated with the lower sampling rate. Figure 4 shows an example of a 2.5 Mbps QPSK signal centered at 20 MHz. Note the low spurious content.

Output frequency agility could be achieved without interpolation filtering; however, the FIR filters would have to be very large in order to accommodate the many samples per symbol necessary to run the chip at 100 MHz (1 Megabaud clocked at 100 MHz would require dual 100 tap filters).

Following the interpolation filter is the complex modulator which modulates the signal with a quadrature LO generated by a 24-bit NCO. The STEL-1103 stores three programmable frequency control words, enabling rapid switching of carrier frequencies. The final output of the complex modulator is a modulated carrier signal centered anywhere from DC to 40 MHz. The upper limit is determined by both the 100 MHz maximum clock rate and the requirement to filter out an unwanted alias signal located above one half the NCO clock frequency. It is also required that the master clock rate be selected to be an integer multiple of four times the symbol rate. For example, given a symbol rate of 1.25 Msps and a master clock rate of 100 MHz, the FIR filter will operate at 5 MHz, resulting in the need to interpolate 20 points.

Although the STEL-1103 can be used for continuous data transmission, it was specially designed for burst data transmission. The chip incorporates appropriate control lines to enable each burst to begin and end gracefully. Since the chip contains certain latencies, such as the 8-symbol delay of the FIR filters, the data is flushed at the end of each burst so



INFO/CARD 37



Figure 3. Spectrum of filtered signal without interpolation.

that each successive burst will contain no residue from the prior burst. Also, the output will trail-off to be exactly zero, representing greater than 100 dB on-off ratio, thereby eliminating the need for an RF transmit switch in burst mode applications.

In addition, the chip includes some other useful functions. It provides a re-synchronized DAC clock which has a programmable delay. This greatly simplifies interfacing with various DACs. It also includes a programmable (divide by 1 through 16) prescaled output of the main clock input. This function simplifies building systems which are synchronously locked to the STEL-1103's clock. This is useful for generating the data clock which must be synchronized with the STEL-1103's clock, or vice versa.

A direct analog modulator can be designed to have minimum phase and amplitude error only at singular fre-

quencies. Tuning the output to other frequencies results in performance loss. More sophisticated analog IF modulation schemes require complex hardware and up or down converters. The STEL-1103 digital modulator has the advantage of high performance that remains constant as the output is varied over frequency, while achieving very low system complexity. It has nearly zero phase and amplitude error (the constellation is perfectly centered) over its entire output frequency range, thus enabling the best possible system performance. A result of this accuracy is excellent sideband rejection. Analog QPSK modulators achieve typical sideband rejection of only 40 dB (50 dB if hand trimmed). Spurious signals, such as unwanted sideband feedthrough, appear to a demodulator as an interferer, thereby reducing the receiver's performance. In contrast, the STEL-1103 has inher-



Figure 4. Spectrum of filtered signal with interpolation (1.25 Meg symbol per second, alpha = 0.3).

ent sideband rejection of 75 dB without any need for trimming.

STEL-1103 Analog Filtering Requirements

Since the spectrum generated by the combined STEL-1103 and DAC contains aliases of the desired signal above the Nyquist frequency, a lowpass filter must be included at the modulator output. These aliases occur at integer multiples of the master clock rate plus and minus the center frequency of the desired signal. For example, with a clock rate of 100 MHz and a carrier output at 40 MHz, aliases will exist at 60, 140, 160, 240....MHz. The amplitude of these signals rolls off as a sinc function with nulls at multiples of the master clock rate. For the case of a 40 MHz upstream signal, the first alias, which occurs at 60 MHz, is right next to TV channels 2 and 3, and is only 3 dB



About the Author

down from the desired signal. The required lowpass filter typically must provide enough rejection at this frequency to keep the alias 60 dB lower than the analog TV signal.

Future Versions

The next integration step for this product involves combining the DAC on chip. The mixed-mode technology needed to economically produce complex, high-speed digital functions combined with 100 MHz DACs is just nearing viability. Stanford Telecom is working closely with select foundries on future versions which will incorporate the DAC. For maximum flexibility, however, these two high performance functions are best left as independent chips. The key drivers to further integration will be 1) the advancement of high-speed CMOS DAC technology, and 2) the specific economies associated with combining the two dissimilar functions and technologies.

Stanford Telecom is also presently designing a version of this chip which will generate 24 MHz maximum RF outputs. Many interactive CATV applications do not require the full 40 MHz output. This chip will be lower cost and will be an immediate candidate for having the DAC included onboard since 50 MHz CMOS DAC technology is already mature.

Evaluation Board

The STEL-1203A is an evaluation board based on the STEL-1103. It includes a 10-bit DAC, lowpass filter, programmable output level function, and an output amplifier. Also included is a Windows-based user interface for configuring all of the chips parameters.

Conclusion

The STEL-1103 Digital PSK Modulator chip is a good example of what can be achieved through innovative design and in-depth knowledge of a specific application's requirements. Based on the current selection of this chip by various high volume users, the STEL-1103 may soon become the industry standard choice for many systems. In order to maintain and expand its industry leadership position, Stanford Telecom is on an aggressive path to further advance this product as well as many other specialized communications products. Stanford Telecom is also supplying a number of other products to the interactive CATV market including the STEL-2105, which is an Bill Xenakis is the Program Manager for Cable Products in the Telecom Products Group at Stanford Telecom. He has 10 years of experience in developing digital communications products at Stanford Telecom and holds a BSEE degree from California Polytechnic University. He can be reached at 480 Java Drive, Sunnyvale, CA 94089. Telephone: (408) 745-0818, x5548.

all-in-one digital QPSK receiver chip, as well as a number of custom, lowcost, board-level burst receivers that are being used in the host digital terminal (HDT) of Hybrid Fiber/Coax networks. The STEL-1103 is available in quantities of 10,000 pieces for under \$20 each. For more information please contact the author or circle Info/Card #252. RF



INFO/CARD 39

WR

RF products

Dual Frequency Synthesizers

National Semiconductor's Double PLLatinum LMX233x family of monolithic, integrated dual frequency synthesizers, including prescalers, is designed to be used as a local oscillator for the RF and IF of a dual conversion transceiver. It is fabricated using National's ABiC IV silicon BiCMOS process. Members of the family include the LMX2330 (2.5 GHz and 510 MHz), LMX2331 (2.0 GHz and 510 MHz), and LMX2332 (1.2 GHz and 510 MHz). The LMX233x contains two dual modulus prescalers. A 64/65 or a 128/129 (32/33 or 64/65 in the 2.5 GHz LMX2330) can be selected for the RF synthesizer and a 8/9 or a 16/17 can be

PC-Based Telemetry Receiver The PCTR-500 is a dual con-

The PCTR-500 is a dual conversion, general purpose, synthesized, frequency selectable telemetry receiver integrated with a single slot, full length ISA bus (IBM-PC AT or compatible) personal computer card. The series PCTK-500 receivers provide reception and FM demodulation for telemetry signals transmitted in the L and S frequency bands. The PCTR-500 receivers employ a modular architecture that enables the



user to configure the receiver for a variety of different data rates (up to 20 Mbps), IF bandwidths, FM deviation response and signal output voltage levels. The PCTR-500 receiver offers replaceable plug-in modules for the 2nd IF stage, FM discriminator, and post detection amplifier/filter. The receiver is controlled via a simple menu-driven DOS program that is supplied with the receiver, or can easily be integrated into a custom developed DOS or Windows application program.

Systems Engineering & Management Co. INFO/CARD #146

selected for the IF synthesizer. Using a digital PLL technique, the LMX233x can generate a very stable, low noise signal for the RF and IF local oscillator. Serial data is transferred into the LMX233x via a three wire interface (data, enable, clock). Supply voltage can range from 2.7 to 5.5 V. The LMX233x family features current consumption of 15 mA at 3 V for the LMX2330, 14 mA at 3 V for the LMX2331, and 8 mA at 3 V for the LMX2332. The family is available in a 20-pin TSSOP surface mount plastic package. Thousand unit pricing ranges from \$6.50 to 9.95 per unit. **National Semiconductor** INFO/CARD #147

CDMA Base Station Test

Hewlett-Packard has announced the availability of a code division multiple access (CDMA) adapter for the HP 8921A cell-site test set. The HP 83203B embodies a new measurement concopt called code



domain analysis. The HP 83203B, when connected to the HP test-set, measures power in each code channel, as well as measuring code-channel timing and code-channel phase relative to the pilot. The measure of waveform quality, p, is the normalized correlated power coefficient. It is a measure of the percentage of transmitted power that correlates to an ideal signal. This new measurement. developed by HP, indicates the overall performance level of the CDMA transmitter. In addition, the HP 83203B makes trueaverage and channel powertransmitter measurements, and provides a reverse CDMA channel source with data buffer with interim Standard-95-compliant error correction and channel coding for base-station receiver testing. U.S. price for the HP 83203B CDMA cellular adapter is \$18,000. **Hewlett-Packard Co.**

INFO/CARD #145



Push-Pull Power MOSFET

Motorola has added the MRF166W RF power MOSFET to its portfolio of UHF broadband components. This second generation N-channel enhancement mode device is characterized at 28 V and operates in the frequency range of DC to 500 MHz. Typical performance at 400 MHz is: output power = 40 W, gain = 13 dB, and efficiency = 50%. Typical performance at 175 MHz is: output power = 40W, gain = 17 dB, and efficiency = 60%. Designed with a pushpull configuration to reduce even-numbered harmonics, the MRF166W also offers high thermal stability and a typical power gain of 13 dB at 400 MHz. The transistor is designed primarily for wideband large-signal output and driver applications and has the ability to withstand



30:1 load VSWRs of any phase angle. C₇₅₈ is 4.5 pF at VDS of 28 V. Pricing for the MRF155W is \$83.33 in low volumes. **Motorola Semiconductor INFO/CARD #144**

Bilateral Power Amplifiers

HyperLink Technologies, Inc. has released the HyperAmp 900 and HyperAmp 2400 series of spread spectrum amplifiers/ range extenders for 900 MHz and 2.4 GHz wireless LAN



adapters and radio modems. The devices amplifies in both transmit and receive modes. HyperAmp is a linear, wideband power amplifier suitable for digital and analog modulation. Consisting of a low-noise receive amplifier and a transmit power amplifier, HyperAmp is designed to be remote mounted at the antenna. A fast RF sensing circuit switches the unit between transmit and receive modes in under 3 µs, ensuring reliable operation with even the fastest spread spectrum radio equipment. HyperAmp provides receive gain of 19 - 24 dB, with models available with maximum output power of 100 mW, 250 mW, 1 W, 2.5 W, 5 W, and 10 W (output is variable for all units). Suggested retail prices range from \$595 to \$850. HyperLink Technologies, Inc. INFO/CARD #143

TEST EQUIPMENT

PCS Test Set

Racal Instruments has launched a low-cost, portable test set, designated Model 6113, for base transceiver stations (BTS). Applicable to E-GSM, PCS-1900 and DCS-1800 systems, the tester is well suited to



development, repair and maintenance as well as production testing. The Model 6113 permits E-GSM, PCS-1900 and DCS-1800 BTSs to be fully tested manually and automatically via both A-bis and RF interfaces.

Racal Instruments INFO/CARD #142

Analog ATE Pensar Technologies has released the UAT A-2000, a computer-based system of ATE (automated test equipment) designed for testing analog components on printed circuit boards. The UAT A-2000 is a 2 channel, PC-driven test device and software that can derive and store the L/V curves for parts on known good boards and compare those with the I/V curves of parts on boards to be tested. In addition, the tester automatically creates a database from each board tested. The UAT A-2000 sells for under \$7,500.

Pensar Technologies, LLC INFO/CARD #141

Signal Generators

Tektronix has introduced the SMP03 and SMP04 microwave signal generators. The SMP03 covers 2 to 27 GHz and the SMP04 covers 2 to 40 GHz, both with optional frequency extension down to 10 MHz. These signal sources, developed by Rohde & Schwarz, have comprehensive modulation capabilities, including AM from DC to 250 kHz, PM from DC to 100 kHz, pulse modulation, and FM down to DC. Tektronix, Inc. INFO/CARD #140

Mobile Radio Test

OCTAS by Berkeley Varitronics is a portable multichannel mobile radio test and measurement system for land mobile propagation analysis. Eight receivers can measure signal strength to within 0.5 dB, and navigational information is supplied by internal GPS and LORAN receivers as well as an odometer input from the vehicle. OCTAS is available for 935 to 941 MHz, 851 to 870 MHz, and 405 to 512 MHz. **Berkeley Varitronics**

Systems, Inc. INFO/CARD #139



Bandpass Filter

KEL-Com bandpass filter model number 5MB6-1000/65 has a center frequency of 1000 MHz with a minimum 3 dB bandwidth of 65 MHz. Insertion loss is less than 3.0 dB at 1000 MHz. Maximum group delay deviation over 980 to 1020 MHz is 5 ns. Typical VSWR is 1.5:1, and minimum rejection at 850 and 1165 MHz is 50 dB. Outline dimensions are 0.97" L × 0.50" W×0.25" H. **KEL-Com**

INFO/CARD #138

Directional Coupler

Sage Laboratories announces the availability of a commercial grade 20 dB coupler for use over the 824 to 849 MHz cellular band, Model FC5621 offers insertion loss of 0.2 dB and input VSWR of 1.25:1. Typical directivity is 15 dB and flatness is ±0.20 dB. Average forward and reflected power is 200 W. Type N male and female connectors are utilized on the mainline, and an SMA female connector is used on the coupled port. Sage Laboratories, Inc. INFO/CARD #137

70 MHz X-tal Filter

Piezo Technology's model 7822C is a 70.0 Mhz fundamental crystal filter with a minimum 3 dB bandwidth of ±53 kHz and stopband attenuation of 50 dB at ±220 kHz maximum. Additional features include a 50 dB ulti-



INFO/CARD 45



WE'VE GOT THE POWER\$



We offer the most complete line of application specific and standard switches, attenuators and hybrids in the industry.

JFW...The Power Leader

For more information or for a free catalog, contact:

JFW Industries, Inc. 5134 Commerce Square Drive • Indianapolis, Indiana 46237 Tele. (317) 887-1340 Fax (317) 881-6790 INFO/CARD 27

RF products continued

mate attenuation, 50 dB spurious attenuation and 50 ohm input and output impedances. The unit is packaged in a $1.95 \times$ 0.59×0.40 inch enclosure. Piezo Technology, Inc. **INFO/CARD #136**

TOOLS. **MATERIALS &** MANUFACTURING

Bonding Film

Polyflon bonding film is well suited for bonding single or multi-layered microwave stripline circuit boards. The bonding film is thermally stabilized, irradiated polyolefin co-polymer, and is recommended for use with circuit board substrates consisting of irradiated cross-linked polyolefin; virgin PTFE, PTFE fiberglass; or ABS. Standard thickness is 0.002 inches, and sheet size is 24 x 36 inches. Pricing is \$12.84 per sheet in 100-sheet qty.

Polyflon Co. INFO/CARD #135

Aluminum Nitride Substrates

Sherritt has added R130 to its ThermicEdge line of aluminum nitride substrates. R130 substrates are available in large volumes and provide high lot-tolot consistency. Aluminum nitride has thermal conductivity five times that of alumina and is non-toxic. Sherritt maintains an inventory of standard size substrates.

Sherritt, Inc. INFO/CÁRD #134

AMPLIFIERS

Low Noise Amplifiers

MITEQ offers the NSH series building block LNAs. The NSH is available in either a solderable or screw-mount chassis and



is suitable for drop-in application with a variety of substrates. Typical performance includes a 2 to 18 GHz design with 14 dB minimum gain, 3.0 maximum noise figure, 2:1 input/output VSWR, and typical current consumption of 60 mA at 6 V. MITEQ

INFO/CARD #133

10 W UHF Amp

ENI's model 411LA power amplifier produces 10 W of linear class A output over a frequency range of 150 kHz to 300 MHz. With a gain of 40 dB, the 411LA features low harmonic and intermodulation distortion. and complete protection against short and open circuit loads. The amplifier is also unconditionally stable, and has +13 dBm overdrive protection and infinte maximum load VSWR. The 411LA has integral power supply and forced-air cooling. ENI

INFO/CARD #132

Feedforward Amp

Four, low profile, "laptop" feedforward cellular power amplifiers have been released by AML Communications. These units cover the the four instantaneous 25 MHz, USA and international transmit cellular bands. These amplifiers support 1 W of multicarrier power (10 W PEP) while maintaining intermodulation products at 55 dBc. The amplifiers operate on a single 26 V supply and provide 53 dB gain. AML Communications INFO/CARD #131

DISCRETE COMPONENTS

SMT Crystals The TSMX-1S is a surface mount crystal measuring 7.5 x 5.0 x 1.3 mm. This low profile crystal from Tellurian Technologies was developed for applications where small size and SMD capability are mandatory. The series frequency range is from 12.0 to 150.0 MHz, with an operating temperature range of -10 to +70 °C. Standard stability is ± 100 ppm, with tighter stabilities available on request. Tellurian Technologies, Inc. INFO/CARD #130

ALL YOU NEED TO KNOW ABOUT CRYSTALS....



Over 30 years Experience

... Specializing in quick turn around on non-standard frequencies

... Inventoring common microprocessor frequencies

> Phone 800-526-3935 Fax 800-777-2197

201 BLACKFORD AVENUE MIDDLESEX, NJ 08846

INFO/CARD 42

Integrated Component Systems

WIDE/NARROW BAND VCO'S



Product Features

- 200 to 4200 MHz Frequency Range
- +14 dBm Output Power
- Superior Phase Noise
- Linear Tuning
- Hermetically Sealed
- Low Cost

Price is \$69.00, single piece quantity. Custom Packaging and coaxial resonator models available. Contact Eliot Fenton, Integrated Component Systems Inc., 5440 N.W. 55th Blvd., Ste 11-105, Coconut Creek, FL 33073. 1-800-396-5185

Surface Mount Inductors

Standex Electronics series 166 and 168 surface mount inductors are now available in ten values from 3.5 nH to 84 nH. These inductors have superior performance, especially in "Q", when compared to similar value "chip" inductors. The flat top allows vacuum pick and place. These components are available tape and reel or bulk packed. Prices are \$0.16 each in volume quantities. Standex Electronics

INFO/CARD #129

Multilayer Chip Capacitors

A line of low cost, general purpose multilayer ceramic chip capacitors, manufactured for American Technical Ceramics, is available for high volume, surface mount applications. The capacitors are offered in NPO, X7R, and Z5U dielectrics, in six



standard EIA case sizes: 0603, 0805, 1206, 1210, 1812, and 2225. Capacitance values range from 1 pF to 4.7 μ F. Tolerances are: C, D, G, J, K, M, and Z. American Technical Ceramics INFO/CARD #128

CABLES & CONNECTORS

Low Insertion Loss Cable

40 GHz cables from Storm Products feature an insertion loss of 1.14 dB/ft., with a cable O.D. of 0.125 inches. Part number 421-011, an assembly using K plug connectors yields typical VSWR of < 1.30:1 up to 40 GHz. All cables are manufactured using low density PTFE and feature an operating temperature range of -55 to +150 °C. Storm Products Co. INFO/CARD #127

Patch Cable Kit

RF Industries' Unicable[®] Kit allows users to mix and match any combination of connectors or adapters to the ends of a 48inch cable assembly. The cable is extra flexible RF-58A/U type 50Ω cable with 95% double shielding. The Unidapt[®] universal connectors at each end feature machined brass, silver plated bodies, gold plated contacts, and PTFE dielectric insulators. **RF Industries, Ltd. INFO/CARD #126**

90° 7/16 Plug

A series of 7/16 right angle plugs that is compatible with Andrew LDF4-50A cable is being introduced by Tru-Connector. The right angle plug permits smoother cable runs. All mating dimensions conform to DIN 47223, IEC 1694, VG 95250, and CECC 22 190 specs. The 50 Ω plugs have a voltage rating of 2700 Vrms. The Tru-7631 right angle 7/16 plug is priced from a list price of \$98.00.

Tru-Connector Corp. INFO/CARD #125

45° and 90° BNC Connectors

Trompeter's 45- and 90degree BNCs use the same standard stripping dimensions and standard BNC crimp tools as their straight BNCs. The new BNC connectors feature fully heat-treated beryllium copper outer conductor springs. Cost for the 45-degree BNC, UPLFF220, and the 90-degree BNC, UPLR220, is \$7.72 each in quantities of 1,000. Trompeter Electronics, Inc.

INFO/CARD #124

High Quality ATTENUATORS

ACCURACY, PERFORMANCE, LOW COST, DELIVERY ...



839 Manual Step Attenuator



4550 Programmable Attenuator

Manual Step Attenuators

837	50Ω	DC-1500MHz	0-102.5dB	.5dB Steps
839	50Ω	DC-2000MHz	0-101dB	1dB Steps
1/839	50Ω	DC-1000MHz	0-22.1dB	.1dB Steps
847	75Ω	DC-1000MHz	0-102.5dB	.5dB Steps
849	75Ω	DC-1500MHz	0-101dB	1dB Steps
1/849	75Ω	DC-500MHz	0-22.1dB	.1dB Steps
860	50Ω	DC-1500MHz	0-132dB	1dB Steps
865	600Ω	DC-1MHz	0-132dB	1dB Steps

Programmable Attenuators

4540	50Ω	DC-500MHz	0-130dB	10dB Steps
4550	50Ω	DC-500MHz	0-127dB	1dB Steps
1/4550	50Ω	DC-500MHz	0-16.5dB	.1dB Steps
4560	50Ω	DC-500MHz	0-31dB	1dB Steps
4580	50Ω	DC-500MHz	0-63dB	1dB Steps

For price list and FREE catalog, contact:



Kay Elemetrics Corp.

2 Bridgewater Lane, Lincoln Park, NJ 07035-1488 USA TEL: (201) 628-6200 • FAX: (201) 628-6363

INFO/CARD 44

SEMI-CONDUCTORS

Driver Amplifier

A low-cost driver amplifier from Celeritek operates from a single +5 V power supply and uses less than 10 mA. Model CMM2302 is designed for use as a low-current gain stage in space constrained PCMCIA applications in the 1.7 to 2.5 GHz. The wideband design of the CMM2302 allows the amplifier



to be used in many applications, including DECT DCS1800, PCS, and PHS. The amplifier is internally matched to 50 ohms and internally biased. The device produces about 12 dB of gain at signal levels up to +7 dBm. Production quantities of 1,000 are priced as low as \$3.95 per unit. Celeritek

INFO/CARD #123

High-Speed, Low-Cost Op Amp

The AD8011 operational amplifier offers 300 MHz bandwidth on a maximum supply current of just 1 mA. The op amp from Analog Devices consumes 5 mW maximum power from a single +5 V supply. The AD8011 offers 0.1 dB gain flatness to 25 MHz, 0.02% differential gain, and 0.06° differential phase error. The current feedback op amp also features worst case harmonic distortion of -62 dB at 20 MHz while driving a 150 Ω load. In 1,000 piece quantities, the AD8011 is priced at \$1.95. Analog Devices, Inc. INFO/CARD #122

Low-Cost, High-Speed Op Amps

SGS-Thomson Microelectronics has introduced three new op amps that combine high speed (100 MHz - 300 MHz) with low input current, low noise, and low cost. The TSH10/11/31 use an advanced BiCMOS process, and have standard op-amp pinout and packaging. The voltagefeedback op-amps feature low noise (6 nV/Hz for the TSH10) and high input impedance (2 pA for the TSH11/31) Housed in DIP8 and SO8 packages, these devices cost less than \$1 each in 10,000 piece quantities. **SGS-Thomson Microelectronics INFO/CARD #121**



VCO for Cellular

The miniature U-package VCO-190 series voltage-controlled oscillators from Vari-L is offered with center frequencies from 773 to 992 MHz and bandwidths of 26 MHz. Units operate with a supply voltage of 2.5 V to 5.0 V and exhibit ultra low current draw (typically 3.3 mA at 3.0 V). The VCOs are packaged in a $0.375 \times 0.375 \times 0.117$ inch shielded surface mount package. **Vari-L Co., Inc.**

INFO/CARD #120

Fast Tuning Synthesizer

À fast tuning synthesizer covering the 50 to 100 MHz frequency range has been announced by Communication Solutions. The synthesizer has 1 Hz resolution and <1.0 microsecond lock time. The unit is rack mounted, with a parallel digital input, built-in test, and modular construction for ease in maintenance. Additional frequency ranges are available. **Communication Solutions INFO/CARD #119**

Basestation VCO

Z-Communications has introduced the V502MC03 miniature surface mount VCO for cellular basestation applications operating in the 750 to 850 MHz region. The VCO uses a control voltage of 1 to 8 V and exhibits average gain of 40 MHz/V. The V502MC03 delivers 6 ±2 dBm into a 50 ohm load operating off a nominal +5 VDC bias, while drawing less than 25 mA. Typical phase noise performance is -95 dBc/Hz at 10 kHz offset. The device is packaged in a 0.50 $\times 0.50 \times 0.20$ inch package. **Z**-Communications, Inc. INFO/CARD #118

Save space and money with the Rogers family of high frequency circuit board materials.



The new RO3000[™] series provides low dissipation factors, low etch shrinkage, low Z axis expansion, and low Tck'. That's a lot of lows, and there's one more: the price.

As for performance, you can choose from a wide range of dielectric constants (3.0, 6.15, and 10.2) to optimize your designs. And you can mix and match these products, because every member of the family is mechanically compatible.

ROGERS Microwave and Circuit Materials Division

 Rogers Corporation
 100 S. Roosevelt Avenue, Chandler, AZ 85226
 161: 602-961-1382
 FAX: 602-961-4533

 Rogers Japan Inc., Totyo; Tet: +(81)-33-807-6130
 FAX: +(81)-33-807-6139
 Rogers-Meditron, N.V., Gert, Belgium;

 Tet: +(82) 9 235 36 11
 FAX: +(82) 9 235 36 58
 RO3000, RO3003, RO3003, RO3000, R



Low profile, high stability, small

size, rapid warm-up, low power

Frequencies: 9 MHz to 20 MHz

Size: 35.8 x 27.5 x 16mm max.

Frequency Stability: ±2 x 10⁻⁹

Other options/packages available

consumption.

Output: HCMOS

Voltage: 12VDC & 5VDC

ELECTRONICS CORP.

2315 NW 107 AVENUE MIAMI, FLORIDA 33172 U.S.A. FAX (305) 594-3973 (305) 593-6033

ONLY RALTRON HAS IT ALL CRYSTALS • CRYSTAL OSCILLATORS CRYSTAL FILTERS

CERAMIC RESONATORS

INFO/CARD 46

RF tutorial

Nonlinear Analysis in RF Design

By Steve Maas, Ph.D. Nonlinear Technologies, Inc.

Nonlinear circuit analysis is an important part of modern circuit design. Indeed, the relentless advances in the performance of digital circuits would not have been possible without it, and advances in communications circuits, aithough perhaps not quite as dramatic, owe a great deal to computerized analytical tools. In communications circuits the designer's ability to control phenomena such as nonlinear distortion is critical to the system's performance, so nonlinear circuit analysis is essential.

The importance of nonlinear circuit analysis has never been greater. New types of communications systems are remarkably sensitive to distortion phenomena. Interference – which is often manifest as intermodulation distortion (IM) – presents a fundamental limit to the performance of many types of military and commercial space communications systems, and is already a major concern in wireless applications. Of course, the need for good, "clean" mixers and amplifiers in more conventional RF systems has not diminished.

As the importance of such systems increases, the variety of nonlinear circuit-analysis programs has increased. Only a few years ago, the sole option for nonlinear circuit analysis was SPICE and its variants; now the user can choose between a wide variety of programs (with a wide variety of price tags!) including harmonic balance, time-domain, and Volterra simulators. In this article we will discuss these, describe how they work, and how they're best used.

What's Out There

Since its development at the University of California at Berkeley in the mid-1970s, SPICE [1] has been the circuit-analysis workhorse of the electronics industry. Since SPICE was made available as a public-domain program, a number of software companies have ported it to popular DOS and MacIntosh machines, added graphical and schematic-capture user interfaces, and graphical output. These have the same "engine" underneath the glitzy interfaces: SPICE version 2, or SPICE2 in common parlance. Berkeley has released versions of its next-generation simulator, SPICE3, a completely rewritten program, and it is starting to appear in commercial products. You can buy one of these, or even get your own copy of the source code from the Industrial Liaison office of the Berkeley Computer Science Department.

A more recent addition to the stable is the harmonic-balance (HB) simulator. Several of these are available from mainstream software companies. Again, one of the popular simulators was developed at UC Berkeley [2], but work at Sarnoff Labs and the University of Bologna [3], in Italy, found its way into mainstream programs.

Most of the mainstream HB programs are oriented toward microwave design. Models of RF devices and circuit elements are not widely represented in these simulators. Perhaps for this reason, in the RF community there seems to be some degree of disappointment with these simulators. This is indeed unfortunate, because HB simulators offer the RF user many significant benefits. At the same time, however, there are many things the HB simulators don't do well. We'll examine these issues a little later.

A third product is the Volterra simulator [4]. Volterra-series analysis predates HB, and certainly Volterra simulators existed long before either SPICE or the HB products. However, Volterra analysis never "caught on". This is unfortunate, since Volterra analysis works well for precisely the types of problems where HB is poor. HB and Volterra analysis are nearly perfect complements. At present, only one commercial product is available that uses Volterra analysis, produced by (wouldn't you know it) the author's company [5].

Time Domain Analysis

SPICE performs linear simulations of electronic circuits. It also performs time-domain analysis of nonlinear circuits, which in SPICE's documentation is called transient analysis. To analyze nonlinear circuits, SPICE sets up the circuit equations as a set of nonlinear differential equations, in matrix form, and integrates them in the time domain (see Figure 1). To do the integration, SPICE must obtain a solution iteratively at each of many successive time intervals; depending on the circuit, this is a long process, and is the reason why transient analysis is a slow process.

This simple description already illustrates the greatest difficulty in using SPICE for RF or microwave circuits: how does one describe lossy, dispersive transmission lines and other distributed circuits in the time domain? A circuit analyzed by SPICE



Figure 1. The voltages in the circuit are determined at a series of discrete time points, t_n , by numerically integrating a set of nonlinear differential equations.

SURFACE-MOUNT or PLUG-IN

ALL-WELDED

\$395 FROM \$3(10 qty)

Expose Mini-Circuits' TUF-mixers to 250°C for five minutes, or to the extreme shock and vibration stresses of MIL-M-28837, or to 200 cycles of thermal shock from -55° to +100°C...they'll survive without any change in specs. They are mighty tough mixers!

Available with LO drive levels from +7 to +17dBm, performance features include very low conversion loss flat over the entire band, high isolation (L-R, L-I), and well-matched VSWR at all ports.

All-welded internal and external construction is used to assemble and package the TUF-unit in its tiny 0.5 by 0.2 by 0.25 in metal case, for plug-in or surface-mount* assembly. TUF-Ultra-Rel¹" mixers are guaranteed for five years and boast unprecedented

"skinny" sigma (δ) unit-to-unit repeatability as shown in the Table. Tough, tiny, and with tight repeatability...Mini-Circuits' Ultra-Rel[™] TUF-mixers with a

five-year guarantee, priced from \$3.95...available only from Mini-Circuits.



ULTRA-REL[®] MIXERS 5-YR. GUARANTEE

with extra long life due to unique HP monolithic diode construction, 300°C high temp. storage, 1000 cycles thermal shock, vibration, acceleration, and mechanical shock exceeding MIL requirements.

SPECIFICA	HONS					
Model	LO Power (dBm)	Freq. LO/RF (MHz)	■ Con ▼(c	iv. Loss JB) δ	Isol. L-R (dB)	Price,\$ Ea. 10 qty
TUF-3 TUF-3LH TUF-3MH TUF-3H	7 10 13 17	0.15-400	4.98 4.8 5.0 5.0	0.34 0.37 0.33 0.33	46 51 46 50	5.95 7.95 8.95 10.95
TUF-1 TUF-1LH TUF-1MH TUF-1H	7 10 13 17	2-600	5.82 6.0 6.3 5.9	0.19 0.17 0.12 0.18	42 50 50 50	3.95 5.95 6.95 8.95
TUF-2 TUF-2LH TUF-2MH TUF-2H	7 10 13 17	50-1000	5.73 5.2 6.0 6.2	0.30 0.3 0.25 0.22	47 44 47 47	4.95 6.95 7.95 995
TUF-5 TUF-5LH TUF-5MH TUF-5H	7 10 13 17	20-1500	6.58 6.9 7.0 7.5	0.40 0.27 0.25 0.17	42 42 41 50	8.95 10.95 11.95 13.95
TUF-860 TUF-860LH TUF-860MH TUF-860H	7 10 13 17	860-1050	6.2 6.3 6.8 6.8	0.37 0.27 0.32 0.31	35 35 35 3 8	8.95 10.95 11.95 13.95
TUF-11A TUF-11ALH TUF-11AMH TUF-11AH	7 10 13 17	1400-1900	6.83 7.0 7.4 7.3	0.30 0.20 0.20 0.28	33 36 33 35	14.95 16.95 17.95 19.95

*To specify surface-mount models, add SM after P/N shown.

X = Average conversion loss at upper end of midband ($f_U/2$)

 δ = Sigma or standard deviation



For detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER • MICROWAVE PRODUCT DATA DIRECTORY • EEM • MINI-CIRCUITS' 740- pg. HANDBOOK.

INFO/CARD 47

CUSTOM PRODUCT NEEDS...Let Our Experience Work For You.



Figure 2. The circuit is divided into linear and non-linear subcircuits, and the nodes and loops between the circuits are solved for Kirchoff's equations.

may include ideal transmission lines, but cannot handle anything more complex (a few software companies have modified SPICE to allow more versatility in the use of transmission lines). A second problem is the need to integrate through long transient responses to obtain the steady-state response; this is an especially difficult problem in high-frequency circuits having long time constants. SPICE3 includes some features that minimize this problem, but SPICE2 doesn't. Finally, SPICE goes into cardiac arrest if a circuit contains loops of capacitors and voltage sources or cutsets of inductors and current sources; many matching and filter circuits have such structures.

SPICE is nearly ideal, however, for switching and logic circuits. It can simulate a wide variety of nonlincar devices, circuits, and phenomena. For example, SPICE can be used (although sometimes with difficulty) to design oscillators; HB is relatively poor for this task.

Harmonic Balance

Harmonic-balance analysis effectively partitions a circuit into two subcircuits: the *linear subcircuit*, which contains all the linear parts, and the *nonlinear subcircuit*, which contains only nonlinear elements. The two subcircuits are connected by a number of ports. Figure 2 illustrates this partition.

The voltages at these interconnecting ports – the DC, fundamental frequency, and its harmonics – are treated as circuit variables. The harmonicbalance process iteratively tries to find a set of these voltages that satisfies (1) the linear circuit equations of the linear subcircuit (usually a multiport admittance matrix), and (2) the nonlinear equations describing the nonlinear subcircuit. The linear equations are easily solved in the frequency domain, but the nonlinear equations must be solved in the time domain. The frequency-and time-domain quantities are related by a Fourier series.

Again, an astute reader might anticipate the well known difficulties:

1. The iterative solution process has no guarantee of success. "Convergence failure" is the bane of all HR users.

2. If there is only one excitation frequency, all is well; however, if two frequencies are used (e.g., in a two-tone test for IM), how does one convert between the frequency and time domains? Fourier transforms for such "noncommensurate" frequencies exist, but they don't work as well as classical, single-tone Fourier transforms.

3. Fourier transforms (especially those used for two-tone IM analysis) have limited numerical range. Weak IM products are often lost in the numerical noise of the Fourier transform.

4. Not obvious from the above description is the fact that each iteration of the solution process requires inversion of a huge matrix. For this reason, HB analysis is inherently very slow; reasonably efficient HB analysis of a large circuit requires a lot of memory and computer power.

In spite of these difficulties, and partly because of aggressive marketing, HB simulators have become the most popular tools for analysis of nonlinear microwave circuits, and they are rapidly taking over RF design as well.

Volterra-Series Analysis

Volterra-series analysis can be described as a perturbation method: the RF signal is viewed as a small perturbation of the DC bias voltage at each node in the circuit. This is not much different from the linear equivalent circuits with which we are already familiar. For example, the conductance g_d of a biased diode junction is:

$$g_{d} = \frac{dI_{d}}{dV_{d}} \bigg|_{V_{d} = V_{bias}}$$
(1)

where V_d is the junction voltage, I_d is the current, and V_{bias} is the bias voltage. From this, the small-signal junction current under RF excitation i_d is:

$$\dot{\mathbf{i}}_{\mathrm{d}} = \mathbf{g}_{\mathrm{d}} \mathbf{v}_{\mathrm{d}} = \frac{\mathrm{d}\mathbf{I}_{\mathrm{d}}}{\mathrm{d}\mathbf{V}_{\mathrm{d}}} \mathbf{v}_{\mathrm{d}}$$
(2)

with $V_d = V_{bias}$ and where v_d is the small-signal RF junction voltage. This is simply the linear response of the diode.



Figure 3. The circuit is represented by linear, second-, and thirdorder terms.

Equation 2 can be viewed as the first term in the Taylor-series expansion of the nonlinear drain current,

$$i_{d} = \frac{dI_{d}}{dV_{d}} v_{d} + \frac{1}{2} \frac{d^{2}I_{d}}{dV_{d}^{2}} v_{d}^{2} +$$
(3)
$$\frac{1}{6} \frac{d^{3}I_{d}}{dV_{d}^{3}} v_{d}^{3} + \cdots$$

where the obviously nonlinear v_d^2 and v_d terms account for the distortion in the device. Volterra series analysis provides a recursive method for calculating the current represented by these terms directly in the frequency domain (Figure 3). These currents are then treated as excitations of the linear circuit; as a result, only linear circuit analysis need be performed! For this reason Volterra series analysis is much faster than either harmonic-balance or time-domain analysis. Furthermore, no Fourier transforms are used, so the numerical range is limited only by machine precision. Very low IM levels can be calculated by Volterra analysis.

This remarkable efficiency has a price, evidenced by equation 3: the Taylor series of equation 3 is accurate only for small voltage deviations near the bias point. If the signal is too large, accuracy suffers. Volterra series analysis is useful only for weakly nonlinear circuits, or circuits operated well below saturation. However, it is very good for analysis of intermodulation distortion, and most RF engineers will agree that calculating IM levels is a major interest.

C/NL2 for Windows from Nonlinear Technologies [5] is the only real Volterra simulator on the market. The distortion analysis in SPICE is, in fact, a type of Volterra analysis; however, it is applicable only to diodes and bipolar transistors, and because of poor device modeling, is not very accurate.

Unleash the power of your PC!



Only Compact Software offers a complete family of RF and microwave design tools for Windows!

equency-Domain Simulation - Compact Software offers a implete family of linear and nonlinear circuit simulation tools r the PC. The Super-Compact linear simulator offers curate analysis and optimization of circuits from DC through illimeter-wave frequencies. The Microwave Harmonica inlinear simulator builds on this foundation by adding irmonic-balance nonlinear analysis and optimization. icrowave Scope completes the family by adding models of itoelectronic devices including laser diodes, detectors, and ier-optic links.

me-Domain Simulation - Compact's **Super-Spice** nulator combines the traditional capabilities of SPICE with ph frequency models for active devices and microstrip scontinuties. A unique electromagnetic field solver provides curate modeling of inter-trace coupling effects.

:hematic Capture - Compact's **Serenade Schematic litor** makes capturing RF and Microwave designs quick and isy. Complete symbol libraries are included for both device id layout features, allowing designers to drive the complete pture-simulate-layout process. **Physical Layout** - **Serenade Layout**, based on AutoCAD, uses information from the designer's schematic to automatically generate a finished layout. Data is quickly post-processed to popular manufacturing formats.

System Simulation - The Microwave Success system simulator allows entire systems to be simulated and optimized.

Device Modeling - Compact's **Netcom** and **Scout** programs allow data to be acquired from popular vector network analyzers and fitted to popular device models for simulation.

Best of all, Compact's entire family of high-performance PC CAD software is available NOW!



Device Modeling

Nonlinear analysis is only half the task. Analyzing a circuit without accurately modeling the solid-state device is like painting a house without cleaning and scraping it—the results just won't hold up.

SPICE has been around long enough that large libraries of commercial devices are available. These tempt the user to think that the modeling problem has already been solved. Unfortunately, many of these models are not very accurate; there is a wide variation in the parameters of individual devices, and many models just don't work for certain phenomena. For an example of the latter, few transistor models are adequate for distortion calculations, and the bipolar transistor modeling for distortion analysis in SPICE is seriously flawed.

An enormous amount of work is currently being applied to the modeling of devices – especially FETs – for harmonic-balance analysis. Most of the modeling work has been directed to single-tone power circuits: power amplifiers, frequency multipliers, and similar components. Virtually all the "canned" FET models in HB simulators are inadequate for IM analysis. Bipolar models are better for IM, but still not very accurate. Diode models are OK, but diodes are used primarily in mixers, and HB simulators are so inaccurate that they are useless for mixer IM analysis. HB simulators generally work well for mixer conversion loss calculations.

Volterra-series analysis offers the easiest modeling task [6]-[8]. All that is necessary to model a device for Volterra analysis is a linear equivalent circuit and two more numbers for each nonlinear circuit element: the second and third derivatives in (3). This is true also for nonlinear capacitors and inductors; one need provide only the derivatives of their charge-voltage or flux current characteristics. These can be found by numerical differentiation, or, if the device's nonlinearities are very weak, and numerical differentiation is inaccurate, by RF measurements.

Why Doesn't It Work?

I have observed a general malaise about nonlinear analysis. Many engineers who are comfortable using SPICE have had poor results with harmonic balance, have become disheartened, and seem ready to give up. This is really a pity, because, used correctly, these tools are extremely valuable.

Software companies must accept some of the blame for this situation. For many years, they have approached nonlinear analysis with the attitude that the engineer can treat nonlinear circuit analysis as a "no brainer"; just plug in the problem, crunch the numbers, and accept the result. Linear simulators are more or less tolerant of this type of ignorance, but nonlinear simulators aren't. You must know what you're doing.

Here, then, is a short list of common difficulties and their solutions:

1. HB simulators can't do anything you want. They are best for mixer con-



INFO/CARD 51

version loss analysis and single-tone power circuits. They are virtually useless for mixer IM, IM in saturated power amplifiers, or mixer compression levels. The simulator is OK for IM in small-signal amplifiers, but the device models are probably inaccurate. You might want to consider adding a "user-defined" model for FETs.

2. Remember, your device and circuit-element models must be valid at DC and all harmonics as well as the fundamental frequency.

3. Use conversion-matrix analysis if available, not two-tone HB, for mixer calculations. It is much faster and more accurate.

4. Don't use more harmonics than necessary. Four or five is usually enough for FET circuits, unless they are driven into hard saturation; diode circuits, because of their stronger nonlinearities, may require eight.

5. When you have a new problem, start out simple. Use only ideal elements (e.g., an'ideal transformer instead of a balun) and leave out complex bias circuits, etc. When you have the basic design established, start replacing the idealized elements, one at a time, with real ones. Trying to stuff all the complex things into the circuit at the outset leaves you with too many variables; then you can't optimize the circuit.

6. Accuracy in HB is usually reasonable only for fundamental-frequency outputs and low harmonics. Accuracy degrades for higher harmonics. An attempt to calculate the fifth-harmonic output level of a power amplifier is probably futile.

7. Many nonlinear phenomena (especially high-order IM, spurious responses, and harmonics) are very sensitive to signal level and circuit parameters. This high sensitivity inevitably degrades accuracy. For example, don't expect to be able to simulate fifth-order IM or a high-order mixer spurious response. It just won't work.

8. In the final analysis, harmonicbalance analysis is a poor choice for IM analysis. Consider using Volterra analysis for IM problems.

Convergence problems

1. Make sure that a node is not isolated at DC. For example, a node connecting two capacitors has an indeterminate DC voltage.

2. The process of partitioning the circuit into linear and nonlinear subcircuits can cause difficulties. Often, this leaves part of the linear circuit disconnected, and numerical problems result. Adding large-value resistors (e.g., 1 meg) between nodes of nonlinear elements and ground often solves this problem.

3. It is easy to enter data for device models that just won't work. Be sure your drain current function really reaches zero at pinchoff, and does not rise again below pinchoff. Check the transconductance and linear gain predicted by the nonlinear model, and be sure it is consistent with measured S or Y parameters.

4. Convergence problems are worse at high power levels. Often it is faster to perform a simulation over a range of input power levels instead of just one high level. HB simulators often use the previous result as the initial estimate of the next. Convergence at many small steps is fast; one big step, from zero to a high level, is much slower.

Conclusions

Nonlinear distortion, and other nonlinear effects, are among the meanest beasts in the RF wilderness. Nonlinear circuit simulation is the thing that can tame them. These tools, however, are not enough; inevitably, success requires some intelligent involvement of the user. It is especially important to choose the right tool for the problem at hand. I hope this article helps in that regard. RF

About the Author

Steve Maas is President and Principal Consultant of Nonlinear Technologies, Inc., which specializes in nonlinear circuit analysis, software, and consulting. He received BSEE and MSEE degrees from the University of Pennsylvania in 1971 and 1972, respectively, and a Ph. D. in Electrical Engineering from UCLA in 1984. Steve is the author of Microwave Mixers, (Artech House, 1986 and 1992) and Nonlinear Microwave Circuits (Artech House, 1988). From 1990 to 1992 he was the editor of the IEEE Transactions on Microwave Theory and Techniques. He received the Microwave Prize in 1989 for his work on distortion in diode mixers. He is a Fellow of the IEEE. He can be reached at P.O. Box 7284, Long Beach, CA 90807, or by phone/fax at: (310) 426-1639.

References

l. Nagel, L. W., "SPICE2: A Computer Program to Simulate Semiconductor Circuits," Electron. Res. Lab., Univ. of California, Berkeley, Memo ERL-M520, May, 1975.

2. Kundert, K. A., and Sangiovanni-Vincentelli, A., "Simulation of Nonlinear Circuits in the Frequency Domain," *IEEE Trans. Computer-Aided Design*, vol. CAD-5, 1986, p. 521.

3. Rizzoli, V., Lipparini, A., and Marazzi, E., "A general-Purpose Program for Nonlinear Microwave circuit Design," *IEEE Trans. Microwave Theory Tech.*, vol. MTT-31, 1983, p. 762.

4. Maas, S. A., "A General-Purpose Computer Program for the Volterra-Series Analysis of Nonlinear Microwave Circuits," *IEEE MTT-S International Microwave Symposium Digest*, pp. 311-314, 1988.

5. Maas, S. A., C/NL2 for Windows: Linear and Nonlinear Microwave Circuit Analysis and Optimization, Artech House, Norwood, MA, 1993.

6. Maas, S. A., "Analysis and Optimization of Nonlinear Microwave Circuits by Volterra Series," *Microwave Journal*, vol. 33, no. 4, p. 245 (April, 1990).

7. Maas, S. A., "How to Model Intermodulation Distortion," *Invited Paper, IEEE MTT-S International Microwave Symposium Digest*, pp. 149-151, 1991.

8. Maas, S. A., Neilson, D., "Modeling GaAs MESFETs for Intermodulation Analysis," *Microwave Journal*, vol. 34, no. 5, pp. 295-300 (May, 1991).



INFO/CARD 52

RF design awards

CircleX Program Analyzes S Parameter Data

By Chris Buckingham

CircleX is a simple yet powerful tool for inspecting and investigating transistor S parameter data sheets provided by the industry. With CircleX one can view the stability and gain properties of any given device. By displaying the parameter boundaries on the Smith chart the user is able to visualize the overall properties at a glance. This contrasts dramatically with looking through rows and columns of tabulated data.

NircleX is composed of two blocks: Jan input data editor, and a stability/gain calculator and display module.

Data Editor

CircleX accepts common-emitter (source) two-port data in S, y, or h formats. The input editor can read from one to ten sets of data entered via the keyboard and can be stored and retrieved from disk. The file format can be viewed and edited with any line/screen text editor, allowing the addition of comments, titles, or any other information to the file. While in the editor, the user selects a single set (frequency) at a time, and once selected the user can jump out of the editor and go to the stability/gain calculator.

Stability/Gain Calculator

The stability and gain calculations start out in text mode and give the user the choice of investigating one of four configurations for the same device:

Common-Emitter (Source)

Common-Base (Gate) Common-Collector (Drain)

or Cascode

Once a configuration is selected, the user can proceed with the calculations directly in text mode or use the graphics interface by pressing the "F1" key. We will describe the graphics display to explain the overall function of CircleX, the text mode being the same except that it accesses the equations directly, prompting the user for specific inputs.

After pressing the "F1" key, the display will appear as shown in Figure 1. Here we have entered the common emitter data for a bipolar transistor at 1 GHz and 10 V, 10 mA bias (see HXTR3103.S file), and examine the common-base configuration and some noise gain circles for the purpose of illustration.

There are two planes. The left side is the source-plane, the right side the load-plane. The source-plane represents all possible impedances that can attach to the device input port, and the load-plane represents all impedances that can attach to the output port. These impedances are shown on polar Smith charts and we have simultaneous display of the termination reflection coefficient and its corresponding impedance.

The cursor keys can be used to position the cross-hair anywhere on the chart. The cross-hair represents the independent cursor (the cursor we can move around at will). The opposite plane will have a circular cursor which is fixed (a dependent cursor, to be explained shortly).

By default we are placed actively in the source-plane, but we can jump to either plane (input or output) by pressing the "F1" key for the source side or the "F2" key for the load side. When we say the "active" side we mean that we can select any impedance (source or load) with the arrow (cursor) keys. At default the cursors are homed at the center of the chart. This is the 50 Ω , zero reflection coefficient point on the chart, which is the condition where we measured our S parameters.





Figure 1. CircleX graphics display.



VNA Amplifiers +17.5dBm, 0.5to 2.5GHz only 295

Very New Amplifiers...at a very affordable price, from Mini-Circuits! Yes, VNA-25 RF amplifiers are very small, yet incredibly powerful (+17.5dBm typ. output at 1dB compression). The SOIC-8 pin surface mount units operate directly from a +3V to +5V single DC supply with 18dB typ. gain and cover the popular 0.50-2.50GHz wireless band. These units are very easy to use because all capacitors are internal and RF/DC connections are separate, eliminating the

need for both external coupling capacitors and an RF choke. You can buy these very new amplifiers for the low price of just \$2.95 ea., qty.1000. Development qty.10, only \$4.95ea.! So, call Mini-Circuits today for immediate off-the-shelf availability and guaranteed 1 week shipment.



Freq.(GHz)	.58	.8-1.0	1.0-2.0	2.0-2.5
Gain (dB) typ.	14.0	17.0	18.0	16.0
Max. Output (dBm) @1dB Comp. typ.	+18.0	+18.5	+17.5	+17.0
I P 3rd Order (dBm) typ.	+27	+27	+27	+27
VSWR Output typ. VSWR Input typ.	1.5:1 6.4:1	1.7:1 2.8:1	1.7:1 2.0:1	1.5:1 1.4:1

DC Power.: +5.0V for specified performance. Current,(mA): 85typ., 105 max. Thermal Resistance. Junction-to-case: 125° C/W Price (\$) ea. : 2.95 (qty. 1000), 4.95 (qty. 10).

•All specs at 25°C (case temp. 35°).

•Available in Tape and Reel.

•MTTF at 150°C max, junction temp.: 3 x 10⁷ hrs.typ. "Case" is defined as mounting surface of leads.

Mini-Circuits...we're redefining what VALUE is all about!

P.O Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718)332-4661

For detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER • MICROWAVE PRODUCT DATA DIRECTORY • EEM • MINI-CIRCUITS' 740- pg. HANDBOOK.

CUSTOM PRODUCT NEEDS...Let Our Experience Work For You. INFO/CARD 53

F 180 Rev Orig

WRH

display are shown in Table 1.

Referring back to Figure 1, the stability circles are calculated and plotted for both the source and the load planes and the stable regions are then filled in green. These represent the impedances that produce stable outputs at the opposite port, which can then be conjugate matched. Therefore, any impedance on the Smith chart that is not in the green cannot be conjugate matched, and instability will occur if this is attempted.

If a device configuration is unconditionally stable, then both planes will be completely green, meaning that any combination of source/load terminations can be selected and, therefore, simultaneous conjugate matching at both ports will provide the maximum available gain and the lowest return losses. However, in most cases, particularly at lower frequencies where gain is high, we invariably have a conditionally stable configuration only, which requires careful selection of impedances.

The "F3" Link function

We will describe the "Link" process by illustration. If we select an independent source impedance by moving the cross-hair to some value of choice and then toggle "F3" on, the program will calculate the output impedance of the opposite port (in this case the load side), and will move the circular (dependent) cursor to the conjugate matching impedance and will then calculate the overall transducer gain GT in decibels and display the value next to the "F4" key automatically. This means that the independent cursor can be moved around, and the dependent cursor will track as described. The catch is that if the independent cursor is not in the green area, the dependent conjugate match will not be realizable, and the value of the impedance will fall outside the Smith chart.

When an unstable condition occurs during "Link", the dependent cursor will be placed on the outside periphery of the Smith chart to indicate this condition and will not move off the screen. However, the actual value of the impedance is displayed numerically bellow the respective Smith chart. This is valuable information if one wishes to evaluate the potential of the amplifier as an oscillator! It becomes a sort of reverse logic and we won't delve into it here, but this can be useful in "nega-

F1	selects the Source-Plane (Ts), as the active cursor
F2	selects the Load-Plane (TI), as the active cursor
F3	link(on/off) will toggle the Link function on or off
F4	calculates and displays transducer gain value GT in dB
F5	activates noise parameter data entry/editing
FG	not used
FO F7	alcong on posets the digplay (some as switing and entering again)
F1	clears or resets the display (same as exiting and entering again)
	use this key to unclutter the screen of too many circles, etc.
"Page Up"	(PgUp) increases cursor step size by ten fold
"Page Down"	(PgDn) decreases cursor step size by ten fold
"Home"	returns the independent cross-hair to home base (center of graph)
"Esc"	when in the F5 noise editor, Esc jumps you back to
	previous entry fields
"Esc"	quits the graphics display (all data is erased!), returns to text mode
"Enter"	press to enter numeric data or skip to next entry
"Left/Right" arrows	move the cursor horizontally
"Up/Down" arrows	move the cursor vertically
"Shift/Print Screen"	used to dump graphics display (need GRAPHICS COM)
Sinter rint bereen	used to dump graphics display (need dight mob. com)

Table 1. CircleX command keys.

tive resistance" oscillator design work.

Disabling the "F3" link function will not return the dependent cursor to "home", but will simply leave it where it was last, and GT will not be automatically updated. This leads to the "F4" key, which is used to calculate the transducer gain GT at a pinch, so that it will give us the gain for the existing source and load impedance settings. For example, if we "home" the source and load cursors (both at center of charts) and press "F4", we will get the insertion gain $(10\log_{10}(S_{21})^2)$ dB. This is the gain obtained if the device is driven directly with a 50 Ω source and the output is loaded with a 50 Ω resistor. This condition was used to measure our S parameters on the network analyzer.

The "F5" Noise key

This key allows for the display of noise circles in the source (input) plane and is used to enter optimum source reflection data to minimize amplifier noise. Manufacturers such as HP, Avantek, Motorola, and several others provide this data, particularly with gallium arsenide FETs and bipolars used in UHF and microwave applications. Pressing "F5" will activate an entry field on the left bottom side of the screen. Once noise parameters are successfully entered, we can display constant noise circles on the source plane and evaluate the stability and associated power gains for various source impedances.

Finally, all that is left is the numerical entry that we make. If we are in the source-input plane and the prompt cursor is in the Gp field, entering a number (dB) will display the input constant power circle. The last entry is always highlighted and any previous entries are darkened for reference. The same conditions apply to NF (noise figure in dB). To get into the NF field from Gp, hit the "Enter" key without a numerical entry, and do the same to go from NF to Gp.

When we plot constant power circles, the gain in decibels associated with that circle (Gp operating gain) can only be realized for impedances that fall inside the Smith chart and in the green area as well as on the power circle locus. The power gain circles require or assume a conjugate match at the opposite port.

Interestingly enough, CircleX really doesn't need the power circle. It suffices to turn on "Link" and move around until one obtains the gain required. However, power circles give a sense of range and scale, and indicate the boundaries at a glance.

To wrap up we will describe the filing format used in CircleX and complete the discussion with an example tested in Berkeley 2G.6 Spice.

File Management

We start with data taken from manufacturers or measurements and we enter the data manually via the keyboard using CircleX's editor or, via a word processor. CircleX will only read and write S parameter files. The editor will accept y and h data in rectangular format that is entered directly into the editor via keystrokes. These are then internally converted to polar S format which can be saved to disk.

CircleX has a small library of files to



Figure 3. BFR90A amplifier schematic.

illustrate its operation. The directory is as follows:

AT-00572.S	1758
AT-01672.S	1764
AT-41472.S	1757
AT-8111.S	2088
BFR90A.S	377
BFR96.S	694
MRF901.S	593
HXTR3103.S	2099
EMPTY.S	1657

Each user can create an unlimited number of files.

All files have the "S" extension for convenience, but any DOS path\file naming convention can be used. If you don't remember the file name while in CircleX, then you can "shell" to DOS, by pressing the "F7" key while in the editor window, and then find a "DIR".

To load a file you must type the file name and the extension exactly as it appears in the disk directory into the "FILE NAME" window, then press the "Enter" key. If the file is located and data is found, then the editor will stop at the highest set# found in the file, or stop at set# 10, whichever is smallest. File "EMPTY.S" has no data, and if loaded into CircleX, it clears all set# buffers.

To save a file you must be in the "FILE NAME" window and press control-S to invoke the file save mode, then you type the file name you wish to use and press the "Enter" key. The data will be saved up to the set# displayed in the editor window, this means that to save all sets you must be at the last (highest) set#. Also, CircleX will not alert you of any existing file names, and does not create file backups. Any overwrites will eradicate any existing comment fields created with a text editor. Save the data first with CircleX, and then add comments and additional information with the text editor later.

If we look at file HXTR3103.S with a text editor we can examine the basic rules used to file the data.

* Salad S-Parameter File *

* HP General Purpose BJT 2N6838 (HXTR-3103) VCE=10 V Ic=10 mA 25C * Noise Data

*	Freq	Fmin	Topt	Angle	Rn
	(GHz)	(dB)	(Mag)	-	(Ω)
*	0.5	1.4	0.121	96	114.4
*	1.0	1.7	0.301	121	15.2
*	2.0	2.5	0.461	173	5.2
*	3.0	3.3	0.553	-157	8.4
*	4.0	4.2	0.648	-139	13.4

SET# 1 FREQ1.00000E+08 S11 70.50000E-02 < -5.00000E+01 S21 24.26600E+00 < +1.49000E+02 S22 90.30000E-02 < -2.00000E+01 S12 15.00000E-03 < +6.00000E+01

SET# 2 FREQ 2.00000E+08 S11 64.20000E-02 < -8.60000E+01 S21 19.05500E+00 < +1.29000E+02 S22 74.20000E-02 < -3.10000E+01 S12 25.00000E-03 < +4.90000E+01 SET# 3

FREQ 3.00000E+08

S11 60.60000E-02 < -1.10000E+02 S21 14.96200E+00 < +1.16000E+02 S22 62.40000E-02 < -3.70000E+01 S12 30.00000E-03 < +4.30000E+01

SET#4

FREQ 4.00000E+08 S11 57.90000E-02 < -1.27000E+02 S21 12.02300E+00 < +1.08000E+02 S22 54.80000E-02 < -3.80000E+01 S12 33.00000E-03 < +4.10000E+01

SET# 5

FREQ 5.00000E+08 S11 56.50000E-02 < -1.39000E+02 S21 10.11600E+00 < +1.02000E+02 S22 49.90000E-02 < -4.00000E+01 S12 36.00000E-03 < +4.10000E+01

SET#6

FREQ 6.00000E+08 S11 55.20000E-02 < -1.49000E+02 S21 86.10000E-01 < +9.70000E+01 S22 46.70000E-02 < -4.00000E+01 S12 38.00000E-03 < +4.20000E+01

SET#7

FREQ 7.00000E+08 S11 56.20000E-02 < -1.57000E+02 S21 74.99000E-01 < +9.30000E+01 S22 44.10000E-02 < -4.20000E+01 S12 40.00000E-03 < +4.30000E+01

SET# 8

FREQ 8.00000E+08 S11 55.90000E-02 < -1.62000E+02 S21 66.83000E-01 < +8.90000E+01 S22 43.00000E-02 < -4.20000E+01 S12 43.00000E-03 < +4.40000E+01

SET# 9

FREQ 9.00000E+08 S11 55.80000E-02 < -1.68000E+02 S21 59.57000E-01 < +8.50000E+01 S22 41.20000E-02 < -4.30000E+01 S12 45.00000E-03 < +4.60000E+01

SET# 10 FREQ1.00000E+09 S11 57.10000E-02 < -1.69000E+02 S21 53.30000E-01 < +7.80000E+01 S22 40.80000E-02 < -4.00000E+01 S12 52.00000E-03 < +4.20000E+01

* End of File *

The file shown above was created in CircleX and uses the following key words to define each data field: SET#, FREQ, S11, S21, S22, and S12. The magnitude values are delineated from the angle values by the less than sign "<". A space "", or comma "," is also acceptable. Comments can be placed





anywhere, and should be preceded with an asterisk "*" to avoid confusion with the key data field words. The S values can be entered in any order desired; S_{11} - S_{22} - S_{21} - S_{12} , or S_{21} - S_{12} - S_{11} - S_{22} , etc. Numerical entries can be in any format, as in the following example:

250.450 MIIz - 2.50450E+08 =250450000 = 250450K

In order to demonstrate how CircleX can be used, we will simulate a typical scenario by running a SPICE analysis. Start with a bipolar NPN transistor model. In this case we choose model BFR90A, and bias the device at VCE=10 V, and Ic=5 mA, and also choose to set the temperature at 35° C. The common-emitter S parameters are then measured at 500.000 MHz and entered into CircleX via the editor keyboard.

Once loaded into CircleX, we move to the stability/gain calculator and select Ke (common emitter) configuration, and activate the graphics display. Figure 2 shows the resulting stability regions for this device. The device is conditionally stable, and we choose to evaluate the device for a gain of 20 dB with the input matched to the source. In order to accomplish this, we jump to the load-plane by pressing "F2", and enter 20.0 in the Gp field. We can now move the independent cursor to a point on the 20.0 dB power circle. In this case we move the load impedance to $6.424+19.22j \Omega$ and activate the link "F3" function. The resulting matched source impedance appears in the

upper left quadrant of the sourceplane with a value of $5.721+61.84j \Omega$.

Since we are going to use a 50 Ω measurement system to analyze the amplifier, we design simple matching "L" networks to transform 50 Ω into the source and load terminations indicated above by CircleX at 50 MHz:

Source	Kesistor side C _{series} 1.80 pF	Transform side L _{shunt} 14.96 nH
(50 Ω) Load (50 Ω)	C_{series} 12.06 pF	L _{shunt} 5.79 nH

We can now assemble the amplifier as shown in Figure 3, and submit the network list to SPICE and remeasure the two-port parameters of the BFR90A device with these matching networks attached. The results are shown in Figure 4 and Figure 5, and in this case we get a narrow band response that provides a 20 dB power gain at 500 MHz with a very low return loss at the input port.

The choice of where to pick values on the constant power circle is really a cut and dried process. There are infinite possibilities. However, the characteristics of the amplifier will vary considerably from point to point, and especially from quadrant to quadrant. Experimentation will show that bandwidth, noise, return loss, tunability, stability, and other factors all change along a constant power circle.

Requirements

CircleX will run on 386 or higher PCs with a VGA adapter/display system, platform DOS version 4.0 or



Figure 5. BFR90A input reflection S₁₁ magnitude.

higher.

Program CircleX is a subset of program SALAD version 1.08 (Spice Accessory for Linear Amplifier Design). It is available from Argus Direct Marketing. To order, see ad on page 69. RF

References

1. Carson, Ralph S., High-Frequency Amplifiers, John Wiley & Sons, Inc., 1975.

2. Pozar, David M., Microwave Engineering, Addison-Wesley Publishing Co. Inc., 1990. 3. Bowick, Chris, *RF Circuit Design*, First Edi-

tion, SAMS/Prentice Hall Division, 1992.

4. Gray, David A., Handbook of Coaxial Microwave Measurements, General Radio Co., 1968.

5. Hewlett Packard AN 95-1, "S-Parameter Techniques for Faster, More Accurate Network Design".

6. Hewlett Packard AN 77-1, "Transistor Parameter Measurements".

7. Hewlett Packard AN 77-3, "Measurement of Complex Impedance'

8. Hejhall, Roy "RF Small Signal Design using Two-Port Parameters," Motorola Application Notes.

9. Power Basic Version 3.0, Copyright 1992 by Robert S. Zale.

About the Author

Chris Buckingham graduated with a BSEE from Northeastern University in Boston, MA. He was employed by Teledyne as a test engineer in discrete semiconductors, and later worked for ten years at the Raytheon Company as a product engineer, specializing in small-signal hybrid thick-film RF modules. He is presently engaged in power hybrids development. He can be reached at 158 Summer St., Somerville, MA 02143, tel: (508) 534-5776.

Surface Mount Guide

The new RF/IF Surface Mount Designer's Guide is now available, free of charge, from Mini-Circuits. This 48-page guide features up-to-date and complete product and specification information about Mini-Circuits' lines of RF/IF components for surface mount technology. Products include monolithic amplifiers, fixed attenuators, attenuators, switches, bias-tees, directional couplers, lowpass filters, frequency doublers, frequency mixers, I&Q modulators and demodulators, power splitter/combiners, switches and RF transformers. Mini-Circuits INFO/CARD #158

Decoder Application Note

Qualcomm's VLSI Products Group announces the availability of "Peripheral Data Mode Operation of the Q0256/Q1650 Viterbi Decoder", a 24-page application note describing how to implement the peripheral data mode for forward error correction in applications like INMARSAT, VSATs and other low data rate terrestrial or satellite data links. Qualcomm, Inc.

VLSI Products Group INFO/CARD #157

Military Cross Reference

Analog Devices offers a free Motorola-to-Analog Devices Military Product Cross Reference Guide identifying more than 120 of Analog Devices' products that functionally replace those which Motorola has planned for obsolescence. Analog Devices

INFO/CARD #156

Modulation Meter Data Sheet

A two-page data sheet on the Model 8211 FM/AM modulation meter has been released by Boonton Electronics. The data sheet lists all the specifications and enhancements to the Model 8211. Model 8211 provides high-performance, self-calibration capability, and true peak detection. All specifications are listed, including carrier frequency range, sensitivity, frequency modulation, deviation accuracy, and modulation bandwidth. Boonton Electronics Corp.

INFO/CARD #155

Measurement Equipment

Tektronix has announced the availability of its 1995 Measurement Products Catalog. More than 80 new products are detailed. The 596-page, soft-cover catalog's full-color product section provides a synopsis of Tektronix' business focus and features a variety of new form-factor measurement solutions. The catalog includes Tektronix partnerships/alliance solutions offered by Advantest and Rohde & Schwarz.

Tektronix, Inc. INFO/CARD #154

"Intelligent" Car Report

A new study on the "intelligent" automobile of the future has been released by Strategies Unlimited. The study forecasts a \$4.9 billion market for in-vehicle navigation, radar, and wireless toll collection systems within the coming decade. The comprehensive findings of this study are available in a 189-page report. Both system and RF component requirements are reviewed. The report is available for \$3,950. Strategies Unlimited INFO/CARD #153

Design Software Brochure

Compact Software has a new eight-page, four-color brochure describing the company's PC/Windows-based Serenade 6.5 software for integrated RF, microwave and lightwave design. Serenade software includes schematic capture, linear or nonlinear frequency domain simulation, simulation libraries and optional physical design software tools. Compact Software INFO/CARD #152

RF Design Software

Programs from RF Design provided on disk for your convenience

March Disk - RFD-0395

"CircleX Program Analyzes S Parameter Data" by Christopher Buckingham. For inspection and investigation of published or measured S parameter data, with Smith chart display. (Requires 386 or better, VGA display, and DOS 4.0 or higher).

Monthly program disks: \$25.00 (U.S.) \$30.00 (foreign)

Yearly Disk Sets and Annual Subscriptions Available: Call for Information

All orders must be pre-paid by check, money order, or major charge card. All checks must be in U.S. dollars and payable to a bank located in the U.S. *Prices include shipping*.

RF Design Software — Argus Direct Marketing Dept. 6151 Powers Ferry Rd., N.W. — Atlanta, GA 30339-2941 Tel: (404) 618-0398 — Fax: (404) 618-0347

Finite-Element Software on Alpha AXP

MacNeal-Schwendler has announced that several of its software product lines are available on Digital's AXP 64-bit workstations and servers. These products include MSC/NASTRAN v. 68, MSC/ARIES v. 6.1, and MSC/PATRAN release 1.4. Additional MSC product lines will become available on the AXP platform during 1995.

MacNeal-Schwendler Corp. INFO/CARD #151

Mathematical Software

Waterloo Maple Software has announced the release of THEORIST® 2 for the Macintosh and Power Macintosh. The program, with algebra and graphing, combines the power of advanced mathematics with a simple yet powerful graphical user interface. The "Click and Solve" technology eliminates the need to learn a programming language. THEORIST 2 handles algebraic equations and expressions, and has twoand three-dimensional graphing. THEO-RIST 2 is designed to work with 2 MB RAM and 2 MB on a hard disk. US commercial list price is \$299.00.

Waterloo Maple Software INFO/CARD #150

Active Filter Design

Eagleware has released the program =A/FILTER= which designs active electronic filters. =A/FILTER= synthesizes a wide range of structures, including GIC transform, single feedback, multiple feedback, state variable (biquadratic), dual amplifier, voltage controlled voltage source, and low sensitivity types. The program is a member of Eagleware's System 32 family of synthesis and simulation programs for DOS, Windows 3.1 and Windows NT. Active filter synthesis and simulation packages range from \$1195 to \$2235. Eagleware Corp.

INFO/CARD #149

Analog Simulation

Optimization System Associates is now shipping OSA90/hope[™] v.3.0. OSA90/hope is CAD software for simulation, modeling and optimization of linear an nonlinear circuits. Version 3.0 features 3D graphics, Space Mapping[™], and augmented libraries and optimizers. Space Mapping links "course" and "fine" models, such as empirical and electromagnetic models. The expanded library includes HEMT models. One-sided 11 and one-sided Huber optimization implementations are also included in version 3.0. OSA90/hope version 3.0 runs under X windows on HP, Sun, and DEC workstations. Its base price is \$20.000.

Optimization Systems Associates Inc. INFO/CARD #148

RF oscillators

Analysis and Optimization of Oscillators for Low Phase Noise and Low Power Consumption

By Ulrich L. Rohde and Chao-Ren Chang Compact Software, Inc.

This article presents investigations into the design, analysis and performance of practical voltage-controlled or tunable LC oscillators. Modeled versus measured performance of several common oscillator designs are compared, and the steps taken to obtain more accurate models for CAD analysis are noted.

Modern hand-held radios need low phase noise oscillators which show low power consumption. Traditional choices are either bipolar transistors or FETs. Typically, for frequencies up to 500 MHz, FETs have been considered more favorable, compared to bipolar transistors because of the low phase noise in frequencies above the higher f_{max} of bipolar transistors, which makes them more attractive. In this paper. We intend to evaluate the following topics:

I. AGC action via diode clamping

- A. Performance of FET oscillators in Class A Operation, self-limiting [1]
- B. Performance of Class A oscillators using a clamping diode between gate and source [2]



Figure 1. Comparison of measured and predicted S-parameters for the 2N4416, input and output.

C. Class A oscillator with source resistor [3]

II. Differential Oscillators using FETs and different bias points

The following are bipolar transistor oscillators:

A. 800 MHz Motorola VCO for handheld radios [4]



Figure 3. Equivalent circuit for the linear FET. The non-FET model follows the Spice approach by Statz and Curtice.



Figure 2. Comparison of measured and predicted S-parameters for the 2N4416 reflection coefficients.

- B. Analysis of the Motorola MC 1648M voltage controlled oscillator IC [5]
- C. BIP differential limiter VCOs from [6].

Considerable mystery has surrounded oscillator design and evaluating the above-mentioned circuits should help to shed some light in this area.

Another fascinating topic has been the modeling issue as a whole. For the



Table 1. Equivalent linear parameters for the FET equivalent circuit of Figure 3.
VOLTAGE CONTROLLED OSCILLATORS

1025 MHz

25 to 1025MHz (+7dBm output) From **\$1195** (5-49)

It's a fact! With Mini-Circuits new POS family of shielded, laser sealed voltage controlled oscillators, you pay less but get more... top notch quality, superior performance and value pricing.

25 MHz

Features include wide-band models with near octave linear tuning. Low SSB phase noise characterized at 100Hz to 1MHz offsets. Excellent harmonic suppression, typically more than 25dB. RF power output typically +7dBm, excellent for driving level 7 mixers. Miniature size, only 0.4 X 0.8 inch board space. Hermetically sealed and ruggedly constructed for tough environments. Best of all, Mini-Circuits high performance, highly reliable VCO's can be yours at value prices starting at only \$11.95 each (qty.5-49). To order from stock, call Mini-Circuits today.

DESIGNER'S KITS: K-POS1 \$124.95 (contains 1ea. all models). K-POS2 \$79.95(contains 1ea. all models except POS-75,-150,-300).

Model No.	Freq. Range (MHz) Min.	Phase Noise (dBo/Hz) SSB @10kHz Typ.	Harmonics (dBc) Typ.	Power 12V DC Current mA	Price (Oty.5-49) \$ ea.
POS-50	25-50	-110	-19	17	11.95
POS-75	37.5-75	-110	-27	17	11.95
POS-100	50-100	-107	-23	18	11.95
POS-150	75-150	-103	-23	18	11.95
POS-200	100-200	-102	-24	18	11.95
POS-300	150-280	-100	-30	18	13.95
POS-400	200-380	-98	-28	18	13.95
POS-535	300-525	-93	-26	18	13.95
POS-765	485-765	-85	-21	22	14.95
POS-1025	685-1025	-84	-23	22	16.95

300 MHz

Operating temperature range: - 55 C to +85°C. Current typically 4.5 mA greater at +15V.

PO Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718)332-4661

For detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER • MICROWAVE PRODUCT DATA DIRECTORY • EEM • MINI-CIRCUITS' 740- pg. HANDBOOK.

CUSTOM PRODUCT NEEDS...Let Our Experience Work For You.

F 195 Rev Orig



Figure 4. Oscillator test circuit.

purpose of obtaining data, Compact Software, Inc. has been doing its own parameter extraction and has always maintained that the parameters available from Spice libraries are not sufficiently accurate for high frequency applications. In particular, the use of these transistors in oscillators require reasonable assumptions for flicker noise and other related parameters. Also, one of the tests is to obtain agreement between the measured and simulated values for the same transistor at the same bias-point. Specifically, we mean that the S-parameters obtained from modeling and measured data must agree. Our experience in this area is based on a number of subcontracts. Among those are our activities with Siemens Semiconductors in Munich where CSI modeled their new 25 GHz f_t transistors, as well as GaAs FET lines, including new power FETs.

The FET Model

In our opinion, the best known N junction FET is the 2N4416 or members of its family. Table 1 shows the elements circuit file used for optimization. Figures 1 and 2 show the agreement of measured versus predicted Sparameters.

For the purpose of this paper, we took measured Y-parameters covering



Figure 5. Output DC-IV curves with load line showing case with and without diode.

the frequency range up to 450 MHz and forced an optimization against the complex equivalent circuit for the linear FET.

We will not go into the equivalent procedure for nonlinear parameters but Compact Software's Scout program, using the modified Materka model or the Statz or Curtice models can generate an equivalent nonlinear circuit for junction FETs, which are perfect for this procedure.

FET Oscillator

The first FET oscillators looked fairly similar to those which came from the tube technology. Figure 4 shows an oscillator takon from [1].

This oscillator was both built, measured and modeled. Published reports in [7] and [8] caused considerable interest because no other work had ever mentioned the noise contribution of this diode. The basic oscillator is a modified Colpitts oscillator which has a clamping or rectification diode in parallel at the input. The noise performance and output power of this transistor oscillator depends highly on the nonlinear parameters of the transistor. The purpose of the diode is claimed to provide more uniform performance such as constant output power over tolerances of the transistor



Figure 6. Predicted phase noise of the oscillator of Figure 4 with and without the diode.

or temperature [7, 8]. The diode had been described as increasing the stability, but it only improves the thermal drift, not the SSB noise.

In an effort to better understand this circuit shown in [7], we have done an evaluation of the phase noise for three cases: no diode, a clamping diode and a RF-bypassed source resistor. Starting conditions are essentially the same transistor circuit shown in Figure 4; however, we initially eliminated the diode and the source resistor and then exchanged or added components. We used a specific nonlinear model, as implemented in the nonlinear program Microwave Harmonica with phase noise analysis capabilities, and added the parameters which described the transistor's noise performance.

In the previously mentioned publication, phase noise both with and without the diode was presented and compared to measured data [7]. The diode, which was connected in parallel between the gate and source, is activated only in an RF sense to just look at the noise contribution without affecting the DC bias point. One needs to know that the junction FET already has a diode from gate to source and therefore, the circuit effectively puts two diodes with different threshold levels in parallel. Figure 5 shows the output phase plane of the oscillator for both cases

Next, we looked at the noise prediction with or without the diode. Considering the fact that the diode at this time is fully active and has changed the DC operating point, the output power will change by 8 dB. Since the phase noise is the ratio of two power levels, the absolute power output of the oscillator is irrelevant for close-in phase noise considerations. By looking at Figure 6, we get the same phase noise as reported in [7] and we also show the flicker noise contribution of the FET is the same when the diode is removed. With the diode, the output power is -6 dBm and without the



Figure 7. DC-IV output and load lines with and without the diode for a 2N3819 (library model).



Figure 8. Predicted phase noise with and without the diode for the oscillator of Figure 4, using the 2N3819 library model. Note the absence of flicker noise.

diode, the output power is +2 dBm.

The next step was to evaluate the quality of the Spice library models. Figure 7 shows the simulation of the load line using the parameters supplied by a third party Spice Library (PSPICE). Close examination of the DC/IV curve shows unrealistic behavior of the FET in the saturation mode. This type of early (simple) parameter extraction method is not sufficient for accurate high frequency applications. There is no provision for parasitic elements. Having exchanged the two transistor models for the same circuit, we re-calculated the noise and it again showed a significant difference (with and without the diode) consistent with the measured data previously reported, shown in Figure 8.

The output power for this oscillator was the same as the simulation with our model. This indicates that the calculation of the output power is less sensitive to the parameters which make the difference in the noise calculation. In the noise calculation, the two



Figure 9. DC-IV output curve with load line for a 470 ohm source resistor instead of the diode.

most relevant quantities are the loaded Q under operation, which the simulator predicts; and the noise contribution of the semiconductor. It is interesting to note that the Spice Library significantly underestimated the transistor noise contribution and provides unrealistic low close-in phase noise.

The next logical step was to evaluate the circuit without the diode, but with a resistor in the source. Figure 9 shows the output load line/DC-IV curves for the same circuit with 470 Ω resistor. The resulting output in this case is +1 dBm output which compares favorably with the case without the diode and, of course, the exciting question then arises, "What will the phase noise do?" Figure 10 shows all three cases: phase noise without the diode, AGC action with a 470 Ω source resistor, and with the diode. The phase noise with the diode still remains the worse case and the DC feedback is the best case. This is also consistent with reports in [3]. For further reducing the undesired "warm-up" effect of the FET at high bias point, one must go to



Figure 10. Predicted phase noise of the oscillator of Figure 4 without the diode, with the source resistor, and with the diode.

large emitter resistors as 1 k Ω or much more and may even have to bias the gate positive.

Figure 11 shows the circuit diagram of the 85-119 MHz FET oscillator from the Rohde & Schwarz SMDU signal generator. This signal generator, which is no longer in production, had the same specifications as the HP 8640 and obtained its extremely good phase noise with the use of a helical resonator. It also adheres to the statement made above whereby the DC bias of the transistor was provided by a fairly large source resistor of 1.5 k Ω , and an adjustable resistor at the gate is the optimum bias condition. The large DC feedback compensates for both tolerance in the device and temperature effects. This is the correct method in operating the transistor, rather than using a AGC diode.

Other questions arise in the modeling area. How much does the actual Q of the inductor affect the performance in high-Q cases like the 10 MHz oscillator? Is it permissible to allow the Q to be simulated at Q = 8, whereby Q =



Figure 11. Circuit diagram of the 85-119 MHz FET oscillator used in the Rohde & Schwarz SMDU signal generator.



Figure 12. Predicted phase noise of the circuit of Figure 4 with loaded Q of 135 and Q = 500, which is the same as $Q = \infty$.



Figure 13. Schematic of the HP 8662A VCO, which operates from 260 to 520 MHz.

500, which is obtainable at these frequencies, is used as a point of reference. If we examine a more modest Q, like 135, we get approximately 4 dB deterioration of phase noise, which shows up both close-in and far out. For high frequency applications above 30 MHz, it is certainly important to properly model the Q of the tuned circuit prior to its being connected to the



Figure 14. Predicted phase noise of an FET differential limiter oscillator for low current of 10 mA (lower curve).

transistor. Figure 12 shows the noise for different loaded Qs.

Using integrated circuits for reasons of DC coupling, one has to resort to symmetrical circuit for a differential limiter type oscillator circuit as shown in [3]. These circuit's outputs are more distorted; what about phase noise performance? We took the same circuit and, using FETs, modeled a differen-



Figure 15. Output waveform of an FET differential oscillator for three different bias points.



Figure 16. Extrinsic parasitics used to accurately model high frequency effects of FETs.

tial oscillator circuit. This circuit is consistent [3], but operating at 10 MHz and having a less elaborate DC circuitry (see Figure 13) which shows the differential FET oscillator which has become the heart of the Hewlett-Packard HP 8662 signal generator.

The initial starting condition had the common source resistor at 470 Ω , which produced the phase noise prediction of the first plot of Figure 14. By varying with the output load, the phase noise far out can be improved slightly. We finally decided to take more drastic steps and reduce the source resistor by a factor of 10. As can be seen, this changed the output phase noise significantly, with an improvement of approximately 12 dB across the board. The phase noise calculation is still somewhat optimistic because the FET model supplied is unrealistic in its flicker noise contribution, but it clearly shows the trend.

Figure 15 shows the output waveform as a function of DC bias, with the absolute output of the differential oscillator being -6 dBm.

The N junction FET model in SPICE does not consider any parasitics, which limits its practical high frequency use. Table 1 indicates that the first criteria for successful modeling has to do with a matching between predicted and measured S parameters.

Figure 16 shows the equivalent circuit for the packaged nonlinear FET. In order to model energy traps in the transistor, a series combination of R and C is identified as parasitic labeled CDSD and RDSD. By setting those two values to zero, the DC-IV curve shifts and now looks as shown in Figure 17. The fly-wheel effect to the right of the transistor has disappeared. This is the case with no diode connected and no emitter resistance. Figure 18 shows the time domain display of the device's drain current. It becomes obvious that this has a fairly narrow duty cycle and, therefore, a high harmonic content. For the sake of completeness, one should now look at a SPICE modeling of the same circuit. One should remember that the SPICE models are less complete for high frequencies. Also, the inherent dynamic range is less than that of our harmonic balance simulator. SPICE typically is lucky to get a 60 dB dynamic range. Our harmonic balance simulator has an 180 dB dynamic range. By inspecting Figure 19, it is apparent that there is no difference in resistance as the drain current is numerically unstable compared to the calculation in harmonic balance.

The big advantage SPICE offers is



Figure 17. DC-IV curve of the FET oscillator with the external parasitic effects removed.

that it looks at the transient response and not only at the steady state as supplied by the harmonic balance simulation. Figure 20 shows the "start up" condition for the same oscillator. The "start up" condition begins at the lower left-hand comer with current and voltage being at the zero level. By the time the voltage goes up to 3.5 V and higher, the current begins to saturate, and then oscillation starts. This moves the DC bias point to the left and then automatically settles. This curve then becomes similar as the previously shown DC-IV curve (Figure 19). The final interesting thing is the time it takes the oscillation to actually start. This is done by inspecting the load voltage. The oscillation hesitates 10 μ s, then the oscillation builds up to reach most of its amplitude after 25 μ s, and 50 μ s before it has stable amplitude. This is shown in Figure 21.

This ended our interest in FETs and we decided to look at the bipolar transistor circuits. Most hand-held radios for wireless applications will be built with silicon bipolar technology and the noise of those circuits will become an issue. The single transistor oscillator operating at 800 MHz already had been successfully modeled and was reported previously [4]. Figure 22 shows a plot of the predicted and mea-



Figure 19. SPICE analysis of the FET oscillator showing the drain current. Note the numerical instability, inherent in SPICE.



Figure 18. Drain current of the FET oscillator. Please note the short duty cycle.

sured phase noise as well as its schematic. Oscillators for highly integrated circuits make intensive use of differential types of transistor pairs. Figure 23 shows the standard two differential transistor pairs as offered by many suppliers. It has become the de facto standard for the pairs in either mixers or oscillators.

The first successful medium scale integrated circuit oscillator was built by Motorola (the MC1648M oscillator chip). A first inspection of the circuit indicates that there is no DC voltage difference between the chip and collector of the transistor on the left. Figure



Figure 20. DC-IV curve starting condition of the FET oscillator using SPICE (see comments in text).



Figure 21. Transient accuracy of the FET oscillator. It takes about 50 μ s before achieving a stable amplitude.



Low Noise OCXOS Compact package Fast warm-up Ultra-stable Low aging Vectron reliable

Low Noise OXCOs (4 - 25MHz)

MODEL	CO-717L2	CO-718SL2
Aging	1 x10°/day 3 x10'/yr	5 x10 ¹⁰ /day 1 x10 ⁷ /yr 2-5x10 ⁻⁸ /yr opt
0°C to 50°C -20°C to + 70°C	±1 x10 ^a ±3 x10 ^a	±5 x10° ±1 x10°
Phase 100Hz Noise 1kHz (4-12MHz) 50kHz	-145dBc/Hz -160dBc/Hz -165dBc/Hz	-155dBc/Hz -163dBc/Hz -168dBc/Hz
Size	2"x2"x1"* /4" height option	2"x2"x1"*

Low Noise OCXOs (25 - 200MHz)

TYPE	CO-724SL2	CO-725SL2
Aging	2 x10°/day 5 x10°/yr	5 x10 ¹⁰ /day 1 x10 ⁷ /yr
0°C to 50°C	±5X10 ⁻⁹	±5 x10°
-20°C to + 70°C	±1X10 ⁻⁸	±1 x10°
Phase 100Hz	-130dBc/Hz	-120dBc/Hz
Noise 1kHz	-145dBc/Hz	-135dBc/Hz
(75-125 MHz) 50kHz	-157dBc/Hz	-140dBc/Hz
Size	2"x2"x1"*	2"x2"x1%"
*Red	uced height ava	ilable





Figure 22(a). Schematic of the Motorola 800 MHz VCO.



Figure 22(b). Comparison between predicted and measured phase noise. The resistor between emitter and capacitive feedback divider reduces the flicker noise contribution.

24 shows the schematic of the internal oscillator as published by Motorola.

We were pleased to successfully model this circuit, but the resulting phase noise was quite surprising. Figure 25 shows the phase noise of the bipolar transistor IC. It is well understood that the phase noise of these oscillators is significantly higher than the phase noise of the FETs. It was quite surprising to find that the flicker noise contribution would worsen the



Figure 23. Pair of differential transistor amplifiers found in most modern IC designs.

phase noise to such a degree. We thereafter did an 'experiment wherein we changed the bias of the oscillator and thereby reduced the loop gain. The DC current was reduced from 3 mA to approximately 500 μ A. Since the flicker noise is extremely bias dependent, the phase noise improved, but the output power dropped by about 10 dB. The simulation of this circuit also showed a non-sinusoidal waveform at the output, which, due to



Figure 24. Schematic for the Motorola MC1648 oscillator IC.



Figure 25. Simulated phase noise for the bipolar transistor oscillator at 10 MHz. By reducing collector currents to 500 μ A, flicker noise is improved from 30 dB to 52 dB at 1 Hz.

space constraints, is not being reproduced here. Further, a circuit which typically used for LSI application is shown in Figure 26 and is taken from [1]. These types of oscillators are actually being used for various applications and the interested user should use modern CAD tools to investigate their performance. Due to the heavy feedback in those oscillators, one will see in the simulation that they are not as sensitive to parameter variation of



Figure 26. Oscillator using a differential amplifier and a DC biasing scheme.



Figure 27. Schematic of the Motorola VCO.

CO VCO VCO VCO VCO PLL - Design Kit COMPACT SOFTWARE SSB Phase Noise plot / in dBc/Hz VCO Noise and Closed Loop Noise -20 -30 -40 -50 -60 SYNERGY VCO -70 SYNERGY VCO SYNERGY -80 200-400 MHz VCO -90 MH7 SYNERGY -100 SYNERGY NCO -110 VCO 400-800 MHz -120 -130 800-1600 MH7 SYNERGY -140 **VNERGY** 0.0 -150 -16 VCO 800 MHz KHz 10. KHz 1000-2000 MHz

Now Available From 200-2000 MHz!

Including Coaxial Resonator Models for Specialized Bandwidths

Synergy's new product line of Voltage Controlled Oscillators covers the spectrum of 200 MHz to 2000 MHz. These low cost, high quality models exhibit extremely low phase noise along with linear transfer characteristics. These new Voltage Controlled Oscillators can be supplied in surface mount or plug-in package styles. Additional information and specifications are available from the Synergy Microwave Sales and Applications Department.

ynergy Microwave Corporation 01 McLean Boulevard, Paterson, N.J. 07504 USA hone (201) 881-8800 or FAX (201) 881-8361





Figure 28. Modern ceramic resonator oscillator for hand-held cellular telephones.

the devices as might be expected. A particularly nice application of this type has been a Motorola VCO done entirely on silicon material. Figure 27 shows its schematic representation. The monolithic inductors used in the VCO were designed using Compact Software's Microwave Explorer program to model the effect of various ways of building those inductors. Measured and predicted Qs of the inductors show extremely good agreement. Figure 28 shows a discrete VCO. Considerable progress has been made here in high integration and first hand lavout of these as shown in the older version of Figure 29.

As mentioned, these types of circuits will be found in large integrated circuits. We decided to model the circuit from [6], shown in Figure 30. The difference between this circuit and other previously discussed circuits is that the tuned circuit is coupled very loosely to the transistor. We also made a modification to the circuit whereby we took the feedback from the second transistor rather than the first one and put the second transistor in the loop. Figure 31 shows a proper presentation with modern ICs.

When comparing these two cases with the modified one, we found an improvement in the SSB phase noise of approximately 6 dB with the same output power. Figure 32 shows the predicted phase noise and Figure 33 shows the output wave-form available at the collector. According to our simulation analysis, both circuits only provide +4 dBm output. We were not able to confirm the +17 dBm reported by the authors.

Circuit Optimization

The oscillator circuit itself provides several degrees of freedom over which the designer has control. One of the three key issues to consider is the DC operating point of the transistor. While it varies the output power, it more drastically changes the flicker noise as has been shown several times. Secondly, the feedback circuit as such is responsible for the loop gain and the loaded Q. Thirdly, some negative rather than positive feedback like resistive feedback between the emitter of the bipolar transistor and the capacitive voltage divider is responsible for the phase noise reduction to the flicker noise contribution. The automated optimization procedure for phase noise



Figure 30 Circuit of the K7HFD low-noise oscillator from [6].



Figure 32. Simulated phase noise of the oscillator of Figure 31.



Figure 29. Test oscillator with conventional SMD design for 900 MHz hand-held cellular telephones.

optimization as implemented in Microwave Harmonica can drastically improve the circuit.

Figure 34 shows the phase noise – before and after optimization – of the Motorola 800 MHz oscillator (Figure 16). The close-in phase noise at 1 Hz has been improved by approximately 32 dB and even the phase noise from approximately 1-10 MHz off the carrier was improved. Because of the reduction in amplitude and the resistive feedback, the phase noise at 20 MHz and further away is set at 160 dBc per



Figure 31. Implementation of the oscillator of Figure 30 using an IC.



Figure 33. Output waveform of the oscillator of Figure 31.



Figure 34. Phase noise of the oscillator of Figure 16 before and after optimization.

Hz while the original circuit predicted slightly better performance. This technique is applicable for arbitrary oscillator topologies and active devices for which we have a good understanding of the relationship between the flicker noise and the bias point.

Other Useful Oscillator Circuits

Figure 35 shows a bipolar transistor oscillator in the 2.75 to 3.75 MHz frequency range. By adjusting L1 and C1, the frequency range can be shifted. A good application is 5-5.5 MHz. Inside its oven controlled environment, this bipolar oscillator has a frequency shift of less than 50 Hz per day. Even without the electric heating, it will not drive more than 200 Hz per day after 15 minutes warm up.

For those attempting to build low phase noise VCOs for the 220 MHz amateur band, as shown in Figure 36, here is a unique low phase noise oscillator which should be made part of the synthesizer. Its phase noise at 200 MHz is measured at 150 dB per Hz, 25 kHz off the carrier.

Finally, for those having "fun" with noise in their UHF repeater oscillators, Figure 37 shows a cavity-resonator based low phase noise VCO



Figure 37. Cavity stabilized VCO for application in UHF repeaters.

which may eliminate headaches caused by some noisy designs.

Summary

This paper has analyzed both FET and bipolar oscillators, including circuit combinations which are adapted for high level integration. The general trend seems to be that FETs require more current, but the f, of the available N junction FETs is not sufficient to build oscillators above 400 MHz, and the flicker noise contribution is very small. On the other hand, bipolar transistors are ideally suited for oscillator circuits for high integration. Their bias point has to be chosen very carefully to avoid too much flicker noise contribution. When these types of oscillators are designed as one terminal oscillator circuit, they do not provide an attractive choice of topologies and a good compromise between performance and complexity has to be sought. Most hand-held two-way radios or radio telephones with digital signal processing do not require very high performance oscillators. This paper has sought to provide some guidelines for obtaining high performance circuits. We have also addressed AGC action by self-limiting

the use of DC feedback and diode clamping. There has been some discussion on these three topics within the engineering community and we have used our tools to provide insight on these sensitive circuits. *RF*

References

 Kenneth K. Clark and Donald T. Hess, Communication Circuits: Analysis and Design, Addison Wesley Publishing Company, Reading, MA 1971.

2. The ARRL Handbook, pg. 4-5, Solid State Basics.

3. Ulrich L. Rohde, Digital PLL Frequency Synthesizers - Theory and Design, Prentice-Hall, Inc. Englewood Cliffs, January 1983 pg. 159. Available through Compact Software, Inc. Paterson, NJ.

4. Ulrich L. Rohde, Chao-Ren Chang, and Jason Gerber, "Design and Optimization of Low-Noise Oscillators using Nonlinear CAD Tools", presented at the Frequency Control Symposium, Boston, MA, June 1-2, 1994 proceedings thereof

5. Motorola ECL High Speed Integrated Circuits Data Sheet for MC 1648, circuit schematic, pg. 4-2

6. Wes Hayward and Doug DeMaw, Solid State Design for the Radio Amateur, ARRL, Newington, CT, pg. 126, Figure 26.

7. Ulrich L. Rohde, "All About Phase Noise in Oscillators", *QEX*, Dec. 1993, Jan. 1994, Feb. 1994.

8. Ulrich L. Rohde, "Key Components of Modem Receiver Design, Parts I, II and III," QST, May 1994, June 1994, July 1994, pp. 29-32, pp. 27-30 and pp. 43, 45. respectively.



Figure 35. 2.75-3.75 MHz high stability oscillator with proportional controlled oven.



Figure 36. Low phase noise 200 MHz-range VCO from the Rohde & Schwarz XPC synthesizer.

RF product forum

CAD/CAE Software Accelerates, Simplifies RF Design

This month the product forum highlights the market changes affecting CAD/CAE software. Several manufacturers offer opinions regarding today's marketplace and trends in the industry.

Analog and RF Models

Although the rate has slowed in the last year, the market is still growing. This growth is fed by the lower cost of fast PCs and affordable Spice simulation software for those PCs. Key applications are RF and high-speed, where bench work is often limited by probe loading or probe bandwidth. The outlook for the next six months to two years is somewhere between stable and 10 percent growth.

On the business end, shorter development cycles can only happen when simulation and prototyping are combined. On the technology end, the move toward semi-custom array ASICs and MMICs for many high-speed applications with their high NREs force simulation to be a large part of the picture. We are participating by providing Spice compatible models of RF transistors, RF PIN diodes, laser diodes, and other active high-speed devices.

Compact Software

Efficiency and size are key requirements for RF power amplifiers used in cellular radios, two-way radio systems, and DoD applications. New applications are creating new design problems. For example, digital transmission of data requires that the amplifier's response to pulsed signals be well understood. Compact Software's CAE/CAD tools let designers create and optimize new amplifiers using simulation instead of building multiple prototypes.

In order to create amplifier designs which can be built and work the first time, accurate simulation of high power RF/microwave transistors are very important. Compact Software, Inc. has been cooperating with different device manufacturers and GaAs foundries in order to create and validate simulation models for high power devices. Participating vendors include

Philips and Siemens in Europe, along with Motorola and several GaAs foundries in the United States. Compact has modeled all of Siemen's new bipolar transistors and GaAs FETs for cellular telephone base stations. In a separate effort sponsored by Motorola, Compact Software has developed a mathematically continuous model for power MOS transistors. This has resulted in a new nonlinear model for both time domain and frequency domain simulation that is much faster than existing models and provides better convergence. Compact's expertise in this area has also resulted in SBIR contracts from ARPA, specifically in Class E operation for power amplifiers. This work allows Compact to provide solutions for commercial customers.

Eagleware Corporation

Desktop access to powerful computers has revolutionized the way engineers design. Regardless of the end application or market, software requirements are universal: accuracy, flexibility, speed, ease-of-use and highquality support.



Eagleware's System 32 screens.

Actual use is the ultimate test of software quality and value. At Eagleware, we design, build, and test circuits daily in a fully equipped lab. We have as much capital invested in instrumentation as in computers! This enhances both the practical capabilities of Eagleware tools and the quality of our support.

Most CAE developers focus on simulation and manufacturing tools. Eagle-

ware's System 32 also integrates synthesis into the design process. Eagleware System 32 synthesis programs help design L-C filters, oscillators, microwave filters, matching networks, active filters, and amplifiers. With System 32 programs you choose the operating system: DOS, Windows or Windows NT. Windows programs are 32 bit for fast operation and full access to system memory. All System 32 programs share the same user files for mixed department use and painless upgrades.

Nedrud Data Systems

The CAD/CAE software market will continue to grow as programs become more powerful, hardware becomes more affordable, and as engineers become more aware of the benefits of CAD tools: increased productivity through faster virtual prototyping. The time saved is often spent performing more calculations, which means fewer prototypes and smaller, lighter designs. The truth is that engineers can no longer afford to design without software.

Now that more companies offer competent software, engineers are beginning to evaluate programs less on features and more on how well they perform their functions. The length of a design task depends much less on the computer's clock frequency that it does on the program's user interface; e.g. how quickly the user can tell the computer what to display. This gives an edge to programs like DragonWave which allow engineers to create and analyze circuits in a straightforward and intuitive way.

MicroSim Corporation

As frequencies continue to increase for both analog and digital applications, the modeling of transmission line effects becomes more and more important. Therefore, CAE tools which properly simulate transmission line effects and tools which extract the necessary data from physical layout information are increasing in popularity.

MicroSim[™] PSpice for Windows sup-

ports single and multiple transmission line effects for simulating reflections, loss, dispersion, and crosstalk in both the time and frequency domains. MicroSim's new signal integrity product - MicroSim Polaris for Windows extracts transmission line data from a physical board layout. Whether the parameter extraction is accomplished using MicroSim Polaris, or the parameters are calculated manually, the ability to include the transmission line effects in a simulation allows the proper examination of issues such as amplifier stability, data transmission, and ground bounce. The types of transmission lines which can be modeled include coaxial cables, twisted pairs, PCB traces, striplines, microstrips, and the IBIS models.

Viewlogic Systems, Inc.

Most RF equipment manufacturers now use electronic design automation software to design the printed circuit boards, modules, and ASIC/custom integrated circuits used in their products. Increasingly that includes sophisticated digital technology as well as RF circuits. The digital part of such products may be extremely complex, as seen in frequency synthesizers. With both design complexity and digital content growing, many RF manufacturers find themselves using design methods similar to those used for such products as FAX/modems, multimedia video/ sound, and disk drive interfaces. All must optimize critical analog circuitry while accounting for the effects of digital circuits with thousands of logic gates. Consequently, co-simulation of digital and analog circuits is becoming mandatory to verify total system performance before committing to manufacture. To simplify digital design, the use of VHDL and Verilog Hardware Design Languages is becoming popular. A typical design may therefore use several different simulators, both digital and analog, to promote optimum system design. These "high-level design" approaches also support mixed analog/digital design reuse. Viewlogic Systems provides a suite of EDA tools and graphical design environments that make it possible for customers to build a "best in class" design ensemble. The underlying design environment, available on PCs and Unix workstations, allows the use of both Viewlogic and third-party tools through standard industry interfaces. This enables Viewlogic to provide major RF/wireless manufacturers with advanced EDA software that is targeted to their needs. It will soon include Hewlett-Packard's HP-EEs line of RF/wireless simulators.

Design Automation, Inc.

The explosive growth in portable wireless communications is focusing attention on transmitter power efficiency (increased efficiency, reduced battery drain, reducing battery size and weight and/or lengthening time between battery rechargings). Switching mode RF power amplifiers (Classes E and F) are finding favor because of their increased efficiency and reduced battery drain. Their drawback has been difficulty in optimizing, because of complicated nonlinear and implicit mathematical relationships between the circuit parameters and the resulting efficiency and output power. That drawback has been removed with the availability of fastcomputing software developed specifically for designing such amplifiers, able to automatically optimize the design in about a minute; or to simulate the circuit and compute the voltage and current waveforms and the RF output power, DC input power, and power dissipations in each circuit component in 0.14 second (times are for a 486/33 computer). Outlook: More use of Class E and F amplifiers. RF

ALK Engineering	159	Intusoft	172
Analog and RF Models	160	MacNeal-Schwendler Corp.	173
Ansoft	161	Made-It Associates, Inc.	174
Arden Technologies, Inc.	162	Meta-Software	175
Besser Associates	163	MicroSim Corp.	176
CAD Design Services, Inc.	164	Nedrud Data Systems	177
California Scientific		REMCOM, Inc.	178
Software	165	Somersoft	179
Compact Software, Inc.	166	Sonnet Software	180
Design Automation, Inc.	167	Spefco Software	181
DGS Associates	168	Tatum Labs, Inc.	182
Eagleware Corp.	169	Tesoft	183
HP-EEsof	170	Viewlogic Systems, Inc.	184
Ingsoft, Ltd.	171	Waypoint Software	185

Due to space limitations, our January Product Forum did not include a complete list of companies which manufacuter TCXOs. Below is an expanded listing of these companies. For information, circle the Info/Card numbers below:

Alpha Industries	186
Anghel Laboratories,	107
a Div of Radiation Sys, Inc.	187
Bliley Electric Co	189
Cal Crystal Lab. Inc./Comclok	190
Cambio International	191
Castle Microwave	192
Champion Technologies, Inc.	193
C-MAC Quartz Crystals, Ltd.	194
Connor-Winfield Corp.	195
Crystek Crystal Corp.	196
CIS Corp.	197
Dale Electronics, Inc.	198
FDC Frequency Products	199
Electronic Research Co	201
EMCO High Voltage	202
EMF Systems	203
Fox Electronics	204
Frequency and Time Systems	205
Frequency Electronics, Inc.	206
Frequency Sources, Inc.	207
FTS/Austron	208
Greenray Industries	209
Hybrids International, Ltd.	210
Hytek Microsystems, Inc.	211
International Crystal	~~~~
Manufacturing Co.	212
Isotemp Research, Inc.	213
KVC North America Inc	214
Lostropia Passarah Laha	210
Lectrome Research Labs	217
Magnum Microwave, Inc.	218
Micro Networks Co.	219
Micronetics, Inc.	220
Microwave Device	122
Technology Corp.	221
Microwave Oscillator Corp.	222
MTI-Milliren Technologies, Inc.	223
Murata Electronics	
North America	224
NEL Frequency Controls, Inc.	225
Oak Frequency Control Group	226
Den Datagemm Ing	227
Pan Datacomm, Inc. Bioro Curretal Co. Inc.	220
Piezo Technology Inc.	230
Raltron Electronics	231
RDL. Inc.	232
Reeves-Hoffman	233
Sentry Manufacturing Co.	234
Shokai Far East Ltd.	235
Sokol Crystal Products	236
Standard Crystal Corp.	237
Tauber-Dreyer Corp.	238
Techtrol Cyclonetics, Inc.	239
Tele Quarz Group	240
Teledyne Microelectronics	241
The North America	242
Townson Components & Tubes	243
TRAK Microwaya Com	244
Valney-Fisher Corn	246
Vectron Laboratories Inc.	247
Watkins-Johnson Co.	248
Wenzel Associates, Inc.	249
Westec Communications, Inc.	250

RF LITERATURE/PRODUCT SHOWCASE



INFO/CARD 70

CIRCUIT BOARD COMPONENT SHIELDING

Removable cover allows component accessibility

Leader Tech offers a standard board shielding components: available heights range from .13" to 2.00"; available sizes are from .50" \times .50" to 6.00" \times 24.00", on 1/4" increments.



The STYLE CBS removable cover design provides superior shock and vibration resistance while allowing component accessibility. All STYLE CBS series are available in thru-hole or surface-mount configurations, and, as always, there are no tooling or artwork charges. Contact Leader Tech at 14100 McCormick Dr., Tampa, FL 33626; (813) 855-6921, Fax (813) 855-3291.

INFO/CARD 73

RFD Literature/Product Showcase

RF DESIGN is pleased to announce the availability of the Literature/Product Showcase section. Your ad in this new monthly advertising section will allow you to:

- Introduce New Literature and Products
- Boost Awareness of Existing Lines
- Reach Prime Prospects more than 40,000 readers who are design and R & D engineers, engineering managers and corporate staff in the military, aerospace, communications and electronics industries
- Achieve Four Color Impact in this highly visible cost-effective section
- **Get our Reader Reply Service Free**







No limits to complex geometrics
 Auto Schematic Capture - Finally! One that really
 works in AutoCAD®

works in AutoCAD® GerbArt - AutoCAD® - Gerber Translator

• Recommended by Gerber Systems **DEMO PACKAGES AVAILABLE**:

CAD Design Services, Inc. 2806-C Soquel Avenue Santa Cruz, CA 95062 phone: (408) 462-6494 fax: (408) 475-0738

AutoCAD® is a Registered Trade Mark of Autodesk, INC. SEE US @ PC Design Conf. BTH. #722



GOULD POWERDEX. Thin Lithium Batteries As thin as 0.7 mm



High energy densityCustomized capacity

· Thin rectangular format

Solder or pressure contacts
Available in 3 and 6 volt

POWERDEX family of products:

- Standard: A, B, C sizes
- Ultrathin: less than 1 mm
- Customized: capacity and/or size
- · Rechargeable: call for information

Gould Electronics Inc., Electronic Power Sources 35129 Curtis Blvd. Eastlake, Ohio 44095-4001 Phone: (216) 052-5050 Fay: (216) 052-5152

Phone: (216) 953-5059 Fax: (216) 953-5152 Toll Free: 1-800-722-7890 (U.S.& Canada)

(U.S. & Canada)

INFO/CARD 72

COMMERCIAL-GRADE EMI SHIELDING

This catalog details a variety of economical EMI gaskets, foil tapes, foil/film laminates, and protection systems for cables. It explains basic EMI concepts, typical shielding applications and EMI gasket attachment systems. Chomerics commercial-



grade EMI shielding products help electronic equipment manufacturers meet emission and immunity requirements of international standards, and avoid EMI-induced systems problems.





RF LITERATURE/PRODUCT SHOWCASE

RFD Literature/Product Showcase

RF DESIGN is pleased to announce the availability of the Literature/Product Showcase section. Your ad in this new monthly advertising section will allow you to:

- Introduce New Literature and Products
- Boost Awareness of Existing Lines
- Reach Prime Prospects more than 40,000 readers who are design and R & D engineers, engineering managers and corporate staff in the military, aerospace, communications and electronics industries
- Achieve Four Color Impact in this highly visible cost-effective section
- **Get our Reader Reply Service Free**

 Checks Lease

 Communications

 Communic



INFO/CARD 80

BUYERS' GUIDE

RFD LITERATURE/PRODUCT SHOWCASE

This **NEWLY REVISED** special section in RF TEST & DESIGN puts your sales literature or catalog into the hands of our readers — more than 40,000 design and R & D engineers, engineering managers and corporate staff of military, aerospace, communications and electronics industries.

For rates and closing dates, call Jon Tuck at (404) 618-0217 or fax at (404) 618-0342.



INTRODUCES THE Yellow Page Directory Section

CALL

1-800-443-4969 FOR DETAILS ON AN EXCITING INTRODUCTORY OFFER!



Classified Department 6151 Powers Ferry Road NW Atlanta, GA 30339-2941 (404) 955-2500 Fax: (404) 618-0342

RF marketplace

Classified display ads are available at \$115 per column inch. Frequency rates available for multiple insertions. Please call for further information, 1-800-443-4969, ask for Jon Tuck. Or fax your ad copy for a rate quote to (404) 618-0342.

RECRUITMENT

NCS Jobline has a Job for You! 2897 Mapleton Ave Suite 1A Boulder, CO 80301 303-440-5110 ncs@jobline.com See Career Magazine on the Internet at http://www.careermag.com/careermag/ INFO/CARD 85

Nationwide opportunities in the CELLULAR/WIRELESS industry. Debra Sola-Furnari **TELE-TECH SEARCH** 4773 Split Rail Place W. Melbourne, FL 32904 (407) 951-4200 FAX (407) 951-0808

INFO/CARD 86

OFTWARE -123.5 -196.80 - 2490. 1 -342.0 Full-Featured Conversion System Design Waypoint . **TxRx** Designer Software. Only \$149.95 1950 Bavaria Dr. #317 Colorado Springs, CO 80918 (719) 598-9592 Please call or write for information INFO/CARD 88 RF DESIGN is THE PLACE to **REACH PRIME PROSPECTS** more than 40,000 readers who are design and R&D engineers, engineering managers and corporate staff in the military.

porate staff in the military, aerospace, communications and electronics industries. For rates and closing dates, call Jon Tuck at (404) 618-0217 or fax (404) 618-0342.

CAREER OPPORTUNITIES

MIDWEST



Representing Opportunities In The Country's Leading Communication Corporations.

— Relocation Available — All Fees Paid By Our Clients.

John Nagel • (800) 883-8380

Advanced Communication Search 1189 Richmond Road • Mahwah, NJ 07430 Tel (201) 818-1479 • Fax (201) 818-1510

INFO/CARD 89



IOWA MIDWEST

RF COMMUNICATIONS EQUIPMENT DESIGN ENGINEERS

OPENINGS



SHARPENING THE EDGE... At AT&T Custom Manufacturing Services, (CMS),

our people and their capabilities are our competitive edge and the basis of our success in satisfying customers.

We presently have an opportunity at our facility in Little Rock, Arkansas, for an Engineer with a strong RF background. This technical position is responsible for test development and implementation to support the manufacture of cellular and PCS products. Experience in developing manufacturing test and diagnostic procedures and a thorough knowledge of the cellular AMPS, TDMA, and CDMA technology are required. A BSEE is required and an MSEE is preferred.

AT&T offers excellent compensation and benefits and is an Equal Opportunity Employer.

Interested candidates please send resumes and salary expectations to:



000

Engineering

RF Power Products. Inc., a leading supplier of RF delivery systems from 50 kHz to 100 MHz, with power levels up to 25,000 watts has the following openings. These positions are staff expansions to meet the increasing demands of RFPP's continued growth.

RF ENGINEERS - Design engineers to develop RF power systems consisting of power generators and/or matching networks to meet customer specifications. Working knowledge of RF required. Minimum BSEE, MSEE preferred, and/or 10 years RF related industrial experience. Candidates must be experienced in CAD and have strong communication skills.

RF CUSTOMER SERVICE ENGINEER - To interface directly with customers in various matters relating to our products and applications. BSEE plus several years experience in RF power systems required. Initially requires relocation to Korea/Japan.

RF APPLICATIONS ENGINEER - To work in San Jose office interacting with sales, engineering, and customers in developing RF technology for current and future projects. BS plus 5 yrs, or 10-12 yrs directly related industry experience required. Some travel necessary.

RF Power Products, Inc. offers excellent career opportunities, competitive salaries, comprehensive benefits, and relocation package.

INFO/CARD 92

Respond in confidence to PO Box 490, Mariton, NJ 08053, fax 609-751-2143, EOE.



...YOOUR CAREER Project Leader/Design Engineer: Microwave hybrid and monolithic IC design expensence is required. This person must be experienced in computer aided design, analysis, and measurement techiques. Responsibilities will include analysis of existing MMIC designs for RF portions of digital cellular radios and modifications to designs. Should have extensive experience in active and passive microwave circuits. Concise clear communication skills are required for generation of reports, proposals, and presentations. tion: Will design RF circuits for commercial basestation product line. Design

Filter Design Engineer: B.S. Minimum 3 years experience in the design development of Broad Band, comb-line strip line, interdigital, low pass and pass filters, multiplexers, diode switches, (phase shifters), attenuators microwave sub-systems desirable.

Cellular Basestation: Will design RF circuits for commercial basestation product line. Design responsibilities include specification/evaluation of components & subassemblies, circuit synthesis & analysis, schematic capture, supervising PCB layord, & test, evaluation & integration of design. BSEE, MSEE desirable plus 5-10 yrs. exp. in design and development of commercial radio products.

SemiconductorProcess Enginner: Minimum of B.S. in Physics, Chemistry, Electrical Engineering, or Material Science. Working knowledge of all phases of semicondulor processing including thin film deposition, photolithography and wel/dry etching.

Antenna Engineer: Lead the conception, design and development of a wide variety of antennas and antenna systems including both reflector and array systems using microstrip, stripline, and waveguide technologies. BS/MSEE with 5 years experience.

Propagation Engineer: Five-ten years of experience in propagation measurement and modeling for cellular and personal communication systems operating from 800 to 2000 MHz. Related experience in planning cellular systems and modeling analog and digital communication systems is desirable.

Staff Design Engineer (RF): Responsible for the design of RF Integrated circuits for submicron fabrication facility. BSEE/MSEE and 10 years experience in the RF area, designing transnitters and receivers in the 900/Ms – 3 Ghz frequency range. BCMOS Integrated circuit design very desirable. Must be familiar with SPICE modeling of Integrated RF circuits and systems. Quadrature modulation design experience is valuable.

RF Design Engineer: Responsible for design of analog and Rf systems and circuits for consumer and commercial digital wireless products. Experience with low-cost design techniques for frequency synthesizers, power amplifiers, updown conventiers and baseband circuits for digital communications systems. Familiarity with time division duplex or CDMA a plus.



We specialize in the placement of communications both nationally and internationally FOR THESE AND OTHER OPENINGS CALL COLLECT: TEL: 508-685-2272 FAX: 508-794-5627

INFO/CARD 93

WIRELESS ENGINEERING OPPORTUNITIES with MOBILE SYSTEMS INTERNATIONAL

Mobile Systems International (MSI) currently has engineering positions open for RF and Network engineers. MSI is a world class company with a reputation for providing high quality advanced consulting support to telecommunications, PCS/PCN, ESMR, Cellular, and Paging operators, as well as other wireless system operators worldwide. MSI offers a wide range of services covering CDMA, GSM, IS-54 TDMA, AMPS, MIRS, Paging, and other wireless technologies. Typical services provided to our customers include:

- Radio, Signaling, and Network System Planning and Design
- Technology and Vendor Selection
- New Technology Integration
- Strategic and Management Consultancy

- System Dimensioning
- System Design Audits
- System Performance Monitoring

MSI offers the opportunity not only to be involved with all of the newest wireless technologies but to also work with a group of highly qualified and experienced engineers. At MSI our engineering team takes pride in holding themselves to the highest engineering standards. Applicants must possess a BSEE or MSEE degree with a minimum of 1 year experience in the wireless engineering industry, and must be innovative as well as highly detail and results oriented. Excellent presentation and technical writing skills are also required. Other useful skills include knowledge of DOS and UNIX operating systems, microwave engineering, networking of wireless communications systems including GSM, IS-41 and SS7, development of RF propagation models, traffic engineering, and knowledge of antenna and receiver design principles. Travel may be required.

We at MSI are committed to further expanding our RF and Network engineering consultancy by the addition of experienced, well qualified wireless engineers. Engineers are needed in our Chicago, Dallas, Atlanta and Washington DC offices as well as other customer locations throughout North and South America and Asia. If you are a highly motivated engineer who meets the above mentioned qualifications MSI could be the career move you are seeking. Please send your resume in strictest confidence to the address below. MSI is an equal opportunity employer.

MOBILE SYSTEMS INTERNATIONAL Personnel Department One Lincoln Centre, Ste 200 • Oakbrook Terrace, IL 60181 Fax: (708)261-3028

OPPORTUNITY

U.S. Company is looking for a Leader with national sales experience to direct U.S. sales expansion. Must have experience in R.F. components (including coils and transformers). Importing experience with Japanese customers a <u>must</u>. Engineering degree desirable. Position open in major southern city.

> Send resume to: Box SE12 6151 Powers Ferry Road, NW Atlanta, GA 30339

> > INFO/CARD 95



INTERNATIONAL & DOMESTIC

Judy Wachs, President Phone 212.691.2491 Facsimile 212.691.1670 RF ENGINEERING

INFO/CARD 96

RF DESIGN is **THE PLACE** to **REACH PRIME PROSPECTS** – more than 40,000 readers who are design and R&D engineers, engineering managers and corporate staff in the military, aerospace, communications and electronics industries. For rates and closing dates, call Jon Tuck at (404) 618-0217 or fax (404) 618-0342.

R.F. Engineers

National & International Wireless, Microwave, Etc.

Over 20 years service in the Communications Industry. All Levels, Relocation Available Fees paid by employers Call *Elaine Cohen* or *Steve Young* 1-800-875-2230 Fax: 714-250-8535

Fortune Communications Group 18552 MacArthur Blvd. Suite 345 Irvine, California 92715 WE'RE PUSHING BEYOND PRACTICAL PATHS OF INNOVATION.

AtMotorola Cellular, we believe in pushing beyond the practical paths of innovation to freely experiment with new and exciting technologies. If you are seeking an environment built on innovation, explore opportunities at one of our suburban Chicago locations.

RF ENGINEERS

Positions available for individuals with a minimum of 2 years PCS, GSM, CDMA/TDMA and all other areas of RF design, development and test experience. Candidate must also have solid experience in domestic and international protocols.

PRINTED CIRCUIT DESIGNERS

We have positions open at various levels for those who excel at directing and participating in very complex printed circuit board layouts for both new and redesigned products which conform to quality and manufacturability specifications. You will utilize C.A.D. workstations with application specific software as well as support terminals to access electronic data bases and various input/output peripheral equipment. The successful candidates will have a minimum of 5 years experience in printed circuit design with 3+ years C.A.D. experience

using mentor boardstation software. Indepth knowledge with P.C.B. fabrication and assembly techniques essential.

ELECTRICAL ENGINEERS

You will design and develop circuits for digital cellular base stations. This includes developing RF and analog circuitry while utilizing high performance synthesizers, high dynamic range receivers and low/high power

l low/high power transmitters for our systems. A BSEE along with 4+ years related design experience is required. Post design experience in RF and analog circuitry, as well as a background in

control systems essential. A MSEE preferred.

We offer an excellent salary, complete benefits, 401 (K), profit sharing and more. Forward your resume indicating position of interest to: Motorola Cellular, Department IWRF 1501 W. Shure Drive, Arlington Heights, IL 60004. Fax: 708-632-3873. Motorola is an equal opportunity/affirmative action employer. We

welcome and encourage diversity in our workforce.



RF Design • 1-800-443-4969

INFO/CARD 99

INFO/CARD 98

86



ITS Corporation is a leading manufacturer of television transmitter systems located in a suburb of Pittsburgh. Our total workforce has grown from 110 employees in 1992, to 167 employees in 1993 with 268 current employees. Staffing protections for 1995 indicate continued growth. We are seeking candidates for the following position:

DESIGN ENGINEER

An experienced design engineer with RF and video circuit experience. BSEE required. Substantial growth opportunity for the right candidate.

Interested candidates should forward their resume with salary history to: ITS CORPORATION Human Resources Department 375 Valley Brook Road McMurray, PA 15317-3345 FAX:(412)941-4603

ITS is an equal opportunity employer and

INFO/CARD 100

ANTEC ENGINEERING & ESP

The leading systems design and integrator for the cable television and telecommunications industry is looking or the following seasoned professionals for its Atlanta, GA location. ANTEC emphasizes multimedia technology and access to The Information Superhighway.

Two divisions of Antec – Antec Engineering and Electronic System Products – are looking to fill the following positions:

Sr. Analog or RF Engineers

Solid knowledge of Analog/RF product design concepts such as Modulation, Amplification, Filtering, Mixing and Noise. A familiarity with FSK, BPSK, QPSK, QAM, & VSB demodulators and modulators, is desirable. Requires excellent analytical skills with the ability to design and simulate active and passive circuitry.

Please respond to:

ANTEC ENGINEERING & ESP DEPT. HR-ANTEC-RF 5720 PEACHTREE PARKWAY NORCROSS, GA 30092 OR FAX TO (404)441-2477

EQUAL OPPORTUNITY EMPLOYER

Recruiting RF Engineers? The best buy for your advertising dol-

your advertising dollar is RF Desien, the ONLY technical publication written exclusively for engineers working in the important wireless market. For information on how to reach over 40,000 RF engineers and engineering managers, call Jon Tuck at (404) 618-0217 or fax (404) 618-0312.

SUNBELT OPPORTUNITIES

Several of our growing commercial major electronic companies located in the southeast have asked us to identify candidates in the mid-level experience range.

- 1) BSEE RF Receiver design, Sat Comm, Commercial wireless product Design/Development
- 2) BSEE RF evaluation/QA engineer Spearhead products through design QA.
- 3) BSEE RF Circuit Design Engineer Frequency Synthesizers
- 4) BSEE Section Manager Analog IC Design
- MSEE MMIC for Military Systems L Band thru KU Band (2-18 GHtz) Knowledge of non-linear modeling.

₩-o-r-t-u-n-e

PERSONNEL CONSULTANTS OF RALEIGH, INC. P.O. Box 983888 • Raleigh, NC 27624-8388 Phone: 919-848-9929 • Fax: 919-848-1062 Stan Deckelbaum

INFO/CARD 102



GLENAYRE ELECTRONICS, a prominent world-wide manufacturer of equipment for wireless personal communications services such as radio paging switches, transmitters, controllers and voice processing systems, has the following immediate opportunities in our RF division:

Lead RF Design Engineer – Responsible for the design of high performance narrow band PCS receivers in the 900 Mhz band. Familiarity with paging standards and protocols such as POCSAG, FLEX, REFLEX is desired. Requires BSEE or equivalent and a min.of 5 years experience in the design of receivers or related products, including proficiency in LNA, mixers, filter, oscillator and demodulator design. DSP knowledge a plus, project mgt, skills are preferred.

Sr. Engineers – Responsible for exciter design and project engineering. The successful candidates will have expertise in exciter design such as VCO's, mixers, filters, DDS, DSP, rf amps, synthesizers, etc. Requires BSEE and three years design experience. MSEE preferred.

GLENAYRE offers excellent benefits and a competitive salary commensurate with experience. Qualified applicants send resume and salary history to:



Attn: Human Resources One Quintron Way Quincy, IL 62301

An Equal Opportunity Employer by Choice

INFO/CARD 101



- RF System Design Engineers
- MSC BSC BTS
- Technical/Test Support
- Operations Experts
- Staff Supervisors Managers
- Switch Technicians
- Contract/Full-Time Employees

26941 Cabot Road Suite 115 Laguna Hills CA 92653 Tel: 714-582-7800 • Fax: 714-582-7900 eMail: ksg earthlink.net INFO/CARD 104

RF Design Marketplace 1-800-443-4969

DIRECTOR OF ENGINEERING

We are a leading manufacturer of frequency control devices with a worldwide reputation and marketing for quality and design which has an immediate requirement for a highly motivated engineer.

Qualified candidates should have 10+ years related experience, preferably in both the crystal and oscillator areas along with an EE degree. Prior managerial experience a plus. Competitive salary and excellent benefit package commensurate with this high profile position; reporting to the President. Excellent family orientated northeastern location with a climate offering something for every kind of outdoor enthusiast.

Submit detailed resume of educational background, work and salary history, and references to:

Bliley Electric Company Attn. Richard D. Bliley, President P.O. Box 3428 Erie, PA 16508 EOE M/F

INFO/CARD 105



Just Because Somebody's In Business Doesn't Put Them On The A-List

No part-timers, no pretenders, no padding. Mailing lists from Argus deliver targeted, audited decision makers to maximize your marketing investment. Direct from our blue chip lineup of niche publications, covering everything from golf courses to landscape contractors. Don't just get a list. Get the A-List from Argus. For our complete catalog call Renae or Diane at 404-618-0154 or fax 404-618-0347.





Without Tears

Learn DSP and put your knowledge to work IMMEDIATELY!

To receive an informative brochure on this popular seminar, call Z Domain Technologies, Inc. at **1-800-967-5034** or 404-587-4812. Hours: 9 - 5 EST. Also, a 2-day ADVANCED class in DSP is available on a limited basis -- call for more details.

By taking this 3-Day Course, you will really learn DSP. <u>Guaranteed!</u>

Coming to a City Near You: Chicago IL - San Jose CA - Washington DC - Dallas TX

PRODUCTS & SERVICES

A-COMM ELECTRONICS Refurbished Test Equipment DC-26ghz HP GR Wavetek Tektronix Send for Catalog listing

7198 S Quince Street Englewood, Colorado 80112 303 290 8012 Fax 303 290 8133

INFO/CARD 107

The Problem Solver

Fully Integrated Product Design Facility Microwave, RF, Analog, Digital, and Mechanical Design Fast Response - Exceptional Results

Geotek Design Services 18512 Carrot St. Suite 108, Spring, TX 77379 Ph(713)376-4606 - FAX(713)251-3860

INFO/CARD 108

FCC AUCTION INDUSTRY IMPACT REPORT

Will the FCC Auctions change the communications business? Absolutely! This independent, exhaustive study is must reading if you're a frequency user. (\$89.95 + \$2.50 pstg)

Cynetics Corp. 3824 Jet Drive, Rapid City SD 57709 605-394-6430, FAX-6456

INFO/CARD 109

RF RESOURCE

RF/Wireless Circuits or Systems; Voice or Data RF, IF, mod/demod; detectors, receiver systems Mobile comms., PART 15, narrow or spread-spectrum ADVANCED TROUBLESHOOTING A SPECIALTY Ask about Bit-Error-Rate reduction Call 1-800-890-5427

INFO/CARD 110



Realize the Potential! Contact: Jon Tuck Tel: (800) 443-4969 Fax (404) 618-0342

R.F. SHIELDED ROOM - FOR SALE

FEATURES:

VISA

• Room Size: 16' × 16' × 10' high. (Door size: 4' × 7') (Manufactured by: "Energy Sheilding Inc.)

- Price: CDN \$10,000.00 neg.
- Disassembly and delivery not incl
- For further details, please call: Nick @ Ext. 228

SCIEX - Division of MDS Health Group Ltd. 55 Glen Cameron Road, Thornhill, Ontario, Canada L37 1P2 Tel: (905)881-4647 . Fax: (905)881-9832

INFO/CARD 111



Introduces the **Yellow Page Directory Section**

CALL 1-800-443-4969 FOR DETAILS ON AN EXCITING **INTRODUCTORY OFFER!**

= PLL – DataSender = PLL Universal Programmer "For People Who Build PLLs

- Supports a broad range of 2-line and 3-line serial input. PLL ICs supplied by Fujitsu, Mitsubishi, Motorola, National, Philips, Plessey, Sanyo, Siemens, Toshiba, and others. No other product makes it so easy to program a wide variety of PLLs.
- Each order includes: fully assembled control board in book-sized (8.1" x 10.1" x 1.4") carrying case; 5 customed-specified Programmed Controllers chosen from MYcom's PLL-DataSender's Application List; 3.5" disk containing PLL-DataSender instructions and PC-compatible software for loop filter design; and one 9V battery.
- Customized manufacturing versions of Programmed Controllers are available.



MYcom Instruments 142 N. Milpitas Blvd., Suite 277, Milpitas, CA 95035 TEL 408-262-8552 FAX 408-262-4763

INFO/CARD 114

BE DESIGN IS THE PLACE tO REACH PRIME PROSPECTS – more than 40.000 readers who are design and R&D engineers, engineering managers and corporate staff in the military, aerospace, communications and electronics industries.

For rates and closing dates, call Jon Tuck at (404) 618-0217 or fax (404) 618-0342.

Finally, a synthesized signal generator that's designed to help you generate more than just signals. The Ramsey RSG-10, is the signal generator you can afford, the signal generator that's designed to do what a signal generator is meant to do-provide a very stable, accurate, easy to control signal from 100 Khz to 1.0 Ghz. For the price, you wouldn't expect any more. But, there is more to the RSG-10. An intelligent microprocessor controlled/programmable memory, for example, can store up to 20 of your most commonly used test set-ups. And unlike other units, just one touch of the memory exchange button is all it takes to quickly shift from one test set-up to another. You get more work done, easier and faster. A RS2495, the Ramsey RSG-10 is your profit generator. RAMSEY ELECTRONICS CANNING PARKWAY, VICTOR, NY 14584 Fax: (716) 924-4555 TELEX: 466735 RAMSEY CI

1GHz RF

SIGNAL GENERATOR

AM/FM, 100 KHz through 1 GHz

ORDER DIRECT-CALL 1-800-446-2295

INFO/CARD 112



Phoenix, AZ 85032-2919 Phone & Fax (602) 971-3301



The Buyers' Guide is a convenient guide to suppliers of products and services available for design and development engineers. Buyers' Guide listings are sold on an annual basis at the rates shown.

	Per Issue
Regular Listing	\$22.00
Additional Line	\$19.00
Bold Listing	\$25.00
Additional Line	\$21.00
1" Ad	\$200.00
Drop Out In White	\$25.00

All orders must be prepaid. You can forward your check or charge your ad to:

Total/Year

\$264.00

\$228.00

\$300.00

\$252.00

\$300.00

\$2.400.00



For information on closing dates and details on a special Introductory Offer, call 1-800-443-4969. Ask for your vellow page representative.

DISCRETE COMPONENTS

CAPACITORS Chip

Variable



Tel: 516-334-8700 • Fax: 516-334-8771

Vacuum

COMET North America, 11 Belden Ave., Norwalk, CT 06850(203) 852-1231 Richardson Electronics, Ltd., 40W267 Keslinger Rd., LaFox, IL 60147 ... Surcom Associates, Inc., 2215 Faraday Ave., Suite A, Carlsbad, CA 92008........(619) 438-4420

CRYSTALS/RESONATORS

H.K. Crystals Co., Unit H, 22/F, Shield Ind. Ctr., 34-36 Chai Wan Kok St., T.W. H.K.Tel (852) 4120121 Fax (852) 4985908



Oak Frequency Control Group,



Richardson Electronics, Ltd., 40W	267 Keslinger Rd., LaFox, IL 60147	(800) 348-5580
-----------------------------------	------------------------------------	----------------

INDUCTORS

85
85

	Small Signal & Power GaAs FETs Small Signal & Power Bipolars			
	Silicon & GaAs MMICs: Amplifiers, Prescalers, Downconverters			
I	California Eastern Laboratories			
	4590 Patrick Henry Dr. Santa Clara CA 95054 1817 408-988-3500 FAX 408-988-0279			
N				
1	icro Hybrids, Inc., 2864 Route 112, Medford, NY 11763(516) 732-3448			
1	ESISTORS			
ļ	gh Power			
1	cnaroson Electronics, Ltd., 40W267 Keslinger Rd., LaFox, IL 60147			
	RANSISTORS			
1	r Power Bipolar chardson Electronics, Ltd., 40W267 Keslinger Rd., LaFox, IL 60147			
1	Power FET			
I	charoson Electronics, Ltd., 40W267 Keslinger Rd., LaFox, IL 60147			
	MODULAR COMPONENTS			
I	MPLIFIFRS			
ľ	oadband			
ľ	ontech, Inc., 381 Industrial Way East, Eatontown, NJ 07724(908) 542-113 Fax (908) 542-1118			
1				

Sprague Goodman, 134 Fulton Ave., Garden City Park, NY 11040-5395......(516) 746-1385

NEC Wireless Semiconductor Products

Richardson Electronics, Ltd., 40W267 Keslinger Rd., LaFox, IL 60147 (800) 348-6680 FILTERS

Crystal

Reeves-Hoffman, 400 W. North St., Carlisle, PA 17013	(717) 243-5929
Saw Phonon Corp., 7 Herman Dr., PO Box 549, Simsbury, CT 06070	(203) 651-0211
SAW Components & Subsystems	x (203) 651-8618

MIXERS

Merrimac Industries, Inc.,	
41 Fairfield PI., W. Caldwell, NJ 07006	
MODULATORS FSK	
Merrimac Industries, Inc.,	
41 Fairfield Pl., W. Caldwell, NJ 07006	(201) 575-1300 Fax (201) 575-0531
0.81	(,
Merrimac Industries, Inc.,	
A1 Fairfield PL W Caldwell N107006	(201) 575 1200 Env (201) 575 0521

OSCILLATORS



March 1995

SYSTEM SUBASSEMBLIES

Crystal

Oak Frequency Control Group,	
100 Watts St., PO Box B. Mt. Holly Springs, PA 17065	.(717) 486-3411
Wilmanco 5350 Kazuko Ct. Moorpark, CA 93021	(805) 523-2390

AMPLIFIERS Broadband

Trontech, Inc., 381 Industrial Way East, Eatontown, NJ 07724....(908) 542-1133 Fax (908) 542-1118 LNA Trontech, Inc., 381 Industrial Way East, Eatontown, NJ 07724....(908) 542-1133 Fax (908) 542-1118

Linear Power, RF

PACIFIC AMPLIFIER CORP. (805) 375-5773

- LO-MED-HI-POWER LINEAR AMPLIFICATION
- CELLULAR, TELEPHONY MULTI CHANNEL USE
- -30 dBc STANDARD; -60 dBc FEED FORWARD

RF Power

Trontech, Inc., 381 Industrial Way East, Eatontown, NJ 07724(908) 542-1133 Fax (908) 542-1118 High Dynamic Range

Trontech, Inc., 381 Industrial Way East, Eatontown, NJ 07724 (908) 542-1133 Fax (908) 542-1118

PRINTED CIRCUIT BOARDS

CALL SOUTHWEST CIRCUITS NOW! (800) 279-5572

PROTOTYPES AND SHORT RUNS FOR ALL MICROWAVE AND WIRELESS APPLICATIONS

ALL POPULAR MICROWAVE LAMINATES: PTFE -TEFLON - DUROID - GX

MULTI-LAYERS – QUICK TURN – EXOTICS

Southwest Circuits, 3760 E. 43rd Place, Tucson, AZ 85713 TEL (602) 745-8515 FAX (602) 747-8334 MODEM (602) 747-5108

SYNTHESIZERS

Sciteq Electronics, 4775 View Ridge Ave., San Diego, CA 92123

(619) 292-0500

RF TRANSMISSION COMPONENTS

CABLE ASSEMBLIES

Kaman Instrumentation, 1500 Garden of the Gods, Colorado Springs, CO 80907(719) 599-1821

DIRECTIONAL COUPLERS

FILTER ASSEMBLIES

REEVES-HOFFMAN

For your Crystal Filter requirements from 1 KHz to 150 MHz Fundamentals and up utilizing Overtone Crystals.

400 W. North St., Carlisle, PA 17013, Tel: 717-243-5929, Fax: 717-243-0079

MICROWAVE CONNECTORS

MULTICOUPLERS

Trontech, Inc., 381 Industrial Way East, Eatontown, NJ 07724 (908) 542-1133 Fax (908) 542-1118

PHASE SHIFTERS

Merrimac Industries,	Inc.,	
41 Fairfield Pl., W.	Caldwell, NJ 07006	0 Fax (201) 575-0531

POWER DIVIDERS/COMBINERS

RF CONNECTORS

SWITCHES

Electromechanical

Dow-Key Microwave Corp.,	1667 Walter St., Ventura,	, CA 93003	.(805) 650-0260
and the second se			

VACUUM CAPACITORS

COMET North America, 11 Belden Ave., Norwal	, CT 06850	(203) 852-1231
---	------------	----------------

CAD/CAE SOFTWARE & SYSTEMS - SOFTWARE

MATERIALS AND HARDWARE

COMPONENTS/HYBRID PACKAGES

TEST EQUIPMENT

Quality Reconditioned TEST EQUIPMENT

HP, Tektronix, Fluke, Wavetek, Wiltron, etc.

Oscopes, Analyzers, Signal Generators, Multimeters
Sales and Rentals

We also buy your surplus test equipment!

VAPTECH Phone: 800-336-7723 • Fax: 707-928-1963

SPECTRUM ANALYZERS

DC TO LIGHT, P.O. Box 7140, Bozeman, MT 59771 (406) 586-5399 Fax (406) 586-6556

SERVICES

ANTENNA MEASUREMENT SYSTEMS Jet Consultants, Inc., 8501 Beck Rd., Bldg. 2227, Belleville, MI 48111-1254(313) 482-5505 ANTENNA DESIGN & MEASUREMENT Antenna Design Specialists, 1171 Melayn Dr., Lebanon, OH 45036(513) 932-3385 CONSULTANTS

Management Recruiters of Boulder	
Windy Bradfield CSAM, Bob Sund	
Goldman Research, 12705 Monfort, Dallas, TX 752	30
RF Design & Modeling - Spice, EEsof, Wireless	WNJU80A@PRODIGY.COM

EMC/EMI TESTING Liberty BEL EMC SVCS., P.O. Box 5431, MS20, Compton, CA 90224(310) 537-4235 Above MS20 represents RF Design

OEM PRODUCTS	
Locus, Inc., 1842 Hoffman St., Madison WI	53704

DIGITAL SIGNAL PROCESSING

SYSTEMS DEVELOPMENT REAL TIME Adaptive Technology, Inc., 309 Curtis St Syracuse NY 13208 (800) 724-6968 Fax (315) 472-3279

EMC PRODUCTS

SURGE & TRANSIENT PROTECTORS Polyphaser Corp., P.O. Box 9000, Minden, NV 89423

.(800) 325-7170, (702) 782-2511



RFadvertising index

ADVERTISER	PAGE #	READER SVC #	ADVERTISER	PAGE #	READER SVC
A-Comm Electronics			Marconi Instruments, Ltd	15	1
Advanced Communication Search			Marconi Instruments	47	3
American Tech Ceramics			Merrimac	25	
Amplifier Research			Micro Communications Executive S	earch 85	0
Antec Engineering & ESP			Mini Circuits	16-17, 59, 65, 71	1 3 4 12 47 53 5
AT & T Strategic Support Group			Mobile Systems International	85	
Bliley Electric Co.			Mobility	86	q
Bomar Crystal Co.			Motorola Cellular	86	q
CAD Design Services, Inc.			MTTS Show	32	
California Eastern Labs			MYcom Instruments	89	11
Chomerics			National Semiconductor	21	
Communication Concepts			NCS Jobline	84	8
Compact Software		2	Nedrud Data Systems	1.1	1
Jon Gallagher & Associates			Noise Com Inc.	35	······
Eagleware			PPA Industries	89	10
Electro-Metrics			Pole Zero	20	1
EMI Filter			Programmed Test Sources	31	9
ENI			Rakon Ltd.	48	3
Fortune Communications Group			Raltron/Time & Frequency	57	A
Fortune Personnel Consultants of Ralei	gh, Inc87		Ramsey Electronics	89	11
Geotek Design Services		108	RF Power Products Inc	85	0
Giga-tronics Inc.		7	Richardson Electronics	39	Q
Henayre		103	Rogers Corn		1
Gould Electronics		72	Saratoga Software Corporation	82	7
Ienry Radio			Sciex	89	11
lewlett-Packard/Signal Analog Division	n	29.51	Silicon Valley Power Amps	50	2
Hexawave		20	Southwest Circuits	45	
ntegrated Components Systems		43	Spectrum Electronics	86	0
nt'l Crystal Mfg.		22	Stanford Research	40	A-
sotemp Research, Inc.		70	Surcom Associates	63	E
TS Corporation		100	Sypergy Microwaye	77	
TT G T Č		30	TTE	45	······································
Jan Crystals		40	T-Tech	52	
FW Industries		27	Tele-Tech Search	84	9
Kalmus Engineering	9	6	Temex	18	
Kay Elemetrics		44	Tesoft Inc		
Gingsley Software Group		104	Toko America Inc	51	
S Electronics			V/S Networks	89	
WG North America		18	Valpey-Fisher		
ap-Tech		45	Vectron	75	
CF Enterprises		78.58	Waypoint Software	QA	
æader Tech		73	Werlatone Inc		
PKF CAD/CAM Systems, Inc.		50	Wilmanco		
M/A Com (3 divisions)	23	19 59 60 61 62	Z-Domain		

RF guide to editorial coverage

ABB

ABB	24	Georgia Tech Research Institute	e 20	Polyflon Co.	59
Advanced Technology Acquisitio	n,	Hewlett-Packard Co.	57	Proxim, Inc.	28
Qualification and Reliability Wo	orkshop 20	HP-EEsof	81	Qualcomm, Inc.	69
AEG Transportation Systems, Ir	nc. 24	Hyperlink Technologies, Inc.	57	Racal Instruments, Inc.	58
ALK Engineering	81	IC Card Systems & Design	28	REMCOM Inc.	81
American Meter Co.	28	ingSOFT Ltd.	81	RF Industries, Ltd.	60
American Superconductor Corp.	24	International Conference on		RF Monolithics, Inc.	28
American Technical Ceramics	60	Electromagnetics for Advanced		Rohde & Schwarz	26
Ameritech	22	Applications	22	R & S BICK Mobilfunk	26
AML Communications	59	Intusoft	81	Sage Laboratories. Inc	58
Analog & RF Models	80	Jay-El Products	24	Sematech	20
Analog Devices	61, 69	KEL-Com	58	SGS-Thomson Microelectroni	cs 61
Andrew Corporation	24	MacNeal-Schwendler Corp.	24, 69, 81	Sherritt. Inc.	59
Ansoft	81	Made-it Associates	81	Somersoft	81
Arden Technologies, Inc.	81	Matrix Test Equipment, Inc.	30	Sonnet Software, Inc.	81
Berkeley Varitronics Systems, In	nc. 58	Meta Software	81	Spefco Software	81
Besser Associates	81	MicroSim Corp.	80	Standex Electronics	60
Boonton Electronics Corp.	69	Mini-Circuits	69	Stanford Telecom	46
CAD Design Services	81	MITEQ Corp.	59	Storm Products, Inc.	60
California Scientific Software	81	Motorola International Cellular	26	Strategies Unlimited	69
CDMA Development Group	22	Motorola Semiconductor	57	Systems Eng. & Mngmnt, Co.	57
Celeritek, Inc.	61	NASA	24	Tatum Labs. Inc	81
CliniCom	28	National Semiconductor	57	Tektronix	26 38 58 69
Communication Solutions	61	NEC, Inc.	26	Tellurian Technologies Inc	59
Compact Software, Inc.	69, 70, 80	Nedrud Data Systems	80	Tesoft	81
Conductus Inc.	26	NIST	20	Trompeter Electronics Inc	60
Department of Defense	20	Nonlinear Technologies, Inc.	58	Tru-Connector Corp	60
Design Automation, Inc.	81	Northern Telecom	26	Vari-L Company Inc	24 61
DGS Associates	81	NSF	20	Viewlogic Systems Inc	24, 01
Eagleware Corp.	69,80	Optimization Systems Associate	s. Inc. 69	Waterloo Manle Software	69
Electronic Industries Association	n 20	PCS Group	26	Waypoint Software	81
ENI	59	Pensar Technologies, LLC	58	Xircom, Inc	26
Ericsson Components	24, 26	Piezo Technology, Inc.	59, 81	Z-Communications, Inc	61
			,		01

New System 32 Software...



verify your designs... find better solutions.

- Typical design flow



Initial synthesis in =M/FILTER=

REAL-TIME CIRCUIT SIMULATION

- * Accurate models
- * Easy nodal entry
- Schematic entry
- > Tune by tapping
- * Super-fast optimization
- > Unrestricted noise
- * Statistical analysis
- * 3-D plotting





Tune or optimize in =SuperStar= simulator

- CIRCUIT SYNTHESIS
- =FILTER= (L-C filters)
- Coupled-resonator, zig-zag, symmetric, Blinchikoff, conventional, other structures
- All popular transfer shapes
- A Group-delay equalizers

=M/FILTER= (microwave filters)

- End, edge, hairpin, combline, elliptic, interdigital, stepped-Z, lowpass, bandstop, highpass
- A Microstrip, rod, stripline, coax, generic
- Layout generation

=OSCILLATOR=

- * L-C, SAW, crystal, T-line
- * VCOs
- * Noise estimation



SAME PRICES INTERNATIONALLY DIRECT SALES & USER SUPPORT BY FAX, PHONE OR LETTER

Layout to plotter, printer, HPGL and DXF files

=MATCH=

- A Multiple algorithms
- & General synthesis & order
- Active or passive
- Arbitrary terminations
- =A/FILTER= (active filters)
- > Multiple structures
- All popular transfer shapes
- > Non-ideal op-amps

System 32 available for





Windows versions are 32-bit Complete packages from \$695 Money-back guarantee Free technical support No annual fees

INFO/CARD 57 Free technical suppo No annual fees

Eagleware Corporation * 1750 Mountain Glen * Stone Mtn, GA 30087 * USA TEL (404) 939-0156 * FAX (404) 939-0157 RF POWER AMPLIFIERS (Standard or Custom)

MHz - 2 GHz •

<u>1 W - 1 kW</u>

	Output		MODUL	ES	Output MODULES		ES		
Part No.	Power	Gain	DC Supply	PKG	Part No.	Power	Gain	DC Supply	PKG
2 MHz - 30 MHz					400-225-50-10	50W	10dB	24/28V	41
30-2-5-35	5W	35dB	24/28V	E3	400-225-50-18	50W	18dB	24/28V	A2
30-2-50-35	50W	35dB	24/28V	E3	400-225-50-35	50W	35dB	24/28V	A3
30-2-100-35	100W	35dB	28V	E3				21201	110
30-2-200-35	200W	35dB	28V	E3	400-225-100-10	100W	10dB	28V	AL
					400-225-100-18	100W	18dB	28V	A2
30 MHz - 100 MHz					400-225-100-35	100W	35dB	28V	A3
100-30-5-35	5W	35dB	24/28V	E3					
100-30-100-35	100W	35dB	28V	E3					
FO MIL 160 MIL					225 MHz - 600 MH	Z			
50 MHz - 150 MHz	211/	10.10			600-225-30-10	30W	10dB	24/28V	Al
150-50-2-40	2W	40dB	12/15V	C3	600-225-30-18	30W	18dB	24/28V	A2
150-50-100-35	100W	35dB	28V	A3	600-225-30-30	30W	30dB	24/28V	A3, B3
150 1411. 200 1411									
150 MHZ - 200 MH2	10011	10.10	001/		400 MHz - 600 MHz	2			
200-150-100-10	100W	1008	28V	Al	600-400-30-10	30W	10dB	24/28V	A1
200-150-100-18	100 W	18dB	28V	A2	600-400-30-18	30W	18dB	24/28V	A2
200-150-100-35	100 W	320B	28V	A3 .	600-400-30-30	30W	3 0d B	24/28V	A3, B3
200 150 200 35	20011/	25.10	201/	4.2	0.05 1.444				
200-130-200-35	200 1	3.500	26 V	A3	925 MHz				
50 MHz - 250 MHz					925-1-8	IW	8dB	12/15V	DI
250-50-200-10	160W	10.40	201/	A 1	100 1411 500 1411				
250-50-200-18	160W	18dB	20 V 28 V	A1 A2	100 MHZ - 500 MH2	5111	20.10	A 4/801 /	
250-50-200-35	160W	35dB	281	A2	500-100-5-50	2 M C	30dB	24/28V	A3
250-50-200-55	100 ₩	5.000	20 V	AS	500 100 10 20	1011/	20.10	04/001/	
50 MHz - 400 MHz					500-100-10-50	10w	30018	24/28V	A3
400-50-1-30	IW	30/JB	12/15V	C3	500 100 100 20	10034	20.40	2017	
100 00 1 00		5000	12/15/1	C5	500-100-100-50	100 W	300B	28 V	A3
225 MHz - 400 MHz					500 MH2 1000 ML	I-,			
400-225-1-35		35dB	12/15V	C3	1000 500 10 9	1011/	ar o	24/2011	
		2000	12/13/4	¢,5	1000-500-10-8	1000	60B	24/28 V	AI
400-225-10-35	10W	35dB	24/28V	43	1000-500-10-10	100	2040	24/28 V	AZ
		0.000	2 1 20 1	115	1000-00-10-30	10.44	JUUD	24/28 V	AS
400-225-30-10	30W	10dB	24/28V	Al	10 MHz - 1200 MHz	,			_
400-225-30-18	30W	18dB	24/28V	A2	1200-10-10-30	10W	30/IB	24/281	12
400-225-30-35	30W	35dB	24/28V	A3. B3	1200 10-10-50	1011	50 ub	24/20 V	AS

Test Fixture (Option "B") includes heat sink, fan, thermal shutdown, and electrical fuse protection * Rack-mount amplifiers: 120 Vac - 60 Hz / 240 Vac - 50 Hz

MODULES - SMALL SIZE • HIGH EFFICIENCY



1

• 200 watts

- 150 200 MHz
- 55% overall efficiency
- 35 dB gain
- 4.84" x 2.0" x 1.0"



- 100 watts
- 225 400 MHz
- 45% overall efficiency
- 10 dB gain
- 3.0" x 2.0" x 1.0"

SYSTEMS - LOW COST . RUGGED PROTECTION



dBm	MHz/D.v	MHz	kHz Res
-30	1	11111	1000
-40			
-50			
-60			
-70			
-80	un ferran	the standard	
-90			
-100			
-110		i i	
	0 0000 0dB Att SMALL S'G	1000.0000 Gen -80 dBm NAL GAIN VERSUS FREQU	2000 0000 20ms ENCY CURVE

- 10 MHz 1200 MHz
- 10 watts CW
- 40 dB
- 19" x 7" x 18"
- 35 lbs maximum

LCF ENTERPRISES • 651 Via Alondra, # 712 • Camarillo 93012 USA • Phone: 805-388-8454 • FAX: 805-389-5393