

WIRELESS
16 YRS
LEADERSHIP

RF design™

engineering principles and practices

September 1995

Simulator Analyzes Circuits Using Modulated Signals



HEWLETT
PACKARD


Featured Technology —
Crystal Oscillator Analysis

Industry Insight —
Advances in RF Research

Low Power *is* PLLatinum.

PLLatinum™: the industry's highest performing PLLs.


Our single and dual PLLs are about to take you lower than you've ever gone before. In fact, the PLLatinum family of PLLs consumes just 6mA at 3V. As a result, they deliver increased battery life for all your wireless designs. They also offer better noise performance, improved lock times, and the industry's widest frequency range. So call 1-800-324-4443, Ext. 604* for a free sample and a product selection guide. Because isn't it time you went PLLatinum?

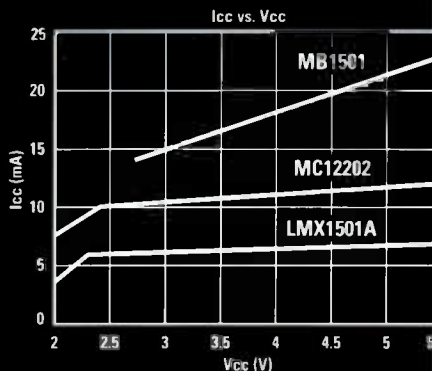

	LMX1501A	LMX1511	LMX2314/15	LMX2320	LMX2325	LMX2330A	LMX2331A	LMX2332A	LMX2335	LMX2336	LMX2337
RF Input - Main PLL	1.1GHz	1.1GHz	1.2GHz	2.0GHz	2.5GHz	2.5GHz	2.5GHz	1.2GHz	1.1GHz	1.1GHz	550MHz
RF Input - Aux PLL						510MHz	510MHz	1.1GHz	1.1GHz	1.1GHz	1.1GHz
ICC (typ) @ 3V	6mA	6mA	6mA	10mA	11mA	15mA	14mA	8mA	9mA	11mA	9mA
Powerdown (typ)	N/A	N/A	30µA	30µA	30µA	1µA	1µA	1µA	1µA	1µA	1µA



National Semiconductor

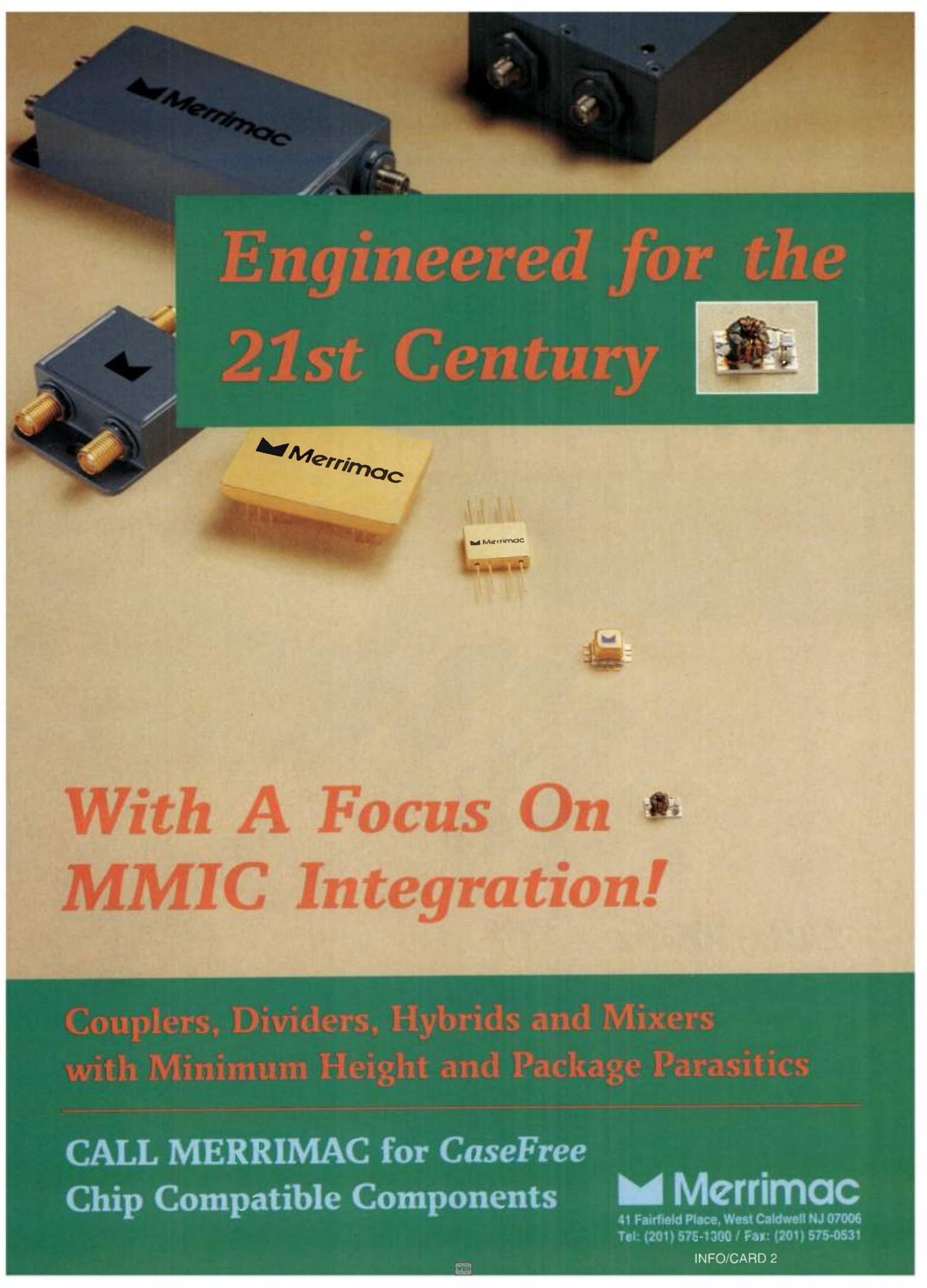

Engineered for the 21st Century

With A Focus On MMIC Integration!

**Couplers, Dividers, Hybrids and Mixers
with Minimum Height and Package Parasitics**

**CALL MERRIMAC for CaseFree
Chip Compatible Components**

 **Merrimac**

41 Fairfield Place, West Caldwell NJ 07006
Tel: (201) 575-1300 / Fax: (201) 575-0531

INFO/CARD 2

THE WORLD'S LARGEST SELECTION


POWER SPLITTERS/ COMBINERS



2kHz-10GHz from **\$2⁹⁵**

Choose from over 480 standard off-the-shelf models from 2-way to 48-way; 0°, 90° and 180°; 50 and 75 ohms; covering 2kHz to 10GHz. Mini-Circuits will also supply your special needs such as wider bandwidths, higher isolation, lower insertion loss, and phase matched ports...all at catalog prices with rapid turnaround time. Models include surface mount, plug-in, flat-pack and standard connectorized designs such as SMA, N, TNC, C, and F connectors as well as custom designs. Ultra-miniature surface mount units provide excellent solutions in cellular communications, cable systems and countless wireless applications. All units come with a 1 year guarantee and "skinny" 4.5 sigma repeatability unit-to-unit and production run to production run. Catalog models are guaranteed to ship within one week.

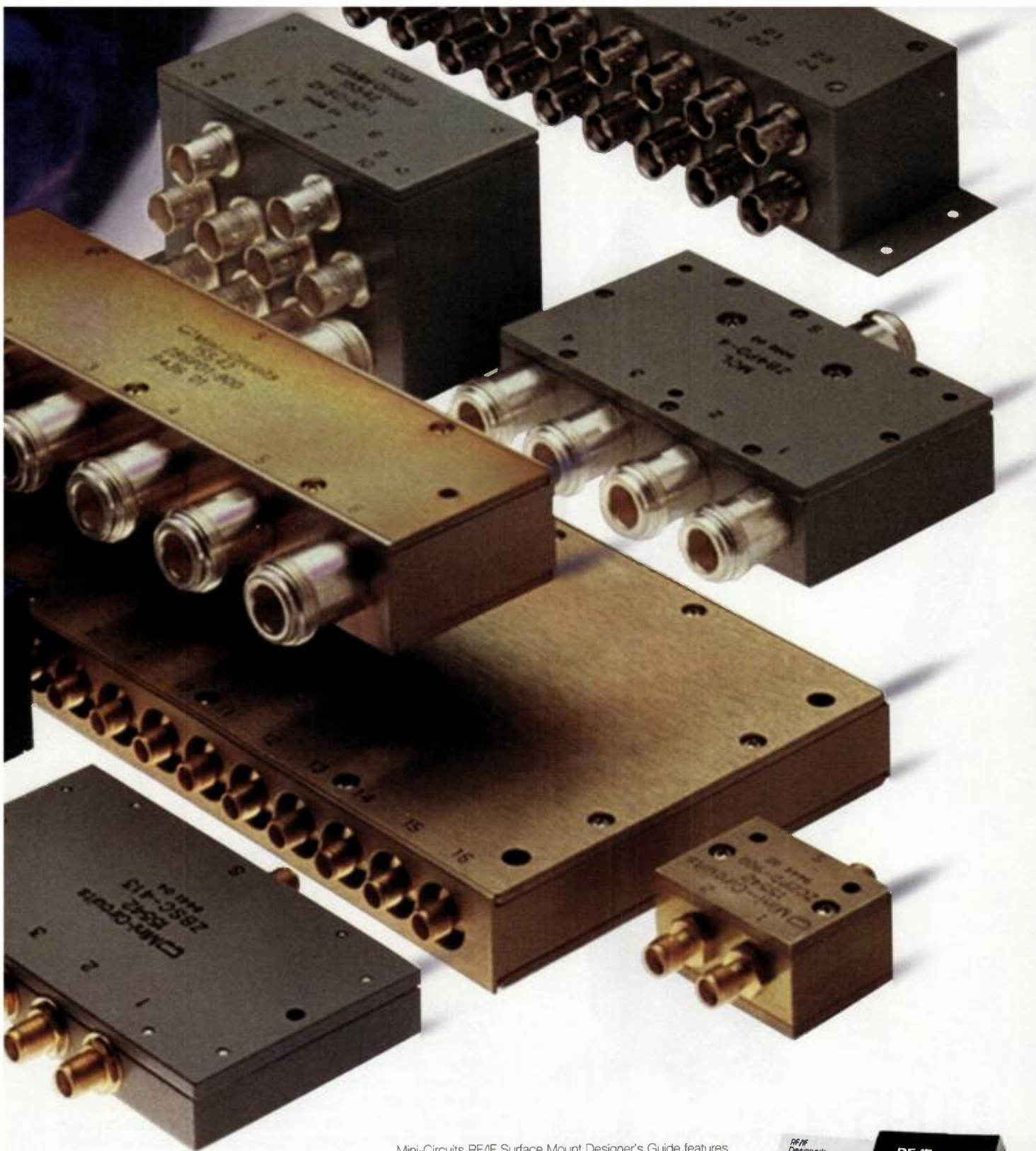Mini-Circuits...we're redefining what VALUE is all about!



Mini-Circuits RF/IF Surface Mount Designer's Guide features 48 pages of the most up-to-date and complete product and specification information about Mini-Circuits surface mount components. The RF/IF Microwave Handbook is packed with 740 pages of articles, selection guides and detailed specifications for Mini-Circuits components.

Call, write or fax for your free Surface Mount Designer's Guide and Handbook today!

INFO/CARD 3



Mini-Circuits®

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661


For detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER • MICROWAVE PRODUCT DATA DIRECTORY • EEM • MINI-CIRCUITS' 740- pg. HANDBOOK.

CUSTOM PRODUCT NEEDS...Let Our Experience Work For You.

F 194 Rev Orig

2.5KHz-8GHz AMPLIFIERS

(3 Piece Set)

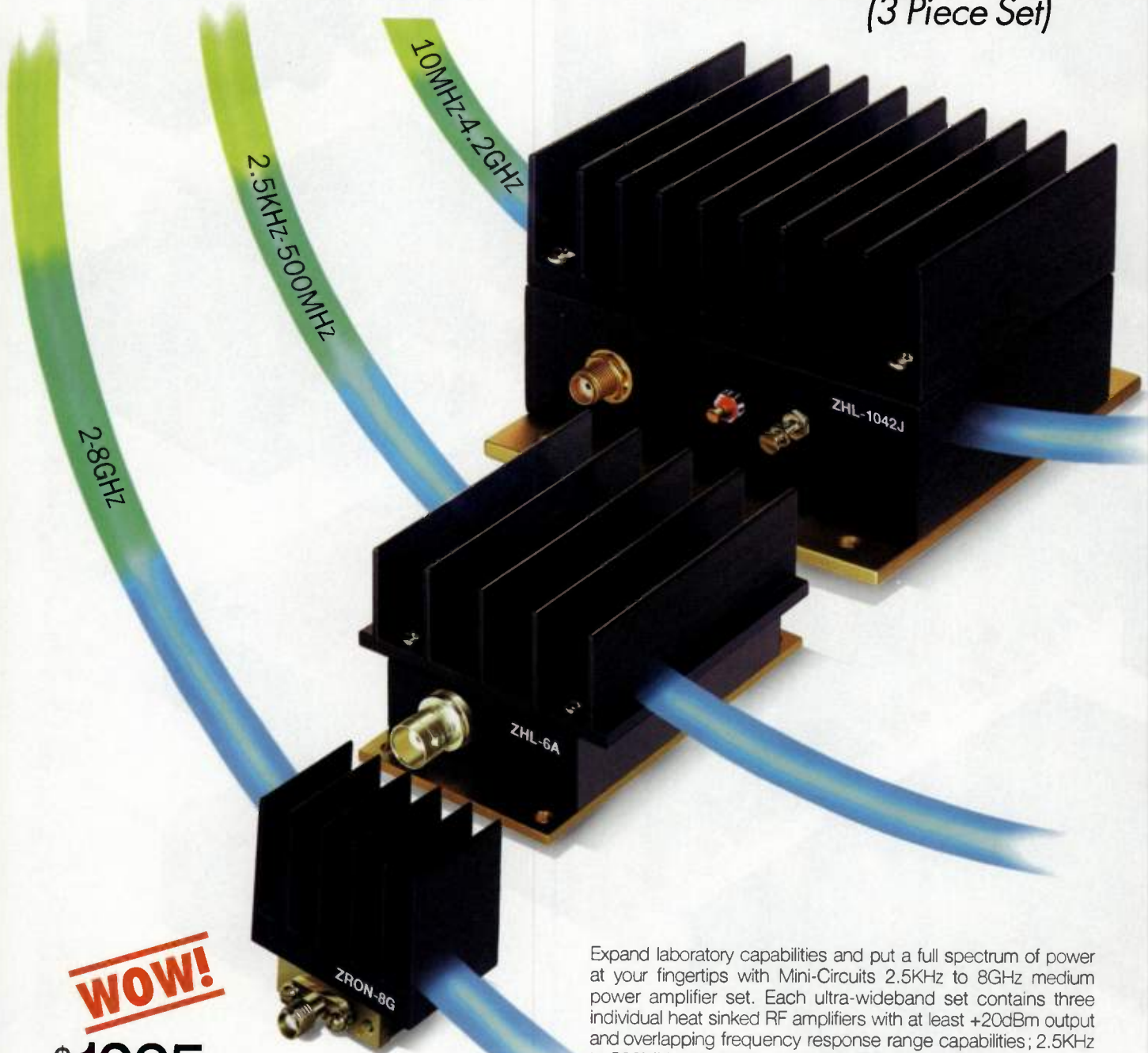

WOW!

\$1095 (Set of 3 1-9 qty.)
only **+20dBm Power Output, 20dB Gain**

Expand laboratory capabilities and put a full spectrum of power at your fingertips with Mini-Circuits 2.5KHz to 8GHz medium power amplifier set. Each ultra-wideband set contains three individual heat sunked RF amplifiers with at least +20dBm output and overlapping frequency response range capabilities; 2.5KHz to 500MHz, 10MHz to 4.2GHz and 2GHz to 8GHz. Applications for these amplifiers include increasing the signal levels to power meters, spectrum analyzers, frequency counters and network analyzers as well as boosting signal generator outputs.

You can buy these amplifiers individually at Mini-Circuits already low prices, or own the full spectrum set for the money saving price of only \$1095 (1-9 qty.) ! To order from stock with a guarantee to ship within one week, call Mini-Circuits today ! ☎

Mini-Circuits...we're redefining what VALUE is all about!

Model :	Freq. (MHz)	Gain (dB)	Power Output, dBm @ 1dB Compression	DC Power Volt V	Current mA	Conn. Type	Indiv. Price (\$) (1-9 qty.)
ZHL-6A	.0025-500	21	+23	+24	350	BNC	199
ZHL-1042J	10-4200	25	+20	+15	330	SMA	495
ZRON-8G	2000-8000	20	+20	+15	310	SMA	495

Set of 3 Amplifiers # KZHL-318: \$1095 (1-9 qty.)

Mini-Circuits®

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661

For detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER • MICROWAVE PRODUCT DATA DIRECTORY • EEM • MINI-CIRCUITS' 740- pg. HANDBOOK.

CUSTOM PRODUCT NEEDS...Let Our Experience Work For You.

INFO/CARD 4

F 176 Rev C

featured technology

26 SPICE Techniques for Analyzing Quartz Crystal Oscillators

The startup transient behavior, open-loop response and Nyquist plots for crystal oscillators are modeled using a free evaluation version of a commercial SPICE simulator. — *T. Kien Truong*

cover story

36 Circuit Envelope Simulator Analyzes High-Frequency Modulated Signals

This article describes a new circuit envelope simulation technology which has advantages over SPICE and harmonic balance when simulating the complex digital modulations used in modern communication systems. — *Andy Howard*

tutorial

54 Initial Guidelines for Layout of Printed Circuit Boards


This tutorial lays out some guidelines for laying out printed circuit boards. The article presents some general rules, examines transmission line behavior of circuit traces, discusses distributing DC power on RF pc boards, and gives some advice for avoiding ground loops. — *Gary A. Breed*

60 Phase Noise Measurements for Under \$250

Using the discriminator/delay line method, along with a few signal processing circuits which interface with a computer, this measurement scheme accurately determines phase noise for low phase noise or fast-drifting oscillators. — *W.A. Suter*

70 Design Parameters for 1- Through 7-Pole Input -Matched Lowpass/Highpass Filters

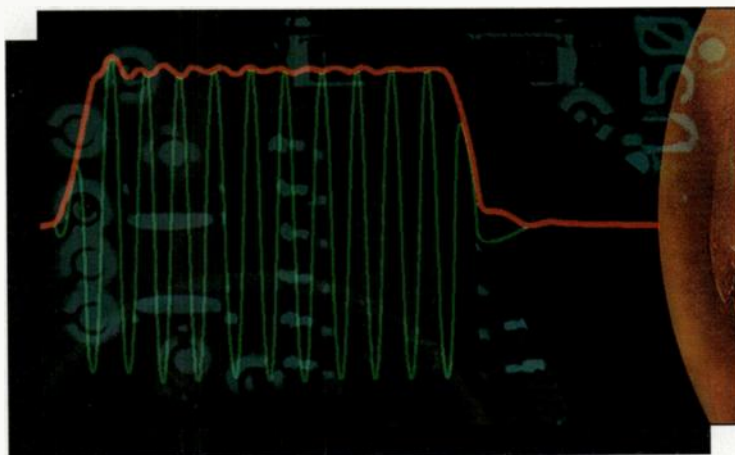This article presents a table to obtain element values for first through seventh-order Butterworth branching filters. Some aspects of the numerical process used to derive the table values are discussed, and the new table values are compared to those given in other references. — *Chase P. Hearn*




departments

- 8 Editorial
- 12 Letters
- 13 Courses
- 16 Calendar
- 20 News
- 24 Industry Insight
- 46 New Products
- 80 Product Forum
- 83 Marketplace
- 95 New Literature
- 96 New Software
- 98 Advertiser Index
- 98 Company Index
- 99 Info/Card

RF DESIGN (ISSN:0163-321X USPS: 453-490) is published monthly and semi-monthly in September. September 1995, Vol.18, No. 9. *RF Design* is a registered trademark of Argus Inc. Copyright 1995 by Argus Business, a division of Argus Inc., 6151 Powers Ferry Road, NW, Atlanta, GA 30339, (404) 955-2500. Editorial and advertising offices at 6300 S. Syracuse Way, Suite 650, Englewood, CO 80111, (303) 220-0600. Printed in USA. Second-Class Postage paid at Atlanta, GA and at additional mailing offices. Subscription office: *RF Design*, P.O. Box 1077, Skokie, IL 60076. Subscriptions are \$42 per year (\$72 for two years) in the United States; \$62 (surface mail) or \$102 (Air Mail) per year for foreign countries. Payment must be made in U.S. funds and accompany request. If available, single copies and back issues are \$8.00 each (in the U.S.). This publication is available on microfilm/fiche from University Microfilms International, 300 Zeeb Road, Ann Arbor, MI 48106 USA (313) 761-4700. Authorization to photocopy items for internal, personal or educational classroom use is granted by *RF Design*, provided the appropriate fee is paid directly to Copyright Clearance Center, 222 Rosewood Drive, Danvers, MA 01923 and provided the number of copies is fewer than 100. For authorization, contact the Copyright Clearance Center at (508) 750-8400. The Transactional Reporting Service fee code is: 0163-321X/95/\$3.00. For those seeking 100 or more more copies, please contact the magazine at (303) 220-0600.

SUBSCRIPTION INQUIRIES: (708) 647-0756.
POSTMASTER & SUBSCRIBERS: Please send address changes to R.F. Design, P.O. Box 1077, Skokie, IL 60076.

HIGH POWER QUADRATURE HYBRIDS

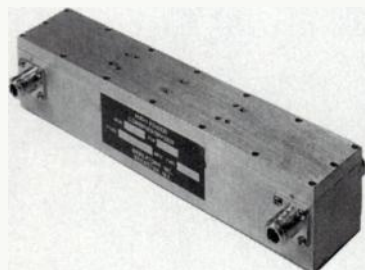

**FREQ. RANGE 100-1000 MHz
POWER 250 WATTS CW**

TYPICAL SPECIFICATIONS

**MODEL QH3198 100-300 MHz
MODEL QH3199 300-1000 MHz**

LOSS0.5db. max.
AMP.BAL..... ± 0.3 db max.
ISOLATION20db typ.
PHASE..... 90 ± 2 deg.
VSWR1.3:1 max.
CONNECTORSN

WERLATONE offers a full line of quadrature hybrids covering the 2-1000MHz frequency range at power levels to 1000 watts.

BROADBAND HIGH POWER

- DIRECTIONAL COUPLERS
- POWER COMBINERS
- HYBRID JUNCTIONS

WERLATONE INC.

DECADES AHEAD
P.O. Box 47
Brewster, NY 10509
Tel. (914) 279 6187
FAX. (914) 279 7404

RF editorial

Announcing the New RF Design Seminar Series

By Gary A. Breed
Editor

At the center of *RF Design's* mission is the delivery of timely and useful information. For ten years, part of that mission has been filled by the technical papers program and the full-day short courses offered at the RF Expo trade shows.

Now, we are taking that core educational program to new places. The *RF Design Seminar Series* has been developed to meet the instructional needs of engineers all around the country, not just on the East or West coast. In 1996, we are holding three events featuring an educational program that is much more comprehensive than we've had at the RF Expos.

The first of the series will be held in Dallas, Texas, January 17-19, 1996. We are excited to have an opportunity to bring *RF Design* to this important technology center. To our knowledge, no RF event like this has ever been held in Texas.

Next, we go to Las Vegas, April 24-26, 1996, where our seminars are part of the International Wireless Communications Expo (IWCE), sponsored by magazines of the Communications Group at Argus Integrated Media. Besides the hundred-plus radio communications suppliers, the RF Technology Pavilion at IWCE already has signed up more than 70 RF component, instrument and software companies to exhibit their wares.

The third venue for 1996 is greater Boston, in early October when the weather is great and fall colors are starting to show. We'll be out in the Route 128 corridor so engineers from high-tech companies in that area will be able to get to our seminars quickly and conveniently.

Now for the program — At the basic level, the *Introduction to RF Circuit Design* taught by Dave Hertling and



Bob Feeney of Georgia Tech has been expanded to three days in order to provide a more thorough treatment of RF basics. The need for engineers to develop new wireless products has created a huge demand for training (and re-training) of new engineers and those adding new RF expertise.

For instruction in specific circuit design areas, the *Practical High Frequency Filter Design* and *Oscillator Design Principles* courses taught by Randy Rhea will be offered. At least two of our 1996 events will also include *Classes of Power Amplifiers and When to Use Them*, taught by Nathan Sokol.

We have a large number of additional courses available to complete an advanced track, as well. We will select from topics like: *Antennas for Wireless*, *Digital Communications*, *Wireless Local Area Networks*, *Advanced Frequency Synthesis Techniques*, and *Low-Noise Amplifiers*. Watch for our announcements of specific seminar events to see which ones are offered.

Note that some of our events will also offer *Wireless Communications for Non-Engineers*, to help sales, marketing and purchasing staff understand new RF-based technologies.

Finally, we will have a technical papers program, too. A day of interesting contributions from you or your colleagues is planned, along with an informal poster session that will include a social reception sponsored by companies who have chosen our forum to exhibit their products and support our RF educational efforts.


We're excited about the new *RF Design Seminar Series*. These three events are just the beginning. Different cities in different corners of the U.S. are on our future "hit list." Your neighborhood may be next!

Over the last couple of years, we've seen EMC issues evolve from technical "what" questions to regulatory "when" statements. EMC is now, and at Kalmus we're addressing it head on."

"Our new Model 7100LC 100 watt RF power amplifier is a case in point. It has been designed specifically for EMC test applications. And, true to the Kalmus tradition of manufacturing highly functional, yet extremely cost competitive amplifiers, the 7100LC, we believe, is the smallest, lightest and least expensive 100 watt RF amplifier for EMC testing on the market."

"Another very important way we're addressing EMC is through our new affiliation with Thermo Voltek Corporation, a company focused upon all aspects of EMC. As a member of the Thermo Voltek family, we share their mission and can now offer our customers enhanced sales and service capabilities through Thermo Voltek's worldwide organization."

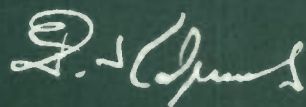"As we move closer to global EMC regulations, Kalmus remains steadfast to its engineering heritage and is committed to producing reliable and cost effective RF amplifiers for EMC testing. Call Kalmus or your Thermo Voltek distributor for complete information."



Frank Kalmus
Technical Director

Frank Kalmus is the founder of Kalmus (formerly Kalmus Engineering Inc.), a division of Thermo Voltek Corporation. As Kalmus' principal design engineer, he has designed over 200 RF amplifiers used for EMC test, medical/MRI, general laboratory, and communications applications.



Designed specifically for EMC testing, we believe Kalmus

Model 7100LC is the smallest, lightest, and least expensive 100 watt RF amplifier on the market. All functions can be remotely controlled via the optional Kalmus Model IF488, pictured (IEEE-488/RS-232 Interface), or hardwired.



MODEL 7100LC **100 Watt Broadband RF Power Amplifier**

STRAIGHT TALK ABOUT EMC AMPLIFIERS.

- Frequency range: 80-1000 MHz Broadband
 - MOS-FET circuitry
 - Power output: 100 watt CW minimum
 - Remote capability and outputs
 - Remote functions: all front panel controls - AC, Gain, Output Limit, ALC Speed, Blanking, VSWR Protection
 - ± 0.8 dB typical ALC gain flatness
 - VSWR tolerance: infinite, without damage
 - Protection: open, short, temperature, excessive drive power
- Forward and Reflected Power meter
 - Automatic Level Control (ALC): output level may be set to a fixed level of $\pm 1/2$ dB, with input variation up to 10 dB; selectable response time
 - Size: 48 cm x 48 cm x 17.8 cm

All Kalmus products are supported through Thermo Voltek's exclusive worldwide network of service and calibration facilities. Please call Kalmus or an authorized Kalmus distributor for complete information on this model, as well as other EMC test systems for EFT, SURGE, ESD, and PQF. 1-800-344-3341



Kalmus • 21820 - 87th S.E. • Woodinville, WA 98072 USA
Tel: (206) 485-9000 • Fax: (206) 486-9657

Distributor:

KeyTek • 260 Fordham Road • Wilmington, MA 01887 USA
(800) 753-9835 • Tel: (508) 658-0880 • Fax: (508) 657-4803

Kalmus and KeyTek are divisions of Thermo Voltek Corporation and Thermo Electron Corporation. Offices and service centers worldwide. ©Thermo Voltek Corporation. Specifications subject to change without notice.

Thermo Voltek

COMTEST BENELUX • COMTEST ITALIA • COMTEST UK • KALMUS • KEYTEK • VERIFIER • UVC

President — Argus Integrated Media
Stephen Stoneburn

Editorial and Advertising Offices
6300 S. Syracuse Way, Suite 650
Englewood, CO 80111
(303) 220-0600 Fax: (303) 267-0234

Vice President and Group Publisher
David Premo

Editor and Associate Publisher
Gary A. Breed

Technical Editor
Andrew M. Kellett

Consulting Editor
Andy Przedpelski, *The Shedd Group*

Editorial Review Board
Madjid A. Belkaid, *Univ. of Central Florida*
Alex Burwasser, *RF Products*
Dave Krautheimer, *MITEQ, Inc.*
Ed Oxner, *InterFET Corporation*
Jeff Schoenwald, *Rockwell International*
Raymond Sicotte, *American Microwave Corp.*
Robert J. Zavrel, Jr., *Consultant*

Corporate Editorial Director
Robin Sherman

Account Executives
Janell Count
Mike Henry
Cindy Solomonson
Gordon Henderson
Tisha Hill

Classified Advertising Manager
Shannon Shuman

Vice President — Special Advertising
Drew DeSarle

Vice President — Production and Promotion
Cherryl Greenman

Production Manager
Jenny Black

Reprints Manager
Vivian Peterson

Vice President — Marketing Research Director
Tina D'Aversa-Williams

Vice President — Circulation
Doug Florenzie

Creative Director
Brian Buxton

Art Director
Pamela Bobe

Staff Artist
Susumu Komatsu

List Rental Manager
Etta Davis

Argus Integrated Media Corporate Offices
6151 Powers Ferry Rd., N.W.
Atlanta, GA 30339-2941
Tel: (404) 955-2500



A Division of Argus Inc.

President — Argus Inc.
Scott Smith

Vice President, Finance — Argus Inc.
Wayne Otterbourg, C.P.A.

Senior Vice President — Argus Inc.
Arthur E. Sweum

President — Argus Trade Shows
Joe Randall

Subscription inquiries: (708) 647-0756

ADVANCED CRYSTAL TECHNOLOGY

VALPEY-FISHER

A SUBSIDIARY OF **MITEC**

Fundamentally Better!

- Ideal for SOMET and fiber optic networks
- Fundamental Crystals to 350 MHz
- Superior spurious response
- Standard and custom designs
- Pullability to 1000 ppm

1-800-982-5737 Ext. 345

VALPEY-FISHER CORPORATION
75 SOUTH ST. HOPKINTON, MA 01748
(508) 435-6831 • FAX (508) 497-6377

IN=O/CARD 7

XTAL

TECHNOLOGIES LTD


OVER THIRTY YEARS
EXPERIENCE IN
THE MANUFACTURE OF
MONOLITHIC CRYSTAL FILTERS
PACKAGE FILTERS
CRYSTALS

- PERFORMANCE • QUICK DELIVERY • PRECISION • RELIABILITY •
- COMPETITIVE PRICING • SERVICE •
- MADE IN THE USA • CUSTOM & STOCKING ORDERS •

APPLICATIONS FOR REGIONAL REPS NOW BEING ACCEPTED

28 MILLRACE DR • LYNCHBURG, VA 24502 • TEL 804-385-8300 • FAX 804-385-8100

INFO/CARD 63

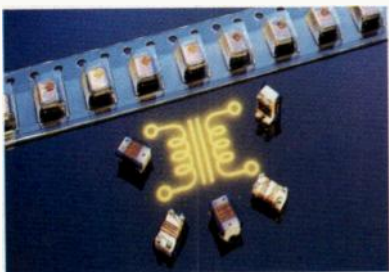

Wideband RF transformers are smallest available


These surface mount wideband RF transformers feature exceptionally low insertion loss and high current ratings. Built on a standard 1812 ferrite/ceramic body, their tops are encapsulated to protect the winding and provide a flat surface for pick and place equipment.

These 1:1 and 2:1 transformers come in 9 models covering the frequency range from 350 kHz to 680 MHz. Insertion loss is less than 1.5 dB and DC current handling ranges from 200 up to 700 mA.

Other turns ratios and ceramic body transformers for higher frequencies are also available.

For more information, contact **Coilcraft**, 1102 Silver Lake Road, Cary, IL 60013. 708/639-6400.

INFO/CARD 9

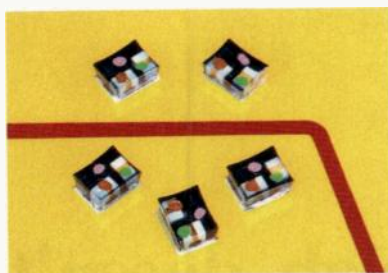

Surface mount LC filters are pretuned, tight tolerance

These space-saving low pass filters are pre-tuned, tight tolerance modules which serve a wide variety of filtering requirements.

They feature 3rd order Butterworth alignment, less than 0.3 dB insertion loss, 50 Ω characteristic impedance, and a compact 1812-size construction ideally suited for auto insertion and reflow soldering.

There are six standard models with 3 dB cutoffs from 15 to 500 MHz. All offer the benefits of an LC design: low insertion loss, high power handling, and controlled group delay.

For more information, contact **Coilcraft**, 1102 Silver Lake Road, Cary, IL 60013. 708/639-6400.

INFO/CARD 11

New "micro spring" inductors. Highest Q. Smallest cube.



Actual size.
1.65 - 12.54 nH.
200 Q at 1.8 GHz.

Now you can get the high Q of an air core inductor. Plus the convenience and cost savings of a true surface mount component.

Coilcraft 0906/1606 springs come in values from 1.65 to 12.54 nH with Qs at high frequencies that reach 200

and higher. Our 2% tolerance versions can help you eliminate circuit tuning altogether!

They're tape and reel packaged and have a jacket with a flat top for auto insertion. We even tin the leads for reliable soldering.

Order our \$50 C108 Designer's Kit or call us for our complete RF and surface mount product catalogs.

Coilcraft

1102 Silver Lake Road, Cary IL 60013
800/322-2645 FAX 708/639-1469


INFO/CARD 10

Introducing one of the world's smallest common mode EMI filters.

Our M2022-A has an 1812-size ceramic body and provides more than 20 dB attenuation from 30 to 500 MHz. Inductance is 4.2 μ H per winding.

Compared to equivalent toroidal

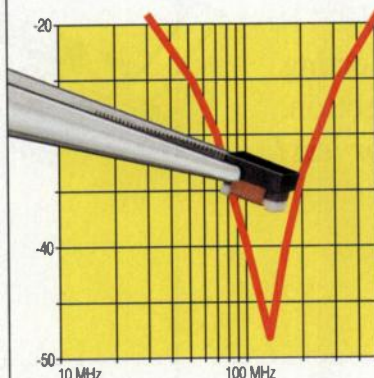We've cut your common mode EMI problems down to size.



designs, this filter is much smaller and less expensive.

DC current capacity is rated at 500 mA, while maximum DCR is only 800 mOhms. Custom filters with special combinations of impedance, frequency response and current handling are also available.

For our complete EMI/RFI filter products catalog, call 800/322-2645.

Coilcraft

1102 Silver Lake Road, Cary IL 60013
800/322-2645 FAX 708/639-1469

INFO/CARD 12

RF letters

Letters should be addressed to:
Editor, RF Design, 6300 S. Syracuse Way, Suite 650, Englewood, CO 80111. Letters may be edited for length and clarity.

What Ever Happened to ...

Editor,

I write to ask you or your staff for information concerning a fine old tube manufacturer – the Machlett Co. No information is to be found as to their address in the material that I have, so if you know what happened to them (absorbed/sold to another company??) I'd appreciate being able to contact them, particularly their chief engineer.

Charles Ratcliffe
Box 1068
Friday Harbor, WA 98250

Editor,

Does anyone know what happened to the Radiometer Electronics Co., which I believe was located near Copenhagen,

Denmark? They made high quality RF test equipment in the 70's and 80's. Is there a successor company or any enterprise supplying info and spare parts?

Charles King
P.O. Box 116
E. Berlin, CT 06023

Don't Oversimplify

Editor,

When I saw the tutorial on filter responses in *RF Design's* July issue, (pp. 68 - 73), I felt somewhat stimulated to read it. I was somewhat disappointed, however, when I read your introduction to the article. You justified your grossly oversimplified presentation (not one actual formula for a filter response!) by referring to your, "...philosophy of presenting concepts that assume a BSEE and no experience..." If your idea that a person with a BSEE and no experience cannot handle simple equations for filter responses is accurate, I have some bad news for these budding engineers: they're

not likely to get any experience! It is ironic that you could have this opinion, yet, in another article in the same issue, you have no problem showing circuit diagrams and Smith charts! Oversimplified tutorials that simply rehash what graduating engineers have likely already been exposed to in their classwork (to much greater, i.e. useful, detail) don't help anyone. I would suggest that you ditch your philosophy of assuming that your readers are technically illiterate.

Glenn Stumpff

For the most part I agree with Mr. Stumpff. Perhaps we chose too broad a subject to cover in the allotted two pages of space. In general, however, reader feedback has been strongly in favor of these simplified tutorials. This approach is confirmed by the kinds of questions asked during classes held at our RF Expo conferences – many engineers are starting with virtually no RF concepts. – Editor

NEVER

Just because our quality is high, doesn't

At Vectron, we've automated our manufacturing, aging and testing so you can enjoy high quality *and* low prices. So when you're selecting oscillators, spec Vectron, *and get the best for less!*



Call now for our
Free 100 page
catalog.



HIGH QUALITY

A Typical Vectron Value:
Subminiature PC Board Mount

OCXOs

- Superior Aging: 1×10^{-7} /year to 2×10^{-8} /year @ 5 MHz
- Ultra-High Stability: $\pm 1 \times 10^{-9}$ over 0°C to $+50^{\circ}\text{C}$
- Very Fast Warm-Up: 3×10^{-8} in less than 4 min.
- Subminiature Size: $1.4'' \times 1.06'' \times 0.76''$
European CO-08 package

RF courses

Introduction to RF & Wireless Engineering

October 10-13, 1995, Atlanta, GA

Principles of Modern Radar

November 6-10, 1995, Atlanta, GA

Far-Field, Anechoic Chamber, Compact and Near-Field Antenna Measurements

November 28-December 1, 1995

Information: Continuing Education, Georgia Institute of Technology, Atlanta, GA 30332-0385. Tel: (404) 894-2547.

Antennas and Antenna Systems: Practical Design, Implementation, and Testing

October 23-26, 1995, Washington, DC

Analog and Digital Cellular Networks: CDMA versus TDMA

October 30-November 1, 1995, Washington, DC

Wireless Telecommunications: An Introduction

November 13-15, 1995, Washington, DC

Digital Transmission Systems

November 13-17, 1995, San Diego, CA

Video Transmission and Broadcasting Via Satellite

November 20-21, 1995, Washington, DC

New HF Communications Technology: Advanced Techniques

December 4-8, 1995, Washington, DC

Information: The George Washington University, Continuing Engineering Education, Academic Center, Room T-308, 801 22nd Street, N.W., Washington, DC 20052. Tel: (202) 994-6106 or (800) 424-9773. Fax: (202) 872-0645.

Antenna Theory Simplified

September 14, 1995, Longmont, CO

Common-Mode Filter Design

September 15, 1995, Longmont, CO

Electromagnetic Compatibility Engineering

October 4-6, 1995, Palo Alto, CA

Information: Henry Ott Consultants, 48 Baker Road, Livingston, NJ 07039. Tel: (201) 992-1793, Fax: (201) 533-1442.

Short Course on Microwave and RF Measurements for Wireless Communications

November 28-29, 1995, Scottsdale, AZ

Information: Robert M. Judish, NIST, 325 Boradway, Boulder, CO 80303. Tel: (303) 497-3380, Fax: (303) 497-3970, email: judish@boulder.nist.gov.

RF & Microwave Measurements & Applications

October 2-5, 1995, Washington, DC

MPEG-2 & Alternative Video Compression Standards & Techniques

November 6-8, 1995, Palo Alto, CA

Error Correcting Codes with Applications to Communications Systems

December 11-14, 1995, Washington, DC

Information: University Consortium for Continuing Education, 16161 Ventura Boulevard, M/S C-752, Encino, CA 91436. Tel: (818) 995-6335. Fax: (818) 995-2932.

ASSUME

mean our prices are ... *they're not!*



LOW PRICES

A Typical Vectron Value:
Low Profile PC Board Mount

OCXOs

- Outstanding Stability: $\pm 5 \times 10^{-8}$ over 0°C to $+50^\circ\text{C}$
- Aging Characteristics: 1×10^{-8} /day, 2×10^{-6} /year @ 10 MHz
- Low Profile: 2" x 2" x 1" (reduced height available)
- Low Cost

\$100 (1000 qty)



The Crystal Oscillator Company
VECTRON LABORATORIES, INC.

P.O. Box 5160 • Norwalk, CT 06856-5160

Tel: 203-853-4433 • Fax: 203-849-1423

A **DOVER** TECHNOLOGIES COMPANY

TEMEX

ELECTRONICS, INC.

Temex Electronics manufactures crystals, crystal filters, LC filters and discriminators. We offer a standard line of 10.7 MHz, 21.4 MHz and 45.0 MHz monolithic filters to whatever your company may require. We cover a frequency range of 3.0 MHz to 200.0 MHz. With our computer aided designs we can realize most types of filters with realistic components and manufacture them at a very competitive price. Plus, we've been in business 12 years.

**ask about our
Monolithic Crystal
Filter Prototyping
Kits !**

OUR STANDARD MONOLITHIC CRYSTAL FILTERS

All 2 pole and 4 pole monolithics ship from stock on hand.

10.7 MHz	NO.	TEMEX	PASSBAND		STOPBAND			LOSS	RIPPLE		ULT. REJ.	TERM.(Rp//Cp)
	POLES	P/N	dB	±KHz	dB	±KHz	dB	dB	dB-MAX	dB-MIN.		OHM/PF
	2	TE5000	3	3.75	20	18.0	-	2	1.0		50	1800//+4
	4	TE5010	3	3.75	30	14.0	-	3	2.0		60	1500//+3
	6	TE5020	6	3.75	60	12.5	-	4	2.0		70	1500//+3
	8	TE5030	6	3.75	60	10.0	90	12.5	5	2.0	80	1500//+3
	2	TE5040	3	6.50	20	30.0	-	1	1.0		50	2700//0
	4	TE5050	3	6.50	30	15.0	-	2	2.0		75	3100//0
	6	TE5060	6	6.50	60	19.5	-	3	2.0		90	3100//0
	8	TE5070	6	6.50	60	13.0	80	17.5	4	2.0	100	3100//0
	2	TE5080	3	7.50	20	35.0	-	1	1.0		50	3000//0
	4	TE5090	3	7.50	30	17.5	-	2	2.0		75	3300//0
	6	TE5100	6	7.50	60	22.5	-	3	2.0		90	3300//0
	8	TE5110	6	7.50	60	15.0	80	20.0	3	2.0	100	3300//0
	2	TE5120	3	15.0	20	70.0	-	1	1.0		35	5000// -1
	4	TE5130	3	15.0	30	35.0	-	2	2.0		60	5000// -1
	6	TE5140	6	15.0	60	45.0	-	2	2.0		90	5000// -1
	8	TE5150	6	15.0	60	30.0	80	40.0	3	2.0	100	5000// -1

21.4 MHz	NO.	TEMEX	PASSBAND		STOPBAND			LOSS	RIPPLE		ULT. REJ.	TERM.(Rp//Cp)
	POLES	P/N	dB	±KHz	dB	±KHz	dB	dB	dB-MAX	dB-MIN.		OHM/PF
	2	TE5180	3	3.75	15	12.5	-	2	1.0		50	850//+6
	4	TE5190	3	3.75	30	12.5	-	3	2.0		70	850//+5
	6	TE5200	6	3.75	60	12.5	-	4	2.0		90	850//+5
	8	TE5210	6	3.75	60	10.0	80	12.5	5	2.0	100	850//+5
	2	TE5220	3	6.50	15	20.0	-	2	1.0		50	1300//+2
	4	TE5230	3	6.50	30	22.5	-	3	2.0		70	1400//0
	6	TE5240	6	6.50	60	22.5	-	4	2.0		90	1400//0
	8	TE5250	6	6.50	60	17.5	80	22.5	4	2.0	100	1400//0
	2	TE5260	3	7.50	15	25.0	-	2	1.0		50	1500//0
	4	TE5270	3	7.50	30	25.0	-	3	2.0		70	1600//0
	6	TE5280	6	7.50	60	25.0	-	4	2.0		90	1600//0
	8	TE5290	6	7.50	60	20.0	80	25.0	4	2.0	100	1600//0
	2	TE5300	3	15.0	15	50.0	-	2	1.0		45	3000//0
	4	TE5310	3	15.0	30	45.0	-	3	2.0		60	3000// -1
	6	TE5320	6	15.0	60	45.0	-	3	2.0		90	3000// -1
	8	TE5330	6	15.0	60	33.0	80	45.0	4	2.0	100	3000// -1


45.0 MHz	NO.	TEMEX	MODE	PASSBAND		STOPBAND		LOSS	RIPPLE		ULT. REJ.	TERM.(Rp//Cp)
	POLES	P/N		dB	±KHz	dB	±KHz	dB	dB-MAX	dB-MIN.		OHM/PF
	2	TE9420	3-OT	3	3.75	18	16.0	3	1		40	2000// -1.0
	4	TE9310	3-OT	3	3.75	30	12.5	3	1		70	2000// -1.0
	2	TE7420	3-OT	3	7.50	18	28.0	2	1		40	3000// -1.0
	4	TE7430	3-OT	3	7.50	40	31.0	3	1		70	3000// -1.0
	2	TE7440	3-OT	3	15.0	15	47.0	2	1		40	8000// -1.5
	4	TE7450	3-OT	3	15.0	30	50.0	3	1		70	8000// -1.5
	2	TE7730	FUND	3	15.0	15	50.0	2	1		40	1100//+1.5
	4	TE7740	FUND	3	15.0	40	60.0	3	1		70	800//+1.0

3030 W. Deer Valley Rd. Phoenix AZ. 85027
 (602) 780-1995 FAX (602) 780-2431

**We deliver great
performance,
by any measure!**

CRYSTALS

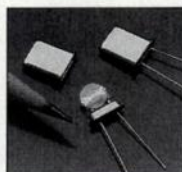- High Frequency fundamental crystals up to 155.52 MHz for oscillator or filter applications.



- Standard AT cut crystals and blanks, fundamental or overtone.

- Rugged, tight tolerance motional parameters.

- Low Frequencies (1 KHz to 1 MHz).



OSCILLATORS

For applications in telecommunications, instrumentation and RF/microwave.

- OCXO's including miniature oscillators for high stability applications, i.e., Telecom Stratum 3 and 3E.

- VCXO's: 14 & 24 PIN DIL packages, discrete packages.

- Special frequency clock oscillators, 14 pin DIL package.

- TCXO's: 14 PIN DIL packages and discrete packages, special applications.

CRYSTAL FILTERS

- From 1 KHz to 155 MHz fundamentals.

- 155 MHz and up utilizing overtone crystals.

HERMETIC SEAL PACKAGING

- Glass to metal sealed crystal bases, TO-styles, terminals, headers, tub plug-ins and microwave power packs.

- Relay headers for sealed relays.

- Battery terminals.

- In-house machining and plating facilities.

For more information on our products or a catalog, call us at 717-243-5929 or FAX 717-243-0079. In Canada call: BIRDE Marketing Inc. at 905-477-7722.

REEVES-HOFFMAN
DIVISION DYNAMICS CORPORATION OF AMERICA
400 W. NORTH STREET • CARLISLE, PA 17013

**ERROR FREE!
ON TIME! EVERY TIME!**

RF calendar

September

20-22

17th Annual Piezoelectric Devices Conference

Kansas City, MO
Information: Components Group, Electronic Industries Association, 2500 Wilson Boulevard, Arlington, VA 22201-3834. Tel: (703) 907-7500. Fax: (703) 907-7501.

26-28

Sixth International Conference on Radio Receivers and Associated Systems

University of Bath, UK
Information: RRAS'95 Secretariat, IEE Conference Services, Savoy Place, London WC2R 0BL UK. Tel: +44 (0) 71 344 5477. Fax: +44 (0) 71 497 3633.

27-29

6th IEEE International Symposium on Personal, Indoor and Mobile Communications

Toronto, Canada
Information: University of Toronto, Dept. of Electrical and Computer Engineering, 10 Kings College Rd., Toronto, Ontario M5S 1A4, Canada; Tel: (416) 978-3652.

October

3-11

TELECOM 95

Geneva, Switzerland
Information: International Telecommunication Union, Place des Nations, CH-1211 Geneva 20, Switzerland. Tel: 41 22 730 5111. Fax: 41 22 733 7256.

8-11

1995 Wireless Circuits, Interconnection, and Assembly Workshop

Tucson, AZ
Information: Wireless Workshop, 100 S. Roosevelt Avenue, Chandler, AZ 85226. Tel: (602) 961-1382. Fax: (602) 961-4533.

22-26

ISHM International Symposium on Microelectronics

Los Angeles, CA
Information: ISHM, 1850 Centennial Park Dr., Suite 105, Reston, VA 22091. Tel: (800) 535-4746 or (703) 758-1060, Fax: (703) 758-1066, email: ISHM@aol.com.

November

30-1

45th Conference, Automated RF Techniques Group

Scottsdale, AZ
Information: Harmon W. Banning, W.L. Gore & Assoc., 1901 Barksdale Road, Newark, DE 19711. Tel: (302) 368-3700, Fax: (302) 292-4607

January

17-19

RF Design Seminar Series

Dallas, Texas
Information: Argus Trade Shows, 6151 Powers Ferry Road, N.W., Atlanta, GA 30339. Tel: (800) 828-0420.

Now to
3.2 GHz
clean, fast
switching.

Split Personality

To ENGINEERS,
we are the
performance-price leader




To OEMs,
we are the ultimate
in reliability.

The Standard for Performance

For over fifteen years engineers and OEMs alike have relied on PTS frequency synthesizers for unmatched stability, speed and spectral purity. These direct analog and direct digital synthesizers meet the most challenging systems development requirements... ATE systems, satcom, wireless, medical imaging, secure communications, and more. You'll also find them in production environments, where they play a key role in quality assurance.

Our synthesizer models cover the 100 KHz to 1 GHz band with 0.1 Hz

Free offer
while supplies
last

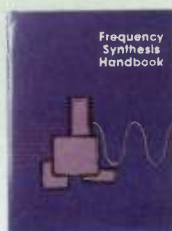

resolution. They are available with switching times from 1 μ sec, spurious outputs as low as -75 dBc and outstanding phase noise characteristics (SSB phase noise at 1GHz, 1 KHz offset, -110 dBc/Hz).

The Standard for Reliability

PTS synthesizers were designed from the outset to deliver the best reliability in the business. We adhere to conservative derating practices, keep power consumption and internal heat buildup to an absolute minimum and subject finished systems to rigorous temperature cycling and electrical testing. The result: a field-proven 25,000 hr MTBF. Since 1985 we've offered a full 2 year warranty and a flat-rate repair fee of just \$350 for years 3 through 10.

It's time you had the best of both worlds. The best performance-price and the best reliability. Call today for

more information and we'll also send you a free copy of the RF Design Frequency Synthesis Handbook.

Features and Options

- BCD or GPIB remote control
- DDS with phase-continuous switching
- OCXO, TCXO or external frequency standard
- Resolution to 0.1 Hz
- Digital phase rotation
- Output power to +13dBm
- Proven 25,000 hr MTBF
- 2 yr warranty
- \$350 repair fee, yrs 3 - 10 (\$500, Model PTS 1000)

PTS

PROGRAMMED TEST SOURCES, INC.
9 Beaver Brook Road, Littleton, MA 01460
Tel: 508 486-3008 Fax: 508 486-4495

INFO/CARD 16

I&Q MODULATORS



DEMODULATORS

1.15MHz to 1880MHz from \$19.95


I&Q Modulators and Demodulators . . . another smart offering from MiniCircuits that's pushing industry standards to new heights (and prices to new lows)!

Infuse your cellular, radar and communication system project with the powerful new I&Q Modulator and Demodulator, surface mount and plug-in units. Units so reliable, the specified statistical data on performance holds up with rock-solid repeatability unit-to-unit.


For high speed assembly operations, I&Q Modulators and Demodulators are available in tape and reel format, so you can bank on consistent assembly performance for production efficiency time after time . . . and with prices starting at just \$19.95, these powerful and compact units truly are the next generation of value on the market today.

So, call your Mini-Circuits distribution center at a number listed below for guaranteed one week shipment or, turn to our applications department with your special specs for custom units at catalog prices.

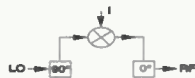We're redefining what VALUE is all about!



MODEL	FREQ. (MHz)		CONV. LOSS (dB)	CARRIER REJ. (-dBc) Typ.	SIDE BAND REJ. (-dBc) Typ.	HARM. SUPPRESS (-dBc) Typ.		PRICE \$ Qty. (1-9)
	f_L	f_U	x	σ		3rd/Q	5th/Q	
MIQA-10M	9	11	5.8	0.20	41	58	68	49.95
MIQA-21M	20	23	6.2	0.14	50	48	65	39.95
MIQA-70M	66	73	6.2	0.10	38	48	58	39.95
MIQA-70ML	66	73	5.7	0.10	38	48	58	49.95
MIQA-91M	86	95	5.5	0.10	38	48	58	49.95
MIQA-100M	95	105	5.5	0.10	38	48	58	49.95
MIQA-108M	103	113	5.5	0.10	38	48	58	49.95
MIQA-195M	185	205	5.6	0.10	38	48	58	49.95
Surface Mount Models								
MIQY-70M	67	73	5.8	0.20	40	47	60	19.95
MIQY-140M	137	143	5.8	0.20	34	45	60	19.95
JCIQ-88M	52	88	5.6	0.1	40	45	65	49.95
JCIQ-176M	104	176	5.6	0.1	35	45	65	54.95

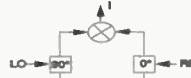

MODEL	FREQ. (MHz)		CONV. LOSS (dB)	AMP. UNBAL. (dB) Typ.	PHASE UNBAL. (Deg.) Typ.	HARM. SUPPRESS (-dBc) Typ.		PRICE \$ Qty. (1-9)
	f_L	f_U	x	σ		3rd/Q	5th/Q	
MIQA-10D	9	11	6.0	0.10	0.15	50	65	49.95
MIQA-21D	20	23	6.1	0.15	0.15	64	67	49.95
MIQA-70D	66	73	6.2	0.10	0.15	56	58	49.95
MIQC-38D	34	38	5.5	0.10	0.10	60	65	49.95
MIQC-60WD	20	60	5.3	0.10	0.15	55	67	79.95
MIQC-895D	868	895	8.0	0.20	0.15	40	55	99.95
MIQY-1.25D	1.15	1.35	5.0	0.0	0.15	59	67	29.95
MIQY-70D	67	73	5.5	0.25	0.10	52	66	19.95
MIQY-140D	137	143	5.5	0.25	0.10	47	70	19.95
Surface Mount Models								
JCIQ-176D	104	176	5.5	0.1	0.15	52	65	54.95
JCIQ-895D	868	895	8.6	0.1	0.2	45	65	99.95
JCIQ-1785D	1710	1785	8	0.2	0.2	50	65	99.95
JCIQ-1880D	1805	1880	8	0.2	0.2	50	65	99.95

☐ NON-HERMETICALLY SEALED

MIQA case .4 x .8 x .4 in. MIQC case .8 x .8 x .4 in.
MIQY case .8 x .8 x .4 in. JCIQ case .9 x .8 x .25 in.

All Models Available in New J-LEAD Surface Mount Package. Consult Factory for Details.



Mini-Circuits®

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661

For detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER • MICROWAVE PRODUCT DATA DIRECTORY • EEM • MINI-CIRCUITS' 740- pg. HANDBOOK.

CUSTOM PRODUCT NEEDS...Let Our Experience Work For You.

F 156 Rev C

INFO/CARD 17



FAA, E-Systems Demonstrate GPS-Based Landing System

E-Systems reports that it has successfully completed a series of flight tests at NASA's Crows Landing facility showing that the Global Positioning System (GPS), combined with Kinematic Carrier Phase Tracking (KCPT) technology, is a potential replacement for the existing Instrument Landing System (ILS) for aircraft. The FAA is expected to have a final analysis and report on the flight data by late summer. The avionics equipment included a modified GPS receiver with KCPT software, an E-Systems D8PSK VHF data link transceiver, a Pentium-based processor, and a Litton IRU for attitude data. Software on a 486-based computer calculated the improved GPS position and ILS-like guidance at a 15 Hz update rate. The ground system consisted of a ground reference station (GRS) and an independent ground integrity monitor (GIM). The ground-based GPS receiver was integrated with the GRS to provide pseudorange and carrier phase information which was then uplinked to the approaching aircraft using the D8PSK link. The system achieved accuracies of 0.31 meter vertical and 1.6 meters laterally, well within the requirement of 1.2 meters and 4 meters, respectively.

BIS Reports Increase in European Consumer Spending

BIS Strategic Decisions reports a predicted growth in home entertainment in Western Europe to \$33 billion through the end of 1995, a nine percent increase over 1994. Interactive multimedia, continued sales of CDs, pay TV and interactive TV play a major role in the increase, according to BIS, who is sponsoring their Third Annual Interactive Conference in Montreaux, Switzerland, September 26-28, 1995. Information on the conference can be obtained from BIS' U.K. office at: +44 1582 405678.

SETI League Relocates

The SETI League, Inc., a non-profit leader in a scientific Search to Extra-Terrestrial Intelligence has moved to new quarters at 433 Liberty Street, Little Ferry, NJ 07643. Offices, labora-

tory and a SETI library have been provided at no cost to membership through the generosity of building occupants Eventide Inc., a longtime supporter of SETI. Since Congress terminated all NASA funding for SETI in 1993, private organizations have attempted to continue experiments. The SETI League, Inc. maintains a membership hotline at (800) TAU-SETI. Dr. H. Paul Shuch is full-time Executive Director of the SETI League, on a one-year leave of absence from the Pennsylvania State University system.

Magnetic Materials Scholarships Offered

The Magnetic Materials Producers Association (MMPA) announces that applications are now being accepted for the Association's Scholars Program. Two \$5000 awards will be made to individuals doing graduate level studies in the field of magnetics. The purpose of the program is to encourage students entering graduate school to pursue a concentration in the area of magnetics. Written applications should be submitted to the MMPA by

Conference News

RF Design Seminar Series Expands Educational Program

RF Design magazine announces the new RF Design Seminar Series, with three educational conferences planned in 1996. The program of short courses and technical papers will expand on the educational program developed for the RF Expo trade shows. Three tracks of formal instruction will offer RF design fundamentals, specific design techniques, and advanced instruction. A one-day technical papers program will allow engineers to present recent work, and a late afternoon poster session will be combined with a social reception for informal technical discussions. The first seminar will be held in late January in Dallas, Texas. The second will be held in conjunction with the International Wireless Communications Expo in Las Vegas in April, and the third is being planned for early fall 1996 in

Boston, Mass. Engineers interested in presenting papers should contact *RF Design* magazine at 6300 S. Syracuse Way, Suite 650, Englewood, CO 80111. Persons wishing to receive more information on the seminars may contact Argus Trade Shows at (800) 828-0420.

Call for Papers — Multichip Modules

The Fifth International Conference on Multichip Modules has issued a call for papers. Topics sought include MCM applications, testing, assembly and interconnection, MCM/PCB interface, management and cost strategies, electrical the thermal performance, telephone and cellular applications. 150-word abstracts should be prepared by October 16, 1995 and submitted to MCM '96 Conference Services, ISHM, 1850 Centennial Park Drive, Suite 105, Reston, VA 22091; Tel: (703) 758-1060, Fax: (703) 758-1066.


October 16, 1995. Awards will be announced by February 15, 1996. For information, contact the MMPA at 11 South LaSalle Street, Suite 100, Chicago, IL 60603; tel: (312) 201-0101, fax: (312) 201-0214.

Colorado Scientists Achieve Bose-Einstein Condensation

Researchers at JILA, a joint program of the National Institute of Standards and Technology and the University of Colorado at Boulder, have announced that they achieved a temperature far lower than any previously produced, creating an entirely new state of matter predicted 70 years ago by Albert Einstein and Satyendra Nath Bose. The team cooled rubidium atoms to 170 nanokelvin (billionths of a degree Celsius) above absolute zero, where individual atoms condensed into a "superatom" that behaved as a single entity. The scientists further cooled the atoms to 20 nanokelvin above absolute zero, the lowest temperature ever achieved. Physicists worldwide have been searching for 15 years to achieve this condensation.

Advanced Power Technology Introduces

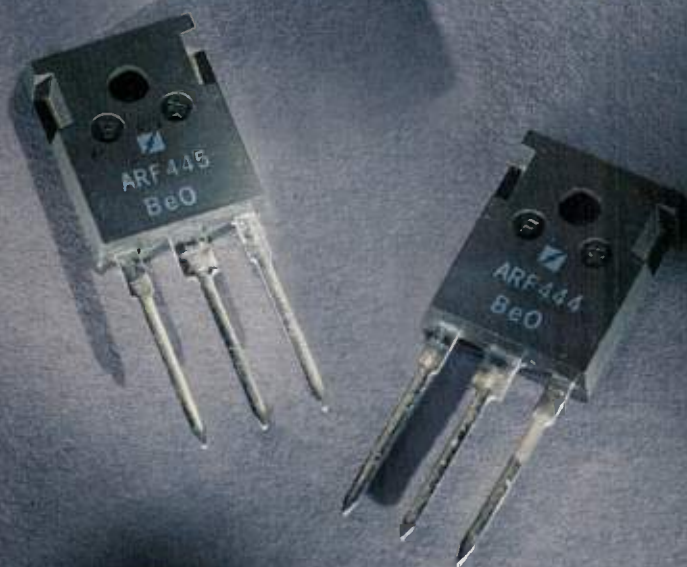Low Cost 300 Watt, 300 Volt RF Power Devices for 13.56 MHz.



Low Cost Quantity Pricing
ONLY \$40
300 Watt Device

With Advanced Power Technology's ARF444 and ARF445 RF components in your 13.56 MHz RF amplifier, you'll immediately notice the combination of high voltage operation, high gain and 80% efficiency. Combine that performance with component costs that allow for multi-kilowatt, 13.56 MHz amplifiers to be built for less \$0.25 per watt. Experience the first real break through in commercial HF, RF power technology in over a decade. Use APT's low-cost 300 Watt, 300 Volt RF devices.

For APT's new application notes, contact Richardson Electronics. You may also refer to

Richardson's Internet address (<http://www.rell.com>) for APT's application notes. As an authorized distributor for APT's products, Richardson offers the newest APT products from stock with the technical assistance to support your application.

Featuring:

- Quantity Pricing \$40
- Symmetric Pair
- 300 Watts
- 13.56 MHz
- 300 Vdc
- 80% Efficiency
- TO-247 Plastic (Common Source) Package

To Receive a
copy of the
application
notes please
fax, call or
circle this
inquiry number.



**Richardson
Electronics, Ltd.**

(800) RF POWER in the U.S.

More than 50 locations worldwide to serve you - U.S. Toll Free: (800) RF POWER/(800) 737-6937, Canada Toll Free: (800) 348-5580; Internet: <http://www.rell.com>, France: (1) 34.26.4000, Germany: Puchheim (089) 800 21 3-1, Hamburg (040) 555 88 4-0, Italy: Sesto Fiorentino (FI) (055) 420.10.30, Milano (02) 331.04.220, Rome (06) 417.33.751, Scandinavia: Sweden (0) 18 386900, Spain: Madrid (1) 528 37 00, Barcelona (3) 415 83 03, United Kingdom: Lincoln (01522) 542631, Slough (01753) 733010, Japan: (3) 3874-9933, Singapore: (65) 744-2128, Taiwan: 886-2-7269256, European Corporate Headquarters: Netherlands 020-6919148, Fax 020-6919378, U.S. Corporate Headquarters: LaFox, IL (708) 208-2200, Fax (708) 208-2550.



**ADVANCED
POWER
TECHNOLOGY®**

Business Briefs

KVG and MORION Join Forces — KVG announces completion of a cooperation agreement with MORION of St. Petersburg, Russia and Staudte Engineering of Cedar City, Utah. MORION, a privatized crystal and oscillator company, is majority owned by KVG and Staudte and specializes in high performance oscillators.

BCP Awarded Encoding Patent — Broadband Communications Products, Inc. has been awarded a U.S. patent for a pre-scramble encoding method and device for digital communication. The purpose of the invention is to ensure that a scrambled data transmission has adequate signal balance and frequent data transitions, maintaining proper randomness.

Stanford Telecom Joins Cable Group — Stanford Telecommunications has announced that it has joined the Cable/Information Technology Convergence Forum, an organization sponsored by Cable Television Laboratories, Inc. (CableLabs). The Forum was created to smooth the exchange of information between high technology companies and cable operators.

TAS in Joint Effort with AT&T Paradyne — Telecom Analysis Systems (TAS) and AT&T Paradyne have initiated a joint effort to develop a new standard for testing cellular modem products. The target is a set of laboratory-based testing procedures that can be used in conjunction with field tests to ensure modem quality. TAS recently introduced GT-Cellular test system is being used as the laboratory test bed for cellular modem evaluation.

Harris Opens Singapore Center — A new Center of Excellence is announced by Harris Corporation, located in the Cencon 1 Building in Singapore. The facility combines functions serving the Asian market, including field engineering, technical support, staff specialists, plus marketing and sales.

BTG Licenses Technology to E.F. Johnson — BTG USA Inc. has licensed its narrowband linear modulation technology to E.F. Johnson Company. The modulation technique, called transparent-tone-in-band (TTIB), can significantly increase the capacity of mobile communications systems. E.F. Johnson will use the technology in products for the 220 MHz band.

Scientific-Atlanta Gets IRIDIUM Contract — Motorola's Satellite Communications Division has placed an order for four additional System Control Segment earth terminals for the IRIDIUM system. With this order, fourteen telemetry and command terminals are being produced by Scientific-Atlanta.

Watkins-Johnson International Moves — Watkins-Johnson International has moved to new offices in Windsor, England. The new address is: St. Leonards House, St. Leonards Road, Windsor, Berkshire SL4 3DG, U.K.; Tel: +44 1753 751300; Fax: +44 1753 621794.

Lasertron Forms Wireless Business Unit — Lasertron has formed a new Wireless Business Unit as a separate division to meet requirements of the cellular and PCS markets for fiber-optic subsystem products, primarily for linking remote antennas with base station equipment.

Rogers Opens Hong Kong Office — Rogers Corporation has established a regional subsidiary, Rogers Southeast Asia, in Hong Kong. The office supports growing activity for Rogers and Durel Corporation in Southeast Asia, providing sales and technical support.

Applied Signal Technology has New Address — Although the company has not moved, the address for Applied Signal Technology, Inc. has been changed. Their mailing address is 400 West California Avenue, Sunnyvale, CA 94086, and the shipping address has become 600 West California Avenue.

Contracts

Anritsu Wiltron Gets Marine Corps Order — Anritsu Wiltron announces a \$3 Million order from the Marine Corps for the 68347M 20 GHz Synthesized Signal Generator. This order is a follow-on to an initial \$2 Million order placed in August 1993, and is part of a five-year contract.

Svetlana Receives British Defence Contract — Svetlana Electron Devices, Inc., the American joint venture partner with Svetlana Electron Devices of St. Petersburg, Russia, announces a major contract for more than 10,000 power electron tubes from the British Ministry of Defence. The power tubes will be used in military shipboard radio equipment. The contract was won in competition with manufacturers in the U.S., France and China.

RFID Runs Underground Traffic System — The Huogito Coal Mine in China has installed a traffic monitoring and control system using Texas Instruments' TIRIS RFID hardware. The underground mine uses operator-driven vehicles rather than the usual rail car system, and the traffic control system helps reduce collisions and traffic jams. The system also tracks each vehicle's location, allowing dispatchers to control their movement efficiently.

W-J Receives \$16M AMRAAM Contract — Watkins-Johnson Company announces a contract for more than \$16 Million from Hughes Aircraft Company, Missile Systems Group. Under the contract, W-J will continue production of electronics subsystems for Lot 9 of the AIM-120 AMRAAM air-to-air missile.

ManTech Gets Test Contract — ManTech Test System has been issued a four-year GSA contract for their family of Aurora test systems, models VTS-1000/7, VTS-1000/39, VTS-1000/99, VTS-2000 and VTS-3000. The systems are used by the Department of Defense, other government agencies and commercial customers for the test and repair of digital, hybrid and RF electronic circuit boards and black boxes. The VTS-1000/7 has been certified as the replacement for the Gen-Rad 2225/2235 (AN/USM-465) system.

The World's Smallest Crystals And Oscillators Just Became Easier To Find.



Look no further, call Richardson Electronics.

Richardson is proud to be the exclusive distributor for the world's smallest SMD and thru-hole crystals (10kHz-32 MHz) and oscillators (0.01-125MHz) from Micro Crystal.

Richardson offers design assistance, technical support and superior service to Micro Crystal customers world-wide.

**Call: 1-800-RFPOWER (in U.S.)
1-800-348-5580 (in Canada)**



Richardson Electronics, Ltd.

Labs Focus on Commercial Applications

By Andy Kellett
Technical Editor

Electromagnetic fields have been fundamentally understood since 1864, when James Clerk Maxwell unified the equations describing the behavior of electric and magnetic fields. However, more than Maxwell's equations are required to produce the advanced communications devices being built today, and researchers are working on developing new devices and new types of systems to exploit the fields Maxwell described in the 19th century.

Semiconductor Devices

Much of the attention given to advances in RF technology is given to new semiconductor devices. Most of the research being done on new RF semiconductors is being done in commercial labs. Most semiconductor device manufacturers are working on ways to make devices that operate at lower voltages, use less power, and incorporate more functionality.

However, some recent advances have their roots in more "pure research" labs. Dr. Bernard Meyerson, leading a team at the IBM Thomas J. Watson Research Center, developed a new semiconductor process that uses a Si/Ge alloy to produce very fast devices. Not only are the devices fabricated in this process fast, they can be manufactured using essentially the same fab lines being used to make silicon circuits. This technology made the leap to the commercial area in the form of a 1 GHz, 12-bit D-to-A converter designed by Analog Devices and fabricated by IBM.

Superconductors

High temperature superconductors garnered a lot of attention when they appeared on the scene in 1987. Since then, commercial products using this technology have been trickling out of the labs and into the market. An example of one of the emerging super-

conducting devices are the very sharp, low loss cellular basestation filters developed by Conductus, Inc.

Most of the research done by Conductus has focused on ways to make fabrication of superconducting devices as predictable and routine as the fabrication of semiconductor devices. "A lot of the work is centered on trying to really understand the correlations between material growth characteristics and material properties, and between material properties and device properties," says Randy Simon, Vice President of Technology Programs for Conductus, "Eventually we would like to control material growth parameters so as to produce ideal device parameters and basically not even have to worry about the material's parameters."

However, work on filter design is also being done. "We are working at the problem from both directions," says Simon, "designing devices so they are more tolerant of variations in material properties, and improving materials so that the devices are less constrained."

Electromagnetic Modeling

Both the materials and geometries used to package RF devices are the subject of research. Reducing package cost and device degradation are the goals of this research.

Refining device geometries to optimize performance requires electromagnetic modeling. Many researchers are working to make electromagnetic modeling algorithms faster and device and material models more accurate. This type of research is particularly attractive to smaller universities, where the cost of cutting edge semiconductor fabrication equipment is out of reach, but a fast powerful computer can be purchased for a small fraction of an annual budget.

System Research

Not all RF research is concerned with devices. Predicting the behavior of RF communications systems and finding ways to make them more reliable is also getting research attention. Not only are service providers doing this kind of research, but there is plenty of this kind of research being done at universities. Members of the Mobile & Portable Radio Research Group at Virginia Tech have done work in propagation prediction, wireless communications simulation and other areas important to system operation.

Lincoln Laboratories is working on ground terminals for military communication systems, says Roger Sudbury, Executive Officer and Director of External Affairs for Lincoln Labs. While this is not a commercial project, "... a lot of things that the Laboratory has done for the Department of Defense ultimately find themselves in commercial applications," says Sudbury.

Laboratory Funding Trends

Whether they produce technology that ultimately becomes commercial or not, many DOD-funded labs have been pared back in recent years. According to Lincoln Labs' Sudbury, funding for Lincoln Labs has shrunk by about 30 percent in the last five years, and in the same time, the number of people employed at the lab has shrunk from just over 2,800 to about 2,250.

Research groups with weaker ties to DOD funds, such as the Georgia Tech Research Institute, have been able to partially replace lost funds.

Finally, the companies producing devices for the new wireless communications services are investing a lot of money in their R&D departments. If those departments are successful in crafting devices and systems that the marketplace finds useful, they may also share in the return on investment. **RF**

FILTERS

low pass, high pass, bandpass dc-3GHz from \$11⁴⁵

- less than 1dB insertion loss • greater than 40dB stopband rejection • surface mount • BNC, Type N, SMA available
- 5-section, 30dB/octave rolloff • VSWR less than 1.7(typ.) • rugged hermetically sealed pin models • constant phase
- meets MIL-STD-202 tests • over 100 off-the-shelf models • immediate delivery



Mini-Circuits®

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661

For detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER • MICROWAVE PRODUCT DATA DIRECTORY • EEM • MINI-CIRCUITS' 740- pg. HANDBOOK.

CUSTOM PRODUCT NEEDS...Let Our Experience Work For You.

F 209 Rev Orig

INFO/CARD 20

SPICE Techniques for Analyzing Quartz Crystal Oscillators

By T. Kien Truong
Boeing Commercial Airplane Group

We can readily find several articles on oscillator analyses published in trade journals but rarely can one find articles on crystal oscillator simulation. In fact, the author knows of no material published on transient simulation. The fact that a quartz crystal is an extremely high Q circuit and the oscillator is free-running with no driving signal makes crystal oscillator simulation difficult. This tutorial introduces new techniques for obtaining the startup transient by inserting power supply noise, and techniques for finding the open-loop response by inserting a pseudo voltage source at the CMOS amplifier input. We will also examine the frequency pulling, resonant and anti-resonant behaviors of the crystal oscillator.

Often in designing ASICs the convenience, controllability, and economy of an embedded crystal oscillator offers a major advantage. Together with the off-chip passive components, the on-chip active circuitry can give a reliable and stable oscillator. In a Pierce oscillator, the on-chip circuitry is an inverting amplifier that provides the gain necessary to build up and maintain the oscillation through a crystal controlled feedback network. In order to oscillate, the circuit must satisfy the Barkhausen criteria that the phase shift around the loop is $n360^\circ$ and the loop gain exceeds unity at the resonant frequency.

Standard SPICE analyses such as transfer function, fourier transform, signal-to-noise plot and closed loop analyses are straight forward, often described in literature and we will not discuss them here. The tutorial will show that we can obtain a wealth of other information such as startup transient, open-loop response and Nyquist plots using the evaluation version of the PSpice simulator from

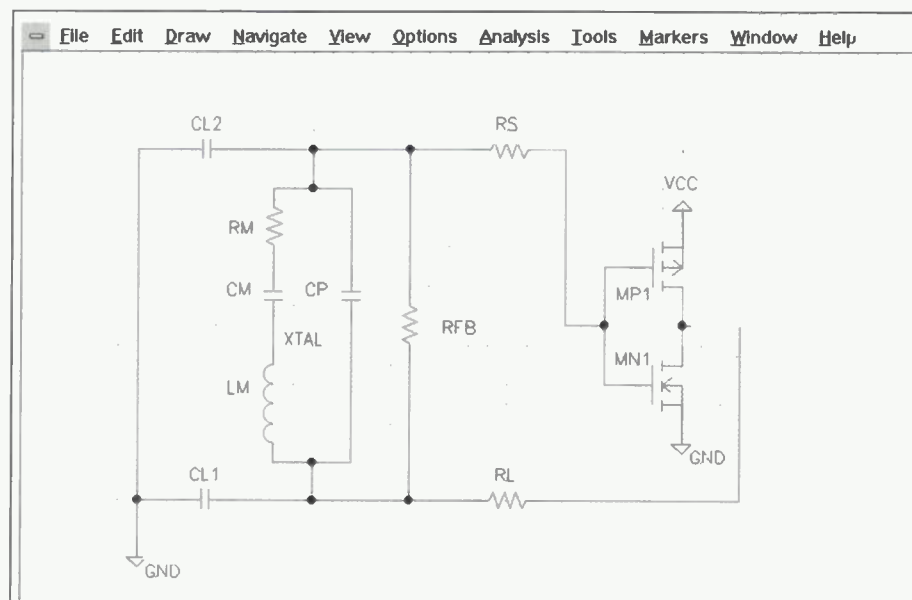


Figure 1. Basic crystal oscillator schematic.

MicroSim. This free version of MicroSim limits the complexity of the design to about 10 transistors, which is enough to simulate our Pierce oscillator circuit. The circuit in this tutorial is a simplified version of the real circuit used in the ASIC. The ASIC circuit includes additional transistors as loading transistors for the gain stage and as high-value feedback resistor for the inverting amplifier. Omitting these elements allows the use of the evaluation software and does not affect the analyses of oscillator behaviors.

This work is part of the design and development of a highly reliable clock ASIC. The ASIC employs redundant oscillators with automatic fault detection, identification and reconfiguration. The digital/analog ASIC was simulated in a mixed mode environment with a full-blown version of SPICE and was successfully fabricated with a

dual-poly NWell CMOS technology.

Circuit Description

We can model the quartz crystal as having a motional resonance arm R_x , L_x and C_x in parallel with the crystal holding capacitance C_p (the mounting electrodes). Most crystal manufacturers can provide the motional parameters. Figure 1 illustrates the Pierce oscillator circuit using a CMOS inverting amplifier and a 24 MHz crystal. All circuit parasitic elements, on-chip or off-chip, are lumped into the bulk capacitors. The on-chip amplifier influences the frequency through its input and output (pin-to-ground) capacitances, and its pin-to-pin capacitance. We can also model the amplifier internal delay as additional output capacitance. Figure 2 shows the circuit listing in PSpice format. The level-2 NMOS and PMOS transistor parameters are from a 2-micron NWell CMOS technology.

The Giga-tronics 8540B is the World's Best Power Meter for Communications Testing. But Don't Take Our Word for It.

“Power meters generally fare well when characterizing simple continuous wave (CW) or pulsed RF/microwave signals. But modern communications signals, with digital information on phase-, frequency-, and amplitude-modulated carriers, pose problems for most power meters. The exception is the 8540B from Giga-tronics. The latest version of this high-speed measurement tool performs true average power measurements even on multitone signals with digital modulation.”

*Microwaves & RF
June 1995*



Call 800-726-GIGA (4442)

or fax 510-328-4700 for more information for a demonstration.

Giga-tronics

Giga-tronics Incorporated ■ 4650 Norris Canyon Road ■ San Ramon, California 94583 ■ Telephone: 800-726-4442 or 510-328-4650 ■ Telefax: 510-328-4700

The amplifier for the crystal oscillator is a high-gain, single-stage CMOS inverter that is biased at its mid range to act as a linear amplifier for the clock signal. The biasing resistor R_f produces a negative feedback signal that competes with the more favorable positive feedback signal through the crystal network. The biasing resistor therefore must be large enough (22 M Ω) not to load down the low impedance crystal

feedback loop and yet is small compared to the CMOS amplifier input impedance. The amplifier provides a nominal 180° phase shift in addition to the 180° phase shift in the feedback loop. The amplifier has to provide enough gain to offset the loss in the feedback loop. Too much gain, however, will facilitate unwanted crystal overtone and spurious effects or even make the oscillator startup unreliable.

```
* Single inverting amplifier
MNI NVOUT NVTN 0 0 NMOS L=2U W=480U
MPI NVOUT NVIN 99 99 PMOS L=2U W=1130U
```

```
* 24 MHz crystal
.SUBCKT XTAL24 1 2
*CP 1 2 4.5E-12
RM24 10.2
CM 3 4 20.937E-15
LM 1 3 2.1E-3
.ENDS
```

```
* Power supply noise to kick start the oscillator
V99 99 0 PWL ON 5V .IUS SV .105US 0V .11US
5V 100MS 5V
```

```
* Feedback circuit
XTAL NXIN NXOUT XTAL24
RL NVOUT NXIN 200
CLI NXTN 0 10PF
CL2 NXOUT 0 10PF
RFB NVOUT NVTN 22E6
RS NXOUT NVIN 200
```

```
* Transient analysis
.TRAN INS 20US 0 10ns
.PROBE
```

```
* N-Well transistor model
.MODEL NMOS NMOS
+ LEVEL=2 VTO=0.825 UO=608.3 TPG=-1
+ TOX=4.0E-8 NSUB=7.755E15 XJ=4.50E-7
+ LD=1.121E-7 DELTA=3.714 VMAX=49.89E+3
+ NFS=.105E12 CJ=323.1E-6 CJSW=929.9E-12
+ MJ=461.5E-3 MJSW=268.3E-3 PB=.44
+ CGSO=96.77E-12 CGDO=96.77E-12
+ CGBO=40.0E-12
+ UCRIT=50E3 UEXP=78.2E-3 NEFF=3.36
```

```
.MODEL PMOS PMOS
+ LEVEL=2 VTO=-0.70 UO=205.1 TPG=-1
+ TOX=4.0E-8 NSUB=1.486E16 XJ=450E-9
+ LD=230.5E-9 DELTA=1.843 VMAX=40.76E3
+ NFS=0.01E12 CJ=804.9E-6 CJSW=749.1E-12
+ MJ=525.0E-3 MJSW=495.4E-3 PB=.958
+ CGSO=199.0E-12 CGDO=199.0E-12
+ CGBO=101.5E-12
+ UCRIT=70E3 UEXP=184.2E-3 NEFF=0.69
```

```
.END
```

Figure 2. Circuit listing for transient analysis.

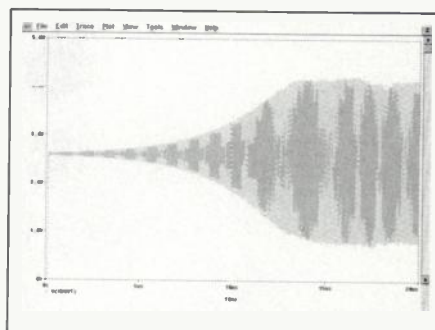


Figure 3. Simulated startup transient waveform.

The crystal in the feedback loop has an extremely sharp phase versus frequency response at the resonant frequency. The series resistor R_L helps set the phase in the feedback loop and also isolate the crystal from the amplifier circuit. R_S and R_L also include the ESD protection resistors in the I/O pads. The bulk capacitors parallel the

Timing is everything!

JUST THE
OSCILLATOR
FOR YOUR
APPLICATION...
IN NO TIME AT ALL!

At Hy-Q, we know what you want... a world-class facility, producing the highest quality product, meeting your exact specifications... all in the most timely delivery schedule possible.

Hy-Q's "D" Series TCXO:

Frequency: 8 MHz. to 30 MHz.

Available Outputs: Clipped Sinewave; TTL; HCMOS

Supply Voltage: 5 vdc

Stability: ± 0.5 ppm 0° to 50°C

± 2.0 ppm -40°C to $+85^\circ\text{C}$

*other stability options available

Various voltage control options available.

Dimensions: Length: 0.8", Width: 0.8", Height: 0.4"

Hy-Q

International (USA), Inc.

1438 Cox Avenue Erlanger, Kentucky 41018

Phone: (606) 283-5000 Fax: (606) 283-0883

```
* Single inverting amplifier
MNI NVOUT NVIN 0 0 NMOS L=2U W=480U
MP1 NVOUT NVIN VCC VCC PMOS L=2U
W=1130U
```

```
* Pseudo voltage source inserted in feedback loop
VPS NVIN 0 DC 2.557 AC 1
```

```
* 24MHz crystal
.SUBCKT XTAL24 1 2
CP 1 2 4.5E-12
RM24 10.2
CM 3 4 20.937E-15
LM 1 3 2.1E-3
.ENDS
```

```
* Feedback circuit
XTAL NXIN NXOUT XTAL24
VC9VCC0DC5V
RL NVOUT NXIN 200
CL1 NXIN 0 10PF
CL2 NXOUT 0 10PF
RFB NVOUT NVIN 22E6
RLD NXOUT 0 1E9
```

```
* Broad band analysis
.AC DEC 1000 1E6 300E6
```

```
* Narrow band analysis for Bode & Nyquist plots
.AC LIN 1000 23.8E6 24.2E6
.PR OBE
```

Figure 4. Circuit listing for open loop analysis.

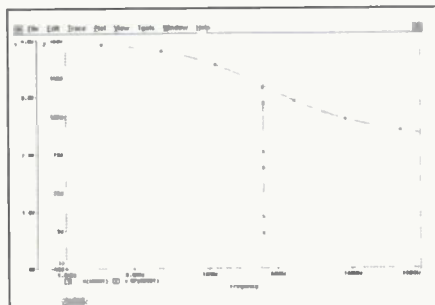


Figure 5. Broadband response.

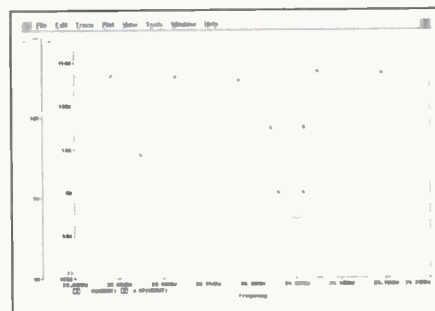


Figure 6. Narrowband response.

internal capacitance of the amplifier and help reduce the effect of amplifier and circuit variation. The feedback loop controls all frequency characteristics. The amplifier influences this frequency only by its gain, bandwidth, and parasitic capacitances, which are added to the load capacitors. We can control the loop gain by sizing the transistors and by selecting the proper

ratio between the crystal load capacitors. Since the crystal inductance varies by a wide range near resonance, the exact value of the load capacitors are not critical. They just have to be small (less than 30 pF in a typical circuit) so as not to load down the crystal.


The crystal in this parallel resonant circuit operates in the inductive region between the resonant and anti-resonant frequencies (the crystal band-

width). Outside this narrow frequency range the crystal looks like a small capacitor (C_p) electrically. Within this bandwidth, the crystal phase varies by a large range with very small change in frequency. In other words, extremely small frequency shift is necessary to change the crystal's impedance to compensate for phase deviation around the loop. The frequency pulling characteristic of the crystal is such that

HCMOS/TTL & Sinewave • Surface Mount & Thru-Hole

**WE'VE GOT A LOT
TO SAY ABOUT
TCXOs...**

**BUT THIS
AD HAS
LIMITED
BANDWIDTH.**

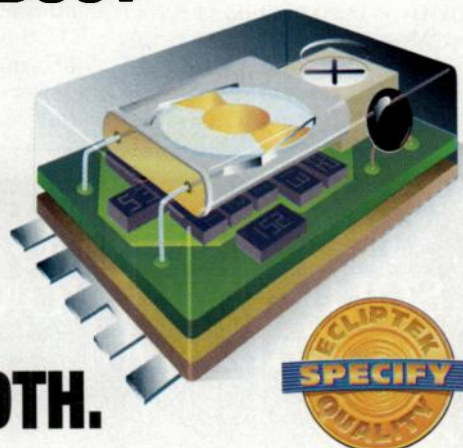

When it comes to TCXOs, you've got more options now than ever before. Logic. Packaging. Frequency stability. Temperature range.

We'd like to tell you everything you need to know, but there's not enough room here. Design specs. Quality stats. Availability. Pricing. You've got questions. We've got answers. If you're wired to the Internet, come visit our web site or **e-mail any questions to ecliptek-sales@ecliptek.com**

If you like the human touch, our customer support team has all the bandwidth you'll ever need. They're knowledgeable, responsive, flexible and reliable. Committed to making Ecliptek your TCXO supplier.

Dial 1-800-ECLIPTEK for accurate answers, guaranteed quality and on-time delivery. Data sheets available 24-hours by fax-on-demand.



1-800-ECLIPTEK • (714) 433-1200 • (714) 433-1234 Fax

<http://www.ecliptek.com/ecliptek/>

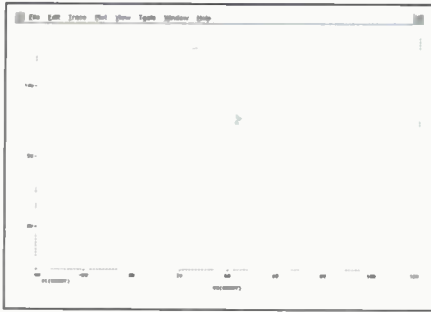


Figure 7. Nyquist plot of open loop response.

additional phase variation incurred in the circuit can be tolerated and is translated into a small frequency shift.

Startup Transient

Transient simulation of extremely high-Q quartz crystal circuits is a real challenge. Most designers rely on the frequency responses (small signal analysis) to judge the ability of their circuits to oscillate. Transient

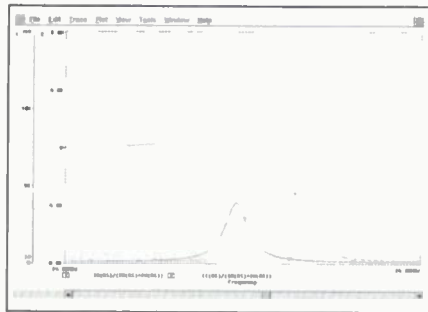


Figure 9. Frequency pulling.

response uses large signal analysis which involves nonlinearity operation, truncation errors and time step estimation which often results in divergence. However, a few tricks can make the oscillation waveform come alive. Figure 3 shows the transient response for the oscillator startup. Here the command, V99 99 0 PWL 0NS 5V .1US 5V .105US 0V .11US 5V 100MS 5V, introduces a voltage spike to the power supply to kick start the oscillator. Note that in a real circuit, oscilla-

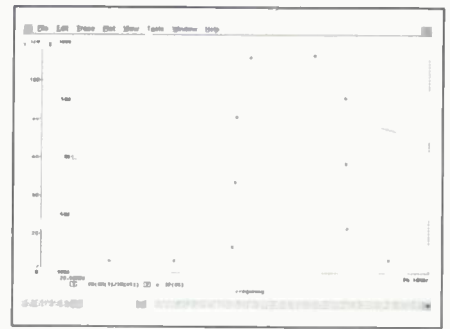


Figure 10 Crystal impedance.

tion is started by random thermal noise in the circuit elements. This noise is amplified by the inverter and is positively fed back through the crystal circuit. The amplitude of the signal increases exponentially as it goes through the loop again and again until saturation is reached. The frequency of the signal is controlled by the crystal. The crystal acts as a narrow band filter that passes only the resonant frequency. We should limit the fourth parameter of the .TRAN command

THE NEW TCXO SOLUTIONS FROM RALTRON.



TX2100/TX2146

- Small size
- Wide temperature range
- +5 VDC, +12 VDC
- Wide frequency range
- Voltage control option
- Custom options
- Lower cost

FREQUENCY STABILITY:

100: -30° C to +70°C: ±1ppm
146: -40° C to +85°C: ±1ppm

DIMENSIONS: 100 146

Length	.8"	1.5"
Width	.8"	1.5"
Height	.4"	.5"

RALTRON

ELECTRONICS CORP.

2315 NW 107 AVENUE
MIAMI, FLORIDA 33172 U.S.A.
FAX (305) 594-3973
(305) 593-6033

ONLY RALTRON HAS IT ALL

Crystals / Crystal Oscillators
Crystal Filters / Ceramic Resonators



LAP-TECH INC.

FREQUENCY CONTROL PRODUCTS

- **QUARTZ CRYSTALS 2 - 250 Mhz**
Precision glass encapsulation
Cold Weld and Resistance weld holders
Leaded and surface mount styles
Standard and custom design
- **CLOCK OSCILLATORS 0.25 - 170 Mhz**
TTL, HCMOS AND ECL
Hermetic packages with through hole and surface mount configurations
- **EMERGENCY SERVICE DELIVERY**
- **QUALITY**
ISO 9002 pending


LAP-TECH Inc.
230 SIMPSON AVE.
BOWMANVILLE, ONTARIO
CANADA L1C 2J3

TEL: 905-623-4101
FAX: 905-623-3886

INFO/CARD 26

INFO/CARD 25

spread spectrum voice & data connection

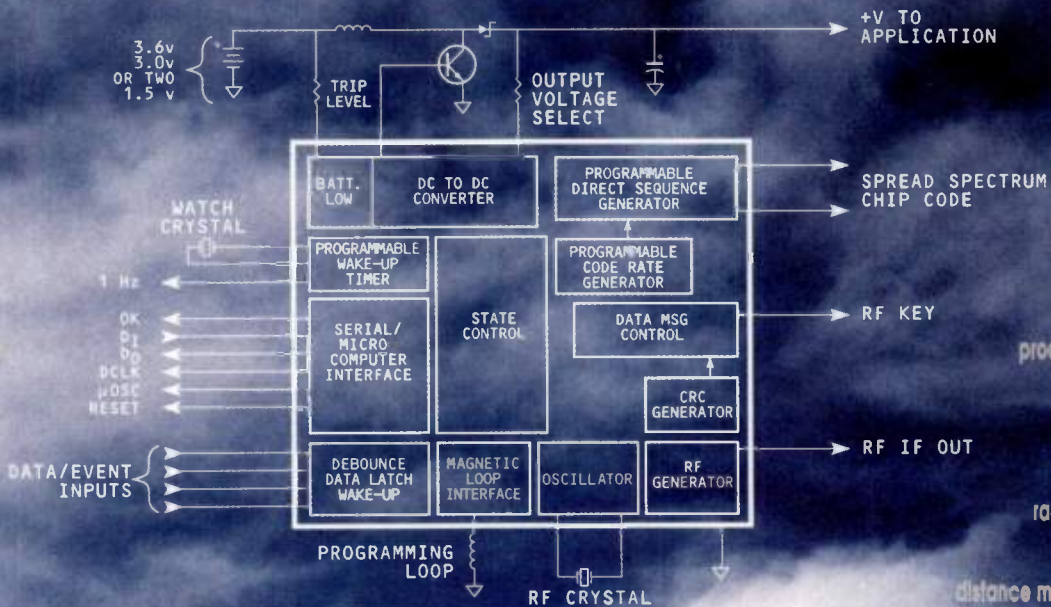

single battery operation

no fee license

data rates up to 300Kb/s

Six years in development, our new
AX-602 SPREAD SPECTRUM core IC*
can send information across offices,
through buildings, and up to 30 miles outdoors.



the innovator in low-cost spread spectrum communication

101 West Robert E. Lee Blvd., New Orleans, LA 70124

504-282-8119

* \$2.75 in volume. Patented custom product design. Licensing required.

INFO/CARD 24

Feedback Analysis

VIN IN 0 AC 1

RS IN 1 100
RM 1 11 10.2
LM 11 12 2.1E-3
CM 12 13 20.937E-15
CP 1 13 4.5E-12
CT 1 0 CMOD 1
CL 13 0 10E-12
RL 13 0 1E9

.MODEL CMOD CAP(C=10PF)
.STEP CAP CMOD(C) 10PF, 20PF, 5PF

.AC LIN 1000 24.01E6 24.04E6
.PROBE

* Plotting xtal reactance (imaginary part)
* -II(RS) / (IM(RS)*IM(RS))
* Plotting xtal resistance (real part)
* IR(RS) / (IM(RS)*IM(RS))

.END

Figure 8. Circuit listing for feedback impedance.

(the maximum stepping time) to one-fourth of the oscillator period. This parameter would prevent the internal step of PSpice to overshoot the oscillator period and results in divergence. To avoid aliasing, we will choose the print interval at 1 ns.

The crystal mounting capacitance C_P also plays an important role in realizing the transient simulation. C_P is in parallel with the motional arm of the crystal and diverts the energy going through the crystal. This reduces loop gain greatly and makes startup much slower. For a typical 24 MHz crystal C_P is about 4.5 pF.

A 40 μ s simulation would take about ten minutes on an 486 based personal computer. Examining the transient waveform would reveal a straight line, i.e. no oscillation. Zooming in the signal would reveal a very small (0.01 V) sine wave that does not grow exponentially as expected. As it turned out, at least 200 μ s simulation time is needed to see the startup waveform. However, we would have to suppress the first 160 μ s of data because the data buffer will be full after 40 μ s. To completely show the transient startup from time zero to saturation, we can temporarily comment out C_P (or artificially reduce its value). Good startup waveform results with only 20 μ s of simulation.

Open-Loop Response

It's relatively easy to obtain closed-loop Bode plots showing the magnitude and phase responses of the circuit with PSpice. All we have to do is to plot the waveform at the output of the oscillator. However, it's more tricky to

obtain the open loop response. It's the open loop response that shows the gain margin and phase margin critical to oscillation.

One common method is to use a large-value capacitor and inductor to break the loop. Another method is to open the feedback loop and reflect the impedances at the break points. A voltage generator can then excite the circuit for open loop measurement.

Whereas the first method can introduce improper loading to the circuit, the second method significantly increases the circuit size and run time. In this circuit we will attempt to open the loop by inserting a 1V AC pseudo voltage source between the output node of the crystal and the input node of the CMOS amplifier. Since the amplifier has almost infinite input impedance and since the ideal voltage source has zero series impedance and infinite parallel impedance, the addition should not disturb the loading of the circuit. The DC level of the voltage source is the DC operating point of the circuit obtained from the transient analysis output file. The command, VPS NVIN 0 DC 2.557 AC 1, accomplishes this task. Figure 4 lists the modified circuit for open loop analysis.

To be certain that no unwanted oscillation modes can occur in the frequency range of interest, we have to consider both broadband and narrowband analyses. Figure 5 illustrates the broadband response of the circuit with the command, .AC DEC 1000 1E6 300E6. Zooming in, the spike in the waveform that indicates the frequency of oscillation will not reveal the detail of the response. Instead, we have to sweep the frequency linearly in the immediate vicinity of the resonant frequency to show the amplitude peaking and the zero-degree phase-crossing at the series (resonant) frequency and parallel (anti-resonant) frequency.

Figure 6 illustrates the narrow band response of the circuit with the command, .AC LIN 1000 23.8E6 24.2E6. As expected, the loop gain peaks at f_1 where the loop phase shift crosses through zero degree. The crystal resonating with C_P and the load capacitors creates a complex pole pair that causes this behavior. At f_2 the loop gain drops below unity and the loop phase once again crosses through zero degrees. f_2 is the parallel resonant frequency formed by the crystal resonating with C_P to form a complex zero pair and a high impedance in the feed-

back circuit.

The oscillator's phase margin is the maximum angle past zero degrees that the loop phase shift has between f_1 and f_2 . The phase margin gives a measure of how much loading the oscillator can withstand and still start-up. If the loading on the oscillator is too much, the phase will not pass through zero degrees and the oscillator will not start. Similarly, the oscillator's gain margin is the maximum magnitude past unity that the loop gain has at the zero-degree crossing phase. The larger the gain margin, the more loss the feedback loop the oscillator can withstand.

Using Probe, we can also obtain a Nyquist plot of the combined amplitude and phase responses by plotting the imaginary part of the crystal output voltage versus its real part using linear frequency scaling. Figure 7 shows that the Nyquist plot encircles the point (1,0) which indicates oscillation for a positive feedback circuit. The Nyquist plot uses the same data file as that of the narrowband plot.

The mathematical signal processing ability of Probe is very useful when it comes to plotting the impedance of the feedback loop. Figure 8 is the new circuit file used for this purpose. The circuit consists of only the feedback loop which contains the series resistor, the crystal and the load capacitors. A large value resistor parallel to the load capacitor provides the DC path to ground. To simplify the analysis, we use a 1V AC voltage source for excitation. From the loop voltage and current expressions and after some complex algebra manipulation, the feedback impedance expressions in Probe become:

$$\begin{aligned} \text{mag}(Z) &= 1 / (\text{IM}(\text{RS})) \\ \text{phase}(Z) &= -\text{IP}(\text{RS}) \\ \text{real}(Z) &= \text{IR}(\text{RS}) / (\text{IM}(\text{RS}) \cdot \text{IM}(\text{RS})) \\ \text{imag}(Z) &= -\text{II}(\text{RS}) / (\text{IM}(\text{RS}) \cdot \text{IM}(\text{RS})) \end{aligned}$$

In a series-resonant oscillator, the crystal operates at its natural series frequency. In a parallel resonant oscillator, the feedback circuit introduces a load capacitance to the crystal. In this case, the crystal operates at the frequency where the crystal reactance cancels the load capacitor reactance. Therefore when the load capacitance changes the resonant frequency also changes. We can examine the frequency pulling characteristic of the crystal oscillator by performing parametric

We've got your number.



Back in the old days, when the first cellular phones hit the road, life was simple: 12 volts, period.

Not anymore. With over a dozen major manufacturers offering a wide variety of models, it's a challenge to supply them with a range of RF power amplifiers to do the job.

But we've met that challenge; our RFIC power amplifiers will work in many of the latest, newest, smallest analog and digital cell phones. And with battery voltages from 3.3 to 5.8 volts and output power levels as high as 1.2 watts.

In other words, we've got your number.

And that's not all: based on our MSAG®-Lite technology, our line of RFIC power amplifiers can help you reduce total system size enough to actually add more features in the same space. Cell phone talk time can be extended by as much as 30% compared to using Si discretes or modules. Plus, you can lighten up the entire system.

And all of this at a *very* affordable number.

Want to hear more? Here's a couple more numbers you'll need: Call us at 540-563-3949. Or fax us at 540-563-3935.




ITT GTC

INFO/CARD 27

IN SPEC. ON TIME. ON BUDGET.

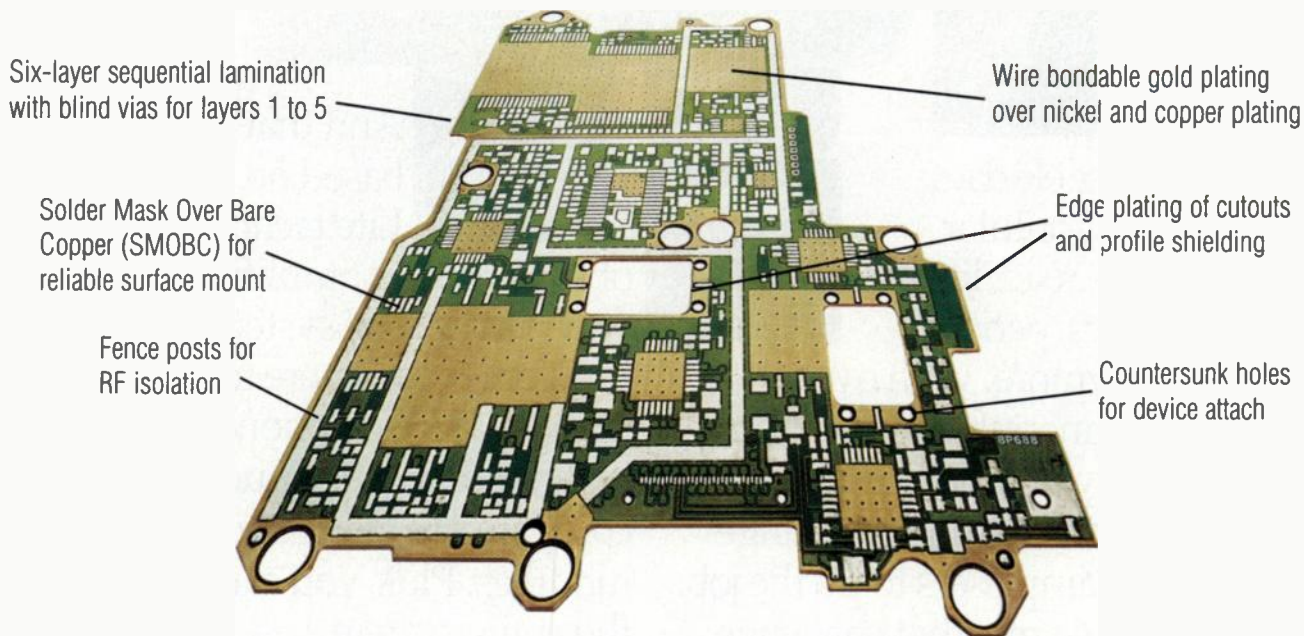What else would you expect from
Methode Electronics?



This high frequency microwave printed circuit board meets all MIL, ANSI, and IPC specifications and standards for electrical performance and physical tolerances. The innovative techniques used to fabricate this board put us head and shoulders above ordinary board shops.

If performance, delivery, and costs are important to you, count on the *resources* of our

multi-million dollar, international organization and the *resourcefulness* of over ten years' experience fabricating quality microwave circuits to meet your precise requirements.

We'll be pleased to discuss your application in detail, and offer proven, cost-effective solutions. Let us hear from you today.

INFO/CARD 28



METHODE ELECTRONICS, INC. EAST

10 Industrial Drive • Willingboro, NJ 08046 • (609) 871-3500 • FAX: (609) 871-0061 • Modem: (609) 871-3347

Methode is growing—contact us about available representative territories.

Global solutions... for all your communications testing needs.

Noise Com noise products and test instruments are being used throughout the world to evaluate the performance of cellular, satellite, and radar communications and data transmission systems.

Whether you require noise sources, modules, or generators, or are interested in our state-of-the-art test instruments such as our multipath fading emulator or Interference Test Set™, we have the products to suit your application.

Every Noise Com product is backed by years of research and testing where it counts...*in the field*. That translates to products that deliver outstanding stability and quality...in the toughest applications.


At Noise Com, the only thing better than our products is our dedication to providing the best technical service and support in the business. We also realize that time is money, so you can count on receiving your custom component, test equipment, or an entire turnkey system on time...every time.

Pictured here are some of our standard products. For more details, ask for our *Complete Line of Broadband Noise Products* catalog. If you're interested in our critically-acclaimed test equipment, make sure you request a copy of our *Test Equipment For Wireless & Telecommunications* catalog. Whatever you decide...we'd love to hear from you.

Noise Com. Your global partner for noise, wireless, and telecommunications testing solutions.



For more information
and a quick response,
call NOISE COM,
the experts in testing,
at 201-261-8797.



When you
need a company
to provide
solutions to
your noise
testing needs...
all points
lead to

NOISE/COM

Chips and Diodes



All Noise Com diodes deliver symmetrical white Gaussian noise and flat output power versus frequency. Noise Com diodes are available in a wide variety of package styles, and in special configurations on request.

TYPICAL STANDARD MODELS

MODEL	FREQUENCY RANGE
NC 302	10 Hz – 3 GHz
NC 305	10 MHz – 11 GHz
NC 401	100 MHz – 18 GHz
NC 406	18 GHz – 110 GHz

BITE Modules




The NC 500 series drop-in noise modules in TO-8 cans and flat packs for surface mounting are an economical solution for built-in test requirements. These devices contain complete biasing networks and need no external components. Also available are TO-39 packages.

TYPICAL STANDARD MODELS

MODEL	FREQUENCY RANGE	OUTPUT ENR
NC 501/15	0.2 MHz – 500 MHz	31 dB
NC 502/15	0.2 MHz – 1000 MHz	31 dB
NC 503/15	0.2 MHz – 2000 MHz	31 dB
NC 506/15	0.2 MHz – 5 GHz	31 dB
NC 511/15	0.2 MHz – 500 MHz	51 dB
NC 513/15	0.2 MHz – 2 GHz	51 dB


Broadband Amplified Modules

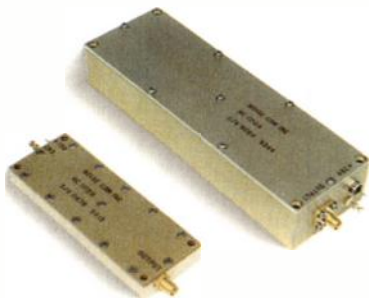

The NC 1000 series amplified noise modules produce white Gaussian noise from -14 dBm to +13 dBm at frequencies up to 6 GHz. They are designed for coaxial test systems, and are available with several bias voltages and connector options.

TYPICAL STANDARD MODELS

MODEL	FREQUENCY RANGE	OUTPUT
NC 1101A	10 Hz – 20 kHz	+13 dBm
NC 1107A	100 Hz – 100 MHz	+13 dBm
NC 1112B	20 MHz – 2 GHz	0 dBm
NC 1126A	2 GHz – 6 GHz	-14 dBm

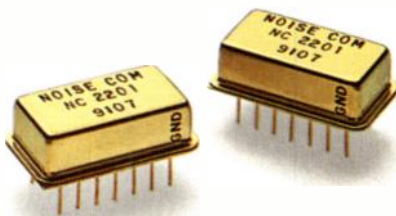

The NC 2000 series amplified noise modules are an excellent choice when a high level noise output is desired and the noise source is to be mounted on a circuit board. 24 pin packages are standard; 14 pins are also available.

TYPICAL STANDARD MODELS

MODEL	FREQUENCY RANGE	OUTPUT
NC 2101	100 Hz – 20 kHz	0.15 Vrms
NC 2105	500 Hz – 10 MHz	0.15 Vrms
NC 2201	1 MHz – 100 MHz	+5 dBm
NC 2601	1 MHz – 2 GHz	-5 dBm

NOISE/COM

A Wireless
Telecom Group
Company

Broadband Precision, Calibrated Coaxial



Noise Com's NC 346 series is designed for precision noise figure measurement applications. These products are available with coaxial or waveguide outputs. For OEM applications, the NC 3200 series provides high performance in a small ruggedized package.

TYPICAL STANDARD MODELS

MODEL	FREQUENCY RANGE	OUTPUT ENR
NC 346A	0.01 GHz – 18 GHz	6 dB
NC 346B	0.01 GHz – 18 GHz	15 dB
NC 346C	0.01 GHz – 26.5 GHz	15 dB
NC 346D	0.01 GHz – 18 GHz	25 dB
NC 346Ka	0.1 GHz – 40 GHz	15 dB

Broadband Calibrated Millimeter-wave



The NC 5000 series noise sources feature outstanding stability and convenience in waveguide bands up to 110 GHz.

TYPICAL STANDARD MODELS

MODEL	FREQUENCY RANGE	WAVEGUIDE
NC 5142	18 GHz – 26.5 GHz	WR-42
NC 5128	26 GHz – 40 GHz	WR-28
NC 5122	33 GHz – 50 GHz	WR-22
NC 5115	50 GHz – 75 GHz	WR-15
NC 5110	75 GHz – 110 GHz	WR-10

Broadband Noise Generators



The NC 6000 and NC 8000 series noise-generating instruments are designed for applications on the test bench or incorporated with other equipment to provide a wide variety of functions. Each instrument contains a precision noise source, amplification, and step attenuators to provide repeatable symmetrical white Gaussian noise with variable output power.

TYPICAL STANDARD MODELS

MODEL	FREQUENCY RANGE	OUTPUT POWER
NC 6107	100 Hz – 100 MHz	+13 dBm
NC 6108	100 Hz – 500 MHz	+10 dBm
NC 6110	100 Hz – 1500 MHz	+10 dBm
NC 6124	2 GHz – 4 GHz	-10 dBm
NC 8107	250 kHz – 100 MHz	+30 dBm
NC 8111	5 MHz – 1 GHz	+30 dBm



The new UFX-7000 series noise-generating instruments are extremely easy to use, combining dedicated keys for control of operations and programming, with a large 4 x 20-character LCD display. Control of output power, filter settings, and attenuator step size for both the noise and the signal (for units with internal combiners) is performed from the front panel or by remotely using the IEEE-488 interface.

TYPICAL STANDARD MODELS

MODEL	FREQUENCY RANGE	OUTPUT POWER
UFX-7107	100 Hz – 100 MHz	+13 dBm
UFX-7108	100 Hz – 500 MHz	+10 dBm
UFX-7110	100 Hz – 1500 MHz	+10 dBm
UFX-7218	2 GHz – 18 GHz	-20 dBm
UFX-7909	1 MHz – 300 MHz	+30 dBm



Your global partner for noise, wireless, and telecommunications testing solutions.

NOISE/COM

A Wireless Telecom Group Company

E. 49 Midland Ave., Paramus, NJ 07652
Tel: 201-261-8797 • Fax: 201-261-8339

analysis on the input load capacitance over a wide range. Figure 9 shows that the range of frequency the crystal can pull to either side of its nominal value is extremely narrow. Note that the reactance curve crosses zero at two frequencies which represent the series resonant and parallel resonant. Between the two frequencies, the reactance is inductive. Below and beyond that range, the reactance is capacitive. The oscillator operates in the inductive region between the two resonant frequencies.

The impedance of the crystal itself can also be plotted by commenting out the series resistor and the load capacitors.

Inserting a zero-volt AC voltage source as a current meter in series with the crystal and again use a IV AC source for excitation, the magnitude and phase of the crystal impedance are expressed as follow:

$$\text{mag}(Z) = \text{DB} (V_M(I) / I_M(V_S))$$

$$\text{phase}(Z) = -IP(V_S)$$

Figure 10 shows the resulting plot. As expected, the response is similar to that of the whole feedback network. The phase of the crystal impedance crosses zero at the series and parallel frequencies. Note that the frequencies of minimum and maximum impedance differ slightly with the series and parallel frequencies. These frequencies would be the same if the motional resistance of the crystal $R_M = 0$. The crystal controls the frequency response of the feedback and the load capacitors only influence this response slightly

Conclusion

We have shown that using transient response, gain and phase margin analysis from the open loop response, the feedback network reactance plot, and the Nyquist plot, we can be confident that the embedded oscillator can reliably start-up and oscillate. We can simulate the crystal operation at an overtone by adding the harmonic motional arm in parallel with the fundamental motional arm of the crystal. A note about temperature analysis is that the cutting angle of the crystal blank governs the performance of the crystal over the temperature range. Most AT-cut quartz crystals have a quadratic temperature dependence. We can model this dependency by giving the

About the Author


Kien Truong graduated from Iowa State University in 1985. he is now a design engineer in Integrated Avionics Research at Boeing. Hie experience ranges from antenna and radar to fiber optic sensors and fault tolerant computing. Kien enjoys sailing, telemarking and family outings. He can be reached at Boeing Commercial Airplane Group, P.O. Box 3707 M/S 6H-EC, Seattle, WA 98124.

motional inductor a quadratic temperature coefficient TC2. Also note that the FET transistors already


have their temperature dependencies built into the models of these devices. **RF**



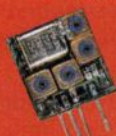The oscillators with the quartz crystals from KVG measure absolutely everything, even before you'll see or hear it.



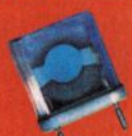Oscillators with quartz crystals deliver the quality you need, quartz-precise.



Communication and measurement technique. Worldwide. KVG.



KVG
North America Inc.
Werner Mueller
2240 Woolbright Rd.
Boynton Beach
FL 33426-6325
Tel. (407) 734-9007
Fax (407) 734-9008


Crystals for GPS, Pager, Telecommunication

■ **Crystals** ■ Frequency range 1 MHz to 360 MHz ■ Low aging ■ Tight temperature stability ■ High shock and vibration resistance ■ Special glass enclosures ■ SMT solutions ■ Reliable and produced under ISO 9001 certified QS-System.



Crystal Components for Telecommunication Networks

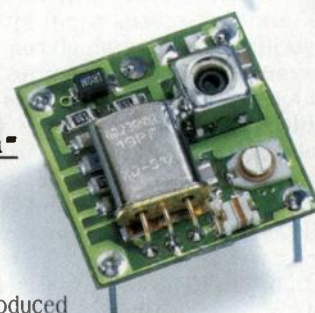
■ **Oscillators** ■ Frequency range 3 kHz to 622,080 MHz ■ Low aging ■ Tight temperature stability ■ SMT solutions ■ Reliable and produced under ISO 9001 certified QS-System.



Frequency (MHz)	PXO	VXO	TCXO	VCTCXO	DTCXO	OCXO
1.544	T-1 (DS 1)	T-1 (DS 1)	T-1 (DS 1)	T-1 (DS 1)	T-1 (DS 1)	—
12.352	T-1 (DS 1)	T-1 (DS 1)	T-1 (DS 1)	T-1 (DS 1)	T-1 (DS 1)	—
16.384	SDH SONET ISDN	SDH SONET ISDN	SDH SONET ISDN	SDH SONET ISDN	SDH SONET ISDN	SDH SONET ISDN
38.880	SDH/STM-1	SDH/STM-1	SDH/STM-1	SDH/STM-1	—	—
44.736	ATM T-3 (DS 3)	ATM T-3 (DS 3)	ATM T-3 (DS 3)	ATM T-3 (DS 3)	—	—
51.840	SONET/STS 1	SONET/STS 1	SONET/STS 1	SONET/STS 1	SONET/STS 1	—
155.520	ATM STM-1/STS-3c SONET/OC-3c	ATM STM-1/STS-3c SONET/OC-3c	ATM STM-1/STS-3c SONET/OC-3c	ATM STM-1/STS-3c SONET/OC-3c	—	—
622.080	—	SDH-STM 4 SONET/STS-12	—	—	—	—

■ **Filter** ■ Frequency range 1 MHz to 200 MHz ■ Discrete and monolithic types ■ Reliable and produced under ISO 9001 certified QS-System.

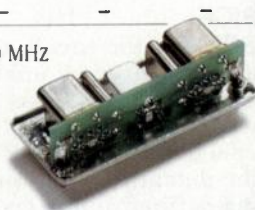■ For superior quartz crystals, oscillator and filter products from the ISO 9001 certified source, talk to us.



KVG North America Inc.
Together for quality.



Circuit Envelope Simulator Analyzes High-Frequency Modulated Signals

By Andy Howard
HP EEsof

Modern communication systems handle RF signals with complex digital modulation. The most commonly used simulators for RF circuit design, SPICE and harmonic balance, have serious shortcomings when simulating such modulated signals. This article describes the new circuit envelope simulation technology and its advantages over SPICE and harmonic balance.

The HP 85148A Circuit Envelope simulator uses a patent-pending hybrid technology, which combines the advantages of time-domain and frequency-domain techniques. Unlike SPICE or harmonic balance, this technology is best suited for circuits with transient or modulated RF or high-frequency carriers. This new technology allows signals to be represented as a few carriers with time-varying modulation "envelope(s)." The Circuit Envelope simulator allows a designer to see how a circuit affects the modulation directly, and see such things as the spectrum of a modulated signal around a carrier, as well as amplitude, phase, and frequency versus time waveforms. Typical applications include analyzing the spectral regrowth or adjacent-channel power leakage generated by an amplifier or mixer circuit, oscillator turn-on amplitude and frequency versus time, automatic level control loop transients, phase-locked loop transients, and subsystem simulation with digitally modulated carriers.

SPICE

SPICE is the circuit simulator most commonly used by analog designers today, but it has some serious drawbacks when simulating transient and modulated RF signals. Because it is a time-domain simulator, it samples user-defined input waveforms and then solves the circuit at successive time steps. For SPICE simulations, three parameters determine the overall simulation time: the time step, the

time required for any initial transient response to die out, and the number of periods of the lowest frequency signal that must be simulated. In most communication systems, the RF signal frequency (1-2 GHz) is much higher than the modulation frequency bandwidth (often <200 kHz). Unfortunately, SPICE treats a modulated RF signal the same as any time-domain waveform, with step size determined by the RF carrier frequency (or its harmonics), and the stop time determined by the number of periods of the modulating signal. This can lead to a very large number of simulation steps (see sidebar example), as well as a large amount of memory for storing the results and post-processing them for display. Another drawback of SPICE simulation is the significant post-processing required to extract the modulation envelopes (or I and Q data) usually desired when simulating digitally-modulated RF waveforms.

Dynamic Convolution

Another SPICE limitation is that it does not handle the frequency-domain models commonly used in high-frequency circuit analysis, instead using lumped element models or transmis-

sion lines with a pure time delay. To overcome this problem, dynamic convolution simulators were invented. They allow complex, frequency-domain models and measured data to be used in nonlinear, time-domain circuit simulations. However, the modulated RF signal is treated the same way as SPICE, without distinguishing between the modulation and the RF carrier. Therefore, simulation times for RF modulated signals are as slow as with SPICE.

Harmonic Balance

Harmonic balance analysis is best suited for simulating the steady-state behavior of nonlinear circuits. However, most communication systems now use digital modulation, which is pseudo-random and cannot be considered steady-state. These modulation waveforms can be modeled with harmonic balance, but only if they are modeled as periodic bit sequences of limited (32 bits or less) length. Harmonic balance models these modulated waveforms with a fundamental tone and a very large number of its harmonics, therefore requiring an excessive amount of memory (and time) to simulate even a short bit sequence.


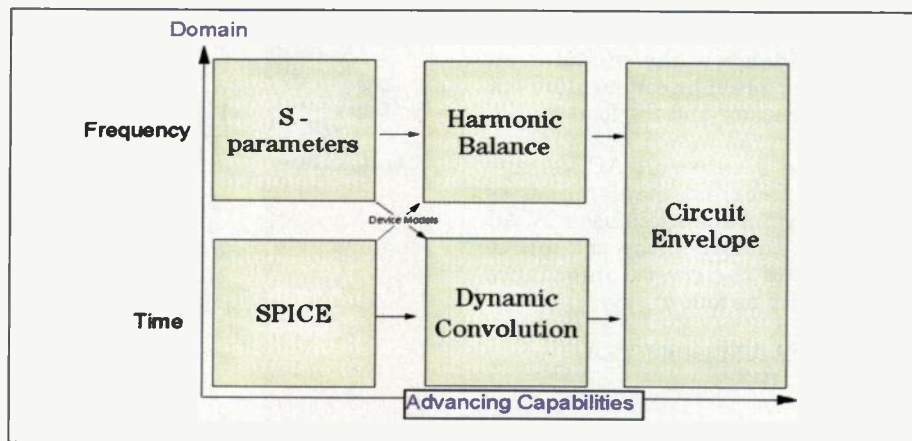


Figure 1. Circuit envelope technology extends HP EEsof's simulation solutions, allowing simultaneous use of time- and frequency-domain techniques.

IMPEDANCE


SMC

TRANSFORMERS

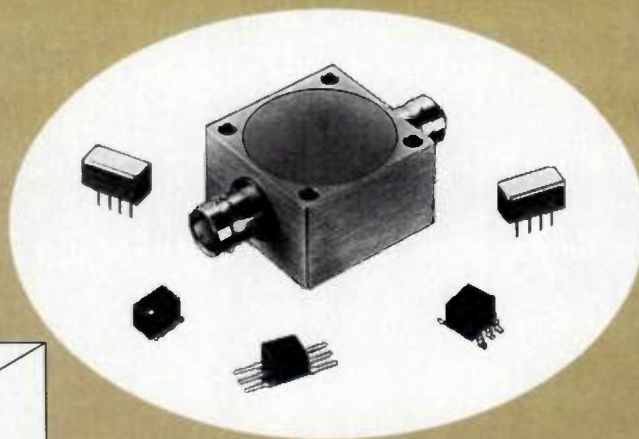

Synergy offers a wide range selection of **low-cost** RF impedance transformers for a wide variety of signal processing applications. These transformers come in various transformation ratios, from 1:1 up to 36:1, and in a large selection of package styles . . . surface mount - plug-in - connectorized . . . all competitively priced. Frequency ranges cover 0.01 MHz up to 1200 MHz in various bandwidths.

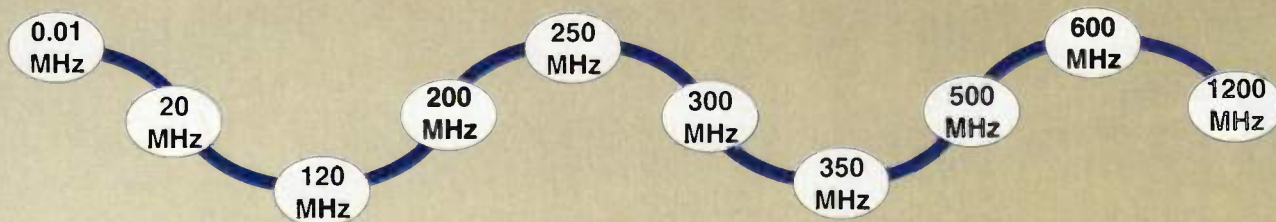And, as always, the experienced **S**ynergy Applications Engineering Team is ready to answer technical questions and help with your high volume or custom designs for transformers, mixers, power dividers, couplers, filters, modulators, and VCOs.



201 McLean Boulevard, Paterson, NJ 07504

TEL: (201) 881-8800 • FAX: (201) 881-8361

SYNERGY
MICROWAVE CORPORATION
INFO/CARD 30

making interactive TV a reality. It's just one of the myriad of ways M/A-COM's unsurpassed expertise in RF/microwave technology is helping manufacturers and their customers around the world. With the industry's broadest product line of innovative wired and unwired network connectivity solutions. So no matter what RF applications you're developing for the home, call M/A-COM. And just ask us how.



RF/microwave network connectivity solutions for the home.



Motion detection/sensing components for RF security systems.



A broad array of RF solutions for cellular and PCS networks – from semiconductors to antennas.



RF electronics for interactive TV, wireless CATV and satellite TV networks. And more.

M/A-COM
an AMP company

Sales offices in 33 countries around the world.

Americas 1-800-366-2266 • Europe/Middle East/Africa 44 (1344) 869 595 • Asia/Pacific 81 (03) 3226-1671

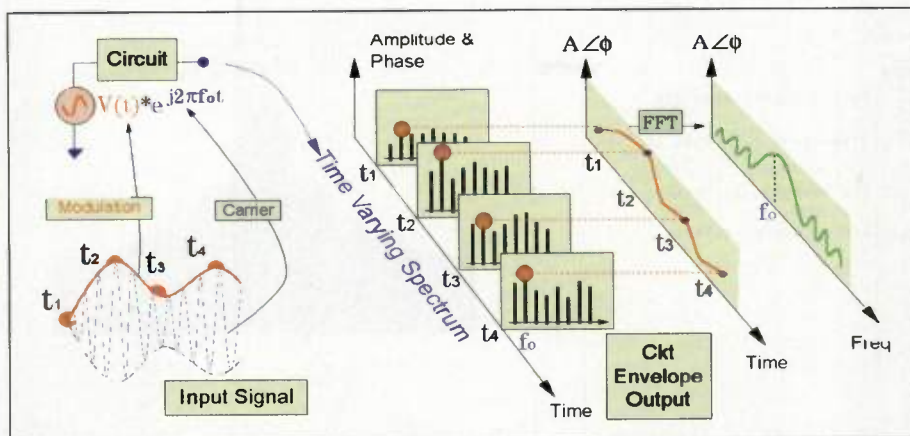


Figure 2. Circuit envelope technology allows the designer to set the time step just small enough to track the modulation envelope.

While harmonic balance has some problems analyzing complex modulated signals, it does have some advantages over SPICE. Harmonic balance is significantly more efficient for the analysis of circuits with widely varying frequency components, such as mixers, as long as a large number of harmonics is not required. Linear devices with arbitrary frequency responses can be easily modeled. At RF and microwave frequencies, many devices cannot be modeled with simple differential equations, and often must be characterized with measured, frequency-domain data. Harmonic balance directly provides the steady-state solution, without having to wait until the transient response dies out.

S-Parameter Analysis

S-parameter analysis is commonly used for RF and microwave circuit design, but it is only applicable for linear analysis. It is not applicable for simulating transient or modulated RF signals in nonlinear circuits.

Circuit Envelope Technology

The Circuit Envelope simulator overcomes the limitations described above by using a combined time- and frequency-domain technology. With this technique, the input waveforms are represented as RF carriers with modulation "envelopes" that are described in the time domain. The solution involves finding the Fourier coefficients, $V_k(t)$, in the following equation:

$$v(t) = \text{real} \left[\sum_{k=0}^N V_k(t) e^{j\omega_k t} \right]$$

Here, $v(t)$ is a voltage at any node in the circuit, including the input. In standard harmonic balance, the Fourier coefficients are complex constants,

whereas with the Circuit Envelope simulator, they are allowed to vary with time. They may represent an arbitrary modulation of each of the carriers. This spectrum may represent transient signals with continuous spectra (such as a digital modulation envelope), or periodic signals with discrete spectral lines (i.e., to generate two RF tones required for intermodulation distortion analysis).

Figure 2 shows how the envelope is represented in the simulator, for the simple case of amplitude modulation. The simulator computes the instantaneous envelope versus time of each spectral component. This allows the computation and display of the amplitude, phase, I, Q, or frequency versus time for any component. Computing the Fourier transform of a time-varying spectral component allows the designer to see the spectrum around a spectral component, similar to a spectrum analyzer display.

Improvements Over SPICE

Simulation efficiency is much better, because the time step is determined by the bandwidth of the modulation, which is relatively narrow, not by the frequency of the RF carrier or its harmonics.

Simulation accuracy is improved. With simulators such as SPICE, the accuracy of the numerical integration routine degrades as the signal frequency approaches the sampling frequency. With the Circuit Envelope simulator, multiple integrations are being performed, each one centered on a carrier, so the highest accuracy is achieved at each signal frequency of interest. The accuracies at the carrier frequencies are as good as those of the basic harmonic balance simulator.

The instantaneous amplitude and phase information (or I-Q signals) are

Call today for
information on how
we can put our
RF/microwave expertise
to work for you.

It seems as if there are new applications for RF/microwave networks emerging every day. But whatever applications you're developing, you can rest assured that M/A-COM has both the products and the experience to help you build them as quickly and economically as possible. From semiconductors to antennas.



From connectors to multi-function assemblies. We have what you need. And we also have a wide range of ways to inform you and keep you up-to-date about our growing family of products and solutions. To find out more, or to reach the M/A-COM sales office nearest you, contact us today.

M/A-COM
an AMP company

Americas 1-800-366-2266
Europe/Middle East/Africa
44 (1344) 869 595
Asia/Pacific 81 (03) 3226-1671

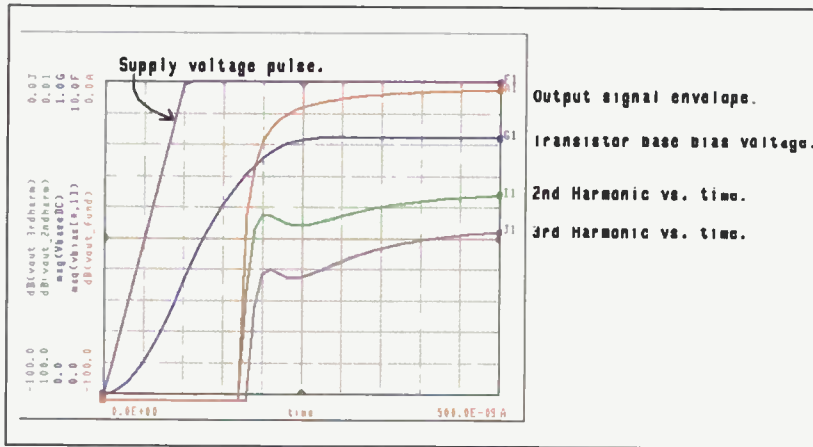


Figure 3. Circuit Envelope simulator predicts the output harmonics of an amplifier plotted versus time. This allows designers to make trade-offs between conserving battery life and output distortion.

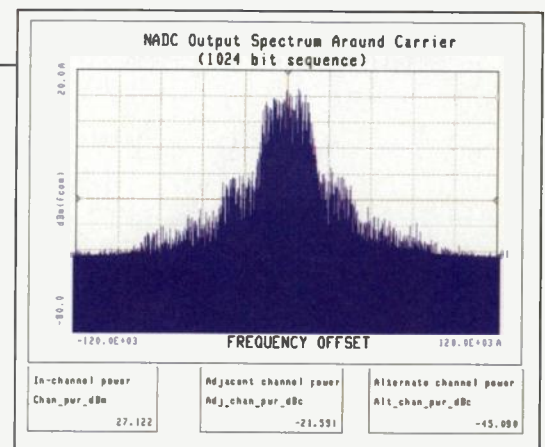


Figure 4. Simulation output showing spectral regrowth around the RF transmission carrier of an NADC power amplifier.

immediately available. This gives the Circuit Envelope simulator the ability to output and/or use such information as signal frequency versus time.

Frequency-domain models are more effectively and accurately incorporated. Circuit Envelope has the advantages of harmonic balance for modeling devices and circuit elements in the frequency domain.

With the Circuit Envelope simulator, the user has the option of starting a simulation from the steady-state solution, or examining turn-on transient responses.

Advantages Over Harmonic Balance

The Circuit Envelope simulator is much more efficient than harmonic balance for simulating digitally-modulated carriers because the modulation waveform is described in the time domain rather than via a fundamental tone and harmonics. This leads to much faster simulations requiring only a fraction of the computer memory.

Applications

The Circuit Envelope simulator is applicable for simulating high-frequency amplifiers, mixers, oscillators, and sub-systems with transient or modulated RF signals. The smaller the modulation bandwidth relative to the RF carrier frequency, the greater the improvement in simulation efficiency over SPICE. The Circuit Envelope simulator is also an excellent tool for simulating transient responses of circuits such as AGC loops and phase-locked loops, where a low-frequency transient signal must be simulated along with a high-frequency RF signal. These applications include:

- Amplifier spectral regrowth and adjacent-channel power leakage,

with digitally-modulated RF signals as the input.

- Oscillator turn-on transients and frequency output versus time, in response to a transient control voltage.
- Phase-locked loop transient responses.
- AGC and ALC transient responses.
- Circuit effects on signals with transient amplitude, phase, or frequency modulation.
- Amplifier harmonics versus time.
- Sub-system analysis with modulation signals such as multi-level FSK, CDMA, TDMA.
- Much more efficient analysis of mixer and amplifier third and higher-order intercept points.
- Time-domain optimization of transient responses.

Amplifier Harmonics Versus Time

A designer of amplifiers for mobile communications gear might be interested in plotting amplifier harmonics versus time. To maximize battery life,

it is necessary to switch on the power supply to the amplifier just before transmitting. There must be a delay between switching on the power supply and transmitting information, because if the amplifier is not completely on, it will generate excessive harmonics. The Circuit Envelope simulator allows designers to simulate the transient bias supply voltage(s) and see how long it takes the voltages at the device to reach steady-state. After an appropriate delay, the signal can be pulsed on, and the envelope of the output harmonics versus time may be plotted. One such simulation result is shown in Figure 3. The time step can be set just small enough to adequately model the variation in the envelopes of each spectral component.

Amplifier Spectral Regrowth with an NADC1 Input Signal

Spectral regrowth and adjacent channel power leakage are critical

Comparing SPICE and Circuit Envelope Technology

The following compares the time step size and the number of time steps required to simulate an amplifier with an input signal consisting of an 890 MHz RF carrier modulated with a 24.3 kHz symbol rate (NADC modulation). Assume that 512 symbols must be simulated. The following table compares the difference in time step size and the number of time steps.

	Time Step Size	Number of Time Steps
SPICE	62.4 picoseconds	168.8 million
Circuit Envelope	4.1 microseconds	5,139

This assumes the circuit generates significant 3rd harmonics, which means that to satisfy the Nyquist sampling criterion, a sampling rate of at least 5.34 GHz must be used. To obtain reasonable accuracy from SPICE's integration algorithms, a sampling frequency of 16 GHz (time step = $1/(16 \text{ GHz}) = 62.4 \text{ ps}$) is a more realistic minimum. The simulation stop time is $512/(24.3 \text{ kHz}) = 21.07 \text{ ms}$. Circuit Envelope does require a vector of complex voltages to be computed at each time point, rather than just a single real value, but the simulation time will still be orders of magnitude faster than SPICE.

specifications for digital communication system designers. Digital modulation is characterized with a power spectral density, whereas analog modulation is characterized with discrete spectra [1]. Until now, designers have characterized amplifier nonlinearities via simulations and measurements of third-order (and higher) intercept points, generated from two unmodulated sinewave input signals. Unfortunately, these signals do not represent digitally-modulated waveforms very well. Consequently, these simulations and measurements do not always predict spectral regrowth and adjacent channel power performance [2]. The Circuit Envelope simulator overcomes the limitations of SPICE and harmonic balance when simulating such waveforms, as described above.

Figure 4 shows the simulated output spectrum resulting when a signal with NADC modulation (1024-bit sequence) is sent through a power amplifier. The output signal's adjacent and alternate channel power ratios are calculated by the post-processor, and eye diagrams and constellation plots may be generated, as well. This simulation required less than 14 minutes and less than 4 MBytes of virtual memory on an HP 9000 Series 715/100 workstation. The simulation may be run with different input signal power levels.

Mixer Nonlinearity Simulations

Mixer nonlinearities are often characterized via a third-order intercept (TOI) simulation, in which two closely-spaced sinewaves (tones) are input at the RF port. These simulations are very time-consuming in SPICE because of the large difference between the beat frequency (the spacing between the two RF tones) and the RF frequencies. Harmonic balance simulations can be very time and memory intensive because three large-signal tones must be modeled. The Circuit Envelope simulator allows a much faster simulation with only a fraction of the memory requirement of harmonic balance, by modeling the two input tones as a single RF tone, with cosine modulation. The cosine modulation splits the RF tone into two signals spaced at twice the modulation frequency:

$$V_{rf}(t) = \text{real} \left[2 \cos(2\pi f_m t) e^{j2\pi f_r t} \right]$$

$$= \text{real} \left[e^{j2\pi(f_{rf} + f_m)t} + e^{j2\pi(f_{rf} - f_m)t} \right]$$

The Lightning Protection Course



Learn from the lightning protection experts!

Register today for one of our upcoming three-day seminars. Let us reserve a place for you.

PolyPhaser
CORPORATION

(800) 325-7170 ■ (702) 782-2511 ■ FAX: (702) 782-4476
BBS: (702) 782-6728 [8-N-1] ■ Internet @ POLYPHASER.COM
2225 Park Place ■ P.O. Box 9000 ■ Minden, NV 89423-9000

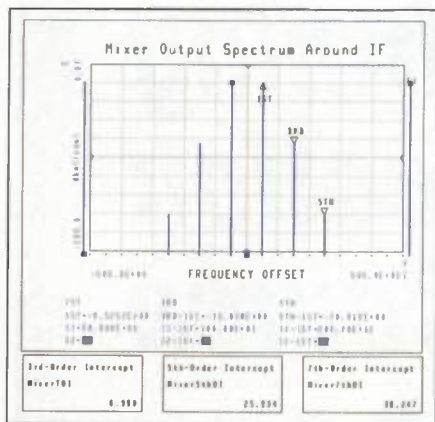


Figure 5. Mixer output spectrum around IF, with computed 3rd, 5th and 7th order intercept points.

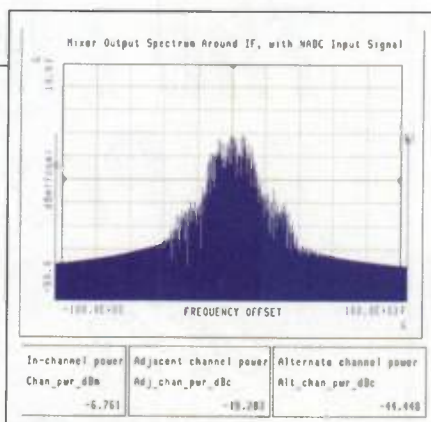


Figure 6. Gilbert cell mixer output spectrum around IF, with NADC modulation on input signal.

The simulation is run over a full period of the modulation signal, and the IF spectral component is computed as a function of time. Taking the discrete Fourier transform of the IF spectral component versus time gives the intermodulation distortion components, as shown in Figure 5. This simulation required 64.5 seconds and 18.4 MBytes of virtual memory, on an HP 9000 Series 715/100 workstation. The mixer analyzed has 14 BJTs.

Of course, using two sinusoids at the input may not adequately characterize the mixer's behavior when it converts digitally-modulated waveforms. The Circuit Envelope simulator allows a designer to simulate a mixer's contribution to adjacent-channel power leakage and spectral regrowth (Figure 6).

Oscillator Simulations

The Circuit Envelope simulator allows very efficient simulation of

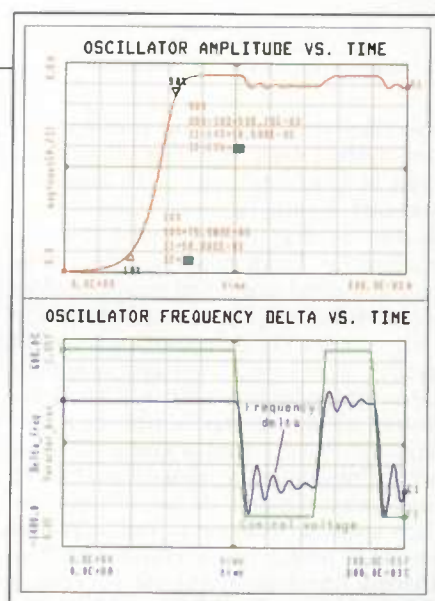


Figure 7. A crystal oscillator's turn-on transient, and its relative frequency in response to a control voltage waveform are shown.

oscillator turn-on time, amplitude versus time, and frequency versus time. In the crystal oscillator example shown in Figure 7, the 10-90% turn-on


WE'VE GOT THE POWER

We offer the most complete line of application specific and standard fixed attenuators and terminations in the industry.


JFW... The Power Leader

For more information or for a free catalog, contact:

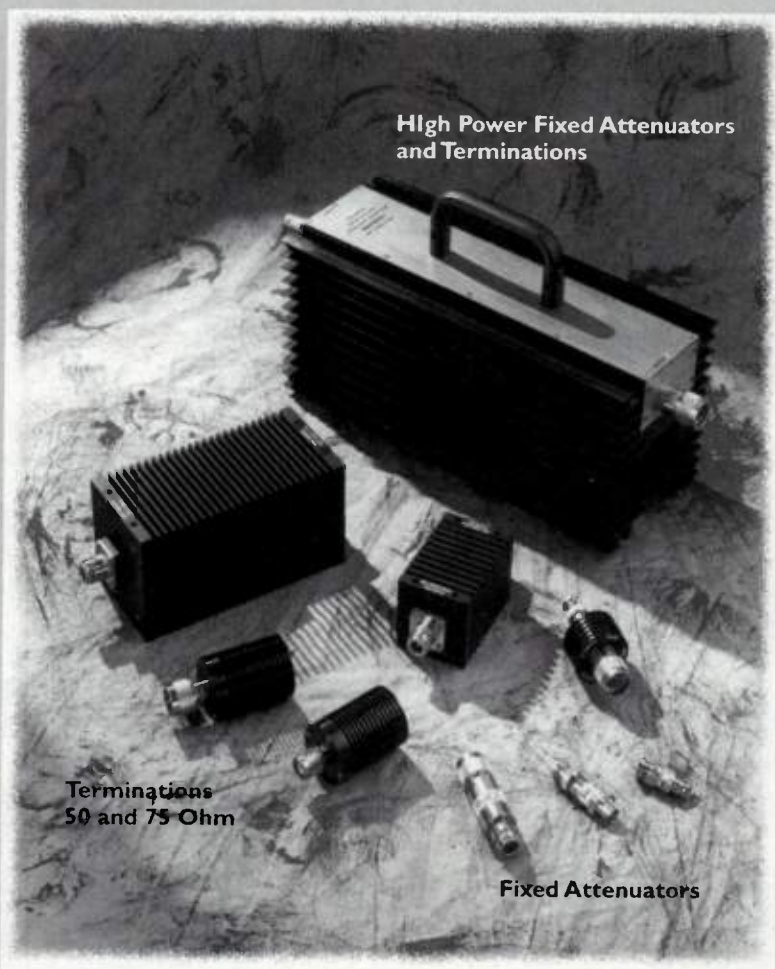JFW Industries, Inc.
5134 Commerce Square Drive
Indianapolis, Indiana 46237
Tele. (317) 887-1340 Fax (317) 881-6790




When the Press Asked "Why Penstock?"

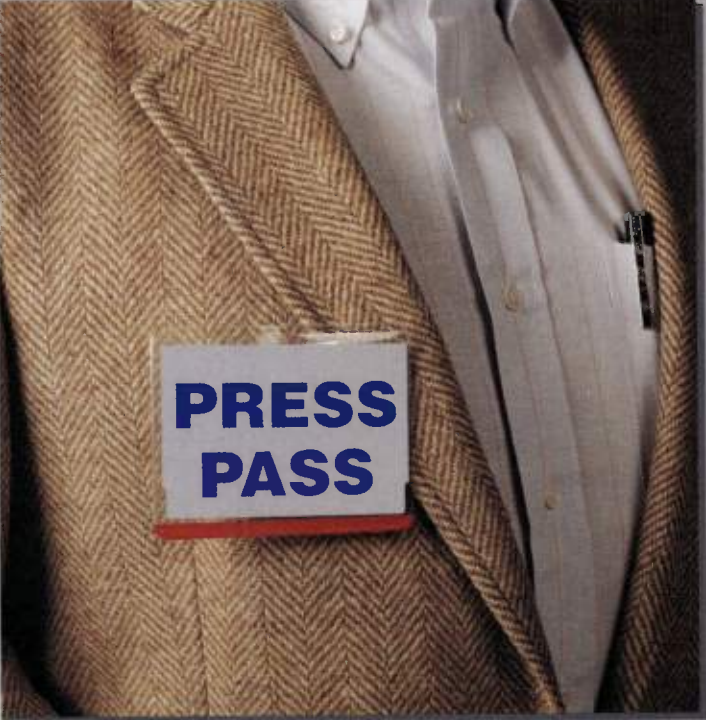

**PRESS
PASS**

Motorola responded:



"I am sure that Penstock's highly trained, technically competent sales force will serve Motorola customers well. We're excited to have Penstock, the premier speciality distributor of RF/Microwave products in North America, distribute Motorola products."

*—Brian Hilton
Corporate Vice President
Director of World Marketing
Motorola Semiconductor Division*

Penstock is honored to have been chosen as Motorola's newest distributor for R.F. and related semiconductors for use in wireless applications. Call 1-800-PENSTOCK for the following application notes and for a Penstock sales engineer to assist you:

AN593

Broadband Linear Power Amplifiers Using Push-Pull Transistors.

AN721

Impedance Matching Networks Applied To RF Power Transistors.

AN878

VHF MOS Power Applications.

AN1025

Reliability Considerations in Design and Use of RF Integrated Circuits

AN1024

RF Linear Hybrid Amplifiers



AN103

Match Impedances in Microwave Amplifiers

AN1107

Understanding RF Datasheet Parameters

AR176

New MOSFETs Simplify High Power RF Amplifier Design

AR346

RF Power FETs, Their Characteristics and Applications

AR511

Biasing Solid State Amplifiers to Linear Operation



MOTOROLA

1-800-PENSTOCK

Northern CA 408-730-0300

Canada 613-592-6088

INFO/CARD 35

PENSTOCK
RF/MICROWAVE DISTRIBUTION
AN AVNET COMPANY

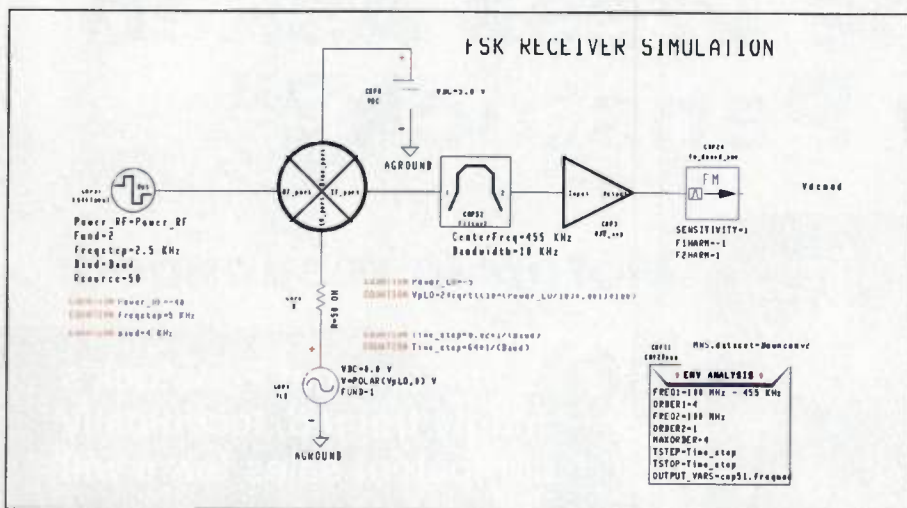


Figure 8. Receiver for four-level FSK demodulation using the mixer of Figure 5.

time is approximately 38.5 milliseconds. It is necessary to simulate from 0 to 150 ms to see the full turn-on transient. The Circuit Envelope simulator can generate the turn-on envelope even with a 5 ms time step (a 0.5 ms time step was used in Figure 7.) This means that only 31 time points are required. SPICE would require approximately 150 million time points, based on an oscillation frequency of 100 MHz and a time step equal to one tenth the period of oscillation.

It is also possible to simulate the oscillator's frequency versus time, in response to a control voltage input, also shown in Figure 7.

Frequency-Shift Keying (FSK) Simulation

The Circuit Envelope simulator can be used to model FSK (and other modulation format) receivers. The designer can see how the demodulated waveform depends on filter bandwidths, modulation waveform shape, frequency step size, interfering signal

strength, and noise. Figure 8 shows a simple receiver, and Figure 9 shows the input modulation and the demodulated waveform, with and without adjacent channel interfering tones.

ALC Loop Simulation and Optimization

In ALC circuits, there is usually a high frequency RF signal and slowly-varying DC voltage that is proportional to the power or voltage of the output RF signal. In this example, shown in Figure 10, an amplitude modulator is used to adjust the output signal power. A portion of the output signal is coupled off and converted to a DC voltage by a diode detector. The difference between this DC voltage and a reference voltage is integrated and becomes the input to the amplitude modulator. The output power can be set by changing the reference voltage. The designer is interested in seeing how the output power envelope changes versus time in response to a change in the reference voltage.

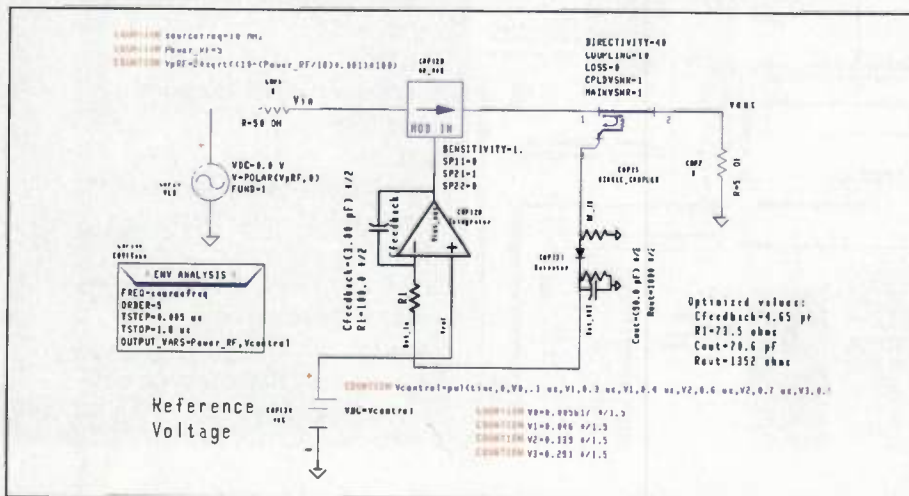


Figure 10. ALC loop setup for transient response simulation.

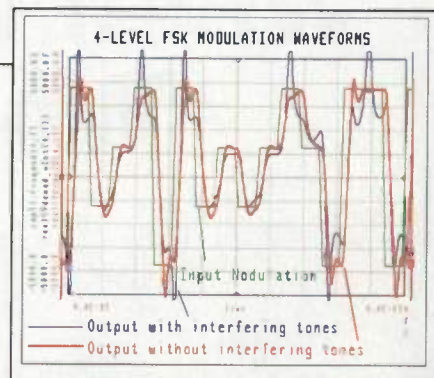


Figure 9. Four-level FSK input and output frequency deviation versus time modulation waveforms are shown.

In this case, the reference voltage is varied in a piecewise linear way to step the output power from 4 dBm to 8, 12 and 16 dBm. One of the traces in Figure 11 shows significant overshoot. The other trace is the output power versus time waveform after time-domain optimization of the detector output capacitor and resistor, integrator resistor and capacitor, and the reference voltage.

Phase-Locked Loop Simulation

Phase-locked loops (PLLs) can be simulated with the Circuit Envelope simulator. This example uses a PLL that could be used to generate the LO frequencies required for the Digital European Cordless Telephone (DECT) standard [3]. The VCO, divide-by-N block, and phase/frequency detector are all simulated using behavioral models. The simulated frequency-versus-time waveform in Figure 12 shows how quickly the VCO frequency settles when the value for N is increased from 1025 to 1026. Figure 13 shows the noise spectrum of a VCO with the PLL open and closed. This PLL did not have a divide-by-N block.

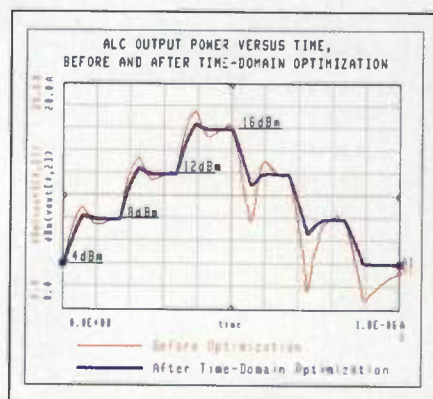


Figure 11. ALC output power versus time, before and after time-domain optimization to minimize overshoot.

Summary

The Circuit Envelope simulator uses a hybrid technology that combines the advantages of time-domain and frequency-domain techniques. This technology overcomes the limitations of SPICE and harmonic balance when simulating circuits with transient or modulated RF or high-frequency carriers. Many applications showing the new simulation capabilities (amplifier and mixer spectral regrowth, oscillator turn-on transient and frequency versus time, ALC transient response, time-domain optimization, efficient mixer TOI, FSK demodulation with and without interfering tones, PLL simulation, etc.) have been included in this article.

Readers desiring more information can contact HP EEsosf at (818) 879-6440, or circle Info/Card #250. RF

References

1. John Sevic, "An Investigation of Nonlinear Analysis Methods for Simulation of Digital Wireless Communication Systems," CAD Design Methodol-

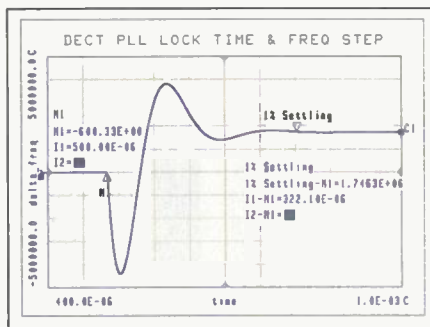


Figure 12. Simulation of the PLL's frequency-versus-time in response to one step in the divide-by-N block's value of N.

ogy for Commercial Applications Workshop, 1995 IEEE MTT-S International Microwave Symposium.

2. Dan Pleasant, "Designing Circuits for Wireless Applications," Hewlett Packard Wireless Communications Design Seminar, 1995.

3. Albert Franceschino, "Phase Locked Loop Primer and Application of Digital European Cordless Phone," *Applied Microwaves & Wireless*, 1995.

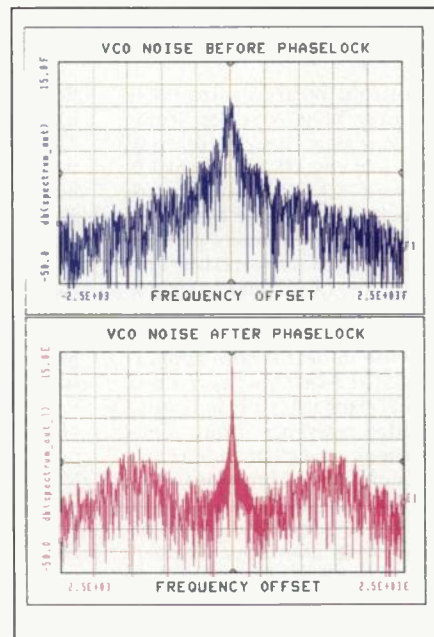





Figure 13. Noise spectrum of a VCO with and without phase lock (using a different PLL without a divide-by-N block).



Microwave ferrite devices for modern telecommunication systems



AEROTEK COMPANY LIMITED
1756 SOI SUKHUMVIT 52, SUKHUMVIT RD.,
BANGJARK
PRAKANONG, BANGKOK 10250, THAILAND
TEL: +66 2 311-4448, 311-6783-5, 322-5035
FAX: +66 2 322-5034



ISOLATORS CIRCULATORS

- Top performance
- Attractive prices & discounts
- Fast delivery
- From 400 MHz to 20 GHz
- Drop-in and Coaxial
- Four port version
- Various types of connectors
- Standard & Custom Designs
- OEM and Joint Ventures
- Import duty exemption in many countries

Call us or our representatives in your area for product updates and information.

EUROPE: MATECH ELECTRONIQUES, France Fax: +33 1 45695197
MICROELIT S.P.A., Italy Tel: +39 2 4817900 Fax: +39 2 4813594
TELEMETER ELECTRONIC, Germany Tel: +49 906 706 930 Fax: +49 906 21706
WESSEX ELECTRONICS, U.K. Tel: +44 117 957 1404 Fax: +44 117 957 3843

ASIA-PACIFIC: HINDITRON SERVICES, India Tel: +91 80 3340068 Fax: +91 80 3345022
NELABA PTY. LTD., Australia Tel: +61 2 759 3982 Fax: +61 2 759 2667

Network Analyzers

Anritsu Wiltron introduces the new 54000A Series Scalar Measurement Systems offering very low cost RF models to 1.0, 2.0 and 3.0 GHz. Microwave models are available to 8.6 and 20 GHz. The analyzers perform traditional transmission and return loss (SWR) measurements for manufacturing applications. A rugged housing allows reliable use in field service applications. The 54000A series has two inputs standard, with an optional third reference input. Measurement modes include transmission (dB), return loss (dB), SWR (linear SWR), and power (dBm). Dynamic range is -55 dBm to +16 dBm. Source resolution

is 10 kHz for RF models, 100 kHz for microwave models. Thirteen sets of front-panel setups and thirteen sets of trace memory can be stored in non-volatile instrument memory. The instrument can perform min/max hold, various cursor functions, and an automated compression test routine. A GPIB interface is standard. The 54000A offers: low harmonic sources, linearized YIG tuning for stable sweeps, 50 ohm and 75 ohm measurement systems, portable package, 10,000 hour MTBF. Starting price for the series is \$9,870

Anritsu Wiltron Co.
INFO/CARD #250



Surface Mount 900 MHz Filter

Kel-Com bandpass filter model number SB-900/200 has an insertion loss of less than 2.0 dB and VSWR of 1.5:1 over the passband of 800 to 1000 MHz. A 1.0 dB per MHz flatness is also specified over the passband. Minimum



stopband rejection is 20 dB at 1170 MHz and 45 dB from DC to 605 MHz. Ultimate rejection is 70 dB from 1969 to 2184 MHz. Outline dimensions are 1.10 x 0.60 x 0.27 with plated through holes for surface mounting.

Kel-Com
INFO/CARD #249

Quick Disconnect RF Connectors

A new line of quick-disconnect RF connectors for sputtering, test, and communications equipment requiring a high integrity connection with fast on/off capability is being introduced by Tru-Connect-



tor. The connectors mate reliably without bayonets, screws or tools. They are available in three types: QDL corresponding to an LC connector, QDS which has the same electrical properties as C and SC types, and QDM which is compatible with BNC and TNC connectors. Featuring positive locking mechanisms employing spring-loaded sleeves on the male that are drawn back to let self-contained balls "click" into grooves on the corresponding females and then slide forward, Tru-Connector Quick Disconnect RF Connectors can be supplied in straight-through and right angle designs. In-between series adapter are also available.

Tru-Connector Corp.
INFO/CARD #248

5 Watt Broadband Amp

Model 5S1G4 from Amplifier Research is an all solid-state broadband microwave amplifier providing 5 watts minimum power over two octaves, from 1 to 4.2 GHz. The full bandwidth is instantly available without band-switching or tuning and permits sweep tests that would typically require two or more amplifiers to cover the same frequency range. The 5S1G4 is rated 5 W (minimum), measured at the output connector. It can be used in test applications which demand no less than 5 watts of RF power over the full bandwidth. An input attenuator with a linearizing circuit results in uniform gain adjustment over a 10 dB (minimum) range. Typical flatness is ± 1.0 dB. Designed to operate Class A, the Model 5S1G4 uses GaAs-FET amplification stages, resulting in delivery of approxi-




mately 99 percent of output power at the fundamental or carrier frequency and very little output power in the form of harmonic or other noise content. Maximum harmonic distortion is -20 dBc at 3.0 W IP3 is typically 43 dBm. Price is \$7,500.

Amplifier Research
INFO/CARD #247

Dual Current-Feedback Op Amps

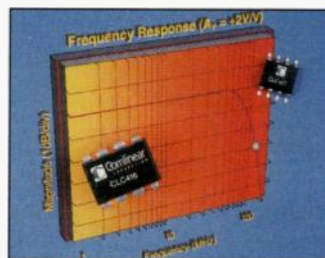Comlinear Corporation has announced the CLC416 and CLC417 dual high-speed current-feedback operational amplifiers. Priced at \$2.39 in 1000 piece quantities, the CLC416 and CLC417 have been designed to complement their single-version siblings (the CLC405 and



CLC407). The dual amplifiers offer 110 MHz small-signal bandwidths, very high 6 M Ω , very low 100 nA non-inverting input single bias currents, high 60 mA output current drive and very low quiescent current of 3.9 mA per amplifier. Differential phase is 0.03° for both amplifiers; differential gain is 0.01% for the CLC416, and 0.03% for the CLC417. The CLC417 provides internal feedback and gain setting resistors for ± 1 and ± 2 V/V gain selections. The dual amplifiers come in an eight-pin package with standard dual pinouts.

Comlinear Corporation
INFO/CARD #246

EMI FILTERS

EMI Filter & Seal

EESeal™ EMI filters and transient suppressors are installed simply by pushing the EESeal over the tips of the pins of the connector to be protected. Made of resilient silicone rubber, these filters easily conform to connectors, even if they have misaligned pins. Filters can be made to custom specs, and seals are available for virtually every connector type.

Metatech Corp.
INFO/CARD #245

Surface Mount EMI Filters

The NFM60R series is an EIA standard 1206 size version of the NFM61R. Its large rated current (6A) and low voltage drop due to small DC resistance (typ. 3 - 4 mΩ) are suitable for DC power line use. The feedthrough capacitor provides excellent high-frequency characteristics. Both flow and reflow soldering methods can be used with the series.

Murata North America
INFO/CARD #244

EMI Filters for Video

The ZJSM series of surface-mount EMI filters from TDK are matched to 75 ohms and have flat passband characteristics, making them well suited to filtering applications for video lines. The series uses high-Q choke coils, obtaining sharp cutoff characteristics and high attenuation through 1000 MHz. Cutoff frequencies of 15, 25, 100, 150, and 220 MHz are available.

TDK Corp. of America
INFO/CARD #243

1500 V_{rms} Isolation

Even with their small footprint and low profile, Coilcraft's new CMB Series of surface mount filters are rated at 1500 V_{rms} isolation between windings. Four models with current ratings from 20 to 80 mA and inductances from 28 to 450 μH are available. Common mode noise attenuation for the 80 mA parts is greater than 20 dB from 6 to 50 MHz. The CMB filters measure just 7.0 × 9.5 × 5.3 mm and cost \$2.95 each in 1k quantities.

Coilcraft
INFO/CARD #242

DISCRETE COMPONENTS

Helical Chip Inductors

The GLY series is composed of inductors measuring 1.6 × 0.8 × 0.8 mm (0603 size). The inductor is made by laser cutting a helix in

Squash EMI.

[literally]



Convert your connector to a filter connector in just seconds.

If compliance with electromagnetic emissions and immunity mandates by the FCC, EC, or your customers has you bent out of shape, your problems may




be solved quickly, easily, and cost-effectively

with an EESeal™ EMI FilterSeal.

Our EESeal™ FilterSeals turn any ordinary connector into a filtered connector in seconds without any special tools. There's no rewiring to do and you don't even need to open your box.


Made of resilient silicone rubber, EESeal™ FilterSeals

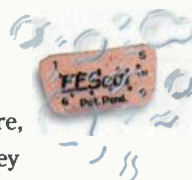can take tremendous physical abuse. Best of all, you'll be the only one who knows they're there, because they don't change the look or feel of your product.



In a rush? We offer rapid prototyping to your custom specs. Don't leave that FCC or EC compliance test without a demonstrated **practical fix!**

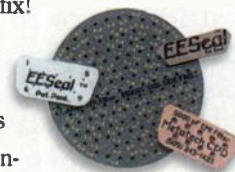To get EESeal™ FilterSeals in your connectors, call us



today at (505) 243-1423 or by fax at (505) 243-9772.

Metatech

Commercial Products Division


2309 Renard Place S.E., Suite 401, Albuquerque, New Mexico 87106

© 1985 Metatech Corp. Commercial Products Division *Patent Pending

NEW PTI OSCILLATORS

Prototype
Quantities
In Stock

Competitive
Pricing

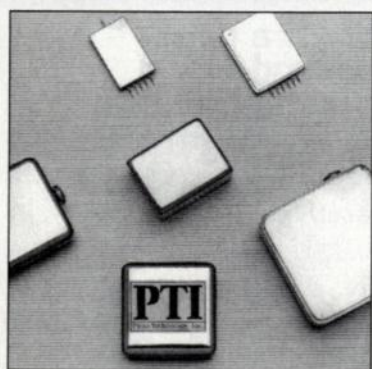

Now you can get selected models of PTI crystal oscillators from stock.

OCXOs for ultra-high stability applications at 10 MHz and TCXOs for high stability applications at 10 MHz or 20 MHz. Other frequencies available on special order.


Call or fax us today with your specs for a prompt response.

Ph (407) 298-2000
Fax (407) 293-2979



2525 Shader Road • Orlando, Florida 32804

INFO/CARD 38

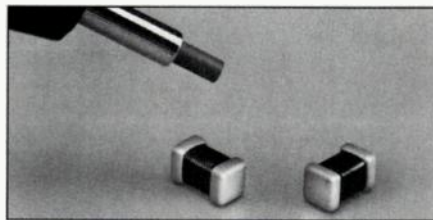

copper deposited on an alumina core. The terminals are nickel plated with a solder coat. The 17 models in the GLY series range in inductance from 2.2 nH to 47 nH. Standard tolerance is ± 5 percent. Self resonant frequency is as high as 3200 MHz. Unit price is \$0.41 for a single reel.

Sprague-Goodman Electronics, Inc.
INFO/CARD #241

Chip Capacitors

M-pulse Microwave announces a new family of chip capacitors packaged in Micro SMTTM packages. The devices exhibit low loss through 18 GHz. They are available in capacitances of 0.5 to 600 pF and standoff voltages ranging from 10 to 100 V. The M-pulse capacitors are available in two sizes: Ms - 0.012 x 0.028 inches (0301) and M24 - 0.04 x 0.02 inches (0402).

M-pulse Microwave
INFO/CARD #240

SEMICONDUCTORS

Dual ADC for DBS

The AD9066 is a dual high-speed, low-cost (\$4.59 in thousands) analog-to-digital converter (ADC) expressly designed for the direct broadcast satellite (DBS) market. It integrates a pair of matched 6-bit converters, each with a 60 Msps sampling speed, required for digitizing high data-rate I and Q signals. The AD9066 draws 400 mW from a single +5 V supply, and is packaged in a 28 lead SOIC.

Analog Devices
INFO/CARD #239

Transmitter Encoder

EXEL Microelectronics has announced their "code hopping", or "rolling code" transmitter encoder, the XL106. The XL106 Transmitter Encoder incorporates a 56-bit transmission code, with 24 fixed and 32 code-hopping bits. The XL106 can be used to control up to five different receivers and provide seven separate functions to a single receiver. The chip operates from 2.7 to 6.3 V, with maximum standby current of 50 nA. EXEL's XL106 Keeloq Transmitter Encoder is priced at \$1.20 in 10k quantities.

EXEL Microelectronics
INFO/CARD #238

I/Q Modulator & Upconverter

The UPC8104GR I/Q modulator with upconverter was developed for use in 900 MHz to 1.9 GHz applications. The chip can be driven by supply voltages of 2.7 to 5.5 V. The chip operates with I/Q signal from DC to 10



MHz modulating a 100 to 400 MHz signal which is then upconverted to frequencies in the range of 900 to 2,500 MHz. Typical power consumption is 28 mA at 3 V. The UPC8104GR includes an internal 90° phase shifter and ports for an external IF filter.

California Eastern Laboratories
INFO/CARD #237

900 MHz SOT-23 Bipolar Transistor

Hewlett-Packard has introduced its lowest-cost, 900 MHz silicon bipolar transistor, the AT-415 series, in the SOT-23 surface mount package. The AT-41533 features a 1 dB noise figure at 900 MHz and power output at 1 dB gain compression of +14.5 dBm (at 5 V, 25 mA). The transistor is also characterized for operation at 2.7 and 8 V. The AT-41533 is \$0.27 in quantities of 50,000 to 99,999.

Hewlett-Packard Co.
INFO/CARD #236

200 W Power Transistors

Advanced Power Technology's new 200 W RF power transistors for narrowband push-pull RF power amplifiers are now available from Richardson Electronics. The ARF442 and ARF443 comprise a symmetric pair of RF power transistors with a combined output power of 400 W when operating at 100 V and 13.56 MHz. Each device has minimum gain of 20 dB and 65 percent efficiency.

Richardson Electronics, Ltd.
INFO/CARD #235

SIGNAL SOURCES

DDS Module

Novatech Instruments introduces the Model DDS4m direct digital synthesizer (DDS) module. The DDS4m is a low cost, 34 MHz signal source packaged on a 3.5 x 4.5 inch circuit board. The DDS4m simultaneously outputs a precise Sinewave and an accurate TTL clock signal. The output frequency is programmable from 1 Hz up to a maximum of 34 MHz in steps as small as 0.02 Hz. The DDS4m is priced at \$395 each.

Novatech Instruments, Inc.
INFO/CARD #234

C Band Synthesizer

Communication Techniques' ISS-2000 series is a C band synthesizer designed for satellite communications. The synthesizers cover the C band (in bands) with standard tuning ranges

available from 12 percent of center frequency to 800 MHz maximum. Price is \$995 each in 100 piece quantities.

Communications Techniques, Inc.
INFO/CARD #233

4-Pin VCXO Line

Oak Frequency Control Group's 794 VCXO, available from 1 to 50 MHz, is housed in an industry standard 4-pin DIP. The internal construction consists of minimal parts count and an OFC-manufactured quartz crystal. Tuning range is greater than ± 100 ppm (0.5 to 4.5 VDC) with temperature stability of ± 24 ppm from 0 to +70 °C. Pricing for the 794 at the 1000-piece level is \$15.00 to \$25.00.

Oak Frequency Control Group
INFO/CARD #232

EMI-Reducing Clock Generators

A series of products that can reduce electromagnetic interference by up to 20 dB has been introduced by International Microcircuits. There are three product groups in the series: spectrum spread clock generators (SSCG), spectrum spread modulator generators (SSMG), and spectrum spread oscillator replacements (SSOR). IMI's SSCG and SSMG are \$3.15 at the 1,000 piece quantity, and the SSOR is \$12 in small quantities.

International Microcircuits, Inc.
INFO/CARD #231

SIGNAL PROCESSING COMPONENTS

Filters

The DMT Division of Jay-El Products has developed a band-reject filter providing out-of-band insertion loss of less than 1 dB and out of band VSWR of 1.5:1. Center frequencies from 500 to 900 MHz are available. Also offered are bandpass filters with center frequencies from 450 to 650 MHz (LB version) and 650 to 860 MHz (HB version). These filters have passband widths typically from 15 to 20 MHz and insertion loss of 3.5 to 4.5 dB.

DMT
INFO/CARD #230

0° Power Splitter

Mini-Circuits has introduced a low cost, 2-way, 0°, 50 ohm power splitter, model ZN2PD - 1900, with SMA connectors, designed for wireless applications in the 1600 - 1900 MHz PCN band. The unit performs with typical isolation of 30 dB, typical phase unbalance of 0.2° and typical amplitude unbalance of 0.02 dB. Typical insertion loss is 0.18 dB, and typical VSWR is 1.08:1. Price is \$69.95 each in quantities of 1 to 9.

Mini-Circuits
INFO/CARD #229

High Level Mixer

MITEQ's TIM0206HC2 is a high level (IP3 = +26 dBm) Schottky diode mixer developed to provide source- and load-VSWR-independent performance over the RF and LO band of 2 to 6 GHz with IF coverage from DC to 2 GHz. The mixer typically has RF and LO input VSWR of 1.25:1, and therefore is compatible with termination of any system filters without phase or amplitude ripples.

MITEQ
INFO/CARD #228

4-Way Power Combiner/Divider

RF Power Components has developed a drop-in 4-way power divider/combiner that provides high isolation and low insertion loss from 180 to 300 MHz. Model RFP-4060 can easily handle 200 W CW with less than 0.5 dB total insertion loss. Isolation is ≥ 20 dB and the device measures $2.5 \times 0.5 \times 0.02$ inches. Model RFP-4060 is priced under \$99.00 each in 1,000 piece quantities.

RF Power Components, Inc.
INFO/CARD #227


8x8 Butler Matrix

Anaren's model 560014 is an 8x8 Butler matrix operating from 750 to 950 MHz. Minimum isolation is 20 dB, maximum insertion loss is 1.10 dB and maximum VSWR is 1.25:1. Maximum amplitude balance and phase balance is specified at ± 0.80 dB and 7 degrees, respectively. Safe power handling in 100 W average CW. The caseless laminated package measures $5.50 \times 3.30 \times 0.19$ inches, not including standard SMA connectors.

Anaren Microwave, Inc.
INFO/CARD #226

5 kW UHF Bandpass Filter

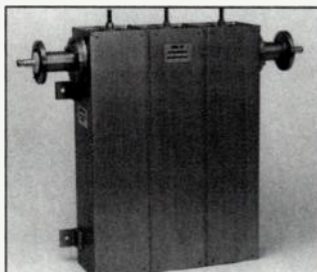Bandpass filter, model 11050-26 is used at the UHF transmitter output, UHF channel 26, to filter out-of-band spurious emissions. This model is available for any channel in the UHF band. The



filter handles 5 kW of video power and 500 W audio power. Passband insertion loss is less than 0.35 dB across the 6 MHz NTSC channel.

Microwave Filter Company
INFO/CARD #225

CABLES & CONNECTORS

Cable Assemblies

MICRO-COAX has introduced the UFB-311A, a UTIFLEX™ flexible microwave cable assembly with insertion loss of 0.20



dB/ft at 18 GHz. The cable assemblies have a power handling capacity of 490 W CW at 5 GHz, a dynamic bend radius of 4.75 inches, RF leakage of -100 dB at 1 GHz, and an operating temperature range of -65 to +165 °C.

MICRO-COAX
INFO/CARD #224

Jumper Cables

Times Microwave Systems announces jumpers offering both low loss and high flexibility. These cable assemblies provide greater than 100 dB shielding effectiveness and have a flame retardant and abrasion resistant jacket. The connectors used on the assemblies are silver plated, with gold plated center pins.

NEW ►► SMV 41



EMI MEASURING RECEIVER

With the frequency coverage of 9 kHz... 1 GHz the SMV 41 measuring receiver meets all specifications for EMI-measurements of CISPR or VDE 0876.

Manually operated, battery powered, measuring receiver.

Self contained automatic measurement receiver.

Fully IEEE remote controlled system measurement receiver.

Full frequency coverage, 9 kHz ... 1 GHz, enables all commercial interference measurement specifications to be met.

Multiple measured value and spectrumrepresentation on LC-graphic display

Memory card for ease of data- and software exchange

Portable (14kg, 18 liters), measurements of CISPR and VDE standards.

Built-in Battery Pack and Optical Serial Interfaces allows complete electrical isolation from mains and accessories.


Comprehensive input and output functions with memory card and digital interfaces

MEB

Messelektronik Berlin

Landsberger Allee 399
D-12681 Berlin
Tel.: (+49.30) 9392 2135
Fax: (+49.30) 9392 2134

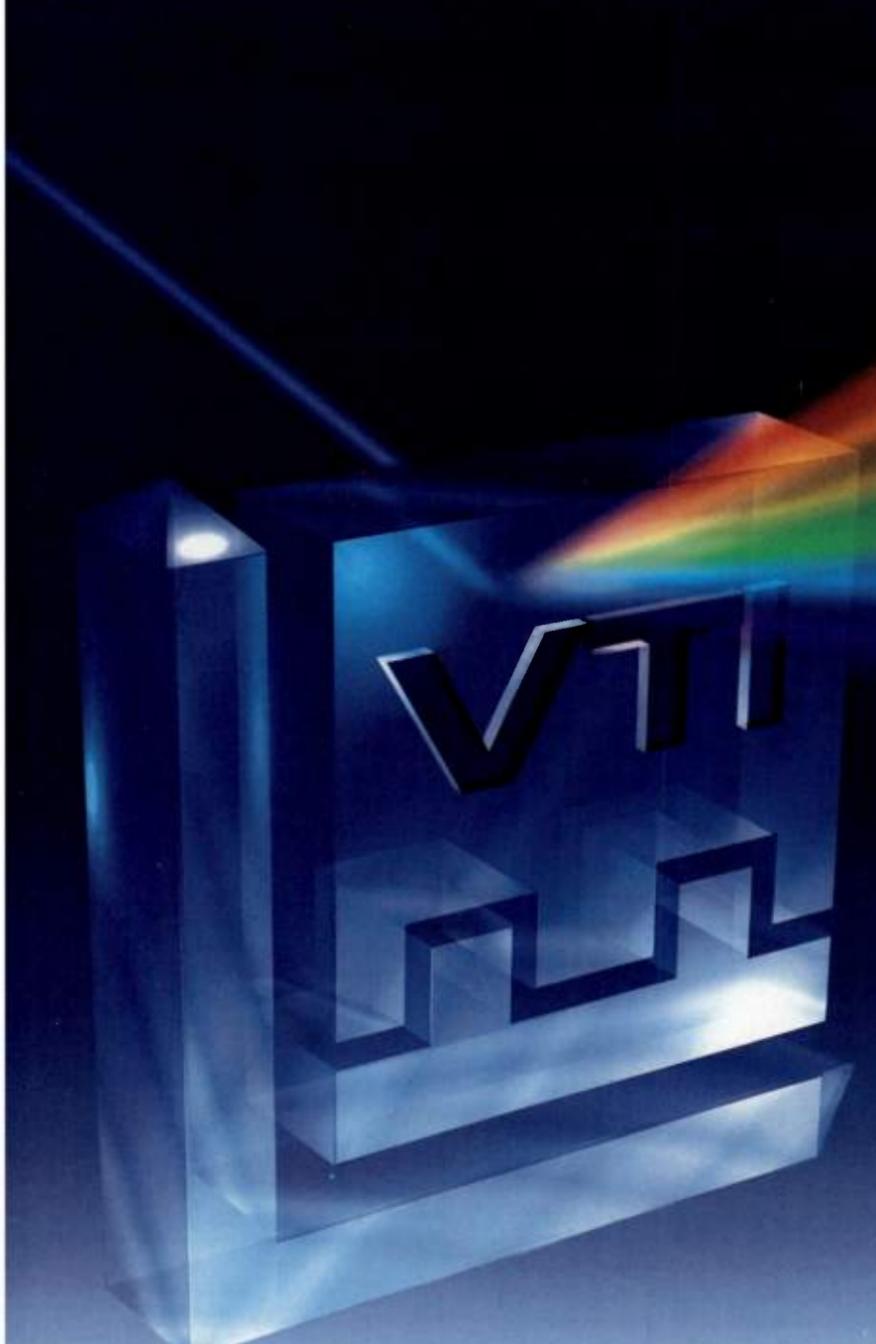for more details contact:
Antenna Research Ass. Inc.
Beltsville MD
Phone 301 937 8888
Fax 301 937 2796



**THE
MOST
EXCITING
EVENT IN
RECENT
OSCILLATOR
HISTORY
HAS JUST
CRYSTALLIZED**

Vectron Technologies, Inc. (VTI)

is born out of the acquisition of the Frequency Control Products division of the world's leading Telecommunications Company. With over 40 years of experience in crystal and SAW product development, Vectron Technologies, Inc. joins Vectron Laboratories, and Oscillatek, leaders in precision crystal oscillators, in providing the broadest range of frequency control products in the world.

This new leader in frequency control products brings you competitively priced, high performance, state-of-the-art clock and voltage-controlled oscillators, SAW filters, and clock recovery and data retiming units for telecommunications and data communications applications.

For more information, call Vectron Technologies, Inc. (VTI) at: 1-800-NEED-FCP



VECTRON
TECHNOLOGIES
INCORPORATED
267 Lowell Road, Hudson, NH 03051
TEL: (603) 598-0070 FAX: (603) 598-0075
A **DOVER** TECHNOLOGIES COMPANY

Connector types available are type N plug, right angle plug and bulkhead jack (7/16 DIN connectors available soon). A typical NM-NM three-foot assembly has a price of \$121.00.

Times Microwave Systems
INFO/CARD #223

F Connectors

The AMP® sealed F-connector offers enhanced performance up to 1 GHz and is designed to meet the requirements of Bellcore TA-NWT-001503 (4.3 and 4.4) and SCTE specifications. Nominal connector impedance is 75 Ω with an operating temperature of -40 to +115 °F.

AMP Incorporated
INFO/CARD #222

TOOLS, MATERIALS & MANUFACTURING

Space Simulation Chamber

The Space Simulation Thermal Chamber (SSTC) from Environmental Stress Systems allows stress testing of RF, microwave and wireless components in pressures ranging from 1 atm to 10^{-6} torr and temperatures from -99 to +200 °C. The system can accommodate components up to 12 x 24 x 8 inches. The system is priced from \$19,950.

Environmental Stress Systems, Inc.
INFO/CARD #221

Radar Absorber

Cuming Corporation's flat sheet radar absorbers are now available with a pressure sensitive adhesive backing for fast and easy installation. The C-RAM product line covers the entire microwave frequency range.

Cuming Corp.
INFO/CARD #220

AMPLIFIERS

Receive Amplifier

AML announces the availability of model R100, a low noise dual diversity receive amplifier assembly. Integral bandpass filters are provided in each of the diversity receive paths. Gain is adjustable from -10 to +16 dB. Maximum noise figure is 3 dB 16 dB gain. The unit operates on a 26 VDC nominal supply and features a self check function.

AML Communications
INFO/CARD #219

SDLVA

Model SDLVA-0120-70 (0.1 to 2.0 GHz) and SDLVA-06135 (600 MHz to 1.35 GHz) are DC-coupled successive detection log video amplifiers (SDLVAs). Specifications include 65/70 dB dynamic range, TSS \leq -67 (20 MHz

video BW), 25 mV/dB log slope, ± 1.0 dB log accuracy, rise time \leq 20 nsec, fall time \leq 25 nsec, and delay times of 8 nsec at -10 dBm limited IF output. These SDLVAs measure 2 x 1.75 x 0.4 inches.

Planar Monolithics Industries, Inc.
INFO/CARD #218


Class A Amplifier

Densitron Microwave has created a new range of Class A linear amplifiers, specifically designed for intermodulation testing applications at PCN/DCS/PCS frequencies. The amplifiers are available in either rack-mounted or modular configurations with output powers of 50 or 80 W covering the 1800 to 1900 MHz band.

Densitron Microwave
INFO/CARD #217

800 - 2450 MHz Amp

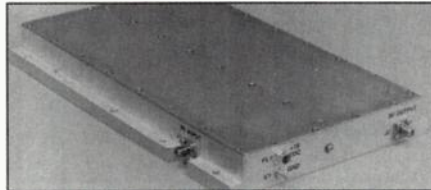Comtech Microwave products has introduced the AM88258-10 a Class A linear




amplifier operating over the full 800 to 2450 MHz frequency range. Power output is 10 W at the 1 dB compression point. Operating voltage is +15 VDC at 7 A, and size is 5.9 x 9.4 x 1.1 inches.

Comtech Microwave Products Corp.
Power Systems Technology Div.
INFO/CARD #216

TEST EQUIPMENT

Noise Source

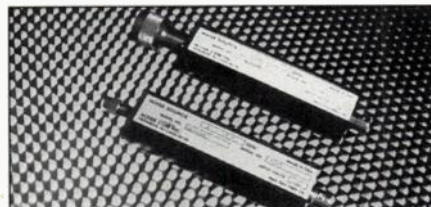Noise Com introduces the NC 346 V, a broadband noise source covering the entire 100 MHz to 65 GHz range. The NC 346 V uses V-male connectors and operates from



standard +28 V noise figure meter power supply. It has low VSWR, good temperature, and voltage stability. Output ENR is from 10 to 17 dB.

Noise Com, Inc.
INFO/CARD #215

Cellular Diagnostics

The CES-1000 cellular system activity moni-

VTI VECTRON TECHNOLOGIES INCORPORATED

FREQUENCY CONTROL PRODUCTS

Leadless SMD Clock

C-Type

1-75 MHz

- TTL or CMOS
- Ultra Low Profile
- Tri-State Output

VCXO

S-Type

1-52 MHz

- TTL or CMOS
- Surface Mount or Thru-Hole
- Miniaturized Ceramic 6-Pin DIP

Voltage Controlled SAW Oscillator

VC0600

155-622 MHz

- 10K ECL Compatible
- Surface Mount
- For High Speed PLL's

Timing Recovery Unit

TRU050

1-52 MHz

- User Configurable PLL
- Surface Mount or Thru-Hole
- Ideal for Frequency Translation and Clock Recovery

SAW-Based Timing Recovery Unit

TRU600


124-622 MHz

- 100K ECL Compatible
- Surface Mount
- Ideal for SONET/SDH and ATM applications

VTI VECTRON
TECHNOLOGIES
INCORPORATED

267 Lowell Road, Hudson, NH 03051
TEL: (603) 598-0070 FAX: (603) 598-0075

RETURN LOSS BRIDGES

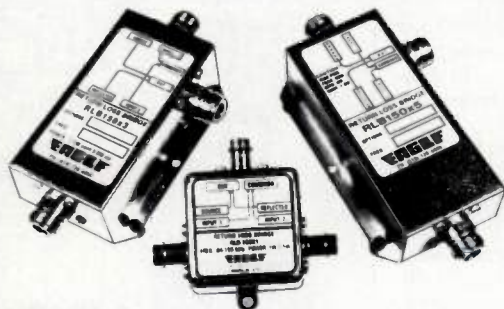

FEATURES:

5 watt power
High directivity
RF reflected port
Replaceable pins
Internal reference
Rugged construction

Return loss bridges from Eagle cover from .04 MHz to 3.0 GHz. A robust five watt power rating, unmatched in the industry, allows for versatile measurements. Optional replaceable center pins allow quick and economical repair of damaged connectors. Why pay more for bridges with fewer features than EAGLE?

FREE APPLICATION NOTE: High Performance VSWR Measurements

Models Available				
NUMBER	FREQ RANGE	DIRECT	O/S Ratio	PRICE
RLB150B1	.04-150 MHz	>45 dB	<0.5 dB	\$279.00
RLB150N3B	5-1000 MHz	>45 dB	<0.5 dB	\$389.00
RLB150N5A	5-3000 MHz	>40 dB	<1.0 dB	\$595.00

EAGLE

VOICE: (520) 204-2597
FAX: (520) 204-2568
P O Box 4010 Sedona, AZ, 86340

INFO/CARD 42

HF POWER AMPLIFIERS

HIGH RELIABILITY, COMMERCIAL QUALITY



◆ 1.8 to 30 MHz
◆ 1500 to 10,000 Watts

HENRY HF Power Amplifiers have been the reliability standard for 30 years. Thousands are in use at commercial, government, and military installations around the world.

If you require trouble-free, 24-hour-per-day, year-round operation, call or write today for prices and specifications.

TOLL-FREE (800) 877-7979

HENRY RADIO



2050 South Bundy Drive
Los Angeles, CA 90025

Phone (310) 820-1234
FAX 310-826-7790

INFO/CARD 43

tor from Cellular Evaluation Systems displays and updates overhead message information in real time for an AMPS connection. The CES-1000 is a serial data interface used to communicate between a computer's 9-pin serial port to an OKI (900, 910, 1145 or 1150) or AT&T (3710, 3730 or 3760) cellular phone. The included software displays and logs RSSI, follows handoffs and decodes DTMF tones as well as controlling the handheld phone.

Cellular Evaluation Systems
INFO/CARD #214

Communications Test Set

A new hardware option is available for the Wavetek STABLOCK 4032 communications test set. The new option allows testing of DCS



1800 and DCS 1900 radiophones or measurements on cordless DECT telephones. The 2.3 GHz option is a fast mounted plug-in module. In addition to Go/NoGo testing, the STABLOCK 4032 can perform more complex tasks such as repair on defective mobiles.

Wavetek Corp.
INFO/CARD #213

Dielectric Constant Measurements

The Damaskos model 0501 cavity measures dielectric constant of low loss materials over the approximate octave of 2 to 4.5 GHz in a non-destructive manner. It is ideal for thin dielectric sheets ranging in thickness from a few mils to the order of 100 mils. The measurement is made on common analyzers under the instrument control and data processing of Damaskos' "CAVITY" software. Other bands are available.

Damaskos, Inc.
INFO/CARD #212


Digital-TV Signal Analyzer

A new option for the HP 89400 vector signal analyzer family allows the analyzer to characterize digital RF modulation. Targeted at designers of HDTV and other advanced TV systems, the analyzer's demodulator can be configured with a few keystrokes for 16QAM, 32QAM, 64QAM and 256QAM formats as well as the 8VSB (broadcast) and 16VSB (cable) formats. QPSK, BPSK, FSK and MSK formats allow analysis of other digital services. Option AYH for the HP 89400 series VNAs is available for \$2,500.


Hewlett-Packard Co.
INFO/CARD #211

September 1995

Traditional high-frequency design.

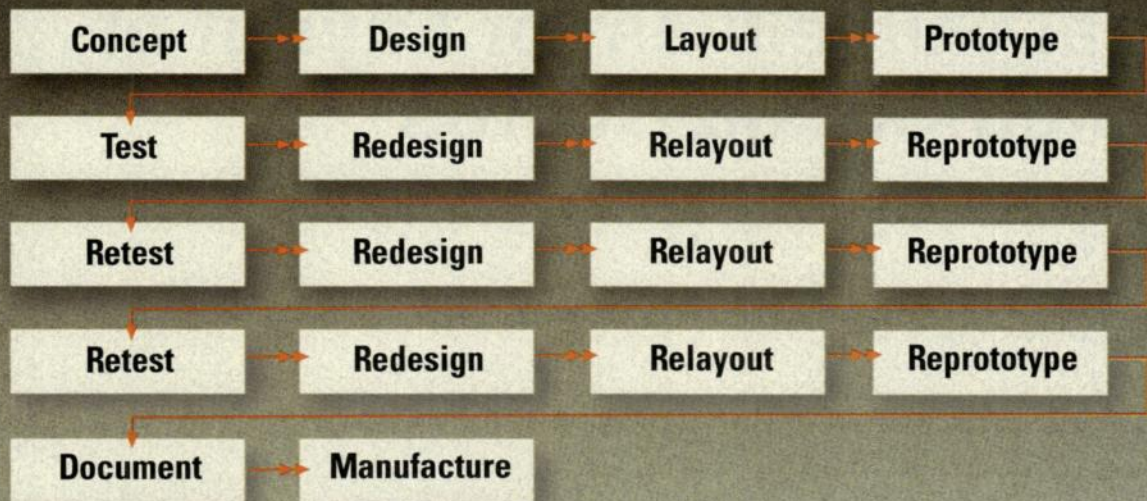

Sophisticated high-frequency design.

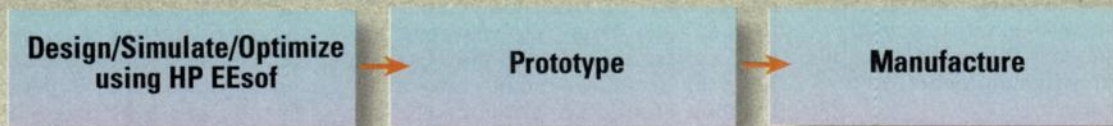

© 1994 Hewlett-Packard Company TMHPPE464

Simple, isn't it?

Designing RF and microwave circuits? Now you can increase the sophistication of these high-frequency designs. And make the

process easier at the same time. How? It's simple, really.




HP EEsof's Windows-compatible software lets you develop, simulate, and optimize circuit performance on your PC. You'll

spend less time testing, redesigning, and retesting your prototype.

You'll reduce design cost, and decrease your time to market.

Our integrated design solution offers schematic capture and links to layout, powerful linear and nonlinear frequency domain circuit simulators, and unparallel model accuracy.

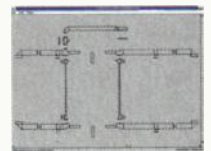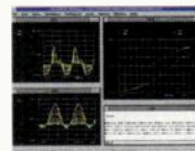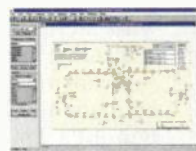With HP EEsof, easily analyze S-parameters, intermodulation distortion, mixer conversion efficiency—and much more—all on your PC.



To find out more about HP EEsof's complete line of PC- and workstation-based high-frequency simulation software, call 1-800-343-3763. We'll make your life a whole lot easier.

There is a better way.

**hp HEWLETT®
PACKARD**

INFO/CARD 44



Microsoft Windows is a registered trademark and Windows and the Windows logo are trademarks of Microsoft Corporation.

Initial Guidelines for Layout of Printed Circuit Boards

By Gary A. Breed
Editor

Although design engineers typically do not do final layout of p.c. boards, many do prototypes and most work with the CAD department to develop the best circuit implementation. This month's tutorial reviews some basic rules for layout of RF circuits on printed circuit boards, including considerations for high frequency performance, EMI, crosstalk, and grounding.

Printed circuit board assembly of electronic products has the purpose of achieving low cost, automated, repeatable manufacturing. The board also provides mechanical support for components. In RF circuits, the board can also become an integral part of the circuit's operation, using microstrip and stripline techniques. Accomplishing all of these tasks simultaneously is an engineering art. We will review a few rules that will help achieve successful designs.

General Layout Planning

Here a few rules of thumb for planning the initial layout of p.c. boards. They are not absolute rules, but they will provide a starting point for grouping the various functional blocks in a manner that avoids major problems.

Keep high power circuits away from sensitive circuits — Yes, this is as obvious as it seems, but there are some subtleties to watch for. The power amplifier of a transmitter will normally be positioned away from low level oscillator, amplifier and modulator stages, but we need to be sure that the DC lines follow the same rule, since they can be a path for RF to follow. Sometimes there are conflicting requirements. For example, a power amplifier stage may have an associated VSWR monitoring circuit. We might be able to put sampling circuits by the amplifier and locate the remaining circuitry elsewhere, but then we have the extra length of the interconnections to deal with. Being aware of this kind of problem at the beginning lets the engineer think out

the problem before the first trial layouts are made.

Avoid crosstalk problems — Crosstalk can take many forms. It can be a control signal getting into an RF signal and modulating it. It can be an outside effect coupled into a phase locked loop, causing unwanted modulation or instability. It can be an RF signal causing errors in monitoring circuits. The easiest solution is physical separation. More complex solutions include routing signals in shielded cables, through layers of a multi-layer board, localized shielding of affected circuits, or locating problem circuits off the board entirely. Whole books could be devoted to this problem area.

Avoid radiating layouts — If RF is not properly contained, it radiates (and any "antenna" receives signals as well as transmitting them). Certain physical structures radiate more readily than others. Long microstrip line sections, even if matched, will radiate. This is because the RF field is not perfectly contained between the conductor and the ground plane. Loops radiate with an efficiency proportional to the area enclosed. A loop can be formed with a cross-over connection in a path that otherwise is a properly-terminated transmission line. A loop can also be made by the combination of a component's leads and body. An often-overlooked area is the loop made between +DC and ground, which can enclose a very large area. Even if bypassed properly for RF, lower frequency radiation and pickup can occur if this rule is not followed.

Design compact circuits with short connections — "RF is where every component is simultaneously an R, L and C and there is no ground." This definition always gets a chuckle because it is true. One way to minimize its effect is to use short, direct connections that have the lowest losses, the least chance for mismatches, and low inductance. This is a rule that always has conflicts. The shortest path might violate one of the previous

rules, or might be physically impossible within the limits of p.c. board construction. When compromises are required, the additional path length needs compensation with transmission line techniques, or with extra care in its routing.

These few rules provide a starting point for board layout. Other engineers will have their favorite additional rules, based on experience with various types of circuits and performance demands.

Transmission Line Behavior

At radio frequencies, all printed circuit board traces have an effect on the behavior of the circuit. As engineers, we all know this, but in the pressure of getting a design finalized, this fundamental fact is often overlooked. As transmission lines, wide traces have a low characteristic impedance, narrow traces are high impedance. Short transmission line sections are inductive when they have higher impedance than the nominal circuit impedance, and they are capacitive when their impedance is lower. These are the characteristics that make microstrip circuits possible.

The magnitude of these effects is proportional to the dielectric constant ϵ_r of the board material. The phase velocity V_p of a signal is: $(c/\sqrt{\epsilon_{eff}})$, where c is the speed of light. Common G10/FR-4 has an ϵ_r of 4.8, which means that a wavelength (λ) is $1/\sqrt{4.8}$ or 0.46 as long as free space. At 1 GHz, λ is 30 cm in free space and just 13.8 cm on FR-4. A 2.5 cm (1-inch) trace on such a printed circuit board is 0.18λ , or 65 degrees, a very "long" distance in transmission line terms. Any variation in impedance between the trace and the impedance of the components it is connecting will result in a significant impedance mismatch, often resulting in reduced performance. Even at 100 MHz, the above 1-inch trace is still 0.018λ , which is 6.5 degrees electrical length, enough to degrade some circuits.



J-LEAD

J MIXERS UNPRECEDENTED IN VALUE.

\$4²⁵

All Ceramic 2 to 1900MHz from 1 (qty. 10-49)

JMS mixers mean unparalleled performance and reliability. Solder plated J leads provide improved reliability of the solder connection while significantly reducing thermal stress and leaching. All-welded internal construction withstands reflow temperatures up to 240°C for 5 minutes, and rugged construction enables JMS mixers to pass tough MIL-M-28837 shock and vibration tests. Additionally, the all-ceramic surface mount package has a cover pull strength of 20 pounds! Other quality features include 4.5 sigma repeatability unit-to-unit, automated assembly for low-cost and fast, guaranteed 1 week shipment, tape and reel availability plus a 5 year Ultra-Rel™ guarantee. If value is a must...specify JMS mixers from Mini-Circuits.

Mini-Circuits...we're redefining what VALUE is all about!

SPECIFICATIONS	MODEL	LO (dBm)	FREQUENCY ¹ (MHz) LO/RF IF	MIDBAND (dB, typ.)			Sea. (qty. 1-9)
				Conv. Loss	Isolation L-R L-I		
JMS-1	+7	2-500	DC-500	5.75	45 45		4.95
JMS-1LH	+10	2-500	DC-500	5.75	55 45		8.45
JMS-1MH	+13	2-500	DC-500	5.75	60 45		9.45
JMS-1H	+17	2-500	DC-500	5.90	50 50		11.45
JMS-2L	+3	800-1000	DC-200	7.0	24 20		7.45
JMS-2	+7	20-1000	DC-1000	7.0	50 47		7.45
JMS-2LH	+10	20-1000	DC-1000	6.5	48 35		9.45
JMS-2MH	+13	20-1000	DC-1000	7.0	50 47		10.45
JMS-2H	+17	20-1000	DC-1000	7.0	50 47		12.45
JMS-2W	+7	5-1200	DC-500	6.8	60 48		7.95
JMS-11X	+7	5-1900	5-1000	6.7	35 37		4.25*

Note: *10-49 qty.

 **Mini-Circuits®**

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661

For detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER • MICROWAVE PRODUCT DATA DIRECTORY • EEM • MINI-CIRCUITS® 740-pg. HANDBOOK.

CUSTOM PRODUCT NEEDS...Let Our Experience Work For You.

F 205 Rev Orig

INFO/CARD 45

Microstrip is intentionally used to make filters and matching networks, taking advantage of its transmission line properties. However, when we want "perfect" conductors, transmission lines are always present. For example, in high speed digital circuits the clock rate may be 66 MHz. To keep a good square wave shape, the harmonics (Fourier coefficients) should be undistorted up to at least five times that frequency, or 330 MHz. Our 1-inch p.c. board trace may be no problem at 66 MHz, but at 330 MHz, it will have a significant effect. Traces that make up a digital bus need to be matched in physical length to avoid timing problems, and they must be properly terminated. Digital signals have reflected waves just like RF signals, and those reflections can alter the shape of the desired square wave.

The behavior of microstrip line is well-documented (see the Bibliography), and this article is not meant to be a microstrip tutorial. However, microstrip techniques are integral to higher-frequency designs. These meth-

ods are so important that specialized printed circuit board materials are constantly being refined to enhance the performance of microstrip circuits. Low ϵ_r substrates with thin dielectric layers improve the dispersion and radiation performance of microstrip circuits. High dielectric constant ceramic substrates reduce the size of circuits, since signal wavelength is much shorter in these materials.


Power Circuits

The portions of the p.c. board circuitry that distribute DC power to the various components can be the source of problems if not properly designed. Bypass capacitors must be placed very close to the components' power pins to avoid making an L-C network of the wrong type. We want the shunt capacitance close to the component and the inductance on the side toward the power supply, since we always assume that the power supply has the lower impedance of the two. If the p.c. board trace or the component leads contribute a significant inductance

between the bypass capacitor and the component, the impedance of the capacitor is effectively raised, making it less effective. In extreme cases, the impedance transformation of the bypass circuit can render it completely ineffective, resulting in instability or oscillation, increased radiation from that part of the circuit, or conduction of RF into the power supply circuitry.

The power supply bus itself must be maintained at the lowest possible impedance. Wide conductors, frequent bypass capacitors, and embedding the bus between layers of a multi-layer board are all commonly-used techniques. All of these methods must be implemented in a manner consistent with microstrip or stripline behavior. Impedances of the traces should be calculated (or at least approximated), and the bypass capacitors must be of the optimum value and type for the frequency of operation. It should also be noted that most techniques that improve RF behavior will also improve the EMI performance of circuits. However, EMI can be a problem at lower

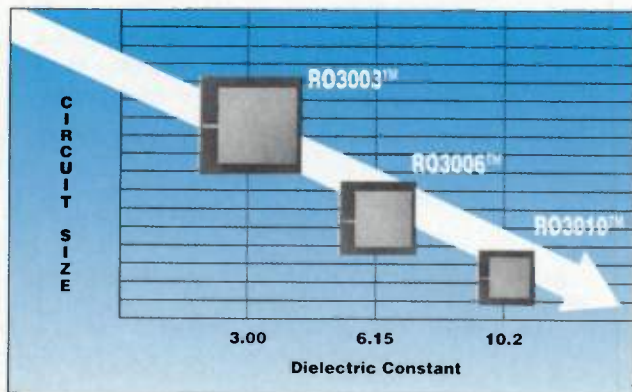Save space and money with the Rogers family of high frequency circuit board materials.



The new RO3000™ series provides low dissipation factors, low etch shrinkage, low Z axis expansion, and low Tck'. That's a lot of lows, and there's one more: the price.

As for performance, you can choose from a wide range of dielectric constants (3.0, 6.15, and 10.2) to optimize your designs. And you can mix and match these products, because every member of the family is mechanically compatible.

ROGERS

Microwave and Circuit Materials Division

ISO 9002 Registered

Rogers Corporation • 100 S. Roosevelt Avenue, Chandler, AZ 85226 • Tel: 602-961-1382 FAX: 602-961-4533
Rogers Japan Inc., Tokyo; Tel: +81-3-307-6430 FAX: +81-3-307-6319 • Rogers-Meldron, N.V., Gent, Belgium;
Tel: +32 9 235 36 11 FAX: +32 9 235 36 58 • RO3000, RO3003, RO3005, RO3010 are trademarks of Rogers Corporation

INFO/CARD 64

1,239,580 Filters

America's Filter Specialist
since 1956

0.1 Hz to 3000 MHz -

1,239,580 standard filter types ☐ Miniature and subminiature sizes ☐ Passive and active types ☐ Stock filters ☐ Gaussian, Butterworth, Chebyshev designs ☐ Call or write for free catalog today.

TTE®

TTE, Inc.
2251 Barry Avenue
Los Angeles, CA 90064
Fax (310) 445-2791
Tel (800) 776-7614

1,239,580
STANDARD
FILTER
DESIGNS

FREE CATALOG

INFO/CARD 65

You Can Look Through
All These Pages *or*
You Can Pick Up the Phone.

Let M-tron
provide the
best solution
to your next
crystal/oscillator
challenge with
our wide variety of
high-quality custom
and off-the-shelf
products.
We'll evaluate
your needs, give
technical assistance
and deliver on time,
all at a competitive
price.



Registered:
ISO 9001
EN 29001
BS 5750: Part 1

Call the

M-tron

Design Line
at

1-800-762-8800

*The quickest way
to get what you need.*

FREE CATALOGS



Call or write
for our catalogs
describing our line
of quartz crystals
and quartz crystal
oscillators in surface
mount and thru-hole
configurations.

M-tron
INDUSTRIES, INC.

P.O. Box 630, Yankton, SD 57078 USA
1-800-762-8800 • Fax: 605-665-1709

© 1995 M-tron Industries, Inc. All Rights Reserved

frequencies where RF concerns are minimal, and additional techniques brought to bear. In a circuit where both RF and EMI performance are being addressed, special attention must be given to both, as it is possible that methods for one can adversely affect the other (e.g., poor RF performance of a "standard" EMI filter above resonance).

Connections to the Board

Our final topic is another often-overlooked area: interconnections that bring signals, power and grounding to and from the board.

First, RF "ground" is somewhat indeterminate. An equipment case or the ground plane of a circuit board is not an infinite current sink of zero impedance! At DC this condition is

approximated, but certainly not at RF. Significant RF currents flow in all conducting surfaces considered to be ground, creating potential differences. Ground loops are the result of two separate ground paths creating a signal that is the difference in their currents. Depending on the nature of the equipment, these can be 50/60 Hz or harmonics, switching power supply frequencies, or RF.

Two ways to minimize the effects of ground currents are: 1) Minimize the number of different ground paths (ideally one — central grounding); and 2) Create the lowest impedance ground possible, which usually means a large surface area of high-conductivity material (copper or aluminum).

Besides the ground loop problems noted above, wires are often unshielded, making them more susceptible to pickup of RF. Routing these wires and cables close to the walls of the cabinet lowers impedances and reduces the area enclosed by the loops they create. Locating them away from cables or circuits with high level signals will further reduce the potential for problems. Proper bypassing and EMI filtering will normally eliminate any remaining problems.

Summary

Layout of a printed circuit board for reliable RF performance is no simple task. The number of potential problems is large, but by starting with these basic rules, you can develop a circuit that maintains good RF performance while meeting the requirements for large-scale manufacturing. *RF*

Bibliography

1. H.O. Granberg, "Good RF Construction Practices and Techniques," *RF Design*, Sep./Oct. 1980, p. 51.
2. R.L. Barron, W.J. Choe, "Manufacturing Considerations for the Design of RF Products," *RF Design*, Oct. 1993, p. 65.
3. T. Cummings, P. Edwards, "Designing With Ultraminiature SMT Semiconductor Packages," *RF Design*, Oct. 1993, p. 44.
4. A. Tam, "Principles of Microstrip Design," *RF Design*, June 1988, p. 29.
5. T. Cefalo, "Microstrip CAD Program," *RF Design*, Oct. 1990, p. 37.
6. J. Ness, J. Dougall, "Microstrip Filters for Lower Frequencies," *RF Design*, Jan. 1987, p. 52.
7. G. Matthaei, L. Young, E. Jones, *Microwave Filters, Impedance Matching Networks, and Coupling Structures*, Artech House 1980.
8. V. Greb, "Near-Field Coupling Between Signal Lines," *RF Design*, Sep. 1991, p. 65.
9. B. Cooperstein, "EMC Design Techniques for Printed Circuit Boards," *RF Design*, June 1991, p. 53.
10. M. Mardiguian, *Controlling Radiated Emissions by Design*, Van Nostrand Reinhold 1992.

FROM THE WORLD LEADER IN VARIABLE CAPACITORS

Johanson

PRODUCT INTEGRITY SINCE 1945

2 GHz
MINIATURE TRIMMER
CAPACITORS



Actual
Size


The 9401 series is an advanced development in miniature capacitors and features operation to 2 GHz and higher. They are ideal for applications in circuits where size and performance are critical.

- Capacitance Range:
.25 - .7 pF to 1.5 - 4.0 pF
- Q > 1000 @ 100 MHz
- Operating Temperature:
-20°C to +85°C
- Working Voltage: 250 VDC

Johanson Manufacturing Corporation
Rockaway Valley Road, Boonton, NJ 07005 USA
201-334-2676 Fax 201-334-2954

Electromagnetic Simulation

Has a New Star!

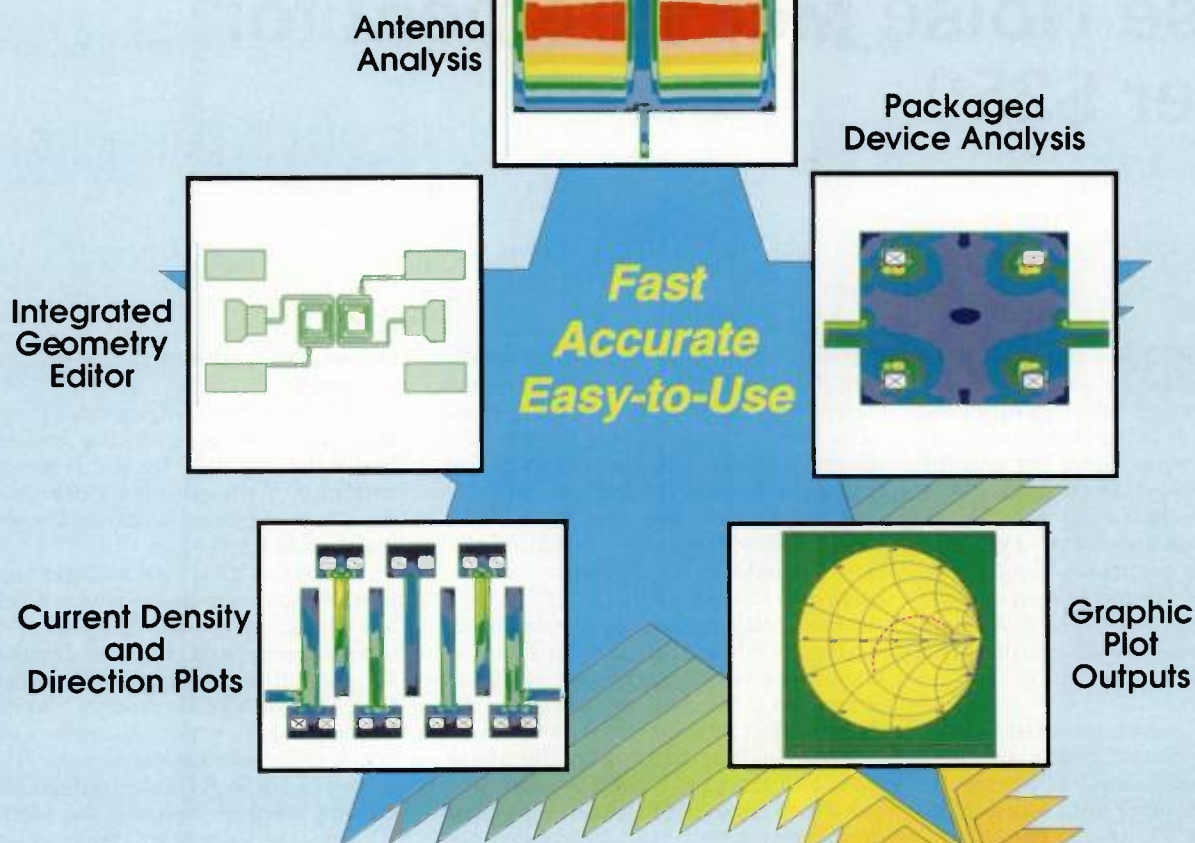

Microwave Explorer offers superior Electromagnetic Simulation in both open and packaged environments!

Compact Software's Microwave Explorer Electromagnetic Simulator provides superior simulation of EM coupling and radiation effects in RF and microwave circuits. Only Microwave Explorer allows designers to model both radiating structures (antennas) and packaged devices using a **single** EM simulation tool!

Microwave Explorer uses the Method of Moments technique to provide accurate 3D analysis of planar circuits in a fraction of the time associated with traditional 3D techniques. Advanced simulation techniques require less memory and CPU time than conventional implementations.

Electromagnetic analysis of complex structures has never been this fast or this easy! The integrated geometry editor includes GDS II import capability. To find out more about the unique capabilities of Microwave Explorer and to obtain the name of the Compact Software Sales Representative for your area, please contact:

North and South America

Compact Software
201 McLean Boulevard, Paterson, NJ 07504
Phone: 201-881-1200 • Fax: 201-881-8361

Asia-Pacific

Compact Asia-Pacific Sales Center
764 Dailey Avenue, San Jose, CA 95123
Phone: 408-362-0363 • Fax: 408-362-0507

Europe

Compact Software
@ Electronic Software Components GmbH
Alpenstrasse 20, D-85614, Kirchseeon, Germany
Phone: +49-8091-6845 • Fax: +49-8091-4804

INFO/CARD 49



Phase Noise Measurement for Under \$250

By W.A. Suter
Amplifonix, Inc.

It is difficult, if not impossible, to measure the close-in phase noise of wide-tuning, free-running, voltage controlled oscillators using direct spectrum analysis. The signal does not remain steady long enough to obtain a clean trace on the spectrum analyzer, with the result that phase noise closer than 100 kHz cannot be accurately measured. Even if external influences such as temperature changes, or electrical and mechanical noise are eliminated, the carrier drifts too fast.

One way to steady the carrier is to lock the oscillator in some way. It is possible to phase-lock one of two identical VCOs to the other with a crystal in the loop as in Figure 1. The signal which drives the "reference" oscillator is a baseband signal which is related to the frequency noise of the device under test (DUT). The locking system is equivalent to a black box with a volts-out vs. frequency-in transfer function.

A system as in Figure 1 was assembled. The signal from the DUT was mixed with the signal from the second oscillator (the "reference"), and an IF of 10 MHz was generated. This 10 MHz signal was then mixed again with a 10

MHz crystal oscillator and the resulting baseband signal used to drive the reference VCO so as to lock the system. The baseband signal was then amplified, digitized, and analyzed to derive the phase noise of the DUT.

The phase-locked loop bandwidth was made wide enough to create a stable phase-locked system for a large-modulation-sensitivity VCO. The method initially seemed to work well, but a number of problems became clear. The transfer function is offset-frequency dependent because of the filtering effect of the phase-locked loop – within the loop bandwidth the phase noise is suppressed by an amount which changes with frequency – and accurately correcting for this was not easy. White noise could be injected into the loop and the loop suppression characteristic measured. However, other problems with this method – such as preventing the system from locking at some harmonic of the crystal, preventing the reference from jumping from 10 MHz below to 10 MHz above the DUT, and the system's overall complexity – led to the setting aside of this method in favor of the delay line discriminator method, which proved to be very sim-

ple, stable, sufficient to the task, and inexpensive.

The delay line discriminator method is a wideband approach, the frequency being limited only by the frequency response of the power divider and/or the mixer. A block diagram of the setup is shown in Figure 2.

A single VCO is required. Its signal is split with an in-phase power divider; one signal drives the LO port of the mixer directly, and the other drives the RF port after passing through a delay line. The two signals produce a voltage at the IF port which depends on the phase difference between them. If the mixer is perfectly balanced and has infinite isolation between the LO and IF ports, the voltage will be negative V volts when they are in phase, zero when they are 90 degrees out of phase, and positive V volts when they are 180 degrees out of phase.

If the delay line length is set so that the two signals are 90 degrees apart (i.e. in "quadrature"), the signal at the IF port will be 0 volts, with an AC signal riding on it proportional to the frequency noise of the oscillator. This will be true regardless of the oscillator frequency. Hence the problem of the drift-

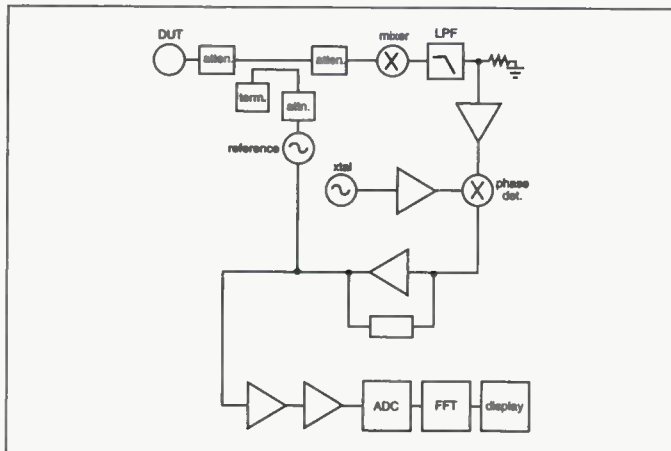


Figure 1. Block diagram of reference oscillator/downconversion phase noise measurement system.


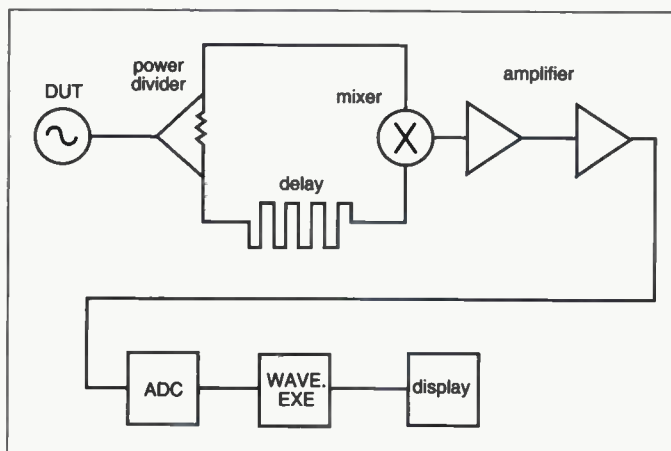


Figure 2. Block diagram of discriminator/delay line set-up for phase noise measurement.

VOLTAGE CONTROLLED OSCILLATORS

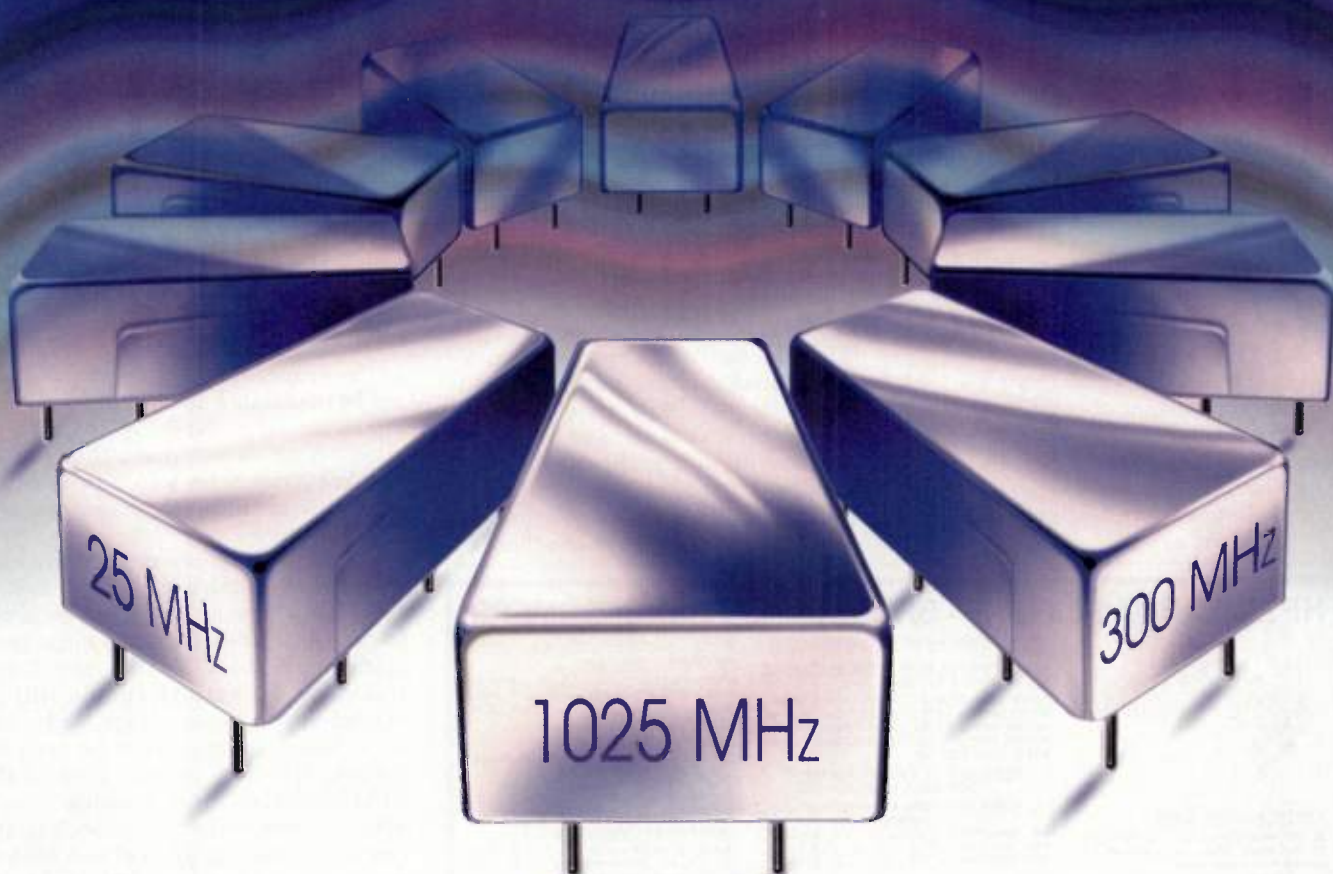

25 to 1025MHz (+7dBm output) From \$11⁹⁵ (5-49)

It's a fact! With Mini-Circuits new POS family of shielded, laser sealed voltage controlled oscillators, you pay less but get more... top notch quality, superior performance and value pricing.

Features include wide-band models with near octave bandwidth and linear tuning. Low SSB phase noise characterized at 100Hz to 1MHz offsets. Excellent harmonic suppression, typically more than 25dB. RF power output typically +7dBm, excellent for driving level 7 mixers. Miniature size, only 0.4 X 0.8 inch board space. Hermetically sealed and ruggedly constructed for tough environments. Best of all, Mini-Circuits high performance, highly reliable VCO's can be yours at value prices starting at only \$11.95 each (qty.5-49). To order from stock, call Mini-Circuits today.

Mini-Circuits...we're redefining what VALUE is all about!

DESIGNER'S KITS:

K-POS1 \$124.95 (contains 1ea. all models).

K-POS2 \$79.95(contains 1ea. all models except POS-75,-150,-300).

Model No.	Freq. Range (MHz) Min.	Phase Noise (dBc/Hz) SSB @10kHz Typ.	Harmonics (dBc) Typ.	Power 12V DC Current mA	Price (Qty.5-49) \$ ea.
POS-50	25-50	-110	-19	17	11.95
POS-75	37.5-75	-110	-27	17	11.95
POS-100	50-100	-107	-23	18	11.95
POS-150	75-150	-103	-23	18	11.95
POS-200	100-200	-102	-24	18	11.95
POS-300	150-280	-100	-30	18	13.95
POS-400	200-380	-98	-28	18	13.95
POS-535	300-525	-93	-26	18	13.95
POS-765	485-765	-85	-21	22	14.95
POS-1025	685-1025	-84	-23	22	16.95

Notes: Tuning voltage 1 to 16V required to cover freq. range.
Operating temperature range: -55°C to +85°C.

Mini-Circuits®

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661

For detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER • MICROWAVE PRODUCT DATA DIRECTORY • EEM • MINI-CIRCUITS' 740- pg. HANDBOOK.

CUSTOM PRODUCT NEEDS...Let Our Experience Work For You.

F 195 Rev A

ing carrier is eliminated.

This AC signal is amplified, digitized, and analyzed for its volts vs. frequency content, and the phase noise of the DUT calculated from this. The single side band phase noise is calculated from:

$$L(f_m) \frac{\text{dBc}}{\text{Hz}} = 20 \log(V_{\text{rms}}) \quad (1)$$

$$-20 \log(K_d) - 20 \log(f_m)$$

$$-10 \log(F_{\text{res}}) - 20 \log(V_{\text{gain}})$$

$$-3 \text{ dB}$$

where

V_{rms} = rms voltage at
offset frequency f_m
 f_m = the offset freq in Hz
 $K_d = 2\pi(T_d)(K_p)$ volts/radian
 T_d = delay line time delay
in seconds

K_p = volts/Hz constant of
the discriminator

V_{gain} = the voltage gain of the base
band amplifier

F_{res} = the frequency resolution of the
FFT routine

The ability of this system to convert frequency noise to voltage noise is dependent primarily on the length of the delay line. If the delay line is long, the rate of change of output voltage with change in input frequency will be large at the zero crossing point, and the system will be very sensitive to input frequency noise. Increasing the length of the delay line, however, also increases its loss, which reduces the RF port drive, which reduces the voltage available at the IF port. For a given mixer there is an optimum delay line loss which will give the correct signal levels at the mixer, and the most IF output for linear mixer operation.

The VCO

Since the oscillator's carrier frequency is eliminated at the mixer, the only limitation on the frequency of the VCO is that it be within the bandwidth of the power divider and/or the mixer. The delay line discriminator method is applicable to any oscillator frequency. The VCOs of interest here are those in

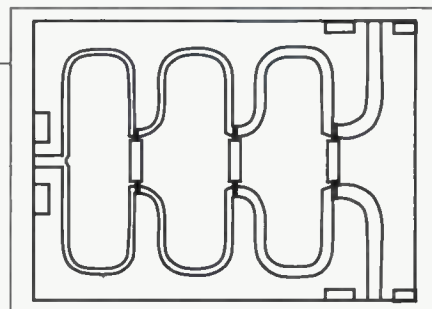


Figure 3. The power divider.

the 500 MHz to 3500 MHz range.

The power requirement of the VCO is that it drive the mixer sufficiently, although an RF amplifier may be used to boost the signal level. If an RF amplifier is used, it must be placed before the power divider and must be operated in its linear range. In this way, the amplifier's residual noise will be correlated out of the measurement at the mixer, and its own 1/f noise will not be modulated up onto the carrier. If it was placed in the delay line path (to allow longer delay lines), the amplifier's frequency noise would be indistinguishable from the frequency noise of the oscillator.

Since the VCOs of interest have high modulation sensitivities (5 MHz/V to 150 MHz/V), great care must be taken to prevent external voltage noise from getting onto the VCO tune line. Often this means a battery supply will be needed for the tune voltage, and a low noise potentiometer must be used for varying the tune voltage. Also, if the VCO has significant pushing figure, external noise may also modulate the carrier via the supply line, so a battery may be useful here too. External noise in the supply lines appear as frequency lines on the phase noise plot.


The Power Divider

A Wilkinson power divider was chosen over a resistive divider for its lower insertion loss and better output port isolation. The Wilkinson divider can easily be made to cover more than an octave. A three-section power divider was designed which covers the 500 to 1500 MHz band. The design, shown in Figure 3, was etched on G-10 and uses axial leaded 1/4 W resistors. Over 500 to 1500 MHz, its insertion loss is 3.5 to 4.5 dB, isolation is greater than 14 dB, and port return loss is greater than 10 dB.

A power divider could easily be made for 1500 - 3500 MHz, though it would be better if this were made on a lower loss circuit board to keep the insertion loss down.

The choice here is between a fixed or a variable delay line. For a fixed delay

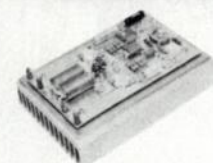HF LINEAR AMPLIFIERS - BROADBAND TRANSFORMERS



2 METER VHF AMPLIFIERS

35 Watt Model 335A \$ 79.95 KR
75 Watt Model 875A \$119.95 KR
Available in kit or wired/tested

For detailed information and prices, call or write for our free catalog.



CCI Communication Concepts Inc.

508 Millstone Drive • Beavercreek, OH 45434-5840 • (513) 426-8600
FAX (513) 429-3811



HF AMPLIFIERS per MOTOROLA BULLETINS

Complete Parts List for HF Amplifiers Described
in the MOTOROLA R.F. Device Data

AN758 300W \$154.15	EB83 140W \$ 86.65
AN762 140W \$ 95.15	EB27A 300W \$136.80
AN778L 20W \$ 83.79	EB104 600W \$371.65
AN778H 20W \$ 93.20	AR305 300W \$346.82
AR313 300W \$366.00	

NEW!! 1K WATT 2-50 MHz Amplifier

MOTOROLA AR347 \$1,100.95

POWER SPLITTERS and COMBINERS

2-30MHz	
600 Watt PEP 2-Port	\$ 89.95
1000 Watt PEP 2-Port	\$ 79.95
1200 Watt PEP 4-Port	\$ 89.95

100 WATT 420-450 MHz PUSH-PULL LINEAR

AMPLIFIER — SSB-FM-ATV

KEB67-PK (KIT).....	\$159.95
KEB67-PCB (PC Board).....	\$ 18.00
KEB67-I (Manual).....	\$ 5.00

We also stock Hard-to-Find parts

CHIP CAPS—Kemet/ATC
METALCLAD MICA CAPS—Unelco/Semco
RF POWER TRANSISTORS
MINI-CIRCUIT MIXERS
SBL-1 (1-500MHz)..... \$ 6.50
SBL-1X (10-1000MHz)..... \$ 7.95

ARCO TRIMMER CAPACITORS

VK200—2048 RF Choke.....	\$ 1.20
56-598-65-3B Ferrite Bead.....	\$ 20

Broadband HF Transformers

Add \$4.00 for shipping and handling.



FREQUENCY PRODUCTS

ELECTRO DYNAMICS CRYSTAL CORP.

Crystals

- Microprocessor
- Military Spec/QPL
- Communication
- Custom Crystals

Oscillators

- Hybrid Clock
- TCXO
- VCXO
- Custom Oscillators

9075 Cody Overland Park KS 66214

Phone (800) EDC-XTAL Fax (913) 888-1260

INFO/CARD 52

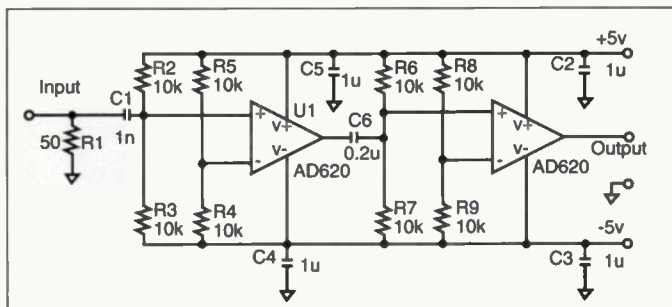


Figure 4. Low noise amplifier to feed A/D converter.

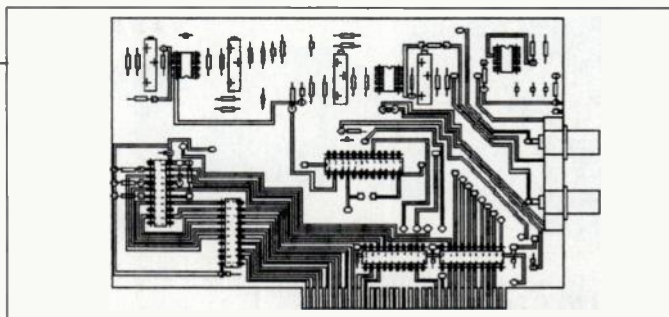


Figure 6. PCB layout for the analog to digital converter.

line, one would need to vary the frequency to achieve quadrature by varying the tune voltage on the VCO. With a variable delay line, one could set the tune voltage and adjust the delay.

A fixed delay was chosen for several reasons. For a fixed delay of the length typically required, there are sufficient nulls within the VCO's tuning band width to adequately characterize a VCO's phase noise performance. If a fixed delay is used, then the value of T_d is known and constant.

Twenty feet of RG-58 coax has a measured delay of 31.2 nsec, and a loss of 2.5 dB at 500 MHz, increasing linearly to 7.5 dB at 3 GHz. The maximum offset frequency which can be measured with a 31.2 nsec delay line is 5.1 MHz. 100 kHz is the maximum offset of interest here, so this is acceptable. For 40 feet of RG-58 coax, the delay is 62.4 nsec and the maximum offset frequency is 2.55 MHz. The maximum offset restriction comes from the desire to avoid having to include the $\sin x/x$ characteristic of the discriminator in the equation for phase noise.

As mentioned above, a longer delay line increases the slope of the volts vs. frequency curve at the zero crossing, increasing the discriminator constant, but also increasing the loss. If the mixer requires an LO drive of +7 dBm and no more than +1 dBm RF level, it is desirable to have a delay line with a loss of about 7 dB. This means that, for 500 to 1500 MHz, 40 feet of RG-58 could be used, while, for 1500 to 3000 MHz, 20 feet of RG-58 would work well.

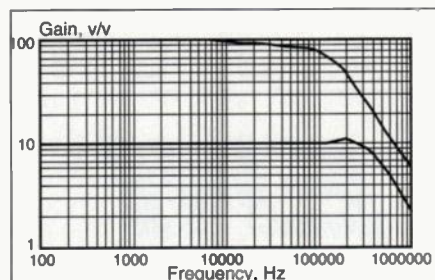


Figure 5. Gain of AD620, as listed on data sheet.

The Mixer

The mixer must be double balanced. This reduces the harmonics present at the IF port, and typically means better isolation between ports. Good isolation and balance will minimize DC offset at the IF port, which must be DC-coupled. To get a large output voltage level a high level mixer could be used, but there must be sufficient signal level to drive it. The RF port must be driven below saturation, (the mixer must operate in its linear region), to minimize the contribution of its own noise.

Given these considerations and the desired operating frequency range, a good choice is the Mini Circuits SRA-

3500. This mixer takes a +7 dBm LO drive, has a 500 to 3500 MHz RF and LO bandwidth, and an IF bandwidth of DC to 1000 MHz. It has acceptable LO-IF isolation and is inexpensive.

The Low Noise Amplifier

This is a critical part of the system. The IF port of the mixer is terminated in 50 ohms and the voltage developed across it is amplified before being fed to the analog-to-digital converter. The input voltage range of the A to D converter is set to ± 1.25 V. By experiment, it was found that a gain of over 1000 was required to amplify the IF output noise to a level that would make suffi-

RAISE YOUR STANDARDS

10 to 25 MHz

38.0 x 26.5 x 15.0 mm

± 0.1 ppm aging
per year



$\pm 5 \times 10^{-9}$ (0 to 70°C)

1.0 W steady state
@ 25°C

+5 V input

Standard package

WE DID...AGAIN.

OFC's newest family of OCXOs offers an unprecedented combination of size and stability features. With excellent technical support, fast delivery and very competitive pricing, OFC is the standard in frequency control product design. For information on the 4598S OCVCXO, or to receive our latest product catalog and application notes, call 717-486-3411 or fax us your request at 717-486-5920.



INFO/CARD 53

...Fast Fax... BROADBAND RF AMPLIFIERS

SOLID STATE POWER FOR:

- EMC/RFI Testing
- Susceptibility Testing
- Laser Modulation
- HF Transmitters
- TV & Signal Distribution
- Ultrasonics
- General Laboratory Use



NEW!
Model 607L
0.8-1000MHz
7 Watts

✓	Model	Class	Freq. Range	Power	Gain
	1040L	B	10kHz-500kHz	400W	55dB(±1dB)
	1140LA	B	9kHz-250kHz	1100W	55dB(±1dB)
	AP-400B	B	80kHz-2.7MHz	400W	55dB(±1.5dB)
	240L	A	20kHz-10MHz	40W	50dB(±1.5dB)
	2100L	A	10kHz-12MHz	100W	55dB(±1.5dB)
	A25-25PA	A	300kHz-30MHz	25W	51dB(±1.5dB)
	A-150	A	300kHz-35MHz	150W	55dB(±1dB)
	A-300	A	300kHz-35MHz	300W	55dB(±1dB)
	A-500	A	300kHz-35MHz	500W	60dB(±1dB)
	A-1000	A	300kHz-35MHz	1000W	60dB(±1.5dB)
	325LA	A	250kHz-150MHz	25W	50dB(±1.5dB)
	3100LA	A	250kHz-150MHz	100W	55dB(±1.5dB)
	3200L	A	250kHz-120MHz	200W	55dB(±1.5dB)
	400AP	A	150kHz-300MHz	3W	37dB(±1dB)
	403LA	A	150kHz-300MHz	3W	37dB(±1dB)
	411LA	A	150kHz-300MHz	10W	40dB(±1.5dB)
	525LA	A	1MHz-500MHz	25W	50dB(±1.5dB)
	550L	A	1.5MHz-400MHz	50W	50dB(±1.5dB)
	5100L	A	1.5MHz-400MHz	100W	50dB(±1.5dB)
	604L	A	0.5MHz-1000MHz	4W	40dB(±1.5dB)
	607L	A	0.8MHz-1000MHz	7W	43dB(±2dB)
	630L	A	400MHz-1000MHz	30W	51dB(±2dB)
	6100L	AB	400MHz-1000MHz	100W	51dB(±2dB)

FOR PRIORITY SERVICE

Copy and fax this ad to us at
(716) 427-7839

Fill in your name, address and fax
or phone in the spaces below!
Place a ✓ in the far left column for
specifications on specific models.

Name: _____

Job Title: _____

Company: _____

Mail To: ☐ _____

Call: ☐ _____

Fax: ☐ _____

Check here to receive complete catalog in mail: ☐

PHONE: (716) 292-7440 • FAX: (716) 427-7839

WORLD HEADQUARTERS

ENI • A Division of Astec America, Inc. • 100 Highpower Road • Rochester, NY 14623
Tel: (716) 292-7440 • Fax: (716) 427-7839

SALES & SERVICE OFFICES

FREMONT, CA • Tel: (510) 353-4ENI (4364); AUSTIN, TX • Tel: (512) 339-8949; WELWYN GARDEN CITY, UK • Tel: (0707) 371558
GERLINGEN, GERMANY • Tel: (0715) 621095; TOKYO, JAPAN • Tel: 0425 229011; OSAKA, JAPAN • Tel: 06 367-0823

INFO/CARD 54

ENI®

RFD 9/95

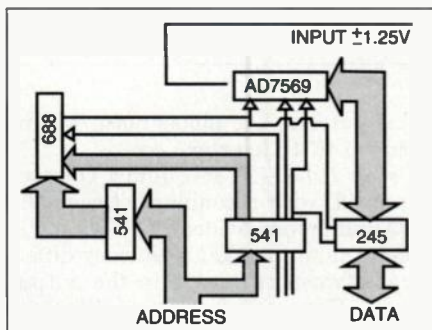


Figure 7. Block diagram of A/D conversion system.

cient use of this ± 1.25 V input range. The amplifier's gain needed to be flat to at least 100 kHz. Since no anti-aliasing filter was used, the amplifier's gain can drop steeply after 100 kHz. The amplifiers must generate little noise.

Figure 4 shows the final configuration. The gain of the Analog Devices AD620 is set by a single external resistor. The data sheet gain is shown in Figure 5. Two stages were used, with the gain shared equally between them. This maintained sufficient bandwidth and gain, and made it easier to balance the amplifiers and measure their gain.

A gain of about 40 per stage was used. The data sheet indicates that for this gain setting, the gain starts to roll off at about 100 kHz, and this was confirmed by experiment. The DC blocking capacitor, C6, was used to enable one to set the balance on the second stage. A potentiometer was not used because it is not sensitive enough and is too noisy. Noise generated by the AD620 is low.

The goal in this part of the system was conversion speed, coupled with simplicity and low cost. The Analog Devices AD7569 8-bit ADC/DAC device is an excellent device for this application. It can convert at a maximum rate of 400 ksamples/second and is easily interfaced to the PC bus. Its input and output voltage can be set for 0 - 1.25 V, 0 - 2.5 V, ± 1.25 V, or ± 2.5 V.

The circuit board which was designed around this device is shown in Figure 6. This board has input and output amplifiers to condition the signal for 0 to 10 V input and output, and a fixed-frequency audio oscillator for the purpose of calibrating the conversion rate. The unipolar, 0 - 10 V input range turned out to be non-ideal for the discriminator method, though it was good for the phase-locked system first used. The circuit was modified for ± 1.25 V. The block diagram in Figure 7 shows the final configuration.

The actual sampling rate is determined by the software and the host PC. In a 486DX33 MHz computer,

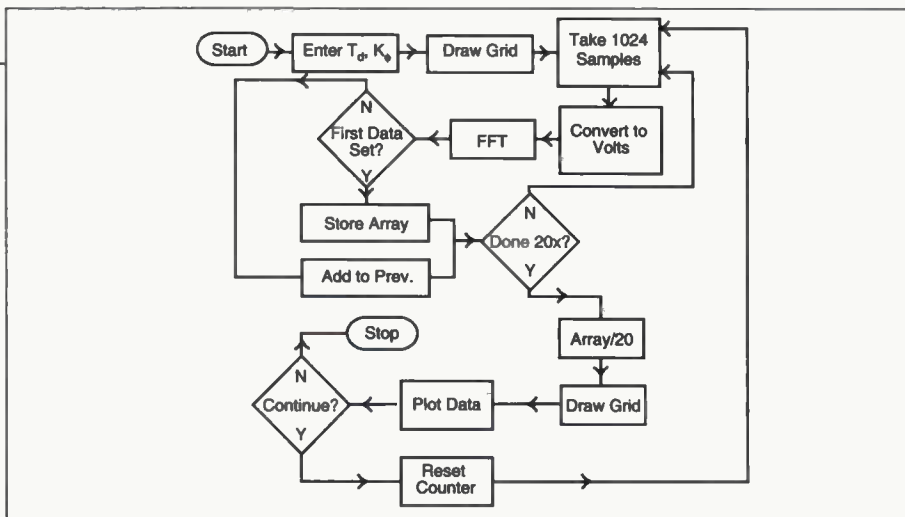


Figure 8. Algorithm used for wave analysis.

using an assembly language input routine optimized for speed, the sampling rate is about 250 kHz, which is adequate for measuring frequency components to 100 kHz.

Wave Analysis Software

The program used to analyze the signal from the discriminator and calcu-

late and display the phase noise was written using Microsoft QuickC, with an embedded assembly language routine for fast sampling of the signal. A listing of the program is included with the documentation for the software used in this measurement scheme [see the end of this article for information on ordering the software, ed.], and a flow

RAISE YOUR STANDARDS

4 pin DIP

Surface mount available

1 to 50 MHz



Tuning range:
 ± 100 ppm min.
(0.5 to 4.5 VDC)

± 24 ppm (0 to 70°C)

+5 V input

OUR NEW VCXO DOES!

OFC's newest family of VCXOs offers a superior combination of size and stability features. With excellent technical support, fast delivery and very competitive pricing, OFC is the standard in frequency control product design. For information on the 794 VCXO, or to receive a copy of our latest product catalog and application notes, call 717-486-3411 or fax us your request at 717-486-5920.



OAK Frequency Control Group

McCoy • Ovenaire • Spectrum • Croven • H.E.S.

INFO/CARD 55

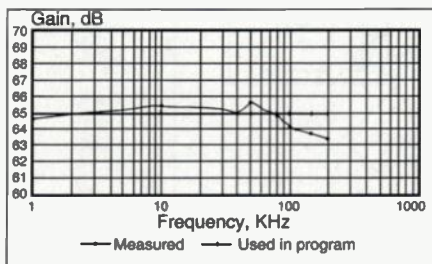


Figure 9. Measured gain of one stage of the low noise amplifier.

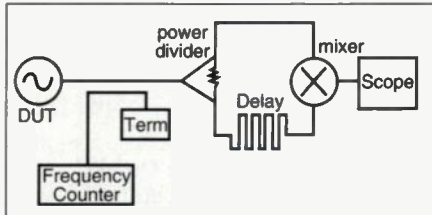


Figure 10. Test setup to measure delay line electrical length.

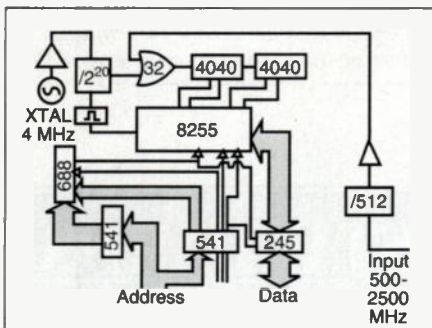


Figure 11. Block diagram of frequency counter card designed to fit in a PC cardslot.

chart is shown in Figure 8.

After sampling has taken place, the data is converted to volts, a Hanning window applied, and the FFT performed. The single sideband phase noise is calculated, and the data stored. After 20 sets of data have been collected and the average calculated, the data is displayed on a 2-cycle log-linear plot. If the wave analysis software is run as a DOS application from Windows, PrintScreen may be used to capture the display, and PaintBrush may be used to print the graph.

The Hanning window is used because, although it may have up to 1.5 dB error in amplitude, it gives good frequency resolution. A flat top window gives good amplitude accuracy, but poor frequency resolution. If no window is used, the amplitude may be up to 4 dB in error. The Hanning window is good for random noise signal analysis.

The number of samples taken is 1024.

This gives 512 data points in the frequency domain (each line contains both magnitude and phase information). An rms voltage is calculated from these points and corrections applied for the discriminator constant, etc., and the single sideband phase noise calculated.

Only frequencies from 1 kHz to 100 kHz are displayed. This is the region of valid data based on the bandwidth of the baseband amplifier and the sampling rate.

System Calibration and Accuracy

The key to accurate measurements is good calibration of the various components. Calibration consists of determining the value of the variables in the equation given above. The variables other than T_d and K_0 may be determined once, and set in the program. T_d , however, must be known, and K_0 measured, prior to making a particular measurement.

The following is a description of how the system was calibrated. An estimate of the effect of various errors was made by examining the effect of small changes in the variables of the single sideband phase noise equation.

Low Noise Amplifier – The gain of one stage was measured using an audio oscillator and a dual-trace oscilloscope. Since the two stages are identical, the overall gain was calculated from the single stage gain. It was too difficult and inaccurate to measure the gain of the two-stage amplifier by this method because of the large gain involved. The gain of the amplifier is shown in Figure 9. The maximum error from gain inaccuracy is less than 1 dB.

Frequency Resolution – This was determined by digitizing a known-frequency signal and determining the sampling rate. Knowing the time between samples and the number of samples used in the FFT routine, the frequency resolution is given by the expression: $1/(\text{\#samples} \cdot \text{time step})$. This was determined to be 247 Hz. An error of ± 2 Hz in this figure would give an error of about ± 0.1 dB in the phase noise plot.

Conversion Accuracy of A to D and FFT Routine – The internal reference voltage of the AD7569 is nominally 1.25 V. The reference voltage was determined by digitizing a known-amplitude signal and determining which reference voltage resulted in the correct digitized amplitude at the output of the ADC. For this particular AD7569, a reference voltage of 1.315 V gave the correct output. If the calculated voltage is in error

by ± 5 percent, the phase noise will be up to ± 0.46 dB in error.

Delay Line – A frequency counter was used, with a coupler between the VCO and power divider (see Figure 10), to determine the VCO frequency difference between two nulls in the output voltage. From this frequency difference the time delay of the delay line can be calculated from

$$T_d = \frac{1}{2\Delta f} \quad (2)$$

The frequency counter was a card which was designed to fit in the PC, and uses an NEC divide-by 512 pre-scaler to divide the RF signal down to the input range of the counter. A block diagram of the counter is shown in Figure 11.

For 20 feet of RG-58 cable this method measured a time delay of 30.937 nsec. The cable was also measured on an HP network analyzer; the delay by that method was measured to be 31.2 nsec. Either result could be used. An error of ± 5 percent in the delay results in about ± 0.45 dB error in the phase noise calculation.

Measurement of K_0

This measurement must be done every time a phase noise measurement is made and involves determining the rate of change of mixer output voltage versus change in input frequency. It is desirable to determine and use the point of maximum sensitivity.

Several factors affect the value of K_0 . For a sine shaped curve, the slope at the zero crossing is equal to the peak value of the sinusoid. The slope can thus be measured by measuring the positive and negative peak voltages on either side of the point at which the phase noise measurement will be done, and then using the average of the two peaks. (The VCO tune voltage is used to set the mixer output to these peaks). This measurement can be made on the mixer IF output using either an oscilloscope or voltmeter.

As frequency increases the delay-line loss increases, which causes the signal level at the mixer's RF port to decrease, which causes the output voltage to be a sine wave of slowly decreasing amplitude. This, along with the fact that real mixers do not have perfect balance or infinite LO-IF isolation, means these two voltages will not be the same, and that the mixer will have some DC offset at the point of maximum sensitivity. The average of the two voltage peaks

**455KHz - 10.7MHz Filter**

Offers excellent sensitivity, optimum stop band attenuation and high stability for wireless applications.

**SMD Trimming Capacitor (TZV02) Series**

Smallest size available – just 2.3mm x 3.2mm x 1.45mm. Excellent stability, rugged construction. Designed for auto placement.

Monolithic Chip Caps


Ultra-miniature sizes — all the way down to 0402. Temperature ranges from -55°C to +150°C.

**Compact VCO**

Small size, low power consumption. 400MHz-2.5GHz. Stability of ± 2 MHz from -35°C to +80°C.

**SMD Inductor**

Ultra-small, tight tolerance inductor with low DC resistance and outstanding high frequency characteristics.

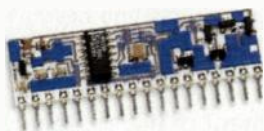**Circuit Module (Hybrid IC)**

Excellent HF and heat dissipation characteristics. The result of Murata's 25 years of thick film technology.

**SAW Filter**

Smaller, thinner design with high performance, even above 1GHz. Zinc oxide printed on sapphire substrate.

**Microwave Filters (GIGAFIL®)**

Low insertion loss for high Q-value dielectric resonators, excellent out-of-band rejection.

A few of the important components of a happy conversation with Grandpa.

A clear mountain lake, a grandson with his first fish and a cellular phone with as many as 140 Murata components. A simple combination that makes a nice surprise for Grandpa. And here's a surprise for you: For wireless devices from pagers to PDAs, you can use Murata components for 70% of any RF front end — components that range from multilayer VCOs and high

frequency filters to chip monolithic hybrid couplers and RF diode switches. You see, we not only want to be an important component of a call to Grandpa. We also want to be the call you make when you specify components for your newest design.



For a free wireless poster, as well as Murata catalogs, call **1-800-831-9172, ext. 450.**

Murata
Innovator in Electronics

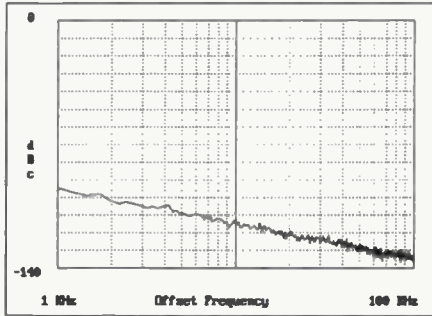


Figure 12. Measured system noise floor.

should be used for the value of K_{ϕ} , and the output voltage should be set to half way between them. An error of $\pm 10\%$ in V_{ϕ} will give an error of about ± 0.92 dB.

It is important that the output voltage remains at the set point during a measurement as departure from this point will give a phase noise that is lower than the true value. How far the output voltage may drift from this set point, given a maximum error allowable in dB, can be found from:

$$\Delta V = K_d \sqrt{1 - 10^{-\frac{\text{error}}{5}}} \quad (3)$$

Overall measurement uncertainty

It can be seen that error in K_{ϕ} is a major contributor to error in the single-side-band phase-noise. If all errors are additive but the output voltage is kept at the set point during measurement, the actual phase noise may be about 3 dB higher or 4.5 dB lower than that displayed. The extra 1.5 dB on the low side is from the Hanning window amplitude inaccuracy. This would be the worst case.

Making a Measurement

A phase noise measurement is simple: set up the equipment as shown in Figure 2; add gain or attenuation as required before the power divider to achieve +7 dBm at the LO port of the mixer, and enough delay line to get about 0 dBm at the RF port; measure K_{ϕ} and then set the mixer output at the point of maximum sensitivity as explained above. Run the program, entering the delay line length in nsec, and K_{ϕ} in volts when requested. After the plot is displayed, it may be printed.

As mentioned above, external noise may easily enter the VCO via the power supply or the tune line and this will appear as discrete lines on the phase noise plot. The sources of this noise include computer displays, line frequency hum, power supply ripple, switching power supplies, oscillators in calculators and digital multimeters,

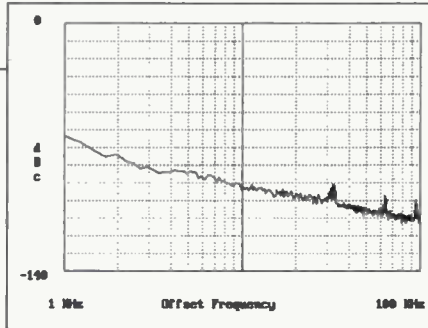


Figure 13. Measured phase noise of an example VCO with center frequency at 1100 MHz..

demodulated radio station audio, radar pulses, and mechanical vibration. The VCO should be shielded from this noise pickup – this is almost a science in itself! This is especially true for VCOs with high modulation sensitivity and non-zero pushing figure.

System Noise Floor

The noise floor is an important measurement because it shows the "signal to noise" ratio of the system and indicates the lowest phase noise that can be measured with a given delay line and discriminator constant. This measurement is easy to make. Simply set up to make a measurement as normal. Once K_{ϕ} is known, break the delay line path and terminate the power divider port in 50 ohms. Then run the measurement using the measured value of K_{ϕ} .

Figure 12 shows the system noise floor, and Figure 13 shows the phase noise of an oscillator. It can be seen that the VCO noise is more than 20 dB higher than the noise floor in this case. The lines at 34 kHz and its harmonics are noise picked up from the PC's monitor – they can be eliminated by making the measurement with the monitor off.

The phase noise of the VCO shown in Figure 13 was also measured by the same discriminator method on the Comstron PN-9000 and the HP 3048 system. The results are compared in Figure 14. The data from the other systems are shown as a solid line drawn between the data at 1 kHz and 100 kHz. The center frequency of this VCO is about 1100 MHz. Figure 15 shows a plot for another approximately 1 GHz VCO with the phase noise as measured on the Comstron PN-9000 plotted in the same way as above. Figure 16 is a plot for an octave tuning VCO.

Usefulness of the system

This phase noise measuring system is useful for measuring free running VCOs with moderately low phase noise. Only one VCO is needed, the problem of its carrier drifting is eliminated, and

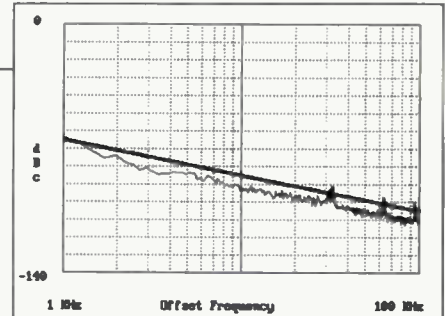


Figure 14. Same measurement as in Figure 13 compared to a measurement done on a Comstron PN-9000

its input frequency range is virtually unlimited. The system is accurate, and is quick and easy to use. Offset frequency is limited to 1 kHz on the low side (by the DC blocks needed in the low noise amplifier), and to 100 kHz of the high side (by the sample rate of the analog to digital conversion).

The various components of the system, including the frequency counter, cost less than \$250. All printed circuit boards were home made. This cost does not include the analog oscilloscope, clean power supplies, and 486DX33 computer. Such a phase noise measurement system is easily within the budget of most involved in the design and manufacture of oscillators for use in personal communication networks, and can make a significant contribution to lowering of capital equipment costs.

Improvement of the system

A 12-bit A to D converter would improve the voltage resolution. Such a converter would require a board which has its own RAM for quick read and store of the data, with transfer and processing of the data by the program after an end-of-conversion signal is received. To enable better frequency resolution in the 1 kHz to 10 kHz region, the sample rate could be slowed down, but this would necessitate the use of a good anti-aliasing filter to remove frequency components above half the sampling rate. These hardware improvements would involve an increase in the complexity of the system, and the cost.

There are several software improvements which could be made. A routine involving the use of the digital to analog section of the AD7569 and the frequency counter could be used to automatically measure T_d and K_{ϕ} . Initial experiments with this indicate that two problems will have to be solved. Digital noise must be prevented from getting to the sensitive tune port of the VCO. The other problem is measuring a voltage of about ± 0.13 V accurately with a

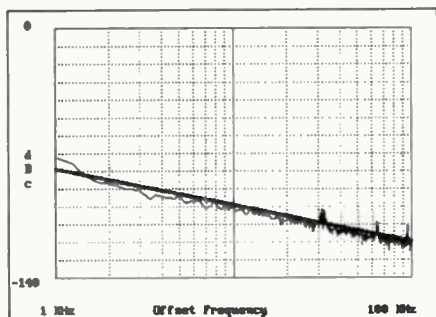


Figure 15. Another approximately 1 GHz VCO with phase noise measured and displayed as in Figure 14.

± 1.25 V input range on the A to D. A 12 bit A to D would be useful for this task. Another software improvement would be the ability to print the phase noise plot directly from the program.

These improvements would add "bells and whistles" to the system. However, as it stands, the system as presented works well and accurately.

Conclusion

The delay line discriminator method is not new. A simple, low cost, implementation has been developed here

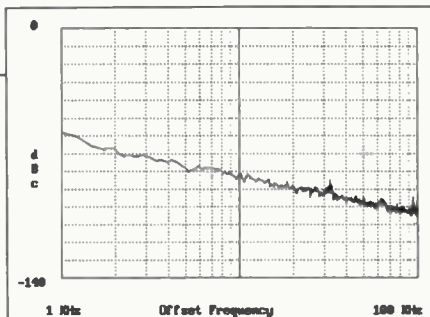


Figure 16. Phase noise plot for an octave-tuning VCO.

which enables one to measure the phase noise of oscillators whose carrier drifts too fast, or whose phase noise is too low, to be measured by direct spectrum analysis.

This system is valuable to the designer and manufacturer of inexpensive VCOs.

The wave analysis program described in this article, is available from Argus Direct Marketing. For ordering information, see page 96. RF

References

1. COMSTRON Application Note 93-

0001, "Phase Noise Theory and Measurement".

2. Scherer, Dieter, The "Art" of Phase Noise Measurement, Hewlett Packard, August 1985.


3. RF & Microwave Phase Noise Measurement Seminar, Hewlett Packard, 1987.

About the Author

Bill Suter received his BSEE from Cape Town University in South Africa in 1976. After emigrating to the USA at the end of that year, he has been involved in many aspects of circuit design and fabrication from audio through RF to 20 GHz; from amplifiers, to oscillators, to mixers, to couplers. His hobbies include writing software, electronics, and especially airplanes. He is currently Senior Design Engineer at Amplifonix, designing primarily oscillators. He may be reached at (610) 559-7178, or (215) 464-4000.

We're Into Real Estate!

FOR SALE

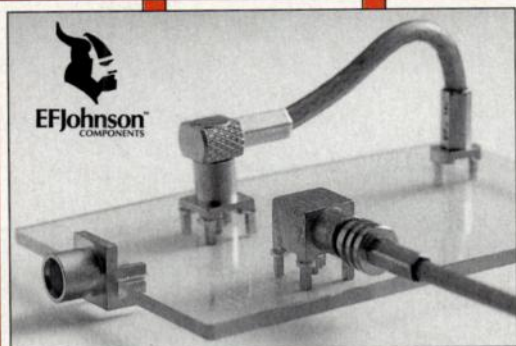

MCX Connectors by E.F. Johnson Company

With the shortage of real estate - why give up valuable board space to larger RF connectors? Our MCX is 30% smaller than SMB connectors and an excellent choice for high density packaging requirements. With a rugged snap-on mating design, these crimpable contact connectors allow for fast and dependable crimp-crimp assembly. Our MCXs employ .020" standoffs for improved board cleaning and are available with .100" leg spacing. The original E.F. Johnson Company end launch connector is also part of the MCX family.

CALL US TODAY!

1-800-247-8256

E.F. Johnson Company, 299 Johnson Ave., Waseca, MN 56093 Fax: (507) 835-6287

INFO/CARD 57

ALL YOU NEED TO KNOW ABOUT CRYSTALS....



BOMAR

Over 30 years Experience

... Specializing in quick
turn around on non-standard
frequencies

... Inventing common
microprocessor frequencies

Phone 800-526-3935

or

Fax 800-777-2197

**201 BLACKFORD AVENUE
MIDDLESEX, NJ 08846**

INFO/CARD 58

Design Parameters for 1- Through 7-Pole Input-Matched Lowpass/Highpass Filters

By Chase P. Hearn
NASA Langley Research Center

The transfer loss mechanism in conventional LC filters is reflective; attenuation is through mismatching of the driving source in the stopband. Filters having constant resistive input impedance in addition to attenuation are desirable for some applications, such as terminating diode mixers. Filters having those properties have been described as branching filters [1], diplexers [2], and constant-resistance filters [3]. Such filters are physically realizable but are not widely used. The work described here was undertaken because the prior work was either limited in scope and/or did not produce the desired performance. These results yield branching filters with low or highpass Butterworth transfer responses through order seven and constant-resistance performance superior to previous designs. With few

exceptions, the element values for these filters differ from standard Butterworth values.

A branching filter is illustrated in Figure 1; a low-pass and a high-pass filter are connected either in parallel or series. Power not dissipated by the load on port 2 is dissipated by the load on port 3. Port 2 has a

low-pass and port 3 a high-pass transfer response. Ideally, the imaginary components of Y_{in} or Z_{in} of the combined networks sums to zero and the real parts sum exactly to $1/R$, or R , respectively [3]; the loss mechanism in a branching filter is therefore absorptive, rather than reflective.

It is possible to achieve n -pole Butterworth lowpass or highpass transfer

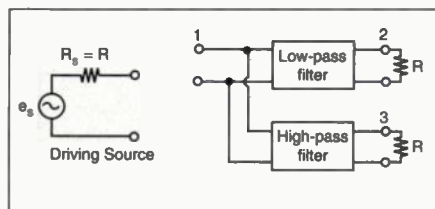


Figure 1a. Shunt-connected branching filter.

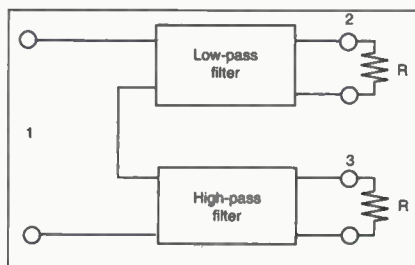


Figure 1b. Series-connected branching filter.


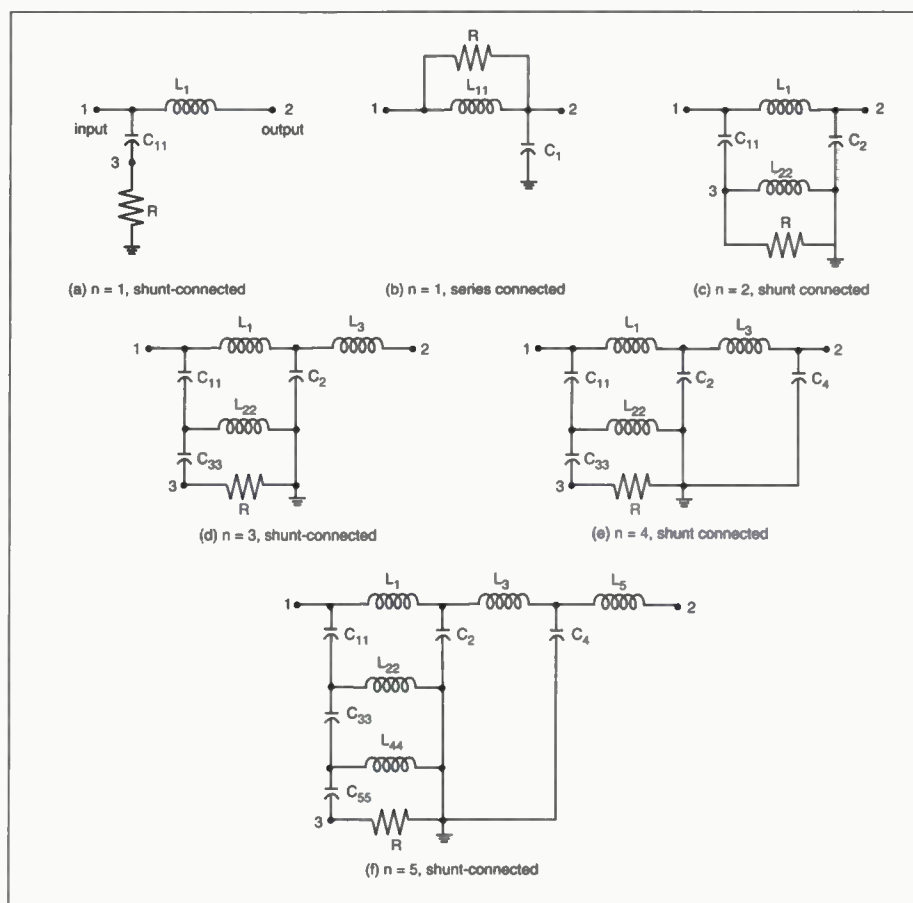


Figure 2. One to 5-pole lowpass branching filters of characteristic impedance R .

Future Electronics
and
Murata
offer

excellence in RF & microwave

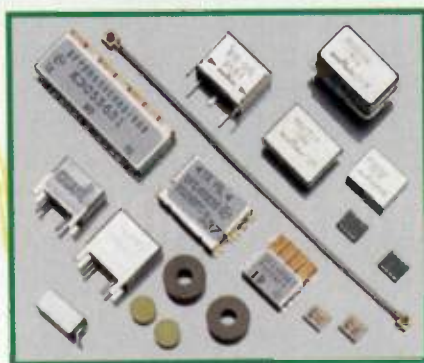

Future Electronics has been delighting customers for more than 25 years now. The electronics industry has recognized this for quite some time. It's because of our outstanding technical expertise, our highly trained personnel, and our innovative support programs such as FIRST — Future's Inventory Replenishment System Technology — the most reliable, automated EDI system supporting the largest installed customer base worldwide.

Future brings you the service and supplier partnerships with an industry leader like Murata.

And with Future Electronics and Murata you're assured of excellence in RF and Microwave components. Future stocks a broad inventory of highly miniaturized, high performance Murata components, including RF and Microwave Ceramics, VCO and Crystal Oscillators, RFI/EMI components for RF and wireless applications including GPS, ISM and PCS.

Quality components that you and your customers expect... and with the service that wins the awards.

For more information call 1-800-FUTURE-1, ext. 2982.



FUTURE ELECTRONICS

EXPERIENCE THE SERVICE THAT WINS THE AWARDS

EUROPE

• THE AMERICAS

• ASIA/PACIFIC

INFO/CARD 60

muRata
Innovator in Electronics



A UNIT OF
FUTURE ELECTRONICS

Not a bird. Not a plane. Just an awesome rf amplifier.



It sweeps. It pulses. It levels. It blanks. It operates manually or by remote control. But most important, it delivers *at least* 500 watts of rf power, regardless of load VSWR.

We designed the new all-solid-state Model 500A100 broadband rf amplifier to be used *wherever* you need reliable rf power over a 10 kHz to 100 MHz bandwidth, including test situations where nothing less than 500 watts will do.

We tested the 500A hard, first by reflecting nearly all forward power back into the amp — it still put out 500 watts (minimum). We shorted its output terminals, then left them open.


We couldn't hurt it. It didn't even shut down.

So if you need 500 watts *minimum*, you're sure to get it, which is where we start with any amplifier we build. But just look over the Model 500A100 front panel: gain control; threshold/leveling; pulse

input; detected rf input and output; mode selector. A front-panel power meter measures either forward or reflected power. And a back-panel connector makes it easy to interface to a computer or other remote controller.

The Model 500A100 is one of eight economical broadband rf amplifiers in our A-Series line, which reaches up to 1,000 watts and 250 MHz. One model, the 40AD1, goes all the way down to dc.

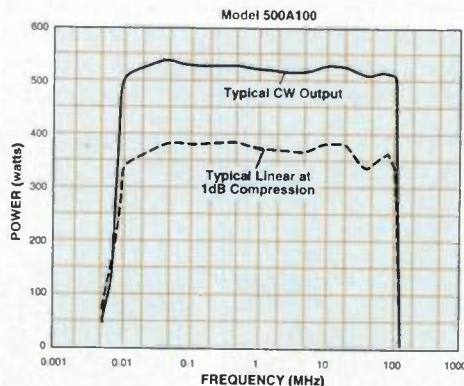Put your wish list together (including all the accouterments) and call us. One of our friendly AR applications engineers will take the call directly. They enjoy challenges. 1-800-933-8181.



160 School House Road • Souderton, PA 18964-9990 USA
TEL 215-723-8181 • FAX 215-723-5688

For engineering assistance, sales, and service throughout Europe, call EMV: Munich, 89-612-8054 • London, 01908-566556 • Paris 1-64-61-63-29.

INFO/CARD 59

responses and purely resistive input impedances with $2n+1$ circuit elements – without introducing additional transfer loss in the passband. However, filters with ripple in the passband (Tchebycheff) or the stopband (m-derived) cannot be made to have constant input resistance with the additional $n+1$ elements [3]. The $(n+1)$ element impedance-correcting network could be applied to the output rather than the input of a filter to achieve a resistive output impedance. This would be desirable if the signal or local oscillator port of a diode mixer was driven from a filter.

Consider the 1-pole shunt-connected branching filter shown in Figure 2(a). With ports 2 and 3 terminated in R , the impedance at port 1 can be expressed as:

$$Z_{in} = R \frac{R + \frac{L}{RC} + j\left(\omega L - \frac{1}{\omega C}\right)}{2R + j\left(\omega L - \frac{1}{\omega C}\right)} \quad (1)$$

If L and C are related by:

$$\frac{L}{C} = R^2 \quad (2)$$

Z_{in} (but not Z_{out}) will equal R ; either L or C can be set arbitrarily to control the cut off frequency. If $L = R/\omega_c$ and $C = 1/\omega_c R$, to satisfy equation 2, the power delivered to the loads on ports 2 and 3 is reduced by 50 percent at $\omega = \omega_c$ and $Z_{in}(\omega)$ equals R for all values of ω .

A series-connected configuration as shown in Figure 2(b) would be used if the filter port to be compensated had a shunt input arm. Symbolic derivations similar to that become increasingly complex when the order of the filter exceeds two. Element-value relationships from Reference 1 for 1- through 3-pole branching filters are shown in Table I. A numerical approach was used to find the element values for 4- through 7-pole shunt-connected branching filters and also to verify the results of Reference 1 for lower-order branching filters.

n	Lowpass Section					Highpass Section					Minimum return loss, dB
	L1	C2	L3	C4	L5	C11	L22	C33	L44	C55	
1	1	-	-	-	-	1	-	-	-	-	00
2	1	1	-	-	-	1	1	-	-	-	9
3	1.5	1.33	0.5	-	-	0.67	1.33	2	-	-	12

Table I. Element values for first through third-order branching filters from Reference 1; questionable values are shaded. Multiply by (R/ω_c) for inductors and $(1/\omega_c R)$ for capacitors.

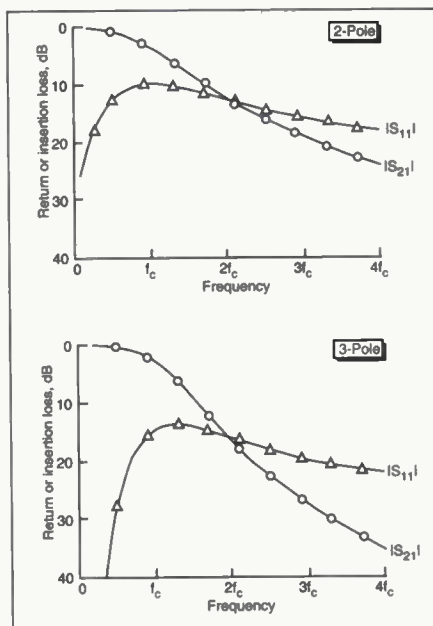


Figure 3. Input impedance, return and insertion loss of branching filters using element values from Reference 1.

Element values for branching filters were derived with a CAD gradient optimization procedure and tabulated in Table II; these values are the same as those in Reference 1 only for the 1-pole case; the shaded entries for 2- and 3 pole filters in Table I differ significantly from those in Table II. Figure 3 shows $|S_{11}|$ and $|S_{21}|$ for 2- and 3-pole filters using the element values from Table I. The minimum input return losses (r.l.) are only 9 dB for the 2-pole filter and 12 dB for the 3-pole filter between $f_c/10$ and $4f_c$, while the values in Table II produce input return losses exceeding 70 dB. Note that there are the same inverse relationships between corresponding L and C elements in the low and high-pass sections of branching filters that are found in conventional filters [4].

Table III contains standard Butterworth element normalized low and high-pass values [4] which were recommended for input-matched diplexers in Reference 2 and the minimum return losses which result when the

Printed circuit board prototypes for MICROWAVE and WIRELESS applications are our specialty.

"When I see it, I'll believe it."

We make flawless printed circuit prototypes for low and high frequency applications.

"When I see it, I'll believe it."

We can build your PTFE printed circuit board prototypes in only 12 hours.

"When I see it, I'll believe it."

**WANNA SEE IT?
CALL 1-800-279-5572**

Lower your printed circuit board costs, not your standards. Don't skip the prototype process when you need printed circuit boards on PTFE, Teflon, Duroid or GX laminates.

SOUTHWEST CIRCUITS specializes in prototyping circuit boards for all MICROWAVE and WIRELESS applications.

Multi-layers, Quick-Turn or Exotics. Our proprietary technologies and processes give us an edge over ordinary printed circuit board fabricators.

Make us prove it. Call Now.

SOUTHWEST CIRCUITS
3760 E. 43rd Pl.
Tucson, AZ 85713
(602) 745-8515
FAX (602) 747-8334
Modem (602) 747-5108



INFO/CARD 61

n	Lowpass Section							Highpass Section							Minimum return loss, dB
	L1	C2	L3	C4	L5	C6	L7	C11	L22	C33	L44	C55	L66	C77	
1	.9979	—	—	—	—	—	—	.9979	—	—	—	—	—	—	99
2	1.413	0.7063	—	—	—	—	—	0.7063	1.413	—	—	—	—	—	126
3	1.499	1.333	0.500	—	—	—	—	0.6661	0.7493	1.998	—	—	—	—	96
4	1.531	1.578	1.085	0.3841	—	—	—	0.6532	0.6335	0.9219	2.603	—	—	—	99
5	1.543	1.692	1.383	0.9013	0.3152	—	—	0.6464	0.5899	0.7245	1.123	3.253	—	—	77
6	1.553	1.760	1.555	1.202	0.7549	0.2562	—	0.6437	0.5675	0.6408	0.8207	1.279	3.675	—	79
7	1.556	1.800	1.662	1.398	1.052	0.6366	0.2239	0.6412	0.5540	0.5976	0.7029	0.9274	1.525	4.699	70

Table II. Normalized element values for first through seventh-order branching filters derived numerically. Multiply by (R/ω_c) for inductors and $(1/\omega_c R)$ for capacitors.

input ports are paralleled to form branching filters. The values in Tables I and III are totally different; seven entries in Table I and only two in Table III agree with Table II.

Conventional Butterworth low-pass filters have input and output return losses which degrade from a good match when $f < f_c$ to 3 dB at f_c . A reasonably good match (r.l. > 20 dB) is had over an increasingly larger fraction of the passband as n is increased, illus-

trated in Figure 4 for 3- and 5-pole filters. Adding the $n+1$ additional circuit elements needed to produce an input-matched filter increases the output r.l. from 3 to 6 dB at f_c .

This is not a theoretical development, so no claim of absolute superiority can be made for the values in Table II. Other combinations might produce equal or better results; however, the values in Table II produce nearly perfect input matches and transfer

responses identical to an n -pole Butterworth response at $f_c/10$, f_c , $2f_c$, and $4f_c$.

The gradient optimization process used to derive the element values became increasingly difficult when n exceeded 3. Sub-optimum minima were encountered and the results of each optimization were highly dependent on the optimization statement and the initial values. The values in Table II for $n > 4$ were obtained only after an extrapolation scheme was devised for selecting the initial values. The element values from the first four successful optimizations were plotted as shown in Figure 6 and extrapolated as indicated by the dotted lines. The $n = 5$ optimization was constrained arbitrarily to a ± 10 percent range around

**LATEST...
LOW COST
PCB PROTOTYPE
SYSTEM FROM THE
WORLD LEADER**

**\$8500
STOCK DELIVERY**



The LPKF Protomat 91S System provides faster turnaround and better throughput of circuit board prototypes than other methods. There is NO better value in prototype PCB fabrication systems—here's why:

- Takes your Gerber or HPGL files and produces Analog, Digital, RF or Microwave circuit board prototypes.
- Windows software with programmable insulation width, multiple tool rub out, and full tool management.
- Small footprint from a fully integrated system package.
- Environmentally safe - uses NO chemicals.
- Fast payback - typically 3-12 mos.
- Full 1 year warranty

FREE PCB INFO PACK

CALL TODAY 1-800-345-LPKF

(800) 345-5753 FAX request to: (503) 297-2820

**LPKF CAD/CAM
SYSTEMS INC.**

6840 SW Canyon Dr. Portland, OR 97225

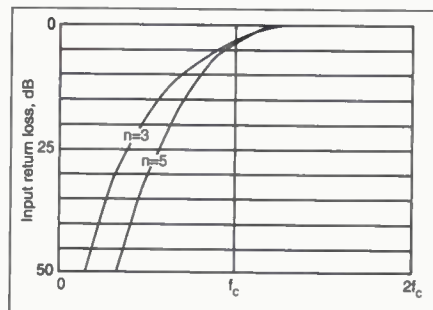


Figure 4. Input return loss in 3 and 5-pole Butterworth filters.

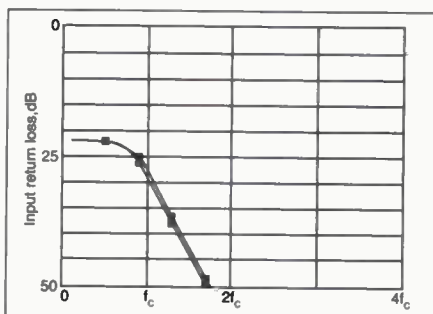


Figure 5. Effect of output port mismatch on a 3-pole branching filter ($\Gamma_L = \pm 0.082$).

n	Lowpass Section							Highpass Section							Minimum return loss, dB
	L1	C2	L3	C4	L5	C6	L7	C11	L22	C33	L44	C55	L66	C77	
1	2.000	—	—	—	—	—	—	0.500	—	—	—	—	—	—	7
2	1.413	1.413	—	—	—	—	—	0.7077	0.7077	—	—	—	—	—	24
3	1.000	2.000	1.000	—	—	—	—	1.000	0.5	1.000	—	—	—	—	7
4	0.7649	1.847	1.847	0.7649	—	—	—	1.307	0.5414	0.5414	1.307	—	—	—	2
5	0.6177	1.617	2	1.617	0.6177	—	—	1.617	0.6177	0.5	0.6177	1.617	—	—	1
6	0.5147	1.414	1.931	1.931	1.414	0.5174	—	1.933	0.707	0.5179	0.5179	0.707	1.931	—	1
7	0.4449	1.247	1.801	2.000	1.801	1.247	0.449	2.248	0.8019	0.5552	0.5000	0.5552	0.8019	2.248	1

Table III. Normalized element values for first through seventh-order branching Butterworth filters from Reference 4 and minimum return loss when connected as branching filters.

the extrapolated initial values. Only the optimized value for L3 (n=5) proved to be out of that range, which became obvious during the optimization process, and the lower limit on L3 (n=5) was reduced. The estimated values for the n = 6 and 7 optimizations obtained with this procedure were within ± 5 and ± 3 percent of the final values, respectively.

It was observed that sub-optimum minima produced element values inconsistent with the curves in Figure 6.

The constrained parameters in the optimization were input impedance

from $f/10$ to $4f_c$ and transfer response, $|S_{21}|$, at f_c , $2f_c$, and $4f_c$. The only specification imposed on the highpass section was indirect, through its effect on Z_{1c} and the low-pass transfer response. The optimization statement for an n-pole low-pass branching filter (BRANCHn) in Touchstone [5] notation is shown in Table IV.

The heavy weight on the -3 dB point was necessary to make the cut-off frequency precisely f_c . The high-pass transfer responses, $|S_{31}|$, after optimization based primarily on the low-pass response were observed to be

```

SWEEP fc/10 4fc fc/10
BRANCHn RE[Z1] = 0 10
BRANCHn IM[Z1] = 0 10
RANGE fc fc
BRANCHn DB[S21] = -3 50
RANGE 2fc 2fc
BRANCHn DB[S21] = (theoretical attenuation at 2fc)
RANGE 4fc 4fc
BRANCHn DB[S21] = (theoretical attenuation at 4fc)

```

Table IV. Optimization for an n-pole lowpass branching filter in Touchstone notation.


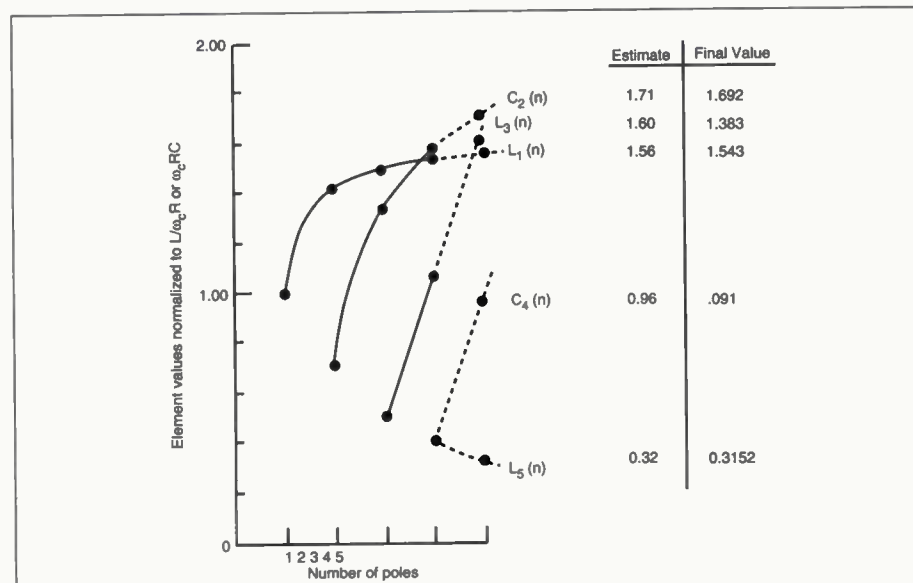


Figure 6. Determination of initial element values by extrapolation for n = 5 from n = 1 through 4 values.

Your Key to High-Frequency Test

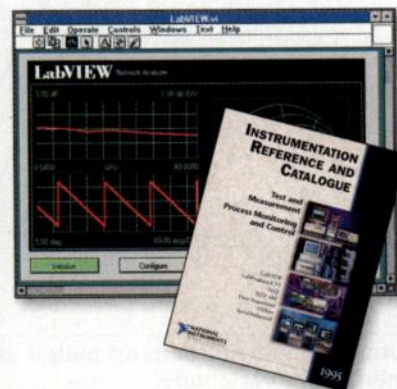

Tools for High-Frequency Automated Test and Measurement from National Instruments

Instrument Control

- **GPB and VXIbus Controllers** – Your connection to any instrument
- **Instrument Driver Library** – More than 500 software modules to control instruments from Anritsu Wiltron, Hewlett-Packard, Rohde & Schwarz, Wandel & Goltermann, and 45 other vendors

Test Development

- **LabVIEW®** – Revolutionary graphical test development environment
 - Graphical programming decreases test development time
- **LabWindows®/CVI** – Interactive C development software
 - Integrated ANSI C programming tools
- **Features**
 - Easy GPIB, VXI, and serial instrument control
 - Numerical analysis and data visualization
 - Built-in graphical user interface

Production Test Automation

- **Test Executive** – Test sequencing and report generation
- **SQL Toolkit** – Database connectivity
- **SPC Toolkit** – Monitor results and improve quality

For more information on these products and a FREE catalogue, call (800) 433-3488 (U.S. and Canada)

NATIONAL INSTRUMENTS™
The Software is the Instrument®

U.S. Corporate Headquarters
Tel: (512) 794-0100 • Fax: (512) 794-8411
E-mail: info@natinst.com • WWW: http://www.natinst.com

© Copyright 1995 National Instruments Corporation. All rights reserved. Product and company names listed are trademarks or trade names of their respective companies.

INFO/CARD 72

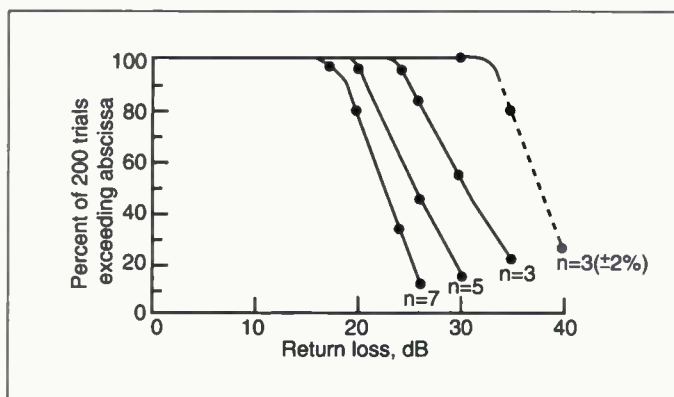


Figure 7. Sensitivity of input match to random ± 5 percent element value variations.

nearly ideal Butterworth.

A practical consideration is the extent to which a mismatched load on the output port ($R_{load} \neq R$) affects the input-port match of an otherwise ideal branching filter. It was determined by trial that the input r.l. is essentially that of the mismatched load resistance in the lower portion of the passband

and improves as frequency approaches and exceeds f_c . This is shown in Figure 5 for a reflection coefficient of ± 0.082 , a r.l. of 21.7 dB.

Another practical concern is the effect of element value tolerances. It was observed that changing a single element value one percent from ideal decreased the minimum r.l. of a 3-

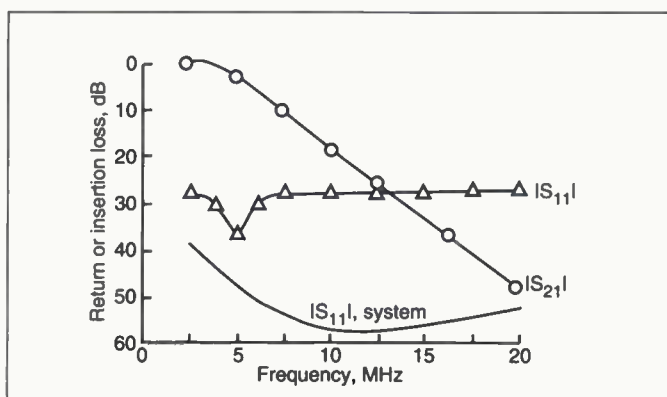


Figure 8. Measured performance of 3-pole branching filter using pre-set components.

pole branching to about 40 dB. Monte-Carlo analyses [5] were run for the $n = 3, 5$, and 7 cases to determine the effect of random element deviations within ± 5 percent of ideal. The solid curves in Figure 7 show that element errors more seriously degrade the performance of higher order filters; tightening the toler-

Real World VCOs.

When your system design calls for a Voltage Controlled Oscillator (VCO) that performs predictably and consistently without tuning, then you should take a look at the Micronetics M3500 VCO Series.

100 MHz to 3.5 GHz.

The M3500 Series features 13 different standard VCOs covering a broad spectrum of the frequency range — from 100 MHz to 3.5 GHz.

With their rugged design and reliable performance characteristics, these VCOs are ideal for use in everything from synthesizers and digital modems to direct broadcast, spread spectrum and wireless communication systems.

And there's another advantage as well: M3500 VCOs offer you this high quality and dependability without the high cost.

Until now, VCOs have either been very inexpensive (\$5 – \$10), with limited performance, or quite costly.

In fact, VCOs for specialized, high performance applications can be priced at several hundred dollars a piece.

The M3500 Series is the answer to the industry's need for a "work horse" VCO — one that can do the job that's required, and do it at a reasonable price. M3500 VCOs were designed to deliver optimum performance, even in the real world.

Why the M3500 Series is so predictable.

Each M3500 VCO is electrically identical to the next — and that's a tremendous plus when it comes to system design. It means you can be sure that an M3500 Series VCO will perform exactly as you expect it to — time and time again.

Even though other VCOs on the marketplace may seem to offer slightly better performance, or lower phase noise, there tends to

be a lot of variability from unit to unit.

When you think about designing a large system — one that may be in production for years to come and require more than a million VCOs — you just can't underestimate the value of a consistently performing VCO.

Designed and developed at QUALCOMM.

The M3500 VCO Series was designed, developed and tested at QUALCOMM, Inc. — an engineering company widely known for its advanced communications systems and products based on digital wireless technologies.

QUALCOMM engineers designed these VCOs with an overall systems perspective, focusing on a wide range of parameters that have a large, although indirect, impact on system noise performance.

On November 1, 1994, Micronetics acquired the sole rights to manufacture and distribute the QUALCOMM VCOs, adding them to their existing MicroSource™ family of low phase noise VCOs for cellular applications.

Now available off-the-shelf.

If you'd like to receive our new catalogue, or place a direct order, call our VCO Hotline at 1-800-9NEEDVCO.

MICRONETICS
WIRELESS

26 Hampshire Drive
Hudson, NH 03051
Tel: (603) 883-2900
Fax: (603) 882-8987
E-Mail: micrnet@aol.com

© Micronetics 1995. Micronetics reserves the right to make changes to the products described herein to modify design or performance.

BIS Strategic Decisions & Arthur D. Little Present...

Arthur D Little



Sponsored by:



DURACELL

Panasonic
Batteries



Philips
Semiconductors



SANYO

VARTA
THE BATTERY EXPERTS

Energizer
POWER SYSTEMS

EXAR

RAYOVAC



Affiliates:

BAPC

Mobile
Office

P.R.B.A.

ELECTRONIC
DESIGN

PCMCIA

Electronics Times

MICROWAVE
ENGINEERING

The Third Annual Conference on Power Requirements for Mobile
Computing and Wireless Communications

The industry's most complete forum for engineers,
designers and developers of mobile computing, wireless
communications, and power supply products to share
ideas and learn from each other.

October 16-18, 1995
Santa Clara Westin Hotel & Convention Center
Santa Clara, California

Highlights Include:

- Design Team Solutions
- End-User Research Data
- State-of-the-Industry Address
- World-Wide Scope
- Chairman's Choice Awards
- POWERPLACE Exhibit Area

Call 1-800-874-9980 or 1-617-982-9500 (x178) or fax to 1-617-982-1724
for your free, no-obligation, 12-page color brochure on POWER '95.
Include code "D309A11" when you request your brochure.

ances greatly improves the input match. The dashed curve in Figure 7 corresponds to tolerance of ± 2 percent, which increased the r.l. for a 90 percent yield to 34 dB, compared to 25 dB with a ± 5 percent tolerance.

A 3-pole branching filter with $Z_0 = 50$ Ohms and $f_c = 5$ MHz was designed from Table II and fabricated for evaluation. The inductors and capacitors were measured and preset to an accuracy of about ± 3 percent prior to being installed; no further adjustments were made. Return and transfer losses were measured with a spectrum analyzer/tracking generator (HP 8553B/8443A) and a high-directivity return-loss bridge and are plotted in Figure 8. The results demonstrate that a good input match and a Butterworth transfer response can be achieved simultaneously in practice.

Conclusions

Normalized element values for first through seventh order shunt-connected branching filters were determined

by numerical methods and are presented here in tabular form. These filters have Butterworth low-pass or high-pass transfer responses but are matched to a resistive source at all frequencies (r.l. > 70 dB) without adding excess transfer loss in the passband. This is accomplished at a cost of additional circuit elements; an n-pole response requires $2n+1$ elements. Branching filters based on these results are superior to those based on previously published design procedures. A 3-pole branching filter was fabricated and evaluated, with good results. RF

References

1. Sebok, Sandor, "Four Laboratory Tests Evaluate MW Synthesizers", *Microwaves*, Vol. 20, No.1, January 1981.
2. Matthaei, G. L.; Young, Leo; Jones, E. M. T., *Microwave Filters, Impedance-Matching Networks, and Coupling Structures*, Artech House Books, 1980, pp. 991-993.

3. Weinberg, Louis, *Network Analysis and Synthesis*, McGraw-Hill Book Co., 1962, pp. 539-540

4. Jordan, Edward C. (editor), *Reference Data for Engineers*, Howard W. Sams & Co., Inc, 1985, Chapter 9.

5. Touchstone Operating Manual, EEsof Corporation.

About the Author

Chase P. Hearn was a NASA research engineer from 1961 until his retirement in 1995. His work there involved analysis, design and development of circuits and systems spanning VLF to mm-waves and microwave measurement theory and practice. He is now pursuing independent R&D. He has been a licensed radio amateur since 1954 and enjoys building HF and VHF amateur equipment and restoring vacuum-tube and discrete component equipment of the forties and fifties.

REPRINTS

Finally. An inexpensive way to promote your products and services.

That's right. Now you can take advantage of a powerful, yet inexpensive way to promote your company. We can reprint any article, ad or section of this magazine and customize it to your specific needs!

- ✓ Increase your company's visibility
- ✓ Enhance your corporate image
- ✓ Position yourself as an expert in the field

How can you use reprints as a solid marketing tool?

- Direct mail pieces
- Sales presentation aids and leave-behinds
- Promotional material at trade shows
- New product announcements
- Internal/stockholder education

Take advantage of this cost-effective marketing opportunity by calling Ed LaBorwit at (404) 618-0481. Minimum order 100.

RFdesign



INCREASE YOUR WIRELESS COMMUNICATIONS COVERAGE

Sponsored Jointly By:

PCS
TODAY

Communications

Cellular Integration



APRIL 24-26, 1996

LAS VEGAS CONVENTION CENTER

LAS VEGAS, NEVADA USA

RF design

SATELLITE

VOZ 4
DATOS

Kee up with the latest in wireless, cellular, PCS, RF and satellite technology at the International Wireless Communications Expo, *featuring* the RF Technology Pavilion.

Explore more than 350 leading suppliers showcasing emerging products and services and an education program delivering timely insights into the wireless applications of today and the future.

NEW FOR IWCE '96

RF Technology Pavilion — featuring an area of more than 6,000 net square feet on the IWCE exhibit floor of RF components. Visit this one-stop shopping source to view and compare the suppliers who facilitate the growing role RF plays in the world of wireless applications.

PCS Pavilion — the Personal Communications Services Pavilion is being introduced as a showcase of new ideas, products and solutions for this emerging technology. It will attract decision makers looking to negotiate their way through this complicated new marketplace. Companies or company PCS divisions participating in the Pavilion will be highly sought out and positioned as a pioneer in providing solutions for new information needs evolving out of the traditional wireless telecom markets.

Make plans now to be in Las Vegas for the most comprehensive industry event covering every inch of RF applications and their impact on the fast-paced wireless market!

**For more information, contact the
International Wireless Communications Expo**

Argus Trade Shows
6151 Powers Ferry Road, NW
Atlanta, GA 30339
404/618-0499 • FAX: 404/618-0441

Robust Power Transistor Market Riding Wave of Emerging Communications Systems

This month's Product Forum covers the RF power transistor market. Several manufacturers offer their opinions regarding the market and technology trends affecting this market segment.


Polyfet RF Devices

Over the past five years Polyfet RF Devices experienced substantial growth and was recognized this year as one of the 50 fastest growing high tech companies in Southern California. Growth came in the areas of cellular base stations, paging base stations and military radios. Polyfet has been offering only gold metallized VDMOS RF transistors. Recently Polyfet introduced a new line of Lateral DMOS transistors. These transistors have the source on the bottom side of the transistor die allowing the die to be directly attached to the heat sink, eliminating the requirement of BeO. Additionally, without having to use wire bonds for the source leads, RF gain is increased by 2-3 dB over the older VDMOS technology. Polyfet sees the trend over the next two years of LDMOS replacing VDMOS and Polyfet is well positioned to support the marketplace with this new technology.

Richardson Electronics

The market continues to grow as applications become more defined and numerous new companies try to grab their niche in this market.

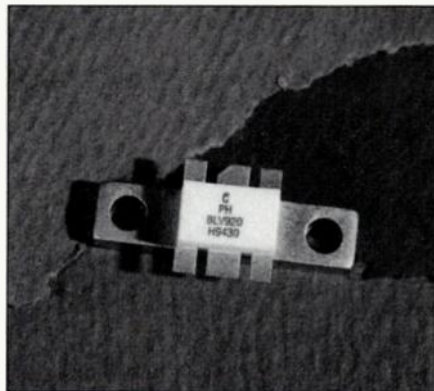In addition to the PCN and Cellular market, one interesting application that has become very active involves reverse cable amplifiers (5 - 100 MHz). For a large variety of reasons, people want to send information through already existing cable TV lines. By not using the standard telephone line, the data rate is 10x faster through the cable TV line. This has



Digital cellular and PCS are driving the production of transistors designed for linear operation in UHF bands. This 20 W transistor, fabricated by Philips and distributed by Richardson Electronics, is designed for class AB amplifiers operating from 820 to 960 MHz.

introduced a variety of new business opportunities.

Time to market is another outstanding variable currently involved in the power transistor market. The customer base that addresses all the different applications are constantly striving to keep themselves up-to-date on the latest products available on the market.

In the last six months we have seen 1.5 - 2.0 GHz PCS applications finally explode as manufacturers have introduced pallets and modules to address them.

Motorola Communications Semiconductor Products Div.

The emergence of PCS has spurred explosive growth in the RF power transistor market. This growth has been driven by two dominant factors, high technology and low cost. The increasing price pressures on the PCS infrastructure market and the need

for high performance microwave devices are now guiding Motorola. We are introducing a new lineup of high performance 2 GHz sub-micron silicon bipolar devices led by the upcoming MRF20060, a 60 W, 9 dB gain base station service device. In addition, we are looking at LDMOS FETs for the same frequency range which could utilize very low cost plastic packaging.

The market should shift into high gear over the next year and be extremely strong for the next three to five years. Motorola is on a program to marshal substantial manufacturing resources, from both wafer fabrication and assembly standpoints, to aggressively service this market need.

SGS-Thomson Microelectronics

The market for RF power transistors is clearly in a growth mode, reflecting the general growth in the total market for RF components, subsystems and systems.

Certain segments are shrinking while others are expanding rapidly - we see the most significant growth in communications and other wireless markets as well as industrial segments. Radar and other military segments on the other hand continue to contract. As a consequence, there is a general move by the suppliers to rationalize product lines and re-orient toward standard products vs. custom in order to be responsive to the price demands of high volume, commercial applications.

While we also see a rapidly expanding market for our power modules in a number of segments, the demand for high power transistors will continue to grow both for both use in modular hybrid amplifiers as well as discrete solutions. The demand will be especially sharp for higher power linear devices, both Class A and AB. RF

RF EXPO PROCEEDINGS

Act Now
And Save!

Quantities
Limited!

Successful engineers like yourself are constantly searching for information to keep them up-to-date on the rapidly changing world of electronic technology. Twice a year, this vital information is presented in the technical sessions and complete tutorial series at the RF EXPOs.

If you were unable to attend a show or particular session — you can now obtain the same information in the RF Expo Proceedings. These proceedings cover almost every paper presented at the shows, topics including:

... PIN diodes, transistors and other RF components ... Direct Digital Frequency synthesizers ... amplifier and oscillator design ... test methods ... and many other essential RF topics.

Now a special opportunity to purchase your own copy of the RF Expo Proceedings at reduced prices.

Hurry, supplies are limited

For editions from 1992 and prior — only \$15 each*

Original price: \$145 each

Please send me the following Proceedings:

- ☐ RF Expo West 95\$145
- ☐ RF Expo East 94.....\$145
- ☐ RF Expo West 94\$100
- ☐ RF Expo West 93\$100
- ☐ RF Expo East 93.....\$100
- ☐ RF Expo West 92 \$15*
- ☐ RF Expo East 92.....\$15*
- ☐ RF Expo West 91\$15*
- ☐ RF Expo East 91.....\$15*
- ☐ RF Expo West 90\$15*
- ☐ RF Expo East 90.....\$15*
- ☐ RF Expo West 89\$15*
- ☐ RF Expo East 89.....**SOLD OUT**.....\$15*
- ☐ RF Expo West 88**SOLD OUT**.....\$15*
- ☐ RF Expo West 87**SOLD OUT**.....\$15*
- ☐ RF Expo East 87.....\$15*
- ☐ RF Expo East 86.....\$15*

Shipping Charge:

\$5 each domestic — outside U.S., add \$30.00 for first proceedings and \$10 for each additional proceedings

Name _____

Title _____

Phone _____

Company Name _____

Address _____

Bldg. No. _____

M/S _____

City _____

State _____

ZIP _____

Country _____

Postal Code _____

Payment: (Payment must accompany order)

☐ Check enclosed

☐ Visa/MC

☐ AMEX

Card # _____

Exp. _____

Signature _____

Date _____

SEND TO: **ARGUS Direct Marketing** • 6151 Powers Ferry Rd NW • Atlanta, GA 30339
OR FAX TO: **(404) 618-0347**

RF DESIGN SEMINAR SERIES

Call for Papers

RF Design Seminar Series — Dallas
January 17-19, 1996 — Sheraton Park Central, Dallas, Texas

Papers are invited for the first RF Design Seminar Series event! Technical presentations on any RF topic are encouraged, with special attention given to papers on recent engineering developments in components and techniques for applications of current interest — Cellular, PCS, WLAN, unlicensed systems, RFID, IVHS, LEO.

Oral Presentations

Oral presentations will be held during the day of January 18. Proposals should indicate whether the paper will require one-half hour or one-hour for presentation, including a question-and-answer period. Papers may cover engineering design or analysis, testing, development case histories, or tutorial material.

Poster Session

A special evening Poster Session will be held from 4 to 6 p.m. on January 17. A social reception will be held in conjunction with this session, providing a relaxed atmosphere for the discussion of your work. Indicate your preference for this session in your proposal. Some papers proposed as oral presentations may be invited to participate in the Poster Session. Exhibiting companies are encouraged to prepare technical papers or applications notes that can be included in this interactive session.

Presenter Benefits

All speakers and poster session participants receive free admission to the technical papers program and a copy of the Proceedings.

In addition, all presenters will be given significant discounts on class fees for the short courses offered at this event. Your contribution to the program is appreciated!

Send a one or two paragraph abstract by October 25, 1995 to:

Gary Breed, Editor
RF Design
6300 S. Syracuse Way
Suite 650
Englewood, CO 80111
Tel: (303) 220-0600
Fax: (303) 267-0234

The RF Design Seminar Series — A Unique Learning Environment for RF Engineers

RF BOOKS

**LOOK AT THESE NEW
1995 PUBLICATIONS!**



RF Design Guide
Peter Vizmuller has written an outstanding reference "cookbook" containing system calculations, circuit examples for the most important RF building blocks, and a great collection of useful formulas for design. Software: A valuable "electronic workbench" database of drawings, text and equations.

(320 pp) #AH-8 \$99.00



Single Sideband Systems & Circuits

A brand-new 2nd edition of this outstanding HF radio handbook by Rockwell-Collins engineers. Includes two new chapters and a disk with filter and amplifier

design programs. Begins with system design and continues with detailed circuit design data on each part of an HF radio.

(650 pp) #MH-2 \$75.00



Mobile Cellular Telecommunications

Updated 1995 edition of a classic reference by William C. Y. Lee. Complete descriptions of cellular systems and concepts. The latest data on GSM, TDMA and CDMA, plus notes on DECT, PCS, PDC, PHS, and other new systems.

(664 pp) #MH-11 \$60.00



Oscillator Design and Computer Simulation

2nd edition of Randy Rhea's #1 guide to oscillator design, presented in a unified approach. Covers a wide range of circuit configurations and resonator types, plus computer design and analysis techniques.

(297 pp) #NP-1 \$64.00

- Order by phone, fax or mail •
- Prices do not include shipping •

Crestone Engineering
5910 S. University Blvd.
Bldg. C-18 #360
Littleton, Colorado 80121
Tel: (303) 770-4709
Fax: (303) 721-1021

VISA • Master Card • American Express/Optima

RF marketplace

Classified display ads are available at \$125 per column inch. Frequency rates available for multiple insertions. Please call for further information, 1-800-443-4969, ask for Shannon Shuman. Or fax your ad copy for a rate quote to (770) 618-0342.

CAREER OPPORTUNITIES

SUNBELT OPPORTUNITIES

Several of our growing commercial major electronic companies located in the southeast have asked us to identify candidates in the mid-level experience range.

- 1) MSEE - Manager R&D - Analog/RF Circuit Design to 90K
- 2) BSEE - Manager - Analog IC Chip Design to 85K
- 3) BSEE - SR RF Design Eng. - Wireless Communications to 70K
- 4) BSEE - SR Design Eng. - Linear IC Chips to 70K
- 5) BSEE - MMIC Design Eng. - L Band Thru KU Band to 70K
- 6) BSEE - RF Test Engineer to 50K

fortune

PERSONNEL CONSULTANTS OF RALEIGH, INC.
P.O. Box 98388R • Raleigh, NC 27624-8388
Phone: 919-848-9929 • Fax: 919-676-5099
Stan Deckelbaum

RF Engineers

Lectrosonics Inc., the world leader in professional wireless microphones, has immediate openings for experienced RF circuit design engineers. Located in the heart of the southwest near Albuquerque for 25 years, Lectrosonics, Inc., has become the recognized wireless standard in broadcast and film/video production.

Two positions are currently available. SENIOR RF DESIGN ENGINEER - BSEE and 10+ years experience; an RF DESIGN ENGINEER - BSEE and 5+ years experience. Both positions are new and result from sustained profitable growth.

Successful candidates will have background in FM receiver and low power FM transmitter design in UHF range, preferably for the commercial/industrial market. Either position requires experience in analog receiver and low powered transmitter design from 500 to 2500 Mhz. Broad knowledge of RF circuitry design and systems to the discrete component level, including use of simulation and analysis software, is essential. Experience with CAD layout of RF PCBs and audio circuitry desirable.

Lectrosonics offers top salaries, excellent benefits, a lower cost of living, the sunny New Mexico climate and a friendly small-company atmosphere where accomplishments are recognized and rewarded.

Qualified candidate should submit cover letter, resume and salary requirements to: Personnel, PO Box 15900, Rio Rancho, NM 87174 or FAX:(505)892-6243 Equal opportunity employer.



LECTROSONICS, INC.

...YOUR CAREER

Filter Design Engineer: B.S. Minimum 3 years experience in the design and development of Broad Band, comb-line strip line, interdigital, low pass and high pass filters, multiplexers, diode switches, (phase shifters), attenuators and microwave sub-systems desirable.

RF Systems Design: Responsible for design of analog and RF systems and circuits for consumer and commercial digital wireless products. Experience with low-cost design techniques for frequency synthesizers, power amplifiers, up/down converters and baseband circuits for digital communications systems. Familiarity with time division duplex or CDMA a plus.

Wireless Consulting Opportunities: Wireless/Cellular, ASIC/DSP/Signal Processing, Algorithm Dev./Distributor Proc., Audio, Speech & Video Compression, Telecommunications/FPGA (XILINX), R.F. Spread-Spectrum/Satellite, Wireless/TDMA/ CDMA/CDPD/Freq. Hop., DataCom/TCP/IP/Network Management, Full Custom CMOS/Mixed-Signal/VLSI, Cellular Engs./Hardware & Software, Analog IC's/MMIC/Device Modeling, Telecom Software/LPOS/PCN/GUI/DOP/ATM/ LAN/WAN/HUB/Ethernet/Gateway; located nationally.

RF Senior Engineers: Aggressive individuals to create and serve new accounts. Positions are located throughout the U.S.A. An engineer who wants to enter sales world is acceptable. Base salary, commission and car. BSEE.

Antenna Engineer: Lead the conception, design and development of a wide variety of antennas and antenna systems including both reflector and array systems using microstrip, stripline, and waveguide technologies. BS/MSEE with 5 years experience.

Regional Field Sales: Aggressive individuals to create and serve new accounts. Positions are located throughout the U.S.A. An engineer who wants to enter sales world is acceptable. Base salary, commission and car. BSEE.

Cellular Engineers: Design/Develop RF and analog circuits for high capacity cellular systems. Requires minimum of 2 years experience in any of the following: DSP, ASIC Design, CAE Development, Digital Modulation, Digital Mobile Communications, Channel Equalizers, Transmitter-Receiver-Synthesizer or Audio Design, Digital Signal Processing.

Wireless Engineers

RF Design Engineers: Design of SI RF-ICs for wireless communication applications (AMPS, DAMPS, GSM, DECT, POS). SI RF-IXC design experience in the 400-2400 Mhz; fast RF PLL synthesizer design experience; RF receiver/transmitter/design experience using Si bipolar and MOS technologies.

RF Small Signal and RF Power AMP System Engineers: Requires detailed technical knowledge of cellular and PCS systems with experience designing RF XMTRS and RCVRs. Need 5+ years' related experience in RF.

Design Engineer Communications ICs: Requires B.S.E.E. (M.S.E.E. preferred) and 5+ years experience. Individual will be responsible for leading the design and characterization of high frequency transceiver ICs for wireless communications applications. Design includes circuit integration of baseband, converter and RF/IF circuitry.

MMIC Engineer: Develop L/S band GAA's MMIC power amplifiers for commercial wireless communications. Requires: M.S. or BSEE, +2 years experience with GAA's MMIC design, simulation, packaging and test.

RF Engineer: Design RF portions of digital video home terminals (set top boxes) in new Video Entertainment Systems now under development. The engineer will be responsible for the design of the RF receivers (tuners)/transmitters. The engineer will join a growing team developing a line of low-cost, high volume terminal for a variety of interactive video services. 5-900 Mhz.

Mechanical Engineers: You will be responsible for the cellular phones and paper design from mock up, detail design, prototyping through production tooling. You must have BSME and 5+ years of product development experience. High volume, consumer electronic product related experience is essential.

MICRO COMMUNICATIONS
EXECUTIVE SEARCH

871 Turnpike St. • North Andover, MA 08145

We specialize in the placement of communications both nationally and internationally.

FOR THESE AND OTHER OPENINGS
CALL COLLECT: TEL: 508-685-2272

FAX: 508-794-5627

RF & CELLULAR POSITIONS AVAILABLE

Immediate RF and Cellular Positions Available

Tel: 1-800-527-0373

Fax: 1-800-784-0499

CDI

CDI TELCOM, INC.
2425 N. Central Expressway
Suite 101
Richardson, TX 75080
EOE

ITS CORPORATION

information
transmission
systems

Visibly Better Technology

ITS Corporation is a leading manufacturer of television transmitter systems located in a suburb of Pittsburgh. We are seeking candidates for the following new position:

DESIGN ENGINEER

An experienced design engineer with RF and video circuit experience. BSEE required.

ITS CORPORATION
HR Department
375 Valley Brook Road
McMurray, PA 15317-3345
FAX: (412) 941-4603

ITS is an EOE and promotes a tobacco-free work environment

RF DESIGN MARKETPLACE WANTS YOU!



**CALL
(800) 443-4969
FOR DETAILS.**



National and International Assignments
RF Engineers/Cellular Installers
CATV Engineers and Strand Mappers
OSP Engineers Right Of Way Agents
Project Managers, OSP Contract Specialists
CAD/Draft Operations
Call: 800-431-2806
FAX: 914-592-7246
Send Resume to: 37 East Main St.
Elmsford, NY 10523

**COMMUNICATIONS
RF DESIGN**
Executive and Technical Openings
Throughout the United States

Lanni Johnson, CPC



OF ALBUQUERQUE, INC.

505-262-1871

FAX 505-268-4954

Excel of Albuquerque, Inc.
excelalb@ix.netcom.com
1700 Louisiana NE, Suite 210
Albuquerque, New Mexico 87110

MIDWEST IOWA MIDWEST OPENINGS

RF COMMUNICATIONS EQUIPMENT DESIGN ENGINEERS
B.S./M.S., 2 to 8+ years experience, base-band to 3.0 GHz, in any of the following: Receivers, Transmitters, Power Amplifiers, Synthesizers, Spread Spectrum, RF ASIC/MMIC Design, Modems, Communications DSP. Desire strong analytical skills and experience in RF circuit simulation using RF CAE tools. Multiple openings with top commercial companies in attractive Midwest locations. Reply with assured confidentiality to:

DON GALLAGHER MSEE
Gallagher & Associates
1145 Linn Ridge RD. MT. Vernon, IA 52314
Phone: 319-895-8042 Fax: 319-895-6455
RF Engineering Recruiting for Midwest Clients Since 1987

ENGINEERING OPPORTUNITIES

**PCS/PCN/CELLULAR/CDPD
RF/HW/SW/FW/DSP
Terminals/Systems**

FITZPATRICK & ASSOCIATES

P.O. Box 32546 • Phoenix, AZ 85064-2546
E-Mail: FITZPAT@ix.netcom.com
FAX: (602) 956-7644



Without Tears™

**Learn DSP and put your knowledge to work
IMMEDIATELY!**

To receive an informative brochure on this popular seminar, call
Z Domain Technologies, Inc. at **1-800-967-5034**,
404-587-4812. Hours: 9 - 5 EST. Or E-mail dsp@mindspring.com
Also, a 2-day ADVANCED class in DSP is available on a
limited basis -- call for more details.

**By taking this 3-Day Course, you will really
learn DSP. Guaranteed!**

Coming to a City Near You:

Washington DC - Dallas TX - Atlanta GA - San Jose CA - Scottsdale AZ

Teradyne is a leader in the fast growing Automated Test Equipment (ATE) industry. We provide customized, creative solutions to some of the world's fastest growing companies. Our diverse product line includes: automatic test systems for all types of integrated circuits (linear, mixed signal, memory), circuit board and telecommunications test systems and design automation software. We offer the opportunity to work in a challenging team-oriented environment in the following areas:

VHF DESIGN ENGINEER

Responsibilities include design and development of high performance, high frequency instrumentation, including DSP based arbitrary waveform generators and digitizers. Product definition, technology development and product design are key elements of this role.

Qualified candidate will possess BSEE (MSEE preferred) with 5-10 years of high frequency analog design experience. Knowledge and instrumentation of high frequency waveform generators and measurement instrumentation operating at frequencies from DC to 500 MHz is a must. Working knowledge of low distortion amplifiers, up-down converters, filters and sample/hold circuits is required. C programming, spice modeling and touchstone simulation are pluses.

MICROWAVE DESIGN ENGINEER

Responsibilities include the design and development of hardware used in RF and microwave test instrumentation. Encompasses all project phases, from concept and proposal through release. Part of a team developing strategy for system architecture and calibration.

BSEE/MSEE or equivalent with 5-10 years' direct experience in microwave front end design (to 12 GHz). A thorough knowledge of RF/Microwave instrumentation calibration methods and microwave test measurement techniques is essential.

MICROWAVE TEST ENGINEER

Responsible for yield, process and reliability improvement for microwave instrumentation. Provide support to test technicians involved in testing, diagnosing and repairing microwave modules and assemblies.

BSEE/BSET or equivalent, along with 3+ years' experience working with microwave applications up to 6 GHz. Strong communication skills are a plus.

Teradyne offers an outstanding compensation and benefits package, profit sharing, stock purchase plan, and a 401(k) savings plan. Please send resume and salary history to: Jim Kennedy, Teradyne, Inc., 321 Harrison Ave., Boston, MA 02118; fax (617) 422-2080. See our home page on the World Wide Web <http://www.teradyne.com> An equal opportunity employer, M/F/H/V.

TERADYNE

Rantec Microwave & Electronic, Inc., a world leader in the construction of shielded Anechoic Test Chambers, is seeking the following individual to join its newly relocated facility in Austin.

RF Engineer

Responsible for the design of EMC/RCS/microwave absorber materials and anechoic chambers. Involves developing new products/processes, performing on-site chamber certification tests and generating technical proposals. Will also interface with customers performing EMC tests and antenna measurements. The successful candidate should have at least a BS degree in EE - majoring in antennas and electromagnetics. The candidate should have a working knowledge of anechoic chamber antenna measurements. RCS testing and instrumentation. Experience with network analyzers, microwave sources/receivers, antennas and positioning equipment is essential, as well as strong programming skills (Fortran, HP basic). C++ and materials science expertise would be ideal. Excellent verbal/written communication skills and the willingness to travel are required for this position.

Rantec offers competitive salaries and an excellent benefit package including a smoke and drug-free environment. For immediate consideration, please send your resume including salary history to:

Rantec Microwave & Electronics, Inc.
c/o EMCO
P.O. box 1546
Austin, TX 78767
Attn: Human Resources

*** RF ENGINEERS - ALL LEVELS ***

Design/Test/Project (BS/MSEE)
Quality/Manufacturing (BSME/IE/EE)

** FOR BROADBAND/CATV INDUSTRY LEADERS **

"Plus" Backgrounds Include:

Analog/Digital Design
Fiber Optics/Lasers
Amplifier/PIN Diode Circuits
Touchstone/Eagleware/Spice/Compact
CAD/AutoCAD/MathCAD

*ASK ABOUT EXCLUSIVE BONUS, ALL POSITIONS *

Females and minorities encouraged to apply. We represent equal-opportunity firms. All fees company paid.

**CHRISTIE
ASSOCIATES**

10955 Jones Bridge Road
Suite 131-264
Alpharetta, Georgia 30202
Telephone: (770) 772-7175
FAX: (770) 772-7177

RF DESIGN ENGINEERS

World-Class Designer of advanced

X'tal oscillators to develop new technologies/packages in well equipped labs. Min 10 yrs rel exp. in high stability/low-noise OCXOs. Knowledge of GPS, Telecom, Space, SMT, Hybrids a plus. MSEE pref.

Project Engineer required to design

quartz X'tal oscillators, TCXOs/VCXOs. Min 5 yrs rel exp. 1 MHz to 1 GHz range, including PLL's, ASICs; use CAD/CAE, simul, hands-on; SMT/Hybrids req. MSEE pref. Excellent benefits. Send resume w/sal requirements to:



VECTRON LABORATORIES
M. Beccarelli
P.O. BOX 5160 • Norwalk, CT
06858
Fax: (203) 849-1423

The Crystal Oscillator Company

EOE/M/F/V/D

Nationwide opportunities in the
CELLULAR/WIRELESS industry.

Debra Sola-Furnari
TELE-TECH SEARCH
4773 Split Rail Place
W. Melbourne, FL 32904
(407) 951-4200 FAX (407) 951-0808


By The Time Other Companies Have Developed The Idea, We've Developed The Technology.

At Ericsson Inc., we've navigated the evolution of communications technology for more than a century. Because our unwavering mission has always been to develop the technological capabilities others have just begun to contemplate.

Our team of inventive and creative visionaries works in symbiotic accord to produce advances that don't just make global communication easier and better — but that make history. Our engineers, scientists and technicians are given the unbridled freedom to imagine. The rare opportunity to turn imagination into technology. And the chance to develop myriad technological firsts, including our imminent development of the world's first dual mode cellular/satellite hand-held portable phone.

It is our goal to continue assembling experts whose level of technical acumen is surpassed only by their level of imagination. And to not only continue moving ahead of our competition, but to move ahead of our time.

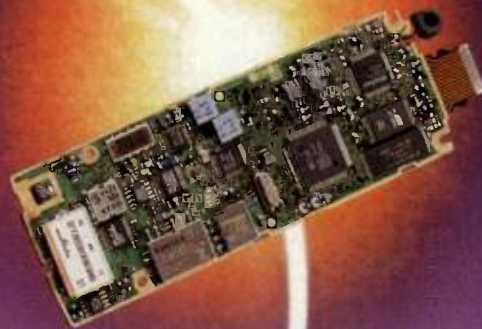So join us. And help us change the way the planet communicates.



R.F. DESIGN ENGINEERS—B.S.E.E. and 5+ years experience in R.F. circuit design to the component level, system design, or receiver/transmitter design within the wireless industry coupled with the desire to work in the areas of transmitters, receivers or synthesizers. Job Code 95RFSE9.

R.F. SENIOR DESIGN ENGINEERS—B.S.E.E. (M.S. desirable) and 7+ years experience in radio R.F. design, R.F. ASIC definition/design or power amplifiers coupled with a desire to work in the areas of transmitters, receivers or synthesizers. Job Code 95ASICSE8.

R.F. ASIC DESIGN ENGINEERS—B.S.E.E. and 3+ years of BiPolar or CMOS radio applications experience. Job Code 94RTP72.

R.F. DEVELOPMENT ENGINEERS—B.S.E.E. and 2+ years R.F. design experience and familiarity with AMPS and DAMPS. Job Code 95RMOA57.

STAFF ENGINEERS, INTEGRATION & CONFIGURATION—B.S.E.E. or B.S.E.T. and 3+ years experience in systems verification and test specification for telecommunications equipment coupled with an interest in cellular radio base station equipment and AKE digital switch test configuration. Job Code 95RMOA128.

If you have what it takes to join the team that's changing the way the world communicates, send your resume to:

Attention: Ernie Leskovec
Ericsson Inc., One Triangle Drive
P.O. Box 13969, Mail Drop RF0995
Research Triangle Park, NC 27709
Or fax us at: 919-685-2610



ERICSSON 
FOR THE HIGH-TECHKNOWLEDGEABLE SM

"AN EQUAL OPPORTUNITY EMPLOYER — AFFIRMATIVE ACTION EMPLOYER. M/F/HDCP"

TV/COM International, Inc., a subsidiary of Hyundai Electronics America, is a world leader in high performance delivery solutions for cable, satellite, and terrestrial television networks including secure access control systems.

RF MODULATOR DESIGN ENGINEERS

RF system analysis, design, performance allocation, and test characterization for QPSK modulators. Knowledge of analog/RF hardware interaction with digital modem hardware, high speed conversion, component/design tradeoffs, statistical yield optimization techniques, and PC based design tools. Some positions require rapid design capture, breadboard, and test of new designs as well as parts selection and evaluation. BSEE/MSEE, 5-10+ years exp. (Code 63H)

RF RECEIVER DESIGN ENGINEER

RF system architecture, analysis, design, performance allocation, and test characterization for high volume/rate consumer digital satellite and cable modem front ends (50-2500 MHz). Knowledge of receiver design, QPSK, QAM, interaction of analog/RF hardware with digital modem hardware, high speed analog-to-digital conversion, component/design tradeoffs, statistical yield optimization techniques, and PC based design tools. BSEE/MSEE, 10+ years exp. (Code 64H)

Send resume to:
Human Resources-RF0901,
TV/COM, 16516 Via Esprillo,
San Diego, CA 92127
or fax to (619) 451-1505.



TV/COM

ENGINEERING MANAGER

HARRIS RF Communications, a leader in the design and production of high performance HF, VHF and UHF radio equipment and communications systems for government and military customers worldwide, has an opening for an Engineering Manager. The successful candidate will head a rapidly growing R&D and program group developing advanced radio products and peripherals. Reporting to an Engineering Director, and working closely with a Business Line Vice President, you will play a significant role in determining product and program strategy.

This position requires a minimum of 8 years' experience in radio product development, and demonstrated project leadership in a team-oriented environment.

Our Rochester location in picturesque upstate New York offers a progressive, modern city with a recognized high quality of life. Cultural and entertainment attractions abound and mountains, lakes, open rural countryside and Canada are all nearby. The school systems are excellent, both for your children and for your advanced studies.

Please send resume to: Rebecca Shaw, Harris Corporation, RF Communications Division, 1680 University Ave., Rochester, NY 14610. e-mail: rls4@RFC.Comm.Harris.Com. FAX: (716) 242-4067 or 242-4711.

We are an equal opportunity employer and value a diverse work force.



WIRELESS ENGINEERING OPPORTUNITIES with MOBILE SYSTEMS INTERNATIONAL

Mobile Systems International (MSI) currently has engineering positions open for RF and Network engineers. MSI is a world class company with a reputation for providing high quality advanced consulting support to telecommunications, PCS/PCN, ESMR, Cellular, and Paging operators, as well as other wireless system operators worldwide. MSI offers a wide range of services covering CDMA, GSM, IS-54 TDMA, AMPS, MIRS, Paging, and other wireless technologies. Typical services provided to our customers include:

- Radio, Signaling, and Network System Planning and Design
- Technology and Vendor Selection
- New Technology Integration
- Strategic and Management Consultancy
- System Dimensioning
- System Design Audits
- System Performance Monitoring
- Technical Training

MSI offers the opportunity not only to be involved with all of the newest wireless technologies but to also work with a group of highly qualified and experienced engineers. At MSI our engineering team takes pride in holding themselves to the highest engineering standards. Applicants should possess a BSEE or MSEE degree with a minimum of 1 year experience in the wireless engineering industry, and must be innovative as well as highly detail and results oriented. Excellent presentation and technical writing skills are also required. Other useful skills include knowledge of DOS and UNIX operating systems, microwave engineering, networking of wireless communications systems including GSM, IS-41 and SS7, development of RF propagation models, traffic engineering, and knowledge of antenna and receiver design principles. Travel may be required.

We at MSI are committed to further expanding our RF and Network engineering consultancy by the addition of experienced, well qualified wireless engineers. Engineers are needed in our Chicago, Dallas, Atlanta and Washington DC offices as well as other customer locations throughout North and South America and Asia. If you are a highly motivated engineer who meets the above mentioned qualifications MSI is the career move you are seeking. Please send your resume in strictest confidence to the address below. MSI is an equal opportunity employer.



MOBILE SYSTEMS INTERNATIONAL
Personnel Department
One Lincoln Centre, Ste 200 • Oakbrook Terrace, IL 60181
Fax: (708)261-3028

Not All High-Tech People Qualify To Be On An Argus List.



Rent the circulation file of
this publication for your
direct mail needs. For our
complete catalog, call
Kristin at
(770) 618-0479.

A
ARGUS
DIRECT
BUSINESS LIST

RECRUITMENT

PCS RF NETWORK ENGINEERS TO MID \$70's
PCS ANTENNA ENGINEERS TO \$80's
PARABOLIC RF & MECHANICAL ENGINEERS TO \$70's
Please fax resume in confidence to
916-549-4168
RANDALL F. CHAMBERS & ASSOCIATES
"Wireless Recruiting Professionals"
PO Box 723, Bella Vista, CA 96008 * Tel 916-549-5331

COMMUNICATIONS ENGINEERS

Our clients are hiring RF engineers with the following skills:

Wireless Telecomm, Cellular, Mobile, Telephony, NPDS, spread spectrum, DSP, AMPS, SMR, GSM, CDPD, TDMA, CDMA, WLAN, WPBX, Transmitters, Receivers, modulators, demodulators, low noise amps, mixers, oscillators, filters, DDS, synthesizers, 900/1900 MHz.

- ✓ Never a fee to applicants.
- ✓ Positions available nationwide.
- ✓ Send email, fax, or call Randy Brei today!

Brei & Associates, Inc.
P.O. Box 445 Marion, IA 52302-0445
(319)377-9196 FAX (319)377-9219
RBREI@NETINS.NET
<http://www.NETINS.NET/showcase/RDBREI/>

MR MANAGEMENT RECRUITERS OF BOULDER, INC.
The search and recruiting specialists

WINDY BRADFELD
RF / MICROWAVE SPECIALIST

CONTINENTAL BLDG., SUITE 301
1401 WALNUT STREET, P.O. BOX 4657
BOULDER, COLORADO 80306
(303) 447-9900
FAX(303) 447-9536

Peter Froehlich & Co.
executive search

SCTE Sustaining Member

Engineering Positions Available:

Senior RF Design,
Test • Digital • Analog
Market Development
Software Applications
Fiber Optic Electrical
Applications • Reliability
Manufacturing

Call or write. Fees paid.
P.O. Box 339 Weatherford, TX 76086
(800) 742-4947 • Fax: (817) 594-1337
E-Mail: 72774.3617@compuserve.com

SOFTWARE

Waypoint Software
1950 Beavaria Drive #317
Colorado Springs, CO 80918
(719) 596-9592
(WaypointSW@aol.com)

Only \$199.95
(+GST)

Reference past advertisements for additional features.
No greater value exists for frequency conversion software

RF DESIGN

Marketplace

(800) 443-4969

PRODUCTS & SERVICES

NOLAN LABORATORIES, INC.
Consulting, Design, Test and Manufacture
FOR
RF, Microwave, Antennas, Electromagnetics, EMI/RFI, Bioelectromagnetic Sensors
Design and Support for Manufacturability
James A. Nolan, MSEE PO Box 567
President Conifer, CO 80433-0567
(303) 838-0057

PS-2A SERIES PORTABLE SPECTRUM ANALYZERS

HIGH PERFORMANCE AND EASY OPERATION



Price \$1895

- 0.1 - 1000MHz range in one scan, (0-1000MHz in 11 selectable span widths)
- Measurable Range -108 dBm to +20 dBm
-118 dBm to +20 dBm (optional PS-2A Special)
- 5 resolution bandwidths (10 KHz - 1 MHz)
- 50dB input attenuator in 10dB steps
- 2 / 10 dB LOG scale display with base line clipper
- Multi-tune tuning
- Built-in AM / FM demodulation with speaker
- Digital controlled center frequency display
- Tracking generator (optional PS-2A TG-01)
- 3 way power sources (optional +12 VDC battery)
- Compact size (10.3"W x 4.0"H x 12.3"D), light weight (approx. 10 lbs)
- Switchable 18V DC power out of the RF input connection (optional)

V TECH Instruments, Inc. 171 Burns Ave., Lodi, NJ 07644
TEL: 201-546-7635 FAX: 201-546-7651

1GHz RF SIGNAL GENERATOR

AM/FM, 100 KHz through 1 GHz
Quality crafted in the USA



Finally, a synthesized signal generator that's designed to help you generate more than just signals. The Ramsey RSG-10, is the signal generator you can afford, the signal generator that's designed to do what a signal generator is meant to do - provide a very stable, accurate, easy to control signal from 100 KHz to 1.0 GHz.


For the price, you wouldn't expect any more. But, there is more to the RSG-10. An intelligent microprocessor controlled/programmable memory, for example, can store up to 20 of your most commonly used test set-ups. And unlike other units, just one touch of the memory exchange button is all it takes to quickly shift from one test set-up to another. You get more work done, easier and faster.

At \$2495, the Ramsey RSG-10 is your profit generator.

RAMSEY

RAMSEY ELECTRONICS
793 CANNING PARKWAY, VICTOR, NY 14584
Fax: (716) 924-4555
TELEX: 466735 RAMSEY CI

ORDER DIRECT—CALL 1-800-446-2295

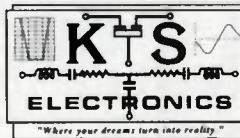

- STD. 5 AND 10 MHZ OXCO
- TCXO • VCXO • TC-VCXO
- VCO's • CLOCK OSCILLATORS
- CUSTOMIZED CRYSTAL FILTERS
- STD. 10.7 MHZ, 21.4 MHZ and 45 MHZ
- L/C FILTERS
- STANDARD IF FREQUENCY CRYSTALS
- SURFACE MOUNT AND LEADED PACKAGE

Call or Fax requirements.
16406 N. Cave Creek Rd. #5
Phoenix, AZ 85032-2919
Phone & Fax (602) 971-3301

RF DESIGN MARKETPLACE (800) 443-4969

RF LITERATURE/PRODUCT SHOWCASE

GOULD POWERDEX

Thin Lithium Batteries
As thin as 0.7 mm



- Thin rectangular format
- High energy density
- Customized capacity
- Solder or pressure contacts
- Available in 3 and 6 volt



family of products:

- Standard: A, B, C sizes
- Ultrathin: less than 1 mm
- Customized: capacity and/or size
- Rechargeable: call for information

Gould Electronics Inc., Electronic Power Sources
35129 Curtis Blvd. Eastlake, Ohio 44095-4001
Phone: (216) 953-5059 Fax: (216) 953-5152
Toll Free: 1-800-722-7890
(U.S. & Canada)



The filter design tool
that does it all...for less.

- Lumped, Distributed and Hybrid Circuits
- Mechanical Dimensions for Distributed Circuits
- Pole Placed Transfer Functions
- Much More

\$995 Complete
Domestic Shipping Included


FILTROID



Distributed By
Amber Technologies, Inc.
(508) 369-0515
FAX (508) 371-9692



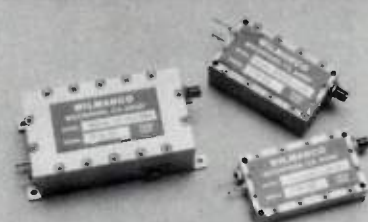LOW COST HIGH PERFORMANCE FREQUENCY SOURCES



- ✓ MODEL VSA - \$195.00 .01 GHz TO 1.0 GHz
- ✓ MODEL USA - \$245.00 1.0 GHz TO 1.8 GHz
- ✓ MODEL SSA - \$295.00 1.8 GHz TO 4.2 GHz

RF OUTPUT: +8dBm min., SMA Connector
FREQ. STABILITY: ±30ppm, -20°C to +60°C
B+: +12 to +16 VDC

Wilmanco

5350 Kazuko Court, Moorpark, CA 93021
(805) 523-2390 FAX (805) 523-0065

NEC-Win Basic for Windows™

\$75.00 !



First Integrated Antenna Design & Analysis Program for Windows Under \$100 Supporting NEC2

Features Include:

- Intuitive Graphical User Interface
- Powerful Azimuth and Elevation Plotting
- Three-Dimensional Radiation Patterns
- Automated VSWR, Beamwidth, F/B Ratio, Input Impedance and Current Calculations

Paragon Technology, Inc.
200 Innovation Blvd, Suite 240
State College, PA 16803
E-mail: NecWin@aol.com
(814) 234-3335 Fax: (814) 234-0228

INFO/CARD 83

TESLA

Communications Simulation



Still Only \$695!

Why is TESLA winning all these awards? It's simple and easy to use, yet it does full RF non-linear, mixed analog & digital simulation. Why not see for yourself? Call now:

800-631-1113

TESOFT Inc. 404-751-9785 Fax 404-664-5817
PO Box 305 Roswell GA 30077

INFO/CARD 84

CRYSTAL OSCILLATORS AND OVENS



- * High stability crystal oscillators and ovens for:
- * Test equipment frequency standards
- * Global position systems
- * Cellular telephone communications
- * Paging transmitters & TV studio equipment
- * Navigation and many other applications
- * OCXOS, TCXOS, VCXOS, AND CRYSTAL OVENS

Write or call us with your requirements
ISOTEMP RESEARCH, Inc. P.O. Box 3389
Charlottesville, VA 22903

INFO/CARD 85

RF/Microwave

Frequency Sources


- CRO, DRO, LC Microstrip Designs.
- Free Running or Phase Locked.
- Designs Matched to Your Requirements.
- Cost Effective, High Quality Custom Design and Development.
- Fax or Send Requirements for Quick Response.

Signal Microwave Electronics

4764 Rayford Street
Jacksonville, Florida 32254
Phone: (904) 384-7023
Fax: (904) 384-9144

INFO/CARD 86

EMC Testing Made Easy

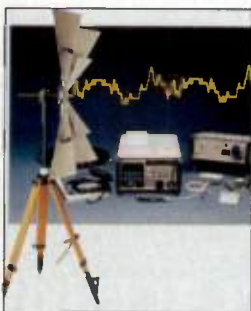

Wayne Kerr's EASY 1 is an Emissions Assessment System for pre-compliance EMC testing of conducted and radiated emissions. The turnkey system works with Windows and includes the SSA

1000A Spectrum Analyzer, GPIB card for the PC, and all required antennas and probes for open area testing from 30 MHz to 1GHz. You can use EASY 1 to meet FCC/VDE/ CISPR/EN/CENLEC/EMC standards. A free demo disk is available.

Wayne Kerr, Inc.
11 Sixth Road
Woburn, MA 01801-1744
Tel: 617-938-8390
Fax: 617-933-9523

INFO/CARD 87

RF POWER AMPLIFIERS



200 W • 150-200 MHz • 55% Efficiency • 35dB Gain

1 MHz-2GHz 1W-1KW

- Small Size • High Efficiency • Durable
- Module and Rack Mount Systems
- Customization Available




651 Via Alondra, #712
Camarillo, CA 90312 USA
TEL: (805) 388-8454
FAX: (805) 389-5393

INFO/CARD 88

GaAs MMIC SPDT Switch

\$1.79ea
(Qty 2500)

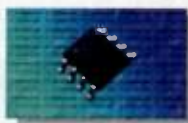- Positive/Negative Control Voltage
- DC-2.5 GHz
- For DCS1800, Wireless LAN, Radio and Cellular Equipments
- SMT SO-8 Package
- Tape and Reel available



Parameter	Test Conditions	Unit	Typ.
Insertion Loss	1MHz-0.5 GHz	dB	0.5
	1MHz-1 GHz	dB	0.6
	1MHz-2 GHz	dB	0.7
Isolation	1MHz-1 GHz	dB	33
	1MHz-2 GHz	dB	25
VSWR	1MHz-1 GHz		1.2:1
	1MHz-2 GHz		1.3:1
Input Power	@ 1 dB compression with 5V control voltage (>100MHz)	dBm	29

For free samples, call (703)690-8909 or fax (703)690-8414

Hexwave, Inc. P.O. Box 7205, Fairfax Station, VA 22039-7205
*High Isolation model also available, please call for catalog.

INFO/CARD 89

Custom Ceramic Filters



- Proprietary Pole/Zero Design Technique yields steep shape factors with low loss
- Frequency Range: 500 - 3000 MHz
- Bandwidths up to 5%
- 4, 6, and 12 mm Profiles
- Moderate to large volume

We give you what you want, not what's on our shelf!



228 Northeast Rd
Standish, Me. 04084
Phone: (207) 642-4535
Fax: (207) 642-0198

INFO/CARD 90

Custom Power Amplifiers at "off the shelf" Prices and delivery

For catalogue call

408-448-3342

FAX

800-416-7934

(510-279-5912)

PTEK


INFO/CARD 91

The Buyers' Guide is a convenient guide to suppliers of products and services available for design and development engineers. Buyers' Guide listings are sold on an annual basis at the rates shown.

Regular Listing	\$22.00
Additional Line	\$19.00
Bold Listing	\$25.00
Additional Line	\$21.00
1" Ad	\$200.00
Drop Out In White	\$25.00

Per Issue	\$22.00	Total/Year	\$264.00
	\$19.00		\$228.00
	\$25.00		\$300.00
	\$21.00		\$252.00
	\$200.00		\$2,400.00
	\$25.00		\$300.00

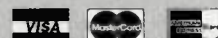All orders must be prepaid. You can forward your check or charge your ad to:



For information on closing dates and details on a special Introductory Offer, call 1-800-443-4969. Ask for your yellow page representative.

DISCRETE COMPONENTS

CAPACITORS

Chip	
Sprague Goodman, 134 Fulton Ave., Garden City Park, NY 11040-5395	(516) 746-1385
Vacuum	
COMET North America, 11 Belden Ave., Norwalk, CT 06850	(203) 852-1231
Surcom Associates, Inc., 2215 Faraday Ave., Suite A, Carlsbad, CA 92008	(619) 438-4420
Variable	
COMET North America, 11 Belden Ave., Norwalk, CT 06850	(203) 852-1231



TRIMMER CAPACITORS, INDUCTORS AND MICROWAVE TUNERS

1700 Shames Drive, Westbury, NY 11590
Tel: 516-334-8700 • Fax: 516-334-8771

CRYSTALS/RESONATORS

H.K. Crystals Co., Unit H, 22/F, Shield Ind. Ctr.,
34-36 Chai Wan Kok St., T.W. H.K. Tel: (852) 4120121 Fax: (852) 4985908



Custom Crystals 60KHz - 200MHz Oscillators and Elements

Sales and Service: 1-800-725-1426

Quartz



American KSS Inc.

QUARTZ CRYSTAL PRODUCTS

Corporate Office	Eastern Regional Office	Southern Regional Office
3295 Scott Blvd., Suite 100 Santa Clara, CA 95054 Tel: (408) 986-9577 Fax: (408) 986-1717	401 E. Louthier St. Carlisle, PA 17013 Tel: (717) 243-6008 Fax: (717) 243-4343	5696 Peachtree Parkway Norcross, GA 30092 Tel: (770) 263-3768 Fax: (770) 263-3769



REEVES-HOFFMAN DIVISION DYNAMICS CORPORATION OF AMERICA

For your AT Crystal requirements, including High Frequency Fundamental Oscillator Crystals up to 155.52 MHz and Filter Crystals to 150 MHz HFF.

400 W. North St., Carlisle, PA 17013, Tel: 717-243-5929, Fax: 717-243-0079

CRYSTAL OSCILLATORS

- AC MOS TTL to 200 MHz
- HCMOS TTL to 80 MHz
- ECL to 630 MHz
- VCXOs to 200 MHz
- SMD to 300 MHz

FUNDAMENTAL Crystals to 350 MHz

800-982-5737 (ext. 244)

Valpey-Fisher Corporation • 75 South Street • Hopkinton, MA 01748 Fax: 508-497-6377



DIODES

Loral Semiconductor Division, 75 Technology Dr., Lowell, MA 01851(508) 256-4113 ext.3311

Varactor

Knox Semiconductor, Inc.
13 Quarry Rd., P.O. Box 609, Rockport, ME 04856(207) 236-6076 Fax(207) 236-9558

INDUCTORS

Ferrite Cores

Sprague Goodman, 134 Fulton Ave., Garden City Park, NY 11040-5395(516) 746-1385

Fixed

Sprague Goodman, 134 Fulton Ave., Garden City Park, NY 11040-5395(516) 746-1385

RF Design

INTEGRATED CIRCUITS/MCM



RF & Wireless Microcircuit Assembly GaAs MMIC • High Speed Analog MCM

Colorado Microcircuits, Inc.

1106A Boise Ave.
Loveland, CO 80537

Call for Free Proposal
(970)663-4145

Micro Hybrids, Inc., 2864 Route 112, Medford, NY 11763(516) 732-3448

NEC Wireless Semiconductor Products

Small Signal & Power GaAs FETs Small Signal & Power Bipolars
Silicon & GaAs MMICs: Amplifiers, Prescalers, Downconverters

California Eastern Laboratories

4590 Patrick Henry Dr. Santa Clara CA 95054-1817 408-988-3500 FAX 408-988-0279

RF, Analog & Mixed-Signal ASICs

Full-Custom Designed ICs: Bipolar, CMOS, BiCMOS
Frequency Synthesis, Mixers, Amplifiers, A/Ds, D/A's, Switched Cap Circuits

RTG, Inc.

TEL: (310) 534-3016 • FAX: (310) 534-3728
P.O. Box 3986, Torrance, CA 90510 • E-MAIL: sales@rtg.com

MODULAR COMPONENTS

AMPLIFIERS

Broadband

Dressler HF Technk GmbH,
Werther Str. 14-16, D-52224, Stolberg, Germany+49-2402-71091 Fax: (-71095)

Trontech, Inc., 381 Industrial Way East, Eatontown, NJ 07724(908) 542-113 Fax (908) 542-1118

RF Power

Silicon Valley Power Amplifiers, 529 Forman Dr. # B, Campbell, CA 95008(800) 986-9700

FILTERS

Delta Microwave Inc., 840 Vira Alondra, Camarillo, CA 93012(805)987-6892

Crystal

Reeves-Hoffman, 400 W. North St., Carlisle, PA 17013(717) 243-5929

I&Q

Merrimac Industries, Inc.,
41 Fairfield Pl., W. Caldwell, NJ 07006(201) 575-1300 Fax (201) 575-0531

Saw

Phonon Corp., 7 Herman Dr., PO Box 549, Simsbury, CT 06070(203) 651-0211
SAW Components & SubsystemsFax (203) 651-8618



RF Monolithics, Inc.

SAW-based RF Components and Modules for the Low-Power
Wireless, High-Frequency Timing, and Telecommunications Markets

Transmitters • Receivers • Resonators • Oscillators • Clocks • Filters
Call, write, or fax for a free product data book.

4441 Sigma Road
Dallas, Texas 75244 U.S.A.
Tel: 214/233-2903, Fax: 214/387-8148

MIXERS

Merrimac Industries, Inc.,
41 Fairfield Pl., W. Caldwell, NJ 07006(201) 575-1300 Fax (201) 575-0531

MODULATORS

FSK

Merrimac Industries, Inc.,
41 Fairfield Pl., W. Caldwell, NJ 07006(201) 575-1300 Fax (201) 575-0531

MODULAR COMPONENTS

OSCILLATORS



REEVES-HOFFMAN
DIVISION DYNAMICS CORPORATION OF AMERICA

For your Crystal Oscillator requirements, Clocks, TCXO's, VCXO's, OCXO's, Hybrid & Discrete.

400 W. North St., Carlisle, PA 17013, Tel: 717-243-5929, Fax: 717-243-0079

Valpey-Fisher Corp., 75 South St., Hopkinton, MA 01748.....(508) 435-6831 Fax (508) 435-5289

Crystal

Oak Frequency Control Group,

100 Watts St., PO Box B, Mt. Holly Springs, PA 17065.....(717) 486-3411

Saronix, 151 Laura Ln., Palo Alto, CA 94303.....(415) 856-6900 (800) 227-8974

Wenzel Associates, Inc., 1005 La Posada Dr., Austin, TX 78752.....(512) 450-1400

Microwave

Electronic Surveillance Co., Inc., 33328 Howe Ln., Creswell, OR 97426.....(503) 895-5071

SYSTEM SUBASSEMBLIES

AMPLIFIERS

Broadband

Trontech, Inc., 381 Industrial Way East, Eatontown, NJ 07724...(908) 542-1133 Fax (908) 542-1118

LNA

Trontech, Inc., 381 Industrial Way East, Eatontown, NJ 07724...(908) 542-1133 Fax (908) 542-1118

Linear Power, RF

PACIFIC AMPLIFIER CORP. (805) 375-5773

- LO-MED-HI-POWER LINEAR AMPLIFICATION
- CELLULAR, TELEPHONY MULTI CHANNEL USE
- -30 dBc STANDARD; -60 dBc FEED FORWARD

RF Power

Trontech, Inc., 381 Industrial Way East, Eatontown, NJ 07724...(908) 542-1133 Fax (908) 542-1118

High Dynamic Range

Trontech, Inc., 381 Industrial Way East, Eatontown, NJ 07724...(908) 542-1133 Fax (908) 542-1118

PRINTED CIRCUIT BOARDS

Harmon Electronics, Inc., 601 N. Main, Warrensburg, MO 64093.....(816) 747-2236

CALL SOUTHWEST CIRCUITS NOW! (800) 279-5572

- PROTOTYPES AND SHORT RUNS FOR ALL MICROWAVE AND WIRELESS APPLICATIONS
- ALL POPULAR MICROWAVE LAMINATES: PTFE -TEFLON - DUROID - GX
- MULTI-LAYERS - QUICK TURN - EXOTICS

Southwest Circuits, 3760 E. 43rd Place, Tucson, AZ 85713

TEL (602) 745-8515 FAX (602) 747-8334 MODEM (602) 747-5108

RF TRANSMISSION COMPONENTS

ANTENNAS

Sinclair Technologies, Inc., Oriskany Dr., Tonawanda, NY 14150.....(800) 288-2763

Syndetix Inc., 2820 N. Telshor Blvd., Las Cruces, NM 88011.....(505) 522-8762

Custom Antenna Design, High Power, Including Flight Certified.....Fax (505) 521-1619

ATTENUATORS

Coaxial

SV Microwave, 3301 Electronics Way, West Palm Beach, FL (407) 840-1800 Fax (407) 844-8551

Syndetix Inc., 2820 N. Telshor Blvd., Las Cruces, NM 88011.....(505) 522-8762

Custom Antenna Design, High Power, Including Flight Certified.....Fax (505) 521-1619

CABLE ASSEMBLIES

Kaman Instrumentation, 1500 Garden of the Gods, Colorado Springs, CO 80907.....(719) 599-1821

SRC Cables, 5590 Skyline Blvd., Santa Rosa, CA 95403.....(707) 573-1900

Storm Products, Advanced Tech Group, 116 Shore Drive, Hinsdale, IL 60521.....(708) 323-9121

Cable Interconnect Systems

C&M Corporation, 51 S. Walnut St., Waukegan, CT 06387.....(203) 774-4812

DIRECTIONAL COUPLERS

Merrimac Industries, Inc.,

41 Fairfield Pl., W. Caldwell, NJ 07006.....(201) 575-1300 Fax(201) 575-0531

FILTER ASSEMBLIES



REEVES-HOFFMAN
DIVISION DYNAMICS CORPORATION OF AMERICA

For your Crystal Filter requirements from 1 KHz to 150 MHz Fundamentals and up utilizing Overtone Crystals.

400 W. North St., Carlisle, PA 17013, Tel: 717-243-5929, Fax: 717-243-0079

RF TRANSMISSION COMPONENTS

INDUCTORS AND CHOKES

Kintronic Labs, 144 Pleasant Grove Rd., Bluff City, TN 37618...(615) 878-3141 Fax (615) 878-4224

ISOLATORS/CIRCULATORS



AEROTEK COMPANY LIMITED

Manufacturers of Circulators and Isolators
Coaxial and Drop-in types, 400 MHz-18 GHz

"TOP QUALITY, REASONABLE PRICE"

1756 Sukhumvit 52, Sukhumvit Rd., Bangkok, Thailand.

AEROTEK Tel: (662) 311-4448, 332-5035 Fax: (662) 332-5034

MICROWAVE CONNECTORS

Applied Engineering Products, P.O. Box 510, New Haven, CT 06513.....(203) 776-2813

Coaxial Connectors, Inc., 1500 N.W. 62nd St., Ste. 501, Ft. Lauderdale, FL 33309.....(305) 772-2664

Southwest Microwave, Inc., 2922 S. Roosevelt St., Tempe, AZ 85282.....(800) 587-5995

MULTICOUPLERS

Trontech, Inc., 381 Industrial Way East, Eatontown, NJ 07724...(908) 542-1133 Fax (908) 542-1118

PHASE SHIFTERS

Merrimac Industries, Inc.,

41 Fairfield Pl., W. Caldwell, NJ 07006.....(201) 575-1300 Fax (201) 575-0531

PRECISION

TELEPLEX, INC. - ALFORD DIVISION

4801 INDUSTRIAL PKWY. - INDIANAPOLIS, INDIANA - 46226-4200 (317) 895 8800

• PRECISION COAX & W/G SLOTTED LINES 30MHZ. TO 40 GHZ

• LOW V.S.W.R. INTERSERIES COAX ADAPTERS 6 1/8" TO 2.40mm.

• HIGH POWER - LOW LOSS BIAS TEES 20 AMPS THRU 3.0 GHZ

• CONSTANT IMPEDANCE LINE STRETCHERS LOW LOSS TO 18 GHZ

• ADJUSTABLE COAX TUNERS MATCH S.W.R. > 14:1, VHF TO 36 GHZ

• ANDREW ALFORD ANTENNA PRODUCTS VHF-UHF-ITS-VOR-MIL.



POWER DIVIDERS/COMBINERS

Merrimac Industries, Inc.,

41 Fairfield Pl., W. Caldwell, NJ 07006.....(201) 575-1300 Fax (201) 575-0531

RF CONNECTORS

Merrimac Industries, Inc.,

41 Fairfield Pl., W. Caldwell, NJ 07006.....(201) 575-1300 Fax(201) 575-0531

Molex, Inc., 2222 Wellington Ct., Lisle, IL 60532.....800-MOLEX78

SV Microwave, 3301 Electronics Way, West Palm Beach, FL...(407) 840-1800 Fax (407) 844-8551

SURGE & TRANSIENT PROTECTORS

Lightning Suppressors • D.C. - 26 GHz
Coaxial • Powerline • Digital

FISCHER CUSTOM COMMUNICATIONS, INC. • (310) 891-0635

Polyphaser Corp., P.O. Box 9000, Minden, NV 89423.....(800) 325-7170, (702) 782-2511

SWITCHES

Electromechanical

Dow-Key Microwave Corp., 1667 Walter St., Ventura, CA 93003.....(805) 650-0260

Matrix Systems corp., 5177 N. Douglas Fir Rd., Calabasas, CA 91302.....(818) 222-2301

MBF Microwave, Inc., Rt. 2, Box 252A, Hardy, AR 72542.....(501) 856-2685

SYNTHESIZERS

Novatech Instruments,

1530 Eastlake Ave. E., #303, Seattle, WA 98102.....(206) 322-1562 Fax (206) 328-6904

TELEMETRY

Verdi, Nevada USA

Will customize to your requirements:

Transmitters & Receivers

Telemetry • Video • Digital • Command • Beacon

Command Encoders & Decoders

Since 1978

TEL (702) 345-2705

FAX (702) 345-2484

VACUUM CAPACITORS

COMET North America, 11 Belden Ave., Norwalk, CT 06850.....(203) 852-1231

VACUUM TUBES



RUSSIAN POWER TUBES
RUSSIAN MICROWAVE TUBES
Quality Engineering and Manufacturing

Tel: (800) 578-3852 • Fax: (415) 233-0439
3000 Alpine Road • Portola Valley, CA 94028

SYSTEMS DEVELOPMENT, REAL TIME

Adaptive Technology, Inc., 309 Curtis St., Syracuse, NY 13208... (800) 724-6968 Fax (315) 472-3279

MATERIALS AND HARDWARE

COMPONENTS/HYBRID PACKAGES

Reeves-Hoffman, 400 W. North St., Carlisle, PA 17013... (717) 243-5929

CRYSTAL BLANKS

Reeves-Hoffman, 400 W. North St., Carlisle, PA 17013... (717) 243-5929

PC BOARDS

Laminates, Polyester Copper Clad

Glasteel Industrial Laminates, P.O. Box 910, Collierville, TN 38027... (901) 853-5070

TEST EQUIPMENT

Racal Instruments, 4 Goodyear St., Irvine, CA 92718... (800) 722-3262

RF TEST & MEASUREMENT EQUIPMENT

COAXIAL DYNAMICS, INC.,

15210 Ind. Pkwy., Cleveland, OH 44135... (216) 267-2233 Fax (216) 267-3142

SPECTRUM ANALYZERS

DC TO LIGHT, P.O. Box 7140, Bozeman, MT 59771... (406) 586-5399 Fax (406) 586-6556

SERVICES

ANTENNA DESIGN & MEASUREMENT

Kintronic Labs, 144 Pleasant Grove Rd., Bluff City, TN 37618... (615) 878-3141 Fax (615) 878-4224

CONSULTANTS

Goldman Research, 12705 Montfort, Dallas, TX 75230... (214) 788-1122
RF Design & Modeling - Spice, EEsol, Wireless... WNJU80A@PRODIGY.COM

EMC/EMI TESTING

Liberty BEL EMC SVCS., P.O. Box 5431, MS20, Compton, CA 90224... (310) 537-4235

Above MS20 represents RF Design

TUV Rheinland of North America, Inc.,

12 Commerce Road, Newtown, CT 06470... (203) 426-0888 Fax (203) 270-8883

EQUIPMENT CALIBRATION

Instrument Repair Labs, Inc., 2100 W. 6th Ave., Broomfield, CO 80020... (800) 345-6140

INSTRUMENT RENTAL/LEASING

Naptech, 12312 Hwy 175, Cobb, GA 95423... (800) 336-7723 Fax (707) 928-1963

OEM PRODUCTS

Locus, Inc., 1842 Hoffman St., Madison WI 53704... (608) 244-0500

TELEMETRY SYSTEMS & ENGINEERING

Telemetry Technologies, Inc., 3307 West St., Rosenberg, TX 77471... (713) 344-9000

SOFTWARE & SYSTEMS, CAD/CAE

SOFTWARE

Circuit Simulation

COMET North America, 89 Taylor Ave., Norwalk, CT 06854... (203) 852-1231

Design Automation, Inc., 4 Tyler Rd., Lexington, MA 02173... (617) 862-8998 Fax (617) 862-3769

ingSoft Ltd. - the providers of the RF Designer® Solution... (416) 730-9611

312 Dunview Ave., North York, ON M2N 4H9, Canada; bbs: 226-9820... Fax: 733-3884

Waypoint Software, 1950 Bavaria Drive, #317, Colorado Springs, CO 80918... (719) 598-9592

SYSTEM SIMULATION

Tesoft, Inc., 205 Crossing Creek Ct., Roswell, GA 30076... (800) 631-1113

Makers of TESLA Com Simulator... Fax (404) 664-5817 Intl (404) 751-9785



Products & Services Directory

The Products & Services Directory is a convenient guide to suppliers of products and services for the EMC/ESD industry. Products & Services Directory listings are sold on an annual basis.

For information on rates, closing dates and details on a special Introductory Offer, call 1-800-443-4969. Ask for your yellow page representative.

ELECTRONIC COMPONENTS AND EQUIPMENT

EMI SUPPRESSION COMPONENTS

Cables and Connectors

Spectrum Control, Inc., 6000 West Ridge Rd., Erie, PA 16506... (814) 835-4000

EMI/RFI Filters

POTTER PRODUCTION CORPORATION, 3004 Hwy. 51 N., Wesson, MS 39191... (601) 643-2215

Santek, 9765 Marconi Dr., #205, San Diego, CA 92173... (619) 661-8119

Ferrite Beads, Rods, Forms

Fair-Rite Products Corp., P.O. Box J, Wallkill, NY 12589... (800) 836-0427

Steward, Inc., 1200 E. 36th Street, Chattonooga, TN 37401... (615) 867-4100 Fax (615) 867-4102

Ferrite Suppression Components

Steward, Inc., 1200 E. 36th Street, Chattonooga, TN 37401... (615) 867-4100 Fax (615) 867-4102

Filtered Connectors

Spectrum Control, Inc., 6000 West Ridge Rd., Erie, PA 16506... (814) 835-4000

Filters, Power Line

Qualtek Electronics Corp., 7675 Jenther Dr., Mentor, OH. 44060... (216) 951-3300

Rtron Corp., P.O. Box 743 Skokie, IL 60076... (708) 679-7180

Transformers/ Filters

Steward, Inc., 1200 E. 36th Street, Chattonooga, TN 37401... (615) 867-4100 Fax (615) 867-4102

ESD AND SURGE CONTROL COMPONENTS

Lightning Arrestors

Fischer Custom Communications, 2905 W. Lomita Blvd, Torrance, CA 90505... (310) 891-0635

Polyphaser Corp., P.O. Box 9000, Minden, NV 89423... (800) 325-7170 (703) 782-2511

CABLE AND CONNECTORS

Connectors And Adapters

ADC Telecommunications, 4900 W. 78th St., Minneapolis, MN 55435... (800) 366-3891 X3000

Optical Fibers And Connectors

ADC Telecommunications, 4900 W. 78th St., Minneapolis, MN 55435... (800) 366-3891 X3000

EMC TEST EQUIPMENT - EMISSIONS

Absorbers

Advanced Electromagnetics, Inc., P.O. Box 711719, Santee, CA. 92072- 1719... (619) 449-9492

Absorbers

IBEX Group, Inc., 23 Markham Dr., Long Valley, NJ 07853... (800) 403-3930

Microsorb Technologies, Inc., 14A Airport Dr. Hopedale, MA 01747... (508) 634-1900

Rantec, P.O. Box 1546, Austin, TX 78767... (512) 835-4684

Anechoic Chambers

Advanced Electromagnetics, Inc., P.O. Box 711719, Santee, CA. 92072- 1719... (619) 449-9492

IBEX Group, Inc., 23 Markham Dr., Long Valley, NJ 07853... (800) 403-3930

Rantec, P.O. Box 1546, Austin, TX 78767... (512) 835-4684

Antennas

Antenna Research Associates, Inc., 11317 Fredrick Ave., Beltsville, MD 20705... (310) 937-8888

Antennas

EMCO, P.O. Box 1546, Austin, TX. 78767... (512) 835-4684

Antennas Above 30 MHz

A.H. Systems Inc., 9710 Cozy Croft Ave, Chatsworth, CA 91311... (818) 998-0223 Fax (818) 998-6892

EMCO, P.O. Box 1546, Austin, TX. 78767... (512) 835-4684

IBEX Group, Inc., 23 Markham Dr., Long Valley, NJ 07853... (800) 403-3930

Antennas Masls

Antenna Research Associates, Inc., 11317 Fredrick Ave., Beltsville, MD 20705... (310) 937-8888

EMCO, P.O. Box 1546, Austin, TX. 78767... (512) 835-4684

IBEX Group, Inc., 23 Markham Dr., Long Valley, NJ 07853... (800) 403-3930

Current Probes

Fischer Custom Communications, 2905 W. Lomita Blvd, Torrance, CA 90505... (310) 891-0635

IBEX Group, Inc., 23 Markham Dr., Long Valley, NJ 07853... (800) 403-3930

Ion Physics Corp., 11 Industrial Way, Atkinson NH 03811... (603) 893-6687

Ferrite Absorber Tiles

IBEX Group, Inc., 23 Markham Dr., Long Valley, NJ 07853... (800) 403-3930

Rantec, P.O. Box 1546, Austin, TX 78767... (512) 835-4684

GTEM Cells

Antenna Research Associates, Inc., 11317 Fredrick Ave., Beltsville, MD 20705... (310) 937-8888

EMCO, P.O. Box 1546, Austin, TX. 78767... (512) 835-4684

Line Impedance Stabilization Networks

EMCO, P.O. Box 1546, Austin, TX. 78767... (512) 835-4684

Fischer Custom Communications, 2905 W. Lomita Blvd, Torrance, CA 90505... (310) 891-0635

IBEX Group, Inc., 23 Markham Dr., Long Valley, NJ 07853... (800) 403-3930

Rantec, P.O. Box 1546, Austin, TX 78767... (512) 835-4684

Near Field Probes

Antenna Research Associates, Inc., 11317 Fredrick Ave., Beltsville, MD 20705... (310) 937-8888

EMCO, P.O. Box 1546, Austin, TX. 78767... (512) 835-4684

IBEX Group, Inc., 23 Markham Dr., Long Valley, NJ 07853... (800) 403-3930

Preamplifiers

IBEX Group, Inc., 23 Markham Dr., Long Valley, NJ 07853... (800) 403-3930

Preselectors

IBEX Group, Inc., 23 Markham Dr., Long Valley, NJ 07853... (800) 403-3930

Shielding Effectiveness Testers

Antenna Research Associates, Inc., 11317 Fredrick Ave., Beltsville, MD 20705... (310) 937-8888

EMCO, P.O. Box 1546, Austin, TX. 78767... (512) 835-4684

EMC TEST EQUIPMENT - SUSCEPTIBILITY

Antennas

EMCO, P.O. Box 1546, Austin, TX. 78767... (512) 835-4684

E-Field Probes

EMCO, P.O. Box 1546, Austin, TX. 78767... (512) 835-4684

GTEM Cells

EMCO, P.O. Box 1546, Austin, TX. 78767... (512) 835-4684

EMC TEST EQUIPMENT - SUSCEPTIBILITY**Power Amplifiers**

Applied Systems Engineering, Inc., 8623 Hwy. 377 S., Fort Worth, TX 76126(819) 249-4180
 Varian Microwave Equip. Prods., 3200 Patrick Henry Dr., Santa Clara, CA 95054....(408) 496-6273

Shielded Fiber Optic Links

Antenna Research Associates, Inc., 11317 Fredrick Ave., Beltsville, MD 20705....(310) 937-8888

Surge Generators

Velonex Corp., 560 Robert Avenue, Santa Clara, CA 95050(408) 727-7370
 Pulse, Surge, Transient, ESD, Hybrid Generators

ESD TEST EQUIPMENT**ESD Event Detectors**

Monroe Electronics, Inc., 100 Housel Avenue, Lyndonville, NY 14098(800) 821-6001
 TREK INC., 3932 Salt Works Rd., P.O. Box 728, Medina, NY. 14103(800) FOR-TREK

Field Strength Meters

Antenna Research Associates, Inc., 11317 Fredrick Ave., Beltsville, MD 20705....(310) 937-8888

Surface & Volume Resistivity Meters

Monroe Electronics, Inc., 100 Housel Avenue, Lyndonville, NY 14098(800) 821-6001
 TREK INC., 3932 Salt Works Rd., P.O. Box 728, Medina, NY. 14103(800)FOR-TREK

MATERIALS, HARDWARE AND PACKAGING**SHIELDING MATERIALS****Antenna Towers**

EMCO, P.O. Box 1546, Austin, TX. 78767(512) 835-4684

Architectural Shielding

Specialty Technical Components, Inc., P.O. Box 2106, Southeastern, Pa 19399.....(610) 647-9000

Broadband EMI

Steward, Inc., 1200 E. 36th Street, Chattonooga, TN 37401.....(615) 867-4100 Fax (615) 867-4102

Conductive Adhesives

Venture Tape Corp., 30 Commerce Rd., Rockland, MA 02370.....(617) 331-5900

Conductive Fiber/Fabric

Venture Tape Corp., 30 Commerce Rd., Rockland, MA 02370.....(617) 331-5900

Ferrite Absorber Tiles

Fair-Rite Products Corp., P.O. Box J, Wallkit, NY 12589.....(800) 836-0427

Gasketing Materials

Venture Tape Corp., 30 Commerce Rd., Rockland, MA 02370.....(617) 331-5900

Laminates

Venture Tape Corp., 30 Commerce Rd., Rockland, MA 02370.....(617) 331-5900

Magnetic Shielding

Ad-Vance Magnetics, Inc., 625 Monroe St., Rochester, IN 46975.....(219) 223-3158

Positioning Controllers

EMCO, P.O. Box 1546, Austin, TX. 78767(512) 835-4684

Shielding Foils and Tapes

Venture Tape Corp., 30 Commerce Rd., Rockland, MA 02370.....(617) 331-5900

SHIELDING MATERIALS**Tripods**

EMCO, P.O. Box 1546, Austin, TX. 78767(512) 835-4684

Turntables

EMCO, P.O. Box 1546, Austin, TX. 78767(512) 835-4684

SHIELDING EMI/RFI SERVICES

Vacuum Platers, Inc., 115 S. Union Street, Mauston, WI 53948(608) 847-5648

SHIELDED ENCLOSURES - EQUIPMENT**Component/Module Cases**

Marmin-Hil Plastics, Inc., 101 Roselle St., Linden, NJ 07036.....(908) 925-2940 (800) 886-2940

SHIELD ROOMS AND CHAMBERS**Shielded Rooms EMI/RFI/Magnetic**

Rantec, P.O. Box 1546, Austin, TX. 78767(512) 835-4684

ESD PACKAGING**Antistatic and Conductive Polyurethanes**

Pad-Tastics, Inc., P.O. Box 50479, Cicero, IL 60650.....(708) 780-8402 FAX (708) 780-1631

ESD ENVIRONMENTAL CONTROL**Antistatic or Conductive Flooring**

Freudenberg Building Systems, Inc./Nora Rubber Flooring
 94 Glenn St., Lawrence, MA 01843.....(508) 689-0530

TEST LABORATORIES AND CONSULTANTS**TEST LABORATORIES**

Spectrum Control, Inc., 6000 West Ridge Rd., Erie, PA 16506.....(814) 835-4000

TUV Product Service, Inc., 1775 Old Hwy. 8, New Brighton, MN 55112.....(800) 472-7990

EMI/EMC CONSULTANTS

EMC&I, 5700 Corsa Ave., #100 Westlake Village, CA 91362(818)889-2242

EMI/EMC TESTING

LambdaMetrics, P.O. Box 1029, Cedar Park, TX 78630-1029(512) 219-8218

FCC listed lab, one EMC Engineer, 30 years RF design experience, Prompt Personal Service

CONSULTANTS

Kimmel Gerke Assoc. Ltd., 1544 N. Pascal, St. Paul, MN 55108(612) 330-3728

EMC Design/Troubleshooting-Medical, Industrial, ITE, Vehicles & More-50+ years exp.

Regulatory Consultants Network, P.O. Box 344, Liberty Hill, TX 78642.....(800) 326-6336

EMC Design, EMC/EMI/EMS/ESD & Electrical Product Safety

You won't get any calls if no one knows your number.



But the RF-Design and EMC Test and Design Directory can help solve that problem. Our directory will put you in touch with over 40,000 decision makers in the RF-Design and EMC industry. There are fantastic introductory offers that make advertising even easier.

Call Shannon Shuman at 1-800-443-4969 for details.

High-Speed/ Wide-Bandwidth Databook

Comlinear's 1995 Databook Supplement is a 256-page reference book providing full detail of Comlinear's broad line of high-speed, wide-bandwidth components for signal conditioning, data conversion and serial digital interface. It includes complete specifications and performance plots for new and updated products introduced since Comlinear's 1993-1994 Databook.

Comlinear Corp.
INFO/CARD #210

Fax-on-Demand Service

Andrew Corporation announces the availability of "Answers from Andrew", an automated fax-on-demand system to better serve the information needs of its customers. The service provides product information, technical documents and news publications. By dialing 1-800-861-1700 (708-873-3614 for international callers), anyone with a touch-tone phone and fax machine can access the system.

Andrew Corp.
INFO/CARD #209

SNA Measurement Accuracy

Anritsu Wiltron offers a new technical seminar along with a companion application note (54100A-7) and free software program. The free seminar identifies common sources of scalar network analyzer measurement uncertainty and provides common sense suggestions for accuracy improvements. An emphasis is placed upon "measurement accuracy" rather than simple "instrumentation accuracy."

Anritsu Wiltron Co.
INFO/CARD #208

Reconditioned Equipment

Catalog no. 35 from Bid Service contains 100 pages of reconditioned electronic manufacturing and scientific/analytical instrumentation. Categories of equipment include: amplifiers, analyzers, filters, component testers, generators, oscilloscopes, power meters, RFI/EMI equipment, telecom/communications testers and others.

Bid Service
INFO/CARD #207

Lightning Protection Newsletter

The latest edition of *Striking News* from PolyPhaser contains articles on the effectiveness of tower down-conductors, lightning current, silicon avalanche diode power line protectors, and information on upcoming trade shows.

PolyPhaser Corp.
INFO/CARD #206

Cable Television Testing

Wavetek's full-color, 28-page Cable Television Selection Guide includes a full range of

products designed to meet cable television's specific testing needs. The newly-expanded guide features Wavetek's newest frequency agile MicroStealth Installer/Service Technician Meters which measure channel signal levels with a display similar to the Stealth SAM 4040 and Stealth 3SR sweep receiver.

Wavetek Corp.
INFO/CARD #205

Test & Measurement Equipment

Tucker Electronics announces the release of their full line catalog. This free test and measurement product guide contains over 5000 new and used instruments plus hundreds of components and specifications.

Tucker Electronics
INFO/CARD #204

Waveform Synthesizers

Pragmatic Instruments has released their new Selection Guide for Waveform Synthesizers. Seven different arbitrary waveform generators with sample clock rates ranging from 100 MHz to 2 MHz, vertical waveform resolution from 12-bits to 16-bits, and waveform capacity up to 1 megaword are featured.

Pragmatic Instruments, Inc.
INFO/CARD #203

Communications Videotapes

George Washington University offers the Keiser Communication videotapes, covering high definition television (5 tapes), microwave radio systems (5 tapes), and satellite communication engineering principles (7 tapes). Prices for each series are \$1,575 for the High Definition Television series, \$1,710 for the Microwave Radio Systems series, and \$2,205 for Satellite Communication Engineering Principles series.

The George Washington University
INFO/CARD #202

Used Test Equipment

GE Capital Test Equipment Management Services has released Volume 1 of the 1995 Buyer's Guide. The 13-page guide contains a list of quality used test equipment, grouped by manufacturer, with a brief description of each available model. Information is available by calling 1-800-GE-RENTS.

GE Capital
INFO/CARD #201

MMDS Amplifier Data

A four page data sheet introducing a series of 2.5 - 2.7 GHz solid-state PAs for MMDS (wireless cable) and ITFS (instructional television) is now available from Chesapeake Microwave Technologies. This data sheet defines critical features and electrical specifications of these solid state, high power amplifiers.

Chesapeake Microwave Technologies, Inc.
INFO/CARD #200

IF/RF Catalog

Daico Industries announces the publication of its 1995-1996 IF/RF catalog. The all new 280-page catalog features DAICO's complete family of IF and RF components. DAICO specializes in the manufacturing of switches attenuators, phase shifters, MMICs, bit detectors, couplers and sub-assemblies. Over 45 new products are featured in the catalog.

Daico Industries, Inc.
INFO/CARD #199

Test & Measurement Catalog

LeCroy announces publication of the new 1996 Test & Measurement Catalog featuring product information, selected applications information and two tutorials on "Fundamentals of Digital Oscilloscopes" and "Waveform Creation Made Easy". Included is information on LeCroy's 1 GHz bandwidth oscilloscope line and the 9362, which has a 10 Gs/s sampling rate.

LeCroy Corp.
INFO/CARD #198

Connector Catalog

Applied Engineering Products has released a 185-page catalog, called the "Blue Book", describing their series of connectors, adapters, and cable assemblies. Besides showing standard connectors, the "Blue Book" shows mounting and cable attachment options, plating options, cable terminations, adaptors, and other features.

Applied Engineering Products
INFO/CARD #197

Signal Switching Handbook

Keithley Instruments has announced the availability of its 3rd edition of the *Switching Handbook*. The expanded and revised handbook is an application guide to signal switching in automated test systems. It provides over 200 pages of information on the theory and practice of automated switching in low level measurements.

Keithley Instruments, Inc.
INFO/CARD #196

Resistive Devices

EMC Technology has released a 98-page, four-color catalog describing their attenuators, terminations, resistors, connectors and surface mount hybrid couplers. The catalog also contains a special section highlighting new products and eight application notes.

EMC Technology, Inc.
INFO/CARD #195

Component Summary Sheet

Analogic announces a component summary sheet for its complete line of high performance data conversion component product lines.

Analogic Corp.
INFO/CARD #194

RF software

Integrated Design Programs

Eagleware has released GENESYS, an integrated set of programs for analog, RF and microwave circuit designers. GENESYS includes a high-speed linear circuit simulator, programs for the synthesis of a wide range of circuits, a schematic interface, and exportation of circuit files for Touchstone, Spice, and em, the electromagnetic simulation program from Sonnet Software. GENESYS is available for DOS, Windows 3.1 and Windows NT. Simulation packages start at \$995; synthesis modules range from \$599 to \$999.

Eagleware Corp.
INFO/CARD #193

Site Management

SoftWright has introduced SiteBase™ for Windows™, a comprehensive communications site management program. A relational database for the user-friendly Windows interface, SiteBase tracks and updates equipment and other management information, as well as creating dozens of customized reports. Using Windows 3.0 or higher, SiteBase runs on 286 (or higher) IBM compatibles. Introductory price is \$395.

SoftWright LLC
INFO/CARD #192

Resonator Selection

Trans-Tech offers CARD (Computer Aided Resonator Design) and COAX (Coaxial Element Designer Guide), Windows™-based software design tools that can assist RF designers in the selection of dielectric and coaxial resonators for oscillators and filters from UHF to Ku frequencies. CARD and COAX provide graphical presentation of the frequency response and equivalent circuit values for insight into the interrelationships among circuit components. Both programs relate component material geometry to predicted performance using a wide choice of materials and models based on proven, established development formulas.

Trans-Tech, Inc.
INFO/CARD #191

SPICE for Networks

Intusoft has introduced a keyless version of its popular SPICE 3F based simulator IsSpice4. The software is licensed for a specific number of copies that "float" on a network. The software may be installed on any machine in a network which acts as the server. Any client machine on the network can run the ICAP/4 software, and special provisions have been made for clients to have their own private model libraries,

symbols, and preferences. Network simulation performance is as good as that of stand-alone versions. "Dongleless" network versions of the ICAP/4 Windows™, ICAP/4Lite and ICAP/4Lite Xtra packages are priced according to the formula: list price $\times (N+1)$, where N is the maximum number of copies to be run at any one time.

Intusoft
INFO/CARD #190

Block-Level Simulator


Visual Systems is shipping VisSim v2.0, a modeling and nonlinear simulation software package. Vis Sim allows users to simulate many types of systems by selecting and connecting icons from a tool bar. RF systems can be simulated using a number of high frequency block models, including Hilbert, Bessel, Chebyshev, Butterworth or inverse Chebyshev filter types. Virtual control panels can be constructed, with user-definable charts, meters, indicator "lamps" and alarms. VisSim operates under Microsoft Windows, Windows NT and UNIX/X operating systems. Prices range from \$495 to \$4,195 depending upon capability and operating platform.

Visual Solutions Inc.
INFO/CARD #189

CERAMIC RF CAPACITORS

C-D/SANGAMO

MICA RF CAPACITORS



JENNINGS

VACUUM CAPACITORS

VACUUM RELAYS

SURCOM ASSOCIATES, INC.

2215 Faraday Avenue, Suite A
Carlsbad, California 92008
TEL (619) 438-4420
FAX (619) 438-4759

INFO/CARD 67

RF Design Software

September Disk — RFD-0995

"Phase Noise Measurement for Under \$250" by Bill Suter. Wave analysis software used with the signal acquisition hardware described in the article. Takes output of A/D converter, applies a Hanning window and performs a FFT. Displays the system noise from 1 kHz to 100 kHz. (Quick C, source code and compiled, executable version. See notes on program usage in article)

August Disk — RFD-0895

"Microstrip Coupled-Line Bandpass Filter Synthesis and Analysis Program" by Sean Mercer and Eric Mabada. The user enters performance specifications, and the program generates a microstrip filter that meets those requirements. Analysis data is created in tabular form; Touchstone and Super Compact files can be generated for further analysis. (Requires QBASIC interpreter in MS-DOS 5 or higher, VGA or SVGA graphics)

ALSO AVAILABLE:

Index of RF Design Articles: 1978-1994 — Disk RFD-INDEX — \$25.00 (U.S.)
Amplifier and Oscillator Design Program — RFCAD — \$99.00 (U.S.)

Programs from RF Design provided on disk for your convenience

Monthly program disks: \$25.00 (U.S.) \$30.00 (foreign)

Yearly Disk Sets and Annual Subscriptions Available: Call for Information

All orders must be pre-paid by check, money order, or major charge card. All checks must be in U.S. dollars and payable to a bank located in the U.S. Prices include shipping.

RF Design Software
Argus Direct Marketing Dept.
6151 Powers Ferry Rd., N.W.
Atlanta, GA 30339-2941
Tel: (404) 618-0398
Fax: (404) 618-0347

Not Everyone In Communications Qualifies To Be On An Argus List.



Rent the circulation file of this
publication for your direct mail needs.
For our complete catalog,
call Diane at (770) 618-0391 or
fax (770) 618-0347.

A
ARGUS
DIRECT
BUSINESS LISTS



RF guide to editorial coverage

AML Communications	50	E.F. Johnson Co.	22	Noise Com, Inc.	50
AMP Incorporated	50	Eagleware Corp.	96	Novatech Instruments, Inc.	48
Amplifier Research	46	EMC Technology, Inc.	95	Oak Frequency Control Group	49
Amplifonix, Inc.	60	Environmental Stress Systems, Inc.	50	Philips Semiconductors	80
Analog Devices	48, 65	EXEL Microelectronics	48	Planar Monolithics Industries, Inc.	50
Analogic Corp.	95	Federal Aviation Administration	20	Polyfet RF Devices	80
Anaren Microwave, Inc.	49	GE Capital	95	PolyPhaser Corp.	95
Andrew Corp.	95	Harris Corp.	22	Pragmatic Instruments, Inc.	95
Anritsu Wiltron Co.	22, 46, 95	Hewlett-Packard Co.	48, 52	Radiometer Electronics Co.	12
Applied Engineering Products	95	HP EEsof	36	RF Power Components, Inc.	49
Applied Signal Technology	22	International Microcircuits, Inc.	49	Richardson Electronics	80
AT&T Paradyne	22	Intusoft	96	Richardson Electronics, Ltd.	48
Bid Service	95	Keithly Instruments, inc.	95	Rogers Corp.	22
BIS Strategic Decisions	20	Kel-Com	46	Scientific-Atlanta	22
Boeing Commercial Airplane Group	26	KVG	22	SGS-Thomson Microelectronics	80
British Ministry of Defence	22	Lasertron	22	SoftWright LLC	96
Broadband Communications Products, Inc.	22	LeCroy Corp.	95	Sprague-Goodman Electronics, Inc.	48
BTG USA Inc.	22	M-pulse Microwave	48	Stanford Telecom	22
Cable Television Laboratories, Inc.	22	Machlett Co.	12	Staudte Engineering	22
California Eastern Laboratories	48	Magnetic Materials		Svetlana Electron Devices, Inc.	22
Cellular Evaluation Systems	52	Producers Association	20	TDK Corp. of America	47
Chesapeake Microwave technologies, Inc.	95	ManTech Test System	22	Telecom Analysis Systems	22
Coilcraft	47	Metatech Corp.	47	Texas Instruments	22
Comlinear Corp.	46, 95	MICRO-COAX	49	The George Washington University	95
Communications Techniques, Inc.	49	MicroSim	26	The SETI League, Inc.	20
Comtech Microwave Products Corp.		Microwave Filter Company	49	Times Microwave Systems	50
Power Systems Technology Div.	50	Mini-Circuits	49, 63	Trans-Tech, Inc.	96
Cuming Corp.	50	MITEQ	49	Tru-Connector Corp.	46
Daico Industries, Inc.	95	MORION	22	Tucker Electronics	95
Damaskos, Inc.	52	Motorola Satellite Comm. Div.	22	University of Colorado	20
Densitron Microwave	50	Motorola Semiconductor Products Div.	80	Visual Solutions Inc.	96
DMT	49	Murata North America	47	Watkins-Johnson International	22
E-Systems	20	NASA Langley Research Center	70	Watkins-Johnson Co.	22
		National Institute of Standards	20	Wavetek Corp.	52, 95

RF advertising index

ADVERTISER	PAGE #	READER SVC #	ADVERTISER	PAGE #	READER SVC #
Aerotek Co., Ltd.	45	36	Meb. Messelektronik Berlin	49	39
Amplifier Research	71	59	Merrimac	3	2
Axxon	31	24	Metatech	47	37
Bis Strategic Decisions	77		Methode Electronics	34	28
Bomar Crystal Co.	69	58	Micro Communications Executive Search	83	
Brei & Associates, Inc.	88		Micronetics	76	46
California Eastern Labs	104	69	Mini Circuits	4-5, 6, 18-19, 25, 55, 61	3, 4, 17, 20, 45, 50
Christie Associates	85		Mobile Systems International	87	
Coilcraft	11	9, 10, 11, 12	Murata Electronics N.A.	67	56
Communication Concepts	62	51	National Instruments	75	72
Compact Software	59	49	National Semiconductor	2	1
Continental Field Service Corp.	84		Nolan Laboratories, Inc.	88	
Control Devices, Inc.	90	90	Oak Frequency Control	63, 65	53, 55
Don Gallagher & Associates	84		Paragon Technologies	90	83
Eagle	52	42	Penstock	43	35
Eagleware	103	68	Peter Froehlich & Co.	88	
Ecliptek Corporation	29	23	Piezo Technology	48	38
EEESOF, Inc.	53	44	Polyphaser Corp.	41	33
Electro Dynamic Crystal	62	52	Programmed Test Sources	17	16
ENI	64	54	PTek	90	91
Ericsson	86		Raltron/Time & Freq.	30	26
Excel	84		Ramsey Electronics	89	
Fitzpatrick & Associates	85		Randall Chambers & Associates	88	
Fortune Personnel Consultants	83		Rantec	85	
Future Electronics	72	60	Reeves-Hoffman	16	15
Geesaman Software	89	81	Richardson Electronics	21, 23	18, 19
Giga-tronics Inc.	27	21	Rogers Corp.	56	64
Gould, Inc.	89	80	Signal Microwave Electronics	90	86
Harris	87		Southwest Circuits	73	61
Henry Radio	52	43	Surcom Associates	96	67
Hexawave, Inc.	90	89	Synergy	37	30
Hy-Q International	28	22	Tele-Tech Search	85	
Isotemp Research, Inc.	90	85	Temex	14-15	14
ITS Corporation	84		Teradyne	85	
ITT GTC	33	27	Tesoft, Inc.	90	84
JFW Industries	42	34	TTE, Inc.	56	65
Johanson Mfg.	58	48	TV/Comm International	87	
E.F. Johnson	69	57	V-Tech	89	
Kalmus Engineering	9	6	Valpey-Fisher	10	7
KVG North America	35	29	Vectron	12-13, 50, 51, 89	13, 40, 41
K.S. Electronics	89		Voltronics	99	
Lap-Tech	30	25	Waypoint Software	88	
Lectrosnics, Inc.	83		Wayne Kerr, Inc.	90	87
LPKF CAD/CAM Systems, Inc.	74	62	Werlatone, Inc.	8	5
LCF Enterprises	90	88	Wilmanco	89	82
M-Tron	57	47	XTAL Technologies	10	63
M/A Com (3 Divisions)	38, 39	31	Z-Domain Technologies, Inc.	84	
Management Recruitment of Boulder	88				

TURBO-CHARGE TOUCHSTONE

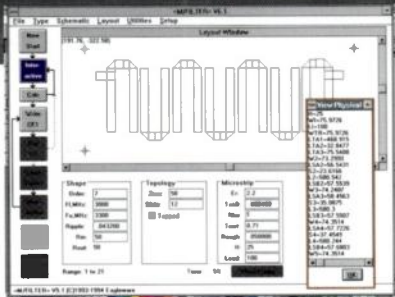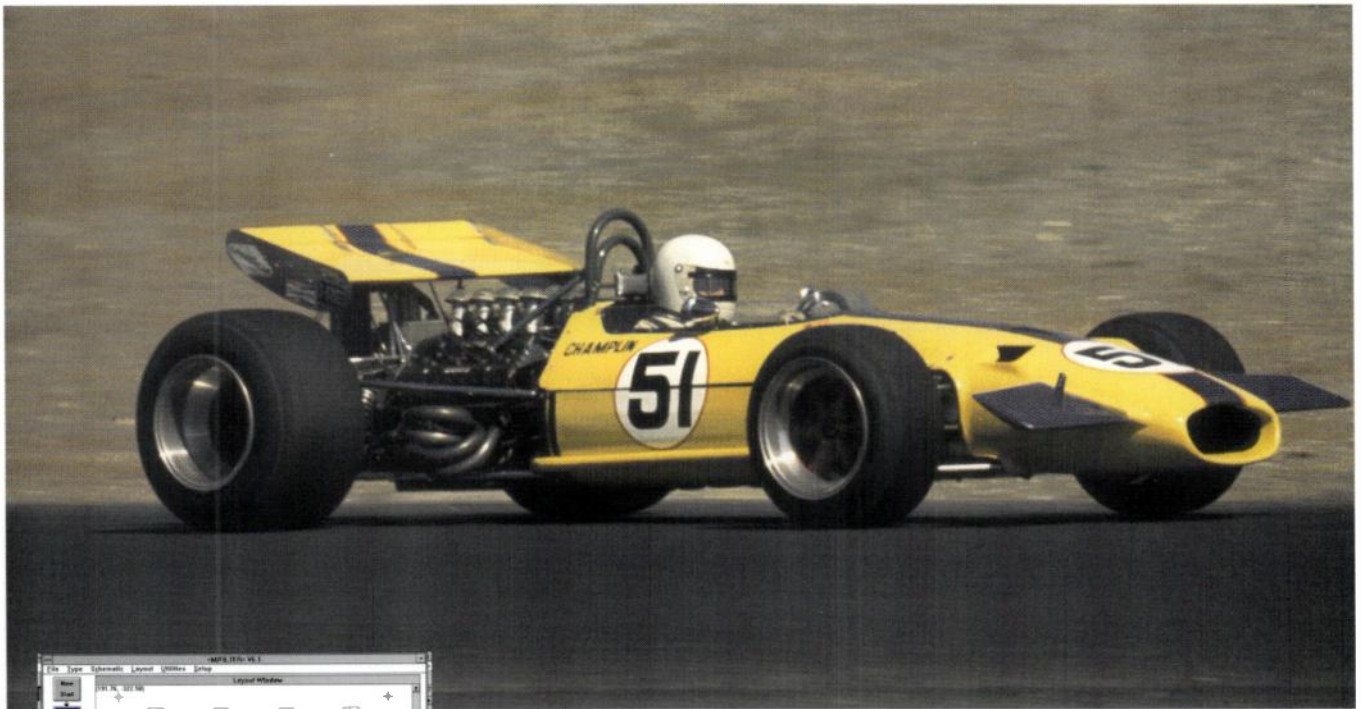

EXAMPLE GENESYS SCREEN

SUPER-CHARGE SPICE

with GENESYS, a suite of programs for synthesizing microwave filters amplifiers, oscillators, active filters, matching networks and L-C filters for your Touchstone, Spice and =SuperStar= simulator.

MICROWAVE FILTERS

End coupled
Edge coupled
Hairpin
Stepped-Z
Combine
Interdigital
Elliptic lowpass
Elliptic bandpass
Sub lowpass
Stub bandpass
Stub bandstop
Edge bandstop

OSCILLATORS

L-C series mode
L-C Colpitts
L-C Clapp
T-line and L-C VCO
VCO with xformer
Cavity bipolar and hybrid
Dielectric resonator
Terminal SAW bipolar
Port SAW hybrid
Port SAW MOSFET
Pierce and Colpitts crystal
Driscoll crystal
Butler overtone
Overtone with multiplier

MATCHING NETWORKS

L-C pi and L
L-C tee
T-line quarter wave
T-line single/double stub
General order bandpass
L-C pseudo lowpass
T-line pseudo lowpass
T-line stepped-Z
Custom with R's and xformers

LUMPED FILTERS

Conventional all-pole
Conventional elliptic
Top-C coupled
Top-L coupled
Shunt-C coupled
Tubular
Blinchikoff flat delay
Zig-zag
Eagleware symmetric

ACTIVE FILTERS

GIC transform
Single feedback
Multiple feedback
Low sensitivity
State variable (biquad)
VCVS
Dual amplifier



GENESYS includes free technical support,
no annual fees and a money-back guarantee
GENESYS is available for



EAGLEWARE


Eagleware Corporation ★ 1750 Mountain Glen ★ Stone Mtn, GA 30087 ★ USA

TEL (404) 939-0156 ★ FAX (404) 939-0157



SAVE PRICES INTERNATIONALLY
DIRECT SALES & USER SUPPORT
BY FAX, PHONE OR LETTER

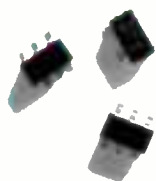...MORE NEW 3 VOLT RF ICs FOR YOUR HANDHELD WIRELESS PRODUCTS



NEC's 3 Volt ICs not only reduce power consumption in your wireless designs, they help reduce your parts count, improve the reliability, and simplify assembly.

We're committed to 3 Volt Silicon technology. These parts are just a sampling of the wide variety of the semiconductors we stock.

We also stock 5 Volt ICs — plus NEC's huge family of discrete devices. Many of these transistors are characterized at 1 to 3 Volts, and most are available in a number of package styles, including the new ultra-miniature 0.8 X 1.6 mm NEC "19" package.

For a FREE Product Selection Guide, call your nearest CEL Sales Office. Or circle the number below.



Dozens of 3 Volt Amplifiers, Prescalers, Up & Downconverters, IQ Mods & Demods, and Transistor Arrays, including:

UPC8104GR **new**

IQ Modulator
with Up Converter
800 MHz to 2.4 GHz
2.7 to 5.5 V Supply Voltage

UPC8106T/09T

Up Converters
800 MHz — 2.4 GHz
7 dB CG @ 1.9 GHz
2.7 to 5.5 V Supply Voltage

UPC2758T

Downconverter
100 MHz — 2.4 GHz
17 dB CG @ 2.0 GHz
+6 dBm IP₃

UPC2762T/63T

Driver Amplifiers
100 MHz — 1.9 GHz
14 or 20 dB Gain and
+7 dBm P_{1dB} @ 1.9 GHz

UPC2768GR **new**

Downconverter
DC — 450 MHz
80 dB Conversion Gain
On-chip Oscillator

UPC2771T **new**

Wideband Amplifier
100 MHz — 2.1 GHz
21 dB Gain and
+11.5 dBm P_{1dB} @ 900 MHz

...plus a wide variety of Silicon Devices for 5 Volt applications, including:

UPC2709T

Wideband Amplifier
100 MHz—2.3 GHz
23 dB Gain
+8 dBm P_{1dB} @ 900 MHz

UPC2766GR **new**

IQ Demodulator
35 dB AGC Dynamic Range
Flat Response to 1 GHz RF
DC—100 MHz I/Q Output

UPC2721GR

High Compression Point
Downconverter
900 MHz — 2.0 GHz
21 dB Conversion Gain

UPB1505GR **new**

Prescaler
÷64/128/256
3 GHz Guaranteed RF Input
High Input Sensitivity

...plus dozens of discrete transistors including three new small signal bipolar series:

new	PART*	NF (dB)	G _A (dB)	V/I _C	f _{TEST} (GHz)
	NE68619	1.7	10.0	2V/3mA	2.0
	NE68719	1.5	8.0	1V/3mA	2.0
	NE68819**	1.6	8.0	3V/7mA	2.0

* AVAILABLE IN SIX DIFFERENT PLASTIC PACKAGES, INCLUDING THE ULTRAMINIATURE NEC "19" PACKAGE
** LOW PHASE NOISE DEVICE

CEL California Eastern Laboratories

NEC

CEL Headquarters 4590 Patrick Henry Drive, Santa Clara, CA 95054-1817; (408) 988-3500 FAX (408) 988-0279 Santa Clara, (408) 988-7846 Los Angeles, CA (310) 645-0985
San Diego, CA (619) 450-4395 Bellevue, WA (206) 644-3307 Richardson, TX (214) 437-5487 Olathe, KS (913) 780-1380 Woodridge, IL (708) 241-3040
Timonium, MD (410) 453-6600 Middleton, MA (508) 762-7400 Hackensack, NJ (201) 487-1155 Snellville, GA (404) 978-4443