

Radio Editors of magazines and newspapers will be given permission to reprint in whole or in part, with proper credit to the Aerovox Corporation, the contents of this issue of the Aerovox Research Worker, upon written request.

The AEROVOX Research Worker

The Aerovox Research Worker is edited and published by the Aerovox Corporation to bring to the Radio Experimenter and Engineer, authoritative, first hand information on capacitors and resistors for electrical and electronic application.

VOL. 20, NO. 1

JANUARY, 1950

Subscription By
Application Only

Television Interference Filters

By the Engineering Department, Aerovox Corporation

THE advent of television broadcasting has brought about many new problems in interference elimination. Much of this interference is caused by spurious radiations from transmitters of other services. The burden of finding solutions to such problems rests upon the licensee of the transmitter causing the interference, and upon the owner of the set being interfered with — or his service technician. Usually, a satisfactory solution can only be arrived at through the complete cooperation of all parties concerned.

The American amateur radio operator, because of greater numbers, closer proximity to owners of TV sets, has spear-headed the technical battle to find cures for this threat to his hobby. Now, with many "hams" again able to operate at full one-kilowatt input in the midst of dozens of TV receivers, the battle has been won. There remains only the job of

educating others in the methods employed.


The most powerful tool which has been applied to the elimination of television interference (TVI) is the frequency selective filter. The theory and design of such filter networks has been treated at some length in the AEROVOX RESEARCH WORKER in the past. (See March, 1940; September, 1942—February, 1943; August-December, 1944.) This issue discusses the application of filter networks to television interference elimination and describes the construction of practical filters for use at the source of the interference, as well as at the TV set.

Causes of Interference

Because of the lack of selectivity inherent in modern television receivers, they are particularly prone to interference by spurious signals of many kinds. When one considers that the minimum band-pass for tuned receivers

"front-ends" is about 6 mc. and that many using untuned grounded-grid r.f. stages will accept signals over a band many times this width, it is seen why this is so. For example, an amateur transmitter operating at 7 mc. may radiate a small amount of power at each of the harmonics (multiples) of this frequency. The amplitudes of these harmonics diminish rapidly with frequency, but multiples up to the sixteenth or eighteenth may be of sufficient strength to interfere with a weak television signal, depending upon the proximity of the amateur transmitter and its adjustment. Thus, with a harmonic falling every 7 mc., the transmitter stands a good chance of interfering with TV channels 2, 3, 4, and 5, since the 8th through 11th harmonics of 7 mc. fall within them. The degree of interference is usually determined by the proximity of the harmonic to the frequency of the picture carrier. If it is close, the harmonic must be weaker by about 50 db. to avoid interference.

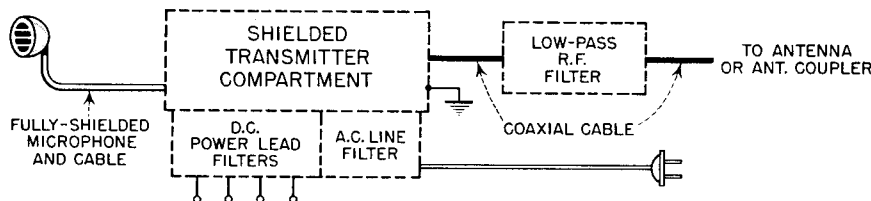By far the most serious harmonic interference is that caused by the second harmonic of "ham" stations operating in the 28 mc. band, since this harmonic falls directly in channel 2 and is usually quite strong. Another such case of troublesome interference is occasioned by the second harmonics of FM stations which fall within the high-band TV channels. The commercial solution to this problem has



ILLUSTRATING USE OF COMPLETE SHIELDING AND FILTERING
AT TRANSMITTER
FIG.1

AEROVOX PRODUCTS ARE BUILT BETTER

been similar to that adopted by amateurs — the use of filters to prevent spurious radiation.

TVI may also be caused by low-frequency signals getting into the receiver i.f. stages, either through the tuner or by direct pick-up in the set wiring. Cases have been observed where picture reception was prevented by signals from European short-wave broadcast stations leaking into the 21.25-25.75 mc. i.f. channel. This type of interference is usually characterized by the fact that all TV channels are effected, regardless of tuning.


TVI Reduction at the Transmitter

Of course, the most effective approach to interference elimination is to start at the source. The harmonic content of the transmitter signal is tremendously affected by circuit adjustments such as grid bias, grid drive, modulation percentage, and tank circuit L-C ratio. If the generation of harmonics and parasitics is first minimized by the selection of the proper values for these variables, the job of preventing the radiation of the remainder is considerably simplified.

In addition, it has usually proven necessary to completely shield the offending transmitter before the work of harmonic suppression by the use of filters can proceed. Otherwise, harmonic radiation may occur from the final tank coil and other parts of the transmitter. Since the wavelength of the harmonics which cause TVI are relatively short, leads of moderate length may act as efficient antennas.

The need for shielding may be determined by loading the transmitter with a "dummy" lamp-load substituted for the antenna. If the TVI clears up, it indicates that the interfering signal is being radiated by the antenna and that the present degree of shielding is adequate. If this test shows that more shielding is needed, the type required need not be elaborate, but must be complete. Commercially built metal cabinets, although neat in appearance, do not always provide effective shielding because of poorly-bonded joints, doors, cracks, and ventilating louvers. The most popular method of shielding employed in amateur practice is to enclose the entire transmitter r.f. chassis in a box made up of close-mesh copper screening, soldered at all junctions to make it absolutely r.f.-proof. This shielded chassis and panel may then be mounted in a standard rack or cabinet to improve the appearance.

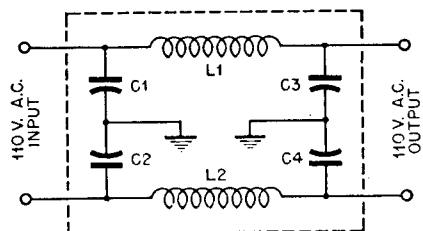With the r.f. portions of the transmitter thus completely shielded, it



L1, L2 - 30T. No.12 E.L. 3/4" FORM
C1, C2, C3, C4 - .005 MFD. MICA (Aerovox Type 1467)

LOW-PASS LINE FILTER
FIG. 2

becomes a relatively simple matter to filter all leads entering this metal enclosure, in the manner indicated in Fig 1. It must be remembered that the key or microphone lead is a potential source of r.f. leakage and must be either shielded or filtered. Any a.c. power leads which enter the chassis must also be filtered. For this purpose, a balanced single pi-section, low-pass filter as shown in Fig. 2 may be employed. A unit of this type may be constructed in a small metal box and bonded solidly to the outside of transmitter shield box for maximum effectiveness. The line filter should not be assembled inside of the transmitter housing because of the danger of the components coupling to harmonics from the tank circuit.

For d.c. leads which enter the shielded compartment, a single L-section low-pass filter of the type illustrated in Fig. 3 has proven effective in preventing r.f. leakage. The values of the components are not critical, but they should be of high quality. Inductances should be of a universal-wound type so that distributed capacitance is reduced. Mica capacitors* should be chosen, according to voltage requirements. A filter of this kind should be used in each d.c. lead which might conduct r.f. out of the shielded housing. Like the line filter, these d.c. filters should also be assembled in a separate metal box which is fastened to the outside of the main shield compartment. A common housing may be used for all power lead filters.


After the job of shielding the transmitter and filtering all power leads has been completed, it should be checked again for TVI. If all signs of interference to nearby television receivers have disappeared when full transmitter power is applied to a dummy load *inside* of the shielded compartment under conditions of full modulation or keying, this part of the job is satisfactory.

*Aerovox Type 1445-47.

If the interference appears when the antenna is again connected, the TVI is reaching the receiver by radiation from the antenna. It may be of the harmonic type or the receiver overloading type. At this point it is well to determine which, since further changes at the transmitter will not eliminate the latter type. The harmonic content of the transmitter signal may be checked by listening on the multiples of the operating frequency with a good VHF receiver, or by building a crystal "harmonic checker." The circuit of a simple device which fulfills this requirement is shown in Fig. 4. It consists of a parallel L-C circuit which tunes to the low TV frequencies and which is link coupled to a crystal rectifier and indicating meter. The tuned circuit must be calibrated in frequency so that harmonics may be identified. Several of the commercial absorption wavemeters may be used for harmonic checking by the addition of the crystal indicating circuit. Alternatively, a grid-dip meter of the type which has provisions for operating the oscillator tube as a diode detector may be employed for locating harmonics.

The harmonic checker should be loosely coupled to the output of the transmitter and a systematic search for spurious frequencies made. The sensitivity of the indicator will be better if a low range microammeter is used. The frequency of all signals detected, other than the carrier, should be carefully tabulated, since this information will prove of value in determining filter requirements.

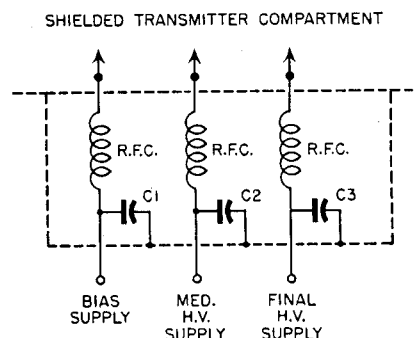If any radiation is detected in the television bands, a filter between the transmitter and the antenna is necessary. Ideally, this filter should be a unit which transmits the amateur frequencies without loss, while present-




R.F.C. - 5 to 10 MICROHENRIES, V.H.F. CHOKE
C1, C2, C3 - .001 to .01 MFD. (SEE TEXT)

SHOWING METHOD OF FILTERING
TRANSMITTER D.C. LEADS
FIG. 3

ATOM SMASHING

with

AEROVOX CAPACITORS

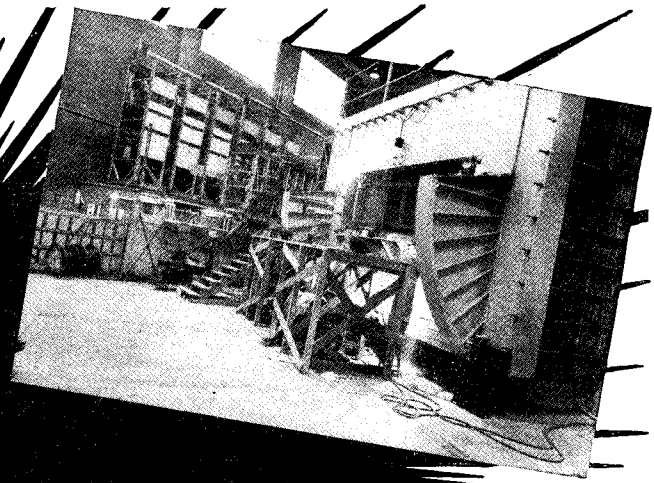

● This Atomic Age calls for huge capacitor banks in atom-smashing installations. Typical is the betatron installation at the University of Illinois, Urbana, Ill., with a capacitor bank totaling 12,960 mfds. made up of 648 units each rated at 20 mfds. 6000 volts D.C. Sufficient energy is stored in this capacitor bank to lift a 3000 lb. car 57 ft.!


Aerovox engineering and experience were important factors in the special design and processing required for the manufacture of these capacitors. Such skill is applied to all Aerovox production, regardless of type or size. Every design is given

individualized attention.

Because of outstanding experience with oil-filled capacitors, together with production facilities difficult to duplicate elsewhere, Aerovox is meeting the rigid requirements of atom-smashing installations.

Likewise for other high-voltage needs such as deep-penetration X-ray, radio transmitting, high-voltage testing, carrier-current coupling, and electronic laboratory equipment, Aerovox offers the widest choice of tried-tested-proven capacitors backed by application engineering second to none.

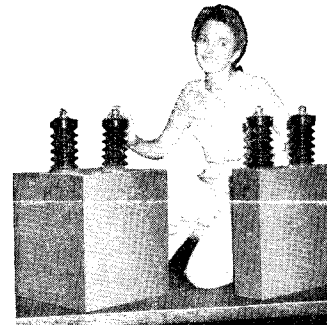Aerovox Series '26 oil-filled stack-mounting capacitors. One or more units can be conveniently banked in series or parallel. Voltage ratings up to 150,000 D.C. Max. per unit.



Aerovox Series '20 steel-case oil-filled capacitors. Voltage ratings up to 50,000 D.C.W. Also dual units of 25,000 v. (12,500-12,500) for voltage doubler circuits.

● Try Aerovox first! Our engineers will gladly share their high-voltage capacitance "know-how" with you in solving your particular problem.



FOR RADIO-ELECTRONIC AND INDUSTRIAL APPLICATIONS

AEROVOX CORPORATION, NEW BEDFORD, MASS., U.S.A.

SALES OFFICES IN ALL PRINCIPAL CITIES • Export: 13 E. 40th St., New York 16, N. Y.

Cable: 'ARLAB' • In Canada: AEROVOX CANADA LTD., HAMILTON, ONT.