

The advertisement features a large, stylized logo at the top. The logo consists of a circular emblem with a scalloped edge. Inside the circle, the letters 'CD' are prominently displayed in a bold, serif font. The words 'CORNELL-DUBILIER' are written in a smaller, sans-serif font along the top inner border of the circle. Above the circle, the word 'The' is written in a large, cursive script. Below the circle, the word 'Capacitor' is written in a large, flowing cursive script.

Below the logo, there are two detailed models of industrial buildings. The model on the left is labeled 'SO. PLAINFIELD, N. J. PLANT' and the model on the right is labeled 'NEW BEDFORD, MASS. PLANT'. Both models show multiple buildings with smokestacks and intricate architectural details.

Vol. 9

NOVEMBER, 1944

No. 11

CORNELL-DUBILIER ELECTRIC CORP.
HAMILTON BOULEVARD
SOUTH PLAINFIELD, N. J.

Sec. 562, P. L. & R.
U. S. POSTAGE
PAID
So. Plainfield, N. J.
Permit No. 1

FOR VICTORY



Mr. George M. Beale
130 25th Ave.
San Francisco, Calif.

WANTED!

Case Histories of **Cornell-Dubilier Capacitors**



HUNDREDS of Dubilier mica and paper capacitors made over a decade ago and more, are still giving efficient and reliable service in radio and electronic equipment. These capacitors are as good today as the day they were made. We are collecting case histories of such units.

If you know of a Dubilier capacitor ten years old or more, in use today, please tell us all about it and in what type of equipment it is used. A post card will do. Thank you.



Address:

EDITOR, THE C-D CAPACITOR
Cornell-Dubilier Electric Corporation,
South Plainfield, N. J.



A Free Market-Place for Buyers, Sellers, and Swappers.

These advertisements are listed FREE of charge to C-D readers so if there is anything you would like to buy or sell; if you wish to obtain a position or if you have a position to offer to C-D readers, just send in your ad.

These columns are open only to those who have a legitimate, WANTED, SELL or SWAP proposition to offer. The Cornell-Dubilier Electric Corp. reserves the right to edit advertisements submitted, and to refuse to run any which may be considered unsuitable. We shall endeavor to restrict the ads to legitimate offers but cannot assume any responsibility for the transactions involved.

Please limit your ad to a maximum of 40 words, including name and address. Advertisements will be run as promptly as space limitations permit.

FOR SALE—Kolster K20 radios for P.M. speakers. Colonial radio chassis and spkr. for model 38; Kolster K5 amplifiers; RCA Victor R32 radio; G.E. chassis and speaker, table mod. K32; Majestic table mod. 370 and speaker; Majestic 90B and 90 spkr. Ultra violet carbon lamp; electric shaver. Louis A. Goldstone, 1279 Sheridan Ave., Bronx 56, New York, N. Y.

FOR SALE—Brand new tube checkers, G.E. model TC-3, test all tubes, past, present and future, portable carrying case. Limited supply. Victor Kozma, 3104 Wilkinson Av., New York 61, N. Y.

FOR SALE—Radiotron Designer's Handbooks, price \$1.10 postpaid. A handbook of receiver design for servicemen and engineers. Description upon request. The Engineers' Book Co., Box 575, Alexandria, Va.

WANTED—Amperite kontak mike, automatic changer, prefer Garrard or Capehart. Will pay cash. Have television parts for sale. F. J. Lydon, 54 Fair St., Norwalk, Conn.

FOR SALE—Superior channel analyzer \$25.00. Rider's Manuals 1 through 8, \$55.00. Prices are F.O.B. Cleveland Roth Radio Lab., 3646 Antisdale, Cleveland Heights, Ohio.

FOR SALE OR SWAP—For photography equipment, test instruments and service books. For complete list write Edw. Podulaly, 1313 N. Vernon, Dearborn, Mich.

WANTED—Late model tube tester, sig. gen., voltohmmeter, condenser tester; also 2-speed recorder and playback and Rider's Manuals. Lew's Radio Service, 233 S. Conn. Ave., Atlantic City, N. J.

FOR SALE—Stancor A pack, new, Master, \$50; Remington rifle, new condition \$20.00, pump action .22 cartridge, 1/4 h.p. G.E. electric motor, A-1, \$10.00; Philco 1941 auto radio, new, \$45.00 Paul Capito, 637 W. 21 St., Erie, Pa.

WANTED—Test equipment, such as Hickok, Supreme, Precision, tube checkers, VOM meters, prefer late models. Send price, condition, etc., in first letter, to Charles F. Elgasser, Jr., 2771 "A" Street, San Diego 2, Calif.

WILL SELL — RCA phono-oscillator with small mike, complete schematic and wiring diagrams included; range 900-1200 kilocycles. Used about 10 hours. Will sell for \$5.00. F. J. Timka, Jr. 1211 Park Ave., Rochester, N. Y.

TRADE—RCA oscillograph model 155A for Hallicrafters SX-24 or S20R plus \$18.00. Has new RCA 3AP1 cathode ray tube. Charles Franklin, 17 W. Keller St., Mechanicsburg, Pa.

FOR SALE—Gardiner-Levering automatic code sender, model S, 115 v. 50/60 cycles ac, with ten tapes. Like new \$10 cash or C.O.D. Howard A. Fischer, 1510 Washington St., Wisconsin Rapids, Wis.

FOR SALE—One $\frac{3}{4}$ h.p. electric a.c. motor, 60 cycles, 110 v., 3450 r.p.m. This is a Craftsman motor, ball bearings. New, never used, \$32.00. Clair E. Breth, Sr., 213 South 4th St., Youngwood, Pa.

WANTED — Superior channel analyzer, model 1230, or American 4103 signal generators. H. R. Ringold, 132 N. Doherty Dr., Beverly Hills, Calif.

WANTED—One modern tube tester which will check all new type tubes. Good condition. State price. Also want following tubes 2 35L6, 2 117Z6GT, 2 1A7, any type. Worden Radio Shop, Friend, Nebraska.

FOR SALE OR TRADE—Rider's Manuals 1 to 6, and No. 13, also two vols. Gernsback. Will sell or trade for Supreme Vedolyzer and signal generator. Frank J. Moch, 5925 South Albany Avenue, Chicago, Ill.

WILL SELL—Supreme Vedolyzer, model 560A, metered A.F. and R.F. oscillator, model 561, multi-meter and analyzer, model 592; Stancor power pack, model 132; Triplet tube tester, model 1213, Triplet multimeter, model 1200E. Joseph Tomalesky, 30 Fabian Place, Newark, New Jersey.

FOR SALE — Hickock counter type tube tester, Philco automatic record changer with cutting arm, Superior channel analyzer, Modern Radio Servicing book by Ghirardi and No. 8 Rider Manual. \$140.00 takes all. Supreme Co., 107 E. Long Ave., New Castle, Pa.

FOR SALE—Meissner 8 tube ac-dc FM tuner complete with new tubes, tuner chassis perfect, cabinet bit marred. Price \$20.00. All letters answered. Also clockwork Instructograph with built-in oscillator and good batteries, complete with ten tapes. Used very little. Price \$23.00. Maurice Rushworth, 531 South Longwood St., Baltimore 23, Md.

FOR SALE—Seven space heaters, Norge and Quaker, all inquiries answered. Frankenstein Sales & Service, 437 Pennsylvania Avenue, Brooklyn 7, New York, N. Y.

WANTED—872A rectifiers, pair of Eimac 1000 tubes, filament transformers for above tubes; No. 0 or 00 wire; 3" or 5" oscilloscope; microammeters; Driver transformers for above tubes. H. N. Luke, 2113 Somerset Place, Oklahoma City 6, Oklahoma.

WANTED—Recorder and play back with 2 speed motor. Must be in excellent condition, also late model analyzer and tube checker. Lew's Radio Service, 233 S. Conn. Ave., Atlantic City, N. J.

FOR SALE—Two Crosley model 417 interoffice communication sets, each unit complete, two-way talk-listen, perfect condition, each has 6I7, 25A7, 25A6. Best offer takes or will trade for first class, all-wave sig. gen. J. B. Tannehill, 210 South College, Salem, Ill.

SWAP—Portrait camera, Voigtlander 37 mm, 13 in. focal length lens. Uses 6x8 film. Rising, falling, removable front. Tilting removable back; 6 film holders; 6 printing frames; 13x12x8 wood case. 5 ft. tripod. Extra lens flange. S. Millen, 40 Wayland Street, Boston, Mass.

WANTED — Capacitor Bridge BN and good ac signal generator. State model, condition, and price in your letter. Will exchange 35Z5 and 12SK7 for 12SA7 and 12SQ7. Tubes to be perfect and in sealed cartons. Louis Fialkoff, 143-48 41st Avenue, Flushing, New York.

FOR SALE—Rider's Manuals 1 to 8 in new condition. Readrite 430 tube checker with Triplet meter. Double button carbon mike with desk stand and cord. C. Klepper, 122-20 Linden Blvd., Ozone Park 20, New York.

FOR SALE—Voltmeter, 9" dial scale, in perfect condition \$55; also signal generator, covers 100 k.c. to 90 m.c. in harmonics, \$45. C. C. Levenburg, 2725 W. Boston, Detroit 6, Mich.

WANTED—Good used tube tester preferably Triplet, to test all tubes to date. Albert W. Johnson, Box 473, Wakefield, Neb.

WANTED—Instructograph with earphones and key. State condition and price wanted. Also want model airplane motors. Robert Phillips, P. O. Box 353, Genoa, Illinois.

FOR SALE—Two $\frac{1}{4}$ horse elec. Frigidaire motors. Buckwheat coal blower, complete with day-night controls, thermostat, wire. Weston 0-200 m.a. meter. Radio Shop, No. 12 Bellevue, 225 No. 63rd St., W. Philadelphia 39, Pa.

WANTED—Second intermediate trans. for Majestic 15 (Grigsby-Grunow) original part no. 8384; 4429, Carrons D-4089, Meissner 20-5310. General Radio Service, 1203 Eckart St., Fort Wayne 5, Indiana.

WANTED—3 dimensional pantograph machine. Cash for Deckel, Gorton or what have you. R. Rosenwasser, 1177 East 14th St., Brooklyn 30, New York.

WANTED—Fresh water casting reel, level wind in good condition. Have meters and parts. H. B. Mawby, 2273 Cove Road, Merchantville, N. J.

(Continued on page 15)

PHASE INVERTER CIRCUITS*

In the search for simplified and more economical circuits for radio receiver and amplifier construction, it was only natural that some means should be developed to eliminate the push-pull input transformer which is bulky, susceptible to hum pickup, and often a source of frequency discrimination. Without doubt, good transformers are available which are capable of supplying the desired results, but good transformers are far more costly than a few resistors and another tube. The development of the beam power with its high power sensitivity, and the general use of inverse feedback to eliminate the effects of cabinet resonance, speaker resonance, and deficiencies otherwise

tually, such perfect phase inversion is seldom obtained, nor is it absolutely necessary, for other considerations render it difficult to detect by ear slight differences in either phase or amplitude of a push-pull signal. This article has been written to point out the advantages and disadvantages of the more common types, and to present a new circuit, which, while not original with the writers, was investigated by them.

The most obvious circuit for phase inversion, and one in common use is that of Fig. 1. The signal is applied to the grid of V_1 , is amplified, and appears at point B, which is to be connected to the grid of one of the output tubes. A portion of that signal is fed back to the grid of the second tube, V_2 , that portion being tapped off at the junction of R_1 and R_2 . R_2 can be determined from the formula

$$\frac{R_2}{R_1 + R_2} = A_2$$

where A_2 is the voltage gain of the stage V_2 . R_3 is presumed to be equal to $R_1 + R_2$. The voltages available for the grids of the following tubes, E_{k1} and E_{k2} , are equal, opposite in phase, and can be represented by $E \times A_1$, where A_1 is the voltage gain of V_1 . With respect to the phase differential, there can be no doubt that there is

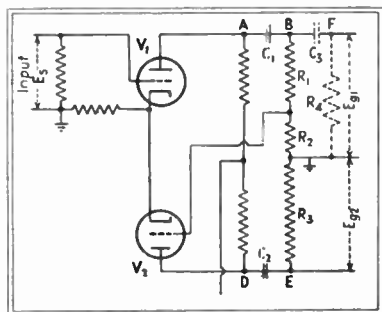


Fig. 1. Conventional two-tube phase inverter circuit.

occurring in a production model, have advanced the use of phase inversion which eliminates the phase shift introduced by the input transformer. This effect is particularly vicious in the "driver" type of transformer.

Theoretically, a perfect phase inverter should be capable of taking a signal applied to its input and converting it to two signals of exactly equal magnitude which are exactly 180° out of phase, and which are exact facsimiles of the input signal. Ac-

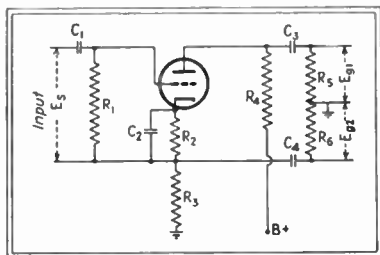


Fig. 2. One-tube phase inverter with input above ground potential.

By C. G. McProud and R. T. Wildermuth in "Electronics."

180 shift between points B and D, but there is a slight shift between D and E, which is caused by C_2 and R_3 . This could be corrected by the addition of another phase shifting element, C_3 and R_4 . Granted that this phase shift is slight, in some cases where large amounts of inverse feedback are used, it contributes to the limiting of the maximum that can be used. The main disadvantage of the circuit lies in the fact that if V_2 should age, or should lose enough emission to seriously affect its amplification, the two output voltages are no longer equal, with attendant distortion. The main advantage lies in the gain obtained from the circuit in addition to the inversion. Variations of this circuit are common enough, in which V_2 is of a different type, or both V_1 and V_2 are in the same envelope, but the same factors apply to all of them.

A circuit which performs the inversion with only one tube is shown in Fig. 2. The main disadvantage here is the necessity for introducing the signal between points which are considerably above ground potential. Differences in capacity between ground and these points will affect the similarity between the signals appearing at the grids. The output voltages here will be seen to be

$$E_{x1} = E_{x2} = \frac{1}{2} A E_s$$

R_3 and R_4 are equal. The bias for the tube is developed across R_2 , with the customary by-pass condenser, C_2 .

This circuit can be improved by introducing the signal between grid and ground, which will remove one of the objections to it. Then the degeneration which occurs across resistor R_3 will reduce the gain of the stage to approximately zero. From the standpoint of cost, this circuit is a satisfactory solution, since, excluding the input condenser C_1 and the output condensers C_3 and C_4 which are common to all of these circuits, only one tube, four resistors, and one high-capacity, low-voltage electrolytic condenser are used.

As long ago as 1937, there appeared in print another circuit, Fig. 3, which is essentially the same as the one just

discussed. In this case, the bias was obtained from a point on the voltage divider. Assuming that the voltage

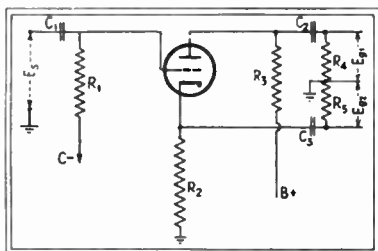


Fig. 3. One-tube circuit with bias obtained from separate supply.

divider would be used anyway, the components are reduced to one tube and three resistors, though it is highly probable that some filtering would be required in the grid circuit. In the article cited, the tube used was a 76, with R_2 and R_3 25,000 ohms each. It was claimed that the output voltages were approximately $0.8 E_s$, resulting in a loss of 2 db. By increasing the values of R_2 and R_3 to 50,000 ohms, the output becomes equal to the input.

In Fig. 4, the phase inverter of Fig. 2 has gone through another stage of simplification, and now requires the tube and four resistors. R_3 and R_4 are 50,000 ohms each. R_1 , representing the input impedance of the stage,

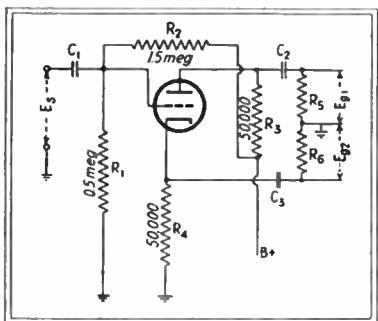


Fig. 4. Method of obtaining bias from plate supply.

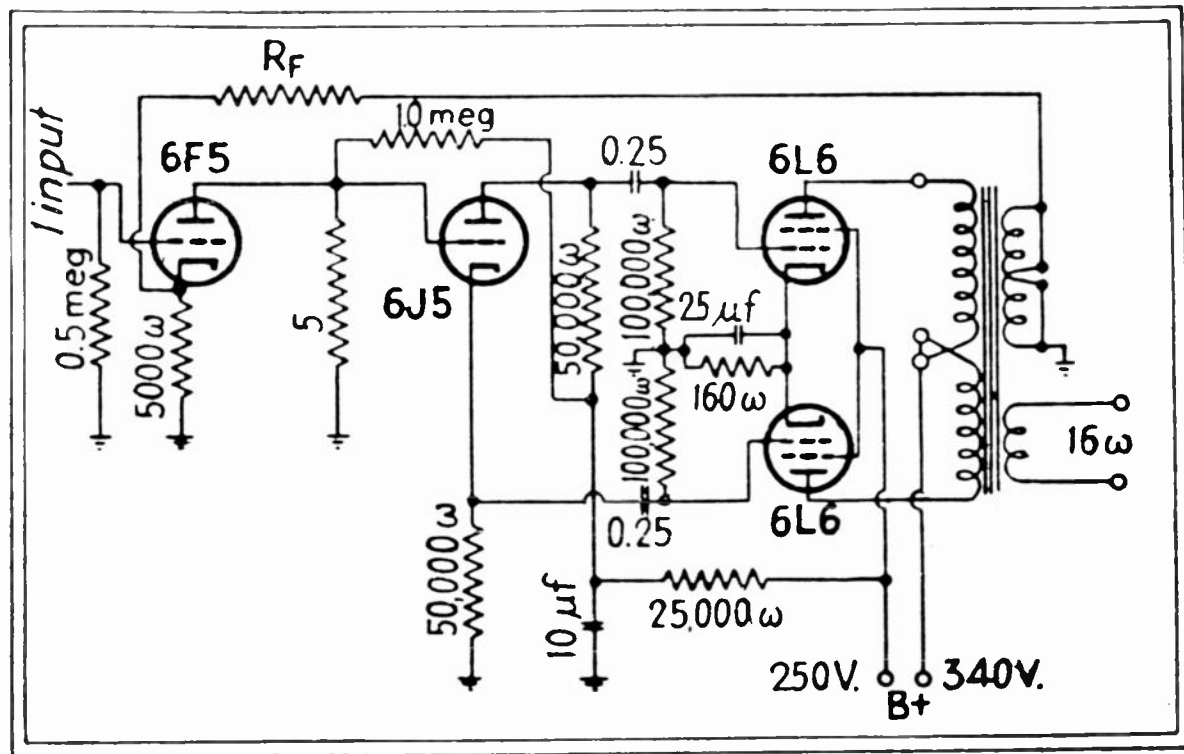


Fig. 5. Complete amplifier with direct-coupled input stage.

is set at 0.5 megohm. R_2 is selected to produce the proper grid bias. With the other values mentioned, R_2 comes out to be 1.5 megohms. This value is not at all critical, and the usual resistance tolerances will be close enough to make an excellent phase inverter. Nor is the circuit critical about what kind of tube is used, a low- μ or a high- μ triode, or a pentode, the output is still the same, equal to the input. The triode is naturally simpler, so a 6J5 or a 6SJ7, triode connected, is preferred. There is no amplification, since in adding up the voltage gain of several stages to obtain the overall of an amplifier, none should be considered as coming from the inverter. There is a slight differential in the phase shift occurring at the two output grids, which was thought to be due to the capacity between cathode and a normally grounded heater. Actually, the shift is around 2° at 8000 cps, which is slight enough to overlook. It can be corrected by decreasing the grid leak on the plate side, but that introduces other difficulties which are more objectionable. For exact equality in amplitude of the output voltages, R_0 and R_1 should be balanced as closely as possible.

At a plate supply potential of 200 volts applied at B+, the plate current is approximately 1.0 ma. Therefore the cathode is 50 volts above ground. The R_2 R_1 network applies 50 volts to the grid. The plate current increases sufficiently to place a bias of about 4.5 volts to the grid, automatically balancing itself to that operating condition, no delicate adjustments being necessary. Measurements show that with a 250-volt supply a r-m-s voltage of 45 volts can be obtained with 2 per cent distortion, which is more than enough to drive a pair of 45's in the 275-volt operating condition, in which they require 39 volts r-m-s. This requires an input voltage equal to that which can be supplied easily by a 6R7 with 250-volt supply and a load resistor of 0.25 megohm. The output voltages obtainable with a 6J5 in this circuit,

with 2 per cent distortion are shown in the curve in Fig. 6.

With 50 volts available on the grid of the inverter tube, the next step is to couple the preceding tube directly to it, using that voltage for its plate supply. Normally, the other tube would be coupled to this grid through a condenser, using a separate load resistor with the attendant decoupling filter resistor and condenser. This has been found unnecessary, for the plate of a 6F5 or 6SF5 can be connected directly to the 6J5 grid with considerable improvement in overall operation, particularly if inverse feedback is to be used. The bias resistor of 5000 ohms, not bypassed, is a logical point for the introduction of the

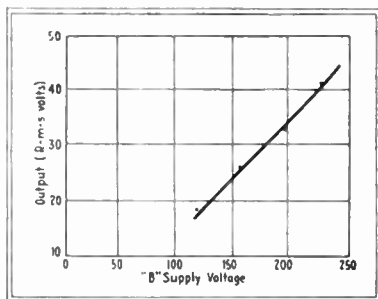


Fig. 6. Output voltage from 6J5 as function of plate supply voltage.

feedback voltage. Figure 5 shows the complete circuit of an amplifier using this system. The bias-balancing resistor has been reduced to 1.0 megohm to make up for the plate current of the 6F5. Without feedback, an input signal of 0.44 volts r-m-s is all that is required to drive the 6L6's to overload. With 17db of feedback, the input requirements increase to 3.1 volts r-m-s for maximum output. In the circuit shown, using two 500-ohm output transformer secondaries in shunt, the feedback resistor, R_f will give 10 db of feedback when its value is 240,000 ohms. 100,000 ohms will give 17

(Continued on page 14)

OPEN-GRID TUBES IN LOW-LEVEL AMPLIFIERS*

For certain applications in amplifiers requiring a high input resistance and low noise level it has been found desirable to eliminate the grid leak, and no undesirable effects resulted from using the tubes in this manner. Examples of such applications are amplifiers operating from a low-level, high-impedance source, amplifiers that must present the smallest possible load to the preceding stage, and amplifiers that must handle signal voltages of the same order as the noise level. Actually, operation of a tube with an open grid is less noisy than operation with a grid leak.

Problems To Be Overcome

Different objections to the use of open grid tubes can be summed up as follows:

(1) It has been suggested¹ that if the operating temperature of the tube is high enough, the grid will emit electrons. When this occurs in a conventional circuit, the resulting current through the grid leak (generally a resistance of about 2 megohms connected between grid and cathode) will make the grid less negative and increase the space current, thus increasing the temperature. If the grid becomes positive, electrons flowing to it will increase the grid temperature and might produce secondary emission. The grid will continue to become less negative as long as the number of electrons leaving the grid exceeds the number entering. This process is cumulative and may result in damage to the tube. The process might be aided initially by the flow of positive ions to the grid when it is negative. This effect would be most pronounced in a soft tube. It has been

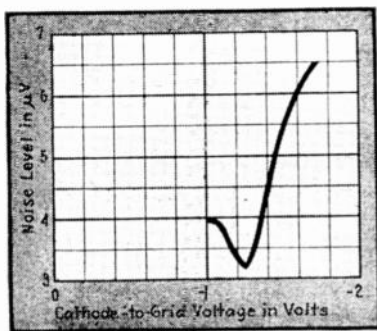


FIG. 1—Noise level vs. cathode-to-grid voltage for a 6SJ7 tube connected as a triode, with $40\ \mu\mu\text{f}$ in the grid circuit to simulate a high-impedance crystal pickup having no shunt resistance

asserted that the use of extremely high cathode-to-grid resistance (such as an open grid) would tend to aid the process by producing large voltage drops in the grid circuit.

(2) If the grid leak is omitted, electrons will flow to the grid from the cathode and the grid will accumulate a negative charge.² Then any slight change in the grid capacitance would change the grid potential and produce fluctuations in the plate current.

(3) There is a small current flowing between the cathode and the grid through the leakage paths. However, these leakage paths are continually changing and thus there is a random fluctuation in the grid leakage current which produces noise in the tube. This effect should be most prominent during the time when the tube is heating.

* By Robert J. Meyer, "Electronics."

Noise in Amplifier Circuits

The three principal types of noise in an amplifier circuit are flicker, shot effect and thermal agitation. These noises can be considered as being developed by equivalent generators in the grid circuit of a noise-free tube.

The flicker voltage, which is produced by irregularities in the temperature of the heating element, is inversely proportional to the square of the frequency.

Shot noise is uniformly distributed throughout the frequency spectrum, independent of the electron velocity and independent of the manner in which the total current divides between the electrodes. The values of the shot voltage E for triodes can be calculated from the formulas³

(1)

$$|E| = 2 \times 10^{-10} \sqrt{\Delta F / g_m}$$

For pentodes, the formula is

(2)

$$|E| = \frac{2 \times 10^{-10}}{g_m} \sqrt{\frac{I_b}{I_b + I_a} (g_m + 8 I_a) \Delta F}$$

The thermal agitation voltage developed by a resistor is

(3)

$$E^2 = 4 K T R \Delta F$$

where R is the resistance, ΔF is the frequency band passed, T is the temperature in degrees Kelvin and K is Boltzmann's constant (1.39×10^{-23}).

If the impedance in the grid circuit is not a pure resistance, the resistive component is a function of the frequency and the voltage can be obtained from:

(4)

$$E^2 = 4 K T \int_{f_1}^{f_2} R(f) df$$

These formulas apply only to wire-wound resistors or to carbon resistors in which no current is flowing.

There is always some capacitance across a resistor and this parallel combination forms a low-pass filter which affects the thermal agitation voltage e as follows:

(5)

$$e = 1.28 \times 10^{-10} \sqrt{R F_0 \left(\tan^{-1} \frac{F_2}{F_0} - \tan^{-1} \frac{F_1}{F_0} \right)}$$

where $F_0 = 1/2\pi RC$ and F_2 and F_1 are the upper and the lower frequency limits, respectively, being considered. It can be seen from Eq. (5) that the thermal agitation voltage output of an RC combination is independent of the value of R , because $F_1 = 0$ and $F_2 = F_0$, reducing e from a function of R and C to a function of C only.

If the noise voltage from an RC combination is applied to an amplifier, some of this voltage may be in a part of the frequency spectrum which is not passed by the amplifier. In this case the voltage passed by the amplifier would be a function of R as expressed in Eq. (5), where F_1 and F_2 would now be the frequency limits of the amplifier, and R and C would be the grid leak and the input capacitance in the amplifier circuit. If F_1 is very much less than the upper frequency limit of the amplifier, Eq. (5) reduces to:

(6)

$$e = 1.28 \times 10^{-10} \sqrt{\frac{1}{2\pi C} \cot^{-1} \frac{F_1}{F_2}}$$

The form of Eq. (5) can be changed to show more clearly the relation between the thermal noise and the value of R .

(5a)

$$e = 1.28 \times 10^{-10} \sqrt{\frac{1}{2\pi C} (\tan^{-1} 2\pi F_2 CR - \tan^{-1} 2\pi F_1 CR)}$$

(5b)

$$\tan \left[\frac{2 \pi C e^2}{(1.28 \times 10^{-10})^2} \right] = \frac{2 \pi C (F_1 - F_2) R}{1 + 4 \pi^2 F_1 F_2 C^2 R^2}$$

Eq. 5 (b) shows that the noise increases as the value of R increases from zero, reaches a maximum at some finite value of R , and decreases as the value of R is increased beyond this value. This equation shows that operation of a tube with an open grid would be less noisy than operation with a grid leak. In an amplifier circuit, to obtain minimum noise, the grid leak is sufficiently high if the thermal noise is less than the shot effect.

Another source of noise is the flow of leakage current between the cathode and the grid. This noise would be at a minimum when the cathode-to-grid voltage is at a minimum. Thus the tube would be quietest with a proper value of bias and it remains to be shown that the open grid tube automatically biases itself to that bias voltage.

To aid in determining the desirability of an open grid, a low noise level, wide-range amplifier was built. The first stage had a 6SJ7, triode-connected, with a gain of 11 db. The next two stages, using 6SJ7 tubes, had a gain of 68 db. The output stage, using a 6J5, was a cathode follower. The frequency response was down 6 db at 200 cycles and at 200 kc. The entire amplifier was built in a copper box which gave excellent shielding. Because flicker noise is a low-frequency effect and not dependent upon the grid leak, a high-pass constant- K filter was placed at the output of the amplifier to suppress frequencies below about 650 cps and thus substantially eliminate the flicker effect.

Experiments With Open-Grid Tubes

The first tests were made with a cathode resistor alternately in and out of the first stage. A 40- μmf capacitor was used in the grid circuit to simulate the condition of an open-grid tube

operating from a high-impedance crystal. For the next two measurements a 35-megohm resistor was put in parallel with the capacitor to give the condition of operation with a high-value grid leak. Finally, the grid was shorted to obtain the value of the tube noises. The noise at the grid was obtained by dividing the noise output by the gain. Typical results are given in Table 1.

TABLE 1. EFFECT OF CATHODE RESISTOR ON NOISE

Cathode Resistor	Grid Circuit Impedance	Noise at Grid (μv)
In	40 μmf	3.32
Out	40 μmf	4.26
In	40 μmf and 35 meg.	3.68
Out	40 μmf and 35 meg.	8.40
In	Short	3.00
Out	Short	3.69

These results show that the noise is less with an open grid than with a grid leak. In all three cases the noise is less with a cathode resistor than without one. This result is to be expected, for the cathode resistor voltage drop reduces the voltage between the cathode and the grid, reducing the leakage current and the noise resulting from it. The value of noise obtained with a grid leak and no cathode resistor is exceptionally high, probably because the zero bias allows a comparatively high value of grid current to flow through the carbon grid leak, greatly increasing the noise across the resistor.

Effect of Cathode Resistor Value

Noise measurements were taken with different sizes of cathode resistors. The test was made with 40 μmf in the grid circuit. The resulting curve of noise level vs. cathode voltage is not so important as the curve of noise level vs. Cathode-grid voltage. Since this voltage cannot be measured directly because any voltmeter would upset the circuit conditions, it was necessary to obtain a calibration curve of plate potential vs. grid voltage without a cathode resistor.

The curve of noise level vs. cathode-grid voltage is given in Fig. 1. Least noise is obtained for that value of cathode resistor which gives cathode-grid voltage of -1.2 volts. The

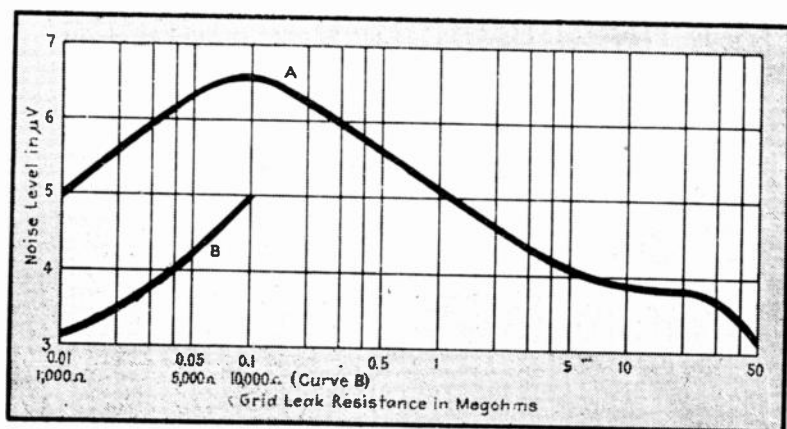


FIG. 2—Noise level vs. grid leak value for a triode-connected 6SJ7 tube. Curve B is for very low values of grid-cathode resistance

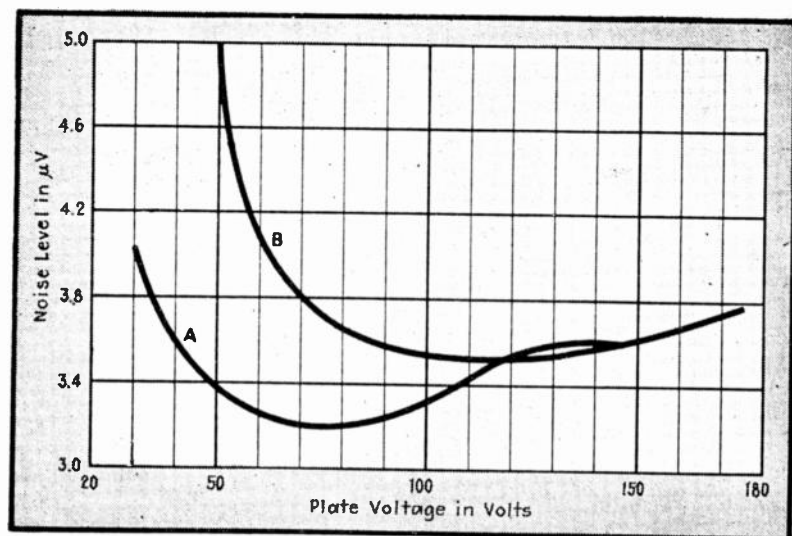


FIG. 3—Noise level vs. plate voltage for a triode-connected 6SJ7 tube with two different grid circuit arrangements. Curve A—40 $\mu\mu f$ in grid circuit; curve B—40 $\mu\mu f$ in parallel with 35 megohms in grid circuit

open-grid tube seems to automatically bias itself approximately to that value which gives the least noise. The effect of electron flow to the grid (which tends to make the grid negative) and the effects of emission from the grid and gas current to the grid (which tend to make the grid positive) balance each other to give the grid a small negative bias.

The foregoing test was repeated with a 35-megohm grid leak in addition to the 40 μf capacitor. The minimum noise obtained was greater than the minimum noise without the grid leak.

Effect of Grid Leak Value

Figure 2 shows the relation between the noise level and the value of grid leak. These readings were taken with a 750-ohm cathode resistor. Except for a shorted or nearly shorted grid the best signal-to-noise ratio is obtained with an open grid. For the constants in this test, i.e., amplifier frequency response and input capacitance, the worst ratio is obtained for a grid leak around 100,000 ohms. For a different amplifier the worst ratio would occur at a different value of grid leak but the general shape of the curve would be the same. These results are in agreement with Eq. 5(b) and the discussion following it.

Effect of Plate Voltage

The relation between the plate voltage on a tube and the noise level at the grid is given in Fig. 3. Again there is less noise without a grid leak than with a grid leak, but in both cases the best signal-to-noise ratio is obtained for a plate voltage of about 90 volts.

It would be expected from Eq. (1) that the noise would continue to decrease as the plate voltage is increased because the g_m is increasing. However, the larger number of positive ions and secondary electrons present in the tube at higher plate voltages tends to make the tube slightly noisier.

Effect of Temperature and Time

In various measurements it was noticed that the noise changed as the

temperature of the tube changed, the noise in a cold tube being greater than the noise in a warm tube. This effect is undoubtedly due to leakage paths, which change as the tube is heated and become saturated when the tube is hot. The change in the noise level is just as great with a grid leak as without one, and thus the addition of a grid leak does not reduce the noise due to the random leakage paths. An attempt was made to reduce this transient effect by boiling the tube and its socket in wax, but this did not help nor did it reduce the noise level.

A long-time test was performed on five 6SJ7 tubes by continuously drawing plate current through the tubes and measuring the noise level at certain time intervals. Typical results are given in Fig. 4. It can be seen that the tubes have a general tendency to become noisier with age, but that in all cases, the noise is greater with a grid leak than without a grid leak.

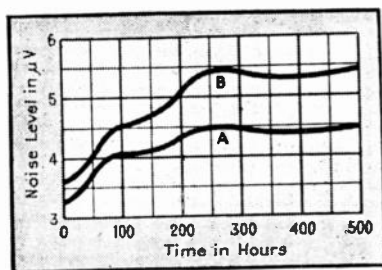


FIG. 4—Noise level vs. number of hours of continuous operation for a triode-connected 6SJ7 tube. Curve A—40 μf in grid circuit; curve B—40 μf in parallel with 35 meg in grid circuit

These tests show that tubes operated without a grid leak do not tend to become any more erratic than tubes operated with a grid leak.

Conclusions

In the experiments performed, the noise level was always less without a grid leak than with one. In no case

did omission of the grid leak lead to excessively high plate current or to high operating temperatures, nor did the grid bias become high enough to block the tube. In the aging test, open-grid tubes also performed better than tubes with a grid leak. The noise is also less with a cathode resistor (of proper size) than without one. With a fixed bias resistor and variable plate voltage the least noise was obtained with a plate voltage of about 90 volts for a 6SJ7 tube.

If the tubes are to be operated with nearly zero grid bias the lower noise level obtained by the omission of the grid leak is especially noticeable. From Table 1 it can be seen that for optimum grid bias the ratio of noise with a grid leak to the noise without a grid leak is 1.11, and for zero bias this same ratio is 1.97. This shows the advantage of operating without a grid leak for zero bias.

Operation of a tube without a grid leak seems practical in applications involving low-level operation, with no

d-c potentials in the preceding stage, and a negative grid bias of not more than about 2 volts.

Tests were also performed on pentode-connected 6SJ7 tubes and on 6J5 tubes, and similar results were obtained.

REFERENCES

- (1) Reich, H. J., "Theory and Applications of Electron Tubes," McGraw-Hill Book Company, 1939, p. 184.
- (2) Everitt, W. L., "Communications Engineering," McGraw-Hill Book Co. 1937, p. 241.
- (3) Harris, W. A., "Fluctuations in Vacuum Tube Amplifiers and Input Systems," *R. C. A. Review*, 5, April 1941, p. 505.

BIBLIOGRAPHY

- (1) King, Ronald, A Screen Grid Voltmeter Without External Leak, *Proc. I.R.E.*, 22, June 1934, p. 771.
- (2) Moullin, E. B., "Spontaneous Fluctuations of Voltage," Oxford Univ. Press, 1938.
- (3) Terman, F. E., "Radio Engineering," McGraw-Hill Book Co., 1937, p. 228.

PHASE INVERTER CIRCUITS

(Continued from page 8)

db of feedback, 68,000 ohms 20 db, 52,000 ohms 22 db, and 36,000 ohms 24 db. The amplifier is perfectly stable with 22 db of feedback. When it was first constructed, the conventional method of coupling the 6F5 and the 6J5 was used, and with that connection, the amplifier became unstable with 17 db of feedback, due to phase turnover. With the slight change to direct coupling, the additional 5db became available, using the same parts throughout otherwise. It will be noted that the output transformer has its two 125 ohm secondaries strapped in parallel, a connection advanced by J. N. A. Hawkins to increase the available feedback due to the reduction in leakage reactance in

the transformer, and consequent decrease in phase turnover.

The complete amplifier shown has a gain of 60 db, figured as most public address amplifiers are, from a 100,000 ohm source. Measured with a gain-set terminated with 500 ohms, with the 500,000 ohm input bridged directly across it, it has a gain of 30 db; with the feedback resistor of 100,000 ohms removed, the gain increases to 47 db. With a suitable input transformer, and using the feedback of 17 db, it makes a very useful power amplifier to follow a pre-amplifier, mixer and booster or similar equipment with a nominal output level of 0 db. It is flat to within 0.2 db from 30 to 13,000 cycles, and has a power output of 35.2 db at 2 per cent distortion, that is, roughly, 20 watts.

THE RADIO TRADING POST

(Continued from page 4)

FOR SALE—Desk type fluorescent lamp adjustable, fastens with screws to bench or desk, with 15 w. bulb, price \$6.50. W. Freising, 1702 6th St., Rensselaer, New York.

WANTED—Late Sprayberry or NRI complete radio course. State condition and lowest price. Albert Spector, 178 Cornell St., Rosindale 31, Mass.

FOR SALE—Meissner F.M. converter, first class shape, make offer. Want crystal pickup, phono motor, recorder. A. M. Stump, 311 Marathon Avenue, Dayton 6, Ohio.

FOR SALE—Three 2½ meter Abbott transmitter, receiver, TR4s, including Mallory Vibrapacks 552s, with auxiliary high voltage filters and Mallory battery chargers. Mikes and cables included, like new. Holden Radio Service, 405 Tarklin Hill Rd., New Bedford, Mass.

WANTED — Test instruments that are broken. Give price and complete description and condition in first letter. Radio-Electronics Lab., Rt. 1, Box 1262-A, Houston, Texas.

WANTED—Handee, Craftsman, or Moto-Tool electric grinder; drill press, lathe, bandsaw, Argus C-3 camera. State make, model, condition and price. J. W. Bourke, 196 Clinton Ave., Brooklyn 5, New York.

WANTED—VOM with 1000 ohms per volt sensitivity with zero adjustment. Also meters with same sensitivity. Will pay cash, or exchange with D5T model American dynamic mike, new. George Uyeda, 858 N. University Ave., Provo, Utah.

FOR SALE—Na-ald 907 kit of 5 adapters, plug, cable, etc., never used, \$5. Super Radio Service, 138 Vine St., Plymouth, Pennsylvania.

FOR SALE — One each of the following guaranteed tubes at OPA list price if entire lot bought: 1C5GT, 1D7G, 1E7G, 1G6G, 1LB4, 1LH4, 1LN5, 1N6G, 3A4, 6A6, 6A8, 6CBG, 6J5, 6K7, 6L6G, 12A5, 12SK7GT, 12SQ7GT, 12SN7GT, 25A6, 25L6GT, 25Z5 or 25Z6, 32L7GT, 35Z3, 35Z5, 35L6GT, 50L6, 50Z7, 82, 112A, 117L7GT, and 117Z6. Goodwin Radio Shop, Ran-kin, Ill.

WANTED—1939 auto radio, Philco, mod. C-1608; price and condition. Rider's manuals from No. 9 to 13. State price and condition. Philann Radio service, 348 Melrose St., Brooklyn 6, New York.

FOR SALE—Supreme 546 3" oscilloscope, Supreme 582-A signal generator, used very little \$125, or best offer. August Wherley, 4813 Oneota St., Duluth 7, Minn.

WANTED—Any condition used Sept. movie cameras, for test equipment, parts, tubes. G. W. Deuchler, 1510 Monroe St., Omaha, Nebraska.

WANTED—Precision 920P tube and set tester or Supreme 504A tube and set tester, Hickok 188X signal generator or Hickok 510X tube set tester. Will pay cash or trade new Rider's Manuals, 7, 8, 9, 10, 11, 12 and cash. Leon S. Schall, 160 Abbott St., Plains, Pa.

FOR SALE—625 radio tubes, 10 for \$5.90 postpaid. Adapters to change 625 to use as 6X5 at 75c each. T. Henshaw, 3313 Delavan, Kansas City 2, Kansas

FOR SALE—Hickok mod. 210S zero current voltmeter 0-2500 v. 0-50 meg., measures capacity, decibels, amps. and mls. Also mod. 153 RCA test osc. and mod. 156-B RCA tube checker, all used less than a month. Maj. L. M. Morehead, 3650 39th St., N. W., Washington, D. C.

WILL TRADE—Kelsey 5x8 printing press with all equipment, excellent condition, for Halicrafters S-20R or similar communications receiver in good shape. Will pay balance cash if necessary. Harry Kellerman, 1127 Pittston Ave., Scranton, Pennsylvania.

FOR SALE—First four experimental kits of 1943 NRI course with instruction booklets. Best offer takes. Ben L. Johnson, 612 8th Str. West, Vinton, Iowa.

WANTED — Riders 7 to 12, Jr. Voltomyst, Solar condenser checker, any 1.4 V tubes, 12 V tubes. State condition of instruments and manuals and price. Seaside Radio Service, Box 886, Seaside, Ore.

WANTED — Solar or C-D Capacitor Analyzer, also modern or late model combination tester and tube checker. State price and condition. J. R. Kinney, 2901 You St., Sacramento 17, Calif.

WANTED — One 84 tube volt ammeter tester for auto generator; exhaust gas analyzer; magneto and generator test bench. Cash for right articles. Pennington's Garage, Wauneta, Neb.

SALE OR SWAP — Record players, amplifiers, Weston tube tester, and volt ohm meter. Want various tubes. C. Morgan, 2209 Edison Ave., Jacksonville 4, Fla.

Keep 'em Listening
with
CORNELL-DUBILIER
Capacitors



*"I Compliment Your
Condensers"*

—writes MR. M. MARTIN
436 Beach 69th St.
Arverne, N. Y. C.

"I have found," continues Mr. Martin,
"that no other condenser can take the
beatings and work-outs that C-D's do.
You can count me as a steady customer."

Mr. Martin, like every radio repair man
who has used them, knows that Cornell-
Dubilier capacitors can "take it." Try
them, and you, too, will want to write
our next advertisement.

SEND FOR CATALOG



MICA • PAPER • DYKANOL • WET AND DRY ELECTROLYTIC CAPACITORS

Cornell Dubilier

ELECTRIC CORPORATION

1049 HAMILTON BLVD. • SO. PLAINFIELD, N. J.

MORE IN USE TODAY THAN ANY OTHER MAKE