



Vol. 14

AUGUST, 1949

No. 8

CORNELL-DUBILIER ELECTRIC CORP.
Hamilton Boulevard, South Plainfield, N. J.

POSTMASTER: If undeliverable for any reason,
notify stating reason, on Form 3547 postage for
which is guaranteed.


Sec. 562, P.L.&R.
U. S. POSTAGE
PAID
So. Plainfield, N. J.
Permit No. 1

MR BERTRAM B HOFFMANN
120 COHASSETT ST
PITTSBURGH 11 PA

HERE'S WHY



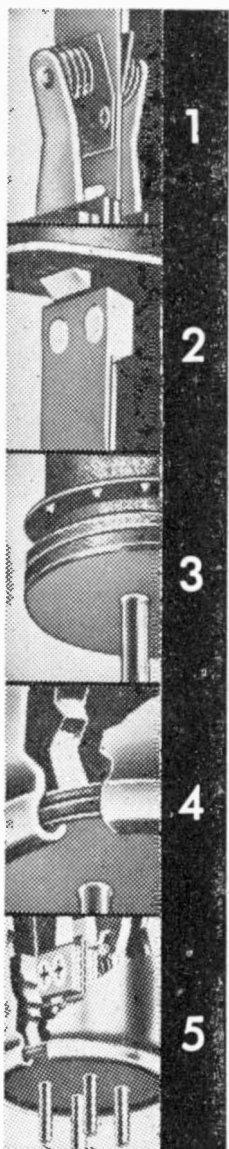VIBRATORS ARE QUIET, RELIABLE
AND LONGER LASTING!



1

C-D designed electronic micrometric equipment removes guesswork in contact point setting and assures consistent high quality.

2

Exclusive C-D pole piece design and armature weight results in a perfectly-balanced unit with greater efficiency.

3

Exclusive C-D base mounting results in a full floating unit. That's why C-D vibrators last longer.

4

Unit completely enclosed in new floating sock — an exclusive with C-D vibrators. Eliminates usual difficulties found in other vibrators.

5

New stack design will take peak voltages of even 4,200 volts with no damage to vibrator.

For the best in Vibrators insist on C-D's.
Now at your local C-D distributor.
Or write for full details to Cornell-Dubilier Electric Corp., Dept. HO9,
South Plainfield, N. J. Other plants
in New Bedford, Worcester, and
Brookline, Mass.; Providence, R. I.;
Indianapolis, Ind.; and Cleveland, Ohio.

A GREAT NAME IN CAPACITORS

A GREAT NAME IN VIBRATORS.



For your nearest C-D Distributor, consult your local Classified Telephone Directory

THE HOW AND WHY OF VIBRATORS

History and Development

PART II

In the preceding issue the basic theory upon which the satisfactory operation of a vibrator depends was developed and illustrated. It was shown that in order to have a satisfactory substitute for a set of "B" batteries, a correctly designed combination of certain components was required. This combination consisted of a low-voltage DC source, such as a storage battery, an inverter, a transformer, a rectifier, and a filter. The inverter was the only unusual component in this group, and was required because the transformer could not function on the DC from the battery. Thus, a device must be inserted between the battery and the transformer to change the character of the DC so that it would appear to the transformer to be AC. The vibrator is to be the inverter in the combination of components listed above.

Our previous discussion also developed the necessary interdependence of the vibrator, transformer, and the "buffer" capacitor, (where the vibrator had progressed as far as the pulsating key in Figure 7), in the correct electrical operation of the power unit. We were at the point where we were ready to convert the manual key into an automatically-actuated vibrating switch, or vibrator, and discuss its performance in the circuit.

Now refer to Figure 8. The circuit shown here is somewhat different from that in Figure 7. The key of Figure 7 has been replaced by a switch controlled by the magnetic coil in series with the battery and transformer primary. When the battery circuit is closed, the magnetizing current for the transformer flows through the

switch and magnetic coil, energizing the latter and pulling the switch arm toward it. This opens the transformer circuit and releases the magnetic pull of the switch coil, allowing the switch to close, again starting the cycle of events just described. So long as the battery has energy available the switch will continue to operate at a regular rate, this depending upon the rate of

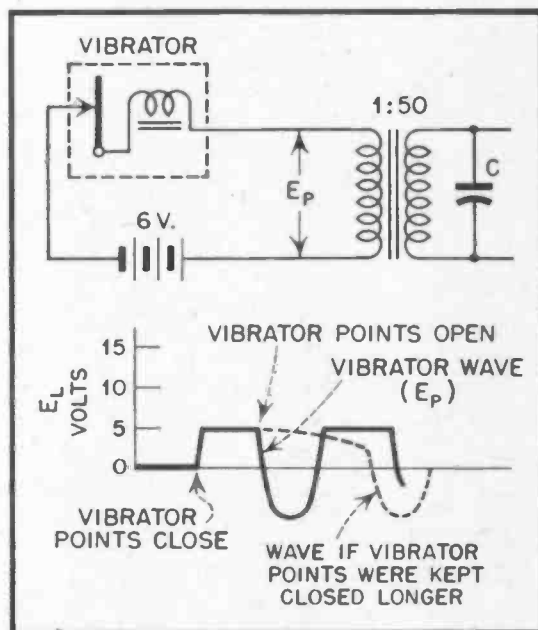


Fig. 8.

build-up of current in the circuit and upon the mechanical characteristics of the switch. Thus the VIBRATOR became a reality, although the similarity to the bell-buzzer of Figure 3 is readily noted.

Another change shown in the circuit of Figure 8 is the moving of the Capacitor "C" from its former location across the primary terminals to a new

location across the secondary terminals of the transformer. Because the primary and secondary coils are usually closely coupled, the effect of the capacitance across the secondary will be almost perfectly reflected into the primary. However, since the tuning effect of the secondary coil as compared to the primary coil is dependent upon the square of the number of turns for each coil, (square of the turn ratio), the value of capacitance needed for proper equivalent tuning usually is much smaller for connection in the secondary than for in the primary circuit. For instance, if the turn-ratio is 50, the square of this number is 2500, and the size of capacitor needed for the secondary will be 1/2500 of that needed in the primary.

The waveform resulting from the circuit shown in Figure 8 is illustrated in the accompanying graph. The vibrator characteristics of frequency and time efficiency can be so matched to the transformer characteristics and the capacitance of "C" that the contacts open before the transformer core begins to saturate and close with the tuned-circuit oscillation voltage practically equal to the battery voltage. This circuit characteristic protects the vibrator contacts from excessive sparking and electrical wear. If we connect a rectifier tube and filter to the secondary of the transformer, as shown in the circuit of Figure 9, we can supply

direct current to a load connected to the terminals marked "B+" and "B-". If the rectifier tube is properly polarized for the primary battery connections, it will conduct current during the portion of the cycle when the vibrator contacts are closed, (the square-topped pulse), and a fairly good efficiency will be realized. If the battery polarity is reversed, however, the polarity of the secondary voltage will be reversed and the rectifier tube will now conduct only during the portion of the cycle when the vibrator contacts are open, (the rounded pulse), and the only energy available will be that stored in the core of the transformer and in the buffer condenser. This results in low output capabilities and poor efficiencies.

Several manufacturers produced "B" eliminators of this type, which met with rather wide acceptance and gave reasonably good life and performance. One radio manufacturer produced a receiver in which he built in the power unit and thus made the forerunner of the present type of set. There were several inherent drawbacks to such a design of power-unit, however, and it is desirable to outline these in order to see the reasons for future developments. The first, and possibly most obvious, difficulty lay in the method of driving the vibrator. Since the

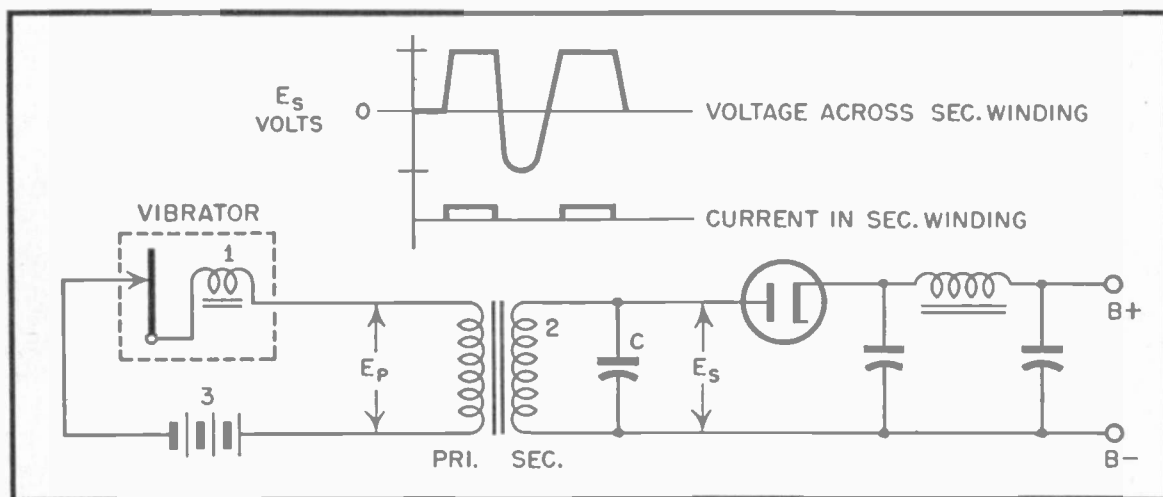


Fig. 9.

driving-coil was in series with the primary circuit, all of the magnetizing and load current passed through the coil and thus produced the magnetic pull affecting the movement of the reed. Therefore, if the load current changed, the magnetic pull changed and directly affected the operating characteristics of the vibrator. Under a no-load condition, the pull would be slight and the reed would merely flutter. Under an overload condition, the pull would be great and the reed amplitude would be excessive. Under both conditions the tuning of the circuit would be bad and severe sparking would result. With excessive amplitude, reed breakage would probably occur. Thus, for a given design of power-unit, only a narrow range of loads could be handled. This was partially met by the introduction of a series of units with different values of output loads, each having a vibrator with a coil designed for that load. These varied from a low of about 135 volts at 15 ma to a high of 180 volts at 40 ma. The no-load condition was sometimes taken care of by the use of a "phantom load", which was a resistor connected across the output until the set load became large enough to operate a relay having a coil in series with the output circuit.

The fact that the system operated "half-wave" was another source of difficulty. The transformer core was subjected to pulses of DC load current, with the result that inefficient transformer action occurred, the core having a large residual magnetization in one direction. This fact limited the amount of energy that could be transferred to the load circuit. In addition, it necessitated the use of an exceptionally large transformer in order to operate at low flux-densities. The other problem has already been discussed in a preceding paragraph, where the relation between the polarity of the battery and that of the rectifier tube affects the unit's efficiency. A method of providing for this difficulty had to be arranged for, such as switching the input leads, switching of transformer terminals, etc.

After considerable thought, a simple change in the design of the vibrator enabled the engineers to correct the difficulty encountered in driving the vibrator. If we did not want the unit to be sensitive to load current, we should make its driving power dependent upon the battery voltage instead, which remains substantially constant. By supplying a high-resistance voltage coil instead of the low-resistance current coil, and connecting this across the vibrator contacts instead of in series with them, we can make the unit drive independently of the load current. In Figure 10 we see this arrangement, where the coil is ener-

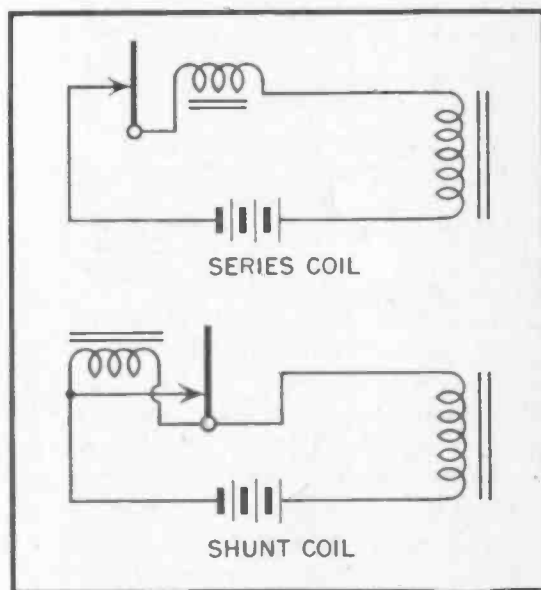


Fig. 10.

gized when the contacts are open, and is shorted out when the contacts close. One other major difference is now involved. At rest, the vibrator contacts must be open in order to start the vibrator with the shunt coil, while they must be closed in order to start the vibrator with the series coil.

To correct the inherent difficulties of operating the circuit half-wave, however, meant that some means would have to be developed to change to full-wave operation if all of the desirable features were to be secured. If we wind the transformer coils in

duplicate and place them on the same iron core, we can cancel the residual magnetism caused by the pulsating DC if we pass the current through one set of coils in one direction on one half-cycle and through the other set of coils in the opposite direction on the other half-cycle. Thus the energy that can be transferred is greatly increased, the size of the transformer can be reduced by operating at much higher flux-densities, and a full-wave rectifier can be used which will operate equally well regardless of the battery polarity. To operate such a transformer, however, required two vibrators of the type we have just considered, mechanically synchronized 180 degrees out of phase. One set of contacts had to be closed while the other set was open. Naturally, the next step was to combine the two vibrators into one, having sets of contacts on both sides of the moving reed which engaged on opposite half-cycles of operation. This arrangement is illustrated in Figure 11. As there is an appreciable percentage of the total time of each half-cycle required to switch the contacts from one side to the other in the circuit, the on-contact time for each cycle is always less than 100% of the total time. The actual percentage of contacting time is referred to as the time-efficiency, or in some instances as the time-constant, of the vibrator.

Because the time-efficiency is less than 100%, there will be gaps in the horizontal voltage trace between successive half-cycles. However, we have the timing, or buffer capacitor con-

nected to the transformer, which can be so selected that the rate of oscillation on the break of each half-cycle will permit filling in this gap with a voltage reversal. Thus the trace shown in the graph of Figure 11 has the voltage wave with slanting lines connecting the horizontal portions. When the induced counter-voltage in the transformer primary is as indicated by the voltage graph, the current pulses passed by the rectifier tube will be as shown. Naturally, after going through the tube the pulses will be all of the same polarity. Thus we have arrived at the basic vibrator circuit still used today in the large majority of auto radio receivers, as well as many other applications. Without the rectifier, and with a few refinements, this is the basic arrangement for the power converters made by Cornell-Dubilier for providing AC power from a DC source. The vibrator is commonly called the "INTERRUPTER TYPE", the full-wave feature now being taken for granted. When correctly designed, and when used with properly matched components, this vibrator structure has worked very satisfactorily and provides excellent life characteristics.

Early in the history of vibrator power supplies for auto sets there was a desire to reduce the overall size and weight as well as cost. Because the early rectifier tubes were gas-filled half-wave types, and were large and costly, this appeared to be one logical place to start in achieving the reductions. Additional insulated sets of contacts were added to the

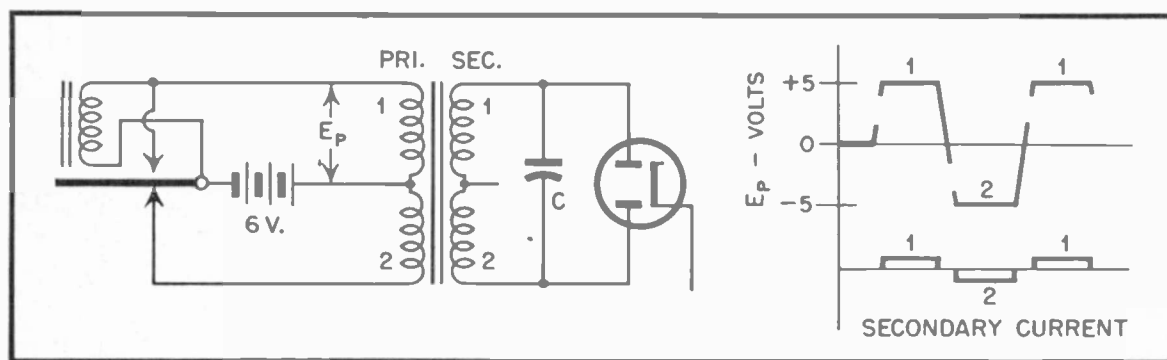


Fig. 11.

vibrator structure which were operated in synchronism with the already present interrupter contacts. This was first done on the half-wave structure, and resulted in a synchronized half-wave rectifier of a mechanical type re-

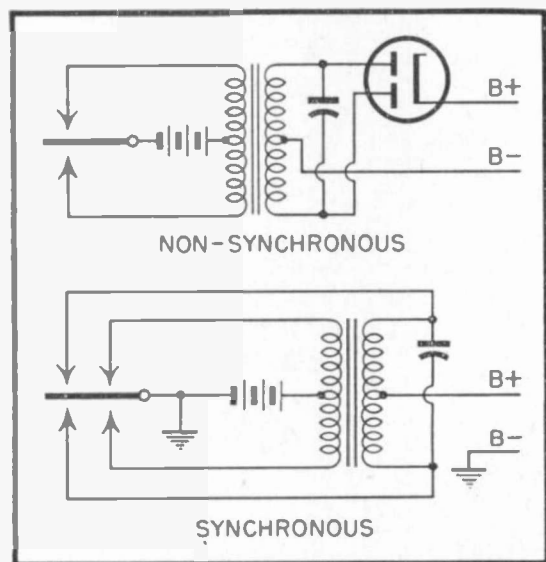


Fig. 12.

placing the tube. Decided disadvantages resulted from this arrangement in addition to those already described for the half-wave interrupter. However, the feasibility of the synchronous rectifier was demonstrated, and the same principle was then applied to the full-wave unit after its introduction. This arrangement is shown in Figure 12, where the Non-Synchronous (or Interrupter) and the Synchronous (Self-Rectifying) types are compared.

This structure permits the elimination of the tube rectifier for a cost and space reduction, gives slightly higher efficiency because of the elimination of tube losses (both plate voltage drop and filament current must be considered), and in general gives a longer vibrator life. The use of this type of self-rectifying unit, however, introduces several disadvantages. First, the output DC circuit must be electrically connected to the input DC circuit, as both use the

common vibrating reed as a switch. Usually B— is connected to the grounded terminal of the battery, and this may be positive or negative, depending upon the car manufacturer's choice. This is of little moment at the present, since cathode-bias is common practice in receivers and indirectly-heated cathode-type tubes are used. However, the fact that the rectification is done mechanically results in a reversal of the output polarity when the battery ground is reversed. Since receivers won't operate with the plates negative, and other difficulties such as polarized capacitors arise, it is obvious that this condition must be corrected where receivers are manufactured for use in any make of car. Of course, where custom-built original equipment is considered, this reversed condition need never occur.

Figure 13 illustrates the effect of the reversal of battery polarity on a power unit using the Non-Synchronous type and on another using the Synchronous type of vibrator. On the left of the illustration we see that the rectifier tube acts as an automatic valve, so that, regardless of the battery polarity (and therefore the transformer secondary polarity), the output circuit is always polarized correctly. On the right we have substituted a mechanical selector switch for the tube for the purpose of rectification. In the upper circuit we see that, regardless of the position of the vibrator reed, the output circuit is always positive at the secondary center-tap because when the current through the primary is reversed, the connection to the secondary winding is reversed also. In the lower circuit, the connections to the vibrator and transformer have remained the same, but the battery polarity has been reversed. As a result, the polarity of the output circuit is now the opposite of that formerly prevailing, with the center-tap connection being maintained negative.

(Continued on page 10)

NOW! from C-D...



POWERCON

*a complete line of
CONVERTERS
for all purposes*



MODEL 110R10:

MODEL 32 RU15

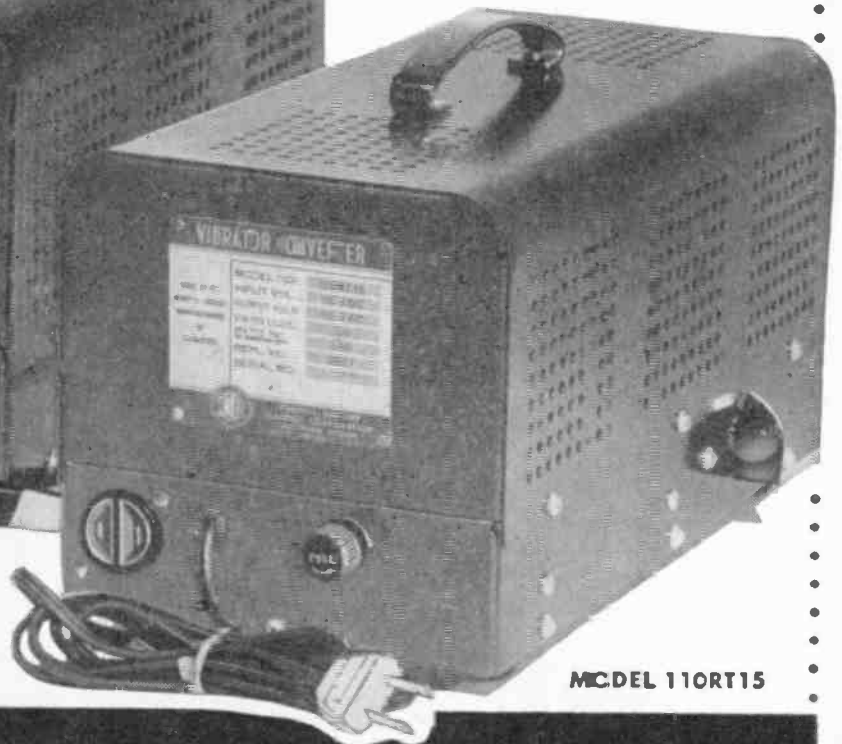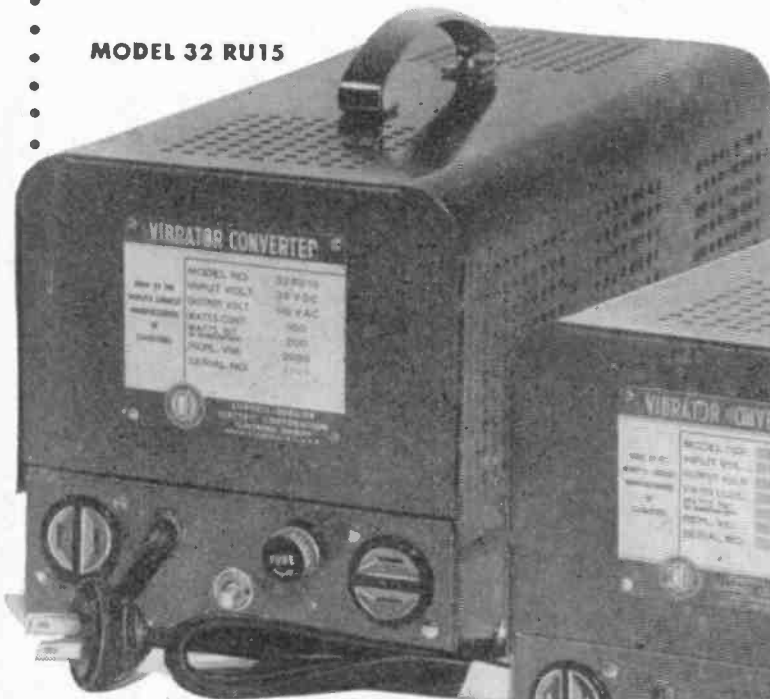

MODEL 110RT15

Think of the new sales opportunities open to you now that you have the dependable name of C-D in back of a complete line of converters. More TV installations! More work on farm power supplies! Marine work! And always you work with confidence in the quality, dependability and trouble-free performance of these converters, because they're typical C-D products.

SEND FOR *FREE CATALOG* FOR DETAILS ON THESE *C-D POWERCON CONVERTERS*

| | |
|--|--|
| • MODEL 6R5: | For 50-watt radio equipment. 110-volt 60-cycle AC output from 6-volt battery. |
| • MODEL 12R8: | Operates radio equipment up to 80-watts. For 110-volt 60-cycle AC output from 12-volt battery. |
| • MODEL 6R10: | For mobile, portable and stationary operation up to 100 watts. 110-volt 60-cycle AC output from 6-volt battery. |
| • MODEL 12RU15: | For marine, truck, trailer, bus, aircraft, etc. Rated at 150 watts. For 110-volt 60-cycle AC output from 12-volt battery. |
| • MODEL 32R8: | For farm and marine power—up to 80 watts. 110-volt 60-cycle AC output from 32-volt DC power source. |
| • MODEL 110R10: | Adjustable to 40, 70 and 100 watt loads. For 110-volt 60-cycle AC output from 110-volt DC power supply. |
| • MODEL 32 RU15: | For quick, easy conversion of farm and marine power. 110-volt 60-cycle AC output from 32-volt DC power source. |
| • MODEL 110RT15: | For television receivers and other radio applications. 110-volt 60-cycle AC adjustable output in 110-volt DC areas |
| • MODEL 110RT25: | For television and radio uses. Rated at 250 watts. 110-volt 60-cycle AC adjustable output in 110-volt DC areas |
| • MODEL 110RT35: | For television, radio, small power tools, food mixers. 350 watt output. For 110-volt 60-cycle AC output in 110-volt DC areas. |
| • MODEL 110PA5: • 110PB5: | For automatic and manual record players. Supplies 110-volt 60-cycle AC power from 110-volt DC source. |
| • MODEL 110BA6: | Multi-use AC-to-DC power supply for auto-radio demonstrating, servicing and battery charging. To supply 6 volts DC from 110-volt 60-cycle AC source. |
| • MODEL 110BA12: | For servicing, testing, demonstrating auto, truck and small boat radio equipment and appliances. Supplies 6 or 12 volts DC from 110-volt 60-cycle AC source. |

C-D POWERCON Converters are Honestly Rated for Dependable Trouble-Free Long Life

If the Cornell-Dubilier line of POWERCON converters is not available at your local jobber send your order to us here in South Plainfield, N. J., and we will fill it through the nearest Cornell-Dubilier jobber carrying a converter stock.



CORNELL-DUBILIER
CONSISTENTLY DEPENDABLE

★ CAPACITORS
★ VIBRATORS
★ ANTENNAS
★ CONVERTERS

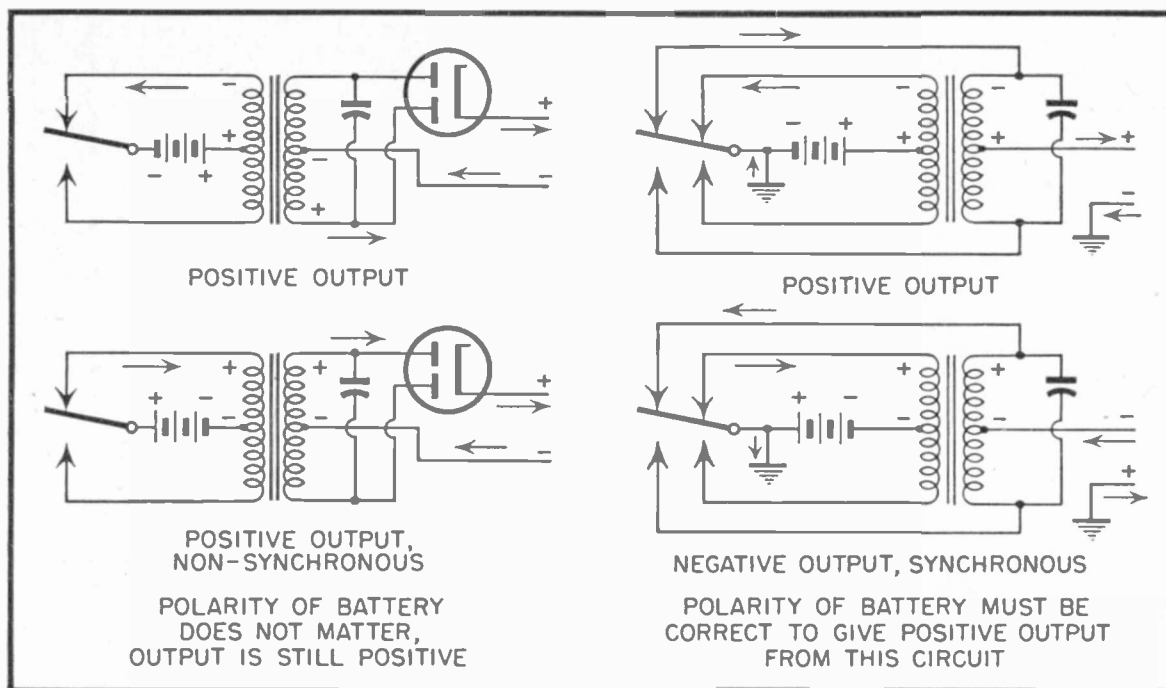


Fig. 13.

Thus it would be desirable to incorporate in the receiver some easy method of interchanging the connections of either the primary or the secondary of the transformer to the vibrator when the receiver is to be installed in cars with opposite battery polarities. Early models incorporated a terminal board to which transformer leads were connected. Later the vibrator basing shown at the left in Figure 14 was developed in order to use the vibrator itself as a reversing switch. This is used with a symetrically arranged socket, as shown at the right, which will receive the vibrator in either of

two positions, 180 degrees apart. By connecting the transformer to the socket as shown, provision is made to reverse the secondary or rectifier side-reeds when the vibrator is reversed in its position, but the cross-connection provides no reversal of the primary, (or interrupter), side-reeds; therefore, output reversal can be corrected by vibrator positioning. This type of vibrator has been highly successful, and permits the full realization of the real advantages of the self-rectifying vibrator without its most important disadvantage.

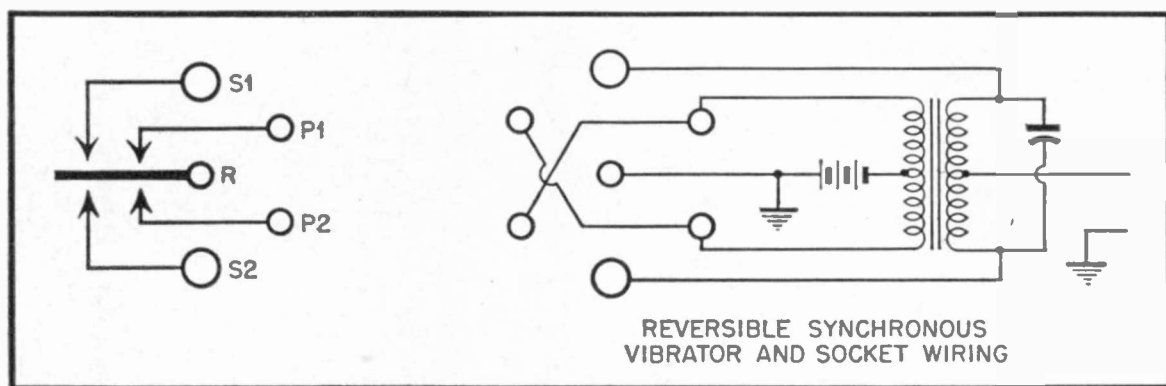


Fig. 14.



A Free Market-Place for Buyers, Sellers, and Swappers.

These advertisements are listed FREE of charge to C-D readers so if there is anything you would like to buy or sell, if you wish to obtain a position or if you have a position to offer to C-D readers, just send in your ad.

These columns are open only to those who have a legitimate WANTED, SELL, or SWAP proposition to offer. The Cornell-Dubilier Electric Corp. reserves the right to edit advertisements submitted, and to refuse to run any which may be considered unsuitable. We shall endeavor to restrict the ads to legitimate offers but cannot assume any responsibility for the transaction involved.

Please limit your ad to a maximum of 40 words, including name and address. Advertisements will be run as promptly as space limitations permit.

WANTED—2 speed recording unit or system, G.I. R90 or equiv. Also want Humphrey's spinning reel. Will trade new Heddon deluxe tubular casting rod, new Ashaway spinning reel and other fishing tackle. What have you? Frank E. Popma, Orange City, Iowa.

SELL OR SWAP—Gonset 10 meter converter with noise clipper; Jackson audio oscillator, model 652; Sprague Tel-omike condenser analyzer, model 16. Harper K. Richards, East St., Argyle, New York.

WANTED—Prewar 5" television chassis, such as RCA TT5, Garod 100, or any prewar TV chassis converted or not. With or without tubes or cabinet. Send details and price. Robert Flory, 29 Harold Ave., Princeton, N. J.

FOR SALE—5" oscilloscope, sensitivity 2" per rms volt, \$60; A10 bubble sextant, \$30; 410 Stevens shotgun, \$15. Edward Matthews, 171-35 Courtney Ave., Flushing, New York.

FOR SALE—Antenna, AN/128-A, part of radar unit RC-48-C, \$30 fob Chicago. Also several 7C5 at 2 for a \$1 and one RCP VOM model 447, excellent condition, \$13. Edward Tanrath, 3151 W. Monroe St., Chicago 12, Ill.

FOR SALE—Model 10 semi-professional Wilcox-Gay recorder, 40 watt capacity, play or cuts 12" records. Also one 16-mm Keystone movie camera. Both in excellent condition. Or will trade for Wire recorder or printing press. D. W. Harper, 117 W. Main St., Albertville, Alabama.

SWAP—New 4X Hensoldt Wetzler scope with leather lens covers, mount and base plate for attachment to receiver, (valued at \$85); new Luxor spinning fishing reel; also one pair Peals English boots, 9½D, with trees, in good condition; all for Riders' Manuals. G. T. Mackenzie, University of Kentucky, Lexington, Kentucky.

FOR SALE—Approved sig. gen., model A 200, \$30. Will ship COD. Reed's Radio Service, P.O. Box 264, Lansford, North Dakota.

TRADE—Complete set of Coyne's Applied Practical Electricity, seven vols., never used. Want a complete course in radio. Stanley March, 1019 N. Liberty St., New Castle, Pa.

FOR SALE—Thriving radio and television business in Ionia, Michigan. Located on main highway M21 east of Ionia. Stage set for television sales and service. Floyd E. Colley, North St., Ionia, Mich.

WANTED—Collins 310A-1 or 310B-1 exciter; Philco CR-10 auto radio; late model television console; RMEDB20, VHF152; 4-125A, 4-250A, 4-65A, 100TH's, 35T, 2A3, Tubes. Pasquale, 9421 Thornhill Road, Silver Spring, Md.

SWAP—Auto radio; "A" eliminator; 50 watt CW xmitter; bat. charger; PA system (phono on top); 100 QST and 100 Radio Craft magazines; 10" TV lenses. Want 50lbs No. 5 SCC enam. wire, port. typewriter, welder, printing press, movie camera and projector, or what have you? Stanley, 2748 Meade St., Detroit 12, Mich.

TRADE—We will develop ideas and inventions and make patent searches in exchange for electrical test instruments. Inventions Unlimited, 3509 Hyde Park Blvd., Los Angeles 43, Calif.

WANTED—Riders' Manuals, vols. 1, 3, and 9. Write giving condition and price. Also have Schick Colonel electric razor, like new, for sale or trade. What have you? E. Yeager, 5302 West 57th St., Mission, Kansas.

TRADE—Ham radio items for photographic items. Have parts, transformers, complete sets, etc. Want any 35mm camera, 4x5 press, dark room items, or movie. W. T. Golson, 502 Lakeland Drive, Baton Rouge, La.

TRADE—Hallcraft Ultra Sky rider, bands 11.-5.5mc, 20.-11mc, 38.-20mc, 79.-38mc, excellent condition. Want SX28 and will pay some cash. A. H. Dreesen, Mansfield Centre, Conn.

FOR SALE—Transmitting tubes, slightly used: one 813, \$8; two RK-20's, \$5 ea.; two 807's, \$1 ea. Also 25 receiving type tubes, all for \$5 and Cooke's Radio Slide Rule, \$5. Justin M. Walker, 1000 College, Canton, Mo.

URGENTLY NEED—3" DC millimeters all ranges. Prefer Western Electric types. Ed Howell, Box 441, Gastonia, N. C.

SWAP—Radio parts, communication rec. for late model magnetic tape recorder in operating condition. Also can use television receiver units. Radio Communication Service, 4475 Myrtle St., San Diego 5, California.

FOR SALE—All standard makes of fine used radios, power packs, transformers. Send stamp for bulletin. Goldstone Radio, 1279 Sheridan Ave., Bronx 56, N. Y.

SELL OR TRADE—Radio and photographic equip., 35mm silent projector. Want Bubble or Marine sextant, binoculars or telescope. William Hansen, 165 Silverbrook, Niles, Mich.

WANTED—Philco oscillator coil, part No. 06620, for model 89 or 19 radio, or model 89 chassis. Joseph A. Spalla, Plaza, N. Dak.

FOR SALE—6 tube Motorola auto set, fits any 1940 to 1948 Dodge, Ply., Chrys., or DeSoto. Perfect condition and complete, \$20. C. Wm. Haberstroh, 1521 Larrabee St., Chicago 10, Ill.

WANTED—Altec Lansing speaker in good condition. H. A. Rollins, 113 Central Park Drive, Brownsville, Texas.

FOR SALE—Dumont 164 3" scope; RCA Chanalyst. Both in good condition. Make offer. H. G. Lutz, Bolton Rd., New Hartford, N. Y.

SWAP—Fourteen books on radio and machine work, nearly new condition. Want radio tubes. Charles C. Butler, 16108, S. Main, Gardena, Calif.

WANTED—Voltohm meter with more than 2000 ohm/volt meter and both ac and dc ranges. P. C. Yu, 4725 11th Ave., N. E., Seattle 5, Wash.

FOR SALE OR TRADE—Hammarlund HQ-120X in very good condition; Philco recording arm unit for Philco combinations. Will trade for photographic equip. R. A. West, 111 Waddell Pl., Oak Ridge, Tenn.

WANTED—Precision EV-10 VTVM and 912 tube tester. Also used communication type receiver, condition not important. Will exchange lists or pay cash. Glenn Watt, Chanute, Kansas.

WANTED—4" or 5" lens, f1.9 or better. Will trade any surplus radio, phono, or television part I have for what have you? Louis DuRaun, 1128 Wagner Ave., Philadelphia 41, Pa.

FOR SALE OR TRADE—Approved electronic model A-200 sig. gen., \$25; NRI service manual, \$10; 522 2 meter transmitter, \$10. Want FM tuner, television set or what have you? Mathew J. Duniphin, Box 1091, Wewoka, Okla.

SELL OR TRADE—Motorola FM receiver; Schick and Remington electric razor; Kodak f1.9 16mm magazine movie camera; Vokar slide projector. Want test Equip. D. Buck, 32 Ardmore Ter., Collingswood, N. J.

SELL—Kodak Duo-620II with everyready case, chrome finish, f3.5 lens, compur rapid shutter 1 sec. to 1/500 sec., excellent condition. Worth \$65, best offer. Louis Fialkoff, 143-48 41 Ave., Flushing, L. I., N. Y.

FOR SALE—Crystaliner, fine condition, \$10. Howard Clewett, Rt. 1, Box 261A, Ripon, Calif.

SALE—16mm Pathe sound projector, with push-pull 6F6's and 10" dynamic speaker, all in carrying case, used but in good condition. Best offer takes it. Henry Lulli, 2352 - 27 St., Long Island City 5, N. Y.

FOR SALE—Over 1,000 radio tubes, condensers, resistors, and Alnico 4" and 5" speakers. Very reasonable, send for list price. Knight Radio, 9418 Ave. A, Brooklyn, N. Y.

WANTED—0-25 volt Million tube tester chart. E. Reeser, Benedict, Kansas.

FOR SALE—Model 458 ac-dc ohm-volt-milliammeter (Chicago Industrial Co. manufacturer). Best cash offer takes it. Higgins Radio Service, Mineral, Ark.

FOR SALE—Brand new Philco model 7050 tube tester. First \$34.95 money order takes it. Williamson Radio Service, Cooper, Texas.

WANTED—Alignment and service data on army surplus FM receiver BC-683-A or B. Will pay reasonable price. F. E. Francisco, Canal Winchester, Ohio.

FOR SALE—High voltage power pack, 110V ac in and 1000 - 750V dc at 225ma out., choke input filter, ruggedly built, \$16. Simon Dresner, 322 W. 72 St., N. Y. 23, N. Y.

FOR SALE OR TRADE—One 5CP1 cathode ray tube and socket and one 2AP1 cathode ray tube and socket. New Radio Clinic, 603 SW Road, Shenandoah, Iowa.

FOR SALE—Model 920 Precision tube tester, in perfect condition, \$60. Sgt. E. DePrisco, Apt D92, Baldwin Manor, Aberdeen Md.

WANTED—One 2AP1A cathode ray tube as used in Philco 022 oscilloscope. State price. L. R. Van Sickle, 2915 Allen, St. Louis 4, Mo.

FOR SALE—S-38 Hallicrafters receiver, excellent condition, complete with instructions and service bulletin. Need cash badly, Best offer takes it. John R. Grimm, 52 Conway St., Carlisle, Pa.

FOR SALE—Series 920, 1000 ohm per volt, combination VOM by Precision: E-200 Precision sig. gen. Both like new, \$75. Charles W. Kern, Sherman, Ill.

FOR SALE—Brand new Hallicrafters 7" television set; 10" magnetic speaker; used Packard electric razor; back issues of QST and Radio Craft magazines. Want folding camera, binoculars and a small electric refrigerator. Charles Holstein, 246 E. 148, Bronx 51, N. Y.

SELL OR SWAP—Sunkraft cold quartz mercury vapor lamp, used as a tanning or sterilamp, built-in timer, wood carrying case, cost \$69.50 new, hardly used. Want camera and test equip. Emanuel Batler, 46 W. 76 St., N. Y. 23, N. Y.

FOR SALE—Complete radio equip. to start your own radio shop, including test equip., parts, diagrams, and work bench. Will sell all or part for one-third less than cost. Alfred A. Johnson, 5604 N. Western Ave., Chicago 45, Ill.

FOR SALE—450mc oscillators. Basic unit of the BC-645, uses a 955 tube. Less tube, \$1 each. Wagner Radio Service, 5904 S. Princeton, Chicago, Ill.

TRADE—\$30 foreign stamp collection for used ham gear. Includes the Modern Stamp Album. Herb Ridderbusch, Box 902, Rainier, Oregon.

FOR SALE—New No. 88 NRI sig. gen., \$38; New Crossman single shot 22 air pistol, \$14; Brook dc to ac 50 watt converter 110V, \$7; Everybody's Radio Manual, 75 cents. Ship postpaid. L. John Moy, Box 169, Canal St. Sta., New York 13, N. Y.

FOR SALE—SW3 receiver, has extra stage of audio built in, fine condition, with 80 and 40 meter coils, \$15, or will swap for 10 meter converter. Steward Ringler, 121 S. 11th St., Reading, Pa.

FOR SALE—Brand new Supreme 543S 5000 ohm per volt multimeter, \$12; new GE unimeter, \$29.95. Wagner Radio, 5904 S. Princeton, Chicago, Illinois.

TRADE—Chemicals, chemical apparatus, chemistry books, list on request. Want radio books or apparatus. Gerald Specter, 158 Chestnut St., Lakewood, N. J.

FOR SALE—Complete radio repair shop, tools, instruments, parts, manuals, Riders' 1 to 13, Sam's 1 to 3. Will trade for HO gauge electric train equip. Write for list. Stan's Radio Repair, E-6051 Myrtle Court, Flint 7, Mich.

FOR SALE—Rider Chanalyst, practically new, \$85. K. D. Boyd, 4300 W. Central Albuquerque, N. Mex.

REWARD—Large reward for locating the following stolen meters: One Voltohmyst, RCA model 195-A, serial No. 10593 and two Simpson model 260, serial No. 19195. A. L. McNealus, 90-15 138th Place, Jamaica 2, N. Y.

SWAP—Sound equip. (microphones, amplifiers, speakers, etc.) for pair of good binoculars, 6 x 30 or 7 x 50 either German or American. Longer Radio and Sound, 43 N. Hazel St., Danville, Ill.

FOR SALE—4' x 5' electric neon sign for radio service shops, practically new, will sell very cheap. Write for details. Reinisch Radio Service, New Rockford, N. Dak.

WANTED—3" or 5" television kit less sound channel, complete. Will trade a BC-654 radio and transmitter with high and low voltage supplies, mike and key and speaker or will trade for surplus oscilloscope BC-412. John Arnold, P.O. Box 84, Bluffs, Ill.

FOR SALE—Vomax 900, \$45; Precision model 612-C tube checker, \$60. Both testers as new. J. W. Landon, Box 6425, Pittsburgh, Pa.

FOR SALE—Model 33 NRI professional sig. tracer, nearly new, perfect condition, original cost \$52, will take \$40. Paul Cutting, 21 Ranger Rd., East Greenwich, R. I.

FOR SALE OR TRADE—2000 I.R.C. BTA 1 watt resistors, brand new; Supreme No. 85 tube tester, with adapters for octal tubes; dual charging rate bat. charger, 6V at 2A, 4V at 1A. Make offer. Want typewriter. Stubby, 140 So. 4th St., Reading, Pa.

SELL OR TRADE—Airplane engines—Ohlsson 23's, \$7; Merlin super B's, \$6; G.H.Q.'s, \$9; coils, condensers, and spark plugs for same. Want multitester, small oscilloscope or what have you? Allan Morrell, 78 Stephen Place, Valley Stream, N. Y.

FOR SALE—Latest radio books in good condition, very reasonably priced. Send for list. Leon Medler, 2109 Daly Ave., Bronx 60, N. Y.

POSITION WANTED—Can repair any make radio. Recent graduate of Philco Television Training Course. Want job in vicinity, full or part time. M. Maultasch, 535 Grand St., Brooklyn 11, N. Y.

FOR SALE—First quality radio tubes. Nos. 3S4, 12SQ7G/GT, 50L6G/GT, 12SG7GT/G and 70L7, 69 cents each postpaid. No order to small. Jones Radio Co., Box 93, Douglassville Pa.

FOR SALE—G.E. television set, model 171. Will sell cheap. H. Latko, 1922, Dickens, Chicago, Ill.

SALE OR TRADE—Hickok 4955-S, 4" face, V.O.Ma. meter, 0-10 meg. 4 ranges, 0-500 ma. 3 ranges, 0-1000 ac or dc volts, 5 ranges, separate output jack. \$25 plus postage, or what? C. Elgasser, Jr., 1920 Fern St., San Diego, Calif.

SWAP—Equal amount of tubes for 0-150 micro-ammeter. State price and I will send equal cost of tubes wanted. P. Shavel, 941 Grand St., Brooklyn 6, N. Y.

WANTED—25B8 tube, will pay your price, new or used. Also manual for Precision meter, series 40. State price. Paul Quayle, West Main St., Madison, Ohio.

FOR SALE—400' RG-8/U coax cable, 4 cents per ft.; 3 wire telephone, weather-proof, 2 cents per ft.; 25B8GT tubes, while they last, \$4.80 each. Everything new. Oler Radio Service, New Madison, Ohio.

TRADE—63 vols. Popular Science magazine, Oct., 1938 thru Dec., 1945. Also 17 vols. Science and Mechanics, Aug., 1939 to summer edition 1943. All in good condition and clean. A. Paul Rabito, 2835 Paris Ave., New Orleans 19, La.

FOR SALE OR TRADE—Colored sea-shell brooch and earring sets, \$2; preserved seahorses, 50 cents; 100 yrs. old American newspaper, \$1. Missouri land, \$3.75 per acre. Want Riders' Manuals, small oscilloscope. Your trade list for mine. George Calvert, Rt. 2, Winter Haven, Florida.

WANTED—Philco 84 radio in any condition, but coils must be good; also Riders' 5 and 14. For sale, Utah record player on a Zenith display case. Saxton's Radio and Electric Service, Route 1, Pontiac, Illinois.

FOR SALE OR TRADE—Speco sig. tracer; Heath sig. gen. Want Hickok 156 trace-o-meter or what have you? W. F. Daniels, 1123 Central, Harper Kansas.

FOR SALE—Riders' vols. 7 and 3, perfect condition, \$11, plus code for both vols. Also 6-2D-21 Thyatron tubes, best offer. Augustine Mayer, 561 So. Sandusky St., Tiffin, Ohio.

FOR SALE—Radio Physics course by Ghirardi, new, \$4; Mathematics for Electricians and Radiomen by Cooke, new, \$4. Both received as duplicate gifts. Louis G. Ousborne, 915 Wildwood Parkway, Baltimore 29, Maryland.

WANTED—One 25D8 tube. Masline Radio Parts, 192 No. Clinton Ave., Rochester, N. Y.

FOR SALE—3 channel Transvision television set, less cathode ray tube, \$50, or will swap for good sweep gen. C. Witter, 28 Elizabeth Av., Newark 8, N. J.

FOR SALE—Used Detrola record changer; mounted 1,000kc xtal; 838, R14 high resistance phone units. E. W. Barth, 333 Washington, Chelsea, Mich.

FOR SALE—Model 505 Hickok 5" oscillograph, \$179; model 156 Hickok indicating traceometer, \$195; model 909 McMurdo Silver TV sweep sig. gen., \$48.50. Will sell all for \$325. William J. Madigan, 56 Lincoln Ave., Brooklyn 8, N. Y.

FOR SALE—Pontiac super deluxe auto radio, 8 tubes, for 1948 car. Also tubes for sale. Lincoln Estates Radio Co., Rt. 1, Frankfort, Ill.

FOR SALE—Riders' vols. 6, 7, 8, 9, 10, \$62. A-1 condition and we mean it. Carrs Radio Center, 17 Kelley Sq. Worcester 4, Mass.

why they* all flock to
**servicemen, that is*
C-D SKYHAWK
AUTO AERIALS



You use this C-D auto aerial with full confidence. It won't rust — all stainless. It's the most popular model on the market. Completely protected against the elements, fully shielded lead — so durable it will outlast the car you install it on. Fits any cowl or fender contour.

MODEL 8B \$5⁹⁵ each

CORNELL-DUBILIER can now supply you with a full line of AUTO, TV and FM aerials. If your jobber does not stock them, send your order directly to us. We will ship to you through the C-D jobber nearest your shop. Write:
CORNELL-DUBILIER ELECTRIC CORPORATION
 Dept. HO8, South Plainfield, N. J.


 1910 1949
Reg. U. S. Pat. Off.

CORNELL-DUBILIER
 CONSISTENTLY DEPENDABLE
 ★ CAPACITORS
 ★ VIBRATORS
 ★ ANTENNAS
 ★ CONVERTERS

a complete capacitor department

FOR ONLY



WITH THIS
METAL CABINET

FREE

HERE'S WHAT YOU GET:

CAPACITORS IN ASSORTMENT (LIST \$50). YOUR COST \$29.99

Plus 3-DRAWER METAL CABINET **FREE**

| | |
|------------|------------|
| 1 UP-2045 | 10 PTE-651 |
| 1 UP-1145 | 5 PTE-652 |
| 1 UP-2245 | 10 PTE-655 |
| 1 EDL-4215 | 5 PTE-6P1 |
| 1 EDL-5315 | 1 BR-252A |
| 1 EDL-2215 | 5 BR-2015 |
| 5 PTE-6D1 | 5 BR-845 |
| 5 PTE-6D2 | 5 BR-1645 |
| 5 PTE-6D3 | 3 BR-1045 |
| 5 PTE-6D5 | 2 BR-2045 |

YOU BUY THE CAPACITORS ONLY!

- an assortment of your most popular capacitors, list price \$50
- 20 different types of capacitors in the quantities you need them for day-to-day servicing.
- a 3-drawer metal cabinet with separate compartments for each type of capacitor and free space for additional stock,
- cabinet can be hung on wall or kept near work bench without cluttering work area,
- convenient...time-saving.

ORDER FROM YOUR JOBBER NOW!

If your jobber cannot supply you with this C-D capacitor kit, write us: Cornell-Dubilier Electric Corporation, Dept. HO 99, South Plainfield, N. J., and we will ship your order through your nearest C-D distributor. Other plants in New Bedford, Brookline and Worcester, Mass.; Providence, R. I.; Indianapolis, Ind.; and subsidiary, The Radiart Corporation, Cleveland, Ohio.



Printed in U.S.A.