


# the CORNELL-DUBILIER Capacitor



Subsidiary  
The Radiart Corp.  
Cleveland, Ohio



C-D  
Venice, California

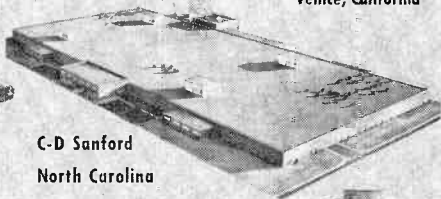

C-D Sanford  
North Carolina



C-D Indianapolis, Ind.




C-D  
Providence, R.I.




C-D Fuquay Springs, N.C.



C-B Hope Valley, R.I.

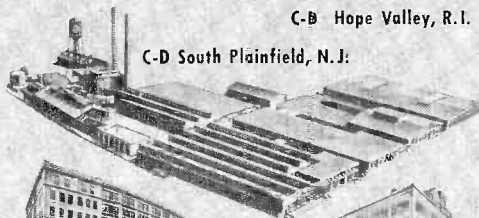

C-D South Plainfield, N.J.

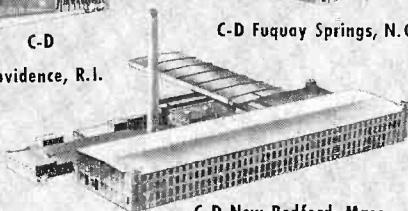

C-D New Bedford, Mass.



C-D Worcester, Mass.



C-D Cambridge, Mass.

Vol. 23

FEBRUARY, 1958


No. 2

CORNELL-DUBILIER ELECTRIC CORP.  
Hamilton Boulevard, South Plainfield, N. J.


POSTMASTER: If undeliverable for any reason,  
notify stating reason, on Form 3547 postage for  
which is guaranteed.

MR. MARSHALL L. COLE  
P.O. BOX 257  
FORTVILLE, IND.

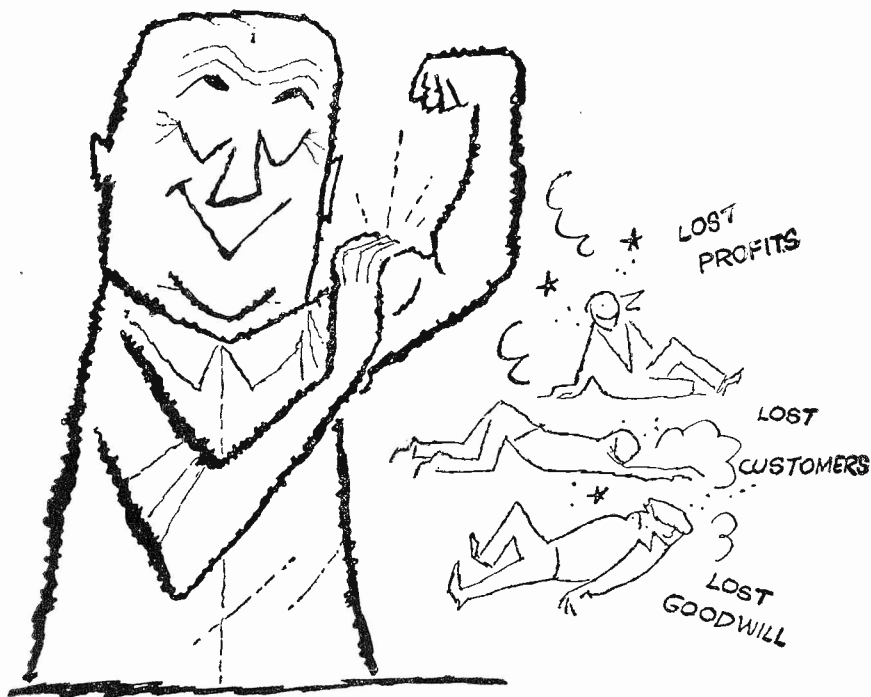Sec. 34.66 P.L.&R.  
U. S. POSTAGE  
PAID  
So. Plainfield, N. J.  
Permit No. 1



# STOP CB\* WITH C-D

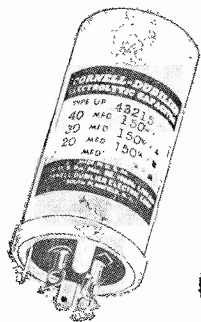

\*STOP SERVICE CALL BACKS with Cornell-Dubilier's popular "UP" Twist Prong Electrolytics—specified by leading manufacturers as original equipment, adopted by "profit-conscious" technicians and the top choice for wide-coverage replacement service. Call-back-free dependability is the big reason why more C-D Capacitors are in use today than any other make. Complete catalog available. Write to Dept.

Cornell-Dubilier Electric Corp., South Plainfield, New Jersey.

SAVE TIME AND MONEY—INSIST on C-D Twist Prong ELECTROLYTICS.

*stop call backs...insist on*



## CORNELL-DUBILIER CAPACITORS

SOUTH PLAINFIELD, N. J.; NEW BEDFORD, WORCESTER & CAMBRIDGE, MASS.; PROVIDENCE & HOPE VALLEY, R. I.; INDIANAPOLIS, IND.; SANFORD, FUQUAY SPRINGS & VARINA, N. C.; VENICE, CALIF.; & SUB.: THE RADIART CORP., CLEVELAND, O.; CORNELL-DUBILIER ELECTRIC INTERNATIONAL, N. Y.

# SIMPLE METHODS OF MEASURING TRANSISTOR IMPEDANCES

By nature the transistor has the configuration of an active network. In the equivalent network, the impedances differ markedly in magnitude from comparable vacuum-tube impedances. Furthermore, certain of the transistor impedances have no counterpart in the tube.

A knowledge of the magnitude of each transistor impedance aids in the efficient transistorization of circuits. While the average values of these parameters and their spreads are obtainable from some manufacturers' literature, exact values for an individual transistor often are required and must be measured by the user.

Transistor test sets are offered by several instrument manufacturers. However, these complete instruments ordinarily are to be found only in laboratories doing the large amount of transistor work which would justify their cost. In all other instances, the circuit designer is expected to measure transistor impedances with conventional test equipment. This article discusses some of the methods which may be used.

## Resistive Parameters

At low audio frequencies, the principal transistor parameters closely approximate the d-c resistive values. Sometimes, it is more convenient and always it is simpler to measure these d-c values.

When the equivalent circuit of the transistor is considered as a T-network (Figure 1), input, output, and transfer resistances are determined in terms of internal base resistance ( $r_b$ ), collector resistance ( $r_c$ ), and emitter resistance ( $r_e$ ). To understand the methods of measurement, it is necessary to

see how these internal resistances, or low-frequency impedances, in combination affect the magnitude of the input, output, and transfer resistances.

Since different pairs of transistor electrodes are used for input and output in common-base, common-emitter, and common-collector circuits, it is readily apparent that different internal resistances will be involved in the determination of the parameters. In highly-simplified form, input resistance ( $R_{11}$ ) is equal approximately to  $r_e + r_b$  in the common-base and common-emitter circuits, and  $r_b + r_c$  for the common-collector. Output resistance ( $R_{22}$ ) is approximately  $r_b + r_c$  in the common-base;  $r_e + r_c$  in the common-emitter and common-collector. Forward transfer resistance ( $R_{21}$ )

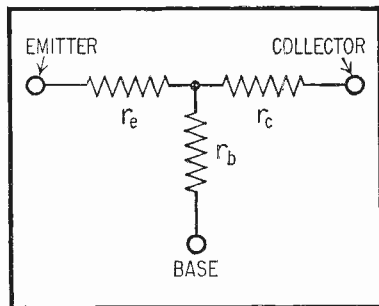


Fig. 1. Simplified 3-Terminal Equivalent of Transistor.

is approximately  $r_b + r_m$  for the common-base (where  $r_m = \alpha r_e$ ,  $\alpha$  being the emitter-to-collector current amplification factor),  $r_e - r_m$  for the common-emitter, and  $r_e (1 - \alpha)$  for the common-collector. Reverse transfer (or feedback) resistance ( $R_{12}$ ) is approximately  $r_b$  for the common-base,

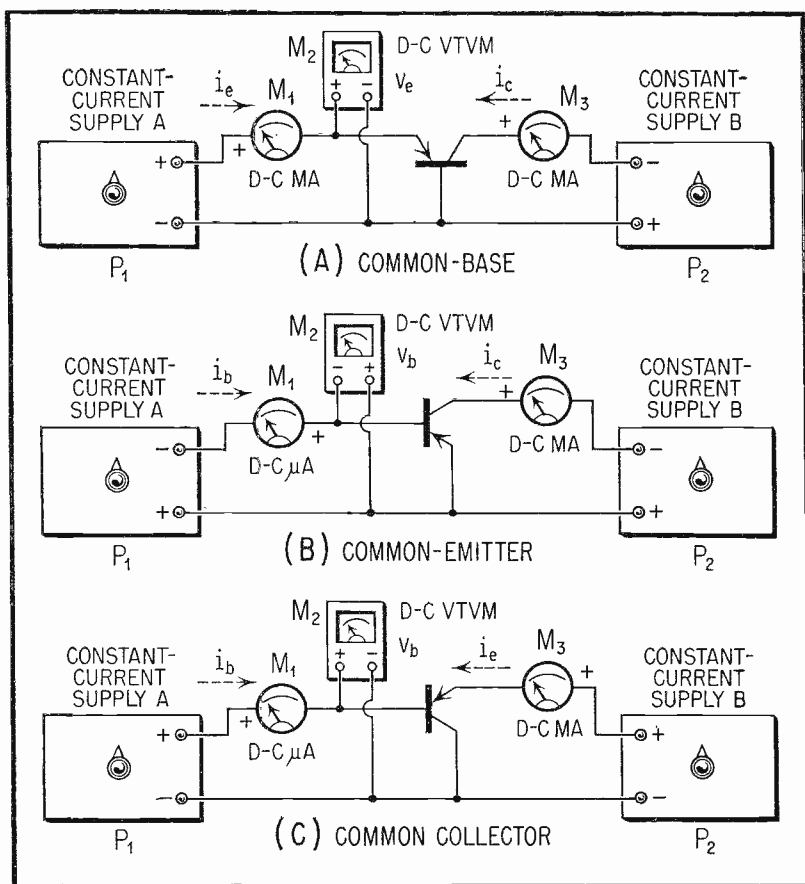


Fig. 2. Setups for Checking  $R_{11}$  and  $R_{12}$ .

$r_e$  for the common-emitter, and  $r_c$  for the common-collector. Exact formulas may be obtained from transistor theory textbooks.

#### Measurement of Resistive Parameters

The resistive impedances may be measured with simple combinations of d-c vacuum-tube voltmeters, milliammeters or microammeters, and adjustable constant-current d-c supplies. In the following examples, the polari-

ties shown are correct for PNP transistors. When checking NPN transistors, reverse the polarities of all meters and power supplies.

**Input Resistance  $R_{11}$ .** The test circuits are shown in Figure 2. In the common-base circuit (Figure 2A), emitter current  $i_e$  is varied while holding collector current  $i_c$  constant. The resulting emitter voltage  $v_e$  is indicated by the vtvm. A curve of  $v_e$  vs.  $i_e$  is plotted.

The slope of this curve is  $R_{11}$ . A family of curves may be plotted for various constant values of  $i_c$ .

In the common-emitter circuit (Figure 2B) and common-collector (Figure 2C), base current  $i_b$  is varied while holding collector current  $i_c$  constant. The resulting base voltage  $v_b$  is indicated by the vtvm. A curve of  $v_b$  vs.  $i_b$  is plotted. The slope of this curve is  $R_{11}$ . A family of curves

may be plotted for various constant values of  $i_c$ .

Output Resistance  $R_{22}$ . The test circuits are shown in Figure 3. In the common-base circuit (Figure 3A), collector current  $i_c$  is varied while holding emitter current  $i_e$  constant. The resulting collector voltage  $v_c$  is indicated by the vtvm. A curve of  $v_c$  vs.  $i_c$  is plotted. The slope of this curve is  $R_{22}$ . A family of curves may

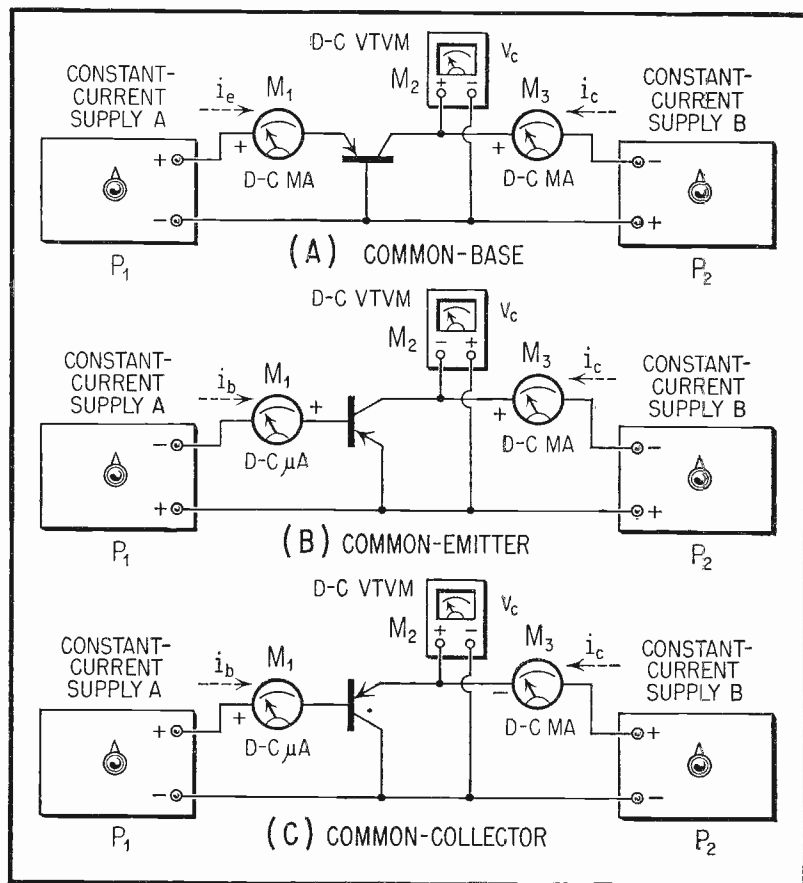


Fig. 3. Setups for Checking  $R_{21}$  and  $R_{22}$ .

be plotted for various constant values of  $i_e$ .

In the common-emitter (Figure 3B) and common-collector (Figure 3C), collector current  $i_c$  is varied while holding base current  $i_b$  constant. The resulting collector voltage  $v_c$  is indicated by the vtvm. A curve of  $v_c$  vs.  $i_c$  is plotted. The slope of this curve is  $R_{22}$ . A family of curves may be plotted for various constant values of  $i_b$ .

**Reverse Transfer (Feedback) Resistance  $R_{12}$ .** The test circuits are shown in Figure 1. In the common-base circuit (Figure 1A), collector current  $i_c$  is varied while holding emitter current  $i_e$  constant. The resulting emitter voltage  $v_e$  is indicated by the vtvm. A curve of  $i_c$  vs.  $v_e$  is plotted. The slope of this curve is  $R_{12}$ . A family of curves may be plotted for various constant values of  $i_e$ .

In the common-emitter (Figure 1B) and common-collector (Figure 1C), collector current  $i_c$  is varied while holding base current  $i_b$  constant. The

resulting base voltage  $v_b$  is indicated by the vtvm. A curve of  $i_c$  vs.  $v_b$  is plotted. The slope of this curve is  $R_{12}$ . A family of curves may be plotted for various constant values of  $i_b$ .

**Forward Transfer Resistance  $R_{21}$ .** The test circuits are shown in Figure 3. In the common-base circuit (Figure 3A), emitter current  $i_e$  is varied while holding collector current  $i_c$  constant. The resulting collector voltage  $v_c$  is indicated by the vtvm. A curve of  $v_c$  vs.  $i_e$  is plotted. The slope of this curve is  $R_{21}$ . A family of curves may be plotted for various constant values of  $i_c$ .

In the common-emitter (Figure 3B) and common-collector (Figure 3C), base current  $i_b$  is varied while holding collector current  $i_c$  constant. The resulting collector voltage  $v_c$  is indicated by the vtvm. A curve of  $v_c$  vs.  $i_b$  is plotted. The slope of this curve is  $R_{21}$ . A family of curves may be plotted for various constant values of  $i_c$ .

**Relationships between Parameters.** For

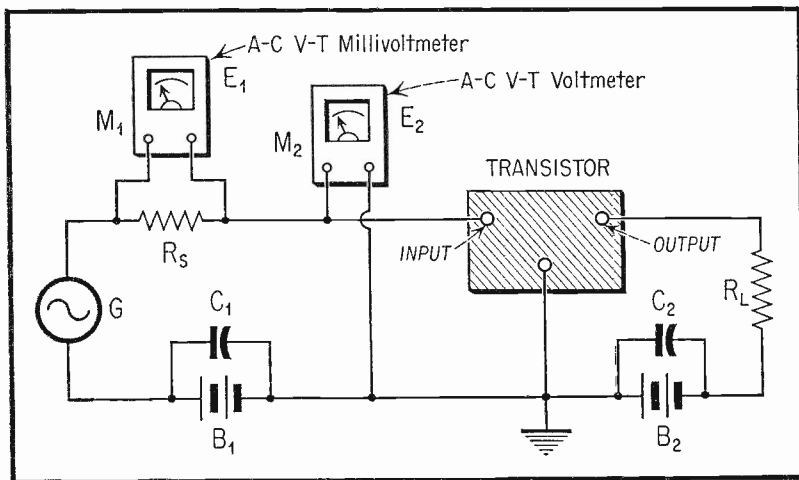


Fig. 4. Circuit for Input Impedance Measurement.

the common-base configuration,  $R_{12} = r_b$ ; therefore,  $r_e = R_{11} - R_{12}$ . Also,  $R_{21} = r_b + r_m$ , and  $r_m = a r_e$ . Alpha ( $\alpha$ ) is the slope of the curve  $i_c$  vs.  $i_e$  for constant  $v_e$ . For the common-emitter configuration,  $R_{12} = r_e$ ; therefore,  $r_b = R_{11} - R_{12}$ . Here,  $R_{21} = r_e - r_m$ , and beta ( $\beta$ ) is the slope of the curve  $i_c$  vs.  $i_b$  for constant  $v_e$ . For the common-collector configuration,  $R_{12} = r_e$ ; therefore,  $r_e = R_{22} - R_{12}$ . Also,  $R_{21} = r_e(1 - \alpha)$ . Here, beta ( $\beta$ ) is the slope of the curve  $i_e$  vs.  $i_b$  for constant  $v_e$ .

### Basic A-C Measurements

The resistance values obtained by d-c measurements in the manner just described will be approximately correct for impedances at low audio frequencies. However, the input and output impedances and amplification factor undergo significant changes at higher frequencies. In the common-collector circuit, for example, when the load resistance is constant,  $R_{11}$  often shows a reduction of 90 percent between 100 cycles and 50 kc with conventional audio-type transistors, and voltage amplification may undergo an 8 per cent decrease between 10 and 50 kc.

Frequency-sensitive parameters other than the internal resistances of the transistor include alpha, beta, and collector capacitance. In one high-frequency transistor, power gain decreases from its low-frequency value (45 db at 1.5 Mc) to unity at 132 Mc.

When a transistor is to be employed at high frequencies, its input and output impedances, which are extremely important in circuit design, should be measured under a-c conditions, preferably at the actual frequency of operation.

Figure 4 illustrates one method of determining transistor input impedance ( $Z_i$ ) in terms of alternating voltage and current. The configuration

may be either common-base, common-emitter, or common-collector as required, hence the transistor is shown here as a block with three terminals. Batteries  $B_1$  and  $B_2$  represent the d-c bias voltages required by the input and output electrodes, respectively, to set the transistor operating point. A low-impedance generator,  $G$ , supplies a test-signal voltage at the operating frequency and this voltage alternates between peak values slightly higher and lower than the d-c voltage of  $B_1$ . Thus, the input signal to the transistor fluctuates over a small increment. Usually, this generator is an a-f or r-f signal generator having low output impedance. High capacitances,  $C_1$  and  $C_2$ , bypass the d-c sources at the generator frequency. The a-c input voltage ( $E_2$ ) is indicated by a high-impedance vtvm,  $M_2$ . An a-c vacuum-tube millivoltmeter,  $M_1$ , is shunted by resistance  $R_s$  which is much lower than the input impedance of any transistor to be tested. Its deflection therefore is proportional to the a-c signal-input current. Thus, meter  $M_1$  effectively is an a-c milliammeter. The a-c input current is equal to  $E_1/R_s$ , where  $E_1$  is the deflection of meter  $M_1$ .

The transistor is terminated in the normal load impedance,  $R_L$ , into which it is to operate in the circuit to which it will be applied. This is a necessary condition, since input impedance is sensitive to load impedance.

Since  $Z = E/I$ , the input impedance  $Z_i$  of the transistor is calculated from the deflections of  $M_1$  and  $M_2$ . Thus,  $Z_i = E_2/(E_1/R_s) = (E_2 R_s)/E_1$ ; where  $R_s$  and  $Z_i$  are in ohms, and  $E_1$  and  $E_2$  in volts.

Figure 5 illustrates a similar 2-meter method of determining transistor output impedance ( $Z_o$ ). As in the preceding example, batteries  $B_1$  and  $B_2$  represent the d-c bias voltages required by the input and output electrodes,

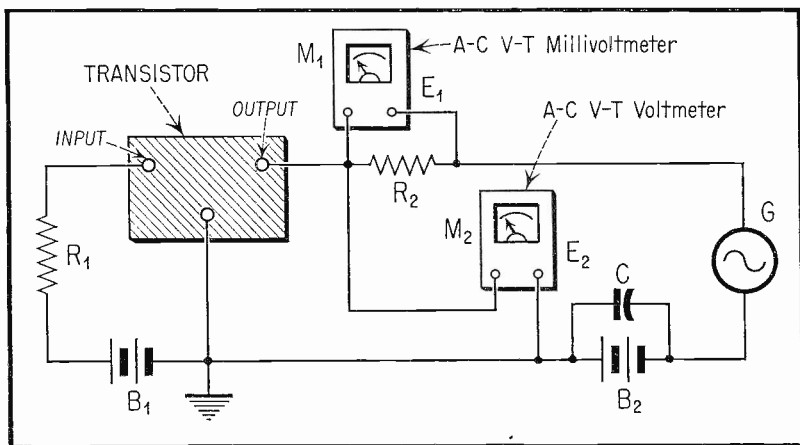


Fig. 5. Circuit for Output Impedance Measurement.

respectively, for the desired operating point of the transistor. The low-impedance generator,  $G$ , supplies a test-signal voltage which alternates between peak values slightly higher and lower than the d-c voltage of  $B_2$ . Thus, the test signal applied to the output electrodes of the transistor fluctuates over a small increment. Resistor  $R_1$  provides an input impedance path equal to the impedance out of which the transistor will operate in the circuit to which it will be applied. High capacitance  $C$  bypasses d-c source  $B_2$  at the operating frequency. The a-c test voltage ( $E_2$ ) is indicated by a high-impedance a-c vtm,  $M_2$ . An a-c vacuum-tube millivoltmeter,  $M_1$ , is shunted by resistance  $R_2$  which is much lower than the output impedance of any transistor to be tested. Its deflection therefore is proportional to the test-signal current. As in the preceding example, meter  $M_1$  effectively is an a-c milliammeter. The a-c test-signal current is equal to  $E_1/R_2$ .

Using Ohm's Law, output impedance is calculated from the deflections of  $M_1$  and  $M_2$ :  $Z_o = E_2/(E_1/R_2) = (E_2 R_2)$

$/E_1$ ; where  $R_2$  and  $Z_o$  are in ohms, and  $E_1$  and  $E_2$  in volts.

It should be noted that considerable care is required for successful measurements using the schemes illustrated by Figures 4 and 5, especially at radio frequencies. To begin with, meter  $M_1$  in each instance is operated above ground, hence it should be of the self-contained battery type to avoid power line complications. All leads in the test circuit must be as short as practicable, but stray capacitances and interaction due to close spacing of instruments must be avoided. The shunt resistor ( $R_s$  in Figure 4;  $R_2$  in Figure 5) must be non-inductive. The load ( $R_L$  in Figure 4) and the equivalent driving impedance ( $R_1$ , Figure 5) must be the identical impedance devices which will be used in the final circuit, although they are represented here as simple resistances. The d-c electrode bias currents must be set exactly to the desired levels (by adjustment of  $B_1$  and  $B_2$ ) to maintain the transistor at the desired operating point. A d-c milliammeter or microammeter, inserted temporarily in series



with  $B_1$  and then  $B_2$ , may be used for this purpose.

### Use of Bridge

The resistive and reactive components of transistor input and output impedances may be evaluated separately by conventional a-c bridge methods. The input or output circuit of the transistor constitutes the unknown arm of the bridge.

For this purpose, the transistor must be dc-biased in a manner somewhat similar to the application of a polarizing d-c voltage to an electrolytic capacitor or iron-core choke during bridge measurements. The bias currents must be measured accurately with suitable d-c milliammeters or microammeters and set to the desired operating level. Both the input and output electrodes of the transistor should be dc-biased during the measurement. Suitable choke coils or isolating resistors must be employed to block the flow of the a-c bridge currents into the bias supplies. The bridge signal must be held low enough to prevent exceeding either the normal

operating voltage or peak inverse voltage ratings of the transistor.

### Amplifier Impedances

Figure 6 shows a simple setup for checking the input impedance ( $Z_i$ ) of a transistorized amplifier. In this arrangement, the amplifier is terminated in its normal load impedance,  $R_L$ . The latter may be the actual load device, such as a loudspeaker, or may be an equivalent resistance.

The test signal is supplied by a suitable signal generator or test oscillator. A calibrated, non-inductive, variable resistor ( $R$ ) is connected in series with the generator and the amplifier input terminals. An a-c vtm is arranged with a spdt switch ( $S$ ) to read signal voltage  $e_1$  before the resistor (Position a) or  $e_2$  after the resistor (Position b).

In operation, switch  $S$  first is thrown to a and voltage  $e_1$  observed. The switch then is thrown to b, and resistor  $R$  is adjusted carefully to set  $e_2$  equal exactly to  $\frac{1}{2}e_1$ . At this point, the resistance setting of  $R$  equals

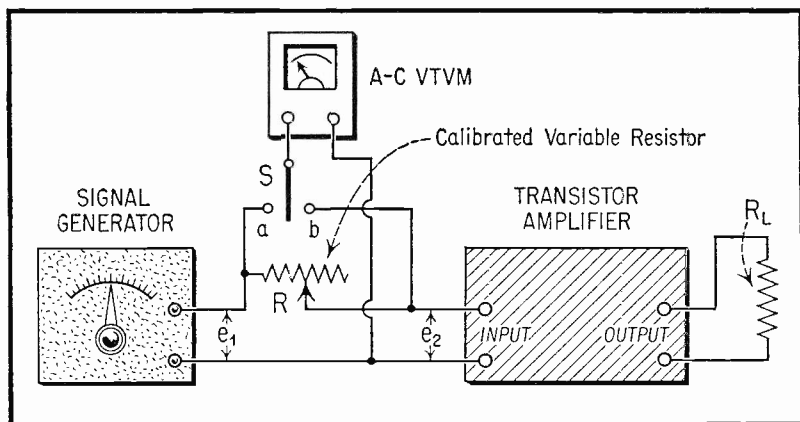


Fig. 6. Checking Transistor Amplifier  $Z_i$ .

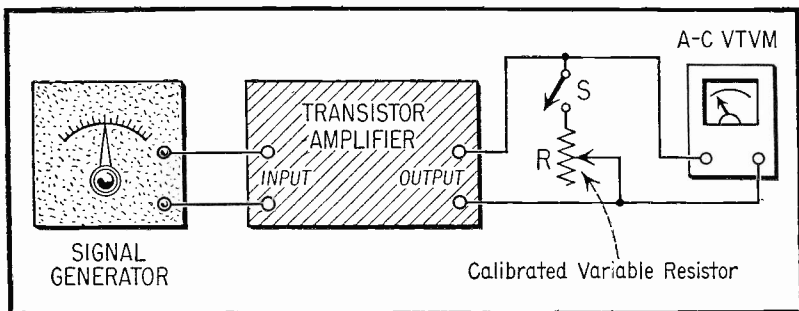


Fig. 7. Checking Transistor Amplifier  $Z_o$ .

the input impedance of the amplifier and may be read directly from the resistor calibration. If the resistor is not direct-calibrated, it may be removed from the circuit and its resistance setting measured with an ohmmeter or bridge. Throughout the measurement, the test voltage must be held to an amplitude low enough to prevent overdriving of the amplifier. The test may be repeated at a number of frequencies to determine the variation of  $Z_i$  with frequency.

Figure 7 shows a similar circuit for measuring the output impedance ( $Z_o$ ) of a transistorized amplifier. In this arrangement, the signal generator or test oscillator supplies a signal voltage to the input of the amplifier. The amplitude of this voltage must be restricted to prevent overdriving the amplifier. A calibrated, non-inductive, variable resistor ( $R$ ) is connected to the amplifier output terminals through a spst switch ( $S$ ). An a-c vtm indicates the amplifier output voltage.

The output voltage ( $e_1$ ) is read with switch  $S$  open. The switch then is closed and resistor  $R$  adjusted to set the voltage to a new level  $e_2$  equal exactly to  $\frac{1}{2}e_1$ . At this point, the resis-

tance setting of  $R$  equals the output impedance of the amplifier which may be read directly from the resistor calibration. If an uncalibrated resistor is employed, it may be removed from the circuit and its resistance setting checked with an ohmmeter or bridge.

When checking an amplifier employing a power-transistor output stage, resistor  $R$  must be rated to dissipate safely at least twice the expected power output of the amplifier.

Additional, detailed data on transistor impedance measurements may be found in the following sources.

1. Principles of Transistor Circuits. Richard F. Shea, Editor. (John Wiley & Sons, Inc.; New York, N. Y.). pp. 485-503.
2. Transistors, Theory & Practice. Rufus P. Turner. (Gernsback Library, Inc.; New York, N. Y.). pp. 109-121.
3. Transistor Characteristics at Low and Medium Frequencies. L. J. Giaconetto. TELE-TECH & ELECTRONIC INDUSTRIES, March 1953. p. 97.
4. Surface-Barrier Transistor Measurements and Applications. Roland J. Turner. TELE-TECH & ELECTRONIC INDUSTRIES, August 1954. p. 79.



This CORNELL-DUBILIER Advertising Service is FREE to "Capacitor" readers. If there is anything of general interest or appeal in the line of electronic equipment or service that you want to BUY — SELL — or SWAP . . . if you want a job or need help, these columns are at your service.

Please PRINT or TYPE your Ad clearly and limit it to 40 words including your name and address. Because of space limitations — only one Ad at a time — please.

Ads are published in the order received and as space permits.

CORNELL-DUBILIER ELECTRIC CORP. reserves the right to edit your Ad to conform to its policies and is the final judge of its suitability for publication. We do not assume any liability or responsibility for any transaction that results. Make your deal direct with the advertiser listed in the Ad.

If you have a "CHANGE OF ADDRESS" — give both your OLD and NEW and mark your request "For C-D Capacitor Mailing List."

IF YOU ARE RECEIVING DUPLICATE COPIES FOR WHICH YOU HAVE NO USE, PLEASE ADVISE YOUR LETTER CARRIER STATING — "DUPLICATE — NOT WANTED".

**FOR SALE** — Hi-Fi speaker system: Philips of Holland 9762 12" woofer and coaxial tweeter, ruggedly installed in Cabinart mahogany finish corner horn enclosure, both perfect, \$50. Monroe Schere, 208 East 58 St., Brooklyn 3, N. Y.

**SELL OR SWAP** — RME 2-11 rcvr., 6 m. Tecraft transmitter, JT 30 astatic crystal mike, Tecraft power supply, antenna relay, and Telorex 3-element beam. A complete 6 m. station, \$140. Thomas A. LaZot, 1558 Fifth St., Rensselaer, N. Y.

**SELL OR TRADE** — Commercial Trades Institute TV course, books only, 1 thru 100, \$25; Timex recorder, \$15. What have you? Vernon J. Kroh, New Salem, N. D.

**FOR SALE** — Hallicrafter S-76 rcvr., built-in speaker, headphones, perfect, \$89; Globe Scout 65 w. xmitter, factory wired, with Shure mike, key, antenna relay, crystals, \$79; DeVry 25 w. PA amplifier, PP6L6, speaker and mike, \$20. F. McCabe, 2318 Terrace Rd., Hypoluxo, Fla.

**WANTED** — Tube checker in good cond.; power transformer for Regal TV 2217; Gramer T140-12; Merit P3053 or 3066; Thoradson 26R95 or 26R18; Stancor P8169; Triad R 38BC; Halldorson P9731. S. Cutler, 1954 Unionport Rd., New York 62, N. Y.

**SELL OR SWAP** — Electronics megaphones, \$25; West. Elec. 30-40 mc rcvrs., \$10; ship/shore rcvr, \$15; 12 v. vibrator supplies, 200 v. output, \$7.50; 30 w. 6 & 10 m. mobile xmitter, \$35; 150/162 mc RCA xmitter, \$35. Want Lampkin freq. meter; technical manuals on Doolittle FM equip; broadcast xmitter. Hingley, 82 Lower Main St., Matawan, N. J.

**WANTED** — Operator's manuals for Simpson 215 VOM. Elmore Moss, R 1, Cave City, Ky.

**FOR SALE** — Sams Photofacts in binders, 90 to 270, \$10 each job. Joe's TV, Box 247, Farmington, Ill.

**FOR SALE** — Zenith console ranges: 540-1620 Kc, 88-108 FM, 42-48.5 FM 9 tubes I. n., power transformer, output speaker transformer, 117 VAC 100w., I. n cabinet. Bill Lee, 4932 S. Forrestville Ave., Chicago 15, Ill.

**WANTED** — Chokes, transformers, xmitting tubes in excellent cond. for use in missionary short-wave station; RF choke coil to handle 2 or 3 amps. State price. Milton I. Feivre, Box 1862, Tampa 1, Fla.

**WANTED** — IRE proceedings from 1952 and older. R. Davidson, 87-10 204 St., Holliswood 23, N. Y.

**WANTED** — Berlant BA-1 with 5 kc and 15 kc adj. Cash or have RCA WV87A, Precision ES-500A and SP-5 probe set, and Simpson 488 field strength meter, all l. n. Robert Childress, 128 W. 6th St., Cookeville, Tenn.

**FOR SALE** — Fischer SWD-1 and Rose CX2 old medical diathermy units in operating cond., \$25 each; radar indicator units with PPI tube, \$15 each. R. V. Welsh, 306 Prospect St., Cambridge, Mass.

**WANTED** — Adding machine, tape type, and check protector. Describe, giving price and cond. and sample of work. Jerome Tannenbaum, 5240 S. Harper, Chicago 15, Ill.

**FOR SALE** — Precise 300k 7" scope; RCA jr voltohmmyst; Eico 1050 bat elim. 6-12 v.; Heathkits SG-8 RF sig. gen. and C-3 condenser checker; 25 Sam's Photo-facts; 6 radio and TV books, \$175. Local preferred. Mike Nardotti, 233 Lawrence St., Hempstead, L. I., N. Y.

**FOR SALE** — "High-Fidelity" mag. from vol. 1 No. 1 to vol. 6 No. 12. Also want 3.5 to 6.0 mc antenna coil for BC-348-Q. I. O. Ebert, 1810 Linden St., East Lansing, Mich.

**SELL OR TRADE** — Radio City scope; Superior TV 30 sig. gen.; Hickok 225 VTVM; American automatic scientific tube checker, mod. TV20; Triplett 3413A tube checker; Earl's TV, 524 So. Western Ave., Dayton 7, Ohio.

**FOR SALE** — Scott SWL SLR12-B rcvr., \$50; vibrator power supply units 32 and 110 DC input with 117 VAC output, 80 w, \$7.50 each. Jud Rourke, 181 Erie St., Cambridge 39, Mass.

**SWAP** — Argus 100 mm telephoto lens for C-3 camera, and Universal 200M type finder, both l. n. Want Polaroid Highlander camera. Michel Katz, 147-11 76th Ave., Flushing 67, N. Y.

**SELL OR TRADE** — GE 250 portable scarcely used, home-built electronic high voltage photoflash in carrying case, including Sylvania R4330 tube, less reflector only. Want Leica copying (BOOWU) attachment for 3c. A. Martin, 406 Queens Ave., Massapequa, L. I., N. Y.

**SELL OR TRADE** — BK-401 soundmirror tape recorder, mechanically ok, cabinet needs touching up. Need 10 w. FM transceiver in 155 mc range, need not be in working cond. Herb Ailing, Strasburg, Ohio.

**WANTED** — Instruction manual for McMurdo-Silver 909 sweep gen., range 2-226 mc. or permission to photostat. Mason DeCamillis, 325 Shadowlawn Dr., Inkster, Mich.

**SELL OR TRADE** — Gonset G66B unused; Almac PMR6 with 12 v. supply; Hallcrafters SP44 pan adaptor, very clean; Leece-Neville unit complete for 6 or 12 v.; Bendix T12 trans. 100 w. Need Ranger, must be clean. Samuel Lieberman, 130-29 228th St., Laurelton 13, Queens, N. Y.

**FOR SALE** — Over \$600 worth of tubes, condensers, resistors, speakers, transformers, 40 Sams Photofacts in binders, NRI multimeter, models No. 34 sig. tracer, 88 sig. gen., 69 tube tester, l. n., \$175 complete. Robert Garrison, 14800 Martell Ave., San Leandro, Calif.

**FOR SALE** — Hallcrafters R-46 speaker, A-1 cond., \$10; Taco 400 ohm open wire line, 100 ft. package roll, \$2.50. John J. Oskay, 70 Senior St., New Brunswick, N. J.

**FOR SALE** — Heath LP-1 pattern gen. with factory added sync terminal and lead same as on LP-2, factory checked, unused, \$22.50. E. Hoonstra, 722 E. Spruce St., Sault Ste. Marie, Mich.

**SELL OR TRADE** — Heath TS-3 sig. gen. and marker, assembled but never used, \$35 or trade for good used 2-speed tape recorder, working or not. Donald Rockwell, R 1, Box 193-A, Goshen, Ind.

**FOR SALE** — Matched pair of Thordarson Hi-Fi push-pull transformers, T15A74 and T15S90, complete with pictorial and schematic circuit, 15 w. output, inverse feedback.  $\pm 1$  DB, 40-15,000 cycles with bass boost, \$9 for pair. Vincent Pelletier, 5523 31 Ave., Woodside 77, L. I., N. Y.

**WANTED** — Simpson 488 field strength meter. State price and cond. V & M Radio & TV Service, Box 141, New Roads, La.

**SWAP** — PA system, disc recorder, geiger counter, "bug" or various parts for electric train set or photographic equip. R. F. Graf, 215 W. 92 St., New York City, N. Y.

**WANTED** — Lampkin 105 freq. meter; 205 modulation monitor; Measurements Corp. microvoltage model 80; 30-50 mc mobile units complete with cables and control heads. State lowest cash price and cond. George Tate, Artillery Rd., RFD 4, Taylors, S. C.

**SELL OR SWAP** — Unused 1951 Philco push-button auto radio, never installed; Sunbeam shavemaster. What have you? M. Gianfrocco, 1 Bell St., Providence 9, R. I.

**SELL OR TRADE** — 4" reflector telescope, with tripod, altazimuth mount, 2 eyepieces for magnification of 64x and 192x, and 7 power finder scope. Want Hallcrafters rcvr. L. Suchow, 1915 University Ave., New York 53, N. Y.

**FOR SALE** — Browning RJ12 tuner and power supply; Bogen DB20DF amplifier; UTC LS-33 high level matching transformer. Donald Keiser, Gladbrook, Iowa.

**FOR SALE** — Riders 2 thru 7, 1 n., \$8 each. Local preferred. James Daniele, 449 4th St., Elmont, L. I., N. Y.

**FOR SALE** — Hammerlund HQ129X rcvr, \$100; Precision E-200-C sig. gen., \$30; Precision 954 tube and set tester, \$65; vibrator power supply 6 v. input, 300 v., 100 mls., \$10. All in good cond. M. Vassallo, 99 Greenpoint Ave., Brooklyn, N. Y.

**FOR SALE** — Heath TS-4 sweep gen., \$40, and 0-10 5" scope, \$55. Probes \$4 extra; Motorola 7" TV, needs repair, \$10; Dumont 17" TV console with FM, \$35, needs repair. All F.O.B. Donald E. Zeitz, 247 Conant St., Hillside 5, N. J.

**FOR SALE** — RCA TV eye camera, excellent cond., \$375; RCA ATJ TV camera as pictured on page 114 August C. Q. mag., \$295, includes tripod, power supply, monitor etc. T. V. Labs, 111 Main St., Waterville, N. Y.

**FOR SALE** — Radio & TV tubes; GE elec. foot-warming pad, \$3, Blonder-Tongue 4-tube automatic booster HA-1L, \$10. Andrews, 740 Maple St., Bethlehem, Pa.

**FOR SALE** — Mon-Key, \$15; Millen 90700 variarm VFO, \$20; 838 tubes, \$3 each; TS-117-GP test set, \$15. Robert Roske, 306 Prospect St., Cambridge, 39, Mass.

**SELL OR TRADE** — 2 sheets unpainted & unpunched aluminum 10 1/2" x 19" x 1/8", and 2 sheets of 153/4" x 19" x .091", \$13 or trade for 115 v. AC isolation transformer 125 w. Ray Bohnert, Medford, Wisc.

**FOR SALE** — Past issues of Electronics, QST, CQ, and Radio/TV News, 15c each, plus shipping; Meissner 9-1090 sig. shifter, \$37.50; 10m ST-203 A xmtr, \$37.50. Roswel Electronics, 306 Prospect St., Cambridge, Mass.

**WANTED** — 110 VAC and 12 v. power supplies for BC-669-B, or diagram of the 12 v. DC supply. William Hansen, 165 Silverbrook, Niles, Mich.

**WANTED** — For cash, UTC S48, S35, and S36 reasonable. Have Heath gen. TS 1A for sale, \$35. A. R. Tuttle, 25010 Ford Rd., Dearborn, Mich.

**FOR SALE** — Drake 900 soldering gun, 135 w., 1 n., only \$6.50 cash. T. J. Englert, Jr., 1601 Frances St., New Orleans 17, La.

**TRADE** — Unused 16EP4A TV tube for a Precision or equal tube tester and VOM both in working cond. C. W. Bently, Box 236, Talent, Ore.

**WANTED** — HW Sams, any amount, parts or complete set if reasonably priced. Will pay postage. Jack's Shop, R 1, Lewisburg, Pa.

**SELL OR SWAP** — Heath sweep gen. TS-1 for condenser tester of like value. Joseph Blahoves, 134 Berry St., Dover, N. J.

**SELL OR TRADE** — Hearing aids; metal locator; duplicator. Want transistors; tube tester. John Haynes, Doe Run, Mo.

**WANT** — Heath A-7E or A-7D amplifier, kit preferred, late model, new cond. Cash or trade. T. Ferguson, 171 E 91 St., New York 28, N. Y.

**FOR SALE** — Two model 79 Webster wire recording mechanisms. Both in A-1 cond. Best offer takes either or both. G. C. Hologa, Winchester, Wis.

**SELL OR TRADE** — Have Vomax, Weston Master 2, Riders 12, Photofact 1, 2, 4. Want short wave rcvr. L. Putnam, Woodward, Iowa.

**FOR SALE** — Perfect color 156GP22 pix tube. Make offer. Ray Fernick, 1376 Crosby Ave., Bronx 6, N. Y.

**FOR SALE** — Unused Vol. 1 NRI radio book, \$12.50; Riders 1 to 5 abridged and 6 to 15 (Vol. 12 missing), \$35 plus postage. Chas. J. Morris, 620 Frame St., Denton, Texas.

**WANTED** — Two-way radio for truck, 50-mile limit, also PA amplifier. Forest Donaldson, Slayton, Minn.

**WANTED** — RCA scope mode WO-55A. Botbyl Radio Shop, 1009 Sophia St., Muskegon, Mich.

**SWAP** — Need tube tester. Have A elim. and battery charger, meters, tubes, parts; 16" console TV in working cond. Sam Berenblum, 417 Greenwich Ave, Greenwich, Conn.

**WANTED** — 10-15 hp Evinrude or Johnson outboard motor A-1. Have RCA 36-A gen. never used, FS meter, Rimco analyzer, Dumont 274 scope or ? G. E. Howarth, 216 1 Ave. East, Oskaloosa, Iowa.

**WANTED** — Q multiplier and mobile converter, 3-30 Mc. Will swap 829B's; Wilcox CW-3; or 3" meters. Henry Wemple, Norton Rd., Vernon Center, N. Y.

**FOR SALE** — Hallicrafter rcvr. model 38, good cond., \$20. Leroy Tresselt, 3122 N. George St., Franklin Park, Ill.

**SELL OR TRADE** — Radio and S F magazines for cash or parts, etc. V. Johannes, 1541 Metropolitan Ave., Bronx 62, N. Y.

**WANTED** — 3" Heathkit scope; also tube checker, 625 Eico or equal. Will swap for ham gear or test equip. Lee Terry, Sr., 1914 Ballinger Rd., Seattle 55, Wash.

**SWAP** — Bell 3 speed hi-fi tape recorder, volume and tone controls, fast wind and rewind, erase interlock, response 40 to 15,000 cps. Want hi-fi power amplifier and AM-FM tuner in excellent cond. H. Pillier, 451 Thieriot Ave., Bronx 72, N. Y.

**WANTED** — Service Notes and diagrams of the G.E. rcvr., type E-155. State price and description. Dan L. Stevens, 34 Yale Sq., Morton, Pa.

**WANTED** — Alliance H1R-2 rotator. State price. Glen Johnson, Seymour, Tenn.

**FOR SALE** — Precision WW resistors, 3485, 5400, 20,000, 5,000, 750, 1600, and 2215 ohms, 1% tolerance, 50c each. A. Himmelbaum, 141-55 85 Rd., Jamaica 35, L. I.

**WANTED TO BUY** — GE BM-1A FM freq and modulation monitor with power supply. State price and monitor's present frequency. F. C. Hervey, Chief Engineer, WLFM, Lawrence College, Appleton, Wis.

**FOR SALE** — Outdoor business neon sign, metal for 4 lines of lettering with transformer 6" x 2" x 10" deep. Best offer, local. T. Wasek, 40 Ackerson Ave., Pequannoc, N. J.

**WANTED** — Hallicrafters SX-17 rcvr. Cash or trade. Norman Carignan, 3 Curtis St., Providence 9, R. I.

**WANTED** — Small portable disc recorder in working cond., any make or model. D. Teague, Box 964, Hurley, N. Mex.

**SELL OR TRADE** — "Galaxy" SF mag. Nov. 51-Nov. 57, except 1 issue; "Astounding" SF, Oct. 49-June 57, complete except 5. Want good communications rcvr., National, Hallicrafters, or Ham-murlund. Stephen Swerling, 132 Bloom-ingdale St., Chelsea 50, Mass.

**SELL OR TRADE** — Back issues of Service Technician and Service Dealer; also misc. books. Send for list. Need Technician Digests prior to set 31 (March 1955). Farmer's Radio & TV Service, Brady, Texas.

**WANTED** — Heath AV-3 audio VTVM. Jerome Mendel, 938 Kenyon Ave., Plain-field, N. J.

**WANTED** — Sams Photofacts in good shape from No. 1 through 150. Must be in this general territory. Will pay cash or trade test instruments. Thompson's Radio & TV, Box 330, Fayetteville, Tenn.

**WANTED** — 2 matching Hi-Fi cabinets 26" max. width, with or without speakers. Will trade used TV in good working cond. or Sams, or Riders for same. Arch Campbell, 78 Main, Dublin, Pa.

**SELL OR TRADE** — Heath DX-35 xmitter, VFO \$90; Hallicrafters SX-99 rcvr., \$100; Simpson: 269 VOM \$75, tube tester \$75, sig. gen. \$75. All A-1 cond. Want DX-100 and SX-100 or equivalent. Walter Conway, 3229 Maddux Dr., Palo Alto, Calif.

**FOR SALE** — Sound-Scriber portable model PCRICBC, \$50; Leeds & Northrup standard cell, \$10; GE fil trans pri 115 v, sec. 5 & 5v, kva. 065, ins. 12 kv. \$10; United choke LS-92, \$10. R. Bronson, 252 Matec Way, St. Petersburg 4, Fla.

**FOR SALE** — (N. Y. Metropolitan Area) Components including makings of 300 w. fone xmitter; meters, chokes, xformers, 6 v. vibropack, many small parts, tubes, etc. Buy singly or all, very cheap. Diamond, 550 W. 20 St., New York, N. Y.

**TRADE** — Japanese military xmitter, rcvr., and hand gen. Rcvr. range 400-6,000 kc, transmitter range 600-5,000 kc; VFO or crystal oscillator. CW and phone for tape recorder. Wesley W. Harris, R 5, Box 2325, Bremerton, Wash.

**FOR SALE** — Heath FM-3 tuner, factory calibrated. Never used. Ship post-paid \$30. Ben Marconi, 120 Gatling Pl., Brooklyn 9, N. Y.

**FOR SALE** — Zenith H500 transoceanic, \$65; Granco UHF converter, \$10; Heathkit TS-2 sweep gen., \$20. All i. n. Might trade for LF or VHF aircraft rcvrs. R. J. Faulstick, 4800 Kolmar Ave., Dayton 3, Ohio.

**FOR SALE** — RCA BC & SW radio AC; AC-DC table radios: Temple BC & SW, Motorola, Bendix, \$25 for the lot, all perfect. Local only. Thomas Byrne, 331 Calhoun Ave., Bronx 65, N. Y.

**WANTED** — RME VHF 152-A or B in good cond. W. J. Wilson, 418 Grandview Ave., Indiana, Pa.

**SELL OR TRADE** — Meissner 8C FM tuner, \$20; Heath V7A VTVM, \$18; AW-1 audio wattmeter, \$20; GE 260 portable radio, \$25. Want Magnocord low level mixer, 10" ext. arms. Gene Blash, 1839 So. 12 Ave., Maywood, Ill.

**FOR SALE** — Globe Chief built by owner, perfect cond. Most reports 59EX, \$55. Can't ship, will demonstrate on request. Herman Nied, 57 Patton Blvd., New Hyde Park, N. Y.

**SWAP** — Philco model 61 12.5 amps 1/2 ton window air conditioner used very little for good color bar gen. Vincent Iavarone, 1218 Leland Ave., Bronx 72, N. Y.

**FOR SALE** — Tubes and surplus equip. Send 2c stamp for list. Bill Storey, 254 Fairgreen Ave., Youngstown 4, Ohio

**WANTED** — TV sets, 14", 16", 17", in good or repairable cond. in Brooklyn Area. State asking price and make. Sal's Television Servicing, 1653 East 55 St., Brooklyn 34, N. Y.

**FOR SALE** — Precise 630 sig. gen., \$44; as is 10" TV chassis, \$4.50 and 12" chassis, \$6.50. H. Bell, 3917 Ely Ave, New York 66, N. Y.

**WANTED TO BUY** — Tuner for CBS Sky-King TV model 10-100 same as Silvertone 117-17, uses a 6BC5 RF and 6V6 osc-mixer. Albert C. Hart, Certified Radio Service, 207 N. Raymond St., Griffith, Ind.

**WANTED** — Hammurlund HQ 129X rcvr with speaker; Spanish record course. Have Hallicrafter S40A rcvr. Norman McHale, 77 Turner Ave., Buffalo 20, N. Y.

**SWAP OR SELL** — Projection TV with screen; Heath SG-6 sig. gen.; RCA wire recorder; Bromeco 10 in mobile xmitter; other misc. radio equip. Want all types ham and ham test equip. Selwyn Wynstock, 5002 S. Lawler, Chicago 38, Ill.

**WANTED** — Low to medium priced communications rcvr.; also slide projector. State price and cond. Frank Gibes, 4941 Crystal St., Chicago 51, Ill.

**WANTED** — One or two man Radio & TV Shop in North Carolina, eastern part preferred. V. Dunne, 1526 Randolph Ave., Greensboro, N. C.

**FOR SALE** — GE synchro rcvr. and synchro xmitter, \$10 for both. Aram J. Barsoomian, 21 Porter St., Watertown 72, Mass.

**FOR SALE** — HQ 150 rcvr. in perfect cond. Sacrifice \$225. No shipments. Andy Rogers, 5 Stuyvesant Cval, New York 9, N. Y.

**FOR SALE** — Zenith FM-AM Super Symphony table model 725 radic rcvr. in excellent working cond. Best cash offer. D. Landesberg, 179 Marcy Ave., Brooklyn 11, N. Y.

**WANTED** — RCA Pict-O-Guide Vol. II; Jackson selenium rectifier tester. L. M. Mick, 202 N. Peoria Ave., Dixon, Ill.

**FOR SALE** — National NC-173 rcvr.; Meissner EX sig. shifter; BC-610 exciter deck; BC-610 PA coils and misc. parts. Want to buy Supreme AF-100 xmitter. E. L. Felder, Tylertown, Miss.

**FOR SALE** — Heath: G-5 sig. gen., \$14.75; T-2 sig. tracer, \$19.50; LP-1 linearity pattern gen., \$22.50; Eico 360 sweep gen., \$22.50; i. n. with manuals and leads Weiss Radio-TV Service, 1427 Glencoe St., Denver 20, Colo.

**FOR SALE** — Complete Radio-TV business, stock, equipment, tools, misc. Net value \$4,000, will sacrifice at once. For complete inventory write Eugene Byram, Box 128, DeLeon Springs, Fla

**TRADE** — Stromberg-Carlson AM-FM 11-tube radio chassis, 550-1750 kc, 40-50 mc, Electro-Voice 606-20 mike. Need SW rcvr, code oscillator. David DeCobert, 609 Henrietta Ave., Gillespie, Ill.

**TRADE** — Dumont 241 lab. oscilloscope. Want recent Hickok tube tester. Prefer Boston area. Edward Withey, 22 Anselm Ter., Brighton 35, Mass.

**SELL** — Unused Rek-O-Kut TR-12-H recording turntable, with M-12 lathe and 8-ohm cutter, \$150; Dejur PTR-90 tape recorder, warranty, reg. card, and dynamic mike, \$225; Shure 55S and E-V 664 mikes, choice, \$40; 17" professional lathe, slightly used, less head, \$75. All items FOB. John T. Moore, Box 63, Seneca, S. C.

**WANTED** — Webcor tape recorder in any cond.; good communications rcvr. with xtal filter or Q multiplier; Heathkit test equip. complete with manuals; Sams Photofact folders. All for cash or trade. Wood Radio & Television Service, 213 Springer Dr., Coraopolis, Pa.

**WANTED** — Tubes: TV, receiving, transmitting, power, etc.; also test and communications equipment. Surplus acceptable. Cash or swap. Lou Dollin, 172 Washington St., New York 7, N. Y.

**FOR SALE** — Century "In Circuit" condenser checker, \$20. S. Cutler, 1954 Unionport Rd., New York 62, N. Y.

**FOR SALE** — Hickok 610A sig. gen. used very little, \$75; Simpson genescope 480, excellent cond., all cables, instructions, \$200, or \$250 for both. Anderson L. Lowe, 717 Devon Dr., Greensboro, N. C.

**TRADE** — 7" Sylvania oscilloscope, excellent cond plus cash for ham rcvr. Gonset 2-meter converter, \$25; Heath TV alignment gen., \$20. Want used rcvrs. any cond. for cash. Conrad Radio & TV, 12908 Lorain, Cleveland, Ohio.

**FOR SALE** — Complete amateur station: Johnson Adventurer xmitter, Elmac PMR-6A mobile rcvr., Heath VFO, Dow-key coax. relay. All excellent cond., complete, \$155 plus shipping. R. H. Will, 306 Willowbend Rd., Tonawanda, N. Y.

**WANTED** — For cash RCA TV Servicing course, 1953 or later. Don Meek, 210 N. Rock, Sheridan, Ark.

**FOR SALE** — 2 UHF converters, Regency RC 600, and all-channel 99; also 6AF4 and 2AF4 brand name tubes, all for \$20. B. J. Laporte, Jr., 2285 Sere St., New Orleans 22, La.

**WANT** — To buy VTVM; 5" scope; tube checker, in working cond. or repairable. State make, cond. and price. Voldemars Rage, 1638 W. 6, Anderson, Ind.

**FOR SALE** — Pilot FM tuner in excellent cond., \$20. Local deal only. Milton Wendroff, 2016 Avenue N, Brooklyn 10, N. Y.

**FOR SALE** — Heathkit A7-E amplifier with preamp, A-1 cond.; 45-rpm automatic record changer, holds 11 records in A-1 cond. Best offer cash or trade for ham gear. Will sell separately. DuWayne Bostow, Max, N. D.

**WANTED** — Regency FM televerter, Heathkit FM tuner and Miller reflex tuner. O. Zetlmeier, 1123 Woodycrest Ave., New York 52, N. Y.

**WANTED** — Tubes and ham gear. Any type or quantity tubes, rcvr, xmitter, etc., plus RTTY equipment. Setting up new ham station. Send list and details in first letter. Sy Denby, 78 Cortland St., New York 7, N. Y.

**WANTED** — Winchester 1897 shotgun and 40 w. modulator with power supply. Have for swap Evinrude 1 hp trolling motor, weighs 16 lbs. E. Harvey Cunningham, P.O. Drawer H, Rio Grande City, Tex.

**SELL OR SWAP** — Some QST's 1931 to '49 and Electronics, 1938 to '40, neither complete; collectors' items, i.e., old tubes and transcriptions (local only), Wasp, Super Wasp-coils, no power supplies. Want Johnson matchbox, S. W. R. bridge. I. Diamond, 130 Walnut St., Paterson 2, N. J.

**SELL OR SWAP** — Two sound powered U. S. Army hand set phones TS10-M. Were used for antenna installations — original cost, \$29.95 each. Make offer. Ed Tatar, Box 75, Keisterville, Pa.

**WANTED TO BUY** — Usable Taylor T-55 xmitting tubes at reasonable prices. Advise quantity, price, and cond. Shad Whitt, Airport Dr., Princeton, W. Va.

**FOR SALE** — Heath TS-2 sweep, \$20; SQ-1 square wave, \$20; S-2 switch, \$15; Eico 352 bar gen., \$10; Simpson 20,000 o.p.v. VOM, \$7; Terado inverter 6 v 60 w. vibrator, \$14. Plus postage. R. Rogers, 28 Bellamy St., Boston 35, Mass.

**WANTED** — RCA 1 and 2 Pictoguide. Or will buy complete series 1, 2, and 3 if available. Advise cash price. John A. Fels, 801 Silver Spring Ave., Silver Spring, Md.

**WANTED** — Books: Servicing and Calibrating Test Equipment, Milton S. Kiver; Radio Receiver Servicing, John T. Frye; Repairing Television Receivers, Cyrus Glickstein. Must be reasonable. Also resistance decade Heathkit, or Precise 1/2% to 1% accuracy. Quote prices. R. Chlupsa, 45-56 189 St., Flushing 58, N. Y.



**WANTED** — Schematic for linear Equip. Lab., Video amplifier cathode ray oscilloscope, model HF-1; and Pierce School of Radio-TV, multimeter, model 630P. Robert Wendel, 160-20 Grand Central Pkwy., Jamaica 32, L. I., N. Y.

**WANTED** — Link FM radio xmitter-rcvr. type 2365, also Leece 6 v. altnator. Edward C. Hoggie, Bena, Va.

**FOR SALE** — GE 640 portable 3-way, \$25; 16 mm 100 ft camera spools, 5c each. Cas, 85-61 66 Rd., Forest Hills 74, N. Y.

**FOR SALE** — BC-645 and 654; 12GP7 CRT; MR-3-10-20-75 rcvr.; Supreme 680 audio osc. A. Turturro, 146-26 No. Hempstead Tpke., Flushing 55, N. Y.

**FOR SALE** — Jackson TV62 sweep-marker gen. with cables and inst., A-1 cond., \$150; Hickok 191X microvolter, \$45. Val Obal, 4165 J St., Omaha 7, Neb.

**FOR SALE** — Complete Heathkit LP-1 linearity pattern gen., R.F., bars or dots, \$25. Bill's TV Service, 25 Sylvan Pl., New Rochelle, N. Y.

**FOR SALE** — Heath TS-4 TV alignment gen. recalibrated by the Douglas Instrument Co. Make offer. Want good clean 8773 R.C.P. servishop instrument. Ritts Radio Service, 644 No. 7 Ave., Tucson, Ariz.

**SELL OR TRADE** — BC 224A rcvr., excellent cond., low voltage version of type BC 348 with same frequency coverage and features. Cash \$40. Roland St. Louis, 209 Cresthill Ave., Clifton, N. J.

**SELL OR TRADE** — 4X5 Graphic, enlarger, printer, etc., \$300 or ham equip. Local only. Joseph Schwartz, 742 New Jersey Ave., Brooklyn 7, N. Y.

**WANTED** — PA system complete with horns to run off 6 v. battery for mobile PA speaking. Bob's TV Ser., Box 37, Wabasso, Fla.

**FOR SALE** — BC-312 SW rec., 6 bands-1500 Mc to 1800 Mc, turn dial to change bands, 10" speaker in cabinet. Converted from 28V to 110VAC, \$50. Spencer White, 162 Market St., Passaic, N. J.

**FOR SALE** — Meissner 9-1090 sig. shifter, \$29; 1. n. Webster wire recorder 80-B 80A, needs repairs, \$19; 2 Edison cylinder type phonographs; Bendix MRT3 mobile FM transceiver, needs repairs, \$19; SR-20 Hallicrafters, \$49. All fob. Louis, 204 Charter St., Clarksburg, W. Va.

**SELL OR TRADE** — Heath AR-2; AT-1 modulator and mike; photography magazines and equipment. Need DX-100 and ham gear. Will deliver where possible. M. Feigenbaum, 21 Boothbay St., Hartford 12, Conn.

**SELL OR TRADE** — Best offers Set of 2 Canon cameras with F2 50 mm and F4 135 lenses; 16" recorder-playback with 70 blank discs, 1. n. Bob Townsley, 5939 Almaden, Oakland 11, Calif.

**FOR SALE** — Tel Rad 18A freq. standard, 1000, 100, 19 kc., \$20; NC-173 rcvr., matching speaker, \$130; 32V3 converted from 32V2, \$400. Want Collins 4:1 knob for rcvr. J. Taylor, Stanwood Rd., Mt. Kisco, N. Y.

**SWAP** — High grade telescope with extremely stable tripod, micrometer adjustment; 8 x 35 French binoculars; BC-348M; Heath AR-2 for ham equip. of all kinds. Kenneth G. Davis, R 4, Severn Ridge Rd., Annapolis, Md.

**FOR SALE** — Unused Port-A-Temp portable air conditioner in sealed factory carton, \$35. Jack Fives, 2916 Rockrose Ave, Baltimore 15, Md.

**WANTED** — Weston 983 scope or something comparable. Pratt's Radio TV Service, 170 7 Ave., W. N., Kalispell, Mont.

**WANTED** — Mobile ham gear, 2 v. system, rcvr, xmitter, pwr supply, VFO, antenna, etc., in good shape. State price. Alan York, 35 Main St., East Hampton, N. Y.

**FOR SALE** — Pair Vocaline transceivers 12 v and 115 v, pair Ground Plane antennas, used less than 5 hours, all for \$100; Gonset Tri-Band converter 6 v and noise clipper, A-1 cond., \$25 fob. J. Y. Wilfong, R 1, Newton, N. C.

**SWAP** — Simpson 260 multimeter not operating, for pocket size multimeter 2,000 ohms per volt on AC and DC. Seymour Needelman, 261 East 55 St., Brooklyn 3, N. Y.

**FOR SALE** — 630 TV 10", in 21" console, yoke, hi-volt transformer, CRT bracket, parts to convert to 21", \$75 fob; Hallicrafters 18", GE 10", and Emerson 10", \$25 each; Transvision 12" with FM radio, \$30. Nick's Radio, 170 Wellington Rd., Elmont, N. Y.

**SELL OR TRADE** — Hallicrafters SX42, fair shape, \$125, or trade for Hi-Fi, amplifier, and tuner. Herman Horn, R 1, West Lafayette, Ohio.

**SELL OR SWAP** — Rider's Vols 1 thru 13, \$25 plus postage. Michael Hubans, 6303 Landover Rd., Hyattsville, Md.

**FOR SALE** — Photofact folders, 1-324 including two Photofact filing cabinets; \$500 cash. Roy O. DeVoe, 7 Beaumont Circle, Madison, Wis.

**FOR SALE** — Heath DX-20 xmitter, excellent cond., with WRL modulator for tone and CW operation, \$49 fob, or express collect. J. Richmond, 2 Hiawatha Rd., Boston 26, Mass.

**WANT FOR CASH** — Hallicrafters Sky Buddy S-19-R or SX 24 or 25. State cond. and price. Harry Register, 25-94 42 St., L. I. City 3, N. Y.

**FOR SALE** — Bendix police xmitter converted to 6 m, complete with PE 103 cables, control box, etc.; Webcor 2030-A Hi-Fi tape recorder, A-1 cond.; German Luger automatic pistol. Best cash offers. Ed Nicks, R 1, Box 169-C, Dubuque, Iowa

**FOR SALE** — 2500 w power plant complete, in excellent cond., \$195 fob; refrig. ser manifold, gauges, hoses, 2-1 tanks and misc. with tool box, \$35, or used rcvr. Robert Schmauss, 3903 Swann Ave., Tampa 9, Fla.

**FOR SALE** — Complete radio control outfit, never used: ECE-T-11 transmitter, Bonner escapement, O.K. Cub .099 engine, "Gazistor" rcvr. with relay (built from kit) less tube and transistor, plus many extras, \$40 cash postpaid. A. A. Saunders, 11 Daniel Dr., Bridgeport 6, Conn.

**WANTED** — Schematics and plans for converters for use with HQ129V rcvr. for all bands from 6 m, 2 m on down. John G. Morrice, 57 Rockaway Ave., Rockaway, N. J.

**SELL OR TRADE** — Rider's TV manuals 1 thru 5, 1 n., \$7 each fob; RCA battery sig. gen., \$10; Hickok 305A scope, \$35; Heathkit scope, push-pull, \$35. N. Denaro, 116-14 120 St., Ozone Park 17, N. Y.

**SWAP** — 93 lessons plus law course by American Extension School for course in either Radio, TV, Electronics, or short-wave rcvr. E. J. Arsenaault, No. Oxford, Mass.

**SELL OR TRADE** — RCA mobile xmitter, carbon mike, 6 v. dynamotor 375 v. output at 250 mls. Interested in medium or low power xmitter; VFO; communications rcvr. N. Preston, 313 East Chicago St., Marceline, Mo.

**FOR SALE** — Hammerlund HQ129X all-band short-wave rcvr., excellent cond., \$125. William Ungvarsky, 157 Hawthorne Ave., Yonkers, N. Y.

**WANTED** — Diagram for Espey 20K o/p multimeter. Sell RCA 17" 2-door console, \$20; Granco UHF converter, \$5. J. Leach, Box 336, Milton, Del.

**FOR SALE** — Rider's Volumes 2, 3, and 8; Rider's TV Vol. 2, 3, 4. Make cash offer or swap. G. Epstein, 200-27 46 Ave., Bayside 61, N. Y.

**WANTED** — PR-9 or similar type police alarm rcvr. covering 152-174 Mc. R. V. Weakley, 141 General St., Providence 4, R. I.

**FOR SALE** — Harvey-Wells TBSS0D deluxe with VFI VFO and power supply, \$100 plus shipping. Want SX42, 43, or equiv. Don H. Miller, 601 Harrison St., Taft, Calif.

**FOR SALE** — 6 v gasoline gen.; SCR 522 with plugs, PE 94B power; BC 611E handy-talky; 100 A Emerson DC gen.; BC 224B; navy LM freq. meter, uncalibrated; Meas. Corp. 78B gen., disassembled. H. McEntee, 490 Fairfield, Ridgewood, N. J.

**TRADE** — ST203 mobile xmitter 10 m, factory wired, with tubes, for Heath DX35 or 40. Arthur Stauch, 541 Princeton Rd., Linden, N. J.

**FOR SALE** — Hammurund HQ-129-X rcvr. in excellent cond., \$125. Bill Burton, 1728 Peach Ave., Memphis 12, Tenn.

**FOR SALE** — 10 w Hi-Fi amplifier good for Hi-Fi phono, compact, gold plate for mounting, \$21. Eastern U.S. only. Gordon Simington, 1520 Field Ave., South Plainfield, N. J.

**FOR SALE** — Sams 2 to 340, broken sequence, \$1.25 each postpaid; ICS servicing course, books, test equipment, tubes, and parts. Send for list. Avon TV and Radio, 57541 Lorie Blvd., Avon, Ohio.


**FOR SALE** — Complete 522 rack mounting 2-meter station, \$37.50; 500 w band-switching 813 CW transmitter less power, \$40; BC221 capacitor, condenser, and gears, \$10. Audio freq. meter with 1000-10,000 cycle scales, \$10. Eggen-sperger, 101 Christie St., Tenafly, N. J.

**FOR SALE** — 200 B G R. variac, \$6 and C G.R., \$10; 420 A W.E. tweeter, \$15. W. Zinsmeister, 146 N. 16 St., Bloomfield, N. J.


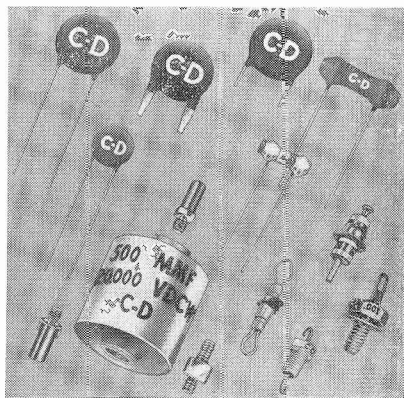
## The Ceramic Capacitor with the "Million Dollar" Body

Over a million dollars was spent to make C-D the only plant in the world in which a ceramic capacitor is completely made from raw powder to finished unit. Scrupulous supervision and control of quality is paramount in the production of a C-D Ceramic. "Quality"—had top priority. The "Million Dollar Body" is proof of the rugged stability, the consistent uniformity and dependable long life of C-D Ceramics. Ask your nearby C-D Distributor for a catalog or write direct to Cornell-Dubilier Electric Corporation, South Plainfield, N. J.



# Cornell-Dubilier capacitors

South Plainfield, N. J.; New Bedford, Worcester & Cambridge, Mass.; Providence & Hope Valley, R. I.; Indianapolis, Ind., Sanford, Fuquay Springs & Varina, N. C.; Venice, Calif., & subsidiary, The Radiart Corporation, Cleveland, Ohio.

# C-D's CUB

## BEST-BAR NONE



### IN MOLDED TUBULAR CAPACITORS

The C-D "Cub" capacitor has proven itself the best on the market today—by out-lasting, out-performing, out-selling any other replacement capacitor for radio or TV. For consistent high quality—always rely on C-D, the only tubulars with the built-in extras required in servicing sets today. That's why distributors *who know*, carry the complete Cornell-Dubilier line.

*\*Special! "Cub-Kit" with bonus plastic service dispenser.*

Ask your C-D Distributor. He's listed in your local Classified Telephone Directory.

*There are more C-D capacitors in use today than any other make*



CONSISTENTLY DEPENDABLE  
**CORNELL-DUBILIER CAPACITORS**

Plants in South Plainfield, N. J.; New Bedford, Worcester and Cambridge, Mass.; Providence and Hope Valley, R. I.; Indianapolis, Ind.; Sanford, Varina and Fuquay Springs, N. C.; Venice, Calif.; and subsidiary, The Radiant Corp., Cleveland, Ohio.