
AMATEUR RADIO,

April 1962 40¢

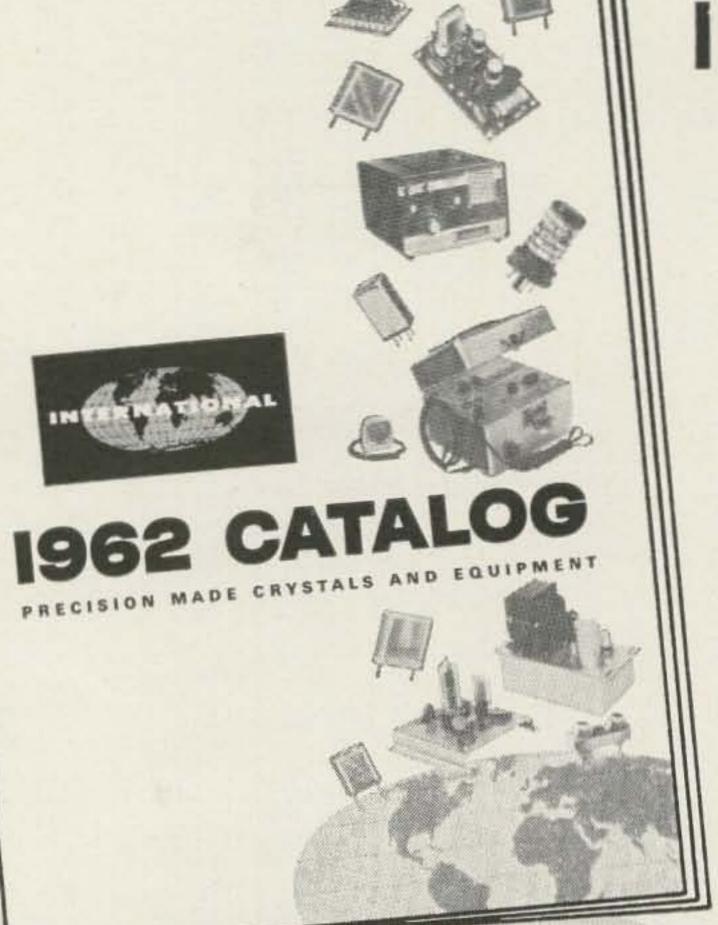

6M SSB Xmtr
Accurate S-Meter
40M ZL Special





INTERNATIONAL 1962 CATALOG

... your buying guide for precision radio crystals and quality electronic equipment ...

- Amateur Crystals
- Commercial Crystals
- Citizens Band Crystals
- Transmitters
- Oscillators
- Converters
- Transistor Subassemblies
- Power Supplies
- Citizens Band Transceivers
- Citizens Band Antennas/Accessories

AMATEURS • EXPERIMENTERS • CITIZENS LICENSEES

Mail today for your FREE copy of International's 1962 complete catalog.

CRYSTAL MFG. CO. INC.

18 NORTH LEE - OKLA. CITY, OKLA.

International Crystal Mfg. Co., Inc. 18 North Lee, Oklahoma City, Okla. Please rush FREE 1962 International Catalog.

Please Print

CITY____ZONE__STATE____

Cover: Design by Bob Kelly K2VLO

1379 East 15th Street—Brooklyn 30, New York

Wayne Green W2NSD—Editor, etcetera	Phone: DE 6-8880	
		6
Six Meter SSB Exciter/Transmitter	soldering.	0
Using a imager loaded whip to improve the sensitivity of your F.S.	M.	4
As the sunspots go, so go the higher bands. Try this 40M amplifier.	Davis Cainas WAAVE	10
13 lests the Poly-Comm 628	Day Dafankann \A/A\A/V\A	12
Polytronics has really done it: six and two in one li'l package. Ham Radio in Finland On the spot reporting.	John Volama OH2VV	10
On the spot reporting.	. John Velamo Orizi V	18
Dot Maker	. James Lee W6VAT	20
An Accurate S-Meter	. Jim Kyle K5JKX/6	22
"You're 80 over nine here, OM." LCU'S Michigan Long Wire		
Interesting 80M antenna. Somebody's always thinking up something	new.	
Station Control Unit	. Ernie Austin W7AXJ	28
Universal Antenna	. John Ellison W6AOI	30
Works on all bands from 160M to 10M and inbetween too. One Tube Vox	Fred Cupp K8AOF	37
Now you, too, can learn to talk steadily to keep the rig on the air.		
Quartz Crystal Checking Wee gadget to check frequency and activity of your quartz chips.	Adam McLaren W¢CGA	
Before the Breadboard	. Staff	40
Transistorized Cathode Modulator	Burt Yellin K2STV	46
Kilowatt transistorized modulator. Let us know if it works.		
AGC for the Swan Transceiver		
18 watt rig for 160M. Let's get more activity up there. And more	. Carl Martin K9PAL	52
Improve Weak Signal RTTY Reception	. Woody Davey W7CJB	54
We may eventually run a new TT converter every month. This one Pre-Amp Curve Shaping	looks good.	56
Getting a lot more nunch out of the crystal mike preamp		
BC453 Conversion	. Dick Gridley K6JHJ	58
Linear Scope Monitor	. John Reeder WøMWJ	62
Linears are hard to adjust sometimes, this sure helps. FM to AM	Roy Pafenberg W4WKM	64
Quick conversion for surplus FM gear.		
The Band Warmer	Louis Huffon WΦKQF	66
Propagation Charts	. Dave Brown K21GY	
Precision Measurement for the Amateur	. Roy Pafenberg W4WKM	72
W2SKE/MM (Mobile Motel)	. Bill Leonard W2SKE	78
73 Tests the Heathkit IM-10 VTVM	Don Smith W3U7N	81
Nice.		
	k Meter	
Letters	e Calibration 67	
	Plugs 84	000
Associate Editors:		
Western Representative: Jim Morrisett WA6EXU, 2103 India S		
C D : I D I K II KOVI O		

73 Magazine is published monthly by Amateur Radio Publishing, Inc., 116 Main Street, Norwalk, Connecticut. Please note that the address of the business office where you are to send all correspondence, subscriptions, submitted articles, etc., is at the top of this page. The telephone number is there too and we dare you to try to get it from the phone company. Subscription rates, while covered rather completely in the regular subscription ad, are: U.S.A. and possessions, APO, FPO, Canada and Mexico; one year for \$3.50, two years \$6.50, three years \$9.00. Foreign: One year \$4.00. Second class postage paid at Norwark, Connecticut and other offices. Printed in the U.S.A. Entire contents copyright 1962 by Amateur Radio Publishing, Inc. Postmaster: Please send form 3579 to 73 Magazine, 1379 East 15th Street, Brooklyn 30, New York.

. de W2NSD

. . . never say die

Columns

We have, so far, been able to keep successfully away from running any regular monthly columns. The thinking behind this, as you probably know, is that while most columns start out to be very interesting, after a while the authors run out of ideas and things get pretty dull. Of course there are several general types of columns that are presently available elsewhere . . . there is the operating news type thing where you can look up and see what has happened in your own special interest of late. One drawback of this type of reporting is the two months delay in getting the news in print that is part and parcel of publishing a monthly magazine. By the time you read about a DX pedition it is all over, etc.

A second type is the "listing of calls" style of column which attempts to get as many calls in print as possible on the premise that people like to see themselves in print. Unfortunately this makes terribly dull reading for everyone else. A third (very rare) type of column is that devoted to technical matters. Something like this would be printed in 73, were it to be submitted as individual articles.

Then along comes something like this Ham-TV, which has quite a need for a lot of communication between the interested parties. A monthly column would be a big help for the fellows getting on TV. But, again, it would be pretty dull stuff for all the other readers. The obvious answer to this is a monthly bulletin. Something like this can be printed inexpensively and fast, getting the information out in a matter of days instead of months. We could provide an eight page monthly (six to twelve a year) bulletin to all subscribers to 73 who pay one extra dollar per year. Since we are so well set up for producing things like that I think we could split the dollar with whoever was editing the bulletin, giving him a little incentive. While this wouldn't amount to much over \$500 to \$1000 a year, it still isn't a bad deal for a part time project.

We are all set for the Ham-TV bulletin, I believe. Mel Shadbolt, the author of our Ham-TV Manual, has been so swamped with requests for information on who is getting on where and with what that he has offered to take on the job of turning out a bi-monthly

bulletin for the TV-ites.

This still leaves several other special interests that could well use some better communications. The moonbouncers and other UHF'ers sure do need some coordinating. I haven't seen anything national in the way of a traffic bulletin, but then maybe there aren't enough fellows interested in having one. There used to be a fine RTTY bulletin, but I haven't seen one of those for over a year now, which leaves another field wide open. The DX Bulletin by Don Chesser is doing a fine job, but perhaps there is a need for a lower cost monthly bulletin in this field. You can probably think up a lot more that would serve a useful purpose.

If you are seriously interested in editing a monthly bulletin for some special interest and you have the experience to know what you are talking about in that field, then maybe we can get together. We can shoulder the entire cost of printing and mailing the bulletins if you can provide us with the manuscript all set to be printed each month on a fixed immutable schedule. We can advertise the bulletin in 73 and charge one dollar per year for it, sending you one half of the receipts as your payment. Sure, we'll lose money on the deal, but it'll be a valuable service and it will be worth it. If all this sounds reasonable and you want to sign over your soul to the publishing field, then drop a line.

Navassa Island

Back in 1958 a group of us got together and had a little DXpedition to Navassa Island, using the call KC4AF. This was probably one of the most successful DXpeditions in history,

Air Force Mars Technical Forum

Sundays: 2-4 PM EST 3295kc-7540kc-15,715kc

April I—Advantages of compactron multi-function tubes in electronic equipment.

April 8—What computers can do.

April 15—Latest trends in military type transistors.

April 22—Transistorized citizens band transceivers.

April 29—Use of transistors as high power amplifiers and oscillators.

LAFAYETTE RADIO

AMERICA'S HEADQUARTERS FOR HAM EQUIPMENT

THE LAFAYETTE HE-30

Professional Quality Communications Receiver





TOP VALUE COMMUNICATIONS RECEIVER

in Kit Form



TUNES 550 KCS TO 30 MCS IN FOUR BANDS

BUILT-IN Q-MULTIPLIER FOR CROWDED PHONE OPERATION

 CALIBRATED ELECTRICAL BANDSPREAD ON AMATEUR BANDS 80 THRU 10 METERS . STABLE OSCILLATOR AND BFO FOR CLEAR CW AND SSB RECEPTION . BUILT-IN EDGEWISE S-METER

Sensitivity is 1.0 microvolt for 10 db, Signal to Noise ratio. Selectivity is ± 0.8 KCS at -6db with Q-MULTIPLIER. TUBES: 6BA6-RF Amp, 6BE6 Mixer, 6BE6 OSC., 6AV6 Q-Multiplier-BFO, 2-6BA6 IF Amp., 6AV6 Det-AF Amp. ANL, 6AQ5-Audio output, 5Y3 Rectifier.

TUBES AND RECTIFIER TUBE . BUILT-

IN "S" METER WITH ADJUSTMENT CONTROL . FULL COVERAGE 80-10 METERS . COVERS 455KC TO 31 MC . VARIABLE BFO AND RF GAIN CONTROLS . SWITCHABLE AVC AND AUTOMATIC NOISE LIMITER

The Communications Receiver that meets every amateur needavailable in easy-to-assemble kit form. Signal to noise ratio is 10 db at 3.5 MC with 1.25 microvolt signal. Selectivity is -60 db at 10 kc, image reflection is -40 db at 3 MC. Tubes: 3-6BD6, 2-6BE6, 2-6AV6, 1-6AR5, 1-5Y3.

- Highly Sensitive Superheterodyne Receiver Section for 50-54 Mc
- Effective Series Gate Noise Limiter
- 3-Stage, 12-Watt Transmitter with 2E26 Final
- Illuminated Panel Meter for Plate Current and "S" Readings
- Pi-Network Transmitter Output
- Built-in 117 VAC and 12 VDC Power Supplies
- Push-To-Talk Ceramic Microphone

Provides maximum convenience and flexibility in either mobile or fixed operation.

LAFAYETTE HE-50 10-METER TRANSCEIVER

Similar to above except for 10 meter operation



LAFAYETTE HE-29A

9-TRANSISTOR C.B.

HE-29A

NO MONEY

"WALKIE TALKIE" 39.95 2-For-78.88

- 9 Transistors plus Diode and Thermistor Transmits and Receives up to 1.5 Miles Crystal Control on Transmit and Receive
- Uses Inexpensive Penlight Batteries
- 46" Telescoping Antenna
- Push-To-Talk Operation
 - Complete With Leather Case, Earphone, Batteries and Crystals for Channel 10

LAFAYETTE 6 - METER VFO

- Highly Stable Oscillator Circuit
- 8 MC Output
- Illuminated Dial 50-54 MC Range
- Fully Wired Not a Kit

ONLY NO MONEY

DOWN

Made in U.S.A. HE-61




LAFAYETTE RADIO, DEPT. 73D-2 P.O. BOX 10 SYOSSET, L. I., N. Y.

Send FREE 1962 340 page Catalog 620 featuring the full line of Lafayette Amateur Equipment

enclosed for Stock No..... Name

Address

City_____Zone State

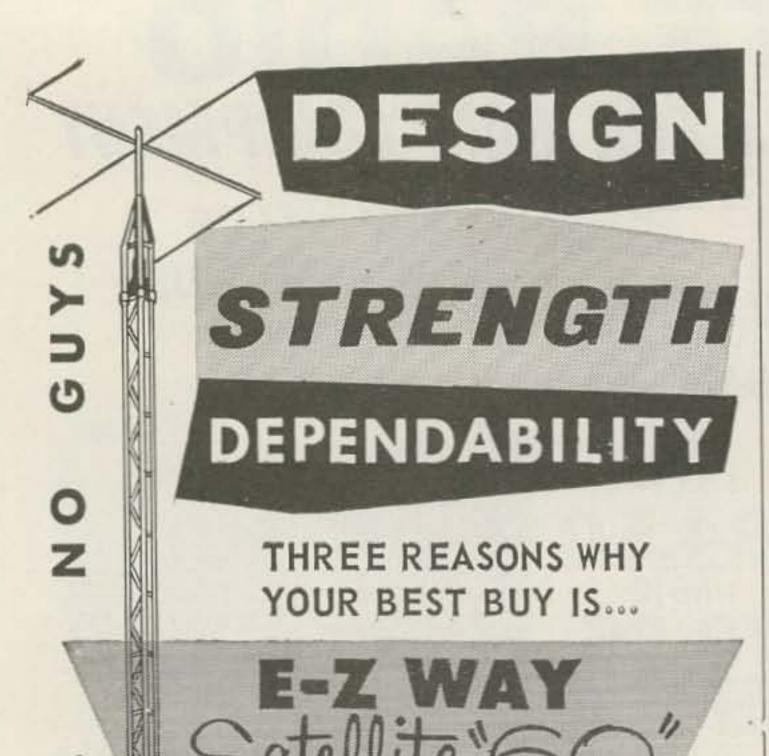

E-Z WAY AERO-DYNAMIC design decreases wind load and provides telescoping action that permits raising and lowering of tower sections.

CRANK UP TO 60 FEET, DOWN TO 25 FEET and TILTS OVER FOR ACCESS TO ROTOR OR BEAM.

STRENGTH is built-in to every E-Z Way Tower...Heavy wall steel tubing legs, continuous diagonal bracing of solid steel rod and electric-cally welded throughout....no loose bolts or nuts here. E-Z Way design and strength are your assurance of DEPEND-ABILITY that you can count on year after year. See your nearest distributor today or write for free literature.

The SATELLITE

Model RBX-60-3P (Painted) \$335.00 Model RBX-60-3G (Galvanized) \$410.00

MOUNTING KITS:

GPK X60-3 (Ground Post) \$125.00 BAK X (Wall Bracket) \$17.00 Freight Prepaid anywhere in (48) U. S. A.



with over 7000 contacts made in just four days of operating. The six of us that went on the trip had quite an experience. The trip was exceedingly difficult and very expensive by our standards. The main things left over from the trip at this late date are fond memories of the hardships and fun and the pictures we took at the time.

When I left CQ Magazine back in January 1960 my entire collection of slides of the Navassa trip were on loan to a radio club, along with a tape recorded commentary. These were returned to CQ later and I have so far been unable to get them back. I would like to be able to again enjoy the slides of this trip and perhaps be able to show them at occasional ham clubs and conventions. They are good and they are interesting. Perhaps if you would help me in this matter we could influence the Publisher: S. R. Cowan, the Acting Publisher: Richard Cowan, or the Production Manager: Cary Cowan, that it would be the fair thing to return these slides. If you just drop any of them a QSL card with a note at 300 West 43rd Street, New York 36, we might get some action.

How To Help

Many subscribers have written in to ask what they can do to help boost 73. There are two necessary ingredients to the success of 73: readers and advertisers. Anything you can do to help with either of these departments will be greatly appreciated and will result in a bigger and even better magazine. There sure is a lot yet to be done in both of these directions.

In the readership end of things there are few fellows who have not by now at least heard about 73. There are still a lot that are not subscribing. This can be attended to at your club meetings (we have special subscription rates for five or more received at once: 50¢ off on each subscription) where the subject can be broached regularly until resistance wears down and the pinch-penny members part with their worn faded dollar bills. Many articles in 73 make fine discussion on the air and who knows, you might convert someone from Brand X. With a little persistence you can easily brainwash several unsuspecting fellows a day.

You might keep a sharp eye on the advertisers and encourage new companies with re-

(Turn to page 86)

CERAMIC HAM JEWELRY

Beautiful custom stamped, hand painted, permanently fired "Call Bars" or "Handle Bars" (limit 6 letters). Lapel Pin \$1.50, alligator Tie Clasp \$2.00, matched pair \$3.00 (plus 10% Federal Excise Tax). Please allow 4 - 6 weeks for delivery.

DONNA'S CERAMICS

P. O. BOX 111

SYLVANIA, OHIO

4

ш

00

Z

4

8

2

-

Feature Packed! The three hottest transmitters on the air!

• INVADER • INVADER 2000 • RANGER II

INVADER—More exclusive features than any other Transmitter/Exciter on the market today! Specially developed high frequency, symmetrical, multi-section band-pass crystal filter for more than 60 db sideband suppression—more than 55 db carrier suppression! Instant bandswitching 80 through 10 meters—no extra crystals to buy—no realigning necessary. Delivers solid 200 watts CW and P.E.P. SSB input; 90 watts input AM. Built-in VFO—exclusive RF controlled audio A6C and ALC (limiter type) provide greater average speech power. Wide range pi-network output circuit—extremely smooth VOX and anti-trip circuits. Fully TVI suppressed. Self-contained heavy-duty power supply. Wired and tested with tubes and crystals.

Cat. No. 240-302-2-Amateur Net \$619.50

HIGH POWER CONVERSION—Take the features and performance of your "Invader" . . . add the power and flexibility of this unique Viking "Hi-Power Conversion" system . . and you're "on the air" with the "Invader 2000". Completely wired and tested, includes everything you need—no soldering necessary—complete the entire conversion in one evening.

Cat. No. 240-303-2-Amateur Net \$619.50


INVADER 2000—Here are all of the fine features of the "Invader", plus the added power and flexibility of an integral linear amplifier and remote controlled power supply. Rated a solid 2000 watts P.E.P. (twice average DC) input on SSB; 1000 watts CW; and 800 watts input AM! Wide range output circuit (40 to 600 ohms adjustable). Final amplifier provides exceptionally uniform "Q". Exclusive "push-pull" cooling system. Heavy-duty multi-section power supply. Wired and tested with power supply, tubes and crystals.

Cat. No. 240-304-2-Amateur Net \$1229.00

RANGER II—Now—a new version of the popular 75 watt CW or 65 watt AM "Ranger". The "Ranger II" transmitter also serves as an RF/audio exciter for high power equipment. Completely self-contained instant bandswitching 160 through 6 meters! Operates by built-in VFO or crystal control. High gain audio-timed sequence keying, TVI suppressed. Pi-network antenna load matching from 50 to 500 ohms. With tubes, less crystals.

Cat. No. 240-162-1 Viking "Ranger II" Kit—Amateur Net . . . \$249.50

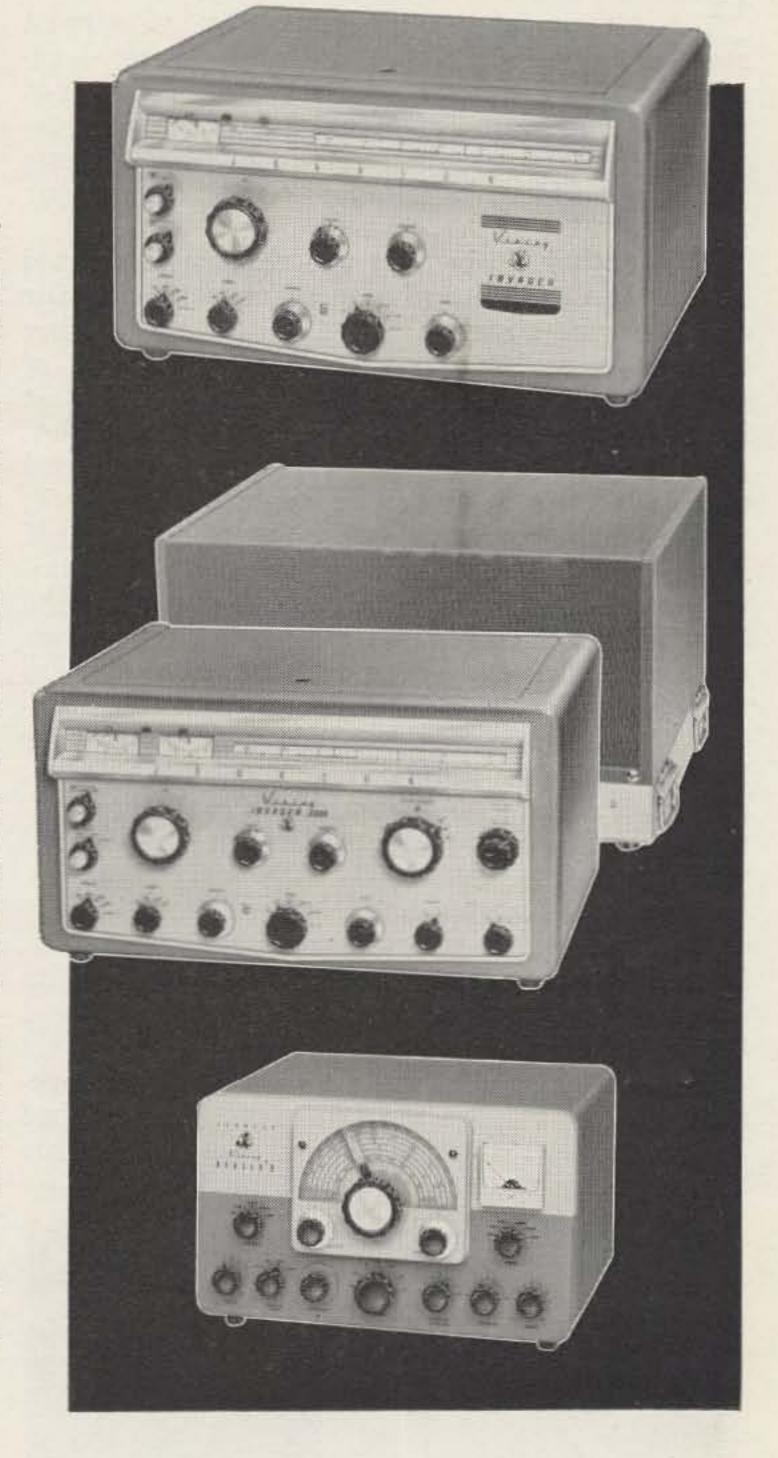Cat. No. 240-162-2—Viking "Ranger II"
Wired and tested—Amateur Net \$359.50



FREE New Catalog Write today for our newest amateur

Write today for our newest amateur Catalog! Available now...contains photos, schematics and detailed specifications!

FIRST CHOICE AMONG THE NATION'S AMATEURS



E. F. JOHNSON COMPANY . WASECA, MINNESOTA

Six Meter SSB

Dyess AFB, Texas

139 Nebraska Road

Photos by Ben Head K5HWF

Capt. John J. Sury W5JSN/K8NIC

Exciter/Transmitter


HAVE you been thinking of getting on side-band on six, but financially it almost seemed impossible. Now is your chance—especially the Technician who probably does not own a HF sideband exciter—to go with a transverter. Quite an investment is involved in our modern exciters available on the amateur market.

The author feels that the exciter presented here is the minimum he could construct as for cost, but the effort is a little bit more. During the design and construction stages, several of the circuits have been modified or remodified at least a dozen times. It is about the most simplest that could be built and still give good quality sideband, either upper or lower.

Most builders have quite an assortment of junk—resistors, capacitors, tubes, transformers, etc.—and from this assortment plus the bargain basement electronic parts this exciter can be fabricated. The most expensive item in the exciter is the B&W type 2Q4 model number 350 plug in phase shift net. The other larger items are the 2E26 or a 6146 if you desire it, 1:3 step up transformer, and two universal audio output transformers rated at 4 watts each.

Since the 6 meter band is dead in this part of the country only local checks could be made. The exciter was complimented in every case. Its output is approximately 5 watts PEP using a 300 volt 200 ma. power supply.

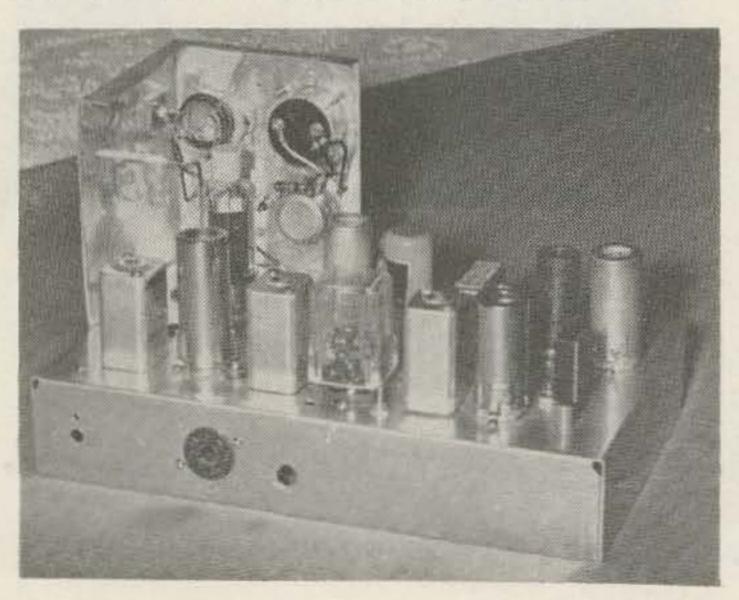In this article a suggested lay-out is presented. The author used it with success, but it is not what could be called beautiful. This was strictly an experimental model.





No hetrodyning is done in this exciter. It is strictly a straight thru type. Starting with an 8 mc. rock, using the third overtone and doubling it into the balanced modulators. (Refer to block diagram.) The balanced modulator was constructed in a plug in the eight pin octal accessory case. Refer to sketch for pins that the 1N34's are soldered to. This method was used because of the natural shielding and that various types of diodes could be tried without disturbing the other wiring. The bargain 10 for \$1.00 diodes were tried and they worked fine.

Three slug-tuned ceramic coil forms with aluminum shields were used for L₂L₃, L₅ and loop, and L₆L₇. L₄ is a standard % coil form tuned to the desired frequency. The ceramic coil forms can be obtained from Burstein-Applebee, part number 18B120 for less than a half dollar each. They can be dismantled for rewinding your own coils. The coil forms are ½ inch in diameter.

Let's get with the building of the exciter. Each section of the exciter will be described separately except for the chassis. Refer to the lay-out drawing and photographs for location of components. Cut all holes in the chassis and install all sockets.

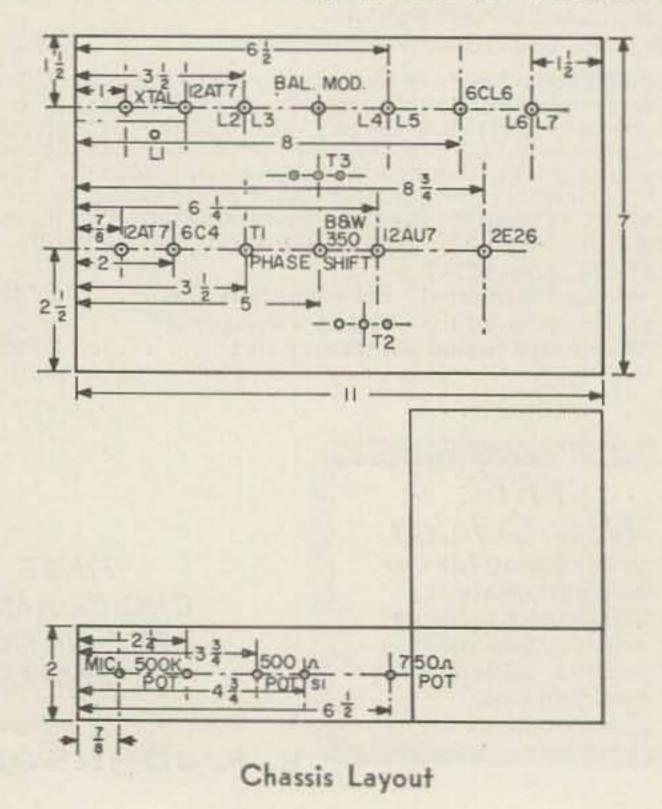For L₁ a % inch ceramic slug tuned coil form coil was used. Wrap 22 turns of #24 beldenamel wire closely wound over the form.



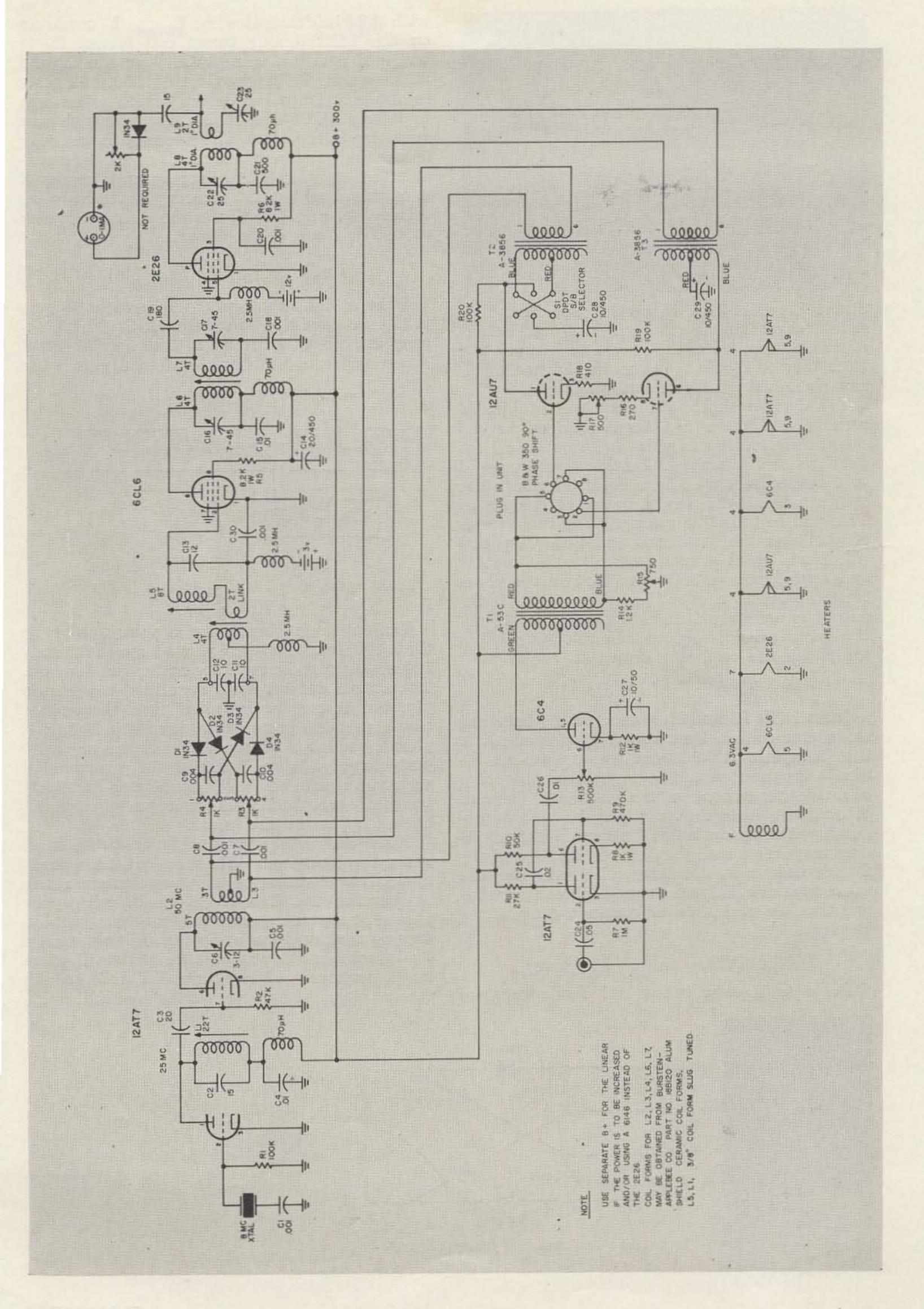



Shunt L₁ with C₂ a 15 mmfd capacitor. This should cover between 25 and 25.5 mc. Follow schematic and wire the oscillator. Apply 300 volts thru a 70 uh choke to the bottom of L₁

and check the oscillator output.

The doubler should come next. If a shielded ceramic coil form has been obtained as described above, disassemble and remove all capacitors and windings. Rewind five turns of #20 beldenamel wire in a location where the slug can be all the way in or out of the winds. This will be your fine tuning. Wind three turns of #24 over the five turns and center tap this which will go to ground. Assemble the doubler and apply voltage 300 volts. Locate the three turns up or down over the five turns until the output is near equal at both ends of L₃. Check the output with a vacuum tube volt meter. This completes the oscillator sections.

Balanced Modulators

Install 1K, R₃ and R₄ pots near the balanced modulator socket. Fabricate the modulators in the Lafayette RY-262 equipment case as indicated in the figure. The modulators may also be made permanent in the exciter if desired. The author feels that the plug-in type of assembly is more desirable, because different diodes may be checked for best results. L₄ and the 2 turn link is on the same coil form. Use the same type of coil form as the doubler and wind one turn on each side of center tap of L₄ for the link.


6CL6 Driver and 2E26 Linear

L₅ is a % slug tuned coil form wrapped

with #24 beldenamel wire. L₆ and L₇ made up on the 18B120 slug tuned coil forms. L₇ is wrapped over L₆, using #20 wire for L₆ and #24 wire for L₇. Approximately 300 milliwatts is obtained from the driver, which is enough to drive a 2E26 or 6146. No neutralization was needed with the 2E26. The linear indicated may be used or your own design. L₅ and L₉ are constructed of #14 solid wire; enamel insulated wire was used for L₉. Mercury batteries were soldered in permanently in the circuit for bias on the driver and the linear.

Audio and Phase Shift Net

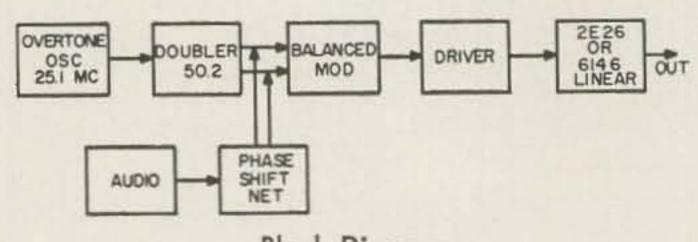Wire as indicated on the schematic and no problems should be encountered. S₁ DPDT selects the sideband desired. The plug in B&W phase shift net is a jewel and really does the job.




Block Diagram

Power Supply

The only requirement for a power supply is that it delivers 300 v B plus at approximately 180 ma. and of course 6.3 v ac for the filament. The author did not use a regulated power supply, but it can be expected that the exciter would perform better with one. If a higher B plus is used it is recommended that a separate plate supply be used and a 300 v regulated supply. Refer to the Radio Amateur's handbook for plate, screen and bias voltages when using higher B plus on the linear.


After completing the construction check all wiring, making sure that no mistakes were made. If everything checks good you are ready to fire her up. Use an rf probe with your vacuum tube volt meter in connection with a dummy load to tune and peak up the exciter. To inject a carrier unbalance the modulators and a low level will be obtained. This is enough for peaking. With the power applied adjust R₁₇



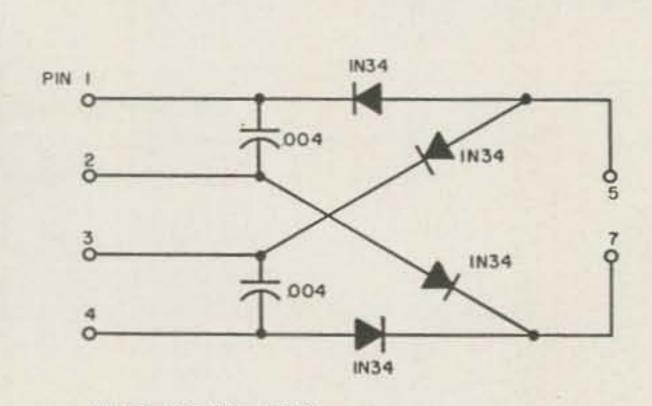

PINS . 6 8 8 NOT USED.

Balanced Modulator

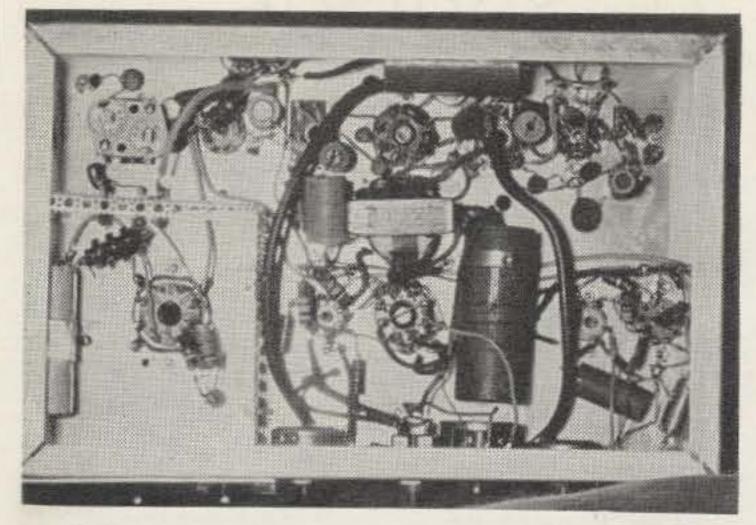


until both plates of the 12AU7 are approximately 175 volts. When the modulators are balanced, the carrier should drop almost to zero. Using an audio oscillator or a mic, adjust R₁₈ and R₁₅ for quality; you may check this on your receiver. Watch the meter swing up when modulating. To get a real check of the exciter put an SWR meter in your antenna line and check with your buddies for best settings of R₁₈ and ₁₅. Good luck during next summer's Sporadic E season. Give me a call. ... K8NIC

Field Strength Meter for 6 and 10

Allan Schechner W3YZC

field strength meter doesn't have to have transistors or tunnel diodes to be sensitive. Just observing a few basic principles such as tuning and matching helps. Most hams are familiar with the timeworn field strength meter circuit using an rf choke, diode and a milliameter; in fact it is probably the most commonly used type. With this arangement, however, there is a large mismatch between the low impedance meter and the whip antenna. Not only that, the meter will respond to spurious frequencies. This meter incorporates an antenna "loading coil," which in one fell swoop tunes and matches the circuit, and effectively lengthens the antenna. The secret is that the coil is constructed by "cut and try" so that it

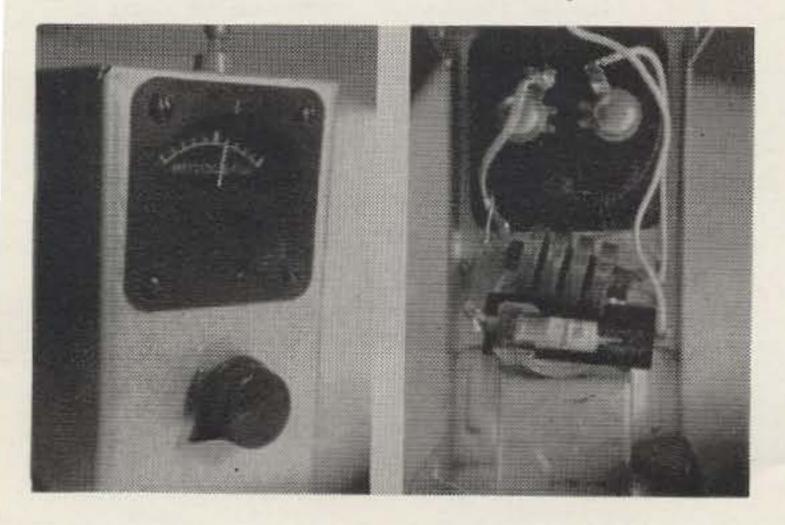

matches the builder's particular circuit.

Using a surplus 500 microamp meter commonly available for \$1.75, the circuit is wired as in Fig. 1. This wiring is not critical as to layout; winding the coil is.

Cement a seven inch length of #12 tinned wire into the body of a banana jack by first forming a loop in the wire to obtain a pressure fit. Drill a 1/64 inch hole as in Fig. 2 and fish the end of a five foot length of #24 enamel wire into it. Solder the end of the wire to the metal part of the jack and screw this part into the plastic, while twisting the wire

in the hole to take out the kinks.

Start the winding with 45 turns, which should take you to the end of the plug and tap solder the wire to the antenna. Loosely couple a grid-dipper to the coil and check frequency. Remove two turns at a time until you hit 29 mc. First check the grid-dipper with a communications receiver to be sure you know where 29 mc is with some degree of accuracy.

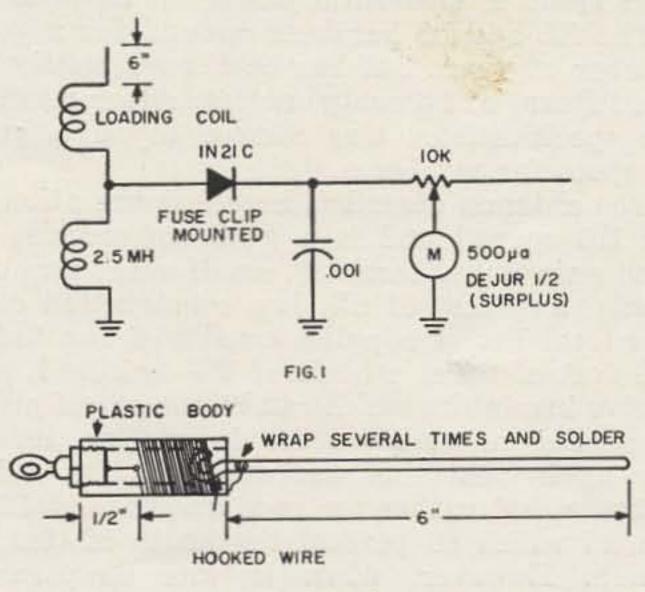


FIG 2

During the coil pruning operation, the griddipper should be far enough from the F.S.M. so that only a slight indication is noted on the microammeter. This prevents detuning of the loading coil. When the coil is completed, permanently solder the end of the winding to the antenna, covering the whole assembly lavishly with coil dope.

After completing the electrical portion the author found that an Ajax magnetic door latch could be fastened into the bottom of the case. This allows the tiny meter to be firmly attached to metal surfaces such as the roof, trunk or dashboard of a car. Cut a 5/16 inch by 1% inch slot as indicated for the magnet to protrude through the bottom and cover this with a thin piece of tape to protect it from scratching.

By removing more turns the unit will operate on six meters. Using the banana jack makes it convenient to construct a set of antennas. Start with thirty five turns for the six meter winding. When in use, you will almost certainly find a need to use gain control R₁ to reduce sentitivity. ... W3YZC

Forty Meter ZL Special

Doug Gaines W4AXE 2323 S. E. 11th Street Gainesville, Florida

A FTER struggling through the morass of commercial broadcast stations around 7135 kc to copy the Florida RTTY Emergency Net one Sunday afternoon, I staggered out of the shack swearing never again. Unless you've had the experience of being kicked in the head by several foreign soap operas crying to the tune of 50 kilowatts or so each, it's hard to imagine the exasperation involved in trying to work RTTY on forty from this location. As I had the coverage of Florida primarily in mind, and the working of stations on the Eastern Seaboard as a second consideration, I decided that a fixed antenna with good forward gain and high front to side ratio would fill the bill.


The ZL special has been around for a good number of years but has been used mostly on ten, fifteen, and twenty meters. After reading the specifications, this seemed to be a good

prospect for my beam.

The antenna described here is a variation of the ZL special and is a good compromise of good gain and directivity, small space requirements, and best of all, low construction cost. The total list of supplies consist of two 2x2's, 300 feet of wire, a hank of TV twinlead, and twelve insulators which can be cut out of plexiglass. Before we begin the description, let me say again that this was not built for a DX antenna, but rather for good coverage of Florida, of which 80 percent lies south of this location. However, when it was temporarily raised to sixty feet, the first contact was in South America.


Basically, the antenna is a pair of folded dipoles fed 135° out of phase. The ends of the elements are drooped downward to form a pair of inverted V's hung from a common boom. All wires on each side of the boom are in the same plane, resulting in the whole array looking something like a four element beam.

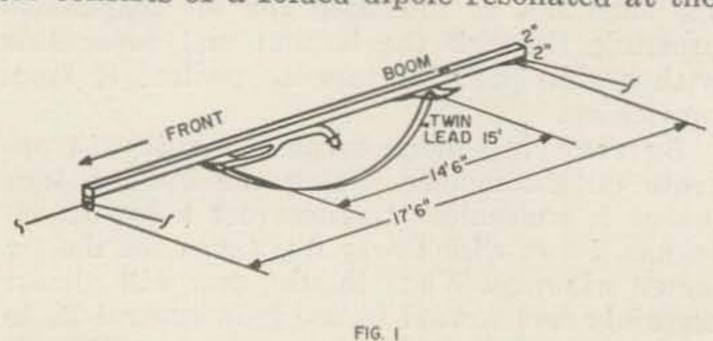Construction begins with the boom which can be of either wood or tubing cut to 17 feet 6 inches. I used two 2x2's butt-jointed and reinforced at the center to reduce sagging. Insulators were fastened at each end and at 18 inches in from each end as shown in Fig. 1. The director consists of a folded dipole resonated at the




desired frequency. The reflector is cut about 8 percent longer until the antenna is raised and tuned. Between the feedpoints of the two elements, a length of 300 ohm TV lead-in is connected with a half twist for the phase shift. This lead-in handles my kilowatt okay in this application. The feedline is connected at the feedpoint of the director. With the dimensions given for 7140 kc or using the formulas in Fig. 2 for other frequencies, the impedance is close to 75 ohms. I played around with 75 ohm twinlead and baluns for my transmitter. Needless to say, bandswitching became a dismal affair. In desperation, I tied on RG-11, and, wonder of wonders, it worked! The pi-network of my linear was quite happy with the new load.


The end wires of the director were adjusted in and out until a low point was found in the SWR at the desired frequency. When the best point was found, the wires were soldered in place. The reflector was tuned in the same way for maximum gain, using a field strength meter. This was done with the boom raised to its permanent height and the elements stretched out to their approximate tie points. At this location, the apex of each V is at 40 feet and the apex angle is 60 degrees. Sharper angles tend to decrease the usable bandwidth and directivity. As this angle is decreased, a point is reached where the array becomes too critical to tune. This point seems to be at an angle of 30°.

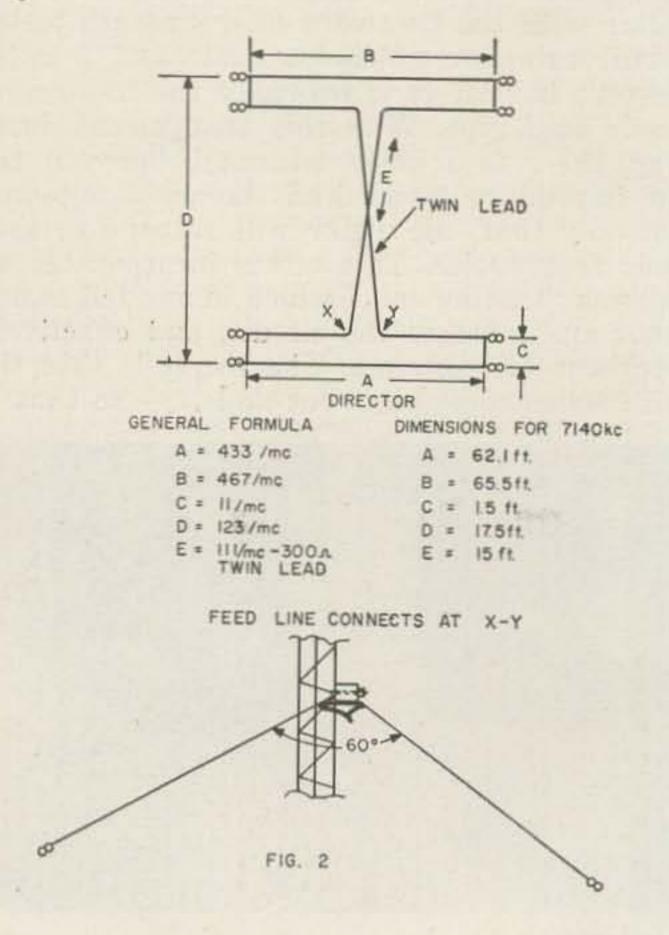

175 WATTS SSB ON SIX METERS

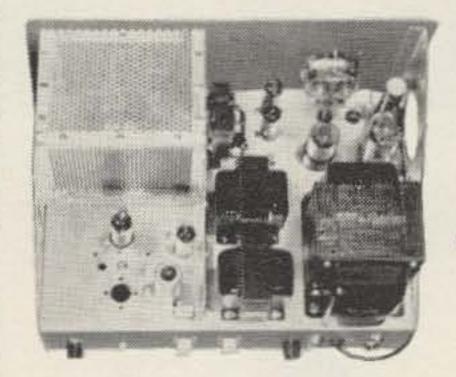

P & H 6-150 TRANSMITTING CONVERTER

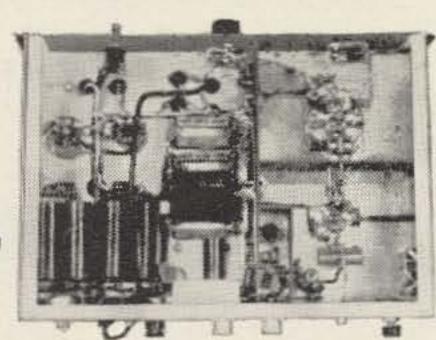

Here's the simple, easy way to go VHF on SIX METERS! Just feed the 20 meter output of your present SSB, AM or CW exciter into the P&H 6-150 and you have 175 Watts PEP on SIX METERS, either crystal or VFO controlled, depending on your exciter features. Resistive Pi-Pad and switchable Half-Power Pad permits operation with any 5 to 100 Watt exciter. Since the 6-150 is a high stability mixing device, the output signal stability is the same as that of your exciter. Uses a 6CX8 crystal oscillator/Class A buffer; a 6360 Balanced Mixer and a NEW AMPEREX 8117 push-pull output tube. Power input to 8117 final: 175 Watts PEP on SSB, 165 Watts

Complete — With Built-in Power Supply, All Tubes and Crystal, for Only \$299.95

WRITE FOR LITERATURE

CW, 90 Watts linear AM. Entire chassis and all shielding is COPPER PLATED. Output jack provided to furnish oscillator signal injection for receiving converter. Quiet 200 CFM forced-air cooling. 50-70 ohm input and output impedances. Husky built-in power supply has three separate rectifiers and filter combinations. Meter reads; PA GRID, PA PLATE and RELATIVE RF OUTPUT. Modernistic curved corner grey cabinet; 9" X 15" X 10½". The P&H 6-150 is so thoroughly shielded, by-passed and parasitic-free that it operates as smoothly as an 80 meter transmitter. COMING SOON! THE P&H 2-150 FOR TWO METERS!




This is a simple antenna to build if you have a structure such as a pole, tree, or tower that can support the boom at 30 feet or more. 40 feet seems to be a good height for working stations out as far as 400 miles. The labor is well worthwhile when the performance is considered.

I checked gain against my dipole, which is 20 feet higher than the beam. When transmitting, forward gain to stations 100 miles or closer is about 6 db better than the dipole. On longer hauls, it is closer to 10 db as reported on good receivers, such as 75A4's, HQ-180's, 75S-1's, etc. On receive, a real mystery pops up. When I switch from the dipole to the beam, signals from the South jump at least three S-units. This dipole is a good one, too. The high readings may be due to a greatly different radiation angle or to the presence of obstacles in the field of the antennas. I think that a more likely reason is the same thing that makes the cubical quad and dual-diversity beam such good receiving antennas. All have a large cross-section and each has nearly an equal proportion of vertical to horizontal components. Front to side ratio is about 25 db measured with a field strength meter. Front to back was purposely kept low, as I did not want to lose northern stations. Stations to the East and West are down far enough to make forty meters much more comfortable to work.

So, fellows, let's don't let forty fall by the wayside as a reliable band because of small


space. This antenna can take up almost as little space as a full sized twenty meter beam and is still full sized on forty. Don't be persecuted by Russian propaganda stations or get involved in John Loves Mary in Spanish. Put up the Inverted-V ZL-Special and live! ... W4AXE

A Grabber

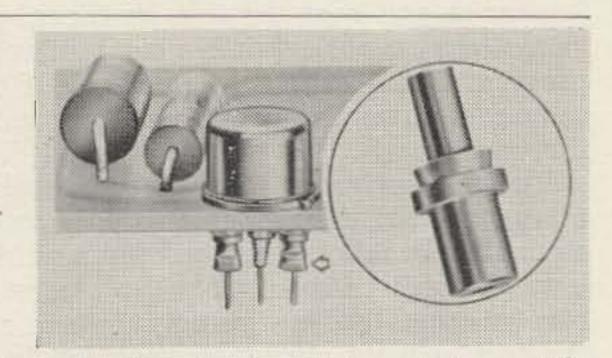

Soldering leads shortens transistors life. Heat sinks, often not infallible, necessitate undesirably long transistor leads. What do we do? We build transistors, beautiful little gems, expensive little gems. Then we blithely ruin them by the thousands trying to solder them into the circuit. The solution? Classically simple. Don't solder transistor leads. Insert and solder special crimpable eyelets in the circuit. Then slip the transistor leads thru these and crimp, giving a positive electrical connection and the shortest one possible. I know. I should have thought of it, too. Vector has them all ready to go. They're called TRANSCRIMPS, available from Vector Electronics, 1100 Flower St., Glendale 1, Calif.

73 Tests the Poly-Comm 62B

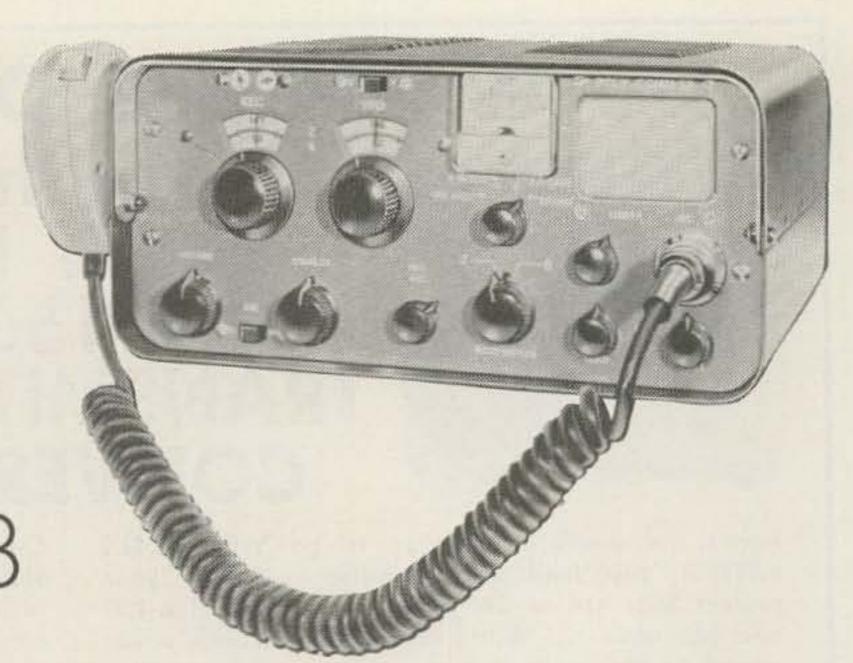

6 & 2 Meter Transceiver

Roy E. Pafenberg W4WKM

A strong newcomer in the VHF equipment field is the Poly-Comm Model 62B, 6 and 2 meter transceiver. This compact little unit is designed for mobile and home station use, containing a universal power supply for both modes of operation. Study of the specifications will show that the manufacturer, Polytronics Lab Inc., really took on a task in designing the unit.

This transceiver proved to be very difficult to evaluate. The time proven approach is to compare any new equipment with the competition in the areas of features provided, performance and cost. In this instance, the usual yardsticks do not exist. No competitive product provides 6 and 2 meter coverage, self contained universal power supply and self contained VFO for both bands.

The photo shows the external details of this attractive little package. A universal mobile mounting bracket, provided but not shown, allows the unit to be mounted in almost any mobile location. Before going into the results of the test, a brief circuit description is in order. Reference to the block diagram and the specifications will assist in understanding the following discussion.


The receiver section, designed for AM reception only, consists of a 12 tube superheterodyne circuit using triple conversion on 2 meters and double conversion on 6 meters. A high gain, cathode coupled, dual triode rf stage works into a Nuvistor first mixer. A 94 mc, crystal controlled Butler oscillator supplies the injection signal. On 6 meters, the oscillator is disabled and the signal idles through the first mixer. A voltage regulated, Colpitts oscillator, operating at 46.595 ±2 mc is used to supply injection to the second mixer. The oscillator resulting in a second if frequency of 5.405 mc. A stage of amplification follows, feeding the third mixer. Here, a 4.95 mc crystal oscillator is used to produce the final 455 kc if frequency. Two stages of 455 kc amplification are used to obtain the desired selectivity.

It will be seen that the rf-if portion of the receiver section is essentially a good design, double conversion 6 meter receiver with a high performance, crystal controlled converter used to provide 2 meter coverage. The results are very good and actual tests show that the claims of image rejection and selectivity are actually exceeded in production. The price paid for this superior performance is the presence of the two spurious responses pointed out in the specifications.

Silicon diodes are used in the detector, AGC delay and ANL circuits to provide excellent, hum-free performance. A dual triode is used in the squelch and first audio stages which drive the parallel connected 6BQ5 audio output tubes. These tubes, which are also used as modulators in the transmit condition, drive an internal 2½" PM speaker. Rear-chassis terminals are provided for use of an external speaker if desired.

The 62B transmitter section is more or less conventional except for the inclusion of the internal two band VFO. A switch permits selection of the VFO or a front panel mounted crystal. The oscillator frequency is tripled in the plate circuit and feeds a frequency doubler, driving the 7551 output stage on 6 meters. An additional tripler stage is switched in to give 2 meter coverage. The modulator consists of a high gain pentode followed by a triode which drives the 6BQ5 modulator tubes. The ceramic microphone supplied with the transceiver is and second grid mixer circuits are gang-tuned, matched to the speech system for optimum re-

BULSEYE BUYS ROWS

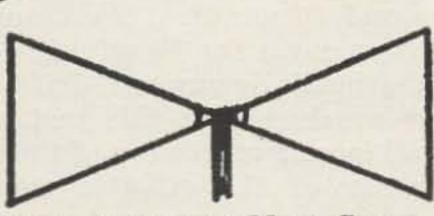


"Wonder Bar" 10 Meter Antenna

As featured in Nov. 1956 QST. Complete with B & W 3013 Miniductor. Only 8 ft. long for 10 meters. Wt. 5 lbs.

Amateur Net

\$7.85

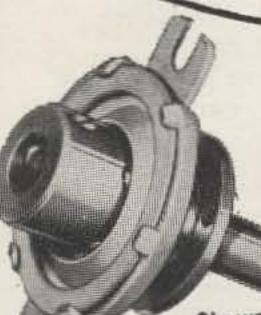


PRECISION PLANETARY-VERNIER

for exceptionally fine tuning Superb craftsmanship by Jackson Bros. of England. Ball bearing drive, 1/4" dia. shaft, 11/8" long, 6:1 ratio, Vy FB for fine tuning. Easily adaptable to any shaft. Comparable value - \$5.95.

> Amateur Net \$1.50 ea. 10 for \$13.50

Shown approximately actual size

PRECISION BALL DRIVE DIAL

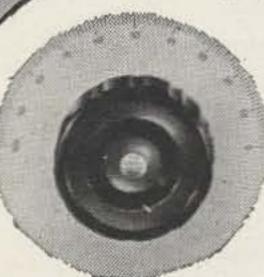

Another superb product of Jackson Bros. of England, 4" dia. dial with 6:1 ball drive ratio, Fits standard 1/4" shaft. For that velvet touch ...

Amateur Net \$3.95



Versatile Miniature Transformer

Same as used in W2EWL SSB Rig - March 1956 QST. Three sets of CT windings for a combination of impedances: 600 ohms, 5200 ohms, 22000 ohms. (By using centertaps the impedances are quartered.) The ideal transformer for a SSB transmitter. Other uses: interstage, transistor, high impedance choke, line to grid or plate, etc. Size only 2" h. x 34" w. x 34" d. New and fully shielded.

Amateur Net \$1.39 10 for \$10.75 3 for \$3.49 ARROW Authorized distributor of HEATHKIT equipment

TO SAVE C.O.D. CHARGES, PLEASE INCLUDE SUFFICIENT POSTAGE WITH YOUR ORDER. ANY EXTRA MONEY WILL BE RETURNED.

ALL PRICES F.O.B. N. Y. C. Arrow's Export Dept. Ships To All Parts Of The World! Prices Subject To Change Without Notice.



99'er 6 Meter TRANSCEIVER


A true ham station, ideal for both fixed station and mobile operation.

Double conversion superhet gives you extreme selectivity and freedom from images and cross modulation.

Transmitter section has an ultra-stable crystal oscillator which also may be controlled by

external VFO. Efficient, fully modulated 8 watt final works into flexible Pi network tank circuit. Large S meter serves for transmitter tune-up procedure.


Amateur net price \$139.95

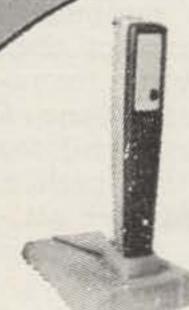

ELECTROVOICE Mod. 729 CERAMIC CARDIOID MIKE

Lowest cost, yet includes every feature essential for SSB operation. Flat, smooth response from 300 to 3,000 cps. Litts from stand for mobile or desk operation. Hi-Z, output -60 db. Ceramic element unaffected by heat or humidity. Price includes relaycontrol switch, stand and 81/2' shielded cable. Mike size 73/4" x 11/2" wide.

Model 729 \$15.90

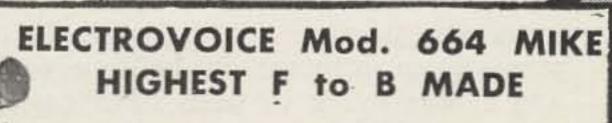

Flat response (40 to 15,000 cps) penetrates QRM, allows actual increase in RF power out. Efficient cardioid pattern, essential for SSB cuts accidental tripping of VOX ckt. Output -55 db. On/off switch (can be' wired for remote control). 150 ohms or Hi-Z output selected at cable connector. Mike size 7-3/16" x 17/8". Price includes mike and cable.

Model 664 \$51.00

Matching desk stand with DPDT switch \$9.00 Stand, less switch \$6.00

MAIL ORDERS PROMPTLY PROCESSED SAME DAY SHIPMENT FROM STOCK



ARROW ELECTRONICS, INC.

65 Cortlandt Street, New York 7, N. Y. . Digby 9-4730 525 Jericho Turnpike, Mineola, N. Y. • Ploneer 6-8686

TRADE-INS WELCOMED

sponse. A side advantage is that the audio gain may be fixed and still provide good performance.

Antenna feed requirements for both the transmitter and receiver are a reasonably flat 51 ohm termination. SO-239 connectors are used for separate 6 and 2 meter antennas. In the event one of the increasingly popular two band antennas is used, an internal strap connection will permit using a single connector for both bands.

The internal power supply employs a special power transformer which allows operation from the ac line or, using a conventional vibrator circuit, operation from 12.6 volts dc. Circuit switching is accomplished by inserting the appropriate power cord in the chassis connector. Four silicon diodes in a voltage doubler configuration supply the high voltage requirements. Another silicon diode powers the dc relays when the transceiver is operated from the ac line.

The unit loaned for the test, Serial Number 12B719, was accompanied by a letter from Bud Hargreaves, W2SXB, Chief Engineer of Polytronics. The letter said, in part, "... We have found that evaluations of equipment have been stilted and have been directed toward the good points, etc. We hereby authorize you to mention any undesirable features which you may find in the unit. . . ." Bud went on to specifically mention a couple of problems in the equipment. Some problems exist in any product but they are normally kept a dark secret by the manufacturer. If an unwitting user points out one of these problem areas, the manufacturer all too often expresses shocked surprise that such a condition could exist. The frank and open attitude of Polytronics is indeed a refreshing change.

Bud's statement was taken at face value and the transceiver really put through its paces, both on the air and on the bench. A local amateur, who prefers not to be identified, had expressed an interest in looking over the 62B and I was quick to take advantage of his experience. His competence is based on many years of professional and amateur VHF equipment design experience and backed up by some rather extensive test facilities. After inspection and limited testing, the unit was hauled to the basement lab and given the works. The tests resulted in 8 pages of notes, too lengthy to reproduce here. Environmental testing equipment was not available so specifications relating to temperature, shock, humidity and vibration were not checked. I don't claim that fullfledged compliance testing was conducted but a wealth of equipment was available and the balance of the specifications were checked out to the extent required to detect any serious departure from the manufacturer's published claims.

The 62B appeared capable of meeting or exceeding all specifications except those on transmitter VFO stability. As noted in the specifica-

tions, frequency stability of the VFO is cited as being within $\pm .02\%$ from -20° C to $+60^{\circ}$ C. This figures to be ± 29.2 KC at 146 MC. Bench tests showed drift in excess of this. Tests were conducted at room temperature of 21.5° C, using thoroughly warmed up and calibrated equipment. The 62B was turned on after being off for 24 hours and the VFO "spot" switched on only long enough to accomplish the measurements conducted at 5 to 10 minute intervals. Results, from a starting frequency of 144.312 MC, were as follows:

VFO drifted down 106.0 kc in 1st 30 minutes VFO drifted down 24.0 kc in 2nd 30 minutes VFO drifted down 12.0 kc in 3rd 30 minutes VFO drifted down 2.5 kc in 4th 30 minutes

At 5 hours and 36 minutes, the transmitter was operated key down for 10 minutes, resulting in an adidtional downward drift of 600 cycles. At the conclusion of this test, a thermometer placed loosely on the top of the cabinet read 53° C, a rise of 31.5° C over ambient.

Receiver stability measurements were conducted on 2 meters and performance was within specifications of ±.06%. This test was conducted by accurately measuring the second oscillator frequency. From a cold start, the unit drifted up 27 kc in 35 minutes and then drifted down 12 kc in 1 hour and 37 minutes. Drift on 6 and 2 meters is essentially the same.

Inclusion of the VFO feature in a 6 and 2 meter transceiver of compact construction poses many problems. Extreme supply voltage and temperature variations, vibration and shock are present in mobile operation. The oscillator tank switching problem is another obstacle that must be overcome. Polytronics has chosen the oscillator-frequency multiplier approach and the results serve to highlight the problem. The stability, while certainly not the best, is probably as good as can be expected in a competitively priced equipment of this type.

While the "state of the art" approach of a limited range, high frequency VFO and crystal controlled frequency converters could be used, a number of tuning ranges would be required for full coverage of both bands. Further, the increased circuit complexity required to reduce spurious output frequencies would probably price the equipment out of the market.

The balance of the test proceeded nicely. Receiver performance is all that is claimed. Selectivity was found to be even better than that cited in the specifications. 6 db bandwidth was measured at 3.9 kc and 40 db bandwidth at 19.5 kc. This degree of selectivity is very comforting to have, however it imposes more stringent stability requirements on the receiver circuitry and makes any drift in the received signal more pronounced. Retuning of the 62B is required during warm up. Sensitivity is excellent and overall performance such that weak signals really come up over the noise. S-meter readings were correlated with input level and each S-unit between S1 and S8 reflected an

average of 5.4 db increase in signal level. Image rejection is exceptionally good. The second and third if frequencies could not be detected on the 2 meter band, with the full 2 volt output of a General Radio 805-C signal generator pumped into the antenna connector. The two 2 meter spurious responses were present at the predicted intensity.


The receiver audio system is more than adequate and no trouble was encountered with microphonics when using the internal speaker. The shock mounting used for the receiver tuned circuit assembly and the transmitter VFO really shows its merit under conditions of vibration and shock. The squelch circuit works well and can be set to trip on signals way down in the noise. The squelch threshold is fully adjustable and the adjustment holds for extended periods.


Power output of the transmitter was measured, using a Bird Termaline Model 61 RF Wattmeter. Measured power output into this 50 ohm load of 9 watts on 54 mc and 5.5 watts on 148 mc agreed with the final inspection check list packed with the transceiver.

I was very much impressed by the quality of components used in the 62B. Teflon insulated wire is used throughout the unit and all metal parts are heavily plated. The quality of workmanship in the assembly and wiring is uniformly good. Careful attention to mechanical details, including the shock mounting of the receiver tuning elements and VFO, contribute to the overall performance. Physical layout of the front panel is good although the compact size of the unit does make some compromise necessary. The front panel mike connector is comparatively large and, as a consequence, the PA tuning and loading controls are a bit difficult to reach. Fortunately, these controls do not require constant attention so no hardship is imposed. The recessed front panel provides ideal protection for the controls in the mobile environment and this feature should not be sacrificed. However, when the unit is placed on the operating table, the meter and dials are somewhat obscured by the cabinet overhang. Flip-out extension feet mounted on the bottom front of the cabinet would tilt the transceiver at a convenient viewing angle.

On the air performance was excellent and, except for some comments on VFO drift, reports were consistently good. Modulation quality was reported as excellent. Receiver drift was noticeable during warm up but, once stabilized, the receiver is a real pleasure to operate. I believe the logical approach is to accept the VFO as a bonus feature, to be used as a crystal substitute only as required. The dual band coverage and many other desirable features result in overall performance of the 62B that places it ahead of competitive factory assembled products on the basis of dollar value received. ... W4WKM

(Turn page for Specs.)

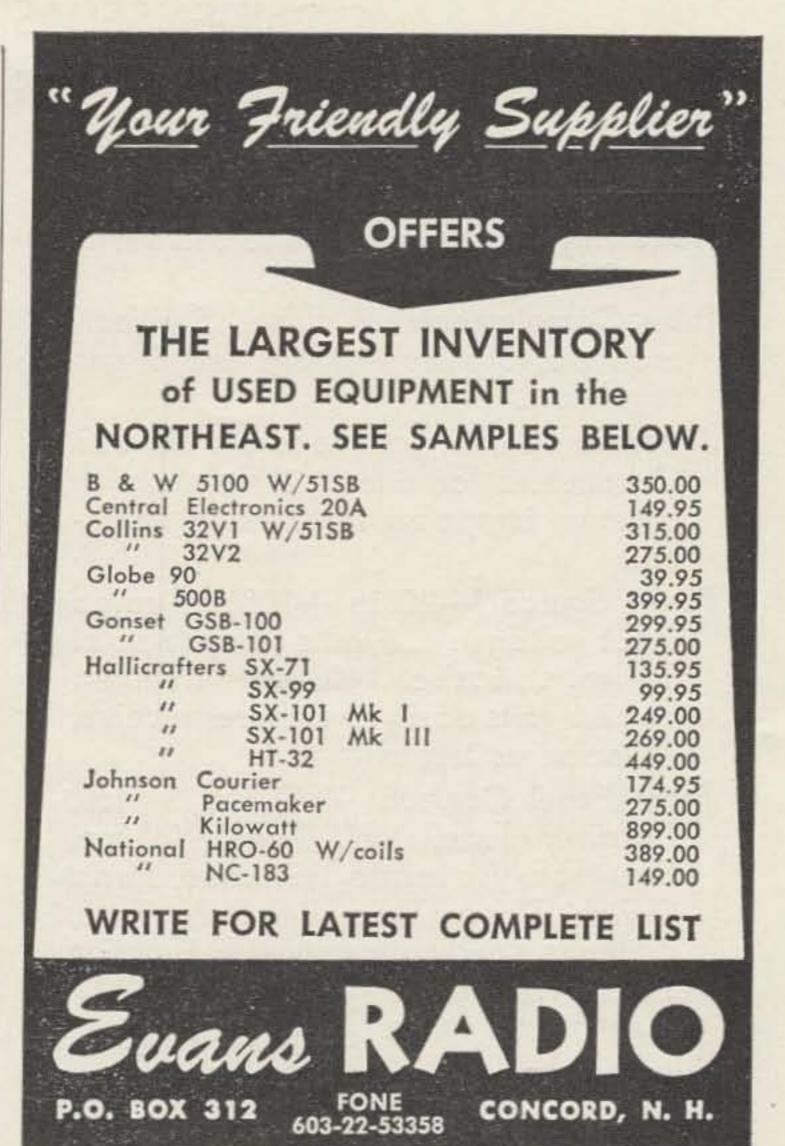

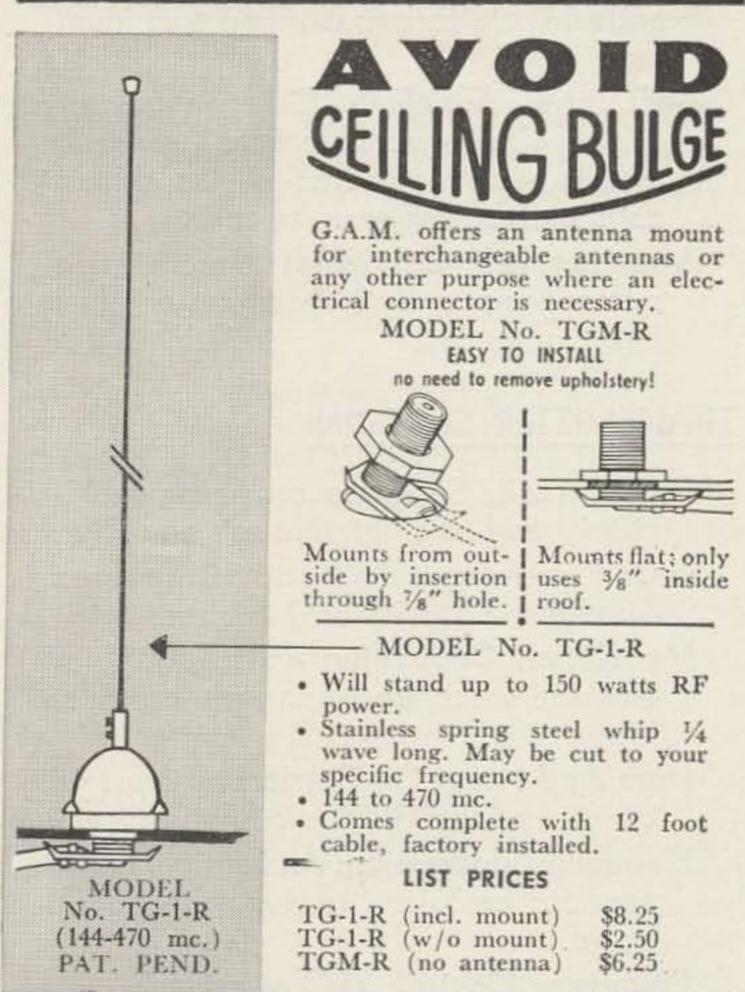

SEE YOUR DISTRIBUTOR OR WRITE GAM DIRECT

I. 81 1 .

138 Lincoln St., Manchester, N. H.

CONDENSED SPECIFICATIONS

Polycom 62B

TRANSCEIVER:

Frequency Coverage: 49.75 to 54.25 mc; 143.75 to 148.25 mc.

Tube Complement: 16 tubes, 5 silicon rectifiers, 3 silicon diodes and 5 gas regulators.

Antenna: 50 ohm line. Separate SO-239 Connectors for 6 and 2 meters with optional strapping for 2 band antennas.

Power Source (-20 to +10% of rated input voltage): 117 volts 60 cycle ac at 90 watts receive, 140 watts transmit, or 12.6 volts dc at 10 amperes receive, 16 amperes transmit.

Front Panel Controls: VFO-Xtal Switch, Receiver Tune, VFO Tune, Volume, Squelch, Antenna Trimmer, Band Switch, Driver Tune, PA Plate Tune, Antenna Loading and Meter Function Selector.

Size: II" wide x 10" deep x 5" high.

Weight: 15 pounds.

Finish: Marine gray with maroon knobs and white lettering; brushed aluminum grill.

Accessories Supplied: Ceramic microphone with retractable cord, universal mobile mounting bracket, ac power cord and battery power cord.

Accessories, Optional: Base station microphone and 2 & 6 meter dual band antennas.

TRANSMITTER SECTION:

Type Circuit: Separate oscillator, multiplier(s) and straight through amplifier.

Plate Power Input To Final: 18 watts on 6 meters, 17 watts on 2 meters.

Modulation Capability: 85 to 100% at average voice level using plate modulation.

Hum And Noise On Carrier: At least 40 db down from 30% modulation level.

Harmonic Suppression: All harmonics and spurious emissions better than 50 db down.

Frequency Control: VFO or crystal.

Crystal Stability: ±.005% -30°C to +70°C.

Crystal Circuit Stability: ±.006% -20°C to +60°C.

VFO Stability: ±.02% -20°C to +60°C.

RECEIVER SECTION:

Type Circuit: Triple conversion superheterodyne on 2 meters, double conversion on 6 meters.

Calibration: 100 kc graduations every 4° with 6:1 tuning ratio.

Sensitivity: Better than .2 microvolt on 6 meters and .3 microvolt on 2 meters for 6 db S+N at 30%, 1000 cycle modulation.

Selectivity: -6 db bandwidth 8 kc ± 2 kc; -60 db bandwidth 25 kc ± 5 kc.

Delayed AGC: Audio output varies less than 3 db for inputs between I microvolt and .I volt.

Squelch, Adjustable: .08 microvolt threshold on 6 meters, .1 microvolt on 2 meters.

Noise Limiter: Floating series gate type.

Audio Output: At least 2 watts into 21/2" internal speaker or 3 watts into external 4 ohm speaker with less than 15% distortion at 1 watt.

Hum And Noise: Better than 40 db down from I watt output.

Frequency Response: Within +1 db to -5 db from 250 to 3000 cycles.

Image Rejection: 1st image better than 85 db down, 2nd image better than 60 db down and 3rd image better than 85 db down.


Spurious Responses: Better than 60 db down except within ±20 kc of desired signal.

Internal Generated Spurious Signals: 145.17, approximately 90 microvolts (S9); 147.80, approximately 80 microvolts (S8).

Cross Modulation and Desensitization: Better than 50 db down at ±20 kc.

IF Frequencies: 52.00 mc (±2 mc), 5.405 mc and 455 kc.

Stability: ±.06% from -20°C to +60°C.

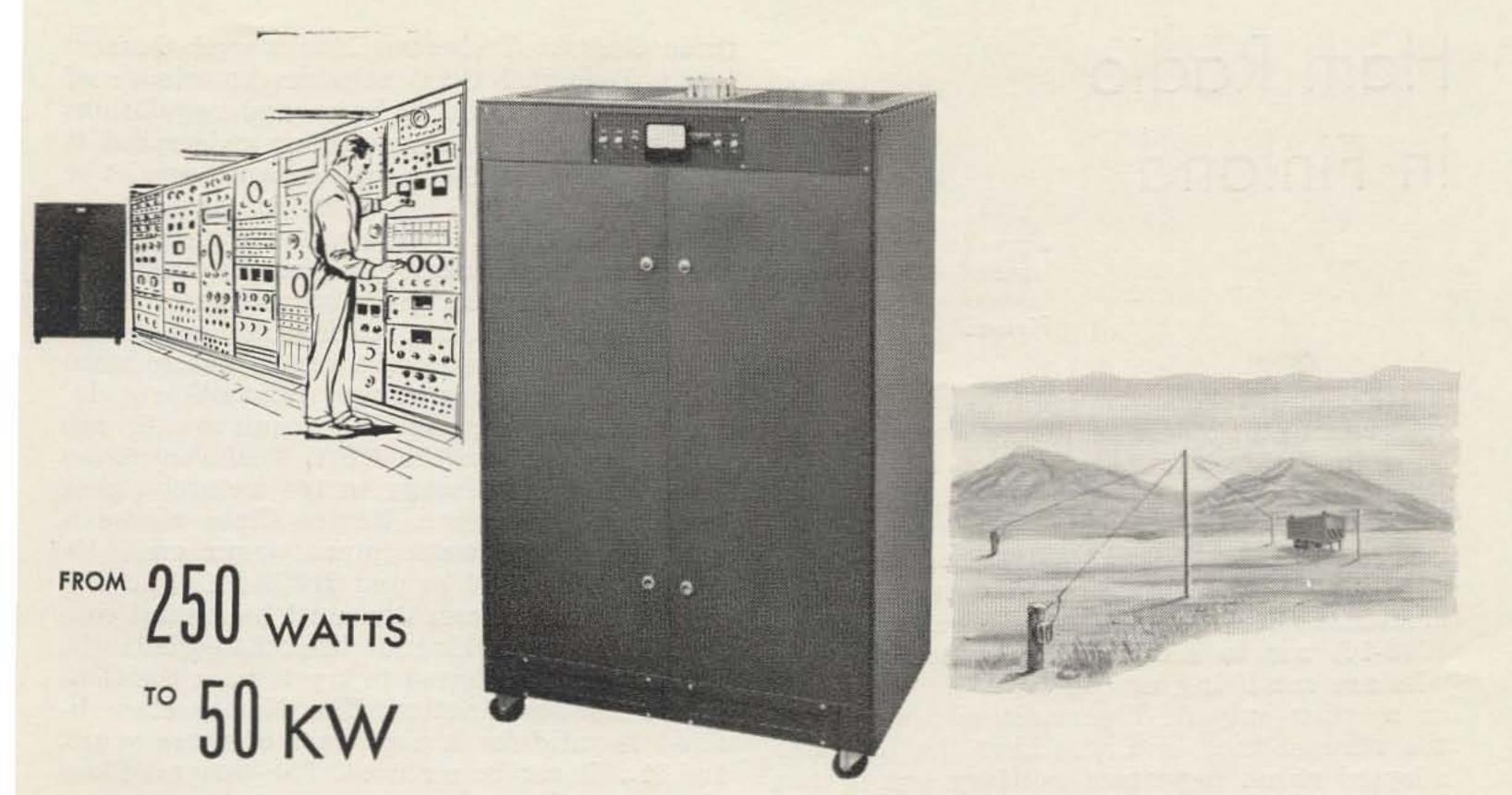

DUMMY LOADS AND ANTENNA TERMINATORS/DISSIPATORS)

TMC MODEL NUMBER	MILITARY NOMENCLATURE	FREQUENCY	AVERAGE POWER (In warts)	PEAK ENVELOPE POWER (In warts)
TER-250-300 U		DC to 30 mc	250	500
TER-500-70 U		DC to 30 mc	500	1000
TER-500-600 B	DA-199/U	DC to 30 mc	500	1000
TER-1800-300 U		DC to 30 mc	1800	3600
TER-3500-70 U		DC to 30 mc	1750	3500
TER-3500-600 B	DA-200/U	DC to 30 mc	1750	3500
Tiony Se				
TER-5000-70 U	DA-210/U	DC to 30 mc	5000	10,000
TER-5000-300 U		2-30 mc	5000	10,000
TER-5000-600 B	DA-201/U	DC to 30 mc	5000	10,000
TER-18KA-50 U		DC to 30 mc	18,000	36,000
TER-18KC-50 U		DC to 30 mc	18,000	36,000
TER-18KA-70 U		*	18,000	36,000
TER-18KC-70 U		7.	18,000	36,000
TER-18K-600 B		4-28 mc	18,000	36,000
TER-18K-600 BF		4-28 mc	18,000	36,000
TER-25KA-50 U		DC to 30 mc	25,000	50,000
TER-25KC-50 U		**	25,000	50,000
TER-25KA-70 U		(se	25,000	50,000
TER-25KC-70 U		*	25,000	50,000
TER-25K-600 B		4-28 mc	25,000	50,000

For companion RF Broadband Transformers refer to Sales Service Bulletin #8015. WITH TMC Models

TEN

Request Technical Bulletin 8009

Models TER-18K and Model TER-25K are new additions to TMC's family of dummy loads and antenna terminators/dissipators that cover the power range of 250 watts average to 50 kw peak. Models TER-18K and TER-25K are provided in 50, 70, and 600 ohm terminations and are housed in metal cases provided with casters for mobility. A meter to indicate forward and reflected power for computation of VSWR is provided as an optional item. Model TER-18K-600-BF, a 600 ohm terminating unit in a fiberglass reinforced plastic case, is used to terminate a Rhombic antenna in high powered transmission service of up to 50 kw PEP, over the frequency range of 4 to 26 megacycles.



The TECHNICAL

MATERIEL

CORPORATION

MAMARONECK, NEW YORK

OTTAWA, CANADA • ALEXANDRIA, VIRGINIA • GARLAND, TEXAS
LA MESA, CALIFORNIA • POMPANO BEACH, FLORIDA

Ham Radio in Finland

John Velamo OH2YV Isokaari 4-B-30 Lattasaari, Helsinki Finland

THE Finnish Amateur Radio League, SRAL, is among the oldest amateur radio organizations in Europe. It was founded officially in 1921, so this spring means the 41-year milestone to it. However, long before this there was considerably strong amateur radio activity in Finland; some of the still active Finnish amateurs were 'in the business' already around 1913-14, not to mention the actual pioneers who are not living among us any longer. Let us mention only A. Tigerstedt who developed the vacuum tube in a way that the Germans adopted as an important military secret that time. Leo Lindell OH1NA, silent key in 1936, is said to be the founder of SRAL, also the first Finnish radio amateur. In addition to these the amateur radio has many traditions in Finland.

The membership of SRAL (Suomen Radio-amatooriliitto) is about 1800. Approximately 1600 of them are licensed amateurs. The country is divided into ten districts, $OH1\text{-}OH\phi$, $OH\phi$ Aaland Islands having selfgovernment and thus counting as a separate country from Finland in the Amateur World. The maximum input power allowed to OH stations in the General class is 200 watts on 80-40-20-15-10 meter bands as well as on the VHF bands. There are possibilities that special permission will be granted to OH amateurs for operating on 160 meter band with a maximum of 10 watts input power.

The amateurs in Finland are divided into



W6AM visiting Finland in 1961 summer. OH2XK, OH2RM, K2RKN/OH2QZ, OH2XZ of U.S. Embassy, W6AM, in shack of OH2XZ.

three classes: Technical, Novice and General Class. Technical Class requires knowledge of electrical and radio technics and regulations for amateur radio. However, no code speed is required. Novice Class requirements consist of basic knowledge of electrical and radio technics, code speed of 8 wpm plus regulations for amateur radio. General Class requirements are 12 wpm code speed, good knowledge of radio and electrical technics, considerably good ability to communicate on the bands, not to mention good knowledge of amateur radio regulations etc. In general the requirements are much like those in the USA. Technical Class license allows 200 watts on 144 mc and higher bands, CW or phone. Novice Class allows a maximum of 15 watts input power on 3510-3545 ke, 7020-7050 ke and 21060-21150 ke CW only, and the transmitter must be crystal controlled. After making at least 300 QSOs the Novice will be allowed to try to pass the General Class examination. The Novice class license is valid for a maximum of three years, and it will not be renewed. The General Class rights are those already mentioned.



OH2YV John Velamo, General Secretary of the SRAL of Finland, honorary Secretary of the Award Hunters' Club, President of the local radio club, member of A1-OC, Tops-CW-Club, HSC, Rcc, etc.

In Finland there are possibilities to any foreigner to get an amateur license and an OH call. However, this is based mainly on the reciprocal agreements, but many exceptions have been done, too. At the present time there is one American (OH2XZ), one Australian, and one Norwegian amateur licensed in Finland. Earlier there have been a few Englishmen, a few Swedes, etc. At the present time it seems that the Finnish authorities are in favor of the reciprocal agreements because applications of some amateurs of "non-reciprocal" countries have not been accepted. In Finland the authorities have given SRAL the rights to control the radio amateur activities; probably Finland is the only country in the world where the official league has such duties and privilege! This system is working well, and

violations against radio laws happen very seldom among the Finnish radio amateurs. The control work of SRAL is mainly advising but in serious cases SRAL has right to propose cancelling of certain amateur radio licenses. Thus the amateur radio activity in Finland is extremely free, however the system gives SRAL very serious duties and sometimes causes certain difficulties especially when violations are notified.

The DX activity in Finland is on a high level, as an average. The high top man probably is OH2NB with approximately 300 countries worked. OH5NW comes with some 260 countries on phone alone. Over 30 OH amateurs have more than 180 countries worked; they represent about 7-8% of the continuously active OH amateurs. The contest activity in Finland is high, especially in the international contests like WAE-contest, ARRL Competition etc., and before all the Scandinavian Activity Contest which usually show very strong OH activity on the bands. The number of OH's in these contests usually is among the highest in the whole world. SRAL issues three awards, OHA, OHA-100 and OHA-300, for contacting OH amateurs. Rules of these are available from Box 306, Helsinki.

Among other international activities in Finland there can be mentioned also the WDT and CRC awards, WDT being issues by the Tampere gang (OH3), and CRC award by the Radio Club of Cafe de Colombia (hi!). CRC has meetings daily, at the luncheon time, and thus it can be said to be the most active amateur radio club in the world! Furthermore, the oldest and original award and certificate hunters' organization, the Award Hunters' Club (AHC) has its headquarters in Finland. Newest addition to the Finnish certificates is the VRCC for the Finnish Railroads 100-year jubileum, issued by the railroad amateurs.

The local club activity in Finland is lively, too. There are nearly 30 clubs altogether, representing practically all Finnish cities. These clubs include most of the active OH amateurs



OH7NF Eino Toivanen, the 7 mc specialist with 156 countries on forty cw. Old Timer, one of the European pioneers on 28-mc—operating world-wide in the early '30s.



President of the OH YL amateurs, Marie OH2FB (XYL of OH2YV).

in their membership. The biggest of them is the OH2-Club, "Kakkosten Kerho," with a membership of approximately 300. The smallest clubs contain around 5-6 members. The Club stations usually have call signs beginning with the letter 'A,' OH1AA, OH2AA, OH5AC, OH6AB etc. The Headquarters call is OH2A, having also been used as OH4A, OH9A and $OH\phi A$.

There are approximately 35 YL and XYL amateurs in Finland. A few of them are in the Novice Class. Their activities are not extremely strong on the bands; merely they seem



OH2NB Armas Valste, the top DXer of Finland. Old Timer, one of the first Finnish Radio Amateurs.

to like to arrange meetings. Mostly the OM's of the XYL amateurs are licensed hams, too.

The youngest OH amateur is OH2BAD, 13 years of age, good "runner-up" being OH2BL with 14 years of age. They both are still in the Novice Class but very soon they will be changing the final tube to bigger . . . The Novice Class system has given very good experience in Finland as to the operating ability and skill of amateurs. The General Class amateurs coming from the Novice Class regularly show a very good skill on the bands; this is

(Turn to page 77)

An Extra Hand in the Shack

Dot Maker

Many times while trying to track down TVI, BCI, Parasitics, etc., in a transmitter, two hands are just not enough to key the transmitter, tune an absorption wavemeter and TV set all at the same time. If there is someone else around to assist this is no problem, but when one is alone it is impossible to be in two places at once. "DOT MAKER" can

help solve this and other problems.

The basic circuit, shown in Fig. 1, is a free-running multivibrator. This circuit is due to Courtney Hall', and is probably one of the simplest multivibrator circuits to be found. Yet, it is reliable, stable, consumes very little power, can be synchronized, and can be wired in only a matter of minutes. In Fig. 1, when voltage is applied, C begins to charge through V1 and R2; the current through R2 cuts off V2. When C has charged, V1 cuts off. Since no more current is flowing through R2, V2 conducts and discharges C through R1. The original condition is now restored and the cycle starts over again. V1 and V2 can be combined into a single tube envelope such as a 12AU7, 12AX7, 12AT7, and other similar types. Capacitor C may be switched to provide different rates, and if synchronization is desired, the grid of Vz can be returned to ground through about 200K ohms and sync voltage coupled to the grid of V_2 through a capacitor. The output should only be taken from the cathode of V_2 since it is not very sensitive to loading impedances as is the cathode of V_1 . V_2 acts as a cathode follower in this case.

The frequency is changed by changing the capacitor and/or the resistors. Making R₂ variable and switching in different values of C gives a very wide frequency range.

Referring to Fig. 2, the actual circuit of "DOT MAKER," one 12AU7 is used as a low frequency multivibrator to operate relay K1, an 8000 ohm Sigma 4F relay. Its contacts key an external circuit by way of the terminal posts mounted on the edge of the Minibox. The second 12AU7 is an audio oscillator which can be used with phones, a speaker and output transformer, a pre-amp, or other reasonably high input impedance audio device for monitoring purposes. The 500K pot in the keyer gives a pulse rate of approximately 2 cps to 70 cps, and although this particular Sigma relay will not follow over this entire range, it does follow over a major portion. There are two reasons why just any relay wouldn't follow over the whole resistance range. One is that the current is drawn in short pulses and at the high resistance end of the pot, i.e., low pulse fre-


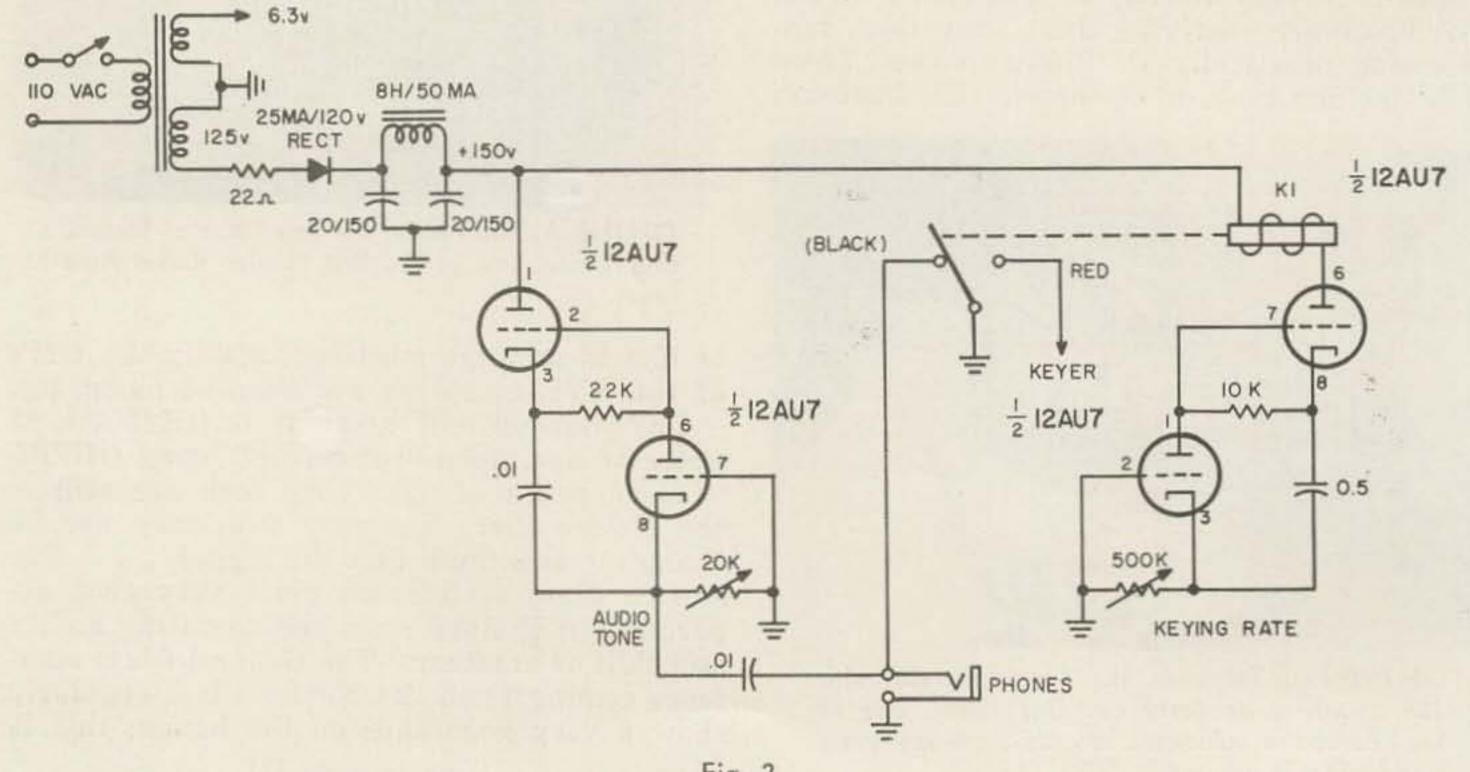


Fig. 2

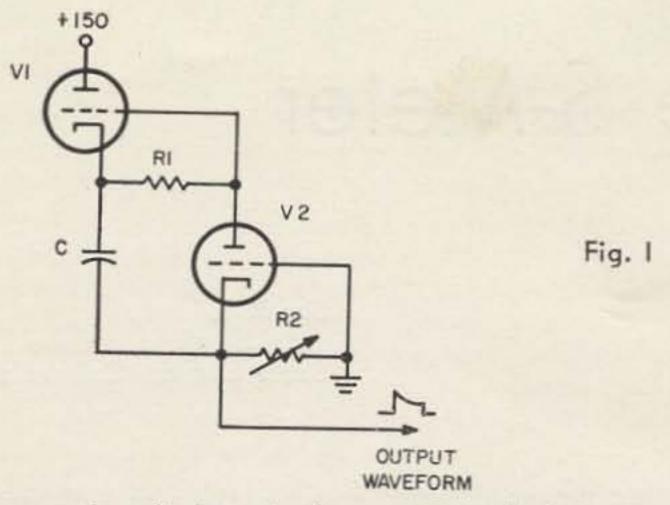

quencies, it is not always enough to cause the relay to operate. The second is that at the low resistance end of the pot, the relay cannot follow because of the armature inertia.

The Sigma relay used in this version has both adjustable contacts and spring tension, consequently it can be adjusted for maximum range. This is a desirable feature, although not absolutely necessary. As long as the relay will operate on 1 to 2 milliamperes no problems should be encountered. The armature contact need not be grounded if desired; however, if it is not, the insulation voltage of the relay may be exceeded when keying in certain circuits.

The audio oscillator may not appear very useful here, but it serves several purposes. Plugging a speaker and output transformer into the phone jack allows an audio monitor of the keying rate when checking for TVI, BCI, etc. For checking AM operation the pulsed audio can be fed into the modulator and the rf envelope synchronized on a scope for detailed examination. If desired, it can be wired separately from the keyer and used as a code practice oscillator or as a keying monitor.

The "DOT MAKER" is wired in a 3 x 5 x 7 inch Minibox and there is plenty of room to spare. The power supply is straightforward and the actual votage is not critical. Current drain is very small in this particular circuit. Wiring is not critical nor is placement of parts, so no special care is needed for the construction of the "DOT MAKER." Any way you use it, "DOT MAKER" will be that extra hand in the shack you've always needed.

... W6VAT

"STABLE FREE-RUNNING MULTIVIBRATOR," Courtney Hall, p. 38, July 1960, Electronic Equipment Engineering.




EASY TO LEARN CODE

Learn to increase speed with an Instructograph—the Code Teacher that takes the place of an operator-instructor and enables anyone to master code without further assistance. Available tapes from beginners alphabet to typical messages on all subjects. Speed range 5 to 40 WPM. Always ready—no QRM. Thousands have "acquired the code" with the Instructograph System. Write today for convenient rental or purchase plans.

INSTRUCTOGRAPH COMPANY

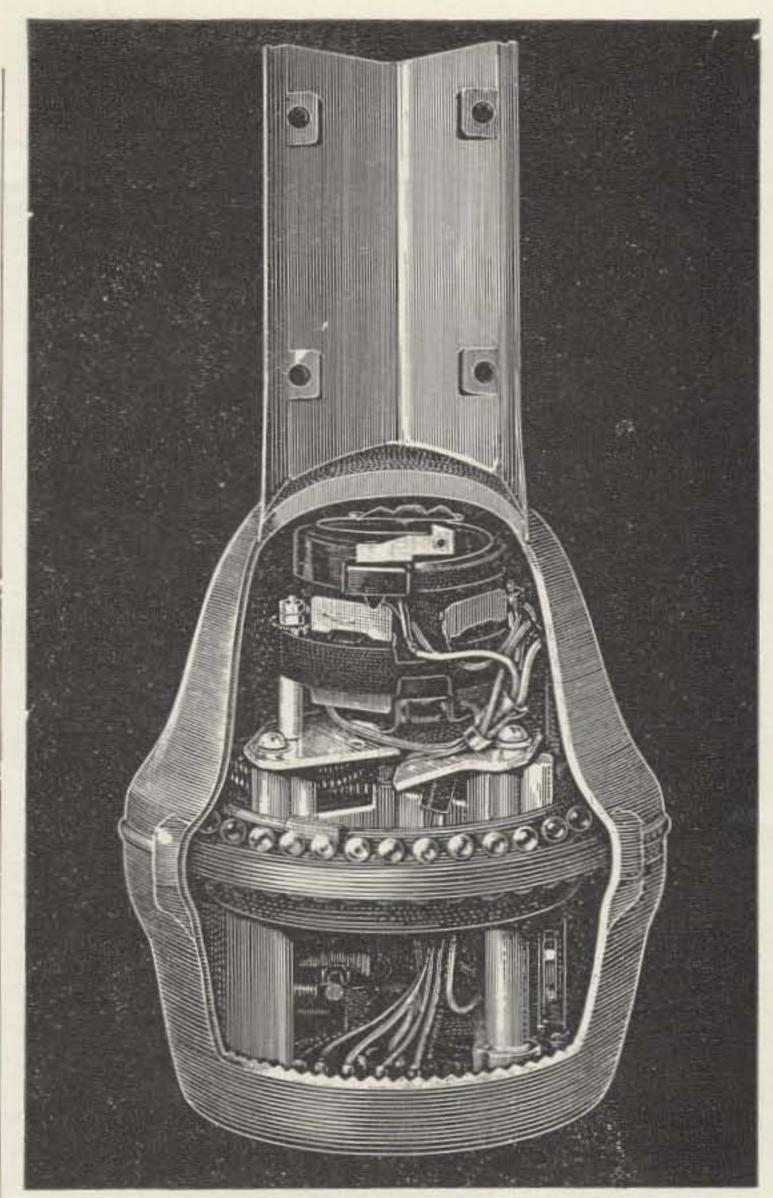4713 SHERIDAN ROAD, CHICAGO 40, ILL. 4700 Crenshaw Blvd., Los Angeles 43, Calif.



DESIGNED FOR HALF-TON ANTENNAS

We've designed our HAM-M antenna rotors to support a dead weight of 1000 lbs. Your antenna probably weighs a small fraction of that, so see for yourself the kind of safety margin the HAM-M gives you!

But there's more! A positive electromechanical locking mechanism provides 3500 inch-pounds of resistance to the side thrust and whipping action of hurricane-force winds. And its bell-shaped, high tensile strength aluminum alloy housing is completely waterproof, assures brilliant performance even when caked with 5 inches of ice!

At \$119.50 amateur net, the HAM-M is the greatest rotor value around! Ask your local CDE Radiart Distributor for all details.



CORNELL-DUBILIER ELECTRONICS, DIV. OF FEDERAL PACIFIC ELECTRIC CO., 50 PARIS ST., NEWARK 1, N. J.

An Accurate S-Meter

Jim Kyle 1851 Stanford Avenue Santa Susana, California

WOULD you like to be honest, for a change, in the matter of giving signal-strength reports?

Those are strong words, yes, but if you rely on the scale of your receiver's S-meter and blithely quote a "60 db over S-9" reading, you're being far from honest. Let's take a closer look and see why.

To start, let's assume that our ancient tradition that one S-unit equals a 6 db change in signal strength is true. That means that every S-unit change in level doubles the voltage present at the receiver input.

Let's also assume that the non-existent "S-O" level represents a signal just exactly equal to the noise level of the receiver and the band in use. On 10 meters, this is usually equivalent to about 10 microvolts fed into the antenna terminals.

Now since every S-unit represents a doubling of the voltage at the antenna terminals, S-1 would equal a 20-microvolt signal. S-2 would be 40 microvolts, S-3 80, and so on until we find that S-9 equals 5,120 microvolts or 0.00512 volt. At S-9, we begin running into "db over"; these usually increase 20 at a whack-but 20 db represents a tenfold increase in input voltage. Thus, "20 db over S-9" would be 0.0512 volt, "40 over 9" would be just over half a volt, and "60 over 9" would be a whopping 51/8 volts! The largest voltage yet recorded at the input terminals of a receiver which wasn't connected directly to a transmitter is only a bit over 1 volt; therefore, unless the scientists who measure received signals are all wet, a "60 over 9" signal is just an optimistic figment of our imaginations.

The blame, though, doesn't rest entirely on our shoulders. Virtually every receiver built today which includes an "S-meter" is graduated to 20, 40, and 60 db over S-9—and the needle stays there much of the time, on most bands.

These S-meters have other faults, too-

earlier we said let's assume that one S-unit equals a 6 db change in signal strength. With most S-meters, this is not so. The spread between S-1 and S-9 is actually 256 times, in voltage input, but most meters swing their needles across this range with less than a 10-time voltage change.

If you want more of a sales talk, read almost any of Ed Tilton's writings—he has long conducted a campaign against meaninglessly inflated "S-Meter" reports; the purpose of this article isn't so much to convince you, as it is to show you what you can do about the situation for yourself.

You can build an accurate S-meter, capable of measuring incoming signals to the decibel in the range S-0 to S-9, for under \$10 (less, if your junkbox is well-stocked). The accompanying schematic shows the circuit; here's how it works:

Basically, this "S-Meter" is a balancing type voltmeter measuring the voltage across the detector load resistor in 6 db increments, with a fine adjustment to allow continuous interpolation between the steps.

The voltmeter consists of three basic circuits: a reference voltage source, providing 10 reference voltages in 6 db switched steps; a "Kirschoff adder" which adds together the reference voltage and the input voltage; and an output indicator to show us when the output voltage is zero.

If the meter is adjusted to give zero output when both the coarse and fine knobs are set at "0" and the receiver is bringing in only noise, then the strength of an incoming signal in Sunits and db above the noise level can be quickly determined by re-balancing the meter with the two knobs until the indicator once more reads "0", then reading the S-units from the coarse scale and the "db over" from the fine scale.

The heart of the circuit is the "Kirschoff adder," consisting of three fixed resistors and a potentiometer. This circuit is shown separately in Fig. 1; you can see that resistor R1 and pot R2 form one leg of a Tee, while resistors R3 and R4 form the other two legs.

With the resistance values shown, and R2 in its zero-resistance position, the two input voltages are added together algebraically and their sum appears at the output. However, since the reference is positive while the de-

tector voltage is negative, this "addition" will result in an output voltage of zero if both inputs are equal.

Now let's take another look, but assume that R2 is in its maximum-resistance position this time. Now, the output voltage will be proportional to the algebraic sum of the detector voltage and *half* the reference voltage; the reference voltage has been multiplied by the ratio of R3 to R1+R2.

Actually, the output voltage is only proportional to the sums of the input voltages in both cases, because R4 acts as the lower leg of a voltage divider. Since we are interested only in one output voltage—zero—this fact is

not important.

The maximum-resistance position of R2 corresponds to the +0db scale reading, and the zero-resistance position is the +6db scale reading. By switching the reference voltage in 6 db steps with R2 set to +0db, the coarse adjustment covers a range of detector voltages from approximately 1/16 volt to approximately 32 volts. Adjustment of the fine pot (R2) expands this range upward to 64 volts. Few receivers will handle a 64-volt signal level at the second detector, but most will produce 1/16-volt output with only noise input.

At this point, you may be wondering what will happen to detector performance, with a path from B+ to the detector. Here's where the voltage divider formed by R4 comes in. At its worst, the positive voltage at the top of R4 can be only 1/1000 of that at the top of the reference string—or 0.064 volts. This is further cut down by isolation through R1 and


R2, to only microvolts at the detector.

The low voltages across R4 also make necessary the rather elaborate zero-indicator system composed of V1 and its associated resistors, in addition to the 50-0-50 microammeter. This circuit is a conventional bridge-type VTVM except that the cathode resistances are higher than normal; the meter indicates the difference in current flow in the two halves of the tube.

When the S-Meter is balanced, the current flow will be equal and the meter needle will rest in the center of its scale. When the S-Meter reading is weaker than the incoming signal, the needle will be above center; when the S-Meter reads less than the incoming signal strength, the needle will be below center.

Resistance of R2 in Circuit	Scale Calibration
1 meg	+0
782 k ohms	+1
589 k ohms	+2
415 k ohms	+3
262 k ohms	+4
125 k ohms	+5
0 ohms	+6

Table I. Calibration of R2 Scale.

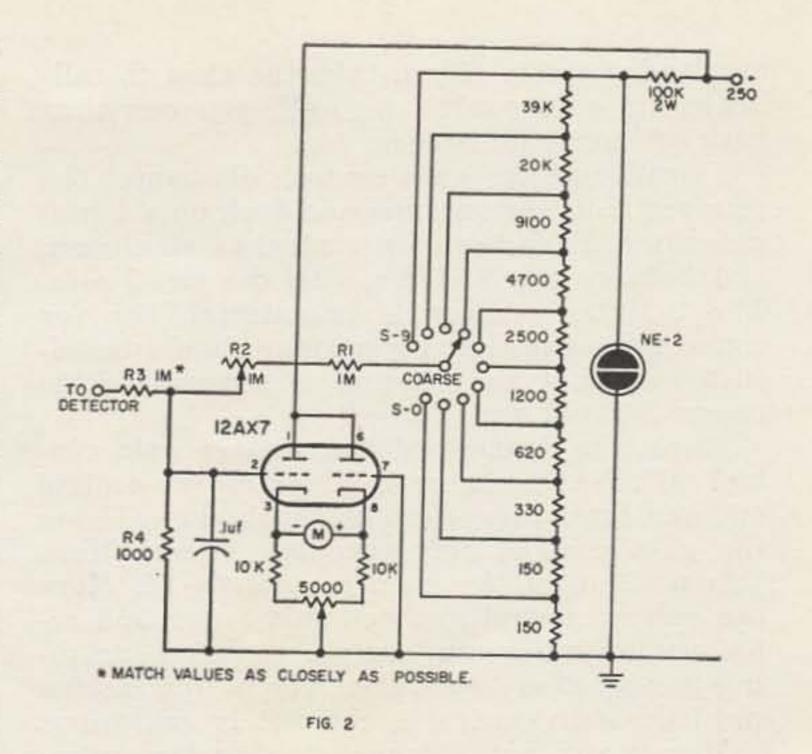

The meter used was chosen for price; Lafayette Radio sells this model for \$2.95. However, you can use any meter of similar current capacity you may have; the zero-center feature is not necessary, since a zero-set adjustment is provided in the meter circuit. To use a zero-left meter, simply adjust the zero-set until the needle rests in the center of the scale with the indicator disconnected from the adder and the R4 terminal of the indicator grounded.

The only critical part of construction and installation concerns R3—this resistor should be located right at the detector load resistor, and a shielded lead run from it to R4. The rest of the circuit can be an outboard unit. Power can be taken from any source capable of supplying 10 ma at 200 to 300 volts dc and 600 ma at 6.3 volts for the filament.

To use the S-Meter after it's built and installed, start by setting both the coarse and fine knobs to their zero settings. Turn the receiver to the band in use, and disable the AVC by switching to manual. Find a vacant spot on the band. Using the receiver RF and/or IF gain control, balance the S-Meter for a center-scale indication. This calibrates the instrument to the prevailing noise level for the band, the receiver, and the particular conditions at the time.

Now, secure the receiver rf or if gain control in position with a strip of masking tape. If it is moved, you'll lose calibration. Tune across the band to signals, and at each signal you want to measure, balance the S-Meter with the coarse and then the fine knobs.

Note that the *fine* knob provides only an increase, not a decrease, in indication. Start with both knobs at zero; the needle will be to the left of center. Increase the *coarse* setting until the needle moves to the right of center, then decrease the *coarse* setting one unit and center the needle with the *fine* knob.

When you have the receiver calibrated to the meter, you'll occasionally find signals which overload the set; if you take the time to calibrate the gain control as well, you can then back off and handle them too.

To calibrate the gain control, disconnect the receiver from the antenna and hook up a signal generator. Turn the gain control to maximum, and balance the S-Meter with the two knobs. The S-Meter reading is immaterial, but for convenience the signal generator should be adjusted so that the reading is somewhere between S-9 +0 and S-9 +6.

Mark this position of the receiver gain control "0". Next, set the S-Meter coarse control one unit lower; leave the fine knob alone. Using the gain control, rebalance the meter. Mark this position of the gain control "+1". Move the coarse control another unit lower and rebalance with the gain control as before, marking this position "+2". Continue in this fashion until the gain control is completely calibrated.

If you run out of range, losing the signal or going below "S-0" during this procedure, return to the last accurately calibrated position. Then move the coarse control back to S-9 and increase signal-generator output until the meter is rebalanced (you can use the fine control to rebalance after the signal generator output is in the right range). This establishes

a new reference level, and you can continue calibration.

To use the calibrated gain control with the S-Meter, first proceed as before-tuning to noise, setting both coarse and fine controls to zero, and balancing with the gain control. Now, note the gain-control reading. When you run into a signal so strong that it overloads the receiver, back the gain control down an integral number of steps (if the original reading was $+4\frac{1}{2}$, you can back it down to $+5\frac{1}{2}$, plus $6\frac{1}{2}$, $+7\frac{1}{2}$, but not to +7 or +6). Note how many steps you moved, and add this number of S-units to the strength you measure (if you moved down four steps and read S-9 plus 5, the true reading would be S-13 plus 5 or in more conventional terms, 30 over 9-but you won't find this kind of signal around).

. . . K5JKX/6

PARTS LIST

- 1 single-pole, 10-position rotary switch (COARSE Control)
- 1 1-megohm, linear taper potentiometer (R2)
- 1 5000-ohm, linear taper potentiometer (ZERO SET)
- 1 50-0-50 microammeter (Lafayette TM-13 recommended; any 50- er 100-microammeter will work)
- 1 9-pin tube socket
- 1 chassis box
- knobs, panel decals, wire, and solder

LCU's Michigan Long Wire

Ralph Burch W8LCU

THE following antenna was designed to be used with a 35 watt, 75 meter station which I spent a great deal of time installing in my 1959 Shasta camp trailer.

The thing that really got me into trouble was falling over tent stakes and getting mixed up in campers clothes lines while trying to erect a 75 meter doublet in one of many Michigan

3.9 M.C.

50.0

MATCH

SOLUTION

SOL


parks. Right then and there I knew I would have to come up with a new approach on portable antennas.

The antenna had to meet certain specifications:

- No. 1. It couldn't take to much space.
- No. 2. It had to be erected easily in a minimum amount of time.
- No. 3. It must be supported at one end by the trailer making it easy to fasten the other end to some convenient tree, post, or mast.

No. 4. The antenna must be fairly efficient. With this goal in mind, I set out to design what I call the LCU portable antenna.

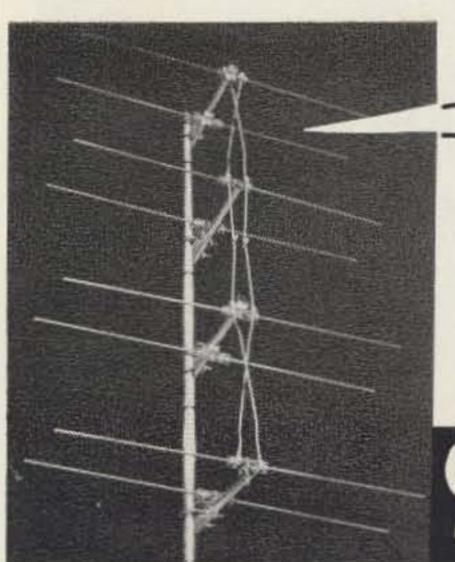This antenna consists of nothing more than a piece of copper clad 300 ohm TV ribbon cut exactly 60 feet long (for 3.9 mc). At one end the ribbon is fed into a standard coax fitting and one wire is soldered to the shield or ring.



TERRIFIC! COLINEAR ARRAYS

LOOK TO CUSHCRAFT for SUPREME PERFORMANCE

- LIGHT WEIGHT
- HIGH FORWARD GAIN
- LARGE CAPTURE AREA
- MECHANICALLY BALANCED
- HIGH FRONT TO BACK RATIO

32 & 64 ELEMENT STACKING KITS ARE AVAILABLE

430 Mc.-\$9.25; 220 Mc.-\$12.95; 144 Mc.-\$16.00 (16 ELEMENTS)

WRITE FOR CATALOG

Cush

621 Hayward Street

A FULL LINE OF

USII Craft

AMATEUR COMMUNICATION

Manchester. N. H. Craft

ANTENNAS

The other wire is fastened to the center. At the other end the ribbon is simply shorted together with an insulator installed (see sketch). Fastened to the insulator is about 30 feet of heavy sash cord.

On the trailer near the top on one side, I am using a 4 inch coax feed thru fitting. On the inside of the trailer I use approximately 3 feet of 50 ohm coax to get to the station. In addition to the antenna system, I have a small metal stake with a wire about 3 feet long and a battery clip fastened to the end.

Once I have arrived at the desired camp site and parked the trailer, all that is necessary is to screw the coax fitting on the feed thru near the top side of the trailer, pick out a convenient tree about 65 feet away, tie a pair of pliers or a weight on the sash cord, toss it up over a limb, pull the antenna tight, push the ground rod in and fasten the battery clip to radio ground. Then on the air I go.

In every case the antenna height should be 8 feet above ground at the trailer end and about 30 feet at the far end.

The antenna is essentially the same as a commercial Unipole which normally sets vertically with 4 radials at 90 degrees and the impedance match is approximately 50 ohms. This antenna works somewhat the same except it is erected horizontally. The return wire to ground lowers the ground resistance, causing the antenna to radiate more efficiently. This antenna doesn't radiate as well as a folded dipole, however, its efficiency is very close. At 3.9 mc the swr should be 1.5 to 1 or less.

Height has a great effect on the feed point impedance. In other words, if the antenna wire were raised at the feed end the swr might go up as high as 5-1. Whenever the antenna is used under the conditions listed, its efficiency is at optimum.

The same antenna could be used on many other frequencies, in fact it lends itself beautifully to 160 meter operation. The formula for figuring the length in feet for the 300 ohm ribbon is 234 divided by frequency in megacycles.

I hope this will give some of you fellows some new ideas on portable antennas. ... W8LCU

WALKIE-TALKIE RADIOPHONES



from

2498

Send for free literature on the Springfield semikits and Vanguard factory assembled radiophones. All models are fully transistorized and are available with either superregenerative or su-

perhet receivers. Printed circuit converters also available. We have been supplying amateurs and industry direct from our factory since 1951.

VANGUARD ELECTRONIC LABS

190-48 99th AVENUE . Dept. H-3 . HOLLIS 23, N. Y.

NEW

T-R SWITCH

MODEL 381


...with selectable bandswitching


This compact electronic T-R switch (4¾" x 4" x 4½") does a big job in automatic break-in operation on CW-SSB-AM-DSB. Bandswitch covers 80 through 10 meter bands. Integral power supply. For commercial applications, it will handle more than 1KW AM phone and up to 5KW SSB. "Failsafe" design automatically keeps transmitter connected to antenna when unit is not energized. Matches 52-75 ohm coaxial lines.

This is the switch you've been looking for. See it at your local dealer, or write the factory direct.

Barker & Williamson, Inc.

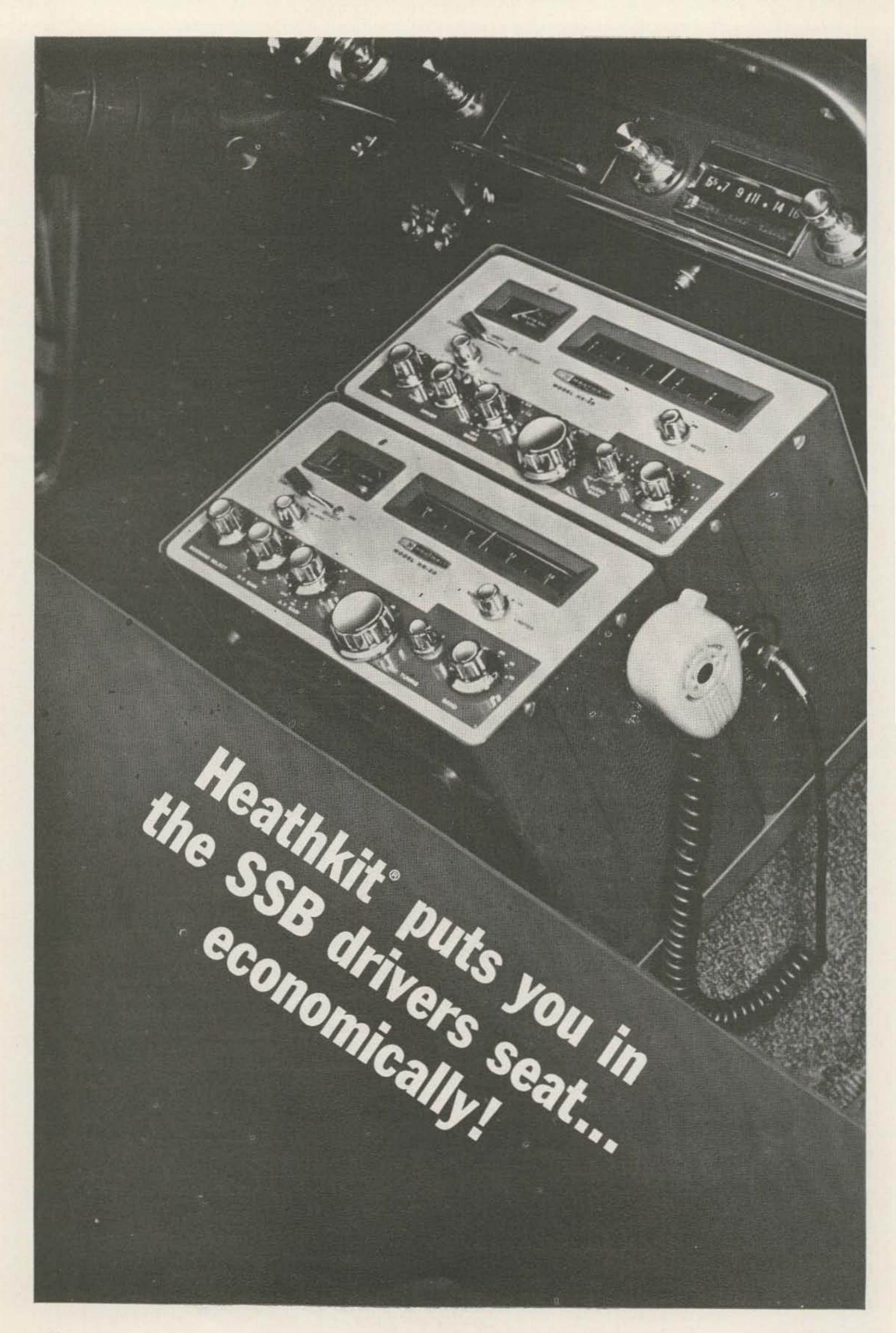Canal Street & Beaver Dam Road Bristol, Pennsylvania



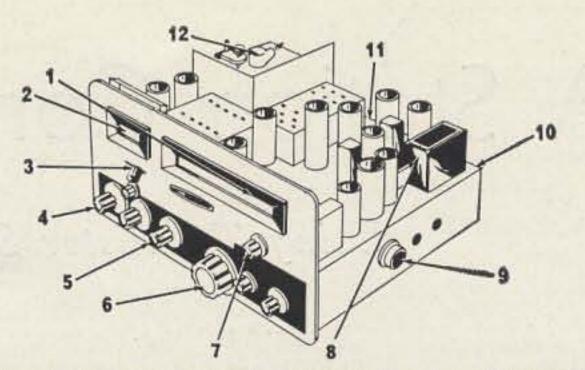


HEATHKIT HX-20 SSB MOBILE TRANSMITTER... A SENSATIONAL VALUE AT ONLY \$199.95

1. Easy-to-read, edge-lighted, slide-rule dial 2. Relative power output indicator for ease of tuning 3. Spot function for zero-beat or talk-on frequency setting 4. Fixed 50 ohm loading for easy tuneup 5. Bandswitching 80 through 10 meters—all crystals furnished 6. Full gear drive vernier VFO tuning 7. Mode switch for LSB, USB or CW 8. Hermetically sealed crystal bandpass filter 9. VOX or push-to-talk operation 10. External linear amplifier cutoff bias 11. Built-in antenna relay plus external antenna relay control 12. 6146 for 90 watts P.E.P. input. Automatic level control for maximum talk power, low distortion Crystal control, dual conversion, heterodyne circuitry. Frequency stability 100 cps overall, after warm-up. 50 db carrier suppression, 55 db unwanted sideband suppression.

SSB Portable, fixed station or mobile

\$39500 with power

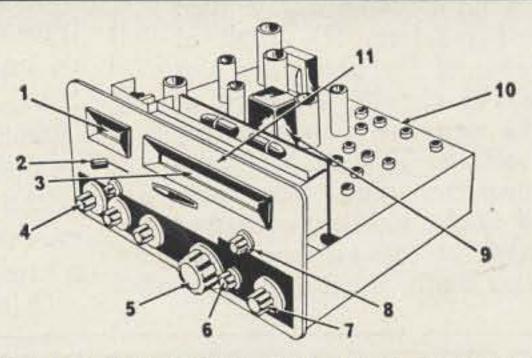All the features you want and need for top mobile performance. Handsomely styled with die-cast panel, chrome-plated knobs. Units require only 1 cubic foot of space for easy installation in auto. Rack mounting allows easy removal for fixed or portable use. Operates with Heathkit HP-10 or HP-20 power supplies. Here's quality, economy and versatility that can't be beat anywhere!



HEATHKIT HR-20 SSB MOBILE RECEIVER . . . MANY EXTRAS FOR TOP PERFORMANCE \$134.50

1. Built-in calibrated "S" meter 2. Fast or slow AVC selection 3. Rotating slide rule dial 4. Crystal controlled BFO for selectable sideband reception 5. 30-1 gear drive vernier tuning 6. Antenna tuning control, 1 uv sensitivity on all bands 7. Full coverage 80 through 10 meters 8. Series noise limiter for AM reception 9. Crystal bandpass I.F. filter 10. Additional 500 ohm output for anti-trip circuit or headset 11. Die-cast control panel & knobs. Product detector for SSB & CW, diode detector for AM. Fully compatible for use with HX-20. Excellent mechanical and electrical stability.



FREE Catalog!

Send in today for your free 100-page catalog. Over 250 kits in this most complete catalog of kits. Every piece is top quality . . . save up to 50%



HEATH COMPANY Benton Harbor 11, Michigan

Please send my FREE 100 page 1962 Heathkit Catalog


Name_____

Address

City_____State_____

A Station Control Unit

Using Transistor Switches

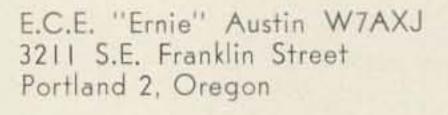

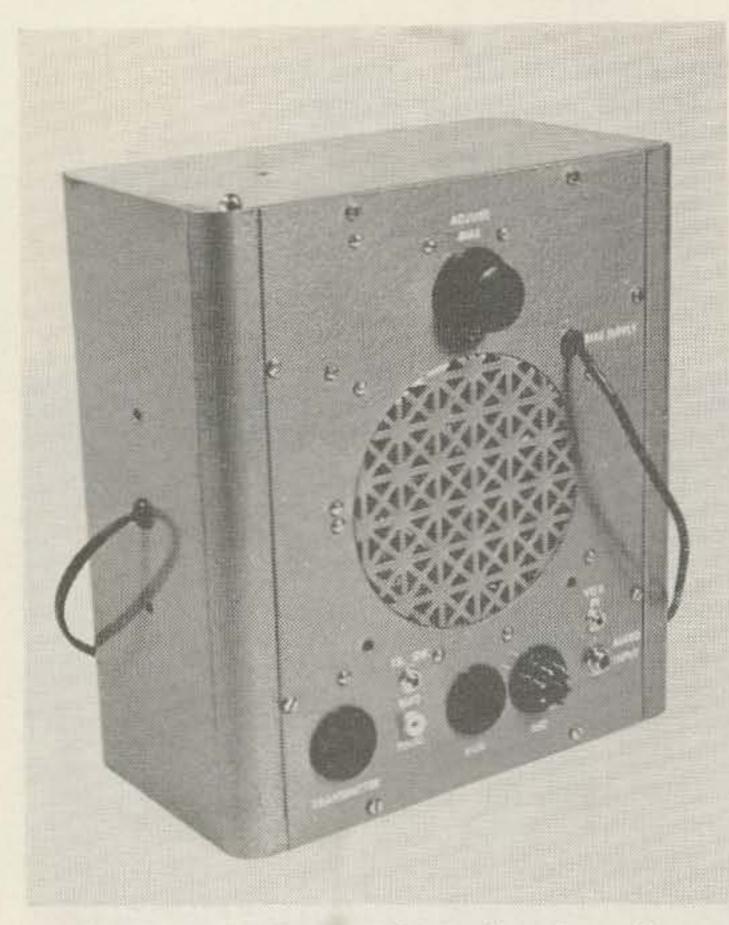


Fig. 1. 5" x 91/2" x 101/2" loudspeaker cabinet containing interconnecting circuitry for a ham station transmitter and receiver. The knob at the top is for adjustment of the operating bias for the transistor break-in circuit. The cord at the right connects the negative power supply which is used to cut off the TR switch. Across the bottom are: transmitter plug, bias jacks for the TR switch and final amplifier, accessory plug, receiver plug and, at the extreme right, the VOX input and audio input jacks.


Picture by Deane Bond

The small size and relatively simple wiring layouts for transistors make them lend themselves to small equipment units without requiring special miniaturizing techniques. The station control unit shown in Fig. 1 is a good example. The speaker box, which is 5" x 9½" x 10½" in size, houses all of the accessories required to connect a transmitter and a receiver together to form a complete station, except a small bias supply and a TR switch. There is enough space left in the box for these also, if desirable.

The speaker box contains a 5" x 9" oval speaker, a W5LAN "Transistorized Electronic Key," (QST, May, 1959), an AC supply for the key, a "Break-In a la Transwitch" circuit, additional transistor circuitry to provide for VOX operation without relays and all of the necessary wiring to interconnect the transmitter and receiver.

Fig. 2 shows the interior of the box. The transmitter and receiver plugs are extended to connecting blocks to simplify inter-connection. The plugs and connecting blocks are attached to the removable back of the loud speaker cabinet. Jacks for taking cut-off bias to the TR switch and final amplifier make it easier to rearrange the station or to remove a unit for servicing.

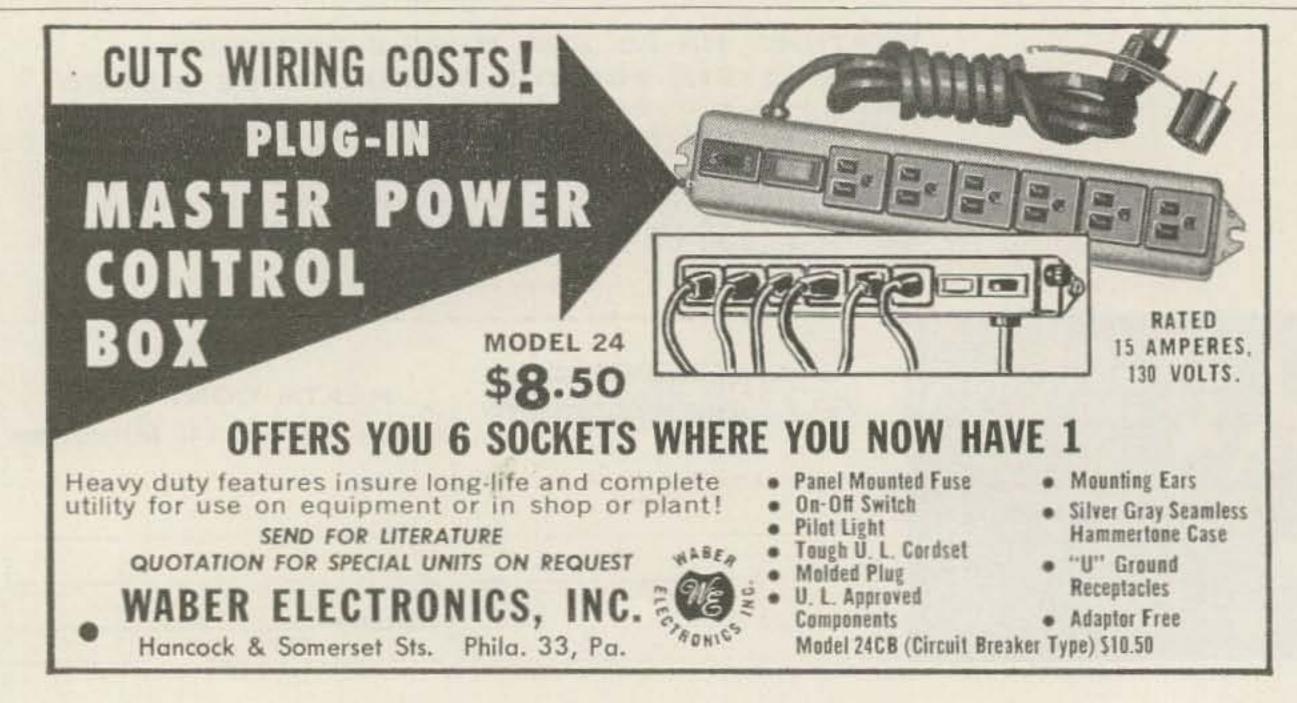Also fastened to the cabinet back is a home-



made chassis on which is mounted the "Transwitch" circuit. A multivibrator circuit, connecting the transmitter "VOX" circuit to the "Transwitch" circuit, and a bias circuit for cutting off the final amplifier while receiving have also been mounted on the chassis. This circuitry will be the subject of a later article.

Notice the small line-to-voice coil transformer at the lower right. This is used to permit taking the receiver output through the "anti-trip" circuit in the transmitter at a 500 ohm impedance level, cutting it to 3.2 ohms for the speaker voice coil. This increases the amount of control available for adjusting the anti-trip feature.

Inside the speaker cabinet can be seen the "Electronic Key" unit and the loudspeaker. Out of sight at the right is a small 22½ volt dc supply for the "Key." This accounts for the power cord seen in Fig. 1. Controls for the electronic bug and the "Muting Level Control" are mounted on the face of the cabinet.

The construction of the unit is as simple as the pictures make it appear. There is plenty of space under the transistor chassis for all of the resistors, condensers and wiring for the circuits without crowding or creating difficult assembly problems.

The box is adequately ventilated to dissipate the small amount of heat generated in the circuits.

This unit was developed to permit using the main station HT-32 and SX-88 in our 23 foot house trailer for those times when weather or darkness keeps us off our favorite mountain lake. The whole assembly is powered by a light plant mounted in the trunk of our car. But that's another story! ... W7AXJ


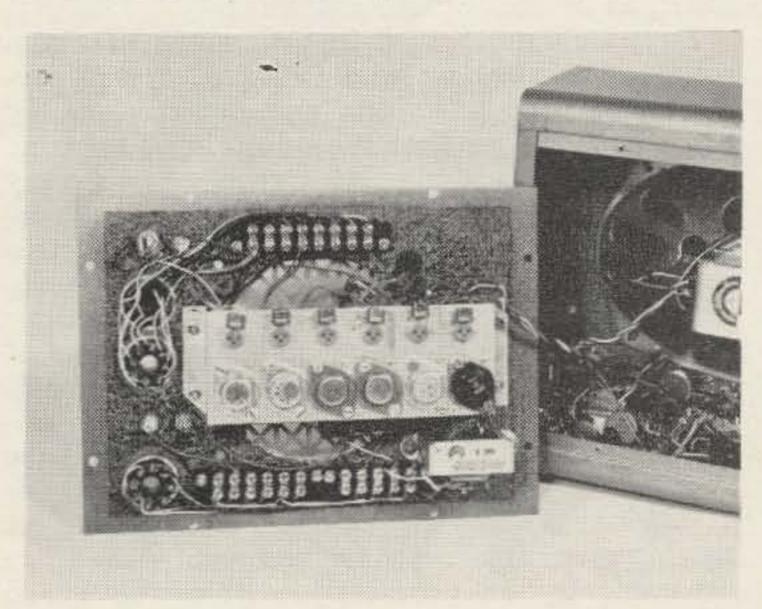


Fig. 2. Interior view of the control unit. The receiver and accessory plug are at the left, wired in parallel and extended to the connecting block at the top. The transmitter plug and connecting block, similarly connected, are at the bottom. The line-to-voice coil transformer is at the lower right. Across the middle is the transistor chassis. Inside the box can be seen the electronic bug components and the loud-speaker.

Picture by Deane Bond

NOW! TWO ANTENNAS IN ONE*

*another FIRST from FINCO

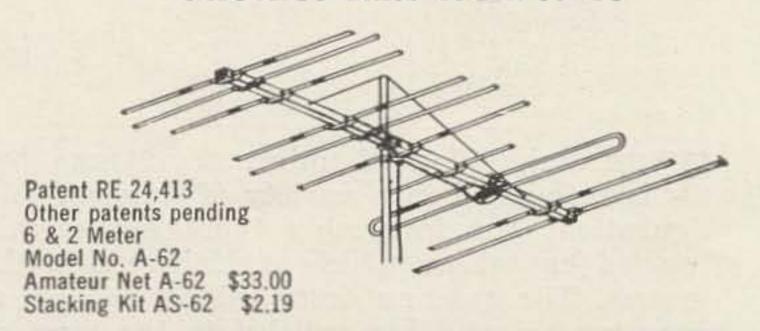

The Only Single Feed Line
6 & 2 METER
COMBINATION YAGI ANTENNA

from FINCO

- Heavy Duty Square Aluminum Boom, 10 Ft. Long
- All Elements are Sleeve Reinforced And Completely Pre-assembled With "Snap-Out" Lock-Tite Brackets
- Boom Suspension Rods Are Supplied Completely Pre-assembled, Ready To Be Snapped Into Upper End Of Mast

ON 2 METERS:

18 Elements

1—Folded Dipole Plus Special Phasing Stub

1-3 Element Collinear Reflector

4-3 Element Collinear Directors

ON 6 METERS:


Full 4 Elements

1—Folded


Dipole

1—Reflector


2-Directors

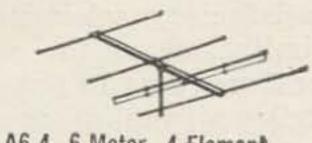

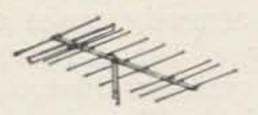A6-4 6 Meter 4 Element Amateur Net \$17.16 Stacking Kit AS-6 \$2.19



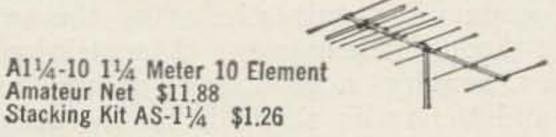A2-10 2 Meter 10 Element Amateur Net \$11.88 Stacking Kit AS-2 \$1.83



See Your FINCO Distributor or write for Catalog 20-226 to: THE FINNEY COMPANY Dept. 20, 34 W. Interstate St., Bedford, Ohio

A Universal Antenna

and some

Comparative Measurements

John Ellison W6AOI 1720 Holly Ave. Capt. U.S.N. (ret.) Menlo Park, California

The designation of universal antenna has been applied to a variety of antenna conbeen applied to a variety of antenna configurations but invariably there are certain implied limitations which are inherent in the system. The antenna described herein is perhaps more justifiably entitled to the term of "universal antenna" from several viewpoints. Before enumerating them, let me hasten to disclaim any "exotic circuitry," "sophisticated configuration" or "technilogical breakthrough!" This is a review of a time-tested horizontal antenna system in the light of present day knowledge and equipment available to the amateur which can assure proper adjust-

ment for maximum performance.

The designation of universal antenna is applied chiefly for two important reasons, first, the system may be operated with no compromise of efficiency on not only any amateur band from 160 meters to 10 meters but also on practically any other frequencies between the amateur bands, such as are used for Army, Air Force MARS and the Naval Communication Reserve. Second, the antenna can be erected on practically any residential lot and lends itself to nearly any conceivable topographical arrangements of trees, houses and the like. Considering these two reasons we note that perhaps the chief perennial problem that besets the amateur seeking a suitable antenna system is not lack of information but rather an excess of information, so much so that he can scarcely make a satisfactory selection in view of the different limitations of the various systems. Just to mention a few in passing (which will probably strike a familiar nostalgic note for many), system A requires the shack to be about mid-way between the skyhooks, system B requires bringing the antenna hot end through the house to the shack location. system C requires a good short ground connection (and the radio shack is on the second or third floor!) system D requires tuned feeders (which are invariably too long or too short) system E will work on only one band, system F requires a few acres, system G requires only one mast (about 100 feet high!) and so on. paratively little directivity experienced so

Everyone can recall going through this phase of deciding on what to put up and where. Most of our amateur heritage of antenna knowledge stems from the time when all transmitters were home-built, and band-switching transmitters were not too widely used. With such transmitters a single band or two band antenna was adequate. However, with the present day commercially built complete transmitters or kits, there exists a transmitter capability which cannot be exercised with many of the simple antenna systems in vogue. Even though the operator may confine his operations largely to one or two bands, he would like to "visit occasionally" on some of the other bands. He may also want to join the MARS or NCR nets, although this desire is frequently circumvented as much by the frequency limitations of commercially built equipment, as by inadequate antennas.

Suppose we start off in pedagogical fashion considering what we would like to have in performance versus what we can reasonably achieve. Consider first the question of antenna height. Height in absolute terms is necessary only to get reasonably clear of adjacent structures. With reasonable clearance of this nature, height becomes related to frequency and is more properly considered in fractions of wavelength rather than in feet. In terms of wavelength, if we want to get low angle radiation of 30° or less we have to get the antenna up at least a half wavelength above ground. It is immediately apparent that for 160, 80 or 40 meters we are not about to get up high enough with any supports that are economically or physically within the grasp of the average amateur. So we accept this fact and consider what we can get with limited height and we learn that the major radiation we will get is mostly high angle, 60° or more. Actually, this is not a serious disadvantage since it gives us fairly solid coverage within the range of most contacts on these frequencies, under average propagation and QRM conditions. By the same token, there is comthat for all practical purposes the antenna is omnidirectional. This feature is particularly attractive for Net operations.

Last but not least, there is considerably greater freedom from multipath transmissions (fading) with high angle radiation. On 20, 15 and 10 meters (when they are open) where long distance contacts are sought we would like low angle radiation, and at these frequencies a half wavelength or more in actual feet becomes quite reasonable. So in summary, we may properly conclude that an average height of 35 feet would be quite satisfactory for an all-band antenna, or even as low as 30 feet will not be unacceptable. This height is easily within the reach of any amateur in view of house and tree heights and economical telescoping TV antenna masts. This is one of those rare occasions where what we can attain within reason is just about what we would like to have.

Next let us discuss the questions of antenna location and length. These two must be considered together. Naturally, the antenna must be located reasonably in the clear if we are not to lose too much power by absorption in adjacent structures in the strong antenna field. However, clear areas may not accommodate the required length, and in many cases, the length required for a low frequency antenna just isn't available anywhere on the property. In these cases we are told that we can bend the low current ends without reducing the efficiency seriously, and thereby squeeze the antenna into the available space. Now, if it were possible to combine the bent end with the flat top to get the length and use the former as the feed system we would be getting closer to an answer. There are disadvantages in bringing the antenna end into the shack, but if we bring the bent end down to a matching network, several desirable aims may be achieved. We may bring the bent end down wherever it is physically and electrically most suitable, the bent end/feeder end reduces the linear space required for a given antenna length, the matching network may be connected at the bent down end where it is conveniently accessible for tuning and adjustment, the antenna can be tuned to any desired frequency or harmonic and the matching net can be fed with a low impedance line such as coax of any length running to the transmitter location.

Now that we have reviewed the general picture, let us get down to practical cases. First, it must be realized that this is a fundamental and harmonic operated antenna, and as such, has no gain over other fundamental or harmonic antenna types.

However, as distinct from many other types, it operates as a resonant system without compromise of efficiency on any frequency to which it is tuned, it may be conveniently and accurately tuned to any desired frequency and

NEW FOR SIX & TWO!



HIVERTER 50

Extends use of your present 14 Mc SSB, AM and CW Transmitter to 50 Mc Band

Tubes: 6CL6 Oscillator, 5763 Mixer, and 6146 Linear Amp., with 2-0B-2 Regulators.

Pi-Net Output to match 50-100 ohm Antenna Load

Cabinet Size: 8" x 7" x 10"

Power Supply Requirements; (Heathkit HP-20 or similar)
6.3 V. AC-2.7 Amps (Filaments)
300 V. DC-60 Ma. (Osc.-Mixer)
600 V. DC-120 Ma. (Amplifier)
-130 V. DC-(Amp. Bias)

PREVERTER 50 & 144



Uses Low moise Phileo Transistor - Less than 3 Db on 6M, 3.5 Db on 2M


Efficient - Requires 1.25 Ma at 12 V. DC

Input and output 50 Ohm, with connectors for RG 8/U Bendpass circuitry gives full 4 Mc response on both Bands.

Rugged and Low loss construction with silver plated chassis and input circuits.

WRITE FOR COMPLETE INFORMATION

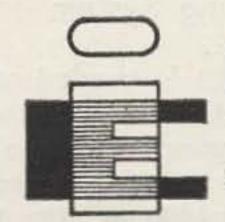HIVERTER-COMPLETE WITH TUBES AND
CRYSTAL, LESS POWER SUPPLY\$99.50
3 Db PAD-FOR 20-50 WATT EXCITERS \$ 6.00
6 Db PAD-FOR 50-100 WATT EXCITERS\$10.50
PREVERTER 50-6 METER PREAMP\$14.95
PREVERTER 144-2 METER PREAMP\$14.95



Irving Electronics

P. O. Box 9222 San Antonio 4, Texas it may be fed with a flat (non-resonant) line of any convenient length. This insures the maximum performance of the antenna as a radiating system and the maximum freedom from critical feeder lengths when changing frequencies.

The antenna height has previously been indicated as 35 feet. The over all antenna length should be chosen so that it is slightly short for the highest frequency we expect to use. The purpose in making the antenna slightly short is to permit resonating it to any desired frequency or harmonic with a loading coil only. If we just picked a random length we would find some frequencies where a series condenser instead of a series coil would be required. This would introduce an additional tuning element with no compensating advantage. So we make up a table using the Handbook formula for lengths at various frequencies.

Length (ft) = (Number of half waves - 0.95) × 492

	Freq. in mc	
Freq	Resonant Mode	Length inFt.
3295	½ wave	142
4000	½ wave	117
7300	1 wave	131.5
7832.5	1 wave	122.5
14350	2 wave	135.7
	5	
21450	— or 3 wave	113.5 or 136.5
	2	
20700	7	222
29700	— or 4 wave	115 or 131.7
	2	The tellectual oat

From the above table we select the maximum length of our wire antenna as 113.5 feet and then reduce that figure by an allowance for the length of the ground lead and something for the resonating coil. Actually, in practice, it turns out that a length of about 105 feet is satisfactory, but it can be even less, realizing that a shorter length simply requires more turns on the resonating coil. This 105 foot length is the length of the flat-top portion plus the vertical portion down to the coupling network. If the vertical portion is 35 feet, we need a horizontal top of 70 feet. If space does not permit a 70 foot run, bend the far end down or sideways to get the required over all length. As you can see, the length is not too critical.

Resonating and Coupling System

The downlead of the antenna is tapped onto a coil which in turn is connected to the matching network. It will be necessary to be able to tap onto any turn of the coil for reasons which will be explained later. Hence, for the antenna coil a 38 turn coil, 3 inches in diam-

eter at 8 turns per inch is used. This is half of a standard ten inch length of AIRDUX #2408 and with the 8 turn per inch pitch it is possible to clip on to any turn. There is one catch I should warn you about right here! Note that if a coil is at the very end of the antenna where it connects to the matching network the vanishingly small antenna current makes the coil inductance almost ineffective. But if we put the coil in from the antenna end a few feet we have moved up on the antenna current curve sufficiently to get an inductive loading effect with a reasonably small coil. In the actual antenna herein described, the 38 turn coil (52 microH) and a 3 foot lead from the coil to the coupling network made a suitable combination.

The coupling network is an L net which must match the end impedance of the resonated antenna to the impedance of the coax feedline. An L net is the simplest and most efficient form of impedance matching known but as a rule it is not a trial and error device. Usually, the two impedances to be matched must be known within a few percent, whereupon the calculation becomes very simple. For the sake of completeness, I am going to digress briefly on the subject of end impedance of a resonant antenna system. This is not a rigorous approach nor on the other hand is it "cracker-barrel" theory,-let's call it a median approach. The technical literature is quite vague on the subject at hand unless you have infinite time and unlimited access to all printed matter. The value of the end point impedance is affected by the height above ground, wire size, proximity to structure, antenna configuration, mode of operation and other variables, -probably including "Murphy's Law." With so many intangibles to reckon with, the best we can do is to take a statement in the reference books that tells us that for a half wave antenna a quarter wave above ground the end impedance is on the order of 15,000 ohms. As the frequency is raised the physical height in terms of wavelength changes and the impedance becomes less, the minimum value being on the order of 3000-3500 ohms for wire antennas. This is of interest only when making the first approximations to get started on the L net design. From experimenting with this antenna to achieve a practically perfect match, and then from the net values working backwards to calculate the antenna impedance, it appears that the maximum value (which occurs at half wave operation at the lowest frequency) is between 9000 and 10,000 ohms. This means in actual practice, that the L net constants for all our purposes can be met with a multi-tapped coil whose maximum inductance is about 45 micro-henries and a variable condenser with a 20-120 mmf. range. The remaining half of the 10 inch length of AIR-DUX coil will do admirably for the L net inductance and should have about 12 taps run

from it to a switch. One word of caution,-the

end voltages are high! The condenser should have spacing for 1500 volts for medium power rigs and 2000 for high power rigs and the switch should have comparable insulation. The coil should be tapped to short out turns from the maximum value about as follows:

777	1 . 1	100	-4
Ta	n	0	1.
T 0	130	LC.	1

	Active	Approximate
Tap	coil turns	band suitability
1	whole coil	
2	29	80 meter
2 3	25	80 meter
	21	
4 5	16	40 meter
6	14	40 meter
7	12	
8 9	6	
9	5	20 meter
10	4	20 meter
11	3	15 meter
12	1	10 meter

The antenna coil taps may vary considerably from one installation to another because the antenna end impedance will vary with the local installation conditions but in general they will follow this pattern:

	Table 2.
Freq.	Active coil turns
3.3	38.5
3.6	36.5
3.8	36.5
4.0	36.5
7.15	17.5
7.83	12.5
14.3	8.5
21.3	3.5 or 9.5
29.0	1.5 or 7.5

Tuning and Adjusting

The antenna, network and transmitter are connected together as shown in Fig. 1.

Since we do not know the end point impedance of the resonant antenna at the various frequencies we have to get the proper match indirectly. We do know, however, that there are three points on a resonant antenna where the current and voltage are 180° out of phase, namely, at the middle of a current loop and at the ends of the antenna. At these points, and only these points, can we get a purely resistive load, without providing some reactance compensation in the coupling device. So, to get the antenna resonant we use a SWR bridge or preferably a reflected power meter (or directional coupler, as it is also called) in the coax line. Then, if we can effect a proper impedance match the transmitter will load to its proper value.

1. For theory of L net design see GRAMMER, QST, March 1957. For practical application to antenna matching see my article CQ, July 1960.

HARMONIC PROBLEMS?



WE HAVE THE SOLUTION FOR YOU
IN THIS NEW SERIES OF FILTERS
WITH EXCEPTIONALLY LOW
INSERTION LOSSES

6 METERS

"MAVERICK" The only low pass filter designed expressly for 6 meters. With 9 individually shielded sections and 5 stages tuneable forming a composite filter of unequaled performance. Providing the sharpest cutoff, the highest attenuation of harmonics with the lowest insertion losses.

Less than 1 DB loss on the 6 meter band. Accepts up to 400 watts at antenna. An honest 35 DB rejection of the harmonics of 8 mc crystals and other spurious signals in the Channel 2 band.

Size 5" by 2" by 3".

Price \$16.95

"MAVERICK II" Same as above but with 6 meter power indicator calibrated in watts output. Supplied with 4 foot cable which plugs into receptical on filter.

Indicator Size 4" by 4" by 4%".
Slant Face. Price \$29.75

80 THRU 10 METERS

"MODEL F810" — Here's 5 separate filters housed in one package. One for each band, and are selected by a front panel switch. Each filter consists of 2 shielded stages of the constant K type and is tuned for maximum attenuation of the second harmonic for that particular band. Band switching of filters that are designed for each specific band is obviously superior to any single, broad band, filter. Resulting in greater attenuation of second harmonic with less insertion loss. Second Harmonic Attenuation — 35 DB. Insertion Loss — Less than ½ DB. Accepts up to 1 kw. Price \$24.95


PRICES INCLUDE SHIPPING COST

Available direct or through the following Federated Purchaser Stores:

1021 U. S. Rte. 22, Mountainside, N. J.
114 Hudson St., Newark, N. J.
483 Broad St., Shrewsbury, N. J.
1115 Hamilton St., Allentown, Penna.
925 Northampton St., Easton, Penna.
11275 W. Olympic Blvd., Los Angeles, Cal.
Write for complete brochures.

GAVIN INSTRUMENTS, INC.

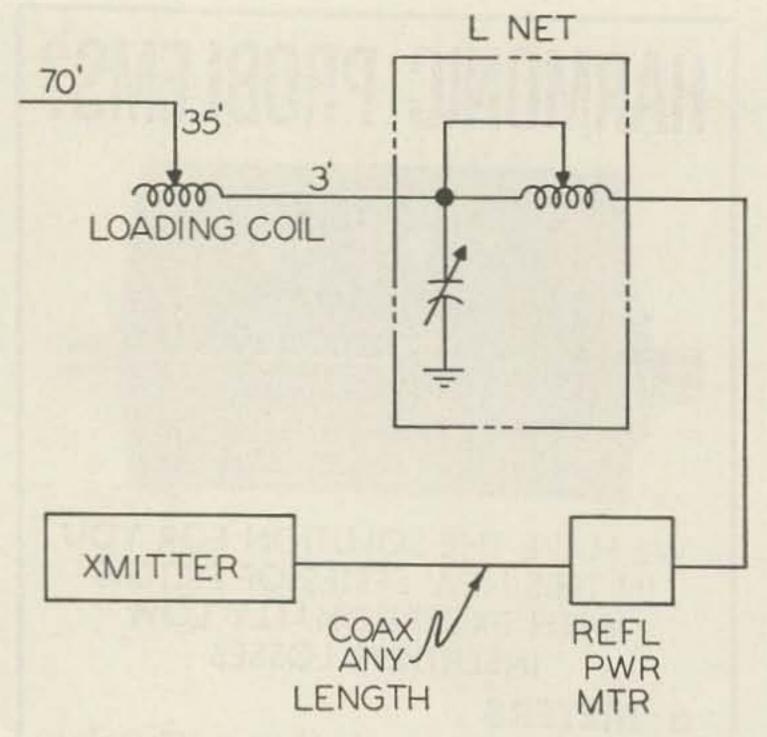POST OFFICE BOX 413 SOMERVILLE, NEW JERSEY



Because of interaction among the various elements of the system, the following adjustment method is recommended as the simplest and most foolproof. Since the L net acts not only as an impedance matching device but is also capable of compensating to a minor degree for a reactive component in the antenna it is necessary first to have one part of the entire system accurately and finally set, and second to have a means of measuring power transfer. The one part that must be set first is the transmitter. It must be tuned up to a non-reactive load (resistors only!) and its control settings logged and kept constant while the remainder of the system is adjusted. You understand, of course, that this procedure is necessary only when making the first adjustments of the entire system. Once the settings of taps, condensers, controls, etc. are found they can be recorded and thereafter changing bands is quick and accurate,—and dependable. This eliminates, permanently, the oft-repeated phrase on the air, "Just a moment while I dip my final tank." This is not only unnecessary but if resorted to will definitely "louse up" the entire system. This may come as a terrible blow to the characters who like to "peak it up a bit." The second step requires as an absolute necessity, a reflected power meter. Either buy a kit or build the one in the late ARRL Handbook. The latter is simple and easy and inexpensive, and may be left in the line as a continuous monitor.

The actual detailed steps are, first, tune up the transmitter to the dummy load of 52 ohms. You can and should use reduced power for this tune up as long as you maintain the ratio of plate voltage to plate current the same as it will be at full power. This maintains a constant "generator impedance" from the final into the transmitter coupling system to the coax line. Next, couple up the transmitter to the coax line, coax line to the L net and L net to the antenna and loading coil.

Set the L net inductance tap and the antenna coil tap from tables 1 & 2. Set the reflected power meter to read reflected power and the transmitter at reduced power and tune the L net condenser through its range while observing the reflected power. There will be some setting where it will be lower than anywhere else. Then add or subtract antenna coil turns, retuning the L net condenser each time, until the reflected power goes practically to zero, which it will at some setting. This establishes antenna resonance for that particular frequency,-all your power is going out. Then check the transmitter loading at normal power input. If it is low or high, reduce or increase the L Net inductance and retune the L net condenser for minimum reflected power. This establishes the proper impedance match to give proper transmitter loading. The question may arise regarding the use of a Pi net or link coupling between the antenna and the coax rather than the L net. Calculations will show that since an L net is a rudimentary Pi net (one condenser having zero capacity) any other Pi net will of necessity have a higher Q than an L net. Since the high impedance transformation already requires a high Q, we would prefer a system which has the least "high Q" to obviate retuning within a band, -this dictates the use of the L net. The mechanical considerations, inflexibility and unpredictability of link coupling rules it out completely for this use. Another word of caution on constructing this antenna system. A moment's consideration will make it immediately apparent that the 3 foot length of antenna between the loading coil and the L network will be extremely sensitive to any physical movement since it has a small capacity to ground which in effect is "tuning" a large inductance. Any shift in position of the 3 foot length will throw off all your various band settings. You can avoid this by using a rigid rod (such as a 3 foot length of one-eighth brass brazing rod) mounted on stand-off insulators between the antenna loading coil and the L network. If this is done before any tune up measurements are made you will avoid a lot of trouble. This effect we are dodging is similar to the detuning effect of the swaying tip on a mobile antenna.

Operation

Because the antenna is loaded with lumped constants, the Q is higher than with a conventional full length wire antenna. This means in practice that retuning will be required if the percent frequency change is large, such as when going from one end of the 80 meter band to the other. However, not many transmitters will accept such wide frequency changes without retuning, either. You will find when using this antenna for receiving, that the high Q is a distinct advantage as it peaks up noticeably those signals which are in the

OPERATE MOBILE WITH FIXED STATION RESULTS


ON 10-15-30-40-75 METERS

NEW-TRONICS MOBILE ANTENNA

You can reach unlimited distances and get exceptional transceiving results on every band with this outstanding mobile assembly. Buy only the mast and resonators for the band you operate. No need for matching devices, use any feed line length of 52 ohm cable. Each of the five resonators has a coil specially designed for maximum radiation for a particular band. Center frequency tuning is by means of an adjustable stainless steel rod in the resonator.

The 54-inch fold over, heat treated, ½" aluminum mast permits instantaneous interchange of resonators. The outstanding feature of the mast is that it can be folded over for entering garage or carport. When operating the mast and resonator assembly

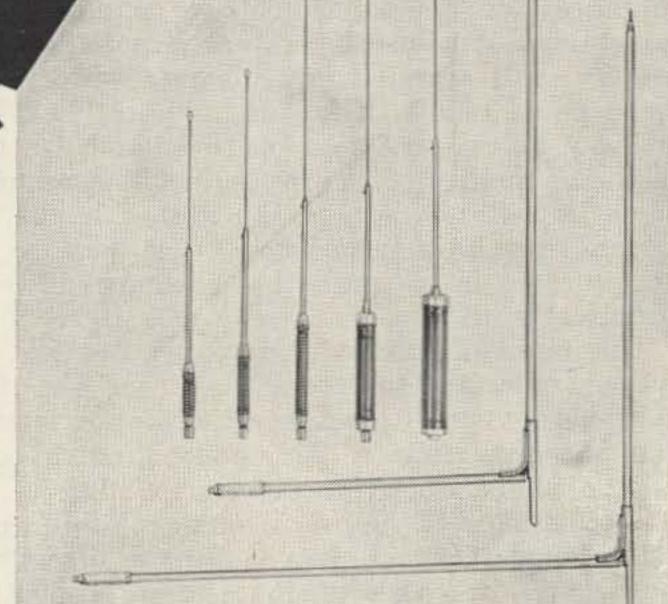is erected to full height. The two sections of the permanently hinged mast are held rigidly in the vertical position by a shake proof sleeve clutch arrangement. Mast has \\ \frac{3}{8}-24 \text{ base stud to fit all standard mobile mounts. SWR is less than 2 to 1 for any center frequency range within the band. Power rating: A.M., dc input 75W; SSB, dc input 250W. PEP.



ANTENNA ASSEMBLY CONSISTS OF:

Part No.	Description	Total Height of Antenna	Amateur Net
MO-1	54" Mast folds at 15" from base	(For Rear Deck or Fender Mount)	\$ 7.95
MO-2	54" Mast folds at 27" from base	(For Bumper Mount)	7.95
RM-10	10 Meter Resonator	Maximum 80" — Minimum 75"	5.95
RM-15	15 Meter Resonator	Maximum 81" — Minimum 76"	6.95
RM-20	20 Meter Resonator	Maximum 83" — Minimum 78"	7.95
RM-40	40 Meter Resonator	Maximum 92" — Minimum 87"	9.95
RM-75	75 Meter Resonator	Maximum 97" - Minimum 91"	11.95


ANY MAST OR RESONATOR MAY BE PURCHASED SEPARATELY.

FITS MORE CARS THAN ANY OTHER BUMPER MOUNT!

MODEL BM-1 Flat alloy steel strap fits tightly against any shape bumper yet is inconspicuous. Length of strap permits its attachment to both large and small bumpers.

Assembly is held in place by two "J" bolts at the top of the bumper and strap clamp at the bottom. "J" bolts may be inserted between top of bumper and car body where clearance is as low as 1/4".

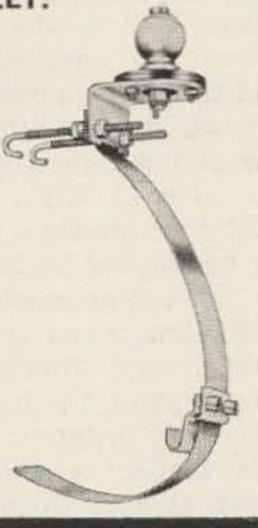See these outstanding NEW-TRONICS products at your electronics distributor. If he cannot supply you send check or money order for immediate delivery. Write for literature on the complete NEW-TRONICS line.



NEW-TRONICS DIVISION

3455 Vega Avenue . Cleveland 13, Ohio

pass band. Also, in retuning from say 3.5 kc to 3.9 kc it is possible to change either the antenna loading coil or the L net condenser. It is easier in practice to find one antenna coil tap for an entire band and use the reactance compensating feature of the L net which occurs automatically when retuning the L net condenser for minimum reflected power.

The use on 160 meters has been deliberately avoided up to now because it differs from the procedure on all other bands. For 160 meters simply by-pass the L net completely and connect the coax between the antenna loading coil and ground. This operates the antenna as a quarter-wave grounded antenna and the loading coil will permit tuning over a wide range from about 1650 kc to about 2200 kc. The SWR will not be over 1.5 to 1 on this band. On this band the quality of the ground system assumes some importance but on the higher bands the ground is relatively not important because the end current is so small that the power loss is practically nil.

One point of discussion remains, namely, the mixed polarization resulting from the fact that both vertical and horizontal portions of the antenna radiate. This may disturb some of the purists but for my part I find it not objectionable. It helps on some close-in contacts where transmission is by the direct ray path, and in cases of ionospheric reflection, both waves come down horizontally polarized in any case.

Comparative Tests

Now, since the ultimate proof is in the performance of the antenna in question, some comparative tests were run and are described below. No serious minded amateur is going to be content with mere impressions collected over a period of time when there are so many variable factors impossible to evaluate. I have in operation a 40 foot vertical that has been giving satisfactory service on frequencies from 3295 kc through 7832.5 kc over a four year period. It was decided to test the horizontal versus the vertical under as near identical conditions as possible. While this does not give an absolute measure of performance, it does give a comparative evaluation. A test was run on an A.F. MARS net on 3295 kc at night and another test was run on a different day net on 7832.5 kc. The test conditions were:

1. The transmitter was first loaded up to a 50 ohm resistive load to determine proper tuning, and thereafter the tuning controls were kept at the loading settings.

2. Each antenna was tuned up with its own coax feeder to show less than 1% reflected power (better than 1.2 to 1 SWR).

3. Each observer set his receiver rf gain at a level to give about half-scale reading on his S meter and did not touch any tuning control or gain during the test.

4. A two minute transmission was made on one antenna while the observers noted the average signal strength on their S meters.

5. The coax feedlines were shifted and a two minute transmission was made with the second antenna.

6. Each station then reported S meter strength for each antenna. Absolute S meter readings have little significance since they depend on location, receiver settings, receiver type, etc., but when normalized (i.e. reduced to a common base) they permit a direct comparison of the two antennas under as near identical simultaneous conditions as is possible to create. The significance of this is that since these were comparative tests, the same comparative performance might reasonably be expected at any location. For the night test on 3295 kc there were 12 stations reporting within a 70 mile radius and 3 stations at 350 miles. All stations reported better signals from the horizontal antenna and were reasonably consistent in an average advantage of 6-12 db in favor of the horizontal. For the daytime test on 7832.5 kc there were 25 reporting stations over a 500 mile radius. Most of them were within a 350 mile radius and their average report was a 12-18 db advantage in favor of the horizontal antenna. Those few stations around 500 miles reported that the two antennas were about equal. One other significant point in both the day and night tests was that nearly all stations remarked that signals from the horizontal antenna were much freer from fading or flutter. Only a few stations in either test were close enough to be receiving a direct signal so this represents nearly all skywave transmission. To avoid any possibility of the "brute force and ignorance" method overcoming antenna performance, these tests were run with a low power transmitter with a plate input of 95 watts. Because there were no operating nets on higher frequencies, no similar comparative tests were possible but the antenna has been operated on both 14 and 21 mc bands, when openings permitted, and the performance has been equally satisfactory.

As you may have surmised by now, this antenna was investigated primarily for the purpose of finding a system that would be completely satisfactory for several widely separated A.F. MARS frequencies as well as for the amateur bands. In this regard it has performed with considerable success, permitting rapid reliable shifts between bands with complete confidence in efficient operation and proper transmitter loading. However, the proven versatility has made it highly attractive for strictly amateur band use.

Credit must be given and acknowledgement is made for the assistance rendered in making the comparative tests by many of the members of the Conac West Coast Central division #2 and the members of the A.F. Western Technical Net. . . . W6AOI

One Tube VOX

Fred Cupp, K8AOE

For some obscure reason unknown to this writer, VOX operation seems to be used only by the sideband operators. VOX operation however is very practical for other modes and has been used with excellent results by the author for AM, FM, and MCW on six meters for at least six months. Perhaps the complexity of most VOX circuits drives operators away, so here is a simple yet effective VOX using only one tube which acts as the mike

pre-amp as well as the VOX.


The schematic diagram and parts values are shown in Fig. 1. V1a, one half of a 6AN8 is used as a conventional pentode audio pre-amp. The audio signal is coupled from the plate to the gain control and following stages of the modulator. The audio signal is also coupled into the .5 meg VOX Trip Level potentiometer. Audio from this pot is fed into the grid of V1b, the triode section of the 6AN8, and is amplified, appearing across the plate load resistor and relay. The audio is coupled from the plate and then rectified by the silicon diodes and charges the .25 mfd storage capacitor. This negative dc voltage is applied to the grid of V1b through the trip level potentiometer, thus changing the operating point of the triode. This reflex action allows the relay to de-energize thus turning on the transmitter.

This reflex circuit as it is known may be familiar to radio control model enthusiasts, as many R. C. receivers use this principle. The values in this adaptation have been optimized for use as a VOX circuit, however if the builder wishes to have more knobs to twist, the resistor across the storage capacitor may be replaced with a 5 meg. pot. This will allow the operator to set the amount of time delay

after he stops speaking.

Any plate relay of greater than 4K ohms resistance may be used in this circuit, and resistor Rx should be selected to give reliable pick-up of the relay with no audio input. With less sensitive relays it may be necessary to eliminate the resistor completely and also raise the plate voltage to get sufficient current. Be sure however to stay within the maximum current ratings of the tube. With a Potter-Brumfield #PW5LS, 10K ohm relay, Rx was 47K ohm. Germanium diodes such as the 1N34 or 1N38 will not work in this circuit as their reverse leakage is excessive. Silicon computer diodes such as the 1N457 or 1N660 are excellent but expensive. A very satisfactory compromise is the power silicon diode types 1N2069 through 1N2071. These have much greater current ratings than necessary but are quite inexpensive and work very well.


Fig. 2 shows the modifications necessary to add anti-vox to prevent receiver noise

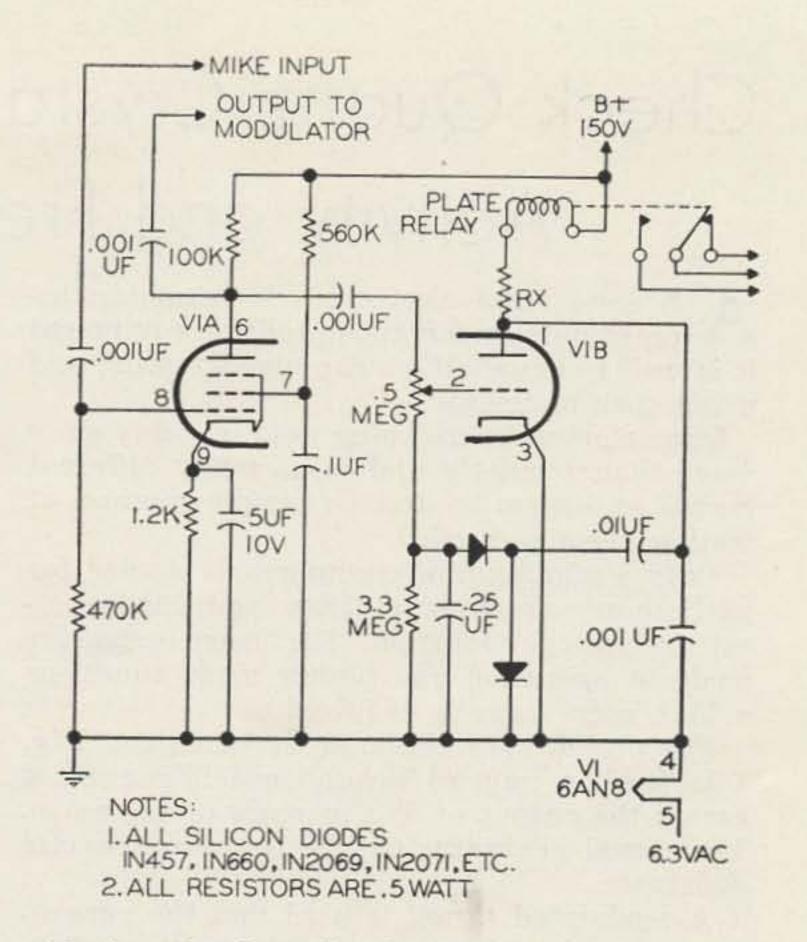

Audio from the receiver output is rectified positive and bucks the voltage from the VOX rectifier, thus preventing operation of the relay due to receiver noise. If your receiver has a 500 ohm output it may be applied directly to the diode as shown, or a 3.2 ohm speaker output may be stepped up with a small ac-dc radio type output transformer.

As with any VOX controlled station, the operator will have to condition himself to ignore the relays clicking in and out and also avoid the habit of saying, "Ahhh—Ummm—and Uhhh—," in an attempt to keep the station on the air when in reality he has nothing worthwhile to say but won't admit it. Just think how much quieter the band would be if VOX operation was mandatory!

... K8AOE

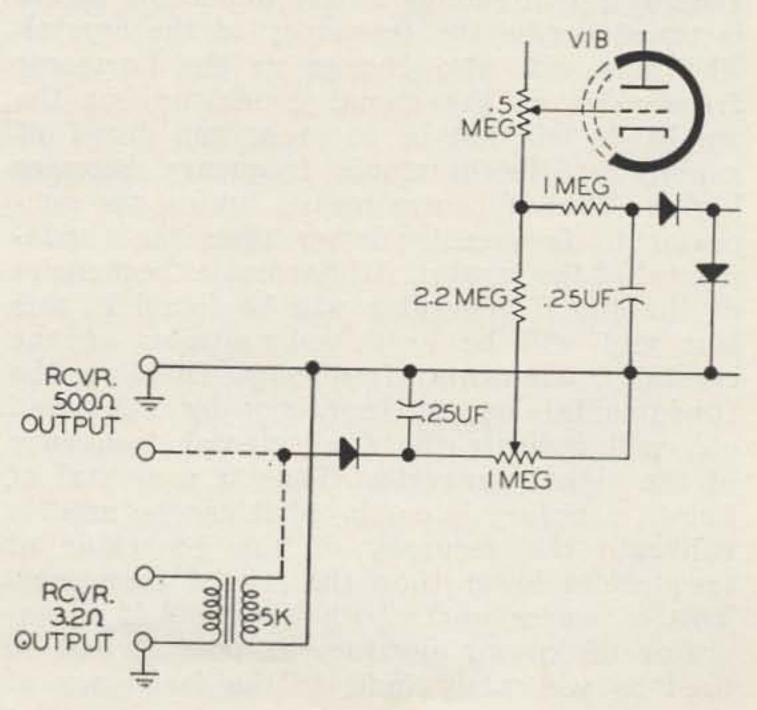

Check Quartz Crystal Activity and Frequency

Adam McLaren WøCGA 213 South 16th St. St. Joseph, Missouri

A S solid state electronics is becoming increasingly important in today's equipment it is well to know all we can about testing and using such materials.

Quartz crystals are being used in many more ways than formerly and in so many different modes of operation that a simple method of


testing them is needed.

Only a minimum of equipment is needed for preliminary checking activity and fundamental frequency operation. For more extensive mode of operation and higher mode functions a high gain scope is required.

For preliminary checking the circuit of Fig. 1 is used, a pair of headphones is connected across the output of T 2 in place of the scope. The signal generator can be the usual service

generator.

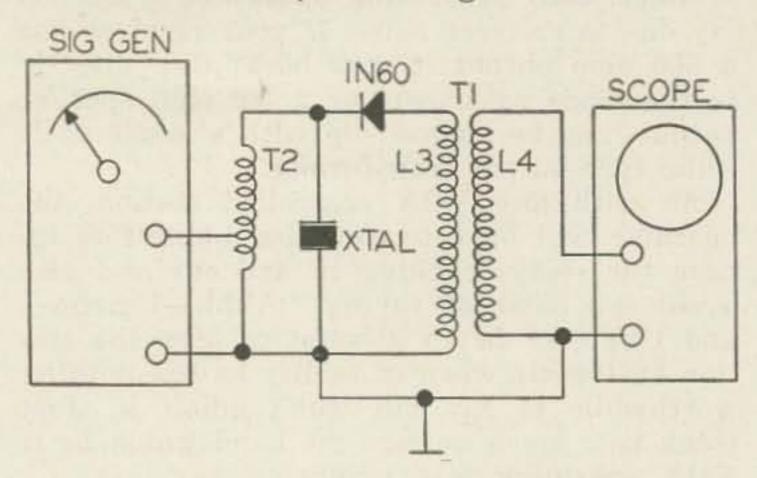A modulated signal is used and the generator is tuned to the approximate supposed fundamental frequency. These frequencies usually will be below 10 megacycles although crystals are made for frequencies higher than this.



The audio frequency tone from the signal generator will change as the generator signal is tuned across the frequency of the crystal. The tone will also change at the harmonic frequencies of the signal generator but the amplitude will not be as great and drops off rapidly as the harmonic frequency becomes higher. This of course means tuning the generator to frequencies lower than the fundamental of the crystal. All harmonic frequencies of the signal generator will be found in this test and will be exact submultiples of the crystal fundamental frequency. Dividing the fundamental crystal frequency by 2-3-4 and etc. will indicate the fundamental frequency of the signal generator. Thus if a crystal of known accuracy is employed it can be used to calibrate the accuracy of the generator at frequencies lower than the crystal frequency. This of course works both ways and if a generator of known accuracy is used it can be used to accurately indicate the frequency of

the crystal. If a high gain scope is used instead of headphones harmonic frequencies of the generator as high as the 10th. will be indicated.


When a crystal oscillates on an overtone it breaks down into layers and oscillates at odd harmonics of the fundamental. Multiplying the fundamental frequency by any odd number indicates the frequency of the higher mode at which the crystal will oscillate. Thus a 3910 kc crystal operating in the 3rd. mode would be 3910 kc multiplied by 3 equals 11,730 kc. Overtones are seldom exact multiples of the fundamental frequency. Ordinary crystals will usually operate very well on the 3rd. mode depending on the type of holder. Crystals ground for higher order mode operation will usually show greater activity at all higher modes.


For indicating higher mode operation of crystals the scope must be used. The indications on the scope show a notch in the sine wave pattern in much the same way as in receiver filter circuits. These points are very sharp and may be passed over if the generator is not tuned slowly.

The activity factor of the crystal is indicated by the depth and sharpness of the notch. A good active crystal will pull the notch down to almost the zero voltage line. Fig. 2 shows the sine wave with the notch shown in the

first half cycle of the scope pattern.

To check a crystal of unknown frequency tune the generator over a band of frequencies in which the crystal frequency is suspected to be. If an indication is found note the frequency and if this is the fundamental the next lower frequency of the generator at which an indication will be found will be one half the first frequency noted. Also if this is the fundamental frequency the next higher frequency at which an indication will be noted will be three times the first indication, or the 3rd mode. If this is true other indications will also be found at five or seven times the first frequency. Note that frequencies above the fundamental will never be indicated at 2-4-or 6

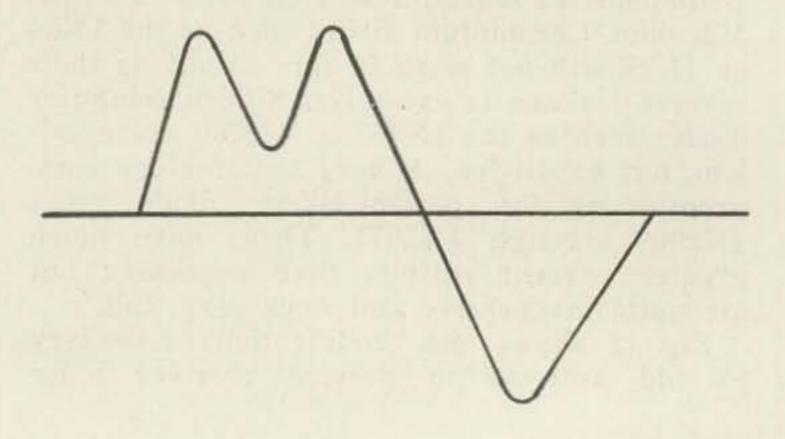

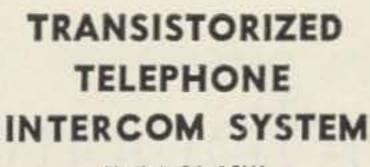



Model SA-10W

\$23.95 2-unit set

FULL-SIZE PHONES w/SPIRAL CORDS!

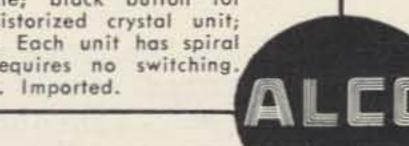Ideal for few feet or up to 9 miles. Each phone has separate red button, which when depressed sends pleasing signal tone; black button for talking. Receiver is transistorized crystal unit; transmitter is carbon unit. Each unit has spiral phone cord. Operation requires no switching. Use several units together. Imported.



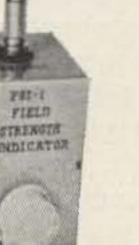

R.F. FIELD STRENGTH METER


Single Band 1 to 250 MC.

\$6.95

Model PSI-1 21/6 x 31/6 x 11/6 Compact! Sensitive! Checks antenna efficiency, load matching, etc. Requires no battery or other power source. RF measured on accurate meter. Telescoping antenna to 103/4", Earphone jack provided for monitoring; case has powerful magnet to grip fender, etc. Imported.

SEND FOR FREE CATALOG Available direct or through your local distributor



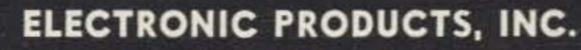

Dept. 666 — 3 Wolcott Ave., Lawrence, Mass.

times the fundamental frequency. For instance a fundamental frequency of 4

megacycles will have indications also at 12-20-or 28 megacycles. Also below the fundamental frequency, indications will be at 2 megacycles, 1,333.3 kilocycles, 1000 kilocycles and etc.; these being the harmonic frequencies


of the generator.

Tuning the generator through the different bands of frequencies going higher in frequency a point will be found where the next higher frequency indication will be 3 times the frequency of the point before mentioned. This last is the 3rd harmonic and the point first referred to is the fundamental frequency. A very slight indication may be found between the fundamental and the 3rd mode frequency. This is due to the 2nd harmonic of the generator exciting the crystal on the 3rd mode and can be ignored.

Also note that if the fundamental frequency is 4 megacycles and the 2 megacycle point had been found first then the next lower frequency indication point will not be 1 megacycle but will be 1,333.3 kc and the next lower frequency indication will be 1 megacycle. This shows that the 2 megacycle point was not the

fundamental.

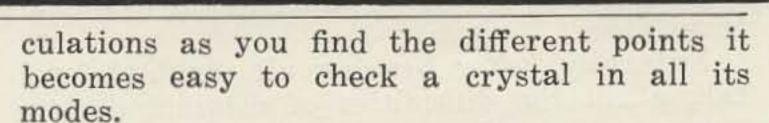All this is much easier to do than to explain but simply by tuning the generator through the different frequencies watching for the stronger blips and making a few mental cal-



The coil T 2 in Fig. 1 works well at frequencies from 400 kc to 20 megacycles. It was found quite critical and dimensions should be followed closely. . . . WøCGA

Sig. Gen.-Usual service signal generator.

T2-11 turns #20 cotton covered wire, tapped at center on 2.5 inch form.

T1-4 to 1 audio interstage transformer.

L3-Primary.

L4-Secondary.

Scope-High gain.

Letter

Dear Wayne:


It isn't often that I drop people a line voicing my opinion, but a recent article in the February edition of 73 demands response.

I want to express my thanks for printing Paul Barton's article on FINAL TANKS on page 12, etc. This is the kind of technical information that I crave for, and you have made one ham very pleased. Convey my best regards to W6JAT, assuring him that K2SKK has read it all and is putting this to good use. In my estimation, this article was worth the entire year's subscription; anything else you print as good as that will be "ice cream & cake" for me!-For second choice, I enjoyed WA6QFD's article on Silicon Rectifiers, p. 38. Keep up the excellent work!

Bon voyage to you and the XYL on your forthcoming trip to West Germany et al. Drive that Porsch€ carefully; we want you back to keep 73 going!

100-27!

Paul Boivin, Jr., K2SKK

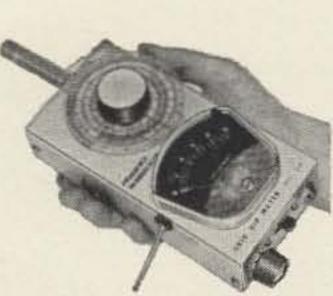



20,000

High sensitivity — 20,000Ω/V

 New design; wide scale arc Compares with 4½" meters

Compact black bakelite case

DC V. ranges: 5-25-250-500-2500

AC V. ranges: 10-50-100-500-

DC current: 50 µa, 2.5 ma. Imported

Measures 31/4"W x 41/2"

1000 @ 10,000Ω per V.

@ 20,000Ω per V.

ohms per volt

MULTITESTER

Completely calibrated Freq. coverage 1.5 to 300 MC in 6 ranges

\$36.99

Ranges color-coded to match coils, undamped 1

WITH FREE LEATHER CASE

MA meter. Variable sensitivity control for optimum grid current adjustment. Calibrated dial, adjustable hairline, allows precise accuracy. Phone jack permits use as modulation monitor. Oscillator tube is 6AF4. 61/2 x 31/8 x 11/2". 6 coils supplied, 117V, 50-60 cps. 2 lbs. Imported.

Model TS-60

Before the Breadboard

Staff

I F the response to our articles means anything, we hams are building equipment again; receivers, transmitters, test equipment, station accessories, you name it and chances are that somebody is working on it right this minute.

This is a wonderful situation; we like it! But the average response to a 73 article shows something else, too, which we find a bit disturbing: many of these people who are building gear now have an alarming lack of knowledge about the fundamentals of circuit techniques.

It's not really their fault; just about the only place to get these fundamentals is from an engineer (or material written to be read by an engineer) and all too many professionaltype engineers seem to believe that these details cannot be communicated in anything but engineeringese-which leaves us poor hams out in the cold unless we happen to be technical translators.

Naturally, after hearing all the high-level talk about the difficulties of original design, we as neophyte designers begin to get the idea that it's a difficult project; the vicious circle is complete, and we stay in our somewhat befuddled state, believing that the art of original design is far too complicated for us.

"T'ain't necessarily so," in the words of the song. Sure, original design of a completely reliable communications system capable of handling 512 independent messages at the same time, on the Earth-Moon-Earth circuit, may be a bit beyond our capabilities. But not all design work is difficult; most of it is simpler than you think.

And if you think that any sort of understanding of the basics of circuit design are beyond you, take a look at Fig. 1.

Simple, isn't it? Just three resistors in series. But let's look at this circuit a bit, and study it.

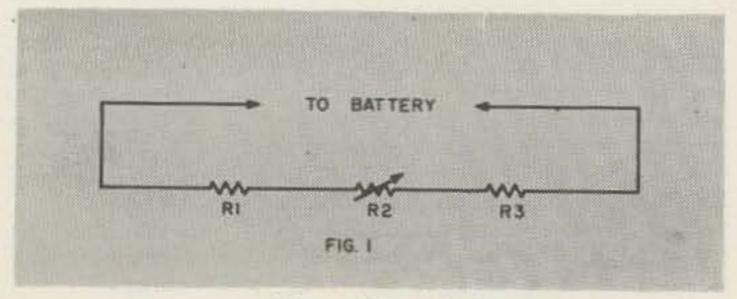


Fig. 1 Class A Circuit.

Since the three resistors are in series, all the current which passes through any one of them must pass through the other two. Since there are no other components in the circuit, the total voltage drop across the entire string must be equal to the total voltage applied to the circuit; there's no place else for it to go.

That's simple enough, isn't it? Yet the two sentences of the preceding paragraph state the two fundamental laws of network theory (usually considered the exclusive domain of the BSEE). "All the current that flows into a series junction between two circuit elements must flow on out" is the current law, while "the sum of the voltage drops across circuit elements in series is equal to the applied voltage" expresses the voltage law.

All very interesting, you may say, but what earthly good are three resistors in series to me in the design of a circuit? Let's take another look.

Suppose that the center resistor of the string were a variable resistor instead of having a definite fixed value. Suppose, also, that a constant-voltage battery were hooked up across the entire string. Finally, suppose that R1's resistance were considerably lower than that of either R2 or R3, and that the values of R2 and R3 were approximately equal. Now, let's examine the voltage acoss R3.

With R2 set for maximum resistance, the voltage across R3 would be just less than half that of the battery. Resistor R1, with its low value, would drop some of the supply voltage, but most of it would be divided equally between the two larger resistors.

If R2 were set for minimum resistance, on the other hand, the voltage across R3 would be almost equal to the battery voltage.

Now let's suppose that we have a trained Mongolian Midget operating R2; our Midget cranks the value of R2 up or down instantaneously according to prearranged signals we give him. The voltage across R3, naturally, varies in perfect step.

If the signals we send our Midget are very small voltages, and if the battery voltage is very large, the voltage across R3 will also be large-and you might say we have an amplifier.

This amplifier, of course, depends for its operation on a very special kind of Mongolian Midget-you might say, a Mythical Midget.

GENERAL COVERAGE . . .

IN A CLASS BY ITSELF!



\$429.00*

Amateur Net

*24 hour clock-timer-\$10 optional

HAMMARLUND HQ-180

+ A Good Converter ='s VHF as you have never heard it before!

SSB---CW---AM---500 cy. to 6 KC. Adjustable passband.

50 MC---144 MC---220 MC---432 MC--- YOU NAME IT!!

For the best results—use the very best Amateur radio equipment—HAMMARLUND



HAMMARLUND

MANUFACTURING COMPANY, INC.

A Giannini Scientific Company

53 West 23rd Street, New York 10, N.Y.

Except that he isn't mythical at all; you can purchase him outright for less than a buck anywhere. What's more, he comes complete with variable resistor. Our Mythical-Midget-resistor combination is nothing more nor less than the conventional electron tube; the cathode-to-plate resistance is the variable resistor, while the grid is the midget.

In the electron tube (and also in the transistor), the operating technique is exactly the same as our three-resistor circuit of Fig. 1. The tube itself corresponds to resistor R2; R1 represents the internal resistance of the power supply (this is what makes the voltage drop as you increase the load; the smaller it is, the better); and R3 is the load resistor.

You can see from the three-resistor circuit that the output voltage available is directly dependent on the value of R3; the larger R3 is, the larger the output voltage will be. In no case, though, can output voltage swing farther than the original supply voltage (except in the case of inductive coupling, which is a bit complicated for this stage of the game).

Electron-tube circuits work the same way, with one important addition: since a certain amount of current is required by the tube, R3 cannot be too large. If R3 is made too large, the tube will be starved and will fail to operate properly. But within this limit—and it's wide—the gain will go up directly as the load resis-

tance is increased.

If, at this point, you're thinking it can't possibly be this simple, you're only half right. Actually, you can make almost any tube do almost anything you want with no more information than that already given—but that's doing it the hard way, and may prove to be a bit costly if it takes you five or six burned-out tubes to find out just what values are permissible for R3.

To avoid this problem, manufacturers make available "characteristic curves" for their tubes. Every tube has a number of unique characteristics, mostly determined by the spacing and type of grid structures inside the tube. Any or all of these characteristics may be measured, and the results presented either as tables or as graphs in which key characteristics are presented together.

The most common means of presenting these characteristics is graphically, using what is known as the "plate family" of curves in which plate current is plotted against plate voltage, for certain fixed values of screen and control-grid voltage. Such a curve, for a type 12AU7 triode, is shown in Fig. 2.

From this graph (commonly known simply as the tube curve), you can determine the value of the tube's resistance (R2 in Fig. 1) in ohms by applying Ohm's law to the values of voltage and current which intersect at a

5814A, 30 MILLIAMPERES TAUT. EACH UNIT 5814A, 5963 CURRENT MAX. DC E. GRID CHARACTERISTICS OR 150 350 400 450 500 100 200 PLATE VOLTAGE - VOLTS

Fig. 2 Typical Plate-Family Characteristic Curves for 12AU7. Sample Load Line (10,000 ohm resistor

AVERAGE CHARACTERISTICS: 6C4, 6135, EACH UNIT 7AU7, 12AU7, 5814A, 5963

given grid voltage. For instance, if plate voltage is 150 and grid voltage is —2, the curve tells us that plate current will be 13.5 ma. Since resistance is equal to voltage divided by current, the resistance equivalent to R2 would be 150 volts divided by 0.0135 amperes, or 11,100 ohms.

It would be possible to use this procedure to determine the values of R2 over a wide range of voltages, then choose a fixed value for R3, and come up with an amplifier circuit—but such a set of calculations would be tedious. Since all the information we need about the tube is already shown in graphical form on the characteristic chart, it only makes sense to continue the design by graphic methods. This approach almost completely eliminates arithmetic, and rapidly produces a design.

The heart of the graphical design procedure is an item called a "load line." This is simply a straight line drawn on the chart through all the positions whose voltage-current relations come out to the value of R3, the load resistor.

Note that we said it goes through "all" the positions; however, you don't have to calculate them all. Since the resistance is fixed, the line will be straight—and this means that only two points need be calculated. Two points which are exceptionally convenient to calculate are those at which voltage equals zero, and at which current equals zero. If you know the value of supply voltage, this means that only one calculation is necessary; when current equals zero, voltage will equal that of the supply, but when voltage equals zero, current will equal the supply voltage divided by the value of R3.

To put this procedure into step-by-step form, first choose the tube you're going to use and obtain a chart for this tube type. Next, pick the supply voltage. Third, select a trial value for the load resistor (remember that the higher the value of the resistor, the greater the gain). Fourth, draw a dot at the point where the voltage line corresponding to the supply voltage intersects the zero-current line. Fifth, calculate the value of current when voltage is equal to zero, and place a second dot where this value of current intersects the zero-voltage line. Finally, using a ruler or straightedge, draw a line connecting the two dots.

What do you have, now? Basically, you have plotted the possible operating points of the tube. Let's do an example before discussing how it works. Since we have already used the 12AU7 curve, let's use it again. Pick a supply voltage of 250, and a trial load resistor of 10,000 ohms. The value of current at zero voltage will then be 250/10,000 ampere, or 25 ma, and we draw the load line connecting 25 ma at 0 volts with 0 ma at 250 volts as shown in Fig. 2.

Now, looking at Fig. 2, let's see how this works. Assume that the grid voltage is zero.

The tube (if R3 were not in the circuit) would try to draw a large amount of current—but the load line shows us how R3 limits the current in the series circuit, and the operating point for the tube and R3 together is thus the intersection between the 0-volt grid bias curve and the load line itself, or a plate voltage of 110 volts and a current of just under 14 ma.

Since most amplifiers don't work right when the grid voltage goes positive, it's usual practice to bias the grid negatively so that incoming signals (which alternate on either side of zero) won't drive the grid positive, ever. Let's see what happens when we put 2 volts negative bias on our circuit.

The first thing we see is that our operating point has shifted. It's now fixed by the intersection of the load line and the —2 volt bias curve, at a plate voltage of 135 volts and a plate current of 11.5 ma. This means that, going back to the simple circuit of Fig. 1, 11.5 ma is flowing through the entire circuit. This current through the 10,000 ohms of R3 develops a voltage drop of 115 volts, leaving 135 for the tube itself—which checks with our earlier figures (we omit the voltage drop in R1 as negligible—and hope that it really is).

Now, let's put a 4-volt peak-to-peak signal in at the grid of the amplifier we're designing. On the positive half-cycle, this input signal will reduce the grid bias to 0; plate voltage will swing down to 110 volts as the current through the tube increases. On the negative half-cycle, grid bias is increased to —4 volts. The load line tells us that plate voltage at this point is 160 volts, with a current of 9 ma.

Thus, the 4-volt input signal has resulted in a change of output voltage between the limits 110 to 160 volts, or a 50-volt output swing. To determine the gain, divide the output voltage swing by that of the input voltage—in

this case, it's 12.5.

So far, we've examined only the gain; the amplifier may produce plenty of gain yet not be usable because of distortion. We'll go into that in more detail before long, but at this stage you can make a rapid check by comparing the gain on positive half-cycles with that on negative half-cycles.

If these two half-cycle gain figures are the same, the chances are the amplifier's distortion

will be low.

In our example, the positive half-cycle gain was 12.5, corresponding to an output-voltage swing from 135 to 110 for a 2-volt input change. The negative half-cycle gain, also, was 12.5 (swing from 135 to 160 for similar 2-volt input). Distortion probably will be low.

This load-line technique is valuable in the design of audio amplifiers; it works just as well for low-level amplifiers and for high-power modulators. You can even make it work for push-pull circuits, but those are a bit beyond the scope of this article.

Naturally, this is not the only approach to amplifier design—just the simplest. The graph-

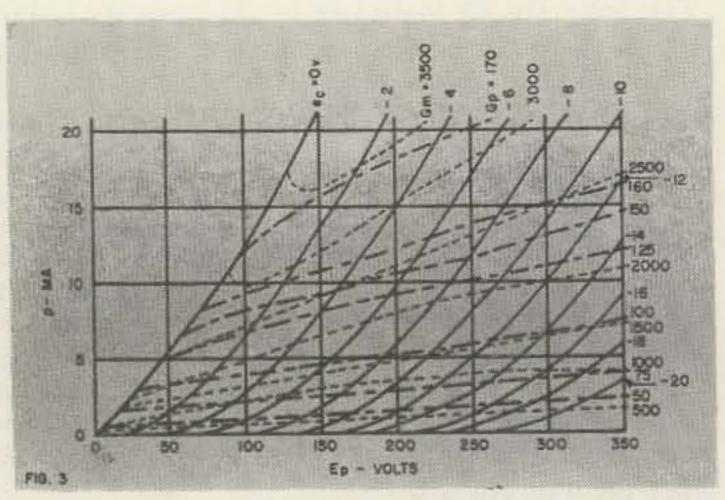


Fig. 3 G-Curves for 12AU7.

ical technique eliminates all algebra and higher mathematics usually associated with circuit design. However, if you feel that it's too simple this way, you can use the standard gain formulae and techniques to be found in Eastman's book (or almost any other handbook). A completely different approach, which includes many practical effects ignored in the conventional design technique, is to be found in Pullen. Pullen's technique, for instance, is the only one commonly available which allows for the effects of cathode resistors, loading of the next stage, and variations between tubes of the same type—but it does require algebra and the ability to plot your own tube curves, since he uses "G-curves" which manufacturers don't furnish. A G-curve for the 12AU7, which may be compared to the conventional curve, is shown in Fig. 3. Don't let it scare you.

A few paragraphs back, we promised some more words on distortion. Here they are.

The cause of distortion in an amplifier is simple: the gain of the stage changes as the input signal varies. If the change in gain is small, the distortion is unnoticeable; if the change is large, the distortion becomes obvious.

To calculate the precise amount of distortion produced in a stage, we have to know the precise amplification at the positive and negative peaks of the input signal—and this in turn requires the exact techniques of either Pullen's procedure or the conventional mathematical approach.

However, for our purposes we can do quite well by comparing the average gain on positive half-cycles with the average for negative half-cycles; that's what we did earlier. If these gains are the same, distortion will be negligible. If they differ (positive peak gain will be higher), distortion will appear.

To determine how much distortion to expect, subtract the lower gain from the higher one and record the difference. Then add the two gains together, and divide the difference you just noted down by their sum. Multiply the quotient thus obtained by 25, and the result will be the approximate amount of 2nd-harmonic distortion, in percent, which will be produced.

Naturally, harmonic distortion includes more than just 2nd harmonic. However, 2nd-harmonic distortion appears first and becomes objectionable long before the other components are large enough to calculate by this process, so if it's a reasonably small amount, the other components can be ignored.

So far, we've talked only about audio amplifiers. The same principles apply to RF and IF amplifiers in receivers, except that two load lines must usually be plotted for these.

The reason for two load lines instead of one is that the stages of such amplifiers are usually coupled by transformers or chokes, instead of by resistors; this means that the DC supply to the plate sees little resistance, while the AC component of the plate current (which is the desired output signal) sees quite a large "resistance" which forces it to go to the next stage.

To plot these dual load lines, draw a vertical line at the supply voltage for the DC load line; this shows that the tube's current is controlled only by the grid voltage. For the AC load line, a bit of figuring is necessary.

First, calculate the amount of current increase which would be produced by a 100-volt increase of voltage through the "resistance" (AC value) of the coil concerned. If the resistance is, say, 100,000 ohms, the current change would be 100 volts divided by 100,000 ohms or 1 ma.

Now, put your pencil at the point where the DC load line crosses the selected grid-bias value. This is the operating point. Measure off 100 volts toward zero (an increase in voltage across the load resistance is a decrease in voltage to the tube) from this point, and then measure up 1 milliampere (the calculated value) from the current at the operating point. Draw a line from this point you just located, through the operating point, and extending to zero plate voltage and to twice the DC supply voltage. This line is the AC load line; gain can then be found from it by employing the following variation of the procedure already described:

As in the single-load-line procedure, assume an input signal of the largest value you intend to handle. Follow the grid-bias curve corresponding to the resting bias plus the positive-peak value of input signal until it intersects the AC load line. Drop down to the plate voltage scale to determine plate voltage at this point.


Now, follow the grid-bias curve corresponding to the resting bias plus the negative-peak value of input signal until this curve also intersects the AC load line. This intersection point will be to the right of the DC load line; drop down to the plate voltage scale to determine the plate voltage for this point.

Don't let the fact that the negative-peaksignal plate voltage value is larger than the voltage supplied to the stage scare you; this

LEO SAYS:

NO MONEY DOWN!

ON THESE # hy-gain ANTENNA SYSTEMS

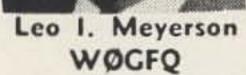

WITH WRL'S **NEW** REVOLVING Charg-A-Plan

hy-TOWER

REVOLUTIONARY

Model 18HT

Rapidly becoming the world's most permanent all-band antenna system, the hy-Tower uses no traps and is designed for operating on the 10 thru 80M bands. It also works well on 6M and can be used for 160M with base loading coil. Top mast extends tower to 50' overall. Completely self-supporting with concrete base cycolac base insulators. Wt.: 100 lbs.

Hy-Tower Anchor Base. Steel beam "Y" base with earth anchors. May be easily installed and removed. No concrete required. 80 lbs.

Only


Amateur Net

\$26.50

NEWEST DOUBLETS

HY-GAIN TRAP DOUBLET TAKES UP TO 500 WATTS AM: 1 KW PEP

New high level of radiation efficiency is made possible for the first time by using a matched set of Slim Line traps for each band. This exclusive feature produces true halfwave resonance at every design frequency. Antennas can be adjusted for phone or CW. Will equal or surpass the performance of any other doublet system. SWR 2:1 or less at resonance on every band. Fed with 52 ohm coax (not supplied). Guaranteed to survive winds up to 100 mph. An ideal system for any ham with multi-band capability.

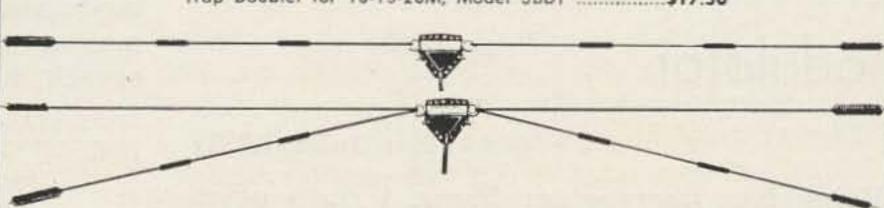

HY-FAN DOUBLETS TAKE UNLIMITED POWER ON 40 AND 80 METERS

Complete antenna system, single 52 ohm coax fed, and constructed of copper clad steel stranded wire, cycolac insulators and coax center insulator assembly. Fan configuration increases bandwidth and is virtually impervious to all weather conditions. Takes unlimited power. SWR less than 1.5:1. Models 4BDT and 5BDT take 1 KW P.E.P., 500 watts

> Fan Doublet for 15-40-80M, Model 2BDP Trap Fan Doublet for 10-15-20-40M, Model 4BDT\$24.50 Trap Fan Doublet for 10-15-20-40M, Model 5BDT\$34.95

*Reliability of the Hy-Gain Slim Line traps has been proven by the more than 100,000 in daily use throughout the world operating under every conceivable condition and climate. This enviable record is made possible by the unique triple molding process which completely embeds the trap circuit in tough, ageless polypropylene. In addition to this high degree of weatherability, the Slim Traps are practically indestructable mechanically and will survive even greater strain than will the copper clad steel doublet wire. Fully guaranteed for one year.



Slim Line Trap Doublet Center Doublet Insulator Coax Feed, Model CI End Doublet Insulator, Unbreakable, Model El

Model El Insulator

COMPLETE HY-GAIN ANTENNA LINE

WRL stocks the complete line of Hy-Gain antennas, including the great new 20 and 40M Duobanders, the 6 and 2M VHF Duobander, the Thunderbirds and the Verticals, as well as the Hy-Gain Citizens Band Line. Write for brochures on the complete Amateur and Citizens Band lines.

THE NATION'S TOP TRADES OFFERED! WARRANTY SERVICE DEPOT FOR LEADING MANUFACTURERS

LATEST RECONDITIONED EQUIPMENT

WRL is the nation's best source for reconditioned equipment. Each item is carefully aligned and tested just prior to shipment . . . carries a 90-day warranty, 2-week trial, and a 90-day full credit trade back plan. Write for our latest listing up to 1,000 pieces.

No Down Payments or "contracts" once you open the new WRL Charg-A-Plan. Carrying charges only on the balance remaining each month. Easy Add-Ons. Write for Charg-A-Plan information.

SEND FOR DESCRIPTIVE BROCHURE ON COMPLETE LINE OF COMET KITS!

MIDI	WORLD RADIO LABORATORIES, Inc.
MAKE	3415 W. B'dway . Council Bluffs, la.
Model_	want the Hy-Tower Doublet I prefer to use the Charg- with no money down. Rush informa-
Name	Call
Address.	
City	State

is natural, since the coil in the plate circuit stores up energy while current flows, so that a signal which reduces current flow releases the stored energy. This stored energy then appears at the plate of the tube as excess voltage, above the plate-supply value.

Once you have found the positive-peak and negative-peak plate voltage values, you can calculate the gain by dividing the swing by the peak-to-peak value of the input signal, just as for the resistive amplifer discussed before.

Not yet mentioned has been the problem of designing Class C amplifiers for transmitters; they are put together in a completely different manner. However, space has run out for this month, so we'll have to postpone that until a later technical article. Until then, keep in mind the three simple resistors—they're the heart of every circuit-design problem!

BIBLIOGRAPHY

Anonymous, Reference Data for Radio Engineers. Fourth Edition, Federal Telephone and Radio Co.

Anonymous, RCA Receiving Tube Manual, Technical Series RC-19, Electron Tube Division, Radio Corporation of America, Harrison, N. J.

Eastman, A. V., Fundamentals of Vacuum Tubes, Mc-

Graw-Hill Book Co., New York, 1949.

Pullen, K. A., Conductance Design of Active Circuits. John F. Rider Publisher Inc., New York, 1959.

Transistorized Modulator


Burt Yellin K2STV

Being like many other hams, I have often sought an efficient, compact, universal modulator. Although only 75% modulation is obtainable through the use of this circuit, it is efficient in that it requires a minute amount of power. Battery current is in the order of microamps, therefore allowing the battery to last its entire shelf life.

The modulator shown in Fig. 1 is capable of cathode modulating any transmitter up to the full power input of one kilowatt. In many instances the transmitter will not have to be modified. If the transmitter uses cathode keying, all you do is simply plug the modulator in, instead of the key.

The circuit uses four NPN transitors compound connected. Compound connected transistors have the following characteristics: a high input impedance, and an extremely high current gain. This is perfect for cathode modulation, as a crystal mike can be used, and the circuit will control the cathode current of the power amplifier in the transmitter. The circuit has one other advantage, and that is that it will act as a clamp tube. Should the final lose drive, the modulator will limit the amount of cathode current, which is determined by the setting of R₁.

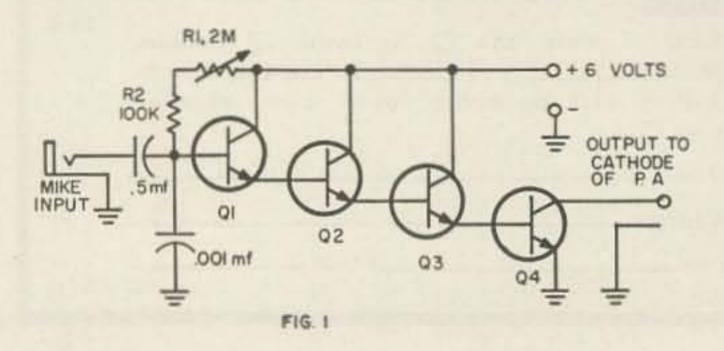Any NPN transistors can be used for Q₁, Q₂, and Q₃ providing their beta is 30 or greater. Q₄ must be chosen by the amount of cathode current that will be flowing through it.



To use the circuit, tune your transmitter as is normally done for CW operation, insert the modulator, and adjust R₁ until you get the maximum change in cathode current with speech input.

... K2STV

TAPE TIP

An ever increasing number of "do-it-your-self" decorative and finish materials are reaching the market. One item that should be attractive to the amateur constructor is an adhesive backed, metal tape that is available in several patterns.

This tape and one application are shown in the photograph. While the tape may be used for strictly decorative purposes, it is convenient for covering equipment finish imperfections and unused holes. Application is a snap. Simply cut the strip to size with a pair of shears, peel off the adhesive protector paper and apply to any clean, dry surface.

The particular product shown in the photograph is a metalized, Mylar tape, sold under the Trimbrite label. The manufacturer is Marglo, Inc., New Britain, Conn. and the tape is available in most hardware stores.

... W4WKM

Photograph by: Morgan S. Gassman, Ir.



POSS BLE

They said a Two AND Six Meter Transceiver couldn't be made

ALMOST

It sure wasn't easy-

We Worked

We Slaved

We Starved

We Sweated

We Starved

We Built

We Rebuilt

We Cajolled

We Starved

We Tested

We Detested

We Starved

We DID IT!

We Had-

Birdies

Parasites

Low Drive

Hi Drive

Parasitic Birdies

Low Modulation

No Modulation

Headaches

Dyspepsia

Fights with the XYL

Low Bank Balance


No Bank Balance

And VFO Drift

Somehow, some way we solved all these, except the VFO drift, but read

YTRONICS LAB inc.

CLIETON NEW JERSEY

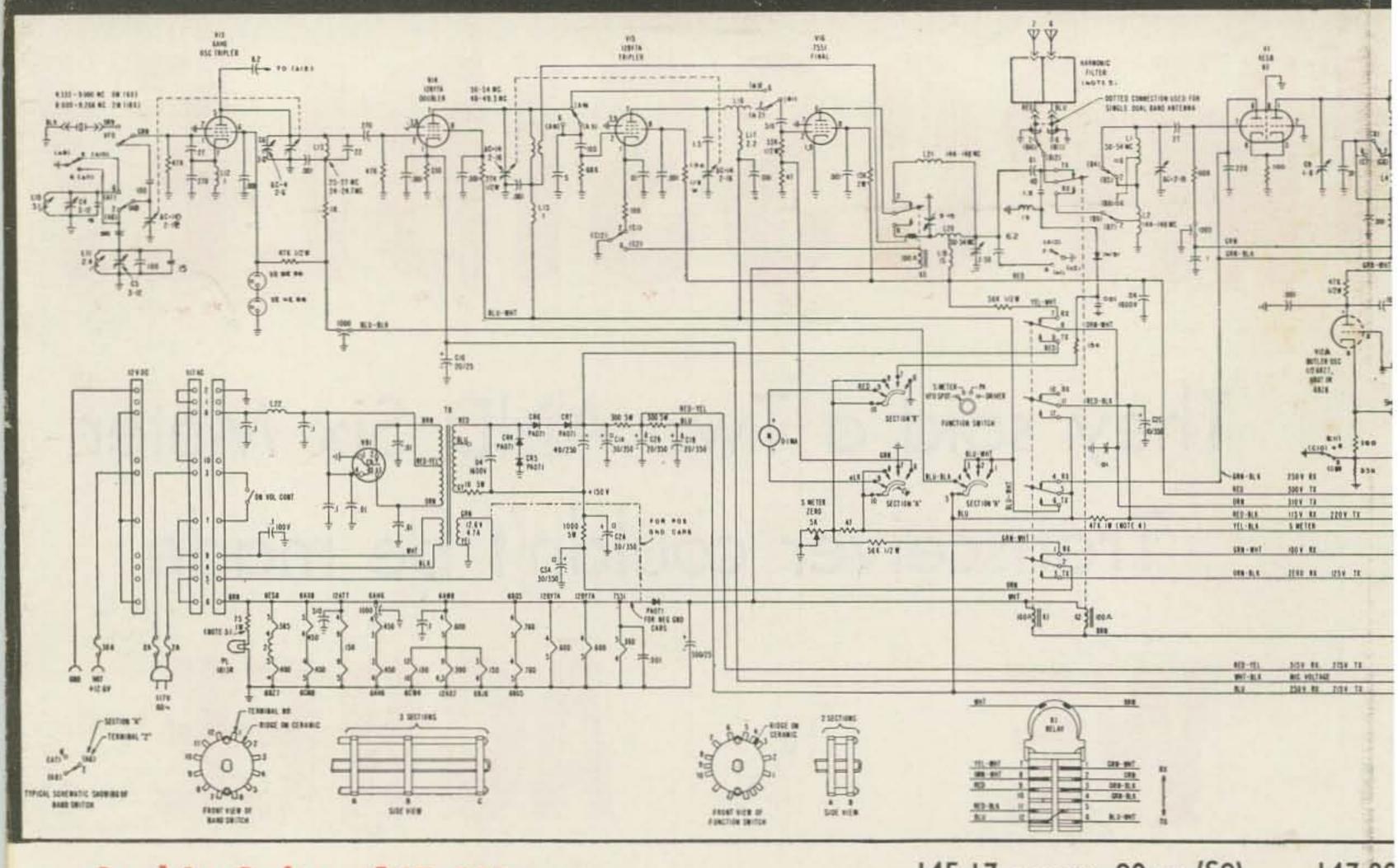

And In Spite of IT ALL; Receiver: (triple conversion superheterodyne)

Frequency Range: 49.750 to 54.250 MC and 143.750

148.250 MC. (Includes C. A. P. Frequency.)

Calibration: 100KC graduations every 4°.

Tuning Ratio: 6:1.

Sensitivity: Better than .2 uv on 6 meters and better than .8 uv on 2 meters for 6 db s + n @ 30% @ 1000 cps modulation.

Selectivity: -6 db bandwidth 8 KC ± 2 KC. -60 db bandwidth 25 KC \pm 5 KC.

AGC: Audio output varies less than 3 db from I uv to .I

Delayed AGC: Knee of AGC occurs between 3 and 10 uv. Squelch (adjustable): At threshold receiver will awaken for carriers of .08 uv or greater on 6M and will awaken for carriers of .I uv or greater on 2M. At stop receiver will awaken for carriers of 10 uv or greater. (Stop limit adjustable from 3 to 30 uv).

Noise Limiter: Floating series gate type operates on all noise peaks. Audio unaffected by modulation levels less

than 85%.

Audio Output: At least 2.0 watts into 21/2" PM internal speaker or at least 3.0 watts into external 4 ohm speaker. Provisions for 5W into external speaker.

Distortion: Less than 15% from 250 to 3000 cps at I watt

output.

Hum and Noise: Better than 40 db down from I watt output. Freq. Response: Within + 1 db to - 5 db from 250 to 3000 cps (reference 0 db at 1000 cps at 30% at 100 uv). 1st Image: Better than 85 db down on 2M. Better than 40 db down on 6M.

2nd Image: Better than 60 db down. 3rd Image: Better than 85 db down.

Spurious Responses: Better than 50 db down everywhere except within ± 20 KC of desired signal.

Internal Generated Spurious Signals

147.80 145.17 approx. 90 uv (S9) Cross Mod and Desensitization: Better t ± 20KC.

IF Frequencies: 52.00 MC (± 2 MC) 5.405 MC 455 KC

Compliance: Meets FCC Rules Part Radiation Device.

Stability: Less than ± 15KC During 4 Less than ± 2KC/HR thereafter.

Transmitter (separate osc, multiplier through final amplifier)

Plate power input to final: 18w 6M 17w RF Power Output: At least 9.0 watts ou At least 4.0 watts ou

Mod. Cap.: 85 to 100% at average spea modulation.

Hum and noise on carrier: at least 40 c modulation level.

Harmonic Suppression: All harmonics sions better than 50 db down. Excee quirements.


Microphone (all press-to-talk): unit norn grey plastic high impedance detacha phone with 5' retractable coil cord. hardware.

Frequency Control: VFO or crystal. Crystal Stability: ± .005% -30° C. to Crystal Circuit Stability: ± .006% - : VFO Stability: Less than ± 25KC on

40 minute warm up. Less than ± 6 Humidity: Will perform after being sub 95% relative humidity for 8 hours.

Vibration: Will withstand 10G shake from for 30 minutes in three planes.

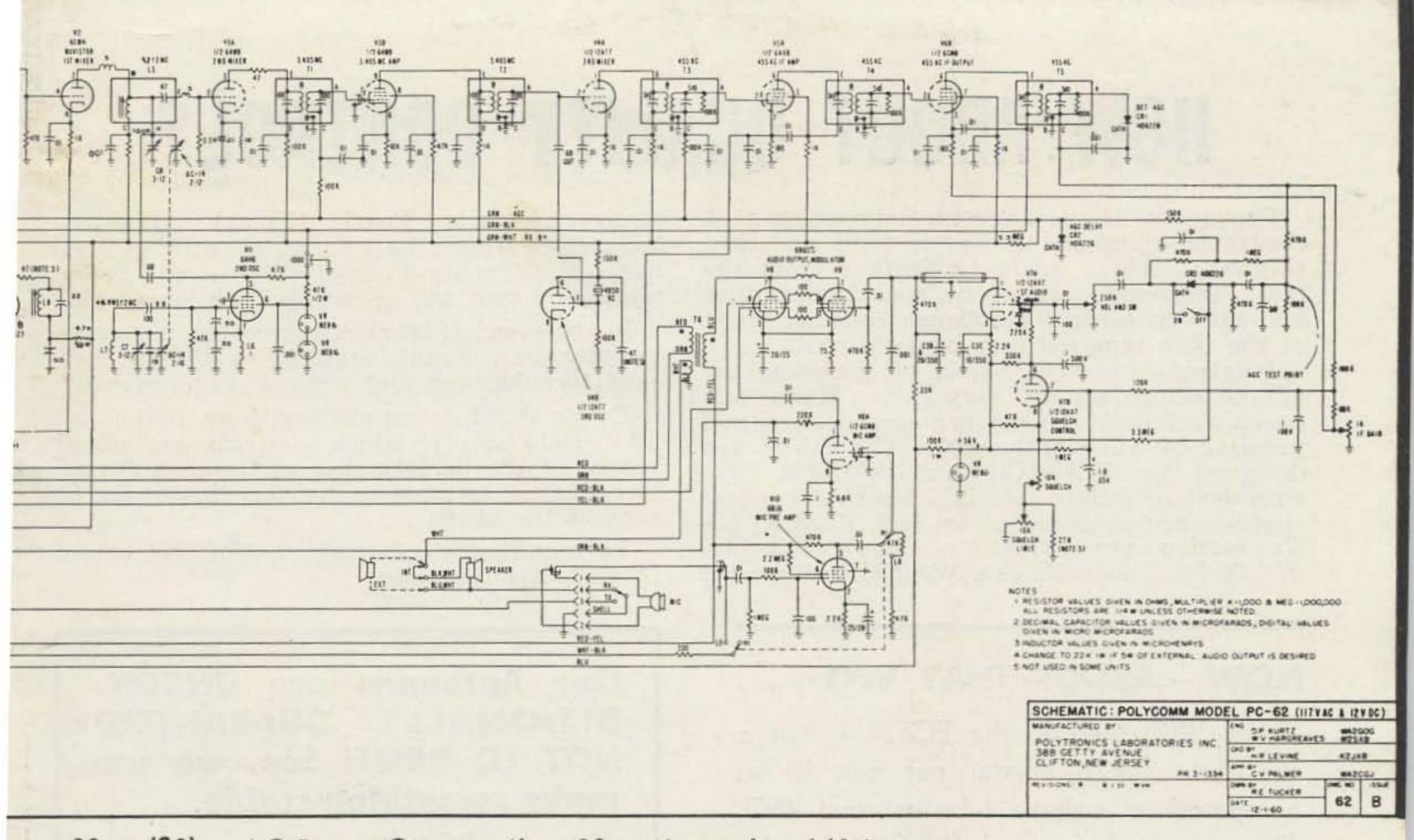Shock: Will withstand 15G shock in thre Supply Voltage Variation: — 20 to + 1 voltage.



50 db down at

re: Incidental

inute warm up.


and straight

AC Power Consumption: 90 watts receive, 140 trans. DC Current: 10 Amps rec. 16 Amps trans. @ 12.6 volts.

Size: 11" wide x 10" deep x 5" high. Weight: 15 lbs. total system weight.

Color: Marine grey, maroon knobs, white lettering,

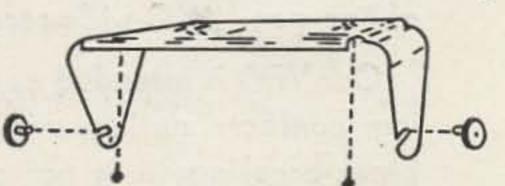brushed aluminum grill. Shipping Weight: 23 lbs. The PC 62B is a COMPLETE 2 band mobile/base station ready to operate. Well almost, need an Antenna? Turn



on 6M t on 2M g level via plate lown from 30% spurious emis-

y supplied with ceramic microludes mounting

latest FCC re-

- 70°C. C. to + 60°C. er band during /HR thereafter. ted to 90°C. at

60 to 1800 cps.

lanes. 6 of rated input



INCLUDES, replaceable microphone with hang-up clip, universal mounting bracket for mobile operation, AC and DC cords, separate antenna connectors (5O 239) and all mounting hardware.

HOW ABOUT QUALITY CONTROL?

Frequently Hams have the impression that electronic equipment is simply built and then shipped. Nothing could be further from the truth. Inspection, alignment, operation, testing and quality control assurance consume most of the time required to produce a unit.

Polytronics is very proud of the fact that all its technicians are very active Hams well acquainted with the performance desired and required by VHF enthusiasts. The PC-62 was designed by WA2GOG and W2SXB. The President of Polytronics is K2JXB. All power supplies are checked out by Hal, K2SGX, the Tx section specialist is Steve Fancher, WA2ZNE. Shade M. Lee, WA2OJB aligns the

receivers, while Pearl (Tiger) Maguire, WA2QNY, tracks the VFO. After all this, Joe, K2QLW, (Quality Control) gets a chance to reject any unit not up to his high standards.

In the event of trouble, thereafter, our service manager, Frank Siggins, WA2TDD, can expertly diagnose and correct any problems.

Every PC-62 is supplied with an Individual Test Data Sheet, which contains an actual record of the performance of the unit during test and is attested to by the signatures of each of the above.

Personalized performance? You bet. Drop in and meet the gang.

NOW - ABOUT THAT VFO . . .

...The VFO used in the PC62B is not a substitute for a crystal nor can it be compared to a single tube external VFO. Our specs call for a drift of no greater than \pm 25 KC on either band during a warm up period of 40 minutes, thereafter the VFO will remain within the pass band of any good 6KC wide receiver.

Our VFO is intended as an aid in obtaining contacts during skip, field days, or break-breaking; it is not a secondary frequency standard, but it is a darn good VHF HAM TYPE VFO.

Our Antennas are UNCON-DITIONALLY GUARANTEED NOT TO DRIFT! See, we can make something stable.

Antennas :PCA-251: Whip only. 2 & 6 meter dual band antenna. Standing wave ratio of 1.1 to 1 at resonance and no greater than 1.5 to 1 at any point in the band. \$13.95.

PCA-249: Same as above with cowl mounting. Complete with 15 ft. RG-58/u cable and PL/259 connectors at both ends. \$21.95.

PCA-250: Same as above with standard stud, ball mount, cable and connectors. \$23.95.

The PC62 CD (also \$379.50) has been approved as meeting specification CD I-100 in connection with any bids to State and Local subdivision requiring its use for Civil Defense.

OCD Item No's, T-34/R-04, T-36/R-06, M-48, & M-50

OK YOU	GUYS:			
	CARE IF YOUR		TAKE A	HALF HR.
☐ PSE SE	CAN I BUY ON ND COPY OF CE ND ADDITIONAL	AUTHORIZ		
Name		c	all	****
Address				
City	*****	St	ate	******



Clifton, N. J. Phone: 772-1334

AGC for the Swan Transceiver

Lawrence Frazier K6SHC

THE Swan 100 series transceivers have caught the eye of many hams, both for mobile and fixed use. These transceivers are sensitive and have a good punching signal on the air.

In talking with many of the fellows who have these transceivers, the one slight improvement desired was an AGC system. When in a round-table with several stations, some are bound to be much louder than others. This requires one hand on the gain control, or a good set of nerves.

The AGC board will be very easy to construct and can be built from parts in the average junk box. The audio choke CH1 can be made from the high impedance (plate) winding of a small audio output transformer. The diode should have a peak inverse rating of at least 300 volts. The current rating need be only a few milliamps, as the current is very low. Good back resistance is very important to keep the positive level set voltage from loading the circuit.

In working with the mounting problem, it was decided to mount the AGC parts all on one board and then mount the board on the side of the metal cover which covers the 5.5 mc crystal filter. Care should be taken in placing the screw holes so that the screws will not touch the crystals or the coil in the center. The wires which go below the chassis can be put through the rubber grommet through which the wires to the relay already go. Small wire should be used so that they will all fit through the grommet easily.

Connection of the AGC to the transceiver should be done as follows: With the AGC wired, tested, and mounted, there should be five wires (including the ground wire) which should go through the grommet to the underside of the chassis. Connect the wire from terminal (1) to the plate of the audio output tube (6AQ5 pin 5). Connect the wire from terminal (2) to the plus 150 volts on the OA2 pin (1, 5). Locate the 1 meg resistor connected to pin (1) of the 1st RF amplifier (6BA6). Remove the end of this resistor which goes to the terminal lug with the rf choke also connected to it. Connect the wire from terminal (4) to the loose end of the resistor just removed. Insulated sleeving should be used to protect against shorts. Connect the wire from terminal (5) to the terminal lug from which the 1 meg resistor was removed. The last wire, from terminal (3) should be connected to a convenient ground terminal on one of the tube sockets.

The only control is the level set potentiometer R1 which is used to set the relative level of the clamping action. After this level set has been adjusted for the particular rig, it will not require any further adjustment. Therefore, it can be placed inside the rig out of sight. After the AGC has been installed and checked out, it may be desirable to change the recovery delay time slightly. In order to make the receiver recover faster after a loud signal goes off, the value of R4 should be decreased, but by no more than 40K. To make the receiver recover slower, thereby making quieter operation, the value of R4 should be increased. The value of 100K seems to hit a happy medium.

This AGC is in use in several units and functions quite well. There is little or no attenuation of the weak signals, and the loud signals are clamped to a comfortable level. The gain control on the front panel still functions to control the gain and relative audio output level. Some checks were made, using a sharp cut-off tube (6AK5) in the input stage, and it seemed to produce a more pronounced clamping action.

This circuit has been tried in other receivers with very good results. The best clamping action seems to be with a high gain, sharp cut-off tube in the front end.

With this AGC in your Swan, there will be no more need to keep one hand on the volume control when in a round-table, or while signals fade in and out while driving down the road.

K6SHC

AGC BOARD **6AQ5** .0047 mf **6V6** +SG R2 30K CRI IN538 RI + 220 +220 VRIO5 R3 10mmf 6BA6 TO PA. O-C2 I mf SIOOK NOTE POLARITY!

Note: The audio output tube may be a 6V6, in which case the proper pin changes should be made. Also in later models, the type relay has been changed so that there is no grommet by the relay. In this case, the wires to the under side will have to go through one of the other grommets.


160 Meter

Mickey Mouse

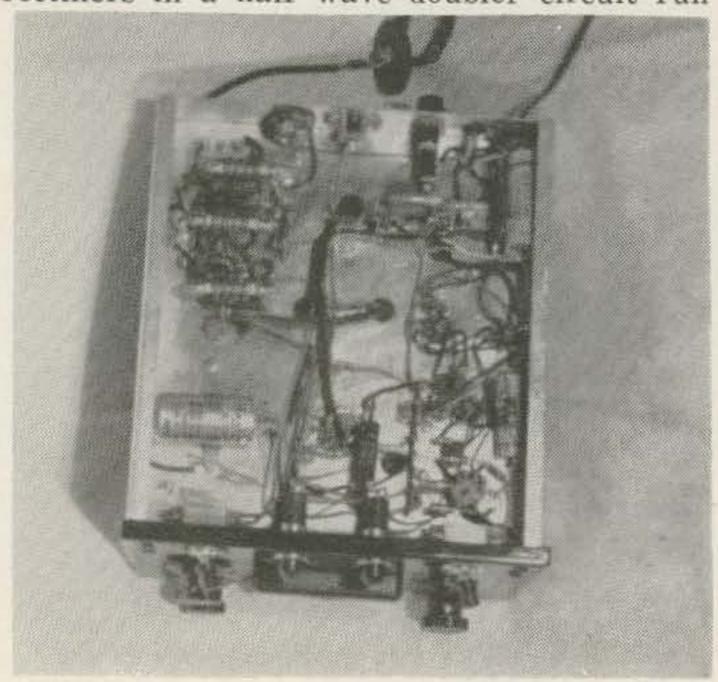C. L. Martin K9PAL Instrument & Electronic Tech. General Electric Company Bloomington, Illinois

WITH the increased amount of activity on the amateur bands these days, it becomes even more difficult to find the frequency space to carry on the famous "rag chew" session with the local brothers of the profession without "tromping" on some poor soul in the next state who is trying to stretch some range out of the "Half Quart" rig, or move that piece of traffic thru the QRM. Faced with these problems, it becomes even more sensible to make use of that 25 kilocycle hunk of frequency in the 160 meter band for the "local" activity. Range of 25 miles or so is consistent on these frequencies with occasional real DX reported on quite low power. So, to this I add the question "Why not a rig that is portable enough to carry to the over night fishing hole or on the vacation"? The rig described here, combined with a "tuned over" AC/DC set or, small portable provides this portability as well as reasonable power on a vertical or half of the old 75 meter dipole.

Circuit and construction is along conventional lines with the exception of the power supply, which is less common. Here the circuit makes use of a pair of the modern silicon rectifiers in a half wave doubler circuit run-






ning straight out of the 115 volt line. Two things are accomplished by this. First the familiar power transformer is absent (a sizeable cost reduction) and second, the ac ground system is used to advantage with the portable whip. To do this without making the cabinet "hot," a built in line polarity indicator is used. With the power switch OFF and the chassis connected to the line "hot" side, the neon will provide enough glow thru leakage to be seen, even if no ground is present on the cabinet. If the neon glows, the line plug need only be turned ½ turn to correctly polarize. A 2 amp fuse in the ground side provides protection in case of a mistake in polarity when the rig is attached to an earth ground. Such a system is not dangerous when handled properly. It is strongly advised that an earth ground be attached to the cabinet whenever possible, however.

Parts placement is not critical and no shielding between components should be necessary. It is suggested that the modulator be placed as far as possible on the chassis from the rf section. The familiar 6L6 was selected for the final stage because it operates efficiently at the relatively low plate voltage and is usually readily available from the junk box. Grid drive should be adequate when the OSC tuning coil is peaked. If more drive is required, this can be accomplished by decreasing the 20K dropping resistor in the oscillator plate. Grid drive should be near 3 ma.

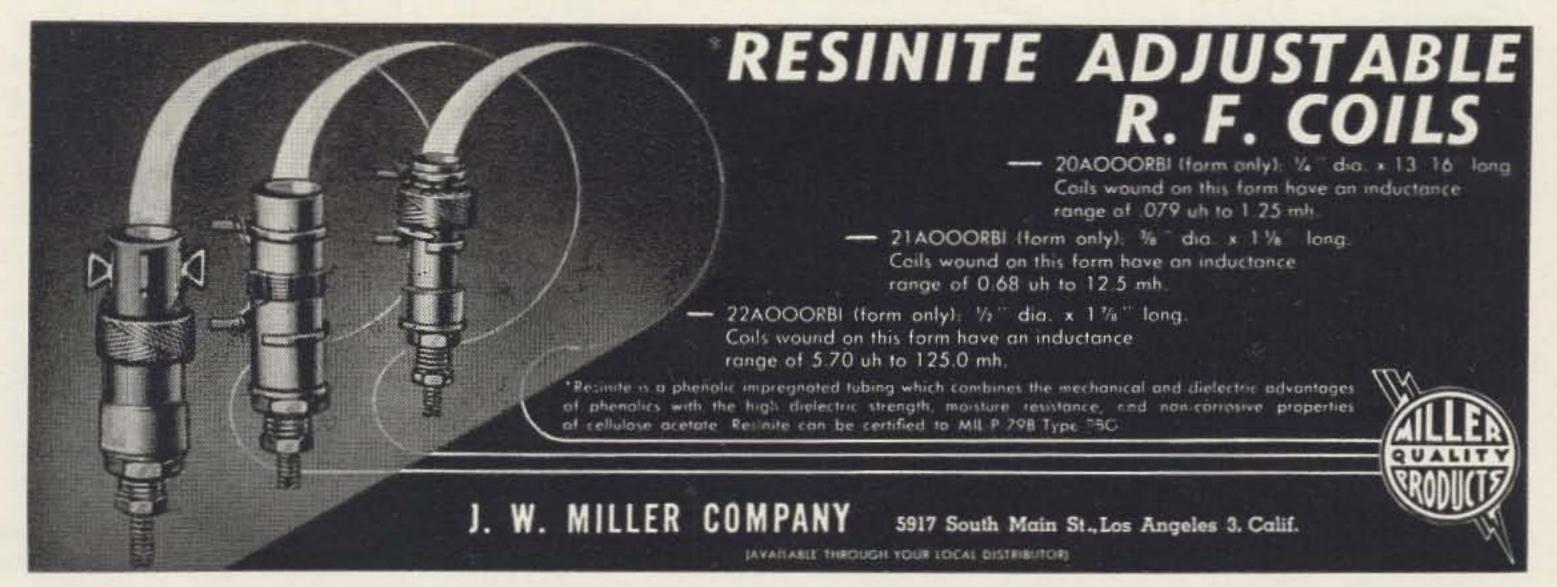
Although the final is capable of more than the 18 watts indicated, the modulator is good for only about 9 watts. If 100% modulation is to be realized the final must be held down to this value.




Cabinet construction is three piece with the 1½" chassis fixed to the front plate by the switches and indicating lamps. The cabinet is wrap around constructed with a partial back panel installed. Two ¾" chassis punch holes are made in the cabinet, one to allow mounting of the whip and the other to allow the banana jack antenna terminal clearance. This jack is sub-mounted on a piece of ¾" Plexiglass for insulation. Cabinet dimensions are 6" H x 9" W x 10" deep.

The whip is a 60" automotive replacement antenna. The base loading coil is constructed of Textolite or similar dowel, 1½" dia. 8" long. A 2½" x 2½" square of ¾" Plexiglass forms the base. This is mounted to the dowel

with a single #8-32 screw which is first placed over a solder eyelet. Connection for the winding is obtained by drilling and tapping for a #4-40 of length to jam the #8-32 mounting bolt. An appropriate size hole into the top of the dowel will mount the whip. Again the winding solders to a #4-40 jam bolt (see sketch). The coil is close wound of #22 enamel over 7" of the diameter of the coil. Total turns should be approximately 260. Actual loading of the coil can be accomplished by on the air tests. A simple way to achieve this is to extend the whip fully and tune the final to resonance with the loading capacitor fully closed. The plate switch may be turned off and on, the final "dipped" and the extension whip

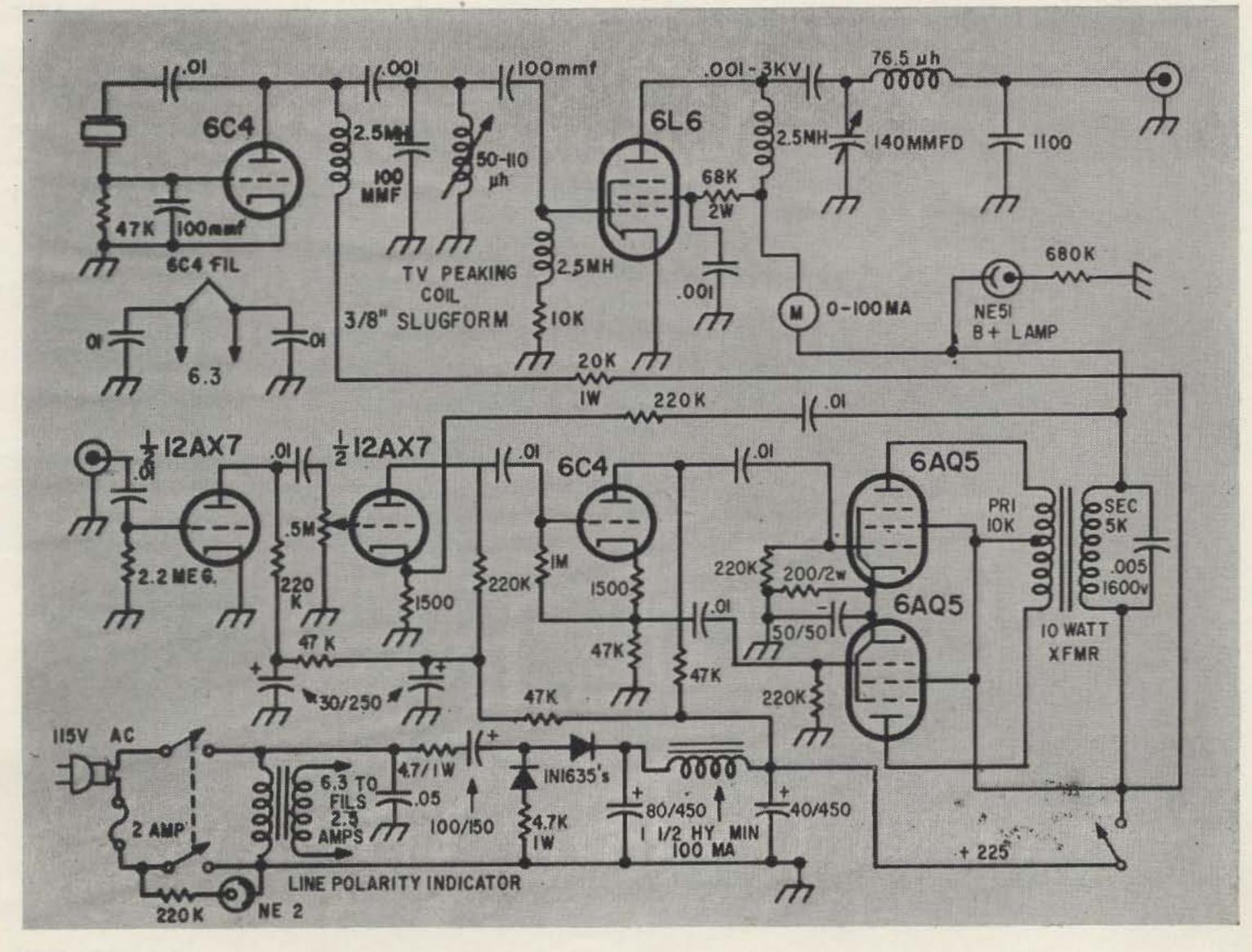

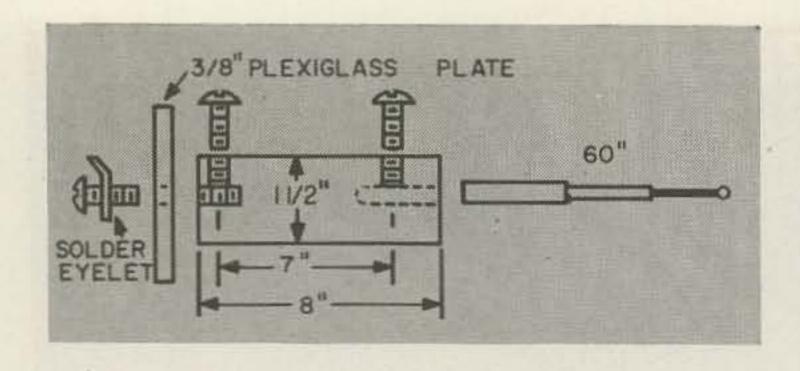


slid down to the point where maximum plate current is drawn while in resonance. This is the tuned point for the antenna. To load it will probably be necessary to extend the antenna ½ inch or so from the tuned point. It is then only necessary to remove a few turns from the whip and extend it again to the tuned point. Remove enough turns to tune the whip about 4 inches from fully extended. This will then allow for variables in loading in different locations where the antenna system is influenced by metal, etc.


Improve Weak Signal Radio-Teletype Reception

Woody Davey W7CJB 329 East Kent Missoula, Montana

THE circuit in Fig. 1 is somewhat conventional, but with balanced detector, trigger and keyer tubes. A filter circuit consisting of an .02 mfd condenser, two 100K resistors and the 220K resistor form a long time constant circuit in the detector output which completely wipes out noise spikes that could trigger the keyer stage when signals are weak. Observations on the scope indicate all traces of noise spikes are eliminated by this circuit. It can be shown that removal of these condensers during noisy reception will cause very bad garbling

of otherwise perfect copy. Note coupling resistors R1 and R2 on the grid of the driver tube. Both resistors are identical, their value being determined by the voltage developed at the plates of the 6AL5 detector. These are nothing more than part of a voltage divider to drop the dc voltage on the grids of the 12AU7 to —8 volts as measured on a VTVM, when the respective half of the 6AL5 is conducting. Transformers T1 and T2 are approximately 1:1 but if substitutions are made it will only be necessary to adjust the coupling resistors R1

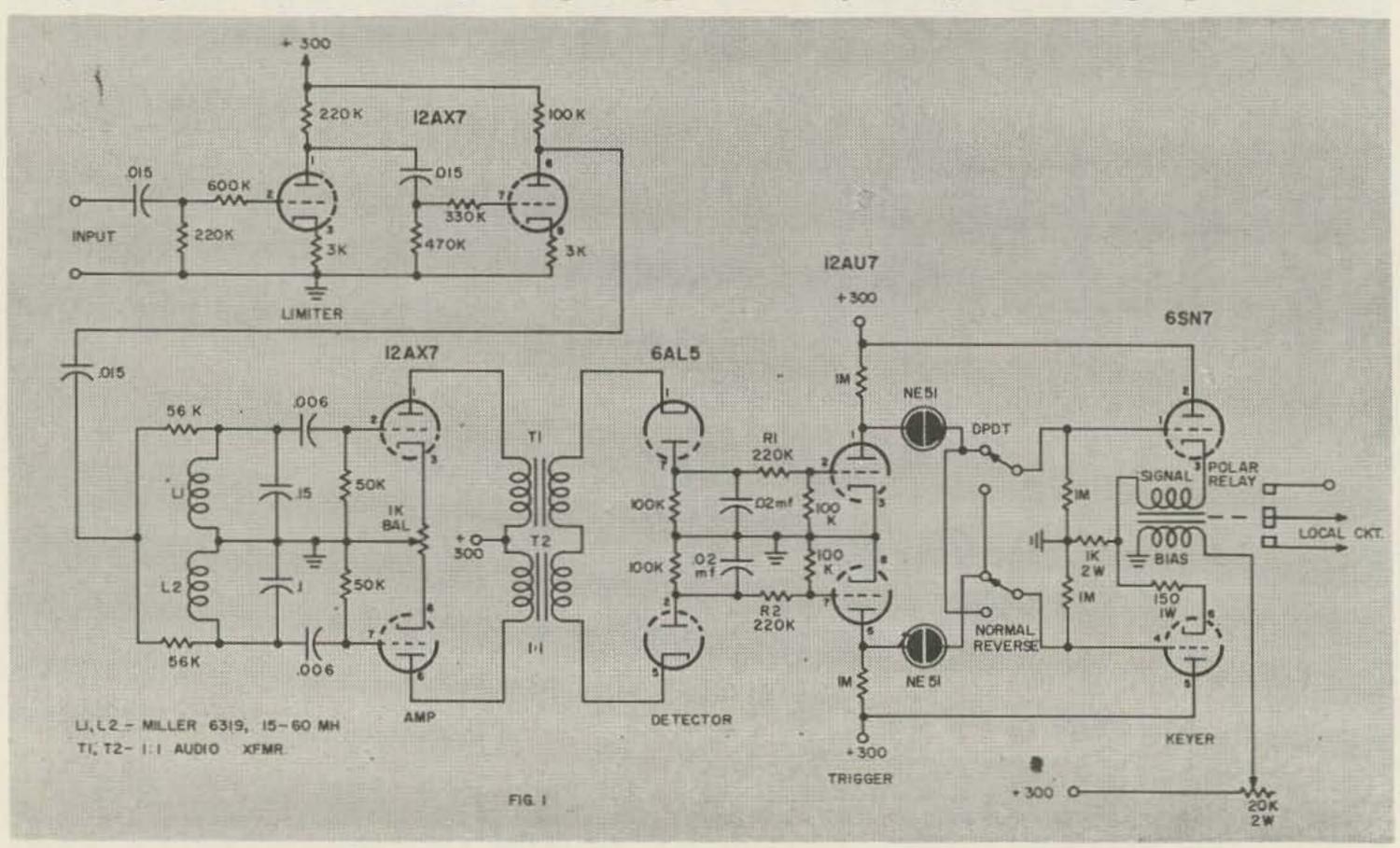

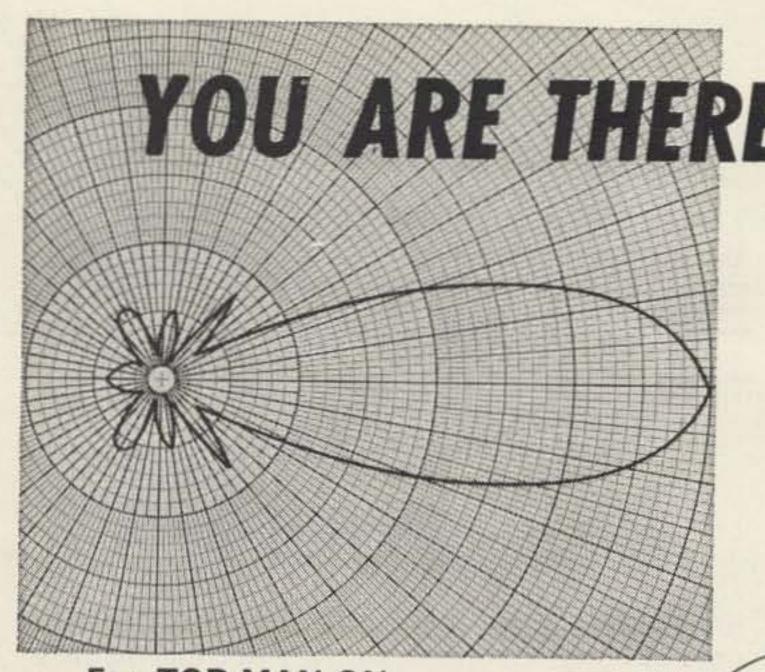

For TOP-MAN-ON-THE-FREQUENCY results...

Install a Telrex antenna...dollar for dollar better in every way! Antenna systems from \$6.95 to \$12,000.00

YOU ARE THERE! TELEX

with The-performance-line"—

with a "MATERIAL" difference!

NOW! A Broad-Band 'Balun' for your 10, 15 and 20 Meter Tri-Band

\$1685

MODEL BA1430/1-1



and R2 so that —8 volts appears on the 12AU7 grids when the limiter is saturated and with the proper tone at the converter input. The K1 balance control in the cathode of the 12AX7 amplifier is adjusted to equalize the voltages on the 12AU7 grids when the respective mark or space frequencies are selected. Minus 8 volts on the 12AU7 grid will cause an increase in the plate voltage to at least 60 volts which will fire the neon properly.

The 6SN7 keyer tube could operate balanced with one winding of a type 255A polar relay in each cathode, but I prefer to replace one winding with a 150 ohm resistor and to provide bias current to the disconnected winding. In this case the actual keying is done on space signals, but you have a built-in "mark." The polar relay bias current should be adjusted to exactly ½ the current value of the "signal" winding when that portion of the 6SN7 is conducting. In this case 30 ma in the signal winding necessitated a bias current of 15 ma.

The DPDT switch on the NE-51's allow copy of "normal" or "reversed" signals. Prior to the development of this circuit I had tried several discriminator type detectors followed by various trigger and keyer circuits, but with signals down in the noise, the above converter would outcopy the disciminator type of converter. Comparison was direct, with the two converters

side by side.

The TV width coils can be replaced with 88 mh toroids by tuning them to the proper frequencies. The toroids give somewhat better selectivity, and due to the higher "Q" there is an incease in the detector output voltage of approximately 8 or 9 times (who said TV coils were high Q?). With toroids it will be necessary to increase the value of R1 and R2 to 1.5 megohms.

As a matter of interest selectivity curves were run on both the toroids and the TV width coils. The width of the selectivity curve at the ½ voltage point (6db down), is as follows:

2125 center freq 2975 center freq

TV width coil 570 cps 890 cps
88mh Toroid 180 cps 330 cps
It can be easily seen that toroids would be a definite improvement when the QRM is bad.

Another real problem in radio-teletype reception is selective fading. One does not notice this unless the audio is either metered or observed on a scope. This can be quite severe at times and I have observed as much as 20 db difference in the two tones, fist one and then the other being the stronger. I might suggest the use of separate audio limiters in each channel to help overcome this. Tuned circuits should be used ahead of the limiters to separate the two tones, prior to limiting. ... W7GJB

Positive Transistor Protection


In most transistorized equipment, if the polarity of the power supply is connected backwards, the result is a mass of melted germanium, damaged electrolytics, and an abundance of profanity. With the nine volt or penlight batteries it is quite easy to connect them backwards, especially if you are anxious to try the equipment out or go somewhere. To prevent this, it is only necessary to put a small diode in series with the battery. If the polarity is connected incorrectly, no current will flow so no damage will result. For small, low power equipment, a general purpose diode will work. Where the current is higher than 20 ma. or the voltage higher than 6 volts, a small, low piv silicon diode should be used. ... WA2INM

Pre-Amp Curve Shaping

Charles E. Landahl W5SOT 121 Barranca Road Los Alamos, New Mexico


THE following microphone pre-amplifier is presented as a helpful suggestion, and, is a small commentary upon the simplicity of resistor—capacitor filtering. A glance at the experimentally derived curves shows the narrowing of the audio pass band of a common type of microphone pre-amp, when the tube and associated circuit values are changed. The original circuit is found in many amateur applications and borders upon high fidelity practices. It is possible to find transformers for the following stages which will sharpen the bandwidth of the modulator system, however, such transformers are costly to make and are seldom found in moderately priced equipment.

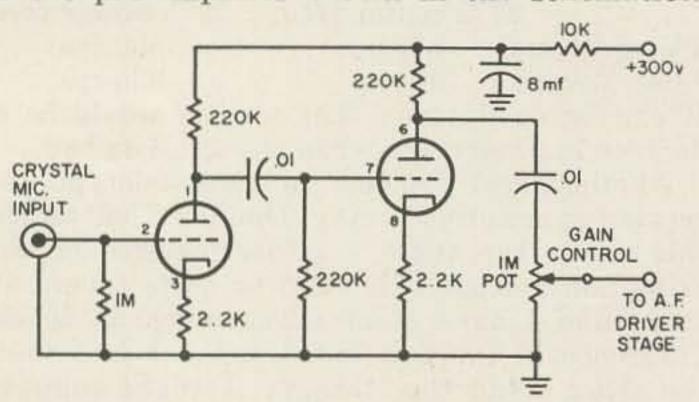It was fun to experimentally determine an optimum compromise between microphone, tubes, coupling capacitors and plate resistors, which would help narrow the audio pass band of the pre-amplifier shown in the schematics.



Don't be frightened by the low value of input grid resistor, nor the high values of the plate resistors. Remember? We want to restrict the audio range and occupy fewer of the precious kilocycles available to us. The low value of input grid resistor helps to get rid of the low frequency response of a high impedance crystal microphone. The high value of plate resistors tend to keep the voltage gain up and assist with the attenuation of frequencies either side of 750 cycles per second. The .001 mfd coupling capacitors contribute to low frequency roll off, while the .001 mfd plus the 39K series resistor shunting the grid of the second stage puts the finishing touch to the higher frequency roll off. The results obtained with the completed change is demonstrated in the curves and makes you feel as though you have done something to help your transmitter put out a more conservative frequency spectrum.

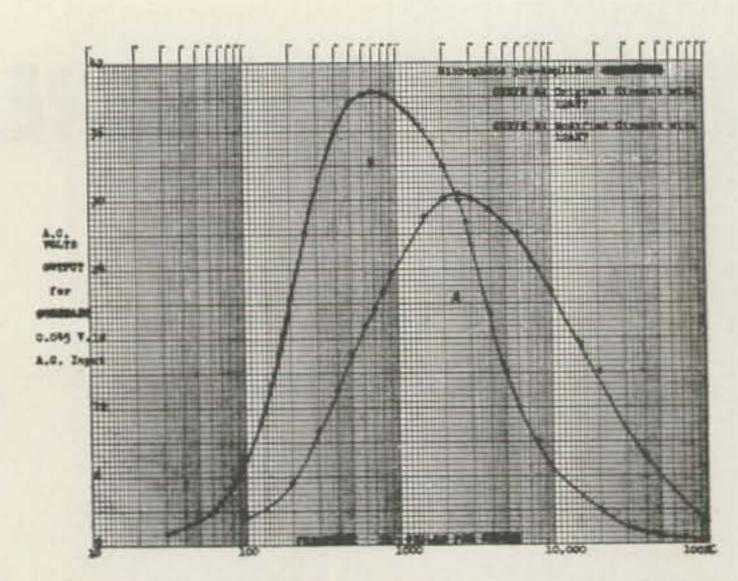A detailed inspection of the curves show "A" as the amplification characteristic of the original circuit. Curve "B" is the character-




istic developed by the changed circuit. In both cases the input voltage to the microphone jack was held at 0.045 volts ac, rms, as measured by a vacuum tube volt meter. Output was taken at the junction of the 47K resistor and the 250 mfd capacitor shown to the right of the gain control by means of VTVM. Note that the band width at the half voltage points is approximately 19.5 kc for the original circuit. It becomes approximately 3.8 kc for the modified circuit at the same point. Further comparison at the 3 dbv down points show 10 kcs for the original versus 2.3 kc for the modified. This is a modest but valuable improvement. It is especially valuable for those of us with low resonant voices. A high impedance crystal microphone, rated at -54 dbv* will produce full undistorted output from a Central Electronics Model 10-B exciter, with the gain control adjusted to 34 open. Another application might well be found for the Heathkit SB-10 since it uses the 12AX7 tube in its pre-amp circuit.

A few words of caution: Experiment has shown that there must be no substitution of types of tubes in the modified circuit. Those other than the 12AX7 will produce insufficient gain and the amplification curve will be shifted to the right and undo the apparent good. Also, remember that this is a *crystal* microphone pre-amp. Don't drive the circuit with a carbon microphone. Hold the input voltage to 0.045 volts or less.

Crisp intelligible communications is the best recommendation for this circuit. Why not try it? . . . W5SOT

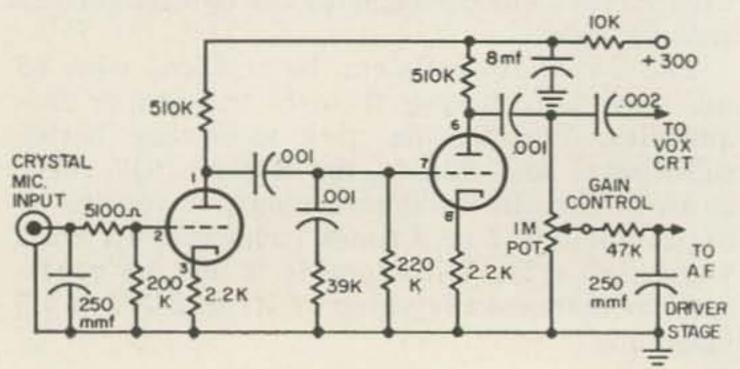*Like the one on page 173 of Burstein-Applebee Co. Catalog #621—stock #18A536 (\$2.19).




MILITARY and COMMERCIAL

ACHTUNG

users of converters and pre-amps

ASK about our unbelievably low noise designs from zero to 10,000 mc. We also design and build Nuvistor and solid state (varactor type) frequency multipliers.

for instance:

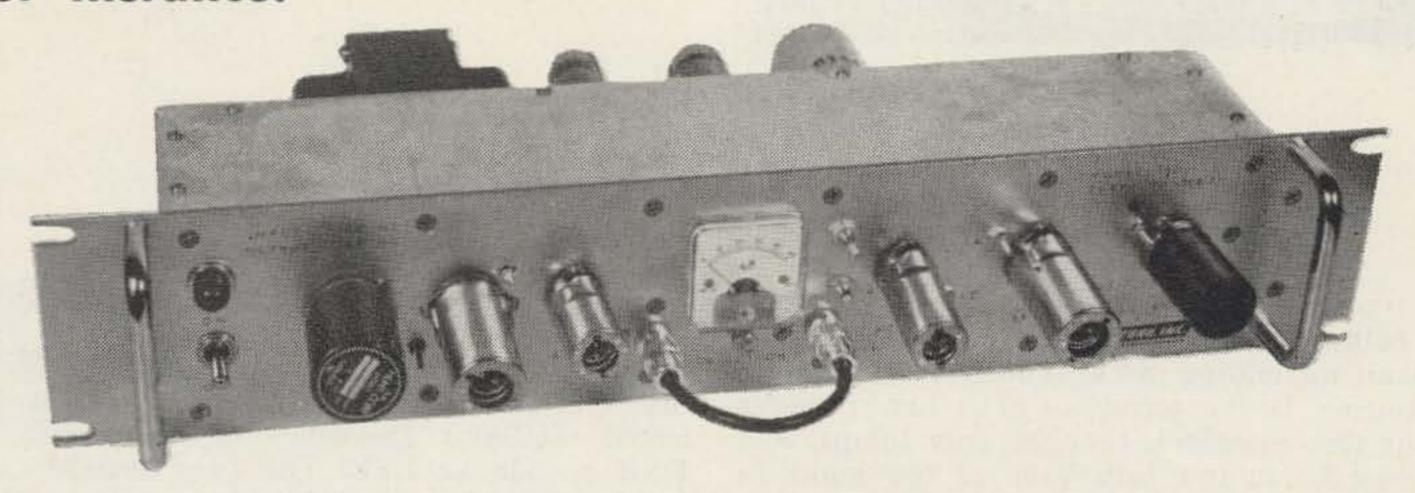

The Model 100 converter for fixed frequency commercial and military applications anywhere from 20 to 200 mc. This unit uses the 417A for the best possible noise figure, and includes a regulated power supply. rack panel, 31/2" high. Also available is the 100A for 200-500 mc. This uses the latest nuvistor type 8058 in a two stage RF amplifier.


We also make Amateur equipment:

SIX METER NUVISTOR

Converter Model 201


Noise Figure: less than 3.0 db I.F.: 14-18 mc, Input-Output: 50 ohms, BNC Power Required: 6.3v and 150 vdc Tubes: 6CW4 and 6U8 Shielded Case: 6" x 3" x 11/2" A carefully conceived design

incorporating good quality at low cost.

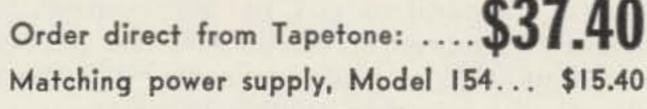

Other TELco products

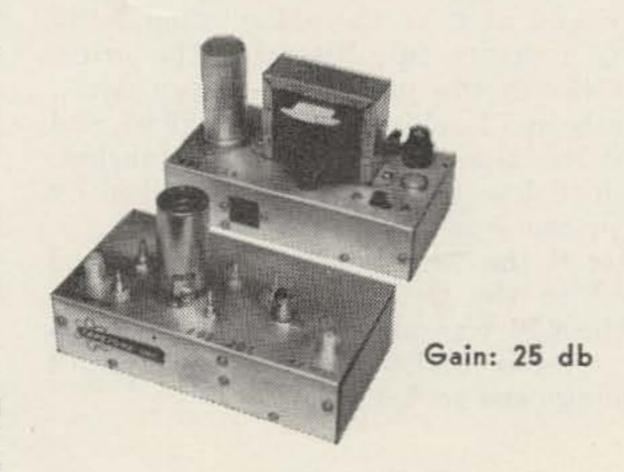XC-144, 2 meter, 417A converter, 2.8 db, 35 db . Price \$150.00 SB50 Heterodyne SSB converter, 25 watts output. Less



Model 202, 2 meter converter, overload proof companion to the Model 201. Less power supply.

Price \$45.00

Model 206, noise blanker. For use with six and two meter converters. Eliminates pulse type noise.

Price \$65.00

TAPETONE ELECTRONIC LABORATORIES, INC.

99 ELM STREET

WEST NEWTON 65

MASSACHUSETTS



Dick Gridley K6JHJ Edison Powerhouse #8 Auberry, California

Photography by Linda Gridley

The BC453,

One More Use


The slicer to be described here came into being because of crowded band conditions and an unyielding XYL. The simple solution, of course, is the purchase of a new receiver—but this approach brought only lumps, and I knew I couldn't talk 75% of the hams in California to leave the air.

The need was for a sharper receiver for CW and a good method of detecting Single Sideband. Both of these requirements were filled, plus a fine method of detecting AM was gained.

The heart of the slicer is the 85 kc filter which is constructed from the *if* transformers of the BC453. The filter is not flat on top, but it has a good shape factor. The 3 kc points are 5 DB down and at 6 kc the attenuation is 35 DB. This is a pretty fair filter for the price. I had a BC453 in the junk box—if you don't, there are ads in 73 selling them for \$9.95 and this is a lot less than any filter on the market.

The product detector is the one described by ZL1AAX in the August '59 CQ magazine.

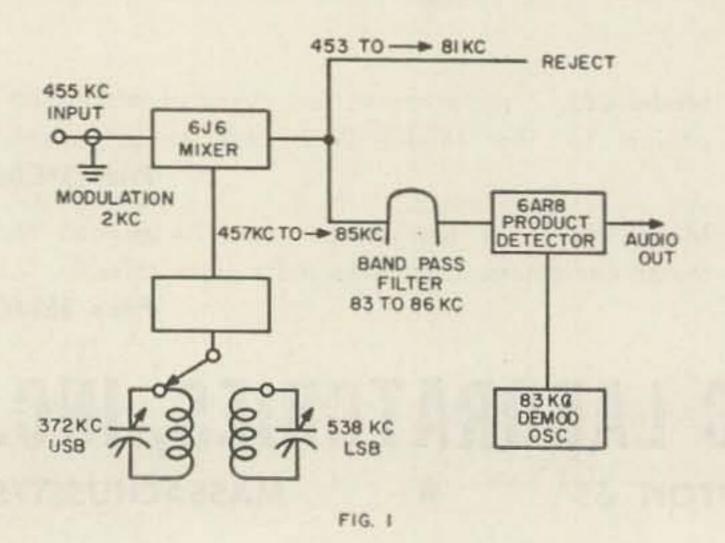The mixer is the "like-new" mixer described by the staff in the October issue of 73. The choice of the 6J6 was made because the original slicer used a 6BE6 mixer and I didn't want to change the socket.



The operation is simple, and if you follow the block diagram Fig. 1, it is easy to see. Starting with the incoming signal of 455 kc into the 6J6 mixer, it is mixed with the selected oscillator frequency of either 372 kc USB or 538 kc LSB. The fundamentals tell us that in this conversion there will be four frequencies—the incoming frequency, the oscillator frequency, and their sum and difference. In this slicer we are only concerned with the difference.


A little math at this time will show that 455 kc less 372 kc is 83 kc, and 538 kc less 455 kc is 83 kc. The differences are the same. However you will note that we position the oscillator either 83 kc above, or below the carrier frequency of 455 kc. We will now add a 2 kc modulating frequency to the carrier. Going once more to fundamentals, we know that we now have the 455 kc carrier with a 457 kc USB and a 453 kc LSB.

For simplicity of explanation, let us leave the 455 kc carrier at this point and consider only the sidebands as they enter and leave the mixer. If the selector switch is placed on the USB position the oscillator will inject into the mixer a frequency of 372 kc. The upper sideband of 457 kc will convert to and leave the mixer at 85 kc and the lower sideband of 453 kc will convert and leave at 81 kc. If the selector switch is set on the LSB position, the oscillator will inject into the mixer a frequency of 538 kc, and now the upper sideband of 457 kc converts and leaves the mixer at 81 kc and the lower sideband of 453 kc converts and leaves the mixer at 85 kc. Simple, what?

Looking now at Fig. 2, the band pass filter, you will note that the 85 kc point is in the middle of the filter and the 81 kc point is placed down the skirt of the filter to a point that gives a rejection of 40 DB. Thus, with the selection of the sideband switch, we can select or reject the sideband we want.

The selected sideband is then fed to the product detector and is beat against the low frequency demod oscillator. The output to the audio stage is the difference (85 kc less 83 kc) 2 kc. It will be noted, I hope, that this explanation is for the purpose of understanding the slicer operation, and in practice is just the reverse of the alignment.

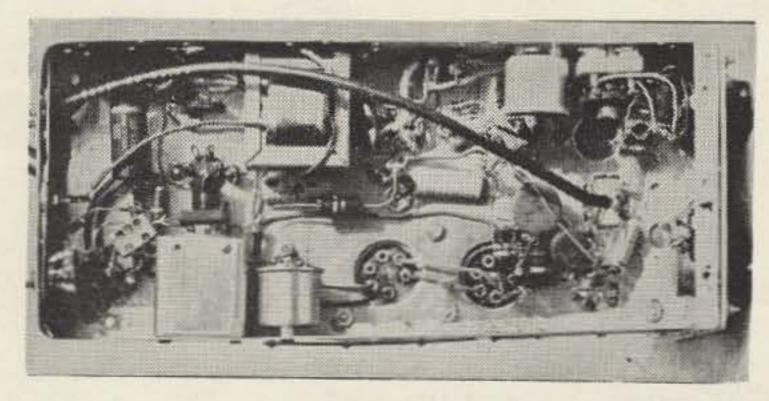The use of the sheetbeam tube as a product detector has been covered in many good articles and will not be repeated here.



The audio section is also skipped as any pet circuit will work as well as this one. In fact, the choice of tubes and components in my slicer was a matter of what was in the junk box and not a matter of choice. ZL1AAX said in his article that the 6AR8 is as extinct as a Dodo bird, and it might be well to consider the 6BU8 or the 7360.

Construction is straightforward. Extra care should be taken in the construction of the oscillators. They must be stable within 30 cycles. This is easily accomplished by the use of high quality parts and rigid mounting. My unit was constructed on the old BC453 chassis, fitted with a new face and deck made of 3/32 aluminum. The only question that might arise is power. The base station here uses a common power supply and has power to spare. If your receiver does not have enough reserve, it might be well to consider a chassis big enough to make the unit self contained with its own power supply.

Before dismantling the BC453, you should have a schematic. If not, you can mark the BFO coil and the *if* transformers when removing them. The BFO coil was used as is, the *if*


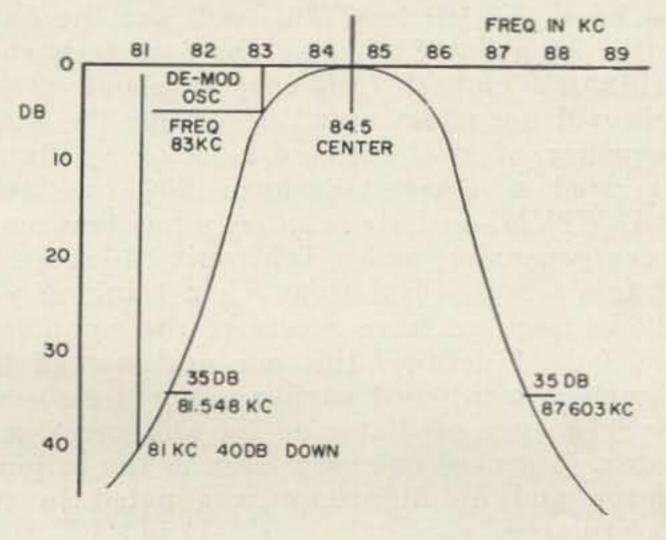


FIG. 2

were soldered to the inside lugs and brought out the bottom. This way I was able to use the base mounting ears to mount them to the new chassis with 4/40 machine screws.


A note of warning here, the 3X.05 capacitors in the BC453 should be checked for leakage. Remember these are at least fifteen years old, and I have found that about 50% of them are bad—this kind of trouble we don't need.

T1 is a Miller K-TRAN 12C1 455 if transformer. T2, T3, and T4 are the 85 kc if transformers from the BC453. T2 is the input, T4 is the output. The gimmick between T2 and T3 is three turns of the two leads twisted together and doped. T5 is a Stancor A53C, 1 to 3 interstage, plate to grid transformer connected in reverse. T6 is a standard audio output transformer. The one I used was removed from a Philco TV set. T7 is the 85 kc oscillator coil removed from the BC453.

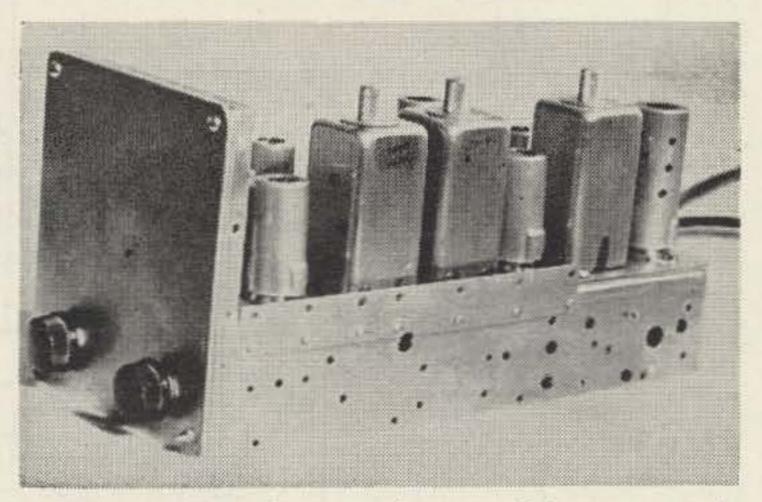

Now comes the tough one. L1 was made from an old 262 kc if transformer that was way down in the junk pile. I believe it came from an old car receiver. I removed the shield can and kept the ceramic form and both padders in tact. The two padders are C1 and C2 which are mounted on the chassis with one winding of the 262 kc if transformer. L2 was made from a self-supporting 2.5 mh RFC. I removed about 20 feet of wire from the winding of L1. L2 was made by removing 1 pie from the RFC. However, I think the best way to approach these coils is with a BC-221 which is covered in the alignment. I do feel this is the one point of failing in this unit. It would be better to pick up a couple of slug tuned inductors, for you who are lucky enough to live near a radio store, as these if trimmers were never made for vernier tuning.

The first step in putting the slicer into operation is the pruning of L1 and L2 to frequency. So let's take L1, this will be the 372 kc oscillator. Compress C1 and C2 about ¾ closed. Fire up the BC221 and check the frequency at pin #5 of the 6J6 mixer. Start removing turns until you are close. I removed about 20 feet of winding from this one I used. Then repeat the process on L2, which is the 538 kc oscillator coil. From this one I removed one full pie from the RFC. You should come

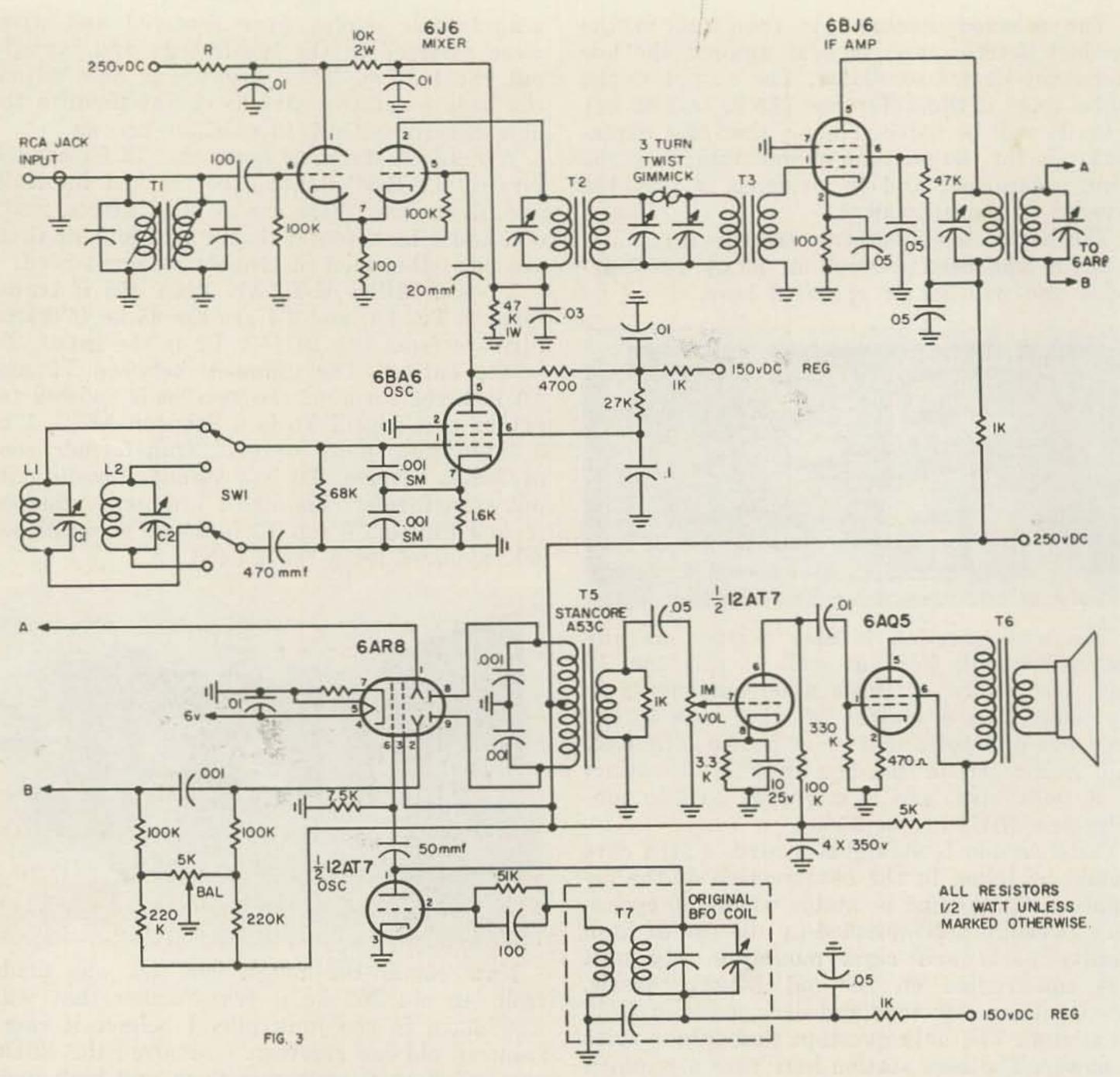


close enough so you can change the frequency about 4 kc each side of the desired frequency.

Set the resistor, marked R on the schematic Fig. 3, until you have 150v at pin #1 of the 6J6 mixer.


If you have a low frequency oscillator, such as the Hewlett-Packard 200 and a VTVM, the alignment of the filter is standard and should be peaked up at 84.5 kc—then set the slicer's low frequency oscillator at 83 kc.

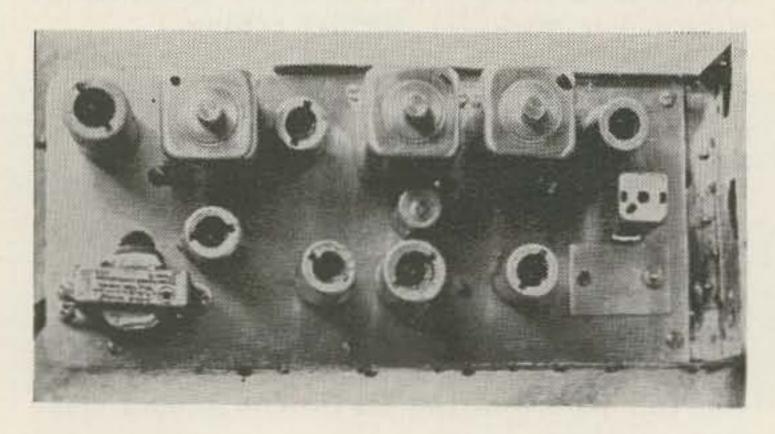Another way that works out well is to use the low frequency oscillator of the slicer for the alignment generator. Make sure that the



low frequency oscillator is running at its highest frequency. This check is best made by removing the cover and making sure the condenser is fully opened, minimum capacity. Remove the 50 mmfd condenser from pin #6 of the 6AR8 and use this to insert the signal into the filter. Peak the filter for maximum output at pins #1 and #2 of the 6AR8 and then slide the oscillator's frequency down until you have a 5 DB loss. This will put the filter center at about 83 kc, as the low frequency oscillator's highest frequency is about 83 kc. This will not effect anything except the exact frequency of the sideband selector oscillator.

I used a Hewlett-Packard 200 oscillator, 400D VTVM, an Erie counter, a low frequency sweep generator, and a Tektronix 316 scope to set this one the first time. Then thinking you fellows may not have access to the equipment that I do, I detuned this one and worked the alignment mentioned earlier using the slicer's low frequency oscillator as the alignment generator. It proved out very close to the original figures and no difference was noted in the performance.

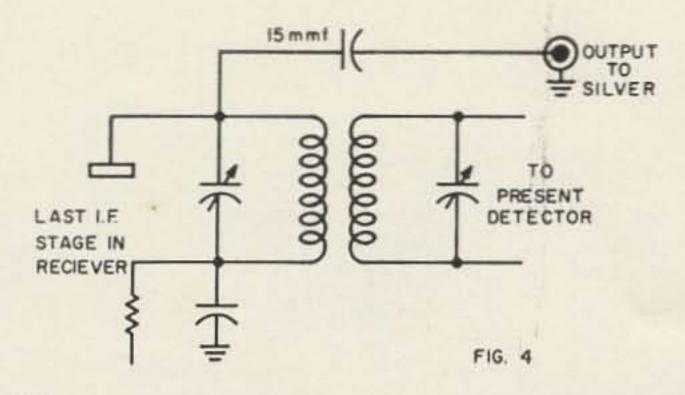

The next step is to make sure that the injection level is correct at both mixers. With an rf probe on the VTVM, check at pin #6 of the 6AR8, it should be between 2 and 3 volts. The coupling shown gave me 2.7 volts. Next, check pin #5 of the 6J6 mixer for 2 volts. The coupling shown gave me 2.1 volts.

We are now ready to put the slicer into operation. Connect the slicer to the output of the last if stage in the receiver through a 15 mmfd condenser, Fig. 4. Tune in a strong AM. signal and peak up on the S. meter. Turn off the AVC and turn the rf gain to about 1/2 open. Turn the audio up on the slicer and tune C1 or C2 (which ever one is in service) to zero beat. This will give natural sounding audio. Now change the selector switch and repeat for the other trimmer condenser. You should be able to switch from USB to LSB with no noticeable change. Adjust the 5K bal- time it takes to build it. ance pot in the 6AR8 circuit for minimum

intermodulation distortion and that is it.

The only check left is for your own satisfaction and proof that the product detector is doing all that it is supposed to. All the articles tell you that the only thing demodulated in a product detector is that which beats against the oscillator. Therefore, if you kill the low frequency oscillator, the slicer should go dead and if it is working correctly, it will. The measured carrier leak with the oscillator off, in my slicer, is down 45 DB.

This unit will please the most discriminating ham with its performance not only on SSB. detection, but on CW. and AM. phone as well.

I feel the big bonus is the use of it on AM. If you are copying a station and another station comes in close enough to cause heterodyne, all that is needed is a flip of the switch to select the other sideband and exit heterodyne.

The first time I tried it on CW I thought the slicer was dead, but tuning across the band the signals seemed to jump out from dead silence.

It is a real nice addition to any shack, and if all the parts were purchased from scratch I don't know how the cost could go over \$20.00.

All that is left to say now is-start digging into the junk box and heat the soldering iron. The enjoyment received from the hetereodynefree operation of this unit is well worth the

. . . K6JHJ


SSB, AM, CW ON SIX METERS AT A REASONABLE FROM CONTINENTAL ELECTRONICS



"Where Quality Counts First"

THE CONTINTAL "SIX" TRANSMITTING CONVERTER

\$99.95

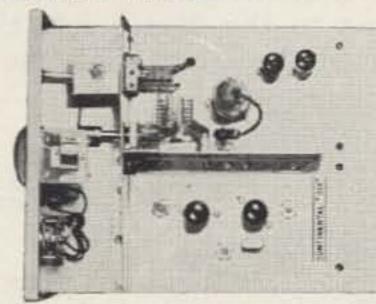


HERE'S A RIG BASED ON THE DESIGN OF K4RLX (See August 1961 VHF Magazine). 36 STATES CONFIRMED ON 6 METER TWO-WAY SSB.

FEATURES:

- Low drive requirements—Can be driven by any AM or SSB exciter with 20 meter output, such as 20-A, 10-B, DX-35, HT-37, KWM-2, etc.
- Power Requirements: 400 volts @ 75 mils, 150 volts regulated, 6.3 volts filaments.
- 30 Watts P. E. P. SSB, reduced output on AM.
- Horizontal meter reads PA plate and relative RF output.
- Uses minimum of operating adjustments when changing frequecy.
 - Extremely high "Q" circuit, high stability, excellent shielding and straightforward design to provide many hours of trouble-free operation.
 - Modern two-toned grey low temperature cabinet, only 5 3/4" high, 8 11/16" wide, 11 1/4" deep, and exceptionally lightweight.
 - Individually factory aligned and tested.

SEPARATE POWER SUPPLY AVAILABLE, WILL MATCH CONTINENTAL "SIX".-COMING SOON: THE CONTINENTAL "SIXTY-ONE" 100 WATTS P.E.P. ON SIX METERS AND THE CONTINENTAL "TWO" 175 WATTS P.E.P. ON TWO METERS.

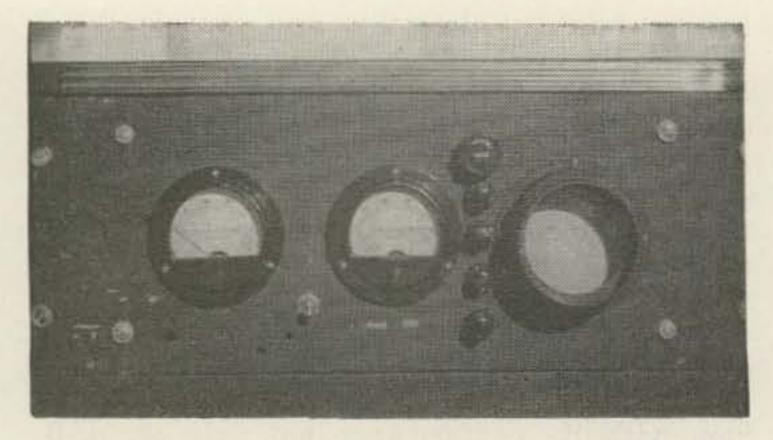Order Direct From: CONTINENTAL ELECTRONICS — Sumter, S. C.



John T. Reeder WøMWJ Route I Kennett, Mo.

Linear Scope Monitor

O NCE the excitement of getting the big gun on the air has subsided and you are satisfied that you are getting out, there eventually comes a time when the SSB operator begins to wonder just what his signal looks like.

This is one approach to getting a visual monitor, using a minimum of readily available parts and it can be incorporated as a permanent part of the rig.

This is not an all purpose scope. It is designed to produce a trapezoid pattern for monitoring a linear amplifier.

A sample of the signal from the exciter is taken off through a "T" connection between the exciter and the input to the final. This signal is rectified and filtered by the 1N58A's in series and associated circuit. Two diodes were used to provide ample voltage to drive the deflection plates of the scope tube without further amplification. The voltage divider at the input to the diodes sets the width of the pattern on the scope tube and must be re-set


for each band.

Vertical deflection is derived by a simple rf pick-up from the final tank coil. A piece of insulated wire looped through the turns of the final coil can be adjusted to produce the correct amount of drive to match the input to the horizontal plates.

If the final output is linear with the input you get a nice straight sided triangle. Overmodulation and loading difficulties show up readily.

A blocking bias can be applied to point "Y" from the exciter to provide cut-off of the beam during periods of stand-by to prevent burning the picture tube. Or, if you're not fussy, simply turn down the intensity after you have tuned up and are operating. If you change bands or move enough to re-load, it's a simple matter to turn up the intensity and say HALO a time or two while watching the scope.

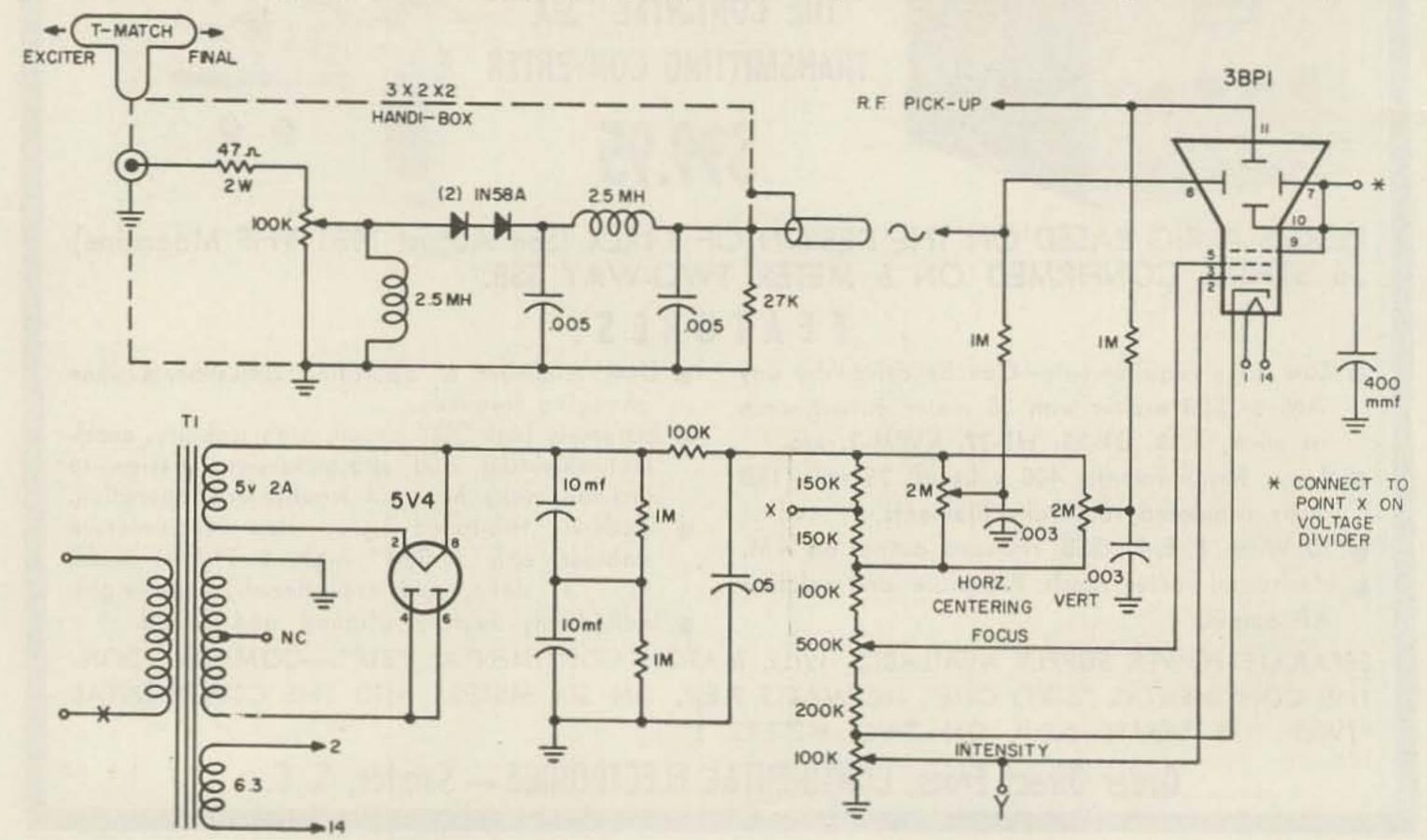The construction can be adapted to match your rig. In our case the rig had a meter panel



Radio Bookshop's

"Ve get too soon oldt unt too late schmart."

. . . . vane green

5—ANTENNAS—Kraus (W8JK). The most complete book on antennas in print, but largely design and theory, complete with math. \$12.00

13—REFERENCE DATA FOR RADIO ENGINEERS. Tables, formulas, graphs. You will find this reference book on the desk of almost every electronic engineer in the country. Published by International Telephone and Telegraph. \$6.00

17—ABC's OF HAM RADIO—Pyle (W7OE). Designed for the Novice ham. Includes all of the information needed to qualify for the Novice License. 112 pages. \$1.50

23-NOVICE & TECHNICIAN HANDBOOK - Stoner (W6TNS). Sugar coated theory: receivers, transmitters, power supplies, antennas; simple construction of a complete station, converting surplus equipment. How to get a ham license and build a station. \$2.85

24—BETTER SHORT WAVE RECEPTION—Orr (W65AI). How to buy a receiver, how to tune it, align it; building accessories; better antennas; QSL's, maps, aurora zones, CW reception, SSB reception, etc. Handbook for short wave listeners and radio amateurs. \$2.85

28—TELEVISION INTERFERENCE—Rand (W1DBM). This is the authoritative book on the subject of getting TVI out of your rigs and the neighbors sets. \$1.75

32—RCA RADIOTRON DESIGNERS HANDBOOK—1500 pages of design notes on every possible type of circuit. Fabulous. Every design engineer needs this one. \$7.50

48-BASIC ELECTRONICS - Covers subject completely. Written for use with RCA Institute training course. \$9.25

49—ELECTRONIC COMMUNICATION—Shrader. Huge book aimed at giving all information mecessary for FCC commercial and amateur licenses.

52—HOW TO READ SCHEMATIC DIAGRAMS—Marks.
Components & diagrams; electrical, electronic, ac, dc, audio, rf, TV. Starts with individual circuits and carries through complete equipments.
\$3.50

53—BASIC ELECTRONIC TEST PROCEDURES—Turner. This book covers just about every possible type of electronic test equipment and explains in detail how to use it for every purpose. Testing: audio equipment, receivers, transmitters, transistors, photocels, distortion, tubes, power . . . etc. \$8.00

58-ANTENNAS FOR CITIZENS RADIO—Or (W6\$AI)
General coverage, mobile and directional antennas for 27 mc. band. Build & tune 'em. \$1.00

59-CITIZENS BAND RADIO (Rider). EVERYTHING TOU

70—ELECTRONIC PUZZLES & GAMES—Matthew Mandl. 124 pages. \$1.95

76—MODERN OSCILLOSCOPES & THEIR USES—Ruiter. Second edition. Shows what a 'scope is, what it does and how to use it for radio, TV, transmitters, etc. 346 pages. \$8.00

86-CONVERTING BC453 TO SSB

\$3.00

87—MRT-90 CONVERSION MANUAL—This 12-page booklet contains full information on converting the 19 tube MRT-9 or MRT-90 transceivers into hot little dual conversion rigs for two meters. Complete conversion plus original diagram. \$.50

88-WESTERN ELECTRIC 255A POLAR RELAY-This accessory will be of interest primarily to the RTTY ops. \$2.50

90—TELEPRINTERS, MODEL 31A—This midget printer, complete with case, measures only 11" x 16" x 12" and is light enough to throw in the car for portable use. Complete with keyboard, ready to operate. \$100.00

G-93—RADIO CONTROL HANDBOOK by McEntee. This is the largest and most complete book ever published on the subject. 304 pages! It covers in detail every possible aspect of radio control. \$4.95

Noll (W3FQJ). Everything you need to know to pass the FCC exam and get started servicing two-way equipment. Much more than just a Q & A manual \$3.95

731—HAM TV—WΦKYQ. This is the only book available on this fascinating branch of ham radio. Describes complete ham TV station that costs under \$50. Very simple.

732—FULL SCALE PRINTS FOR MARK III IMPEDANCE BRIDGE FROM AUGUST 1961 ISSUE OF 73. These entargements of the published scale drawings greatly simplify home construction of this terrific piece of test equipment. A complete copy of the original article is also included.

734—INDEX TO SURPLUS—Bibliography of all surplus articles printed in all radio magazines to date. Brief description, etc. \$1.90

735-BOUND VOLUME-October 1960 through December 1961, 15 issues (Vol. 1). \$15.00

736—Yearly Binders for "73" Magazine October 1960 through 1961, or 1962.

of the International Radio Amateur Year Book is now out. It contains a review of the years VHF activities, a synopsis of DX activities and new countries activated, a propagation forecast for the coming year for the Eastern, Central and Western U.S., to all parts of the world, an ARRI countries list, world QSL bureaus, etc. Published in England. \$.75

SEE MARCH '73" FOR BOOKS ON SURPLUS CONVERSION, OR WRITE US FOR LIST.

Order Form

5 13 17 23 24 28 32 48 49 52 53 58 59 70 76 86 87 88 90 G93 QAN 731 732 734 735 736 IYB

Circle the book numbers you wish to order. Please include cash, check, money order . . . or something we can deposit in the bank.

Name	 		Ca	ıll .	 S & .	
Address	 				 	
City	 	Sta	te.		 	

RADIO BOOKSHOP

1379 East 15th Street, Brooklyn 30, N. Y. (N.Y.C. add 3% tax)

which included a thermo-couple RF meter that didn't tell us much. The scope tube was mounted to occupy the hole left when we took the meter out. The works were mounted on a "U" shaped chassis from an old BC-191 tuning unit. The panel controls were sub-Mounted on a strip of bakelite and extended through the front panel with polystyrene rods.

All resistors are 1 watt unless otherwise noted and the condensers should be chosen to match the voltage encountered at the point of use. The voltage divider potentiometer in the

horizontal pick up unit is a TV insulated shaft model to prevent rf break-down. The power transformer can be any available small receiver type which will produce about 800 volts total in the high voltage winding. This voltage will produce sufficient intensity for easy observation in room light and allows direct drive of the deflection plates without amplification.


Two tubes and a few parts from your junk box and you're sure your final is clean.

... WøMWJ

FM to AM

A recurring problem in surplus application is the conversion of an FM receiver to receive AM signals. This requirement often demands that the original FM circuitry be retained and either AM or FM reception be possible on a switched basis. Although many approaches to

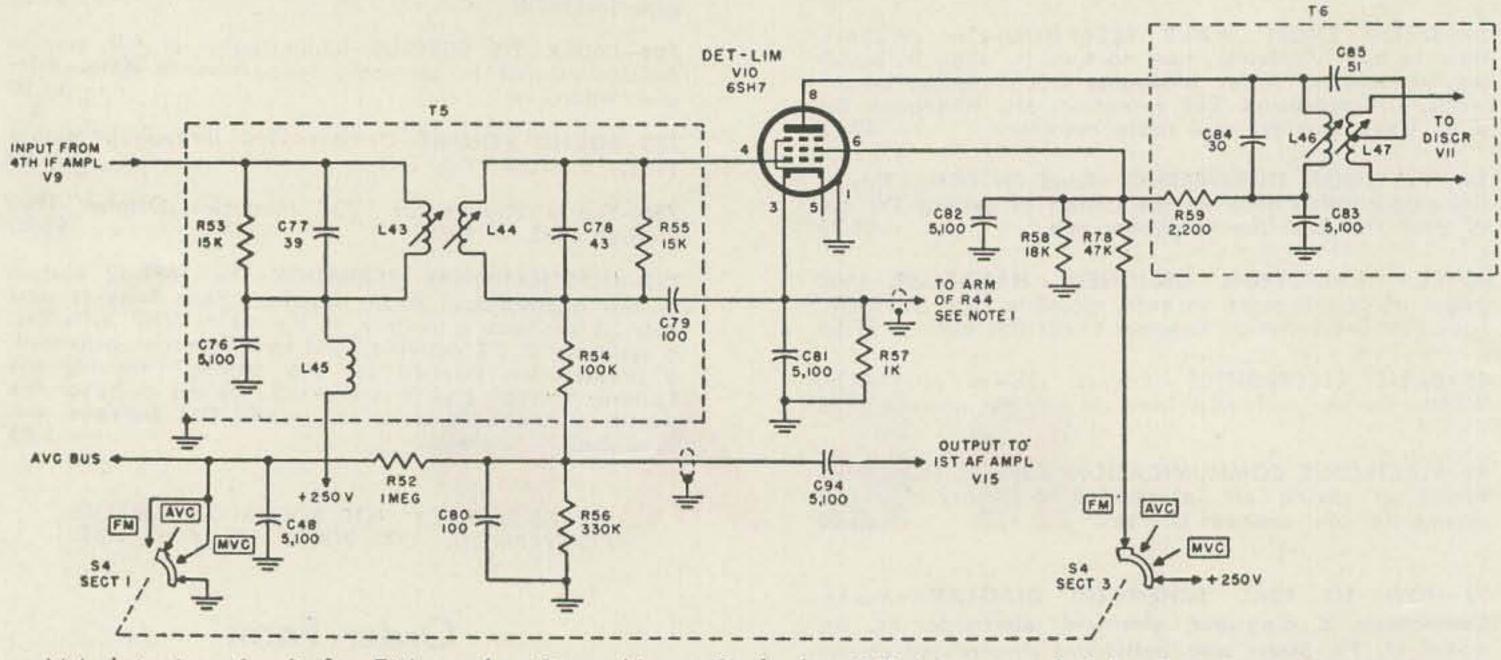Also, unless excessive distortion or signal leakage occurs, there should be no requirement for removal of the limiter plate voltage in the AM mode. The technique described has considerable merit and should have wider application than is now the case. . . W4WKM



AM detector circuit for FM surplus Gear. Note: Cathode of VIO is grounded by R44 for AM reception.

this problem have been employed, the circuitry is often complicated and the results are not always the best.

This problem is solved in a very straightforward manner in some of the older military equipment. The SCR-616 Radio Receiving Set, which used either the BC-1269, BC-1269A or the R-593/GRR Radio Receiver, is the case in point. In these receivers, the audio component developed across the limiter grid resistor is used to drive the audio amplifier directly. In addition, the dc component developed is filtered and used as the AVC voltage source in the AM mode of reception.

The schematic diagram shows this application in detail. There is nothing sacred in the component values shown or in the switching circuit used. Normal precautions in the area of

Don't Wreck That Meter


Fred Conner W9CUK

A recent article in 73 described a method of protecting meters from burnout. Perhaps an elaboration of this will be of interest.

Probably each of us has at one time or another overloaded an instrument. Simple fusing will not prevent burnout, or bent pointers in the case of severe overload.


Let us examine the ordinary direct current meter movement. Most milliammeters, microammeters, and ammeters have a full scale AVC isolation and filtering should be observed. deflection voltage of 0.1 V, or less. Inquiries

to meter manufacturers, and tests on typical meters indicate that overloads of about 10 times normal full scale voltage, or 1 volt, will seldom damage coils or pointers. Now, most silicon diodes have a very high resistance at 0.1 volts. However, as forward voltage across the silicon diode exceeds about 0.1 volts, the diode resistance becomes relatively low and, until the diode current reaches a level greatly exceeding the current rating of the diode, will seldom exceed a volt. Extreme overload will cause the diode to short rather than open.

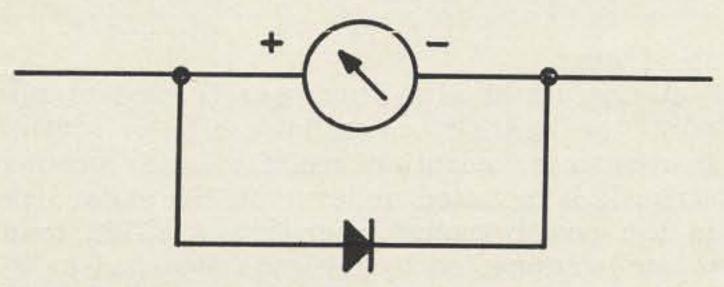

In Fig. 1 the diode is paralleled with the meter terminals. This may be a meter in current measuring usage or a voltmeter, bridge, etc. At normal meter full scale or less the diode will not effect the meter accuracy, however, in overload the diode will clamp at less than harmful currents and no damage will ensue to either meter or diode, up to the current rating of the diode. When the overload is removed, everything will be normal and undamaged.

The ordinary inexpensive "top hat" silicon power diode of ½ ampere and about 400 v PIV rating will protect even sensitive microammeters up to 500 ma. or more. At great surge or overload the diode will short and be destroyed but will still save the meter. Where a possibility of greater current exists, diodes of larger ratings may be employed. Fig. 2 shows the use of 2 diodes. Here, as is not true in Fig. 1, overload of any polarity will not cause meter damage. Circuit 2 will also protect against any ac overloads, within the limitations of the diodes.

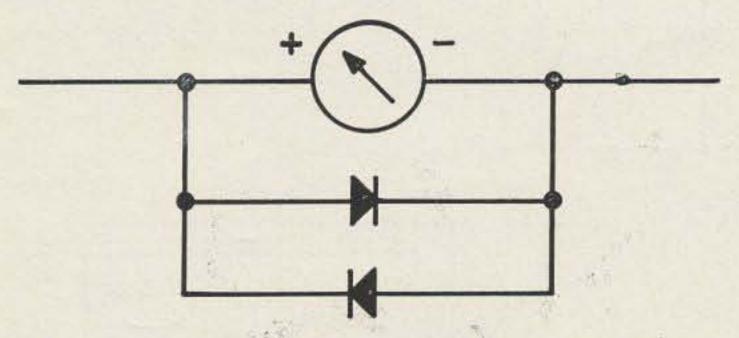

In conlusion, mention is made of experience in a large communications manufacturing plant. For the past several years the methods described above have virtually eliminated burnt out or bent pointer damage in many pieces of factory equipment which are normally subjected to frequent and severe overloading. Sensitive meter type relays have also been thus protected with complete elimination of previous frequent and costly damage.

.. W9CUK

Amateur & CB Crystals

\$3.00 2500 kc to 15,000 kc, fundamental frequencies 15 mc to 30 mc, third mode

\$3.50 30 mc to 50 mc



All crystals for amateurs are set at 20 mmfd, hermetically sealed with pins optional: .050" (CR-1); .093" (FT-241/3); .125" (HC-6); ½" centers.

Citizens Band transmitter crystals in stock for the following equipment: JR-800, 761A, CD1, GW10, CD5, CD100, CD100A, TR330, C27, AT20, Messenger, MK7, R2700, TR910, 27C2, ED27, CR117, CDD5, CT1, RP115, CD27, TECT. Guaranteed .004% of nominal: \$3.00.

AMERICAN CRYSTAL CO. P.O.BOX 2366 • KANSAS CITY 42, MO.


HY-TRACK TOWERS

The biggest improvement in crank-ups yet — you crank up the antenna and not the tower. It takes a minimum of space, is fast to erect, and you can never fall off! Makes it a snap to change beams or make adjustments whenever you please. You can even crank the beam up to the best height for current propagation conditions. See the photos on page 15 of the March '62 73 for a better idea of what this is all about. Send for literature and prices:

TOWERS
SULLIVAN
ILLINOIS


Louis Hutton WORQF 2608 South Fern Wichita 17, Kansas

The Band Warmer

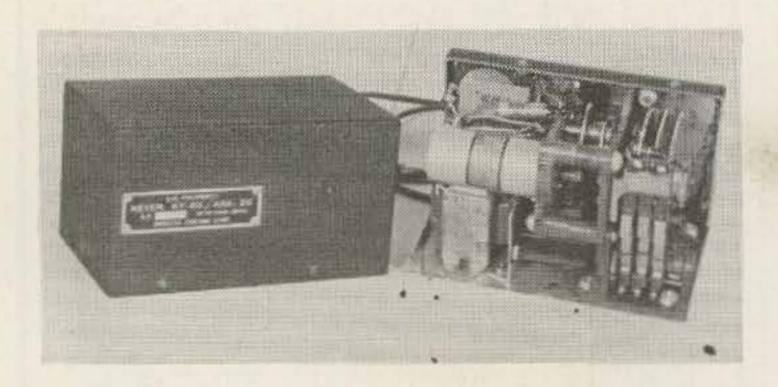

THIS modification to the Keyer KY-65/ARA-26 provides the builder with a unit that will automatically key a transmitter in the CW mode or will modulate a transmitter in the MCW mode. Code discs are used to determine the message sent.

The KY-65/ARA-26 Keyer is available from several surplus houses. I purchased mine from R & W Electronics, Chicago, Illinois. The first thing I did was strip out all parts down to the bare chassis. A new overlay panel was fabricated for the front of the box to cover up the connector holes and improve appearance. The motor and disc assembly was disassembled, cleaned, and the micro-switches removed from

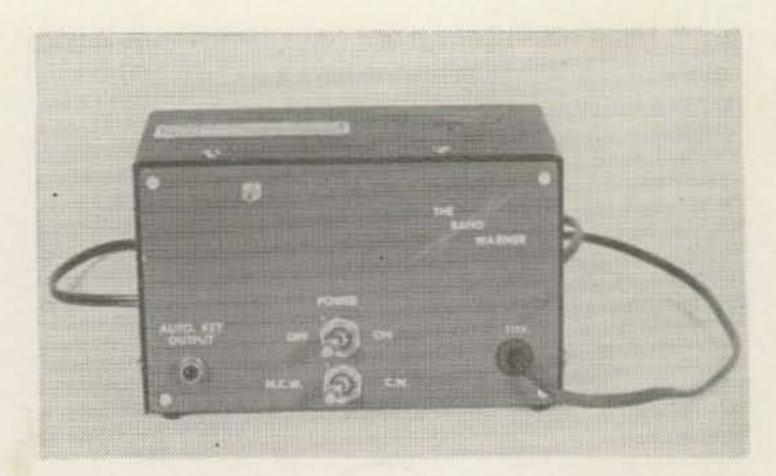


the frame.

A bracket of aluminum was formed to support the transistor audio oscillator output transformer, selenium rectifier, and terminal strip. It is mounted underneath the motor next to the power transformer. The CK-722 transistor is supported by its leads attached to the terminal strip. The SOS disc and the plastic code disc were replaced with new discs. The disc in the SOS position now sends DE-WφRQF and the identification disc sends $W\phi RQF$. The center disc is usable as is or may be replaced with one cut to send CQ. The new discs should be filed and sanded as smooth as possible to prevent excessive wear to the wiping contacts on the keyer assembly.

When using the unit in MCW mode on the VHF bands, the output is connected to the telephone patch or microphone input of the modulator.

On the HF bands in the CW mode the output is plugged into the key jack of the transmitter.

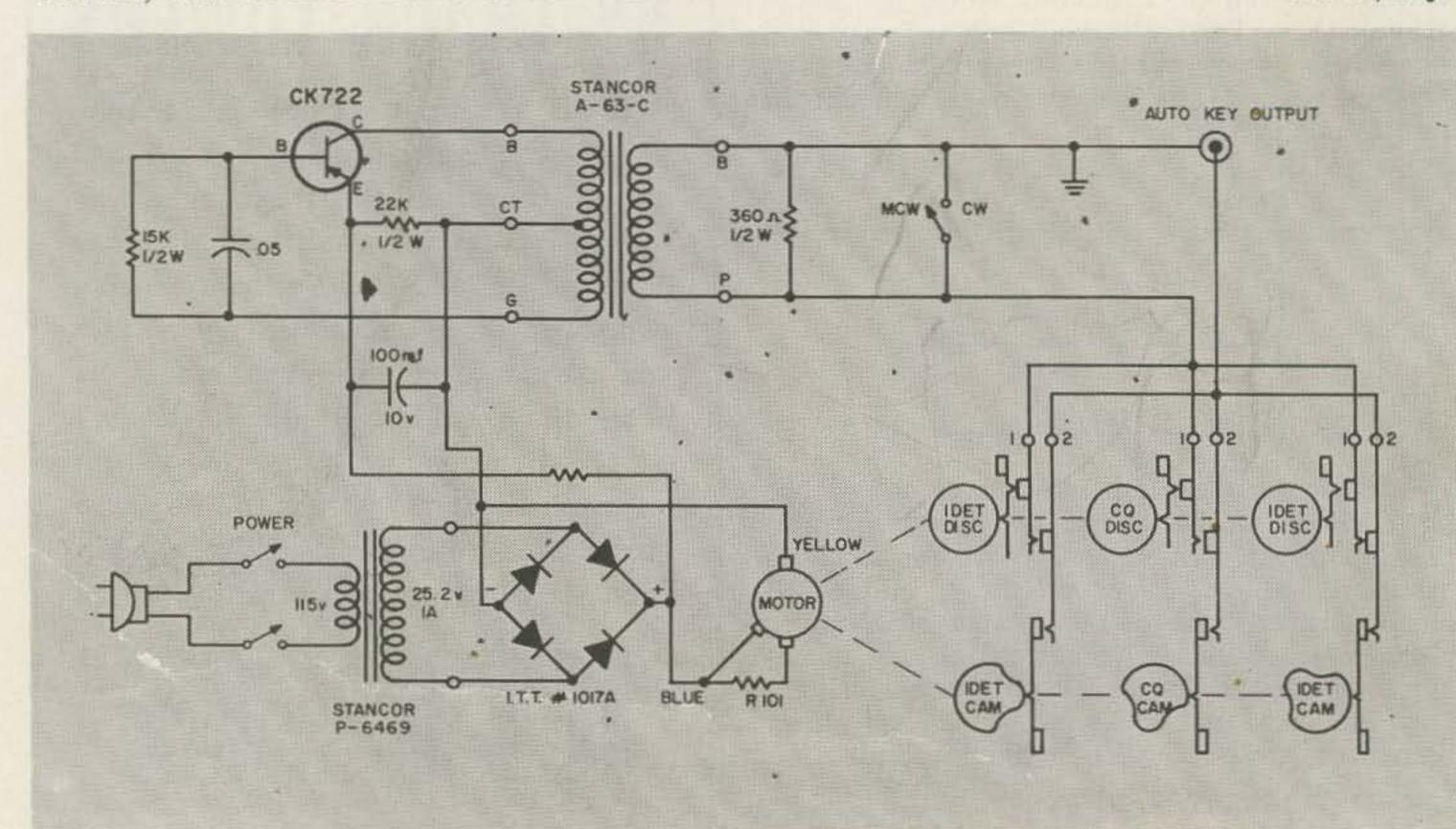This gadget is very handy on VHF DX contests, warming up the band, equipment testing, and propagation studies—any other ideas? $\dots W \phi RQF$



Home Brew Bridge Calibration

This table is useful for all homebrew SWR bridges and gives the % reflected power and the % full scale reading in the reflected mode, when the meter is set at full scale in the forward mode.

SWD	of D D a				
SWR	% Pwr. Refl.	Refl. Rdg. in % of Full Scale			
1.1	.2%	4.8%			
1.2	.8	9.1			
1.3	1.7	13.1			
1.4	2.8	16.7			
1.5	4.0	20.0			
1.6	5.3	23.1			
1.7	6.7	25.9			
1.8	8.2	28.6			
1.9	9.7	31.1			
2.0	11.0	33.3			
2.1	12.6	35.5			
2.2	14.0	37.5			
2.3	15.5	39.4			
2.4	17.0	41.2			
2.5	18.4	42.9			
2.6	19.7	44.4			
2.7	21.1	45.9			
2.8	22.5	47.4			
2.9	23.8	48.7			
3.0	25.0	50.0			
4.0	36.0	60.0			
5.7	49.0	70.0			
9.0	64.0	80.0			
19.0	81.0	90.0			
		W40AB			



Unmatched performance, mobility, versatility with the DAVCO Model DR30 communications receiver:

double conversion, mechanical filter selectivity, extreme stability; all the features you want and need for only \$289.50 ready to go. Write for full information on the receiver and associated exciterlinear units.

(Our orders are still on a waiting-list basis, and thanks again for your tremendous interest in our new product line!)

davco electronics company

113 Norwood Avenue . Asheville, North Carolina

TOPAZ 250 WATT CONVERTERS



- · Short circuit protected
- . Compact only 3 15 " x 4 % " x 6 16"
- · Epoxied magnetic components
- Epoxy fiberglass printed circuit board
- . Accessible resistors, condensers and transistors
- · Regulated drive power for extra long life and high efficiency
- Unconditionally guaranteed against defects in materials and workmanship for a period of 6 months

MOBILE POWER AT EXCEPTIONALLY LOW COST

Topaz Static Converters operate the majority of mobile transmitters and receivers. Through new concepts in converter circuitry* these units deliver more watts per dollar than any comparable unit. In addition, they are smaller and lighter in weight, and higher in efficiency. This means increased savings through longer life of batteries and generators.

New models are now available designed specifically for or adaptable to the following applications:

600 vdc (.415A) 300 vdc (.5A) 120 vac 400 cps	C10WG 600 vdc (.415A) 300 vdc (.5A) 0-120 vdc bias	C10WDG 600 vdc (.415A) 300 vdc (.5A) 0-120 vdc and Relay	650 vdc (.325A) 270 vdc (.13A) LC filter and 2 Relays	C10XDG 800 vdc (.325A) 280 vdc (.21A) LC Filter and Relay -50 to -90 vdc bias	
Johnson Viking Mobile	Collins KWM-2	Swan, all models, Collins KWM-2	Gonset "G-76"	Collins KWM-1, 2	
\$79.50	\$89.50	\$99.50	\$119.95	\$134.95	

NOTE: Any combination of above outputs - up to 250 VA total maximum, except C10XDG - 260 watts.

GENERAL SPECIFICATIONS FOR ALL MODELS

Input requirements: Voltage 11-15 VDC, 13 volts nominal

Efficiency: 85%

Approximately 7 lbs.

Weight: *Patent Pending.

**SW12A (Swan part number) is made by Topaz for Swan Engineering for use with Swan Transceivers. Order from your local Swan dealer.

California Residents Add 4% Sales Tax to unit price. Enclose \$2 for Insured Parcel Post, No C.O.D. Orders.





TRANSFORMER PRODUCTS, INC.


3802 HOUSTON ST., SAN DIEGO 10, CALIFORNIA - CYpress 7-4815

Order from local electronics distributor - if unavailable order factory direct.

PROPAGATION CHART

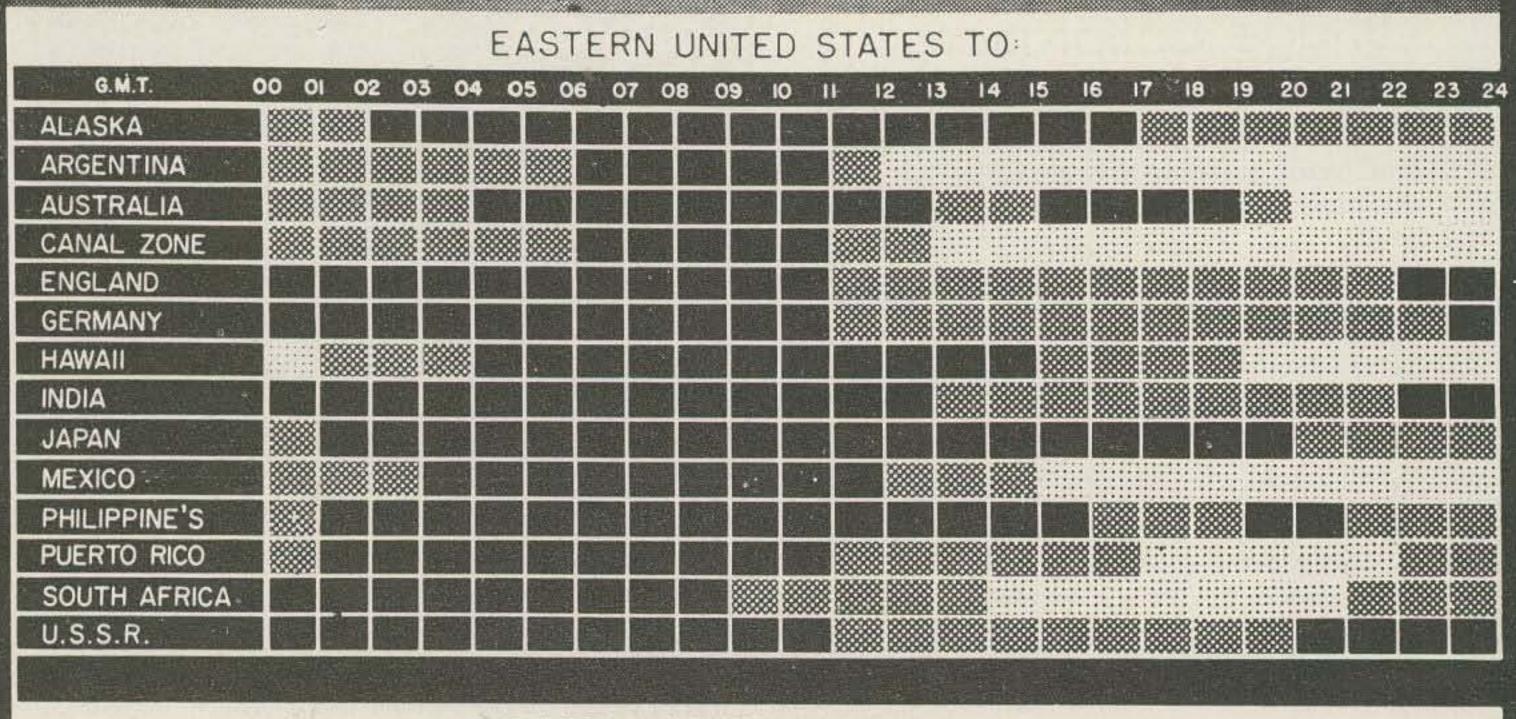

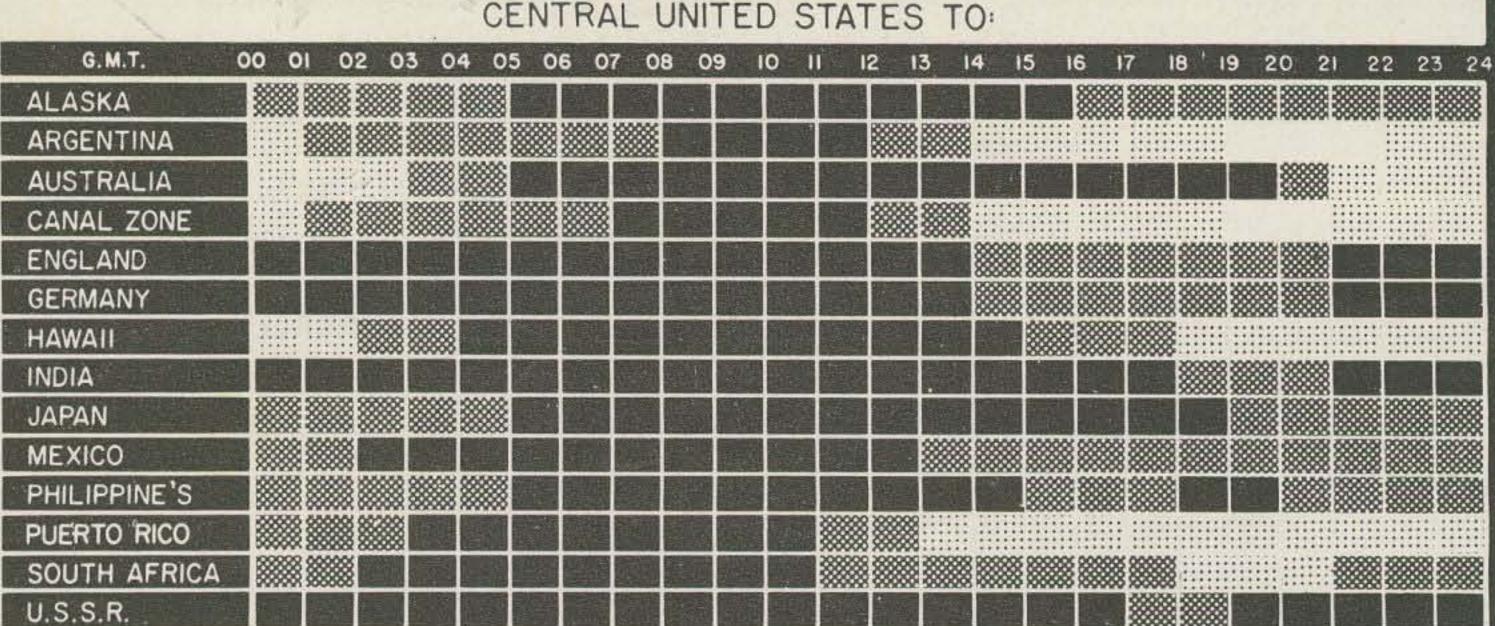

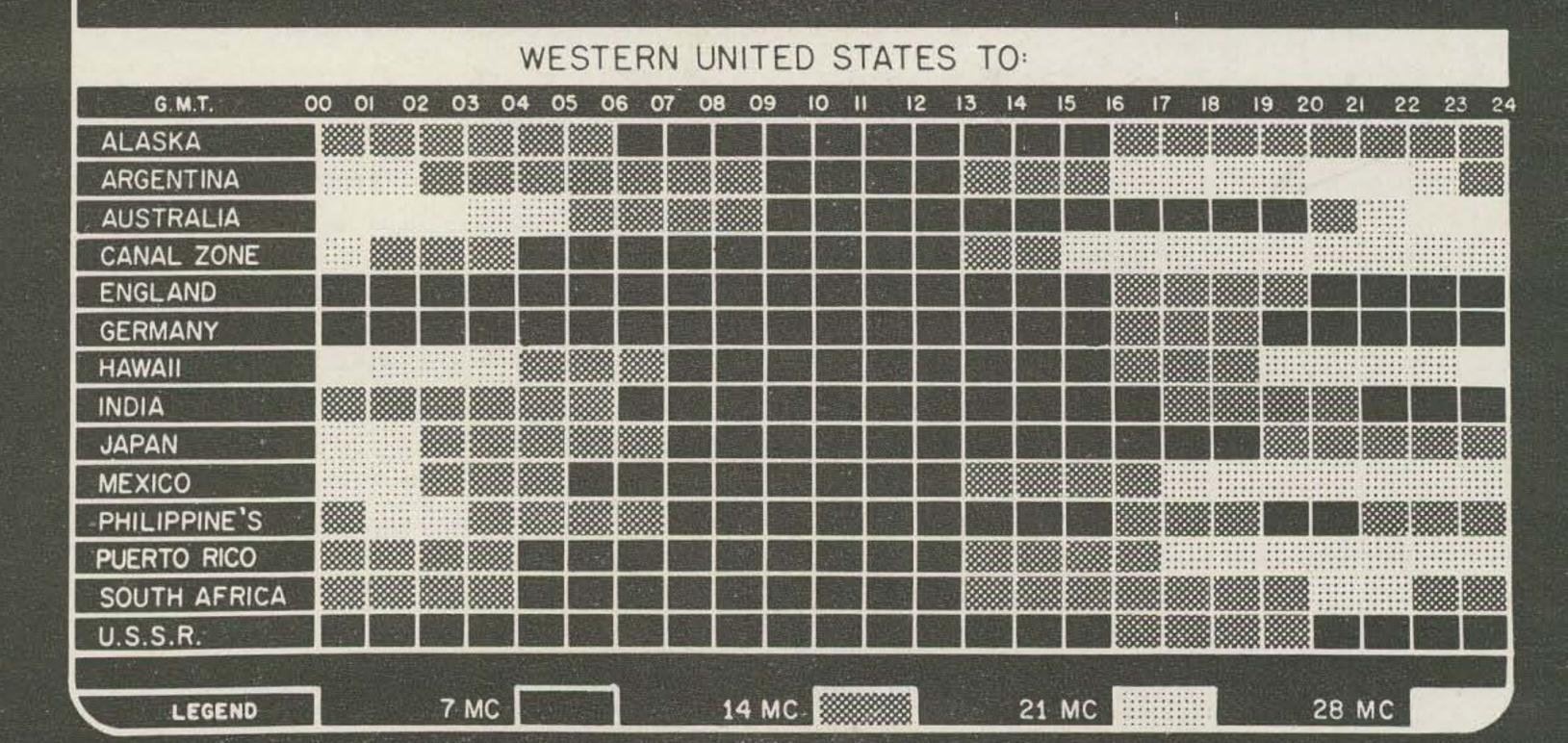

Propagation Charts

David A. Brown K2IGY 30 Lambert Avenue Farmingdale, N. Y.

For the DX propagation chart, I have listed the HBF which is the best Ham Band Frequency to be used for the time periods given. A higher HBF will not work and a lower HBF sometimes will work, but not nearly as well. The time is in GMT, not local time.

The Short Path propagation chart has been set up to show what HBF to use for coverage between the 48 states. Alaska and Hawaii are is somewhat different than the DX chart. First, the time is the local time centered on the mid-point of the path. Second, the distance given in miles is the Great Circle path distance because of the Earth's curvature. Here are a couple of examples of how to use the chart. A.) To work the path Boston to Miama (1250 miles), the local time centered on the mid-

Advance Forecast: April 1962


Good: 8-11, 17-20, 23-29

Fair: 1-3, 6-7,12-13, 15-16,


21, 30

Bad: 4-5, 14, 22

Things could be worse

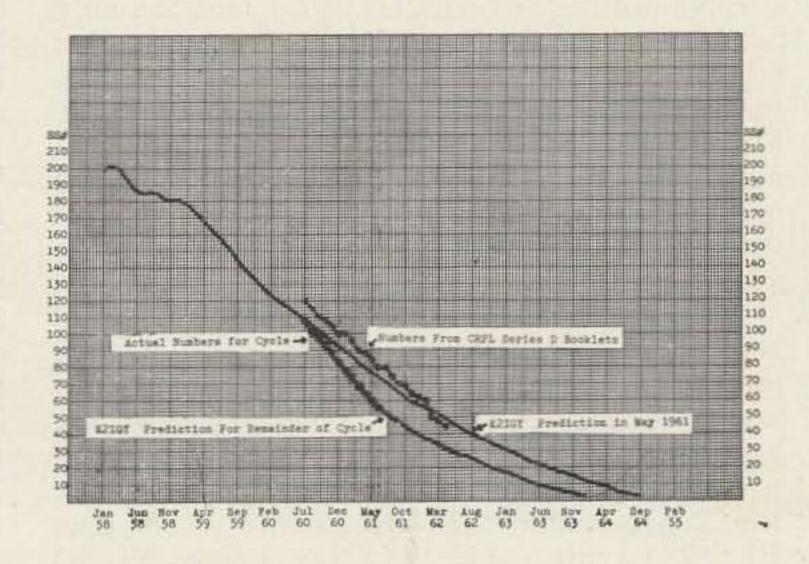

point of the path is the same in Boston as in Miama. Looking up the HBF's next to the 1250 mile listings will give the HBF to use and the time periods given will be the same at each end of the circuit. B.) To work the miles), the local time centered on the mid-point of the path will be 1½ hours later than at San Francisco and 1½ hours earlier than in New York (the time difference between New York and San Francisco is 3 hours). Looking up the HBF's next to the 2,500 mile listings will give the HBF to use. In San Francisco subtract 1½ hours from the time periods listed for local time and in New York add 1½ hours to the time periods listed for local time periods listed for local time.

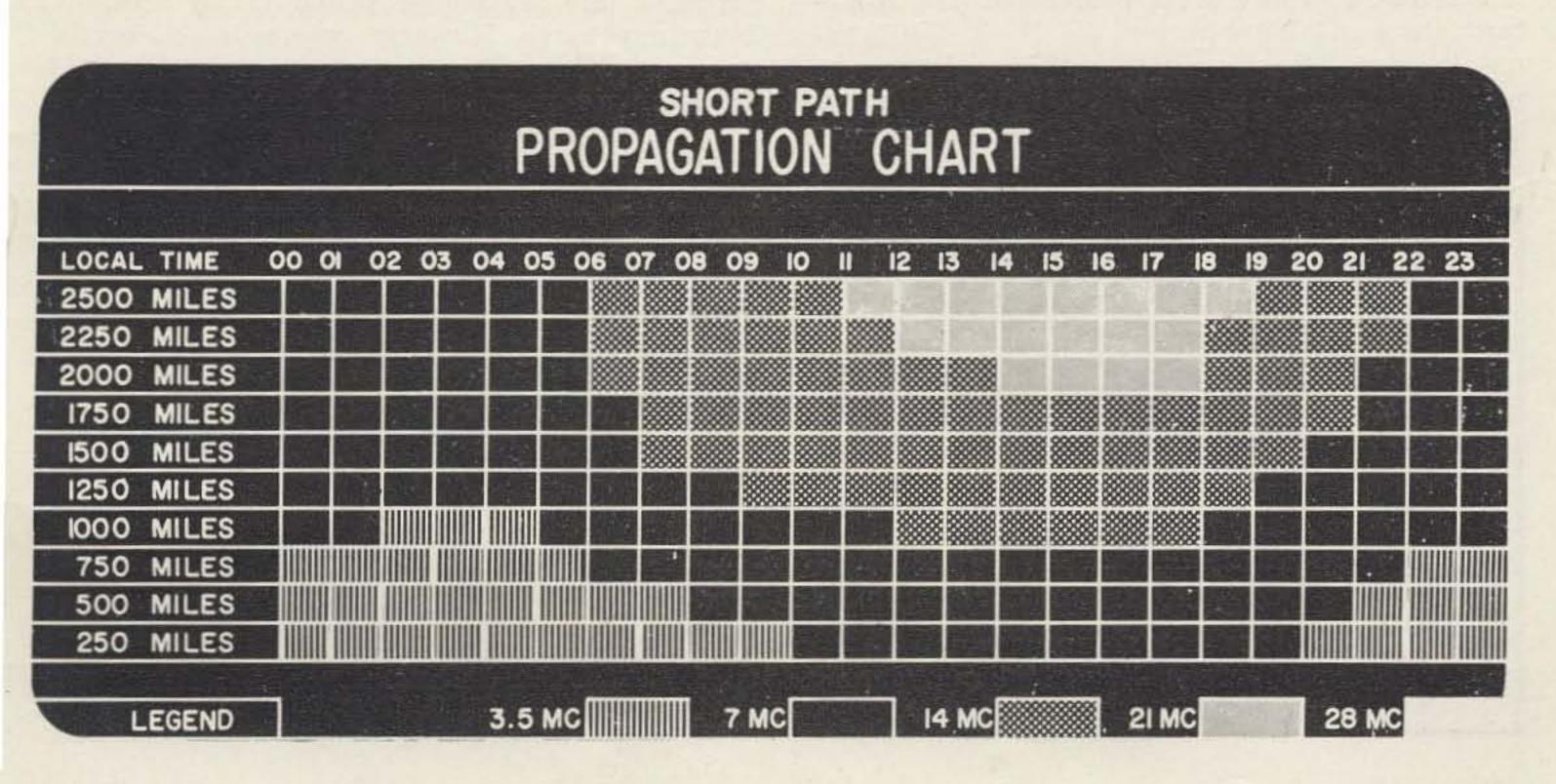

Technical Manuals for Surplus Equipment

Non-availability of technical information on surplus military electronics equipment has long been a serious problem. While certain surplus dealers specialize in the sale of such manuals, the selection is anything but complete. The Superintendent of Documents, U.S. Government Printing Office, Washington 25, D. C., is one source of manuals published by the military services but, once again, the selection is very small.

Manuals stocked are limited to general reference books and texts and few, if any, instruction manuals on specific equipments are available from this source. Publications on the general subject of radio are listed in several price lists which may be obtained by writing the Superintendent of Documents. Price lists PL 19 (Army), PL 63 (Navy) and PL 82 (Radio) are pertinent. Of the 22 Signal Corps Technical Manuals listed by GPO in PL 19, 19 are general reference manuals or training texts and 3 deal with air navigational facilities.

Incidentally, one item in PL 19 is deserving of special mention. Army Technical Manual, TM 11-690, "Basic Theory and Application of Transistors," at \$1.25, is a very fine buy. This book packs a lot of information in its 263, 8" x 10" pages. This book starts with the basic principles of solid state devices and carries you through advanced circuits.

One little used and quite productive source of current Army Technical Manuals is the Department of the Army, Office of the Adjutant General, Washington 25, D. C. Unfortunately, this office does not publish a listing of publications that are available for sale since the status and price varies unpredictably. Of the unclassified, current Signal Corps Techni-

cal Manuals, approximately half may be bought from this source. The balance may not be sold, either because of limited stocks or because they contain copyrighted or proprietary material.

Manuals are still stocked for some of the World War II, and earlier, equipment, although availability is quite spotty. One category of equipment poses almost insurmountable problems. Old Army Air Corps equipment manuals that were phased out of Army channels and not picked up by the Air Force are simply not available. The publications should be ordered by number to insure that you get what you want. This may be a problem, although most Army surplus equipment has a warning plate or decal installed which reads something like "Before Operating This Equipment, Review TM 11-..."

All in all, the AG source is quite productive and it is certainly worth a letter to the Department of the Army to determine the status of the manual you need. Address your request to the above listed Washington office, attention: AGAM.

Those who live in the Washington area may take advantage of the services offered by The Library of Congress. Extensive microfilm files of military publications are maintained and photographically reproduced copies of a single page or an entire publication may be purchased. Prices are in line with commercial charges for photostats, so reproduction of a complete manual would probably be prohibitively expensive. However, a single schematic diagram could well meet your requirement and, for a single page, the cost is within reason.

... W4WKM

QTH AMATEUR RADIO


UNITED STATES & ADJ. PARTS CANADA-MEXICO

BRAND NEW — UP TO DATE!

SHOWS MANY CITIES OF 250 POP. & ALL OVER 5,000 TOPOGRAPHIC FEATURES, RAILROADS, HIGHWAYS & RIVERS

PERTINENT DATA ALL STATES IN THE LOWER MARGIN IN 6 BEAUTIFUL COLORS 52" x 34" IDEAL MURAL SIZE CO-ORDINATES FOR QUICK QTH DETERMINATION A CALLBOOK COMPANION — IDEAL PIN MAP CHART SHOWS ALL FREQUENCIES OF RADIO SPECTRUM (AMATEUR & COMMERCIAL) (500 KC—30,000 MC) SCALE 1" — 65 MILES; MAILED IN STURDY MAP TUBE PRICE: \$3.00 — ORDER FROM W5GO8

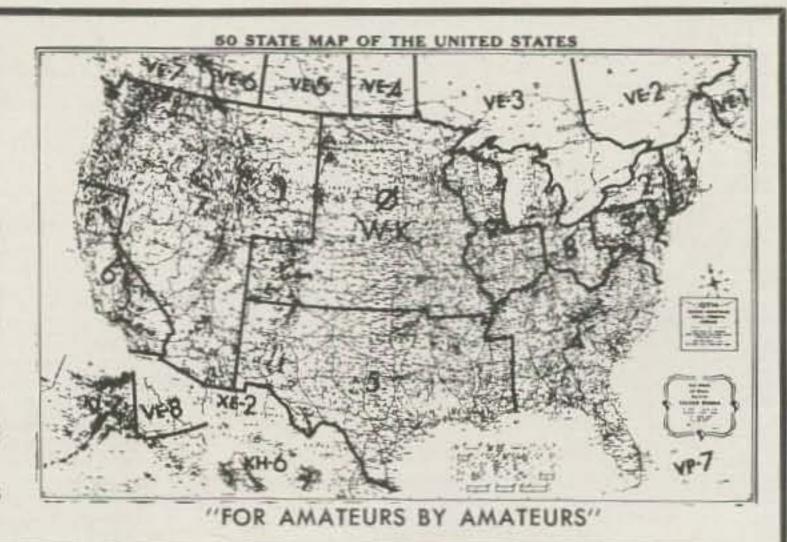905 Midland Savings Bldg., Midland, Texas
ADDL. POSTAGE OUTSIDE U.S.A.



..... BARRY ELECTRONICS CORP...... ELECTRO-VOICE/RME 6900-SSB/AM/CW

HAM-BAND RECEIVER





THIS CAN BE YOURS and BARRY will Make it EASY for you to buy it.

BUY FOR CASH . . . OR, BARRY ELECTRONICS WILL OFFER YOU THE MOST **FABULOUS TRADE-IN IN HISTORY. WRITE!**

The RME 6900 offers optimum performance on SSB, AM, or CW with no compromises or apologies to competitive high-priced receivers. Units are in factory-sealed cartons, and are covered by Electro-Voice/ RME full-factory warranty. Whether you operate SSB, CW, or AM, you feel that the RME 6900 was designed solely for you.

Has Complete function controls necessary for a modern communications receiver . . . Vernier control knob with over-ride clutch for fast tuning; RF gain; AF gain; Antenna Trimmer; Band-Selector; Stand-By/Receiver/Calibrate/Transmit; ANL Limiter; "T"-Notch Filter; Internal 100 Kc Hermetically-sealed crystal calibrator. Some additional important features on the RME 6900 are:

- CONTROLS: 111/2" Single Slide Rule Tuning Dial: Logging Scale.
- COVERAGE: 80, 40, 20, 15 and 10 on 5 Bands, plus 10 to 11 Mc for WWV or WWVH.
- · PEAK Selectivity plus tunable "T" Notch.
- 500 and 4 Ohm Outputs.
- NOISE Limiter for SSB and CW, AM.
- SEPARATE Detector for Single Sideband.
- S METER Calibrated in 6 db Steps above S9 for Better Reading.
- IMPROVED Fast Attack AVC Circuit.
- SELECTABLE Sideband. Upper or Lower.

Amateur RME 6900. \$369.00

RME 6901 Matching

Speaker \$19.50 Amateur Net

RME/PREPAID ANYWHERE: USA OR FOREIGN

ONE-HAND control knob of the Modemaster Switch gives five distinct functions. The AM band width is 3.5 Kc with fast attack AVC System. In upper and lower side-band the AVC System is also switched to fast attack with the BFO automatically turned on and positioned for desired side-band reception. An advanced Product Detector switches in to replace the Diode Detector in all SSB and CW positions. When switched to the CW position, the band pass on the IF system is reduced to 500 CPS with the BFO Injection Control and Pitch becoming operational. The AVC System is changed for optimum use when operating under CW conditions. The RME 6900 is truly the paramount CW/SSB/AM Receiver. You are cordially invited to visit us and listen for yourself.

FABULOUS trade-ins on your present receiver will be given. Let us know of your interest and we will give you the BEST POSSIBLE DEAL available! The top DX'ers now using this receiver have attested to its capabilities PARTICULARLY when QRM conditions prevail or when the rare DX shows up.

ELECTRO-VOICE MICROPHONES:

Model 664 Dynamic, HI-Z with Models 419S Desk Stand. \$57.00.

Model 911 Crystal, HI-Z. \$19.50. Model 715 Ceramic, HI-Z. \$7.80.

Model 715S Ceramic, HI-Z with Switch, \$9.00.

Plate Transformer:

Pri.: 115 VAC @ 60 CPS.

Sec. 3200 V.C.T. @ 350 Ma. Compact, shielded, Net wt: 21 lbs. 6" H x 4\%" W x 6\%" D.

Order stock #ET-18A. \$13.95.

Mobile Radio Power Supply: Mfd by Minneapolis Honeywell Model W612A. Input: 12.6 VDC (Nominal) with 17 AMP Maximum current draw at full load. All transistorized. Output: Dual voltage-250 and 500 VDC, Nominal. Current — 300 Ma. on 500 V. tap. 200 Ma. on 250 V. tap. $6\frac{1}{12}$ " H x $5\frac{1}{2}$ " W x $3\frac{1}{4}$ " D. \$54.95. 700 Volt Dynamotor: Input: 12.6 (21 Amps.) Output: 700 VDC at

260 Ma. Brand new. \$13.95.

Brand New Jan RCA 4X150A Tubes......\$12.50

BARRY ELECTRONICS CORP. Dept. 73 512 Broadway, New York 12, N.Y. Phone: 212 WAlker 5-7000

Enc.	is my	order	with	money	order	or check
Send	new	1962	Barry	s Gre	ns eet	Catalog.
Cand	inform	mation	on D	ME 60	no Da	COLLIGIE

Send in	formation	n on	RMI	£ 6900	Rec	eiver.	
I have	available	for	trade	in for	the	6900	Re-
ceiver the	followin	g					
Condition							
Name							

Company Address

Prices FOB, N.Y., except RME Recvr FOB destination.

Precision Measurement for the Amateur

Roy Pafenberg W4WKM

A s his construction projects become more complex, the amateur often discovers that the general run of test equipment designed for the service industry does not completely meet his requirements. In addition to the generally accepted lack of accuracy existing in the trade instruments, there are certain circuit parameters and component characteristics which are simply not measurable with equipment of that category. If at this time the basement work shop amateur is exposed to the test equipment and techniques of a modern research or engineering activity, his dissatisfaction with his own equipment and methods increases space.

The cost of laboratory instruments to equip a small electronics engineering or development shop with the basic minimum of modern test instruments can easily exceed \$25,000. This figure does not include specialized equipment for work in such areas as microwave, but is limited to general purpose instrumentation. Obviously, such an investment is not warranted for even the most inveterate amateur constructor.

A review of the precision instrument catalogs of the last two decades will reveal that many types of instruments have increased in cost far more than the shrinking purchasing power of the dollar would justify. Comparison of formerly available instruments with the current crop does not, in most cases, show any great improvement in basic accuracy. While there have been some changes in the approach to precision measurement, most instruments have simply become more complex in order to provide increased operating convenience and to conserve valuable engineering time.


Good examples of this developmental trend may be found in the field of audio and radio frequency measurement. Frequency meters, along with primary and secondary frequency standards, have been available for years and the basic limitation on accuracy has been that of the standard or calibration oscillator. These instruments, through the use of transfer and interpolation oscillators, detectors and indicators, can precisely determine the frequency of an unknown signal. Frequency counters were then developed to speed up these measurements. These instruments, using computer techniques, continuously and repetitively display the frequency of the signal being measured by means of read out indicators on the

front panel of the instrument. This instrument saved much manpower, however a technician or engineer was still required to read and record the readings displayed. To eliminate this requirement, the recording printer was developed for use with the frequency counter. This device prints, at any previously determined rate, the frequency read by the counter. The precision, convenience and lack of human error of these automated instruments leads to a great saving of engineering and scientific manpower in research and developmental testing.

While most amateurs would undoubtedly desire to possess such instruments, the initial cost and the maintenance required by such complex equipment would, in most instance, be prohibitive. However, all is not lost. The ubiquitous kit manufacturers have made available, at very reasonable cost, a wide variety of laboratory type test equipment. These instruments, for the most part, are adequate for amateur, experimental and routine production work. They fill a definite requirement for better performance than the common service equipment and sell at a price most amateurs can afford. Examples are the Heathkit laboratory signal generator, wide band oscilloscope and ac voltmeter which perform the same functions as their service instrument counterparts, but with increased precision and accuracy. While their performance may not equal that of the best commercial laboratory equipment, it is fully adequate for most purposes. Rarely are laboratory instruments operated in such a manner as to obtain the accuracy of which they are capable and, if this accuracy is obtained, it is often meaningless since other variables may well be the limiting factors.

Another category of kit laboratory type instruments permits measurement of circuit paramaters and component characteristics not measurable with equipment designed for the service industry. Examples are the Heathkit impedance bridge and the laboratory Q-Meter. Once again, these instruments are fully adequate for routine experimental and production work.

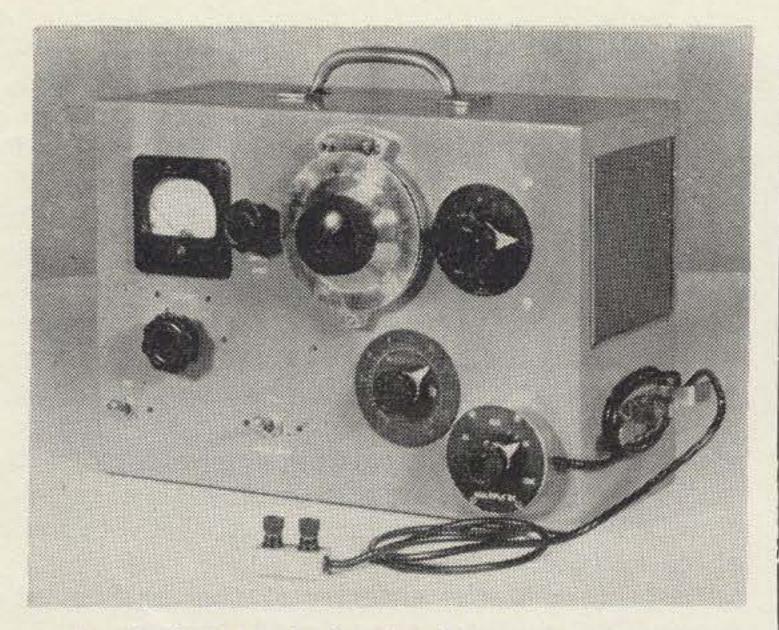were then developed to speed up these measurements. These instruments, using computer techniques, continuously and repetitively display the frequency of the signal being measured by means of read out indicators on the



Ferris 'Microvolter' signal generator, completely rebuilt. A spray lacquer finish and commercial decals restored the instruments appearance.


Simple circuitry, coupled with rugged mechanical design and precision components, resulted in equipment that was practically invulnerable to normal use and that would resist much actual abuse. Private industry, educational institutions and the Armed Forces are continually disposing of older precision test equipment and a wide variety is available to those who will search for it. Much of this equipment is in the hands of dealers and is often very reasonably priced. It is an interesting commentary on our present economy, but some of this used equipment is a bargain at the price it originally sold for many years ago.

Rather than wait for specific instrument requirements to arise, the amateur is advised to be continually on the lookout for the good buys and to purchase the more desirable equipment as it becomes available. It is axiomatic that the person buying to meet an immediate need will pay more than one who is able to wait and choose from the best as it filters into the market.

A few pointers are in order on the selection of instruments from those that may be found. Beware of paying undue attention to external appearance. Equipment being disposed of almost invariably suffers a period of neglect prior to disposition. Deterioration of the external surfaces is usually the first indication of this lack of care. Internal condition is of greater importance, since the instrument may be easily cleaned, polished and even painted if required. Of course if the equipment is working, try it out. Check operation, completeness and, if possible, calibration. Bear in mind, though, that an instrument displayed in working condition and inviting an operational check will usually demand a premium price.

The approach that has proved most feasible in the acquisition, rehabilitation and improvement of older laboratory test gear can best be illustrated by following through a specific ex-

-Swan SSB Transceiver-

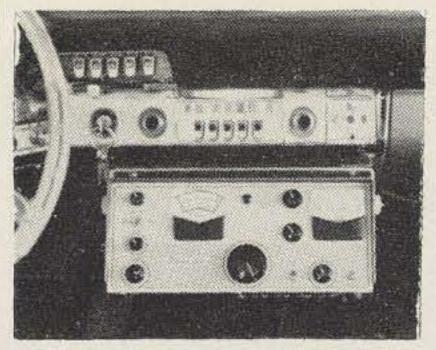

\$275

Net

One band 130-watt transceiver.

See our ad in January 73 or send for spec, sheet. Available for immediate shipment SW-120-140-175.

ELLIOTT ELECTRONICS, INC.

418 N. 4th Ave.,

Tucson, Arizona




SHIPSHAPE SHACK

No more screwing and unscrewing connections, no more dangling, sloppy leads when you have B&W multi-position coaxial switches.

Model 550A conveniently selects any one of five transmitters, antennas, exciters, receivers or other r-f equipment. Model 551A is a two-pole, two-position unit for switching equipment such as r-f power amplifiers in or out of a circuit. Both switches can be used with 52 or 75 ohm lines.

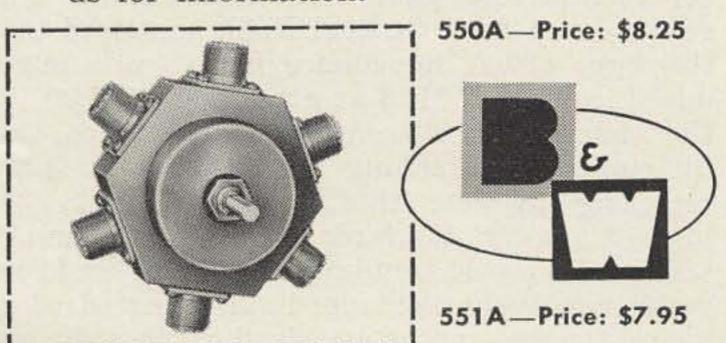See these efficient, reasonably-priced switches at your B&W dealer, or write us for information.



Barker & Williamson, Inc.

Canal Street & Beaver Dam Road Bristol, Pennsylvania



The renovated General Radio Type 650A Impedance Bridge with the fabricated null detector-indicator installed.

ample. The writer had the opportunity to purchase a General Radio Company Type 650-A Impedance Bridge in what appeared, at first glance, to be in very poor condition. Since the price was extremely reasonable and a genuine and immediate requirement existed for such an instrument, the transaction was completed.

The General Radio 650-A Impedance Bridge is powered by self contained batteries and uses an internal galvanometer as null detector for the dc resistance ranges. The ac functions of the bridge use an internal 1000 cycle tone source but requires the use of an external null detector. Ranges provided are as follows:

Function	Vo	ilue	Accuracy	
	Mini-	Maxi-	Maxi-	Mini-
	mum	mum	mum	mum
Resistance	.01 ohm	1 megohm	1%	2%
Capacitance .	1 uuf	100 uf	1%	2%
Inductance .	1 uh	100 h	2%	10%
Dissipation				
factor	.002	1	5%	20%
Storage fact.	.02	1,000	5%	20%

The photograph shows one model of this instrument. It is well built, with a 4" aluminum panel and is housed in a copper lined, mahogany case. The interior is typical General Radio quality, using solid bare wiring, large precision potentiometers and other components representative of laboratory instruments. Correspondance with General Radio disclosed that the Type 650-A Impedance Bridge was introduced in May of 1933 at a price of \$175.00. At the time of its discontinuance in 1959, this instrument was selling for \$285.00. It is interesting to note that, by building to the highest quality standards and by using simple, straightforward circuitry, this device could remain, relatively unchanged for a period of 26 years, the undisputed standard of the industry.

The Type 650-A Impedance Bridge was finally replaced by the Type 1650-A in 1959. with internal batteries, transistorized tone source, null amplifier-detector and indicator. While the new instrument claims greater operating convenience, increased range and improved accuracy, the March, 1959 issue of "The General Radio Experimenter" noted that the fundamentals of good instrumentation still apply: "While specialized and unusual circuits often have advantages for single-purpose bridges, no satisfactory replacements have been found for the simple, classical circuits in a general-purpose bridge. Their accuracy and simplicity are difficult to surpass for direct measurements of inductance, capacitance, storage factor, dissipation factor, and both dc and ac resistance."

Inspection of the exterior of the instrument seemed to confirm a reported history of 15 years hard service. The panel paint was chipped and the aluminum eroded, the case was damaged and the dials were unreadable because of corrosion and dirt. The interior of the bridge told a completely different story. The typical General Radio odor, compounded of high quality Bakelite and honest rosin flux, was noted when the case was opened and appearance was as good as new. Although the lubricant used on the switches and potentiometers had hardened, there was no visible mechanical damage of any kind and a hasty continuity check disclosed no defective components.


The necessary cabinetwork was accomplished first. The instrument panel was removed, hardware stripped from the case and the old finish removed with paint and varnish remover. The case was sanded smooth, a coat of sealer applied and lightly sanded, followed by two coats of clear lacquer which provided a finish indistinguishable from a factory job. The handle was given a flat black lacquer finish and was installed, using new screws. New rubber feet, screwed to the bottom of the case, completed the cabinet.

Next, all control dials, knobs and their associated hardware were removed and thoroughly cleaned in a solvent bath. Both the Bakelite and nickel plated surfaces were buffed to a high luster on a buffing wheel. Buffed coats of Simoniz restored this hardware to new condition. The instrument proper was then given the solvent treatment. Brushes and cloths were used to remove all traces of grease, dirt and corrosion from the panel and interior components. Extreme care was used to avoid damage to the fragile potentiometers and other parts. After the instrument was completely dry, contacts and moving parts were carefully lubricated with Vaseline.

The front panel now received attention. Corrosion was scraped from the panel where chipped paint had exposed the bare aluminum. Matching flat lacquer was carefully puddled into the resultant depressions in the wrinkle finish. After the lacquer was dry, two coats of This instrument is completely self contained, Simoniz, buffed to a high gloss finish, completed renovation of the front panel. The knobs, dials and other hardware were then installed.

The completed instrument was connected to a battery source and a pair of headphones. A few quick checks showed that the dc bridge was operating properly, although no ac measurements could be made. Tests disclosed that the microphone hummer, identified as 0-1 in Figure 1, was not oscillating. Adjustment of the microphone button linkage restored its operation to normal and the bridge functioned on the inductance and capacitance ranges.

There is nothing sacred in the approach described above. Actual work required will differ in each case and there are many methods that may be used. Common sense, lots of elbow grease and careful attention to detail will lead to good results. The writer was fortunate in the example cited as no component replacement was required. Such replacements, if necessary, usually pose no serious problem. Rugged simplicity is the keynote in design of such equipment and repairs, either electrical or mechanical, are not too difficult. The increasing availability, from local outlets, of precision components in a very wide range of values, greatly simplifies such repairs. The occasional special part that is required may generally be obtained from the manufacturer and, while prices on these components are high, the value of the end product usually justifies the expenditure.

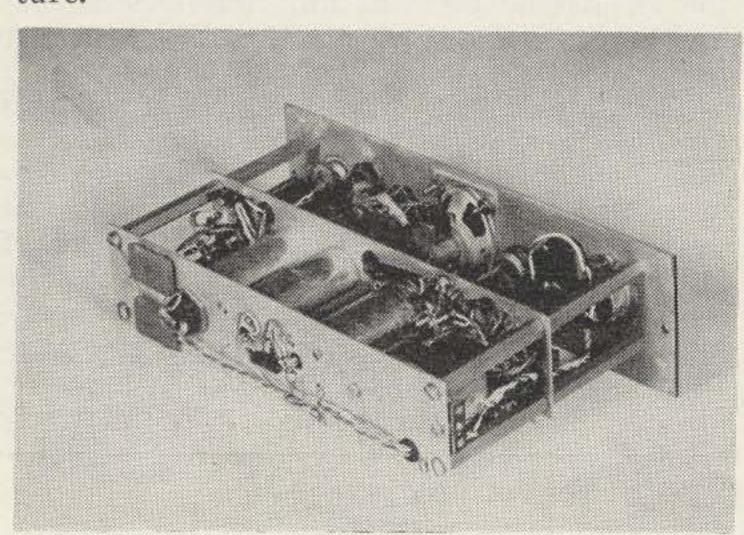

The impedance bridge power supply and amplifier-indicator unit. Note the extreme versatility of the 'post and plate' type of construction.

Once the equipment is restored to mechanical newness and the obvious electrical faults corrected, access to precision measurement instruments will permit adjustment of calibration circuits and verification of the over-all accuracy of the repaired device. All is not lost if you do not have the required instruments in your own shop. In todays diversified industry, it is not at all unusual to have a precision electronics laboratory just around the corner. Schools and other institutions also have precision measuring equipment which may be made available. Social contacts or a casual conversation at the local ham club will often

10-15-20M QUADS

*PRE- CUT *PRE-TUNED *TRIBAND

\$595 DEPT. C \$95
Bamboo EXTRA PARTS AVAILABLE

Skylane PRODUCTS 406 BON AIR DR

WRONG FREQUENCY?

Change crystal frequency with this crystal etching kit. This popular SAFE WAY kit supplies everything needed (even for the plated type), ammonium bi-fluoride, containers, holders and complete instructions. Shipped postpaid for \$1.00. De Lux model \$2.00. Guaranteed.

HAM KITS - Box 175s, Cranford, New Jersey

EXCLUSIVE.

Did you know Bob Graham deals enly in Amateur Radio Equipment? Did you know he has two stores handling only equipment such as Collins, National, Hallicrafters, Hammarlund, Gonset, Johnson, Central Electronics, Clegg, Globe, etc.? Did you know he services all types of ham gear as well as buys, trades, swaps, rents, and installs equipment? Did you know he has a large selection of reconditioned and guaranteed used gear? You didn't! Well now you do.

GRAHAM RADIO INC.
505 Main St., Reading, Mass. Tel. 944-4000
1105 No. Main St., Randolph, Mass. Tel. WO 3-5005

BOUND VOLUMES

We have spared no expense (to you) to provide the most beautiful library binding for Volume I of 73. Each Bound Volume is individually numbered and autographed by the editor. The binding is in bright red! Volume I consists of the fifteen issues from October 1960 through December 1961, plus the cumulative index for the period. This is about the only way of getting one of those elusive January 1961 issues of 73, which are now selling for as much as \$5 each when you can find Bound Volume I . . . \$15.00 red.

Bound Volume I . . . \$15.00 red.

BINDERS

Alright, stop writing. We now have binders available for the 1960-61 and 1962 issues of 73. The first binder has room for 15 issues, the second 12 issues. These binders are in bright red to match our balance sheet. Each is stamped in solid 14K gold with enough identification to eliminate any mystery as to what you have on your library shelves. Now that your issues of 73 are already dog-eared, here is a handy way to preserve them that way. Specify 1960-61 or 1962 binders. \$3.00 73 • 1379 E. 15th St. • Brooklyn 30, N. Y.

TONS OF AMATEUR EQUIPMENT IN STOCK

WIESTIEIRN RAIDIO

1331 India Street


BE 9-0361

MON - FRI 8:30 to 8:00

SAT 8:30 to 5:00

1961-1962 AMATEUR RADIO YEARBOOK

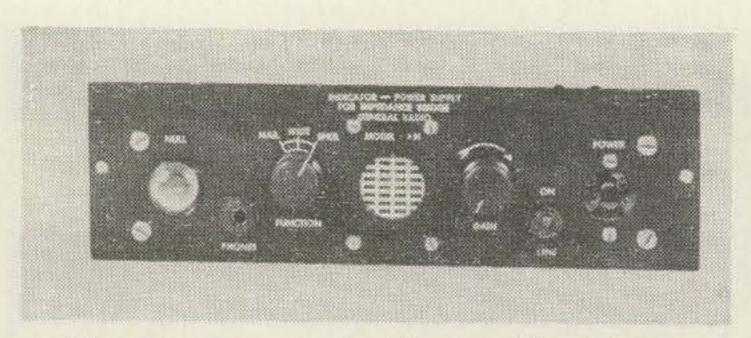This International Yearbook is published in England and regularly sells for 75¢. We have a few on hand for only 50¢, while they last. This lists ARRL countries, QSL bureaus, Propagation conditions world-wide, and all sorts of other data.



The appearance of this amplifier-indicator assembly, ready for installation in the General Radio Type 650 Impedance Bridge, is enhanced by the use of commercial decals.

produce the required equipment.

Calibration of reconditioned equipment is not as difficult as would be expected. The calibration of most instruments can be restored to normal by calibrating at a single reference point for each range of the equipment. An example of this line of thinking may be cited by assuming a laboratory signal generator for which the accuracy of the calibrated output level is questioned. A resistance check shows that the step and variable attenuator resistors are near their proper values. Setting the calibration adjustment to produce a measured output voltage equal to that indicated by the attenuators, on a single frequency and at a single output level, will probably hold good for all frequencies and all output levels within the range of the instrument.

While the results that can be obtained with the older instruments have been covered, minor modifications and additional features can greatly enhance the value of such equipment. The General Radio Type 650-A Impedance Bridge provides a good example of this. While this instrument had been restored to its original condition, it still left something to be desired in operating convenience. Use of the internal batteries was expensive and presented a recurring maintenance problem. Headphones, used as the null detector, were awkward and were relatively insensitive.

The panel access battery compartment, measuring 6%" x 2¾" x 10%", provides sufficient room to install a low voltage dc bridge supply, selective audio amplifier, null indicator, loudspeaker and power supply. The photographs show assembly details of the added unit and its installation in the renovated bridge. The "post and plate" method of construction shown is ideally suited to modification work where available space may prohibit use of the conventional chassis and panel approach. This added assembly is shown as an example of a successful approach to instrument modification and the convenience of the self contained null detector and indicator more than justifies the cost and effort.

Basically, the circuit consists of one half of a 12AT7 as an input amplifier, followed by the other section of this tube as a phase-shift, selective feedback amplifier. Standard tolerance components are used to roughly

tune the phase shift network to the bridge oscillator frequency and feedback is set just short of oscillation by selection of resistor "R". This stage is coupled to a 6E5 indicator tube for visual indication of bridge balance and to a 6C4 amplifier stage which feeds a small PM speaker.

Other categories of instruments may require different approaches to their repair and modernization. The end result of another renovation project is shown is the photographs. The signal generator is one of the family of "Microvolter" HF and VHF laboratory generators manufactured by the Ferris Instrument Corporation of Boonton, New Jersey. These instruments were used in great quantities during the last war and are widely available on the surplus market. The case and panel of this particular unit was in poor condition and complete refinishing was required. A spray lacquer finish and the use of commercial marking decals gave the instrument a "good as new" appearance. The rf section of the generator was in very good condition and the only work required was replacement of the output cable and cleaning of the band change turret and attenuator contacts. The power supply chassis was another story since all capacitors required replacement. Surplus, oil filled units were installed in the line filter assembly. New wiring was installed between the sub-assemblies. The unit was checked out and performance found equal to that of a new instrument.

This article has described the advantages that can accrue from the use of kit instruments and older, precision test equipment. It has further demonstrated how a laboratory may be assembled on a limited budget. Application of the techniques outlined herein should result in a high degree of success; broaden the experience and increase the capability of any amateur who enters into this field of endeavor.


. . . Pafenberg

Letter

Dear Wayne,

The transistor mike preamp (p. 10, November 73) was rather interesting. Naturally I put one together to use with my Gonset II. I cut the distortion from 2.8% to about half of that by making a few small changes in the circuit, as follows:

LeVaughn Shipley K6CFF

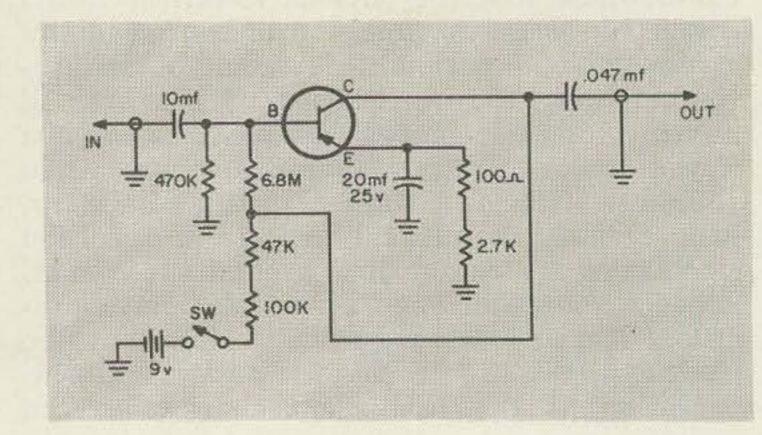


(Finland from page 19)

due to the fact that they must have certain number of CW contacts before they are allowed to pass the General Class examination.

SRAL Board consists of the President plus nine members. SRAL Bureau has a regular personnel of one man (OH2XK) in full-day work, and the Secretary, Magazine Editor, Treasurer etc. just take their share of the activities in their 'leisure times.' Both in- and outgoing QSL cards are handled free of charge at SRAL QSL Bureau, all costs are covered by the annual membership fees. No economical help is received from outside. The annual budget is of a class of approximately \$12,500 US, the membership fee being 2000 mk (\$6) per year. The license itself, being valid for five years, costs 1100 mk (\$3.40). In this connection it may be of interest to mention that in Finland every licensed amateur must be member of SRAL. This is a regulation of the Finnish 'FCC' (Post and Telegraph Ministry) and probably due to the control system.

Every day you may hear an OH on the air. Listen to the low end on 7 mc, or to the high end of 14 mc, always OH stations welcome calls from you. Don't ask us to teach you Finnish; it may be a bit difficult to you. Anyway, if you seriously want it, let's start right now: Here are a few words which you may use on the bands to surprise your Finnish friends. Hi! terve!, Cheerio! = hei!, cuagn = nakemiin (a = . - . - . -), thanks = kiitos, many thanks = kiitoksia, and finally, when you take a drink and try to say "Prosit!", or "Rendez vous" or something like that, you can as well try to say it in pure Finnish: "hölökykölôkyn!", but you must have something really strong in your glass then, hi. Just a declaration about a and ö letters: a, or "a with two dots" is pronounced like 'a' in the word 'mad', and ö like 'o' in the word 'work'. On CW they are as follows: a = .-.-, ö = -

Hölökynkölökyn! 73! . . . OH2YV

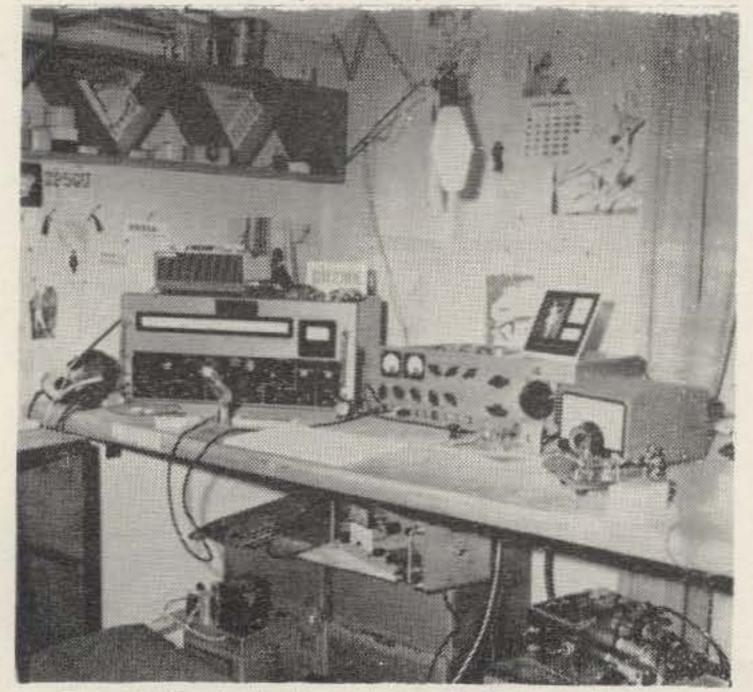

One of the typical experimenter's ham stations. OH2MK shack is in the attic.



All 22 Frequencies in Stock CLASS "D"

3rd overtone. .005% tolerance—to meet all F C C requirements. Hermetically sealed HC6/U holders. " pin spacing-.050 pins (.093 pins available, add 15¢ per crystal).

The following Class "D" Citizen Band frequencies in stock (frequencies listed in megacycles): 26.965, 26.975, 26.985, 27.005, 27.015, 27.025, 27.035, 27.055, 27.065, 27.075, 27.085, 27.105, 27.115, 27.125, 27.135, 27.155, 27.165, 27.175, 27.185, 27.205, 27.215, 27.225.

Matched crystal sets for all CB units. . . \$5.90 per set. Specify equipment make and model numbers

RADIO CONTROL CRYSTALS IN HC6/U HOLDERS

Specify frequency, 1/2" pin spacing . . . pin diameter .05 (.093 pin diameter, add 15¢).....\$2.95 ea.

FUNDAMENTAL FREQ. SEALED CRYSTALS

in HC6/ holders From 1400 KC to 2000 KC .005% Tolernce.....\$4.95 ea. From 2000 KC to 10,000 KC any frequency .005% Tolerance\$3.50 ea.

SEALED OVERTONE CRYSTALS

Supplied in metal HC6/U holders Pin spacing .486, diameter .050 15 to 30 MC .005 Tolerance...... 45 to 60 MC .005 Tolerance \$4.50 ea.



QUARTZ CRYSTALS FOR EVERY SERVICE

All crystals made from Grade "A" imported quartz-ground and etched to exact frequencies. Unconditionally guaranteed! Supplied in:

FT-243 holders Pin spacing 1/2" Pin diameter .093

MC-7 holders Pin spacing %" Pin diameter .125

CRIA/AR holders Pin spacing 1/2" Pin diameter .125

FT-171 holders Pin spacing %" Banana pins

MADE TO ORDER CRYSTALS . Specify holder wanted 1001 KC to 2600 KC:

..\$4.50 ea. .005% tolerance.... 2601 KC to 9000 KC:\$2.50 ea. .005% tolerance.... 9001 KC to 11.000 KC\$3.00 ea, 005% tolerance....

Amateur, Novice, Technician Band Crystals

.01% Tolerance . . \$1.50 ea. -80 meters (3701-3749 KC), 40 meters (7152-7198 KC), 15 meters (7034-7082 KC), 6 meters (8335-8650 KC) within 1 KC FT-241 Lattice Crystals in all frequencies from 370 KC to 540 KC (all except 455 KC and 500 KC)........................50¢ ea. Pin spacing 1/2" Pin diameter .093 Matched pairs + 15 cycles \$2.50 per pair

200 KC Crystals, \$2.00 ea.; 455 KC Crystals, \$1.25 ea.; 500 KC Crystals, \$1.50 ea.; 100 KC Frequency Standard Crystals in HC6/U holders \$4.50 ea.; Socket for FT-243 crystal 15¢ ea.; Dual socket for FT-243 crystals, 15¢ ea.; Sockets for MC-7 and FT-171 crystals 25¢ ea.; Ceramic socket for HC6/U crystals 20 cea.

Write for new free catalog #961 complete with oscillator circuits

ASK YOUR PARTS DEALER FOR TEXAS CRYSTALS See big red display . . . if he doesn't stock them, send us his name and order direct from our Florida factory.

NOW! Engineering samples and small quantities for prototypes now made either at Chicago or Ft. Myers Plant. 24 Hour Service!

IN CHICAGO, PHONE GLadstone 3-3555

RUSH YOUR ORDER TO OUR NEW PLANT Use coupon below for 1st Class shipment.

TEXAS CRYSTALS

Dept. G-42, 1000 CRYSTAL DRIVE, FORT MYERS, FLA. For extra fast service, Phone WE 6-2100

ATTACH THIS COUPON TO YOUR ORDER FOR SHIPMENT VIA 1ST CLASS MAIL AT NO EXTRA COST

TERMS: All items subject to prior sale and change of price without notice. All crystal orders must be accompanied by check, cash or M.O. with PAYMENT IN FULL. G-42.

W2SKE/MM [Mobile Motel]

Bill Leonard W2SKE

A DDING it up the other day, W2SKE's total operating time in the past two years came to just about 500 hours. But of this total, less than 200 took place from the home QTH. The rest involved temporary locations—more than 20 of them scattered across a dozen states and half a dozen countries. These temporary set-ups provided more fun and more memories than conventional hamming, perhaps because they offered something of a challenge. They meant not only operating, but 'getting on the air', as well. And as every ham knows, getting on the air is usually more fun than being on the air.

W2SKE operated from a hotel in the Chicago loop, from another in the Dominican Republic, from a fishing camp in Canada, summer homes in Long Island and New York State — but most often of all from motels. Motels of all sorts and descriptions and price ranges, motels perched on hills in the quiet country that might have been designed with ham radio in mind, motels dominated by traffic and noisemaking neon signs, motels in Miami and Tallahassee, San Juan and San Isidro, Des Moines and Dubuque, Hanover, New Hampshire and Avon, Connecticut, Boston and Los Angeles. The DX score from these one-or two-or three-night stands runs to something like 50 countries on 10, 15, 20, 40 and 80 SSB, in all countries. But much more important is the fact that with an absolute minimum of fuss and feathers one was able to stay 'in touch' with the gang or the family. A ham who travels as part of his job, or a ham who travels for vacation fun usually has more time for hamming 'away' than 'at home.' That's why motel mobile has meant so much to me. The trick is to make it-no pain, no strain. Here's how.

The requirements for 'motel mobile,' or any type of 'quickie portable' operation are (1) equipment that is small, light, easily packed,

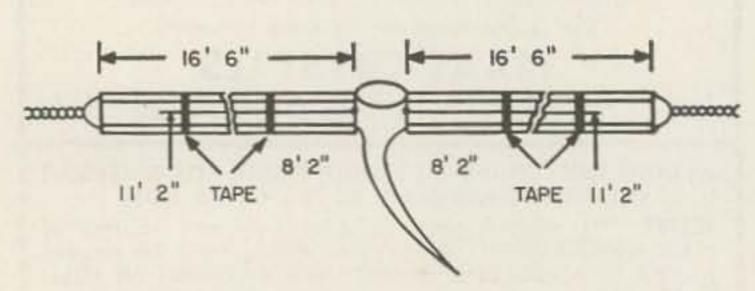


Fig. 2. The quickie triband doublet.

rugged and reliable, (2) an antenna system and equipment that combine to provide a station that will 'get out good' (it's just no fun to get on the air with flea power and talk only to flares), and (3) the station that is easy to put up and take down (a half hour or so to get going, and as much to pack up is all the effort a one-day stand is worth, but proportionately more effort can go into a vacation set-up).

In these days of SSB and miniaturization none of the above is difficult. The author is fortunate in having a Collins KWM'-2 as his basic piece of equipment. Though this hunk of gear goes a long way in fulfilling the requirements above, it is by no means essential to 'quickie portable' operation. What is essential is a transceiver—or rather, a station that's all of a piece, one hunk of gear. No matter how compact the equipment, the process of hooking up a receiver and transmitter after lugging them around in at least two packages makes the whole operation more trouble than it's worth. The real secret in 'motel mobile' is that it not be 'more trouble than it's worth.'

So if you're building, build a transceiver, or a transmitter in a receiver cabinet. If you're buying, buy a transceiver.

Weight? If you do your travelling by car, weight's not the factor it is if your motel, hotel or camp is at the end of a plane trip. But, obviously it's just no fun lugging a couple of hundred pounds of gear in and out of a car. Besides, it clutters up that motel room. A fifty pound limit for everything, including spares, mike, antennas, etc., is practical.

Assuming then you have fifty or fewer pounds of dynamite. Assume you can unpack it and plug it in the wall within five or ten minutes. The only problem then is the skywire. And here's where experience pays off. The veteran motel mobiler knows that no two motels, like no two women, are exactly alike. He may or may not be able to drive around looking for the Ham's Paradise Motel (TV, Free Baby Sitter, Coax Outlet to 3 element beam in every room). Chances are he'll arrive in the gathering dusk by car, or taxi from the airport, and have about twenty minutes to case the joint and rig a skywire before the XYL and darkness descend. He must, therefore, be prepared! I always carry the following (in addition to a small, basic tool kit):

A 500 foot spool of wire (#20 or 22

enamel or bare copper).

A pre-fabbed 20-meter dipole, with small egg insulator at the ends, a small egg insulator in the middle, and 50-100 feet of RG58 U attached.

A small L-match unit (see later text).

A pocket compass.

4 small insulators.

1 roll of electrical tape.

50 feet of thin nylon rope or clothesline. This combination is guaranteeed to get you on the air on at least 20 meters, and probably on all bands in very short order from any motel and from practically any resort hotel. For a mid-city hotel I have used the Mosley Tote-tenna with very good results.

Anyway, let's assume you arrive at Paradise Motel. Rule #1 is— case the QTH before asking for your room. Behind almost every motel there's a field. At the far end of almost every field there's a tree, a fence, or at least a bush. Try to get a room facing the field (second story if it's a two story motel). Visualize a long wire streaming from this room to that 'hook.' There may be several rooms in a row that 'qualify.' Ask for one of them. If there's no field or wide open space, chances are almost 100% there'll be a light stanchion, or telephone pole nearby. Get a room with clear line of sight to one or more of these supports.

What you have in mind—and what you'll be able to rig in almost no time in almost all motel QTHs is a thin, random length wire stretched as far as possible, preferably in a favored direction. Any wire 110 or more feet long at any height will, when matched, work on any and all bands from 10 to 80. The longer the better and the easier to match. Also—the longer the more directional, and the higher the band the more the wire will tend to fire off the ends of the wire.

The important thing—forget about pruning, measuring, or getting a 'resonant' hunk of wire. Practical considerations come first-run it out 'thataway' and let it go at that. Don't be upset if your hunk of wire averages only 6 feet off the ground. Just get it as high as you can. Use the hunk of clothesline or nylon line to help you get over the top of a tree limb. Hook the near (or motel) end to a nail, balcony or what have you near your room (through an insulator, of course). Run the lead-in through door or window sash into the motel room. Wrap the section of wire that passes close to the window or door jamb with plastic tape.

A few motels do not come equipped with built-in fields or woods. In that case forget about everything but 20 meters. String your readi-built dipole between two light stanchions, two palm trees, two balconies, or two blondes.

One other trick some of the motel mobile gang uses. Even those who don't go to the trouble of putting a mobile in their car will

GENERALIZE YOURSELF!

LEARN RADIO CODE

The EASY WAY

REVOLUTIONARY WORD METHOD RADIO CODE PRICE \$9.95

No Books To Read-No Visual Gimmicks To Distract You. Just listen and learn

Based on modern psychological techniques - This course will take you beyond 13 w.p.m. In

LESS THAN 1/2 THE TIME Available also on magnetic tape See Your Dealer Now!

Album Contains EPSILON 21/2 Hr. Instruction

2769 CAROLINA RECORDS REDWOOD CITY, CALIF.

- 2 METER CONVERTER, Xtal controlled, 4 db noise figure, 5 low noise VHF transistors. Requires 15 ma @ 11-15 VDC. Complete with instructions, \$ 49.95
- 6 METER CONVERTER, Xtal controlled, 4 db noise figure, 4 low noise VHF transistors. Requires 13 ma @ II-15 VDC. Complete with instructions, \$ 44.95
- 2 METER PREAMPLIFIER, 4 db noise figure, 21 db gain, only 1 x 2-3/8 inches for easy installation. Requires 2.5 ma @ 11-15 VDC. Complete with instructions, \$ 12.95

JAMDN OED 00 0 OED OED OED 0000

PINECASTLE, FLORIDA P. O. BOX 13158


ESL NUVISTOR PREAMP

Hi Gain 20 db Lo Power Drain Lo Noise Figure

Models for 220 mc, 144-160 me, 50-54 me, and 27-30 mc

Wired and tested \$8.95 prepaid Kit Form

\$5.95 prepaid

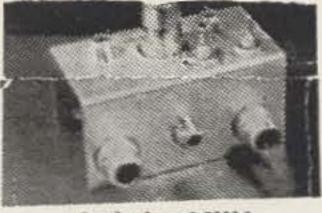

Includes 6CW4 Includes 6D54 2" x 15/8" x 15/8"

All nuvistor converters tailored for your use \$56.95 with power supply; \$45.95 without power supply, prepaid. Inquiries invited.

Electronic Specialists Laboratories 301 S. Ayer St. Harvard, Illinois

DOW-KEY CONNECTORS PANEL MOUNT

Durable, silver plated, precision made. Only 58" hole is needed. no screws.

ea. 70

DOUBLE MALE Favorite everywhere. Precision made, rugged locking type. Silver plated.

ea. . . . 1.25



DOW-KEY COMPANY, Thief River Falls, Minn.

DX-100 OWNERS

Increase power by 50%.

Run 240 watts AM-300 watts CW or SSB. Complete kit and instructions for adding another 6146 to final only \$19.95. Similar kit for TX-1. Order or write. W4KUV-W4NZS.

BEST RADIO SERVICE

610 N. Madison

Goldsboro, N. C.


install a ham antenna on the family buggy. Then, when sack-down time comes, they simply run coax to the car antenna and away they go.

The random length of long wire across the open field is best. On the higher frequencies it exhibits real gain in favored directions. A length between 180 and 270 feet is ideal.

Some sort of simple coupler-matching device is almost always necessary in feeding this long wire into a pi-network final. It's probably a mistake to call this device an antenna tuner—it's simply an L-network for matching the relatively high impedance of the end-fed antenna down to the 52 ohm pi final. If all hams used long wires, pi networks could simply be designed to accommodate higher impedance ranges.

I have always used the Globematcher Jr. AT-3, a tiny little package with a neon bulb loading indicator and two controls. Proper loading on the final, coupled with maximum soup in the neon bulb indicates proper tuning.

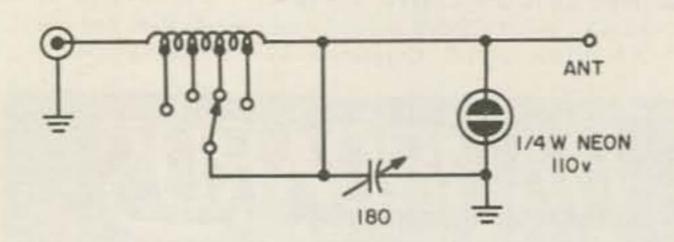If you want to build your own, the matcher looks like this:



The coil is a one inch diameter Miniductor, 25 turns with 5 taps at 2, 5, 10, 20 and 25 turns.

One other antenna has been used with success when operation above 20 meters was not desired. It is for use at locations where a long wire is not practicable. This is about the simplest tri-bander we know of. Take a 33 foot piece of twin lead, tie the ends together and attach two small insulators. Cut the twin lead wires at the center, insert insulators, and attach RG-58/U. Cut one wire 8 ft. 2 inches each side of center and pull off enough of the *outer* wire to reach up the half inch or so to the *top* wire, to which it is fastened.

Just one more step. Cut two 11 ft. 2 inch sections of insulated bell wire and lay them along the middle of the twin lead, soldering to the coax at the center, and securing them along the length of the twin lead every 18 inches or less with electrical tape. Reinforce the center section.

A low swr is obtainable on 10, 15 and 20 this way. Build and prune and tune before you set it out.

In summary . . . modern motels and modern ham radio make it possible to get on the air fast and effectively, and get off the air and ready to move on while the XYL is packing the unimportant things, like clothes.

... W2SKE

POSITION OPEN

Many people spend all of their lifetimes not working for ham radio magazines. This is a terrible waste. If our country is to really prosper we have to cut waste to the bone and trim the fat. Help America to prosper, work for a ham magazine. Perhaps you are worried that you do not have the proper qualifications to apply for such a position. Please check the following application blank and send it in immediately, together with the customary

\$3.50 job application processing fee. Your duties as a staff worker on the magazine will be to read each issue carefully, ignoring the gross technical mistakes that abound and to talk as many friends as possible into subscribing. A certain amount of time should be spent inducing advertisers to make more use of the 73 pages. Should these duties seem a bit harsh, we have a few supervisory positions open; however, the application fee for these is \$6.50.

name	call	name	call
address (QTH)		address (QTH)	
city	zone state	city	zone state
☐ \$3.50 one year	☐ \$40 LIFE	\$3.50 one year	□ \$40 LIFE
☐ \$6.50 two years	Renewal (I think)	☐ \$6.50 two years	Renewal (I think)
☐ \$9.00 three years	☐ New subscription (I think)	☐ \$9.00 three years	☐ New subscription (I think)
Start with: current issue	next issue 🗌	Start with: current issue	next issue
123 les	1370 FACT IEIL CENTER		

13 Magazine BROOKLYN 30, N. Y. 1 13 Magazine

80

BROOKLYN 30, N. Y.

73 Builds

and Tests the


Heathkit IM-10 VTVM


H EATH'S new VTVM, though not strictly a piece of ham gear, none-the-less is equipment that no ham should be without. It's almost impossible to check out or repair a piece of gear without a good, reliable, VTVM.

The IM-10 has a number of features over its predecessor, the V7A. One of the most important, is the new 6" meter which really spreads out the scales. To make its use even more convenient, the scales are color coded. Zero and Ohms adjusts are thumb adjustments instead of knobs. Two new low ac scales have

been added for more accurate measurement of low ac voltages. No printed circuit board is used in the IM-10, as it is in the V7A. 1% precision resistors are used as multipliers and the 6", 200 microampere meter has a full scale accuracy of 2%.

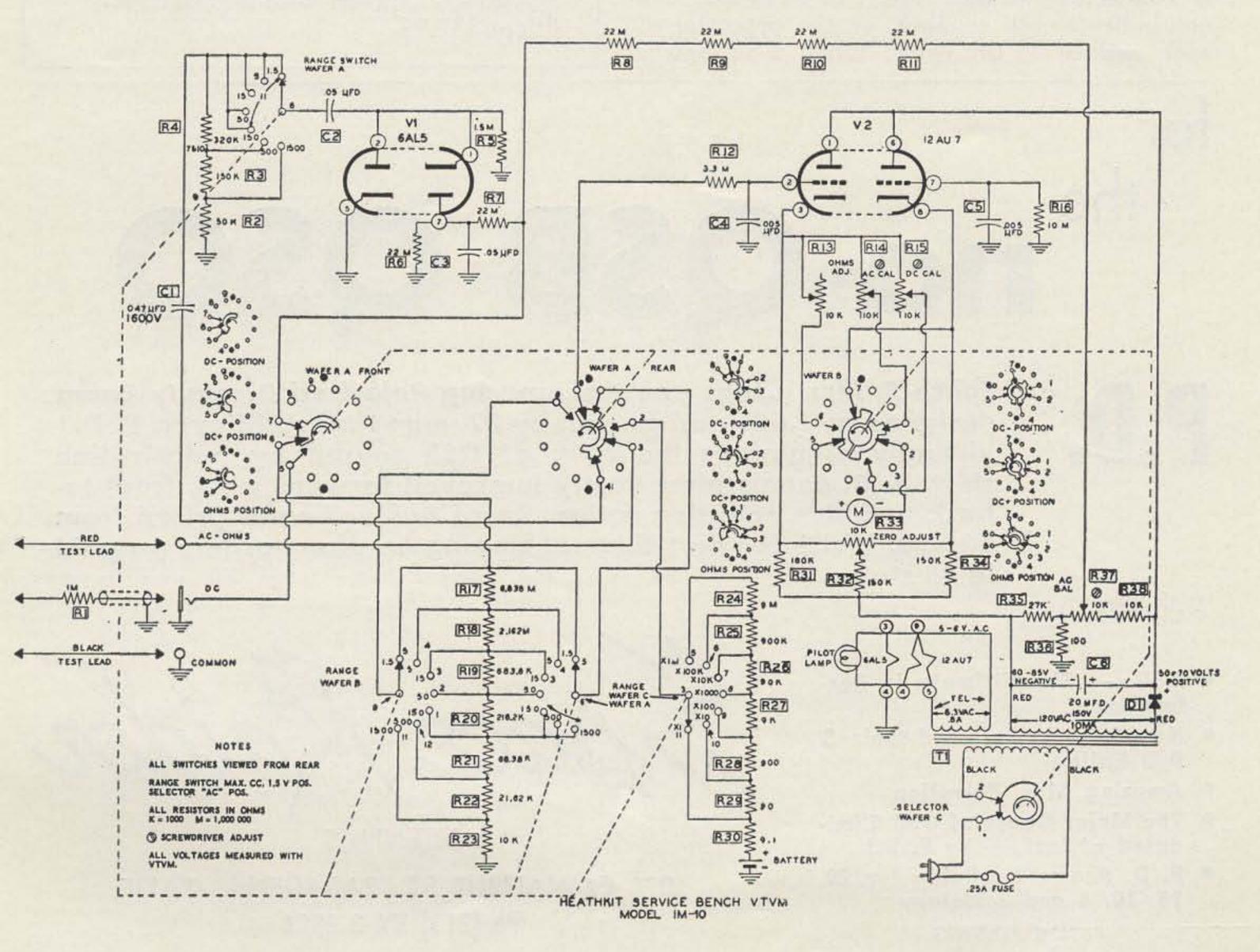A dual triode, 12AU7 tube is used in a balanced-bridge circuit, with the meter reading any imbalance. With no voltage input to the 12AU7, as would be the case when not actually measuring a voltage, each section of the tube will draw the same current. The meter, which



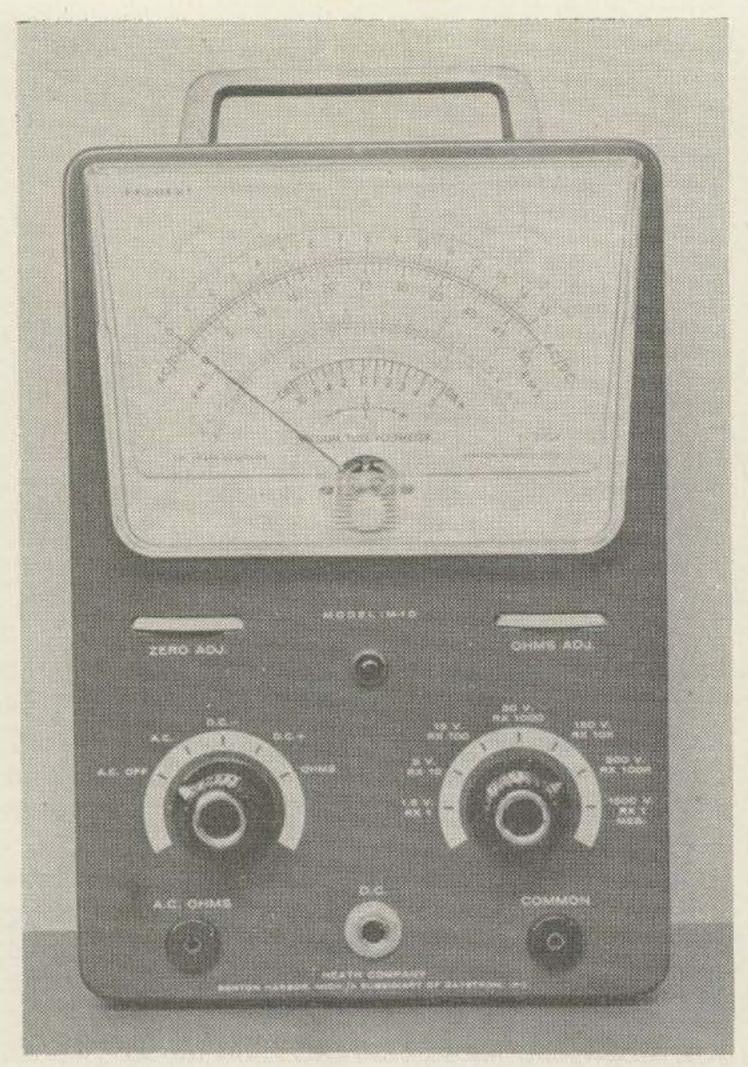

is connected between the two cathodes, can not indicate any reading, as the potential of each cathode is the same. When a voltage is applied to one of triodes, one half of the tube will draw more current than the other, causing a difference of potential to exist between the two cathodes. In this case, current will flow through the meter because of this difference in potential or unbalance and the needle will indicate the amount of voltage in the circuit being measured. A zero adjust control is pro-

Heathkit VTVM...IM-10

Weight: 5 lbs

Size: 61/2" x 91/2" x 5" deep Power: 105-125 vac 50/60 cy Ohmmeter Battery: 1.5 v "C"

DC Ranges: 1.5, 5, 15, 50, 150, 500,

1500

AC Ranges: Same as DC

Ohmmeter: 1000 ohms (10 ohms center

scale)

Multiplier: X10, X100, XIK, X10K,

XIOOK, XIM

Construction Time: 7 hours

DC Input Impedance: | | megohms

AC Input Impedance: 320K

Accuracy: 3% on DC: 5% on AC

Price: \$32.95

for

the

no-QSB Q50

PD
**
Space Raider brings you the amazing Polarized Diversity Beam designed by K6CT and proven by DX men the world over. P. D.* virtually eliminates the 80% of QSB caused by polarization shift. P. D. Beams offer vastly improved forward gain, front-to-back and side rejection ratios. Space Raider beams priced from \$44.50. Write for particulars. Shipping on direct orders prepaid in 48 states.

*Polarized Diversity


- P. D. The Ultimate in Performance
- New High in Forward Gain &
 F/B Ratio
- Amazing Side Rejection
- The Major Cause of QSB Eliminated at last by P. D.!
- P. D. Beams Available for 20,
 15, 10, 6 and 2 Meters

PATENT PENDING



ANTENNAS

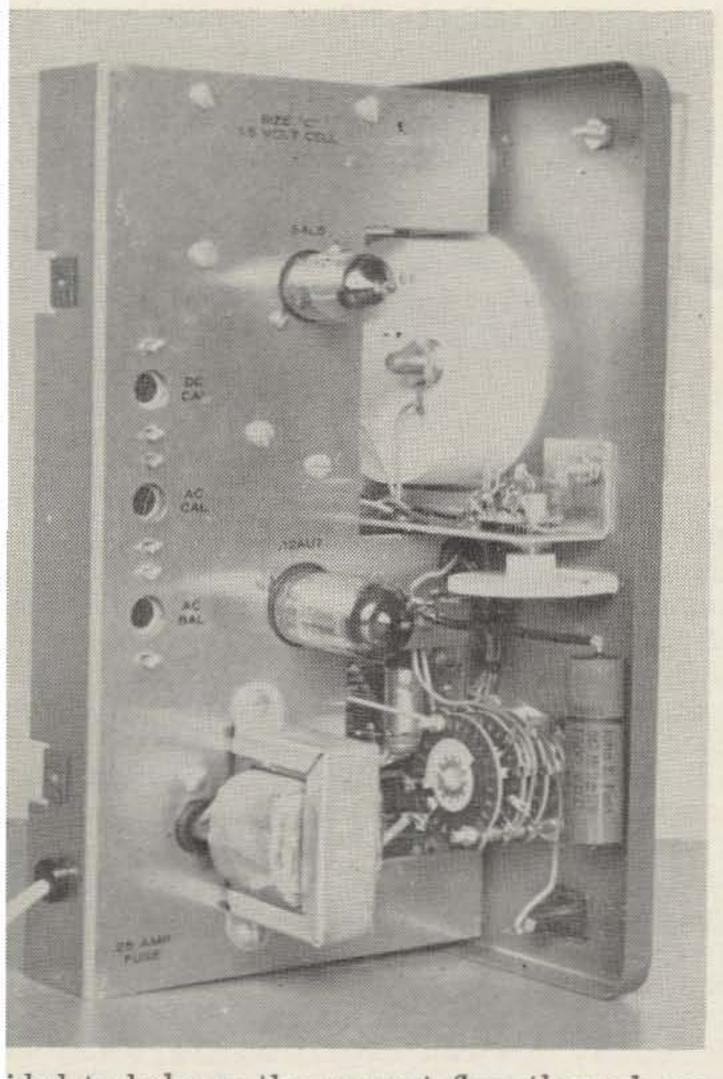1076 E. WALNUT ST., PASADENA, CALIF. Ph (213) SY 2-2526



alf of the tube (no voltage being measured), o that both triode currents will be the same. Of course not all voltages between zero and 500 volts can be applied to the grid of one f the triodes, so multiplier resistors are used extend the basic voltage range up to 1500 olts. These multiplier resistors are 1% precision resistors, as any inaccuracy in these reistors would be reflected in the voltage read in the meter and hence affect the over-all acuracy of the instrument.


On ac, operation is basically the same, exept that a 6AL5 is used in a half-wave oltage doubler circuit and ac to be measured connected to it. When the ac voltage being leasured is greater than 150 vac, multiplier esistors are switched in (by the range selector witch), to keep the input to the 6AL5 with-in as rating. The output (dc) of the 6AL5 is roportional to the applied ac voltage and is connected by the function switch to the dc nultiplier section. Here the voltage is handled the same manner as when the instrument is eing used on dc.


The electronic Ohmmeter section of the TVM uses a 1.5 volt battery connected in eries with multiplier resistors as well as the esistance to be measured. How much battery oltage fed to the 12AU7 tube depends on he ratio between the resistance to be measured and the multiplier resistance of the ohmmeter section. Though the ohmmeter section oes have a battery, the instrument must still e connected to the ac line and turned on, so

NEW LOW PRICE: \$14.95 BUYS 2-METER RECEIVER & 2/6/10 METER XMTR

SCR-522 rcvr, xmtr, rack & case, exc. cond. 19 tubes include 832A's. 100-156 mc AM. Satisfaction grtd. Sold at less than the tube cost in surplus! Shpg wt 85 lbs. FOB Bremerton, Wash. \$14.95

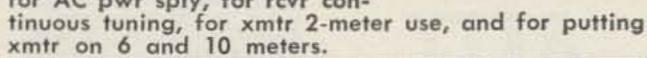Add \$3.00 for complete technical data group including original schematics & parts lists, I.F., xtl formulas, instruct. for AC pwr sply, for revr con-



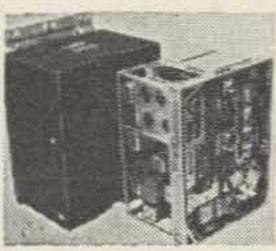

with these Navy cameras CRV-59AAC W/sync unit Block 1 C-T, as removed from operating Navy Aircraft, with ALL the tubes (all!) plus the VHF xmtr for it, same condition, T-61/AXT-2, plus schematics/ conversion instr. to home TV syncs, fob Los Ang.\$149.50

POPULAR Q-5'ER

QX-535 RECEIVER

See p. 66 Dec. 73 or write us for reprint. This is the BC-453-B in handsome case with xfrmr-type pwr sply, speaker, all controls, phone jack, \$37.50 ready to plug in and use......

NAVY'S PRIDE RECEIVER

RBS: 2 to 20 mc 14-tube superhet has voice filter for low noise, ear-saver AGC, etc. Strictly for communications! Very hot! I.F. 1255 kc. Checked, aligned, w/power supply, cords, schematic, instructions, fob Charleston S.C. or Los Angeles, Calif. \$99.50

ALL-BAND RECEIVER

R-45/ARR-7: 0.55 to 43 mc A1, A2, A3. Unused Air Force surplus, cost Gov't \$750.001 Includes our own 60 cy pwr sply for htrs, B+, and the DC for the rcvr's automatic tuning motor. This rcvr has everything! Xtl IF filter, 6 selectivities, BFO, S-Meter, AF/ RF Gain, Noise Limit., etc. Sharp and Hot! Best buy today for DX. IF is 455 kc, ideal for double conversion with either BC-453 or QX-535 described above. Before shipping, we have a painstaking Communications radioman inspect each unit thoroughly, check it, align it, bypass reradiation suppressor, improve ant. impedance match and hang his OK tag on it. W/schematic, align, data, etc. absolutely ready to plug in and use . . . nothing else \$179.50 to do. FOB San Antonio, Texas..... Time Pay Plan: \$17.95 down, 11 mos at \$16.03

RCVR/SPECTRUM ANALYZER

AN/APR-4 rcvr is 11-tube superhet as I.F., S-meter, etc. for the 30 mc output of the tuning \$69.50 units. Aligned, OK, fob Los Angeles... \$69.50 TN-16, 17, 18 tune 38-1000 mc; checked \$85.00 OK; the set of 3......\$59.50

LM FREQUENCY METER

Crystal-calibrated every 1000 kc w/data to use many minor xtl checks in between. Xtl is .005% or better. 125-20,000 kc w/usable harmonics far beyond. W/matching-serial calib book, xtl, schematic, pwrsply data, CHECKED OK FOB Los \$49.50 Angeles

AC PWR SUPPLY for TBX & LM

EAO is TBX-rcvr sply, 115 v 60 cy, furnishes all voltages. Very neat. New, w/spares, plug, schem. dwgs, and conv. to standard pwr sply, fob San Diego \$8.95 Add \$1.00 for extra parts needed for an LM supply, plus the revised schematic for the LM use.

TIME PAY PLAN available for any purchase over \$150.00 total.

R. E. GOODHEART CO.
BOX 1220-GC BEVERLY HILLS, CALIL



GOV'T SURPLUS BARGAINS:

Transmitters, Receivers, Meters, Microphones, Headsets, Amplifiers, Antennas, Power Supplies, Filters, Indicators, Converters, Dynamotors, Cable, Control Boxes, Test Equipment,

Phones, etc. Send for Free Catalog. Dept. 73.

FAIR RADIO SALES . P.O. Box 1105 . LIMA, OHIO

RTTY Handbook



" by Fiel Davine treatme.

Since we have a new RTTY Handbook in preparation it is only natural that I should have quite an interest in the recent RTTY book put out by CQ and written by Byron Kretzman. I have to admit that they have done a nice job of publication . . . good paper, nice type. I am somewhat disappointed in the content. A great deal of the book seems to be lifted bodily out of the book that Byron and I put together back in 1956. Many of the photographs are the very ones that I took with my old Pony Premo #5 camera and several of the diagrams are the same ones that I originally drafted for my column in CQ back in 1952. It is nostalgic to read all of my own words again, lifted out of the old RTTY columns of eight to ten years ago. Though I have been relatively inactive in RTTY since becoming an editor, it is nice to know that I am still considered the authority for the field. Ha.

Work on our handbook has taken a lot longer than Byron's modified reprint of my old book. I've been out there with my new Rolli taking pictures of all my old and new TT gear. It is quite a job rounding up information on all the newer equipment and publishing an upto-date handbook. I think you'll like the result. It has none of that text-bookish approach. It tells you the facts about what gear is best and what to stay away from. It tells you where to get the equipment. It tells you how to hook it up and how to use it. There are several types of converters, some with complete construction details. There are instructions on frequency shifting most commercial rigs. This is a practical book. Though the book was largely assembled by Fred DeMotte W4RWM, you'll find my light touch everywhere you look. Y'all better send in your order right now. Hear? \$3, not \$3.95.

. . . wayne


that supply voltage will be available to the 12AU7 tube.

Filament and B+ voltages are provided by an AC power supply and selenium-rectifier. A ¼ amp fuse is placed in the primary of the power transformer to protect the instrument. Calibration controls consist of AC balance, Ohms adjust, AC calibrate and DC calibrate. The meter can not be burned out in the circuit which is used, but it can be moved to the right so rapidly by incorrect settings so that the needle could be bent.

There is more than ample room in the chassis for all parts and wiring, which greatly simplifies building for the inexperienced. The manual is very complete, not only in the construction and calibration of the instrument, but also in explaining the advantages and uses of the VTVM over a VOM.

On any instrument which will be used to repair or adjust other equipment, plenty of time should be allowed for the building, testing and adjustment of the kit. If you can't trust your instruments, you really are in bad shape! No difficulties were found with the IM-10 and calibration was a snap. No special test equipment is required to do the job properly. I think you will agree when you finish building it, that it will be used more than any other piece of test equipment in the shack. With its large 6" meter, you can even read the scales at 4 a.m., blood shot eye-balls and all! ... W3UZN

Chassis Mounted Phone Plug

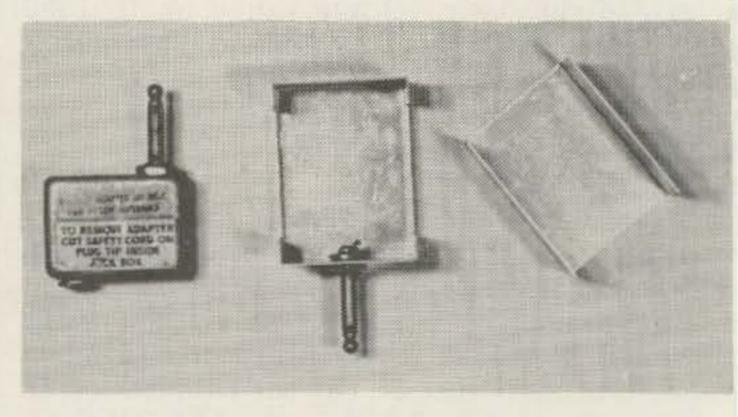

An occasional requirement exists for a chassis mounted phone plug. Construction of station accessory items is often simplified if they can plug directly into the equipment without the use of cords.

The MC-385, high to low impedance headset adaptor is still available on the surplus market at give away prices. Certain models of this unit have a phone plug which is secured to the case with a standard %" nut.

The plug is easily removed and can be installed as required. The photograph shows the adaptor, as supplied, and one application of the plug.

... W4WKM

Photo Credit: Morgan S. Gassman, Jr.

WANTED)

YOUR SURPLUS EQUIPMENT

Trade-Ins on New Factory Boxed 1962 Hammarlund Gear


ALL RECEIVERS WITH CLOCK AND MATCHING SPEAKER




HQ-100AC \$213.95



HQ-110C

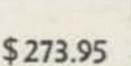

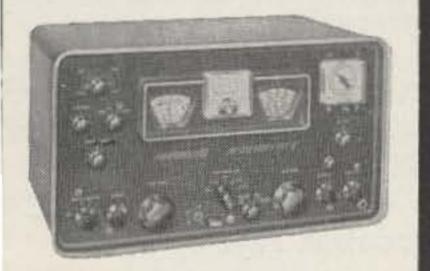

HQ-145XC



HQ-180C

\$458.95

TRANSMITTERS

\$298.95





HQ-170C \$388.95

Big Trade-In For Your Surplus Equipment WE NEED . . .

BC - 221, BC - 312, BC - 342, BC - 224, BC - 348, BC - 610, BC - 611, BC - 639, BC - 779, RT-68, RT-70, RT-77/GRC-9, R-388, R-390, R-391 / URR, URR - 13, URR - 32, ARC - 27, ARC - 33, ARC - 34, ARC - 38, ARC - 44, ARN - 14, ARN - 21, ARN - 30, ARN - 31. Test Sets with SG, URM, UPM, USM, and TS Prefixes. Also Surplus Technical Manuals, Military RTTY Equipment and Panadaptors.

Advise what equipment you have and Hammarlund Equipment you want. Top trades given on surplus and civilian gear.

Name	Dear Bill, W4FHY:
Address	
City S	I'm interested in a Hammarlund

BILL SLEP CO., 301 HIGHWAY, ELLENTON, FLORIDA, PHONE 722-1843

Commercial Notes

Irving Electronics surprised us with their new Hiverter and Preverters. Up 'til now Pappy has been taking it sort of easy down there in San Antonio turning out a whole series of printed circuit boards and kits. He has circuit boards available for almost every piece of ham gear ever written up using a board. Now, all of a sudden, he is making complete units. The Preverters are one band (six or two) transistorized preamps operating from 12 volts. These are obviously designed for mobile use and should meet a need for something to hop up the front ends of most of the commercial transceivers. The Hiverter is the answer to SSB on six meters. I know from my mail that a lot of fellows want to try SSB up on six, but not much has been available commercially to help them out. I've been after several manufacturers to get something out for this, so I'm happy to see it available.

The last time I decided to make a maximum effort to beat the ignition noise gremlins I found it a major job to locate the needed components. If it is difficult to do it here in New York where we are supposed to be able to find anything we need, I can imagine the problem a fellow would face out away from everything. Sprague has an answer to the difficulty, their new Suppressikit Type SK-1. This nets for \$17.85 and is supposed to suppress everything below 400 mc! It works with either six or twelve volt systems. The kit comes with complete instructions and everything is ready to use.

While on the subject of cars. . . . I discovered that Bill Slep (ad page 85) not only does a lot of business with surplus down there in Florida, but has his finger in this electronic ignition deal too. He will have kits available for this before long. I'm looking forward to trying one on my Porsche. I'd better not tell the factory, they'd probably take a dim view of it. It looks good to me though and will be very simple to install. Bill seems to have quite a new idea there with his taking of surplus gear in trade for new ham gear.

(W2NSD from page 4)

quests for information. Whenever you write to a company that does advertise you might thank them for helping to bring you the magazine . . . and encourage non-advertisers to rework their ad budget to include 73. You'll notice that a couple of the major manufacturers in the ham field are terribly conspicuous by their absence. I don't know whether this is because they hate me in particular or whether they don't want to have their products associated with such informality as we sport here. It is probably more the former for I am basically pretty rotten, as should be obvious in my editorials by now.

Your local parts distributor could probably stand a little pressure too. This fellow should have 73 on his counter, carry a goodly stock of our HAM-TV book and our INDEX TO SURPLUS book. If he has enough ham trade to carry magazines and books, then he should be advertising a bit too. Maybe he isn't big enough for a full page, but how about one of those 2"ads? They are only a little over \$25


a month.

I realize that these are a lot of things that I should be doing myself, but by the time Virginia and I get through sorting out subscriptions, reading articles, getting the magazine ready, calling advertisers for their promised ads, and preparing books, there isn't any time left to do anything else. Good grief, what will happen to everything while we're away for a month buzzing around Europe? We'll never catch up.

Reciprocation Again

Every time I talk to a radio club I ask for a show of hands on who has written to their Congressman about the Senate Bill 2361. So far I have seen one or two hands, and I get around to quite a few clubs. You can even add in a couple of conventions that I have addressed without getting much more of a response. This is very discouraging. Perhaps I am over emotional about this, but I feel that our showing on this matter is a key to our whole attitude toward the hobby. A lot of fellows are participating in ham radio without giving the hobby any personal support. They seem to feel that once they've subscribed to QST they have their own obligation out of the way.

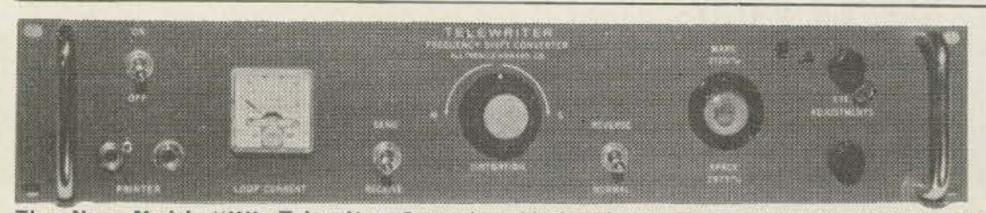If we allow this bill to die in committee



TELEWRITER FREQUENCY SHIFT CONVERTER

\$189.00 Rack Mounted-\$14.50 for Cabinet

The New Model "K" Telewriter Converter (designed by M. J. "Don" Wiggins W4EHU) includes: I. Linear audio discriminato with high Q toroids for maximum interference rejection. 2. Advanced keying tube circuit to compensate for distortion with front pane control. 3. Separate magnet current supply with milliammeter. 4. Dual eye indicator. 5. Chassis terminals for polar relay bias, S-F relay, and loop. 6. Front panel jacks for keyboard and printer. 7. Send-Rec. and Polarity Reversing switches. For further information and reconditioned teletype list, write; Alltronics Howard Coa., Box 19, Boston I, Mass. (Richmond 2-0048).

without any attempt to administer artificial respiration then we deserve everything that I believe will happen to us as a result. First and foremost we will find that the indignation of the DX hams is high when we have gone so far as to have a bill sponsored and then permitted it to die in committee. Almost every foreign amateur in the world feels a personal interest in this insignificant piece of legislation. Under our present rules no foreign amateur can get permission to operate while visiting the U.S. Senate Bill 2361 will change this to permit the F. C. C. to permit foreign licensed amateurs visiting the U.S. to operate, providing there is no possible question of security.

In many foreign countries quite a few of the amateurs are high in the government or leaders in business. Many of them swing a lot of weight. At international conferences on radio we find that an extraordinary number of the delegates turn out to be amateurs. These are the chaps that will be deciding in a couple of years just how the amateur bands are going to be re-allocated. These are the chaps who have occasion to visit the U.S. frequently and are prohibited from getting on the air during their visits to talk with us as locals and to talk home to friends.

If I tell you what I think may well happen at the next Geneva Conference you will dismiss me as an alarmist and heretic. Other magazines will editorialize on my "scare techniques" and so on. I think I know what I'm talking about and I have yet to meet one responsible ham who is in touch with current events who thinks any differently than I. The last conference taught me a lot, and little of it had any soothing effect on me as far as the brightness of our future is concerned. I feel that any amateur who has an interest in his hobby has a duty to write a letter to his Conggressman asking him to support Senate Bill 2361 and help get it out of committee.

If we should fail in this effort then we will be branded as ineffectual and we can be walked over by every other interest who covets our frequencies. Where will such a demonstration of weakness get us when the Citizens Banders get a lobby in gear asking for more CB channels? These fellows already outnumber us by two-to-one. We lost Eleven meters to them even when we had them outnumbered. If you

don't start writing we're sitting ducks.

Speaking of lobbies, how come we don't have a small group (even one man) down in Washington on a matter as vital as this? As I have said before, even one man could probably get this bill over the rough spots. If no amateur organization has a man free for the job, what about our manufacturers? Don't you fellows care what happens to the ham market in three or four years? You're selling about \$30 million worth of gear to hams a year, put a few hundred into keeping us going even if we're



COLUMBIA ELECTRONICS

4365 WEST PICO BLVD. LOS ANGELES 19, CALIF.

too busy talking on the air to drop a line in our own behalf. Have your rep in the Washington area check into things and push a little where it will help.

End of tirade.

Books & Booklets

Some time ago I editorialized about our publishing some small books and booklets. The response was rather good to this suggestion and we are now in the process of publishing the first of these. Our HAM-TV book doesn't count on this because we started work on that over a year ago. One of our first books under the new plan is the Index To Surplus by W4WKM. This is a prodigious effort by Roy and lists every surplus conversion article ever published in any of the popular radio magazines or con-

(W2NSD from page 87)

version manuals, along with a brief description of the conversion.

This book just came back from the printer and it is one I'm proud of. Everything went well with it . . . the print job is first class, the cover looks nice, and we have found no mistakes in it. This will be available through 73 directly, from Radio Bookshop, and should start appearing on the counters of the parts distributors soon. In particular I expect that surplus dealers will be wanting to sell this gem.

Fred DeMotte W4RWM of the Florida RTTY Society is putting the finishing touches on the new RTTY Handbook. Fred wanted to

CANDEE

COMMAND SET SPECIALS!

Famous Q-5'er. 190-550 kc. The receiver you've	All the late of th
looking for at only	\$9.95
BC-454/R-26: 3-6 Mc	7.95
BC-455/R-27: 6-9.1 Mc	
MD-7 MODULATOR: Special	3.95
T-18/ARC-5 XMTR. 2.1-3 MC excellent condition	4.95
T-19/ARC-5 XMTR. 3-4 MC excellent condition.	6.95
T-20/ARC-5 XMTR. 4-5.3 MC excellent condition	4.95
T-21/ARC-5 XMTR. 5.3-7 MC excellent condition	4.95

HEADSET BARGAINS!

HS-23: Hi impedance. Leather covered head-	
band. Brand new. Great buy. Only	\$5.95
HS-33: Low impedance. Leather covered head-	
band. Brand new. A J. J. Candee Special	6.95
Hi Fi Headset: 15,000 cycles! Brand new with	
chamois cushions. Terrific! Only	9.95
CD-307A Headset Extension Cord: Brand new.	
Approximately 5 ft. length. Only	.98

APX-6 TRANSPONDER

A midget warehouse of parts! Blowers, three Veeder-Root counters, I. F. strips, cavity, over 30 tubes, etc. Includes 3E29 tube. Good cond. A STEAL AT ONLY\$14.95 APX-6 Manual\$1.49

WALK-IN BARGAINS GALORE!

J. J. Candee has purchased the lion's share at a closing auction of one of the world's largest surplus warehouses. Our opportunity is yours. Come see all the goodies! We'll list some next month for mail order.

YOU GOT IT! WE WANT IT! LET'S DEAL!
We're paying top \$\$\$ for GRC-9; PRC-6, -8, -9,
-10. All electronic test equipment and lab eqpt.

All items FOB Burbank, Calif., subject to prior sale.
In Calif. add 4%. Min. order \$4.95.

J. J. CANDEE CO.

509 No. Victory Blvd., Burbank, Calif.
DDD area 213 — VI 9-2411

244 S. Park Avenue, Tucson, Arizona DDD area 602 — 624-2014 finish it earlier, but I held him up in order to get in some last minute commercial equipment. I also wanted to wait until CQ brought out their recently announced RTTY book to make sure that we covered everything that they missed. I'm happy to report, after seeing the CQ effort, that our book is much less text-bookish and is written from the practical application aspect rather than the heavy theory angle. I suspect that most TT devotees will invest in both in order to have as full a library as possible.

Carole Hoover K9AMD and I talked over the booklet idea out at the Springfield (Ill.) convention last year (where my transistor radio was stolen from my room at the St. Nicholas Hotel). Carole followed my suggestions and has done a magnificent job of preparing a booklet on ham radio clubs. She went into a lot of research, writing to dozens of ham clubs and interviewing hundreds of ham club officers to find out what aspects were important to the survival of a ham club. Her booklet, well illustrated, is now available under the title, "The Care and Feeding of a Ham Club." This booklet is not only interesting reading for everyone, but will be invaluable to all hams who want to help their own club grow and prosper.

K8LFI, one of our regular authors, sent in a manuscript recently that was much too long to publish in 73. I suggested that we put it out as a booklet and Bill went along with the idea. This one is called, "Simplified Math for the Ham Shack." This is the best math article I've ever seen and it makes the whole process quite simple. I know that a lot of people have a great fear of math. This is a shame, for once brought out of the school book and given the breath of life the subject is simple and interesting. Bill is a wonderful explainer and he leads you gently from one step to the next, covering the whole subject with expert finesse.

What with trying to get 73 ahead enough to let us go to Europe for the month of April, it is incredible that we should also be able to produce even more booklets. $W\phi OPA$ sent in a piece on the "Mickey Miker" which just had to be published. Again it was too long to print in 73 unless we chopped the daylights out of it. This is now a little eight page booklet. Harvey gives exhaustive details on the building of this fine piece of test equipment which will measure capacity right down to the fraction of a mmfd.

K8BYN sent in a fine piece on coils. I've long felt that there was a need for a basic series of booklets on radio. This one does a wonderful job of explaining about all the various types of coils that are used in radio construction and is magnificently illustrated.

As more book and booklet manuscripts come in we'll be publishing more booklets. I am quite sure that we are giving the best deal by a very

(Turn to page 90)

TEST EQUIPMENT

SCOPES

TRANSMITTERS AND RECEIVERS

Dumont 5 inch # 241 — \$79.00	, #208 — \$59.00
Dumont 3 inch # 224A — \$49.00, W.ETS-34	
RCA 9 inch #304A — \$75.00, RCA	3 inch — \$19.00
Heath 5 inch — \$24.00OS-8A/U —	3 inch — \$65.00

SIGNAL GENERATORS, ETC.

Hickok #610, universal TV, 0-230 MC\$6	9.00
Precision #E-200, 50 KC — 44 MC\$3	5.00
Hickok #188X, AM and FM, 100 KC - 110 MC\$6	5.00
Federal #804, 8-330 MC	9.00
I-208, FM, 1.9-4.5 MC, and 19-45 MC\$3	5.00
Ferris Model 18-B, 18-155 MC	9.00
RCA #710-A, 370-445 MC, 450-500 MC\$3	5.00
BC-338-A100-155MC — \$39.00. Kay Megasweep — \$4	9.00
E1co #315, 75 KC-150 MC\$2	4.00
Clough-Bringle Model OCA, 100 KC-30 MC\$1	8.00
Frequency Meter, Lavoie 105-SM, 375-725 MC\$3	5.00
OAP, Wavemeter-Oscillator, 150-230 MC\$2	9.00
Hewlett-Packard 200 BR audio generator 20-20 K\$4	9.00
Western Electric, 19-C audio Gen. 20-15 K\$4	9.00
Tube checker, Precision Series 10-15, counter type\$4	5.00
Precise #116 tube checker\$7	9.00
V.T.V.M. Precision model EV-10\$2	4.00
Ballantine model 300 V.T.V.M\$6	5.00
Freq. meter B.C. 221 or Navy LM\$4	9.00
Power supply (115V A.C.) for LM Freq. meter\$1	5.00
Hewlett-Packard #520-A, high speed decade scaler. New \$19	5.00
General Radio 605-B, 9.5-30 MC. Sig. Gen\$9	5.00
G.R. P-522-A Sig. Gen. 250-1000 MC\$19	5.00
G.R. 700-A, BFO, 50 cy5 MC\$15	0.00
G.R. 561-D, Vacuum Tube bridge\$12	5.00
Sig. Gen., Measurements #75, 50-400 MC\$15	0.00

Heath DX-100\$145.00	B&W 651 matchmaster \$30.00
Johnson Viking I\$95.00	Sonar SRT-120\$69.00
Globe Scout 680\$69.00	Hallicrafters S-85\$79.00
	S-36-A or S-27\$95.00
Eldico TR-75-TV\$29.00	5-50-A 01 5-21 \$40.00
Viking Mobile\$65.00	RAK-7 or RAL-7, 115V.\$49.00
Globe Chief 90A\$59.00	RBM or RBS, 115V\$49.00
Eico 720\$65.00	Poly-Comm. C.B\$110.00
Viking Mobile VFO\$29.00	Heath DX-35\$45.00
Globe Chief De Luxe\$59.00	National HRO\$59.00
Central Electronics #20-A with	VFO and QT-1\$195.00
Gonset Communicator IV for 6 M	[eter\$245.00
Eldico 500 SSB, 500 Watt linear	Amp. 80 thru 10 Meter\$225.00
Super-Pro #794, to 40 MC, 115 V	7 \$145.00
Super Dec #770 with 115 W	00.0112
Super-Pro #779 with 115 V	ec= 00
Gonset G-11 C.B. Transceiver	
Gonset G-77-A Xmitter and powe	r supply\$175.00
Gonset G-66-B Receiver	\$95.00

MISCELLANEOUS

Pulse generator, Teletronics PC-100-R	\$65.00
Underwater sounding, CPK-50175 of DAX-1	\$39.00
Masco, MA-125, 100 Watt amplifier	\$65.00
Receiver, type RCK	\$35.00
ART-13, 2 meter Xmitter	\$35.00
TCS Xmitter, receiver and power supply	\$69.00
ARC-1, 2 meter Xmitter	\$29.00
Sweep Calibrator, Browning Lab. GL-22A	\$65.00
LAD, Hi Freq. Sig. Gen. 2700-2900 MC	\$35.00
RF Monitor type CHZ for RTTY, used with OCT-2 and	
OCT-3 Equipment	\$35.00
PE-103 Dynamotor 6-12 V. New	\$15.00
Power supply for ARC-1, 115 V. A.C	\$29.00

Prices are based on fair relative values, some items are new, some are used. Enclose sufficient postage, excess will be returned. (Avoid delay.) F.O.B. Hempstead. 25% with COD orders.

ALGERADIO CO.

37 GREENWICH ST., HEMPSTEAD, N. Y.

SIGNAL EYE OPENERS!

Q-5er - 190-550kc. Use for receiver, tunable i.f., double or triple conversion, tremendous selectivity. Excellent cond., with tubes...\$9.95

1000 ohms-per-volt Pocket Tester. Reads AC or DC volts in 3 ranges, 0-15, 0-150, 0-1000V. DC current 0-150 MA. Resistance 0-100,000 ohms. Convenient thumb - operated zero ohms adjust, pin jacks for all 5 ranges. 4" x 21/4" x 1 1%". With test leads, self-contained battery & instructions. Not surplus, but brand new manufacture THIS MONTH ONLY\$6.50

ALL EICO KITS in stock. Kits shipped postpaid anywhere in U.S.

BC-604 Transmitter, 20-27.9 MC Crystal-Controlled 80-channel transmitter. Brand new in original cartons. Ideal for CB, easy to put on 10 Meters. Only\$4.50 Set of 80 brand new Crystals for above, includes 1 500KC Calibration crystal\$5.95 Both for\$9.95

CB & 10 Meter 16-Tube Transceiver. Famous BC-1335, Freq. range 27-38.9 MC, 2-channel xtal-controlled, small compact unit. Has built-in 6 and 12 volt power supply. Inside like new, outside needs retouching. Some tubes missing, but WOW! \$14.95

Limited supply COLLINS ART-13 TRANSMITTERS 2-18.1 MC. As is, most in pretty nice shape. If possible, come in and see them. AS LOW AS \$12.95 each!

CHECK THESE BARGAINS:

2N398 RCA TRANSISTORS.50¢ ea. 2N499 PHILCO TRANSISTORS50¢ ea.
NE2A Neon Lamps 5 for 25¢
#47 Pilot Lamps7¢ ea.
BC-1206 Beacon Receiver less tubes\$1.95
0-130 V 5 amp Variac\$15.95
RG-58/U not surplus41/2¢/ft.
6AU6 TUBE guaranteed OK 69¢
12AT7 TUBE guaranteed OK 89¢
6X4 TUBE guaranteed OK 49¢
66' roll Plastic Insulating Tape. 79¢
HS-33 Headsets, 600 - ohm, used, good condition\$3.95
NEW Commercial-type Carbon Hand Mike, push-to-talk, coiled cord (not surplus). Only\$6.95

OPEN DAILY 9-6 MONDAY & FRIDAY 9-9 SUNDAY 10-4

7 DAYS A WEEK

WRITE FOR FLYERS

SIGNAL ELECTRONIC SUPPLY GARDENA, CALIF. FA 1-4867 (213)

SAVE AT SIGNAL!

All orders FOB Gardena, Calif. Minimum 25% with order. Minimum order \$3. Calif Res. add 4% state tax.

(W2NSD from page 88)

wide margin to all authors of books. For that matter we are giving the best deal to all authors in 73 too.

Look over the list of booklets and stint not.

Write

If you've been reading the editorials at all it should come as no surprise that Virginia and I are leaving for Europe on April first via Lufthansa chartered jet. The Porsche Club of America is sponsoring the trip. As you may know, a charter flight costs less than half of

ALL BAND TRAP ANTENNA!

Reduces interference and Noise on All Makes Short Wave Receivers. Makes World Wide Reception Stronger. Clearer on All Bands!

For ALL Amateur Transmitters. Guaranteed for 500 Watts Power for Pi-Net or Link Direct Feed, Light, Neat, Weatherproof

Complete as shown total length 102 ft. with 87 ft. of 72 ohm balanced feedline, Hi-impact molded resonant traps. (Wt. 3 oz. 1" x 5" long). You just tune to desired band for beamlike results. Excellent for ALL world-wide short-wave receivers and amateur transmitters. For NOVICE AND ALL CLASS AMA-TEURS! NO EXTRA TUNERS OR GADGETS NEEDED Eliminates 5 separate antennas with excellent performance guaranteed. Use as Inverted V for all band power gain, NO HAYWIRE HOUSE APPEARANCE! EASY INSTALLATION! 80-40-20-15-10 meter bands. Complete.....\$14.95 40-20-15-10 meter bands. 54-ft. ant. (best for w-w swl's) 13.95 20-15-10 meter bands. Dual Trap. 24-ft. antenna...... 19.95 SEND ONLY \$3.00 (cash, ck., mo) and pay postman balance COD plus postage on arrival or send full price for postpaid delivery Available only from:

WESTERN RADIO - Dept. A7-3 Kearney, Nebraska

R-267/ARR-27 RCVR. tunable approx. 450-510 mcs contains 28 tubes, blower, coax relay, 2 gearhead motors, etc. BRAND NEW IN DOUBLE SEALED CARTONS. Shipping wt. approx. 50 lbs. WAS \$24.50 Closeout Special \$19.50

MODEL 15 TTP in good operating condx. \$275.00 KY-42/ARR-27 DECODER contains 43 tubes new \$29.50

BIRD MOD. 74 coax switch 6 posn. brand new 22.50

Min order \$5.00. Pse include postage. Excess refunded immediately. All prices FOB our Warehouse, Bronx, N. Y.

Space ELECTRONICS CO.

218 West Tremont Ave., Bronx 53, New York TRemont 8-5222 the regular tourist class fare. We will arrive in Stuttgart on the second and be driven to Solitude Castle where all of the new Porsches ordered by the club members will be spread out on the huge lawn. Among them will be my old 1958 Porsche Speedster which I shipped over in January to have reconditioned.

I was all for ordering one of the nice new model Porsches, but Virginia pointed out that we are much too close to pauperism to even consider putting a down payment on a new

car. Practical gal.

You're probably getting pretty tired of hearing about Porsches all the time, perhaps I'd better explain. All Porsche owners are absolutely certain that the Porsche is the finest car in the world at any price. Dr. Porsche was a fanastic genius and is responsible for many of the best features of todays cars. He designed the little VW. He thought up the flat opposed piston air cooled engine which makes the VW (and Porsche) so unbeatable. He invented torsion bar suspension, synchromesh transmission, and was one of the first designers to streamline cars. There are whole books written about the amazing works of this man. His masterpiece is the Porsche car. If you follow sports car racing you know what successes Porsche has had.

Several European amateurs have written and I've set up a fast schedule of talks during my trip. The exact route is: Stuttgart, Munich, Innesbruck, Venice, Florence, Pisa, Genoa, Milan, Geneva, Bern, Luzen, Zurich, Frieburg, Paris, Luxembourg, Heidelberg, Darmstadt, Frankfurt, Berlin, Frankfurt, Wiesbaden, Nurburgring, Bitburg, Koln, Mulheim, Arnhem, Rotterdam, Amsterdam, Hamburg, and New York. It sure would be fun to get a card or letter during the trip from any of you that care to write. You can write to me in care of American Express, Paris, France where I will pick up all mail on the 14th of April, or American Express, Berlin, Germany on the 19th. Airmail letters take about four days, so leave time. Airmail is 15¢ to Europe, but I'm not worth it. May be a QSL, at least?

April Last Year

The April 1961 issue of 73 was quite an issue. We still have a few left in case there was something you missed in it. The most interesting article (according to reader votes) was K8BYN's Six Meter Nuvistor Converter. This unit used two 6CW4's in cascode and resulted in a very low noise figure circuit. K8ERV came up with a dummy "next stage" device, a continuous tuning link coupled absorption wavemeter with a loaded and metered rf indicator. W4WKM has an article on how to protect silicon rectifiers in case of a shorted capacitor. K4ZGM's Let's Modulate, Not Crepitate explores Heising modulation . . . rather successfully. Jim Kyle K5JKX has a new noise limiter circuit for us. Many readers

ave written in telling us how well this one orks and recommending it. W4WQT writes bout the importance of calibration. W6VVZ's P 304TL gallon final may not be new, but it oes show us how to get maximum power conomically. K2SJN comes up with all of the nswers TVI committee needs to handle the ifficult cases. W9HOV (Gain, Inc.) presents chart of the lengths of 1/2 wave, 1/2 wave oax, 1/4 wave coax and 41/2 waves for the fferent ham bands. K8HDR came up with a ever method of getting a lot more audio out the Command Receivers KL7DLC sold a lot the April issues with his transistorized 40 att modulator. Great for mobile operation. 3UZN tested the Heath Twoer for us. Bill shby K2TKN had a fine article on noise ppression. Our big technical article for this onth is on if selectivity and it covers ceramic ters, Collins filters, crystal filters, lattice ters, Q-multipliers, L-C filters, Q-5'ers, etc. cap the whole works we have an article on ow to write for 73 and get rich beyond your ildest dreams. While they last they are 50¢ ch.

Reader

Shortly after the March issue of 73 was ablished I got a frantic phone call from E.G. Sales. It seems that Sam has thousands those FL-8 and FL-5 filters on hand and is lling to force himself to part with them at low figure (\$2.49). I believe you'll find more tails on this situation back on page 94. In ecking the fantastically complete list comled by W4WKM and published by us under e title of Index to Surplus (\$1.50) I find ne other references to FL-8 and FL-5 ticles. The most important is the one I pubhed in CQ in November 1957 wherein you n achieve almost unbelievable selectivity th cascoded FL-8's.

Oh Rally?

A letter from KZ5SW Ted Wilds asks, Where . . . was the rig in your Porsche? I dn't see it in the photo in Foreign Car Guide. Here was a lot of other expensive equipment." ok closely Ted, down under the dash is a anscon-6! This makes the dozenth magane to print this picture of the most accessied sports car ever seen. This is the cockpit my 1958 Porsche Speedster, all duded up

rallying.

What's a rally? Where've you been! A rally a completely non-ham radio event (which is no business in 73, except that it is an enusiasm of the editor and sometimes you have take the bad with the good) primarily of cerest to sports car addicts. Most sports car abs put on several rallies a year, and they e about the only source of rallies. In a rally u have a driver and navigator. You are wen a set of instructions and started out one minute intervals. The object is to follow the instructions as closely as possible, eping on the roads specified and driving at

2 METER STATION \$27.50!!

The Fabulous ARC-3 Transmitter and Receiver, both NATURALS for 2 Meters! Buy them separately at this low, low price, or together for an even better bargain. Transmitter uses 2 832A's in final. Automatic tuning assembly aligns itself automatically. Both transmitter and receiver can be used on 2 Meters right away with hardly any changes. For a deluxe job on the receiver see conversion article on p. 22 Dec. 73 Magazine. Don't miss this bargain! If you're on 2 already you can't afford to miss this opportunity to set up that extra station to monitor repeaters, favorite channel, etc. Leave it on all the time—rugged gov't specs!

ARC-3 2-Meter Transmitter \$14.95
ARC-3 2-Meter Receiver \$14.95
Both units \$27.50
Complete with Tubes. New, Beautiful!
Just unpacked!

KEYERiminy WHAT A BARGAIN! ARA-26

KY-65/ARA-26 KEYER—for versatile applications see article Oct. 73 page 22, then buy at our like give-away price of\$3.50 Real handy around the shack. Look up the article!

GLASS'S GASSERS! Bargains you would boot yourself around the block for missing, in our new Catalog—send for it. Remember, too, we buy or swap gear, esp. APR, TS, GRC, PRC.

J. J. GLASS CO.

1624 S. Main St., Los Angeles 15, Calif. RI 9-1179 (213) Fridays 'til 9

Surplus at Surplus Prices

SOLA constant voltage transf. 95v — 125v 1 phase 60 cy. .520 amps excel condition wgt. 11 lbs \$7.00 Glide slope rec. #443 apn w/tubes & xtals good cond. lots of good parts approx wt. 11 lbs. \$2.00 VARIACS 1 amp \$3.00 0-135v 60cy wt 5 lb 3 amp \$5.00 Meter dc 2.5ma either side of center on 1st scale 25ma either side of center on 2nd scale w/built in schunts 3" rnd good for transistor work 1 lb. .\$2.00 Nichol cadmium battery 10 amp hour rechargeable 5000 times or more $41/2 \times 25/8 \times 3/4$ " 1.37v wt 1 lb \$2.00 All prices f.o.b. San Antonio Tex. IN TEXAS add 2%

tax. Please send postage, excess refunded immediately. Prices subject to change without notice.

TEXONIC COMPANY


P. O. Box 13103, San Antonio, Texas

HAM SHACK NOVELTY

Authentic-looking, two-color certificate claiming tongue-in-cheek ownership of an acre on the Moon's surface. Ideal gift or conversation piece for shack, bar, den or office. (See Pg. 119—Jan. 61, CQ.) With gold seal and name and call inscribed only \$1.00 each. Six for \$5.00. Send check or M.O. to—

BOX DXG, 1738 — 201 St., Bayside 60, N. Y.

INDEX TO SURPLUS

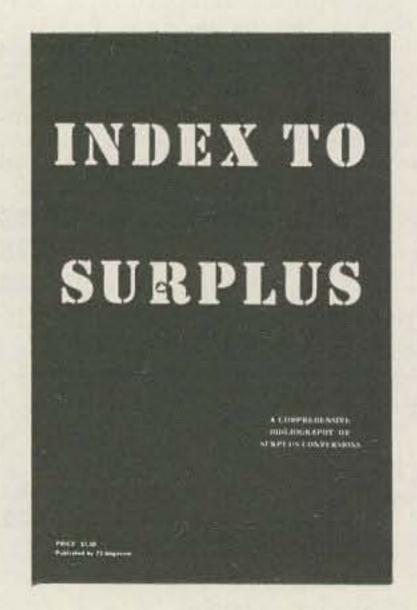

Roy Pafenberg W4WKM has accomplished a major effort in this compilation. It lists every known surplus conversion article, giving a capsule rundown on the conversion accomplished and the magazine in which it was published. If you do any surplus conversion work this book can save you a lot of time by telling you exactly what conversions have already been published. 64 pages packed with information.

Price . . . \$1.50

73 Magazine 1379 East 15th St., Brooklyn 30, N. Y.

DUMMY LOADS

52 OHMS NON-RADIATING SWR BELOW 2:1 ALL BANDS THRU 2 METERS



100 Watts......ICAS \$4.95 Wired 200 Watts.....ICAS \$7.95 Wired Write for new catalog (Wired, Add \$4.00) Postpaid U.S.A.

Coming soon: Filter for SSB.

HAMKITS SEE YOUR DEALER OR DIRECT
308 EDGAR AVE., CRANFORD, N. J. Box 1755


HAM **GEAR**

BUYS **TUBES EQUIPMENT**

Barry **Electronics**

512 Broadway New York 12 WA 5-7000

Send for Catalog

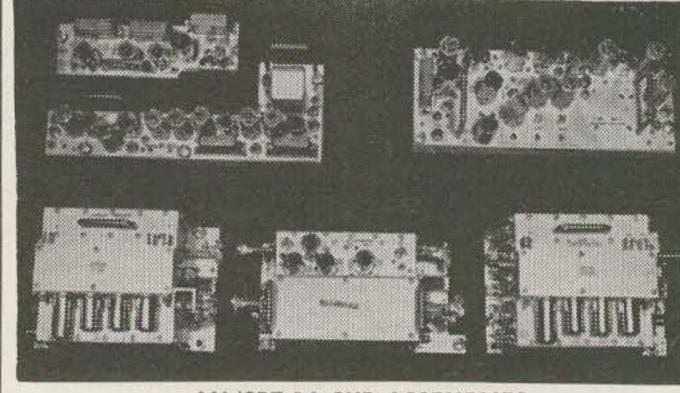

AN/SRT-14 SUB-ASSEMBLIES

Left to right, top to bottom: Frequency Converter Uni-11B; One mc Step Generator Unit 10; Frequency Converter Unit 9; 100 kc Step Generator Unit 8; Frequency Converter Unit 5; and Frequency Converter Unit 11A These are described in more detail in the article or page 44 of the February 73.

Unit 5. Sold Out Unit 8. . \$10.00

Unit 11B. 10.00

Unit 10 Sold Out Unit 11A. \$5.00 Unit 9.. 10.00

All four units.....\$24.00

These units are all brand new in their original cartons and are complete with tube shields, less tubes. Manufactured in 1955-56.

Cash FOB Annandale

RITCO

Box 156 Annandale, Virginia

COME IN FOR OUR FREE PARKING-SATURDAY SPECIALS

THOUSANDS OF ITEMS - THOUSANDS OF BARGAINS

APX-6—UHF transponder, perfect for 1215 mc. Very little conversion needed — complete w/tubesNEW \$18.95 ATK/BC-1211—TV camera w/iconoscope and all tubes. At about 1/3 last surplus price and 5% of government priceL/NEW 99.50 AXR—Receiver-Monitor for ATKEXC 29.95 ATX—Transmitter used w/ATK-camera, incl. antenna
EXC 39.95
S-98-Voltage divider, dummy loadNEW .95
3C-221—Freq. meter w/calib. chart 72.45
S-35-X-Band freq. & pwr. meterEXC 61.45
-196B-Sig. Gen. 150-230mc-terrific buyNEW 1.45
NSEPT -
NSERT s
DY-17-Dyn for ART-13, w/filter, 28 v toEXC 11.45
E-73—Dyn 24vdc to 1000v @ 0.3a, w/filterEXC 7.95
Q-15-Dyn 12/24 to 265/540v 120/26maNEW 8.45
00-1-Inverter 24-28dc to 115/1/800 @ 1 kva used for
oran
ets AN/APN-9 etc. Mfr: Eclipse-Pioneer4/45.00
C-342/BC-312—RCVR 1.5-18mcs
C-348-RCVR 950kc-18mcsEXC 75.00
C-1206 PCVP 105 420kg 5 tubes 4 lbs EVC 9.05
C-1206—RCVR 195-420kc, 5 tubes, 4 lbsEXC 8.95

BC-617—RCVR 30-50mc, FM, xtal controlledEXC 22.45 R/8ARN8—RCVR 75mc, 1/tubes, FB for partsEXC 2.95 BC-929—3" Scope, Station monitor, eas. conv. for bench. EXC 12.95
ASB—Indic'r. Scope w/5BPI, easy convNEW 15.45 ID/6B/APN-4—5" Loran Scope w/5 easily convEXC 11.95 TS-239—Famous lab Scope by Lavoie SpecialEXC 169.45 RT-45—XCVR 14-50mc, 807 final, w/0-200ma mtr.
SCR-522—XCVR 100-156mc, 832 final, 30 WattsEXC 18.45 BC-620—XCVR 20-27-9mc, w/tubesNEW 12.45 BC-659—XCVR BC-1158—XMTR 50-97mc, 815 final AM—few left—
BC-458—XMTR 5.3-7mc, can run 120 WattsEXC 6.95 GO-9—XMTR 0.3-18mcs, 100 Watts, 2 803's final. NEW 54.50
BC-604—XMTR 20-27-9mc, 30w, 10ch—bargainNEW 9.45 H-63/U—Headset & Boom Mikelow priceEXC 4.50 T-26—Mobile chest carbon micNEW 4/4.00 1.25 J-5—Flameproof keybuy twoNEW 2/1.25 .69 AN/CRT-1B—Sonobuoy w/tubes & p'chute 70-90mcs
A-62—Phantom ant. 20-29mc, handles 50wNEW 11.45

X150A 8.00	829A4.00	6Н6
E29 4.95	837	6SS7
07A2/1.00	6AKS	1625
07B	6AC7	1626
03	6SN7	169825.00
071.10	6SH710/12.00	9004

ELECTRONICS

a division of Amber Industrial Corporation


All prices FOB Linden, N. J. Some quantities limited. Prices subject to change without notice. Min. order \$4.00.

1920 E. Edgar Road Linden, New Jersey on Highway U.S. 1 — across from Esso Research Labs

(W2NSD from page 91)

e specified speeds. Every so often you will ne across a checkpoint where you are timed. ey know exactly what time you should pass e point and you lose points for every second rly or late there. It takes great attention to tail to consistently win these events.

Many hams have been attracted to rallying. is a rare Sunday rally in this area that es not see at least a half a dozen hams paripating. Harold Winston W2DIR, who arted rallying about two years ago, is now esident of the Town & Country Sports Car ab. This is remarkable when you consider at he drives a Desoto! I notice that old end Bob Schoening WøTKX is high on the CA rally list for 1961. Porsche driver. Most

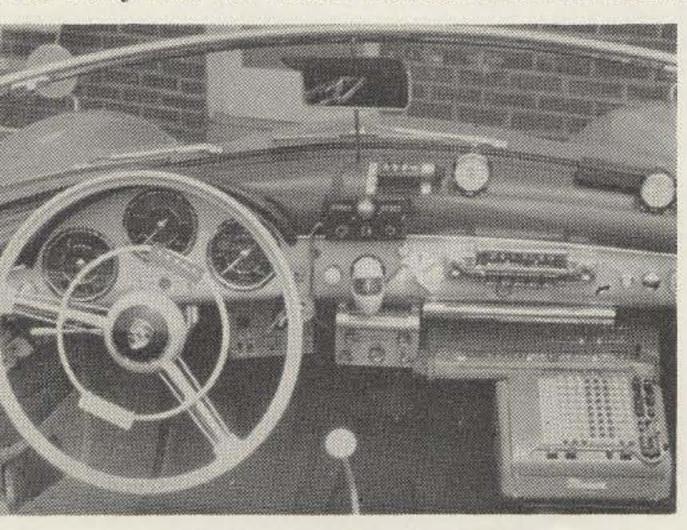



SURPLUS TUBE SPECIALS—GUARANTEED

HAM-TV

Complete instructions for getting on TV for under \$50.00. Join the Fun.

73 MAG, 1379 E 15, Bklyn 30, N.Y.

of the gang up at ARRL HQ are rallying these days and now and then one of them ventures down this way to compete.

There is something fascinating about striving for absolute perfection for from three to five hours. Everything fights you. It takes many days to adjust a stopwatch to hold its time to the quarter of a second over a period of hours. All through the rally we tune in CHU on 7335 kc and make sure that the watch is still accurate. Even with an electric odometer you have to be very careful to measure your mileage to the half a hundreth of a mile (25 feet). Every time you have to speed to make up time for a wrong turn your tires get warmer and expand and you have to allow for this. Both driver and navigator (Virginia) are kept busy every minute.

You've got a lot of writing ahead, you'd better get started. Write our advertisers, your senator, CQ for my slides, and don't forget to drop me a note in Paris or Berlin.

Wayne

FL-8 FL-5F FILTERS

These extremely selective audio filters have six tuned circuits and can be used to either peak a signal of 1020 cycles or reject it. The filter is very simple to use, just connect it in the headphone line or at the input to your last audio stage and you are set to go. The filters are an outstanding success for CW operations where they are one of the greatest single-signal circuits ever devised. When you switch to "peak" all you hear are 1020 cycle signals, everything else is filtered out. On phone you switch to "null" and take out heterodynes. You can read all about the filter in the March 1962 issue of 73 in the W4THU article: "Cure That Angry Band". The one filter gives you better than .5 kc (to 60 db down) selectivity. If you are interested in seeing what two or more will do you might check the November 1957 issue of CQ, page 60, where four are used for a selectivity of 150 cycles at 50 db down! You have to build a small amplifier to make up for the loss of gain of four units cascaded like that. These filters normally sell for about \$5 each, when you can find them. Note our "halfprice" sale. The FL-8 has a switch built in the box, the FL-5 requires an external switch to change from peak to null to out. The FL-5 is a bit better for building into things, while the FL-8 is handier to use outboard. Just try one of these filters and see what a difference it makes.

POSTPAID \$2.49

ORDER BLANK

Please send me FL-8 at \$2.49 FL5F each.

ADDRESS

CITY..... STATE....

SEG SALES

1306 Bond Street, Los Angeles 15, Calif.

ADVERTISERS

Alco	39
Algeradio	89
Allied Radio	96
Alltronics-Howard	86
American Crystal	65
Arrow Electronics	13
Barry	1, 92
Roct	79
Best	77
Conde	23-73
Candee	88
Clegg	
Columbia	87
Continental	61
Cornell-Dubilier	21
Cushcraft	25
Davco	67
Donna's Ceramics	4
Dow Key	3. 79
Electronic Specialists	79
Elliott (Swan)	73
Epsilon	79
Evans	15
E-Z Way	4
Fair	84
Finney	15
Gavin	
Gavin	33
J. J. Glass	91
Goodheart	
Graham	75
Ham Boards	. 79
Ham Kits	5, 92
Hammarlund	41
Heath	26-27
Instructograph	21
International Crystal	ver II
Irving	31
Johnson	5
KTV Towers	65
Lafayette Radio	. 05
FULLIAGILIS RUUIU	- 2
Miller	53
Miller	53 er IV
Miller	53 er IV 35
Miller	53 er IV 35
Miller National Radio Newtronics Novelties P & H	53 er IV 35
Miller National Radio	53 er IV 35 11 47-50
Miller National Radio	53 er IV 35 11 47-50 63
Miller National Radio	53 er IV 35 11 47-50 63
Miller National Radio	53 er IV 35 11 47-50 63
Miller National Radio	53 er IV 35 11 47-50 63 92 94
Miller National Radio	53 er IV 35 11 47-50 63 92 94 89
Miller National Radio	53 er IV 35 11 47-50 63 92 94 89 75
Miller National Radio Newtronics Novelties P & H Polytronics Radio Bookstop Reyco Ritco S.E.G. Sales Signal Radio Skylane Slep	53 er IV 35 11 47-50 63 92 94 89 75 85
Miller National Radio	53 er IV 35 11 47-50 63 92 94 89 75 85 90
Miller National Radio	53 er IV 35 11 47-50 63 92 94 89 75 85 90 82
Miller National Radio	53 er IV 35 11 47-50 63 92 94 89 75 85 90 82 80
Miller National Radio	53 er IV 35 11 47-50 63 92 94 89 75 85 90 82 80
Miller National Radio Covenance Newtronics Novelties P & H Polytronics Radio Bookstop Reyco Ritco S.E.G. Sales Signal Radio Skylane Slep Space Electronics Space Raider Subscribe to 73 or else TAB Tapetone	53 er IV 35 11 47-50 63 92 94 89 75 85 90 82 80 95 57
Miller National Radio Covenance Newtronics Novelties P & H Polytronics Radio Bookstop Reyco Ritco S.E.G. Sales Signal Radio Skylane Slep Space Electronics Space Raider Subscribe to 73 or else TAB Tapetone	53 er IV 35 11 47-50 63 92 94 89 75 85 90 82 80 95 57
Miller National Radio Covered Newtronics Novelties P & H Polytronics Radio Bookstop Reyco Ritco S.E.G. Sales Signal Radio Skylane Slep Space Electronics Space Raider Subscribe to 73 or else TAB Tapetone Technical Material Corporation	53 er IV 35 11 47-50 63 92 94 89 75 85 90 82 80 95 57 17
Miller National Radio	53 er IV 35 11 47-50 63 92 94 89 75 85 90 82 80 95 57 17 55
Miller National Radio	53 er IV 35 11 47-50 63 92 94 89 75 85 90 82 80 95 57 17 55 77
Miller National Radio	53 er IV 35 11 47-50 63 92 94 89 75 85 90 82 80 95 57 17 55 77 91
Miller National Radio Newtronics Novelties P & H Polytronics Radio Bookstop Reyco Ritco S.E.G. Sales Signal Radio Skylane Slep Space Electronics Space Raider Subscribe to 73 or else TAB Tapetone Technical Material Corporation Telrex Texas Crystals Texonic Topaz	53 er IV 35 11 47-50 63 92 94 89 75 85 90 82 80 95 57 17 55 77 91 67
Miller National Radio	53 er IV 35 11 47-50 63 92 94 89 75 85 90 82 80 95 57 17 55 77 91 67 93
Miller National Radio Newtronics Novelties P & H Polytronics Radio Bookstop Reyco Ritco S.E.G. Sales Signal Radio Skylane Slep Space Electronics Space Raider Subscribe to 73 or else TAB Tapetone Technical Material Corporation Telrex Texas Crystals Texonic Topaz U. S. #1 Vanguard	53 er IV 35 11 47-50 63 92 94 89 75 85 90 82 80 95 57 17 55 77 91 67 93 25
Miller National Radio Newtronics Novelties P & H Polytronics Radio Bookstop Reyco Ritco S.E.G. Sales Signal Radio Skylane Slep Space Electronics Space Raider Subscribe to 73 or else TAB Tapetone Technical Material Corporation Telrex Texas Crystals Texonic Topaz U. S. #1 Vanguard Waber	53 er IV 35 11 47-50 63 92 94 89 75 85 90 82 80 95 57 17 55 77 91 67 93 25 28
Miller National Radio Covered Newtronics Novelties P & H Polytronics Radio Bookstop Reyco Ritco S.E.G. Sales Signal Radio Skylane Slep Space Electronics Space Raider Subscribe to 73 or else TAB Tapetone Technical Material Corporation Telrex Texas Crystals Texonic Topaz U. S. #1 Vanguard Waber Western Radio (Nebraska)	53 er IV 35 11 47-50 63 92 94 89 75 85 90 82 80 95 57 17 55 77 91 67 93 25 28 90
Miller National Radio Covered Newtronics Novelties P & H Polytronics Radio Bookstop Reyco Ritco S.E.G. Sales Signal Radio Skylane Slep Space Electronics Space Raider Subscribe to 73 or else TAB Tapetone Technical Material Corporation Telrex Texas Crystals Texonic Topaz U. S. #1 Vanguard Waber Western Radio (Nebraska) Western Radio (San Diego)	53 er IV 35 11 47-50 63 92 94 89 75 85 90 82 80 95 57 17 55 77 91 67 93 25 28 90 75
Miller National Radio Newtronics Novelties P & H Polytronics Radio Bookstop Reyco Ritco S.E.G. Sales Signal Radio Skylane Slep Space Electronics Space Raider Subscribe to 73 or else TAB Tapetone Technical Material Corporation Telrex Texas Crystals Texonic Topaz U. S. #1 Vanguard Waber Western Radio (Nebraska) Western Radio (San Diego) World Radio Labs	53 er IV 35 11 47-50 63 92 94 89 75 85 90 82 80 95 57 17 55 77 91 67 93 25 28 90 75 45
Miller National Radio	53 er IV 35 11 47-50 63 92 94 89 75 85 90 82 80 95 57 17 55 77 91 67 92 94 95 75 85 96 75 87 97 97 97 97 97 97 97 97 97 97 97 97 97
Miller National Radio Newtronics Novelties P & H Polytronics Radio Bookstop Reyco Ritco S.E.G. Sales Signal Radio Skylane Slep Space Electronics Space Raider Subscribe to 73 or else TAB Tapetone Technical Material Corporation Telrex Texas Crystals Texonic Topaz U. S. #1 Vanguard Waber Western Radio (Nebraska) Western Radio (San Diego) World Radio Labs W5GOS US MAP 73 Back Issues	53 er IV 35 11 47-50 63 92 94 89 75 85 90 82 80 95 57 17 55 77 91 67 93 25 28 90 75 45 75 94 95 75 96 97 97 97 97 97 97 97 97 97 97 97 97 97
Miller National Radio Newtronics Novelties P & H Polytronics Radio Bookstop Reyco Ritco S.E.G. Sales Signal Radio Skylane Slep Space Electronics Space Raider Subscribe to 73 or else TAB Tapetone Technical Material Corporation Telrex Texas Crystals Texonic Topaz U. S. #1 Vanguard Waber Western Radio (Nebraska) Western Radio (San Diego) World Radio Labs W5GOS US MAP 73 Back Issues 73 Binders	53 er IV 35 11 47-50 63 92 94 89 75 85 90 82 80 95 57 17 55 77 91 67 93 25 28 90 75 45 75 94 97 97 97 97 97 97 97 97 97 97 97 97 97
Miller National Radio	53 er 35 11 47-50 63 92 94 89 75 80 95 57 17 55 77 91 67 92 94 95 75 75 77 91 75 75 75 75 75 75 75 75 75 75 75 75 75
Miller National Radio Newtronics Novelties P & H Polytronics Radio Bookstop Reyco Ritco S.E.G. Sales Signal Radio Skylane Slep Space Electronics Space Raider Subscribe to 73 or else TAB Tapetone Technical Material Corporation Telrex Texas Crystals Texonic Topaz U. S. #1 Vanguard Waber Western Radio (Nebraska) Western Radio (San Diego) World Radio Labs W5GOS US MAP 73 Back Issues 73 Binders 73 Bound Volume 73 Index to Surplus	53 er 35 11 47-50 63 92 94 89 75 80 95 57 17 55 77 91 67 93 25 28 90 75 75 75 92 94 75 75 75 75 75 75 75 75 75 75 75 75 75
Miller National Radio Newtronics Novelties P & H Polytronics Radio Bookstop Reyco Ritco S.E.G. Sales Signal Radio Skylane Slep Space Electronics Space Raider Subscribe to 73 or else TAB Tapetone Technical Material Corporation Telrex Texas Crystals Texonic Topaz U. S. #1 Vanguard Waber Western Radio (Nebraska) Western Radio (San Diego) World Radio Labs W5GOS US MAP 73 Back Issues 73 Binders 73 Bound Volume 73 Index to Surplus 73 Ham-TV	53 er 35 11 47-50 63 92 94 89 75 80 95 57 17 55 77 91 67 92 94 95 75 75 97 97 97 97 97 97 97 97 97 97 97 97 97
Miller National Radio Newtronics Novelties P & H Polytronics Radio Bookstop Reyco Ritco S.E.G. Sales Signal Radio Skylane Slep Space Electronics Space Raider Subscribe to 73 or else TAB Tapetone Technical Material Corporation Telrex Texas Crystals Texonic Topaz U. S. #1 Vanguard Waber Western Radio (Nebraska) Western Radio (San Diego) World Radio Labs W5GOS US MAP 73 Back Issues 73 Binders 73 Bound Volume 73 Index to Surplus 73 Ham-RTTY 73 Ham-RTTY	53 er 35 11 47-50 63 92 94 89 75 80 95 77 91 67 92 93 95 75 97 97 97 97 97 97 97 97 97 97 97 97 97
Miller National Radio Newtronics Novelties P & H Polytronics Radio Bookstop Reyco Ritco S.E.G. Sales Signal Radio Skylane Slep Space Electronics Space Raider Subscribe to 73 or else TAB Tapetone Technical Material Corporation Telrex Texas Crystals Texonic Topaz U. S. #1 Vanguard Waber Western Radio (Nebraska) Western Radio (San Diego) World Radio Labs W5GOS US MAP 73 Back Issues 73 Binders 73 Bound Volume 73 Index to Surplus 73 Ham-RTTY 73 Subscriptions	53 er 35 11 47-50 63 92 94 89 75 80 95 77 91 67 93 25 80 95 75 77 91 75 75 92 93 84 80 80 80 75 80 80 80 80 80 80 80 80 80 80 80 80 80
Miller National Radio Newtronics Novelties P & H Polytronics Radio Bookstop Reyco Ritco S.E.G. Sales Signal Radio Skylane Slep Space Electronics Space Raider Subscribe to 73 or else TAB Tapetone Technical Material Corporation Telrex Texas Crystals Texonic Topaz U. S. #1 Vanguard Waber Western Radio (Nebraska) Western Radio (San Diego) World Radio Labs W5GOS US MAP 73 Back Issues 73 Binders 73 Bound Volume 73 Index to Surplus 73 Ham-RTTY 73 Subscriptions	53 er 35 11 47-50 63 92 94 89 75 80 95 77 91 67 93 25 80 95 75 77 91 75 75 92 93 84 80 80 80 75 80 80 80 80 80 80 80 80 80 80 80 80 80
Miller National Radio Newtronics Novelties P & H Polytronics Radio Bookstop Reyco Ritco S.E.G. Sales Signal Radio Skylane Slep Space Electronics Space Raider Subscribe to 73 or else TAB Tapetone Technical Material Corporation Telrex Texas Crystals Texonic Topaz U. S. #1 Vanguard Waber Western Radio (Nebraska) Western Radio (San Diego) World Radio Labs W5GOS US MAP 73 Back Issues 73 Binders 73 Bound Volume 73 Index to Surplus 73 Ham-RTTY 73 Ham-RTTY	53 er 35 11 47-50 63 92 94 89 75 80 95 77 91 67 93 25 80 95 75 77 91 75 75 92 93 84 80 80 80 75 80 80 80 80 80 80 80 80 80 80 80 80 80

BACK ISSUES 73

JANUARY 1961 - - \$5.00 All others - - - - 50c

While They Last.

73 • 1379 E. 15th • BROOKLYN 30 • N. Y.

"TAB" FOR THE BEST KITS!

Gtd! Octal Silicon-5U4G-Tube Replacement 1120 RMS 1600 Piv \$4 @ 2 for \$6; 4 for \$10

LO PRICED SILICON TUBE REPLACEMENTS WITH BUILT IN SURGE AND SERIES BALANCING PROTECTION

TYPE VRMS/PIV AMPS PRICE T866 5000/10400 0.3 \$4

1900/2800

T5R4

General Purpose - PNP - Computer RF, IF Amplifier-Oscillator-HiFi Logic-Servoamp-Power Supply Pulse Amplifler or High Current Sw Veb, Vce, Veb Approx. 40V 2N670 rated 300 Mw. 50¢ @, 10 for \$4 2N671 rate one watt 75¢ @. 10 for \$6

\$9

0.5


SILICO Operati	N POWER	DIODE S	
D.C.	200Piv	100Piv	300Plv
Amps.	140Rms	70Rms	210Rms
2	.55	.35	.80
3	1.25	.85	1.50
6	1.50	1.00	1.75
12 35 70	1.70 2.90	1.20 2.15	2.00 4.95
240	5.60 8.40	4.50 5.70	19.60
50Piv	150Piv	D.C.	400Piv
35Rms	105Rms	Amps	280Rms
.25	.45	2	1.00
.60	1.00	3	1.80
.70	1.25	6	2.00
.85	1.50	12	2.20
1.80	2.50	35	6.10
3.75	4.95	70	15.30
4.80	6.90	240	29.75

*Derate 20% for Battery or Capacitive Load or D.C. Blocking! *Stud mounted on Heat-sink

Kit Glass Diodes equiv. 1N34A, 46, 48, 51, 60, 64, 87, 105, 109, 147, 267, 268, 295, 12 for \$1, 100 for \$6,

Transistor Power CONVERTER 12VDC to 500VDC

up to 200MA 100 Watts; Tap at

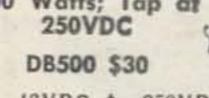

12VDC to 250VDC up to 150MA Type DB250 \$27

TWO 866A's and FILAMENT\$6



Factory Tested ***MFGRD in U.S.A. Replaces Medium and HiWattage Types (3 Amp) 2N155, 2N156, 2N234, 2N256, 2N307, 2N554

SPECIAL TO3GP 49¢ ea., 25 for \$10 \$10 or more this item we pay P.P./U.S.A.

Send 25¢ for New Catalog

THAT'S A BUY

"TAB" Tubes Factory Tested, Inspctd, Six Months Guaranteed! No Rejects! Boxed! GOVT & MFGRS Surplus! New & Used

	OAC W		New & Used
ı	OA289	6BZ7 1.25	I We Buy & Sell
l	0A380	6C4	43
Į	0 B265	6C569	45
	OC370	6C6 1.08	
	0D350	6C8 1.08	DIVEO + N
	0Z4	We Trade!	DVC0 3 15
	1A790	6CB689	LIVES DOL
l	IB3	6CD6 1.49	75
l	IL482	6CF685	HY75 5.00
l	IR45/\$1	6CL6 1.40	0217
l	We Swap		o/U Have? .95
ŀ	IR578	6CB689	
	18478	0000	4PR60A37.50
	18568	00350	4-125A27.50
	1T485	0000	4X150G15.00
	IT595	COLLA	4X250B41.00
	IU46/\$1	The second secon	4-400A 41.75
	10575	A	4E27A39.00
	1X299	PP4	250TL19.45
	2C39A Q	CP-	307A2/\$1
	2C40 5.50	CFC	316A5/\$1
			VR925/\$1
	2043 6.50	od 25¢ for Catal	
	2051 2.00	CFA	388A3/\$1
	2D2165	cue vo	350A 2.45
	2E22 1.75		350B 1.75
	2E24 1.90	***	371B95
	2E25 2.50	***************************************	5146 3.90
	2E26 2.75	A 2 W	
	2E30 Q		111111111111111111111111111111111111111
	2E35 1.60		450TH43.00
	2K25 9.75	P1/4	450TL43.00
			46011.50
	2K2634.00	es Stocked at Lou	
	2K2830.00	6K899	703A Q
		6L6 1.19	707B 3.50
	48. S. F. SE.	6SN772	715C10.90
		6T898	717A5/\$1
		6V6GT90	723AB 5.00
	3A5 1.00	6X549	725A 2.75
	3API 5.95	12AT659	803 3.50
	3BPI 3.99	12AT789	804 8.85
	3C24 3.50	12AU663	805 6.00
	3D23 3.95	12AU769	We Trade!
	We Buy!	We Sell!	W C TIMAG.
	3E29 6:00	12AX779	807 1.10
	304 68	12AV7 1 90	007 1.10

...... .68 | 12AY7 1.29 | 5/\$5, 10/\$12 3Q586 12B4 *****13.50 4-65A 12BA6 811 3.45 4-125A 27.50 12BA7 811A 4.41 4-250A34.00 12BD6 4X150A .. Q 12BE6 813 9.95 4X250 12BH636.00 815 4X50037.00 12BH7 2.95 826 12BY7 5API Wanted Test Sets and Equipment 12BZ7 7.95 12H6 *****

5BPI 828 9.00 5BP4 829B 8.00 5CPI 4.99 12J5 832A 6.00 ******* 5CP7 9.00 833A ... 36,00 1217 ******* 837 2/\$2 5R4 1218 1.35 1.00 866A ... 2.25 12K8 .90 .89 ***** 5U4 12SA7 .69 95410/\$1 ******* 5 V 4 12SC7 .89 955 3/\$1 ******* 5Y3 12SF569 957 3/\$12/\$1 958A 12SG7 Send 25¢ for Catalog! 15GP22 ..89.00 12SH7 9915/\$1 12SJ7 2.75 6A7 1.00 1614 12SK7 .7599 6AB 1619

.....5/\$1 .59 12SL7 6AB4 1620 2.00 *****3/\$1 12SN7 .69 1625 BAC7 ****** 12807 .69 16265/\$1 6AG5 .65 ****75 12SR7 1629 6AG7 6AK569 15E 20504/\$159 5517 1.25 GAL5 15R FG17 5608 Q 3.95 6AQ5 .66 Top \$\$\$ Paid for 304TL, 813, 811A, 812A Tubes 1.95 19T8 1.16 5618 3,25 6AR6 3.49 3.50 24G 5651 1.35 6AS7 25A6 1.192/\$1 5654 1.20 6AT6 25A7 2.19 5656 4.25 6AU6 25C581 5663 1.15 1.35 5670 25L690 6BA659 4.00 25T 1.7559 5686 6BE6 25Z572 5687 1.49 1.15 25Z6 569179 4.70 3.69 5725 26A7 Top \$33 Paid for XMTT R Tubes!

6BG6 **6BH6** 6BJ6 FG27 8.28 6BK7 5732 2.00 ... 1.35 H V 2719.39 6BL7 573685.00 28 D 7 5749 6BN4 1.95 1.08 FG3315.00 5750 6BN6 EL34 3.49 5751 **6BN7** 1.99 1.25 35A569 1.20 1.19 5814 6BQ6 35L659 5879 6BQ7 1.11 4.49 35T 6BX7 5894\$12.00 35Z5 1.25 1.19 6BY5 2.99

RK39

6BZ691

TERMS: Min Order \$3-25% with order F.O.B. New York. day guarantee, price of mdse. only. Our 18th year.

No See-Write

Prices shown are subject to change. 111D Liberty St., N. Y. 6, N. Y. RE 2-6245

'TAB FOR TRANSISTORS & DIODES!" Full Lath Leads Factory Tested & Gtd1



PNP Hi Power 15 Amp, T03 Diamond & T036 Round Pkg. 2N441, 2N277 \$1.25 @ 10 for \$11

2N442, 2N278 \$30, 4 for \$10 2N443, 2N174 \$40, 4 for \$14 USA Mfg. 2N677 \$10, 12 for \$10; T03 2N677A \$20, 6 for \$10; T03 2N677B \$30. 4 for \$10; T03 2N677C \$50, 2 for \$8; T03 \$10 or More. This Item Postpaid U.S.A.!

RND(T036), or Diamond (T03) mica kit 30¢ ea. Power Heat Sink Finned (80" sq.) \$1.39.

SELENIUM F.W. BRIDGE RECTIFIERS 18VAC 36VAC 72VAC 130VAC 28VDC 54VDC 100 V D C 14VDC \$1.00 \$5.00 \$1.90 \$3.85 1.30 2.00 4.90 8.15 11.10 2.15 6.25 3.00 8.60 13.45 2.90 4.00 31.90 4.15 18.75 8.00 10 26.30 41.60 6.10 12.15 38.95 43.45 7.75 14.90 20 12.85 24.60 Write For 24 Rectifier Catalog 15.00 29.45

D.C. POWER SUPPLY 115V/60 to 800 Cys. Input 330 and 165 VDC up to 150 MA. Cased! SPECIAL \$5.

2N123 PNP 45¢, 12 for \$5, 100/\$37 2N292 NPN 45¢, 12 for \$5, 100/\$37 2N293 NIN 45¢. 12 for \$5, 100/\$37 2N223 PNP 80¢ 100/\$65 2N597 PNP \$1.93 6/\$10 2N598 PNP \$1.90 6/\$10 2N599 PNP \$3.50 3/\$10 \$10 or More. This item Postpaid U.S.A.

ZENER DIODES 150 to 400 MW cased TO24 Pekg. Kit ZENER DI-ODES up to 400 MW. Single and double ended 2 for \$1. Within 20% V'Range \$1 @; 3 for \$2.

"TAB" SILICON 750MA" DIODES Factory Tested Gtd.!

NEWEST TYPE! LOW LEAKAGE D.C. or Batty. Derate 20%

rms/plv rms/piv rms/plv rms/plv 210/300 70/100 140/200 35/50 .31 .22 .17 .09 rms/plv rms/piv rms/piv rms/piv 490/700 350/500 420/600 280/400 .77 .63 .38 .50 rms/plv rms/piv rms/piv rms/plv 630/900 700/1000 770/1100 560/800 .98 1.08 1.35 .83

Low Priced T300 Silicon Diodes Rated 400 pvi/280rms @300Ma @100°C .25 each; 30 for \$7; 100 for \$22; 50 for \$100; 100 for \$180

Diode order \$10 shipped Post free

"SUPERIOR" Powerstat Type 10 165W to 132V \$6 each; 2 for \$10

NEW BATTERY CHARGER BC6-12V FOR 6V OR 12VOLT BATTERIES, TRICKLE & FULL CHARGE up to 10 AMPS



Built BC6-12V10. Price Complete \$14. Leece Neville Charger Systems Sealed Silicon Stud Rectifier

Finned Stack, Direct Replacement FOR 6 or 12VDC @ 100A, Type YJ9 \$18

"TAB" BARGAINS

866A Xfmr 2.5V/10A/10KV Insl....\$3.95 Microswitch R1/SPNC/30A \$.49 @, 3 for \$1 Tube Clamps Birtcher 5 for \$1 .012 at 25Kv CD Condenser \$4@, 3 for \$10 WE Choke 4Hy/450Ma/270hms \$4@

Line Filter 50A/250VAC \$10@, 2 for \$18 Line Filter 200A/130VAC \$18@, 2 for \$30 Bruning Parallel 6" Rule \$.69@, 2 for \$1 KS15138 Linear Sawtooth Pot 2 for \$1 "CTC" Delay Line 1 Mese'd \$1@, 3 for \$2 Vacuum Conders 50Mmfd/7.5Kv \$3@ 4 for \$10

We buy! Swap & Sell Semiconductors Wanted Transistors, Diodes, Zeners!

ONLY AT SI ALLIED

Hy-Gain

TH-3

smash-value SIGNAL BOOSTER
DX BONUS PACKAGE!

SAVE \$80

WHAT A BUY!

GONSET GSB-201 LINEAR AMPLIFIER, Reg. \$419.50

HY-GAIN TH-3 3-ELEMENT
TRI-BAND BEAM, Reg...\$ 99.75
Regular Price..\$519.25

ALLIED SPECIAL BONUS \$
PACKAGE PRICE, ONLY

\$439²⁵

NO MONEY DOWN



GIVE YOUR SIGNAL A REAL SEND-OFF WITH THE GONSET LINEAR AND HY-GAIN TRIBAND-ER FOR 10/15/20! Big news for Ham value hunters—save \$80 on this DX-getting combination! Popular GSB-201 Linear operates at 1500 watts on SSB, 1000 watts CW, and 400 watts AM. Can be driven by any 60-150 watt exciter. Bandswitched coverage of 10, 15, 20, 40 and 80 meters with pi-net output. Panel meter reads plate current or relative RF output. Antenna relay and bias supply built in.

Exclusive ALLIED Pre-Spring Specials on New and Reconditioned Equipment

QUANTITIES LIMITED ... ALL ITEMS SUBJECT TO PRIOR SALE—ORDER NOW!

Pierson KE-93 Mobile Receiver

w/6-12 v DC Supply. Only \$159.00

w/AC Supply. Only \$159.00

Elmac PMR-6 Mobile Receiver.
Only......\$65.00

Elmac PMR-7 Mobile Receiver.
Only......\$109.00

Elmac PMR-8 Mobile Receiver.
Only......\$139.50

Hallicrafters HT-31 500-Watt Linear. A real buy for SSB/AM or CW.
Only.....\$149.00

Hallicrafters HT-32 SSB/Exciter

/Transmitter. Only......\$379.00

price, only......\$24.95

NO MONEY DOWN. Allied Credit Fund Plan gives you bigger buying power.

15-DAY FREE TRIAL on equipment 90-DAY NEW GEAR WARRANTY KING-SIZE TRADES AVAILABLE!

If you don't have this 1962 Catalog, send for it



order ALLIED RADIO

ALLIED RADIO, Dept. 221-02 100 N. Western Ave., Chicago	IUDAI
Ship me the following	
\$enclosed (or buy on our N	Io Money Down Credit Fund)
Name	To Money Down Credit Fund)
Address	
City	ZoneState



Here's the VHF Receiver you've dreamed of—CLEGG'S new INTERCEPTOR for 6 & 2!

Clegg's new Interceptor Receiver for 6 & 2 meters introduces revolutionary new concepts in VHF receiving techniques. Now you can realize the benefits of engineering features that are years ahead of their time!

Just imagine, for example, a receiver so free of cross modulation, images and noise, and so sensitive that it's possible to work duplex (on antennas separated by no less than 60') with stations transmitting within 25 kc of your own frequency. Imagine, too, tuning in SSB with the ease of amplitude modulation . . . selecting any CW signal from the "pile-up" at will.

Take a look at all of the advantages you get with this great new receiver:

- * Virtually no cross modulation.
- ★ Maximum rejection of spurious signals and responses.
- ★ Nuvistor RF stages that give minimum noise figures on both 6 & 2 meters.
- ★ Stability equal to exacting requirements of SSB and CW.
- ★ Hermetically sealed 10.7 Mc crystal lattice filter that provides optimum selectivity for both AM and SSB. Selectivity 3.1 kc at 6 db points; 8 kc at 75 db points.

- * Sensitivity of better than .1 microvolt.
- ★ Frequency tuning accuracy of less than 3 kc in calibrated 1 Mc ranges.

And that isn't all! Here are some other great Interceptor features — ones that will help make your station second to none:

- ★ Input provision for 220 Mc, 432 and other UHF converters.
- ★ A slide rule dial with full electrical band-spread and flywheel loaded, no backlash tuning makes it easy to separate the weak ones.
- ★ Maximum hash suppression with specially designed noise limiter.
- ★ Output terminal for Pan-adapter and monitoring scope.
- ★ Tuning meter calibrated in both S units and db above reference.
- ★ Cabinet and panel matching the Zeus transmitter.

No doubt about it — if you are a serious operator on 6 & 2, don't wait!— see the Interceptor at your Clegg dealer's today. Or write for complete information!

Amateur Net Price: \$473.

Clegg LABORATORIES

OAkwood 7-6800.

504 ROUTE 53, MT. TABOR, NEW JERSEY

On the lab bench and in the field . . . NATIONAL NG-270 provides exceptional stability . . . sensitivity!


National's NC-270 proves itself the *only* way — in actual performance on the lab bench and under adverse operating conditions in the field. CQ and QST experts gave the NC-270 truly remarkable reviews. Of equal importance — letters from amateurs all over the world cite astounding performance under almost unbelievable receiving conditions.

FROM QST - JANUARY 1961

"Stability, both mechanical and electrical, is exceptional . . . The NC-270 works well enough on 50 Mc. to encourage a v.h.f. enthusiast to design his converters . . . so that they will work into the 6-meter range rather than into the lower bands. This would give him full coverage of the 144-Mc. band and a four-megacycle spread in any of the bands from 220 Mc. up . . , and he can skip the construction of a 50-Mc. job. The NC-270 should do all he'll need in that range."

FROM CQ - MAY 1961.

"... retains all the "feel" of the more expensive receivers for which this company is known... It is unusual to see a front panel NOTCH DEPTH control in this price class... The a.n.l. circuit in the NC-270 is exceptionally good... Mechanical stability is impressive. It is possible to tune a s.s.b. signal on one of the high frequency bands, lift the front of the receiver up several inches and let go. Unless the main tuning knob moves, the signal will still be there... (The National NC-270) is an extremely stable and sensitive receiver..."

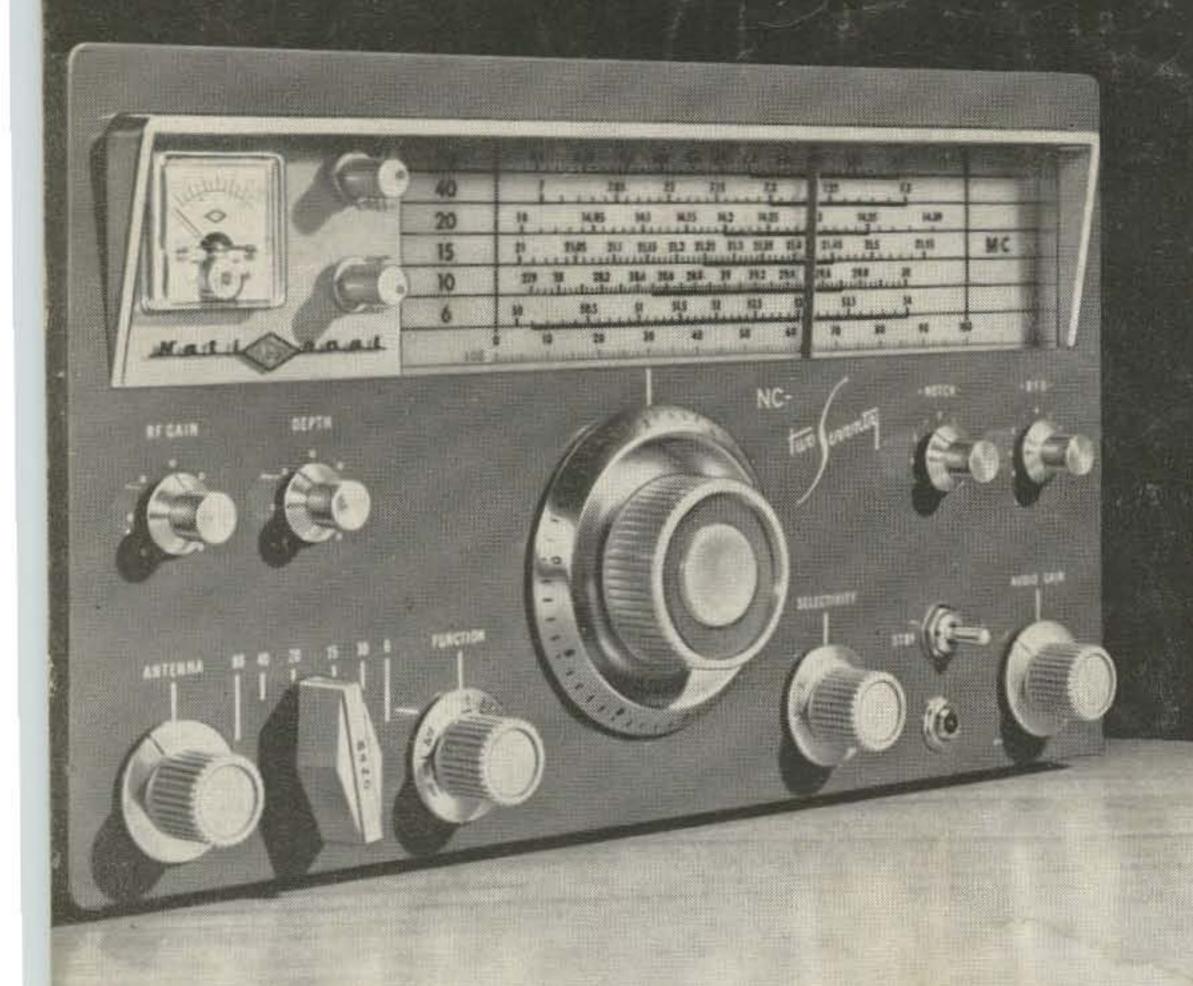



BRUCE W. BUTLER W5PXN/5 CITES OUTSTANDING 270 PERFORMANCE DURING HURRICANE CARLA

"I would like to congratulate you on one of the finest communications receivers on the market; the NC-270. (At RACES center during hurricane Carla) communications were maintained with schools and hospitals . . . Your receivers performed for over 60 hours. The thing that impressed me most was its extreme stability under the most adverse conditions. Emergency power and, at best, poor antennas did not help our situation, nor the 70 mph winds which blow at the airport where we were set up. The selectivity of the NC-270 helped to maintain contact with other stations with low power and bad antennas. On 6 meters, we rarely needed a relay and when this did happen it was due to their receiving conditions, not ours . . performed like a high priced receiver..."

If you want a proven medium priced receiver, we strongly suggest that you hear the NC-270 at your dealer's. Write today for technical information.



National Radio Company, Inc. Melrose 76, Mass. A Wholly Owned Subsidiary of National Company, Inc.

Export: Ad Auriema Inc., 85 Broad St., N.Y.C.

Canada: Tri-Tel Assoc., 81 Sheppard Ave. W.,

Willowdale, Ontario

Rush me	free,	com	plete	informa
tion on the	e Nati	ional	NC-27	70.

Name.....

City.....State....

Address.

If you would like a copy of National's 270 instruction manual enclose 25¢. 73-03

\$279.95 — Slightly higher west of Rockies and outside USA.