December 1982 \$2.49 1/2 Issue #267

## **Amateur Radio's Technical Journal**

A Wayne Green Publication

W2XO

84

90

101

108

116

122

### **11 New** Projects To Build!

Simple **One-Tube** Receiver Page 64

### Improved **K2OAW IDer** Page 51

Unbelievable **Dropped Array** Page 10

### \$9 Signal Generator Page 116

Detailed **1982 Index** Page 156



#### Shack from Scratch 2-Meter Collinear Building a ham shack in a new home Make your tower do double duty. can be a breeze. Just plan ahead. Drop this array from the top and get 6-dB gain 10 W1GV/4 Winning the Coax War The electrical length of feedline de-**Deep-Six Squelch Tails** Kerchunks take a dive with the addition of this audio delay. 14 WA2NYF **Build Yourself** A Paralyzed Beam Go from east to west in less than a second with this 2-meter array. And put your rotator out to 24 WB2WIK Taming the 2-Meter Linear It lives in the forest of spurious oscillations and answers to the call of the correct bias. Catch one for 28 VE3LMP N The Frugal Floppy Bazooka This 2-meter antenna coils up into a small package, but it shoots a 32 straight signal. N7BGZ **Taking It Higher** Raising a repeater's antenna is the way to wider coverage, right? Wrong. help W4MLF 36 **Dial-A-Frequency** Let your fingers do the walking with this remote control. All you need is a spare telephone. **K1WGN** 44 Improving God's IDer Put more flexibility in the K2OAW circuit-and save the advantages of the original 51 K9XI The Bunesti Caper The two British agents needed a power amp-fast. Could the American ham W9PIF 56 The Tube Returns Move over, ICs. This receiver is easy to build, cheap, and works 64 like a dream W1BG The Program That Knows It All Repeater info, third-party agree-

10 ments, you name it-this TRS-80 BASIC program knows it.

#### W8XW

72

76

#### **Berserk Direction-Finding**

The Hangman's

pasture.

yourself

huild one?

Zero in on transmitters in seconds with this TRS-80 program. It will tell you how to get there, too WD8CBF

pends on its velocity factor. Don't get caught short . W9PIF Red-Hot and Ready to Go Anyone who has ever soldered knows that the cord gets in the way. Find freedom with this homebrew cordless iron. W7RXV **Cutting Current to Size** Measuring large ac currents can be difficult unless you know a trick or two. W7CRY explains how. W7CRY Construct This All-American Audio Signal Generator The perfect project for starting a test bench or rounding one out. WA2SUT Maximum Modulation for CB Conversions Many CB rigs lack the gain for full modulation. This preamp will AIØP



One-Tube Receiver-64

Never Say Die-6	Corrections-144
Reader Service-130	Review-148
Circuits—	Contests-150
132, 139, 153	1982
Ham Help-133, 134,	Index—156
144, 160, 170, 171, 186	Awards—166
Social Events-133	DX—170
RTTY Loop—134	Satellites — 171
Fun!—135	Propagation—193
Letters-136	Dealer
New Products-140	Directory-193

The Commercial Grade Communications Receiver that everyone has been asking for ...... at a price you can afford!

IC-R7



#### GENERAL COVERAGE RECEPTION AT ITS BEST

Listen to the world of HF with the R70, a 100KHz to 30MHz commercial grade receiver designed by ICOM Incorporated, the leader in advanced receiver design. Built from knowledge gained by designing receivers for commercial, marine, and amateur use, the R70 surpasses other receivers on the market...even receivers costing more than twice as much.

Utilizing ICOM's DFM (Direct Feed Mixer), the R70 is a receiver which in normal usage is virtually immune to intermodulation distortion or cross modulation, yet still maintains superior sensitivity. Whether you are a SWL (short wave listener), Ham (amateur radio operator), maritime operator or commercial user, the R70 provides the features you need.

#### DESIGN

The R70 incorporates an UP conversion system, utilizing a direct feed mixer proven to be the best design for minimizing interference from strong adjacent signals. A preamp is provided for making the weakest of signals readable. High grade filters in conjunction with the built-in PBT (pass band tuning) system and notch filter, provide the ultimate in interference rejection. Selectable AGC (fast/slow/off), noise blanker (wide or narrow), and tone control improve readability under the worst conditions. An AGC derived squelch, operative in all modes, adds to operating ease.

Dual VFO's with three tuning rates provide quick QSY (frequency change), memory for an important station, or by equalizing the VFO's (A=B), a digital RIT. 13.8 VDC operation is provided as an option, 117 VAC is standard.

#### HAM' ING

The R70 is an ideal general coverage receiver to complement any ham shack. Use it with your existing transmitter or transceiver to provide dual receiver capability.

The R70's built-in monitor system lets you listen to your own transmitted audio and a mute input automatically protects the R70's receiver from your signal.

An option for FM allows listening to the 10 meter FM activity.

As an additional plus to ICOM IC-720A owners, the R70 has an optional interface that will allow the R70 to control the transmit frequency of the 720A for the ultimate in hamming versatility.

#### **SWL'ING**

For the short wave listener, the readout section of the R70 gives all the information for logging a station to be returned to at a later time. Frequency, mode, VFO, signal strength are all displayed. A dial lock prevents accidental loss of a signal.

A front mounted speaker provides 3 watts of crisp clear audio. A record jack allows easy attachment of a tape recorder.

#### **ICOM SYSTEM**

Like all ICOM HF products, the R70 fits into the ICOM system concept of accessories allowing you to use previously purchased accessories such as the HP1 headphone, SP3 external speaker, and AH1 auto bandswitching antenna.

#### PRICE

Check with your local ICOM dealer for pricing on the R70. You will be amazed.



ICOM America, Inc., 2112-116th Ave NE, Bellevue, WA 98004 (206)454-8155/3331 Towerwood Drive, Suite 307, Dallas, TX 75234 (214)620-2780. All stated specifications are approximate and subject to change without notice or abligation. All ICOM radios significantly exceed FCC regulations limiting spurious emissions.

## **5-STORE BUYING POWER** in action!



Prices, specifications, descriptions subject to change without notice. Calif. residents please add sales tax

#### SWR & Power Meter



- The most advanced automatic computing RF measuring instrument in amateur radio.
- Logarithmic SWR scale.
- Power ranges 20/200/2000 watts.
- Frequency range 1-30 MHz.

Automatic. No "set" or "sensitivity" control. Computer sets full scale so SWR reading is always right. Complete hands-off operation.

Light bar display. Gives instant response so you can see SSB power peaks. Much faster than old-fashioned panel meters. Baton switch selects three power ranges.

Logarithmic SWR display. Computer expands the display where you need it so it's easier to see, easy to use.

Computer operated. Now an analog computing circuit and digital comparator automatically compute SWR regardless of power level. Frees you from checking zero, setting a "sensitivity" knob and from squinting at old-fashioned cross pointer mechanical meters. With this new meter computing is done electronically and displayed with moving light bars. Individual bars for SWR and power.

Model M-827 Automatic SWR & Power Meter \$119.95 in the U.S. and Canada. Add \$3 shipping/handling. California residents add sales tax.



#### **ORDER YOURS NOW!**

VISA

Send for FREE catalog describing the SWR & Power Meter and our complete line of Noise Bridges, Preamplifiers, Toroids, Baluns, Tuners, VLF Converters, Loop Antennas and Keyers.

### Palomar Engineers

1924-F West Mission Rd. Escondido, CA 92025 Phone: (619) 747-3343



### INFO

#### Manuscripts

Contributions in the form of manuscripts with drawings and/or photographs are welcome and will be considered for possible publication. We can assume no responsibility for loss or damage to any material. Please enclose a stamped, self-addressed envelope with each submission. Payment for the use of any unsolicited material will be made upon acceptance. All contributions should be directed to the 73 editorial offices. "How to Write for 73" guidelines are available upon request.

#### Editorial Offices:

Pine Street Peterborough NH 03458 Phone: 603-924-9471

#### Advertising Offices:

Elm Street Peterborough NH 03458 Phone: 603-924-7138

#### **Circulation Offices:**

Elm Street Peterborough NH 03458 Phone: 603-924-9471

#### Subscription Rates

In the United States and Possessions: One Year (12 issues) \$25.00 Two Years (24 issues) \$38.00 Three Years (36 issues) \$53.00

#### Elsewhere:

Canada and Mexico-\$27.97/1 year only, U.S. funds. Foreign surface mail-\$44.97/1 year only, U.S. funds drawn on U.S. bank. Foreign air mail-please inquire.

#### To subscribe, renew or change an address:

Write to 73, Subscription Department, PO Box 931, Farmingdale NY 11737. For renewals and changes of address, include the address label from your most recent Issue of 73. For gift subscriptions, include your name and address as well as those of gift recipients.

#### Subscription problem or question:

Write to 73, Subscription Department, PO Box 931, Farmingdale NY 11737. Please include an address label.

73: Amateur Radio's Technical Journal (ISSN 0745-080X) is published monthly by 73, Inc., a subsidiary of Wayne Green, inc., 80 Pine Street, Peterborough NH 03458. Second class postage paid at Peterborough NH 03458 and at additional mailing offices. Entire contents copyright© 1982, Wayne Green, Inc. All rights reserved. No part of this publication may be reprinted or otherwise reproduced without written permission from the publisher. Microfilm Edition—University Microfilm, Ann Arbor MI 48106. Postmaster: Send address changes to 73, Subscription Services, PO Box 931, Farmingdale NY 11737. if IPansee

### NEW DIMENSION IN PERFORMA • U.S. Made • Competitive Price • All Solid State • 12V DC • SWR Protected •

• Broadband • No Tune Up • Full Break-in CW • 150 Watts PEP, SSB or CW Input • • High Dynamic Range • Excellent Sensitivity/Selectivity • Digital Readout • • 160-10 Meters Plus WARC Bands and MARS Coverage\*•

Front panel switching allows independent MODE and optional crystal filter selection.

A passive double balanced mixer is employed in the receiver front end. This stage is preceeded by a low noise high dynamic range bipolar rf amplifier to provide good, strong signal performance and weak signal sensitivity.

Accurate digital readout of operating carrier frequency is displayed to 100 Hz.

A rugged, solid-state PA provides continuous duty in SSB and CW modes. A cooling fan (FA7) is available for more deman-ding duty cycles, such as SSTV or RTTY. The PA also features very low harmonic and spurious output.

DRAKE

VOX GAIN, VOX DELAY, VOX disable, QSK, selectable AGC time constants, RIT and noise blanker selection are front panel controlled for ease of operation.

The TR5 is designed with modular construction techniques for easy accessibility and service.

#### GENERAL

Frequency Coverage: 1.8-2.0\*, 3.5-4.0, 7.0-7.5, 10.0-10.5, 14.0-14.5, 18.0-18.5\*, 21.0-21.5, 24.5-25.0\*, 28.0-28.5\*, 28.5-29.0, 29.0-29.7\* MHz. (\*With accessory range crystal).

Modes of Operation: Usb, Lsb, Cw.

Frequency Stability: Less than 1 kHz drift first hour. Less than 150 Hz per hour drift after first hour. Less than 100 Hz change for a ± 10% line voltage change.

Readout Accuracy: ± 10 ppm ± 100 Hz. Power Requirements: 13.6 V-dc regulated, 2 A. 12 to 16 V-dc unregulated, 0.8 V rms maximum ripple, 15 A. **Dimensions:** 

Depth: 12.5 in (31.75 cm), excluding knobs and connectors. Width: 13.6 in. (34.6 cm). Height: 4.6 in. (11.7 cm) excluding feet. Weight: 14 lb. (6.35 kg)

Power Input (Nominal): 150 Watts, PEP or Cw. Load Impedance: 50 ohms. Spurious and Harmonic Output: Greater than 40

TRANSMITTER

dB down Intermodulation Distortion: Greater than 30 dB

below PEP Carrier Suppression: Greater than 50 dB.

Undesired Sideband Suppression: Greater than 60 dB at 1 kHz.

**Duty Cycle:** 

Ssb, Cw: 100%. Lock Key (w/o FA7 Fan): 30%, 5 minutes maximum transmit.

Lock Key (w/FA7 Fan): 100%.

Microphone Input: High Impedance. Cw Keying: Instantaneous full break-in, adjustable delay.

#### ACCESSORIES AVAILABLE

Model 7021 SL300 CW Filter Model 7022 SL500 CW Filter Model 7027 SL1000 RTTY Filter Model 7023 SL1800 RTTY Filter

**R.L. DRAKE COMPANY** 

Model 7026 SL4000 AM Filter Model 7024 SL6000 AM Filter Model 1570 PS75 AC Power Supply Model 1545 RV75 Synthesized Remote VFO

DRAKE

RECEIVER

Sensitivity: Less than 0.5 uV for 10 dB S + N/N except less than 1.0 uV, 1.8-2.0 MHz.

SPECIAL ANNIVERSALV IN UUSINESS STAD OS SARY PRICE

Selectivity: 2.3 kHz minimum at -6 dB. 4.1 kHz maximum at - 60 dB (1.8:1 shape factor).

Ultimate Selectivity: Greater than -95 dB.

Age: Less than 5 dB output variation for 100 dB input signal change, referenced to agc threshold.

Intermodulation: (20 kHz or greater spacing) In-tercept Point: Greater than 0 dBm. Two-Tone Dynamic Range: Greater than 85 dB.

I-f Frequency: 5.645 MHz.

Model 1531 MS7 Speaker

Model 1507 CW75 Keyer

Model 7077 Microphone

Model 1558 NB5 Noise Blanker

I-f Rejection: 50 dB, minimum,

Image Rejection: 60 dB, minimum below 14 MHz. 50 dB, minimum above 14 MHz.

Audio Output: 2 watts, minimum @ less than 10% THD (4 ohm load)

Spurious Response: Greater than 60 dB down.

540 Richard St., Miamisburg, Ohlo 45342. USA Phone: (513) 866-2421 • Telex: 288-017



### W2NSD/1 NEVER SAY DIE editorial by Wayne Green

#### SHOULD DXCC BE PROHIBITED?

The blatant arrogance of the PY0SB DXpedition shook the amateur bands, bringing on wild attacks of jamming In retaliation. Frankly, after trying to use the twenty-meter band for an hour, I didn't blame the jammers much. Not since Don Miller have I heard such a total disregard for the hobby.

This was, in my estimation, amateur radio at its worst. Those refugees from CB set up on one of the most rare spots in the world and then, transmitting outside of the American phone band, asked US hams to call them anywhere from 14,200 to 14,300. This went on, totally killing the band for any other use as thousands of stations called steadily, hour after hour. There was no possible way to make a normal contact anywhere in that entire band while this was going on.

This is totally unnecessary, as anyone with even a small amount of DXing experience knows. It is arrogant. It is a shameless flaunting of the power of one group to bring the whole band to a halt. It isn't even a fast way of making contacts. There is not even a remote excuse for such a display.

I've operated from some fairly remote spots and have faced as big pileups as anyone. I got started in seriously working DX in late 1945, the day our first DX band opened after the war. When I moved to New Hampshire, I started all over again, working 100 countrles in the first week on twenty phone, 200 in the first month, and 300 in the first year. So I know the receiving end of the stick.

In 1958, I went on my first serious DXpedition ... KC4AF, Navassa Island, Since then, I've operated from a bunch of places...come to mind 5Z4. ZS6, 3D6, 7P8, OD5, YK1, YA1, VU, 9N1, HL6, VR2, 5W1, KS6, FO8, HH, JY, OH0, KH2, KW6. and a bunch of non-rare countries. I've tried every way known to ham to get the most contacts per hour on the air from these rare places, so I have a good idea of what works and what does not work. Hmmm, I forgot to mention VP5, J6, and a revisit to Navassa in 1972.

The results of all this? Well, unless your signal is particularly weak, the fastest operation is when you operate on a fixed

#### HAM BILL SIGNED

It began as S.929, turned into H.R.5008, and came out of the Washington mill as H.R.3239, but the effect is the same: sweeping changes in amateur radio.

The bill, which has been signed by President Reagan, will give hams more control over licensing and policing and may also expand the 5-year ticket into a license renewable every 10 years.

With this moneysaving measure, FCC-approved hams and ham organizations will be both writing and administering exams. However, the exams may be written only by a ham with at least the class license that the exam is for, and tests can be given only by hams with a higher-class license. Extras, of course, will be allowed to test Extras.

Amateur radio's traditional self-policing policies have also been given a shot in the arm by the bill. The FCC can now use hams to track down illegal transmissions and accept reports on illegal activities which have been filed by hams. This bill gives the FCC permission to "recruit and train" hams for this purpose, and these amateurs will also be allowed to send warning notices to offenders. However, the amendment does not give hams authority to officially charge violators.

The self-regulatory aspect of the bill is the brainchild of Sen. Barry Goldwater K7UGA, who drafted the initial version as S.929. But to get it enacted, the concepts of S.929 were incorporated into a larger house bill, H.R.5008, which addresses a wide variety of changes in the Communications Act of 1934.

Hams plagued by RFI will find some respite under this bill, which will "establish minimum performance standards for home electronic equipment and systems to reduce their susceptibility to interference from radio frequency energy." However, the bill does not affect equipment already manufactured.

Other changes in the Communications Act eliminate licenses for CBers and radio control operators. Though CB operators will still be expected to comply with regulations, the change allows the Commission to officially wash its hands of the 27-MHz band.—WB8JLG.

channel, thus containing the band mayhem to one single pileup, I've found that out by making regular announcements to this effect: "I will be listening for about ten seconds on this channel for the last letter of your call. Please do not all jump in immediately, but wait so your calls will be spaced a bit. I will make a note of the last letter of your call and call you with it after writing down as many as I can hear. Do not...l repeat...do not call more than a couple of times. If I hear anyone pushing and shoving on channel I will work you, but there will be no QSL. Neither of us wants that."

The result is a relatively orderly sorting out of the problem, which is to get the call letters of those on channel as quickly as possible. The rest of the contact is a matter of a couple of seconds. The long, hard part is getting the calls through.

By asking for the last letter, I am able to quickly get things down to two or three, at most, responding when I break. It makes everyone shut up and listen. I can then confirm the call, exchange signals, and be on to the next. With this system, I can double or triple the throughput of any system which calls for tuning a band of frequencies, looking for calls in the open.

The calling stations, perceiving that I am able to cope with the chaos and that they will have a fair chance of getting through, respond very positively and line up, doing as I ask. Megawatts of power are saved. The entire band, except for about 6 kHz which I am using, is open for everyone...and at least twice as many operators are made happy with a new one. And think of the agonizing frustration saved for the thousands of ops, calling hour after hour, hoping to get through.

Another solution to the whole problem would be, of course, to get the League to cancel their Honor Roll and DXCC certificates so we wouldn't have this enormous pressure to make a radio contact with some stupid island somewhere. That would spoil a lot of fun for thousands of us DXers, but it would at least stop such carnage as the Peter and Paul jokers dumped on us.

This whole DX thing, while it may be fun for amateurs in most of the ordinary countries, is a royal pain in the...er...ear for the ham who lives in a rare spot.

## "Comm-packed."

### **BIG performance...** small size ... smaller price!!!

The TR-2500 is a compact 2 meter FM handheld transceiver featuring an LCD readout, 10 channel memory, lithium battery memory back-up, memory scan, programmable automatic band-scan, Hi/Lo power switch and built-in sub-tone encoder.

#### TR-2500 FEATURES:

· Extremely compact size and light weight

Measures 66 (2-5/8) W x 168 (6-5/8) H x 40 (1-5/8) D, mm (inches). Weighs 540 grams (1.2 lbs) with Ni-Cd pack.

- · LCD digital frequency readout Shows frequencies and memory channels, four "Arrow" indicators.
- · Ten channel memory Nine memories for simplex or ±600 kHz offset. "M0" memory for nonstandard split frequency repeaters.
- · Lithium battery memory back-up (Estimated 5 year life.) Maintains memory when Ni-Cd pack is fully discharged or removed



- HI/LOW power selection 2.5 watts or 300 mw.
- Memory scan Scans only channels in which frequency data is stored.
- · Programmable automatic band scan Upper and lower frequency limits and scan steps of 5-kHz and larger.
- UP/DOWN manual scan
- · Built-in tuneable sub-tone encoder Tuneable (variable resistor) to desired CTCSS tone
- · Built-in 16-key autopatch encoder "SLIDE-LOC" battery pack
- · Repeater reverse switch
- Keyboard frequency selection
- · Extended frequency coverage
- Covers 143.900 to 148.995 MHz in 5-kHz steps.
- Optional power source Using optional MS-1 mobile or ST-2 AC charger/power supply, radio may be operated while charging. (Automatic drop in connections.)



#### Actual size

- · High impact plastic case
- · Battery status indicator
- Two lock switches
- Prevent accidental frequency change and accidental transmission.
- Standard accessories include:
- · Flexible antenna with BNC connector
- · 400 mAH Ni-Cd battery pack · AC charger
- **Optional accessories:**
- ST-2 Base station power supply/ charger (approx. 1 hr.)
  MS-1 13.8 VDC mobile stand/charger/
- power supply

# **FR-3500**

000

.....

#### 70 CM FM Handheld

- · 440-449.995 MHz in 5-kHz steps
- TX OFFSET switch keyboard
- programmable ±5 kHz to ±9.995 MHz 1.5 W/300 mW HI/LOW power switch
- · Auto. squelch position on squelch control · Tone switch for TU-35B optional
- programmable CTCSS encoder
- · Other features include 10 memories, lithium battery memory back-up, programmable automatic band scan, memory scan, UP/DOWN manual scan, repeater reverse, 16-key autopatch, keyboard frequency selection, slide-lock battery.
- VB-2530 2-M 25 W RF power amp.. w/cables. mtg. brkt. (TR-2500 only)
- TU-1 Programmable CTCSS encoder (TR-2500 only)
- TU-35B Programmable CTCSS encoder (mounts inside TR-3500 only)
- PB-25 Extra 400 mAH Ni-Cd battery
- PB-25H Heavy-duty 490 mAH Ni-Cd battery
- DC-25 13.8 VDC adapter.
- BT-1 Battery case for manganese/ alkaline AA cells
- SMC-25 Speaker-microphone
- 1.H-2 Deluxe leather case
- BH-2A Belt hook
- RA-3 m 3/8 telescoping antenna (for TR-2500)
- · WS-1 Wrist strap
- EP-1 Earphone

More information on the TR-2500 and TR-3500 is available from all authorized dealers of Trio-Kenwood Communications, 1111 West Walnut Street, Compton, California 90220



## STAFF

PUBLISHER/EDITOR Wayne Green W2NSD/1 EXECUTIVE VICE PRESIDENT Sherry Smythe ASSISTANT PUBLISHER/EDITOR Jeff DeTray WB8BTH MANAGING EDITOR John Burnett ASST. MANAGING EDITOR Susan Philbrick EDITORIAL ASSISTANTS Nancy Noyd **Richard Phenix** Steve Jewett TECHNICAL EDITOR Avery L. Jenkins WB8JLG ASSISTANT TO THE PRESIDENT Matthew Smith KA1IEI ASSOCIATES Robert Baker WB2GFE John Edwards KI2U Bill Gosney KE7C Sanger Green Chod Harris VP2ML Dr. Marc Leavey WA3AJR J. H. Nelson Bill Pasternak WA6ITF Peter Stark K2OAW PRODUCTION MANAGER PUBLICATIONS Nancy Salmon ASST. PRODUCTION MANAGER/PUBLICATIONS Michael Murphy ADVERTISING GRAPHICS MANAGERS Steve Baldwin Fiona Davies Bruce Hedin Jane Preston PRODUCTION Frances Benton Linda Drew Denzel Dyer Phil Geraci Donna Hartwell Louis Marini Scott Philbrick Dianne K. Ritson Anne Rocchio Mary Seaver Deborah Stone Theresa Verville Judi Wimberly David Wozmak PHOTOGRAPHY Sandra Dukette Laurie Jennison Irene Vail Robert M. Villeneuve Thomas Villeneuve TYPESETTING Sara Bedeil Melody Bedell Marie Barker Michele DesRochers Jennifer Fay Lynn Haines Linda Locke Nancy Wilson-Newman **Debbie Nutting** Karen Stewart GENERAL MANAGER Debra Wetherbee CONTROLLER Roger J. Murphy ACCOUNTING MANAGER Knud Keller KV4GG/1 CIRCULATION MANAGER Patricia Ferrante 603-924-9471 BULK SALES MANAGER Ginnie Boudrieau 1-(800)-343-0728 ADVERTISING 603-924-7138

You wouldn't believe how soon the thrill of working stations for ten-second contacts palls. You might not find it as difficult to believe what a nuisance being expected to fill out and mail thousands of QSL cards is. Imagine, if you will, the excitement with which a ham in Tonga receives his 780th QSL from a WB2 station. It just goes into the nearest leftover washing machine carton.

Even with a QSL manager to take on the brunt of the card chore, the responsibility for keeping the log, getting a copy to the manager, and forever making instant contacts, with growing resentment whenever you stop to try to make friends with anyone forcing you to shut down...it's driven most hams in rare spots off the air.

With so many things of value which people can accomplish in this world, I am saddened when I see some ham who has gotten




#### **QSL OF THE MONTH: XE1JRV**

This month's QSL Contest winner Is Jesus Retana XE1JRV. This modern rendition of an ancient temple is highlighted by the bright yellow sun, adding warmth and contrast to an otherwise stark scene.

To enter 73's QSL of the Month Contest, put your QSL card in an envelope with your choice of a book from 73's Radio Bookshop, and send it to 73, Pine Street, Peterborough NH 03458, Attn: QSL of the Month. Entries without an envelope or book choice will not be considered.

swept up in the DX Honor Roll excitement. What a frivolous waste of life it is to devote it to trying to make this silly list... and stay there...often at almost any expense.

Continued on page 172

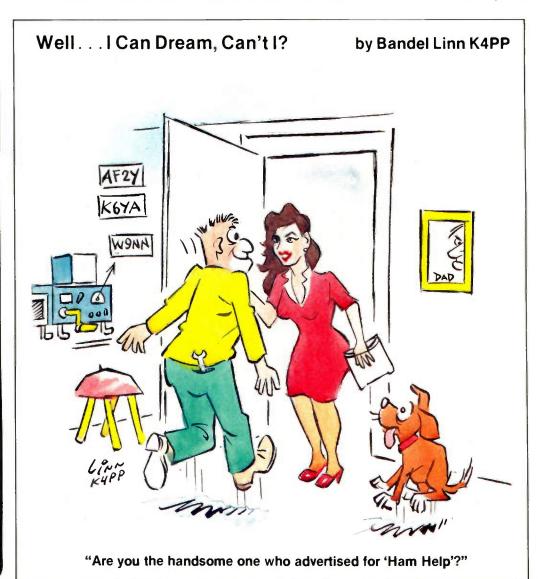

Jim Gray W1XU, Mgr. Nancy Clampa, Asst. Mgr Ross Kenyon KA1GAV Cornella Taylor

### THE RTTY ANSWER



### Now...300 Baud & Super-RATT

for either iRL terminal unit

□ All circuits on small module inside TU □ No changes to our outstanding filters □ Just add one switch and the module □ Factory installed or you can do it the most powerful RTTY program for your Apple computer

- □ 65 pages of excellent documentation
- D Features galore
- Available with or without custom cable

### and still the finest in RTTY

the FSK-1000 Terminal Unit

Unparalleled selectivity achieved with sophisticated true limiterless design

- Ultra sharp active filters
- □ Tuneable shift (80-1000 Hz.)
- Selectable bandwidths (100/55 Hz.)
- □ Three mode autostart
- □ Positive dynamic range indicator
- DExtruded aluminum enclosure
- □Adjustable "mark hold" □Keyboard activated transmit
- Doptional AFSK keyer
- Dinternal loop supply, RS232, & TTL

the FSK-500 Terminal Unit

Superior selectivity
Selectable bandwidths
All standard shifts
3 shift AFSK keyer included
Narrow shift I.D. included
Preselector included for QRM supression
Economically priced
Fully wired and tested
Compact size
RS232 or TTL
Optional loop supply

from iRL 700 Taylor Road Columbus, Ohio 43230 (614) 864-2464 Visa or Master Card accepted.

If you write RTTY computer programs, call us. We are looking for new ideas in software.

## The Hangman's 2-Meter Collinear

Make your tower do double duty. Drop this array from the top and get 6-dB gain.

Here is a 2-meter FM base-station antenna that's inexpensive, easy to build, and has about 6 dB omnidirectional gain. It can be mounted on the side of a tower or put on a mast of its own. No special tuning equipment is required. All you need is an swr meter.

#### Design

The antenna described here is a 6-element vertical collinear array. It consists of six half-wave radiators placed end-to-end and fed in phase. The resulting directional pattern is theoretically a circle in the horizontal plane, with a gain of about 6 dB over a dipole. Results of testing at W1GV/4 indicate substantial improvement, both for transmitting and receiving, over a 5/8-wave antenna with ground plane at 25 feet.

Fig. 1 shows the configuration of the collinear antenna. Each element is 38 inches long. The end-to-end spacing between elements is negligible, about 1 inch. Allowing for a foot or two at the top and bottom, the entire antenna requires a vertical space of about 22 feet. Of course, the higher the system is placed, the better the performance will be.

Proper phasing is obtained by quarter-wave stubs between the elements. For all practical purposes, these stubs do not radiate, provided they are cut to the correct length. At 146.5 MHz, 18 inches with 2-inch spacing gives a reasonant, ultra-low-loss matching section. Fig. 2 illustrates the construction details for each stub.

The antenna can, as previously mentioned, be mounted on the side of a tower or alongside a TV mast; it can even be hung from a tree branch! If the antenna is mounted on the side of a tower, the directional pattern will be modified slightly. The gain will be reduced in the direction of the tower and increased in the direction away from the tower. Therefore, you should position the antenna to provide the most gain in whatever direction you desire the best coverage (Fig. 3).

If the antenna is suspended next to a TV mast or hung from a tree limb, the pattern will be omnidirectional.

#### Construction

To put this antenna on a tower, you will need the following hardware, in addition to the usual tools and soldering apparatus:

• 6 42-inch lengths No. 12 solid uninsulated copper wire

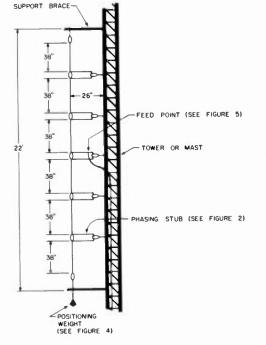


Fig. 1. Configuration of the 6-element, 2-meter wire collinear antenna. The overall height is 22 feet. The array is fed at the physical center.

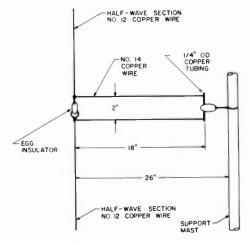


Fig. 2. Construction details for the tuning stubs. A spacing of 2 inches provides minimum loss while allowing essentially no radiation. When the stub is pulled tight, the wires will stay in place because of their stiffness.

10 73 Magazine • December, 1982

• 10 20-inch lengths No. 14 solid uninsulated copper wire

•1 20-foot (approx.) roll No. 12 solid wire

• 5 2-inch lengths 1/4-inch

o.d. copper tubing

•5 porcelain insulators (non-egg type)

7 small egg insulators

• 2 3-foot, 2-inch o.d. wooden dowel rods

• 2 screw-in-type TV standoff insulators

- 1 15- to 20-pound weight
- 1 roll of electrical tape
  1 strong set of legs

First, screw the TV standoffs into one end of each dowel. Then, attach the rods sideways to the tower braces, 22 feet apart. (If the tower braces do not exactly line up to 22 feet, use the next brace that will allow a spacing greater than 22 feet.) Of course, the higher the overall position, the better! The dowels should extend 26 inches out from the tower. Use No. 12 wire to secure the dowels to the tower braces

To assemble the antenna attach the seven egg insulators at the ends of the six antenna elements, making a long chain. Wrap and solder each wire end to the egg insulators. To minimize interelement capacitance, it's best to loop the wires through the egg insulators as shown in Fig. 2, in such a way that if the insulator should break, the wires will come apart. The elements should each measure exactly 38 inches from loop tip to loop tip. Attach an 18-inch length of No. 12 wire to one end of the array and a 48-inch length to the other end.

To construct the phasing stubs, solder two 20-inch lengths of No. 14 wire to each element end (see Fig. 1). Wrap 1 inch of wire around each element end. Space the wires 2 inches apart. Put a 2-inch piece of copper tubing through one end of a standard porcelain or glass insulator and twist a short piece of stiff wire

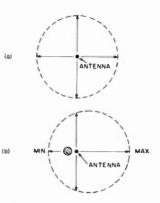


Fig. 3. Radiation patterns for a vertical array in free space (a) and near an obstruction such as a tower (b). The viewing position is directly overhead. The obstruction tends to reduce the gain in some directions while increasing it in others.

around the tubing if necessary to keep it from slipping up and down in the hole. Wrap 1 inch of the free ends of the stub wires around the ends of the tubing and solder them in place. When you are done, you should be able to pull the stub tight and have both wires evenly spaced, straight, and 18 inches long (Fig. 2). You will have to construct five of these stubs, in locations shown by Fig. 1.

Now you're ready to hang this contraption. Grab the top end-the one with the 18-inch piece of wire attached-climb the tower (don't forget your safety belt!), and affix the wire to the TV standoff insulator at the end of the upper dowel. Then, climb back down to the lower dowel and run the 48-inch end wire through the standoff insulator there. Rotate the plastic inside the standoff so the wire can't pop out, and crimp the insulator ring to keep it in place. Cut the lower wire so that roughly 8 inches remains below the standoff. Then attach the weight to the end of the wire (Fig. 4). This weight keeps the array taut as the wires expand and contract with changes in temperature. An alternative arrangement to the weight is

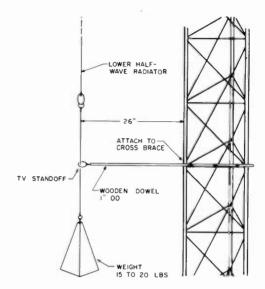


Fig. 4. Arrangement for keeping the array taut. The distance between the weight and the TV standoff should be great enough to allow for contraction with cold weather, but small enough to prevent excessive swinging of the weight.

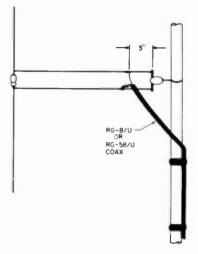


Fig. 5. Feedpoint diagram. The array should be fed at the center stub. A good starting point is 3 inches from the shorted end; however, some adjustment will probably be necessary to get a perfect match. Here, the center conductor of the transmission line is connected to the top part of the antenna and the shield to the bottom part. However, they could just as well be reversed.

to use an elastic band in place of the lower section of wire; however, the array may have a tendency to "oscillate" in the wind if this scheme is used.

To position the stubs, you'll need five pieces of wire about two feet long. Run one end through the insulator at the end of the stub, twist the wire onto the insulator, and pull the stub reasonably tight. Twist the other end of the wire around the tower support nearest the array (Fig. 2).

#### The Feedpoint

You can rest a bit now. As you're sipping a cool drink, admire the new appendage to your antenna farm. But don't get carried away; you still don't have it hooked up. And the final tuning procedure may require three or four more excursions up the tower.

Fig. 5 shows the matching section for the 6-element wire collinear. The transmission line is connected to the center stub. A good starting point is 3 inches from the shorted end, as shown. However, you'd better not solder the wires there right away. The size of your tower will have some effect on the exact final position. Larger towers will lower the impedance for any given tap point, as compared to smaller towers.

The feedpoint should be moved slightly toward or away from the shortened end of the stub until the swr is minimum at 146.5 MHz. It should be possible to get a nearly perfect match (at W1GV/4, a 1.3 swr was obtained). Always keep the coax shield and center-conductor taps at the same distance from the end of the stub; don't try to get fancy by putting them in different places.

The final tap position will be about 15 percent of the way from the shorted end of the stub to the antenna end. When the ideal position has been found, solder the wires in place and wrap the connections with electrical tape. Or, better, use silicone rubber cement. Tape the feedline cable to the inside of the tower to minimize possible induced currents on the coax from antenna coupling.

#### **Closing Remarks**

This antenna is a pleasure to use and requires essentially no maintenance. Since it is made from materials usually available at flea markets, the cost can be very low. I had much of the necessary hardware already in my junk box.


A gain of 6 dB over a dipole represents a quadrupling of the effective radiated power. But you get this gain on receive, too! With my Azden PCS-3000 at 25 Watts, I'm running 100 Watts effective radiated power, neglecting line losses. My installation, being attached to a TV mast with the bottom almost at ground level, is essentially omnidirectional. It is generally possible, in this pancake-flat South Florida area, to communicate with mobile stations via simplex out to 50 or 60 miles. Before, with the 5/8-wave antenna at 25 feet, the reliable range was only 30 to 40 miles. Of course, repeater operation is a breeze. I'm full-Q into all of the local repeaters.

There isn't any reason why more elements cannot be added to this array, except for height limitations and certain engineering requirements. An 8-element array would require about 28 feet of vertical space and would produce about 7.5 dB gain over a dipole; a 10element array would give around 8.5 dB gain.

As the number of elements is further increased, tuning of the stubs and elements becomes more and more critical, and special

equipment will be required to ensure correct phasing for optimum performance. (Even with a 1-inch error on each element, the total discrepancy would be 5 inches at the top and bottom of a 10-element array; this is 23 degrees at 146.5 MHz! Such an imprecision would surely degrade the performance of the antenna.) Furthermore, as the number of elements increases, the bandwidth of the array gets narrower because the error adds up for each element off resonance. There is a point of diminishing returns.

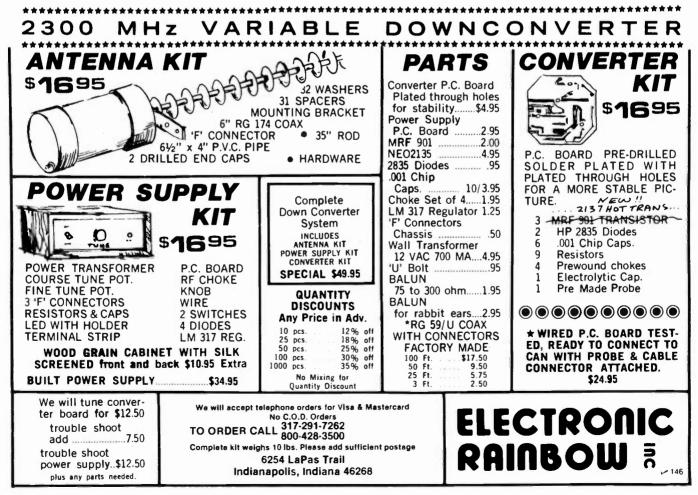A 6-element array can provide good communication without the headaches of painstaking adjustment and narrow bandwidth, and so it represents a good compromise. This antenna is ideal for the 2-meter FM operator who wants omnidirectional operation, but is presently using only a ground plane.



### **Entirely professional level!** You'll find the difference the more you use it. ULTIMATE QUALITY, NRD-515



Receiver, NRD-515 SPECIFICATIONS Receiving frequency

Receiving modes: Receiving system

Sensitivity (S/N 10dB). 1.6 to 30MHz 100 to 1600kHz Selectivity:

Stability: Power requirements:

Dimensions and Weight: Preset memory (Option): Frequency stability:

IF rejection ratio: Input impedance: AF outputs Image rejection ratio: IF rejection ratio:

outputs, Speaker output: Record/line output;

100kHz to 30MHz continuous (30 bands) US8/LS8/CW/RTTY/AM US8/LS8/LS8/LS4/HTTY/AM Up conversion type Double superheterodyne First IF 70 455MHz CW/SS8 AM 0.5/W 2μV 2μV 6μV 6kHz/2.4kHz/0.6kHz/0.3kHz (\*Ontion) 6kH2/2.4kH2/0 вкла/9.5kH (\*Option) Within 50H2/one hour AC 100/117/220/240V,50/ 60H2, 50VA 340mm(W)×140mm(H)× 300mm(D). Approx. 7.5kg 24ch Less than 50H2 per hour after warming up. warming up. 70d8 or more 70d8 or more 50 to 75 ohms, unbalanced



Best for 59

#### Transmitter, NSD-515



SPECIFICATIONS Nated output power: Frequency range:

100W NSD-515 (50W 28MHz band) 100W NSD-515 (50W 28MHz 55Ad) 1 8MHz 2 0MHz/3 5MHz-4.0MHz/ 7 0MHz 7 3MHz 14 0MHz-4.35MHz/ 21 0MHz 7 145MHz/82 0MHz-29.0MHz/ 29 0MHz 29.7MHz/0ptional new bands approved by WARC 79 10 1MHz-10 15MHz 18 068MHz-18 168MHz-24 99MHz/ A3J (USB;LSB) A1 (CW) F1 (RTTY)

Mode of emission

MAIN OFFICE: Morl Building Fifth, 17-1, Toranomon 1-chome, Minato-ku, Tokyo 105, Japan Cable Address: "JAPANRADIO TOKYO" Tokyo 105, Japan Cable Address: 'JAPAN Phone: (03) 591-3451 Telex: 0222-3068 U.S.A. BRANCH OFFICE: T. Hayashi.

120 East 56th Street, New York, New York 10022

Phone: 212 355-1180 Telex: 230-645636 JAPANRADIO NYK

SWITZERLAND: SEICOM AG Phone 064 515566 U.K.: Derbyshire-LOWE ELECTRONICS, LTD. Phone 0629-2430 U.S.A.: N.J.-GLIFER ASSOCIATES, INC. Phone: 2013917887 Ohlo-UNIVERSAL ELECTRONICS, INC. Phone: (614) 866-4605

NEW ZEALAND: Dunedin MALVICOM INTERNATIONAL, LTD. Phone: 697-625

1W or more (4 ohms) 1mW or more (600 ohms)

For more information please contact to;



AUSTRALIA: N.S.W. -EMONA ELECTRONICS PTY LTD. Phone: 398-6378 Victoria-VICOM IMPORTS PTY LTD. Phone: (03) 62 6931 FINLAND: Kotka-VISI RADIO OY Telex, 53260 VISI SF FRANCE: Paris-SOCIETE G.E.S. (GENERAL ELECTRONIC SERVICES) Phone (1) 345 35 92 CANADA: Vancouver-GLENWOOD TRADING CO., LTD. Phone 604 984 0404 GERMANY: Hannover RICHTER & CO. Phone (0511) 352 1111 ITALY: Milanese -TECHNOVENT, ITALIA, SRL. Phone 02 32 83 089

## **Deep-Six Squelch Tails**

Kerchunks take a dive with the addition of this audio delay.

**S** quelch tails are ugly. Few things are more annoying to repeater users than a long squelch tail every time someone drops his carrier. At WR3AFM, a Baltimore Amateur Radio Club (BARC) multiple-receive-site repeater,<sup>1</sup> this problem is compounded by a second squelch tail, that of the link receiver. The resulting overall squelch tail is approximately 110 milli-

seconds in duration. However, thanks to the circuit described below, it is no longer audible.

A squelch tail is the noise heard at a receiver's audio output after the transmitting station has dropped its carrier but before the receiver's squelch circuit can mute the audio output. This is what you hear whenever the repeater carrier drops off the air, for example. The

w- duration of the squelch tail
 iit is a function of your par ticular receiver.

Another source of squelch tails is a repeater receiver. Consider first a conventional single-site machine. Whenever the transmitting station drops its carrier, the repeater receiver's output follows with a burst of squelch noise. Since the repeater transmitter is still on the air at this point, this squelch tail is heard by all stations monitoring the machine.

Next, consider a split-site repeater (or a multiple-site repeater like WR3AFM) as shown in Fig. 1. In this type of setup, the repeater receiver (or each satellite receiver in a multiple-site scheme) is coupled to the repeater transmitter via a link, often on 450 MHz. The

repeater receiver operates as before, appending a squelch tail to each transmission. The receiver output is sent by the link transmitter to the repeater transmit site, where it is received by the link receiver. When the link transmitter carrier drops, shortly after the repeater receiver squelch tail ends, the link receiver will append a squelch tail of its own to the audio output. Since the link receiver feeds the repeater transmitter (or voter, in the multiple-site case, which, in turn, feeds the transmitter), this (link) squelch tail also is heard by all monitoring stations.

In order to eliminate the squelch tail nuisance, a delay line was inserted into the audio-signal path. To see how this will allow the squelch tail to be silenced,

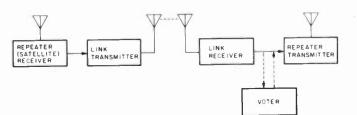


Fig. 1. Split-site (or multiple-site) diagram.

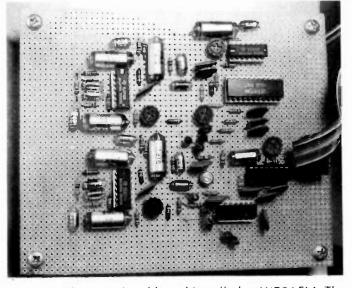


Photo A. The completed board installed at WR3AFM. The delay line is in the upper right. The I/O connector is in the far right. (Photo by N3IC)

### introducing a new dimension ...

## **ED ANTENNA CONTROL** PRO-SEARCH<sup>TM</sup>

For Contesters, DX'ers, Handicapped Operators and General Purpose Ham Operators:

The Most Advanced Antenna Control Available...

- The Only **Computerized Unit** The Only Talking
  - Unit The Only Scanning
- Unit The Only
- Programmable Unit The Only Automatic **Blaking Unit**

#### Contesters:

ro-Search seeks out a pre-programmed heading, plus tores various common headngs and automatically scans or those rare multipliers, iving the operator hands-free peration and more time for cntesting.

#### X'eis

rc-Seeich loads in short path rd long path headings and ith the touch of a button, the ystem works between both ead rgs. Plus you have all of a other features of the Proearch to aid you in catching at are DX station.


#### andicapped Operators:

ro-Secich offers ease of peration...control the entire tem with just one touch. A k loop...vocally calls out the ad rgs, allowing blind opera-rs to accurately program and ar their headings.
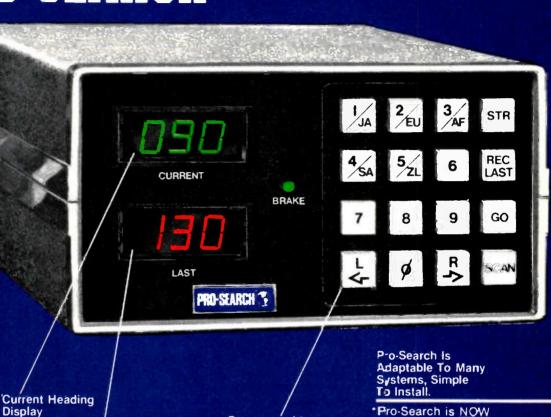
#### eneral Purpose Operators:

Search has numerous es.

e-sat beam headings for CEDS, VHR WORK, and many ners Current headings can read, by displaying the sent directions with LEDS Search also displays and cres the last station worked, ch can be recalled by the to-Locate system with the ich of a button.



Last Heading Display and Visual Confirmation of Computer Instructions

**PRO-SEARCH** Reaching The World

Programmable Keyboard and Memory Functions

### Pro-Search is NOW available for most

Popular rotors. <u>CDE</u>, <u>PY-GAIN, TELREX,</u> <u>WILSON, ALLIANCE</u>, and <u>PROP-PITCH</u>. **Cisconnect** your present antenna

control system and connect ours.

Some modifications a e necessary depending on type of rotor

#### To Order:

1-800-325-4016 1-314-994-7872 (Missouri)

#### Or write:

**Fro-Search Electronics** A Division of Wurdack and Associates, Inc. 10411 Clayton Road Suite 305 St. Louis, Missouri 63131 · Patent Pending

refer to Fig. 2. Note that although the figure specifically illustrates the multiple-site (or split-site) system, by ignoring the link (second) squelch tail it is valid also for a single-site system.

Fig. 2(a) shows the audio output of a satellite receiver and its associated squelch tail. This signal is sent via a link transmitter to a link receiver, and from there to the voter, with the added link receiver squelch tail. The audio output of the voter, shown in Fig. 2(b), contains the satellite receiver squelch tail and the link receiver squelch tail. The carrier-operated switch (COS) depicted in Fig. 2(c), with logic high equivalent to on and logic low equivalent to off, changes state after both squelch tails are completed. Since the COS is usually employed to gate (switch on or off) the repeater transmitter audio (or the transmitter itself), both squelch tails are transmitted by the repeater.

Fig. 2(d) shows the voter audio output delayed in time. It can be seen that the

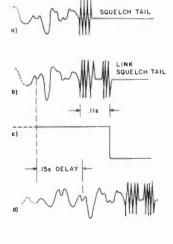




Fig. 2. Using delayed audio to eliminate squelch tails. (a) Repeater (satellite) receiver audio output. (b) Link receiver audio output. (c) COS. (d) Delayed link receiver (voter) audio output. (e) Gated repeater transmitter audio.

16 73 Magazine • December, 1982

squelch tails in Fig. 2(d) occur after the COS goes low. Using the COS signal to gate the audio in Fig. 2(d) gives Fig. 2(e). This audio contains no squelch tail at all.

The length of the satellite-receiver squelch tail is somewhat dependent on the received signal. Since the link transmitters and receivers are fixed, the link squelch tail is always the same length. To take this variability into consideration, the length of the delay was chosen to be longer than the worst squelch tail usually encountered. This ensures absolutely no transmitted squelch tail, but also chops off a small amount of audio in some cases. At worst, however, if the carrier is dropped immediately following a word, one syllable might be lost. This turns out to be insignificant in practice. Of the almost 500 members of BARC, only one seems ever to have problems with lost syllables, and then only on one-word transmissions! Overall performance has been great, and the total parts cost of approximately \$70 puts the project within reach of most everyone.

#### **General Theory**

A block diagram of the overall system is shown in Fig. 3. Starting with the delay itself, the various blocks will be examined.

The heart of the circuit is a Reticon R5101 Charge-Coupled Device (CCD) which performs the delay. The CCD acts as an analog shift register. It stores time samples of the analog input signal as packets of charge. The amount of charge in each packet is proportional to the amplitude of the analog input at the time of sampling. The packets of charge are shifted through 2000 stages before they reach the output of the CCD. Thus, the chip has 2000 samples of the input stored at any given time, each separated in time by T seconds, where T is the time between samples. The CCD uses two clock cycles per shift, and hence the overall delay time (Td) is given by  $Td = 2000 \times (2/Fc)$ , where Fc is the clock frequency supplied by the oscillator block and is equal to 2/T.

Instead of using a CCD, other schemes could be used to achieve the desired delay. These include tape loops and digital sampling, which are discussed briefly below.

The tape-loop scheme involves continuously recording and simultaneously playing back the received audio on a tape recorder. Since there is a physical gap between the record head and the playback head, a time-delay is introduced (Td = G/V, where G = gaplength in inches and V =tape speed in inches per second). A Td of up to one second is typical at slow tape speeds with this approach. This scheme is the simplest to implement, but was not used because of the problems of reliability of such factors as the tape transport mechanism, tape breakage, and dirt on the tape heads.

The digital-sampling scheme is similar to the CCD technique except that the audio signal is first digitized by an analog-to-digital converter, then stored in a digital shift register, and finally converted back to analog form by a digital-toanalog converter. This approach has the advantage of being able to achieve any desired delay by adding more shift registers. To get a reasonable signal-to-noise ratio and still preserve the dynamic range of speech, we would need either many bits (12 or more) in the digital words or we would have



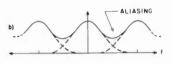






Fig. 4. Aliasing. (a) Spectrum of signal to be sampled at  $F_s$ (b) Spectrum after sampling without first low-pass filtering. (c) Spectrum of input signal after low-pass filtering with cutoff at .4  $F_s$ . (d) Spectrum after sampling the low-pass-filtered signal.

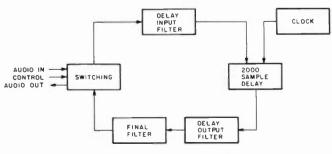


Fig. 3. System block diagram.





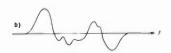


Fig. 5. CCD output filtering. (a) Before filtering. (b) After filtering.
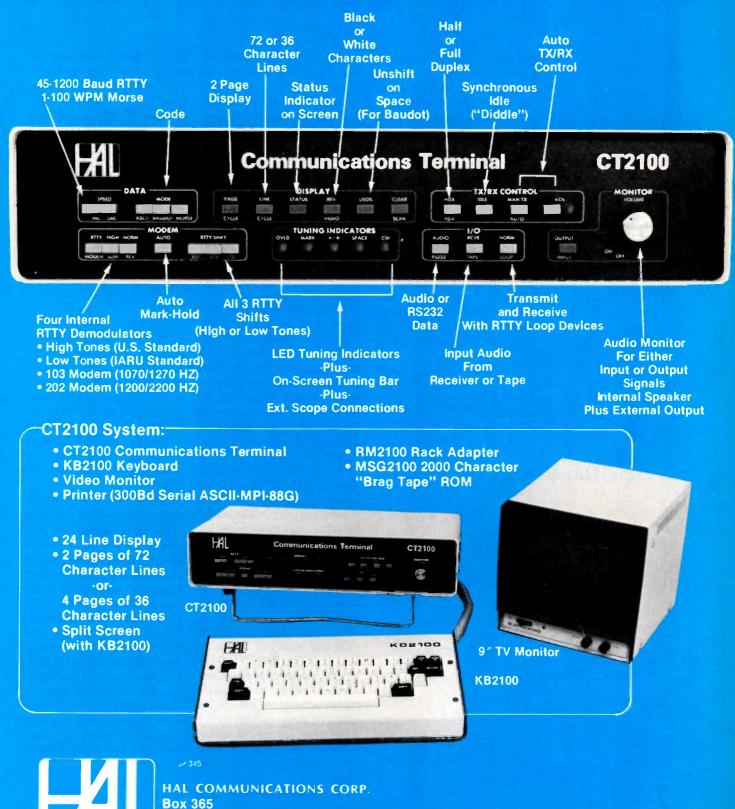
## CT2100 HAL Puts MORE Behind The Buttons



Urbana, Illinois 61801 217-367-7373

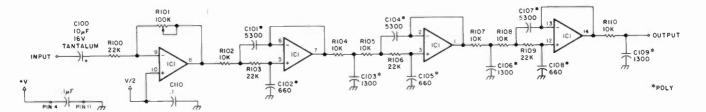

to use a compression-ex-

pansion (companding) tech-

nique. Either way, due to

the high cost of analog-to-

digital converters and digi-

tal memory (the shift regis-

ters) and because of its

higher total package count,

these approaches were un-

As in any time-domain

sampling system, the input

must be a band-limited pro-

cess. In a low-pass applica-

tion, such as with speech,

any input components


whose frequency is greater

desirable.

Fig. 7. Delay input and delay output filtering. Note: IC1 and IC2 are TL074Cs. IC1-100 series; IC2-200 series.

Frequency Gain (dB) (Hz) (I/O 2 to I/O 6) 12 -3 20 -1.3250 - .21 0 100 .53 1k 2k 1.59 2.2k 1.63 1.59 2.37k 0 3k -3 3.43k -104k -305k 6k - 51

Fig. 6. Measured overall response. Conditions: 1)  $Delay = 150 \text{ ms} (F_{clock} = 26.67 \text{ kHz}); 2) \text{ two-pole ad$ justable low-pass filter setfor 0 dB at 3 kHz.

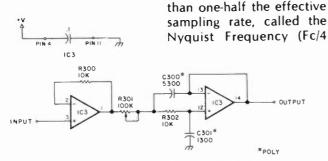



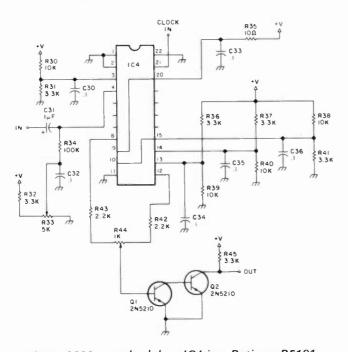


Fig. 9. 2000-sample delay. IC4 is a Reticon R5101. 18 73 Magazine • December, 1982

here), must be removed prior to sampling to prevent a form of distortion called "aliasing." If not removed by filtering, these components will appear at the output as lower frequency (alias) signals (see Fig. 4).<sup>2</sup> Once aliasing occurs, it cannot be removed by filtering, since the aliased components are indistinguishable from the original components. The necessary filtering is performed here by a 3-section, 9-pole lowpass filter.

Since the CCD is a discrete time system (that is, its output changes only at specific times, resembling a staircase), the output also contains high-frequency terms which must be removed by filtering (see Fig. 5). This filtering is again performed by a 3-section, 9-pole low-pass filter.

Since the frequency response of the CCD is somewhat dependent on the clock frequency selected, a tunable low-pass filter is provided. By tweaking this filter, the overall response may be optimized for a particular clock rate. The response for the board at WR3AFM is given in Fig. 6. The tunable filter was set so that the response at 3 kHz was equal to that at 100 Hz (0 dB). Notice the excellent flatness over the speech bandwidth (-0 dB, +1.6dB). The steep roll-off past 3 kHz also serves to attenuate wideband noise from other sources preceding the delay line.

Variable-gain input and output buffers are provided. The input buffer is set to limit the input to the CCD

to less than 1 volt peak to prevent overloading the device, and the output buffer is set to achieve unity overall gain (0 dB) at 100 Hz. Thus, the whole board is transparent to the rest of the repeater.

The switching stage allows the delay to be bypassed (if desired) and permits the audio to be gated with the COS signal. This eliminates the need for any external audio switching.

#### **Circuit Design**

Filters

The circuit was designed in a fairly straightforward manner. Quad bi-FET op amps were chosen because their high input impedance makes designing with them simple. Specifically, the TL074 is a low-noise version of the popular TL084, which could be substituted, as could many other audio op amps.

Since the frequency response of the CCD starts to roll off at about 1.5 kHz when set for a 150-millisecond delay, some form of equalization was required to extend the usable bandwidth of the system. Highfrequency pre-emphasis (that is, boosting the high-frequency components ahead of the CCD, as opposed to post-emphasis) has the advantage that the input signal is kept large with respect to the noise at all times. However, since the CCD overloads at about 1-volt peak input, any boost in the spectrum ahead of the CCD must be accompanied by an overall cut in the input level (relative to that permissible with no pre-em-

**\* AZDEN** AZDEN ★ NEW! NEW!  $\star$ **\* AZDEN**  $\star$ NEW! **\* AZDEN** 

### THE GIANT COMPANY **REVOLUTIONIZES THE STATE OF THE ART** AWE AND AZDEN. INTRODUCE THE BRILLIANT NEW PCS-2800

### **MICROCOMPUTER CONTROLLED** SUPERIOR COMMERCIAL GRADE

FM TRANSCEIVER



#### **COMPARE THESE FEATURES** WITH ANY UNIT AT ANY PRICE

- ۲

- FREQUENCY RANGE: Receive and transmit: 28.000 to 29.995 MHz, 10KHz steps with built-in 100 KHz repeater offset. ALL SOLID STATE-CMOS PL DIGITAL SYNTHESIZED. SIZE: UNBELIEVABLE! ONLY 63/4" x 23/8" x 93/4".COMPARE! MICROCOMPUTER CONTROLLED: All scanning and frequency-
- control functions are performed by microcomputer. DETACHABLE HEAD: The control head may be separated from the radio for use in limited spaces and for security purposes. SIX-CHANNEL MEMORY: Each memory is re-programmable. Memory is retained even when the unit is turned off.
- MEMORY SCAN: The six channels may be scanned in either the "busy" or "vacant" modes for quick, easy location of an occupied or unoccupied frequency. AUTO RESUME. <u>COMPARE!</u> FULL-BAND SCAN: All channels may be scanned in either "busy"
- or "vacant" mode. This is especially useful for locating repeater frequencies in an unfamiliar area. AUTO RESUME. <u>COMPARE!</u> INSTANT MEMORY-1 RECALL: By pressing a button on the microphone or front panel, memory channel 1 may be recalled for
- immediate use
- MIC-CONTROLLED VOLUME AND SQUELCH: Volume and squelch can be adjusted from the microphone for convenience in mobile operation.
- DIRECT FREQUENCY READOUT: LED display shows operating frequency, NOT channel number. COMPARE! TEN (10) WATTS OUTPUT: Also 1 watt low power for shorter

distance communications. LED readout disclays power selection when transmitting

SPECIAL

- DIGITAL S/RF METER: LEDs indicate signal strength and power output. No more mechanical meter movements to fall apart! LARGE 1/2-INCH LED DISPLAY: Easy-to-read frequency display
- minimizes "eyes-off-the-road" time. PUSHBUTTON FREQUENCY CONTROL FROM MIC OR FRONT
- PANEL: Any frequency may be selected by pressing a microphone or front-panel switch.
- SUPERIOR RECEIVER SENSITIVITY: 0.28 L¥ for 20-dB quieting. The squelch sensitivity is superb, requiring less than 0.1 uV to open. The receiver audio circuits are designed and built to exacting specifications, resulting in unsurpassed received-signal intelligibility.
- TRUE FM, NOT PHASE MODULATION: Transmitted audio quality is optimized by the same high standard of design and construction as is found in the receiver. The microphone amplifier and com-
- pression circuits offer intelligibility second to none. OTHER FEATURES: Dynamic Microphon€, built in speaker, mobile mounting bracket, external remote speaker jack (head and radio) and much, much more. All cords, plugs, fuses, microphone
- hanger, etc. included. Weight 6 lbs. ACCESSORIES: 15' REMOTE CABLE....\$29.95. FMPS-4R A/C POWER SUPPLY....\$39.95. TOUCHTONE MIC. KIT....\$39.95. EXTERNAL SPEAKER .... \$18.00.

#### AMATEUR-WHOLESAL RONICS ORDER NOW TOLL FREE 2 8817 S.W. 129th Terrace, Miami, Florida 33176 Telephone (305) 233-3631 • Telex: 80-3356 U.S. DISTRIBUTOR DEALER INQUIRIES INVITED . ~ 5 CREDIT CARD HOLDERS MAY USE OUR TOLL FREE ORDERING NUMBER.

phasis). Post-emphasis completely avoids this problem, but it also boosts any noise added by the CCD circuitry. As a compromise, equal amounts of pre- and postemphasis were employed.

The low-pass filters were designed to provide the needed boosting as well as to attenuate the high-frequency components. In order to achieve a 150-millisecond delay, Fc = 26.67kHz from the equation, above. Thus, the Nyquist Frequency (Fc/4 here) is 6.67 kHz. The low-pass filters must attenuate at and above this frequency. The 9-pole filters shown in Fig. 7 have a peak (boost) of approximately 6 dB before rolling off at -54 dB/octave. The overall response is shown in Fig. 6.

The final output filter, a buffer and 2-pole low-pass filter combination, is shown in Fig. 8.

#### CCD/Clock

Fig. 9 shows the circuitry surrounding the CCD that was suggested by the manufacturer, which was found to work well. The clock signal is produced from a simple two-inverter oscillator and is shown in Fig. 10.

#### Switching

Since WR3AFM is controlled by an 8080 microprocessor, all control signals are supplied by TTL open-collector outputs. Thus CMOS 4066 analog switches were a natural choice to handle the audio gating. The switching circuits are shown in Fig. 11.

#### **Construction Notes**

The board was built using point-to-point techniques. The actual layout, shown in Fig. 12, was carefully planned to ensure neat wiring and no ground loops. Any popular construction technique should work. Whatever method is used, however, the ground leads should be heavy enough to keep op-amp noise reasonable.

All op-amp Vcc inputs were bypassed to ground with a 1-uF disc capacitor right at the chip, on the underside of the board. Polystyrene capacitors were used in the filters to achieve close tolerance and good temperature stability. Sockets were used for all chips, with the one for the CCD being a must.

The input and output

audio, switching, and power-supply connections can conveniently be made using ribbon cable and a 14-pin DIP socket. A suggested pin configuration is shown in Fig. 13. Unused lines should be grounded at the board end only, to reduce noise and prevent ground loops. The ground lead from the DIP socket should be connected to the ground bus on the board at the spot that results in the smallest amount of noise on the audio-output line. In the layout shown in Fig. 12, the best spot was found to be near the inverter chip.

Finally, as shown in Fig. 14, a 10-uF filter capacitor was placed from Vcc to ground and from Vcc/2 to ground. Tantalum capacitors were used because of their small size and low leakage, but any type capacitor will do.

#### Parts

The CCD is available for \$50 from Reticon Corporation, 910 Benicia Avenue, Sunnyvale CA 94086, and their distributors (write to them for info). For most other parts, a good supply house is Digi-Key Corporation, PO Box 677, Thief River Falls MN 56701.

#### Adjustment

To set the clock fre-

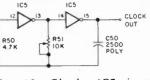


Fig. 10. Clock. IC5 is a CD4049AE.

quency, adjust R21 while observing pin 15, IC5, on a scope or frequency counter. The desired frequency may be found from the equation, above. For a 150-millisecond delay, Fc = 26.67 kHz.

R101 is adjusted to prevent overloading the CCD. Since the maximum pre-emphasis is 6 dB, the maximum signal at pin 8, IC1, must not exceed .5 volts peak for any input signal. However, to achieve the best signal-to-noise ratio, it is desirable to keep the signal as large as possible. Therefore, apply a sine wave at the maximum level to be encountered in operation (such as the level that gives 5-kHz deviation on the repeater) to the input (I/O pin 2) and adjust R101 until the level at pin 8, IC1, is .5 volts peak.

To adjust the bias and symmetry of the CCD, apply an audio-frequency sine wave to the input (I/O pin 2). Adjust the amplitude of the sine wave until distortion is just evident at pin 14, IC2. Next, set R33 and R44

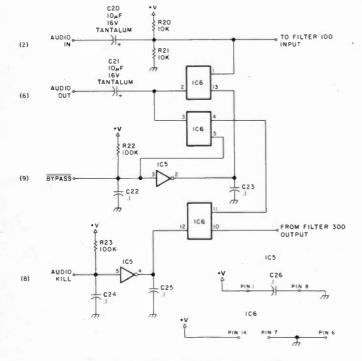


Fig. 11. Switching. IC6 is a CD4066. 20 73 Magazine • December, 1982

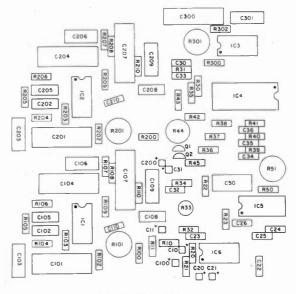


Fig. 12. Parts layout.

## NEW! POLAR RESEARCH'S

#### Multi-Directional, Motor Driven Antenna Mounting Systems For Discriminating Radio Operators!

(ANTENNAS NOT INCLUDED)

Never before has an antenna mounting system been available to radio operators with the advantages and features of Polar Research's Li'l Slipper. The tremendous versatility and widespread applications of the Li'l Slipper system eliminate any cumbersome, awkward, inefficient and inaccessible antenna configurations due to the old normal single mast, vertical antenna stacking. Greatly reducing tower interference to the radiation pattern of the antenna, the Li'l Slipper's design effectively distributes wind-load evenly on the tower's structure while maintaining all antennas in a true perpendicular position, tangent at any point to the rotor's arc.

Exclusive Li'l Slipper features include a high torque geared drive motor; all electric, end-of-rotation circuitry; acceptance of masts up to 2'' O.D. on all four housings; and limitless applications with VHF, Split-Boom, H.F. Beams, Quads, TV/FM antennas, and even UHF Dishes and Corner Reflectors.



### Call Toll Free 1-800-328-2041

The

U.S. AND FOREIGN PATENTS PENDING

Polar Research, Inc. P.O. Box 781 Thief River Falls, MN 56701; Phone (218) 681-7413 to minimize the distortion, and then increase the input until the distortion is again visible. Continue this process until no further reduction in distortion is observed.

Adjust R301 so that the overall gain is equal (1/O pin 2 to 1/O pin 6) at 100 Hz and 3 kHz. This gives a desirable

Pin	2—Audio input
Pin	6-Audio output
Pin	7—Ground
Pin	8—Audio kill
Pin	9—Bypass
Pin	14-+ 12 volts

Fig. 13. I/O connector wiring.

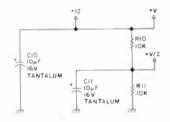


Fig. 14. Power supply filtering.

response for a voice channel.

Finally, adjust R201 so that the overall gain (I/O pin 2 to I/O pin 6) is unity (0 dB) at 100 Hz (or 3 kHz).

#### Echoes, Etc.

Since the unit introduces delay in the audio path, a rather interesting echo effect can be observed. Referring to Fig. 15, notice that due to the delay some audio output continues from the repeater after the transmitting station's carrier drops. The length of this audio is equal to the length of the combined squelch tails. Depending on the speed of the station's T-R switching, the operator will hear the end of his transmission coming back.

The only drawback of the device also is visible in Fig. 15. The final portion of audio is chopped by the circuit. The amount of audio lost is equal to the difference between the length of

the delay and the length of the combined squelch tails. Since the usual squelch tail lasts for 110 milliseconds (at WR3AFM), if a short squelch tail was acceptable, the delay could be shortened to 110 milliseconds. In practice, almost everyone holds their PTT for a short amount of time after they stop speaking, so this is really a moot point.

The delay also causes a strange phenomenon if an operator is monitoring the repeater on a secondary receiver. It is virtually impossible to talk while listening to your own voice delayed by 150 milliseconds. This effect has encouraged the more fun-loving walkie owners to engage in the friendly game of sneaking up behind an unsuspecting repeater user while he is transmitting and then turning up the volume on the walkie. This fun alone justifies the work involved in building the delay line.

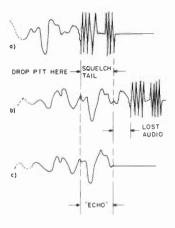


Fig. 15. Echo. (a) Transmitted audio plus squelch tails. (b) Delayed audio. (c) Repeater output.

#### References

1. Glaser, R., "An 8080 Repeater Control System," *73 Magazine*, February, 1979.

2. For a more complete discussion of sampling and signal processing in general, see, for instance, Schwartz, M., Information Transmission, Modulation, and Noise, McGraw-Hill, 1970 (second edition), or Rabiner, L. and Schafer, R., Digital Processing of Speech Signals, Prentice-Hall, 1978.


SPEEDCALL'S NEW #312 TOUCH-TONE DECODER ENDS RADIO BACKGROUND "CHATTER" FOREVER.

VISA


Quiput Single open collector output. 200mA Inout Signal Range: 20 mV to 6V (Hat Input) Code Capacity: 3 to 8 digits address plus select any of the 16 (ouch-tone digits at desired. Bettery Voltage: 138 VOC Norm (9 to 16 VOC) 30 mA nominal on standoy. Assembled Dimension: 33(4\* high, 2-1/8\* wide and 3.3(4\* jong.



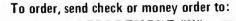LOW COST COMMERCIAL GRADE KIT!
 EASY TO ASSEMBLE COMPACT UNIT!
 STATE-OF-THE-ART FLEXIBILITY!





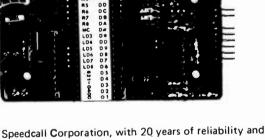

\$5

Speedcall Corporation, with 20 years of reliability and know-how in the Mobile Radio Industry, now offers the Model 312K; a unique, low-cost DTMF selective call Touch-Tone<sup>®</sup> Decoder. It's specially designed in kit form for radio buffs, with all of the quality and performance that made Speedcall #1 in signaling!

No more annoying background chatter, no more missed calls. At last it's possible for individuals and repeater groups to have their own personal and emergency touch-tone DTMF network! And you may use all 16 touch-tone digits to expand your selection of formats and permit special control applications.

#### SWD-1 VIDEO CONVERTER

FOR CABLE TV he SWD-1 Video Converter is uti-lized on cable TV systems to remove the KHz's signal from a distorted video (channel 3 in/ out) and also pass thru the normal undistorted/detected audio signal. Rocker switch selects operating mode to remove KHz's distortion from the video or pass all other channels normally. Simple to assemble—less than 30 inutes. Pre-tuned. Input/output Channel 3. Impedance

75 ohms. 117VAC. SWD-1 Video Converter Kit S69.95

#### **VTR ACCESSORIES** SIMPLE SIMON VIDEO STABILIZER

Simple Simon Video Stabilizer Model VS-125, eliminates the ver tical roll and jitter from "copy guard"

video tapes when playing through large screen projectors or on an-other VTR. Simple to use, just adjust the lock control for a stable picture. Once the control is set, the tape will play all the way through without further adjustments, includes 12V power supply

#### SIMPLE SIMON VIDEO SWITCHING BOX

Control Center

routing system. Simple Simons VSB-300 Video Switching Box enables

BEVS-1

at a time

Model

push of a button.

BAMBI P 

Wired

Electronically

easy as pushing buttons.

Bambi Electronic Video Switch ...

makes switching of your VCR/VTR,

Pay TV Decoders, Cable TV, Video

Discs, Video Games, Closed Circuit

TV, Antennae and Microcomputer as

ing network which can accept up to six different

sources of video signals and provide the flexibility of directing the inputs to any or all of the three outputs.

The Bambi Electronic Video Switch is an electronic switch-

Now you can eliminate ... the drudgery of disconnecting and reconnecting your video equipment each time you use it

the tangled mess of cables which are impossible to trace

out ... not being able to use more than one function

Bambi lets you enjoy using your video equipment the way it should be ... electronically and on line at the

Bambi's front panel was designed with the user in mind. Computer styled construction with soft-touch keyboard (rated for over 10 million operations), arranged in matrix form allows easy input/output selection without refering to charts. Functions selected through the keyboard are immediately displayed on the 1B LED status Indicators.

7+11 SWD PARTS KITS

Check the quality of Rambi against that of much higher priced competition. All solid state electronic switching provides low atten uation (3dB), wide frequency response (40-890 MHz), and excellent isolation between signal sources (each I/O section individually sheilded for 65dB min. isolation)

\$**129**<sup>95</sup>

Switch to Bambi<sup>™</sup>!

vcn	8
C .	
bi's Specifications:	
<ul> <li>Input/Output Impedance</li> </ul>	75 ohr
Signal Loss	3d8 ±1d
Noise	4d8 ±1d
A Jamest Datum Lana	1.2 -10 1-

0 0 0 0 0 0 0 HET US. WEB GAME HUS DIE

65dB min solation Power Req. 117VAC 60 Hz, 2W 10% W × 6% D × 3% H

#### 7+11 PWD PARTS KITS

(i) m

0



Ka	PART	
No	NO	DESCRIPTION PRICE
1	1VT1-PWD	Varactor UHF Tuner, Model UES-A56F
2	2CB1-PWD	Printed Circuit Board, Pre-drilled
3	3TP11-PWD	PCB Potentiometers 4-20K, 15K, 2-10K, 2-5K,
		1-1K. and 1-50k. (11 pieces)
4	4FR-31-PWD	Resistor Kit, 14W, 5% 29-pcs, 1/2 W 2-pcs 4.95
5	SPT1-PWD	Power Transformer, PRI-117VAC, SEC-24VAC
		at 500ma
6	6PP2-PWD	Panel Mount Potentiometers and Knobs, 1-1KBT
		and 1-5KAT with switch
7	7SS17-PWD	IC's 7-pcs, Diodes 4 pcs, Regulators 2-pcs
		Transistors 2-pcs. Heat Sinks 2-pcs
8	BCE14-PWD	Electrolytic Capacitor Kit, 14-pieces 6.95
9	9CC20-PWD	Ceramic Disk Capacitor Kit, 50 WV, 20-pcs 7.95
10	10CT5-PWD	Varible Ceramic Trimmer Capacitor,
		5-65pfd, 5-pieces
11	11L5-PWD	Coil Kit, 18mhs 3-pcs, .22µhs 1-piece (prewound
		inductors) and 2 T37-12 Ferrite Toroid cores
		with 6 ft. # 26 wire
12	12ICS-PWD	IC Sockets, Tin inlay, 8 pin 4-pcs, 14 pin 1-pc
		and 16 pin 2-pcs
13	13SR-PWD	Enclosure with PM Speaker and Pre-drilled
		Backpanel for mounting PCB and Ant. Terms 14.95
14	14MISC-PWD	Misc. Parts Kit, Includes Hardware, (6/32, 8/32
		Nuts & Bolts), Hookup Wire, Solder, Ant. Terms
		OPDT Ant. Switch, Fuse, Fuseholder, etc 9.95
15	15MC16-PWD	Mylar Capacitors, 14-pcs and Silver
		Mica Capacitors 2-pieces
Wh	en Ordering All	Items, (1-15), Totel Price

Available by Mail Order Only Send Check\* or Money Order. Minimum Order: \$16.95. Add 10% Shipping and Handling on orders under \$40.00. For orders over \$40.00, add 5%. Minimum Shipping and Handling \$2.00. Cat. \$1.00 - VISA and Mastercard Acceptable "Check orders will be held 30 days before shipping

2.56Hz ★ 🛛			
Magazine's UHF	MITSUMI		
be for maximum		TALL	
hour assembly.		VA	RACTOR
\$34.95			TUNER
r Supply			I UES-A56F
etely assembled		2	24.95
cy Control and	QZ4.33 ₫, ₫ /0		
.,	F		2 UHF470 - 889MHz
\$23.95			a Input 75 ohms
	CI	hannels 14	-83 Output Channel 3
E ITEMS	KIT	PART	
S7 A95	NO	ND VT1-SW	DESCRIPTION PRICE
· 14° I			Varactor UHF Tuner, Model UES-A56F \$24.95
ately \$82.85		CB1-SW TP7-SW	Printed Circuit Board, Pre-Orilled
INCLUDED -	3	187-244	P.C.B. Potentiometers, 1-20K, 1-1K, and 5-10K ohms, 7-pieces 5.95
Amelitian	4	FR35-SW	
Amplifier	5	PT1-SW	Power Transformer, PRI-117VAC, SEC-24VAC,
T			250ma 6.95
	6	PP2-SW	Panel Mount Potentiometers and Knobs, 1-1KBT
			and 1-5KAT w/Switch
	7	S\$14-SW	the second s
			Heat Sink 1-piece 29.95
nolifiers		CE9-SW	Electrolytic Capacitor Kit, 9-pieces
			Ceramic Disk Capacitor Kit. 50 W.V., 33-pieces 7.95
Gain	10	CT-SW	Varible Ceramic Trimmer Capacitor Kit,
Gain my purposes and is	- 11	L4-SW	5-65ptd, 6-pieces 5-95 Coil Kit, 18mhs 2-pieces, 22µhs 1-piece (prewound
dance is 75 ohms		F#-244	inductors) and 1 T37-12 Ferrite Torroid
minutes No colla,			Core with 3 ft of #26 wire. 5.00
	12	ICS-SW	I.C. Sockets, Tin inlay, 8-pin 5-pieces
supply \$34.95			and 14-pin 2-pieces 1.95
supply 44.95	13	SR-SW	Speaker, 4x8" Ovel and Prepunched
LEMENT			Wood Enclosure
	14	MISC-SW	Misc. Parts Kit Includes Hardware. (6/32, 8/32
ENNA (			Nuts, & Bolts), Hookup Wire, Ant. Terms, DPDT
			Ant Switch Fuse Fusebolder etc. 9.95

NEED 5 OR MORE OF AN ITEMP WRITE FOR QUANTITY DISCOUNTS

Outside Nevada Call:

S1 45 m

3871 S. Valley View, Suite 12, Dept. 7, Las Vegas, NV 89103

In Nevada Call: 702-871-2892

1-800-782-3716



VS-125 Video Stabilizer, wired .

### The Affordable Video

Excellent in isolation and no loss

you to bring a variety of video components ogether for easy viewing/dubbing. Also you gain the ability to record one channel while viewing another. Unit Includes two F-type quick

nector ended cables VSB-300 Video Switching Box, wired

S19.95 **UHF ANTENNAS and ACCESSORIES** MOC ABAATELLD CTV 00 FLEMENT

MUS-AMATEUR-ETV 32 ELEMENT
YAGI ANTENNA
VAGI ANTENNA • Not A Kit • 23dB Average Gain • Commercial Grade
• 23dB Average Gain • Commercial Grede • Die Cast Waterproof Housing with 4%" x 2%" Area for Electronics • Includes P.C. Probe. F-61 Connector and Mounting Hardware
MAE-2 32 Element YAGI Antenna
Kato Sons' Down Converter Kit +1.9 - 2.56Hz+
Designed for Simple Simon by former Japanese CD Amateur Magazine's UHF

Editor/Engineer. Unit utilizes new ingenious Printed Circuit Prob gain. Circuit board fits inside MAE-2 antenna housing Requires 1 IC and capacitors pre-soldered Model KSDC-KIT 1.9 - 2.5GHz Down Converter Kit

Kato Sons' Regulated Varible DC Power For use with KSDC-KIT 1.9 - 2 5GHz Down Converter, Comole with Attractive Cabinet, TV/Converter Mode Switch, Frequence LED Indicator. Model KSPS-1A Assembled Power Supply



STVA-3 Yagi Ant ina 14.5dB Gain, Selectable 75 or 300 Channel 60-80 \$19.95 STVA-4 Yaqi Antenna 14.5dB Gain Selectable 75 or 300 ohm Channel 44-52 \$19.95 1 G-59/U 75 ohm Low Loss Coas Cable . S.12p/m. F-59 Coas Connector. S .39 mm

Special UHF 75-300 ohm Matching Transforme

MT-1

Steven D. Katz WB2WIK 24 Louis Drive Budd Lake N/ 07828

## **Build Yourself A Paralyzed Beam**


Go from east to west in less than a second with this 2-meter array. And put your rotator out to pasture.

73 and thanks for the point. click ... 30 seconds later Anyone else calling?" Bzzz, whoosh ..... "three" ter, bzzz, whrrr. "Oh, gosh ing, are you still there? Try the W3 calling, you're in the noise here, but you're off the back of the beam;

vour diern New Jersey, OM. rection ...... Click, click, click, click, click. "OK, ... sput- now: the W3 who was callagain now."

What a waste of time to be constantly turning

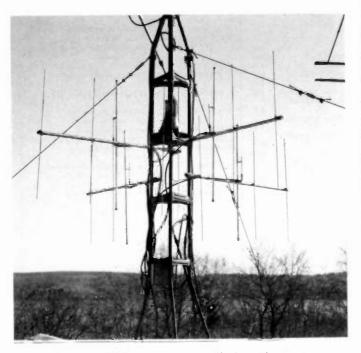beams during a VHF contest. Especially on FM, where a good operator in the metropolitan area can run 60 or more contacts per hour on 146.52 MHz or other popular simplex channel, if only he doesn't have to spend half his time turning a beam. But in a densely-populated area (and there are many such regions. in the US) one simply cannot use an omnidirectional



The four A147-4 beams installed on the tower. 24 73 Magazine • December, 1982



The relay box mounted on the tower. Note the well-taped PL-259s.

gain array, due to high QRM levels. What to do? Thought you'd never ask.

How about four vertical yagis, aimed at compass points or areas of known activity, side-mounted on your tower or mast, with remote switching from a single feedline? Too expensive? Not really. Cumbersome? Not as much as a rotator. Tricky? Not at all. Simple, in fact, and requiring little time or homebrewing expertise. And the benefits are attractive, not only to the VHF contester, but to any active FMer; of course, the principle described lends itself to a varietv of other interesting applications, such as diversity reception experiments or phasing of HF steerable arrays.

Personally, I used four Cushcraft A147-4 shortboom 4-element 146-MHz yagis, for their ease of matching to an unknown line impedance, light weight, and low cost. If all the control box parts listed in the parts list are purchased new at list prices per the 1980 Allied Electronic catalog and added to the 73 advertisers' prices for the coax and antennas listed, the total cost of this entire project is \$159.88. The only additional expense would be the feedline (hardline sells for 49¢ per foot from several 73 advertisers), the hardline connectors (brand new for \$8.00 each from Phelps-Dodge, or available for much less at flea markets), and the 4-conductor control cable (the Belden cable listed sells for \$12.00 per 100' list price).

Sound like a lot of dough? Lagree; that's why L bought most of the stuff (except for the antennas) at local surplus stores, which brought the cost of this project down to less thansixty bucks (minus antennas). The Cushcraft antennas specified sell for \$21.00


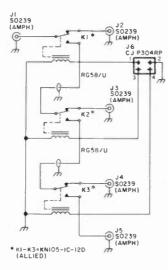


Fig. 1. Relay box.

each, but could be replaced with home-brew antennas—either yagis or quagis—for a fraction of that.

The A147-4s were selected here because they are small and light, they are end-mount types ideal for direct tower mounting, and they develop slightly over 6 dB gain, which is a tad more than my omnidirectional Phelps-Dodge Stationmaster. The Stationmaster, a well-respected, 20-footlong fiberglass monster, sells for about \$240.00; my 4-beam system works as well, and offers the advantage of selectable directivity for QRM reduction. and it costs far less.

See Fig. 1 for the circuit of the relay box and Fig. 2 for the control box. Real Novice stuff. Mount  $K_1, K_2$ , and  $K_{1}$  in a line on one flat, removable panel of the Bud AU-1029 cabinet. Mount the four output SO239 connectors in a line parallel to and about an inch away from the relays. Mount the SO239 "common" or "input" connector an inch from  $K_1$ , on the opposite side of the relay from the four output connectors. Mount the Cinch Jones P304RP connector in whatever space is left on the same panel. Now all components and all wiring are on just one flat aluminum

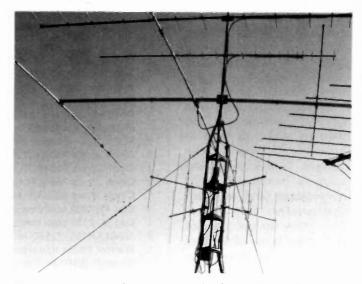

Here you can see the company the four A147-4s have: 4 el on 20, 15, and 10 meters; 19 el on 70 cm; 16 el on 2 meters. Guys are broken up with ceramic insulators.

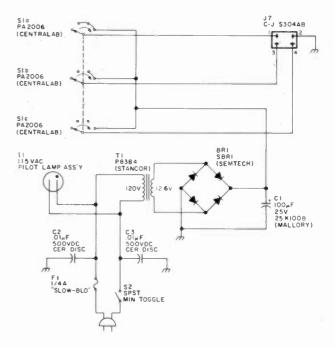


Fig. 2. Control box.

panel. The rest of the utility cabinet is only a weatherproof box for the relays.

Use the flattened braid from RG-58/U for the connections from each UHF receptacle to each corresponding relay terminal, per the schematic in Fig. 1. Keep these braid jumpers as short as possible—mine are about one inch long each. If this box is intended for use at 146 MHz, this is important. Use short lengths of RG-58/U to make the K<sub>1</sub>-to-K<sub>2</sub> and K<sub>2</sub>-to-K<sub>3</sub> jumpers (see Fig. 1), keeping all exposed leads short. Solder the RG-58/U braid to ground lugs installed near each relay for this purpose.

The three relay coils must operate independently but they can have a common ground: thus, the wiring shown and the four-pin connectors.

After all the wiring in both the relay and control boxes is completed and double-checked, make up a short 4-conductor cable with the appropriate Cinch Jones connector at each end, and bench-test the two units together. The dc output from the bridge rectifier should measure slightly over 17 volts with the rotary switch in position 1 (no load). This will drop to less than 17 volts with the switch in position 2, and then to about 16 volts in positions 3 and 4. The 12-volt relays specified seem to handle the slight overvoltage (and resultant overcurrent) just finetheir coils do not get hot even after hours of applied voltage. The maximum power dissipated in each relay coil is about 1.8 Watts.

Before the final installation of the relay box, drill two holes through one side of the box for a suitable U-bolt to clamp the box to your tower leg or mast. Then assemble the box on the tower or mast and caulk all corners and joints with the specified silicone caulking compound. I also wrapped the corners with Scotch 33 vinyl electrical tape.

The relay box provides a nice low vswr through about 50 MHz, but at 146 MHz it does not. Using my Bird model 43 wattmeter, a range 25C slug, a Dielectric Communications model 4050 50-Ohm, 50-Watt microwave dummy load, and a 146-MHz, 25-Watt transmitter, I measured the vswr looking into the box (with each output terminated in the 50-Ohm load) and found it to be less than 1.5:1 in position 1, but over 2:1 in the other three positions. However, there was no actual loss through the relays. just an impedance mismatch. What to do? Simple; tune the antennas to match the box!

Here's what to do to make it all work well at 146 MHz:

• Connect each antenna, once mounted in its permanent position, to its respective port on the box, using the 64" RG-8/U foam cables

#### Parts List

- lengths of RG-8/U foam coax (Belden 8214), cut 64" long each
- 1 length of RG-58/U, about 36" long

4

1

- suitable length of RG-331/U (1/2" alumifoam "hardline") feedline
- 8 PL-259 UHF plugs, silver-plated (Amphenol 83-1SP)
- 1 Phelps-Dodge #66-654 UHF hardline connector
- 1 Phelps-Dodge #66-656 UHF hardline connector
- 5 SO239 UHF receptacles (Amphenol 83-1R)
- 1 Cinch Jones P304CCT, 4-conductor cable plug
- 1 Cinch Jones S304CCT, 4-conductor cable receptacle
- 1 Cinch Jones P304RP, 4-conductor recessed panel plug
- 1 Cinch Jones S304AB, 4-conductor flush panel receptacle
- 1 Bud AU-1029 utility cabinet
- 1 Bud SC-2133 cowl minibox
- 3 Allied KN105-1C-12D relays (SPDT, 12 V dc/150-Ohm coil, 10-A contact rating)
- 1 Stancor P8384 transformer (12.6 V c-t, 1 A)
- 1 Semtech SBR1 bridge rectifier (100 piv/leg, 1.5 A dc)
- 1 Centralab PA2006 rotary switch (3 pole, 4 position)
- 1 Allied #652-0503 SPST miniature toggle switch
- 1 Mallory 25X100B electrolytic capacitor (100 µF, 25 W V dc)

Miscellaneous: #4-40 and #6-32 hardware and solder lugs; knob for rotary switch; pilot lamp assembly, 120 V ac; zip-cord/ac line plug assembly; GE silicone bathtub caulk, waterproof; terminal strips; grommet for ac line cord; hookup wire.

Note: None of the parts listed is particularly critical, and each may be substituted for as desired. However, I strongly recommend the following:

• Use only Amphenol rf connectors. Cheap substitutes may work at low frequencies, but at 146 MHz, PL 259s are marginal performers unless they're good ones and assembled properly.

• Use Cinch Jones 4-conductor plugs and sockets. They're easier to work with and are far more durable than cheap substitutes.

• Use Belden 8214, Times FM-8, or other high-quality, foam-dielectric cable for antenna/relay-box interconnects. Avoid CB-grade coax.

• If you cannot find truly high-quality foam coax, use Belden 8237 or any brand MIL-Spec RG-8/U cable (be sure the cable says "MIL" or "MIL-C-17" right on it) and change the length from 64 " each to 53" each.

• Do use hardline as transmission line if your run to the shack is more than 50 feet. The difference in loss at 146 MHz is well worth the slightly higher cost. Why use a gain antenna system if that gain is thrown away in the feedline?

• The relays listed are somewhat critical. Avoid miniature and encapsulated relays; also avoid the plug-in type. Usually, the built-in interconnect leads are far too long for rf work, especially at VHF.

and PL259 connectors. The 64" is a nice length because it reaches, and also because it is one wavelength (in foam cable) at 146 MHz, thus making the box think the antenna is coupled directly to it.

• Connect the control box to the relay box with a length of 4-conductor cable. Locate the control box on your roof or tower for this temporary arrangement.

• Connect a 10-to-25-Watt two-meter exciter through 50-Ohm cable (any length) to a 50-Ohm coupler (I used a Bird 43) which is connected directly (like with a double-male UHF adapter) to the "common" port of the relay box.

• Apply power to the rig and the control box. With the control box switch in position 1, transmit and measure vswr. If it's low, great. If not, adjust the gamma match on antenna 1 to bring reflected power to a minimum.

• Perform the same gamma-match adjustments on antennas 2 through 4, switching to each in turn by using the control box. It should be possible to bring the vswr of each antenna down to reasonable proportions with the gamma match provided on each A147-4.

Now the system is adjusted. Remove the wattmeter, etc. Locate the control box in the shack, run the feedline and control cables down into the shack, and you're on the air.

Voila! A really high-class antenna system in just an afternoon's work. My whole installation (pictured) took about four hours, including wrestling with the hardline. The two boxes took just one evening to assemble. It was worth it. As you can see in the picture, I do own a Stationmaster for 146-MHz FM work, and although it is an excellent antenna, it is 20' long, weighs over 25 lbs., catches a lot of wind (and ice), and cost over \$200.00. The four beams are more versatile, occupy less space, work at least as well, and were far less expensive.

Now, when I hear a weak station calling, I can "turn the beam" in less than one second to pull him in. What a difference!■

26 73 Magazine • December, 1982

Call for Quotes Dealer Inquiries Invited



inc.

#### THE PERFECT GIFTS FOR CHRISTMAS

#### **HF TRANCEIVERS**

720-A- The Top of the Line 730- A Great Mobile Rig 740-The Newest Model

**MOBILE RIGS** 25A for 2m 35A 220 MHz 45A 440 MHz

1

E

I

Г

HANDHELDS IC 2A/2AT-2m IC 3AT- 220 MHz IC 4AT-440 MHz

New for SWL Listening The R70 A Complete Line of Accessories In Stock—CALL for Quotes

SANTEC

		MICKO
144up 2m Synthesized Hand-held 440up MHz Synthesized Hand-held		THE COMPLE
AMPLIFIERS — TOKYO HY-POWER HL32V 2m Amplifier, 2 in, 30 out. HL82V 2m Receive Preamp, 2 in, 80 out HL160V 2m Receive Preamp, 2/10 in, 10 HL20U 440-450 MHz Amplifier, 2 in, 20 o HL90U 430-440 MHz Amplifier, 10 in, 90	149.95 60 out	RTTY/MORSE SYSTEM CALL FOR OUR LOW PRICE MONITORS 9" and 10" Gree
TUNERS – TOKYO HY-POWER HC150 200-watt SWR/Watt Meter HC2000 2000-watt with Meters and Swit COMPLETE LINE OF FILTERS AND ACCES —CALL FOR QUOTES— —Shipping not included in pri	ch	THA 2 DAYS C Special "Hamfe
ASTRON POWER SUPPLIES (13.8 VDC)           RS-7A 5 amps continuous, 7 amp ICS	CDE Ham IV AZDEN PCS 300 Hand-helo NEW! PCS 4000 2m XCVR KDK FM 2030 25-watt FM X	89.95 195.95 1. 279.95 283.95 CVR 278.95
989 New 3 kW Antenna Tuner.       285.95         962 1.5-kW Tuner switch/meter.       185.95         940 300-watt Deluxe Tuner.       119.95         941 200-watt Tuner switch/meter.       78.95         940 300-watt Tuner switch/meter.       79.95         202 Noise Bridge.       48.95         401 Econo Keyer.       41.95         406 Deluxe Keyer with Meter.       60.97         408 Deluxe Keyer with Bencher.       87.95         404 Keyboard II.       285.95         7528 Dual Tunable SSB/CW Filter       78.95         BENCHER PADDLES Black/Chrome.       34.95/42.95         AEA KEYERS, READERS, ANTENMAS.       CALL         MM-2, CK-2, KT-2, MBA/RO, MBA/RC, Isopoles       -CALL FOR OUR LOW PRICES-         BENJAMIN MICHAEL CLOCKS       1732 24-hour Crystal Clock.       29.95         1732 24-hour Crystal Clock.       29.95         1732 C4-hour Crystal Clock.       29.95         1732 C4-hour Chock       56.95         973A Analog 24-hour 14-Inch Clock.       36.95         DAIWA /MCM/J.W. MILLER       CN-540 SWR/Watt Meter.       69.95	S25 Argosy HF XCVR S46 Omni-C HF XCVR Complete Line of Filters a — CALL FOI MIRACE VHF / UHF AMP B23 2m Amplifier, 10 in, 0 B108 2m Amplifier, 10 in, 0 B1016 2m Amplifier, 10 in, 0 A 2 watts in, 25 watts out 2m 200 mW in, 25 watts out 2m 2 watts in, 50 watts out 2m 2 watts in, 50 watts out 2m 2 watts in, 50 watts out 2m 2 watts in, 100 watts out 2m Power Pocket for ICOM 2 CABLE BY SAXTON RC213 Mil Spec RC8/U Foam 95% Shield. 8-wire Rotor 2 #18, 6 #22. Mini-8 <b>TELEX HEADSETS / HEAD</b> C1210/C1320 Headphone. PRO COM 200 Headset/D)	COM, YAESU F AMPLIFIERS quotes — 399.95 499.95 1069.90 and Accessories in Stock R QUOTE — LIFIERS/METERS outCALL 80 outCALL 160 outCALL 160 outCALL AMPLIFIERS ntenna
ORDER TOLL FRE	E 1-800-	336-4799 (Orders Only, Please)


#### **MORSE/RTTY SYSTEMS FOR CHRISTMAS**

Information and Virginia Orders: (703) 643-1063

13646 Jefferson Davis Highway, Woodbridge, Virginia 22191 Store Hours: M-W-F 12 noon-8 p.m.; T-Th-S 10 a.m.-4 p.m.

HOLIDAY SPECIA

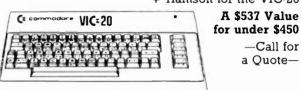A Complete Ham Computer System VIC-20 + Kantronics Interface + Hamsoft for the VIC-20



MICROLOG THE COMPLETE RTTY/MORSE

SYSTEM -CALL FOR OUR LOW PRICE-

MONITORS -Call for Quotes-9" and 10" Green or Amber Screens In Stock

#### THANKSGIVING SALE 2 DAYS ONLY-NOVEMBER 26-27

Special "Hamfest Pricing" Limited to Stock Items

. 89.95 . 195.95 . 279.95 . 283.95	ANTENNAS AVANTI AP 151.3G 2m On-glass Antenna
.278.95	HY-GAIN ANTENNAS       CALL FOR QUOTES         TH3MK3S 10-15-20m Tribander       215.95         TH5MK2S New Model Tribander       307.00         TH7DX 10-15-20m Tribander       375.95         V2S 2m Vertical       37.50         14AVQ 10-40m Vertical       51.95         18AVO 10-80m vertical       99.50         HY-GAIN ANTENNA/TOWER PACKAGES       CALL
.399.95 .499.95 1069.00 Stock .CALL .CALL .CALL	CUSHCRAFT (Other antennas in stock)           A4 New Triband Beam 10-15-20m         224.95           A3 New Triband Beam 10-15-20m         172.95           AV3 New 10-15-20m Vertical         44.50           ARX-2B New Ringo Ranger 2m         34.50           A22-19 2m "Boomer" DX Beam         81.95           220B 220 MHz "Boomer"         74.95           214B "Jr. Boomer" 144.146 MHz, SSB         68.20           214FB "Jr. Boomer" 144.5148 MHz, FM         68.20           214FB "Jr. Il 1-element 2m         37.95
14.95 66.95 78.95 99.95 .157.95 .179.95	KLM ANTENNAS (Other antennas in stock)           KT34A 4-element Triband Beam         .309.95           KT34K 4-element Triband Beam         .459.95           144-148-13LB 2m 13-element with Balun         .77.95           144-148-16C 2m 16-element for Oscar         .93.55           420-450-14 420-450 MHz 14-element Beam         .77.95           420-450-18C 420-450 MHz 14-element Beam         .78.70           432-16LB 16-element 430-434 MHz Beam/Balun. 60.70         .77.95
.26°/ft .24°/ft .16°/ft .12°/ft 5/40.95 .78.95 .71.95	HUSTLER         99.95           S-BTV 10-80m Vertical         79.95           4-BTV 10-40m Vertical         79.95           3-TBA New 10-15-20m Beam         188.95           HF MOBILE RESONATORS         Standard           Super         10 and 15 meter           02 meters         11.25           40 meters         13.00           19.00         75 meters
99	Send stamp for a flyer. Terms: Prices do not include shipping. VISA and Master Charge accepted. 2% dis

-336-4799 shipping. VISA and Master Charge accepted. 2% dis-count for prepaid orders (cashler's check or money order). COD fee \$2.00 per order. Prices subject to change without notice or obligation. No personal checks accepted. Returns subject to 10% restocking fee. (Orders Only, Please) Order Hours: M-F 11 a.m. to 7 p.m.; Saturday 10 a.m. to 4 p.m. Bonus: 2% Discount for Prepaid Mail Orders (Cashiers Check or Money Order) v 453

Calvin McCarthy VE3LMP 98 Windsor Street Thunder Bay, Ontario Canada P7B 1T7

## **Taming the 2-Meter Linear**

It lives in the forests of spurious oscillations and answers to the call of the correct bias. Catch one for yourself.

lass C amplifiers for the two-meter band are a "dime a dozen," with commercial models, kits, and schematics available from a good number of suppliers. Linear amplifiers are another story. Their design and construction is all black magic, and manufacturers are the only wizards in on the mystery. With a little sleuthing, I found that Motorola would sponsor my initiation into this exclusive cult, allowing me to build an amplifier to boost the output of my 2-meter

OSCAR station from 2.5 Watts to 20 Watts.

In order to linearize a solid-state rf power amplifier, you must solve two problems. First, you must bias the transistor into the linear region while supplying a substantial amount of varying base current. Secondly, you must tame any spurious oscillations generated by the high-gain transistor used.

First, the biasing problem will be faced. A small-signal transistor amplifier is usually biased with a voltage-dividing network such as that shown in Fig. 1(a). The current flowing through the network resistors is set to be about ten times the current needed by the base. With our amplifier needing from. 10 mA to 100 mA of base current at any time, this circuit would not be practical. As well, the bias voltage must be held at a constant stiff value for all values of base current, which is not possible with a resistive voltage-divider network.

An alternate solution to this biasing problem, which

the total bias supply current is greater than the maximum base current and the surplus current is shunted to ground by the reference diode, or the series pass regulator of Fig. 1(c) can be used. The series regulator reduces the current which must flow through the reference diode by ibase/hfe, and the total bias current used becomes virtually the base current needed at each instant. The bias voltage is set by the forward voltage drop of the diode reference which is approximately 0.6 volts. The series regulator bias is set by two forwardbiased diodes in series, the second diode voltage drop compensating for the baseemitter junction drop of the series pass transistor so that the bias supply voltage output will equal only one PN junction voltage drop. Now for a very important

satisfies the need for a con-

stant bias voltage while

supplying varying currents,


is the solid-state voltage

regulator. Either the shunt

regulator of Fig. 1(b), where

Now for a very important point! As a transistor warms, its base will draw more current, which increases collector current, which warms the transistor more, and this will continue until the component selfdestructs. To offset this, the base bias voltage must be reduced as the transistor warms. By mounting D<sub>ref</sub> as



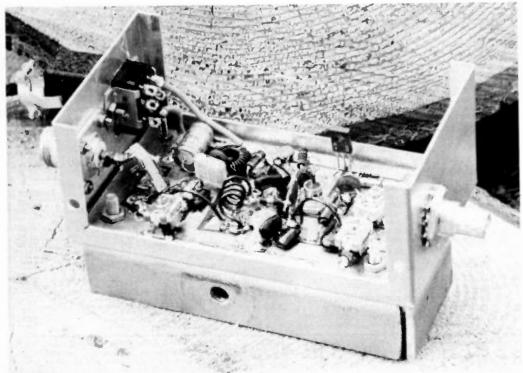

MRF 2-meter linear amplifier.

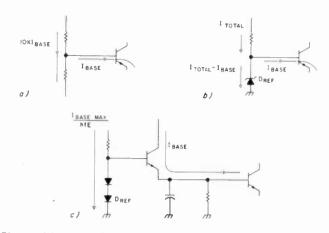


Fig. 1. Bias possibilities. (a) Voltage divider arrangement. (b) Zener diode stabilized. (c) Pass transistor circuit.


close to the rf transistor as possible to provide thermal contact, the diode junction voltage will decrease as the diode warms, neutralizing the base-emitter junction change of the rf transistor and thus keeping the base current under control. Remember! Attach the reference diode so that it will be warmed by the rf power transistor. Either physically attach it to the transistor body or to the heat sink as close to the transistor as possible. Do not expect the reference diode to thermally track if the thermal path is broken by air.

Low-frequency oscillations also are a problem. My amplifier first oscillated in the HF band because at these frequencies the transistor has very high gain. Bypassing the collector current feed did not tame these troublsome responses, so 1 took the brute-force method and fed back the collector signals to the base through a feedback network. The rf choke is a virtual short for the oscillations but an open circuit for the desired VHF response. The capacitor is a virtual short for the undesired oscillation but an open circuit for the collector supply. This network was placed between the collector and base with very short leads and the unwanted oscillations were completely suppressed.

The amplifier which I built (Fig. 2) is a modified version of the class C amplifier described by W4MNW in the November, 1977, issue of 73 Magazine. I lifted RFC1 from ground, added bypass capacitors to the lifted end so the rf input would continue to see a ground, then connected the base bias supply to RFC1. The low-frequency feedback network was added to stabilize the amplifier and the linear amplifier was a reality. It would appear to be quite possible to linearize many of the class C amplifiers now in EM and CW use in the same way.

The testing of this amplifier was done with a regulated and current-limited power supply. This saved the transistor from destruction before I had tamed the low-frequency oscillations. The transistor is rated for a collector current of four Amperes, but I set the supply to limit current to a maximum of one Ampere until I was satisfied that the amplifier would not hurt itself.

Low-frequency oscillations manifest themselves by a sudden jump in collector current and corresponding drop in supply voltage. The first time this happened 1 thought 1 had destroyed the transistor, but the power supply protection

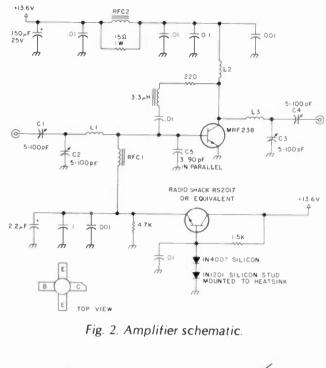

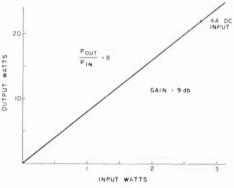


Fig. 3. Amplifier linearity.

had saved it. I was able to continue my study of the problem and a wideband oscilloscope revealed a pulse-type response on the collector output. This was suppressed by the feedback network shown in the schematic.

I made an interesting observation about amplifier efficiency while tuning the amplifier. There is a particular collector current needed to give a particular output power—not so collector voltage. Thus 0.5

Watts input will become 4 Watts output at 2 Amperes collector current whether the collector voltage is 5 or 12 volts. Under the same conditions, the dc input power changes from 10 Watts to 24 Watts. For maximum efficiency, it seems that the amplifier should be operated at the maximum linear power output possible for the applied collector voltage, or if it is desired to operate the amplifier at reduced power, the collector voltage should be re-

#### Coil Construction Details RFC1 10 turns #22 on 270-Ohm, ½-Watt resistor RFC2 13 turns #22 on T50-6 toroidal core L1 ½ turn #16, approx. 1½" L2 4 turns #16, 1/4" i.d. L3 Curved wire, #16, 1-1/4" long

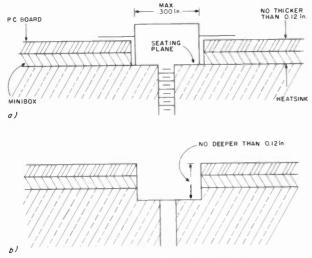


Fig. 4. MRF238 mounting details.

duced. Linear operation at 4-Ampere dc input is shown in Fig. 3.

The amplifier was built in a 51/4" × 3" × 21/2" minibox on double-sided epoxy glass PC board. The circuit lands were etched, but islands of PC board epoxied to the ground plane would serve as well. Be very certain that the capacitors that

FE0201

make up C5 are soldered with short leads as close to the transistor body as possible. Connect the ground plane on both sides of the board with eyelets or wire running through the board and solder on each side. A heat sink is necessary. My heat sink has 35 square inches of radiating area and it seems to be just satisfactory. A larger one is recommended.

The mounting of the MRF238 is very critical (see Fig. 4). Careless technique will result in a destroyed transistor if stress is placed on the leads. Mount the transistor seating plane with very good thermal contact to the heat sink. The thickness of the case metal and the PC board must not be greater than .120 inch. If it is, the transistor leads will be forced up, putting a strain on the transistor cap. On heating, the bonding material will fail and you will be out buying a new expensive transistor. If the PC board and case thickness together is much less than .120 inch, you may want to mill out the heat sink as in Fig. 4(b) so the transistor leads will not be bent down when soldered to the PC board. Do not solder the leads before tightening the stud mount-

ing nut. Do not hold the transistor leads while tightening the nut. Do hold the transistor securely by the wrench flat on the end of the stud while tightening the nut. Only after the mounting nut has been tightened carefully may you solder the leads to the board

The MRF238 Motorola transistor is available from Ramsey Electronics and Semiconductor Surplus, both 73 advertisers.

#### References

1. Charles F. Clark AF8Z, "Solid-State Linear Amplifiers," Ham Radio, January, 1980, p. 48. 2. D.J. Lynch W4MNW, "Build a 2-Meter Power Amp," 73 Magazine, November, 1977, p. 96. 3. Motorola Semiconductor Products, Inc., Box 20912, Phoenix

AZ 85036: AN546-Solid-state linear amplifier design.

AN555-Mounting stripline-opposed emitter (SOE) transistors. AN791-A simplified approach to VHF power amplifier design.





### **Microprocessor Controlled**



The ultimate in communications versatility, the Drake Theta 9000E provides complete transceive capability of CW (Morse Code), RTTY

(Baudot), and ASCII. A full computer RS232 interface, cassette tape storage port, selective calling feature with answer-back, light pen graphics, printer interface and word processing software are all standard.

Seven large 256 character memories are backed up with battery power so there is no need to reload information with each use. Memories may also be partitioned providing up to 29 separate storage locations. A type-ahead buffer of 3120 characters makes it easy to compose your response while still receiving. Operator controlled scrolling permits review of up to 10,720 previously received characters. Line length is selectable at 40 or 80 characters, your choice, and all

mode and speed indicators are displayed on the screen for instant status recognition. The 9000E has 3 tone groups and 3 shifts which are all keyboard selected.



You won't buy any other communications terminal once you have studied all the advanced operating convenience built into the **Drake Theta 9000E**. It's complete.





The Drake Theta 550 is a compact receive-only communications terminal and is designed to demodulate and display the three most popular over-

the air modes of data communications: CW (Morse Code), RTTY (Baudot), and ASCII. Any standard TV monitor can be used.

A full-featured microprocessor controlled unit, the Drake Theta 550 has selective calling, battery backed-up memory, audio monitor, and informative L.E.D. tuning indicators. There is also interfacing to permit the addition of a dot matrix printer for "hard" copy and a keyer paddle input to permit CW transmission with full iambic operation.

CW automatically tracks over a speed range of 5 to 50 words per minute and RTTY modes offer nine selectable standard speeds of transmission. 12 volts DC is required.

This unit is ideal for shortwave listeners and hams who have been missing the increasing volume of data communications over the air.



#### LA7 Line Amplifier

Line output, input levels as low as 15 mV rms (47 kilohm) will result in an output of 1 mW nominal into a 600 ohm balanced line. Output level adjustable by internal preset level control. Interfaces low level audio to RTTY terminal unit or phone line that requires a 600 ohm balanced/unbalanced input. One 36" phono to phono cable supplied.

**R.L. DRAKE COMPANY** 



540 Richard St., Miamisburg, Ohio 45342. USA Phone: (513) 866-2421 • Telex: 288-017

## The Frugal Floppy Bazooka

This 2-meter antenna coils up into a small package, but it shoots a straight signal.

nother 2-meter anten-Ana for your handietalkie? You bet! When you combine low cost, portability, and reasonable gain as this antenna does, it is well worth covering the subject again. The design of this gain vertical was inspired by the excellent article by W11S in the May, 1981, issue of 73 Magazine. One of the current-distribution charts reminded me of the "bazooka" coax-to-dipole decoupling scheme which uses a grounded sleeve in place of radials, and the ''floppy bazooka'' was born.

#### Construction

My prototype antenna was assembled from RG-58A/U (with the stranded center conductor), which is (a) very flexible and (b) what I had on hand. I started with about 20 feet of the cable and terminated one end with a BNC male to match the connector on my HT. The next step is to remove approximately 34 inches of

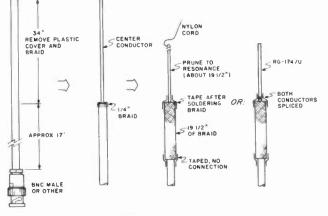


Fig. 1. The floppy bazooka. 32 73 Magazine • December, 1982 the outer cover and braid from the loose end of the coax, leaving about ¼ inch of braid exposed and the center conductor intact.

Why 34 inches if a quarter wave at 146 MHz is about 19 inches? Because I had to compress the braid slightly, increasing its diameter and decreasing its length, to slide it over the feedline. After doing so, 1 carefully soldered the 1/4 inch of exposed braid on the feedline to the braid sleeve, taking care to not melt the center conductor dielectric. I provided as much coverage as possible with the braid splice.

I covered the splice with heat-shrink tubing, although electrician's tape will do fine. Pull the braid down snug on the feedline and now measure the 19½ inches you expected, from the splice just covered to the lower end of the sleeve. I found this dimension to be very noncritical, but the shortening with compression varied from sample to sample of coax, which is why I started with 34 inches! After cutting the sleeve to length, I secured the end to the feedline in the same way I covered the splice.

#### Testing

The first test I made was with an ohmmeter: checking at the BNC end for a potential short. Don't trust the ability to receive a full-quieting signal as proof of proper wiring—I live less than a mile from a local repeater, which breaks the squelch on my HT fine without any antenna plugged in at all!

After avoiding the "smoke test," it was time to prune that 34-inch center conductor to resonance. My first cut was to 20½ inches, and out came the swr bridge. One quarter of an inch at a time, I marched up the band—on low power and avoiding repeater inputs, of course. I found that the antenna would give better than a 2:1 swr over about a 1.5-MHz range,

with 19¼ inches hitting 146 MHz on the nose.

I wasn't thrilled with that bandwidth. so I opted for a simple modification; a "thicker" radiator. I started with a 20-inch piece of RG-174/U, with the center conductor and braid shorted together where they are spliced to the center conductor of the RG-58A/U and shrink tubing again covering the evidence. After the same pruning procedure, this came much closer to my expectations, covering the entire 144-148-MHz band with a worst-case swr of 1.8:1.

#### Use

l attached some 1/8-inch nylon cord to the top of the center conductor with two small wire ties, and the installation problem of a nonself-supporting antenna was solved. The antenna can now be suspended almost anywhere. Bear in mind that it has a very low angle of radiation and must be kept quite vertical to take advantage of its gain characteristics. I chose the 17-foot length of feedline as a reasonable trade-off between losses and the ability to put the antenna in better (higher) places. The antenna and nylon "mount" bundle neatly into a tiny package hardly larger than my HT, making it an ideal traveler's antenna.

My comparison of the floppy bazooka's performance to other antennas was not rigorous, but very satisfying. It significantly outperformed my ¼-wave ground plane in fixed-station use and incredibly outperformed the rubber ducky.

The floppy bazooka is cheap, easy to build, and works very well. It also lends itself well to modification and experimentation. Try it!



COMMUNICATIONS DIVISION



## (We Speak Your Language.)

Backed by over 54 years of experience, Harvey continues to offer the broadest selection and finest service available for the amateur radio community. This experience has taught us that the ham needs special treatment and that is why Harvey has established a special division dedicated to the needs of the U.S. and foreign ham alike.

One thing is for certain. A ham will never get the run around from Harvey. If we don't have something in stock, we say so and will order it for you-or-tell you where to get it. However, we are sincerely dedicated to the ham community and, as a result, our



## **DO ANTENNAS WORRY YOU?**

(NOT TO SCALE)

We feel a novice student has enough to learn without immediately diving into antenna construction. Our new novice antenna is fully assembled and covers all the novice bands and beyond. One of its better features is the price. (At last glance the competition wanted \$123.50 for their fully assembled antenna with coax fitting that covers the four novice/tech bands.)

#### FEATURES:

- 118 feet long
- Heavy Copperweld<sup>®</sup> construction
- 100 feet of 450# test Nylon rope included
- Waterproof center connector with female coax fitting
- · No antenna tuner needed
- 2 KW PEP input rated (750 W on 21 mHz)
- · Retunable when you upgrade
- Installs as low as 25 feet
- Average Bandwidths for 2:1 VSWR:
- 80 meters = 200 KHz plus
- 40 meters = 125 KHz
- 15 meters = 600 KHz plus
- 10 meters = 700 KHz plus

ALL PRICES ARE UPS PAID CONTINENTAL USA Available at your favorite dealer or order direct from:

Van Gorden Engineering P.O. Box 21305 · South Euclid, Ohio 44121

Dealer Inquiries Invited





Includes: • 0.3 µV Rcvr. 8 Pole IF Filter

- Crystals-high stability .0005%
- Local Mic
- Your Call programmed into IDer
- Provision for Auto-Switchover to Btry. Pwr.
- Built-in 115/230V AC Supply; basic Panel Controls, Spkr., LED Indicators

If you're looking for a new Repeater, but you really don't need (or can't afford) all the features and options on our world famous, 'Super Deluxe' SCR1000/4000, then our new economy line of SCR77 Repeaters is ideal for you!

These new Repeaters maintain the quality of design, components and construction which made Spectrum gear famous. However, all of the "bells & whistles" which you may not need or want have been eliminated—*at a large cost savings to you!* The SCR77 is a real "workhorse" basic machine designed for those who want excellent, super-reliable performance year after year—*but no frills!* ('PL', 12 Pole IF Filter, Front End Preselector, and a 30Wt. Transmitter are the only "built-in" options available; but Autopatch, Remote Control, and other equipment can be connected via the rear panel jack.) A complete line of duplexers, antennas, cabinets, cable, etc., is also available.



Of course, if you do want a full featured/super deluxe repeater, with higher power and a full list of available 'built-in' options, then you want our SCR1000 or 4000 "Dream Machine". These units will continue to be available for those who want 'The Ultimate in Repeaters'.

SCR77 Pricing (15Wt.): 2M or 220MHz, \$995.00 Amateur Net. 440MHz, \$1150.00. For no 'plug-in' ID board (Export), deduct \$40.00. Call or write today for a data sheet, or to place your order! Sold Factory Direct or through Export Sales Reps only.

Now located in our new, larger plant! Thanks for your 8+ years of support!



1055 W. Germantown Pk, S12 • Norristown, PA 19401 • (215) 631-1710 • Telex: 846-211

## **Taking It Higher**

Raising a repeater's antenna is the way to wider coverage, right? Wrong.

When it comes to repeaters, higher is better! Right?

Not necessarily. It depends on what you want to accomplish.

Sooner or later, every repeater organization in the country gets the urge to move the repeater antenna up to twice as high as it already is, to improve coverage. Most of the time, it does improve. Every once in a while, though, some unexpected glitches result.

The Tallahassee Amateur Radio Society went through the process of moving from a downtown site with an antenna elevation of about 350 feet to a new commercial tower near the edge of town with an elevation of 800 feet above mean sea level (MSL). Sure enough, coverage was considerably extended. But sure enough, there were several surprising developments. What happened, and why, makes an interesting case study.

We knew from experience that the downtown w 36 73 Magazine • December, 1982

site gave us an effective coverage range of about thirty miles in all directions over fairly mild terrain. South of the city, the coastal plain stretches away to the Gulf of Mexico, flat as a pizza, with an elevation of about 50 feet above MSL. But right in the middle of the city the terrain rises abruptly at the limestone scarp which, a few million years ago, was the coastline when sea levels were higher than now. These hills rise to elevations of 150 to 230 feet, with an average elevation of perhaps 175 to 200 feet above MSL on any bearing in the northern semicircle centered on Tallahassee.

What would happen when we moved from 350 feet to 800 feet? Would we be able to work 75 miles? 100 miles, as some members predicted?

The visual line-of-sight distance from an antenna to the horizon is expressed by the formula  $R = \sqrt{2H}$ , where R is the range (or

radius) in miles and H is the height in feet of the antenna above average terrain. It is the basis, in commercial antenna engineering, for computer calculations of the antenna's performance, cranking in corrections for such things as absorption of radio energy by foliage and buildings, shadowing by hills, and the fact that radio signals can nearly always be heard beyond the visual horizon.

Without benefit of a computer, I modified the formula based on empirical observations of repeater performance in actual operation. The formula is intended to be an approximation, not a precise prediction. I cranked in a number of assumptions about ham radio which do not apply to commercial and public safety services.

For example, most amateurs are willing to settle for less than 100% reliability over a given path. And most of us are willing to accept a noisy signal if it is still readable. The modified formula turned out to be:  $R = \sqrt{2.5H}$ .

Applied to our downtown antenna site, it predicted a contour which agreed well with our experience with the repeater. Here it must be said that a number of other assumptions also must be made. For example, we assume that most mobiles will use about 15 Watts output to a quarter-wave whip, that they will be in motion, that they will have little or no ignition interference, that they have receivers with a sensitivity of half a microvolt or less for 20 dB of quieting, and that the ambient acoustical noise in the mobile will be fairly high.

The critical parameter was defined as the point at which "practical communication" through the repeater becomes possible between a mobile at the fringe of the coverage and a mobile or fixed station located within the full-quieting contour of the repeater. In effect, this boils down to: "Can I use the repeater to get useful information on road directions or weather conditions?"

Once the repeater was installed in the new location, I began collecting data by the simple expedient of working mobiles as they passed through the area and noting their positions when effective practical communication became impossible. Each such observation was noted on a large scale map (half an inch per mile) as a big red dot. Eventually, each of the roads into town became plastered with dots which sometimes covered several miles of road. These "smeared" observation points resulted from the variations between observations. One mobile might be using 25 Watts to a 5/8-wave whip. The next might be running only 10 Watts to a guarter wave. Another might suffer severe ignition noise on reception or his receiver might be "hot" or slightly "deaf." **Propagation** conditions might exert some influence from day to day. The final point on the road was chosen at about the middle of the "smear."

The results of the tests were plotted on a map, with the observation points on the highways being connected by a smoothed line. Circles, also centered on the repeater site, showed the 40- and 50-mile radii. The formula predicted an effective working range of 44 miles, disregarding terrain effects.

The interesting distortions of the working contour are almost entirely the result of terrain. A peculiar flattening in the northwest quadrant results from a ridge of hills along the eastern bank of the Apalachicola River. Mobile signals almost "wink out" when they drop over the crest of the hill into the river flood plain. The southern semicircle bulges outward because the terrain in that sec-



Fig. 1.

tor is substantially lower than Tallahassee and is dead flat coastal plain. The Gulf coast itself cuts off the bottom of what would be a rough circle. No observations were taken from boats in the Gulf. I suspect that the contour would bulge outward in that sector because of the high conductivity of the salt-water ground.

One unexpected side effect is that the repeater signal in the city of Tallahassee is not strong enough to quiet fully most mobile receivers. A possible reason is that the antenna is designed to provide some gain and it does this by taking energy away from the upper and lower hemispheres of the radiation pattern and concentrating it around the "equator." The antenna is so high that most of the city lies in the deprived cone directly below it. The favored lobe of radiation widens gradually as it goes away from the tower, and at 10 miles or so the signal at ground level is quite strong.

Another unexpected

problem arose in early work at the new site. We tried to use the top antenna at 800 feet for receiving and a side-mounted antenna at 485 feet for transmitting. Reflections and other effects resulting from the tower, guy cables, and other factors produced a radiation pattern which was pulled in strongly to the west and had a powerful lobe to the northeast with an effective range of nearly one hundred miles in the favored direction. We solved the problem by using the top omni antenna for both transmit and receive.

The repeater is on 146.31/.91 MHz, and in this area we have very little, if any, co-channel interference unless there's a strong band opening. For a few days, we experimented with a 146.16/.76 machine on that tower. The results illustrate one of the problems which go along with great height. Mobiles trying to bring up the Valdosta, Georgia, repeater on .16/.76 eighty miles away also brought up the Tallahasee repeater. And because of

the strong northeast lobe, our signal was nearly as strong in Valdosta as the Valdosta signal was!

In urban areas, it is entirely possible to cover so large a ham population that the traffic load on a repeater becomes unacceptably high unless access is restricted in some way. When contemplating a repeater on a tower at 2,000 or 3,000 feet above average terrain, it may be desirable to choose a site considerably distant from any expected concentration of ham stations. Otherwise, the area deprived of signal by the antenna gain effect may become a real problem. The effect is greater on UHF than on VHF.

The Stone Mountain repeater near Atlanta, for example, covers Atlanta and most of the surrounding country like a blanket, but it is located about twenty miles east of the city itself. Repeaters located in the Great Smoky Mountains of Kentucky, Tennessee, and northern Georgia cover enormous ranges in their favored directions (where

EAS	ΓМ	IEETS	5 W	EST
Ceco is	now	your num	ber 1	source

for all Japanese semi conductors

TYPE	PRICE	TYPE	PRICE	TYPE	PRICE
AN214	.77	STK439	3.41	2SC1675L	.10
AN241	.71	TA7130	.47	2SC1678	.48
AN313	1.54	TA7193	2.64	2SC1946	8.93
AN7150	1.09	TA7203	1.06	2SC1946A	10.10
BA301	.37	TA7204	.77	2SC1947	3.25
BA311	.37	TA7205	.77	2SC1966	6.05
BA511A	.61	TA7210	1.70	2SC1968	9.49
BA536	.92	TA7222	.68	2SC1969	.91
BA1320	.67	UPC566	.24	2SC1970	.97
BA1330	.74	UPC1025	1.84	2SC1971	2.25
HA1322	1.00	UPC1156	.79	2SC1972	5.45
HA1339	1.10	UPC1181	.56	2SC2026	.24
HA1342	1.15	UPC1185	1.30	2SC2075K	.42
HA1361	.88	UPC1350	.68	2SC2131	2.32
HA1366W	1.05	2SA564	.09	2SC2237	3.72
HA1366WR	1.05	2SA684	.19	2SC2407K	.36
HA1367	.89	2SA733P	.10	2SC2458BL	.08
HA1377A	1.30	2SA950Y	.13	2SC2458Y	.08
HA1388	1.82	2SA1048Y	.08	2SC2459	.11
HA1397	1.63	2SA1048LY	.15	2SC2549	.11
HA1398	1.42	2SB172	.15	2SC2668-0	.09
LA1111	.41	2SC730	2.00	2SC2695	11.69
LA4030	.90	2SC940	.88	2SC3019	1.39
LA4031	.90	2SC945	.08	2SC3021	8.35
LA4032	.95	2SC945AQ	.08	2SC3022	12.49
LA4050	.86	2SC1096	.25	2SD388	1.09
LA4101	.86	2SC1165	3.45	2SD588	.91
LA4400	1.07	2SC1172B	1.99	2SK102GR	.40
LA4420	.70	2SC1177	7.25	2SK117GR	.19
M51513L	.80	2SC1306	.65	2SK168E	.16
STK013	4.30	2SC1307	1.60	25K241Y	.22
STK435	2.95	2SC1308K	2.66	3SK39	.55
STK437	3.07	2SC1314	14.68	1	

Ceco is also your largest source for semi conductors including RF transistors, RCA SK replacements, RCA MRO, ECG's & GE. Take advantage of CeCo's money saving prices and off the shelf service.

Remember Ceco Fe	or All Your Tube, Video a Cetalog on Request	nd CCTV Requirements
Celo	Call Toll Free: 800-221-0860 Telex: TWX 235125 Cat 2115 AVENUE X + BR(	

mountainous terrain doesn't block the signals) and they serve a largely rural population without the dense concentration of stations which might cause problems in, say, New York City, Chicago, or Los Angeles.

It should be kept in mind, when trying to apply our rule-of-thumb range formula to other locations, that terrain is often a much bigger factor than it is in Tallahassee. The formula will give reasonably accurate results only when it is applied to one particular radius using the "average terrain elevation" along that particular line. A repeater in Iowa may well have an almost circular pattern. A repeater located in California or West Virginia is likely to be a totally different matter. The formula is not applicable directly to repeaters on bands other than two meters because

terrain losses will not be the same. However, on any band, range will vary in direct proportion to the square root of the height of the antenna, and it should not be difficult to work out a new H multiplier which would give reasonably accurate results on, say, 50, 220, or 450 MHz.

Clubs which put up repeaters with wide coverage areas should be prepared to welcome and to serve many itinerant mobiles travelling through the area who may frequently be more interested in working each other than in working locals. Repeater groups that want to communicate among themselves for rag-chew, emergency, or other purely local communications purposes should give serious consideration to using a lower antenna site or a closed repeater operation using some form of restricted access.





Requires only 60" corner space Formica desk top and shelves Shelf height adjustable Solid maple legs \$495.00 check or M.O. Shipped freight collect Allow 30-45 days delivery Send for detailed brochure

> CQ PRODUCTS 8280 Janes Ave. Suite 137–1700 Woodridge, IL. 60517

152



Weight of table is 250 lbs.

# Put Your Computer "On-The-Air"

## CW Off RTTY-CW-UP Terminal Unit CW Off RTTY On Tune

### The interface<sup>tm</sup> Sugg. Price \$189.95

Your personal computer becomes a complete CW/ RTTY/ASCII send and receive terminal with The Interface linking it to your transceiver.

If you own an Apple II or Apple II Plus, Atari 400 or 800, TRS-80 Color Computer, or VIC-20, The Interface will put your computer "On-The-Air".

Software for each system features split screen display, buffered keyboard, status display, and message ports. Attach any Centronics compatible printer for hard copy. Software is available, on diskette for the Apple and program boards for the others, at an additional cost.

Apple	Atari	VIC-20	TRS-80C
diskette	board	board	board
\$29.95	\$49.95	\$49.95	\$59.95

See The Interface at your authorized Kantronics dealer, or contact:



(913) 842-7745 1202 E. 23rd Lawrence, Kansas 66044






wave

8/8

Drive Level	Output Power	Model Number
150-200 mW	25W	2C025-200 mW
1.5 W	20-25W	2C025-2W
1.5W	45-50W	2C050-2W
1.5W	80-90W	2C100-2/25
2W-5W	>30W	2C025-2W
2W-5W	>50W	2C050-2W
2W-5W	>100W	2C100-2/25
10W	100W	2C100-10/25
25W	100W	2C100-2/25
25W	100W	2C100-10/25

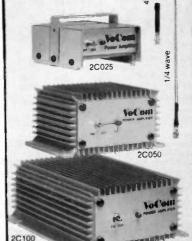

#### with range-extending products from VoCom

25, 50, or 100 Watts Power -- Whatever your present output level - from 200 mW handheld on "battery saver" mode to 25W mobile or base - you can use that to drive a compact, 12V power amp from VoCom for much more talk-out power (see chart). Each model has a front panel switch to let you go "barefoot" for short hauls, plus an L.E.D. indicator to show the mode you're in. Full 10 MHz bandwidth gives you virtually unchanged power across the entire 2-meter band. High efficiency design holds down generated heat, low input VSWR saves battery drain by your radio's final amp. Use the chart to see which VoCom Power Amplifier gives you the power out you'd like from the power that you now have.

Power Pocket<sup>™</sup> Mobile Amplifier/Charger — Simply plug in your Icom IC-2A(T) and you have a 25W synthesized mobile rig take it out again, all charged and ready, when you want hand-held operation. Accepts any IC-2A version. Delivers 25W RF output, 2½W audio with 4" speaker to overcome road noise. Charge pocket accepts all Icom battery packs, has independent charging switch, indicator. MIc preamp makes Power Pocket compatible with any mobile microphone and with Icom speaker/mic.

5/8 HT Gain Antenna boosts reception while giving your hand-held full quieting out of spots you're nearly dead in with a rubber duck; provides excellent improvement. Only 8" telescoped, 47" extended. Better than 1.5:1 VSWR. BNC connector.

Spring-loaded 1/4 wave antenna and 4" stubby duck also available. See your favorite amateur radio dealer.





#### PRIVATE PATCH

Introducing Private Patch. A giant step forward in non-sampling Autopatch/ Interconnect technology, capability and standard features. Our revolutionary new techniques of audio and digital signal processing offer several advantages over conventional sampling/ scanning type Autopatches: 1. The annoyance of continuous squelch tails eliminated. Makes totally is conversation much more natural and enjoyable. 2. In addition to superb simplex capability, operation through repeaters is made possible. 3. The only connections made to your base transceiver are to microphone and NO jacks. INTERNAL speaker CONNECTIONS OR MODIFICATIONS **NECESSARY! Use Private Patch simplex** for local operation, through a repeater for extended range. CW ID makes your Autopatch legal, and alerts you to incoming calls when ringback is turned on. Channel monitor logic precludes ringback transmission if channel is in prior use. Eliminates accidental interference. Five digit owner programmable access code and operator/long distance inhibit switch assure security and protect your phone bill. Positive control is assured by Private Patch logic functions. A fully digital timing approach eliminates all Timing adjustments. Three/six minute timer shuts down Private Patch if you drive out of range. Resettable with reset code for additional talk time as required. Self contained AC supply. Modular phone jack and modular phone cord provided. All electronics contained on one high quality glass circuit card. Private Patch contains 42 integrated circuits and 16 transistors. Send for additional information. Compare our features. (State callsign when ordering.)



Power Pocket

## **BARKER & WILLIAMSON** VERTICAL ANTENNAS

#### MODEL 370-31

Slim Line Vertical designed for 10, 15, 20 and 40 meters. All traps pretuned. Overall height 21 feet. Can be used with or without ground radials. Model 370-33 - 75 meter add on kit. 75 and 80 meter operation optional with model 370-33 add on kit. Power rating 1 KW-2 KW P.E.P.

#### MODEL 370-30

Economy model vertical for 10, 15, 20 and 40 meter operation. High Q factory tuned traps. Overall height 21 feet. Can be used with or without ground radials. Model 370-32 — 75 meter add on kit. 75 and 80 meter operation optional with model 370-32 add on kit. Power rating 1 KW-2 KW P.E.P.

#### MODEL 370-34

Radial Kit. Radial Kit for Models 370-30 and 370-31 Vertical antennas. All necessary wire and hardware for two ground plane radials. Write for more details and other antenna products.

Barker & Williamson, Inc. 10 Canal St Bristol, Pa. 19007 215-788-5581 -11

#### **RTTY - 50 Basic Terminal Unit**

• 60 mA Loop Keying PLL Demod w/2 pole filter AFSK Generator

• AESK **7Q**00

Call or write for FREE catalog with over 65 P.C. Boards & Kits.

**RTTY - 100** Expanded Version of the Popular **RTTY - 50** 

• 850/170 • TTL & RS232

• 60 mA Loop

 Loop Supply · Auto Start

• 4 Pole Filters • AGC (80db)

\$18900

#### COMMUNICATIONS DESIGN INC.

1105 Lehr St. - West Memphis, Arkansas 72301 (501) 735-4568

Surge protection plus master control for all your equipment

### At \$79.95. new Alpha Delta MACC is very low cost "insurance" on your total investment

Modern solid-state circuitry is even more vulnerable to that old bugaboo, lightning. Strikes miles away can cause damage. So can transient currents from such common things as electric motors and fluorescent lights.

But Alpha Delta Master AC Control Console's 3-stage automatic restorable circuitry clips off the power surges and spikes to provide clean AC power. Its resettable circuit breaker adds further protection.

MACC gives you control convenience, too. It provides 8 plug-in "U" ground outlets for your components-including one "hot" for a continuously powered appli-

- 193

-• [] • ]

cation such as your clock. Seven "on/off" rocker switches let you control individual components. And you can turn your entire system on or off with a single master rocker switch.

All switches light up when "on" to confirm system condition.

MACC is tested to IEEE pulse standards and rated at 15A, 125VAC. 60 Hz, 1875 watts continuousduty total for console. See label for surge protection limitations.

Get MACC protection. Whatever the price, it can be the most important buy you make.

ALPHA DELTA Model MACC Master AC Control Console \$79.95 (U.S.)

At your Alpha Delta dealer. Or in U.S., order direct, adding \$4 for postage/handling to check or money order. (Ask for quotes on overseas postage and 240VAC MACC-E with VDE-approved sockets.) MasterCard and VISA accepted. Ohio residents add Sales Tax. Sorry, no C.O.D.'s


COMMUNICATIONS D P.O. Box 571, Centerville, Ohio 45459 • (513) 435-4772 A



## peace of mind vour 0L

wind-load area etermine

	ANTENNA WIND	ANTENNA WIND-LOAD CAPACITY
ROTATOR MODEL	MOUNTED INSIDE Tower	WITH STANDARD Lower Mast Adapter
AR22XL or AR40	3.0 sq. ft. (.28 sq. m)	1.5 sq. ft. (.14 sq. m)
CD45 II	8.5 sq. ft. (.79 sq. m)	5.0 sq. ft. (4.6 sq. m)
HAM IV	15.0 sq. ft. (1.4 sq. m)	N/A
Τ²Χ	20.0 sq. ft. (1.9 sq. m)	N/A
HDR300	25.0 sq. ft. (2.3 sq. m)	N/A
	For HE antenness with boome over	boomo outor

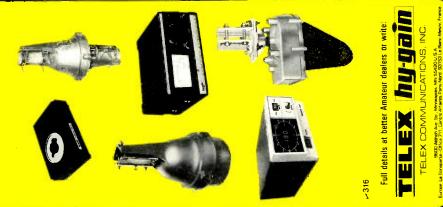





## **ORDER TOLL FREE 1-800-448-9338**

FEATURING: Kenwood, Yaesu, Icom, Drake, Ten-Tec, Cubic, Dentron, Alpha, Robot, AEA, Telrex, Astron, Avanti, Belden, CES, Daiwa, J.W. Miller, Panasonic, B&W, Mirage, Vibroplex, Bencher, Info-Tech, Universal Towers, Callbook, ARRL, Astatic, Shure, Tempo, VoCom, KLM, Hy-Gain, Larsen, Cushcraft, Hustler, Mini-Products, Bird, CDE, Rohn, Alliance, MFJ, Bearcat, Telex, Nye, Palomar Eng., Kantronics, Havden, Ameco, Collins, Saxton

We provide factory authorized warranty service for most major lines of equipment, and after-warranty service on all other brands. Write or call for a quote. You Won't Be Disappointed.

We are just a few minutes off the NYS Thruway (I-90) Exit 32



ONEIDA COUNTY AIRPORT TERMINAL BUILDING **ORISKANY, NEW YORK 13424** -397 N Y Res Call (315) 736-0184

Warren - K2IXN Bob - WA2MSH AI - WA2MSI

HF BROADBAND VERTICALS WORK THE WORLD state rigs, require minimal space and provide low angle radiation without the expense or the problems of support structures.

hy-gain.

18AVT/WBS (80-10 meters) The most successful vertical antenna of all and for good reasons. Broadband performance covers the 40, 20, 15 and 10 meter bands in their entirety. Automatic 5 band switching is accomplished by mechanically superior, highly efficient factory tuned Hy-Q traps with large coils for consistent perform-ance at 2:1 or lower VSWR on 40-10 meter band edges; bandwidth on 80 meters is approximately 40 kHz with VSWR below 2:1 A factory tuned matching network for 50 ohms impedance is dc grounded for lightning protection and reduced precipitation static The mechanical integrity of this antenna is so stable that performance does not change with the weather. The 18AVT withstands winds to 80 mph (128 km/h) without guying. All stainless steel hardware is included


14AVQ/WBS (40-10 meters) Offers very similar construction and the same excellent broadband performance as 18AVT over the entire 40, 20, 15 and 10 meter bands; automatic band switching with mechanically superior large-coil Hy-Q traps and very low angle radiation pattern. The smaller, low visibility size also makes the 14AVQ very suitable for roof mounting. The optional 14RMQ roof mounting kit includes base plate, mast and radial/guy wires All antenna hardware is stainless steel

18 HTS (80-10 meters, 160 meters with optional loading coil) The superb reliabliity of the 18 HTS is manifest in installations now over 20 years old. And, with the Improvements we made over the years, the 18HTS is now better than ever. Automatic band selection is achieved through a unique stub decoupling system which effectively isolates various sections of the antenna so that an electrical ¼ wavelength (or odd multiple ¼ wavelength) exists on all bands. For example, outstanding broadband performance on 20, 15 and 10 meters is achieved with an extended 3/4 wave collinear. On 80 meters bandwidth is approximately 250 kHz at 2:1 VSWR. With the optional base loading coil exceptional performance Is also provided at 160 meters. The galvanized tower requires no guying and withstands winds to 100 mph (160 km/h). A special hinged base allows complete assembly at ground level and permits raising and lowering. Includes stainless steel hardware Pasy WARC kits to be available.

Other Hy-Gain vertical multiband antennas are available though not shown here. The 12AVQS (20, 15, 10 meter) is similar to 18AVI above but with VSWR of 1.5:1 or less on all bands. The 18VS (80-10 meter) comes with a base loading coil and may be installed on a short mast driven into the ground. All include stainless steel hardware.
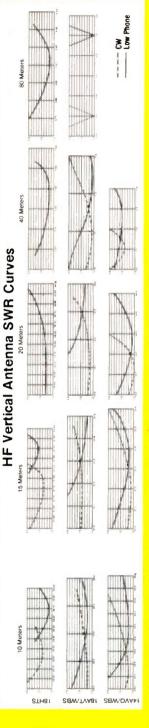
#### PHASE FOR GAIN

Any two identical Hy-Gain verticals can be phased for excellent gain and directivity. A great system for beam performance on 40, 80 and 160 meters or for 10, 15 and 20 meters where space is limited. Send for our free technical report "Phased Verticals".







9600 Aldrich Ave. So., Minneapolis, MN 55420 U.S.A. Europe: Le Bonaparte-Office 711, Centre Affaires Paris-Nord, 93153 Le Blanc-Mesnil, France.

HTS 50' (15.2 m)

14AVQ/WBS 18' (5.5 m)

Ê

AVT/WBS 25° (7.6

## **Dial-A-Frequency**

Let your fingers do the walking with this remote control. All you need is a spare telephone.

Ave you ever had a need to remote control a multi-channel radio over a distance but didn't want to run a multi-conductor cable? I have a Heathkit® HW-202 two-meter radio that is located in my shop which is in a barn about 150 feet from the

house. I wanted to be able to use the radio in both the barn and the house without moving it. One solution to this problem is described here.

The system I developed allows me to dial up any one of four channels in my two-meter radio. This is done using a standard dial telephone with a minor modification for push-totalk operation. The telephone is connected to a controller via a single pair of wires that can be several hundred feet long. Several phones may be connected to the line, although only

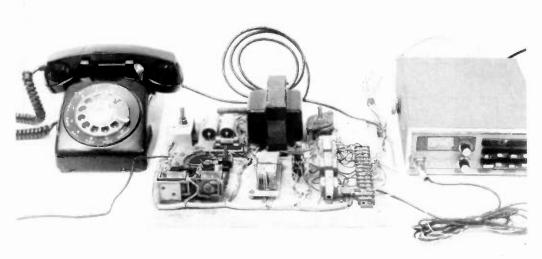



Photo A. Overall view of the remote two-meter dial-up system. The telephone can be located several hundred feet away from the radio and its controller.


one may be used at a time. Of course, the telephone may be moved about by using jacks.

I'll review a little of telephone basics, go into the development of the system, talk about construction details and adjustments, and offer some afterthoughts that you may want to include in your version. Successful duplication of the ideas presented depends on how resourceful you are, as some of the relays and transformers may be difficult to find.
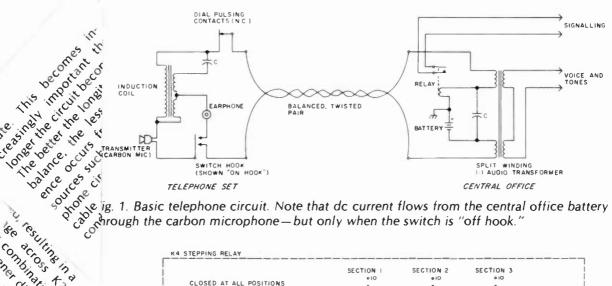
#### **Basic Terminology**

We all use the telephone every day. It seems to be a simple enough device, and on close inspection, it is. Fig. 1 shows the basic circuit from the telephone to the central office. The two wires that connect these two locations are a twisted, balanced pair with a typical characteristic impedance of 600 Ohms. Longitudinal balance describes how closely each conductor matches the other along the



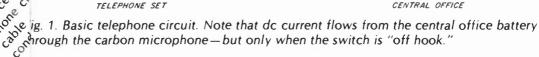

K4 STEPPING RELAY SECTION SECTION 2 SECTION 3 •10 CLOSED AT ALL POSITIONS EXCEPT POSITION #1 RESET STEP CHANNEL CONTROL 6.3 VAC 12 VDC RADIO SUPPLY + 12 VDC TO PADIO (SEE EIG 5) ALL UNMARKED DIODES ARE LAMP - 50 PIV 48 V D C - 35 VDC к2 PUSH TO TALK COMMON P 200 12 V T2 6000:60 60 FROM T3 600Ω:60# 11 6000:6000 60K TO MICROPHONE к 3 } 1-2µF IOK TRANS-MIT LEVEL PAPER TELEPHONE

Fig. 2. Schematic diagram of the dial-up two-meter remote controller.

applicable) are coupled through to the other side of the transformer. The capacitor shunting the power supply and relay coil on the line side of the transformer bypasses audio frequencies

The circuit shown in Fig. 1 is the basis of my two-meter dial-up remote controller. I won't go further into the operation of the central office, but if anyone is interested in further study in this area, Basic Telephone Switching Systems by David Talley (Hayden Book Company, New York NY) makes good reading.

#### Development of the Dial-**Up Remote**

There are three control

functions that must be provided in the two-meter dialup system: the off-hook condition, dial pulses, and push-to-talk function. These three functions are provided by relays K1, K2, and K3, respectively, in Fig. 2. The telephone set itself must be modified to provide push-to-talk operation. More about this later.

73 Magazine • December, 1982 45

the than a k Joltage abour 10,1314 AC1055 , pops in Citor Sice ,ent continuity .ement of the cir-Jr signaling and to ide a dc bias current or the carbon microphone in the telephone. When you lift the telephone "off hook," the dc circuit is completed with current flowing through the microphone. When you turn the dial clockwise to the stop, a spring is wound up in the dial. When the dial is released, the spring returns the dial and a set of contacts opens and closes once for each digit dialed at a rate of 10 pulses per second. Many modern central offices can respond to 20 pulses per second, so some phones are so equipped. A tone-dial phone still requires a dc continuous circuit to tell the central office when it is off hook and to have dc bias for the carbon microphone and tone generating circuits.

Creasingly

route.

80

vas used in

o combination tenet diode

to

2

This

At the central end of the circuit note the one-to-one ratio transformer with a split winding on one side. This transformer allows the insertion of dc current and the picking off of the control signals while maintaining the circuit balance to ground. At the same time, voice and tone signaling (if

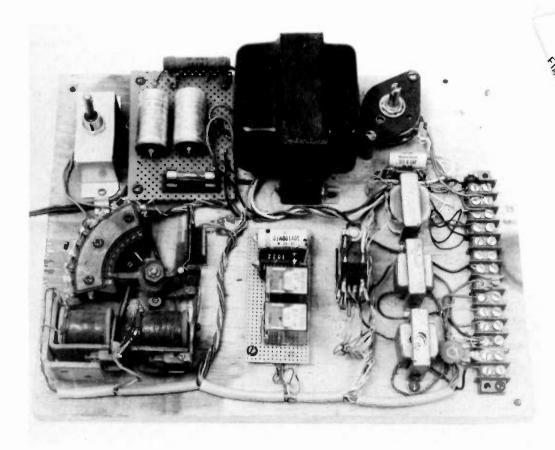


Photo B. The controller with power supply at the rear, stepping relay at the left, K1, K2, and K3 in the middle, and the audio transformers next to the terminal strip on the right.

When the telephone receiver is lifted off hook, the dc circuit is completed from the 35-volt source to K2 and to the series combination of the 12-volt zener diode and K3. Contacts on K2 apply 35 volts to K1 and charge C1 through R1. R1 is necessary to prevent contact arcing on K2. Now that K1 is picked up, the 48-volt source is removed from the reset coil on the stepping relay and applied to contacts on K2 which are connected to the stepping coil. A separate 48-volt source was necessary because of the particular stepping relay that I had available.

What happens now if the dc loop to the telephone set is broken for a fraction of a second by dialing a "1"? Relay K2 drops out for a brief period and picks up again when the dc loop is again completed. This removes the 35-volt source from K1 briefly, but the charge on C1 holds K1 closed through the diode. The 48-volt supply is therefore maintained to the contacts on K2 which close for the brief time that K2 drops out. This applies a single pulse of 48 volts to the stepping coil, advancing the switches one step to position two.

If you were to hang up at

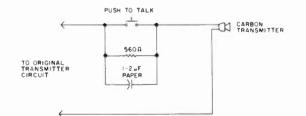


Fig. 3. Telephone set modification for push-to-talk operation.

this time, relay K2 would immediately drop out. Relay K1 would remain energized for about one-half second because of the charge on C1. When K1 finally drops out, the 48-volt supply is applied to the reset coil. Because the switches are not in position one, the reset contacts on the stepping relay are closed. The reset coil will therefore reset the switches to position one, at which point the reset contacts on the stepping relay again would be open.

If we now lift the receiver and dial, for example, a three, the switches will advance to position four and stay there until we hang up again. Note that the stepping and reset coils never have voltage applied for any length of time. They usually are rated for intermittent duty only. Note also that dialing 12 or 21 has the same effect as dialing a three.

3 shows the modifi to, in modifier at a, loop, o, o, " II alle When the ton in X pressed, t tor is short higher volt and the serie of K3 and the A zener diode series with K3 ra resistor so all of th difference brough by pushing the push button would appear the relay. The capa shunts the resistor for v frequencies.

Relay K3 must be selected carefully. It must have a drop-out voltage not much less than its pick-up voltage. The unit I used has a 12-volt coil and is a plugin type from an old IBM keypunch machine. Most 12-volt relays will pick up at about 10 volts but many will not drop out once picked up until the voltage is less than three or four volts. The variable resistor in the power supply (Fig. 5) is adjusted for proper pushto-talk operation. You may want to experiment with electronic circuits to sense the push-to-talk voltage change and which would, in turn, drive the push-to-talk relay. Another alternative would be to run a separate pair of wires for the push-totalk button.

The push-to-talk relay, K3, grounds the push-totalk line to the radio and switches the 600-Ohm audio from the split-winding transformer, T1, between the radio microphone input and speaker output. Impedance matching is required on both of these circuits. I used some small, 120-to-12volt (10:1 ratio) filament

46 73 Magazine • December, 1982


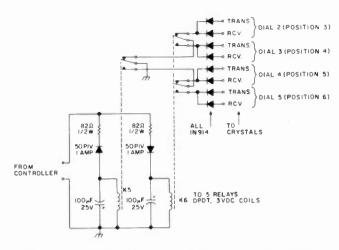


Fig. 4. Channel-change circuit located in the radio.

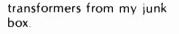

The stepping relay that I used has three switch sections. It is a C.P. Clare model A321033 that was salvaged from an electrical circuit recloser. One section is used to connect the telephone circuit to the radio. This allows me to dial up other devices on other positions of the stepping relay, such as a weather receiver. The second section turns on the power to the two-meter transceiver. The third section changes channels in the radio. Stepping relays are available from time to time from surplus outlets such as Fair Radio Sales, 1016 East Eureka Street, PO Box 1105, Lima OH 45802

Fig. 4 shows the channelchange circuit. Two miniature relays are used to select the appropriate crystals in the Heath HW-202. The resistors in series with the relays are necessary because the relays I had available have 3-volt coils. Note that when the stepping relay is in position three, neither relay is energized. When in position four, K6 is picked up, when in position five, K5 is picked up, and when in position six, both relays are picked up.

In each case, a different pair of crystal switching diodes is grounded. I disconnected the radio switch grounds from the chassis ground and reconnected them to be grounded when neither relay is energized, position three. This allows me to select with the radio switches which channel will be selected when dialing a two. It also allows the radio channel switches to function normally when not connected to the controller or when the controller is switched off. The other three positions are con-

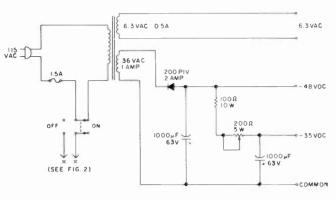


Fig. 5. Power supply schematic diagram.

nected to the crystals of the most commonly used channels.

The power supply, Fig. 5, is straightforward. A small amount of 6.3-volt ac power is required for the channel-changing circuit. The 36-volt secondary on the transformer gives about 48 to 50 volts dc for the stepping relay. It must be capable of supplying the intermittent current requirements of the stepping relay, about 1 Ampere in my case.

Dropping resistors are used to supply a lower volt-

age for operation of K1, K2, and K3. This voltage should be relatively hum free as it is also used to bias the carbon microphone. The dropping resistor is made variable to allow setting the push-to-talk operating point. Positive grounds are used as this is telephone system convention but it certainly isn't necessary. If negative grounds are desired, it is only necessary to reverse the polarity of C1, the diodes associated with K1 and K3, and, of course, the power supply capaci-



Photo C. Modified telephone set. Note the push-to-talk button in the handset and the resistor-capacitor combination mounted on the added terminal strip.

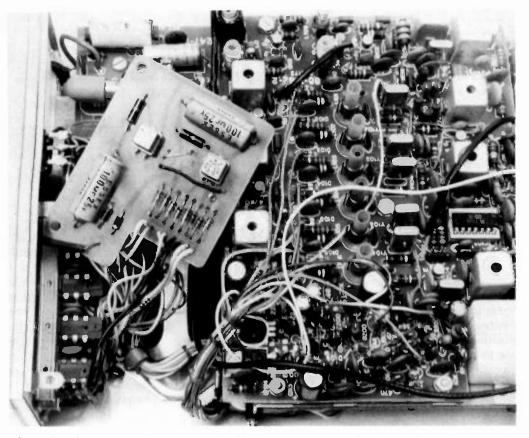


Photo D. Channel-change relay circuit board. The ungrounded side of the circuit pokes through the plastic filler where the burst encoder push-buttons would be located.

tors and diodes. Power supply requirements for other versions will probably be different depending on what relays the junk box and local surplus outlet may yield. Switch S1 turns on the power to the radio when switching the controller off so that the radio can be used in a normal fashion.

#### Construction

As can be seen by the photos, I mounted all components on a piece of wood. While this method of construction is simple and effective, it is not terribly attractive. I plan to reconstruct the unit in a  $3'' \times 10'' \times 17''$  chassis mounted on a  $3\frac{1}{2}'' \times 19''$  relay rack panel. Layout is not critical.

Modification of the telephone consists of removing the bells to make room for a terminal strip on which to mount the added resistor and capacitor. See Photo C. The handset must be changed to a push-to-talk type (available from Graybar Supply, 345 Harrison Avenue, Boston MA 02118, and from Fair Radio Sales, previously mentioned). The resistor-capacitor-switch combination can be inserted anywhere in the dc current loop.

The channel-change relay circuit board (Photo D) was etched using a Radio Shack etch resist pen and etchant. The board is simple enough that no fancy techniques are required. Foil layout will vary depending on your radio and the relays you can find. The ungrounded side of the channel-change circuit clips to the wire poking through the plastic filler where the burst encoder would go. This can be seen in Photo A.

Cables between the controller and the radio should be only a few feet long because of the high-impedance microphone circuit. Run a separate return lead for the channel-change circuit. Otherwise, the return current will flow on the microphone cable sheath resulting in transmitted hum.

The 12-volt dc leads should be fairly heavy to carry the 2.5 Amperes or so required on transmit. The push-to-talk lead goes into the microphone connector with the microphone cable. Make the speaker connection to the remote speaker outlet and throw the speaker switch on the radio.

The connection between the telephone and the controller is a single pair of telephone wires, typically number 19. I use about 150 feet of ordinary telephone wire, but distances up to one-half mile or possibly more should work. The limiting factor will probably be getting the push-to-talk relay to operate properly due to additional resistance of the phone line.

#### Adjustments and Operation

The first adjustment is to set the variable resistor in the 35-volt portion of the power supply. Start by setting it for maximum resistance. Then with the pushto-talk button on the telephone pressed, decrease the resistance until K3 picks up. Note the position of the resistor shaft. Releasing the button should cause the relay to drop out. If it doesn't, the push-to-talk relay you've selected must be replaced with a different type with a higher drop-out voltage. Assuming your relay did drop out, continue decreasing the resistance while pressing and releasing the button. Note the point where the relay will no longer drop out. Set the variable resistor midway between this point and the point where the relay first picked up.

Setting the transmit level can be done several ways. The ideal way would be to use a deviation meter. Barring that, connect a VTVM set for ac to the microphone connector terminals at the radio. Note the level range for normal speech while using the radio's microphone. Now disconnect the microphone and connect the controller. Adjust the transmit level on the controller for a similar range while speaking normally into the telephone microphone. A third possibility would be to use onthe-air reports.

Once you've gotten everything working, operation is very simple. Lift the telephone receiver and dial a two for the channel selected on the radio switches, a three, a four, or a five for the specific channels you've chosen. You'll need to set the volume for a comfortable level in the telephone receiver. By switching the power supply to the off position, reconnecting the microphone, and switching back to the internal speaker, the radio is restored to normal operation including the channel selector switches.



#### Afterthoughts

If you don't mind running extra conductors between the controller and the radio, it would be simpler to run separate conductors for each channel rather than to use the relay switching scheme. The 6.3-volt winding wouldn't be required on the power transformer and there would be no concern about transmitting hum from the channel-change circuit. Also, more channels could be dialed.

Some stepping relays available from surplus outlets have more than 20 positions. All positions could be used by dialing digits that add up to the desired position minus one. For instance, to step to position 19 you would dial "99", "80", or "08".

The output of a dial-tone generator could be connected to position one of section one of the stepping relay. You might leave power connected to the radio at all times and have a tonedial decoder on the audio output ring a bell. Fellow hams can then reach you by using their tone-dial pads without you having to monitor the channel. Position one of section three of the stepping relay would select the appropriate channel.

#### Conclusions

I've described a system that will dial up channels remotely in a two-meter FM radio using a standard dial telephone. With it you can place as many remotes as vou want at considerable distance from the radio on a single pair of wires. It has been in everyday operation. I've also offered some ideas for expansion to include other services. With this system as a basis, use your imagination and you can develop a great system to suit your own needs.

#### WHEN YOU NEED JUST A LITTLE MORE AUDIO

The **F4STR4K®** model 2003 audio amplifier module produces 250 mW of low THD audio. This transformerless design has a low parts count and does not require a heatsink.

The model 2003 features a dc-operated volume control. Output level is selected by changing a dc voltage with an on-board pot, remote pot or micro-computer D/A interface.

- Low-Z, ac-coupled output drives speaker or headphones.
- Dc-type volume control assures hum-free operation without using shielded cable to the volume control.
- No interstage transformers or heatsinks.
- Compatible with other FASTRAK® modules, such as the model 2002 sound synthesizer.
- One evening assembly using 3.6 by 1.0 inch pc board and instructions supplied.
- Price: \$9.45

Price includes: glass-epoxy, etched, plated, drilled pc board; instruction manual; postage in U.S.A. (Ohio residents add 5% sales tax).

Send \$1.00 for illustrated F4STT44K\* product catalog and refund coupon.





# You've got to get a Santec

Compare Santec to anything you like, and you'll see — you've got to get a Santec to get: memory channels which store standard repeater offsets for instant recall less than 10 ma drain in receive to conserve power while you're monitoring extremely wide power options of 0.1 W, 1.0 W or even 3.5 W for varying conditions an accurate 24 hour clock for instant reference and a full two year extended service plan which no one else will match.

When you get a Santec, you also get:  $\blacksquare$  the widest frequency range of any handheld  $\blacksquare$  odd offsets other than  $\pm$  600 kHz  $\blacksquare$  variable step sizes in bandscan a 500 ma battery with charger a full six digit back-lighted LCD display for full frequency readout plus the memory channel number 🔄 the easiest keyboard entry of any handheld 🔜 eight modes of scan, search, manual control and open scan 🔳 the ability to change batteries without losing memory data deasily programmable bandscan a frequency lock switch on the keyboard data an automatic low battery indicator data much more.

FEATURE	SANTEC ST-144	YAESU FT-208	KENWOOD TR-2500
Size (mm)	68 x 170 x 47	61 x 168 x 49	66 x 168 x 40
Weight with Batt	600 gm	720 gm	540 gm
Readout	LCD (full 6 digits)	LCD (4 digits)	LCD (4 digits)
Memory Channels	10	10	10
Memory of Offsets	YES	NO	NO
Memory Backup	YES, Capacitance	Yes, Lithium Batt.	Yes, Lithium Batt.
Search Mode	YES	NO	NO
Step Size	5-100 kHz	5 or 10 kHz only	5-30 kHz
Battery	Quick Change Pack 500 ma-hr, 9.6 V	Quick Change Pack 450 ma-hr, 10.8 V	Slide-on Pack 400 ma-hr, 8.4 V
Frequency Coverage	142-148.995 Tx (149.995 optional) 142-149.995 Rx	143.5-148.495 <b>Tx/</b> Rx	143.9-148.995 Tx/Rx
Power (max)	3.5 W High 1.0 W. Med.	2.5 W High	2.5 W High
	0.1 W Low	0.2 W LOW	
Priority	YES (in Mem Scan)	Yes (Priority Ch.)	NO
Clock	YES	NO	NO
Computer Current			
Saver	YES (~ 10 ma)	NO (20 ma)	NO (27 ma)
Display	6 Digits - Mem. #	4 Digits + Mem. #	4 Digits

New! Affordable Price! See your Authorized Santec Dealer for details.

Competitors' specifications were obtained from published specifications sheets, and they are subject to change without notification to Santec or Encomm, Inc.



Shown with optional SM-3 speaker microphone



Accessories for SANTEC Handheld Radios clockwise from upper left Leather Case (ST-L)

Base Charger & Power Supply (ST-58C) Remote Speaker (#5-50S) Mobile Charger (ST-MC) Speaker Microphone (SM-3) The ST 144 µP is approved under FCC Part 15



1982, Encomm, Inc. 2000 Avenue G, Suite 300, Plano, Texas 75074 Phone (214) 423-0024 • ILX 79-4783 ENCOMM DAL Repairs, Parts & Ser-ce Available

All stated specifications are	subject to change without
Encomm, Inc. 2000 Avenue G	Please send me more in The ST-144/µP

Encomm, Inc. 2000 Avenue G Suite 800 Plano TX 75074	Please send me more information about: The ST-144/µP Authorized SANTEC Dealers

CALL

otice or obligation

NAME

ADDRESS

STATE ZIP CITY YOU MAY SEND A DUPLICATE OF THIS FORM.


## **Improving God's IDer**

Put more flexibility in the K2OAW circuit and save the advantages of the original.

have been a fan of Peter Stark's K2OAW IDer ever since the original design first graced these pages back in 1973. The simplicity

of programming the thing, the low parts count requirement, and the lack of those hated Kernaugh maps made this, for me, the ideal IDer circuit. In the years since its first appearance, I have built maybe half a dozen of these circuits for my various repeaters and those of a few of my friends.<sup>1</sup>

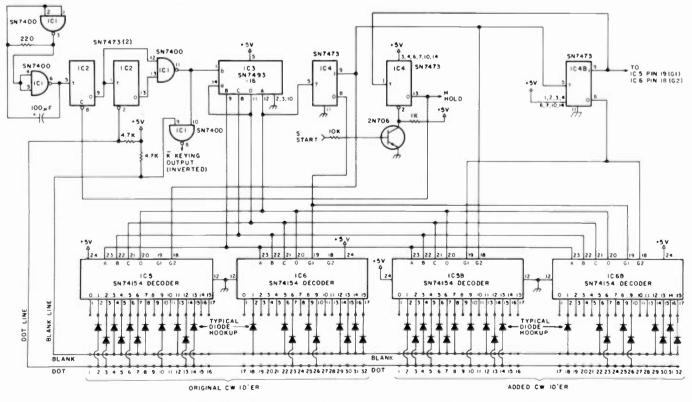With the advent of the FCC's decision to drop "R" calls for repeaters, regular





73 Magazine • December, 1982 51

amateur callsigns, followed by "RPT" or "/R", have generally necessitated more character space than the old K2OAW circuit could provide. So, a couple of years ago, Peter obliged the troops with an update of that original design which doubled, from 32 to 64 characters, the amount of information available for use in the IDer.<sup>2</sup>

However, though a lot of us need more than 32 characters for our ID, we don't always need all 64 of 'em, particularly those of us who believe that a repeater ID should say its legal piece and shut up. So, for those who wish to keep the ID process from continuing long after the CW is gone and to save a lot of diodes for the blank line, I hereby propose the "K2OAW IDer Update Update." As you will see, the improvements cover a lot more than what I've talked about so far.

Fig. 1 is the K2OAW ID circuit update as it appeared in the June, 1979, 73. Peter added just 3 ICs, a 7473 (IC4B), and two 74154s (IC5B and IC6B) to accomplish the doubling of capacity. I changed the "ID hold" half of the original 7473 IC4B to a 74C76 (C? Yeah. Read on.), now called Z11A. and added one more IC, Z8, a 74CO2 guad NOR gate. A 4001 would work just as well. To top things off, IC1A and IC1B, which comprised the clock oscillator in the original K2OAW circuit and its update, were scrubbed in favor of one half of an NE556 timer chip, running in the astable mode, with the other half being used for the ID audio oscillator. More on this later.


Fig. 2 shows how the two IC changes were implemented in the circuit. At the point in the ID where a stop bit is desired, two diodes are run to the appropriate pin on the 74C154 matrix, with one diode further connected to the dot line and the other attached to the blank line. The inputs of one gate of the 74CO2 (Z8B) are connected to the dot and blank lines. This gate actually functions as a negative logic AND gate. When this aforementioned stop pin pulls both lines low together, the output of Z8B goes high.

This output is sent to two places, the "zero set" pins of Z3, which heretofore were grounded, and an inverter made from Z8A. Bringing the zero set pins on Z3 high sets all of its BCD outputs low. Grounding them allows the IC to operate normally.

The output of inverter Z8A feeds the "set" input on one half of the 74C76, Z11. A momentary low on this pin drives the  $\overline{Q}$  output (also known as the ID hold line) low, halting the ID process in its tracks.

Z7A, half of the NE556, replaced IC1A and IC1B in the old circuit because the 556 is a much more reliable circuit, in my experience. The other half of the 556 is used in the astable mode as the ID tone generator.

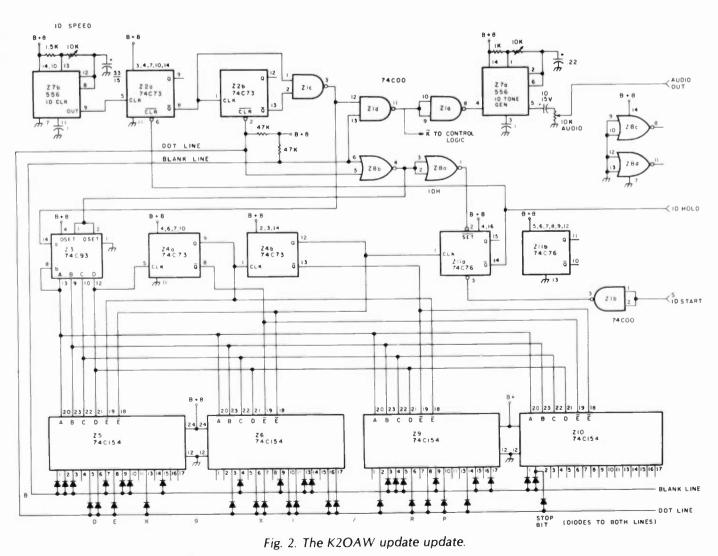IC1A and IC1B are not wasted, however. IC1B, now Z1B, is used to replace Q1, a 2N706 from the original ID circuit. It is connected as an inverter between the start line and the clear input of the 74C76. IC1A, now Z1A, is also used as an inverter, the input



## ERMINA 21

#### APPLE REVIEW WINDOW

D IFOX TEST 1 INY TEST 3 ( ) I I (LALF ) ITIME ) I LOUV - A DIDS PREFINERMIASCI7 110 OLV - A DIDS 1237 46 1715 IS THE REVIEW WINDOW IT LETS YOU LCOR BACK AT HISTORICAL TEXT WHICH HAS SCROLLED OFF THE SCREEN THE REVIEW W NCOW IS SEVEN LINES LONG CR LI

THIS IS THE SHORT DIALOGUE WINDOW IT IS JSED FOF TEXT THAT IS CURRENTLY BEING TRANSMITTED. IT IS NINE LINES LONG Arv

TERMINALL is a hardware and software system that converts your personal com-puter into a state of the art communications terminal. Terminall features simple connections to your computer and radio plus sophisticated and reliable software.

#### Simplicity

TERMINALL was designed from the outset to be easy to connect to your radio and easy to use. Plug into your receiver headphone jack and copy Morse Code or radioteletype (RTTY). Plug into your CW key jack and send Morse Code. Attach a microphone connector and send Baudot of ASCII RTTY using audio tones (AFSK). That's all there is to hooking it up

The software is loaded into your computer from disk or cassette. Enter your callsign and the time and you will start receiving immediately. No settings or adjustments are necessary to receive Morse Code, t's fully automatic -and it works! You may type your message while receiving or transmitter. transmitting.

You will be on the air, receiving and transmitting in any mode, in minutes. As we said, TERMINALL is simple.

#### More for your money.

TERMINALL has the RTTY terminal unit - demod and AFSK - built in. This results in a lower total cost.

Fantastic Morse reception. Six stage active filter demodulator copies the weak ones. Auto acaptive Morse algorithm copies the sloppy ones. Received code speed displayed on status line

Outstanding documentation. Professionally written, 90 page user manual contains step-by-step instructions.

Built in, separate, multi-stage, ac-tive filter RTTY and CW demodulators. No phase lock loops. RTTY demodulator has 170 and either 425 or 850 Hz shift-

eyboard selectable - and uses either the canel meter or scope outputs for easy tunng. Copy the weak ones. Copy the noisy ores. Copy the fading ones.

Built in crystal controlled AFSK. Rock stable for even the most demanding ✓HF or HF applications. A must on many ✓HF RTTY repeaters.

Built in 110 or 220 volt AC power sup-21-

Built in parallel printer driver software. Simply attach a parallel ASCII anner (e.g. the EPSON MX-80) to your or nter port to obtain hardcopy in all mades

Multi level displays - allows examin-ng and editing of historical text.

Vord wrapping, word mode editing, diddle, ignore carriage returns, use proirammable end of line sequence, ad-istable carriage width, multiple userselined WRU, transmit delay (fixed, none

#### TRS-80 NORMAL DISPLAY

	Four line edit winds	ne to create text	
REVINDEN	MORSERWAY 158WAY	1021 m + 170 + 071 V-MICL 1021	8 26
-			_
e¢v			
		$\sim$	
RCV			
•••1			
		Window	
		Scrolls	
West ream	Lincoland text!		

or auto adaptive), break mode and morel

The all-in-one TERMINALL design makes it great for use or HF or VHF, Ham, Commercial, SWL or MARSI SWL's: TERMINALL may be jumpered for either 425 or 850 Hz reception to copy news and weather services.



15 Day Money Back Trial Period on Factory Direct Orders System Requirements

TERMINALL T1 Communications terminal for the TRS-80 Model I. Requires a Model 1 TFS-80, 16K RAM and are II BASIC. Includes software on cassette and disk, assembled and tested hardware and an extensive instruc-to in manual. 1499.

TERMINALL T3 Communications terminal for the TRS-80 Model III. Requires a Model III TRS-80, 16K RAM and Mcdel III BASIC, Includes software on cassette and disk, assembled and tested hardware and an extensive instruc-tog manual, 1499.

TERMINALL T2 Communications terminal for the APPLE II. Requires an APPLE II or APPLE 1 PLus with 48K RAM and disk. Software is provided on disk in DOS 3.2 format, Use MUFFIN utility to convert to DOS 3.3 format. Includes approximate on disk, assembled and tested hardware and an extensive instruction manual. \$458.

Add \$4.00 shipping U.P.S. reg. delivery - CA residents add 6% sales tax TO ORDER (209) 634-8888 or 667-2888 We are experiencing telephone difficulties. Please keep trying. FREE! MACROTRONICS, inc. (R) **TO TERMINALL** 1125 N. Golden State Blvd TI & T3 OWNERS Turlock, California 95380 UPDATE TO DISK RS-80 is a Registered Trademark of Tandy Corp. Apple is a Registered Trademark of Apple Computer Inc. Atari is a Registered Trademark of Atari Computer Inc. \* yr. parts & labor limited warranty. VERSION 2.0 Adda save to Disk & more. Reg. \$20.00. Send original distrib⊥ion disk. We pay return postaç∉. Offer expires 12-31-82 VISA The communications terminal that does it all

### HAL'S CHRISTMAS SPECIALS

HAL 2304 MHz DOWN CONVERTERS (FREQ. RANGE 2000/2500 MHz)
2304 MODEL #1 KIT BASIC UNIT W/PREAMP LESS HOUSING & FITTINGS \$19.95
2304 MODEL #2 KIT (with preamp) \$29.95
2304 MODEL #3 KIT (with High Gain preamp)
MODELS 2 & 3 WITH COAX FITTINGS IN & OUT AND WITH WEATHER-PROOFED DIE CAST HOUSINGS
BASIC POWER SUPPLY
POWER SUPPLY KIT FOR ABOVE WITH CASE
FACTORY WIRED & TESTED \$34.95

ANTENNAS & OTHER ACCESSORIES AVAILABLE. SEND FOR MORE INFO.

T	2100-2500 MHZ
1 AS	COMPLETE SYSTEM AS SHOWN. NOT A KIT. INCLUDES A PC BOARD, POWER SUPPLY, CABLES &
AN I	CONNECTORS-PRE-ASSEMBLED AND TESTED. 24dB
	GAIN OR GREATER. 1 UNIT
	2 UNITS\$139.95 ea.
	3 OR MORE UNITS
A S	'HAM MICROWAVE RECEIVER

#### PRE-SCALER KITS

HAL 300 PRE HAL 300 A/PRE HAL 600 PRE HAL 600 A/PRE

#### (Same as above but with preamp). (Pre-drilled G-10 board and all components) \$29.95 (same as above but with preamp) \$39.95 TOUCH TONE DECODER KIT

(Pre-drilled G-10 board and all components)

\$14.95

\$24.95

HIGHLY STABLE DECODER KIT. COMES WITH 2 SIDED, PLATED THRU AND SOLDER FLOWED G-10 PC BOARD, 7-567's, 2-7402, AND ALL ELECTRONIC COMPONENTS. BOARD MEASURES 3-1/2 x 5-1/2 INCHES, HAS 12 LINES OUT. ONLY \$39.95 NEW-16 LINE DELUXE DECODER \$69.95

DELUXE 12-BUTTON TOUCHTONE ENCODER KIT UTILIZING THE NEW ICM 7206 CHIP ROVIDES BOTH VISUAL AND AUDIO INDICATIONS! COMES WITH ITS OWN TWO TONE ANODIZED ALUMINUM CABINET MEASURES ONLY 21/4 "x31/4" COMPLETE WITH TOUCH-TONE PAD. BOARD, CRYSTAL, CHIP AND ALL NECESSARY COMPONENTS TO FINISH THE KIT PRICED AT \$29.95 \$39.95 NEW-16 LINE DELUXE ENCODER

HAL ECD-16 LINE DELUXE ENCODER INCLUDES PC BOARD, ALL PARTS & CASE \$30.05

HAL ECD-12 LINE DELUXE ENCODER COMPLETE WITH PC BOARD, ALL PARTS & CASE \$29.95

ACCUKEYER (KIT) THIS ACCUKEYER IS A REVISED VERSION OF THE VERY POPULAR WB4VVF ACCUKEYER ORIGINALLY DESCRIBED BY JAMES GARRETT, IN OST MAGAZINE AND THE 1975 RADIO AMATEUR'S HANDBOOK \$16.95 \$16.95

ACCUKEYER-MEMORY OPTION KIT PROVIDES A SIMPLE, LOW COST METHOD OF ADDING MEMORY CAPABILITY TO THE WB4VVE ACCUKEYER, WHILE DESIGNED FOR DIRECT ATTACHMENT TO THE ABOVE ACCUKEYER. IT CAN ALSO BE ATTACHED TO ANY STANDARD ACCUKEYER BOARD WITH LITTLE DIFFICULTY \$16.95 BUY BOTH THE MEMORY AND THE KEYER AND SAVE

COMBINED PRICE ONLY \$32.00

#### PRE-AMPLIFIER

HAL-PA-19 WIDE BAND PRE-AMPLIFIER, 2-200 MHz BANDWIDTH (- 3dB POINTS). 19 dB GAIN

FULLY ASSEMBLED AND TESTED \$8.95

HAL-PA-1.4 WIDE BAND PRE-AMPLIFIER, 10 MHz TO 1.4 GHz. 12dB GAIN FULLY ASSEMBLED \$12.95



CLOCK KIT—HAL 79 FOUR DIGIT SPECIAL-\$7.95. OP-ERATES ON 12-VOLT AC (NOT SUPPLIED) PROVISIONS FOR DC AND ALARM OPERATION

#### 6-DIGIT CLOCK • 12/24 HOUR

COMPLETE KIT CONSISTING OF 2 PC G-10 PRE-DRILLED PC BOARDS, 1 CLOCK CHIP, 6 FND COMM. CATH. READOUTS, 13 TRANS., 3 CAPS, 9 RESISTORS, 5 DIODES, 3 PUSHBUTTON SWITCHES AND INSTRUCTIONS. DON'T BE FOOLED BY PARTIAL KITS WHERE YOU HAVE TO BUY EVERYTHING EXTRA. WILL RUN OFF ANY 12-VOLT AC SUPPLY. PRICED AT \$12.95

CLOCK CASE AVAILABLE AND WILL FIT ANY ONE OF THE ABOVE CLOCKS. REGULAR PRICE.... \$6.50 BUT ONY \$4.50 WHEN BOUGHT WITH CLOCK

SIX-DIGIT ALARM CLOCK KIT FOR HOME, CAMPER, RV, OR FIELD-DAY USE. OPERATES ON 12-VOLT AC OR DC, AND HAS ITS OWN 60-HZ TIME BASE ON THE BOARD. COMPLETE WITH ALL ELECTRONIC COMPONENTS AND TWO PIECE, PRE-DRILLED PC BOARDS. BOARD SIZE 4" × 3". COMPLETE WITH SPEAKER AND SWITCHES. IF OPERATED ON DC, THERE IS NOTHING MORE TO BUY

PRICED AT \$16.95 TWELVE-VOLT AC LINE CORD FOR THOSE WHO WISH TO OPERATE THE CLOCK FROM 110-VOLT AC WHEN PURCHASED WITH CLOCK KIT \$2.95

SHIPPING INFORMATION: ORDERS OVER \$25 WILL BE SHIPPED POST-PAID EXCEPT ON ITEMS WHERE ADDITIONAL CHARGES ARE REQUESTED. ON ORDERS LESS THAN \$25, PLEASE INCLUDE ADDITIONAL \$2.00 FOR HANDLING AND MAILING CHARGES. SEND 20¢ STAMP FOR FREE FLYER: DISTRIBUTOR FOR



connected to the  $\overline{K}$  (keying) line, and the output connected to the reset pin of Z7B, keving the tone for the ID. The  $\overline{K}$  line is still used for logic purposes.

The remaining two gates of Z8 are not used in this design and their inputs are grounded. Don't forget to tie all inputs of the other half of the 74C76 high. Leave the outputs floating.

Although this circuit adds 2 ICs to the design, it subtracts one transistor, and if your ID is short enough, you may be able to leave out Z10 as well, thus saving that expense. And you get a tone generator, a more reliable clock, and other improvements in the bargain.

About the 74C series: I switched all of my TTL to CMOS/TTL (by National Semiconductor) some time back. The savings in current is worth it, and the voltage requirement is not finicky like TTL. I use 8 volts on all my CMOS and timers.

One caveat: The 74C ICs used here are pin-for-pin replacements for their TTL counterparts except for the 74C93. If you're planning to retrofit an existing circuit and convert your 7493 to CMOS, you will have to rewire that part of the circuit.

With these modifications, I feel that the K2OAW IDer is the ultimate ID circuit. If you have one in use now and update to the circuit described here, I think you'll agree that the best has been made better.

#### References

1. Stark, "A Complete Repeater Control Circuit and ID," 73, February and March, 1973. 2. Stark, "Update on the K2OAW ID Circuit," 73, June, 1979.



**ORBIT** is the Official Journal for the Radio Amateur Satellite Corporation (AMSAT), P.O. Box 27, Washington, DC 20047. Please write for application.

For a **FREE SAMPLE COPY** please send \$1 to cover First Class Postage and handling to: Orbit, 221 Long Swamp Road, Wolcott, CT 06716.



Paul Swearingen W9PJF RR 1, Box 485 Benton IL 62812

## The Bunesti Caper

The two British agents needed a power amp – fast. Could the American ham build one?

**D** ecember 7, 1941, was a day of glory and achievement for the Japanese Empire because of the unbelievably effective attack upon military installations in Hawaii. In England, the long hoped-for involve-

ment of America in the war now seemed assured. The "Day of Infamy," however, also brought a special sort of gloom and silence to one small segment of the American population—the amateur radio operators.

In the midwest that night. most of the ham bands were full of stations relaying the FCC announcement that all radio amateur activity was to cease immediately. It seemed that almost every ham in the country was trying to make as many contacts as possible that last night. I kept my 20-Watt AM rig (push-pull 45s modulated by 47s) going on 160 meters until well past midnight, but finally closed down when I got too sleepy to continue.

The next morning, I turned on my Howard 435A receiver and heard a couple of guys yakking away just as though the Pearl Harbor attack had never occurred. Naturally, I cranked up the rig and told them of the FCC notice. They claimed that my call was the first they had heard about it and that they thought their receivers



Photo A. The crew of Destiny Deb prior to its final combat mission to Ploesti, Rumania. (The little guy on the left in the front row is W9PJF.)

had finally paid off, since I had finally paid off, since I hours of close-order drill. had been of course end hours of close-order drill. had been of course end hours of close-order drill. The Air Corps ator/ment believe but that 1941 Delieve mem roleven B December 1941 Norld War 12m AS 2 ishigh-schat illusiack w our Nion that skimvere ht be PU out e, of , as a time ∠ years away Jure when they eful in a way I could er have imagined.

After graduation from high school, I found that the Army Air Corps was glad to have my services. but they insisted that I go to Miami Beach for basic training. This was to introduce me to the finer points of the military organization, to teach me discipline and respect for authority, to enable me to distinguish between my left foot and my right foot, and to educate me in a host of related subjects such as KP. policing the area, saluting, scrubbing the barracks, why all relationships with females are dangerous, etc.

During my third day at basic, an announcement was made that all personnel who knew Morse code were to report to the administrative office at 1300 hours. I reported as ordered and was given a short code test that was sent at about 10 wpm. 1 don't think that 1 missed a letter, and the next day I was on a troop train bound for the radio school at Sioux Falls, South Dakota. In my hands were records showing that I had completed basic training (?) and a promotion order making me a PFC! Those long hours practicing code in or-

radio repair. It included an almost frightening amount of material in a very short time, but I was having a ball. The films. lectures. and demonstrations expanded and solidified my knowledge of the theories I had struggled with as a ham. The code classes were pretty much of a bore and I did not advance my speed very rapidly, but I did manage to pass 35 wpm. We were not allowed to use typewriters, however, so I felt that printing at 35 wpm wasn't too bad.

The practical part of the course was a snap, and I became reasonably proficient at the operation and maintenance of such items as the BC-221 frequency meter, BC-375 transmitter, BC-342 and BC-348 receivers, ARC-5-series HF trans-

mitters and receivers, BC-610 transmitter. SCR-522 VHF transceiver, and miscellaneous aircraft electronic gear such as beacon receivers, the radio compass, interphone systems, etc. I was happy to be expanding my knowledge of electronics and was actually a bit sorry when I completed the course.

I declined an invitation to stay at Sioux Falls as an instructor and requested an assignment as a flight radio operator. Within a couple of days I was on another train, now enroute to Kingman, Arizona, this time to qualify as an aerial gunner. 1 spent some time on the train sewing on my new corporal stripes.


Gunnery school did not have the same fascination for me that I had felt at radio school. While all of the radio operators at gunnery school had to participate in weekly code practice sessions in order to maintain proficiency, 1 learned a lot more than 1 thought possible (or necessary) about the 50- and 30-caliber air-cooled machine guns, the 20 mm cannon, hydraulically- and electrically-operated gun turrets, and how to lead or lag moving targets in flight. We spent a few hours in the air shooting at airborne targets, but I enjoyed the skeet shooting part of the course most of all. We learned the basics of leading or lagging moving targets by shooting at clay pigeons from the back of a moving truck! On days off, we were encouraged to shoot regular skeet-the guns and ammo courtesy of Uncle Sam. After the moving truck training, the normal skeet seemed easy and I was soon 25 for 25 most of the time.

I was not sorry to finish the gunnery course although it had gualified me for the first "flight pay" of my life. I left Kingman as a brand new "Buck" Sergeant, and headed for a combat crew assignment at Tucson, Arizona.

It would take a whole



Photo B. Back in Italy just before returning to the USA, W9PJF points to the souvenir Rumanian Air Force pilot wings worn by "Charlie" Kourvelas, the tail gunner.

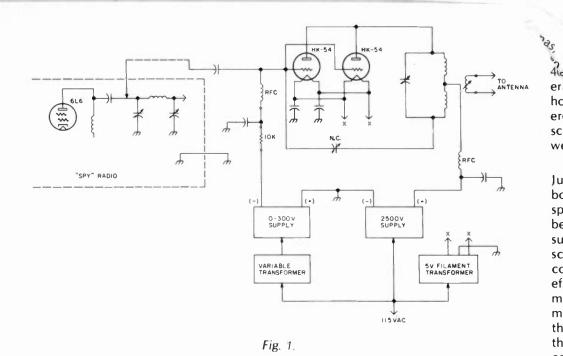

book to express my memories and feelings about our ten-man crew formed at Tucson. That crew became my family away from home, and a closeness developed between us that I have not experienced with any other group. Ten semitrained civilians (four second lieutenants and six buck sergeants) became a reasonably competent crew for a B-24 Liberator, a heavy bomber. We soon were enroute overseas via Natal. Brazil, Dakar, West Africa, Marrakesh, and eventually to an austere base in southern Italy where our 450th Bomb Group joined the newly formed 15th Air Force

I will always believe that aerial combat was at least as frightening as combat on the ground. Most of the time, our activities were conducted far inside enemy territory with the obvious risk of capture or death a long way from home base. We bombed a number of tough targets. We got shot at and were hit by fire from antiaircraft guns and fighter aircraft. We saw friends disappear in the cloud of an exploding aircraft, and we held back unmanly tears as corpsmen removed bodies from riddled airplanes. Our

crew completed 34 missions with many close calls but with no physical wounds. Our flight engineer and I had been promoted to tech sergeant, and the other enlisted men now were staff sergeants. We were flying our third B-24, however: a nearly new one called *Destiny Deb*. Our first two aircraft had been totaled in crashes.

Our 35th mission was to bomb a target that was probably as well guarded as any in Europe. It was the oilfield/refinery complex at Ploesti, Rumania, which was a major source of petroleum products for the Nazi war effort. It was to be our second trip to Ploesti, and memories of the fighters and the intense antiaircraft fire were still fresh in our minds.

That mission turned out to be our last, as Destiny Deb was rocked by an enormous explosion just after we dropped our bomb load and while we were making a right descending turn to take up the return compass heading for Italy. An 88 mm shell had exploded between number two engine and the main fuselage, tearing a large hole in the fuselage and rupturing some fuel lines. Only God knows why we were not immediately surrounded by flames. The number two engine quit immediately, and number three on the other side began to smoke. We fell well behind the squadron and obviously would soon be alone, an easy prey for any Luftwaffe fighters that saw our plight.

The Fates were again kind to us that day, however, and while the number one engine soon failed and power had to be reduced on number three, the old gal flew long enough for us to get well away from the target area. We realized that we would not see Italy very soon as reluctantly we parachuted out over open country near the small town of Bunesti, and soon we were uninvited and unwanted guests of the Rumanian government.

The life and times of a POW in that era cannot be described very well in a few sentences, but a great deal of my time was spent in planning what I might build as my postwar ham station. I was still constrained by my depression views, however, and my most grandiose design turned out to be a T-55 modulated by a pair of TZ-40s. For anten-

Adand Jodered erad Jodered hossep and berha Blk ered the for berha Blk schemer, 80 aps a weird pt adio and The Adarest

The Arac Arac Arac Arac June of 1970 June of 1970 boost to oui spirit of cauti began to spre summer we treas scrap of inform could get about th efforts in France. I manians, however, more concerned at their own future in view the failures of the Na. campaign in Russia.

The news of the war on the Eastern front reached us occasionally and, as the Russians advanced, our food improved measurably. The black bread was replaced by brown and the amount of meat in our thin stews seemed to be increased. The lieutenant in charge of our guards sometimes gave us copies of the local newspapers, and the rapid approach of the Russian troops to the Bucharest area was always a headline item. An aura of uncertainty and suspense appeared to envelope our captors and the element of fear could almost be felt. We heard rumors that British paratroopers had been captured, but it seemed hardly likely that any significant British airborne operation could be supported at this great distance from Italy.

One morning, an American major, accompanied by a Rumanian colonel and two men dressed in civilian clothes, entered our enlisted compound and asked if anyone had had any experience in building radio equipment. I explained my background in amateur radio and was told that two British agents had indeed parachuted into the area and that they needed a



power amplifier for use with their small suitcasesized radio station. Their transmitter provided only about 20 Watts of power, and they had been unable to contact their station in Egypt.

I must admit that I was a little confused by a situation wherein an agent of a nation at war with Rumania was to be assisted by an American prisoner of war in establishing radio contact with an Allied radio station in Egypt. The Rumanian colonel told me that the rapidly approaching Russian forces had created serious political problems and that the British communications arrangements had been approved by "high government officials."

I said that I could build a suitable amplifier if I had the necessary parts, and one of the civilians replied that parts were available. After trading my flying suit for a pair of pants and a shirt, in order to appear less military, I gathered up my small collection of personal belongings and left the prison camp by car in the company of the civilians and two other radio operators, Charlie P. Brewer from Beaumont, Texas, and Ray Jones, RAF, from Sutton, Surrey, England.


We were taken to a large building which must have been part of a university physics department. I was escorted to a room that was full of electronic equipment and told to select whatever I needed. I found many American-made parts and some power supplies that appeared to be operational. I selected some triode transmitting tubes (they were either the HK-54 Gammatrons by Heintz and Kaufman or the 35TGs by Eimac-my memories have been somewhat dimmed by the passage of some 37 years), a 2500-volt power supply, a 300-volt power supply, tube sockets, variable capacitors, wire, solder, a variable transformer (Variac), and an assortment of rf chokes, resistors, insulators, and fixed capacitors.

There was no heavy solid wire available, and I could find no meters or test equipment. I explained my need for wire or tubing to make coils, and one of the civilians said that he would bring some later. The parts that I selected were placed on a bench, and the civilian said they would be delivered to the transmitter location that afternoon.

We left the building and were driven to the Banca Nationale A Romania (The National Bank of Rumania). In one of the basement rooms we were introduced to the two British agents. One was a British captain and the other a Rumanian national who also was a lieutenant in the British army. They showed me their small transmitter/receiver. and I was happy to see that they had several extra coil sets available which I could use in the amplifier circuit.

When the parts from the school were delivered, I assembled a simple power amplifier on a piece of pine board. Electrically, it was a pair of power triodes in parallel (see Fig. 1). The 2500-volt supply provided the plate voltage, and the 300-volt supply, Variac controlled, provided the bias. I used two of the spare coils from the "spy" radio for the amplifier-plate coil and checked for approximate tuning by coupling the output from the small transmitter to the antenna link on the plate coil. Resonance was easily established by tuning for maximum rf voltage in the tank coil.

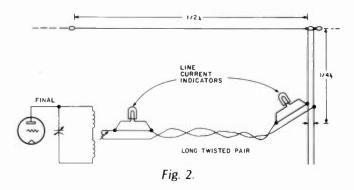Next, I capacity-coupled the grids of the power amplifier to the plate of the 6L6 output tube in the small transmitter. I hooked a flashlight bulb to the output link and carefully read-



justed the amplifier plate, tuning for maximum output. Then the neutralizing capacitor was adjusted for minimum output, and the amplifier was ready for the first trial run. The flashlight bulb was replaced by a 300-Watt bulb, the bias voltage was set for maximum (-300 V) and the 2500-volt supply was turned on.

Surprisingly, nothing blew and no smoke appeared. By decreasing the bias voltage slowly and observing the intensity of the blue glow of the mercury-vapor rectifiers (866s) in the high-voltage supply, I could tell when the amplifier tubes began to draw plate current. I set the bias to a point where a definite plate current was evident and then keyed the small transmitter now being used as a driver for the amplifier. I was rewarded with a brilliantly glowing 300-Watt bulb and a large increase in the mercury-vapor glow.

The amplifier was indeed working and obviously was producing more radio energy than I had ever achieved with any of my ham gear. The only missing element now was an antenna, and the roof of the bank building was an awfully long way from the basement.

It was during this time period that a group of Rumanian leaders formed a provisional government, declared themselves the legal spokesmen, and agreed to cease combat activities against all Allied forces. I was introduced to Dr. Maniu who headed the provisional government and whose temporary abode was also in the basement of the bank. I understood that he had a long history of public service and was well thought of by the Rumanian people.


A man from the telephone company provided us with a large reel of twisted-pair telephone cable, a small reel of bare copper wire, and a great many glass insulators. Charlie, Ray, and I put a half-wave antenna with a quarter-wave matching stub on the roof and used the phone cable as a transmission line to the transmitter (see Fig. 2). The elevator shaft provided the shortest path for routing the cable between the roof and the basement.

During the installation of the antenna, the local German military authorities reacted immediately and harshly to the new government. Several Rumanian civilian facilities were bombed, and, for a few minutes one day while we were on the roof, we watched ME-109s dive-bomb nearby buildings. Luckily, the bank was not selected as a target.

I was concerned about the suitability of the phone cable as a radio-frequency transmission line because of the poor insulation and extreme length of the cable. (No one else there had ever heard about EO-1 cable). As it turned out, the phone cable was very lossy and the

# oman → a world ahead of the competition
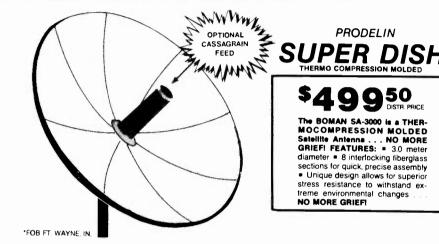
#### TOLL FREE INSIDE CA: (800) 352-2553 OUTSIDE CA: (800) 421-2533



## The NEW" Polar-matic Ultra Feed



Improve your system qualtiy with the EFH-75 Microwave Feed. It offers precision polarity selection using the attractive control shown here.

INSTALLATION FEATURES: 130 ft. of 3 conductor wire included-TERMINALS attach at each end - NO MORE SPLICING - Molded terminal posts on motor cover-Painted parts prevent corrosion - ON-OFF switch on control box - Power-on light on control box - All necessary hardware included.



Toll Free Inside Ca.: (800) 352-2553 Outside (800) 421-2533

WEATHER PROOF TERMINAL STRIP TO INSURE YEAR ABOUND CONNECTION (NO MORE SPLICING)

PRECISION CONTROL WITH

ON OFF SWITCH AND LED INCLUDES "NO SLIP" CONTACT TAPE

SAMPLE VOLUME DISCOUNT COUPON Submit this coupon with your order, and/or payment, and receive one EFH-75 POLAR-MATIC FEED for evaluation purposes at the 24 lot price (Limit one per

STATE ZIP

customer) \$9950

NAME COMPANY ADDRESS CITY

PHONE

RIGHT ANGLE ADAPTER PERMITS VERTICAL OR RIGHT ANGLE LNA MOUNTING

### **SR-800 RECEIVER**

The Boman SR-800B Satellite Receiver uses advanced technology to provide high quality reception at a very affordable price. Features: ■ 24 channel capability ■ 6 audio channels ■ fine tuning control ■ AFC ■ illuminated signal strength meter attractive design fits any decor.



#### MODEL LNA-915 LOW NOISE AMPLIFIER 110° K OR BETTER

ORDER WITH

C - Down Converter

A - 100° Low Noise Converter (LNC)

B - 110° Low Noise Converter (LNC)

All BOMAN MICROWAVE AMPLIFIERS are 100% tested and marked for each guaranteed test parameter before they are released. All measurements are taken with equipment calibrated and maintained in accordance with military standard MIL-C-45662.

QTY.	OPEN ACCT	Pay w Order
10 UNITS	\$443.89	\$39950
30 UNITS	\$421.67	\$37950
60 UNITS	\$388.33	\$34950
600 UNITS	\$366.11	\$329 50
1000 UNITS	\$332,77	\$29950

9



BOMAN INDUSTRES



J 157

950 DIST PRICE

### UNIVERSAL M-600 MULTI-MODE AND CRYPTO-DECODER

## - NEW - DECODES:

TOR-SITOR BIT INVERSION WEATHER FORMAT NON STANDARD SHIFT



The M-600 converts these Codes plus RTTY (Baudot & ASCII) to video and will drive a Serial or Parallel printer for hard copy. Baudot speeds from 60 to 132 WPM and ASCII from 110 to 1200 Baud rates. Morse reception, auto range up to 60 WPM. The M-600 has 3 fixed shifts and 1 tunable shift. Multiple scroll inhibit and un-shift on space are included along with a built-in self-test system. Isolated loop MIL-188 or RS232 and optional parallel ASCII.

#### CONTACT US FOR FURTHER INFORMATION

Phone: (614) 866-4605 MC & VISA Accepted \$799.95 (shipping extra)

UNIVERSAL ELECTRONICS INC. 1280 AIDA DRIVE, REYNOLDSBURG, OHIO 43068 current flow into the antenna matching stub was much less than the current flow from the amplifier into the cable. In the final version of the antenna, the telephone cable was used as a single conductor connected to a water-pipe ground through the amplifier-output link. The cable length to the antenna was adjusted for best loading. This worked very well, and the British agents were soon in contact with the Allied radio station in Egypt. I have no idea of the purpose or content of their conversations as the messages were all encrypted-by use of the Bucharest telephone book.

The opportunity to improvise electronic equipment had been a splendid diversion, however, and during the two or three day period involved, I was directly concerned in an urgent project that was of value to our allies. During this period, I slept in the basement of the bank and food was sent in from a nearby restaurant. This was overwhelming in it's quantity, and I was never able to eat the entire portion. I took particular delight in the dill pickles since I had not tasted any since being shot down.

Within a few days, Russian troops entered Bucharest and the British and American POWs were flown to Italy in B-17 bombers with the protection of many P-51 fighter aircraft. We spent a few days visiting our respective squadrons and then departed from Naples for a fantastic voyage to the USA. By October of 1944, I was home on leave. I planned to ask for an assignment to a B-29 group so that I could get to the Pacific. That would also give me a chance to tinker with that new Collins rig, the ART-13.



#### 812-422-0231 MON-FRI 9AM-6PM • SAT 9AM-3PM



### 808 N. Main • Evansville, IN 47711

	80
AEA MBA-RO Reader	269.00
MBA-RC Rcv/Code Conv. Xmt	
MM-2 MorseMatic Ultimate Keyer	150.00
CK-2 Contest Memory Keyer KT-2 Keyer/Trainer	
BT-1 Trainer	
Isopole 144 Jr/220 Jr	. 30.00
Isopole 144/220 MHz	
Isopole 440 MHz	. 59.00
HD73 (10.7 sq. ft.) Rotator	\$99.00
U-100 Small Rotator	.45.00
83 Handbook	\$12.00
Antenna Book	8.00
License Manual. Large Assortment of Publications	4.00
ASTRON	can
RS7A 5-7 Amp Power Supply	
RS12A 9-12 Amp Power Supply	. 69.00
RS20A 16-20 Amp Power Supply RS20M 16-20 Amp w/meter	109.00
RS35A 25-35 Amp.	135.00
RS35M 25-35 Amp w/meter	149.00
RS50M 37-50 Amp w/meter	225.00
PCS 4000 2M Xcvr	
PCS 300 Handheld	
Speaker/Mic	
Leather Case	
Mobile Operating Cord	.35.00
Dual PL Tone encoder/decoder	. 39.00
B&W Folded Dipole 80-10 Meter	135.00
3756 pos. coax switch	
3765 pos. coax switch	
593 3 pos. coax switch 595 6 pos. coax switch	
SWL Antenna	
BASH	
General, Advanced, Extra Theory Books	
Novice Study Guide	
	. 9.95
BENCHER	
BY-1 Paddle	\$36.00
	\$36.00
BY-1 Paddle BY-2 Chrome Paddle BUTTERNUT HF6V 80-10 Meter vertical	\$36.00 .45.00 119.00
BY-1 Paddle BY-2 Chrome Paddle BUTTERNUT HF6V 80-10 Meter vertical RM Kit Root Mount w/radials	\$36.00 .45.00 119.00 .39.00
BY-1 Paddle. BY-2 Chrome Paddle. BUTTERNUT HF6V 80-10 Meter vertical. STR Stub Tuned Radials. STR Stub Tuned Radials.	\$36.00 .45.00 119.00 .39.00 .23.00
BY-1       Paddle         BY-2       Chrome Paddle         BUTTERNUT       HF6V 80-10         MF6V 80-10       Meter vertical         RM Kit Roof Mount w/radials       S         STR Stub Tuned Radials       TBR 160         TBR 160       Meter Coll Kit         CALLBOOK       Coll	\$36.00 .45.00 119.00 .39.00 .23.00 .49.00
BY-1 Paddle BY-2 Chrome Paddle BUTTERNUT HF6V 80-10 Meter vertical. RM Kit Roof Mount w/radials STR Stub Tuned Radials. TBR 160 Meter Coll Kit. CALLBOOK U.S.	\$36.00 .45.00 119.00 .39.00 .23.00 .49.00 \$19.95
BY-1       Paddle         BY-2       Chrome Paddle         BUTTERNUT       HF6V 80-10         MF6V 80-10       Meter vertical         RM Kit Roof Mount w/radials       S         STR Stub Tuned Radials       TBR 160         TBR 160       Meter Coll Kit         CALLBOOK       Coll	\$36.00 .45.00 119.00 .39.00 .23.00 .49.00 \$19.95 .18.95
BY-1 Paddle BY-2 Chrome Paddle BUTTERNUT HF6V 80-10 Meter vertical. STR Stub Tuned Radials STR Stub Tuned Radials TBR 160 Meter Coll Kit. CALLBOOK U.S. DX. Map Library. CUBIC	\$36.00 .45.00 119.00 .39.00 .23.00 .49.00 \$19.95 .18.95 4.50
BY-1 Paddle BY-2 Chrome Paddle BUTTERNUT HF6V 80-10 Meter vertical. STR Stub Tuned Radials. TBR 160 Meter Coll Kit. CALLBOOK U.S. DX. Map Library. CUBIC Astro 103. \$1,	\$36.00 .45.00 119.00 .39.00 .23.00 .49.00 \$19.95 .18.95 4.50 150.00
BY-1 Paddle BY-2 Chrome Paddle BUTTERNUT HF6V 80-10 Meter vertical. STR Stub Tuned Radials STR Stub Tuned Radials TBR 160 Meter Coll Kit. CALLBOOK U.S. DX Map Library CUBIC Astro 103 CN-102 CW Filter	\$36.00 .45.00 119.00 .39.00 .23.00 .49.00 \$19.95 .18.95 4.50 150.00 .72.00
BY-1 Paddle BY-2 Chrome Paddle BUTTERNUT HF6V 80-10 Meter vertical. STR Stub Tuned Radials TBR 160 Meter Coll Kit. CALLBOOK U.S. DX. Map Library. CUBIC Astro 103. S1, CN-102 CW Filter. 1500ZA Amplifier.	\$36.00 .45.00 119.00 .39.00 .23.00 .49.00 \$19.95 .18.95 4.50 150.00 .72.00 500.00 .89.00
BY-1 Paddle BY-2 Chrome Paddle BUTTERNUT HF6V 80-10 Meter vertical. STR Stub Tuned Radials STR Stub Tuned Radials TBR 160 Meter Coll Kit. CALLBOOK U.S. DX. Map Library CUBIC Astro 103. CN-102 CW Filter. 1500ZA Amplifiler. WM2000A HF PEP Meter. PSU-6A Power Supply.	\$36.00 .45.00 119.00 .39.00 .23.00 .49.00 \$19.95 .18.95 4.50 150.00 .72.00 500.00 .89.00
BY-1 Paddle BY-2 Chrome Paddle BUTTERNUT HF6V 80-10 Meter vertical. STR Stub Tuned Radials TBR 160 Meter Coll Kit. CALLBOOK U.S. DX. Map Library. CUBIC Astro 103. S1, CN-102 CW Filter. 1500ZA Amplifier.	\$36.00 .45.00 119.00 .39.00 .23.00 .49.00 \$19.95 .18.95 4.50 150.00 .72.00 500.00 .89.00 170.00
BY-1 Paddle BY-2 Chrome Paddle BUTTERNUT HF6V 80-10 Meter vertical. STR Stub Tuned Radials STR Stub Tuned Radials TBR 160 Meter Coll Kit. CALLBOOK U.S. DX. Map Library CUBIC Astro 103. CN-102 CW Filter. 1500ZA Amplifiler. WM2000A HF PEP Meter. PSU-6A Power Supply. CUSHCRAFT A3 Tribander 3 EL. A4 Tribander 4 EL.	\$36.00 .45.00 119.00 .39.00 .23.00 .49.00 \$19.95 .18.95 4.50 150.00 .72.00 500.00 .89.00 170.00 179.00 229.00
BY-1       Paddle         BY-2       Chrome Paddle         BUTTERNUT       HF6V 80-10 Meter vertical         FSV 80-10       Meter vertical         STR Stub Tuned Radials       STR Stub Tuned Radials         TBR 160 Meter Coll Kit       CALLBOOK         U.S.       DX         Map       Library         CUBIC       Astro 103         CN-102       CW Filter         1500ZA       Amplifier         WM2000A       HF PEP Meter         PSU-6A       Power Supply         CUSHCRAFT       A Tribander 3 EL         A743/744 40 Meter Add-on       A	\$36.00 .45.00 119.00 .39.00 .23.00 .49.00 \$19.95 .18.95 4.50 150.00 .72.00 .500.00 .89.00 170.00 229.00 .69.00
BY-1 Paddle BY-2 Chrome Paddle BUTTERNUT HF6V 80-10 Meter vertical. SR Kit Roof Mount w/radials STR Stub Tuned Radials. TBR 160 Meter Coll Kit. CALLBOOK U.S. DX. Map Library. CUBIC Astro 103. S1. CN-102 CW Filter. 1500ZA Amplifier. WM2000A HF PEP Meter. PSU-6A Power Supply. CUSHCRAFT A3 Tribander 3 EL. SA4 Tribander 3 EL. ST 43/744 40 Meter Add-on. R3 Motor Tuned Vertical.	\$36.00 .45.00 119.00 .23.00 .49.00 \$19.95 .18.95 .4.50 150.00 .72.00 .500.00 .89.00 170.00 179.00 229.00 .69.00 229.00
BY-1       Paddle         BY-2       Chrome Paddle         BUTTERNUT       HF6V 80-10 Meter vertical         HF6V 80-10 Meter vertical       S         RM KIt Roof Mount w/radials       S         STR Stub Tuned Radials       T         TBR 160 Meter Coll Kit       CALLBOOK         U.S.       DX         Map Library       CUBIC         Astro 103       \$1         CN-102 CW Filter       1500ZA Amplifier         VM2000A HF PEP Meter       PSU-6A Power Supply         CUSHCRAFT       A3 Tribander 3 EL       \$         A4 Tribander 4 EL       \$         A4743/744 40 Meter Add-on       R3 Motor Tuned Vertical         AV580-10 Meter Vertical       214B Boomer 14 EL 2M	\$36.00 .45.00 .39.00 .23.00 .23.00 .49.00 \$19.95 .18.95 .18.95 .18.95 .150.00 .72.00 500.00 .89.00 170.00 229.00 .29.00 .95.00 .69.00
BY-1       Paddle         BY-2       Chrome Paddle         BUTTERNUT       HF6V 80-10 Meter vertical.       S         RM Klt Roof Mount w/radials       S         STR Stub Tuned Radials.       TBR 160 Meter Coll Kit.         CALLBOOK       U.S.         DX       Map Library.         CUBIC       Astro 103.         S1022       Astro 103.         S1022       Astro 103.         CN-102 CW Filter       S         1500ZA Amplifiler.       WM2000A HF PEP Meter         PSU-6A Power Supply.       CUSHCRAFT         A3 Tribander 3 EL       S         A4 Tribander 4 EL       A743/744 40 Meter Add-on         A3 Motor Tuned Vertical.       AV580-10 Meter Vertical.         214B Boomer 14 EL 2M       214FB Boomer 14 EL 2M	\$36.00 .45.00 .39.00 .23.00 .49.00 \$19.95 .18.95 .18.95 .4.50 150.00 .72.00 500.00 .89.00 170.00 179.00 229.00 .69.00 .95.00 .69.00 .69.00
BY-1       Paddle         BY-2       Chrome Paddle         BUTTERNUT       HF6V 80-10 Meter vertical         HF6V 80-10 Meter vertical       S         RM Kit Roof Mount w/radials       S         STR Stub Tuned Radials       T         TBR 160 Meter Coll Kit       CALLBOOK         U.S.       DX         Map       Library         CUBIC       Astro         Astro       103         S1       CN-102 CW Filter         1500ZA       Amplifier         WM2000A       HF PEP Meter         PSU-6A Power Supply       CUSHCRAFT         A3 Tribander 3 EL       S         A4 Tribander 4 EL       A743/744 40 Meter Add-on         R3 Motor Tuned Vertical       AV580-10 Meter Vertical         214FB Boomer 14 EL 2M       214FB Boomer 14 EL FM         228FE Power Pack 28 EL 2M FM       228FE Power Pack 28 EL 2M FM	\$36.00 .45.00 119.00 .23.00 .23.00 .49.00 \$19.95 .18.95 .18.95 4.50 150.00 .72.00 500.00 .89.00 179.00 229.00 .69.00 .69.00 .69.00 .69.00 .69.00
BY-1 Paddle BY-2 Chrome Paddle BUTTERNUT HF6V 80-10 Meter vertical. SR Kit Roof Mount w/radials STR Stub Tuned Radials. TBR 160 Meter Coll Kit. CALLBOOK U.S. DX. Map Library. CUBIC Astro 103. S1. CN-102 CW Filter. 1500ZA Amplifier. WM2000A HF PEP Meter. PSU-6A Power Supply. CUSHCRAFT A3 Tribander 3 EL. SA4 Tribander 3 EL. ST43/744 40 Meter Add-on. R3 Motor Tuned Vertical. 214B Boomer 14 EL 2M 214FB Boomer 14 EL 2M 224FB Power Pack 28 EL 2M FM 32-19 Super Boomer 19 EL 2M. 2200 Bhomer 17 EL 220 MHz.	\$36.00 .45.00 119.00 .23.00 .23.00 .49.00 \$19.95 .18.95 .18.95 .4.50 150.00 .72.00 500.00 .89.00 170.00 229.00 .69.00 .29.00 .69.00 .69.00 .83.00 .75.00
BY-1       Paddle         BY-2       Chrome Paddle         BUTTERNUT       HF6V 80-10 Meter vertical         HF6V 80-10 Meter vertical       S         RM Kit Roof Mount w/radials       STR Stub Tuned Radials         STR Stub Tuned Radials       S         DS       DX         Map       Library         CUBIC       Astro         Astro       103         S1       CN-102 CW Filter         1500ZA       Amplifier         WM2000A HF PEP Meter       PSU-6A Power Supply         CUSHCRAFT       A3 Tribander 3 EL       S         A4 Tribander 4 EL       A743/744 40 Meter Add-on       R3 Motor Tuned Vertical         AV580-10 Meter Vertical       214FB Boomer 14 EL PM       228FB Power Pack 28 EL 2M FM         228FB Power Pack 28 EL 2M FM       32:19 Super Boomer 19 EL 2M       228B Boomer 17EL 220 MHz         ABX-28 Ringo Ranger II 2M       ABX-28 Ringo Ranger II 2M       Mag	\$36.00 .45.00 119.00 .23.00 .23.00 .23.00 \$19.95 .18.95 .18.95 .18.95 .18.95 .18.95 .18.95 .150.00 .50.00 .69.00 .69.00 .69.00 .69.00 .69.00 .69.00 .69.00 .69.00 .69.00 .88.00 .75.00 .36.00
BY-1       Paddle         BY-2       Chrome Paddle         BUTTERNUT       HF6V 80-10 Meter vertical.         HF6V 80-10 Meter vertical.       S         RM Kit Roof Mount w/radials       STR Stub Tuned Radials.         TBR 160 Meter Coll Kit.       CALLBOOK         U.S.       DX         Map Library.       CUBIC         Astro 103.       \$1,         CN-102 CW Filter.       1500ZA Amplifler.         VM2000A HF PEP Meter.       PSU-6A Power Supply.         CUSHCRAFT       A3 Tribander 3 EL.       \$ \$ \$ \$ \$ \$ \$ \$ \$ \$ \$ \$ \$ \$ \$ \$ \$ \$ \$	\$36.00 .45.00 119.00 .23.00 .23.00 .23.00 .49.00 \$19.95 .18.95 .18.95 .18.95 .150.00 .72.00 500.00 .89.00 170.00 229.00 .69.00 .69.00 .69.00 .69.00 .69.00 .69.00 .69.00 .69.00 .75.00 .38.00 .38.00
BY-1       Paddle         BY-2       Chrome Paddle         BUTTERNUT       HF6V 80-10 Meter vertical         HF6V 80-10 Meter vertical       S         RM Kit Roof Mount w/radials       STR Stub Tuned Radials         STR Stub Tuned Radials       S         DS       DX         Map Library       CUBIC         Astro 103       \$1         CN-102 CW Filter       1500ZA Amplifter         VM2000A HF PEP Meter       PSU-6A Power Supply         CUSHCRAFT       A3 Tribander 3 EL       \$ A         A4 Tribander 4 EL       A743/744 40 Meter Add-on         R3 Motor Tuned Vertical       24V580-10 Meter Vertical       214B Boomer 14 EL FM         228FB Power Pack 28 EL 2M FM       32-19 Super Boomer 19 EL 2M       228B Borner 17EL 220 MHz         ARX-28 Ringo Ranger II 2M       ARX450B Ringo Ranger II 450 MHz       A144-107 Vert. & Horiz. 10EL 2M         A144-105 Satelijte 10EL 2M       204 Mitor 10EL 2M       204 Mitor 10EL 2M	\$36.00 .45.00 119.00 .23.00 .23.00 .23.00 \$19.95 .18.95 .18.95 .150.00 .72.00 500.00 .89.00 170.00 170.00 179.00 .69.00 .69.00 .69.00 .69.00 .69.00 .89.00 .69.00 .89.00 .69.00 .89.00 .69.00 .69.00 .80.00 .80.00 .80.00 .38.00 .38.00 .63.00 .45.00
BY-1       Paddle         BY-2       Chrome Paddle         BUTTERNUT       HF6V 80-10 Meter vertical         HF6V 80-10 Meter vertical       S         RM Kit Roof Mount w/radials       S         STR Stub Tuned Radials       T         TBR 160 Meter Coll Kit       CALLBOOK         U.S.       DX         Map Library       CUBIC         Astro 103       \$1         CN-102 CW Filter       1500ZA Amplifiler         VM2000A HF PEP Meter       PSU-6A Power Supply         CUSHCRAFT       A3 Tribander 3 EL       \$         A4 Tribander 4 EL       A743/744 40 Meter Add-on         R3 Motor Tuned Vertical       2245B Power 14 EL FM         228FB Power 14 EL ZM       2248B Power 14 EL FM         228FB Power 14 EL ZM       2248B Power 14 EL FM         228FB Power 14 EL ZM       2248B Power 14 EL ZM         219 Super Boomer 19 EL 2M       2285B Ringo Ranger II 2M         ARX-28 Ringo Ranger II 2M       ARX-48 Ringo Ranger II 2M         ARX450B Ringo Ranger II 2M       ARX450B Ringo Ranger II 2M         A144-10T Satellite 10EL 2M       A144-10T Satellite 20EL 2M	\$36.00 .45.00 119.00 .23.00 .23.00 .23.00 .49.00 \$19.95 .18.95 .18.95 .18.95 .18.95 .18.95 .18.95 .19.00 .50.00 .89.00 .69.00 .69.00 .69.00 .69.00 .69.00 .69.00 .75.00 .38.00 .38.00 .38.00 .38.00 .63.00 .45.00 .69.00
BY-1       Paddle         BY-2       Chrome Paddle         BUTTERNUT       HF6V 80-10 Meter vertical.         HF6V 80-10 Meter vertical.       S         RM Kit Root Mount w/radials       STR Stub Tuned Radials.         TBR 160 Meter Coll Kit.       CALLBOOK         U.S.       DX         Map Library.       CUBIC         Astro 103.       \$1,         CN-102 CW Filter       1500ZA Amplifier.         VM2000A HF PEP Meter       PSU-6A Power Supply.         CUSHCRAFT       A3 Tribander 3 EL.         A3 Tribander 3 EL.       \$1,         A743/744 40 Meter Add-on.       R3 Motor Tuned Vertical.         214B Boomer 14 EL ZM.       214B Boomer 14 EL ZM.         220B Boomer 17EL 220 MHz.       ARX450B Ringo Ranger II 2M.         ARX450B Ringo Ranger II 2M.       ARX450B Ringo Ranger II 450 MHz.         A144-20T Vert. & Horz. 10EL 2M.       A144-20T Satellite 10EL 2M.         A144-20T Satellite 20EL 2M.       A432-20T Satellite 20EL 2M.	\$36.00 .45.00 119.00 .23.00 .23.00 .23.00 .49.00 \$19.95 .18.95 .18.95 .18.95 .18.95 .18.95 .18.95 .19.00 .50.00 .89.00 .69.00 .69.00 .69.00 .69.00 .69.00 .69.00 .75.00 .38.00 .38.00 .38.00 .38.00 .63.00 .45.00 .69.00
BY-1       Paddle         BY-2       Chrome Paddle         BUTTERNUT       HF6V 80-10 Meter vertical.         HF6V 80-10 Meter vertical.       S         RM klt Roof Mount w/radials.       STR Stub Tuned Radials.         TBR 160 Meter Coll Kit.       CALLBOOK         U.S.       DX         Map Library.       CUBIC         CUBIC       Stro 103.         CN-102 CW Filter.       1500ZA Amplifiler.         VM2000A HF PEP Meter.       PSU-6A Power Supply.         CUSHCRAFT       A3 Tribander 3 EL.       S         A4 Tribander 4 EL.       A743/744 40 Meter Add-on.       R3 Motor Tuned Vertical.         214FB Boomer 14 EL ZM.       214FB Boomer 19 EL 2M.       228FB Power Pack 28 EL 2M FM.         32:09 Super Boomer 19 EL 20 MHz.       ARX:450B Ringo Ranger II 450 MHz.       A147-20T Vert. & Horiz. 10EL 2M.         A144-10T Satellite 10EL 2M.       A144-20T Satellite 20EL 432 MHz.       DAIWA.	\$36.00 .45.00 119.00 .23.00 .23.00 .49.00 \$19.95 .18.95 .18.95 .4.50 150.00 .72.00 .500.00 .89.00 170.00 179.00 229.00 .69.00 .229.00 .69.00 .83.00 .69.00 .36.00 .38.00 .63.00 .63.00 .63.00 .63.00 .63.00
BY-1       Paddle         BY-2       Chrome Paddle         BUTTERNUT       HF6V 80-10 Meter vertical.         HF6V 80-10 Meter vertical.       S         RM Kit Roof Mount w/radials       STR Stub Tuned Radials.         TBR 160 Meter Coll Kit.       CALLBOOK         U.S.       DX         Map Library.       CUBIC         Astro 103.       \$1,         CN-102 CW Filter       1500ZA Amplifier.         VM2000A HF PEP Meter       PSU-6A Power Supply.         CUSHCRAFT       A3 Tribander 3 EL.         A3 Tribander 3 EL.       \$2         A4 Tribander 4 EL.       A743/744 40 Meter Add-on.         A743/744 40 Meter Vertical.       214FB Boomer 14 EL ZM.         214FB Boomer 14 EL ZM.       220B Boomer 17EL 220 MHz.         ARX450B Ringo Ranger II 2M.       ARX450B Ringo Ranger II 450 MHz.         A147-20T Vert. & Horiz. 10EL 2M.       A144-10T Satellite 10EL 2M.         A144-20T Satellite 20EL 2M.       A432-20T Satellite 20EL 2M.         A144-20T Satellite 20EL 2M.       A432-20T Satellite 20EL 2M.         A144-20T Satellite 20EL 2M.       AA432-20T Satellite 20EL 2M.         A144-20T Satellite 20EL 2M.       AA32-20T Satellite 20EL 2M.         A144-20T Satellite 20EL 2M.       AA432-20T Satellite 20EL 2M. <t< td=""><td>\$36.00 .45.00 .39.00 .23.00 .23.00 .23.00 .49.00 \$19.95 .18.95 .18.95 .18.95 .150.00 .500.00 .500.00 .500.00 .229.00 .69.00 .229.00 .69.00 .69.00 .69.00 .69.00 .75.00 .38.00 .39.00 .30</td></t<>	\$36.00 .45.00 .39.00 .23.00 .23.00 .23.00 .49.00 \$19.95 .18.95 .18.95 .18.95 .150.00 .500.00 .500.00 .500.00 .229.00 .69.00 .229.00 .69.00 .69.00 .69.00 .69.00 .75.00 .38.00 .39.00 .30
BY-1       Paddle         BY-2       Chrome Paddle         BUTTERNUT       HF6V 80-10 Meter vertical         HF6V 80-10 Meter vertical       S         RM klt Roof Mount w/radials       STR Stub Tuned Radials         TBR 160 Meter Coll Kit       CALBOOK         U.S.       DX         Map Library.       CUBIC         CUBIC       Astro 103       \$1,         CN-102 CW Filter       1500ZA Ampliter         VM2000A HF PEP Meter.       PSU-6A Power Supply.         CUSHCRAFT       A3 Tribander 3 EL       \$         A3 Tribander 3 EL       \$       \$         A4 Tribander 4 EL       \$       \$         A743/744 40 Meter Add-on       R3 Motor Tuned Vertical       \$         A14 Tribander 4 EL       \$       \$         A28B Boomer 14 EL FM       228B Boomer 17EL 220 MHz       \$         214FB Boomer 19 EL 2M       \$       \$         220B Boomer 17EL 220 MHz       \$       \$         A147-20T Vert.       \$       \$         A144-20T Satellite 10EL 2M       \$       \$         A144-20T Satellite 10EL 2M       \$       \$         A144-20T Satellite 20EL 2M       \$       \$         A144-20T Satellite 20EL 2M <td>\$36.00 .45.00 .39.00 .23.00 .23.00 .23.00 .59.00 \$19.95 .18.95 .18.95 .18.95 .18.95 .18.95 .18.95 .19.00 .229.00 .69.00 .69.00 .69.00 .69.00 .69.00 .69.00 .88.00 .38.00 .36.00 .29.00 .29.00 .29.00 .36.00 .36.00 .29.00 .29.00 .29.00 .36.00 .29.00 .29.00 .36.00 .29.00</td>	\$36.00 .45.00 .39.00 .23.00 .23.00 .23.00 .59.00 \$19.95 .18.95 .18.95 .18.95 .18.95 .18.95 .18.95 .19.00 .229.00 .69.00 .69.00 .69.00 .69.00 .69.00 .69.00 .88.00 .38.00 .36.00 .29.00 .29.00 .29.00 .36.00 .36.00 .29.00 .29.00 .29.00 .36.00 .29.00 .29.00 .36.00 .29.00
BY-1       Paddle         BY-2       Chrome Paddle         BUTTERNUT       HF6V 80-10 Meter vertical.         HF6V 80-10 Meter vertical.       S         RM Kit Roof Mount w/radials       STR Stub Tuned Radials.         TBR 160 Meter Coll Kit.       CALLBOOK         U.S.       DX         Map Library.       CUBIC         Astro 103.       \$1,         CN-102 CW Filter       1500ZA Amplifier.         VM2000A HF PEP Meter       PSU-6A Power Supply.         CUSHCRAFT       A3 Tribander 3 EL.         A3 Tribander 3 EL.       \$2         A4 Tribander 4 EL.       A743/744 40 Meter Add-on.         A743/744 40 Meter Vertical.       214FB Boomer 14 EL ZM.         214FB Boomer 14 EL ZM.       220B Boomer 17EL 220 MHz.         ARX450B Ringo Ranger II 2M.       ARX450B Ringo Ranger II 450 MHz.         A147-20T Vert. & Horiz. 10EL 2M.       A144-10T Satellite 10EL 2M.         A144-20T Satellite 20EL 2M.       A432-20T Satellite 20EL 2M.         A144-20T Satellite 20EL 2M.       A432-20T Satellite 20EL 2M.         A144-20T Satellite 20EL 2M.       AA432-20T Satellite 20EL 2M.         A144-20T Satellite 20EL 2M.       AA32-20T Satellite 20EL 2M.         A144-20T Satellite 20EL 2M.       AA432-20T Satellite 20EL 2M. <t< td=""><td>\$36.00 .45.00 .39.00 .23.00 .23.00 .23.00 .49.00 \$19.95 .18.95 .18.95 .18.95 .18.95 .10.00 .72.00 .50.00 .50.00 .69.00 .229.00 .69.00 .69.00 .69.00 .69.00 .69.00 .38.00 .39.00 .30.00 .39.00 .30.00</td></t<>	\$36.00 .45.00 .39.00 .23.00 .23.00 .23.00 .49.00 \$19.95 .18.95 .18.95 .18.95 .18.95 .10.00 .72.00 .50.00 .50.00 .69.00 .229.00 .69.00 .69.00 .69.00 .69.00 .69.00 .38.00 .39.00 .30.00 .39.00 .30.00

	-
CN-550 144-250 MHz SWR/Pwr Mtr.	80.00
CN-620B 1.8-150 MHz SWR/Pwr Mtr.	
CN-630 140-450 MHz SWR/Pwr Mtr CN-720B 1.8-150 MHz SWR/Pwr Mtr	129.00
CS-201 2-position switch	
CS-2012-position switch	
RM-940 Wireless Mic	
DRAKE	
TR7A Xcvr\$	1,439.00
R7A Receiver	
TR5 Xcvr	
L7 2KW Amplifier w/tubes	1,149.00
L75 1.2KW Amplifler w/tube	
MS7 Speaker	
WH7 Watt Meter	
ENCOMM (SANTEC)	.209.00
ST-144/µP	\$285.00
ST-440/µP	
Leather Case	
Battery Pack	24.00
Base Charger	
Charge Adapter	
Sub Tone	
Speaker/Mic	32.00
HAL DS3100 Terminal	1 960 00
MSO3100	
CT2100 Terminal	
KB2100 Keyboard	
BS2100 Scope	289.00
MSG2100 Message Storage ROM	25.00
DS2050 Terminal	. 569.00
MR2000	
CWR685A TeleReader	
ST-6000 Deluxe Demodulator	
ST-5000 Demodulator	
12 "Monitor	
HY-GAIN	. 435.00
TH7 DXS 7EL Tribander	\$375.00
TH5 MK2S 5EL Tribander	
TH3 MK3S 3 EL Tribander	
TH3 JRS 3 EL Tribander	
402BAS 2EL 40 Meter Beam	
205BA 5EL 20 Meter Long John	260.00
204 BAS 4EL 20 Meter Beam	.229.00
203BA 3EL 20 Meter Beam	.229.00
203BA 3EL 20 Meter Beam	.229.00 .119.00 .159.00
203BA 3EL 20 Meter Beam 155BA 5EL 15 Meter Beam 66BS 6EL 6 Meter Beam	.229.00 .119.00 .159.00 .109.00
203BA 3EL 20 Meter Beam. 155BA 5EL 15 Meter Beam. 66BS 6EL 6 Meter Beam. 18HTS 80-10 Meter Vertical.	.229.00 .119.00 .159.00 .109.00 .339.00
203BA 3EL 20 Meter Beam. 155BA 5EL 15 Meter Beam. 66BS 6EL 6 Meter Beam. 18HTS 80-10 Meter Vertical. 18AVT/WBS 80-10 Meter Vertical.	.229.00 .119.00 .159.00 .109.00 .339.00 .95.00
203BA 3EL 20 Meter Beam. 155BA 5EL 15 Meter Beam. 66BS 6EL 6 Meter Beam. 18HTS 80-10 Meter Vertical.	.229.00 .119.00 .159.00 .109.00 .339.00 .95.00 .19.00
203BA 3EL 20 Meter Beam 155BA 5EL 15 Meter Beam 66BS 6EL 6 Meter Beam 18HTS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical BN86 Balun	.229.00 119.00 159.00 .109.00 .339.00 .95.00 .19.00 .36.00
203BA 3EL 20 Meter Beam 155BA 5EL 15 Meter Beam 66BS 6EL 6 Meter Beam 18HTS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical BN86 Balun 214 14EL 2 Meter Beam 208 8EL 2 Meter Beam 205 5EL 2 Meter Beam	.229.00 .119.00 .159.00 .109.00 .339.00 .95.00 .19.00 .36.00 .33.00 .23.00
203B 3EL 20 Meter Beam. 155BA 5EL 15 Meter Beam. 166BS 6EL 6 Meter Beam. 18HTS 80-10 Meter Vertical. 18AVT/WBS 80-10 Meter Vertical. BN86 Balun. 214 14EL 2 Meter Beam. 208 8EL 2 Meter Beam. 205 5EL 2 Meter Beam. CD45 8.5 sq. ft. Rotator.	.229.00 119.00 159.00 339.00 .95.00 .19.00 .36.00 .33.00 .23.00 .119.00
203B 3EL 20 Meter Beam. 155BA 5EL 15 Meter Beam. 166B5 6EL 6 Meter Beam. 18HTS 80-10 Meter Vertical. 18AVT/WBS 80-10 Meter Vertical. BN86 Balun. 214 14EL 2 Meter Beam. 208 8EL 2 Meter Beam. 205 5EL 2 Meter Beam. CD45 8.5 sq. ft. Rotator. Ham IV 15 sq. ft. Rotator.	.229.00 119.00 159.00 339.00 .95.00 .36.00 .33.00 .23.00 119.00 195.00
203BA 3EL 20 Meter Beam. 155BA 5EL 15 Meter Beam. 66BS 6EL 6 Meter Beam. 18HTS 80-10 Meter Vertical. 18AVT/WBS 80-10 Meter Vertical. BN86 Balun. 214 14EL 2 Meter Beam. 208 8EL 2 Meter Beam. 205 5EL 2 Meter Beam. CD45 8.5 sq. ft. Rotator. Ham IV 15 sq. ft. Rotator. T2X 20 sq. ft. Rotator.	.229.00 119.00 159.00 339.00 .95.00 .36.00 .36.00 .33.00 .23.00 119.00 195.00 .249.00
203B 3EL 20 Meter Beam. 155BA 5EL 15 Meter Beam. 165B3 6EL 6 Meter Beam. 18HTS 80-10 Meter Vertical. 18AVT/WBS 80-10 Meter Vertical. BN86 Balun. 214 14EL 2 Meter Beam. 205 5EL 2 Meter Beam. 205 5EL 2 Meter Beam. CD45 8.5 sq. ft. Rotator. Ham IV 15 sq. ft. Rotator. T2X 20 sq. ft. Rotator. HDR300 25 sq. ft. Rotator.	.229.00 119.00 159.00 339.00 95.00 19.00 36.00 33.00 23.00 119.00 195.00 249.00 435.00
203B 3EL 20 Meter Beam. 155BA 5EL 15 Meter Beam. 165B3 6EL 6 Meter Beam. 18HTS 80-10 Meter Vertical. 18AVT/WBS 80-10 Meter Vertical. BN86 Balun. 214 14EL 2 Meter Beam. 205 5EL 2 Meter Beam. 205 5EL 2 Meter Beam. CD45 8.5 sq. ft. Rotator. Ham IV 15 sq. ft. Rotator. T2X 20 sq. ft. Rotator. HDR300 25 sq. ft. Rotator.	.229.00 119.00 159.00 339.00 95.00 19.00 36.00 33.00 23.00 119.00 195.00 249.00 435.00
203B 3EL 20 Meter Beam. 155BA 3EL 15 Meter Beam. 165B3 6EL 6 Meter Beam. 18HTS 80-10 Meter Vertical. 18AVT/WBS 80-10 Meter Vertical. 18AVT 2000 Meter Vertical. 18AVT 2000 Meter Vertical. 18AVT 2000 Meter Beam. 205 8EL 2 Meter Beam. 205 SEL 2 Meter Beam. 205 5EL 2 Meter Beam. 205 5EL 2 Meter Beam. 205 2000 Meter Vertical. HDR300 25 sq. ft. Rotator. 12X 20 sq. ft. Rotator. HDR300 25 sq. ft. Rotator. V2S 2 Meter Vertical. Procomm 200 Dual Headobones/Mic.	.229.00 .119.00 .159.00 .339.00 .339.00 .35.00 .36.00 .36.00 .23.00 .119.00 .119.00 .195.00 .249.00 .435.00 .39.00
203B 3EL 20 Meter Beam. 155BA 5EL 15 Meter Beam. 165B3 6EL 6 Meter Beam. 18HTS 80-10 Meter Vertical. 18AVT/WBS 80-10 Meter Vertical. 18AVT/WBS 80-10 Meter Vertical. 18AVT 2005 8EL 2 Meter Beam. 205 5EL 2 Meter Beam. 205 5EL 2 Meter Beam. CD45 8.5 sq. ft. Rotator. Ham IV 15 sq. ft. Rotator. T2X 20 sq. ft. Rotator. HDR300 25 sq. ft. Rotator. V2S 2 Meter Vertical. Procomm 300 Headphones/Mic.	.229.00 .119.00 .159.00 .109.00 .339.00 .95.00 .36.00 .36.00 .33.00 .23.00 .119.00 .249.00 .435.00 .39.00 .89.00 .89.00
203B 3EL 20 Meter Beam 155BA 5EL 15 Meter Beam 16BS 6EL 6 Meter Beam 18HTS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical BN86 Balun 205 8EL 2 Meter Beam 205 5EL 2 Meter Beam 205 5EL 2 Meter Beam CD45 8.5 sq. ft. Rotator Ham IV 15 sq. ft. Rotator TZX 20 sq. ft. Rotator HDR300 25 sq. ft. Rotator V2S 2 Meter Vertical Procomm 200 Dual Headphones/Mic Procomm 300 Headphone/Mic	.229.00 .119.00 .159.00 .109.00 .339.00 .95.00 .36.00 .36.00 .33.00 .23.00 .119.00 .249.00 .435.00 .39.00 .89.00 .89.00
203B 3EL 20 Meter Beam 155BA 3EL 15 Meter Beam 155BA 5EL 15 Meter Beam 18HTS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical BN86 Balun 214 14EL 2 Meter Beam 208 8EL 2 Meter Beam 205 5EL 2 Meter Beam CD45 8.5 sq. ft. Rotator Ham IV 15 sq. ft. Rotator TZX 20 sq. ft. Rotator HDR300 25 sq. ft. Rotator HDR300 25 sq. ft. Rotator V25 2 Meter Vertical Procomm 200 Dual Headphones/Mic 1210 Headphones Free Shipping on all crank-up towers	.229.00 .119.00 .159.00 .109.00 .339.00 .95.00 .36.00 .36.00 .33.00 .23.00 .119.00 .249.00 .435.00 .39.00 .89.00 .89.00
203B 3EL 20 Meter Beam 155BA 3EL 15 Meter Beam 165B3 6EL 6 Meter Beam 18HTS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18A8 Balun 214 14EL 2 Meter Beam 205 5EL 2 Meter Beam 205 5EL 2 Meter Beam CD45 8.5 sq. ft. Rotator Ham IV 15 sq. ft. Rotator T2X 20 sq. ft. Rotator 12X 20 sq. ft. Rotat	.229.00 .119.00 .159.00 .339.00 .95.00 .36.00 .33.00 .23.00 .19.00 .19.00 .36.00 .19.00 .435.00 .249.00 .435.00 .39.00 .89.00 .79.00 .35.00
203B 3EL 20 Meter Beam 155BA 3EL 15 Meter Beam 165BA 6EL 6 Meter Beam 18HTS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical BN86 Balun 205 8EL 2 Meter Beam 205 5EL 2 Meter Beam 205 5EL 2 Meter Beam CD45 8.5 sq. ft. Rotator Ham IV 15 sq. ft. Rotator TZX 20 sq. ft. Rotator HDR300 25 sq. ft. Rotator V25 2 Meter Vertical Procomm 300 Headphones/Mic Procomm 300 Headphones/Mic Procomm 300 Headphones/ Free Shipping on all crank-up towers ICOM R70 General Coverage Receiver 720A General Coverage Xcvr	229.00 119.00 159.00 295.00 19.00 339.00 95.00 19.00 23.00 119.00 23.00 119.00 240.00 200
203B 3EL 20 Meter Beam 155BA 3EL 15 Meter Beam 155BA 5EL 15 Meter Beam 18HTS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT 2005 2000 2000 2005 5EL 2 Meter Beam 2005 5EL 2 Meter Beam 205 5EL	.229.00 .119.00 .159.00 .339.00 .95.00 .38.00 .33.00 .23.00 .19.00 .33.00 .23.00 .195.00 .249.00 .435.00 .435.00 .39.00 .89.00 .35.00 \$669.00 1,140.00
203B 3EL 20 Meter Beam 155BA 3EL 15 Meter Beam 155BA 5EL 15 Meter Beam 18HTS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18A8 Balun 214 14EL 2 Meter Beam 205 5EL 2 Meter Beam 205 5EL 2 Meter Beam CD45 8.5 sq. ft. Rotator Ham IV 15 sq. ft. Rotator T2X 20 sq. ft. Rotator 12X 20 sq. ft. Rota	.229.00 .119.00 .159.00 .339.00 .95.00 .36.00 .33.00 .23.00 .19.00 .19.00 .36.00 .19.00 .36.00 .19.00 .23.00 .19.00 .249.00 .249.00 .39.00 .249.00 .39.00 .39.00 .39.00 .39.00 .39.00 .39.00 .39.00 .39.00 .39.00 .39.00 .39.00 .39.00 .249.00 .39.00 .39.00 .249.00 .39.00 .39.00 .249.00 .39.00 .25.00 .29.00 .20.0
203B 3EL 20 Meter Beam 155BA 3EL 15 Meter Beam 155BA 5EL 15 Meter Beam 18HTS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 205 8EL 2 Meter Beam 205 5EL 2 Meter Beam 205 5EL 2 Meter Beam 205 5EL 2 Meter Beam CD45 8.5 sq. ft. Rotator Ham IV 15 sq. ft. Rotator T2X 20 sq. ft. Rotator HDR300 25 sq. ft. Rotator V2S 2 Meter Vertical Procomm 300 Headphones/Mic Procomm 300 Headphones/Mic Procomm 300 Headphones/Mic Free Shipping on all crank-up towers ICOM R70 General Coverage Receiver 720A General Coverage Xcvr 730 Xcvr 740 Xcvr 251A 2 Meter All Mode	229.00 .119.00 .159.00 .339.00 .95.00 .339.00 .339.00 .33.00 .33.00 .23.00 .19.00 .23.00 .195.00 .249.00 .435.00 .39.00 .39.00 .39.00 .595.00
203B 3EL 20 Meter Beam 155BA 3EL 15 Meter Beam 155BA 5EL 15 Meter Beam 18HTS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT WBS 80-10 Meter Vertical 208 5EL 2 Meter Beam 208 5EL 2 Meter Beam 205 5EL 2 Meter Beam 205 5EL 2 Meter Beam CD45 8.5 sq. ft. Rotator. T2X 20 sq. ft. Rotator. T2X 20 sq. ft. Rotator. T2X 20 sq. ft. Rotator. HDR300 25 sq. ft. Rotator. V2S 2 Meter Vertical. Procomm 200 Dual Headphones/Mic. Procomm 300 Headphone/Mic. C1210 Headphones. Free Shipping on all crank-up towers ICOM R70 General Coverage Receiver. 720A General Coverage Receiver. 730 Xcvr. 740 Xcvr. 251A 2 Meter All Mode. 451A Oscar Xcvr.	.229.00 .119.00 .159.00 .339.00 .339.00 .36.00 .33.00 .22.00 .19.00 .435.00 .435.00 .435.00 .435.00 .39.00 .35.00 \$669.00 1,140.00 .231.00 .575.00 .755.00
203B 3EL 20 Meter Beam 155BA 3EL 15 Meter Beam 155BA 5EL 15 Meter Beam 18HTS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18A8 Balun 214 14EL 2 Meter Beam 205 SEL 2 Meter Beam 205 SEL 2 Meter Beam CD45 8.5 sq. ft. Rotator Ham IV 15 sq. ft. Rotator T2X 20 sq. ft. Rotator HDR300 25 sq. ft. Rotator V2S 2 Meter Vertical Procomm 200 Dual Headphones/Mic Procomm 300 Headphone/Mic C1210 Headphones Free Shipping on all crank-up towers ICOM R70 General Coverage Receiver 720 A General Coverage Xcvr 730 Xcvr 251A 2 Meter All Mode 451A Oscar Xcvr	.229.00 .119.00 .159.00 .339.00 .95.00 .339.00 .36.00 .330.00 .23.00 .19.00 .19.00 .36.00 .19.00 .19.00 .19.00 .249.00 .39.00 .39.00 .39.00 .39.00 .35.00 \$669.00 1,140.00 call .575.00 .759.00
203B 3EL 20 Meter Beam 155BA 3EL 15 Meter Beam 155BA 5EL 15 Meter Beam 18HTS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT WBS 80-10 Meter Vertical 208 5EL 2 Meter Beam 208 5EL 2 Meter Beam 205 5EL 2 Meter Beam 205 5EL 2 Meter Beam CD45 8.5 sq. ft. Rotator. T2X 20 sq. ft. Rotator. T2X 20 sq. ft. Rotator. T2X 20 sq. ft. Rotator. HDR300 25 sq. ft. Rotator. V2S 2 Meter Vertical. Procomm 200 Dual Headphones/Mic. Procomm 300 Headphone/Mic. C1210 Headphones. Free Shipping on all crank-up towers ICOM R70 General Coverage Receiver. 720A General Coverage Receiver. 730 Xcvr. 740 Xcvr. 251A 2 Meter All Mode. 451A Oscar Xcvr.	229.00 .119.00 .159.00 .339.00 .95.00 .339.00 .339.00 .33.00 .23.00 .19.00 .23.00 .195.00 .249.00 .435.00 .39.00 .39.00 .55.00 \$6669.00 1,140.00 call
203B 3EL 20 Meter Beam 155BA 3EL 15 Meter Beam 155BA 5EL 15 Meter Beam 18HTS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 208 3EL 2 Meter Beam 208 3EL 2 Meter Beam 205 3EL 2 Meter Beam CD45 8.5 sq. ft. Rotator Ham IV 15 sq. ft. Rotator T2X 20 sq. ft. Rotator HDR300 25 sq. ft. Rotator V2S 2 Meter Vertical Procomm 300 Headphones/Mic C1210 Headphones Free Shipping on all crank-up towers ICOM R70 General Coverage Receiver 720 A General Coverage Receiver 720 A General Coverage Xcvr 730 Xcvr 740 Xcvr 251A 2 Meter All Mode 451A Oscar Xcvr 255 4 Meter 29H 2 Meter All Mode P515 Power Supply.	.229.00 .119.00 .159.00 .339.00 .95.00 .36.00 .33.00 .23.00 .19.00 .19.00 .36.00 .19.00 .33.00 .23.00 .19.00 .445.00 .39.00 .39.00 .39.00 .39.00 .35.00 \$669.00 1,140.00 .call .call .call .575.00 .759.00 .395.00 .299.00 .475.00 .135.00
203B 3EL 20 Meter Beam 155BA 3EL 15 Meter Beam 155BA 5EL 15 Meter Beam 18HTS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 208 8EL 2 Meter Beam 205 5EL 2 Meter Beam 205 5EL 2 Meter Beam 205 5EL 2 Meter Beam CD45 8.5 sq. ft. Rotator Ham IV 15 sq. ft. Rotator T2X 20 sq. ft. Rotator HDR300 25 sq. ft. Rotator 12X 20 sq. ft. Rotator	229.00 .119.00 .159.00 .339.00 .95.00 .339.00 .339.00 .33.00 .23.00 .19.00 .23.00 .195.00 .249.00 .435.00 .39.00 .39.00 .39.00 .39.00 .5669.00 1,140.00 .call
203B 3EL 20 Meter Beam 155BA 3EL 15 Meter Beam 155BA 5EL 15 Meter Beam 18HTS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 208 3EL 2 Meter Beam 208 3EL 2 Meter Beam 205 5EL 2 Meter Beam 205 5EL 2 Meter Beam CD45 8.5 sq. ft. Rotator HDR300 25 sq. ft. Rotator TXZ 20 sq. ft. Rotator HDR300 25 sq. ft. Rotator V2S 2 Meter Vertical Procomm 200 Dual Headphones/Mic Procomm 200 Headphone/Mic C1210 Headphones. Free Shipping on all crank-up towers ICOM R70 General Coverage Receiver. 720 Xcvr. 740 Xcvr. 251A 2 Meter All Mode 451A Oscar Xcvr. 25A 2 Meter. 29H 2 Meter All Mode. PS15 Power Supply. PS20 Power Supply. PS20 Power Supply.	.229.00 .119.00 .159.00 .339.00 .95.00 .33.00 .33.00 .23.00 .19.00 .33.00 .23.00 .195.00 .249.00 .435.00 .249.00 .435.00 .79.00 .35.00 .575.00 .395.00 .299.00 .299.00 .135.00 .299.00 .35.00 .299.00 .35.00 .299.00 .35.00 .299.00 .35.00 .299.00 .35.00 .299.00 .35.00 .299.00 .35.00 .299.00 .35.00 .299.00 .35.00 .299.00 .35.00
203B 3EL 20 Meter Beam 155BA 3EL 15 Meter Beam 155BA 5EL 15 Meter Beam 18HTS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 208 3EL 2 Meter Beam 208 3EL 2 Meter Beam 205 5EL 2 Meter Beam CD45 8.5 sq. ft. Rotator Ham IV 15 sq. ft. Rotator T2X 20 sq. ft. Rotator HDR300 25 sq. ft. Rotator V25 2 Meter Vertical Procomm 200 Dual Headphones/Mic Procomm 300 Headphone/Mic C1210 Headphones. Free Shipping on all crank-up towers ICOM R70 General Coverage Receiver 720 A General Coverage Xcvr 730 Xcvr 740 Xcvr 251A 2 Meter All Mode P515 Power Supply. PS20 Power Supply. SM2 Desk Mic SM5 Desk Mic	.229.00 .119.00 .159.00 .339.00 .95.00 .33.00 .19.00 .33.00 .19.00 .33.00 .19.00 .33.00 .19.00 .435.00 .435.00 .39.00 .35.00 \$669.00 1,140.00 .35.00 \$669.00 1,140.00 .35.00 .395.00 .299.00 .475.00 .395.00 .135.00 .135.00 .36.00
203B 3EL 20 Meter Beam 155BA 3EL 15 Meter Beam 155BA 5EL 15 Meter Beam 18HTS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 208 8EL 2 Meter Beam 205 5EL 2 Meter Beam 205 5EL 2 Meter Beam 205 5EL 2 Meter Beam CO45 8.5 sq. ft. Rotator Ham IV 15 sq. ft. Rotator T2X 20 sq. ft. Rotator 12X	229.00 .119.00 .159.00 .339.00 .95.00 .339.00 .339.00 .33.00 .23.00 .19.00 .23.00 .19.00 .249.00 .435.00 .39.00 .39.00 .39.00 .39.00 .575.00 .575.00 .395.
203B 3EL 20 Meter Beam 155BA 3EL 15 Meter Beam 155BA 5EL 15 Meter Beam 18HTS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT WBS 80-10 Meter Vertical 208 3EL 2 Meter Beam 208 3EL 2 Meter Beam 205 5EL 2 Meter Beam 205 5EL 2 Meter Beam CD45 8.5 sq. ft. Rotator. HDR300 25 sq. ft. Rotator. TZX 20 sq. ft. Rotator. HDR300 25 sq. ft. Rotator. V2S 2 Meter Vertical Procomm 200 Dual Headphones/Mic. Procomm 200 Headphone/Mic. C1210 Headphones. Free Shipping on all crank-up towers ICOM R70 General Coverage Receiver. 720A General Coverage Receiver. 730 Xcvr. 251A 2 Meter All Mode. 451A Oscar Xcvr. 25A 2 Meter Xelf Mode. 251A 2 Meter All Meter All Mode. 251A 2 Meter All Meter Al	.229.00 .119.00 .159.00 .339.00 .95.00 .33.00 .23.00 .19.00 .33.00 .23.00 .195.00 .249.00 .435.00 .249.00 .435.00 .249.00 .435.00 .79.00 .35.00 .575.00 .395.00 .299.00 .135.00 .299.00 .355.00 .299.00 .355.00 .299.00 .355.00 .299.00 .355.00 .299.00 .355.00 .299.00 .355.00 .299.00 .355.00 .299.00 .355.00 .299.00 .355.00 .299.00 .355.00 .299.00 .355.00 .299.00 .355.00 .299.00 .355.00 .299.00 .355.00 .299.00 .355.00 .299.00 .355.00 .299.00 .355.00 .355.00 .355.00 .355.00 .355.00 .355.00 .355.00 .355.00 .355.00 .355.00 .355.00 .355.00 .355.00 .355.00 .355.00 .355.00 .355.00 .355.00 .355.00 .299.00 .355.00 .355.00 .299.00 .355.00 .299.00 .355.00 .299.00 .355.00 .299.00 .355.00 .299.00 .355.00 .295.0
203B 3EL 20 Meter Beam 155BA 3EL 15 Meter Beam 155BA 5EL 15 Meter Beam 18HTS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT 2005 2000 2005 2000 2000 2005 2000 2000 2005 2000 2000 2005 2000 2000 2005 2000 2000 2000 2000 2000 2000 2000 20	.229.00 .119.00 .159.00 .339.00 .95.00 .33.00 .33.00 .23.00 .19.00 .35.00 .435.00 .435.00 .435.00 .39.00 .35.00 .35.00 .35.00 .35.00 .35.00 .35.00 .35.00 .35.00 .355.00 .395.00 .395.00 .395.00 .36.00 .35.0
203B 3EL 20 Meter Beam 155BA 3EL 15 Meter Beam 155BA 5EL 15 Meter Beam 18HTS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 205 8EL 2 Meter Beam 205 5EL 2 Meter Beam 205 5EL 2 Meter Beam 205 5EL 2 Meter Beam CD45 8.5 sq. ft. Rotator Ham IV 15 sq. ft. Rotator T2X 20 sq. ft. Rotator 12X	229.00 .119.00 .159.00 .339.00 .95.00 .339.00 .339.00 .33.00 .23.00 .19.00 .23.00 .19.00 .249.00 .435.00 .39.00 .39.00 .39.00 .55.00 .299.00 .475.00 .395.
203B 3EL 20 Meter Beam 155BA 3EL 15 Meter Beam 155BA 5EL 15 Meter Beam 18HTS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 208 3EL 2 Meter Beam 208 3EL 2 Meter Beam 205 5EL 2 Meter All Rotator. TZX 20 sq. ft. Rotator. TZX 20 sq. ft. Rotator. 15X 20 sq. ft. Rotator. VZS 2 Meter Vertical Procomm 200 Dual Headphones/Mic. Procomm 200 Dual He	.229.00 .119.00 .159.00 .339.00 .95.00 .33.00 .33.00 .23.00 .19.00 .33.00 .23.00 .195.00 .249.00 .435.00 .249.00 .435.00 .79.00 .35.00 .575.00 .395.00 .299.00 .395.00 .299.00 .135.00 .135.00 .135.00 .135.00 .135.00 .135.00 .125.00
203B 3EL 20 Meter Beam 155BA 3EL 15 Meter Beam 155BA 5EL 15 Meter Beam 18HTS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 205 8EL 2 Meter Beam 205 5EL 2 Meter Beam 205 5EL 2 Meter Beam 205 5EL 2 Meter Beam CD45 8.5 sq. ft. Rotator Ham IV 15 sq. ft. Rotator T2X 20 sq. ft. Rotator 12X	229.00 .119.00 .159.00 .339.00 .339.00 .36.00 .33.00 .22.00 .19.00 .33.00 .22.00 .19.00 .435.00 .249.00 .35.00 .39.00 .39.00 .35.00 .35.00 .36.00 .35.00 .35.00 .395.00 .395.00 .395.00 .395.00 .395.00 .395.00 .36.00 .36.00 .36.00 .36.00 .36.00 .35.00 .3
203B 3EL 20 Meter Beam 155BA 3EL 15 Meter Beam 155BA 5EL 15 Meter Beam 18HTS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT/WBS 80-10 Meter Vertical 18AVT 2005 8EL 2 Meter Beam 208 8EL 2 Meter Beam 205 5EL 2 Meter Beam CD45 8.5 sq. ft. Rotator. Ham IV 15 sq. ft. Rotator. 12X 20 sq. ft. Rotator. HDR300 25 sq. ft. Rotator. V2S 2 Meter Vertical Procomm 200 Dual Headphones/Mic. Procomm 300 Headphone/Mic. C1210 Headphones. Free Shipping on all crank-up towers ICOM R70 General Coverage Receiver. 720A General Coverage Receiver. 740 Xcvr. 740 Xcvr. 251A 2 Meter All Mode 451A 0Scar Xcvr. 255 6 Meter Acvr. 255 6 Meter All Mode. PS15 Power Supply. PS20 Power Supply. SM2 Desk Mic. SM5 Des	229.00 .119.00 .159.00 .339.00 .95.00 .33.00 .23.00 .19.00 .33.00 .23.00 .19.00 .249.00 .435.00 .249.00 .435.00 .39.00 .79.00 .35.00 \$669.00 1,140.00 call c

1	
IC2KL Solid State Amp	13.95
AT500 Automatic Tuner	
2AT/3AT/4AT Handhelds	
BC-30 Base Charger BP5 425ma 8.4v Battery	
BP4 Battery Case	
BP3 250ma 8.4v Battery	
BP2 425ma 7.2v Battery	
DC-1 DC Operating Module HM-9 Speaker/Mic	
KLM	
KT34A 4EL Triband Beam	\$309.00
KT34XA6 EL Triband Beam	465.00
144-148-13LBA 2M Long Boomer	
KANTRONICS	
Interface	
Mini-Reader Pkg. Mini-Terminal	
Software for:	. 249.00
Apple	
Atari	
VIC20	
KDK	
2030 2M Xcvr	.275.00
LARSEN NLA-150-MM 5/8 Wave 2M Mag. Mt.	\$30.00
NLA QMM 1/4 Wave 2M Mag. Mt.	
MFJ	
989 3KW Roller Inductor Tuner	
949B Tuner. 941C Tuner.	
940B Tuner	
901 Tuner.	
900 Tuner	
482 Keyer	
481 Keyer.	
408 Keyer	
406 Keyer 405 Keyer w/paddle	
401 Econokeyer	
496 Super Keyboard	
422 Keyer/BENCHER Paddle combo	
422 Keyer/BENCHER Paddle combo 722 Filter 624 Phone Patch w/meter 250 Dummy Load w/coil	
422 Keyer/BENCHER Paddle combo 722 Filter 624 Phone Patch w/meter 250 Dummy Load w/coil 812 VHF Meter	
422 Keyer/BENCHER Paddle combo 722 Filter. 624 Phone Patch w/meter. 250 Dummy Load w/coil. 812 VHF Meter. 814 HF Meter.	89.00 .63.00 .59.00 .32.00 .29.00 .45.00
422 Keyer/BENCHER Paddle combo 722 Filter 624 Phone Patch w/meter 250 Dummy Load w/coil 812 VHF Meter 814 HF Meter 816 HF Meter 820 Meter	89.00 63.00 59.00 29.00 45.00 29.00 63.00
422 Keyer/BENCHER Paddle combo 722 Filter 624 Phone Patch w/meter 250 Dummy Load w/coil 812 VHF Meter 814 HF Meter 816 HF Meter 820 Meter 825 Deluxe Meter	
422 Keyer/BENCHER Paddle combo 722 Filter 624 Phone Patch w/meter 250 Dummy Load w/coil 812 VHF Meter 814 HF Meter 816 HF Meter 820 Meter 825 Deluxe Meter 959 Rcvr Tuner w/preamp	
422 Keyer/BENCHER Paddle combo 722 Filter 624 Phone Patch w/meter 520 Dummy Load w/coil 812 VHF Meter 814 HF Meter 816 HF Meter 820 Meter 825 Deluxe Meter 959 Rcvr Tuner w/preamp 1040 Deluxe Preselector MIRAGE	89.00 63.00 59.00 29.00 45.00 29.00 63.00 105.00 81.00 89.00
422 Keyer/BENCHER Paddle combo. 722 Filter. 624 Phone Patch w/meter. 250 Dummy Load w/coil. 812 VHF Meter. 814 HF Meter. 816 HF Meter. 825 Deluxe Meter. 959 Rcvr Tuner w/preamp. 1040 Deluxe Preselector. MIRAGE B23 2/30 Amp.	
422 Keyer/BENCHER Paddle combo 722 Filter 624 Phone Patch w/meter 250 Dummy Load w/coil 812 VHF Meter 814 HF Meter 816 HF Meter 825 Deluxe Meter 959 Rcvr Tuner w/preamp 1040 Deluxe Preselector MIRAGE 823 2/30 Amp 8108	
422 Keyer/BENCHER Paddle combo           722 Filter           624 Phone Patch w/meter           520 Dummy Load w/coil           812 VHF Meter           814 HF Meter           816 HF Meter           820 Meter           822 Deluxe Meter           959 Rcvr Tuner w/preamp           1040 Deluxe Preselector           MIRAGE           82 //30 Amp           8108	
422 Keyer/BENCHER Paddle combo.           722 Filter.           624 Phone Patch w/meter.           250 Dummy Load w/coil.           812 VHF Meter.           814 HF Meter.           816 HF Meter.           825 Deluxe Meter.           959 Rcvr Tuner w/preamp.           1040 Deluxe Preselector.           MIRAGE           823 2/30 Amp.           8108           81016           90101 0//f60 440 MHz.	
422 Keyer/BENCHER Paddle combo. 722 Filter. 624 Phone Patch w/meter. 250 Dummy Load w/coil. 812 VHF Meter. 816 HF Meter. 826 Deluxe Meter. 825 Deluxe Meter. 827 Deluxe Preselector. MIRAGE 823 2/30 Amp. 8108. 81016. 83016. D1010 10/160 440 MHz. MP1/MP2 Watt Meters.	
422 Keyer/BENCHER Paddle combo. 722 Filter. 624 Phone Patch w/meter. 250 Dummy Load w/coil. 812 VHF Meter. 814 HF Meter. 816 HF Meter. 825 Deluxe Meter. 959 Rcvr Tuner w/preamp. 1040 Deluxe Preselector. <b>MIRAGE</b> 823 2/30 Amp. 81016.	
422 Keyer/BENCHER Paddle combo. 722 Filter. 624 Phone Patch w/meter. 250 Dummy Load w/coil. 812 VHF Meter. 814 HF Meter. 816 HF Meter. 825 Deluxe Meter. 959 Rcvr Tuner w/preamp. 1040 Deluxe Preselector. MIRAGE 823 2/30 Amp. 8108 81016 83016 D1010 10/160 440 MHz. MP1/MP2 Watt Meters. C106 220 MHz. C22 220 MHz. NYE	. 89.00 . 63.00 . 59.00 . 29.00 . 45.00 . 29.00 . 63.00 . 105.00 . 81.00 . 88.00 . 155.00 . 239.00 . 205.00 . 205.00 . 275.00 . 100.00 . 169.00
422 Keyer/BENCHER Paddle combo.         722 Filter.         624 Phone Patch w/meter.         250 Dummy Load w/coil.         812 VHF Meter.         814 HF Meter.         816 HF Meter.         825 Deluxe Meter         959 Rcvr Tuner w/preamp.         1040 Deluxe Preselector.         MIRAGE         823 2/30 Amp.         81016         83016         D1010 10/160 440 MHz.         MP1/MP2 Watt Meters.         C106 220 MHz.         NYE         Phone Patch.	. 89.00 . 63.00 . 59.00 . 32.00 . 29.00 . 45.00 . 29.00 . 63.00 . 105.00 . 81.00 . 88.00 . 155.00 . 239.00 . 275.00 . 100.00 . 169.00 . 80.00 . \$54.00
422 Keyer/BENCHER Paddle combo.         722 Filter.         624 Phone Patch w/meter.         250 Dummy Load w/coil.         812 VHF Meter.         814 HF Meter.         816 HF Meter.         825 Deluxe Meter.         959 Rcvr Tuner w/preamp.         1040 Deluxe Preselector.         MIRAGE         823 2/30 Amp.         8106         D1010 10/160 440 MHz.         MP1/MP2 Watt Meters.         C106 220 MHz.         C22 220 MHz.         NYE         Phone Patch.         Straight Key.	. 89.00 . 63.00 . 59.00 . 32.00 . 29.00 . 45.00 . 29.00 . 63.00 . 105.00 . 81.00 . 88.00 . 155.00 . 239.00 . 275.00 . 100.00 . 169.00 . 80.00 . \$54.00
422 Keyer/BENCHER Paddle combo.         722 Filter.         624 Phone Patch w/meter.         250 Dummy Load w/coil.         812 VHF Meter.         814 HF Meter.         816 HF Meter.         825 Deluxe Meter         959 Rcvr Tuner w/preamp.         1040 Deluxe Preselector.         MIRAGE         823 2/30 Amp.         81016         83016         D1010 10/160 440 MHz.         MP1/MP2 Watt Meters.         C106 220 MHz.         NYE         Phone Patch.         Straight Key.         ROBOT	. 89.00 . 63.00 . 59.00 . 22.00 . 29.00 . 45.00 . 29.00 . 63.00 . 105.00 . 81.00 . 89.00 . \$80.00 . 155.00 . 205.00 . 275.00 . 169.00 . 80.00 . \$54.00 . 13.00
422 Keyer/BENCHER Paddle combo.         722 Filter.         624 Phone Patch w/meter.         250 Dummy Load w/coil.         812 VHF Meter.         814 HF Meter.         816 HF Meter.         825 Deluxe Meter.         959 Rcvr Tuner w/preamp.         1040 Deluxe Preselector.         MIRAGE         823 2/30 Amp.         8106         90101 10/160 440 MHz.         MP1/MP2 Watt Meters.         C106 220 MHz.         C22 220 MHz.         NYE         Phone Patch.         Straight Key.         ROBOT         400 SSTV Scan Converter.         800 ASCII/Baudot/CW Terminal.	. 89.00 . 63.00 . 59.00 . 22.00 . 29.00 . 45.00 . 29.00 . 63.00 . 105.00 . 81.00 . 89.00 . \$80.00 . 155.00 . 205.00 . 275.00 . 169.00 . 80.00 . \$54.00 . 13.00
422 Keyer/BENCHER Paddle combo.           722 Filter.           624 Phone Patch w/meter.           250 Dummy Load w/coil.           812 VHF Meter.           814 HF Meter.           816 HF Meter.           825 Deluxe Meter.           959 Rcvr Tuner w/preamp.           1040 Deluxe Preselector.           MIRAGE           823 2/30 Amp.           8108           81016           93016           91010 10/160 440 MHz.           MP1/MP2 Watt Meters.           C106 220 MHz.           C22 220 MHz.           NYE           Phone Patch.           Straight Key.           ROBOT           400 SSTV Scan Converter.           800 ASCII/Baudot/CW Terminal.           SHURE	
422 Keyer/BENCHER Paddle combo.         722 Filter.         624 Phone Patch w/meter.         250 Dummy Load w/coil.         812 VHF Meter.         814 HF Meter.         816 HF Meter.         825 Deluxe Meter.         959 Rcvr Tuner w/preamp.         1040 Deluxe Preselector.         MIRAGE         823 2/30 Amp.         8106         90101 10/160 440 MHz.         MP1/MP2 Watt Meters.         C106 220 MHz.         C22 220 MHz.         NYE         Phone Patch.         Straight Key.         ROBOT         400 SSTV Scan Converter.         800 ASCII/Baudot/CW Terminal.	
422 Keyer/BENCHER Paddle combo.         722 Filter.         624 Phone Patch w/meter.         250 Dummy Load w/coil.         812 VHF Meter.         814 HF Meter.         816 HF Meter.         825 Deluxe Meter         959 Rovr Tuner w/preamp.         1040 Deluxe Preselector.         MIRAGE         823 2/30 Amp.         81016         D1010 10/160 440 MHz.         MP1/MP2 Watt Meters.         C106 220 MHz.         NYE         Phone Patch         Straight Key.         ROBOT         400 SSTV Scan Converter.         800 ASCII/Baudot/CW Terminal.         SHURE	
422 Keyer/BENCHER Paddle combo.         722 Filter.         624 Phone Patch w/meter.         250 Dummy Load w/coil.         812 VHF Meter.         814 HF Meter.         816 HF Meter.         825 Deluxe Meter         959 Rovr Tuner w/preamp.         1040 Deluxe Preselector.         MIRAGE         823 2/30 Amp.         81016         B1016         B3016         D1010 10/160 440 MH2.         MPI/MPZ Watt Meters.         C106 220 MHz.         NYE         Phone Patch         Straight Key.         ROBOT         400 SSTV Scan Converter.         800 ASCIl/Baudot/CW Terminal.         SHURE         44D Desk Mic.         414A Hand Mic.         TEN-TEC	
422 Keyer/BENCHER Paddle combo.         722 Filter.         624 Phone Patch w/meter.         250 Dummy Load w/coil.         812 VHF Meter.         814 HF Meter.         816 HF Meter.         825 Deluxe Meter         959 Rcvr Tuner w/preamp.         1040 Deluxe Preselector.         MIRAGE         823 2/30 Amp.         81016         83016         D1010 10/160 440 MHz.         MP1/MP2 Watt Meters.         C106 220 MHz.         NYE         Phone Patch.         Straight Key.         ROBOT         400 SSTV Scan Converter.         800 ASCII/Baudot/CW Terminal.         SHURE         444D Desk Mic.         414A Hand Mic.         TEN-TEC         525 Argosy.         645 Keyer.	
422 Keyer/BENCHER Paddle combo.         722 Filter.         624 Phone Patch w/meter.         250 Dummy Load w/coil.         812 VHF Meter.         814 HF Meter.         816 HF Meter.         825 Deluxe Meter.         959 Rovr Tuner w/preamp.         1040 Deluxe Preselector.         MIRAGE         823 2/30 Amp.         81016         93016         D1010 10/160 440 MH2.         MPI/MPZ Watt Meters.         C106 220 MHz.         NYE         Phone Patch.         Straight Key.         ROBOT         400 SSTV Scan Converter.         800 ASCIl/Baudot/CW Terminal.         SHURE         444D Desk Mic.         414A Hand Mic. <b>TEN-TEC</b> 525 Argosy.         645 Keyer.         227 Antenna Tuner.         444 Hercules Amplifier.	
422 Keyer/BENCHER Paddle combo.         722 Filter.         624 Phone Patch w/meter.         250 Dummy Load w/coil.         812 VHF Meter.         814 HF Meter.         816 HF Meter.         825 Deluxe Meter         959 Rcvr Tuner w/preamp.         1040 Deluxe Preselector.         MIRAGE         823 2/30 Amp.         81016         83016         D1010 10/160 440 MHz.         MP1/MP2 Watt Meters.         C106 220 MHz.         NYE         Phone Patch.         Straight Key.         ROBOT         400 SSTV Scan Converter.         800 ASCII/Baudot/CW Terminal.         SHURE         444D Desk Mic.         414A Hand Mic.         TEN-TEC         525 Argosy.         645 Keyer.         227 Antenna Tuner.         444 Hercules Amplifier.         217, 218, 219, 220 Filters.	
422 Keyer/BENCHER Paddle combo.         722 Filter.         624 Phone Patch w/meter.         250 Dummy Load w/coil.         812 VHF Meter.         814 HF Meter.         816 HF Meter.         816 HF Meter.         816 HF Meter.         816 Unter Meter.         825 Deluxe Meter.         959 Rcvr Tuner w/preamp.         1040 Deluxe Preselector.         MIRAGE         823 2/30 Amp.         81016         83016         D1010 10/160 440 MHz.         MP1/MP2 Watt Meters.         C106 220 MHz.         NYE         Phone Patch.         Straight Key.         ROBOT         400 SSTV Scan Converter.         800 ASCII/Baudot/CW Terminal.         SHURE         444D Desk Mic.         414A Hand Mic.         TEN-TEC         525 Argosy.         645 Keyer.         227 Antenna Tuner.         4244 Hercules Amplifier.         217, 218, 219, 220 Filters.         229 2KW Tuner.	
422 Keyer/BENCHER Paddle combo.         722 Filter.         624 Phone Patch w/meter.         250 Dummy Load w/coil.         812 VHF Meter.         814 HF Meter.         816 HF Meter.         825 Deluxe Meter.         929 Rovr Tuner w/preamp.         1040 Deluxe Preselector.         MIRAGE         823 2/30 Amp.         8108         81016         83016         D1010 10/160 440 MHz.         MP1/MP2 Watt Meters.         C106 220 MHz.         C22 220 MHz.         NYE         Phone Patch.         Straight Key.         ROBOT         400 SSTV Scan Converter.         800 ASCIl/Baudot/CW Terminal.         SHURE         444 Desk Mic.         414A Hand Mic.         TEN-TEC         525 Argosy.         645 Keyer.         227 Antenna Tuner.         444 Hercules Amplifier.         217, 218, 219, 220 Filters.         229 2KW Tuner.         TOKYO HY-POWER	
422 Keyer/BENCHER Paddle combo.         722 Filter.         624 Phone Patch w/meter.         250 Dummy Load w/coil.         812 VHF Meter.         814 HF Meter.         816 HF Meter.         816 HF Meter.         816 HF Meter.         816 NF Meter.         816 MF Meter.         816 NF Meter.         816 NF Meter.         825 Deluxe Meter         959 Rovr Tuner w/preamp.         1040 Deluxe Preselector.         MIRAGE         B23 2/30 Amp.         B1016         B3016         D1010 10/160 440 MH2.         MP1/MP2W att Meters.         C106 220 MHz         NYE         Phone Patch.         Straight Key.         ROBOT         400 SSTV Scan Converter.         800 ASCII/Baudot/CW Terminal.         SHURE         444D Desk Mic.         414A Hand Mic.         TEN-TEC         525 Argosy.         645 Keyer.         227 Antenna Tuner.         444 Hecues Amplifier.         217, 218, 219, 220 Filters.         229 ZW Tuner.         TOKYO HY-POWER         HU32V 25W Amp.	
422 Keyer/BENCHER Paddle combo.         722 Filter.         624 Phone Patch w/meter.         250 Dummy Load w/coil.         812 VHF Meter.         814 HF Meter.         816 HF Meter.         825 Deluxe Meter.         929 Rovr Tuner w/preamp.         1040 Deluxe Preselector.         MIRAGE         823 2/30 Amp.         8108         81016         83016         D1010 10/160 440 MHz.         MP1/MP2 Watt Meters.         C106 220 MHz.         C22 220 MHz.         NYE         Phone Patch.         Straight Key.         ROBOT         400 SSTV Scan Converter.         800 ASCIl/Baudot/CW Terminal.         SHURE         444 Desk Mic.         414A Hand Mic.         TEN-TEC         525 Argosy.         645 Keyer.         227 Antenna Tuner.         444 Hercules Amplifier.         217, 218, 219, 220 Filters.         229 2KW Tuner.         TOKYO HY-POWER	
422 Keyer/BENCHER Paddle combo.         722 Filter.         624 Phone Patch w/meter.         250 Dummy Load w/coil.         812 VHF Meter.         814 HF Meter.         816 HF Meter.         825 Deluxe Meter         959 Rovr Tuner w/preamp.         1040 Deluxe Preselector.         MIRAGE         823 2/30 Amp.         81016         81016         93016         D1010 10/160 440 MH2.         MPI/MPZ Watt Meters.         C106 220 MHz.         NYE         Phone Patch.         Straight Key.         ROBOT         400 SSTV Scan Converter.         800 ASCIl/Baudot/CW Terminal.         SHURE         444D Desk Mic.         414A Hand Mic. <b>TEN-TEC</b> 525 Argosy.         645 Keyer.         227 Antenna Tuner.         444 Hercules Amplifier.         217, 218, 219, 220 Filters.         228 XW Tuner.         TOKYO HY-POWER         HL32V 25W Amp.         HL32V 25W Amp.         HL32V 25W Amp.         HL32V 25W Amp.         HL32V 30W Amp.         HL32V 50W Amp.	
422 Keyer/BENCHER Paddle combo.         722 Filter.         624 Phone Patch w/meter.         250 Dummy Load w/coil.         812 VHF Meter.         814 HF Meter.         816 HF Meter.         825 Deluxe Meter         939 Rcvr Tuner w/preamp.         1040 Deluxe Preselector.         MIRAGE         823 2/30 Amp.         81016         83016         D1010 10/160 440 MHz.         MP1/MP2 Watt Meters.         C106 220 MHz.         NYE         Phone Patch.         Straight Key.         ROBOT         400 SSTV Scan Converter.         800 ASCII/Baudot/CW Terminal.         SHURE         444D Desk Mic.         414A Hand Mic. <b>TEN-TEC</b> 525 Argosy.         645 Keyer.         227 Antenna Tuner.         444 Hercules Amplifier.         217, 218, 219, 220 Filters.         229 2KW Tuner.         TOKYO HY-POWER         HL32V 25W Amp.         HL32V 36W Amp.         HL32W 160W Amp.	

Send SASE for our new & used equipment list.

## **The Tube Returns**

Move over, ICs. This receiver is easy to build, cheap, and works like a dream.

**B** ored with cranking out the contacts on your expensive transceiver? Been looking for a simple construction project to put some of the thrill back into ham radio? Maybe you'd just like to build something for the fun of seeing what you can make with that collection of old parts wasting away in the basement? If the answer is yes then this is for you.

Believe it or not, here is a surprisingly effective onetube shortwave receiver you can build in a weekend. The cost is 0 to 15 dollars, depending on your resourcefulness. No slouch on performance, it will pull in just about every signal on the 80-meter ham band that an expensive commercial receiver will hear. As described here, it tunes from 3.5 to 7.5 MHz but the frequency range is determined by plug-in coils and can be extended easily in either direction.

Old-timers have already recognized this project as a regenerative receiver. This type of detector has its roots in the misty past of radio lore and its reputation for high sensitivity is well earned. Early amateurs found that putting an adiustable amount of positive feedback around a detector had several benefits: An astounding amount of gain was available, the selectivity of the associated tuned circuit was vastly in-

Photos by W1GSL



The one-tube wonder at work. 64 73 Magazine • December, 1982

creased, and with proper adjustment either AM or CW signals could be copied easily. If a dual triode is chosen for the tube, then one section can be the regenerative detector and the other an audio amplifier. The resulting receiver is easy to construct, sensitive, and inexpensive. It was a very popular design in the 1920s and 30s.

There are, of course, several drawbacks. To receive code signals the feedback is adjusted so the detector is just barely oscillating, and with that setting a long antenna blowing around in the wind can cause frequency instability on the higher bands. Since the detector is oscillating, a steady carrier can be broadcast via the antenna. A few microwatts isn't going very far but the ham next door might hear it. Furthermore, any receiver with a single tuned circuit will tune rather broadly. While that isn't too much of a problem when all of the signals in the band are of similar strength, a really strong station on a nearby frequency (within 30 kHz or so) can cause problems.

All of these problems were eventually solved with the development of the superheterodyne receiver, but the regenerative detector continued to be used, if to a lesser extent, because of its simplicity and sensitivity. Until the mid 1950s there was always a one-tube regen featured as a good beginner's receiver in the ARRL Handbook. Even in the 60s there were designs for simple superhet receivers using regenerative detectors and controlled amounts of i-f regeneration to sharpen selectivity.

So much for history; let's turn to the project at hand. This circuit is a distillation from several described in the literature of the 50s. I tried not to use components that would be difficult to locate today and I'll point out a lot of circuit alternatives to take care of the most likely junk-box shortages.

The receiver uses a plugin coil—wound on the glass bulb of an extra octal tube—and covers 3.5 to 7.5 MHz. With that coil, the 80-meter band is covered with plenty of bandspread and the 40-meter band tunes pretty rapidly. You can wind other coils easily to cover 40 and 20 meters with plenty of bandspread.

The 80-meter tuning range is a good place to start since that band is not too crowded and the shortcomings of this simple receiver will be more pronounced on the higher frequency bands. The construction is genuine breadboard: very simple and easily adapted to whatever parts you collect. The performance is remarkable. With a 30- to 50-toot endted wire you will be able to copy just about everything on 80 meters, SSB included, without much problem. In fact, the 80-meter performance compares guite favorably with that of a 5- or 6-tube "allwave" receiver. The regenerative detector won't tune as conveniently as the superhet, but with a little practice the results are the same.

#### **The Circuit**

The circuit diagram for my receiver is shown in Fig. 1. You can copy it exactly or use it as the starting point for your own version. Before getting into possible variations let's take a close look at Fig. 1.

The antenna is linkcoupled to the detector coil through three or four turns of wire. This is the swinging coil visible in the photograph. There are two tuning knobs. One 365-pF section of the tuning capacitor from an old tube-type broadcast radio does the main tuning while a smaller, 140-pF variable, tapped down on the coil, is the slower tuning bandspread capacitor. A three- to fourturn feedback winding on the bottom end of the plugin coil allows the detector to oscillate when the regeneration control is set high enough.


The plate lead from the detector triode is filtered clean of rf after running through that feedback winding and the audio is capacitively coupled into the grid of the audio-amplifier triode. An inductor (the primary of an audio-output transformer) keeps the audio from getting back to the power supply and a 25k pot sets the regeneration level by adjusting the detector's plate voltage.

The audio amplifier is pretty straightforward, except perhaps that the headphones are connected directly into the plate lead. This is simple and works well but please note that the B+ runs through the headphones and you should be mindful of the shock hazard. The headphone jack is wired so that the voltage doesn't appear on the external part of the jack (which is normally grounded) until the 'phones are plugged in and, of course, the jack is insulated completely from the front panel

The power supply is correspondingly simple. Two small filament transformers feed each other back to back to provide both the 6.3 volts for the filament and a transformer-isolated 115 volts for the B+ supply.
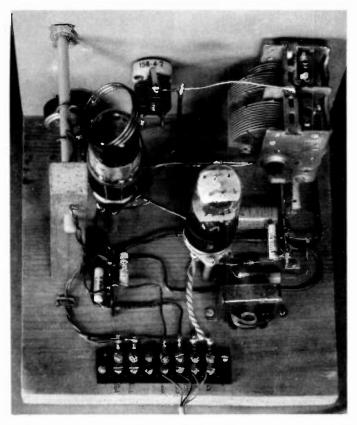
#### Construction

The physical design is straight out of the 50s. A  $7\frac{1}{2}$ - by 8-inch board is the base for the receiver, and most of the parts are mounted on terminal strips screwed to this board. The two tube sockets are mounted on 1-inch standoffs. The front panel is a piece of 1/16-inch aluminum to which are mounted the various controls. Most of the rf wiring is hung on the tuning capacitors, so it



Behind the dials: A simple circuit and classic breadboard construction.

is important that the front panel be mechanically rigid and electrically shielding. These two conditions ensure a minimum of problems due to microphonics (audio noise in the headphones due to mechanical disturbance of the electrical parts) or hand effect (frequency shifts caused by circuit capacitance variations due to motion of the operator's hands near the receiver).

The antenna is coupled into the tuned circuit by means of a swinging link coil. As can be seen in the photograph, this link is mounted near the middle of a 5-inch length of 1/4-inch-

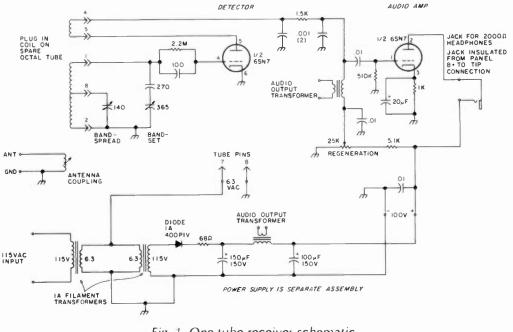



Fig. 1. One-tube receiver schematic.

diameter plastic rod. The rod need not be plastic any insulating material will do, even wood. The rod is supported at the front panel by a bushing (which was salvaged from an old volume control in keeping with the spirit of the project) and at the other end by a wooden pillar having a 1/4-inch hole through it in the appropriate spot.

The link was formed by winding stiff wire around a wooden dowel slightly larger in diameter than the 6SN7 coil form. The wire is kept under as much tension as possible while winding. The time-honored method is to clamp one end of the length of wire in a vise and, with the wooden form held in both hands, lean back to put tension on the wire as you wind your way toward the vise.

The coil will spring out some when it is taken off the form and probably several turns at the start will be distorted. Save three or four good turns with an inch and a half or so of lead on them. When the rod and 6SN7 coil form are both mounted, you can measure where the antenna link will have to go on the shaft in order to swing over the coil. Drill a pair of wire-diameter-sized holes at the appropriate spots and mount the link through them.

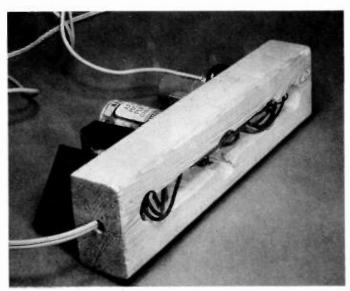The rest of the receiver layout is pretty well defined in the photographs. I used heavy wire for all of the rf wiring so that vibrationinduced microphonic effects would be at a minimum. Your layout doesn't have to match mine exactly as you surely won't have a




The power supply: built on a hollowed-out length of  $2 \times 3$ .

matching collection of parts.

The construction style of the power supply is also historically motivated. The supply is built as a separate unit to minimize 60-cvcle pickup in the receiver. I used a 1-foot-long section of wooden 2 by 3 with a slot jigsawed down the middle to contain the wiring. One concession was made to modern electronic design in the form of a silicon rectifier mounted on a terminal strip hidden under the "chassis." In earlier years, there would have been a 5Y3 or type-80 rectifier tube in the supply.
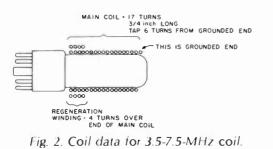
#### **Alternate Parts and Circuits**

Half the fun of building the one-tube receiver is coming up with a suitable collection of parts. The circuits are so noncritical that the builder can substitute with wild abandon and still have excellent results. This is especially true of the power-supply circuit.



volts ac at .6 Amps and 90 to 200 volts dc at 8 to 20 mA. If you're lucky, you will have a single small transformer providing these voltages and probably 5 volts as well (for a rectifier filament) that you won't need. I didn't have any suitable small power transformers, but I did have a collection of filament transformers. Two were wired back to back as indicated in Fig. 1.

The receiver needs 6.3

Of course, it is all right to use a single large transformer if that's what's available. If the voltage is too high (250 volts or more), a 10 or 15k, 1-Watt resistor can always be used in place of the filter inductor. A really large transformer, like that from an old TV set, should probably be mounted on a metal chassis for safety's sake—an inverted cake pan will serve if the junk box lacks a chassis.

The rectifier I used is a small silicon unit rated at 1 Amp and 400 peak inverse volts. A full-wave bridge rectifier would be nicer since the 120-cycle ripple is easier to filter than the output of a single diode. The more filter capacitance the better. Don't be afraid to experiment with smaller amounts than I used, but be prepared to add more if hum is a problem. Be sure the capacitors are rated to work at voltages higher than they will see in the circuit. The filter inductor would ideally be a small 5- to 20-Henry unit rated at 20 mA or more. Small chokes, like small power transformers, are not too plentiful these days, so I used the primary of a salvaged TV set audio-output transformer instead.

An entire alternate receiver schematic is shown in Fig. 3. I haven't built a receiver using this schematic, but it is included here to illustrate a number of circuit variations. You can mix and match circuit features from Figs. 1 and 3 to make maximum use of the parts you have on hand. Note first how the antenna is capacitively coupled to the tuned circuit. If you have a small variable capacitor and a big knob, you may find this version easier to build than the swinging link. Both sides of the capacitor must be insulated from the panel and the large knob is desirable since placing your hand near the control shaft may influence the antenna coupling. This circuit arrangement was used in the 1952 ARRL Handbook receiver with a homemade capacitor constructed much along the lines of my swinging link-though plates were used instead of coils, of course.

If you have another small capacitor with a suitable shaft, you can use it as a bandspread capacitor. The smallest variable I had was 140 pF, so when I wound my coil I put a tap a few turns up from the ground end and connected that larger capacitor across only part of the coil. A 10- or 15-pF variable can go across the entire coil as shown in Fig. 3. and if you only have several 365-pF units, you can use a tap on the coil even closer to ground than mine. Don't overlook old FM radios as a



source of small-value variable tuning capacitors. UHF TV tuners are another possibility and they often have 'a built-in vernier dial as well.

The 100-pF coupling capacitor can be any value from 50 to 250 pF and the grid-leak resistor can range from 1 to 10 megohms. Even the tube itself can be changed; a 12AU7 or 6CG7 will work as well as the 6SN7, though the base wiring and filament needs will be different. Naturally a real plug-in coil form will work as well as the spare 65N7 | used, and anv straight-sided glass octal tube will do the job as well as a 6SN7. Be careful not to use both filament pins of a tube for coil connections unless the filament is burnt out. I used #24 solid insulated wire for winding the coils. The coil ends are brought down over the outside of the tube base and soldered to the ends of the pins. A dab of cement holds the wires in place on the glass

One big change in the circuit of Fig. 2 is that the regeneration control has been replaced by a 365-pF variable capacitor. There is a good reason for this circuit change: lower adjustment noise. The trouble with the 25k pot used in Fig. 1 is that it has dc flowing through it. Carbon pots, unlike wirewound ones, develop con-

tact noise when used this way and eventually sound scratchy when rotated. I used the carbon pot because wire-wound ones are hard to find, but the variable-capacitor approach is a better solution to the problem and you may want to try it.


A 1- or 2.5-mH rf choke is used in the plate circuit and an audio-interstage transformer provides coupling to the audio amplifier. The audio-output transformer used for this purpose in Fig. 1 could also be replaced with any power-supply-type choke rated at more than 10 mA and 2 H or so inductance Also shown in Fig. 2 is an audio transformer or supply choke used as a dc feed path for the audio amplifier. This permits ac coupling to the headphones and gets them out of the dc side of the circuit. If your main interest is in CW work, you may want to add some audio selectivity by placing a capacitor across the transformer winding as shown. The resulting tuned circuit can be set to the desired audio frequency by adjusting the capacitor value on a cut-and-try basis. The actual value will depend on the inductance of the transformer you have. Try starting with .01 or .05 uF and listen for an audio peak as you tune across a CW signal. Use a larger- or smallervalue capacitor to lower or

raise the peak frequency as necessary.
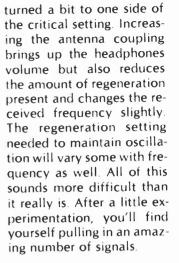
#### Operation

Getting the most out of this little receiver is going to require some practice because the controls interact more than they do on a modern superhet. Peaking the preselector control on a transceiver may change the speaker volume a little, but you don't expect it to alter the i-f bandwidth or receiver tuning! Basic operation of the receiver is as follows: The main tuning is set to the approximate frequency of interest and the bandspread control to the middle of its range. The antenna-coupling link is positioned over the top of the coil and the regeneration control advanced. A "plop-hiss" noise in the headphones announces that the detector has started to oscillate. The control is positioned just after the oscillation starts and the receiver is tuned to a signal with the two tuning capacitors.

You will find that the sensitivity and selectivity are greatest with the regeneration set so the detector is close to the oscillation threshold. CW and SSB signals are copied with the detector oscillating, while for AM reception the regeneration is backed down just below the threshold. Often it is easiest to find a signal with the regeneration



### Troubleshooting and Calibration

One side benefit of this design is that there is so little to go wrong. If the receiver is built according to the schematic and with good parts, it will most likely work when turned on. If it doesn't, and a series of circuit and voltage checks indicates that everything is OK, then the problem is probably with the regeneration coil. Try reversing the connection of the link winding. If the receiver cannot be made to oscillate on the lower end of the tuning range, then slide the feedback winding closer to the main coil. The coil dimensions recommended in Fig. 2 will surely get you off to a good start but you may wish to experiment with different geometries.

Once the receiver is pulling in signals, you will want to calibrate the dials. This is easy to do with the help of another receiver since the oscillating regenerative detector generates a weak carrier on the frequency to which it is tuned. Set the calibrated receiver to a given frequency, turn up the regeneration control on the little set, then sweep its bandset knob until you hear its carrier in the other receiver. At that setting the two receivers are listening to the same frequency. I glued a paper scale behind my tuning knobs and marked the bandset-dial

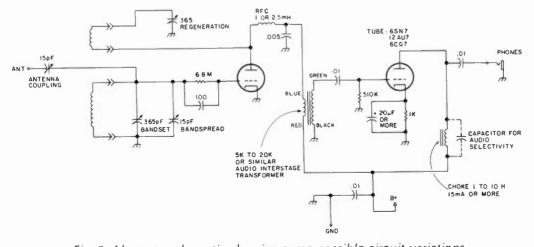


Fig. 3. Alternate schematic showing some possible circuit variations. 68 73 Magazine • December, 1982


position at every half megahertz. The bandspread dial was marked for the 80meter Novice band and the whole 40-meter band. Of course, the bandspread calibration is only accurate when the bandset knob is set properly.

#### **Other Coils**

Changing the tuning range means winding other plug-in coils. Simply use more turns to go down in frequency and fewer to go up. On the higher bands. space out the turns so the whole coil is 1/2 to 3/4 of an inch long. The number of regeneration turns should also increase or decrease one or two, in step with the main coil change. If your main tuning capacitor has two sections, you can place jumpers across otherwise unused coil pins and wire the socket to use both capacitor sections on low bands and only one on the higher frequencies.
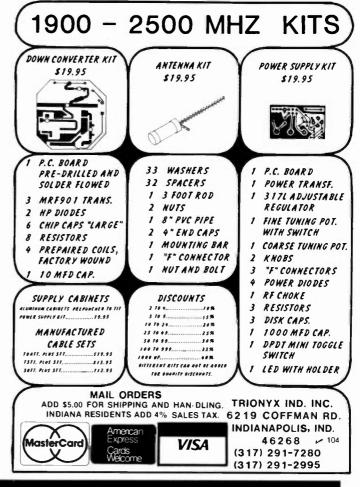
#### A Word of Warning

This little receiver is really a lot of fun to operate. It is cheap to build and can be thrown together in a weekend. If there are a few spare octal tubes on hand, the frequency range can easily be extended in either direction. One word of caution is necessary though. The time will come when you tune across 80 meters with this set and realize that you can hear just about every signal on the band. In fact, you could actually use this little gem to make some real contacts (and enjoy shaking up the ham on the other end with a description of your receiver)! After you do that several times you'll naturally start to think about onetube QRP transmitters. So when nosing around the local flea market for 6SN7s keep an eye out for a slightly larger power transformer, a 6AG7, some 80-meter crystals, and maybe a few old B&W plug-in coils.



## Big TEN-TEC OMNI-C & ARGOSY Overstock Sale

TEN-TEC Model 546 0MNI/Series-C All solid-state, 200w SSB/CW HF Transceiver. 9 HF bands, 160-10m including 10, 18 & 24.5 Mhz & 10 MHz WWV; 40 KHz VFO overrun. Instant band change, no tune-up. Digital readout, six 0.43" LEDs - read to 100 Hz. 8-pole 2.4 KHz SSB filter and audio active filter. Select standard SSB filter, optional 1.8 KHz SSB filter or optional CW filter plus 450 Hz or 150 Hz of audio filtering, 50 dB notch filter, ± 500

Hz & ± 4 KHz offset tuning, QSK CW break-in, VOX or PTT.

adj. ALC, S/SWR meter, sidetone, built-in spkr. 13.8vdc

@ 18A: 5½"h × 14½" w × 14"d. 14½ lbs... SAVE \$389

Regular \$1289 - Sale Price \$89995

Common OMNI-C/ARGOSY access	sorie	S:
215PC Ceramic microphone w/coil cord		
217 500 Hz 8-pole CW filt. (Reg. \$59)	SALE	5495
218 1.8 KHz 8 pole SSB filt. (Reg. \$59)	SALE	5495
219 250 Hz 6 pole CW filter (Reg. \$59)	SALE	5495
234 Speech Processor (Reg. \$139)	SALE	\$12495
214 Electret microphone		
OMNI-C accessories:		
	SALE	\$15495
	SALE	17995
	SALE	16995
1140 DC circuit breaker.		1000
645 Dual paddle keyer (Reg. \$85)	SALE	7995
ARGOSY accessories:		
225 9A power supply (Regular \$129)	SALE	\$11995
220 2.4 KHz 8 pole SSB filt. (Reg. \$59)	SALE	5495
222 Mobile mount		2500
223A Noise blanker		3400
224 Audio CW filter		3400
226 25 KHz crystal calibrator		3900
670 Single paddle keyer		3900
1125 DC circuit breaker w/cable		1800



#### rder Toll Free: 1-800-558-0411 In Wisconsin (outside Milwaukee Metro Area) 1-800-242-5195 EUR ELECTRONIC SU Inc. 4828 W. Fond du Lac Avenue; Milwaukee, WI 53216 - Phone (414) 442-4200 **AES** BRANCH STORES Associate Store WICKLIFFE, Ohio 44092 **ORLANDO, Fla.** 32803 LAS VEGAS, Nev. 89106 CLEARWATER, Fla. 33515 CHICAGO, Illinois 60630 621 Commonwealth Ave. Phone (305) 894-3238 28940 Euclid Avenue 1072 N. Rancho Drive ERICKSON COMMUNICATIONS 1898 Drew Street Phone (216) 585-7388 5456 N. Milwaukee Avenue Phone (813) 461-4267 Phone (702) 647-3114 Fla. WATS 1-800-432-9424 Ohio WATS 1-800-362-0290 No In-State WATS No In-State WATS Phone (312) 631-5181 Outside 1-800-321-3594 Outside Nevada 1-800-634-6227 Outside 1-800-327-1917 Outside 1-800-621-5802 No Nationwide WATS





## Just in time for Santa to get the word!

## Here's where to check out the Microlog of your choice:

Santa's Microlog Workshop 18713 Mooney Drive Gaithersburg, MD 20879 (301) 258-8400 TELEX: 908153

#### EASTERN UNITED STATES

Amateur Electronic Supply 28940 Euclid Avenue Wickliffe, OH 44092 (216) 585–7388 800–321–3594

The Comm Center Route 198 Laurel, MD 20810 (301) 792-0600 Jerry

EGE Inc. 13646 Jeff Davis Highway Woodbridge, VA 22191 (703) 643–1063 John

EISCO 11305 Elkin Street Wheaton, MD 20902 (301) 946-1088 Rolando

G & G Electronics 16424 Grande Vista Drive Rockville, MD 20855 (301) 948-7388 Jeff

Hamtronics/Trevose 4033 Brownsville Road Trevose, PA 19047 (215) 357-1400 Jim

Tufts Electronic Dept. Store 61 Lowell Road Hudson, NH 03051 (603) 883-5005 Chuck

#### MIDWEST

Amateur Electronic Supply 4828 West Fond Du Lac Avenue Milwaukee, WI 53216 (414) 442–4200 Paul 800–558–0411 The Ham Shack 808 North Main Street Evansville, IN 47711 (812) 422–0231 Dan

Madison Electronic Supply 1508 McKinney Houston, TX 77010 (713) 658–0268 Don

Midcom Electronics 8516 Manchester Road St. Louis, MO 63144 (314) 961–9990 Dolores

#### SOUTHERN

Amateur Electronic Supply 1898 Drew Street Clearwater, FL 33515 (813) 461-4267

Amateur Electronic Supply 621 Commonwealth Orlando, FL 32803 (305) 894–3238 800–327–1917

Amateur Radio Center 2805 N E 2nd Avenue Miami, FL 33137 (305) 573-8383 Arturo

Amateur Radio Supply of Nashville 615 South Gallatin Road Madison, TN 37115 (615) 868–4956 Frank

Britts 2-Way Radio 2508 N Atlanta Road Smyrna, GA 30080 (404) 432-8006 Dan

High Technology Electronics 3229A S Andrews Avenue Ft. Lauderdale, FL 33316 (305) 764-8308 Jeff

HELP Radio 1055 Liberty Street Jacksonville, FL 32206 (904) 356–8546 Al

#### WESTERN

Amateur Electronic Supply 1072 North Rancho Drive Las Vegas, NV 89106 (702) 647-3114 800-634-6227

Burghardt Amateur Center 208 East Kemp Avenue Watertown, SD 57201 (605) 886-7314 Jim

Conley Radio Supply 318 N 16th Street Billings, MT 59101 (406) 259–9554 Ron

CW Electronic Sales 800 Lincoln Street Denver, CO 80203 (303) 832-1111 Pete

Ham Radio Outlet 2620 West La Palma Anaheim, CA 92801 (714) 761-3033 Earl 800-854-6046

Ham Radio Outlet 999 Howard Avenue Burlingame, CA 94010 (415) 342–5757

Ham Radio Outlet 2811 Telegraph Avenue Oakland, CA 94609 (415) 451-5757

Ham Radio Outlet 5375 Kearny Villa Road San Diego, CA 92123 (714) 560-4900

Ham Radio Outlet 6265 Sepulveda Blvd. Van Nuys, CA 91401 (213) 988-2212

#### CANADA

Colmay Products 14902 Beachview Avenue White Rock, BC V4B 1N8 (604) 536-3058 Colin

### - Current Microlog Equipment and Accessory Price List

ATR-6800 System, 9" B&W Video, Application Module, Cable Kit \$ 2	
As Above, Less Video \$ 2	370
Morse Trainer Module\$	189
ARQ Mode B Receive Module\$	
Data Ecryption Board\$ 1	
BASIC/Mailbox/16K Bat\$	599
Epson MX 80 Print, Custom Cable & Ser. Board\$	
Okidata 82A Print, With Custom Cable\$	600
Extra ATR-6800 Manual Set\$	25

ACT-1 System	\$ 995	5
Bat Backup/Print (new) Add \$25 for Previously Shipped Unit	\$ 12	5
RF Video Modulator	\$ 3	
Monitor Ext. Legs		0
Custom Interface Cable for MX80 or 82A Printer (Specify ATR or ACT-1)		
9" B&W Video	\$ 19	9
12" B&W Video	\$ 22	9
9" Green Video		9
Extra ACT-1 Manual	\$ 1	0



## **MEMORY BACK-UP** AND HIGH SPEED PRINTER OUTPUT\*

### **Never Lose Your Memory Again!**

All "Here-is" memories, ID's **and** all keyboard input parameters are retained for 2 weeks by the internal Ni-Cad battery & charging circuit. Load up the memories, carry the ACT-1 out to your field-day site and be ready to go as if you never turned it off! Also included in this option package is the high speed code converted RS-232 serial printer output.

The best gets better at MICROLOG Corp. 18713 Mooney Dr., Gaithersburg, MD 20879 Tel. 301-258-8400 TELEX 908153.



• SIMPLE DIRECT CONNECTION to your Transceiver. • COMPLETE SYSTEM, built-in Demodulator & AFSK Modulator with keyboard programmable tone pairs from 500 to 3000 Hz. • SPLIT-SCREEN operation with keyboard selectable line location • 1400 character text buffer. • TEN, 40 CHAR. programmable message memories (doubles with BATT. BACKUP), plus ID's WRU & SELCALS.

RANDOM CODE generator & hand key input for practice.
Baudot 60 to 132
WPM.
ASCII 110 & 300 baud.
SYNC-LOC MODE for improved ASCII operation.
RECORDER INTERFACE for "BRAG-TAPE" or recording off-the-air.
CODE CONVERTED printer output in Baudot or ASCII.
SSTV/GRAPHICS transmit.
FULL 63 KEY Computer grade keyboard.

\*9" monitor \$199. Battery Backup & RS232 print \$125.

Jack Martin W8XW 701 Radar Squadron Box 1774 Kure Beach NC 28449

## The Program That Knows It All

Repeater info, third-party agreements, you name it this TRS-80 BASIC program knows it.

#### Hey, OM. Shall I QRQ?"

"Er, uh, yeh. 1 guess." Boy, I sure wish I knew what he meant! Where did I put that list of Q-signals?

I operate contests quite a bit. I keep a dupe sheet in front of me, but I sure wish I could search through those calls faster!

Has it been ten minutes since I last IDed? Six minutes? Or 12?

Just showed that FCC examiner a few things and upgraded my license. Now let's explore this new territory...umm, how far down can I go? Am I in the phone portion of this new band?

Familiar situations? Well,

MENU OF COMMANDS 1. REPEATER INFO 2. CONTEST OPERATOR 3. Q-SIGNALS 4. THIRD-PARTY AGREEMENTS 5. IDER 6. FREQUENCY CHECK 7. EXIT COMMAND?

Fig. 1. Sample run of commands available for user. now you can relax. This versatile program will put fun and pleasure back into your hamming. Just by inputting a bit of information about a repeater station (last three letters of its call, its frequency pair, or its location), the program will provide all the information concerning that repeater. If you are a contest operator, this program was made for you. It provides dupe sheet capability with memory and fast recall. No more lost contacts while you check your log to see if you worked that station. Those infrequently used Q-signals are now available when you need them and there is no more wondering whether that country has a thirdparty agreement before running the phone patch.

		$\vee$			
_	Т	1	T	T	
3.5	3.6	3.7	3.8	3.9	4.0
0		Frequences	,		

display showing 3.5-MHz band with operating frequency of 3.7 MHz. A display is provided for each band, 80-2 meters.

I remember when I upgraded and was operating on new and unfamiliar bands, I was constantly referring to a chart to see where the band limits were and if I was still in the phone or CW portion of the band. Before using this program, 1 still had to resort to that chart when I would occasionally operate on a seldom used band. Now the computer will verify the legality of my operating freguency and visually display where I am operating within that band.

Last but not least, the program provides a visual reminder to satisfy the station identification requirement and will give a flashing reminder when it is time to identify.

Written for the Radio Shack Level II TRS-80 with 16K memory, the program requires about 9K to run. Since there are no unique statements, it should readily adapt to other BASICs. The overall program is actually composed of seven different subprograms. By compartmentalizing it in this manner, the user may choose all or portions of the program to fit his particular needs or memory capability.

Program action is simple to follow. Just respond to the computer's requests and you cannot go astray. The program should be loaded and ready to use when the operator sits down for a hamming session. Then he will have all these capabilities at his fingertips.

**Program** Introduction: Statement lines 1 through 52 graphically introduce the program and ask the user to input his choice of subprograms. I have made extensive use of the INKEY\$ function throughout the program. This allows faster responses and saves wasted effort by not having to use the ENTER key to input data. Safeguards have been incorporated to prevent the program from crashing if a wrong key is inadvertently hit.

Favorite Repeater: Statement lines 100 through 288 comprise the repeater infor-

72 73 Magazine • December, 1982



### MFJ-941C 300 Watt Versa Tuner II

Has SWR/Wattmeter, Antenna Switch, Balun. Matches everything 1.8-30 MHz: dipoles, vees, random wires, verticals, mobile whips, beams, balanced lines, coax lines.



Fastest selling MFJ tuner . . . because it has the most wanted features at the best price. Matches everything from 1.8-30MHz: dipoles,

inverted vees, random wires, verticals, mobile whips, beams, balanced and coax lines. Run up to 300 watts RF power output.

SWR and dual range wattmeter (300 & 30 watts full scale, forward/reflected power). Sensitive meter measures SWR to 5 watts.

#### **MFJ-900 VERSA TUNER**



MFJ-900 \$4995 (+ \$4)

Matches coax, random wires 1.8-30 MHz. Handles up to 200 watts output; efficient airwound inductor gives more watts out. 5x2x6". Use any transceiver, solid state or tube.

Operate all bands with one antenna. 2 OTHER 200W MODELS:

MFJ-901, \$59.95 (+ \$4), like 900 but includes 4.1 balun for use with balanced lines.

MFJ-16010, \$39.95 (+ \$4), for random wires only. Great for apartment, motel, camping, operation. Tunes 1.8-30 MHz.

#### MFJ-984 VERSA TUNER IV



Up to 3 KW PEP and it matches any feedline, 1.8-30 MHz, coax, balanced or random.

10 amp RF ammeter assures max, power at min. SWR. SWR/Wattmeter, for./ref., 2000/200W. 18 position dual inductor, ceramic switch.

7 pos. ant. switch. 250 pl 6KV cap. 5x14x14". 300 watt dummy load. 4:1 ferrite balun. 3 MORE 3 KW MDDEL1: MFJ-981, \$239.95 (+\$10), like 984 less ant. switch, ammeter.

MFJ-982, \$239.95 (+ \$10), like 984 less ammeter. meter, SWR/Wattmeter. MFJ-980, \$209.95 (+ \$10), like 982 less ant. switch. Flexible antenna switch selects 2 coax lines, direct or through tuner, random wire/balanced line, or tuner bypass for dummy load.

12 position efficient airwound inductor for lower losses, more watts out.

Built-in 4:1 balun for balanced lines. 1000V capacitor spacing.

Works with all solid state or tube rigs.

Easy to use, anywhere. Measures 8x2x6", has

#### MFJ-949B VERSA TUNER II



MFJ's best 300 watt Versa Tuner II.

Matches everything from 1.8-30 MHz, coax, randoms, balanced lines, up to 300W putput, solid-state or tubes.

Tunes out SWR on dipoles, vees, long wires, verticals, whips, beams, guads.

Built-in 4:1 balun. 300W, 50-ohm dummy load. SWR meter and 2-range wattmeter (300W & 30W).

6 position antenna switch on front panel, 12 position air-wound inductor, coax connectors, binding posts, black and beige case 10x3x7".



New smaller size matches new smaller rigs - only 10-3/4Wx4-1/2Hx14-7/8D".

3 KW PEP. 250 pf-6KV caps. Matches coax, balanced lines, random wires 1.8-30 MHz.

Roller inductor, 3-digit turns counter plus spinner knob for precise inductance control to get that SWR down.

Built-in 300 watt, 50 ohm dummy load. Built-in 4:1 ferrite balun.

Built-in lighted 2% meter reads SWR plus forward/reflected power. 2 ranges (200 & 2000W). -47 6 position ant. switch, Al. cabinet. Tilt bail.

#### Ham Radio's most popular antenna tuner. Improved, too.



S0-239 connectors, 5-way binding posts, finished in eggshell white with walnut-grained sides. 4 Other 300W Models: MFJ-940B, S79.95 (+ \$4), like 941C less balun. MFJ-945, S79.95 (+ \$4), like 941C less antenna switch. MFJ-944, S79.95 (+ \$4), like 945, less SWR/Wattmeter, MFJ-943, S69.95 (+ \$4), like 944, less antenna switch. Optional mobile bracket for 941C, 940B, 945, 944, \$3.00.

#### MFJ-962 VERSA TUNER III



Run up to 1.5 KW PEP, match any feed line from 1.8-30 MHz.

Built-in SWR/Wattmeter has 2000 and 200 watt ranges, forward and reflected.

6 position antenna switch handles 2 coax lines (direct or through tuner), wire and balanced lines. 4:1 balun. 250 pf 6KV cap. 12 pos. inductor.

Ceramic switches. Black cabinet, panel.

ANOTHER 1.5 KW MODEL: MFJ-961, \$189.95 (+ \$10), similar but less SWR/Wattmeter.



For tech. info., order or repair status, or calls outside continental U.S. and inside Miss., call 601-323-5869.

800-647-1800

- All MFJ products unconditionally guaranteed for one year (except as noted).
- Products ordered from MFJ are returnable within 30 days for full refund (less shipping).
- Add shipping & handling charges in amounts shown in parentheses.



```
REM JACK MARTIN - WEXW
  2 REH NEW 1986
9 CLERRI800
10 DIME&(18)
11 DIME&(18)
12 CLS:RPINTCHR&(23)
14 PRINT448,"**** H A M H E L P E R ***"
15 FOR*=1705
18 PRINT&718,"C 0 - C 0 - C 0"
26 FORX=170260*NEXTX
22 PRINT&710,"
34 FORX=170200*NEXTX
24 FORX=170200*NEXTX
                              HEXTY
CLS:PRINT"MENU OF COMMANDS"
PRINTSTRING$(55, "=");
    26
28
38
28 CLS:PRINT"HENU OF COMMENDS"

30 PRINT:PRING(SS, """);

31 PRINT:PRING(SS, """);

32 PRINT"RING(SS, """);

33 PRINT"L. REPEATER INFO"

34 PRINT"L. REPEATER INFO"

35 PRINT"S. OF SIGNALS"

40 PRINT"S. OF SIGNALS"

41 PRINT"S. ID "EP"

42 PRINT"S. ID "EP"

43 PRINT"S. FREQUENCY CHECK"

44 PRINT"S. FREQUENCY CHECK"

46 PRINT"S. FRENTE FREQUENCY CHECK"

46 PRINT"S. FRENTE FREQUENCY CHECK"

47 PRINT"S. FRENTE FREQUENCY CHECK"

46 PRINT"FRENTE FREQUENCY CHECK"

47 PRINT"FRENTE FREQUENCY CHECK"

47 PRINT"FRENTE FREQUENCY CHECK"

47 PRINT"FRENTE FREQUENCY CHECK"

48 PRINT"THES PROGRAM WILL PROUIDE INFORMATION ABOUT"

49 PRINT"FREE LETTERS OF ITS CALL OR THE LAST"

49 PRINT"FREE LETTERS OF ITS CALL OR THE LAST"

40 PRINT"FREE LETTERS OF ITS CALL OR THE CHECT"

41 PRINT"FREENTER IS LOCATED."

41 PRINT"FREENTER IS LOCATED."

41 PRINT"FREENTER IS LOCATED."

42 PRINT"GSTATION":S$

43 REGUINE"FRETORS="34/94"ORS$="BECKLEY"GOSUE200

41 IFSI="FRE"ORS$="34/94"ORS$="BECKLEY"GOSUE200

41 IFSI="FRE"ORS$="28/28"ORS$="CHEKKEESTON"GSUE201

45 IFSI="FREE"ORS$="28/28"ORS$="CHEKKEESTON"GSUE201

45 IFSI="FREE"ORS$="28/28"ORS$="CHEKKEESTON"GSUE201

46 IFSI="FREE"ORS$="28/28"ORS$="CHEKKEESTON"GSUE201

47 IFSI="FREE"ORS$="28/28"ORS$="CHEKKEESTON"GSUE201

49 IFSI="FREE"ORS$="28/28"ORS$="CHEKKEESTON"GSUE201

40 IFSI
        198
                                             IFX20THEN282
                                      IFX30THEN282

GOT0280

PRINT"WR8HC0.34/94,350 ";DI;" ,BECKLEY,WJ":X=1:RETURN

PRINT"WR8HC0.34/94,350 ";DI;" ,CHARLESTON,WJ:X=1:RETURN

PRINT"WR8HCF.28/86,76 ";DI;" ,ROHNOKE.WT:X=1:RETURN

PRINT"HR4HCF.28/86,76 ";DI;" ,ROHNOKE.WT:X=1:RETURN

FRINT"HR4HCF.28/86,76 ";DI;" ,ROHNOKE.WT:X=1:RETURN

FRINT"HR4HCF.28/86,70 (]] ,ROHNOKE.WT:X=1:RETURN

FRIN
          199
        201
202
280
282
284
        237
                                         CLS
PRINT"JUST ENTER CALL SIGH AND COMFUTER WILL LET"
PRINT"YOU NADW IF IT IS A DUPLICATE."
PRINTPRINT
INFUT"STATION (INFUT 'S' TO STOP):";AN
            302
        304
            386-
1.00
                                      INFUT*STATION (INFUT 'S' TO STOP):";AN

IFFA="S"GOTO28

LETX:0

X:X+1

IFC4(X)="THEN322

IFC4(X)=AITHEN322

IFC4(X)=AITHEN325

GOTO314

PRINT:PRINT"HAT IS A NEW ONE -- CALL IT"

PRINT:PRINT"HAT IS A NEW ONE -- CALL IT"

COSURIDORS
        310
        312
314
316
          318
            320
        322
                                           G05UB10005
IFKB=89G0T0332
IFKB<)78G0T0326
IFKB=73G0T0306
          327
          328
330
                                           LETCICO-AS
                                           GOTO306
PRINT"ALREADY WORKED HIM --"
GOTO306
          334
            377
            87.7
            478
                                         CLS:INPUT"Q - SIGNAL (ENTER 'S' TO STOP):":Q$
IFQ8="S"GOTO28
          500
502
504
          502 IF QF=151001028
504 X=0
506 RESTORE
506 RESTORE
508 FORJ=11024
510 RERDAS
512 IF HS=1END*G0T0550
514 IF HS=010G0T0520
               516 NEXTI
                                               TEX10
TEX30THEN552
            518 1FX2014EN552
520 0N1050UB525 526,527,528,529,530,531,532,533,534,535,536,537,538,539,
540,541,542,543,544,545,546,547;6010518
525 PRINT*0RL: ARE YOU BUSY?:X=1:RETURN
526 PRINT*0RH: ARE YOU BUSY?:X=1:RETURN
```

527 PRINT"ORN: 15 THERE STATIC?":X=1:RETURN
528 PRINT"ORD: SHALL I LICKERSE POWER?":X=1:RETURN
529 PRINT"ORD: SHALL I DECKERSE POWER?":X=1:RETURN
530 PRINT"ORD: SHALL I SEND FRSTER?":X=1:RETURN
531 PRINT"ORD: SHALL I SEND SKOME?":X=1:RETURN
532 PRINT"ORD: SHALL I SEND SKOME?":X=1:RETURN
533 PRINT"ORD: HOVE VOU HANTTHING FOR HE?":X=1:RETURN
534 PRINT"ORD: HOVE VOU HANTTHING FOR HE?":X=1:RETURN
535 PRINT"ORD: HOVE VOU HANTTHING FOR HE?":X=1:RETURN
536 PRINT"ORD: HOVE VOU HANTTHING FOR HE?":X=1:RETURN
537 PRINT"ORD: HOVE VOU HANTTHING FOR HE?":X=1:RETURN
538 PRINT"ORD: HOVE VOU HANTTHING FOR HE?":X=1:RETURN
539 PRINT"ORD: HOVE VOU HANTTHING FOR HE?":X=1:RETURN
539 PRINT"OSE: HOV DU HANDE SERGE/IN?":X=1:RETURN
549 PRINT"OSE: HOVE VOU HOVE SERGE/IN?":X=1:RETURN
541 PRINT"OSE: HOVE VOU HOVE SERGE DO VO'S?":X=1:RETURN
542 PRINT"OSE: SHALL I SEND A SERGES DO VUN'?":X=1:RETURN
543 PRINT"OSE: SHALL I CHARGE FREQUENCY":X=1:RETURN
544 PRINT"OSE: SHALL I SEND A SERGES DO VUN HAVE?":X=1:RETURN
545 PRINT"OSE: SHALL I SEND A SERGES DO VUN HAVE?":X=1:RETURN
546 PRINT"OSE: SHALL I CHARGE FREQUENCY":X=1:RETURN
547 PRINT"OSE: SHALL I CHARGE FREQUENCY":X=1:RETURN
548 PRINT"OSE: SHALL I CHARGE FREQUENCY":X=1:RETURN
549 PRINT"OSE: SHALL I SEND A SERGES DO VO HAVE?":X=1:RETURN
549 PRINT"OSE: SHALL I CHARGE FREQUENCY":X=1:RETURN
549 PRINT"OSE: SHALL I CHARGE FREQUENCY":X=1:RETURN
540 PRINT"OSE: SHALL I CHARGES DO VO HAVE?":X=1:RETURN
541 PRINT"OSE: SHALL I CHARGE FREQUENCY":X=1:RETURN
544 PRINT"OSE: SHALL I CHARGE FREQUENCY":X=1:RETURN
545 PRINT"OTE: HOUNHARY IS VUN LOCATION?":X=1:RETURN
546 PRINT"OTE: HOUNHER ONE (V/N)?"
550 PRINT:PRINTMANTHER ONE IS NOT ON FILE"
550 PRINT:PRINTMANTHER ONE (V/N)?"
551 PRINT=PRINT"OSEO (EL) LIBERIA" (XE) MEXICO" (YN) NICREAGUA" (HP) PARABUAY" (2P) PARABUAY" (2P) PARABUAY" (2P) PARABUAY" (3P) PERU" (SY) UENEZUELA" 938 GOT0911 940 LETOS=1NKEV4 942 [FG3="R\*GOT0906 944 [FG1="S\*GOT028 956 PRI-HT4832," 952 PRI-HT4832," 954 DF0146 954 QF0146 954 QF0146 ": FORX=1T0200: NEXTX 
 952
 PRINTRES2.\*\*
 \*\*\*PURCET10286\*\*\*

 1108
 CLS\*PRINT\*CLASS\_OF\_LICENSE\*\*
 1102

 1102
 PRINT\*CLASS\_OF\_LICENSE\*\*
 1102

 1104
 PRINT\*CLESS\_OF\_LICENSE\*\*
 1104

 1104
 PRINT\*CSEURATCE\*\*
 1104

 1106
 PRINT\*CSEURATCE\*\*
 1104

 1108
 PRINT\*CSEURATE
 CONDITIONAL>\*

 1119
 PRINT\*CSEURATE
 CONDITIONAL>\*

 1114
 PRINT\*CSEURATE
 CONDITIONAL>\*

 1119
 GOSUBIO005
 CONDITIONAL>\*

 1121
 IFKB=7800KKB=8400KB=710FKB=6500KG
 CONDITIONAL>\*

 1121
 IFKB=780KKB
 CONDITIONAL>\*

 1121
 IFKB=780KKB
 CONDITIONAL>\*

 1122
 IFKB=780KKB
 CONDITIONAL\*

 1124
 CLS\*PRINT\*\*
 1124 CLS:PRINT"BANDS OF OPERATION" 1126 PRINTSTRING\$(55, "=");

mation program. When the user responds with the last three letters of the repeater's callsign, its frequency pair (e.g., 13/73), or the city where it is located, the computer will display pertinent information concerning that repeater. One helpful bit of data provided is the proper beam heading for that repeater. Lines 120 through 197 and 200 to 279 are reserved for the user to insert information pertaining to his favorite repeaters. I have put data in these lines just to provide formatting examples.

Contest Logger: This routine is the answer to the contester's prayers. It resides from lines 300 to 338. It will ask for the callsign of the station, check memory, and, if not already logged, will tell the operator that it is a new contact and to call it. If contact is made, the call can be saved in memory for recall later. If the station was previously logged, the user will be informed so that a different station can be checked. Searching action is completed in seconds-a lot easier than trying to find a callsign in a stack of dupe sheets! Statement line 11 is initialized for 100 contacts. This can be adjusted if desired.

Q-Signals: How many times have you heard a Q-signal used and tried to remember its meaning? Statement lines 500 through 603 provide instant recall. The user enters his own catalog of Q-signals into DATA statements beginning on line 600. I have already inserted 23 signals. These can be altered to suit individual needs. The only program modification required is changing the DATA statements and lines 525 through 547 to support the changes made. Be sure the last DATA element is "END".

Third-Party Agreements: This program will display the list of countries with which the United States has third-party agreements. Statement lines 700 to 732 support this function. The list includes call letter prefixes. If the country is not listed, do not make that phone patch!

Station Identification: The operator can initiate this program when the QSO

1128 PRINT 1130 PRINT"1. 3.5 (30M) 1132 PRINT"2. 7.0 (40M) 1134 PRINT"3. 14.0 (20M) 1136 PRINT"4. 21.0 (15M) 1136 PRINT 5. 28.0 (10M)" 6. 50.0 (6M)" 7. 144.0 (2M)" 1424 1FF>21.251H4DFF=21.4560T01560 1420 1FF>28.66H0FK=25.5060T01440 1420 IFF>28.51H4FK=29.7060T01440 1420 IFF>=58.66H0FK<29.7060T01440 1420 IFF>=58.1H4FK<54.6660T01500 1431 IFF>=144.66H0FF=144.1660T01446 1430 IFF>=144.11H0FK=148.6660T01566 1438 G0T01178 1440 IFF=60T0ENPENT\*ETTER GET BRCK IN THE PHONE BRND\*:G0T01182 1440 IFF=60T0ENPENT\*ETTER GET BRCK IN THE PHONE BRND\*:G0T01182 1140 PR1NT 1142 PRINT"WHICH BAND ARE YOU OPERATING ON?" 1144 GOSUB10000:IFURL(KB\$)(IORVAL(KB\$))7GOTO1144 1144 GOSUBIGBOB: FUEL VOU CHE VOU CHEATING UN: 1144 GOSUBIGBOB: FUEL (KB3)>/COUNT 1442 GOT01500 1500 ONEGOTO1510, 1550, 1570, 1590, 1600, 1610, 1620 1510 GOSUB1700 1512 X=255:A=3,5:H=3,6:M=3,7:D=3,8:E=3,9:G=4,0:J=127 1514 PRINTeX,A:PRINTeX+10,H:PRINTeX+20,H:PRINTeX+30,D:PRINTeX+40,E:PRINTeX+50, 1514 PRINTeX.A: FRINTEX.+10.H: PRINTEX.+20.H: PRINTEX.+30.D: F G 1515 X=832 1516 GUT01900 1556 GUSUB700 1552 X=835:A=7.0:H=7.1:M=7.2:D=7.3:J=127 1554 PRINTEX.A: PRINTEX.+10.H: PRINTEX.+20.H: PRINTEX.+30.D 1555 IFF)=FRINTEX.+10.H: PRINTEX.+20.H: PRINTEX.+30.D 1556 IFF)=FRINTEX.+10.H: PRINTEX.+20.GUSUB1800:GUT01182 1558 IFF)=FRINTEX.+10.H: PRINTEX.+20.GUSUB1800:GUT01182 1550 IFF)=FRINTEX.+10.H: PRINTEX.+20.GUSUB1800:GUT01182 1550 IFF)=FRINTEX.+10.H: PRINTEX.+20.GUSUB1800:GUT01182 1551 IFF)=FRINTEX.+10.H: PRINTEX.+20.GUSUB1800:GUT01182 1572 X=835:R=14.0:H=14.1: M=14.2:D=14.3:E=14.35:J=127 1166 INPUT"FREQUENCY (1.E., 14.320";F 1169 IFC-#S6001328 1170 IFC-#8400T01328 1172 IFC-#160T01338 1174 IFC-#5600T01378 1176 LFTX-HT(FRNC5)) 1188 0N2005UB1190-1192.1194,1196,1190 1182 PRINT:PRINT"D0 YOU WISH A NEW FREQUENCY CHECK (Y/N)?" 1194 GYSUE16085 1972 X=833;Am14.0;H=14.1;M=14.2;D=14.3;E=14.3;J=127 1572 X=833;Am14.0;H=14.1;M=14.2;D=14.3;E=14.35;J=127 1574 PRINT@(.A:PRINT@K+10.H:PRINT@K+20.M:PRINT@X+40.E 1014 FRINTEN. H. FRINTEN DE HERRING 2010 FRINTEN 30,00 FRINTEN 30,00 1575 (2010206) 1576 (2010206) 1596 (20102076) 1596 (20102076) 1591 FRINTEN, FRINTEN 10, HERRINTEN 20, HERRINTEN 30, DERINTEN 40, EERRINTEN 50, 1184 G05UE10605 1186 IFKB=89G0T01124 1188 IFKB<>73G0T01124 1189 IFKB=73G0T028 

 1184
 GrSuB10005

 1185
 [FKBK->7500701124

 1185
 [FKBK->75007028

 1190
 [FKBK->75007028

 1191
 [FKBK->75007028

 1192
 [FKBK->75007028

 1192
 [FKBK->75007028

 1194
 [FKBK->75007028

 1195
 [FKBK->75007028

 1196
 [FKBK->75007028

 1197
 [FKBK->75007048

 1198
 [FKBK->75007028

 1199
 [FKBK->75007048

 1190
 [FKBK->75007048

 1191
 [FKBK->75007048

 1192
 [FKBK->75007048

 1194
 [FFF=58]

 1195
 [FFF=58]

 1196
 [FFF=58]

 1197
 [FFF=58]

 1198
 1595 X=814 1596 60101900 1600 605181700 1662\_X=8517.4=28\_0+H=26\_5+M=29\_0+D=29\_5+E=29\_7+J=127 1664\_PRINT#X/A+PRINT#X+10\_H=PRINT#X+20\_H=PRINT#X+30\_D=PRINT#X+40\_E 1405 1605 X=607 1606 G0702006 1610 G02U017060 1612 X=235: H=50.0: H=51.0: H=52.0: D=53.0: E=54.0: J=127 1614 PRINTMC, A: FRINTMC+16, H: PRINTMC+20, H: PRINTMC+30, D: PRINTMC+40, E 1615 X=765 1616 G0702000 1620 G03U01706 1620 X=635: H=144.0: H=145, 0: H=146, 0: D=147, 0: E=148, 0: J=127 1624 PRINTMC+0: PRINTMC+10, H: PRINTMC+20, H: PRINTMC+30, D: PRINTMC+40, E 1625 X=691 1625 X=691 1626 60T02000 1760 CLS: V=36 1762 F65X=16T0110 1764 SET(X,Y) 1766 NEXTX 1766 Y=37 1706 MEXTX 1700 Y=37 1710 SET(10./V) 1712 SET(50./V) 1714 SET(50./V) 1716 SET(70./V) 1718 SET(50./V) 1720 SET(110./V) 1720 SET(110./V) 1720 SET(110./V) 1720 RETURN 1800 PRINT\*(X\*V\*2)-J," U"; 1800 PRINT\*(X\*V\*2)-J," U"; 1810 LETOS=INKEV\* 1812 IFOS="C"RETURN 1812 IFOS="C"RETURN 1810 LETOS=INKEV\* 1810 LETOS=INKEV\* 1810 LETOS=NKEV\* 1980 IFF>=HRNDF<HTHENZ=(F-A>+A: Y=0: G05UB1880: G0T01182 2100 CL3:PM:INTCHR01233 2102 PR:INT4448."7 3 8 G 0 0 D D X ! !" 2104 FORX=1T01660:NEXTX 2106 CL3:END 10000 KB=INKEV4:1FKB4=""GOT016060 10001 LETX=VML(KB3):RETURN 10005 KB=INKEV4:1FKB4=""GOT016665 10015 KB=ASC(KB4):RETURN 1402 G0101566 1412 G0101566 1418 IFF>=3.566H6F<=3.775G0101440 1412 IFF>=3.7766H6F<=4.606UT01566 1414 IFF>=7.064H6F<=7.15G0101440 1416 IFF>=7.166H6F<=7.36G0101566

(where's that Q-signal program!) begins. A visual timer will be displayed, updated each minute, and provide a flashing reminder when the time limit has expired and station identification must be made. When the ID has been made, the time can be reset and the sequence repeated. Reset can occur any time by hitting the "R" key. Hitting "S" returns the program to the menu of commands. This IDer routine is in statement lines 900 to 954. The timing sequence is software controlled (FOR ... NEXT loop)

and may have to be adjusted to allow for differences in machines. Line 914 controls this timing.

Frequency Check: The largest and most complex subprogram, it resides from lines 1100 to 2007. Don't let that scare you, though. If you answer all prompts and data requests when required, the computer will provide the proper response. The program is designed to give the operator the security of knowing his operation is within the band limits established for his license. This verification is supported as the program is run and then reinforced by graphically displaying the operating frequency.

The frequency program can be customized for specific requirements. For example, if you always intend to remain a General, eliminate lines 1102 through 1121 and change lines 1100 and 1122 to read:

#### 1100 CLS 1122 LET C = 71

This eliminates answering the class of license question each time the program is run. If your operation is confined to one band, make variable B at line 1146 the applicable value. Also, if you never use CW, make M=80 at line 1160 to establish phone-only operation (also delete lines 1156 and 1157).

As previously stated, this is a highly versatile and useful program, either piecemeal or in its entirety. I believe it contains some routines which every ham will find helpful. I hope it will take some of the paperwork out of your operation and give you more time to rag-chew!

## **Berserk Direction-Finding**

Zero in on transmitters in seconds with this TRS-80 program. It will tell you how to get there, too.

n any radio direction finding operation, whether it be tracking a jammer or a distress signal, the time factor is important. The Radio Amateur RDF Assistant minimizes the time involved in tracking a transmitter. The program allows the operator to determine the general location of the transmitter instantly by entering the headings to the transmitter from two stations whose locations are known. The advantages of this method over the standard map, protractor, and straightedge approach are speed and accuracy. The high speed of the operation allows for comparison of headings from different stations and for quick, repeated calculations if the transmitter is moving.

Other features of the program include the giving of directions to the transmitter for field units and providing a listing of the DF committee members and repeater users, with their calls, phone numbers, and distances and directions to the transmitter, allowing the RDF net control to coordinate the efforts of the stations in reaching the transmitter site. The data for this listing is stored on tape, so the user may have different tapes for different repeaters or bands.

#### Instructions

After you have CLOADed the program and entered RUN, the computer will ask vou if you want the data tape loaded before continuing with the program. You would normally do this when stations will not be giving you bearings immediately, such as right after a jammer or ELT has appeared on frequency. If you need to determine the transmitter's location immediately and have the appropriate information, enter N and the program will continue. You may load the tape later if needed by selecting that option from the menu.

Next, the computer will ask you for the coordinates of station A. Type in the horizontal coordinate, a comma, and the vertical coordinate of the first station that you will be taking a bearing from. (This information can be found by preparing an RDF Map and a Station Data Sheet described later.) Press ENTER and the computer will then ask you the bearing that that station has on the transmitter. Type in this and press ENTER. Repeat the procedure for station B, using a second station. It should be noted that you should not enter two stations that have the same bearings or whose bearings have a difference of 180°. This will result in a divideby-zero error. This situation is rare and even if the computer were not used the results would be meaningless. The user should simply select another station to replace one of these.

Once this has been done, the transmitter's location is printed along with directions and distances from stations A and B to the transmitter. To see the list of options available, press ENTER.

The first option is DF-Fix Calculations, which was just described. You would select this option if you want to enter a new set of headings to the transmitter. This is the only option that affects the transmitter's location. The other options only use this data to provide related information.

The second option provides directions to the transmitter for a field unit. The computer will ask you for the coordinates of the



95

field unit. Enter these coordinates. The coordinates can be found by finding the field unit on the RDF Map and finding its corresponding coordinates. The computer will then display the transmitter's location and the distance and directions to the transmitter from the field unit. This information is presented in two forms to allow for different types of field units. If the field unit is a car restricted to streets, the north/south and east/ west directions are more appropriate. On the other hand, if the field unit is on foot or in open country, distance and bearing information is more relevant.

The third option is the DF-Net Listing. To use this option, you must have loaded the data tape in or inserted new data (option 5.2) during the current run of the program. The computer will first ask you for a maximum report range. The computer will list only those stations which are within the number of miles you entered to the transmitter. The computer will then ask if you want only DF committee members (those with asterisks at the front of their calls) to be listed. Enter either Y or N. The computer will then list the stations on the screen. It will only show eleven stations at one time, so merely press ENTER to see the next set of eleven. After the computer has listed all of the stations that have met the given requirements, it will tell how many stations were within the given range. You must press ENTER to see the list of options.

The fourth option is to load the data tape. The computer will guide you through the process of loading the tape. The menu will be displayed after the tape has been loaded.

The fifth option allows you to modify the data tape of the DF-Net stations (callsign, phone number, and lo-

4 REM RADIO AMATEUR RDF ASSISTANT 5 REM PROGRAM BY EDWARD W. CRANDELL 6 REM RT 8 BOX 79 7 REM WARSAW, IN 46580 7 REM 10 CLEAR5000 10 CLEAR3000 11 M-100 12 DIM DK(M):E:(M):X(M):Y(M) 15 CLS:PRINT RADIO AMATEUR ROF ASSISTANT\*:PRINT 28 INPUTO YOU HANT TO LOAD THE DATA TAPE NOW (Y OR N)\*:G0:CLS 21 IF G:="Y"THEN GOSUB240 39 REM DF-FIX CALCULATIONS 40 CLS:PRINT\*STATION A\*:INPUT\*COORDINATES\*:A+B 45 INPUT\*BARING\*:ERINT 50 PRINT\*STATION B\*:INPUT\*COORDINATES\*:A+B 45 INPUT\*BARING\*:ERINT 75 G=A30-C:F=450-F 90 G=TAN(C-13.14159/100)IF=TAN(F-3.14159/100) 120 G=(F\*-D+0E=-(C+A))/(F-C):H=C\*(G-A)+B 120 G=15.14159/100) 90 GTANICS 1.14159/18011F=TANIF.3.14159/1801 180 Get(F):0F8F=C(CA)1/FFC:1HCA)1/FFC:1HCA)1/FFC:1HCA) 180 GetNT(G-10.51/10:H=INT(H+10+.57/10 110 X=A:Y=0:GOSUE.3000:CLSIPENTH'TERNSHITTER'S COORDINATES: \*1G\*.\*H 111 PRINT:PRINT'DISTANCE FROM STATION A:\*1U\*HILES':GOSUB1900 113 X=01Y=CLS:GOSUE.3000:TRINT'DISTANCE FROM STATION B:\*1U\*HILES':GOSUB1900:INPUT\*PRESS ENTER TO CONTINUE\*:P:CLS:GOT0300 140 REM FIELD UNIT ROUTINE 145 INPUT\*FIELD UNIT'S COORDINATES: 'I.\*' 150 PRINT'TRANSHITTER'S COORDINATES: 'I.\*' 150 PRINT'TRANSHITTER'S COORDINATES: 'I.\*' 150 PRINT'TRANSHITTER': COORDINATES: 'I.\*' 160 REM DF-NET LISTING 161 IFFF-0THENPRINT'\*\*\*DATA TAPE HAS NOT BEEN LOADED\*\*\*\*:PRINT\*PLEASE LOAD DATA TAPE OR SELECT ANDTHER OPTION\*ELSE105 182 GOT0300 182 GOTOJ00 185 INPUT\*MAIHUM REPORT RANGE\*1. 196 INPUT\*MAIHUM REPORT RANGE\*1. 198 INPUT\*MAIHUM REPORT RANGE\*1. 198 INPUT\*DE-COMMITTEE MEMERES ONLY\*IME 191 R=0:V=0:RN=1 195 CALL PHONE # DISTANCE BEARING 196 IFRN:TRIEN230 206 SN=RM\*1 DIRECTIONS\* PRINT RN=RN+1 TEASC(H)1<-R9THENGOSUB2000:60T0220 210 IPASC(H)) = 0911ENG650E20003:0010:220 215 IF ASC(D) = 421FENG605E20002:ES224 220 IPU(=LTHENPENINT:D:ITAE(9):E:ITAE(0):U:ITAE(3)):IZITAE(3):STATTAE(52)T:B\*ELSE224 221 REME:IVM-VI:IFVCUTHEN24 222 RENT:INPUTPRESS ENTER TO CONTINUE\*:P:V=0 223 GOT0:95 224 GOT0:95 230 PRINT:PRINTR:\*STATIONS WITHIN\*L\*HILES OF TRANSMITTER\*:INPUT\*PRESS ENTER TO CONTINUE\*:P:CLS:GOT0:300 230 GOSUB240:0010300 230 GOSUB240:0010300 230 PRINT:PRINTR:\*STATIONS WITHIN\*L\*HILES OF TRANSMITTER\*:INPUT\*PRESS ENTER TO CONTINUE\*:P:CLS:GOT0:300 239 GOSUBE240 GOTOJ00 240 REN DATA INPUT ROUTINE 241 PRINT-INSERT DATA TAPE ::PRINT-PRESS PLAY-:PRINT\*PRESS ENTER WHEN READY TO LOAD :INPUTP 242 RNN-INSERT DATA TAPE ::PRINT-FILE LOADING\* 243 INPUTF -IDS(RN)=SE(RN)-XE(RN)-XE(RN)-YE(RN) 244 INFT-IDS(RN)=SE(RN)-XE(RN)-XE(RN)-YE(RN) 245 IRF D4(RN)=FEND\*THEN240 247 RNN=RN-I:GRTOVA 250 REM MODIFY DATA TAPE 252 PRINT\*1) LIST RECORDS\*:PRINT\*2) [NSERT RECORD\*:PRINT\*3] DELETE RECORD\*:PRINT\*4) WRITE DATA TAPE\*:PRINT\*5; RETURN TO MAIN PROGRAM \*:PRINT 253 INPUT:ENTER SELECTION\*:01:CLS 254 ON 01 GOT0256-263-277:283-300 255 GOT0252 23% ION BI GOIDGREAD.27/1083.000 25% FOR RE:IOTR 25% PRINTERNI'''DU(RN)!'''LEK(RN)!'''LEK(RN)!'''Y(RN) 25% PRINTERNI'''DU(RN)!'''LEK(RN)!'''Y(RN) 25% PRINTERNI'''DU(RN)ENTER TO CONTINUE''IF:LLS:V=0 26% INFUT:IFV.IATERNAT 26% INFUT:IFV.IATERNAT 26% INFUT:ENTER STATION'S COUNDINATES'IX:Y 27% INFUT:ENTER STATION'S ELEPTERS 27% INFUT:ENTER STATION'S ELEPTERS 27% INFUT:ENTER STATION'S ELEPTERS 27% INFUT:HICLSIGOTOS2 27% 276 TRATEFICLSIGGT0:252 277 INPUT-WHICH RECORD NUMBER SHOULD BE DELETED:1DR 278 IF DR:HT THER.200 DT 279 PRINT-RECORD NOT FOUND::GOT0:277 200 PR:FR=CDF:JITO TR 201 NN:FR=TDL(NI)DEL(FR):EG(IN)=EG(FR):X(NN)=X(FR):Y(NN)=Y(FR):NELTER 202 TRATEFILCLS:GOT0:252 203 RN:11:LR=0 204 PRINT:INSERT DATA CASSETTE IN RECORDER AND PRESS PLAY AND RECORD::PRINT=PRESS ENTER\* 201 NN=FR-1:D1(NN)=D1(FR):E(NN)=E(FR):K(NN)=K(FR):K(NN)=Y(FR):NE\TFR 202 Th=T1:LLS:GOTO222 203 RN=1:LR=0 204 PRINT=ILCLS:GOTO222 205 NN=1:LR=0 204 PRINT=ILCLS:GOTO222 205 NN=1:LR=0 206 PRINT=INSERT DATA CASSETTE IN RECORDER AND PRESS PLAY AND RECORD\*:PRINT\*PRESS ENTER\* 205 PRINT=1.DE(NN)=E(RN),K(RN)+Y(RN):NEXTRN 206 PRINT=1.TEND\*:END\*:0=.0 207 PRINT=1.TEND\*:END\*:0=.0 208 PRINT=1:TEND\*:END\*:0=.0 209 PRINT=1:TEND\*:END\*:0=.0 209 PRINT=1:TEND\*:END\*:0=.0 200 PRINT=1:TEND\*:END\*:0=.0 200 PRINT=1:D\*FILE UNIT CALCULATIONS\* 200 PRINT=1:NPUTFENTER SELECTION\*:0:LGS 200 PRINT=1:D\*FILE UNIT CALCULATIONS\* 200 PRINT=1:NPUTFENTER SELECTION\*:0:LGS 200 PRINT=0:D\*FRENTER 200 SGGT:TEM=Y 200 SGGTT:TEM=

#### Program listing.

cation). How to determine the station's location will be discussed later. This option has five options of its own. The first merely lists the data. This allows you to check the data and see what, if anything, needs to be changed. The number displayed on the extreme left is a record number. This is the record number you will use in options 2 and 3. Before using options 2 and 3, it is a good idea to check the listing to make sure that you select the right number. To insert a new record, first determine after which record you would like the new record inserted. If it is the first record to be inserted, insert it after Ø.

The third option is the

delete option. If you have a station which is no longer active or needs to be deleted for some other reason, find it on the listing (option 1) and note its record number. Then select option 3. Enter this number in response to the computer's question about which record number should be deleted. If you choose to de-

### WORLD TIME WATCH the first microprocessor watch made especially for hams 24 hr. timer

24 hr. timer microprocessor water resistant

solar assist

New Low Price -\$59.95

The HAM-1 functions include local time, world time, (G.M.T. too) count-up and count down chronometer, day, month, date, alarm and hourly chime. It's ideal for log-keeping, DX time conversion and 10 minute I.D. timing. The HAM-1 features a high contrast Seiko display and solar cell battery assist. Battery life is better than 4 years. The HAM-1 is water resistant to 20 meters, the case is 100% solid stainless steel and the crystal is scratch resistant mineral glass. The HAM-1 1 is rugged and durable and has a 1 year warranty.

#### 2 METER AMPLIFIER \$39.95



• 2 Watts In, 10 Watts Out • V.S.W.R. Protected • Can be Used for F.M. & S.S. B. • Led Status Indicators • Low Loss SO-239 Connectors • Current Drain Less Than 2.5A at 13.6 V.D.C. • Massive Heatsink • Built In T/R Switch

#### TEMPO S-1 UPGRADE KITS \$39.95

Upgrade your early Tempo S-1 to current Production Specifications, kits include: •450 M.A.H. Battery Pack • New Case Assembly • All New Escutcheons • Spkr./Mic. Jack •/Dust Cap • New Earphone & Jack • P.C.B. and Parts for Easy Installation • Detailed Instruction Manual • For Radios With & Without T.T. Pad.

Other Accessories Available:

Spkr/Mic. Designed for	S-	11	s.		\$24.95	
Heavy Duty Belt Clip.					7.50	
Flex Antenna					6.00	
To Order Call or Write	fo	:				

ADVANCED COMMUNICATIONS INTERNATIONAL 2411 Lincoln Avenue Belmont, CA. 94002 U.S.A. (415) 595-3949

Add \$3.00 per order for shipping & handling. California residents add 6% sales tax. Visa, Master Charge accepted.

## WHY COMPRO-MISE

Others claim more gain for their antennas than the IsoPole<sup>™</sup> antennas, but none can beat the IsoPole for HONEST on-the-horizon omni-directional gain unless you are willing to spend at least THREE TIMES AS MUCH!!! The IsoPole is easiest of ALL competitive models to assemble, has a weather protected, factorytuned matching network, (no more aggravating SWR variations with weather changes), uses all stainless steel hardware, and is designed to withstand severe icing and wind conditions. The IsoPole antenna is UPS shippable without the standard 10 foot 11/4 inch TV mast. You can buy the mast from your local ham dealer, hardware store, or Radio Shack<sup>™</sup> store for less than the shipping costs of a single mast. When good strong, low cost 10 foot sections of mast are so easily available, why compromise by using several shorter pieces that have to be joined together?

For more details, please write for our latest catalog or visit your favorite dealer.

Prices and Specifications subject to change without notice or obligation.

ADVANCED ELECTRONIC APPLICATIONS, INC. -2 P.O. Box C-2160, Lynnwood, WA 98036 (206) 775-7373 Telex: 152571 AEA INTL





New MFJ VHF converter turns your synthesized scanning 2 meter handheld Into a hot Police/Fire/Weather band scanner.

144-148 MHz handhelds receive Police/Fire on 154-158 MHz with direct frequency readout. Hear NOAA weather, maritime coastal plus more on 160-164 MHz.

Mounts between handheld and rubber ducky. Feedthru allows simultaneous scanning of both 2 meters and Police/Fire bands. No missed calls.

Highpass input filter and 2.5 GHz transistor gives excellent uniform sensitivity over both bands. Crystal controlled.

Bypass/OFF switch allows transmitting. Won't burn out if you transmit (up to 5 watts) with converter on. Low insertion SWR. Uses AAA battery.  $2\frac{4}{x1\frac{1}{x}x1\frac{1}{x}}$  in. BNC connectors.

Enjoy scanning, memory, digital readout, etc. as provided by your handheld on Police/Fire band.

#### 220 MHz Converter for 2 M Handheld



MFJ-314, like MFJ-313 but lets you receive 221-225 MHz on your 2 meter handheld.

Police/Fire/Weather Band Converter for 2 Meter Mobile Rigs.



MFJ-312, like MFJ-313 but for mobile 2 meter rigs. Transmit up to 40 watts thru converter without damage. SO-239 connectors. Mobile mounting brackets. Rugged. "ON" LED. Use 12 VDC or AAA battery. 3x4x1 in.

Order from MFJ and try it-no obligation. If not delighted, return it within 30 days for refund (less shipping). <u>One year unconditional</u> guarantee.

Order today. Call toll free 800-647-1800. Charge VISA, MC or mail check, money order for amount indicated plus \$4,00 each shipping. Hear police/fire/weather. Order now. 47



lete a record number that does not exist, the computer will print RECORD NOT FOUND and ask you for the record number to be deleted again. If a record has some incorrect information on it, you must insert the complete correct record and then delete the incorrect one.

The fourth option will write a new data tape with all of the new changes or duplicate the old data tape if it has been loaded in and no changes have been made. To use this option, place the tape you want to put the data on in the recorder. Press the Play and Record buttons on the recorder and then press EN-TER on the computer. After the data tape has been written, the computer will return to the main program and display the menu.

The fifth option simply returns you to the main program and displays the menu. You would select this in case you did not want to write a new tape or did not want to write immediately after making the changes.

#### **RDF** Map


In order to use this program, you must prepare a

map with a coordinate system on it. First obtain a map of the coverage area. This map should have an appropriate scale for RDF use, that is, it should not be so small that one inch equals twenty miles. After the map has been obtained, you should determine what length on the map corresponds to a distance of one mile; for example, 0.5 inch=1 mile. Then, starting in the left-hand corner, you should make a mark every mile along the bottom edge of the map (see Fig. 1). Do the same along the top edge, starting in the upper left-hand corner. Repeat this procedure for the sides, starting in the lower leftand right-hand corners. Next, label them, starting with Ø and going from left to right and bottom to top. The markings on the side of your map should be similar to those in Fig. 1 (different scales and more numbers of course).

After you have prepared the map, you are ready to prepare the DF-Net station data sheet (see Fig. 2). Fill in the call and phone number columns with appropriate information. The first coordinate is the number on the top or bottom of the map which corresponds to the horizontal position of the station. The second coordinate is the number on the sides of the map which corresponds to the vertical position of the station. This sheet is sufficient for using options 1 and 2 of the program.

As has been stated before, in order to use the DF-Net Listing option, you must have previously inserted stations onto the data tape using option 5.2. The option will guide you through the procedure, but a few things should be mentioned before you use the option. First, answer all of the questions the computer asks about the station. Do not leave any answer blank. If a radio direction finding station does not have a call, (e.g., a future ham or SWL), type his name (if it is six or less letters) or his initials in response to the question about the station's callsign. If a station does not have a phone or his number is not known, type in NO PHONE or N/A in response to that question. If you would like a station to be included in a selective printout in the DF-Net Listing, put an asterisk in front of the station's callsign. The asterisk can be used to denote a station who is part of the DF committee or to denote those who have special RDF equipment in their cars, etc.

As well as using the program to find stations, it can be used to calibrate the members' antenna-heading indicators. To use the program for this purpose, RUN the program and load the data tape. Next, you need to insert the coordinates of the station that everyone will be aiming at. To do this, enter station A's coordinates as follows: first coordinate of station being aimed at, Ø. For the bearing, enter Ø. Enter B's coordinates as follows: Ø, the second coordinate of the station being aimed at. For the bearing, enter 90. Press EN-TER to get to the menu, and select the DF-Net Listing option. Answer the questions as you normally would. The number in the bearing column of the listing is the direction that each station's heading indicator should show. This information should be relayed to each station so that he can either correct his indicator or make a note of the error and correct for it when he is tracking a station. A good station to calibrate on would be the repeater.

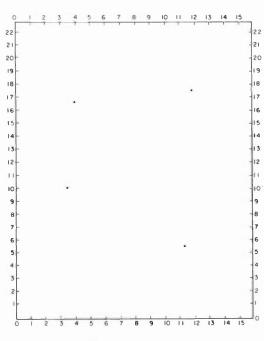



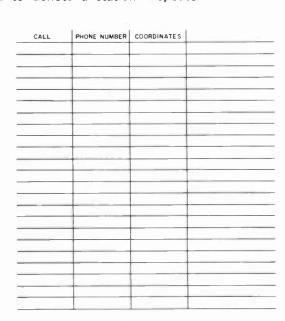


Fig. 2. DF-Net station data sheet.

## **DO ANTENNAS WORRY YOU?**

We feel a novice student has enough to learn without immediately diving into antenna construction. Our new novice antenna is fully assembled and covers all the novice bands and beyond. One of its better features is the price. (At last glance the competition wanted \$123.50 for their fully assembled antenna with coax fitting that covers the four novice/tech bands.)



#### FEATURES:

- 118 feet long
- Heavy Copperweld<sup>®</sup> construction
- 100 feet of 450# test Nylon rope included
- Waterproof center connector with female coax fitting

(NOT TO SCALE)

- No antenna tuner needed
- 2 KW PEP input rated (750 W on 21 mHz)
- Retunable when you upgrade
- Installs as low as 25 feet
  - Average Bandwidths for 2:1 VSWR:
- 80 meters = 200 KHz plus
- 40 meters = 125 KHz
- 15 meters = 600 KHz plus
- 10 meters = 700 KHz plus

ALL PRICES ARE UPS PAID CONTINENTAL USA

Available at your favorite dealer or order direct from: **Van Gorden Engineering** P.O. Box 21305 • South Euclid, Ohio 44121

Dealer Inquiries Invited



Organize your shack with a CLUTTERFREE MODULAR CONSOLE \$203.35

- Large, 42" H x 57" W x 29"D
- Strong groove-construction
- Mar-resistant wood grain finish
- Options, drawers & face plate
- For ham or home computer
- Visa and Master Charge

### CLUTTERFREE MODULAR CONSOLES

**MFJ/Bencher Keyer Combo** 

Deluxe MFJ Keyer fits on Bencher Paddle. Curtis 8044 IC. lambic. Adjustable weight, tone, volume, speed. Semi and automatic modes. Solid state keying. RF proof.



MFJ-422 Combo



The best of all CW worlds - a deluxe MFJ Keyer in a compact configuration that fits right on the Bencher iambic paddle! You can buy the combination or just the keyer for your Bencher.

New MFJ Keyer—small in size, big in features. Curtis 8044 IC, adjustable weight and tone, front pa iel volume and speed controls (8-50 wpm). Built-in dot-dash memories. Speaker, sldetone, and push button selection of semi-automatic/tune or automatic modes.

Ultra-reliable solid state keying: grid-block, cathode and solid state transmitters (-300 V, 10 mA max., +300 V, 100 mA max.). Fully shielded. Uses 9 V battery or 110 VAC with optional adapter, MFJ 1312, \$9.95.

Beautiful functional engineering. The keyer mounts on the paddle base to form a small  $(4 \ 1/8 \ x \ 2 \ 5/8 \ x \ 5 \ 1/2'')$  attractive combination that is a pleasure to look at and use.



MFJ-422X Keyer only



The Bencher Paddle is a best seller. Fully adjustable gold-plated sliver contacts, lucite paddles, chrome plated brass, heavy steel base with non-skid feet.

Grder from MFJ and try it - no obligation. if not delighted, return it within 30 days for refund (less shipping). One year unconditional guarantee.

Order today. Call toll free 800-647-1800. Charge VISA, MC or mail check, money order for amount indicated plus \$4.00 each shipping and handling. Enjoy CW. See dealer or call MFJ now.



You also may want to include the repeater in your DF-Net Listing so you can estimate the station's transmitter power by comparing the distance to the repeater with the signal strength into the repeater.

#### **Technical Data**

The program is divided into six subprograms (DFfix calculations, field-unit calculations, DF-Net Listing, loading the data tape, modifying the data tape, and the menu) and one major subroutine.

Statements 5 through 12 merely initialize the program. String space (5000 bytes) is set aside and the arrays are DIMensioned to a value of 100. Statements 15 through 21 give the user the option to load the data tape before he actually starts to use the program.

The DF-fix routine (lines 39 through 113) determines the location of the transmitter from the information entered by the user. This location (G,H) is used in all of the other routines for determining the transmitter's relationship to the positions of the other stations.

Statements 40 through 60 prompt the user to input the tracking station locations and beam headings. Statement 75 converts these headings from compass bearings  $(0^\circ = North, in$ creasing in a clockwise direction) to polar bearings used by the computer. Statement 90 converts these headings from degrees to radians and takes the tangent. Statement 100 solves the simultaneous equations representing the lines from the tracking stations at the given bearings. Statement 105 rounds the results of the calculations (G,H-the transmitter's coordinates) to the nearest tenth. Statement 110 passes station A's coordinates to the variables used in the calculations subroutine. The results are then printed out.

Subroutine 1900 is called to print the directions, since it is used many times. This is again done for station B in line 113. The last half of line 113 is a dummy input used to pause the program and allow the user to continue when he is ready. This is done frequently throughout the program.

The field-unit routine prompts the user to input the field-unit's coordinates, calls the calculations subroutine, and displays the results. It then jumps to the menu. This routine is straightforward in that all it does is format the input and output of the calculations subroutine.

The DF-Net Listing first checks the data flag (DF) to see if data has been loaded in (line 181). The computer then prompts the user to input different parameters for the listing (lines 185 and 190). RN is the record number and specifies which element of the array is to be read. The computer compares the record number with the total number of records (TR). When RN exceeds TR, the listing routine then summarizes the results of the listing. If the user selects the selective printout, the program then checks to see if the first character of the callsign string (D\$) is an asterisk (line 215). R is the "stations within range" counter and V is a line counter for limiting the number of stations printed on the screen at one time so that the results do not go flying off the screen before they can be read.

The data tape input routine is also straightforward. DF=1 sets the data flag. One record, D\$,E\$,X,Y, is input off the tape and stored in an array, with the subscript being incremented after each record. The computer checks D\$ for the end of file indicator, END. TR is found by taking the total number of records read (RN) and decreasing it by one to remove the end-of-

file indicator from the count.

The modify data tape routine has five options. The first option merely prints out the contents of the arrays. The second option (263 through 276) inserts a new record into the file. First, the user types the information in, then the computer moves all of the records after where the new one is to be inserted up one record number. The new record then is put in the hole left by the records moved

The delete routine merely moves all of the records above the record to be deleted down one. This destroys that record by writing over it. The program checks to make sure the user does not try to delete records that do not exist.

The fourth option (283 through 289) just outputs

D\$-Station's call

E\$-Station's telephone number

the arrays to the tape recorder, using a similar approach to the way they are read in. The fifth option is merely a jump to the menu.

The menu is straightforward, using an ON/GOTO statement to branch. Line 326. takes care of inputs that are not covered in line 325.

The calculations subroutine calculates the distance to the transmitter (lines 2001 and 2005), bearings to the transmitter, and directions to the transmitter (lines 2006-2220). The subroutine is made up of different branches used to correct the ambiguity of the ATN function.

It is hoped that this program and the presence of a good RDF committee will reduce the amount of jamming and be a valuable tool in locating emergency locator transmitters quickly.

#### Variable List

A-First coordinate of station A's location B-Second coordinate of station A's location C-Bearing to transmitter from station A D-First coordinate of station B's location E-Second coordinate of station B's location -Bearing to transmitter from station B E-G-First coordinate of transmitter's location H-Second coordinate of transmitter's location L-Maximum report range M-DIMension of arrays P-Dummy variable for pausing program Q-Menu selection R-Number of stations within given radius of transmitter S-Horizontal distance between a station and transmitter T-Vertical distance between a station and transmitter U-Distance from transmitter V-Line counter in listing X-First coordinate of station's location when using calculation subroutine Y-Second coordinate of station's location when using calculation subroutine Z-Bearing to transmitter DR-Record number to be deleted DF-Data flag FR-Former record number NN-New number of record after being renumbered NR-New record number (inserted record number) Q1-Option selection under option 5 RN-Record number TR—Total number of station records in arrays A\$-"EAST" or "WEST" B\$-"NORTH" or "SOUTH" GS-"Y" or "N" to load data tape at beginning of program H\$-"Y" or "N" to "DF-COMMITTEE MEMBERS ONLY?"



## Food for thought.

Our new Universal Tone Encoder lends its versatility to all tastes. The menu includes all CTCSS, as well as Burst Tones, Touch Tones, and Test Tones. No counter or test equipment required to set frequencyjust dial it in. While traveling, use it on your Amateur transceiver to access tone operated systems, or in your service van to check out your customers' repeaters; also, as a piece of test equipment to modulate your Service Monitor or signal generator. It can even operate off an internal nine volt battery, and is available for one day delivery, backed by our one year warranty.

- · All tones in Group A and Group B are included.
- Output level flat to within 1.5db over entire range selected.
- Separate level adjust pots and output connections for each tone Group.
- Immune to RF
- Powered by 6-30vdc, unregulated at 8 ma.
- Low impedance, low distortion, adjustable sinewave output, 5v peak-to-peak
- · Instant start-up.
- Off position for no tone output.
- · Reverse polarity protection built-in.

67.0 XZ	91.5 ZZ	118.8 2B	156.7 5A
71.9 XA	94.8 ZA	123.0 3Z	162.2 5B
74.4 WA	97.4 ZB	127.3 3A	167.9 6Z
77.0 XB	100.0 1Z	131.8 3B	173.8 6A
79.7 SP	103.5 IA	136.5 4Z	179.9 6B
82.5 YZ	107.2 1B	141.3 4A	186.2 7Z
85.4 YA	110.9 2Z	146.2 4B	192.8 7A
88.5 YB	114.8 2A	151.4 5Z	203.5 M1

• Frequency accuracy, ± .1 Hz maximum - 40°C to + 85°C

· Frequencies to 250 Hz available on special order

Continuous tone

**Group B** 

TEST-TONES:	TOUCH	-TONES:	E	URST	TONES	S:
600	697	1209	1600	1850	2150	2400
1000	770	1336	1650	1900	2200	2450
1500	852	1477	1700	1950	2250	2500
2175	941	1633	1750	2000	2300	2550
2805			1800	2100	2350	

- Frequency accuracy,  $\pm 1$  Hz maximum 40°C to + 85°C
- Tone length approximately 300 ms. May be lengthened, shortened or eliminated by changing value of resistor

#### Model TE-64 \$79.95

### COMMUNICATIONS SPECIALISTS

426 West Taft Avenue, Orange, California 92667 (800) 854-0547/ California: (714) 998-3021



## **Shack from Scratch**

Building a ham shack in a new home can be a breeze. Just plan ahead.

Thomas R. Sundstrom W2XQ Box 175 Vincentown NJ 08088 A man's home may be his castle, but have you tried to install a 6-ele-

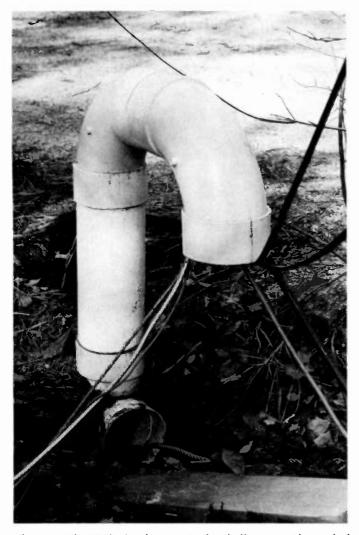


Photo A. The PVC pipe has a couple of elbows on the end of it to keep out rain and snow. A pull rope is left in the pipe to move additional antenna and rotor cables through; otherwise, the open end is capped and covered with dirt.

ment, 20-meter beam on a parapet lately? Most homes built or renovated today are not conducive to installing an amateur radio station.

The problem of what to do with the radio equipment confonted me when my wife and I opted to have a new home built in a semirural area. In our old home on a suburban lot, it had been make-do in a third bedroom with the attendant problems of running antenna feedlines, supplying adequate electrical power, and establishing decent grounds for the equipment.

My solutions will not necessarily be your solutions, but variations of these ideas may help you in solving your installation problems. Funds were a consideration-the overall objective was, after all, to build the house! But when it was all done. I wound up with a fair amount of operating room, all the electrical power I needed, and a TVI-free environment for less than two percent of the total cost of the house and property.

#### **Review the Plans**

Once you have selected the location (no zoning restrictions on towers, right?) and a builder, look over the plans carefully to determine options for the radio room.

In our case, the locale dictated no basement because of the water table. We chose an L-shaped ranch on a slab of concrete. The options were to put the equipment into a bedroom or in the back of the garage. Neither option was desirable.

The solution was relatively simple. The garage was on one end of the house on the long side of the L. We had the builder expand the long side of the L by adding a 6-foot-wide room between the living area and the garage and adding one wall and door. See Fig. 1.

The additional room provided space for the amateur radio equipment, enabled my wife to get the washer-dryer out of an interior closet in the living area, and gave us a mudroom in which to leave boots, raincoats, and other items that should not be trailed across carpeting.

In solving your installation problem, factors to consider would be (1) accessibility to the back yard (or the side yard) for antennas, with a minimum feedline run, (2) keeping the station away from the sleeping areas of the house so that late night and early morning DXing sessions don't disturb the rest of the family, (3) keeping the family TV antenna, TV, and audio equipment apart from the radio equipment, and (4) the location of overhead power lines coming into the house.

If you opt to expand the house or add an addition to solve the location problem of your equipment, you can hold costs down by doing it in such a way that no new corners are created, needing additional forms for concrete and framing. For example, it would have been more costly for us to tack a room on to the back of the garage, extending that by 10 feet or so. Additional costs would have been incurred for laying forms around two additional corners, a redesign of the roof and supporting rafters in that part of the house, and a reconfiguration of the heating and cooling systems: considerably more concrete, lumber, and siding would have been needed.

#### Antenna Feedthroughs

Because space for antennas was available in the back yard, I agreed not to punch holes in the sides or roof of the new house and to see that everything was put in the back and out of sight.

Before the slab was poured, I had the builder lay down 4-inch PVC pipe extending from beyond the foundation of the house to the rear of the proposed station operating area. A 90-degree elbow and a short section of pipe at the desk end put that end above the floor level. The poured concrete anchored the 10-foot sections; a board temporarily capped the end outside the house.

Later, 1 purchased additional sections of PVC pipe and extended the run further into the backyard, bringing it above ground beyond the normal traffic patterns and behind some ground cover. Two 90° elbows are needed so that rain and snow do not enter the pipe. See Fig. 2.

In retrospect, I probably should have put two runs of PVC pipe into the shack area. While one handles a number of RG-8 and RG-8/X and control cables, hardline takes up a lot of room in a hurry.

Factors to consider in planning your own installation include (1) keeping runs of PVC pipe as straight as possible to minimize difficulties in routing cable, (2) leaving a "pull" rope in the pipe so that cable can be fed through from either end at any time (and don't forget to anchor it so that it's not accidentally pulled into the pipe beyond your reach), and (3) consideration of how many antennas and types of feedlines will be installed in the coming years.

Variations on the theme of using PVC pipe to route cable might include using PVC pipe inside the house to route cable to an exterior wall. Place the pipe inside the walls before the sheetrock is hung. Depending upon the design of the house, you may choose to route the pipe and cable to the attic from an interior first- or second-floor room chosen as the "shack," or route it to the basement or the garage before entering the underground run to the antenna tower.

Another variation, for those setting up the operating station in a basement or family room below ground level, would be to bring the PVC through the exterior wall to a point flush with the inside wall. Make up an appropriate bulkhead with connectors and label the lines. In times of electrical storms, shorting plugs can be put on each of the antenna feedthroughs and grounded through the ground attached to the bulkhead plate.

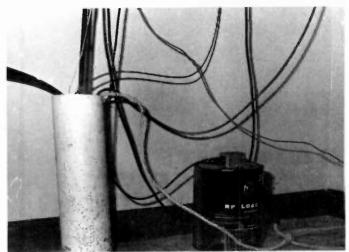


Photo B. The PVC pipe comes up under the operating desk. One of the two ground rods is visible on the right.

#### Grounds

At the same time that the PVC pipe was laid for the antenna cable runs and before the floor was poured, I installed 10-foot, ¼-inch ground rods at the rear of the area where the operating desk was to be placed. I left them about 8 inches above the finished floor.

That simple move has paid off handsomely in the reduction of in-house TVI and RF1 on the operating desk compared with what I had been used to in the previous house. Ground leads are a maximum of 3 feet now.

In your installation, consider the shortest run possible. If you are setting up in an interior room, drop the ground leads through the walls directly to the basement. Use ground rods as long as possible; those 4-foot lengths just won't do the job. Run heavy wire; #4 would be fine. As the heavier wire is a bit difficult to work with, consider tying the heavy ground lead to a heavy-gauge metal plate that has been drilled and tapped with 3/8- or 1/2-inch bolts and place that behind the operating desk. The individual ground leads from the several pieces of equipment can be terminated with spade lugs and bolted to the plate.

#### **Electrical**

Before the wall between the added utility room/ham shack and the garage was closed, I had an electrician wire a separate electrical panel for the radio equipment. At the main electrical panel in the garage, a 70-Amp circuit breaker was installed. A three-wire line was run into the shack wall: another panel was installed with a 70-Amp main circuit breaker, and separate circuit breakers were installed to provide 220 and 110 V ac to a number of outlets.

Perhaps this was overkill, but the family members have instructions on how to turn off either main breaker in case of an emergency. Everything goes down when

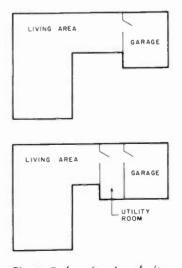


Fig. 1. Before (top) and after (bottom) adjustments to original house plan.



that switch is thrown. (That panel is low enough for even my youngster to reach.)

Plan your needs carefully. I had eight 110 V ac outlets installed, and still I ran out. Also consider height and placement of the outlets. Don't install outlets at tabletop height if the surface of the operating area runs wall-to-wall; put them above or below the tabletop. ahead activities to consider as the house is framed and before the sheetrock is hung are all based around pre-wiring the house for a variety of items.

Don't forget to get the telephone installer at work before the sheetrock goes on. The job is a lot easier and cleaner. Run a telephone line into the shack, and consider having the house wired for two (or more) telephone lines. If you change your mind at the time the installer returns to

#### Odds and Ends

Some other planning-

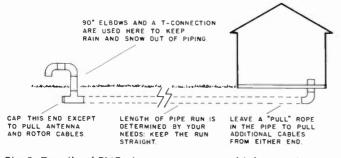


Fig. 2. Details of PVC pipe arrangement which contains coax and control cables

fish out the lines to telephone jacks, there is no problem reverting to one line. There is no charge for pre-wiring the framed house.

Want to install a burglar alarm system? A wired perimeter system tends to be the cheapest, and it's easy to do yourself. Supplies can be acquired from a number of wholesale and retail outlets. Pick the system best for you; it may be easiest to install before the walls are closed. Don't forget about electrical power to the system (most systems also have a battery backup).

Also consider pre-wiring for your stereo system. It's a lot easier to run speaker leads in the walls and over ceilings than under rugs or behind wall moldings. Use some larger-size electrical zip cord, such as #12 or #14. rather than the light stuff. Plan ahead for the day when you upgrade to a larger, more powerful amplifier and have speakers in other areas of the house. You can always leave the wires in the walls until you actually have speakers in hand.

An intercom system is also very easy to put in before the walls are closed. Plan ahead. (It's your choice to put one in the shack so that you can be called to do chores in the middle of a contest!)

Be sure to install 75-Ohm coaxial cable for the household TV and FM antenna system before closing the walls. Consider the placement of the antennas with respect to the ham equipment when routing the cable. I opted to install an antenna to take care of both the TV and the FM stereo receiver under the roof of the house, rather than outside, and hung it in the end of the house away from the shack. Plan ahead if you want multiple outlets for multiple TV sets, and don't forget an electrical source for a distribution amplifier if your plans require one. Using shielded cable and picking the right spot for your TV/FM antenna(s) will go a long way to eliminating in-house TVI.

I also took advantage of the open walls to install a coaxial cable which was later hooked up to an atticmounted scanner antenna and a scanner in the family room; my wife and I eavesdrop on one or two police and fire frequencies, some remote broadcast stuff, and one or two 2-meter frequencies.

#### In Closing

The building of a new home or of a major addition to an existing home is a massive undertaking. Attention has to be given to everything, and the smallest detail has to be reviewed on a continuing basis. If you tell the builder before he begins that you want to install certain wires and pipes for the amateur radio station, there shouldn't be any problems. In my case, the builder gave me a schedule of construction and permission to come in to install the ground rods and the prewiring described above; he placed the PVC pipe for me, and the electrician came after I took title to the house.

Keep receipts on everything you purchase and install. That's all part of your tax records for calculating the adjusted cost of the house and the improvements, depending upon the dates involved.

Some of the ideas described above are not necessarily new or original, but they are intended as food for thought. Your needs are different from mine, but if I have reminded you to think about a particular installation problem before you begin a project, then I have been successful. Good luck in your building. AZDEN PCS-300

# 5.820



## New 2-M Handheld FM Transceiver

ndard for Comparison

8 MHZ COVERAGE • 142 to 149.995 MHz in 5 kHz steps, including CAP and

IDEAL SIZE & WEIGHT DISTRIBUTION = 7.3" high by 2.5" wide by 1.8"

MICROCOMPUTER CONTROL • All frequency operations are done by means of a microcomputer keyboard with acquisition tone. LCD DISPLAY WITH TIMED LAMP . Draws almost no current. Lamp

times out automatically after 20 seconds.

16 KEY AUTOPATCH . Keyboard works as a Touchtone\* pad while

PL TONE SWITCH • Actuates optional subaudible tone module. PROGRAMMABLE "ODD SPLITS" . Transmit and receive on any

possible frequency combination. Reset in seconds. 9 CHANNEL MEMORY WITH SCAN - Eight addressable channels and one externally accessible up/down channel retain frequency and standard offset.

AUTOMATIC INCLUSIVE OR EXCLUSIVE PROGRAMMABLE Backup drain is a scant 10 microamps! BAND SCAN . Limits may be reset in seconds ... Scans either Inside or

BUSY AND VACANT SCAN MODES . Scan for either an occupied or outside the limits.

KEYBOARD LOCK 

Prevents accidental change of frequency or scan status.

TRANSMIT LOCK . Avoids unintentional transmission. DIGITAL S/RF AND MEMORY ADDRESS METER . Shows relative signal strength on receive, relative power on transmit. Also shows

HIGH OR LOW POWER . 3 watts high, 1 watt low. Low power is

continuously adjustable from 0.5 to 3 watts. TRUE FM . Not phase modulation - Unparatieled audio quality,

AUTOMATIC FRONT END TUNING . RF stage is varactor tuned for

RUGGED COMMERCIAL-GRADE MODULAR CONSTRUCTION superior sensitivity and selectivity, The PCS-300 is built to take years of the toughest operating conditions,

SUPERIOR RECEIVER . Sensitivity is 0.25 uv for 20.dB quieting.

0.2 uV for 12 dB SINAD. STANDARD ACCESSORIES . Heavy duty NICAD battery pack (500 BNC ANTENNA CONNECTOR mAh), belt clip, hand strap connector, flexible rubber antenna, earp sene,

ac charging unit, and special stand for table-top operation. OPTIONAL ACCESSORIES • Deluxe leather case, mobile do charging cord, external speaker/microphone, and PL tone module.

No. 12-17, 1-chome, Kami-Renjaku, Mitaka, Tokyo, Japan, Telex: 781-2822652 JAPAN PIEZO CO., LTD.

Shown

Actual

u

8817 S.W. 129 Terrace, Miami, Florida 33176 Telephone (305) 233-3631 Telex 80-3356 Toll-free (800) 327-3302 EXCLUSIVE DISTRIBUTOR AMATEUR-WHOLESALE ELECTRONICS, INC. AZDEN

## COMPUTERIZED MORSE KEYE


AEA, the first company to introduce microcomputerized products to the Amateur Radio market, is proud to announce the second generation of computerized electronic keyers. Each keyer is preprogrammed, no computer language is required of the operator. The easy to use keypads eliminate up to 75 switches or potientiometers, thereby greatly simplifying the operation of such sophisticated keying systems. We invite you to compare the features of our keyers (shown below) to ANY others.

IMPORTANT KEYER AND/OR TRAINER FEATURES	AEA MM-2	AEA KT-2	AEA CK-2
Speed Range (WPM)	2-99	1-99	1-99
Memory Capacity (Total Characters)	500	N/A	500
Message Partitioning	Soft	N/A	Soft
Automatic Contest Serial Number	Yes	N/A	Yes
Selectable Dot and Dash Memory	Yes	Yes	Yes
Independent Dot & Dash (Full) Weighting	Yes	Yes	Yes
Calibrated Speed, 1 WPM Resolution	Yes	Yes	Yes
Calibrated Beacon Mode	Yes	N/A	No
Repeat Message Mode	Yes	N/A	Yes
Front Panel Variable Monitor Frequency	Yes	Yes	Yes
Message Resume After Paddle Interrupt	Yes	N/A	Yes
Semi-Automätic (Bug) Mode	Yes	Yes	Yes
Real-Time Memory Loading Mode	Yes	N/A	Yes
Automatic Word Space Memory Load	Yes	N/A	Yes
Instant Start From Memory	Yes	N/A	Yes
Message Editing	Yes	N/A	Yes
Automatic Stepped Variable Speed	No	No	Yes
2 Presettable Speeds, Instant Recall	No	No	Yes
Automatic Trainer Speed Increase	Yes	Yes	N/A
Five Letter or Random Word Length	Yes	Yes	N/A
Test Mode With Answers	Yes	Yes	N/A
Random Practice Mode	Yes	Yes	N/A
Standard Letters, Numbers, Punctuation	Yes	Yes	N/A
All Morse Characters	Yes	Yes	N/A

For more information write AEA, or better yet see your favorite dealer for a demonstration.

Software ©copyright by AEA.

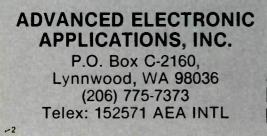PRICES AND SPECIFICATIONS SUBJECT TO CHANGE WITHOUT NOTICE OR OBLIGATION.



**MM-2** 



**MorseMatic™** 

KT-2



**Keyer Trainer** 





**Brings you the** breakthrough!

### **Preamplifiers**



The famous Palomar Engineers preamplifier has been updated and packaged in an attractive new cabinet.

For the SWL there is the P-305 (9-v DC powered) and the P-308 (115-v AC powered) featuring full shortwave coverage, selection of two antennas, 20 db attenuator, 15 db gain control and on-off-bypass switch.



For transceivers, the P-310X (115-v AC powered) and the P-312X (12-v DC powered) feature automatic bypass on transmit, adjustable delay for return to receive, and 350 watt transmit capability.

All models have these features:

- Up to 20 db gain. Covers 1.8 to 54 MHz in four bands.
- Low noise figure.
- Reduces image and spurious response.
- 8" x 5" x 3". Brushed aluminum control panel. Black vinyl cover.
- SO-239 connectors.
- LED pilot.

naster charc

Order direct or from your favorite dealer. Model P-305 Receiver Preamplifier for 9-v DC \$99.95. Model P-308 for 115-v AC \$109.95. Transceiver Preamplifier Model P-310X \$129.95. Model P-312X \$129.95. Add \$3 shipping/handling. Calif. residents add sales tax.




Don't wait any longer to pull out weak, rare DX.

Send for FREE catalog describing the Preamplifiers and our complete line of Noise Bridges, SWR Meters, Toroids, Baluns, Tuners, VLF Converters, Loop Antennas and Keyers.

## Palomar ngineers

1924-F West Mission Rd. Escondido, CA 92025 Phone: (619) 747-3343

## 1983 CALLBOOKS

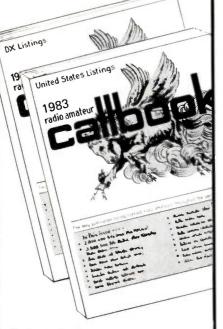

Clegg

Standard

Drake

Wilson

Kenwood Midland

Lafayette Tempo

Icom

Regency

VHF Eng

Yaesu

#### Order today! NEW 1983 RAOIO AMATEUR CALLBOOKS READY DECEMBER 1ST!


The latest editions of the world-famous Radio Amateur Calibook will be available soon. The U.S. edition features over 400,000 listings, with over 75,000 changes from last year. The Foreign edition has over 370,000 listings, over 50,000 changes. Each book lists calls and the address information you need to send QSL's. Special features include call changes, census of amateur licenses, world-wide QSL bureaus, prefixes of the world, international postal rates, and much more. The new 1983 Callbooks will be published December 1, 1982. Order your coples now.

	Each	Shipping	Total
US Callbook	\$19.95	\$3.05	\$23.00
Callbook	\$18.95	\$3.05	\$22.00
Order both boo \$41.95 including			time for

Order from your dealer or directly from the publisher. All direct orders add shipping charge. Foreign residents add \$4.55 for shipping. Illinois residents add 5% sales tax.




Lake Bluff, IL 60044, USA

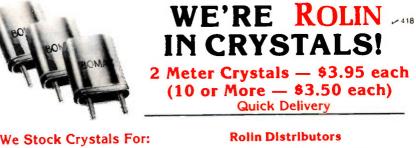

P.O. Box 436 Department 7 Dunellen, N.J. 08812 201-469-1219

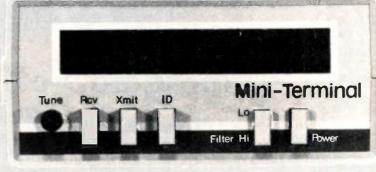(Custom Crystal Orders Accepted.) Precision Cut Land Mobiles Available





### Mini-Terminal<sup>tm</sup> suggested price \$299.95

All in one package—CW, RTTY, ASCII send/receive and hard copy capability for under \$300. Unbellevable, but true! Again, Kantronics puts all the features you want in a single unit: The Kantronics Mini-Terminal.<sup>tm</sup>

You send CW with your key or keyboard, and the Mini-Terminal<sup>tm</sup> converts to RTTY or ASCII. Mini-Terminal<sup>tm</sup> also reads all Incoming CW, RTTY, and ASCII messages and reads out on a bright green 10-digit display. For hard copy simply attach any Centronix compatable printer, such as the Epson MX-80 or the Paper Tiger, and watch the Mini-Terminal<sup>tm</sup> do the rest.

A complete code reader and RTTY terminal, with printer compatability all in one package only 2½"x5"x5½". Get all you can for your dollar; get the Kantronics Mini-Terminal.<sup>tm</sup>

See your local Kantronics dealer, or contact


(913) 842-7745 1202 E. 23rd Lawrence, Kansas 66044

travel through glass having a dielectric constant of 5, the distance it would move during the time period of one wavelength would be much shorter. In fact, one wavelength would be only 44.72% of the equivalent length in space. When converted to a decimal figure, .4472, this dielectric correction is the "velocity factor" (VF) of the glass. It is equal to the reciprocal of the square root of the dielectric constant or VF =  $1/\sqrt{5}$ = 1/2.236 = .4472. This formula describes the mathematical relationship between "dielectric constant" and "velocity factor."

So, what can we do with dielectric constants or velocity factors? Actually, 1 can think of very few occasions when changing the dielectric in a capacitor would be necessary, desirable, or feasible. It would be fairly easy, though, to make a low-capacity variable capacitor by using two pieces of aluminum and to insert a variable amount of a plastic dielectric via a shaft and a dial system.

The velocity factor, though, is a much used and occasionally misused factor.

All of the coaxial and parallel-wire feedlines using solid dielectrics are characterized by higher losses than found in equivalent air-insulated lines and by having velocity factors of less than 1. These velocity factors mean that radio waves are propagated along these lines at velocities less than in free space. When the electrical length of the feedline to be used is critical, the velocity factor must be considered in calculating the physical length. If you wanted an electrical length of  $1/2\lambda$  and the velocity factor was .80, then the desired formula for the physical length in feet would be:  $1/2\lambda = (492)$  $\times$  .80)/frequency (MHz).

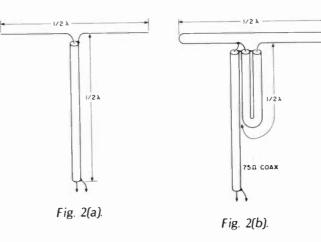

The velocity factors for some common coaxial feedlines range from .80 for polyethylene foam dielectrics to .66 for solid polyethvlene. Some 300-Ohm parallel-conductor feedlines using a solid dielectric of polyethylene have a velocity factor of about .82. Why should that be? Fig. 1(a) shows a cross-sectional view of a piece of 300-Ohm line. The oval represents the solid dielectric and the dots represent the conductors. The arrowed lines represent an instantaneous electric field that might exist at a given moment in time. The fact that a portion of this field exists outside the solid dielectric is the reason that the 300-Ohm line velocity factor of about 82 lies between the .66 factor of solid polyethviene and the value of 1.0 for air. This also explains the sensitivity of oval 300-Ohm line to external influences such as rain, snow, and ice, or to the proximity of metallic objects.

Fig. 1(b) shows the cross section of a 100%-shielded coaxial cable. In this case, the electric field is wholly contained within the shield, and surrounding influences are minimal. That's why coaxial cable can be taped to your tower, run along gutters, or even buried with little observable effect upon its performance.

The velocity factor is used to determine the physical length of the line whenever a particular electrical

length of feedline is required, and when in the feedline's use an electric field will exist between the feedline conductors as a result of current flow along the conductors. Fig. 2 shows some of the typical cases wherein the velocity factor would be used in calculating the physical length of the required feedline. In Fig. 2(a), a feedline  $1/2\lambda$  long is used so that the impedance at the center of the antenna will be repeated at the ground end for easy impedance measurements. The desired physical length of a  $1/2\lambda$  line would be the free-space length times the velocity factor, or  $1/2\lambda$  (ft.) = (492  $\times$  VF)/frequency (MHz). In this case, the line could be made any whole number multiple of the correct length if a single  $1/2\lambda$ wasn't long enough.

Fig. 2(b) shows a 4:1 coaxial balun connected to a folded dipole radiator. The length of the  $1/2\lambda$  U-shaped piece of coax is calculated with VF. Fig. 2(c) shows broadside radiating elements, each fed through a gamma match. Any equal lengths of cable could be used for pieces X and Y to satisfy the phasing requirements of the broadside array. The  $3/4\lambda$  sections, however, also serve as impedance transformers between the radiators and the feedline junction. The physical length of the  $3/4\lambda$  lines should be computed with the VF.

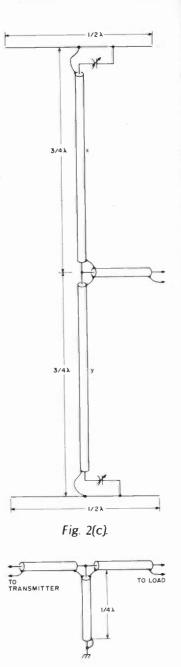


Fig. 2(d) shows a  $1/4\lambda$  section of coaxial cable used as an rf choke. The shorted end of the  $1/4\lambda$  section is transformed into a very high impedance at its connection point to the coaxial feedline. It has no effect upon the feedline as far as the operating frequency is concerned, but it keeps both sides of the coax at ground potential for dc or lightning protection. In addition, the  $1/4\lambda$  section will act as a dead short across the coaxial cable at the second harmonic!

Fig. 2(d).

Fig. 2(e) shows  $1/4\lambda$  ver-Reader Service for facing page  $\sim 83^{-4}$ 

92 73 Magazine • December, 1982

### FT-230R: QUITE A SIGHT! (AND EASY TO SEE, TOO!!)

Sporting an all-new Liquid Crystal Display, the FT-230R is Yaesu's high-performance answer to your call for a very affordable 2 meter mobile rig with an easy-to-read frequency display! The FT-230R combines microprocessor convenience, a sensitive receiver, a powerful yet clean transmitter strip, and the new dimension of LCD frequency readout. See your Authorized Yaesu Dealer today — and go home with your new FT-230R!

- LCD five-digit frequency readout with night light for high visibility day or night.
- Two VFOs for guick QSY across the band.
- Ten memory slots for storage and recall of favorite channels.
- Selectable synthesizer steps (5 kHz or 10 kHz) in dial or scanning mode.
- Priority channel for checking a favorite frequency for activity while monitoring another.
- Unique VFO/Memory Split mode for covering unusual repeater splits.
- Up/Down band scan plus memory scan for busy or clear channel. Scanning microphone included in purchase price.

Full 25 wette of DF serves suted

AFSU

SALE SUBJECT

 Full 25 watts of RF power output from extremely compact package.


YAESU

482


- Built-in automatic or manual tone burst
- Optional synthesized CTCSS Encode and Encode/Decode boards available.
- Lithium memory backup battery with estimated lifetime of five years.
- Optional YM-49 Speaker/Microphone and YM-50 DTMF Encoding Microphone provide maximum operating versatility.

And don't forget! Yaesu has a complete line of VHF and UHF handheld and battery FT-208R FT-708R portable transceivers using LCD display !!! **FM Handheld FM Handheld** 2 Meters 70 cm FT-290R - 2 Meters SSB/CW/FM Portable FT-690R - 6 Meters **USB/CW/AM/FM** Portable Price and Specifications Subject To e radio. Change Without Notice or Obligation

> YAESU ELECTRONICS CORP. 6851 Walthall Way, Paramount, CA 90723 • (213) 633-4007 Eastern Service Ctr., 9812 Princeton-Glendale Rd., Cincinnati, OH 45246 • (513) 874-3100

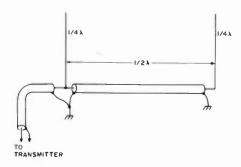



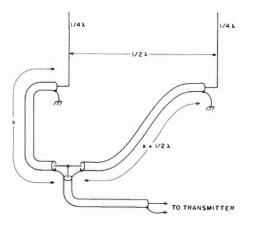

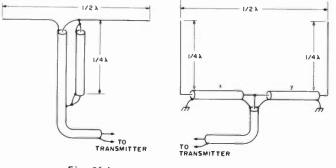


Fig. 3(b).

tion pattern. Fig. 2(f) shows

similar antennas spaced

 $1/4\lambda$  apart and fed 90° out

of phase to produce a unidi-

rectional pattern. The ve-

locity factor would apply to

these phasing lines. Please

note that Figs. 2(e) and (f)

are just basic representa-

tions of an antenna system

and not a practical arrange-

How could you make a

 $1/2\lambda$  of coax (free space  $1/2\lambda$ 

 $\times$  VF) stretch between two

verticals spaced a 1/2 $\lambda$  (free-

space value) apart? It

would be impossible unless


you used an air-dielectric

coax and then, of course, its

proper length would be

ment.



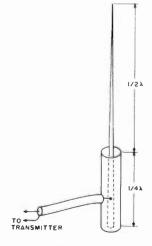



tical antennas spaced  $1/2\lambda$  apart and fed 180° out of phase through a  $1/2\lambda$  line to achieve a figure-eight radia-

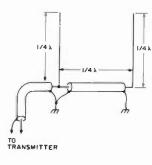


Fig. 2(f).

equal to the antenna spacing.

The proper phasing with solid-dielectric coax can be achieved as shown in Fig. 2(g). Dimension X is any convenient length of coax. The  $1/2\lambda$  portion is computed with the VF. While this feedline system provides the proper phasing, it doesn't provide the necessary impedance matching. The same scheme could be used to provide the correct phasing for Fig. 2(f), but then the lines would be X, and X  $+ 1/4\lambda$ 

Fig. 3 shows some cases where the velocity factor is not used in determining the physical length of solid-dielectric cables. In Fig. 3(a), a  $1/4\lambda$  of coaxial cable is paired with a portion of the feedline to act as a decoupling stub or balun. Its length is approximately equal to the free-space length of a  $1/4\lambda$ . The VF of the coax does not apply because no electric field exists between the inner conductor and the shield of the  $1/4\lambda$  of coax. In fact, the inner conductor could be cut off flush with the dielectric, or even removed, as it has no function in this application other than to provide increased physical rigidity. In Fig. 3(b), line segments X and Y could be of any equal lengths and still provide the correct phasing for the broadside array. VF does not apply because a particular electrical length of feedline is not required.

The effects of velocity factor/dielectric constant in places other than feedlines

can sometimes be important to the correct functioning of antennas or resonant circuits. For example, a coaxial version of a "J" antenna is shown in Fig. 4. The lower 1/4 $\lambda$  could be an airinsulated high-Q resonant section which matches the high end impedance of the 1/2 $\lambda$  radiator to the coaxial feedline.

This is a good, simple antenna for VHF. If it were to be built, though, you might be tempted to fill the lower  $1/4\lambda$  section with plastic potting compound for improved physical rigidity or to minimize the effects of weather. Any dielectric added, however, would change the electrical length of the section, thereby detuning the system. A better approach would be to use the velocity factor of the plastic filler beforehand to determine the correct length of a plasticized  $1/4\lambda$ section.

Why have I persisted in using the free-space formulas times the velocity factor to compute specific physical lengths? What's wrong with the old, tried and true formula, 468/frequency (MHz), to find the length of a  $1/2\lambda$ ? The reason is that antenna design is influenced by something called "end effect." This necessitates just about a 5% reduction of the freespace lengths when calculating the physical length of wire antennas. This phenomenon does not occur in transmission lines, so for these applications we just have to adjust the freespace figures with the velocity factor.

There is no doubt that coaxial cable is the mostused amateur feedline today. Its ease of use more than compensates for its small losses. If you need a critical electrical length, however, don't forget to use the velocity factor established by the cable manufacturer.

94 73 Magazine • December, 1982

## step up to the best...

Without doubt LR-1 is the repeater value leader! Compare its outstanding performance with any repeater -- then look at its price. LR-1 features include individual die-cast shielding of receiver and transmitter plus a separately shielded 6-stage receiver prefilter for peak performance in harsh RF environments • Front panel metering of all vital functions • CW identifier • Symmetric hard limiting for clean natural audio • Low power MOS control logic • Even the cabinet is included -- just plug in and go! The price? Only \$1095 (US amateur club net).


**LINKING?** The LR-1 is also available with control circuitry for Link Transceiver operation. Now link repeater sites with the flexible control capability you've always wanted.

**HIGH POWER?** Our PA-75 power amplifier is the champion! Ruggedly built to give years of dependable operation in continuous duty repeater service.

Mark 3C repeaters and controllers have no equal in performance. Both units feature auto patch, reverse autopatch, autodial, 13 Morse messages and a total of 39 functions. Both feature microprocessor control and both have been proven in the field from icy Alaska to tropical Brazil. A Mark 3C supercontroller can make any repeater a super performer. The Mark 3CR repeater is in a class by itself. It combines superbly designed RF circuitry in one handsome package. It is without doubt the world's most advanced repeater!
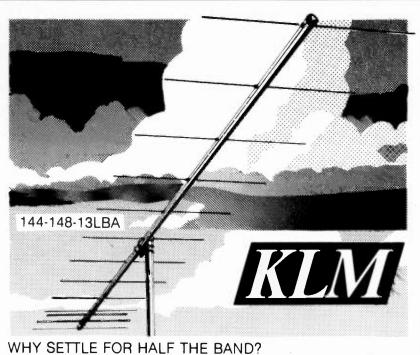
## SEE US AT DAYTON CALL OR WRITE FOR FULL DETAILS MICRO CONTROL SPECIALTIES

23 Elm Park • Groveland, Massachusetts 01834 • Telephone (617) 372-3442




Enjoy super-gain, low VSWR, and FULL COVERAGE, 144 through 148 MHz, with less weight and windload. Dual-driven elements, balanced feed for a better match and clean pattern.

Bandwidth:	144-148 MHz	Balun:	2KW 4:1
Gain:	15.5 dBd	Boom:	21' .5/11/2"
VSWR:	1.2:1 & less	Windload:	1.6 sq ft
Beamwidth:	28°	Weight:	9 lbs
	the second se	the second se	and the second se

CIRCULAR POLARIZED For the Phase IIIB satellite and terrestrial DX, ATV, and FM. Minimizes multipath and flutter fading. Rugged symmetrical construction.

A Designation of the local division of the	the survey of th
Bandwidth:	420-450 MHz
Gain:	12 dBdc
VSWR:	1.5:1 & less
F/B:	20 dB
Baluns:	2KW, 4:1 (2)
Boom:	88''/1''
the second s	

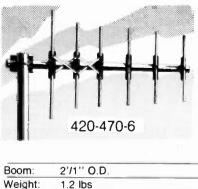

TAN	
420-450-18C	
Windload: .5 sq ft	
Weight: 3.6 lbs	

IDEAL for point-to-point and repeater control. Rearmounted, vertically polarized, compact. Continuous coverage, 420-470 MHz. Direct coax feed suitable for most installations.

Bandwidth:	420-470 MHz
Gain:	8dBd
VSWR:	1.2:1 & less
Beamwidth:	60°
F/B:	20 dB, min

SEE YOUR KLM DEALER:

*KLM* Electronics, Inc. P.O. Box 816, Morgan Hill, CA 95037 (408) 779-7363



CW TEACHING SYSTEMS

Twin Oaks Associates is a partnership of mental health professionals who are hams interested in helping others to learn CW. Twin Oaks has developed three Morse code teaching systems on tape which represent the careful application of psychological principles to learning. They help students learn to recognize and copy Morse characters at a very high speed.

The first set of tapes is called System 12©. It is designed for the ham who may have a Novice or Technician class license but can't "get over the hump" to pass the General class code test. System 12 takes students past 15 words per minute on five carefully-structured, successive-demand, 60-minute cassettes.

The second training program is called System 24©. It assumes that the student is able to copy comfortably at 9 or 10 words per minute but would like to go after the amateur Extra class license. This program is on five 60-minute cassettes and carries the student past 30 words per minute.

The third teaching system, the System 12 Alphabet Book , is designed for persons who know absolutely nothing about Morse code. It may be used, however, by persons who are not thoroughly comfortable at 5 words per minute, and it is useful for either classroom or selfinstruction.

Each program, or system, comes with its own carefullywritten study guide. Systems 12 and 24 cost \$30 each, and the System 12 Alphabet Book costs \$15.





#### A modular approach... for your own custom-designed ATV system . . . . Here's how TXA5-4 ATV EXCITER/MODULATOR.\$89 ppd



PA5 10 WATT ATV POWER MODULE \$89 ppd

The PA5 will put out 10 watts RMS power on the sync tips when driven with 80 mw by the TXA5 exciter 50 ohms in and out, plus bandwidth for the whole band with good linearity for color and sound. Requires 13.8 vdc regulated @ 3 amps.



#### TVC-2 ATV DOWNCONVERTER.... \$55 ppd

Stripline MRF901 (1.7 db NF) preamp and double balanced mixer module digs out the weak ones but resists intermods and overload. Connects between uhf antena and TV set tuned to charned 2 or 3. Varicap tunes 420 to 450 mHz. Requires + 12 to 18 vdc @ 20 ma. Super sensitive TVC-2L with NE64535 preamp (.9db NF) stage ... \$69 ppd.

#### \*TXA5, PA5, FMA5 and TVC Basic Module Pkg.

FAST

SCAN

\*\$249

This wired and tested module is designed to drive the Motoroia MHW-710 module in the PA5 10 watt linear amp. The crystal in the 100 mHz region keeps har-monics out of two meters for talk back. The video modulator is full 8 mHz for computer graphics and col-or. Requires 138 vd creg gr 70 ma. Tuned with tation 439 25, 434.0, or 426.25 mHz. Provision for sync ex-panding. Two faceworks and solve and the solve and th

FMA5 AUDIO SUBCARRIER GENERATOR

Puts audio on with your camera video just as broad

cast TV does at 4.5 mHz. Puts out up to 1 v p-p to drive the TXAS or VM-2, 3, or 4 modulators. Requires low 2 mic (150 to 600 ohms), and + 12 to 18 vdc @ 25 ma. Works with any xmtr with 5 mHz video bandwidth.

\$29 ppd

panding. Two frequencies available.

Call or write for our complete list of specifications, station set-up diagrams, and optional accessories which include antennas, modulators, detectors, test generators, cameras, etc. WE ARE A FULL-LINE SUPPLIER OF ALL YOUR ATV NEEDS.

TERMS: VISA or MASTER CARD by telephone or mail, or check or money order by mail. All prices are delivered in USA. Allow three weeks after order for delivery. (213) 447-4565 Charge card orders only

P.C. ELECTRONICS 2522 Paxson Lane, Arcadia, California 91006 Tom W6ORG Maryann WB6YSS



The New Standard in High Performance Repeater Control...

□ FRIENDLY, POWERFUL, EASY TO USE - Human engineered to be your "assistant" at the repeater, with capability second to none.

**REMOTELY CONFIGURABLE** -Change command codes, messages, tone characteristics. timing, and more, remotely! Reliable storage in E<sup>2</sup>PROM.

Call or write for detailed specifications.

Manual and demonstration cassette tapes available separately.

- □ Room to grow: BUILT IN! -Features intelligent remote control and meter readback. Interfaces to synthesized remote bases and links. Planned software upgrade path.
- □ SUPPORT We invented the Computer Controlled Talking Repeater," so we know how to provide the applications assistance, and long term support so crucial to a computer based product.
- □ BRING YOUR REPEATER SYSTEM INTO THE 80'S - Starting at less than \$1200!


The RC-850 **Repeater Controller!** 



10816 Northridge Square Cupertino, CA 95014 124 (408) 253-8085


Ŧ 9 11. TE-35Asp

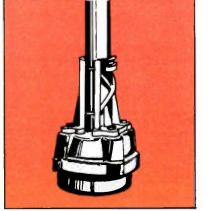**Roof Tower** 11.6 ft. \$194.95 6<sup>1</sup>/<sub>2</sub> ft. extension sections \$70.00



**ROTATE YOUR BEAM** 

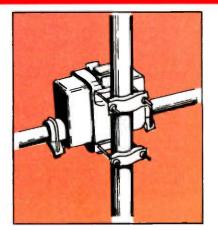**KR400** Azimuth Rotator\* 8<sup>1</sup>/<sub>2</sub> sq. ft. **\$119.95** 




**KR500 Elevation Rotator\*** 71/2 sq. ft. \$189.95

\* Rotators come complete with an attractive control box that indicates beam heading.

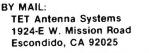Send for free catalog describing our rotators, towers, thrust bearings, VHF beams, Swiss Quads, Tribanders, and more.





BY PHONE: 714-743-7025



AL ST

## HAL COMMUNI **RTTY & CW**

### **PROFESSIONAL SYSTEM!**

The DS3100ASR Terminal and ST6000 Demodulator are the choice of professional RTTY operators the world over. Some of the advanced features offered by this equipment are:



ic mail box" to DS3100 • Extends DS3100 storage by 32K . Works with all codes, Baudot, ASCII, or CW 
 Userprogrammable call-up code 
May be used with 'KOS to switch TX and RX on/off ● Inserts CW ID when required ● Sends user "HELP" and "RYRY" and "QBF" test messages when requested • Lists directory contents, size, and date created . Allows password for delete or read protection of files . Use for brag tapes as well as for message storage Commands include: ".DIR .SDIR .READ WRITE ENDFILE HELP SEND FILE-HELP .KY1ON .KY1OFF .KY2ON KY2OFF .PRINTON .PRINTOFF .QBF .RYS .DELETE .EXIT' . Factory installation only

#### **DS3100ASR:**

• True ASR capabilities • 200 line display storage • 150 lines receive • 50 lines transmit • Baudot, ASCII, and Morse Codes • 45 to 9600 baud RTTY • 5 to 175 WPM CW • WORD, LINE, and CONTINUOUS modes 
SYNC idle ("diddle") 
Unshift on space (USOS) • WRU answerback • Selective call printer control (SEL-CAL) • Serial ASCII printer output for received text in any code • Four keyboard controlled accessory switches • RS232 or loop RTTY I/O • 10 user-programmable HERE IS messages • EAROM non-volatile storage of 4 HERE IS messages and operating conditions On-screen status indicators
 Custom labeled 3-legend keytops for non-confusing control operations 
Built-in 12 Inch P31 display ● 120/240V, 50/60 Hz AC ● 13.5" × 20.5" × 15.25" ● 60 lbs. (two cartons)

### **PORTABLE RTTY and CW**

The HAL CWR6850 brings a new dimension to amateur RTTY operation - PORTABILITY! Even though the size is small, the features are many:

#### CWR6850:

Built-In display screen and demodulators • 5" green CRT display • 32 character display lines ●4 pages of display ●6 user-programmable HERE IS messages Internal RTTY demodulator for both "high" and "low" RTTY tones, three shifts each (170-425-850) • Baudot or ASCII baud rates of 45 to 300 baud 
Morse code send and

receive 3 to 40 wpm 
Parallel ASCII printer output for received text • Separate, small keyboard Tape input/output connections 
 Requires 12 VDC, 1.8 Amperes ●12.75" × 11.75" × 5" (CWR6850); 13.75" × 2" × 7.25" (Keyboard) • 20 lbs, including keyboard





### LOW COST AND COMPACT!

The DS2050KSR is a time-proven RTTY terminal, combining the best of the popular HAL DS2000 and ST5000. Some of the DS2050 features are:

#### **DS2050KSR:**

• One cabinet for keyboard, display generator, and demodulator • Full 72 character line by 24 line screen • 2 programmable HERE IS messages • Built-in RTTY demodulator for two shifts (170 or 850 Hz) Send and receive Baudot RTTY at 45 to 100 baud and ASCII RTTY at 110 to 300 baud . Send CW at 5 to 100 wpm • Receive CW (with MR2000 option) from 5 to 100 wpm • RTTY CW ID is built-in • KOS (Keyboard operated switch) • Full current loop interface for send and receive RTTY loop (external loop supply required) • SYNC idle • USOS • WORD mode • Bright-dim video to distinguish TX and RX text • 120/240V, 50/60 Hz AC • 14.1" × 8.8" × 4.7" • 18 lbs • Two-tone tan cabinet • External TV monitor required (HAL KG12 or ESM914 recommended)

#### ST6000:

 Super RTTY demodulator
 Perfect companion to DS3100 in "dream station" • All three standard RTTY shifts (170-425-850 Hz) Receive and Transmit circuitry
 Transmit tones crystal controlled ● Transmit CW ID - 100 Hz shift down in frequency ● Available for "high" or "low" tones (High tones recommended for United States -2125 Hz mark) • Wide bandwidth limiter for superior signal capture FM or AM operation 
Multipole active filter front-end
Active filter discriminator • Active low pass filter • Synthesized transmit tone outputs • ATC (automatic tone threshold control) • DTH (decision threshold hysteresis) • RS232, MIL188, CMOS, and current loop 1/O • Built-in 175 VDC, 60 ma neutral loop supply • Motor control relay for autostart • Antispace • Built-in tuning oscilioscope • 120/240V, 50/60 Hz AC • Table or Rack cabinet (specify which) •  $3.5^{"} \times 9^{"} \times 17^{"} • 15$  lbs.

## **CATIONS CORP. EQUIPMENT**



### **COMMUNICATIONS TERMINAL**

The CT2100 and KB2100 make up a very versatile and convenient RTTY and CW communications terminal. The CT2100 offers capabilities available in no other single-unit RTTY system. Some of these features are:

#### **RS2100 - NEW RTTY TUNING SCOPE:**

 Matches CT2100 cabinet Gives crossed-ellipse type of RTTY tuning indication for CT2100 • Also includes bullt-in 175 VDC, 60 ma current loop



supply 
 Connects directly to CT2100 rear panel 
 Also may be used with these other HAL products: DS2050, DS2000, ST5000, CWR685, CWR6850, CWR670, CWR6700, and ST5 or ST6 (with modification) ● One inch green phosphor CRT • Front panel positon, focus, and intensity controls • 120/240V, 50/60 Hz AC • 3.5" × 8.25" × 10.156" • 12 lbs.

#### MSG2100 · Message Storage ROM Option:

 Installs in CT2100
 Stores 7 - 256 character and 1 - 192 character "brag-tape" or reply messages 
 Also stores contents of both HERE IS messages 
 Non-volatile storage is not lost when power is turned off • Type 2716 EPROM programmed by HAL or by anyone with EPROM programmer 
 Have several made - one for home, 10.375"; 19 lbs (CT2100) • 14" × 2.375" × 7"; 7 lbs (KB2100) • Two-tone gray cabinet with one for field day, etc. • Coding forms included with each CT2100 - KB2100 color front panel graphics • External monitor required - HAL KG-12 or ESM914 recommended. system.

### SWL - RTTY and CW, TOO!

Now you can also enjoy shortwave listening to RTTY and Morse code transmissions with a unit designed for that purpose. The CWR6700 offers many advance features, previously available only in more expensive transmit-receive terminals. Some of these features are:

#### CWR6700:

• Receive ASCII, Baudot, or Morse code transmissions and see the decoded characters on the TV monitor screen • RTTY speeds from 45 to 300 baud (60, 66, 75, 100, and 300 wpm) CW speeds from 4 to 50 wpm 
 Unshift on space (UOS) for Baudot reception 
 Parallel

CT2100 & KB2100:

KSR or split screen operation
 Large or

small character video • 72 or 36 character display lines •

24 lines per display page • 2 pages of 72 character per line display or 4 pages of

36 character lines • 12 line split screen transmit pretype buffer • 2 user-programmable HERE IS

messages 
Very large brag tape storage in MSG2100 (2K characters) 
4 Built-in RTTY demodula-

tors • "High" tone RTTY (170-425-850 shift) • "Low" tone RTTY (170-425-850 shift) • 103 Mo-

dem RTTY (1070-1270 Hz; to 300 baud) ● 202 Modem RTTY (1200-2200 Hz; to 1200 baud) ●

Baudot, ASCII, or Morse code ● 45 to 1200 baud Baudot or ASCII RTTY ● 5-100 WPM CW ● Crystal controlled synthesized transmit tones match receive filters • RS232, Loop, or audio I/O Interface 
 Tape in/out connections
 KOS (keyboard operated switch) for auto TX/RX
 HDX or

FDX • Transmit data from loop device (paper tape distributor, etc.) • Small separate keyboard with

flexible cord for comfortable lap operation 

On-screen status line and tuning indicator

Serial

ASCII printer output to print all received text • 120/240V, 50/60 Hz AC • 16.75" × 3.625" ×

ASCII printer output 
Printer prints received ASCII, Baudot, or Morse signals • Requires external TV monitor (HAL KG12 or ESM914 recommended) • Runs on 12 VDC, 0.8 Ampere ●8" × 2.85" × 12.6" ●8 lbs

### **RTTY DEMODULATORS:**

00

HAL has long been a leader in the RTTY demodulator market. Our first two demodulator products, the ST5K and ST6K, are still in use all over the world and are still available on special order from HAL Communications (kit form only). The ST6000, as mentioned above, is a "standard of comparison" for performance and reliability. The ST5000 is a simplified version of the ST6000, particularly suited for limited budget installations where high performance is still a reguirement. Some of the ST5000 features are:

Į



#### ST5000:

 Two shifts - 170 and 850 Hz (others available on custom order) 175 VDC, 60 ma current loop supply 
Motor control autostart with motor relay and outlet 
Built-in AFSK transmit tone generator with narrow-shift CW ID Meter tuning indicator with provision for external tuning scope (RS2100 recommended) ● 2.75" × 8" × 12" ● 9 lbs shipping ● Two-tone blue and beige cabinet

### HAL COMMUNICATIONS, YOUR RTTY COMPANY:

HAL Communications Corp. P.O. Box 365 Urbana, Illinois 61801 (217) 367-7373 - 345

Since 1969, we have been designing and selling RTTY equipment for amateur and commercial use. We can claim many firsts in this business, including the first amateur video display of RTTY (RVD1001 and RVD1002) and the first commercial electronic amateur Baudot keyboard (DKB2010). The HAL people are proud of the equipment they sell and have a lot of experience in interfacing many types of equipment for RTTY and CW. Yes, RTTY can be confusing, but we'll be glad to help you if you give us a call.

## ICOM HF Three Choices—Three Great Radios

#### **IC-720A**

Listen to signals from around the world with a 100 KHz — 30 MHz receiver. Talk with a 160 — 10 meter transceiver — ready to go WARC 79 bands, dual VFO's — split operation. ICOM's DFM (Direct Feed Mixer), passband



tuning, speech compressor, 100 watts, SSB, CW, AM, RTTY (FSK), computer compatible tuning, 12 volt operation, all features standard except CW & AM narrow filters. *ICOM system*<sup>+</sup> accessories are available for a complete station.



ICOM America, Inc., 2112-116th Ave NE, Bellevue, WA 98004 (206)454-8155/3331 Towerwood Drive, Suite 307, Dallas, TX 75234 (214)620-2780, All stated specifications are approximate and subject to change without notice or abligation. All ICOM radios significantly exceed FCC regulations limiting spurious, erritions

## **Red-Hot and Ready to Go**

Anyone who has ever soldered knows that the cord gets in the way. Find freedom with this home-brew cordless iron.

Here's a simple, oneevening project that has proved to be very worthwhile. The end result is an instant portable soldering iron that is heavy enough for most soldering jobs short of antenna and chassis work. Since the tip can be changed from high to low power, the battery life may be extended when only light duty work is involved.

A  $6-1/2'' \times 2'' \times 1-5/8''$ box neatly holds the parts, which consist of two size D nicads, two barrier strips, an on/off switch, a pilot lamp, a replacement soldering gun tip, and a diode to facilitate recharging the batteries. The pilot lamp is a #222 (2.25 V, 0.25 A).


Do use the lamp, as it is a very practical visual voltmeter and will give an indication as to when the battery needs a recharge. The tip still will get hot even if one of the cells is run down, and that can lead to deep discharge of the cell. Besides that, the lamp helps you to see where the solder is supposed to go inside of those dark and mysterious projects. (With 3.5-Ah cells and the tip removed, the thing makes an excellent

14-hour emergency flash-light.)

Without a doubt, there are better ways than the one shown to secure the tip, but this method is adequate and allows the business end of the instrument to get into tight places. If you wish to duplicate this mess, use a convenient length of #12 wire. The two-inch length shown has a voltage drop of about 10 millivolts per leg.

The heavy-duty tip, Wahl #7546, draws 8.5 A at 2.5 volts. The regular tip draws 6.5 A. With that kind of current, it is no surprise to find less than 2.5 V at the tip. The measured voltage is close to 2.1. The batteries fell to 2.25 volts.

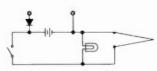With that kind of current, the on/off switch must be a heavy-duty type. The least expensive on/off switch that I could get happened



REPLACEMENT SOLDERING GUN TIP #222 PILOT LAMP SOCKET FOR LAMP ON/OFF SWITCM SIZE D CELLS IAH OR 3.5AH BARRIER STRIP BOX IN4001

Fig. 1.

to be a push-on/push-off type. Since the iron stands by itself, this allows both hands to be used for bringing the work to the iron which is often the most convenient way to do it. With the lamp glowing and the point smoking, you are not likely to go off and leave the thing turned on.

A quick word concerning the batteries is now in order. With 1.2-Ah size D cells, expect about 8 minutes operating time. Allowing 10 seconds to reach operating temperature and another 10 seconds to make the connection, that would



Instant soldering iron.

figure out to be about 25 connections (that's the high-power tip). With 3.5-Ah batteries, the arithmetic says to expect about 73 connections. The lighter tip should give about 23% more operating time.

The batteries may be recharged by means of a suitable current source connected to the second barrier strip. The battery manufacturers normally state on the battery how much current should be used and for how long. The diode is included to ensure that the current is not fed in backwards.

Since this is a cordless iron, there is no cord to use for storing solder. (You do keep a chunk of solder on your regular iron handle or cord, don't you?) The way the solder is stored here ensures an adequate supply and is almost self-feeding.

All of the parts for this project, except the batteries, were purchased new! (Don't faint!) The heavyduty 3-4 Ah nicads are quite expensive if purchased from the regular wholesale outlets, so try to get them from one of the surplus sources.

The unit has proved itself after many hours of reliable operation.

## "DX-traordinary."



### Superior dynamic range, auto. antenna tuner, QSK, dual NB, 2 VFO's, general coverage receiver.

The TS-930S is a superlative, high performance, all-solid state, HF transceiver keyed to the exacting requirements of the DX and contest operator. It covers all Amateur bands from 160 through 10 meters, and incorporates a 150 kHz to 30 MHz general coverage receiver having an excellent dynamic range.

Among its other important features are SSB slope tuning, CW VBT, IF notch filter, CW pitch control, dual digital VFO's, CW full break-in, automatic antenna tuner, and a higher voltage operated solid state final amplifier. It is available with or without the AT-930 automatic antenna tuner built-in.

#### **TS-930S FEATURES:**

### • 160-10 Meters, with 150 kHz-30 MHz

general coverage receiver. Covers all Amateur frequencies from 160-10 meters. Including new WARC bands. on SSB, CW, FSK, and AM. Features 150 kHz-30 MHz general coverage receiver. Separate Amateur band access keys allow speedy band selection. UP/DOWN bandswitch in 1-MHz steps. A new, innovative, quadruple "UP" conversion, digital PLL synthesized circult provides superior frequency accuracy and stability, plus greatly enhanced selectivity

- Excellent receiver dynamic range. Receiver two-tone dynamic range. 100 dB typical (20 meters, 50-kHz spacing, 500 Hz CW bandwidth, at sensitivity of 0.25  $\mu$ v. S/N 10 dB), provides the ultimate in rejection of IM distortion.
- All solid state, 28 volt operated final amplifier.

The final amplifier operates on 28 VDC for lowest IM distortion. Power input rated at 250 W on SSB. CW, and FSK, and at 80 W on AM. Final amplifier protection circuits with cooling fan, SWR/Power meter built-in.

#### • CW full break-in.

CW full break-in circuit uses CMOS logic IC plus reed relay for smooth, quiet operation. Switchable to semi-break-in.

- · Automatic antenna tuner, built-in. Covers Amateur bands 80-10 meters including the new WARC bands. Tuning range automatically pre-selected with band selection to minimize tuning time. "AUTO-THRU" switch on front panel.
- Dual digital VFO's.

10-Hz step dual digital VFO's include band information. Each VFO tunes continuously from band to band. A large, heavy, flywheel type knob is used for improved tuning ease. T.F. Set switch allows fast transmit frequency setting for split-frequency operations. A-B switch for equalizing one VFO frequency to the other. VFO "Lock" switch provided. RIT control for ±9.9 kHz.

Eight memory channels. Stores both frequency and band information. VFO-MEMO switch allows use of each memory as an independent VFO. (the original memory frequency can be recalled at will), or as a fixed frequency. Internal Battery memory back-up, estimated I year

life. (Batteries not Kenwood supplied) • Dual mode noise blanker ("pulse" or "woodpecker"). NB-1, with threshold control, for pulse-type

- noise. NB-2 for longer duration woodpecker" type noise. SSB IF slope tuning.
- Allows independent adjustment of the low and/or high frequency slope of the IF pass-band, for best interference rejection. HIGH/ LOW cut control rotation not affected by selecting USB or LSB modes.
- · CW VBT and pitch controls. CW Variable Bandwidth Tuning control tunes out interfering signals. CW pitch controls shifts IF passband and simultaneously changes the pitch of the beat frequency. A "Narrow/Wide" filter selector switch is provided.
- IF notch filter. 100 kHz IF notch circuit gives deep. sharp. notch, better than -40 dB.
- Audio filter built-in.
- Tuneable, peak-type audio filter for CW. • AC power supply built-in.
- 120, 220, or 240 VAC. switch selected (operates on AC only)

- Fluorescent tube digital display. Six digit readout to 100 Hz (10 Hz modifiable), plus digitalized sub-scale with 20-kHz steps. Separate two digit indication of RIT frequency shift. In CW mode, display indicates the actual carrier frequency of received as well as transmitted signals.
- RF speech processor.
- RF clipper type processor provides higher average "talk-power," improved intelligibility.
- One year limited warranty on parts and labor.

#### Other features:

SSB monitor circuit, 3 step RF attenuator, VOX. and 100-kHz marker.

#### **Optional** accessories:

- AT-930 automatic antenna tuner. · SP-930 external speaker with selectable
- audio filters. • YG-455C-1 (500 Hz) or YG-455CN-1 (250 Hz)
- plug-in CW filters for 455-kHz IF
- YK-88C-1 (500 Hz) CW plug-in filter for 8.83-MHz IF.
- YK-88A-1 (6 kHz) AM plug-in filter for 8.83-MHz IF.
- · SO-1 commercial stability TCXO (temperature compensated crystal oscillator). Requires modifications.
- · MC-60A deluxe desk microphone with
- UP/DOWN switch. pre-amplifier, 8-pin plug TL-922A linear amplifier (not for CW QSK)
- · SM-220 station monitor (not for pan-adapter).
- HS-6, HS-5, HS-4, headphones.

More information on the TS-930S is available from all authorized dealers of Trio-Kenwood Communications, 1111 West Walnut Street, Compton, California 90220.





Specifications and prices are subject to change without notice or obligation.



#### "Top-notch"...VBT, notch, IF shift, wide dynamic range

The TS-830S has every conceivable operating feature built-in for 160-10 meters (including the three new bands). It combines a high dynamic range with variable bandwidth tuning (VBT), IF shift, and an IF notch filter, as well as very sharp filters in the 455-kHz second IF.

#### **TS-830S FEATURES:**

- LSB, USB, and CW on 160-10 meters. including the new 10. 18, and 24-MHz bands Receives WWV on 10 MHz.
- · Wide receiver dynamic range, Junction FETs in the balanced mixer, MOSFET RF amplifier at low level, and dual resonator for each band.
- Variable bandwidth tuning (VBT). Varies IF filter passband width.
- · Notch filter high-Q active circuit in 455-kHz second IF.
- · IF shift (passband tuning)
- · Noise-blanker threshold level control.

- · Puilt-in digital display. (fluorescent tube), with analog dial.
- 6146B final with RF negative feedback. Runs 220 W PEP (SSB)/180 W DC (CW) input on all bands.
- · Built-in RF speech processor.
- · Narrow/wide filter selection on CW.
- SSB monitor circuit.
- · RIT and XIT (transmitter incremental tuning)

#### **Optional accessories:**

- SP-230 external speaker.
- VFO-230 external digital VFO with five memories, digital display.
- VFO-240 external analog VFO.
- AT-230 antenna tuner.
- YG-455C (500 Hz) or YG-455CN (250 Hz) CW filter for 455 kHz IF.
- YK-88C (500 Hz) or YK-88CN (270 Hz) CW filter for 8.83 MHz IF.
- KB-1 deluxe heavyweight knob.

#### "Cents-ational"...IF shift, digital display, narrow-wide filter switch

The TS-530S SSB/CW transceiver covers 160-10 meters using the latest, most advanced

circuit technology, yet at an affordable price.

#### **TS-530S FEATURES:**

- 160-10 meters. LSB, USB, CW. all amateur frequencies. including new 10, 18, and 24 MHz bands. Receives WWV on 10 MHz.
- · IF shift tunes out interfering signals.

- Built-in digital display (six digits. fluorescent tubes), with analog dial
- · Narrow/wide filter selector switch for CW and/or SSB.

-----

- Built-in speech processor, for increased talk power.
- Wide receiver dynamic range. with greater immunity to overload.
- Two 6146B's in final. allows 220W PEP/180 W DC input on all bands.
- Advanced single-conversion PLL. for better stability. improved spurious characteristics.
- · Adjustable noise-blanker, with front panel threshold control.

 RIT/XIT front panel control allows independent fine-tuning of receive or transmit frequencies.

#### **Optional accessories:**

BCEIVER

- · SP-230 external speaker with selectable audio filters.
- VFO-240 remote analog VFO. • VFO-230 remote digital VFO
- AT-230 antenna tuner/SWR/ power meter.
- MC-50 desk microphone
- · KB-1 deluxe VFO knob.
- YK-88C (500 Hz) or YK-88CN
- (270 Hz) CW filter YK-88SN (1.8 kHz) narrow SSB filter



#### The TS-660 "GUAD BANDER" covers 6, 10, 12, 15 meters.

- FM, SSB (USB), CW, and AM
- · Dual digital VFO's
- · Digital display
- IF shift built-in 5 memories with memory scan
- UP/DOWN microphone
- · All-mode squelch
- · Noise blanker
- · CW semi break-in/sidetone . 10 W on SSB, CW, FM;
- 4 W on AM.
- **Optional accessories:** PS-20 power supply
- VOX-4 speech processor/VOX
- SP-120 External speaker
- MB-100 Mobile mount YK-88C. YK-88CN CW filters YK-88A AM filter.
- TRIO-KENWOOD COMMUNICATIONS 1111 West Walnut, Compton, California 90220



## **R-600**

#### "Now hear this"...digital display, easy tuning

The R-600 is an affordably priced, high performance general coverage communica-tions receiver covering 150 kHz to 30 MHz in 30 bands. Use of PLL synthesized circuitry provides maximum ease of operation.

#### **R-600 FEATURES:**

- 150 kHz to 30 MHz continuous coverage. AM, SSB, or CW.
- 30 bands, each 1 MHz wide, for easier tuning. · Five digit frequency display, with 1 kHz resolution
- 6 kHz IF filter for AM (wide), and 2.7 kHz filter for SSB, CW and AM (narrow).
- · Up-conversion PLL circuit, for improved sensitivity, selectivity, and stability.

- Communications type noise blanker eliminates "pulse-type" noise.
- RF Attenuator allows 20 dB attenuation of strong signals.
- Tone control. Front mounted speaker.
- "S" meter, with 1 to 5 SINPO "S" scale, plus standard scale.
- Coaxial and wire antenna terminals. • 100, 120, 220, and 240 VAC, 50/60 Hz. Selector switch on rear panel.
- · Optional 13.8 VDC operation, using DCK-1 cable kit.
- Other features include carrying handle. headphone jack, and record jack.
- Optional accessories for R-600 and R-1000: DCK-1 DC Cable kit. 
   SP-100 External
- Speaker. • HS-6, HS-5, HS-4 Headphones.
- HC-10 Digital World Clock.



High performance, easy tuning, digital display

The R-1000 high performance communications receiver covers 200 kHz to 30 MHz in 30 bands. An up-conversion PLL synthesized circuit provides improved sensitivity, selectivity, and stability.

#### R-1000 FEATURES.

- · Covers 200 kHz to 30 MHz.
- · 30 bands, each 1 MHz wide.
- Five-digit frequency display with 1-kHz resolution and analog dial with precise gear dial mechanism.
- · Built-in 12-hour quartz digital clock/timer. • RF step attenuator.
- Three IF filters for optimum AM, SSB, CW.
- Effective noise blanker.
  Tone control.
  Built-in 4-inch speaker.
  Dimmer switch.
- · Wire and coax antenna terminals.
- Voltage selector for 100, 120, 220, and 240 VAC. Operates on 13.8 VDC with optional DCK-1 kit.



**TS-130SE** "Small talk"...IF shift,

#### Processor, N/W switch, affordable.

A compact, all solid-state HF SSB/CW transceiver for mobile or fixed base station, covering 3.5 to 29.7 MHz.

- TS-130SE FEATURES:
- 80-10 meters including the new 10, 18, and 24 MHz bands. Receives WWV on 10 MHz.
- TS-130SE runs 200 W PEP/160 W DC input on 80-15 meters, 160 W PEP/140 W DC on 12 and 10 meters. TS-130V version at 25 W PEP/20 W DC, all bands,
- also available. · Digital display, built-in.
- IF shift circuit.
- · Speech Processor, built in.
- · Narrow/wide filter selection on CW and SSB with optional filters.
- Automatic SSB mode selection (LSB on 40 meters and below, USB on 30 meters and up). SSB reverse switch provided.

- · RF attenuator, built-in.
- Effective noise blanker.
- · Final amplifier protection circuit assures maximum reliability. Output power is reduced if abnormal operating conditions occur. For very severe operations, optional cooling fan, FA-4, is available.
- Dimensions: 3-3/4 H x 9-1/2 W x 11-9/16 D (inches). Weight: 12.3 lbs.
- · Other features: VOX, CW semi break-in with sidetone, one fixed channel, and 25 kHz marker.

TRIO-KENWOOD COMMUNICATIONS 1111 West Walnut, Compton, California 90220



**Optional DFC-230 Digital Frequency Controller** Frequency control in 20-Hz steps with UP/DOWN microphone (supplied with DFC-230). Four memories and digital display. (Also operates with TS-120S, TS530S, and TS-830S.)

#### **Optional accessories:**

- PS-30 matching power supply (TS-130SE).
- KPS-21 power supply (TS-130SE).
- PS-20 power supply (TS-130V).
- SP-120 external speaker.
- VFO-120 remote VFO
- FA-4 fan unit (TS-130SE)
- YK-88C (500 Hz) and YK-88CN
- (270 Hz) CW filters YK-88SN (1.8 kHz) narrow SSB . filter
- AT-130 antenna tuner.
- MB-100 mobile mounting
- bracket.

## **TR-2500**

#### size. smaller

The TR-2500 is a compact 2 meter FM handheld transceiver with every conceivable operating feature.

#### **TR-2500 FEATURES:**

- Weighs 540 g, (1.2 lbs). 66 (2-5/8) W x 168 (6-5/8) H x 40 (1-5/8) D, mm (inches)
- LCD digital frequency readout.
- . Ten memories includes "MO" for non-standard split repeaters.
- Lithium battery memory back-up. built-in, (est. 5 year life). Memory scan.
- Programmable automatic band scan, and upper/lower scan limits; 5-kHz steps or larger.
- · Repeater reverse operation. • 2.5 W or 300 mW RF output. (H1/LOW power switch).
- · Built-in tunable (with variable resistor) sub-tone encoder.
- · Bullt-in 16-key autopatch encoder.
- · Slide-lock battery pack.
- · Keyboard frequency selection.
- . Covers 143.900 to 148.995 MHz.

## TR-7950/7930

#### Big LCD, Big 45 W, Big 21 memories, Compact.

Outstanding features providing maximum ease of operation include a large, easy-to-read LCD display, 21 multi-function memories, a choice of 45 watts (TR-7950) or 25 watts (TR-7930), and the use of microprocessor technology throughout.

#### TR-7950/TR-7930 FEATURES:

- · New, large, easy-to-read LCD digital display. Easy to read in direct sunlight or dark (backlighted). Displays TX/RX fre-quencies, memory channel. repeater offset, sub-tone number, scan, and memory scan lock-out.
- · 21 new multi-function memory channels. Stores frequency,

sub-tone channels. Memory pairs for non-standard splits. Lighted memory selector knob. 1 position.

KENWOOC

TR-2500

- · Lithium battery memory back-up. (Est. 5 yr. life.)
- HI/LOW power switch for reduction to 5 watts.
- Automatic offset. Pre-programmed for simplex or ±600 kHz offset, in accordance with the 2 meter band plan. "OS" key for manual change in offset.
- May be programmed in any memory.
- channels during scan.
- · Programmable band scan width. · Center stop circuit for band
- Scan resume selectable. Selectable automatic time resumescan, or carrier operated
  - Scan start/stop from up/down

- AC charger/supply for operation while charging.
- · Battery status indicator.
- Complete with flexible antenna, 400 mAH Ni-Cd battery, and AC charger.

#### **Optional accessories:**

- ST-2 Base station power supply/ charger (approx. 1 hr.) • MS-1 13.8 VDC mobile stand/
- charger/power supply.
- VB-2530 2-M 25 W RF power amps., (TR-2500 only)
- TU-1 Programmable CTCSS encoder (TR-2500 only).
- TU-35B Programmable CTCSS encoder (mounts inside
- · PB-25H Heavy-duty 490 mAH Ni-Cd battery pack.
- DC-25 13.8 VDC adapter.
- · BT-1 Battery case for AA
- manganese/alkaline cells.
- SMC-25 Speaker microphone. · LH-2 Deluxe leather case.
- · Programmable priority alert.
- · Programmable memory scan lock-out. Skips selected memory
- scan, with indicator.
- resume-scan.
- microphone.


- · BH-2A Belt hook. • RA-3 2 m 3/8 & telescoping antenna (for TR-2500).
  - · WS-I Wrist strap.
- EP-1 Earphone.
- · Programmable three sub-tone channels with optional TU-79 unit (encoder).
- · Built-in 16-key autopatch encoder. with monitor (Audible tones)
- Front panel keyboard control.
- Covers 142.000-148.995 MHz in 5-kHz steps
- · Repeater reverse switch. (Locking)
- · "Beeper" amplified through speaker.
- · Compact lightweight design.
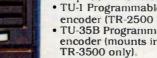
#### **Optional accessories:**

- TU-79 three frequency tone unit.
- KPS-12 fixed-station power supply for TR-7950.
- KPS-7A fixed-station power supply for TR-7930.
- SP-40 compact mobile speaker.




TRIO-KENWOOD COMMUNICATIONS 1111 West Walnut, Compton, California 90220









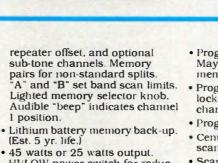

đ

etitast p

MR



· Six memories. On FM, memories

offset. All six memories may be

• Internal battery memory back-up, using 9 V Ni-Cd battery, (not

KENWOOD supplied). Memories are retained approx. 24 hours,

1-5 for simplex or ±600 kHz offset, using OFFSET switch, Memory 6 for non-standard

simplex, any mode.

• Memory scan.

TR-7730

### All mode (FM/SSB/CW) 25 watts, plus ... !!!

The TR-9130 is a powerful, yet compact, 25 watt FM/USB/LSB/ CW transceiver. Available with a 16-key autopatch UP/DOWN microphone (MC-46), or a basic UP/DOWN microphone,

#### **TR-9130 FEATURES:**

- · 25 Watts RF output on all modes, (FM/SSB/CW),
- FM/USB/LSB/CW all mode. Selectable tuning steps of 100-Hz, 1-kHz, 5-kHz, 10-kHz.

## **TR-7730**

#### Dyna-"mite"... miniaturized, 5 memories, memory/ band scan.

The TR-7730 is an incredibly compact, reasonably priced, 25 watt, 2 meter FM mobile transceiver, with five memories, memory scan, automatic band scan, plus other convenient operating features. It is available with a 16-key autopatch UP/DOWN microphone, (MC-46), or with a basic UP/DOWN microphone.

#### **TR-7730 FEATURES:**

- Dimensions: 5-3/4 W x 2 H x 7-3/4 D, inches. Weighs 3.3 lbs.
- · Extended frequency coverage, 143.900-148.995 MHz, in 5 or 10-kHz steps.

adequate for the typical move

- · 25 watts RF output power, with HI/LOW power switch. • Five memories. Simplex or
- repeater operation, with transmit offset switch. The 5th memory stores receive and transmit frequencies independently, for non-standard splits. Memory back-up terminal on rear panel.
- · Memory scan, plus automatic band scan. Locks on busy channel, resumes when signals disappear, or when scan switch is pressed. Scan HOLD

from base to mobile. External back-up terminal on the rear. Automatic band scan.

- · Dual digital VFO's.
- Transmit frequency tuning for OSCAR operations.
- Squelch circuit for FM/SSB/CW.
- · Repeater reverse switch.
- · Tone switch.
- · CW semi break-in; sidetone.
- Compact size and lightweight.
- Covers 143.9 to 148.9999 MHz.
- · High performance noise blanker.



9500

· Covers 430-440 MHz. in steps of 100-Hz, 1-kHz, 5-kHz, 25-kHz

CW-FM Hi-10 W, Low-1 W.

· Automatic band/memory scan.

Search of selected 10-kHz seg-

• HI/LOW power switch. 25 or 5

• RF gain control. • RIT circuit.

70 CM SSB/CW/FM

ments on SSB/CW · 6 memory channels.

watts on FM or CW

**Optional accessories:** 

(TR-9500 only).

back-up.

• KPS-7A AC power supply.

• PS-20 AC power supply

· BO-9A system base with

memory back-up supply.

TK-1 AC adapter for memory

SP-120 external speaker.

transceiver

or 1-MHz.

**SSB 10 W** 

cancels scan.UP/DOWN manual scan on microphone, either version. Four digit LED frequency

or PTT switch on microphone

- display.
- S/RF bar meter. LED indicators for BUSY, ON-AIR, REPEATER operation
- Tone switch for internal tone encoder (not Kenwood supplied).
- · Offset switch ±600 kHz, or simplex. Fifth memory for nonstandard offset.

#### **Optional Accessories:**

- MC-46 16-key autopatch UP/ DOWN microphone
- SP-40 Compact mobile speaker.
- **KPS-7A** Fixed station power supply.



mobile rig

- Covers 440-450 MHz, in 25-kHz steps, with two VFOs. • Transmit offset switch for
- ±5 MHz. Non-standard offset uses fifth memory.
- · HI/LOW power switch selects 10 or 1 watt RF output.
- Similar to TR-7730 in other features, including five memories, memory scan automatic band scan, UP/ DOWN manual scan, four digit display. S/RF bar meter, LED indicators, tone switch, and same optional accessories.
- Basic UP/DOWN microphone supplied with unit.

KENWOOD 2m FM TRANSCEIVER

TRIO-KENWOOD COMMUNICATIONS 1111 West Walnut, Compton, California 90220



## **TL-922**

#### Maximum legal power on 160-15 meters

The TL-922A linear amplifier provides maximum legal power on the 160-15 meter Amateur bands.

#### **TL-922A FEATURES:**

· 2000 W PEP (SSB)/1000 W DC (CW, RTTY) input power on

160, 80, 40, 20, and 15 meters. with 80 W drive

- Excellent IMD characteristics.
   Pair of EIMAC 3-500Z highperformance transmitting tubes
- Safety protection.
  Blower with automatic turnoffdelay circuit.
- · Variable threshold level type ALC

· Two meters, one indicating plate current, and the other indicating grid current, relative RF output, and high voltage.

ACCESSOR



### SM-220

**High-performance** oscilloscope for various monitoring functions

The SM-220 Station Monitor provides a variety of waveformobserving capabilities, and an optional pan display.

#### **SM-220 FEATURES:**

- Monitors transmitted SSB and CW waveforms from 1.8 to 150 MHz.
- · Monitors signal waveforms in receiver's IF stage.
- · Functions as high sensitivity. wide-frequency-range (up to 10 MHz) oscilloscope
- Tests linearity of linear amplifiers (provides trapezoid pattern)
- Allows observation of RTTY tuning points (cross pattern). • Built-in two-tone (1000-Hz and
- 1575-Hz) generator. Expandable to pan-display
- capability for observing the number and amplitude of stations within a switchable ±20 kHz/±100 kHz bandwidth.

#### **Optional accessories:**

- · BS-8 pan-display module for TS-180S, TS-830S, and TS-820 Series.
- BS-5 pan-display module for TS-520 Series.

A wide selection of optional accessories is offered for optimum operating flexibility. In addition to the optional items listed with each piece of equipment described in this catalog, the following accessories are also available:



(FCC Part 68 registered)

**PC-1A Phone Patch** PC-1A Phone Patch with hybrid circuit and VU meter for null and audio gain measurements.



BO-9A System Base (for TR-9130, TR-9500. TR-9000) With memory backup supply. speaker sound port, ST-B switch, power switch, headphone jack.




VB-2530 25 W RF Power Amplifier (for TR-2500). BNC-BNC cable, and mounting bracket supplied.

#### DM-81 Dip Meter

The DM-81 dip meter is highly accurate and features, in addition to the traditional inductive-coupling technique, capacitive coupling for measuring metal-enclosed coils and toroidal coils.
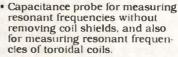
#### **DM-81 FEATURES:**

• Measuring 700 kHz-250 MHz in • MC-60N4 Deluxe desk microseven bands.



- Built-in storage compartment for colls, and accessories.
- · All solid-state and built-in battery
- HC-25U and FT-243 sockets for checking crystals and marker-generator function.
- · Amplitude modulation.
- function
- transmitted signals.



#### **HC-10 Digital Quartz Clock**

The HC-10 digital world quartz clock with dual 24-hour display shows local time and the time in 10 preprogrammed plus two programmable time zones.

#### MICROPHONES:

- MC-60A Deluxe desk microphone with UP/DOWN switch. pre-amplifier. 50 kg/500g, 8-pin. Adapter cords PG-4A (4-pin). PG-4B (6-pin), available. PG-4C, supplied with MC-60A.
- phone. 50 kΩ/500Ω, 4-pin. (UP/

- DOWN switch, pre-amp. (not included). PG-4C available.
- MC-50 Desk microphone, 50 k/ 500Ω, 4-pin.
- MC-46 16-key autopatch UP/ DOWN microphone, 6-pin.
- · MC-42S Hand microphone with UP/DOWN switch, 5000, 8-pin.
- · MC-30S Hand microphone, 500Ω, noise-cancelling, 4-pin. • MC-35S Hand microphone.
- 50 kΩ, noise-cancelling, 4-pin. Microphone Plug Adapters:
- MJ-48 (4-pin microphone to 8-pin transceiver).
- MJ-84 (8-pin microphone to 4-pin transceiver)
- MJ-86 (8-pin microphone to 6-pin transceiver). HEADPHONES:
- HS-5 Deluxe headphones.
  - · HS-6 Lightweight headphones.
  - HS-4 Standard headphones **GENERAL PURPOSE AC POWER**
- SUPPLIES:
- KPS-7A.13.8 VDC, 7A intermittent • KPS-12 13.8 VDC. 12A
- intermittent. KPS-21 13.8 VDC, 21A
- intermittent.
- **OTHER ACCESSORIES:**
- SP-40 Compact external mobile speaker.
- RD-20 Dummy load, 502, DC-500 MHz, 50 W intermittent, 20 W continuous.
- PG-3A DC line noise filter for mobile

#### SERVICE MANUALS:

· Available for most transceivers. receivers, and major accessories.

NOTE: Prices and specifications of all Trio-Kenwood products are subject to change without prior notice or obligation.



#### · FET for good sensitivity. Absorption frequency meter · Earphone for monitoring



## **Cutting Current to Size**

Measuring large ac currents can be difficult unless you know a trick or two. W7CRY explains how.

Larry T. Wier W7CRY 1068 149 Pl. SE Bellevue WA 98007

Ave you ever tried to measure large ac currents and found your trusty VOM somewhat short? Welcome to the club. I was stuck with the problem of finding the current used by an electric hot water heater but no way of measuring it. I also found my wallet short after letting my fingers walk through several instrument catalogs. Several hours of thrashing around the workbench yielded a simple and, best of all, inexpensive way of measuring large ac currents using an ordinary 88-mH choke, a trick or two, and Ohm's law.

#### Theory

Perhaps a little transformer theory should be covered before Ohm's law and the tricks are applied.

By definition, a transformer is exactly what its name implies: It transforms one voltage (or current) to a different level. The major differences between a voltage transformer and current transformer are the turns ratio and power-transfer characteristics. Depending on design, the voltage transformer has a low turns ratio, i.e., approximately 19 to 1 (118/6.3) for a filament transformer. The current transformer, on the other hand, has a turns ratio from around 300 to greater than 10,000 to 1, depending on the burden (load) on the secondary.

The current transformer always has the burden specified along with the current ratio. For example, a typical 50-Amp to 5-Amp current transformer will require a burden of .25 Ohms. If the secondary burden were to open or be removed, the transformer would be destroyed because the voltage developed across the resulting open circuit would cause arcing within the windings.

An additional consideration is that the current transformer should not introduce significant changes in the circuit being measured.

#### Hybrid Current Transformer Design

Fig. 1 shows the basic technique in utilizing the 88-mH choke as a current transformer. The term hybrid is used because in using the choke, a "halfway in-between" turns ratio will result. The approximate number of turns is determined by measuring the resistance of the coil, finding



The almost-completed ac current transformer. The transformer is mounted on a piece of styrofoam<sup>TM</sup> which is

glued to the box. Contact or rubber cement can be used for

both the foam and transformer. The signal wires (not shown)

can be routed out through any of the knockouts.

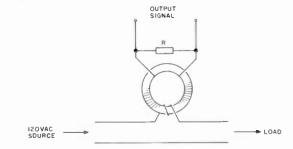


Fig. 1. Basic hybrid current transformer.

108 73 Magazine • December, 1982

# More Transceiver

Contest or rare DXthe world is waiting to hear from a new breed of HF operators who'll have the power of a microcomputer at their instant command. The Heath SS-9000 signals a new era in Amateur Radio, full of exciting promise. Challenge. And opportunity...

#### MORE WORLD HORIZONS

In the SS-9000, we met a major design goal: provide the highesttech, most versat le transceiver possible. Our objective? Nothing less than setting the pace for transceiver performance in the next decade. And transforming the state-of-the-art in amateur telecommunications potential.

As a microprocessor-based, fully-synthesized nine band Transceiver, your SS-9000 leads the new revolution in computerenhanced hamshacks – with an array of applications yet to be



discovered. At your command under direct or RS-232 control, it could break all known records for station performance.

#### MORE MICRO CONTROL

Harness the SS-9000 to a video terminal, ASCII teletype or home computer. Commands are available to select, display and change all 27 operating and memory frequencies, assign and toggle T/R/Tr status on the dual readout, and freely manipulate the three stored frequencies on each band, with full diagnostic error-prompting. Keyboard command also allows you to set and switch the band, mode, passband shift, baud and scan rates, plus switch to one of five antennas automatically.

#### MORE POWER AS A PAIR

The FS-9000 AC Power Supply has an incabinet speaker and two digital 12 or 24-hour clocks. Both units benefit from thermal and over-current protection with high VSWR cutback. Test-prove the assembled System 9000. Get a hands-on tryout at your nearby

#### MORE DETAILS IN CATALOG

Heathkit Electronic Center.\*



10 10

-

000

FREE! For complete details and specs, get a copy of the latest Heathkit calalog. Write: Heath Company, Dept. 311-964, Benton Harbor, MI 49022

Company

## There's more for the Ham at Heath

19 0107 1 192856

0

<sup>•</sup>Units of Veritechnology Electronics Corporatic in the U.S., a subsidiary of Zenith Radio Corp. the wire size, and, from a wire table, finding the resistance per foot. By taking the average diameter of the donut and average cross section, a rough turns count can be calculated.

For those not willing to take the time to play with the math, a quick test can be found in the calibration section. If the ratio is found to be in excess of about 300, the choke is a good candidate.

Apparently, there are several so-called surplus 88-mH-type chokes. I found some with and some without center tap. I have also found some with two separate windings. These can be used if the windings are connected in series adding. Even though the choke defined here was intended for the audio frequencies, it works well at 60 Hz if the power levels are kept low.

#### Construction

The only construction required is covering the existing windings with tape. Once the value of R is determined, it can be soldered to the windings and taped to the body of the coil or mounted as shown in Fig. 3. The signal wires are attached across the resistor and routed where necessary. Wire length is not critical, but wires should be routed away from highnoise areas.

#### Calibration

Fig. 2 shows the test setup used to calibrate the current transformer. It is not necessary to use the 120-volt, 60-Hz line to do the calibration. As shown, a low-voltage, high-current voltage transformer with an adjustable input is the quickest and safest.

For calibration purposes, R can be a quality pot. The 100-Ohm resistor is used to prevent shorting the transformer, but is part of the burden. The source and load will depend on what is 110 73 Magazine • December, 1982

available. Use the following steps to calibrate the transformer:

1) Make sure that there are ten complete turns of #18 insulated wire wound as shown in Fig. 2.

2) Adjust the load for 10.0 Ohms.

3) Adjust the voltage to the load for 10.0 V ac.


4) Adjust R (1k pot) for an even value of voltage preferably 0.1 V ac. Remove power.

(If 0.1 volt was not obtainable, replace R with a 2k pot. If the measured voltage was higher than 0.1 V ac, set the value to any even value above 0.1 V, e.g., 0.3 V ac.

(The current ratio is calculated as follows: I = E/R, where E was set to 10.0 V ac and R was set to 10.0 Ohms. Therefore,  $I = 10 \text{ V}/10\Omega = 1$ Amp.

(Then 1 Amp through 10 turns equals 10 Amp/turns which is also equal to 10 Amps with 1 turn through the transformer. With one turn in the primary and the measured value across R of 0.1 V ac, the ratio becomes 10 to 0.1. By Ohm's law, E is equal to I times R, and if R is held constant, then E must be proportional to I.

(What this boils down to is that the current through the transformer will generate a proportional voltage across R as long as R stays constant. If the ratio has been set correctly, adjusting the load to 1.0 Ohms and again adjusting the voltage across the load to 10.0 V ac, a value of 1 V ac should be measured across R.)

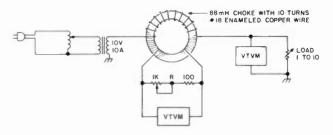



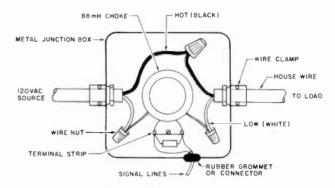


Fig. 3. Mounting fixture.

5) Determine the wattage for R by measuring the value of R and calculating as follows:  $P_{Watts} = E^2/R$ . Generally, a ½-Watt resistor will be more than sufficient. Replace the pot and 100-Ohm resistor with a fixed value equal to the combination of the two in series.

#### Application

Obviously, this combination can be used with any current range. It is limited only by the size of wire capable of being wound (1 turn) through the donut. Note that at least one turn is necessary to excite the transformer core. Passing the wire through the hole is not sufficient. Practically speaking, a #5 (solid enameled) wire is about the maximum-size wire which can be formed into one turn around the donut. This

limits the upper current range to around 50 Amps.

The number of turns wound on the current transformer will depend on the current range to be measured and wire size. As an example, suppose a motor rated at 15 Amps (running) is to be monitored. We know from our calibration that 10 Amps gave us 0.1 V ac across R. Therefore, one turn of #12 wire through the donut should give us 0.15 V ac across R. The #12 was chosen because it is the smallest size generally used for motors in this range.

Another example is the case where only 1 Amp is to be measured. In this case, the wire size (assumed to be #14) is too large to pass a large number of turns through the donut. If you can assume also that nothing larger than approximately 5 Amps will be

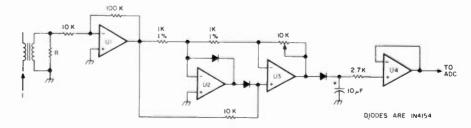


Fig. 4. Precision rectifier/buffer.

# The ultimate team...the new Drake Twins



### The URIA and RIA offer performance and versatility for those who demand the ultimate!

### **TR7A Transceiver**

• CONTINUOUS FREQUENCY COVERAGE — 1.5 to 30 MHz full receive coverage. The optional AUX7 provides 0 to 1.5 MHz receive plus transmit coverage of 1.8 to 30 MHz, for future Amateur bands, MARS, Embassy, Government or Commercial frequencies (proper authorization required).

• Full Passband Tuning (PBT) enhances use of high rejection 8-pole crystal filters.

New! Both 2.3 kHz ssb and 500 Hz cw crystal filters, and 9 kHz a-m selectivity are standard, plus provisions for two additional filters. These 8-pole crystal filters in conjunction with careful mechanical/electrical design result in realizable ultimate rejection in excess of 100 dB.

New! The very effective NB7 Noise Blanker is now standard. New! Built in lightning protection avoids damage to solid-state components from lightning induced transients.

New! Mic audio available on rear panel to facilitate phone patch connection.

• State-of-the-art design combining solid-state PA, up-conversion, high-level double balanced 1st mixer and frequency synthesis provided a no tune-up, broadband, high dynamic range transceiver.

### **R7A Receiver**

• CONTINUOUS NO COMPROMISE 0 to 30 MHz frequency coverage.

- Full passband tuning (PBT).
- New! NB7A Noise Blanker supplied as standard.

• State-of-the-Art features of the TR7A, plus added flexibility with a low noise 10 dB rf amplifier.


New! Standard ultimate selectivity choices include the supplied 2.3 kHz ssb and 500 Hz cw crystal filters, and 9 kHz a-m selectivity. Capability for three accessory crystal filters plus the two supplied, including 300 Hz, 1.8 kHz, 4 kHz, and 6 kHz. The 4 kHz filter, when used with the R7A's Synchro-Phase a-m detector, provides a-m reception with greater frequency response within a narrower bandwidth than conventional a-m detection, and sideband selection to minimize interference potential.

• Front panel pushbutton control of rf preamp, a-m/ssb detector, speaker ON/OFF switch, i-f notch filter, reference-derived calibrator signal, three agc release times (plus AGC OFF), integral 150 MHz frequency counter/digital readout for external use, and Receiver Incremental Tuning (RIT).
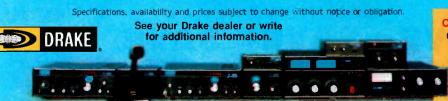
### The "Twins" System

• FREQUENCY FLEXIBILITY. The TR7A/R7A combination offers the operator, particularly the DX'er or Contester, frequency control agility not available in any other system. The "Twins" offer the only system capable of no-compromise DSR (Dual Simultaneous Receive). Most transceivers allow some external receiver control, but the "Twins" provide instant transfer of transmit frequency control to the R7A VFO. The operator can listen to either or both receiver's audio, and instantly determine his transmitting frequency by appropriate use of the TR7A's RCT control (Receiver Controlled Transmit). DSR is implemented by mixing the two audio signals in the R7A

• ALTERNATE ANTENNA CAPABILITY. The R7A's Antenna Power Splitter enhances the DSR feature by allowing the use of an additional antenna (ALTERNATE) besides the MAIN antenna connected to the TR7A (the transmitting antenna). All possible splits between the two antennas and the two system receivers are possible.



### COMING SOON: New RV75 Synthesized VFO Compatible with TR5 and 7-Line Xcvrs/Rcvrs

• Frequency Synthesized for crystal-controlled stability • VRTO (Variable Rate Tuning Oscillator\*) adjusts tuning rate as function of tuning speed. • Resolution to 10 Hz • Three programmable fixed frequencies for MARS. etc. • Split or Transceive operation with main transceiver PTO or RV75

\* Patent pending

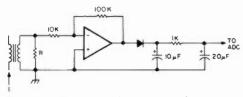


Fig. 5. Half-wave rectifier.

passed through the donut, then ten turns of #18 (solid enameled) will generate 0.1 V ac across R. In most cases, the number of turns will be determined by the measurement requirements.

### Installation

According to most electrical codes, any splices of power lines must be located in a box. An outlet or junction box will work equally well. The transformer should not touch the metal box, and make sure that only the circuit being measured is in the box. It is best to use the low side (white wire) because the voltage between the low side and ground will not exceed the voltage rating of the enameled wire.

When measuring a 220-V ac line it will be necessary to use either of the two hot (red or blue) lines. In this case, the donut should have at least one layer of electrical (plastic) tape between the two sets of windings. Fig. 3 shows one method of mounting the donut and resistor R. Any method which meets your local code requirements will work.

### Use

Now that you have a current transformer, how can it be used? The answer to that depends on why it was built. The easiest use of the current transformer is with an ac voltmeter. In my case, it is being used in a computer-controlled power system. Since a computer does not know ac from dc (or much else) the ac signal across R must be signal conditioned. There are many ways to signal-condition, but the method I chose was determined by the analog-to-digital converter (ADC) used with my computer. It has ±15 V dc available, so that the use of operational amplifiers seemed to be the best solution.

Fig. 4 is an example of how the ac signal is conditioned from ac to dc for the ADC. It is beyond the scope of this article to dissect the operation of Fig. 4 except to note that U2 and U3 form an absolute value (precision-rectifier) circuit. U1 is an inverting amplifier and U4 is used as a unity-gain buffer. U1 and U4 are in one LM747 and U2 and U3 are in another. Any generalpurpose operational amplifier will work. (More information on this particular absolute-value circuit may be found in the November 8, 1979, issue of *Electronic Design*, page 94.)

A simple amplifier and diode arrangement also will work if accuracy and response time are unimportant. Fig. 5 is the method used in this case.

### Summary

No matter what the requirement, a simple arrangement such as described here will provide a reasonably accurate measurement of ac line current. Sources of 88-mH chokes are found in the back of most electronic magazines and cost around \$3.00.

Now I need to look into a method of measuring the gas pressures in my heat pump!



# At Last.

A microthin, synthesized, programmable, sub-audible tone encoder that fits inside the ICOM IC-2AT.

Need we say more?

\$**29**95

SEND



426 West Taft Avenue, Orange, CA 92667 800/854-0547 California: 714/998-3021



# Santa's Gone Soft!



# With Help From Instant Software

### **BUSINESS AND APPLICATIONS**

Electronic Breadboard 32K, Mod I &	
III, disk	\$59.95
Electronic Breadboard 16K, Mod I &	
III, tape	\$49.95
Electronic Breadboard 32K, Apple,	
disk	\$59.95
Easy Calc 48K, Mod III only, disk	\$49.95
Easy Calc 48K, Mod I only, disk	\$49.95
Personal Bill Paying 16K, Mod I & III,	
tape	\$14.95
Master Directory 32K, Mod I only,	
disk	\$29.95
Business Analysis 32K, Mod I & III,	
disk	\$99.95
Business Analysis 32K, Mod I & III,	
tape	\$75.00
Scriptr 48K, Mod I only, Disk	\$34.95
ATION	
Typing Teacher 16K, Mod I & III, tane	\$17.95
	W11.00
	\$14.95
	\$19.95
	010.00
	\$49.95
Geography Explorer Mid East 22K	D43.90
	III, disk Electronic Breadboard 16K, Mod I & III, tape Electronic Breadboard 32K, Apple, disk Easy Calc 48K, Mod II only, disk Easy Calc 48K, Mod I only, disk Personal Bill Paying 16K, Mod I & III, tape Master Directory 32K, Mod I only, disk Business Analysis 32K, Mod I & III, disk Business Analysis 32K, Mod I & III, disk Business Analysis 32K, Mod I & III, tape Scriptr 48K, Mod I only, Disk ATION Typing Teacher 16K, Mod I & III, tape Video Speed Reading 16K, Mod I & III, tape Triangle Trig 16K, Mod I & III, tape Geography Explorer: USA 32K, Mod I & III, tape

0099 <b>R</b>	Typing Teacher 16K, Mod I & III, tape	\$17.95
0100R	Video Speed Reading 16K, Mod I &	
	III, tape	\$14.95
0309 <b>R</b>	Trlangle Trig 16K, Mod I & III, tape	\$19.95
0071RD	Geography Explorer: USA 32K, Mod I	
	& III, disk	\$49.95
0276RD	Geography Explorer: Mid East, 32K,	
	Mod I & III, disk	\$49.95
0111R	Word Watch 16K. Mod I & III, tape	\$14.95
0257R	Math Master 16K, Mod I & III, tape	\$17.95
0127R	Surveyors Apprentice 16K, Mod I & III,	
	tape	\$14.95

### GAMES

0332R 0017R	Space Shuttle 16K, Mod I & III, tape Air Flight Simulation 16K, Mod I & III,	\$19.95
	tape	\$14.95
0148A	Air Flight Simulation 16K, Apple, tape	\$14.95
0159R	Jet Fighter Pilot 16K, Mod I & III, tape	\$14.95
0329AD	Jet Fighter Pilot 32K, Apple, disk	\$24.95
0223R	Cosmic Patrol 16K, Mod I & III, tape	\$19.95
0224RD	Cosmic Patrol 16K, Mod I & III, disk	\$24.95
0237R	Danger in Orbit 16K, Mod I & III, tape	\$19.95
0247RD	Danger in Orbit 16K, Mod I & III, disk	\$24.95
0051R	Ball Turret Gunner 16K, Mod I & III,	
	tape	\$14.95
0240R	Allen Attack Force 16K, Mod I & III,	
	tape	\$14.95
0171R	Flight Path 16K, Mod I & III, tape	\$14.95
0043R	Santa Paravia 16K, Mod I & III, tape	\$14.95
0229AD	Santa Paravla 48K, Apple, disk	\$24.95
0273TI	Santa Paravia 16K, TI 99/4, tape	\$14.95
0174A	Santa Paravia 48K, Apple tape	\$14.95
0312R	Swamp War 16K, Mod I & III, tape	\$14.95
0141R	Battleground 16K, Mod I & III, tape	\$14.95
0378RD	Master Reversi 16K, Mod I only, disk	\$24.95
0117R	Night Flight 16K, Mod I & III, tape	\$14.95
0183A	Skybombers III 32K, Apple, tape	\$14.95
0271AD	Skybombers II 32K, Apple, disk	\$24.95
5020RC	Tower of Fear 16K, Color Computer,	
	tape	\$19.95
0084R	Music Master 4K, Mod I & III, tape	\$14.95
0106R	Air Mail Pilot 16K, Mod I & III, tape	\$14.95
0205RD	Flying Circus 32K, Mod I only, disk	\$39.95
0163AD	Paddle Fun 32K, Apple, disk	\$19.95

	tape	\$14.95
0325RD	Mission: Mud 32K, Mod I & III, disk	\$19.95
0387RD	Sparrow Commander 32K, Mod I & III,	
	disk	\$19.95
0386RD	Kitchen Sink 32K, Mod I & III, disk	\$19.95
0161AD	Apple Fun 32K, Apple, disk	\$19.95
UTILIT	IES	
0230R	TLDIS 16K, Mod I & III, tape	\$19.95
0231RD	DLDIS 32K, Mod I only, disk	\$24.95
5700RD	Super>>Terminal 32K, Mod I & III,	
	disk	\$95.00
5003R	Ultra-Mon 16K, Mod I & III, tape	\$24.95
0232R	The Disassembler 16K, Mod I & III,	
	tape	\$14.95

House of 30 Gables 16K, Mod I & III,

0219R

### TO ORDER:

Disk Scope 32K, Mod I only, disk

TRS-80 Tests 16K, Mod I only, tape

\$14.95

\$24.95

\$14 95

See your local Instant Software dealer or call toll-free 1-800-258-5473 Dept. A-65 In New Hampshire 1-603-924-9471 Dept. A-65

> Mon.-Fri. 8:00 am-4:30 pm E.S.T. Include \$2.50 for Shipping & Handling

\*TRS-80 is a trademark of Radio Shack a division of Tandy Corporation

\*\* APPLE is a trademark of Apple Computer Inc.

Instant So Peterborough, N.H. 03458 USA A subsidiary of Wayne Green Inc.

114 73 Magazine • December, 1982

PRICES SUBJECT TO CHANGE

tape

0139RD

0184R

				. 1
	)a)	CIQ	<b>JNC</b>	
		_		-
	ZCCI	0	NK'	
Mission	N C O N P	. C.	lotorf:	
Micropro	6845	12.95	OAC-0800	3.99
1791 34 95	6850	4 4 9	IN \$8250	14.90
21LO2 1.49 2112 1.65	8085A 8212	8.95	MM58167 TMS9900	12.75 29.95
2516 4.75	8214	3 95	TR16028	2.49
2532 7 95 2651 12 95	8216 8224	2.75	SC-01 ZBOA-CPU	55.00 7.95
4044L-2 2.49	8226	2 7 9	ZBOACTC	7.49
6502 8 99 6800 6.99	8228	4 4 9 6 9 5	Z80ADart Z80API0	19.95 7.49
6802 11 95	8255	6 4 9	ZBOASIO	17.95
6809 1995 6821 4.95	AY5-1013A AY5-2376	4 95 12 39	28603 28671	74.95 29.95
				-
1 Amp TO-		-	-	
PART #	_	-	25-99 10	
7805 (LM340		35	.75	.65
7812 (LM340 7815 (LM340		35 35	.75 .75	.65 .65
7815 (LM340		35	.75	.65
Linear	ntegra	ted .97	MC3 302	τs <sub>90</sub>
8038 3.95 LF351 75	LM393	.97	MC1458	.59
LF353 129	LM741-8	35	MC1514	1 39
LF357 139 LM301 45	LM741-14 LM747	35 77	NE555 NE556	.45
LM307 49	LM748	49	NE565	1 25
LM311 95 LM318 1.75	LM1310 LM1458	1 69 69	NE5534 NE5538	1 99
LM324 90	LM1800	2 4 9	SSM2010	7.50
LM339 79 LM358 .90	LM1818 LM1889	349 299	SSM2020 SSM2030	7.50 7.50
LM377 249	LM2900	69	SSM2040	7.50
LM380N-14 1 25 LM381 1 89	LM3900 LM3905	89 149	SSM2044 SSM2055	575 6.50
LM381 189 LM383 329	LM3914	3.79	xR2206	5.19
LM384 1 95	LM3915	3.79	XR4136 XR4741	99
LM386 99 LM387 149	LM3916 LM4500	3.29	XA558	1.99
5% Car	bon Fi	Im F	Resist	ors
We stock all				
	hm and 1			
10				
1/4 Watt				
V Watt Package of 5				1.50
V Watt Package of 5 Package of 10	00 (one va	lue) .		1.50
1/4 Watt Package of 5 Package of 10 Package of 10	00 (one va	lue) .		1.50
½ Watt       Package of 5       Package of 10       Package of 10       ½ Watt       Package of 5	00 (one va 000 (one v	ilue) value)		1.50 9.75
V Watt Package of 5 Package of 10 Package of 10 V Watt Package of 5 Package of 10	00 (one va 000 (one v 000 (one va	ilue) value) ilue)		1.50 9.75 
½ Watt       Package of 5       Package of 10       Package of 10       ½ Watt       Package of 5	00 (one va 000 (one v 000 (one va	ilue) value) ilue)		1.50 9.75 
V Watt Package of 5 Package of 10 Package of 10 V Watt Package of 5 Package of 10 Package of 10 Sampler box	00 (one va 000 (one v 000 (one va 000 (one v consisting	ilue) value) ilue) value)	each of a	1.50 9.75 25 1.75 15.00 all 169
½ Watt         Package of 5         Package of 10         Package of 10         ½ Watt         Package of 5         Package of 10         Sampler box         standard 5%	00 (one va 000 (one va 000 (one va 000 (one va 000 (one va consisting values bet	ilue) value) value) value) of 5 ween	each of a	1.50 9.75 25 1.75 15.00 all 169
½ Watt         Package of 5         Package of 10         Package of 10         ½ Watt         Package of 5         Package of 10         Sampler box         standard 5%         Meg Ohm (84)	00 (one va 000 (one va 000 (one va 000 (one va consisting values bet 5 pieces	ilue) value) value) value) of 5 ween total).	each of a 1 Ohm a	1.50 9.75 25 .1.75 15.00 all 169 and 10
V Watt Package of 5 Package of 10 Package of 10 V Watt Package of 5 Package of 10 Package of 10 Sampler box standard 5% Meg Ohm (84 V Watt Samp	00 (one va 000 (one va 000 (one va 000 (one va 000 (one va consisting values bet 5 pieces Jer Box	ilue) value) value) value) of 5 ween total).	each of a 1 Ohm a	1.50 9.75 1.25 1.75 15.00 and 10 25.00
V Watt Package of 5 Package of 10 Package of 10 V Watt Package of 5 Package of 10 Package of 10 Package of 10 Sampler box standard 5% Meg Ohm (84 V Watt Samp V Watt Samp	00 (one va 000 (one va 000 (one va 000 (one va 000 (one va consisting values bet 5 pieces der Box	ilue) value) value) value) of 5 ween total).	each of a 1 Ohm a	1.50 9.75 1.75 15.00 all 169 and 10 25.00 28.00
½ Watt         Package of 5         Package of 10         Package of 10         ½ Watt         Package of 5         Package of 5         Package of 10         Package of 10         Sampler box         standard 5%         Meg Ohm (84         ¼ Watt Samp         ½ Watt Samp         We Also	00 (one va 000 (one va 000 (one va 000 (one va 000 (one va 000 (one va consisting values bet 5 pieces der Box der Box	ilue) value) value) value) of 5 ween total). Watt	each of a 1 Ohm a Resistor	1.50 9.75 1.75 15.00 and 10 25.00 28.00 rs
½ Watt         Package of 5         Package of 10         Package of 10         ½ Watt         Package of 5         Package of 5         Package of 10         Package of 10         Sampler box         standard 5%         Meg Ohm (84         ¼ Watt Samp         ½ Watt Samp         We Also         1% ¼ Wat	00 (one va 000 (one va 000 (one va 000 (one va 000 (one va 000 (one va consisting values bet 5 pieces der Box der Box 0 Stock Va tt Meta	ilue) value) value) value) of 5 ween total). Watt	each of a 1 Ohm a Resistor n Resis	1.50 9.75 1.75 15.00 all 169 and 10 25.00 28.00 rs
½ Watt         Package of 5         Package of 10         Package of 10         ½ Watt         Package of 5         Package of 5         Package of 10         Package of 10         Sampler box         standard 5%         Meg Ohm (84         ¼ Watt Samp         ½ Watt Samp         We Also	00 (one va 000 (one va 000 (one va 000 (one va 000 (one va 000 (one va consisting values bet 5 pieces der Box der Box bet Box Stock Va tt Meta ck all 481	ilue) value) value) of 5 ween total). Watt	each of a 1 Ohm a Resistor n Resis dard EIA	1.50 9.75 1.75 15.00 all 169 and 10 25.00 28.00 rs
½ Watt         Package of 5         Package of 10         Package of 10         ½ Watt         Package of 5         Package of 10         Sampler box         standard 5%         Meg Ohm (84         ¼ Watt Samp         ½ Watt Samp         We Also         1% ¼ Wat store         between 10 0	00 (one va 000 (one va 000 (one va 000 (one va 000 (one va 000 (one va consisting values bet 5 pieces ler Box ler Box stock Va tt Meta ck all 481 Dhms and	value) value) value) of 5 ween total). Watt I Filr Stand 1 Me	each of a 1 Ohm a Resistor n Resis dard EIA g Ohm.	1.50 9.75 1.25 1.75 15.00 all 169 and 10 25.00 28.00 rs stors values
<ul> <li><sup>1</sup>/<sub>4</sub> Watt Package of 5 Package of 10 Package of 10 V/<sub>5</sub> Watt Package of 10 Package of 10 Package of 10 Sampler box standard 5% Meg Ohm (84 V Watt Samp Ve Also</li> <li>1% V/4 Wat We now stoo between 10 0 Package of 5 Package of 10</li> </ul>	00 (one va 000 (o	ilue) value) value) of 5 ween total). <b>Watt</b> I Filr Stand 1 Me	each of a 1 Ohm a Resistor n Resis dard EIA g Ohm.	1.50 9.75 1.25 1.75 15.00 all 169 and 10 25.00 28.00 rs stors values 
½ Watt         Package of 10         Package of 10         Package of 10         ½ Watt         Package of 5         Package of 10         Package of 5         Watt Samp         We Also         1% ¼ Watt Samp         We now stoo         between 10 0         Package of 5	00 (one va 000 (o	ilue) value) value) of 5 ween total). <b>Watt</b> I Filr Stand 1 Me	each of a 1 Ohm a Resistor n Resis dard EIA g Ohm.	1.50 9.75 1.25 1.75 15.00 all 169 and 10 25.00 28.00 rs stors values 
<ul> <li><sup>1</sup>/<sub>4</sub> Watt</li> <li>Package of 5</li> <li>Package of 10</li> <li>Package of 10</li> <li><sup>1</sup>/<sub>4</sub> Watt</li> <li>Package of 10</li> <li>Package of 10</li> <li>Package of 10</li> <li>Package of 10</li> <li>Sampler box</li> <li>standard 5%</li> <li>Meg Ohm (84</li> <li><sup>1</sup>/<sub>4</sub> Watt Samp</li> <li><sup>1</sup>/<sub>2</sub> Watt Samp</li> <li>We Also</li> <li>1% <sup>1</sup>/<sub>4</sub> Wat</li> <li>We now stood</li> <li>between 10 00</li> <li>Package of 10</li> <li>Box of 1000</li> <li>Send for our f</li> </ul>	00 (one va 000 (o	Ilue)	each of a 1 Ohm a Resiston n Resis dard EIA g Ohm. f IC's, Re	1.50 9.75 1.25 1.75 15.00 and 10 25.00 28.00 rs stors values 45 5.50 28.00 sistors,
<ul> <li><sup>1</sup>/<sub>4</sub> Watt</li> <li>Package of 10</li> <li>Sampler box</li> <li>standard 5%</li> <li>Meg Ohm (84</li> <li><sup>1</sup>/<sub>4</sub> Watt Samp</li> <li><sup>1</sup>/<sub>2</sub> Watt Samp</li> <li><sup>1</sup>/<sub>2</sub></li></ul>	00 (one va 000 (o	ilue) value) value) value) o of 5 wween total). Vwatt 1 Filr Stand 1 Me alue) alue) value)	each of a 1 Ohm a <b>Resisto</b> <b>n Resis</b> dard EIA g Ohm. f IC's, Re	1.50 9.75 1.25 1.75 15.00 and 10 25.00 28.00 rs stors values 5.50 28.00 sistors, Trim
<ul> <li><sup>1</sup>/<sub>4</sub> Watt</li> <li>Package of 5</li> <li>Package of 10</li> <li>Package of 10</li> <li>Package of 10</li> <li>Package of 5</li> <li>Package of 10</li> <li>Package of 10</li> <li>Package of 10</li> <li>Sampler box</li> <li>standard 5%</li> <li>Meg Ohm (84</li> <li>Watt Samp</li> <li>We Also</li> <li>1% <sup>1</sup>/<sub>4</sub> Wat</li> <li>We now stoo</li> <li>between 10 0</li> <li>Package of 10</li> <li>Send for our f</li> <li>Capacitors, D</li> <li>Pots, Switch</li> </ul>	00 (one va 000 (o	ilue) value) value) value) o of 5 wween total). Vwatt 1 Filr Stand 1 Me alue) alue) value)	each of a 1 Ohm a <b>Resisto</b> <b>n Resis</b> dard EIA g Ohm. f IC's, Re	1.50 9.75 1.25 1.75 15.00 and 10 25.00 28.00 rs stors values 5.50 28.00 sistors, Trim
<ul> <li><sup>1</sup>/<sub>4</sub> Watt</li> <li>Package of 5</li> <li>Package of 10</li> <li>Sampler box</li> <li>standard 5%</li> <li>Meg Ohm (84</li> <li><sup>1</sup>/<sub>4</sub> Watt Samp</li> <li><sup>1</sup>/<sub>2</sub> Watt Samp</li> <li><sup>1</sup>/<sub>2</sub></li></ul>	00 (one va 000 (one va 000 (one va 000 (one va 000 (one va 000 (one va 05 pieces 05 pieces 05 stock % 14t Meta 14t Meta 15 pieces 05 stock % 14t Meta 100 (one va 100 (one v	llue) alue) value) value) of 5 wween total). <b>Watt</b> <b>I Filr</b> Stand alue) e) alog o yulatoi	each of a 1 Ohm a <b>Resisto</b> <b>n Resis</b> dard EIA g Ohm. f IC's. Re rs. Crystal Connecto	1.50 9.75 1.25 1.75 15.00 and 10 25.00 28.00 rs stors values 5.50 28.00 sistors, Trim
<ul> <li><sup>1</sup>/<sub>4</sub> Watt</li> <li>Package of 5</li> <li>Package of 10</li> <li>Sampler box</li> <li>standard 5%</li> <li>Meg Ohm (84</li> <li><sup>1</sup>/<sub>4</sub> Watt Samp</li> <li><sup>1</sup>/<sub>2</sub> Watt Samp</li> <li><sup>1</sup>/<sub>2</sub></li></ul>	00 (one va 000 (one va 000 (one va 000 (one va 000 (one va 000 (one va 05 pieces 16r Box 16r Box 100 (one va 100 (on	llue)	each of a 1 Ohm a <b>Resisto</b> <b>n Resis</b> dard EIA g Ohm. f IC's. Re rs. Crystal Connecto	1.50 9.75 1.25 1.75 15.00 and 10 25.00 28.00 rs stors values 5.50 28.00 sistors, Trim
<ul> <li><sup>1</sup>/<sub>4</sub> Watt</li> <li>Package of 5</li> <li>Package of 10</li> <li>Sampler box</li> <li>standard 5%</li> <li>Meg Ohm (84</li> <li><sup>1</sup>/<sub>4</sub> Watt Samp</li> <li><sup>1</sup>/<sub>2</sub> Watt Samp</li> <li><sup>1</sup>/<sub>2</sub></li></ul>	00 (one va 000 (one va 000 (one va 000 (one va 000 (one va consisting values bela 15 pieces 16r Box 16r Box 16	Ilue)	each of a 1 Ohm a Resiston n Resis dard EIA g Ohm. f IC's. Re s. Crystal Connecto 0.00 50.00	1.50 9.75 1.25 1.75 15.00 all 169 and 10 25.00 28.00 28.00 sistors values sistors, RF
½ Watt         Package of 5         Package of 10         Package of 10         Package of 5         Package of 10         Sampler box         standard 5%         Meg Ohm (84)         ½ Watt Samp         We Also         1% ¼ Watt Samp         We Also         1% ¼ Watt Samp         We now stoc         between 10 0         Package of 1         Box of 1000         Send for ourf         Capacitors, D         Pots, Switch         Chokes, and	00 (one va 000 (one va 000 (one va 000 (one va 000 (one va consisting values bela 15 pieces 16r Box 16r Box 16	Ilue)	each of a 1 Ohm a Resiston n Resis dard EIA g Ohm. f IC's. Re rs. Crystal Connecto 0.00	1.50 9.75 1.25 1.75 15.00 all 169 and 10 25.00 28.00 28.00 sistors values sistors, RF
½ Watt         Package of 5         Package of 10         Package of 10         Package of 5         Package of 10         Sampler box         standard 5%         Meg Ohm (84         ¼ Watt Samp         ½ Watt Samp         We Also         1% ¼ Watt Samp         We now stoc         between 10 0         Package of 11         Box of 1000         Send for our f         Capacitors, D         Pots, Switch         Chokes, and         10-24.99         25-49.99         WESTLA	00 (one va 000 (one va 000 (one va 000 (one va 000 (one va consisting values beta 15 pieces 16r Box 16r Box 16	Ilue)	each of a 1 Ohm a Resiston n Resis dard EIA g Ohm. f IC's. Re rs. Crystal Connecto 0.00 50.00 A CTRON	1.50 9.75 1.25 1.75 15.00 all 169 and 10 25.00 28.00 rs stors values 45 5.50 28.00 sistors, S. Sistors, RF FREE FREE 
½ Watt         Package of 5         Package of 10         Package of 10         Package of 10         Package of 10         Package of 5         Package of 5         Package of 10         Package of 10         Package of 10         Sampler box         standard 5%         Meg Ohm (84         ¼ Watt Samp         ½ Watt Samp         We Also         1% ¼ Watt Samp         We now stood         between 10 00         Package of 10         Box of 1000         Send for our f         Capacitors, D         Pots, Switch         Chokes, and         10-24.99         25-49.99         WESTLU         37387 Foi	00 (one va 000 (o	Ilue)	each of a 1 Ohm a Resiston n Resis dard EIA g Ohm. f IC's. Re s. Crystal Connecto 0.00 50.00 A TRON nd, MI 48	1.50 9.75 9.75 15.00 all 169 and 10 25.00 28.00 28.00 7s stors values 
V Watt Package of 5 Package of 10 Package of 10 V Watt Package of 10 Package of 10 Package of 10 Package of 10 Package of 10 Sampler box standard 5% Meg Ohm (84 V Watt Samp Ve Also 1% VA Watt Samp We Also 1% VA Watt Samp We Also 1% VA Watt Samp Ve Also 1% VA Watt Samp Ve Also 1% VA Watt Samp Ve Also Package of 10 Package of 5 Package of 10 Box of 1000 Send for our f Capacitors, D Pots, Switch Chokes, and N 10-24.99 25-49.99 WESTLA 37387 Fot Order	00 (one va 000 (one va 000 (one va 000 (one va 000 (one va consisting values beta 15 pieces 16r Box 16r Box 16	Ilue)	each of a 1 Ohm a Resistor n Resistor n Resistor n Resistor on R	1.50 9.75 1.75 15.00 all 169 and 10 25.00 28.00 28.00 28.00 sistors values sistors, ls, Trim rs, RF . FREE dd 1.50 NICS 3185

### **DISPLAY YOUR YOUR STUFF** With the AEA MBA-RO Reader

Automatic display of transmitted and received Morse and RTTY coded signals has come of age. It is proving to be most worthwhile for improving one's own transmitted "fist" and for allowing SWL's or visitors the opportunity to experience the thrill of Amateur Radio coded transmission.



While no machine can yet match the ability of a skilled CW operator in copying poor fists or signals buried in the noise, the MBA-RO by AEA excells even when compared against units costing much more. The large 32 character display allows much easier reading than shorter displays, especially at higher speeds such as 60 WPM or 100 WPM RTTY. The MBA-RO also features dual filters for RTTY decoding of either 170 Hz or 425 Hz (easily changed to 850 Hz) shift transmissions.

For more details, write for our latest catalog or visit your favorite dealer.

Prices and Specifications subject to change without notice or obligation. Software ©copyright by AEA.

ADVANCED ELECTRONIC APPLICATIONS, INC. ~2 P.O. Box C-2160, Lynnwood, WA 98036 (206) 775-7373 Telex: 152571 AEA INTL



## Attention radio amateurs!



Model 33ASR SF Good Working Condition



Code: ASCII Speed: 10 cps, 100 baud. Interface: 20/60 mA, EIA optional Data Set Optional From RCA Service Company. Nationwide Service Available.

### RСЛ

Write:

K-248

J. H. Bell RCA Service Company Bldg. 204-2, Route #38 Cherry Hill, New Jersey 08358 Or call collect the RCA Data Services Region Office in your area:

New York	212-267-1550
Philadelphia	609-234-8900
Atlanta	404-934-9333
Dallas	817-640-0900
Chicago	312-595-4910
Los Angeles	213-728-7473

# Construct This All-American Audio Signal Generator

The perfect project for starting a test bench or rounding one out.

t is still possible for the average builder to design and make equipment that is competitive in cost and effectiveness with that which is store-bought. Many simple, standard design concepts can be applied to modern technology.

### The Circuit

This FET audio signal generator is an easy project derived from the audio oscillator circuit presented in "Working with FETs—part 1," in 73 in November, 1979. There are some simple additions in the finished circuit which make it far more useful than just the basic circuit (see Fig. 1).

I could have used a switch and a selection of fixed values, but it would have cost more and built in a fixed limit. The easy way out was to put the frequency-determining capacitor outboard so that it can be changed quickly. You can use a substitution box or your junk-box selection with ease, but most of the time you can just leave the fixed value in place. I have rarely needed more than the one tone for testing.


Potentiometer R2 gives you an adjustable output level. This is very handy for testing or troubleshooting. Resistors R3 and R4 form an output attenuator network that gives you a low-level adjustable output. This is useful when working with high-gain circuits. Using an attenuator network gives you a cleaner low-level signal than trying to use a highlevel signal at the lowest setting.

A 9-volt transistor radio battery or a power supply can be plugged in at J3. This way you can change quickly between battery and fixed supply, or use your battery or supply with other equipment. It's handy. The low power drain, about 2.2 mA, makes this a really practical project for battery and portable operation.

There are only a few parts values that are at all critical. The design center was for 10% tolerance and in most cases it is much wider. Except in one important case, the voltage rating is anything reasonable over 20 WV dc.

L1 is an 88-mH unpotted toroid. It is a common surplus item, but you may have to look around. They are often used for filters in RTTY equipment.

C1 in combination with L1

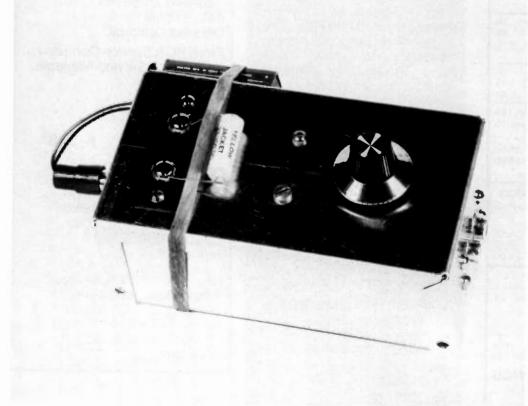

Top view of FET audio signal generator. 116 73 Magazine • December, 1982

is what actually sets the audio tone. My substitution box gave usable tones from 0.22 uF up, but the highest tones were out of the comfortable audio range. I think that 0.1 uF to 0.22 uF would be a good starting point. Get out the junk box and play around.


R1 limits the voltage swing of the output waveform at the gate of Q1. If it were not there, under some conditions the signal might be large enough to damage the transistor. The value is not critical; 3.3k or more will do, but have something there for protection.

Q1 is a Motorola HEP-801, a commonly available audio FET. It has four pins, the fourth being a connection to the outer case. When I made the prototype circuit, the matrix board automatically connected the case to the source pin. It worked well that way so 1 left it in the finished circuit.

Drain bypass capacitor C5 is not critical. Anything from 20 to 100 uF at 20 volts or more should do. The circuit worked well without it, but it might be needed to keep any noise from getting in from your supply. Keep in mind that to further decouple the circuit you can also add a 2.2k or so resistor in series with the drain line if vou have a stubborn noise problem. The greater the capacitance of output coupling capacitor C2, the better the low frequency response. I used a 0.1-uF 50-V-dc disc ceramic that was on hand.

Output level control R2 is a 50k linear-taper potentiometer. A linear taper is used because it is a voltage divider application, not a true volume control. Mine has an ac switch (SW1) right on the back, but you can use a separate switch.

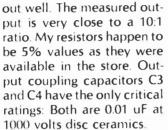R3 (470k) and R4 (47k) form the attenuator network. The textbook values would be different, but since I aimed for a wide 10% tolerance, it worked




The voltage rating is critical. They block any dc voltage in the test circuit (such as a tube-type amplifier) from getting back into the generator and frying all the little parts. Use at least 500-volt capacitors, preferably higher. You should not be using equipment like this in really high-voltage circuits. It's unhealthy. But a good safety margin will keep you going when you work with most tube-type equipment.

These two capacitors also will determine the frequency response of your generator and it's hard to find high capacitance at high working voltage. This means that your lowest audio tones will have less output voltage than mid or high tones.

I should stress that the low-frequency loss comes from the coupling capacitors in the circuit, not the oscillator, which will provide far flatter output across the audio spectrum.
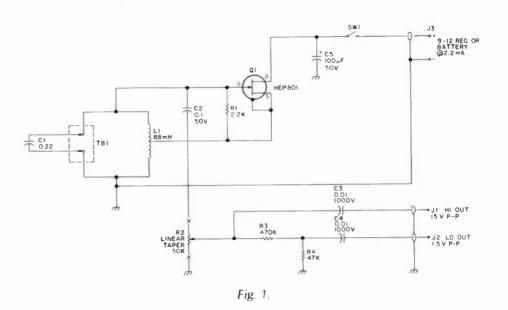
### Construction

Construction is easy. There are only a few me-



t- chanical problems to watch for. The photos show the parts layout and there are a few tricks to make it easier. I used cardboard at the

top and bottom of toroid L1 and a short length of insulation over the screw where it went through the toroid to prevent any shorting.

There is one potential trouble area. Clean the enamel off the magnet wire ends of the toroid very carefully. I mean really get in there with a sharp penknife and scrape it off. I was sloppy the first time. It looked good but it didn't work. It took me a while to find the problem. Check for a good clean contact with your ohmmeter. It doesn't matter which end is grounded when you install it, but when you make the center-tap, look for the two ends that are closest together.

Use a good quality transistor socket. The cheap one I tried at first fell apart. I soldered the leads to the socket first and then wired it to the terminal strip. I was going to tack it down with silicone sealer, but the wire was stiff enough that it didn't wander.


RCA jacks were used throughout. They are not the last word in connectors, but they are cheap and easy to get.

There are many styles of enclosure available; it just has to all fit. I did not try

### Parts List

C1-0.22-uF, 20-volt or greater C2-0.1-uF, 50-volt disc ceramic C3,C4-0.01-uF, 1000-volt disc ceramic (voltage rating critical) C5-100-uF, 50-volt electrolytic J1, J2, J3-RCA jacks L1-88-mH toroid R1-2.2k, 1/2-Watt 5 or 10% R2-50k, linear-taper pot. (Radio Shack 271-1716) R3-470k, 1/2-Watt 5 or 10% R4-47k, 1/2-Watt 5 or 10% SW1-ac switch, part of R2 (Radio Shack 271-1740) Q1-Motorola HEP-801 n-channel FET Miscellaneous Minibox-5-1/4" x 3" x 2-1/8" (Radio Shack 270-238) Knob-Radio Shack 274-413 TB1-2-screw terminal strip Solder terminal strip (see photo) Transistor socket

Mounting hardware

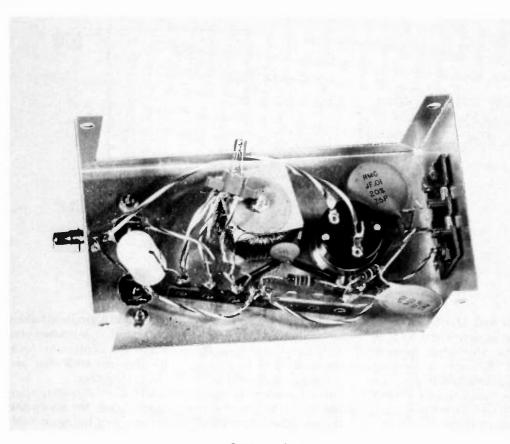

### Bottom view.

to miniaturize. It's small enough now to be handy but large enough to service easily. Notice that the leads are not as short as they could possibly be. It's neat, but there is room and length to work with.

The only part that might be a problem to buy is the toroid. They are still common mail-order items if you check the RTTY supply houses. Get a few; they're useful. Almost any of the other parts are common enough that you may be able to use some of them to make up a minimum order requirement.

I spent a little under \$9 to build the signal generator. I had the toroid, transistor, and some of the small parts, but I bought the rest new to get the prices. I would estimate that it can be built for about \$12 if you are careful, and within \$15 without too much trouble.

### Testing

When you have it put together, check for wiring errors and shorts. Put your milliammeter in the power lead and check the current as you turn it on. Don't forget to put some capacitance value at TB1 (C1) so there will be a complete LC circuit.

Use your scope or highimpedance headphones to check for a tone. If it works, use your scope or VTVM to measure the output voltage at both output jacks as it may vary between units. Don't try to use a VOM on the low-level output. It will load it down to almost nothing. Check for proper operation of the level control and the on-off switch. If you get past all that, you are in business.

The first time I tried mine it didn't work and I designed it! Here are the most likely troubles to look for:

1) Transistor inserted incorrectly in the socket, or you have the wrong pin configuration to the circuit.

2) Weak or dead battery. Check yours under load with meter.

3) Wiring error. Recheck schematic.

4) Coil doesn't make connection with rest of circuit. Unsolder and clean again. Ohmmeter might help here.

The signal should be at the gate of the FET. Lifting one lead of C2 will isolate the output circuit. If there is still no signal at the gate, then the trouble is in the oscillator circuit itself.

### Performance

I checked the performance of mine with my usual assortment of ancient and out-of-tolerance test gear and got the following.

The output voltage varies only slightly over the supply-voltage range of 9 to 20 volts. This is a fringe benefit of R1. It holds the output voltage constant over a wide range of supply voltages.

The output drops off slightly with a supply voltage between 9 and 5 volts. At the design center of 9 to 12 volts, the drain current is about 2.2 mA.

The output voltage at the HI output jack (J1) is 15 volts peak-to-peak on the scope.

At the LO jack (J2), it is 1.5 volts p-p. Pretty good for a rough and ready attenuator network.

The calculated rms voltage by formula was not what one meter showed. The VOM indicated 4.2 volts rms. The LO range was loaded down too much by the meter. The output across the "output" jack was about +15 dBm enough for many purposes.

The minimum signal voltage available is about 0.01 volt p-p on the scope. The voltage is still controllable below this level, but you are at the extreme end of the range and there is a higher level of hum vs. signal. Some noise will get in from any test setup, but at very low levels, noise and crud are a higher percentage of your actual test signal.

Your performance measurements will probably vary from mine because of differences in the unit and test equipment used. The absolute values are not as significant as knowing the relative values as measured by your own equipment. This gives you a way to check the performance against a recorded value.

Always keep records on the operating characteristics of equipment you make when you complete it. Then you will have figures to use for comparison when you need them. It won't be guesswork or vague memory.

### **Odds and Ends**

There are a few little odds and ends to really finish the project properly.

Make a full-size schematic diagram of the circuit showing all parts and values, voltage and current, and the actual output at both jacks (use scope if available). A clear drawing of the parts layout will help if you ever have to work on yours. You may not remember it that well in time. You might even make a copy of this article for your service package.

118 73 Magazine • December, 1982



10

K.

HI-O

Balun

Small, rugged, lightweight

Replaces center insulator

Rugged, lightweight, injection molded of top quality

material, with high dielectric qualities and excellent

weatherability. End Insula-tors are constructed in a spiral unending fashion to

permit winding of loading colls or partial winding for

ing coils or multiband traps

PRICE WITH

\$31.95

28.95

27.95

26.95

25 95

35.95

32.95

43.95

37.95

39.95 33.95

SD models

All prices are postpaid USA 48

130

66 33

22

16

90

45

130

66

130

66

WITH HI-Q CENTER INSULATOR

\$27.95

24.95

23.95

22.95

21.95

31.95

28.95

39 95

33.95 35.95

29.95

\$11.95 pr \$10.95 pr

\$4 49

.55

Handles full legal power

weatherproof


and more

tuned traps.

antennas

May be used for Guy wire strain insulators
 End or center insulators for

~ See List of Advertisers on page 130

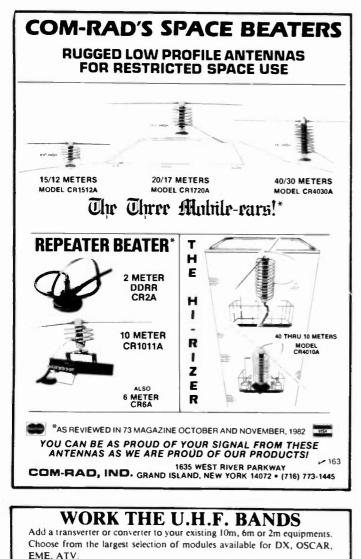

MMT 50-144 \$209.95 TRANSVERTERS MMT 144-28 \$199.95 MMT 432-28 (S) \$299.95 MMT 439-ATV \$349.95 MMT 1296-144 \$374.95 OTHER MODELS AVAILABLE write for details **POWER AMPLIFIERS** all models include RF VOX & Low Noise RX Pre-Ampl. (no pre-amp in MML432-100) 2 Meters: 100W output MML144-100-LS 1W or 3W in \$284.95 100W output 10W input MML144-100-S \$264.95 50W output MML144-50-S 10W input 1W or 3W in \$239.95 30W output MML144-30-LS \$124.95 25W output MML144-25 3W input \$114.95 100W output 432 MHz: MML432-100 10W input \$444.95 50W output MML432-50 10W input \$239.95 30W output MML432-30-L IW or 3W in as 1268-1296 MHz: Coming soon. Watch for details ANTENNAS (incl. 50 ohm balun) 2 Meter J-Beams: 12.3 dBd gain 8 over 8 Horizon'l pol D8-2M \$63.40 8 by 8 Vertical pol D8-2M-vert 76 95 D8/2M 1250-1300 MHz Loop-Yagi 1296-LY \$49.75 Send 36¢ stamps for full details of all our VHF/UHF items. Pre-selector filters Transverters Low-pass filters Converters Varactor triplers Antennas Pre-amplifiers **Crystal Filters** Spectrum International, Inc. Post Office Box 1084S -436 Concord, Mass. 01742 USA

Put all this in the file of service information you keep for your other gear. You do have one, don't you? Then it will be there when you need it. No guesswork.

This is one of the simpler pieces of test gear to use, but there are a few cautions I would like to stress.

If you have been used to working with transistor equipment, you may not be street-wise to the dangers of working in higher voltage tube circuits. This unit will help troubleshoot tube receivers and audio amplifiers, but make sure you observe all safety precautions for working with high voltage. Tube voltage levels are lethal.

Working with transistor equipment is a lot safer for you, but the oscillator has a husky output that easily can blow many transistor stages. Observe all safety precautions for working with transistor circuits, too.

As a general rule, set the controls of the unit under test as they would be for normal operation. Start with the lowest level signal you have and use the least signal that will do the job. You can damage a transistor stage with too much signal or even a static charge. It would be hard to damage a tube stage with this unit, but too much signal can cause distortion. You could be trying to fix a problem that you are causing while testing.

This unit will do a lot for you, but to use it safely and effectively you have to know what you are doing and why.

A good book or two on troubleshooting and repair will give you lots of ways to get the most out of your test equipment. Make sure your library covers both tube and solid-state gear.

A little hands-on experience working with this unit also will tell you a lot about its capabilities.

1	2 Gł	<b>iz Mic</b>	rowa	ve Re	ceivi	ng Syst	tems	
parat feed- manc regul lead, The M Micro Micro	polic poin e RF ated inclu Micro p-Sys	reflect down preamp power uding a	or for conve blifier supply 3' jur n inclu S-021) S-578)	maxin rter wi transist and 5 nper ar udes a f	num e th cer or, a va 0' of i nd mat full 6 n	a mach fficiency amic hig ariable 1: 7512 coas ching tra nonth wa	7, a line gh perf 2 to 18 v xial dov ansform arranty. 	ear or- olt vn- ier. 9*5 9*5
Shipp	oing	& Handl	ing:	USA		K, HI &		
	3	<b>Serv</b> 110 Ev	elyn			612-6: MasterCard	36-946 184	9



Alaska	
Microwave Lal	DS
4335 E. 5TH STREET ANCHORAGE, ALASKA (907) 338-0340 D	99504 Ept 73
CHIP CAPACITORS	
1.2, 2.2, 3.3, 4.7, 6.8, 10, 18, 22, 27, 47, 100, 120, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1.2K, 1.8K, 3.9K, 8.2K, 10K, 100K	5.60
GaAs FETS	3.00
MGF1400 NF 2 0DB @ 4GHZ MAG 15DB MGF1412 NF 0.8DB @ 4GHZ MAG 18DB MCF1200 NF 1.0DB @ 1GHZ NF 2.2DB & MAG 14DB @	\$19.00 \$85.00
4GHZ	\$14.00
COAX CONNECTORS	
BNC CHASSIS MOUNT SOUARE FLANGE BNC PLUG FOR RG-58 SMA CHASSIS MOUNT SOUARE FLANGE	\$1.95 \$1.95 \$6,10
SMA CHASSIS MOUNT PLUG SO. FLANGE SMA CHASSIS MOUNT STRIP-LINE TAB SMA PLUG FOR RG-58 SMA PLUG FOR RG-174	\$8.50 \$6.75 \$6.75
SMA FLUGFUN RG-174 SMA PLUGFOR 141 SEMI RIGID TYPE N CHASSIS MOUNT SOUARE FLANGE TYPE N PLUGFOR RG-9/RG-8	\$6.75 \$3.98 \$3.75 \$3.75
TYPE N DOUBLE MALE TYPE N FOR 141 SEMI-RIGIO TYPE N CHASSIS MOUNT PLUG SQUARE FLANGE	\$7.25 \$15.00 \$14.00
SILVER PLATING KIT Will plate Copper, Brass, Bronze, Nickel, Tin, Pewter,	
Gold, and most white metal alloys.	\$36.00
V10 V72T-1 2.7GHZ TO 3.2GHZ MIN POWER OUT 10 MW TUNING VDLTAGE 0 TO 20V Vcc •15 VDC @ 60 MA V82T-1 SAME AS V72T-1 BUT FRED 3.6GHZ TO 4.2GHZ	598 00 598 00
TEFLON CIRCUIT BOARD DBL SIDED APPROX 3 25" \$ 0" - 010 APPROX 3 25" \$ 0" - 0312	1 OZ \$5 50
APPROX 3.25 * 5 0 * 0312 APPROX. 3.25 * 5.0"= 0625 FEED-THRU CAPACITORS	\$6 50 \$10 50
1000 PF SOLDER TYPE 470 PF SOLDER TYPE	\$.50 \$.50
LEADLESS CERAMIC CAPACITO	_
1000 PF NO WARRANTEE ON SEMICONOUCTORS	\$ 25
OPEN AT 8 PM EST CLOSED 8PM PST ORDERS ARE POSTAGE PAID COO - VISA - MASTERCHARGE	

### CW MORSE for the TRS-80\* COLOR COMPUTER

Our Plug-in Morse-Pak© interfaces the Color Computer to your transceiver and allows you to communicate in CW Morse Code through the computer.

\*Installs in minutes\*
\*Simple to operate\*
\*Handles code speeds
 up to 60 wpm\*
 many more features

We stock a complete line of color computer accessories, including: -Floppy disk controllers Serial 1/0 Ports - Add on EPROM kits - Plug-in Breadboards - RAM Expansion kits, 16K-64K - and more

Write for brochure to:

ATOMTRONICS <sup>186</sup> 3195 ARIZONA AVE. LOS ALAMOS, NM 87544

### IRON POWDER and FERRITE PRODUCTS

AMIDON.


Fast, Reliable Service Since 1963


Small Orders Welcome

Free 'Tech-Data' Flyer

Toroidal Cores, Shielding Beads, Shielded Coil Forms Ferrite Rods, Pot Cores, Baluns, Etc.

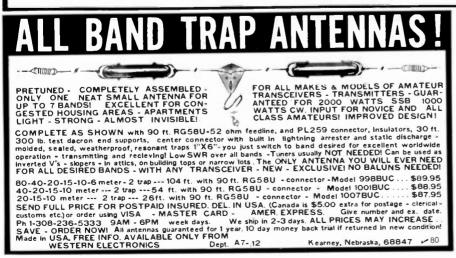12033 OTSEGO STREET, NORTH HOLLYWOOO, CALIFORNIA 91607



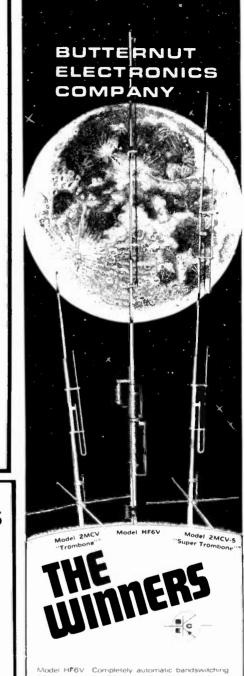

Model HF6V Completely automatic bandswitching 80 through 10 ptus 30 meters. Outperforms all 4- and 5-band 'trap' verticals of comparable size. Thousands in use worldwide since December '81L 160 meter option available now, retrofit kits for remaining WARC bands coming soon. Height: 26 ft/7.8 meters: guying not required in most installations.

Model 2MCV "Trombone" — omnidirectional collinear gain vertical for 2 meters having the same gain as "double-%3" types, but the patented "trombone" phasing section allows the radiator to remain unbroken by insulators for maximum strength in high winds. No coils plumber's delight" construction and adjustable gamma match for complete D.C grounding and lowest possible SWR Height 98 ft/2.98 meters.

Model 2MCV:5 "Super-Trombone" - Same advanced features as the basic 2MCV but a full wavelength taller with additional "Trombone" phasing section for additional gain Height 15 75 tt/4 8 meters

All BUTTERNUT ANTENNAS use stainless steel hardware and are quaranteed for a full year. For further information on these and other BUTTERNUT products write for our FREE CATALOG!

> BUTTERNUT ELECTRONICS GARY AIRPORT BOX 356 E RTE 2 SAN MARCOS TEXAS 78666

# Maximum Modulation for CB Conversions

Many CB rigs lack the gain for full modulation. This preamp will help.

f you have recently converted a CB for 10-meter operation or if your present ham rig has insufficient mike gain, you may be interested in building this simple microphone preamplifier. The majority of CB rigs in the lower to middle price ranges do not provide adequate mike gain for optimum modulation. Typical modulation levels obtained are from 30 to 60 percent. The addition of a preamplified mike can significantly increase the "talk power" of these rigs; just ask any CBer.

There are several commercially-available preamplified mikes on the market that will provide the added audio gain for a price tag of \$25.00 to \$50.00. A much cheaper alternative is the single field-effect transistor (FET) circuit shown in Fig. 1. I purchased all components for under \$5.00 at a local Radio Shack store.

The circuit can be constructed in a separate minicabinet by using mating microphone connectors to match those used by your CB or it can be mounted inside the CB. When mounting within the CB, the additional mike connectors, switch, cabinet, and 9-volt battery are not required.

122 73 Magazine • December, 1982

You probably won't have enough room to install the potentiometer (R4) inside the CB, but it can be replaced with two fixed resistors once the proper mike gain adjustment level is established.

To provide similar circuit-operating parameters when installing inside a CB, substitute a 33k-Ohm resistor for R3 and connect it to a  $\pm$ 12-volt power point in the CB. Also connect the common ground point of the preamplifier circuit to CB ground. Unsolder the existing microphone lead from the printed circuit board and connect it to the input of the FET circuit. Use a short piece of shielded wire to connect the output of the FET circuit to the printed circuit board and ground the shield to minimize hum pickup.

Adjustment is simply a matter of setting the potentiometer for optimum modulation level. This can be accomplished through the use of a modulation meter connected to the antenna feedline connector of the

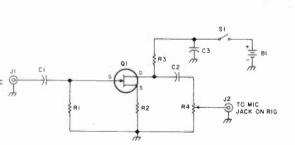


Fig. 1. Mike preamp circuit.

Parts List
B1-9-volt transistor radio battery
S1—SPST switch
Q1—FET, Radio Shack 276-2028
C1-0.01-µF capacitor
C2—0.1-µF mylar <sup>™</sup> capacitor
C3-100-µF, 10-V-dc capacitor
R1-2-megohm, 1/2-Watt resistor
R2-3300-Ohm, 1/2-Watt resistor
R3—10k-Ohm, 1/2-Watt resistor


- R4-50k-Ohm (or 100k) audio-taper potentiometer
- J1,J2-Phone jacks to match equipment

\_\_\_\_\_ nec

CB or during an actual QSO. Don't forget that the FCC limits the maximum permissible modulation level at 100 percent, so make sure that the gain setting used does not cause audio distortion or splatter.

When you have established the optimum level setting, the potentiometer can be replaced by two fixed resistors connected as a series voltage divider. To determine the proper resistor values, measure the resistance between the center lug of the potentiometer and each outside lug. Obtain two resistors having the same approximate values. connect them in series, and substitute these in place of the potentiometer. Connect the mike lead to the junction between the two resistors. Check that the resistors are installed in the circuit so that they have the same relationship as the measured resistance values on the potentiometer.

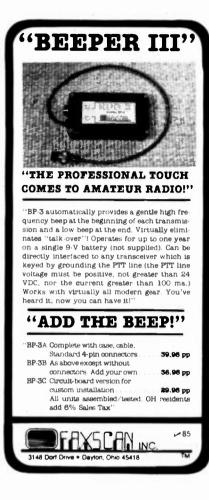The circuit can be constructed on any suitable piece of insulating material. I used a piece of cardboard measuring about 1-1/2" by 3" and mounted the components on one half of the area. I then folded and taped the cardboard under to protect against possible shorting of the circuit connections. ■



*QUALITY* 

\*PERFORMANCE

Tunable Audio Demodulator — Tunes from 5.4 to 8.2 MHz. Switchable 5 KHz. LP filter for

Canadian birds. Varactor tuning diodes included. Use two for MTV.

Bare Board (M81-020B) . . . . \$24.95 Two Boards (M81-021B) . . . . \$39.95

Canadian Audio Descrambler - Takes the

normal audio output from your receiver and decodes the 'chirping' sub-carriers heard on

NEW! Canadian Audio Filter — A very sharp low-pass filter designed to remove the 'chirping' from the Canadian audio.

Developed for high performance

in weak signal areas:

85 MHz. Wide bandwidth. Lower C/N. reduced 'tearing'. May be remotely tuned.

All prices include complete and comprehensive

documentation, U.S. postage & handling, For overseas postage & handling, add \$2.00.

\*PRICE

Anik A/B.

Kit (R82-020K)

Kit (M82-010K) .

SATELLITE



DRGA

**DigiCom Engineering**,

P.O. Box 1656

Kodiak, Alaska 99615

(907) 486-5118

(907) 486-6215

(213) 967-4611 • (213) 967-3846 - 194

### RAC



### TRAC\*ONE + DELUXE **CMOS KEYER**

### \$119.95

#### Features:

### Model TE-464

- True CW signal reproduction-Single signal reception
- Removes all QRM and QRN
- Digs out CW signal, decodes it with Phased Lock Loop Tone Decoder then reproduces it with full operator control over Gain, Freq, Tone, Delay.
- All controls on front panel
- \*Freq control variable 300 Hz to 2500 Hz will match any rig.
- LED flashes during decoder operation
- Operates in line with rig audio--leave in line on OFFIRYPASS
- Built in speaker
- Headphones jack rear panel
- \*Battery or AC-adaptor, 9VDC operation

### PLUS:

- "Defuxe CMOS Keyer-"State-of-the-art" CMOS circultry
- Self-completing dots and dashes
- \*Both dot and dash memory \*lambic keying with any squeeze paddle \*5.50 w.p.m.
- \*Speed, Volume, Tone, Tune and Weight controls
- Sidetone and speaker
- Semi-auto switch for bug or straight key \*Deluxe quarter-Inch Jacks for keying and output
- Keys grid block or solid state rigs



### TRAC\*ONE CW PROCESSOR




### Features:


### Model TE 424

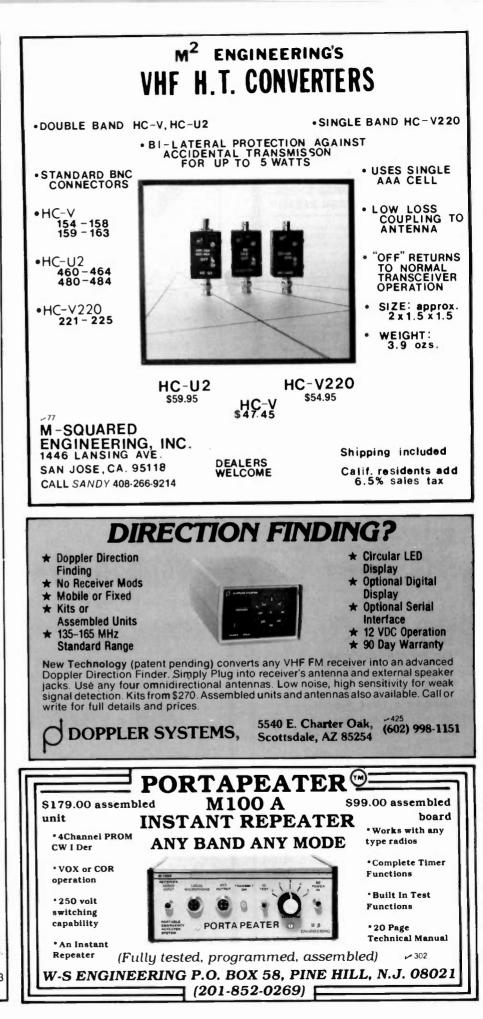(716) 852-8188

\*True CW signal reproduction-Single signal reception Removes all QRM and QRN Digs out CW signal, decodes it with Phased Lock Loop Tone Decoder then reproduces it with full operator control over Gain, Freq. Tone, Delay All controls on front panel Freq control variable 300 Hz to 2500 Hz will match any rig. LED flashes during decoder operation Operates in line with rig audio-leave in line on OFF/BYPASS Bullt-in speaker •Headphones jack rear panel •Battery or AC-adaptor, 9 VDC operation ~ 76 SEND FOR BROCHURE ON OUR FULL PRODUCT LINE ELECTRONICS, INC 1106 RAND BLDG. BUFFALO, NY 14203


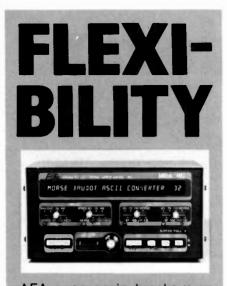
### Better by the dozen. NEVER SAY DIE-If you want controversy, Wayne Green W2NSD/1 will give it to you. His Send me a dozen issues of popular column ranges from travelogue to tirade and is guaranteed to entertain, inspire and MAGAZINE enlighten you. for the dozen reasons listed! DX-This globe-trotting column keeps you informed about the news of the DX world from King-Check enclosed for 1 year for only \$19.97 man Reef to Bahrain. Bill: MC VISA AMEX ME **CONTESTS**—You get all the news on the contest Card#\_\_\_\_\_Interbank#\_\_ world from Robert Baker WB2GFE. He'll give you Exp. date \_\_\_\_\_ Sig. \_\_ information on upcoming events and results from recent contests. Name FUN-Just for fun, John Edwards KI2U provides Address you with wacky puzzles, quizzes, and games that \_\_\_\_\_State\_\_\_\_Zip\_\_\_ City test your ham mettle. FCC-If you're looking to the future, these out-32DR6 Canada & Mexico \$22.97 1 year U.S. funds takes from the Federal Register chronicle changes Foreign surface \$39.97.1 year U.S. funds drawn on US bank only in policy and regulations that relate to amateur Foreign airmail-please inquire radio. 73 Magazine•PO Box 931•Farmingdale, NY•11737 RTTY LOOP-To keep you abreast of radiotele-Please allow 6-8 weeks for delivery type developments, Marc Leavey WA3AJR explains the new RTTY equipment, the increasing role of computers in RTTY, and other matters of interest to digital communications fans. **REVIEWS**—Before you buy, save yourself some money....check 73's in-depth evaluation of the latest gear. HAM HELP—As a service to you, 73 prints your questions in our magazine. This helps you to ob-MAGAZINE tain hard-to-get parts, schematics, and owner's manuals. FOR RADIO AMATEURS SATELLITES - From Phase III to TVRO, 73 Magazine covers the news of the satellite world like no Subscription Department other radio amateur magazine. P.O. Box 931 Farmingdale, NY 11737 NEW PRODUCTS - This brief look at the latest 1-800-258-5473 ham equipment on the market keeps you on top of new developments in amateur radio. For orders only please. Foreign air mail, please inquire. AWARDS-To find out what certificates are available where, read Bill Gosney KE7C's coverage of all the ham radio awards. **CONSTRUCTION**—The builder's magazine. that's 73. You get the best projects from the best authors every month.



AEA once again breaks new ground in the code communications field with the new model MBA-RC reader/code converter. The MBA-RC decodes Morse, Baudot or ASCII signals off the air and displays them on a large 32 character alphanumeric vacuum fluorscent display. In addition, it will output Morse code for keying your transmitter. It will also generate RTTY (Baudot or ASCII AFSK two tone output. (170 or 850 Hz shifts.) Any of the acceptable input codes can be converted to any of the specified output codes (any speed to any speed). If you have any of the common Baudot RTTY terminals as an example, you can now send and receive Morse and ASCII with your keyboard and printer. You can even generate ASCII or BAUDOT RTTY using your Morse hand key or memory kever.

Get the details. Write for our free product catalogue or better yet, see your favorite dealer.

Prices and Specifications subject to change without notice or obligation. Software ©copyright by AEA,

ADVANCED ELECTRONIC APPLICATIONS, INC. P.O. Box C-2160, Lynnwood, WA 98036 (206) 775-7373 Telex: 152571 AEA INTL





RADIO ROOKSHC

## FOR THE NOVICE

New, updated editions

of our famous novice

license study guide and novice study tapes.


NOVICE LICENSE STUDY GUIDE—by Timothy M. Daniel N8RK. Here is the most up to date novice guide available. It is complete with information about learning Morse Code, has the latest FCC amateur regulations and the current FCC application forms. This guide *is not* a question/answer memorization course but rather it emphasizes the practical side of getting a ham license and putting a station on the air. It reflects what the FCC expects a Novice to know without page after page of duil theory. The most current information still available at last year's price. SG7357 \$4,95.\*

• NOVICE STUDY TAPES—If you are just getting started in ham radio, you'lt find these tapes indispen-sable! This up-to-the-minute revision of the 73 Study Course is the perfect way to-learn everything you need to breeze through the Novice written exam. Theory, FCC regulations, and operating skills are all covered, and you'lt be amazed at how fast you learn using these tapes! Once the test is behind you, these tapes will go right on being useful, because they are packed with the latest information on setting up your own ham station, and getting on the air. Thousands of people have discovered how easy learning from cassette can be—order now and enter the fascinating world of ham radio! CT7300 Set of 3—\$15.95.\*

Scientists have proven that you learn faster by listening than by reading because you can play a cas-sette tape over and over in your spare time—even while you're driving! You get more and more info each time you hear it. You can't progress without solid fundamentals. These three hour-long tapes give you all the basics you'll need to pass the Novice exam easily. You'll have an understanding of the ba-sics which will be invaluable to you for the rest of your life! Can you afford to take your Novice exam without first listening to these tapes?

Special Offer! Both Novice License Study Guide and Novice Study Tapes \$19.95 Order NP7300.

### GENERAL LICENSE STUDY GUIDE

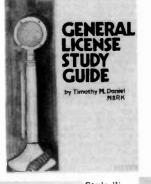

**GENERAL LICENSE STUDY GUIDE**—By Timothy M. Daniel N8RK This is the complete guide to the General License. Learning rather than memorizing is the secret. This is not a question-andanswer guide that will gather dust when the FCC issues a new test. Instead, this book will be a helpful reference, useful long after a ham upgrades to General. Includes up-to-date FCC rules and an application form. Order yours today and talk to the world. SG7358 \$6.95

Figure bound

W2NSD/I

For Your

Ham Shack

73 Magazine

Binders


Style Y

Style W SD/I

-----

 OSL CARDS-73 turns out a fantastic series of QSL ● QSL CARDS — 73 turns out a tantastic series of QSL cards at about half the cost of having them done elsewhere because they are run as a fill-in between printing books and other items in the 73 Print Shop. 250 Style W—QW0250—for \$8.95°; 500 Style W—QW0500—for \$13.95°; 250 Style X—QX0250—for \$8.95°; 500 Style Y—QV0500—for \$8.95°; 500 Style Y—QV0500—for \$13.95°; 4110w 6-12 wks. for delivery.

• LIBRARY SHELF BOXES—These sturdy white, cor-rugated, dirt-resistant boxes each hold a full year of 73, *Kilobaud Microcomputing or 80 Microcomputing.* With your order, request self-sticking labels for any of the following: 73, *Kilobaud Microcomputing, 80 Microcom-puting, CO, QST, Ham Radio, Personal Computing, Radio Electronics, Interlace Age,* and Byte. Order 1— BX1000—for \$2.00°; order 2-7—BX2002—for \$1.50 each°; order 8 or more—BX1002—for \$1.25 each°.

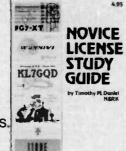

### Code Tapes any four tapes for \$15.95! \$4.95 each

### "GENESIS"

5 WPM — CT7305 — This is the beginning tape for people who do not know the code at all. It takes them through the 26 letters, 10 numbers and necessary punctuation, complete with practice every step of the way using the newest blitz teaching techniques. It is almost mirac-ulous! In one hour many people — including klds of ten are able to master the code. The ease of learning gives confidence to beginners who might otherwise drop out.

### "THE STICKLER"

6+ WPM—CT7306—This is the practice tape for the Novice and Technician licenses. It is made up of one solid hour of code, sent at the official FCC standard (no other tape we've heard uses these standards, so many people flunk the code when they are suddenly—under pressure—faced with characters sent at 13 wpm and spaced for 5 wpm). This tape is not memorizable, unlike the zany 5 wpm tape, since the code groups are entirely random characters sent in groups of five.

### "BACK BREAKER"

13 + WPM—CT7313—Code groups again, at a brisk 14 per so you will be at ease when you sit down in front of the steely-eyed government inspector and he starts sending you plain language at only 13 per. You need this extra margin to overcome the panic which is universal in the test situations. When you've spent your money and time to take the test, you'll thank heaven you had this backbreaking tape.

### "COURAGEOUS"

20 + WPM-CT7320-Code is what gets you when you go for the Extra class license. It is so embarrassing to panic out just because you didn't prepare yourself with this tape. Though this is only one word faster, the code groups are so difficult that you'll almost fail asleep copy-ing the FCC stuff by comparison. Users report that they can't believe how easy 20 per really Is with this fantastic one how it tape. one hour tape

### "OUTRAGEOUS"

25 + WPM—CT7325—This is the tape for that small group of overachieving hams who wouldn't be content to simply satisfy the code requirements of the Extra Class license. It's the toughest tape we've got and we keep a permanent file of hams who have mastered It. Let us know when you're up to speed and we'll inscribe your name in 73's CW "Hall of Fame."

• BACK ISSUES—Complete your collection; many are prime collectables now, classics in the field! A full col-lection is an invaluable compendium of radio and electronics knowledge! 73300 73 BACK ISSUE-BEFORE JULY 1980 73 BACK ISSUE JULY 1980 THRU OCT. 1981 \$ 3.50 73350 73350P 73 BACK ISSUE NOV. 1981 TO PRESENT \$ 3.50 73005 73 BACK ISSUE-5 YOUR CHOICE \$10.75 73 BACK ISSUE-10 YOUR CHOICE 73010 \$16.00 73 BACK ISSUE-25 YOUR CHOICE 73025 \$27.00 73 BACK ISSUE-25 OUR CHOICE 73125 \$14.00 Shipping: Please add \$1.00 per magazine. Orders of ten magazines or twenty-five magazines add \$7.50 per order.

• Preserve and protect your collection for a lifetime! Order these handsome red binders with gold lettering. \$7.50 for 1, 3 for \$21.75, 6 for \$42.00. (Postpaid within USA, please add \$2.50 per order outside USA.) Check or money orders only, no phone or C.O.D. ord Binders, P.O. Box 5120, Philadelphia, PA 19141. orders, 73 "NOTE-Above address for Binders only

Style X

\*Use the order card in this magazine or itemize your order on a separate piece of paper and mail to: 73 Radio Bookshop ● Peterborough NH 03458. Be sure to include check or detailed credit card information. No C.O.D. orders accepted, \$1.50 for the first book, \$1.00 each additional book for U.S. delivery and foreign surface. For foreign airmail \$10.00 per book. Please allow 4-6 weeks for delivery. Questions regarding your order? Please write to Customer Service at the above address. (Prices subject to change on books not published by 73 Magazine.)

FOR TOLL FREE ORDERING CALL 1-800-258-5473


# RADIO BOOKSHOP

### HAND BOOKS FOR THE HAMSHACK

THE COMPLETE SHORTWAVE LISTENER'S HAND-BOOK, 2nd EDITION by Hank Bennett and Harry L. Helms. This comprehensive volume contains loads of new information from all over the world on the latest developments in SWL technology clubs, associations, practices and stations. A thorough guide to stations of the world by general continental area and frequency is included. BK1241 \$9.95

THE TEN METER FM HANDBOOK—by Bob Heil K9EID. This handbook has been published to help the ten meter enthusiast learn more about the many methods of conversions and tricks that are used to make existing units work better. Join the great "tinkerers" of the world on ten FM and enjoy the fantastic amount of fun in communicating with amateur stations worldwide on ten meter FM. BK1190 \$4.95."

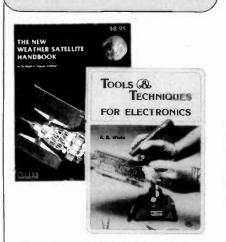THE PRACTICAL HANDBOOK OF AMATEUR RADIO FM REPEATERS—by Bill Pasternak WA6ITF (author of 73 Magazines monthly column "Looking West") This is the book for the VHF/UHF FMer, compiled from material submitted by over a hundred individuals, clubs, organizations and equipment manufacturers. A "must have" for your ham shack shelf. BK1185 \$12.95.\*



TOOLS & TECHNIQUES FOR ELECTRONICS—by A. A. Wicks is an easy-to-understand book written for the beginning kit-builder as well as the experienced hobbyist. It has numerous pictures and descriptions of the safe and correct ways to use basic and specialized tools for electronic projects, as well as specialized metalworking tools and the chemical aids which are used in repair shops. BK7348 \$4.95.\*

BEHIND THE DIAL—This book explains, in detail, what's going on on all the frequencies, from shortwave up to microwave. It gives the reader a good idea of what he can find and where to find it, including some of the secret stations such as the C.I.A. and the F.B.I. Everything is covered short of microwave monitoring. Anyone interested in purchasing a shortwave receiver should have a copy of this book. surveillance, station layout consideration, antenna systems, interface, and the electromagnetic spectrum. are included. BK7307 \$4.95

THE NEW WEATHER SATELLITE HANDBOOK — by Dr. Raiph E. Taggart WB8DQT. Here is the completely updated and revised edition containing all the information on the most sophisticated and effective spaceenced amateur satellite enthusiast and the newcomer. It is an introduction to satellite watching, providing all the information reguired to construct a complete and highly effective ground station. Solid hardware designs and all the instructions necessary to operate the equipment are included. For experimenters who are operating stations, the book details all procedures sents a unique blend of Interests encompassing electronics, meteorology and astronautics. Join the privileged few in watching the spectacle of earth as seen from space on your own monitoring equipment. BK7383 \$8.95.

### THE 73 TEST EQUIPMENT LIBRARY

VOL. II AUDIO FREQUENCY TESTERS—Jam-packed with all kinds of audio frequency test equipment. If you're into SSB, RTTY, SSTV, etc., this book is a must for you... a good book for hi-fi addicts and experimenters, too! LB7360 \$1.95.\*

VOL. III RADIO FREQUENCY TESTERS—Radio frequency waves, the common denominator of amateur radio. Such items as SWR, antenna impedance, line impedance, RF output, and field strength; detailed Instructions on testing these items includes sections on signal generators, crystal calibrators, grid dip oscillators, noise generators, dummy loads, and much more. LB7361 \$1.95.

VOL. IV IC TEST EQUIPMENT—Become a troubleshooting wizard! Here are 42 home construction projects for building test equipment to work with your ham station and in servicing digital equipment. Plus a cumulative index for all four volumes for the 73 TEST EQUIPMENT LIBRARY. LB7362 \$1.95.\*

### ALL THREE OF THE ABOVE ONLY \$4.95 ORDER LB7365

RF AND DIGITAL TEST EQUIPMENT YOU CAN BUILD—BK1044—Rf burst, function, square wave generators, variable length pulse generators—100 kHz marker, I-I and rf sweep generators, audio osc, alfri signal injector, 146 MHz synthesizer, digital readouts for counters, several counters, prescaler, microwave meter, etc. 252 pages. BK1044 \$5.95.

### THE 73 TECHNICAL LIBRARY




THE CHALLENGE OF 160—The growth of amateur radio today is encouraging the use of 160 meters. All the information necessary to get started on this unique band, the all-important antenna and ground systems are described in detail. Also, how to get on, top-band operating tips, top-band transmitters, propagation, weather receiving equipment, and more are covered in full. The introduction contains interesting photos of Stew Perry's (the King of 160) shack. This reference is useful to new and experienced top-band operators. BK7309 \$4.95

INTERFERENCE HANDBOOK—by William R. Nelson, WA6EQG—This timely handbook covers every type of RFI problem and gives you the solutions based on practical experience. Covers interference to TV, radlo, hi-fi, telephone, radio amateur, commercial and CB equipment. Power line Interference Is covered In depth —how to locate it, cure it, work with the public, safety precautions, how to train RF/I Investigators. Written by an RFI expert with 33 years of experience, this profuseunderstand information. BK1230 \$8.95.\*

OWNER REPAIR OF RADIO EQUIPMENT—by Frank Glass K6RQ. Here's a book that will teach you an approach to troubleshooting without a shack full of test equipment. Written in a narrative, non-mathematical style, it will encourage you to successfully flx your own rig problems 80 to 90% of the time. Even if you don't want to flx, you can learn a lot about how things work and fail. Add to your library and personal expertise. BK7310 \$7.95.\*
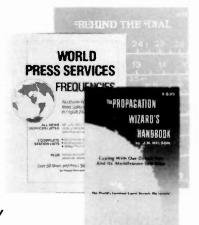
### FOR THE CONTESTER

THE CONTEST COOKBOOK—This book reveals the secrets of that elite group of operators who top the list when the contest results are published. It contains detailed suggestions for the first-time contester as well as tips for the advanced operator. Domestic, DX, and specialty contests are all discussed, complete with photographs and diagrams showing the equipment and operating aids used by the top scorers. For the serious contester. BK7308 \$5.95.



### NEW

EVERYTHING YOU ALWAYS WANTED TO KNOW ABOUT AMATEUR TELEVISION, (but were afraid to ask) —By Mike Stone WB©CCD. This book is a complete guide to setting up your own amateur radio television station. It contains—A history, what equipment you need, video theory, cameras, recorders, lighting, special effects; sound ATV DXing, mobile FSTV, ATV repeaters, ATV groups, building projects, test equipment, dealer directory, a cumulative index of over 1000 articles on amateur TV and much more. This is the new, 1982 edition. From the publishers of Amateur Television Magazine. \$9.95 BK1244

WORLD PRESS SERVICE FREQUENCIES—by Thomas Harrington Can't wait to hear the evening news, or are you wondering about the news that you aren't hearing? Receive by Radio Teletype (RTTY) all the world news and financial happenings from the world capitols on a 24 hour a day basis. This book gives you the frequencies and times of broadcast of such news services as AP, UPI, Reuters, TASS, VOA and London Press. Also included is an introduction to RTTY with information on equipment, antennas, abbreviations—everything you need to get started in RTTY. BK1202 \$7.95

SSB...THE MISUNDERSTOOD MODE—by James B. Wilson. Single Sideband Transmission...thousands of us use it every day, yet it remains one of the least understood facets of amateur radio. J. B. Wilson presents several methods of sideband generation, amply Illustrated with charts and schematics, which will enable the ambitious reader to construct his own sideband generator. A must for the technically-serious ham. BK7351 55.0.\*

PROPAGATION WIZARD'S HANDBOOK— by J. H. Nelson. When sunspots riddled the worldwide communications networks of the 1940s, John Henry Nelson looked to the planets for an answer. The result was a theory of propagation forecasting based upon interplanetary alignment that made the author the most reilable forecaster in America today. The book provides an enlightened look at communications past, present, and future, as well as teaching the art of propagation forecasting. BK7302 \$6.95.\*

IC OP-AMP COOKBOOK—by Walter G. Jung. Covers not only the basic theory of the IC op amp in great detail, but also includes over 250 practical circuit applications, Ilberally illustrated. 592 pages,  $5\% \times 8\%$ , softbound. BK1028 \$14.95.

\*Use the order card in this magazine or ItemIze your order on a separate piece of paper and mail to: 73 Radio Bookshop • Peterborough NH 03458. Be sure to include check or detailed credit card information. No C.O.D. orders accepted. \$1.50 for the first book, \$1.00 each additional book for U.S. delivery and foreign surface. For foreign airmail \$10.00 per book. Please allow 4-6 weeks for delivery. Questions regarding your order? Please write to Customer Service at the above address. (Prices subject to change on books not published by 73 Magazine.)

FOR TOLL FREE ORDERING CALL 1-800-258-5473

### ROOKSH ANTENNA BOOKS





VHF ANTENNA HANDBOOK—The new VHF Antenna Handbook details the theory, design, and construction of hundreds of different VHF and UHF antennas...a practical book written for the average amateur who takes joy in building, not full of complex formulas for the design engineer. Packed with fabulous antenna projects while DK 276 65 06: you can build. BK7368 \$5.95.\*

BEAM ANTENNA HANDBOOK (New 5th edition)-by William I. Orr & Stuart D. Cowan. Yagi beam theory: con-struction and operation, Information on wire beams, SWR curves and matching systems. A "must" for serious DXers, BK1197 \$5,95.

VHF HANDBOOK FOR RADIO AMATEURS—BK1198— Contains information on FM theory, operation and equipment, VHF antenna design and construction, satel-lite-EME, and the newest solid-state clrcuist \$6.95°

THE RADIO AMATEUR ANTENNA HANDBOOK— BK1199—All about wire antennas, beams, tuners, baluns, coax, radials, SWR and towers. Clear and com-plete information. 56.95

SIMPLE, LOW-COST WIRE ANTENNAS FOR RADIO AMATEURS—All new data and everything you want to know about low-cost, multi-band antennas, inexpensive beams, "invisible" antennas for hams in "tough" loca-tions. \$6.95 LOW-COST WIRE ANTENNAS FOR RADIO



73 DIPOLE AND LONG-WIRE ANTENNAS—by Edward A DIPOLE AND LONG-WITE AN TENNAS — Dy Baward M. Noll W3FQJ. This is the first collection of virtually every type of wire antenna used by amateurs. Includes dimensions, configurations, and detailed construction data for 73 different antenna types. Appendices describe the construction of noise bridges, line tuners, and data on measuring resonant frequency, velocity factor, and swr. BK1016 \$5.50.\*

ALL ABOUT CUBICAL QUAD ANTENNAS (2nd ed) tion)—The "Classic" on Quad design, theory, con-struction, and operation. New 2nd edition contains new feed and matching systems and new data. BK 1196 \$5.95

HOW TO DEFEND YOURSELF AGAINST RADAR—BK1201-by Bruce F. Bogner and James R. Bodnar, a lawyer and radar expert. This book gives you the ammunition to challenge the radar "evidence" that usually leads to a speeding conviction. The major part of the book details the inner workings of radar—you'll become more of an expert than most police officers and judges. The remainder of the book outlines how to defend yourself against a speeding ticket—the observations, measures and testimony you must obtain to defend yourself without the help of a lawyer. The price is a lot less than a fine! \$6.95.

### MICROCOMPUTER BOOKS

ANNOTATED BASIC—A NEW TECHNIQUE FOR NEO-PHYTES. VOL 1 & 2—Annotated BASIC explains the complexities of modern BASIC. It Includes complete TRS-80: Level II BASIC programs that you can use. Each program is annotated to explain in step-by-step fashion the workings of the program. Programs are flowcharted to assisted you in following the operational sequence. And—each chapter includes a description of the new concents which have been intrduced. concepts which have been introduced. Volume 1 BK7384 \$10.95 Volume 2 BK7385 \$10.95

HOBBY COMPUTERS ARE HERE!If you want to come HOUDEY COMPOSERS ARE REPERENT you want to come up to speed on how computers work—hardware and software—this is an excellent book. It starts with fun-damentals and explains the circuits and the basics of programming, along with a couple of TVT construction projects, ASCII, Baudot, etc. This book has the highest recommendations as a teaching aid. \$2.47. BK7322

KILOBAUD KLASSROOM—By George Young and Peter Stark. Learning electronics theory without practice Isn't easy. And it's no fun to build an electronics project that you can't use. *Kilobaud Klassroom* the popular series first published in *Kilobaud Microcomputing*, combines theory with practice. This is a *practical* course in digital electronics. It starts out with very simple electronics projects, and by the end of the course you'll construct your own working microcomputer! BK7386 \$14.95

• 40 COMPUTER GAMES-BK7381-Forty games in all 

man. 57.95 eunDERSTANDING AND PROGRAMMING MICRO-COMPUTERS—BK7382—A valuable addition to your computing library. This two-part text includes the best articles that have appeared in 73 and Kilobaud Microcomputing magazines on the hardware and soft-ware aspects of microcomputing. Well-known authors and well-structured text helps the reader get involved. \$10.95' \$10.95

TEXTEDIT—A Complete Word Processing System in kit form—by Irwin Rappaport. *TEXTEDIT* is an inexpen-sive word processor that you can adapt to suit your needs, from writing form letters to large texts. It is writ-ten in modules, so you can load and use only those por-tions that you need. Included are modules that perform right justification, ASCII upper/lowercase conversion, one-key phrase entering, complete editorial functions, and much more! *TEXTEDIT* is written in TR5-80°. Disk BASIC, and the modules are documented in the author's admirably clear tutorial writing style. Not only does Irwin Rappaport explain how to use *TEXTEDIT*; he also explains programming techniques implemented also explains programming techniques implemented in the system. *TEXTEDIT* is an inexpensive word pro-cessor that helps you learn about BASIC program-ming. It is written for TRS-80 Models I and III with TRS-DOS 2.2/2.3 and 32K. 'TRS-80 and TRSDOS are trade-marks of the Radio Shack Division of Tandy Corpora-tion. BK7387 \$9.97

SOME OF THE BEST FROM KILOBAUD/MICROCOM PUTING — BK7311 — A collection of the best articles that have recently appeared in Kilobaud/ MICROCOMPUT-ING, included is material on the TRS-80 and PET systems, CP/M, the 8080/8085/Z80 chips, the ASR-33 tersystems, CPIM, the 8080/8080/280 chips, the ASH-33 ter-minal. Data base management, word processing, text editors and file structures are covered too. Programming techniques and hardcore hardware construction proj-ects for modems, high speed cassette interfaces and TVTs are also included in this large format, 200 plus page edition. \$10.95.

THE NEW HOBBY COMPUTERS—This book takes up from where "HOBBY COMPUTERS ARE HERE!" leaves off, with chapters on Large-Scale Integration, how to choose a microprocessor chip, an introduction to programming, low-cost I/O for a computer, com-puter arithmetic, checking memory boards...and much, much more! Don't miss this tremendous value! Only \$2.47. BK7340


### COOK BOOKS

TTL COOKBOOK—by Don Lancaster. Explains what TTL is, how it works, and how to use it. Discusses practical applications, such as a digital counter and display system, events counter, electronic stopwatch digital voltmeter and a digital tachometer BK1063 \$9.50.\*

CMOS COOKBOOK—by Don Lancaster. Details the application of CMOS, the low power logic family suitable for most applications presently dominated by TTL. Required reading for every serious digital ar TTL. Required reading for every serious digital ex-perimenter! BK1011 \$10,50.\*

TVT COOKBOOK-by Don Lancaster Describes the use of a standard television receiver as a micropro-cessor CRT terminal. Explains and describes charac-ter generation, cursor control and interface information in typical, cursor control and interface informa-tion in typical, easy-to-understand Lancaster style. BK1064 \$9.95.1

### THE WELL EQUIPPED HAM SHACK

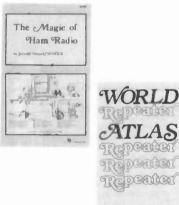

WORLD REPEATER ATLAS-Completely updated, over 230 pages of repeater listings are indexed by location and frequency. More than 50 maps pinpoint 2000 repeat-er locations throughout the USA. Foreign listings in-clude Europe, the Middle East, South America, and Africa. \$4.95° BK7315

\$4.95

THE MAGIC OF HAM RADIO—by Jerrold Swank W8HXR. Under various calisigns, W8HXR has been heard on the ham bands since 1919. He has watched amateur radio grow from the days of Model A spark coils to an era of microprocessors and satellike communica-tions. Jerry has responded to calls for help from earth-quake-striekn Managua and tornado-ravaged Xenia. Ant-arctica, one of man's loneliest outposts, has been a bit less lonely, thanks to Jerry's tireless phonepatching ef-forts. Drawing on his own colorful experiences and those of many other hams, Jerry has compiled this worc-picture of ham radio during the past six decades. BK7312 \$4.95

A GUIDE TO HAM RADIO—by Larry Kahaner WB2NEL. What's Amateur Radio all about? You can learn the basics of this fascinating hobby with this excellent beginner's guide. It answers the most frequently asked questions in an easy-going manner, and it shows the best way to go about getting an FCC license. A Guide to Ham Radio is an ideal introduction to a hobby enjoyed by people around the world. \$4.95.\* BK7321

WORLD RADIO TV HANDBOOK 1982, 25TH EDITION This book is the bible of international broadcasters, providing the only authoritative source of exact informa-tion about broadcasting and TV stations world wide. This 1981 edition is completely revised, giving com-prehensive coverage of short, medium and long wave, 560 pages of vital aspects of world listening. \$16.50, BK1184

Use the order card in this magazine or itemize your order on a separate piece of paper and mail to: 73 Radio Bookshop Peterborough NH 03458. Be sure to include check or detailed credit card information. No C.O.D. orders accepted, \$1.50 for the first book, \$1.00 each additional book for U.S. delivery and foreign surface. For foreign airmall \$10.00 per book. Pie :se allow 4-6 weeks for delivery. Questions regarding your order? Please write to Customer Service at the above address. (Prices subject to change on books not published by 73 Magazine.)

FOR TOLL FREE ORDERING CALL 1-800-258-5473

### -H-

R.S.No.

144 Digatek Corp.

R. S. No. Page 2 AEA/Advanced Electronic Applica-tions . 164 A & W Productions .38 448 Advanced Communications Inter-. . . . 79 national . 475 Albia Electronics. 5 Amateur-Wholesale Electronics .... 19, 87, 165 334 Amidon Associates Applied Invention 154 71 483 Applied Invention 143 Associated Radio 112 186 Atomtronics .... 121 130 Auto Connect ... Autek Research. 40 165 Barker & Williamson, Inc. 11 305 Barry Electronics Corp.... 439 Ben Franklin Electronics 59 173 153 Bit 'O' Byte. 155 157 Boman Industries .61 **BEC/Bullet Electronics** 12 186 Butternut Electronics Corp. 121 187 Call Letter Hats 145 92 Ceco Communications, Inc. 38 102 Centurion International .4 89 Clutterfree Modular Consoles 81 163 Com-Rad Industries 120 150 Commtek 133 382 Communications Concepts, Inc. . 157 Communications Design .41 15 Communications Specialists 83, 113 184 Contemporary Electronics Products 145 190 Control Products Unlimited . 155 152 CQ Products . . 39 Crown Micro Products Current Development Corp. 77 21 161 106 Cushcraft Corp. . 157 346 Data Service Co. 482 DenTron Radio Co., Inc. 120 142 DGM Electronics, Inc. . 38 477 DGM Electronics, Inc. 143

Digi Com Englneering, Inc. . . . . 123

144	Digatek Corp 175
57	Discount Ham Radio
425	Doppler Systems
453	EGE, Inc
447	Electronic Hobby Innovations 144
	,
146	Electronic Ralnbow Industries, Inc.
	Electrovalue Industrial, Inc 173
24	Encomm, Inc
400	Engineering Consulting Service
85	Faxscan, Inc. 123
23	Flesher Corp
323	Fox-Tango Corp. 162, 165
151	Francis Enterprises, Inc. 131
149	
	G & R Design, Inc
178	Galaxy Electronics
479	Ghost Fighters
37	Gillasple & Assoclates
489	Gillaspie & Associates 140
143	GLB Electronics
	Global Specialties
417	Gotham Antenna
195	Goldsmith Scientific Corp
352	Grove Enterprises, Inc
487	Guild Radio Rack
86	H & R Communications
31	Hal-Tronix
345	Hal Communications
•	Ham Radlo Outlet
33	Hamtronics, NY
491	Hamtronics, NY
129	Harvey
303	Heath Co
320	Hoosier Electronics
	ICOM Cov. II, 100, 142, 149
78	Independent Crystal Supply 175
445	Instant Software
440	Amateur Radio Programs
	114, 163, 167
165	Integrated Electronics Unlimited
105	152
	IRL
38	Jameco Electronics
	Japan Radio Co
72	JDL Industries
490	JL Industries
•	JWL Electronics
	Kantropics Inc. 39.89

Page

. . . . . . . . . . 175

\*Please contact these advertisers directly. To receive full information from our advertisers please complete the postage-paid card.

R. S.	No. Page	R.
81	KDK Distributing Comp., Inc 147	•
•	Kenwood Cov. IV. 7, 102-107	1
•	KLM Electronics	3
452	Lewis Construction Co 161	4
77	M-Squared Engineering, Inc 124	
44	Macrotronics, Inc	-
46	Maggiore Electronics	1
134	Martin Engineering	•
139	Memphis Amateur Electronics 146	6
47	MFJ Enterprises	4
48	MHz Electronics	1
49	Micro Control Specialties	6
50	Microcraft Corp	1
51	Microlog	1
196	Microtek	3
•	Mor-Gain	
318	National Comm. Group Co 33, 168	1
492	National Comm. Group Co 148	4
412	Nemal Electronics	
•	Orbit Magazine	1
*	P. C. Electronics	4
•	Palomar Engineers 4, 88, 140	5
182	Peterson Electronics	4
176	Polar Research, Inc	7
199	Proham Electronics	1
•	Proham Electronics	1
191	Pro-Search Electronics	•
61	Radio Amateur Callbook, Inc	1
454	Radiokit	
493	Radio Society of Great Britain 150	1
397	Radio World	4
105	Radios Unlimited	1
62	Ramsey Electronics	
185	Ramsey Electronics	
147	Randall Sherman 162	4
•	RCA Service Co	
156	RF Electronics 161	
171	Ridge Systems Co., Inc 119	
485	Right Time Corporation 141	č
133	Rivendell Associates	
•	R. L. Drake	
418	Rolin Distributors	
•	RQ Service Center	
65	S-F Amateur Radio Services 119	
500		1
	Books 127-130, 133, 169, 171	
	Dealer Ad	
	Moving 167	8
	Subscriptions 125, 147, 164, 173	
	University Microfilms	-
194	Semi Conductor Super Mart 123	

. S. No. Page				
		•		
•	Simple Simon Electronics Kits			
112	Sintec Co.			
<b>3</b> 67	Slep Electronics			
476	Smith Kettlewell Eye Research			
	Foundation			
•	SMP	126		
162	Space Electronics			
•	Spectronics	40 190		
68	Spectrum Communications .			
436	Spectrum International, Inc			
198	Speedcall Corp			
69	Surplus Electronics			
192	Synergistic Systems	175		
183	Tayco Communications	175		
316	Telex Communications	.42,43		
•	Ten-Tec, Inc.	91		
170	TET Antenna Systems			
480	TET Antenna Systems			
•	The Antenna Bank			
118	The Blacksburg Group	. 145		
449	The Ham Shack			
57	The Tuned Antenna			
481	Thermax Corp			
76	Trac Electronics			
104	Trionyx Industries			
197	Twin Oaks & Associates			
•	Universal Communications .			
155	Universal Distributors			
	Universal Electronics			
189	Universal Software			
488	Universal Software			
179	Users International			
	Radio Club	164		
	V-J Products, Inc.			
484	Valor Enterprises			
	Van Gorden Engineering			
	34, 39,	91 110		
		01,119		
311	Vanguard Labs			
90	VoCom Products	40, 152		
	W9INN Folded Unirold			
	Antennas	145		
302	W-S Engineering			
79	Wacom Products			
478	Wayne R & D	143		
80	Western Radio Electronics			
154	Westland Electronics	115		
83	Yaesu Electronics Corp.			
		93, 194		
486	Yaesu Electronics Corp	143		
336	Z Associates			
_				



Catalo	g# Item	Price
73300	73 BACK ISSUE-BEFORE JUL	/ 1980
		\$ 3.00
73350	73 BACK ISSUE - JULY 1980 TH	RU
	OCT 1981.	\$ 3 50
73350P	73 BACK ISSUE-NOV 1981 TO	PRESENT
		\$ 3.50
/ 3005	73 BACK ISSUE - 5 YOUR CHOI	CE
		\$10.75
	Add \$1.00 per magazine for shipping	ng
73010	73 BACK ISSUE 10 YOUR CHO	ICE
		\$ \$6,00
3025	73 BACK ISSUE - 25 YOUR CHO	ICE
		\$27.00
3125	73 BACK ISSUE-25 OUR CHOIL	CE
		\$14.00
A	dd \$7.50 per order for shipping	
_		
K1196	ALL ABOUT CUBICAL OUAD ANT	ENNAS
		\$ 5.95
K7384	ANNOTATED BASIC, VOL. 1.	\$10.95
K7385	ANNOTATED BASIC. VOL 2.	\$10.95
K1197	BEAM ANTENNA HANDBOOK	\$ 5.95
K7307	BEHIND THE DIAL	\$ 4.95

atalo	ng# Item	Price
309	CHALLENGE OF 160	\$ 4.95
011	CMOS COOKBOOK	\$10.50
305	CODE TAPE-5 WPM	\$ 4.95
306	CODE TAPE-6 . WPM.	\$ 4.95
313	CODE TAPE-13 + WPM.	\$ 4.95
320	CODE TAPE-20 + WPM.	\$ 4.95
325	CODE TAPE-25 + WPM	\$ 4.95
394	CODE TAPES (ANY FOUR ABOV	E) \$15.95
241	THE COMPLETE SHORTWAVE	
	LISTENER'S HANDBOOK	\$ 9 95
/308	THE CONTEST COOKBOOK	\$ 5.95
381	40 COMPUTER GAMES.	\$ 7 95
244	EVERYTHING YOU ALWAYS WA	ANTED TO
	KNOW ABOUT AMATEUR TV	\$ 9.95
321	A GUIDE TO HAM RADIO	\$ 4.95
322	HOBBY COMPUTERS ARE HER	E \$ 247
201	HOW TO DEFEND YOURSELF A	GAINST
	RADAR	\$ 6.95
028	IC OP AMP COOKBOOK	\$14.95
230	INTERFERENCE HANDBOOK.	\$ 8.95
386	KILOBAUD KLASSROOM	\$14.95
312	MAGIC OF HAM RADIO.	\$ 4.95
340	THE NEW HOBBY COMPUTERS	\$ 2.47
383	THE NEW WEATHER SATELLIT	E
	HANDBOOK.	\$ 8.95
300	NOVICE THEORY TAPES	\$15.95

To order, complete the postage-paid card, or itemize			
your order including detailed credit card informa-			
tion or check and mail to: 73 Magazine/Mail Order			
Dept./Peterborough NH 03458.			

Catalog	;# Item	Price	Catalog#	Item	Price
BK7310	OWNER REPAIR OF RADIO EOUI	PMENT	SG7358	STUDY GUIDE GENERAL CLASS	\$ 6.95
		\$ 7.95	BK1190	THE TEN METER FM HANDBOOK	\$ 4 95
BK1185	THE PRACTICAL HANDBOOK OF	FM	LB7360	TEST EQUIP LIB V2-AUDIO TEST	TERS
	REPEATERS	\$12.95			\$ 4.95
BK7302	PROPAGATION WIZARD'S HAND	BOOK	LB7361	TEST EQUIP LIB V3-RADIO EQUI	P \$ 4.95
		\$ 6 95	LB7362	TEST EQUIP LIB V4-IC TEST EQ	\$ 4.95
QW0250	OSL CARDS-STYLE W-250	\$ 8 95	BK7387	TEXTEDIT-WORD PROCESSING	KIT
OW0500	OSL CARDS-STYLE W-500.	\$13.95			\$9.97
QX0250	OSL CARDS-STYLE X-250.	\$ 8 95	DS7387	TEXTEDIT-DISK	\$19.97
QX0500	OSL CARDS-STYLE X-500	\$13.95	BK7348	TOOLS & TECHNIQUES.	\$ 4 95
QY0250	OSL CARDS-STYLE Y-250.	\$ 8.95	BK1063	TTL COOKBOOK	\$ 9 50
QY0500	OSL CARDS-STYLE Y-500	\$13.95	BK1064	TVT COOKBOOK	\$ 9.95
BK1199	THE RADIO AMATEUR ANTENNA	4	BK7382	UNDERSTANDING & PROGRAMM	IING
	MANDBOOK	\$ 6.95		MICROCOMPUTERS.	\$10.95
BK1044	RF & DIGITAL TEST EQUIPMENT	\$ 5 95	BK7368	VHF ANTENNA HANDBOOK	\$ 5.95
BK1016	73 DIPOLE & LONG WIRE ANTEN	INAS	BK1198	VHF HANDBOOK FOR RADIO AM	ATEURS
		\$ 5.50			\$ 6.95
BX1000	SHELF BOX-1	\$ 2.00	BK1202	WORLD PRESS SERVICE FREQUI	ENCIES
BX1001	SHELF BOXES-2-7 \$	1 50 each			\$ 7.95
BX1002	SHELF BOXES-BAND UP. \$	125 each	BK 1184	WORLD RADIO TV HANDBOOK.	\$16.50
BK1200	SIMPLE. LOW COST WIRE ANTE	NNAS	BK7315	WORLD REPEATER ATLAS	.\$ 2.00
	FOR RADIO AMATEURS.	\$ 6.95			
BK7311	SOME OF THE BEST FROM KILC	BAUD			
		\$10.95	SHIPPING	AND HANDLING CHARGES: \$1.5	0 for the
BK 7351	SSB THE MISUNDERSTOOD MOD	DE. \$ 5.50	first book.	\$1 for each additional book for US	delivery
SG7357	STUDY GUIDE NOVICE CLASS	\$ 4.95	and foreig	n surface, \$10 per book for foreign	airmail

### CUSHCRAFT

A3 3 Element 1riband Beam	\$167.00
A4 4 Element Triband Beam	\$204.00
A743 7 & 10 MHz Add On for A3	\$55.00
A744 7 & 10 MHz Add On for A4	\$55.00
AV3 3 Band Vertical 10-20m.	\$41.00
AV4 4 Band Vertical 10-40m	\$82.00
AV5 5 Band Vertical 10-80m	\$88.00
R3 14.21.28 MHz Ringo	\$204.00
32-19 Boomer 19 Element 2m	\$75.00
214B Jr. Boomer 14 Element 2m	\$61.00
A147-11 2m 11 Element Antenna	\$34.00
A147-4 2M 4 Element Antenna	\$23.00
ARX-2B 134-164 MHz Ringo Ranger II	\$34.00
A144-10T 145 MHz 10 Element	\$41.00
A432-20T 432 MHz 20 Element	\$41.00
A14T-MB Twist Mounting Boom & Brack	ket. \$21.00

Full Line Available on Sale.Call.

### ROHN

20G 10 ft. Stacking Section	\$32.00
25G 10 ft. Stacking Section	
45G 10 ft. Stacking Section	
25AG 2.3 or 4 Top Section	
HDBX 48 48 ft. Free Standing Tower	
HBX56 56 ft. Free Standing Tower	
FK2548 48 ft. 25G Foldover Tower	\$725.00
TB3 Thrust Bearing	
SB25G Short Base for 25G	
BPH25G Hinged Base Plate	
AS25G Accessory Shelf	\$9.50
HB25AG 14" House Bracket	\$14.50
BPC25G Cement Base Plate	\$32.00
BAS25G Short top section w/acc. shelf.	\$36.00
M200 16 gauge, 10 ft, 2" O.D. Mast	\$19.50
M200H 1/8" wall, 10 ft. 2" O.D. Mast	
Events areanid on Eoldover lowers	Prices

Freight prepaid on Fold-over towers. Prices 10% higher west of Rocky Mts.

### MINI-PRODUCTS

HQ-1 Mini-Quad 6/10/15/20m Antenna.	129.95
B-24 2 Element HF Mini-Beam 6/10/15/20m.	\$99.00
RK-3 3rd Element Add-on for B-24.	
Improves 10-20m	\$67.00
C-4 Mini-Vertical 6/10/15/20m	<b>\$59</b> .00



#### \$79.00 5BTV 80-10 Mtr. Vertical \$100.00 M01/M02 HF Mobile Mast \$18.00 HE Mobile Resonators, Std. 400W . SUPER 2KW \$9.00 10 or 15m \$13.00 \$16.00 20m. \$11.00 \$13.00 \$18.00 40m 75 or 80m \$14.00 \$29.00 BM-1 Bumper mt. with S.S. Strap \$13.00 SSM-2 Commercial S.S. Ball \$14.00 SF-2 5/8 Wave, 2 Meter Antenna \$9.00 HOT Hustloff Mt. with Swivel ball \$14.00 G6-144B 2M Colinear fixed Station 6db \$68.00 G7-144 2M Colinear, fixed Station, 7db \$99.00 Full Line Available on Sale Call



Van Gordon and B&W in stock at special prices

HQ-2S Hy-Quad. 2 Element	\$235.00
TH5DXS Thunderbird, 5 Element	\$215.00
TH3MK3S Thunderbird, 3 Element	\$195.00
TH2MK3S Thunderbird, 2 Element	\$128.00
TH7DX Thunderbird, 7 Element	\$336.00
392S TH6DXX Conversion Kit to TH7DX	\$135.00
105BAS 5 Element 10m "Long-John"	\$114.00
155BAS 5 Element 15m "Long-John".	\$161.00
205BAS 5 Element 20m "Long-John"	\$269.00
14AVQ/WBS 10-40m Vertical	\$49.95
18AVT/WBS 10-80m Vertical	\$87.50
V-2S Colinear Gain Vertical 138-174 MHz	\$33.75
BN-86 Ferrite Balun, 10-80 meters	\$13.00
HDR-300 Deluxe Rotor, Digital Readout	\$378.00
SUPER HY-GAIN PACKAG	E

HY-GAIN

\$150.00

1

We

TH3JRS Jr. Thunderbird, 750W PEP

HG52SS 52' Self Sup. Crank-Up TH7DX Thunderbird. 7 Element HM IV Rotor COA (3) Coax Arms Free Freight
TH7DX Thunderbird, 7 Element 05% OF
HM IV Rotor Freight
COA (3) Coax Arms Free
HG-10 Mast Mast 10
\$1377 SALE SAVE \$449.90
HG50MT2 50 ft. side sup. Crank-up tower
HG50MT2 50 ft. side sup. Crank-up tower TH3MK3S 3 Element Thunderbird CD-45 Rotor COA 3 Coax-Arms HG5 Mast
CD-45 Rotor 25% croight
COA 3 Coax-Arms
HG-5 Mast
\$1005.00 SALE SAVE \$303.45
Philly Stran Guy Cable in stock
NO SUBSTITUTIONS PLEASE
ROTORS & CABLES
CDE HAM IV Rotor \$175.00

CDE HAM IV Rotor	\$175.00
CDE T2X Rotor	\$244.00
CDE 45 Rotor	
Alliance HD-73 Rotor	
Alliance U100 Rotor	
RG-8/U Foam Coax 95% Shield	
RG-213 Coax, Mil. Spec.	
Mini-8 Coax 95% Shield	
Rotor Wire 8 Conductor	
4 Conductor.	

### NEW FAST CHARGE For Your Battery Packs

RECHARGE YOUR HAND HELD ONE UNIT DOES IT ALL RADIO BATTERY PACKS TO FULL CAPACITY IN AS LITTLE AS 45 min. EXAMPLE-Fully Charge ICOM BP3 in 30-45 Minutes.

SEPERATE FUSES PROVIDED INTERNALLY FOR A.C. AND D.C. OPERATION. —BUILT IN REVERSE POLARITY PROTECTION.

Charge, ICOM, YAESU, **KENWOOD**, TEMPO, SANTEC and Others Automatically in Your Home, Car, Boat, R.V. or Airplane with Built-in Heavy Duty Power Supply or 12 to 24 V. External D.C. Supply Such as Cigar Lighter in Your Car.

DESIGN INC

- 149

All Solid State All shild State Precision Components Used Throughout, In A Unique Circuit Alliws Last Changing Without Any Perceptible Heating OF Cells, Charger Measures Remaining Charge In Cells Constantly and Turns OH Automatically When Battery Is Fulls Charged Batters Can Be Left Connected Indefinitely.

INCLUDES: Removable 6 Ft. Cord for A.C. Operation and 2 Mating Connectors for D.C. Input and Battery Leads HATURES: High Quality, Custom Designed Heavy Gauge Aluminum Cabinet. FULL 1 YR. WARRANTY ON PARTS AND WORKMANSHIP

ACCESSORY CONNECTOR TO FIT ICOM BATTERY PACKS, BP-2, BP3, BP4, BP5, \$3 PRE-PAID ORDERS INCLUDE \$3 SHIPPING & HANDLING CALIF. RESIDENTS PHONE ORDERS-CALL [209] 586-7059 MAIL PRE-PAID ORDERS TO:

**DEALER INQUIRIES INVITED** 

P.O. BOX 4463 SONORA, CALIF. 95370


Build Quality Into Ponior Bluff Mo Our 314-989-3248 Products OCATE MANUFACTURERS DISTRIBUTORS GRAIN BINS - INDUSTRIAL - ELECTRICAL - IRRIGATION EQUIP Satellite Television Whether you need 1 system or 100 we have the highest quality antenna to meet your utmost expectations and quality standards, at easy to live with prices. Send: \$7.95 for Introduction to Satellite manual. Pictured is our 11 ft Dish with our easy setting one man installation trailer. 151 Write or call us for more information.


SB-220 ORIGINAL ALC CKT

CIRCUITS


Do you have a technique, modification, or easy-to-duplicate circuit that your fellow readers might be interested in? If so, send us a concise description of it (under two pages, double-spaced) and include a clear diagram or schematic if needed.

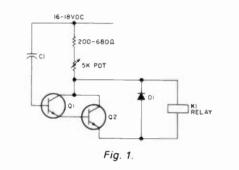In exchange for these technical gems, 73 offers you the choice of a book from the Radio Bookshop, to be sent upon publication. Submit your idea (and book choice) to: Circuits, Editorial Offices, 73 Magazine, Peterborough NH 03458. Submissions not selected for publication will be returned if an SASE is enclosed.



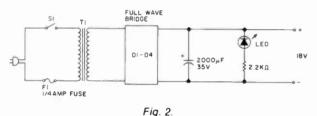


THE KEYLESS KEYER: This circuit can be used to key a transmitter with just a touch. In Fig. 1, Q1 and Q2 are any NPN transistors. C1 can be any disc capacitor. Make sure the leads are long enough so that you can touch them. When the leads are shorted by your finger, the small signal from your body makes the relay drop from 5 volts to less than one volt. The relay toggles. The SPDT leads of the relay can be used to key a transmitter. No dangerous voltages pass through the capacitor. Diode D1 suppresses any high inductive kickback and thus protects the transistors. Use either two 9-volt batteries in series or build the power supply shown. The LED and 2.2-kilohm resistor serve to indicate when the supply is on and to bleed off any dangerous voltages from the 2000-uF capacitor.—Alan Weinberg KR7D, Tucson AZ.

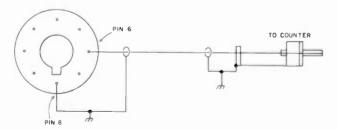


FREQUENCY ADJUSTMENT FOR THE YAESU FT-101: You can use an ordinary frequency counter to tell if your FT-101 is slightly off frequency. Pin 6 on the rig's accessory plug is connected to the vfo output, while pin 8 is ground. Connect a frequency counter to these two pins and check to see if the radio has the same frequency on transmit and receive. The counter will display the vfo frequency — between 8.7 and 9.2 MHz—not the frequency shown on the main dial. You can correct for any difference between the transmit and receive frequency by adjusting the control marked zero, located under the top cover.—Doc Hall W8ZJQ, Elyria OH.




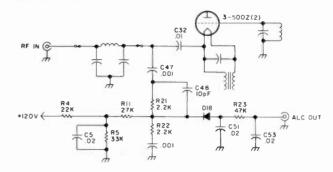

ALC THRESHOLD MOD

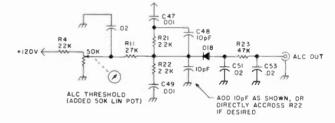


ALTERNATE MOD

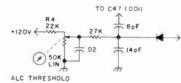


THIS ALTERNATE MODIFICATION REMOVES R21, R22, C49, C48 AND SUBSTITUTES THE 8pF ANI 14pF SHOWN. THIS INVOLVES MORE WORR REMOVING COM-PONENTS FROM THE TIE STRIP AND HAS NO ADVANTAGE OVER THE MODIFICATION SHOWN

RELATIVE POWER METER CIRCUIT MOD

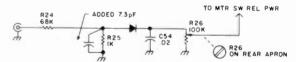

ALC MODIFICATION FOR THE HEATH SB-220: The ALC level in the Heath SB-220 is virtually unusable with the Collins 32S-3. This modification will provide an adjustable, stable ALC voltage for the SB-220. Install the ALC control in the front-panel position normally occupied by the Relative Power Sensitivity control. The RPS control is then installed on the left rear chassis apron about 4½ inches inboard from the left side. By adding a small capacitor across the R25, the response is made more uniform with respect to frequency. After modification, set the RPS to a reading of 270-280 measured on the grid milliameter.—E. A. Wingfield W5FD, Little Rock AR.

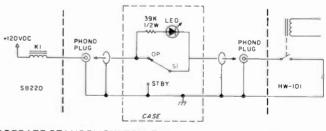

OPERATE-STANDBY SWITCH: This circuit is ideal for a linear amplifier, such as the SB-220, which does not have a standby switch. The circuit requires only three components and a miniature box in which to house them. When S1 is in the OP mode, the 39-kilohm resistor and LED are shorted. Thus, when K1 is energized, the linear is on the air. In the STBY mode, the LED cathode is grounded and energizes. Selection of the resistor is critical: If too low a value, the relay will close in the STBY mode. The exciter can be tuned for maximum power with the antenna connected through the linear's bypass relay. S1 is then switched to OP and the linear can be loaded into the antenna.—F. T. Marcellino W3BYM, Rockville MD.

# HAM HELP

I would like to obtain schematics or manuals for the following:

 E. F. Johnson "Ultracom" 30-50-MHz FM transcelver
 Tempo One 80-10-meter transcelver (the

black version)

 Unimetrics "Dura-Scan" 30-50-MHz scanner

 Lafayette "Micro" P-50 30-50-MHz tunable FM receiver

• J. C. Penney model 6237A citizens band transcelver

•Kris model XL-70 citizens band transceiver

International Crystal "Executive" model
 1500 citizens band transceiver

Heath HP-20 power supply
 If copies are sent, please specify if they

are to be returned or are for me to keep. Gary B. Trustle WB8SPV

424 Franklin Ave. Waverly OH 45690

I am looking for:

•Someone who has modified a Heath HD-1410 keyer for use with a Hallicrafters HT-37 transmitter.

•Firms who sell Motorola MV1404 tuning diodes; MAN-1, MAN-64, and MAN-6680 LED displays; and .25% to 1% precision resistors with values of 243k Q,  $\frac{1}{2}$  W, 11.2k

 $\Omega$ ,  $\frac{1}{6}$  W, 2.43k  $\Omega$ ,  $\frac{1}{6}$  W, and 243  $\Omega$ ,  $\frac{1}{6}$  W. Since the resistors are special items, the firms must be able to conduct business with an individual buying very small quantities.

Paul Kemp WB9CJB 1025 E. Loula Olathe KS 66061

I would like to find manuals or schematics for the following:

- AMPEX model CC323 TV camera
- AIL model R1283/GRC receiver

AIL model IP805/GRC display
 Tektronix model 1401A spectrum

analyzer
 Dumont model 1062 oscilloscope

model DM10-12A0-16-A04 video display

Fred Wolf N5ARO 1920 Ridgelawn Dr. Gautier MS 39552

I am looking for the instruction manual, service manual, and any modifications for the Tennelec Memoryscan MS-2. I also need the service manual and paperwork for the Motorola LO3GB transceiver. I will pay for postage and copying costs.

> Mark Kiziuk N2DMI 2623 E. 11th St. Brooklyn NY 11235

I need an Eico or similar VFO for a local Novice study group.

> G. Samkofsky N4ZB 1420 Mt. Vernon Dr. Holiday FL 33590

Wanted: drive belts for an Aiwa TP708.4" reel-to-reel tape recorder, as well as schematics and info on how to build a good communications receiver.

> Derek H. Rout 3-137 Champion St. Christchurch, New Zealand

Wanted: an external vfo for the Sears 412.35730600 2-meter FM rlg or a schematic of it. I will pay postage for the schematic.

> SSG Gary E. Kohtala DA2XF USAFS-A Box 1415 APO NY 09458

I am looking for a Hunter Bandit linear amplifier.

Ray Warner W7JU/K7JU 2200 Jamaica Cove Riviera AZ 86442



ListIngs in this column are provided free of charge on a space-available basis. The following information should be included in every announcement: sponsor, event, date, time, place, city, state, admission charge (If any), features, talk-in frequencies, and the name of whom to contact for further information. Announcements must be received at 73 Magazine by the first of the month, two months prior to the month in which the event takes place. Mail to Editorial Offices, 73 Magazine, Pine Street, Peterborough NH 03458.

#### FARIBAULT MN DEC 4

The annual Handi-Ham Winter Hamfest will be held on Saturday, December 4, 1982, at the Eagles Club, Faribault MN. Registration will start at 9:00 am, followed by a Handi-Ham equipment auction, dinner at noon, and a program. Talk-In on .19/.79. For more information, contact Don Franz W0FIT, 1114 Frank Avenue, Albert Lea MN 56007

#### HAZEL PARK MI DEC 5

The 17th annual Hazel Park Amateur Radio Club Swap and Shop will be held Sunday, Dec. 5. at Hazel Park High School, Hazel Park MI. Hazel Park High School Is located on Hughes Street at 9½ Mile Rd., 1 mile east of 1-75. Tickets are \$1.50 in advance or \$2.00 at the door. Tables are \$1.00 per foot. Doors open at 8:00 am. Plenty of food and parking will be available. Talk-in on 146.52. For tickets, table reservations, and information, send an SASE to Hazel Park Amateur Radio Club, PO Box 368. Hazel Park MI 48030 or telephone (313):398-3189.

### SOUTH BEND IN JAN 2

A hamfest swap & shop will be held on Sunday, January 2, 1983, at Century Center, downtown on US 33 One Way North between the St. Joseph Bank bullding and the rlver, South Bend IN. Tables are \$3.00 each in a carpeted, half-acre room. The Industrial History Museum is in the same building. Four-lane highways lead to the door from all directions. Talk-in on .52/.52, .99/.39, .93/.33, .78/.18, .69/.09, .145.43, and .145.29. For more information, contact Wayne Werts K9IXU, 1889 Riverside Drive, South Bend IN 46616, or phone (219)-233-5307.

### RICHMOND VA JAN 16

The Richmond Amateur Telecommunications Society will hold Richmond Frostfest '83, the annual winter ham radio and computer show, on Sunday, January 16, 1983, at the state fairgrounds, Richmond VA. General admission is \$4.00. All fleamarket and commercial exhibit spaces will be indoors in a 30.000-square-foot exhibit building.

### PRESERVE **73** JAOAZJNE BINDERS & FILE CASES


Keep your issues of 73 Magazine together, handy and protected in handsome and durable library files or binders. Both styles bound in red leatherette with the magazine logo stamped in gold.

Files: Each flie holds 12 Issues, spines visible for easy reference, \$5.95 each, 3 for \$17.00, 6 for \$30.00

Binders: Each binder holds 12 issues and opens flat for easy reading. \$7.50 each, 3 for \$21.75, 6 for \$42.00

(Postage paid in USA. Foreign orders Include \$2.50 per Item)

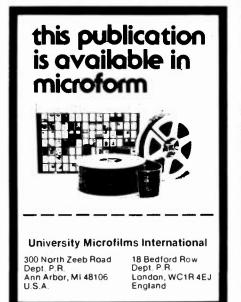Please state years: 1977 to 1983 Send check or money order to: JESSE JONES BOX CORP. P.O. Box 5120 Philadelphia, PA 19141 Allow 4 to 6 weeks for delivery



#### An ultra sophisticated yet simple to operate RTTY System for the demanding operator at an affordable price. Features: •Disk I/O; SAVE, LOAD, KILL & DIR.... •TRI-SPLIT screen, user defined.... •10 CANNED MESSAGES •DYNAMIC BUFFER ALLOCATION..... •Live HARDCOPY for parallel printers...

Keyboard CONTROL of STATION.

CONTACT-80

# RTTY LOOP

### Marc I. Leavey, M.D. WA3AJR 4006 Winlee Road Randallstown MD 21133

For the past few days, I have been reading a book that has struck a responsive chord within me. Detailing some of the goings on behind the scenes of my favorite radio show, National Public Radio's "All Things Considered," the book describes how the show starts with the rudimentary outline first laid out in a morning conference, goes through edits and revisions, and then bursts upon the public at 5:00 pm sounding fresh and spontaneous.

The reason for the empathy I feel is the way RTTY Loop falls together each month. For the December issue, for example, I usually try to take a look at items which could be given as gifts to the ham involved In RTTY or computers, "'tis the season," and all that. Several rough outlines are penciled In over the months untII now, when I try to assemble an exciting column

Well, yes, Maryland (Virginia is a bit to my south), there is a Serendipity. For just as I was casting around, looking for something novel or unique, what comes in the mall but a packet from Tom Harrington of Universal Electronics, Inc.

Tom, you may recall, is the gentleman who produced the book World Press Service Frequencies, a tome reviewed in RTTY Loop back in August, 1981. For those who came in late, I shall explain. This publication, now in its third edition, covers the full specs on over 65 stations transmitting press information worldwide in English. Also covered is information on antennas. terminal units, and the like. Well, Tom has a few more goodles up his sleeve. A glant List of Worldwide Radioteletype Stations in Frequency Order contains 2198 frequencies of stations logged this year. The frequency, callsign, name of station, ITU country symbol, times of reception, and details are included. Over eighty press and news agencies are listed, along with weather, military, and other services using RTTY

Not to stop there. Tom has another rather unusual offering. Did you know that there is a five-level code for Arabic, Cyrlllic, Hebrew, Greek, and Korean-not to mention a six-level Japanese code? If we throw in Hebrew, Arabic, Cyrlllic, Greek, and Japanese Morse codes and then top it all with over 500 identified Arabic words and station names in RTTY, would you be interested? Well, Tom's new work, List of Special RTTY and CW Alphabets and Codes, has all this, plus quite a bit more. Write to Tom at Universal Electronics, Inc., 1280 Alda Drive, Dept. L. Reynoldsburg OH 43068. Use order code "R" for the Worldwide Stations list. \$12; order "P" for the Press Service list, \$8; and "X" for the ATTY and CW Code booklet. \$8. Be sure to mention RTTY Loop in the order, too, OK?

Before we leave Universal Electronics, and while we are on the subject of gifts, i think I have something for the high-powered RTTY types among you. Their Universal M-600 RTTY code receiver may be the ultimate demodulator on the market. This unit decodes signals using bit inversion, TOR, SITOR, and nonstandard shifts. Weather as well as standard format is supported with all speeds of ASCII, Morse, and Murray. Output is both standard video as well as ASCII or Murray printers, complete with a printer buffer of 2K. This brief description only summarizes the material I have In hand. I am sure that Universal would love to send you the full details If you drop them a note at the above address. At \$799.95, this is quite a package.

If that's too much money for you, but you are looking for an object in the "sizable but not ridiculous" category, have you considered one of the new small microcomputers? For under \$300, you can buy an Atari 400 (which has some of the finest graphics I have ever seen and can be expanded to a full system including disk), the TI99/4 (sold in many retail outlets), a Radio Shack Color Computer, or (pushing under the \$100 mark), the Sinclair ZX-81, now marketed by Timex and widely discounted. These and other small computers can serve either as a first system or, as my Atarl does, as an intriguing second computer for someone already afflicted with the computer bug.

Computers aside, and I will admit that it is becoming harder these days to put them there, there are quite a few products around that appeal to the RTTY buff. I don't know about your wife, but mine enjoys windowshopping during the holiday sale season. How do you window shop in a magazine? You look at the ads! Let's see what is available, right here in the pages of 73. I must point out that information I have on some of these items is from literature or the advertisements themselves. If you want more details, write to the company, not to me. By the way, I recognize that many products covering a wide range are of interest to the amateur involved in RTTY, but let's look only at specific RTTY items. If you will follow me around the next corner.

I see that RCA is selling off old, used ASR-33 teleprinters. This is a usable terminal for ASCII circuits and would make a reasonable first start for the amateur interested in getting onto ASCII RTTY. We have covered the hookup of the ASR-33 in past RTTY Loops, and many hams have them on the air. Supporting uppercase ASCII only, these 110-baud machines include punched paper tape facilities. At \$300, the price may be above what you would pay at a hamlest, but I presume the units are checked out and working. If you are interested, contact J. H. Bell at the RCA Service Company, Bldg. 204-2, Route 38, Cherry Hill NJ 08358.

Going from the earliest to one of the latest, Kantronics offers their "The Interface." For about \$190, this box, plus software available separately, will put many popular microcomputers onto RTTY. Software for the Apple II computer is supplied on a diskette for about \$30. Program boards, presumably containing ROMs, are available for the Atari 400/800 or VIC-20 for \$50, or for the TRS-80C Color Computer for \$60. Drop a line to Kantronics at 1202 E. 23rd Street, Lawrence KS 66044, for details.

Producing a fine stand-alone terminal, our old friend Microlog, located at 18713 Mooney Drive, Gaithersburg MD 20879 (just north of WashIngton DC), is still turning out their 6800-based systems. The ATR-6800, reviewed in this column some time back, is an expandable system which can be turned into a general purpose computer. Their newer ACT-1 (not to be confused with a simple computer terminal of the same name available a few years ago) is a dedicated RTTY/CW/SSTV computer. Both use the Motoria 6800 CPU, of which you all know I am guite fond, and appear to be very weil engineered. The ACT-1 is a shade under \$1000; I don't have a recent price on the ATR-6800. I'm sure the guys at Microlog would be happy to fill you In.

Another way to get onto computerized RTTY Is with a package offered by Tufts Electronics, 61 Lowell Road, Hudson NH 03051. The experts up there will sell you the Kantronics Interface detailed above, with a VIC-20 computer, cables, speaker, and instructions for the package price of \$499, as of this writing. Sounds like It might be worth a peek.

Another advertised system is the MFJ Super Keyboard. This box operates on CW Murray, ASCII, and as a memory kever and Morse practice machine. Two versions are available. The MFJ-494 features a 50-character buffer, 30-character memory, and automatic messages, and sells for about \$280. For another \$60, the MFJ-496 increases the buffer and message memory to 256 characters each and adds serial numbering and a repeat message function. Options of AFSK keying, loop keying, and clock module are also available. Drop MFJ Enterprises, Inc., a letter at Box 494, Mississlppi State MS 39762, If you would like further information

We can't forget our old friends IRL, at 700 Taylor Road, Columbus OH 43230. Their two converters, the FSK-1000 and FSK-500 (reviewed in this column in the past), remain excellent products. They also tell me that they can interface their terminal units to many popular computer systems. Just ask them a question—they say they have the answer.

A common question in the mail has been whether there is an adapter made just for the TRS-80C Color Computer for RTTY. Well, Ridge Systems Co., Inc., is advertising their 4511 RTTY Interface. Seliing for about \$170, this ROM board supports Murray and ASCII, a split screen, and messages stored to cassette tape. Drop them a note at PO Box 772, Acton MA 01720, for more Information.

Xitek, one of the first companies out with a single-board terminal, is still featuring their SCT-100 ASCII/Murray terminal. Listing at \$229, it may be of interest to some of you. Their malling address is PO Box 2952, Garland TX 75041.

Speaking of originals, Macrotronics, Inc., 1125 N. Golden State Blvd., Turlock CA 95380, was one of the first with Interlacing to microcomputers. Their "TERMINALL" is a hardware/software system for the Apple II or TRS-80 (Model I or III) that combines terminal unit, computer interlace, and bells and whistles Into one neat package. For about \$500, this is guite a system, supporting ASCII, Murray, or Morse.

Another computer interface, the ROM-116, is available from Crown Micro-Products, 606 State Street, PO Box 892-R, Marysville WA 98270. This package requires an external terminal unit and Includes facilities to save text to disk along with other features similar to other systems. Write Crown for a brochure and pricing details.

The TRS 80 remains the most often supported computer for the RTTY interface, with another one offered by Commtek. Their Contact-80 is available for Model III disk or tape systems, selling for \$279 or \$229, respectively. With split screens, canned messages, date and time, and Identiflers from the computer, this looks like a versatile package. Write them at 4493 Orleans Drive, Dunwoody GA 30338, if you are interested.

Another item we will look at in the window-shopping tour is a window in itself. AEA's MBA-RC reader/code converter. This decodes Morse, Murray, or ASCII and displays the data on a 32-character internal display. Not only that, but it can convert between codes, so that an old Murray machine could speak ASCII or Morse on the air. Looks quite interesting, and full details are available from the manufacturer, Advanced Electronic Applications, Inc., PO Box C-2160, Lynnwood WA 98036.

Last, but not least-by any means-Is old standby Hal Communications, whose name is almost synonymous with RTTY. You have a complete choice of station accessories and options... enough to build a complete RTTY system or any part of it. For example, the HAL DS3100ASR and ST6000, when combined with the MS03100 Message Storage Option and a hard-copy printer, give you a top-notch station. If you're not prepared at this time to spend all your money on a complete layout, what about the RTTY tuning scope? HAL's RS2100 gives you an accurate display of the signal amplitude and phase of the received signal and a flock of other internal goodles. If you're a travelin' man, you'd like the HAL CWR-6850 Telereader...the smallest RTTY and CW terminal available, according to their specs, and complete with CRT display screen. Communicate with Hal Communications at PO Box 365, Urbana IL 61801.

You know, I often say to mention both 73 and RTTY Loop when you write an advertiser for information or to order something. Let me tell you why. This is not just to toot our own horns. Advertisers spend thousands of dollars putting their name and product before you in various media. They want to know which ones work, and where you hear of them, so that they can better direct future campaigns. The better directed the ads, the less "wasted" money, and the more that can go into better products for you and me. So, you see, telling them that you "saw it in 73's RTTY Loop column" is a wise move.

Still stumped for a gift? How about the one that comes a dozen times a year? Less than twenty bucks will get you a one-year subscription to 73, the magazine that brings the active ham so much more of what you read magazines for. Besides, you wouldn't want to miss the next installment of RTTY Loop, would you?



I am a wheelchair-bound amateur in need of equipment capable of working the MARS two- and six-meter bands. Please telephone me at (417)-561-4685 or write me.

Edward L. Maranville KA9COJ/AAT7GX PO Box 512 Rockaway Beach MO 65740 I need a schematic and manual for a Hallicrafters CRX-2 (152-174 MHz) receiver. Any information will be sincerely appreclated. I will pay all costs involved, but please advise me of same first.

> L. E. Taylor K9REB Box 420 Mount Prospect IL 60056

### FUN!

John Edwards KI2U 78-56 86th Street Glendale NY 11385

### HAM GEOGRAPHY

I'm always amazed at the average ham's grasp of geography. As if it weren't enough that most of us are already experts on electronic theory, radio propagation, and telegraphy, we can also claim a knowledge of virtually every square inch of this tired old planet's surface. Who else but a ham is intimately acquainted with such places as East and West Kiribati, Bajo Nuevo, Bouvet, and Chagos? When Great Britain and Argentina began fighting over a forsaken bit of territory known as the Falkland Islands, most of the world ran for an atlas. For hams, VP8-land was an old friend.

This month, Fun! tackles the field of ham geography. Think you know it all? Read on.

### ELEMENT 1-CROSSWORD PUZZLE

(Illustration 1) Down

1) DL-land

(2 words)

10) EP-land 13) Peru prefix

2) Southern state (abbr.)

3) African country (abbr.)

9) Face or type of cup

4) Far East country (abbr.)

5) A ham radio commercial (abbr.) 6) Belonging to a group of northern states

#### Across

- 1) G-land (2 words)
- 7) From
- 8) Eastern European land
- 11) Western state (abbr.)
- 12) New England state (abbr.)
- 13) Austria prefix
- 14) African country
- 16) To borrow
- 17) Agency involved in extreme DX (abbr.)
- 18) Arab country
- 21) Xmas in France 22) Type of power measurement (abbr.)
- 24) China (abbr.)
- 25) 49th state (abbr.)
- 26) This column
- 27) Vermont flow product
- 28) Ø-land state (abbr.)
- 29) Green Mountain State (abbr.)
- 31) Soviet preflx
- 33) Midwest state (2 words)
- 15) 6 down district number 19) El-land 20) US York and Orleans New Guinea 23) Lauderdale 26) 29) India prefix
- 30) Chad prefix 32) Australia prefix

#### ELEMENT 2-MATCHING

Sure, you know all sorts of rare countries by prefix. But do you know their capital cities? Master this subject, and surprise your friend in Paraguay by asking him how things are do-Ing in downtown Asuncion.

#### Column A

- 1) Malta
- 2) Bulgaria
- 3) Romania
- 4) Nepal
- 5) Maldives
- 6) Bhutan
- 7) Burma
- 8) Philippines

- A) Bogota B) Reykjavik C) Manila D) Tripoli E) Nicosia F) Rangoon
- G) Caracas
- H) Katmandu

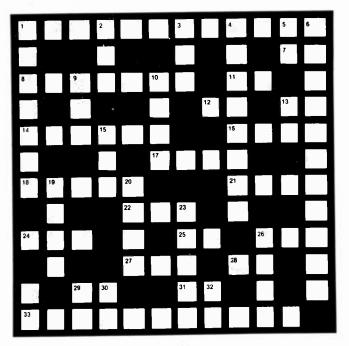


Illustration 1

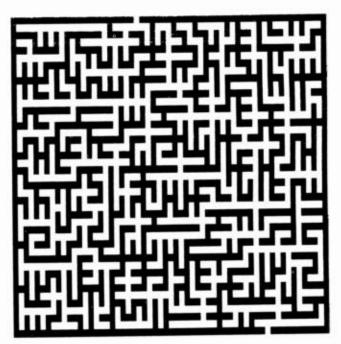


Illustration 2



Column B

9) Ir	ndonesia	I) Baghdad	
10) A	ustralia	J) Lagos	
11) A	Igeria	K) Luanda	
12) S	enegal	L) Islamabad	
13) N	ligeria	M) Sofia	
14) L	ibya	N) Suva	
15) S	iudan	O) Paramarit	ю
16) A	ingola	P) Djakarta	
17) V	enezuela	Q) Khartoum	
18) C	Colombia	R) Valletta	
19) C	Cyprus	S) Dakar	
20) T	urkey	T) Algiers	
21) Io	celand	U) Bucharest	(
22) Ir	raq	V) Thimphu	
23) P	akistan	W) Ankara	
24) F	aya .	X) Canberra	
25) S	Surinam	Y) Male	

#### ELEMENT 3-TRUE-FALSE

#### True False 1) In 1977, the president of the Comoros (D6) had every dog in his capital city of Moroni killed. 2) North Yemen (4W) used to be known as Aden. 3) The movie The King and I is banned in Thailand (HS). 4) In Tanzania (5H), wearing a wig is punishable by flogging. 5) When visiting Nepal (9N), one can stop in government-approved hashish stores. 6) Timbuktu is located in Mali (TZ). 7) Half of the population of Kenya (52), is less than 16 years old. 8) Paraguay (ZP) is the only country with two faces to its flag. 9) In South Africa (ZS), only whites may hold ham tickets

10) Dueling is legal in Uruguay (CX).

### (Illustration 2)

You know, ham radio is a lot like a maze. Thousands of frequencies, dozens of modes hundreds of antenna types—it can all get very confusing. Here's a much simpler maze. All it requires is a pencil and some time. No money or physical effort is needed. Thanks go to my Radio Shack TRS-80 Model II for creating it.

ELEMENT 4-MAZE

### THE ANSWERS

Element 1: See Illustration 1A. Element 2: 1-R, 2-M, 3-U, 4-H, 5-Y, 6-V, 7-F, 8-C, 9-P, 10-X, 11-T, 12-S, 13-J, 14-D, 15-Q, 16-K, 17-G, 18-A, 19-E, 20-W, 21-B, 22-I, 23-L. 24-N, 25-O. Element 3: 1-False At his witch doctor's request. 2-False No, that was South Yemen. 3-True They believe the film presents a false view of their history. No Yul. 4-True Yul 5-True Mount Everest ain't the only thing high in Nepal. 6—True Once a great city, it's now a town of about 6,000. 7-True Thanks to a very high mortality rate. 8-True Boon to flag manufacturers. 9-False Not officially, but what's the difference? 10-True Great way to settle frequency disputes. Element 4: See Illustration 2A.

#### SCORING

Element 1: Twenty-five points for the completed puzzle or one-half point for each question correctly answered.

- Element 2: One point for each correct answer.
- Element 3: Two and one-half points for each correct answer.
- Element 4: Twenty-five points for the completed puzzle.

How worldly are you?

1-20	points-	Hermit
21.40	nainta	Dealuae

- 41-60
- points-Know where your area repeater is located 61-80 points-Armchair traveler

81-100 + points-Man of the World



#### Illustration 2A



TALK FAST

While reading your response to W6EOT's letter in the September Issue, it dawned on me just why the "already-known techniques" for high-speed communication are not used in the ham bands.

You say we can communicate at 8,500 words per minute using these techniques. That would be great for traffic handlers (of which W6EOT is one) and maybe contesters if one could figure out how to program the system to be fast enough. One could conceivably work two or three thousand stations per minute!

However, you often expand on how nice good old rag chewing Is. I can't understand how you propose to rag chew at 8500 wpm!

Some simple testing of my talking speed netted only 235 wpm. I sure can't talk coherently or even think at 1000 wpm, much less 8500 wpm!

Therefore, to communicate at 8500 wpm, I would have to preprogram some device at

my own speed (say 200-400 wpm), contact another station, and punch the proper button to transmit my message at 8500 wom. I could no doubt say everything on my mind at the time in less than thirty seconds, if I had 4000 words to say.

The other station's reply would then be transmitted to me at 8500 wpm, but I would have several minutes to wait while he programmed reply comments into his "super QRQ box." And, of course, he would have several minutes to walt for my next round of comments

The fact that actual transmission time is

very small and more stations can use the available spectrum is a nice idea but needs some human engineering, namely, a QRQ to QRS receive converter that would convert the high-speed transmission to normal talking speed with a voice synthesizer, either synced to the other station's voice tones or to a pleasing blonde (for OMS) or tall, dark, and handsome buck (for YLs).

The transmit converter would take a few dozen words spoken into the microphone and blip-transmit them at 8500 wpm, take a few dozen more and blip, and so on.

The receive converter takes the 8500-wpm transmission and begins "talk-Ing" to the receive operator at 200 or so wpm (ad]ustable of course).

And there you have a high-speed system compatible with us relatively slow humans. Dennis Younker NE6I

Lancaster CA

So what's the difference if your transmitter is on the air, keeping anyone else from using a channel while you mumble inconsequentials at 200 words per minute? Why not have your processor save all that garbage up, put it into a compactor, and dump it at 8500 wpm? Then a bunch of other people could use the same channel. Dunno why we're talking about volce anyway...unless all of the code lovers have suddenly died. There are still a few old-time hams around, graduates of early American schools where reading and writing were taught. We could consider opening up classes in our ham clubs on the first two Rs so newcomers could cope with code and printed types of communications. --- Wayne

### LETTER ACCELERATION

For some time I have been practicing CW just for the fun of it, as in the HK zone, code is regulred only for the first-class Ilcense:

When getting on the air I find many Novlces eager to make the HK contact. They go at my speed when they are calling CQ, but surprise, surprise, once they get to their own callsign, their speed increases by several words per minute, so even if I know that they would immediately answer when they hear the HK coming back to their CQ call, I am not able to call them. Maybe you could write something about this in your magazine.

I usually try to answer CQ calls because when I call CQ with my HK there are just too many stations who come back on my call, even if I sign the HK only once.

I intend to keep you posted on my adventures in CW land.

> Rudolf Aumann HK1ESU Cartagena, Colombia

### **TOPFSHUTTLER?**

My grandmother would say you are a Topfshuttler—a pot stirrer. Isn't that just what an editor is supposed to do? Make people think! You do that well. Obviously, you allow your writers the same freedom.

73's view from Olympus must be a heady one. However, the view is occasionally obscured. Could it be from too much looking down the nose at mortal hams?

A case in point is John Edwards' comment in his column in the July issue, page 123. Commenting on his question, "Do you own a microcomputer?" he stated, "I can't see how a technically-inclined person can be without one." That is editorial nailbuffing from a have to the have-nots and is anything but constructive.

Wayne, please tell the lesser gods at 73

that it ain't 'xactly necessary to have a microcomputer or the latest flamethrower from Japan In order to have fun (and fulfill our responsibilities under Parl 97). Yes, 73 should tell us what is new and keep us up to date. But, too often, you promote the idea that the ham should be measured by his equipment when the equipment should be measured by the ham.

#### Robert F. Solon WD8LKI Toledo OH

Never let it be said that I interfered with your inalienable right to be totally, thoroughly, ridiculously wrong.—Wayne.

### WHAT'S THE FUSS?

You all wanted more teenagers in ham radio? Here I am! I'm 15 years old and just received my Tech ticket. I skipped the Novice test and was really surprised at how simple the FCC exam was. I finished my first year of electronics in high school, which provided all the theory I needed to know, but I had to learn Morse code on my own. I don't know what the blg fuss is over learning Morse code. Anyone can do It. Even with the end of the school year approaching and final exams just around the corner. I was able to find time to study code. Everywhere I went I carried a set of phonetic flash cards with me. When I would finish an assignment in class, I would pull out my cards and study a group of letters. I even found time to study during my Spanish final exam! Nobody can use the excuse: "I just don't have the time to study code."

It took me two months before I was ready for the FCC code test. After I took the code test I continued to study Morse code. With-In two days I was up to 13 wpm. It kind of made me wish I had held out one more week to take the General code test. I do plan to update to General or Advanced sometime in the near future.

I remember reading a letter In which someone said that the high price of ham gear was keeping kids out of the hobby. I say that is 100% untrue. I agree that prices these days are a little steep, but you do not have to own gear to be a ham. My ham shack consists of a DX-302 receiver and several dipole antennas. My school has a transmitter/receiver combination but we do not have a ham radio club, so I cannot use the equipment. I do plan on starting a club at school but that will take some time. In the meantime, I am asking any ham in the Springfield, Va., area to get In touch with me at 455-1490, I'm dying to get on the alr.

I would like to thank the hams who work 3999 kHz at night. I never miss a night listening to this frequency. The more I listened to these fellows, the more I wanted to get my license. Unfortunately, I can't tell them this because I cannot work 75-meter phone. Oh well, this just gives me more incentive to update to Advanced.

> Jim Jones N4HQC Burke VA

### STILL BUILDING

Having been involved in ham radio for half a century, I look back at what ham radio was and what it is today.

In the "Good Old Days," the talk during a QSO was largely technical, dealing with home-made projects. Traffic was handled In an era when telephones were considered a luxury. Parts for your favorite projects were always available at "downtown" distributors. A less affluent society made hams more ingenious in their needs. Today's OSOs are far different! Each new contact allows the ham to list his Japanese-made appliances as If owning a \$3,000 layout reflected on his technical ability. But let a transistor or IC go bad, and the appliance is quickly returned to a "repair depot."

The irony is also that, even for those few hams who can handle difficult repairs, manuals for said appliances lack sufficient information or cost fairly large amounts of money!

It is indeed fortunate for current hams that 73 Magazine is alive and klcking today! For myself, now 65 and retired, the many construction articles have given me many enjoyable evenings. At the same time, local newcomers (age 12-80) likewise were able to discover the "joys of building" vla 73.

Perhaps many readers may disagree with my viewpoints, but I bet the old-timers who remember building a Bearcat receiver or a 47-46-46 push-pull transmitter will agree, the golden years of hamming are past.

#### Geraid Samkofsky N4ZB Holiday FL

Oh, guano, Gerald. I started in 1938 and I visited every active ham I could find. They were a bunch of turkeys, just like today. Nothing has changed except your memory. Remember that the first ham contact with Europe was made by a pirate and we never found out who it was. If you've read any 30s ham magazines (or still survive those days) you know that QRM is no better today than it was fifty years ado. Yeah. the old-timers did build, but they didn't know what the hell they were doing and as often as not blew out the filaments by hooking them to the plate voltade. Gerald, I get on 20m and talk with DX that wasn't even imagined 50 years ago and I do it without a lot of trouble. I had a 20-minute contact this morning with a chap in Apia. Western Samoa...then a shorter one with a chap in Colombo. Ceylon... followed by a nice long chat with HS1ALV. We've never in the history of ham radio had it this good!---Wayne.

### DESTINATED

After a few years of operating K10IQ/R at the summit of Mount Washington, and then this recent summer of traveling about the countryside, I have the following observations and comments to make. This letter was originally a reply to one that I received after criticizing a fellow's operating habits. I would like to give this opinion wider coverage, as it is meant for the entire amateur community.

Lapologize only for the way I sometimes come across: tact Is one of the things I am still learning. Really, Bill, those of us here are not trying to impose "custom" on anyone's operating habits. Some of it Is rather complex—some, kind of stupid I suppose; but I would like very much to get a cheery reply when I call CQ, CQ, rather than some jerk's admonishment: "That's not the way-..." Here, at least you get some logic, advice, and conversation as well.

I submit that most hams, like most of the public, are being Madlson Aved into an abortion of the language. I am not opposed to such a word as "destinated" (though I hear from a lot who are). I don't know of a shorter, more to the point way of saying, "I'm at to where I'm goin'." The colning of such new words is how our language grows: some day Mr. Webster may even include it in his book. However, I do object to the misuse of language (words and grammar), the sometimes cliquish use of words

and phrases, the double question to which one can always answer yes and/or no and still be right, and the long-winded, nonstop monolog method of two-meter operation when, as I think, it should be more like face to face (eyeball, hi hi) or telephone like. Not to mention the editorial we—and the sometimes never ending ID.

Now that I've got this started I shall continue (might even send this in to my friend Wayne Green, hi hi—I might even write a book).

Handel (?)...no, I think that's supposed to be handle... yes that's better; "handle' is bad enough... Is for pots... is made of wood... the vandals stole my handles so I have to use my name (hope you don't mind)... Have you been asked for your "personal"? "....the personal here is "What's a personal?" said t in reply: and the new ham apologized for having been a CBer. "No apology expected nor required." I said. "Some of my best friends used to be CBers; a lot of us have taken that same promotion. No ham shack is complete if it doesn't have a working CB radio. But let us try speaking English here, not some silly dialect.

And then there is the editorial we. We did thIs and We dld that and We are going and We are using... I was listening in one day (needless to say I've got LISTENERS NET LISTENING CERTIFICATE #1) when a friend of mine replied to one of those wewe-we monologs by saying how It was "...so wonderful that you and your wife can do everything together..." The we didn't even respond. What ever happened to I? Is it taboo or something to say "I did thIs...."?

And the never ending ID. Bad enough again, what with ID required only once every ten minutes, that two hams will ID back and forth after every speech...

"...WWW this is ZXC and back to you before I time this thing out. Ya ZXC this is WWW fine business...blah blah and OK on this, that, and the other thing...ZXC this is WWW. OK WWW, ZXC right back..." and on It goes. But when there are four or five of 'em and each one has to say the calls, in proper turn mind you, they spend more time blowing all the horns than they do in any meaningful conversation.

SO! if one wants to "listen" or "monitor." calling out and announcing same once a day should be sufficient. Also, I feel it should be a "custom" that one who has previously announced that he is "listening" should announce "not listening" when rot.

ABC signed on "IlstenIng." A minute or so later ZXC announced he was "listening." ABC "listened" agaIn a short time later and before the tail dropped, ZXC "listened" a little louder. Finally, after a pregnant pause. ABC called ZXC and the usual "...fine business, nice to meet you, hope to see you further on down the log..." QSO followed. Now tell me Bill, was that a "customary Initiation of QSO" or was that a "power struggle"?

If what one really wants is to OSO, then I respectfully submit that what one should do is call. Call, as In CQ, CQ. Or, if that is too straightforward and meaningful. then at least something like "Hullo radio!..."

In this arena I am not concerned with custom; I am not trying to promote any particular way over any other way; I merely want people to say what they mean, be concise, and not be afraid to say "I" once in a while so that when they say "we" you'll *know* there is more than one of them.

However, I'll turn right around and fall back on custom when it comes to badmouthing the shortcomings of the tourists. I know it is the tourist money that "helps keep New Hampshire green." But I also

COAXIAL C	CTRONICS	
This Month's Multi This Month's Day Same Day Same Day Same Day	RG8U-20 ft., PL-259 ea. end. RG214U dbi silver shield, 50 ohm 100 ft. RG8U with PL-259 on each end S BELDEN Coax in 100 ft. rolls RG58U #9201 Grounding strap, heavy duty tubular t 3/16 in. tinned copper 3/8 in. tinned copper	\$1.35/ft. 19.95 \$11.95 braid 10¢/ft.
POLYETHYLENE DIELECTRIC           RG213 noncontaminating 95% sheild mil spec. 36e/tt.           RG174/U mil spec. 96% sheild.         10c/tt.           RG110 96% sheid, 75-ohm mil spec.         25c/tt.           RG8U 96% sheid, mil spec.         527.95/100 ft. or 31c/tt.           RG6A/U double shield, 75-ohm.         25c/tt.           RG6A/U double shield, 75-ohm.         25c/tt.           RG58AU stranded mil spec.         12c/tt.           RG58 mil spec.         11c/tt.           LOW LOSS FOAM DIELECTRIC         RG8X 95% shield (black, white or gray)\$14.95/100 ft.	CONNECTORS MADE IN USA Amphenol PI-259 PL-259 push-on adapter shell PL-259 & SO-239 Double Male Connector PL-258 Double Female Connector. 1 ft patch cord w/RCA type plugs each end. Reducer UG-175 or 176. UG-255 (PL-259 to BNC). Elbow (M359). F59A (TV type).	10/\$3.89 10/\$5.89 \$1.79 98c 3/\$1.00 10/\$1.99 \$3.50 \$1.79 10/\$2.15
RG8U 80% shield         17c/tt.           RG8U 80% shield         07c/tt.           RG58U 90% shield         07c/tt.           RG58U 90% shield         10c/tt.           RG59U 100% foil shield, TV type.         \$7/100 ft.           RG8U 97% shield 11 ga. (equiv. Belden 8214)	UG 21D/U Ámphenol Type N Male for RG8 BNC UG88C/U. male 3/16 Inch Mike Plug for Collins etc UG273 BNC to PL-259 FREE CATALOG COD'add \$1.50—FLA. Res. add 5% Sales	\$3.00 \$1.25 \$1.25 \$3.00
Rotor Cable 8-con. 2-18 ga, 6-22 ga	0% add'l 2 50 minimum	412

know what it is to be a tourist...and hear all the speed demons from Massachusetts griping about being behind a slow-moving farmer.

I censor neither what nor who gets talked about on this repeater. I encourage and even incite lively debate. It seems to me that most of the folk on the receiving end of these barbs are so serious and uptight about their lnanities that they fail to see the humor in a serious debate.

If only I could run the repeater on all this hot air.

Al Oxton K10IQ Mount Washington NH

Feel better now?---Wayne

### THE \$1.98 LICENSE

I just finished reading the code vs. nocode gangfight letters in the October issue. Frankly, I felt'like throwing up. Such lack of imagination; such lack of perception. What we need is negotiation. You know what negotiation is: that's where them what have agree to give all or part of it away in return for return of a hostage, or not getting their heads busted, etc.

In the spirit of negotiation, let me suggest that no one has tried to unite all the factions of this argument by proposing an amateur radio licensing program with something for everyone. Let me then address it from that standpoint.

First, we need to set a goal; hell, anyone familiar with success can tell you that you must establish a goal. The goal must be reasonable—one you can expect to be able to fulfill by a certain time.

Amateur radio's goal then should be to find the method by which everyone will be licensed within 3 years...Change that: everyone who wants to be a ham; we don't want anyone bitching about how we forced him or her to become a ham.

I hear It already: someone saying, "Where would we put them all?" We have literally millions of amateur radio frequencies which are relatively unused. No one said everybody had to be on 20 meters.

The reason for not proposing to include any life forms in other galaxies is twofold. First, it is unreasonable, and the goal must be kept reasonable to be feasible. Second. although the life form known as "slime" must be integrated into amateur radio if we are to meet our goal (a belief in the "Inherent goodness of man" being implicit), we do not know whether or not we would want to share our frequencies with other life forms. Between slime and upright man, we should be able to bring enough hams into amateur radio to make it worthwhile for manufacturers and others with pecuniary interests, thereby assuring the future of our bands

It thus being established that our goal should be to make available an amateur radio operator's license to anyone and everyone who desires one within 3 years, let's look at how to accomplish our goal.

First, the US should lead the way and show the rest of the world how it's done. Wayne Green has stated many times that the FCC has stifled the growth of amateur radio here. Anyone familiar with the doldrums which followed the incentive licensing system imposed back in the 60s should require no further proof. Anyone, though, who needs more proof as to whether or not the FCC should administer the amateur radio service, is reminded of the Citizens Band class-D service and the monumental FCC mismanagement there. Clearly, we do not need the FCC, and responsibility for amateur radio management should be moved to the private sector. More recommendations on that later.

The blg hang-up seems to be inflexibility by all parties. I would remind you, if you ad-

mit you are inflexible, that when it became apparent Johnny could not read, rather than universities going out of business they provided new innovation. Their goal remained unchanged: to pass out the degrees. Only the requirements changed. Rather than being compelled to submit to remedial reading classes, colleges gave credits for music appreciation, penny pitch-Ing, ant watching, etc. This innovation, coupled with sports scholarships and the introduction of new specialties in the liberal arts, kept the degrees flowing. It didn't do a damn thing about Johnny's reading dlfficulty, nor technically staying ahead of the Russlans, but the universities remained open

US hams are accustomed now to the multiple-choice examination style. Our solution lies in going a step further. We should allow the amateur radio aspirant the greatest possible latitude in the entry requirements for our fraternity, within certain reasonable limits necessary to protect the integrity of amateur radio, lest someone succeed in obtaining a license for his dog, etc. There is enough bltching without that. An either-or testing format would allow the aspirant to choose only subjects they feel confident in.

As an example: Code is a requirement for the HF bands, but, as letter writer Roger E. Berube points out In the October 73, code is our link to nostalgia. Machines can now send and receive code, usually faster and cleaner than humans. If an inability to learn code is the only obstacle keeping out an aspirant, then he should be allowed to demonstrate some other skill in lieu of sending and receiving code by hand. Perhaps he is a skilled typist, or could learn to type easier than he could learn to copy code. If so, he should be allowed to appear for testing with his computer keyboard and digital code readout under his arm. Provided he successfully operates his machinery and has ample reading skills, he should pass the code test without investing in the 73 *Magazine* code tapes.

We could also simply fail to honor our commitment to ITU and drop the code requirement, as some countries do, upon demonstration that the aspirant has finely tuned his "money" skills. An aspirant with money should be permitted to substitute money for code skill. This would just be a liberalization of a policy popular in the Third World... or perhaps there is some other explanation why many of their phone (or nhony) ons clutter up the bands which gentlemen have long reserved for CW only. ending each sentence with "Boger, OSI ?" and refer to the CW underneath them as "portadoras" (carriers?). Alouien nos esta poniendo una portadora...Roger, QSL? (Someone is putting a carrier on us, Roger, QSL?)

The Roger, QSL? kind of operator, when allowed a reciprocal license to operate in the US, is the subject of considerable anguish at the FCC, which threatens to stop third-party traffic for all reciprocal licensees (If not all US hams). Further evidence that the FCC should not be involved in administering amateur radio! Our fraternity should be turned over to the private sector for administration and the second step after the abolishment of code should be to strike out the requirement that amateur radio communications be noncommercial. No other aspect of amateur radio is noncommercial; why shouldn't we allow tow-truck dispatchers to use it and foreign visitors to conduct their financial dealings via amateur radio? Nets could even be set up to allow hams to manage their stock transactions right on ham radio. since eventually our goal is to license everyone on Wall Street as well.

People are basically good; everyone will behave himself or herself. Remember that. If they won't, we can just legalize the offense.

Or, perhaps the trouble Is not with the code at all, but with the theory, or the rules. We can be flexible here as well. If a person can copy 20 wpm, but can neither read nor write coherently and without moving his lips, he should not be denied access to an amateur radio license so he may participate in our fraternal brotherhood, In lieu of a theory or rules examination, he should be permitted to demonstrate some other skill, or possess money. Such substitute skills should of course be radio-related: wire splicing, tube replacement, etc.

Now the big question about who should replace the FCC In administering amateur radio. If the Job were turned over to the ARRL, then Ham Radio, 73 Magazine, and perhaps CQ (is there still a CQ?) would cry foul. I submit that the federal government should, as an expedient to our reaching our goal In 3 short years, sell the management of amateur radio to the highest bidder In the free enterprise market, to be operated as a concession.


Cereal companies have an inherent edge here, since they have the box-top and \$1.98 marketing technique down to a science. Providing an aspirant can demonstrate the ability to properly fill out the coupon, locate the proof of purchase seal on the package, and has the regulsite \$1.98 or equal value in food stamps, nobody should have any difficulty in becoming a genuine radio amateur, state of the art.

A test frequency has been set aside where this is essentially the licensing technique. If you care to listen, it's 27.185 MHz.

> Robert G. Wheaton W5XW San Antonio TX


Thank you, you've been most helpful. Now, does anyone else have any more gasoline to throw on this here fire?—Wayne.

# CIRCUITS

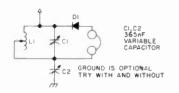


AM BROADCAST RECEIVER: Here is a neat project for a firsttime builder. The gimmick is the coil L1. By using an alligator clip

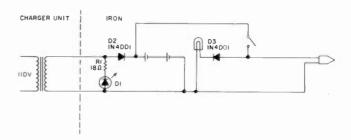
at the various taps on the coil, stations are shifted to the lower frequencies on the capacitor. This enables you to separate the stations more easily. D1 is a 1N34A—don't use a cheap diode. C1 and C2 are both 365-pF variable capacitors. A good earth ground is required (the finger-stop on a dial telephone is ideal).—Jim Burtoft N3BQH, Washington PA.




SOLDERING IRON MODIFICATION: To have a better rechargeable soldering iron, remove the diode from the charging unit and install it on the soldering iron. Because the nicads in the iron will now be isolated from the charging pins, it will be impossible to short out. By placing an LED with a current-limiting resistor into the iron, you will get a visual indication every time the battery is charging. Installing the circuit shown here will enable you to charge your battery from either ac or dc. By installing a power diode in the headlamp circuit, the lamp is protected against accidentally burning out when the battery is at full charge.—Richard J. Molby WB7NZG/DA1DB, APO NY.

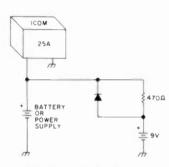

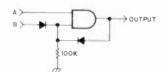
IC-25A BATTERY BACKUP: Here is a simple but effective battery backup for retaining memory when the rig is temporarily removed from the power supply. In tests, the battery retained the memory over eight hours.— Francis J. Piraino WA3KKM, Pocono Summit PA.



SIMPLE AND/OR LATCH: This circuit can be used to trip a repeater relay in a timer circuit. For example, if A is high and B is pulsed by a timer, the output will latch high until the input signal ceases. The high output can be used to disable the transmitter. This eliminates the necessity of having a timer which remains high until well after the desired count is reached. A brief pulse is all that is required. The resistor is needed to hold the B input low since the diodes isolate the input. An OR gate could be used in place of the diodes, but the diodes work well. The gate is a CMOS 4081 or a 4011 NOR gate coupled to an inverter at the output.-John Ackermann AG9V. Green Bay WI.

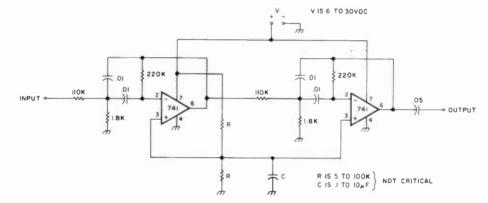

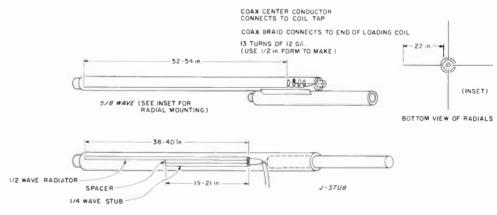TWO-STAGE ACTIVE FILTER: This filter passes an 800-Hz signal. A single section has a bandwidth of about 150 Hz; the two-stage version's bandwidth is approximately 100 Hz. Gain is close to unity at the passband center. The circuit should be added in a low-drive-level section of the audio amplifier if a 12-volt power supply is used.—Penn Clower W1BG, Andover MA.



THE PVC PRINCIPLE VHF ANTENNA:Take one 6' and one 9' piece of 12-gauge copper wire and pull each piece until both are slightly longer. This serves to stiffen the copper. Wind the 6' piece 13 turns on a ½-inch form. Leave ½ inch unwound to make a connection. Remove the coil form and cut the "one piece" radiator as shown. Solder one end of a short length of 28-gauge copper wire to the center terminal of an SO-239 and the other to an alligator clip. Attach the clip to the coil about 2 turns from the radiator. Cut the 9' piece into four equal lengths (2¼') and attach them to the SO-239 as shown. Hang the antenna so that you can trim it for vswr adjustment. Vswr is adjusted by 1) coil tap position, 2) spacing of coil turns, 3) radiator length, and 4) length/angle of radials. After vswr is optimum, solder the coil tap in place. The trimmed antenna can be slid into PVC pipe and epoxied into place. To make the J-stub, take three pieces of RG-8 coax, two 19-21 inches and one 38-40 inches. Carefully remove the outer insulation and braid. Lay the three pieces on a flat table and tape them together temporarily. Solder the coax to the antenna, and connect it to the radiator and the braid to the stub. The radiator/stub assembly can be slid into a PVC pipe. Unsolder the coax, thread it through the hole, and solder it back. The end can be capped and coax putty applied.—Jack Sammarco KC2FS, Union NJ.

# **NEW PRODUCTS**

### **16 DIGIT DTMF DECODER**

Palomar Engineers has announced a new low-cost 16-digit decoder, model P-411. The decoder features high-input Impedance so it does not load the line, crystal control for long-term stability and operation over a wide temperature range, dual bandpass filters ahead of the detector, and digital logic that makes It almost entirely free of false outputs. The P-411 operates from + 12 volts dc and has a 16-line output as well as BCD code and strobe on 5 lines.

For further information, contact Palomar Engineers, 1924F W. Mission Road, Escondido CA 92025; (714)-747-3343.

### PORTABLE EARTH STATION

The first completely portable, batterypowered Earth station for receiving satellite transmitted television has been introduced by Gillaspie and Associates, manufacturers of state-of-the-art satellite equipment. The system can be tossed into a station wagon or recreational vehicle and used by campers to watch up to 105 channels of TV. The product also has more serious applications because of its ability to provide visual and audio information and data to remote, communicationspoor areas.

The system can provide nine to ten hours of television before the batteries have to be recharged, so it could be used to communicate in civil defense emergencies or natural disasters and in areas susceptible to power outages. The system consists of an 8- or 10-foot metalized-fabric dish antenna that collapses like an umbrella, and a batteryoperated satellite receiver complete with a five-inch screen. It can be hooked up to a battery-powered television set if a larger picture is desired.

The portable unit, like the larger home systems, collects microwave beams sent from satellites circling 23,000 miles above. It electronically amplifies less than one Watt of power more than 10,000 times to produce clear, undistorted picture and sound.

Additional information may be obtained through Diane McNutt, Donald J. Sherman & Associates, 4300 Stevens Creek Boulevard, San Jose CA 95129; (408)-247-7300. Reader Service number 489.

### LOW-COST WIND POWER

Thermax has announced a new wind generator design for small power systems. The TC25WG helius rotor kit was developed as a low-cost battery charger for remote sites and applications, including power for camping, boats, radio operation, RVs, cottages, experimentation, and emergency power. The patented helius design offers several advantages: It responds to winds from any direction and is self-starting. The TC25WG rotor operates at low rpm and avoids overspeed problems common in propeller designs. Virtually no maintenance is required, and the Lexan' vanes resist sun. snow sleet, and extreme temperatures. Assembly is easy with regular hand tools.

A free Information package and further Information are available from Thermax Corporation, One Mill Street, Burlington VT 05401. Reader Service number 481.

### SUPER-RATT SOFTWARE

With the Super-Ratt radioteletype and CW program for the Apple II, you can have your own RTTY RBBS statton on line quickly and easily, according to Universal Software Systems. Super-Ratt is the lowestpriced RTTY/CW program which also contains a full radio builetin board system.

The program will operate in ASCII as well as Baudot at any speed from 40 to 300 baud. CW speeds range from 5 to 100 wpm, with an automatic speed adjust on receive.

The program may be run In either manual or RBBS modes. Extensive use of disk files permits storage of "canned" material for



The helius rotor kit by Thermax for low-cost wind power.

manual operation. In the RBBS mode, the system automatically saves nearly one hundred user messages to the disk. There are thirty-flve different commands on the RBBS. They are all simple English words and quite memorable.

Almost any modern terminal unit or converter, such as IRL, Flesher, Kantronics, HAL, or others can be used with Super-Ratt as well as such devices as the "RADCOM" card by AF6W. The program is not protected against copying. The Basic portion may be listed and modified to suit your tastes. (The registered owner's call is installed in the machine code by the factory.)

A free one-year subscription to the user newsletter, *The Ratt's Nest*, is included in the purchase price of \$59.95, which also covers shipping via UPS or first-class mail.

For a complete data sheet or other Information, write or call Universal Software Systems, Inc. 9 Shields Lane, Ridgefield CT 06877: (203):438:3117. Reader Service number 488.



The portable Earth station—in operation.



The portable Earth station from Gillaspie and Associates-ready to put up



The Synchronar 2100 solar watch.

### SOLAR WATCH

Right Time Corporation has just announced a new technological breakthrough In wristwatches, the Synchronar 2100, powered by the sun and programmed to the year 2100 with no resetting required, even for daylight saving time or leap-year adjustments. Miniature silicon solar cells automatically gather and store energy from the sun, daylight, or even an ordinary lightbulb, and this energy is used to drive a complex integrated circuit. The solar cells also measure the ambient light and adjust the brightness of the readout so that it may be viewed under any lighting conditions ranging from full sunlight to total darkness. Synchronar's system totally eliminates the problem of battery replacements, and even if left in a drawer for months. It will continue to operate

Synchronar 2100 has dual time zones and is available in either standard or international time modes or a combination of both. It is guaranteed accurate to within plus or minus four seconds per year. An exclusive self-calibration system enables the wearer to adjust the watch to run faster or slower, should environmental extremes require recalibration.

A discrete alarm system, or "polite" alert, is provided which, at a prescribed time, causes the display to flash on and off for a period of one minute. Synchronar 2100 features a patented, totally-sealed construction in which all electronic systems are encapsulated within a transparent Lexan' module which can withstand shocks up to 25,000 G and water depths up to 750 feet.

Light enters the top surface of the transparent module and charges the solar cells, and the lighted display shines out through the edge above the band, providing a naturally-positioned side view. Control switches are magnetically operated from outside the watch, meaning that the seal of the module is never broken.

For further information, contact *Rlehl Time* Corporation, 53 South Jefferson Road, Whippany NJ 07981. Reader Service number 485.

### RADIO RACK

The Gulld Radio Rack comes In finlshed solid ash. No assembly Is required. Gulld's rack comfortably holds Kenwood's TS8305/ VF0230/SP230 or TS820 series, or any similar rigs. Exact measurements are (overall) 16-7/8" W times 14-3/4" H times 14-1/2" D; (top compartments) 7-1/2" W times 6" H, and (bottom compartment) 15-5/8" W times 7" H. It is also fully vented.

For more information, contact Guild Radio Rack, 225 West Grand St., Elizabeth NJ 07202; (201)-351-3002. Reader Service number 487.

### TRIBAND BEAM

TET Antenna Systems has announced that their top-of-the-line HB35T triband beam is now available. This is a 5-element dual-drive antenna for 20, 15, and 10 meters. With the dual drive concept, both the radiator and the reflector are driven with a phase difference that provides extra gain and improved front-to-back ratio.

The beam has only one pair of traps per element for simplicity and reiiability. The trap capacitors are coaxial rods mounted inside the elements to give low losses and weatherproof operation.

The HB35T has a 25' boom, weighs 50 lbs., and provides excellent gain for DX work.

For further information, contact TET Antenna Systems, 1924E W. Mission Road, Escondido CA 92025. Reader Service number 480.

### HAMTRONICS FM REPEATER

Hamtronics, Inc., has announced the availability of the REP-100 line of complete repeater packages, including all the hardware and controls.

The REP-100 is constructed on a 7-inch rack panel, with an uncluttered control arrangement. Electrical features include excellent sensitivity (0.15 uV at VHF and 0.2 uV on UHF), both 8-pole crystal filter and ceramic filter for  $\pm$  12 kHz at - 100 dB, afc and hysteresIs squelch to lock onto driftIng or fadIng signals, a clean, easy-to-tune transmitter, and up to 20 Watts output. A proportional-controlled crystal oven option provides 2 ppm frequency stability down as low as  $-30^{\circ}$  C ( $-22^{\circ}$  F), If needed.

The REP-100 repeater is available for the 6m, 2m, 220-MHz, and 440-MHz bands and



#### The Guild Radio Rack

adjacent frequencles. It is available also in configurations for remote linking and crossbanding, including 10 meters. The 2m and 220-MHz models employ a 3-section helical resonator in the receiver front end. The UHF version uses 6 tuned lines in the receiver. (That is Important if you share a site with other transmitters.)

A complete catalog on the REP-100 repeater, and other information, is available from Hamtronics. Inc., 65-F Moul Rd., Hilton NY 14468-9535; (716)-392-9430. (For overseas mailing, please enclose \$1.00 or 4 IRCs.) Reader Service number 491.

### SATELLITE TV ANTENNA KIT

Ghost Fighters, television antenna specialists, has announced the Space Cowboy P-600 series of parabolic antenna kits.


The Space Cowboy P-610 is a 10-foot hex-

agonal parabolic microwave antenna specifically designed to receive signals from all the domestic satellites, with over 60 channels of video and audio programming to choose from. It tracks the satellite orbit belt on a polar mount and changes from satellite to satellite in seconds. This kit is for the home-video enthuslast who wants to save money and have the satisfaction of building.

The P-610 model, compared with most 10-foot fiberglass dishes, has a surfaceintercept area 10% larger and a longerthan-average focal length, Surface accuracy Is proofed-on-site and fully tunable over the entire surface on a point-by-point basis (patent pending) for maximum galn and good plcture quality. The surface is heavy-duty galvanized steel screen. The P-610 is a true parabolic reflector with at-



The Hamtronics REP-100 repeater.

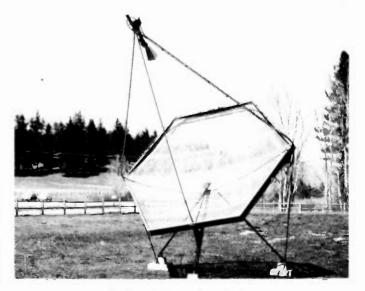

The Space Cowboy by Ghost Fighters



DenTron's MLX Mini transceiver

tached feedhorn assembly and adjustable polar mount for easy selection of satellites.

The klt comes complete with all materlals pre-cut and ready for assembly. Some portions of the assembly will require two persons. Assembly and installation of the antenna can be accomplished by the average homeowner in a weekend or two. The polar mount is set on three concrete footings requiring 4 to 6 bags of pre-mix concrete.

Other models in the P-600 series include the P-613 and P-616 (13- and 16-foot antennas respectively).

For further information, contact Ghost Fighters, TV Antenna Specialists, Route 2. Box 136-B, Stevensville MT 59870: (406)-642-3405. Reader Service number 479.

### **NEW MICRO SIDEBAND** TRANSCEIVER

DenTron Radio Company has announced production of its new mini-sized, monoband transceiver. Titled the MLX Mini, It operates at 25-W PEP and 20-W CW with an LED frequency readout of ± 100 Hz accuracy. Available in models from 160-6 meters. the MLX Mini has selectivity of 2.1 Hz with sensitivity better than .35 uV for 10-dB signal-to-nolse ratio. Receiver design is the single-conversion superheterodyne type with total power requirements of 12-14 V dc.

For more Information contact Tim Neill, Technical Sales Representative. DenTron Radio Company, Inc., 1605 Commerce Drive. Stow OH 44224; (216)-688-4973. Reader Service number 482

### GLOBAL'S DIGITAL PULSER KIT

The DPK-1, a new digital pulser kit designed for use as a pulse injector in stimulus/response testing of digital circuitry, has been introduced by Global Specialties Corporation.

This pulse generator is a portable test instrument featuring multi-logic-family compatibility: It operates on both TTL and CMOS circuits. Its pulse width is 1.5 seconds ± 30% for TTL and 5-V CMOS and 3.0 seconds ± 30% for 15-V CMOS.

One touch of the pulse button and the DPK-1 attempts to Inject a positive pulse. then a negative pulse. One of these pulses is ignored, depending on the logic state the DPK-1 output is biased at (determined from node under test). Keep the pulse button depressed and after one second the DPK-1 delivers a continuous pulse train of positive and negative pulses at a rate of 150 pulses per second. In the same manner as the single-shot event, one of these pulses will be ignored, leaving a positive- or negativegoing pulse train at a 75-pulse-per-second rate.

An LED indicator flashes once to confirm single-pulse output and remains on for continuous pulse train confirmation.

Pulse voltage level is determined by the current requirements of the node under test. The DPK-1 output pulses are capable of sinking or sourcing up to 100 mA, which Is sufficient drive to permit forcing most nodes to an opposite state without desoldering.

This digital-pulse generator offers shortcircuit protection. High impedance output (minimum, 20-meaohm) when not pulsing allows the DPK-1 to pulse into a short circuit continuously without damage.

The DPK-1 is circuit-powered at 5-18 V dc from Vcc of the circuit under test. A power cable, wired directly into the unit, terminates in two color-coded vinyljacketed alligator clips.

The DPK-1 digital pulser comes as a complete kit, including all parts, solder, wire, PCB, etc., and a comprehensive construction and operating manual. Kit construction and testing can usually be completed In one to three hours. Its dimensions are 5.8" x 1.0" x 0.7", and it weighs 3 oz.

For further information, contact Global Specialties Corporation, 70 Fulton Terrace, PO Box 1942. New Haven CT 06509. (203)-624-3103

### AIDS FOR THE BLIND AMATEUR

Although many textbooks have been translated into braille and onto recorded media, blind hams, technicians, and scientists are faced with the continual frustration of obtaining current and supplemental materials

The Rehabilitation Engineering Center publishes a newsletter quarterly in braille. large print, and recorded form which will serve as a guide to the current technology as applied to the needs of the blind and persons with impaired vision. The newsletter. called Technical File, facilitates the pursuit of electronics interests among technicallyoriented, visually-impaired persons by serv-Ing as a reference source, a teaching tool. and a hands-on guide for construction projects through lists of materials already transcribed, catalog abstracts, data on integrated circuits, manufacturers' applications notes, and construction details, to list just a few of the contents.

General interest, do-it-yourself descriptions of such processes as soldering, project layout on circuit boards, and the use of power tools focus directly on techniques



Global's digital pulser kit. 142 73 Magazine • December, 1982

"Vocational Aids Catalog" were among the features. Bill Gerrey's "Editor's Corner" and "Editor's Crystal Ball" are always popular.

used by the blind. The articles in Technical

File are submitted by readers, trainingfacility personnel, and other interested pro-

In the Winter, 1982, Issue, for example,

"Soldering, Part IV," "Singing Chips," "A

Tactile Read-Out for Digital Instruments,"

"Earphones for the Blind Traveler." and

fessionals and non-professionals.

For your subscription to the Braille Edltion (\$12 per year), the Large PrInt Edition (\$12 per year), or the Talking Book Edition (\$6 per year for half-track cassette, 15/16 IPS) contact Bill Gerrey. Editor, Smith Kettlewell Eye Research Foundation. 2232 Webster Street. San Francisco CA 94115. Reader Service number 476.

### PROHAM'S FASTRAK ELECTRONIC KITS

Proham Electronics, Inc., has just introduced a new line of electronic kits dubbed the Fastrak\* series, wherein each kit is a functional building block that can be assembled in less than one evening. Fastrak modules are for the novice and experienced home-brewer alike, providing not only versatility but complete documentation as well. Each module is built on a commercial grade printed circuit board that conforms to the HAM (Hardware Application Module) Standard described In the May, 1982, issue of QEX magazine, and is uniform in size. Exact board dimensions are governed by the amount of space required to accomplish the Intended electronic function, but connector arrangements, bus wiring, and PCboard form factor are uniform and constant for simplicity of assembly and interconnection between units.

Fastrak modules feature a top-down system design, making it easy to configure and assemble complete receivers, transmitters. controllers, and instruments from standard "family" members. Ten Fastrak modules are available, with another ten coming within six months. Functions performed range from basic voltage-regulator and audio-amplifier modules to a 2-chip DTMF decoder and a 1-chip TV.

Fastrak kits come with complete documentation and use readily available components. For more information, write Proham Electronics, Inc., 34620 Lakeland Boulevard Eastlake OH 44094

### ICOM IC-45A SYNTHESIZED UHF MOBILE

Icom has announced availability of the IC-45A, providing FM mobile coverage of 440-450 MHz. Major features are its small slze (2" H x 51/2" W x 7" D), easy-to-read LEDs, 5 memories, priority channel, band and memory scan with automatic resume. memory backup provisions. 1-MHz upbutton for quick QSY, and variable duplex offsets. The touchtone<sup>TM</sup> microphone is included.

For more information, contact Icom America, Inc., 2112 116th Ave. NE, Bellevue WA 98004; (206)-454-8155.

### **MOBILE ANTENNAS**

Valor Enterprises, Inc., Introduced a new series of mobile high-frequency antennas at the Chicago CES Show last June. These HF mobile antennas for the professional and amateur operator are approximately 8 feet in length, and are of a heavy-duty, sllm line construction designed for HF amateur bands on 75, 40, 20. 15, and 10 meters. Heavy-gauge copper wire wound on 1/2 fiberolass with nickel-chrome brass fittings, and 17-7 taper ground stainless-steel

The Icom IC-45A synthesized UHF mobile

whips ensure dependable mobile operation. The 4' stainless-steel whip is fieldtuned for lowest vswr and double-locked with stainless-steel set screws. The antennas feature 3/8-24 ferrules to fit standard mobile mounts and are power-rated at 500 Watts PEP for top mobile performance.

For further details, contact Valor Enterprises, Inc., 185 W. Hamilton St., West Milton OH 45383. Reader Service number 484.

### RETICON ACTIVE FILTER

Applied Invention is the source for the recently introduced Reticon R-5620 programmable active filter—a complex MOS integrated circuit. The R-5620 uses switched-capacitor technology to synthesize a two-pole pair active filter that requires no external components and operates cver the range of 0.05 to 25 kHz.

The five basic filter types: low-pass, highpass, bandpass, band reject, and all-pass can all be implemented by the R-5620, and a programmable sine-wave oscillator is also possible.

Switched-capacitor filters (SCFs) are analog filters in which fixed resistors are replaced by time-division-variable switched capacitors, resulting in very stable filters that can be tuned with a variable clock source.

The simple programmability of this new SCF makes it attractive for computercontrolled synthesizers and other analog/ digital systems applications.

For additional information, contact Applied Invention, RFD #2, Route 21, Hillsdale NY 12520. Reader Service number 483.

#### YAESU'S ACTIVE ANTENNA

Yaesu Electronics Corporation recently announced the Introduction of the FRA-7700 active antenna for the FRG-7700 deluxe HF receiver.

The FRA-7700 utilizes a four-foot (1.2-meter) whip in conjunction with a low-distortion MOSFET preamplifiler, providing shortwave reception for receiver owners unable to erect an outdoor antenna. The FRA-7700 includes front-panel gain control, tunedclicult peaking, and a preamplifier on/off switch for maximum versatility.

For details on the FRA-7700, contact Yaesu Electronics Corp., PO Box 49, Paramount CA 90723. Reader Service number 486.

### RT-1100 MULTIMODE TERMINAL

DGM Electronics has just Introduced the RT-1100 receive terminal for Baudot, ASCII. and Morse. The BT-1100 converts the audio from your receiver, decodes it, and displays the words on a video monitor or TV set (using rf modulator). The RT-1100 incorporates an active filter demodulator with scope-tuning outputs. It will copy 170-, 425-, and 850-Hz-shift RTTY signals at speeds of 60, 66, 75, and 100 wpm on Baudot and 110 baud on ASCII. The unit will copy 6-60 wpm Morse signals using automatic or manual speed tracking. The RT-1100 has a parallel ASCII printer output for hard copy. The video output provides 16 lines of 32 characters per line with 2 pages. The second page is stored in memory and can be recalled by using the page 1-2 switch on the front panel. The unit has a built-in 110-V-ac power supply and is housed in an attractive 3" x 10" x 10" case with brushed, anodized front and rear panels. The cover is a gray wrinkle finish. The unit comes with a oneyear warranty on parts and labor.

For more information, contact DGM Electronics, Inc., 787 Briar Lane, Beloit WI 53511; (608)-362-0410. Reader Service number 477.

### MOBILE ANTENNA CONVERTER

JL Industries has just announced their new X-Panda-Five mobile antenna adapter, which enables the owner of a Hustler, Hy-Gain, or simllar mobile antenna to convert hls antenna to a five-bander by addlng resonators.

The X-Panda-Five consists of a precisionmachined aluminum hub fitted with five rustproof 3/8" by 24" studs made from hightensile-strength carbon steel. The hub is attached to the antenna mast, and each of the five resonators screws onto the hub. One resonator is mounted vertically and four are mounted horizontally.

When the adapter is Installed on your antenna, you can use either regular or supersize resonators and change bands without leaving the driver's seat. This assumes, of course, that you pre-tune each resonator to your favorite operating frequency in that band. No antenna tuner is required.

The X-Panda-Five also makes a good antenna for apartment houses and condominlums when fitted with the appropriate resonators and ground planes. It can be



DGM Electronics' RT-1100 receive terminal.

used to make a multiband antenna system for vans, campers, motor homes, and travel trailers. For more Information, contact *JL Indus*-

### tries, PO Box 030413, Fort Lauderdale FL 33303. Reader Service number 490. ANTENNA COUPLER

Wayne Research & Development has announced the availability of a new antenna coupler that replaces the center insulator of a balanced rf antenna system. The Wayne B-T-L antenna coupler contains an alr balun, a tapped inductor, and a variable capacitor. The coupler is housed in an ABS plastic box with a removable lid for Inspection and servicing. The strain insulator is made of Delrin" plastic.


With the aid of graphs in the Instruction booklet (supplied) and an swr meter, the user can design a matching network to match the low impedance of his loop antennas. Using the network as a T or an L, the Wayne B-T-L antenna coupler will match impedances over a frequency range from 1.8 to 30 MHz.

The insertion loss Is not more than - 0.006 dB from 1.8 to 25 MHz, and mInImal from 25 to 30 MHz. The Introductory price is



The Wayne B-T-L antenna coupler

\$49.95. For further information, contact Wayne L. Jamison W5FJS. Wayne Research & Development, PO Box 75144, Houston TX 772'34. Reader Service number 478

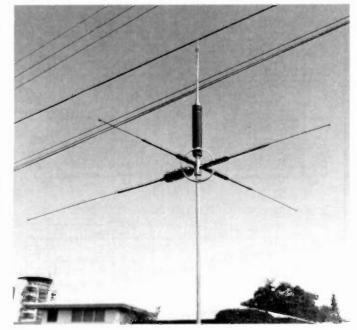




The X-Panda-Five mobile antenna adapter by J. L. Industries 73 Magazine • December, 1982 143



# CORRECTIONS

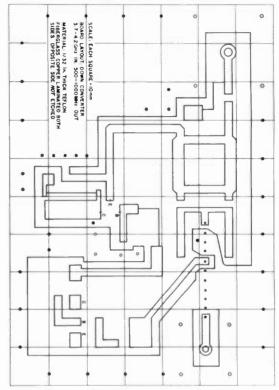

G. W. Legel's (N6TO) article "Dissertation Upon Roast Pig" (October) offers an interesting and useful suggestion for transformer salvage, but Ignores an extreme-

Old transformers were frequently filled with polychlorinated biphenyls (PCBs). This is a dangerous, toxic material that should be dealt with by trained professionals. Old, oilcooled transformers must be presumed contaminated. Unless they bear a green certification sticker, they should not be handled by

#### Tom Archer KC8MR Huron OH

Box 17

The \$100 TVRO receiver is a real winner. I'm going to build one, except for one small detail. The August issue of 73 (on page 64) has the layout of the downconverter used in Rex's "Cheap Trick." The only problem is that In Fig. 4 the scale is 10mm per division. The printed version Is 128mm long when it should be 100mm. I'm sure that was done for clarity, but it is hard to interpolate 128mm to 100mm. I'm also sure that you know the dimensions at the frequency are critical.

What I'm asking is If you have an actualsize drawing from Steve Gibson, could you print it in the next issue at 1:1? Please??

> David Lawson WA1YMC/5 Dallas TX

Here you go.-Ed

Fig. 1 in "The Vertical Deuce," on page 81 of the September issue, was drawn incorrectly. As drawn, closing the relay would put a short across the center conductor and braid of the feedline. Instead, the braid should be connected directly to ground and the center conductor should be hooked up to the coll at the opposite end from the antenna.


> Avery Jenkins WB8JLG 73 Staff

I would appreciate information on using the Interact computer in amateur radio applications.

> George W. Moran W2DGZ 950 Erten Drive York PA 17402

I need a schematic for a Majestic Falrfax model 200 superhet broadcast receiver. I will pay copy/mail costs.
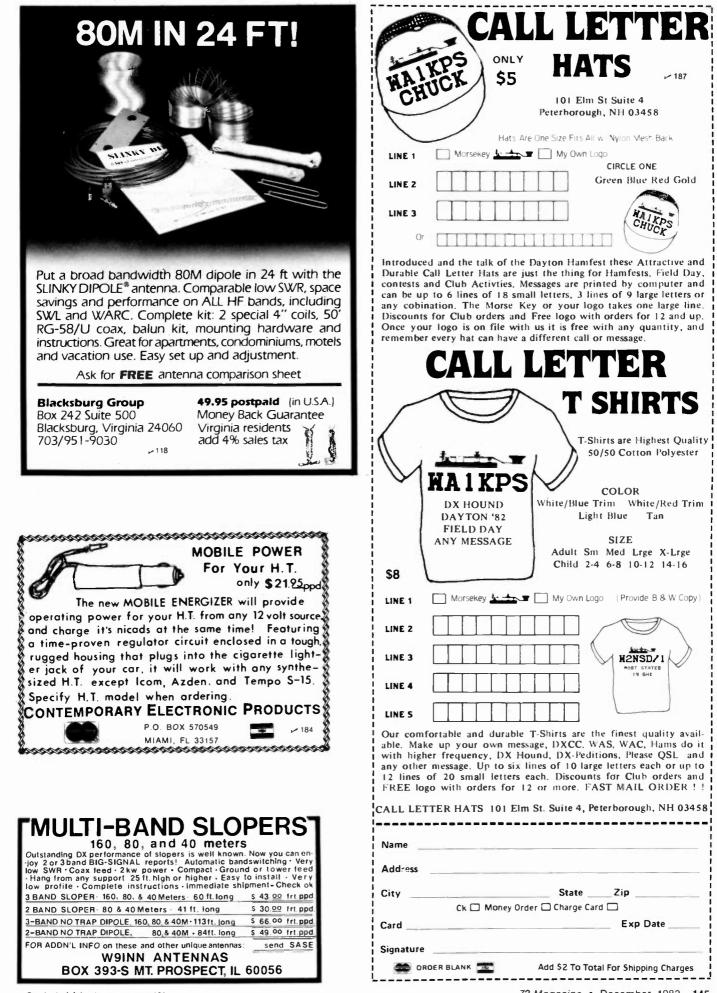
> Dan Sindort KSC 11937 McCoy Drive Omaha NE 68123



	Season's Greetings	
	UNIVERSAL COMMUNICATIONS P.O. BOX 339 ARLINGTON, TEXAS 76004-0339 (817) 860-1641	
KITSDOWN CONVERTER.\$19VARIABLE P/S.\$19CIGAR ANTENNA.\$19KIT SPECIAL(ORDER ALL THREE & SAVE).\$49HIGH-GAIN TRANSISTOR.\$10DRIFT MODIFICATION.\$10KD 44 DISH ANTENNA.\$41	9.95ASSEMBLED POWER SUPPLY\$29.959.95CIGAR ANTENNA\$19.95ULTIMATE SPECIAL9.95(ALL THREE ABOVE PRODUCTS)\$79.956.95SUPERVERTER I—CRYSTAL NOT INCL.1.25(ASSEMBLED ONLY)\$109.957.95SELECTIVE PREAMP\$26.95	
OUR PRODUCT MAY BE COPIEDBUT THE PERFORMANCE IS NEVER EQUALLED		
MC-VISA WELCOME	8:30-5:30 MON-FRI	
HOW CAN I INTERCEPT SMUGGLERS? SECRET SATELLITES? RESCUE MISSIONS? SIGNALS FROM SPACE? WHAT IS THE TRUTH ABOUT ANTENNAS? TUNERS? PREAMPLIFIERS? HOW CAN I CHOOSE THE BEST RECEIVER? ANTENNA?	CALL TOLL FREE 1-800-238-6168	
WHAT ARE THE LAWS REGARD- ING LISTENING IN? UNCOVER LISTENING EXCITEMENT YOU NEVER THOUGHT POSSIBLE!	In TN. call 901-683-9125 <b>MEMPHIS AMATEUR</b> <b>ELECTRONICS</b> (Formerly-Germantown-Sere-Rose) Authorized Dealer for: Kenwood, Icom, Drake, Mirage, AEA, Info-Tech, Ten-Tec, MFJ, and B&W.	
For your <u>FREE</u> COPY of MONITORING TIMES <u>CALL NOW!</u> Toll-free 1-800/438-8155 (cont. US except NC). Others dial 1-704/837-2216 or write to Grove Enterprises, Dept. D , 140 Dog Branch Road Brasstown, NC 28902 , 352	Used Equipment MON-FRI 9:00—5:00 SAT 9:00—12:00 Write: 1465 Wells Stat. Rd., Memphis, Tn. 38108	



INCLUDES Tone Pad Microphone and all accessories.

Shipping: \$5.00 Eastern U.S.A. \$7.50 Western U.S.A.

See List of Advertisers on page 130

tone module built-in ... and much, much more! Call or write for brochure.

80

ORDER NOW DIRECT CALL TOLL FREE

This number for ORDERS ONLY!

**DRDER DIRECT** or at your dealer!

KDK DISTRIBUTING CO., INC.

Central & South American orders: PHONE: (305) 592-7016

181

762 S. GALLATIN RD. (MADISON SQUARE SHOPPING CTR.) - MADISON, TN 37115 - PHONE (615) 865-7949 - TLX56-8652

-25

DISTRIBUTED BY

Mail Order – COD – Bank Cards Company reserves the right to change specifications

and prices without notice.

FM2030

## REVIEW

#### THE HF 10/160 SOLID-STATE PLL TRANSCEIVER

The voice at the other end of the telephone line belonged to Bruce Stwertnik, president of National Communications Group, Inc., Importers of that nice little NCG 15-meter monoband rig which was reported on in the July, 1981, 73. Now, it Isn't unusual for Bruce to call and chat, but I sensed that he had something special up his sleeve this time. After the usual chitchat, he dropped the other shoe: "Jim, I've just got a new rig in from Japan; how'd you like to put it through its paces?"

At the hInt of something new and possibly different, my mind began racing with questions such as what kind of rig? For which bands? How much power? What does it look like? How does it play? What features? You know the kind of things I mean...but I barely managed to get a few of them across to Bruce as I quickly stammered a "Sure, I'd be delighted!"

Bruce hastened to explain that this rig would be a scoop for 73 since there are only two in the States at the moment, but a lot more on the way. I was to get the first one to test and Bruce was to keep the other for himself. As a matter of fact, the English-language manuals weren't quite ready yet, he said, so I could expect only a spec sheet and a brief translation of some of the features, operating hints, and comparisons with similar rigs currently on the market.

The NCG HF 10/160 transcelver is much as one would expect. It is definitely a newgeneration transceiver, with solid-state circuitry and PLL frequency synthesis. And apparently, If one can judge from the plctures in *CO-Ham Radio*, the Japanese amateur radio magazine, It has been In use in Japan for some time.

#### **Physical Description**

148

The transceiver Is manufactured by Matsushita Electronic Industries Company Ltd., a parent company of Panasonic, among others. It measures approximately 13 inches wide by 5-1/2 inches high by 16 inches deep (if you count the massive rearpanel heat sink) and weighs just shy of 21 pounds... but walt a minute: that includes both ac and dc supplies—built in! No need for an external supply, whether you are mobile or fixed. The usual tilt bail on the bottom to raise the rig to a comfortable angle for viewing the front panel is provided, and there is the side carrying handle intended to make the rig conveniently portable. The case is dull black and has a vaguely military, i.e., functional, look. Perhaps the first thing you notice is the centrally-located spinner dial on the front panel, just below the large digital readout frequency display whose green alphanumerics are nearly onehalf lnch high and are easy to read. There are prefix letters ahead of the numbers when the rig is operated in its various modes: "C" for CW, "U" for upper sideband, and "L" for lower sideband.

The VOX sensitivity, VOX delay, and anti-VOX controls are on the left-hand side of the rig, and the VOX sensitivity control knob has a concentric switch for the 100-kHz frequency marker provIded in addition to the synthesized readout, because this permits the on-board phase-lockedloop circultry to be zeroed against WWV, for example.

The new bands are provided for as well, and the rig covers all amateur frequencies with generous overlap on the ends for MARS or other use. The S-meter dial is In the upper left-hand corner, and Indicates relative power output or ALC (your choice) in the transmit mode and S-meter readings In the receive mode. As a matter of fact, I think you would be particularly pleased with the S-meter, as It doesn't seem to be particularly scotch or particularly generous. Somehow, I have the feeling that it is about right—and consistent—from band to band.

The power on-off switch is a toggle in the upper left-hand corner; below the meter is a row of switches that control receiver functions such as noise blanker, meter scale, fast-slow agc, and tuning rate. The tuning device is an optical chopper which permits simple dial lock to a desired frequency simply by disengaging the manual dial. There is a tuning-rate switch that permits you to tune each band in 25 Hz, 100 Hz, or 1-kHz increments. Right next to that manual selector is an auto-tuning switch that functions in the up or down modes, and changes frequency at the rate selected by the adjacent rate switch. I never thought I would need-or want-such a device, but It's handy and I use it a lot

Below the switches just mentioned are the microphone connector (standard Japanese 4-pin) and the phone jack (standard 1/4-inch diameter) right next to it. Then comes the key jack, which uses the smallerdiameter plug of the size used to plug in speakers and the like (I believe it is 158" diameter). Fortunately, another rig I tested recently had this size key jack, so I was ready, but on the *front* panel? Why there of all places? The answer is simple—convenience; I realized that as I recalled the many times I have fumbled around the back of a rig in the dark trying to find the key lack.

The HF 10/160 has a built-in speaker placed on the bottom plate of the rig, and a lack for an external speaker should you wish to use one. I found the audio quality to be quite good, even with the small enclosed speaker...and that certainly is the way to go for portable/mobile...unless or until you wear headphones, of course. An external speaker is normally used in my shack, however, so I used that for the evaluation.

Next to the key jack is the mode-selector switch—permitting wide or narrow CW and upper or lower sideband...you have to choose which. On the dial escutcheon you will find two small push-buttons that activate the dial lock (left button) and the TX/RX REV switch. On the upper right-hand side of the panel you will find the Delta F switch and the RX offset switch (RIT).

The Delta F control corresponds to the receiver incremental tuning control (RIT) on the other rigs. By pushing the switch, a red LED comes on to show that the circuit is activated. Now, by varying the Delta F knob, you can adjust the receive frequency higher or lower than the dial-set frequency by about 1 kHz.

The TX/RX REV control permits further adjustment of the transmit or receive frequencies separately. When the switch is depressed, a red LED is illuminated to show that the circuit is active. Here's how it works. Suppose you want to leave your transmit frequency where it is but wish to change the receive frequency. Push in the TX/RX REV switch to lock the transmitter frequency on the existing dial setting. Now the receive frequency can be adjusted by the main tuning dial. This gives the effect of a dual vfo, and permits you to set the transmitter "up five," for example, when working DX on a split frequency, and then use the receiver and main dial to tune the DX station. If you wish to listen to your frequency momentarlly, turn the TX/RX REV switch off, and presto, you're back on the transmit frequency with the receiver

The memory-selection push-buttons are next, and require a separate discussion—so we'll come back to them later. You should know, however, that you can store up to four different frequencies and scan between any part of them at a variable rate, using "autowatch."

If you really want to get fancy about all this, you can use all these features In concert: TX/RX REV, Delta F, and memory select. I am sure that an accomplished dial twister and button pusher could really play a symphony on this rig after a few evenings of practice. Versatility is the name of the game with the HF 10/160 from NCG, and It's unlikely you will run out of permutations and combinations to try.

The main control knobs of the trans-

celver lie below the switches, and include in the top row: transmit frequency variation (Delta F), i-f tuning ( $\pm$  1 kH2) and the audio/rf gain controls on concentric shafts for the receiver; and in the bottom row: the mike gain/CW carrier-control knob, the audio-compressor/speech-processor control, and finally the bandswitch covering 1.8-29.7 MHz.

I found that all controls fall more or less conveniently to hand, and that if you have used any of the modern solid-state rigs from Japan, you will find everything about where you expect it. I was Impressed with the nice manual tuning feel and the utter simplicity of using the rig.

#### **Electrical Description**

The NCG HF 10/160 contains 30 integrated clrcults, 6 FETs, and 124 diodes/transistors. Power consumption is nominally 50 Watts on receiving in the ac mode, and 0.6 Amperes current drain in the dc mode. Transmitting consumes 550 Watts in the ac mode, and 20 Amperes current drain in the dc mode. Nominal dc voltage requirements are 13.8 volts (negative ground) at 20 Amps—enough to require that you have a battery charger, if portable, or a good alternator system if mobile and operating at the full-power capability. Ac requirements are the usual 120 volts. 50 cycles.

#### Band Coverage

The HF 10/160 covers 1.8-2.0 MHz in the 160-meter band, 3.5-4.0 MHz in the 80-meter band, 7.0-7.3 MHz in the 40-meter band, 10.0-10.5 MHz in the 30-meter band (providing some general reception, too), 14.0-14.35 MHz in the 20-meter band, 18.068-18.168 MHz in the 17-meter band, 24.89-24.99 MHz in the 15-meter band, and 29.0-29.7 MHz in the 10-meter band.

Stability is given as less than  $\pm 200 \text{ Hz}$  within one hour and less than  $\pm 20 \text{ Hz}$  after one hour. A comment about the extraordinary frequency stability was received from a ham on 40 meters who had been listening to me for a half an hour. He mentioned that my frequency as measured on his frequency meter had not changed one cycle during the entire time he had been monitoring! This means that both voltage and temperature stability is excellent. The comment, by the way, was unsolicited.

#### Transmitter Description

The final-stage input is 200 Watts (160-12 meters) and 100 Watts on 10 meters. Balanced-type modulation is used, and carrier suppression is more than 40 dB. Sideband suppression is more than 50 dB, and spurtous radiation is at a level below - 40 dB. Microphone impedance is about anything you want, and a range of 600 to 50k Ohms is acceptable. The output connector for rf is the usual 50-Ohm UHF type SO-238.



NCG's HF 10/160 transceiver. 73 Magazine • December, 1982

-			
Feature	NCG 10/160	TS-830	FT-101
Tuning	PLL-synthesized	Vfo (capacitor)	Vfo (capacitor)
Power Supply	Ac/dc bullt in	Ac	Ac (dc optional)
Weight	21 pounds	30 pounds	32 pounds
Dimensions			
$(H \times W \times D)$	5.2 × 2.68 × 12.44	5.24 × 13.11 × 13.11	6.18 × 13.58 × 12.83
Frequency memory	Yes	No	No
Autoscan	Yes	No	No
Dual vfo	Yes	No	No
Tuning rate	3-step	N/A	N/A
Passband tuning	No	Yes	Yes
I-f tune	Yes	Yes	No
Notch filter	No	Yes	Yes
CW/af	Yes	No	Yes
Tone Control	No	Yes	No
Drift-free tune	Yes	No	No
All solid state	Yes	No	No

#### **Receiver Description**

The receiver is a single-conversion superheterodyne of the type well known for its good sensitivity and lack of images, yielding a factory-measured sensitivity figure of less than - 12 dB (.25 V) at 10-dB S/N ratio. The I-f frequency is 9.0007 MHz on CW and 9.000 MHz on phone. Selectivity on SSB or wide CW is 2.2 kHz at -6 dB, less than 3.0 kHz at - 20 dB, and less than 6 kHz at - 60 dB down, for a shape factor of about 2.7. On narrow CW, the figures are 400 Hz at -6 dB. 1 kHz at - 20 dB. and 1.6 kHz at - 60 dB, respectively. This gives a shape factor of about 4:1 for narrow CW. The narrow CW option could not be observed at the time of testing because the sharp filter had not yet been received.

Spurious images are down more than 60 dB, I-f rejection is likewise more than 60 dB, and other spurious response is down more than 70 dB.

With the built-in speaker (nominal 8-Ohm Impedance), the audio output power is 0.5 Watts (10% THD) and with an external speaker, the audio output power is t Watt (16% THD).

#### Using the Rig

This report is necessarily a preliminary and admittedly sketchy evaluation because the manual I have Is in Japanese. The English versions should be available (along with the rigs) by the time you read this. In spite of, or perhaps because of, the lack of an English-language manual, I found that I pald more careful attention to the drawings and photos than usual. These are abundantly clear, and it would be almost impossible to set up the rig incorrectly if you have had any experience at all in putting a "transceiver-from-the-box" on the air.

Carefully unpacking the rig from the usual sanitary plastic bags and foamshettered security of the container, I found a separate bag containing the microphone and still another small box with the ac and dc power cords inside. Selecting the ac cord, I plugged It into the polarized multipin socket on the back. My ground wire was put on the terminal, underneath the usual washer and wing nut. The microphone plugged into the usual 4-pin front-panel connector.

One obtains a first impression of any rig as it comes from its cocoon, and this one was no exception. Its general appearance, weight, and feel lend the impression that It is functional and business-like, with Its matte black finish and vaquely military look.

Being a CW man at heart, I wanted to try that mode first, so I plugged my electronic keyer Into the rig, switched the operate switch to VOX, and set the sensitivity control and delay control for comfortable semiautomatic break-in. Keying the rig produced a fine sidetone—pleasant to the ear—and my power-output meter showed a power output of approximately 70 Watts on 40 meters. A quick twist of the Mic Gain/CW CAR control brought the output to 100 Watts. The stations I worked on 80, 40, 20, and 5 meters ail reported fine keying and good solid signals with a nice CW note.

The only small objection I had was from an operator who claimed that on the initial make (when the relay came on) there was a slight frequency warble which disappeared once the relay held in. (This will be corrected in subsequent production rigs.) However, if you choose to set the VOX delay to a long duration, there will be only one little warble at the beginning of the first character. This would also be true, of course, in the manual mode, and thereafter you should hear no complaints. Not having heard this myself, I can only report what that one operator told me. Significantly. perhaps, no one else mentioned It.

I was somewhat bothered by the lack of a narrow-CW filter, but I found that I could operate in all but the worst of crowded conditions by using the i-f shift control to move the i-f window into a better location with respect to the carrier. This gave the impression of an improved selectivity by removing part of the bandpass through which extraneous signals could slide. All in all, I found CW operation very satisfactory, and was delighted to be able to work about anything I could hear. Although I did not find the sidetone pitch and volume controls which are internal, I must confess that I didn't search for them either. Once the Englishlanguage manual arrives, it will be a snap to adjust them to one's own special comfortable listening level and tone. With earphones on, I found everything to be exactly right, so I didn't bother trying to change them

Single-sideband operation is where this rig really shines. I am not much of a phone operator, and because of this I was perhaps a bit overconcerned about the modulation and signal levels that I would be able to produce. I needn't have worried; each report was outstanding.

The first evening of sldeband operation went somehting like this: "W1XU, this is W—; you are five by nine here. By the way, what rig are you running? The audio is outstanding!" (Mic Gain control positioned at 10 o'clock.)

"W—, this is W1XU right back. Thanks, OM, for the fine report. The rig is a new one undergoing test for 73. I'm not at liberly to tell you the make and model just yet, but I can tell you it is nominally a 100-Wattoutput rig, made offshore."

(Breaker)"W1XU, this is K---; what kind of rig did you say you were running? The audio is superb. Are you running a processor?"

"K----, thanks for the good report. I appreciate it. Can't tell you what the rig is, but you'll read about it in 73 one of these months."

(Breaker) "W1XU, this is W--. I just wanted to tell you that I have been listening to you for half an hour, and your frequency Is rock steady. You haven't varied by one cycle since I started listening. I also wanted to tell you that your rig Is super, whatever it Is."

(Later that evening) "W1XU, this is WA-.... Your audio certainly doesn't sound any better with that compressor in your circuit. In fact, it sounds better without it. Are you sure you don't have some audio processing? It's crystal-clear and has magnificent 'ounch.' "

Rather than bore you with further reports of the same or similar content. I'll just mention that every report has been outstanding. I have been very careful about avoiding requests for an audio quality report, and each one was unsolicited. In spite of the fact that I consider myself a dyed-in-the-wool CW operator, this rig has gone a long way to turn me back to SSB. Maybe It will help to understand that when I admit that my voice is one of those mid-range voices that could be described as soft-spoken. It does not "talk up" a rig like many that you hear. In fact, I usually use a mike amplifier to help out. but with this rig it surely isn't necessary and probably is not desirable.

Of course, being solld-state, no tune-up is required, and full output is achieved into a matched antenna. I did not notice any swr shutdown protection at swr values up to about 1.5 to 1. Inadvertently, I once attempted to transmit with the antenna shorted to ground. Obediently, the finals shut down, and—fortunately—no damage was done. This was immediately obvious by the power output meter, which didn't even flicker. Not having any swr values in the 3:1 range, I can't be sure at what point shutdown began, but I would guess that 3:1 would result in a power output of about 50 Watts or less ... in other words, a progressive protection. Nice.

The memory function had me a bit perplexed, but I got brave enough to finally give it a whirl. I dialed in two frequencies about 50 kHz apart and committed them to memory as follows: 14.007 on dial, punch the Write button, followed by button 1. t4.007 is now in memory 1 and also displayed on the screen. (Punch the vio button and you are able to dial in another frequency.) This time, I dialed up 14.012, depressed Write and button 2, followed by vfo. 14.012 was now in the memory 2 location. Next, I wanted to put in two more frequencies in memories 3 and 4... which I did, according to the previously described method. Now, by merely selecting any of the four memory buttons. I could instantly recall the frequency in memory. Nothing special, you'll agree -and about like any transceiver with memory.

Now, what about the autowatch function? Well, I pushed It-and guess what? The receiver goes into a scanning mode and scans between the two frequencies in memories 3 and 4! It scans very slowly-1 would guess no faster than about 10 Hz/second. When it reaches the top frequency it returns to the lower one and begins scanning again. Although I don't have any particular need for that feature at the moment, I can visualize a few occasions when it might be very worthwhile to have. For example: Suppose you are looking for a friend on a particular frequency, "plus or minus QRM." Just set two frequencles above and below the intended frequency and punch autowatch! When your friend comes on, you'll hear him because the scan rate is slow enough to permit call identification before it moves on. Neat.

Frankly, I have not used audio compression except on some DX contacts, where the reports have indicated an improved readability—perhaps because of the higher average power output. There were no adverse comments as there had been on local contacts.

So far, I've not been able to find the time to install the rig in the car...but may do so in time to drive to a hamfest this coming weekend. It's a longish trip—about 400 miles each way—so that should provide ample opportunity to give the rig a real mobile shakedown. I have no reason to believe that it will perform other than spectacularly.

Is this rig for you? Well, of course, it depends upon what you are looking for. Certainly it has many nice features, including some that aren't available in the run-of-themill modern transceiver, and it is rugged and functional. The price is competitive, as it is squarely in the range of similar transceivers. I felt the dial was very satisfactory, and the knobs, switches, and controis equally so. The only picky-picky complaint I have (and this wouldn't bother anyone else, I'm sure) is that the small knobs have skirts that are decorated with a plastic trying to simulate metal...and it looks like plastic, not metal. If I were the manufacturer, I'd forget trying to dress it up with this charade. Leave 'em all black, and they'll be that much better for it.

You may find there is enough information available on the metering modes; all you get is rf output, S-meter, and ALC information. Upon further consideration, what more do you really need?

With this article is a handy comparison chart for you, between the HF 10/160 and two other contemporary rigs in the same price class. Look it over and decide for yourself whether you're interested. If you're like me, I think you will be...very much so!

For more information, contact NCG

Company, 1275 North Grove Street, Anaheim CA 92806. Reader Service number 492.

> Jim Gray W1XU 73 Staff

#### ICOM IC-290A/E ALL-MODE 2-METER TRANSCEIVER

The Icom IC-290A/E (A Is the American version and E is the European model) is just what the doctor ordered if you are looking for an all-mode 2-meter rig. It has all the features a 2-meter op could want, and even a seasoned VHF operator would be pleased with the unit. The capabilities of the IC-290 are astounding for its small size. It operates USB, LSB, FM, and CW from 143.8 MHz to 148.2 MHz. In addition to two completely independent vfo's the 290 features flve memories and a flexible band-scanning system. Yet, at 64 mm (H) × 170 mm (W) × 218 mm (D), it is smaller than many FM rigs.

#### On the Road

I had been wanting to try 2-meter SSB mobile for years, and finally had the chance the day the IC-290 arrived. So, I installed the radio and headed out on a business trip from Peterborough NH to New York. Before leaving, I programmed the memories for five of the repeaters I might encounter enroute and put vfo. A on 144.200 MHz, the calling frequency for SSB. I set vfo B on 146.52 and set the scanner for memory scan. This allowed me to scan all seven frequencies.

Although SSB during the day is not as busy as FM, there is still a considerable amount of activity, with new stations on the air every day. I could leave the rig in FM scan, and when a station came on 144.200 MHz the squeich would open and all I had to do was switch to USB to see who was calling. This system worked very well. I worked several stations between New Hampshire and New York. The added range on 2 SSB and the lack of beepers, timers, and kerchunkers is truly a pleasure. My friends on "the low end" may be upset by my publicizing their secret, but there is plenty of room for everyone. It reminds me of a bumper sticker seen on a car up here in New Hampshire after a particularly large influx of "flatlanders." "Keep NH a Secret," it read. Well, it's hard to keep a secret about something so great, and 2-meter SSB is the same.

#### **Technical Highlights**

The rf amplifier and first mixer circuits of the IC-290 use MOSFETS which allow for a receiving system that is more sensitive than any other 2-meter multi-mode rig I have tried. Unlike other transceivers, the 290 does not need a preamplifier for successful operation. I took the rig with me on a trip to Boston and tried to work a repeater in NH while in the back yard of another that was 15 kHz away. Contrary to other receivers that I had put through the same test, the IC-290 came through with flying colors. The receiver features selectable agc in SSB and CW plus a noise blanker that worked very well in removing ignition noise that was being radiated by my auto and adjacent vehicles as well.

The Icom 290 has two continuous-tuning vlo's. What this means is that when you get to the end of the tuning range (i.e., 148.200) the vfo automatically switches to the pottom edge (143.800). This feature saves a lot of time if you are on 147.51 MHz and you want to QSY to 144.220 MHz. In the SSB and CW modes, quick tuning in 1.kHz steps is available or, with a push of the front panel tuning rate switch, fine tuning in 100.Hz steps. On FM, the tuning knob has click stops which allow for eyes-on-the-road tuning.

priority switch allows you to sample any one of the memory channels every five seconds, regardless of whether the scanner is on or another frequency is being listened to. The S-Meter/Rf-Output Indicator is of the currently-popular LED-bar type

The transmitter in the IC-290 has a high output of 10 Watts. By pulling out on the squeich knob, you are in low power which comes through from the factory set at 1 Watt and is internally adjustable. Transmitted audio reports that I received were all favorable. The repeater offsets are controlled by two front panel switches. To the left of the main tuning knob is a three-position offset switch, selecting either up, down, or simplex. The offset frequency is selected by placing the mode switch in the Offset/Write position and dialing the main tuning knob to the desired offset frequency Then you return the mode switch to the FM position and your offset is set until you change it. Internal transmitter controls include everything you should need from deviation-adjust in FM to CW sidetone-adjust.

icom has provided an excellent operating manual. It includes Inside photographs with all internal adjustments very well labeled. In fact, the manual Is so good that Jeff DeTray WB8BTH used it to describe to me over the phone where the deviation pot was located. The manual with all its descriptive pictures was at his house and the rig was on my bench. He found the pot and described to me exactly where it was in just a matter of seconds. There is no need for an extra-cost service manual just to make adjustments.

With the IC-290A/E, Icom has once again demonstrated its ability to pack many features into an extraordinarily small package. And yet they've done it without sacrificing operator convenience. As the sunspot cycle declines and all-mode rigs proliferate, we can expect to see more and more SSB and CW activity on 2 meters. Radios like the IC-290 will bring lots of new blood to the low end of two

For further information, contact /com

America, Inc., 2112 116th Ave. NE, Bellevue WA 98004; (206)-454-8155.

> Bob Cunningham K1XR 73 Staff

#### **HF ANTENNAS** FOR ALL LOCATIONS

L. A. Moxon G6XN scarcely needs an in troduction to at least two generations of antenna enthusiasts. His fascinating descriptions of antennas of all kinds, ranging from beams to vertical and from wire antennas to space-saving and "hidden" antennas. have inspired thousands of radio amateurs in this country and abroad to try their hand at just one more antenna. More often than not, the G6XN antenna will exactly fit the requirements and will perform at least as well as-and sometimes better than-whatever you may have tried before.

Les Moxon's articles, sketches, and ideas have appeared in the RSGB publications, in QST, and in collections and manuals everywhere. Now, at last, we have the man all by himself in a book that is bound to become a must for the bookshelf of every right-thinking antenna experimenter: HF Antennas for All Locations, published by the Radio Society of Great Britain, 35 Doughty Street, London WC1N 2AE, England (\$12).

Here is a book you can really get your teeth into-one that you can use to answer questions you may have about a particular aspect of theory or to build a practical antenna from a concise sketch with exact dimensions for the frequency of your choice. Not only that, the English seem to have a unique way of making difficult subjects seem very simple, and Moxon's book is no exception. His explanations and drawings of the ionosphere, for example, are quite fascinating, and show a threedimensional space in two dimensions by some very clever art work.

Let's for just a moment peek into the contents and see what's there that may interest you and have application to your par ticular situation. (I'm convinced that Les has something for every antenna taste and persuasion.) The book Is divided into two basic parts. Part I is titled "How antennas work," and covers in ten chapters the following subjects: Taking a new look at HF antennas; Waves and fields; Gains and losses; Feeding the antenna; Close-spaced beams; Arrays, long wires, and ground reflections; Multiband antennas; Bandwidth; Antenna design for reception, and The antenna and its environment.

Part II covers "Theory into practice," and includes these chapters: Single-element antennas; Horizontal beams; Vertical beams; Large arrays; Invisible antennas; Mobile and portable antennas; What kind of antenna?; Making the antenna work, and Antenna construction and erection.

As you can see, there's enough material there to fuel your winter's needs for reading matter, and sufficient practical "how to" information to occupy several year's worth of summertime building frenzy.

Take the first chapter in Part I, for example, which invites the reader to take a new look at HF antennas. Just what does Les Moxon mean by a new look? Well, let him speak for himself

"Amateurs have been using HF antennas for 60 years or more so that some slowing down in the rate of progress might be expected. As evidence of this, some of the best antennas in use today were designed 20 to 30 years ago yet, impelled by strong incentives, the search for the 'better' ones continues unabated. At times of slow progress it is not a bad idea to look at problems from new angles, and a possible first step is to erase from one's mind the picture of 'things as they are' and concentrate, for a few moments at least, on the way one would like them to be. Listing the reasons why they are not and challenging each in turn can be good fun; moreover, before accepting once again the status quo, one feels entitled to convincing evidence that there are no alternatives

In the following pages the reader will

find few such proofs but Instead several challenges to existing beliefs and practices, 'proof of impossibility' being reserved mainly for the antenna gain figures frequently claimed by authors and advertisers

Les then goes on to explain that weight. size, and cost of beam antennas must be considered to be fair game for investigation and that a reduction in these values without compromising performance is a worthy goal. Another goal is minimizing interfering signals, and G6XN questions whether that goal is incompatible with the goal of increased gain. Today's thinking suggests that there is no answer, but Les points out a new and striking possibility: Why not change the antenna characteristics between transmitting and receiving?

In fact, the contents of the book suggest that the desired objectives can be met with dipole elements only, and that loops or other configurations are not necessary-provided that one doesn't think that a straight dipole is necessary!

Well, this is just a taste of what the book holds, and it goes into great detail explaining how new configurations can be achieved, what they might look like, and what may be possible.

In Part II, there are some concrete examples given on the construction of minimum-size antennas that more or less fulfill the promise of the earlier portion of the book. Whatever your antenna problem may be or however limited your space or budget, G6XN has something for you.

No one suggests or would dream of suggesting that HF Antennas for All Locations is a panacea for antenna problems, but it is interesting and requires some study. I'd be willing to bet that seventyfive percent of us could greatly improve our HF antenna installations by reading what Les Moxon has to say. Ask your book dealer today to get you a copy. Reader Service number 493.

> Jim Gray W1XU 73 Staff

CONTESTS

Robert Baker WB2GFE 15 Windsor Dr Atco NJ 08004

#### CONNECTICUT QSO PARTY

#### Starts: 1100 GMT December 4 Ends: 1100 GMT December 5

Sponsored by the Candlewood Amateur Radio Association (CARA). Phone and CW are considered to be the same contest. Sta tions may be worked once on each band and each mode

#### EXCHANGE

Send QSO number and ARRL section or Connecticut county.

#### SCORING

Out-of-state stations multiply total QSOs by the number of Connecticut counties worked (8 maximum). Connecticut stations multiply total QSOs by the sum of ARRL sections and provinces. Additional DX contacts count for QSO points but only one DX multiplier overall is allowed. W1QI, the club station, will be operating CW on the odd and SSB on the even hours, and counts as 5 points on each band and mode. Novice con tacts count as 2 points each and OSCAR contacts count 3 points each.

#### FREQUENCIES

CW-40 kHz up from the bottom of each band.

SSB-3927, 7250, 14295, 21370 and 28540 Novice-3725, 7125, 2119, and 28125

ENTRIES & AWARDS.

A Worked All Connecticut Counties certi-

ficate will be awarded to each station working all the counties. Other awards given as usual, minimum of 5 QSO points! Logs must show category, date/time (GMT), stations, numbers, bands, QSO points, and claimed scores. Enclose a large SASE for results. Logs must be postmarked by January 2nd and sent to Steve Grouse KA1ECL. 3 Queens Court, Danbury CT 06810

#### CANADA CONTEST Starts: 0000 GMT December 19 Ends: 2400 GMT December 19

Sponsored by the Canadian Amateur Ra

## CALENDAR

ARRL 160-Meter Contest Connecticut QSO Party ARRL 10-Meter Contest **CARF** Canada Contest 73 Magazine 40-Meter World SSB Championship 73 Magazine 80-Meter World SSB Championship World Communication Year Amateur Radio Activity 73 Magazine 160-Meter World SSB Championship Hunting Lions in the Air Contest **QRP CW Contest** YL ISSB QSO Party-CW **RTTY World Championship Contest** YL ISSB QSO Party - Phone

dio Federation (CARF), the contest is open to all amateurs and everybody works everybody. Entry classes include single-operator allband, single-operator single band, and multi-operator single-transmitter allband. There are separate single-operator ORP (5 W dc, 10 W PEP out) and single-operator non-Advanced amateur classes.

Use all bands from 160 to 2 meters on CW and phone combined. All contacts with amateur stations are valid. Stations may be worked twice on each band, once on CW and once on phone. No crossmode contacts, and no CW contacts in the phone bands are allowed

#### EXCHANGE


Signal report and consecutive serial number starting with 001; VE1 stations also should send their province (NS, NB, PEI).

#### SCORING

Score 10 points for each contact with Canada, 1 point for contacts with others. VEC counts as Canada. Score 10 points for each contact with any CARF official news station using the suffix TCA or VCA. Multipliers are the number of Canadian prov-Inces/territories worked on each band, on each mode (12 provinces/territories x 8 bands x 2 modes for a maximum of 192 possible multipliers). Contacts with sta-

Dec 4-5 Dec 4-5 Dec 11-12 Dec 19 Jan 8 Jan 9 Jan 15 Jan 15-16 Jan 15-16 Jan 15-16

Feb 19-20 Feb 26 Mar 12-13

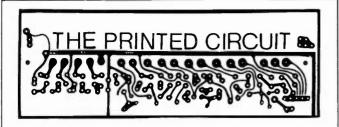

#### NEWSLETTER OF THE MONTH

This month's winning newsletter is the *Printed Circuit*, published by the Lubbock Amateur Radlo Club in Lubbock, Texas.

As well as its unique masthead, the *Printed Circuit* offers a variety of features not found in most newsletters. For example, one Issue features a full-page profile of a local old-timer, which was followed by a column on personal computers.

Not leaving out other areas of interest, the editors of the *Printed Circuit* Included a story on amateur participation in a recent disaster drill and devoted another full page to DX news and propagation predictions.

And that's not all-There is also a regular technical column, public service announcements, repeater update, puzzles, and a monthly activity calendar.

One sure way of divining the success of a publication is by the activity of its letters section, and the *Printed Circuit* is not lacking in that area, either. Many newsletter editors must dream of getting the number of letters received by the *Printed Circuit*.

To top It all off, the *Printed Circuit* publishes a Q & A session with "The Old Ham." The Old Ham addresses timely and pertinent subjects, such as what to do In a Toronado warning and how to tell a Toronado from a Chevy.

Hats off to Becky Swann WD5KBO and her staff for putting out a newsletter with more stuffed into it than a five-flavor banana split.

73 encourages clubs to send in their club newsletters. Just address them to 73, Pine Street, Peterborough NH 03458. Keep us up to date with what is happening in your area, and maybe even win the Newsletter of the Month contest.

tions outside Canada count for points but not multipliers.

#### FREQUENCIES:

Phone—1820, 3770, 3900, 7070, 7230, 14150, 14300, 21200, 21400, 28500, 50.1, and 146.52.

CW-1810, 3525, 7025, 14025, 21025, 28025, 50.1, and 144.1.

Suggest phone on the even hours (GMT), CW on the odd hours (GMT). Since this is a Canadian-sponsored contest, remember to stay within the legal frequencies for your country!

#### AWARDS:

A plaque will be awarded to the highest score single-operator, allband entry. Certificates will be awarded to the highest score in each category in each province/territory, US call area, and DX country.

#### ENTRIES:

A valid entry must contain log sheets, dupe sheets, a cover sheet showing claimed QSO points, a list of multipliers, and a calculation of final claimed score. Cover sheets and multiplier check lists are available. Entries should be mailed within



#### 1982 A5 MAGAZINE WORLDWIDE DX SSTV CONTEST

1st DX 1st US	FM7CD KE1Y	1622 pts. 810		
2nd	VE4ADG	453		
3rd	KB6WP	410		
4th	VE3JW	368		
5th	WD9IPX	331		
(63 entries total were received) Next SSTV contest is the WAS				
SSTV in January.				

one month of the contest, with your comments, to: CARF, PO Box 2172, Stn. D. Ottawa, Ontario K1P5W4, Canada.

Results will be published In TCA, the Canadian amateur magazine. Non-subscribers may include an SASE for a copy of the results.

#### 2ND ANNUAL 40-METER WORLD SSB CHAMPIONSHIP

#### Starts: 0000Z January 8 Ends: 2400Z January 8

#### SPONSOR:

73, Peterborough, New Hampshire 03458.

#### MISCELLANEOUS RULES:

Work as many stations as possible on 40-meter phone during the specified times of allowable operation. The same station may be worked once. Crossmode contacts will not count. Single-operator stations may operate a total of 16 hours. All the multi-operator stations may operate the entire 24hour period. Off periods must be noted in your log(s) and on your summary sheet. Off periods are no less than 30 minutes each.

#### OPERATOR CLASSES:

(Å) Single operator, single transmitter, phone only. (B) Multi-operator, single transmitter, phone only.

#### EXCHANGE:

Stations within the continental 48 US states and Canada transmit an RS report and state, province, or territory. All other stations, including Alaska and Hawail, transmit RS report and DX country.

#### POINTS:

1 QSO point is earned for each station worked in the continental 48 US states and Canada or within your own country. All other contacts are two points each. List points for each contact on your logsheet.

#### MULTIPLIERS:

1 multiplier point is earned for each US

state (48 maximum), each Canadlan prov-Ince or territory (13 maximum), or DX country worked.

#### FINAL SCORE:

Total QSO points times total multiplier points equals claimed score.

#### CONTEST ENTRIES

Each entry must include a contest log, a contest summary, and multiplier checklist. We recommend that contestants send for a copy of the contest forms. Send an SASE to the contest address listed below.

#### CONTEST DEADLINE:

Each entry must be postmarked no later than February 12, 1983.

#### DISQUALIFICATIONS:

Omission of any required entry form, operating in excess of legal power, manipulating of contest scores or times to achieve a score advantage, or fallure to omit duplicate contacts which would reduce the overall score more than 2% are all grounds for Immediate disgual/fication.

#### AWARDS:

Contest awards will be issued in each operator class in each of the continental 48 US states, Canadian provinces and territories, and each DX country represented. A minimum of 5 hours and 50 QSOs must be worked to be eligible for contest awards.

#### CONTEST ADDRESS:

To obtain entry forms or to submit an entry, forward an SASE to: 40-Meter Contest, BIIIy E. Maddox, 468 Century Vista Drive, Arnold MD 21012.

#### 2ND ANNUAL 80-METER WORLD SSB CHAMPIONSHIP Starts: 0000Z January 9 Ends: 2400Z January 9

#### SPONSOR

73, Peterborough. New Hampshire 03458.

#### MISCELLANEOUS RULES:

Work as many stations as possible on 80-meter phone during the specified times of allowable operation. The same station may be worked once. Crossmode contacts will not count. Single-operator stations may operate a total of 16 hours. All the multi-operator stations may operate the entire 24hour period. Off periods must be noted in your log(s) and on your summary sheet. Off periods are no less than 30 minutes each.

#### OPERATOR CLASSES:

(A) Single operator, single transmitter, phone only. (B) Multi-operator, single transmitter, phone only.

#### EXCHANGE:

Stations within the continental 48 US states and Canada transmit an RS report and state, province, or territory. All other stations, including Alaska and Hawaii, transmit RS report and DX country.

#### POINTS:

1 QSO point is earned for each station worked in the continental 48 US states and Canada or within your own country. All other contacts are two points each. List points for each contact on your logsheet.

#### MULTIPLIERS:

1 multiplier point is earned for each US state (48 maximum), each Canadlan province or territory (13 maximum), or DX country worked.

#### FINAL SCORE:

Total QSO points times total multiplier points equals clalmed score.

#### CONTEST ENTRIES:

Each entry must include a contest log, a contest summary, and multiplier checklist. We recommend that contestants send for a copy of the contest forms. Send an SASE to the contest address listed below.

#### CONTEST DEADLINE:

Each entry must be postmarked no later than February 12, 1983.

#### DISQUALIFICATIONS:

Omission of any required entry form, operating in excess of legal power, manipulating of contest scores or times to achieve a score advantage, or failure to omit duplicate contacts which would reduce the overall score more than 2% are all grounds for immediate disqualification.

#### AWARDS:

Contest awards will be issued in each operator class in each of the continental 48 US states, Canadian provinces and territories, and each DX country represented. A minimum of 5 hours and 50 QSOs must be worked to be eligible for contest awards.

#### CONTEST ADDRESS:

To obtain entry forms or to submit an entry, forward an SASE to: 80-Meter Contest, Billy E. Maddox, 468 Century Vista Drive, Arnold MD 21012.

#### 2ND ANNUAL 160-METER WORLD SSB CHAMPIONSHIP

#### Starts: 0000Z January 15 Ends: 2400Z January 16

SPONSOR:

73, Peterborough, New Hampshire 03458.

#### OBJECT:

To work as many stations as possible on 160-meter phone in a maximum of 30 hours allowable contest time. Multi-operator stations may work the entire 48-hour contest period. Stations may be worked only once.

#### ENTRY CATEGORIES:

(1) Single operator, single transmitter, phone only. (2) Multi-operator, single transmitter, phone only.

#### EXCHANGE:

Stations within the continental US and Canada transmit an RS report and state, province, or territory. All other stations, transmit RS report and DX country.

#### POINTS.

All valid two-way contacts score five (5) QSO points each.

#### MULTIPLIERS.

1 multiplier point is earned for each US state (48 maximum), each Canadian province or territory (13 maximum), and DX country outside the continental 48 US states and Canada.

#### FINAL SCORE:

Total QSO points times total multiplier points equals claimed score.

#### CONTEST ENTRIES:

Each entry must include logsheets, dupesheet for 100 or more contacts, a contest summary sheet, and a multiplier checksheet.

#### ENTRY DEADLINE:

Each entry must be postmarked no later than February 19, 1983.

#### DX WINDOW

Stations are expected to observe the DX window from 1.825-1.830 MHz as mutually agreed by top band operators. Stations in the US and Canada are asked not to transmit in this 5-kHz segment of the band. During the contest all stations are requested to utilize those frequencies from 1.808-1.825 and 1.830-1.900 MHz.

#### DISQUALIFICATIONS

Operator omits a required entry form, operates in excess of legal power authorized for his/her given area, manipulates operating times to achieve a score advantage. or fails to omit duplicate contacts which reduce the overall score more than 2%.

#### AWARDS

Contest awards will be issued in each en try category in each of the continental US states, each Canadian province and territory, and each DX country represented. A minimum of 5 hours and 50 QSOs must be worked to qualify.

#### CONTEST ADDRESS

To obtain entry forms or to submit a contest entry, forward an SASE to : 160-Meter Contest, Billy E. Maddox, 468 Century Vista Drive, Arnold MD 21012.



#### Starts: 0000Z February 26 Ends: 2400Z February 26

#### SPONSORS

73 and The RTTY Journal.

MISCELLANEOUS RULES:

The same station may be worked once on each band. Crossmode contacts do not count. Single-operator stations may work 18 hours maximum, while the multi-operator stations may operate the entire 24-hour period. Off periods are no less than 30 minutes each and must be noted in your log(s).

#### OPERATOR CLASSES:

(A) Single operator, single transmitter, phone only. (B) Multi-operator, single transmitter, phone only

#### ENTRY CATEGORIES:

(A) Single band, (B) Allband, 10-80 meters,

#### EXCHANGE

Stations within the continental 48 US states and Canada must transmit an RST report and state, province, or territory, All other stations, including Alaska and Hawall, transmit RST report and consecutive contact number.

#### OSO POINTS

1 QSO point is earned for each valid contact.

#### MULTIPLIER POINTS:

1 multiplier point is awarded for each of the 48 continental US states, Canadian provinces or territories, and DX countries worked on each band.

#### FINAL SCORE

Total QSO points times total multiplier points equals claimed score.

#### CONTEST ENTRIES:

Entries must include a separate log for each band, a dupesheet, a summary sheet. a multiplier checklist, and a list of equipment used. Contestants are asked to send an SASE to the contest address for official forms

#### ENTRY DEADLINE:

All entries must be postmarked no later than March 26, 1983.

#### DISQUALIFICATIONS

Omission of any required entry form, operating in excess of legal power, manipulating of contest scores or times to achieve a score advantage, or failure to omit duplicate contacts which would reduce the overall score more than 2% are all grounds for immediate disgualification.

#### AWARDS

Contest awards will be issued in each entry category and operator class in each of the US call districts and Canadian provinces and territories, as well as in each DX country represented. Other awards may be issued at the discretion of the awards committee. A minimum of 5 hours and 25 QSOs must be worked to be eligible for awards.

#### CONTEST ADDRESS

Send an SASE to RTTY World Championship Contest, c/o The RTTY Journal, PO Box RY, Cardiff CA 92007.

#### WORLD COMMUNICATION YEAR

Next month's World Communication Year amateur radio activity will be using the 75 ITU zones for scoring multipliers. Be sure you use the correct ITU zones and not the ARRL zones for this contest. Copies of a world map and prefix list showing the ITU zones can be obtained from the contest sponsors, the Potomac Valley Radio Club, by sending an SASE or an IRC to: PVRC, PO Box 337, Cromsville MD 21032. Complete rules will appear here in my January column

.



### Introducing the POWER PACKET from VoCom

An innovative new product that you can combine with your VoCom Power Amplifier to obtain the functions of the famous VoCom Power Pocket" using any handheld radio

AF POWER - 2 to 3 watts of road-noiseovercoming audio to your vehicle speaker or to external Packet Speaker\*\* (optional). EASY HOOK-UP - Packet Bracket!" at bottom of Power Packet, provides place to clip almost any make or model handheld. Connects to handheld through pin jacks. Hooded light on Power Packet illuminates portable's front panel.

CHARGE POWER - 35 mA charge on receive, 400 mA when mic is keyed. Unless your handheld draws more than 400 mA.

you can talk as long as you wish and the batteries will be at least as charged as when you started.

MIC PREAMP - adjustable; tie in your handheld directly without changing its mic input. Also makes Power Packet compatible with most standard mobile mics. Optional Packet Mic" available.

Suggested retail \$84.95. See your favorite amateur radio dealer



-90

cket Bracket, Packet Mic, Packet Speaker and VoCom are trademarks of VoCom Products Corp

**MICROWAVE AND SATELLITE TELEVISION** 

The standard RP downconverter package shown below gives you a proven 2150 Mhz downconverter mounted in a weathertight antenna that features low wind loading and easy installation.

All downconverters use microstrip construction for long and reliable operation. A low noise microwave preamplifier is used for pulling in weak signals. The downconverters also include a broad-band output amplifier matched to 75 ohms. The RP model is recommended for up to 15 miles. Over the range of 15 to 25 miles the RP + which has a lower noise and higher gain RF amplifier stage, provides better television reception. For installations over 25 miles, an RPC unit which uses a separate antenna is available. All models are transient voltage protected by surge protection on both the power supply and the converter inputs. All models are warranted for one year.

The DCI 466 is a completely self-contained IMAGE REJEC-TION DOWN CONVERTER that is used for TVRO downconversion at the Satellite antenna where optimum signal to noise ratio can be obtained. The DCI 466 converts the TVRO band to 70 Mhz. The unit's DC power and a 17 to 25 volt local oscillator tuning voltage are superimposed on a single RG 59 line for easy installation. The unit has an on board IF amplifier matched to 75 ohms that gives plenty of drive for long cable runs. The overall conversion gain is 25db. Image rejection is a minimum of 14db. \$300 in singles.

Write for details on our low priced model VCO 40 voltage controlled oscillators in the four pin TO-8 package that cover the TVRO band. Also check our 120 degree low noise amplifier for low cost satellite ground stations.

165

INTEGRATED ELECTRONICS **PO BOX 204** CARLISLE MA 01741 617-369-0536




\$<del>\$\$\$\$}\$\$\$}}</del>

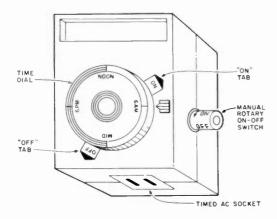
## CIRCUITS

Do you have a technique, modification, or easy-to-duplicate circuit that your fellow readers might be interested in? If so, send us a concise description of it (under two pages, double-spaced) and include a clear diagram or schematic if needed.


In exchange for these technical gems, 73 offers you the choice of a book from the Radio Bookshop, to be sent upon publication. Submit your idea (and book choice) to: Circuits, Editorial Offices, 73 Magazine, Peterborough NH 03458. Submissions not selected for publication will be returned if an SASE is enclosed.




**OVERTIME PROTECTION FOR NICADS: Nicad batteries are prone** to damage if the batteries are charged for more than 12 to 16 hours. Unfortunately, most timers don't have a timer. To protect your batteries from possible overcharge and venting, you can add an outboard timer and thus protect your batteries. 24-hour appliance timers are available for less than \$10. The timers have sliding "on" and "off" tabs which trip a switch when the dial rotates. There is also a rotary-type override switch on the back or side of the unit. To use this timer for your nicad charger, first disassemble the timer. Remove the tab from the "on" switch. To use the modified timer, set the dial to noon and set the "off" switch to a time 16 hours later. This would be 4:00 am. Plug in the charger to the timer, and turn the timer on with the manual override switch. If you have to interrupt the charging cycle and move the unit into another location, your unit will have a "memory" and the charging cycle will resume at the same time when you reconnect the unit.-John F. Sehring WB2EQG, Oradell NJ.

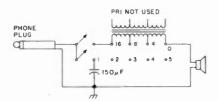


SIMPLE FILTER SPEAKER: There is nothing magical about this circuit. It consists of a universal output transformer which is secondary-tapped at 4, 8, and 16 Ohms, a 150-uF paper capacitor, and a two-deck five-position rotary switch to select combinations as shown. The clockwise position goes straight through to the speaker and each step to the left cuts more high frequencies in the manner of a typical tone control on a broadcast receiver. There is some attenuation of the overall signal (chiefly above the male voice range), so you can reduce the heterodynes from Radio Moscow and the adjacent channel sideband QRM to a tolerable level. You could use a transformer with more taps or more than one capacitor if that is what your junk box offers.—W. B. Cameron WA4UZM, Tampa FL.

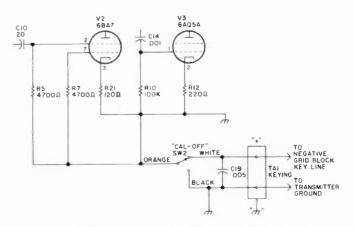

HALLICRAFTERS HA-5 GRID-BLOCK KEYING CONVERSION: The Hallicrafters HA-5 vfo is cathode-keyed. This conversion will enable the rig to be grid-block-keyed with a minimum of surgery to the unit. Begin by disconnecting cathode resistors R12 and R21 from the orange lead of the "Cal-Off" switch, grounding them to chassis. Open R22 at the TA1 keying terminal strip. Disconnect R5, R7, and R10 from chassis, and connect their junction to the orange lead of the "Cal-Off" switch. To reconvert to cathode keying, disconnect the ungrounded ends of R5, R7, R10, and R22, leaving them bent out, while installing new R5, R7, and R10 resistors whose long leads will more readily reach to the orange "Cal-Off" switch lead. The gridblock transmitter lead (negative) then connects to the terminal marked "+", and the transmitter ground connects to the terminal marked "ground" on the vfo keying terminal strip.—Tuckerman S. Jalet AA1C, Stamford CT.

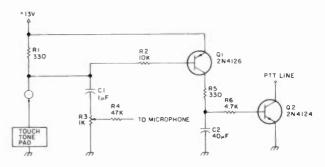

TOUCHTONE<sup>™</sup> TECHNIQUES: This circuit allows for one-hand operation of any surplus-type touchtone pad. Q1 and Q2 form a highlow switching circuit controlled by R1. When any key is depressed, Q1 will conduct, applying 12 volts to the pad. Then Q2 conducts, keying the transmitter. After you have completed dialing, the keying circuit returns to the "rest" mode and the transmitter must be keyed by the PTT. Delay time is controlled through selection of C2 and R6. Component values are not critical.—Joseph A. Taylor W9JO, Green Bay WI and Hugh Kelley WB9NON, Rhinelander WI.

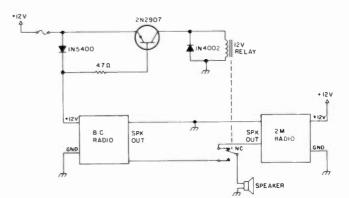

SUPER AUTOMATIC SPEAKER SWITCH: This circuit will switch a speaker between your broadcast radio and your two-meter rig, depending on which radio is turned on at the time.—Haim Sandel KB2IV, Flanders NJ.



\$37 50 \$37 50 \$34.50

\$41.00

\$100.00 \$146.00

0 7

\$ 1.50

\$ 2.50

\$ 1.00

-143

MH<sub>2</sub> \$17.00

### $\geq$ BIT "O" BYTE $\ll$

All Prices Include Shipping and Tax in the U.S.A. ALL DISK are WARRANTED against material de fects for 90 days from date of purchase.

 5 1/4 inch Diskettes (soft sectored), Center Rein forcing Ring, Jacket and plastic box-stand. = \$27 for box of 10 to 20. 20 to 100 is \$25 per box.
 SYMTEC HIGH RES LIGHT PEN—With soft

- ware = \$185.00 • 16K RAM CARD for the APPLE II or II +
- BARE BOARD = 30.00
- PADDLE-ADAPPLE only = \$27.50
- MAGIC KEYBOARD only = \$86.00
   MICROBUFFER II For most printers 32K = \$250.00

Epson Parallel 16K = \$135.00 Epson Serial 8K = \$135.00

- ECHO II Speech Synthesizer with Software on 3.3 disk and Speaker = \$170.00
- THUNDERCLOCK PLUS with software = \$125.00 BSR X-10 INTERFACE OPTION = \$45.00 DOS-DATER DISK = \$20.00
- PASCAL SOFTWARE DISK = \$20.00 • RAMDISK-320 = \$1225.00

Advertised in SoftTalk. • I will carry other items in the future. If you don't see what you need let me know. Coming soon VISA charging and computer ordering.

Most products carry a 90 day warranty The prices may change without notice. Please send ORDERS with payment and inquiries to:

BIT "O" BYTE
 P.O. Box 60972
 Sunnyvale, CA 94088

### SATELLITE TV KIT



Featured in a Radio Electronics magazine cover story (May 82), the reliable R2B Sat-tec TV receiver is now operating in thousands of locations. The R2B is easy to build; pre-etched, plated boards with screened component layout assures accurate component placement and the critical IF section and local oscillator are preassembled and aligned! All parts are included for the R2B; attractive case, power supply, descriptive operating manual as well as complete assembly instructions. Features of the receiver include; dual conversion design for best image rejection, fully tunable audio to recover 'hidden' subcarriers, divide by two PLL demodulator for excellent threshold performance, tight tracking AFC to assure drift free reception, and of course, full 24 channel tunable coverage.

Build your satellite TV system around the R2B, close to ten thousand others already have and now it's available in kit form at a new low price. Order yours today.

A complete Satellite TV System re a dish antenna, LNA (low noise fier), Receiver and Modulator. R2B Receiver Kit R2B Receiver, Wired and Tested 120° K Avantek LNA RM3 RF Modulator Prices include domestic UPS st and insurance.	ampli- \$359.00 \$595.00 \$495.00 \$49.95
RAMSEY ELECTRONICS INC. 2575 BAIRD RD. 2575 BAIRD RD. PENFIELD, NY 14526 ORDER TO 716-586-3950 - 185 1-800-824	

#### — NICAD MEMORY ERASE – WHAT??

- Complete automatic operation
- Erases + Charges + Checks
- Rapid charges in 35 min. (typically)
- Automatically repairs shorted cells
- No dangerous heat build up
  Front panel selects up to 3 different
- Pront panel selects up to 3 unre packs
- Unlimited battery combinations with program modules (user programable)
- LED status indicators
- Supplied with universal EZ hook wire leads

Specify Voltage of Battery Pack(s) with order.

\$79.95 plus \$3.00 Shipping (PA Residents add 6% sales tax)

**Coming Soon** – Multiple pack memory erase charger for municiple commercial applications write for information or send requirements.



The GMS 401 is a complete automatic NICAD conditioner and rapid charger. Never before has this been offered anywhere at any price and it's so good it's being patented. NICAD memory characteristics must be dealt with otherwise your battery pack is not delivering all it could. The GMS 401 will automatically erase and rapid charge any type NICAD pack from 1 to 10 cells automatically.

CONTROL PRODUCTS UNLIMITED, INC. P.O. Box 10, Downingtown, PA 19335 215-383-6395



Yes, now you can take it with you! The new HAL CWR-6850 Telereader is the smallest RTTY and CW terminal available, complete with CRT display screen. Stay active with your RTTY and CW friends even while traveling. Some of the outstanding features of the CWR-6850 are:

- Send and receive ASCII, Baudot, and Morse code
- RTTY and Morse demodulators are built-in
- RTTY speeds of 45, 50, 57, 74, 110, and 300 bau -
- High or Low RTTY tones
- Send and receive CW at 3 to 40 wpm
- Built-in 5 inch green CRT display
- Four page video screen display
- Six programmable HERE IS messages
- Pretype up to 15 lines of text
- External keyboard included
- Runs on +12 VDC @ 1.7 Amperes
- Small size (12.75" × 5" × 11.5")

Write or call for more details. See the CWR-6850 at your favorite HAL dealer.

HAL COMMUNICATIONS CORP. BOX 365

URBANA, ILLINOIS 61801

217-367-7373

## **1982 INDEX**

#### AMPLIFIERS

AMPLIFIERS				
Egad! A 9-Tube Linear The Fun-Amp Taming the 2-M Linear	Amplifier Design 20-Watt CW Construction	W7CSD WAØRBR VE3LMP	Jan 12 May 32 Dec 28	
ANTENNAS				
The Great Compromiser Those Amazing Bobtails Top-Notch for Top Band The CCD Ant. Revisited Americanizing the	Wideband Doublet Why They Work Antennas for 160 CCD Design for 40-M	W5JJ W1XU N3BEK W4ANL	Jan 104 Feb 30 May 26 May 40	
German Quad 2epp and Sons The Vertical Deuce The J-Pole Love Affair Pleasures and Perils	Horizontal Quad End-Fed 40 and 75 Meters 2-Meters and Mobile		May 76 May 96 Sep 80 Sep 84	
of Crankup Towers The Incredible Antenna	Tower Tips	K4TWJ	Oct 40	
Mark 2 The Multiband Vertical The Campbell J The Coax Matcher A Tuner for Antenna	Space-Saving 20, 15, 10 Meters 2M Soup Can Tuner	KL7ISA W1GV W4YVY W9PFJ	Oct 44 Oct 54 Oct 60 Oct 84	
Fanatics The Hangman's 2-Meter	Save Your Finals	Staff	Nov 42	
Collinear Build Yourself A	6-Element Array	W1GV	Dec 10	
Paralyzed Beam	2M Array	WB2WIK	Dec 24	
ATV AND SSTV				
ATV's Stripper	ATV Converter	VE3CYC	Mar 20	
CB CONVERSIONS				
Peaking and Tweaking Surplus CB Boards CB to CW?	Hy-Gain Boards Hy-Gain Boards	WBØNPN W1BG	Mar 38 Jul 18	
Maximum Modulation for CB Conversions	Audio Preamp	AJØP	Dec 122	
CONSTRUCTION				
Building for Beginners Coping With PC Boards	Soldering, Etc. Make Your Own	N1II KC7M	Jun 42 Jun 48	
CORRECTIONS				
"Lab QualitySupply" "New Freqs. for IC-2" "ATV's Stripper" AFA Code Reader Review "TVRO Signal Source" "ATV's Stripper" "The Hesitator" "The Masher" "VHF Converter" CHF Gonverter" "VHF Converter" "Coherent CW for VHF" "Coherent CW for VHF" "TheBest CW Filter" "Counter Evolutionary." Double Trouble" "Dissertation OnPig" "The Vertical Deuce"	Mar-Apr '80 Oct '81 Mar '82 Jan '82 Jan '82 Jan '82 Jan '82 Apr '82 Apr '82 Apr '82 Apr '82 Apr '82 Jul '82 Jul '82 Jul '82 Oct '82 Oct '82 Sep '82		Jan 146 Jan 146 Mar 104 Mar 104 Apr 145 Apr 145 Jun 64 Jul 121 Jul 121 Jul 121 Jul 121 Sep 141 Sep 141 Oct 142 Oct 142 Dec 144 Dec 144	
CW				
Hands Across the Water A Three-Piece CPO Coherent CW for VHF The Very, Very Best	CW on Cape Cod Quick and Simple Matched Filtering	KA1D WB5WAF W3QVC	Jul 38 Jul 46 Jul 48	
CW Filter The True-Blue Keyer Touch-Type CW CW-The Air Force Way CW and the Apple II Keyer on a Shoestring	Low-Cost Filter Keyer With Display TRS-80 Program How They Teach It Morse Program Cheap	WB4TYL W3BYM K8TT Metzler N5MR WB5PPV	Jul 56 Jul 60 Jul 64 Jul 72 Nov 84 Nov 104	
EQUIPMENT MODIFICATIONS				
Police Freqs for the				
TR-2400 CQ Mars de IC-2A Polishing Kenwood's	HT Modification Mars/CAP Capability	N9AK WD8JLW	Feb 26 Feb 46	
R-1000 Scanning With the	Several Easy Mods	K9EUI	Mar 34	
IC-280 A Split Personality for	Drill No Holes	N7 AAD	Apr 36	
the KDK FM2015R Fl for the HW-101 Fine-Tune Your IC-280 A Gem of an RIT	Split Frequency True FSK 5 kHz-Step Tuning For the SB-104	KØBV KØJH K4SB KK5R	Jun 40 Sep 20 Oct 68 Oct 70	

156 73 Magazine • December, 1982

N2GW HB9BLU WB6IQN 14 70 76 TS-180 Modification MARS Capability Tempo MARSer Speed Demon Nov WPM for H-1418 Nov 102 K4ZHM GADGETS The Simplex Autopatch Repeaterless Patch WA7VZR 26 Jan The Cheapskate The Hesitator: A Diode Checker K9QLL Jan 30 Wiper Control Touch-Tune Wit Thumbwheels Rainy Day Project N4UH Jan 40 With Feel the Frequency ZL4LM Jan 110 The Masher Line Voltage at a Speech Processor W5VSR Mar 76 Glance Voltage Monitor Overmod Warning W4RNL The Splattometer Aug Oct 84 10 W1BG Dissertation Upon Roast Pig Automatic Beam Aimer Surplus Transformers Set and Forget N6 TO 28 Oct K9AZG Nov 22 Dial-A-Frequency Red-Hot and Ready To Go Remote Control KIWGN Dec 44 Cordless Solder Gun W7XRV Dec 101 HISTORY Messages from Station Charlie The Father of FM Spy Communications E.H. Armstrong Tibet, 1936-1937 Ham Builds Spy Rig Phenix 88 Jan Hammond Feb 50 The AC4YN Story GSYN Aug 32 56 The Bunesti Caper W9PJF Dec 1/0 Micro-Programmed Controllers CW Interface Control Concepts K2OAW Jan 68 Feb 104 Construction W9JD Compugrams Are Here Got an Apple? Want RTTY? Message Handling WAGZZL Apr 76 Apple Interface PET BASIC Program Contest PET Program WB6FBN Oct 34 Amazing Beam Header Award-Winning Program The Program That Knows Oct Nov 46 94 WA4NAG WB2GFE It All Berserk Direction Finding BASIC for TRS-80 W8XW Dec 72 TRS-80 BASIC WD8CBE Dec 76 MISCELLANEOUS Drama on Mt. McKinley Indian Hams Rejoice Licensing for Americans High Altitude Hams W7KUF Jan 18 Restrictions Lifted Rama Mar 64 Overseas DX Licensing KA3B Mar 68 Innovation or Consternation Let's Go Shopping The Sinkhole That Ate Winter Park Detect Killer Tornadoes Radio Patents Used Gear AKØO 78 88 Mar WD4SKH Mar Hams vs. Hole Use a TV KA4RUL Apr Apr 18 50 K2VJ Flash and Crash 101 Weather the Storm DXpedition KINYK 94 Apr Pacific Odyssey Antenna Raising: the KB7NW May 12 Good Neighbor Policy Surviving the Unthinkable Ham PR AK50 May 42 After the Bomb-Pt. I AKØQ May 110 Surviving the Unthinkable Part II AKØO Jun 30 84 Crime-Stopper's Text Electric Health Rules of Thumb Diefenbach Jun Via Negative Ions All Tied Up in Knots? Shack from Scratch Ion Generation Knot-Tying Planning Ahead WØOGX KC7M 52 78 Jul Oct W2XO Dec 84 MOBILE AND PORTABLE Life-Support System for HTs Charger and Box WB6BHI 26 32 Nov Frugal Floppy Bazooka HT Antenna N7BGZ Dec NEVER SAY DIE Power Struggle ARRL Board War ARRL Politics Ham Clubs Personal History Power Strüggle Dannals New Manager Club 'Em Greedy Green? Fruit Basket Leaks Bunk in 73 Jan 6 Jan 6 Jan Jan 148 Hussein in L.A. CW vs. Phone Computers Call for Articles Jan 148 Jan 148 148 Synergism Articles Needed More Detectors Jan Jan Jan 150 Radar Detectors New Legislation 150 Now, The Good News Friendly Clubs Deregulation Feb 6 Advice for Clubs Feb Feb 131 131 FCC Paper Replacing Batteries Ham Watch Repair Getting Rich Morse and the Demised Feb 133 Work and Money Feb 133 Morse and the Demised Plain Language Rules Code Courses the Pits It's Up To Us! We've Been Bashed The CD Debacle Emergency Operation Mar 6 Modern Methods Alien Radio Messages Mar 118 Mar 120

Critique

Killing the Woodpecker ARRL Attacked Building

The Dannals Deal

Good ARRL News Reader Responses

Favors Smith Charts

Civil Defense Self-Defense

Ham Radio Magazine Call for Articles ARRL Director

FCC Shenanigans World Tour Contest Rules Change

Survey Results

Apr 6

Apr 6

Apr Apr Apr 8

Apr Apr Apr 44 45 45

Apr Apr 45 46

44

Several Functions

Nov

1

Remote-Control Your

The Sound of Silence

IC-701



RANGERI

7dB GAIN HIGHEST GAIN 2 METER OMNI

OUTPERFORMS CONE AND DOUBLE ZEPP WORK MORE STATIONS

ELIMINATE NOISE LIGHTNING PROTECTED

INSTALL QUICKLY

A COMPLETE ANTENNA

ALL PARTS INCLUDED 600,000 HAPPY USERS

BECOME ONE TODAY

ARX-2B 134-164MHz

ARX-220B 220-225MHz

ARX-450B 435-450MHz

MOBILE

5/8 ASTAINLESS WHIP

CHROME PLATED BASE

THUMB LOCK ADJUSTMENT

AMS-220 220-225 MHz TRUNK LIP MOUNTS

ATS-147 146-148 MHz

OBPOBATION

-106

NEAT APPEARANCE

NO WHIP CUTTING

LOW PRICE MAGNETIC MOUNTS AMS-147 146-148 MHz

**GRIP TIGHT 90LB** 

MORE RANGE

3 dB GAIN

MAGNET

RANGERS

ACCESS MORE REPEATERS ASSEMBLE EASILY


Walkman Talkman Energizer...or Nicad? A Word for DX Ops Blitz Code Learning Foreign Aid Fighting Back Hooked Coping With Emergencies The Next Step Harry Thrown Out! National Policy What's That Cloud? No News vs. Good News Harry, Where Are You? Instant Licenses Dayton '82 We Need Kids Navassa Time Chinal An ARRL Responsibility General Notes Articles The Phone The World's Fair--Knoxville Saddle Stitching A New Cover...Again? Rochester Travel Radioaficionados Success Ionized Emergencies Ham Publications The Old Man The Non-DXpedition Someone Needs Help! Untold Wealth S-9 Gone, Too Circuits, Circuits Where's the Solder? CQ Fails Code Test No Second Languages Bunch Gets Bashed Should DXCC Be Prohibited? Hamfest Catastrophe The Great American Ham Club...Disaster NEW PRODUCTS Advanced Analog Systems Advanced Computer Cont. Advanced Electronic Advanced Electronic Alpha Delta Alpha Delta Aluma Tower Applied Invention Arco Solar Arunta Engineering AutoConnect Benjamin Michael Bilal Co. Blacksburg Group Centurion International CES CES Channel Master Channel Master Com-Rad Industries Com-Rad Industries Commsoft Inc. Contest Software CO Products Current Development Cushcraft Cushcraft Daiwa Daiwa DenTron DenTron DenTron Desco Industries Electronic Specialists Electronic Specialists Electronic Specialists Encomm Inc. Encon Corp. Fox Tango Corp. Frontier Enterprises G&T Service Co **Ghost Fighters** Gillaspie and Assoc. Global Specialties Global Specialties Global Specialties Gould Inc. Grove Enterprises Grove Enterprises Grove Enterprises Guild Radio Rack HAL Communications HAL Communications Hamtronics Hamtronics Heath Heil, Ltd. Henry Radio Hustler Hustler Hy-Gain Icom

New Product Battery Costs Education New Approach DX Ragchewing Non-Smoker's Rights Becoming a Ham Organization Plans Future Strategies ARRL Politics Hams and CD Cigarette Sales Cigarette Sales Daily News Days ARRL History FCC Test Sales Hamvention Success Mercenary Teaching DXpedition Travel Fighting Back Magazine Policy Call for Articles Getting Through Fair Station 73 Changes 73 Changes Hamfest Review Home and Abroad Finding Foreign Hams Teaching Values Ion Generators Communications Magazines Decline Reminiscences CEØX Story Repeater Alarms Entrepreneurship Publishing Business Call for Circuits Construction Misspelled Ad Immigrants FCC Exam Changed PY0SB Dxpedition Mail-Order Lotteries Making Clubs Succeed Compandor Kit Repeater Controller Keyer Update Reader/Converter Control Console Surge Protectors Tower Trailer Active Filter Solar Module TVRO Receiver TVRO Receiver Autopatch 24-Hour Wall Clock Compact Antenna Straight-Key Keyer Flexible UHF Antenna Phone Interconnect Microdialer Earth Stations Earth Stations Earth Station Rovr 2M DDRR Antenna Antennas Apple SSTV Logging Program Operator's Desk Mobile Connection No-Radial Vertical Base Station Antenna Speech Processor Speech Processor Electronic Keyer Linear Amplifier 5-Band Transceiver Monoband Transceiver Flashlight/mirror Power Line Phone Interconnect Microdialer Transceiver Photovoltaic Catalog TS-830 Filter Kit CW Instruction Pgm. Callsign Display Satellite TV Ant. Portable Earth Stn. Breadboard 'Scope Multiplexer Digital Pulser Kit Standby Power System Antenna Tuner Wideband Antenna Scanner Converter Shack Furniture RTTY/CW Terminal Telereader Terminal VHF Kits FM Repeater Oscilloscope Mike Equalizer Marine Portable 1:1 Balun 6-Meter Antenna 7-Element Tribander 6-Meter Multimode

Apr	46	Icom
May	6	Icom
May May	6 117	IIX Equip Imac Prod
May	117 118	Internati Internati
May Jun	6	JL Indust Jon Presl
Jun Jun Jun	121	Jon Presl Kalglo El
	123	Kantronic
Jun	123 123 124 124	Kenwood Kenwood
Jun Jun	124	Kenwood
Jul Jul	6 6	Kenwood Kettlewel
Jul	6	Lance Joh
Jul Jul	8	Larsen An Larsen An Leader In
Jul	8 118 120	Leader In
Jul	120	LNR Commu Lunar Ele
Jul Jul	121 121	
Jul	121	Macrotror Martin Er MFJ Enter MFJ Enter MFJ Enter MFJ Enter MFJ Enter
Aug	6	MFJ Enter
Aug	139 139 139	MFJ Enter
Aug	139	MFJ Enter MFJ Enter
Sep Sep	6 128	Micro-Cor
Sep Sep Sep Sep	130	Microcraf
Sep	130	Microwave Mirage Co
Sep	132	MLM Assoc
Oct Oct	6	MORTTY Non-Linea
Oct	100	Palomar E Palomar E Palomar E Palomar E Palomar E Palomar E Pegasus E Pogasus E
Oct Oct	100 101	Palomar E
Nov	6	Palomar B
Nov Nov	6 8	Palomar E
Nov Nov	140 140	Pegasus E
	140	Proham El
Dec Dec	6 172	R.L. Drak R.L. Drak Ridge Sys Richl Tim
		Ridge Sys
Dec	174	Riehl Tim Rivendell
		Snyder Ar
		Stellmake Telecom I Telecom I
May	124 123 124 107 136	Telecom I Ten-Tec
May	123	Ten-Tec TET Anten
May Jul	107	TET Anten Thermax
Nov	136	Tuned Ant
Nov Apr Feb Dec	124 107 136 133 136 143 127 125 118 119	Twin Oaks
Dec	143	Valor Ent Valor Ent Valor Ent Valor Ent VHF Commu
May	125	Valor Ent
Sep	118	Valor Ent
Jun	119	VHF Commu VoCom Pro
Jul Mav	104	W-S Engin W-S Engin
FeD Dec Aug May Sep Jun Jun Jun Jul May Jul	104	W-S Engir W.H. Nail
Oct Oct	118	W.H. Nail Wahl Clip
Nov	138	Wayne Res Yaesu
Oct	124	Yaesu
Aug	127	Yaesu
Jul	104	
Oct	118	OPERATING
Sep	118	OPERATING
Jan Jun	153	The Art o Operation
Aug	126	Tune In t
Dec	142	Tinderbox The Color
Jan	154	I Got My Now What?
Jul	104	Now What?
Oct	118	
Nov	136	POWER SUP
Nov	138	
Sep	118	Constant A Voltage
Dec	141	A Voltage The Ultim
Sep	119	Avoid an Nightmare
Oct	116	Protect Y
May	123	Transisto The Money
Mar	125	Supply Build the
Oct	120	Build the No Smokir
Dec Feb	141	Ham Shack
May	123	
Dec	141	
May	125	RECEIVING
May	123	Stormy We
Aug Oct	127	"Smart" S Another A
Apr	118 116 138 124 127 127 104 112 120 104 112 120 126 126 126 126 127 128 128 129 126 123 104 142 118 138 138 138 138 138 141 142 123 120 141 123 126 123 126 123 126 123 127 121 123 127 121 123 126 123 126 123 126 123 126 126 127 127 128 128 128 128 128 128 128 128 128 128	Stormy we "Smart" S Another A Project The Tube
Aug	126	The Tube

	IC-740 Transceiver		Sep 118
pment	IC-45A UHF Mobile Ginpole		Dec 142 Jun 119
ducts	Weather Station		Jul 106 Aug 127
ional Crystal ional Satellite	Satellite Receiver 3.3 Meter Dish		Mar 110
tries ley	Antenna Converter DX Prefix List		Dec 143 Mar 110
lectronics	Surge Suppressors		Oct 118
cs	CW to RTTY Converter R-600 Receiver		Apr 133 Jan 152
	TR-2500		Jan 152 Mar 110
	4-Band Transceiver TS-930S Transceiver		Mar 110 May 122
11 Eye Research	Aids for Blind Hams		May 122 Dec 142
hnson Eng. ntennas	Ground Plane Buss Mobile Radio Mount		Jun 119 Jun 120
ntennas nstruments	Quarter-Wave Ant.		Oct 120 Jan 152
unications	Quarter-Wave Ant. Digital Multimeter TVRO Downconverter VHF/UHF Amplifiers		Feb 135
ectronics nics	VHF/UHF Amplifiers Comm. Terminal		Nov 134 Aug 126
ngineering	Tower Aid		Jun 120
rprises rprises	Antenna Tuner Keyers SWR/Wattmeter Inductive Modem Active Antenna Police Converter Repeater Power Amp CW Beader		Jan 153 Peb 135
rprises rprises	SWR/Wattmeter		Mar 111
rprises	Active Antenna		Apr 132 Sep 119
rprises ntrol	Police Converter		Nov 138
ft	CW Reader		Jun 120 Jan 153
e Filter Co. ommunications	CW Reader Interference Trap 220 MHz Amplifier Heath Programs		Aug 127 May 122
ciates	Heath Programs		Apr 132
ar Systems	Comm. Software Circuit Analyzer		Nov 136 Sep 119
Engineers	Antenna Baluns		Apr 133 Apr 134 Jun 119 Jul 106
Engineers	Auto SWR Meter		Apr 134 Jun 119
Engineers	Antenna Tuner		Jul 106
Engineers	DTMF Decoder		Sep 118 Dec 140
Electronics	Comm. Software Circuit Analyzer Antenna Baluns VLF Converters Auto SWR Meter Antenna Tuner Electronic Keyer DTMF Decoder Diversity Reception Coax Antenna Modular Kits Surge Shunt		Nov 136
lectronics	Modular Kits		Mar 110 Dec 142
ke ke	Surge Shunt Transceiver and Rcvr		Jan 153
stems	RTTY Interface		Apr 132 Oct 118 Dec 141 Jun 120
me 1 Associates	Solar Watch 20 MHz Scope		Dec 141 Jun 120
ntenna Corp.	20 MHz Scope Compensating Dipole Etching system TVRO Receiver Earth Station		Aug 120
Industries	TVRO Receiver		Jan 152 Mar 111
Industries	Earth Station		Oct 118
	Antenna Tuner Satellite Station		Feb 135 Jul 106
nna Systems	Triband Beam Low-Cost Wind Power		Dec 141 Dec 140
tenna Co.	Low-Cost Wind Power HT Antenna CW Teaching Systems CW and RTTY Program Mobile HT Charger Mike Stand Pro-Ham Antennas Mobile HP Antennas Novice Course Amplifier/Power Pack Porta-Peater M-100 Simplex Link		Mar 111
s Associates 1 Software	CW Teaching Systems CW and RTTY Program		Oct 120 Dec 140
terprises	Mobile HT Charger		Feb 136
terprises	Mike Stand Pro-Ham Antennas		Apr 133 May 122
terprises	Mobile HF Antennas		Dec 142
oducts Corp.	Amplifier/Power Pack		Aug 127 Nov 138
neering neering	Porta-Peater M-100 Simplex Link		Nov 134 Nov 134
1 Co.	RTTY Program		May 123
pper search	Soldering Station Antenna Coupler		Jul 104 Dec 143
	Portable Transceiver		Dec 143 Jul 107
	FT-102 Transceiver Active Antenna		Nov 134 Dec 143
G			
of Listening	Speakers, etc.	W8FX	Feb 64
n Skywarn	Tracking Tornadoes	WB5ZAM	Apr 24
the World's x	Mideast SWL'ing	Peterson	Jun 66
rado Queen	Raft Transmissions	K3PUR	Jul 12
Ticket! ?	Advice	NIII	Nov 106
PPLIES			
Current from			
e Regulator mate Fuse	Solid Supply Overload Protection	WA4WDL W2OLU	Jan 39 Aug 52
Electrical			
e Your Pass	Ground Faults	N4UH	Oct 64
ors	Keep Them Cool	K8JL	Oct 76
y-Maker Power	12V Low-Cost	WAGTTY	Nov 56
e Re-Fuser ng in the	Reusable Fuse	K5CN	Nov 72
k k	Overvoltage Reg.	N7JJ	Nov 74
G			
eather	Weather Broadcasts	W9CGI	Apr 102
Squelch for SSB Audio Filter	Voice-Only Squelch	W9MKV	Aug 44
	A QRM-Crusher	W4MLE	Nov 32
Returns	l-Tube Receiver	W1BG	Dec 64

1

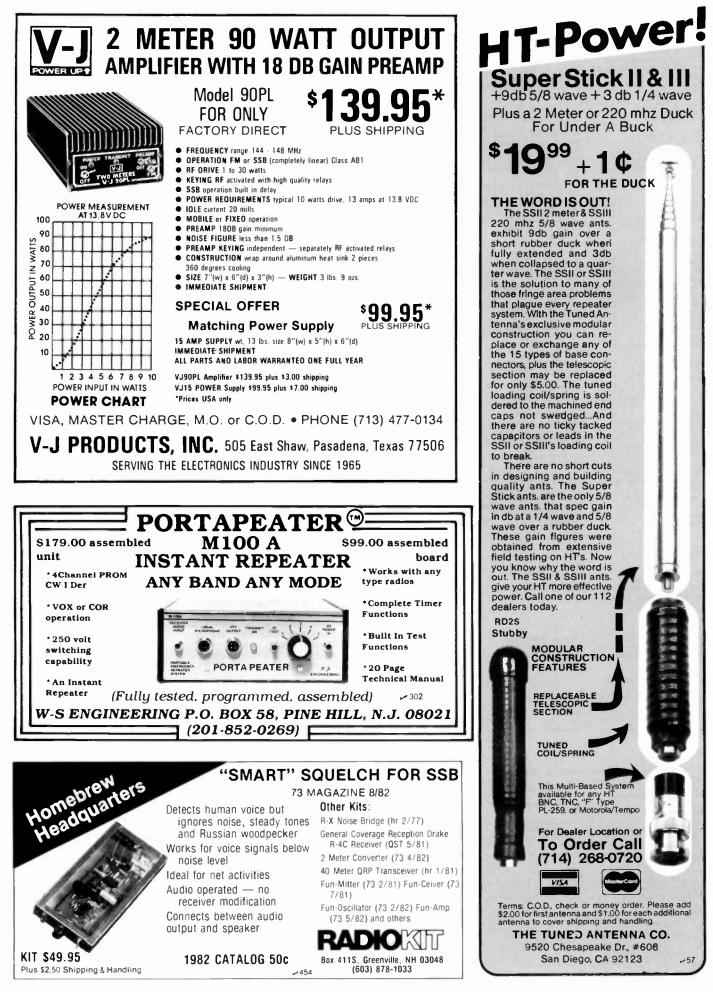

#### REPEATERS

REFERIERS				
Put Talking Time on Your Repeater The Porta-Peaterthe Instant Communicator Death for Squelch Tails Taking It Higher	Antenna Height	WA4VYR WA2BHB WA2NYE W4MLE	Jan Mar Dec Dec	12 14 36
Improving God's IDer	K2OAW Modifications	K9XI	Dec	51
REVIEWS				
AEA Astron CES Com-Rad Industries Curtis Cushcraft Daiwa Debco DFD Systems Digital Electronics Electric Motion Co. Flesher Corp. Heath Heath Heath Heath Heath Heath Heath Heath Heath Com Icom Icom Icom Icom Icom Icom Icom Ic	DTMF Decoder The Morse Talker	KAllR ABlz KAlLR WlXU WlXU WlXU WlXU WlXU WlXU WlXU WlXU	Jan Aug May Oct Sep Jan Jul Jul Jul Jul Jul Jul Jul Jul Jul Jul	$131\\1144\\107\\1095\\120\\130\\130\\130\\130\\130\\130\\130\\130\\130\\13$
RTTY	F 1-600K	KA1LR	Mar	142
Micro Modem No-Frills RTTY Incredibly Simple RTTY RTTY/Tribander Marriage	TU for Computers Surplus TRS-80 Interface Full Duty Cycle	WA4GKO WA4STO WØXI KØARG	Sep Sep Sep Sep	10 24 28 32
SATELLITES				
Shoot the Moon! OSCAR Pathfinder Watching the Weather	Visual Tracking Apple II Program FAX Reception	W9CGI WB6NQK KA9DGL	Feb Mar Apr	34 46 10
TECHNICAL AND THEORY				
Fighting Air Pollution Digital Basics Digital Basics Digital Basics Winning the Coax War	Tuner Theory Part I Part II Part III Feedline Theory	W2AET K4IPV K4IPV K4IPV W9RTF	May Sep Oct Nov Dec	68 72 20 46 90
TEST GEAR				
Build This Antennalyzer Measure Ohms with Your Calculator?	Antenna Tester For High Ohms	W1BG Johnson	Feb Apr	16 28
Poor Man's Spectrum Analyzer	Scope Add-On	WB5IPM	Aug	10
Multi-Purpose Peak Adapter VUM:Volume Units Meter Analog Isn't Dead	Read Meter Peaks Easy dB Meter Use of Meters	K9EUI W4MLE WB6AFN	Aug Aug Aug	54 72 76
Confessions of a Counter Evolutionary Confessions of a	Deluxe Counter	WA2FPT	Aug	100
Counter Evolutionary A Perfect "10" Everyman's Audio Amp. Cutting Current to Size	Part II 10 Function Meter 1-Chip Amplifier Current Measurement	WA2FPT WA2BHB W3KBM W7CRY	Sep Nov Nov Dec	38 10 90 108
All-American Audio Signal Generator	Variable Frequency	WA2SUT	Dec	116
TRANSMITTING				
The Fun-Oscillator Build This Digital Vfo Double Trouble on 50 MHz	QRP Vfo Microprocessor DSB QRP	WAØRBR WA5VQK KL7GLK	Feb Jun Sep	12 12 58

160 73 Magazine • December, 1982

#### TVRO

TVRO Signal Source	Test Gear	NIBEP	Jan	46
Satellite TV Glossary	Part II	Reed Pub.	Jan	54
Going Bird Hunting?	Sat. Central Pt. III	Gibson	Jan	60
A Dish Antenna Anyone				
Can Build	Parabolic	W8DJY	Feb	88
Job's Own LNA	Low Noise Amplifier	WA4CVP	Feb	92
Microwave Master	Wave Behavior	WB4APC	Feb	96
Which TVRO Antenna				
Is Best?	Sat. Central Pt. IV	Gibson	Mar	52
Home-Brew a TVRO				
Downconverter	Construction	WA4CVP	Mar	58
TVRO Q&A	Part I	WBØPOP	Mar	62
TVRO Dish Selection				
Tactics	Sat. Central Pt. V	Gibson	Apr	54
Taylor Howard:				
TVRO Trailblazer	Profile	N8RK	Apr	60
TVRO Q&A	Part II	WBØPOP	Apr	62
'Lite Receiver IV	Part I	WA4CVP	May	48
TVRO Sound Decoders	Sat. Central Pt. VI	Gibson	May	58
'Lite Receiver IV	Part II	WA4CVP	Jun	52
TVRO Transducer	Antenna to LNA	WA4CVP	Jun	58
The MTV Music Box	Sat. Central Pt. VII	Gibson	Jun	60
TVRO: Georgia Style	Antenna From Junk	N8RK	Jul	96
The \$100 TVRO Rovr	Sat. Cent. Pt. VIII	Gibson	Aug	60
The \$100 TVRO Rcvr	Sat. Central Pt. IX	Gibson	Sep	60
TVRO Q&A	Part III	WBØPOP	Nov	64
VHF AND UP				
VHF Converter	2M Receiving	Edwards	Apr	68
Omni-Gain: A Collinear				
For 70 and 23 Cm	For ATV and FM	WA6SVT	May	64
Are You Ready				
For 900 MHz?	Using Microwaves	WB4LNM	Jun	74
Try the GHz Getter	Antenna	WA4WDL	Oct	50

## HAM HELP

I need a manual or a copy of it for the Globe Scout model 680-A. I will gladly pay all costs.

> Dennis Cornell 7835 Captain St. Millington TN 38053

I am looking for the following: MK 731/ARC-51X, H-157/AIC, H-158/AIC, ME-57/U, USM 281E, ME-11/U, URM-120, URM-127, O-1131/GRC, URM-103, AN/ AIC-25 PRC-49, PRC-90, URC-10, ARA-50, SRD-7, URD-4, OA-3633/ORC, R442/VRC, RT524/VRC, PRC-74B, RT-662/GRC, R1051/VRR, 61BT, ARC-159. I also need modules for the following: ARC-58, SG-179A, AM1528B/URC, CV465C/URC, RE-284/URC, 0-655/URC, MC-286B/URC, KY-305/URC, CV-466A/URC, CV-987/GRC-110A, AM1525/URC, AM-476C/AIC-10 unpotted, CU786/TRC-75, CU749/TRC-75, C2848/TRC-75, URM-124, MK-500/U, 878L-3. GRM-21. GRM-10. CU-523/ARC-58. C 1939/ARC-58, R1149/ARC-58(v), C-1940/ ARC-58, R-1283/GRC, R484/APR-14, APR-13, URT-23(v), AM-1780/VRC, H-250/U, RT834/GRC, R1123/ARC-73, C-4074/ RC-73, C-3940/ARC-94, URM-205, VRM-1, and USM-223. I am also seeking any documentation on the ARC-58, TRC-75, and ARC-159, and I would like to hear from anyone using the TRC-75.

Leroy Ritta
PO Box 102
St. Marys 5042
South Australia
Australia

I need the 20-meter heterodyne oscillator coll (part no. 40-771) for my Heath SB-301 receiver.

#### George Savino KV2V 368 N. Monroe Ave. Lindenhurst NY 11757

I would like a schematic for an Allied Star Roamer receiver, number 22-3993-710042-713.

> Joe Hustak WA5ZNO 6821 NW 27th St. Bethany OK 73008

I am in need of videotapes (VHS format) of Novice- and General-class theory material. I also need good audio tapes for mastering Morse Code.

> Robert M. Gallery 9214 Weathervane Place Gaithersburg MD 20879

I need a 3CV1500 tube for my Alpha Vapor amplifier.

#### David Ornee KA9JKO 4615 Howard Ave. Western Springs IL 60558

I need help correcting a severe drift problem in the Imo/vfo of my Heath SB-102. Anyone with information on this problem or who can fix it, please write.

> Harold Wright K4MFN Rt. 1 Box 259 Chancellor AL 36316

I am trying to find a 3-inch picture tube, type C6407, for a Symphonic model TPS-30 television. I would also be interested in buy-Ing the entire set if the picture tube is good.

#### AI Duester 179 Woods Hole Rd. Falmouth MA 02540

I am badly in need of the manual or schematic for Navy surplus receiver R808/ GRC-14, a unit of radio set AN/GRC14.


> Lee A. Grunewald K5JGZ 1020 K St. NW Miami OK 74354

I need the construction manual and schematic for a Dycomm 2-meter linear amplifier. I will pay for the original or copying costs and postage.

> Marvin Rosen N3BQA 20 W. Madison St. Baltimore MD 21201

Wanted: 40-kV, 0-200-pF vacuum variable capacitor
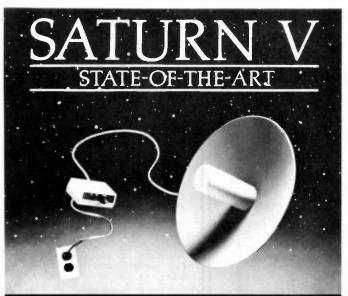
> Cliff Young WA2TGY PO Box 790 Parker CO 80134



The Saturn V is a deep fringe microwave receiver for homeowners that are outside of the service area of local pay TV stations (i.e., HBO, Showtime). It is normally used within line of sight of a transmitting tower in a 50 mile range and is simply attached to your TV antenna mast. This unit is completely ready to install including all cable and mounting hardware. It is designed to be installed by the homeowner.

Microwave and Satelite Systems

We accept MasterCharge & Visa.



1.3	<b>\$16</b> 5.00
4-11	\$120.00
12.49	\$105.00
50-99	\$ 95.00
100-149	\$ 85.00
150-up	\$ 80.00


4558 Auburn Blvd., Suite 208 Sacramento, California 95841 (916) 454-2190 --72

#### SATELLITE TV SYSTEMS "COMPARE OUR QUALITY, PRICES AND SERVICE!"

WE MANUFACTURE: MOTORIZATION SYSTEMS PARABOLIC DISHES POLAR MOUNTS. LNA HOLDERS DEMO TRAILERS ALUMINUM HORNS CUSTOM PARTS WE STOCK: WASHBURN GILLASPIE ALLIANCE KLM. DRAKE ATV AVANTEK LOWRANCE CABLE & CONNECTORS GARDINER SWITCHES & HARDWARE CALL, WRITE OR 🛩 FOR OUR LATEST BROCHURE AND PRICES. LEWIS CONSTRUCTION CO AUSTINIC. LEWIS K4GGC P.O. BOX 100 901-784-2191 HUMBOLDT, TN. 38343 "IN BUSINESS AT THIS LOCATION SINCE 1964" \_\_452



NEW MODE	ENEW WORLD OF TV VIEWING WITH L CVU-40, 40 CHANNEL CABLE TV C De EXTRA CABLE TV "MIDBAND" & S	ONVERTER		POPULAR IC'S OUALITY SECONDS	Sm	-
	on your UMF DIAL		TYPE	DESCRIPTION	1 1.9	10.0
Eliminates t	he need for renting or leasing. This	stable and	I M 380N	2 watt Audio Power Amp	\$1.49	\$1 29
Use of thes unit may be subject to the received of			LM 386N-3	Low Voltage Audio Amp .500W/9V	1.59	1 29
	FOR VIDEO TAPING FROM CAL	SLE /VI	NE-564N LM-565N	Digital Phase Locked Loc		3.15
cable channels for taping on any V			LM-733N	Phase Locked Loop Video Amo	1,49	1.2
watching a different channel on your	TV Now ZC		MC-1330	Video Detector	2.49	1.85
Simple to install and operate on any	make of TV with UHF PLUS PO	STAGE	MC-1349	Video If Amp	2.08	1.85
NOW AVAILAB	LE		WC-1350	Video It Amp	1.75	150
NEW TUNEABLE DELUX M		95	MC-1352 MC-1358	Video If Amp AGC Audio If Amp	2 69	2.01
			MC-1374P	R.F. Modulator	3.19	2.8
WINEGARD	BRAND NEW UHF		MC-1458	Dual Comp Op Amp	88	7
75 DHM UHF YAGI ANTENNA	S VARACTOR TUNERS		MC-1496N	Balanced Mod/Demodula		1.5
A.	Contract of the local division of the local		MC-5121	Hybrid Amplifier	13.72	Cal
	····		LM-1800 LM-1889	PLL Stereo Decoder Video Modulator	4 49	3.9
			CRETOOD	LINEAR VOLTAGE REGULATOR		6.43
12 db GAIN	VITT THE	C.B.	LM-7805	5 Volt Positive Volt Reg	1 39	1.25
MANNELS 44 - 52 OPTIONAL	Sanvo YOUR	Mitsumi	LM-7808	8 Volt Positive Volt Reg	1.39	1.2
5895 EA. Winegard UHF Antenna Preamp	45 MHz CHOICE	45 MHz	LM-7812 LM-7815	12 Volt Positive Volt Reg 15 Volt Positive Volt Reg	1 39	12
S OR MORE 18db Gain	Dutput \$24.95 m	Output	LM-7818	18 Volt Positive Volt. Reg	1.39	12
36"5 EA. 339" an.	Call for Quantity P		LM-7824	24 Volt Positive Volt. Reg		1.2
MRF 601         \$2,75           9-00         216           9-00         316           MRF 2017         3-45           MRF 2019         3-46           9-00         30-20           28-00         30           28-00         30           28-00         30           28-00         30           28-00         30           28-00         30           28-00         30           29-00         30           29-00         30           2000         30           2000         30           2000         30           2000         30           2000         30           2000         30           2000         30           2000         30           2000         30           2000         30           2000         30           2000         30           2000         30           2000         30           2000         30           2000         30           2000         30           2000         30	5% MICA CAPS 5% 1001 422 ea 360pt 605 ea 43pt 365 ea 1200pt 895 ea 11001 365 ea 3000pt 139 ea TUSA MAX-2 LOW LDSS MATCHING TRANSFORMERS Indoor 75: 300 a129 10. Up 96	6 ½ "D w aluminum	12 or more 135V	4/9 = a         3300 m/dg 3/9           69 = a         3300 m/dg 3/9           69 = a         109 e a           109 e a         Call us for           109 e a         Call us for           109 e a         UHF           50 m a         Si           51 m a         Si           52 m a         Si           53 m a         Si	VHF - F	159- 198- 1.79- DrScS M 900 M TUS
25¢ ee.	Outdoor 75 - 300 1.69			LOW LOSS 3.	5-4 db, Lov	w VSV
100 tor 514.70	10 · Up 1.49		more \$10.		32	.49
SURPLUS AUDIO & VIDEO RF MODULATORS Mock up sheet included Now *5.49 s.	For CATV - MATV - VCR 75 ohm - 90 db Isolation Write Trey Last <sup>16</sup> , 95 se.	SURPLUS SYLVANIA VHF VARIA 45 MHz of through 11 band chart cluded. WHIL	17 74	ERS he mid- taitic in- try Type to the period to the perio	PULĂR NEDUS P Control 'switch mbwheei	ART:
ORDER NO Toll FREE 800-854-46 OUTSIDE CALIFOR 714-635-50 INSIDE CALIFOR	55 ELECTRO 1056 N. STATE COLL ANAHEIM, CAL	EGE BLVD. IFORNIA 9	., DEPT. G 2806	156 OPEN TUES - FR 10 - 6 SAT 10 - CLOSED SUN & MO	Can FR Mail Catal	or Win or EE Datier

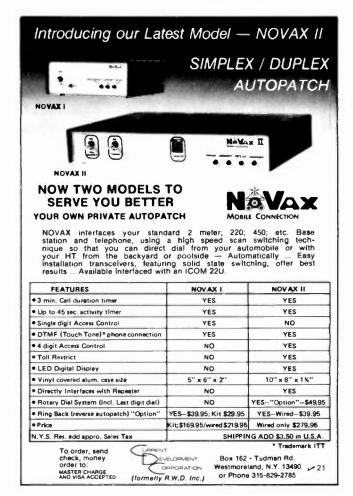

DX-Notes Have Gained Wide Acceptance *In the Amateur Media	! JARL Awards Kit
*At DAYTON Hamvention *All across the USA *With DX TOO	! *Highly Acclaimed Worksheets
5B DXCC PLUS : DX-Notes Invites Comparison	*AJD 1D Call Areas
•SEVEN wide W/C Columns : •Compare Accuracy	! *WAJA 47 Prefectures
•Log Entire DX Callsign : *Compare Efficiency	JCC 647 Cities
•YOU Choose Modes/Bands : •Compare Useability	*JCG 569 Guns
PLUS *Buro *3rd Party *More : *Compare Convenience	! Complete with JARL Information
◆Enter YOUR Atlas Page # : ◆Compare Completenes	
	*Efficiency Engineered
•Unique "Rareness" Guide : 1200+ Current, Commemorative	
•Latitude *Longitude : Special Event & Historic	
PLUS Info Computed for YOUR QTH: Prefixes Indexed	
•Time Zone Difference : PLUS COUNTRY Cross Reference	
•EXACT Beam Heading : 500+ Possessions, Islands,	
<pre>*Miles *Kilometers : Oeleted, ETC Names Listed</pre>	**3075 US Counties Listing
PLUS FREE Bonus **5B WAZ Kit : BUY DX-Notes Just \$12.95PPd	i ! JARL Awards Kit Just \$7.95PPd
Send Call, Name, Address, Latitude, Longitude, Time Zone AND Ch	
KH6MD Randall Sherman POB 158 Kahului, Maui, HA	AWA11 96732



### See What You've Been Missing!

Stay in touch with world events, monitor weather, ship traffic, and radio amateurs. Connect to your receiver and display shortwave radio teleprinter and Morse code transmissions with the new receive-only HAL CWR-6700 Telereader.

- **Receive ASCII or Baudot RTTY**
- Six standard RTTY speeds •
- **3 RTTY shifts for low or high tones**
- Adjustable space for fine tuning
- Receive Morse code 4 to 50 wpm
- 16 lines by 36 or 72 character display
- Two page video display
- Parallel ASCII printer output
- Requires ±12 VDC and external TV monitor
- One year limited warranty

**BOX 365** 

Small size  $(8'' \times 3'' \times 12.75'')$ 

Write or call for more details. See the CWR-6700 at your favorite HAL dealer.

KH6MD

### HAL COMMUNICATIONS CORP.

**URBANA, ILLINOIS 61801** 

217-367-7373 - 345

Д	NT	ENN	AS		1
•	(305)	294-203	3	VISA	
	· ·	TRAP DIPOLES		- 417	
	MODEL	BANDS	LGTH	PRICE	
	TSL 8040	80.40	78	\$49.95	
	TSL 4020	40.20.15	40'	\$47.95	
	SMALL LO	T SHORTENED	DIPOLES		
	SL-8010	80,40,20. 15.10	75	\$59.95	
	SL-160	160	130	\$38.95	
	SL-80	80	63	\$37.95	
	SL-40	40.15	33	\$36.95	
	FULL SIZE	PARALLEL DIPO	OLES		
	FPD-8010	80.40.20. 15.10	130	\$49.95	
	FPD-4010	40.20.15.10	63	\$44.95	
		TABLE VERTIC			
		Package No F			
	MODEL	BANDS	HGHT	PRICE	
	PV-8010	80.10	13'	\$59.95	
	and successful the successful the	ESIGN GOTHAN	ALL BA	ND	
Ψ	VERTICALS				
	V-160	160.80.40.20. 15.10.6	23	\$44.95	
	V-80	80.40.20 15.10.6	23	\$42.95	
	V-40	40.20.15.10.6		\$40.95	
		MOUS GOTHAN			
	CHAM Full	nts—3 Bands Co PIONSHIP GOT Size Complete ALER INQUIRIE	HAM BE	MS 95	
		SEND LARGE S			
		ping: Dipoles &			
		\$7.00 Canada;			
		Quads Shipped		reight	
		a. Add 5% Sale			
1	415 Firs	t St. • Key	West,	FL 33040	)

GOTHAM

### FILTER CASCADING

The most cost-effective way to improve the selectivity of any receiver – old or new – is to improve its IF filtering. A Fox-Tango CascadIng KIt puts a high-quality steep-sided 8-pole filter in series with your present filter(s), both SSB and CW. The result is narrower Bandwidth and better Shape Factor, both of which dramatically reduce adjacent channel QRM - a necessity in today's crowded bands.

#### CONSIDER THESE KIT FEATURES

- Easy installation 30 minute average.
  No drilling, switching, alignment.
  16 poles of filtering yield: Filter Shape Factor as high as 1,19. Ultimate Rejection better than 100dB. Works wonders on SSB; improves CW
- Compensates for Filter Insertion loss
- Complete instructions, clear diagrams. No RX audio impairment, TX unaffected. ٠
- Includes Filter and all needed parts
- Fits all models of Series any letter. All Filters 8-pole Guaranteed One Year

SPECIFY KIT WANTED WHEN ORDERING YAESU FT101 \$75; FT101ZD \$70; FT107 \$75; FT901/2 \$65; FR101 \$55 (filter only). KENWOOD TS520/R599 \$70; TS820 \$70; TS830/RB20 \$150 (Two Filters). HEATH SB104A \$60.

Shipping \$3 (Air \$5). FL Sales Tax 5%

In addition to the above, FOX-TANGO stocks a wide line of \$55 SSB, CW, and AM 8-pole filters for Yaesu, Kenwood, Drake R4C and 7-line, and Heathkit. Also, special filters made to order. Send specs for quote



GO FOX-TANGO - TO BE SURE! Order by Mail or Telephone. AUTHORIZED EUROPEAN AGENTS Scandinavia: MICROTEC (Norway) Other: INGOIMPEX (West Germany)

FOX TANGO CORPORATION Box 15944S, W. Palm Beach, FL 33406 Phone: (305) 683-9587

# FREE! Brand New Catalog With Over 150 Programs

under The Sun

Best

Software

Instant Software's new catalog is free and it offers 150 of the finest programs you can find. At reasonable prices ... and a variety you've never seen before in one catalog. And they're all contained in the new 16 page 1983 Instant Software catalog. You'll find:

ASSEM/ZSIM—2 great utilities in one super package. Assembly language programmers, this package solves all your programming problems from ASSEM to ZSIM.

Super Utility Plus—the most powerful program of its kind. A must for every serious TRS-80\* disk installation.

Geography Explorer Series—the exciting, attention-holding series that teaches your children essential geographical facts.

**Phaser Blast**—phaser-armed robots, enemy Hovertanks...prepare for a journey into the war of the future.

Space Shuttle—experience the ultimate flight as you pilot America's Columbia through launch, orbit, re-entry and landing.

Plus dozens of other practical, mind-boggling or spine-tingling programs.

And now you can get the new 1983 Instant Software Catalog absolutely free. You don't even have to pay for the phone call. Just dial toll free:

### 1-800-258-5473

and ask for your free copy of Instant Software's 1983 Catalog. It could be the smartest call you'll make all year.

Instant Software. The best software under the sun.

Instant Software

(a subsidiary of Wayne Green Inc.)

Route 101 & Elm St.

Peterborough, NH 03458

APLORER IN


\*TRS-80 is a registered trademark of the Radio Shaek division of Tandy Corp

Yes, I want a free catalog! Please send my free copy to:

Name		
Address		
City	State	Zip
I have a		computer
		1273NC

The best software under the sun.

Instant Soft

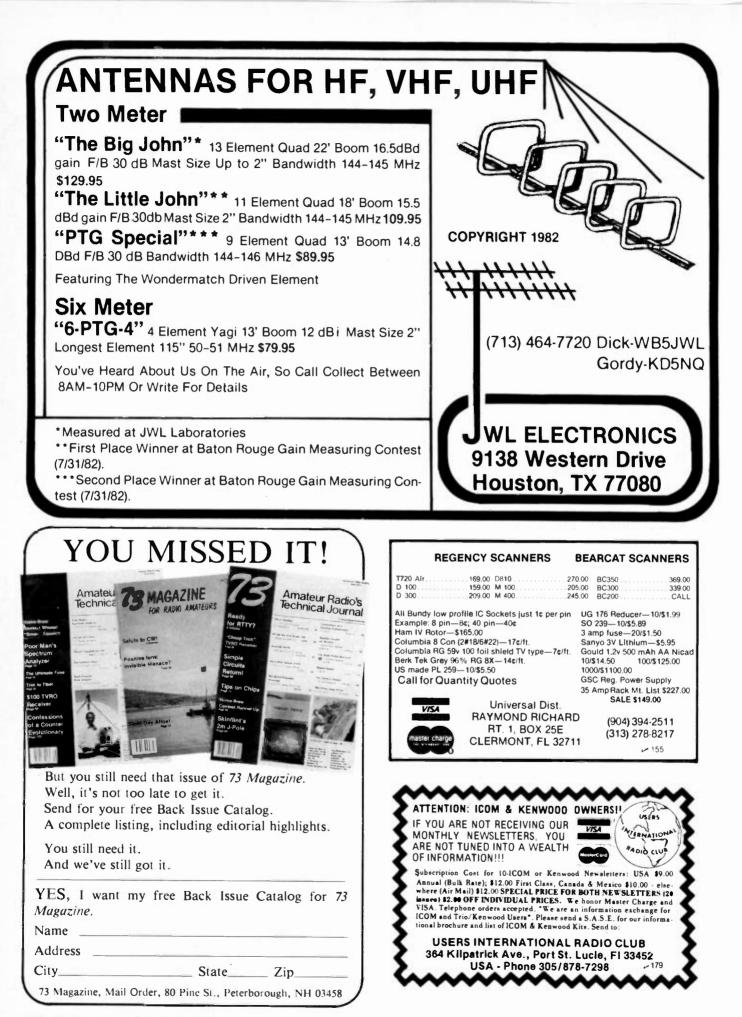



Don't Be Left Out in the Cold with the Russian Woodpecker

## **GET A** MOSCOW MUFFLE

Another first from AEA. The Woodpecker Blanker, WB-1 really works. This unit effectively blanks the pulsing interference of the Russian Woodpecker. Two versions are available, the WB-1 for use with communication receivers and WB-1C for use with all popular transceivers.



This extremely useful accessory is designed for direct insertion between your receiver (or transceiver) and the antenna. It is both MORE EFFECTIVE than I.F. type blankers and requires NO MODIFICATIONS to your receiver! The unit operates from a 13 VDC  $\pm 2$ VDC power source at less than 575 mA. (AEA AC wall unit AC-1 will operate the blanker.)

The blanker works well on both CW and SSB modes that are being interfered with by a woodpecker. Controls on the front panel include; four push button switches, a synchronize control and a width control The WB-1 also features a low-noise untuned broadbanded 6 db gain pre-amp which can be selected with or without the blanker enabled. The WB-1C uses the same circuitry but includes a carrier operated relay (COR). This provides protection to the receiver section during transmissions from the attached transceiver.

For more details, write for our latest catalog or visit your favorite dealer.

Prices and Specifications subject to change without notice or obligation.

ADVANCED ELECTRONIC APPLICATIONS, INC. P.O. Box C-2160,

Lynnwood, WA 98036 (206) 775-7373 Telex: 152571 AEA INTL





## AWARDS

Bill Gosnev KE7C Micro-80, Inc. 2665 North Busby Road Oak Harbor WA 98277

#### LMRE AWARDS

Here are the details of an awards program recently instituted by the Liga Mexicana de Radioexperimentadores (LMRE) and open to all amateurs anywhere; there are currently four awards offered.

#### 676 Award

Available for confirmed contact with any 6 Mexican stations after January 1, 1980

#### American Award

Requires confirmed contact with 40 countries in the Western hemisphere (ARRL DXCC list) plus 10 contacts with XE stations

#### Mexico Award

Requires confirmed contacts with 20 stations in Mexico

#### Worked All XE (WAXE)

Regulres 25 confirmed contacts, 15 with XE1. 5 with XE2, and 5 with XE3 stations.

Awards cost US \$3.00 or 10 IRCs each and require that either the QSL cards or a list certified by the awards secretary of the local league be submitted to the LMRE of Mexico City. If QSL cards are submitted, be sure to include sufficient funds for return of same via international registered air mail. The address for applications is: LMRE Awards Manager, c/o Manuel De Lera, PO Box 907, Mexico 1, DF, Mexico,

#### JOLIET AMATEUR **BADIO SOCIETY**

The Jollet Amateur Radio Society is sponsoring the JARS award. Illinois stations must contact 10 JARS members. Continental US stations must contact 5 JARS members. No repeater contacts. An updated membership list is available on request for an SASE or 2 IRCs. Send list of log information and \$1.00 (DX station may send 3 IRCs) for the award to: Paula Franke WB9TBU, Certificate Chairman, PO Box 873. Beecher II. 60401

#### THE IOWA AWARD

An award will be issued to any amateur who has worked 19 lowa counties. Cost will be \$1.00. Each additional 20 counties will earn a new award, OSLs not required. Send usual log information and statement by two other amateurs or one club officer to the Mississippi Valley Radio Club, 3518 Colum bia, Davenport IA 52804

#### THE PLANET EARTH AWARD

The South West Ohio Repeater Club (SWORC) takes great pleasure in presenting the Planet Earth Award. To qualify, applicants must submit proof of QSOs with 10 different stations on the planet Earth. There are no restrictions, but ORP operations will be noted. Send your list of contacts along with the award fee of \$4.00 or 12 IRCs with an SASE to the Awards Chairman, South West Ohio Repeater Club, PO Box 18005, Cincinnati OH 45218

#### WORKED ALL MORTON AWARD

The Morton Amateur Badio Club has announced its new award program. The Worked All Morton award is issued to those hams who have had QSOs with five members of the Morton Amateur Radio Club, or hams living in Morton, Illinois. Only contacts made on or after January 1, 1981, will count. To receive the award, applicants should send log information listing at least five Morton contacts along with a large SASE to Morton Amateur Badio Club. 701 Columbus Avenue. Morton IL 61550.

The club operated a special events station, W9EEB, during the Annual Morton Pumpkin Festival. An attractive certificate for the Pumpkin Award will be sent to all who QSL. The operation was held September 16 through 18, 1981, on 7.280, 14.280, 21.380, and 28.680 MHz. The award will be Issued on receipt of QSL and a large SASE by W9EEB, 701 Columbus Avenue, Morton IL 61550.

In an effort to restore good operating practices to the amateur bands, a group of Morton Amateur Radio Club members have undertaken the sponsorship of the All American Alligator Award. This probably least-coveted certificate will be issued to those stations which exhibit acts Inconsistent with the spirit or laws of amateur radio. We hope the award will be recelved in the same spirit with which it is being issued.

#### **TEN-METER FM AWARDS**

Sponsored by the North Whidbey Island Repeater Association (NWIRA), all contacts must be made on or after January 1. 1981. Crossmode contacts do not count. Contacts must be two-way ten-meter FM. Special endorsements include All-Mobile, All-Simplex, Single-Frequency accomplishments, and contacts made within a single day, week, month, or year. Do not send QSL cards; forward your list of contacts showing the date, time, and frequency of each OSO and provide a brief station description. Send with the fee of US \$4.00 for each award to the attention of: Ten-Meter FM Awards Program, 2665 North Busby Road, Oak Harbor WA 98277

#### Worked All Districts

To qualify, applicants must work one ten-meter FM station in each of the ten US call districts.

#### Worked All States

Applicants must work a minimum of 50 US states on ten-meter FM.

#### Centurion

This award requires the applicant to work a minimum of 100 stations on tenmeter FM

#### DX Decade

Applicants must work a minimum of ten DX stations outside the fifty US states and Canada on ten-meter FM.

#### North American

To qualify, applicants must work all ten US call districts, a minimum of six Canadian provinces and/or territories, and at least four DX countries within the North

American continent (other than the US and Canada) on ten-meter FM.

#### OTHER AWARDS

#### 3rd Call District Maryland

Worked all Bowie ARC in two classes. First figure US stations, second, DX stations: class 1 = 4/2: class 2 = 2/1. Log data SASE. No charge. To: John Rouse KA3DBN, PO Box Drawer M, Bowie MD 20715.

#### 4th Call District Florida

Elorida Skin Certificate of Merit issued on recommendation of two other amateurs for outstanding service, \$1.00, Send to: Florida Skip, Box 501, Miami FL 33166.

#### XYL Award by Florida Skip

Only requirement is to render aid and comfort to your husband in and out of the shack. \$1.00 or 4 IRCs to: Elizabeth Clark W4GGO, 41 Lenape Drive, Miami FL 33166

#### Three Thousand DX Award

North Florida ARS. Work three or more stations 3,000 miles or more distant, ragchew-type QSOs only. Two certificates will be awarded, one to you and one to the DX stations, \$2.00 to: Dale Mann N4AWI. 5433 Glorianne Circle North, Jacksonville FL 32207

#### Worked Broward County Cities

Broward ARC. Stations in the Florida counties of Broward, Colllers, Dade, Glades, Henry, Lee, Martin, Monroe, or Palm Beach must work all 29 cities: others, 15. Work mobiles in Broward county. No awards for your mobile. GCR, US \$1.00; DX, 10 IRCs, to: WD4RAF, 1921 NW 41st Street, Oakland Park FL 33309.

#### 6th Call District

CHC Worked All Counties California. Issued in five classes: Class D = 20 to 28; class C = 30 to 38; class B = 40 to 48; class A = 48 to 57; class AA = 58; GCR, SWL. \$3.00 endorsements. \$1.00 to: Scott Douglas KB7SB, PO Box 46032, Los Angeles CA 90046.

#### 7th Call District

CHC awards, to: Scott Douglas KB7SB, PO Box 46032, Los Angeles CA 90046.

Washington State Counties Award, Issued in five classes: Class D = 10 to 15 counties; class C = 15 to 20; class B = 20 to 30; class A = 30 to 43; class AA = 44.

Oregon State Countles Award. Issued In four classes: Class C = 10 to 15 counties; class B = 20 to 25; class A = 30 to 35; class AA = 36.

Nevada State Counties Award, Issued in three classes: Class C = 8 to 10 countles; class B = 10 to 15; class A = 15 to 17. Utah State Counties Award, Issued in

three classes: Class C = 7 to 10 counties; class B = 18 to 24; class A = 22 to 29. Wyoming State Counties Award, Issued

in three classes: Class C = 7 to 10 countles; class B = 15 to 20; class A = 20 to 23.

Idaho State Counties Award, Issued in four classes: Class C = 15 to 20 countles: class B = 20 to 30; class A = 30 to 43; class AA = 44

Montana State Award, Issued in five classes: Class D = 15 to 20 counties; class C = 20 to 30; class B = 30 to 40; class A = 40 to 55; class AA = 56.

GCR, SWL, \$3.00; endorsement, \$1.00.

#### Morocco

CN8 Award by AREM. Work 15 CN8 stations on 1 band, 12 stations on 2 bands, or 8 stations on 3 bands, GCR and 3 IRCs to

AREM, PO Box 2060, Casablanca, Morocco

Diploma De La Ville Rahat by Assoc. Royale Des Radio Amateurs De Maroc, c/o CN8OB. PO Box 299. Rabat, Morocco. Work 10 stations in Rabat after January 1, 1968. All others, 5. SWL 10 IRCs, list.

#### India

Worked Republic of India, by ARSI, Box 534, New Delhi, India. Contact 50 different VU stations after January 16, 1950. QSLs, list, 12 IRCs

The Gateway of India Award, by ARS of India, Western Zone. Work VUs in the Western Zone after November 9, 1957. Asia stations work 10; others, 5, GCR, 6 IRCs. To: Dady Major VU2MD, 85 Sleater Road, Petit Manslon, Bombay 7, India.

#### Lebanon

By Lebanese RAA, PO Box 1217, Beirut, Lebanon. Work 10 stations after July 1, 1958; with endorsement seals additional 10. No charge, GCR.

#### Spain

Spanish Diploma, by URE, Apartado De Correos, Num 220, Madrid, Spain. QSLs from 125 Spanish stations on CW with 60 on 3.5 or 7 MHz, 10 on 28, 15 on 21, and 10 on 14 MHz. After January 1, 1952. Send 40 QSLs. list, and return postage.

125 EA Award: By URE. Hortaleza 2. Apartado 220, Madrid, Spain, Work 125 EA stations after January 1, 1952, Including all Spanish call areas. At least three contacts must be made with each (EA1 through EA0) counting EA9 and EA0 as one area. QSLs, list, and return postage.

1

#### Romania

"YO-AD" All Districts Award. Work YO districts as follows: First figure is the number of districts to be worked, second is the number of QSOs per district. Applicants in zones 15, 16, 20: class i = 8/10; class II = 6/6; class III = 3/3. Applicants in zones 14, 17, 21, 33, 34: class I = 8/6: class II=6/4; class III=3/2. Applicants In all other zones: class I = 8/3; class II = 6/2; class III = 3/1. 144 MHz: class I = 4/1; class II = 3/1; class III = 2/1. There are 8 YO districts In all.

#### Canary Island

Work EA8 stations after April 4, 1971. QSLs, SWL, 10 IRCs to: URE, PO Box 860. Las Palmas, Canary Islands, Spain. EA and LX stations work 30, rest of EU, Central and South America, work 20, North America and Africa work 10. Asia, Oceania, VHF and UHF, work 5.

#### Austria

WAOE Diploma. Work OE districts all CW, all phone, or mixed after January 4, 1954. Austria and adjoining countries work three stations each in OE districts 1 through 9 (with OE4 and OE9 counting as one district) using at least two different bands. At least one contact per OE district must have been made on 40 or 80 meters. Rest of EU stations: Same as above but without 40- or 80-meter requirements, GCR stations outside EU. Work one OE station station in each OE district on any band (8 OSLs). GCR. Same station may be worked on all bands. WAOE SWLs for 8 districts. Send list and 10 IRCs.

#### Colombia

100 HK3 Award: by LCRA. Third HK zone. Coordinator for contacts with 100 HK stations after January 1, 1960. SWLs, no charge, GCR, list in alphabetical order and send full log data to: HK3VV, AP 584, Bogota, Colombia.

Double Call Award: Work HK stations with double- or triple-letter calls. Three

Instant Software's prices are going up. Stop waiting for the right time to buy! Stock up now on all the programs you want, and SAVE. Shop early and save \$\$\$\$\$ on your Christmas shopping also.

Beat The Price Increasel Instant Software's prices are going up. Remember, this is the last chance to buy Instant Software's products at the old 1982 prices. Effective November 15, 1982\* Instant Software will be raising its prices on most of its products.

Order today so that you too can beat the Instant Software price increase. Just call toll free:

# 1 - 800 - 258 - 5473



Dealers

Instant Software

'Old prices will not be accepted after this date.

(a subsidiary of Wavne Green Inc.)

Route 101 & Elm St. Peterborough, NH 03458 603/924-9471

Selling 73 Magazine will make money for you. Consider the facts:

Fact #1: Selling 73 Magazine increases store traffic-our dealers tell us that 73 Magazine is the hottest-selling amateur radio magazine on the newsstands.

Fact #2: There is a direct correlation between store traffic and sales-increase the number of people coming through your door and you'll increase sales. Fact #3: Fact #1 + Fact #2 = INCREASED \$ALE\$, which means more money for you. And that's a fact.

For information on selling 73 Magazine, call 800-343-0728 and speak with Ginnie Boudrieau, our bulk sales manager. Or write to her at 73 Magazine, 80 Pine St., Peterborough, NH 03458.



Let us know 8 weeks in advance so that you won't miss a single issue of 73 Magazine.

Attach old label where indicated and print new address in space provided. Also include your mailing label whenever you write concerning your subscription. It helps us serve you promptly. Write to:

magazine

Subscription Department P.O. Box 931 Farmingdale NY 11737

Extend my subscription one additional year for only \$19.97 Payment enclosed Bill me

Canada and mexico \$22.97, US funds, Foreign Surface \$39.97, US funds, drawn on US banks

If you have no label handy print OLD address here.

Name		Call
Address		
City	State	Call Zip
	print NEW address	here:
Name		Call
Address		
City	State	Zip32DR6M

classes: Class C = 10, class B = 20, class A = all 26 double calls (AA to ZZ); AAA counts in lieu of AA. BBB for BB, etc. Contacts after January 1, 1960. No charge, GCR, log data to: HK3VV, AP 584, Bogota, Colombia.

CHK Award: by LCRA. Work HK stations. HK stations work 100 other HK stations, stations in Americas work 50, others work 25. HKs send QSLs, others send certified list authenticated by club official. QSLs must have been sent and received. To: LCRA, AP 584, Bogota, Colombia.

ZHK Award: by LCRA. Confirmed contacts with HK zones. HKs send QSLs from all 10 zones. Americas work 9, rest of the world work 8. All except HKs send list certified by club official. To: LCRA, AP 584, Bogota. Colombia.

(No charges given for any of the LCRA awards.)

HK7 Award: by RC Santander, PO Box 222, Bucaramanga, Colombia. Work 7 HK stations, either all CW or all phone, after January 1, 1962.

10 HK1 Award: by RC Del Atlantico, Apartado Nacional 184, Barranquilla, Colombia. Work 10 HK1 stations post World War II. GRC—certifled by club officer. (No costs given.)

HK5 Award: by LCRA. Work HK5 stations after January 1, 1957. American countries work 12, Colombian stations work 20, rest of the world work 8. GCR list to: Box 6149, Cali, Colombia.

#### US Navy Award

Work 5 US Navy ships. To: Office of Naval Communications, Director, Navy MARS (OP945N), The Pentagon, Washington 25 DC 20301.

Radioman Submarlne Award: Work 2 amateur radio stations on board submarines of Submarine Squadron Twelve plus club station W4YVS or any statlon on board the *Bushnell*. After January 1, 1961. Notarized log information with statement that the Information is true and accurate to: Radio Amateur Club, Submarine Squadron 12, Naval Station, Key West FL 33040.

#### **ARGONNE ARC**

The Argonne Amatuer Radio Club plans to operate the club's memorial station, W9QVE, to commemorate the 40th anniversary of the first controlled nuclear chain reaction experiment conducted at the Alonzo Stagg field on the University of Chicago campus. Two stations will operate from 1500 GMT December 4 through 2400 GMT December 5.

Frequencies: phone and CW—20 kHz up from lower edges of the General portions of the 80-10m bands; Novice—40 kHz up; 2m— 145.19/144.59, 146.52, and 147.42; RTTY— 14.090 and 146.70. Send a business-type SASE or \$1.00 for an 8" × 11" unfolded certificate to AARC, PO Box 275, Argonne IL 60439.

#### **BETHLEHEM WV EXPEDITION**

The Triple States Radio Amateur Club will operate dally from Bethlehem, West Virginla, December 9 through December 12, from 1400 to 2300 UTC. Operating frequencies for WD8DDL/8 will be 7.275, 14.325, 21.425, and 28.550 MHz on SSB, and 7.110, 14.075, 21.110, and 28.110 MHz on CW. A special holiday certificate will be sent to all those contacted who send an SASE to TSRAC, 26 Maple Lane, Bethlehem, Wheeling WV 26003.

#### CHRISTMAS VILLAGE

The K1BCI C/Q Radio Club will operate a special event station honoring the 35th anniversary of the Christmas Village located in Torrington, Connecticut. The club will operate from the Christmas Village from December 11 through 19, 1982, on 10, 15, 20, 40, and 80 meters. Certificates of this event will be issued for contacts made. For further information, contact Jim WA1YZA or Nellie WB1DVC.

#### SANTA CLAUS

The Pike County Amateur Radlo Club of Winslow, Indiana, will operate a special events station from Santa Claus, Indiana, from 1700Z December 18 through 1700Z December 19, 1982. The callsign will be W9CZH. Operating frequencies will be (plus or minus ORM) 21.395, 14.305, 7.265, 3.925 phone, 7.133 CW, 14.093 RTTY, and 146.52 FM. Certificate for QSL and SASE to Santa Claus, PO Box 111, Ireland IN 47545.

#### CHESTER GREENWOOD DAY

The Sandy River ARC will operate KA1CNG on Saturday, December 18th, 1500Z, to Sunday, December 19th, 2100Z, in celebration of Chester Greenwood (inventor of the earmulf) Day. We will also operate mobile from the Chester Greenwood Day Parade and related activities on Tuesday, December 21st, 1400Z to 2100Z. Frequencies: 5 to 10 kHz from bottom of General band edges and 3940 kHz. Certificate for your QSL card and two first-class stamps (no envelopes please) to KA1CNG, 5 Franklin Ave., Farmington ME 04938.


#### HONG KONG ACTIVITY

The Hong Kong Amateur Radio Transmltting Society (HARTS) Is pleased to announce that once again there will be a VS6 activity day between 0001G Saturday, April 2, 1983, and 2359G Sunday, April 3, 1983. As in previous years, many VS6 stations will be active on all bands/modes.

1983 is World Communications Year (WCY), and during 1983 the special callsign VS6WCY will be in use by the HARTS club station. Special QSL cards will be issued for QSOs with VS6WCY. QSLs for WCY station should be sent to the Hong Kong QSL Bureau Manager, PO Box 541, Hong Kong.

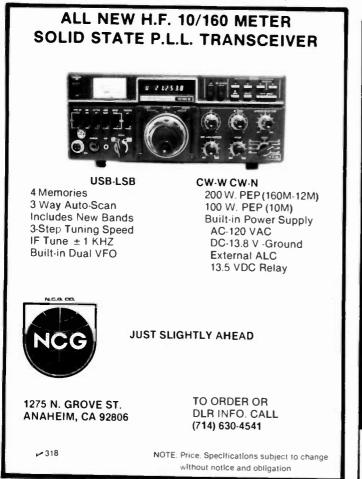
#### WORKED ALL NORTH POLE

The Borealis ARC will present, upon receipt of the request with the callsigns and dates worked of a mInimum of three BARC members and \$2.00, a Worked All North Pole certificate. Operating time will be from approximately 0400-09002, 30 kHz up from the lower edge of the Novice and General bands, plus or minus ORM. The club member whose callsign appears on the largest number of certificate requests during the month of December will win a prize. Certificate requests should be sent to: Borealis ARC, clo Wendall Keller, SR Box 80343, Fairbanks AK 99701.





168 73 Magazine • December, 1982

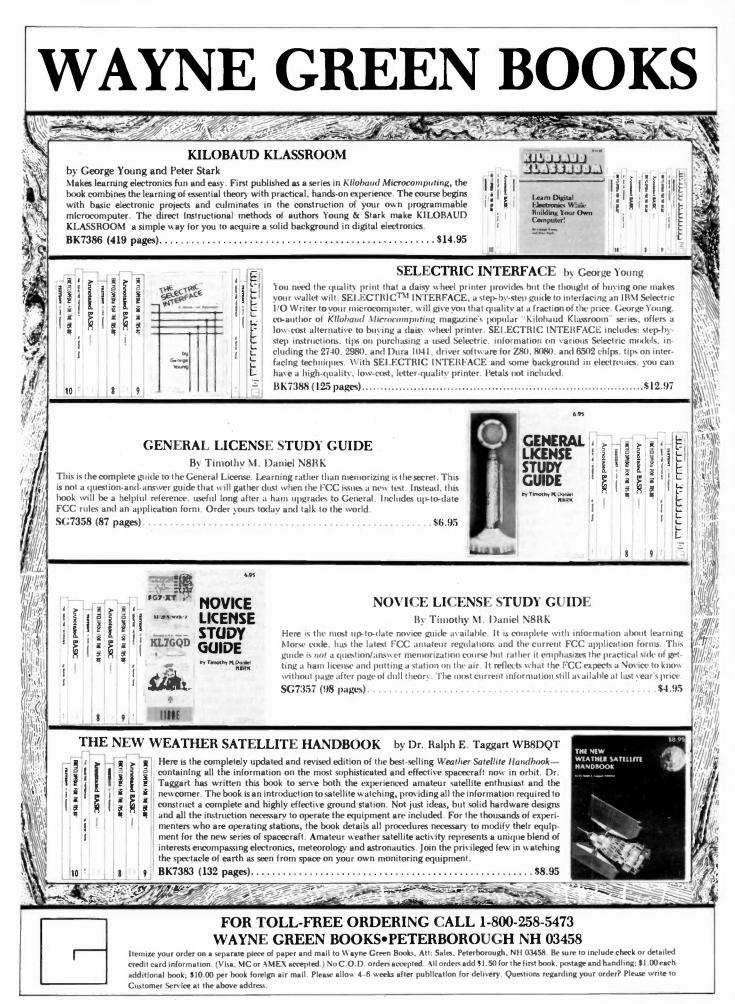



Chod Harris VP2ML Box 4881 Santa Rosa CA 95402

#### THE TEN-METER BAND

Many DXers abandon the 10-meter band as sunspot numbers fall. But 10 meters provides DX excitement even at the bottom of the sunspot cycle. Not as much, to be sure, as when 10 Is wide open to three continents at once, but, still, there is plenty of action. Because 10 meters lies at the dividing line between HF and VHF, it displays some of the propagation features of each part of the spectrum. By learning to recognize the different modes of propagation and practicing the operating patterns unique to each prop agation mode, the DXer can quickly improve his success on 10 meters. The second weekend of the month of December provides a fine opportunity to practice this skill, in the ARRL 10-Meter Contest.

Let's look at the various ways DX signals get from here to there, and how the DXer should modify his operating techniques to take full advantage of each propagation mode.

#### HF Spectrum

Most DX contacts are made via the F2 ionization layer of the ionosphere. The F2 layer is ionized by radiation from the sun and tends to be strongest near the middle of the day. Thus, 10 meters will open up to the east in the morning. As the Earth turns, the band opens farther south, and then it swings around to the west in the late afternoon. The DXer can recognize F2 propagation because It is so widespread, with signals from a large part of the world coming in all at once. This propagation mode is quite steady, building rather slowly and fading gradually. Normal DXing techniques will be successful: Aim your beam at the station and make your call.

Ten meters is not always "open" via F2 propagation. So some DXers will gulckly tune across the band with the beam aimed east, hear nothing, and drop to 15 meters. However, even when the ionization Is not strong enough to provide east-west propagation, it often is strong enough for northsouth contacts. The equatorial region receives more solar radiation than latitudes farther north and often gets enough radiation to open the 10-meter band. Instead of the normal sequence of the band opening up in the east and swinging around to the west, around midday or a little later the band opens up just to the south.

WA1KID used to take advantage of this phenomenon during contests with a 4-element 10-meter beam fixed south. He could switch quickly to that antenna to watch for the trans-equatorial openings and nab the CEs, LUs, and other South Americans. The only trick to working DX via trans-equatorial propagation is to know when and where to look; if your beam is aimed east, for example, you might never hear the South Americans.

This same lonization over the equatorial regions provides one of the more Interesting propagation modes on 10 meters: back scatter. Strong signals aimed south can reflect off the ionization layer over the equator and bounce down to earth, and some small portion of the signal then bounces back along the same path. Not much of a signal gets through, to be sure, since most of the energy is lost or absorbed in the multiple bounces, but directional signals will be scattered enough by the ground at the other end of the hop to send some energy back north.

This means that it is possible to work other stations north of the equator by pointing your beam almost due south! Backscatter signals are very weak, so both stations must point their beams toward the Ionization to the south. If you hear a European signal while your beam is aimed south but the signal fades as you swing your beam up to the northeast, you are probably receiving back- or side-scatter signals. You can recognize these signals because they are weak and peak to the south, no matter in what direction the station is located.

If you hear a scatter signal, resist the temptation to swing your beam according to the beam-heading chart; the signal will disappear. (If it gets louder, you're not hearing a scatter signal!) Instead, swing your beam across the south, listening for the loudest direction, the direction of the most intense lonization, and, therefore, the most scatter. Note that both stations must be beaming south. If the DX station hears your signal and swings his beam up to the west to work you, the contact is lost.

Explaining this under the weak signal strengths of scatter contacts can be frustrating. I remember spending 20 minutes once trying to convince a station that we could make contact only If *both* of us pointed our beams south and not at each other! Whenever this W4 heard my call from New England, he would swing his beam north and lose it.

Side scatter is very similar to back scatter. The radio waves reflect off the side of the ionization region, not the underside. Again, you swing your 10-meter beam back and forth, listening for the loudest signal without regard to the direction of the other station. If you can convince the DX station to do the same thing, you can have a satisfying DX contact.

#### **VHF Spectrum**

Since the 10-meter band is near the VHF region it exhibits some of the exciting propagation modes of VHF bands, including meteor scatter and E-skip. These shortrange propagation modes don't often provide much DX, but it helps to learn how to recognize and operate under each mode.

Meteor scatter is radio propagation off the ionized trails left after a meteor rips through our upper atmosphere. Since the Ten-Meter Contest coincides with a major meteor shower, you might well hear such signals then. Meteor-scatter signals last only a few seconds because the ionization region quickly dissipates. Your contact must be very short; giving your call three times probably will use up the entire opening! Listen for randomly-occuring, quite loud signals which appear and disappear very quickly. If you start a contact on one meteor burst, you may well be able to complete the contact on another burst a minute of two later if you stay on the same frequency and beam heading. Don't expect to exchange much more than a signal report. however, as meteor-scatter QSOs are extremely short.

E-skip enlivens the 10-meter band quite often. The E ionization layer is much lower than the F layer, and the maximum communication distance on a single hop is about 1200 miles, compared to twice that with F2 propagation. But multiple-hop E-skip can provide some DX contacts, thus injecting some life into a "dead" band.

Because the ionization regions in the E layer are much smaller than those in the F layer, the E-skip propagation Is much more restricted in area. You might hear only one or two states or countries at a time, for example. E-skip signals can be very loud as well as very directional, but often you can work stations around the fringes. Say you work a few G stations but don't hear anything else. Try a call for El, GM, GD, etc. People are always listening, and a direct call can pull them out of the woodwork. E-skip propagation is notoriously fickle, appearing and disappearing rapidly. Don't be surprised if your contact fades away in midsentence.

#### **QSL Card Errors**

However your signal gets from here to there, you will probably want a QSL card to confirm the QSO. And you had better fill your card out properly if you expect a return QSL. Almost 25% of all QSLs I have recelved are not filled out properly, yet there are only a half-dozen pleces of information that need to be entered. And any QSL which is Improperly filled out can delay the return QSL or even end up in the circular file! Let's look at the common mistakes and how to avoid them.

The callsign. A surprising number of OSLs arrive without the DX station's call in the appropriate place. If the callsign is anywhere but in the "confirming QSO with" or "radio station" box, the QSL is invalid for awards. Don't confuse the QSL manger's call with that of the DX station.

The date. Almost every country in the world except the United States uses the sequence day/month/year for the date. 12/2/82 is February 12, not December 2. To remove all ambiguity from the date, use Roman numerals for the month, or English ab breviations: 12/182 or 12 Feb. 82. Make sure you changed the date at 2400 UTC, which occurs in the middle of the evening before. local US time. I can't tell you how many cards arrive with the date one day off.

The time. There is no excuse for using anything but UTC on DX QSLs. Local time is for local QSOs only. And if you try to convert your local-time log to UTC for the QSL card, sooner or later you will make a mistake. Keep your log in UTC and keep a UTC clock in the shack. And keep yourclock accurately set to WWV. A DX station or DXpedition operating "contest style" might fill a 50-entry log page in less than 10 minutes. If the time on your QSL is off by more than 5 minutes, the QSLer might have to search through several pages of logs for your contact.

Frequency. Be careful not to put the band in this box—"Frequency 20." for example. If you change bands often (during a contest, for example), watch your log. It is very easy to change bands to work a station and forget to log the band change. Then the card has the wrong band. I always prefer to receive a card with the *exact* frequency, such as, 14205. Since I log my exact transmitting frequency, this can help to find a QSO with the wrong date or time.

Mode. If your QSL has this box labeled "2X," Just write in the mode. If the box is labeled "mode," write "2X CW" or "2X SSB."

RST. Honest signal reports in DX are as rare as Albanlan contacts. I always prefer honest reports, but usually get 59 even if the other station can barely hear me.

QSL. Always ask for the QSL if you want it. I get thousands of cards which I may assume are requests for my card, but nowhere does the station specifically request my card. If things get a little behind, I may assume these cards are answers to cards I sent, and I don't answer them. And If you need a card for a particular reason, say so: "Need 3 more cards for my DXCC, please QSL." or "Please QSL for 5BDXCC."

Other things to remember: If you work a DX station during a contest with consecutive numbers as part of the exchange, write the other station's QSO number on the card: "your number 1024." Don't put your own number on the card, as the DX station could care less. His consecutive number will locate your contact quickly in a long log.

Speaking of contests, be sure to mention that the contact was made during a contest, if it was. Many stations keep separate logs for contest and non-contest operations because of the special logs that contests require. So include "CQ WW SSB contest," as appropriate.

Always send a card for each QSO. Although It is tempting to put all your contest QSOs with a single DX station on one card, It often will slow up your response. The DX station might QSL one band at a time or, as in the case of major DXpeditions, have separate managers for each band. Splurge, and send separate cards.

Finally, write legibly and accurately. Numerous QSLs have the Information so badly written that it is almost Impossible to read. Or the information is mis-copied from the log. These QSLs end up in the "do tomorrow" file or the circular one. And I still have cards from five years ago in my "do tomorrow" file...

And now a special treat for you loyal readers of this DX column. Send me your OSL card by the end of the year and I'll put them all in a hat and draw out three cards. The lucky winners will receive: a 1983 DX Callbook, a one-year subscription to The DX Bulletin, the most prestigious of the DX bulletins, or a one-year subscription to the W6GO QSL List, a list of more than 5000 QSL managers which is updated every two weeks (more about this prize next month)!

So send in your cards to the address at the head of this column, right away. No cost, no obligation; just mail me your QSL card and I'll notify the lucky winners Immediately. Include a slide or black-and-white photo of your shack, and I'll use the best shots. Thanks for being such devoted readers of this column.



Do you need help in getting your Atari computer on RTTY or ASCII? Drop me a line, and I'll be more than happy to get you started.

> Bob Holsti K7ZJD/KH2 PO Box 4426 AAFB BR Yigo, Guam 96912

I would appreciate a copy of a schematic for an RCA #WA 504-A sine/square wave audio generator. I will be glad to pay postage and the cost of copying.

> A. B. Wells WA5COH PO Box 50 Tunica LA 70782

## SATELLITES

#### Ariane Takes a Dive

The amateur radio space program suffered another setback on September 10. On that date, a European Space Agency (ESA) Arlane rocket fell into the Atlantic Ocean instead of achieving orbit as planned. It was the second failure in five launches for Ariane, the vehicle which was scheduled to carry the Phase IIIB amateur satellite aloft in early 1983.

This time, the Arlane carried no amateur birds, but two multi-million-dollar communications satellites on board were lost. Apparently, the rocket dove into the ocean when a thirdstage fuel pump failed. If the problem turns out to be specific to the unit that failed and not a design flaw, the Phase III launch schedule may be only slightly affected and the amateur satellite could still be launched sometime this spring. Amateur satellite enthusiasts can only wait patiently for ESA to work out bugs.

Incidentally, the Arlane failure is a serious blow to ESA, which is in head-to-head competition with NASA and the Space Shuttle in the satellite launching business. With Ariane's success rate running only 60%, some ESA customers are getting edgy and may take another look at what the Shuttle has to offer.

#### MARECS: 0 for 2

One of the satellites lost in the III-fated September launch was MARECS B, the second Maritime European Communications Satellite. What makes the loss particularly devastating is that the first bird in the series, MARECS A, failed in orbit without ever becoming operational. The bottom line is \$250,000,000 spent without a single positive result for MARECS backers. Space flight remains an expensive business.

Thanks to AMSAT Satellite Report. - Jeft DeTray WB8BTH, 73 Staff.

#### Amateur Satellite Reference Orbits

	OSCAR 8	D.C. F.	<b>DC</b> (	<b>DQ Z</b>		
Date	UTC EQ		RS-6 UTC EOX	RS-7	RS-8	Date
====	=======				UTC EQX	Date
Dec 1		7 0127		========		
2				0010 343	0009 342	1
			2 0154 14	0000 343	0006 342	2
3	0050 8		2 0138 11	0150 12	0003 343	3
4	0054 9			0140 11	0000 344	4
	0059 9			0130 10	0157 15	5 6 7
6	0103 9			0121 9	0154 16	6
7	0108 9		3 0037 2		Ø152 17	7
8	0112 9		0021 0	<b>91</b> 91 8	Ø149 17	8
9	0116 9		0006 358	0052 7	0146 18	9
10	0121 9			0042 6	Ø <b>143</b> 19	10
11	0125 9			9032 5	0140 20	11
12	0130 9			0023 4	0137 21	12
13	0134 10			0013 3	0135 22	13
14	0138 10		6 8848 16	0004 2	0132 23	14
15	0000 7			Ø153 32	0129 23	15
16	0004 7		5 <b>Ø917 1</b> 2	0143 31	Ø126 24	16
17	0009 7	8 9992 6	6002 9	0134 30	8123 25	17
18	8013 8	0 0156 37	0145 37	0124 29	0120 26	18
19	0017 8	1 0150 37	0129 35	0114 28	0118 27	19
20	0022 8			0105 27	0115 28	20
21	0026 8			0055 27	0112 28	21
22	0031 8			0046 26	0109 29	22
23	0035 8			0036 25	0106 30	23
24	0039 8	6 9124 38		0026 24	0104 31	24
25	3044 8			0017 23	0101 32	25
26	3048 8	8 0113 39	0140 48	0007 22	0058 33	26
27	0053 8			0156 51	0055 33	27
28	0057 9			0147 51	0052 34	28
29	0102 9			0137 50	8849 35	29
30	0106 9			0128 49	0047 36	30
31	0110 9			0118 48	0044 37	31
Jan						
1	Ø115 9	4 0041 40	0008 35	9108 47	0041 38	1
2	0119 9			0059 46	0038 38	2
3	0124 9			0049 46	0035 39	3
4	0128 9			0039 45	0032 40	4
	0132 9			0030 44	8838 41	r,
5	0137 10			0020 43	0027 42	5
7	0141 10			0010 42	0024 43	7
8	0002 7			0001 41	0024 43	8
9	0007 7			0150 70	0018 44	9
10	0011 7			0130 70	0016 45	10
11	8016 7			0131 69	0013 46	11
11	0020 8			9121 68	0010 47	12
13	0025 8			0112 67	0007 48	13
14	0029 8:	2 0131 74	9945 65	0102 66	0004 49	14




Wanted: a relay for the Heathkit HW-12 monoband transcelver. Please send price info on how I can get one. Thank you very much.

> Rick Dill WA9EDH 3007 S. 44th St. Lincoln NE 68506

I'm looking for a 40m QRP SSB transceiver for mobile use. If anyone has a 40m QRP rig or info on converting a CB to 40, I would appreciate it if they would contact me.
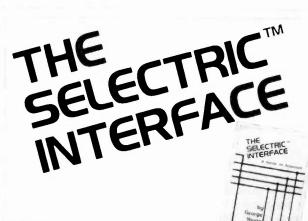
> Roosevelt Hamilton WD4PSW 1112 Lownde Ave. Pensacola FL 32507



### Daisy wheel quality without daisy wheel expense.

You need the quality print that a daisy wheel printer provides but the thought of buying one makes your wallet wilt. Selectric<sup>TM</sup> Interface, a step-by-step guide to interfacing an IBM Selectric I/O Writer to your microcomputer, will give you that quality at a fraction of the price. George Young, co-author of *Microcomputing* magazine's popular "Kilobaud Klassroom" series, offers a low-cost alternative to buying a daisy wheel printer. Selectric Interface includes:

• step-by-step instructions

- tips on purchasing a used Selectric
- information on various Selectric models, including the 2740, 2980, and Dura 1041
- driver software for Z80, 8080, and 6502 chips
- tips on interfacing techniques

With *Selectric Interface* and some background in electronics, you can have a high-quality, low-cost, letter-quality printer. Petals not included.

Credit card orders call TOLL-FREE 1-800-258-5473. Or mail your order with payment plus \$1.50 shipping and handling to: Wayne Green Inc. Attn: Retail Book Sales, Peterborough, NH 03458. Dealer inquiries invited.

ISBN 0-88006-051-4 128 pages \$12.97

□ Yes, I want Selectric Interface (BK7388). Enclosed is \$12.97 per

copy plus \$1.50 for shippi	ng and handling.	
MASTER	□ VISA	
Card #	Expires	
Signature		
Name		
Address		
City		
State and Zip		
All orders shipped UPS if complete	e street address is given.	SS12

## W2NSD/1 NEVER SAY DIE editorial by Wayne Green

#### from page 8

But this pursuit is a totally selfish one. There are no benefits to the hobby...to society. The world is not inched ahead one whit by these chaps. The League has let loose a monster on the world of amateur radio with their Honor Roll.

My own solution to this problem was to work hard and have fun as I worked toward 300 countries. Once I got to that level, I stopped counting. Today, when I hear a new one, I'll take a few minutes to get him in the log...preferring to talk with him if at all possible. If things are too frantic, I have better uses of my time...a lot better. I haven't the vaguest idea of how many countries I've worked and I don't intend to try to count 'em up. Perhaps, if the League would let newcomers to DXing get credit for countries worked up to 300...with no further listings after that...we might be able to put a stop to this thing.

Remember that working DX and getting up on the Honor Roll requires mainly that one be able to spend enormous amounts of time at it. This is not time spent In learning anything or in developing a skill of use to the world. Once you have a decent station, you can make a contact anywhere in the world, so it's just a question of sticking around, being there at the right time, and then bludgeoning your way through.

One of the supposed purposes of amateur radio is to help develop world friendships. Show me a hint that DX pileups and the badgering of ops in rare countries for instant contacts and a QSL generates anything but a disdain. Much of this is aimed at Americans, who are by far the worst in this regard, though at times I find the Germans pushing us hard for bad manners awards. Oddly enough, those hundreds of thousands of no-code Japanese hams are about the best-mannered operators in the whole world...and they have almost one million licensed amateurs today!

Those no-code hams, trained by their local ham clubs, often make us look like the CBers. They put most Americans to shame when it comes to real operating skills. And I don't think we can excuse our behavior on the air by explaining that learning the code made us crazy. I know that a lot of hams use the Morse Code as an excuse for being such terrible operators, but I don't believe that something that simple could explain what happens when a PY0 comes on the air.

And I don't think we can shrug our shoulders and put the whole thing down to basic cultural differences. The Japanese may bow when they meet, but they knock you around in the subways and in stores just as hard as you get bumped in America. No, the difference is, I believe, in

#### UNCLE WAYNE WANTS YOU!

When was the last time you wrote an article for 73? Never??!! Then it is time you got started.

We are going to make 1983 the best year ever for fun, exciting articles in 73. To do this, we'll need articles on many different topics. That's where you come in. Even if you've never written an article for us before, we want to hear from you.

#### What Do I Write About?

Ham radio is really about two dozen hobbies all rolled into one, so there is no shortage of interesting topics. Here are just a few: • Antennas. Almost every ham experiments with antennas. Whether you've built a 2-meter yagl, an 80-meter quad, a helix for Phase III, or a multiband dipole, other hams can't walt to try your design. Tell 'em all about it in 73.

DX. Been on a DXpedition? We all enjoy reading about exotic people and places. Here's a chance to recount your adventure.
Special Events. Hams get involved in some wacky and wonderful activities. Like Field Day from a floating raft or operating from hot air balloons. If it's worth a story, let us here from you.

Reviews. New ham gear is released every week, so how does anyone know what to buy? You can help by writing reviews of your new equipment for other hams to read. Check with us first though; we don't want you to duplicate the efforts of someone else.
Accessories and Gadgets. Home-brewing small projects is an amateur radio tradition. If your latest preamp, digital clock, or electronic sock warmer is a good performer, the rest of us want to hear about it.

Major Projects. The design and construction of a transmitter, receiver, or power amplifier is a task requiring knowledge and skill.
 We want to publish the details so that other hams can enjoy the satisfaction of building a big project.

• Test Gear. Hams love to save money. That's why they'll be interested in your homemade test equipment. We'll have room for lots of transistor checkers, capacitance meters, logic probes, diode testers, and the like during 1983.

Satellites. Whether it's OSCAR, RS, or TVRO, hams want to know more about building their own satellite gear. Downconverters, antennas—you name it and our fellow amateurs are eager for plans and information.

Digital Communications. Microcomputers make RTTY neat and simple, but we can do so much more. If you are experimenting
with higher baud rates, packet radio, new TU designs, coherent CW, or any of a host of other possibilities, you can tell the amateur
world about it by writing articles for 73.

Computers. Microcomputers are fast becoming a fixture in many shacks. What are you doing with yours?

Those are just a few of the many ideas for articles. You'll think of more if you work at it.

#### What's In It for Me?

Cash. Unlike some ham magazines, 73 pays for the articles we publish. It may not buy you a new tower, but it might get you that new beam.

Prestige: Just imagine how impressed your friends and relatives (not to mention your boss) will be when they see your article published in an international magazine!

Enthusiasm. When you write for 73, you help to generate the excitement that makes ham radio so much fun. Both simple and complex articles find an eager audience.

#### What to Do Next

For a full description of the nuts and bolts of article preparation, send for the 73 Author's Guide. If you can't walt that long, double space your manuscript, leave generous margins, carefully organize your diagrams and photos, and send the whole package to us. Our address is: 73, Peterborough NH 03458. Now, don't just sit there—start writing!

basic ham training...in their club-trained hams. That's where they get across the concept of pride in being a ham and the responsibility of being a good operator.

Or, as old and good friend Bob Sullivan used to say, "I may not be wrong, but I'm not far from it."

#### SMALL HAMFEST CATASTROPHE

Some years ago, a disgruntled ham almost got the New England ARRL Convention closed down. The problem hinged around the breaking of federal laws having to do with the advertising of lotteries through the mail. You can't, yet most hamfests and conventions continue to do this, ignoring the federal laws they are breaking.

Please note that it is presently against the law for any hamfest or convention to send a brochure through the mail which promises prize drawings if there is a charge for attendance... and there always is. Further, it is illegal for any magazine or other publication which uses the mails to mention that prizes will be given where there is a charge for attendance.

T.

If you want to give prizes, fine but it is illegal for you to mention that in anything which is going to be sent through the mails. You cannot send flyers or posters with this information on them through the mail. Got it?

No one has ever determined just how much prizes build up attendance at hamfests. As far as I know, every hamfest gives prizes, so no one *could* yet have tested the concept. With the veil of secrecy on prizes being lowered by the post office (we have heard from them in no uncertain terms), it may get a whole lot more difficult to get cooperation from manufacturers in the way of donated equipment.

Before the "incentive licensing" debacle of '63, it was much easier to get prizes. The ham industry was growing rapidly, meeting the needs for the thennew sideband equipment, so they were happy to donate nice prizes for our hamfests. Today, with only a handful of American firms left, most of the hamfest prizes have had to be bought, so the munificence has not been awesome. If hamfest committees decide to spend less on prizes, this would leave them



FREE! FREE! FREE! FREE! FREE! FREE! FREE SEND FOR OUR NEW FRI 1982/1983 FREE PARTS CATALOG THOUSANDS OF FREE! F SURPLUS ELECTRONIC PARTS, SUPPLIES AND DEVICES. FREE ALL ELECTRONICS CORP FREE 905 S. Vermont Ave. P.O. Box 20406 Los Angeles, Cal. 90006 FREE REEL

FREE! FREE! FREE! FREE! FREE

BOARD		POWER
SINGLE BOARD COMPUTER	µщľ	AND MORE!
<ul> <li>202 TYPE MODEM Be audio xfmrs. TTL digita</li> <li>8080A CPU BOARD</li> </ul>	al IIO, 5 x 5.5" With sockets fi	ud, separate 600 oh or 4ea 2708s. Also
sockets; 8251 Prog (USART), 8253 Tripi System Controller/3-st support ICs, xtal, clock	ie Programmable tate Bus Driver, 25 < IC, 7.5 x 10"	Interval Timer, 822 6 bytes RAM, 29 oth
<ul> <li>ENCLOSED POWER</li> <li>(a) 2.5A, +12V (a) 350</li> <li>voltages for display 3</li> </ul>	0ma, -5V (r 250m	
DOCUMENTATION P nically Oriented User N		es schematics & Tec
<ul> <li>MISC.: 20 Key Decimicent Display, Mag St MORE.</li> </ul>	al & Function Keyb	
Units are removed from High quality modern con- off-line test before shipme buy a lot of turkeys before	struction throughou enLLarge quantity	ut. Each is given a fi in stock. You'd have
PRICE, SURFACE UPS		
ELECTROVALUE INDU	STRIAL INC.	Phone proers ar questions welcom



316-947-2269


439

73 Magazine does not keep subscription records on the premises, therefore calling us only adds time and doesn't solve the problem.

Please send a description of the problem and your most recent address label to:

73 Magazine Subscription Dept. PO Box 931 Farmingdale, NY 11737

Thank you and enjoy your subscription

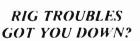

YOU COULD SHIP YOUR RIG TO THE FACTORY FOR REPAIR.
YOU COULD SHIP IT TO RQ SER-VICE CENTER FOR REPAIR.
BUT YOU STAND A GOOD CHANCE OF FIXING IT YOUR-SELF WITH HELP FROM YOUR OWN COPY OF "OWNER REPAIR OF RADIO EQUIPMENT"
THIS BOOK WILL BE SHIPPED POSTPAID FROM K6RQ FOR \$8.95

> RQ SERVICE CENTER 14910 LG Blvd. Los Gatos, CA 95030



50 ohms • Operates on 12 Vdc @ 1/2 Amp • Avallable for immediate delivery • \$349.95 plus shlpping • Add-on Accessories available to extend freq, range, add Infinite resolution, voice and sub-audible tones, AM, precision 120 dB calibrated attenuator • Call for details • Dealers wanted worldwide.

> VANGUARD LABS ~311 196-23 Jamaica Ave., Hollis, NY 11423 Phone: (212) 468-2720





### Microwave Field Disturbance Motion Detector Kit

- Range 100' unobstructed
- · Safe low power 10mW output
- Detects motion from 0.1 to 20 MPH

Unlike ultrasonic motion detectors, the Microwave Field Disturbance Motion Detector, can see thru nonmetallic walls. Output is N.O. or N.C. relay contacts which can operate alarms, lights, or electric doors. Output can be programmed from seconds to hours and will reset automatically.

Kit contains: 10.525 GHz transceiver module, 10 db diecast horn antenna, all components, PC board, and instructions. Requires 10-14 VDC, 70mA standby, 110mA activated.

Model MT2 \$89.95 PPD in U.S. COD add \$2. N.J. residents add 5% sales tax.

MicroTek (201) 548-4321 35 West Francis St., 196 Iselin, New Jersey 08830 with some cash to invest in better speakers.

It's been my observation that hams will drive for hundreds of miles to hear someone interesting talk about their favorite subject. I don't know of anyone crazy enough to drive a couple hundred miles for 1/10,000th chance at an HT. You know, you can help. Hamfest committees really don't know who to ask to come talk at their shows. If you'd take the time to write a short review of any interesting talks you've attended at hamfests, this might get the word around.

The fact is that we do have a number of hams who get to fascinating DX spots and go through all kinds of remarkable hell in the process. Some of these chaps are most interesting, if we could only hear about it. Please take the time to pass the word to us here at 73 ... and we'll get your material into the letters column as guidance to other hamfests.

The opposite side of the coin is that a few of our best known DXers are turkeys. It is most incredible how someone can go through some of the adventures these chaps have and be able to make it sound so incredibly dull to hear about. I once fell asleep at the dinner table trying to get anything of even the slightest interest out of two very wellknown DXpeditioners.

There are plenty of interesting people around our hobby. Why not get one of our well-known ham publishers to tell about how he got his ham ticket in the '60s without knowing diddly squat about either the theory or the code? I'll bet we'd love to hear about his trip to northern Maine to get a "Conditional" license and his later trials with the FCC when they found out.

Then there is Jean Shepard K2ORS, with two successful PBS films to his credit and a third in production. Jean is by far the best humorist we have in the hobby and our hamfests should grab him when they can. I understand his latest film, "The Great American Fourth of July...and Other Disasters," is up for an award. If you do get him to speak, be sure to tape it and send me a copy. Shep isn't inexpensive to get, but he will pull 'em in...and be worth every dollar you spend.

No one really interesting is prize 174 73 Magazine • December, 1982

going to be cheap to get. That's the law of supply and demand. And, as Shep found out long ago, few people really appreciate anything they get for nothing.

My own experience has been that when I speak for free I often find a lack of support by the hamfest committee which results in two or three dozen in attendance. If I cost \$1,000 plus all travel expenses (first class), you can bet they will be doing everything they can to get people to listen to me. Then I find myself facing two to three thousand in the audience instead of dozens. Between my alreadymade show commitments and trying to run my steadilygrowing publishing firm while keeping up with two fastgrowing industries, I'm not fishing for more work. If I do have extra time, it goes for writing, consulting, and even a touch of hamming. Most hamfests are on weekends, which is prime writing time.

In addition to getting interesting speakers for hamfests, with the no-longer-useful prize money, committees might look into putting on some really good demonstrations of new ham communications modes. I suspect that many amateurs would love to see some good slow-scan demonstrations. They'd also like to see fast-scan television. Then there is a growing interest in packet communications. But, for heaven's sake, watch out for some of the super turkey "experts" who flaunt their doctor titles. Several of these birds are crashing bores. Hamfest committees might, if they don't have personal recommendations on the "experts," ask for an audio tape preview and judge it as they might a radio audition.

If you have some hamfest committee members who are enthusiastic about the Morse code, why not try to inspire hams to accept code as a fun activity instead of merely something the government forces them to learn ... and run codecopying contests, with certificates for the winners to display in their shacks. You can help bring some pride to knowing the code, something sadly lacking today. How can one have pride in something which is mandated by the government? Some of the prize money can go for awards for code skills. There's no lottery aspect to *that*.

You might get some of your more fanatic DXers to bring in their rare cards for a display...and for a talk on how to get the darned things. That is an art in itself. A big board for attendees to pin up their cards, with a QSL contest (also not a lottery, obviously), won't hurt.

I realize that bribery and greed are time-honored movers of people, but let's try to cope with the post office laws and find alternate ways of getting hams to come to hamfests.

#### THE GREAT AMERICAN HAM CLUB...DISASTER

When I see the Japanese ham magazine each month, with a whole section devoted to club activities...often with 70 or more pages of news about the clubs and pictures of their activities...I think of how little our clubs are doing...and reporting. I don't think we could generate that much news in a year, much less every month.

Even the best of our ham clubs seem to have their ups and downs. One thing that might help would be an updated series of articles on how to run a ham club. I did run such a series nearly twenty years ago and it was very well received. It's about time for an updated series, eh?

Running a ham club is show business, which many of us seem to forget. Many club presidents gather weak people around them to help make the club go. They do little to organize exciting meetings and often let business intrude on the fun ... only to find that in a few months they have little left of the club.

I'd like to see some articles on how to make ham clubs succeed. I believe that the real strength of amateur radio lies in the strength of the clubs, not in a small group of professionals who are, for the most part, working for their own benefit first and ours second. How about some pictures of club groups and reports on club activities?

With amateur radio being a keystone, to my way of thinking, as far as providing our country with emergency communications, we're talking about club organization, not just individuals. Clubs can help get amateur radio set up so that it will be able to keep going after any kind of disaster. This means cooperative efforts to have both personal and mobile portable equipment, emergency repeaters, automated relaying, lowband interlinks, and—above all—experience. The duty is there, we already have the technology, and the work will be both fun and of help to tie us together, strengthening our clubs and our own value to our communities and country.

Then there is the responsibility of clubs to help amateur radio grow. This means devising schemes to interest teenagers in the hobby through talks at high schools, demonstrations at shopping malls, service for local groups, and participation in things like the March of Dimes. It means making sure that club activities are properly exploited with the local media. When there is a Field Day exercise, the local newspapers and television stations should get the word and be offered cooperation on the story.

1

Just getting the interest of teenagers isn't enough. Clubs should try to work with school officials to see that there is a radio club in the school which meets at least weekly. Schools have a serious problem about this which clubs can help solve. Any school activity has to have an adult advisor on hand. Since few schools have the budget to pay a teacher for this after-school work, the result has been a serious cutting down of after-school clubs. By providing the needed adult advisor, the local ham club could encourage the development of the school radio club.

Then there is the growing need for license classes to be put on by clubs. One of the really sad results of the Bash cheatbook approach to getting a ham ticket has been the lack of ham club members with even the small technical background it takes to teach the rudiments of theory required for the Novice exam. In some clubs, it is a case of those with scant information trying to teach newcomers, spreading confusion.

All of these problems have been solved by many clubs, so I'd like to see some letters and articles on these subjects for possible publication.



REMOTE 40 CHANNEL C.B. Remotes have a metal frame Speaker, plastic case, and control mic not included Sold as is \$14.95 ea

C.B. BARGAIN C.B. boards missing parts or damaged Can be used for spare parts. Buy several<sup>11</sup>

\$3.50 ea Order information Please add \$4.00 for S/H via UFS COD's accepted for orders totaling \$50.00 or more. Florida residents add 4% sales tax. Minimum order \$15.00 Foreign orders US funds only add 20% for S/H MASTER CARD and VISA accepted

Surplus Electronics Corp. 7294 NW 54th St. ▶ 69 Miaml FL 33166







converted C.B.'s in stock ANEXTER MARK ANTENNAS You saw them at Davton. Now in stock the HW-3 three band helewhip that covers 10-15-20 meters with no traps FREE CATALOG-Write or call today INDEPENDENT CRYSTAL SUPPLY COMPANY 141 Rt. 6A, Box 183 Sandwich, Ma. 02563-0183 (617) 888-4302 178

- See List of Advertisers on page 130

#### FACIT 4555 SERIAL PAGE PRINTER

The Facit 4555 alphanumerical serial printer is complete. Equipped with RS232C Interface, printing mechanism, control electronics, drive electronics, power supply and character generator. The adaptation electronics can be modified in four versions: Bit-parallel data transfer, CCITT (EIA, RS232C) for bit-serial data transfer and the current loop (TTY) interface also for bit serial data transfer. The Facit 4555 prints on ordinary paper and is adjustable for different paper widths and formats, 9.5" paper width with 66 lines per page or DIN A4 with 70 lines per page.

	SPECIF	ICATIONS	
Print speed Printing mode Max. # of ch/line Matrix Char. Size Height Char. Size Width	up to 60ch.s. Incremental. 80 alt. 132. 7 X 5 dot matrix. 2.7mm/1/8" 1.3mm/0.05" 132ch/line 2.1mm/0.083" 80ch/line	Char. spacing Char. Code Char. Set Feed mechanism	2.54mm/1/10" 80ch/line 1.55mm/0.06" 132ch/line ECMA-6 7-bit coded char. set 63 Char. various national versions. Sprocket feed.

THESE UNITS WERE PULLED OUT OF SERVICE IN GOOD WORKING CONDITION. WE CHECK EACH UNIT ON A RADIO SHACK TRS-80 COLOR COMPUTER.



\$129.99 PRINTER ONLY

Printer with linecord, box of paper, inter-connect cable for TRS-80 COLOR COMPUTER. \$149.99

GENEVA CALCULATOR WATCH

Featured in Black Plastic

This attractive watch has the following modes: Normal Time Setting, Calendar Setting, Daily Alarm Time Setting, Weekly Alarm Time Setting, Chronograph, Calculator.

\$24.99

or Featured in Stainless Steel

\$29,99

27L32/25L32 \$10.00 each

SILICON DIOL	DES				FEED THRU SOLDER RF CAPACTORS
MR 7 5 1	100vdc	6Amps	10/\$5.00	100/\$38.00	470pf +-20%
MR 510	1000vdc	3Amps	10/\$3.75	100/\$24.00	
HEP 170	1000vdc	2Amps	20/\$2.00	100/\$15.00	5/\$1.00 or 100/\$15.00 or
1N3209	100vdc	15Amps	\$2.00	10/ \$15.00	1000/\$100.00
BYX21/200	200vdc	25Amps	\$2.00	10/ \$15.00	
1N2138A	600vdc	60Amps	\$5.00	10/ \$40.00	1000pf/.001uf +-10%
DS85-04C	400vdc	80Amps	\$10.00	10/ \$80.00	
1N3269	600vdc	160Amps	\$15.00	10/\$120.00	4/\$1.00 or 100/\$20.00 or
275Z41	300vdc	250Amps	\$20.00	10/\$175.00	1000/\$150.00
7-5754	300vdc	400Amps	\$30.00	10/\$250.00	
RCD-15	1 5KVDC	20ma.	\$3.00	10/ \$20.00	5. 30.010
SMFR20K	20KVDC	20ma.	\$4.00	10/ \$30.00	E PROMS
1N4148	signal		30/\$1.00	100/ \$3.00	2708 1024x1 \$2.00 each
FAIRCHILD 4	116 16K DYNA	MIC RAMS 20	Ons. Part #	16K75	2716 2048x8 \$4.00 each

25 For \$25.00 or 100 For \$90.00 or 1000 For \$750.00

#### HEWLETT PACKARD MICROWAVE DIODES

1N 57 1 1	(5082-2800)	Schottky	Barrier	Diodes		\$1.00 0	or 10	for	\$ 8.50
1N 57 1 2	(5082-2810)	11				\$1.50 0	or 10	) for	\$10.00
1N6263	(HSCH-1001)	**				\$ .75 0	or 10	for	\$ 5.00
5082-2835		11	11			\$1.50 0	or 10	) for	\$10.00
5082-2805	Quad Matched	21	94	" pe	r set	\$5.00 0	or 10	) for	\$40.00

**Toll Free Number** 800-528-0180 (For orders only) PRICES SUBJECT TO CHANGE WITHOUT NOTICE

### MHz electronics

	"MIXERS"	
WATKINS JOHNSON WJ-M6 Double Ba	alanced Mixer	
LO and RF 0.2 to 300MHz IF DC to 300MHz \$21.00		
Noise Figure (SSB)	6.5dB Max. 1 to 50MHz 8.5dB Max2 to 300M	
Conversion Compression	same as above 8.5dB Max. 50 to 300M	1H z
	.3dB Тур.	
NEC (NIPPON ELECTRIC CO. LTD. N		
NF Min         F=2GHz         dB         2.4         Typ.           F=3GHz         dB         3.4         Typ.           F=4GHz         dB         4.3         Typ.	MAG F=20 F=30 F=40	
Ft Gain Bandwidth Product at Vc Vcbo 25v Vceo 11v V	e=8v, Ic=10ma. GHz 4 Mi ebo 3v Ic 50ma.P	
UNELCO RF Power and Linear Ampl	ifier Capacitors	
These are the famous capacitors manufacturers, and described in	used by all the RF Power the RF Data Book.	and Linear Amplifier
5.1pf 12pf 22pf 6.8pf 13pf 25pf 7pf 14pf 27pf	30pf         43pf         100pf           32pf         51pf         110pf           33pf         60pf         120pf           34pf         80pf         130pf           40pf         82pf         140pf	220pf 11 to 50pcs. \$ .90 ea 470pf 51 up pcs. \$ .80 ea 500pf
Valley Pt. Current ma. Peak Pt. Voltage mv. Projected Peak Pt. Voltage mv. Series Res. Ohms Terminal Cap. pf.	MODEL 1S2199 Ip 9min. 10Typ. 1 Iv 1.2Typ. 1.5max Vp 95Typ. 120max.	. 1.2Typ. 1.5max. 75Typ. 90max. . 630max. 440min. 520Typ. 600max. 2Typ. 3max.
FAIRCHILD / DUMONT Oscilloscope	Probes Model 4290B	
Input Impedance 10 meg., Input ( 10:1, Cable Length 4Ft., Freque These Probes will work on all Te PRICE \$45.00	Capacity 6.5 to 12pf., Div ency Range Over 100MHz.	
MOTOROLA RF DATA BOOK		
Listsall Motorola RF Transistors more.	s / RF Power Amplifiers, Va	aractor Diodes and much much
PRICE \$7.50		
Toll Free Number 800-528-0180 (For orders only)	<b>M</b> 9	Lz electronics
	PRICES	S SUBJECT TO CHANGE WITHOUT NOTICE

î

178	73 Magazine		December	1982
1/0	13 Wayazine	-	December.	1902

-	11.90	
	<b>Toll Free Number</b>	
	800-528-0180	
	(For orders only)	

## 


RF TRAM	SIST	DRS, MIC	ROWA		DES
PART P	RICE	PART	PRICE	PART	PRICE
152199 \$	7.50	2N6083 \$	13.25	CA2612 (TRW)	\$ 25.00
152200	7.50	2N6084	15.00	CA2674 (TRW)	25.00
2N1561	25.00	2N6094 /M9622	11.00	CA2881-1(TRW)	25.00
2N1562	25.00	2N6095 /M9623	12.00	CA4101 (TRW)	25.00
2N2857	1.55	2N6096 /M9624	15.50	CA4201 (TRW)	25.00
2N2857JAN	2.55	2N6097	17.25	CA4600 (TRW)	25.00
2N2876	11.00	2N6136	21.85	CD1889	20.00
2N2947	18.35 15.50	2N6166	40.25 50.00	CD2545	20.00
2N2948 2N2949	3.90	2N6201 2N6459	18.00	CMD 5 1 4AB D 4 9 5 9	20.00 10.00
2N2950	4.60	2N6603	12.00	D4987M	20.00
2N3375	8.00	2N6680	80.00	D5147D	10.00
2N3553	1.57	2SC756A	7.50	D5506	10.00
2N 36 32	13.80	2SC781	2.80	D5827AM	20.00
2N3818	5.00	2SC1018	1.00	DMD6022	30.00
2N3866	1.30	2SC1042	12.00	DMS-2A-250	40.00
2N3924	3.35	2SC1070	2.50	HEP76	4.95
2N 392 7	17.75	2SC1239	2.50	HEPS3002	11.30
2N3950	25.00	2SC1251	12.00	HEPS3003	30.00
2N4072	1.80	2SC1306	2.90	HEPS 3005	10.00
2N4127	21.00	2SC1307	5.50	HEPS3006	19.90
2N4427 2N4428	1.30 1.85	2SC1760 2SC1970	1.50 2.50	HEPS3007	25.00
2N4428 2N4957	3.45	2SC2166	5.50	HEPS3010	11.34
2N4958	2.90	8B1087 (M.A.)	25.00	HTEF2204 H.P. 5082-0112 H.P.	112.00 14.20
2N4959	2.30	A50-12	20.00	5082-0253 H.P.	105.00
2N5090	13.90	A283B	5.00	5082-0320 H.P.	58.00
2N5108	4.00	ALD4200N (AVANTEK)		5082-0386 H.P.	POR
2N5109	1.70	AM123	97.35	5082-0401 H.P.	POR
2N5160	3.45	AM688	100.00	5082-0438 H.P.	POR
2N5177	21.62	BB105B	. 52	5082-1028 H.P.	POR
2N5179	1.00	BD4/4JFBD4 (G.E.)	10.00	5082-2711 H.P.	23.15
2N 5583	4.00	BFQ85	1.50	5082-3080 H.P.	2.00
2N 5589	8.65	BFR90	1.30	5082-3188 H.P.	1.00
2N 5590	10.35	BFR91	1.65	5082-6459 H.P. 5082-8323 H.P.	POR
2N 5 59 1 2N 5635	13.80 10.95	BFW92 BFX89	1.50 1.00	35826E H.P.	POR POR
2N 5635 2N 5637	15.50	BFY90	1.00	35831E H.P.	29.99
2N 5641	9.20	BGY 54	25.00	35853E H.P.	71.50
2N5642	10.95	BGY 55	25.00	35854E H.P.	75.00
2N5643	15.50	BGY74	25.00	HPA0241 H.P.	75.60
2N 564 5	13.80	BGY75	25.00	HXTR3101 H.P.	7.00
2N5646	20.70	BL161	10.00	HXTR3102 H.P.	8.75
2N 5691	18.00	BLX67	11.00	HXTR6101/2N6617	
2N 57 64	27.00	BLY568CF	25.00	HXTR6104 H.P.	68.00
2N 58 36	5.45	BLY87	13.00	HXTR6105 H.P.	31.00
2N 5842	8.00	BLY88	14.00	HXTR6106 H.P.	33.00
2N 5849	20.00	BLY89 BLY90	15.00 20.00	QSCH1995 H.P.	POR
2N5913 2N5922	3.25 10.00	BLY351	10.00	JO2000 TRW JO2001 TRW	10.00 25.00
2N 592 3	25.00	C4005	20.00	J02001 TRW J04045 TRW	25.00
2N5925	23.00	CA402 (TRW)	25.00	K3A	10.00
2N5942	40.00	CA405 (TRW)	25.00	MA450A	10.00
2N5944	9.20	CA612B (TRW)	25.00	MA41487	POR
2N5945	11.50	CA2100 (TRW)	25.00	MA41765	POR
2N 5946	19.00	CA2113 (TRW)	25.00	MA43589	POR
2N6080	9.20	CA2200 (TRW)	25.00	MA43636	POR
2N6081	10.35	CA2213 (TRW)	25.00	MA47044	POR
2N6082	11.50	CA2418 (TRW)	25.00	MA47651	25.50
<b>Coll Free</b>	Number	~		ECT TO CHANGE WITH	
800-528-0		ŐN	l <sup>e</sup> Hze	lectron	cs

0		TUNINE			
C C	aaas,	TUNNEL	עטוע	E3, EIC.	
PART	PRICE	PART	PRICE	PART	PRICE
MA47100	\$ 3.05	MRF 503	\$ 6.00	PT4186B	\$ POR
MA47202	30.80	MRF504	7.00	PT4209	POR
MA47771	POR	MRF 509	5.00	PT4209C	POR
MA47852	POR	MRF511	8.65	PT4566	POR
MA49558	POR	MRF605	20.00	PT4570	POR
MB4021	POR	MRF629	3.47	PT4571	POR
MBD101	1.00	MRF644	23.00	PT4571A	POR
MDO 513 MHW 1171	POR 42.50	MRF816	15.00	PT4577	POR
MHW1182	42.50	MRF823	20.00	PT4590	POR
MHW4171	49.35	MRF901 MRF8004	3.00	PT4612	POR
MHW4172	51.90	MS261F	2.10 POR	PT4628 PT4640	POR POR
MHW 4342	68.75	MT4150 Fair.	POR	PT4642	POR
MLP102	25.00	MT5126 Fair.	POR	PT5632	POR
MM1 500	32.32	MT5481 Fair.	POR	PT5749	POR
MM1550	POR	MT5482 Fair.	POR	PT6612	POR
MM1552	50.00	MT5483 Fair.	POR	PT6626	POR
MM1553	50.00	MT5596 Fair.	POR	PT6709	POR
MM1614	10.00	MT5764 Fair.	POR	PT6720	POR
MM2608	5.00	MT8762 Fair.	POR	PT8510	POR
MM3375A	11.50	MV109	.77	PT8524	POR
MM4429	10.00	MV1401	8.75	PT8609	POR
MM8000	1.15	MV1624	1.42	PT8633	POR
MM8006	2.30	MV1805	15.00	PT8639	POR
MO277L	POR	MV1808	10.00	PT8659	POR
MO283L	POR	MV1817B	10.00	PT8679	POR
MO3757	POR	MV1863B	10.00	PT8708	POR
MP102	POR	MV1864A	10.00	PT8709	POR
MPN 3202	10.00	MV1864B	10.00	PT8727	POR
MPN 3401	. 52	MV1864D	10.00	PT8731	POR
MPN 3412	1.00	MV1868D	10.00	PT8742	POR
MPSU31 MRA2023-1.5 TRW	1.01 42.50	MV2101	.90 .90	PT8787	POR
MRF212/208	16.10	MV 2 1 1 1 MV 2 1 1 5	1.55	PT9790 PT31962	41.70 POR
MRF223	13.25	MV 2201	.53	PT31962 PT31963	POR
MRF224	15.50	MV 2203	. 53	PT31983	POR
MRF237	3.15	MV2209	2.00	PTX6680	POR
MRF238	12.65	MV2215	2.00	RAY-3	24.99
MRF243	25.00	MWA110	7.45	40081	POR
MRF245	34.50	MWA120	7.80	40281	POR
MRF247	34.50	MWA 1 30	8.25	40282	POR
MRF304	43.45	MWA210	7.80	40290	POR
MRF315	23.00	MWA220	8.25	RF110	25.00
MRF420	20.00	MWA230	8.65	SCA3522	POR
MRF421	36.80	MWA310	8.25	SCA3523	POR
MRF422	41.40	MWA320	8.65	SD1065	POR
MRF427	16.10	MWA330	9.50	SS43	POR
MRF428	46.00	NEC 57835	5.30	TP1014	POR
MRF450/A	13.80	ON 382	5.00	TP1028	POR POR
MRF453/A	17.25	PPT515-20-3 PRT8637	POR POR	TRW-3 UTO504 Avantek	70.00
MRF454/A MRF455/A	19.90 16.00	PSCQ2-160	POR	UTO511 Avantek	70.00
MRF4557A MRF458	19.90	PT3190	POR	V15	4.00
MRF463	25.00	PT3194	POR	V 3 3B	4.00
MRF472	1.00	PT3195	POR	V100B	4.00
MRF475	2.90	PT3537	POR	VAB801EC	25.00
MRF477	11.50	PT4166E	POR	VAB804EC	25.00
MRF 502	1.04	PT4176D	POR	VAS21AN20	25.00

### Toll Free Number 800-528-0180 (For orders only)

## MHz electronics

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

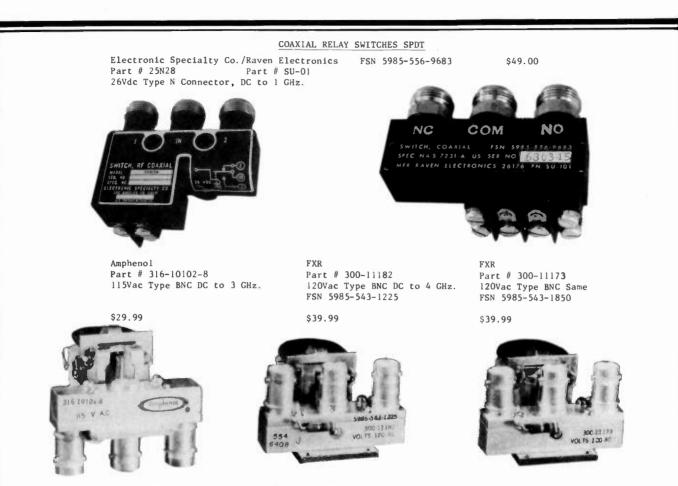

BNC To Banana Plug Coax Cable RG-58 36 inch or BNC to N Coax Cable RG-58 36 inch.

5vdc turn on

\$7.99 or 2 For \$13.99 or 10 For \$50.00

\$8.99 or 2 For \$15.99 or 10 For \$60.00



SOLID STATE RELAYS

P&B	Mo	del	ECT1DB72
PRIC	CE	EAC	\$5.00

RICE EACH \$5.00

Digisig, Inc. Model ECS-215 5vdc turn on PRICE EACH \$7.50

Grigsby/Barton Model GB7400 5vdc turn on PRICE EACH \$7.50



120vac contact at 7amps or 20amps on a  $10^{\prime\prime}x$   $10^{\prime\prime}x$  .124 aluminum. Heatsink with silicon grease.


240 vac contact l4amps or 40amps on a  $10^{\prime\prime}\text{x}$   $10^{\prime\prime}\text{x}$  .124 aluminum. Heatsink with silicon grease.

240vac contact at 15amps or 40amps on a  $10^{\prime\prime}x$   $10^{\prime\prime}x$  .124 aluminum. Heatsink with silicon grease.

NOTE: \*\*\* Items may be substituted with other brands or equivalent model numbers. \*\*\*



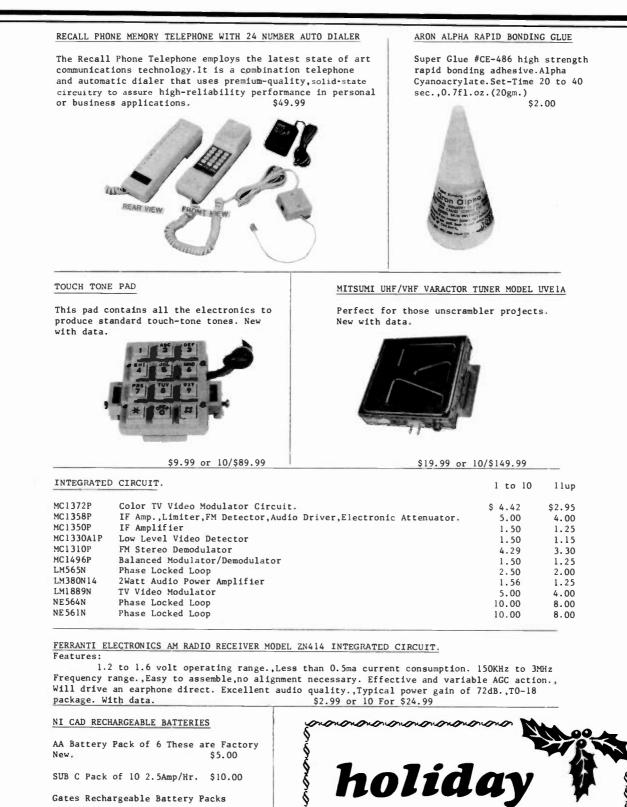Toll Free Number 800-528-0180 (For orders only) PRICES SUBJECT TO CHANGE WITHOUT NOTICE



Gates Rechargeable Battery Packs

12vdc	at	2.5Amp/Hr.	\$11.99
12vdc	at	5Amp/Hr.	\$15.99



MH z electronics



### **"SOCKETS AND CHIMNEYS"**

EIMAC TUBE SOCKETS AND CHIMNEYS

SK110 SK300A SK400		R,J, 4CX10,000D, 4CX15,000A,J 0A,400A,400C,4PR125A,400A,4-5		\$POR \$520.00 260.00	
SK406	Chimney For 4-250A,4			74.00	
SK416	Chimney For 3-400Z	Pp1000+ /p		36.00	
SK500	Socket For 4-1000A/4 Socket For 4CX250B,E			390.00 51.00	
SK600 SK602	Socket For 4CX250B,E			73.00	
SK606		BC, FG, R, 4CX350A, F, FJ		11.00	
SK607	Socket For 4CX600J,J			60.00	
SK610	Socket For 4CX600J,J			60.00	
SK620	Socket For 4CX600J,J			66.00	
SK626 SK630	Chimney For 4CX600J, Socket For 4CX600J,J			10.00 66.00	
SK636B	Chimney For 4CX600J,			34.00	
SK640	Socket For 4CX600J,J			36.00	
SK646	Chimney For 4CX600J,	JA		71.00	
SK700	Socket For 4CX300A,Y			225.00	
SK711A	Socket For 4CX300A,Y			225.00	
SK740	Socket For 4CX300A,Y Socket For 4CX300A,Y			86.00 86.00	
SK770 SK800A	Socket For 4CX1000A,			225.00	
SK806	Chimney For 4CX1000A			40.00	
SK810	Socket For 4CX1000A,			225.00	
SK900	Socket For 4X500A			300.00	
SK906	Chimney For 4X500A			57.00 650.00	
SK1420 SK1490	Socket For 5CX3000A Socket For 4CV8000A			585.00	
	TUBE SOCKETS AND CHIMNEYS				
124-111/:		OB,BC,FG,R, 4CX350A,F,FJ		\$ 10.00	
122-0275		, 4-125A, 250A, 400A, 4-500A,	, 5-500A	(pair)15.00	
124-0113		B BC EC D //CY3EOA E EL		15.00 55.00	
124-116/		B,BC,FG,R, /4CX350A,F,FJ B,BC,FG,R, /4CX350A,F,FJ		55.00	
124-115-	813 Tube Socket	b, be, ro, k, 7 + ex 5 > on fr fro		20.00	
				TUBE CAPS (Plate)	
CHIP CAP	ACITORS			HR1, 4	\$11.00
.8pf			430pf	HR2,3,6&7	
	10pf	100pf*			13.00
lpf	12pf	110pf	470pf	HR5, 8	14.00
1pf 1.1pf	12pf 15pf	110pf 120pf	470pf 510pf		
1pf 1.1pf 1.4pf	12pf 15pf 18pf	110pf	470pf 510pf	HR5, 8 HR9	14.00 17.00
1pf 1.1pf 1.4pf	12pf 15pf	110pf 120pf 130pf	470pf 510pf 560pf	HR5, 8 HR9	14.00 17.00
1pf 1.1pf 1.4pf 1.5pf 1.8pf 2.2pf	12pf 15pf 18pf 20pf 22pf 24pf	110pf 120pf 130pf 150pf 160pf 180pf	470pf 510pf 560pf 620pf 680pf 820pf	HR5, 8 HR9 HR10	14.00 17.00
1pf 1.1pf 1.4pf 1.5pf 1.8pf 2.2pf 2.7pf	12pf 15pf 18pf 20pf 22pf 24pf 27pf	110pf 120pf 130pf 150pf 160pf 180pf 200pf	470pf 510pf 560pf 620pf 680pf 820pf 1000pf/.00	HR5, 8 HR9 HR10 	14.00 17.00
1pf 1.1pf 1.4pf 1.5pf 1.8pf 2.2pf 2.7pf 3.3pf	12pf 15pf 18pf 20pf 22pf 24pf 27pf 33pf	110pf 120pf 130pf 150pf 160pf 180pf 200pf 220pf*	470pf 510pf 560pf 620pf 680pf 820pf 1000pf/.00 1800pf/.00	HR5, 8 HR9 HR10 Luf* 18uf	14.00 17.00
1pf 1.1pf 1.4pf 1.5pf 1.8pf 2.2pf 2.7pf 3.3pf 3.6pf	12pf 15pf 18pf 20pf 22pf 24pf 27pf 33pf 39pf	110pf 120pf 130pf 150pf 160pf 180pf 200pf 220pf* 240pf	470pf 510pf 560pf 620pf 820pf 1000pf/.00 1800pf/.00 2700pf/.00	HR5, 8 HR9 HR10 Luf* 18uf 27uf	14.00 17.00
1pf 1.1pf 1.4pf 1.5pf 1.8pf 2.2pf 2.7pf 3.3pf	12pf 15pf 18pf 20pf 22pf 24pf 27pf 33pf	110pf 120pf 130pf 150pf 160pf 180pf 200pf 220pf*	470pf 510pf 560pf 620pf 680pf 820pf 1000pf/.00 1800pf/.00	HR5, 8 HR9 HR10 Luf* 18uf 27uf Dluf	14.00 17.00
1pf 1.1pf 1.4pf 1.5pf 2.2pf 2.7pf 3.3pf 3.6pf 3.9pf 4.7pf	12pf 15pf 18pf 20pf 22pf 24pf 27pf 33pf 39pf 47pf	110pf 120pf 130pf 150pf 160pf 180pf 200pf 220pf* 240pf 270pf	470pf 510pf 560pf 620pf 820pf 1000pf/.00 1800pf/.00 2700pf/.00 10,000pf/.00	HR5, 8 HR9 HR10 Luf* 18uf 27uf D1uf D12uf	14.00 17.00
1pf 1.1pf 1.4pf 1.5pf 1.8pf 2.2pf 2.7pf 3.3pf 3.6pf 3.6pf 3.9pf 4.7pf 5.6pf 6.8pf	12pf 15pf 18pf 20pf 22pf 24pf 27pf 33pf 39pf 47pf 51pf 56pf 68pf	110pf 120pf 130pf 150pf 160pf 200pf 220pf* 240pf 270pf 300pf 330pf 360pf	470pf 510pf 560pf 620pf 820pf 1000pf/.00 1800pf/.00 2700pf/.00 10,000pf/.1	HR5, 8 HR9 HR10 27uf 27uf 21uf 212uf 212uf	14.00 17.00
1pf 1.1pf 1.4pf 1.5pf 2.2pf 2.2pf 2.7pf 3.3pf 3.9pf 4.7pf 5.6pf 6.8pf 8.2pf	12pf 15pf 18pf 20pf 22pf 24pf 27pf 33pf 39pf 47pf 51pf 56pf 68pf 82pf	110pf 120pf 130pf 150pf 160pf 200pf 220pf* 240pf 270pf 330pf 360pf 390pf	470pf 510pf 560pf 620pf 680pf 1000pf/.00 1800pf/.00 2700pf/.00 10,000pf/.00 10,000pf/.1 12,000pf/.1	HR5, 8 HR9 HR10 	14.00 17.00
1pf 1.1pf 1.4pf 1.5pf 2.2pf 2.2pf 2.7pf 3.3pf 3.9pf 4.7pf 5.6pf 6.8pf 8.2pf	12pf 15pf 18pf 20pf 22pf 24pf 27pf 33pf 39pf 47pf 51pf 56pf 68pf 82pf 1 to 1099¢ 101 to 1 11 to 5090¢ 1001 & U	110pf 120pf 130pf 150pf 160pf 200pf 220pf* 240pf 270pf 300pf 330pf 360pf 390pf	470pf 510pf 500pf 620pf 620pf 680pf 1000pf/.00 1800pf/.00 10,000pf/.00 10,000pf/.1 15,000pf/.1 18,000pf/.1 18,000pf/.1 18,000pf/.1	HR5, 8 HR9 HR10 	14.00 17.00
1pf 1.1pf 1.4pf 1.5pf 2.2pf 2.2pf 2.7pf 3.3pf 3.9pf 4.7pf 5.6pf 6.8pf 8.2pf	12pf 15pf 18pf 20pf 22pf 24pf 27pf 33pf 39pf 47pf 51pf 56pf 68pf 68pf 1 to 1099¢ 101 to 1 11 to 5090¢ 1001 & U 51 to 10080¢	110pf 120pf 130pf 150pf 160pf 200pf 220pf* 240pf 270pf 300pf 330pf 360pf 390pf 000 .60¢ * IS A SPECIAL PR P .35¢	470pf 510pf 560pf 620pf 620pf 1000pf/.00 1000pf/.00 10,000pf/.10 12,000pf/.15,0000pf/.15,000pf/.15	HR5, 8 HR9 HR10 101f* 18uf 27uf 01uf 012uf 012uf 015uf 018uf r \$7.50 or \$65.00 for \$350.00	14.00 17.00
1pf 1.1pf 1.4pf 1.5pf 1.8pf 2.2pf 2.7pf 3.3pf 3.6pf 3.6pf 4.7pf 5.6pf 6.8pf 8.2pf PRICES:	12pf 15pf 18pf 20pf 22pf 24pf 27pf 33pf 39pf 47pf 51pf 56pf 68pf 82pf 1 to 1099¢ 101 to 1 11 to 5090¢ 1001 & U 51 to 10080¢	110pf 120pf 130pf 150pf 160pf 200pf 220pf* 240pf 270pf 300pf 330pf 360pf 390pf 000 .60¢ * IS A SPECIAL PR P .35¢	470pf 510pf 510pf 620pf 620pf 680pf 1000pf/.00 1800pf/.00 2700pf/.00 12,000pf/.1 15,000pf/.1 18,000pf/.1 18,000pf/.1 100 f 100 f	HR5, 8 HR9 HR10 	14.00 17.00
1pf 1.1pf 1.4pf 1.5pf 1.8pf 2.2pf 2.7pf 3.3pf 3.6pf 3.6pf 4.7pf 5.6pf 6.8pf 8.2pf PRICES: WATKINS	12pf 15pf 18pf 20pf 22pf 24pf 27pf 33pf 39pf 47pf 51pf 56pf 68pf 82pf 1 to 1099¢ 101 to 1 11 to 5090¢ 1001 & U 51 to 10080¢	110pf 120pf 130pf 150pf 160pf 200pf 220pf* 240pf 270pf 300pf 330pf 360pf 390pf 000 .60¢ * IS A SPECIAL PR P .35¢	470pf 510pf 510pf 620pf 620pf 680pf 1000pf/.00 1000pf/.00 2700pf/.00 12,000pf/.1 15,000pf/.1 15,000pf/.1 18,000pf/.1 100 f 100 f	HR5, 8 HR9 HR10 	14.00 17.00
1pf 1.1pf 1.4pf 1.5pf 1.5pf 2.2pf 2.2pf 2.7pf 3.6pf 3.9pf 4.7pf 5.6pf 6.8pf 8.2pf PRICES: WATKINS	12pf 15pf 18pf 20pf 22pf 24pf 27pf 33pf 39pf 47pf 51pf 56pf 68pf 82pf 1 to 1099¢ 101 to 1 11 to 5090¢ 1001 & U 51 to 10080¢ JJOHNSON WJ-V907: Voltage Co y range 3.6 to 4.2GHz, Power	110pf 120pf 130pf 150pf 160pf 200pf 220pf* 240pf 270pf 300pf 330pf 360pf 390pf 000 .60c * IS A SPECIAL PR P .35c htrolled Microwave Oscillator ouput, Min. 10dBm typical, 8	470pf 510pf 560pf 620pf 620pf 1000pf/.00 1000pf/.00 10,000pf/.00 10,000pf/.1 12,000pf/.1 15,000pf/.1 15,000pf/.1 1000 f 1000 f 1	HR5, 8 HR9 HR10 luf* 18uf 27uf D1uf D12uf D12uf D15uf D18uf r \$7.50 or \$65.00 for \$350.00 0 eed.	14.00 17.00
<pre>lpf l.lpf l.4pf l.5pf l.5pf l.5pf 2.2pf 2.2pf 2.7pf 3.6pf 3.6pf 3.6pf 5.6pf 6.8pf 8.2pf PRICES: WATKINS Frequenc Spurious</pre>	12pf 15pf 15pf 18pf 20pf 22pf 24pf 27pf 33pf 39pf 47pf 51pf 56pf 68pf 82pf 1 to 1099¢ 101 to 1 11 to 5090¢ 1001 & U 51 to 10080¢ 	110pf 120pf 130pf 150pf 160pf 200pf 220pf* 240pf 270pf 300pf 360pf 390pf 000 .60c * IS A SPECIAL PR P .35c 	470pf 510pf 510pf 620pf 620pf 620pf 1000pf/.00 1800pf/.00 10,000pf/.10 12,000pf/.1 12,000pf/.1 12,000pf/.1 12,000pf/.1 12,000pf/.1 12,000pf/.1 1000pf/.1 1000 1000 \$110.0 84Bm Guarant -Band Non-H	HR5, 8 HR9 HR10 	14.00 17.00
1pf 1.1pf 1.4pf 1.5pf 1.5pf 2.2pf 2.2pf 2.7pf 3.3pf 3.9pf 4.7pf 5.6pf 6.8pf 8.2pf PRICES: WATKINS Frequenc Spurious 60dB typ	12pf 15pf 18pf 20pf 22pf 24pf 27pf 33pf 39pf 47pf 51pf 56pf 68pf 82pf 1 to 1099¢ 101 to 1 11 to 5090¢ 1001 & U 51 to 10080¢ JOHNSON WJ-V907: Voltage Co y range 3.6 to 4.2GHz, Power output suppression Harmonic ical, Residual FM, pk to pk,	110pf 120pf 130pf 150pf 160pf 200pf 220pf* 240pf 270pf 300pf 330pf 360pf 390pf 000 .60¢ * IS A SPECIAL PR P .35c 	470pf 510pf 510pf 620pf 620pf 620pf 1000pf/.00 1800pf/.00 10,000pf/.100 12,000pf/.100 12,000pf/.1 12,000pf/.1 13,000pf/.1 13,000pf/.1 1000 \$110.0 Compare the second sec	HR5, 8 HR9 HR10 27uf 27uf 21uf 212uf	14.00 17.00
1pf 1.1pf 1.4pf 1.5pf 1.5pf 2.2pf 2.7pf 3.3pf 3.9pf 4.7pf 5.6pf 6.8pf 8.2pf PRICES: Frequenc Spurious 60dB typ (1.5:1 V	12pf 15pf 18pf 20pf 22pf 22pf 24pf 27pf 33pf 39pf 47pf 51pf 56pf 68pf 82pf 1 to 1099¢ 101 to 1 11 to 5090¢ 1001 & U 51 to 10080¢ JOHNSON WJ-V907: Voltage Co y range 3.6 to 4.2GHz, Power output suppression Harmonic ical, Residual FM, pk to pk, SWR), Max. 60MHz, Tuning vol	<pre>110pf 120pf 130pf 130pf 150pf 160pf 180pf 200pf 220pf* 240pf 300pf 330pf 360pf 390pf 000 .60c * IS A SPECIAL PR P .35c ntrolled Microwave Oscillator ouput, Min. 10dBm typical, 8 (nf<sub>0</sub>), min. 20dB typical, In Max. 5KHz, pushing factor, M tage range +1 to +15volts, Tu </pre>	470pf 510pf 510pf 620pf 620pf 680pf.00 1800pf.00 10,000pf.00 10,000pf.100 10,000pf.11 12,000pf.1 15,000pf.1 15,000pf.1 15,000pf.1 15,000pf.1 15,000pf.1 15,000pf.1 15,000pf.1 15,000pf.1 10,000	HR5, 8 HR9 HR10 	14.00 17.00
<pre>lpf l.lpf l.4pf l.5pf l.5pf l.5pf 2.2pf 2.7pf 3.3pf 3.6pf 3.9pf 4.7pf 5.6pf 6.8pf 8.2pf PRICES: Frequenc Spurious 60dB typ (l.5:1 V modulati</pre>	12pf 15pf 18pf 20pf 22pf 22pf 24pf 27pf 33pf 39pf 47pf 51pf 56pf 68pf 82pf 1 to 1099¢ 101 to 1 11 to 5090¢ 1001 & U 51 to 10080¢ JOHNSON WJ-V907: Voltage Co y range 3.6 to 4.2GHz, Power output suppression Harmonic ical, Residual FM, pk to pk, SWR), Max. 60MHz, Tuning vol	110pf 120pf 130pf 150pf 160pf 200pf 220pf* 240pf 270pf 300pf 330pf 360pf 390pf 000 .60¢ * IS A SPECIAL PR P .35c 	470pf 510pf 510pf 620pf 620pf 680pf.00 1800pf.00 10,000pf.00 10,000pf.100 10,000pf.11 12,000pf.1 15,000pf.1 15,000pf.1 15,000pf.1 15,000pf.1 15,000pf.1 15,000pf.1 15,000pf.1 15,000pf.1 10,000	HR5, 8 HR9 HR10 	14.00 17.00
1pf 1.1pf 1.4pf 1.5pf 1.5pf 2.2pf 2.7pf 3.6pf 3.9pf 4.7pf 5.6pf 6.8pf 8.2pf PRICES: WATKINS Frequenc, Spurious 60dB typ (1.5:1 V modulati Bias +15 <b>TOIL F</b>	12pf 15pf 15pf 12pf 20pf 22pf 24pf 27pf 33pf 39pf 47pf 51pf 56pf 68pf 82pf 1 to 1099¢ 101 to 1 11 to 5090¢ 1001 & U 51 to 10080¢ JOHNSON WJ-V907: Voltage Co y range 3.6 to 4.2GHz, Power output suppression Harmonic ical, Residual FM, pk to pk, SWR), Max. 60MHz, Tuning vol on sensitivity range, Max. 1 +-0.05 volts @ 55mA, Max.	<pre>110pf 120pf 130pf 150pf 160pf 200pf 220pf* 240pf 270pf 300pf 330pf 360pf 390pf 000 .60c * IS A SPECIAL PR P .35c ntrolled Microwave Oscillator ouput, Min. 10dBm typical, 8 (nf<sub>0</sub>), min. 20dB typical, In Max. 5KHz, pushing factor, M tage range +1 to +15volts, Tu 20 to 30MHz/V, Input capacita</pre>	470pf 510pf 510pf 560pf 680pf 820pf 1000pf/.00 1000pf/.00 2700pf/.00 12,000pf/.1 15,000pf/.1 15,000pf/.1 15,000pf/.1 15,000pf/.1 1000 f 1000 f	HR5, 8 HR9 HR10 luf* 18uf 27uf 01uf 012uf 012uf 015uf 015uf 018uf r \$7.50 or \$65.00 for \$350.00  0 eed. armonic, min. Pulling figure t, Max0.1mA, 00pf, Oscillator	14.00 17.00 20.00
1pf 1.1pf 1.4pf 1.5pf 1.5pf 2.2pf 2.7pf 3.6pf 3.6pf 3.9pf 4.7pf 5.6pf 6.8pf 8.2pf PRICES: WATKINS Frequenc Spurious 60dB typ (1.5:1 V modulati Bias +15 <b>BOO-52</b>	12pf 15pf 15pf 18pf 20pf 22pf 24pf 27pf 33pf 39pf 47pf 51pf 56pf 68pf 82pf 1 to 1099¢ 101 to 1 11 to 5090¢ 1001 & U 51 to 10080¢ JOHNSON WJ-V907: Voltage Co y range 3.6 to 4.2GHz, Power output suppression Harmonic ical, Residual FM, pk to pk, SWR), Max. 60MHz, Tuning vol on sensitivity range, Max. 1 +-0.05 volts @ 55mA, Max. ree Number 28-0180	<pre>110pf 120pf 130pf 150pf 160pf 200pf 220pf* 240pf 270pf 300pf 330pf 360pf 390pf 000 .60c * IS A SPECIAL PR P .35c ntrolled Microwave Oscillator ouput, Min. 10dBm typical, 8 (nf<sub>0</sub>), min. 20dB typical, In Max. 5KHz, pushing factor, M tage range +1 to +15volts, Tu 20 to 30MHz/V, Input capacita</pre>	470pf 510pf 510pf 560pf 680pf 820pf 1000pf/.00 1000pf/.00 2700pf/.00 12,000pf/.1 15,000pf/.1 15,000pf/.1 15,000pf/.1 15,000pf/.1 1000 f 1000 f	HR5, 8 HR9 HR10 	14.00 17.00 20.00
1pf 1.1pf 1.4pf 1.5pf 1.8pf 2.2pf 2.7pf 3.3pf 3.6pf 3.9pf 4.7pf 5.6pf 6.8pf 8.2pf PRICES: WATKINS Frequenc Spurious 60dB typ (1.5:1 V modulati Bias +15 <b>B00-52</b>	12pf 15pf 15pf 12pf 20pf 22pf 24pf 27pf 33pf 39pf 47pf 51pf 56pf 68pf 82pf 1 to 1099¢ 101 to 1 11 to 5090¢ 1001 & U 51 to 10080¢ JOHNSON WJ-V907: Voltage Co y range 3.6 to 4.2GHz, Power output suppression Harmonic ical, Residual FM, pk to pk, SWR), Max. 60MHz, Tuning vol on sensitivity range, Max. 1 +-0.05 volts @ 55mA, Max.	<pre>110pf 120pf 130pf 150pf 160pf 200pf 220pf* 240pf 270pf 300pf 330pf 360pf 390pf 000 .60c * IS A SPECIAL PR P .35c ntrolled Microwave Oscillator ouput, Min. 10dBm typical, 8 (nf<sub>0</sub>), min. 20dB typical, In Max. 5KHz, pushing factor, M tage range +1 to +15volts, Tu 20 to 30MHz/V, Input capacita</pre>	470pf 510pf 510pf 560pf 680pf 820pf 1000pf/.00 1000pf/.00 2700pf/.00 12,000pf/.1 15,000pf/.1 15,000pf/.1 15,000pf/.1 15,000pf/.1 1000 f 1000 f	HR5, 8 HR9 HR10 luf* 18uf 27uf 01uf 012uf 012uf 015uf 015uf 018uf r \$7.50 or \$65.00 for \$350.00  0 eed. armonic, min. Pulling figure t, Max0.1mA, 00pf, Oscillator	14.00 17.00 20.00

G

PupSob pp st v

# TUBES

TYPE	PRICE	TYPE	PRICE	TYPE	PRIOR
2E26	\$ 5.69				PRICE
2K28	\$ 5.69 100.00	KT88	\$ 20.00	6562/6974A	\$ 50.00
2X1000A	300.00	DX362	50.00	6832	22.00
3B22		DX415	50.00	6883/8032A/8552	7.00
3B28/866A	19.75	572B/T160L	49.00	6897	110.00
3-500Z	7.50	592/3-200A3	144.00	6907A	75.00
	102.00	807	7.50	6939	15.00
3-1000Z	400.00	811	10.00	7094	125.00
3CX1000A/8283	428.00	811A	15.00	7117	17.00
3CX1500A7/887	533.00	812A	35.00	7211	60.00
3X2500A3	200.00	813	50.00	7289/3CX100A5	34.00
3CX3000A7	490.00	829B	38.00	7360	11.00
4-65A/8165	45.00	832A	28.00	7377	67.00
4-125A/4D21	58.00	4624	310.00	7408	4.00
4-250A/5D22	75.00	4662	80.00	7650	250.00
4-400A/8432	90.00	4665	585.00	7695	8.00
4-400C/6775	95.00	5675/A	25.00	7843	58.00
4-1000A/8166	300.00	5721	200.00	7854	83.00
4B32	22.00	5768	85.00	7868	5.00
4E27A/5-125B	155.00	5836	100.00	7894	12.00
4CS250R	146.00	5837	100.00	8072	65.00
4X150A/7034	30.00	5861/EC55	110.00	8117A	130.00
4X150D/7035	40.00	5876A	25.00	8121	
4X150G/8172	100.00	5881/6L6W	6.00	8122	60.00
4X250B	30.00	5893	45.00	8236	100.00
4CX250B/7203	45.00	5894/A	50.00	8295/PL172	30.00
4CX250F/G/8621	55.00	5894/B	60.00	8462	506.00
4CX250K/8245	100.00	5946	258.00	8505A	100.00
4CX250R/7580W	69.00	6080	10.00	8533W	73.50
4CX300A/8167	140.00	6083/AX9909	89.00	8560/A	92.00
4CX350A/8321	83.00	6098/6AK6	14.00		65.00
4CX350F/J/8904	95.00	6115/A	14.00	8560AS	90.00
4X500A	282.00	6146	7.00	8608	34.00
4CX600J/8809	607.00	6146A	7.00	8637	38.00
4CW800F	625.00	6146B/8298A		8643	100.00
4CX1000A/8168	340.00	6146W	8.50	8647 8737/580/m	123.00
4CX1500B/8660	397.00	6156	14.00 66.00	8737/5894B	60.00
4CX5000A/8170	932.00	6159	15.00	8873	260.00
4CX10000D/8171	990.00	6161		8874	260.00
4CX15000A/8281	1260.00	6291	233.00	8875	260.00
4PR60A	100.00		125.00	8877	533.00
4PR60B/8252	175.00	6293 6360	12.00	8908	12.00
4PR400B/8252 4PR400A/8188		6360 6524	5.00	8930/651Z	71.00
4PR400A78188 5CX1500A	192.00	6524	53.00	8950	12.00
	569.00	6550	10.00		
6BK4C	6.00	6JM6	6.00	6LQ6 (Sylvania)	7.50
6DQ5	5.00	6JN6	6.00	6LU8	6.00
6FW5	6.00	6JS6B	6.00	6LX6	6.00
6GE5	6.00	6KG6/EL505	6.00	6ME 6	6.00
6GJ5	6.00	6КМ6	6.00	12BY7A	4.00
6HS 5	6.00	6KN 6	6.00	12JB6A	6.00
6JB5/6HE5	6.00	6LF6	6.00	6KD6	6.00
6JB6A	6.00	6LQ6 (GE)	6.00	6JT6A	6.00
				6KD6	6.00
NOTICE ALL PRICES	ARE SUBJECT T	O CHANGE WITHOUT	NOTICE !!!!!!!!!		
NOTICE ALL PRICES ARE SUBJECT TO CHANGE WITHOUT NOTICE !!!!!!!!!!!!!!!!!!!!!!!!!!!!!!!!!!!!					

Toll Free Number 800-528-0180 (For orders only)

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

MHz electronics

## **"TVRO BOARD LIST"**

70 MHZ IF BOARD: This circuit provides about 43dB gain with 50 ohm input and output impedance. It is designed to drive the Demodulator. The on-board bypass filter can be tuned to bandwidths between 20 and 35 MHz with a passband ripple of less than ½ dB. Hybrid IC's are used for the gain stages.

SINGLE AUDIO BOARD: This circuit recovers the audio signals from the 6.8 MHz frequency. The Miller 9051 coils are tuned to pass the 6.8MHz subcarrier and the 9052 coil tunes for recovery of the audio.

.15

1.00

1.00

1.00

1.00

1.00

1.50

1.50

1.50

DUAL AUDIO BOARD: Duplicate of the single audio but also covers the 6.2 range. DC CONTROL BOARD: No description.

3 10K 1/4w

1

1

1

. 59

.15

330pf sm

l00pf sm

91pf sm

100uh choke

4.7uh choke

2.7uh choke

3pf sm

DUAL AUDIO BOARD	PRICE EACH
Printed Circuit Board	\$ 25.00
2 3pf sm	1.00
2 12pf sm	1.00
2 50pf sm	1.00
2 68pf sm	1.00
4 91pf sm	1.00
5 .001mfd	. 35
6 .Olmfd	. 35
2 .047mfd	. 35
1 .47mfd 25vdc	. 35
2 lmfd lOvdc	. 59
4 4.7mfd 35vdc	. 59
1 470mfd 25vdc	1.29
2 220K 1/4w	.15
2 150K 1/4w	. 15
2 6.8K 1/4w	.15
2 3.3K 1/4w	.15
2 2.2K 1/4w	.15
4 1K.1/4w	.15
2 10 ohm 1/4w	. 15
2 50K pots	1.00
1 5K pot	1.00
2 CA3065	2.16
1 LM380	1.56
1 7812 Voltage Reg.	1.17
5 2N2222	. 50
4 Miller 9051	5.99
2 Miller 9052	5.99
TOTAL KIT PRICE	97.62
DC CONTROL BOARD	8749 - 197
Printed Circuit Board	15.00
2 470mfd 25vdc	1.29
2 / 7 (1 25 1	5.0

3.3K 1/4w	.15
2.2K 1/4w	.15
1K 1/4w	.15
5K 10 turn trimpot	1.00
10K 10 turn trimpot	1.00
10K 10 turn with dial	10.00
7815 Voltage Reg.	1.17
LM324	2.50
5 pole rotary switch	2.50
SPDT switch	1.00
DPDT swich	1.00
0-lma meter	5.00
18 to 24vdc at 1 amp	
power supply	24.99
DTAL KIT PRICE	74.27
ODULATOR BOARD	PRICE EACH
nted Circuit Board	\$ 40.00
lmfd 35vdc	. 59
.Olmfd 50vdc disc	. 35
470mfd 25vdc	1.29
100mfd 16vdc	. 69
22mfd 35vdc	. 59
4.7mfd 35vdc	. 59
4300pf sm	2.00
	2.2K 1/4w IK 1/4w SK 10 turn trimpot 10K 10 turn trimpot 10K 10 turn with dial 7815 Voltage Reg. LM324 5 pole rotary switch SPDT switch DPDT switch 0-lma meter 18 to 24vdc at 1 amp power supply DTAL KIT PRICE DDULATOR BOARD nted Circuit Board 1mfd 35vdc .01mfd 50vdc disc 470mfd 25vdc 100mfd 16vdc 22mfd 35vdc

<ul> <li>4 100K 1/4w</li> <li>1 51 ohm 1/4w</li> <li>1 27K 1/4w</li> <li>5 10K 1/4w</li> <li>8.2K 1/4w</li> <li>2 4.7K 1/4w</li> <li>1 2.2K 1/4w</li> <li>1 1.2K 1/4w</li> <li>3 1K 1/4w</li> <li>3 560 ohm 1/4w</li> <li>4 370 ohm 1/4w</li> <li>300 ohm 1/4w</li> <li>1 50 ohm 1/4w</li> <li>1 50 ohm 1/4w</li> <li>1 10K pot</li> <li>1 NE564</li> </ul>	.15
1 51 ohm 1/4w	.15
1 27K 1/4w	.15
5 10K 1/4w	. 15
1 8.2K 1/4w	.15
2 4.7K 1/4w	.15
1 2.2K 1/4w	.15
1 1.2K 1/4w	.15
3 1K 1/4w	.15
3 560 ohm 1/4w	. 15
1 470 ohm 1/4w	. 15
1 390 ohm 1/4w	.15
1 300 ohm 1/4w	.15
1 270 ohm 1/4w	.15
1 150 ohm 1/4w	.15
1 41 ohm 1/4w	.15
1 10K pot	1.00
1 NE592/LM733N	2.50
1 NE 564	5.00
1 MWA120 (Motorola)	7.80
	1.17
1 7815 Voltage Reg.	1.17
3 2N2222	. 50
2 IN34/38	. 50
1 HP5082-2800	.50 2.20
	1.00
TOTAL KIT PRICE	92.25
COMPLETE KIT WITH DUAL AUDIO	\$923.23
COMPLETE KIT WITH SINGLE AUDIO	
LESS 10% ON ALL COMPLETE KIT OF	DERS

BOARDS AND PARTS MAY BE PURCHASED SEPERATELY

ALL PRICES ARE SUBJECT TO CHANGE WITHOUT

AT THE PRICES LISTED ABOVE.

13

Pri	nted Circuit Board
2	470mfd 25vdc
2	4.7mfd 25vdc
1	lmeg 1/4w

#### TVRO BOARD DESCRIPTION AND PARTS LIST

2 to 8pf ceramic trimmer

DUAL CONVERSION BOARD: This board provides conversion from the 3.7-4.2 band first to 900 MHz where gain and bandpass filtering are provided and, second, to 70 MHz. The board contains both local oscillators, one fixed and the other variable, and the second mixer. Construction is greatly simplified by the use of Hybrid IC amplifiers for the gain stages.

DEMODULATOR BOARD: This circuit takes the 70 MHz center frequency satellite TV signal in the 10 to 2000 millivolt range, detects them using a phase lock loop, de-emphasizes and filters the result to produce standard NTSC video. Other outputs include the audio subcarrier, a DC voltage proportional to the strength of the 70 MHz signal, and AFC voltage centered at about 2 volts DC.

80	00-528-0180		TO CHANGE WITHOUT NOT	. M	H z electro	ηις
	nted Circuit Board Dil Free Number	25.00	3 .001mfd 3 .01mfd	. 35		55.18
70 1	HZ 1F BOARD		2 91pf sm	1.00	I Miller 9052 TOTAL KIT PRICE	5.99 55.16
			1 68pf sm	1.00	2 Miller 9051	5.99
TOT	AL KIT PRICE	572.64	l l2pf sm l 50pf sm	1.00	3 2N2222	. 50
8	SMA Male Connector	5.00	1 3pf sm	1.00	1 7812 Voltage Reg.	1.17
1	MLP102 (Engleman)	25.00	Printed Circuit Board	\$ 15.00	1 LM380	1.56
1	DBM500/1100 (Varil)	125.00			I CA3065/MC1358P	2.16
2	1N4005	. 39	SINGLE AUDIO BOARD	PRICE EACH	1 5K pot	1.00
ł	VT08240	156.25			1 50K pot	.15
1	VT08090	150.00	TOTAL KIT PRICE	86.45	1 10 ohm 1/4w	. 15
1	7815 Voltage Reg.	1.17	l 7815 Voltage Reg.	1.17	3 IK 1/4w	.15
2	MWA320 (Motorola)	8.65	5 J.W. Miller 4500-4	4.99	1 3.3K 1/4w 1 2.2K 1/4w	. 15
2	470 ohm 1/4w	.15	2 330 ohm 1/4w	. 15	1 6.8K 1/4w	. 15
	trimmer cap	5.99	l 33pf sm	1.00	1 150K 1/4w	.15
4	1.5 to 8pf piston		l l8pf sm	1.00	1 220K 1/4w	. 15
2	.01mfd 50vdc disc cap	. 35	5 22pf sm	1.00	1 470mfd 25vdc	1.29
2	4.7mfd 35vdc	.59	l lOpf sm	1.00	3 4.7mfd 35vdc	. 59
6	47pf chip caps	1.00	2 4.7mfd 35vdc	. 59	l lmfd l0vdc	. 59
Pri	nted Circuit Board	\$ 25.00	7 .Olmfd 50vdc	.35	1 .47mfd	. 35
DUA	L CONVERSION BOARD	PRICE EACH	3 MWA120	7.80	l .047mfd	.35

# "CHIPS"

FAIRCHILD	VHF AND UHF PRESCALER CHIPS	PRICE
95H90DC	350MC Prescaler divide by 10/11	\$ 8.50
95H91DC	350MC Prescaler divide by 5/6	8.50
11C90DC	650MC Prescaler divide by 10/11	15.50
11C91DC	650MC Prescaler divide by 5/6	15.50
11C06DC	UHF Prescaler 750MC D Type Flip Flop	12.30
11C05DC	1GHz Counter Divide by 4	
	(Regular price \$75.00)	50.00
11C01FC	High Speed Dual 5/4 Input NO/NOR Gate	15.40
82590	Presettable High Speed Decade/Binary	
	Counter used with the 11C90/91 or the	
	95H90/91 Prescaler can divide by 100.	
	(Signetics)	5.00
11C24DC	This chip is the same as a Motorola	
	MC4024/4324 Dual TTL Voltage Control	
	Multivibrator.	3.37
11C44DC	This chip is the same as a Motorola	
	MC4044/4344 Phase Frequency Detector.	3.37

#### **GENERAL ELECTRIC CO. GUNN DIODE MODEL Y-2187**

Freq. Gap (GHZ) 12 to 18, Output (Min.) 100mW, Duty (%) CW, Typ. Bias (Vdc) 8.0, Type. Oper. (MAdc) 550, Max. Thres. (mAdc) 1000, Max, Bias (Vdc) 10.0 \$39.99 VARIAN GALLIUM ARSENIDE GUNN DIODES MODEL VSX-920155 Freq. Coverage 8 to 12.4GHz, Output (Min.) 100mW, Blas

Voltage (Max.) 14vdc, Blas current (mAdc) Operating 550 Typ. 750 Max., Threshold 850 Tup. 1000 Max \$39.99 VARI-L Co. Inc. MODEL SS-43 AM MODULATOR Freq. Range 60 10 150MC, Insertion Loss 13dB Nominal, Signal Port Imp. 50ohms Nominal, Signal Port RF Power

+ 10dBm Max., Modulation Port BW DC to 1KHZ, Modulation Port Blas 1ma. Nominal. \$24.99

AVANTEK CAS	SCADABLE
-------------	----------

MODULAR AMPLIFIERS		Model U	TO-504	UTO-511
Frequency Range		5 to 500	MHz	5 to 500 MHz
Gain		6dB		15dB
Noise Figure		11dB		2.3dB to 3dB
Power Output		+ 17dB		- 2dB to
				– 3d B
Gain Flatness		1dB		1dB
Input Power Vdc		+ 24		+ 15
mA		100		10
	PRICE	\$70.00	PRICE	\$75.00

ORDERING INSTRUCTIONS DEFECTIVE MATERIAL: All claims for defective material must be made within sixty (60) days after receipt of parcel. All claims must include the defective material (for testing purposes), our invoice number, and the date of purchase. All returns must be packed properly or it will void all warranties.

DELIVERY: Orders are normally shipped within 48 hours after receipf of customer's order. If a part has to be backordered the customer is notified. Our normal shipping method is via First Class Mall or UPS depending on size and weight of the package. On test equipment it is by Air only, FOB shipping point.

FOREIGN ORDERS: All foreign orders must be prepaid with cashier's check or money order made out in U.S. Funds. We are sorry but C.O.D. Is not available to foreign countries and Latters of Credit are not an acceptable form of payment either. Funder information is available on request.

HOURS: Monday thru Saturday: 8:30 a.m. to 5:00 p.m.

INSURANCE: Please include 25c for each additional \$100.00 over \$100.00, United Parcel only

ORDER FORMS: New order forms are included with each order for your convenience. Additional forms are evailable on request.

POSTAGE: Minimum shipping and handling in the US, Canada, and Mexico is \$2.50 all other countries is \$5.00 On foreign orders include 20% shipping and handling.

PREPAID ORDERS: Order must be accompanied by a check

PRICES: Prices are subject to change without notice.

RESTOCK CHARGE: If parts are returned to MHZ Electronics due to customer error, customer will be held responsible for all extra fees, will be charged a 15% restocking fee, with the remainder in credit only. All returns must have approval

SALES TAX: Arizona must add 5% sales tax, unless a signed Arizona resale tax card is currently on file with MHZ Electronics. All orders placed by persons outside of Arizona, but delivered to persons in Arizona are subect to the 5% sales tax

SHORTAGE OR DAMAGE: All claims for shortages or damages must be made within 5 days after receipt of parcel. Claims must include our invoice number and the date of purchase, Customers which do not notify us within this time period will be held responsible for the entire order as we will consider the order complete.

OUR 800 NUMBER IS STRICTLY FOR ORDERS ONLY

NO INFORMATION WILL BE GIVEN. 1-800-528-0180

HEWLETT PACKARD		
MIXERS MODELS	10514A	10514B
Frequency Range	2MHz to 500MC	2MHz to
		500MC
Input/Output Frequency L & R	200KHz to	200KHz to
	500MC	500MC
X	DC to 500MC	DC to 500MC
Mixer Conversion Loss (A)	7dB	7dB
(B)	9dB	9dB
Noise Performance (SSB) (A)	7dB	7dB
(B)	9dB	9dB
PRICE	\$49.99 PRICE	\$39.99

#### FREQUENCY SOURCES, INC MODEL MS-74X MICROWAVE SIGNAL SOURCE

MS-74X: Mechanically Tunable Frequency Range (MHz) 10630 to 11230 (10.63 to 11.23GHz) Minimum Output Power (mW) 10, Overall Multiplier Ratio 108, Internal Crystal Oscillator Frequency Range (MHz) 98.4 to 104.0, Maximum Input Current (mA) 400

The signal source are designed for applications where high stability and low noise are of prime concern, these sources utilize fundamental transistor oscillators with high Q coaxial cavities, followed by broadband stable step recovery diode multipliers. This design allows single screw mechanical adjustment of frequency over standard communications bands. Broadband sampling circuits are used to phase lock the oscillator to a high stability reference which may be either an internal self-contained crystal oscillator, external primary standard or VHF synthesizer. This unique technique allows for optimization of both FM noise and long term stability. List Price Our Price-\$289. is \$1158.00 (THESE ARE NEW)

#### **HEWLETT PACKARD 1N5712 MICROWAVE DIODE**

This diode will replace the MBD101, 1N5711, 5082-2800, 5082-2835 ect. This will work like a champ in all those Down Converter projects. \$1.50 or 10/\$10.00

#### **MOTOROLA MHW1172R LOW DISTORTION**

WIDEBAND AMPLIFIER MODULE.

Frequency Range: 40 to 300 MHz., Power Gain at 50MHz 16.6min. to 17.4max., Gain Flatness ±0.1 Typ. ±0.2 Max. dB., DC Supply Voltage - 28vdc, RF Voltage Input + 70dBmV PRICE \$29.99

#### GENERAL ELECTRIC AA NICADS

Model #41B905HD11-G1

Pack of 6 for \$5.00 or 60 Cells, 10 Packs for \$45.00 These may be broken down to individual cells.

TERMS: DOMESTIC: Prepaid, C.O.D. or Credit Card FOREIGN: Prepaid only, U.S. Funds—money order or cashler's check only. C.O.D.: Acceptable by telephone or mail. Payment from customer will be by cash, money order or cashier's check. We are sorry but we cannot accept personal checks for C.O.D.'s.

CONFIRMING ORDERS: We would prefer that confirming orders not be sent after a telephone order has been placed. If company policy necessitates a confirming order, please mark "CONFIRMING" boldly on the order. If problems or duplicate shipments occur due to an order which is not properly marked, customers will be held responsible for any charges incurred, plus a 15% restock charge on returned parts CREDIT CARDS: WE ACCEPT MASTERCARD VISA AND AMERICAN EXPRESS.

DATA SHEETS: When we have data sheets in stock on devices we do supply them with the order.



(For orders only)

### SLEP ELECTRONICS

GIVES TOP TRADE on your used AT-LAS, COLLINS, DRAKE, ICOM, KEN-WOOD, TEN-TEC amateur gear... plus we accept your used solid state TEK-TRONIX and HEWLETT-PACKARD test equipment, used AVIONIC equipment, and military surplus avionic and ground electronic equipment.

WE OFFER new factory-boxed latest models of: COLLINS, CUBIC/SWAN, DENTRON, DRAKE, ETO, HENRY, ICOM, TEN-TEC, plus all major antenna and accessory lines.

Tell us what you want and what you have to trade. We'll do the rest.

Write or phone Bill Slep (704) 524-7519



- 12

## Slep Electronics Company

P. O. BOX 100, HWY 441, DEPT. 73 OTTO, NORTH CAROLINA 28763

# HAM HELP

We are happy to provide Ham Help listings free, on a space-available basis. We are not happy when we have to take time from other duties to decipher cryptic notes scrawled illegibly on dog-eared post cards and odd-sized scraps of paper. Please type or print your request (neatly!), double spaced, on an 81/2" x 11" sheet of paper and use upper- and lowercase letters where appropriate. Also, please make a "1" look like a "1," not an "l," which could be an "el" or an "eye," and so on. Hard as it may be to believe, we are not familiar with every piece of equipment manufactured on Earth for the last 50 years! Thanks for your cooperation.

Does anyone have information on RTTY software for a TRS-80 Model I Level II?

Gary Hansen KA6UUM Route 1 Box 103 Deerwood MN 56444

I am looking for hams with RTTY equipment who would like to help deaf students attending school in Washington DC communicate with their families back home.

> Jeffrey A. Meyer N8AHA 26366 Greythorne Trail Farmington Hills MI 48018

I am looking for a used LCR bridge such as the Leader LCR 740.

> Jim Buckwalter WA6FGM 3212 Millcreek Visalia CA 93291

I need a service manual and schematic diagram for a Hy-Gain Galaxy GT-550-A SSB transceiver. I will pay reasonable copying costs or copy and return.

> Jose Sanabrais Av. Hidalgo No. 99 Queretaro, Qro. 76000 Mexico

I would like to buy the following WWII surplus receivers, In at least good used condition (they need not include power supply, dynamotor, etc.): ARB, RBB (0.5 to 4.0 MHz), and BC-946 (broadcast band ARC-5 receiver).

> Meyer Gottesman W6GIV 3377 Solano Avenue, #312 Napa CA 94558

I am blind and bedridden and searching for someone to donate a Kenwood 600 receiver or any other shortwave receiver.

> Richard Jastrow Long Beach General Hospital 2597 Redondo Ave. Long Beach CA 90806

My club's 5-page Novice-class study guide is offered in exchange for your club's Novice-and/or General-class handouts. Ours is a brief description of the items listed in the current FCC syllabus and has a 95% pass rate in our classes.

> Jim Koski KT6W 1714 Austin Avenue Los Altos CA 94022

\* B E C \* Bullet Electronics Corp. P.O. Box 401244E Garland, TX. 75040 (214) 278-3553


# THE PRESIDENT SAYS: "HOGWASH!!"

After taking one look at the TRIPUT POWER SUPPLY our engineer declared that the units were worth several hundred dollars each. He pointed out the engineering, high quality construction and state-of-the-art integrated design in support of his position. The President of **BEC** more pragmatically pointed out the already full warehouse and the two trailer truck loads of power supplies waiting in the parking lot, and set the price to move them **QUICKLY!** We have a large quantity, but the supply won't last long. The only thing we ask is *please* read the ordering rules.

QUALITY DOUBLE SIDED GLASS BOARD



REGULATOR ASSEMBLY (part of unit)

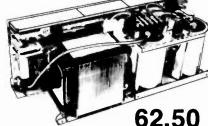

**Plus Freight** 

#### COMPLETE UNIT (as you receive it)

(as you receive it) 21 lbs. ORDERS SHIPPED WITHIN CONTINENTAL U.S. ONLY! 6 x 5¼ x 12 ORDERING RULES

- 1. Mail check or MO for \$62.50 + \$5.00 for shipping or phone (214) 278-3553 to charge VISA/MC or COD order. (UPS COD only, add \$2.50 COD fee)
- 2. Texas residents include 5% sales tax.
- Orders for this unit will be shipped within 48 HOURS or we pay the freight! (weekends or holidays excluded)
- 4. ONE TIME OFFER! LIMIT TWO (2) SUPPLIES PER CUSTOMER.

#### 13.6V @ 20A MODIFICATION By changing a few parts on the board the Triput

Power Supply will do 11 - 14V (adjustable) at up to 20A. Perfect for that 2 meter linear ampl We send step by step instructions and necessary parts. Modlification per instructions will not void the 30 day warranty.

+12V @ 7A; +5V @ 10A; -12V @ 5A

- UNIT IS COMPLETELY ASSEMBLED!
- Fused primary and DC sections
- HUGE SHIELDED TRANSFORMER
- 2% Load & Line Regulation
- Low Ripple (< 100mv)</li>
  Short Circuit Protection
- Short Circuit Protection
- Overvoltage Protection on all three outputs
- 25A Bridge Rectifier
- Over 60,000 mfd of filters
   High Efficiency Cultables
- High Efficiency Switching Regulator reduces heatsink area
- Schematics and service guide included
  Thermal Shutdown
- Statis LED's (3)

## lauzei



AL I year warranty 90 day parts war

ranty AC 1 AC adopter BP 1 Nicad pack \* AC Adopter/Charger OV-1, Micro-power Oven

nal time base inou

\$129.95

109 95

12.95

49,95

# the first name in Counters! 9 DIGITS 600 MHz \$129 95

The CT-90 is the most versatile, feature packed counter available for less than \$300.00! Advanced design features include: three selectable gate times, nine digits, gate indicator and a unique display hold function which holds the displayed count after the input signal is removed Also, a 10mHz TCXO time base is used which enables easy zero beat calibration checks against WWV. Optionally; an internal nicad battery pack, external time base input and Micropower high stability crystal oven time base are available. The CT-90, performance you can count on!

Range:	ATIONS: WIRED
Sensitivity:	Less than 10 MV to 150 MHz
	Less than 50 MV to 500 MHz
Resolution	0.1 Hz (10 MHz range)
	1.0 Hz (60 MHz range)
	10.0 Hz (600 MHz range)
Display:	9 digits 0.4" LED
Time base:	Standard-10.000 mHz, 1.0 ppm 20-40°C.
	Optional Micro-power oven-0.1 ppm 20-40°C
Power:	8-15 VAC @ 250 ma

## 7 DIGITS 525 MHz \$9995 WIRED

#### SPECIFICATIONS

Range:	20 Hz to 525 MHz
Sensitivity:	Less than 50 MV to 150 MHz
	Less than 150 MV to 500 MHz
<b>Resolution</b> :	1.0 Hz (5 MHz range)
	10.0 Hz (50 MHz range)
	100.0 Hz (500 MHz range)
Display.	7 digits 0.4" LED
Time base:	1.0 ppm TCXO 20-40°C
Power.	12 VAC @ 250 ma

The CT-70 breaks the price barrier on lab quality frequency counters. Deluxe features such as, three frequency ranges - each with pre-amplification, dual selectable gate times, and gate activity indication make measurements a snap. The wide frequency range enables you to accurately measure signals from audio thru UHF with 1.0 ppm accuracy - that's .0001%! The CT-70 is the answer to all your measurement needs, in the field, lab or ham shack.



PRICES	
CT-70 wired, I year warranty	\$99.95
CT-70 Kit, 90 day parts war-	
ranty	84.95
AC-1 AC adapter	3.95
BP-1 Nicad pack + AC	
adapter/charger	12.95

## DIGITS 500 MHz \$79 95 WIRED

PRICES:	
MINI-100	wir

warranty	\$79.95
AC-Z Ac adapter for MINI-	
100	3.95
BP-Z Nicad pack and AC	
adapter/charger	12.95

ed, 1 year

Here's a handy, general purpose counter that provides most counter functions at an unbelievable price. The MINI-100 doesn't have the full frequency range or input impedance qualities found in higher price units, but for basic RF signal measurements, it can't be beat' Accurate measurements can be made from 1 MHz all the way up to 500 MHz with excellent sensitivity throughout the range, and the two gate times let you select the resolution desired. Add the nicad pack option and the MINI-100 makes an ideal addition to your tool box for "in-the-field" frequency checks and repairs.

#### SPECIFICATIONS:

Range 1 MHz to 500 MHz Sensitivity: Less than 25 MV Resolution 100 Hz (slow gate) 1.0 KHz (fast gate) 7 digits, 0.4" LED Display 2.0 ppm 20-40°C Time base 5 VDC @ 200 ma Power

# 8 DIGITS 600 MHz \$159<sup>95</sup> WIRED



#### SPECIFICATIONS: 20 Hz to 600 MHz

Sensitivity Resolution 10.0 Hz (600 MHz range) Display 8 digits 0.4" LED Time base: 2.0 ppm 20-40°C 110 VAC or 12 VDC

The CT-50 is a versatile lab bench counter that will measure up to 600 MHz Less than 25 my to 150 MHz with 8 digit precision. And, one of its best features is the Receive Frequency Less than 150 mv to 600 MHz Adapter, which turns the CT-50 into a digital readout for any receiver. The adapter is easily programmed for any receiver and a simple connection to the receiver's VFO is all that is required for use. Adding the receiver adapter in no way limits the operation of the CT-50, the adapter can be conveniently switched on or off. The CT-50, a counter that can work double duty!

2		5
PRIC CT-5 CT-5	CES: 0 wired, 1 year warranty 0 Kit, 90 day parts	\$159.95

warranty 119.95 RA-1, receiver adapter kit 14.95 RA-1 wired and pre-programmed (send copy of receiver 29.95 schematic)

SPECIFICATIONS:

DC/AC

current

DC/AC volts: 100 uV to 1 KV, 5 ranges

0.1 uA to 2.0 Amps. 5 ranges

#### DIGITAL MULTIMETER \$99 % WIRED hiif

The DM-700 offers professional quality performance at a hobbyist price. Features Include; 26 different ranges and 5 functions, all arranged in a

convenient, easy to use format. Measurements are displayed on a large 31/2

digit, ½ inch LED readout with automatic decimal placement, automatic

#### PRICI DM-70 DM-70 warran AC-L BP-3. 1 adapter MP-I.

		_
Probe kit	2.95	
r/charger	19.95	
Nicad pack +AC		
AC adaptor	3.95	
ty	79.95	
00 Kit, 90 day parts		
0 wired, 1 year warranty	\$99.95	
ES:		

AC-1, AC adaptor BP-3, Nicad pack +AC adapter/charger MP-1, Probe kit	79.95 3.95 19.95 2.95	ranges, making it virtually	ion and overload protection up to 12 goof-proof: The DM-700 looks grea e with convenient retractable tilt by p.	50 volts on all t, a handsome,	current Resistance Input impedance Accuracy: Power:	0.1 uA to 2.0 Amps, 5 ranges 0.1 ohms to 20 Megohms, 6 ranges 10 Megohms, DC/AC volts 0.1% basic DC volts 4 'C' cells
AUDI	O SCALE		ACCESSORIE	- 1	COUN	NTER PREAMP
For high resolution audio measurements, multiplles UP in frequency. • Great for PL tones • Multiplies by 10 or 100 • 0.01 Hz resolution! \$29.95 Klt \$39.95 Wired		Ites High impedance p Low pass probe, for Direct probe, gene Tilt bail, for CT 7 Color burst calibra	ntenna - BNC plug. robe, light loading or audio measurements ral purpose usage 0. 90, MINI-100 	15.95 15.95 12.95 3.95	MHz. Small size, Flat 25 db ga BNC Connec Great for sni	
<b>ramsey elec</b> 2575 Baird Rd.			PHONE ORDERS CALL 716-586-3950	retu insu	n in originat form rance to a maximum	I esamine for 10 days of not pleased. For refund Add 5≈ for shipping on of \$10.0 versea add 15∞ COD add add \$1.50. NY residence, add 7 for

#### NEW LOW-NOISE PREAMPS **RECEIVING CONVERTERS TRANSMIT CONVERTERS**

New low-noise microwave transistors make preamps in the 0.9 to 1.0 dB noise figure range possible without the fragility and power supply problems of gas-fet's. Units furnished wired and tuned to ham band. Can be easily retuned to nearby freq.



Models LNA( ) P30, and P432 shown

Model	Freq Range	Noise Figure	Gain	Price
<b>LNA 28</b>	20-40	0.9 dB	20 dB	\$39.95
LNA 50	40-70	0.9 dB	20 dB	\$39.95
LNA 144	120-180	1.0 dB	18 dB	\$39.95
LNA 220	180-250	1.0 dB	17 dB	\$39.95
LNA 432	380-470	1.0 dB	18 dB	\$44.95


## ECONOMY PREAMPS

Our traditional preamos, proven in years of service. Over 20,000 in use throughout the world. Tuneable over narrow range. Specify exact freq. band needed. Gain 16-20 dB. NF = 2 dB or less. VHF units available 27 to 300 MHz. UHF units available 300 to 650 MHz.

- P30K, VHF Kit less case P30C, VHF Kit with case \$14.95 \$20.95 P30W, VHF Wired/Tested \$29.95 .
- P432K, UHF Kit less case \$18.95
- P432C, UHF Kit with case \$24.95 \$33.95
- P432W, UHF Wired/Tested

P432 also available in broadband version to cover 20-650 MHz without tuning. Same price as P432; add "B" to model #.

#### **HELICAL RESONATOR** PREAMPS

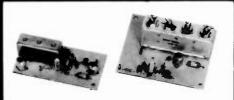

Our lab has developed a new line of low-noise receiver preamps with helical resonator filters built in. The combination of a low noise amplifier similar to the LNA series and the sharp selectivity of a 3 or 4 section helical resonator provides increased sensitivity while reducing intermod and cross-band interference in critical applications. See selectivity curves at right. Noise figure = 1 to 1.2 dB. Gain = 12 to 15 dB.

Model	Tuning Range	Price
HRA-144	143-150 MHz	\$49.95
HRA-220	213-233 MHz	\$49.95
HRA-432	420-450 MHz	\$59.95



Models to cover every practical rf & if range to listen to SSB, FM, ATV, etc. NF = 2 dB or less.

	Antenna Input Range	Receiver Output
VHF MODELS Kit \$44.95 Exec \$39.95 Wired \$59.95	28-32 50-52 50-54 144-146 145-147 144-144,4 146-148 144-148 220-222 220-224 222-226 220-224 222-224	144-148 28-30 144-148 28-30 27-27.4 28-30 50-54 28-30 144-148 144-148 50-54 28-30
UHF MODELS Kit \$54.95 Less Case \$49.95	432-434 435-437 432-436 432-436	28-30 28-30 144-148 50-54
Wired \$74.95	439.25	61.25

SCANNER CONVERTERS Copy 72-76, 135-144, 240-270, 400-420, or 806-894 MHz bands on any scanner. Wired/tested Only \$79.95.

SPECIAL FREQUENCY CONVERTERS made to custom order \$119.95. Call for details

#### SAVE A BUNDLE ON **VHF FM TRANSCEIVERS!**

FM-5 PC Board Kit - ONLY \$159.95 complete with controls, heatsink, etc. 10 Watts, 5 Channels, for 6M, 2M, or 220




For SSB, CW, ATV, FM, etc. Why pay big bucks for a multi mode rig for each band? Can be linked with receive converters for transceive. 2 watts output.

	Exciter Input Range	Antenna Output
For VHF.	28-30	144-146
	28-29	145-146
Model XV2	28-30	50-52
Kit \$79.95	27-27.4	144-144.4
Wired \$119.95	28-30	220-222
(Specify band)	50-54	220-224
(0000.)/	144-146	50-52
	50-54	144-148
	144-146	28-30
	28.30	432-434
For UHF,	28-30	435-437
Model XV4	50-54	432-436
Kit \$99.95	61.25	439.25
Wired \$149.95	144-148	432-436*
	*Add \$35 f	or 2M Input


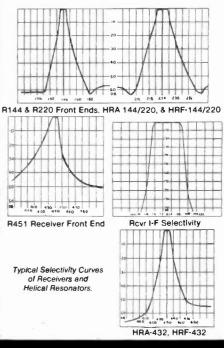
#### LOOK AT THESE **ATTRACTIVE CURVES!**



 Call or Write for FREE CATALOG (Send \$1.00 or 4 IRC'c for overseas mailing) Order by phone or mail ● Add \$2 S & H per order (Electronic answering service evenings & weekends) Use VISA, MASTERCARD, Check, or UPS COD.

65-W MOUL RD. • HILTON NY 14468 Phone: 716-392-9430 Hamtronics <sup>®</sup> is a registered trademark J 33

hamlronics, inc.

For years, Hamtronics • Modules have been used by individual hams and manufacturers to make repeaters. Now, in the Hamtronics tradition of top quality and superb value, we are proud to offer a complete repeater package.

#### JUST LOOK AT THESE PRICES!

Band	Kit	Wired/Tested
6M,2M,220	\$595	\$745
440	\$645	\$795

Both kit and wired units are complete with all parts, modules, hardware, and crystals.

#### CALL OR WRITE FOR COMPLETE DETAILS.

Also available for remote site linking/crossband & 10M.

#### **FEATURES:**

- SENSITIVITY SECOND TO NONE; TYPICALLY
   0.15 uV ON VHF, 0.2 uV ON UHF.
- SELECTIVITY THAT CAN'T BE BEAT! BOTH 8 POLE CRYSTAL FILTER & CERAMIC FILTER FOR GREATER THAN 100 dB AT ± 12KHZ. HELICAL RESONATOR FRONT ENDS. SEE R144, R220, AND R451 SPECS IN RECEIVER AD BELOW.
- OTHER GREAT RECEIVER FEATURES: FLUTTER-PROOF SQUELCH, AFC TO COMPENSATE FOR OFF-FREQ TRANSMITTERS, SEPARATE LOCAL SPEAKER AMPLIFIER & CONTROL.
- CLEAN, EASY-TUNE TRANSMITTER; UP TO 20 WATTS OUT.

## HIGH QUALITY MODULES FOR REPEATERS, LINKS, TELEMETRY, ETC.

#### INTRODUCING — NEW 1983 RECEIVERS



R144 Shown

- R144/R220 FM RCVRS for 2M or 220 MHz. 0.15uV sens.; 8 pole xtal filter & ceramic filter in i-f, helical resonator front end for exceptional selectivity (curves at left). AFC incl., xtal oven avail. Kit only \$119.95
- R451 FM RCVR Same but for uhf. Tuned line front end, 0.2 uV sens. Kit only \$119.95.
- R76 FM RCVR for 10M, 6M, 2M, 220, or commercial bands. As above, but w/o AFC or hel. res. Kits only \$109.95. Also avail w/4 pole filter, only \$94.95/ kit.
- R110 VHF AM RECEIVER kit for VHF aircraft band or ham bands. Only \$84.95.
- R110 UHF AM RECEIVER for UHF uses, including special 296 MHz model to hear SPACE SHUTTLE. Kit \$94.95.



 HELICAL RESONATOR FILTERS available separately on pcb w/connectors.

 HRF-144 for 143-150 MHz
 \$34.95

 HRF-220 for 213-233 MHz
 \$34.95

 HRF-432 for 420-450 MHz
 \$44.95

(See selectivity curves at left.)



- COR KITS With audio mixer and speaker amplifier. Only \$29.95.
- CWID KITS 158 bits, field programmable, clean audio. Only \$59.95.



• A16 RF TIGHT BOX Deep drawn alum. case with tight cover and no seams. 7 x 8 x 2 inches. Only \$18.00.




 T51 VHF FM EXCITER for 10M, 6M, 2M, 220 MHz or adjacent bands. 2 Watts continuous. Kits only \$54.95



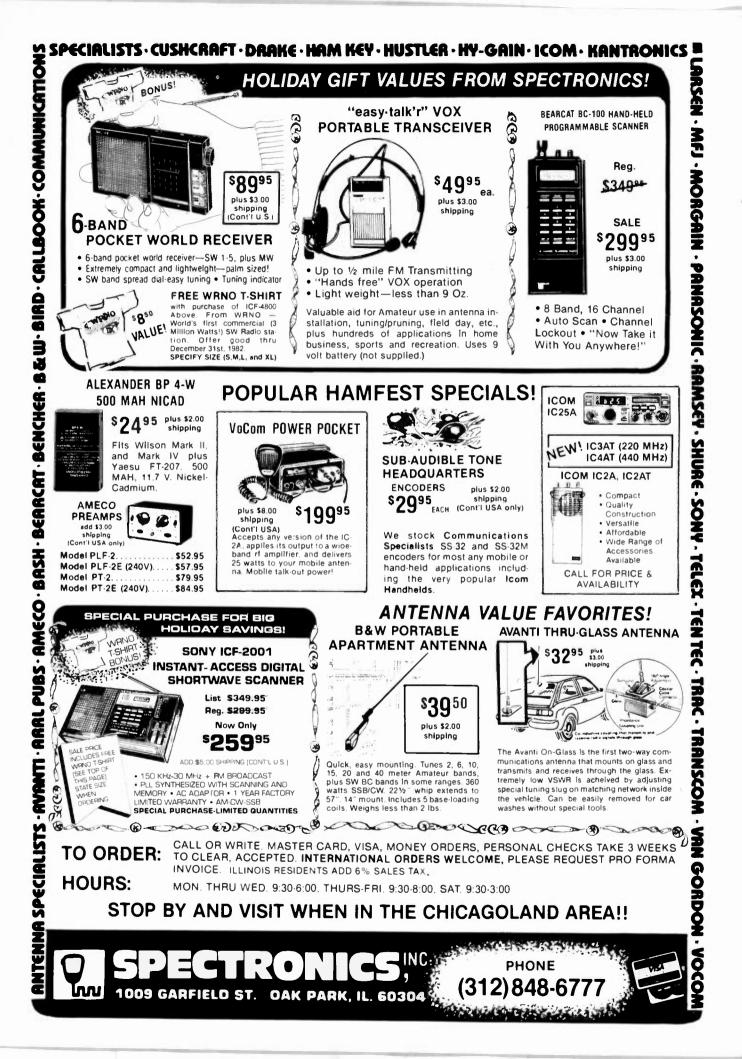- T451 UHF FM EXCITER 2 to 3 Watts on 450 ham band or adjacent. Kits only \$64.95.
- VHF & UHF LINEAR AMPLIFIERS. Use on either FM or SSB. Power levels from 10 to 45 Watts to go with exciters & xmtg converters. Kits from \$69.95.







RAMSEY ELECTRO		Wend	TS WARE	n of goodies too <b>716-586-3950</b>
HERE A	RE OLD FAV	E SEEN THES	D bypass. Items are limited BE BEFORE NOW EW ONES TOO. DN HOBBY.	Call Your Phone Order in Today TERMS: Satisfaction guaranteed or mon refunded. C.O.D. add \$2.00. Minimum ord \$6.00. Orders under \$10.00 add \$1.50. Add 5 for postage. insurance, handling. Overse add 15%. N.Y. residents add 7% tax.
FM MINI MIKE A super high performance less mike kitt Transmit signal up to 300 yards wi tional audio quality by m built in electret mike. Ki case, mike, on-off switch battery and super instruc- is the finest unit available FM-3 Kit FM-3 Kit	See mu: alive! 3 lights fli muslc. each for mid-rang tows. E vidually able and to 300 WC to 300 WC completion Completion Miterial Completion Miter	Organ sic come different cker with One light ach indi- adjust- drives up rus on ete klt, -1 organ zet klt, dr. cpo-1 sc. come the market Led Bi A great at ter which Runs on 3- ter which Runs der which Runs der which Runs der which Runs der	Video Modulator Kit by TV to video monitor. Super bile over ch. 4-6. Runs on 5- s std video signal Bestuniton Complete kit VD-1 \$7.95 Super Steuth A super sensitive amplifier alternately umbo LEDs arme badges. to any or as general pur pose amplifier. Full 2 W rms output, runs on 6 to 15 voits, uses 8-45 ohm speaker. Complete kit, BN-9 \$2.95 12 Vdc 1 wall out, 1 KHZ good for CPO. io Oscillator. Complete kit \$2.95	CLOCK KITS Your old favorites are here again. Over 7,000 Sold to Date. Be one of the gang and order yours today! Try your hand at building the finest looking clock on the market. Its satin finish anodized aluminum case looks great anywhere, while six .4" LED digits provide a highly readabl display. This is a complete kit, no extras needed, and it only takes 1-2 hours to assemble. Your choice of case colors: silver, gold, black (specify). Clock kit. 12/24 hour, DC-5 \$24.9 Clock with 10 min. ID timer, 12/24 hour, DC-10 \$29.9 Alarm clock, 12 hour only, DC-8 \$29.9 For wired and tested clocks add \$10.00 to kit price.
FM Wireless Mike Kit ransmits up to 300' to ny FM broadcast ra- ny FM broadcast ra- lo, uses any type of like. Runs on 3 to 9V. as added sensitive mi tage. M-1 kit \$3.95 FM-2	Type FM-2 ke preamp	hisper Light Kit esting kit, small mike sounds and converts light. The louder the he brighter the light. mike, controls up to uns on 110 VAC. mplete kit, WL-1 \$6.95	board. Features: 400- 5000 Hz adjustable range via 20 turn pot, voltage regu-	Car Clock The UN-KIT, only 5 solder connections Here's a super looking, rugged and accurate auto clock, which is a snap to build an install. Clock movement is completely assembled — you only solder 3 wires and switches, takes about 15 minutes' Display is bright green with automatic brightnese control photocell — assures you of a highly readable display, day or night. Comes in satin linish anodized aluminum case which can be attached 5 different ways using 2 side
Universal Timer I Provides the basic parts board required to provide of precision timing a generation. Uses 555 tim ncludes a range of parts iming needs. UT-5 Kit	s and PC e a source Produces nd pulse attention g ter IC and Can supp	ad Blaster Kit LOUD ear shattering and jetting siren like sound ify up to 15 watts of audio. Runs on 6-15 VDC \$4.95	Siren Kit Produces upward and downward wall characteristic of a police siren. 5 W peak audio output. runs on 3-15 volts. uses 3-45 ohm speaker. Complete kit. SM-3 \$2.95 Puns on 5-15 VOC Low current (2 Sma) 1 mm/month accuracy 18-7 Kit 18-95	12/24 hour, snoože, 24 hour alarm, 4     year calendar, baltery backup and lots more The super 7001 chip is used Size 5x4x2 inches. Complete kit, less case (not avaitable)     21.9     21.1     21
IC SPE		Resistor As Assortment of Popula watt. Cut lead for PC center, % leads. bac	s't ar values - ¼ Crystals mounting, ½" 3.579545 MHZ \$1.50	scrolling upper and lower case (optional) and has BS-232 and 20ma loop interfaces on board. Kit industry and the state of
LINEAR 01 5.35 80 5.5 81.50 85 81.50 85 81.00 85 81.00 85 81.00 85 81.00 85 81.00 87 81.25 41 10/32.00 45 8 5.50 900 8.50 914 82.95	74500 \$.44 7447 \$.66 7475 \$.57 7490 \$.50 74196 \$1.33 SPECIAL 11C90 \$15.00	Mini toggle SPDT Red Pushbuttons N.( Earphon: 3" leads. 6 ohm. good speakers. alarn clu Mini 8 ohm. Speaker	\$1.50         5 248800 MHZ         \$5.00           AC Adapters         Good for clocks, nicad chargers, all 110 VAC plug one end         one end           01 small tone         85 vdc @ 20 mA \$1.00         10 vAC plug one end           0cks, etc         16 vac @ 160mA \$2.50         12 vac @ 250mA \$1.00           000         12 vac @ 250mA \$1.00         50Hd State Buzzers	<ul> <li>instrument tuning, PL tones, etc. Multiplies audio UP in frequency, selectable x10 or x100, gives 01 HZ resolution with 1 sec. gate time! High sensitivity of 25 mv, 1 meg input z and bullt-in filtering gives great performance. Runs on 9V battery, all CMOS. PS-2 kit</li> <li>S29,95 PS-2 wired</li> <li>S39,95</li> <li>Kit, PS-1B</li> <li>S44,95</li> </ul>
CMOS CMOS CMOS CMOS 50 50 51 50 51 50 51 50 51 50 51 50 51 50 51 50 51 50 51 50 51 50 51 50 50 50 51 50 51 50 50 50 50 50 50 50 50 50 50 50 50 50	10116         \$ 1.2           7208         \$17.5           7207A         \$ 5.5           7216D         \$21.0           7107C         \$12.5           5315AB/G         \$ 2.9           7001         \$ 6.5	by type for radios, mike etc.           3 for \$2.00           Sing Tuned C           Small 3/16" Hex Slugs           3 turns.           CAPACITORS           TANTALUM           0:oped Ebory           1.5 uF 25V 3/\$1.00           1.8 uF 25V 3/\$1.00	output on 5-12 vdc at 10-30 mA, TTL           compatible         \$1.50           Colls         AC Outlet           s turned coll         Panel Mount with Leads           10 for \$1.00         USK CERAMIC           LLUMINUM         DISK CERAMIC           Uetrotytic         DI 16V disk 20151.00           00 uf 25V Arail 35:00         116V v           00 uf 25V 2015.00         100 115V 2015.00	30 Watt 2 mtr PWR AMP Simple Class C power amp features 8 times power gain. 1 W in for 8 out, 2 W in for 15 out, 4W in for 30 out. Max output of 35 W incredible value, complete with all parts, less case and T-R relay PA-1, 30 W pwr amp kit TR-1, RF sensed T-R relay kit E Rever Supply 51
\$1.35           \$399         \$1.75           READOUTS           ND 399 4° CC         \$1.00           ND 507510 5°CA         1.00           AN 72/HP730 33°CA         1.00           P 7651 43°CA         2.00	With info and specs         15/81 or           6 Hole Balun Beads         5/81 or           5 Ockets         8 Pin           10/\$2.00         16 Pin           16 Pin         10/\$2.00           16 Pin         10/\$2.00           24 Pin         4/\$2.00           28 Pin         4/\$2.00           40 Pin         3/\$2.00	22 uF 25V 3/\$1.00 til OC-DC Conve -5 vdc input prod -9 vd. -9 vdc produces -15 vdc 25K 20 Turn Trim Pot \$1 1K 20 Turn Trim Pot \$	0 uF 15V Radial 10/\$1.00         0.17 TeV         20/\$1.00           orter         Ceramic IF Filters         20/\$1.00           @ 35ma \$1.25         Ceramic IF Filters 7 kH2           0.00         State \$1.50         Filters 7 kH2           0.00         Filters 7 kH2         State \$1.50           0.00         Filters 7 kH2         State \$1.50           0.01         State \$1.50         State \$1.50	a. 10db gain 150 mbz     \$11.95       B-10db gain 150 mbz     \$11.95       RF actuated relay senses RF (1W) and closes DPDT relay. For RF sensed T-R relay TR-1 Kit \$6.95     Complete triple regulated pow supply provides variable 6 to 18 volts 200 ma and +5 at 1 Amp. Excellent loa regulation. good Illiering and smi size. Less transformers. requires 6.3 ra 1 A and 24 VCT. Complete kit, PS-3LT       OP-AMP Special
TRANSISTORS 13904 MPN C+F 15/81.00 13906 PNP C+F 15/81.00 14403 PNP C+F 15/81.00 14401 PNP C+F 15/81.00 4916 FET C+F 4/81.00 5401 PNP C+F 5/81.00 020 C+F 4/81.00	Diodes 5.1 V Zener 20/\$1.00 1N914 Type 50/\$1.00 1KV 2Amp 8/\$1.00 100V 1Amp 15/\$1.00 	Crystal mike cartridge	thick \$.75 Nini HG-174 Coax 10 ft. for \$1.00 Voli Battery Clips Nice quality clips 5 for \$1.00 % Rubber Grommets 10 for \$1.00 Connectore	723 5.50 7905 51.25 309K 51.15 7912 51.25
8027 C 1* Sincon \$1,50 15170 UNF NEN 3/\$2,00 www.rbs.NPN 40W 3/\$1,00 www.rbs.NPN 40W 3/1,00 PF 102/2N5484 \$50 PF 102/2N5484 \$50 UP 3906 Type T+R \$6/\$2,80 0055 \$60 2046 UJT \$1\$2,00	25 AMP 100V Bridge \$1.50 each Mini-Bridge 50V 1 AMP 2 for \$1.00	transistors diodes MICA ca m bag (100 pc) \$1.00 ig bag Leds - your choice. Mini Red, Jumbo Red, Mini Yellow, Jumbo Y	ps eic mÅ-1003 car clock module (300 pc) \$2.50 price .75 ea. please specify High Intensity Red. Illuminator Red. \$/\$1	Shrink Tubing Nubs Nice precut pces of shrink size 1" x %" shrink to %" Great for splices 50/\$1.00 Onto Isolators - 4N28 type

192 73 Magazine • December, 1982

# PROPAGATION

J. H. Nelson 4 Plymouth Dr. Whiting NJ 08759


EASTE	RN		UN	IT	EC	)	ST	A	ſξ	S	тс	):
GMT	: 00	02	04	06	08	10	12	14	16	18	20	22
ALASKA	14	7A	7	3A.	34	34	1 -	7	14	14	21	214
ARGENTINA	14	7	7B	7B	7B	7	14	14	_		21	21
AUSTRALIA	21	14	7B	7B	7B	7B	71	14E	144	21	21	21A
CANAL ZONE	7	7	7	7	7	7	7A	14	21	2 1A	21	14
ENGLAND	7	7	7	3A.	7	7B	14	140	214	144	78	2
HAWAII	21	7A	7B	7	7	7	7	78	14	144	21	214
INDIA	7B	7B	7B	7B	7B	7B	14	14A	14	7B	7B	78
JAPAN	144	14B	7B	7B	_7	7	7		78	78	14B	14
MEXICO	14	7	7	7	7	7	7	14	14A	21A	21A	21
PHILIPPINES	14A	7B	7B	7B	7B	7B	7B	7B	14B	14B	14B	14
PUERTO RICO	- 7A	7	7	7	7	7	78	148	21A	21A	21	14
SOUTH AFRICA	7A	7B	7B	7B	7B	7A	14	21	21A	21A	21	14A
U.S.S.A.	7	7	3A	3A	7B	7B	14	214	148	14	7B	7
WEST COAST	14A	7A	7	7	7	7	7	14	21	21A	21A	21
CENTF	<b>AL</b>		UN	IIT	ΕĽ		ST	'A'	ГΕ	S	TC	):
ALASKA	14A	7	7	3A.	AE	AL	7	7	7A	14	21	21A
ARGENTINA	14	14	7	7B	7B	7	7A	14	21	21A	21A	21
AUSTRALIA	21	14	7B	7B	7B	7B	7B	7B	14	14	21A	21A
CANAL ZONE	14	7	7	7	7	7	7	14	21	21A	21A	14
ENGLAND	7	7	7	3A	7	7	7B	14	21A	14	7B	7B
HAWAII	21A	7	7	7	7	7	7	7	14	21	21A	21A
INDIA	7B	7B	7B	78	7B	7B	7B	14B	14B.	7B	7R	78
JAPAN	21A	14	7B	7B.	7B	7	7	7	7B	7B	14	21
MEXICO	14	7	7	7	7	7	7	14	14A	21A	21A	21
PHILIPPINES	21	14	7B	7B	7B	7B	7B	7	7B	7B	14B	14
PUERTO RICO	14	7	7	7	7	7	7	_14	14A	21A	21A	14A
SOUTH AFRICA	7	7B	7B	7B	7B	7B	7	14	21A	21A	21	14
U. S. S. R.	1 7B	7	38	3A	7	7B	7B	14A	14A	14B	7B	7B
WESTE	RN		UN	IT	ED		ST	'A1	I	S	TC	):
ALASKA	21A	7A.	7	AL	JA	3A.	JA	AE	7	14	21	21
ARGENTINA	21A	14	7	7B	7B	7B	7B	14	21	21	21A	21A
AUSTRALIA	21A	14	7A	7	7B	7B	78	78	14	14	21	21A
CANAL ZONE	21	14	7	7	7	7	7	14	14	21A	21A	21
ENGLAND	7B	7	7	AE	7	7	7B	14B	21	14A	14B	7B
HAWAH	21A	14	14	7	7	7	7	7	14	21	21A	21A
INDIA	7B	14	7B	7B	7B	7B	7B	7B	7A	7B	7B	7B
JAPAN	21A	14	7B	78	7	_ 7	7	7	7	7B	14	21
MEXICO	21	14	7	7	7	7	7	7A	14	21A	21A	21
PHILIPPINES	21A	14	7B	78	7B	7B	7B	7B	7B	14	14	14
PUERTO RICO	21	7	7	7	7	7	7	14	21	21A	21A	21
SOUTH AFRICA	7	78	78	7B	7B	7B	7B	14	21	21A	21	14
U.S.S.R. EAST CDAST	7B	78	3B	3B	7B	7B	7B	7B	14	14B	7B	7B
EAST COAST	14A	7A	7	7	7	7	7	14	21	21A	21A	21

A = Next higher frequency may also be useful. B = Difficult circuit this period.
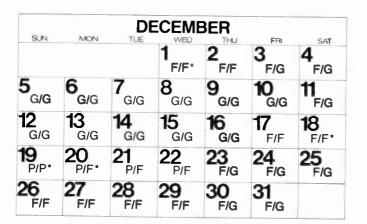
#### First letter = night waves. Second = day waves.

G = Good, F = Fair, P = Poor. \* = Chance of solar flares. # = Chance of aurora.

NOTE THAT NIGHT WAVE LETTER NOW COMES FIRST.



# DEALER DIRECTORY

#### Culver City CA

Jun's Electronics. 3919 Sepulveda Blvd., Culver City CA 90230, 390-8003. Tracks 463-1886 San Diego. 827-5732 (Reno NV).

#### Fontana CA

Complete lines ICOM, DenTron, Ten-Tec, Mirage, Cubic, Lunar, over 4000 electronic prod-uets for hobbyist, technician, esperimenter. Also Ch radio, landmobile, Fontana Electronics, 8628 Sierra Ave., Fontana CA 92335, 822-7710.

#### San Diego CA

We buy and sell Surplus Army Navy Electronics, also Terminated Material. What do you want to sell? Write for catalogue. Electronictown, Inc., 440-7th Avenue, PO Box 2048, San Diego CA 92112, 232-9379.

#### New Castle DE

Factory Authorized Dealer! Yaesn, ICOM, Ten-Tec, KDK, Azden, AEA, Kantronies, Santec, Fill Line of Accessories, N.S. assertiones, Santer Print, One mile off 1-95. Delaware Amateur Supply, 71 Meadow Road, New Castle DE 19720, 398-7798 328-7728

#### San Jose CA

Bay area's newest Amateur Badio store. New & used Amateur Badio sales & ervice. We feature Kenwond. ICOM. Azden, Yaesi, Ten Ter, San-tee & many more. Shaver Badio, Inc., 1378 So. Bascom Ave., San Jose CA 95128, 998-1103.

#### Smyrna GA

For your Kenwood, Yaesu, ICOM, Drake and other amateur needs, come to see ns. Britt's Two-Way Radio, 2506 N, Atlanta Rd., Smyrna GA 30080, 432-8006.

#### Preston ID

Ross WB7BYZ has the Largest Stock of Amateur Gear in the Intermountain West and the Best Prices. Call me for all your ham nexts. Ross Distributing, 78 So. State. Preston ID 83263. 852-0830.

#### **Terre Haute IN**

Your ham headquarters located in the heart of the midwest. Hoosier Electronics, Inc., 19 Meadows Center, P.O. Box 3300, Terre Haute IN 478003, 2020 arXiv 238-1456

#### **Baltimore MD**

buying lab grade test equipment HP, Tek, Always buying lab grade test equipment HP. Tek, Gr. L&N, Etc. Also buy microwave coaxial & waveguide HP, fxr, wavelline, etc. Prefer "K", "P", "B" but will consider larger wg too. Cadiseo 514 Ensor St., Balto, MD 21202, 685-1893

#### Littleton MA

The Reliable Ham Store Serving N.E. Full line of The Reliable Ham Store Serving N.E. Full line of ICOM & Kenvood Yaseu HTS, Drake, Daiwa, B&W accessories. Curtis & Trac keyers, Larsen, Hustler, Telex/Hy-Gain products. Mirage amps., Astron P.S., Alpha Della protectors, ARRI, & Kantronics instruction aids. Whistler radar detec-tors. Full line of coast fittings. TEL-COM Elec-tronic Coumunications 675 Great Rd. (Rt. 119), Littleton MA 01460, 617-486-3400/3040.

#### Ann Arbor MI

See us for products like Ten-Tec, R. L. Drake, Den Fron and many nore. Open Monday through Saturday, 0830 to 1730. WB8VCB, WB8UXD, WD80KN and W8RP behind the counter. Pur-chase Radio Supply, 327 E. Hoover Ave., Ann Ar-hor M1 48104, 668-8666.

#### Hudson NH

New England's Distributor and Authorized Ser-vice Center for all Major Amateur Lines. Tufts Radio Electronics, Inc., 61 Lowell Road, Hudson NH 03051, 883-5005.

#### Somerset NJ

New Jersey's only factory-authorized ICOM and Yaesu distributor. Large inventory of new and used specials. Most major brands in stock. Com-plete service and facilities. Radios Unlimited, 1760 Easton Avenue, P.O. Box 347, Somerset NJ 08873, 469-4599.

Buffalo NY WESTERN NEW YORK Niagara Frontier's only full stocking Amateur dealer. Also Shortwave, CB, Scanners, Marine, Commercial. Operating displays featuring Ken-wood and others. Towers, Antennas, Sales and Service. DX Communications, 3214 Transit Road, West Seneca NY, 668-8873.

#### Amsterdam NY **UPSTATE NEW YORK**

Kenwood, ICOM, Drake, plus many other lines, Amateur Dealer for over 35 years. Adirondack Ra-dio Supply, Inc., 185 West Main Street, Amster-dam NY 12010, 842-8350.

#### Syracuse-Rome-Utica NY

Featuring: Kenwood, Yaesu, ICOM, Drake, Ten-Tec, Swan, DenTron, Alpha, Robot, MFJ, Tem-po, Astron, KLM, Hy-Gain, Modey, Larsen, Cushcraft, Hustler, Min Products, You won't be disappointed with equipment/service. Radio World, Omeia County Airport-Terminal Build-ing, Oriskany NY 13424, 736-0184.

#### Columbus OH

The biggest and best Hum Store in the midwest featuring quality Kenwood products with work-ing displays. We sell only the best. Authorized Kenwood Service. Universal Amateur Radio Inc., 1220 Aida Dr., Revnoldsburg (Columbus) OH 43068, 866-4267.

#### Bend OR

Satellite TV. Known brands. Call today for more information and inquire about our dealer pro-gram. WESPERCOM. P.O. Box 7226, Bend OR 97708, 339-0996.

#### Philadelphia PA/ Camden NJ

Waveguide & Coaxial Microwave Components & Equipment, Laboratory Grade Test Instruments, Power Supplies, Buy, Sell & Trade all popular makes—HP, CR, FXR, ESI, Sorensen, Singer, etc. Lectronic Research Labs, 1423 Ferry Ave., Camden NJ 08104, 541-4200.

#### Scranton PA

ICOM, Bird, Cusheraft, Beckman, Fluke, Lar-Berger, Hulo, Custerart, Beckman, Fuike, Lar-sen, Hinstler, Antenna Specialists, Astron, Avanti, Belden, W2AU/V2VS, CDE, AEA, Vibroplex, Ham-Key, CES, Amphenol, Sony, Fanou/Couri-er, B&W, Ameco, Shure, LaRue Electronics, 1112 Grandview St., Scranton PA 18509, 343-2124.

#### San Antonio TX

Amateur, Commercial 2-way, Selling Antenna Specialists, Avanti, Azden, Bird, Hy-Gain, Stan-dard, Vibroplez, Midland, Henry, Cuskvraft, Dielectric, Hustler, ICOM, MFJ, Nye, Shure, Cubic, Tempo, Ten-Tec and others. Appliance & Equipment Co., Inc. 2317 Vance Jackson Road, San Antonio TX 78213, 734-7793.

#### DEALERS

Your company name and message can contain up to 25 words for as little as \$150 yearly (prepaid), or \$15 per month (prepaid quarterly). No mention of mail-order business or area code permitted. Directory text and payment must reach us 60 days in advance of publication. For example, advertising for the Feb. '83 issue must be in our hands by Dec. 1st. Mail to 73 Magazine, Peterborough NH 03458. ATTN: Nancy Ciampa.

# World Class Performance and Features

The FT-ONE is the culmination of an all-out design project by Yaesu's top engineering team. Working without the usual cost constraints, Yaesu's design group is proud to unveil the instrument they "always wanted to design," a revolutionary blend of computer and RF technology.

#### GENERAL COVERAGE, ALL SOLID STATE

The FT-ONE is a full-coverage all-mode transceiver, equipped for reception on any frequency between 150 kHz and 29.99 MHz, with transmit coverage on all nine present and proposed amateur bands. In countries where permitted, the FT-ONE may be programmed to transmit throughout the 1.8-29.99 MHz range.

#### **KEYBOARD FREQUENCY ENTRY**

Fully digitally synthesized, the FT-ONE uses a front panel keyboard for initial frequency entry. Frequency change is then accomplished via the main tuning dial or the pushbutton scanner, with tuning in either 10 Hz or 100 Hz steps possible. Truly the contester's dream, the FT-ONE permits extremely fine tuning and instantaneous band change with equal facility.

#### **DUAL VFO SYSTEM**

Ten digital VFO's with memory are provided, in conjunction with an A-B selection scheme that allows instant recall of any transmit, receive, or transceive frequency desired. For split-frequency operation, such as on 7 MHz SSB, the operator may select TX on VFO-A and RX on VFO-B, automatically storing the calling and listening frequencies for each pile-up. For net operations, a non-volatile memory board is available as an option, to eliminate the possibility of dumping memory.

#### **FULL CW BREAK-IN**

Recent advances in solid-state technology have finally made full CW break-in reliable enough to be incorporated into a Yaesu product. Now you can select traditional semi-break-in (for use with amplifiers not equipped for full break-in) or full high-speed break-in. When using amplifiers so equipped, the keyer output lead may be interrupted via a rear panel jack and routed to the break-in sequencing input on your amplifier.

#### SWITCHING REGULATOR POWER SUPPLY

Extremely compact and light in weight, the switching regulator power supply reduces substantially the space required to produce the operating voltages used in the FT-ONE. Highly efficient and uniquely stable, the switching regulator supply provides superb reliability in a field of design long neglected by amateur manufacturers.

#### ELITE CLASS PERFORMANCE FEATURES

In addition to the full break-in and superb receiver filters, Yaesu's design team packed the FT-ONE with subtle virtues that others might have overlooked. Rear panel jacks allow the use of both an external receiver and an independent receive antenna, such as a 160 meter Beverage. While scanning, automatic halting on a received signal may be programmed. . . perfect for watching a band for openings. If you're a DX-peditioner, an optional Curtis 8044 keyer board is available, so you won't need an external keyer that only wastes suitcase space. And if your amplifier fan is louder than it should be, there's even a microphone squelch (AMGC) to reduce background noise pickup between words and sentences!

#### **ONE YEAR FACTORY WARRANTY**

Because of the level of attention to design detail, parts selection, and factory quality control, your FT-ONE is backed by a one-year factory warranty for the original purchaser at retail. Prompt and meticulous attention to your warranty needs will be provided by our Ohio And California Service Centers. In addition, all units sold in the United States will be inspected and tested after clearing Customs, and will include a Service Manual in the puchase price.

#### GAIN/INTERCEPT OPTIMIZED RECEIVER FRONT END

Utilizing up-conversion with a first IF of 73 MHz, the FT-ONE RF amplifier stage uses push-pull power transistors configured to produce a typical output intercept of +40 dBm. The first mixer utilizes a diode ring module followed by a low noise post amp, for optimum noise figure consistent with modern day intercept requirements. The result is a receiver with a typical two-tone dynamic range well in excess of 95 dB (14 MHz, CW bandwidth). Additional gain tailoring is provided via a PIN diode attenuator controlled from the front panel.

#### FILTERS READY FOR COMPETITION

Three filter bandwidths are available for CW operation (two for FSK!), using optional 600 Hz or 300 Hz crystal filters. Filter insertion losses are equalized for constant IF gain. Both IF Shift and Variable Bandwidth are provided, and two CW filters may be cascaded, for competition-grade selectivity. For SSB work, the Variable Bandwidth feature eliminates the need for costly 1.5 kHz or 1.8 kHz filters, as any infermediate bandwidth may easily be programmed using the standard, cascaded SSB filters. To top it all off, a high-performance audio peak and notch filter is standard equipment.

#### EXPANDED OPERATING DISPLAYS

Digital displays for the VFO Frequency, memory channei, and RIT offset are provided for quick frequency identification. The large front panel meter provides easy viewing of transceiver operating parameters, including final transistor collector current, input DC voltage, FM discriminator center tuning, speech processor compression level, and forward/reflected relative power.

#### NOT AVAILABLE AS OPTIONS

It's hard to believe that other manufacturers still insist on making such essential items as a noise blanker or speech processor extra-cost options. We find that these are less expensive to incorporate and more reliable in operation when installed on our assembly line. No AC power supply is available as an option for the FT-ONE, either; it's equipped for operation from 100/110/117/200/220/234 volts AC, or 13.5 volts DC. And it goes without saying that there will not be an external VFO offered for the FT-ONE — we're confident that ten VFO's are quite enough !

Experience the FT-ONE in your Authorized Yaesu Dealer's showroom today. This may be the last Amateur transceiver you will ever own.



# FTEONE



# A Bold Adventure In Engineering!



YAESU ELECTRONICS CORPORATION, 6851 Walthall Way, Paramount, CA 90723 ● (213) 633-4007 Eastern Service Ctr., 9812 Princeton-Glendale Rd., Cincinnati, OH 45246 ● (513) 874-3100

# Watts to see...



# Big LCD, Big 45 W, Big 21 memories, compact.

# R-7950/7930

NEV

Outstanding features providing maximum ease of operation include a large, easyto-read (direct sunlight or dark) LCD display, 21 multi-function memories, automatic offset, programmable priority channel, memory and band scans, built-in lithium battery memory back-up, built-in 16-key autopatch encoder, and a choice of a hefty 45 watts output (TR-7950), or 25 watts output (TR-7930).

#### TR-7950/TR-7930 FEATURES:

 NEW, large, easy-to-read LCD digital display

Easy to read in direct sunlight or dark (back-lighted). Displays transmit/receive frequencies, memory channel, repeater offset, (+,S,-), sub-tone number (F-0, 1, 2, 3). tone, scan, and memory scan lock-out. Includes LED S/RF bar meter, and LED indicators for REVERSE. CENTER TUNING, PRIORITY, and ON AIR.

- 21 NEW, multi-function memory channels Stores frequency, repeater offset, and optional sub-tone channels. Memories I through 15 for simplex or ± 600 kHz offset. Memory pairs 16/17, and 18/19 are paired for non-standard repeater offset. Memories "A" and "B" set upper and lower scan limits, or for simplex or ± 600 kHz offset. In MEMORY mode, a circle of light appears around the memory selector knob. When the memory selector knob is rotated in either direction to channel 1. an audible "beep" will sound.
- Choice of 45 or 25 watts output The TR-7950 provides a hefty 45 watts output, while the TR-7930 features a more modest 25 watts. A HI/LOW power switch allows power reduction to approx. 5 watts.

- Long-life lithium battery memory back-up Programmable sub-tone channels Built-in lithium battery has an estimated 5 year life.
- Automatic offset

The microprocessor is pre-programmed for simplex or ± 600 kHz offset, in accordance with the 2 meter band plan. "OS" key allows manual change in offset.

- Programmable priority alert The PRIORITY channel may be programmed in any of the 21 memories. With ALERT switch "ON," a dual "beep" sounds when a signal is present on the PRIORITY channel. An OPER switch allows an easy move to the PRIORITY channel.
- Programmable memory scan lock-out "LO" key for programming scan to skip selected memory channels, without erasing the memory
- Programmable band-scan width The lower limit may be programmed into memory "A," and the upper limit into memory "B."
- Center stop during band-scan, with indicator Stops in center of channel during band-
- scan, with center tuning indicator. Scan resume selectable Scan stops on busy channel. Selectable automatic time resume-scan (approx. 5 sec., adjustable), or carrier operated resume-scan. A scan delay of approx. 1.5 seconds built-in.
- Scan control using up/down microphone Momentarily pressing UP or DOWN button on microphone tunes one step in the selected direction, on memory or on 5-kHz step tuning. Holding the button for about 2 seconds starts UP or DOWN automatic scan action. Scan start also possible using "SC" key on keyboard. Scan may be cancelled by momentarily pressing the PTT switch, or by pressing both UP/DOWN buttons simultaneously

- Optional TU-79 3 frequency sub-tone unit provides keyboard selectable sub-tone channels. which may be stored in memory
- Built-in 16-key autopatch, with monitor The keyboard functions as a 16-key autopatch encoder during transmit. DTMF tones appear in the speaker output when a key is pressed during transmit.
- Front panel keyboard control Used for selecting frequency. offset, programming memories, controlling scan, and autopatch encode. Keyboard lighting is provided.
- Extended frequency coverage Covers 142.000-148.995 MHz. in 5-kHz steps.
- Repeater reverse switch Locking-type switch, with indicator.
- "Beeper" amplified through speaker
- Compact, lightweight design
- Easy-to-install adjustable-angle mobile mounting bracket

#### **Optional accessories:**

- TU-79 three frequency tone unit. KPS-12 fixed-station power supply
- for TR-7950 KPS-7A fixed-station power supply
- for TR-7930.
- · SP-40 compact mobile speaker.

More information on the TR-7950 and TR-7930 is available from all authorized dealers of Trio-Kenwood Communications. 1111 West Walnut Street. Compton. California 90220



Specifications and prices are subject to change without notice or obligation.