

Morse Maniac's Keyboard Project

W5LFL Orbits Page 95

Are MSOs For You?

Supply With A Surprise!

Micro Help For Hams:

QSLs—Page 46

LOGS—Page 58

Rcvr Specs—Page 36


Nets—Page 62

1983 Contest Results: 40/75/160m, RTTY

0

Amateur Radio's Technical Journal

A Wayne Green Publication

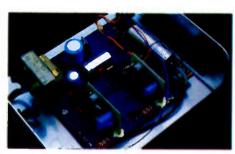

Scanner Squelch—84

Construct the Callsign Power Supply

	KA10	QΖ μ	out	toge	ther	aesi	thetic	25	an
that	gives	you	mo	re th	nan g	good			
								/ A 1	10

The Magical Audio Filter

8	A variable-frequency notch filter plus a								
	A variable-frequency notch filter plus a peaking circuit will do wonders for								
your	reception. And this project will almost								
build	litself	1							

Keyboard Your Way to Happiness

	If h	appin	ess is	perfect e heave	Moi	rse, the	n this
	proj	ect i	s pure	e heave	n.	Special	con-
struc	tion	tips	make	putting	git	togeth	er as
much	n fun	as us	ing it.			N	7AGK

Reveal the Receiver Behind the Specs

0	Here's	a	program	that	will	make	sense	
	Here's a program that will make out of all those numbers.						N6RY	36

Terrific Top-Band Conversions

X	Jump	up	to	160	meters drought.	and	beat	the	
	comin	g s	uns	pot	drought.	Sur	plus	gear	
will g	et you	the	re c	hear	oly		K	QLL	40

CardSoft:

The Transportable QSL Generator

1	If y	our	machine	runs	Basic,	it	can	run	
40	this	prog	gram	Basic, it can run WB5LLM				46	

The Six-Meter Vfo That Won't Quit

	This hybrid has the best It's as steady as a rock	of both worlds.
. \	It's as steady as a rock	and has broad-
band	tuning	N7APE

Foolproof Logging

I	KL7GRF	designed a	a logbook	program
40	that any	TRS-80 ow	ner can us	e. And it
mana	ages your	OSLs. too.		.KL7GRF

The Program No Net Control Should Be Without

1	Eve	ery ne	t gene	lists. Ke	ts. Keep yours up RS-80 Basic pro-		
40	to	date	with	this	TRS-80	Basic	pro-
gram)					WA4	VLE

The World's Cheapest Modification

X	All you meters	ne	ed to	put	the	FI	-101	on	30
- \	meters	is t	hre e	piec	es o	of	wire.	WI	nai
coul	d be che	ane	r tha	n tha	it?				

... WB9DDF, WØUR 70

....KØVKH 86

A Two-Tone Squelch to Solve Your Scanner Woes

X	Selec	tive lister squelch	ning is	the k	ey to	succ	ess.
	This	squelch	will	help	you	cut	the
chatt	er				١	WAR	REV

Electronic Mail Comes of Age

		0	
These	mailboxes may	be thousands o	f mile:
away.	but they're insta	antly accessible	

Octal Ingenuity

lt's	an	old	radio	. You	can'	t fi	nd a	a re
plac	cem	ent	tube.	Now	what	do	you	do
							MA/C	9512





6m Vfo-48

20

48

58

62

Never Say Die-6
Gift
Subscriptions-67
73 International — 76
Social Events—92
Ham Help—
93, 107, 132
Satellites—95
Dr. Digital—96
Review—97
Contests—101

DX—109
Fun!—110
Reader
Service—114
New Products—115
Awards—117
Letters—119
RTTY Loop—138
Dealer
Directory—146
Propagation—146

ICOM IC-25H

45 Watts of Compact Power



45 watts / green LED readout / compact size / touchtone® scanning
microphone / 2"H x 5½"W x
8%"D / 2 VFO's / 5 memories
make the IC-25H the best 2 meter mobile value on the market.



New Green LED. Easier to read In bright sunlight, and not glaring at night, the IC-25A's new readout provides good visibility under all conditions.

Dual VFO's. Dual VFO's give

an extra stored frequency for

scanning (memory scan scans 5 memories plus 2 VFO's) and each VFO has a different tuning rate for easy QSY.

5 Memories. Instant access to most frequencies: VFO A information is transferred to the selected memory by pushing the write button

Priority Channel. Any memory channel may be monitored for activity on a sample basls, every 5 seconds, without disruption of a QSO conducted on a VFO frequency.

HM14 Microphone. Smaller

and lighter . . . the HM14 microphone provides a 16 button touchtone® pad as well as up and down scan buttons, adding easy frequency control of the radio and repeater access tones.



Watts / 2 meters

The IC-25A is a very compact 2 meter FM mobile. Only 2"H x 5½"W x 7"D, the IC-25A features a green LED readout which is visible in any lighting condition, a touchtone® /

scanning microphone and 25 watts of output.

These standard features have made the IC-25A the most popular 2 meter mobile on the market.

Scanning. Pushing the S/S button initiates the scan circuitry. With the mode switch In a memory position the unit will scan all 5 memories plus the 2 VFO frequencies. With the mode switch in a VFO position, the unit will scan the entire band or the portion of the band defined by memories 1 and 2.





5-STORE BUYING POWER

Unlike some retailers, when Ham Radio Outlet guarantees satisfaction there'll be no question. YOU CAN COUNT ON IT!

in action!

BIG VALUE COMBINATIONS

TS-930S



with Antenna Tuner Plus

3 Free Bonus Items

- 1) SP-930 Speaker.
- 2) MC-60A microphone.
- 3) YK-88C-1 filter.

REG. \$2029 VALUE

A \$230 SAVING

TW-4000A FM "Dual Bander"





Buy a TW 4000A for

and select two of the following items absolutely free!

- 1) VS-1 Voice Synthesizer. \$39.95 value.
- 2) TU-4C sub-audible tone generator. \$39.95 value.
- 3) MA-4000 Duo-band Mobile Antenna. \$44.95 value.

TS-430S



Buy a TS 430S for **\$899.95**

and select your free package from among the following three groups:

- 1) MB-430, FM-430, YK-88A \$119.85 value.
- or 2) MB-430. MC-42S. YK-88-SN.\$112.85 value.
- or 3) Ham Radio Outlet \$90 CASH REBATE.

PLUS FREE SHIPMENT UPS (Surface) ALL COMBOS

NEW!!

ICOM



\$1399 PRICE INCLUDES: FREE

PS-35 POWER SUPPLY (Mounts internally) REG. \$160 VALUE



W-51 LE \$799 W-36 ALL FOR PRICE LM-470D CALL FOR PRICE

SERVING HAMS BETTER.

North...south...east...west.

personalized

service

Bob Ferrero,W6RJ Jim Rafferty, N6RJ

other well known hams

give you courteous,

KT-34A SALE \$299

KT-34XA

SALE \$459

PRICES ARE FOR CALIF. PLEASE INQUIRE



FT-708R **PRICES ON HAND-HELDS** and all YAESU ITEMS.



B-3016 REG. \$239.95 **SALE \$199.95**

B-1016 REG. \$279.95 **SALE \$249.95**

B-108 REG. \$179.95 \$159.95 SALE B-235 REG. \$89.95

\$79.95

SHIPMENT CONTINENTAL U.S.A.

ON MOST ITEMS THAT CAN BE SHIPPED UPS BROWN. THERE ARE SOME EXCEPTIONS IN ALPHA TRI-EX AND KLM

FREE 854-6046 PHONE

9:30AM to 5:30PM PACIFIC TIME.

OVER-THE-COUNTER, 10AM to 5:30PM. MONDAY THROUGH SATURDAY

CALIFORNIA CUSTOMERS PLEASE PHONE OR VISIT LISTED STORES.

ANAHEIM, CA 92801 2620 W. La Palma, (714) 761-3033 (213) 860-2040 Between Disneyland & Knott's Berry Farm

BURLINGAME. CA 94010 999 Howard Ave., (415) 342-5757 5 miles south on 101 from S.F. Airport.





OAKLAND, CA 94609

2811 Telegraph Ave., (415) 451-5757

AEA • ALLIANCE • ALPHA • AMECO • AMPHENOL • ARRL • ASTRON AVANTI * BELOON * BENCHER * BERK-TEC * BIRO * B & W BUTTERNUT * CALLBOOK * CDE * COLLINS * CURTIS * CUSHCRAFT

Hwy 24 Downtown. Left 27th off-ramp.

SAN DIEGO, CA 92123

5375 Kearny Villa Road (619) 560-4900 Hwy 163 & Clairemont Mesa Blvd.

DAIWA • DRAKE • DX EDGE • DX ENGINEERING • EIMAC MUSTLER • MYGAIN • ICOM • J. W. MILLER • KANTRONICS KENWOOD • KLM • LARSEN • LUNAR • METZ • MFJ • MICRO-LOG


VAN NUYS, CA 91401 6265 Sepulveda Blvd., (213) 988-2212 San Diego Fwy at Victory Blvd.

NI-PRODUCTS . MIRAGE . NYE . PALOMAR . ROBOT . ROHN SHURE . SIGNAL-ONE . TEMPO . TEN-TEC . TRISTAO . VOCOM YAESU and many more

Prices, specifications, descriptions subject to change without notice. Calif. residents please add sales tax



1984 CALLBOOKS

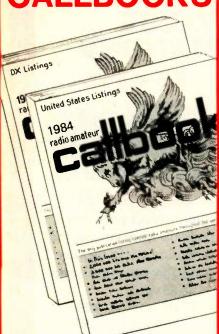

Order today!
NEW 1984
RADIO AMATEUR CALLBOOKS
READY DECEMBER 1st!

Known throughout the world for accuracy, the 1984 Callbooks are a better value than ever before. The U.S. Callbook contains over 430,000 listings; the Foreign Callbook has over 400,000. More than 75,000 changes have been made in each edition since last year. Special features include call changes, Silent Keys, census of amateur licenses, world-wide QSL bureaus, international postal rates, prefixes of the world, and much more. You can't beat this value! Order your 1984 Callbooks now for earliest delivery.

Each Shipping Total

DU.S. Callbook \$19.95 \$3.05 \$23.00

D Foreign Callbook 18.95 3.05 22.00

Order both books at the same time for \$41.95 including shipping within the USA.

Order from your dealer or directly from the publisher. Foreign residents add \$4.55 for shipping. Illinois residents add 5% sales tax.

Keep your 1984 Callbooks up to date.

The U.S. and Foreign Supplements contain all activity for the previous three months including new licenses. Available from the publisher in sets of three (March 1, June 1, and September 1) for only \$12.00 per set including shipping. Specify U.S. or Foreign Supplements when ordering. Illinois residents add 5% sales tax. Offer void after November 1, 1984.



925 Sherwood Dr., Box 247 Lake Bluff, IL 60044, USA

Tel: (312) 234-6600




\$15 DTMF DECODER \$15

The LJM2RK decoder kit converts your receiver into a special receiver or control. When a user-selected timetone combination is received, the output provides a relay control for activating speakers or other devices.

INPUT: Audio from transceiver, scanner, etc. OUTPUT: SPST (N.O.) relay.

FEATURES: Single or dual tones adjustable over the 16 digit. Touch Tone range. Adjustable response time. Relay output. Manual or auto reset. Single tone ON latching with different single tone reset OFF. Operates on 12VDC. Interfacing of multiple boards for multi-digit sequential activation and reset.

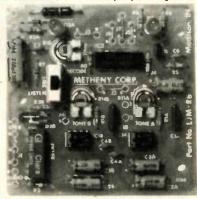APPLICATIONS: Call-up system • Repeater or commercial controls • Etc. limited only to your imagination •



Actual Size 3"x3" - Shown Assembled

LJM2RK decoder kit includes all component, relay, and P.C. Board. . . . \$15 plus \$1.50 shipping.

LJM2RC enclosure kit includes molded case, speaker, input cable. . . .\$5 pius \$1.50 shipping.

For information and to order write:

THE METHENY CORPORATION
204 Sunrise Drive, Madison, IN 47250 > 205

The Computer Specialty Store Inc.

428 Central Ave. Johnstown, PA 15905 AN AUTHORIZED KANTRONICS DEALER

The Interface by Kantronics for:

Apple TI 99 Atari TRS-80C Commodore 64 VIC-20

Announcing also, Amtorsoft for the C-64, VIC-20, and Apple.

COMPLETE SALES & SERVICE.







r 11:

Call for package deals or "one of a kind"; 1-814-535-2432

Software • Hardware • Telecommunication

INFO

Manuscripts

Contributions in the form of manuscripts with drawings and/or photographs are welcome and will be considered for possible publication. We can assume no responsibility for loss or damage to any material. Please enclose a stamped, self-addressed envelope with each submission. Payment for the use of any unsolicited material will be made upon acceptance. All contributions should be directed to the 73 editorial offices. "How to Write for 73" guidelines are available upon request.

Editorial Offices:

Pine Street
Peterborough NH 03458
Phone: 603-924-9471

Advertising Offices:

Peterborough NH 03458 Phone: 603-924-7138

Circulation Offices:

Eim Street Peterborough NH 03458 Phone: 603-924-9471

Subscription Rates

In the United States and Possessions One Year (12 issues) \$25.00 Two Years (24 issues) \$38.00 Three Years (36 issues) \$53.00

Elsewhere:

Canada and Mexico—\$27.97/1 year only, U.S. funds. Foreign surface mail—\$44.97/1 year only, U.S. funds drawn on U.S. bank. Foreign alr mail—please inquire.

To subscribe, renew or change an address:

Write to 73, Subscription Department, PO Box 931, Farmingdale NY 11737. For renewals and changes of address include the address label from your most recent issue of 73. For gift subscriptions, include your name and address as well as those of gift recipients.

Subscription problem or question:

Write to 73, Subscription Department, PO Box 931, Farmingdale NY 11737, Please include an address label.

73: Amateur Radio's Technical Journal (ISSN 0745-080X) is published monthly by Wayne Green, Inc., 80 Pine Street, Peterborough NH 03458. Second class postage paid at Peterborough NH 03458 and at additional mailing offices. Entire contents copyright 9 1983, Wayne Green, Inc. All rights reserved. No part of this publication may be reprinted or otherwise reproduced without written permission from the publisher. Microfilm Edition—University Microfilm, Ann Arbor MI 48106. Postmaster Send address changes to 73, Subscription Services, PO Box 931, Farmingdale NY 11737.

PLANE TALK . . .



The TR-720 contains the latest microprocessing technology which is responsible for its amazing size (6.6" x 2.6" x 1.5") and weight (1.2 lb.). Features include 3 memory channels, 720 COM and 200 NAV channel operation, twist-off rechargeable battery pack, and multi-function LED to indicate receive signal or low battery. A full set of standard accessories including rechargeable battery, AC and DC chargers, case, flex antenna, and earphone put you straight on the air. Optional accessories are available.

The TR-720 increases the operating safety of balloons, sailplanes, and ultralights by providing communication with ground crews or ATC. It allows receipt of IFR clearances prior to engine start and is indispensible for search and rescue, forest fire fighting,

or law enforcement to coordinate aircraft operations. Sport aircraft, homebuilts, or experimental planes (even those without electrical systems) can now have reliable 720 channel communication. But perhaps the best advantage is the peace of mind that comes from having an emergency back-up transceiver.

The TR-720 comes with a full 1 year warranty with guaranteed 72 hour turnaround and is available for immediate delivery factory direct or from your local Avionics Dealer or FBO.

The TR-720, rugged, reliable communications in the palm of your hand.

\$795.00 Aircraft Owners Net FCC and DOC Approved







426 West Taft Avenue Orange, CA 92665-4296 (800) 854-0547 (714) 998-3021

W2NSD/1 NEVER SAY DIE

editorial by Wayne Green



WHAT'S GREEN **REALLY UP TO?**

A few years ago, I wrote in my editorials in 73 my prediction that microcomputers would one day grow to the size of the car industry. I also pointed out that this growth was a golden opportunity for those interested in getting rich.

Based on that concept, I first started Byte magazine as a vehicle to help that industry to speed up its growth (Byte was the largest consumer magazine in America last year) and then 80 Micro to help entrepreneurs get a piece of the action (the third largest consumer magazine in America last year).

The computer field is still in its early growth stages, so there are lots of opportunities yet to make fortunes there. You'll see me starting even more magazines to help it grow and deal entrepreneurs in on the action.

One of the benefits to me of amateur radio has been the interest I've gained in travel. Talking with hams in virtually every country of the world has interested me in getting to personally see their countries and meet them in person. And in each country I visit, I can't help but compare their quality of life with that we enjoy in America.

Most of the Third-World countries have it pretty tough. They are prisoners of poverty, ignorance, and, as a result, tyrannical governments. We've tried throwing money at these countries, but that is divided up among the tyrants, providing little for the people. The answer, of course, is to provide them with education. In the long run, this will change the patterns of poverty.

That, my friends, is Green's

Goal. It is my intention to provide the entire world with a highquality, low-cost education, using high-technology techniques. I'll make this prediction: Education is going to be a marketable product and the industry manufacturing and selling this product is not only going to be larger than the car industry, but also larger than OPEC.

Being one of the early ones to see what is coming, I'm in a position both to help this come about and also to profit from it, as I did with computers. Indeed, I think several thousand brainwashed ARRL members were pretty surprised when they heard that I'd sold my magazines for \$60 million. That didn't tie in very well with the League theory that I'm a blundering idiot who is destroying amateur ra-

You know, I got started in hamming 45 years ago and it is depressing to me to get on the air and see how little things have changed in all that time. About the only significant changes are sideband and repeaters (both of which I helped make happen with my magazines). It's getting time for some major changes to bring amateur radio into our high-tech age. Perhaps, from that viewpoint, it is time to "destroy" amateur radio-and that seems to be the ARRL position. I want hamming to progress, to be able to provide the quality of communications modern technology allows, and not be stuck fifty years in the past, held to our ancient Morse-code traditions inflexibly.

Continued on page 108



QSL OF THE MONTH

The high-tech city: That's Rochester, New York, and this winning QSL card from the Rochester Amateur Radio Association reflects Rochester's claim to fame. According to the Department of Commerce, this city leads the nation in high-technology exports, and RARA is proud of amateur radio's contributions to the community. There is no doubt that the scene makes for a striking QSL card. It represents the way an area can be linked, not only by streets and sidewalks, but also by the communications network provided by ham

To enter your QSL card in 73's QSL of the Month contest, put it in an envelope with your choice of books from 73's Radio Bookshop and mail it to 73, Pine Street, Peterborough NH 03458, Attn: QSL of the Month. Entries not in envelopes or without a book choice will not be considered.

PUBLISHER/EOITOR Wayne Green W2NSD/1

ASSISTANT PUBLISHER/EDITOR Jeff DeTray WB8BTH

MANAGING EOITOR John Burnett

ASST. MANAGING EOITOR Susan Philbrick

EDITORIAL ASSISTANTS

Nancy Noyd Richard Phenix Steve Jewett

TECHNICAL EDITOR Avery L Jenkins WB8JLG

ASSISTANT TO THE PRESIDENT

Matthew Smith KA1IEI

ASSOCIATES

Robert Baker WB2GFE John Edwards KI2U Bill Gosney KE7C Chod Harris VP2ML Dr. Marc Leavey WA3AJR

J. H. Nelson Bill Pasternak WA6ITF Peter Stark K2OAW Robert Swirsky AF2M

PRODUCTION MANAGER

Nancy Salmor

ASST. PRODUCTION

David Wozmai ADVERTISING GRAPHICS

MANAGER

Scott W. Philbrick DESIGN DIRECTOR

Christine Destrempes PRODUCTION

Patricia Bradley Linda Drew

Michael Ford Marjorie Gillies

Donna Hartwell

Alfred Huston

Taylor Morris Kimberly Nadeau

Paula Ramsey

Lynne Simonson

Kenneth Sutcliffe

Theresa Verville

Robert M. Villeneuve Karen Wozmał

PHOTOGRAPHY

Sandra Dukette

Nathaniel Haynes

Laurie Jennison Sturdy Thomas

TYPESETTING

Darlene Bailey Prem Krishna Gongaju

Lynn Haines

Cynthia Letourneau

Len Lorette Debbie Nutting

Lindy Palmisano

Heidi Thomas Sue Weller

GENERAL MANAGERVICE PRESIDENT

CONTROLLERAVICE PRESIDENT

Roger J. Murphy

ACCOUNTING MANAGER

Knud Keller KV4GG/1 CIRCULATION MANAGER

Patricia Ferrante

603-924-9471

BULK SALES MANAGER Ginnie Boudrieau

1-(800)-343-0728

ADVERTISING

603-924-7138 Jim Gray W1XU, Mgr.

Nancy Clampa, Asst. Mgr. Ross Kenyon KA1GAV

Cornella Taylor, Office Coordinator

FM "Dual-Bander."



2 m & 70 cm in single compact package, LCD, 25 W, optional voice synthesizer.

KENWOOD's TW-4000A FM "Dual-Bander" provides new versatility in VHF and UHF operations, uniquely combining 2 m and 70 cm FM functions in a single compact package.

TW-4000A FEATURES:

- 2 m and 70 cm FM in a Compact Package Covers the 2 m band (142.000-148.995 MHz), including certain MARS and CAP frequencies, plus the 70 cm FM band (440.000-449.995 MHz), all in a single compact package. Only 6-3/8 (161)W x 2-3/8 (60)H x 8-9/16 (217)D inches (mm). and 4.4 lbs. (2.0 kg.)
- · Large, Easy-to-Read LCD Display A green, multi-function back-lighted LCD display for better visibility. Indicates frequency, memory channel, repeater offset, "S" or "RF" level, VFO A/B, scan, busy, and "ON AIR." Dimmer switch.
- · 25 Watts RF Power on 2 m/70 cm. Hi/Lo power switch.
- Optional "Voice Synthesizer Unit" Installs inside the TW-4000A. Voice announces frequency, band, VFO A or B. repeater offset, and memory channel
- Front Panel Illumination

• 10 Memories with Offset Recall and Lithium Battery Backup

Stores frequency, band, and repeater offset. Memory 0 stores receive and transmit frequencies independently for odd repeater offsets, or cross-band operation.

- Programmable Memory Scan Programmable to scan all memories, or only 2 m or 70 cm memories. Also may be programmed to skip channels
- Band Scan in Selected 1-MHz Segments Scans within the chosen 1-MHz segment (ie., 144,000-144,995 or 440,000-440,995). etc.). The scanning direction may be reversed by pressing either the "UP" or "DOWN" buttons at the control of t "DOWN" buttons on the microphone.
- Priority Watch Function Unit switches to memory 1 for 1 second each 10 seconds, to monitor the activity on the priority channel.
- Common Channel Scan Memory 8 and 9 are alternately scanned every 5 seconds. Either channel may be recalled instantly.
- Dual Digital VFO's Selectable 5-kHz or 10-kHz for 2 m, and 5-kHz or 25-kHz for 70 cm. Depress "UP" or "DOWN" key on the front panel for band change in 1-MHz steps.
- 16-Key Autopatch UP/DOWN Microphone (Supplied)
- Repeater Reverse Switch

· High Performance Receiver/Transmitter GaAs FET RF amplifiers on both 2 m and 70 cm, high performance MCF's in the 1st

IF section, provide high receive sensitivity and excellent dynamic range. The high reliability RF power modules assure clean and dependable transmissions on either band.

- · Rugged Die-cast Chassis
- Optional Two-Frequency CTCSS Encoder Easily mounted inside the radio, allows DIP switch programming of two different tone frequencies, for 2 m and 70 cm.
- · "BEEPER" sounds through speaker.
- · Easy-to-Install mobile mount
- TW-4000A accessories:
- VS-1 Voice Synthesizer
 TU-4C Two-Frequency Programmable CTCSS Encoder
- KPS-7A Fixed station power supply
- · SP-40 Compact mobile speaker

More information on the TW-4000A and TS-780 is available from all authorized dealers of Trio-Kenwood Communications. 1111 West Walnut Street, Compton, California 90220.

pacesetter in amateur radio

All mode "Dual-Bander"

S=780

2 m & 70 cm all mode. dual digital VFO's, 10 memories, scan, IF shift...

TS-780 FEATURES:

- · USB, LSB, CW. FM all mode, covering the 2 m band (144.000-148.000 MHz) and the middle 70 cm band (430.000-440.000 MHz). UP/DOWN band switch.
- Dual digital VFO's with normal/ tight drag switch. VFO steps in 20-Hz, 200-Hz, 5-kHz, or 12.5-kHz, plus "FM CH" channel-

ized tuning. Split (cross) frequency operation possible. F. LOCK switch provided.

- · 10 memories include band and frequency data, backed up by internal batteries (not supplied). Battery life exceeds one year. Memories 9 and 10 for priority instant recall
- Band scan, with selectable 0.5, 1, 3, 5, and 10-MHz scan bandwidth.
- Memory scan selectable for all memories, or 2 m or 70 cm only.
- · IF shift circuit rejects adjacent interference.
- High sensitivity and wide dynamic range • 7-digit


fluorescent tube digital display • 10 watt RF output • 2 m ±600kHzTX offset switch with reverse switch . Tone switch for optional TU-4C two frequency tone


encoder unit . VOX and semi break-in CW built-in . FM centertune meter . Noise blanker for SSB. CW.



Blueprint for Success

THE INTERFACE

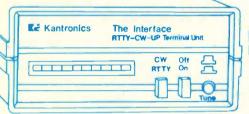

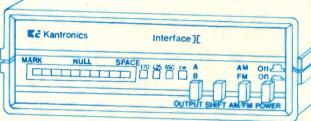

THE INTERFACE 1

Kantronics

TITLE: THE INTERFACE - INTERFACE 1 [PROPOSAL

THE INTERFACE is the original Kantronics terminal unit that broke through the barrier of multi-computer compatibility. THE INTERFACE is an amateur modem for transceiver-to-computer communication. With THE INTER-FACE and Hamsoft or Hamtext for your computer you can send and receive Morse Code, Radioteletype, and ASCII. THE INTERFACE is also compatible with our new software for AMTOR communication, AMTORSOFT. THE INTERFACE is our most popular unit combining active filtering, easy tuning, six-computer compatibility, and low price for an unbeatable pack-

Suggested Retail 169.95

INTERFACE II is the new Kantronics transceiver-to-computer interface. INTERFACE II features a new highly sensitive front end with mark and space filtering and a unique new tuning system. Even the most discerning operator will be surprised with the INTERFACE II's ability to dig out signals in poor band conditions, and our new tuning system even displays signal fading.

X-Y scope outputs and dual interface outputs for VHF and HF connections make INTERFACE 11 compatible with almost any shack. All three standard shifts are selectable and INTERFACE 11 is compatible with the industry standard Kantronics programs: Hamsoft, Hamtext, and Amtorsoft. Step up to state of the art in computer-amateur communications with INTERFACE 11.

Suggested Retail 1269.9

For more information see your Kantronics dealer, or contact:

**EXAMPLE AND CONTROL OF THE PROPERTY OF THE PRO

KANTRONICS SOFTWARE Hamsoft,™ Hamtext,™ and Amtorsoft™

MORSE 00:00:00
TRANSMIT SPEED 25
RECEIVE SPEED 28

ENJOY YOUR MEAL AND
WE'LL TALK TO YOU
REAL SOON ... 73'S
WA5RGU
WEATHER HERE IS WARM TODAY
WITH LOTS OF SUN...XYL SAYS
TIME FOR DINNER SO 73'S WØXI

Kantronics has led the amateur community in software and total computer communications systems with our original program, HAMSOFT. With five-computer compatibility and reasonable prices HAMSOFT has become the industry standard. HAMSOFT includes split screen display, type ahead buffer, message ports, and complete keyboard control for Morse Code, Radioteletype, and ASCII communications. With THE INTERFACE or INTERFACE 11, HAMSOFT can make any of five computers a complete amateur communications terminal. All programs are on a ROM board, except the Apple diskette.

VIC-20 - \$49.95, ATARI - \$49.95, APPLE - \$29.95, TRS-80C - \$59.95, TI-99/4A - \$99.95

00:00:00

PROGRAM OPTIONS

A. RETURN TO BASIC

B. EDIT MESSAGE PORTS

C. SAVE MESSAGE PORTS

D. LOAD MESSAGE PORTS

E. SET XMIT BUFF SIZE

F. EDIT HOLDING BUFFER

G. SAVE HOLDING BUFFER

H. LOAD HOLDING BUFFER

I. SET TIME

00:00:00 KANTRONICS AMTORSOFT COPYRIGHT 29 JUNE 1983

CHOOSE
S (AMTOR SLAVE)
M (AMTOR MASTER)
L (AMTOR LISTENER)
P (PROGRAM OPTIONS)
T (T/R OPTIONS)

On January 27th, 1983, AMTOR, Amateur RadioTeletype Over Radio, became a legal mode for the amateur service. AMTOR is an essentially error-free radioteletype form of communication. AMTORSOFT, Kantronics' newest software package, gives your computer the ability to become an AMTOR communications terminal when used with The Interface or interface 1 I. AMTORSOFT is currently available for the Apple, VIC-20, and COM-64 computers. AMTORSOFT brings you the newest in computer-amateur communications at an affordable price.

Suggested Retail*89.95

For more information see your Kantronics dealer, or contact: **E&** Kantronics 1202 E. 23rd Street Lawrence, KS 66044

Construct the Callsign Power Supply

KA1QZ put together aesthetics and electronics to produce a power supply that gives you more than good regulation.

imited funds along with the hassles of apartment living and QRO hamming forced me to explore QRPp operation as a last-ditch attempt to preserve some form of my ham radio hobby. A friend's donation of a Ten-Tec PM-3 5-Watt CW transceiver and a spare 12-V battery put me on the air while keeping QRM from my neighbors to a minimum. Eventually the battery expired, and I made the decision to dust off the soldering iron and build a small power supply rather than spend precious allowance for expensive batteries. I also wanted to have a power supply that would provide the necessary power for an Argonaut which I eventually hope to acquire.

Visions of state-of-the-art ham equipment with its fancy lights and whistles inspired me to construct something similar in terms of a functional conversation piece for my QRP station. Apart from a power supply to power the rig, few ham shacks can be found without a clock, so a digitalclock module seemed the ideal complement for the supply. Much to my delight, I found that the clock chips currently on the market were inexpensive enough to allow me to purchase a pair: one a 12-hour format and the other a 24-hour format. Thus, I could have the 12-hour clock set to local time and the other to UTC. Finally, a late-night flash of inspiration led me to complete the power supply/ clock console with a callsign that lights up when the supply is on. Combining all into a Ten-Tec-style enclosure resulted in a real conversation piece as well as a multi-functional addition to the QRP station. Most important, the whole project did not bankrupt me and required only a few evenings worth of time.

The Power Supply

The power supply was designed to provide an adequate amount of power at minimum cost for QRPp rigs in the 5-to-6-Watt class with some reserve for 12-V station accessories. The PM-3 requires 480 mA in the transmit mode, but the Argonaut draws 1 Amp in the transmit mode. The ac power supply available for the Argonaut delivers 13 V ± 0.5 V at 1.2 A. I decided that a 13-V supply capable of delivering 1.5 A to 2.0 A output current would be desirable.

The next step was to select an IC regulator. I ruled out the 78XX series of fixedvoltage regulators. Even though these regulators can be used for current output in excess of their guaranteed 1-A rating, it is not recommended operating these regulators at or above their

maximum current rating for extended periods of time.

To my knowledge, there are no readily-obtainable 2-A IC regulators. Going to the 3-Amp and above class of regulators was more money than I was willing to part with, especially when that much current capacity wasn't really needed. To utilize the full current capacity of these large regulators would also require a larger, more expensive transformer. A good compromise for this project was reached by using the LM317 variable-voltage regulator.

The LM317 is a 3-terminal positive voltage regulator with a guaranteed current output of 1.5 A. The output voltage is variable from 1.2 V to 37 V. Two external resistors are used to set the output voltage (see Fig. 1). The regulator output voltage is given by the equation: Vout = Vref(1 + R2/R1)+ ladiR2.

Vref refers to the 1.25-V reference voltage generated between the output and the adjustment terminal (terminal 2). The constant voltage across R1 causes a constant current to flow through output resistor R2, giving the desired output voltage. For most purposes, the last term in the equation can be ignored since the ladj term has units

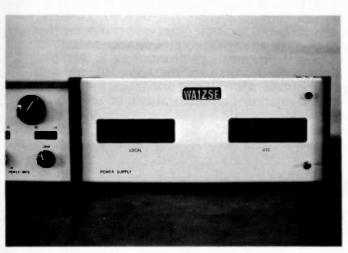


Photo A.

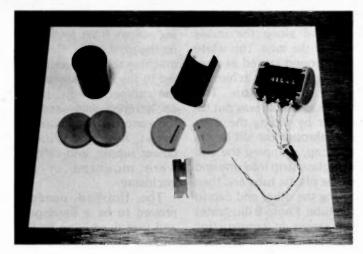


Photo B. Construction of callsign housing using 35mm plastic film cans. Completed unit is shown on the right. (My call then was WA1ZSE.)

of microamps making the entire term insignificantly small.1 The equation can be arranged to allow for easier calculation of the R2 value. given a desired output voltage and assuming R1 = 220Ohms-an arbitrary but common value: R2=(Vo-1.25)220/1.25.

For a 13-V output in my supply, R2 = 2068 Ohms. A slightly higher value of R2 (say an additional 100 Ohms) may be necessary to offset the tolerance error of the resistors if an exact output of 13 V is desired. However, none of these values is critical as long as Vo lies within the 12-14-V range re-


expensive TO-3 version of this regulator, the TO-220

3047, Scottsdale AZ 85257.

package would work equally well provided it is mounted to an adequate heat sink.

The complete power supply circuit is shown in Fig. 1. Regulator circuit protection is provided by the current-limiting feature of the LM317. Overvoltage protection of the load is provided by the "crowbar" circuit.

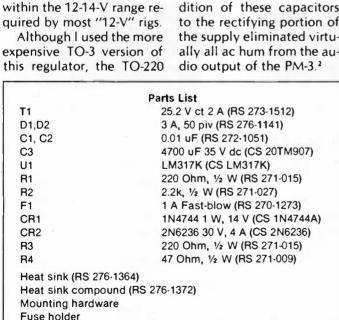Since direct-conversion receivers like the one in the PM-3 are prone to picking up hum from an ac power supply, 0.01-µF capacitors were inserted parallel to each rectifier diode. The addition of these capacitors to the rectifying portion of the supply eliminated virtually all ac hum from the audio output of the PM-3.2



Note: RS = Radio Shack; CS = Circuit Specialists, PO Box

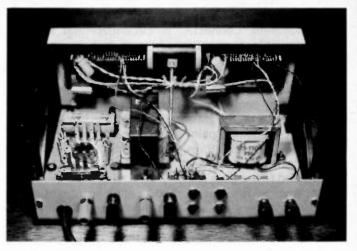


Photo C. Assembly of components into enclosure. Transformer on right powers both clock chips. ORP power supply is on the left. Two sets of binding posts allow for connection of QRP rig and an additional 12-V station accessory. Knobs at far right on the back panel are clock-dimmer pots (optional). The callsign housing in the center background is held in position by a 4" × 1/8"-diameter machine screw anchored to the bottom of the enclosure. An L-shaped bracket attaches the callsign housing to the mounting screw.

The Clocks

The digital-clock circuits used in this project were the MA1008A (National MM5385 12-hour-format chip) and the MA1008D (National MM5386 24-hourformat chip). Both clock chips were purchased new (close-out specials from Digital Research Parts) for under ten dollars for the pair. They came ready to use and required only a 12-V, 1.2-A transformer (which powered both chips) and momentary SPST switches (for setting the clocks) to be put into operation

These chips were purchased in 1980, so their current availability and price may be different. However, there are a number of other parts-supply sources offering similar clock chips at very reasonable prices.3

Flea markets and ham conventions are other possible sources.

The Callsign

The basic idea for the callsign came from the Heathkit SB-104 I once owned back in the preneighbor days. The lighted callsign in that rig consists of peel-and-stick letter blocks mounted on a transparent panel behind a red plexiglas™ filter. Each block has a black opaque background except for the outline of the letter which is clear to allow light to pass through when the panel light is turned on. It's a nice effect, and to my knowledge is a féature found only on the SB-104.

A $2'' \times 1/2''$ piece of window glass was obtained from the local hardware store as scrap. A dry transfer press-on letter set (#M12

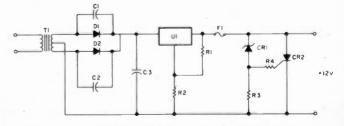


Fig. 1. Power supply schematic.

made by the C-Thru Ruler Co., Bloomfield, Connecticut, obtainable from stationery or art supply stores) was used to apply the call letters to the glass. The call letters were centered in both directions on the glass strip. Black enamel paint (obtainable at hobby stores selling modeling supplies) was applied to the glass surface using a fine-tipped brush. All of the glass surface surrounding the outlines of the letters was painted black. Two or three coats were necessary to ensure that no light could pass through the glass except through the letter outlines. By holding the glass up to a strong light after each coat of paint had dried, it was possible to see if a sufficient amount of paint had been applied to block out stray light.

A plastic 35mm film canister was used as the callsign housing. The end of the plastic film can was removed with a razor blade. A circumferential strip of about 1/4 inch was removed lengthwise from the plastic can creating an incomplete cylinder. The end cap from this can and the end cap from another film can were fitted to the tube. The caps were then cut flush with tube edges.

Next, slits were cut in the end caps corresponding to the width and thickness of the glass strip. Illumination of the callsign was achieved by three 12-V bulbs (Radio Shack 272-1141) which were mounted equally spaced along the bottom surface of the tube. Holes were punched in the tube and the bulbs were snug-fitted. (Three small bulbs were used rather than a single, larger bulb in order to ensure even illumination of the callsign and to ensure that the bulbs remained hidden from view.)

A small piece of white

poster paper was cut and wrapped along the inside wall of the tube. This white background served as a reflector to aid in achieving even illumination. The whole assembly was put together by sliding the glass strip through the slit in one end cap, snapping the end cap/glass strip into one end of the plastic tube and then fitting the other end cap to the tube. Photo B illustrates the stages in constructing the callsign housing.

The Enclosure

The enclosure used in this project was a Ten-Tec Model MG-10 (43/16"HX $9\frac{1}{6}$ "W × $6\frac{1}{6}$ "D) obtained at a flea market. Any type of metal cabinet with similar dimensions would do equally as well. The cutouts for the clocks and the callsign light were done using square Greenlee tools. The edges of the resulting holes were rounded with a file. In order to eliminate unsightly clock-chip mounting screws from protruding on the front panel, flathead machine screws were epoxied to the inside surface of the cabinet. Finally, presson lettering was used for the various labels. Photo C shows how the clocks, power supply, and callsign were mounted in the enclosure.

The finished product proved to be a handsome and useful addition to the station. Low cost and construction simplicity are two of the most attractive features of this project.

References

- 1. National Semiconductor Voltage Regulator Handbook, 1980. 2. Anderson, J. R., "Direct Conversion Receiver Hum," in "Hints and Kinks," QST, August,
- 3. Other sources for the clock chips include: Jameco Electronics, 1355 Shoreway Road, Belmont CA 94002 and Circuit Specialists, PO Box 3047, Scottsdale AZ 85257.

1-800-821-732

KENWOOD TS-430S



- All Bands
- Dual VFO's
- General Coverage
- 8 Memories
- 200 Watts

ICOM IC-740



- 1.8 to 30 MHZ
- Super Receiver
- 200 Watts Selectable IF/PBT

YAESU -NEW FT-77



- Extremely Compact 3.5 to 30 MHZ
- 200 Watts Inexpensive

ANTENNA SALE

CUSHO	RAFT	HY-GAIN T	OWERS	BUTTERN	UT	HY-GAIN	1
A-3	\$175	HG37SS	\$ 649	HF6V	\$109	TH5MK2S	\$318
A-4	\$226	HG52SS	\$ 919	KLM		TH7DXS	\$378
R-3	\$226	HG54HD	\$1429	KT34A	\$299	TH3MK3S	\$218
AV-5	\$ 90	HG70HD	\$2339	KT34XA	\$449	TH3JRS	\$158
214-FB	\$ 69	HG50MTS	\$ 749	144-148LBA	\$ 69	TH2MKS	\$138
32-19	\$ 82					18AVT/WS	\$ 94
40-2CD	\$260	LARSEN	CALL	AEA	CALL	18HTS	\$335
ANIXTER	R-MARK					V25	\$ 37
HW-3 TRIBAND MOBILE \$34		Call "TOLL FI	REE" For All	Antennas & Acces	sories	EXPLORER 14	\$275

2900 N.W. VIVION RD. / KANSAS CITY, MISSOURI 64150 / 816-741-8118 -258

HAM RADIO CENTER

IS GOING OUT FOR BUSINESS WITH

CASH DISCOUNTS AND TERRIFIC TRADE-INS

CALL TOLL-FREE 1-800-325-3636

- FOR CASH PRICES
- FOR TRADE-IN QUOTE
- FOR USED EQUIPMENT PRICES

WE FEATURE-DRAKE-ICOM-KENWOOD-TEN-TEC-YAESU WE TRADE ON NEW OR USED EQUIPMENT



8340-42 Olive Blvd. ● P.O. Box 28271 ● St. Louis, MO 63132





The Magical Audio Filter

A variable-frequency notch filter plus a peaking circuit will do wonders for your reception.

And this project will almost build itself.

Audio filtering is a well-known process for improving receiver selectivity and many articles have

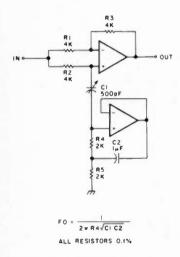


Fig. 1. Original circuit.

been written on the subject. Because I have been in the process of building a directconversion receiver. I have been most interested in the subject. However, in order to further improve the receiver, I wanted more than the usual passband type of filter. Since one of the receiver modes is CW, I wanted a notch filter with a variable frequency and a variable-frequency peaking circuit. The notch filter could also be used on SSB reception to reject heterodynes from AM stations. Some of the requirements that I wanted for the notch filter were:

• a high Q (so the bandwidth at the 3-dB point of

the notch frequency was approximately 200 Hz with a rejection of greater than 20 dR)

- the capability of shifting the notch frequency from 500 to 3 kHz
- a minimum number of parts.

The Frequency-Notching Circuit

Most articles I'd seen on this subject showed at least three or four operational amplifiers plus a multitude of resistors and capacitors and therefore did not satisfy my third requirement.

One day, I accidentally ran across a number of circuits in a National Semiconductor Linear Applications

Manual. The circuit that interested me the most was the one providing variable frequency-notching using a variable capacitor. This circuit was constructed on a proto board and performed quite well, but the frequency range was limited by the maximum value of the capacitor. The basic circuit is shown in Fig. 1. The major drawback of this circuit was the large physical size of the capacitor as compared with the rest of the circuit.

Looking at the formula for the notch frequency (Fig. 1), one can see that the frequency is a function of R4, C1, and C2. The frequency varies directly as R4 and by the square root of C1 and

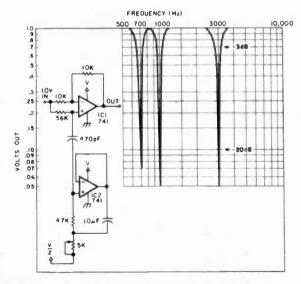


Fig. 2. Notch circuit.

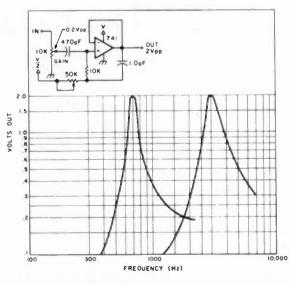


Fig. 3. Peaking circuit.

C2. Thus, if the resistor is doubled in value, the frequency doubles. Doubling the capacitors only gives 1.4 times the change. I decided to build the circuit with R4 variable and again results were very good. The frequency-range requirements were met and the rejection was greater than 20 dB. It did have one problem that was also experienced with the variable-capacitor circuit. In order to achieve maximum rejection at the high end vs. the low end, R3 had to be varied. Experimenting further, I found that if R5 were varied and R3 and R4 were properly chosen, only one control was necessary. Almost equal rejection could then be achieved across the whole range. A typical response is shown in Fig. 2.

The Peaking Circuit

Since the above circuit was rather novel (there is no signal inversion from input to output at the off null point), I started to look at voltages at various points with an oscilloscope. To my amazement, I found that when the output was going to null on IC1, the output was peaking on IC2. Eureka! - Here was the second circuit I was looking for. To accomplish peaking, only IC2 was needed. This circuit was constructed and the results are shown in Fig. 3. R_{in} is necessary to prevent saturation of the amplifier. The gain of this stage is about 10-therefore the input must be less than 0.5 volts. The power supply used was plus and minus 8 volts to be equivalent to the supply to be used in the final construction.

It will be noticed that there is an additional resistor that can be switched in or out in the final circuit. When the resistor is in, the peak is broadened and the circuit can be used on AM or SSB to modify the speech characteristics of the trans-

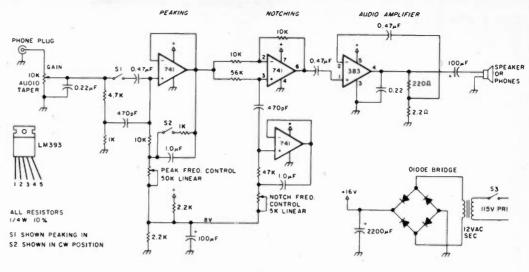


Fig. 4

mitted signal being received. It can reduce the low frequencies and accentuate the frequencies that transmit the spectrum that contains the most intelligence. It also reduces higher frequencies, thereby reducing background noise.

Combination Notch and Peaking Circuit

Fig. 4 shows the final circuit combining the two circuits. The circuit was constructed on a perfboard using wire-wrap sockets. The perfboard is mounted in a Radio Shack box with 1-inch spacers. Both the LM383 and the transformer are mounted to the box. One note of caution-the 0.22uF capacitor on the output to ground on the LM383 should be mounted on the device terminals. The input cable, the output jack, and the 115-V-ac input all come in on one end of the box and the potentiometers mount on top.


For some reason, not many articles ever use perf-boards and wire-wrap sockets. PC boards should be used for rf work, but the perfboard does very well for audio frequencies. The nice thing about wire-wrap circuits is that if you make a mistake, it can be corrected or modified easily. The following are some hints on building with a perfboard and wire-wrap sockets.

	Parts List	
Quantity	Part	R. S. part#
3	LM741	276-007
1	LM383	276-703
1	Phone plug	274-1536
1	Phone jack	274-252
1	50k linear pot	271-1716
1	10k audio taper pot	271-1723
1	5k linear pot	271-1714
2	470-pF capacitors	272-125
3	1.0-uF capacitors	272-996
2	100-uF capacitors	272-1016
2	0.22-uF capacitors	272-1070
1	2200-uF capacitor	272-1020
1	12-V-ac transformer	273-1505
3	8-pin DIP w-w sockets	276-1988
1	SPST switch pwr	275-602
2	SPST switches	271-612
1	Chassis box	270-238
1	Line cord	278-1255
3	Knobs	Your choice
1	Perfboard	276-1395
1 pkg	Push-in terminals	270-1392
1	Wire-wrap tool	276-1570
3	10k 1/4-W resistors	
2	2.2k 1/4-W resistors	
1	56k 1/4-W resistor	
1	47k 1/4 -W resistor	
1	4.7k 1/4-W resistor	
2	1k 1/4 -W resistors	
1	220-Ohm 1/4-W resistor	
1	2.2-Ohm 1/4-W resistor	
1	Bridge rectifier	276-1151
	Wire-wrap wire	Your choice
		of colors
	Misc. hardware	

- 1. Make a Xerox® copy of the schematic; every time you put in a wire, mark it down. This is especially helpful should you put the project away and come back to it later.
- 2. Using a marking pen on the wire side of the board, indicate which pin is #1 for

the IC sockets. Remember that the numbering on the wire side is opposite to that on top.

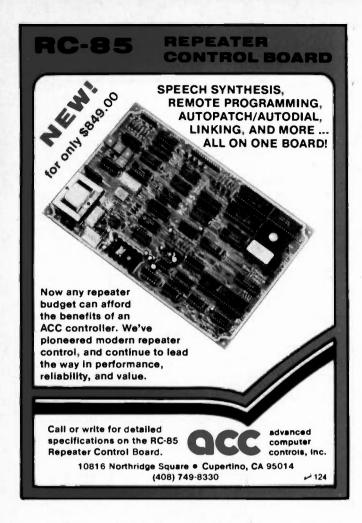3. I use model-airplane cement to hold the IC sockets in place. If you want to reuse the perfboard, this type of glue allows the socket to be easily removed.



Clean the board with acetone when the sockets are removed.

- 4. It is also helpful to use different colors of wire for different parts of the circuitry.
- 5. Push-in teminals (Radio Shack #270-1392) are used to mount the resistors and capacitors. The wire-wrap wires are soldered to these terminals on the wire side of

the board. (A special tool is available to insert these terminals but is not available from Radio Shack. Longnose pliers can be used but are nowhere near as satisfactory as the tool.)

6. Mount the components when the push-in terminals are in place so as not to lose track of which terminal goes with which component.

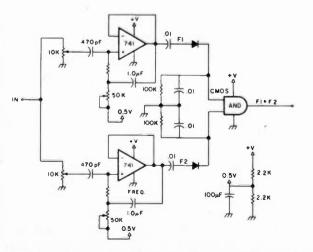


Fig. 5. Another application for peaking-circuit decoder.

7. Wire-wrapping is done with a manual tool to conveniently allow interchanging of wire colors. If you have never used a wire-wrap tool. the operation is very simple. In learning, the best way is to measure the distance between the two points to be wired and add 114 inch if wire-wrap to wire-wrap, add 7/8 inch for wire-wrap to teminal, and add 1/2 inch for terminal to terminal. For good measure, add on about 1/2 inch so the wire will not be too tight. Strip both ends 5/8 inch for wire-wrapping and ¼ inch for terminals. Stripping is done with a special tool provided with the wire-wrap tool. The bare wire is inserted into the end of the wire-wrap tool with the wire entering the smallest hole on the end of the tool. Place the tool over the terminal post to be wrapped and rotate the tool in a clockwise direction for about ten turns. The connection is now made. If you make a mistake, a tool is available to rotate in the opposite direction to remove the wire.

Circuit Operation

When the project is finished, the input cable can be plugged into the phone jack of any receiver and the output to either a speaker or headphones. Set S1., the peaking-circuit switch, to OUT. Tune in a CW signal and adjust the signal frequency to give about an 800-Hz tone. Throw \$1 to IN and turn the peaking control to a point where the maximum audio is heard. The first thing you will notice with the peaking switch in is the reduction in noise. As you approach the peaking point, the signal will increase greatly in volume. Of course, if some other frequency suits you better than 800 Hz, that is the listener's choice.

The next thing to check is the notch filter. With the

800-Hz signal coming in, adjust the notch control to a point where the signal drops in volume. On some CW signals with key clicks and thumps, the 800-Hz signal will drop out but the clicks and thumps will still be there. I have found that it is easier to remove a heterodyne with the peaking circuit out; then bring in the peaking circuit, producing an even greater reduction in the interfering signal. When the notch circuit is not used. the pot should be set to the low-frequency end.

Frequency-Selection Circuit

Another circuit is shown in Fig. 5. Although I have not tried this circuit, it could be of interest. I have tried LM567s in frequency-selective circuits, but noise spikes seem to get through, creating an unwanted output signal. A case in point is my garage-door opener. This unit had a vibrating-reed type of frequency detector and I replaced it with a pair of LM567s. Every once in awhile the door will open without a command due to noise. After I finish this project, reworking the opener will be my next project.


Conclusion

The peaking/notching circuit should be a worthwhile addition to any receiver for a parts cost of about \$35 excluding the wire-wrap tool and wire that can be used on many other projects. It is a simple but effective way to gain a bit more selectivity that should improve any old receiver and maybe some of the newer ones.

A list of parts is given with all but one being available from Radio Shack. Of course, most hams will have many of these parts available in their junk boxes, bringing the overall cost down.

References

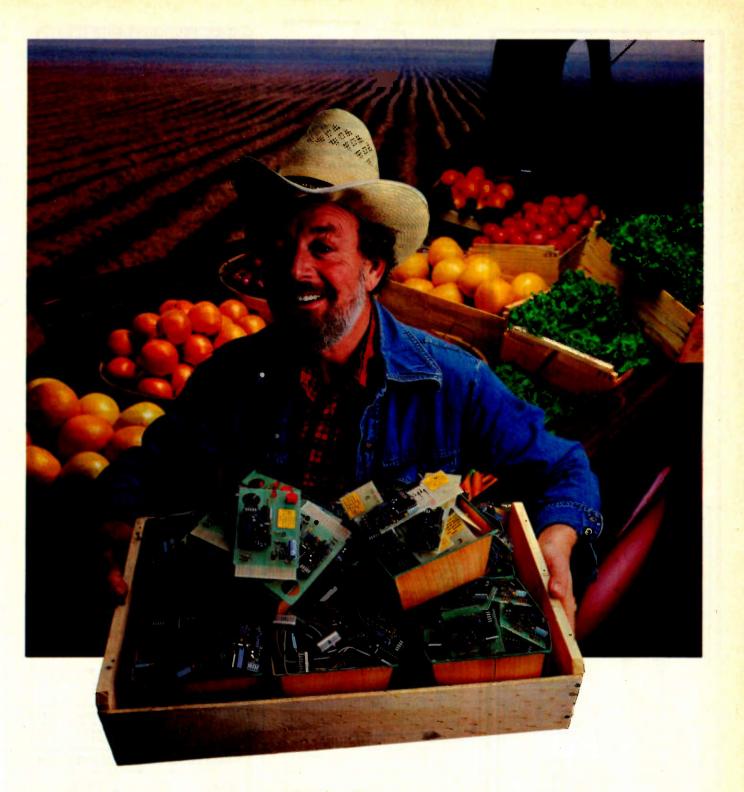1. National Semiconductor Linear Applications Manual, January, 1972, page AN 31-14.



Plug-In Bumper Crop

From the fertile grounds of Communications Specialists comes our fresh harvest of direct CTCSS plug-ins to spade through valuable installation time and cultivate profits. They're available for most popular mobiles, portables, and repeater panels, and all incorporate our industry standard, field programmable TS-32.

Just call our sales or engineering departments toll free from anywhere in the USA (including California) and reap what we've sown.



426 West Taft Avenue, Orange, CA 92667 714/998-3021 Entire USA 800/854-0547



HUSTLER RELIABLE ALL BAND HF **PERFORMANCÉ**

Hustler's new 6-BTV sixband trap vertical fixed station antenna offers all band operation with unmatched convenience. The 6-BTV offers 10, 15, 20, 30, 40, and 75/80 meter coverage with excellent bandwidth and low VSWR. Its durable heavy gauge aluminum construction with fiberglass trap forms and stainless steel hardware ensures long reliability. Thirty meter kits (3O-MTK)

for 4-BTV and 5-BTV

are also



Don't miss our 30 meter excitement. HUSTLER -STILL THE STANDARD OF PERFORMANCE.



Kissimmee, Florida 32741 An CHINATRON Company

812-422-0231



HAM SHACK Evensville, IN 47711

808 N. Main

Prices and Availability Subject to Change

CP-1 New Computer Interface	****
AMT 1 Amtor Terminel	.\$189.00
CP-1 New Computer Interface AMT-1 Amtor Terminal 144 Isopole Antenna	40.00
ALLIANCE HD73 (10.7 sq ft) Rotator U-110 Small Rotator ASTRON	
HD73 (10.7 sq ft) Rotator	\$99.00
U-110 Small Rotator	49.00
O-110 Small Hotator ASTRON RSTA 5-7 Amp Power Supply RS12A 9-12 Amp Power Supply RS20A 18-20 Amp Power Supply RS20M 18-20 Amp Mmeter RS35A 25-35 Amp RS35M 75-35 Amp Wmeter	\$40.00
PS124 0.12 Amp Power Supply	69.00
RS20A 16-20 Amp Power Supply	89.00
RS20M 16-20 Amp w/meter	109.00
RS35A 25-35 Amp	135.00
RS35A 25-35 Amp w/meter . RS5DA 37-50 Amp . RS5DA 37-50 Amp w/meter .	149.00
RS50A 37-50 Amp	199.00
B&W	225.00
Continuous Coverage Ant. 2-30 MHz	
Continuous Coverage Ant. 2-30 MHz No Tuner Necessary	.\$135.00
BASH	
Books and Tapes	, \$9.95
BENCHER	00/45 00
BY-1 Paddle/BY-2 Chrome. \$3 ZA-1A Balun. BUTTERNUT	18.60
PHYTERNIT	10.30
HF6V 80-10 Meter Vertical	\$119.00
HF6V 80-10 Meter Vertical	
	\$215.00
A4 Tribander 4EL	285.00
214FB Boomer 14EL FM	06.00
32-19 Super Boomer 19EL 2M	39.00
A3 Tribander 3EL. A4 Tribander 4EL. 214FB Boomer 14EL FM. 32-19 Super Boomer 19EL 2M. ARX-28 Ringo Ranger II 2M. 416-TB Satellite Ant. DAIWA	65.00
DAIWA	
CN-520 1.8-60 MHz SWR/Pwr Mtr	\$63.00
CN-520 1.8-60 MHz SWR/Pwr Mtr	110.00
DRAKE	\$1 426 DO
TRTA Xcvrw/PS7 R7A Receiver. TR5Xcvrw/PS75	1.189.00
TR5 Xcvr w/PS75	675.00
ENCOMM (SANTEC)	
TR5 XCV W/PS75. ENCOMM (SANTEC) ST-144/uP, 220/uP, 440/uP	
The Handhelds Offering the Most Features Call for Your Discount Price	
HAL	
DS2100/MPT/ST6000	\$2 825.00
DS3100/MPT/ST6000 CT2200/KB2200 CWR6850 Telereader	945.00
CWR6850 Telereader	745.00
HY-GAIN TH7 DXS 7EL Tribander TH5 MK2S 5EL Tribander	
TH7 DXS 7EL Tribander	\$375.00
Explorer 14 Tribander	279.00
V2S 2 Meter Vertical	39.00
V2S 2 Meter Vertical Ham IV 15 sq ft Rotator	195.00
	249.00
Free Shipping on all crank-up towers	
ICOM	
We Many All the Great ICOM Transcellers to S	tock
We Have All the Great ICOM Transceivers in S	
We have All the Great ICOM Transceivers in S Call About the New Ones Now Available	
We have All the Great ICOM Transceivers in S Call About the New Ones Now Available	
We have All the Great ICOM Transceivers in S Call About the New Ones Now Available	
We Have All the Great ICOM Transceivers in S Call About the New Ones Now Available IC-2AT	235.00 305.00
We Have All the Great ICOM Transceivers in S Call About the New Ones Now Available IC-2AT	235.00 305.00
We Have All the Great ICOM Transceivers in S Call About the New Ones Now Available IC-2AT	235.00 305.00
We Have All the Great ICOM Transceivers in S Call About the New Ones Now Available IC-2AT	235.00 305.00
We Have All the Great ICOM Transceivers in S Call About the New Ones Now Available IC-2AT	235.00 305.00
We Have All the Great ICOM Transceivers in S Call About the New Ones Now Available IC-2AT	235.00 305.00
We Have All the Great ICOM Transceivers in S Call About the New Ones Now Available IC-2AT. ANTACH Handheids. 25A new display & mic. 290H 2M All Mode. 2714 All Mode. 2714 All Mode. 7714 Oscar All Mode. 751 Ultimate Transceiver. 74S New General Coverage Xcvr. 45A 440 MHz. R70 Rcvr/Free World Clock KLMI	sly \$215.00 .235.00 .305.00 .479.00 .625.00 .Call .1,250.00 .Call .349.00 .629.00
We Have All the Great ICOM Transceivers in S Call About the New Ones Now Available IC-2AT. Now Or 3AT/4AT Handheids. Now Or 3AT/4AT Handheids. Now Or 25A new display & mic. 290H 2M All Mode. 271A All Mode. 471A Oscar All Mode. 751 Ultimate Transceiver. 745 New General Coverage Xcvr. 45A 440 MHz. R70 RcvriFree World Clock KLM.	oly \$215.00 .235.00 .305.00 .479.00 .625.00 .Call 1.250.00 .Call .349.00 .629.00
We Have All the Great ICOM Transceivers in S Call About the New Ones Now Available IC-2AT. Now Or 3AT/4AT Handheids. Now Or 3AT/4AT Handheids. Now Or 25A new display & mic. 290H 2M All Mode. 271A All Mode. 471A Oscar All Mode. 751 Ultimate Transceiver. 745 New General Coverage Xcvr. 45A 440 MHz. R70 RcvriFree World Clock KLM.	oly \$215.00 .235.00 .305.00 .479.00 .625.00 .Call 1.250.00 .Call .349.00 .629.00
We Have All the Great ICOM Transceivers in S Call About the New Ones Now Available IC-2AT. Now Or 3AT/4AT Handheids. Now Or 3AT/4AT Handheids. Now Or 25A new display & mic. 290H 2M All Mode. 271A All Mode. 471A Oscar All Mode. 751 Ultimate Transceiver. 745 New General Coverage Xcvr. 45A 440 MHz. R70 RcvriFree World Clock KLM.	oly \$215.00 .235.00 .305.00 .479.00 .625.00 .Call 1.250.00 .Call .349.00 .629.00
We Have All the Great ICOM Transceivers in S Call About the New Ones Now Available IC-2AT. Now Or 3AT/4AT Handheids. SA new display & mic. 290H 2M All Mode. 271A All Mode. 271A All Mode. 751 Ultimate Transceiver. 745 New General Coverage Xcvr. 45A 440 MHz. R70 Rcvr/Free World Clock KLM KT34A 4EL Triband Beam. KT34XA 6EL Triband Beam. KT34XA 6EL Triband Beam. KT34XA 9EL Triband Beam. 144-148-13LBA 2M Long Boomer. 143-150-14C 2M Satellite Ant. 420-470-18C Satellite Ant.	aly \$215.00 .235.00 .305.00 .305.00 .479.00 .625.00 .Call 1.250.00 .Call .349.00 .629.00 .8299.00 .459.00 .79.00 .79.00
We Have All the Great ICOM Transceivers in SCall About the New Ones Now Available IC-2AT. Handheids Now Or 3AT/4AT Handheids Now Or 25A new display & mic. 290H 2M All Mode 271A All Mode 271A All Mode 711A IM Mode 711A IM Mode 751 Ultimate Transceiver 74S New General Coverage Xcv 45A 440 MHz R70 RcvriFree World Clock KLM KT34A 4EL Triband Beam KT34XA 6EL Triband Beam KT34XA 6EL Triband Beam 414-148-13LBA 2M Long Boomer 143-150-14C 2M Satellite Ant 420-470-18C Satellite Ant 4420-470-18C	oly \$215.00 .235.00 .305.00 .479.00 .625.00 .Call 1.250.00 .Call .349.00 .629.00
We Have All the Great ICOM Transceivers in S Call About the New Ones Now Available IC-2AT. AT AT AT Handheids. 25A new display & mic. 2900 2M All Mode. 2714 All Mode. 2714 All Mode. 751 Ullimate Transceiver. 745 New General Coverage Xcvr. 45A 440 MHz. R70 Rcvr/Free World Clock KLM KT34A 4EL Triband Beam. KT34XA 6EL Triband Beam. KT34XA 6EL Triband Beam. 44-148-13LBA 2M Long Boomer. 143-150-14C 2M Satellite Ant. 420-470-18C Satellite Ant. Maximizer Antennas. KANTRONICS	aly \$215.00 .235.00 .305.00 .305.00 .479.00 .625.00 .Call 1.250.00 .Call .349.00 .629.00 .8299.00 .459.00 .79.00 .79.00
We Have All the Great ICOM Transceivers in S Call About the New Ones Now Available IC-2AT. Now Or 3AT/AAT Handheids. SA new display & mic. 290H 2M All Mode. 271A All Mode. 271A All Mode. 271A All Mode. 751 Ullimate Transceiver. 745 New General Coverage Xcvr. 45A 440 MHz. R70 Rcvr/Free World Clock. KLM. KT34A 4EL Triband Beam. KT34XA 6EL Triband Beam. KT34XA 6EL Triband Beam. KT34XA 9EL Triband Beam. 44-148-13LBA 2M Long Boomer. 143-150-14C 2M Satellite Ant. 420-470-19C Satellite Ant. Maximizer Antennas. KANTRONICS. The Fantastic Interface for CW, RTTY, ASCII. Software Available for VIC20. VIC54. APPLE.	aly \$215.00 .235.00 .305.00 .305.00 .479.00 .625.00 .Call 1.250.00 .Call .349.00 .629.00 .8299.00 .459.00 .79.00 .79.00
We Have All the Great ICOM Transceivers in S Call About the New Ones Now Available IC-2AT. Now Or 3AT/AAT Handheids. SA new display & mic. 290H 2M All Mode. 271A All Mode. 271A All Mode. 271A All Mode. 751 Ullimate Transceiver. 745 New General Coverage Xcvr. 45A 440 MHz. R70 Rcvr/Free World Clock. KLM. KT34A 4EL Triband Beam. KT34XA 6EL Triband Beam. KT34XA 6EL Triband Beam. KT34XA 9EL Triband Beam. 44-148-13LBA 2M Long Boomer. 143-150-14C 2M Satellite Ant. 420-470-19C Satellite Ant. Maximizer Antennas. KANTRONICS. The Fantastic Interface for CW, RTTY, ASCII. Software Available for VIC20. VIC54. APPLE.	aly \$215.00 .235.00 .305.00 .305.00 .479.00 .625.00 .Call 1.250.00 .Call .349.00 .629.00 .8299.00 .459.00 .79.00 .79.00
We Have All the Great ICOM Transceivers in S Call About the New Ones Now Available IC-2AT. Now Or 3AT/AAT Handheids. SA new display & mic. 290H 2M All Mode. 271A All Mode. 271A All Mode. 271A All Mode. 751 Ullimate Transceiver. 745 New General Coverage Xcvr. 45A 440 MHz. R70 Rcvr/Free World Clock. KLM. KT34A 4EL Triband Beam. KT34XA 6EL Triband Beam. KT34XA 6EL Triband Beam. KT34XA 9EL Triband Beam. 44-148-13LBA 2M Long Boomer. 143-150-14C 2M Satellite Ant. 420-470-19C Satellite Ant. Maximizer Antennas. KANTRONICS. The Fantastic Interface for CW, RTTY, ASCII. Software Available for VIC20. VIC54. APPLE.	aly \$215.00 .235.00 .305.00 .305.00 .479.00 .625.00 .Call 1.250.00 .Call .349.00 .629.00 .8299.00 .459.00 .79.00 .79.00
We have All the Great ICOM Transceivers in SCall About the New Ones Now Available IC-2AT. ANTAAT Handheids. 25A new display & mic. 290H 2M All Mode. 271A All Mode. 271A All Mode. 271A Oscar All Mode. 7751 Ultimate Transceiver. 74S New General Coverage Xcvr. 45A 440 MHz. R70 Rcvr/Free World Clock KLM KT34A 4EL Triband Beam. KT34AA 5EL Triband Beam. KT34AA 5EL Triband Beam. 44-148-13LBA 2M Long Boomer. 143-150-146 2M Satellite Ant. 420-470-18C Satellite Ant. 420-470-18C Satellite Ant. Maximizer Antennas. KANTRONICS The Fantastic Interface for CW, RTTY, ASCII Software Available for VIC20, VIC64, APPLE, ATARI, TR80C, Tiple Call for a Package Price LARSEN.	ily \$215.00 235.00 305.00 479.00 479.00 625.00 Call 1,250.00 629.00 \$299.00 79.00 79.00 59.00 Call
We Have All the Great ICOM Transceivers in SCall About the New Ones Now Available IC-2AT. 3AT/4AT Handheids. 25A new display 8 mic. 250H 2M All Mode. 2711 A All Mode. 2711 A All Mode. 2713 All Mode. 2714 A Ill Mode. 745 New General Coverage Xcv. 45A 440 MHz. R70 Rcvr/Free World Clock. KLM KT34A 4EL Triband Beam. KT34AA 6EL Triband Beam. 144-148-13LBA 2M Long Boomer. 143-150-14C 2M Satellite Ant. Maximizer Antennas. KANTRONICS. The Fantastic Interface for CW, RTTY, ASCII Software Available for ViC20, VIC64, APPLE, ATARI, TRBOC, T199 Call for a Package Price LARSEN.	ily \$215.00 .235.00 .305.00 .479.00 .625.00 .Call .1250.00 .Call .250.00 .629.00 .629.00 .599.00 .599.00 .599.00 .599.00 .599.00
We Have All the Great ICOM Transceivers in SCall About the New Ones Now Available IC-2AT. 3AT/4AT Handheids. 25A new display 8 mic. 250H 2M All Mode. 2711 A All Mode. 2711 A All Mode. 2713 All Mode. 2714 A Ill Mode. 745 New General Coverage Xcv. 45A 440 MHz. R70 Rcvr/Free World Clock. KLM KT34A 4EL Triband Beam. KT34AA 6EL Triband Beam. 144-148-13LBA 2M Long Boomer. 143-150-14C 2M Satellite Ant. Maximizer Antennas. KANTRONICS. The Fantastic Interface for CW, RTTY, ASCII Software Available for ViC20, VIC64, APPLE, ATARI, TRBOC, T199 Call for a Package Price LARSEN.	ily \$215.00 .235.00 .305.00 .479.00 .625.00 .Call .1250.00 .Call .250.00 .629.00 .629.00 .599.00 .599.00 .599.00 .599.00 .599.00
We Have All the Great ICOM Transceivers in SCall About the New Ones Now Available IC-2AT. 3AT/4AT Handheids. 25A new display 8 mic. 250H 2M All Mode. 2711 A All Mode. 2711 A All Mode. 2713 All Mode. 2714 A Ill Mode. 745 New General Coverage Xcv. 45A 440 MHz. R70 Rcvr/Free World Clock. KLM KT34A 4EL Triband Beam. KT34AA 6EL Triband Beam. 144-148-13LBA 2M Long Boomer. 143-150-14C 2M Satellite Ant. Maximizer Antennas. KANTRONICS. The Fantastic Interface for CW, RTTY, ASCII Software Available for ViC20, VIC64, APPLE, ATARI, TRBOC, T199 Call for a Package Price LARSEN.	ily \$215.00 .235.00 .305.00 .479.00 .625.00 .Call .1250.00 .Call .250.00 .629.00 .629.00 .599.00 .599.00 .599.00 .599.00 .599.00
We Have All the Great ICOM Transceivers in SCall About the New Ones Now Available IC-2AT. 3AT/4AT Handheids. 25A new display 8 mic. 250H 2M All Mode. 2711 A All Mode. 2711 A All Mode. 2713 All Mode. 2714 A Ill Mode. 745 New General Coverage Xcv. 45A 440 MHz. R70 Rcvr/Free World Clock. KLM KT34A 4EL Triband Beam. KT34AA 6EL Triband Beam. 144-148-13LBA 2M Long Boomer. 143-150-14C 2M Satellite Ant. Maximizer Antennas. KANTRONICS. The Fantastic Interface for CW, RTTY, ASCII Software Available for ViC20, VIC64, APPLE, ATARI, TRBOC, T199 Call for a Package Price LARSEN.	ily \$215.00 .235.00 .235.00 .479.00 .479.00 .Call .1250.00 .629.00 .\$299.00 .\$299.00 .\$299.00 .\$299.00 .\$299.00 .\$299.00 .\$299.00 .\$299.00 .\$299.00 .\$299.00 .\$299.00 .\$299.00 .\$299.00 .\$299.00 .\$299.00 .\$299.00
We have All the Great ICOM Transceivers in SCall About the New Ones Now Available IC-2AT. 3ATAAT Handheids. 25A new display & mic. 290H 2M All Mode. 271A Minate Transceiver. 74S New General Coverage Xcvr. 45A 440 MHz. R70 Rcvr/Free World Clock KLM KT34A 4EL Triband Beam. KT34AA 5EL Triband Beam. KT34AA 5EL Triband Beam. 44-148-13LBA 2M Long Boomer. 143-150-146 2M Satellite Ant. 420-470-18C Satellite Ant. 420-470-18C Satellite Ant. Maximizer Antennas. KANTRONICS The Fantastic Interface for CW, RTTY, ASCII Software Available for ViC20, ViC64, APPLE, ATARI, TR80C, Tip9 Call for a Package Price LARSEN. NLA-150-MM 5/8 Wave 2M Mag Mt. MFJ 1224 New Computer Interface. 941CTuner/Meter/Ant. Switch/Balun. 422 Keyer/BENCHER Paddle combo. 313 VHF Cony for HT.	ily \$215.00 .235.00 .235.00 .479.00 .479.00 .Call .1250.00 .629.00 .\$299.00 .\$299.00 .\$299.00 .\$299.00 .\$299.00 .\$299.00 .\$299.00 .\$299.00 .\$299.00 .\$299.00 .\$299.00 .\$299.00 .\$299.00 .\$299.00 .\$299.00 .\$299.00
We Have All the Great ICOM Transceivers in SCall About the New Ones Now Available IC-2AT. An Art An Art Andheids. 25A new display & mic. 250H 2M All Mode. 271 A All Mode. 271 A All Mode. 271 A All Mode. 271 A All Mode. 273 A West And Mode. 745 New General Coverage Xcv. 45A 440 MHz. R70 RcvriFree World Clock KLM KT34A A EL Triband Beam KT34AA 5EL Triband Beam 144-148-13LBA 2M Long Boomer. 143-150-14C 2M Satellite Ant. Maximizer Antennas. KANTRONICS The Fantastic Interface for CW, RTTY, ASCII Software Available for VIC20, VIC64, APPLE, ATARI, TRBOC, TIPS Call for a Package Price LARSEN NLA-150-MM 5/8 Wave 2M Mag Mt. MFJ 1224 New Computer Interface. 941C-Tuner/Meter/Ant, Switch/Balun 422 Keyer/BENCHER Paddle combo. 313 VHF Conv for HT. 989 3KW Tuner.	ily \$215.00 .235.00 .305.00 .479.00 .625.00 .Call .1250.00 .Call .250.00 .629.00 .629.00 .599.00 .599.00 .599.00 .599.00 .599.00
We have All the Great ICOM Transceivers in SCall About the New Ones Now Available IC-2AT. 3ATAAT Handheids. 25A new display & mic. 290H 2M All Mode. 271A All Mode. 271A All Mode. 471A Oscar All Mode. 751 Ultimate Transceiver. 74S New General Coverage Xcvr. 45A 440 MHz. R70 Rcvr/Free World Clock KLM KT34A 4EL Triband Beam. KT34A4 SEL Triband Beam. KT34A4 SEL Triband Beam. 44-148-13LBA 2M Long Boomer. 143-150-146 2M Satellite Ant. 420-470-18C Satellite Ant. 420-470-18C Satellite Ant. Maximizer Antennas. KANTRONICS The Fantastic Interface for CW, RTTY, ASCII Software Available for ViC20, ViC64, APPLE, ATARI, TR80C, Tipp Call for a Package Price LARSEN. NLA-150-MM 5/8 Wave 2M Mag Mt. MFJ 1224 New Computer Interface. 941C Tuner/Meter/Ant, Switch/Balun. 422 Keyer/BENCHER Paddle combo. 313 VHF Conv for H. 989 3KW Tuner. MIRAGE	ily \$215.00 235.00 235.00 479.00 479.00 625.00 Calil 349.00 629.00 \$299.00 \$499.00 79.00 79.00 Calil \$39.00 Calil \$39.00 Calil \$39.00 Calil
We Have All the Great ICOM Transceivers in SCall About the New Ones Now Available IC-2AT. Now Or 3A174AT Handheids. 25A new display 8 mic. 290H 2M All Mode. 2714 A III Mode. 2714 A III Mode. 2714 A III Mode. 2714 A III Mode. 2715 New General Coverage Xcv. 45A 440 MHz. R70 RcvriFree World Clock KLM KT34A 4EL Triband Beam KT34AA 5EL Triband Beam KT34AA 5EL Triband Beam 144-148-13LBA 2M Long Boomer. 143-150-14C 2M Satellite Ant. Maximizer Antennas. KANTRONICS The Fantautic Interface for CW, RTTY, ASCII Software Available for VIC20, VIC64, APPLE, ATARI, TR80C, TI99 Call for a Package Price LARSEN ILA-150-MM 5/8 Wave 2M Mag Mt. MFJ 1224 New Computer Interface. 941C-Tuner/Meter/Ant, Switch/Balun 422 Keyer/IBENCHER Paddle combo. 313 VHF Conv for HT. 989 3KW Tuner.	ily \$215.00 .235.00 .235.00 .305.00 .479.00 .625.00 .Call .1250.00 .629.00 .629.00 .59.00 .79.00
We Have All the Great ICOM Transceivers in SCall About the New Ones Now Available IC-2AT. Now Or 3A174AT Handheids. 25A new display 8 mic. 290H 2M All Mode. 2714 A III Mode. 2714 A III Mode. 2714 A III Mode. 2714 A III Mode. 2715 New General Coverage Xcv. 45A 440 MHz. R70 RcvriFree World Clock KLM KT34A 4EL Triband Beam KT34AA 5EL Triband Beam KT34AA 5EL Triband Beam 144-148-13LBA 2M Long Boomer. 143-150-14C 2M Satellite Ant. Maximizer Antennas. KANTRONICS The Fantautic Interface for CW, RTTY, ASCII Software Available for VIC20, VIC64, APPLE, ATARI, TR80C, TI99 Call for a Package Price LARSEN ILA-150-MM 5/8 Wave 2M Mag Mt. MFJ 1224 New Computer Interface. 941C-Tuner/Meter/Ant, Switch/Balun 422 Keyer/IBENCHER Paddle combo. 313 VHF Conv for HT. 989 3KW Tuner.	ily \$215.00 .235.00 .235.00 .305.00 .479.00 .625.00 .Call .1250.00 .629.00 .629.00 .59.00 .79.00
We have All the Great ICOM Transceivers in SCall About the New Ones Now Available IC-2AT. 3ATAAT Handheids. 25A new display & mic. 290H 2M All Mode. 271A Minate Transceiver. 74S New General Coverage Xcvr. 45A 440 MHz. R70 Rcvr/Free World Clock KLM KT34A 4EL Triband Beam. KT34AA 5EL Triband Beam. KT34AA 5EL Triband Beam. 44-148-13LBA 2M Long Boomer. 143-150-146 2M Satellite Ant. 420-470-18C Satellite Ant. 420-470-18C Satellite Ant. 420-470-18C Satellite Ant. Maximizer Antennas. KANTRONICS The Fantastic Interface for CW, RTTY, ASCII Software Available for ViC20, ViC64, APPLE, ATARI, TR80C, Tipp Call for a Package Price LARSEN NLA-150-MM 5/8 Wave 2M Mag Mt. MFJ 1224 New Computer Interface. 941C Tuner/Meter/Ant. Switch/Balun. 422 Keyer/BENCHER Paddle combo. 313 VHF Conv for HT. 989 3KW Tuner. MIRAGE D1010/N 440 MHz Amp. B1016 10/160 Preamp. B3016 30/160 Preamp. B30H BOH	ily \$215.00 .235.00 .235.00 .479.00 .479.00 .625.00 .Calil .1250.00 .629.00 .\$299.00 .\$499.00 .\$499.00 .\$79.00 .79.00 .79.00 .Calil .\$39.00 .Calil .\$39.00 .Calil .\$39.00 .Calil .\$39.00 .Calil .\$39.00 .Calil .\$39.00 .39.00
We Have All the Great ICOM Transceivers in SCall About the New Ones Now Available IC-2AT. 3AT/4AT Handheids. 25A new display & mic. 250H 2M All Mode. 271A All Mode. 74S New General Coverage Xcv. 45A 440 MHz. R70 Rcvr/Free World Clock KLM KT34A 4EL Triband Beam KT34AA 6EL Triband Beam 144-148-13LBA 2M Long Boomer. 143-150-14C 2M Satellite Ant. Maximizer Antennas. KANTRONICS The Fantastic Interface for CW, RTTY, ASCII Software Available for ViC20, VIC64, APPLE, ATARI, TRBOC, Tipe Call for a Package Price LARSEN NLA-150-MM 5/8 Wave 2M Mag Mt. MFJ 1224 New Computer Interface. 941C Tuner/Meter/Ant. Switch/Balun. 422 Keysr/BENCHER Paddle combo. 313 VHF Conv for HT. 989 3KW Tuner. MIRAGE D1010/N 440 MHz Amp B1016 10/160 Preamp.	ily \$215.00 .235.00 .235.00 .479.00 .479.00 .625.00 .Calil .1250.00 .629.00 .\$299.00 .\$499.00 .\$499.00 .\$79.00 .79.00 .79.00 .Calil .\$39.00 .Calil .\$39.00 .Calil .\$39.00 .Calil .\$39.00 .Calil .\$39.00 .Calil .\$39.00 .39.00

Send SASE for Our New & Used Equipment List Prices ere FOB Evansville

Now in Stock. Cali for Prices 726R Multiband & Mode Oscar Rig. Cali

TEN-IEC
New 2M Handheld
Argosy II Digital
2KW Tuner Kit.
The Fantastic Corsair.
TOKYO MY-POWER

HL30V 2/30W Amp.
HL160V 3 or 10/160W Preamp.
HC2000 2KW Tuner.
HL90U 440 MHz w/Preamp.
YAESU

TOLL FREE ORDERS • 1-800-826-5432 INFORMATION - (213) 380-8000

MINIATURE 6 VDC RELAY



SUPER SMALL SPDT RELAY; GOLD COBALT CONTACTS. RATED 1 AMP AT 30 VDC;

HATED 1 AMP AT 30 VDC; HIGHLY SENSITIVE, TTL DIRECT DRIVE POSSIBLE, OPERATES FROM 43 TO 6 V, COIL RES. 220 OHM. 13/16" × 13/32" × 7/16"

AROMAT # RSD-6V \$1.50 EACH 10 FOR \$13.50

120V INDICATOR

NEON INDICATOR, RATED 120 V 1/3 W. MOUNTS RED LENS. 5/16" HOLE 754 EACH

100 FOR \$65.00 METERS

5/16" SQUARE

\$5 50 EACH

0 - 15 V.D.C.



THIS 2-1/4"
SQUARE METER
MEASURES
0-15 VDC.

13 YDC RELAY
CONTACT: S.P.N.C.
10 AMP @ 120 VAC
ENERGIZE COIL TO
OPEN CONTACT...
COIL: 13 YDC 650 OHMS
SPECIAL PRICE \$1.00 EACH

KEY ASSEMBLY

5 KEY \$1.00 EACH CONTAINS 5 SINGLE-POLE NORMALLY OPEN SWITCHES

MEASURES 3 3/4" LONG 6 KEY \$1.25 EACH

CONTAINS & SINGLE-POLE NORMALLY OPEN SWITCHES MEASURES 4 1/4" LONG.

L.E.D.'S

STANDARD JUMBO DIFFUSED

RED 10 FOR \$1.50 CREEN 10 FOR \$2.00 YELLOW 10 FOR \$2.00

FLASHER LED 5 VOLT OPERATION A RED JUMBO SIZE \$1.00 EACH

BI POLAR LED

LED HOLDERS TWO PIECE HOLDER SPOR JUMBO LED 10 FOR 654 200 FOR \$10.00

MULTI-SWITCHES

5 STATION INTERLOCKING

3 - 2PDT AND 2 - 8PDT SWITCHES ON FULLY INTERLOCKING ASSEMBLY, 31/4" BETWEEN MOUNTING CENTERS. \$2.50 EACH

5 STATION NON-INTERLOCKING SAME AS ABOVE, EXCEPT EACH SWITCH OPERATES INDEPENDENTLY. \$2.50 EACH

SEND FOR LARGERIE

COMPUTER GRADE CAPACITORS

1700 mfd. 150 VDC \$2.00 2 1/2" DIA × 4 3/4" HIGH 3,600 mfd. 40VDC \$1.00 3,600 mfd. 1 3/6" DIA. = 3" HIGH 6,400 mfd. 60 VDC \$2.50 HIGH 1 3/8" DIA. = 4 1/4" HIGH 18,000 mfd. 75 VDC \$4.00

2 1/2" DIA. # 4 1/2" HIGH 22,000 mfd. 15 VDC 2" DIA. # 2 1/2" HIGH 22,000 mfd. 40 VDC GH \$2.00 24,000 mld. 30 VDC 1 3/4" DIA. = 4" HIGH 31,000 mfd. 15 VDC 1 3/4" DIA. × 4" HIGH \$2.50 72,000 mfd. 15 VDC 2" DIA. × 4" HIGH \$3.50 180,000 mfd. at 6V

2 1/2" DIA. = 4 1/2" HIGH \$1.50 CLAMPS TO PIT CAPACITORS SEE on.

48 PAGE CATALOG

TRANSFORMERS

E.6 VOLTS at 750 MA \$1.00 6 VOLTS at 150 MA \$1.25 16.5 V. at 3 AMPS \$6.50 \$3.50 6 VOLTS at 150 MA 16.5 V, at 3 AMPS 16 V at 650 MA 16 VOLTS at 1 AMP \$5.50 \$2.50 \$4.50 \$4.50 42 V.C.T. at 1.2 AMP

WALL TRANSFORMER



ALL ARE 118 VAC PLUG IN

4 VDC at 70 MA 6 VDC at 225 MA \$3.00 \$3.50 18.5 VAC at 10 VA 17 VAC at 500 MA \$4.00 \$2.50 22 VDC at 60 MA

MINIATURE TOGGLE SWITCHES ALL ARE RATED 5 AMPS @ 125 VAC

S.P.D.T. (On-On)
P.C. STYLE
NON-THREADED BUSHING.
THE EACH THE ACH TO FOR \$7.00 100 FOR \$50.00 100 FOR \$5

S.P.D.T.

. 185.00

S.P.D.T.

S.P.D.T. S.P.D. I. (on-off-on) SOLDER LUG SOLDER LUG TERMINALS. \$1.00 EACH 10 FOR \$9.00 100 FOR \$80.00

(on-on) (on-off-on) P.C. LUGS. THREADED

NON-THREADED BUSHING.
P.C. STYLE STORM STO

D.P.D.T. (on-on)




ALL ELECTRONICS CORP

905 S. VERMONT + P.O. BOX 20406 - LOS ANGELES, CA 90006

- OUANTITIES LIMITED MINIMUM ORDER \$10.00 USA \$2.50 SHIPPING
- FOREIGN ORDERS
 INCLUDE SUFFICIENT
 SHIPPING
 CALIF RES ADO 6 T 7

CHAMPAGNE RTTY/CW on a Beer Budget

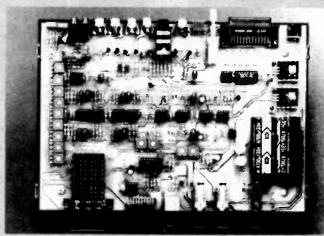

CP-1 Computer Patch™ Interface

The AEA Model CP-1 Computer Patch™ interface will let you discover the fastest growing segment of Amateur Radio: computerized RTTY and CW operation.

When used with the appropriate software package (see your dealer), the CP-1 will patch most of the popular personal computers to your transceiver for a complete full-feature RTTY/CW station. No computer programming skills are necessary. The CP-1 was designed with the RTTY neophyte in mind, but its sophisticated circuitry and features will appeal to the most experienced RTTY operator.

The CP-1 offers variable shift capability in addition to fixed 170 Hz dual channel filtering. Auto threshold plus pre and post limiter filters allow for good copy under fading and weak signal conditions.

Transmitter AFSK tones are generated by a clean, stable function generator. Plus (+) and minus (-) output jacks are also provided for CW keying of your transmitter. An optional low cost RS-232 port is also available. The CP-1 is powered with 16 VAC which is supplied by a 117 VAC wall adaptor included with the CP-1.






THE HAM SHA

Brings you the

Keyboard Your Way to Happiness

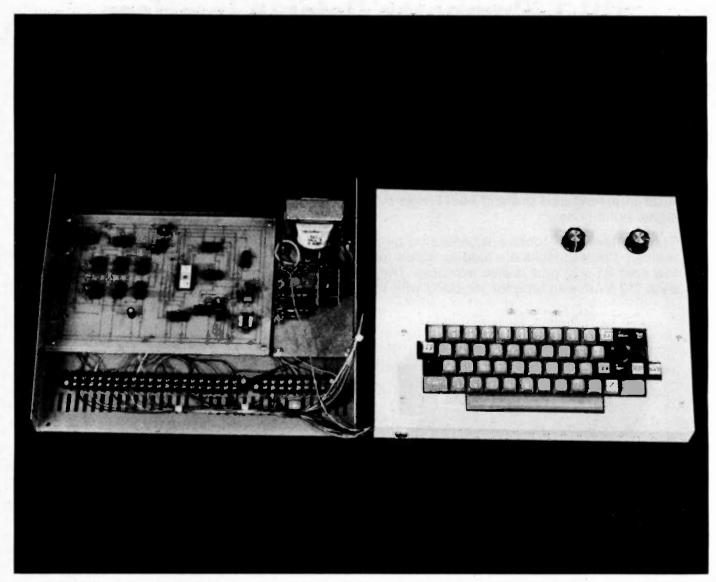If happiness is perfect Morse, then this project is pure heaven. Special construction tips make putting it together as much fun as using it.



ending Morse code ac-Ocurately and at relatively high speeds has been made possible with the advent of the Morse keyboard. Perfect Morse code with perfect spacing is possible with a Morse keyboard with a buffer memory. Many of the physical limitations that are encountered while using other manual keving methods have been overcome by the Morse keyboard. The Morse keyboard has become a valuable instrument for sending Morse code and will continue to play an important role in communications.

This article will describe a Morse keyboard with a 192-character buffer memory. It will send perfect Morse code with perfect spacing as long as the operator stays ahead of the outgoing code. If the Morsecode operator tends to fall behind, the spacing may become erratic, but the Morse code itself will not be affected.

The Morse keyboard is made up of an ASCII communications keyboard, a buffer memory, and an ASCII6-to-Morse converter. The 192-character buffer memory allows the operator to type as many as 192 characters and word spaces ahead of the outgoing Morse code. An experienced operator may type ahead and then take time out to fill out the log book while the Morse code is being sent out.

The Morse keyboard may also be used as a code-practice device, allowing a person who does not already know the Morse code to send perfect code to a student who is learning the code.

I have been using the Morse keyboard at speeds of up to 40 words per minute on the ham bands and have checked the Morsecode waveforms on an oscilloscope at much higher speeds. The waveforms indicate that the Morse keyboard is working satisfactorily at speeds well over 80 words per minute.

ASCII Keyboard

The ASCII keyboard is an ASR-33, 53-key, data-communications type of keyboard. There are several manufacturers who make this type of keyboard. A microcomputer may also be used as an ASCII signal

I am using 26 letters, 10 numbers, 4 punctuation marks, and the special Morse-code characters AS (wait). BK (break). AR (end of message), and SK (end of transmission) for a total of 44 Morse-code characters. All of the characters for this particular Morse keyboard are arranged for the lowercase position on the keyboard and some of the keytops have been rearranged so that all of the characters are readily available without having to use the keyboard shift keys. The question mark, which is normally an uppercase character, has been moved to a lowercase position on the key-

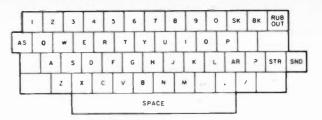


Fig. 1. The N7AGK ASR-33 Morse keyboard layout

board. Some of the special Morse-code characters do not have an ASCII equivalent, but have been substituted for other unused characters

A strobe or keypunch pulse is supplied by the ASCII keyboard each time a character key is pressed and is used to enter data into the buffer memory. This arrangement allows the operator to type at an uneven rate and to enter data into the buffer memory whenever a key is pressed.

Fig. 1 shows the keyboard layout for the Morse keyboard. Most ASCII keyboards have been designed so that the keytops may be easily removed and placed in a different location on the keyboard. Keytops are available that have special titles.

Buffer Memory

Fig. 2 is a schematic of the buffer memory. The buffer memory is a type of digital storage system which allows the Morsekeyboard operator to enter data at different rates or to store data in the buffer memory until needed. Data will remain stored in the buffer memory as long as power to the buffer memory is not interrupted.

The 192-character buffer memory is made up of 3 pairs of 3341 first-in/firstout shift registers. Each pair will handle 64 ASCII6 characters. (The Morse keyboard uses only 6 bits of the ASCII data from the ASCII keyboard.) Each 3341 FIFO shift register handles 4 bits of information in a 64-by-4 configuration. The buffer memory accepts parallel

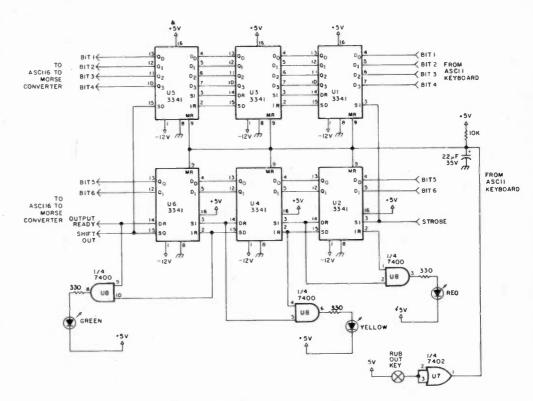


Fig. 2. 192-character buffer memory.

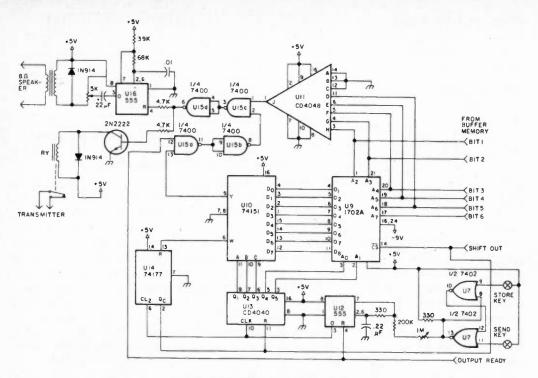


Fig. 3. ASCII6-to-Morse converter.

data only from the ASCII keyboard.

The 3341 FIFO has separate input and output data terminals and has separate input and output clock circuits that can operate at different clock rates. The input clock pulse is called a shift-in pulse and the output clock pulse is called a shift-out pulse. The shift-in pulse is the ASCII keyboard strobe or keypunch pulse which allows data to be entered into the buffer memory whenever a key is pressed. The shift-out pulse is supplied by a Morse-code character-space circuit in the ASCII6-to-Morse converter and will be described in detail later in the article.

The buffer memory may

be thought of as a pipe which will hold up to 192 marbles. The shift-in rate is the rate at which marbles are placed in the pipe. The shift-out rate is the rate at which marbles are removed from the pipe. If marbles are not added to the pipe, but are removed, the pipe will become empty after a period of time. If marbles are entered and removed from the pipe at the same time and at the correct rates, a continual supply of marbles will be present in the pipe.

Too short a buffer memory may require a Morse-code operator to stop and wait during an inconvenient part of the Morse-code transmission or may cause

the operator to stop and wait in the middle of a sentence, thereby interrupting his chain of thought. A large buffer memory will allow the Morse-code operator to type in a larger portion of a message without having to stop and wait as often.

The buffer memory has 3 functions available which are controlled by 3 function keys on the ASCII keyboard. A Store key allows the operator to enter data into the buffer memory without data being removed. A Send key allows the operator to remove data from the buffer memory. Data may be removed from the buffer memory while data is being entered. A Rub Out key is used as a

master reset for the buffer memory and erases any information stored in the buffer memory when pressed.

The function keys supply +5 V when pressed and supply zero or ground potential when not pressed. The Send key and Store key supply signals to a simple flip-flop circuit which ensures that either one or the other function is operating at any given time, but that they are not operating simultaneously. The simple flip-flop circuit is half of U7 or 2 NOR gates of a quad 7402 NOR gate. When the Store function is operating, the ASCII6-to-Morse converter clock generator, U12, is shut off. During this function, data is prevented from leaving the buffer memory.

During the Send mode, the clock generator is allowed to operate, thus allowing data to be shifted out of the buffer memory.

There is an LED indicator light for each pair of 3341 FIFO shift registers. These indicator lights are used as warning or indicator lights for the convenience of the Morse-keyboard operator. I chose a green LED for the first pair of 3341s, a yellow LED for the second pair, and a red LED for the third pair. The red LED blinks whenever a character is typed and acts as a warning that the buffer memory is close to being full. The green LED is lit when there are between one and 64 characters in the buffer memory. The yellow LED is lit when there are between 64 and 128 characters in the buffer memory. The red LED is lit when there are between 128 and 192 characters in the buffer memory. If the buffer memory is empty, none of the LED indicator lights will be lit. The LED indicator lights are positioned on the Morse keyboard so that they may be easily observed by the Morse-keyboard operator.

	ASCII		Buff	er Me	mory		1702A			74151	
Ke	yboard	A	SCHE	Cha	racte	rs	Memor	y Circu	uit	Demu	ltiplexer
		3	Z	8	Ε	В	Address	Outp	out	Input	
	Bit 6	1	0	1	0	0	A7	01	1	A	W
	5	1	1.	1	0	0	A6	02	1	В	
	4	0	1	1	0	0	A5	03	1	С	
	3	0	0	0	1	0	A4	04	0	D	\longrightarrow
	2	1	1	0	0	1	A3	05	1	Ε	00011101
	1	1	0	0	1	0	A2	06	0	F	Letter A
		Par	allel	ASCII	6 Dat	a		07	0	G	Serial
		Flo	w of I	Data				08	0	Н	Morse
		****				>		Lette	er N		Code
								Para	llel		
								Mors	se Code		

Fig. 4. Flow of data from the ASCII keyboard to the 74151 demultiplexer output.

SHIP WORLDWIDE Your one source for all Radio Equipment!

For the best buys in town call: 212-925-7000

Los Precios Mas Bajos en Nueva York...



Amateur & Commercial

Radios"

KITTY SAYS: WE ARE NOW OPEN 7 DAYS A WEEK. Saturday & Sunday 10 to 5 PM

Monday-Friday 9 to 6:30 PM Come to Barry's for the best buys in town. For Orders Only Please Call: 1-800-221-2683.



ICOM

IC-R70, IC-720A, IC-730, IC-740, IC-25A/H, IC-35A IC-45A, IC-251A, IC-2KL, IC-471A, IC-290H, IC-751



FT-ONE, FT-980, FT-102, FT-77, FT-707, FT-230R FT-757 FT-726R, FT-480R, FT-720RU, FT-290R, FRG-7700, FT-625RD



ROCKWELL/COLLINS KWM-380

RSCII BRILLY

KANTRONICS

Field Day 2, Mini-Reader,

Interface, Software &

Code Tapes

VoCom/Mirage Tokyo Hy-Power Amplifiers & 5/8 \ HT Gain Antennas IN STOCK FT-708R FTC-1903

Computer Interface

stocked: MFJ-1224

AEA CP-1, Kantronics

YAFSU

FT-208R

Land-Mobile H/T Midland **ICOM** Wilson Mini-Com II IC2AT IC3AT Yeesu FTC-2203, FT-4703 Icom IC-M12 (Marine) IC4AT

SMART PATCH

EARTH SATELLITE STATION ESS-2250

CES-Simplex Autopatch 510-SA Will Patch FM Transceiver To Your Telephone. Great For Telephone Calls From Mobile To Base. Simple To Use - \$319.95

SANTEC ST-220/UP ST-144/UP ST-440/UP **NEW IMPROVED**

MURCH Model MFJ

UT2000B

900, 940B, 941C, & 496 HAM MasterTapes-Spectrum SCR-1000, 4000, & 77 Beta or VHS Tapes

Big Ham Clock/Ham Tags ICOM IC-RP 1210 (1.2 GHz) Complete Butternut Antenna Inventory In Stock!

Repeaters in Stock:

ICOM IC-RP 3010 (440 MHz)

Robot 800C - 1200C Color Mod Kits

Long-range Wireless Telephone for export

MAIL ALL ORDERS TO BARRY ELECTRONICS CORP., 512 BROADWAY, NEW YORK CITY, NY 10012.

BENCHER PADDLES & Vibroplex Keys In Stock!!

New TEN-TEC

DIGITAL FREQUENCY COUNTER Trionyx-Model TR-1000

0-600 MHz Digimax Model D-510 50 Hz-1GHz



Models

Tri-Ex Towers ly-Gain Towers & Antennas. and Rotors will be shipped direct

to you FREE of shipping cost.

AEA 144 MHz AEA 440 MHz ANTENNAS

In Stock

BIRD attmeters & **Elements**

EIMAC

3-500Z

572B, 6JS6C

12BY7A & 4-400A

2591 HT, Corsair In Stock

LARGEST STOCKING HAM DEALER COMPLETE REPAIR LAB ON PREMISES New York City's

"Aqui Se Habia Espanol"

BARRY INTERNATIONAL TELEX 12-7670 TOP TRADES GIVEN ON USED EQUIPMENT STORE HOURS: Monday-Friday 9 to 6:30 PM Parking Lot Across the Street

Saturday + Sunday 10 to 5 p.m. (Free Parking) AUTHORIZED DISTS. MCKAY DYMEK FOR SHORTWAVE ANTENNAS & RECEIVERS

IRT/LEX-"Spring St. Station" BMT-"Prince St. Station" IND-"F" Train-Bwy. Station"

Bus: Broadway #6 to Spring St.

Hell Sound Eq. Mike cartridges and books in stock.

We Stock: AEA, ARRL, Alpha, Ameco, Antenna Specialists, Astatic, Astron, B & K, B & W, Bash, Bencher, Bird, Butternut, CDE, CES, Collins, Communications Spec. Connectors, Covercraft, Cubic (Swan), Cushcraft, Daiwa, Dentron, Digimax, Drake, ETO (Alpha), Eimac, Encomm, Heil-Sound, Henry, Hustler (Newtronics), Hy-Gain, Icom, KLM, Kantronics, Larsen, MCM (Daiwa), MFJ, J.W. Miller, Mini-Products, Mirage, Newtronics, Nye Viking, Palomar, RF Products, Radio Amateur Callbook, Robot, Rockwell Collins, Saxton, Shure, Swan, Telex, Tempo, Ten-Tec, Tokyo HI Power, Trionyx TUBES, W2AU, Waber, Wilson, Yaesu Ham and Commercial Radios, Vocom, Vibroplex, Curtis, Tri-Ex, Wacom Duplexers, Repeaters, Phelps Dodge, Fanon Intercoms, Scanners, Crystals, Radio Publications.

WE NOW STOCK COMMERCIAL COMMUNICATIONS SYSTEMS DEALER INQUIRIES INVITED. PHONE IN YOUR ORDER & BE REIMBURSED.

COMMERCIAL RADIOS stocked & serviced on premises.

Amateur Radio & Computer Courses Given On Our Premises, Call Export Orders Shipped immediately. TELEX 12-7670

The Rub Out key is a function of the ASCII keyboard and is used when the Morse-keyboard operator desires to erase all of the information that is in the buffer memory. One-fourth of a quad 7402 NOR gate is used as an inverter. The master-reset voltage is zero. The master-reset line is held at +5 V by a 10k resistor and will not reset until a zero-volt level is received from the 7402 NOR gate inverter.

A 22-microfarad electrolytic capacitor from the master-reset line to ground ensures that the master reset has reset the buffer memory when the Morse keyboard is first turned on. If the capacitor was not there, the buffer memory could contain some unwanted information when the power is first turned on.

ASCII6-to-Morse Converter

The ASCII6-to-Morse converter portion of the Morse keyboard (Fig. 3) is made up of circuitry that converts the ASCII6 data from the buffer memory to usable Morse code. The ASCII6-to-Morse converter contains a memory circuit that is used as a code converter, a space-bar-operated word-space circuit, an automatic character-space circuit, a clock generator, a divider circuit, a sidetone generator, and output circuitry for operating the keying relay.

1702A Memory Circuit

A 1702A EPROM (erasable programmable memory), U9, is used as an ASCII6-to-Morse converter and converts the data from the buffer memory to Morse code. The 1702A has a total of 2048 storage locations and has an overall configuration of 256 by 8. This means that there are 256 address locations with 8 parallel outputs for each address location.

I have chosen 4 groups of

Signal source		Address inputs			
CD4040 Address	Q1 Q2 Q3	A B C	74151 Demultiplexer		
Divider	Q4 Q5	A0 A1			
ASCII6 From Buffer	Bit 1 2 3 4	A2 A3 A4 A5	1702A Memory circuit		
Memory	5 6	A6 A7			

Table 1. Address and divider information.

8 outputs for a total of 32 storage locations for each Morse-code character. This arrangement allows room for up to 62 Morse-code characters and a word space in the 1702A memory circuit.

The ASCII6 data addresses the 1702A for the desired Morse-code character. (The ASCII keyboard will supply 8 bits of information for each character, but with the Morse keyboard, only the ASCII6 or bits 1 through 6 are used.) The ASCII6 data addresses the 1702A memory circuit so that a respective 32-baud storage section of the memory circuit is selected for the desired character.

The 1702A memory circuit is programmed so that each storage location is equivalent to one baud. The Morse-code characters are broken down so that a dot is one baud in length and is programmed into the memory circuit as a 1; a dash is 3 bauds in length and is programmed as 3 ones in a row. A character space is 3 zeroes in a row. A space between dots and dashes is 1 zero. A word space is 7 zeroes in a row and will be handled in a special way in the ASCII6to-Morse converter circuitry. (The 1702A memory circuit normally contains all zeroes until programmed.)

None of the Morse-code characters uses all of the 32 bauds or 32 storage locations assigned to them. The shortest Morse-code character, the letter E, uses 1

baud for the code character plus 3 bauds for the character space for a total of 4 bauds. The longest Morse-code character used in the Morse keyboard is the number zero. It uses 19 bauds or storage locations for the Morse-code character plus 3 bauds for the character space for a total of 22 bauds or storage locations in the memory circuit.

74151 Demultiplexer

The output of the 1702A memory circuit is in an 8-bit parallel form and must be converted to a serial form in order to key a transmitter properly. The parallel information from the 1702A memory circuit is converted to serial information with a 74151 demultiplexer integrated circuit, U10. The 74151 demultiplexer uses 3 binary address signals to assist in converting from the 8 parallel inputs to the serial outputs. Output Y is inverted.

Fig. 4 shows a flow of the data from the ASCII keyboard to the output of the 74151 demultiplexer. Some examples of code characters are shown in the buffer memory and at the output of the 1702A and 74151.

Character-Space and Shift-Out-Pulse Circuit

The ASCII6-to-Morse converter circuitry is designed so that it will accept the Morse-code information for each Morse-code character plus 3 zeroes at the end of the character for a character space. If there

are more than 3 zeroes at the end of a character, the character-space circuitry will accept the first 3 zeroes and then proceed to the next Morse-code character, ignoring the remaining zeroes. In the memory circuit, a letter E, for example, will be followed by 31 zeroes, but the character-space circuitry will accept only the first 3 and ignore the remaining 28 zeroes.

The 74177 characterspace-divider circuit, U14, is connected so that it will accept 3 zeroes in a row and then supply a very short duration shift-out pulse to the buffer memory. The shift-out pulse initiates the start of the next Morsecode character or word space and also resets the 1702A memory circuit and a CD4040 address-divider circuit, U13. When the memory circuit and divider circuit have been reset, the ASCII6-to-Morse converter circuitry is ready to accept the next ASCII6 character from the buffer memory. The reset and shift-out pulse from the 74177 character-space divider is extremely short in duration. It will not interfere with the timing of the first baud of the next Morse-code character.

The character-space divider is reset every time a dot or dash is received from the 74151 demultiplexer. The Morse-keyboard clockgenerator signal is fed into the input of the characterspace divider. When 3 zeroes in a row are present at the reset input of the character-space circuit, a pulse is then present at the divider output, Qc, which is the buffer-memory shift-out pulse and also the reset pulse for the CD4040 address divider and the 1702A memory circuit. As soon as the shift-out pulse is generated, a new ASCII6 character is shifted out of the buffer memory and presented to the 1702A memory cir-



Connect your computer to the air!

The "AIRWAVES" that is, thru the Microlog AIR-1, a single board terminal unit AND operating program in ROM that needs no external power supply or dangling extras to put your computer on CW & RTTY. And what a program! The famous Microlog CW decoding algorithms, superior computer enhanced RTTY detection, all the features that have made Microlog terminals the standard by which others are compared. Convenient plug-in jacks make connection to your radio a snap. On screen cross tuning indicator and audio pitch reference tone make it easy to use. The simple, one board design makes it inexpensive. And Microlog know-how makes it best! There's nothing left out with the AIR-1. "HARD-WARE" front end has: AFSK, PTT, ± CW/FSK keying

loop switch, hand key input and dual tone mark/ space RTTY DEMOD plus single tone CW detector. "SOFTWARE" in onboard ROM has: split screen, large type ahead transmit buffer, automatic keyword controlled receive data storage, WRU, SELCAL printer control and user programmable memories that can dump/store on disc and tape. Full speed RTTY, 60 to 132 wpm, CW to 150 wpm, 110/300 ASCII and optional 4 mode AMTOR operation covers all the bases. If you've been waiting for the right system at the right price, or you've been disappointed with previous operating programs, your time is now. At \$199, the complete AIR-1 is your answer for VIC-20 and "64" (with 4 mode AMTOR, \$279). Join the silent revolution in RTTY/CW and get ON-THE-AIR! See it at your local dealer or give us a call at Microlog Corporation, 18713 Mooney Drive, Gaithersburg, Maryland 20879. TEL (301) 258 8400. TELEX 908153.

Note: VIC-20 is a trademark of Commodore Electronics, Ltd.

MICROLOG

√ 51

INNOVATORS IN DIGITAL COMMUNICATION

	Address	Output	AS	01101100	10111010
Α	00000100	10111000		01101101	10100000
В	00001000	11101010	,	10110000	11101110
	00001001	10000000		10110001	10101110
C	00001100	11101011	D14	10110010	11100000
	00001101	10100000	ВК	10110100 10110101	11101010 10111010
D	00010000	11101010		10110101	11100000
E	00010100	10000000		10111000	10111010
F	00011000	10101110		10111001	11101011
	00011001	10000000		10111010	10000000
G	00011100	11101110	1	10111100	11101010
	00011101	10000000		10111101	11101000
Н	00100000	10101010	Wor	d Space	
t	00100100	10100000		10000000	10000000
J	00101000	10111011	0	11000000	11101110
	00101001	10111000		11000001	11101110
K	00101100	11101011		11000010	11100000
	00101101	10000000	1	11000100	10111011
L	00110000	10111010		11000101	10111011
	00110001	10000000		11000110	10000000
М	00110100	11101110	2	11001000	10101110
N	00111000	11101000		11001001	11101110
0	00111100	11101110	3	11001100	10101011
	00111101	11100000	4	11010000	10101010
P	01000000	10111011	4	11010000	11100000
	01000001	10100000	5	11010100	10101010
Q	01000100 01000101	11101110	5	11010101	10000000
-		10111000	6	11011000	11101010
R	01001000	10111010	·	11011001	10100000
S	01001100	10101000	7	11011100	11101110
T	01010000	11100000		11011101	10101000
U	01010100	10101110	8	11100000	11101110
V	01011000	10101011		11100001	11101010
	01011001	10000000	9	11100100	11101110
W	01011100	10111011		11100101	11101110
	01011101	10000000		11100110	10000000
X	01100000 01100001	11101010	SK	11101000	10101011
V		11100000	4.0	11101001	10101110
Υ	01100100 01100101	11101011 10111000	AR	11101100 11101101	10111010
Z	01100101	11101110	?		
_	01101000	10100000		11111100	10101110

Table 2. 1702A programming truth table.

cuit which in turn is routed through the 74151 as a Morse-code character and resets the 74177 character-space divider. The 74177 character-space divider does not have a chance to generate a very long duration pulse because of the quick action of the 1702A memory circuit and the 74151 demultiplexer.

Clock Generator and Address Divider

The ASCII6-to-Morse converter uses a 555 timer

as a clock generator (U12). The clock generator operates at 2 times the bit rate of the Morse code. The clock generator is varied in frequency in order to vary the speed of the outgoing Morse code. The clock-generator signal is fed to the 74177 character-space divider and a CD4040 binary address divider, U13.

The ASCII6 data from the buffer memory addresses the 1702A memory circuit for the respective 32-baud storage section assigned

the Morse-code character. However, additional addressing is needed to break down the Morse-code signals to the 8 parallel outputs of the 1702A memory circuit and to further break down the signal to a serial form in the 74151 demultiplexer. The additional binary addressing is supplied by the CD4040 divider circuit. Table 1 shows a breakdown of the signal sources and address locations. Q1, Q2, and Q3 are binary signals used to address the 74151 demultiplexer; U10 and O4 and Q5 outputs are address signals for the 1702A memory circuit.

1702A Programming Information

Table 2 is the truth table for programming the 1702A EPROM. The address and output information for the 1702A memory circuit is shown in binary form for simplicity. There are 8 address bits. The first 6 address bits are the ASCII6 data and the last 2 bits are needed to break down the information in the 32-baud storage sections into the 8 parallel outputs of the 1702A memory circuit. Of the 8 address bits, the first 6 bits reading from left to right are bit 6, bit 5, bit 4, bit 3, bit 2, and bit 1 of the ASCII6 data. The 7th address bit, reading from left to right, corresponds to the Q5 output of the CD4040 address divider and the 8th bit corresponds to Q4. The address inputs of the 1702A memory circuit, reading from left to right, are A7. A6, A5, A4, A3, A2, A1, and AO.

The address for the letter A will be 00000100. The letter B, which is more than 8 bauds in length, will have 2 addresses. They are 00001000 and 00001001. Note that bit 8 of the address has changed. The output programming of the 1702A memory circuit will be 11101010 and 10000000.

Note that the first 3 bauds are a dash. Bauds 5, 7, and 1 of the next group are dots. They make up the dash and 3 dots of the letter B. Longer Morse-code characters such as the number zero will take 3 sets of addresses for the programming of the memory circuit.

The 1702A memory circuit is normally all zeroes before programming. The memory circuit need only be programmed for 1s. A special programmer must be used with the 1702A EPROM and the memory circuit may be erased with ultraviolet light and programmed again if desired.

CD4048 Word-Space Gate

The Morse keyboard uses an ASCII-keyboard space-bar-operated word space that is handled in much the same way as a regular Morse-code character. The one big difference is that it is silent at the output of the Morse keyboard. The word space must be 7 bauds in length and must work correctly with the 74177 character-space divider.

The ASCII6 code for a word space is 100000. It is the only ASCII6 character that has zeroes for bit 5, bit 4, bit 3, bit 2, and bit 1. There is an ASCII6 blank that has all zeroes, but it is not used with the Morse keyboard. The 1702A programming address for the word space is 10000000. An E is programmed into the 1702A for a word space and is shown as 10000000 also.

An 8-input expandable gate is used as the word-space gate and is connected as an 8-input OR gate. 3 of the inputs to the OR gate are grounded and the other 5 inputs are connected to bit 5, bit 4, bit 3, bit 2, and bit 1. If any input of the CD4048 OR gate is receiving a 1, the output will show a 1. If all of the inputs are zero, then the output will be zero. If there is a zero at the output of the CD4048

step up to the best...

Without doubt LR-1 is the repeater value leader! Compare its outstanding performance with any repeater -- then look at its price. LR-1 features include individual die-cast shielding of receiver and transmitter plus a separately shielded 6-stage receiver prefilter for peak performance in harsh RF environments . Front panel metering of all vital functions • CW identifier • Symmetric hard limiting for clean natural audio . Low power MOS control logic . Even the cabinet is included -- just plug in and go!

LINKING? The LR-1 is also available with control circuitry for Link Transceiver operation. Now link repeater sites with the flexible control capability you've always wanted.

HIGH POWER? Our PA-75 power amplifier is the champion! Ruggedly built to give years of dependable operation in continuous duty repeater service.



Mark 3C repeaters and controllers have no equal in performance. Both units feature auto patch, reverse autopatch, autodial, 13 Morse messages and a total of 39 functions. Both feature microprocessor control and both have been proven in the field from icy Alaska to tropical Brazil. A Mark 3C supercontroller can make any repeater a super performer. The Mark 3CR repeater is in a class by itself. It combines superbly designed RF circuitry in one handsome package. It is without doubt the world's most advanced repeater!

CALL OR WRITE FOR FULL DETAILS

MICRO CONTROL SPECIALTIES

23 Elm Park • Groveland, Massachusetts 01834 • Telephone (617) 372-3442

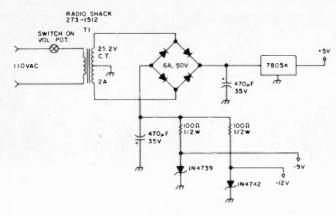


Fig. 5. Power supply schematic.

word-space OR gate, the output circuitry of the ASCII6-to-Morse converter will be silenced. There will be a silent E present at the output of the Morse keyboard which is 4 bauds long. When added to the 3 zeroes of the previous character space, there will be a total of 7 silent bauds, which is the length of a word space. Since the word space is treated much the same as an ASCII6 character, it will be treated like one in the buffer memory.

Output Gates

In the output circuitry of the ASCII6-to-Morse converter, there are 4 NAND gates, designated U15A, U15B, U15C, and U15D. U15B and U15D are connected as inverters.

U15A is connected as a NAND gate and combines the output-ready signal from the buffer memory and the serial-output signal from the 74151 demultiplexer, U10. The outputready signal also resets the 555 clock generator, U12. The output-ready signal is used to synchronize the buffer-memory output signals and the clock generator. Without the synchronizing of the signals, it would be possible to miss a part of the first baud of the Morse-code character.

U15C is also connected as a NAND gate and combines the output of the word-space gate with the signal from U15B and determines whether the output will be silenced for a word space or enabled for a regular Morse-code character.

U15D is an inverter and a buffer for the output signal.

Sidetone Generator

A 555 timer, U16, is connected as a sidetone generator for monitoring the outgoing Morse code. It generates an audio tone and is keyed by the signal from U15D. The sidetone generator has an output transformer with an output for an 8-Ohm speaker or 8-Ohm headphones. The frequency of the sidetone generator is approximately 800 Hertz. The sidetone generator has a volume control. The volume may be turned up when using a speaker and turned down if headphones are used. The 1N914 diode across the primary of the output transformer furnishes a more pleasant tone at the output of the sidetone generator.

Keying Relay

I am using a Radio Shack #275-215, double-pole double-throw miniature plug-in relay for the transmitter keying relay. It is a 5-volt relay with a 50-Ohm relay coil. I bent the relay contacts closer together to improve the response time of the relay. A 2N2222 transistor amplifier is used as a relay driver. The relay plugs into a regular 16-pin DIP socket.

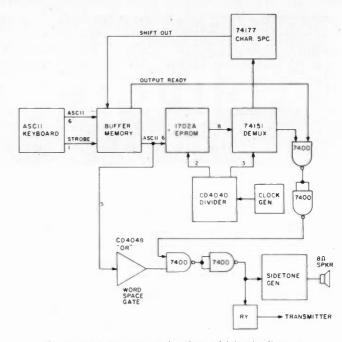


Fig. 6. N7AGK Morse keyboard block diagram.

Power Supply

Fig. 5 is a schematic of the Morse-keyboard power supply. It supplies 5 volts at approximately 1 Ampere, minus 9 volts at approximately 25 milliamperes and minus 12 volts at approximately 25 milliamperes. A Radio Shack #276-1363 power transformer is used for the low-voltage power source. The secondary winding of the transformer supplies 25.2 volts at 2 Amperes. A bridge rectifier is connected so that one side of the rectifier supplies the plus voltage in reference to the transformer center tap and the other side of the rectifier supplies a minus voltage in reference to the center tap. The plus side goes to a 5-volt regulator and the minus 9 volts and the minus 12 volts are taken from zener-diode circuits. The transformer center tap is at ground potential. The 1702A memory circuit uses plus 5 volts and minus 9 volts. The 3341 first-in/firstout shift register uses plus 5 volts and minus 12 volts. All of the other circuits just require plus 5 volts. A good heat sink must be used with the 5-volt regulator to prevent overheating of the regulator.

Operating Instructions

The Morse keyboard has been designed to send perfect Morse code with perfect spacing. It has a buffer memory which allows the Morse-code operator to type up to 192 characters ahead of the outgoing Morse code. The buffer memory will store the characters until they are needed. If the operator presses the Store key, he may store a small message and then send it out when the Send key is pressed. The message will be stored in the buffer memory as long as power is supplied to the Morse keyboard. I have stored a message overnight and then listened to it in the morning when I pressed the Send key.

The buffer memory also allows the Morse-code operator to type at an uneven rate and to stop at certain intervals if desired. If the Morse-code operator pauses too long, he may find that the buffer memory has emptied of information and there will be uneven spacing of the Morse-code characters until he has gained a head start on the outgoing Morse code again.

A message or transmis-



HF Transceivers:	Regular SALE
IC-740 9-band 200w PEP Xcvr	\$ 1099.00 94995
plus FREE PS-740 internal po	ower supply &
\$50 Factory Rebate	until gone!

plus FREE PS-740 internal power	er supp	ly &
\$50 Factory Rebate	intil go	one!
PS-740 Internal power supply		
*EX-241 Marker unit	20.00	175
*EX-242 FM unit	39.00	
*EX-243 Electronic keyer unit	50.00	
*FL-45 500 Hz CW filter (1st IF)	59.50	
*FL-54 270 Hz CW filter (1st IF)	47.50	
*FL-52A 500 Hz CW filter (2nd IF)	96.50	
*FL-53A 250 Hz CW filter (2nd IF)	96.50	
*FL-44A SSB filter (2nd IF)	159.00	14495
SM-5 Electret desk microphone	39.00	
HM-10 Mobile scan microphone	39.50 19.50	
MB-12 Mobile mount		3
*Options also for IC-745 listed by		E0085
IC-730 8-band 200w PEP Xcvr w/mic FL-30 SSB filter (passband tuning)	59.50	299"
FL-44/A SSB filter (2nd IF)	159.00	1 4 4 9 5
FL-45 500 Hz CW filter	59.50	144
EX-195 Marker unit		
EX-202 LDA interface; 730/2KL/AH-1		
EX-203 150 Hz CW audio filter		
EX-205 Transverter switching unit	29.00	
SM-5 Electret desk microphone	39.00	
HM-10 Mobile scan microphone	39.50	
MB-5 Mobile mount	19.50	
IC-720A 9-band Xcvr/.1-30 MHz Rcvr \$		89995
FL-32 500 Hz CW filter	59.50	
FL-34 5.2 KHz AM filter	49.50	
MB-5 Mobile mount	19.50	
IC-7072 transceive interface, R-70		
IC-745 9 band xcvr/.1-30 MHz rcvr		
PS-35 Internal power supply	160.00	14495
CF5-455K5 2.8 KHz wide SSB filter		
SM-6 Desk microphone	39.00	
HM-12 Hand microphone		*
See IC-740 list above for other o	ptions (7



0.000	C	
IC-751 9-band xcvr/.1-30 MHz rcvr\$	1399.00	1229
PS-35 Internal power supply	160.00	
FL-52A 500 Hz CW filter	96.50	8995
FL-53A 250 Hz CW filter	96.50	8995
FL-33 AM filter	31.50	
SM-6 Desk microphone		
HM-12 Hand microphone		
External frequency controller	TBA	
High stability reference crystal	TBA	
Options: 720/730/740/745/751	Regular	
PS-15 External 20A power supply	\$149.00	13495
EX-144 Adaptor; CF-1/PS-15	6.50	
CF-1 Cooling fan for PS-15	45.00	
PS-20 20A switching ps w/speaker	229.00	19995
CC-1 Adaptor; HF radio to PS-20	10.00	

TOO	<u> </u>	Ш
Options - continued	Regular	SALE
CF-1 Cooling fan for PS-20	45.00	
SP-3 External speaker	49.50	
Speaker/phone patch (specify radio) BC-10A Memory back-up	139.00 8.50	12955
EX-2 Relay box w/marker	34.00	
AT-100 100w 8-band automatic ant tuner	349 00	31495
AT-500 500w 9-band automatic ant tuner	349.00 449.00	39995
MT-100 Manual antenna tuner	249.00	
AH-1 5-band mobile ant w/tuner GC-4 World clock	289.00 99.95	
	33.33	33.
HF Linear amplifier 1C-2KL 160-15m/WARC solid state linear	1795.00	1299
VHF/UHF Multi-modes IC-251A 2m FM/SSB/CW xcvr	\$749.00	549 ⁹⁵
\$50 Factory Rebate	intil go	one!
IC-551D 80w 6m Xcvr	\$699.00	59995
PS-20 20A switching ps/spkr	229.00	19999
EX-106 FM adaptor	125.00	11295
BC-10A Memory back-up	8.50	
SM-2 Electret desk microphone	39.00	76095
IC-451A 430-440 SSB/FM/CW Xcvr/ps IC-451A/High 440-450 MHz Xcvr/ps	899.00	76995
AG-1 15 db preamp, IC-451A/45A	89.00	7995
Z 1111111 ()		
IC-271A 2m, 25w xcvr	699.00	
IC-471A 430-450 MHz, 10w xcvr PS-25 Internal power supply	799.00 TBA	/19.
HM-12 Hand microphone	39.50	
SM-6 Electret desk microphone	39.00	
VHF/UHF FM	Regular	SALE
IC-25A 2m, 25w, up-dn-ttp mic, grn leds IC-25H as above, but 45 watts	389.00	31973
IC-45A 440 FM xcvr, 10w, TTP mic	399.00	35995
BU-1 Memory back-up	38.50	
IC-22U 10w 2m FM non-digital Xcvr	299.00	24995
EX-199 Remote frequency selector	35.00	
RP-3010 440 MHz repeaterVHF/UHF multi-modes:	999.00	
IC-290H 25w 2m SSB/FM Xcvr, TTP mic	\$549.00	48995
IC-560 10w 6m SSB/FM/CW Xcvr	489.00	43995
IC-490A 10w 430-440 SSB/FM/CW Xcvr	649.00	5/955
VHF/UHF Portables: IC-202S 2m port. SSB Xcvr, 3w PEP	\$279 00	24995
IC-505 3/10w 6m port. SSB/CW Xcvr	449.00	39995
IC-505 3/10w 6m port. SSB/CW Xcvr IC-402 432 portable SSB xcvr	389.00	29995
BP-10 Internal nicad battery pack	79.50	
BC-15 AC charger EX-248 FM unit	12.50 49.50	
SP-4 Remote speaker	24.95	
LC-10 Leather case	34.95	
IC-3PS Power supply for portables	95.00	8995



Hand-held Transceivers

Synthesized; 800 channels; 1.5/.15 watts; 250 ma. NiCd Pak; AC wall charger; flexible antenna; earphone; wrist strap; belt clip. Models with or without Touch Tone® Pad (TTP).

Model	Regular	SALE
IC-2A for 2 meters \$	239.50	21495
IC-2AT with TTP	269.50	21995
IC-3A for 220 MHz	269.95	23495
IC-3AT with TTP	299.95	23995
IC-4A for 440 MHz	269.95	23495
IC-4AT with TTP	299.95	23995
ar Hand holds	D.	agular

Accessories for Hand-helds:	Regular
BC-25U Extra 15-hour wall charger	.\$10.00
BC-30 1/15-hour drop-in charger for BP-2/3/5	69.00
BP-2* 450 ma, 7.2v 1w ext. time battery	39.50
BP-3 Extra std. 250ma 8.4v 1.5w battery	
BP-4 Alkaline battery case	
BP-5* 450 ma, 10.8v 2.3w hi-power battery	49.50
*BC-30 required to charge BP-2 & BP-5	45.50
	10.00
FA-2 Extra 2m flexible antenna	10.00
CA-2 Telescoping 1/4-wave 2m antenna	10.00
CA-5 5/8-wave telescoping 2m antenna	18.95
CA-3 Extra 220 flexible antenna	
CA-4 Extra 440 flexible antenna	
CP-1 Cigarette lighter receptacle chgr for BP-3.	
DC-1 DC operation module	
HM-9 Speaker/microphone	
LC-2A Leather case without TTP cutout	
LC-2AT Leather case with TTP cutout	34.95
ML-1 2m 2.3/10w HT amp. (Reg. \$89)SALE	79.95
3A-TTN 16-button TTP front for 2A/3A/4A	39.50
CommSpec SS-32M 32-tone encoder	29.95
ML-25 2m 20w HT amp. (Reg. \$199.50) SALE	
IC-M12 12 ch Marine hand-held SPECIAL	
IO-MIZ IZ CII INGILIIC IIGINU'IICIU SFECIAL	200.00



Short R-70	wave 100KHz	receive -30MHz	r digital	recei	ver	r SALE 59995

til 10/30/83 - purchase R-70 and receive certificate for free GC-4 World Clock (\$9995 Value) from ICOM.

EX-257 FM unit	38.00
IC-7072 Transceive interface, 720A	112.50
FL-44/A SSB filter (2nd IF)	159.00 14495
FL-63 250 Hz CW filter (1st IF)	48.50
SP-3 External speaker	49.50
EX-299 (CK-70) 12V option	9.95
MB-12 Mobile mount	19.50





HOURS: Mon. thru Fri. 9-5:30; Sat. 9-3 Milwaukee WATS line 1-800-558-0411 answered evenings until 8:00 pm, Monday thru Thursday. Please use WATS line for Placing Orders. For other information, etc. please use Regular line.

Order Toll Free: 1-800-558-0411

In Wisconsin (outside Milwaukee Metro Area) 1-800-242-5195

IC-20L 2m amp, 10w PEP or FM

RP-1210 10w 1.2 GHz repeater

Cabinet for RP-1210 or RP-3010.....

IC-30L 432 amp, 10w PEP/FM...... 105.00

1.2 GHz equipment IC-120 1w 1.2 GHz FM xcvr \$499.00 449*

4828 W. Fond du Lac Avenue; Milwaukee, WI 53216 - Phone (414) 442-4200

AES BRANCH STORES -

WICKLIFFE, Ohio 44092 28940 Euclid Avenue Phone (216) 585-7388 Ohio WATS 1-800-362-0290 Outside 1-800-321-3594

ORLANDO, Fla. 32803 621 Commonwealth Ave. Phone (305) 894-3238 Fla. WATS 1-800-432-9424 Outside 1-800-327-1917

1898 Orew Street Phone (813) 461-4267 No In-State WATS

No Nationwide WATS

CLEARWATER, Fla. 33575 LAS VEGAS, Nev. 89106 1072 N. Rancho Orive Phone (702) 647-3114 No In-State WATS

98.00 8995

TBA

249.00

Outside 1-800-634-6227

Associate Store

CHICAGO, Illinois 60630 ERICKSON COMMUNICATIONS 5456 N. Milwaukee Avenue Phone (312) 631-5181 Outside 1-800-621-5802

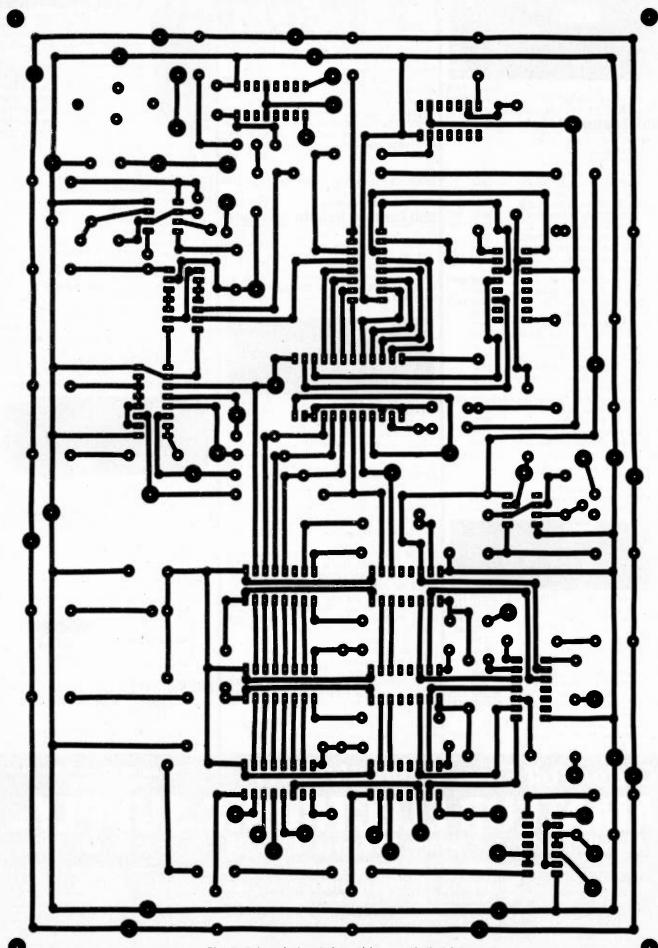


Fig. 7. Printed circuit board layout (foil side).

sion should always be started with at least one word space. If the operator desires to get a good head start on the Morse keyboard, he may need to press several word spaces in rapid succession. If the Morsecode operator desires to store a message, he should start with a word space. If a message is started with a character instead of a word space while in the Store mode, the operator will hear a steady tone. The steady tone may be used to tune the transmitter. To stop the steady tone, press the Rub Out key or the Send kev.

Sometimes it is convenient to type part of a message into the buffer memory while receiving Morse code from the other station being worked.

At first, some people may become confused when hearing the Morse code going out after they had previously typed it into the

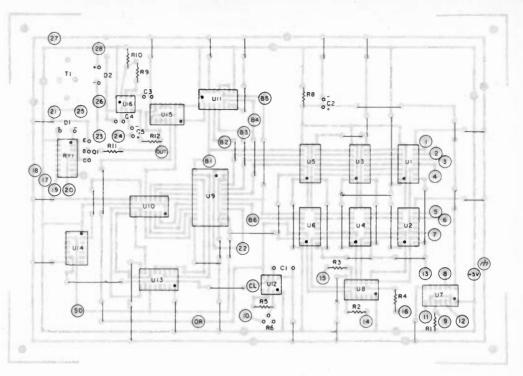


Fig. 8. Component layout.

Morse keyboard. The Morse keyboard has a sidetone generator for monitoring the outgoing Morse code, but not for monitoring the code before it enters the

buffer memory. It would be almost impossible to monitor the Morse code as it is being typed into the Morse keyboard. It would not be practical to use the

extra circuitry that it would require to do it. After a little practice, the Morse-code operator will find that it is very easy to type a message correctly while monitoring

PRINTED CIRCUIT BOARD ASSEMBLY

The printed circuit for the N7AGK Morse keyboard has been laid out on a 7-inch by 10-inch single-sided printed circuit board. The printed circuit layout has been especially arranged for ease of assembly. All external wiring connections to the printed circuit are made with push-in terminals.

All jumpers, sockets, terminals, and parts are shown on the printed circuit parts drawing. The drawing shows the parts side of the printed circuit board which is opposite the foil side.

The Jumpers should be installed and soldered first. The Jumper wire is pre-tinned, 24-gauge, copper bus wire. The Jumper wires are shown as dark lines on the parts-side printed circuit drawing.

The resistors and diodes should be installed and soldered next

Sockets are recommended for the Integrated circuits and the keying relay. The sockets must be installed so that the notch end corresponds to the black dot on the parts-side printed circuit drawing. Extreme care must be taken when soldering sockets to prevent bridging across of the solder. A low-power solder iron and good quality, small-diameter, rosincore solder is recommended. Do not overheat the solder connections and do not use excessive amounts of solder for the solder connections.

When installing C2 and C5, be sure to watch for correct polarity.

Install the 2N2222 keying driver transistor with approximately 3/8 inch of the transistor lead remaining between the transistor and the solder connection. Be careful not to use excessive heat when soldering the transistor leads to the printed circuit.

The black lead of T1 is not used. It may be clipped off if desired.

Install the push-in terminals as shown on the printed circuit drawing. Install output transformer T1 and solder the leads to their respective push-in terminals as shown in Printed Circuit Board Terminal Connections for connections 25, 26, 27, and 28.

Install and solder C4, C3, C1, and R6. (This should complete the printed circuit board assembly.)

Check the assembled printed circuit board carefully before attempting to use the circuit board in your Morse keyboard.

PRINTED CIRCUIT BOARD TEST TERMINALS

B1, B2, B3, B4, B5, and B6 are the ASCII information bits coming from the output of the buffer memory and going into the 1702A EPROM, U9, and the CD4048 word-space OR gate, U11.

SO is the shift-out pulse line from the 74177 characterspace divider, U14. The shift-out pulse initiates the presentation of the next ASCII6 character from the buffer memory. It may be used as an external sync trigger pulse when viewing the outgoing Morse code on an oscilloscope.

OR is an output-ready signal line from the buffer memory. It resets the clock generator and ensures that the outgoing Morse code is in sync with the clock generator.

CL is the clock-generator output. It has a pulse rate that is 2 times the baud rate of the outgoing Morse code.

OUT is the outgoing Morse-code test point.

The ground and +5-volt connections for the ASCII keyboard may be taken from the extra terminals shown at the right of the parts-side drawing.

PRINTED CIRCUIT BOARD TERMINAL CONNECTIONS

The N7AGK ASCII6-to-Morse converter printed circuit board uses small push-in terminals (Radio Shack 270-1394) for all external connections and test points. They are inserted from the parts side of the printed circuit board and soldered in place. When wiring to the printed circuit board, all connections should be made on the foil side.

Connections 1, 2, 3, 4, 5, and 6 are the ASCII6 bit connections from the ASCII keyboard. Bit 1 is pin 7 on the ASCII keyboard. Bit 2 is pin 6, bit 3 is pin 5, bit 4 is pin 4, bit 5 is pin 11, and bit 6 is pin 10. (See the Keytronic data sheets.)

Connection 7 is a strobe- or keypunch-pulse connection to the ASCII keyboard. It is connected to pin 12 on the ASCII keyboard.

Connection 8 is Rub Out and is connected to the Here Is key, pin K on the ASCII keyboard.

Connection 9 is to the speed potentiometer counterclockwise terminal (looking from the bottom).

Connection 10 is to the center terminal of the speed potentiometer.

Connection 11 is Store and is connected to the Rept key, pin H on the ASCII keyboard.

Connection 12 is Send and is connected to the Break key, pin J on the ASCII keyboard.

Connection 13 is -12 volts and comes from the power supply.

Connection 14 is a connection to the green LED buffer memory indicator light. The connection is made to the negative side or flatted side of the LED. The positive lead of the LED goes to +5 volts.

Connection 15 goes to the negative side of the yellow LED. Connection 16 goes to the negative side of the red LED. Connection 17 is +5 volts from the power supply.

Connection 18 is to ground.

Connections 19 and 20 are the relay contacts for keying the transmitter. Connection 19 goes to the ground connection of the keying jack at the rear of the Morse-keyboard cabinet and connection 20 goes to the other connection of the keying jack. The keying jack is a standard phone jack.

Connection 21 goes to the phone or speaker jack on the front of the Morse keyboard. The other connection is grounded.

Connection 22 is -9 volts from the power supply.

Connection 23 is the counterclockwise connection to the volume potentiometer (looking from the bottom).

Connection 24 is the center connection to the volume pot. The remaining connection on the volume pot goes to +5 volts.

Connection 25 is for the red wire from T1. Connection 26 is for the green wire from T1. Connection 27 is for the white wire from T1. Connection 28 is for the blue wire from T1.

the outgoing code. An error in typing is easily recognized by the Morse-code operator and may be corrected by hitting the word-space bar and then sending a question mark and then hitting the word-space bar again and then sending the word or characters again correctly.

The Morse keyboard is an excellent device for learning the Morse code or for increasing one's code speed. A portion of a Morse-code practice transmission may be copied on the Morse keyboard by pressing the Store key and copying the Morse code and then playing the Morse code back at a slower speed by adjusting the speed control and pressing the Send key. The Morse code is played back at a slower speed to check for accuracy of receiving the practice transmission.

Another person who does not know the Morse code

himself may type characters into the Morse keyboard and send them at a speed that is comfortable for a person learning the Morse code. The Morse-code speed may be set for a certain speed and the characters spaced for several seconds if desired.

As the Morse-code learner becomes better at receiving the code, the spacing between characters may be gradually decreased until it becomes the normal character spacing. Another method of spacing is to use a word space or two in place of a character space and then add several word spaces in place of a normal word space to distinguish between words or groups of Morse-code characters.

The speed of the Morse keyboard may be set for a range of approximately 5 words per minute to over 70 words per minute. It is easy to stay ahead of the outgoing Morse code when operating at the slower speeds, but at the higher speeds it becomes increasingly more difficult to stay ahead. The Morse-code operator should never send out Morse code at a higher speed than he can copy comfortably unless he is using a video readout for monitoring the transmission. Even with a video readout it can be risky business when external interference prevents the video readout from receiving the Morse code correctly.

Typing will be no problem for the beginning operator as long as he is careful to type according to standard typing procedure. An operator should never type using the "hunt and peck" system because it will hinder him later when he desires to increase his Morse code and typing speed.

Most beginning Morsecode operators will find that it is usually easier to increase one's typing speed than it is to increase one's Morse-code speed. A beginner should endeavor to type faster than he normally can receive the Morse code in order to stay ahead of the outgoing Morse code when using the Morse keyboard. For instance, a Morse-keyboard operator who can send and receive code at 15 words per minute must be able to type faster to stay ahead of the outgoing Morse code. If he cannot type faster than the outgoing Morse code, he may have trouble when short Morse-code characters like E and I, etc., appear frequently in the message.

One of the principal advantages of the Morse keyboard is the ability to send perfect Morse code at higher speeds than is possible otherwise. Many Morsecode operators reach the limit of their code-sending abilities at approximately 30 words per minute. The Morse keyboard extends the range that the Morsecode operator may otherwise attain. The ability to send and receive Morse code more accurately and more easily is a decided advantage for the Morse-code operator.

Construction

The printed circuit board is a single-sided, 7-inch by 10-inch board that has been laid out for easy assembly and soldering. I spaced the layout so that none of the jumper connections or terminal connections is very close to any other one. The closest solder connections are for the integrated-circuit socket connections.

I have used push-in solder terminals for the connections to and from the printed circuit board and for some of the test terminals.

The photograph shows two Jones terminal strips for connections between the printed circuit board and other locations of the Morse keyboard. These are not absolutely necessary and may be omitted. I have been using them for testing purposes

The printed circuit board and the metal plate for the power supply are mounted on the bottom of the keyboard cabinet on metal standoffs. The wiring from the printed circuit board to other parts of the Morse keyboard is brought out from the bottom side or the foil side of the board.

Availability of Components

I will supply a drilled and etched printed circuit board for \$25.00 postpaid in the US and Canada along with complete instructions for wiring and assembly. I will supply a programmed 1702A EPROM for \$10.00 or program a reader-supplied 1702A EPROM for \$6.00 postpaid

I will supply a Keytronic model 1.1648, 53-key, ASR-33 data - communications ASCII keyboard with the proper keytops for \$100 postpaid in either the US or Canada. The ASCII kevboard uses a capacitancetype keyswitch and has over a 100-million-keystroke reliability. The keyboard is fully assembled and has a rigid mounting frame and removable twoshot molded keytops. (A two-shot molded keytop is one that has the character molded within the keytop so that it will not wear off with continued use.) The ASCII keyboard is available with schematic and data sheets.

The Morse-keyboard cabinet is a 14-inch-wide by 11.3-inch-deep sloping panel keyboard cabinet manufactured by Hammond. The bottom portion is #1456 PL3 CBU and the matching top portion is #1456 PL3 PWH. It is the same keyboard cabinet as is shown in the photograph.

If the Morse-keyboard builder already has an ASCII keyboard, he may use it with the Morse keyboard. If the ASCII kevboard is of the same configuration as the one mentioned in the article, he may use it without making any changes to the truth table or the 1702A memory-circuit programming. If the keyboard is different, a new set of truth tables will need to be made and the 1702A memory circuit will need to be programmed for the ASCII keyboard. A layout of the keyboard should be worked out and a list made of the ASCII6 outputs for each of the keys to be used.

RTTY

*

RTTY

*

RTTY

*

RTTY

*

RTTY

*

RTTY

*

œ

Power must be applied to the ASCII keyboard and the voltages read for bits 1 through 6 for each character. A one will usually be plus 5 volts and a zero will be zero volts or ground potential. (Some characters may have the same ASCII6 data as other characters and this must be allowed for in the keyboard layout.)

The 1702A memory circuit does not need to be programmed according to the ASCII6 data but should follow it as closely as possible. There will be no problem with the letters and numbers characters, but some of the punctuation may not follow a strict ASCII6 conformity. None of the special communications characters such as break, wait, end of message, and end of transmission will follow any kind of ASCII pattern. Three function keys should also be selected for the Store, Send. and Rub Out keyboard functions.

Foreign characters may be selected for the Morse keyboard. The keytops will need to be labeled if the keytops are not available. A larger keyboard may be reguired for alphabets that require a larger number of characters such as the Japanese Kata Kana radio code. None of the foreign characters will be too long * RTTY * RTTY * RTTY * RTTY **BUILT TO WORK** WHEN OTHERS WON'T!

D

D

*


RTTY

*

D

*

D

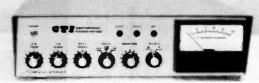

TMC-1B Computer Interface for RTTY/CW

The best performing unit under adverse band conditions, TMC-1B is designed to compare with the professional equipment that has been on the market for years, not just a piece of gear to get you into computer RTTY. No computer experience needed. Software is included for Vic-20. Will work with most micro computers and with most of the popular software available. Only CTI gives you all this and more * Auto start with a variable control on front panel, will only print on properly tuned RTTY signal * L C tuned circuit filters (no active filters) * Easy to tune with large meter for greater accuracy, also mark and space LEDs * Switchable between 2 rigs (no wires to change) * Built-in monitor speaker for monitoring the signal as you send it * High gain on input, turn your rig way down * Relay isolated CW key and P.T.T. * Simple hook-up * RS 232 * All metal cabinet * One year guarantee. \$299.95

Price Includes VIc-20 software in basic on cassette and computer cable VISA

Write or call for more information:



CONTEMPORARY TECHNOLOGY, INC.

P.O. BOX 1083 • SALEM, OR. 97308

503 - 399-7406

★ RTTY ★ RTTY ★ RTTY ★ RTTY

for the Morse keyboard, since the number zero is the longest Morse-code character used. All of the other characters are shorter than the number zero.

If more than 62 characters are needed, it would be best to redesign the Morse keyboard, use ASCII7 data, and use a larger capacity memory circuit. A 2704 EPROM would supply as many as 126 characters and a word space if there were that many Morse-code characters available. Both uppercase and lowercase positions would need to be used on the ASCII keyboard. There would be very few requirements for that type of arrangement.

Most of the integrated circuits are readily available at most of the large electronics parts houses. Prices are still coming down for some of the integrated circuits being used in the Morse keyboard. The prices are down quite a bit since I started designing the Morse keyboard.

In the future, I will be selling some assembled printed circuit boards and possibly some completely assembled Morse keyboards.

Summary

I have enjoyed designing the Morse keyboard and have been using it consistently on the ham bands ever since it was a breadboard circuit. Many hams have mentioned that it was easy to copy code from the Morse keyboard. Many have indicated a desire to try out a Morse keyboard for themselves to see how well they work. Some hams who previously showed very little interest in Morsecode operation have found that it is very enjoyable after all. Morse keyboards are catching on and it looks like there will be very many on the ham bands in the future.





48 Perimeter Road, P.O. Box 4680 Manchester, NH 03108 USA TELEPHONE 603-627-7877

YOUR DEALER THE HAM SHACK

808 NO. MAIN STREET **EVANSVILLE IND 47711** TEL. 812-422-0231

DIRECTION FINDING?



- * No Receiver Mods
- * High Sensitivity
- ★ 135-165 MHz Standard Range
- * Mobile. Base or Remote Use
- * Bright LED Display
- * Optional Digital Readout
- * Optional Serial Interface
- * Kits or Assembled Units
- ★ 12VDC Operation
- * 90 Day Warranty

New Technology (patent pending) converts any VHF FM receiver into an advanced Doppler Direction Finder. Simply plug into receiver's antenna and external speaker jacks. Use any four omnidirectional antennas. Low noise, high gain for weak signal detection. Use serial AFSK option for remote display or tape recording data. Kits from \$270. Assembled units and antennas also available. Call or write for full details and prices.



DOPPLER SYSTEMS 5540 E. Charter Oak Scottsdale, AZ 85254 (602) 998-1151

UNIVERSAL AMATEUR RADIO INC. **AUTHORIZED DEALER** FOR • KENWOOD

- DRAKE
- YAESU
- · ICOM
- TEN TEC
- DENTRON
- · SONY
- AZDEN
- DENTRON
- KANTRONICS MFJ
 - NYF
- MILLER ROBOT
- INFO-TECH
- CUSHCRAFT
- LARSEN
- SHURE
- TEMPO
- ROHN
- PANASONIC

JAPAN RADIO CO. NRD - 515

Complete Stock of all Antennas and Towers

Excellent Warranty on Used Equipment -Oualified and Authorized Service -Same Day Shipment - MC - VISA

614-866-4267

UNIVERSAL AMATEUR RADIO INC. 1280 AIDA DRIVE

REYNOLDSBURG (COLUMBUS) OHIO 43068

TRSDOS: **COMPATIBLE**

PROGRAM	D	13	K	•	P	7.	U	5	ı			RE	GULA
Super-Log	. ,											\$	19.95
Custom Be	eam	1	le	a	C	li	n	g				\$	26.95
Compu-Lo	g.											\$	16.95
Antenna A	nat	or	n	y								\$	14.95
Super Dup	er.										. !	\$	9.95
Micro-Cloc	ck .										. !	\$	9.95
Micro-DX											. !	\$	9.95
IRC Manag	gem	e	٦t								. !	\$	9.95
											-	ē.	110 60

ONLY **349**95

\$118.60 VALUE

ADD \$3.00 Shipping/Handling

PROGRAM	DISK-PAK	II	RE	GULAR
Novice Th	eory Review .		 .\$	19.95
General Th	heory Review		 . \$	19.95
Advanced	Theory Review	w		19.95
Extra Theo	ory Review		 . \$	19.95
Morse Cod	de Trainer		 .\$	16.95

96.75 VALUE

OFFER BY MAIL ORDER ONLY Write For Detailed Brochure

2665 SOUTH BUSBY ROAD OAK HARBOR, WA 98277



TU-470 WIRED \$429.95 HOLIDAY SPECIAL



TU-300 WIRED \$349.95



ROM-116 TRS-80 RTTY/CW

- Split Screen Video
- Real Time
- Fourteen Buffers
- Text Editer
- Auto CW/ID
- · Selcal, WRU
- Word Wrapping For Model I, III, IV
- Many More Features
- Mall Box software available too
- Call for Prices TRS-80 Trademark of TANDY CORP.

TERMINAL UNIT FEATURES • • 3 Shifts (Hi-Tones Standard) • Single Shift (Hi-Tones) • • ● ● ● ● 3 Stage Active Filters AFSK Crystal Controlled RS-232C Compatible 000 000 0000 TTL Compatible FSK Output Demod Loop Transistor Keying Output • Remote Send RS-232C Compatible Remote Send TTL Compatible . . . Remote Controlled Bi-Polar PTT output 000 Autostart AC Output ● ● ● ● Scope Outputs Meter Tuning . . . Bar Graph Tuning . . . Status Indicators . . . Receive & Send Up To 300 Baud Receive & Send Up To 110 Baud Loop Supply Internal . . Loop Supply External & Optional 170 HZ Preselector Filter CW Demodulator Standard CW Demodulator Optional . . Complete Assembly in Case Board & Parts Only Complete With Connectors



TU-170A

WIRED \$289.95 **KIT** \$189.95



TU-170

KIT \$149.95



DM-170

KIT \$47.95

For more information & sales 1-800-HAM-RTTY

SERVICE 1-913-234-0198



Flesher Corporation P.O. Box 976

TOPEKA, KS 66601

ABLE MICROWAVE DOWN CONVERT

THIS IS NOT A KIT!!

QUANTITY DISCOUNT

74.95 69.95 64.95 59.95

To order by Visa or Master Charge No C.O.D. orders

Call 800-428-3500 Information 317-291-7262

All down converters built

with New HOT Transistor

for more amplifier gain.

GREATER DISTANCE

Indianapolis, Indiana 46268

NEW—Power supply built with push button simplicity ABC Switch built in

★ Coax cable not included

PLEASE ADD SUFFICIENT POSTAGE

1 Unit weighs 5 lbs.

Reveal the Receiver Behind the Specs

Here's a program that will make sense out of all those numbers.

Recently, I found myself coming down with a dread disease. I'm sure you've had it, too. It usually starts with a visit to a friend's shack, a hamfest, or the local radio emporium. You begin to experience an itch that can be relieved only by buying a new piece of ham gear.

As the disease progresses, you pore over glossy spec sheets and read equipment reviews in the ham magazines. It doesn't take long to realize that comparing brand K to brand D is almost impossible when it comes to the receiver specifications.

In one spec sheet, receiver sensitivity is given in microvolts for a 10-dB signal-plus-noise-to-noise ratio. For another rig, the measurements in the lab test give the minimum discernible signal. On occasion you may find a mention of the receiver frontend noise figure. And all of these are tested in different bandwidths. How can you cope?

If that's not enough, today's solid-state transceivers are good enough so that the manufacturers are actually beginning to tell us how their equipment is at handling strong nearby signals. Usually they will spec this as the two-tone dynamic range, but sometimes it is given as the third-order intercept. Is there a way to make a direct comparison?

Fortunately, it isn't too hard to make these comparisons. It's especially easy if you use a computer to do all of the math. Before we get to the program that does this, let's refresh our memories about the specifications that I just mentioned.

Sensitivity

For HF receivers, sensitivity is a measure of the noise generated by the amplifier stages and mixers in the signal path between the antenna and the speaker. It has nothing at all to do with the gain or amplification of the receiver. This is a point of confusion with many hams.

The most common way of specifying sensitivity is with the voltage required to give a signal-to-noise ratio of about 10 dB. The test is easy. Just use a calibrated generator to feed a signal to the receiver and watch an audio voltmeter connected to the audio output. Increase the level of the signal at the input until the voltmeter reads 10 dB higher than it did with no

signal. By using the calibration of the output level of the generator, the 10-dB S+N/N sensitivity results.

The reason it is called signal-plus-noise to noise is that you can't turn off the noise when the signal is applied because the noise is made by the receiver itself. Notice that there is no absolute reference to the output level of the receiver. Only the change in the output was measured. Two rigs can have the same sensitivity. but one may produce a very high level of received signal in the speaker while the other may hardly produce an audible output. A spec on overall gain would be nice, but I wish you good luck finding it on the glossy spec sheet!

MDS

The minimum discernible signal that can be heard with a receiver is measured in much the same way as the 10-dB S+N/N sensitivity. The only differences are that the generator level is raised until the audio voltmeter goes up 3 dB, and that usually the MDS is given in dBm (dB referred to one milliwatt in 50 Ohms). By measuring in this way, the signal power and the noise power are exactly the same. To put it another way, the signal-to-noise ratio is 0 dB. Converting MDS to μ V for 10-dB S+N/N is mostly an exercise in logarithms.

One trap in the sensitivity specs involves the receiver bandwidth that was used when it was measured. An easy way to make the spec look good is to use a narrower i-f filter. Cutting the bandwidth in half cuts the noise power in half. Then the signal power has to be only half as large as before to give the same S/N ratio. It's not that the manufacturers are sneaky, but they do use different receiver bandwidths in their normal SSB position. To make direct comparisons, you have to take the different bandwidths into account.

Noise Figure

On occasion, the sensitivity of a receiver will be specified as a noise figure. To understand noise figure, imagine that you have a receiver which is entirely noiseless. Connect a 50-Ohm resistor to its input and measure the output of the receiver. Surprise! There is noise there! But you knew that all resistors produce just a tiny bit of noise due to the molecular motion of the resistive material. Your noiseless receiver just amplified that tiny noise.

Program listing.

```
R C V R S P E C BY TERRY CONBOY, NGRY.
COMPARES RECEIVER SPECIFICATIONS FOR SENSITIVITY AND
DYNAMIC RANGE IN STANDARD BANDWIDTHS.
10
       REM
20
30
       REM
                  VIRGIN 1.00 ON 06 JUN 82 ORIG
VIRGIN 1.10 ON 18 JUL 82 APPLE
40
       REW
50
       REM
90
       REM
       HEM
                VARIABLE LIST.
        REM BO=KNOWN SENSITIVITY BW
REM B9=KNOWN DYN RANGE BW
DIM B(2): REM =STANDARD BW'S
REM DO=KNOWN 2-TONE DR
100
102
104
108
        DIM D(2): REM =STD 2-TONE DR'S
REM I=INTERCEPT POINT
110
        REM J=L(X)P INDEX
REM MO=KNOWN MDS
DIM M(2): REM =STD MDS'S
REM N=NOISE FIGURE
112
114
116
120
                   P=TYPE OF SENS SPEC KNOWN
Q=TYPE OF DR SPEC KNOWN
        REV
        REM
124
        REN
                    SO=KNOWN TO DB SENS
                 SET CONSTANTS
130
        REM
140 F = 10 / 1
150 B(1) = 500
        REM INPUT KNOWN SENSITIVITY
PRINT "SPECIFY INPUT SENSITIVITY PARAMETER:"
PRINT " 1) MINIMUM DISCERNIBLE SIGNAL (DRW)"
PRINT " 2) UV FOR 10 DB S+N/N"
PRINT " 3) NOISE FIGURE (DB)"
INPUT P
160 B(2) = 2400
170
190
200
210
220
230
240
290
        REM
300
        PRINT
        ON P GOTO 400,500,600
310
        GOTO 240
320
300
         INPUT "MDS (DBW) ":40
        GOSUB 900
V = MO + 174.0 - F + LOG (RO)
410
        0001 0100
430
         INPUT "UV FOR 10 DB S+N/N ":50
        GOSUB 900
```

```
520 N =
            2 + F + 10G (SO) - F + 10G (PO) + 57.47
5 30
       GOTO 1000
590
        REM
        INPUT "NOISE EIGHRE (DR) "IN
600
        GOTO 1000
790
       REM
        INPUT "MEASUREMENT BANDWIDTH (HZ) "+BO
910
        RETURN
990
               INPUT KNOWN DYNAMIC RANGE
1000
         PRINT "SPECIFY DYNAMIC RANGE PARAMETER:"
PRINT " 1) TWO-TONE THIRD-ORDER"
PRINT " 2) INPUT INTERCEPT POINT"
1010
1020
1030
          INPUT O
1040
          PRINT
1050
         REM
         ON O GOTO 1200,1300
GOTO 1040
1110
1190
          REM
11900 REM
1200 INPUT "IWO-TONE DYNAMIC RANGE (DP) ":DO
1210 INPUT "MEASUREMENT BANDMIDTH (HZ) ":R9
1220 I = DO * 3.0 / 2.0 + N - 174.0 + F * LOG (B9)
1230
1290
          GOTO 2000
         REM
          INPUT "INPUT INTERCEPT POINT (DBM) "+I
1300
          GOTO 2000
1310
1390
         REM
         REM CALCULATE EQUIVALENT SPECS
2000 F0R J = 1 F0 2

2010 M(J) = N - 174.0 + F + L0G (B(J))

2020 S(J) = 10.0 ^ ((M(J) + 116.53) / 20.0)

2030 D(J) = (I - M(J)) * 2.0 / 3.0
2040
         NEXT J
2090
         REM
2990
3000
         PRINT : PRINT
PRINT "
         REM
                 OUTPUT RESULTS
3005
                                             500 HZ
                                                                     2400 HZ#
         PRINT "

PRINT "

PRINT "MDS": TAB( 15):M(1): TAB( 29):M(2)

PRINT "10 DB S+N/N": TAB( 15):S(1): TAB( 29):N

PRINT "NOISE FIGURE": TAB( 15):N: TAB( 29):N
3007
3010
3020
                                                                             29) (5(2)
3040
3050
         PRINT "TWO-TONE DR": TAB( 15) D(1) TAB( 29) D(2)
PRINT "INTERCEPT": TAB( 15) II: TAB( 29) I
3060
3080
          PHINT
```

Now connect my receiver to your 50-Ohm resistor. Set it for the same gain as your noiseless receiver and connect the voltmeter to the output. The difference in dB of the reading on your perfect receiver and that of my real receiver is the noise figure of my receiver.

Since you can't make a perfectly noiseless receiver, you can't measure the NF that way. Instead, a calibrated source of noise is connected to the input of the rig and the output noise is compared to the output with only an input terminating resistor. With suitable calculation, the NF can be found.

One of the interesting things about NF is that the i-f bandwidth has no effect on the spec. This comes about because we are measuring noise-to-noise ratios. Both the receiver internal noise and the noise from the calibrated noise source go through the same filter. This is convenient for the computer program. Internally, it converts all sensitivity specs to NF for ease of calculation.

Dynamic Range

For the contester in a multi-transmitter operation or for the poor soul with another ham just down the street, having a receiver with good dynamic range can mean the difference between enjoying operating or just giving it up altogether.

Solid-state receivers today can be excellent in handling strong signals while listening to weak ones. There are still lots of rigs around, both tube and transistor, that really don't do this well.

The most common way of specifying dynamic range is in terms of the two-tone, third-order intermodulation test. This involves using two signals of the same level separated by about 20 kHz. These signals are fed to the receiver through a combiner and a variable attenuator. The receiver is tuned 20 kHz away from one of the tones. Then the signal level is raised until an audio voltmeter at the receiver output shows a 3-dB change. The difference between the level of one of the tones and the

MDS, in dB, is the two-tone dynamic range.

What happens is that the third-order intermod produced by the receiver came up in level enough to be discernible. Because the distortion signal is being compared to the noise, it is also dependent on the i-f bandwidth.

Intercept Point

With the two-tone test, for every dB that the level of the signals is raised, the intermod product goes up 3 dB. By raising the level of the two signals high enough, the intermod product will, in theory, finally rise enough to catch up with the level of the two tones causing the intermod. In fact, this does not happen, but we can extrapolate measurements that were made at lower levels to find out where it would happen. This imaginary point is called the third-order intermodulation-intercept point. It is specified in dBm.

Because we are comparing test signal amplitudes to

```
SPECIFY INPUT SENSITIVITY PARAMETER:
  1) MINIMUM DISCERNIBLE SIGNAL (DBM)
2) UV FOR 10 DB S+N/N
3) NOISE FIGURE (DB)
UV FOR TO DB S+N/N
MEASUREMENT BANDWIDTH (HZ) 2200
SPECIFY DYNAMIC RANGE PARAMETER:
  1) TWO-TONE THIRD-ORDER
2) INPUT INTERCEPT POINT
TWO-TONE DYNAMIC RANGE (DB) 88
MEASUREMENT BANDWIDTH (HZ) 2200
```

	500 HZ	2400 HZ
MDS 10 DB S+N/N NOISE FIGURE	-135.005727 .119182823 12.0045734	-128.193314 .261116483 12.0045734
TWO-TONE DR	92.2896846 3.42880021	87.7480763 3.42880021

Sample run.

WATCH FOR HAL'S NEW PRODUCTS

HAL 2304 MHz DOWN CONVERTERS (FREQ. RANGE 2000/2500 MHz) 2304 MODEL #1 KIT BASIC UNIT W/PREAMP LESS HOUSING & FITTINGS \$19.9 2304 MODEL #2 KIT (with preamp) \$29.9 2304 MODEL #3 KIT (with High Gain preamp) \$39.9	5
MODELS 2 & 3 WITH COAX FITTINGS IN & OUT AND WITH WEATHER-PROOFED DICAST HOUSINGS	E
BASIC POWER SUPPLY \$19.9 POWER SUPPLY KIT FOR ABOVE WITH CASE \$24.9 FACTORY WIRED & TESTED \$34.9	95
ANTENNAS & OTHER ACCESSORIES AVAILABLE, SEND FOR MORE INFO.	



2100-2500 MHZ

'HMR-II COMPLETE UNIT COMPLETE SYSTEM AS SHOWN, NOT A KIT, INCLUDES A PC BOARD, POWER SUPPLY, CABLES & CONNECTORS—PRE-ASSEMBLED AND TESTED, 24dB GAIN OR GREATER.

1-4 units.						.\$89.95 ea.
5 or more	units		,			.\$79.95 ea.

'HAM MICROWAVE RECEIVER

PRE-SCALER KITS

HAL 300 PRE	(Pre-drilled G-10 board and all components)	\$14.95
HAL 300 A/PRE	(Same as above but with preamp)	\$24.95
HAL 600 PRE	(Pre-drilled G-10 board and all components)	\$29.95
HAL 600 A/PRE	(same as above but with preamp)	\$39.95

TOUCH TONE DECODER KIT

HIGHLY STABLE DECODER KIT. COMES WITH 2 SIDED, PLATED THRU AND SOLDER FLOWED G-10 PC BOARD, 7-567's, 2-7402, AND ALL ELECTRONIC COMPONENTS. BOARD MEASURES 3-1/2 x 5-1/2 INCHES. HAS 12 LINES OUT. ONLY \$39.95

NEW-16 LINE DELUXE DECODER

DELUXE 12-BUTTON TOUCHTONE ENCODER KIT UTILIZING THE NEW ICM 7206 CHIP PROVIDES BOTH VISUAL AND AUDIO INDICATIONS! COMES WITH ITS OWN TWO-TONE ANODIZED ALUMINUM CABINET MEASURES ONLY 2 ½ "x3" "COMPLETE WITH TOUCH-TONE PAD. BOARD, CRYSTAL, CHIP AND ALL NECESSARY COMPONENTS TO FINISH THE KIT.

NEW-16 LINE DELUXE ENCODER

\$39.95

\$69.95

HAL ECD—16 LINE DELUXE ENCODER INCLUDES PC BOARD, ALL PARTS & CASE \$39.95

HAL ECD—12 LINE DELUXE ENCODER COMPLETE WITH PC BOARD, ALL PARTS & CASE \$29.95

ACCUKEYER (KIT) THIS ACCUKEYER IS A REVISED VERSION OF THE VERY POPULAR
WB4VVF ACCUKEYER ORIGINALLY DESCRIBED BY JAMES GARRETT, IN QST
MAGAZINE AND THE 1975 RADIO AMATEUR'S HANDBOOK
\$16.95

ACCUKEYER—MEMORY OPTION KIT PROVIDES A SIMPLE, LOW COST METHOD OF ADDING MEMORY CAPABILITY TO THE WB4VVF ACCUKEYER. WHILE DESIGNED FOR DIRECT ATTACHMENT TO THE ABOVE ACCUKEYER. IT CAN ALSO BE ATTACHED TO ANY STANDARD ACCUKEYER BOARD WITH LITTLE DIFFICULTY \$16.95

BUY BOTH THE MEMORY AND THE KEYER AND SAVE

COMBINED PRICE ONLY \$32.00

PRE-AMPLIFIER

HAL-PA-19 WIDE BAND PRE-AMPLIFIER, 2-200 MHz BANDWIDTH (– 3dB POINTS). 19 dB GAIN

FULLY ASSEMBLED AND TESTED \$8.95

HAL-PA-1.4 WIDE BAND PRE-AMPLIFIER, 10 MHz TO 1.4 GHz. 12dB GAIN

FULLY ASSEMBLED \$12.95



CLOCK KIT— HAL 79 FOUR-DIGIT SPECIAL—\$7.95. OP. ERATES ON 12-VOLT AC (NOT SUPPLIED) PROVISIONS FOR DC AND ALARM OPERATION.

6-DIGIT CLOCK • 12/24 HOUR

COMPLETE KIT CONSISTING OF 2 PC G-10 PRE-DRILLED PC BOARDS, 1 CLOCK CHIP, 6 FND COMM. CATH. READOUTS, 13 TRANS., 3 CAPS, 9 RESISTORS, 5 DIODES, 3 PUSHBUTTON SWITCHES AND INSTRUCTIONS. DON'T BE FOOLED BY PARTILL KITS WHERE YOU HAVE TO BUY EVERYTHING EXTRA. WILL RUN OFF ANY 12-YOLT AC SUPPLY.

PRICED AT \$12.95

CLOCK CASE AVAILABLE AND WILL FIT ANY ONE OF THE ABOVE CLOCKS. REGULAR PRICE....\$6.50 BUT ONY \$4.50 WHEN BOUGHT WITH CLOCK.

SIX-DIGIT ALARM CLOCK KIT FOR HOME, CAMPER, RV, OR FIELD-DAY USE. OPERATES ON 12-VOLT AC OR DC, AND HAS ITS OWN 60-Hz TIME BASE ON THE BOARD. COMPLETE WITH ALL ELECTRONIC COMPONENTS AND TWO-PIECE, PREDRILLED PC BOARDS. BOARD SIZE $4^{\prime\prime}\times3^{\prime\prime}$, COMPLETE WITH SPEAKER AND SWITCHES. IF OPERATED ON DC, THERE IS NOTHING MORE TO BUY $^{\prime\prime}$

PRICED AT \$16.95

*TWELVE-VOLT AC LINE CORD FOR THOSE WHO WISH TO OPERATE THE CLOCK FROM 110-VOLT AC WHEN PURCHASED WITH CLOCK KIT \$2.95

SHIPPING INFORMATION: ORDERS OVER \$25 WILL BE SHIPPED POST-PAID EXCEPT ON ITEMS WHERE ADDITIONAL CHARGES ARE REQUESTED. ON ORDERS LESS THAN \$25, PLEASE INCLUDE ADDITIONAL \$2.00 FOR HANDLING AND MAILING CHARGES. SEND 20¢ STAMP FOR FREE FLYER.

DISTRIBUTOR FOR

Aluma Tower+AP Products
(We have the new Hobby-Blox System)





HAL-TRONIX

P. O. BOX 1101 SOUTHGATE, MICH. 48195 PHONE (313) 285-1782 the amplitude of the intermod product, the ifbandwidth is not a factor in the measurement. The computer program uses this for internal calculations because of the bandwidth independence.

The Program

Once the formulas for the conversions are derived, the program is really quite simple. It has five sections. The first part takes care of opening stage business by dimensioning the arrays and setting the constant values.

In the second part, the program asks for the sensitivity spec from the glossy sheet or equipment review. The third section takes in the known dynamic-range specification. Then the computer calculates the equivalent specs for "standard" bandwidths of 500 and 2400 Hz. Lastly, the program tells the computer to print these specs.

To help you modify the program for your own use, the variables used in the pro-

gram are defined in the beginning of the program listing. So that you will know that your CDC Cyber is finding the right answers, a sample run is included as a check. The program listed was on an Apple II, but the syntax is pretty ordinary and shouldn't present much of a problem in translating to other dialects of Basic.

Trivial

Be wary of anyone who tells you that any particular task for a computer is trivial. Usually those trivial tasks take months to accomplish (as my boss reminds me afterward). It did take me a while to reduce this program to the simple form that you see here. After I was done, even the job done by the program seemed triviuntil I remembered how long it took to punch in the calculations on my scientific calculator.

I hope this short program makes it easy to compare the competing cures for your itch for new gear.



ASSOCIATED RADIO 8012 Conser Overland Park, KS 66204 (913) 381-5900

AFRAID?

You won't get the BEST deal?

CALL US
WE
BUY-SELL
ALL BRANDS
NEW, USED
OR WHOLESALE

LARGE STOCKS LOW PRICES

⁶⁴HAM HEAVEN⁹⁷ U.S.A.

> Send \$2.00 for our Catalog and Wholesale List.

MORE PERFORMANCE FOR YOUR DOLLAR!


COMPETITORS KNOW ABOUT THE ISOPOLE^M

DO YOU? STUDY THE FACTS

The IsoPole antenna is building a strong reputation for quality in design and superior performance. Innovative IsoPole conical sleeve decouplers (pat.

pend.) offer many new design advantages.

All IsoPole antennas yield the maximum gain attainable for their respective lengths and a zero degree angle of radiation. Exceptional decoupling results in simple tuning and a significant reduction in TVI potential. Cones offer greater efficiency over obsolete radials which radiate in the horizontal plane and present an unsightly bird's roost with an inevitable "fallout zone" below. The IsoPoles have the broadest frequency coverage of any comparable VHF base station antenna. This means no loss of power output from one end of the band to the other when used with SWR protected solid state transceivers.

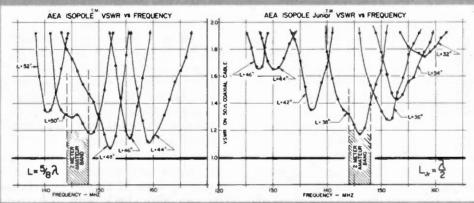

Outstanding mechanical design makes the IsoPole the only logical choice for a VHF base station antenna. A standard Amphenol 50 Ohm SO-239 connector is recessed within the base sleeve (fully weather protected). With the IsoPole, you will not experience aggravating deviation in SWR with changes in weather. The impedance matching network is weather sealed and designed for maximum legal power. All IsoPole antennas are D.C. grounded. The insulating material offers superb strength and dielectric properties. plus excellent long-term ultra-violet resistance. All mounting hardware is stainless steel. The decoupling cones and radiating elements are made of corrosion resistant aluminum alloys. The aerodynamic cones are the only appreciable wind load and are attached directly to the support (a standard TV mast which is not supplied).

IsoPole antennas have also become the new standard for repeater applications. They all offer low angle of radiation, low maintenance, easy installation, and low cost with gain comparable to units costing several times as much. Some repeater installations have even eliminated the expense of a duplexer by using two IsoPole antennas separated vertically by about twenty feet. This is possible because of the superior decoupling offered by the IsoPole antennas.

The IsoPole antenna is now available in a 440 MHz version which is fully assembled and tuned.

Our competitors have reacted to the IsoPole, maybe you should too! Order your IsoPole or IsoPole Jr. today from your favorite Amateur Radio Distributor. **ADVANCED ELECTRONICS**

Brings you the Breakthrough!

P.O. Box C-2160, Lynnwood, WA 98036 TELEX: 152571 AEA INTL

APPLICATIONS

PRICES AND SPECIFICATIONS SUBJECT TO CHANGE WITHOUT NOTICE OR OBLIGATION.



ISOPOLE 144JR ISOPOLE 220JR MAST NOT SUPPLIED

ISOPOLE 144 ISOPOLE 220 MAST NOT SUPPLIED

Terrific Top-Band Conversions

lump up to 160 meters and beat the coming sunspot drought. Surplus gear will get you there cheaply.

esigning ham gear involves many compromises; unfortunately for those of us who operate 160. it seems that many of them end up taking away performance on the top band.

With the new regulations and decreasing sunspots, the number and strength of signals on 160 are going to increase. Will your rig be able to cope? Are you looking for a simple and inexpensive way to add a preselector/preamp to your station? This cheap and easy conversion may be just what you're looking for.

I'm not going to provide a treatise on filter design, so

check the references for the data that you need. What this article will do is show you how to adapt any of the HE/ME command-set receivers to provide a foundation for the front-end adjunct that you need.

I chose the command sets for this project for several reasons. The main one is that they are almost a readymade front end as they are. and the coils lend themselves to easy modification and rewinding. The components are of exceptional quality. In addition, my junk box contains a very high proportion of command-set components.

If you price the components for the Cohn-type filter from the Handbook. you'll find that the current cost of the inductors will be around \$50. A used R-11A is \$12.95 from Fair Radio (R-22 and R-25 are still available. but about twice as expensive). At our local hamfests they bring from \$1 to \$10. You can also check with your local OTs; there has to be at least one command receiver left for every ham in the US.

When choosing a unit at a hamfest, the only caution is that those units that have been bandspread (the dial will have homemade markings covering one band) should be bought for coils only as the variable capacitor in these conversions is gutted. Happily, most conversions don't affect the parts used for this conversion. The command sets are probably the most converted piece of surplus gear ever, so your chances of finding one at a hamfest that is completely original are slim.

The command-set receivers cover the range of 190 kHz to 9.1 MHz. Any of them will work for this conversion. See Table 1

The last command receiver (civilian version) rolled off the assembly lines 20 years ago, the first well over 40 years ago, so even the diehards will have to admit that their usefulness as receivers is about at an end. With this in mind, get out the hacksaw and get ready for the very last commandset conversion.

The simplest passive unit (Fig. 2) uses the variable capacitor and two of the frontend coils (the small cans under the variable capacitor). The others make use of all the front-end coils and

	1,00		
			U
		0.00	
1000			

Photo A. The receivers before modification.

Frequency	Model	Notes
190-550 kHz	R-23, BC-453, R-11	Modify variable
520-1500 kHz	R-24, BC-946, R-22	Scarce, seldom
1.5-3 MHz	R-25, BC-454	Least modifica needed for 160
3-6 MHz	R-26, BC-454	
6-9.1 MHz	R-27, BC-455	Padding neede able capacitor

Notes
Modify variable
Scarce, seldom found at hamfests
Least modification needed for 160
needed for 160
Padding needed for vari-

the i-f coils; shield cans may be used also.

The front-end coils and i-fs on the early models plug in: those on the later models (no dial) do not. The plug-in feature is nice while testing and constructing, but it is not a necessity. Each of the front-end coils is colorcoded for frequency range and function as follows: brown - 190/550, orange -1.5/3, yellow -3/6, green -6/9.1, red - .52/1.5. This color code is on the screw holding the coil form to the shield-can base.

The function color code, located in one corner of the shield-can base, is as follows: red-antenna, yellow-rf, blue-mixer

The i-f cans can be used to house a second filter, as a housing for the amplifier circuit, or as the center inductors for a Cohn-type filter. The 2830-kHz i-fs from the 6/9.1 receiver have a very nice coil form that is easily rewound or modified. The i-f cans can be screw-mounted to the chassis or the tube socket holes can be enlarged and the original plugs used. The mounting brackets will have to be removed to fit the three i-f cans across the chassis as shown in Photo D.

If you do not wish to use the original dial mechanism, or if your unit has no frequency dial, you will have to modify the variable capacitor

The variable capacitors are rated as follows: 6/9.1.75 pF; 3/6, 150 pF; the rest are 450 pF. These values are for one section and are approximate as there are some variations in the different models. To lower the capacity. you must remove plates; this is not difficult, but it must be done carefully.

Basic Conversion

First strip the chassis and then the front panel. Set aside the hardware, the front-end coils, the variable capacitor and its shield, the

i-f cans, and the small variable capacitor from the front panel. If you have one of the dial-less units, remove the plugs from the front panel. If the aluminum cup is still in your unit, remove it from the front panel also. The front panel should be clean with the exception of the spline shaft holder. If you intend to use the original right-angle setup, leave it on the panel. If not, remove the two pins and then unscrew the nut that holds it to the chassis.

Are you going to use the i-f cans? If so, remove the two tube sockets located immediately behind the variable capacitor shield. Also remove the i-f plugs (if present) by running a screwdriver under the rolled edges and prying up gently.

Now, using a hacksaw with a fine-tooth blade, cut off the rear of the chassis right behind the two i-f holder nuts. This is 5" measured from the front panel. If you will not be using the i-f cans, cut between the shield holder nuts and the first i-f holder nuts. This is 3-3/16" measured from the front panel. Of course, you can leave more rear apron if you need it for relays, power supply, or whatever.

What you now have is a three-section variable capacitor with coils, shield cans, and an enclosure to mount it all in. Now to assemble the finished product.

See Fig. 2. Using the antenna and rf coils, this unit covers the original frequency range of the receiver.

Modify the antenna coil by adding a two-turn coil to the bottom using #20 wire. Connect one end to the ground end of the original coil and the other to an unused pin. Modify the rf coil by removing the pie-wound coil on top of the form and adding a two-turn link as in the antenna coil. Remove the core locks from both coils and screw the cores all the way into the coil form. At this point you may wish



Photo B. The parts used showing a modified variable capacitor.

to remove the shield cans from the bracket and drill holes in them to clear an alignment tool. The shield cans do change the frequency of the tuned circuit. Now, plug or mount the two coils in the first two sockets or holes using the first two sections of the variable capacitor (the ones with the trimmers). Wire the unit to agree with Fig. 2. Make sure that the coupling capacitor does not interfere with the variable capacitor.

Using the trimmers and adjusting the cores, the unit should track across approximately the original range of the receiver. The response is a bit broad on 6/9.1 and adequate on 3/6 and 1.5/3

See Fig. 3. This adds a preamp and another tuned cir-

cuit to Fig. 2. You will have to rewind the mixer coil using the antenna coil as a model. The link is the same and the tap will depend on the gain desired from the amplifier. A dual-gate device could be used here with a gain-control voltage applied to G2. You can use your favorite amplifier circuit here, or even one of the commercial gain blocks. Just remember to use only the amount of gain needed to overcome filter loss or Rx antenna inefficiency—overdoing it will defeat the purpose of the device

To cover frequencies other than that for which the receiver was designed, you will of course have to rewind (or unwind) the coils and perhaps add some pad-

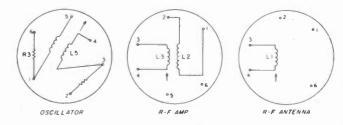


Fig. 1. Typical command-set coils.

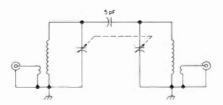


Fig. 2. Simple two-section unit.

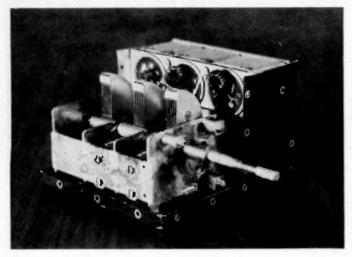


Photo C. Multi-section filter using R-11a parts (no dial assembly), variable capacitor shield removed to show details. Note position of bottom coupling toroid coils.

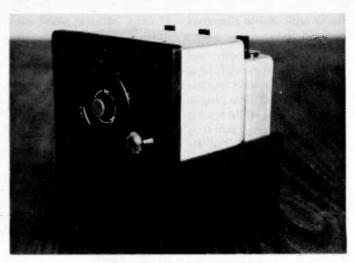


Photo D. Completed unit showing possible placement of i-f cans.

ding to the variable capacitor. If you use the 3/6 and 6/9.1 units, a good starting place for 160 is about an inch of closewound turns of #32 wire. The 190/550 units can be modified by either rewinding the coils or unwinding them. The variables have a bit too much capacitance. but they will work. See Fig. 4. This filter can be made with the coil set from the 190/550 units by unwinding the antenna coil, removing the large coil from the top of the mixer coil, unwinding the small coil, and then unwinding the two coils on the rf coil form until they reach the proper inductance. Unwind only enough from each of the four coils for it to reach the right frequency. This involves a bit of extra "cut and try" time, but it is worth it. Remember that the two center inductors are twice the inductance of the outside coils and that the bottom coupling links and in/out links should be in place as you bring the inductors to frequency.

I have covered only a few of the possibilities for this conversion here; your needs will determine the final form vours takes

There is room inside the shield can to build the amplifier. The i-f coils can be used to build a second filter for a different range. The switch should have each section shielded to prevent stray coupling. To modify the 450-pf variable capacitors to reduce capacity, do the following:

First, remove the end rotor plate, using long-nose pliers, working it gently back and forth until it breaks free. Remove the next rotor plate the same way. This one and the rest will have to be freed from the band stop bar. Trim the band stop bar after removing each plate. The stator plates are a bit easier to remove. Twist gently at the attachment point opposite the trimmers until it breaks free, then work it up and down until the other side breaks free. Do not put too much pressure on either the shaft or the stator plates or the ball bearings will break free and you will have a Chinese puzzle to assemble. If one or more of the glass beads the stator plates are mounted on is missing, acceptable substitutes can be found at your local crafts shop. Leave six rotor and six stator plates in each section and make sure that the plates are properly aligned. More plates may be removed if the capacity is still too high.

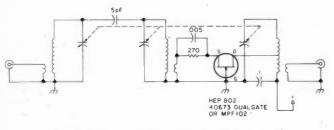


Fig. 3. Preamp and tuned circuit attached.

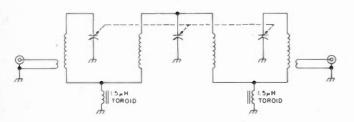


Fig. 4. Multi-coil setup.

More **Capacitor Modifications**

The antenna section of the variable capacitor either has no trimmer or, if there is one, it has fewer plates than the others. The capacitor that you removed from the front panel can be remounted and used for a trimmer or the trimmer on the shaft end can be used by running an insulated wire from it to the antenna section under the variable capacitor, along the front panel.

To remove the angle drive, first remove the pin in the worm gear shaft, then remove the two gears from the bottom of the capacitor by prying off the retainers with a small screwdriver. Pull the splined end out and then remove the end nut and the worm gear. Remove the gear from the end of the shaft by driving out the pin gently-remember the ball bearings. If the pin is stuck, drill it out. Then remove the triangular plate (this plate helps support the shaft while you remove the pin) and pull the gear off the shaft.

I used as much of the original covers as I could to house the unit. If you remove the drive, you will have to cut a U-shaped slot in the capacitor shield to clear the shaft and coupler.

The time that you spend getting the unit to track will pay off in performance. Take your time and get it right.

I used a GDO to get the circuits close to frequency and then used a signal gen-



CTRONICS RPORATIO

SEMICONDUCTOR PARTS & PRODUCTS

FACTORY PRIME DEVICES INCLUDE:

- Capacitors
- all types & styles Chokes & Coils
- Connectors
- Digital & Linear IC's
- Hardware & Accessories
- IC Sockets
- Memory
- Microwave Semiconductors
- Resistors
- fixed & variable
- **Transformers**
- Transistors & MORE!

MANUFACTURERS SUCH AS: Motorola, National, NEC. J.W. Miller, Texas Instruments and more!

WE STOCK & SUPPLY DEVICES FOR: OEM's,

Distributors, Hobbiests, Magazine Projects, Engineers, Schools, Technicians & You!

> Call or Write for Quantity Pricing and FREE Catalog.

P.O. Box 33205 Phoenix, AZ 85067 **(602) 274-2885**

MICROWAVE TV ANTENNA SYSTEMS

Freq. 2.1 to 2.6 GHz • 34 db Gain +



TWO YEAR WARRANTY



COMPLETE SYSTEMS (as Pictured) Commercial 40" Rod Style \$ 89.95 Parabolic 20' Dish Style \$ 79.95 COMPONENTS **Down Converters**

(both types) \$ 34.95 **Power Supplies** (12V to 16V) \$ 24.95

Oata Info (Plans) \$ 9.95 CALL OR WRITE FOR

KITS. PARTS, INDIVIDUAL COMPONENTS

We Repair All Types Down Converters & Power Supplies

Phillips-Tech Electronics

P.O. Box 34772 Phoenix, AZ 85067 (602) 265-8255

Special Quantity Pricing **Dealers Wanted**





COD'S



TEN-TEC 560 Corsair 9-band Digital Transceiver Regular \$1169 - Sale Price \$1029

Corsair accessories:	Regular	SALE
260 Deluxe power supply with speaker	\$199.00	\$17995
263 Remote VFO	199.00	17995
220 2.4 KHz 8-pole crystal SSB filter	59.00	
282 250 Hz 6-pole crystal CW filter		
285 500 Hz 6-pole crystal CW filter		
288 1.8 KHz 8-pole crystal SSB filter		
214 Electret desk microphone		

TEN-TEC Corsair SPECIAL!

From September 15th, 1983 to January 15th, 1984 purchase a Corsair at our Sale Frice and receive a COUPON for (1) FREE accessory Crystal Filter of your choice (a \$59.00 value) direct from TEN-TEC.

Also - Operate the Corsair for 30 Days. If you are dissatisfied for ant reason, you may return it to AES for FULL CREDIT toward other merchandise or a FULL REFUND, not including any Shipping Charges.





AES® STORE HOURS: Mon. thru Fri. 9-5:30: Sat. 9-3 Milwaukee WATS line 1-800-558-0411 answered evenings until 8:00 pm, Monday through Thursday.

Please use WATS line for Placing Orders For other information, etc. please use Regular line.

Order Toll Free: 1-800-558-0411

In Wisconsin (outside Milwaukee Metro Area) 1-800-242-5195

4828 W. Fond du Lac Avenue; Milwaukee, WI 53216 - Phone (414) 442-4200

AES BRANCH STORES

WICKLIFFE, Ohio 44092 28940 Euclid Avenue Phone (216) 585-7388 Ohio WATS 1-800-362-0290 Outside 1-800-321-3594

621 Commonwealth Ave. Phone (305) 894-3238 Fla. WATS 1-800-432-9424 Outside 1-800-327-1917

ORLANDO, Fla. 32803 1898 Orew Street Phone (813) 461-4267 No In-State WATS

No Nationwide WATS

CLEARWATER, Fla. 33575 LAS VEGAS, Nev. 89106 1072 N. Rancho Orive Phone (702) 647-3114 No In-State WATS

Outside 1-800-634-6227

Associate Store

CHICAGO, Illinois 60630 ERICKSON COMMUNICATIONS 5456 N. Milwaukee Avenue Phone (312) 631-5181

15 mln. from O'Harel



- Computer Damage
- Brownout Interruptions
- Disruptive Line Noise
- Program Errors

Regulator • Filter • Suppressor

250 Watt Load \$291.95 KLR-250A-1SO 250 Watt Load: Patented Filter Isolated Sockets \$346.95 KLR-500A 500 Watt Load \$390.95 KLR-500A-1SO 500 Watt Load; Patented Filter Isolated Sockets \$445.95

Shipping: \$12.75 Land; \$45.50 Air

Ask Your Local Dealer

ESP. Electronic Specialists, Inc.

171 South Main Street, Box 389, Natick, Massachusetts 01760

Toll Free Order Desk 1-800-225-4876 MasterCard, VISA, American Express

erator and scope for final adjustment. If you have access to a sweep generator, it makes alignment very easy.

If you use the unit with a transceiver, automatic switching is a must-the coils don't last long with 100 Watts of rf in them.

If you use the i-f cans to house commercial coil forms, you may have to drill out the center hole for an alignment tool.

For the time spent, this conversion provides a definite improvement in performance at a minimum cost.

A Note to Elmer:

When one of your current crop of KAs brings this article to you and asks if you might have one of these things lying around, don't get misty-eyed and try to explain why you've kept it all these years. He won't understand the sacrilege of applying a hacksaw to a pristine Q-Fiver. 1 know how you feel, I know how many you

converted and passed on to prospective Novices (remember, I was one of them), and yes, I remember the R-24 you put in the '54 Chevy. You saved a hundred bucks and the dynamotor didn't make a bit more noise than a vibrator. I remember, too, when we rewound the coils and put it on 15 and my first VK came back. But, to him it's just a homely box. So bite the bullet and help him out; after all, a ham shack without an ARC-5 (or part of one) isn't really complete!

References

Command Sets, Cowan Publishing Corporation, 1957, Wayne Green, Editor.

The Radio Amateur's Handbook, 55th Ed., ARRL publica-

DeMaw, "His Eminence the Receiver," QST, June and July,

Pafenberg, "The AN/ARC-5 Command Receivers," 73. June.

White, "The First and Last Q-Fiver," 73, March, 1966.

Introducing The SRT-3000 A High Performance RTTY Communications Send-Receive Terminal

 Built-in demodulator & AFSK modulator for 170,425,850 Hz shifts, high and low tone pairs • 60,66,75,100,132 WPM Baudot, 110,300 Baud ASCII, 5-99 WPM Morse • 1000 character text buffer with BREAK feature • Ten 80 character message memories with battery backup •

SRT-3000 List Price \$ 995.00 **INTRODUCTORY PRICE \$ 795.00**

Selectable display formats, 24 lines x 72 characters (2 pages), 24 lines x 36 characters (4 pages), 16 lines x 36 characters (6 pages) • Split screen operation • On screen status line displays a tuning bar, mode, speed, shift, tone pair, normal/reverse, USOS, WRU, SELCAL, buffer mode and buffer count • Cassette interface for long "Brag Tapes" or unattended message storage • Baudot and ASCII printer outputs • Built-in audio monitor • Built-in 110 VAC power supply • Other features-PTT control, WRU, SELCAL, sync idle, CW ID, USOS, autostart, full or half duplex, scope outputs, weight control, intercharacter spacing, reverse video, RS-232, word wrap around • Compact size only 13.3 x 10.3 x 4 inches • Made in USA.

Send For

Free Information



Optional 9" video monitor shown \$149.00

787 BRIAR LANE, BELOIT, WISCONSIN 53511

(608) 362-0410

ALL HF BANDS! VIIALIY The SLINKY DIPOLE® Antenna

A broadband, low SWR dipole that really works in apartments, small yards, attics, anywhere a small antenna is a must. Indoors or out, you can work ANY HF BAND, including 10 MHz. No gimmicks or add-ons. Imagine 80M in as little as Z4 ft.! Complete kit and instructions, plus 50 ft. of coax. Easy to set up and adjust. More information available - just call or write.

Blacksburg Group Box 242 Suite 500 Blacksburg, Virginia 24060 703/951-9030 \$67.95 postpaid (in U.S.A.) Money Back Guarantee Virginia residents add 4% sales tax

MAXCOM"

AUTOMATIC

ANTENNA MATCHER

TUNES

ONE ANTENNA

.3 MHZ TO 70 MHZ

VSWR LESS THAN

DIPOLE OR LONGWIRE MODELS 200 TO 2KW PEP


CONTACT :

MAGNUM DISTRIBUTORS INC 1000 S. DIXIE HY. W. #3 POMPANO BEACH, FL 33060 (305) 785-2002

Now you can get in on the fun on packet radio!

- Low cost!
- Adaptable to any transceiver
- Easy to learn, easy to use.
- Built-in packet Modem and CW identifier.
- Use with teletype machines, computers, terminals.
- RS232 serial interface-45 to 9600 baud!
- Uses both ASCII and Baudot
- Vancouver protocol-AX.25 to be released soon.
- Optionally write your own protocol on host computer.
- Nearly 50 commands.
- Stores received messages until requested at a
- Operates in 'connected' and 'general' modes
- Activates teletype motor to print messages.
- Board accepts up to 14K of RAM.
- Model PK1 can be customized for Commercial Systems.

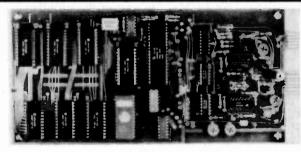We offer a complete line of transmitters and receivers, strips, preselector preamps, CWID'ers & synthesizers for amateur & commercial use. Request our FREE catalog, MC & Visa welcome, Allow \$2 for UPS shipping.



MODEL PK1 (shown with 14K RAM and 8K ROM)

Protocol can be changed by swapping ROM chips. Board designed to accept 6264°s for up to 56K of RAM with minor modification.

Dimensions: 4.5 x 8.5 inches; 1" vertical clearance. Power requirement: +12 VDC, approx. 200 ma.

Standard equipment includes 4K of RAM (expandable to 14K).

Model PK1, wired & tested— \$149.95 additional memory, installed & tested (up to 12K) \$10/2K RTTY adaptor board

Connecting cables & enclosure—optional

GLB ELECTRONICS

1952 Clinton St., Buffalo, NY 14206 716-824-7936, 9 to 4

Call or Write for Free 1983 Catalog

CardSoft: The Transportable **QSL** Generator

If your machine runs Basic, it can run this program.

nyone out there priced QSL cards lately? Have you noticed how often you get (or send) an SASE with the ole pasteboard? Well, possibly the day is fast coming when the familiar QSL "penny" postcard will be only a memory (or fading on the wall). I, personally, haven't sent or received OSL

cards in several years without an SASE being involved, and at the cost of Uncle's postal service, who can afford it these days? Well, for those who have their own microprocessor (and printer) - and there seem to be rapidly growing numbers of them-here's a solution to part of the problem.

CERTIFICATE

TO ALL WHOM THESE PRESENTS COME: GREETINGS!

KNOW YOU by the Ruthority invested in Us by the Federal Communications Commission, a rebulatory spency of the Government of the United States of Rmerica. We do hereby certify that on the date, and at the time and on the frequency herein inscribed;

Two-way radio communication was established between:

WB5LLM

A RADIO STATION licensed by the above referenced leval Agency, to Us, in accordance with the Rules & ulations of the Amateur Radio Service.

WD4EDQ

a radio station operating in the aforesaid Service.

#QSO DATA#

DATE 28 / 9 / 82 / TIME(UTC): 1254Z FREQUENCY 14.878 MHZ.
TRANS.-Hallicrafters MT-32a/RCVR.-Hammarlund MQ-188/R
RTTY/SSTV - TRS-88C() w/ CV-89A/URA-88 Converter
ANT. SYSTEM: 28M. VERT. REMARKS: GUD LUCK WID YR.W.R.S.,8088Y
SIGNAL REPORT R= 5 S= 9 T= 9 MODE: RTTY

FURTMERMORE, know you that this CERTIFICATE shall be accepted as Confirmation of said contact and exchange of Signal Reforts, etc., for any, and all, purposes that the aforesaid Awardee deems his want; be it Contest, Derating Awards, etc., in use of the above referenced Station in the Amateur Radio Service.

THEREFORE, In recognition of the above. We hereby set our Mand and Seal, this, the 20TH day of SEPTEMBER, 1982.

JOE RYAN, LICENSEE A.L.S. WB5LLM P.O. 80X 622 FLORENCE, MS. 39873

WB5LLM's QSL certificate.

The main reason that all this QSL swapping goes on these days, in view of the growth of RTTY, SSTV, FAX, and FSTV, is the need to have the confirming operator's signature on the written confirmation of a completed two-way contact. With this program and your trusty printer, you'll be able to crank out your QSLs neatly, efficiently, and with little cost in either money or time.

Nothing in the book says that a QSL must be on a postcard in two or more colors, costing anywhere from 5 to 10 cents each (or more). So, I sat down one day and faced my Tandy TRS-80C, which I use for RTTY and SSTV, and considered the problem. What I came up with is a program that is usable by almost anyone with the above micro/printer combination that will run in Basic. Some minor changes, such as changing the PRINT#-2 statements to LPRINT, etc., will let this program run on any Tandy micro, Apple, Star, etc., and even on those dedicated micros sold for RTTY use (if they have the Basic capability).

Now to the program itself. First, you'll notice that the DIM statement is in the middle of the program. That's because we're changing the values in the DIM statement every time we run the program and possibly during the program operation. This is when you've run off one or more certificates and then decide that you missed some.

Notice that in line 1 we have cleared 13000 for stringarray space. There are fifteen inputs, three of which don't change from certificate to certificate. These are the date statements for the date of the certificate. Since you may be running a bunch at a time, you might as well leave that set at one date (saves typing it in repeatedly). With a space of 13000 cleared, you will be able to enter the data for at least 100 certificates. Of course, this was written on a micro with 32K of memory available (no, I didn't clear out the video area for additional space). If you have a 16K memory, reduce this statement in line 1. That will, of course, reduce the number of certificates you can make in one run.

Lines 200 to 480 cover the actual printing of the text of the certificate and were merely figments of my imagination. The wording was more or less copied from certificates issued by the State of Mississippi but probably is close enough to that used in most certificates to be acceptable. However, if you want to modify it-go to it! Don't forget to follow the REM statements and insert your own call letters and name and address to replace mine

Lines 550 to 670 are the query and data input area. I don't recommend exceeding 20 characters or more of text in the COMMENTS or ANT. SYS. inputs as this will throw off the balance of the finished certificate. Other than that, have at it.

I've used this for a while now and have had no kickback, and it certainly beats spending an evening writing out QSL cards, one after

another after another, etc., ad nauseam. Once you get it debugged (if you make typing errors like 1 do), just run the program (don't forget to save it, either on tape or disk) and enter the date for the certificates and the number you're running at this time. From then on, follow the prompts.

When you've entered all the callsigns and QSO data for the number of QSLs you're sending out, check your printer. I should mention here that this was written for use with the Tandy Line Printer VII, so if you have a different printer you will want to experiment with the PRINT#-2 (or LPRINT or what have you) statements. You can replace these with control characters that your printer recognizes (vou know, CHR\$(?)); I didn't bother, as the VII printer seems to like the PRINT#-2 just as well.

Once you have it all in and your printer is ready with the paper lined up at the top, you can follow the instructions and hit ENTER and go on about your business-watch TV, get on the air and let out with a CO. meet vour favorite net. etc. The program and printer will carry on until done and, if you are using the TRS-80C. will sound a tone (if you have the TV volume up, that

is) when finished. Alternatively, you can stand or sit there and watch the screen (it displays the data and certificate number of each certificate as it is printing same) and the printer—it doesn't care!

Oh, one last thing-type carefully and don't forget to sign and mail 'em!■

```
1 CLEAR 13000
10 CLS4-PRINT040, "OSL CERTIFICATE"
15 PRINT-PRINT
20 PRINT-INPUT"MON HANY CERTIFICATES ";N
30 PRINT"CERTIFICATE OATE"
40 INPUT"PONYIE, 1ST., 17TM.ETC.> ";D$
50 INPUT"PONYIE, 1ST., 17TM.ETC.> ";D$
60 INPUT"PONYIE, 1982>";"Y
60 INPUT"PONYIE, 1982>";"Y
60 INPUT"PONYIE, 1982>";"Y
60 INPUT"CERTIFICATE OATE (EXAMPLE - 23RD AUGUST 1982>"
100 INPUT"DAY",D$:INPUT"HONTH";H$:INPUT"YEAR (ALL 4 DIGITS)";Y
100 INPUT"DAY",D$:INPUT"HONTH";H$:INPUT"YEAR (ALL 4 DIGITS)";Y
120 INPUT"ITHE(IN UTC)",T:INPUT"FREQUENCY";F
121 INPUT"TIME(IN UTC)",T:INPUT"REGUENCY";F
140 PRINT"RS-T RPTT, !INPUT"R=";R:INPUT"S=";S:INPUT"T=";T
140 PRINT"RS-T RPTT, !INPUT"R=";R:INPUT"S=";S:INPUT"T=";T
150 INPUT"ANT. SYSTEM";H$
160 INPUT"RATH.SYSTEM";H$
161 CLS-PRINT064, "CHECK YOUR PRINTER - I'LL PRINT NENT"
190 INPUT "PRESS CENTER» TO START";CR$-GOTO 218
100 INPUT "PRESS CENTER» TO START";CR$-GOTO 218
10 PRINTS-2:PRINTS-2:PRINTS-2:PRINTS-1, CHA-64 31:) 1884 14.1 "FERTIFICATE PRINT
       210 PRINTO-2:PRINTO-2:PRINTO-2:PRINTO-2;PRINTO-2;PRINTO-2:PRINTO-2:PRINTO-2:PRINTO-2:PRINTO-2:PRINTO-2:PRINTO-2:PRINTO-2:PRINTO-2:PRINTO-2:PRINTO-2:PRINTO-2:PRINTO-2:PRINTO-2:PRINTO-2:PRINTO-2:PRINTO-2:PRINTO-2:PRINTO-2:PRINTO-2:PRINTO-2:PRINTO-2:PRINTO-2:PRINTO-2:PRINTO-2:PRINTO-2:PRINTO-2:PRINTO-2:TAB(15):"KNOW YOU by the Authority invested in Us by
    #ILL HMUT IMESE PRESENTS CUTE.

220 PRINTE-2. PRINTE-2. TAB(18); "KNOW YOU by the Ruthority invested in Us by the Federal"

230 PRINTE-2. TAB(18); "Communications Commission, a resulatory agency of the "PRINTE-2. TAB(18); "Government of the United States of America, He do hereby"

240 PRINTE-2. TAB(18); "certify that on the date, and at the time and on the "PRINTE-2.

250 PRINTE-2. TAB(18); "Two-way radio communication was established between:" PRINTE-2

260 PRINTE-2. TAB(18); "Two-way radio communication was established between:" PRINTE-2

270 PRINTE-2. CHRE(31); TAB(17); "WBSLLM" "REM INSERT YOUR OWN CALLSIGN MERE, NOT MINE.

270 PRINTE-2. CHRE(30); TAB(16); "R RADIO STATION licensed by the above referenced" "PRINTE-2; TAB(18); "Federal Reency, to Us, in accordance with the Rules &"

290 PRINTE-2. TAB(18); "Regulations of the Amateur Radio Service."

360 PRINTE-2. TAB(18); "Regulations of the Amateur Radio Service."

360 PRINTE-2. TAB(18); "Regulations of the Amateur Radio Service."

360 PRINTE-2. TAB(18); "Regulation of the Amateur Radio Service."
      388 PRINTE-2: PRINTE-2: TABK:18); "AND": PRINTE-2: PRINTE-2; CMRS(31); IMBK:17; JUBUA:

): PRINTE-2:
310 PRINTE-2: SCHRS(38); TABK:11); "a radio station operatino in the aforesaid S
ervice; ": PRINTE-2: PRINTE-2: TABK:18); CMRS(
18); CMRS(28); CMRS(255); CMRS(192): PRINTE-2; TABK:18); CMRS(
18); CMRS(28); CMRS(255); CMRS(192): PRINTE-2;

320 PRINTE-2; CMRS(38); JTBK:12); "OPTE-10C(X); "/"; MC(X); "/"; YC(X); "/"; PRINTE-
2;" TIME(UTC): "; TSK(X); "Z"; "PRINTE-2;" FREQUENCY: F(X); "MXZ";

330 PRINTE-2; TABK:11; "TRANS. - HAILicrafters HT-32a/RCVR; - Hammarlund HQ-188/R
": PRINTE-2; TABK:11; "TRANS. - HAILicrafters HT-32a/RCVR; - Hammarlund HQ-188/R
REH INSERT YOUR OHN STATION EQUIPT; HERE, NOT MIME.

340 PRINTE-2: TABK:11; "SYSTEM: "INSEXX); PRINTE-2: " REMARKS: "; R8(X)
      340 PRINTO-2.TAB(12)"ANT. SYSTEM: ";As(X);PRINTO-2; REMARKS:";Rs(X)
350 PRINTO-2.TAB(17);"SIGNAL REPORT ";"R=";R(X);" ";"S=";S(X))" ";"T=";T(X
);:PRINTO-2;"NBOE: ";NGS(X)
360 PRINTO-2;TAB(18);CHRs(18);CHRs(28);CHRs(255);CHRs(192);PRINTO-2;PRINTO-2;PRINTO-2;
      378 PRINT#-2,CHR$(38);TAB(15);"FURTHERMORE, know you that this CERTIFICAT
       E shall be" 388 PRINT#-2,TRB(18); "accepted as Confirmation of said contact and exch
      ande of 390 PRINTE-2, TAB(10); "Signal Reports, etc., for any, and all, purposes t
       hat the" 488 PRINT=-2,TAB(18); "aforesaid Awardee deems his want; be it Contest, CP
    erating"
410 PRINT8-2,748(10)) "Awards, etc., in use of the above referenced Station
in the" (FRINT8-2,TA8(10)) "Amateur Radio Service."
420 PRINT8-2
430 PRINT8-2,TA8(15), "THEREFORE, In recognition of the above, We hereby s
PRINTE-2: THREE TO THE REPORT IN PROCRETE OF THE REPORT SET OF THE REPORT OF THE REPOR
       440 PRINT#-2,TRB(10); "our Hand and Seal, this, the ";D$(X);" day of ";M$(X)
```

The Six-Meter Vfo That Won't Quit

This hybrid has the best of both worlds. It's as steady as a rock and has broadband tuning.

here are certain features I like in a vfo. The prime one is stability as near to a crystal as possible, another is ease of tuning (bandspread), and a third is the ability to tune to any frequency-right down to a Hertz or so. For crystal stability over a narrow range of frequencies, the vxo (variable crystal oscillator) permits infinite resolution. Mixing various crystal frequencies can extend that range, but with considerable complexity and cost. Now that we have ICs that greatly reduce their component count, though, a PLL (phaselocked loop) can provide precise frequencies, at equal spacing over a wide band, guite economically.

The block diagram shows how a PLL with 5-kHz intervals over a range of 500 kHz is combined with a vxo that has analog tuning over a 5-kHz range to give an output of 5.5 to 5.0 MHz. In this configuration, the 5.5 represents the low transmitter frequency and the 5.0 represents the high transmitter frequency. It was chosen because that's what is required by the Heath SB-104 with which it was to be used. By careful selection of the vxo and PL frequencies, the output can be any 500-kHz segment desired, and by choosing the vxo frequency to sum with the PLL generator, the output will not be inverted.

With a 5-kHz reference


for the PLL, the "warping" of the vxo at 7.42 MHz is easily attained and guite linear. It also lets us use most any of the PLL chips found in the later CBs as well as the 10.24-MHz crystal associated with it.

The circuit is relatively simple. Q1 is the 10.24-MHz reference oscillator. Q2 amplifies and shapes its output to drive the 7473 divide-bytwo counter. Further division takes place in the PLL (MC145109) to get the 5-kHz reference. Q10 is the vxo; its output goes to the mixer (Q11). The vco is Q8, and its frequency is controlled by the output of the phase detector in the PLL chip. The output of Q8 is the other mixer input and also goes to the LM703 buffer/amplifier. It, in turn, drives Q9, the vfo output stage. The mixer output is filtered and amplified by Q12 and then applied to the signal input of the PLL.

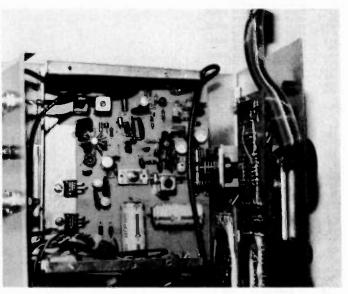Q4 adds or removes a 4.7-uf tantalum capacitor in the timing network of the 555. The 555 runs all of the time, but its output is diodegated by the UP or DOWN switches, which also determine which way the 4029



Vfo in operating position, showing panel layout.




Inside view of oscillator circuit board shows vxo frequency trimmers, tuning capacitor, and voltage regulators.

counters count. Q3 shapes the gated output to ensure clean counting. The first counter is for the 5-kHz increment, and the other counter outputs step the remaining digits. SO1 is for the display connections. If the display is omitted, SO1 can be eliminated or jumpered (pin 2 to 14, 3 to 13, 4 to 12, 5 to 11, 6 to 10, and 7 to 9; pins 1 and 8 are left connected to the other circuitry)

The LD LED is enabled by O5 when the PLL is in lock. When the PLL is not in lock. O6 disables the vfo output by applying excessive bias to the LM703 through diode DA. Q7 enables the out-ofband indicator LED and disables the vfo output in the same way as Q6. Out-ofband in this circuit is anything outside of 5.0 to 5.5 MHz and may need modification (or elimination) if, because of the accuracy of the

other transceiver crystals, the vfo must be shifted up or down.

The display portion is not needed with the SB-104 or similar transceivers with self-contained counters. For use with other rigs, it's a nice feature. When the display is used, PI-1 replaces the jumper in SO1, and the 4029 counters are set in the BCD mode by inserting a jumper from pin 9 to ground on the two most significant digit 4029s. The counters directly drive 4511 BCD-to-7-segment encoders and also two 4008 full adders to convert the BCD to binary for the PLL. Another 4008 allows adding 5 to the third digit (hundred thousand Hz) of the display. This permits setting the bandswitch of the vfo to 3.5 and 28.5 and counting from there on those band segments. The two most significant digits

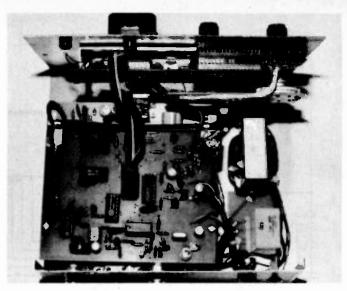

Upper portion is the display board and the PLL section is in the lower left. Power transformer is on the right

of the display are not a part of the counter but are set by a diode matrix and the bandswitch.

The RIT circuit uses a varactor and a 10k pot to vary the frequency of the vfo in the receive mode. In the transmit mode, a positive regulated voltage is applied to the varactor to reduce its effect to a minimum. This is accomplished by Q13 and Q14 by the ap-

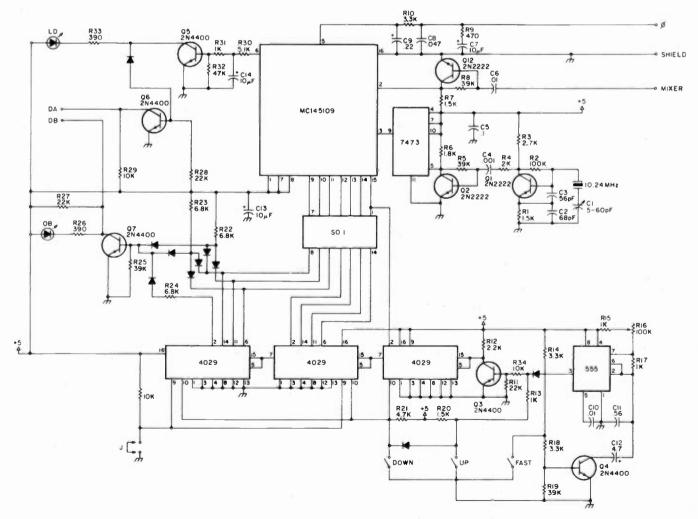


Fig. 1(a). PLL.

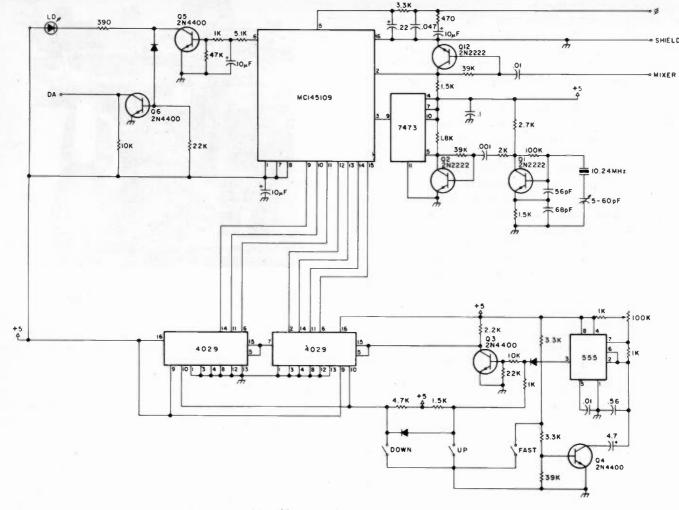


Fig. 1(b). Simpler layout for PLL.

plication of a positive voltage to the T/R terminal. In the same action, C_A is diodeswitched into the circuit to cause the vxo to operate at the mid-frequency of the receive RIT range. Because the varactor is, in effect, in series with the tuning control (C_T), the RIT range varies from $\pm 200\,$ Hz at the minimum setting of C_T to $\pm 360\,$ Hz at its maximum setting.

Any regulated power supply providing +12 and +5 volts is satisfactory. The simple one shown in Fig. 4 was used in the prototype. Current requirements, including display, are about 300 mA total.

Although I used three circuit boards because that worked out best with the case I wanted, there is no good reason why it cannot be built on one or two boards. Layout is not particularly critical except for the

usual considerations given to rf and digital construction, such as short rf leads and good decoupling. The bypass capacitors for the oscillators and integrated circuits should be placed as close as possible to the relative component. Except for LA and LR, all of the inductors are high-Q ferrite chokes. LA and LB are miniature rf transformers removed from a CB board and rewound. Because of the variations in permeability and winding area, the turns and wire sizes are not given. Both LA and LB should have unloaded Qs above 50 and be adjustable. T1 consists of a 60-turn primary and a 30-turn secondary of #30 enamelled wire, on a T-37-2 core. In the frequency-controlling portions of the oscillators, NPO capacitors are recommended. The other small capacitors can be mylarTM, ceramic, or mica; the polarized ones, either tantalum or electrolytic. The nominal frequency of the crystal in the vxo (Q10) is not critical. Crystals from 7.422 to 7.425 were easily tuned.

Although many of the parts used can be salvaged from a CB board, two lowcost transistors were used throughout. In most cases, any of the NPN rf low-power transistors in a CB will probably work in place of the 2N2222, and audio and switching NPNs can replace the 2N4400. C_T is the finetuning control that covers only 5 kHz, so it doesn't need much knob reduction. I used a 5:1 vernier and I wouldn't recommend any larger ratio.

The first step in tune-up is preliminary adjustment of the vco. With power applied, temporarily ground the phase-detector output

by shorting the .022 capacitor in the Ø line, set CE to minimum capacity, and determine if Q8 is oscillating. This can be done with a counter or by placing a lead from a shortwave-receiver input near CD and tuning the receiver in the area of 4.5 to 6 MHz. If it is not oscillating. increment CE to larger capacities and continue to check until its signal is picked up. Then adjust L_A so the generated signal is about 5.55 MHz. Remove the short across the @ line.

The initial adjustment of the vxo (Q10) is done in the receive mode with no voltage applied to the T/R terminal and with the RIT pot at its middle position. Loosely couple a frequency counter or receiver input to the source of Q10, set C_A to its middle position, and set C_B and C_C to their minimum capacities. Check the frequen-

Morse Keyers & Trainers by A

AEA produces the finest Morse keyers and trainers in the world. All AEA keyers operate with any standard keyer paddle and offer selectable monitor tone, selectable dot and dash ratios, full weighting and selectable dot and/or dash memory. In addition, all our kevers offer full, semiautomatic or straight key modes. The keyers and trainers are keypad controlled which significantly reduces the complexity of operation for all the features offered. Each keyer has separate + and - keyed outputs for keying any modern transmitter. All keyers and trainers operate from 12 VDC (or 117 VAC with optional model AC-1 wall adaptor) which makes them ideal for portable operation. AEA microcomputer-based products are all subjected to a full burnin and test prior to shipment, as well as being designed for maximum R.F. immunity.

NEW BT-1



The BT-1 Basic Trainer is a hand-held computerized unit which teaches the code one character at a time at 18 or 20 words per minute. The BT-1 contains a self-paced training program that allows seriou\$ students the possibility of learning Morse to 20 wpm in as little as one month! Each character represents a separate practice session in which the character is first introduced by itself, and then presented 50% of the time along with all previously learned characters. There are no tapes to memorize, wear out, or break. No programming skills are necessary; the BT-1 is very easy to use. The tone oscillator can also be keyed for sending practice. An earphone jack is provided for private listening. The BT-1 will go as high as 99 WPM

in 1 WPM increments. A battery operated version, the BT-1P, is

available with wall charger and internal NICAD batteries.

The KT-3 Keyer-Trainer unit uses the teaching program used in the BT-1 trainer. In addition, the KT-3 features a full function Morse automatic keyer for keying any modern transceiver, or for sending practice. Speed range is 18-99 wpm for transmitting and 1-99 wpm for training.

The KT-2 Keyer-Trainer is a computerized keyer with all the features shown above, plus

KT-2 Keyer Trainer



a Morse proficiency trainer. It is designed to increase your existing code as quickly as possible. The unit can be set for beginning practice speed, ending practice speed, and

duration of practice. The microcomputer does all the rest by gradually increasing the speed during the practice time selected. You can even select between fast code (Farnsworth) or slow code methods. The characters are sent in 5 letter groups, or random word lengths. Two levels of difficulty can be selected; common Morse characters or all English Morse characters. A 24,000 character answer book is provided for the 10 separate starting positions. There is also random practice mode for which no answers are available.

The CK-2 Contester™ Keyer is the lowest cost automatic keyer available featuring an automatic serial number generator for contesting. The CK-2 keyer features a large 500 character message memory that can be softpartitioned into as many as 10 sections. An exclusive AEA edit mode makes it possible to correct mistakes made while entering messages or to insert words into previously established messages. Two different speeds can be set for fast recall in addition to

MM-2 MorseMatic™



a stepped variable speed control. The CK-2 features an automatic message repeat mode with variable delay-before-repeat for automatic CQ transmissions or TVI testing.

The MM-2 Morsematic Keyer represents the most sophisticated paddle keyer ever designed and features two powerful microcomputers. The Morsematic incorporates virtually all the features (except the preset and stepped variable speeds) of both the CK-2 and KT-2 shown above. In addition, the MM-2 offers an exclusive automatic beacon mode which is invaluable for meteor scatter, moonbounce scheduling,

or beacon operation.



Advanced Electronic Applications, Inc.

P.O. Box C-2160, Lynnwood, WA 98036 (206) 775-7373 Telex: 152571 AEA INTL



NEW

KT-3



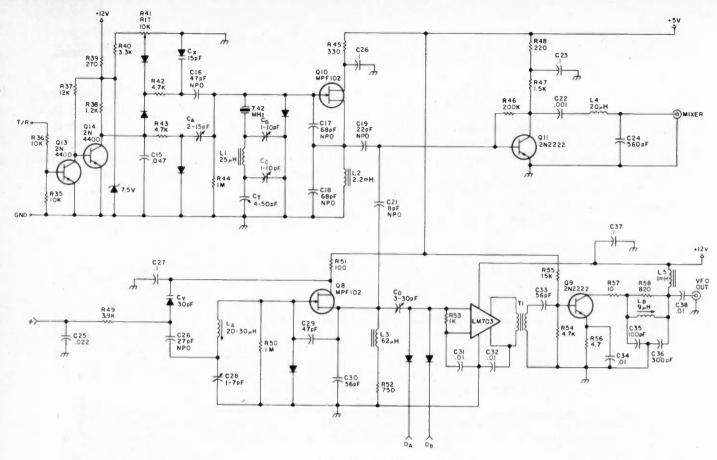


Fig. 2. Oscillators

cy of Q10 at maximum and minimum settings of C_T. At 10 degrees short of minimum capacity, the desired frequency is 7.420 MHz. At 10 degrees short of maximum capacity, it should be 7.415 MHz. The ten degrees

on either end allows for some overlap and keeps the dial markings in the more linear range of the capacitor. As C_B and C_C interact with each other, it is necessary to repeat their adjustments using C_C when C_T is

near minimum and C_B when C_T is almost fully meshed.

When these adjustments are completed, set C_T near maximum and note the frequency. With ± 12 volts applied to the T/R terminal, adjust C_A to the same frequen-

cy. Leave the 12 volts connected to the T/R terminal until the rest of the alignment is done. If there are circuit errors, much time can be saved if the rest of the checks and adjustments are done systematically.

Check the waveform at pin 9 of the 7473 with a scope. It should be a clean 5.12-MHz square wave. In lieu of a scope, loosely couple a receiver input to pin 9 by laying the antenna lead close to it and tune the receiver to 5.12 MHz. If the signal is steady and pure, the reference oscillator can be assumed to be working OK.

To check out the counter, measure the dc voltage present at pin 15 of the PLL (MC145109). It should swing from zero to nearly +5 volts as the counters are enabled by either the UP or DOWN switches. Check each of the counter output lines, pins 14 through 9 on the PLL. They, too, should alternate between zero and +5 volts, but at successive-

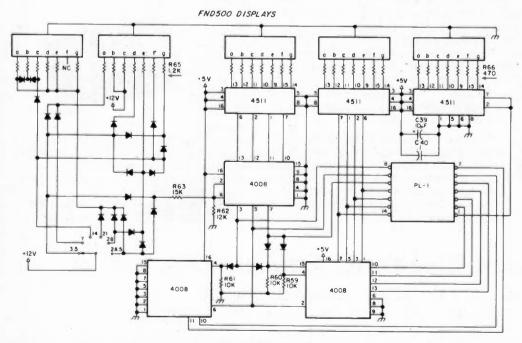


Fig. 3. Display.

P.C. BOARDS FOR MOTOROLA BULLETINS SEMI CONDUCTORS: AN-762 - 14.00 MRF-208 - 12.00 MHW-252 - 50.00 ER-18A - 12.00 MRF-240 - 15.50 MHW-710-1 - 61.00 EB-27A - 14.00 AN-791 - 10.00 MRF-247 - 34.80 MPSH-81 .50 EB-63 - 14.00 EB-67 - 14.00 KEMET CHIP CAPACITORS:56 pf, 82 pf, MRF-309 - 27.60 MV2205 .58 MRF-422 - 41.40-78L08CP . 50 100 pf, 390 pf, 470 pf; -. 50 ea .75 MRF-454 - 20.00 2N4401 680 pf, 1000 pf; -.55 ea MRF-901 -1.75 2N5190 1.50 5600 pf, 6800 pf, .1 µf;-1.00 ea SBL-1 Double-Balance Mixer -6.50 .33 µf;-1.90 ea .68 µf;-3.90 ea CAMBION RF CHOKES: .15 µh, .22 µh, .33 µh, 4.7 µh, 10 µh - 1.20 ea BROADBAND TRANSFORMERS PER MOTOROLA BULLETINS: AN-762, EB-27A, EB-63 UNDERWOOD/SEMCO METAL-CLAD MICA CAPACITORS:5pf,10pf,15pf,25pf,30pf, 40pf,56pf,60pf,68pf,80pf,91pf,100pf,200pf,250pf,390pf,470pf,1000pf We also carry a line of VHF, UHF amplifiers and ATV equipment. Call or write for our free catalog.



Communication Concepts Inc.



2648 North Aragon Ave• Dayton, Ohio 45420•(513) 296-1411 - 14



BOUTE 286 PRESOUR ISLE PLAZA TTSBURGH, PA 15239 (412) 733-1555





CORSAIR SPECIAL OFFER

Buy Ten-Tec's Fantastic HF Transceiver, and get

- 1) FREE! Your choice of IF Filter from Ten-Tec
- 2) 30 Day Money Back Guarantee!
 - -- EXCLUSIVE WESTECH BONUS--
- 3) FREE! Model 220 1st IF Filter (8-pole, 2.4khz) ALL FOR ONLY \$1019

WESTECH ELECTRONICS is your dealer for Ten-Tec, Azden, Astron, Hy-Gain, Cushcraft, Butternut, Bencher, Vibroplex, Nye-Viking, MFJ, Dalwa, Kantronics, Digimax, and more

FREE SHIPPING (UPS Brown) on prepaid orders (Cashier's Check/M.O.). Prices and Availability subject to change; please call for latest information.

MON. 10-6 TUES. 10-8 WED. 10-8

CALL (412) 733-1555 THUR. 10-8 FRI. 10-6 SAT. 10-4 C

RF TRANSISTORS

FRESH STOCK - NOT SURPLUS

2-30 MHz Match/F P/N MRF412 MRF421 MRF450 MRF450A MRF453 MRF435A MRF454 MRF454A MRF455 \$13.50 MRF455A 13.50 MRF458 18.00 MRF492 20.00 \$30.00 30.00 40.00 \$18.00 \$39,00 27.00 12.50 58.00 SRF2072 SRF2769 33.00 33.00 CD2545 CD3424 & Quads P/N MRF475 MRF476 MRF477 SD1407 SD1487 Marched Net 5.00 3.50 13.00 37.00 MRF406 MRF422 MRF433 39.50 14.50 MRF435 S10-12 14.50 \$10-12 F TRANSISTORS MHz 145-175 130-175 130-175 27-50 130-175 130-175 130-175 VHF & UHF Typė MRF238 MRF240 MRF245 MRF247 MRF492 Net/ea 13.00 15.00 27.00 27.00 20.00 29.50 37.00 83.50 SD1416 SD1477 125W SD1477 SD1441 2N6081 2N6082 2N6083 2N6084 2SC1955 2SC2289 130-175 25W 30W 40W 1W 5W 15W 25W 45W 60W 130-175 130-175 130-175 130-175 130-175 430-470 430-470 430-470 MRF641 MRF644 MRF646 MRF648 Technical Assistance and cross-reference Information on CD, PT, RF, SRF & SD PIN's; (619) 744-0728 C.O.D. or VISAIM.C. Call our Engineering Dept. WE SHIP SAME DAY Add \$3.50 Shipping Minimum Order \$20.00 RF Parts Catalog Avail. OEM & Ouantity Discounts
ORDERS ONLY: 800-854-1927





LIQUID CRYSTAL 1 GHZ FREQUENCY COUNTER

- ★ .75" 9 Digit L.C.D. Display
- ★ 24 Hr Clock Hr.-Min.-Sec.
- ★ 10 Min. Timer with warning tone
- ★ Low-Low sensitivity less than 15 Mv from 10 Hz to 1 GHz
- ★ 4 Gate Times .5, 5., 1., 10. Sec.
- ★ Resolution: .1 Hz to 20 MHz 10Hz to 1 GHz

- ★ Time Base: .1 PPM TCXO Standard (10 MHz Crystal)
- **★** Push Button simplicity
- Liquid Crystal Easy to read in direct sunlight
- Size 1114" W x 4" H x 814" D OPTIONS:
- ★ Internal battery source available
- ★ .01 Crystal oven timebase available

100% Parts and Labor guarantee for 1 year

DEALER **INQUIRIES** To order by Visa or Master Charge No C.O.D. orders

Call 800-428-3500 Information 317-291-7262

6254 La Pas Trail Indianapolis, Indiana 46268 ELECTRONIC

ly slower rates, when the UP or DOWN switches are closed. When you're satisfied with the results, run the counter up or down until pins 9 through 15 are all at zero volts. This represents a setting of 384 for the divide by N counter in the PLL. As the reference frequency is 5 kHz, the phase detector will lock on a frequency of 1.92 MHz (384×5000). If the vxo

tuning capacitor (C_T) is set near minimum to a frequency of 7.420 MHz, then the phase detector in the PLL will try to tune the vco to 5.5 MHz (7.42 – 1.92). Note that the varicap in the vco returns to a positive voltage so the vco frequency will be lowered as the 0 voltage becomes more positive. Adjust L_A until it locks with a voltage of about \pm 3 volts at pin

5 of the PLL. Run the count from the 4029s to 483 (2.415 MHz) to make sure it stays in lock, then stabilize the slug of L_A with hot wax.

To adjust the vfo buffer and output, temporarily connect a 47- or 51-Ohm, 2-Watt carbon resistor across the vfo output jack and tune L_B for maximum output at 5.2 MHz. Adjust the rf output to about one

volt with C_D, and remove the 2-Watt resistor.

The 10.24-MHz reference oscillator is most easily trimmed with the aid of a frequency counter. If the vfo is to be used with a transceiver with a built-in counter, precise alignment is not that important. In any case, you may want to calibrate the 5-kHz dial of C_T.

For the UP, DOWN, and

	Parts	s List	
Resistors (1/4-Watt carbon):		(mylar):	
R56 (1)	4.7 Ohm	C25 (1)	.022 uF
R57 (1)	10 Ohm	C9 (1)	.22 uF
R51 (1)	100 Ohm	(tantalum):	.22 01
* *			50 5
R48 (1)	220 Ohm	C11 (1)	.56 uF
R39 (1)	270 Ohm	C12 (1)	4.7 uF
R45 (1)	330 Ohm	(25-volt electrolytic):	
R26 (1), R33 (1)	390 Ohm	C7 (1), C13 (1), C14 (1), C39 (1), C43 (1), C45 (1)	10 uF
R9 (1), R66 (21)	470 Ohm	C41 (1), C42 (1)	1000 uF
R52 (1)	750 Ohm	(varicaps):	
R58 (1)	820 Ohm	C _X (1)	15 pF
R13 (1), R15 (1), R17 (1), R31 (1), R53 (1)	1k	C _V (1)	30 pF
R38 (1), R65 (13)	1,2k	(miniature ceramic trimmers):	
R1 (1), R7 (1), R20 (1), R47 (1)	1.5k	C28 (1)	1-7 pF
R6 (1)	1.8k	C _B (1), C _C (1)	1-10 pF
R4 (1)	2.0k	C _A (1)	2-15 pF
R12 (1)	2.2k	C1 (1)	5-60 pF
R3 (1)	2.7k		5-60 pr
R10 (1), R14 (1), R18 (1), R40 (1)	3.3k	(mica compression trimmer):	0.00 - 5
		C _D (1)	3-30 pF
R49 (1)	3.9k	(standard air variable):	
R21 (1), R42 (1), R43 (1), R54 (1)	4.7k	C_{T} (1)	4-50 pF
R30 (1)	5.1k	Inductors (hi-Q, fixed):	
R22 (1), R23 (1), R24 (1)	6.8k	L4 (1)	20 uH
R29 (1), R34 (1), R35 (1), R36 (1), R59 (1), R60 (1),		L1 (1)	25 uH
R61 (1)	10k	L3 (1)	62 uH
R37 (1), R62 (1)	12k	L5 (1)	1 mH
R55 (1), R63 (1)	15k	L2 (1)	2.2 mH
R11 (1), R27 (1), R28 (1)	22k		2.2 1111
R5 (1), R8 (1), R19 (1), R25 (1)	39k	(shielded, variable):	7 40 11
R32 (1)	47k	L _B (1)	7-10 uH
R2 (1)	100k	L _A (1)	20-30 ul
R46 (1)	220k	Transformers:	
R44 (1), R50 (1)	1 meg	T1 (1) (described in text)	rf
1144 (1), 1130 (1)	Timey	T2 (1) 115-V:12.6-V, 1-A	power
Potentiometers (standard 2-Watt carbon):		Transistors:	
R41 (1)	10k		MPF102
R16 (1)	100k	Q8 (1), Q10 (1)	
	,	04 (4) 00 (4) 00 (4) 044 (4) 030 (4)	FET
Capacitors (ceramic NPO):		Q1 (1), Q2 (1), Q9 (1), Q11 (1), Q12 (1)	2N2222
C21 (1)	8 pF	Q3 (1), Q4 (1), Q5 (1), Q6 (1), Q7 (1)	2N4400
C19 (1)	22 pF	Diodes:	
C26 (1)	27 pF	2 LED OB, LD	
C16 (1), C29 (1)	47 pF	35 1N4148 signal diodes	
C3 (1), C30 (1), C33 (1)	56 pF	1 1-A, 50-V bridge rectifier	
C35 (1)	100 pF		
(polystyrene):	100 p	Integrated circuits:	
C36 (1)	300 pF	1 LM340T12 voltage regulator	
C24 (1)		1 LM340T5 voltage regulator	
OL4 (1)	560 pF	1 LM703K rf amplifier	
Capacitors (disc ceramic):		3 4029 counters	
C4 (1), C22 (1)	.001 uF	3 4008 adders	
C6 (1), C10 (1), C31 (1), C32 (1), C34 (1), C38 (1)	.01 uF	3 4511 BCD-to-7 segment decoders	
C8 (1), C15 (1)	.047 uF	1 7473 dual flip-flop	
C5 (1), C20 (1), C23 (1), C27 (1), C37 (1), C40 (1).	.U-7 UI	1 MC145109 PLL circuit	

SOLE SOURCE?

According to Kenwood's Parts Department, all CW and other crystal filters for its older models such as the TS511, R599, TS520, and TS820 have been discontinued. If so, FOX TANGO becomes the sole known source of high-quality 8-pole crystal filters for drop-in installation in these fine rigs, all of which have a 3395 kHz intermediate frequency.

3395 kHz FILTER BANDWIDTHS IN STOCK CW: 250 and 400Hz. SSB: 1.8

For newer models like the TS130, TS430, TS530, TS830, TS930, and R820, FOX TANGO is the sole source of superior 8-pole discrete-crystal substitutes for the smaller YF-88 Monolithic and CF-455 ceramic units. Since they are larger in size, the FOX TANGO filters must be patched into the circuit with coax but all needed materials and detailed instructions are included in the price of the filters; no drilling is reguired. All have an 8830 kHz center frequency (CW 8830.7 except TS930)

8830 kHz FILTER BANDWIDTH IN STOCK CW: 250 and 400 Hz. SSB: 1.8 and 2.1 kHz. AM: 6.0 kHZ\$60 each

The more sophisticated TS830, TS930, and R820 use the above 8830 filters plus 455 kHz units for their final intermediate frequency (CW455.7 except TS930).

455 kHz FILTER BANDWIDTHS IN STOCK CW: 400 Hz. SSB: 2100 kHz. Price reduced. Now only \$110 each. Replacing (or supplementing) both 8830 and 455 kHz original filters with a matched-pair of FOX TANGO discrete-crystal SSB units results in a dramatic improvement of selectivity in both SSB and CW! Indeed, the VBT is so effective at narrow frequencies that separate CW filters are needed by only the most dedicated CW operators. For a detailed report send an SASE for a free reprint of a threepage article from "73" magazine and comparative characteristic curves.

FILTER CASCADING KITS

The TS830, TS930, and R820 owe their exceptional selectivity (with superior filters) to the fact that I-f signals must pass through two filters with 16 poles of filtering. Essentially the same effect can be achieved in the other sets by adding an additional 8-pole FOX TANGO SSB filter and a board for impedance matching and insertion-loss compensation. This is known as Filter Cascading and FOX TANGO kits include a recommended 2.1 kHz filter (1.8 optional) and all needed parts and instructions; wired and tested, ready for easy installation.

CASCADING KITS FOR TS520

and TS820 .\$75 each (An improved kit for the TS430S will be available shortly for \$85)

ORDERING INSTRUCTIONS: Specify the MODEL in which the filter(s) or kit(s) is to be used and the filter bandwidth and frequency desired. Order by mail or telephone. We accept VISA/MC or ship COD. Add for shipping: \$3 (COD \$1 extra), Airmail \$5, Overseas \$10.

> ONE YEAR WARRANTY GO FOX-TANGO—TO BE SURE!
> Order by Mall or Telephone. Order by Mall or Telephone.
>
> AUTHORIZED EUROPEAN AGENTS

Scandinavia: MICROTEC, Makedien 26, 3200, Sandefjord, NORWAY Other: INGOIMPEX, Postfach 24 49, D-8070, Ingolstadt, W. GERMANY

FOX TANGO CORPORATION Box 15944 S. W. Palm Beach: FL 33416 Telephone: (305) 683-9587







- Features:
 State of the Art CMOS Circuitry
 Charice of Message Storage
 A Sir So Character messages
 B Tweeve 28 Character messages
 C 27 combinations of message
 C programming

- PLUS:

- Self comprehing dats and deshes
 80m dat) and deshes
 80m dat) and desh memory
 80m dat) and desh memory
 850m dat) and memory
 850m dat)
 850

DELUXE MESSAGE MEMORY KEYER



\$89.95

Features:

- neo 25 character messes storage Records at any speed plays at
- eny speed
 Memory operating &ED
 Use for daily QSO or confests
- Model TE-284

CHAMPION MESSAGE

MEMORY KEYER

\$125.95

Model TE-292

- partie
 \$50 e.p.m
 \$500 e.p.m
 \$500
- STATE OF THE STEEL FULLY
 GUARANTEED LESS BATTERY



Features:

Advanced CMOS message memory
Fino 150 char each message
slorage
Repeal function
Records at any speed—prays back
Longer message capacity
Example send CC OC CD DX de
WBZYJAM WBZYJAM K—then play
second message on contact—de
Paul X
Follow CD X NY WS 750 X7 Paul
Faul X
Use for daily QSOs or contests

State of the art CMOS keyer
Self completing dots and dashes
Both dot and dash memory
I ambic keying with any squeeze
partitle

• Tambot keving with any squeete paddle
• \$50 epm

or only the square fone, tune and
exempt controls
• Suderone and Speaker
• Low current drain CMOS battery
operation—portable
• Deluxe quater inch is too depring and output
• Why gird book TESTED FULLY
GUARAN (FED—LESS BATTERY

Model # TE201

\$75.95

MESSAGE

MEMORY

KEYER

V 76

MODEL TE144 - Deluxe CMOS Electronic Keyer

MODEL TE133-same as TE144 with wgt. and tone control internal, less semi-auto keying.

\$55.95 MODEL TE122 - same as TE133 less wgt., tune solid state keying

AT YOUR DEALER OR SEND CHECK OR

MONEY ORDER.

(pius 12 00 sin ELECTRONICS, INC 1106 RAND BLDG. RAC BUFFALO NY 14203 TRIONYX INC MANUFACTURER OF ELECTRONIC TEST

COMPLETE SYSTEMS

Barren Ba **BUILT ANTENNA** 1.9 TO 2.5 GHZ AND VARIABLE TUNER OPERATES ON TV CHANNELS 2 THRU 6



\$59.95

ALL SYSTEMS INCLUDES DETAILED INSTRUCTION

DOWN CONVERTER BOARD & PARTS KIT

MICROWAVE SYSTEMS AND

AMATEUR

95



VARIABLE POWER SUPPLY BOARD & PARTS KIT



EQUIPMENT

600

MHZ FREQUENCY

COUNTERS

ALUMINUM CABINET ALL HOLES PRE-PUNCHED \$6.95

MICROWAVE ANTENNA KIT \$9.95 **DOWN CONV KIT.... \$9.95** POWER SUPPLY KIT \$9.95 CABINET \$6.95

ALL RG59/U COAX CABLES COME WITH CONNECTOR N ATTACHED

TACHED	>
100 FT\$15.95	METER
75 FT\$13.95	ER
50 FT\$10.95	
3 FT\$2.50	5/8
	~




\$36.80

6219 COFFMAN RD. INDIANAPOLIS, IN 46268 ADD \$3.50 FOR SHIPPING

(317)

PHONE OR MAIL



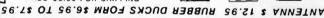

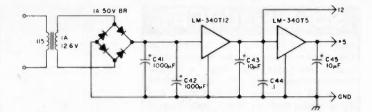


Fig. 4. Power supply.

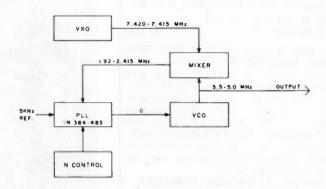


Fig. 5. Block diagram.

FAST switches. I used calculator keypads and the shaft and bushing of a discarded pot. A clockwise pressure closes the UP switch, counterclockwise the DOWN, and a gentle push puts it in FAST.

Construction and adjustment were not difficult. And best of all, several months of use have demonstrated its stability, reliability, and operating ease. It gives me what I want: A rock-hard signal with a soft touch.

COMPLETE READY-TO-USE SYSTEMS

WAVE

HT

ATV TRANSMITTER/CONVERTER



TC-1

\$399

- High resolution and color video
- 10 watts output
- Broadcast standard sound
- Tunable downconverter and preamp

Connect to the antenna terminals of any TV set, add a good 450 MHz antenna, a camera and there you are . . . Show the shack, home movies, computer games, video tapes, etc.

ATV DOWNCONVERTER

For those who want to see the ATV action. before they commit to a complete station, the TVC-4 Is for you. Great for public service setups, demos, and getting a buddy interested. Just add an antenna and a TV set tuned to CH. 2, 3, or 4 and plug in to 117 volts'a.c. \$89.00



TVC-4

TVC-4L extra low-noise version . . . \$105 delivered in USA

MODULES



TXA5-4 Exciter/Modulator



TVC-2 ATV Downconverter . Striptine MRF 901 preamp and double balanced mixer Striptine man 30 per solution of the weak ones and resists intermod and overload. Connects between UHF antenna and TV set. Dutput channels 2 or 3. Varicap tuner 420 to 450 MHz. Requires 12 to 18 VDC @ 20 ma.

Extrasensitive TVC 2L with NE64535 preamp \$59.00 ppd.

(.9 dB NF) . \$59.00 ppd.
Supersensitive TVC 2G with GaAs Fet preamp (.5 dB
NF) ant. mount . \$79.00 ppd.


Let P.C. put you on the air and SAVE! All four modules — Complete System price \$245.00

SAVE \$11.00 over price if purchased individually



FMA5 Audio Subcarrier Generator . \$29.00 ppd

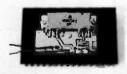Puts audio on your camera video just as broadcast does at 4.5 MHz Puts out 1 V p-p to drive TXA5. Requires tow Z mike. 150 to 600 Ω and 12 to 18 VDC @ 25 ma. Works with any transmitter with 5 MHz video band-



PA5 10 Watt ATV Power Amplifler . \$89.00 ppd. The PA5 will put out 10 watts RMS power on sync tips when driven with 80 mw by the TXA5 exciter. 50 ohms in and out plus bandwidth for the whole band with good linearity for color and sound. Requires 13.8 VDC reg. @ 3 amps

Call or write for our complete catalog of specifications, station setup diagrams, and optional accessories which include: antennas, modulators, test generators, cameras and much, much more. See Ch. 14 1983 ARRL Handbook.

TERMS: VISA or MASTERCARD by telephone or mall, or check or money order by mall. All prices are delivered in USA. Charge orders normally shipped within 24 hours. Personal checks must clear first.

(213) 447-4565





P.C. ELECTRONICS 2522 Paxson Lane

Arcadia, California 91006

Tom W6ORG

Maryann WB6YSS

The solution to most interference, intermod, and desense problems in AMATEUR and COMMERCIAL systems.



±600 Khz@144 Mhz: -28dB

± 1.6 Mhz@220 Mhz: -40dB

Mhz@450 Mhz: - 50dB

Typical rejection:

. 40 to 1000 Mhz - tuned to your frequency . 5 large helical resonators

Low noise - High overload resistance
8 dB gain - ultimate rejection > 80 dB

10 to 15 volts DC operation
Size - 1.6 x 2.6 x 4.75" exc. connectors

FANTASTIC REJECTION!

Price - \$79.95 bipolar w/RCA jacks Connector options: BNC \$5, UHF \$6, N \$10

SUPER HOT! GaAs Fet option \$20





ID-2

For transceivers and repeaters - AMATEUR and COMMERCIAL
 Automatic operation - adjustable speed and amplitude
 Small size - easy installation - 7 to 15 volts DC
 8 selectable, reprogrammable messages - each up to 2 min. long
 Wired, tested, and programmed with your message(s)
 Model ID-1 - \$39.95 Model ID-2 w/2 to 10 minute timer - \$59.95

We offer a complete line of transmitter and receiver strips

and synthesizers for amateur and commercial use.

Request our free catalog. Allow \$2 for UPS shipping. Mastercard and VISA welcome

1952 Clinton St. Buffalo, NY 14206 716-824-7936, 9 to 4

WORK THE U.H.F. BANDS

Add a transverter or converter to your existing 10m, 6m or 2m equipments. Choose from the largest selection of modules available for DX, OSCAR, EME, ATV

TRANSVERTERS

2 Meters:



MMT 50-144 \$189.95 MMT 144-28 \$179.95 MMT 432-28 (S) \$269.95 MMT 439-ATV \$349.95 MMT 1296-144 \$339.95 OTHER MODELS AVAILABLE write for details

POWER AMPLIFIERS

all models include RF VOX & Low Noise RX Pre-Ampl. (no pre-amp in MML432-100)

100W output MML144-100-LS 1W or 3W in \$254.95 100W output MML144-100-S 10W input \$264.95 \$214.95 50W output MML144-50-S 10W input 30W output MML144-30-LS 1W or 3W in \$109.95 25W output MML144-25 3W input \$114.95

10W input \$399.95 432 MHz 100W output MM1.432-100 50W output 10W input 1W or 3W in MM1.432-50 \$239.95 \$199.95 30W output MMI.432-30-1. Coming soon. Watch for details.

1268-1296 MHz:

ANTENNAS (incl. 50 ohm balun) 2 Meter J-Beams: 12.3 dBd gain

8 over 8 Horizon'l pol D8-2M \$63.40 8 by 8 Vertical pol D8-2M-vert 1250-1300 MHz Loop-Yagi 1296-LY

70 cm/MBM 48 \$75.75 70 cm/MBM 88 \$105.50 \$76.95 70/MRM 48 \$44.95

Send 36¢ stamps for full details of all our VHF/UHF items.

Pre-selector filters Pre-amplifiers Antennas Low-pass filters Transverters Crystal Filters Varactor triplers Converters

Spectrum International, Inc. Post Office Box 1084S Concord, Mass. 01742 USA -436



TUBES



AERO ELECTRONICS

Electron Tubes for Industry

TOIL Free (except CA) (800) 421-4219


(800) 556-6700

2129 Venice Boulevard Los Angeles California 90006 USA

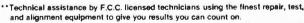(213) 737-7070

Telex 673565 Cable Aero LSA

AMATEUR AND COMMERCIÁL COMMUNICATION SERVICES



• REPAIRS

TESTS

•INSTALLATIONS

ALIGNMENTS

•MODIFICATIONS •EVALUATIONS

· General Radiotelephone (ship radar endorsed)

Second Class Radiotelegraph (ship radar and aircraft radiotelegraph endorsed)

Amateur Extra Class





13313 FOREST HILL RD. Geff N8CE **GRAND LEDGE, MICHIGAN 48837** 517-626-6044



Introducing System 80A

With the Permanent 7'11" Antenna

The size you've been waiting for, at a price you can afford. Our one piece spun aluminum dish resists corrosion. Its sturdy offset unipole mount withstands even the strongest winds.

System includes:

SAT-TEC 5000 24 Channel tuning with AFC, Meter and Modulator

LNA - 120° or Better POLAROTOR II

100 ft, cable kit

1495∞



847 West First, Hastings, NE 68901 (800) 228-4407 (In Nebr. (402) 463-3598)

Foolproof Logging

KL7CRF designed a logbook program that any TRS-80 owner can use. And it manages your QSLs, too.

s all amateurs know, the rules for logbookkeeping have been relaxed considerably by the FCC in recent years. For most amateurs, however, the log is akin to a ship's log. It is kept and kept accurately. In these days when home

computers are invading households all over America, the ham shack is one of most likely places to find a home computer. One of the most common of these is the Radio Shack TRS-80*. the largest-selling home computer in the world.

Software is plentiful for the TRS-80, and programs of almost any kind can be found at your local computer store, which brings me

to the subject of this article.

The home computer is a natural for keeping a log and keeping it well. Described herein is a logkeeping program that should satisfy the requirements of almost any amateur. In designing this

*TRS-80 is a trademark of Radio Shack, a division of Tandy Corporation.

Program listing.

```
Program listing.

10 CLEAR7000
20 CLESIDIM. $ (100,10):FORT=ITDJ0:READLE$ (II):NEXTI
30 DATADATE: ITHE.STATION.SIGNAL SENT, SIGNAL RCVD, MODE, FREQUENCY, REMARKS, OSL SENT
, OSL RCVD
40 RESTORE
50 C&="KL7GRF":CA$="LOG ROOK FOR AMATEUR RADIO STATION ":T&="UTC":E&=CHR$ (255):D
50 C&="KL7GRF":CA$="LOG ROOK FOR AMATEUR RADIO STATION ":T&="UTC":E&=CHR$ (255):D
50 C&="KL7GRF":CA$="LOG ROOK FOR AMATEUR RADIO STATION ":T&="UTC":E&=CHR$ (255):D
50 C&="KL7GRF":CA$="LOG ROOK FOR AMATEUR RADIO STATION ":T&="UTC":E&=CHR$ (255):D
50 CA="KL7GRF":CA$="LOG ROOK FOR AMATEUR RADIO STATION ":T&="UTC":E&=CHR$ (255):D
50 CA$="KL7GRF":CA$="LOG ROOK FOR AMATEUR RADIO STATION ":T&="UTC":E&=CHR$ (255):D
50 CA$="KL7GRF":CA$="LOG ROOK FOR AMATEUR RADIO LOGROOD BY JOHN E. FAIL KL7GRF."
50 GES="THENSOO"
100 PRINTBJ98, "AMATEUR RADIO LOGROOD BY JOHN E. FAIL KL7GRF."
120 PRINTBJ98, "AMATEUR RADIO LOGROOD BY JOHN E. FAIL KL7GRF."
120 PRINTBJ98, "AMATEUR RADIO LOGROOD BY JOHN E. FAIL KL7GRF."
120 PRINTBJ98, "AMATEUR RADIO LOGROOD BY JOHN E. FAIL KL7GRF."
120 PRINTBJ98, "AMATEUR RADIO LOGROOD BY JOHN E. FAIL KL7GRF."
120 PRINTBJ98, "AMATEUR RADIO LOGROOD BY JOHN E. FAIL KL7GRF."
120 PRINTBJ98, "AMATEUR RADIO LOGROOD BY JOHN E. FAIL KL7GRF."
120 PRINTBJ98, "AMATEUR RADIO LOGROOD BY JOHN E. FAIL KL7GRF."
120 PRINTBJ98, "AMATEUR RADIO LOGROOD BY JOHN E. FAIL KL7GRF."
120 PRINTBJ98, "INPUTS ARE ENCLOSED WITHIN PARENTHESES, EXAMPLE ———) (C)."
120 PRINTBJ98, "INPUTS ARE ENCLOSED WITHIN PREDATE ENTRY. SINGLE KEY"
140 PRINTBJ98, "INPUTS ARE ENCLOSED WITHIN PREDATE OSL INFORMATION"
150 PRINTBJ98, "INPUTS ARE ENCLOSED WITHIN PRINTBJP."
150 PRINTBJ98, "YOUR SELECTION PLEASE (I-G) P";
150 PRINTBJ9, "YOUR SELECTION PLEASE (I-G) P";
150 PRINTBJ98, "YOUR SELECTION PLEASE (I-G) P";
150 PRINTBJ98, "YOUR SELECTION PLEASE (I-G) P";
150 PRINTBJ98, "YOUR SELECTION PLEASE (I-G) P";
150 PRINTBJ99, "YOUR SELECTION PLEASE (I-G) 
       380 PRINTajaga, "LOG ENTRY NUMBER: (A; FRINTa/L), 1004.

390 PRINTajaga, LE$(2); IPRINTajaga, STRING$(4, 136); IPRINTajaga, T$; PRINTajaga, CHR$(14); IINPUTL&(X, 2); PRINTajaga, CHR$(128)

400 IFLEN (L$(X, 2); PRINTajaga, CHR$(128)

400 IFLEN (L$(X, 2)) = CORLEN (L$(X, 2)) > 4THENPRINTajaga, CHR$(14); INFUTL$(X, 3); PRINTajaga, LE$(3); IPRINTajaga, CHR$(128); PRINTajaga, CHR$(124); INFUTL$(X, 3); PRINTajaga, CHR$(136); PRINTajaga, CHR$(14); INFUTL$(X, 3); PRINTajaga, CHR$(14); INFUTL$(X, 4); PRINTajaga, CHR$(14); INFUTL$(X, 4); PRINTajaga, CHR$(128); PRINTajaga, CHR$(128); PRINTajaga, CHR$(128); PRINTajaga, CHR$(128); PRINTajaga, CHR$(14); INFUTL$(X, 4); PRINTajaga, CHR$(128); PRI
```

```
450 PRINT3512, LE$(5): PRINT3526, STRING$(4, 13a): PRINT3524, CHR$(14):: INPUTL$(X,5)
:PRINT3524, CHR$(12B)
400 IFLENT(L$(X,5))<10RLEN(L$(X,5))>4THENPRINT3512, E$: GOSUB1720: GOT0450
470 PRINT3576, LE$(6): PRINT3590, STRING$(7, 136): PRINT3588, CHR$(14):: INPUTL$(X,6)
:PRINT3580, CHR$(12B)
| IPRINT3524, CLE*(6):11PRINT3590, STRING$(7,136)::PRINT3588, CHR*(14)::INPUTL$(X,6) | PRINT3588, CHR*(6):InPRINT3590, STRING$(7,136)::PRINT3588, CHR*(14)::INPUTL$(X,6) | PRINT3588, CHR*(14)::INPUTL$(X,6) | PRINT3589, CHR*(128) | 480 | IFLEN(L$(X,6)) (LORLEN(L$(X,6)) > THENDRINT3652, CHR*(128) | 490 | PRINT3640, LE$(7):InPRINT3654, STRING$(7,136)::PRINT3652, CHR*(14)::INPUTL$(X,7) | PRINT3652, CHR*(128) | 500 | IFLEN(L$(X,7)) | PRINT3716, CHR*(128) | 510 | PRINT3760, CHR*(128) | 510 | PRINT364, CHR*(128) | 510 | PRINT3640, C
          840 IFLEN(L*(X.10))>3THEMPRINT3512,E4:GOSUB1720:GOTO830
850 PRINT3661, "DATA CORRECT (Y/N) ?"
```

program, I attempted to make it versatile and easy to change to fit an individual amateur's requirements. Most of all, I attempted to make it compatible with 16K cassette TRS-80 owners, as well as those with disk-drive systems. It's a toss-up as to which peripheral most will upgrade to from the cassette-based system, a printer or disk drives. Another consideration was keeping it suitable for those who use cassettes with a printer, but don't have disk drives.

The program uses sequential I/O techniques instead of random-access files. I chose this method so that the program could be easily modified to run on cassette as well as disk. Some purists will argue that random I/O is the only way to go. However, the average amateur does not make more than 10-15 contacts a day. Therefore, the in-memory storage of information is practical if the log and its data are based on daily files instead of keeping a month's log in one file on a disk.

This program is written in Microsoft Basic for the

TRS-80, but should be easily adaptable to other computers, such as Apple, North Star, and others.

The program features the following:

- 1. In-memory log for all contacts in a day's operation.
- 2. Add-on to a log or previously-filed log.
- 3. QSL information and management of received QSL as well as outgoing QSL information. Manipulation of QSL files is provided.
- 4. A hard-copy printout of each day's log data.
- 5. Permanent filing of log data on disk or cassette on a daily basis.
- 6. Compatibility with 16K as well as larger systems.
- 7. Day's log summary is provided on the video terminal.
- 8. Allows for 100 entries a day (as is), which should be changed for smaller systems and increased for larger systems if desired (details on this later).
- "Customizing" the log to fit your requirements is easy.

The Program

The program is numbered starting at line 10 in increments of 10, so just set

```
1. CREATE A NEW DAYS LOG.
2. ADD TO EXISTING LOG.
3. UPDATE OSL INFORMATION
4. SAVE LOG TO DISK.
5. LOAD LOG FROM DISK.
6. SUMMARY OF DAYS LOG.
7. DUTPUT LOG TO PRINTER.
YOUR SELECTION PLEASE (1-7) ?
```

Fig. 1. Sample of directory on video display.

```
TIME STATION SENT RCVD MODE
5. 1513UTC W6DOW 59 59 SSR
REMARKS AMSAT NET
OSL SENT 7 YES
OSL RCVD 7 NO.
                                                                                FREQUENCY QSL S QSL R
OSL SENT
```

DATA CORRECT (Y/N) 7 Fig. 2. Sample of QSL update on video display.

the TRS-80 to AUTO 10.10 and start entering the program. Lines 10-80 set up the variables, DIM statement for the actual data entries (L\$), and establish data statements for use later in the program. Change string variable C\$ in line 50 to your own callsign. String variable T\$ in line 50 is set to UTC (Universal Coordinated Time); if you desire to set time inputs to local time, change T\$ to "PDT" or whatever. Do not exceed three letters in T\$ or it will throw off the PRINT@ strings in lines 60, 70, and 80. The CLEAR statement in line 10 should be changed for smaller systems as well as the DIM stratement in line 20 (more on this later). Variables SK and SW are switches used to reset all variables to null for restarting a new log or loading data from disk or cassette.

Lines 110-160 are merely there to prompt you through the first few times you use the program; they can be deleted when you are familiar with the program, shortening execution time and saving memory. The remainder of the program should be unchanged except as described later when detailing changes for the cassettebased system. Disk-drive operators can use the program "as is."

```
890 G010860
900 PRINT@661, "ANOTHER UPDATE (Y/N) 7-
910 G0SUB1690
920 [FB8="N"THEN730
930 [FB8="N"THEN950
970 | FP86-"Y-THEN730 | 970 | FP86-"Y-THEN730 | 970 | FP86-"Y-THEN750 | 970 | FP86-"Y-THEN750 | 970 | FP86-"Y-THEN750 | 970 | FLENTH-1701905 | 970 | FLENTH-1701905 | 970 | FLENTH-1701905 | 970 | FLENTH-1701906 | 970 | FLENTH-1701906 | 970 | FP86-"D-THEN1030 | 970 | 970 | 970 | 970 
  1060 FORX=1T0100
1070 IFLEN(Ls(X, 2))=OTHEN1130
1060 PRINTD=483.X
1090 FORZ=1T010
100 PRINTD=1, X,CHR$(34);L$(X, Z);CHR$(34)
1110 NEXTX
1120 NEXTX
1130 CLOSE:GOTD170
1140 'LOAD FROM DISK
1150 IFLEN(L$(1, 2))>OTHENGOSUB1790ELSE1190
  1150 IFLEN(L$(1,21)>OTHENGGSUB179QELSE1)90
1160 GOSUB1690
1170 IFB6="C"THENGGT01740
1180 IFB6="C"THENGT0170
1190 FS6="":SK=00[CLS:PRINT9448,"(ENTER) FILE DESIRED,USE EXAMPLE, -> MAY2181 (EN TER) 'X' TO EXIT":INPUTFS6; IFFS6="X"THEN170
1200 IFLEN(FS6)<>>THENGGSUB1710:GOT01190
    1200 GOUBIETOO
1220 GOUBIETOO
1220 GOUBIETOO
1220 GOUBIETOO
1230 IFBS="D"THEN1260
1230 IFBS="X"THEN170
1250 GOTO1220
1260 ONERRORGOTO1360
1270 FSS="$5$="X|ST"**ICLS:PRINT9468,"LOADING ENTRY #1"
1280 OPEN"I",1,FS$
      1290 FORX=1T0100
      1300 PRINT9484.X
1310 FORZ=1T010
1320 IFEOF(1)THEN1360
  1320 | FEOF(1) THEN1360
1330 | INPUTEN1X, $\( (x, z) \)
1340 | NEXTX |
1350 | NEXTX |
1350 | NEXTX |
1360 | CLOSE(1): DY$=LEFT$(FS$,7): GOSUB1780: GOTO170
1370 | GOTO170
1380 | "PRINT SUMMARY
1390 | IFLEN(L$(1,2)) = OTHENGOSUB1730: GOTO170
1400 | P=128: x=1
1410 | CLS: PRINTTAB(20) "LOG SUMMARY: "; DA$
```

```
1420 IFX=101THENGGSUB1770;GGSUB1690;GGTG170
1430 PRINT@64,USINGH6;LE$(2),LE$(3),RIGHT$(LE$(9),4),RIGHT$(LE$(10),4),LE$(6),LE$(7),LEFT$(LE$(9),5),LEFT$(LE$(10),5)
1440 IFLEN(L$(X,2))=0=0HENGGSUB1770;GGSUB1690;IFB$="R"THENI70ELSE1440
1450 PRINT@P,USINGF$(X,L$(X,2),T$,L$(X,3),L$(X,4),L$(X,5),L$(X,6),L$(X,7),L$(X,9)
1450 PRINT3P, USINGF%;X,L%(X,2),T%,L%(X,3),L%(X,4),L%(X,5),L%(X,6),L%(X,7),L%(X,5),L%(X,6),L%(X,7),L%(X,5),L%(X,6),L%(X,7),L%(X,7),L%(X,5),L%(X,6),L%(X,7),L%(X,7),L%(X,5),L%(X,6),L%(X,6),L%(X,7),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(X,6),L%(
1920 GOTG1490
1530 'PRINT LDG
1540 IFLENCL$(1,2))=OTHENGOSUB1730:GOTG170
1550 CLS:PRINT3460, "LINE UP PAPER, PLACE PRINTER ON LINE.":PRINT3523, "PRESS (P)
TO PRINT, PRESS (X) TO ABORT."
   1570 IFB4="P"THEN1600
1580 IFB4="X"THEN170
                                  G0T01560
   1590 GUILISOU

1600 CLS:PRINT9470, "PRINTING LOG":PG=0:BOSUB1820

1610 FORX=1T0100

1620 IFLEN(Ls(X, 2))=OTHEN1660

1630 LPRINTTAB(5)USINGF5;X,L6(X,2),T6,L5(X,3),L5(X,4),L5(X,5),L5(X,6),L5(X,7),L5
     (X,9),L$(X,10)
1640 LPRINTTAR(9)USINGG$;LE$(8),L$(X,8):LPRINTLL$;LC=LC+3;GOSUR1850
   1640 CPRINTING (9) USING SILES (8), LS (X, B) ILPRINTE

1650 NEXTX:

1660 LPRINT": ILPRINTING (25) "END OF LOG FOR "DAS

1670 GOTO! TO

1680 END :

1690 BS=INKEYS: IFRS=""THEN1690
     1700 RETURN
1710 RETURN
1710 CLS:PRINT@473, "IMPROPER ENTRY":FORT=110700:NEXTT:RETURN
1720 PRINT@7974, "NO ENTRY PROVIDED OR IMPUT 100 LONG"::FORT=110400:NEXTT:PRINT@96
   O.E&;:RETURN
1730 CLS:PRINT0459, "THERE IS NO DATA PRESENT IN THE FILE !!!":FORT=1T0800:NEXTT:
     RETURN
1740 CLEAR: SK=1: GDT020
1740 CLEAR; SM=1:GOTO20
1750 C
```

1870 CLS:PRINT9470, "THE LOG IS FULL!!!":FORT=ITO600:NEXTT:RETURN

	TIME				FREQUENCY		OSL R
1.	REMARKS	WASP JOHN RAN	59 59 ICHO PALOS	SSB VÉRDES	144 CA. OSL DI	YES	NO
2.	0615UTC	W6WNF VIC DUAR	TE CA.	OSCAR 8	MODE J	YES	NO
3.		WOHEW	54 54 CLEMENTE	OSCAR 7	MODE 9	NO	NO
4.			59 59 MARYLAND		14282.0 A BUREAU	YES	NO
5.		WADOW AMSAT NET	59 59	SSP	3850.1	YES	NO
6.	1514UTC REMARKS	WACE AMSAT NET	59 59	SSB	3850.0	NO	NO

END OF LOG FOR MAY 21, 1981

Fig. 3. Sample of printer output.

Operation of the Program

Extensive use is made of the INKEY\$ function in the program, making it faster in use. The only time the ENTER key is used is when more than one character is to be entered. When you see a letter in parentheses, "(C)". it means that a single key input is requested and the ENTER key is not required. When the ENTER key is required, it will appear as "(ENTER)" a value. Lots of error trapping is included, so it is hard to make a mistake. Wherever a mistake is possible or imminent, a message is provided on the screen and the opportunity to exit the danger area is provided by an exit function.

No delete-entry routine is provided, since a log is defined by law as a legal docu-

- 1. Change line 10 to: CLEAR4000
- 2. Change DIML\$ statement in line 20 to: L\$(50,10)
- 3. Change "DISK" to "CASSETTE" in lines 180 (2 times), 950, 960, and 1140
- 4. Change line 330 to: FORX = 1TO51
- 5. Change line 340 to: IFX = 51THENGOSUB1870:GOTO170
- 6. Change line 1610 to: FORX = 1TO50

SAVE TO CASSETTE SECTION

- 7. Change line 1000 to: IFB\$ = "D"THEN1050
- 8. Delete line 1030
- 9. Delete line 1040
- 10. Add line 1055: PRINT#-1,DY\$
- 11. Change line 1060 to: FORX = 1TO50
- 12. Delete line 1070
- 13. Add line 1095:
- IFLEN(L\$(X,2)) = OTHENL\$(X,2) = "##":PRINT#-1,L\$(X,2):GOTO170
- 14. Change line 1100 to PRINT#-1,X,L\$(X,Z)
- 15. Change line 1760 to: CLS:PRINT@384,"1. PLACE DATA TAPE IN RECORDER.":PRINT"2. SET RECORDER TO 'PLAY' AND 'RECORD'.":PRINT"3. PRESS (D) TO SAVE OR (X) TO ABORT." :RETURN

LOAD FROM CASSETTE CHANGES

- 16. Change line 1210 to: GOSUB1880
- 17. Add line 1880: CLS;PRINT@448,"1. PLACE DATA CASSETTE IN RECORDER, ADVANCE COUNTER TO LOCATION":PRINT"DESIRED. PRESS (D) TO LOAD, (X) TO ABORT.": RETURN
- 18. Change line 1260 to: ONERRORGOTO1370
- 19. Change line 1270 to: CLS:PRINT@468,"LOADING ENTRY #:"
- 20. Change line 1280 to: INPUT#-1,DY\$
- 21. Change line 1290 to: FORX = 1TO50
- 22. Change line 1320 to: INPUT#-1,X,L\$(X,Z)
- 23. Change line 1330 to: IFL\$(X,Z) = "##"THEN1360
- 24. Change line 1360 to: GOSUB1780:GOTO170
- 25. Change the 100 in line 120 to 50

Table 1.

ment. Corrections should be made by drawing a line through the deleted or changed entry. They should then be initialed by the person making the change(s). Any changes to the log can be inserted on the hard copy produced by the printer. The printer output routine is based on an 80-column printer. The format of the output to the printer is shown in Fig. 3

The DIRECTORY video display (Fig. 1) is single-key entry. Selecting "1. CREATE A NEW DAYS LOG" clears and resets all variables. If data is present in memory. you will be warned and given the opportunity to exit to the directory and save the data to disk. If the data has already been saved and you want to start a new log, merely press the (C) key and the program will proceed to start the new setup. If no log data is present in memory, the program will proceed normally. A word of warning: When starting a new log, you will be asked for the date in a specific input manner, i.e., MAY2181. Note that no spaces are allowed. The date display is derived from this input and, more importantly, the Filespec for writing to disk is derived from it. The program checks to make sure you did in fact put 7 characters in and gives you an error message if it detects any fewer or more than 7 characters. No checking is done for proper sequence. A disk and cassette file will not accept a number as the first character of a filespec, so pay particular attention to this question.

"2. ADD TO EXISTING LOG." If data for a given day is already in memory and you wish to add to it, just press 2 and it will select the next available sequential number available and display the data input form. If you wish to add on to a filed log (on disk or cassette), load that log through the "LOAD LOG FROM DISK" function and then select the "ADD" function. Don't forget to save the log back to disk. Killing the old file is not needed since sequential techniques write over the old file which will have the same Filespec as what you write back out after additions to the log. This is a bit of a problem for cassette systems, as will be described later.

"3. UPDATE QSL INFOR-MATION" is a routine to account for outstanding QSL cards received. The procedure for this is to load the file for the data to be updated through the "LOAD FROM DISK" function. Then use the "SUMMARY" function to locate the entry you wish to update (or use the printed copy previously printed to locate the entry number). Enter the "UP-DATE" function and make the corrections. The display for "UPDATE" is shown in Fig. 2.

"4. SAVE LOG TO DISK." When completing a day's operation, use this function to save the data to disk. The Filespec is automatically created using the date question described earlier. Use this function to save back to disk after using the "UP-DATE" function or "ADD TO LOG" function if a file was loaded for addition of entries.

"5. LOAD LOG FROM DISK" is used to retrieve old files for QSL manipulation or "ADD." You will be asked the date question again here. Use care: The computer creates the Filespec from this information.

"6. SUMMARY OF DAYS LOG" gives a rundown of the day's operation (see Fig. 5). This can be looked at after loading an old file or with data already in memory.

"7. OUTPUT LOG TO PRINTER" provides neat, orderly output to a line printer for permanent record purposes. It is based in format on many of the commonly available logbooks (see Fig. 3). Full pagination is

Fig. 4. Sample of data entry on video display.

DATA CORRECT (Y/N) 7

provided for 8.5 by 11 inch paper including page numbering.

Data Input to Log

Data input format to the log is shown in Fig. 4. When this display is presented, a series of graphic blocks will be displayed to indicate the maximum length of the input. You must put an entry into each data block. Merely pressing ENTER will cause an error message and a return to that data entry. On the other hand, exceeding the blocks will also cause an error and a reprint of the requested data. The only entries that will accept no data input are REMARKS, QSL SENT, and QSL RCVD. Since this is optional information, the leeway is allowed. After completing the "form," you will be asked if the data is correct; if not, the program returns to the same entry number and resets the block in order for you to retype the entry. If it is correct, the program will ask if you want to add another entry. If not, you return to the directory. The time entry is done in military 4-digit style, i.e., 2343, 0416, etc. No commas or quotes are allowed by the TRS-80 and any data entered after a comma is inserted will be cut off. Periods are OK. The requirement for power input in the log was not forgotten. The TRS-80

video display is limited to 64 characters and addition of power input would have crowded the display quite a bit. So. I chose to leave the power input for the remarks data input.

QSL Update

This operates in a manner similar to that of DATA ENTRY, except that you only manipulate the QSL information

Hints

Save your data off to disk often during a day of operation to prevent loss of data from accidental turning off of the computer, power failures, etc. Use particular care in entering the PRINT@ variables in lines 60, 70, and 80, and make sure you see and enter the % sign on the extreme right of variable G\$ For disk systems, set the clock in the expansion interface from DOS prior to going to Basic; the time will then appear right next to your callsign through most of the program. Single-diskdrive owners can use this program by killing off all of the programs on a TRS-DOS diskette and loading this program and maintaining all data files on the same disk. Multiple-drive owners should maintain separate data diskettes. If you own a printer, then hard-copy files only could be kept, elimi-

```
LOG SUMMARY: MAY 21, 1981

TIME STATION SENT RCVD MODE FREQUENCY OSL S OSL R
1. 0413UTC W6SP 59 59 58 144 VEB NO
REMARKS JOHN RANCHO PALOS VERDES CA. OSL DIRECT
2. 0613UTC W6WWW 36 57 OSCAR 8 MODE J VES NO
REMARKS VIC DUARTE CA.
3. 0612UTC W6WEW 54 54 OSCAR 7 MODE B NO NO
REMARKS MORT SAN CLEMENTE CALIF.
4. 1213UTC W10GEY 59 59 SSB 14282.0 VES NO
REMARKS JAN KING MARYLAND OSL VIA BUREAU
5. 1513UTC W6DOW 59 39 SSB 3850.1 NO NO
REMARKS AMSAT NET
6. 1514UTC W6CG 59 59 SSB 3850.0 NO NO
```

PRESS (C) TO CONTINUE SUMMARY, PRESS (R) TO EXIT TO DIRECTORY

Fig. 5. Sample of summary on video display.



MORSE CODE from **MITRONIX**



Turn your Radio Shack Color Computer into a complete Morse Code terminal

MITRONIX MODEM—Interfaces the computer to your transceiver via the ROM PAC slot.

Cartridge: \$54.95

-You have your choice of 5 CW programs to pick from including:

-MITRONIX TRANSLATOR

This Machine Language program allows you to transmit & receive from 5-60 WPM. Features split-screen with reverse video receive, a 1024 character TX buffer, auto CQ, & 4 message memories.

Cassette: \$26.95

KA9FSQ PERSONAL CW MAILBOX-

Written in COLOR BASIC, this program allows you to transmit to 50 WPM, & receive to 30 WPM. In the MAILBOX mode, it will answer a CW call, get other station's call letters, message, data & time, and store it in memory for instant recall when you return. Also hard copy

Cassette: \$21.95

-240

For additional information and programming, write to:

Michael L. Rice, Jr. KA9FSQ MITRONIX 5953 N. Teutonia Ave. Milwaukee, WI 53209 (414) 466-6151

Sales please include 5% postage

nating the need for data diskettes or cassettes. To increase the handling capabilities for larger systems, change the CLEAR statement to a larger value, such as 10-12000, and change all 1 to 100 FOR NEXT loops to a value of 300 or so. Contest logs are possible by fixing certain variables to fixed values and inserting a duplicate-checking routine. Write if you want information on this; the changes are beyond the scope of this article

Those having heavy fingers on the keyboard should beware: If you are not used to single key entry, it's fast. Be sure to experiment with small amounts of data until you get the feel of the program, rather than commit large amounts of data

Cassette Operation and Changes

Ah, yes, the cassettes, the one true headache of homecomputer operation. This program will work very well with cassette-based I/O, but it will be very slow on the I/O operations (probably slower than you could ever believe). You must have a minimum of 16K memory for this program. I have intentionally reduced the CLEAR, DIM, and FOR NEXT loops, since you will have trouble finding a digital tape long enough to hold 100 entries. The changes to the program required for cassette operation are shown in Table 1

Summary

Contained in this article is a program that is versatile. fast, and easily changed to fit individual requirements. I hope you have fun with it. Write me with any ques-

If demand is high enough, I would consider producing this program on formatted disk and/or cassette. Contact me for information on

The Program No Net Control Should Be Without

Every net generates lists. Keep yours up to date with this TRS-80 Basic program.

Soon after we began the Central North Carolina Weather Net on the twometer band, the net-control station needed a better way of keeping track of the hams who had joined the net. In order to facilitate call-up, the net-control stations decided to maintain a sequential list of members, each with an assigned number. At the same time, we needed to determine quickly whether a station checking in had been assigned a number-that is, whether he was already listed as a member of the net. After inadvertently assigning several stations multiple numbers, I wrote a net roster program to keep track of the net membership.

The program lists stations in numeric sequence, thirty at a time, for net call-up and searches for a given call to determine if it is in the register; it corrects an erroneous entry and adds a new member's call to the register.

This program is organized as a series of subroutines called by a main calling program. This approach simplifies programming and debugging; if I want to change one of the features in the program, I change only one subroutine.

Overview

The program stores each member's call letters, county of residence, and name. The program includes the following routines: read data from tape, save data to tape, list a block of 30 net members, search for and display a specified call, sort the data by call letters, change an entry, and add an entry. The Search routine is fast—about ½ second to search up to 511 entries for a specified call.

Fig. 1 shows a flowchart of the program. The program first initializes variables (lines 10-20), reads a look-up table of county names (subroutine at line 590), and reads the file of net members from tape (subroutine at line 80). You can bypass this taperead routine if you plan to make all the entries from the keyboard. Immediately after reading the tape, the

program sorts the data by call letters. The Sort routine, does not move the main files around physically, but sets up a list of integer pointers indicating the alphabetic order of the callsigns. The callsigns and related data remain in their original order. You can reenter this routine later to include any new entries in the sorted array of pointers.

At this point the program prints the menu of commands (line 50): #—LIST, 'C'—CHANGE, 'SAVE', 'A'—ADD, 'S'—SORT. The # tepresents a numeric input. Any entry other than those on the menu initiates a search for that entry among the list of call letters.

When you enter a number, the computer lists the net member with that number, plus the next 29 members (subroutine at line 410). For example, if you enter 25, the program lists the call, county of residence, and name of the operator of the twenty-fifth through the fifty-fourth members of the net. This facilitates calling up the net. At the start

of the net session, you, as net-control station, announce, "Net members, numbers one through thirty check in now." With the first thirty members on the screen, you can greet each member by name even if your memory for names is terrible

When a member checks in who does not remember his number, enter his call letters. The computer checks to see whether the entry is a C. S. SAVE, or A. If it is none of these, the computer presumes the entry to be call letters, calls the subroutine at line 460, and initiates a binary search through the net roster for that call. Even though it is programmed in BASIC, you can search more than 500 entries in less than 1/2 second. If a match is found, the call letters, county of residence, and the operator's name are displayed at the center of the screen. If a match is not found, you can add the new station to the roster.

To add a new member to the roster, enter A. The subroutine at line 530 requests call letters, county name, and operator's name. The program stores the call letters and operator's name in memory, but does not store the entire county name. The program stores an integer number that identifies the appropriate county from the list of counties which you read in at program start. This allows many more entries in my 16K machine than would otherwise be possible

To change an entry, enter C (subroutine at line 330). You can reenter a call. county name, or an operator's name to correct an error. If you do not wish to change the entry, press Enter to retain the original content.

The binary Search routine finds only those calls which have been ordered by the Sort routine. Any time you enter one or more new calls or change one or more call letters, you need the Sort routine. This routine begins at line 120

In order to save an updated roster to tape. Enter SAVE. At this point, the program gives you an option to turn on the recorder in order to cue the tape or to continue with the Save routine (subroutine at line 270). Outputting 4 to port 255 cues the tape. This turns on the tape recorder motor in Model I machines. Then the program enters a timing loop for a few seconds before turning the recorder off. This same routine spaces into the tape a few seconds before saving the data when you continue with the Save routine. The cueing routine may not work on Model III TRS-80s. As presently constructed, the program causes the computer to first CSAVE the program, then save the data to tape.

Sort and Search Routines

A children's guessing game goes like this:

"I'm thinking of a

number between one and fifty. Guess what it is."

"Is it 10?"

"No, you're too low."

"Is it 40?"

"No, now you're too high."

And so on. The first time you played this game, you probably guessed numbers randomly until you guessed the correct number. In the example above, that could mean as many as fifty guesses. After a few such games, you may have discovered that you could guess the correct number much faster if you first guessed the middle number of the range of possible numbers-25 or 26 in the example above. If that guess is too low, the correct answer must be between 26 and 50. You then guess the middle of that range - 38. If that is too high, you next guess the midpoint of the range from 26 to 37, and so on. Each time you divide the size of the range of possible answers by two-hence the name binary search. Using the binary search, the correct number between one and fifty will always be found by the sixth guess, at the worst. That is a lot faster than 50 guesses! More than 500 entries can be searched by this method with no more than nine guesses.

In the net roster program, membership is sorted by call letters. A pointer table indicates the order; the master list is not reordered. Moving integers in memory is faster than moving strings. The master list remains in numerical order, which is convenient for display during net call-up.

The first entry in the pointer table is the subscript of the call which would be first in alphabetical order. The second entry in the pointer table is the subscript of the call which is second in alphabetical order, and so on. For example, suppose there are seven net members, with

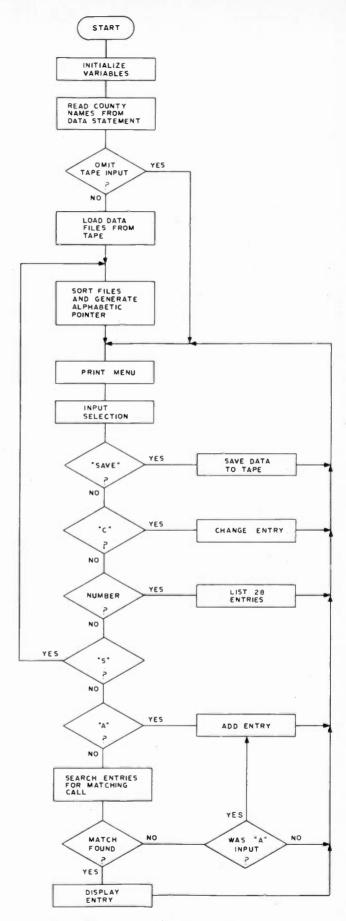


Fig. 1. Flowchart of the ham-radio-net roster.

their call letters stored in the A array as follows:

A(1) W4CBC A(2) W4BAA

```
10 CLS: CLEAR 6000: DEFINT I, J, K, N, M, L: DEFSTR A, B: MX=512
20 DIM A(MX), IC(MX), AN(MX), IA(MX), AC(105): GOSUB 590
30 INPUT "TO OMIT TAPE INPUT, ENTER '1', OTHERWISE SIMPLY PUSH 'ENTER'"; I: IF I=
1 THEN 50 ELSE GOSUB 80
 40 GOSUB 120
50 PRINT@ 960,;: INPUT "$-LIST, 'C'-CHANGE, 'SAVE', 'A'-ADD, S-SORT";B
60 IF B="SAVE" THEN GOSUB 270 ELSE IF B="C" THEN GOSUB 330 ELSE IF VAL(B) <>0
THEN GOSUB 410 ELSE IF B="S" THEN 40 ELSE IF B="A" THEN GOSUB 530 ELSE GOSUB
    460
 70 GOTO 50
 80 INPUT#-1,N
 90 FOR I=1 TO N STEP 8
100 INPUT#-1, A(I), IC(I), AN(I), A(I+1), IC(I+1), AN(I+1), A(I+2), IC(I+2), AN(I+2), A(I+3), IC(I+3), AN(I+3), A(I+4), IC(I+4), AN(I+4), A(I+5), IC(I+5), AN(I+5), A(I+6), IC(I+6), AN(I+6), A(I+7), IC(I+7), AN(I+7)
110 NEXT I: RETURN
 120 M=N: FOR I=1 TO N: IA(I)=I: NEXT I
130 M=INT(M/2)
140 IF M=0 THEN 260
150 J=1: K=N-M
 160 I=J
 170 L=I+M
 180 IF A(IA(I)) <= A(IA(L)) THEN 230
 190 IT=IA(I): IA(I)=IA(L): IA(L)=IT
            I=I-M
 210 IF I<1 THEN 230
 220 GOTO 170
 230 J=J+1
240 IF J>K THEN 130
 250 GOTO 160
 260 RETURN
 270 PRINT "PUSH 'R' KEY TO QUEUE TAPE FOR 10 SECONDS": PRINT "PUSH 'C' TO CONTIN
 HE?
 280 XX$=INKEY$: IF XX$="" THEN GOTO 280 ELSE IF XX$="R" THEN GOSUB 710 : GOTO
 280
                                               : CSAVE "W": GOSUB 710
                                                                                                                         : PRINT#-1,N: FOR I=1 TO N STEP 8
 300 PRINT*-1, A(I), IC(I), AN(I), A(I+1), IC(I+1), AN(I+1), A(I+2), IC(I+2), AN(I+2), A(I+3), IC(I+3), AN(I+3), A(I+4), IC(I+4), AN(I+4), A(I+5), IC(I+5), AN(I+6), A
 5), A(I+6), IC(I+6), AN(I+6), A(I+7), IC(I+7), AN(I+7)
310 NEXT I
 320 RETURN
 330 INPUT "NUMBER OF ENTRY TO BE CHANGED"; I
 340 GOSUB 550
 350 B=A(I): INPUT "CALL";B: A(I)=B
360 B=AC(IC(I)): INPUT "COUNTY";B: FOR J=0 TO 105: IF B<>AC(J) THEN NEXT J: GOTO
    360 ELSE IC(1)=J
 370 B=AN(I): INPUT "NAME"; B: AN(I)=B
 380 GOSUB 550
390 PRINT
 400 RETURN
             I=VAL(B): CLS
 420 FOR J=0 TO 14: IF I>N THEN RETURN ELSE PRINT@ J*64,;: GOSUB 550 : I=I+1: NE
 XT J
 430 FOR J=0 TO 14: IF I>N THEN RETURN ELSE PRINT@ J*64+32,;: GOSUB 550 : I=I+1:
    NEXT J
 440 B=STR$(I)
 450 RETURN
460 M=2[(INT(LOG(N-1)/LOG(2))+1)
470 J=M/2: I=J/2
 480 IF B>A(IA(J)) THEN J=J+I ELSE IF B<A(IA(J)) THEN J=J-I ELSE 510 490 IF I=0 THEN PRINT "*** CALL NOT FOUND ***": GOTO 520 500 I=I/2: GOTO 480
 510 I=J: GOSUE 570 : RETURN
520 INPUT "ENTER 'A' TO ADD"; B: IF B<>"A" THEN RETURN
  530 I=N+1: N=I
 540 GOTO 350
 550 PRINT USING "### %
                                                                                                                   8 8
                                                                                                                                                     %"; I, A(I), AC(IC(I)), AN(I);
  560 RETURN
 570 CLS: PRINT@ 448, USING "### %
                                                                                                                                                                                           %"; IA(I), A(IA(I)),
     AC(IC(IA(I))), AN(IA(I));
 580 RETURN
590 FOR I=1 TO MX
 600 A(I)=CHR$(191):IA(I)=MX
610 NEXT I
620 AC(0)="": FOR I=1 TO 105
 630 READ AC(I)
640 NEXT I
  650 RETURN
  660 DATA "ALAMANCE", "ALEXANDER", "ALLEGHANY", "ANSON", "ASHE", "AVERY", "BEAUFO
RT", "BERTIE", "BLADEN", "BRUNSWICK", "BUNCOMBE", "BURKE", "CABARRUS", "CALDWELL
", "CAMDEN", "CARTERET", "CASWELL", "CATAWBA", "CHATHAM", "CHEROKEE", "CHOWAN",
 RT", "BLA...", "CAMDEN",
 ", "CAMDEN", "CARTERET", "CASWELL", "CATAWBA", "CHATHAM", "CHEROKEE", "CHOWAN", "CLAY", "CLEVELAND"

670 DATA "COLUMBUS", "CRAVEN", "CUMBERLAND", "CURRITUCK", "DARE", "DAVIDSON", "DAVIE", "DUPLIN", "DURHAM", "EDGECOMBE", "FORSYTHE", "FRANKLIN", "GASTON", "GATES ", "GRAHAM", "GRANVILLE", "GREENE", "GUILFORD"

680 DATA "HALIFAX", "HARNETT", "HAYWOOD", "HENDERSON", "HERTFORD", "HOKE", "HYDE ", "IREDELL", "JACKSON", "JOHNSTON", "JONES", "LEE", "LENOIR", "LINCOLN", "MADIS ON", "MAATIN", "MCDOWELL", "MECKLENBURG", "MITCHELL", "MONTGOMERY", "MOORE", "NA SH", "NEW HANOVER"

690 DATA "NORTHAMPTON", "ONSLOW", "ORANGE", "PAMLICO", "PASQUOTANK", "PENDER", "PERQUIMANS", "PERSON", "PITT", "POLK", "RANDOLPH", "RICHMOND", "ROBESON", "ROCKI NGHAM", "ROWAN", "RUTHERFORD", "SAMPSON", "SURRY", "SWAIN", "TRANSYLVANIA", "TYRR ELL", "UNION", "VANCE", "WAKE", "WARREN", "WASHINGTON", "WATAUGA", "WAYNE", "WIL KES", "WILSON", "YADKIN", "YANCEY", "GA", "KY", "TN", "SC", "VA"

710 OUT 255,4: FOR I=1 TO 8000: NEXT I: OUT 255,0: RETURN
```

Program listing.

A(3) W4AFF A(4) W4GGO A(5) W4HLK A(6) W4JXW A(7) W4JAV

The pointer table is stored in array IA and indicates the alphabetical order of the calls:

IA(1) 3 IA(2) 2 IA(3) 1 IA(4) 4 IA(5) 5 IA(6) 7 IA(7) 6


The first call alphabetical order is A(IA(1)). Since IA(1) is 3, the call is in A(3), and this is W4AFF. Similarly, the second call, alphabetically, is A(IA(2)), which is A(2), or W4BAA. A search for W4HLK would proceed this way. The first guess is the fourth call in the alphabetical order, or A(IA(4)), which is A(4), or W4GGO. This is too low. The next guess is the sixth in alphabetical order, A(1A(6)), or A(7) which is W4JAV. This is too high. The next guess is the fifth call in alphabetical order. That is A(IA(5)), or A(5) which is W4HLK-the correct call. The call was found on the third try. A list of up to 511 entries can be searched by checking nine entries at most by this method.

Another "trick" to speed up the search process even more compares only one letter of the call at first. then looks at the rest of the call only when necessary. Unfortunately, if we start the comparison (and the original sorting of the data) with the first letter of the call, we will be comparing Ws with Ws so often that no time will be saved. Another solution is to sort the calls initially by the most variable letter position in the call, and search first on that letter position. Then we can take advantage of the time saved by looking first at only one character.

The first character of any call can be only A, K, N, or

NEW BARKER & WILLIAMSON!

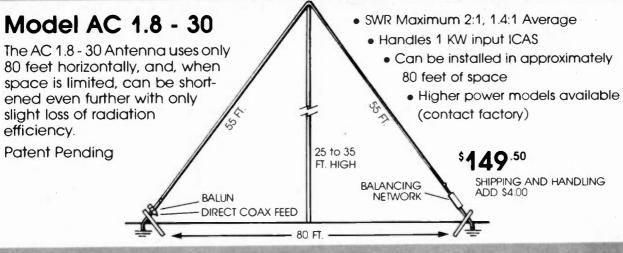1.8 - 30 MHz. Continuous Coverage Antenna for Commercial and Amateur Service





397

Barker & Williamson

ALL OUR PRODUCTS MADE IN USA

Quality Communication Products Since 1932 At your Distributors write or call, 10 Canal Street, Bristol PA 19007



THE WORLD FAMOUS

(215) 788-5581

ICOM IC-720 DRAKE TR7-DR7

Featuring Kenwood, Yaesu, Icom, Drake, Ten-Tec, Swan, Dentron, Alpha, Robot, MFJ, Tempo, Astron, KLM, Hy Grain, Mosley, Larsen, Cushcraft, Hustler, Minl Products, Bird, Mirage, Vibroplex, Bencher, Info-Tech, Universal Towers, Callbook, ARRL, Astatic, Shure, Collins, AEA. We service everything we sell:

Write or call for quote. You Won't Be Disappointed. We are just a few minutes off the NYS Thruway (I-90) Exit 32

ONEIDA COUNTY AIPORT TERMINAL BUILDING ORISKANY, NEW YORK 13424 N Y Res Call (315) 736-0184

Warren - K2IXN Bob - WA2MSH AI - WA2MSI

OUT OF STATE 800-448-9338

> REACH OUT. REACH W-A-A-A-Y OUT with the DX HIDDEN ASSET LOOP ANTENNA

This high performance, low-cost, do-it-yourself loop antenna is designed for indoor installation. Ideal for an attic, closet or any location where space is a factor. It's simple and quick to build and you'll be pleased with the remarkable results. For complete instructions and diagrams, send check or money order for \$12.50 to:

H. STEWART DESIGNS >119 P.O. BOX 643 OREGON CITY, OR 97045

PLANS FOR 2 THROUGH 15 METERS.



world famous \$3 Canadian & subscription to 304 page han OWN EARTH 360 pages MA TELEPHONES. FREE · sample	PAGES (cash OK);
Name	
Address	
City	

15 Meter Mobile CW & USB

START YOUR DAY ON A GOOD KEY!!! WORK OTHER HAMS LIKE: XE2BGM, ZL1PQ, KL7JFV, EA7EU, NN3SI, DJ8RR, DL0BBC, US6AK, JA3JMP, PY2-CPQ, FO8GW, KM6FF, VK2BD **OE8MOK G3BRW OA4ARB** CE1BLL **VE7DYX**



High 10W (PEP) low 2W (PEP): VFO tuning: noise blanker: fine-tuned SB, KHz ± CW off-set; digital frequency counter; 13.8V dc @ 3A, negative ground; L 9.5" x W 9" x H 2.5"; weight (2.3 kg) 5.7 lbs.; mobile mounting bracket.



W1AW

JUST SLIGHTLY AHEAD

DLR. INFO. & ORDER, CALL 1275 N. GROVE ST. ANAHEIM, CALIF, 92806 (714) 630-4541

NOTE: Price, specifications subject to change without notice and obligation.

Advertisement

Advertisement

Why the Spider™ Antenna?

- the ultimate in mobile antennas

C.F. (Fred) Shmitka, KOAQI 8554 Lurline Avenue Canoga Park, CA 91306

his antenna is truly amazing. I have operated H.F. mobile off and on for the past thirty years or so, and I

thought I enjoyed it. But with the combination of a solid state, no-tune rig and the Spider Antenna, hey, it's great! No stopping to change resonators or retune. Just switch the rig from band to band and enjoy your QSO's! I used a matching network at the base of the antenna in the old days, but not with the Spider. The base impedance on all four bands, 10 through 40 meters, is approximately 50 ohms. Another plus for the Spider is that it can be used in many varied and unusual installations, plus mobile on most any vehicle. Mount it on the roof of a house or mobile home; use it for back-packing or civil defense workany portable use. It can be mounted at ground level, using radials laid out on top of the ground.

There is also a Spider Maritimer Antenna made especially to withstand the corrosive action of salt water breezes and spray. Mast is non-magnetic stainless steel, the fittings are nickel-chrome plated bronze.

For complete information on the Spider Antennas and installation accessories write or call Multi-Band Antennas, 7131 Owensmouth Ave., Suite 463C, Canoga Park, CA 91303. Telephone (213) 341-5460.

W-four possibilities. The about two minutes. Even second character can be A, B. D. N. or a number. Although that number can be any value from 0 through 9, only one or two are likely to predominate in any given area. That is little improvement over the first character. The third character can be any letter of the alphabet or a number. but numbers—usually one number-will dominate because most calls begin with a two letter prefix (WA, WB. WD. KA. and so on). The fourth character is the best choice. Any alphabetic character is possible and equally likely. In this program, the calls could be sorted by the fourth character and the search carried out first on the fourth character.

Improvements

The most time-consuming part of the program is the Sort routine. It takes

though it is normally used only during program initialization, a faster routine would be desirable. One possible approach is to use a machine-language subroutine. A much easier approach is to eliminate the sort altogether, and substitute a subroutine that automatically makes the necessary changes in the pointer table whenever you add a new entry or correct an existing entry. Then the pointer table would be saved to tape along with the rest of the data.

Another useful improvement might be the addition of a map with the counties outlined on it to be displayed on the screen whenever you want. Some intriguing possibilities exist for compact storage of such a map in a string variable using the space compression codes - ASCII codes 192-255.









ORBIT is the Official Journal for the Radio Amateur Satellite Corporation.

For a **SAMPLE COPY** please send \$2 to:

(AMSAT), P.O. Box 27, Washington, DC 20047.

CES INTRODUCES THE NEW 510SA "SMART PATCH"

The State of the Art Simplex Interconnect

Communications Electronics Specialties introduces the CES 510SA "Smart" Simplex Autopatch, with many important new features never available before: • Three digit control codes with user programming.

- A sophisticated toll restrict provides positive long distance lock out.
- Time-out and COR activity timers with warning beeps and digital programming.

 Rotary or DTMF dialing.

 Phone line in-use detector prevents interrupting a call in progress, and sends unique CW sequence.

 Phone ring detection logic enables unique CW sequence.

 Digital programming of the sample rate and width, and noise gate sensitivity control, for easy interfacing with most rad os. Simple and direct connections to radio.

Options available: • Smart CW identifier with unique CW messages for each patch function.
• FCC type accepted phone line coupler. • Special tone squelch kit to operate patch through repeaters.

CES POWER NOISE PTT CONNECT HINNING STREET PATCH HINNING CONNECT OF RESTRICT POWER BIOSA



CES

The 510SA—the newest advance in interconnect technology, from the innovators at: Communications Electronics Specialties, Inc.

Post Office Box 507 • Winter Park, Florida 32790
(305) 645-0474 • Toll-free (for orders only): (800) 327-9956

UP IN THE AIR ABOUT A CHRISTMAS GIFT FOR YOUR HAM?

3 Amateur Radio's Technical Journal

Come down to Earth. give a gift subscription to 73; Amateur Radio's Technical Journal. Every issue is filled with practical information. Now your favorite ham can:

have hours of fun in the shack with over 200 construction projects per year.
 keep abreast of the latest developments in amateur radio around the world with the monthly column, "73 International".
 save money through our candid reviews and new-product announcements. Christmas shopping has never been easier. Just fill out the coupon and return it to: 73 Subscription Department, P.O. Box 931, Farmingdale NY 11737.
 It's only \$19.97 for a full-year subscription. That's a savings of 33% off the newsstand price.

This year, avoid the holiday crowds and pushy salesmen. Give your ham the gift that will keep him happy on the air. . . 73 Amateur Radio's Technical Journal.

YES! I'll give a useful gift! Send 12 issues of 73: Amateur Radio's Technical Journal for only \$19.97 to the person named below:

CHECK/M.O.
MC VISA AMEX BILL ME

CARD#_____EXP. DATE_____
SIGNATURE_____MY NAME_____

ADDRESS ______STATE ZIP

Send gift subscription to:

Canada & Mexico \$22.97/1 year only, US funds drawn on US bank. Foreign surface \$25.00/1 year only, US funds drawn on US bank. Foreign air mall please inquire. All gift subscriptions begin with the January 1984 issue.

73.

Amateur Radio's Technical Journal P.O. Box 931 Farmingdale, NY 11737 63NR6

1 1 (• (• = 5 5 (•) ?) |

300 WATT ANTENNA TUNER HAS SWR/WATTMETER, ANTENNA SWITCH, BALUN. MATCHES EVERYTHING FROM 1.8 to 30 MHz.



\$99.95 MFJ-941D

NEW **FEATURES** MFJ's fastest selling tuner packs in plenty of new features!

. New Styling! Brushed aluminum front. All metal cabinet.

 New SWR/Wattmeter! More accurate. Switch selectable 300/30 watt ranges. Read forward/reflected power.

• New Antenna Switch! Front panel mounted. Select 2 coax lines, direct or through tuner, random wire/balanced line or tuner bypass for dummy load.

 New airwound inductor! Larger more efficient 12 position airwound inductor gives lower losses and more watts out. Run up to 300 watts RF power output. Matches everything from 1.8 to 30 MHz: dipoles, inverted vee, random wires, verticals, mobile whips, beams, balanced and coax lines. Built-in 4:1 balun for balanced lines. 1000V capacitor spacing. Black. 11x3x7 inches. Works with all solid state or tube rigs. Easy to use, anywhere.

RTTY/ASCII/CW COMPUTER INTERFACE MFJ-1224 \$99.95



Send and receive computerized RTTY/ASCII/ CW with nearly any personal computer (VIC-20. Apple, TRS-80C, Atari, TI-99, Commodore 64, etc.). Use Kantronics or most other RTTY/CW software. Copies both mark and space, any shift (including 170, 425, 850 Hz) and any speed (5-100 WPM RTTY/CW, 300 baud ASCII). Sharp 8 pole active filter for CW and 170 Hz shift. Sends 170. 850 Hz shift. Normal/Reverse switch eliminates retuning. Automatic noise limiter. Kantronics compatible socket plus exclusive general purpose socket. 8x11/4x6 in. 12-15 VDC or 110 VAC with adapter, MFJ-1312, \$9.95.

RX NOISE BRIDGE

Maximize vour antenna performance!



Tells whether to shorten or lengthen antenna for minimum SWR. Measure resonant frequency, radiation resistance and reactance

New Features: individually calibrated resistance scale, expanded capacitance range (±150 pf). Built-In range extender for measurements beyond scale readings. 1-100 MHz. Comprehensive manual. Use 9 V battery. 2x4x4 in.

INDOOR TUNED ACTIVE ANTENNA

"World Grabber" rivals or exceeds reception of outside long wires! Unique tuned Active Antenna minimizes intermod, improves selectivity, reduces noise outside tuned band, even functions as preselector with external antennas. Covers 0.3-30 MHz. Telescoping antenna Tune, Band, Gain,

On-off bypass controls. 6x2x6 in.Uses 9V battery, 9-18 VDC or 110 VAC with adapter, MFJ-1312, \$9.95.



POLICE/FIRE/WEATHER **2 M HANDHELD CONVERTER**

\$39.95

MFJ -313

MFI VHF CONVERTER

112

Turn your synthesized scanning 2 meter handheld into a hot Police/ Fire/Weather band scanner! 144-148 MHz handhelds receive Police/Fire on 154-158 MHz with direct frequency readout. Hear NOAA maritime coastal plus more on 160-164 MHz. Converter mounts between handheld and rubber ducky. Feedthru allows simultaneous scanning of both 2 meters and Police/Fire bands. No

missed calls. Crystal controlled. Bypass/Off switch allows transmitting (up to 5 watts). Use AAA battery, 21/x11/2x11/2 In. BNC connectors.

MFJ/BENCHER KEYER COMBO

MFJ-422 \$99.95 The best of



a deluxe MFJ Keyer In a compact configuration that fits right on the Bencher iamble paddle! MFJ Keyer - small in size, big in features. Curtis 8044 IC, adjustable weight and tone, front panel volume and speed controls (8-50 WPM). Built-In dot-dash memories. Speaker, sidetone, and push button selection of semi-automatic/tune or automatic modes. Solid state keying. Bencher paddle is fully adjustable; heavy steel base with non-skid feet. Uses 9 V battery or 110 VAC with optional adapter, MFJ-1305, \$9.95.

VHF SWR/WATTMETER MFJ-812 \$29.95

Low cost VHF SWR/ Wattmeter! Read SWR (14 to 170 MHz) and forward/



reflected power at 2 meters. Has 30 and 300 watts scales. Also read relative field strength. 4x2x3 In.

1 KW DUMMY LOAD MFJ-250 \$34.95

TERS (IAM

Tune up fast, extend life of finals, reduce **QRM!** Rated 1KW CW or 2KW PEP for 10 minutes. Half rating for 20 minutes, continuous at 200 W CW, 400 W PEP. VSWR under 1.2 to 30 MHz. 1.5 to 300 MHz. Oil contains no PCB.


50 ohm non-inductive resistor. Safety vent. Carrying handle. 71/2x63/4 in.

24/12 HOUR CLOCK/ID TIMER

23:59 🚃

MFJ-103 \$34.95 Switch to 24

hour GMT or 12 hour format!

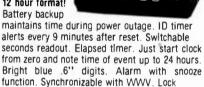

function prevents mis-setting. Power out, alarm

on indicators. Black. 5x2x3 in. 110 VAC. 60 Hz. DUAL TUNABLE SSB/CW FILTER MFJ-752B \$89.95



Dual filters give unmatched performance! The primary filter lets you peak, notch, low pass or high pass with extra steep skirts. Auxiliary filter gives 70 db notch, 40 Hz peak. Both filters tune from 300 to 3000 Hz with variable bandwidth from 40 Hz to nearly flat. Constant output as bandwidth is varied; linear frequency control. Switchable noise limiter for Impulse noise. Simulated stereo sound for CW lets ears and mind reject QRM. Inputs for 2 rigs. Plugs into phone jack. Two watts for speaker. Off bypasses filter. 9-18 VDC or 110 VAC with optional adapter, MFJ-1312, \$9.95.

ORDER ANY PRODUCT FROM MFJ AND TRY IT-NO OBLIGATION. IF NOT DELIGHTED, RETURN WITH-IN 30 DAYS FOR PROMPT REFUND (LESS SHIPPING).

- · One year unconditional guarantee · Made in USA.
- · Add \$4.00 each shipping/handling · Call or write for free catalog, over 100 products.

MFJ ENTERPRISES, INC. -9 Box 494, Mississippi State, MS 39762

TO ORDER OR FOR YOUR NEAREST **DEALER, CALL TOLL-FREE** 800-647-1800. Call 601-323-5869 in Miss, and outside continental USA Telex 53-4590 MFJ STKV



NEW PRODUCTS **TINY 2 M POWER AM** MOUNTS ON HANDH

7 to 20 watts out for 0.1 to 3 watts in. Carrier operated T-R switch. MFJ-2040, 144-148 MHz, \$79.95. MFJ-2045, 430-440 MHz, \$99.95. MFJ-2041, Portable Power Pack, \$89.95.



This tiny MFJ-2040 2 meter power amplifier mounts on your handheld between your antenna and HT. You can also mount it separately with a cable

It provides 7 to 20 watts output for .1 to 3 watts input. T-R switching is carrier operated. Covers 144-148 MHz. Die cast aluminum body is 11/2x33/4 inches. Weighs

about 6 oz. BNC connectors. Regulres 12 to 13.8 VDC at 50 ma. for receive and 1 to 2 amps for transmit.

MFJ-2045, \$99.95. Like MFJ-2041 but for 430 to 440 MHz. 4 to 15 watts output for .1 to 3 watts input.

MFJ-2041, \$89.95. Portable Power Pack Batteries provides 120 minutes operation of MFJ-2040 or MFJ-2045 at 10 watts output. Has battery check meter. Has carrying case with belt loop and shoulder strap. 11/2x21/4x71/2 inches. Weighs 2 pounds.

Cross Needle SWR/

monitor SWR, forward and reflected power at a single

glance in 3 ranges (20/200/2000 watts forward and

2/20/200 watts reflected) and SWR from 1:1 to 6:1 on a

2 color scale. Works from 1.8 to 60 MHz. Accuracy is

±10% full scale. Mechanical zero adjustment, push

button range selection. All aluminum, black w/brushed front panel. 6½x3½x4½. SO-239 connectors.

New Antenna Isolators

Wattmeter

New Cross Needle SWR/

MFJ-815

Wattmeter lets you



2 Meter Handheld Wattmeter



MFJ-1700 69⁹⁵ If you have

than

several coax

feedlines and

more

MFJ-840 lets accurately vou check the output

of your 2 meter handheld transceiver. 5 watts full scale. 50 ohm load. BNC connector. 2x21/x11/2 inches. Black

Antenna/Transmitter Switch

2 Meter Handheld SWR/ Wattmeter



MFJ-841. Con-

nects in line with

MFJ-815

your 2 meter HT. Read SWR from 1:1 to 6:1 and forward power to 5 watts. Expanded scale. 50 ohm impedance. BNC connectors 2x21/x11/2 inches Black

MFJ-1620 All Band Doublet



one rig, this MFJ-1700 gives instant selection of 1 of 6 antennas and 1 of 6 transceivers in any combination. Also plug in an antenna tuner, SWR/wattmeter, linear, etc., so that they are always in the circuit for any antenna/transceiver combination. Handles up to the full legal limit of 2 KW PEP for 50-75 ohm loads. SO-239 connectors. All aluminum, black with brushed aluminum front. 8x2x6.

Operate all bands 160 thru 10 meters including the new WARC bands with this new MFJ-1620 All Band Doublet. Use as

doublet, sloper, inverted-V or as V-beam. Completely assembled, 130 ft.(hard drawn stranded copper antenna wire) but can be trimmed to fit your lot. Center fed with 100 feet of low loss 450 ohm balanced transmission line. You need only add rope to the ends and pull into position. Antenna tuner with balanced output required.



New MFJ-782 HF/2 Meter Antenna Isolator lets you use a single coax line to feed a 2 meter antenna and any antenna below 30 MHz. The new MFJ-780 Antenna Isolator feeds separate 10,15,20 meter antennas (tri bander, etc.) Both isolators handle 2 KW PEP at 50/75 ohms. Negligible insertion loss. Completely automatic with no relays, switches or other moving parts. Easy outdoor mounting (includes hardware), SO-239 connectors.

ORDER ANY PRODUCT FROM MEJ AND TRY IT-NO OBLIGATION. IF NOT DELIGHTED, RETURN WITH-IN 30 DAYS FOR PROMPT REFUND (LESS SHIPPING).

- One year unconditional guarantee Made in USA.
- Add \$4.00 each shipping/handling . Call or write

for free catalog, over 100 products.

MFJ ENTERPRISES, INC. Box 494, Mississippi State, MS 39762 TO ORDER OR FOR YOUR NEAREST DEALER, CALL TOLL-FREE 800-647-1800. Call 601-323-5869 in Miss, and outside continental USA Telex 53-4590 MFJ STKV



The World's Cheapest Modification

All you need to put the FT-101 on 30 meters is three pieces of wire. What could be cheaper than that?

Fred Johnson WB9DDF 307 Walnut Street Knoxville IL 61448

The new WARC bands present a problem to the owner of an older transceiver. How do you modify the receiver and transmitter circuits to operate on these new amateur bands? New crystals and tuned circuits will be needed to put most rigs on the new bands, but I have found that my trusty

old FT-101 needs only three pieces of wire added to be fully operational on the 30-meter (10-MHz) band. This modification should work on the later versions such as the FT-101B, FT-101E, FT-101EE, etc. I have not yet tried it on any of these rigs, but their schematic diagrams are similar and the same modification should work.

The Yaesu FT-101 already has 10-MHz receiving capability built in to allow the operator to check the internal crystal calibrator against

WWV. After studying the schematic for some time. I decided that the only things stopping transmission on this band were the lack of tuned circuits in the driver and final plate circuits. Unlike the 11-meter band upon which the rig was designed to operate, the FT-101 was never built to transmit on the 30-meter band. There is no brightly colored jumper wire disabling the transmitter on 30 meters. In fact, there are no connections at all to several of the bandswitch waters in the 30-meter position.

The tuned circuit in the driver plate circuit is gangtuned with circuits in the driver grid circuit and in the gate circuit of the receiver's first rf transistor (T103, T102, and T101 respectively on the schematic). The frontpanel preselector control tunes all of these coils at once by running their ferrite slugs in and out together. Whatever I did to modify the FT-101, I had to maintain the proper tracking of all of these tuned circuits in both the transmitter and receiver sections of the FT-101.

The Driver

In the 10-MHz receive mode, the gate and drain circuits of the first rf transistor are connected to the 20-meter trimmer capacitors. The tuning range of the preselector is such that 10-MHz WWV can be received by running the ferrite slugs further into their coils and resonating the 14-MHz coils at 10 MHz. The FT-101's design made life easy for me in theory. All I had to do was connect the 20-meter and 30-meter band positions together in the transmitter and tune the preselector control for maximum drive.

The tuned circuit (T102) at the drain of the receiver rf stage is diode-switched to the grid of the driver tube during transmit, so no additional modification is needed here. The driver plate circuit (T103) has no connection on 10 MHz, so I had to add a jumper on wafer S1g of the bandswitch from the 20- to the 30-meter positions. The correct lugs to solder to can easily be located by rotating the bandswitch and watching where the wiper points. This operation is simple but requires a soldering iron with a very long thin tip, a pair of long-nose pliers, and the necessary skill to use these tools in tight quarters without burning or melting any important parts. A bright light with a magnifying lens will help tremendously with the modification to the bandswitch throughout this operation. (Bandswitch modifications



The outside appearance of the FT-101 remains essentially unchanged. Only the bottom cover plate and internal shield need be removed during the 30-meter modification. The position of all front-panel controls should be as shown after tuning up on 30 meters.

are definitely not for cowardly or nervous types.)

The Finals

With the driver stage taken care of, only the pi network (and the FCC) was standing in the way of my 10-MHz signal. I imagined that tying the 30-meter position to the 20-meter bandswitch position on wafer S1m would work here just as it did in the driver section, but for maximum power transfer and harmonic suppression, the coil in the pi network should have an inductance between that for the 40- and 20-meter bands. There were five turns between the 40-meter and 20-meter taps. I guessed and soldered the 30-meter tap on at a point three turns from the existing 40-meter tap. Be very careful to avoid shorting adjacent turns of the coil, as this results in very strange operation on most bands later. (This is the voice of experience speaking!) Pushing down one turn on each side of the new tap's location helps avoid shorting turns. (Yes, those tricks in the handbook really do work.) Since there is considerable rf current at this point, I used a piece of number 14 solid copper wire to connect the new tap to the 30-meter position on the bandswitch.

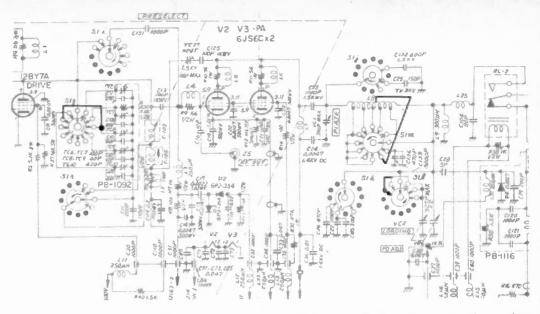



Fig. 1. Schematic diagram from the owner's manual showing the location of the three wires added to allow the FT-101 to transmit on 10 MHz.

The only other modification needed is to switch in the extra section of the variable loading capacitor. On my particular vintage FT-101, there was not a contact on wafer S11 of the bandswitch at the position that I needed to switch the extra loading capacitor section into the pi network. To get around this problem, I bent a short piece of wire to the shape of a contact. Since the 160-meter band used the extra capacitor section that I needed, I soldered the home-brew wire contact to the 160-meter position adjacent to the new 30-meter position. By care-


fully shaping and bending this piece of wire, it was made to function as a switch contact on the 30-meter band position. A little TV tuner grease will lengthen the life of this contact considerably.

Results

Testing was performed using a Bird 43 wattmeter and a Heathkit Cantenna dummy load. No change was noted in the performance of the modified FT-101 on any of the existing six bands. I made a comparison of the transmitter operation on the 20- and 30-meter bands. The modified FT-101 produced 125 Watts output for 180 Watts input power (300 mA @ 600 volts) on both bands for an efficiency of 70 percent. The only dif-

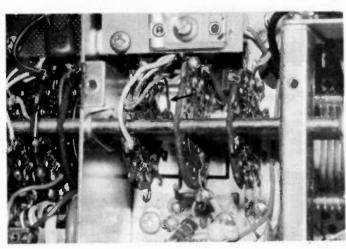

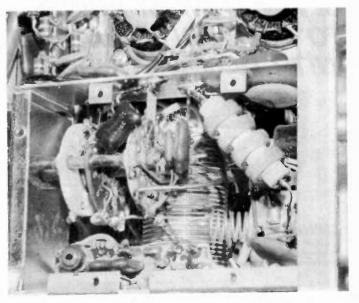The jumper wire from the 20-meter to the 30-meter position on wafer g of the bandswitch is indicated by an arrow in this photograph. Wafer g is located at the front of the driver plate compartment.



Bottom view of PA plate compartment. The home-brew switch contact can be seen on the center wafer, \$11, of the bandswitch. Also seen in this photograph is the heavy wire added from the rear ceramic wafer, \$1m, to the new tap on the pi network coil. Since the second harmonic of the 30-meter band is not an amateur band, you will need all the shielding available. Be sure that you replace all of those screws in the PA compartment's bottom shield.

OPTIONAL MOD

An additional modification may be made to the FT-101 which is not necessary to fire it up on 30 meters, but will center the load control while operating on that band.

Without this change, the antenna loading position will be about "2" when tuned for maximum rf output into a 50-Ohm load at 400 mA. However, by adding a fixed 270-300 pF, 500-600-V silver mica capacitor parallel with the variable loading capacitor (VC2), the loading position will move to about "4" or "5" when fully tuned. The capacitor should be added to the 30-meter position of bandswitch wafer S1k which faces the front of the rig.

First, however, a contact must be added to the 30-meter position of the wafer. Remove capacitors C26, C27, and C105 to get a clearer view of the wafer, then inspect the contacts on S1k closely so that you will be able to identify the correct style of contact to mount. The wrong style could result in damage to the rotating wiper of the wafer.

When you know what you are looking for, head for the junk box and find an unused wafer with the proper contacts. Remove a contact from the "donor" wafer by carefully drilling out the rivets that secure the contacts to the wafer. Mount the contact on the 30-meter position of S1k using a small bolt. Make sure that the contact is mounted on the side facing the front of the rig and tighten the bolt securely. Run the switch wiper across the new contact a few times to ensure that they make proper contact, then solder the 270- or 300-pF capacitor between the contact and ground. Don't forget to resolder capacitors C26, C27, and C105 when you are done.

> James R. Snyder WOUR 1050 Hawthorn Avenue Boulder CO 80302

ference noted was that 30-meter operation required slightly more drive. During the tune-up, 180 Watts input were produced on 20 meters with the carrier control set at 6, but when operating on 30 meters, the carrier control had to be advanced to 8 to produce the same 300-mA cathode current indication.

More Bands

The other obvious modification would be to convert the unused (I hope) 11-meter band to the new 18-MHz or 24.5-MHz band. This will require a new crystal 6.02 MHz higher than the bottom edge of the band. In other words, a 30.52-MHz crystal would be needed to operate on the 24.5-MHz band, and a 24.02-MHz crystal to operate on 18 MHz. Since the existing 10/11-meter tuned circuits will probably work fine on 24.5 MHz, only a new crystal should be needed for this band.

If you want to convert the 11-meter band to 18-MHz operation (to get better DX like 20 meters), then the existing tuned circuits cannot be stretched that far and the 15-meter trimmer capacitors will have to be connected to the 11-meter position in all stages of both the transmitter and the receiver. (Sections c, e, g, and m of \$1, the bandswitch, will all need this modification.) Adjusting the preselector to a lower frequency should be all that is then needed to be operating on 18 MHz.

Conclusion

With 10-MHz operation now a reality, the modification to get on 30 meters is simple and cheap. Very cheap! Now that the band is opened, let's use it.

Now, let's see, where is that antenna formula? Hmmmm...a bit over 23 feet on each side of a dipole.

DAIWA

GET MAXIMUM POWER TO YOUR ANTENNA SYSTEM WITH DAIWA TUNERS!



CNW-419 All Band Tuner

Specifications

●Frequency Range:1.8~30MHz. CONTINUOUS ●Power Rating:200 watts CW, 500 watts SSB ●Impedance Range:10 - 250 ohms ●Dimensions:225W X 90H X 245D



DK-200/DK-210 **Electronic Kevers**

CW is both communication and art Sharpen your "fist" with Daiwa precision!



AF-606K/AF-406K All Mode Active Filters

Luxurious selectivity at an affordable price!



CNW-518 **High Power Tuner**

Specifications

●Frequency Range:3.5~30MHz. (8 bands) ● Power Rating:1 kw CW (50% duty) ●Impedance Range:10 - 250 ohms ● Dimensions: 225W X 90H X 275D%



CL-680 Economy Tuner

Specifications

- ●FrequencyRange:1.8 ~ 30MHzCONTINUOUS
- ●Power Rating: 200 watts CW, 500 watts SSB ● Impedance Range:10 - 250 ohms ● Dimensions:165W X 75H X 97D -



CN-520/CN-540/CN-550 Cross Needle Meters

Daiwa cross-needle convenience in a compact case Get SWR and Power readings in a single glance.



858 E Congress Park Dr. Centerville, Ohio 45459, Phone 1-513-434 0031 Exclusive U.S. Agents for these DAIWA products. Dealer inquity invited



MAXIMIZE YOUR POTENTIAL **WITH 73!**

73: Amateur Radio's Technical Journal gives you more easy-to-build construction

projects and circuit designs than any other magazine of its kind. Informative articles by the dozens, on all phases of amateur radio, written by hams for hams.

73 always keeps you one step ahead with...

- ·Scores of useful building projects you'll enjoy by the hour.
- •In-depth equipment reviews, guaranteed to save you time, trouble and money.
- •73 International—delivers all the facts you need about licensing laws, club news, contests, and awards all around the globe.
- •DXing-valuable tips for newcomers, the personalities behind the callsigns, what's happening on the DXpedition scene, and much, much more!
- •New Ham Bands-timely reports on the new WARC bands, how to modify your rig to use them, what to do about antennas.
- •Satellite TV-keep up with the technology and all the latest developments in satellite communications.

PLUS

- •RTTY—with over 30,000 hams owning microcomputers, RTTY is developing a whole new life. 73 gives you more articles on RTTY than all the other magazines combined.
- •Ham Help-puts you in touch with other readers to get hard-to-find parts, schematics, and owner's manuals.
- •Contests-rules and results keep you informed about ham radio's competitive side.

Subscribe to 73 today! We'll keep you involved, informed, and completely entertained. To order, simply send in the attached order form, the coupon, or call toll free 1-800-258-5473. And if you include payment or charge card information you'll get a 13th issue FREE!

	Yes, I want to subscribe to 73:
A	mateur Radio's Technical Journal.
Lunderst	and that with payment enclosed or
	eard order I will receive a free issue
	aking a total of 13 issues for \$19.97

	□ Check enclosed/MO	□MC	□VISA	□AE	□Bill me
Card#			Ехі	o. Date_	
Signatu	ire		<u> </u>		
Name_					
Addres	s				
City		Sta	te	Zip_	
Foreign s	b Mexico \$22.97/1 yr, only US f urface \$25.00/1 yr, only, US fun irmail please inquire.				33NF6

73: Amateur Radio's Technical Journal PO Box 931 Farmingdale, NY 11737

Please allow 6-8 weeks for delivery

Now's The Time To Buy That New Repeater! -

- To Replace "The Old Klunker"
- For That "New System" you've been


Thinking about

Spectrum's Got-

- The widest line of Repeater/Link Equipment
 - The Highest Performance—by far!
 - The Finest Quality



SCR77 Basic Repeater/link Xcvr.

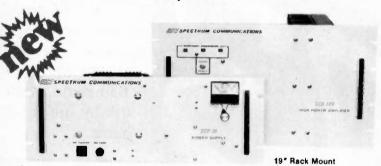


SCA100W UHF AMP w/companion SCP30 30A Power Supply.

Both Super Heavy Duty! Also 150W VHF.

There's never been a better time to buy a Spectrum Repeater or Link Equipment.

Deliveries are the fastest ever—4-5 wks. as of this writing, with some models in stock. And, with the introduction of our New 100W Repeater Amp/Pwr. Supply Package and UHF Rcvr. Helical Resonator Front End Assembly, we have the best performing, most complete line available!

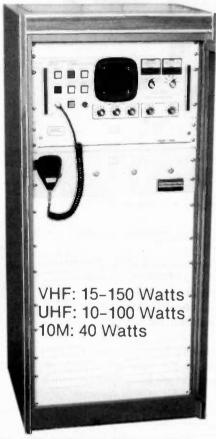Go With The Leader! Call or write today for a brochure & prices. Sold Factory Direct or through Export Sales Reps.



SCR 4000 SUPER DELUXE REPEATER WITH OPTIONAL CABINET & ACCESSORIES

AVAILABLE WITH

- Autopatch, w/Reverse Patch & Land Line Control
- Touch Tone Remote Control Functions
- Various Tone & Timer Units
- "Emergency Power ID"
- Duplexers, Cabinets, Antennas, etc. for a complete system

F.C.C. TYPE ACCEPTED FOR COMMERCIAL SERVICES



SPECTRUM Export Orders Welcomed

■1055 W. GERMANTOWN PK., DEPT S11

— Spectrum Repeater Boards & Sub-Assemblies

New FL-4 UHF **Helical Resonators** These are professional "Commercial Grade" Units—Designed for Extreme Environments (-30 to 60° C.)

All Equipment Assembled & Tested. For 10M, 2M, 220 MHz, & 450 MHz



SCR 200-VHF SCR 450 UHF

- Totally Advanced Design!
- •8 Pole Front End Fi'r. + wide dynamic range-reduces overload, spurious Resp. & IMs!
- Sens. 0.3 uV/12dB SINAD typ.
- Sel. -6dB @ ± 6.5 KHz. -130dB @ ± 30KHz. (8 Pole Crystal + 4 Pole Ceramic Fitrs.
- 'S Meter', Discriminator & Deviation Mtr. Outputs!
- Exc. audio quality! Fast squeich! w/0.0005% Crystal. ("Super Sharp" IF Filr. also avail.)

Complete Receiver Assemblies

- · Royr. Bd. mounted in shielded housing.
- Completely asmbid & tested, w/F.T. caps, SO239 conn
- · As used in the SCR1000. Ready to drop into your
- UHF Rcvr. Assy. Now Available w/Super Sharp FL4 Helical Resonators. Greatly reduces IM & 3 "out of band" Interference!



SCAP Autopatch Board

- · Provides all basic autopatch functions
- Secure 3 Digit Access; 1 Aux On-Off function. Audio AGC; Built-In timers; etc. Beautiful Audio
- 0/1 inhibit bd. also available
- · Write/call for details and a data sheet

- Used w/SCAP board to provide "Reverse Patch" and Land-Line Control of Repeater
- · Includes land line "answering" circuitry

Lightning Arrester For SCAP

- Gas Discharge Tube shunts phone line, surges to ground
- · Handles up to 20,000 Amps!
- . The Best device available to protect Au topatch equipment from lightning damage. \$14.00 + S/H.



FL-6 Rcvr. Front-End Preselector

- 6 Hi Q Resonators with Lo-Noise Translstor Amp (2M or 220 MHz
- Provides tremendous rejection of "out-of-band" signals wout the usual loss! Can often be used instead of large expensive cavity filters
- Extremely helpful at sites with many nearby VHE transmit ers to "filter-out" these 'out-of-band' signals



VHF/UHF LINK CONTROL RCVR. Complete Shielded RX Assy. With 19" Rack Mount.

ID250 CW ID & Audio Mixer Board

- 4 Input AF Mixer & Local Mic. amp.
- PROM memory—250 bits/channel.
- Up to 4 different ID channels! AF Mute circuit. · Many other features. Factory programmed.

CTC100 Rptr. COR Timer/Control Bd.

- · Complete solid state control for rptr. COR, "Hang"
- Timer, "Time-Out" Timer, TX Shutdown/Reset, etc. • Includes Inputs & Outputs for panel controls & lamps
- Repeater Tone & Control Bds. For SCR1000/4000

& CTC100/ID250 only

- TMR-1 "Kerchunker Killer" or "Time Out Warning Tone" Bd.
- TRA-1 "Courtesy Tone Beeper" Board

PRM200 Power Supply Filter Cap/Regulator/Metering Board

◆ As used in the SCR1000 as main part of 13.8VDC/8A Pwr. Sply

PSM-1 Repeater Power Supply Mod Kit

● For SCR1000 or ACR4000. Replaces Darlington Pass Tr. for improved reliability.

SCT110 VHF Xmtr/Exciter Board

SCT410 XMTR. ASSY.

10M ALSO AVAILABLE

- 10 Wts. Output. 100% Duty Cycle!
- Infinite VSWB proof.
- True FM for exc. audio quality
- Designed specifically for continuous rptr ser vice. Very low in "white noise.
- Spurious -70 dB. Harmonics 60 dB
- With .0005% xtal.
- BA-10 30 Wt. Amp board & Heat Sink, 3 sec. L.P. Filter & rel. pwr. sensor. BA75 75 Wt. unit also available.

SCT110 Transmitter Assembly

- SCT110 mounted in shielded housing
- Same as used on SCR1000
- · Completely assmbld. w/F.T. caps, SO239 conn.
- 10, 30, or 75 Wt. unit.

SCT 410A UHF Transmitter Bd. or Assy.

- · Similar to SCT110, 10 Wts. nom.
- * Now includes "on board" proportional Xtal Osc./Oven circuitry for very high stability!
 - BA-40 40W. UHF AMP. BO. & HEAT SINK.

PCB-1 Xmtr. Power Control Board

- For SCT110 or SCT410 Exciters
- Varies B+ to control Pwr. Out
- · Switchable Hi, Low, or Med. Pwr. out, locally or remotely. Adj. levels.



TTC 100 Touch Tone Control Board

Interface to any Radio or AF system!

- · 3 digit ON, 3 digit OFF control of a single repeater function, or (optional) 2 functions (2 digits ON/OFF
- · Can be used to pull in a relay, trigger logic, etc.
- . Typically used for Rptr., ON/OFF, HI/LO Pwr PL ON/OFF, Patch Inhibit/Reset, etc.
- · Stable anti-falsing design 5s limit on access
- For add'l function(s), add a "Partial TTC" board

COMMUNICATIONS

Call. or Send for Data Sheets!

INQUIRE ABOUT 'SURPLUS' RX & TX BOARDS. REDUCED PRICE! Norristown, PA 19403 • (215) 631-1710

73 INTERNATIONAL

Each month, 73 brings you amateur radio news from around the world. In this collection of reports from our foreign correspondents, we present the latest news in DX, contests, and events, as well as keep you abreast of the technical achievements of hams in other countries.

If you would like to contribute to your country's column, write to your country's correspondent or to 73: Amateur Radio's Technical Journal, Pine Street, Peterborough NH 03458, USA, Attn: Avery L. Jenkins WB8JLG.



AUSTRALIA

Jim Joyce VK3YJ 44 Wren Street Altona 3018, Australia

Perhaps the best way of explaining amateur radio in Australia would be to let you know what frequencies we are allowed to operate on and what our different license classes are.

We have 3 classes of license, the first being a Novice license. To obtain this, you have to pass an exam of 50 multi-choice questions on electronic theory (at a fairly easy level), 30 questions on regulations, and a CW exam at 5 wpm, send and receive. The Novice operators are easily recognized, as they have a 3-letter suffix starting with either N, P, or V, e.g., VK3NOL, POL, VOL. They can operate on phone or CW on the 75m, 15m, or 10m bands.

The next grade is the Limited license. For this you have to sit a much harder exam on theory and regulations, with no CW. This license entitles you to operate on all bands allocated to Australian amateurs above 50 MHz. They also have a 3-letter suffix, starting with X, Y, or Z.

The Full Call on AOCP (Amateur Operators Certificate of Proficiency), sometimes called the Full Call, entitles you to use all bands and modes available to Australian amateurs. The only difference between this license and the Limited license is that you have to sit a CW exam at 10 wpm, send and receive. The suffix for the Full Call is either 2 letters or 3 letters, starting with A, B, C, D, or E.

It has been sald that 10 wpm is below the world standard of 12 wpm. But with our exam on CW, we have to send the equivalent of 25 words (averaging five letters per word), in mixed plain language and figures (each figure counting as two letters), in 2½ minutes. More than four incorrect or improperly corrected errors or failure to complete the test in 2½ minutes will result in failure. In the receiving test, you have to receive 50 words (average five letters per word), in mixed plain language and figures (each figure counting as two letters), in 5 minutes. Each figure or letter incorrectly received counts as one error,

with a maximum of 3 errors being counted in one word or group of figures. More than 7 errors will result in a fallure.

This test, I think, is much harder than having to listen to a text sent in CW at 12 wpm, with no sending involved, when all that is required is that you write a rough draft of what has been sent (and, providing you get a fair glst of the message sent, you pass). Even at 16 wpm, I know which one I would prefer to sit for, but we cannot get the reciprocal licenses in some countries unless we get a 12-wpm endorsement on our license.

Speaking of reciprocal Ilcensing, overseas amateurs visiting Australia for less than 12 months may get a license equivalent to their own home privileges. They also have to adhere strictly to the Australian amateur-radio conditions under which the license is issued. To obtain a Ilcense in Australia, you must write to the Superintendent of Regulatory and Licensing In the state you propose to visit, with at least 3 months advance notice prior to your visit.

In the next article, I will start to explain something of what Australia is like, with information on our DX locations.



BRAZIL

Gerson Rissin PY1APS PO Box 12178 Copacabana 20000 Rio de Janeiro, RJ Brazil

CB OPERATION ON 28 MHZ

The Brazilian Department of Communications (DENTEL) has been focusing its efforts to find pirate stations using CB equipment to operate at the beginning of the 10-meter CW band.

The CB band ends at 27.605 MHz, but they use modified equipment to extend their operations as far as 28.1 MHz. In this way, it is very difficult to have a QSO on 10-meter CW, especially during the weekends. We can hear pirates from a few countries in South America as well as from Europe.

All Brazilian CW groups are encouraging their members to use the 10-meter band as much as possible and banish the pirates.

ONE MORE BRAZILIAN BEACON

For propagation purposes, the Brazilian Amateur Radio League/Department of Americana, in the state of Sao Paulo, has constructed a QRP beacon with 10 Watts output on 28.300 MHz. Carlos PY2VRX, Roberto PY2FUZ, and D'Orssay PY2CRI all assisted in establishing the transmitter.

The station is already on the air, with the callsign PY2AMI, and transmits the following message: VVV DE PY2AMI PWR 10W ANT GP LAT 22 45 S LONG 47 16 W AMERICANA SAO PAULO. Any report or QSL may be sent to PY2AMI, Beacon Project, PO Box 31, 13470 Americana, SP, Brazili.

10-MHZ BAND

Brazilian amateurs are not yet allowed

to use the 10-MHz band. Most of them have already bought new equipment using the WARC bands, but the authorities are still studying the treaty.

GPCW AWARD

Sponsored by the Grupo Praiano de CW, the GPCW Award is available to all licensed amateurs for confirmed contacts with three GPCW members.

Contacts must have been made after November 5, 1973, on any amateur band. Only 2-way CW contacts with a minimum RST of 338 are allowed. No QSL is necessary.

Send a list of stations worked (call, date, time, band, mode, and report) and 5 IRCs for malling expenses to GPCW, PO Box 556, 11100 Santos, SP, Brazil.

GPCW members are: PR7CM, PS8AUJ. PT8AVV. PY1AFA, PY1CMS, PY1DG. PYZARX. PY2BBO, PY2BKT, PY2BOP PY2CE, PY2CAR, PY2CJW, PY2CZL PY2DBU, PY2DCP PY2DV PY2DHP PY2ESW. PY2DYX, PY2ETW. PY2EW. PY2EYF. PY2FDO. PY2FHC. PY2FK PY2FNB. PY2FNE, PY2FRW, PY2GCP. PY2HAB. PY2HAF PY2IBH. PY2IEG. PY2IEM, PY2JN, PY2KL, PY2OIL, PY2OIN, PY2ORF. PY2RAD, PY2RAN, PY2RRG. PY2SCR. PY2SFI, PY2SLS. PY2TT. PY2UGR. PY2TUE. PY2US PY2VFA PY27FR PY2ZV. PY3BU. PY3CJI. PY4FTW. PY5CMS. PY6WF. PY7BOS PY8BI, PY9AY, F6HSX, and CT1CFG.



CYPRUS

Arls Kaponides 5B4JE PO Box 1723 Limassol, Cyprus

BEACONS IN CYPRUS

For many years, the Cyprus Amateur Radio Society has been running experimental transmitters as beacons for the study of radio-wave propagation.

At the moment, there are three beacons in operation:

a) 28.220 MHz—This beacon is used for the study of shortwave propagation and transmits the call 5B4CY. This beacon is watched by many amateurs throughout the world who often send reports or OSL cards with Information about the reception of its signal. The power of this beacon is 15 to 20 W and the antenna is a quarterwave vertical on the ground with lots of radials under the soil.

b) 50.5 MHz—A transmitter on this frequency aids the study of many phenomena such as sporadic-E and TEP (Transequatorial Propagation), and during the period of maximum sunspot activity, it was heard in all continents. The transmitter was home-brewed by 5B4AZ and has an output of 15 W and a ground-plane antenna.

c) 70.11 MHz—This beacon is also used for sporadic-E and TEP studies and has been heard in Europe and South Africa. The transmitter was donated to CARS by G4BPY, whom the Cyprus amateurs would like to thank very much for his most useful and generous offer. We do hope that other amateurs will help our society in other fields. Because of its small size, it is running on a shoestring and every little bit of help is greatly appreciated. The 70.11-MHz beacon gives 15 W, and the antenna is a 4-element yagl beaming to Europe between May and August and beaming to South Africa the rest of the time.

All beacons are located at Zyghi at the

site of the BBC relay station, and they all transmit the callsign 5B4CY.

The beacon keeper is Nick 5B4AZ and all reports of 5B4CY should be sent to him.



Jimmy Bruzon ZB2BL 27/2 Flat Bastion Road Gibraltar

On June 18, the 1st Battalion, The Duke of Wellington's Regiment, celebrated the 168th anniversary of the Battle of Waterloo, and to mark the occasion, an open day was held at Lathbury Barracks where the Gibraltar Services Amateur Radio Club set up an amateur-radio station using the callsign ZB2DWR. Unfortunately, due to poor conditions and the fact that the date coincided with some contest, not too many stations were worked. The station was operated by lain Morris ZB2HC and Peter Green ZB2HM. QSL information is either via the Bureau or to PO Box 292, Gibraltar.

Another bit of news was the first-ever two-way QSO on 6 meters between Gibraltar and the United Kingdom. This took place on May 6, when Ken G5KW and I managed to work each other, first on CW and then on SSB. Ken has been doing quite extensive monitoring of the ZBZYHF 6-meter beacon. For those of you who are also operational on 6 meters, the ZBZYHF 6-meter-beacon frequency is 50.035 MHz, running 30 Watts to a 5-element yagl. Reception reports are most welcome and should be maliled to me via the Bureau or, preferably, to my home address.

The oldest licensed amateur still resident on the Rock is Gordon Black ZB2J. Gordon's interest in amateur radio was aroused through ZB2A, the RAF Amateur Radio Club, back in 1948. Of course, home-brewing was the In thing in those days; the RAF Amateur Radio Club station consisted of a couple of T-1131 transmitters, AR-88 and HRO receivers, and other bits and pieces of wartime equipment. Some time later, Gordon and some of his work-mates at the Royal Navy wireless station decided to form the Royal Navy Amateur Radio Club, Through their Commanding Officer, they applied for a club callsign and were issued ZB2G. The RN Amateur Radio Club was active for a number of years on 7, 14, and 28 MHz, and in those days, there was stacks of room to operate in, so receiver selectivity was not necessary. All one had to do was to QSY some kHz up or down the band and find a clear spot to operate on.

In 1950, Gördon decided it was about time he got his own tloket, so after sitting the RAE and CW test, he was Issued call-sign ZB2J. He then constructed his own receiver and transmitter which he used until he got posted to the UK. While in Wales, Gordon was issued the callsign GW3HIJ, and since the rigs were far from portable in those days, it was a matter of home-brewing once again. From Wales, Gordon operated on CW for a couple of years until he got posted, and then came a period of inactivity.

In 1955, Gordon returned to Gibraltar and re-applied for his ZB2 call. He was active mostly on CW until 1964-65 when he joined the Gibraltar Broadcasting Corporation. With work taking up most of his time, ZB2J was inactive until 1979.

The days of home-brewing were now over, and since the idea of playing around



And you can see it—in color—again and again when you own the N2NY Ham MasterTapes.

Ever see a cap discharge in slow motion? You will on Ham MasterTapes. Ham MasterTapes can perform the dozens of complicated demonstrations necessary for a beginner's understanding of Ham Radio Theory.

Finally, a step-by-step course in Ham Radio Theory is available on color videotape. The Larry Horne N2NY Ham-MasterTapes video course is a unique, effective teaching technique expertly produced by New York's leading professionals in studio and field videotape.

☐ Video Graphics highlight important details

☐ Carefully worked-out demonstrations on video avoid the problem of getting complex gadgets to work on command in front of a class.

☐ Working examples of every ham radio component, device, or system covered in the FCC guide can be clearly understood.

The N2NY Ham MasterTapes give you a basic grasp of concepts that build theory background—not only for passing the FCC tests, but for understanding electronics.

The hobby has long needed better, clearer, hightech teaching aids to help newcomers into our wonderful world of Ham Radio.

These six-hour tapes cover completely all the material needed to understand Novice and Tech/General Theory and operations, and include the new 200-question FCC syllabus used beginning September 1983.

Only \$199.95. Order direct and specify Beta or VHS format. Call or write: Larry Horne, N2NY or

Virginia Hamilton, N2EGJ at Ham MasterTapes 295 Park Avenue South New York, N.Y. 10010 212-673-0680.





Gordon ZB2J operating his station. Note the home-built ATU on top of the TS-520.

with a soldering iron and voltmeter at home didn't appeal to him any more (having been Chief Engineer for the Gibrattar Broadcasting Corporation for a number of years), he decided to get a TS-520, which forms part of his present setup. The antennas are a 10-meter dipole a 20- and 15-meter dipole on a single feeder, and a longwire for 40 meters. He eventually Intends to get a beam antenna, possibly some compact triband beam.

Gordon is active just about every morning and most evenings on 20 meters; he prefers operating on 15 or 10 meters when it's open. Being a rag-chewer, he prefers to keep away from those "my-name-is-Gordon-you're-RST-599-please-QSL" style QSOs. Gordon has worked about 180 countries, though he admits he is not a wallpaper collector. His QTH is located on the west side of the Rock; from there he has a very good take-off towards the southwest, west, and north.

Though Gordon does not enjoy contest operating, he does enjoy working DX stations and adding new countries to his collection. At present he is the General Manager of the Gibraitar Broadcoasting Corporation.

Next month we shall be visiting John ZB2AT. John is also the license holder for the 1st/4th Scout Group ZB2FFG.

Currently, the Gibraltar Amateur Radio Society is experiencing some TVI problems. However, as soon as that's sorted out, ZB2BU shall be active on 10, 15, and 20 meters. The GARS meets on Tuesday evenings and if all goes well, I shall be able to provide you with more details next month.

Best 73 es CU next month, or perhaps work you before then.



GREAT BRITAIN

Jeff Maynard G4EJA 10 Churchfields Widnes WA8 9RP Cheshire, England

THE UK SCENE

Those of you awaiting QSL cards for recent contacts with G2MT probably do not appreciate the historical significance of that call.

Some sixty years ago, the callsign 2MT was used to introduce the first scheduled entertainment broadcasting in the United

Kingdom. Recently, the Home Office (the then-regulatory authority for amateur radio in the UK) approved the use of G2MT by the Marconi Radio Society, whose members are drawn from the employees of Marconi Space and Defence Systems Ltd. in North London.

The station will operate from the Stanmore headquarters of the Marconj Radio Soclety, but bands and operating schedules are subject to prevailing propagation conditions.

At the time of this writing, we are well into the summer mobile rally calendar with two or three events each weekend. (Even though the English summer sometime lasts only a week or two, the rallies are held resolutely through October!)

On a slightly smaller scale than, say, the Dayton Hamvention, mobile rallies are

very popular over here and are characterized by big crowds, warm beer, and curly sandwiches.

Local events often are held in school or social halls with only a handful of regular trade stalls; filling the remaining space are weekend traders and tables rented by individuals.

Regional events attract more traders who exhibit their full range of Japanese black boxes. Unfortunately, these invariably remain in their shrink-wrap protective covers and no facilities exist for demonstrations (any operating station is usually being provided by a local club). It never ceases to amaze me that fellow hams will part with vast sums of money (a Yaesu FT-One currently retails here at about \$2200) for equipment chosen in these conditions.

Far better to visit one's local store as a do occasionally. Not only do I get to try any gear in which I am interested, but I also get a cup of coffee and a chat with Peter G4KKN (who runs the local Amateur Radio Exchange).

Despite all this, mobile rallies can be fun—particularly listening to the talk-in channel whilst approaching. I recently heard a ham three times do the opposite of the Instructions given him and then wonder why he remained lost.

A big complaint against mobile railies is that they occupy the OM on a Sunday and provide little if any attraction for the family. In one event, at least, this is not so. The RSGB National Mobile Raily is held at Woburn Abbey, seat of the Marquis of Tavistock. Surrounded by beautiful parkland, the house alone is worth a visit, but the intrepld can always take in the wildlife game reserve.

The RSGB's advertising for this event highlights the many side attractions of Woburn but fails to mention the area's most interesting sideline—Woburn Golf Course, home of the Masters and other tournaments. Perhaps the organizers do not share my loterest in golf.



GREECE

Manos Darkadakis SVIIW Box 3751 Athens, Greece

This month's column will bring you all the necessary information for getting an SV ilcense while in Greece. (See box.) At the moment, reciprocity agreements exist with the US, Canada, and Cyprus. Therefore, only amateurs from these three countries can obtain an SV call during their stay in our country.

Please note that for the first category the minimum requested time for the issue of the license is 3 to 4 weeks, and it is 3 months for the second. Therefore, applicants must apply in-advance of that time.

Lately, many efforts have been directed toward the establishment of a guest license in Greece. This one will be valid for a maximum of three months and will be available to every licensed amateur worldwide. Anyway, we will be back with more details after the agreement.



INDIA

James Kalassery VU2ARL PO Box 1446 36/677 Monastery Road Cochin 682 011, India

Under the 1978 Indian Wireless Telegraph (Amateur Service) Rules which are currently In force, we have four categories of licenses—Advanced, Grade II, Grade II, and Grade II (VHF).

Grade II and Grade I are available to anyone who is at least 14 and 16 years old respectively and has passed the respective Amateur Station Operator's Certificate (ASOC) examination. However, an Advanced ASOC examination can be taken only by those who have held a Grade I license for 2 years or a Grade II IIcense for 3 years. Morse-code requirements are the same (12 wpm) for both Grade I and Advanced licenses, and therefore Grade I amateurs need pass only the theory portion of the Advanced ASOC examination, which is of a slightly higher standard, to qualify for the Advanced license. Those who do not qualify in the Morse-code test (5 wpm) of the regular Grade II ASOC examination can get the Grade II (VHF) license, which will permit them operation on 2-meter phone.

Out of the around 1800 amateurs in India, only about 30 are Advanced Ill-censees; almost the same number hold the Grade II (VHF) license. The rest of the ham community is almost equally divided among Grade I and Grade II.

The largest representative body of radio amateurs in India is the Federation of Amateur Radio Societies of India (FARSI), which has more than 60 affiliate clubs and a total membership well over 1000. Most of these clubs are in cities, but some smaller towns also have very active clubs. The largest affiliate is the Radio and Electronic Society of India (RESI), followed by Madras Amateur Radio Society (MARS)

INSTRUCTIONS FOR FOREIGN AMATEUR-RADIO OPERATORS

(Legislative Decree 1244/72 Official Gazette 181/A/16 Oct 72)

Foreign amateur-radio operators who are citizens of countries having a reciprocal agreement with Greece may operate amateur-radio stations in Greece if they submit an application with the following supporting documents to the: Ministry of Communications, General Directorate of Posts and Telecommunications, Directorate of Radio Communications Control, Section III, 49 Leoforos Syngrou, Athens, Greece.

1) Amateur-radio operators who wish to operate stations in Greece for less than one year must submit:

 a) An application giving full personal identification data, the intended location of the radio station, and the point and manner of entry of the radio equipment into Greece.

b) A photocopy of the amateur-radio license notarized by the appropriate government agency or amateur-radio club of the applicant's home country. If the license has no expiration date, the applicant must provide a certification by the appropriate government agency or amateur-radio club in his home country that the license is still valid.

c) Technical characteristics of the radio station.

The above documents must be submitted to the Ministry before a permit to operate is granted. This will be valid for a period equal to the applicant's intended stay in Greece, not to exceed one year, and will not be renewable.

- 2) Amateur-radio operators residing permanently in Greece must submit:
 - a) An application bearing a 10-Drachma revenue stamp.
 - b) Identification data
 - c) A photocopy of the amateur-radio license notarized by the appropriate government agency or amateur-radio club of the applicant's home country.
 d) Technical characteristics of the station.
 - e) A document showing the applicant's membership in the Greek Amateur Radio Club.
 - f) A 300-Drachma fee.
 - g) A 50-Drachma revenue stamp.

The permit will be valid for two years and will be renewable. Amateur-radio operators in this category are entitled to transmit using the output wattage permitted by their license, but not to exceed 300 Watts PEP.

Grab a fistful of TEN-TEC's new 2 meter FM talkie

LAMO

it has features never before available in one handheld, it's made in the USA and it's priced right!

COMPARE TENNESSEE TECHNOLOGY WITH THE OTHERS...

Do their handhelds have memory lockout?

Exclusive memory lockout on the TEN-TEC 2591 allows scanner to temporarily bypass channels for quick lockout of busy frequencies yet retain them in memory for normal operation on demand.

Do theirs store transmit offset?

The 10 memories of the 2591 allow stored offset for easiest operation. And memory channel 0 accepts any non-standard offset.

Do theirs offer selectable SKIP or HOLD?

When scanning with the 2591, choose HOLD to stop and stay on a busy frequency. Choose SKIP to stop for several seconds and continue.

Do theirs offer modifiable Band Scan without complete reprogramming?

With the 2591 you can scan any section of the band with user defined upper and lower limits in steps of 5, 10, 15, 25, or 30 kHz. Change step size, upper and lower limits independently. Manual Scan also, up or down, n 5 kHz steps.

Do theirs have Quick-Release NI-CAD Battery Pack?

The 2591 battery pack slides off easily, yet is secure in use, has a heavy duty 450 mAH rating at 8.4v, and the 2591 has capacitive memory retention to permit pack changing without reprogramming.

THE TEN-TEC 2591 HAS ALL THE RIGHT FEATURES...

Memory Scanner scans only programmed channels and has user selectable HOLD or SKIP • Selectable 2.5 Watts or 300 Milliwatts power, top panel switched • Extended Frequency Coverage—143.5 to 148.995 MHz. Covers full Amateur Band plus some CAP and MARS frequencies. • 4-Digit LCD Readout with Switchable Back Light —large, easy-to-read digits, selectable for frequency of memory channel number.
 Key-Pad Frequency and Function Control —16 key dual tone encoder

Dual Function LED—shows battery status and transmit mode.
 Electret Microphone plus separate speaker for superior audio.
 Compact, Lightweight, Complete—easy to handle and rugged. Standard equipment includes flexible antenna with BNC connector, AC charger, belt clip, connectors for mike and speaker. Options include: adaptor pack for +12 VDC mobile operation, speaker/mike, 25 watt power amplifier, leather case, desk charger, subaudible tone module, and spare NI-CAD pack.

DESIGNED AND MANUFACTURED IN TENNESSEE and it carries the famous TEN-TEC 1 year warranty. See your dealer for the best in 2 meter FM—the TEN-TEC 2591. Or write for information to TEN-TEC, Inc., Sevierville, TN 37862.



2 METER FM TRANSC

and Kerala Amateur Radio League (KARL). Many clubs conduct regular classes, assisting candidates preparing for the ASOC examinations. Being World Communications Year, more and more clubs are being formed and affiliated with FARSI this year.

One of the main projects of FARSI is the All-India Convention held every three years. The last one was held in Bombay in 1981 and the next one is expected to be held soon. FARSI also publishes a monthly journal, Radio, which is sent free to the members of all affiliate clubs.

With the arrival of many more rigs imported under the Open General License of the Import Policy, more and more Indian amateurs are now being heard on the bands, which means more QSOs and more QSLs. To take care of the flow of these cards, FARSI runs a well-managed QSL Bureau (PO Box 6538, Bombay 400 026), which serves all radio amateurs in India, irrespective of their membership.



ISRAFI

Ron Gang 4Z4MK Kibbutz Urlm Negev Mobile Post Office 85530 Israel

VHF IN ISRAEL

One of the most popular aspects of ham radio in Israel today is VHF operation-more specifically, two-meter FM. Please note: We do not have a code-free VHF class of license here, so those operating on VHF also have full HF privileges. Thus, Israelis chose two meters on its own merits alone.

Although the widespread use of these shorter wavelengths has occurred here only in the last decade, it would be wrong to assume that the world above 30 MHz was unknown until the early '70s. In the tast yearbook of the Israel Amateur Radio Club, we see a couple of snapshots of Bruno 4X4DH taken on a field day in 1965 at Kibbutz Sasa In the mountains of the Upper Galilee. The first one shows him raising a two-meter yagi on the kibbutz's water tower, and the second depicts him crouched over an SCR-522 making the first contact between Sasa and Halfa. A year earlier, in 1964, Bruno had made news by being the first amateur to make satellite contact between Europe and Asia via OSCAR 3. Bruno also had received the signals of pioneer OSCAR 1 transmitting its famous HI beacon.

The real boom in VHF happened in the spring of 1974 when the police department decided to update its communications equipment. The Ministry of Communications, perhaps because of the prompting of a few hams holding key posts there, deemed that the equipment being retired was untit for commercial use. This left only one possible area for the release of the gear-the radio hams!

So, for a small fee you became the proud possessor of a Motorola D43GGV high-band FM transceiver, sporting about thirty tubes, including a 6146 final. If you were fortunate, you had an ac supply built in-otherwise you had to deal with a real humdinger of a 12-volt vibrator.

The other item made available to the ham population was the Japan Radio Corporation hand-held FM transceiver. This was a real beaut—totally solid state, dual channel, although about 21/2 times the volume of today's hand-helds. You may recall that we then called such units "bricks." I don't remember what these cost us, but the Ministry did give a few of these free of charge to club stations.

Well, through the Israel Amateur Radio Club, a bulk order of crystals was made from Tadiran, Israel Electronic Industries, and two meters came to life! People were having a ball, tasting the joys of this new mode of communications. There we all were on 145.725, thinking that this intercom party line was great, not knowing that bigger and better things were just around the corner.

A few of the boys in Beersheva took a Motorola GGV and turned It into a primitive repeater, Israel's first. The next Issue of HaGal (The Wave), the IARC periodical, came out with a band plan, allocating repeater and simplex frequencies for the various cities and districts. This was based on the European scheme with 25-kHz spacing between channels-145.000 to 145.225 being the repeater uplinks for R0 to R9, and 145.250 to 145.575 being simplex channels S10 to S23. Of course, 145.600 to 145.825 are the repeater outputs going from R0 to R9-standard 600-kHz splits. (R8 and R9 have been dropped in the last couple of years to accommodate amateur satellites as per the IARU hand plan.)

Your correspondent, living in the Negev, had been content to chit-chat on the Beersheva frequency with his GGV. occasionally making a DX contact with the Tel Aviv repeater on the other crystal channel when tropo ducting permitted. One day, I visited a nearby ham who had a synthesized rig, and I was astounded to hear the Haifa repeater 250 km north of here coming in full quieting. I was hooked, and by January, 1979, I had purchased a scanning transcelver

This was indeed the time of the real two-meter boom here-people had had a lot of fun with the "junk" rigs and were now buying commercial synthesized gear The repeater and simplex channels were buzzing day and night. By virtue of a few amateurs holding key positions in Motorola Israel, retired repeaters and duplexers were donated to the IARC, and at this time, there are five two-meter machines In operation (R0-Haifa, R1-Jerusalem, R3-the Galilee, R5-Beersheva, and R7-Tel Aviv) and one 70-cm repeater in the center of the country.

Israel, located on the Mediterranean coast and having frequent high-pressure weather systems, is a VHFer's paradise. All summer long (6 months!) there is tropospheric ducting, making long-range contacts commonplace and two-meter OSOs with Cyprus a regular affair, Sometimes sporadic E appears, and on FM I've worked into Greece, Italy, and Yugoslavia and have heard Hungary. Of course, the serious two-meter DXers are on CW and SSB around 144,300, and some have contacted England. But for us run-of-the-mill FMers, this DX is really the icing on the

Two meters has really changed the face of Israeli ham radio almost beyond recognition. Some sneaky fellows have lent their two-meter gear to "retired" oldtimers and have thus rekindled their fire, getting them back on the air. Previously, the only local meeting ground was 40 meters for a few hours on the Sabbath, but now hams in the country are in touch with each other all week long at all hours. For better or for worse, the hams now are acquainted with each other very well, and Israell hamdom has become a kind of village!

The repeaters are now less active than they were a year or two ago. It seems that either the novelty has worn off or the long roundtables have talked themselves out Still, I suspect, just as many people are monitoring-it's simply that they don't reach for the microphone as often.

Every time Shimshon 4X4GF, "Gefilte Fish," meets a new operator on two meters, he enters him into his list and tells him what number station he is that he's worked on the band. The last time I heard, he had just passed the 380 mark, definitely deserving a place on the Honor Roll!

Visiting amateurs are always very welcome on our straight carrier-access repeaters. Should you be coming here, by all means bring along that portable rig. It will add another warm human dimension to your trip to Israel. Reciprocal licensing is no problem, and details may be found in my column in the June, 1983, Issue of 73.



Mario Ambrosi I2MOP Via Stradella, 13 21029 Milano, Italy

RECIPROCITY IN ITALY

In accordance with the Telecommunications Act of March 29, 1973, foreigners are granted permits for short visits and station licenses for longer stays in Italy. A temporary permit is granted for a maximum of three months, and it cannot be extended. However, a foreigner can submit a new application in order to obtain another permit, although consecutive permits will not be granted for more than a 12-month period.

Any foreigner who intends to stay in Italy for more than one year must first register his residence. Then he can request that his amateur license be converted into an Italian operating license, which will then be granted in the same way that Italian nationals receive theirs.

Applications sent from abroad may be written on plain paper, while applications from Italy must be on revenuestamped paper. All must be filled out in Italian and accompanied by a 3000-lira revenue stamp and an additional 2100 lira for postage. IRCs may be substituted at an exchange rate of about 500 lira per coupon. In addition, the license granted in the country of origin must be valid for the entire period of the Italian temporary permit.

A photocopy of the station license must be mailed with the application, and I recommend that you post the envelope as a registered letter. For overseas airmail service, add 3700 lira, and if the application is handled through the reciprocal licensing department of the ARI, only \$8 US is required to cover expenses.

It is advisable to apply for a temporary permit at least 45-50 days prior to the expected date of arrival in Italy

You must also pay a fee of 2000 lira at any post office when you fill out the form attached to the permit. Prior to payment, fill out the front sides, and on the back write "Canone per l'autorizzazione temporanea rilasciata a cittadino stranlero per limpianto e l'esercizio di una stazione di radioamatore in Italia" (Art. N; 331 D.P.R. 156 del 29/3/73).

The postal address of the licensing administration is: Ministero Delle Poste E Delle Telecomunicazioni, Direzione Centrale del Servizi Radioelettrici, Divisione 5 Sezione 3, Viate Europa 160, 00100 Roma. The telephone number is: International

+ 39 6 54601, extension 4975, All correspondence and calls should be in Italian.

The address of the reciprocal licensing department of the ARI is: ARI-R.L.D., Via Giorgione 16, att. Manuel F. Calero 14CMF, 40133 Bologna. The telephone number is: International + 39 51 389502. Phone calls are answered in English, French, or Spanish after 8 am GMT, except weekends

Here are instructions on how to fill out the application form:

1) When you fill out the form, please remember that mobile operation is allowed only on VHF and UHF.

2) Indicate the manufacturer and model number of your equipment. The input must not exceed 300 W.

3) It is very convenient to apply to the reciprocal licensing department of the ARI, since they will take care of many of the administrative details.

4) If you do any travel in Europe, it is worthwhile to purchase The International VHF-FM Guide, by J. Baldwin G3UHK, 41 Castle Drive, Maidenhead, Berks SL6 6DB, Great Britain. The book contains lots of useful information regarding VHF and UHF repeaters all over Europe, It also provides the addresses of various postal administration offices in Europe and procedures for obtaining temporary licenses. The cost of the book is \$3 US, plus postage, and the editor's phone number is: International + 44 628 37837.



Brother "Don" Donard, Steffes, C.S.C. EL2AL/WB8HFY Brothers of the Holy Cross St. Patrick High School PO Box 1005 Monrovla, Republic of Liberia

Liberia amateur radio, when the truth is out, is primarily expatriate amateur radio. Missionaries, doctors, teachers, and even business people like to have an amateurradio license so that they can talk to their friends and relatives back home. When they travel, they like to pass on information regarding airplane schedules, arrival times, and things like that.

There are many of these people in Liberia. To say that they number in the hundreds is conservative. Not all of them have radios, but as it works out, there are more expatriates operating amateur radios than there are natives. This is not a desirable situation, and we in the Liberia Radio Amateur Association are trying to do something about it.

The point of this article is to discuss amateur radio in Liberia in its relation to medicine. There are a few major cities in Liberla that have hospitals, doctors, and other medical facilities. People who can reach these places can be cared for, but the greater part of the population lives in villages where there may be no communication, difficult transportation, and no doctors or medical facilities. Some of these villages are served by medical missionaries who operate mobile clinics, and some of them are not served at all.

One day, I was turning the dial on my radio when I heard a call come in from one of these outlying areas. The amateur up there was in communication with a doctor, an amateur, here in Monrovia. He was describing severe leg infection which could involve the loss of the limb. The doc-



American made RF Amplifiers and Watt/SWR Meters of exceptional value and performance.

•5 year warranty • prompt U.S. service and assistance

RF AMPLIFIERS

2 METERS-ALL MODE

\$89.95 **B23** 2W in = 30W out (useable in: 100 mW-5W)

B108 10W in = 80W out \$179.95 (1W = 15W, 2W = 30W) RX preamp

B1016 10W in = 160W out \$279.95

(1W=35W, 2W=90W) RX preamp **B3016** 30W in = 160W out \$239.95

(useable in: 15-45W) RX preamp (10W - 100W)

220 MHz ALL MODE

\$199.95 C106 10W in = 60W out (1W=15W, 2W=30W) RX preamp

C1012 10W in = 120W out \$289.95 (2W=45W, 5W=90W) RX preamp

C22 2W in = 20W out \$89.95 (useable in: 200mW-5W)

RC-1 AMPLIFIER

REMOTE CONTROL \$24.95

Duplicates all switches, 18' cable

WATT/SWR METERS

- · peak or average reading
- direct SWR reading MP-1 (HF) 1.8-30 MHz

MP-2 (VHF) 50-200 MHz \$119.95

430-450 MHz ALL MODE

D24 2W in = 40W out \$199.95 (1W = 25W)

D1010 10W in = 100W out (1W = 25W, 2W = 50W) \$319.95

Available at local dealers throughout the world.



P.O. Box 1393, Gilroy, CA 95020 (408) 847-1857

tor stated simply that the patient would have to go to a hospital. The answer came back-there isn't any. The next suggestion-he must see a doctor; again the answer-it is out of the question, the nearest doctor is forty miles away and there is no way of getting there.

Running out of alternatives, the doctor here in Monrovia began to ask detailed questions about the situation and to prescribe over the air. A schedule was set for 24 hours later at which time a decision had to be made as to whether or not the infected area would be lanced.

Medical consultation on amateur radio is common here. Many times there are emergencies where this medium is the only communication available. Some weeks ago. I received a frantic call from an amateur in the vicinity of one of the leper colonies. They were out of a medicine which the lepers must have on a regular basis to hold the disease in check. I drove downtown to bring the message to the leprosy control center.

We, the amateurs, lack numbers. We have other commitments; radio is a hobby. So, it is difficult, but we are trying to set up a network of communications (the Liberian Net) which will operate on a reqular, dally basis. As we expand our numbers and equipment, we may make this a reality.



MEXICO

Mark K Toutilan XE1MKT Apartado Postal 42-048 06470-Mexico, D.F.

Since Mexico borders with the United States and has a lot of tourist attractions in all of its 32 states, many questions have come up in the minds of our fellow hams from outside the country with regards to regulations here, happenings, and anything to do with radio-wave activity from down "south of the border." I hope to answer some of these questions one by one as a correspondent for 73. Some have asked about what awards are offered here. Let's take a peek at one of these awards this month.

THE MEXICO CERTIFICATE

Well, one of the unique awards that the Mexican Radio Experimenters League offers to hams around the world is the Mexico Certificate or diploma, with the following requirements

1) Confirm at least 50 Mexican stations; anything from January 1, 1957, on is accepted.

2) Confirm 15 different states within Mexico, including what we call "D.F" (Mexico City) (See box)

3) Stations confirmed should be legally authorized by the Secretary of Communications and Transports (SCT).

4) Combining CW and phone is not accepted, although either of the two is OK as are SSTV and RTTY

5) Your registered correspondence should be sent to La Liga Mexicana de Radio Experimentadores, A.C., PO Box 907, 06000 Mexico, D.F.

6) The Mexican ham operators who apply for this award have to confirm bilateral contacts with at least 20 different states besides Mexico City.

7) You should include with your application the confirmed QSL cards, the corresponding list, and \$3.00 US for postage and handling. Don't forget, CW, AM, SSB, RTTY, and SSTV are accepted.

There are quite a few other awards that are available through our Radio Experimenters League here in Mexico and from different radio clubs; I will deal with them In future columns

Personal satisfaction can be derived through obtaining one of these awards, since time and experience as a radio operator is obviously a factor. Part of the etiquette of the Mexican ham operator is the importance for one to be balanced, not letting the radio control your daily activities: rather you should control the rig so that It doesn't push aside the more important things in life. I, personally, live by that standard. That's the good thing about obtaining awards now and then. You're not pressed for time in order to obtain them You can take your sweet time (days, weeks, or even years) and eventually begin framing those lovely certificates. And, of course, your ability to work "over the air" and set up your antennas and equipment in emergency situations should improve as time goes on.

So, try for the Mexico Award! Get started soon! And for those of you who already have some QSLs saved up from Mexico, work on the states you lack still, and happy DXing!



THE NETHERI ANDS

Henk Meerman PD0DDV Zandvoorterweg 33 2111 GR Aerdenhout The Netherlands

A TEMPORARY LICENSE IN HOLLAND

When you're planning a visit to the Netherlands and would like to talk to the Dutch amateurs, you'll need a license for it. I will give you all some tips:

The application for a temporary amateur-radio license must be sent to Holland at least six weeks in advance of the date that you desire the license to be used. For the application form that you'll have to fill in and a copy of the Dutch amateur-radio license conditions, send your request to: Radio Control Services, PO Box 570, 9700 AN Groningen, The Netherlands.

Remember, too, that the Dutch Radio Control Services will not deal with any IIcense requests before you have paid the annual charge of D. fls. 65-- (about \$20.00) in advance. Unfortunately, you have to pay for a whole year even if you only stay for a week or so. Furthermore, your payment can only be made by International Money Order addressed to: P.T.T. Centrale Dienst, Kortenaerkade 12, 2518 AX The Hague, The Netherlands.

Note that your callsign must be stated on your money order.

Together with your application form, you have to send a verified photostat copy of your license and a copy of your money order. The copy of your license must be verified by your postal service or the authorities that deal with licenses in your country. There must be a clear indication. on your license that it is still valid

To be granted an amateur-radio license in The Netherlands, you have to be at the age of sixteen or over.

The license conditions, as you know, vary from country to country. For Holland, they are gathered in a small 39-page booklet in the English language that you'll receive together with your application form. When you open this booklet, you'll find out that 50 and 220 MHz are not amateur frequencles in Holland, Licenses for those bands are very rarely given.

Other things that are not allowed in Holland are:

- a) The use of transmitters in aircraft.
- b) The transmission of messages from third parties.
- c) The transmission of messages of a commercial nature.

It is interesting to know that most of the Dutch amateurs on 2 meters use horizontally-polarized antennas at their QTHs. while most of the mobile stations and repeaters use verticals.

When you arrive at Schiphol Airport (Amsterdam), give a shout on the nearest repeater there: PI3HLM on 145.775 MHz. Almost all Dutch amateurs speak English In some way and they will be glad to hear you and will answer any question you'll ask them. If you have a bit of luck, you will find a YL or an OM who will show you around the beautiful city of Amsterdamthe museums, buildings, etc. If you are in for a romantic trip, take a boat trip through the canals of Amsterdam at night!

So, if you are planning a trip to Amsterdam, there are reasons enough to bring your HT along. Don't forget fresh batteries (Hi).



NEW ZEALAND

D. J. (Des) Chapman ZL2VR 459 Kennedy Road Napier, New Zealand

Kia Ora atu i Aotearoa! (Hello from New Zealand.) This month I will continue with the special groups within the New Zealand Association of Radio Transmitters: I shall cover the OTC, the Old-Timer's Club. New Zealand's equivalent of the QCWA in the USA

The formation of the Old-Timer's Club was approved at the 1952 Annual Conference of NZART at Dunedin. During the ensuing year, the old-timers throughout the country worked towards the inaugural meeting of the group to be held during the 1953 Annual Conference of the Association at Palmerston North.

Quintana Roo

Sinaloa

Sonora

San Luis Potosi

The first meeting was duly held at 1940. NZTime on May 31, 1953, in a convenient room, after the conference sessions were finished. Sixteen eligible "old hams" attended and had discussions on the proposed objectives of the club and the conditions of eligibility for joining the club. The following was decided and remains applicable today, 30 years later.

Membership is available to any ZL amateur who has held an amateur license for the last 25 years or more and is still an active amateur.

The objectives of the Old-Timer's Club (ZL) as set out in its constitution adopted in 1954 are as follows:

- (i) To recognize service to amateur radio.
- (ii) To revive and maintain interests and good fellowship among the older members in the common cause.

(III) To offer aid to the "young-timers."

Within the first three months, the numbers of the OTC had grown to 55, and they all were Issued with Certificates of Membership on September 30, 1953, and all deemed to be foundation members of the club. The certificates were donated by two old listener members, Monty and Old Fred, and were designed by one of the members.

The OTC has continued to flourish. Today it has over 500 members, 150 who have received their 50-year certificates and one his 60-year certificate. The club meets regularly "on the air" in OTC Nets on 80 and 40 meters on Sunday mornings. Eveball QSOs also are maintained in the main cities, where old-timers get together during the afternoon for meetings or on the weekends during the summer for picnic outlings. The Old-Timer's Club has its Annual Meeting and Reunion during the NZART Annual Conference each year, when they elect their president, the Grand Old Man, who holds office for one year.

There is no set subscription or entry fee for membership, but any small donations made with applications for membership do assist with the club's expenses for postage and stationery. Also, there is usually a collection made at the club's annual meeting each year to supplement the finances.

The OTC also has a regular column in the Association's magazine. Break-In. and offers an award, the Old-Timer's Cup. to the elected Grand Old Man each year. A certificate in keeping with this grand office is presented to the holder of the cup as a permanent reminder of his year in office. The Montgomery Cup, another OTC award, is presented to the member or members who have contributed the most worthy item or article to Break-in each

Recently, the OTC published a Directory of Members containing the names of all members at the date of publication, along with other relevant information such as present call, radio name, original call, other calls held, year first licensed, QTH, and QTC number. The Directory is available to Interested overseas amateurs by writing to the Secretary, OTC-G. E. Brown ZL2BD, 35 Chamberlain Street, Nelson, New Zealand, enclosing US\$3.00 or 12 IRCs, which includes return postage.

BITS 'N' PIECES

OTC Dlamond Jubilee operators, Dan Wilkinson ZL2AB and Len Spackman ZL1AC, are joined by another two oldtimers who also celebrate 60 years of ham radio this year. They are George Blake ZL3FX and Bob Robinson ZL4AC. Congratulations, George and Bob, on joining that elite corps of 60-year operators! Also two honorary OTC members have achieved

STATES IN THE MEXICAN REPUBLIC

D.F. (Mexico City) Aquascalientes Baja California (Northern) Baja California (Southern) Campeche Coahuila Colima Chiapas Chihuahua Durango

Guanajuato

Guerrero Hidalgo Jalisco Mexico Michoacan Morelos Nayarit Nuevo Leon Oaxaca Puebla Queretaro

Tabasco Tamaulipas Tlaxcala Veracruz Yucatan Zacatecas

AMT-1 The Definitive AMTOR Terminal Unit



\$49995 Introductory Price

AMTCR is the system of error correcting RTTY which has been rapidly overtaking conventiona RTTY in Europe, just as its marine equivalent, SITOR, has been taking over in ship to shore communications.

It was originated by Peter Martinez G3PLX (see June 1981 QST, p. 25) He first interpreted the international marine CCIR 476-1 specification for amateur use. Virtually all of the 400+ stations presently on AMTOR world wide are using software/hardware designs originated by Peter. The AMT-1 is a proven product which represents his latest and most highly refined cesign. It represents the culmination of over three years of development and on the air testing, and sets the standard against which all future AMTOR implementations will be judged.

Not only does it incorporate the latest AMTOR specification, but it gives super ative performance on normal RTTY, ASCII and CW (transmit only). As well as some fairly incredible real time microprocessor software, the AMT-1 boasts a four pole active receive filter, a discriminator type demodulator, a crystal controlled transmit tone generator, and a 16 LED frequency analyzer type tuning indicator, which is very easy to use.

Driven from a 12 volt supply, the AMT-1 connects to the speaker, microphone and PTT ines of an HF transceiver and to the RS-232 serial interface of a personal computer or ASCII terminal All mode control is via ESCAPE and CONTROL codes from the keyboard (or computer program).

It used to be that C.W. was the ultimate mode for "getting through" when QRM and fading were at their worst. That's no longer true — AMTOR will get through with perfect error-free copy when all other conventional transmission modes become useless.

ADVANCED ELECTRONICS APPLICATIONS

P.O. Box C-2160; Lynnwood, WA 98036 (206) 775-7373 TELEX: 152571 AEA INTL **AEA** Brings you the Breakthrough!

A Two-Tone Squelch to Solve Your Scanner Woes

Selective listening is the key to success. This squelch will help you cut the chatter.

f you're like me and listen to a scanning monitor much of the time that you're at home, then you probably have the same problem I've had: The monitor either drowns out the wife and kids or the family retaliates, turning up the TV and winning the battle of Television vs. Scanner.

Go ahead—try to explain to your wife how important

it is for you to hear the location of that fire or ambulance call if you're a volunteer fireman or paramedic. Or tell her that you're waiting for a call on the local amateur repeater. You'll probably agree with me that you need more than an explanation. I figured I needed a quick and dirty sequential tone squelch to silence the "10-21 or furnish a number" and "QTH is Pine Grove and

the rig is an Icom 2-AT" that filled the scanner's speaker.

I'm not an engineer and I wasn't about to re-invent the wheel or the tone squelch. Instead, I searched through back issues of QST, Ham Radio, and 73 looking for an easy-to-build two-tone sequential squelch. The closest circuit I could find appeared in the October, 1974, issue of 73 written by Earl Dunn W5LCT. His squelch

used 567 decoders to detect four sequential tones. I wanted to build a squelch for the two tones of my local fire department. So, out came the protoboard and my well-stocked junk box.

Redesigning the Squelch

Since I was interested in decoding only two tones, I set out to simplify W5LCT's circuit. I used Ramsey Electronics TD-1 tone-decoder kits for each tone. Their PC boards are easy to assemble, reliable, and cheap. Check the ads in the back of any 73-1 believe Ramsey has advertised in every 73 since they opened their doors for business. (Kind of reminds me of the antenna company "In QST since '53 without missing an issue." OK, oldtimer—name that company.) Back to decoder kits

The Ramsey TD-1 kit sells for \$5.95 and comes complete with an on-board 5-volt zener. Since I needed 5 volts for the control logic and the TD-1 decoders, I built a regulated supply using a 7805 and eliminated the zener diode and series resistor, D1 and R3, that came with the Ramsey kits. The TD-1 boards are mount-


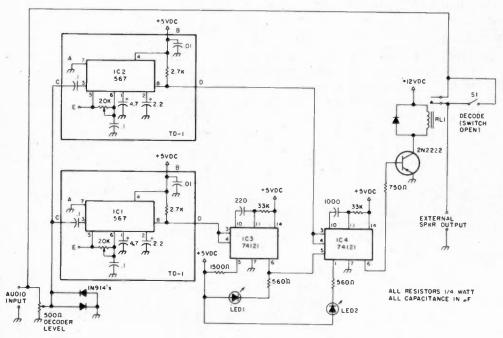


Fig. 1. Schematic.

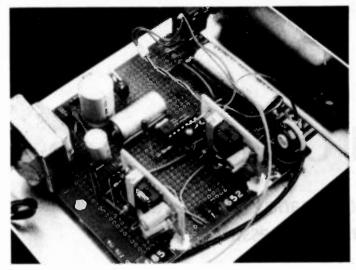

Inside view of the tone squelch. The TD-1 decoder kits are mounted vertically.

ed vertically on the main ters A through E marked on the schematic refer to points on the Ramsey TD-1 decoder boards. Relay RL1 came from my junk box. It's marked 360 Ohms at 12 volts and is a good starting point for substitution. I built a simple power supply using a 12-volt clock-kit transformer. A 1-Amp bridge rectifier followed by a 7805 regulator provides the 12 volts and 5 volts shown on the Logic and LEDS schematic. Both sides of the ac line are protected with an

> The decoders are adjusted with the tone squelch's input disconnected from the scanner. A frequency counter is attached to point E on the decoder board. The 20k pot is adjusted until the counter reads the frequency you want to decode. Remember. IC1 must be set for the first tone and IC2 set for the second tone in the 2-tone sequence.

Elmenco fused plug.

To operate the squelch, I plugged the audio input of the tone squelch into the external output of my scanner through a mating plug. An 8-Ohm speaker was connected to the output of the tone decoder. I used the idle tone from a local 152-MHz mobile-telephone channel to set the decoder levels. With the tone present, I set the decoder level pot for about 100 millivolts mea-



Overall view of the completed tone squelch. The squelch fits easily on top of the scanner.

board. The photo of my tone squelch shows the TD-1 boards next to the labels marking the decoder frequencies. The control logic, relay, and power supply are on the board behind the decoders. I used the copper pads on the board (Radio Shack 276-156) to wire the control and power-supply circuits.

For my squelch to open, a 585-Hz tone must first be received, followed by a 652-Hz tone. Looking at the schematic, IC1 is tuned to 585 Hz. When that tone is received, the output of the decoder goes low. IC3 starts timing a six-second window and LED1 goes off. During this six-second period, a 652-Hz tone must be received and decoded by IC2. LED2 lights when the secand tone is decoded, LED2 stays lit for about 25 seconds. During this time (set by the 1000-uF cap between pins 10 and 11 of IC4), the 2N2222 is turned on and relay RL1 pulls in, connecting an external speaker to the output of my scanner.

Building and Operating the Squelch

Building the tone squelch isn't all that difficult and layout isn't critical. The let-

sured with an ac voltmeter at point C on the decoder boards.

Keep the decoder audio input as low as possible to narrow the bandwidth of the decoders. Also, with sequential tones as closely spaced as those in my squelch, the center frequency of each decoder can be slightly offset in opposite directions if decoder-falsing is a problem. In all cases use the minimum amount of audio at point C that permits reliable decoder operation.

After the decoders are set

to frequency and the input level is adjusted, place switch \$1 in the open or decode position. Audio from your scanner will be heard only after the correct tones are decoded in the right seguence. The 25 seconds of audio from your scanner can be adjusted by changing the value of the 1000-uF capacitor between pins 10 and 11 of IC4.

With the help of this squelch you, too, might end the battle with your televiand hear those toneencoded calls.

Parts List

2 Tone decoders, Ramsey Electronics, TD-1	\$11.90
3 Diodes, 1N914 (276-1122)	.33
1 Transistor, 2N2222 (276-2009)	.79
2 LEDs (276-026)	.79
1 Potentiometer, 500 Ohms (271-226)	.59
2 Resistors, 560 Ohms	.19
1 Resistor, 750 Ohms	.10
1 Resistor, 1500 Ohms	.10
2 Resistors, 33k	.19
1 Capacitor, 220 uF (272-956)	.79
1 Capacitor, 1000 uF (272-958)	.79
1 Relay, RL1 (273-213)	4.49
	\$21.05

Optional Power Supply

1 Transformer, 12 volts, 1.2 Amps (273-1505)	\$3.99
1 Diode bridge, 1.4 Amps at 50 piv (276-115)	1.09
1 Voltage regulator, 7805 (276-1770)	1.59
1 Capacitor, 1000 uF, 35 WV dc (272-1019)	1.59
2 Capacitors, .22 uF, 50 WV dc (272-1070)	1.78
	\$10.04

All numbers are from the 1982 Radio Shack Catalog No. 354.

Electronic Mail Comes of Age

These mailboxes may be thousands of miles away, but they're instantly accessible.

as your mailbox had a little dust in the bottom of it recently? Have your friends forgotten how to write? Are you tired of all of the junk mail you've been receiving? Well, maybe it's just because you haven't been checking the right mailbox!

This article is designed to acquaint you with the new Message Storage Operation, more affectionately known as the MSO or Electronic Mailbox, and to give you some hints on proper ways to exploit the systems. where to find them, and a bit about on-frequency ethics: I hope to present the most important facts about the MSO, but since it is a wideranging subject. I'm sure that I will miss something and take this opportunity to invite you not only to experiment with the various MSOs to answer your questions. but also to correspond with me at the above address should you feel it necessary.

The Message Storage Operation is an adjunct to the ever-popular Hal DS-3100 Automatic Send-Receive Terminal, manufactured by the Hal Communications Corporation, Urbana, Illinois. For those of you who presently own a DS-3100 without the MSO, it can be added to your unit with a minimum of trouble and expense. The MSO is a completely solid-state device which adds mass stor-

age to the DS-3100 and which can be accessed either locally or by remote users. It has a 32,768-byte capacity (approximately 450 lines of message storage or retrieval), which has shown to be more than adequate storage.

Control of the MSO can be accomplished by the local or remote user simply by typing a series of commands recognizable by the MSO. Files (messages) can be written to, read from, or deleted from the system by use of these commands, and a "Help" command is provided to assist in using the system. At this point, I would like to mention that the system is fully automatic, written with "fail-safe" features in mind, and cannot be harmed in any way by either the local or remote user. Evervone is a novice when he first uses any sophisticated system; the MSO is not only forgiving, but also will tell you quickly if you make any mistakes.

First and foremost concerning the use of the MSOs is a basic understanding of our frequency usage. No frequency is reserved, set aside, allocated, or otherwise designated for only MSO usage! It is important to observe some very basic rules and precautions before you activate one of the MSOs in order to prevent QRM to other users of the frequency, whether they be

other MSO users or an already-established OSO on or near the frequency. Just as with any other frequency or mode you use. please listen on the frequency before you activate one of the systems. Propagation conditions vary from hour to hour, and it is important to listen for a few minutes on the frequency to keep from stepping on someone else who may be in QSO or using one of the MSOs. Your cooperation in this one area alone will do more for smooth operation of the MSOs than all of the other areas combined!

Just where do you find these mysterious electronic MSOs? Both 20 and 40 meters have well-established MSO operations. The frequencies of 14,085,625 Hertz and 7,096,375 Hertz are popular with many stations, and other smaller operations are appearing daily. I'm told that there is at least one MSO operating on 80 meters (in the western part of the United States), although I'm unaware of its frequency. Those who maintain MSO systems on the various bands almost without exception use some form of crystal control for their transmitters/receivers. Consequently, you can count on these MSOs appearing at the same spot on your dial in day-to-day operations.

This brings up our next

most important subject relative to good frequency usage. It is very important that the tones emanating from your equipment match as closely as possible the tones output from the MSO. In this regard, tradition states that it is the mark frequency with which we measure RTTY frequencies. For instance, in order to successfully activate and use the MSO systems maintained on 20 meters, your mark tone (which is 2125 Hertz lower than your operating or carrier frequency) must land on 14,085,625 Hertz. Your digital readout may read 14,087.7 or some other reading, but it is the mark tone frequency that is important to match with the MSO. Off-frequency operation causes many difficulties, some of which are: unsuccessful activation and de-activation of the MSO, QRM from "fishing expeditions" trying to find the frequency, unsuccessful .WRITE, READ, and .DE-LETE commands, and a general lack of smooth operation of the MSO. Modern demodulators have sharp front-end filters and, as such, require a very close match to successfully demodulate RTTY signals!

Now that we are sure that the frequency is clear and that we have our transmitting/receiving equipment on the correct frequency, let's talk a bit about some "golden rules" for MSO usage: 1) Anonymity is great, but the FCC requires that you properly identify your station! So, please properly identify your station when you are utilizing the MSOs.

2) Always start your transmissions to the MSOs with a short "mark hold" of 2 to 3 seconds, followed by at least one carriage return/line feed (CR/LF). This stabilizes both your equipment and that of the MSO.

3) Each command to the MSO must be preceded by a period, (.WRITE, .READ, .DELETE, etc.) and the command must be "left justified" (positioned on the extreme left margin). Commands sent to the MSO from other than the left margin or without the period are ignored. The only exceptions to this are the Access Code and the four Ns (NNNN), which may be sent from any position in the print line.

4) Limit your messages to that information necessary

to get the message across. In all cases, limit your message to less than ten minutes in length, in order to comply with FCC identification requirements.

5) Please utilize the .DE-LETE command to remove messages directed to you from the MSO after you have .READ them.

6) Please use the .SDIR (short-form directory) in lieu of the .DIR (long-form directory) unless you need the information in the long-form directory.

7) Be sure to use the EXIT command to deactivate the MSO when you are through. Failure to shut down one MSO means that it may respond to commands directed to another MSO on the frequency. This does cause a bit of confusion!

As stated earlier, the MSO system does contain a HELP command to refresh your memory on the various commands available and a


FILEHELP command to help in constructing files and passwords. Please note that there is a mandatory space character between the .WRITE command and the file name and mandatory carriage return/line feed immediately after the file name. (A carriage return/line feed after each command to the MSO is highly recommended!)


The file name can be any combination of letters and numbers that the receiving station will recognize. Typically, the file name is something like this: .WRITE KØVKH DE K4KOZ (CR/LF). This immediately tells KOVKH that he has a message waiting for him in the MSO and that it is from K4KOZ. The MSO will not accept duplicate file names, so if it is necessary to .WRITE a second message to the same station (while the first one is still on file in the MSO), then make the second file name distinctive by adding a number or letter, e.g., WRITE KØVKH2 DE K4KOZ (CR/LF).

Since file names are very distinctive, it is additionally important to send the exact information to the MSO when using the .READ or DELETE commands, even if it is misspelled in the directory. Without the correct file name, the system will return the "file not found" statement

In conclusion, the MSOs are providing a very satisfactory service on RTTY, CW, and ASCII, both on the HF and the VHF bands. MSO owners derive a lot of personal pleasure in providing these mailbox services and, speaking for myself, I encourage all those who have need for this service to use my MSO at their leisure. I maintain it on 14,085,625 Hertz during the daylight hours and my access code is MSOVKH (no spaces between letters). Hope to see you on RTTY soon!

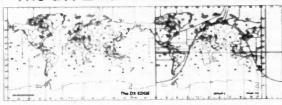The DX EDGE: The Hottest DX Aid Since Sunspots



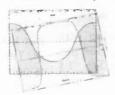

Improve Your DX Achievements on All Bands

See times of sunrise & sunset propagation peaks instantly for any QTH in the world. Know when to look for the DX you need;

Long path and Gray Line possibilities seen at a glance. Plastic slide rule format - Easy to use - Large size

Price: \$14.95 ppd. in U.S., Canada, Mexico. \$18.95 elsewhere, by air. Please make check or M.O. in U.S. funds payable to the DX Edge and mail to:

The DX EDGE, P.O. Box 834, Madison Square Stn., New York, N.Y. 10159

aption fiver is available free of charge.

A product of Xantek, Inc. 1983

PRETUNED - COMPLETELY ASSEMBLED - ONLY ONE NEAT SMALL ANTENNA FOR UP TO 7 BANDS! EXCELLENT FOR CONGESTED HOUSING AREAS - APARTMENTS LIGHT - STRONG - ALMOST INVISIBLE!



COMPLETE AS SHOWN with 90 ft. RG58U-52 ohm feedline, and PL259 connector, insulators, 30 ft. 300 lb. test dacron end supports, center connector with built in lightning arrester and static discharge-molded, sealed, weatherproof, resonant traps 1"X6"- you just switch to band desired for excellent worldwide operation - transmitting and receiving! Low SWR over all bands - Tuners usually NOT NEEDEDI Can be used as inverted V's - slopers - in attics, on building tops or narrow lots. The ONLY ANTENNA YOU WILL EVER NEED FOR ALL DESIRED BANDS - WITH ANY TRANSCEIVER - NEW - EXCLUSIVE! NO BALUNS NEEDEDI

80-40-20-15-10-6 meter -- 2 trap --- 104 ft. with 90 ft. RG58U - connector - Model 998UC. \$99.95 40-20-15-10 meter -- 2 trap --- 54 ft. with 90 ft. RG58U - connector - Model 1001BUC. \$99.95 20-15-10 meter --- 2 trap --- 54 ft. with 90 ft. RG58U - connector - Model 1001BUC. \$97.95 SEND FULL PRICE FOR POSTPAID INSURED. DEL. IN USA. (Canada is \$5.00 extra for postage - clerical-customs etc.) or order using VISA - MASTER CARD - AMER. EXPRESS. Give number and ex. date. Ph.1-308-236-5333 9AM - 6PM week days. We ship in 2-3 days. ALL PRICES MAY INCREASE. SAVE - ORDER NOW! All amennas guaranteed for 1 year. 10 day money back trial if returned in new condition!

Made in USA. FREE INFO. AVAILABLE ONLY FROM WESTERN ELECTRONICS

Dept. A7- 11 Kearney, Nebraska, 68847 >80

9000000000000 APPLIED INVENTION THE SOURCE FOR BOLD STATE / STATE-OF-THE-ART GaAs FETS by MITSUBISHI — Ku Band, Very low noise and medium power. 1-4 MGF 1100 Dual Gate GaAs FET 2.5dBNF @ 4GHz \$ 7.35

MGF 1202 (1402 chip in a 1200 package) 9.70 MGF1402 CHRAMTEED 0.6558BNF @ 46Hz \$56.65 MGF1402 - 0.4 dBNF @ 432, 1.1 dBNF @ 4GHz \$14.00 MGF1412 GUARANTEED 0.8, 0.9 or 1.0 dBNF @ 4GHz \$21. - \$34.75 MGF1801 10GHz finear PO 150mW MITSUBISHI X BAND Hybrid Integrated Circuits with funeable

\$39.37

\$36,22

\$43.05

\$49.00

Directing Resonator (0.12MHz/"C) GaAs FET Oscillators F0-1010X -10.4 GHz, 15mw out, UER100 Flange F0-1210Y -11.5 or 12.0 GHz, UER120 Flange FD-UP11KF - Complete Heterodyne Rx, 10.468 GHz L0 Can be used for 12.5 GHz terrestrial and DBS
* FO-DP13KF Doppier Module 10.525 GHz UER100 Flange * X Band 15 dBG die cast horn antenna (UER100)
* GaAs FET Preamp 1,7-2.1 GHz. 2.0-2.35 GHz. 2dBNI

At: THE SOURCE for RETICON Universal Audio Active Filter's NEW R5620 digitally programmed switched capacitor audio filter R5621 dual section resistor programmed SCF \$ 6.51 R5622 quad section resistor programmed SCI Out performs National MF-10! Application notes \$ 2.00

OPTOELECTRONICS from MITSUBISHI and SIEMENS CALL CW LASER DIODES, HIGH DUTPUT IRLEDS, PIN PHOTO DIODES. MITSUBISHI BIPOLAR POWER TRANSISTORS FOR 900/1296 CALL 2SC2931, 2, 3, 4 (1.4 to 30 Watts P0)

MRF 901 Substitute 2SC2876, Ft=7GHz, 2.2dBNF @ 1GHz

NEC 64535 direct replacement: Siemens BF0 74
LEAOLESS DISK CAPS 100, 220, 470, 680, pF \$ 9.66 10/\$ 2.50 MICROWAYE CHIP CAPS - Very low loss VITRAMON P7800.series G02(0.7-1.4 GHz) G04(1.3-2.6 GHz) G01(2.6-4.2GHz) \$ 1.25 VITRAMON VHF/UHF NPO chips: 10, 100, 1000 pf
A-8 type FWSH 1000pF discoidal Feedthru 5/ \$ 2.50 \$ 0.75

STRIPLINE SHUTTLE TRIMMERS (VOLTRONICS) 0.1-2.5, 0.5-9.0pF \$ 3.34 SAPPHIRE TRIMMERS For WA2GFP preamp Thermo Electric Heat Pumps & Sub-Miniature Cryogenic Refrigerators CALL 3M GX250 glass/tie board, Er = 2.55 @ 10GHz 0.031 0.062

F F JOHNSON SMA'R: Sq flange female \$3.50. Male cable \$ 2.88 PROMPT SERVICE SENO FOR CATALOG MINIMUM ORDER \$5.00 VISA/MASTERCARD Accepted. CASH prepay take 5% discount. S&H * ITEMS (UPS) \$3.75 - ALL OTHER ITEMS \$2.50 (1st CLASS)

NY STATE RESIDENTS ADD 7% SALES TAX ROUTE 21 HILLSDALE, NY 12529 518-325-3911 -71

0000000000

Octal Ingenuity

It's an old radio. You can't find a replacement tube. Now what do you do?

ne day my mother-inlaw handed me an old Philco "antique radio" and said, "Franklin, you're a ham. How about fixing my radio?" I took one look at that old ac/dc battery thing and was about to say I was too busy, but then those words, "you're a ham," shook me up. If I didn't fix it, ham radio would be defamed and I would be one degraded Extra-class amateur. If I did fix it, both ham radio and I would still be

highly esteemed, at least in her mind.

"Sure, I'll give it a try," I said. And the fun began.

Now this old thing was typical for its day. (See the block diagram in Fig. 1.) There were no doubt millions of these sets built, and this particular one looked well-built, mechanically. Electrically, too, it must have been pretty good to survive this long.

After plugging it in and

getting not a peep out of it, I decided to use the usual plan of attack for these jobs. Check the tubes first.

This had to be done without the help of a tube tester. Time to think. If the set is completely dead, a tube fault causing this would probably be catastrophic. Most common in this category is an open filament; then come short circuits and open elements.

It's a good thing I kept that old beat-up RCA tube manual. A check for which pins to test with the ohmmeter didn't take long, and neither did finding the problem. The 3Q5 audio power amplifier filament was open. What luck! I'll just walk right down to my nearby radio store and get a new one.

What, no 3Q5?! And still no 3Q5 three days later, with a telephone bill to raise my wife's ire. Say, this thing is an antique radio. Oh, I found a place where I



Photo A.

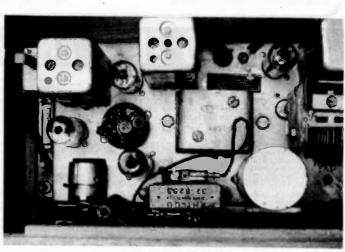


Photo B.

could get a 3O5 for \$4.00, but minimum orders were for \$25.00.

Why sweat the small stuff? I'll simply transistorize the stage.

Now here begins my story for fellow hams. Not being of the mathematical type, but having a good supply of parts and test equipment, I'll use the tried and proven practical approach.

First, we'll want to know as much as needed about the tube to be replaced. The RCA tube manual gives the essentials: filament 2.8 V at 0.05 A, maximum plate current 8.5 mA, maximum power output 330 mW at 8.5% THD. Obviously, we are not working with high power or high fidelity, so the replacement job looks easy so far.

Next, we'll need to determine what circuit characteristics must be known. Remember, this is an ac/dc battery-type radio. This type had some strange circuitry which was not well standardized. No schematic is available, so an hour or so must be spent in tracing out what is required of the circuit.

The power supply circuit as traced out is shown in Fig. 2. Notice how the filaments of all but the 117Z3 rectifier are supplied from the B+ through suitable dropping resistors R1 and R2. The 3O5 cathode resistor (680 Ohms) must be viewed as both shunted by the series string of filaments and as affecting the division of B+ current supplied to the filaments. Notice the 30-uF capacitor at pin 7 of the 3Q5 to common. If this is shorted, it could be the cause of open filaments in the 305. Now is the time to check this. (It was OK in this set.)

Further circuit checks show this amplifier as a straightforward pentode

power-amplifier stage (see Fig. 3). The main features to note here are associated with the power supply of Fig. 2. The grid resistor is returned to common through the 1R5 filament. This places the grid 1.4 V dc above common. The 3Q5 filaments are above common by four 1.4-V filaments. This places the 3Q5 cathode potential at about 7 V dc above common. Grid bias was about 1.4-7=-5.6 V

Now we should decide on what type of transistor amplifier circuit to use. Here is where past experience and a general knowledge of transistor amplifier circuits comes in handy. For this case we'll use Darlington-connected, high-voltage transistors such as the 2N5058 (Radio Shack RS-2008); see Fig. 4. This circuit provides a high input impedance as needed for the first af amplifier stage and more than enough gain and power output capability. The choice of transistors meets or exceeds the voltage and power needs.

Resistor R1 is the base bias resistor. It will be determined by experimentation and added as part of the transistor amplifier plug-in module. Resistor R2 is the base bias divider resistor, which may be the 2.2-meg resistor already in the radio. Resistor R3 is added to control the division of current

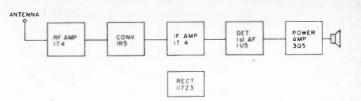


Fig. 1. Block diagram.

between Q1 and Q2. Resistor R4 is the emitter swamping resistor used for temperature stability. It is shown entirely bypassed by C2, but we will experiment with the circuit to determine how much we need or want bypassed. Capacitors C1 and C3 as well as the output transformer are already in the radio. These are used as is.

Let's begin the design and construction. First, use CAUTION. Use an isolation transformer as you always should when working on ac/dc equipment not having its own transformer.

Make up an octal plug with wires out to a breadboard setup. This can be done nicely in this case because we are working with low frequencies and relatively low gain. The octal plug is inserted into the 3Q5 socket and the breadboard set up near by

Initially, calculate or determine component values by Ohm's Law and past experience examples. The resistor replacement for the 3Q5 filament, for example, is determined by Ohm's Law as R = E/I = 2.8/0.05 =

56 Ohms. Power is P = E1 = $2.8 \times 0.05 = 0.14$ Watts. So use some value near 56 Ohms having a power of at least 1/4 Watt to start with.

Resistor R3 in Fig. 4 is calculated to guarantee at least 250 uA in Q1 by assuming that this amount of current will be through it when the Q2 normal VRF of 0.65 V is present. R = E/I =0.65/250 uA = 2.7 k. Power inthis resistor is insignificantly low

Install the 56-Ohm and 2.7k-Ohm resistors on the breadboard. Use resistor substitution boxes or junkbox resistors for R1 and R4. Initially, set R1 for its highest value (10 meg). Set R4 at 1k Ohms initially. Capacitor C2 may have a starting value of 10 uF at 10 V or more. Try all of the three possible near common pins (2, 8, and 7) of the 3Q5 socket one at a time for the circuit common.

Check radio operation for output at about 1/3 volume-control setting. Also check and record filament voltage at pin 7 relative to common, de current through R4 (via voltage drop and Ohm's Law), and


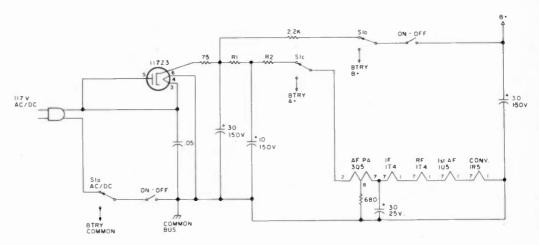


Fig. 2. Power supply.

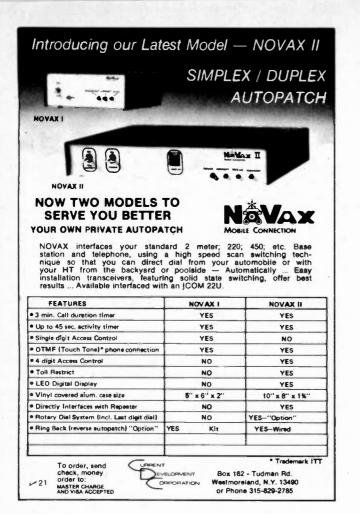



feel the transistors for heat. Caution: Remove voltage just prior to touching the transistors, as up to 100 volts may be present. Change values of components in small steps until yoù obtain correct filament voltage (5.6 V), less than maximum current (8.5 mA),

sufficient output volume with low distortion, and operation with neither transistor more than slightly warm to the touch.

My final circuit was easily constructed on an octal plug (see Photo A) and provided what seemed to Mother more volume and

clearer tones than she had ever heard from this set.

The final circuit is shown in Fig. 5. The original 680-Ohm resistor was disconnected inside the set so that pin 8 could be used as a tie point on the plug. The final filament résistor value was 150 Ohms (not the calculated value of 56 Ohms). This also was wired inside the set although it could have been placed on the octal plug. Final amplifier current was a surprisingly low 2 mA. Both transistors were at only body temperature or less

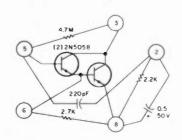


Fig. 5. Final circuit. (Top view of octal plug.)

Notice that the 2.2k-Ohm resistor is bypassed with a 0.5-uF capacitor, but connection to pin 2 for the common return effectively places the 150-Ohm filament resistor in the circuit unbypassed. This helped to raise input impedance as well as to lower distortion. The increased input impedance must have offset gain reduction in this stage because gain was still more than enough.

The 220-pF capacitor was added to eliminate high-frequency hiss. The source of this may have been a poorly filtered signal from the detector or a parasitic oscillation in the transistor stage.

For the last two years now, my mother-in-law hasn't had one bad thing to say about ham radio. She seems well satisfied as she sits in her rocking chair listening to those far-away stations.

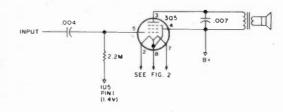


Fig. 3. Af power amplifier.

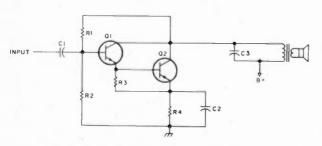


Fig. 4. Transistorized af power amplifier.



. . . at last . . . your shack organized!

A beautiful piece of furniture - your XYL will love it!

\$184.50 S-F RADIO DESK

Deluxe - Ready to Assemble

Designed with angled rear shelf for your viewing comfort and ease of operation.

FINISHES: Walnut or Teak Stain. Floor Space: 39" Wide by 30" Deep

Additional Information on Request. Checks, Money Orders, BankAmericard and Master Charge Accepted.

F.O.B. Culver City. (In Calif. Add 6% Sales Tax.) DEALER INQUIRIES INVITED.

S-F Amaleur Radio Jervices

You've earned your Ham ticket. Now What?

Now you're ready to get on the air but you're not sure about how to actually install that antenna; or how to solder a PL-259 connector; or how to properly ground your station; or identify unknown transistor leads; etc.

Here's the perfect companion for exploring the more practical aspects of the world's greatest hobby.

The new Heil Ham Radio Handbook was written by the 1982 Radio Amateur of the Year Bob Heil, K9EID. Bob heads his own elec-tronic manufacturing



This book doesn't stop at the intermediate level however; you'll find handy hints no matter how long you've been licensed, and unlike other publications you won't need a PhD in engineering to understand the material.

It's a money-saver too-you can make your own 5amp 12VDC power supply at 1/3 the cost, as shown in this handbook, from parts you may have on hand

In fact, once you own and start using this Handbook you'll wonder why "somebody" didn't publish it sooner! And the sooner you send for it, the sooner you'll be en-Amateur joying more aspects of Radio Send \$9.95 (plus \$1.00 ship ping) directly to:

MELCO Publishing

P.O. Box 26 Marissa, IL 62257

SYNTHESIZED SIGNAL GENERATOR

MADE IN



SG100D **\$349.95** plus shipping

. Covers 100 to 185 MHz in 1 kHz steps with thumbwheel dial . Accuracy 1 part per 10 million at all frequencles • Internal FM adjustable from 0 to 100 kHz at a 1 kHz rate . Spurs and noise af least 60 dB below carrier . RF output adjustable from 5-500 mV at 50 ohms . Operates on 12 Vdc @ 1/2 Amp . Available for Immediate delivery . \$349.95 plus shipping

· Add-on Accessories available to extend freq. range, add infinite resolution, voice and sub-audible tones. AM, precision 120 dB calibrated attenuator · Call for details · Dealers wanted worldwide.

> **VANGUARD LABS** 196-23 Jamaica Ave., Hollis, NY 11423 Phone: (212) 468-2720

Custom Mailing Lists on Labels!

Amateur Radio Operator NAMES

Custom lists compiled to your specifications

- . Geographic by ZIP and/or State
- . By License Issue or Expiration Date
- · On Labels of Your Choice

Total List: 435,000 Price: \$25/Thousand

Buckmaster Publishing

Whitehall, Mineral VA 23117

R



ANNOUNCING 73 CLASSIFIEDS

BARTER 'N' BUY

Beginning with the December issue, 73 will accept classified advertising. Individual and non-commercial rates-15¢ per word; commercial rates-50¢ per word; prepaid by check or money order. Ads must pertain to amateur radio products or services, and must be submitted typewritten, doublespaced, 100 words maximum. Include full name and address in ad; telephone number optional. Copy must be received in Peterborough by the 5th of the second month preceding cover date. Example: December Issue ad must be in our hands by October 5th. Ads received after deadline will be run in the next issue. Direct all material and inguirles to

> BARTER 'N' BUY 73 ADVERTISING DEPARTMENT Elm Street, Peterborough, New Hampshire 03458. Telephone: (603) 924-7138

HI-Q BALUN

- · For dipoles, yagis, inverted vees & doublets
- · Replaces center insulator
- · Puts power in antenna · Broadbanded 3-40 MHz
- · Small, lightweight and weatherproof
- 1 1 Impedance ratio
- · For full legal power and more
- Helps eliminate TVI
- With SO 239 connector

only \$13.95



HI-Q ANTENNA CENTER INSULATOR



Small, rugged, lightweight weatherproof

Replaces center insulator Handles full legal power and more

\$6.95 With SO 239 connector

HI-Q ANTENNA **END INSULATORS**



Rugged, lightwelght, injection molded of top quality material, with high dielectric qualities and excellent weatherability. End insulators are constructed in a spiral unending fashion to permit winding of loading colls or partial winding for tuned traps.

- May be used for
 - Guy wire strain insulators
 End or center insulators for

\$4.95 • Construction of antenna load ing coils or multiband traps

DIPOLES

MODEL	BANDS	LENGTH		WITH	WITH HI-C CENTER INSULATOR
Olpoles					
D-80	80),75	130	\$31,95	\$27.95
D-40	40	0,15	66	28.95	24.95
D-20		20	33	27.95	23.95
D-15		15	22	26.95	22.95
D-10		10	16	25 .95	21.95
Shortened d	ipoles				
SD-80	80),75	90	35.95	31.95
SD-40		40	45	32.95	28.95
Parallel dipo	oles				
PD-8010	80,40,	20,10,15	130	43.95	39.95
PD-4010	40,20	0,10,15	66	37.95	33.95
PD 804Q	80,	40.15	130	39.95	35.95
PD-4020	40,	20,15	66	33.95	29.95
Olpole short	leners - onl	y, same as in	cluded in	\$0 mode	is

80.75 \$11.95 pr \$10.95 pr S-40 40

All antennas are complete with a HI-Q Balun or HI-Q Antenna Center Insulator, No. 14 antenna wire, ceramic insulators, 100 nylon antenna support rope (SD models only 50) rated for full legal power. Antennas may be used as an inverted V and may also be used by MARS or SWLs.

Antenna accessories—available with antenna orders Nylon guy rope 450# test 100 feet Ceramic (Dogbone Type) antenna insulators \$1.50 pr 55 SO-239 coax connectors

All prices are postpaid USA 48 Available at your favorite dealer or order direct from

Dealer Inquiries Invited Van Gorden Engineering

BOX 21305 B. SOUTH EUCLID. OHIO 44121

SOCIAL EVENTS

Listings in this column are provided free of charge on a space-available basis. The following information should be included in every announcement: sponsor, event, date, time, place, city, state, admission charge (if any), features, talk-in frequencies, and the name of whom to contact for further information. Announcements must be received by 73 Magazine by the first of the month, two months prior to the month in which the event takes place. Mail to Editorial Offices, 73 Magazine, Pine St., Peterborough NH 03458.

SOUTH GREENSBURG PA NOV 5

The Foothills ARC will hold its fifteenth annual hamfest on Saturday, November 5. 1983: at St. Bruno's Church, South Greensburg PA. Tickets are \$2.00 or 3 for \$5.00: indoor flea-market tables are \$5.00. Refreshments and food will be available Talk-in on 146.07/.67. For further information, advance tickets, or tables, contact WA3HOL, or write FARC, PO Box 236, Greensburg PA 15601

STONE MOUNTAIN GA

The Alford Memorial Radio Club, Inc., will host its 11th annual Hamvention on November 5-6, 1983, at Stone Mountain Park, Stone Mountain GA, Hours on Saturday are 9:00 am to 5:00 pm and on Sunday. 9:00 am to 3:00 pm. The admission fee of \$3.00 Includes a Saturday night cookout for the entire family and variety entertainment. There will be FCC exams, seminars, dealers, a gigantic flea market, and free parking. Camping will be available in the park. Talk-in on 146.16/146.76. For further details, send an SASE to Lew Howard W4LHH, 4132 Creek Stone Court, Stone Mountain GA 30083, or phone (404)-292-

TAYLOR MI NOV 6

The RADAR seventh annual hamfest. flea market, and swap will be held on Sunday. November 6, 1983, from 8:00 am to 3:00 pm, at Kennedy High School, Kennedy Drive, corner of Northline, Taylor Mi. Admission is \$2.00. Tables are \$1.00 per foot (8-foot tables) and reserved tables must be paid for in advance. Dealers may set up at 7:00 pm on Saturday and 6:00 am on Sunday. Send check or money order to RADAR, Inc., PO Box 386, Taylor MI 48180.

Talk-in on 147.93/.33 and 146.52. For more information, phone Bea Johnson at (313)-

WEST MONROE LA

The Twin City Ham Club will hold a hamfest on Saturday, November 12, 1983, from 8:00 am through 5:00 pm, at the West Monroe Convention Center, West Monroe LA There will be a variety of dealers as well as plenty of space for swap tables. Talk-in on .25/.85 and .52/.52. For further information, contact Benson Scott AE5V, 107 Contempo, West Monroe LA 71291.

MT. PROSPECT IL **NOV 13**

The Mt. Prospect Amateur Radio Club and Tri-County Emergency will sponsor RA-COM '83 on November 13, 1983, beginning at 8:00 am, at Prospect High School, 801 W. Kensington, Mt. Prospect IL. Features will include a large indoor electronics flea-market area, commercial exhibits. and seminars. Talk-in on 146.52. For more information and flea-market or commercial booth reservation forms, send an SASE to RA-COM, PO Box 452, Mt. Prospect IL 60056

NORTH HAVEN CT **NOV 13**

The Southcentral Connecticut Amateur Radio Association (SCARA) will hold its 4th annual electronics show and flea market on Sunday, November 13, 1983, from 9:00 am to 3:00 pm, at the North Haven Recreation Center, Linsley Street, North Haven CT. Admission for all events all day is \$1.50; children under 12 accompanied by an adult will be admitted free; tables are \$7.00 in advance and \$10.00 at the door. Features will include the latest in ham radio, computer, and domestic electronics and software. There will be free technical seminars. ARRL information and programs, a bake sale, and a Christmas/Chanukah gift bazaar featuring nonelectronic gifts. Tables for the gift bazaar will be available only in advance. Doors open for vendors at 8:00 am. Food will be available all day. For reservations, send a check, payable to SCARA, to Ed Goldberg WA1ZZO, 433 Ellsworth Avenue, New Haven CT 06511, and include an SASE for confirmation and directions. For further information, phone (203)-773-0646 (home) or (203)-852-7876 (work).

FORT WAYNE IN **NOV 13**

The Allen County Amateur Radio Technical Society (AC-ARTS) will hold its 11th Fort Wayne Hamfest on November 13, 1983, at the Allen County Memorial Coliseum. Fort Wayne IN. Tickets are \$2.50 in advance and \$3.00 at the door; children under 12 will be admitted free. Regular tables are \$6.00, premium tables are \$20.00, and parking is \$1.00. There will be forums on OSCAR, fast- and slow-scan TV, 10m FM, audio, computers, and traffic handling. Talk-in on .88 and .52. For advance tickets (include an SASE with your request and send before the November 1st deadline) and more information, write to Hamfest Chairman, AC-ARTS, Inc., PO Box 10342, Fort Wayne IN 46851

SELLERSVILLE PA **NOV 13**

The R. F. Hill Amateur Radio Club will hold Its annual Winterfest Amateur Radio Flea Market and Exhibit on Sunday, November 13, 1983, at the Sellersville Nationat Guard Armory, PA route 152, Sellersville PA. Take Sellersville or Perkasie exits from PA route 309. The location is approximately halfway between Philadelphia and Allentown, Admission for buyers is \$2.00. Rates for sellers for indoor space is \$4.00 and for outside tallgating space, \$3.00. Refreshments will be available on site and there are many good places to eat nearby. Flying hams should land at Pennridge Airport in Perkasie PA. Talk-in on 144.71/ 145.31 (Almont PA), 146.28/146.88 (Souderton PA), and 146.52 simplex (local area). For additional Information, write PO Box 29. Colmar PA

MASSILLON OH **NOV 13**

The Massillon Amateur Radio Club will present the ARRL-approved Auction Fest '83 on Sunday, November 13, 1983, at the Massillon Knights of Columbus Hall, 988 Cherry Road NW, Massillon OH. Tickets are \$2.50 in advance and \$3.00 at the door, and children under 12 will be admitted free. Each 8-foot table is \$5.00. The flea market will begin at 7:00 am, doors will open at 8:00 am, and the auction will begin at 11:00 am. Food will be available and the hall is easily accessible for the handicapped, Talk-in on 147,78/.18. For advance reservations and tickets, send an SASE to Massillon ARC, 920 Tremont Avenue SW, Massillon OH 44646.

AI PINE NJ **NOV 19**

The Stateline Amateur Radio Club of New York and New Jersey will hold Radiosport '83 on Saturday, November 19, 1983, at the Alpine Boy Scout Campgrounds, Alpine NJ (just off exit 2 of the Palisades Interstate Parkway). Children under 12 will be admitted free. The demonstrations, technical discussions, and dealer and commercial displays will be in a large. Indoor, well-lit, heated facility with ample parking, including spaces for taligating (weather permitting). A refreshment stand will be available, as well as an engineering table with special test equipment available for checking deviation, output, swr, etc. Talk-in on 146.235/.835 and 146.52. For further information and/or table or booth reservations, contact Abel David, Jr. KX2F, 82 Lexington Avenue, Dumont NJ 07628, or phone (201)-387-8129.

BILLERICA MA NOV 19

The Honeywell 1200 Radio Club and the Waltham Amateur Radio Association will hold their annual amateur radio and electronics auction on Saturday, November 19, 1983, beginning at 10:00 am, at the Honeywell Plant, 300 Concord Road, Blllerica MA (exit 27 off route 3). There will be a snack bar, a bargain parts store, and free admission and parking. Talk-in on 147.72/.12 and 146.04/.64 (club-sponsored repeaters). For more information, contact Doug Purdy N1BUB, 3 Visco Road, Burlington MA 01803.

VERO BEACH FL **NOV 19**

The Treasure Coast Hamfest will be held on November 19, 1983, at the Vero Beach Community Center. Admission is \$2.50 in advance and \$3.00 at the door. Features will include tailgating and a QCWA luncheon. Talk-in on 146.13/.73. 146.04/.64, and 222.34/.94. For more information, write PO Box 3088, Beach Station, Vero Beach FL 32960.

CLEARWATER FL NOV 26-27

The Florida Gulf Coast Amateur Radio Council will sponsor the Florida State ARRL Suncoast Convention on November 26-27, 1983, from 9:00 am to 4:00 pm both days, at the Sheraton Sand Key Resort, Clearwater FL Registration is \$3.00 in advance (until November 18th) and \$4.00 at the door. Saturday will feature a QCWA luncheon (\$7.00 per ticket), the ARRL forum hosted by Frank Butler W4RH, and a luau in the evening (\$15.00 per ticket). Sunday will feature a ladies' luncheon (\$7.00 per ticket). Activities will include a flea market (\$12.00 for both days for swap tables), technical talks, and demonstrations. Talk-in on .37/.97, .96/.36, and in Tampa, .16/.76. For hotel room reservations, write Sheraton Sand Key Resort, 1160 Gulf Boulevard, Clearwater FL 33515. or call (813)-595-1611 (mention the Sun-



WE INV	TITE YOU T	O COMPA	KE :
QUALITY*	#SERVI	CE# #	PRICE
Alpine	Drake	Luxor	S.G.C.
Arunta	General Inst.	M & L	Sat-Tec
Auto-Tech	Gillaspie	Macon	Saxon
Avantek	Home Cable	MTI	Sharp
Beddingfield	Janiel	Paraclipse.	T.D.F.
El onder - l'onque	KLM	Polatron	Wilson
Calif. Amp.	Lindsay	Prodelin	Winegard
Chaparral	Locom	Regency	Vector
	Electroni 0. Box 100 Wes		pany
	Humboldt, TN (901) 784-2	38343	▶100
"MANUFACTURER	AND DISTRIBUTOR O	F QUALITY TYRO	SVSTEMS"

coast Convention). For advance tickets or swap-table reservations, send an SASE and check to the order of FGCARC to Florida Gulf Coast Amateur Radio Council, Box 157, Clearwater FL 33517. For more information, write FGCARC at the above address.

GREENSBORO NC NOV 26-27

The Guilford Amateur Radio Club will hold its annual Hamfest/Computerfest on November 26-27, 1983, beginning at 9:00 am each day, at the National Guard Armory, Greensboro NC. Pre-registration is \$3.50 and registration at the gate is \$5.00. Taifgating is allowed with the price of admission. An equipment check-out booth with test equipment and a technician will be available as a free service for those

wishing to check used equipment prior to purchase. Food and free parking will also be available. Talk-in on 144.65/145.25 and 146.52 simplex. For more information and advance tickets (checks to be made payable to GARC, send an SASE to GARC, PO Box 7007, Greensboro NC 27407.

OAK PARK MI NOV 27

The Oak Park High School Electronics Club will hold its 14th annual Swap-n-Shop on Sunday, November 27, 1983, from 8:00 am to 4:00 pm, at the Oak Park High School, Oak Park MI. The east and west doors will open at 6:00 am. Admission is \$2:00 and 8-foot tables are \$6:00. Refreshments will be available. For more information, send an SASE to Herman Gardner, Oak Park High School, 13701 Oak Park

Boulevard, Oak Park MI 48237, or phone (313)-968-2675.

STONY BROOK LI NY NOV 27

The Radio Central ARC will sponsor its 5th annual Ham-Central, 1983 edition. This ARRL hamfest will be held on Sunday, November 27, 1983, from 9:00 am to 3:00 pm, in the social half of Temple Isalah, 1404 Stony Brook Road, Stony Brook LI NY. General admission is \$3.00; children under 12 and XYLs will be admitted free. An 8-foot table space is \$7.00 and includes one free admission. Doors will open at 7:30 am for dealers and sellers (ham-related items only). There will be food, drinks, and free parking available. Seminars will feature speakers Art Greenburg W2LH and Madeline Greenburg W2LH and Madeline Greenburg

W2EEO on antennas and Harry Dannals W2HD on the future of ham radio. Talk-in on 144.550/145.150 and 146.52. For reservations and additional information, contact Scotty Policastro KA2EQW, 80 7th Street, Bohemia NY 11716, (516)-589-2557, or Bob Yarmus K2RGZ, 3 Haven Court, Lake Grove NY 11755, (516)-981-2709.

FARIBAULT MN DEC 3

The annual Handi-Ham Winter Hamfest will be held on Saturday, December 3, 1983, at the Eagles Club In Faribault MN. Registration will begin at 9:00 am. There will be a Handi-Ham equipment auction and a dinner at noon. Talk-in on .19/.79. For more information, contact Don Franz W0FIT, 1114 Frank Avenue, Albert Lea MN 56007.

HAM HELP

I need the schematic for a Digi Scan 8 by Unimetrics. This is an 8-channel scanner.

Dan Quinn KA4CJE Rt. 3, Box 816 Palatka FL 32077

Does anyone have a spare range selector switch for the Heath MM-1 VOM? It is no longer available from Heath.

Charles Guthy 24 Pinewood Ave. Sudbury MA 01776 Wanted: maintenance manuals for the Alda 103 and 103A HF transcelvers. I want to convert the 103 to include 15 meters.

Fr. Joseph Vaughan KC2LJ Frontier Rd. Churubusco NY 12923

I need manuals and schematics for the following equipment: the Eico model 323 VTVM and model 324 signal generator; the Heath model IM-18 VTVM; and the Du-Mont 401-A oscilloscope. I also need a spare power transformer for the DuMont 401-A. I am willing to purchase originals,

copy and return the original, or reimburse your copying and mailing costs.

H. W. Hall WB4OGM 492 Selfridge Drive Colorado Springs CO 80916

I have been searching for the service manual, schematic, and parts list for the Telequipment S-54A oscilloscope. I will gladly pay copying costs.

Raymond L. Wood WB4MQM Rt. 5, Box 93 Elizabeth City NC 27909

I need modification information for the Yaesu FT-2 (B or F version). I am especially interested in frequency-synthesis modifications.

> Richard Metro KA2QWH 201-D Springmeadow Drive Holbrook NY 11741

I need a copy of the manual for the Heath model QF-1 Q-multiplier.

Robert Schlegel N7BH 2302 286th St. East Roy WA 98580

I need the schematic and operating manual for the Heath HX-11 CW transmitter. I will pay for copyling and mailing costs.

Carl Walczewski KB1EH 141 Booth St. New Britain CT 06053

I need help in locating the wiring diagrams for the Hewlett-Packard model 150 oscilloscope and model 152-B dual-trace amplifier

> Charlie Welss 3625 Lochiane North Little Rock AR 72116

"AUTHOR AUTHOR!"

The call for authors is out!

Wayne Green Books announces a December 31, 1983 deadline for submitting manuscript proposals for the upcoming publication list. Ideas for booklength manuscripts about any microcomputer system or area of electronics will be considered. In addition to payment and royalties, we offer our distribution channels and the marketing support your book deserves.

Send proposals or requests for a copy of our Writer's Guide to:

Editor, Wayne Green Books
Peterborough, NH 03458.
Or call toll-free 1-800-343-0728.

ALL NEW H.F. 10/160 METER SOLID STATE P.L.L. TRANSCEIVER



Model 10/160 M

USB-LSB

4 Memories
3 Way Auto-Scan
Includes New Bands
3-Step Tuning Speed
IF Tune ± 1 KHZ
Built-in Dual VFO
Narrow CW filter optional

CW-W CW-N

200 W. PEP (160M-12M) 100 W. PEP (10M) Built-in Power Supply AC-120 VAC DC-13.8 V -Ground External ALC & Relay RTTY, FAX, ASCII



JUST SLIGHTLY AHEAD

1275 N. GROVE ST. ANAHEIM, CA 92806 Cable: NATCOLGLZ TO ORDER OR DLR INFO. CALL (714) 630-4541

-254

NOTE: Price, Specifications subject to change without notice and obligation



THE BARGAIN AT \$1

A no frills directory of over 435,000 U.S. Radio Amateurs. 81/2 x11, easy to read format. Completely updated.

Also available for the first time ever-

(Alphabetically arranged-Sold separately)

Geographical Index

by State, City and Street No. and Call

Name Index

by Name and Call

Ordering Information

- Directory-\$14.95
- Geographical Index-\$25.00
- Name Index-\$25.00

Add \$3.00 Shipping to all orders

Dealer / Club inquiries welcome

Send your order-enclosing check or money order in U.S. dollars to

Buckmaster Publishing

BEEPERS!

Whitehall

Mineral, VA 23117 U.S.A

New CMOS DTMF Chip Kit

Teltone's TRK-957 Kit makes it easier and less expensive to breadboard a low-power, central office quality DTMF detection system. All you need is a power source from 5 to 12 VDC. The sensitivity, wide dynamic range; noise immunity, and low-power consumption make the TRK-957 ideal for telephone switching, computer, and remote control applications. The TRK-957 DTMF Kit is only \$24.75. To order call:

> (800) 227-3800, ext. 1130. In CA. (800) 792-0990, ext. 1130.

> > TELTONE'

-224

N8BKR Introduces A...

8 FT. 40M ROTATABLE DIPOLE



Width 6-ft. Turning Radius

Send for Free Literature

MOLER ANTENNA CORP. 2623 Morris Lane • Girard, OH 44420 (216) 530-2059

YOU'RE NOT LISTENING!

What's a BEEPER? Sometimes called a "courtesy beep," both Faxscan BEEPERS add a gentle high frequency beep automatically to the beginning of each transmission and a low beep at the end, "Talk-over" is a thing of the past! INTRODUCING BP-4 "The PRO" BEEPER The PRO is state-of-the-art beeping! Includes a digitally-programmable timer (use it for ID or timeput warnings), an automatic "Slumber Mode" for long battery life (9V battery required-not included), and programmable volume control of the unique double 4-beep timeout warning. No

YOU HAVEN'T HEARD OUR BEEPERS

speaker! Uses a piezo-transducer! Hook-up's a snap with either model! Interfaces to virtually all modern gear. Manual supplied with each BEEPER. Available in three versions:

- versions are complete with case, cable, industrystandard 4-pin connectors
- versions are the same as above but without connec tors. Add your own!
- versions are circuit-board models for sustom installations. Perfect for repeaters or building INTO your rig

BEEPERS ARE A

BP-4 "The	PRO" BEEPER	BP-3 "The Original"	BEE	PER
A- \$79	All units are	assembled tested,	A-	\$59
B- \$69	carry a 90-day	limited warranty,	B-	\$48
C- \$49	and shipped	i pre-paid in US.	C-	\$29
		Ohio residents add 6%	sale	s taj
	PAX50	INC99		
3148 Do	orf Drive . Dayton C			TN





RTTY your TRS-80 with CONTACT 80 MARK II for 1983

TRS-80, MOD III/IV INTERFACE (included with system) gives keyboard STATION CONTROL and connects with the TTY TU of your choice

(No other equipment needed for CW operation)

Cassette & Disk Features:

- BAUDOT, ASCII & MORSE...
 CW RX speed AUTOSYNC & unique FIST-FIXER...
- TRI-SPLIT screen (user sets HIS way).
 "Unlimited" STORED MSG. sizes....
- Automatic DYNAMIC BUFFER ALLOCATION.
- Live HARDCOPY plus other Line-printing AUTO-ID, TIME/DATED transmissions.
- On screen "OSCILLSCOPE", CLOCK, COUNTERS.
 Unique EDITOR, CLOCKED-KEYING, NAME-LINE.
- · AUTO-DIDDLE, K/B ROLLOVER, REPEATING KEYS. ast CASSETTE I/O and many other features

Additional Disk Features

- Two-way message SELCALL. A "PERSONAL MSO"
 AUTO-MONitor frequency activity to disk...
 SAVE, LOAD, KILL & DIR plus other I/O...
- INTRODUCTORY SPECIAL

CASSETTE VERSION CASSETTE, later upgrade to DISK \$20.00 Guaranteed Include Amateur CALLSIGN-POST PAID

ROYAL J 150



\$199.00

SAVEMONEY HIGH QUALITY FAST DELIVERY We are utilizing the latest equipment and latesi equipment and lechnology to maintain reasonable prices · General Communication Industry Marine VHF Scanners Amateur Bands **CB** Standard **CB** Special Microprocessor J 39 Call or Write **JAN CRYSTALS** P.O. Box 06017 Ft. Myers, Fl. 33906-6017 All Phones (813) 936-2397

Your Ham Tube Headquarters!

TOLL 800-221-0860 FREE

3-400Z	\$85.00	6883B	\$6.75
3-500Z			\$9.15
4-400A	\$80.00		\$29.50
4CX250B	\$55.00	8122	\$98.00
572B	\$48.50	8156	\$10.95
811A	\$12.00	8844	\$29.50
813	\$29.50	8873	\$175.00
6146B	\$6,50	8874	\$180.00
6360	\$4,25	8877	\$450.00
		8908	\$10.50

RF CONNECTORS SEMICONDUCTORS PL 259 10/\$4.95 PL 258.... UG 175/176 10/\$8 95 MRF 245/5D1416 \$30.00 10/\$1.60 \$2.50 ea. MRF 455 \$12.50

UG 273/U \$2.25 ea. \$2.50 ea. M 358 M 359 \$1.75 00 2N3055 2N6084 \$.95 \$12.50

TOP BRAND Popular Receiving Tube Types FACTORY BOXED 75/80% OFF LIST FREE LIST Available Includes full line of RF Power Transistors. Minimum Order \$25

Allow \$3.00 Minimum for UPS Charges Write or phone for free catalog. TUBES-BOUGHT, SOLD AND TRADED

Premium Prices Paid For EIMAC Tubes

COMMUNICATIONS, Inc. 2115 Avenue X Brooklyn, NY 11235 Phone (212) 646-6300

SATELLITES

Physics Laboratory just off I-95, between Baltimore and Washington. The planned programs include: how to get on the new OSCAR 10 satellite, tracking OSCAR 10 with/without a computer, a report on the W5LFL Space Shuttle operation, PACSAT, and, much, much more! Admission is free but advanced reservations are required. For further information and reservations, contact AMSAT, PO Box 27, Washington DC 20044, or call (301)-589-6062.

UTC EQX

0058 154

0043 152 0027 150

0012 147

8124 170

0109 168

0038 163 0023 161

0155 0140

EOX

155

0123

0118 0113 0107

0102 0057 0051

0025

0046 156

0035 156 0030 157

UTC EQX 0153 163 0143 162

0134 161 0124 161 0114 160

0105 159 0055 158 0045 157

0036 156 0026 155

0137 181

0016

0007 0156

155 154

UTC

0009

0006 0003

0001

0158

0155 0152

0149

0141

0018 135 0015 0012

Amateur Satellite Reference Orbits OSCAR 8 UTC EQX

Date

12

0059 103 0103 104

0108 106

0121 109 0125 110 0129 111

0134 112

0008

108

98 91 92 0004

INITIAL ORBITAL TIMES FOR STS-9

Any given orbit begins as the spacecraft crosses the equator traveling west to east. The following orbital operating times are based on an 11:30 AM EDT launch on October 28th, If the launch is delayed for any reason, you must add the amount of the delay to the times stated here to obtain new orbital track timing for an operating pass. Also, what we are listing here are only the "official operating periods" scheduled as of September 3rd. Dr. Garriott says he will attempt to provide other "unofficial" operating periods as well, but these will have little advance notification. Whenever possible, advance notice of these extra operating times will be made available over W1AW, in bulletins issued by NASA-affillated radio clubs (such as W5RRR in Houston), and on the dally updates of the Westlink Radio Network Hollywood newsline: (213)-465-5550. All North American passes are listed in local time, while those for foreign contacts with the spacecraft are in UTC. All times are approximate for the start of a given pass. You may calculate the specific time over your QTH by adding the forward speed of the space vehicle, which is 17,000 miles per hour

	K6DUE and the Westlink Report.				0021 94 0025 95	0009 157 0003 158	0120 181 0104 179	0127 180 0118 179	0135 178 0132 178	16 17
Orbit #	Date	Ground Track	AOS Time	18 19	0030 96 0034 98	0158 188 0152 188	0049 177 0034 174	0108 178 0058 177	0129 179 0126 180	18 19
		areana maan	AOS TIME	20	0038 99	0147 188	0018 172	0049 176	0124 181	20
39	10/30	Spokane, Denver, Dallas, Houston, New	2000 CDT	21	0043 100	0142 188	0003 170	0039 175	0121 182	21
		Orleans, S. America		22	0047 101	0136 189	0146 197	0029 174	0118 182	22
40	10/30	N. California, down Pacific coast E. of	1930 PDT	. 23	0051 102	0131 189	0131 195	0020 174	0115 183	23
•••	10/00		1930 PD1	24	0056 103	0125 189	0115 193	0010 173	0112 184	24
		San Francisco and LA, Mexico		25	0100 104	0120 189	0100 190	0000 172	0109 185	25
47	10/31	W. Australia, S. America, Europe	1430 UTC	26	0104 105	0115 189	0044 188	0150 201	0107 186	26
		NOTE: Standard Time begins this date		27	0109 107	0109 190	0029 186	0140 200	0104 187	27
63	11/1	S. America, USSR, India, Australia	1330 UTC	28	0113 108	0104 190	0014 183	0131 199	0101 187	28
64				29 30	0117 109	0059 190	0157 211	0121 198	0058 188	29
-	11/1	Iran, Scandinavia, USSR	1555 UTC	Dec 1	0122 110 0126 111	0053 190	0142 208	0111 197	0055 189	30
77	11/2	NW Africa, E. Europe, Poland, China	0850 UTC	Dec 1	0130 112	0048 190 0043 190	0126 206 0111 204	0102 196	0052 190	1
79	11/2	N. tip of S. America, Caribbean, N.	1250 UTC	3	0135 113	0037 191	0055 201	0052 195	0050 191	2
		Europe, USSR, India	1500 010	Δ	0139 114	0032 191	0040 199	0042 195 0033 194	0047 191	3
0.0				5	0000 90	0027 191	0024 197	0023 193	0044 192 0041 193	4
80	11/2	Caribbean, all E. Coast states, New-	0815 EST	6	0004 91	0021 191	0009 194	0013 192	0038 194	2
		foundland, UK, central Europe		7	0009 92	0016 191	0152 222	0004 191	0035 195	7
				8	0013 93	0011 192	0137 220	0153 220	0033 195	Ŕ
		ANICAT CVALDOCUM		9	8817 94	0005 192	0122 217	0144 219	0030 196	' 9
		AMSAT SYMPOSIUM		10	0022 95	0000 192	0106 215	8134 218	0027 197	10
AMS	AT will hold	d an Amateur Radio Satellite Symposium in conjunction	on with ite on	11	0026 96	0154 222	0051 213	0124 217	0024 198	11
				12	0031 97	0149 222	0035 210	0115 216	0021 199	12
mual me	etting on 5a	iturday, November 12, 1983, at the Johns Hopkins Univ	ersity Applied	13	0035 99	0144 223	0020 208	0105 216	0018 200	13

PACKET RADIO



ASCII-USA/AX.25 **HDLC CONVERTER**

USA/AX.25 is the AMRAD approved digital format STANDARD used on amateur packet radio networks.

PAC/NET board only \$80.00 Assembled/Tested, NoICs, 90 day warranty

Package of all ICs except 2-2716 **EPROMs** \$80.00

PAC/NET SYSTEM

PAC/NET SYSTEM System Tested 4.5 x 6" board complete with all ICs and programmed EPROMs personalized for each purchaser. Requires only single 8-10 volt ½ amp power. 1 year guarantee of hardware/soft-ware/AX.25 standard RS232 serial ASCII at any user baud rate. RS232 HDLC for 202 modem used for AFSK or direct to RF equipment for FSK.

Custom Systems Custom Programming

 $oldsymbol{B}$ ILL $oldsymbol{A}$ SHB arphi

AND SON -KA20EG 201-658-3087 **BOX 332 PLUCKEMIN N.J. 07978**

AFFORDABLE HARDCOPY

Put your personal computer to work printing the log, QSLs, or RTTY...The **Gemini 10** by Star Micronics is a versatile dot-matrix printer that we feel is the best buy for the money. Parallel interface and both friction and tractor feed are included at this low price.

TO ORDER: Mail order only, check or money order. Add 6% sales tax on California orders. Allow 2 weeks for personal checks to clear. Price includes UPS shipping in continental US. Prices subject to change without notice. Circle reader service number for print sample.



GEMINI 10\$325

Ampersand electronics

6065 Mission Gorge Rd. # 66 San Diego, CA 92120

NEW EGBERT II RTTY-CW for THE APPLE COMPUTER

SOFTWARE ONLY

REQUIRED

Many Standard and UNIQUE FEATURES (ALL ON ONE DISK)

any MARK and SPACE frequency. 500 Hz to 3000 Hz

CAN BE USED WITH TTY FOR THE DEAF Requirements: Apple II 48K, 3.3

TRANSMIT OR RECEIVE

ALSO ACCEPTS TTL INPUT TO GAME I/O C.W. VERSION AVAILABLE

PRICES: RTTY \$39.95 Back-Ups each \$ 7.50 RTTY with CW \$59.95 Shipping \$ 2.50

WRITEFOR DETAILS OR ORDER FROM:

W.H. NAIL COMPANY I

275 Lodgeview Drive Oroville, Ca. 95965 244 (916) 589-2043 T

Foreign Shipping = \$6.00 (Calif. Residents add 6% tax)

DR. DIGITAL

Robert Swirsky AF2M 412 Arbuckle Avenue Cedarhurst NY 11516

Practically every mode of communication used by an amateur-radio operator makes use of sound. Obviously, in voice communications, sound is directly processed by our brains. In CW communications, unless you are using a code reader or a flashing light, the radio signal is converted into a tone for us to hear. What is not so obvious is that sound is also cruclal for "digital" communications. The only way to send a digital signal over communications equipment designed for voice is to convert it into tone signals. On the receiving end, special hardware is needed to convert the tone signals back into digital pulses.

All modern computers employ digital circultry; they can only deal with signals that are either "high" or "low" (commonly represented with +5 V and 0 V in TTLbased computer systems). Since sound is of an analog nature, computers cannot deal with it directly. One way of dealing with sound is with circuitry adjusted to respond to certain frequencies. This method is useful if only a small number of sound frequencies needs to be detected. A common example of this is a RTTY decoder. Usually a pair of tuned circuits for sometimes phase-locked loops) is usedone circuit is tuned to the "mark" frequency while the other is tuned to the "space" If, however, more than a few tones must be decoded, more sophisticated circultry is needed. For applications such as speech digitizing (recording speech in digital computer memory), usually an analog-to-digital converter circuit is used. These are available as integrated circuits. Some of the more expensive A/D converter chips are quite fast; conversion time is just a few microseconds.

I am a software-oriented person. I-will go to extremes to solve a problem by using fancy software techniques rather than hardware. Perhaps it's because I am the world's worst solderer, or maybe because I am totally uncoordinated when It comes to handling small electronic components, that I have developed my distaste for electronic construction projects.

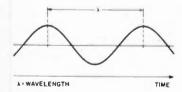


Fig. 1. How a wavelength is measured.

ZERO CRDSS

Because of my software vs. hardware attitude, I use software to deal with sound problems. Using some surprisingly simple algorithms, it is possible to analyze audio Information with a microcomputer.

Before I go into software techniques for dealing with sound, let's review what the phenomenon of sound is all about. As you probably know, sound is carried by waves in some sort of a medium. When a reed, for instance, is set vibrating, it compresses the air immediately surrounding it. Due to the elastic nature of air molecules, the compressed air spreads out and compresses its neighboring molecules. It is this "bucket-brigade" effect that causes sound to travel. (Note that the molecules themselves aren't being compressed, it is the space between them.) In a denser medium, such as water, steel, or air at a higher pressure, sound will travel faster because the elasticity is greater. Conversely, less dense media will carry sound at a slower rate.

Sound frequencies that human beings can hear range from about 16 Hertz to about 25,000 Hertz, a Hertz being a cycle per second. Another way of measuring the frequency of a sound is by wavelength. Fig. 1 shows a diagram of a wavelength; a measure of the distance from one point on a wave to another corresponding point. The example I used shows it being measured from peak to peak. wavelength can be expressed in terms of length in linear units (e.g., inches) or in time units (e.g., milliseconds). When working with a computer, it is convenient to measure wavelength in time units. After all, everything in a computer is clocked to a stable reference frequency.

Last month, we discusse a circuit known as a zero-cross detector. This simple circuit, consisting of an operational amplifier and a few additional components, makes it possible to do a number of things with sound waves. While you can only measure frequency information with such a circuit (any waveshape information is undetected), that is enough for many applications. Besides, the Apple II, II+, and Ile computers have the zerocross detector built in: It is what the cassette interface uses. This means with an Apple or Apple-compatible computer, no additional interface hardware is needed to measure the frequency of a tone.

When writing software to process audio signals, it is necessary to use assembly language; high-level languages are just too slow to be useful. Also, with assembly language, it is possible to know exactly how much time an instruction takes to execute. This is critical when accurate timing loops are needed. Since the Apple II

ZERO LINE

computer uses a 6502 microprocessor. the programs here will be written for that microprocessor. The algorithms, however, will be the same for any microprocessor

Perhaps the simplest way to measure frequency is to have the computer count from one state change of the cassette port (zero-cross detector) to another. Looking at Fig. 2, we see that the state changes every half-cycle. Using this information, an algorithm to measure frequen-

- 1. Wait for the port to become negative.
- 2. Increment a counter by 1.
- 3. Check the port.

4. If negative, go to step 2: if not, stop Now, to determine frequency from the result in the counter, some things need to be calculated. Take a look at Program 1. Notice the numbers in parentheses after some of the instructions; these are the execution times (i.e., the amount of time it takes for the computer to perform the instruction) measured in clock cycles. The Apple computer runs at a speed of 1,023,000 clock cycles per second. Once around the loop in the program takes 9 clock cycles. If, after exiting the loop, the counter has counted to 50, this means that 50 x 9 x 1/1023000 seconds have elapsed, or that one half-cycle takes 0.0004399 seconds. Since these are halfcycle, we multiply this by 2 to get 0.0008798 and take the reciprocal. This leaves us with 1136.66667 as the frequency in Hertz.

This method of counting a time interval between half-cycles is simple and quick, but not very accurate. The resolution (i.e., the closest frequencies that can be distin guished) is poor, and gets worse at higher frequencies. Some ways of improving this would be to raise the clock frequency of the computer, or count for a number of cycles. The problem with counting for a number of full cycles, as opposed to one

SDURCE FILE: PRDG4

half-cycle, is that the counting loop gets more complex and takes more clock cycles to execute. If the loop takes a longer amount of time to execute, frequency resolution is lost. Still, this is probably the best method when high speed is needed and close resolution is not. Certainly this method would be useful for decoding wide-shift RTTY, or even the tones needed for SSTV if you are only testing for a limited number of gray levels. The program in listing 1 has some limitations. Perhaps its greatest one is that it uses an 8-bit register to store the count. Because of this, low frequencies cause it to loop around to zero and start again. One possible solution, at the cost of 2 clock cycles per Iteration, would be to add a BEQ OUT Instruction after the INY. This way, if a result of zero is returned from the subroutine, you know to Ignore it. Of course, one can make use of the counter 'wraparound' to measure low frequencies

The most accurate way of measuring frequencies on a microcomputer is to actually count the cycles for 1 second. The result would be directly in Hertz, and resolution would be to 1 Hertz. If a computer has an interrupt timer, it can be used to ensure that the count program runs for one second and then stops. Unfortunately, due to the way the Apple's sytem ROM is configured, it makes it very difficult to deal with interrupts.

The way around this problem is to have run through the program that counts cycles a fixed number of times. It is essential that the cycle-counting portion of the program take exactly the same amount of time to execute each time it runs. This is

0000: Program listing 1. 0000: \$C060 C060 CASS EQU OOFC: 170 OOFD: EQU NEXT DEJECT FILE IS PRDG4.DEJ0 0302: DRG LDA AND STA 0302:AD 60 C0 INIT 0305129 An 0307:8D 4E 030A:A9 00 030C:A8 LAST LDA 14 TAY 030D:AA 030E:A9 LDA 1124 0310:85 0312:20 FD 28 03 STA HL DDP LDDF JSR 0315:98 0316:A0 00 • 0 CLC CL 23 ADC CL 1500 CH CH 031B:85 STA 25 26 27 0310:29 031F:65 FE 0321:85 FE ADC 0323:06 28 DEC 0325:D0 EB HLDDP 0327:40 0329:E8 0329:F0 032E:AD 032E:29 LDOF LEAVE 60 C0 LDA CASS ##80 (9) 34 35 AND 0330:85 STA (3) 4B 03 0332:4D FOR LAST 36 37 38 39 (4) (2/3) (6) (4) (3) BMI LSR LDA 0335:30 4A 4A 28 0337:4E 033A:AD 033D:4C 03 WASTE JMP LDOP CA:0PE0 FC 46 03 ADD1 LOA (3) 0342:8D STA LAST 0345:CB 0346:4C 0349:60 28 COBK LODP JMP : (3) LEAVE RTS WASTE 0346: LAST

*** SUCCESSFUL ASSEMBLY: ND ERRORS

0340 ADD1 70346 GDBK 0328 LDDP FD ZP	C060 70302 0312		0348	CH LAST TZP		CL LEAVE WASTE
---	-----------------------	--	------	-------------------	--	----------------------

Fig. 2. Apple cassette-port operation.

CASSETTE PORT VALUE POSITIVE

NEGATIVE POSITIVE NEGATIVE T5

trickler than it sounds; if a conditional branch takes place, the entire routine must execute in the same amount of time as it would if the branch did not occur. Also, to measure reasonably high frequencies, the counting loop must take as little time as possible.

Program 2 shows a frequency-counting subroutine that counts zero crossings on the Apple cassette port for a fixed amount of time. When used with Program 3, a Basic program to do some floating point calculations, it can measure frequencies with a resolution of 1 Hertz. If your Apple's clock is running at the proper frequency, it should give you fairly accurate results.

Lines 10 through 18 of Program 2 Initialize various memory locations. The current status of the cassette port is examined and stored in memory location LAST. The X and Y index registers are set to zero. and the zero-page memory location ZP is set to 124. ZP controls the number of iterations that the LOOP, starting at line 31, is executed. As each iteration of LOOP takes 8192 clock cycles, the timing portion of the program will take 1.015.808 clock cycles - just a little bit under a second. (The difference is corrected in Program 3.) Now look at the LOOP portion of the program (line 31). I have indicated the number of clock cycles that each instruction takes in parentheses. (The 2/3 means that the instruction can take 2 or 3 cycles, depending on whether the branch is

POKE 254.0: POKE 255.0 PORE 254,0: FURE 255, CALL 770 ZC = PEEK (254) = 256 + PEEK (255) TF = ZC / 2 FRO = TF = 1.0070801 VIAB 4: HTAB 27: FRINT " VTAB 4: PRINT "THE FREQUENCY IN HERTZ IS "; INT (FRO)

Program listing 3.

taken.) This routine will always take 32 clock cycles to execute, while it is performing the actual counting. The time spent before it starts to count is irrele vant. Notice that whenever the Iteration counter goes through 256 Iterations, it returns to MLOOP at line 20. MLOOP clears the registers, accumulates the zero-cross count, and calls the subroutine LOOP again, it does this 124 times (remember lines 17 and 18) and then exits, returning control of the computer to the Basic Interpreter. By using the technique of "emptying" the counting register every so often, one can overcome the problem of the 6502's 8-bit register. (Remember that an 8-bit register can only hold 256 different values.) The frequency information is contained in memory locations 254 and 255. These zero-page locations (so called because they are on the bottom 256-byte memory page) take less time for the computer to use: one less clock cycle per in-

ILIST

Listing 3, the Basic program, clears the

zero-cross count locations (line 10). It then calls the routine and calculates the number of zero crosses detected in the counting period. This figure is divided by 2 (line 40) to convert from zero crosses to cycles and multiplied by 1.0070801 to correct the count for a 1-second sampling period. Finally, since the fractional portion of the number isn't accurate, it is discarded, and the integer portion is displayed on the screen as the frequency in Hertz.

To enter the assembly-language portion of the program into the computer, enter the monitor with the command CALL-151 from Basic and enter the hexadecimal data from address 0302 to 0349 hex. After the information is typed in (consult the reference manual if you don't know how to enter hex data), save the information with the command: BSAVE PROG4.OBJ0,A\$302,L79. You might wish to add the statement: 7 Print"BLOAD PROG4.OBJO" to the Basic program in listing 3. This will ensure that the machine-language routines are loaded in each time the program is run. (Remember to put a CTRL-D before the BLOAD.)

I found this frequency-counting program to be quite useful. One of the first things I did with it was to measure receiver drift. With the program running, I turned my receiver's calibrator on and tuned the vfo until I heard a tone, which I fed into the Apple's cassette port. By noting the frequency of the tone when the rig was first turned on, and comparing it after a Half hour, I was able to determine how many Hertz the receiver had drifted.

If the 1-second sampling time is too long for your needs, you can shorten it, sacrificing some resolution. For example, if you use a 1/100-second sampling rate, the result would be accurate to 100 Hertz. To accomplish this, change the 124 In line 17 of listing 2 to 12. This would make the sample time equal to 12 x 8192 clock cycles, or .00960938 seconds. Multiply by the reciprocal, 10.406494, and divide by 2 (or multiply by 2 and divide by the reciprocal) to get the frequency in Hertz. Obvlously, any sampling time can be selected in steps of 8192 clock cycles. (Remember that the LOOP portion of the program always takes 32 x 256 or 8192 clock cycles to execute.)

Next month, we'll take a look at tone and waveform generation on computers. Keep the letters coming in-just remember to include an SASE.

MHz). This is the normal power-up fre-

quency for vfo A. If the vfo B button were

pushed, the unit would power up on

I want to look around 432.1 MHz. so I depress the MHz button. This allows me

to move one whole MHz for each click of

the main-tuning knob. One complete revo-

lution is 50 clicks, so J can move around

the band pretty quickly. One click down

puts me on 432,000, but now I have to

move 100 kHz up in frequency. I push out

430 000 MHz

REVIEW

THE KENWOOD MULTI-MODE TR-9500 TRANSCEIVER

Are those declining sunspot numbers making you think about a new challenge in the hobby for the coming years? Have you wondered about all that talk of the new OSCAR satellite and its fantastic DX potential? Or possibly a friend has told you about how interesting and sunspotproof VHF/UHF propagation can be.

Well, a number of manufacturers have now extended the multi-mode-radio concept to the 70-cm band (420-450 MHz). These radios are ideal as a satellite uplink/downlink or for terrestrial DX as well. Kenwood's latest offering is the TR-9500 transceiver. This radio covers the frequency range of 430-440 MHz and provides FM, CW, and SSB modes.

(A word of caution to US and Canadian amateurs: Although the radio is accurately described as being multi-mode, the FM capabilities will not find much use here since present band plans place FM use in the 440-450-MHz portion of the band above the radio's band edge. Don't blame Kenwood for this, however; in most areas of the world, only the 430-440-MHz segment is allocated for all modes of amateur use, and most other radios on the market are similarly designed.)

The TR-9500 is a microprocessor-controlled unit complete with scanning, memories, and 10 Watts of rf power output. An optional base unit which includes a memory backup function, an external PS-20 power supply, and SP-120 speaker make it equally at home under the dash or on the operating table. It can be moved quickly from either thanks to its stide-in-type mobile mounting bracket. The 9500's 2m cousin is the very popular TR-9130, which

makes an ideal companion radio, espe cially for OSCAR users.

In an approach similar to many state-ofthe-art transceivers on the market, the TR-9500 employs a dual-vfo frequencycontrol system. For example, you could use vfo A for the 432-MHz portion and vfo B for 435-MHz and OSCAR activities. The radio does permit you to change frequency while transmitting-an important consideration for OSCAR users which has been overlooked on some other radios. Either vfo can be used to program the six memory channels. Once programmed, each memory channel can be recalled with a multiple-position switch or scanned automatically by the unit's microprocessor.

Although such features are usually associated with FM operation, I found it useful both for OSCAR and terrestrial QSOs to keep tabs on band activity. During an OSCAR pass, you can program the beacon frequency in one memory and use the other memories for busy stations you hear and want to work. Just switch between channels and wait for the first QSO to end. I also used this technique during a con-

For those who can make use of the FM capabilities, the TR-9500 is well equipped. Two standard repeater offsets, 5 MHz and 1.6 MHz, are provided as well as a programmable offset for the frequency programmed into memory channel 6. In this case, both transmit and receive frequencles are individually programmed for those odd split repeaters.

Now that we are familiar with some of the basics, let's sit down and actually go through the operation.

I push on the combination power switch and volume control and the bright green LED display shows 3.000.0 (for 433.000

the MHz button and now each click moves me 100 Hz. This will take a long time. The manual says that the FM2 position on the mode switch will provide steps of 1 kHz and the FM1 position, steps of 25 kHz. Hmmm...maybe this FM mode will be of some use after all. I quickly switch from USB to FM1; four clicks of the main-tuning knob and I'm on-432, 1 MHz. Sounds pretty quiet, so I try a CQ. As I let go of the push-to-talk button on the mike, the back-light meter jumps to nearly full scale. It's my friend Glen.

K1GW. He sounds just a bit off frequency. so I depress the RIT button A red LED lights to let me know the RIT is on and I tune him in a little better on the combination RIT/rf-gain control. We quickly get our frequencies netted and off goes the RIT. Glen gives me an excellent report both signal strength and audio.

I depress the power switch to the 1-Watt low-power position with equal readability at his end. We decide to QSY up 10 kHz to get off the calling frequency, but before I do I want to put the frequency into memory. I set the memory switch to position 1 and press the button right under it marked M. The radio beeps at me. I guess it wants to tell me I've done something important.

Let's see now, I have to move up to 432.110 MHz. If I tune the main-tuning knob, I should be there in about two revolutions (about 100 steps), or I can switch to the FM2 mode and be there in 10 steps. I opt for the latter. There's Gien and this time there are no netting problems.

We try it on CW for a while. The sidetone sounds good and is just about the



The Kenwood TR-9500.

right level. My keyed signal is reported as clean. The TR-9500 uses the same filter for both SSB and CW. It also switches from a slow ago characteristic on SSB to a fast one on CW.

After we finish. I decide to explore further the scanning and memory features. First, I program in several channels at random. I depress the MR (Memory Recall) button and the channel selected on the memory switch is displayed. A green LED lights to fell me I'm in memory mode. Now I can switch between six channels just like on those old-fashioned radios from way back in the 1970s. Without crystals, of course. I depress the MS (Memory Scan) button and now I don't even have to touch the memory selector. The radio automatically steps through the channels, carefully jumping over those channels which are not programmed. When a signal is heard, the radio stops or stays put until you reinstate scan mode

Next, we'll try scanning the vfo frequencies. I push out the MR button and the last frequency set on the vfo Is displayed. Push the button marked SCAN and the vfo begins scanning up the band continuously in the normal steps according to the mode selected. I can stop it by pushing the HOLD button or the push-to-talk (PTT) button on the mike. Or it will stop automatically when it comes across a signal.

Speaking of the microphone, Kenwood has included an up/down remote-tuning feature which is especially useful for mobile use. Each push of the appropriate button moves you 1 step and lets you know with a beep. To QSY several steps, just count the beeps. Hold down either the up or down button continuously and the tuning rate increases—and so do the beeps.

During the evaluation period, I became quite proficient in using all those buttons and dials on the 9500 and found the radio to be functionally well thought out and a pleasure to use. On-the-air reports have been consistently good and no problems were encountered.

The manual provided is clear and concise, but it does not cover details of circuit design and repairs. There is an optional service manual available which presumably covers these details for those so inclined. I recommend to new owners of the radio that they thoroughly familiarize themselves with the operating manual in order to get the most out of the radio. Although operation is relatively simple, there are some sophisticated features which are not immediately obvious.

Only a couple of minor suggestions for future product revisions: There is no squelch function for SSB or CW operation, and although it's not a necessity as it is on FM, it would be handy. Also, I personally prefer the fast ago time constant even in SSB mode, and the automatic-switch feature did not allow me the option. I did appreciate the use of a type-N antenna, in a number of 70-cm radios on the market, this feature has been overlooked.

For more information, contact Trio-Kenwood Communications, 1111 West Wainut, Compton CA 90220.

> Dave Mackey K1KA Amherst NH

THE AEA INC. AMTOR TERMINAL UNIT

New modes of communication have always intrigued me. In past years, I have tried them all: RTTY, SSTV, high-speed CW, fast-scan TV, and even FAX. My favorite mode, by far, has been RTTY. If you are using a CRT, this mode can be completely silent. It also doesn't require continuous



Photo A. The AMTOR terminal unit from AEA, Inc.

concentration, as does CW. One can step out of the shack for a minute and not miss a thing—every word will still be on the CRT.

While RTTY signals are fairly QRM resistant, noise and fading still can distort the copy, leaving a number of "hits" (the RTTY op's term for errors) in the printout. Now that computer-controlled circultry has become more affordable, it only makes sense that someone would try to come up with a solid-state solution for detection and correction of transmission errors in RTTY communication. One method of accomplishing this is to use the AMTOR protocol.

AMTOR originally was developed for commercial users of RTTY. The AMTOR code is based on the Murray (Baudot) code and has the same character-set restrictions. Each AMTOR letter consists of seven bits arranged so that each letter has four 1 bits and three 0 bits. If, on the receiving end of the teletype circuit, a character is received that does not have the 4:3 ratio, an error has been detected.

AMTOR has two modes. In the first mode (ARQ), data are transmitted in blocks of three characters. If an error is detected by the receiving computer, it sends a control signal back that means "send the 3-character block again." If no errors were detected (all the characters had that 4:3 ratlo), the receiving RTTY computer sends a character telling the sender to send the next three letters.

The second mode (FEC) has each letter sent twice. If an error is detected in one character, it ignotes it and copies the other one. This mode does not require the transcelver to be constantly switching from transmit to receive.

AMTOR was Implemented originally using mechanical devices, but as computer technology improved, it made sense to use microprocessors. Earlier this year, AMTOR was approved for use on the low

bands (any digital code is legal above 50 MHz, but below it only AMTOR, ASCII, and the Baudot code), and various companies have started to support it.

The AMTOR AMT-1 terminal unit by AEA (Advanced Electronic Applications. Inc.) was designed to make it easy for a ham to use the AMTOR standard for RTTY. Consisting of a terminal unit, microcomputer, ROM software, and control circuitry in one integrated package, it makes AM-TOR operation fairly automatic; all you have to do is add a computer with a serial port. When I first saw It, I was impressed by the modern design-there are absolutely no switches to be found on the unit! All control of the AMT-1 is accomplished by sending special character combinations through the serial port. The AMT-1 indicates its status via the LED display on the front panel and by sending special information back to the computer.

Setting the unit up takes a little while. In AMTOR operation, it is essential that the transceiver being used can switch from transmit to receive in 50 ms or less. (Remember that the TU takes care of T/R switching and has to switch back and forth between every three characters.) The shorter the T/R switching time, the better: Maximum distance is limited by too long a switching time. My TS-520S just made it. I would imagine that most new solld-state rigs would have absolutely no problems. The AMT-1 connects to the rig's microphone Jack, the PTT lines, and the audio output (Photo A). It is convenient to tap the audio from the rig at a point before the volume control. This allows adjusting the rig's audio without disturbing the AMT-1.

Connecting a computer to the AMT-1 requires an RS-232-compatible port set to either 75 or 110 baud, full duplex. It is important to have the full-duplex mode because the unit echoes back as soon as any characters are typed (this can be dis-

abled, but it is better to use the AMT-1 echo feature). AEA included two DIP jumper plugs which bypass the TTL to RS-232 conversion circultry. While this is mainly for VIC-20 and Commodore-64 computers which use TTL level signals in their serial ports, it can be used in conjunction with other micros. I was able to write a program for my Apple II which "converted" the game port to a full-duplex serial port. After wiring up an appropriate connecter, I plugged in the AMT-1 and it worked flawlessly.

The AMT-1 provides for word wraparound, but only for terminals that are over 60 columns wide. On a 40-column computer, the display looks a bit strange. (See Photo B.) Fortunately this can be disabled, causing the text to go from one end of the screen to another. If you want word wraparound for a 40-column machine, you can provide for it easily in software. Many terminal control programs incorporate this feature already. While a custom program might provide the most flexibility for using the AMT-1, any ferminal communications package that allows control characters and escape characters to be transmitted should do the trick.

When first turned on, the AMT-1 goes through a testing sequence that causes all the LEDs to turn on and off in a pattern. (I don't know if that accomplishes anything, but it looks nice.) It then enters the "escape mode" and is ready to accept a command from the computer. Typing a Q gives the unit's status:

V:03 I:???? T:30 B:45 S:20 L:1 N:1

The V is the revision number of the software. Mine is revision #3. I is for the selcal code. When nothing has been entered, it shows question marks. T is the AMTOR ARQ timeout: how long the unit should wait to receive the confirmation character before indicating an error. B is the baud rate for conventional RTTY operation (the unit also works nicely for "regular" RTTY). S is the CW sending speed, and L and N refer to word-wrap and echo-back modes.

To change a parameter, one types an ESC character followed by the proper letter. For example, to put the selcal code AFTM (no numbers are allowed) in memory, type ESC I. The unit will prompt with a colon, after which you enter a four-letter code of your choice. All the other parameters are changed in much the same way.

After I got through the 16 pages of documentation and wired up all the necessary cables, I tried it out on the air using the Baudot mode. One thing about this TU that took a bit of getting used to is the fact that it copies "upside down"; the receiver must be set for USB instead of the more traditional LSG. There is no disadvantage to doing things this way; it's just different from the way most terminal units operate.

Tuning around 20 meters, I found the TU to be fairly good. It uses an unconventional design: The audio is fed through a 4-stage active 300-Hz bandpass filter and then to a frequency-to-voltage converter. This is to facilitate a bar-code-tuning display. Tuning in a signal is easy; the receiver is tuned until one sees a centered pair of flashing LEDs on the display.

Before actually trying an AMTOR QSO, I decided to try copying the ARRL AMTOR bulletin. The League transmits their RTTY bulletin in the FEC (forward error-correction) mode—the one where each letter is transmitted twice. Absolutely flawless copy was the result; the same bulletin I copied using the Baudot mode did have a number of hits.

Most AMTOR activity is centered around 14.075. I went to this frequency and called CQ in the FEC mode. (It is usual practice to call CQ in the FEC mode and switch to the ARQ mode once communi-



Photo B. AMT-1 output display sample on a 40-column computer.

cation has been established.) There was no reply. I tried again in a few days when the band conditions improved and met with success—I contacted WB2VJN running AMTOR on an IBM-PC using a homebrew interface.

The copy was flawless. Not a single error (except typographical ones) appeared on the copy. The ARQ mode-the one which waits until the other station's computer acknowledges correct reception of the data before sending more datamakes it very difficult for an error to creep through. Of course, if the band dies out completely, both stations will be waiting forever for the other station to reply (although, I would imagine, one would catch on after a little while). Just as with any other mode, if the signal Isn't there, it can't be copied. But If conditions are bad and copy would be rough with conventional RTTY, AMTOR can get through-it would just slow down a bit.

Unfortunately, there isn't (as of this writing) much in the way of software support for the unit. Although one can probably get by nicely with a standard modem control program, it is nice to have a custom-tailored ham-radio communications program. Be sure you have the necessary programming skills to control your computer's RS-232 serial port (this can often be done easily in Basic). I was able to get the AMT-1 running on an Apple II, an Atari 400, and an IBM-PC without too much difficulty. Certainly, the necessary computer programming is well within the abilities of even the most casual computer hobbyist.

Based aroung a 6800 microprocessor, the AMT-1 is of sound design. All the parts are off-the-shelf TTL and linear. The metal enclosure effectively shields out any RFI that the TTL circuitry might generate. I was able to dectect absolutely no RFI on a receiver a few inches from the unit.

I found the AEA AMT-1 a pleasure to use. Not only did it make the transition to AMTOR easy to implement, but also it made conventional RTTY more enjoyable. Because the unit controls TiR switching, you can run KOX (Keyboard-Operated Transmitter). All you have to do to switch from transmit to receive is start typing. Oh, yes... the unit also sends CW at any speed from 1 to 100 wpm for those of you who still like to do things the "old-fashloned" way.

For further information, contact AEA, Inc., PO Box C-2160, Lynnwood WA 98036; (206)-775-7373.

Robert Swirsky AF2M Cedarhurst NY

ELECTRONICS IN YOUR POCKET

When I think of all the books I used to study for my "ticket," I just marvel at the fact that anything worthwhile ever happened. I used several college texts, license study guides, reference books, and stacks of back issues of 73. I really wanted to be successful in my venture. One thing I immediately learned is that too much information can be just as bad as too little. This idea is universal, whether you are studying to pass a test or just want to build a simple circuit. The main key is in limiting your resources to a few that you can really study; forget the library approach.

There are literally hundreds of good reference books on the market. The real problem is that the total number of these books is growing at an alarming rate. This leaves the average, uninformed, "I-want-to-learn-ham-radio-on-my-own" person with a very difficult problem. How does a

person cut through the glut of electronic reference books and select the one which will do the most good? Well, one thing which I will not attempt is to tell everyone which is the best. Instead, I will tell you about one text which has helped me in my work as an engineering technician and as a ham.

The book to which I'm referring is Electronics Pocket Handbook, by Daniel L Metzger. I will briefly describe this book, pointing out various aspects, good and bad, which I've encountered while using It. The Electronics Pocket Handbook is exactly that. It is just slightly longer than a 3" x 5" index card and not quite as wide. The size makes It ideal for briefcase, coat pocket, or purse. You don't have to worry about all the pounds of books usually associated with study.

The book is sectioned into seven separate chapters and an index. Chapter 1, "Definitions, Formulas, and Charts," contains information very similar to that found in the ARRL Handbook. It gives you information on Ohm's Law, inductors, capacitors, complex notation, power-supply formulas, etc. Other information which isn't so typical in this section is on Boolean formulas and thermal, geometric, and bridge formulas. These latter formulas can be very difficult for the lay person to pin down when needed.

Some very needed component information is contained in Chapter 2. The title. "Component Data and Characteristics." says it all. This chapter contains information on wire insulation, wire characteristics, popular connectors, conductivity of various conductors, color codes for resistors, capacitors, and inductors, etc. You will learn how to read component values from any passive component, whether vintage 1932 or 1983. You also will learn how to read MIL-STD resistor designations such as those used on NASA surplus boards. This chapter can provide the individual with new knowledge which can help refine his ability as a scavenger. If the information in this chapter is actively applied when purchasing from the surplus market, a great savings should be realized.

In Chapter 3, "Simplified Circuit Analysis and Design," we start getting into the meat of electronic theory. You will work with resistive circuits, learn about several popular network theorems such as Thevenin's, Norton's, and Miliman's, and the reciprocity theorem. You also will get into general circuit analysis, nodal analysis, and ac circuit analysis. In spite of the fact that some of these names may sound a bit scary, don't worry. The author has tried to make these as painless as possible and still maintain some authority in the text. If this information is not enough, you will also find transistor-biasing formulas and a small section on op-amp design. This is a good section to work through to help prepare your mind for any type of circuit analysis. Especially on tests!

In Chapter 4, "Units, Conversions, and Constants:" we are introduced to the international system of units-Systeme internationale d'Unites (SI). This is the system which the international engineering community has adopted as a standard. This chapter goes into detail on the various aspects of the system. You will learn shortcuts and keys which will enable you to use the system more efficiently. In addition to this, you will learn how to perform various unit conversions, such as quarts to liters or meters to feet. There is also a section on the most-frequently-used constants from science. These aren't all pertaining to electronics. This particular chapter has quite an appeal to all students of the sciences.

In Chapter 5, "Standards, Symbols, and Codes," you will learn about broadcasting frequency standards, wavelengths, electrical wiring practices, hardware standards, etc. included in the mechanical section is information on drill sizes, metal gauges, and general hardware tidbits. There is also a review (briefly) of teleprinter codes such as Baudot and ASCII. Sorry, no SITOR or AMTOR in this section. If some readers are still latent CB hounds, then the 10-code listing should prove useful for them. This chapter, especially the hardware information, should be interesting to the avid home-brewer.

In Chapter 6, "Test Procedures," you will learn how to test meters, batterles, Inductors, capacitors, inductor Q, and resistors. You will learn the ins and outs of semiconductor testing and even get into the mechanics of amplifier testing. If home-brew isn't really your bag, you still could do well to read this even if you only occasionally service your rig.

Finally, in Chapter 7, "Glossary of Electronic Terms," we have a very comprehensive listing containing most of the commonly-used technical terms. This should be especially appealing to the newcomer. This will help give everyone, an understanding, even if only rudimentary, of a term and its various associations. Several popular books neglect including this kind of information. They treat it as an unnecessary option. I disagree with that line of thinking totally. This little text has a full sixteen pages of definitions and terms which are extremely useful as well as educational.

Another aspect of this book which I like is the Index. Most people, including several new technical writers, take this section of a book for granted. It is very frustrating when you need to find something in a hurry and it takes an hour. The lack of an index is a good indication that the author really doesn't care about the readers at all. This isn't the case with this book. The index could stand to be a little more comprehensive, but the book is organized in such a manner that finding most subjects is easy anyway.

Electronics Pocket Handbook is published by Prentice-Hall, Inc. In case you want your local bookstore to order you a copy, the ISBN number is: 0-13-251835-X. (This usually is needed when they have to place a special order.) You can expect to pay about nine dollars for this. In my opinion, it is probably the best nine-dollar investment I've made in quite a while. Now I can think about upgrading no matter where I may be. This is an excellent companion on trips when you can't carry tons of regular references with you.

Samuel G. Williams WB5YNI Hiawatha IA

THE PRIVATE PATCH BY CONNECT SYSTEMS

The Private Patch II, by Connect Systems, is perhaps the most sophisticated simplex autopatch yet to hit the market. Hook the Private Patch up to an FM transceiver and a telephone and you're on the air with your own autopatch. It puts a simplex patch, control system, and CW IDer all in one box.

This patch is different from the other simplex patches on the market because it uses a VOX circuit for control rather than a sampling system. Most simplex patches are designed to switch the transmitter off every few seconds to quickly sample the receiver input. Since the system is simplex (it's either talking or listening, but not

both at once), that's the only way they can tell if a mobile station wants to talk—If a carrier is present during the sampling period, the system stays in receive mode to allow the mobile to talk.

The sampling method works, but it has two disadvantages. First, it's annoying to listen to the squelch tails that are generated every time the unit samples. Second, and more important, the transcelver used with a sampling system has to be able to switch between transmit and receive very rapidly. That means that radios with relay switching won't work, and most radios will need modifications to speed up the action of the squelch circuit.

The Private Patch II avoids these problems by using a sophisticated VOX circuit to control T/R switching. If the party on the telephone stops talking for more than about a half second, the unit switches from transmit to receive. The mobile unit can break in during the normal pauses that occur in conversation. To provide backup control, if the unit stays in transmit mode for more than about 20 seconds, it automatically goes back to receive for about 3 seconds. Thus, the mobile user will never be locked out for more than 20 seconds.

The VOX switching system also allows the Private Patch to work through repeaters since the repeater carrier won't lock the system into receive mode. Because the transceiver switches less often and stays in the receive mode longer, the stringent T/R-switching requirements of sampling-type patches are avoided.

The only disadvantage of the VOX switching system in the Private Patch is that mobile access is also VOX controlled. In other words, you can't capture the system merely by mashing down on the mike button. You actually have to say something before you're in control

The Private Patch II works very well. It took only a few minutes to get everything hooked up to my Midland 220-MHz radio, and no internal modifications to the radio were necessary—all the connection points were available on the back panel of the Midland. The Private Patch needs only microphone, keying line, and speaker audio connections.

I did have one problem with the unit—the Midland T/R relay draws over 100 milliamps, and a power surge when the relay closed fried the switching transistor in the Private Patch the first time the transmitter switched on. The Midland relay probably draws more current than the average, so this problem shouldn't commonly occur, and the factory reports that they know of no other such failures. My solution was to use the keying circuit to drive a smaller reed relay which in turn drives the T/R relay.

Once the keying problem was taken care of, the Private Patch played well. It was very easy to adjust the audio-level controls to get the proper volume levels, and everyone who used the unit (both radio and landline users) commented on the good audio quality.

The patch has a built-in tone decoder, and control codes are provided for access, disconnect, and timer-reset functions. Front-panel switches allow long-distance dial restriction (by shutting the patch off if the first number dialed is a 1 or 0) and ringback enable and disable.

If the ringback circuit is enabled, the unit will operate as a reverse autopatch. When the telephone rings, the Private Patch will identify once and the telephone can be answered by sending the timer-reset code. The system then works as if a normal autopatch call had been placed.

A lot of thought went into the design of the Private Patch II. Many features that

aren't strictly necessary but are sure nice to have are included. For example, the IDer operates during the last minute before timeout so that the mobile operator has plenty of advance warning to reset the timer. The access codes can be changed to protect system security.

The reverse-patch ringback is disabled if a QSO has been in progress on the channel within the last few moments (so you won't get other users of the channel upset with your machine). A tone-to-rotary converter is built in so that the patch will work on any phone line.

All In all, the Private Patch II is quite an amazing box. The VOX switching system makes it unique, and it has all the other features necessary to make it a thoroughly practical machine. For more information, contact Connect Systems, PO Box 4155, Torrance CA 90510; (213)540-1053.

John Ackermann AG9V Green Bay WI

THE TR-720 VHF TRANSCEIVER

Many hams and readers of 73 are pliots and aircraft owners. Therefore, this month we present a review that deals with an AM transceiver for use on the 118–136-MHz aircraft band. We think that this unit will find much favor with pilots because of its small size, light weight, and extreme portability, providing a versatility seldom seen in aircraft equipment, with little if any sacrifice in performance.

One of life's nicer surprises is to find a piece of equipment that performs better than you expected. The TR-720 aircraft-band VHF transceiver is one of these; it is a joy to own and operate.

Although Communications Specialists is well known for its line of amateur and commercial encoders and decoders, it is less well known for its other products...Including this new venture into two-way communications equipment for the aircraft owner and pilot...and it is a real pleasure to find that the equipment is almost ideally suited to fill a real need.

The VHF aircraft band extends from 118 MHz to 136 MHz and—unlike other VHF communications services—it is AM, not FM. In the frequencies encompassed by this band, there exist 200 navigation "channels" and 720 communications "channels."

The navigation channels are occupied by VORs (ground-located VHF Omni Ranges), stations which permit a pilot to home in from any point of the compass by means of an instrument mounted on the instrument panel. All the pilot needs to do is tune in the station, center the needle by turning the OBS (Omni Bearing Selector), and then fly the plane on that bearing so that the needle remains centered.

This, of course, is an oversimplification, but it will serve to describe one general way in which the VOR system is used. The instrument tells the pilot whether the radial that he is on is To or From the station (there are 360 radials...one for each full degree of the compass). When the plane passes over the station, the "To-From card" flips over.

While the pilot flies the needle, he also can listen to the VOR station itself and receive the Morse-code indentifier plus voice transmissions of weather and other information needed to fly safely to his destination.

The 720 communications channels are used for the purpose of talking to airport control towers, Unicom stations, other aircraft, Flight Service Stations, and the like. It was the advent of equipment having su-

SPECIFICATIONS

Model Frequency range

Number of channels

Frequency stability

Power consumption

Antenna type

Battery type

Size

Weight

RECEIVER

Sensitivity

Selectivity

Audio output

Squelch sensitivity

I-f Image rejection

Spurious response

TRANSMITTER

Rf output power

Modulation type

Frequency stability

Spurious & harmonics

Receiver type

Frequency determination

TR-720 airband transceiver
118.000 MHz-135.975 MHz (Com
band), receive and transmit
108.000 MHz-117.975 MHz (Nay band),

receive only

720 (Com band) with 25-kHz spacing 200 (Nav band) with 50-kHz spacing Microprocessor-controlled CMOS phase-

locked loop

±.001% (-10°C to +60°C) ±.002% (-30°C to +60°C)

± .002% (– 30° C to 39 mA squelched

165 mA @ 300 mW audio output

650 mA transmit

Flexible rubber 50-Ohm unbalanced type 9.6-V/450-mAh nicad battery pack (CS-15), or 9.6-V/750-mAh nicad battery pack (CS-18), or 12-V, 8 AA alkaline batteries (CS-19) 6.6" (169 mm) x 2.6" (64 mm) x 1.5" (38 mm)

1.2 lb. (19 oz./.544 kg) with battery

Dual conversion superheterodyne Less than .5 uV for 10 dB (S + N)/N (Com

band)

Less than 2 uV for 10 dB (S + N)/N (Nav band)

60 dB at 25 kHz

.5-uV threshold, FM noise type* 500 mW maximum, less than 10% THD

Greater than 60 dB Greater than 60 dB

1 Watt nominal, 800 mW minimum,

3 Watts PEP into 50-Ohm load ± .002% (-30° C to +60° C) Greater than 60 dB below carrier 6A3, high level Class B collector

modulation (AM)

perior selectivity and frequency stability that made possible the increase in the number of communications channels from 90 to 360 and then to 720... permitting expansion and growth of the system to meet current needs.

Most of the users of larger aircraft, including the airlines, corporate fleets, and the like, have several sets of VHF communications and navigation radios on each airplane. Some are redundant, for safety's sake, while others are needed for simultaneous reception/transmission and navigation. All of the equipment is expensive, and much of it is beyond the financial reach of many private pilots and aircraft owners who fly for fun. As a consequence, many smaller airplanes have only one radio: a Navcom unit that combines both functions of communications and navigation. Often, these radios are older tube types and are limited in channel spacing to only 90 or 360 channels, thus limiting-or even prohibiting-many smaller. privately-owned aircraft from full use and enjoyment of the national air-traffic system.

Pilots of saliplanes (gilders), balloons, experimental and home-built aircraft, fire-fighters, ultralights, and other types of aircraft may have a sometime need for VHF communications and navigation radios and often cannot or will not spend the larger amounts of money required for permanent installation of expensive equipment.

Communications Specialists, recognizing the need in this area for small, light-weight, inexpensive rigs, has introduced to the marketplace its new TR-720, a hand-held transceiver of outstanding performance. Here is a unit that is crystal-synthesized to cover all 720 communications channels and 200 navigation channels; it operates on an internal nicad bat-

tery pack which can be recharged from either an automobile or aircraft dc supply of between 12 and 28 volts or from the 115-volt-ac house mains. Further, and still more convenient, the TR-720 has the standard aircraft BNC connector for its antenna. Thus, a coaxial cable may be connected from the aircraft antenna, or the standard flexible (rubber ducky) supplied with the unit may be used.

Just a tiny handful, weighing only 1.2 pounds with the standard nicad battery pack, and measuring 6.6 x 2.6 x 1.5 Inches, the TR-720 has glant-size performance. Receiver sensitivity is exceptional, and power output on transmit is nominally 1 Watt dc or 3 Watts PEP, voice modulated. An adapter for an external microphone and headset is provided for those who prefer them for use in the cockpit. One of the prime advantages of a transceiver operated from its own supply is the obvious backup capability it provides in case of failure of the aircraft radio system. Almost as important is the capability of portable operation, where FAA (Federal Aviation Agency) personnel may need to direct traffic from an emergency runway, a helicopter landing pad, or another location where no permanent radio installation exists.

The pilot of a sailplane, which often has no permanent battery or radio setup, would find the TR-720 ideal for his purposes...for contacting the tower at a controlled airport, for example, when wishing to land. The TR-720 is easily and handlily carried aboard and mounted by means of its belt loop on the leather carrying case. It can be suspended from the belt, of course, and carried portable in that manner as well. One can visualize stuffing the hand-held into an available glove box (it fits into the glove compart-

ment on my Cessna 150 with plenty of room to spare) or mounting it temporarily somewhere in the vicinity of the instrument panel for quick reference and use.

I was very surprised to find that the TR-720 was hearing stations in flight better than my standard aircraft radio—which, by the way, is one of the older 90-channel types, unable to receive or transmit on the split frequencies in common use today. Thus, for me, the TR-720 allows access to airports and FAA communications facilities that I could not otherwise use.

The TR-720 receives even distant stations on its flexible antenna Inside the cabin of my all-aluminum Cessna. I have not yet found the need to use the aircraft external antenna for receiving, but I have discovered that it works best on the handheld for transmitting to distant stations... as you would expect, considering the amount of output power.

Enjoying the TR-720's internal battery pack and its isolation from the aircraft electrical system, I find that much of the hash generated by my engine and its accessories is absent when I try to hear another station. This means that I don't have to ask for a repeat of the transmission, and it certainly saves wear and tear on the ears. I seem to be approaching the situation where I plan to use the TR-720 as my main transceiver for communications and my aircraft radio for navigation only!

I took the TR-720 on vacation with me and found that it attracted attention wherever I went. One FBO (fixed base operator) told me that It was "... the best-sounding radio on the field!" Another told me that he wanted to stock them for his local clientele and for transient visitors to his field. The pilots themselves are really interested, and two local pilots who fly a lot of formation with their Piper Cubs want a pair of them for plane-to-plane communications.

Civil Air Patrol personnel would find these units ideal for search-and-rescue operations. In particular, a recent airplane crash at a remote mountaintop site required ground search teams. Their work and coordination from aircraft in the area might have been greatly simplified and speeded up had some TR-720s been available.

One of the features you will like is the twist-off battery pack, permitting almost Instant replacement by a fresh pack when needed, while the original pack is being recharged. Battery packs of 450-milliampere-hour capacity are standard but 750-mAh packs are available. Supplied accessories include: flex antenna (rubber ducky), simulated leather case, 115-V-ac wall charger, dc charger (cigarette-lighteradapter plug), earphone, and operating manual. Available accessories are: alkaline battery pack (batteries not supplied), nicad rapid charger (1 hour), desktype drop-in charger, 220-V-ac wall charger, simulated leather case for use with larger battery pack, remote handheld speaker/mike, cable adapter for PJ-068 and PJ-055 to TR-720 and cable adapter for U-174 to TR-720.

An outstanding feature of the TR-720 that I have not seen on similar units for aircraft-band use is the 3-position memory. You can store three different frequencies in the memory merely by setting them, one at a time, on the dial, switching to memory locations 1, 2, or 3, and pushing the memory-store butfon. This way, for example, you could set up in advance an ATIS frequency, a control-tower frequency, and a ground-control frequency. Perhaps you might want approach-control, tower, and

departure-control frequencies. Another possibility would be the split-frequency or half-duplex option where you set a Nav frequency (VOR, for example) into memory and a Com frequency on the dial. Then you can communicate with a Flight Service Station and hear its reply over the VOR station closest to your location.

Frequency selection is by thumbwheel

dials, and a noise-type squelch circuit as used on FM equipment is incorporated so that you don't have to listen to "white between transmissions. This saves the battery, too.

The TR-720 employs 1 microprocessor, 10 integrated circuits, and 50 transistors. Transmitter and receiver incorporate 12 varactor-tuned stages which track with the selected frequency for optimum performance from band-edge to band-edge. The TR-720 is ECC Type Accepted (US) and DOT Certified (Canada).

Communications Specialists places a 1-year warranty on the TR-720, with a quaranteed 72-hour turnaround for repair or replacement

Aircraft owner's net price is \$795, in-

cluding the standard supplied accessories described above. For further information, call or write Communications Specialists, 426 West Talt Avenue, Orange CA 92665-4296; (800)-854-0547; (714) 998-3021. Dealer inquiries invited. Reader Service number 485.

> Jim Gray W1XU 73 Staff

CONTESTS

Robert Baker WB2GFE 15 Windsor Dr. Atco NJ 08004

ARRL SWEEPSTAKES CW

Starts: 2100 GMT November 5 Ends: 0300 GMT November 7 Phone

Starts: 2100 GMT November 19 Ends: 0300 GMT November 21

US and Canadian stations work other US and Canadian stations using the 1.8through 28-MHz bands, excluding 10 MHz. Operate no more than 24 of the 30 hours with on/off times noted clearly in your log. Listening time counts as operating time. Operating categories include single operator and multi-operator with a single

No cross-mode contacts will be allowed and each station can only be worked once. regardless of frequency band. A transmitter used to contact one or more stations may not subsequently be used under any other call during the contest period (with the exception of family stations where more than one callsign is assigned by FCC/DOC). One operator may not use more than one callsign from any given location during the contest period. The use of two or more transmitters simultaneously is not allowed.

EXCHANGE

Consecutive serial number, precedence (A if you run 150-W output or less, B if more than 150 W), your callsign, check (last two digits of the year you were first licensed), and your ARRL section

EREQUENCIES

CW: 1800-1810, 3550-3650, 7050-7100 14050-14100, 21050-21100, 28050-28100, Novice: 3710, 7110, 21110, 28110.

Phone: 1855-1865, 3850-3950, 7200-7250, 14250-14300, 21300-21400, 28550-28650

SCORING:

Count 2 points for each completed 2-way QSO. Multipliers are each ARRL section plus VE8/VY1 (74 maximum), KP4, KV4/KP2, and KG4 stations are in West Indies section, while KH6 and other US possessions In the Pacific count as the Pacific section. Final score is QSO points times the number of ARRL sections (plus VE8/VY1).

AWARDS.

Certificates to the top single-operator CW and phone scorers in both the A and B categories in each ARRL section, and the top multi-operator entry in each ARRL Divi-

ENTRIES:

Contest forms (log sheets, summary sheet, dupe sheet) are available from ARRL HQ for an SASE. Official forms are recommended. Any entry claiming more than 200 QSOs must submit duplicate checking sheets. Incomplete or late entries will be classified as checklogs. Logs should include dates. QSO times, exchange sent/received, band, and mode, Postmark your entry for either mode by December 21 and send it to: ARRL, New-Ington CT 06111.

Each entrant agrees to be bound by the provisions as well as the intent of the official ARRL rules, the regulations of his licensing authority, and the decisions of the ARRL Awards Committee. The usual disqualification rules apply.

INTERNATIONAL POLICE ASSOCIATION CONTEST 0000-0300, 0700-1000, 1400-1800 GMT

November 5-6 Sponsored by the IPARC, this contest will be conducted on both CW and phone.

Signal report and serial number, US stations also send state; IPA member send

FREQUENCIES

Phone: 3.650, 3.775-3.8, 7.075, 14.295, 21,295, 28,650

CW: 3.575, 7.025, 14.075, 21.075, 28.075.

SCORING:

Non-IPA stations can work IPA members only, and each station can only be worked once per band. 4 points per QSO on 20, 15, and 10 meters. Each QSO on 40 and 80 meters counts two points, except DX, which is worth 8 points per QSO.

ENTRIES:

Mail entries by December 31 to: Anton Kohten DK5.IA PO Box 40 01 63, 4152 Kempen 1, Federal Republic of Germany

RESULTS

1983 RESULTS **WORLD CHAMPIONSHIP RTTY CONTEST** Sponsored by The RTTY Journal and 73

Indicated are callsign, points, multipliers, and total score.

- **World champion
- "DX champion
- *W/VE champion

State, provincial, and DX country awards will also be given in recognition of this year's accomplishments

Single Operator, Multi-Band

	,				
· · · G3ZRS	_	164	—96	_	15,74
"SM6ASD	_	167	-92	-1	15,364
XT2AU	_	163	-85	-1	13,855
14JXE		158	-84	1	13,27
*W3BE	_	163	-66	_1	0,758
W3FV	_	147	-73	_1	0,73
.SM5FUG	_	123	-74	_	9,102
IT8EAI	_	101	-87	_	8,787
K4AGC	_	118	-66	_	7,788
TO6AUS	_	101	62	_	6,262
N7AKQ	-	139	-45	_	6,255
G4NJW	_	96	-58	_	5,568
K6WZ	_	89	-55	_	4,895
			-55		
			-55		
WOLHS					
			-38		
SM7LSU					
JA1BYL					
W2DNO					
			-38		
N5DSK					
GW3EHN	_	64	-36	_	2,304
NN6F	_	52	-44	_	2,288
SM3EZD					
SM5AAY	_	63	-34	_	2,142
ON7EP	_	55	-37	_	2,035
VE3ZX	_	52	-39	_	2,028
K4JAF	_	51	-37	_	1,887
TO6HKR					
OK1AWC					
VE7VP	—	42	—28	_	1,176

W7CBY - 36 - 30 - 1,080 VK2BQS - 40-17- 1,080

- 45 -22 -SM6AEN - 35 -27 -

- 31 -27 -G4KHX - 40-17-

TI2DO

KE6T

G4OJJ	_	34 -12 -	408
KJ2N	_	15 —14 —	210
LU3DSU	_	13 - 9 -	117
SM3GT	_	27 - 4 -	108
YR3ON	_	41 - 1 -	41

Single Operator, 20 Meters

***KJ8N	—71	-35	-2,485
**YB2BLI	-65	-22	-1,430
GM4KHE	-54	-22	-1,188
DVEACD	42	27	4 404

Single Operator, 15 Meters

***K7NO	_1	41	-59	—8	,319
**OH5YW	_	83	-24	-1	,992
JA3EOP	_	50	-28	-1	,400
I5AZX	_	58	-17	_	986
YO3RF	_	26	-12	_	312

Single Operator, 10 Meters

***OH5IY -10 -10 -100

Multi-Operator, Multi-Band

AT8HO***	_	143	—70		10,010
*KA4MKG	—	113	-57	7 —	6,441
W8UPU	_	69	-39	-	2,628
VE3NEX	_	52	-37	7 —	1,924
**OK3KGI	_	57	-29	-	1,653
OK3RJB	_	48	-27	_	1,296
OK3RMW	_	45	-22	_	990
OK10AZ	_	26	-23	3 —	598
OK3KII	_	34	-21	—	522
ОК3КХМ	_	11	— δ	3 —	88
Multi Onorate		00.4			

K8EX	—195 —6	32 - 12,210
"SL5AR	-178 - 2	29 — 2,262

Check Logs

DL1VR, OZ6SM, N6ELP, W6JOX

CALENDAR

Nov 5-6	International Police Assn. Contest
Nov 5-7	ARRL Sweepstakes—CW
Nov 6	DARC Corona 10-Meter RTTY Contest
Nov 12	OMISS QSO Party
Nov 12-13	Delaware QSO Party
Nov 12-14	CQWE Contest
Nov 12-14	Rhode Island QSO Party
Nov 19-21	ARRL Sweepstakes-Phone
Dec 3-4	ARRL 160-Meter Contest
Dec 10-11	ARRL 10-Meter Contest
Jan 7	73 40-Meter World SSB Championship
Jan 8	73 75-Meter World SSB Championship
Jan 14-15	73 160-Meter World SSB Championship
Jan 14-15	Hunting Lions In The Air Contest
Feb 4-5	South Carolina QSO Party
Feb 18-19	America Radio Club International DX Contest
Feb 18-19	YL-ISSB Commo System QSO Party—Phone
Feb 25	RTTY World Championship Contest
Mar 17-18	YL-ISSB Commo System QSO Party—CW

RESULTS

15NPH, 4M3AZC, K3TUP, AND KC5NQ: 1983 WORLD 40-METER CHAMPS

Multi-band contests are won or lost on the 40-meter band! All the top contest stations will admit that a decent score on 7 MHz may spell the difference between first- and second-place finishers. Why is it, then, that 40 seems to be the forgotten band by so many? The answer is congestion!

Broadcast signals make for a very hectic experience if one is to roost on 40. That is why 73 recognized the rare opportunity to prove that 40 meters can in fact be the born-again band it used to be. With all the elements against you, the top contester would be the one who could survive the strong carriers of AM broadcast stations overseas, the sometimes unbearable QRN that even the best filter cannot overcome. To top that, to obtain those necessary multiplier points, here's a band that tests your skill in crossband operation once and for all.

The majority of contestants indicated that the DX paths were excellent to most parts of the world, particularly to Europe and Asia. Stations added a host of new countries to their DX tailles! Stateside conditions were reported to be the best they had been in many weeks.

After all the smoke had cleared and the entries were received and tallied, KC5NO led the pack for single-operator stations. This championship station managed 756 OSOs in less than 16 hours of 40-meter operation and worked 61 states and provinces and 45 DX-countries. A distant second was afforded Florida contester N4BAA, who accumulated 559 OSOs, 55 states and provinces, and 48 countries. For single-operator DX stations, our good friend 4M3AZC of Venezuela became the world champ with 578 OSOs, 53 states and provinces, and 56 DX countries for his total. K3TUP took top honors for all WIVE multi-operator stations with a super tally of 1214 OSOs, 58 states and provinces, and 56 DX countries. DX multi-operator honors went to I5NPH, who worked 667 OSOs, 43 states and provinces, and 64 DX countries.

Of all the classes and categories in the 40-meter contest, the W/VE multioperator final heat was the closest. Close on the heels of champion K3TUP was 160-meter contest winner K8ND with 1129 QSOs, 57 states and provinces, and 37 DX countries. Only 85 QSOs and roughly 6,500 points separated these first- and second-place finishers.

In the W/VE single-operator class, statlons with 500 or more QSOs were KC5NQ (756), KA1XN (718), KC3N (702), KG1E (676), KM9P (618), K4HAV (617), KC8JH (600), WA0IDK (590), N4BAA (559), KA1GHR (523), WA4SVO (506), and KA1WJ (503). DX single-operator statlons with 400 or more QSOs included 4M3AZC (578), IO3MAU (478), IO6NOA (438), OK1TN (438), and CT4NH (426). In the multi-operator class, 500 or more QSOs were obtained by K3TUP (1214), K8ND (1129), K5LZO (813), KC0SZ (764), I5NPH (667), I4OUT (648), N8EKE (592), and K80QA (584).

Well over 50% of the 40-meter contestants worked 40 or more states and provinces, many stating that they worked all states in the 24 hours of the contest period. KC4NQ managed to get a clean sweep of 61 state and provincial multipliers, the only one in the contest to get all W/VE multipliers possible. KA1XN lacked only 2 to match KC5NQ's feat, while KC8JH, VE3ICR, K3TUP, and KC0SZ all recorded 58 out of the 61 possible states and provinces.

In DX, the following stations worked 30 or more DX countries: I5NPH (64), I4OUT (62), OK1TN (59), 4M3AZC (56), I06NOA (56), I03MAU (50), N4BAA (48),

CT4NH (47), KC5NO (45), VE3ICR (42), PY5EG (41), DL8NBE (41), OK1AYP (38), K8ND (37), DA1TN (37), KG1E (36), K5LZO (35), KC0SZ (33), VO2CW (32), KA1GHR (32), KA1WJ (32), and KA2CDE (31).

With January just around the corner, it's time to prune those dipoles and inverted vees and get ready for the 3rd annual event. If propagation is in our favor and we can get the word out to as many DX stations as possible, we expect to see some fantastic scores and some new world records!

You still have time, so send in your 1984 contest forms today! Enclose an SASE and send your request to Dennis Younker NE6I, 40-Meter Contest Chairman, 43261 Sixth Street East, Lancaster CA 93535.—Bill Gosney KE7C.

40-METER CONTEST SOAPBOX

KG1E: "Will try a beam next year instead of a dipole at 50 feet!"

KA1RC: "A great contest. New delta loop worked well on DX. Blew the linear halfway through the contest though. Will definitely be back next year despite problems this time around."

KC3N: "Working 35 DX stations split frequency without an external vfo gives one fast fingers! Loads of fun but couldn't the broadcast stations QSY? Age 16. See you next year."

K3TUP: "24 hours is a perfect amount of time for any contest."

WA3SPJ: "Enjoyed both 40- and 80-Meter Contests a lot.

N4BAA: "Great contest again! Next year will have 4 elements at 140 feet."

WC4E: "Thank you, 73, for the opportunity to participate in such a fine contest." WD4RCO: "Most enjoyable contest. Good representation of DX, most of whom willingly listened up."

W4TMR: "This is my first 40-Meter Contest, can't walt until next year!"

KC5NQ: "The DX was better this year and the band was in extremely good shape. Thank you, 73 and the contest bunch."

N7BUP: "Had a great time—wish I had better prepared to go the distance overnight."

KC7PA: "Next year, I definitely am getting a second vfo. Hate to miss the rare DX. Got five new countries, however. How about a low-power category next year? Otherwise, I'll need an amp."

K9GDF: "My wife (N9DIJ) almost beat me in this contest."

KCOSZ: "Would have been nice to have Europeans listening upband. We had several openings but no one would listen up frequency, it seemed."

EA1OF: "A great opportunity to work new states or countries."

HI8GB: "Thanks very much for an interesting phone contest—It's long overdue!"

IO6NOA: "I expected more participation from Europeans. Many asked what contest was going on."

VE3ICR: "Didn't expect to be so involved in the contest. However, once I started, it was hard to quit!"

40-METER ANTENNA SURVEY

	1982	1983	Delta loop	9.3	3.8
Dipole/inverted vee	39.8%	44.6%	2-element wire beam	2.3	.0
1/4 - or 1/2 - wave vertical	13.9	4.8	3-element yagi	2.3	3.8
Trap vertical	9.3	11.5	4-element yagi	.0	5.7
2-element yagi	7.0	9.6	Longwire	.0	4.9
1/4 -wave sloper	4.6	.9	Log periodic	.0	.9
1/2 -wave sloper	2.3	6.7	2-element guad	2.3	.0
2-element delta loop	4.6	2.8	Bobtail curtain	2.3	.0

DARC CORONA 10-METER RTTY CONTEST Starts: 1100 GMT November 6 Ends: 1700 GMT November 6

This is the last of four tests during the year sponsored by the DARC eV to promote RTTY activity on the 10-meter band. Use the recommended portlons of the 10-meter band. Each station can be contacted only once. Operating classes include single-multi-operator and SWL printer.

EXCHANGE:

Each completed 2 x RTTY QSO is worth 1 point. Multipliers include the WAE and DXCC lists, each US state, and each district in VE/VO and VK. The final score is the total QSO points times the total multiplier.

AWARDS.

Appropriate awards to the leading stations in each classification, assuming reasonable scores.

ENTRIES

Logs must contain name, call, and full

address of participants. Also show class, times in GMT, exchange, and final score. SWLs apply the rules accordingly. Logs must be received within 30 days after the test. Send all entries to: Klaus K. Zielski DF7FB, PO Box 1147, D-6455 Erlensee, West Germany.

DELAWARE QSO PARTY Starts: 1700 GMT November 12 Ends: 2300 GMT November 13

Sponsored by the Delaware ARC. Stations may be worked once per band and mode for QSO and multiplier credits.

EXCHANGE:

CW—1805, 3570, 7070, 14070, 21070, 28070

SSB—1815, 3975, 7275, 14325, 21425, 28650.

Novice-3710, 7120, 21120, 28120.

SCORING

Delaware stations score 1 point per QSO. Multiply total by the number of ARRL sections and DX countries worked.

Others score 5 points per Delaware station worked. Multiply total by the number of Delaware countles worked on each band and each mode (maximum of 36 multipliers possible).

ENTRIES AND AWARDS:

Appropriate awards will be given to the top scorers. In addition, a certificate will be given to all stations working all three Delaware counties. If you work all three counties and want the WDEL Award, send two 20-cent stamps and an address label

'Malf logs by December 16 to: Charlie Sculley AE3H, 103 E. Van Buren Avenue New Castle DE 19720. Send an SASE for a copy of the results.

OMISS QSO PARTY Starts: 0000 GMT November 12 Ends: 2400 GMT November 12

Sponsored by the Old Man International Sideband Society. Work stations once per band. Exchange RS, name, state, and OM number (if any). Count 5 points per OMISS member, 2 points per nonmember. Multiply by total states, VE provinces, and DX countries. Plaque to top-scoring member and nonmember. Certificate to top-scoring members in each US call district, Mall logs.

and cover sheet within 15 days to: Rich Besitka KA1HGY, 480-B Radmere Road, Cheshire CT 06410. Include an SASE for further information.

CQWE CONTEST Starts: 1900 GMT November 12 Ends: 0500 GMT November 14

Sponsored by the Bell System Amateur Radio fraternity, the contest contains various sessions during the period. The contest is open to present and retired employees of Bell, Western Electric, AT&T, and subsidiarles of AT&T. Contact your local interworks coordinator for logs and complete rules, or write to: Phil Pearson WA1LXY, Bell Telephone Laboratories, 1600 Osgood St., North Andover MA 01845, Room 3E-46. Telephone: (617)-681-6179 (work) or (603)-362-4297 (home).

RHODE ISLAND QSO PARTY 1700 GMT November 12 to 0500 GMT November 13 1300 GMT November 13 to 0100 GMT November 14

Sponsored by the East Bay Amateur

Wireless Association. RI stations work other RI stations and the rest of the world. All others work only RI stations. The same station may be worked twice on each band, once on phone and once on CW.

EXCHANGE:

RS(T) and state, province, country, or RI city.

FREQUENCIES:

Phone—3900, 7260, 14300, 21360, 28600, 50.110, 144.2, 146.52.

CW—1810, 3550, 3710, 7050, 7110, 14050, 21050, 21110, 28050, 28110.

Use FM simplex, no repeaters.

SCORING:

All stations score 2 points per phone QSO, 3 points per CW QSO, and 5 points for QSOs with Novices and Technicians. RI stations multiply QSO points by the number of states, provinces, and countries worked. Others multiply total QSO points by the number of different RI cities and towns worked (39 maximum).

AWARDS.

Certificates awarded to top-scoring station in each state, province, country, and RI county, plus top-scoring Novice and Technician in RI and out of state.

ENTRIES:

Logs must show date/time in GMT, call, exchange, band, and mode. Include your name, call, malling address, club affiilation if any, total QSO points, multipliers claimed, and final score. Entries must be postmarked no later than December 15 and addressed to: East Bay Amateur Wireless Association, PO Box 392, Warren RI 02885. Include an SASE for results.

3RD ANNUAL 40-METER WORLD SSB CHAMPIONSHIP 0000Z to 2400Z January 7, 1984

SPONSORED BY:

73: Amateur Radio's Technical Journal.

MISCELLANEOUS RULES:

Work as many stations as possible on 40-meter phone during the specified times of allowable operation. The same station may be worked once. Crossmode contacts will not count. Single-operator stations may operate a total of 16 hours. All multi-operator stations may operate the entire 24-hour period. Off periods must be noted in your log(s) and on your summary sheet. Off periods are no less than 30 minutes each.

OPERATOR CLASSES:

(A) Single operator, single transmitter, phone only. (B) Multi-operator, single transmitter, phone only.

EXCHANGE:

Stations within the continental 48 United States and Canada transmit an RS report and state, province, or territory. All other stations, including Alaska and Hawaii, transmit RS report and DX country.

POINTS:

5 QSO points for contacts with W/VE stations located within the continental 48 United States and Canada. All other contacts score 10 points each. List points for each contact on your log sheet(s).

MULTIPLIERS:

1 multiplier point is earned for each US state, 48 maximum (a District of Columbia contact may be substituted for a Maryland

1983 RESULTS 40-METER WORLD SSB CHAMPIONSHIP

Indicated are callsign, QTH, QSOs, states/provinces worked, DX worked, and total score.

"World champion

*State/province/country champion

W/VE Single	Opera	tor		KJ2N	⊢NJ	- 48 -	-23 13	- 2,376	
··KC5NQ	-TX	-756 -61	45 86,496	*NL70		- 58 -	-34 - 3	- 2,257	
'N4BAA	-FL		-48 -65,714	KC8F				- 2,046	
*KA1XN	-MA	—718 —59	-27 -65,188		JG/4 —VA			- 1,775	
KG1E	-MA	-676 52	-36 -64,592	*W5EI				- 1,710	
*KC3N	-PA	—702 —55	—27 —60,926	KD4F				- 1,664	
*VE3ICR	-ONT	-467 -58	—42 —57 ,200	· Wolz				- 1,593	
·KC8JH	-OH	-600 -58	—29 —57,072	KB9F				- 1,508	
*K4HAV	—GA	-617 -55	—22 —50,127	WC4I			-22 — 1 -19 — 0	- 1,219	
.MAGIDK	-MN		—23 —48,901	K9GE KB7N			-19 - 0 -20 - 0		
	-MA		— 32 — 43,932	KH6I			-13 - 0		
KA1WJ	-MA		-32 - 43,761	KI7F	_OR		-16 — 1		
*KM9P	-IL		-1242,612	AA6E		_ 7 _			
*W5JW	-NM		-29 -42,245	,,,,,,,				20	
NBATR	-OH		-25 -41,080	DX Sing	le Operator	r			
*KI7M	-OR		19 38,880 15 33,880	**4M3A	ZC —Ve	nezuela	-578	-53 -56 ·	-124.805
	-NY		-31 - 32,370	*103M			-478	-41 -50	- 83,447
·VO2CW			-32 - 29,326	*OK1T				-31 -59	
·WB4UFL			- 8 -29,169	*CT4N	H -Po	rtugal	-426	-41 -47	- 74,888
'W9UP	-wi		-13 -26,136	*PY5E	G —Bra	azil	-389	-48 -41	- 69,0 64
WD8IVL	-он		-12 -25,805	IO6N	OA —Ital	ly	-438	-17 - 56	— 68,558
*W4TMR	-NC		-24 -25,718	*DL8N		Germany		—16 —41	
-KB0C/4	-VA	-503 -46 -	— 3 —24,990	OK1A				-30 -38	,
*KA1RC	-VT	—287 —55 -	-21 -24,528	*HI8GI		m. Rep.		-44 -17	
·W9RE	-IN	-300 -51 ·	-21 -24,192	*CN8C		rocco		-37 -27	
·W3USS	MD		—15 —24 ,080	*LX1J				-15 -24	
'N1BFS	-CT		<u>4 —23,550</u>	*EA1Q		ain stralla		-35 - 0 $-20 - 18$	
K4JPD	—GA		-20 -22,440	I4CSF				-12 -22	
KO2W	-NY		-23 -21,714	*F8WE				- 0 -22	
K3GYD	-PA		-24 -21,181	OK1A				- 2 -23	
*W8FGA WD4RCO	-MI		- 3 - 19,875	*JM1N				-17 - 9	
N4FKF	-IN		-28 -19,327 - 0 -16,497	18ZLV				- 0-22	
KU2W	-NY		- 7 - 15,176	ZS6W		Africa		- 3 - 17	
W1WEF	-CT		_ 1 _ 13,728	OK3C	RH -Cze	ech.	- 24	- 0 -12	- 732
NODQS	—IA		- 7 - 12,485	EA3D	MP —Spa	ain	_ 25	- 3-11	70 0
'VE4RP			-15 - 9,576	LA2T	O No	rway	_ 18	-10 - 0	- 360
KA2EAY	-NY	-212 -42 -	-2-9,416	YU7S	_	goslavia		- 0 - 9	
*N7BUP	-AZ	-150 -41 -	-14 - 9,350	OZ4Z		nmark		-0-5-	
*NF4F	-TN	-170 -42 -	8 — 9,050	OK3Y				-0-5-	
KA8PPJ	-OH		-0-7,812	DL7Q		Germany		- 0 - 4	
W3ARK	-PA		- 0 - 7,650	JL1E.				-0-1-	
KA4MTK			- 4 - 7,544	OZ1A		nmark	_ 2	- 0 - 2	- 8
WAITCA			- 7 - 6,768	W/VE M	ulti-Operato	or			
·K3OX	— NJ		- 1 - 6,493 -11 - 6,480	**K3TU	P —PA		-1214	-58 - 35 -	-120, 063
*N5BMD	-LA		- 7 - 6,345	*K8ND				—57 —37 -	
KBCV	-MI		- 5 - 6,232	*K5LZ0				 5735 -	
	-ME		- 2 - 6,040	*KC0S				-58 -33 -	
·W8VEN	-wv		4 - 5,719	*KB0Q				-55 -16 -	
*KC7PA	_UT	-114 -40 -	- 7 - 5,687	*KD4T				-55 -28 -	
WA3JXW	—PA	—172 —32 -	- 0 5,504	*KF2X	-NY			-54 -24 - -48 -29 -	
KF1B	-CT	- 95 -35 -	-13 - 5,280	*WA3S				-51 - 7 -	
	-NY		-12 - 5,040	N8EK				-44 - 0 -	,-
*WB8ZRL/0			- 4 - 4,950	*KOUR	—он			-46 -25 -	
	-CA		-17 - 4,326	*KW7Y				-47 -13 -	
	—NY		-17 - 4,324 - 2 - 4,380	*WB1G	TV- HM			<u>-41</u> - 8 -	
	—AL —NJ		- 2 - 4,280 - 0 - 4,200	DX Mult	-Operator				
	—AL		- 0 - 4,200 - 0 - 3,502					40 5	440.00
WB8YEW		- 97 - 35 -		*15NPH				-43 -64 -	
	-CT	- 81 -35 -		*140UT *DA1T!				-32 -62 - -31 -37 -	
	-NY		- 0 - 3,069	*JI1QQ				-12 - 9 -	
		- 59 - 33 -					31	12 - 3 -	1,000
W9LYN	—IL	- 62 -34 -		SWL Sta					
N8EOH	-MI	— 87 — 28 —	- 0 - 2,436	DL-104	_W. (Germany	— 183	— 1 —23 -	- 8,784

multiplier), each Canadian province or territory (13 maximum), and DX country (excluding the continental US and Canada).

FINAL SCORE

Total QSO points times total multiplier points equals claimed score.

CONTEST ENTRIES:

Each entry must include a contest log, a dupe sheet, a contest summary, and multi-

plier checkilst. We recommend that contestants send for a copy of the contest forms. Send an SASE to the contest address listed below.

CONTEST DEADLINE:

Each entry must be postmarked no later than February 12, 1984.

DISQUALIFICATIONS:

Omission of any required entry form,

operating in excess of legal power, manipulating of contest scores or times to achieve a score advantage, or failure to omit duplicate contacts which would reduce the overall score more than 2% are all grounds for immediate disqualification. Decisions of the contest committee are final.

AWARDS:

Contest awards will be issued in each

RESULTS

YV3BRF, I5NPH, KG1E, AND N4TY: 1983 WORLD 75-METER CHAMPS

The 1983 World 75-Meter Championship is now history. The scores have been tabulated, checked, and cross-checked. There are four clear-cut winners.

In the W/VE single-operator class, it was definitely a photo finish. Only 48 points separated the first- and second-place stations. World Champion KG1E took top honors with 722 QSOs, 98 multipliers, and a total score of 83,104 points. Close on his heels with 777 QSOs, 94 multipliers, and 82,156 points was secondplace finisher N5AU of Texas with K5ZD at the helm. Whowee...I wonder if each of them knew how close they were to each other in the closing hours of the

The single-operator class for DX stations was practically no contest for worldchampionship station YV3BRF of Venezuela. With 655 QSOs, 101 multipliers, and 132,108 total points, this station led second-place contestant IO3MAU of Italy by nearly 44,000 points.

In the W/VE multi-operator category, we had another close finish. Here again, if the two stations had known how close they were to each other, would we have seen different strategy in the closing hours? N4TY of Kentucky becomes the World Champ with 655 QSOs, 62 multipliers, and 41,106 points. Second place goes to K1WW of New Hampshire, who trailed the leader by only 1,073 points. Though the winner had 212 more contacts than his opponent, the scoring gap closed rapidly as K1WW accumulated 81 multipliers compared with only 62 for the champion. Next year, I'm sure both stations will monitor each other's activity more closely

In DX, ISNPH and crew became the 75-Meter World Champions for DX multioperator stations. Scoring 520 QSOs and 91 multipliers, they tallied a grand total of 101,092 points.

The following stations worked 500 or more QSOs: N5AU (777), N8II (730), KG1E (722), N4TY (655), YV3BRF (655), WBØNCR (606), KC8JH (600), KA4JNC (571), W3USS (563), IO3MAU (548), I5NPH (520), and K9EC (516).

in the contest, stations could work a total of 61 US states and Canadian prov inces and territories. N5AU came the closest to the maximum with 60 worked, closely followed by YV3BRF with 59. Other stations with 50 or more W/VE multipliers included N8II (58), KC8JH (57), KG1E (57), K9EC (56), W3USS (56), KB3A (56), WBONCR (55), N4TY (55), N1BFS (54), KIOF (54), KVOI (53), K1WW (53), HI8GB (52), N8AKY (52), WA1ZAM (52), C6ADV (51), K17M (51), K5LZO (51), KA4JNC (50), K2GKK/5 (50), and KOUR (50).

Working DX countries on 75 meters is a challenge all its own. From the looks of the DX multipliers claimed, propagation played a big roll in the outcome of contest scoring. Naturally, European stations logged the most countries worked due to their close proximity to one another (as compared with their North American counterparts). IO3MAU had the most countries worked, with a total of 54. He was closely challenged by multi-operator champion I5NPH, who tallied 52 total DX countries. Other stations loggling 25 or more included YV3BRF (42),

KG1E (41), N5AU (34), W3USS (31), HI8GB (29), CT4NH (29), K1WW (28), and K8MNG (25).

Of all the contests sponsored by 73, this 75-meter event has got to be the toughest. It has become an event participated in largely by Advanced- and Extraclass operators within the States. This, of course, is due to the band allocations and the fact that General-class licensees are extremely limited in available frequencies for contesting purposes. Adding to this dilemma is the fact that DX countries for the most part all have different parts of the spectrum in which to operate, making simplex operation rather difficult for the majority. In view of these obstacles, FCC action in the future which would further expand phone privileges for American amateurs on this band would greatly enhance the capability stations would have to maneuver. The 75-Meter Contest would see a dramatic increase of activity as a result.

With the rules changed slightly to encourage more DX participation, we expect to see even greater scores and a much larger turnout in the 1984 contest. The sunspot cycle promises to make 75 even more exciting than it has been in the past. It'll be your chance to get another "new one," so plan to attend. Obtain your forms as soon as possible by sending an SASE to Jose Castillo N4BAA, 75-Meter Contest Chairman, 1932 Highland Drive, Amelia Island FL 32034.-Bill Gosney KE7C.

75-METER CONTEST SOAPBOX

KA1DZV: "Enjoyed the contest-very unique!"

KG1E: "Excellent test! Propagation to all parts of the world was fantastic! Sure was a great contest,"

WA1ZAM: "A great time again for the second year in a row. I'll be back." KR3A

"Had the best of both worlds, multi-op for 40 and single op for 80." KI3S: "Nice contest. Next year, I will plan to spend more time on the air."

W3USS: "Tremendous conditions and turnout!" 4BAA: "Wish I had had more time this year. See everyone next year for sure."

K4JPD: "I really enjoyed the contest!" N4TY: "This was a super contest!" W4TMR: "Can't wait until next year!"

AA6EE: "Learned that I need a better DX antenna than an inverted vee."

K8MNG: "This contest surpassed my expectations; worked 8 new countries on 75."

K9GDF: "Great contest!"

KIOF: "FB contest. Glad to be part of it. Where was Mississippi?"

JA2YKA: "Nice contest indeed. See you again next year.

VY1DV: "Too cold to stay in the shack even with the heater going. Outside temperature was 40° C. Conditions were poor, to say the least!'

75-METER ANTENNA SURVEY

Dipole/inverted vee	65.9 %	W3DZZ array	2.2
Vertical	10.0	3-element yagi	1.1
Sloper (1/4- and 1/2-wave)	7.7	18 AVT	1.1
Delta loop	5.4	Windom	1.1
Longwire	2.2	Phased vertical	1.1





NEWSLETTER OF THE MONTH

From the top of Georgia's Stone Mountain and the heart of Atlanta comes this month's newsletter contest winner, Top O' The Rock. Printed with pride by the Alford Memorial Radio Club, this newsletter has undergone an amazing metamorphosis in recent months

Though once it was just another no-name newsletter, shortly after becoming Top O' The Rock the publication biossomed. Now it is stuffed with feature articles, news, and humor. The large number of letters to the editor received by Faye Garner N4HLE attests to the interest club members have in their publication.

In addition to the well-designed cover, Top O' The Rock sports a table of contests, monthly calendar, and, of all things, advertising. Though many clubs mean and grean about the expenses of printing and distributing a newsletter, the Alford Memorial Radio Club has found a way to support its product. In addition to the supplemental income, the newsletter benefits from a dedicated staff including Alan Langford N4HUD. Production Manager, Jim Garner KE4BI, Advertising Manager, Cary Dingler N4GPL, Circulation Manager, Reed Kreen WA3JBQ, US Post Office Liaison; and, last but not least, Big Willie GO4KILL, Master of Broken Arms.

Congratulations to Faye and her crew for an outstanding publication.

To enter your club's newsletter in 73's Newsletter of the Month Contest, send it to 73, Pine Street, Peterborough NH 03458, Attn: Newsletter of the Month.

operator class in each of the continental 48 United States, Canadian provinces and territories, and each DX country represented. A minimum of 100 QSOs must be worked to be eligible for contest awards.

CONTEST ADDRESS:

To obtain entry forms or to submit an entry, contact: 40-Meter Contest, Dennis Younker NE61, 43261 Sixth Street East, Lancaster CA 93535.

3RD ANNUAL 75-METER **WORLD SSB CHAMPIONSHIP** 0000Z to 2400Z January 8, 1984

SPONSORED BY

73: Amateur Radio's Technical Journal.

MISCELLANEOUS RULES:

Work as many stations as possible on 75-meter phone during the specified times of allowable operation. The same station may be worked once. Crossmode contacts will not count. Single-operator stations may operate a total of 16 hours. All multi-operator stations may operate the entire 24-hour period. Off periods must be noted in your log(s) and on your summary sheet. Off periods are no less than 30 minutes each.

OPERATOR CLASSES:

(A) Single operator, single transmitter, phone only. (B) Multi-operator, single transmitter, phone only.

EXCHANGE-

Stations within the continental 48 United States and Canada transmit an RS report and state, province, or territory. All other stations, including Alaska and Hawaii, transmit RS report and DX country.

5 QSO points for contacts with W/VE stations located within the continental 48 United States and Canada. All other contacts score 10 points each. List points for each contact on your log sheet(s).

MULTIPLIERS:

1 multiplier point is earned for each US state, 48 maximum (a District of Columbia contact may be substituted for a Maryland multiplier), each Canadian province or territory (13 maximum), and DX country (excluding the continental US and Canada).

FINAL SCORE:

Total QSO points times total multiplier points equals claimed score.

CONTEST ENTRIES:

Each entry must include a contest log, a

1983 RESULTS 75-METER WORLD SSB CHAMPIONSHIP

Indicated are callsign, QTH, QSOs, states/provinces worked, DX worked, and total score.

"World champion

*State/province/country champion

W/VE Single Oper	rator			W6LFB —CA — 15 —11 — 0 — 165
		*N4BAA	−FL −150 −40 − 3 − 6,600	VY1DV —YUK — 16 — 5 — 1 — 102
	A -722 -57 -41 -83,104	*K2MK	-NJ -155 -36 - 4 - 6,440	AA6EE —CA — 8 — 7 — 0 — 56
		*VE4RP	-MAN -149 -38 - 3 - 6,191	N9DIJ —WI — 2 — 2 — 0 — 4
(K5ZD, op.)		WA1TCA		
	V -730 -58 -21 -61,146	KA1DZV	-CT -169 -34 -0 $-5,746$	DX Single Operator
	D —563 —56 —31 —54,984	·KC7PA	—UT —124 —41 — 2 — 5,418	DA Single Operator
(K3ZJ, op.)		K8MNG	—OH — 98 —19 —25 — 5,405	"YV3BRF — Venezuela — 655 — 59 — 42 — 132,108
	H —600 —57 —12 —42,297	W8VEN	—WV —131 —37 — 2 — 5,187	*IO3MAU —Italy —548 —30 —54 — 88,284
WBONCR -IA		WB2TKD	-NY -129 -36 - 2 - 4,978	*HI8GB —Dom. Rep. —466 —52 —29 — 75,330
	T —482 —54 —19 —37,011	"N4ARO/6	-	*C6ADV —Bahamas —398 —51 —24 — 32,550
·K9EC —W		.NOCMC	—ND —103 —38 — 3 — 4, 3 46	*CT4NH —Portugal —129 —21 —29 — 10,700
*K4JPD —GA	A —437 —48 —22 —32,480	KI3S	—PA —108 —33 — 5 — 4,332	*EA3CCN — Spain — 81 — 17 — 22 — 6,123
*KB3A —PA	→ 522 —56 — 5 —32,147	*KT4U	—VA —115 —32 — 4 — 4,284	OK3CRH — Czech. — 57 — 0 — 23 — 2,622
*KV0I — NE	= -479 - 53 - 7 - 29,160	W2FTY	-NY -108 -35 - 3 - 4,218	14CSP Italy 55 7 14 2,376
KB3ND —PA	4 —445 —47 —11 —26,448	N5AF	-TX - 92 - 35 - 7 - 4,200	*HA8IE —Hungary — 51 — 0 —19 — 1,938
*WA1ZAM -MA	A -406 -52 - 9 -25,376	KB5DQ	-NM -109 -36 - 2 - 4,142	*F8WE —France — 39 — 8 — 15 — 1,794
*KI7M — OF	R -356 -51 -10 -24,095	W2GKZ	-NY - 80 - 34 - 7 - 3,567	EA2AQW—Spain - 54 - 0 - 14 - 1,442
*K2GKK/5 -OF	-360 -50 -10 -22,814	*KV7L	-WY - 80 - 38 - 4 - 3,528	*DH0FAV -W. Germany - 55 - 0 -12 - 1,296
*NR4S —TN	1 −379 −45 −12 −22,572	KJ2N	-NJ - 90 - 29 - 4 - 3,135	OK3FON — Czech. — 26 — 1 — 10 — 550
<pre>'KOUR —KS</pre>	-291 - 50 - 18 - 21,148	W7CB/6	-CA - 79 - 35 - 2 - 3,071	YU7SF — Yugoslavia — 9 — 0 — 7 — 126
*KIØF -MI	N -323 -54 - 3 -18,582	N1SR	-MA - 75 - 32 - 3 - 2,765	
*W4TMR -NC	2 -256 -49 -12 -16,592	*KB8KW/7	-MT - 75 - 32 - 0 - 2,400	W/VE Multi-Operator
*W8UVZ -MI	-298 -48 - 5 -16,059	KA2EAY	-NY - 94 -23 - 0 - 2,068	
N8ATR —OF	-281 -47 - 5 -15,158	W3BGN	-PA - 41 -24 -13 - 2,035	"N4TY — KY —655 —55 — 7 —41,106
N8TN —OH	H -262 -43 - 3 -12,190	W1LUG/4	-VA - 67 - 26 - 1 - 1,836	*K1WW —NH—443 —53 —28 —39,933
KB8WB -OF	-240 -45 - 3 -11,664	VO2CW	-LAB - 41 -15 - 9 - 1,320	*K5LZO —TX —446 —51 —16 —31,088
'K4ADI —SC	-200 - 44 - 7 - 10,557	K1NCD	-CT - 60 - 21 - 0 - 1,260	*KA4JNC -VA -571 -50 - 4 -31,050
KC3AF —PA	-225 -42 - 4 -10,350	WB8ZRL/0	NE - 47 -26 - 0 - 1-222	*N8AKY —MI —381 —52 —12 —25,216
W3ARK —PA	-181 - 39 - 1 - 7,684	K9GDF	-WI - 46 - 26 - 0 - 1.196	*WA3SPJ —PA —380 —49 — 8 —21,660
'KA2CDJ NY	4 - 163 - 41 - 4 - 7.515	KB7M	-WY - 36 -28 - 0 - 1.008	*KF2X —NY —355 —47 —20 —20,703
*KN1M ME	E -156 -35 -11 - 7.176	KB9PB	-IL - 38 -23 - 0 - 874	*WB1GMH—VT —245 —44 — 3 —11 656
K8CV -MI	-147 - 42 - 4 - 6,946	VE4AKN	-MAN - 36 -24 - 0 - 864	
*KS5A/4 -AL	-134 - 43 - 6 - 6,860	WA4LDU	-SC - 29 -28 - 1 - 600	DX Multi-Operator
*N5ACP -NN	M = 121 - 47 - 6 - 6,731	W5SOD	-TX - 30 - 18 - 1 - 589	**I5NPH — Italy — 520 — 39 — 52 — 101.092
KB9S —WI	-144 - 42 - 4 - 6,716	AA2Z	-CT - 16 - 8 - 3 - 231	*JA2YKA-Japan - 51 - 8 - 7 - 1.185



MICROWAVE COMPONENTS

25 MW EXCITER \$49.95 45 MHZ SUBCARRIER \$19.95 AM VIDEO MODULATOR \$19.95 50 MW UP CONVERTER \$149.95

GIZMO ELECTRONICS, INC.

P.O. BOX 1205 PITTSBURG, KS 66762 PH. 316-231-8171

-229

Kansas residents 3% sales tax



MAKE IT EASY TO SAVE your copies of



73 Magazine

Your magazine library is your prime reference source—keep it handy and keep it neat with these strong library shelf boxes. They are made of white corrugated cardboard and are dust resistant. Use them to keep all your magazines orderly yet available for constant reference.

Self-sticking labels are available for the following: 80 Micro 73 Magazine Radio Electro

Microcomputing QST inCider CQ

73 Magazine Radio Electronics
QST Personal Computing
CQ HOT CoCo

Desktop Computing Ham Radio Interface Age

One box $\{BX1000\}$ is \$2.00, 2-7 boxes $\{BX1001\}$ are \$1.50 each, and 8 or more boxes $\{BX1002\}$ are \$1.25 each. Be sure to specify which labels we should send.

Call TOLL-FREE for credit card orders:

1-800-258-5473

73 Magazine

Attn: Book Sales, Peterborough, NH 03458

SHIPPING AND HANDLING CHARGES \$2.00 per order, up to and including a quantity of eight. 25¢ for each additional box ordered.

RESULTS

K8ND AND KC8JH: 1983 WORLD 160-METER CHAMPS

"Keep this fine gentlemen's contest on the agenda forever"..."the contest support was overwhelming"..."it's the best 160-meter contest going!" This was the general feeling of contestants about this year's World 160-Meter Sideband Championship!

If you participated this year and are from Ohio, we don't need to tell you how devastating the competition was there. Out of the top four scores in the contest, three stations were from the state of Ohio. Between K8ND, WB8JMB, and KC8JM, a total of 2,798 contacts were made totaling 898,930 contest points. That's 160-meter contesting at its best—championship-style!

In the single-operator class, KC8JH (Ohlo) accumulated 900 QSOs to become the 1983 World Champ. K8ND earned the same distinction with 1001 QSOs in the multi-operator category.

Stations achieving 500 or more single-operator contacts Included KC8JH (900), AA1K (796), K0HA (710), K9QLL (663), KVØG (627), N5CG (605), N5JB (597), KC8P (591), K6SE (590), W8FGA (588), W8GIO (564), K4AQQ (560), W8UP (558), and W4TMR (532). In the multi-operator class, 500 or more contacts were earned by K8ND (1001), W8BJBM (897), W4CN (890), WA2SPL (879), N7DF (664), KBØTJ (586), and KC5DX (523).

According to contestants, propagation was truly fantastic; the majority of entries cited 40 or more W/VE multipliers worked. Many indicated they were able to earn that last-needed state or two for their WAS award.

The greatest difference noted in the scores was the amount of DX multipliers earned by competing stations. Single-operator stations working 6 or more DX countries included EA3CCN (13), NAIN (13), OKTJDX (12), AA1K (11), K6SE (9), K0HA (7), KV0G (7), K4AOO (7), W5GFR (7), WA4SVO (7), N5CG (6), W8GIO (6), KC8JH (6), W0CM (6), and K7VIC (6). Multi-operator stations with 6 or more DX multipliers were WASSPL (18), Y07JDE (16), K8ND (9), and W88JBM (7).

Tabulating all the entries and cross-checking all scores revealed that more than 1300 stations were logged during this weekend event. It also appears that over 20 DX countries were represented 1983's contest was the best ever! If you were from Alabama, Arkansas, Connecticut, Idaho, Louisiana, Minnesota, Missouri, North Dakota, or Utah, sending an entry to our contest manager would have made you an award winner from your state. Though there were many stations participating in all states, not a station from the states listed above submitted an entry. That's unfortunate. Likewise, no entries were received from Alberta, Prince Edward Island, Yukon Territory, Northwestern Territories, Labrador, or Newfoundland. With the 1984 event just around the corner, stations from these states and provinces will get a second chance to represent their areas.

Of particular interest every year is the opportunity to prove to our readers that most hams can in fact get on 160 without owning a lot of real estate. Every style

of inverted vee, delta loop, and wire beam has been tried—even on small city lots! Here are some statistics extracted from contestants' entries.

160-METER ANTENNA SURVEY

	1981	1982	1983
Dipole/inverted vee	54.9%	59.6%	64.2%
1/4-wave vertical	9.1	15.8	3.8
Trap vertical	19.8	9.3	16.0
Full-/half-wave vertical	2.2	.5	1.2
Wire beam	2.1	.9	2.4
Delta loop	1.7	.9	.0
2/3-element yagi	1.4	.9	.0
1/4-wave sloper	4.4	9.3	7.4
1/2-wave sloper	4.4	2.8	5.1

Awards for the 1983 contest are being prepared at this time and should be to recipients shortly. We congratulate all the winners for their dedication to this year's effort and all the participants who made it all possible, it's been great!

As for 1984, it's promised to be the biggest year ever in 160-Meter Contest history. With the sunspot cycle in our favor, the band should be filled with new ones for the deserving DXer. Just who will be the new World Champs for 1984? Will K8ND and KC8JH retain their titles? Will former champs W9RE, W8NGO, W8LRL, or W4CN regain top honors or will it be someone from the west coast this time? Mark the dates on your calendar; the 5th annual 160-Meter World Championship is slated for January 14 and 15, 1984.

If you intend to enter this year's event, why not send for your contest entry forms today? Foreign stations especially should obtain their forms as soon as possible due to delays in mail-handling between countries. Send your SASE to: Harry Arsenault K1PLR, 160-Meter Contest Chairman, 603 Powell Avenue, Erie PA 16505.—BIII Gosney KETC.

160-METER CONTEST SOAPBOX

K1LPS: "Did not hear any nasty remarks or complaining in splite of very crowded conditions, although there were a few instances of deliberate jamming...something that is thankfully rare on 160."

K3MO: "Was handicapped with a sore throat. Elixia of Kentucky eased the pain."

K4IN: "The present rules discriminate against the DX station. It is much harder to work a second G or VY than another W2 in New Jersey, yet all count the same!" (Editor's note: 1984 rules will allow 5 points per W/VE contact and 10 points for all others.)

N8AKY: "Was able to work my last state for WAS! Keep this fine gentlemen's contest on the agenda forever."

W8GIO: "Could have had a couple more multipliers but refused to operate in the window."

W9LNO: "Glad to be back on 160 after a 25-year absence. The band sounds absolutely great!"

K9QLL: "The spirit was willing but the flesh went to sleep."

dupe sheet, a contest summary, and multiplier checklist. We recommend that contestants send for a copy of the contest forms. Send an SASE to the contest address listed below.

CONTEST DEADLINE:

Each entry must be postmarked no later than February 12, 1984.

DISQUALIFICATIONS:

Omission of any required entry form, operating in excess of legal power, manipulating of contest scores or times to achieve a score advantage, or fallure to omit duplicate contacts which would reduce the overall score more than 2% are all grounds for immediate disqualification. Decisions of the contest committee are final.

AWARDS

Contest awards will be issued in each operator class in each of the continental 48 United States, Canadian provinces and territories, and each DX country represented. A minimum of 100 QSOs must be worked to be eligible for contest awards.

CONTEST ADDRESS:

To obtain entry forms or to submit an entry, contact: 75-Meter Contest, Jose A. Castillo N4BAA, 1832 Highland Drive, Amelia Island FL 32034.

5TH ANNUAL 160 METER WORLD SSB CHAMPIONSHIP 0000Z January 14, 1984 to 2400Z January 15, 1984

SPONSORED BY:

73: Amateur Radio's Technical Journal.

OBJECT:

To work as many stations as possible on 160-meter phone in a maximum of 32 hours allowable contest time. Muttl-operator stations may operate the entire 48-hour contest period. Stations may be worked only once.

ENTRY CATEGORIES:

(A) Single operator, single transmitter, phone only. (B) Multi-operator, single transmitter, phone only.

EXCHANGE:

Stations within the continental US and Canada transmit RS report and state or province/territory. All others transmit RS report and DX country.

POINTS:

5 QSO points for contact with W/VE stations contacted within the continental 48 United States and Canada. All other contacts earn 10 points each.

MULTIPLIERS:

1 multiplier point will be earned for each of the continental United States, 48 maximum (a District of Columbia contact may be substituted for a Maryland multiplier), each of the Canadian provinces/territories (13 maximum), and each DX country outside the continental 48 United States and Canada.

FINAL SCORE:

Total QSQ points times total multiplier points equals claimed score.

CONTEST ENTRIES:

Each entry must include log sheets, dupe sheet for 100 or more contacts, a contest summary, and a multiplier check sheet.

ENTRY DEADLINE:

All entries must be postmarked no later than February 19, 1984.

DX WINDOW:

Stations are expected to observe the DX window from 1.825-1.830 MHz as mutually agreed by top-band operators. Stations in the US and Canada are asked not to transmit in this 5kHz segment of the band. During the contest, all WVE stations are requested to utilize only those frequencies from 1.808-1.825 and 1.830-1.900 MHz.

DISQUALIFICATIONS:

Disqualification may result if a contestant omits any required entry form, operates in excess of legal power authorized for his/her given area, manipulates operating times to achieve a score advantage, or falls to omit

duplicate contacts which reduce the overall score more than 2%. Decisions of the contest committee are final.

AWARDS

Contest awards will be issued in each entry category in each of the continental United States, each Canadian province/territory, and each DX country. A minimum of 100 OSOs must be worked to qualify.

CONTEST ADDRESS.

To obtain Information or entry forms (enclose an SASE) or to submit a contest entry, contact: 160-Meter Contest, Harry Arsenault K1PLR, 603 Powell Avenue, Erie PA 16505.

3RD ANNUAL RTTY WORLD CHAMPIONSHIP 0000Z to 2400Z February 25, 1984

SPONSORED BY:

73: Amateur Radio's Technical Journal and The RTTY Journal.

OPERATOR CLASSES:

(A) Single operator, single transmitter. (B) Multi-operator, single transmitter.

ENTRY CATEGORIES:

(A) Single band. (B) Allband, 10-80 meters.

EXCHANGE:

Stations within the 48 continental United

1983 RESULTS 160-METER WORLD SSB CHAMPIONSHIP

Indicated are callsign, QTH, QSOs, states/provinces worked, DX worked, and

* *World champion

*State/province/country champion

	W/VE Single	e Operat	or	WA9TZE	-WI	-222 -53 - 1 - 55,920	VE3NBE	-ONT - 70 -31 - 0 - 10.850
**AAIK	**KC8JH	OH	-900 -56 - 6 -279.000					
NAMA			· ·					·
NEON		-NE	· ·					·
MSSE		-co				· · · · · · · · · · · · · · · · · · ·		
NASOLL		-CA	·					· · · · · · · · · · · · · · · · · · ·
NSSG		-IL						
NS.B	*N5CG	-ok						
KAGOP	*N5JB	-TX	-597 - 56 - 4 - 180,600					·
'KAGOO FL −560 − 55 − 7 − 173,600 'W/FT −WY −202 − 50 − 0 −50,500 WBAGOO WW −564 − 55 − 6 − 172,020 XBAGO −E − 208 − 45 − 2 − 48,800 WBAGO −E − 208 − 45 − 2 − 48,800 WBAGO −E − 208 − 45 − 2 − 48,800 WBAGO −E − 208 − 45 − 2 − 48,800 WBAGO −E − 208 − 45 − 2 − 48,800 WBAGO −E − 208 − 45 − 2 − 48,800 WBAGO NE − 208 − 40 − 2 − 44,400 WBAGO NE − 208 − 40 − 2 − 44,400 WBAGO NE − 208 − 40 − 2 − 40 − 5,600 WBAGO NE − 208 − 2 − 2 − 2 − 5,610 WBAGO NE − 208 − 2 − 2 − 2 − 5,610 WBAGO NE − 20 − 2 − 2,610 WBAGO NE − 20 − 2 − 2,510 VESKU − 100 − 2 − 2,560 WBAGO NE − 20 − 2 − 2,560 WBAGO NE − 20 − 2 − 2,560 NBAGO NB − 20 − 2 − 1,600 WBAGO NB − 20 − 2 − 1,600 NB − 20 − 2 − 1,600 NB − 20 − 2 − 2,560 <	*KC8P	-MI	-591 - 57 - 3 - 177,300			·	N9KS	·
W8GIG	*K4AQQ	-FL	-560 - 55 - 7 - 173,600	*W7FT			AXA8W	
W5GA —M —588 —54 — 1 —161,700 W5GB —TX —497 —54 — 7 —153,720 W3DHM —PA —177 —45 — 5 — 41,170 W3DHM —PA —177 —45 — 39,345 W3CM —RI —36 —18 — 0 — 3,240 W3CM —RS —472 —55 — 6 —143,865 W3CM —RI —36 —58 —6 —133,656 K8STI —W1 — MT —69 —53 — 6 —138,355 K8STI —SD —480 —54 — 1 —132,000 WBUFL —IA —169 —44 — 0 — 34,980 W6SMO —PA —448 —55 — 5 —130,210 WASYVO —FL —438 —52 — 7 —129,210 WATWW —SC —136 —41 — 2 —31,240 WBODS —IA —421 —54 — 2 —117,880 VE3CVX —ONT —449 —52 — 4 —125,720 WBVEX —W0 — W8 — WV —142 —41 — 0 — 26,840 WBSKX —MI —244 —52 — 0 —110,240 NBAKY —MI —244 —52 — 0 —110,555 W3STI —PA —374 —53 —3 —104,720 NSAFU —IA —335 —54 — 3 —95,975 W3FI — NA —334 —60 — 2 —110,555 W3FI — NA —374 —53 —3 —104,720 NSAFU —IA —335 —54 — 3 —95,975 WGENE —IN —338 —46 — 0 —17,740 VEARU —IN —338 —46 — 0 —83,490 NGALVI — NA —304 —4 —7 —7 —7 —7 —7 —7 —7 —7 —7 —7 —7 —7 —7	*W8GIO	-wv	-564 - 55 - 6 - 172,020	K3LGC			KB8UQ	-MI - 51 -22 - 0 - 5,610
W5GFA — MI — 588 — 54 — 1 — 161,700 W5GFR — TX — 497 — 754 — 7 — 153,720 W3DHM — PA — 177 — 45 — 0 — 39,825 W3GFM — NC — 532 — 54 — 5 — 148,385 "W6CM — NS — 472 — 55 — 6 — 149,960 K7VIC — MT — 469 — 53 — 6 — 138,355 K89ST — OH — 182 — 43 — 0 — 39,130 WASYJA — MD — 32 — 16 — 0 — 2,860 K89STI — SD — 480 — 54 — 1 — 132,000 WBEUFL — IA — 169 — 44 — 0 — 34,980 WASYJA — MD — 32 — 16 — 0 — 2,560 K83MO — PA — 448 — 55 — 5 — 139,210 WASYJA — MD — 32 — 16 — 0 — 2,560 WSGFR — NT — 499 — 27 — 17,725 WASSY — ONT — 449 — 52 — 4 — 125,720 WBODS — LA — 421 — 54 — 2 — 117,880 VE3CUX — ONT — 449 — 52 — 4 — 117,980 NBAKY — MI — 424 — 52 — 0 — 110,240 NBAKY — MI — 424 — 52 — 0 — 110,240 NBAKY — MI — 244 — 52 — 0 — 110,240 NBAKY — MI — 244 — 52 — 0 — 110,240 NBAKY — MI — 244 — 52 — 0 — 110,5550 WBST — PA — 374 — 53 — 3 — 3 — 104,720 NSAFIT — NE — 349 — 50 — 5 — 55,975 W3ST — PA — 374 — 53 — 3 — 3 — 104,720 NSAFIT — NI — 383 — 46 — 2 — 91,720 WFEIT — NI — 383 — 46 — 0 — 117,800 KGHNZ — CA — 333 — 46 — 2 — 91,920 VEARP — NI — 383 — 46 — 0 — 83,490 KZEL — NI — 383 — 46 — 0 — 83,490 NSAFT — NI — 383 — 46 — 0 — 83,490 NSAFT — NI — 383 — 46 — 0 — 77,740 VEARD — NI — 336 — 46 — 0 — 83,490 NSAFT — NI — 383 — 46 — 0 — 77,740 VEARD — NI — 360 — 60 — 60,808 NSAFT — NI — 384 — 46 — 1 — 80,860 NSAFT — NI — 384 — 46 — 1 — 73,085 NSAFT — NI — 384 — 46 — 1 — 73,085 NSAFT — NI — 384 — 46 — 0 — 68,608 NSAFT — NI — 384 — 46 — 1 — 73,085 NSAFT — NI — 388 — 46 — 1 — 73,085 NSAFT — NI — 388 — 46 — 0 — 77,740 VEZIVI — NI — 360 — 66 — 68,088 NSAFT — NI — 388 — 46 — 0 — 77,740 VEZIVI — NI — 365 — 66 — 68,088 NSAFT — NI — 388 — 46 — 0 — 77,740 VEZIVI — NI — 365 — 66 — 68,088 NSAFT — NI — 388 — 46 — 0 — 65,768 NSAFT — NI — 388 — 46 — 0 — 66,576 NSAFT — NI — 388 — 46 — 0 — 66,576 NSAFT — NI — 388 — 36 — 0 — 66,576 NSAFT — NI — 388 — 36 — 0 — 66,576 NSAFT — NI — 388 — 36 — 0 — 66,576 NSAFT — NI — 388 — 36 — 0 — 66,576 NSAFT — NI — 388 — 36 — 0 — 66,576 NSAFT — NI — 388 — 36 — 0 — 66,576 NSAFT — NI — 388 — 36 — 0 — 66,576 NSAFT — NI — 388 — 36 — 0 — 66,576 NSA	*W9UP	-WI	-558 -56 - 5 -170,190	K2DWI	-NY	-202 - 41 - 0 - 43,460	*VE1BRA	-NB - 52 -21 - 0 - 5,460
Wath No. Color Sale	W8FGA	-MI	-588 -54 - 1 -161,700	N7CKD	-WA	· ·	KA9JDW	-IL $-49-21-0-5,145$
WATMR	W5GFR	-TX	-497 - 54 - 7 - 153,720	W3DHM	-PA	-177 - 45 - 0 - 39.825	K1GZM	-RI - 36 - 18 - 0 - 3,240
WACK	*W4TMR	-NC	-532 - 54 - 5 - 148,385	*VE5XU			KB7M	-WY - 32 - 18 - 0 - 2,880
***NST	*W@CM	-KS	-472 -55 - 6 -143,960			· ·	WASYJA	-MD - 32 - 16 - 0 - 2,560
**************************************	*K7VIC	-MT	-469 - 53 - 6 - 138,355	KB9Q	-wi	-161 - 45 - 0 - 36,225	K8VNP	-FL - 30 - 17 - 0 - 2,550
WA4SVO	*KØSTI	-SD	-480 - 54 - 1 - 132,000	WBOUFL	-IA	-169 - 44 - 0 - 34.980	W6PFE	-CA - 24 - 18 - 0 - 2,160
*VE3ABG ONT -449 -52 - 4 -125,720 W8VEN	*K3MO	-PA	-448 - 53 - 5 - 130,210	KA7BRE	-NV	-169 - 40 - 0 - 33,800	W1GCH	-VT - 23 - 15 - 0 - 1,725
W@DQS	WA4SVO	-FL	-438 - 52 - 7 - 129,210	W4TWW	-sc	-136 - 41 - 2 - 31,240	KB8HW	-MI - 5 - 1 - 0 - 25
VE3CVX — ONT — 445 — 51 — 1 — 115,700 *N8CGK — OH — 483 — 46 — 0 — 111,090 MAIXAM — MA — 140 — 38 — 0 — 26,680 N8AKY — MI — 424 — 52 — 0 — 110,240 *WILOV — RI — 170 — 31 — 0 — 26,350 N4IN — FL — 326 — 52 — 13 — 105,950 MAMM — VA — 128 — 44 — 0 — 26,240 *WA1SAM — VA — 128 — 44 — 0 — 26,240 *WA1SAM — VA — 128 — 44 — 0 — 26,240 *WA1SAM — VA — 128 — 44 — 0 — 26,240 *XE1HHA — Mexico — 71 — 24 — 1 — 8,875 *WAST — PA — 374 — 53 — 3 — 104,720 *WA1DV — IA — 335 — 54 — 3 — 95,475 *WASPU — IA — 335 — 54 — 3 — 95,475 *WASPU — IA — 335 — 54 — 3 — 95,475 *WAFFI — NH — 363 — 46 — 0 — 91,780 *WZFJ — NJ — 328 — 46 — 1 — 80,360 *WZFJ — NJ — 328 — 46 — 1 — 80,360 *WZFJ — NJ — 328 — 46 — 0 — 77,740 *WE7CRU — BC — 301 — 51 — 0 — 76,755 *WIYN — MA — 310 — 44 — 4 — 74,400 *WA1DM — WA — 110 — 40 — 1 — 22,230 *WAYN — SC — 311 — 46 — 1 — 73,085 *KAND — ONT — 264 — 51 — 2 — 69,960 *WA1DM — WA — 110 — 40 — 1 — 17,835 *WA1DM — WA — 110 — 40 — 1 — 17,835 *WA2SPL — NY — 879 — 56 — 18 — 325,230 *	*VE3ABG	-ONT	-449 - 52 - 4 - 125,720		-wv			
**NBCGK	WODQS	-LA	-421 -54 - 2 -117 ,880	WD8LXA	— ОН	-160 - 35 - 0 - 28,000		
N8AKY — MI — 424 — 52 — 0 — 110,240 N4IN — FL — 326 — 52 — 13 — 105,950 N4IN — FL — 326 — 52 — 13 — 105,950 N4MM — VA — 128 — 41 — 0 — 26,240 'X51HHA — Mexico — 71 — 24 — 1 — 8,875 'X61PE — ME — 349 — 50 — 5 — 95,975 'KA1PE — ME — 349 — 50 — 5 — 95,975 'W9RE — IN — 338 — 46 — 2 — 91,920 'K6HNZ — CA — 353 — 52 — 0 — 91,780 'W2FJ — NJ — 328 — 46 — 1 — 80,360 'W2FJ — NJ — 328 — 46 — 0 — 83,490 'V2FCRU — BC — 301 — 51 — 0 — 76,755 'W1YN — MA — 310 — 44 — 4 — 74,400 'X64CNW — SC — 311 — 46 — 1 — 73,085 'K4CNW — SC — 311 — 46 — 1 — 73,085 'K4CNW — SC — 311 — 46 — 1 — 73,085 'VEIRY — NF — TN — 318 — 44 — 0 — 69,960 'V2IX — NS — 249 — 47 — 9 — 69,720 'WA1UJU — WI — 286 — 46 — 0 — 68,080 'WA1UJU — WI — 286 — 46 — 0 — 68,080 'WA1UJU — WI — 286 — 46 — 0 — 68,080 'WASS — MD — 316 — 39 — 2 — 64,780 'W3BS — MD — 316 — 39 — 2 — 64,780 'W3USS — MD — 316 — 39 — 2 — 64,780 'W3USS — MD — 316 — 39 — 2 — 64,780 'W3USS — MD — 316 — 39 — 2 — 64,780 'W3USS — MD — 316 — 39 — 2 — 64,780 'W3USS — MD — 316 — 39 — 2 — 64,780 'W3USS — MD — 316 — 39 — 2 — 64,780 'W3USS — MD — 316 — 39 — 2 — 64,780 'W3USS — MD — 316 — 39 — 2 — 64,780 'W13 — MA — 10 — 266 — 48 — 2 — 65,170 'W3USS — MD — 316 — 39 — 2 — 64,780 'W19 — W315S — MD — 316 — 39 — 2 — 64,780 'W315D — 10 — 10,595 NAMM — VA — 128 — 44 — 1 — 0 — 22,755 NAMM — VA — 126 — 55 — 1 — 65,170 'W19 — MA — 110 — 10 — 17,835 'W315D — 10 — 10,595 'W316D — 10 — 10 — 10 — 10 — 10 — 10 — 10 — 1	VE3CVX	-ONT	-445 - 51 - 1 - 115,700	*VE4WR	-MAN	1 - 122 - 44 - 0 - 26,840	DX Single O	perator
NAIN	*N8CGK	-OH	-483 - 46 - 0 - 111,090	WA1ZAM	-MA	-140 -38 - 0 - 26,600	**YV3AZC	-Venezuela -118 -34 - 4 -22,420
W3ST	N8AKY	-MI	-424 -52 -0 $-110,240$	*W1LOV	-RI	-170 - 31 - 0 - 26,350	*YV2IF	Vene zu ela 62 25 4 10,005
**KA1PE	N4IN	-FL	-326 -52 -13 -105,950	N4MM	-VA	-128 - 41 - 0 - 26,240	*XE1HHA	-Mexico - 71 - 24 - 1 - 8,875
W@PJV —IA —335 —54 — 3 — 95,475 KC8A —MI —126 —36 — 0 — 22,680 *LU9EIE —Argentina 1 — 1 — 0 — 5 *W9RE —IN —383 —46 — 2 — 91,920 VE4RP —MAN —110 —40 — 1 — 22,550 WVE Multi-Operator *AF1T —NH —363 —46 — 0 — 83,490 K2FL —NJ —128 —34 — 1 — 22,400 **K8ND —OH —1001 —57 — 9 —330,330 *W2FJ —NJ —328 —46 — 1 — 80,360 *N5ACP —NM —106 —42 — 0 — 22,260 *WA2SPL —NY —879 —56 —18 —325,230 *KD4NI —VA —338 —46 — 0 — 77,740 VE4QZ —MAN —114 —39 — 0 — 22,230 *WBBJBM —OH —897 —57 — 7 —289,600 *VE7CRU —BC —310 —44 — 4 — 74,400 WD8MRF —OH —113 —29 — 1 — 22,035 *W4CN —KY —890 —57 — 4 —271,450 *W4YN —MA —310 —44 — 4 — 74,400 WD8MRF —OH —113 —38 —0 —21,470 *KB0TJ —CO —586 —56 —4 —175,200 *NF4F —TN —318 —44 — 0 —69,960 —WA9FTV —IL —100 —39 — 0 —19,500 *KC5DX —XC5DX —X	W3ST	-PA	-374 -53 -3 $-104,720$	N5AFV	-TX	-126 - 37 - 0 - 23,310	*EA3CCN	—Spain — 56 — 0 — 13 — 3,640
'W9RE -IN -383 -46 2 91,920 VE4RP -MAN -110 -40 1 -22,550 WVE Multi-Operator 'AF1T -NH -363 -46 0 83,490 K2FL -NJ -128 -34 1 -22,550 WVE Multi-Operator 'W2FJ -NJ -328 -46 1 80,360 'N5ACP -NM -106 -42 0 -22,260 'WASPL -NY 879 -56 -18 -325,230 'KD4NI -VA -338 -46 0 77,740 VE4QZ -MAN -114 -39 0 -22,230 'WASPL -NY 879 -56 -18 -325,230 'VE7CRU -BC -301 -51 0 76,755 'VE1BPY -PEI -113 -29 1 -22,035 'WACN -KY 890 -57 7 -289,600 'KACNW -SC -311 -46 1 73,085 KBHF	*KA1PE	-ME	-349 - 50 - 5 - 95,975	*N7AEH	-OR	-111 - 41 - 0 - 22,755	*OK1JDX	-Czech 26 - 0 -12 - 1,560
K6HNZ CA 353 - 52 - 0 - 91,780 VETERY BC -110 - 40 - 1 - 22,550 W/VE Multi-Operator 'AF1T NH -363 - 46 - 0 - 83,490 K2FL NJ -128 - 34 - 1 - 22,400 'K8ND OH -1001 - 57 - 9 - 330,330 'W2FJ NJ -328 - 46 - 1 - 80,360 'N5ACP NM -106 - 42 - 0 - 22,260 'WA2SPL NY 879 - 56 - 18 - 325,230 'KD4NI -VA -338 - 46 - 0 - 77,740 VE4QZ -MAN - 114 - 39 - 0 - 22,230 'WB&BBM -OH -897 - 57 - 7 - 289,600 'VE7CRU -BC -301 - 51 - 0 - 76,755 'VE1BPY -PEI - 113 - 29 - 1 - 22,035 'W4CN -KY -890 - 57 - 4 - 271,450 'W1YN -MA -310 - 44 - 4 - 74,400 WD8MRF -OH -120 - 36 - 0 - 21,600 'N7DF -KS -664 - 57 - 2 - 195,880 'K4CNW -SC -311 - 46 - 1 - 73,085 K8HF -OH -113 - 38 - 0 - 21,470 'KB0TJ -CO -586 - 56 - 4 - 175,200 'NF4F -TN -318 - 44 - 0 - 69,960 WA9FTV -IL -100 - 39 - 0 - 19,500 'KC5DX	WOPJV	—IA	-335 -54 -3 $-95,475$	KC8A	-MI	-126 - 36 - 0 - 22,680	*LU9EIE	-Argentina - 1 - 1 - 0 - 5
**AF1T	*W9RE	-IN	-383 - 46 - 2 - 91,920	VE4RP	-MAN	1 - 110 - 40 - 1 - 22,550		
*W2FJ -NJ -328 -46 - 1 - 80,360	K6HNZ	-CA	-353 - 52 - 0 - 91,780	VE7ERY	-BC	-110 - 40 - 1 - 22,550	W/VE Multi-	Operator
*W2FJ -NJ -328 -46 - 1 - 80,360	*AF1T	-NH	-363 - 46 - 0 - 83,490	K2FL	-NJ	-128 - 34 - 1 - 22,400	**K8ND	-OH -1001 -57 - 9 -330,330
*KDANI	*W2FJ	-NJ	-328 - 46 - 1 - 80,360	*N5ACP	-NM	-106 - 42 - 0 - 22,260		
*VE7CRU — BC — 301 — 51 — 0 — 76,755 *VE1BPY — PEI — 113 — 29 — 1 — 22,035 *W1YN — MA — 310 — 44 — 4 — 74,400 *WBMRF — OH — 120 — 36 — 0 — 21,600 *K4CNW — SC — 311 — 46 — 1 — 73,085 *K8HF — OH — 113 — 38 — 0 — 21,470 *VE3INQ — ONT — 264 — 51 — 2 — 69,960 *VE1YX — NS — 249 — 47 — 9 — 69,720 *WACN — KBCV — MI — 99 — 34 — 0 — 16,830 *WACN — KY — 890 — 57 — 4 — 271,450 *KB0TJ — CO — 586 — 56 — 4 — 175,200 *KC5DX — TX — 523 — 55 — 1 — 146,440 *WE1YX — NS — 249 — 47 — 9 — 69,720 *WB4RCO — GA — 87 — 41 — 0 — 17,835 *WECM — KS — 398 — 53 — 1 — 107,460 *WA1UJU — WI — 296 — 46 — 0 — 68,080 *WATUJU — WI — 296 — 46 — 0 — 68,080 *WB7FDQ — AZ — 286 — 45 — 1 — 65,780 *W3BGN — PA — 305 — 41 — 2 — 65,575 *W4KMS — VA — 82 — 34 — 0 — 13,940 *WB1GMG — VT — 294 — 42 — 0 — 61,740 *AE5H — MS — 246 — 52 — 1 — 65,190 *WB1LH — OH — 266 — 48 — 2 — 65,170 *W3USS — MD — 316 — 39 — 2 — 64,780 *WB1GN — FL — 72 — 31 — 2 — 11,880 *WACN — KY — 890 — 57 — 4 — 271,450 *N7DF — KS — 664 — 57 — 2 — 195,880 *N7DF — KS — 664 — 57 — 2 — 195,880 *KB0TJ — CO — 586 — 56 — 4 — 175,200 *KB0TJ — CO — 586 — 56 — 4 — 175,200 *KC5DX — TX — 523 — 55 — 1 — 146,440 *W6ECM — KS — 398 — 53 — 1 — 107,460 *W92UH — IN — 372 — 52 — 4 — 104,160 *W41ZEB — RI — 322 — 45 — 0 — 75,670 *N24B — VA — 272 — 48 — 0 — 65,280 *N6BSA — CO — 258 — 48 — 0 — 61,926 *WB1GMG — VT — 294 — 42 — 0 — 61,740 *VE1CM — MD — 74 — 33 — 0 — 12,125 *W3USS — MD — 316 — 39 — 2 — 64,780 *WALN — MD — 74 — 33 — 0 — 12,125 *WALN — FL — 72 — 31 — 2 — 11,880 *WACN — KY — 890 — 57 — 4 — 271,450 *N7DF — KS — 664 — 57 — 2 — 195,888 **KBDT — CO — 586 — 56 — 4 — 175,200 **KB0TJ — CO — 586 — 56 — 4 — 175,200 **KB0TJ — CO — 586 — 56 — 4 — 175,200 **KB0TJ — CO — 586 — 56 — 4 — 175,200 **W3USS — MD — 305 — 41 — 0 — 69,960 **WALN — NY — 294 — 42 — 0 — 61,926 **WB1GMG — VT — 294 — 42 — 0 — 61,740 **W3USS — MD — 316 — 39 — 2 — 64,780 **WALN — NY — 258 — 44 — 1 — 57,050 **WALN — NY — 258 — 44 — 1 — 57,050 **WALN — NY — 258 — 44 — 1 — 57,050 **WALN — NY — 258 — 44 — 1 — 57,050 **WALN — NY — 258 — 44 — 1 — 57,050 **WALN	*KD4NI	-VA	-338 - 46 - 0 - 77,740	VE4QZ	-MAN	1 - 114 - 39 - 0 - 22,230	*WB8JBM	-OH - 897 -57 - 7 -289.600
*W1YN -MA -310 -44 - 4 - 74,400	*VE7CRU	-BC	-301 - 51 - 0 - 76,755	*VE1BPY	-PEI	-113 - 29 - 1 - 22,035		
**K4CNW -SC -311 -46 - 1 - 73,085	*WIYN	-MA	-310 - 44 - 4 - 74,400	WD8MRF	-OH	-120 -36 - 0 - 21,600		· · · · · · · · · · · · · · · · · · ·
*NF4F	*K4CNW	-sc	-311 - 46 - 1 - 73,085	K8HF	-OH	-113 - 38 - 0 - 21,470	*KBOTJ	· · · · · · · · · · · · · · · · · · ·
VE3INQ ONT -264 -51 -2 -69,960 *WD4RCO -GA -87 -41 0 -17,835 W0ECM -KS -398 -53 1 -107,460 *VE1YX -NS -249 -47 -9 -69,720 K8CV -MI -99 -34 0 -16,830 *K9ZUH -IN -372 -52 4 -104,160 *WA1UJU -WA1UJU	*NF4F	-TN	-318 - 44 - 0 - 69,960	WA9FTV	-IL	-100 - 39 - 0 - 19,500		
WA1UJU —WI — 296 — 46 — 0 — 68,080 KI7M —OR —108 —30 — 0 — 16,200	VE3INQ	-ONT	-264 -51 - 2 - 69,960	*WD4RCO	-GA	-87 - 41 - 0 - 17,835	WOECM	
WA1UJU -WI -296 -46 - 0 - 68,080 KI7M -OR -108 -30 - 0 - 16,200 WA1ZEB -RI - 322 -45 - 0 - 75,670 MARQM -MI -282 -48 - 0 - 67,680 M9AW -WI - 89 -36 - 0 - 16,020 NZ4B -VA - 272 -48 - 0 - 65,280 W3BGN -PA -305 -41 - 2 - 65,755 W4KMS -VA - 82 -34 - 0 - 13,940 W3BGM -PA -246 -52 - 1 - 65,190 WD8LCN -MI - 65 -38 - 0 - 12,350 W3BGM -OR -266 -48 - 2 - 65,170 W3ICM -MD - 74 -33 - 0 - 12,210 W3USS -MD -316 -39 - 2 - 64,780 M4RRO -CA - 97 -25 - 0 - 12,125 (K3ZJ, op.) K8NJA -FL - 72 -31 - 2 - 11,880 WMIII-Operator	*VE1YX	-NS	-249 - 47 - 9 - 69,720	K8CV	-MI	- 99 - 34 - 0 - 16,830	*K9ZUH	-IN - 372 -52 - 4 -104.160
*WB7FDQ -AZ -286 -45 - 1 - 65,780	WA1UJU	Wi	-296 - 46 - 0 - 68,080	KI7M	-OR	-108 - 30 - 0 - 16,200	*WA1ZEB	· · · · · · · · · · · · · · · · · · ·
W3BGN — PA — 305 — 41 — 2 — 65,575	K8AQM	MI	-282 - 48 - 0 - 67,680	N9AW	-WI	— 89 —36 — 0 — 16,020	*NZ4B	-VA - 272 - 48 - 0 - 65,280
*AE5H —MS —246—52 — 1 — 65,190 WD8LCN —MI — 65—38 — 0 — 12,350 VE2CAR —QUE — 279 —43 — 1 — 61,380 W3ICN —MD — 74 —33 — 0 — 12,210 K5NA —NY — 258 —44 — 1 — 57,050 K8NJA —FL — 72—31 — 2 — 11,880 DX Multi-Operator	*WB7FDQ	-AZ	-286 - 45 - 1 - 65,780	W3ASS	-PA	- 94 -32 - 0 - 15,040	NOBSA	-CO - 258 - 48 - 0 - 61,926
W3ICH —OH —266—48—2—65,170 W3ICM —MD — 74—33—0—12,210 K5NA —NY — 258—44—1—57,050 W3USS —MD —316—39—2—64,780 N4ARO —CA — 97—25—0—12,125 K8NJA —FL — 72—31—2—11,880 DX Multi-Operator		—PA		W4KMS	-VA			
W3ICH — OH — 266—48— 2—65,170 W3ICM — MD — 74—33— 0—12,210 K5NA — NY — 258—44— 1—57,050 W3USS — MD — 316—39— 2—64,780 N4ARO — CA — 97—25— 0—12,125 K8NJA — FL — 72—31— 2—11,880 DX Multi-Operator		-MS					*VE2CAR	-QUE - 279 -43 - 1 - 61,380
(K3ZJ, op.) K8NJA —FL — 72 — 31 — 2 — 11,880 DX Multi-Operator			· · · · · · · · · · · · · · · · · · ·	W3ICM	-MD			· · · · · · · · · · · · · · · · · · ·
(N323, 00.)	*W3USS	-MD	-316 -39 - 2 - 64,780				DY M	orator
W2FCR —NJ —283 —43 — 0 — 60,845 N8OID —MI — 69 —34 — 0 — 11,730 *YU7DJE —Yugoslavia —46 —0 —16 —3,680								
	W2FCR	-NJ	—283 —43 — 0 — 60,845	N8OID	-MI	-69 - 34 - 0 - 11,730	*YU7DJE -	-Yugoslavia —46 —0 —16 —3,680

States and Canada must transmit RST and state or province/territory. All others must transmit RST and consecutive contact number.

MISCELLANFOUS BULES:

The same station may be worked once on each band. Crossmode contacts do not count. Single-operator stations may work 16 hours maximum, while multi-operator stations may operate the entire 24-hour period. Off times are no less than 30 minutes each and must be noted in your log(s).

QSO POINTS:

5 QSO points for contacts with W/VE stations located within the continental United States and Canada. 10 QSO points for all other contacts.

MULTIPLIER POINTS:

1 multiplier point is awarded for each of the 48 continental United States (a District of Columbia contact may be substituted for a Maryland multiplier), Canadian provinces/ter-

ritories, and DX countries worked on each band (excluding US and Canada).

Total QSO points times total multipliers equals claimed score.

CONTEST ENTRIES:

Entries must include a separate log for each band, a dupe sheet, a summary sheet, a multiplier checklist, and a list of equipment used. Contestants are asked to send an SASE to the contest address for official forms.

ENTRY DEADLINE

All entries must be postmarked no later than April 15, 1984.

DISQUALIFICATIONS:

Omission of the required entry forms, operating in excess of legal power, manipulating scores or times to achieve a score advantage, or fallure to omit duplicate contacts which would reduce the overall score more than 2% are all grounds for immediate disqualification. Decisions of the contest committee are final.

Contest awards will be issued in each entry category and operator class in each of the US call districts and Canadlan provinces/territories, as well as in each DX country represented. Other awards may be issued at the discretion of the awards committee. A min-Imum of 25 QSOs must be worked to be eligible for awards.

CONTEST ADDRESS:

RTTY World Championship, c/o The RTTY Journal, PO Box RY, Cardiff CA 92007.

HAM HELP

I desperately need QSL information for the following stations: P29NDX, ZK2DX, SVØAT, FY7BC, 9K2EW, TF3JB, VU2TF, 5N20DOG, TZ4AQS, FK0BW, and 3D2DB. All of the stations were contacted during

> Kenneth Ramirez WB2KQO/KP4 RR 169, Carr. 307 Cabo Rojo PR 00623

I would like to have a schematic of the Southwest Technical Products (SWTPC) 6800 System interface circuit. The unit is designated MP-L and is used to interface parallel devices with the SWTPC 6800

> John H. Davison W6ZFN 316 N. Taylor Ave. Kirkwood MO 63122

W2NSD/1 NEVER SAY DIE

editorial by Wayne Green

from page 6

Now, getting back to education as a product, let's walk this through step by step so you can follow my reasoning. First, 1 hope you'll grant me that 73 has been educational. And perhaps you've noticed that it is fun to read. Well, that's a big key to what I have in mind. I figure that education can be made into a saleable product if it is fun. People will educate themselves if it is more fun to do that than other things. All of my computer magazines are educational and all are fun to read.

The concept of learning because it is fun instead of because one is a prisoner of the system is one which we will gradually have to get used to. I didn't like school much. I didn't like the idea of being forced to attend, whether I wanted to or not. And damned few of the courses were fun. Having enslaved students, the teachers and schools had no need to worry about whether the classes were fun. I was forced to be there by the government whether the classes were fun or not.

What was the most popular television program in England last year? If you missed all the fuss, it was Woodhouse teaching people how to train their dogs. Education-and fun. Got the idea?

Okay, now the next step. I've already written about my plans to start a high-tech college. This school is aimed at helping our country to get back into the high-tech race against Japan and will be set up as a pilot model of a new type of college, geared to the needs of the 80s. But once we have the college going, what better place to start developing the education/fun courses which we may eventually merchandise to the world?

The first step is to develop the new genre of education and put it on video tape. The next is to start selling this via an educational cable television network to get the ball rolling. Then, as video-disk technology is simpler and less costly, move to an interactive video-disk educational system which can be sold anywhere in the world in any language.

The courses should cover everything taught in grade, high, college, and graduate schools. They should go on to those courses which should be taught in school, but aren't. They should also cover business and industrial courses now being taught by businesses. They should cover all aspects of arts and crafts. Anything people may be interested in learning about should be available.

Just as we have several thousand small firms creating wealth for the entrepreneurs who are now producing software for computers, I expect we'll have thousands of small firms producing educational programs which can be distributed by larger firms, creating even more wealthy entrepreneurs

We'll need larger firms to set up and run the distribution. That's where I think my early start with the concept may give me some leverage. In addition to having the major magazines in this new field to help it develop, I'm going to try to build IDG's present network of 42 magazines in 18 countries into an international educational distribution system.

When I think back on my time in college, I can remember one course that actually was fun. Most of them were dreadful bores, alternating memorization with written exams. Maybe it's significant that the teacher of that one exciting course eventually committed suicide. If a teacher can make accounting exciting, anything is possible.

The courses in my college will be modeled after those I took in the Navy, which were fun, and will be nothing like those I suffered in college. These will lay the groundwork for the interactive video-disk courses later on.

My recent editorials have encouraged guite a number of readers to send resumes. Obviously my plans are going to call for help from a large number of dedicated people-talented people, hard-working people. I have the ideas, know how to make them work, and have the money for it, but the end result still lies in the people I can find to make all this happen.



POLYETHYLENE DIELECTRIC RG59/U mil spec 96% shield..... 140/ft RG213 noncontaminating 95% sheild mil spec 36e/tt.
RG114/U mil spec 96% shield mil spec 36e/tt.
RG11U 96% shield, 75-ohm mil spec 25e/tt.
RG80 96% shield, mil spec 25e/tt.
RG68AU double shield, 75-ohm 25e/tt.
RG68AU stranded mil spec 12e/tt.
RG58 mil spec 96% shield 11e/tt.

LOW LOSS FOAM DIELECTRIC RG8X 95% shield.... RG59/U 70% copper braid.... ... \$14.95/100 ft. or 17g/ft. ...9¢/ft. .18¢/ft. .07¢/ft. RG8U 80% shleid... RG58U 80% shleid. RG58U 95% shleid. 10e/ft 36c/ft. RG58U #9201 Grounding strap, heavy duty tubular braid 3/16 in. tinned copper 10e/ft. 3/8 in. tinned copper 30c/ft.

CONNECTORS MADE IN USA

Amphenol PI-259 .79€ PL-259 Teflon/Silver \$1.59 PL-259 Teflon/Silver
PL-259 upsh-on adapter shell
PL-259 & SO-239
Double Mate Connector
PL-258 Double Female Connector
If patch cord w/RCA type plugs each end
Reducer UG-175 or 176
UG-255 (PL-259 to BNC)
Elbow /M359) 10/\$3.89 10/\$5.89 ..\$1.79 ..98¢ 3/\$1.00 10/\$1.99 \$2.95 \$1.79 Elbow (M359).
F59A (TV type)
UG 21D/U Amphenol Type N Male for RG8.
BNC UG88C/U, male. 10/\$2.15 \$3.00 \$1.25 3/16 Inch Mike Plug for Collins etc. UG273 BNC to PL-259 \$3.00

FREE CATALOG
COD add \$2.00—FLA. Res. add 5% Sales Tax

Rotor Cable 8-con. 2-18 ga. 6-22 ga Orders under \$30.00 add \$2.00 Connectors—shipping 10% add'l, \$3.00 minimum V 412 Cable-Shipping \$3.00 per 100 ft. 12240 NE 14th Ave., Dept. 73, No. Miami, FL 33161 Call (305) 893-3924



Missing those weak ones? Become an elephant with new ears. Models available from 28-220 MHz bands. Simply Insert between your transceiver and antenna, apply 12 VDC and enjoy. Standard SO-239 connectors on RF ports - BNC available. Typical performance at 144 MHz: 1.4 dB NF 10 dB gain, Low noise performance from Lunar - simply, the best.



2775 Kurtz Street, Suite 11 San Diego, Ca 92110 (619) 299-9740 • Telex 181747

DX

Chod Harris VP2ML Box 4881 Santa Rosa CA 95402

THE SOUTHERNMOST AMATEUR IN THE UNITED STATES

A DXer in Hawaii has some of the best of both worlds: He's a DXer himself and has a good DX location as well. Hawaii counts as a separate "country" for DXCC, and although not hard to work, Hawaiian amateurs are more rare than Texas stations, for example. And Hawaii is far enough south to make it one of the best radio locations in the United States. On the southern island of the Hawaiian chain, at the southernmost tip of the island, resides Dean Paterson KH6OA.

Dean Paterson KH6OA enjoys a beautiful condominium overlooking the black sand beaches of the Island of Hawaii in addition to the excellent radio propagation associated with the tropics. On the other hand, Dean feels the same restrictions as other apartment-bound hams: no outside antennas and TVI complaints. His solutions might inspire some DXers whose antennas weren't big enough to come down last winter.

Dean's fascination with radio began at the age of 9 with his first crystal set. However, It was 1973 before he received his first amateur-radio license. At that time, his main interest was rebuilding ARC-5 military radios. A few years later, Dean found himself moving to Hawaii into a condominium complex managed by his wife.

As is common with such projects, the sale-and-lease agreements prohibit any outside antennas. So Dean took advantage of the isolated location of the complex and the unpredictable nature of Hawali's voicances and volunteered to provide emergency communications for the complex if he could have an antenna outdoors.

The owners of the condominium complex agreed to an unobtrusive vertical right outside Dean's door in the bottom corner of the complex. That proved to be enough.

Dean pounded a steel stake a couple of feet into the hard lava and attached a Hustler vertical. A few radials stretch under the vegetation, but the building blocks many of the possible radial directions. Not the best antenna system, but adequate.

To provide true emergency communications, Dean assembled a 12-volt, 2-Amp solar panel with two batteries to give 18 hours of operation. 12-volt, 2-meter rigs and low-band gear complete the emergency station.

The two-meter antenna was another problem. The main repeater on Hawaii, the one that connects into the network which serves the entire Hawaiian chain, was on the other side of the Island. Dean could hit the repeater with an 11-element beam, but he couldn't get permission to erect it. He finally settled for an indoor setup. The first four elements of the beam attach to the ceiling-fan support above his head. The four elements and an 80-Watt amplifier provide a copyable—signal through the massive Mauna Loa volcano.

To complete his antenna farm, Dean stretched a 60' longwire along the edge of the property to improve signals on the Big Island Emergency Nets on 40 and 80 meters. You really have to look closely to spot it, so it probably falls into the "Invisible-antenna" category.

But the antenna restrictions were not the only problems in Murphy's bag of tricks. Dean soon discovered that the combination of salt spray and tropical sun dissolves antennas in months. He recently installed his third vertical in 6 years. He says his present antenna, a Butternut, is "the best vertical I've ever had, by far!"

Even that was not the end of his problems, however. Dean suffers from a common problem among apartment-dwelling hams: lack of ground. Electrical ground, that is. The hard lava of Hawaii doesn't conduct at all, and the 3" layer of top soil trucked in to grow grass is not much help. Television interference (TVI) and radio frequency interference (RFI) were, and continue to be, a serious problem.

His remote location, miles from the only television transmitters on the Island, means signals in the community cable-



SM3CXS, who handles the QSLs for SM0AGD on his far-flung travels, met some of the DXers he has helped over the years at the Dayton Hamvention. Photo via The DXers Magazine.

television system are marginal at best. Dean employs three Drake low-pass filters on his HF gear, and he uses toroids liberally on all power cords. But even so, he says, "If there's a football game on, I either have to go QRP or get off the air entirely."

Dean has turned this restriction into an avocation and has become a QRP enthusiast, using an Argonaut 515. He overcomes the difficult combination of apartment-style antennas and QRP power with two important advantages: his southern location and the KH6 calisign.

The low latitude means greatly enhanced radio propagation. Anyone who has operated from the tropics knows what this means: The bands open earlier in the day and close later at night. Signals from the north are much stronger than similar signals from the east or west. This tropical advantage helps to compensate for increased static and reduced grey-line communications.

And that KH6 callsign is good for a few decibels, Dean concurs. In a recent pileup on a Hong Kong station, Dean tried calling "QRP" In the pileup, without success. Then he tried "KH6" and got right through!

Dean's success with QRP shows in his results: Worked All States and Worked All Continents on QRP. He lacks only a few confirmations before earning his DXCC with 5 Watts or less.

THE CARE AND FEEDING OF QSL MANAGERS

"Thanks for the contact, and please OSL through my manager, K1RH." How often have you received a DX OSL card through a OSL manager? These dedicated volunteers who facilitate the exchange of OSLs are the unsung heroes of the DX world. Treat them well, as they make the task of collecting DX OSLs more efficient and much less expensive.

Let's look first at how a QSL manager operates, and then we'll see what we can do to make his or her task easier to speed our return QSL.

A QSL manager serves as a go-between for the DX station and the hams who work that DX station. After an amateur works the DX station, he sends the QSL card and a self-addressed, stamped envelope (SASE) to the manager. The manager confers with the DX station, checks that the contact is in the log, and fills out and mails the DX QSL.

There are many advantages to this process over direct QSL exchange with the DX station, First, the QSL manager is usually a stateside ham, so the problems and expense of airmail overseas are greatly reduced. No matter how much you criticize the US Postal Service, they do a remarkable job, especially compared to POs in tiny, out-of-the-way DX locations. In the Galapagos Islands, for example, the mail is handed to any boat going in the right direction from the airport toward the only town. If that ship decides to change course, the mail could be delayed for months, if it ever arrives. QSL exchange with a stateside (or European or Japanese) manager eliminates this risk, is potentially faster than overseas mail, and is much less expensive.

The use of QSL managers simplifies the preparation of your own SASE. Stateside hams can usually use US postage, or, in the case of European or Japanese managers, can use a Green Stamp (US \$1 bill), IRCs, or airmail stamps of that country from a DX stamp service.

So QSL managers make QSL exchange faster, cheaper, and more reliable for the DXer, QSL managers are also of benefit to the DX station. The DX station is relieved of the burden of handling volumes of mail. opening, sorting, etc., as well as the task of filling out the cards, stuffing the envelopes, and mailing. Also, the DX station's QSLs are safer in the States than in his own country. Bob YS9RVE once lost all his QSLs, including some excellent 80meter DX, in a riot. And few DX stations want to trust several years worth of work in the form of DX QSLs to the international postage system. So when a DX station applies for an award (and they do, you know), the QSL manager can send in the cards, a much safer and more reliable procedure.

Are there any disadvantages to the use of a QSL manager? The major problem with QSL managers is that the logs are in one remote location and the cards are in another. Somehow the DX station must get his or her log information to the QSL manager to check the contacts. If the DX station mails the logs to the manager, you are right back to trusting the erratic Inter-



Dean Paterson KH6OA, the southernmost amateur in the United States, operates this well-equipped station into a vertical, a longwire, and other hidden apartment-style antennas.

national postal system. Mail to Pitcairn Island, for example, depends on infrequent visits by yachts and cruise ships. Also, the logs can take months to reach the manager, who obviously cannot answer the QSL until he or she receives the logs.

Fortunately, there is another way the QSL manager can get the log information from the DX station; on the air. To take a typical example, let's look at how a state-side station would get a VP2ML QSL card. After the DXer works VP2ML and hears "QSL via K1RH," he fills out his QSL and puts it and an SASE in an envelope addressed to K1RH. When Ralph Hirsch K1RH receives the envelope, he opens it and sorts the contacts into date and time order, just like a logbook, until his next schedule with VP2ML.

During the on-the-air schedule, Raiph reads the date, time, and callsign. VP2ML checks his logbook and returns with the band, emission, and report, entering a checkmark in the log for "OSLed." Ralph confirms the band and emission and writes the report in pencil on the incoming OSL card. He then goes to the next card.

With practice, this procedure can be very fast. The on-the-air time to confirm the contact can be a matter of a few seconds, although Ralph still has more work after the contact with VP2ML. Ralph takes the stack of checked, incoming QSL cards and types out a stack of VP2ML cards, reading the reports from his note on the

card. He then puts the blue VP2ML card into the SASE provided and drops it in the mall

This procedure works so well that some DXers get their VPZML cards within days of their contact. The DXer sends his card and SASE the same day as the contact with VP2ML. Ralph receives the card the next day, confirms the contact in the sked with VP2ML that night, and mails the return card later that evening. The DXer gets his VP2ML card back the next day, less than 48 hours after the contact!

Of course, all this supposes everything goes well. Reality seldom achieves this ideal. What can go wrong? The worst problem is poorly filled out incoming QSLs, especially those with bad dates and times.

VP2ML keeps his log in Coordinated Universal Time (UTC), as just about every DX station must. If the incoming QSL card has local dates and times or has miscalculated the UTC date or time, quick confirmation of the contact is impossible. VP2ML must search the log for the callsign, often over a span of several pages. If there are many other QSL cards awaiting responses, any card with incorrect information goes to the bottom of the pile for another day.

The most common date/time error is to forget to advance the day to the next UTC day during local evening operation. The next most common problem is miscalculating the time difference between UTC

and local time, either adding the wrong number of hours or subtracting instead of adding.

This became so much of a problem for Ralph that he made a rubber stamp saying that he was unable to locate the contact in the VP2ML log at the date and time specified and suggesting the amateur check his OSO information again, especially the date and time.

There is really no excuse for date/time errors of this sort. Anyone interested in DX should have a clock reading UTC by the rig and keep their entire log in UTC. You can buy a tiny, stick-on digital clock for a couple of dollars. Set it to UTC and use it for all your amateur contacts. The QSL managers will love it.

Another problem which slows confirmation is multiple contacts on a single card. This card is first filed under the first contact time. But after this contact is checked, the card must be refiled into date/time order for the next contact. This increases the on-the-air time and increases the chance that interference or fading will end the schedule for that day.

Some OSL managers, including Ralph, handle cards for more than one DX station. The best way to address the envelope to the manager is to give both the DX station's call and that of the manager. YP2ML c/o K1RH OSL Manager. Then the manager can immediately sort the cards for the different stations he serves.

And finally, a short note thanking the

4) The Leonids meteor

November

5)

shower occurs in

Meteors form an

ionized trail in the

QSL manager for his services would gladden the heart of many an under-appreclated manager. These volunteers receive nothing tangible for their efforts. They are not paid, and the few dollars which do arrive with the cards barely cover printing and postage.

So why would anyone want to handle the QSL card for a DX station? A QSL manager gets a modicum of publicity for his work, especially if he handles major DX-peditions, such as SM3CXS who handles the cards for Eric SM0AGD on his far-reaching travels. But the real satisfaction comes from the service these amateurs provide to the rest of the DX community.

Have you ever considered handling the cards for a DX station yourself? Consider these qualifications for a good manager: The QSL manager should not move around, so his or her address is good in old, new, and future callbooks. The manager should have a good enough station to maintain communication with the DX station under a variety of conditions. month after month. And the manager should be willing to work hard for remarkably little reward. Infinite patience, the ability to decipher hieroglyphic handwriting, a little ESP (for the QSL cards without date), and an understanding postman are useful but not essential additional qualifi-

Be kind to your friendly QSL manager; he or she makes your DXing a lot more pleasant.

FUN!

John Edwards KI2U PO Box 73 Middle Village NY 11379

SPACE COMMUNICATIONS

This is shaping up to be quite a year for amateur radio and space communications. With the launch of Phase III OSCAR and W5LFL's little DXpedition into the final frontier, future ham historians may well peg 1983 as a turning point in the development of the hobby.

I, for one, can't wait until amateur space communications really take off. At age 28, I'm still hoping to see the day when hams collect planets and space settlements the way we currently chase after new countries. Imagine heading down to your local ham club to compare QSLs from Mars, Titan, and Europa. Think of the picture possibilities on those pasteboards!

Of course, some things won't change. We'll probably still be grumbling about slow OSL bureaus, DX nets, and pileups. But like today, the excitement will be worth all the hassles. At least the weather reports should be interesting, for a change.

Let's get going and leave the rest to squabble about code/no code.

ELEMENT 1 MULTIPLE CHOICE

- 1) A blue whizzer is:
- A meteor that creates a very strong ion trail
- 2) The name of a new privately-funded amateur satellite

- The name of Phase III OSCAR's mode A transponder
- 4) A type of space antenna
- 2) OSCAR 6's 10-meter antennas were made out of:
 - 1) Tin
 - 2) Silver
 - 3) Molybdenum
- A disassembled pocket rule
 Owen Garriott's son has also made quite a name for himself. He is:
 - 1) Also an astronaut
 - 2) General Manager of the ARRI
- A best-selling computer game designer writing under the pseudonym, "Lord British"
- 4) A pro tennis player
- 4) On which one of the following dates did amateurs first bounce a signal off of the Moon:
 - 1) July 4, 1976
 - November 21, 1954
 December 4, 1934
- 4) January 27, 1953
- 5) OSCAR 1 was launched from
 - 1) Cape Kennedy
 - 2) Cape Canaveral
 - 3) Edwards Air Force Base
 - 4) Vandenberg Air Force Base

ELEMENT 2 TRUE-FALSE

		i rue	raise	
1)	OSCAR 1's output			
	was 10 Watts.			
2)	OSCAR 5 was built			
	in Australia.			
3)	A Technician-class			
	amateur may be a			,
	satellite trustee.			

- troposphere. The first successful EME transmission used the old 5-meter band. No amateur satellites were launched In 1965 through OSCAR 8 travels in a north-to-south orbit. One needs to run at least 1000 Watts in order to access OSCAR. 10) In ham satellite ter-
- 10) In ham satellite ter minology, LOS stands for "linked oscillator system."

ELEMENT 3 SCRAMBLED WORDS

Unscramble these space communication terms:

REOTEM SASBPNDA
PLOPRED YRTTELEME
KLINWODN ETILLEAST
DEOM NOCABE
ELTTUHS TRHAE
LOPRA GINP

THE ANSWERS

Elèment 1:

- 1—1 Some have been known to reflect signals for up to two minutes.
- 2-4 Cheap, but practical.
- 3-3 No, he didn't write Space Invaders.
- 4-4 Ross Bateman W4AO and William Smith W3GKP did the deed.

5—4 Personally, I've always had a soft spot for oi' Edwards.

Element 2:

- 1—False One-tenth of a Watt. Good antenna height heips.
- 2—True University of Melbourne, to be precise.
- 3—False Extras only, according to the FCC.
- 4—True November 14-18.
- 5-False lonosphere.
- 6-False It was on 2 meters.
- 7—True Dry spell.
- 8-False Depends which side of the world you're on.
- 9—False Hardly, 100 Watts ERP is more like it.
- 10-False "Loss of signal."

Element 3:

(Reading from left to right): METEOR, PASSBAND, DOPPLER, TELEMETRY, DOWNLINK, SATELLITE, MODE, BEA-CON, SHUTTLE, EARTH, POLAR, PING.

SCORING

Element 1:

Six points for each correct answer. Element 2:

Three and one-half points for each correct answer.

Element 3:

Three points for each term unscrambled.

Where do you stand in the radio space

race? 1-20 points—Stuck on the

launch pad

21-40 points—Still listening for Sputnik

41-60 points—Confuse OSCAR signals for a

band opening 61-80 points—Satellite Communi-

cator's Club member

81+ points—OSCAR DXCC certificate holder



Fact #2: There is a direct correlation between store traffic and sales-increase the number of people coming through your door and you'll increase sales.

Fact #3: Fact #1 + Fact #2 = INCREASED \$ALE\$, which means more money for you. And that's a fact. For information on selling 73, call 800-343-0728 and speak with Ginnie Boudrieau, our bulk sales manager. Or write to her at 73, 80 Pine St., Peterborough, NH 03458.

Amateur Radio's Technical Journal

80 Pine Street Peterborough, NH 03458 800-343-0728

miss a single issue of 73.

Attach old label where indicated and print new address in space provided. Also include your mailing label whenever you write concerning your subscription. It helps us serve you promptly. Write to:

Amateur Radio's Technical Journal

Subscription Department P.O. Box 931 Farmingdale NY 11737

Extend my subscripti	on one additional	year for	only \$19.97
Payment enclosed	☐ Bill me		

,	, p	OLD uddress he
Name		
Address		
City	State	Zip
p	rint NEW address	here:
Name	7	
Address		
City	State	Zip

MAKE SAVING MONEY A WAY OF LIFE

With LIVING ON A SHOESTRING: A Scrounge Manual for the Hobbyist. Almost anything you find can be put to good use if you follow the techniques of a master scrounger. George Ewing WA8WTE shows you how to:

- Find electronic parts
- Locate tools and other surplus
- Scrounge by the rules
- Read up on scrounging
- Scrounge a vehicle
- Scrounge a place to live

Cartoons and case histories of scroungers add a humorous touch. With LIVING ON A SHOESTRING, you can't always get something for nothing, but you can certainly get it fo

less. \$7.97 Softcover, 7 x 9, 128 pp. approx..


ISBN 0-88006-059-X

Call TOLL FREE 1-800-258-5473 for credit card orders. Or mail you order with payment or complete credit card information. Include \$1.50 for shipping and handling. Send to:

Wayne Green Inc. Attn: Book Sales Peterborough, NH 03458

A Wayne Green Publication

Dealer Inquiries Invited

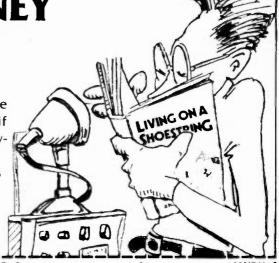

ľ	YES, I want to scrounge! 33NB	6L
Ì	Send me copies of LIVING ON A SHOESTRIN	G.
1	Enclosed is \$7.97 (BK7393) per copy plus \$1.5	50
r	shipping and handling.	
e	□ MASTERCARD bank # □VISA □ AN	1EX
ŀ	Card#Expires	
ľ	Signature	
i	Name	
i	Address	
d i	City State and ZIp	
_ =		_

RADIO BOOKSHOP

VHF ANTENNA HANDBOOK.—The new VHF Antenna Handbook details the theory, design and construction of hundreds of different VHF and UHF antennas...a practical book written for the average amateur who takes joy in building. Not full of complex formulas for the design engineer. Packed with fabulous antenna projects you can build. BK7368 \$5.95.

THE COMPLETE SHORTWAVE LISTENER'S HAND-BOOK, 2nd Edition by Hank Bennett and Harry L. Helms. This comprehensive volume contains loads of new information from all over the world on the latest developments in SWL technology clubs, associations, practices and stations. A thorough guide to stations of the world by general continental area and frequency is included. BK1241 \$9.95.



IC OP.AMP COOKBOOK—by Walter G. Jung. Covers not only the basic theory of the IC op amp in great detail, but also includes over 250 practical circuit applications, Ilberally Illustrated. 592 pages, $5\frac{1}{2}\times8\frac{1}{2}$, softbound. BK1028 \$14.95.

EVERYTHING YOU ALWAYS WANTED TO KNOW ABOUT AMATEUR TELEVISION, (but were afraid to ask)—By Mike Stone WB@QCD. This book is a complete guide to settling up your own amateur radio television station. It contains—A history, what equipment you need, video theory, cameras, recorders, lightling, special effects, sound ATV DXIng, mobile FSTV, ATV repeaters, ATV groups, building projects, test equipment, dealer directory, a cumulative index of over 1000 articles on amateur TV and much more. This is the new, 1982 edition. From the publishers of Amateur Television Magazine. BK1244 \$9.95

THE MAGIC OF HAM RADIO—by Jerrold Swank W8HXR. Under various callsigns, W8HXR has been heard on the ham bands since 1919. He has watched amateur radio grow from the days of Model A spark coils to an era of microprocessors and satellite communications. Jerry has responded to calls for help from earthquake-striken Managua and tornado-ravaged Xenia. Antarctica, one of man's lonellest outposts, has been a bit less lonely, thanks to Jerry's tireless phonepatching efforts. Drawing on his own colorful experiences and those of many other hams, Jerry has compiled this word-picture of ham radio during the past six decades. BK7312 \$4.95

PROPAGATION WIZARD'S HANDBOOK— by J. H. Nelson. When sunspots riddled the worldwide communications networks of the 1940s, John Henry Nelson looked to the planets for an answer. The result was a theory of propagation forecasting based upon interplanetary alignment that made the author the most reliable forecaster in America today. The book provides an enlightened look at communications past, present, and future, as well as teaching the art of propagation forecasting. BK7302 \$6.95.

TOOLS & TECHNIQUES FOR ELECTRONICS—by A. A. Wilcks is an easy-to-understand book written for the beginning kit-builder as well as the experienced hobbyist. It has numerous pictures and descriptions of the safe and correct ways to use basic and specialized tools for electronic projects, as well as specialized metal-working tools and the chemical aids which are used in repair shops BK7348 \$4.95."

70 YEARS OF RADIO TUBES AND VALVES—by John Stokes "Great, the best book on the history of radio tubes that I've èver seen!" raved 73's technical editor. Written by an expert who has been involved in radio since '29, this book will be of special interest to "old-timers" and will provide those younger hams with a unique sense of the history of their hobby. BK1272

SSB... THE MISUNDERSTOOD MODE—by James B. Wilson. Single Sideband Transmission... thousands of us use it every day, yet it remains one of the least understood facets of amateur radio. J. B. Wilson presents several methods of sideband generation, amply illustrated with charts and schematics, which will enable the ambitious reader to construct his own sideband generator. A must for the technically-serious ham. BK7351 \$5.50.

THE CONTEST COOKBOOK.—This book reveals the secrets of that ellte group of operators who top the list when the contest results are published. It contains detailed suggestions for the first-time contester as well as tips for the advanced operator. Domestic, DX, and specialty contests are all discussed, complete with photographs and diagrams showing the equipment and operating alds used by the top scorers. For the serious contester, BK7308 \$5.95.

A GUIDE TO HAM RADIO—by Larry Kahaner WB2NEL. What's Amateur Radio all about? You can learn the basics of this fascinating hobby with this excellent beginner's guide. It answers the most frequently asked questions in an easy-going manner, and it shows the best way to go about getting an FCC Ilcense. A Guide to Ham Radio is an ideal introduction to a hobby enjoyed by people around the world. BK7321 \$4.95.*

OWNER REPAIR OF RADIO EQUIPMENT—by Frank Glass K6RQ. Here's a book that will teach you an approach to troubleshooting without a shack full of test equipment. Written in a narrative, non-mathematical style, it will encourage you to successfully fix your own rig problems 80 to 90% of the time. Even if you don't want to fix, you can learn a lot about how things work and fall. Add to your library and personal expertise. BK7310 \$7.95.*

THE 73 TEST EQUIPMENT LIBRARY

VOL. II AUDIO FREQUENCY TESTERS—Jam-packed with all kinds of audio frequency test equipment. If you're into SSB, RTTY, SSTV, etc., this book is a must for you... a good book for hi-fi addicts and experimenters, too! LB7360 \$1.95.*

VOL. III RADIO FREQUENCY TESTERS—Radio frequency waves, the common denominator of amateur radio. Such Items as SWR, antenna impedance, line impedance, RF output, and fleld strength; detalled instructions on testing these items includes sections on signal generators, crystal calibrators, grid dip oscillators, noise generators, dummy loads, and much more. LB7361 \$1.95.*

VOL, IV IC TEST EQUIPMENT—Become a troubleshooting wizard! Here are 42 home construction projects for building test equipment to work with your ham station and in servicing digital equipment. Plus a cumulative index for all four volumes for the 73 TEST EQUIPMENT LIBRARY. LB7362 \$1.95.*

ALL THREE OF THE ABOVE ONLY \$4.95 ORDER LB7365

RF AND DIGITAL TEST EQUIPMENT YOU CAN BUILD—BK1044—Rf burst, function, square wave generators, variable length pulse generators—100 kHz marker, i-f and rf sweep generators, audio osc, aft/rf signal injector, 146 MHz synthesizer, digital readouts for counters, several counters, prescaler, microwave meter, etc. 252 pages. BK1044 \$5.95.

BEHIND THE DIAL—This book explains, in detail, what's going on on all the frequencies, from shortwave up to microwave. It gives the reader a good idea of what he can find and where to find it, including some of the secret stations such as the C.I.A. and the F.B.I. Everything is covered short of microwave monitoring. Anyone interested in purchasing a shortwave receiver should have a copy of this book, surveillance, station layout consideration, antenna systems, interface, and the electromagnetic spectrum, are included.

BK7307 \$4.95

WORLD PRESS SERVICE FREQUENCIES—by Thomas Harrington Can't walt to hear the evening news, or are you wondering about the news that you aren't hearing? Receive by Radio Teletype (RTTY) all the world news and financial happenings from the world capitols on a 24 hour a day basis. This book gives you the frequencies and times of broadcast of such news services as AP, UPI, Reuters, TASS, VOA and London Press. Also included is an introduction to RTTY with information on equipment, antennas, abbreviations—everything you need to get started in RTTY.

INTERFERENCE HANDBOOK—by William R. Nelson, WA6EOG—This timely handbook covers every type of RFI problem and gives you the solutions based on practical experience. Covers interference to TV, radio, hl-fit, telephone, radio amateur, commercial and CB equipment. Power line interference is covered in depth—how to locate it, cure it, work with the public, safety precautions, how to train RFI Investigators. Written by an RFI expert with 33 years of experience, this profusely illustrated book is packed with practical easy-to-understand information. BK1230 \$11.95

THE NEW WEATHER SATELLITE HANDBOOK—by Dr. Ralph E. Taggart W88DQT. Here is the completely updated and revised edition containing all the information on the most sophisticated and effective space-raft now in orbit. This book serves both the experienced amateur satellite enthusiast and the newcomer. It is an introduction to satellite watching, providing all the information required to construct a complete and highly effective ground station. Solid hardware designs and all the instructions necessary to operate the equipment are included. For experimenters who are operating stations, the book details all procedures necessary to modify equipment for the new series of spacecraft. Amateur weather satellite activity represents a unique blend of interests encompassing electronics, meteorology and astronautics. Join the privileged few in watching the spectacle of earth as seen from space on your own monitoring equipment. BK7383 \$8.95.

AROUND THE WORLD

WORLD REPEATER ATLAS—Completely updated, over 230 pages of repeater listings are indexed by location and frequency. More than 50 maps pinpoint 2000 repeater locations throughout the USA. Foreign listings include Europe, the Middle East, South America, and Africa. BK7315 \$2.00

WORLD WIDE RADIO TELETYPE STATIONS IN FREQUENCY ORDER—8th EDITION Compiled by Universal Electronics, Inc. Contains 2198 frequencles of stations that have been logged in 1982. Frequency, call sign, name of station, ITU country symbol, times of reception and details are included. All types of RTTY stations are listed including schedules of 82 press and news agencies operating on 637 frequencies. Covers 77 meteorological stations on 279 frequencies. Covers all RTTY stations from 3 MHZ to 30 MHZ, air, metro, government, military, diplomatic, covers all services. This is the most accurate RTTY list there is and a must for the serious RTTY enthusiast. BK1270 \$10.95.

WORLDWIDE RADIO TELETYPE CALL SIGN LIST OF UTILITY STATIONS—8th EDITION Compiled by Universal Electronics, Inc. Contains more than 4000 call signs in alphanumerical order. All types of stations are listed. 183 utility station memonics and name abbreviations. Plus abbreviations for regional states in Australia, Canada, USA and USSR. All ITU Symbols designating countries or geographical areas. Table of allocation of international call sign series. Revised radio regulations on indentification of stations, including formation or call signs. All services listed. BK1271 \$4.95


WORLD RADIO TV HANDBOOK 1983, 26TH EDITION
—This book is the bible of international broadcasters, providing the only authoritative source of exact information about broadcasting and TV stations world wide. This 1983 edition is completely revised, giving comprehensive coverage of short, medium and long wave, 560 pages of vital aspects of world listening. BK1184 \$16.50

*Use the order card in this magazine or Itemize your order on a separate piece of paper and mall to: 73 Radio Bookshop • Peterborough NH 03458. Be sure to include check or detailed credit card information. No C.O.D. orders accepted. \$1.50 for the first book, \$1.00 each additional book for U.S. delivery and foreign surface. For foreign airmall \$10.00 per book. Please allow 4-6 weeks for delivery. Questions regarding your order? Please write to Customer Service at the above address. (Prices subject to change on books not published by 73 Magazine.)

FOR THE NOVICE

New, updated editions of our famous novice

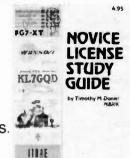license study guide and novice study tapes.




- NOVICE LICENSE STUDY GUIDE—by Timothy M. Daniel N8RK. Here is the most up to date novice guide available. It is complete with information about learning Morse Code, has the latest FCC amateur regulations and the current FCC application forms. This guide is not a question/answer memorization course but rather it emphasizes the practical side of getting a ham license and putting a station on the air. It reflects what the FCC expects a Novice to know without page after page of dull theory. The most current information still available at last year's price. SG7357 \$4.95.*
- NOVICE STUDY TAPES—If you are just getting started in ham radio, you'll find these tapes indispensable! This up-to-the-minute revision of the 73 Study Course is the perfect way to learn everything you need to breeze through the Novice written exam. Theory, FCC regulations, and operating skills are all covered, and you'll be amazed at how fast you learn using these tapes!
 Once the test is behind you, these tapes will go right on being useful, because they are packed with the latest information on setting up your own ham station, and getting on the air.
 Thousands of people have discovered how easy learning from cassette can be—order now and enter the fascinating world of ham radio! CT7300 Set of 3—\$15.95.*

Scientists have proven that you learn faster by listening than by reading because you can play a cassette tape over and over in your spare time—even while you're driving! You get more and more into each time you hear it. You can't progress without solid fundamentals. These three hour-long tapes give you all the basics you'll need to pass the Novice exam easily. You'll have an understanding of the basics which will be invaluable to you for the rest of your life! Can you afford to take your Novice exam

Special Offer! Both Novice License Study Guide and Novice Study Tapes \$19.95 Order NP7300.

GENERAL LICENSE STUDY GUIDE

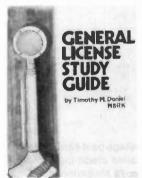

GENERAL LICENSE STUDY GUIDE—By Timothy M. Daniel N8RK This is the complete guide to the General License. Learning rather than memorizing is the secret. This is not a question-andanswer guide that will gather dust when the FCC issues a new test. Instead, this book will be a helpful reference, useful long after a ham upgrades to General. Includes up-to-date FCC rules and an application form. Order yours today and talk to the world. SG7358 \$6.95

Style W

W2ASD/I

Style X

• QSL CARDS—73 turns out a fantastic series of QSL cards at about half the cost of having them done elsewhere because they are run as a fill-in between printing books and other Items in the 73 Print Shop. 250 Style W—QW0250—for \$8.95': 500 Style W—QW0500—for \$13.95': 250 Style X—QX0500; 250 Style Y—QY0250—for \$8.95': 500 Style X—QX0500; 250 Style Y—QY0500—for \$13.95.' Allow 6-12 wks. for delivery.

LIBRARY SHELF BOXES—These sturdy white corrugated, dirt boxes each hold a full year of 73. Microcomputing or 80 Micro Desktop Computing, inCider. With your order, request self-sticking labels for any of the following: 73, Microcomputing, 80 Micro, CQ, QST, Ham Radio Personal Computing, Radio Electronics, Interlace Age, and Byte. Order 1—BX1000—for \$2.00°; order 2-7—BX2002—for \$1.50 each*; order 8 or more—BX1002—for \$1.25 each*.

For Your Ham Shack 73 Magazine Binders

• Preserve and protect your collection for a lifetime!
Order these handsome red binders with gold lettering.
\$7.50 for 1, 3 for \$21.75, 6 for \$42.00. (Postpaid within USA please add \$2.50 per order outside USA). Check or money orders only, no phone or C.O.D. orders. 73 money orders only, no phone or C.O.D. or Binders, P.O. Box 5120, Philadelphia, PA 19141.

*NOTE-Above address for Binders only

Code Tapes any four tapes for \$15.95! \$4.95 each

"GENESIS"

5 WPM — CT7305 — This is the beginning tape for people who do not know the code at all. It takes them through the 26 letters. 10 numbers and necessary punctuation, complete with practice every step of the way using the newest blitz teaching techniques. It is almost miraculous! In one hour many people—including kids of tenare able to master the code. The ease of learning gives confidence to beginners who might otherwise drop out. confidence to beginners who might otherwise drop out.

"THE STICKLER"

6+ WPM—CT7306—This is the practice tape for the Novice and Technician licenses. It is made up of one solid hour of code, sent at the official FCC standard (no other tape we've heard uses these standards, so many other tape we've neard uses these standards, so many people flunk the code when they are suddenly—under pressure—faced with characters sent at 13 wpm and spaced for 5 wpm). This tape is not memorizable, unlike the zany 5 wpm tape, since the code groups are entirely random characters sent in groups of five.

"BACK BREAKER"

13 + WPM — CT7313 — Code groups again, at a brisk 14 per so you will be at ease when you sit down in front of the steely-eyed government inspector and he starts sending you plain language at only 13 per. You need this extra margin to overcome the panic which is universal in the test situations. When you've spent your money and time to take the test, you'll thank heaven you had this back-

"COURAGEOUS"

20 + WPM—CT7320—Code is what gets you when you go for the Extra class license. It is so embarrassing to panic out just because you didn't prepare yourself with his tape. Though this is only one word laster, the code groups are so difficult that you'll almost fall asleep copying the FCC stuff by comparison. Users report that they can't believe how easy 20 per really is with this fantastic one hour tape.

"OUTRAGEOUS"

25 + WPM—CT7325—This is the tape for that small group of overachieving hams who wouldn't be content to simply satisfy the code requirements of the Extra Class license. It's the toughest tape we've got and we keep a permanent file of hams who have mastered it. Let us know when you're up to speed and we'll inscribe your name in 73's CW "Hall of Fame."

BACK ISSUES—Complete your collection; many are prime collectables now, classics in the field! A full collection is an invaluable compendium of radio and electronics knowledge! 73300 73 BACK ISSUE-BEFORE JULY 1980

73 BACK ISSUE JULY 1980 THRU OCT. 1981 73350 73 BACK ISSUE NOV. 1981 TO PRESENT \$ 3.50 73350P 73 BACK ISSUE-5 YOUR CHOICE 73005 73 BACK ISSUE-10 YOUR CHOICE 73010 73 BACK ISSUE-25 YOUR CHOICE 73025 73 BACK ISSUE-25 OUR CHOICE 73125 \$14.00

Shipping: Please add \$1.00 per magazine. Orders of ten magazines or twenty-five magazines add \$7.50 per order

*Use the order card in this magazine or itemize your order on a separate piece of paper and mall to: 73 Radio Bookshop • Peterborough NH 03458. Be sure to include check or detailed credit card information. No C.O.D. orders accepted. \$1.50 for the first book, \$1.00 each additional book for U.S. delivery and foreign surface. For foreign airmail \$10.00 per book. Please allow 4-6 weeks for delivery. Questions regarding your order? Please write to Customer Service at the above address. (Prices subject to change on books not, published by 73 Magazine.)

FOR TOLL FREE ORDERING CALL 1-800-258-5473

ADVERTISERS

*Please contact these advertisers directly.

To receive full information from our advertisers please complete the postage-paid card.

R.	. S. No. Page	R. S. No.	Page R.	S. N	lo. Page	R. S.	No. Page
	AEA/Advanced Electronic	* Computer Trader	141	33	Hamtronics, NY142, 14	3 61	Radio Amateur Callbook, Inc 4
	Applications 19, 39, 51, 83, 98	* Connect Systems	99	97	Hastings Antenna		
124	Advanced Computer Controls 16	37 Contemporary Te	chnology, Inc.	59	Hell Sound, Ltd		Ramsey Electronics
20	All Electronics		071		Hustler, Inc		Rivendell Associates
	Amateur Communications, Etc.	21 Current Developm	ent Corp 90			150	Royal
		106 Cushcraft Corp	34		ICOMCov.	65	
	Amateur Electronic Supply	12 C. Z. Labs			Jan Crystals9	SOT	73
		476 Daiwa			KCS Electronics 4	3	Books
75	Ampersand Electronics 95	 DGM Electronics, 		114	KSGTechnologies14)	93, 105, 111–114, 130, 132, 141
109	gg,	425 Doppler Systems		•	Kantronics)	Dealer Ad
71	Applied Invention 87	219 E-Tek		•	Kenwood 7, 97, Cov. I'	,	Moving111
108		477 Electra		•	KLM Electronics		Subscriptions 67, 73, 131, 140
	Associated Radio 38	58 Electronic Rainbor	w, Inc 53	100	Lewis Electroniss	367	Slep Electronics
11	Barker & Williamson, Inc 65	73 Electronic Rainbo	w, Inc	220	Lunar Electronics		Spectronics144
305	Barry Electronics	18 Electronic Special	ists, Inc 44	32	MCM Electronics	68	Spectrum Communications
	Barter 'n' Buy91	483 Encon		•	Macrotronics, Inc9		74.75
	Bill Ashby & Son95	29 Esoteric Engineeri	ng 141 4	45	Madison Electronics 13	436	Spectrum International, Inc 57
	Blacksburg Group45	248 Etco Electronics.	65 5	54	Magnum Distributing 4		Spider Antenna
226		22 Fair Radio Sales.	141 9		MFJ Enterprises 68, 69		Tayco Communications 141
255	Buckmaster Publishing91	99 Faxscan Corp			MHz Electronics 120-129		Teltone94
53	California Antenna Systems	484 Faxscan		103	Melco Publishing9		Ten-Tec
		23 Flesher Corp		27	Micro-80, Inc	46	The Ham Shack
111	e de de de la	88 Fox-Tango Corp			Micro Control Specialties2	449	
102		95 Fox-Tango Corp			Microlog Corporation	205	
13	Coin International140	480 Fox-Tango Corp		•	Mirage Communications8	76	
14	Communications Concepts, Inc.	481 GSM, Inc			Missouri Radio Center	104	Trionyx Industries
400	53	178 Galaxy Electronics		240	Mitronix	478	US Fiberglass
462	Communications Electronics	107 Gary Woodall & Co			Moler Antenna, Inc	•	Universal Electronics, Inc
405	Specialties, Inc 67	482 Gary Woodall & Co			N. P. S., Inc	*	Van Gorden Engineering91
485	Communications Specialists, Inc.	229 Gizmo Electronics			National Comm. Group Co 93		Vanguard Labs91
15		105 GLB Electronics			National Comm. Group Co 66		W9INN Antennas
15	Communications Specialists, Inc.	143 GLB Electronics			Nemal Electronics108		Westcom53
117	Communications Specialists, Inc.	119 H. Stewart Designs			Nuts & Volts141		Westech Electronics Co 53
117		479 Hal Communicatio			Orbit Magazine66		Western Radio Electronics 87
34	Communications Specialists, Inc.	31 Hal-Tronix			P. C. Electronics		W. H. Nail Co
34	Communications Specialists, Inc.	101 Ham Masters Tape			Parsec Communications		Xantek, Inc
112	Computer Specialty Store, Inc 4	nam nadio center			Phillips-Tech Electronics Corp 43		Yaesu Electronics Cov. III
''3	Computer opecialty affire, IIIC 4	* Ham Radio Outlet		8	Procast140		



BOOKS, ETC.

To order, complete the postage-pald card, or itemize your order including detailed credit card information or check and mail to: 73 Magazine/Mail Order Dept./Peterborough NH 03458.

Catal	og# Item	Price	Catalog#	Item	Price	Catalog	# Item	Price	Catalogs	Item	Price
				LLENGE OF 160	\$ 4 95	BK7310	OWNER REPAIR OF RAC	DIO EQUIPMENT	SG 7358	STUDY GUIDE GENERAL CLAS	5 8 6 96 .
73300	72 G 1 C 1 1 C C 1 C C C C C C C C C C C C			S COOKBOOK	\$10.50			5 7 95	BK 1190	THE TEN METER FM HANDBOO	
7 3300	73 BACK ISSUE -BEFORE JUL			E TAPE-5 WPM	\$ 4.95	BK 1185	THE PRACTICAL HANDI	BOOK OF FM	LB7360	TEST EQUIP LIB V2-AUDIO TES	
73350	12 0 10 4 100 100 100 100 100 100 100 100	\$ 3 00		E TAPE -6 - WPM	\$ 495		REPEATERS	512 9		TEST EGGIT EIG TE AGDIO TES	\$ 495
73330	73 BACK ISSUE JULY 1980 TH OCT 1981			E TAPE-13 - WPM	\$ 495	BK7302	PROPAGATION WIZARD	SHANDBOOK	LB7361	TEST EQUIP LIB V3-RADIO EQU	
73350P		\$ 3 50		E TAPE - 20 + WPM	\$ 4.95			\$ 69	5 LB7362	TEST EQUIP LIB V4-IC TEST EQ	
73330P	73 BACK ISSUE -NOV 1981 TO			E TAPE - 25 · WPM	\$ 4.95	QW0250	QSL CARDS -STYLE W	-250 \$ 8 9		TEXTEDIT - WORD PROCESSING	
73005	33.04.00 (00.05)	\$ 3 50			\$15.95	QW0500	QSL CARDS-STYLE W	-500 \$13.9	5	201 201 1101011100233114	\$9.97
73003	73 BACK ISSUE -5 YOUR CHO			COMPLETE SHORTWAVE		QX0250	QSL CARDS-STYLE X-	-250 \$ 8 9	5 DS7387	TEXTEDIT - DISK	319 97
	A 44 5 1 00 a	\$10.75		ENER'S HANDBOOK	\$ 9 95	Q×0500	QSL CARDS -STYLE X-	-500 \$13.9		TOOLS & TECHNIQUES	\$ 4 95
73010	Add \$1.00 per magazine for shippi			CONTEST COOKBOOK	\$ 5 95	QY0250	QSL CARDS -STYLE Y-	-250 \$ 8 9	5 BK 1063	TTLCOOKBOOK	\$ 9 50
13010	73 BACK ISSUE - 10 YOUR CHO			OMPUTERGAMES	\$ 7.95	QY0500	OSL CARDS-STYLE Y-	-500 \$13.99	5 BK 1064	TYT COOKBOOK	\$ 9 95
73025	73 BACK ISSUE - 25 YOUR CHO	\$16.00		RYTHING YOU ALWAYS WAN	TED TO	BK1199	THE RADIO AMATEUR A		BK7382	UNDERSTANDING & PROGRAM	
73023	13 BACK ISSUE - 25 YOUR CHO			VI RUSTAMA TUOBA W	\$ 9 95		HANDBOOK	\$ 6.99	5	MICROCOMPUTERS	\$10.95
73125	13 DACH (CC)	\$27.00		JIDE TO HAM RADIO	\$ 495	BK1044	RF & DIGITAL TEST EQU	IPMENT \$ 59	BK7368	VHF ANTENNA HANDBOOK	\$ 5.95
13125	73 BACK ISSUE -25 OUR CHOI			BY COMPUTERS ARE HERE	\$ 247	BK 1016	73 DIPOLE & LONG, WIR	EANTENNAS	BK1198	VHF HANDBOOK FOR RADIO AN	
	Little # 7 FO man and a day to a second	\$14 00		Y TO DEFEND YOURSELF AGA	AINST			\$ 5.50)		1 6 95
	dd \$7 50 per order for shipping		RAD		\$ 6.95	BX 1000	SHELF BOX 1	\$ 200	BK1202	WORLD PRESS SERVICE FREQU	
_				P AMP COOKBOOK	\$14.95	BX1001	SHELF BOXES-2-7	\$1.50 each		The second service the Go	\$ 7.95
				REFERENCE HANDBOOK	\$ 8 95	BX 1002	SHELF BOXES -B AND L	JP \$1.25 each	BK1184	WORLD RADIO TV HANDBOOK	\$16.50
BK1196	ALL ABOUT CUBICAL QUAD AN			BAUD KLASSROOM	\$14.95	BK1200	SIMPLE LOW COST WIR		BK7315	WORLD REPEATER ATLAS	\$ 2.00
		\$ 5.95		IC OF HAM RADIO	\$ 4 95		FOR RADIO AMATEURS	\$ 6.95		WOULD HE CATCHATERS	\$ 200
BK7384	ANNOTATED BASIC, VOL. 1	\$10.95		NEW HOBBY COMPUTERS	\$ 2 47	BK7311	SOME OF THE BEST FRO				
BK7385	ANNOTATED BASIC, VOL 2	\$10.95	BK7383 THE	NEW WEATHER SATELLITE				\$10.94	SHIPPING	AND HANDLING CHARGES \$15	O for the
BK 1197	BEAM ANTENNA HANDBOOK	\$ 5.95		DBOOK .	\$ 8 95	BK7351	SSB THE MISUNDERSTO			\$1 for each additional book for U	
BK7307	BEHIND THE DIAL	\$ 4 95	CT7300 NOV	ICE THEORY TAPES	\$15 95		STUDY GUIDE -NOVICE			n surface. \$10 per book for foreign	

NEW PRODUCTS

SOFTWARE, ONLY MORSE CODE INTERFACE

Gary Woodall has announced a new concept in amateur radio and computer interfacing. Comp-Code 1.0 is a softwareonly Morse code interface for the Radio Shack Models I, III, and IV microcomput-

This program uses the standard TRS-80 cassette I/O ports for input and output connections to a communications receiver and transmitter or transcelver. The results obtained from this software-only interface have been found to equal those of other hardware and software interface packages

This 12K + machine-language program has special routines that check the incoming signal to make sure it is valid code and not noise. Bursts of noise are disregarded and only code is processed and displayed on the video screen. There also is a routine that allows you to view the incoming signal and fine-tune your receiver. The program then samples the received code and automatically adjusts to the proper speed.

The transmitter mode features five programmable buffers for a 200-character total, a type-ahead buffer, and user-selectable sending speeds up to 70 wpm.

For more information, contact Gary Woodall Software, Box 284, Plainfield IN 46168; (317)-271-2565. Reader Service number 482.

NEW DAIWA/MCM MANUAL ANTENNA TUNER

Dalwa has announced its new CNW419 manual antenna tuner featuring continuous coverage from 1.8 to 30 MHz. It is rated at 200 Watts CW, 500 Watts PEP SSB. Input Impedance is 50 Ohms, with the output impedance variable from 10 to 250 Ohms

The CNW419 also features dual antenna outputs and a switchable tuner bypass option. The tuner comes equipped with Daiwa's cross-needle meter that simultaneously shows forward power, reflected power, and swr without the sensitivity adjustments commonly found in other meters

For more Information, contact MCM Communications, 858 E. Congress Park Dr. Centerville OH 45459; (513)-434-0031. Reader Service number 476

ELECTRA'S FIRST SHORTWAVE RADIO

Electra Company, marketer of Bearcate scanner radios, has announced that It is entering the shortwave-radio market with the Bearcat DX-1000, a radio that makes dialing in the BBC comparable to dialing a push-button telephone.

Utilizing the same microprocessor digital technology found in Bearcat scanner radios, the DX-1000 features direct-access keyboard tuning. This makes it simple to tune from the BBC (for example) to Radio Ghana without bandswitching. Covering 10 kHz to 30 MHz continuously, with PLL-synthesized accuracy, the Bearcat DX-1000 will monitor all shortwave bands, longwave, standard broadcast-band AM, amateur-radio broadcasts, and the marine

The DX-1000 has 10 memory channels, a digital display measuring frequencies to 1 kHz which, at the touch of a button, doubles as a two-time-zone. 24-hour digital quartz clock, and a built-in timer which can be programmed to activate peripheral equipment like a tape recorder to record up to ten broadcasts, in any frequency or mode, while the user is asleep or at work.

i-f filters to help separate high-powered stations on adjacent frequencies, a two-Russian pulse-radar interference, a twotrol, tone control, battery back-up system to Hold memorized frequencies and time if fast/slow automatic gain control, and sep-USB, CW, or FM modes. The unit comes with a built-in telescoping antenna for portable use and includes an SO-239 antenna connector for 50-Ohm leads and a screw-connector for "High Z."

The Bearcat DX-1000 can be operated with batteries (12 V dc) or from an electrical outlet (120/240 V ac). The unit measures 14-1/2" W x 5" H x 9-3/8" D and weighs 17 lbs. Each radio comes with a free shortwave Information guide that includes listings of stations from all corners of the world

Further details are available by contacting Electra Company, 300 East County Line Road, Cumberland IN 46229, Reader Service number 477.

WARC BANDS KIT FOR YAESU FT-101 SERIES

Fox Tango Corporation has announced a new kit which provides receive/transmit capability on all three WARC bands for all models of the FT-101 except the ZD. While

Other features Include independent selectivity selection, with 12-, 6-, and 2.7-kHz position noise-blanking system that stops position rf attenuator, FM squelch conpower fails, LED indicators for modes and functions, a front-mounted speaker, arate push-buttons for selecting AM, LSB,

> **QUARTZ CRYSTAL GUIDE AND DIRECTORY**

only the 10-MHz band has been authorized

for use to date, not much additional effort

or expense is required to add all the bands while the circuit changes for 10 MHz are

being made. In addition to making the old

101 feady when the new bands become

available, the added capability increases

G3LLL, the WARC bands kit is complete

with all needed crystals, relay switch, and

detailed instructions for moderately easy

Installation. For more information, con-

tact Fox Tango Corporation, Box 15944S,

West Palm Beach FL 33416. Reader Ser-

Based on a tried and tested design by

the trade-in value of the set

vice number 480.

GSM, Inc. publisher of the Quartz Crystal Industry Guide and Directory, has announced availability of its 1983-84 edition. Companies engaged in the production of quartz-crystal products and frequencycontrol devices, as well as suppliers of goods and services to the industry, are listed. The directory describes the products, capabilities, and specialized services of hundreds of companies located in the United States, Canada, Europe, and Asia. Each company's key personnel, address, telephone number, TWX, and other pertinent information are detailed.

Features of this issue include expanded worldwide listings, used equipment for sale or trade, and technical publications pertinent to the industry that can be ordered from GSM

Lucille A. Hope, editor-in-chief, is now planning the Mid-Year Update scheduled for December. For Information regarding advertising in the update or listing your company, contact the editor at GSM, Inc., PO Box 10277, Fort Lauderdale FL 33334. Reader Service number 481.



Flectra's new Bearcat DX-1000 shortwave radio

THE HAL ARQ1000 **AMTOR TERMINAL**

The ARQ1000 is a full send-receive terminal for the AMTOR ARQ code. All features of the CCIR 476-2 Recommendation are supported. Modes include: ARQ, FEC, SEL-FEC, and MONITOR. The ARQ1000 may be used with the Hal DS3100 and ST-6000, CT2200, CT2100, or CWR6850 terminals or any ASCII or Baudot terminal at baud rates from 45 to 300 baud. Non-volatile keyboard-programmable ARQ access code, selcal code, and WRU answer-back codes are included. The ARQ1000 is housed in a cabinet that matches the CT-2200 and CT2100. Available options include the DM170 internal demodulator and ARQX10 encryption module.

For further information, write Hal Com-



The Dalwa/MCM manual antenna tuner.



The ARQ1000 send-receive terminal from Hal Communications Corp.

munications Corp., Box 365, Urbana IL 61801, Reader Service number 479.

PHOTOVOLTAIC PANELS FROM ENCON

Encon Corporation has announced to the amateur-radio community two new photovoltaic panels, the SX-10 and the SX-20. The SX-10 is rated at 10 Watts and has different current/voltage selections, 8 V dc at 1.05 Amps and 17.3 V dc at .52 Amps, that the ham can wire himself. The SX-20 is 20 Watts, 8.6 V dc at 2.09 Amps and 17.3 V dc at 1.05 Amps.

According to Paul DeNapoll WD8AHO, Communications Director for Encon, these two new panels can be used for mobile ORP operations or mounted permanently to the roof for charging batteries.

The panels have a 30 + year life expectancy, an environmental survivability of wind loads over 160 mph and golf-ball-size hail stones, and are waterproof.

For more information, contact Encon Corp., 27584 Schoolcraft Rd., Livonia MI 48150; (313)-261-4130. Reader Service number 483.


LAND MOBILE TUNABLE ANTENNAS

A land mobile antenna, available in either UHF or VHF, that's tunable over varled ranges was introduced by U. S. Fiberglass at the Yecent Land Mobile Expo in Denver.


The patented Stage 2 antennas utilize a voltage-fed system, differing from conventional current-fed antennas. The result is an efficient utilization of rf energy and a low angle of radiation that provides increased transmission and reception range.

A patented reactance-canceling tuning sleeve allows the antenna to be tuned for optimum performance and then locked into position. The tuning section also allows the antenna to be tuned for a lower swr than conventional anténnas.

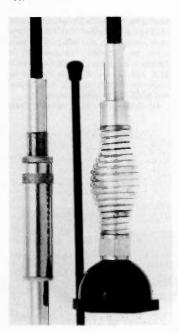The new antennas are suited to today's synthesized radio technology since they perform over a wilde band range. They are available in eight different models, including mobile applications and base antennas.



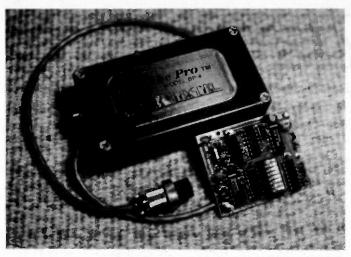Land mobile antennas from U. S. Fiberglass.



The Pro model BP-4 beeper from Faxscan, Inc.

For further information, contact *U. S. Fiberglass*, 5010 N.W. 36th Ave., Miami FL 33142; (305)-634-1115. Toll-free, nationally. 14800)-327-6790; Florida: 1-(800)-432-7142. Reader Service number 478.

THE PRO—FAXSCAN'S BP-4 BEEPER

Faxscan, Inc., has announced the Introduction of their model BP-4 beeper. The ProTM The Pro continues the concept of a "courtesy beep" to signal the beginning and end of each transmission by automatically injecting a gentle high-frequency beep into the mike line at the start of the transmission and a low one at the end. This basic idea has been used for years in commercial and military applications and NASA has used it for ground-to-space voice communications. The Pro is an upgraded version of Faxscan's model BP-3 which has been marketed to the amateur radio community worldwide for the past three years

The Pro adds several features not found In the BP-3. Most notable Is the inclusion of a sophisticated digitally-programmable timer. The user may select timing periods from approximately 43 seconds to 10.5 minutes. Programming Is accomplished by setting tiny DIP switches on the circuit board. The timer may be used as an ID timer or to warn you of impending time-out on

a repeater. Time-out is noted by a unique double 4-beep sequence via a piezoelectric transducer; there is no speaker. Volume of this warning is also programmable and the warning is not transmitted.

Unlike the earlier BP-3, the beginning beep can be deleted by the setting of a switch. In this mode, a beep is added only to the end of your transmission.

Finally, The Pro incorporates a "slumber mode" to extend battery life. There is no on/off switch. Instead, the unit senses the lack of activity and shuts itself down. A single 9-V battery (not supplied) powers the unit continuously for up to a full year.

Faxscan includes a 5-page manual with The Pro, detailing theory of operation, instructions for programming the various functions, and a full-page schematic/layout along with Interfacing tips. In general, The Pro will work with virtually all modern gear. Specifically, this beeper will interface directly to any rig employing a positive potential on the PTT line of less than +24 V dc and which transmits when the PTT line is pulled down to +0.7 V dc at less than 100 mA current.

The beeper comes in three versions. The A version includes a cast-aluminum enclosure, cable, and standard 4-pin mike connectors, installed. The B version is the same but without connectors. You simply add those of your choice. The C version is a circuit-board model for custom installation. For instance, the C version can be

tucked inside your rig or is a perfect repeater accessory. The Pro is easily modified for most any application and the manual contains full details.

All units are fully assembled, tested, and carry a 90-day limited warranty. Fax-scan ships all units postage-paid in the US.

For more information, contact Faxscan, Inc., 3148 Dorf Drive, Dayton OH 45418; (513)-263-8475. Reader Service number 484.

THE NEW HUSTLER TRIBAND VERTICAL

Hustler, Incorporated, has announced the addition of a new three-band vertical antenna for 10-, 15-, and 20-meter operation. A two-in-one trap design allows for excellent bandwidth while maintaining an overall height of only 12 feet.

Designated 3-BTV, the antenna is designed for permanent ground mounting with radials or for portable use on travel trailers, condo balcony railings, or wherever there is a sufficient groundplane. Construction is of high-quality aluminum with stainless-steel hardware; supplied is a heavy-duty bracket for pipe or bulkhead mounting.

For additional information on the 3-BTV or other Hustler amateur products, contact your dealer or write Hustler, Inc., 3275 North B Avenue, Klssimmee FL 32741.

KREEPIE-PEEPIE FOR AMATEUR TV

You may want to call it a handle-lookie rather than a kreepie-peepie, which was what the first cordless TV cameras were called. P. C. Electronics has come out with the KPA5, a 1-Watt UHF ATV-transmitter module board which will allow you to use any portable consumer color-TV camera.


When mounted in an aluminum box above a portable color camera, the KPA5 allows freedom to move around to catch all the action at parades, races, and other such events. If you are into videotaping you won't have to lug around a portable VCR. In fact, a standard ac-powered home VCR can be used with just an ATV downconverter ahead of the tuner set to channel 3.

DX depends a lot on antennas, terrain, etc., but up to a mile is typical under most conditions and 50 miles has been done from an airplane. For base-station use or higher-power mobile, it can be matched to the Mirage D24N amplifier for 40 Watts output. Other applications include video from R/C model airplanes, robots, computer video, weather-radar video, or practically any case where cables become too long for composite video from any source.

The KPA5 is a wired and tested board capable of full color and sound. Output is a nominal 1-Watt PEP of amplitude-modulated rf with standard 4.5-MHz sound subcarrier into 50 Ohms. It comes standard with one crystal on either 439.25 (east), 434.0 (west), or 426.25 MHz, Two channels are available with the addition of a second crystal and an external SPST switch. Inputs are: composite video from a camera, VCR, or computer, low-Z microphone, and line audio from a VCR, camera mike, or computer. Power requirement is 13.8 V dc at 280 mA. Board size is 4 x 3.25 inches.

Buyers must hold Technician-class or higher amateur licenses to operate or purchase from the manufacturer.

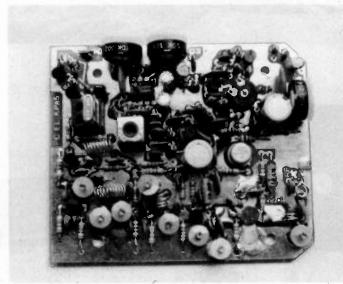For more information or a complete catalog of ATV products, call or write P. C. Electronics, 2522 Paxson Lane, Arcadia CA 91006; (213)-447-4565.



The P. C. Electronics portable ATV transmitter.

AWARDS

Bill Gosney KETC Micro-80, Inc. 2665 North Busby Road Oak Harbor WA 98277

WORKED ALL LA AWARD

The WALA Award is available to any amateur who can provide evidence of having the following requirements of the award:

Applicants in Denmark, Finland, Sweden, and Norway must have two contacts on separate bands with a total of 20 counties of Norway.

Applicants outside Scandinavia must work 20 different LA/LB stations on any amateur band. At least 6 of these stations must be located north of the Arctic Circle. Contacts with stations from JW (Svalbard), JW (Bear Island), and JX (Jan Mayen) count for this award.

All contacts must be made after January 1, 1950. Usual logbook information is required for claiming your contacts, along with the exact OTH of the station worked. Award fee is Nkr. 10, or 10 IRCs mailed to: NRRL Award Manager, Alf Almedal LA5QK, N-4052 Roeyneberg, Norway.

WORKED NORWEGIAN CITIES AWARD

This award requires applicants to work a minimum of Norwegian cities with no limit to date, band, or mode. It should be noted that this award will not recognize contacts with LJ, LF, or LH stations. The three classes are: Class 3—DX station work 5 cities, Europeans must work 10 cities; Class 2—DX station work 10 cities; Class 2—DX station work 20 cities; Class 1—DX station work 20 cities; Class 1—DX station work 15 cities, Europeans work 30 cities.

GCR apply. Send your completed llst of contacts and application along with the award fee of 10 IRCs to: Larvik Society of NRRL, PO Box 59, N-3251 Larvik, Norway.

Valld Norwegian cities are: Alesund, Arendal, Bergen, Bodo, Drammen, Egersund, Fredrikstad, Gjovik, Halden, Hamar, Hammerfest, Harstad, Haugesund, Horten, Kongsberg, Kragero, Kristlansand S., Kristlansund N., Larvik, Lillehammer, Mandal, Mo i Rana, Molde, Mosjoen, Moss, Namsos, Narvik, Notodden, Oslo, Porsgrunn, Sandefjord, Sandnes, Sarpsborg, Sklen, Stavanger, Stelnkjer, Tonsberg, Tromso, Trondheim, Vardo.

From the Vadso Society of the Norwegian Radio Relay League come details about the worked all "communes" award for this Scandinavian country.

WORKED ALL NORWEGIAN COMMUNES AWARD

Licensed amateurs and SWLs world-wide are encouraged to pursue the requirements of this very challenging awards program. This award is issued for contact with 25 different Norwegian communes; an endorsement sticker recognizes each additional group of 25 communes. At present there are over 454 communes and 5 Norwegian arctic/antarctic areas which qualify for contacts. A special award will be issued to those who can work all communes and all arctic/antarctic areas. Only contacts on or after January 1, 1975, will count for WANCA.

All bands or modes may be used; no crossmode contacts or contacts via repeater will be allowed for credit. QSOs via OSCAR satellites do count. Minimum reports in all cases must be RST 338 or RS 33. Mobile or portable contacts count, but QTH must be stated on the QSL card.

QSL cards are not required. GCR apply. Award fee is Nkr. 30 for the basic award (10 IRCs) and Nkr. 10 (3 IRCs) for endorsement stickers. No fee for handicapped amateurs/SWL stations.

A record book listing all Norweglan communes and areas is available from the Award Manager for 15 Nkr. (3 IRCs).

Certificates are issued for mixed mode, CW only, SSB only, all RTTY, all SSTV, Novice, mobility (only contacts with mobile or portables), and All WANCA.

All fees are contributed to the LA5LG Fund for Norweglan Bilind-Handicapped Amateurs. All Inquiries should be accompanied with at least 2 IRCs for an expected reply.

All applications should be forwarded with the appropriate fee to: WANCA Award Manager, Sverre J. Schmidt LA1QK, PO Box 3, N-9801 Vadso, Norway.

DX AWARDS FROM NEW ZEALAND

I just received a very informative packet of information from NZART, the national amateur society of New Zealand. Jock White ZL2GX, as awards manager, indicates that all NZART awards are available for a nominal fee and QSL cards are not required where verified lists can be provided as an alternative. To qualify, all contacts claimed for NZART awards must be made on or after November 1, 1945. Special endorsements are given for single-band or mode accomplishments. Send all applications to ZL2GX, 152 Lytton Rd., Gisborne, New Zealand.

Worked All Pacific Award

To qualify for the WAP Award, an applicant must confirm two-way contacts with 30 different Oceanic countries from the WAP list below. The cost of this award is 2 IRCs or US \$.60.

Eligible Oceanic contacts: Port Timor, Philippines, Adelie Land, New Caledonia, French Oceania, Wallis Island, New Hebrides Baker/Howland/American Phoenix Islands, East Carolines, West Carolines, Mariana Islands, Marcus Island (Minami Torishima), Guam, Hawaiian Islands, Johnston Island, Midway Island, Palmyra, American Samoa, Wake Island, Marshall Island, Java, Sumatra, Borneo, Celebes, West Irlan, Australia, Lord Howe Island, Willis Island, Macquarie Island, New Guinea, Norfolk Island, Papua, Nauru, Christmas, Cocos, Gilbert, Ellice, British Phoenix Islands, Fiji, Fanning and Washington Islands, Solomon Island, Tonga, Pitcairn, Sarawak, Brunei, North Borneo, North Cook Islands, South Cook Islands, Samoa, Tokelau Islands, Kermadec Islands, Niue Island, New Zealand, Chatham Island, Auckland and Campbell Island, Antarctica (ZL5 only).

New Zealand Award

The NZA is available to all radio amateurs other than ZL. A total of 101 contacts is required to qualify for this award. All contacts must be made after December 8, 1945.

Applicants must make the following contacts: 35 ZL1 contacts, 35 ZL2 contacts, 20 ZL3 contacts, and 10 ZL4 contacts, plus 1 contact with a ZL "territory" (either New Zealand, Antarctica, Chatham Island, or Campbell Island). This one contact may be substituted by 20 additional ZL contacts not already claimed.

Worked All New Zealand Award

The WAZL Award requires that contact be made with 45 different branches of NZART—except for overseas applicants, for whom only 35 contacts are required.

A special endorsement is given if the WAZL Award is accomplished within a 12-month period. Mobiles operating outside their regular branch area must sign the branch from which they are mobile while operating. Endorsements are also given for single-band or -mode operations. All contacts must be made after November 1, 1945, to qualify.

NZART branches are as follows: 01 Ashburton, 02 Auckland, 03 Western Suburbs, 04 Cambridge, 05 Christchurch, 06 Danne virke, 07 Blank, 08 East Southland, 09 Eqmont, 10 Franklin, 11 Gisborne, 12 Hamilton, 13 Hastings, 14 Hawera, 15 Hawke's Bay Central, 16 Horowhenua, 17 Huntly, 18 Hutt Valley, 19 Inglewood, 20 Manawatu, 21 Manukau, 22 Mariborough, 23 Marton, 24 Motueka, 25 Napier, 26 Nelson, 27 New Plymouth, 28 Northland, 29 North Shore, 30 Otago, 31 Pahiatua, 32 Rahotu Coastal, 33 Rotorua, 34 South Canterbury, 35 South Otago, 36 South Westland, 37 Southland, 38 Taumarunul, 39 Tauranga, 40 Te Awamutu, 41 Thames Valley, 42 Titahl Bay, 43 Walhi, 44 Matamata Radio Club, 45 Waimarino, 46 Wairarapa, 47 Waltara, 48 Wanganul, 49 Westland, 50 Wellington, 51 Eastern Bay of Plenty, 52 Walroa, 53 Te Puke, 54 Patea, 55 Waitomo, 56 Hornby, 57 Tokoroa, 58 Helenville, 59 Mangakino, 60 Taupo, 61 Central Otago, 62 Reefton Buller, 63 Upper Hutt, 64 North Otago, 65 Papakura, 66 Auckland VHF, 67 Kawerau, 68 North Canterbury, 69 Kapiti, 70 Fielding, 71 Rodney, 72 Opotlki, 73 Hobson, 74 Western VHF.

New Zealand Counties Award

The Basic NZC Award requires contacts with 20 different New Zealand countles. Endorsements are made for 40, 60, 80, and 100 contacts, with a special certificate for 112. A map showing the countles is available by writing NZART (ZL2GX) directly. Enclose 10 cents or 1 IRC to cover handling.

The initial award with any or all endorsements costs 45 cents or 3 IRCs. Separate endorsements thereafter cost 10 cents or 1 IRC. The special NZC 112 Award costs 45 cents.

Contacts may be made single band or any mode to qualify. GCR apply. Applicants must provide a list of contacts detalling the usual logbook data.

5 x 5 Award

This premier award has been instituted to recognize the increasing interest in 5-band DX operation. The initial award requires that the same station be contacted on 5 bands repeated with 5 different countries.

A certified list with full QSO data and fee of \$1.00 is required. The certificate is outstanding and is overprinted in embossed gold. Contacts must date from 1945.

ZLA Award

To qualify for this award, applicants must contact Auckland City ZL1, Wellington City ZL2, Christchurch City ZL3, Dunedin City ZL4, Antarctica ZL5, Campbell Island, Chatham Island, and Kermadec Is-

land. There are endorsements given for single band or mode.

Award fee is 45 cents or 3 IRCs. GCR ap-

Individual ZL District Awards

All ZL district awards are 35 cents each or 3 IRCs. Later endorsements are accessed at 10 cents or 1 IRC apiece, All contacts must be dated post war.

ZL1 Award—Contact 125 different ZL1 stations. Endorsements are recognized for 175 and 250 contacts.

ZL2 Award—Basic award requires contact with 100 different ZL2 stations, with endorsements given for 150 and 200.

ZL3 Award—Basic award requires 50 ZL3 contacts, and endorsements are given applicants claiming 75 and 100.

ZL4 Award—This award requires only 25 ZL4s be worked, with endorsements given for 35 and 50.

Captain James Cook Award

The CJC award, as it is called, perpetuates the memory of this world famous navigator and seaman—in three classes. 1. The basic "Sailor" class requires contacts with G in Yorkshire, FO8, ZL2, VK2, and KH6. 2. For "Officer" class, applicant must first possess all the Sailor-class contacts plus ZL1, ZL3, ZL4, VK3, VK4, VK9 New Guinea, and any Antarctica station. 3. For "Command" class, both the previous classes must be earned plus five of the following: VE2, VO, A35, YJ8, FK8, CE0, and KL7.

Cost of this award is 45 cents in stamps or IRCs. GCR apply.

YL ZL Award

The Women Amateur Radio Operator Award (WARO) requires VK and ZL stations to work at least 12 members of the WARO. DX stations must work at least 5 members. All contacts must be made after June 1, 1969, and must include one each from ZL1, 2, 3, and ZL4.

Net contacts do not qualify. There are no band or mode limitations; however, all contacts must be made from the same OTH for all.

Unlike all the previous awards shown so far, send your list of contacts along with your OSL cards to the Award Custodian, Thelma Souper ZL2LO, 62 Kirk Street, Otaki, New Zealand.

There was no mention of an award fee, but to be safe and courteous, it is advisable to enclose at least an amount for sufficient postage to return your cards.

In the event you missed the address for all applicants for NZART awards, please forward your requests to Mr. Jock White ZL2GX, 152 Lytton Road, Gisborne, New Zealand. Be sure to tell Jock you heard about the NZART awards from 73 magazine.

CANADIAN AWARDS FROM CARE

The Canadian Amateur Radio Federation (CARF), Inc., is pleased to announce the following radio-amateur awards available to operators worldwide.

Canadaward

A colorful certificate will be issued to any amateur who confirms two-way contact with all Canadian provinces and territories. Awards will be issued for any band, six to 160 meters, and any mode via OS-CAR satellite. Modes may be mixed, CW, SSB, RTTY, SSTV, or any other authorized emission.

All contacts must be made after July 1, 1977. To qualify, applicants must forward QSL cards with \$2.00 or 10 IRCs plus sufficient funds for the safe return of your

cards. CARF members need only submit sufficient funds for returning QSLs. Mail your fee, application, and QSLs to: Canadawards, PO Box 76752, Vancouver BC, Canada V5R 5S7.

List of Canadian provinces and territories which qualify for this award: VO1/VO2 Newfoundland and Labrador, VE1 Prince Edward Island, VE1 Nova Scotla, VE1 New Brunswick, VE2 Quebec, VE3 Ontario, VE4 Manitoba, VE5 Saskatchewan, VE6 Alberta, VE7 British Columbia, VE8 Yukon Territory, VE8 Northwest Territories, Note: VO1 or VO2 count as one required contact.

5-Band Canadaward

A special plaque will be issued to any amateur who confirms two-way contact with all Canadian provinces and territories on each of five separate bands (12 cards per band for a total of 60 cards). All contacts must be made after July 1, 1977. Submit the 60 cards with \$10.00 or 70 IRCs plus sufficient postage for the safe return of your QSLs. Should you work 6 or 7 bands using the same Canadaward criteria, special endorsements will be provided upon proof of your claim. As with the basic Canadaward, forward your applications to PO Box 76752, Vancouver BC, Canada V5R 5S7.

NIAGARA FALLS

The Niagara Falls Radio Club, Inc., will operate a special-event station during the Festival of Lights, from Niagara Falls, New York, seventh wonder of the world. The Festival of Lights is one of New York's top ten winter attractions. The callsign will be W2QYV. Dates are November 26th through January 8th; time will be from 1500 UTC to 0300 UTC. All contacts will be in the General portion of 20, 40, and 80. To apply for this award, send QSL card and \$2.00 donation, along with an SASE (81/2 by 11) with \$.55 postage for the color photograph award, to: Awards Manager, Angelo Zino WA2UJR, 16 Council St., Niaga-

CW GROUP OF **RIO DE JANEIRO CWRJ AWARDS PROGRAM**

Important Notes: LOG-GCR apply. 1. All awards CW only, 2-way, or SWL. All bands mixed unless otherwise noted, 2, A single CWRJ Operator Team Member may be used for more than one CWRJ award, but only if worked on other bands, or on a different date, 3, CWRJ Associate Membership is available to foreign amateurs, see: WAMAW Award, below. 4. Endorsement seal fee: none, send an SAE and 1 IRC for surface mail.

CWRJ Operator Team Members (Oct 82): PY1s: AFA, AFG, AJK, ASI, BFZ, BGI, BMF, BOA, BQQ, BUG, BUL, BVY, CBW, CC, CCX, CCY, DCG, DEA. DFF, DGB, DIN, DJY, DN, DPG, DUB, DUH, DWM, EBK, EWN, FB, HQ, LG, MHQ, MKA, RJ, TCJ, UET, URQ, VB, VEC, VKA, VLR, VMV, VOY, WDS, WO.

CWRJ Award: CWRJ

CW only. Work 20 different PY1 stations including 5 members of the CWRJ Operator Team. Endorsements: 6, total. Each 5 new PY1 stations, including 1 new Operator Team Member.

Log: complete. Fee: 6 IRCs. Valid: after Dec. 16, 1980. Manager: PY1EWN, PO Box 621, 24000 Niteroi, RJ, Brazil.

Brazilian Stations Award: BSAW

Work 75 Brazillan stations including 10 Federation Units (states/territories) and 2 CWRJ Operator Team Members, CW only,

CONNECTORS

TYPE 'N'

UG-21/BU(MALE) \$2.35 UG-27/CU(RIGHT ANGLE) \$4.45 UG-57/BU(DOUBLE MALE) \$3.15 UG-29/BU(DOUBLE FEMALE) \$3.15

PL-259 57¢ ea. UG-175/U OR 176/U .16¢

Each state/terr. has different prefix: PY1, PT2. Endorsements: 2. First: 50 additional Brazilian stations. Second: 25 additional Brazilian stations

Log: call/date. Fee: 6 IRCs. Valid: after Jan. 1, 1982. Manager: PY1EWN, PO Box 621, 24000 Niteroi, RJ, Brazil.

Rio De Janeiro State Cities Award: **RJCAW**

Work 10 cities of Rio de Janeiro State (RJ)-PY1-including 2 CWRJ Operator Team Members, CW only, Endorsements: none (on initial application, any award will be endorsed QRP upon request and proof).

Log: call/date/cities. Fee: 6 IRCs. Valid: after Jan. 1, 1982. Manager: PY1DWM, PO Box 24039, 20522 Rio de Janeiro, RJ, Bra-

Diploma Brasil Geografico: BGAW

Work 3 stations of each geographical region of Brazil, 15 total contacts, including 1 S.E. region CWRJ Operator Team Member, Endorsements: none (on initial application, any award will be endorsed QRP upon request and proof). CW only.

Geographic regions: Norte (NO-North): PP8, PT8, PU8, PV8, PW8, PY8. Nordeste (NE-Northeast): PP6, PP7, PR7, PR8, PS7, PS8, PT7, PY6, PY7. Sudeste (SE-Southeast): PP1, PY1, PY2, PY4. Sul (SU-South): PY3, PP5, PY5. Centro Oeste (CO-Midwest): PP2, PT2, PT9, PY9.

Log: call/date. Fee: 6 IRCs. Valid: after Jan. 1, 1982. Manager: PY1DFF, PO Box 1045, 24000 Niteroi, RJ, Brazil.

Worked CWRJ Associate Members Award: WAMAW

CW only. Work 10 CWRJ Associate Members and/or CWRJ Operator Team Members, Endorsements: 2, First: 5 additional CWRJ Associate Members. Sec-

Log: call/date. Fee: 6 IRCs, Valid: after Jan. 1, 1982. Manager: PY1EWN, PO Box 621, 24000 Niterol, RJ, Brazil. Note: CWRJ Associate Membership is available to foreign amateurs with a profound interest in Brazilian CW Groups' activities, awards, etc. SASE to W5XW for details in English; PY1EWN in Portuguese; DJ3WM in Ger-

Brazil's Frontiers Award: BFAW

CW only. Work 5 countries which have frontiers (borders) with Brazil: (FY, PZ, 8R, YV, HK, OA, CP, ZP, LU, CX).

Log: call/date. Fee: 6 IRCs. Valid: after Jan. 1, 1982. Endorsements: none (on initial application, any award will be endorsed QRP upon request and proof). Manager: PY1DFF, PO Box 1045, 24000 Niteroi, RJ, Brazil.

CWRJ "YL" Flowers Award: YLAW

CW only. With the first letter of the suffix of the callsigns of stations worked in the 10-meter (28-MHz) band, spell the names of 5 (five) flowers (English or Portuguese names); stations worked must include 5 (five) YL operators. YL stations may be used to substitute letters in the names of flowers (as in poker: wild cards); YL contacts may be on any band. Contacts may be any country. Endorsements: none (on initial application, any award will be endorsed QRP upon request and proof).

Log: call (listed in order to form names of flowers)/YL info/date. Fee: 6-IRCs. Valid: after Jan. 1, 1982. Manager: PY1DWM, PO Box 24039, 20522 Rio de Janeiro, RJ. Brazil

Worked CWRJ Awards: WRJA

CW only. Applicants must have the basic CWRJ Award plus 5 others from the

CWRJ Award Program. Endorsements: none (on initial application, any award will be endorsed QRP upon request and proof).

Log: numbers/names of awards. Fee: 6 IRCs. Manager: PY1DFF, PO Box 1045, NIteroi, RJ, Brazil.

GAITHERSBURG MD

The NBS-BRASS will operate K3AA November 3 through November 6, 1983, in observance of the dedication of the first active amateur-radio club station at the National Bureau of Standards. Multi-op activities on CW, phone, and RTTY will be near the low end of the 80- to 10-meter Novice- and General-class bands. Certificates can be obtained by sending an SASE to BRASS, c/o National Bureau of Standards, Mailroom, Washington DC 20234

CHESAPEAKE APPRECIATION DAYS

The Anne Arundel Radio Club will operate W3VPR from Sandy Point State Park, near Annapolis, Maryland, as part of the annual Chesapeake Appreciation Days celebration, October 29 and 30, 1983. Operation will be from 1000 until 1600 EDT in the lower part of the General-class CW and phone bands, 40 and 20 meters, and CW in the 15-meter Novice band. Certificate via PO Box 604, Glen Burnie MD 21061.

SPECIAL EVENT STATION WA2UEC

Rocky Point, New York: The Radio Central Amateur Radio Club will operate WA2UEC from the former RCA High-Frequency Radio Station, called "Radio Central," on Saturday, November 5, and Sunday. November 6, to commemorate the 62nd year of the station (now silent), part of the New York State Park. Operations for the 24-hour period will be on 2-160 meters, up 10 kHz from the edge of the General band, and on two meters on these frequencies: 146.52, and 144.550/145.150 repeat. Novice-band operation will be on 7,110 kHz

A special QSL card showing a photo of the former station will be available. Send your QSL with a large SASE to Radio Central Amateur Radio Club, PO Box 680, Miller Place NY 11764, or QSL to the Callbook address.

MICHIGAN AMATEUR RADIO LADY OF THE YEAR

The recipient of the 1982 Michigan Amateur Radio Lady of the Year Award was Alleen Gagnon WA8DHB of Gladstone, Michigan

Alleen has been a very active member of the amateur-radio community since she was first licensed in April of 1962. Her particular area of interest is public-service communications and she is highly involved in various aspects of the national traffic system. Alleen is an assistant section manager (for Michigan's upper peninsula), official relay station, net manager of the upper peninsula net, member of the TASYL, UPYL, MACS and MITN Michigan Nets, a net control for the MITN, and is active on the MATW (Michigan amateur traffic workshop). She also is very active in emergency communications and is net control for the upper peninsula ARES net as well as prime organizer for net activities during the SET.

Alleen has received two certificates of

THE ONE STOP SOURCE SINCE 1959!!

COAXIAL CABLE RG-8/U (95% BRAID-FOAM)\$235/M' MICRO 8/U (95% BRAID-FOAM)115/M' RG-213/U (96% BRAID-POLY)270/M' RG-214/U (2-96% BRAIDS-POLY)495/M'

ROTOR CABLE 8/C HAMLINE (2-18/6-22)\$150/M' 8/C HAMLINE HD (2-16/6-18)340/M'

CALL COLLECT CALL FOR LARGE QUANTITY DISCOUNT





UHE

PL-258 79¢



P.O. Box 95-55 Railroad Ave. Garnerville, New York 10923

(914) 947-1554-1555

MICROWAVE COMPONENTS

25 MW EXCITER \$49.95 45 MHZ SUBCARRIER \$19.95 AM VIDEO MODULATOR \$19.95 50 MW UP CONVERTER \$149.95

GIZMO ELECTRONICS, INC.

P.O. BOX 1205 PITTSBURG, KS 66762 PH. 316-231-8171

-229

Kansas residents 3% sales tax

merit from the ARRL and is a past president of her local radio club, the Delta County Amateur Radio Society, and a member of the local repeater association.

During her very rare spare moments, Aileen keeps a constantly updated card file of all the upper peninsula hams. This is used to print an annual UP ham directory.

Alleen is a busy housewife (hubby is Melvin), and she has a son, a daughter, two stepdaughters, a stepson, and six grandchildren, Also, Alleen and Mel have one of the truly outstanding vegetable gardens in Delta County,

The Michigan Amateur Radio Lady of

the Year Award is presented each year at the ARRL state convention in Muskegon, Michigan, by the section manager,

WORKED ALL "QST" AWARD

if you like to collect awards, here is a new one for you. The Worked ALL "QST" Award, sponsored by the CRRL.

As most of you might already know, the "QST" suffix has been assigned to the CRRL in all Canadian call areas, VE_QST calls are used by official bulletin stations across the country. These stations are active during League contests and publicservice events. They also provide regular bulletin services to local nets and on a nationwide basis to Canadian hams.

This Worked ALL "QST" Award is available in five categories: CW, phone, RTTY, mixed, and QRP, with four endorsements: VE0, VO2, VE8, and VY1.

To qualify, one must work all eight stations from VO1, VE1 through VE7. Once you have all eight "QST" QSL cards, you can send them to CRRL, Box 7009, Station E, London, Ontario, Canada N5Y 4J9, or directly to the award manager, John Gowron VE4ADS.

The licensees who control the use of "QST" calls and maintain logbooks for QSL purposes are: William Kremer VE7CSD (VE7QST), Bill Gillespie VE6ABC (VE6QST), William Munday VE5WM (VE5QST). Peter Guenther VE4PG (VE4QST), Dick Reiber VE3IBV (VE3QST), Don Welling VE1WF (VE1QST), and Clarence Mitchell VO1AW (VO1QST).

The four endorsement calls will be active from time to time. Watch these pages for announcements.

LETTERS

COMPU-KIDS

Just a note of appreciation regarding 73. I find it informative, timely, accurate, and comprehensive. I read your editorials with an open mind and feel you do have a progressive attitude. I don't always agree, however. For example: The young fellows I have Elmered had no difficulty with the code but really can't cope with the written. Part of the problem, of course, is the lack of study-habit training in our school systems. However, I agree that amateur growth is the primary necessity.

The VIC-20 code program in the August, 1983, issue is what prompted me to write. This is an excellent little program and it works: This approach should help lots of computer kids get started. I had my nephew type it in and after a few corrections (his mistakes) it ran nicely. I am going to rework it to run on my TI99/4A and will send it in if somebody doesn't beat me.

I, too, am an ex-submariner, Wayne. I served as a Torpedoman on the Puffer, Morey, Boarfish, and S-12 (training). A great experience!

Well, I'd better get back to learning how to use my new word-processing program so that I can retire this turkey typewriter.

J. W. Guthrie KF6FC Carmel CA

JW, the more I get involved with my college project, the more I understand how much change is needed in our schools. We need to stop thinking of them as public baby-sitting systems and start teaching 'em things again. I can't believe how much lower grade education has changed since I went to school fifty years ago. - Wayne.

CW CLUTTER

I have been following your editorials about the elimination of code requirements for a ham license. For over 25 years. I was involved in non-communication electronics. My work involved design, prototype construction, and supervision of technicians.

For over 50 years (since I was about 15), I have wanted to become a ham, but I have refused to clutter my mind with code just to pass some test. I have never had any interest in CW communication and once the test was passed I would never use the code again. As the result of my conviction. I have never had a license.

Keep trying, but I don't think we will live long enough to see the day when "Reason rules the day."

I like 73 very much and find the construction articles very good. Keep up the

> James C. Anderson Albuquerque NM

BUY AMERICAN?

It is truly amazing the powers encompassed in the printed word. Your excellent reporting of the contents of Joe Vegh's (W5VSV) letter regarding his attitude about buying American was thought-provoking and meaningful. What a powerful statement was made when he stated he would "straighten screws, glue on decals, touch up paint, and complain like hell before buying foreign products." The only thing I ever did was "complain like hell" because it did not occur to me to do the other things mentioned. The domestic products I have purchased recently seem to need more than screws straightened or decals re-glued. Hell fire, I have some items total rebuilding cannot cure. When I raise hell with the manufacturer, all I get in return are nasty letters or excuses such as: "The union members do not do their Job" or "American workers cannot do a dollar's worth of work for a dollar anymore; they have to have \$5.00 and two men to do one man's job." I wonder if Joe gets better results raising hell than I get.

I, too, suffered at the hands of our Nipponese friends in World War II. During their attack on Pearl Harbor, December 7, 1941, my ship (U.S.S. Utah) went down so fast many of my friends falled to swim to safety, so I, too, can see where Joe can conjure up ill will toward the Japanese. My father nearly had a stroke in 1974 when I drove up in a brand new Toyota. No amount of explaining could ever convince him my reasoning was sound. "But the car is built better than modern American cars," "But, Dad, my time can be better spent than straightening screws or re-gluing decals and touching up paint," "But, Dad, this car actually runs for days on end without benefit of a push or pull from out-

All of this fell on deaf ears because my father did what Joe advocates: Buy no foreign products...unless you need-them or want them. My father did not use Joe's disclaimer, however. He did not buy foreign! Not to his knowledge, anyway.

When I pointed out his clock radio was made in Talwan, his color television was 96% Japanese made, his car radio (in his 100% American-made car) was a Japanese product, and several other Items in his household were also foreign, his second near-stroke of the day was not long in

After reading your editorial on the subject, my wife and I decided to re-evaluate our position and become 100% American in our daily purchases. After all, I used to give talks about "Americanism" at local high schools and service clubs. What a traitor! Talking about being loyal on one hand and then going out availing myself of foreign products. So we came up with ideas we think everyone should follow.

No more Italian sausage, French wine, German beer, Swedish meatballs, Russian vodka, caviar (unless the sturgeon checks out to be born and raised in American waters), Spanish rice, Hungarian goulash, French, Italian, and Vienna bread, Chinese noodles, borscht, Irish stew, Soul Food (didn't we import those people from Africa?), Danish rolls, Sukiyaki, Chinese egg rolls, Spanish omelets, spaghetti, Irish potatoes, and many, many other things. For a complete list, don't send me a letter. Just forget it. My wife and I are contemplating losing a lot of weight.

Then we got into wearing apparel. We came to the conclusion that naked is as naked does. There isn't much available that is not made in its entirety or assembled in foreign manufacturing plants. This is going to be tougher than we thought.

Our final conclusion was to buy clothes and food from the only true American extant, the American Indian, There is, however, a rumor that even these people sneaked into the United States via some land bridge between Russia and Alaska. Can anyone confirm or deny this? If this cannot be solved, we simply do not know what we are going to do for survival. By the way, can anyone inform me whether or not the indians make automobiles and television sets? Radios? Lawn mowers? Computers? I know they make rugs and lewelry, but I don't think I would look good wearing a formal rug, jewelry, and nothing

Joe could have refrained from writing and you, Wayne, could have let well enough alone and not commented on it. As it now stands, we (my wife and I) can't find too much to eat, enough clothing, automobiles that don't break down the day after warrantles expire, products that don't need screws straightened and decals glued back on, and worst of all-how about that ham I just heard calling CQ? He had a terrible accent and a foreign call! Do I dare invite him into our country by answering his call?

Wayne, you and Joe are troublemakers. Why didn't both of you just keep still so I could go on buying products on merit and

not because it was made here or there? All this time I thought I was a discerning purchaser picking and choosing that which worked best for me, and now you two come along and shatter my whole style of living. I'm thinking of giving up on 73 as I heard a rumor your stapling process for the magazine is of dubious parentage.

> Jim Oberto WA9YYV/7 Phoenix AZ

P.S. Was the /7 needed? I am confused now -- 10

BOOTLEGGER!

For the past six months, we have been receiving QSL cards for contacts made with EL7M. All attempts on our part to pinpoint the location of this illegal operator have falled.

Please be advised that the callsion EL7M is not a legally issued callsign by the Ministry of Post and Telecommunications. Republic of Liberia. The user of this callsion is therefore a bootlegger.

It would be appreciated if all legally licensed ham operators would assist us in trying to identify this individual and pass the word around of this illegal operation.

Please note that all QSL cards received by the EL Bureau for contacts made with EL7M will be discarded.

H. Walcott Benjamin EL2BA, President Liberia Radio Amateur Association Monrovia, Liberia

Sonofagun, you mean that two-meter contact with EL2M was a pirate? Damn!-Wayne.

TO THE HILT

The first thing I read when I get my 73 is your editorial and I always enjoy it to the hilt. If I ever have the chance to meet you face to face, I would like to shake your hand-I've always been an outspoken person myself.


As a new ham-a Novice at the age of 56-I got started late and sure wished I had known about amateur radio 30 years ago. I am now working with my wife and 14-year-old grandson on code.


Keep the good work up-we need more people like you to speak out.

> Gene Smith KASZAH Oroville CA

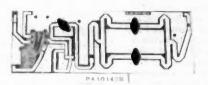A pox on the hams of Oroville for managing to keep amateur radio a secret from you all those years. I sure hope you won't carry on in the Oroville tradition Get out to the high school and get a ham club started, using your grandson balt.-Wayne.





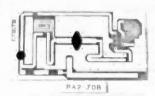

EIMAC 4CX10,000D/8171 with SK300 and SK1306

\$1200.00

SK300 and SK1306 Only.

\$ 350.00

(These are all new not used.) Limited Supply.

KLM ELECTRONICS, INC. VHF AMPLIFIER PC BOARDS AND RF TRANSISTOR KITS.

Model PA2-70B RF power input 2watts at 144 to 148MHz output 70watts 13.5vdc at 10amps. \$49.99 with data PC Board Only \$14.99

MODEL PA101408 RF power input 10wotts at 144 to 148MHz output 140watts 13.5vdc at 18amps. \$89.99 with data PC Board Only \$19.99

GENEVA CALCULATOR WATCH

This attractive watch has the following modes: Normal Time Setting, Calendar Setting, Daily Alarm Time Setting, Weekly Alarm Time Setting, Chronograph, Calculator.



Featured in Black Plastic

\$18.99

Featured in Stainless Steel or

\$29.99

SILICON DIODES

MR 7 5 1	100vdc	6Amps	10/\$5.00	100/\$38.00
MR 510	1000vdc	3Amps	10/\$3.75	100/\$24.00
HEP 170	1000vdc	2Amps	20/\$2.00	100/\$15.00
IN3209	100vdc	15Amps	\$2.00	10/ \$15.00
BYX21/200	200vdc	25Amps	\$2.00	10/ \$15.00
1N2138A	600vdc	60Amps	\$5.00	10/ \$40.00
DS85-04C	400vdc	80Amps	\$10.00	10/ \$80.00
1N3269	600vdc	160Amps	\$15.00	10/\$120.00
275Z41	300vdc	250Amps	\$20.00	10/\$175.00
7-5754	300vdc	400Amps	\$30.00	10/\$250.00
RCD-15	1 5KVDC	20ma.	\$3.00	10/ \$20.00
SMFR20K	20KVDC	20ma.	\$4.00	10/ \$30.00
1N4148	signal		30/\$1.00	100/ \$3.00

FAIRCHILD 4116 16K DYNAMIC RAMS 200ns. Part # 16K75

25 For \$25.00 or 100 For \$90.00 or 1000 For \$750.00

FEED THRU SOLDER RF CAPACTORS

470pf +-20%

5/\$1.00 or 100/\$15.00 or 1000/\$100.00

1000pf/.00luf +-10%

4/\$1.00 or 100/\$20.00 or 1000/\$150.00

E PROMS

2708 1024x1

\$2.00 each

2716 2048x8

\$4.00 each

27L32/25L32

\$10.00 each

HEWLETT PACKARD MICROWAVE DIODES

1N5711	(5082-2800)	Schottky	Barrier	Diodes	\$1.00 or 10 for	\$ 8.50
1N5712	(5082-2810)	11	11	11	\$1.50 or 10 for	\$10.00
1N6263	(HSCH-1001)	11	11	17	\$.75 or 10 for	
5082-2835		***	11	11	\$1.50 or 10 for	
5082-2805	Quad Matched	9.9	11	" per se	t \$5.00 or 10 for	

For information call: (602) 242-3037

Toll Free Number 800-528-0180 (For orders only)

MHz electronics

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item.

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

"MIXERS"

wATKINS JOHNSON WJ-M6 Double Balanced Mixer

LO and RF 0.2 to 300MHz

Conversion Loss (SSB)

IF DC to 300MHz 6.5dB Max. 1 to 50MHz 8.5dB Max. .2 to 300MHz

WITH DATA SHEET

\$21.00

Noise Figure (SSB)

same as above 8.5dB Max. 50 to 300MHz

Conversion Compression

.3dB Typ.

NEC (NIPPON ELECTRIC CO. LTD. NE57835/2SC2150 Microwave Transistor

NF Min F=2GHz F=3GHz

dB 2.4 Typ. dB 3.4 Typ. MAG F=2GHz

dB 12 Typ. dB 9 Typ.

\$5.30

F = 4 GHz

F=3GHz F=4GHz

dB 4.3 Typ.

dB 6.5 Typ.

Ft Gain Bandwidth Product at Vce=8v, Ic=10ma. GHz 4 Min. 6 Typ. Vcbo 25v Vceo 11v Vebo 3v Ic 50ma. Pt. 250mw

UNELCO RF Power and Linear Amplifier Capacitors

These are the famous capacitors used by all the RF Power and Linear Amplifier manufacturers, and described in the RF Data Book.

5pf	10pf	18pf	30pf	43pf	100pf	200pf 1	to	10pcs.	\$1.	.00	ea
5.1pf	12pf	22pf	32pf	5lpf	110pf	220pf 11	to	50pcs.	\$.	.90	eal
6.8pf	13pf	25pf	33pf	60pf	120pf	470pf 51	up	pcs.	\$.	. 80	ea
7pf	14pf	27pf	34pf	80pf	130pf	500pf	•	•			- 1
8.2pf	15pf	27.5pf	40pf	82pf	140pf	1000pf					

NIPPON ELECTRIC COMPANY TUNNEL DIODES

\$7.50 MODEL 1S2199 1S2200 Peak Pt. Current ma. 9min. 10Typ. 11max. 9min. 10Typ. 11max. Ιp Valley Pt. Current ma. Ιv 1.2Typ. 1.5max. 1.2Typ. 1.5max. Peak Pt. Voltage mv. 95Typ. 120max. Vp 75Typ. 90max. Projected Peak Pt. Voltage mv. Vpp Vf=Ip 480min. 550Typ. 630max. 440min. 520Typ. 600max. Series Res. Ohms rS 2.5Typ. 4max. 2Typ. 3max. Terminal Cap. pf. 1.7Typ. 2max. 5Typ. 8max. Ct Valley Pt. Voltage my. VV 370Typ. 350Typ.

FAIRCHILD / DUMONT Oscilloscope Probes Model 4290B

Input Impedance 10 meg., Input Capacity 6.5 to 12pf., Division Ratio (Volts/Div Factor) 10:1, Cable Length 4Ft. , Frequency Range Over 100MHz.

These Probes will work on all Tektronix, Hewlett Packard, and other Oscilloscopes.

PRICE \$45.00

MOTOROLA RF DATA BOOK

Listsall Motorola RF Transistors / RF Power Amplifiers, Varactor Diodes and much much more.

PRICE \$7.50

For information call: (602) 242-3037

Toll Free Number 800-528-0180 (For orders only)

MHz electronics

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

RF TRANSISTORS, MICROWAVE DIODES

	ICE		ICE	PART	PRICE
152199 \$	7.50	2N6083 \$	13.25	CA2612 (TRW)	\$ 25.00
1S2200	7.50	2N6084	15.00	CA2674 (TRW)	25.00
2N1561	25.00	2N6094 /M9622	11.00	CA2881-1(TRW)	25.00
	25.00	2N6095 /M9623	12.00	CA4101 (TRW)	25.00
2N2857	1.55	2N6096 /M9624	15.50	CA4201 (TRW)	25.00
2N2857JAN	2.55	2N6097	17.25	CA4600 (TRW)	25.00
	11.00	2N6136	21.85	CD1889	20.00
	18, 35	2N6166	40.25	CD2545	20.00
	15.50	2N6201	50.00	CMD514AB	20.00
2N2949	3.90	2N6459	18.00	D4959	10.00
2N2950	4.60	2N6603	12.00	D4987M	20.00
2N3375	8.00	2N6680	80.00	D5147D	10.00
2N3553	1.57	2SC756A	7.50	D5506	10.00
	13.80	2SC781	2.80	D5827AM	20.00
2N3818	5.00	2SC1018	1.00	DMD6022	30.00
2N3866	1.30	2SC1042	12.00	DMS-2A-250	40.00
2N3924	3.35	2SC1070	2.50	HEP76	4.95
2N3927	17.75	2SC1239	2.50	HEPS 3002	11.30
2N3950	25.00	2SC1251	12.00	HEPS3003	30.00
2N4072	1.80	2SC1306	2.90	HEPS 3005	10.00
	21.00	2SC1307	5.50	HEPS 3006	19.90
2N4427	1.30	2SC1760	1.50	HEPS3007	25.00
2N4428	1.85	2SC1970	2.50	HEPS3010	11.34
2N4957	3.45	2SC2166	5.50	HTEF2204 H.P.	112.00
2N4958	2.90	8B1087 (M.A.)	25.00	5082-0112 H.P.	14.20
2N4959	2.30	A50-12	20.00	5082-0253 H.P.	105.00
2N5090	13.90	A283B	5.00	5082-0233 H.P.	58.00
2N5108	4.00	ALD4200N (AVANTEK)	395.00	5082-0320 H.P.	POR
2N5109	1.70	AM123	-97.35	5082-0401 H.P.	POR
2N5160	3.45	AM688	100.00	5082-0401 H.F.	POR
	21.62	BB105B	. 52	5082-1028 H.P.	POR
2N5177 2N5179	1.00	BD4/4JFBD4 (G.E.)	10.00	5082-1028 H.F.	23.15
2N5583	4.00	BFQ85	1.50	5082-3080 H.P.	2.00
2N5589	8.65	BFR90	1.30	5082-3188 H.P.	1.00
2N5590	10.35	BFR91	1.65	5082-6459 H.P.	POR
2N5590 2N5591	13.80	BFW92	1.50	5082-8323 H.P.	POR
2N 5 6 3 5	10.95	BFX89	1.00	35826E H.P.	POR
2N5637	15.50	BFY90	1.00	35831E H.P.	29.99
	9.20		25.00		71.50
2N 564 1 2N 564 2	10.95	BGY 54 BGY 55	25.00	35853E H.P. 35854E H.P.	75.00
2N 5642 2N 5643	15.50	BGY74	25.00		75.60
	13.80	BG174 BGY75	25.00	HPA0241 H.P. HXTR3101 H.P.	
2N5645			10.00		7.00
2N5646	20.70 18.00	BL161 BLX67	11.00	HXTR3102 H.P.	8.75
2N5691		BLY568CF	25.00	HXTR6101/2N6617	
2N5764	27.00		13.00	HXTR6104 H.P.	68.00
2N 5836	5.45	BLY87	14.00	HXTR6105 H.P.	31.00
2N5842	8.00	BLY88		HXTR6106 H.P.	33.00
2N5849	20.00	BLY89	15.00	QSCH1995 H.P.	POR
2N5913	3.25	BLY90	20.00	J02000 TRW	10.00
2N5922	10.00	BLY351	10.00	J02001 TRW	25.00
2N5923	25.00	C4005	20.00	J04045 TRW	25.00
2N5941	23.00	CA402 (TRW)	25.00	K3A	10.00
2N5942	40.00	CA405 (TRW)	25.00	MA450A	10.00
2N 5944	9.20	CA612B (TRW)	25.00	MA41487	POR
2N5945	11.50	CA2100 (TRW)	25.00	MA41765	POR
2N5946	19.00	CA2113 (TRW)	25.00	MA 4 3 5 8 9	POR
	9.20	CA2200 (TRW)	25.00	MA43636	POR
2N6080°					DAD
2N6080 2N6081	10.35	CA2213 (TRW)	25.00	MA47044	POR
2N6080			25.00 25.00		25.50

Toll Free Number 800-528-0180 (For orders only)

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

For information call: (602) 242-3037

MHz electronics

GaAs, TUNNEL DIODES, ETC.

PART	PRICE	PART	PRICE	PART	DD T CD
MA47100	\$ 3.05	MRF503	\$ 6.00	PT4186B	PRICE
MA47202	30.80	MRF 504	7.00	PT4209	\$ POR
MA47771	POR	MRF 509	5.00		POR
MA47852	POR	MRF511	8.65	PT4209C	POR
MA49558	POR	MRF605	20.00	PT4566	POR
MB4021	POR	MRF629		PT4570	POR
MBD101	1.00	MRF644	3.47	PT4571	POR
MD0513	POR		23.00	PT4571A	POR
MHW1171	42.50	MRF816 MRF823	15.00	PT4577	POR
MHW1182	48.60		20.00	PT4590	POR
MHW4171	49.35	MRF901	3.00	PT4612	POR
MHW4172	51.90	MRF8004	2.10	PT4628	POR
MHW4342	68.75	MS261F	POR	PT4640	POR
MLP102	25.00	MT4150 Fair.	POR	PT4642	POR
MM1500	32.32	MT5126 Fair.	POR	PT5632	POR
MM1550	POR	MT5481 Fair.	POR	PT5749	POR
MM1552		MT5482 Fair.	POR	PT6612	POR
MM1553	50.00	MT5483 Fair.	POR	PT6626	POR
MM1614	50.00	MT5596 Fair.	POR	PT6709	POR
MM2608	10.00	MT5764 Fair.	POR	PT6720	POR
	5.00	MT8762 Fair.	POR	PT8510	POR
MM3375A	11.50	MV 109	.77	PT8524	POR
MM4429	10.00	MV 1 4 0 1	8.75	PT8609	POR
MM8000	1.15	MV 1 624	1.42	PT8633	POR
MM8006	2.30	MV 1805	15.00	PT8639	POR
MO277L	POR	MV 1808	10.00	PT8659	POR
MO283L	POR	MV1817B	10.00	PT8679	POR
MO3757	POR	MV 1863B	10.00	PT8708	POR
MP102	POR	MV1864A	10.00	PT8709	POR
MPN 3202	10.00	MV 1864B	10.00	PT8727	POR
MPN3401	. 52	MV 1864D	10.00	PT8731	POR
MPN 3412	1.00	MV1868D	10.00	PT8742	POR
MPSU31	1.01	MV2101	.90	PT8787	POR
MRA2023-1.5	TRW 42.50	MV 2 1 1 1	.90	PT9790	41.70
MRF212/208	16.10	MV2115	1.55	PT31962	POR
MRF223	13.25	MV2201	.53	PT31963	POR
MRF224	15.50	MV2203	. 53	PT31983	POR
MRF237	3.15	MV2209	2.00	PTX6680	POR
MRF238	12.65	MV2215	2.00	RAY-3	24.99
MRF243	25.00	MWA110	7.45	40081	POR
MRF245	34.50	MWA120	7.80	40281	POR
MRF247	34.50	MWA130	8.25	40282	POR
MRF304	43.45	MWA210	7.80	40290	POR
MRF315	23.00	MWA220	8.25	RF110	25.00
MRF420	20.00	MWA230	8.65	SCA3522	POR
MRF421	36.80	MWA 310	8.25	SCA3523	POR
MRF422	41.40	MWA320	8.65	SD1065	POR
MRF427	16.10	MWA330	9.50	SS43	POR
MRF428	46.00	NEC57835	5.30	TP1014	POR
MRF450/A	13.80	ON 382	5.00	TP1028	POR
MRF453/A	17.25	PPT515-20-3	POR	TRW-3	POR
MRF454/A	19.90	PRT8637	POR	UTO504 Avantek	70.00
MRF455/A	16.00	PSCQ2-160	POR	UTO511 Avantek	75.00
MRF458	19.90	PT3190	POR	V15	
MRF463	25.00	PT3194	POR		4.00
MRF472	1.00	PT3195	POR	V33B	4.00
MRF475	2.90	PT3537	POR	V100B	4.00
MRF477	11.50	PT4166E		VAB801EC	25.00
MRF 502	1.04	PT4176D	POR	VAB804EC	25.00
302	1.04	F141/0D	POR	VAS21AN20	25.00

Toll Free Number 800-528-0180 (For orders only)

"All parts may be new or surplus, and parts may be substituted with comparable parts If we are out of stock of an item."

MHz electronics

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

For information call: (602) 242-3037

COAXIAL RELAY SWITCHES SPDT

Electronic Specialty Co./Raven Electronics Part # 25N28 Part # SU-01 26Vdc Type N Connector, DC to 1 GHz.

FSN 5985-556-9683

\$49.00




Ampheno1 Part # 316-10102-8 115Vac Type BNC DC to 3 GHz. SPEC NA 5 7231-A US SER NO MER RAVEN ELECTRONICS 26176 PN SU 101

\$39.99

FXR Part # 300-11182 120Vac Type BNC DC to 4 GHz. FSN 5985-543-1225

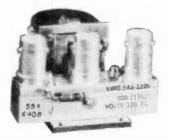FXR Part # 300-11173 120Vac Type BNC Same FSN 5985-543-1850





\$39.99

BNC To Banana Plug Coax Cable RG-58 36 inch or BNC to N Coax Cable RG-58 36 inch.

\$7.99 or 2 For \$13.99 or 10 For \$50.00

\$8.99 or 2 For \$15.99 or 10 For \$60.00





SOLID STATE RELAYS

P&B Model ECT1DB72 PRICE EACH \$5.00

5vdc turn on

120vac contact at 7amps or 20amps on a 10"x 10"x .124 aluminum. Heatsink with silicon grease.

Digisig, Inc. Model ECS-215 5vdc turn on PRICE EACH \$7.50

240vac contact 14amps or 40amps on a

10"x 10"x .124 aluminum. Heatsink with silicon grease.

Grigsby/Barton Model GB7400 5vdc turn on PRICE EACH \$7.50

240vac contact at 15amps or 40amps on a 10"x 10"x .124 aluminum. Heatsink with silicon grease.

NOTE: *** Items may be substituted with other brands or equivalent model numbers. ***



"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

Toll Free Number 800-528-0180 (For orders only)

For information call: (602) 242-3037

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

RECALL PHONE MEMORY TELEPHONE WITH 24 NUMBER AUTO DIALER

The Recall Phone Telephone employs the latest state of art communications technology. It is a combination telephone and automatic dialer that uses premium-quality, solid-state circuitry to assure high-reliability performance in personal or business applications.



ARON ALPHA RAPID BONDING GLUE

Super Glue #CE-486 high strength rapid bonding adhesive. Alpha Cyanoacrylate. Set-Time 20 to 40 sec., 0.7fl.oz.(20gm.)



TOUCH TONE PAD

This pad contains all the electronics to produce standard touch-tone tones. New with data.



MITSUMI UHF/VHF VARACTOR TUNER MODEL UVEIA

Perfect for those unscrambler projects. New with data.



\$9.99 or 10/\$89.99

\$19.99 or 10/\$149.99

INTEGRATED	CIRCUIT.	l to 10	llup
MC1372P	Color TV Video Modulator Circuit.	\$ 4,42	\$2.95
MC1358P	IF Amp., Limiter, FM Detector, Audio Driver, Electronic Attenuator.	5.00	4.00
MC1350P	IF Amplifier	1.50	1.25
MC1330A1P	Low Level Video Detector	1.50	1.15
MC1310P	FM Stereo Demodulator	4.29	3.30
MC1496P	Balanced Modulator/Demodulator	1.50	1.25
LM565N	Phase Locked Loop	2.50	2.00
LM380N14	2Watt Audio Power Amplifier	1.56	1.25
LM1889N	TV Video Modulator	5.00	4.00
NE564N	Phase Locked Loop	10.00	8.00
NE561N	Phase Locked Loop	10.00	8.00

FERRANTI ELECTRONICS AM RADIO RECEIVER MODEL ZN414 INTEGRATED CIRCUIT.

1.2 to 1.6 volt operating range.,Less than 0.5ma current consumption. 150KHz to 3MHz Frequency range. Easy to assemble, no alignment necessary. Effective and variable AGC action., Will drive an earphone direct. Excellent audio quality., Typical power gain of 72dB., TO-18 package. With data. \$2.99 or 10 For \$24.99

NI CAD RECHARGEABLE BATTERIES

AA Battery Pack of 6 These are Factory

SUB C Pack of 10 2.5Amp/Hr. \$10.00

Gates Rechargeable Battery Packs

12vdc at 2.5Amp/Hr. \$11.99 12vdc at 5Amp/Hr. \$15,99 MOTOROLA MRF559 RF TRANSISTOR hfe 30min 90typ 200max. ft 3000mhz gain 8db min 9.5typ at 870mhz 13db typ at 512mhz output power .5watts at 12.5vdc at 870mhz.

\$2.05 or 10/\$15.00



For information call: (602) 242-3037

Toll Free Number 800-528-0180 (For orders only) PRICES SUBJECT TO CHANGE WITHOUT NOTICE

MHz electronics

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

"SOCKETS AND CHIMNEYS"

EIMAC TUBE SOCKETS AND CHIMNEYS

SK110	Socket	\$POR
SK300A	Socket For 4CX5000A,R,J, 4CX10,000D, 4CX15,000A,J	\$520.00
SK400	Socket For 4-125A,250A,400A,400C,4PR125A,400A,4-500A,5-500A	260.00
SK406	Chimney For 4-250A, 400A, 400C, 4PR400A	74.00
SK416	Chimney For 3-400Z	36.00
SK500	Socket For 4-1000A/4PR1000A/B	390.00
SK600	Socket For 4CX250B, BC, FG, R, 4CX350A, F, FJ	51.00
SK602	Socket For 4CX250B, BC, FG, R, 4CX350A, F, FJ	73.00
SK606	Chimney For 4CX250B, BC, FG, R, 4CX350A, F, FJ	11.00
SK607	Socket For 4CX600J, JA	60.00
SK610	Socket For 4CX600J, JA	60.00
SK 620	Socket For 4CX600J, JA	66.00
SK626	Chimney For 4CX600J, JA	10.00
SK630	Socket For 4CX600J, JA	66.00
SK636B	Chimney For 4CX600J,JA	34.00
SK640	Socket For 4CX600J, JA	36.00
SK646	Chimney For 4CX600J, JA	71.00
SK700	Socket For 4CX300A,Y,4CX125C,F	225.00
SK711A	Socket For 4CX300A,Y,4CX125C,F	225.00
SK740	Socket For 4CX300A,Y,4CX125C,F	86.00
SK770	Socket For 4CX300A,Y,4CX125C,F	86.00
SK800A	Socket For 4CX1000A,4CX1500B	225.00
SK806	Chimney For 4CX1000A,4CX1500B	40.00
SK810	Socket For 4CX1000A, 4CX1500B	225.00
SK900	Socket For 4X500A	300.00
SK906	Chimney For 4X500A	57.00
SK1420	Socket For 5CX3000A	650.00
SK1490	Socket For 4CV8000A	585.00
JOHNSON TUB	E SOCKETS AND CHIMNEYS	
124-111/SK6	O6 Chimney For 4CX250B,BC,FG,R, 4CX350A,F,FJ	\$ 10.00
124 111/ JRO	diffiliney for some some some some some some some some	(-1-)15 00

124-111/SK606	Chimney For 4CX250B, BC, FG, R, 4CX350A, F, FJ	\$ 10.00
122-0275-001	Socket For 3-500Z, 4-125A, 250A, 400A, 4-500A, 5-500A	(pair) 15.00
124-0113-00	Capacitor Ring	15.00
124-116/SK630A	Socket For 4CX250B, BC, FG, R, /4CX350A, F, FJ	55.00
124-115-2/SK620A	Socket For 4CX250B, BC, FG, R, /4CX350A, F, FJ	55.00
	813 Tube Socket	20.00

				22.00.00	
				TUBE CAPS (Plate)	
CHIP CAPACITO	RS		= 19	HR1, 4	\$11.00
.8pf	10pf	100pf*	430pf	HR2,3, 6 & 7	13.00
1pf	12pf	110pf	470pf	HR5, 8	14.00
1.1pf	15pf	120pf	510pf	HR9	17.00
1.4pf	18p f	130pf	560pf	HR10	20.00
1.5pf	20pf	150pf	620pf		
1.8pf	22pf	160pf	680pf		
2.2pf	24 pf	180pf	820pf		
2.7pf	27pf	200pf	1000pf/.	001uf*	
3.3pf	33pf	220pf*	1800pf/.	0018uf	
3.6pf	39pf	240pf	2700pf/.	0027uf	
3.9pf	47pf	270pf	10,000pf	7.01uf	

330pf 15,000pf/.015uf 5.6pf 56pf 6.8pf 68pf 360pf 18,000pf/.018uf 390pf 82pf 8.2pf .99¢ 101 to 1000 .60¢ * IS A SPECIAL PRICE: 10 for \$7.50 PRICES: 1 to 10 -100 for \$65.00 11 to 50 - .90¢ 1001 & UP 51 to 100 - .80¢ 1000 for \$350.00

300pf

WATKINS JOHNSON WJ-V907: Voltage Controlled Microwave Oscillator \$110.00

Frequency range 3.6 to 4.2GHz, Power ouput, Min. 10d8m typical, 8d8m Guaranteed. Spurious output suppression Harmonic (nf_0), min. 20d8 typical, In-Band Non-Harmonic, min. 60d8 typical, Residual FM, pk to pk, Max. 5KHz, pushing factor, Max. 8KHz/V, Pulling figure (1.5:1 VSWR), Max. 60MHz, Tuning voltage range +1 to +15volts, Tuning current, Max. -0.1mA, modulation sensitivity range, Max. 120 to 30MHz/V, Input capacitance, Max. 100pf, Oscillator Bias +15 +-0.05 volts @ 55mA, Max.

Toll Free Number 800-528-0180 (For orders only)

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an Item."

51pf



12,000pf/.012uf

For information call: (602) 242-3037

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

TUBES

TYPE	PRICE	TYPE	PRICE	TYPE	PRICE
2C39/7289	\$ 34.00	1182/4600A	\$500.00	ML7815AL	\$ 60.00
2E26	7.95	4600A	500.00	7843	107.00
2K28	200.00	4624	310.00	7854	130.00
3-500Z	102.00	4657	84.00	ML7855KAL	125.00
3-1000Z/8164	400.00	4662	100.00	7984	14.95
3B28/866A	9.50	4665	500.00	8072	84.00
3CX400U7/8961	255.00	4687	P.O.R.	8106	5.00
3CX1000A7/8283	526.00	5675	42.00	8117A	225.00
3CX3000F1/8239	567.00	5721	250.00	8121	110.00
3Cw30000H7	1700.00	5768	125.00	8122	110.00
3X2500A3	473.00	5819	119.00	8134	470.00
3X3000F1	567.00	5836	232.50	8156	12.00
4-65A/8165	69.00	5837	232.50	8233	60.00
4-125A/4D21	79.00	5861	140.00	8236	35.00
4-250A/5D22	98.00	5867A	185.00	8295/PL172	500.00
4-400A/8438	98.00	5868/AX9902	270.00	8458	35.00
4-400B/7527	110.00	5876/A	42.00	8462	130.00
4-400C/6775 4-1000A/8166	110.00	5881/6L6	8.00	8505A	95.00
4CX250B/7203	444.00 54.00	5893	60.00	8533W	136.00
4CX250FG/8621	75.00	5894/A 5894B/8737	54.00 54.00	8560/A	75.00
4CX250K/8245	125.00	5946	395.00	8560AS 8608	100.00
4CX250R/7580W	90.00	6083/AZ9909	95.00	8624	38.00 100.00
4CX300A/8167	170.00	6146/6146A	8.50	8637	70.00
4CX350A/8321	110.00	6146B/8298	10.50	8643	83.00
4CX350F/8322	115.00	6146W/7212	17.95	8647	168.00
4CX350FJ/8904	140.00	6156	110.00	8683	95.00
4CX600J/8809	835.00	6159	13.85	8877	465.00
4CX1000A/8168	242.50*	6159B	23.50	8908	13.00
4CX1000A/8168	485.00	6161	325.00	8950	13.00
4CX1500B/8660	555.00	6280	42.50	8930	137.00
4CX5000A/8170	1100.00	6291	180.00	6L6 Metal	25.00
4CX10000D/8171	1255.00	6293	24.00	6L6GC	5.03
4CX15000A/8281	1500.00	6326	P.O.R.	6CA7/EL34	5.38
4CW800F 4D32	710.00	6360/A 6399	5.75	6CL6	3.50
4E27A/5-125B	240.00	6550A	540.00	6DJ8	2.50
4PR60A	200.00	6883B/8032A/8552	10.00 10.00	6DQ5 6GF5	6.58
4PR60B	345.00	6897	160.00	6GJ5A	5.85
4PR65A/8187	175.00	6907	79.00	6GK6	6.20 6.00
4PR1000A/8189	590.00	6922/6DJ8	5.00	6HB5	6.00
4X150A/7034	60.00	6939	22.00	6HF5	8.73
4X150D/7609	95.00	7094	250.00	6JG6A	6.28
4 X 2 5 0 B	45.00	7117	38.50	6JM6	6.00
4X250F	45.00	7203	P.O.R.	6JN6	6.00
4X500A	412.00	7211	100.00	6JS6C	7.25
5CX1500A	660.00	7213	300.00*	6KN6	5.05
KT88	27.50	7214	300.00*	6KD6	8.25
416B	45.00	7271	135.00	6LF6	7.00
416C 572B/T160L	62.50 49.95	7289/2C39	34.00	6LQ6 G.E.	7.00
592/3-200A3	211.00	7325 7360	P.O.R. 13.50	6LQ6/6MJ6 Sylvania	9.00
807	8.50	7377	85.00	6ME 6 12AT7	8.90 3.50
811A	15.00	7408	2.50	12A77	3.00
812A	29.00	7609	95.00	12BY7	5.00
813	50.00	7735	36.00	12JB6A	6.50

NOTE * = USED TUBE

NOTE P.O.R. = PRICE ON REQUEST

"ALL PARTS MAY BE NEW, USED, OR SURPLUS. PARTS MAY BE SUBSTITUTED WITH COMPARABLE PARTS IF WE ARE OUT OF STOCK OF AN ITEM.

NOTICE: ALL PRICES ARE SUBJECT TO CHANGE WITHOUT NOTICE.

Toll Free Number 800-528-0180 (For orders only)

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an Item."



PRICES SUBJECT TO CHANGE WITHOUT NOTICE

"FILTERS"

COLLINS Mechanical Filter #526-9724

POWER OUTPUT 58K OHM 1WAT OTRON MUF	T BALLAST 100 FIN FANS Model	OVDC +-100VDC At 3.7MA	TARTING VOLTAGE DC \$59
OWER OUTPUT 58K OHM 1WAT	T BALLAST 100	OVDC +-100VDC At 3.7MA	
	1.6MW. REA	M DIA75MM REAM DID 2 7MD 0000 0	TIN DOTTING TIOT OF THE
SPECTRA PH	1100 11101 1100		
	YSICS INC Mod	el 088 Hene LASER TUBES	
ATSUSHIRA	EFC-L455K	455KHz	7.
OKIN	CF455A/BFU455K	455KHz +-2KHz	10.
	LF-C18	455KHz	2.
	LF-B6/CFU455H	455KHz +-1KHz 455KHz	2.
IPPON	LF-B4/CFU455I LF-B6/CFU455H		2.
TDDON1	SFG10.7MA	10.7MHz	10
	SFE10.7MS	10,7MHz 230KHz +-50KHz at 3dB , 570KHz at 20dB	2
	SFE10.7MA	10.7MHz 280KHz +-50KHz at 3dB , 650KHz at 20dB	2
	SFD455D	455KHz +-2KHz , 3dB bandwidth 4.5KHz +-1KHz	2 5
	SFB455D	455KHz 455KHz at 60B , 455KHz at 40dB	2
	CFW455H	455KHz +-10KHz at 6dB , +-20KHz at 40dB 455KHz +-3KHz at 6dB , +-9KHz at 40dB	2
	CFU455I CFW455D	455KHz +1KHz bandwidth +2KHz at 6dB , +6KHz at 4	
	CFU455H	455KHz +1KHz bandwidth +3KHz at 6dB , +9KHz at	40dB 2
	CFU455G	455KHz +-1KHz bandwidth +-4.5KHz at 6dB , +-10KHz a	at 40dB 2
	CFU455C	455KHz +-2KHz bandwidth +-12.5KHz at 6dB , +-24KHz	at 40dB 2
	CFU455B	455KHz +-2KHz bandwidth +-15KHz at 6dB, +-30KHz at	40dB 2
	CFR455E	455KHz +5.5KHz at 3dB , +8KHz at 6dB , +16KHz at	t 60dB 8
	CFM455D	455Niz +7KHz at 3dB , +10KHz at 6dB , +20KHz at	50dB 6
	CFM455E	455KHz +-5.5KHz at 3dB , +-8KHz at 6dB , +-16KHz at	50dp 6
NATES	BFB455L	455KHz 455KHz	2
JRATA	TCF4-12D36A BFB455B	455KHz+-1KHz bandwidth 6dB min 12KHz, 60dB max 36KH	
LEVITE	TO-01A	455KHz+-2KHz bandwidth 4-7% at 3dB	5
XEL	4F449	12.6KC Bandpass Filter 3dB bandwidth 1.6KHz from 1	1.8-13.4KHz 10
ERAMIC F	ILTERS		
******	*************	*************	******
ILTECH	2131	CF 7.825MHz	10
RC	ERXF-15700	20.6MHz 36KHz wide	10
OMTECH	A10300	45MHz 2pole 15KHz bandwidth	6
rı	1479	10.7MHz 8pole bandwidth 7.5KHz at 3dB, 5KHz at 6dB	20
TI	5426C	21.4MHz 2pole 15KHz bandwidth	5
TI .	5350C	12MHz 2pole 15KHz bandwidth	5
OTOROLA	4884863B01	11.7MHz 2pole 15kHz bandwidth	5
YCO/CD	001019880	10.7MHz 2pole 15KHz bandwidth	19
AMA	TF-31H250	CF 3179.3KHz	10
DK	FEC-103-2 SCH-113A	10.6935MHz 11.2735MHz	10
IKKO EW	FX-07800C	7.8MHz	\$10
RYSTAL F			
DVCTAL F	IL TEDO		*********
Lowe:	r sideband. (ZL)	**********************	19.99
Uppe	r sideband. (ZU)	mency of 453.5KC. Carrier Frequency of 455KHz 2.36KC	Bandwidth.
4550	Un at Contan Dans	Thecharical Firter #HF-455-ZL/ZU-ZIM	
KUKIIS	SAI FLECTRIC CO	. Mechanical Filter #MF-455-ZL/ZU-21H	
6 pol	e 2.7KHz wide at	dB. Impedance 680ohms 7pf In/300ohms 8pf out. CW-159	99Hz 19.99
9.0US			
4 pol	e 500 cycles wide	CW. Impedance 800ohms 15pf In/800ohms Opf out.	19.99
5.595	500/4, 5.5955	00/4/CW	
8 pol	e 2.7Khz wide Upp	er sideband. Impedence 800ohms 15pf In/800ohms 0pf ou	ıt. 19.99
5.595	-2.7/8/U, 5.595-2	.7/USB	
		er sideband. Impedence 800ohms 15pf In/800ohms 0pf on	ıt. 19.99
	-2.7/8/LSB, 5.595	-2.7/ISB	
HILAS CIY	stal Filters		
ALLAC CEL			
		May be other models but equivalent. May be used or	

MHz electronics

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

Toll Free Number 800-528-0180 (For orders only) "All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an Item."

For information call: (602) 242-3037

HEWLETT PACKARD SIGNAL GENERATORS

606A	50KHz to 65MHz in 6 bands •-1%,Outout level odjustable 0.lu to 3V inta 50 ohms. Built-in crystal calibratar. 400 -1000Hz		6168	Same as above but later model.	\$ 600.00
606B	modulation. Some as obove but has frequency control feature to allow	\$ 650,00	6188	3.8 to 7.6GHz range, with collibrated autput and selection of pulse-FM or saudre wave modulation.	\$ 600.00
	operation with HP 8708A Synchronizer.	\$1100.00	61 8 C	Same as above but later model.	\$2200.00
6080	10MHz to $48OMHz,0-1uV-1V$ into 50 ohms,AM,CW,ar bulse modulation, calibrated attenuator.	\$ 500.00	620A	7 to 11GHz range, with calibrated output and selection of pulse-FM or sauore wave modulation.	\$ 750.00
608D/ 1S510	10MHz to 420MHz, 0.1uV-0.5V into 50 ohms,+-0.5% accuracy, built-in crystal calibrator, AM-CW or pulse output.	\$ 375.00	620B	Same as above but later model.	\$2200.00
608E	Improved version of popular 608C. Up to 1V output. Improved stability, law residual FM.	\$1450.00	626A	10 to 15GHz,10mw autput power with calibrated output and pulse-sauore wave or FM modulation.	\$4200.00
608F	10MHz to 455MHz in 5 pands1% frequency accuracy with built-in crystal calibrator.Can be used with HP 8708A Synchronizer. Outbut continuously adjustable from .luV to .5V into 50 ahms.	\$1100.00	870 8 A	Synchronizer used with 606B,60BF. The synchronizer is a phase-lock frequency stabilizer which provides crystal-ascillator frequency stability to 450MF in the 60BF signal generator. Phase locking eliminates microphonics and drift resulting in excellent frequency stability. The 870BA included a vernier which can tune the reference oscillator over a round the stability of the stab	le s
612A	450-1230MHz ,o.luV-Q.5V into 50 ohms,calibrated output.	\$ 750.00		of +-0.25% permitting frequency settability to 2 ports in 1 to the seventh.Provides a very stable signal that satisfies	0
614A	900-2100MHz with many features including calibrated output and all modulation characteristics.	\$ 500.00		many critical applications. (With HP 606B ar 608F) (Without)	\$ 350.00 \$ 450.00
616A/ TS403	Direct reading and direct control from 1.8 to 4.2GHz. The H.P.616A features *-1.5d8 calibrated output accuracy from -3127dBm to -dBm. The output is directly calibrated in micro valts and dBm with continuous monitoring. Simple operation frequency olido occuracy is *-1% and stability exceeds 0.005		EMC-10	ELECTROMETRICS EMC-10 RFI/EM1 RECEIVER Low frequency analyzer covering 20Hz to 50KHz frequency range.Extendable to 500 KHz in wideband mode.	\$2500.00
	/ C change in ambient temperature. Collbrated attenuator is within ~ 1.5dB over entire output band, 50 ohm impedance un has internal pulse modulation with rep rate variable from 4 Hz to 44Hz, variable pulsewidth(1 to 10usec) and variable pul	it 0 se	NF-105F	Empire Devices Field Intensity Meter Has NF-105/TA,NF-105/TX,NF-105/T1,NF-105/T2,NF-105/T3. Covers 14KHz to 1000MHz.	\$2100.00
	delay(3 to 300usec).External modulating inputs increas versatility.	\$ 375,00		ALL EQUIPMENT CARRY A 30 DAY GUARANTEE.	

UNEX LABORATORIES THS-2 FLEXICOM HEADSET.

these headsets come with data to hook up to a ICOM radios and many other equipment.

Perfect for Airplanes , Helicopters , Mobile Radios , or Just the Telephone.

These Are Factory New In Sealed Boxes, Limited Supply Only



ORGERING INSTRUCTIONS

EQUIPMENT IS NOT CALIBRATED.

DEFECTIVE MATERIAL. All claims to defective material must be made within sixty (60) days after receipt of parcel. All claims must include the defective material (for testing purposes), our invoice number, and the date of purchase. All returns must be packed property or it will void all warranties.

DELIVERY: Orders are normally shipped within 48 hours after receipt of customer's order. It a part has to be backordered the customer is notified. Our normal shipping method is via First Class Mail or UPS depending on size and weight of the package. On test equipment it is by Air only, FOB shipping point.

FOREIGN ORDERS: All foreign orders must be prepaid with cashier's check or money order made out in U.S. Funds. We are sorry but C.O.O. is not available to foreign countries and Letters of Credit are not an acceptable form of payment either. Further information is available on request.

HOURS: Monday thru Saturday: 8:30 a.m. to 5:00 p.m.

INSURANCE: Please include 25¢ for each additional \$100,00 over \$100.00, United Parcel only

ORGER FORMS: New order forms are included with each order for your convenience. Additional forms are

POSTAGE: Minimum shipping and handling in the US, Canada, and Mexico is \$2.50 all other countries is \$5.00 On foreign orders include 20% shipping and handling.

PREPAID ORDERS: Order must be accompanied by a check.

PRICES: Prices are subject to change without notice.

RESTOCK CHARGE: If parts are returned to MHZ Electronics due to customer error, customer will be higgsonsible for all extra fees, will be charged a 15% restocking fee, with the remainder in credit only. All returnust have approval.

SMORTAGE OR DAMAGE: All claims for shortages or damages must be made within 5 days after receipt of parcel. Claims must include our invoice number and the date of purchase. Customers which do not notify us within this time period will be held responsible for the entire order as we will consider the order complete.

OUR 800 NUMBER IS STRICTLY FOR ORDERS ONLY NO INFORMATION WILL BE GIVEN, 1-800-528-0180

TERMS: DOMESTIC: Prepaid, C.O.D. or Credit Card

TERMIS 'DOMESTIC: Prepaid, C.O.D. or Lireoit Lairo
FOREIGN. Prepaid only, U.S. Funds—money order or cashier's check only
C.O.O.1: Acceptable by telephone or mail. Payment from customer will be by cash, money order or cashier's
check. We are sorry but we cannot accept personal checks for C.O.D. CONFIRMING ORDERS: We would prefer that confirming orders not be sent after a telephone order has been

placed. If company policy necessifates a confirming order, please mark. "CONFIRMING" boildy on the order if problems or duplicate shipments occur due to an order which is not properly marked, dustomers will be neld responsible for any charges incurred, plus a 15% restock charge on returned parts.

CREDIT CARDS: WE ACCEPT MASTERCARD VISA AND AMERICAN EXPRESS.

QATA SHEETS. When we have data sheets in stock on devices we do supply them with the order



"All parts may be new or surplus, and parts may be substituted with comparable parts

if we are out of stock of an item.

For information call: (602) 242-3037 2111 W. CAMELBACK ROAD PHOENIX, ARIZONA 85015

> Toll Free Number 800-528-0180 (For orders only)

WAYNE GREEN BOOKS

KILOBAUD KLASSROOM

by George Young and Peter Stark

Makes learning electronics fun and easy. First published as a series in Kilobaud Microcomputing, the book combines the learning of essential theory with practical, hands-on experience. The course begins with basic electronic projects and culminates in the construction of your own programmable microcomputer. The direct instructional methods of authors Young & Stark make KILOBAUD KLASSROOM a simple way for you to acquire a solid background in digital electronics.

BK7386 (419 pages).....\$14.95





THE SELECTRIC INTERFACE by George Young


You need the quality print that a daisy wheel printer provides but the thought of buying one makes your wallet wilt. The SELECTRICTM INTERFACE, a step-by-step guide to interfacing an IBM Selectric I/O Writer to your microcomputer, will give you that quality at a fraction of the price. George Young, co-author of *Kilohaud Microcomputing* magazine's popular "Kilohaud Klassroom" series, offers a low-cost alternative to buying a daisy wheel printer. The SELECTRIC INTERFACE includes: step-by-step instructions, tips on purchasing a used Selectric, information on various Selectric models, including the 2740, 2980, and Dura 1041, driver software for Z80, 8080, and 6502 chips, tips on interfacing techniques. With The SELECTRIC INTERFACE and some background in electronics, you can have a high-quality, low-cost, letter-quality printer. Petals not included.


BK7388 (125 pages)......\$12.97

GENERAL LICENSE STUDY GUIDE

By Timothy M. Daniel N8RK

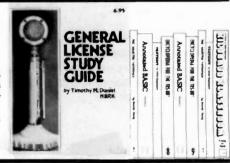This is the complete guide to the General License. Learning rather than memorizing is the secret. This is not a question-and-answer guide that will gather dust when the FCC issues a new test. Instead, this book will be a helpful reference, useful long after a ham upgrades to General. Includes up-to-date FCC rules and an application form. Order yours today and talk to the world.



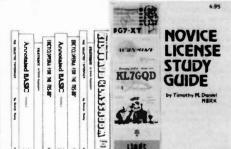

NOVICE LICENSE STUDY GUIDE

By Timothy M. Daniel N8RK

Here is the most up-to-date novice guide available. It is complete with information about learning Morse code, has the latest FCC amateur regulations and the current FCC application forms. This guide is not a question/answer memorization course but rather it emphasizes the practical side of getting a ham license and putting a station on the air. It reflects what the FCC expects a Novice to know without page after page of dull theory. The most current information still available at last year's price.


SG7357 (98 pages). \$4.95

THE NEW WEATHER SATELLITE HANDBOOK by Dr. Ralph E. Taggart WB8DQT




Here is the completely updated and revised edition of the best-selling Weather Satellite Handbook—containing all the information on the most sophisticated and effective spacecraft now in orbit. Dr. Taggart has written this book to serve both the experienced amateur satellite enthusiast and the newcomer. The book is an introduction to satellite watching, providing all the information required to construct a complete and highly effective ground station. Not just ideas, but solid hardware designs and all the instruction necessary to operate the equipment are included. For the thousands of experimenters who are operating stations, the book details all procedures necessary to modify their equipment for the new series of spacecraft. Amateur weather satellite activity represents a unique blend of interests encompassing electronics, meteorology and astronautics. Join the privileged few in watching the spectacle of earth as seen from space on your own monitoring equipment.

BK7383 (132 pages).....\$8.95

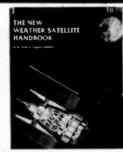

FOR TOLL-FREE ORDERING CALL 1-800-258-5473 WAYNE GREEN BOOKS • PETERBOROUGH NH 03458 Wayne Green Books • Att: Sales, Peterborough, NH 03458, Be sure to

Itemize your order on a separate piece of paper and mail to Wayne Green Books, Att: Sales, Peterborough, NH 03458. Be sure to include check or detailed credit card information. (Visa, MC or AMEX accepted.) No C.O.D. orders accepted. All orders add \$1.50 for the first book, postage and handling; \$1.00 each additional book; \$10.00 per book foreign air mail. Please allow 4-6 weeks after publication for delivery. Questions regarding your order? Please write to Customer Service at the above address.

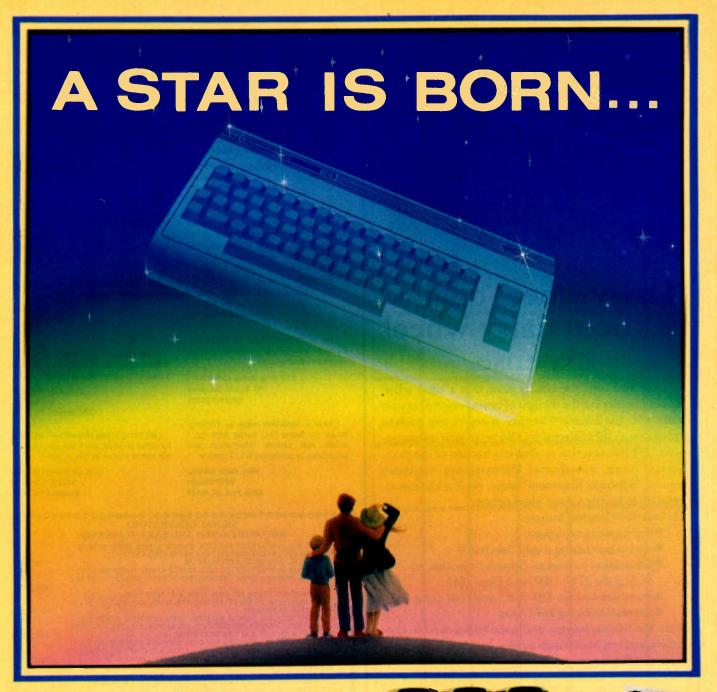

RUN has arrived for your Commodore 64 and VIC-20 computers.

RUN, the exciting new monthly that takes you beyond your instruction manual. RUN, packed with current information, entertaining programs, sage advice, and pure fun. RUN takes you from

- beginning BASIC to advanced graphics.
- candid product reviews to exciting new programs to type in and use.
- games to applications to informative tutorials.

Information. Entertainment. Advice. Fun. .. RUN has it all and for only \$19.97 per year. Subscribe today and get a 13th issue FREE with pre-payment by check or credit card.

Catch a rising star. . . RUN.

Start your subscription sooner by calling toll-free 1-800-258-5473

Send me a subscription to RUN for only \$19.97 per year. I understand that with payment enclosed or credit card order, I will receive a FREE is-

sue for a total of 13 issues for \$19.97. ☐ MC ☐ VISA ☐ Check/MO ☐ AE

☐ Bill me \$19.97 for 12 issues.

_____ Exp. Date_ Signature_


Name

___ State__ Zip 33NC8

Canada & Mexico \$22.97/1 year only, US funds drawn on US bank. Foreign Surface \$39.97/1 year only, US funds drawn on US bank. Foreign airmail, please inquire. Please allow 6-8 weeks for delivery.

RUN • PO Box 954 • Farmingdale, NY 11737

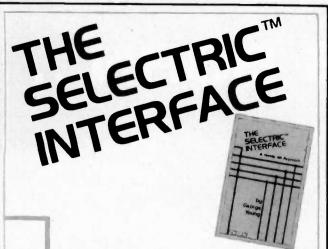Commodore 64 and VIC-20 are registered trademarks of Commodore Business Machines, Inc.



Daisy wheel quality without daisy wheel expense.

You need the quality print that a daisy wheel printer provides but the thought of buying one makes your wallet wilt. The Selectric™ Interface, a step-by-step guide to interfacing an IBM Selectric I/O Writer to your microcomputer, will give you that quality at a fraction of the price. George Young, co-author of Microcomputing magazine's popular "Kilobaud Klassroom" series, offers a low-cost alternative to buying a daisy wheel printer.

The SelectricTM Interface includes:

- step-by-step instructions
- ●tips on purchasing a used Selectric™
- information on various Selectric™ models. Including the 2740, 2980, and Dura 1041
- driver software for Z80, 8080, and 6502 chips
- tips on interfacing techniques

With The Selectric Interface and some background in electronics, you can have a high-quality, low cost, letter-quality printer. Petals not included.

Credit card orders call TOLLIFREE 1-800-258-5473. Or mail your order with payment plus \$1.50 shipping and handling to: Wayne Green Inc. Attn: Retail Book Sales, Peterborough, NH 03458.

Dealer inquiries invited.

ISBN 0-88006-051-4	128 pages	φ12.97
☐ Yes, I want Selectric copy plus \$1.50 for shipp		Enclosed is \$12.97 per
□MASTER	□VISA	□AMEX
Card #		ге
Signature		
Name		
Address		
City		
State and Zip		
All orders hipped UPS if complete	te street address is given.	33NB6S

HAM HELP

I am looking for the service and instruction manuals for the CDE HAM III/CD 44 rotor, manufactured by Cornell-Dubiller. I will pay copying and postage costs.

> Karl Mesquita Leite PS7KM Caixa Postal 385 59000 Natal, RN Brazil

Can anyone help me find the service manual or any other information on the Galaxy III transceiver? It was made by World Radio Labs some years back. I also need a base or mobile power supply for the Galaxy III.

> James E. Crawford KD5YD PO Box 643 Lovington NM 99260

I am trying to Interface my VIC-20 with my ham rig and would like any software or hardware information.

> SFC Skip Barley KA4ROY/13 167 Signal Company APO NY 09221

I have a hand-held made by Westinghouse Air Brake Co., model RPN-150. I would like service information and assistance in converting it to 2 meters.

> Mike Antio KASRIJ 9940 Hubert Allen Park MI 48101

I need the service manual or schematics for a Sonar 40 transceiver. I will pay copying and postage costs.

> Alvaro Alberto P. Miranda R. Joaquim Borges, 706 13300 ITU-SP, Brazil

I want to convert my 9-V broadcastband radio to receive between 5.4 and 16 MHz. Does anyone have any suggestions?

> Kevin Neal Rt. Box 221A Flippin AR 72634

For a CB conversion project, I need the schematic for a Hy-Gain 2710X.

> Kenneth Aston 650 La Seda Rd., Sp. 3-A La Puente CA 91744

I need the service manual and schematic for the Bearcat 250 scanner, I will make a copy of the original and return.

> C. Frazier K9FWF/4 PO Box 972 Windermere FL 32786

I am trying to use Motorola HT batteries for other projects, but I can only draw 20 mA before tripout, is this proper

> G. C. La Grange W5AKQ 3188 E. Circle Dr. Baytown TX 77521

> > \$285.00

\$245.00 \$325.00

\$550.00 \$850.00

\$ ********************************** SIGNAL GENERATORS RECONDITIONED AND LAB CALIBRATED

AN/URM-25 MILITARY SIG GEN, RANGE 10 KHZ THRU 50 MHZ, AM/CW, MODULATION 400/1000 HZ, CALIBRATED OUTPUT. PRECISION 50 OHM STOP ATTENUATOR AN/URM-26 MILITARY SIG GEN RANGE 4 MHZ THRU 405 MHZ, 400/1000 HZ MODULATION, CALIBRATED OUTPUT, SMALL COMPACT STAFF \$285.00 400/1000 HZ MODULATION, CALIBRATED OUTPUT, SMALL COMPACT SIZE
TS-510/U MILITARY SIG GEN, RANGE 10 MHZ THRU 420 MHZ,
OUTPUT VOLTAGE. 5V TO 1V, MODULATION 400/1000 HZ AM/CW OR
PULSE, SAME AS HP-608D
HP-614 SIG GEN, RANGE 900 MHZ THRU 2100 MHZ, AM/PULSE
MODULATION CALIBRATED OUTPUT, IDEAL FOR AMATEUR 1.2 GHZ,
MICROWAVE OR AIRCRAFT RADIO REPAIR
SG-557/URM-52 MILITARY SIG GEN, RANGE 3.8 GHZ THRU 7.8
GHZ, AM/PULSE CALIBRATED ATTENUATOR, MILITARY EQUIVALENT
TO HP-618A, IDEAL FOR SATELLITE OR MICROWAVE REPAIR
TS-418/URM-49 RANGE 400 MHZ THRU 1000 MHZ, AM/CW OR
PULSE MODULATION, CALIBRATED ATTENUATOR
TS-419/URM-64 RANGE 900 THRU 2100 MHZ, CW OR PULSE
MODULATION, CALIBRATED ATTENUATOR
SG-13/U AIRCRAFT VOR/ILS MILITARY SIG GEN, RANGE 108
THRU 135.9 MHZ AND 329.9 TO 335 MHZ, OUTPUT SIGNALS INCLUDE
VOR, LOC AND GLIDESLOPE AND 1000 CPS, SAME AS COLLINS 479T-2.
OPERATES FROM 28 VDC AT 3½ AMPS BENCH POWER SUPPLY OR
AIRCRAFT BATTERY, IDEAL FOR AIRCRAFT RADIO REPAIR
SG-66/ARM-5 AIRCRAFT OMN SIG GEN, RANGE 108 MHZ THRU
132 MHZ, CALIBRATION OUTPUT AND MODULATION IDEAL FOR
AIRCRAFT ASTITERY, IDEAL FOR AIRCRAFT RADIO REPAIR
SG-66/ARM-5 AIRCRAFT VOR RECEIVERS, MILITARY VERSION OF
ARC H-14A
IERROILD 900A SWEEP GENERATOR. RANGE 0.5 THRU 1200 MHZ. \$285.00 \$345.00 \$345.00 \$345.00 \$225.00 \$225.00

ARC H-14A

JERROLD 900A SWEEP GENERATOR, RANGE 0.5 THRU 1200 MHZ.

0.5 TO 400 MHZ SWEEP WIDTH, OUTPUT FLAT .5DB TO 800 MHZ, 1.5

DB TO 1200 MHZ, BUILT-IN RF DETECTOR

MARCONI TF-1066B AM/FM SIG GEN, RANGE 10 MHZ THRU 470

MHZ, INTERNAL FM OF 1 AND 5 KHZ WITH 100 KHZ VARIABLE

DEVIATION, AM MODULATION OF 1 AND 5 KHZ, CALIBRATED

OUTPUT, HAS MANY EXCELLENT FEATURES

HP 608E SIG GEN, RANGE 10 MHZ THRU 480 MHZ, CALIBRATED

OUTPUT, PRECISION ATTENUATOR, INTERNAL AND EXTERNAL AM, CRYSTAL CALIBRATOR

MOTOROLA T-1034 FM SIG GEN, RANGE 25-54 MHZ, 130-175

MHZ, 400-470 MHZ AND 890-960 MHZ, VARIABLE OUTPUT FROM 0.1

MY TO 100,000 MY, CALIBRATED ATTENUATOR

MV TO 100,000 MV, CALIBRATED ATTENUATOR

WE SHIP BEST WAY, SHIPPING CHARGES COLLECT, 30-DAY MONEY-BACK GUARANTEE. SEND CHECK, VISA OR M/C...PHONE BILL SLEP, 704-524-7519.



Slep Electronics Company

P.O. BOX 100, HWY. 441 OTTO, NORTH CAROLINA 28763:

RAMSEY **ELECTRONIC'S**

PARTS WAREHOUSE

2575 Baird Rd. Penfield, NY 14526 716-586-3950

We now have available a bunch of goodies too good to bypass. Items are limited so order today

GREAT FOR THAT AFTERNOON HOBBY.

MINI KITS - YOU HAVE SEEN THESE BEFORE NOW HERE ARE OLD FAVORITE AND NEW ONES TOO.

FM MINI MIKE



A super high performance FM wireless mike kit! Transmits a stable signal up to 300 yards with exceptional audio quality by means of its built in electret mike. Kit includes case mike on-off switch antenna 110 VAC battery and super instructions. This is the finest unit available

FM-3 Wired and Tested

has added sensitive mike preamp

Universal Timer Kit

Provides the basic parts and PC

board required to provide a source

of precision timing and pulse generation. Uses 555 timer IC and

ncludes a range of parts for most

FM Wireless Mike Kit

Transmits up to 300° to

any FM broadcast ra-dio, uses any type of mike Runs on 3 to 9V

FM-1 kit \$3.95

timing needs

UT-5 Kit

19.95

Type FM-2

\$5 95

MB 1 Kit

FM-2 kit \$4.95

Color Organ

See music come 3 different lights flicker with music One light for, high mid-range and lows. Each indiand vidually adjustable and drives up to 300 W runs on

> Complete kit. ML-1 \$8.95

Video Modulator Kit

Converts any TV to video monitor. Super stable, tunable over ch. 4-6. Runs on 5-15V accepts std video signal. Best uniton the market! Complete kit. VD-1. \$7.95.

Super Sleuth

Led Blinky Kit A great attention get-ter which alternately flashes 2 jumbo LEOs. Use for name badges buttons warning panel lights, anything Runs on 3 to 15 volts Complete kit, BL-1 \$2.95

A super sensitive ampli-fier which will pick up a pin drop at 15 feet Great for monitoring baby's for monitoring baby's room or as general pur-pose amplifier Full 2 W rms output runs on 6 to 15 volts, uses 8-45 ohm speaker Complete kit, BN-9

Runs on 3-12 Vdc 1 wall out. 1 KHZ good for CPO. Alarm. Audio Oscillator Complete kit \$2.95

Whisper Light Kit

An interesting kit, small mike picks up sounds and converts them to light. The louder the sound, the brighter the light The louder the Includes mike, controls up to 300 W, runs on 110 VAC. Complete kit. WL-1

\$6.95

Mad Blaster Kit

Produces LOUD ear shattering and

attention getting siren like sound Can supply up to 15 watts of obnoxious audio Runs on 6-15 VDC

\$4.95

Tone Decoder Tone Decoder
A complete tone decoder on a single PC
board Features 4005000 Hz adjustable
range via 20 turn pot voltage regulation, 567 IC. Useful for touch-tone burst detection, FSK, etc. Can also be used as a stable tone encoder Runs on 5 to 12 v Complete kit. TD-1 \$5.95

Siren Kit

volts

Produces upward and downward wait characteristic of a police siren. 5 W peak audio output, runs on 3-15 volts, uses 3-45 ohm speaker

Complete kit, SM-3

60 Hz Time Base

\$5 50 \$9 95



Call your Phone Order in Today, TERMS: Satisfaction guaranteed or money refunded. C.O.D. add \$2.50. Minimum order \$6.00. Orders under \$10.00 add \$1.50. Add 6% for postage, Insurance, handling. Overseas add 15%. N.Y. residents add 7% tax.

CLOCK KITS

Your old favorites are here again. Over 7,000 Sold to Date. Be one of the gang and order yours today!



Try your hand at building the finest looking clock on the market. Its satin finish anodized aluminum case looks great anywhere, while six .4" LED digits provide a highly readable display. This is a complete kit, no extras needed, and it only takes 1-2 hours to assemble. Your choice of case colors: silver, gold, black (specify).

Clock kit, 12/24 hour, DC-5

Clock with 10 min. ID timer, 12/24 hour. DC-10

\$29.95

For wired and tested clocks add \$10.00 to kit price SPECIFY 12 OR 24 HOUR FORMAT

SATELLITE TV KIT



image rejection, fully tunable audio to recove hidden subcarriers, divide by two PLL demodu-lator for excellent threshold performance, light racking AFC to assure drift free reception, an of course, full 24 channel tunable coverage.

Build your satellite TV system around the R28 close to tenthousand others already have and now it's available in kit form at a new low price. Orde

NEW, LOWER PRICES!

Featured In a Radjo Electronics magazine cover story (May 82), the reliable R28 Satilec TV receiver Is now operating in thousands of locations. The R28 is easy to build, pre-etched, plated boards with screened component layout assures accurate component placement and the critical IF section and local oscillator are pre-assembled and aligned! All parts are included by the R28 attractive case power supply. descriptive operating manual as well as com-plete assembly instructions. Features of the re-ceiver include: dual conversion design for best A complete Satellite TV System requires a dish antenna, LNA flow noise amplifierl, Receiver and Modulator. R2B Receiver Kit \$295.00 R2B Receiver, Wired and Tested \$295.00 RM3 RF Modulator \$199 Prices include domestic UPS shipping and insurance

PARTS PARADE

Audio IC SPECIALS Resistor Ass't Prescaler Crystals PRESCALER Assortment of Popular values Make high resolution audio watt Cut lead for PC mounting. 3 579545 MHZ \$1.50 measurments, great for musical instrument tuning, PL tones, etc. Multiplies audio UP in frequency, selectable x10 or x100, gives 01 leads, bag of 300 or 10 00000 MHZ \$5.00 5 248800 MHZ \$5.00 74S00 7447 7475 7490 74196 \$.40 \$.65 \$.50 \$.50 \$1.35 301 324 380 555 556 565 566 567 741 1458 3900 3914 8038 Switches Mini toggle SPDT Red Pushbuttons N O HZ resolution with 1 sec gate time! High sensitivity of 25 mv. 1 gate AC Adapters AC Adapters Good for clocks nicad chargers, all 110 VAC plug one end 8 5 vdc @ 20 mA \$1.00 16 vac @ 160mA \$2.50 12 vac @ 250mA \$3.00 3/\$1.00 meg input z and built-in filtering gives great performance. Runs on 9V battery, all CMOS Earphones speakers alarm clocks 5 for \$1.00 \$1,00 \$1,25 10/\$2.00 \$.50 \$.50 \$2.95 \$2.95 SPECIAL Mini 8 ohm Speaker Approx 2'- diam Round type for radios mike etc 3 for \$2.00 PS-2 kit PS-2 wired \$29 95 Solid State Buzzers small buzzer 450 Hz 86 dB so output on 5-12 vdc at 10-30 mA compatible 11C90 10116 7208 7207A \$15.00 1.25 30 Watt 2 mtr PWR AMP \$17.50 \$ 5.50 \$21.00 Simple Class C power amp features 8 times power gain, 1 W in Slug Tuned Coils Small 3/16" Hex Slugs turned coil AC Outlet 7216D **CMOS** Panel Mount with Leads 4/\$1.00 \$12.50 \$ 2.95 \$ 2.95 7107C .50 .50 \$1.85 5314 3 turns 10 for \$1.00 5375AB/G 4013 4046 4049 4059 4511 4518 5639 CAPACITORS 7001 PA-1, 30 W pwr amp kit \$ 6.50 TANTALUM Dipped Epory 1.5 UF 25V 3/\$1.00 1.6 UF 25V 3/\$1.00 1.7 UF 25V 3/\$1.00 1.8 UF 25V 3/\$1.00 1.9 UF 15V Radial \$50 1.9 UF 25V 3/\$1.00 1.9 UF 15V Radial 10/\$1.00 OISR CERAMIC 31 16V dish 20/\$1 00 1 16V 15/\$1.00 001 16V 20/\$1 00 00 pF 20/\$1 00 147 16V 20/\$1,00 TR-1, RF sensed T-R relay kit 01 16V disk 1 16V 001 16V 100 pF 047 16V FERRITE BEADS Power Supply Kit \$2.00 MRF-238 transistor as used in PA-1 8-10db gain 150 mhz \$11.95 \$1.35 With info and specs 15/\$1.00 6 Hole Balun Beads 5/\$1.00 DC-DC Converter 5 vdc input prod -9 vdc @ 30ma 9 vdc produces -15 vdc @ 35ma \$1.25 B.W SOLD OUT / kH. B.W SOLD OUT / kH. Sockets 10/\$2.00 RF actuated relay senses RF READOUTS (1W) and closes DPDT relay 14 Pin 10/\$2.00 FNO 359 4" C C FNO 507/510 5"C A MAN 72/HP7730 33"C A HP 7651 43"C A \$1.00 For RF sensed T-R relay 16 Pin Sprague - 3-40 pi Stable Polypropylene .50 ea. Trimmer Cape Sprague - 3-40 pf 24 Pin 28 Pin 40 Pin 4/\$2.00 4/\$2.00 3/\$2.00 TR-1 Kit \$6.95 25K 20 Turn Trim Pot \$1,00 1K 20 Turn Trim Pot \$.50 BI-FET LF 13741 - Direct pin for pin 741 corporation but 500,000 MEG input z, super low 50 pa input current power drain 50 for only \$9,00 for second 10 for \$2,00 Crystal Microphone Diodes Mini RG-174 Coax TRANSISTORS Small 1" diameter %" thick crystal mike cartridge \$.75 5 1 V Zener 1N914 Type 50/\$1.00 1KV 2Amp 8/\$1.00 100V 1Amp 15/\$1.00 10 ft. for \$1.00 2N3904 NPN C-F 2N3906 PNP C-F 2N4403 PNP C-F 2N4410 NPN C-F 2N4916 FET C-F 2N5401 PNP C-F 2N8028 C-F 15/\$1.00 15/\$1.00 15/\$1.00 15/\$1.00 4/\$1.00 5/\$1.00 9 Volt Bettery Clips 5 for \$1.00 78MG \$1.25 \$1.25 Coax Connector Chassis mount BNC type \$1.00 Regulators Nice quality clips %" Rubber Grommets 10 for \$1.00 Connectors 6 pin type gold contacts for mA-1003 car clock module

price

Leds - your choice, please specify
Mini Red, Jumbo Red, High Intensity Red, Illuminator Red 8/\$1
Mini Yellow, Jumbo Yellow, Jumbo Green 6/\$1

Varactors

Motorola MV 2209 30 PF Nominal cap 20-80 PF - Tunable range .50 each or 3/\$1.00

Paris Bag
Asst Of Chokes, disC caps I ant resistors transistors diodes MICA caps etc sm bag (100 pc) \$1,00 lg bag (300 pc) \$2,50



Extend the range of your counter to 600 MHz Works with all counters. Less than 150 my sensitivity specify 10 or -100

Wired, tested, PS-1B \$59.95 Kit, PS-1B \$44.95

for 8 out, 2 Win for 15 out, 4Win for 30 out, Max output of 35 W. incredible value, complete with all parts, less case and T-R relay. \$22.95 6.95

Complete triple regulated

supply provides variable 6 to 18 volts at 200 ma and .5 at 1 Amp Excellent load regulation, good filtering and small size Less transformers, requires 6 3 V 14 1 A and 24 VCT \$6.95 Complete kit. PS-3LT

\$1.00 \$1.00 \$1.25 79MG 723 \$1.15 \$1.00 7915 \$1.25 Shrink Tubing Nubs Mini TO-92 Heat Sinks

Thermalloy Brand To-220 Heat Sinks Nice precut poes of shrink size 1" x %" shrink to % Great for splices 50/\$1.00 Onto Isolators - 4N28 type Opto Reflectors - Photo diode + LED

\$.50 ea. \$1.00 ea.

Molex Pins precut in length of 7 Perfect CDS Photocelle Resistance varies with light, 250 ohms Molex already precut in length of 7 Peril for 14 pin sockets 20 atripe for \$1.00

\$1.50

2N3771 NPN Silicon 2N5179 UHF NPN

2N5179 LIHE NPN Power Tab NPN 40W Power Tab PNP 40W MPF 102/2N5484 NPN 3904 Type T-R PNP 3906 Type T-R

2N2646 LIJT

25 AMP

100V Bridge

\$1.50 each

Mini-Bridge 50V

1 AMP

2 for \$1.00

73 INTERNATIONAL

from page 82

the 60-year mark this year. They are M. W. Coutts of Auckland and W. M. (Soupy) Groves W5NW, whose original US call in 1923 was U5NW, according to the OTC Directory.

Arthur (Jumbo) Godfrey ZL1HV, retiring president of NZART, was made a Life Member of the Association at the Annual Conference at Dunedin. Jumbo was also recently appointed a Director of IARU Region III Association in the place of Tom Clarkson ZL2AZ, who retired from the position

Honors: Tom Clarkson ZL2AZ was hon-

ored by Her Majesty Queen Elizabeth in her New Zealand Birthday Honors List, being awarded the medal of Ordinary Member of the Order of the British Empire (M.B.E.) for his services to amateur radio. Tom has had a long association with ham radio since he was first licensed in 1925; he has been NZART President, an NZART Councillor, a foundation Director of IARU Region III Association, and a Life Member of NZART. The recognition by the Queen in her Birthday Honors is well deserved.

Changes to amateur-radio frequency allocations in ZL from August 1, 1983, have been issued by the regulatory body, the New Zealand Post Office. The main changes are the extension of Grade II licenses and Novice licenses and an extension of the 160-meter band.

Grade II licensees may now operate the 10-meter band between 28 MHz and 29.70 MHz, as well as the other bands previously allocated. The Novice operators have also been allocated a segment of the 10-meter band between 28.10 and 28.60 MHz. The extension of the 160-meter band, which now covers 1800 to 1959 kHz. will be of benefit to Grade I and Grade II operators.

Another change introduced by the NZ Post Office has been the deletion of the Modes of Emission from the Frequency Allocation List. They have placed the responsibility on NZART to set the band plans for each band, based on IARU recommendations, and on all of us to ensure that the mode of emission employed is compatible with other hand users and that the bandwidth of the emission is not excessive and does not interfere with others. The NZART Frequency Management Working Group has produced a draft proposal for the New Zealand band plan which is in line with the modes of emission that are in use now (the time of writing this is July), and basically there are no changes, just a shift of responsibility in the allocation and implementation of the modes of emission

The new 18-MHz and 24-MHz bands are still in the pipeline, but there has been a small change in the 10-MHz band. It is now open from 10.10 to 10.15 MHz for Grade I operators only.

There are many alterations in the VHF and UHF bands; nine new bands are being added above 47 GHz as well as many new segments for the Amateur Satellite Service, which corrects the near-tragic outcome of the 1971 WARC Space Conference when meager provision was made for the Amateur Satellite Service. Provision has also been made for the use of certain bands for international traffic at a time of natural disaster. This is a new provision for many countries as a result of WARC-79 Resolution 640, but it is an amateur-radio function that NZART has always supported.



PANAMA

Miss Dayra Z. Chang HP1AZC Apartado 6-1175 El Dorado Panama, Panama

From L. O. Mathieu HP1ALX: Any radio amateur who visits the city of Panama would be very happy with the courtesy and the friendly treatment that radio amateurs offer in this country.

It can be a great surprise for a visitor to see that such a small city with just a little more than half a million inhabitants has been able to produce many repeaters in order to offer better service and communications to radio amateurs. We have in Panama various organizations of radio amateurs which we should mention. Liga Panamena de Radioaficionados has the leadership in Panama because the majority of radio amateurs throughout the Republic are members. We would also like to mention Radio Club de Panama, another outstanding organization, and also Asociacion de Radioaficionados and Club Experimentadores de Colon. There is another organization that we would like to bring to your attention; it is the Club Geminis de Panama. All of its members are also part of the firefighters division of Panama, and as radio amateurs they have been one of the most outstanding clubs in Panama. Finally, I should mention the Canal Zone Amateur Radio Association an organization that was founded when the United States was administering the Canal Zone territory. Most of the members of this club are US citizens, and it is one of the most active clubs, especially on HF.

With this information, I feel that I have presented a general view of amateur radio in the Republic of Panama, which offers three classes of licenses. Class A is for those radio amateurs who have technical capacity in the electronics field and have passed the correspondent test in addition to the Morse-code and the general-theory exams. Class B is for those who pass only the theory and Morse-code exams. Finally,

AZDEN MINI-PRODUCTS 6,10,15.20M MINI QUAD......129.50 PCS-300 .142-150MHZ 3W 8 MEM.HANDHELD..265.95 HQ-1 PCS-4000 142-150MHZ 25W 16 MEM.MOBILE..265.95 MACO POWER SUPPLIES **BUTTERNUT ANTENNAS** 2006 BAMP SURGE. 6AMP INT., 4AMP CONT..46.00 2010 12AMP SURGE.10AMP INT., 6AMP CONT..55.25 2020 24AMP SURGE.20AMP INT.,12AMP CONT..69.00 2030 36AMP SURGE,30AMP INT.,18AMP CONT.100.00 MFJ PRODUCTS CUSHCRAFT 32-19 144-144MHZ 19 ELEMENT BEAM. ... 88. 41 AV-4 10.15.20,400 TRAP VERTICAL. ... 88. 41 AV-5 10.15.20,400 TRAP VERTICAL. ... 88. 41 AV-5 10.15.20,40,80M TRAP VERTICAL. ... 95. 00 10.3CD 10M 3 ELEMENT SKY WALKER BEAM. 108. 85 15-3CD 15M 4 ELEMENT SKY WALKER BEAM. 108. 85 20-3CD 20M 5 ELEMENT SKY WALKER BEAM. 108. 85 20-3CD 20M 4 ELEMENT SKY WALKER BEAM. 258. 30 40-2CD 40M 2 ELEMENT SKY WALKER BEAM. 272. 00 AMS-147 146-148MHZ HOBILE MAGNET MOUNT. 27. 95 AMS-147 146-148MHZ HOBILE TRUNK MOUNT. 27. 95 AMS-147-2DT 1448-147 MHZ 20 ELEMENT BEAM. ... 44. 25 ARX2B 134-164MHZ RINSO RANGER II. ... 34. 00 ARX4B 134-161 145 MHZ 10 ELEMENT BEAM. ... 44. 25 ARX4B 134-161 145 MHZ 10 ELEMENT BEAM. ... 44. 25 AMS-147-20T 145 MHZ 10 ELEMENT BEAM. ... 44. 25 AMS-148 134-161 145 MHZ 10 ELEMENT BEAM. ... 44. 25 AMS-148 146-148MHZ 14 ELEMENT BEAM. ... 47. 60 CALL FOR PRICES ON OTHER CUSHCRAFT PRODUCTS MIRAGE AMPLIFIERS 2M FM/SSB/CW 2 IN 30 OUT. 2M FM/SSB/CW 10 IN 80 OUT. 2M FM/SSB/CW 10 IN 160 OUT. 2M FM/SSB/CW 30 IN 160 OUT. 2M FM/SSB/CW 30 IN 160 OUT. 1.8-30HHZ SWR/WATT METER. 30-20OHHZ SWR/WATT METER. **TEMPO RADIOS & AMPS DAIWA/MILLER** 2 FOS. HEAVY DUTY COAX SWITCH...19.85 4 PDS. HEAVY DUTY COAX SWITCH...61.25 1.8-60**MAZ SWA/POWER METER...58.95 1.8-150 MHZ SWA/FOWER METER...121.00 140-450**MAZ SWA/FOWER METER...121.00 1.8-150 MHZ SWA/FOWER METER...125.00 **ROTORS & CABLES TEN-TEC** (NEW) TENTEC 2M HANDHELD.......270.00 ARBOSY 10W/1100W SSB/CW 10-B0M W/30M. 510.00 CORSAIR 200W SSB/CW 10-100M W/WARC...999.00 HERCULES 1KW AMP WITH 115/230 VAC P/S.1595.00 **HY-GAIN VOCOM PRODUCTS** WILSON BY MACO FM-2030 143-149MHZ 25W 11 MEMORY......265.95 WV-1A GR-1 **KDK 2 METER RADIOS** 10.15.20M 3 ELEMENT BEAM. 194.00 10.15.20M 6 ELEMENT BEAM. 259.00 40 METER ADD ON FOR ABOVE. 67.95 10-40M TRAP VERTICAL 69.00 GROUND RADIAL KIT FOR WV-1A. 27.00 CALL FOR QUOTES ON OTHER RELATED PRODUCTS Amateur FOB ORIGIN Amateur Equipment, Accessories & Antennas. **Export Anywhere** 2317 Vance Jackson Rd. San Antonio TX 78213 COD Available Hours: 8:30 a.m. to 5:00 p.m. Monday thru Friday (512) 733-0334 9:00 a.m. to 2:00 p.m. Saturday · CST Prices subject to change without notice. (Toll free number 800-531-5405)

ALL ITEMS ARE GUARANTEED OR SALES PRICE REFUNDED. PRICES F.O.B. HOUSTON PRICES SUBJECT TO CHANGE WITHOUT ITEMS SUBJECT TO PRIOR SALE.

MADISON **Electronics Supply**

KENWOOD
TS930S The best in its class
TS430S Survivor of the Armadillo Run
FM43049.00
Filters
We'll install accessories at no charge
and check out the rig.
TS530S 639.00
MC60A
NEW TS780 VHF-UHF TW4000A
FC-10 Controller





ALPHA 76PA \$1690.00
BENCHER ZA1A
ZA2A
TENTEC 2591 Handie Talkie 279.00
Corsair
Argosy
UG17630
831J double female
82-61 N male
Transitraps10% stock
VALOR 1/4 + 5/8 Mag Mount
2M Ant
Single-band coils39.00
JANĚL, WELZ, SHERWOOD, FOX TANGO10% off
DRAKE TR5 599.00
SANTEC ST7T
DRAKE TR5 599.00 SANTEC ST7T 230.00 SIGNAL ONE Milspec 1030 4995.00 AEA MM2 149.00 CK2 129.00
CK2
KT2/KT3 99.00 ea. HAL ST6K 229.00
TOKYO HYPOWER
HC200 Tuner
HC2000 Tuner
HL10160V Amp
HL30160V Amp 249.00 KDK 2030 2MFM 259.00
SANTEC ST144µP 279.00
ST440µP
MAXON 49S
TX FM Headset Vox 39.95 ea.
SHERWOOD/WELZ 10% off list ROCKWELL KWM380 3995.00
COAX SEAL, QSL holder2.00
BENCHER ST2 Chrome single lever45.00
BIRD 43 & elements Stock JERSEY SPECIALTY RG213 . 29¢/ft.
JERSEY SPECIALTY RG213290/ft.
RG8X
450 ohm open wire
VAN GORDON Dogbone insulator 50¢ WORLD RADIO TV handbook17.50
VIBROPLEX 10% off list BELDEN CABLE 9258 RG8x 19¢/ft.
BELDEN CABLE 9258 RG8x 19¢/ft. 8214 RG8 foam
8214 RG8 foam
8237 RG8 36c/ft. 8235 300 Ohm kW twinlead 20c/ft. 8000 14 Ga. stranded ant. 12c/ft. 8267 RG213 49c/ft.
8000 14 Ga. stranded ant 126/ft.
8448 rotorcable 294/IL
9405 heavy rotor cable 49¢/ft.
9888 70¢/ft. PARTS
TCG 2.5A/1000 PIV epoxy diode 196
Sprague 500 pF/30ky
doorknob capacitors16.00 1000pF/500V Feedthru1.95
CDE 001/20kV 1.95
6"x9" copper board 2.00 Resistors 1/4, 1/2, 1, 2 Watt 10c ea. Caps to 1MFD, 100V 25c ea.
Caps to 1MFD, 100V
USED - Subject to prior sale
COLLINS 75A4
75S1 200.00 32S1/AC 350.00 DRAKE TR4C/AC4 395.00
DRAKE TR4C/AC4 395.00
RV4C
RV4C 100.00 ALPHA 374 1200.00 KENWOOD T \$520S (gem) 395.00 REPOWER 1 \$600.00
RF PUWER LADS
A1000, C500X demos 995.00 COLLINS KWS1/75A4 parts Call
75S1/32S1 Parts Call

COMPUTERS

PACKAGES	
#1 AEA CP1, VIC 20 Computer, Kan	tronics
Hamsoft, with cables to fit your radios	325.00
#2 Above Package	
with Kantronics Hamtext	375.00
#3 MFJ 1224, Kantronics Hamsoft, VIC	20
Computer, and cables for your radio	225.00
AEA AMTOR + CW Receive	579.00
IRL FSK500	269.00
FSK 1000/1020A AFSK	575.00
AEA CP1	199.00
KANTRONICS Interface	139.95
MFJ 1224	.79.95
10% off on Software in Stock	

YAESU							4
FT980 Transceiver							0
(Best receiver in HF)				,		,	1299.00
FT77							499.00
FT726R	٠						. 699.00
accessorles in stock FT208RA		٠					. 269.00







FT-757

Available shortly

NEW Medium Price \$829.00 Retail

General coverage receiver, CW filter, AM/FM Module, Microphone, Full break-in CW, Keyer FC 757 Automatic Antenna Tuner FP757 AC Supply

SSTV ROBOT

0011110														
800 (limited)	١													447.00
1200C				ř		r							•	1139.00
450C/800C	ead	ch								,				789.00
400C Kit														
800C Kit					Þ	٠			٠					155.00

DB+Enterprises 2 element QUAD

ANTENNAS

in stock \$275.00
HF6V 125.00
2M CV-539.00
6BTV
G7 144 108.00
TH7DXS 369.00
7-10 Kit
Explorer 14
HD7399.00
Ham4 199.00
B&W AV25 10-80 vert85.00
A3 219.00
A4 289.00
V2S Oscar39.00
435 16TB
144-20T twist
ARX2B38.00
HG52SS Hygain/Telex 52' self supporting

Big LCD Clock

crank-up tower to hold 9.5 sq ft at 50 mph Rotator mount inside top section. Nested ht



GMT/Local twin display. black frame with large. easy-to-read display (.6" high) Batteries included.

\$29.95 - \$1.50 shipping.

HAM TAGS

\$12.95 -\$1.50 shipping.



DON'S CORNER: Our Hurricane Alicia left us with a batch of wet antenna boxes (usable antennas inside). One of the windows blew out right over the antenna department. Take the lowest nationally advertised price you can find, deduct 20%, add suitable shipping or call us with your charge card & we'll check stock for you. Items are subject to prior sale, but we got a bunch of them!

We have a great line-up of repair techs. The crew looks like this:

Tech #1 Kenwood, Icom, Yaesu VHF-UHF + the new digitals

Tech #2 Older tube Kenwoods, Yaesus and older transistor HFs

Tech #3 Drake, C lines, Swan, Galaxy, Tempo

Tech #4 S line and KWM2

Tech #5 KWM 380 and ETO ALPHA

Madisionote: The first Saturday of each month we have a sidewalk sale. Bring your surplus and try to sell it to fellow amateurs.

1508 McKINNEY HOUSTON, TEXAS 77010 *CALL FOR QUOTES 713-658-0268

We stock what we advertise, and much more. **TOLL FREE-ORDERS ONLY** 1-800-231-3057

we have Class C for those who pass only the general-theory exam. This license cannot be renewed and expires after one year. Non-Panamanian citizens also can obtain these licenses if there is mutual agreement between the two countries.

Panama is a country where the radio amateurs are well appreciated because they have always been hard-working people in emergencies and catastrophes of any nature.



POLAND

Jerzy Szymczak 78-200 Bialogard Buczka 2/3, Poland

EQUIPMENT

The rapid development in radio communications makes radios become out of date quickly, and it is difficult to win contests without the latest gear. In countries where there are hundreds of thousands of hams, many manufacturers compete with one another to sell more and more advanced equipment.

But in Poland, where there are only 12,000 or so hams, the situation is quite different. If they have the money, Polish hams buy American or Japanese-made products. But If that is not the case, they construct their transmitters themselves. Individual construction is nearer to the spirit of amateur radio than buying readymade gear; in the past, designing and building stations contributed significantly to the advancement of the state of the art. At any rate, no Polish plant makes radios for hams, and very few amateurs can buy gear from abroad.

So how do they shift for themselves? Radio amateurs belonging to the Polish Scouts Association have some opportunities to obtain gadgets from military stores. Most often, they are given obsolete gear needing repair. Other hams find schematics of transceivers in magazines such as Radio Electrician, and some hams publish their Ideas.

Recently, the bulletin of the PRAA (Polish Radio Amateurs Association) contained details of a 5-band shortwave receiver, a 10-MHz heterodyne receiver, and a frequency synthesizer. In bulletin no. 4, there is a description of a new version of vfo and a mixer. Usually, the lack of parts makes building foreign designs impossible. In technical magazines, one occasionally comes across information on Polish parts. For example, in May it was announced that new 9-MHz SSB filters are being produced. These substitutes for the renowned XF-9B are being made by Omlg. which will also be making PP-9-A1, PP-9-A2, and PP-9-A3 filters.

As you can see, things look rather gloomy, but the Technical Commission of the PRAA has worked out a plan for improvement in the near future. It was decided to put up more measuring laboratories which will enable hams to convert military surplus and test transceivers manufactured in Poland. For example, Zwus will soon be manufacturing an AM heterodyne receiver, a reflectometer, an electronic switch, and the 12 AVQ aerial. The Technical Commission will get professional equipment which is no longer in use and will distribute it to radio amateurs

through the PRAA District Departments. To discover the needs of radio amateurs, two polls were conducted and published in the bulletin of the PRAA. One of the polls referred to the general needs and finances of Polish hams. Every ham in the survey answered questions relative to his wants and needs in components, conductors, cables, sub-assemblies, and test equipment. Additional polls will ask about needs for services, documentation, and technical literature.

The Technical Commission appealed to all radio amateurs for cooperation and asked all industrial electronics plants to begin producing the basic equipment. We hope that as a result of Poland's economic reforms, some plants might say yes.



SWEDEN

Rune Wande SMOCOP Frejavagen 10 S-155 00 Nykvarn, Sweden

SATELLITE-REPEATER COLLISION

The European (Region 1) frequency allocation on 2 meters is 144,0-146.0 MHz. only half of the 2-meter band in America (Region 2). A rapidly-growing ham population using 2-meter repeaters has emphasized the need for more repeater channels.

In Sweden, as well as in the other Reglon 1 countries, there are only 10 repeater channels, designated R0 through R9. Here we usually say only the repeater output frequency, contrary to common US practice to say both the input and output frequencies, e.g., 21/61 for 146.21 in and 146.61 out. Our channel separation is 25 kHz and repeater input is always - 600. Channel R0 is 145.600 and R9 is 145.825. All Japanese 2-meter gear is made in three versions, one for the home market where no repeaters are allowed (yet), one E-version for Europe, with limited frequency coverage but with a 1750-Hz tone oscillator as repeater-opener, and one A-version for America

With the Phase IIIB satellite up and active, severe interference is expected within the repeater coverage for channels R8 and R9, 145.800 and 145.825 MHz respectively.

Solutions

The widely-discussed solution to this problem is to abandon channels R8 and R9. This would mean a remaining maximum of only eight repeaters in a wide area in order not to cause unnecessary interference. Those living in densely-populated areas in the US and elsewhere who can easily access twenty or more repeaters can imagine the problem. There is heavy opposition against moving repeaters 1 MHz lower, i.e., into the 144-MHz band segment, which furthermore is against the Region 1 band plan.

What else? Well, the probable solution will be repeaters on so-called X-channels, i.e., channels split by 12.5-kHz separation. The industry already has European versions of 2-meter equipment capable of this new channel separation. However, interference from repeater channels on both sides is to be expected with existing equipment having a frequency swing designed for 25-kHz separation. In the beginning, repeater traffic on 145.800 and 145.825 MHz will be shared with satellite

traffic, but these two frequencies will probably be abandoned eventually.

QRZ VS. CQ

Or, what's wrong with an old-fashioned CQ call? We sure live in a rapidly changing world. However, sometimes you hesitate and think for a while. Habits change; language changes as well as usage. Dialing across the bands, especially during an SSB contest, gives you a chance to observe the operating techniques used. In such a contest, you more and more often hear "QRZ Contest," and a regular "CQ Contest" is getting rare. According to the Q-code abbreviations, QRZ? means "Who is calling me?" Many of those using QRZ instead of CQ should never get a QSO if the answering station would respect what QRZ? stands for! Is maybe the feeling of being a "big gun" driving us to change old practice? Who will admit that they have to call others? No, probably it is higher status giving the impression that others are always calling them. Would you call this radio-amateur psychology?

DX BULLETIN

SK3SSA is one of many stations transmitting bulletins for radio amateurs in Sweden. This bulletin station is operated by Lars SM3AVQ and transmits in RTTY. There are other SSA bulletin stations on both HF and VHF, on CW, SSB, and FM. Through voluntary efforts by a few dedicated hams in Scandinavia, we can enjoy the superb weekly "DX Bulletin" issued by the Southern New England DX Association. In Denmark, OZ1DJY picks up the RTTY bulletin on 20 meters at midnight local time. During the week, he retransmits it to SM3CFV, who sees to it that the "DX Bulletin" can be added to the domestic "SSA Bulletin" on RTTY each Sunday morning on 80 meters. An excellent service where RTTY is the perfect mode of transmission



WEST GERMANY

Ralf Beyer DJ3NW Opferkamp 14 3300 Braunschweig West Germany

TELEGRAPHY

A lot has been written and said in support of or against CW. But the net outcome is that there is no significant sign of shrinking CW activity, and the CW enthuslasts are getting more organized in order to promote CW. Their arguments are numerous, e.g., better utilization of the frequency spectrum, minimal equipment needs, last chance if everything else fails, and so on. The argument I like best is "CW is fun," and so do many who contribute to the promotion of CW.

Various groups and clubs have been formed in order to support CW. All of them have a common denominator in their bylaws: Telegraphy (CW) is considered the process of mental coding and decoding of Information In Morse code-no machines like keyboards and CW readers are allowed. Assistance is offered to all who are interested in learning the code, and adherence to the recommendations of IARU and the regulations of the respective national radio society is mandatory.

Typical activities of the German "Activity Group Telegraphy-DL" (AGCW-DL),

for example, are rag-chewing, QRP experiments, CW training courses on the air, CW bulletins, contests, awards, and regular meetings. This group has about 1000 members. The individual national AGCWs in Europe are members of the European CW Association (EUCW), a multi-national organization. Everybody interested in the promotion of CW is invited to join the AGCWs, and no particular proficiency level is required. Foreign hams may apply for an associated membership in AGCW-DL, which is free of charge. The point of contact is lise Mueller DL5MAI, Stoffelsberg 3, D-8860 Noerdlingen, Federal Republic of Germany.

The High Speed Club (HSC) founded in 1951 is another CW group. It follows the same fundamental guidelines mentioned earlier but requires some personal achievement in CW by Its members. In order to join HSC, one should be able to complete a CW QSO of 30 minutes duration at 25 wpm with solid copy and excellent keying. Five recommendations by HSC members confirming this achievement and 8 IRCs are all you need to apply for membership. Again, membership is free of charge. Therefore, do not confuse HSC with groups using similar logos and charging annual fees

The HSC is also a member of EUCW and has more than 1100 members in 48 countries. Its club station, DLOHSC, is active on all bands and issues the special DOK number, HSC, for the DLD award. The point of contact is Ernst Manske DL1PM. Ansgarstrasse 14, D-2105 Seevetal 11, Federal Republic of Germany.

"Outrageous" may be your comment regarding a speed of 25 wpm. But there are thousands of hams who communicate regularly at this and even higher speeds comfortably. And there is much more in store. Once you have mastered 40 wpm, you may join the Very High Speed Club (VHSC) administered by PAODIN, D. J. Hoogma, Schoutstraat 15, 6525 XR Nijmegen, The Netherlands. And in case you are looking for further challenges, ask ON5ME about the super and extremely high speed clubs, SHSC and EHSC! In any case, being a high speed fan or not, it is fun to celebrate the art of CW, to promote it by good operating practices, to give a hand to those who want to participate, and eventually to join one of the groups signaling "CW spoken here."



TAIWAN

TIm Chen BV2A/BV2B PO Box 30-547 Taipei, Taiwan Republic of China

FLASH

The Chinese Telecommunications Authority has finally approved the request of Italian hams to operate their rigs and calls followed by BV portable. So far, there is no further information received from the ARI about their boys' departures and arrivals They are required to contact CRA (China Radio Association) for necessary arrangements in this regard.

It has also been learned that permission will be given to a PA ham to be the second operator in the BV2A if he holds a valid and equivalent Ilcense issued by his government to operate on 14 and 21 MHz.



electronics, Inc. KL Full Line Performance

The incredible performance of the World Class KLM 40M-4 is used by many DX ers as a "Standard of Comparison" in Competitive Antenna Equipment.

Obviously, not everyone needs this type of Awesome performance, but its nice to know that the same performance proven design theory and quality construction have been carried over into our full line of quality antennas for all frequency ranges.



Specifications: (2	20M-6)
BÂNDWID IH : 13.9-	4.4 MHz
VSWR:	1.5:1
F/B	35 dB
FEED IMP	50 ohms
ELEMENT LENGTE: .	
BOOM LENGTH:	57 ft
WINDLOAD:	.8 sq. ft
GAIN:	11 dBd

And there's more! See your local dealer or write to KLM, Electronics P.O. Box 816, Morgan Hill, CA 95037.



Specifications: (30N	1-3)
BÂNDWIDTH: 10.1-10.150	MHz
VSWR:	1.5:1
F/B2	
FEED IMP.: 50 ohms u	nbal.
ELEMENT LENGTH:	35'6"
BOOM LENGTH:	
WINDLOAD: 7 s	
GAIN:	0 dB





RTTY LOOP

Marc I. Leavey, M.D. WA3AJR 6 Jenny Lane Pikesville MD 21208

Ever play this game? Take one letter let's say "V". Well, that is either the first few bars of Beethoven's fifth or a common test signal on CW. Two letters? How about those two, back there-CW; or, being involved with radioteletype, we could use its test signal, RY. Three letters? That's easy-FSK. And four letters can be either AFSK or, you asked for it. RTTY! But how about five letters? This month we will take a look at five of the hottest letters to hit RTTY, and they spell AMTOR.

Let's start out by dropping back a bit and examining some of the fundamentals of radioteletype communications. As we have noted before, the commonly used RTTY code is the five-level Murray, sometimes called Baudot, code. Each letter is represented by a unique five-bit code, with most of the codes doubling to represent a figure or punctuation, by use of a shift into a second character set. One of the basic problems with this scheme is that in the world of radio, interference is a given. It is easy to see what would happen to a character code if any of the five bits were randomly changed from mark to space, or vice versa-the resulting character would be incorrect. Now, it might be possible to find or correct the character in plain text copy, using sophisticated computers or a good proofreader; but in code groups, data, or weather reports this would be impossible

Various schemes have been devised to allow for error correction of bit-mangled characters. One technique, used with the American Standard Code for Information Interchange (ASCII), is to add a "parity" bit at the end of the character code. This extra bit is set at either a space (O) or mark (1), determined by the number of marks or spaces within the character code. The end result is to produce either an odd or even number of set (mark) bits. The result is termed odd, or even, parity, respectively.

Used over closed systems, this parity bit gives a remarkable improvement in accuracy. The receiving station is set up to reject any character in which the parity is not correct, and initiate a request for the sending station to repeat the letter or group. Just how this request is accomplished varies with the system, and since we will be getting into a parallel system with AMTOR later, I will not go into computer details here.

The problem with the parity bit is that if multiple bits are messed up, as might well

happen with a noise burst, the computed parity may still be correct. Another, more sensitive, technique for error correction is needed for radioteletype, particularly on high-frequency, noise-prone circuits. Devised for commercial telex circuits, a system for Teleprinter Over Radio (TOR) has been established as an international standard. When adapted for amateur use, this system, which goes by many proprietary names, is called AMTOR. In order to errorproof the system as much as possible, a seven-unit code is used. Rather than depend on one parity bit, however, only combinations of four marks and three spaces are used. Thus, inverting one or more bits is highly unlikely to produce another recognizable (four-mark, three-space) code group. Additionally, code groups should be chosen so that a one-bit change or inversion would not produce a legitimate group. This is analogous to the Gray code, which is a modified binary code which eliminates ambiguity by removing one-bit transitions between digits. Of the total 128 codes available to a seven-bit system (2 to the 7th), there are 35 unique codes which fit the above criteria. Allowing for the fact that a standard Murray teleprinter uses all of the codes available to the fivebit code (2 to the 5th, or 32, characters), it would appear that such a seven-bit code would do nicely.

The resultant code is shown in Fig. 1, comparing the familiar Murray code to the CCIR code used in various TOR circuits. Observant individuals will notice that there are three Control Signal codes given after the 35 noted above, and that these do resemble some other of the codes used for letters. Well, these codes are used in a rather special fashion, which I shall be going into, and are unlikely to be confused with the letter codes when used in that

If all we had right now were the sevenbit codes for each letter, with some means of built-in error correction, that would be nice, but there is more. Imagine two operators talking to each other, using any mode you please, sending traffic. Now these are exceptionally well-trained operators, and at the end of each line of the message the sending station breaks for a confirmation. A quick QSL is issued to confirm receipt of each line, or a SAY AGAIN or IMI (CW for "?") is used to request a repeat of a garbled line. The sending station obeys the receiving station's request 100% of the time, and no errors are ever made in a message again. Of course, if the sending station did not hear the receiving station's answer, he would respond with "WHAT?"; the receiving sta-

etters	Figures	Murray	AMTOR
Α		11000	1110001
B	?	10011	0100111
C	3	01110	1011100
D	\$	10010	1100101
E	3	10000	0110101
F	!	10110	1101100
G	&	01011	1010110
H	stop	00101	1001011
I	8	01100	1011001
J	,	11010	1110100
K	. (11110	0111100
L)	01001	1010011
M		00111	1001110
N	,	00110	1001101
0	9	00011	1000111
P	0	01101	1011010
Q	1	11101	0111010
R	4	01010	1010101
S	bell	10100	1101001
T	5	00001	0010111
U	7	11100	0111001
V	;	01111	0011110
W	; 2	11001	1110010
X	/	10111	0101110
Y	6	10101	1101010
Z	+	10001	1100011
Carria	ge Return	00010	0001111
Line F	eed	01000	0011011
	s Shift	11111	0101101
	s Shift	11011	0110110
Space		00100	0011101
Blank		00000	0101011
Repeat			0110011
Perman		-	1111000
Perman	ent Z (beta)	-	1100110
	l Signal 1	-	1010011
Contro		-	0101011
Contro	l Signal 3	-	1001101
		Fig. 1	

Fig. 1.

tion, presuming he did not get the last block, would send "SAY AGAIN", to which the sending station would respond either 'WHAT??" or "SAY AGAIN WHAT?" and the whole thing would go around again. You get the picture

With people on each end, the whole thing could be resolved with one quick sentence or so. But If we are going to automate this thing, a better form is needed. That is where those Control Signals come in. After some experimentation, it was formulated that the receiving station should respond to each received block with Control Signal 1 (CS1) and CS2 alternately. Thus, receipt of a duplicate Control Signal by the sending station indicates non-receipt. If the sending station does not receive the receiving station's response, it sends a request for signal repetition (RQ) instead of more data. The third Control Signal, CS3, is used to transfer assignation of the sending- and receiving-station status to the other station. In this way, either station can send or receive, alternately, with the other station concurrently confirming receipt.

So what we have at this point is a system which allows the receiving station to tell if the information received is valid. and to automatically request a repeat from the sending station if it is not. But we have done this at the expense, if you will, of two more bits of data to be sent per character. Now, if we are talking about "standard" 60-wpm RTTY, where each data pulse is 21 ms long, this would lengthen each character, now composed of seven data pulses, a start pulse, and a stop pulse, by about 25%, slowing the rate of

transmission to a dismal (in this computer age) 45 wpm. Snore city!

Well, the way to deal with this is by eliminating those start and stop pulses, and speeding the whole thing up anyway so that the error correction becomes less a hindrance, and essentially transparent. Now, let me back up for a bit to explain. Conventional, if I may call it that, RTTY is know as a "start-stop," or asynchronous, system. That means that each character is an entity unto itself, starting and stopping within carefully defined limits. The system may idle for an indeterminate length of time, with a new character arriving at any time, heralded by a start pulse and ending with a stop pulse, which itself merges into the idle state. Contrast that with a synchronous system, where each character is assigned a precise time slot for its existence. By synchronizing clocks at the sending and receiving end, it is nossible to eliminate the start and stop pulses by presuming that a character will be sent during a certain window of time, only. Clearly, loss of synchronization between sending and receiving stations will reduce a signal sent synchronously to garble, but there are ways of minimizing these problems.

So what do we now have? A synchronous, error-correcting way of sending RTTY which can be made to look like Murray, but which can far exceed the older system's reliability. In January we will look into AMTOR some more, and I would appreciate any of you using the technique penning me a note letting me know what you think of it. Next month, our December shopping list, a regular feature of RTTY

MULTI-BAND SLOPERS

160, 80, and 40 meters

Outstanding DX performance of slopers is well known. Now you can enloy 2 or 3 band BIG-SIGNAL reports! Automatic bandswitching · Very
low SWR · Coax feed · 2 kw power · Compact · Ground or 1 ower feed
- Hang from any support 25 ft. high or higher · Easy to install · Very
low profile · Complete instructions · Immediate shipment - Check ok 3 BAND SLOPER: 160, 80, & 40 Meters: 60 ft. long

\$ 43 QO frt ppd 2 BAND SLOPER- 80 & 40 Meters - 41 ft. long \$ 30.00 frt.ppd 3-BAND NO TRAP DIPOLE, 160, 80. 8 40M - 113ft. long \$ 66.00 frt.ppd 2-BAND NO TRAP DIPOLE. 80.8 40M - 84ft. long \$ 49.00 frt.ppd

FOR ADDN'L INFO on these and other unique antennas: send SASE

W9INN ANTENNAS BOX 393-S MT. PROSPECT, IL 60056



Stuck with a problem?

Our TE-12P Encoder might be just the solution to pull you out of a sticky situation. Need a different CTCSS tone for each channel in a multi-channel Public Safety System? How about customer access to multiple repeater sites on the same channel? Or use it to generate any of the twelve tones for EMS use. Also, it can be used to access Amateur repeaters or just as a piece of versatile test equipment. Any of the CTCSS tones may be accessed with the TE-12PA, any of the audible frequencies with the TE-12PB. Just set a dip switch, no test equipment is required. As usual, we're a stickler for 1day delivery with a full 1 year warranty.

- Output level flat to within 1.5db over entire range selected.
- Immune to RF.
- Powered by 6-30vdc, unregulated at 8 ma.
- Low impedance, low distortion, adjustable sinewave output, 5v peak-to-peak.
- Instant start-up.



TE-12PA

67.0 XZ	85.4 YA	103.5 1A	127.3 3A	156.75A	192.8 7A
71.9 XA	88.5 YB	107.2 1B	131.8 3B	162.2 5B	203.5 M1
74.4 WA	91.5 ZZ	110.9 2Z	136.5 4Z	167.9 6Z	
77.0 XB	94.8 ZA	114.8 2A	141.34A	173.8 6A	
79.7 SP	97.4 ZB	118.8 2B	146.2 4B	179.9 6B	
82.5 YZ	100.0 1Z	123.0 3Z	151.4 5Z	186.2 7Z	

- Frequency accuracy, ±.1 Hz maximum -40°C to +85°C
- Frequencies to 250 Hz available on special order.
- Continuous tone

TE-12PB

TEST-TONES:	TOUCH	-TONES:	E	BURST	TONES	3:
600	697	1209	1600	1850	2150	2400
1000	770	1336	1650	1900	2200	2450
1500	852	1477	1700	1950	2250	2500
2175	941	1633	1750	2000	2300	2550
2805			1800	2100	2350	

- Frequency accuracy, ±1 Hz maximum -40°C to +85°C
- Tone length approximately 300 ms. May be lengthened, shortened or eliminated by changing value of resistor


\$89.95



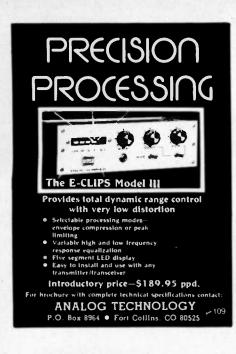426 West Taft Avenue, Orange, California 92667 (800) 854-0547/California: (714) 998-3021







YOU EARNED YOUR CALL!

NOW DISPLAY IT PROUDLY IN A TOP QUALITY

LACOSTE-TYPE KNIT SHIRT.

ONLY \$14.00 With your call in rich embroidery. \$1.50 extra for first name. Choose from 10 great colors: rust, cream, brown, green, yellow, navy, It. blue,

KNAVAS agua, white, and

Adult sizes only S-M-L-XL Club and dealer inquiries invited. Please add \$2.00 for P/H. Make check or money order payable to:

Coin Int'l Inc. 2305 N.W. 107 Ave. Miami, Fl. 33172 -13

Allow 4 weeks for delivery Fl. residents add sales tax

PROPAGATION PREDICTIONS

ON YOUR HOME COMPUTER!

DATE: 15 NOVEMBER 10.7-CM FLUX: 118 FM: W3NIZ MILLERSVL MD TO: COPENHAGEN DENMARK SUNSPOT NR: 68 39-05N 076-37W 55-40N 012-30E DISTANCE: 6476 KM = 4024 MI = 3497 NM BEARING: 042 MUF 19.0 19.3 1200 0100 8.9 8.8 8.7 8.6 0200 1400 19.2 8488 1699 18.2 8.5 1700 0500 15.3 0700 8. 4 1900 11.0 10.4 9900 8.5 2100 13.5 2200

- For VIC-20 (std. or expanded), COMMODORE 64, & PET/CBM
- Cossette or Disk, only \$18.95 ppd.

PROCAST P.O. Box 682, Dept. II Millersville, MD 21108



NEW! HF WATTMETER

- . Digital Resolution (0.1 or 1 Watt)
- Wideband (160 through 10 meters) • Wide range (QRP to 1999 Watts)
- Detachable (RF Sampler un-plugs)
- Battery Saver turns off minutes after RF disappears
- Price includes—Readout, HF Sampler, battery, VSWR nomogram

and complete schematics. • 90 day

warranty

write or call: e-tek P.O. Box 625, Marietta, OH 45750 1-(614)-374-2280

ICOM OWNERS

MAJOR AUDIO BREAKTHROUGH

The ICOM 700 series have MIC pre amps built into their mics. Regular mics can't be used The NEW EQ 200 P EQUALIZER has a pre amp built-in, allowing favorite mics to be used with ICOM. See July 82 QST, CQ. 73 reviews on microphone equalizer

Makes All Mics Sound Great





EQ200P

APPROVED -59 BY ICOM USER'S GROUP

159 95 +\$3. shipping

HEIL, LTD. Marissa, IL 62257 Write For Catalog

(618)295-3000

Subscription Problem?

73 does not keep subscription records on the premises, therefore calling us only adds time and doesn't solve the problem.

Please send a description of the problem and your most recent address label to:

> 73 Amateur Radio's Technical Journal Subscription Dept. PO Box 931 Farmingdale, NY 11737

Thank you and enjoy your subscription.

KSG TECHNOLOGIES High Technology at

Reasonble Prices

Announcing the board all HAMS have awaited:
The KSG TECHNOLOGIES RCW-: RTTY/CW board

Exclusively bullt for the TRS-80° Color Computer using
ABRAMS RTTY/CW SOFTWARE

ABRAMS RTTY/CW SOFTWARE
Adaptable to other computers — write your own software
One 4" x 6" board has all you need for Abrams package:
Active Filter Demodulator (both mark and space)
RTTY APSK modulator
CW Decoder with variable threshold
CW Relay keyer
Regulated on-board supplies for all above functions
Etched and drilled glass epoxy board
Parts easy to find

Parts easy to find Includes instructions, layout, schematic, parts list

For those who bought FACIT 4555 printers from MHZ Electronics and would like to PRINT LOWERCASE LETTERS KSG Technologies' FPM-1 kit is for you:

- Enables the Facit 4555 printer to print lowercase
 96-character ASCII standard (expanded from 64)

96-character ASCII standard (expanded from 64)
Optimized for good recognition
Easy installation in minutes...no traces cut
Complete kit of parts and detailed instructions
90-day written warranty
RCW-1 (Bare Board Only) \$20,00 postpaid
RCW-1K (Board and Parts Kit) \$125.00 postpaid
FPM-1 (Completely Assembled and Tested) \$33.00 postpaid
For additional information write to:

KSG TECHNOLOGIES ~114
900 5TH WAY - PLEASANT GROVE. AL 35127
Check or Money Order Only. No Visa, MasterCard or Phone
Orders Please — Allow three weeks delivery.
TRS-80" is a product of Radio Shack (Tandy Company)

California Antenna Systems Antenna Alternatives for the Radio Amateur

introducing HOT DIPPED GALVANIZED TOWERS TRI-STACK Stacking Towers, 10' to 120' TS10 · 40' side supported package, all hardware complete . \$299. • TRI-TEL Telescoping Crank-up Towers TT237 - 37' self support, 9 sq ft - \$499, * TT354 · 54' self support, 9 sq ft · \$799. • We have a full fine of major brand antennas and accessories. Call for discount price quotes. FREE 2 Meter JAYBEAM -Choice of LW5/2M 5 el. yagi or UGP/2M ground plane with Tower purchase, offer limited. Our way of saying "Thanks"! *Terms: Certified Check or M.O. with order. Prices FOB Shingle Springs, CA 95882: Freight collect: Allow 2 to 6 weeks delivery, Calif. Residents add 6% Tax, Prices subject to change without notice 6020 Windy Ridge Road Shingle Springs. California 95682 Telephone (916) 677-9540

NEW MULTI-CHANNEL **MICROWAVE**

Complete Antenna Systems from \$6995

Full 800 Mhz Range Tune 1.9-2.7 Ghz Includes all **ITFS Channels**

DEALERS WANTED

COD's and Credit Card Orders call TOLL FREE

1-800-247-1151



Glendale, AZ 85301 1-602-247-1151



THE BEST PLACE To Look For New & Used Equipment Buy-Sell-Trade Our 4th Year



NUTS & VOLTS MAGAZINE

PO BOX IIII-G • PLACENTIA, CA 92670 (714) 632-7721 -137

IOIN THOUSANDS OF READERS NATIONWIDE. EVERY MONTH U.S.A. SUBSCRIPTIONS

\$ 7.00 - I YR. 3RD CLASS MAIL \$12.50 - I YR. IST CLASS MAIL \$25.00 - LIFETIME - 3RD CLASS

With Free Classified Ad



HAM & SWL SOFTWARE

Send and receive CW or RTTY with these programs and your TRS-80 Model I or Model III computer, NO HARDWARE OR IS REQUIRED!! All I/O is done via the cassette ports and cable. Results rival hardware/software combinations sold by others. Write or call WD9ECD for details or to order.

- WOODALL SOFTWARE -- 107 P.O. BOX 284 Plainfield, IN 46168

(317) 271-2565 (Eves & Sat)

CIRCUIT BOARD SALE

RS-232C Serial Line Monitor
LED indicators show activity and polarity of the 7 most common signals. DB-25 male and female connectors mount directly on circuit board to form a compact 2" x 3" unit. Mounts in meriem with your RS-232C cable. Kit includes all parts, directions and tips for use. Commercial quality, double sided fiberglas board with plated through holes. Assembled and tested (SLM-1) 29.95 kit (SLM-1X) 21.95 Board only (SLM-1NB) 6.95

Power Supply Board
Provides *5, *12 and -12 volts at 1 amp for your
ham radio project. Uses 78xx series positive
voltage regulators. Needs 2 transformer windings,
18-24 volts (1 center tapped). 3.58" x 4.58"
Assembled and Tested (PS-1). 16.95
Board only (PS-1NB) 16.95

Please add \$2.00 per order shipping and handling. CA residents include tax.

Esoteric Engineering Incorporated PO Box 33692, San Diego, CA 92193 (619) 569-7868

PRESERVE

73 with



BINDERS & FILE CASES.

Keep your issues of 73 Magozine handy and protected in handsome and durable library file boxes or binders. Both styles are bound in red leatherette with the magazine logo stamped in gold.

File boxes: each file box holds 12 issues, with spines visible for easy reference.

\$5.95 each, 3 for \$17.00, 6 for \$30.00 Binders: each hinder holds 12 issues and opens flat for easy reading.

\$7.50 each, 3 for \$21.75, 6 for \$42.00 (USA postage paid. Foreign orders must include \$2.50 per item.)

Please state years desired (1977 to 1984).

Send check or money order to:

Jesse Jones Box Corp., P.O. Box 5120, Philadelphia, PA 19141; please allow 6 to 8 weeks for delivery. Sorry, no C.O.D. or phone orders.

BUY! SELL! TRADE!

COMPUTER & HAM EQUIPMENT

COMPUTER®

TRADER

ANNUAL SUBSCRIPTION \$15.00

Low Ad Rates — Mailed Monthly Foreign Subscriptions - \$30.00 Year FREE 50 Word Classified Ad with Subscription Order **COMPUTER TRADER•**

Chet Lambert, W4WDR 1704 Sam Drive • Birmingham, AL 35235 (205) 854-0271

Sample Copy — \$1.00

WARC for FT-101

Modernize any model of the original FT-101 Series by adding all three WARC bands for RX and TX!

- · Use 10 MHz now; be ready for the others.
- · Increase resale value of your rig.
- Easy installation, detailed instructions.
- · Includes all crystals, relays, etc.

· Tested, fool-proof design for all but 'ZD. FT-101 WARC Kit #4N ONLY \$25. Shipping \$3 (Air \$5). Florida sales tax 5%.

GO FOX TANGO - TO BE SURE!



Order by Mail or Telephone

For other great Yaesu modifications get the top-rated FT Newsletter. Still only \$8 per calendar year (US), \$9 Canada, \$12 Overseas.

FOX TANGO CORPORATION Box 15944 S, W. Palm Beach, FL 33416 (305) 683-9587 295

AZDEN PCS-4000

2 METER TRANSCEIVER AND PCS-300 2M TALKIE

We'll Beat Any Price in This Issue

10 AMP Regulated Supply 10 AMP Continuous \$52

Service Manuals

PCS 4000 \$900

300-3000 \$500 EACH

Order 24 hours a day (215) 884-6010 N.P.S. Inc. WA3IFQ 1138 BOXWOOD RD. JENKINTOWN, PA. 19046

CABLE CONVERTER SALE

MAGNAVOX FV-25 - 26 CHANNEL WITH REMOTE CONTROL - VHF-MIDBAND-SUPERBAND - REG #59,95 - NOW

JERROLD JSX-3DIC - 36 CHANNEL MITH IN BAND GATED SYNC DECODER - REG 6209.95 - NOW \$149.95

JERROLD SB-3 - IN BAND GATED GATED SYNC DECODER - USE WITH ANY CONVERTER WITH DUTPUT ON CHANNEL 3 - REG \$149.95 - NOW \$99.95

UHF BLOCK CONVERTER - CONVERTS MIDBAND AND SUPERBAND TO UHF - REG \$39.95 - NOW

SEND \$1.00 (REFUNDABLE) FOR CATALOG

ADD 44.25 SHIPPING/HANDI ING FOR EACH UNIT ORDERED

NYS ADD SALES TAX -C.O.D.'S OK

24 HOUR ORDER LINE (607) 962-7313

ORDER DIRECT FROM -

TAYCO COMMUNICATIONS R3-146A NARROWS CREEK ROAD CORNING, NEW YORK 14830 - 183

UHF POWER AMP

AM-6155/GRT (ITT 3212) 225-400 Mhz RF amp.



50W output from 4-10W input using Eimac X651Z; silver-plated cavity in removable drawer, Requires 115/ 230 VAC & 20 VDC. 7x191/2x18", 75 lbs.

sh. Used-not tested, excellent condition: \$149.50

R-392 RECEIVER, 0.5-32 Mhz AM-CW in 32 bands; mechanical digital tuning. 2-4-8 Khz bandwidth; 100 Khz calibrator. 25 tubes; requires 24 VDC 5 amps. 11/2x14/2x11", 60 lbs. sh. Used-reparable, \$135. Chkd., \$200. Manual, partial repro: \$15. LS-166 speaker, \$10.95. 24 VDC 6 AMP Supply for 8-392—no conpector us Supply, for R-392 - no connector, used:



TEKTRONIX 516 DUAL TRACE SCOPE, DC-15 Mhz response with 5" CRT. Sensitivity 0.05-20 v/div Mhz response with 5" CRI. Sensitivity 0.05-20 v/div and Sweep 0.2 usec-2 sec/div calibrated; Square-wave Calibrator 0.05-100 volts. Requires 115 VAC 60 Hz. 13½x9¾x21½", 50 ibs. sh. Used-reparable \$165. Checked \$225. Prices F.O.B. Lima, 0. • VISA, MASTERCARD Accepted, Allow for Shipping • Send for New FREE CATALOG '83 Address Dept. 73 • Phone: 419/227-6573

FAIR RADIO SALES -22 1016 E. EUREKA · Box 1105 · LIMA, OHIO · 45802

RECEIVING CONVERTERS TRANSMIT CONVERTERS **NEW LOW-NOISE PREAMPS**

New low-noise microwave transistors make preamps in the 0.9 to 1.0 dB noise figure range possible without the fragility and power supply problems of gas-fet's. Units furnished wired and tuned to ham band. Can be easily retuned to nearby freq.



Models LNA(), P30, and P432

Model	Tunable Freq Range	Noise Figure	Gain	Price
LNA 28	20-40	0.9 dB	20 dB	\$39.95
LNA 50	40-70	0.9 dB	20 dB	\$39.95
LNA 144	120-180	1.0 dB	18 dB	\$39.95
LNA 220	180-250	1.0 dB	17 dB	\$39.95
LNA 432	380-470	1.0 dB	18 dB	\$44.95

ECONOMY PREAMPS

Our traditional preamps, proven in years of service. Over 20,000 in use throughout the world. Tuneable over narrow range. Specify exact freq. band needed. Gain 16-20 dB. NF = 2 dB or less. VHF units available 27 to 300 MHz. UHF units available 300 to 650 MHz.

 P30K, VHF Kit less case 	\$14.95
 P30C, VHF Kit with case 	\$20.95
 P30W, VHF Wired/Tested 	\$29.95
 P432K, UHF Kit less case 	\$18.95
 P432C, UHF Kit with case 	\$24.95
 P432W, UHF Wired/Tested 	\$33.95

P432 also available in broadband version to cover 20-650 MHz without tuning. Same price as P432; add "B" to model #.

HELICAL RESONATOR PREAMPS



Our lab has developed a new line of low-noise receiver preamps with helical resonator filters built in. The combination of a low noise amplifier similar to the LNA series and the sharp selectivity of a 3 or 4 section helical resonator provides Increased sensitivity while reducing intermod and cross-band interference in critical applications. See selectivity curves at right. Noise figure = 1 to 1.2 dB. Gain = 12 to 15 dB.

Model	Tuning Range	Price
HRA-144	143-150 MHz	\$49.95
HRA-220	213-233 MHz	\$49.95
HRA-432	420-450 MHz	\$59.95



Models to cover every practical rf & if range to listen to SSB, FM, ATV, etc. NF = 2 dB or less.

VHF MODELS	Antenna Input Range	Receiver Output		
	28-32	144-148		
VIII WODELS	50-52	28-30		
Kit \$44.95 Less Case \$39.95 Wired \$59.95	50-54	144-148		
	144-146	28-30		
	145-147	28-30		
	144-144.4	27-27.4		
	146-148	28-30		
	144-148	50-54		
	220-222	28-30		
	220-224	144-148		
	222-226	144-148		
	220-224	50-54		
	222-224	28-30		
UHF MODELS	432-434	28-30		
Kit \$54.95 Less Case \$49.95	435-437	28-30		
	432-436	144-148		
	432-436	50-54		
Wired \$74.95	439.25	61.25		

SCANNER CONVERTERS Copy 72-76, 135-144, 240-270, 400-420, or 806-894 MHz bands on any scanner. Wired/tested Only \$79.95.

SPECIAL FREQUENCY CONVERTERS made to custom order \$119.95. Call for details.

SAVE A BUNDLE ON **VHF FM TRANSCEIVERS!**

FM-5 PC Board Kit - ONLY \$159.95 complete with controls, heatsink, etc. 10 Watts, 5 Channels, for 6M, 2M, or 220



with speaker, knobs, connectors, hardware. Only \$59.95

REPEAT OF A SELLOUT!

While supply lasts, get \$59.95 cabinet kit free when you buy an FM-5 Transceiver kit.

Where else can you get a complete transceiver for only \$159.95?


For SSB, CW, ATV, FM, etc. Why pay big bucks for a multi mode rig for each band? Can be linked with receive converters for transceive. 2 watts output.

	Exciter Input Range	Antenna Output
For VHF, Model XV2 Kit \$79.95 Wired \$119.95 (Specify band)	28-30 28-29 28-30 27-27-4 28-30 50-54 144-146 50-54 144-146	144-146 145-146 50-52 144-144.4 220-222* 220-224 50-52 144-148 28-30
For UHF, Model XV4 Kit \$99.95 Wired \$149.95	28-30 28-30 50-54 61.25 144-148 *Add \$20 fo	432-434 435-437 432-436 439.25 432-436° or 2M input




VHF & UHF LINEAR AMPLIFIERS. Use with above. Power levels from 10 to 45 Watts. Kits from \$69.95.

LOOK AT THESE ATTRACTIVE CURVES!

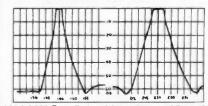


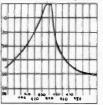R144 & R220 Front Ends. HRA 144/220, & HRF-144/220



R451 Receiver Front End

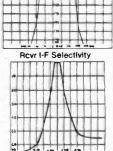Typical Selectivity Curves Helical Resonators.



HRA-432, HRF-432

 Call or Write for FREE CATALOG (Send \$1.00 or 4 IRC'c for overseas mailing)

Order by phone or mail • Add \$2 S & H per order (Electronic answering service evenings & weekends) Use VISA, MASTERCARD, Check, or UPS COD.

hamlronics, inc.

65-X MOUL RD. ● HILTON NY 14468 Phone: 716-392-9430

Hamtronics is a registered trademark

For years, Hamtronics **
Modules have been used by individual hams and manufacturers to make repeaters. Now, in the Hamtronics tradition of top quality and superb value, we are proud to offer a complete repeater package.



JUST LOOK AT THESE PRICES!

Band	Kit	Wired/Tested
6M,2M,220	\$595	\$745
440	\$645	\$795

Both kit and wired units are complete with all parts, modules, hardware, and crystals.

CALL OR WRITE FOR COMPLETE DETAILS.


Also available for remote site linking/crossband & 10M.

FEATURES:

- SENSITIVITY SECOND TO NONE; TYPICALLY 0.15 uV ON VHF, 0.3 uV ON UHF.
- SELECTIVITY THAT CAN'T BE BEAT! BOTH 8 POLE CRYSTAL FILTER & CERAMIC FILTER FOR GREATER THAN 100 dB AT ± 12KHZ. HELICAL RESONATOR FRONT ENDS. SEE R144, R220, AND R451 SPECS IN RECEIVER AD BELOW.
- OTHER GREAT RECEIVER FEATURES: FLUTTER-PROOF SQUELCH, AFC TO COMPENSATE FOR OFF-FREQ TRANSMITTERS, SEPARATE LOCAL SPEAKER AMPLIFIER & CONTROL.
- CLEAN, EASY-TUNE TRANSMITTER; UP TO 20 WATTS OUT.

HIGH QUALITY MODULES FOR REPEATERS, LINKS, TELEMETRY, ETC.

INTRODUCING — NEW 1983 RECEIVERS

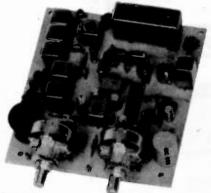

- R144 Shown
- R144/R220 FM RCVRS for 2M or 220 MHz. 0.15uV sens.; 8 pole xtal filter & ceramic filter in i-f, helical resonator front end for exceptional selectivity (curves at left). AFC incl., xtal oven avail. Kit only \$119.95
- R451 FM RCVR Same but for uhf. Tuned line front end, 0.3 uV sens. Kit only \$119.95.
- R76 FM RCVR for 10M, 6M, 2M, 220, or commercial bands. As above, but w/o AFC or hel. res. Kits only \$109.95.
 Also avall w/4 pole filter, only \$94.95/ kit.
- R1.10 VHF AM RECEIVER kit for VHF aircraft band or ham bands. Only \$84.95
- R110 UHF AM RECEIVER for UHF uses, including special 259 MHz model to hear SPACE SHUTTLE. Kit \$94.95





 HELICAL RESONATOR FILTERS available separately on pcb w/connectors.

HRF-144 for 143-150 MHz \$34.95 HRF-220 for 213-233 MHz \$34.95 HRF-432 for 420-450 MHz \$44.95

(See selectivity curves at left.)



- CQR KITS With audio mixer and speaker amplifier. Only \$29.95.
- CWID KITS 158 bits, field programmable, clean audio. Only \$59.95.
- DTMF DECODER/CONTROLLER KITS. Control 2 separate on/off functions with touchtones⁶, e.g., repeater and autopatch. Use with main or aux. receiver or with Autopatch. Only \$89.95.
- AUTOPATCH KITS. Provide repeater autopatch, reverse patch, phone line remote control of repeater, secondary control via repeater receiver. Many other features. Only \$89.95. Requires DTMF Module.
- A16 RFTIGHT BOX Deep drawn alum. case with tight cover and no seams. 7 x 8 x 2 Inches. Only \$18.00.

TRANSMITTERS AND ACCESSORIES



 T51 VHF FM EXCITER for 10M, 6M, 2M, 220 MHz or adjacent bands. 2 Watts confinuous. Kits only \$59.95



- T451 UHF FM EXCITER 2 to 3 Watts on 450 ham band or adjacent. Kits only \$69.95.
- VHF & UHF LINEAR AMPLIFIERS. Use on either FM or SSB. Power levels from 10 to 45 Watts to go with exciters & xmtg converters. Kits from \$69.95.



POPULAR VALUES FROM SPECTRONICS!



AM/FM/AIR/PSB/2 METERS!

THE NEW PANASONIC RF-1405 HAS IT ALL!

> Portability and practicality are built right in to this newest Panasonic receiver. not to mention LOW PRICE!

- * AC/DC power
- * AM 525-1610 KHz.
- * FM 88-108 MHz.
- * AIR 108-136 MHz
- * PSB 136-174 MHz.



FM Transmitting

Valuable aid for Amateur use in antenna installation. tuning/pruning, field day etc., plus hundreds of applications in home business, sports and recreation. Uses 9 volt battery (not supplied.)

Put Your Computer "On-The-Air"

The Interface™

\$149.95 1 ict \$189.95

Plus \$3.DD Shipping



Your personal computer becomes a complete CW/RTTY/ASCII send and receive terminal with The Interface linking it to your trans-

If you own an Apple II or Apple II Plus, Atari 400 or 800, TRS-80 Color Computer, or VIC-20, The Interface will put your computer "On-

Software for each system features split screen display, buffered keyboard, status display, and message ports. Attach any Centronics compatible printer for hard copy. Software is available, on diskette

for the Apple and program boards for the others, at additional cost. TI-99 Apple Atari VIC-20 TRS-80C VIC-20 Commodore 64 diskette

board board board Hamtext board Hamtext \$29.95 \$49.95 \$59.95 \$49 95 \$99.95 \$99.95 599 95

43 23

.7" Red LED Numerals \$ 1995 • 24-Hr. Memory Alarm • 1-Year Warrantee

- - · Drowse Control . Dark Brown Walnut Grain

KEN-TEC

24-HOUR DIGITAL

ALARM CLOCK

MILITARY TIME

. 24 "H x 64"W x 34 "D

ICOM HEADQUARTERS



PLUS \$1.50 UPS

CALLBOOK-COMM

AD.

d

4

BENCHER

BEARCAT

BASH

PMECO

Pues

PVRATTI - ARRL

BATERN

ICOM IC2A IC2AT



- Compact
- Compact

 Ouality
 Construction

 Versatile

 Affordable

 Wide Range of
 Accessories
 Available Available

CALL FOR PRICE & AVAILABILITY

SUB-AUDIBLE TONE **HEADQUARTERS**

ENCODERS DIUS \$2.00 \$2995 Shipping We stock Communication Specialists SS 32 and SS-32M encoders for most any mobile or hand-held applications includ ing the very popular Icom

"easy-talk'r" VOX PORTABLE TRANSCEIVER

"Hands free" VOX operation Light weight—less than 9 Oz

BAW PORTABLE APARTMENT ANTENNA



Quick easy mounting. Tunes 2: 8: 10. 15: 20 and 40 meter. Amateur balliots 50 BCD bands in some langes 3: 60 watts SSBICW 22½ while extends to 57: 14 mount includes 5 base-toading coles. Weighs less than 2: tos.

AMECO PREAMPS add \$3.00

(Cont'l USA only)

Model PLF-2E (240V) \$57.95 Model PT-2F (240V)

FAMOUS "FAVESDROPPER SW RECEIVING ANTENNA



plus \$3,00 \$5995 shipping (Cont'l U.S.)

REPLACEMENT NICAD FOR WILSON/YAESU



玉

PROS.

TELEX - TEN TEC - TRAC - TRANSCOM

•

VAN GOADON -



MORGAIN MULTI-BAND ANTENNAS



Add \$5.00 for shipping (Cont'l U.S.A.)

80-40HD/A 80/40 Mtr bands (69) 75/40HD/A 75/40 Mtr bands (66) 99.00 75-10HD/A 75/40/20/15/10 Mtr (66). 94.50 80-10HD/A 80/40/20/15/10 Mtr (69).

FAMOUS AVANTI THRU-GLASS MOBILE ANTENNA



The Avanti On-Glass is the first twoinications antenna that \$3295

\$3.00 Shipping

ounts on glass and transmits and receives through the glass Ex-tremely low VSWR is achieved by adjusting special tuning slug on matching network inside the vehicle Can be easily removed for car washes without special tools

NEWI 2.8 dbd GAIN **BASE ANTENNA**

\$1500 Please add 2 00 shipping

Here's an inexpensive omni-directional, 144-148 MHz. ½ wave antenna. Fits 1¼'' mast, 50 ohm impedance. A real problem solver

Y VALUES!



- . 6-band pocket world receiver-SW 1-5, plus MW
- Extremely compact and lightweight-palm sized!
- · SW band spread dial-easy tuning · Tuning indicator

9-BAND ICF-7600A \$109.95

plus \$2.00 UPS

TO ORDER:

CALL OR WRITE. MASTER CARD, VISA, MONEY ORDERS, PERSONAL CHECKS TAKE 3 WEEKS TO CLEAR, ACCEPTED, INTERNATIONAL ORDERS WELCOME, PLEASE REQUEST PRO FORMA INVOICE. ILLINOIS RESIDENTS ADD 6% SALES TAX.

HOURS: MON. THRU WED. 9:30-6:00. THURS-FRI. 9:30-8:00, SAT. 9:30-3:00

STOP BY AND VISIT WHEN IN THE CHICAGOLAND AREA!!

OAK PARK, IL. 60304



1009 GARFIELD ST.

PHONE

the first name in Counters! 9 DIGITS 600 MHz



PRICES
CT-90 wired. I year warranty
CT-90 Kit, 90 day parts war-109.95 12.95

The CT-90 is the most versatile, feature packed counter available for less than \$300.00! Advanced design features include, three selectable gate times, nine digits, gate indicator and a unique display hold function which holds the displayed count after the input signal is removed Also, a 10mHz TCXO time base is used which enables easy zero beat calibration checks against WWV. Optionally, an internal nicad battery pack, external time base input and Micropower high stability crystal oven time base are available. The CT-90, performance you can count on!

SPECIFICATIONS:

Range: 20 Hz to 600 MHz Sensitivity

Less than 10 MV to 150 MHz Less than 50 MV to 500 MHz 0.1 Hz (10 MHz range) Resolution

1.0 Hz (60 MHz range) 10.0 Hz (600 MHz range)

Display:

Standard-10.000 mHz, 1.0 ppm 20-40°C. Optional Micro-power oven-0.1 ppm 20-40°C

8-15 VAC @ 250 ma

ranty

7 DIGITS 525 MHz \$99.55



20 Hz to 525 MHz Range Sensitivity: Less than 50 MV to 150 MHz Less than 150 MV to 500 MHz

1.0 Hz (5 MHz range) Resolution 10.0 Hz (50 MHz range) 100.0 Hz (500 MHz range)

7 digits 0.4" LED Display 1.0 ppm TCXO 20-40°C 12 VAC @ 250 ma Time base Power.

The CT-70 breaks the price barrier on lab quality frequency counters. Deluxe features such as, three frequency ranges - each with pre-amplification, dual selectable gate times, and gate activity indication make measurements a snap. The wide frequency range enables you to accurately measure signals from audio thru UHF with 1.0 ppm accuracy - that's .0001%! The CT-70 is the answer to all your measurement needs, in the field, lab or ham shack.



WIRED

CT-70 wired, 1 year warranty \$99.95

84.95

12.95

CT-70 Kit, 90 day parts war

BP-1 Nicad pack + AC adapter/charger

AC-1 AC adapter

DIGITS 500 MHz \$79 95 WIRED

adapter/charger

MINI-100 wired, 1 year \$70 05 warranty AC-Z Ac adapter for MINI-BP-Z Nicad pack and AC

Here's a handy, general purpose counter that provides most counter functions at an unbelievable price. The MINI-100 doesn't have the full frequency range or input impedance qualities found in higher price units, but for basic RF signal measurements, it can't be beat' Accurate measurements can be made from 1 MHz all the way up to 500 MHz with excellent sensitivity throughout the range, and the two gate times let you select the resolution desired. Add the nicad pack option and the MINI-100 makes an ideal addition to your tool hox for "in the field" frequency checks and repairs.

SPECIFICATIONS:

1 MHz to 500 MHz Sensitivity: Less than 25 MV Resolution 100 Hz (slow gate) 1.0 KHz (fast gate) Display: 7 digits, 0.4" LED 2.0 ppm 20-40°C 5 VDC @ 200 ma

8 DIGITS 600 MHz \$159 % WIRED



SPECIFICATIONS:

1295

Range: Sensitivity: 20 Hz to 600 MHz

Resolution

10.0 Hz (600 MHz range) 8 digits 0.4" LED Display: 2.0 ppm 20-40°C 110 VAC or 12 VDC

Time base

switched on or off. The CT-50, a counter that can work double-duty!

The CT-50 is a versatile lab bench counter that will measure up to 600 MHz Less than 25 my to 150 MHz with 8 digit precision. And, one of its best features is the Receive Frequency Less than 150 my to 600 MHz Adapter, which turns the CT-50 into a digital readout for any receiver. The with 8 digit precision. And, one of its best features is the Receive Frequency adapter is easily programmed for any receiver and a simple connection to the receiver's VFO is all that is required for use. Adding the receiver adapter in no way limits the operation of the CT-50, the adapter can be conveniently

PRICES:

\$159.95 CT-50 wired, I year warranty CT-50 Kit, 90 day parts warranty RA-1, receiver adapter kit

RA-1 wired and pre-programmed (send copy of receiver

29.95



DIGITAL MULTIMETER \$99 % WIRED

DM-700 wired, I year warranty \$00.05 DM-700 Kit, 90 day parts warranty AC-1, AC adaptor 3.95 BP-3. Nicad pack +AC adapter/charger MP-1, Probe kit

The DM-700 offers professional quality performance at a hobbyist price. Features include: 26 different ranges and 5 functions, all arranged in a convenient, easy to use format. Measurements are displayed on a large 31/2 digit, 1/2 inch LED readout with automatic decimal placement, automatic polarity, overrange indication and overload protection up to 1250 volts on all ranges, making it virtually goof-proof! The DM-700 looks great, a handsome, jet black, rugged ABS case with convenient retractable tilt bail makes it an Ideal addition to any shop.

SPECIFICATIONS:

DC/AC volts: 100 uV to 1 KV, 5 ranges

DC/AC

Power.

0.1 uA to 2.0 Amps, 5 ranges current 0.1 ohms to 20 Megohms, 6 ranges Resistance Input

10 Megohms, DC/AC volts impedance 0.1% basic DC volts Accuracy 4 'C' cells

AUDIO SCALER

For high resolution audio measurements, multiplies UP in frequency.

• Great for PL tones

Multiplies by 10 or 100

• 0.01 Hz resolution \$29.95 Kit \$39.95 Wired

ACCESSORIES

High impedance probe, light loading. 15.95 Low pass probe, for audio measurements Direct probe, general purpose usage Tilt bail, for CT 70, 90, MINI-100. 12.95 Color burst calibration unit, calibrates counter against color TV signal.

COUNTER PREAMP

For measuring extremely weak signals from 10 to 1,000 MHz. Small size, powered by plug transformer-included:

Flat 25 db gain
BNC Connectors

• Great for sniffing RF with pick-up loop \$34.95 Kit \$44.95 Wired

ramsey electronic's, inc. 2575 Baird Rd. Penfield, NY 14526 - 62





PHONE ORDERS CALL 716-586-3950 TERMS Satisfaction guaranteed. Examine for 10 days, if not pleased return in original form for retund. Add 5% for shipping insurance to a maximum of \$10. Overseas add 15% COD add \$2. Orders under \$10 add \$1.50. NY residents add 7% tax

DEALER DIRECTORY

Culver City CA

Jun's Electronics, 3919 Sepulveda Bivd., Culver City CA 90230, 390-8003. Trades 463-1886 San Diego, 827-5732 (Reno NV).

Fontana CA

Complete lines ICOM, DenTron, Ten-Tec, Mirage, Cubic, Lunar, over 4000 electronic products for hobbyist, technician, experimenter. Also CB radio, landmobile. Fontana Electronics, 8628 Sierra Ave., Fontana CA 92335, 822-7710.

San Jose CA

Bay area's newest Amateur Radio store. New & used Amateur Radio sales & service. We feature Kenwood, ICOM, Azden, Yaesu, Ten-Tec, Santee & many more. Shaver Radio, Inc., 1378 So. Bascom Ave., San Jose CA 95128, 998-1103.

New Castle DE

Factory Authorized Dealerl Yaesu, ICOM, Ten-Tec, KDK, Azden, AEA, Kantronics, Santec. Full Line of Accessories. No Sales Tax in Delaware. One mile off 1-95. Delaware Amateur Supply, 71 Meadow Road, New Castle DE 19720, 328-7728.

Boise, ID

Rocky Mountain area's newest ham dealer. Call RJM first for AEA, Azden, KDK, Ten-Tec, Butternut, Cushcraft, and morel RJM Electronics, 4202 Overland, Boise, ID 83705, 343-4018.

Preston ID

Ross WB7BYZ has the Largest Stock of Amateur Gear in the Intermountain West and the Best Prices. Call me for all your ham needs. Ross Distributing, 78 So. State, Preston ID 83263, 852-0830.

Ann Arbor MI

See us for products like Ten:Tec, R. L. Drake, Dentron and many more. Open Monday through Saturday, 0830 to 1730. WBBVGR, WBBUXO, WDBOKN and WBRP behind the counter. Purchase Radio Supply, 327 E. Hoover Ave., Ann Arbor MI 48104, 668-8696.

Hudson, NH

Look!—Hams, SWLs, and Experimenters: Parts, Books, Gear, Antennas, Towers. Call for quotes. Polean's ELECTRONICS CENTER, 61 Lowell Road (Route 3A), Hudson, NH 03051, 883-5005.

Albany, New York UPSTATE NEW YORK

KENWOOD, ICOM, TEN-TEC, Belden, Cushcraft, Larsen, Hustler, ARRL, Hy-Gain, B&W, MFJ, Mirage. New and Used equipment. Serving the amateur community since 1942, Adirondack Electronics, Inc., 1991 Central Avenue, Albany, New York 12205, 456-0203 (One mile West of Northway exit 2W).

Columbus OH

The biggest and best Ham Store in the midwest featuring Kenwood and other quality products with working displays. We sell only the best. Authorized Kenwood Service. Universal Amateur Radio Inc., 1280 Aida Dr., Reynoldsburg (Columbus) OH 43068, 966-4267.

Stigler, OK

T199/4-4A Basic, Extended Basic, Assembly Language Programs. CW Transceive, CW Practice, DX, 1010, WAS, SSTV, Hamkid's Programs. ACSD Computer Programs, Box 368, Stigler, OK 74462 967-2034.

Scranton PA

ICOM, Bird, Cushcraft, Beckman, Fluke, Larsen, Hustler, Antenna Specialists, Astron, Avanti, Beiden, W2AU/W2VS, AEA, Vibroplex, HamKey, Amphenol, Sony, B&W, Coax-Seal, Cover Craft, J.W. Müller/Diswa, ARRL, Ameco, Shure, LaRue Electronics, 1112 Grandview St., Scranton PA 18509, 343-2124.

Mountaintop PA WILKES-BARRE AREA

WILKES-BARRE AREA
VHF/UHF Equipment & Supplies—From HT's
to kW Amplifiers, Transverters, VHF/UHF
Microwave Linear Amplifiers, GaAsFET
Preamps, OSCAR Equipment, Low Noise
preamps, Antennas, Power Supplies. From:
ICOM, Lunar, Microwave Modules, UHF
Units/Parabolic, Mutek, SSB Electronics, ARCOS, Astron, F9FT-Tonna, Tama, KLM,
Mirage, Santec, Tokyo Hy-Power, Two stamps
for catalog. The VHF SHOP, Dept. S, RD4, Box
349, Mountaintop PA 18707, 868-6565.

Dallas TX

IBM PC/Apple aftermarket products; hobbyists' electronics project list: \$50.00 complete modern list; subscription/satellite TV decoder lists, EPROM programmer/duplicator, popular memory IC testers, data sheets, application notes, and more than 6000 parts in stock. Semiconductors, discretes, video products, tools. .. Please write for your free literature/catalog. Independent Electronics, 6415-66 Airline Rd., Dallas TX 75205.

Baltimore/Washington

Avantek transistors, amplifiers, oscillators and LNAs. Coaxial cable and connectors. Blonder Tongue dealer with Microwave laboratory. Applied Specialties, Inc., 10101G Bacon Drive, Beltsville, Maryland 20705. Wash. 595-5393, Balt. 792-2211. 7:30 a.m. to 6:00 p.m., Monday thru Friday.

DEALERS

Your company name and message can contain up to 25 words for as little as \$150 yearly (prepaid), or \$15 per month (prepaid quarterly). No mention of mail-order business or area code permitted. Directory text and payment must reach us 60 days in advance of publication. For example, advertising for the Jan. '84 issue must be in our hands by Nov. 1st. Mail to 73 Magazine, Peterborough NH 03458. ATTN: Nancy Ciampa.

PROPAGATION

J. H. Nelson 4 Plymouth Dr. Whiting NJ 08759

EASTERN UNITED STATES TO:

GMT:	00	02	04	06	80	10	12	14	16	18	20	22
ALASKA	14	7	7	7	3A	3A	3A	7	14	21	21A	21
ARGENTINA	14	7	7	7	7	7	14A	21A	21A	21A	21A	21
AUSTRALIA	21	14	7B	7 B	7 B	7 B	7 B	14B	14	14A	21	21/
CANAL ZONE	14	7	7	7	7	7	14	21	21A	21A	21A	21
ENGLAND	7	7	3A	3A	7	7B	14	21A	21A	21	14	7
HAWAH	21	14	7	7B	7	7	7	7B	14	21A	21A	21
INDIA	7	7 B	7B	7 B	7 B	7 B	14	14A	14	14B	14B	7 B
JAPAN	14	7 B	7 B	7 B	7 B	7	7	7 B	7B	7B	14B	21
MEXICO	14A	14	7	7	7	7	7	14	21A	21A	21A	21
PHIL IPPINES	14	7 B	7B	7B	7B	7B	7B	7B	14B	148	148	14
PUERTO RICO	14	7	7	7	7	7	14	21	21A	21A	21	14/
SOUTH AFRICA	14	7	7	7	7B	14	21	21A	21A	21A	21A	14/
U. S. S. R.	7	7	3A	3A	7	7B	14	21A	14	7A	7B	7
WEST COAST	14A	14	7	7	. 7 .	7	7	14	21A	21A	21A	21

CENTF	A	4	U	TIV	E)	ST	A	ΓΕ	S	TC) :
ALASKA	14A	7A	7	7	3A	3A	3A	7	14	21	21A	21A
ARGENTINA	14A	7A	7	7	7	7	14A	21A	21A	21A	21A	21A
AUSTRALIA	21A	14A	7A	7B	7 B	7B	7 B	7B	14	14A	21	21A
CANAL ZONE	14	14	7	7	7	7	7A	21	21A	21A	21A	21A
ENGLANO	7	7	3A	3A	7	7B	14B	21	21A	21	14	7
HAWAII	21A	14	7 A	7	7	7	7	7	14	21A	21A	21A
INOIA	7	14B	7 B	7B	7B	7B	7B	14	14	14B	14B	7B
JAPAN	21	14B	7 B	7 B	7 B	7	7	7	7 B	7B	14B	21
MEXICO	14	7A	7	7	7	7	7	14	21	21	21A	21
PHILIPPINES	21	14	7B	7B	7 B	7B	7 B	7	14B	148	14	14A
PUERTO RICO	14	14	7	7	7	7	14	21	21	21A	21A	21
SOUTH AFRICA	14	7	7	7	7 B	7B	14	21	21A	21A	21A	14A
U. S. S. R.	7	7	3A	3A	7	7B	7B	14A	14	7B	7 B	7 B

WESTE	RI	V	U١	ΠĪ	ΈĮ		ST	A.	ΓE	S	TC) :
ALASKA	14A	14	7	3A	3A	3A	3A	3A	7A	14A	21	21A
ARGENTINA	21A	14	7	7	7	7	7 B	21	21A	21A	21A	21A
AUSTRALIA	21A	21A	14	14	14B	7B	7B	7 B	14	14A	21	21A
CANAL ZONE	21	14	7	7	7	7	7	21	21A	21A	21A	21A
ENGLAND	7B	7	3A	3A	7	7B	7B	14B	21A	21	14	7 B
HAWAII	21A	21	14	7 A	7	7	7	7	14	21A	21A	21A
INDIA	14	14	7B	7B	7 B	7 B	7 B	7 B	14	14B	14B	14B
JAPAN	21A	21	14B	7B	7 B	7	7	7	7	7B	14	21A
MEXICO	14A	14	7	7	7	7	7	14	21A	21A	21A	21
PHILIPPINES	21A	21	14	7B	7 B	7B	7B	7	14	14	14	21
PUERTO RICO	14	14	7	7	7	7	7	14	21A	21A	21A	21A
SOUTH AFRICA	14	7	7	7	7B	7 B	7 B	14	21	21A	21A	14A
U. S. S. R.	7B	7	3A	3A	7	7 B	7 B	14	14	7 B	7 B	7 B
EAST COAST	144	14	7	7	7	7	7	14	21A	21A	21A	21

A = Next higher frequency band may also be useful. B = Difficult circuit this period.

First letter = night waves. Second = day waves.

G = Good, F = Fair, P = Poor, * = Chance of solar flares.

= Chance of aurora.


NOTE THAT NIGHT WAVE LETTER NOW COMES FIRST.

NOVEMBER

SUN MON		TUE	WED	THU	FRI	SAT	
		1 F/F	2 F/G	3 G/G	4 G/G	5 G/G	
6 P/F*	7 F/F	8 _{G/G}	9 G/G	10 G/G	11 F/G	12 F/G	
13 F/G	14 F/G	15 F/G	16 G/G	17 G/G	18 F/G	19 G/G	
20 G/G	21 _{G/G}	22 G/G	23 _{G/G}	24 F/G	25 F/G	26 F/G	
27 F/F	28 F/F	29 F/F	30 P/F*				

-230R: QUITE A SIGHT! (AND EASY TO SEE, TOO!!)

Sporting an all-new Liquid Crystal Display, the FT-230R is Yaesu's high-performance answer to your call for a very affordable 2 meter mobile rig with an easy-to-read frequency display! The FT-230R combines microprocessor convenience, a sensitive receiver, a powerful yet clean transmitter strip, and the new dimension of LCD frequency readout. See your Authorized Yaesu Dealer today — and go home with your new FT-230R!

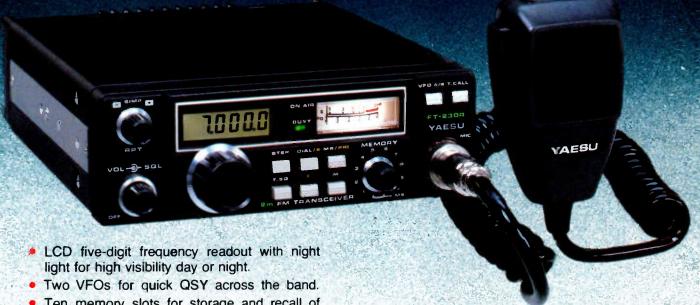

- · Ten memory slots for storage and recall of favorite channels.
- Selectable synthesizer steps (5 kHz or 10 kHz) in dial or scanning mode.
- Priority channel for checking a favorite frequency for activity while monitoring another.
- Unique VFO/Memory Split mode for covering unusual repeater splits.
- Up/Down band scan plus memory scan for busy or clear channel. Scanning microphone included in purchase price.
- Full 25 watts of RF power output from extremely compact package.
- Built-in automatic or manual tone burst.
- Optional synthesized CTCSS Encode and Encode/Decode boards available.
- Lithium memory backup battery with estimated lifetime of five years.
- Now available: FT-730R 10 watt 440-450 MHz FM Mobile Transceiver

FT-208R FM Handheld 2 Meters



FT-708R FM Handheld

And don't forget! Yaesu has a complete line of VHF and UHF handheld and battery portable transceivers using LCD display!!!



FT-290R - 2 Meters SSB/CW/FM Portable

FT-690R - 6 Meters USB/CW/AM/FM Portable

FT-790R - 70 cm SSB/CW/FM Portable 430-440 MHz

Price and Specifications Subject To Change Without Notice or Obligation







YAESU ELECTRONICS CORPORATION 6851 Walthall Way, Paramount, CA 90723 • (213) 633-4007 YAESU CINCINNATI SERVICE CENTER 9070 Gold Park Drive, Hamilton, OH 45011 • (513) 874-3100

"DX-traordinary."



Superior dynamic range, auto. antenna tuner, QSK, dual NB, 2 VFO's, general coverage receiver.

The TS-930S is a superlative, high performance, all-solid state, HF transceiver keyed to the exacting requirements of the DX and contest operator. It covers all Amateur bands from 160 through 10 meters, and incorporates a 150 kHz to 30 MHz general coverage receiver having an excellent dynamic range.

Among its other important features are. SSB slope tuning, CW VBT, IF notch filter, CW pitch control, dual digital VFO's, CW full break-in, automatic antenna tuner. and a higher voltage operated solid state final amplifier. It is available with or without the AT-930 automatic antenna tuner built-in.

• 160-10 Meters, with 150 kHz-30 MHz general coverage receiver.

Covers all Amateur frequencies from 160-10 meters, including new WARC bands, on SSB, CW, FSK, and AM. Features 150 kHz-30 MHz general coverage receiver. Separate Amateur band access keys allow speedy band selection. UP/DOWN bandswitch in 1-MHz steps. A new, innovative, quadruple "UP" conversion, digital PLL synthesized circuit provides superior frequency accuracy and stability, plus greatly enhanced selectivity.

• Excellent receiver dynamic range. Receiver two-tone dynamic range, 100 dB typical (20 meters, 50-kHz spacing, 500 Hz CW bandwidth, at sensitivity of 0.25 μ v, S/N 10 dB), provides the ultimate in rejection of IM distortion.

· All solid state, 28 volt operated final amplifier.

The final amplifier operates on 28 VDC for lowest IM distortion. Power input rated at 250 W on SSB, CW, and FSK, and at 80 W on AM. Final amplifier protection circuits with cooling fan. SWR/Power meter built-in.

• CW full break-in.

CW full break-in circuit uses CMOS logic IC plus reed relay for smooth, quiet operation. Switchable to semi-break-in. · Automatic antenna tuner, built-in. Covers Amateur bands 80-10 meters. including the new WARC bands. Tuning range automatically pre-selected with band selection to minimize tuning time. "AUTO-THRU" switch on front panel.

· Dual digital VFO's.

10-Hz step dual digital VFO's include band information. Each VFO tunes continuously from band to band. A large, heavy, flywheel type knob is used for improved tuning ease. T.F. Set switch allows fast transmit frequency setting for split-frequency operations. A=B switch for equalizing one VFO frequency to the other. VFO "Lock" switch provided. RIT control for ±9.9 kHz.

Eight memory channels.

Stores both frequency and band information. VFO-MEMO switch allows use of each memory as an independent VFO. (the original memory frequency can be recalled at will), or as a fixed frequency. Internal Battery memory back-up, estimated I year life. (Batteries not Kenwood supplied)

· Dual mode noise blanker ("pulse" or "woodpecker").

NB-1, with threshold control, for pulse-type noise. NB-2 for longer duration woodpecker" type noise.

SSB IF slope tuning.

Allows independent adjustment of the low and/or high frequency slope of the IF pass-band, for best interference rejection, HIGH/ LOW cut control rotation not affected by selecting USB or LSB modes.

CW VBT and pitch controls.

CW Variable Bandwidth Tuning control tunes out interfering signals. CW pitch controls shifts IF passband and simultaneously changes the pitch of the beat frequency. A "Narrow/Wide" filter selector switch is provided.

IF notch filter.

100 kHz IF notch circuit gives deep. sharp, notch, better than -40 dB.

- Audio filter built-in.
- Tuneable, peak-type audio filter for CW.
- AC power supply built-in.
 120, 220, or 240 VAC, switch selected (operates on AC only)

• Fluorescent tube digital display. Six digit readout to 100 Hz (10 Hz modifiable), plus digitalized sub-scale with 20-kHz steps. Separate two digit Indication of RIT frequency shift. In CW mode, display indicates the actual carrier frequency of received as well as transmitted signals.

RF speech processor.

RF clipper type processor provides higher average "talk-power," improved intelligibility.

One year limited warranty on parts and labor.

Other features:

SSB monitor circuit. 3 step RF attenuator. VOX, and 100-kHz marker.

Optional accessories:

- AT-930 automatic antenna tuner. SP-930 external speaker with selectable audio filters
- YG-455C-I (500 Hz) or YG-455CN-I (250 Hz) plug-in CW filters for 455-kHz IF.
 YK-88C-I (500 Hz) CW plug-in filter for
- 8.83-MHz IF
- YK-88A-1 (6 kHz) AM plug-in filter for
- 8.83-MHz IF. SO-I commercial stability TCXO (temperature compensated crystal oscillator). Requires modifications.
- MC-60A deluxe desk microphone with UP/DOWN switch, pre-amplifier. 8-pin plug • TL-922A linear amplifier (not for CW QSK)
- SM-220 station monitor (not for pan-adapter).
- . HS-6, HS-5, HS-4, headphones.

More information on the TS-930S is available from all authorized dealers of Trio-Kenwood Communications, 1111 West Walnut Street. Compton. California 90220.



