

\$2.00

ham **radio**



magazine

hr 

APRIL 1979

- propagation predictions 26
- memory keyer 32
- active filter for RTTY 46
- R-4C audio amplifier 48
- audio filter 62
- 432-MHz converter 74

40-meter receiver for home construction

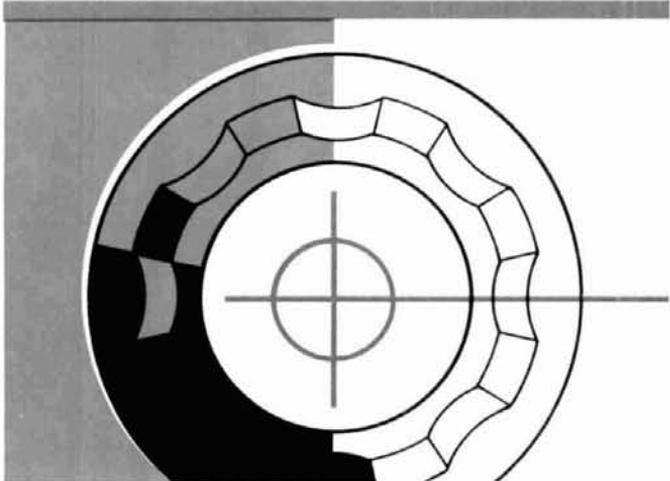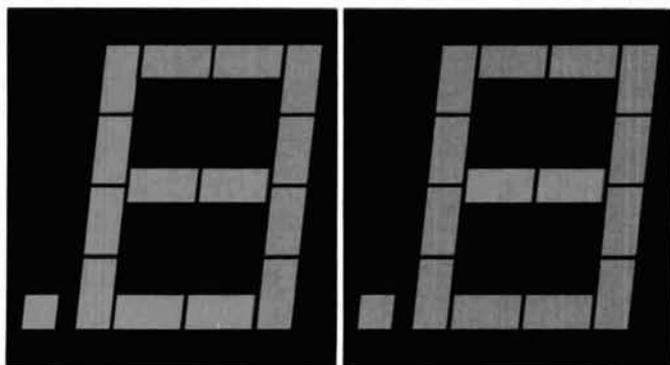

Henry Radio is proud to offer the most important innovation in Amateur Radio since SSB



Historically, Amateur Radio operators have made important contributions to the art and science of communications. Once again Amateur Radio assumes leadership in advanced communications technology. You have the privilege of being one of the first to include a Narrow Band Voice Modulation (NBVM) system in your station. The VBC Model 3000 is the system that you have been hearing about for a year and have read about recently in QST and the 1979 ARRL Handbook. It is the world's first such system.

The VBC Model 3000 provides full audio level compression and expansion... complete intelligibility in only 1300 Hz bandwidth. It permits you to take full advantage of other stations' RF speech clippers and processors... similar to the amplitude compression and expansion used for many years in telephone and satellite communications.

The Model 3000 is for mobile and fixed station use and requires no modifications to your existing equipment. It is completely self contained, including its own audio amplifier. The unit automatically switches into transmit mode when microphone is keyed or voice operation is used. It connects just after the microphone on transmit and just prior to the speaker on receive. In addition to its basic

function of operating in a narrow bandwidth, the Model 3000 also increases the performance of your station in the following ways:

- Reduces adjacent channel interference
- Increases signal to noise ratio
- Increases communications range

Some of its outstanding features include:

- High quality narrow band speech
- Self contained transmit/receive adapter
- Built in audio amplifier
- 5 active filters with a total of 52 poles
- Rugged dependable hybrid IC technology
- Low power consumption

Receive only features, such as sharp voice and CW filtering and amplitude expansion, provide improved reception without requiring a unit at the transmitting station.

For the more advanced experimenter the Model 3000 is available in a circuit board configuration for building into your present transceiver.

Henry Radio is ready to offer technical assistance and advice on the use and servicing of the Model 3000 and will help introduce new owners to others operating NBVM units. Get in on the ground floor... order yours now.

Price: VBC Model 3000 \$349.00

Circuit board configuration \$275.00

For more detailed information please call or write. The Model 3000 will be available from most Tempo dealers throughout the U.S. and abroad.

NEW TOLL FREE ORDER NUMBER: (800) 421-6631
For all states except California
Calif. residents please call collect on our regular numbers.

11240 W. Olympic Blvd., Los Angeles, Calif. 90064 213/477-6701
931 N. Euclid, Anaheim, Calif. 92801 714/772-9200
Butler, Missouri 64730 816/679-3127

Henry Radio

Prices subject to change without notice.



We've given you the best antenna on the market. Now put it on the best tower. The name Hy-Gain says quality ...need we say more?

HG-37LWCB

- Free Standing Crank-Up with lower section secured to building
- 37 ft. high
- 4.0 sq. ft. of Antenna Area

HG-33 MT2

- Free Standing Crank-Up with lower section secured to building
- 33 ft. high
- 8.5 sq. ft. Antenna Area
- 10 ft. sections

HG-35 MT2

- Free Standing Crank-Up with lower section secured to building
- 35 ft. high
- 9.5 sq. ft. Antenna Area

HG-50 MT2

- Free Standing Crank-Up with lower section secured to building
- 50 ft. high
- 8.6 sq. ft. Antenna Area

HG-68 MT2

- Free Standing Crank-Up with lower section secured to building
- 68 ft. high
- 5.0 sq. ft. Antenna Area

HG-37 SS

- Free Standing Crank-Up
- 37 ft. high
- 9.0 sq. ft. Antenna Area

HG-52 SS

- Free Standing Crank-Up
- 52 ft. high
- 9.0 sq. ft. Antenna Area

HG-54 HD

- Free Standing Crank-Up
- 54 ft. high
- 16.0 sq. ft. Antenna Area

HG-70 HD

- Free Standing Crank-Up
- 70 ft. high
- 16.0 sq. ft. Antenna Area

 **hy-gain** electronics
DIVISION OF TELEX COMMUNICATIONS, INC.


8601 Northeast Highway 6 • Lincoln, Nebraska 68505 U.S.A.
Telephone: (402) 467-5321 telex: Hygain Lcn a 48-4324

EUROPE: 22, rue de la Légion-d'Honneur
93200 Saint-Denis - France



NEW MFJ-981 3 KW Versa Tuner IV

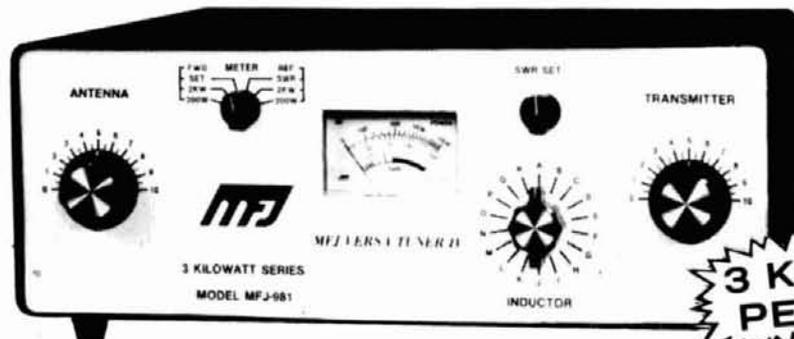For \$199.95 you can run up to 3 KW PEP and match everything from 1.8 thru 30 MHz: coax, balanced lines, random wires. Built-in balun, SWR, dual-range forward and reflected power meter.



FREE MFJ LOGBOOK . . .

Just ask your MFJ dealer to demonstrate these 3 KW Versa Tuner IVs. Logbook quantities are limited.

\$199⁹⁵

The **NEW MFJ-981 3 KW Versa Tuner IV** lets you run up to 3 KW PEP and match any feedline continuously from 1.8 to 30 MHz: coax, balanced line or random wire.

This gives you maximum power transfer to your antenna for solid QSO's and attenuates harmonics to reduce TVI and out-of-band emission.

An accurate meter gives SWR, forward, reflected power in 2 ranges (2000 and 200 watts).

A new all metal, low profile cabinet gives you RFI protection, rigid construction, and sleek styling.

Black finish. Rich anodized aluminum front panel. 5x14x14 inches. A flip down wire stand tilts tuner for easy viewing.

Efficient, encapsulated 4:1 ferrite balun. 500 pf, 6000 volt capacitors, 18 position dual inductor, 17 amp, 3000 volt ceramic rotary switch, 2% meter, SO-239 coax connectors, ceramic feedthru for random wire and balanced line. Binding post for ground.

Every single unit is tested for performance and inspected for quality. Solid American construction,

quality components. Full one year limited warranty.

For your nearest MFJ dealer, call toll-free 800-647-1800. Stop by your dealer. Compare it feature for feature with other tuners. Compare its value, its quality and its performance.

After a truly side by side comparison, you'll be convinced that its value, quality and features make it a truly outstanding value.

Why not visit your dealer today and see the NEW MFJ-981 3 KW Versa Tuner IV? If no dealer is available order direct from MFJ.

MFJ-982 3 KW VERSA TUNER IV has balun, 7 position antenna switch. Matches everything: coax, balanced lines, random wires continuously from 1.8 to 30 MHz.

Flexible 7 position antenna switch lets you select 1 coax thru tuner and 2 coax thru tuner or direct, or random wire and balanced line.

Up to 3 KW PEP. Match any feedline from 1.8 to 30 MHz: coax, random wire, balanced line.

Gives maximum power transfer. Harmonic attenuation reduces TVI, out of band emissions.

Black metal cabinet, anodized aluminum front panel. Flip down wire stand. 5x14x14 in.


Encapsulated 4:1 ferrite balun. 500 pf, 6000 volt capacitors, 18 position dual inductor, 17 amp

- 7 position antenna switch
- 4:1 ferrite balun for balanced lines

\$199⁹⁵

ceramic switches, SO-239 coax connectors, ceramic feedthru for random wire, balanced line, binding post for ground.

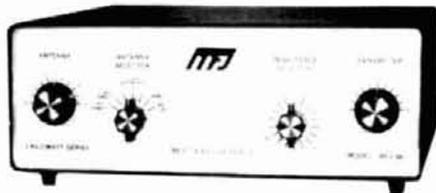Made in USA. One year limited warranty. See it at your nearest dealer. If no dealer is available order direct from MFJ.



If you already have a SWR/wattmeter, the MFJ-982 is for you.

MFJ-980 3 KW VERSA TUNER IV has built-in balun for balanced lines. Matches coax, balanced lines, random wires, 1.8 to 30 MHz.

Up to 3 KW PEP. Match any feedline from 1.8 to 30 MHz: coax, random wire, balanced line. Heavy duty encapsulated 4:1 ferrite balun.

Gives maximum power transfer. Harmonic attenuation reduces TVI, out of band emissions.

Black metal cabinet, anodized aluminum front panel. Flip down wire stand. 5x14x14 in.

500 pf, 6000 volt cap., 18 position dual inductor, 17 amp ceramic switches.

- Encapsulated 4:1 ferrite balun for balanced lines

\$169⁹⁵

Made in USA. One year limited warranty. See it at your nearest dealer. If no dealer is available order direct from MFJ.



This is MFJ's lowest priced 3 KW Versa Tuner IV.

FOR YOUR NEAREST DEALER OR FOR ORDERS

CALL TOLL-FREE 800-647-1800

Order any product from MFJ and try it. If not delighted, return within 30 days for a prompt refund (less shipping).

Order today. Money back if not delighted. One year limited warranty. Add \$8.00 shipping/handling.

For technical information, order/repair status, in Mississippi, outside continental USA, call 601-323-5869.

Order By Mail or Call TOLL FREE 800-647-1800 and Charge It On

MFJ ENTERPRISES, INC.

P. O. BOX 494

MISSISSIPPI STATE, MISSISSIPPI 39762



ham radio

magazine

APRIL 1979
volume 12, number 4

T. H. Tenney, Jr., W1NLB
publisher

James R. Fisk, W1HR
editor-in-chief

editorial staff

Martin Hant, WB1CHQ
administrative editor

Charles J. Carroll, K1XX
Patricia A. Hawes, WA1WPM
Alfred Wilson, W6NIF
assistant editors

Thomas F. McMullen, Jr., W1SL
Joseph J. Schroeder, W9JUV
associate editors

Wayne T. Pierce, K3SUK
cover

publishing staff

C. Edward Buffington, WB1AMU
assistant publisher

Fred D. Moller, Jr., WA1USC
advertising manager

James H. Gray, W1XU
assistant advertising manager

James R. Wales
art director

Susan Shorrock
circulation manager

ham radio magazine
is published monthly by
Communications Technology, Inc.
Greenville, New Hampshire 03048
Telephone: 603 878 1441
Address all editorial and
advertising correspondence to
Greenville, New Hampshire 03048

subscription rates

United States: one year, \$15.00
two years, \$26.00; three years, \$35.00

Canada and other countries (via Surface Mail)
one year, \$18.00; two years, \$32.00
three years, \$44.00

Europe, Japan, Africa (via Air
Forwarding Service) one year, \$25.00

All subscription orders payable in
United States funds, please.

foreign subscription agents

Foreign subscription agents are
listed on page 103

Microfilm copies
are available from
University Microfilms, International
Ann Arbor, Michigan 48106
Order publication number 3076

Cassette tapes of selected articles
from ham radio are available to the
blind and physically handicapped
from Recorded Periodicals
919 Walnut Street, 8th Floor
Philadelphia, Pennsylvania 19107

Copyright 1979 by
Communications Technology, Inc.
Title registered at U. S. Patent Office

Second-class postage
paid at Greenville, N.H. 03048
and at additional mailing offices
ISSN 0148-5989


Subscription inquiries and changes of
address should be directed to ham radio
magazine, Greenville, New Hampshire 03048
Please include address label from most
recent issue if possible

Postmaster send Form 3579 to ham radio
Greenville, New Hampshire 03048



contents

- 12 40-meter receiver**
M.A. Chapman, K6SDX
- 23 CW operator's PAL**
Carleton F. Maylott, W2YE
- 26 calculator-aided
propagation predictions**
Henry G. Elwell, N4UH
- 32 deluxe memory keyer**
Robert C. Cheek, W3VT
- 46 bandpass filter for RTTY**
Nathan H. Stinnette, W4AYV
- 48 audio amplifier
for the R-4C**
J. Robert Sherwood, WB0JGP
George B. Heidelman, K8RRH
- 50 the verti-loop**
Herbert L. Bresnick, WB2IFV
- 56 interesting solutions
to the jammer problem**
Nuryev Sidelbandsk, UX3PU
- 62 variable-frequency audio filter**
Lewis T. Fitch, W4VRV
- 66 tranceive and split operation
with the TR-4/R-4B combination**
William P. Winter, Jr., WB8JCQ
- 74 high-performance 432-MHz converter**
Charles H. Robinson, N9KD
- 80 impedance measurements
using an SWR bridge**
Benjamin J. Lowe, K4QF
- 86 digital techniques:
flip-flop internal structure**
Leonard H. Anderson
- 4 a second look**
- 118 advertisers index**
- 108 coming events**
- 86 digital techniques**
- 103 flea market**
- 112 ham mart**
- 92 ham notebook**
- 6 letters**
- 8 presstop**
- 118 reader service**
- 50 weekender**

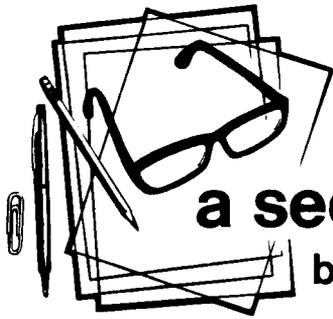

a second look

by Jim Fisk

It's spring and hamfest time again. It seems that no matter where you look, you'll see an announcement for yet another convention, radio auction, hamfest, or fm talk-in, and the Dayton Hamvention in Dayton, Ohio, which is billed as the *original* hamvention, is one of the biggest of the year. Scheduled for the last weekend of April, the Dayton Hamvention draws upon the large amateur population of the Midwest and has provided the model for many successful Amateur Radio conventions around the country. Several years ago, in fact, a contingent of Japanese amateurs came over to take a look at the Hamvention and its management, then returned to Japan where they staged a very popular and successful ham convention in the shadow of Mount Fujiyama.

Growing by leaps and bounds in recent years, more than 19,000 hams were in attendance last year, and even more are expected in 1979! But even with this huge influx of Amateur Radio enthusiasts, everything runs smoothly, and this year, as always, the Dayton Hamvention Committee has gone all out to ensure a lively, interesting weekend for all. Bright and early Friday, April 27th, the Amateur Radio manufacturers and distributors will start setting up their exhibits. At high noon the exhibition doors will be opened to the public — the exhibit hall will remain open until 8:30 PM, so you'll have plenty of time to browse through the many commercial exhibits. And, if this year's exhibit area is anything like those in the past, you can bet some major new Amateur Radio products will be unveiled by the manufacturers.

When the lights go out in the exhibit hall on Friday evening, they'll come on in other parts of town with banquets or gatherings scheduled for the QCWA and Old Old Timers as well as groups interested in DX, slow-scan TV, and fm repeaters (the well-known FM Bash). By early Saturday morning things will really be humming around Hara Arena, weekend home of the Hamvention, as vendors and traders from miles around start setting up shop for the famous Dayton Flea Market. Like other parts of the Hamvention, the flea market grows every year, and now takes up more than 10 acres of real estate behind the main convention hall. Whether you're interested in good used ham gear, replacement parts, vacuum tubes, new components, or antique radios, chances are good that the item you want will be for sale — your problem is to locate it among the thousands of items on display.

At 9:00 AM Saturday morning the first of many forums will be kicked off with sessions devoted to antennas, microwave techniques, space communications, microprocessors, and code proficiency. Between 1130 and 1300 there will be meetings for the DXers and Oscar enthusiasts. After lunch the emphasis will be on contests, QRP rigs, ATV, fm repeaters, vhf/uhf, and moonbounce. The traditional Saturday-night cocktail hour and banquet begins at 7:00 PM.

Early Sunday morning, just about sunrise, the Flea Market will open for another day's business; a few hours later the exhibition hall will open once again and the ARRL Forum will get under way. If you've never been to a major ham convention, the ARRL Forum offers you a chance to ask the ARRL's officers and directors questions about League affairs. The FCC Forum scheduled for Sunday afternoon gives you a similar opportunity to ask questions of FCC staff members from Washington. Both the ARRL and FCC Forums are among the most popular get-togethers at any convention, so be sure you arrive early to get a good seat.

In addition to the various sessions and forums, there will be technical and group meetings for ARPSC, OSSB, and MARS. Other special groups attending the Hamvention are the Buckeye Belles, Mid-Cars, Ten-Ten, Firebirds, Young Ladies Radio League, and others. If past performance and the 1979 schedule are any indication, this year's Dayton Hamvention will be another great show.

For amateurs who arrive in trailers and campers, parking will be permitted only in specially designated areas (no campers or travel trailers will be permitted to park in the Arena lot, including the flea market area). For those who stay in the downtown hotels, free bus service will be provided out to the Hamvention. A large allotment of rooms has been set aside for the Hamvention by the local hotels and motels; all room requests should be directed to the Accommodations Committee so that rooms can be allotted within the available supply. For more information, and a Hamvention brochure, write to the Dayton Hamvention, Post Office Box 44, Dayton, Ohio 45401.

If you've never been to the Dayton Hamvention, but have considered it, this is the year to go. If you've been before, you already know what I'm talking about. See you there!

Jim Fisk, W1HR
editor-in-chief

Optimum Performance Optimum Value / IC-211



2 meter Multi-Mode 4 MHz Transceiver

- Full 4 MHz • Operates new subband • Two VFO's built in • Single knob frequency selection • Variable offset • Remote programming with compatible RM2 microprocessor • Two speed optical chopper dial • Computer input port • LSI circuitry • 117v AC built in • Variable power output • 100 Hz & 5 KHz, 144-146 / 5 KHz, 146-148 • SSB & CW, 144-148 / FM, 144-148 • IF noise blanker • Front panel discriminator • SWR meter • VOX on SSB with adjustable gain level and delay • CW sideband monitor • Semibreak-in CW

"The IC-211 is a very fine piece of electronic equipment. It is every bit what I expected, and more."

John, K2UFA

"Very fine receiver, and easy to operate, even with so much on it. Nice!"

Alex, WD4DGF

"Fantastic rig! ICOM line recommended by dealer, but rigs sold themselves!!!"

Jerry, WB9QKV

"The IC-211 outperforms anything I've used... Regal quality throughout... exceptional cosmetic design and compact ruggedness. Truly a masterpiece of engineering inside and out."

Steve, WD9FRP

"I only buy the best."

Frank, WB4WUY

"An excellent rig. Both my wife (WB9BFY) and myself are very pleased with it."

Neal, WB9ZCU

"An exceptional piece of equipment. Very versatile."

Bernie, WB2FBP

"The one that probably best illustrates our point—that your Amateur Radio dollar buys a lot more these days—is the ICOM IC-211... The key word in any description of the IC-211 is versatility."

**QST Magazine,
"Product Review",
Dec. 1978**

All ICOM radios significantly exceed FCC specifications limiting spurious emissions.

Specifications are subject to change without notice.

IC-211 Specifications: □ Frequency Coverage (any mode): 144.00 to 148.00 MHz □ Modes: SSB (A3J), FM (F3), CW (A1) □ Supply Voltage: DC: 13.8V ± 15%; AC: 117V ± 10% □ Size: 111mm(h) x 241mm(w) x 264mm(d) □ Weight: 6.8 Kg □ TX Output: A3J, 10W (PEP); A1 & F3, 10W □ Spurious Radiation: -60 dB below Carrier □ Microphone Impedance: 600 Ohms □ Sensitivity: A3J & A1, 0.5 microvolt 10 dB S + N/N; F3, 0.6 microvolt for 20 dB quieting □ Spurious Response: -60 dB or better □ Synthesizer Frequency Range: 144.00 MHz to 148.00 MHz □ Synthesizer Stability: ± 1KHz □ Frequency Readout: 7 digit LED 100 Hz Readout □ Antenna Impedance: 50 ohms □ Spurious Response Rejection Ratio: Better than 60 dB □ IF frequencies: SSB, 10.7 MHz; FM 10.7 MHz, 455 KHz □ Carrier Suppression: Better than 40 dB down □ Opp Sideband Suppression: More than 40 dB down □ Selectivity: SSB, CW ± 1.2 KHz at -6 dB, ± 2.4 KHz at -60 dB; FM ± 7.5 KHz at -6 dB, ± 15 KHz at -60 dB

HF/VHF/UHF AMATEUR AND MARINE COMMUNICATION EQUIPMENT

DISTRIBUTED BY:




ICOM

ICOM WEST, INC.
Suite 3
13256 Northrup Way
Bellevue, Wash. 98005
(206) 747-9020

ICOM EAST, INC.
Suite 307
3331 Towerwood Drive
Dallas, Texas 75234
(214) 620-2780

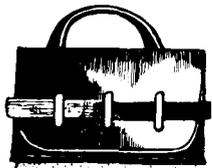ICOM CANADA
7087 Victoria Drive
Vancouver B.C. V5P 3Y9
Canada
(604) 321-1833



comments

Dear HR:

I've just finished reading the article on phase-locked loop demodulators in the September issue, and noticed a couple of minor errors which I'd like to comment on. In the discussion of capture and lock range, the PLL is referred to as a positive feedback system. That is not correct, as a PLL uses negative feedback (like any other closed-loop system) to reduce the error to a minimum. In this case, it is the phase error between the reference (the frequency you want to track) and the controlled variable (the VCO frequency) which is reduced by developing a signal proportional to their difference.

Another gremlin showed up in the caption for Fig. 4 and the accompanying text, where the acquisition beat note is described as sinusoidal. It is not sinusoidal, as an examination of photographs of that signal will show. It can't be a sinusoid, because a sinusoid doesn't have a dc component. As the author points out, the output of the phase detector and low-pass filter has to have a dc component which will drive the VCO toward the reference. The most common phase detector in PLL systems is a multiplier which multiplies the input signal by a squarewave from the VCO. The multiplier produces a positive halfwave rectified output when the inputs are 90 degrees out of phase, and a negative half wave rectified output when the inputs are 180 degrees out of phase. The acquisition beat note consists of a series of these rectified sine waves which

increase in period as the difference frequency decreases. The low-pass filter acts as an integrator which reduces the ripple and provides an average dc voltage which drives the VCO toward the reference. The PLL will lock when the signals are the same frequency and differ in phase by 90 degrees, which is the point where the phase detector and low-pass filter has zero dc output.

Academic nitpicking aside, I was pleased to see a nonmathematical discussion of amateur applications for the PLL. The PLL offers the possibility of some improvement in threshold sensitivity over conventional discriminators, due to its lower noise bandwidth. The noise bandwidth of the PLL is determined by the lowpass filter (approximately 3-5 kHz for an fm speech demodulator). A conventional discriminator must contend with the noise from the full i-f bandwidth. Since the i-f bandwidth for amateur fm is usually 14 kHz (and the noise bandwidth is even higher), the threshold sensitivity of a PLL demodulator should be several dB better than a conventional discriminator. I plan to run some experiments in the near future to determine the actual improvement in practice, and hope to see more discussion of this subject in *ham radio*.

John J. Murphy, K6JLF
Post Office Box 1875
Ridgecrest, California 93555

pi network design

Dear HR:

A small short circuit in my article on "Pi Network Design" (March, 1978 issue) has surfaced courtesy of correspondence with Robert F. White, W6PY. Three values at the top left-hand column on page 37

should be:

$$X_c' = -608.64 \quad C_c' = 36.572 \text{ pF}$$

In the second paragraph following the tabulation, total $C_m = 222.59 \text{ pF}$. Total mid-point capacitance, due to improper calculation of the first (prime-valued) section, is off by exactly 5 pF.

Upon checking my original notes, I found there were two calculations for the dual-section pi network; I inadvertently used the wrong set. The equations are correct; only the calculated values are in error. W6PY found the error with his TI-59 calculator program.

Leonard Anderson
Sun Valley, California

data package for the programmable hf receiver

Dear HR:

Because of the large response I received to my programmable high-frequency receiver, which appeared in the October, 1978, issue of *ham radio*, I have put together a limited number of data packages as a help to prospective builders. These data packages include over 40 pages of circuit and wiring diagrams, mechanical diagrams, and other data; the cost is \$9.75 per set, to cover costs of printing and mailing. The data package is intended as an aid in duplicating the receiver or using the same basic scheme to build a receiver to suit your readers' own needs. Printed-circuit layouts are not included, but the mechanical and wiring diagrams will be helpful in circuit-board development.

Norman J. Foot, WA9HUV
293 East Madison Avenue
Elmhurst, Illinois 60126

Instant recall. (and with 10 or 25 watts of power)



NO. TR-7600

MODEL NO. TR-7625

Kenwood offers you a choice. The TR-7600 (10-watt) or TR-7625 (25-watt) with optional RM-76 Microprocessor Control Unit.

TR-7600 and TR-7625...one of them is sure to fit the needs of today's Amateur Operator who's looking for optimum versatility in a 2-meter FM transceiver. And, when either rig is combined with the RM-76, a whole new dimension unfolds in channel memory and scanning capability. Here's what you get:

TR-7600 AND TR-7625 (ONLY)

- Memory channel...with simplex or repeater (± 600 kHz transmitter offset) operation.
- Mode switch for operating simplex or for switching the transmit frequency up or down...or for switching the transmitter to the frequency you have stored in the TR-7600 or TR-7625's memory (while the receiver remains on the frequency you've selected).
- Digital frequency display (large, bright, orange LEDs).

- Dual concentric knobs for fast, easy selection of any 2-meter frequency, in 100-kHz and 10-kHz steps.
- Full 4-MHz coverage (144.000-147.995) on 2-meters; 800 channels; 5-kHz offset switch, and MHz selector switch...for desired band (144, 145, 146, or 147 MHz).
- UNLOCK indicator...an LED that indicates transceiver protection when the frequency selector switches are improperly positioned or the PLL is not locked.

TR-7600 AND TR-7625 WITH RM-76

- Store frequencies in six memories (simplex/repeater).
- Scan all memory channels.
- Automatically scan up the band in 5-kHz steps.
- Manually scan up or down in 5-kHz steps (or fast tune).
- Set lower and upper scan frequency limits.
- Clear scan (for transmitting).

- Stop scan (with HOLD button).
- Scan for busy or open channel.
- Select repeater mode (simplex, transmit frequency offset (± 600 kHz or ± 1 MHz), or one memory transmit frequency).
- Operates on 143.95 MHz simplex (MARS)
- Adaptable to all MARS frequencies.
- Display indicates frequency (even while scanning) and functions (such as auto-scan, lower scan frequency limit, upper scan limit, and error, i.e. transmitting out of band).

See the exciting TR 7600, TR-7625 and RM-76 now at any Authorized KENWOOD Dealer!

 **KENWOOD**
...pacesetter in amateur radio

TRIO-KENWOOD COMMUNICATIONS INC.
1111 WEST WALNUT/COMPTON, CA 90220

presstop

LICENSE FEE REFUNDS came a step closer to reality with Commission adoption of a first Report and Order on its fee refund inquiry, General Docket 78-316. Only fees above \$20 are to be refunded in this first phase, which will begin in April or May, after the necessary fee refund applications and instruction packets can be printed and distributed.

Commission Staff Work has already begun on Phase II of the refund program, which will cover fees of \$20 or less. A Notice of Inquiry on Phase II is supposed to be ready for Commission action in 90 days.

AMATEURS WHOSE LICENSES EXPIRE now have five years instead of one in which to renew them without retaking the exam, the FCC decided at its February 27th meeting. The extended grace period applies only to the operator's license, however; station licenses can be renewed up to one year after they expire, so any Amateur who waits more than a year after expiration to renew will receive a new callsign appropriate for his license class from the group that is currently being issued.

Code Exam Credit, which could formerly be "redeemed" only at the Field Office at which the test had been taken, can now be used at any Commission Field Office.

Five Pending Petitions for Rule Making were also dismissed at the meeting. Four of them had asked for reestablishment of rules permitting Extras to select their own callsigns, while the other (RM-2360) had asked that stations operating on RTTY be permitted to identify by RTTY instead of CW as now required.

FCC's INVESTIGATION of licensing irregularities in the Indianapolis area, which began in mid-1976, is still in progress. A number of central Indiana Amateurs have received letters from the Commission asking them to explain questionable aspects of their licenses or calls.

AMATEUR TRANSMISSIONS of emergency information cannot be rebroadcast by commercial broadcast stations, the Commissioners decided on February 14th. Acting on a petition (RM-2830) filed by the National Association of Broadcasters, the Commissioners agreed to further consider whether CB emergency transmissions should be rebroadcast for public use.

ADDING A "PORTABLE" DESIGNATOR to a callsign has reportedly brought warnings to some Amateurs from FCC field engineers, but if so it's a misunderstanding of the rules. The rules change only eliminated the necessity for indicating portable or mobile status but did not prohibit the practice, which is required by some contest rules. Any Amateur cited or warned for signing portable should pursue the matter with the nearest FCC Field Office, or, if necessary, Washington.

220 MHZ OPERATORS now have a new certificate to shoot for, the "100 CCXX Award" just announced by 220 Notes. Required are 220-MHz contacts with 100 different stations. For an application for the award, which resembles similar 220 MHz incentives offered by the Northrup ARC and the 220 Club of San Diego, write WB9SNZ.

8-BAND WAS has been achieved by K5CM, with — oddly enough — the last holes being on 10 and 40 meters. After finishing up a 2-meter WAS last summer, and already having WAS on 6, Connie realized that he was within striking distance of becoming the first Amateur to earn the WAS award on eight bands. He began working on it in earnest in mid October, and within three months had all 50 cards for 160 in hand and only a few strays on other bands remaining to be cleaned up.

A NEW 2-METER DX RECORD was set February 13, when SV1DM made contact with ZS6DN in Pretoria at 1810Z over a 7117 km path. It didn't stand long, however, as SV1AB (on the north side of Athens) worked ZS6DN just three days later — February 16 — at about the same time to extend it another 10 km.

2-Meter DX is also heating up in the Americas — KP4ES, KP4Q, and KP4AAN all worked Argentina on 2-meter FM, February 19th. Prior KP4-LU contacts had all been SSB or CW.

AN "AMATEUR RADIO OPERATORS ONLY" chain letter seems to be spreading. Most copies seem to be going to DXers, and come from overseas Amateurs.

As Money Is Requested, this letter is strictly illegal under U.S. law. U.S. Amateurs are advised to ignore it.

KHØ CALLSIGNS WILL soon be showing up, as Northern Marianas Amateurs come under FCC jurisdiction. The Commission has decided to "grandfather" those who'd received their Amateur licenses from the former Trust Territory government into FCC licenses, though three KG6s who'd received their licenses as reciprocals must now reapply for an FCC reciprocal permit. Present Northern Marianas stations will be given their choice of keeping their present KG6 or stateside (if any) calls or receiving a new KHØ.

Novice, QRP, 200 w, deluxe — good, better, best — \$299, \$369, \$399, \$699, \$869, \$899, \$1069. TEN-TEC has them all. A choice of seven HF transceiver models — a choice of power levels — a choice of operating features (and accessories) for beginner or old timer. Best of all, there's a wide choice of prices to fit every amateur budget.

TEN-TEC "OMNI" TRANSCEIVERS — REALLY CHOICE.

Top of the line. Deluxe in every respect. Deserving of a place in the finest of operating positions. All solid-state 100% duty cycle 200-watt final amp.; 8-bands (160-10 m plus convertible 10 MHz and "Aux" band positions); broadband design for no tune-up; built-in VOX and PTT; built-in Squelch; 4-position CW-SSB filter and 8-pole crystal filter with separate mode switch to permit using all filters in all modes; 2-speed break-in; 2-range offset tuning; optimized sensitivity from 2 μ V on 160 m to 0.3 μ V on 10 m; greater dynamic range (typically better than 90 dB) plus PIN diode switched 18 dB attenuator; WWV at 10 MHz; front panel control of linear/antenna bandswitching; phone patch jacks; "timed" crystal calibrator (on "A" model only); zero-beat switch; SWR bridge; adjustable ALC and sidetone; dual speakers; plug-in boards; "clamshell" aluminum case with black vinyl covering plus warm dark metal front panel; full shielding, optimum size for convenient operation: 5 $\frac{3}{4}$ "h x 14 $\frac{1}{4}$ "w x 14"d. Model 545 OMNI-A with analog dial, only \$899; Model 546 OMNI-D with six 0.43" LED digital readouts, \$1069. Model 645 keyer, \$85, Model 243 Remote VFO, \$139, Model 248 Noise Blanker, \$49, Model 252MO AC Power Supply, \$119.

TEN-TEC "ARGONAUT" TRANSCEIVER—QRP CHOICE.

The challenge and excitement of working the world on 5 watts. And every feature you need: all solid-state; 5 bands (80-10 m); full amateur band coverage SSB/CW; sensitivity less than 0.5 μ V; offset tuning; 4-pole IF crystal filter, 2.5 kHz bandwidth; analog dial; vernier tuning; automatic sideband selection; built-in speaker; 5-watt input to broadband push-pull final amplifier; PTT; full CW break-in; adjustable sidetone volume and pitch; built-in SWR bridge; TVI filter; plug-in boards; small and light weight enough to go anywhere (4 $\frac{1}{2}$ "h x 13"w x 7"d and 6 lbs.). World beating price, too: Model 509 only \$369; Model 210 AC Power Supply just \$34.

TEN-TEC 540/544 TRANSCEIVERS—POWER CHOICE.

200 watts from the bottom of 80 m to the top of 10 m — SSB or CW. No compromise from the leader in solid-state HF technology. Instant band change without tune-up; sensitivity 0.3 μ V; offset tuning; 8-pole crystal-lattice filter; WWV at 10 & 15 MHz; push-pull solid-state final amp.; 100% duty cycle; adjustable ALC with LED indicator; built-in SWR bridge; PTT; full CW break-in; adjustable sidetone pitch and vol.; zero-beat switch in Model 544. Choose the value leading Model 540 with analog dial and built-in 25 kHz pulsed calibrator for just \$699 or the Model 544 with six 0.43" LED digital readouts for \$869. Model 240 160M converter, \$110; Model 262M AC Power Supply with VOX, \$145; Model 252M AC supply only, \$119.

TEN-TEC CW TRANSCEIVERS—BUDGET CHOICE.


The "Century 21" series. Unique. Modern technology with old-fashioned value. Fine performance, reliability, and simplicity of operation, all at low cost. Win raves from novices and confirmed brass pounders alike. All solid-state; 5 bands (80-10 m) full amateur band coverage; receive CW and SSB, transmit CW; sensitivity 1 μ V or less; offset tuning; 3-position selectivity (2.5 kHz, 1 kHz, 500 Hz); 70 w input to push-pull Class C final amp.; broadbanded for no tune-up or resonating; full break-in; adjustable side-tone level; built-in AC power supply. Choose Model 570 with analog dial for only \$299; Model 574 has a 5 LED digital readouts for only \$399.

The choice is all yours when you choose TEN-TEC HF transceivers; see your nearest dealer or write for full details.

arma

TEN-TEC
SEVIERVILLE, TENNESSEE 37862
EXPORT 5715 LINCOLN AVE., CHICAGO, ILL. 60648

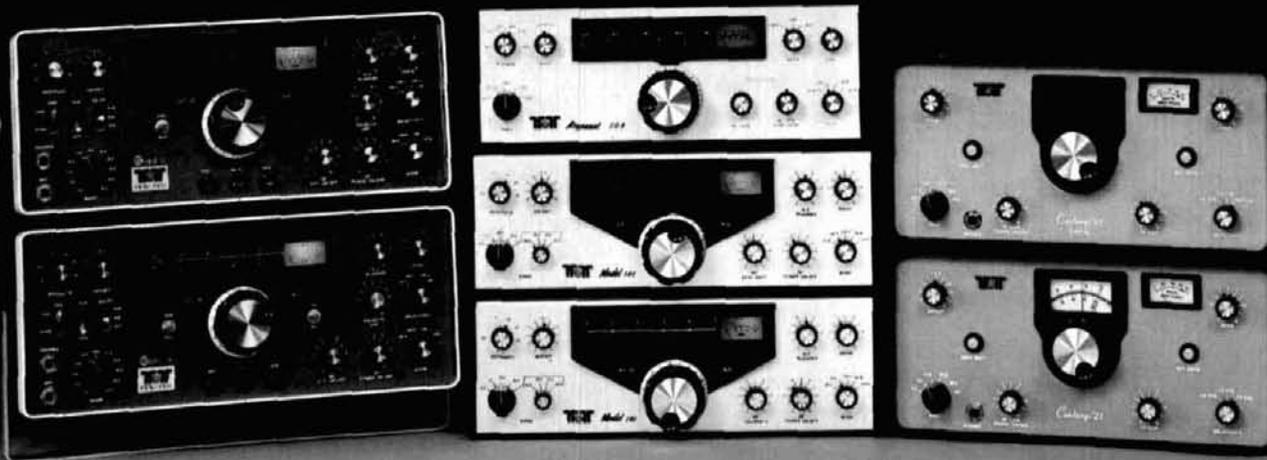WIDEST CHOICE IN HF TRANSCEIVERS: TEN-TEC





TS-1



TS-1JR



PE-2




SD-1

THE DAWNING

The age of tone control has come to Amateur Radio. What better way to utilize our ever diminishing resource of frequency spectrum? Sub-audible tone control allows several repeaters to share the same channel with minimal geographic separation. It allows protection from intermod and interference for repeaters, remote base stations, and autopatches. It even allows silent monitoring of our crowded simplex channels.


We make the most reliable and complete line of tone products available. All are totally immune to RF, use plug-in, field replaceable, frequency determining elements for low cost and the most accurate and stable frequency control possible. Our impeccable 1 day delivery is unmatched in the industry and you are protected by a full 1 year warranty when our products are returned to the factory for repair. Isn't it time for you to get into the New Age of tone control?

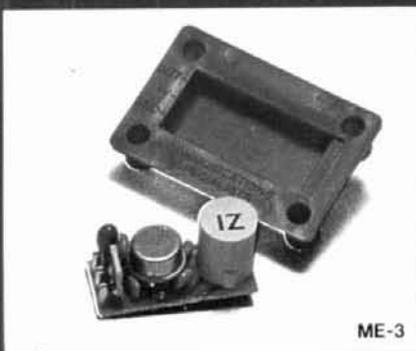

ME-3



TE-8

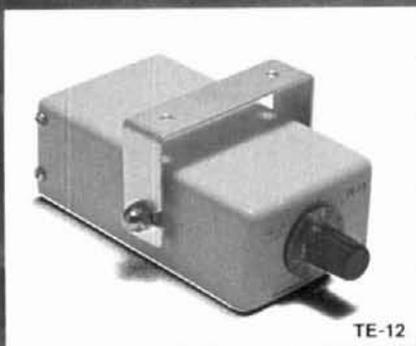

TE-12



TS-1

OF A NEW AGE.

TS-1 Sub-Audible Encoder-Decoder • Microminiature in size, 1.25" x 2.0" x .65" • Encodes and decodes simultaneously • **\$59.95** complete with K-1 element.

TS-1JR Sub-Audible Encoder-Decoder • Microminiature version of the TS-1 measuring just 1.0" x 1.25" x .65", for hand-held units • **\$79.95** complete with K-1 element.

ME-3 Sub-Audible Encoder • Microminiature in size, measures .45" x 1.1" x .6" • Instant start-up • **\$29.95** complete with K-1 element.

TE-8 Eight-Tone Sub-Audible Encoder • Measures 2.6" x 2.0" x .7" • Frequency selection made by either a pull to ground or to supply • **\$69.95** with 8 K-1 elements.

PE-2 Two-Tone Sequential Encoder for paging • Two call unit • Measures 1.25" x 2.0" x .65" • **\$49.95** with 2K-2 elements.

SD-1 Two-Tone Sequential Decoder • Frequency range is 268.5 - 2109.4 Hz • Measures 1.2" x 1.67" x .65" • Momentary output for horn relay, latched output for call light and receiver muting built-in • **\$59.95** with 2 K-2 elements.

TE-12 Twelve-Tone Sub-Audible or Burst-Tone Encoder • Frequency range is 67.0 - 263.0 Hz sub-audible or 1650 - 4200 Hz burst-tone • Measures 4.25" x 2.5" x 1.5" • **\$79.95** with 12 K-1 elements.

ST-1 Burst-Tone Encoder • Measures .95" x .5" x .5" plus K-1 measurements • Frequency range is 1650 - 4200 Hz • **\$29.95** with K-1 element.



COMMUNICATIONS SPECIALISTS

426 West Taft Avenue, Orange, CA 92667
(800) 854-0547, California residents use: (714) 998-3021





40-meter receiver for home construction

A project for those wishing to build their own high-performance superhet — it features double conversion, all-variable-diode tuning, and digital frequency readout

This article describes an easily duplicated 40-meter receiver project. The design minimizes the use of “bells and whistles” and emphasizes performance. A variety of add-on features can be incorporated in the design.

Most Amateurs have at one time or another expressed interest in building their own receiver; however, most receiver projects fail. The reasons are usually ascribed to lack of parts, time, interest, or know-how. Many receiver projects fail simply because the builder tries for too much accessory performance before the basic receiver system is operating. That is, many hours may be spent attempting to incorporate certain special-purpose features such as a fast attack agc in a detector long before the i-f and oscillator sections are operating. The builder usually loses enthusiasm for the project by being engrossed too long in the details of getting some basic function to operate in some superhuman fashion. My recommendation is to concentrate on getting the basic system operating at least to the point where signals are heard; then real improvements and add-on features will keep the inertia of the project moving along to completion.

By **M. A. Chapman, K6SDX**, 935 Elmview Drive, Encinitas, California 92024

Some receiver construction projects can fail because the builder wants long-imagined, ultra-high performance and operating flexibility. To have "everything" in a receiver is impractical. A more rational approach is to think "reasonably." Compromise the first time, learn to get the basic functional blocks operating correctly, then add on the bells and incorporate your own whistles.

some ideas

Fig. 1 illustrates the functional blocks found in a superheterodyne ssb and CW receiver. One can argue the need for an rf stage; however, to reach out and snag the really tough signals and minimize spurious mixer products, the rf stage is preferable.

The biggest single problem with the superhet are image signals also available to the i-f stage. The use of moderate Q values in the rf and mixer tuned circuits can minimize these image effects. In some operating areas, where the image signal strength is many orders of magnitude greater than the principal tuned signal, tuned traps in the antenna feedline can reduce the image-signal amplitude to acceptable levels.

The conversion of the desired signal frequency to an intermediate frequency is the responsibility of the first mixer. Mixers are nonlinear devices, which approach a power-law transfer function; because of this nonlinearity they also send along other spurious products available from the antenna to the i-f amplifiers. These products are usually second- and third-order signals but represent other noise and image sources with which your receiver must contend.

The audio stage. Audio detection normally occurs in the second mixer. The beat oscillator provides an injected carrier for the amplified i-f signal to beat or heterodyne, resulting in a detected audio signal. The signal at the second mixer output contains, in addition to the desired audio, a wide spectrum of mixer-signal components. Most of these are in the rf range and are easily bypassed to dc ground. Some audio harmonic products exist and usually represent

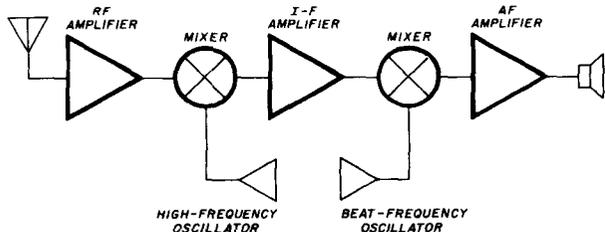


fig. 1. Block diagram of an ssb superhet receiver.

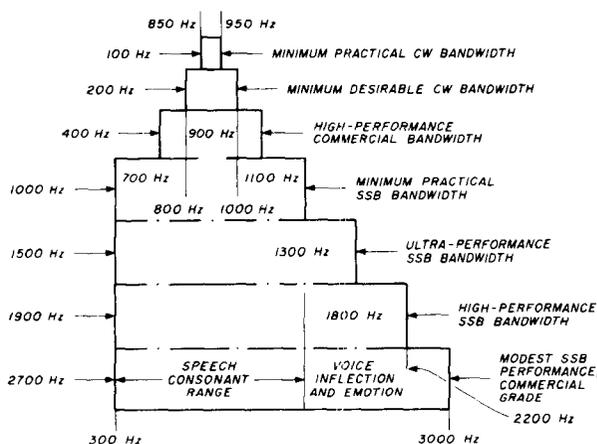


fig. 2. Summary of receiver audio bandwidth requirements for Amateur ssb and CW communications.

receiver background noise. Other noise sources are white noise from the antenna, which has an instantaneous frequency component equal to or near the audio signals of interest, and, active-device thermal noise from the receiver front end. When we speak of signal-to-noise ratio, we are usually referring to the amplitude ratio between a detected signal of say, $1 \mu\text{V}$, with the receiver input grounded or shorted. Many commercial manufacturers also perform this test in an rf-free screened room, where discrete sources can't penetrate the chassis and only the receiver internal noise is actually measured.

Restricting bandwidth. We may improve our system signal-to-noise ratio by restricting the bandwidth of detection to the smallest possible interval that will support communications. In the reception of a CW signal we're accustomed to a tone between 800 and 1000 Hz; one could visualize a system that has only a 200-Hz bandpass. Many superior receiving systems have a CW bandpass on the order of 100 Hz, centered near 900 Hz. The signal-to-noise ratios are extremely good, since only a random number of noise products fall within this bandwidth. For ssb communications, we need only a bandwidth wide enough to pass the voice consonants. Amateur receiving systems exist that employ filters limiting the audio bandwidth to approximately 1000 Hz. Various audio communications tests have shown that the average person requires audible communications bandwidths of 1500-2000 Hz. These ideas are illustrated in fig. 2.

If the useful audio bandwidth requirements for ssb communications are limited to 2 kHz the i-f bandpass need not exceed this interval; however, using LC-tuned circuits in the i-f or rf sections to achieve a

sharp-skirted 2-kHz bandpass would require almost superhuman effort. The value of bandpass can be satisfied using crystal or mechanical filters that have extremely sharp passbands, so that infringing adjacent signals don't spill into the interval of interest.

High-frequency thermal noise in the receiver front-end active devices is normally outside the filter cut-off; however, noise originating in the detector and audio frequency sections should be considered. Most RC cutoff techniques are suitable for a-m and fm broadcast reception but don't provide sufficient attenuation of undesirable audio components for ssb and CW reception. A variety of active low, high, and bandpass circuits exist for audio processing, and most readers are at least tentatively aware of their implementation in a receiver. The *ARRL Handbook* illustrates several audio-processing designs that will provide good post-detector audio processing for optimizing ssb and CW reception.

design

We'll start with **fig. 3**, a block diagram of a 40-meter superheterodyne with all-variable-diode tuning and digital-frequency readout. There's no real difference in the diagrams of **figs. 1 and 3** — only some minor digital equipment, which allows 100-Hz tuned-frequency determination. The i-f has two separate frequencies, hence dual conversion — a desirable feature for high gain and narrow-bandpass tuning.

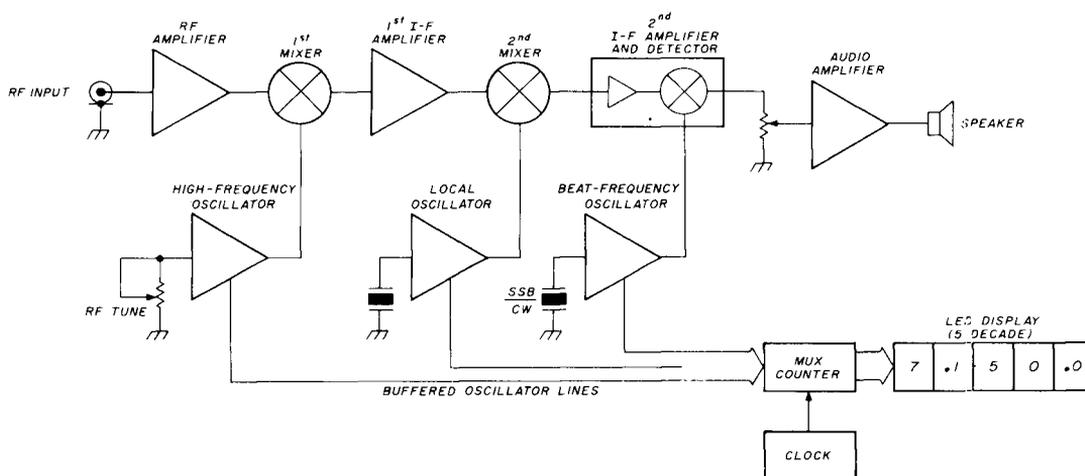


fig. 3. Block diagram of the 40-meter receiver.

Front end. The rf and first mixer tuned circuits are ganged independently from the HFO control voltage for improved signal peaking. Heterodyne oscillators are crystal controlled for stability. Over-all system bandpass shaping is achieved with a Collins mechanical filter in the second i-f. Tuning accuracy is derived

by a summation of signals from each of the principal oscillator sections and displayed using a five-decade LED arrangement.

Referring to **fig. 4**, signal preselection and initial receiver gain are achieved in the rf and first mixer stages, a major role in performance. We should have a good understanding of these circuits. The rf tuned circuit consisting of L1, C1, and VVC1 are parallel connected to Q1 gate 1. This is a parallel-tuned circuit. The 0.001 μ F capacitor in parallel with the 620k resistor puts the bottom end of L1 at ac ground, as does the 0.05- μ F capacitor on the VVC1 cathode. With a little arithmetic it's easy to see that L1 is also series resonant near 1.5 MHz, the i-f.

Parallel-tuned circuit L1, C1, VVC1 provides a high impedance to incoming signals at 7 MHz and a low impedance to signals outside the effective bandwidth.

The parallel-tuned circuit is frequency selective by providing maximum signal voltage to Q1 gate at the frequency of interest and a minimum voltage at frequencies outside the bandwidth. A similar tuned circuit L1, C2, VVC2, is on the input of Q2 gate 1. Variable-capacitance diodes VVC1 and VVC2 are ganged for peaking the incoming rf signal.

The series-tuned circuits in L1 and L2 act as image shunts for signals originating at the input. The shunting action occurs because of the low impedance to ground offered by the 1.5-MHz series-tuned circuit.

Q1 drain circuit is a simple inductive load ac coupled to Q2 input. Q2 drain load is the primary of the first i-f transformer, T1. In both cases, the drain circuits represent reasonably high ac impedances for good voltage gain. Care in the selection of the Q1 drain inductor is important, because stray winding capacitance

can have the opposite effect, *i.e.*, shunting the output signal to ac ground.

Fig. 4 illustrates the Q1 and Q1 mosfet gate bias voltages, which are set for near optimum gain even though Q2 is acting as a mixer amplifier. Because Q1 and Q2 gate currents are small, we can use high volt-

and adequate system gain is available for all but a few very exotic types whose attenuation characteristics exceed 30 dB. Nominal attenuation for the Collins unit is ≈ 10 dB. The selection of 1.9 kHz for bandpass shaping represents a compromise between CW and ssb signal reception. Superior ssb reception

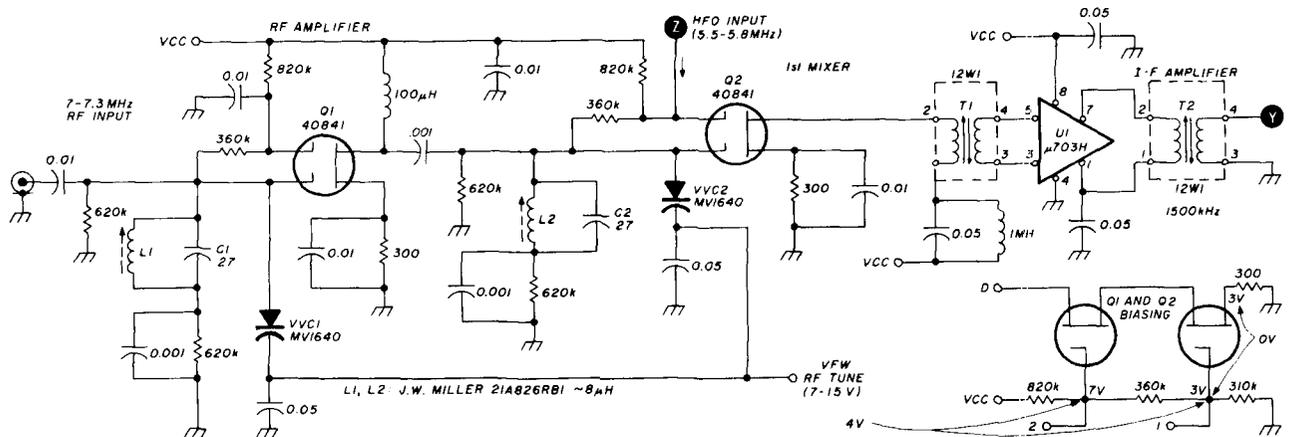


fig. 4. Rf amplifier and first-mixer schematic.

age-dividing resistance values for these circuits and minimize tuned circuit loading.

It may appear strange at first that the rf and first mixer are gate biased at the same point. Readers familiar with the principle of active device power-law mixing, where device biasing is set near the optimum nonlinear portion of the transfer curve, will realize the dual-gate mosfet acting as a cascode arrangement performs a modulation of the drain-circuit current for mixing, rather than a true nonlinear power-law mix. The mosfet can be biased for nonlinear mixing as well, and this is accomplished in the familiar circuit for Q6, the second mixer (see fig. 6).

Second i-f, detector, and BFO. Fig. 5 illustrates the i-f scheme for the second frequency conversion. The first i-f amplifier is a high-gain IC, U1, which provides about 28 dB signal gain. I-f transformers on the input and output preselect the desired signal and attenuate undesired heterodyne first mixer components. Q6, the second mixer, provides little actual system gain; the drain circuit load, T3, is the second i-f transformer. T3 includes a simple ceramic filter in the secondary for initial band shaping. This filter is inadequate for any serious ssb or CW use. The principal i-f amplification and detection occurs in U2, shown in fig. 6.

Preselected 455-kHz signals are ac coupled from T2 and internally amplified before presentation to a highly selective Collins mechanical filter for i-f bandpass shaping. I have used a Collins 1.9-kHz filter here; however, a variety of similar filters can be used,


is accomplished with this filter; however, only good CW reception is possible.

Following the bandpass amplification section of U2 is a product detector agc feedback stage. Detected audio is RC filtered on the output to decouple rf components before audio amplification. The agc feedback circuit is not connected in this design but may be incorporated as an option.

Oscillator circuits. The oscillators are shown in figs. 5, 6, and 7. Each of those oscillator circuits is a simple Colpitts arrangement followed by a fet bipolar isolation and shaper stage. The fet buffer minimizes oscillator loading and the effects of frequency distortion from the CE shaper stage. The high frequency oscillator (HFO) is tuned using a variable-capacitance diode, VVC3. The tuning voltage (V_{FV}) provides the range of reverse bias necessary for tuning the HFO for proper heterodyne-frequency conversion in the first mixer stage.

Audio amplifier and power supply. Detected audio amplification and dc power generation are shown in figs. 8 and 9. Fig. 9 also includes the scheme for deriving the V_{FV} voltage and a method of band spreading the HFO frequency for ≈ 20 kHz/revolution of the front panel tuning control potentiometer.

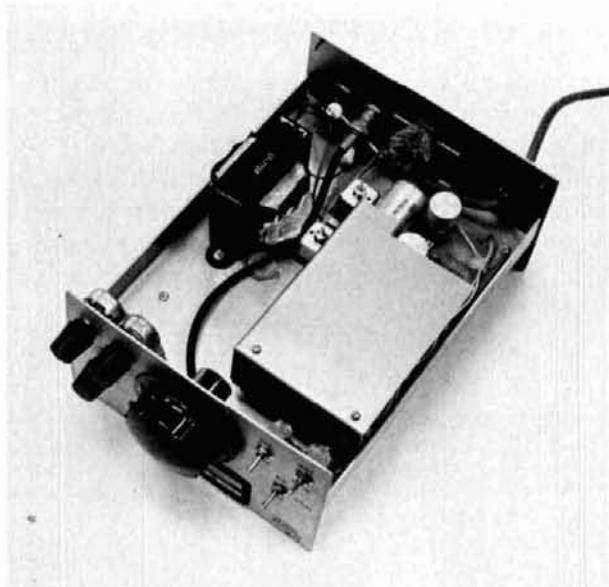Digital counter. Fig. 10 is the schematic of the digital counter. The clock from which the entire accuracy of our system depends is derived from the 10-MHz crystal oscillator, Q1, and multi-decade divided



Underchassis view of the 40-meter receiver.

by U1, U2, and U3. The combination of division in U1, U2, and U3 is 10^6 , which provides a 10-Hz clock pulse. The *QB* and *QC* strobes are used for gate and transfer timing. U4 may be thought of as a ring counter, which further divides our 10-Hz clock into four equal time periods shown on the gate timing diagram, **fig. 11**. U5 is an AND gate to control the count periods. U6 is a large, multiple three-input AND device used to select a discrete period. The oscillator input counts and guides the signal in serial sequence through to the LED display.

We can best visualize how the digital counter works by remembering that the actual tuned frequency is a summation of the various rf stage oscillator outputs. That is, if we take a typical case, the oscillators can be summed to provide our actual

tuned frequency, as in the following example:

HFO: 5.650.0 MHz
 LO: 1.045.0 MHz
 BFO: 0.456.0 MHz
 SUM: 7.151.0 MHz (display)

Our counter works exactly as shown above. It takes each oscillator pulse train and looks at it for 100 ms, transferring the gated pulse train through the final gate, U7, in sequence. If we examine, for instance, the high-frequency oscillator at some nominal case, say 5.65 MHz, we see that there are 5,650,000 counts in one second. But since we have a gate window for the HFO of only 100 ms, then only 565,000 counts are seen by U7 in any one count cycle period. The same is true of the local oscillator and BFO counts. The total number of counts is proportional to the period established by the clock timing interval, and gated as shown in the timing diagram of **fig. 11**. The count cycle periods shown in **fig. 11** are derived from the ring counter AND circuits of U4 and U5. Each complete count cycle is 250 ms wide and has four separate parts:

1. Part 1 is count oscillator 1
2. Part 2 is count oscillator 2
3. Part 3 is count oscillator 3
4. Part 4 is transfer and display

Each of these periods is sequential so that only a serial stream of counts is seen and passed by U7. U8 serves only to delete the unwanted decade before passing the train into the LED display. U8 may be deleted for six-decade presentation if the LED selected has sufficient speed.

The transfer and clear signals are derived during the fourth time periods of our count cycle and are strobed for delayed timing by the *QB* and *QC* pulses so that there is adequate internal ripple and settling time before updating the display.

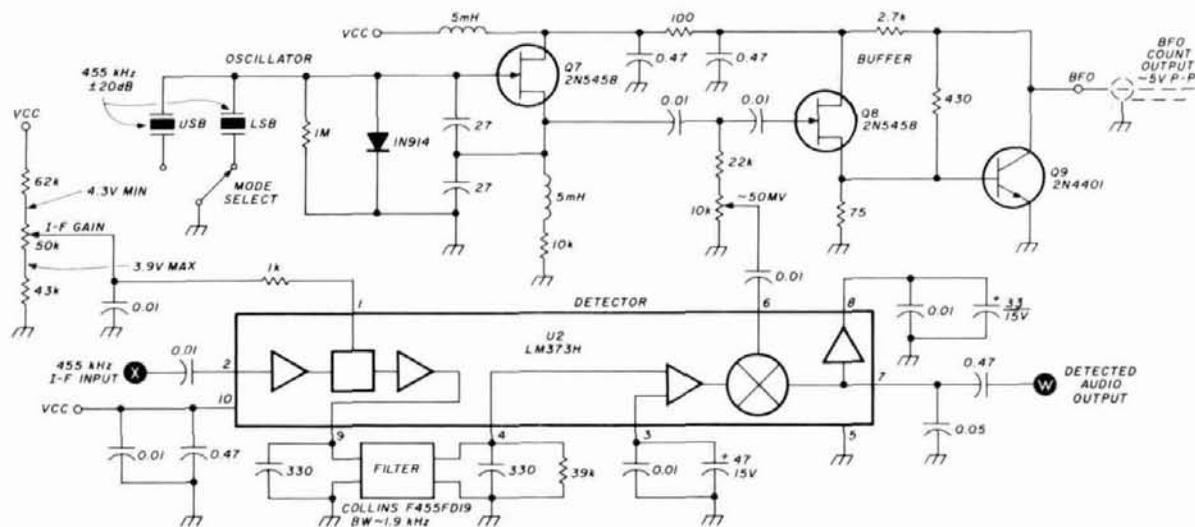


fig. 5. I-f detector and BFO schematic.

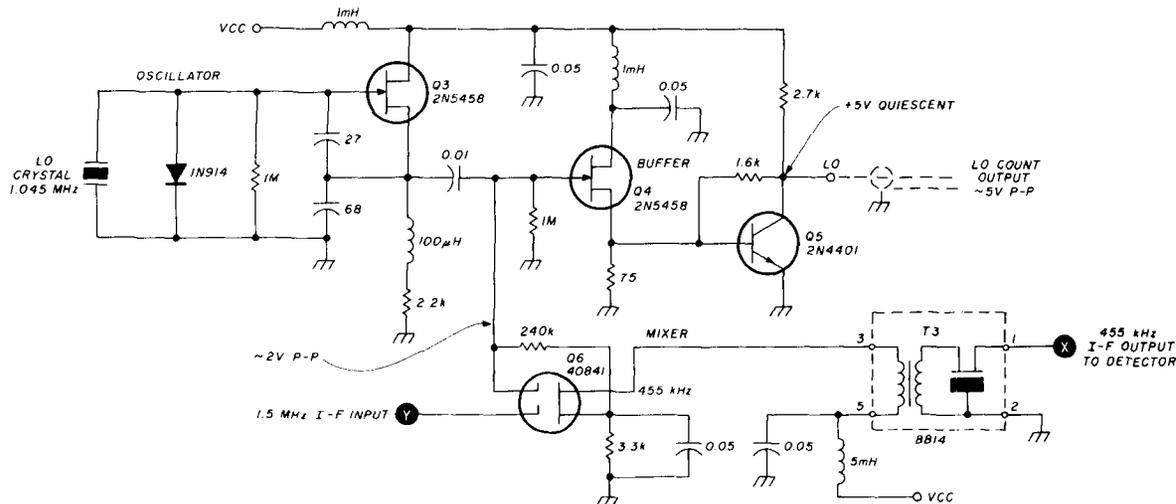


fig. 6. Local oscillator and second-mixer schematic.

U9 through U13 serve as a five-decade count, latch (transfer), and LED display. Notice that a standby switch controls the ± 5 volt bus to the LED display. The purpose here is to provide power dissipation limit control but not to interrupt the continued operation of the oscillators. This will avoid the thermal shock that receiver on-off cycling would effect and minimize oscillator drift.

construction and device selection

Construction of the rf section is on one PC-board assembly.* The digital circuits are divided between two boards, the gate segments and the LED display. There's probably an ideal assembly sequence; however, being practical, one never has all the parts available at the initial starting point and we must compromise by building up various sections of the system. Any of the subfunctional blocks on a PC board can be built and tested, or the entire board assembly can be constructed and initially aligned. †

The chassis assembly shown in the photographs should in no way represent an optimum or the only way to do it; however, your chassis approach should include effective shielding if birdie and image rejection is to be achieved. An rf shield around the gate and low-frequency clock circuitry is necessary to isolate the large 10-Hz pulse from being coupled to the audio or causing harmonic interference to the rf stages.

There's no magic in device selection. With a little

*PC boards for the receiver are available at nominal cost from the author. Send a self-addressed, stamped envelope for prices.

†A copy of the printed circuit board layouts and parts placement diagrams can be obtained by sending a self-addressed, stamped envelope to ham radio, Greenville, New Hampshire 03048.

common sense, each of the discrete devices can be replaced with an alternative that is from a similar family type.

Consider Q1, Q2, and Q3; these are RCA 40841 dual-gate mosfet devices, and there are similar devices within the RCA family and other manufacturers' lines. The key items when considering substitution here is to become familiar with the transconductance characteristics with respect to gate 1 and gate 2 to source biasing and quiescent drain current. Most of the RCA family devices have very similar biasing. Alternatives such as the 40671 and 3N187 are almost identical in operation. Care in the substitution of units such as the Motorola MFE3006, 007, and 008 types is required, because the gate 2-to-source transconductance curve differs. There are a number of mosfet enhancement types available. You should avoid these in this arrangement because of the difficulty in obtaining sufficient reverse bias to properly operate the tuned circuit VVCs.

The 2N4401 device was standardized as the work-horse NPN. This is a general-purpose and switching unit having moderate beta at low collector currents.

Any unit having an $F_b \left(\frac{f_T}{\beta} \right)$ greater than 6.25 MHz, or with similar ratings, can be used here. One needs only to put a small 5k pot in place of the present collector base feedback resistor and adjust the pot until collector saturation occurs, with the output amplitude and frequency as shown in the diagrams. For determining the alternative device feedback resistance value, remove the pot, measure its value, and use the closest standard resistor available.

The N-channel fet, 2N5458, is a general-purpose, medium-frequency device. Any reasonably similar type may be used by placing a pot in place of the source-feedback resistance and adjusting it until the output amplitudes coincide with those shown in the

diagrams. Remove the pot and install a fixed resistor with a value close to that measured on the pot. The output signal should also be examined for obvious harmonic distortion if substitutes are used, because poor mixer gain and increased receiver noise could result.

There are many VVC units that can be used provided they have similar +4 volt ratings and reasonable tuning ratios greater than two. Substitute VVCs should not be self-resonant near these operating frequen-

degeneration, since many CMOS equivalent units are inoperable above 5 MHz in the +5 volt V_{DD} condition. Type LM374 may be used in place of the LM373 by including a 1k resistor between pin 9 and V_{CC} on U2. The LM703LH may be used to replace the LM703H provided the ac decoupling cap on pin 5 is moved to pin 7.

alignment and test

Before alignment or assembly of the rf section to

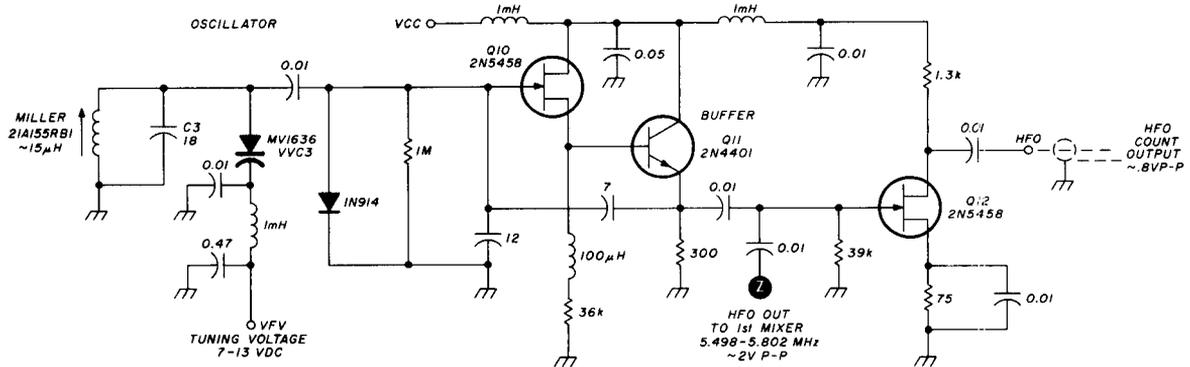


fig. 7. High-frequency-oscillator schematic.

cies. Alternative ICs to those shown exist in manufacturers' data books by various part numbers; however, the TI74490 is proprietary at the time of this writing. It is my understanding that other manufacturers expect to have equivalent devices on the mar-

ket soon (*i.e.*, Motorola, National, and Fairchild). Type 74L, 74LS, and 74H units may be used for all or any of the gate circuit elements with slight increases or decreases in current requirements for this assembly. There are CMOS replacements for the low-frequency portions of the gate circuitry; however, their use should be examined carefully to avoid frequency

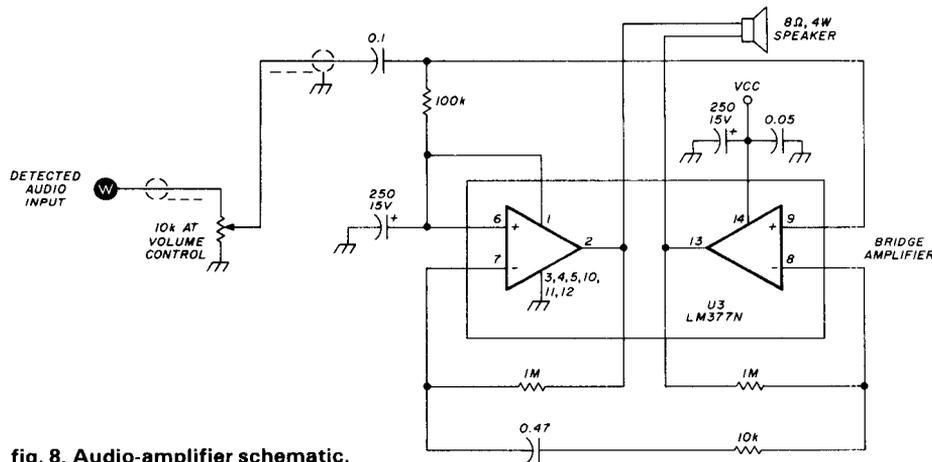


fig. 8. Audio-amplifier schematic.

the schematics. These values were obtained using a high-impedance VOM and a nominal +15 volt V_{CC} voltage. Type 7815 regulators will provide outputs of ± 5 per cent of nominal and may have a mild effect on the expected dc levels; but any circuit having dc values ± 10 per cent from those indicated should be closely scrutinized.

the schematics. These values were obtained using a high-impedance VOM and a nominal +15 volt V_{CC} voltage. Type 7815 regulators will provide outputs of ± 5 per cent of nominal and may have a mild effect on the expected dc levels; but any circuit having dc values ± 10 per cent from those indicated should be closely scrutinized.

test sequence

1. AC couple a 50-mV peak-to-peak 1-kHz signal through a 0.01- μ F capacitor to U3 pin 7. With power applied, a 2-volt P-P signal should be apparent on pin 12 with a 10-ohm resistive load substituted for a speaker load. (All signals are referenced to ground.)
2. Adjust the BFO level on U2 pin 6 for ≈ 50 mV P-P. Adjust the i-f gain control for 4.0 volts on U2 pin 1.

put where a 455-kHz signal appears and T1, T2, and T3 adjusted for maximum.

5. The HFO V_{FV} fine band-edge voltage levels should be set as shown in the schematic. With the tuning potentiometer set at the indicated levels, or using an external supply, apply ≈ 11 volts to VVC3 cathode. With V_{CC} applied, adjust L3 slug until a 5.65-MHz signal is available on Q2 gate 2. Adjust the source swamping resistor (30k) for the output amplitude shown in **fig. 7**. Traverse the tuning range and alter-

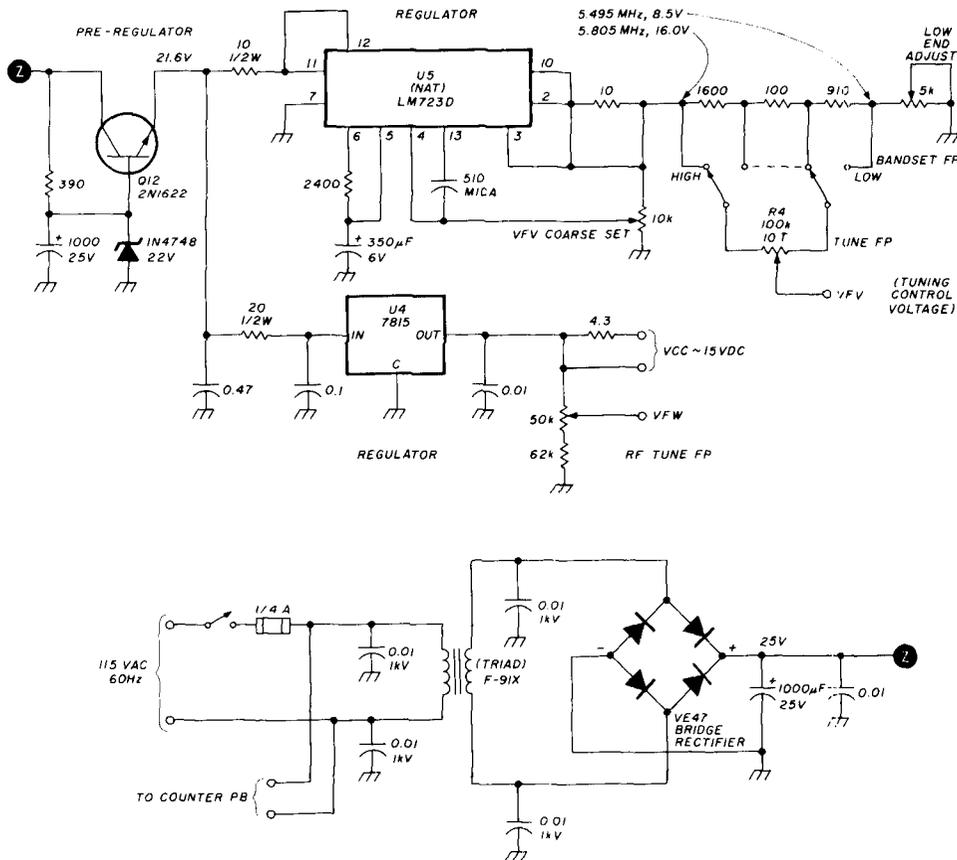


fig. 9. Power-supply schematic.

3. AC couple a 10-mV, 455-kHz rf signal (unmodulated) through a 0.01- μ F to U2 pin 2. Adjust the 455-kHz rf signal for 1 kHz detected audio on U2 pin 7. The amplitude of the detected audio should be 60 mV P-P; detuned noise should be ≈ 5 mV P-P. A verification of i-f gain control should be made by varying the voltage on U2 pin 1 from ≈ 3.9 to 4.5 volts. Maximum gain should occur at ≈ 4.0 volts.
3. AC couple a 455-kHz rf signal of 10 mV into T3 pin 3. Peak T3 for maximum detected audio at U2 pin 7.
4. AC couple a 1.5-MHz rf signal of 100 μ V into T1 pin 2 and peak T1, T2, and T3 for maximum. Detected audio signal on U2 pin 7 should be approximately 200 mV P-P. The signal may also be monitored on U2 in-

nate the bandset switch so that the output signal frequency is 5.498 MHz at the low end and 5.802 MHz at the high end of the HFO. Monitoring should occur at Q2 gate 2.

6. AC couple a 7.15-MHz signal of 100 μ V into Q2 gate 1 and monitor the audio output while adjusting the HFO for detector conversion. After obtaining detected audio from U2 or U3, with the HFO set for conversion of 7.15-MHz signals, repeat T1, T2, and T3 for maximum. Monitoring the rf envelope on U2 pin 2 may provide an easier point for verification of optimum alignment.
7. AC couple a 30- μ V signal of 7.15 MHz into Q1 gate 1. Adjust the HFO frequency for a maximum 455-kHz

envelope. Adjust the rf tuning pot for maximum-detected audio or rf envelope. Inject a 5- μ V signal into the antenna input, and peak L1 and L2 for maximum detected signal; then go back through all tuning elements and peak for maximum. The peak detected rf envelope at U2, for a 1- μ V input of 7.15 MHz, should be 60 mV P-P (\approx 95 dB).

as shown in **fig. 11**; however, scope monitoring of the logic pins should indicate that a pulse exists.

2. Inject a 1-MHz rf signal of 100 mV into oscillator no. 3 input, and monitor U7 pin 12 and U8 for oscillator clock train output occurring at regular 250-ms intervals. If the display board is available, temporarily

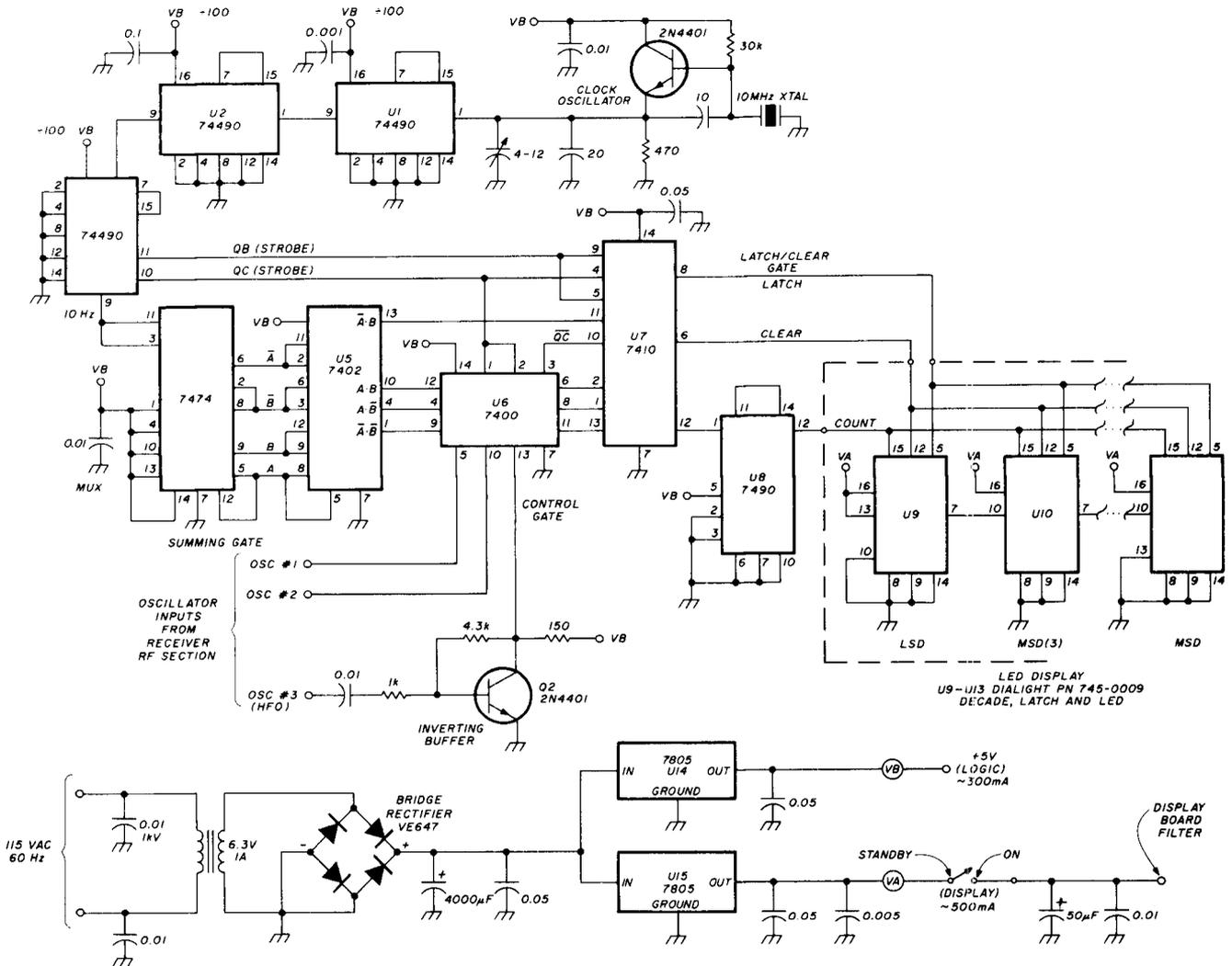


fig. 10. Digital-counter and display schematic.

8. Final alignment should occur after the rf and digital boards have been installed on the chassis, because the effects of stray capacitance will shift all of the oscillators and rf-tuned circuits slightly. This final alignment should occur with rf input signals in the order of 3 μ V.

digital-circuit testing

1. Apply power to the gate control board and monitor the frequency of the quiescent states of the logic circuits, as shown in **fig. 10**. It may not be possible to verify the various timing pulses relative to each other

jumper the latch and clear lines. A display of 1.000.0 should result. Inverted latch and clear lines, or unconnected inputs to the display, will result in LED garbage, or an output of 0.000.0. On occasion, when power is first applied to the display, a residual numerical value will appear. In normal operation the next count cycle coming up (250 ms later) should clear the erroneous display.

3. The 10-MHz clock should be trimmed for the closest possible accuracy by zero beating against WWV at 10 MHz, using a separate receiver and a simple link coupling around the clock oscillator.

hints and kinks

Accuracy in a digital system is defined as time base accuracy ± 1 digit. This accuracy must include aging and temperature stability. The digital-counter accuracy will then be as accurate as the basic 10-MHz clock oscillator. All crystal oscillators have both long- and short-term drifts due either to aging, temperature, or circuit-component changes. The display accuracy then will drift with the crystal-oscillator drift.

Without temperature compensation you can expect to have drifts in the order of 5 ppm/ $^{\circ}$ C plus additional aging drifts of perhaps 10 ppm/year. The net result is that faith in the absolute accuracy of the LSD of this counter is wasted. It might impress visitors, but without constant recalibration of the 10-MHz oscillators against WWV or other prime standard at regular intervals, the LSD is only a guess. The actual consistent counter display accuracy is to the closest kilohertz over any significant period of time. This could be improved to ± 200 Hz ± 1 digit by using TCO (temperature-compensated oscillator) techniques.

Selection of the BFO crystals can be made by measuring the bandpass mechanical filter for the upper and lower 20-dB points. The BFO crystal frequency should coincide with these measured values within ~ 50 Hz. Most suppliers will furnish the filter with this information, marked either on the filter or with the shipping data package, for a small fee. Significant errors in the BFO frequency will degrade ssb detection.

In the local oscillator and BFO circuits, the amplitude of the output signals from the isolation and CE shaper will vary with different crystal types. Excessive CE saturation will cause a 10-Hz clock pulse to be coupled into the V_{CC} line and will result in pinging of the detected audio. Conversely, low outputs will not stimulate the gate levels required for proper counting.

The suggested cure is to temporarily install a 5k

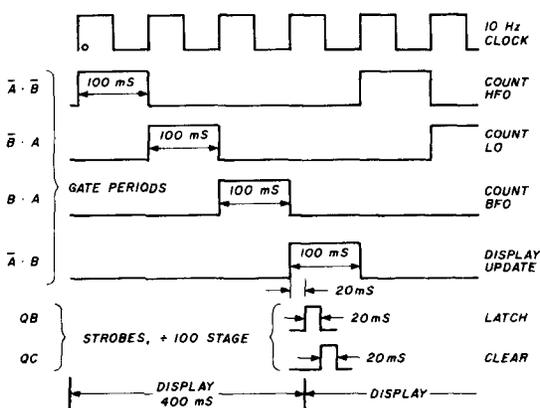


fig. 11. Digital-counter timing diagram.

pot in the 2N4401 collector to V_{CC} load position. Adjust each of these until the amplitude of the output signal is just high enough to stimulate the gate input but will not keep the collector circuit in saturation for a period that allows the 10-Hz signal to load the V_{CC} line. The schematic illustrates the peak-to-peak signal levels I found achieved these goals.

A 100-kHz clock oscillating crystal may be used as a substitute for the 10-MHz unit in fig. 11 by deleting the second divide-by-100 (74490) stage. Some adjustment in the oscillator bias values may be required, and counter accuracy will be limited by your ability to trim the oscillator frequency properly.

improvement suggestions

The following are areas of individual user improvement:

1. RF gain. Wide dynamic range is necessary to meet the demands of the Amateur-band receiving environment. Signal levels vary from parts of a microvolt to perhaps a millivolt — a three-decade range. The front end of this receiver is optimized for maximum transconductance (gain). Strong signals $> 100 \mu\text{V}$ will cause channel saturation in the rf- and first-mixer stages. Two easily implemented methods of controlled rf gain are available to the builder:

- source current limiting:** use a 2k pot in the source lead instead of a 300-ohm resistor.
- gate-2 control:** lift the gate from the board and add a bypassed flying lead to a 0-5 Vdc voltage.

2. Agc. Positive agc voltage is available on U2 pin 8, proportional to detected audio. The quiescent value, ~ 4.0 Vdc, is very close to the i-f gain maximum value. As the audio level from the U2 audio mixer stage increases, this agc voltage may be fed through a 1-k resistor to U2 pin 1.

Agc voltage may be fed through a 1-k resistor to U2 pin 1. The i-f gain circuit must be open or disconnected for the agc feedback system to operate.

3. Variable bandwidths. The addition of a diode switch and other Collins-type filters will allow optimization for both CW and ssb reception.

4. HFO stiffness. Thermal — physical isolation of U5 will improve V_{FV} regulation and drift/ $^{\circ}$ C rate; transient — increased beta characteristics for Q12 will aid in improved ripple rejection for both the HFO and general receiver operation.

5. Images. A simple series-tuned 1.5-MHz shunt in the antenna input will improve the image rejection by 20 dB. Provisions are on the PC board for the installation of the components.


ham radio

Full Features and Superior Performance ST-6000 RTTY DEMODULATOR

Select Rx & Tx Shifts
Accurately Tuned Rx Filters
Crystal Controlled Tx Tones
True Transceive Operation

Invert Both Rx Demod,
and Tx Tones

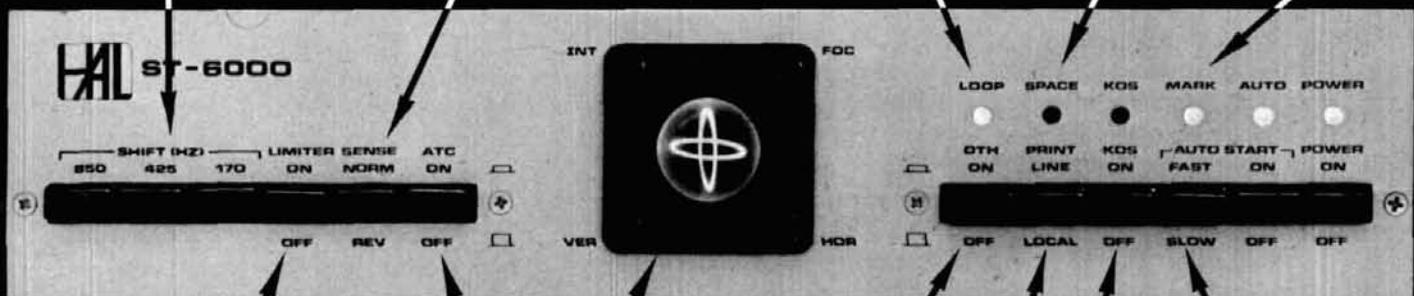Data Status Indicators
Loop 1 Post-Autostart Pre-Autostart



Hard-Limiting [FM]
or
Non-Limiting [AM]
Reception

Correct for
Bias Distortion


Correct For
Multi-Path Distortion

Local Loop Operation

Autostart with:
◦ Motor Control
◦ Mark Hold
◦ Antispace

Tuning Oscilloscope
[Front Panel Controls]
Meter Indicator Option
Also Available

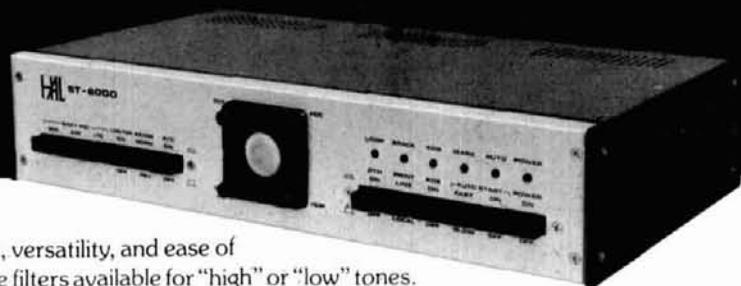Automatic Tx/Rx Station
Control with Keyboard
Operated Switch [KOS]



Why not have the best?

The HAL ST-6000 Demodulator offers outstanding performance, versatility, and ease of operation. The Receive Demodulator features multiple-pole active filters available for "high" or "low" tones. These filters are frequency-matched to the transmit tone crystals for true transceive operation. Input bandpass filters, discriminator filters, and post-detection filters are carefully designed and tested for optimum weak-signal recovery. The ST-6000 has an internal loop power supply, 2 loop keyers, RS-232, MIL-188C, and CMOS data I/O, and rear panel connections to data and control circuits for connection to UART and computer devices. Use it with the HAL DS-3000 KSR for the best in RTTY performance.

\$595.00

Write today for HAL's latest RTTY catalog.



HAL COMMUNICATIONS CORP.
Box 365
Urbana, Illinois 61801
217-367-7373

For our Overseas customers:
see HAL equipment at:
Richter & Co.; Hannover
I.E.C. Interrelco; Bissone
Vicom Imports; Auburn, Vic., Australia

CW operator's PAL

An accessory
for CW operators
that reduces difficulties
with interference,
noise, and fading

Described in this article is a multifunction magic box, called a *Pal*, which I designed to relieve some of the operating problems faced by CW operators. Some of those problems are outlined below. The *Pal* is based upon old, well-known techniques; it is novel primarily because it merges — and modernizes — past solutions to these problems:

1. Many Amateurs endure listening to CW signals but enjoy listening to telegraph sounders. Most Amateurs own or can obtain sounders, which are now obsolete, and old-timers usually retain a nostalgic interest in telegraphy.
2. Received signals vary in pitch, due to frequency drift at the transmitter or receiver, which requires frequent readjustment of the receiver's BFO. Chirps due to poor transmitter power-supply regulation, or jumps due to sudden line voltage changes, can also cause problems for the CW operator.
3. Received signals vary in volume due to fading and due to variable propagation conditions; sometimes gain changes at the transmitter or receiver can occur during warm-up periods. Changing audio volume forces the receiving operator to frequently readjust the gain control to maintain normal volume.
4. Received signals often include annoying interference from adjacent frequencies, even with very selective receivers.
5. Received signals incur variable background noise due to a combination of atmospheric, static, and

manmade electrical noise; noise limiters help but don't eliminate all noise.

6. Transmitter operators are said to have poor "fists" when they send imperfect code characters with straight or semi-automatic keys. Poor sending can often be attributed to inability to monitor a transmitter not equipped with sidetone output.

7. Many Amateurs don't own a code-practice set. Such a set is more than a means of learning and teaching code; it permits high-speed, off-the-air sending practice and proper adjustment of a semi-automatic key.

circuit description

In the *Pal* (fig. 1), a rectifier-filter circuit is used to actuate a telegraph sounder; a tone oscillator-amplifier is used to provide a code-practice set. Both circuits are used to improve CW reception and transmission. The input voltage to drive the *Pal* is derived from either the receiver (J1) or a voltage picked off the transmitter (J2).


The external power supply may be a 12-volt storage battery, eight dry cells in series, a regulated 12-volt power supply (such as Radio Shack's no. 22-124), or a homemade unregulated power supply which delivers 12-15 volts at about 1 ampere. An internal 9-volt transistor radio battery of moderate size will suffice for code practice.

An ac-connected power supply should have a switch and an indicator lamp — either a small 120-volt type across the switched line or a 6.3-volt, 0.15-ampere pilot lamp in series with a 40-50 ohm, 2-watt resistor across the 12-volt output. Lamp types 40 (screw base) and 47 (bayonet base) are suitable.

construction

Nothing in this circuit is critical. The circuits may be breadboarded and simply placed in a box. A 5 × 5 × 7 inch (12 × 12 × 18 cm) metal box is recommended because it will easily house all the parts except for the sounder (on top) and the key.

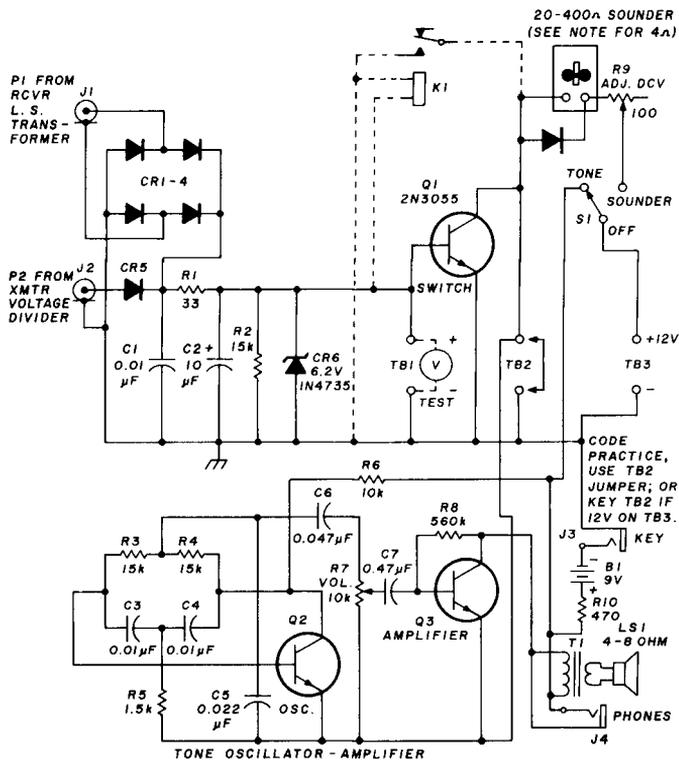By Carleton F. Maylott, W2YE, 279 Cadman Drive, Williamsville, New York 14221



NOTE: ALL DIODES 100 PIV, 1A SILICON.

fig. 1. Schematic diagram of the CW operator's Pal. Q1 is preferred and relay K1 (Radio Shack 275-004) is optional because Q1 is more sensitive; it needs less input and perhaps no step-up transformer if fed directly from a high-impedance phone jack instead of a voice-coil input. Relay K1 can be used to operate a 4-ohm sounder (1.5 Volts, 375 mA) by replacing the latter in the given circuit, setting R9 to 500 ohms (or using a 560-ohm, 1-watt fixed resistor), and putting K1 contacts in series with the sounder and a large dry cell or a 27-ohm 10-watt resistor in the 12-volt line. Transistor Q2 is an NPN low-power device.

sounder operation

Any telegraph sounder with 20 to 400 ohms resistance is usable, but the power supply voltage must be dropped with a series resistance. For example, if a 20-ohm sounder operates at 3 volts and 0.15 ampere, the necessary 9-volt drop requires 60 ohms resistance at 1.35 watt, so a 56-ohm, 2-watt resistor will do. Obviously, if various sounders are to be used, an adjustable resistor or rheostat must be used; a common 12½-watt, 100- or 500-ohm rheostat is a good choice.

A communications receiver usually delivers only a fraction of a volt to a 4-8 ohm loudspeaker. The CW-dc converter must have a higher ac input voltage to deliver about 0.8 volt to a switching transistor or 5 volts to a sensitive relay. The dc output voltage of a full-wave bridge rectifier is, theoretically, 90 per cent of the input ac voltage. Under these conditions, it is necessary to use a step-up transformer unless the output from a high-impedance phone jack is suffi-

cient. The step-up transformer can be made from a filament or output transformer used backwards and shunted across the voice coil of the speaker.

A switch in series with the voice coil will disable the loudspeaker while the Pal is in use, thus avoiding confusion between CW tones and sounder clicks. Before disabling the loudspeaker, advance the receiver gain control to a point somewhat beyond the triggering level. A lower level invites drop-out during fading, and a higher level invites atmospheric static and manmade noise, which seldom affects the sounder under normal operating conditions.

The pitch and volume of the original CW note are of little importance during sounder operation; in fact, the note may be much higher or lower than desired during normal CW operation. Since pitch is now unimportant, you may zero-beat or drop the frequency of an undesired signal so that only the desired signal passes efficiently through the receiver-to-converter transformer. If a phone signal happens to be received, the sounder will faithfully click on voice peaks; no harm is done, and the effect is rather amusing.

tone-oscillator operation

A center-off switch (to avoid needless energy loss) is used to replace the sounder with a tone oscillator, amplifier, and loudspeaker. The converter circuit is unchanged and the operating procedure is much the same. The pitch of the new CW tone is fixed by the circuit constants; the volume is fixed after a preliminary setting of the gain control. Pitch and volume are now unrelated to receiver output; they should never need readjustment regardless of fading, interference, or noise.

During tuneup, there are two tones because there are two loudspeakers with different inputs. Thereafter, confusion between the fixed and variable tones may be avoided by opening the receiver loudspeaker disabling switch.

transmitter operation

The sidetone for transmitter monitoring is produced in much the same way as in the CW-to-CW conversion just described. A separate half-wave rectifier is connected to a voltage divider shunted across the transmitter output. The half-wave rectifier and the bridge rectifier share a common output and their back-to-back polarity connection avoids interaction unless both inputs are active. Fortunately, transmitter and receiver functions do not occur simultaneously, hence the Pal can serve both functions at the same time without changing connections. Thus, both plugs can remain in both jacks (phono and coaxial) regardless of the choice or number of functions desired.

It is easy to obtain the rf voltage needed for the half-wave rectifier input; a typical transmitter which delivers 200 watts to a 50-ohm load also delivers 2 amperes at 100 volts. Even a 50-watt transmitter can deliver 50 volts, of which only a small fraction is required. The proper voltage divider step-down ratio is, therefore, rather large. It is determined easily by experiment but not by calculation. It is useless to know that a half-wave rectifier, in the absence of voltage drop, has a dc output voltage which is 45 per cent of the ac input voltage. Variables include transmitter power, voltage divider resistance, rectifier load, rectifier voltage drop, and rectifier circuitry.

Under these conditions, you can connect the transmitter to a dummy antenna and gradually raise the tap on the voltage divider until the desired dc voltage appears across the relay coil or the switching transistor base-to-emitter input. The dc voltage should not exceed 6 volts or 1 volt, respectively¹.

The voltage divider should be located in or near the transmitter, if possible, to minimize any effect on the VSWR. The divider might be housed in a can, like a filter, in series with a line from the transmitter to the *Pal*. In any case, a short jumper made from RG-8/U or RG-58/U coaxial cable may be provided with PL-259 plugs for attachment to SO-239 jacks at both ends. The transmitter antenna jack may be provided with a T-adaptor which has one male and two female outlets (amphenol M-358), one of which will accommodate the jumper.

code-practice operation

There are at least three possible ways of keying the *Pal* as a code-practice oscillator. The key may be connected across the normally open relay contacts or the collector-to-emitter leads of the switching transistor. If you wish, a small battery may be placed in series with the key to the phone jack used for normal receiver connection, making sure that the plug tip is positive.

A third way of keying the practice oscillator replaces the external 12-volt power supply with an internal 9-volt transistor battery in series with a key jack, thus providing greater portability.

conclusion

There you have it, a multifunction magic CW box, which is a *Pal* to me; other amateurs should be able to obtain similar results. I wish to thank W2SSJ and his correspondents, W9KSR and W9YZE, for their suggestions on CW-to-telegraph converters.

reference

1. Lew McCoy, "An RF Actuated CW Monitor," *QST*, November, 1968, page 39, or *The Radio Amateur's Handbook*, 1971, page 183.

ham radio

SEE YOU IN DAYTON



COMPLETE KITS: CONSISTING OF EVERY ESSENTIAL PART NEEDED TO MAKE YOUR COUNTER COMPLETE. **HAL-600A** 7-DIGIT COUNTER WITH FREQUENCY RANGE OF ZERO TO 600 MHz. FEATURES TWO INPUTS: ONE FOR LOW FREQUENCY AND ONE FOR HIGH FREQUENCY; AUTOMATIC ZERO SUPPRESSION. TIME BASE IS 1.0 SEC OR .1 SEC GATE WITH OPTIONAL 10 SEC GATE AVAILABLE. ACCURACY $\pm .001\%$, UTILIZES 10-MHz CRYSTAL 5 PPM.

COMPLETE KIT \$129

HAL-300A 7-DIGIT COUNTER WITH FREQUENCY RANGE OF ZERO TO 300 MHz. FEATURES TWO INPUTS: ONE FOR LOW FREQUENCY AND ONE FOR HIGH FREQUENCY; AUTOMATIC ZERO SUPPRESSION. TIME BASE IS 1.0 SEC OR .1 SEC GATE WITH OPTIONAL 10 SEC GATE AVAILABLE. ACCURACY $\pm .001\%$, UTILIZES 10-MHz CRYSTAL 5 PPM.

COMPLETE KIT \$109

HAL-50A 8-DIGIT COUNTER WITH FREQUENCY RANGE OF ZERO TO 50 MHz OR BETTER. AUTOMATIC DECIMAL POINT, ZERO SUPPRESSION UPON DEMAND. FEATURES TWO INPUTS: ONE FOR LOW FREQUENCY INPUT, AND ONE ON PANEL FOR USE WITH ANY INTERNALLY MOUNTED HALTRONIX PRE-SCALER FOR WHICH PROVISIONS HAVE ALREADY BEEN MADE. 1.0 SEC AND .1 SEC TIME GATES. ACCURACY $\pm .001\%$. UTILIZES 10-MHz CRYSTAL 5 PPM.

COMPLETE KIT \$109

PRE-SCALER KITS

HAL 300 PRE \$19.95

(Pre-drilled G-10 board and all components)

HAL 300 A/PRE \$24.95

(Same as above but with preamp)

HAL 600 PRE \$34.95

(Pre-drilled G-10 board and all components)

HAL 600 A/PRE \$39.95

(Same as above but with preamp)

TOUCH TONE DECODER KIT

HIGHLY STABLE DECODER KIT. COMES WITH 2 SIDED, PLATED THRU AND SOLDER FLOWED G-10 PC BOARD, 7.567" s, 2-7402, AND ALL ELECTRONIC COMPONENTS. BOARD MEASURES 3-1/2 x 5-1/2 INCHES. HAS 12 LINES OUT. ONLY \$39.95

DELUXE 12-BUTTON TOUCHTONE ENCODER KIT utilizing the new ICM 7206 chip. Provides both VISUAL AND AUDIO indications! Comes with its own two-tone anodized aluminum cabinet. Measures only 2-3/4" x 3-3/4". Complete with Touch-Tone pad, board, crystal, chip and all necessary components to finish the kit.

PRICED AT \$29.95

For those who wish to mount the encoder in a hand-held unit, the PC board measures only 9/16" x 1-3/4". This partial kit with PC board, crystal, chip and components.

PRICED AT \$14.95

ACCUKEYER (KIT) THIS ACCUKEYER IS A REVISED VERSION OF THE VERY POPULAR WB4VVF ACCUKEYER ORIGINALLY DESCRIBED BY JAMES GARRETT, IN QST MAGAZINE AND THE 1975 RADIO AMATEUR'S HANDBOOK. \$16.95

ACCUKEYER — MEMORY OPTION KIT THIS ACCUKEYER MEMORY KIT PROVIDES A SIMPLE, LOW COST METHOD OF ADDING MEMORY CAPABILITY TO THE WB4VVF ACCUKEYER. WHILE DESIGNED FOR DIRECT ATTACHMENT TO THE ABOVE ACCUKEYER, IT CAN ALSO BE ATTACHED TO ANY STANDARD ACCUKEYER BOARD WITH LITTLE DIFFICULTY. \$16.95

6-DIGIT CLOCK • 12/24 HOUR

COMPLETE KIT CONSISTING OF 2 PC G-10 PRE-DRILLED PC BOARDS, 1 CLOCK CHIP, 6 FND 359 READOUTS, 13 TRANSISTORS, 3 CAPS, 9 RESISTORS, 5 DIODES, 3 PUSH-BUTTON SWITCHES, POWER TRANSFORMER AND INSTRUCTIONS. DON'T BE FOOLED BY PARTIAL KITS WHERE YOU HAVE TO BUY EVERYTHING EXTRA.

PRICED AT \$12.95

CLOCK CASE Available and will fit any one of the above clocks. Regular Price ... \$6.50 But Only \$4.50 when bought with clock.

SIX-DIGIT ALARM CLOCK KIT for home, camper, RV, or field-day use. Operates on 12-volt AC or DC, and has its own 60-Hz time base on the board. Complete with all electronic components and two-piece, pre-drilled PC boards. Board size 4" x 3". Complete with speaker and switches. If operated on DC, there is nothing more to buy.

PRICED AT \$16.95

Twelve-volt AC line cord for those who wish to operate the clock from 110-volt AC. \$2.50

SHIPPING INFORMATION

ORDERS OVER \$15.00 WILL BE SHIPPED POSTPAID EXCEPT ON ITEMS WHERE ADDITIONAL CHARGES ARE REQUESTED. ON ORDERS LESS THAN \$15.00 PLEASE INCLUDE ADDITIONAL \$1.00 FOR HANDLING AND MAILING CHARGES. SEND SASE FOR FREE FLYER.



"HAL"
HAROLD C. NOWLAND
W8ZXH



HAL-TRONIX
P. O. BOX 1101
SOUTHGATE, MICH. 48195
PHONE (313) 285-1782

calculator-aided propagation predictions

An automated approach
to propagation predictions
by using
a programmable calculator
and published
ionospheric predictions

Those people who use high-frequency propagation predictions know them to be accurate. Commercial interests use the predictions as part of the normal course of business. DX contest operators use them, among other things, to determine band openings into high-density population areas to establish a high contact per hour ratio before skip lengthens into the rest of their country. DXCC operators use them to determine at what time and on what band a specific long-haul station will be coming through so as not to waste time when no path is possible.

Propagation predictions became practical after World War II through the work of the Central Radio Propagation Laboratory of the National Bureau of Standards. In 1947, Newell Atwood, W3KTR, published an article¹ describing a method whereby CRPL propagation prediction overlay charts were moved over a basic world map, showing what areas of the world were open from a home station for any band and time of day. That information was issued by CRPL three months in advance and proved very useful, as well as accurate.

Much has been written over the years on the subject. At least one magazine² devoted a complete issue to the subject, while another³ devoted a monthly article for many months to prediction techniques and their results. Finally the ultimate was reached in 1971 when *Telecommunications Research*

and *Engineering Report 13* was issued by the United States Department of Commerce.⁴ The report consists of four volumes on ionospheric predictions covering all frequencies, time of day, and day of the year, and by interpolation, for any solar activity with a Zurich sunspot number from 10 to 160.

The use of these predictions is explained in Volume 1, but a detailed description was published by Jerry Hall, K1PLP.⁵ Every Amateur interested in DX should have a copy of these four volumes in his library. The use of these predictions is tedious and time consuming, but well worth the effort. First, let me sell you on their importance by illustrating how you can use the prediction techniques to get that long-haul DXpedition when others can't. Then I will explain how I've streamlined the use of them, and made it more fun by use of an SR52 computing calculator with the PC100A printer.

The programs discussed in this article are directly related to the TI-58/59, newer models of the SR52/SR56; by use of the equations and flow charts, they are applicable to the HP-25 and similar calculators. The PC100A printer is a desirable luxury, but is not necessary to the functioning of these programs.

Back in December, 1975, the Northern California DX Foundation sponsored a DXpedition to CR9AK in Macao, a country I needed. Macao is a long way from New Jersey; since I work from 8:15 AM to 5 PM, I had to know when I could expect to work him — to increase the possibility of being there when his signals were coming through.

The sunspot cycle had not reached bottom in 1975, but it was pretty low, around a Zurich sunspot number of 30. Under those conditions, when could CR9AK be workable in New Jersey, and on what band? A propagation prediction using *Report 13* was performed (see **fig. 1**) and, much to my dismay, there was no opening above 13.8 MHz via the short path. Happily, though, there were two openings via long path, one at 2400 GMT (2400Z) with an MUF of

By Henry G. Elwell, N4UH, Box 20G, Route 2,
Cleveland, North Carolina 27013

14.4 MHz and a second one from 1100Z to almost 1600Z with an MUF peaking to 21.7 MHz.

Unfortunately, that particular week of the DXpedition found the ionosphere very unsettled and nothing was heard on either opening the first three days of the DXpedition; the beam was pointed long path, while I listened on 20-meter CW. Little was heard from anyplace that week. On the fourth day, a very weak pileup was heard around 14025 kHz; it had to be CR9AK. When you are desperate you have to try, so a short call was given after the pileup stood by; he came back to me with a "surprised to hear East Coast." We exchanged signal reports, I was 459, and back to the faint (in New Jersey) pileup he went. Although CR9AK made almost 4000 contacts in 71 countries, few of them were with the East Coast. My working him was part luck, but also planning, as finding him would have been hit and miss without the prediction.

In April, 1976, Bill Rindone, WB7ABK, in cooperation with the NCDX Foundation, visited Christmas Island in the Indian Ocean, operating as VK9XX. Christmas Island is 3700 km farther from New Jersey than Macao. In addition, the Zurich sunspot number was lower than it had been in December — so low that I used 10 to allow me to use *Report 13*, Volume 2 directly. Again, when should I listen for him and on what band? A propagation prediction was made, (see **fig. 2**) and I had several choices, both short and long path on 20 meters. I'll take the short path anytime I can, as the distance is about 18,300 vs 26,000 km (9900 vs 14,000 miles) for the short and long paths respectively to Christmas Island. With a TH6DX antenna at 15.2 meters (50 feet), the signal makes quite a few hops at even 18,300 km (9900 miles).

From **fig. 2**, you can see that the opening at 2400Z is sharply peaked. I have not been very successful with that type of opening and concentrated on the

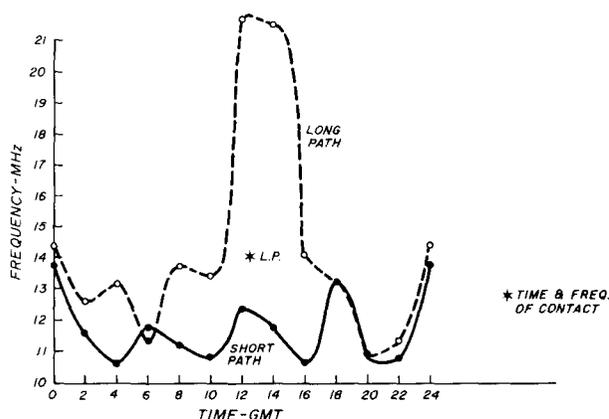


fig. 1. Propagation prediction for the long and short paths to Macao. The prediction showed that for December, 1975, there was no 20-meter short-path opening. However, the long path was open, even as high as 15 meters.

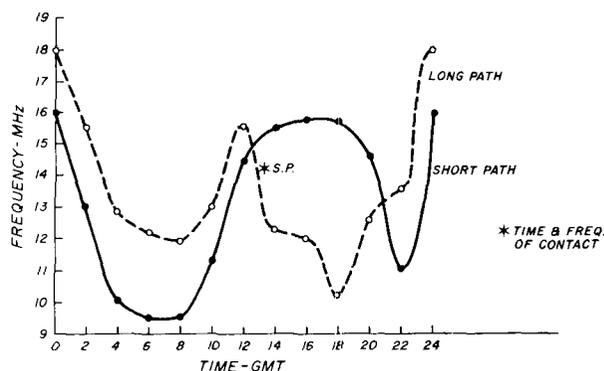


fig. 2. A similar propagation prediction for the path from New Jersey to Christmas Island in April of 1976.

opening at 1200Z. This worked out quite well — I got VK9XX shortly after the band opened on 20-meter ssb before the pack became aware of him. I left for work only 20 minutes after my normal departure time.

I know that many top DXers rely only on their experience, patience, and operating skill to snag elusive DX. But, when it comes to a DXpedition, you know he's going to be continually working. So, why not take advantage of all the miracles of modern science to get him!

Propagation predictions using *Report 13* and reference 5 are easy to do, but they take a long time. You must first draw on transparent paper a great circle route between your home and the desired DX location and then establish an ionospheric control area distance at both ends of the great circle. The great circle is then over-layed on the MUF (Zero) F_2 map for the solar activity level, month and time desired, and the MUFs at the two recorded locations. The process is repeated using the MUF (4000) F_2 .

The F_2 MUF is then determined by means of a chart relating the (zero) and (4000) MUFs, which tends to decrease the MUF for all distances greater than 4000 kilometers. Next, the process is repeated for the MUF (2000) E, as some propagation may be by the E layer as well as the F_2 layer. Actually, the MUF (2000) E exercise is mainly for distances less than 2500 kilometers. By cranking the numbers and filling in the recommended work sheets, you arrive at an MUF for every two hours during the day. A plot such as **fig. 1** or **2** can then be drawn and analyzed. However, if the Zurich sunspot number is not 10, 110, or 160, which are Volumes 2, 3, and 4, the whole thing must be repeated and an interpolation made for the desired sunspot number. It's easy, it's all explained, but it is tedious. I'm sure the dogwork inhibits many from using the technique. Let me repeat: it's well worth it to give you a competitive advantage against the big guns.

Hang in there, though, if you're lazy like me. Pare the work to the bone. Being hams, we are highly op-

LATITUDE	22.0	PRT
LONGITUDE	-115.0	PRT
NAUTICAL MILES	7219.2	PRT
BEARING	343.1	PRT
KILOMETERS	13369.9	PRT

fig. 3. Example of the printout for the great-circle distance (both in nautical miles and kilometers) and bearing to the desired DX station.

timistic when it comes to band openings. Why not ignore the MUF (Zero) F_2 , which tends to decrease the MUF anyhow, forget the MUF (2000) E, unless you're looking for short haul, and record only the lower MUF of the two control areas, since that's the one you are going to use anyhow? That saves a lot of work. Unfortunately, you still have to go through the interpolation procedure until the Zurich sunspot number hits 110, when you can use Volume 3 directly. That won't last long though, as the number will go either up or down.

making the prediction

The first thing you need for the prediction is the great circle distance (in kilometers) between your home station and DX location. *Report 13* shows you how to do it graphically, but why not use the calculator? Other sources of theory include the articles by Marquart⁶ and Hall⁷. If you have a Hewlett-Packard HP-55, Chester Brent, WB4GVE, has the program all worked out for you⁸.

The program for the SR52 provides the beam heading and distance in nautical and statute miles, as well as kilometers. (The kilometer value is automatically stored in memory 98 of the SR-52, a storage location not cleared except by removal of power.) The program is contained on a magnetic card, requiring only the insertion of the DX latitude and longitude, which are also printed out on the PC100A for reference purposes. The home location is part of the program, although a second location may be manually inserted. The equations for D , distance in nautical miles, and H , heading in degrees, are:

$$D = 60 \cos^{-1} [\sin L_1 \sin L_2 + \cos L_1 \cos L_2 \cos (\lambda_2 - \lambda_1)]$$

$$H = \cos^{-1} \frac{\sin L_2 - \sin L_1 \cos (D/60)}{\sin (D/60) \cos L_1}$$

where

L_1 and λ_1 are your respective latitude and longitude

and

L_2 and λ_2 are the respective latitude and longitude of the other station

When the problem is solved, bearing from true north, distance in nautical miles, and distance in kilometers are displayed and automatically printed on the PC100A tape. In addition, by pushing a button, statute miles may be displayed. Fig. 3 shows the printout obtained.

Since 200 of the 222 storage locations were used for the bearing and distance program,* another program is required for the prediction. The prediction program, also on a magnetic card, is inserted in the SR-52 without de-energizing the unit; it is necessary to retain the kilometer value stored in memory location 98. The program is then actuated and the PC100A prints out the number of hops required for the path, the reference hop length, and the ionosphere control area distance (see fig. 4). These equations are very simple:

$$\text{Number of hops} = \text{Great circle distance} / 4000,$$

but increased to the next higher integer; i.e., if the answer is 3.3 hops, increase it to 4 hops.

The flow chart shown in fig. 5 indicates the steps taken by the calculator to arrive at a whole integer for the number of hops.

$$\begin{aligned} \text{Reference hop length} &= \\ \text{Great circle distance} / \text{number of hops} &= \\ \text{Ionospheric control area distance} &= \\ \text{Reference hop length} / 2 & \end{aligned}$$

At this point the smoothed sunspot number is placed into the computer, because from now until 1990, we are going to have to interpolate. There are two buttons to be pushed on the SR-52 while extracting the data from prediction volumes. One will be called Label A for MUFs at the home location, and one Label B for MUFs at the DX location. Open two volumes to the same month, 2400Z and MUF (4000) F_2 . The two volumes cover the sunspot numbers which are to be used for interpolation to the desired sunspot number.

The great-circle overlay is placed on the lower sunspot number chart first, carefully aligning the equator and the vertical line reference. I use a Greenwich meridian vertical line as well as a vertical line on the right border of the charts. The MUF under the home control area point is determined, inserted in the key-

NO. HOPS	4.0	PRT
HOP LENGTH	3342.5	PRT
CONT. AREA DIST.	1671.2	PRT

fig. 4. Printout of the hop length, number of hops, and control area distance as computed by the calculator.

*User instructions and complete coding forms may be obtained from *ham radio* by sending a self-addressed, stamped envelope.

board, and Label A pushed. The MUF under the DX control area point is next determined, inserted into the keyboard, and Label B pushed. The printer will print out the lesser of the two numbers, since the lower MUF is the controlling one for the path. A little time may be saved during this procedure. If the MUF at the DX location is higher than that of the home location, it will be discarded by your calculator. Therefore, rather than inserting that data into the keyboard, just push Label B and it will use Label A data which shows on the computer display.

Next, the great circle overlay is placed on the higher sunspot number chart and the above procedure repeated. The printer tape will now display MUFs for the lower and higher sunspot numbers. I have found it helpful to print these two numbers to verify that the interpolated number which follows appears correct. If a printer is not used, the numbers can be recorded from the display.

The program for this calculation is quite simple and may be performed on any hand calculator that has "If Pos" and "If Flag" features. I wanted to use the same labels for the minimum solar activity and the average solar activity (or the maximum activity). Label A is used for the home location MUF, and Label B is used for the distant location MUF. For any given solar activity we want to save for interpolation use the lower MUF for the high and low sunspot values.

Fig. 6 is the flow chart for the calculation. Check it out with actual numbers. From Volume 2 (SSN of 10) the MUF is 18 MHz at the home control point and goes into the calculator as MUF A, from the same volume, 25 MHz at the distant control point, and goes into the calculator as MUF B. The difference is $18 - 25 = -7$, a negative number. Since it is not "If Pos," it goes to a flag check. Since the test for flag is

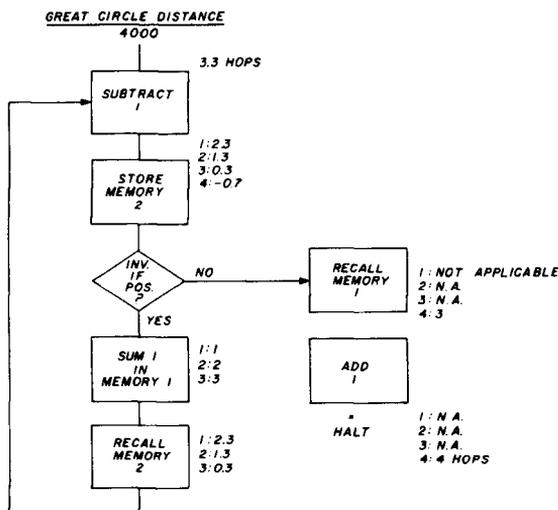


fig. 5. Flow chart for use with the TI-series calculators to determine the number of hops. Hewlett-Packard calculators with the INT function can perform this entire program in five keystrokes.

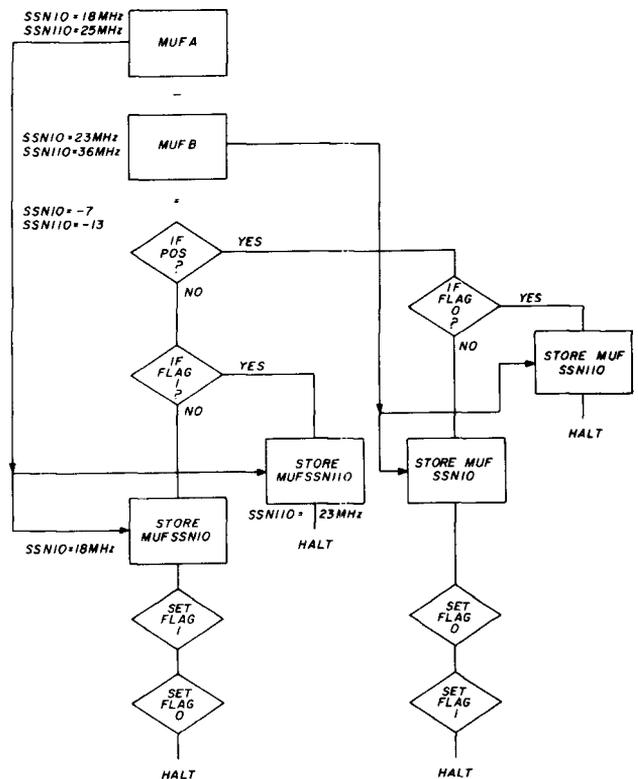


fig. 6. Flow chart to determine and store the lesser MUF value at the home or DX location. This information is needed to interpolate the MUF for the current sunspot number.

the first time through, none exists, and the proper MUF for SSN 10 is 18 MHz. The value is displayed and stored in memory. At the same time, two flags are set to prevent using this path for the MUF determination at SSN of 110.

Transferring to the SSN 110 chart, the MUF at the home location is 23 MHz and 36 MHz at the distant location. Again the "If Pos" check reveals a negative number and the calculator drops to "If Flag 1." Since that flag has been set, the value of 23 MHz is displayed and stored for interpolation purposes. If MUF A had been higher than MUF B, the calculator would have branched to "If Flag 0" with similar results.

To get the final interpolated answer for the hour used, press the Label D button. When that button is pushed, the calculator solves the equation:

$$MUF = MUF_{10} + 0.01(MUF_{110} - MUF_{10})(R_{12} - 10)$$

where

R_{12} is the current sunspot number

MUF_{10} and MUF_{110} are the MUFs at the low and high sunspot numbers.

When the sunspot numbers exceed 110, Volumes 3 and 4 will have to be used, and the program changed to use:

$$MUF = MUF_{110} + 10.02(MUF_{160} - MUF_{110})(R_{12} - 110)$$

Either of the interpolation equations can be programmed in your calculator or done by hand. With the programmable calculator, it is necessary only to recall MUF₁₀ and MUF₁₁₀ from memory and wait for the answers. It is at this point that the two flags have to be reset so that the program can start over for the next time increment.

If a printer is not used, the information is recorded from the calculator's register. When finished, you will have twelve points to plot for a 24-hour period, and the printout will be as shown in **fig. 7**. Plot them on graph paper using a suitable scale for the frequency to give a presentation such as shown in **fig. 1** or **2**. You will now have a 24-hour short-path MUF presentation to your desired DX location. Altogether the procedure has taken 10 to 15 minutes.

Don't stop at this point, however; also compute the long paths. Some of them are rather exciting. Don't be confused by the referral in Volume 1 to short and long paths. When they say short path, they mean a short distance, like Washington, DC, to Ottawa, Canada. A long path to them is Washington, DC, to Berne, Switzerland.

The long-path computation is treated just like the short path computation, but with different numbers and control area points. Since you already know the short-path distance, subtract it from 40,000 km to determine the long path distance. For our purposes, 40,000 km is sufficient for the world circumference.

Now when using the program, the calculator will give long path information to establish the ionospheric control area distance. The long path great circle route and the new control area must be put on the transparent overlay. Before repeating the prediction procedure, it will be necessary to reinsert the sunspot number as that information was cleared from memory when the program was activated. The "clear memory" operation is automatically accomplished when the prediction program is actuated to eliminate stored information from being carried over from the bearing/distant program.

Repeating the prediction exercise will give twelve new points to plot on your graph for the long path.

SUNPOT NUMBER			SUNPOT NUMBER		
30.0		PRT	30.0		PRT
MUF		TIME	MUF		TIME
12.0	0	PRT	12.0	12	PRT
21.0		PRT	14.0		PRT
13.8		PRT	12.4		PRT
10.3	2	PRT	11.2	14	PRT
17.0		PRT	14.0		PRT
11.6		PRT	11.8		PRT
10.0	4	PRT	10.0	16	PRT
13.0		PRT	13.2		PRT
10.6		PRT	10.6		PRT
11.0	6	PRT	13.0	18	PRT
15.0		PRT	13.8		PRT
11.8		PRT	13.2		PRT
10.5	8	PRT	10.0	20	PRT
14.2		PRT	13.5		PRT
11.2		PRT	10.7		PRT
10.1	10	PRT	10.0	22	PRT
13.5		PRT	13.8		PRT
10.8		PRT	10.8		PRT

fig. 7. Calculator printout for the MUFs during two-hour time increments.

Now, you have a complete picture and can establish your strategy and working hours to snag that elusive DX. Sure, you're still going to fight the pileups at times, but you will be there waiting for him with the beam pointed in the correct direction, and get him before many of the other guys wake up to his presence. Or, you'll be listening at a time and on a band which is most favorable to you.


references

1. Newell A. Atwood, W3KTR, "Predicting Amateur Conditions," *QST*, April, 1947, page 21.
2. Propagation Special, *CQ*, November, 1969.
3. Victor R. Frank, WB6KAP, "Ionospheric Propagation," *ham radio*, July, 1968 through August, 1969.
4. *Ionospheric Predictions*:
 Volume 1, The Estimation of Maximum Usable Frequencies from World Maps of MUF (Zero) F₂, MUF (4000) F₂, and MUF (2000) E, stock number 03000318, price \$3.00.
 Volume 2, Maximum Usable Frequencies MUF (Zero) F₂, MUF (4000) F₂, and MUF (2000) E for a Period of Minimum Solar Activity, R₁₂ = 10, stock number 03000319, \$3.00.
 Volume 3, Maximum Usable Frequencies MUF (Zero) F₂, MUF (4000) F₂, and MUF (2000) E for a Period of Minimum Solar Activity, R₁₂ = 110, stock number 03000320, \$3.00.

- Volume 4, Maximum Usable Frequencies MUF (Zero) F₂, MUF (4000) F₂, and MUF (2000) E, for a Period of Minimum Solar Activity, R₁₂ = 160, stock number 03000321, \$3.00.
- Write to the Superintendent of Documents, U.S. Government Printing Office, Washington, D.C. 20402.
5. Jerry Hall, K1PLP, "High Frequency Estimations for the Radio Amateur," *QST*, March, 1972, page 14.
6. W.E. Marquart, W9CKT, "Calculations for Antenna Orientation," *QST*, July, 1945, page 46.
7. Jerry Hall, K1PLP, "Bearing and Distance Calculations by Sleight of Hand," *QST*, August, 1973, page 24.
8. Chester H. Brent, WB6GVE, "Aim Your Beam Right," *73*, June, 1976, page 122.

ham radio

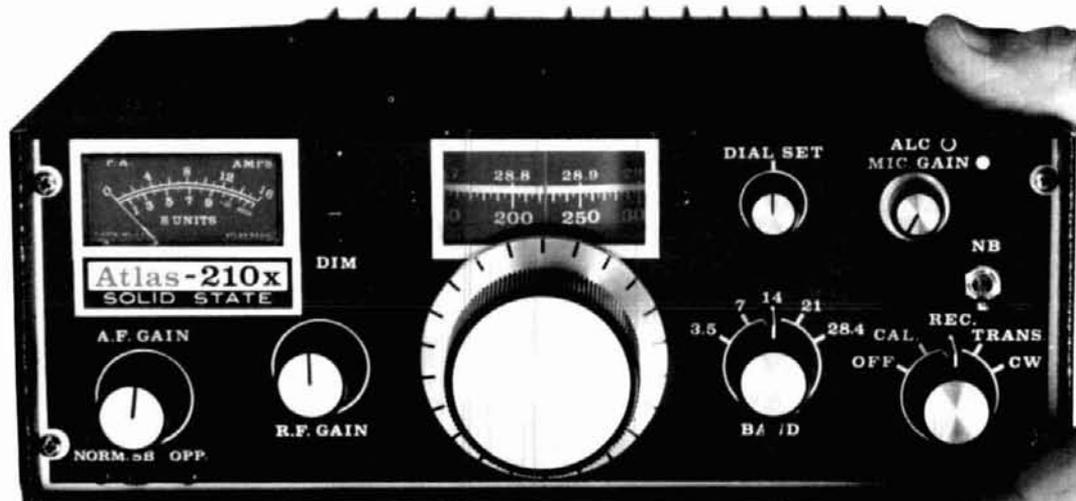More than 15,000 Hams are on the air with the ATLAS 210x!



200 Watts • 5 Bands • All Solid State
3 1/2" x 9 1/2" x 9 1/2" • 7 Pounds

It's a Proven Winner!

- ✓ HF SSB/CW Transceiver
- ✓ No transmitter tuning
- ✓ Plug-in circuit boards
- ✓ Super selectivity with exclusive 8 pole crystal ladder filter
- ✓ Exceptional immunity to strong signal overload and cross modulation
- ✓ Slips in and out of special mobile mounting bracket or AC console in seconds

For complete details see your Atlas dealer, or drop us a card and we'll mail you a brochure with dealer list.

Don't let its fingertip size fool you. The Atlas 210x transceiver has all the power and performance that you find in rigs twice as big and costing twice as much.

And with 15,000 hams on the air, you know you're getting a proven winner.


Model 210x or 215x Transceiver	\$765
(With noise blanker installed add \$45)	
Plug-in Mobile Kit	\$ 55
Portable AC Supply 110/220V	\$105
AC Console 110/220V	\$155
(With VOX and semi-CW installed add \$55)	
10XB Crystal Osc. less crystals	\$ 65



**ATLAS
RADIO INC.**

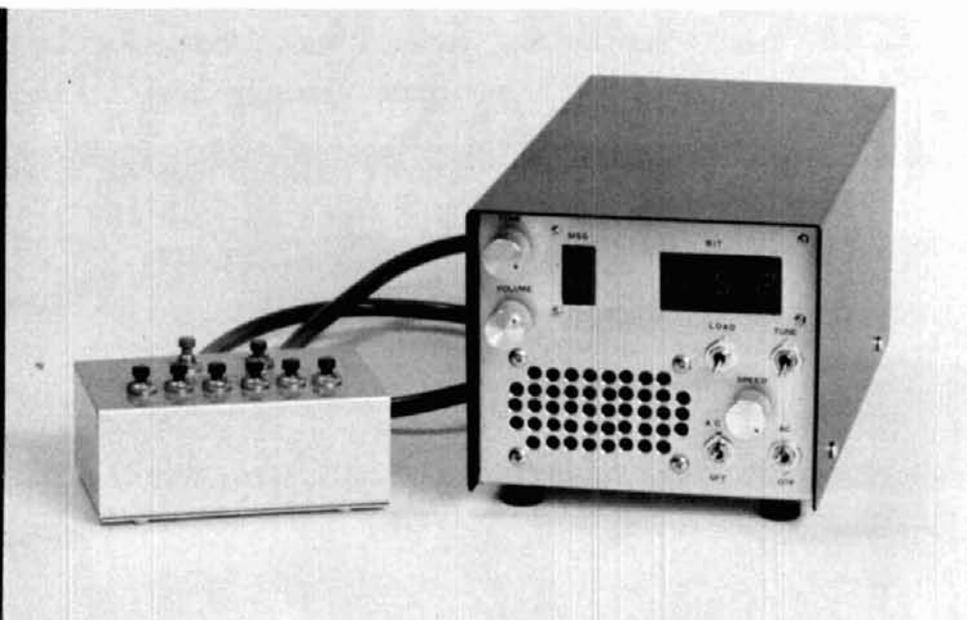417 Via Del Monte, Oceanside, CA 92054
Phone (714) 433-1983





deluxe memory keyer with 3072-bit capacity

A revision of the famous
WB4VVF Accu-Memory,
featuring improved
automatic character spacing,
six-message memory,
and remote control

A memory keyer with the right characteristics offers many advantages in contests, net-control operations, and DX chasing. It can relieve an operator of much of the routine repetitive sending, generally reducing fatigue and providing time for efficient log keeping, checking for duplicate contacts, and occasionally taking a sip of coffee, even during rapid-fire contest exchanges.

The Accu-Keyer,¹ as originally described in *QST*, was a nonmemory keyer with many desirable features. These included self-completing dots and dashes, next-dot and next-dash memories, iambic operation, and optional automatic character spacing (ACS). Later, WB4VVF and W4YUU described the companion Accu-Memory,² which, when used along with the Accu-Keyer, permitted storage of up to 2048 bits (about 200 CW characters) keyed in from the keyer. These could be read out as four individually selectable messages of up to 512 bits each, or as one or more longer continuous messages.*

*The term *bit* is used throughout as the element of information contained in a dot or a space in a CW character. A bit interval is the time duration of a single dot or space. A dash is three bits long, the standard space between characters is three bits, and a normal word space interval is seven bits long.

By Robert C. Cheek, W3VT, c/o Ebara-Infilco Co., Ltd., 1-1-1 Hitotsubashi, Chiyoda-ku, Tokyo 100, Japan


I built a modified version of the Accu-Keयर with the Accu-Memory, incorporating those modifications I thought desirable. My own experience with it, and the comments and questions of others, indicated that further improvements and enhancements could be made. I have now gone through the redesigning and building process five times, with the memory keyer described in this article the final result.

The memory capacity of this keyer is 3072 bits, in six selectable, 512-bit segments or in longer segments up to the full capacity of the memory. The entire system, except for the power supply and the display LEDs, is contained on two circuit boards measuring 80 by 150 mm (approximately 3-1/8 by 6 inches). ICs are used throughout, except for the output, which employs a keying transistor. When the memory is being loaded, the IC clock is synchronized to manipulator movement. Readout from memory may be automatically interrupted at any time by manual keying. A choice of keyer output circuitry to accommodate either grid-block keying or positive-line keying is provided for in the circuit-board layout. A cable-connected, remote-control unit is used for manual start, stop, and message selection functions. It can be conveniently placed on the operating table to be played with the left hand like the buttons on an accordion while the right hand makes log entries and operates the keyer paddle for station calls, nonstandard message insertions, and so on.

system description

A functional block diagram of the complete system is shown in **fig. 1**. Those who wish to follow the ex-

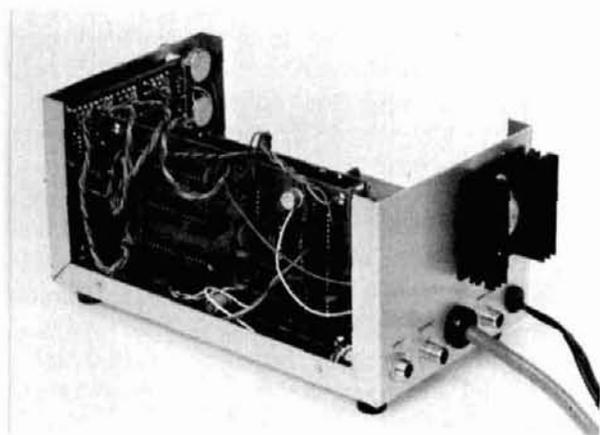Rear view of the six-message memory keyer showing the driver-monitor board; an adequate heatsink must be used on the 5-volt regulator.



planations in detail should also refer to the schematics of the two main boards, **figs. 2** and **3** for the keyer-driver-monitor and memory boards, respectively. This explanation assumes a knowledge of the specific IC characteristics and truth tables given in IC data manuals.

Keyer. The keyer proper (included in **fig. 2**) is basically the well-known Accu-Keयर, with all of the original features retained. Keyer operation was explained in the original article¹ and will not be repeated here, except for those portions of the circuit that have been changed.

The original clock pulse generator, made up of discrete transistors, has been replaced by an NE555 IC clock located on the memory board. As will be explained later, the clock output approximates a square wave rather than sharp pulses. This characteristic is used to greatly reduce the error rate in manual keying when the ACS feature is in use.

The ACS circuitry inserts precision, three-bit spaces between characters, correcting premature timing of one character following another in the manipulation of the keyer lever. Without ACS, this shows up as a shortening of the proper three-bit character interval. For example, *DE* may sound almost like *B* if the *E* is keyed too quickly after the *D*.

However, the original ACS feature is difficult to use at higher speeds without errors, which show up as unintentional extra spaces. This happens because lever manipulation must not only be fast, but must actually slightly lead, or at least never lag behind, in the formation of characters in which a dot is followed by a dash, such as an *A*. Those of us who grew up with the bug or semi-automatic key tend not to lead while keying, but to insert our own approximately correct one-bit interval between the dot and the dash in the formation of such characters. But, if the dash lever is tapped just a fraction of a bit space too late, an *A* becomes *ET* in the original keyer when ACS is in use. This occurs because the outpin at pin 6 of U5A (see **fig. 2**) is always low during the one-bit space following a completed dot or dash, and then always goes high for the next one-bit interval. It is this high transition that transfers a waiting dash or dot from the next-dash or next-dot memory, U1A, U1B, or U2C, U2D, as seen through the iambic gates, to the present dash or dot memory, U3A or U3B, starting the output of the dash or dot. If the lever is tapped even very slightly late, this transition is missed and two additional bit spaces are inserted.

U8 in the keyer has been added to provide some

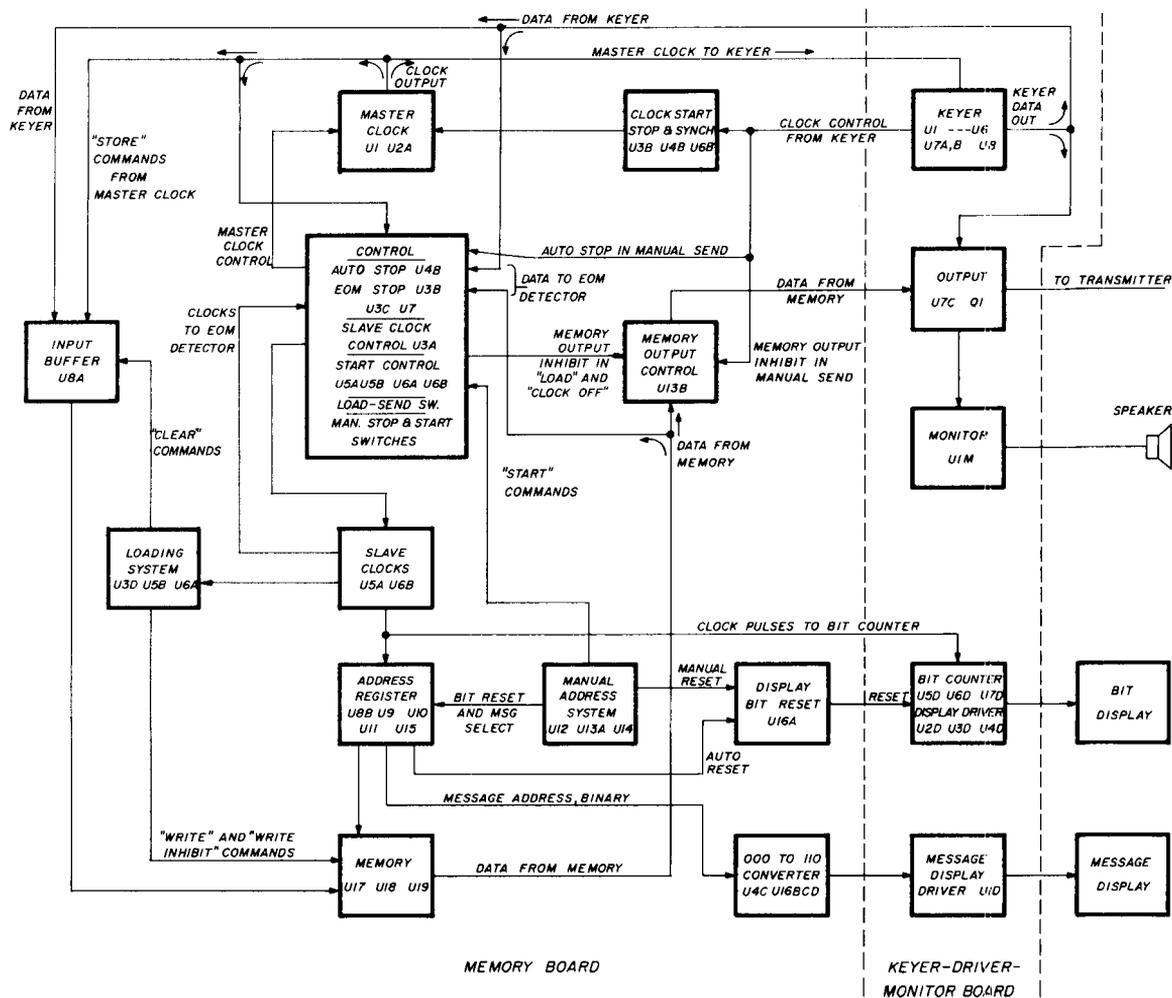


fig. 1. Functional block diagram of the memory-keyer system. Details of the keyer block are not shown; these are given in reference 1.

tolerance for slight manual timing delays in the keying of dashes following dots as described above. The approximate square wave from the clock is high at pin 1 of U8 for the first half of the bit interval after pin 6 of U5 goes high. If neither a dash nor a dot has already been called for, pin 8 of U6 will also be high. If the dash paddle is tapped during this half-bit period, U1D, pin 11, will go low. This low, inverted by U8B, will cause U8A, pin 6, to go low because all four inputs are high. The low will set U3A, pin 6, high and start the dash, although a little late. However, even though the interval between the dot and the dash may be lengthened by as much as half a bit and the dash correspondingly shortened by this amount, the result is almost undetectable to the ear and is far better than the three-bit interval that otherwise occurs, causing a completely erroneous character to be formed. Also, since data as it exists at the end of the bit interval is what is recorded into memory in the loading process, the correct one-bit interval be-

tween the dot and the dash is restored when the message is sent from memory.

The keying of a dash following a dot after the half-bit tolerance interval provided by U8 results in the insertion of the normal three-bit character interval, retaining the desirable features of automatic character spacing. At the beginning of the third-bit interval during a character space, pin 6 of U5A again goes low when the clock pulse starts. The RC filter at pin 1 of U8 delays the clock pulse slightly so that pin 6 of U5A has time to go low before the clock, as seen by U8A, goes high. This prevents a shortened dash from prematurely appearing if the dash lever has by that time been tapped for the next character.

By adding another IC equivalent to U8, it would be possible to provide the same tolerance for manual keying of a dot or dots following a dash. However, nearly all the tendency for errors at high speed is the result of the very short and critical interval for the keying of a dash following a dot. Since the available

interval is inherently much longer going the other way, the extra complication would not be worthwhile.

Clock. The clock, as shown in **fig. 4**, is the heart of the keyer and the memory. Both require a clock signal which is at zero level in the quiescent state, remains at zero for the duration of the first bit interval after the clock is called for, and then provides a steeply rising positive pulse or square wave at the beginning of each bit interval thereafter. With the control scheme adopted, the combination of the NE555 timer and an inverter provides the necessary characteristics, including the square wave required for the ACS error-reducing circuit in the keyer.

Pin 4 of U1, which is normally used as the control input in NE555 applications, is maintained high at all times, keeping pin 3 normally high, with the clock output being low. When pin 11 of U3B is low, calling for the clock to be off, the timing capacitor is essentially discharged through CR1. Pin 3 of U1 remains high and the output of U2 stays low. When the clock is called for by either the keyer or the memory, pin 11 of U3B goes high and the timing capacitor begins to charge at close to a linear rate. The output from the inverter remains low during this process. When the charge reaches $2/3$ of V_{cc} (the supply voltage), pin 3 of U1 goes low, forcing the inverter high, marking the end of the first bit interval. Thereafter, the charge on the timing capacitor oscillates between $1/3$ and $2/3$ of V_{cc} , and the output at U2 goes high at the end of each subsequent bit interval until pin 11 of U3 again goes low, stopping the clock.

CR1 and CR4 permit independent discharge of the timing capacitor for clock synchronizing purposes, as will be explained later.

Memory system (load mode). The basic memory loading system of the Accu-Memory² is essentially retained. In the load mode, with a message address manually selected, the clock control line from the keyer goes low at the moment keying begins and pin 11 of U3B (see **fig. 3**) goes high, starting the master clock. At the same time U6B, pin 1, goes low, causing a pulse at pin 13 of U6. This pulse is passed along by U5B and then appears at pin 5 of U6A, from where it is applied to pin 3 of U7, the end-of-message detector. This pulse at pin 3 performs an AND function with the data at pin 2 of U7, setting the output at U7 pins 1 and 11 to zero, whereupon pin 8 of U3C will go high and pin 12 of U2B low, keeping pin 11 of U3B high. The high at U3C pin 8 also enables slave clock control U3A. Pins 9 and 10 of U3C are both high only when U7 is at a count of nine. Thus, even though the clock control line from the keyer may go high, U7 will keep the clock running until it counts nine consecutive pulses at its pin 14 from slave clock U5A, pin 5,

without being reset by the pulses at pin 3 coincident with data at pin 2.

At the end of the first bit interval, the leading edge of the master clock pulse transfers the data at the D input of the 7474, U8A, pin 12 to U8A pin 9. Halfway through the second bit interval, the trailing edge of the first master clock pulse, having been inverted by U3A and applied to pin 10 of U5A and U6A, causes positive pulses at both Q outputs. The write inhibit, provided by gate U3D, is removed by the pulse from pin 5 of U6A, and the first-bit data is recorded into the memory. The pulse from U5A is somewhat longer in duration. Its negative-going trailing edge, occurring later, advances the address register by one, and at the same time the positive-going \bar{Q} output at pin 12 of U5A causes pin 4 of U5B to pulse low, clearing the buffer, U8A, to zero. At the same time, pin 13 of U5B pulses high, and its subsequent trailing edge causes another positive pulse at pin 5 of U6A, again removing the write inhibit and recording the previously mentioned zero from U8A in the second memory address. All of this takes place during the latter part of the second-bit interval.

At the end of the second-bit interval, the loading process is repeated for the second data bit, and the zero previously stored in the second address is changed to whatever the contents of the data buffer may be for the second bit. If there is a pause in keying, the end-of-message counter U7 will stop the master clock when it counts nine consecutive bits without being reset by pulses from U6A along with the data. The ninth bit will be changed to a one if keying is resumed, and the pause, no matter how long, becomes a word space (slightly lengthened to eight bits) when the message is read out in the send mode. However, if the message has really ended and no additional data is loaded, the zero remains in the ninth bit position, and in the send mode U7 will stop the clock at that point.

The master clock free runs during the word intervals in the load mode, and it is necessary to synchronize the clock to the paddle movements during loading so that shortened dots and dashes do not appear, as they would if the paddle were tapped to start a new word just before a clock pulse was about to occur. Synchronization is accomplished by U6B, U4A, and U2C. When the paddle is tapped during loading, the clock control line from the keyer goes low, calling for the clock (which normally is already running). This low, applied through CR5 to pin 1 of U6B, causes the \bar{Q} output (pin 4) of U6 to pulse low. This pulse forces the output of U4A high and U2C low. The timing capacitor is momentarily discharged through CR2 by this pulse and then allowed to charge normally, ensuring full bit intervals for the

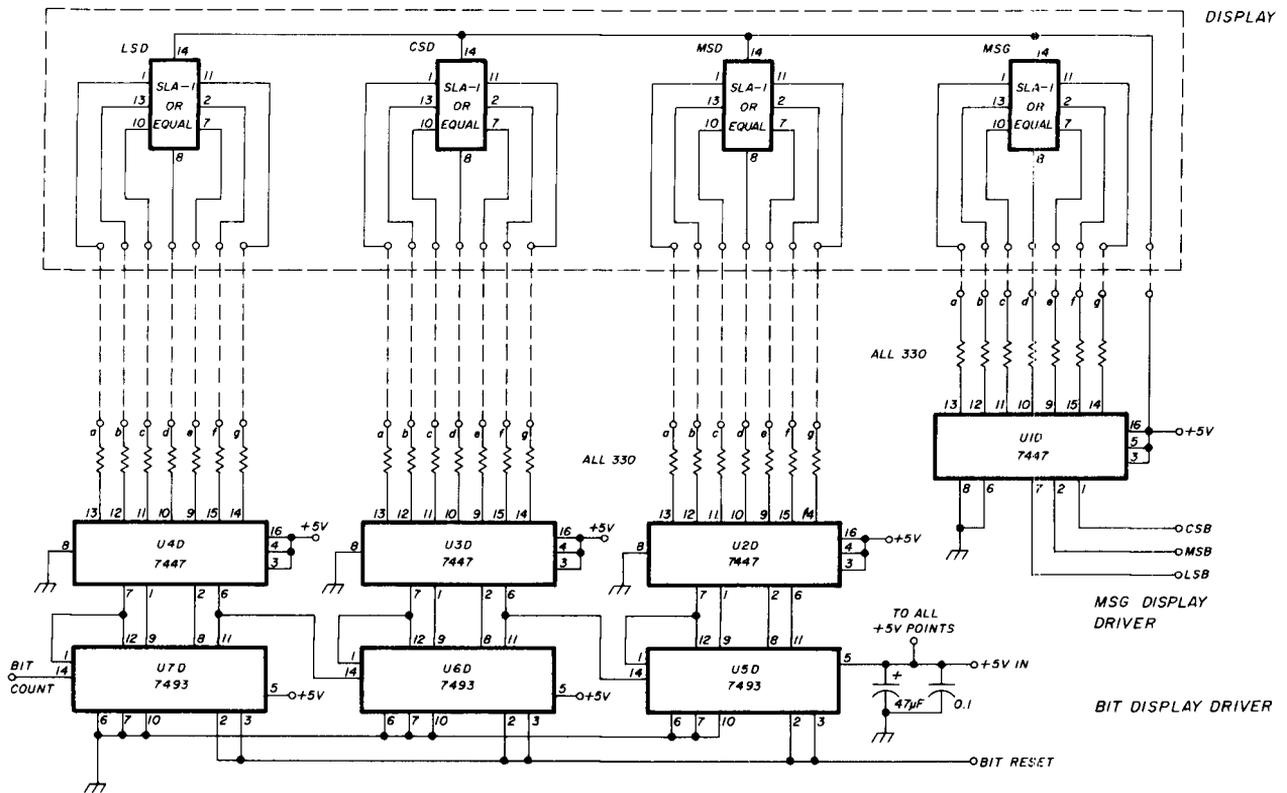


fig. 2. Schematic of keyer-driver-monitor board and display. All resistors are 1/4-watt. Capacitors with polarity indication are upright electrolytic, 15-volt minimum rating; all others are disc ceramic, 25-volt minimum rating unless otherwise specified. The diodes are small signal silicon, switching diodes, 1N4148 or equivalent. Dotted lines indicate connections to external switches and controls. Small circles with labels, except +5V to ICs, indicate similarly labeled points on the board or power supply. In the output circuit for negative grid-block keying, Q1 may be a 2N4888 or any high-voltage audio, switching, or rf silicon pnp transistor with a V_{CE0} rating adequate for the open-circuit voltage to be keyed. The unit pictured uses a Japanese type 2SA510 (RCA SK3025 is also a recommended equivalent). For positive-line keying, an equivalent npn transistor is used at Q1.


first bit and subsequent initial bits of manual sending.

In the load mode, the load/send switch grounds pin 12 of U13, preventing any output of random or previously stored data in the memory from reaching the output data line. While loading is progressing, only the new data from the keyer can key the transmitter.

Address register and manual addressing system. The address register consists of U9, U10, and U11A for the lowest nine binary address bits (512 of the 1024 positions on each memory chip). The tenth address bit, determined by U11B, becomes the least significant message address bit. Thus, U11B divides each 1024-bit memory chip into two 512-bit message segments, selected by making the output from pin 9 either a zero or a one. U8B, U15A, and U15B constitute a shift register or ring counter which activates one memory chip at a time for loading or readout by placing pin 13 of the selected chip low, while maintaining pins 13 on the other two chips high.

The entire address register is controlled by the manual addressing system, consisting of U12, U13A, and U14. When a message button is pushed (assuming the clock is not running) pin 6 of U13 goes high, setting U9, U10, and U11A to zero. Pin 9 of U11 is set either low or high, depending upon the message selection, and the Q output of one of the three flip-flops in the ring counter is set low to address the desired memory chip. The other two Q outputs in the ring counter are simultaneously set high. Whenever a manual message selection is made, the display bit counter is simultaneously reset to zero by U16A.

Since memory-chip selection is made by setting one of the Q outputs in the ring counter low, the \bar{Q} outputs of U15A and U15B are used as the central significant bit and the most significant bit, respectively, of the message address. When both these Q outputs are high (\bar{Q} outputs both low), the memory chip that is activated by a low from the Q output of U8B is in use, and the message address is either 000 or 001 binary (decimal 0 or 1), depending upon the

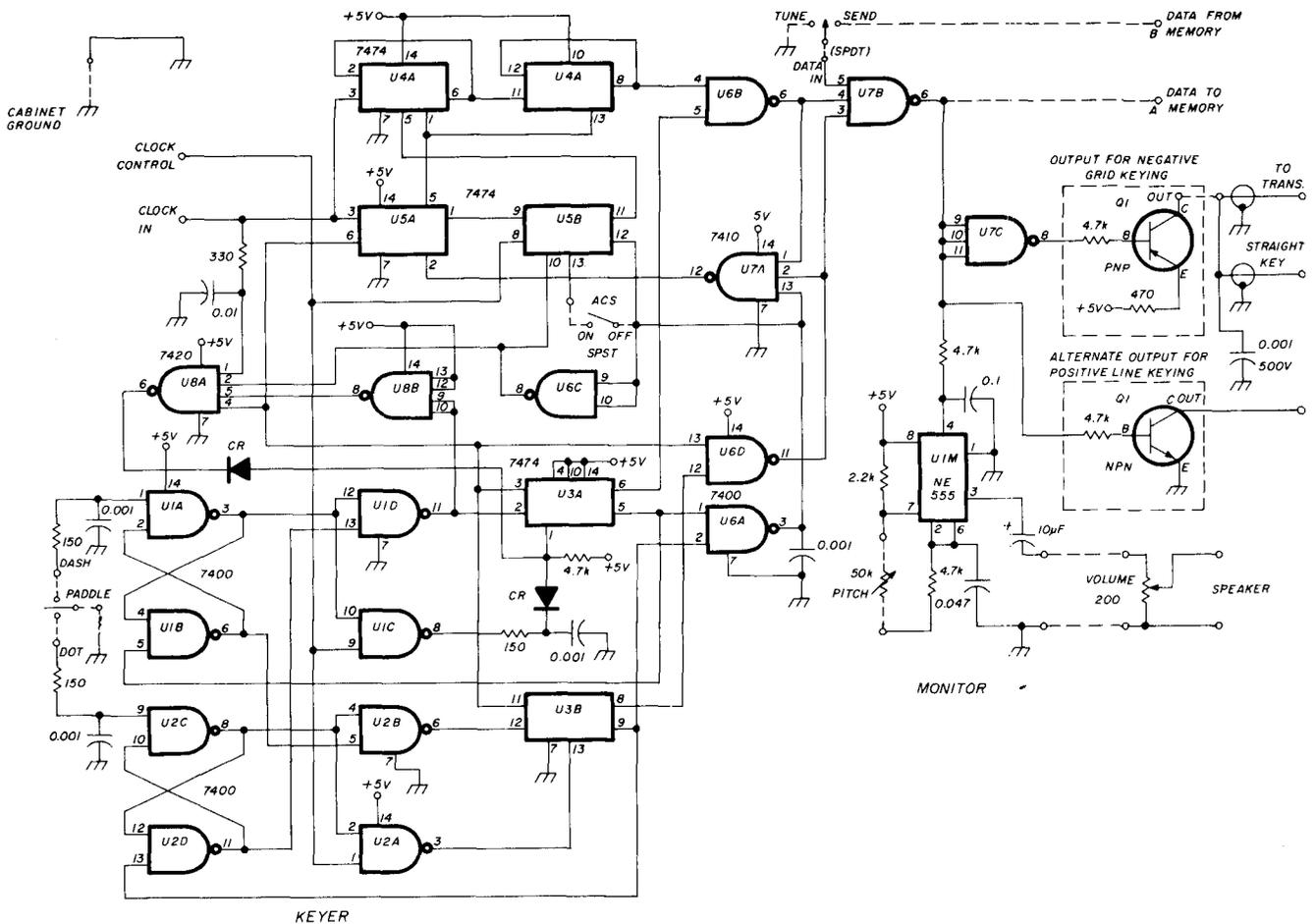

Q output at U11B. The other binary message addresses are 010, 011, 100, and 101 (decimal 2, 3, 4, and 5). Since it is better in operation to have the six messages numbered 1 to 6 rather than 0 to 5, U4C and U16B, C, D were configured to convert 000 binary to 110 binary, leaving the other binary indications unchanged. Thus, message 0 becomes message 6 for all selection, display, and operating purposes. The entire addressing system is a continuous counter, so that a message as long as the entire 3072-bit memory capacity can be started at any selected beginning address and loaded continuously in memory, with automatic transition through the consecutive message segments back to the starting address.

Send Mode. Before a selector button is pushed, the clock is stopped by a low at pin 11 of U3. This low also inhibits U13B, blocking the continuous output that would otherwise appear if the address register happens to be stopped at a memory address where a high exists. When a selector button is pushed, the high at U13, pin 6, which resets the sit address

register to zero, is inverted by U2D, simultaneously causing a low at pin 1 of U6B. The resulting pulse at U6, Pin 13, triggers U5B which in turn causes a pulse at pin 5 of U6A.

A high always exists at memory bit address 000 when a message segment is loaded. This high is applied to pin 2 of U7, and the pulse from U6A is applied to pin 3. The AND function at these two points resets U7 to zero, unblocking the memory output and starting the clock. The high at pin 11 of U3B also causes U13A to return to low, even if the message selector switch is kept closed, removing the reset on the address register. Slave clocks U5A and U6A are enabled through U3A when U7 resets. U5A advances the address as described for the load mode. During each bit interval, a pulse from U6A is applied to U7, resetting U7 whenever data appears at pin 2 of U7. Unless the stop button is pushed, sending from memory continues until U7 counts the nine consecutive bits with zero data which mark the end of the message.

Automatic Stop. A message readout in progress

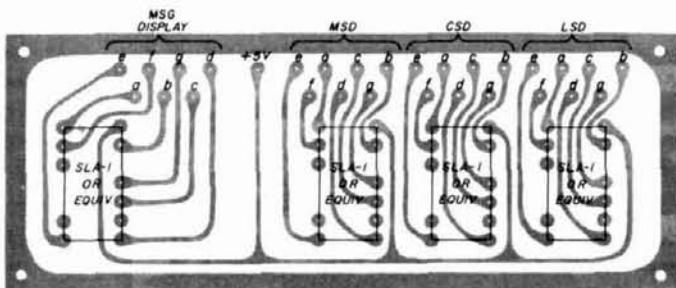
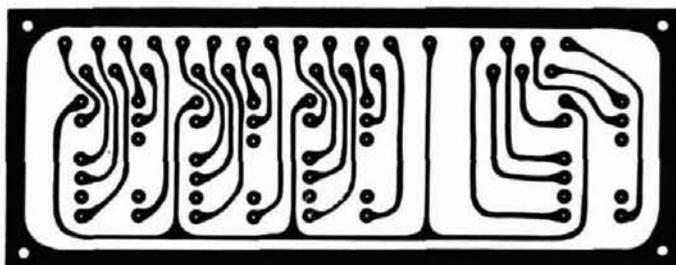


fig. 8. Display-board pattern (above) and LED placement (below). The display LEDs may be SLA-1 or any of several equivalent 8-mm (0.3-inch) common-anode displays with 14-pin DIP pin spacing and the same pin-out configuration for the seven segments. Decimal points are not used and their pin-out locations are not important.

RF shielding of all external leads to the main boards and the use of an all-metal cabinet are absolutely necessary. The leads to the remote-control box (which also must be a metal box) should consist of a shielded cable (11 conductors plus shield are needed) with the shield grounded both in the box and in the main cabinet. The keyer-paddle leads should also be shielded. A two-conductor shielded cable, with the shield used as the ground lead, will be satisfactory.

One last precaution — be sure to insert the correct ICs in the correct locations with the positioning notches in the proper direction, and then recheck each one before applying power. This is very obvious, but I've ruined a few ICs myself by being a bit careless on this point.

initial tests

After assembly and wiring are completed and checked, set the tune/send switch and the mode switch to send, all controls at about two-thirds scale, and apply power by turning on the ac switch. If some gibberish comes out of the monitor, it is a good sign. Pushing the STOP button should stop the output. Check that the output terminal of the regulator is +5 volts. Each display LED should show some digit at this point, although the actual indication is not important.

Next, check the clock, keyer, and monitor for proper operation as follows: Alternately ground the dot and dash inputs to the keyer. Continuous dots and then continuous dashes should be heard from the monitor. Grounding both inputs simultaneously should produce alternating dots and dashes. Switching the tune switch to TUNE should produce a continuous tone. Return it to normal. Now set the mode switch to LOAD and press each message selector button in turn. Bit count indication should be 000 and message numbers 1 through 6 should be displayed in sequence as the associated buttons are pushed. Pushing the START button should cause the bit address to advance by ten bits and then stop.*

Again selecting message 1, ground the dot input to the keyer, causing it to send continuous dots. The bit indication should advance as these dots are loaded into memory and after bit 511 the message address should change to 2 000. Continue loading dots part way into message 6, stop the keyer by ungrounding the dot input, set the mode switch to SEND and again select message 1. The entire series of dots should play back on the monitor without errors or omissions, and it should be possible to stop the playback at any point by pushing the STOP button or by momentarily grounding the dot or dash input of the keyer. Next, in the LOAD mode, again select message 1. While holding the STOP button down, push the START button down once and release it to get a bit count of 001. (Because of contact bounce it may be necessary to try several times to get just a one-bit advance when the button is pushed.) Load continuous dots from 1 001, again part way into message 6. In the SEND mode, select message 1 and this time push the START button to start playback. Again, the whole series of dots should play back smoothly. These two tests will indicate whether all memory cells in this address range of the memory ICs are okay. Perform similar tests by loading dots beginning at addresses 6 000 and 6 001, continuing into message 1 in each case, to check the remaining range of memory addresses.

using the keyer-memory

The memory may be loaded with a message starting at any selected message address. Simply switch to the LOAD mode, select the message number, and start keying. When the message is completed, another may be begun at a different message address until all beginning addresses are used. (If a

*This may seem contrary to the previous statements that U7 stops the clock after counting nine bits with zero data. Actually the START button causes the address register to advance by one bit at the start of the first bit interval as the count at U7 goes from 9 to 0. U7 then counts nine additional bits and stops the clock.

message is too long to fit into a 512-bit memory space, it will continue into the next message address.) In the SEND mode, pushing the message selector button for a particular message will instantly start transmission of that message from memory. In contest work, a CQ SS or CQ DX can be loaded as message 1, with several different replies (different reports, etc.) as the next few messages, and *R TU QRZ* . . . etc. as message 6. For contests in which the exchange requires a variable element such as a QSO serial number, load the standard information up to the point where the variable element must be inserted. Then, holding the stop button down, advance the memory two or three bits by pushing the start button. Continue loading the subsequent standard information. In the SEND mode the memory will stop at the point where variable information is required. After this is keyed manually, the rest of the standard message will continue when the START button is pushed. This technique can also be used to load a request for a repeat after a standard number transmission, both in the same message address, to be used in case you miss the number sent back to you.

If you are going to call a station on a schedule, you may wish to send his call sign more times than provided in the usual 3×3 calling format. To do this from the memory, load his call just once at the message starting address and pause until the bit indication stops advancing. Then continue with *DE*, your own call several times and *AR*. In the SEND mode, hold the message selector button down continuously instead of pressing and releasing it. The called station's call sign will be repeated as long as you hold the button down. When you release it, the rest of the message will continue to conclusion. (You can send long CQs this way too, but they're not recommended!) If you want to reduce the number of times your own call is signed, simply manually send *AR* or *K* at the appropriate point to stop the memory.

To call the same station often, as in a DX pileup, switch to the LOAD mode, select a message segment, and proceed to make your first call. Then, in the SEND mode, press the selector button and the memory will do all the subsequent repetitive calling for you. The above are only a few of the possibilities. Once you have gained some familiarity with the unit's capabilities, many other operating applications will suggest themselves.

references

1. James M. Garrett, WB4VVF, "The WB4VVF Accu-Keyer," *QST*, August, 1973, page 19.
2. James M. Garrett, WB4VVF, and D. A. Contini, W4YUU, "The Accu-Memory," *QST*, August, 1975, page 11.

ham radio

DRAKE R-4C FILTERS AND ACCESSORIES

Spectacularly improve the performance of this excellent time-tested receiver, popular worldwide with the most successful DXers and Contesters, by adding our highest quality 8-pole filters and accessories. Compare our specifications and prices with those of others and you'll buy **FOX-TANGO!**

YF56H8.0 (GUF-1). Broad first IF Filter. Superior 8-pole type (Shape factor 1.5, ultimate rejection >100dB) replaces original unit (Shape factor 4.7, ultimate rejection 65dB). Used in CW/SSB modes. Drop-in replacement of original unit — only two soldered connections. Recommended for use in conjunction with GUF-2. With complete instructions. **GUF-1 \$65** plus \$3 local airmail; \$5 overseas.

YF56H800 (GUF-2). Narrow first IF Filter. (Shape factor as low as 2.0, ultimate rejection > 100dB.) Both GUF-1 and GUF-2 improve dynamic range, reduce intermod due to overloading of second mixer, reduce QRM, etc. GUF-2 includes a relay kit and all parts needed to provide automatic selection of GUF-1 or GUF-2 depending upon the position of the Mode Switch, thus retaining phone capabilities lost if GUF-2 (CW) is used alone. Complete step-by-step instructions simplify installation. **GUF-2, including relays and parts: \$90** plus \$3 local airmail, \$5 overseas.

YF56H125. Sharp 125Hz 8 pole, second IF Filter. (Shape factor as low as 2.0, ultimate rejection > 100dB.) Sharpest CW filter available. See Specs in Table. If you can't get it with this filter, you can't get it — period! Puts selectivity where it counts: in the AGC loop. Eliminates loss of RX gain due to QRM outside of passband, commonly noted with audio filters — yet works well with them. Simple installation; plugs into accessory socket on back of the set. **\$100** plus \$3 local airmail, \$5 overseas.

GUD Product Detector Kit. All parts and instructions needed to convert the existing detector to a double-balanced type to provide better isolation between input and output. Overcomes distortion in audio output and AGC attack. Includes compact PCB with active DBM SN16913, relay switch, and accessory components. Detailed instructions, diagrams and photographs simplify installation. **GUD Kit \$45** plus \$3 local airmail, \$5 overseas.

DIODE SWITCHING BOARDS

DUAL (2 FILTER) TYPE FOR ALL YAESU AND KENWOOD LISTED. Specify make and model — **\$21.00** airmail postpaid. **SINGLE (1 FILTER) TYPE FOR FT/FR-101 ONLY** — **\$12.00** airmail postpaid.

(To avoid error due to similarity of some filter numbers, specify desired unit completely when ordering. Include make and model of set, filter number desired, and center frequency.)

DEALER INQUIRIES WELCOMED — VISA AND MASTER CHARGE ACCEPTED
FLORIDA RESIDENTS ADD 4% (SALES TAX)



FOX-TANGO CORP.
Box 15944, W. Palm Beach, FL 33406

See other ad page 117.

16 ELEMENTS — F9FT — 144 MHz



The 'Tonna' You've
been
hearing about

144/146 MHz SWR 1.2:1
50 ohms Horiz./Vert.
length 6.4 m. Wt. 4.4 kg.
Side lobe attenuation — Superb
Horizontal aperture 2 × 16° (−3 dB)
Vertical aperture 2 × 17° (−3 dB)

\$79.95

9 Element 144-146 **\$39.95**
4 Element 144-146 **\$32.95**

MADISON
ELECTRONICS SUPPLY, INC.

1508 McKINNEY • HOUSTON, TEXAS 77002

713/658-0268

Call **Toll Free** 1-800-243-7765

FREE

- Retail Price Catalog
- Monthly Computerized Used Equipment List
- Courteous, Personalized Service



WILSON
MARK IV



KENWOOD TS-820S



YAESU FT-901



ICOM IC-701



KDK 2016A



CUSHCRAFT ANTENNAS



TEN TEC OMNI-D



GLA-1000



CPU 2500 R/K

OVER 50 BRANDS IN STOCK

- KENWOOD • SWAN • KDK • DENTRON •
- MOSLEY • WILSON • YAESU • DRAKE •
- LARSEN • BENCHER • PIPO • BEARCAT •
- B & W • DATONG • ICOM • PANASONIC •
- ARRL PUBLICATIONS • ALLIANCE • MFJ •
- CUSHCRAFT • TRAC • MICROLOG • CDE •
- FINCO • DSI • DAYBURN INSULATORS •
- BIRD • ASTATIC • HAM KEY • REGENCY •
- HUSTLER • SAXTON • TEN TEC • AMECO •
- AMCOMM • CALL BOOK • KLM • TEMPO •
- ATLAS • ALDA • COVERCRAFT • HY-GAIN •
- J.W. MILLER • MURCH • PFENTONE •
- SHURE • TAB BOOKS • SAMS BOOKS •
- ROHN • BUTTERNUT • Plus Many More!

★ NEW AND USED EQUIPMENT

"Get on our used equipment mailing list"

★ TRADES WELCOME

"The best allowances anywhere"

"We buy good used SSB gear"

★ FREE CATALOG

"Prices of all major manufacturers"

★ SAME DAY U.P.S. SHIPPING

"Just a phone call away"

★ COMPLETE RADIO SERVICE SHOP

"Mail Order Repair Service"

- Fast Efficient Service • We Repair All Brands
- All Work Guaranteed • Amateur Extra/First Class Licenses • Send Us Your Defective Equipment U.P.S. Collect • Please Include Manual and Power Supply
- Free Shipping Both Ways If Work Is Done
- Most Repairs Done and Shipped Within 7 Days

OUR FINE REPUTATION SPEAKS FOR ITSELF

"YOU SHIP IT

WE FIX IT"

THOMAS COMMUNICATIONS

95 Kitts Lane, Newington, Conn. 06111

"Near ARRL Headquarters"

**Call
or Write
for your
super quote
today!**

Connecticut Residents Call:

(203) 667-0811



OPEN MON.-FRI. 10-6 • THURS. 10-8 P.M. • SAT. 10-4

EASY DIRECTIONS: Rt. 15 South — 2 blocks past McDonald's
(Berlin Turnpike)

A Look at



THOMAS COMMUNICATIONS



New Equipment — All new equipment on display is operating for actual "on the air" QSO's. We really know our gear!



Used Equipment — We recondition and guarantee all our used equipment. We make sure it satisfies you!



Service Shop — You've probably heard of our fine service reputation — using Cushman CE4B signal generators, Hewlett Packard oscilloscopes, Bird wattmeters — we fix it right!



Inventory Warehouse — Our large volume assures you the best prices!

And Our Service Is Even Better! Give Us a Call and See For Yourself!



1-800-243-7765

More Details? CHECK — OFF Page 118



THOMAS COMMUNICATIONS

95 Kitts Lane, Newington, Conn. 06111
(203) 667-0811

april 1979  45

active bandpass filter for RTTY

Construction details
for an active
bandpass filter
which will help
eliminate interference
and provide
improved RTTY copy

This active bandpass filter was designed to work ahead of the NS-1A PLL Demodulator,¹ but it will provide improved copy when used ahead of any RTTY terminal unit. The filter is connected between the audio output of a receiver and the input of the terminal unit.

A bandpass filter is just what the name implies. It will pass only a specified band of frequencies, attenuating all frequencies above and below the specified limits. The objective is to make this attenuation as high as possible, passing nothing other than the desired signals. Without complex circuits, this is not always possible. Simpler filters, like the one described here, will always pass some unwanted frequencies, attenuated enough, however, that they are of no consequence.

For RTTY, we want to pass the standard narrow-shift tones, 2125 and 2295 Hz. For this 170-Hz shift the bandpass should be about 200 Hz wide, centered on 2210 Hz.

circuit description

As can be seen from **fig. 1**, the filter consists of two separate, two-section filters using cascade-connected operational amplifiers. It uses only one IC, the LM3900, which contains four so-called "Norton" amplifiers. These op-amps will do almost anything the standard op-amp will do. The principal advantage is that the LM3900 requires only a single power supply. Also, the LM3900 differences the input currents, whereas the conventional-type op-amp differences the voltages. The noninverting input function has been made possible by using what is called a current mirror circuit.

Several formulas are used to determine the required values of the resistors and capacitors. The

By **Nat Stinnette, W4AYV**, 890 Virginia Avenue, Tavares, Florida 32778

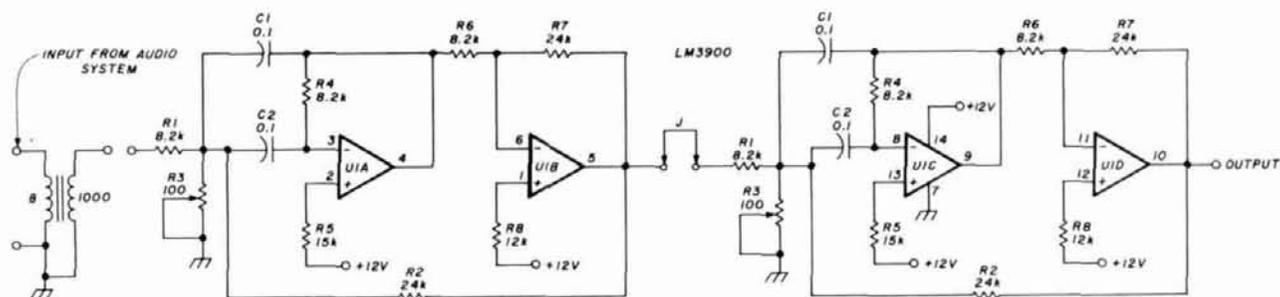


fig. 1. Schematic diagram of the active bandpass filter. The center frequency is 2210 Hz, with a -3 dB bandwidth of approximately 160 Hz. A single LM3900 Norton op-amp is used for the filter.

nearest standard values of 5 per cent resistors are shown in the diagram. The capacitors can be 10 per cent tolerance. R2 sets the Q of the circuit (and also the gain) and works out to be 12.5 kilohms for a Q of 11, or a -3 dB bandpass of 200 Hz centered on 2210 Hz. When both filters are connected together, however, the increased Q makes the bandpass too narrow. The value of 24 kilohms was chosen by trial and error to give the best passband.

The complete filter, with standard resistor values, actually gives a -3 dB passband of 160 Hz, or a Q of 14. This may seem a little narrow for 170-Hz shift, but on-the-air tests have shown this not to be the case. The bandpass can be easily widened by changing R2 or by stagger-tuning one filter 50 Hz below and the other 50 Hz above the center frequency. The filter turns out to be about 800 Hz wide at the -20 dB points. There is no insertion loss; in fact, there is a small gain.

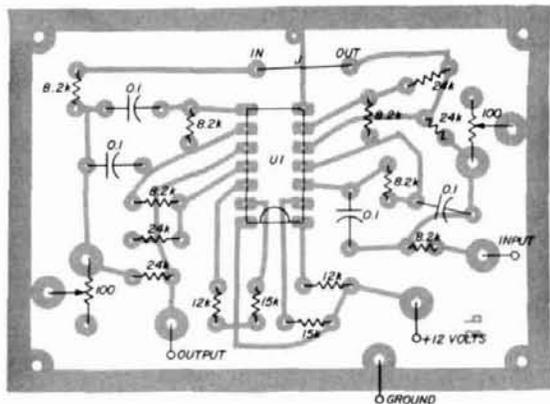
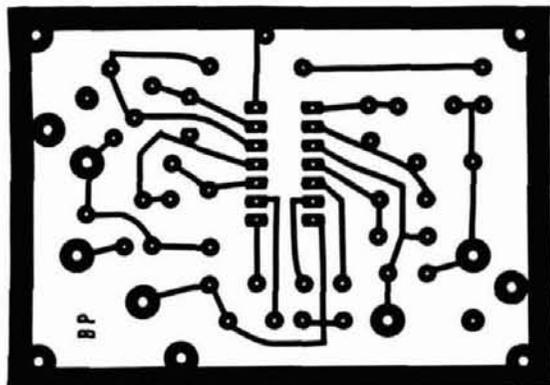


fig. 2. A circuit board foil pattern for the active bandpass filter is shown above. The filter can also be built on a small piece of perforated board using 5 per cent resistors and Mylar capacitors.* The bottom illustration is the parts placement diagram for the circuit board.

alignment and connection

Before connecting the jumper between the two filters, separately tune each filter to 2210 Hz. This can be done by injecting a 2210-Hz signal and adjusting R3 for peak output as shown on a VTVM or high-impedance ac voltmeter. The jumper is then connected between the sections. Another method of tuning the filters, though not as accurate, is to tune in a strong RTTY signal with the filter in the line and adjust R3 on each filter for peak output or best copy.

The transformer is used to step up the input from the receiver speaker output to more closely match the input impedance of the filter. If the output impedance of your receiver is at least 500 ohms, the transformer will not be needed.

A good way to check the performance of the complete filter is to have some means of switching it in and out of the circuit. You will find that the filter will sometimes be the difference between copy and no-copy. High-impedance headphones (2000 ohms) connected across the output will enable you to hear the difference.

*A complete kit of parts and wired/tested units are available from the author. See Flea Market ads.

reference

1. Nat Stinnette, "Update of the Phase-Locked Loop RTTY Demodulator," *ham radio*, August, 1976, page 16.

new audio amplifier for the Drake R-4C

A new audio amplifier
for the Drake R-4C,
suitable for
direct substitution
in all R-4C versions

Improvements in the Drake R-4C receiver, up to now, have been confined mainly to the i-f and detector systems.^{1,2,3} One remaining area which needs improvement is the audio strip, which suffers from buzz and higher-than-desirable distortion; it also dissipates 7 to 10 watts of heat near the PTO. The audio amplifier, diagramed in **fig. 1**, eliminates these problems. While intended as an R-4C retrofit, this circuit performs so well that we also recommend it for other communications uses.

Our circuit is designed around National Semiconductor's LM383T, which, with the R-4C low-voltage supply, can deliver in excess of 2 watts into a 4-ohm load. The LM383 and associated components* can be mounted on a copper-clad board 3.8 cm (1½ inches) square, or another appropriate small heatsink (for a V_{CC} of 16 volts or less). It should be installed just behind the front-panel phone jack, between the passband-tuning capacitor and long i-f shield on which the Sherwood CF-600/6 may be mounted. This location provides access to the speaker lead and detected signal at the audio gain pot. It also keeps the circuit away from power transformer hum fields in the chassis.

circuit precautions

The secret of making the LM383 an uncondition-

*A parts kit will be available from G. R. Whitehouse, Newbury Drive, Amherst, New Hampshire 03031.

ally stable audio amplifier (suitable for field installation in various layout configurations) is our output stabilization network. Proper stabilization is accomplished by connecting a 1.0- μ F monolithic ceramic capacitor (such as Sprague 5CZ5U105X0050C5) with 19-mm (¾-inch) leads directly between pins three and four of the LM383. Use of a lower-value capacitor with significantly longer or shorter leads will virtually guarantee oscillation problems. Tantalum or aluminum electrolytics *cannot* be substituted for the monolithic capacitor.

Other circuit values have been chosen to tailor the audio response for greatest communications intelligibility. As in the original R-4C circuit, low frequencies are rolled off at one end of the needed spectrum; high-frequency shaping is similar to that of our suggested modification.¹ The feedback network has been chosen to provide nearly 40 dB of power-supply ripple rejection, minimizing the need for abnormal amounts of filtering. Gain at 1 kHz is 40 dB.

component selection

As with any high-gain amplifier, feedback and hum loops between the input and output should be avoided. Return all signal and power leads to pin 3, except for V_{CC} bypass, which should be returned to the IC tab with a solder lug.

To reduce component size, the 0.22- μ F and 10- μ F capacitors can be 16-volt (or greater) tantalums. The 200- μ F electrolytic at pin 2 can have a 3-volt rating. The 300- μ F output capacitor should have a minimum rating equal to V_{CC} (20 volts maximum). Sixteen volts is adequate for the R-4C. As mentioned above, a small heatsink is used for a V_{CC} less than 16 volts; above 16 volts a large heatsink. Never exceed a V_{CC} of 20 volts.

installation

To disable the existing amplifier, lift the output

By **J. Robert Sherwood, WBØJGP**, and **George B. Heidelman, K8RRH**, Sherwood Engineering, Incorporated, 1268 South Ogden Street, Denver, Colorado 80210

transistor's collector lead at its solder lug. Also, remove its base or emitter wire, and/or disconnect one end of the driver's 100-ohm collector resistor. Connect the new amplifier's output to the phone jack terminal *with* the sleeved wire from the audio output transformer, and bypass with a 0.01- μ F capacitor. This secondary is still used to provide the needed step-up for anti-vox system.

The only ground return should be a short, thick, insulated wire, run from pin 3 directly to the cable-braid terminal of the audio gain pot (rear section of

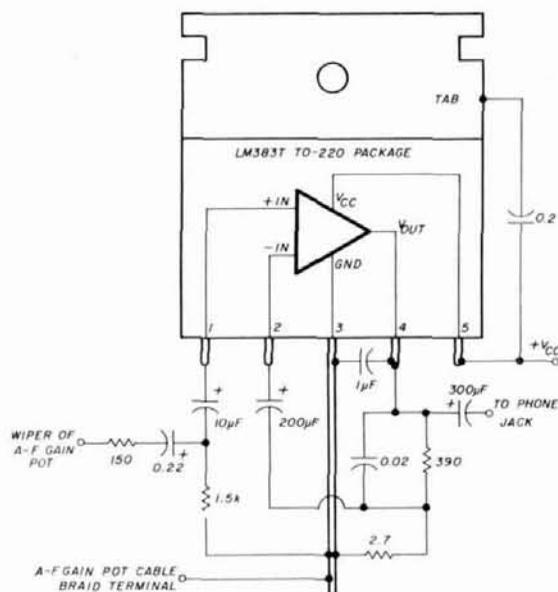


fig. 1. Schematic diagram of the new audio amplifier for the R-4C, based upon the LM3837T audio amplifier IC. Resistors are $\frac{1}{4}$ watt. As pointed out in the text, all ground returns must be made through the connection to pin three to eliminate hum and feedback problems. The 1- μ F monolithic ceramic capacitor *must* have 19-mm ($\frac{3}{4}$ -inch) leads (see text).

the dual control.) Do not allow the board or heatsink to touch any other part of the receiver ground. Next, add a small wire between the audio gain-control braid terminal and a close chassis ground. Disconnect the existing wire from the gain pot center wiper terminal, and connect the new amplifier input to this lug. Connect V_{CC} to the original audio-strip printed circuit board terminal with the blue wire from the audio-output transformer primary.

references

1. R. Sherwood, WB0JGP, G. HeideIman, K8RRH, "Present-Day Receivers — Some Problems and Cures," *ham radio*, December, 1977, page 10.
2. R. Sherwood, WB0JGP, G. HeideIman, K8RRH, "New Product Detector for the R-4C," *ham radio*, (ham notebook), October, 1978, page 94.
3. R. Sherwood, WB0JGP, G. HeideIman, K8RRH, "New Product Detector for the R-4C," *ham radio*, (short circuits), February, 1979, page 94.

ham radio

BUILD YOUR DREAM

ANTENNA

WE SUPPLY THE MATERIALS YOU HAVE THE FUN

Tell us what you need Ask us about our custom antenna packages

6061-T6 DRAWN ALUMINUM TUBING
AIRCRAFT* GRADE PLATED HARDWARE
HIGH* STRENGTH FIBERGLASS SPREADERS
STAINLESS* STEEL ELEMENT CLAMPS
CALL OR WRITE FOR FREE INFORMATION

GL ENTERPRISES

USA

GL ENTERPRISES
ROUTE 1, BOX 10
BROWNSVILLE, WIS.
53008, PH (414) 583-4001

TPL 1/4 KILOWATT LINEAR AMPLIFIER

TPL proudly presents the first true power 1/4KW SSB/AM, FM or CW solid state 2 meter linear amplifier



A remote control plug allows you to operate with the amplifier ON or OFF, or in SSB/AM, FM or CW from the dashboard.

The 2002 utilizes the latest state of the art engineering including micro-strip circuitry and modular construction. The three final transistors combine to produce 250W when driven by 15W or more at 13.8VDC.

POWER INPUT:
5-20W Carrier FM or CW
20W PEP maximum SSB or AM

HARMONIC ATTENUATION:
All Harmonics Attenuated
60 dB or Greater

POWER OUTPUT:
200-250W carrier FM or CW
300W PEP SSB or AM

CURRENT DRAIN:
FM-40 Amps @ 250W
SSB-30 Amps @ 300W PEP

FREQUENCY RANGE:
144 to 148 MHz*
* will operate with slight degradation at 142 150 MHz.

DUTY CYCLE:
FM 50% @ 150W 33% @ 250W
SSB 60% @ 150W 50% @ 250W

Model 2002 \$499.00

can be ordered for repeater application for additional information contact

TPL COMMUNICATIONS INC.

1324 W. 135TH ST., GARDENA, CA 90247 (213) 538-9814

Canada: Lenbrook Industries, Ltd., 1145 Bellamy Rd., Scarborough, Ontario M1H 1H5
Export: EMEC Inc., 2350 South 30th Avenue, Hallandale, Florida 33009

the weekender



the verti-loop a folded whip antenna for vhf mobile operation

Do you want a simple, inexpensive way to improve your 2-meter mobile performance in the fringe areas? How about a 3/4-wavelength vertical on your car roof? The concept sounds mind boggling — but what if it were only 1 meter (3 feet) long? Sound interesting? Try building one of these verti-loops, a name coined for a 3/4-wavelength vertical ground plane compressed to less than 1/2-wavelength long by folding the bottom section into a horizontal loop. The advantage is 2-3 dB gain over the 1/4-wavelength whip, and it still lets you keep the car in the garage. It's an easy weekend project and should cost less than \$3.00 if you already have a roof-mounted antenna or an old discarded mag-mount CB whip. The results will be well worth the effort.

theory

Most vhf mobile operators know that a 1/4-wavelength whip is ideally located in the center of an unobstructed car roof. A compromise, because of physical size, is to use a 5/8-wavelength gain antenna on the trunk lid, where, because of obstructions on most cars, the 2-3 dB of potential gain is usually lost; results may even be inferior to those of the smaller roof-mounted whip.

A 3/4-wavelength ground-plane antenna is resonant, therefore nonreactive, and has a high-current feedpoint. The length of such an antenna may be calculated as half the length of a 3/2-wavelength dipole¹:

$$L = \frac{149.95(N - 0.05)}{f} \quad (1)$$

where L is the 3/2-wavelength dipole length in meters, N is the number of half wavelengths on the

antenna (3), and f is the frequency in MHz (146).

$$L = \frac{149.95(2.95)}{146}$$

$$= 3.03 \text{ meters (119.3 inches).}$$

The vertical length would be half of this, or 1.52 meters (59.6 inches). The antenna impedance would be half of the 3/2-wavelength antenna impedance (105 ohms), or 52.5 ohms.


design

To shorten the 3/4-wavelength vertical to a reasonable size, it was divided into 1/4- and 1/2-wavelength sections, and the 1/4-wavelength section was folded into a loop. The result was the upside-down "halo" antenna depicted in **fig. 1**. The top section was shortened slightly to 91 cm (36 inches), and the bottom section was lengthened slightly to 61 cm (24 inches) for convenient fabrication sizes. When folded into a loop, the bottom section results in a 19-cm (7.5-inch) diameter.

construction

The antenna was constructed very simply using a 2.4 mm × 91 cm (3/32 × 36 inch) stainless-steel welding rod (available at any welding supply shop) as the 1/2-wavelength section, and an ordinary tv uhf loop (available from Sears) as the folded 1/4-wavelength section.

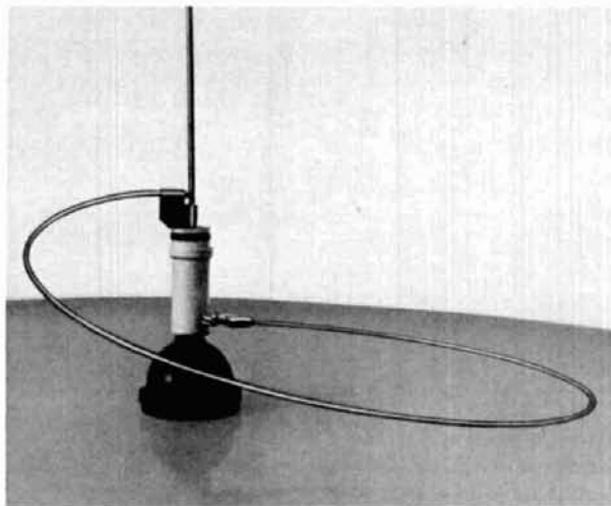To one end of a 5-cm (2-inch) section of plastic tubing (PVC works fine), a threaded stainless steel nut, which matched the threaded end of my rooftop 1/4-wavelength antenna, was epoxied. A piece of wood dowel (or plastic filler) was cemented into the other end of the tube and was drilled for a snug fit for



Close-up of the 3/4-wavelength mobile vertical antenna. It resembles an "upside-down" halo.

By Herb Bresnick, WB2IFV, 16 Creekside Drive, Honeoye Falls, New York 14472

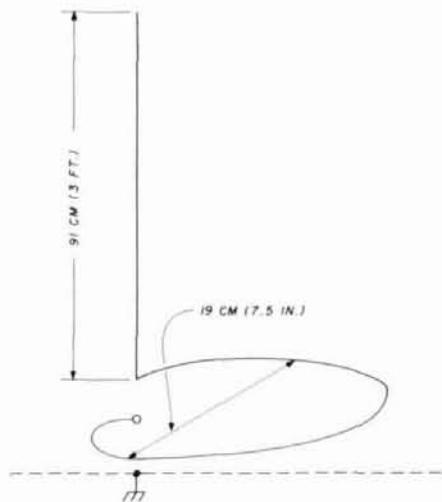


fig. 1. Design of the verti-loop antenna. Antenna is a $\frac{3}{4}$ -wavelength vertical divided into $\frac{1}{4}$ - and $\frac{1}{2}$ -wavelength sections; the $\frac{1}{4}$ -wavelength section is folded into a loop. Total extended length is $\frac{3}{4}$ wavelength on 2 meters. Antenna mounts on your car roof with a plastic base made of PVC tubing.

the stainless rod. A little epoxy will keep it from loosening (fig. 2).

The Sears loop comes with hinged terminals, which were left on to permit fine tuning the antenna. One wire terminal was simply pulled out of its hinge, leaving a spring opening through which the stainless rod was forced. It makes for a snug fit, but permits sliding the loop down to where the rod joins the plastic tube.

The other wire terminal on the loop was cut off (leaving the hinge) and the wire remaining was passed through a small hole drilled in the side of the PVC tube just above the nut, where it was com-


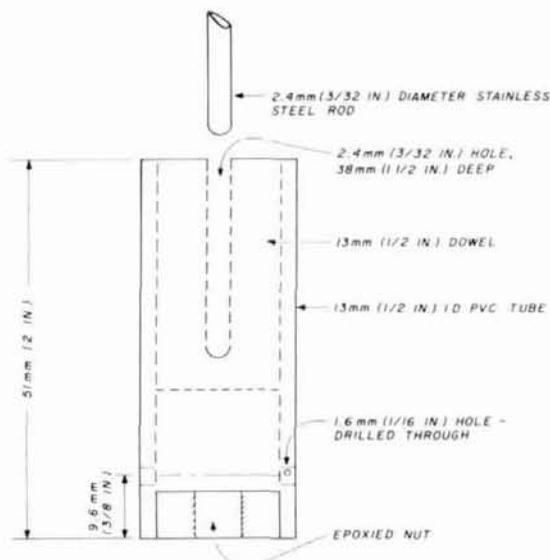


fig. 2. Details of the mounting base. An ordinary tv uhf loop was used for the $\frac{1}{4}$ -wavelength section, or you can use stainless-steel wire.

pressed by the threaded roof stud when the antenna was screwed on.

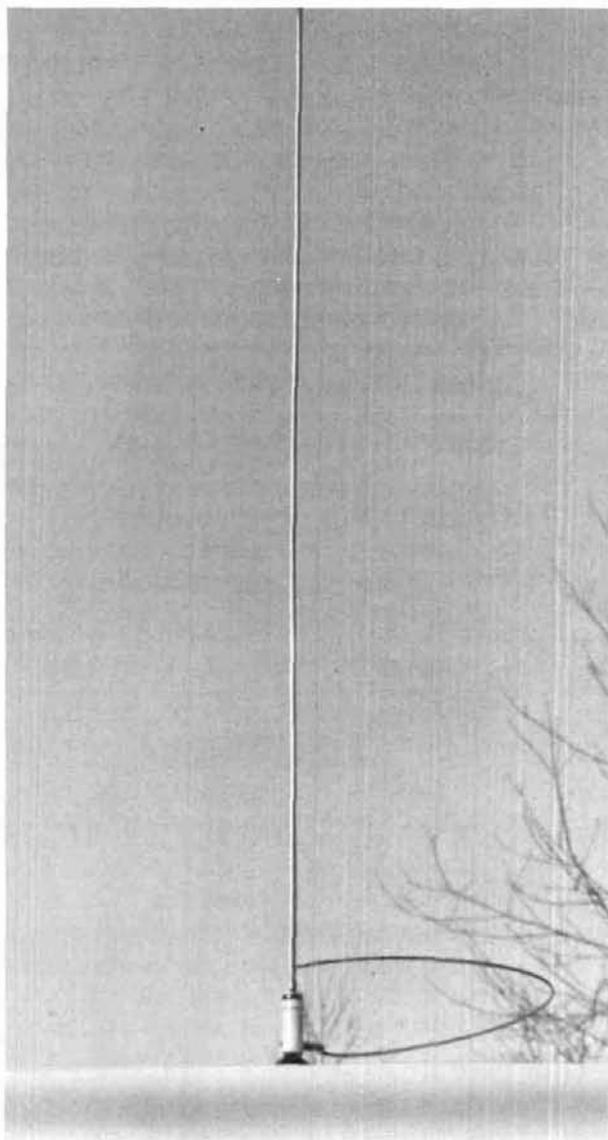The antenna rod should be insulated from the stud except through the loop connection. The design can be modified easily to fit other base mounts or for new installations using a PL259 coax fitting, or even to a



View of the antenna at car-top level.

discarded CB magnetic mount if you don't want to drill a hole into your car roof.

results

With the transmitter on an unused frequency and a SWR meter attached, the loop position was moved on its hinges for minimum SWR. It's not a critical adjustment if the dimensions are followed. I obtained 1.1 to 1.0 SWR with the loop about 2.5 cm (1 inch) from the car roof with the first try. The hinges are stiff enough to maintain the loop position even when

BELDEN

Part Number	MHz	db/100 ft.	db/100 m
 9888 39¢/ft	50	1.2	3.9
	100	1.8	5.9
	200	2.6	8.5
	300	3.3	10.8
	400	3.8	12.5

 8214 25¢/ft.	50	1.2	3.9
	100	1.8	5.9
	200	2.6	8.5
	300	3.3	10.8
	400	3.8	12.5

 8237 21¢/ft	100	2.0	6.6
	200	3.0	9.8
	400	4.7	15.4
	900	7.8	25.6

 8267 25¢/ft	100	2.0	6.6
	200	3.0	9.8
	400	4.7	15.4
	900	7.8	25.6

 8448 16¢/ft	No. of Cond — 8
	AWG (in mm) — 6-22, (7x30), [76], 2-18, (16x30), [119]

 9405 26¢/ft	No. of Cond — 8
	AWG (in mm) — 2-16, (26x30), [152], 6-18, (16x30), [117]

MADISON ELECTRONICS SUPPLY, INC.

1508 McKINNEY • HOUSTON, TEXAS 77002

713/658-0268



GREGORY ELECTRONICS
*The FM Used
Equipment People.*

Save
\$20



Motorola Motrac

U43HHT-1100E, 12 volts, 150-170 MHz, 40 watts, Single Frequency, Fully Narrow Band, with accessories.


NOW

~~\$278~~
\$258.



GREGORY ELECTRONICS CORP.

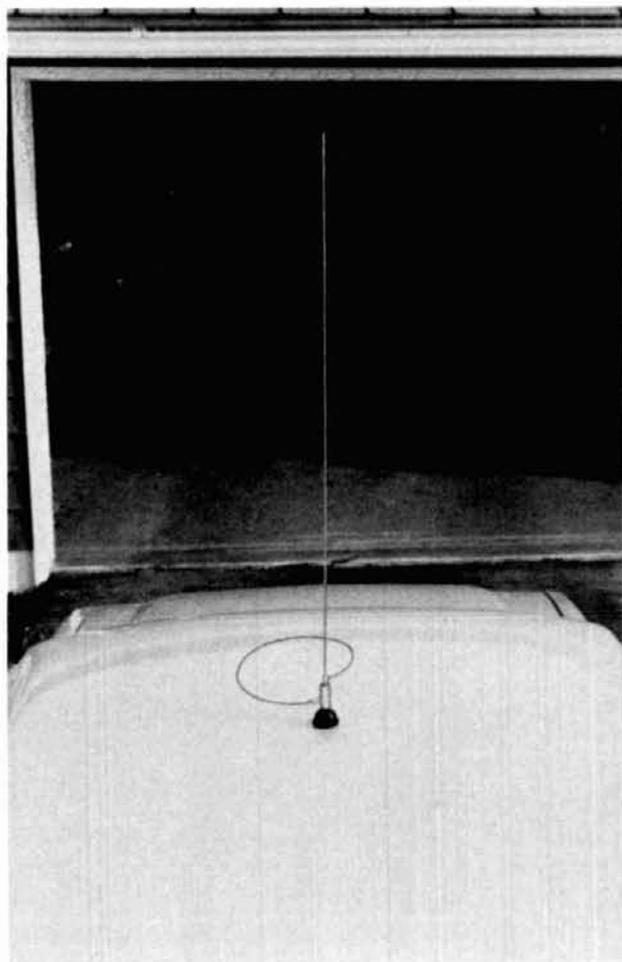245 Rt. 46, Saddle Brook, N.J. 07662
Phone: (201) 489-9000



Author's antenna is a full-fledged $\frac{3}{4}$ -wavelength vertical but fits under garage opening without dismantling. The stainless-steel radiator bends easily to 30-40 degrees from vertical.

driving over bumpy roads. I've built three of these antennas at a cost of \$2.00-\$3.00 each. All have resonated with practically no adjustment.

Actual dB measurements on the antenna have not been made; however, tests indicate a marked improvement over the 1/4-wavelength whip. One repeater that was barely readable is now almost full quieting into my receiver. Reports from friends are that noise on my signal (from a portable HT in the car) was all but gone and no evidence of mobile flutter occurred.

Best of all the car still fits into my garage, and, although the top of the antenna does hit the entrance, the stainless-steel rod is flexible enough to recover from a 30- or 40-degree bend. The antenna has a somewhat futuristic look to it — at least it looks different from your good buddy's 11-meter job!

reference

1. *The ARRL Antenna Book*, 12th edition, 1970, page 33.

ham radio



THE Wilson GIVE-A-WAY

Wilson Electronics announces a factory authorized rebate program. Here's how it works:

Purchase a TT-45 and a System Three at the same time and Wilson will give you a factory 5% rebate from the price you paid for the package. You can use this to pay for the concrete to install it, or buy the XYL a little something to keep her happy! Or... we will give you, at no charge, a M-27, the best 7 element, 2M beam available today! The choice is yours to make!

Just send Wilson the receipt of your purchase from your dealer, showing your cost, and let us know what you want - 5% cash, or a M-27. But hurry! This offer starts April 1, expires midnight, April 30, 1979, and receipt must be mailed before June 1, 1979.

Don't wait! See your nearest dealer to take advantage of this great Give-A-Way!

SPECIFICATIONS

TT-45 TOWER

- Maximum height, 45'
 - 800 lbs. winch with padlock feature
 - 2800 lb. raising cable
 - Totally freestanding with proper base
 - Total weight, 189 lbs.
- Recommended accessories:
RBRF-10, SBRF-10, CBRF-10.


The TT-45 is a freestanding tower. Ideal for installations where guys cannot be used. If the tower is not being supported against the house, the proper base fixture accessory must be selected.

SY-3 TRI-BAND ANTENNA

Band MHz	14-21-28	Turning radius	15' 9"
Maximum power input	Legal limit	Maximum mast diameter	2" O.D.
Gain (dBd)	8 dB	Surface area	5.7 sq. ft.
VSWR at resonance	1.3:1	Wind loading @ 80 mph	114 lbs.
Impedance	50 ohms	Assembled weight (approx)	37 lbs.
F/B Ratio	20 dB	Shipping weight (approx)	42 lbs.
Boom (O.D. x length)	2" x 14' 4"	Direct 52 ohm feed or balun	
No. of elements	3	Maximum wind survival	100 mph
Longest element	27' 4"		

M-27 - 7 ELEMENT 2M BEAM

Band MHz	144-148 MHz	Beam width @ 3 dB pt.	27 degrees
Gain	11 dB	Turning radius	37' 13"
VSWR	1.2:1	Mast diameter (O.D.)	1" - 1 1/2"
Impedance	50 ohms	Surface area	44 sq. ft.
Boom (O.D. x length)	1" x 64"	Wind loading @ 80 mph	5.5 lbs.
Number of elements	7	Shipping weight (approx)	6.5 lbs.
Longest element	40"	Assembled weight (approx)	3.5 lbs.

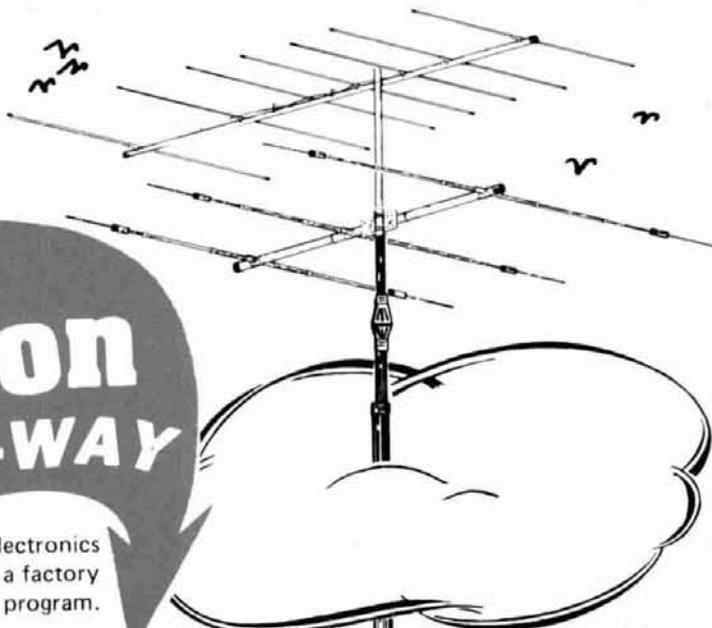

See what just some of the many satisfied Hams say about the Wilson Antennas.

My SY-3 performs like a Monobander, and loads up as easy as a dummy load!
... Jim Rafferty N6RJ

I always boast that my Wilson Antennas are the best in the world.
... Paul Panzera W2POQ

Best move I've ever made in my Hamming career. Tax for a great antenna!
... John Sklephowicz VE3JPR


Don't forget the WV-1 for the best in vertical needs. The WV-1 is the 10-40m Antenna you should consider!

ACT NOW!

Buy the WV-1 and Wilson will treat you to the Radial Kit ... FREE of charge!

WV-1 SPECIFICATIONS:

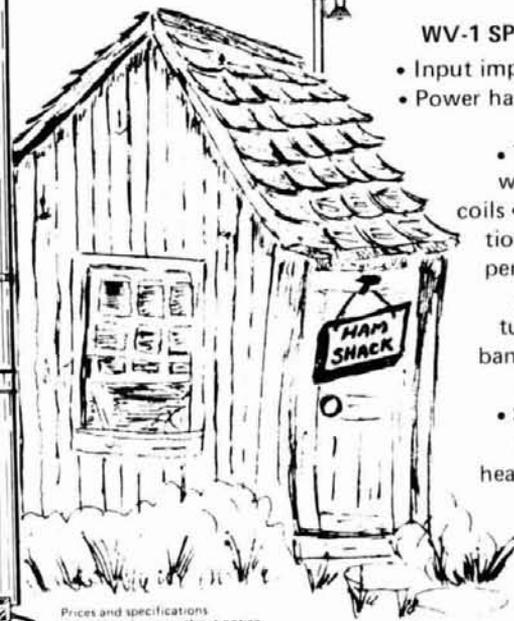- Input impedance: 50 ohms
- Power handling capability: Legal limit
- Two High-Q traps with large diameter coils
- Low angle radiation omnidirectional performance
- Taper swaged aluminum tubing
- Automatic bandswitching
- Mast bracket furnished
- SWR: 1.1:1 on all bands
- 1 1/2" O.D. heavy wall aluminum tubing
- Does not require guying
- Overall length: 19' 8"



Prices and specifications subject to change without notice



Consumer Products Division

Wilson Electronics Corp.

A Subsidiary of REGENCY ELECTRONICS, INC.

4288 South Polaris Avenue • P. O. Box 19000 • Las Vegas, Nevada 89119
Telephone (702) 739-1931 • TELEX 684-522

DSI Super Meter

Transistor Tester — VOM

Diode Protected • Fused • Gold Plated Selector Switch



- DC VOLTAGE
- DC CURRENT
- AC VOLTAGE
- Ω RESISTANCE
- AF OUTPUT — DB
- 20k Ω PER VOLT
- HFE DC AMP FACTOR
- ICEO LEAKAGE

\$ 29⁹⁵
MODEL
YF-370


COMPARATIVE VALUE 49⁹⁵

YF-370 \$29.95
Shipping, Handling and Ins. ... \$3.00

SPECIFICATIONS

Measurement	Measurement Ranges	Accuracy
DCV	0 - .1V - .5V - 2.5V - 10V - 50V - 250V - 1000V	$\pm 3\%$ fs
ACV	0 - 10V - 50V - 250V - 1000V 30Hz to 30kHz	$\pm 4\%$ fs
DCA	0 - 50 μ A - 2.5ma - 25ma - .25A	$\pm 3\%$ fs
Ω	.2 to 20m Ω Range x 1 x 10 x 1k x 10k	$\pm 3\%$ arc
dB	+ 10db ~ + 22db for 10VAC	$\pm 4\%$ fs
ICEO	0 - 150 μ A x 1k 0 - 15ma x10 0 - 150m x 1	$\pm 3\%$ arc
HFE	0 - 1000 @ x 10 $\frac{I_c}{I_n}$	$\pm 3\%$ arc

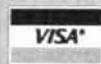Every YF-370 is factory assembled, tested, and includes diode protected meter movement with a fused input and an extra fuse. The switch assembly has double wiping gold plated contacts to assure years of trouble-free service. At this low price buy two...one for the car and one for the shop.



CALL TODAY TOLL FREE: (800-854-2049) Calif. Res.
CALL (800-542-6253) TO ORDER OR RECEIVE MORE
INFORMATION ON DSI's FULL PRODUCT LINE OF
FREQUENCY COUNTERS RANGING FROM 10HZ
TO 1.3GHZ.


TERMS: MC — VISA — AE — Check — M.O. — COD in U.S. Funds.
Orders outside of USA & Canada, please add \$5.00 additional to cover
air shipment. California residents add 6% Sales Tax.

DSI INSTRUMENTS, INC.

7924 Ronson Road, Dept. G, San Diego, CA 92111

DSI COMMUNICATIONS SERIES

1.3GHz — 1GHz — 700MHz

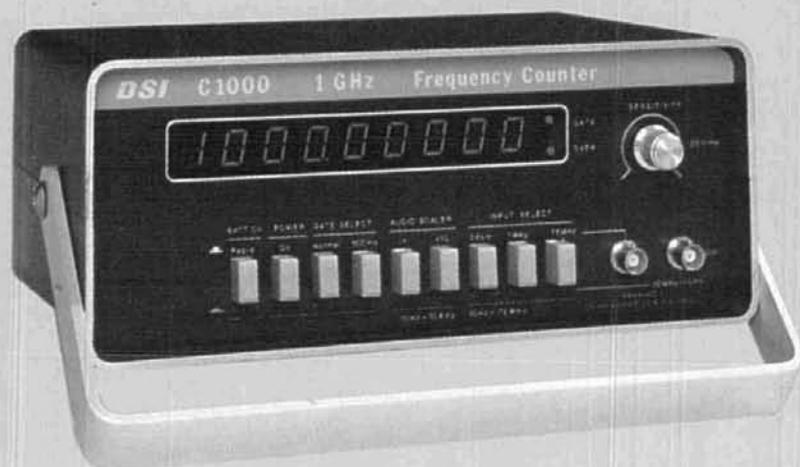

MODEL C1000 10Hz to 1GHz

\$499⁹⁵

- INCLUDES BATTERY PACK
- AUTO ZERO BLANKING
- AUTO DECIMAL POINT
- 10MHz TIME BASE

Accuracy . . . that's the operational key to this rugged advanced design Model C1000 1GHz frequency counter . . . a significant achievement from DSI. That's because you get . . . **.1 PPM** 0° to 40°C proportional oven time base . . . Built in 25dB preamplifier with a 60dB adjustable attenuator . . . x10 & x100 audio scaler which yields .01 Hz resolution from 10Hz to 10KHz equivalent to 10 sec. & 100 sec. Gate Time . . . Selectable .1 & 1 sec. time base and 50 ohms or 1 meg ohm input impedance . . . Built-in battery charging circuit with a Rapid or Trickle Charge Selector . . . Color keyed high quality push button operation . . . All combined in a rugged black anodized (.125" thick) aluminum cabinet. The model C-1000 reflects DSI's on going dedication to excellence in instrumentation for the professional service technician, engineer, or the communication industry.

MODEL C700 50Hz to 700MHz

\$369⁹⁵

- INCLUDES BATTERY PACK
- AUTO ZERO BLANKING
- AUTO DECIMAL POINT
- 10MHz TIME BASE

ALL NEW! All UNPARALLELED DSI QUALITY! The model C 700 700 MHz frequency counter features . . . **.2 PPM** 0° to 40° C proportional oven time base . . . 25db preamplifier with a 60db adjustable attenuator. Built in battery charger with a rapid or trickle charge selector . . . Combined in a rugged (.125" thick) aluminum cabinet makes the C700 ideal for the communication industry and professional service technician.

3600A OWNERS: Up date your 3600A frequency counter to a C 700 includes, new back board, **.2PPM** proportional oven, 25db preamplifier, rugged .125" thick aluminum cabinet, order 3600A-700. Unit must be returned to DSI factory for modification.

DSI — GUARANTEED SPECIFICATIONS — FACTORY ASSEMBLED — MADE IN USA

Model	Frequency Range	Proportional Oven Accuracy Over Temperature	50Hz To 75MHz	75MHz To 500MHz	500MHz To 1GHz	Number Of Digits	Size Of Digits	Power Requirements	Size
C700	50Hz to 700MHz	.2PPM 0° to 40°C	50MV	10MV	NA	8	.5 Inch	115 VAC-BATT 8 to 15VDC	3"H x 8"W x 6"D
C1000	10Hz to 1GHz	.1PPM 0° to 40°C	20MV	1MV	>50MV	9	.5 Inch	115VAC-BATT 8 to 15VDC	4"H x 10"W x 7 1/2"D

— All Units Are Factory Assembled, Tested And Carry A Full 5 Year Limited Warranty —

FREE

Strongest warranty in the counter field.
Satisfaction Guaranteed.

FOR MORE INFORMATION

Call Toll Free: (800) 854-2049
DSI INSTRUMENTS, INC.

California Residents, Call Collect: (714) 565-8402

VISA • MC • AMERICAN EXPRESS • CHECK • MONEY ORDER • COD

7914 RONSON ROAD, #G, SAN DIEGO, CA 92111

Model C 700 **\$369.95**

3600A-700 Factory Update (3600A only)
Includes Labor & Re-Calibration **\$199.95**

Model C 1000 **\$499.95**

Opt. 01 1.3 GHz (C1000 only) **\$ 99.95**

Opt. 02 .05 PPM 10MHz Double Oven
0° to 50° C Time Base (C1000 only) **\$129.95**

Ant. 210 Telescopic Ant./BNC Adapter **\$11.95**

the jammer problem:

some interesting solutions

The incidence of jammers is increasing — here's an interesting approach to the problem

In this paper we use the basic ideas of the scientific method in solving some interesting problems. It is important to have a clear understanding of, and agreement on, the nature of observation, cause and effect, hypotheses and testing of these hypotheses.

Science begins with observation. The scientific worker uses his mind to imagine how something might be constructed or how a problem may be solved. He knows that only by examining his observations can he determine if his imaginings correlate with the real world.

statement of the problem

The locale is a large city in the United States. In this city many Radio Amateurs abound. The problem we are about to address (and solve using the scientific method) concerns specific specimens. These specimens are Radio Amateurs (and others who are not legitimate Radio Amateurs) who persist in jamming the 2-meter repeater stations in this city. These specimens particularly delight in causing a disruption in

radio communications over the repeater links by using various schemes.

The problem is to locate these specimens using three scientific methods: mathematical methods, methods from theoretical physics, and methods from experimental physics.

mathematical methods

Several mathematical methods are available to us to ferret out the offending 2-meter jammer. The mathematical methods we shall enumerate are easily seen to be applicable, with obvious formal modifications, to similar situations in other parts of the globe. As with other branches of knowledge to which mathematical techniques have been applied in recent years, the mathematical techniques of ferreting out 2-meter ham jammers has a singularly unifying effect on the most diverse branches of the exact sciences.

Hilbert, or axiomatic method

We place the culprit in an imaginary cage, which we have previously defined in time and space by using established techniques. We then introduce the following logic system:

Axiom 1. The class of jammers in the cage is non-void.

Axiom 2. If there is a jammer in the city, there is a jammer in the cage.

Rules of procedure. If p is a theorem, and p implies q is a theorem, then q is a theorem.

Theorem 1. There is a jammer in the cage.

Conclusion. Approach the cage with caution. Lift the jammer gently out of the cage, shave his beard, cut his mike cord, and put him in a playpen.

By Nuryev Sidelbandsk, UX3PU

method of inverse geometry

We place a spherical cage in the city, enter it, and lock the cage. We then perform a geometric inversion with respect to the cage. The jammer is then inside the cage and we are outside.

Conclusion. We proceed as in the method of Hilbert, above, except in this case we call in federal troops with Zen guns, who quickly dispose of the specimen. We then donate his equipment to a worthy organization.



"Theorem 1 — there is a jammer in the cage."

method of projective geometry

Without loss of generality, we may regard the city as a plane. We project the plane into a line, then we project the line into an interior point of the cage that contains the jammer. We then perform a geometric involution of catharsis, which in turn projects the jammer into the city jail (without bail).

Bolanzo-Weierstrass method

In this method we bisect the plane by a line running north-south. The jammer is either in the east portion or in the west portion; let us assume he is in the west portion. We bisect this line with another line running east-west. The culprit is either in the north portion or the south portion. Let us suppose he is in the north portion.

We continue this process indefinitely, constructing a sufficiently strong force about the chosen portion



"Call in the troops."

at each step. As the volume of the chosen portion approaches zero, the jammer is ultimately surrounded by a fence of arbitrarily small perimeter. The specimen (jammer, if you will) is thus a victim of the confusion syndrome. He begins to believe he has, at last, become rational. It is now relatively easy to approach the jammer. We place a cowbell into the jammer's left hand and into his right hand we place a telegraph key, which is connected to a code-practice oscillator. It is now a very critical moment for the jammer. He begins to send messages to himself with the cowbell and answers himself with the telegraph key. We realize that the messages make no sense because the jammer is not comfortable with the Morse code.

Conclusion. To reduce the confusion factor in the jammer's mind, we gently tap him on the head with a small mallet. As we manipulate the mallet (which we do using the Morse code), the jammer begins to get the message, to wit: "Jamming is a no-no. Jamming is a no-no. Jamming is a no-no." I shall leave as an exercise for the student the decision as to how long we subject the jammer to this action.

Cauchy, or function-theoretical, method

In this mathematical method we consider a jammer-valued function, $f(x)$, where x is nondimensional but critical to resolving the problem.

Let there be a function, $f(x)$, and let S be the cage




"The jammer is not comfortable with the Morse code."

enclosing the jammer. Consider the integral

$$\frac{1}{2\pi i} \int_0^C \frac{f(z)}{z-s} dz \quad (1)$$

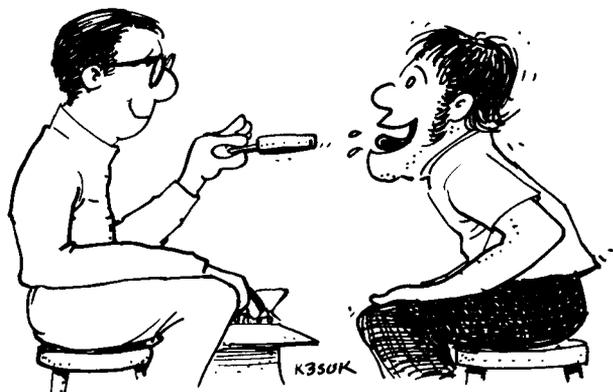where C is the boundary of the plane of encounter. Its value, after appropriate manipulation of eq. 1, is



"Ply him with popsicles."

that of $f(S)$. Therefore, we have a culprit in the cage. We then dispose of him appropriately. In this case we ignore his stupid mouthings on the repeater but send a male nurse armed with ten-dozen Popsicles. The nurse plies the jammer with Popsicles until the jammer decides to throw up (a very effective problem-solving method).

methods from theoretical physics

We now examine some theoretical methods for dealing with the 2-meter jammer. These methods have not been proved in practice but offer some interesting food for thought for the theoretician.

Dirac method

We observe that jammers are known to use wild methods to attract attention. Therefore these jam-



"Perhaps the jammer is not really wild."

mers must be considered wild men. But, according to the scientific method, we must temper our observations with caution. Perhaps the jammer in question is not really wild but is somewhat tame with a rather limited mentality. Perhaps he needs help. Why punish him if, indeed, he's not really responsible for his actions? The author has a proven formula which, if applied to these situations, will produce good results in many cases. For those interested I shall be happy to furnish the method and appropriate action. Please send a self-addressed, stamped envelope for an immediate reply.

methods from experimental physics

Using the methods from experimental physics, we are able to deal positively with the problem of 2-meter jammers. It should be noted that these methods are also valid for other inconsiderate jammers in the other Amateur bands.

thermodynamic method

We construct a semipermeable membrane, permeable to everything except jammers, and sweep it across the plane of interest (*i.e.*, the city in question). We also add a pot of hot water to the apparatus. As the semipermeable membrane is swept across the city, it picks up the jammers. The jammers are enmeshed in the membrane and, having nothing else to do, immediately start brewing coffee. We immediately detect the aroma of brewing coffee, descend on the culprits, and capture them in a loony net. We then enlist the aid of local authorities to dispose of the problem.

magnetomatic method

In implementing this technique we plant a large bed of popcorn arranged in an ellipse, whose major axis lies along the direction of the horizontal component of the earth's magnetic field. At one focus of this ellipse we place a cage (with strong iron bars). We then distribute over the plane in question large quantities of magnetized spinach (*spinacia oleracea*), which has high ferric content.

The magnetized spinach is eaten by various denizens of the locality, which are in turn eaten by the 2-meter jammers. The jammers, having partaken of commodious amounts of popcorn, are then oriented parallel to the earth's magnetic field. This causes a beam of jammers to be focused onto the cage. Since the jammers are full of our specialized popcorn and, by indirect ingestion, magnetized spinach, it is an easy matter to zap the jammers. The benefit of this method is that we can dispose of the culprits in large numbers.

ham radio

A dual HF wattmeter at a great low price!

Reads both forward and reflected power at the same time!

Keep tabs on your transmitter with this handy new dual HF wattmeter. It measures both forward and reflected power for frequencies between 1.8 and 30 MHz (160, 80, 40, 20, 15 and 10 meters). It measures transmitter output up to 200/2000 watts in the forward direction and 50/500 watts reflected. Two front panel meters monitor forward and reflected power and one switches to give you a direct reading of SWR from 1:1 to 3:1. A factory assembled and calibrated sensor gives the HM-2140 far better accuracy and reliability than other kit-type meters. In fact, full scale accuracy in the 200/2000 watt forward ranges is $\pm 5\%$, and $\pm 7.5\%$ on reflected ranges. The front panel

forward power meter can be switched to read PEP or average power. Operation on a single 9-volt battery or optional AC adapter makes the HM-2140 convenient and versatile. At \$69.95, and with just a few hours of enjoyable kitbuilding, you'll have a wattmeter that can be a real aid to your station!

**HEATHKIT®
AMATEUR
RADIO**

See us at the Dayton Hamvention, April 27-29.

Price is mail order net F.O.B., Benton Harbor, Michigan.
Prices and specifications subject to change without notice.



There's More for the Ham at Heath!

Mail coupon at right for your

FREE

Heathkit Catalog!

Read about nearly 400 electronic kits you can build yourself for fun, for satisfaction and for savings!

If coupon is missing, write
Heath Company, Dept. 122-520
Benton Harbor, Michigan 49022



HEATH
Schlumberger

Heath Company, Dept. 122-520
Benton Harbor, Michigan 49022

Please send me my FREE Heathkit Catalog.
I am not receiving your current catalogs.

Name

Address

City State

AM-388 Zip

**FREE
CATALOG**

TS-120S...A big little rig.



EW! It's a compact, up to 200 watts PEP input, all solid-state HF transceiver with such standard features as built-in digital readout, IF shift, new PLL technology ...and requires no tuning!

Exciting and perfect for car or ham shack use! But, there's more to say about the TS-120S! This unique all solid-state HF, SSB/CW transceiver produces a hefty signal and also offers a lot of other great features in a very attractive, compact package.

FEATURES:

- All solid-state with wideband RF amplifier stages. No final dipping or loading, no transmit drive peaking, and no receive preselector tuning! *Just dial your frequency and operate!*
- Five bands, plus WWV. Transmits and receives on 80/75, 40, 20, 15, and all of 10 meters...and receives WWV on 15 MHz.
- 200 watts PEP (160 watts DC) input on 80-15 meters, 160 watts PEP (140 watts DC) input on 10 meters. LSB, USB, and CW.
- Digital frequency display (standard). 100-Hz resolution. Six digits. Special

green fluorescent tubes eliminate viewing fatigue. Analog subdial, too, for backup display.

- IF shift (passband tuning), to remove adjacent-frequency interference and sideband splatter.
- Advanced PLL circuit, which eliminates need for heterodyne crystal element for each band. PLL lock frequency, CAL marker signal, and counter clock circuit use single reference frequency crystal. Simplifies circuitry, improves overall stability. Also improves transmit and receive spurious characteristics.
- Attractive, compact design. Measures only 3½" high X 9¼" wide X 13½" long, and weighs only 4.9 kg (11.7 lbs.). A perfect size for convenient mobile operation and rugged enough for either mobile or portable use. Also has all the desired features for optimum ham-shack operation at home.

- Noise blanker. You'll wonder where the ignition noise went.

See the big little TS-120S rig and matching accessories (VFO-120 remote VFO, SP-120 external speaker, PS-30 AC power supply, MB-100 mobile mounting bracket, AT-120 antenna tuner and YK-88C CW Filter) at your nearest Authorized Kenwood Dealer!



**STILL AVAILABLE...
KENWOOD TS-520S**

The DXer's Choice.



Kenwood's TS-820S has everything the Amateur Operator could want in a quality rig.

Time proven over thousands of hours of operating time, the Kenwood TS-820S has become the preferred rig for those individuals interested in high reliability. And, the TS-820S has every feature any Amateur could want for operating enjoyment, on any band, from 160 through all of 10 meters... plus an RF speech processor in the transmitter, IF shift and sharp filters in the receiver. All combine to give optimum performance under all conditions.

You can always tell who's running a TS-820S. Its superb quality stands out from all the other rigs on the band...and when the QRM gets heavy the TS-820S's adjustable RF speech processor,

utilizing a 455-kHz circuit to provide quick-time-constant compression, will get the message through. RF negative feedback is applied from the final to the driver to improve linearity, and third-order products are at least -35 dB. Harmonic spurious emissions are less than -40 dB and other spurs are less than -60 dB.

RF input power is 200 W PEP on SSB, 160 W DC on CW, and 100 W DC on FSK. Receiver sensitivity is better than 0.25 μ V for 10 dB S/N.

The TS-820S from Kenwood! See it today at your nearest Authorized Kenwood Dealer.

 **KENWOOD**
...pacesetter in amateur radio

TRIO-KENWOOD COMMUNICATIONS INC.
1111 WEST WALNUT/COMPTON, CA 90220

variable-frequency audio filter

Here is a tunable, inexpensive, two-IC audio filter that plugs into the receiver phone jack. It will drive headphones or a low-impedance speaker up to two watts if necessary. It operates from a single power supply that requires no regulation, thus it could be easily incorporated into some of the direct-conversion receivers used in QRP rigs.^{1,2} It will also add to the selectivity of any receiver that lacks a sharp CW filter. Used with an ssb receiver, the tunability of the filter allows you to eliminate an unwanted signal by using the high or low skirt of the ssb filter and then peak the desired signal at whatever frequency results.

The circuit is that of the state-variable filter,³ using three op amps (fig. 1). The LM324 IC used in this design has four op amps on the same chip, so the extra amplifiers don't add much to the cost or wiring

selected as a compromise between sharpness and ringing. Circuit *Q* comes out to 15. While no ringing is noticed, the noise definitely takes on the pitch of the frequency selected. The value of this resistor may be changed to suit your needs without altering the tuning range. The LM380 was added to the filter circuit to drive hi-fi headphones or a loudspeaker directly; the filter will drive almost anything that the receiver will drive.

With the values shown, the tuning range is from 800 Hz - 2 kHz. Voltage gain is close to unity overall, so the receiver gain control sets the signal level.

audio-frequency characteristics

The frequency-controlling network is designed to operate with a dual 1-megohm pot. In one model that was built, a dual linear-action slide pot was used and


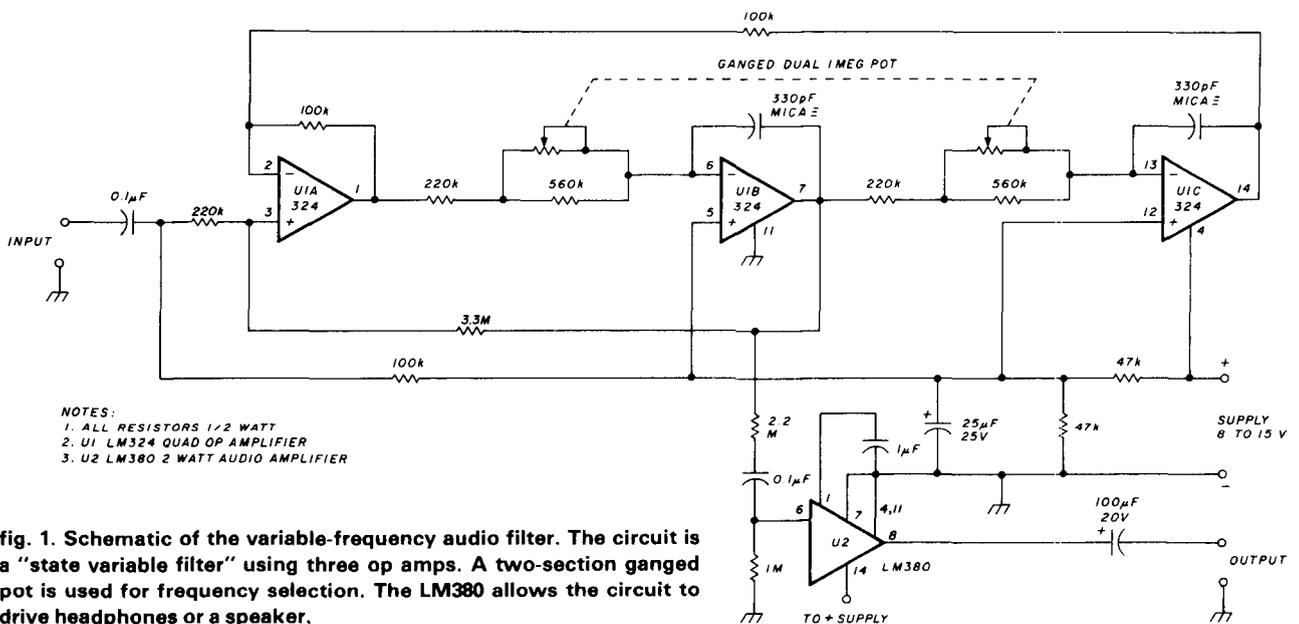


fig. 1. Schematic of the variable-frequency audio filter. The circuit is a "state variable filter" using three op amps. A two-section ganged pot is used for frequency selection. The LM380 allows the circuit to drive headphones or a speaker.

complexity. Two identical integrator circuits control the frequency response, so only a two-section ganged pot is necessary for frequency selection. The *Q*, or sharpness, of the filter is controlled by a single resistor. The 3.3-megohm value shown in fig. 1 was

By Lew Fitch, W4VRV, 109 Robin Street, Clemson, South Carolina 29631

its action was very pleasing. Two single slide pots could probably be mechanically linked to give the same effect. The extra resistors connected in series and parallel with the ganged pots give audio band-spread by allowing the full resistance change of the ganged pots to alter the frequency over less than two octaves. They also make tracking of the ganged pots less critical. If a pot with a logarithmic taper is used,

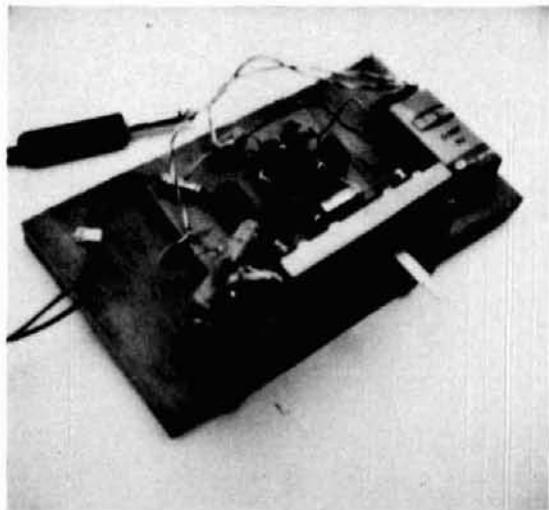

In this model of the variable-frequency audio filter, a dual, slide action linear potentiometer has been used. Because of the high current drain, the 9-volt battery will have to be replaced with an ac supply for permanent installation.

it should be connected for the most linear frequency variation.

If you want to design for a different frequency range, or use a different value of dual pot, the filter peak frequency is given by $f = 1/2\pi RC$. Plugging in the maximum and minimum resistance values will give the frequency extremes. For example, in fig. 1 when the 1-meg pot is at a maximum, total resistance between pins 1 and 6 is 220k in series with 560k, paralleled by 1 meg. This is 578k ohms, and gives 812 Hz in the formula. When the 1-meg pot is at zero resistance, the 560k resistor is shorted and the resistance in the formula is 220k. This gives 2192 Hz. These values are all for capacitors of 330 pF.

The circuit draws about 11 mA at 12 volts with no signal. This current increases to about 35 mA for fairly loud signals. It would be possible to operate the filter from a 9-volt transistor battery, but not for long periods of time. The feedback loops in the circuit and the 47k divider resistors stabilize the operating point of the integrators at half the supply voltage, so regulation isn't necessary.

This filter is not the solution to all interference problems, but it will allow you to selectively boost one frequency 10 dB more than another only 200 Hz away. That can make the difference between a useful contact and a marginal one.

references

1. Jay Rusgrove, W1VD, "A 20-Meter High-Performance Direct-Conversion Receiver," *QST*, April 1978.
2. "A Direct Conversion Kilogram," *The ARRL Handbook*, 1977.
3. Howard Berlin, W3HB, "The State-Variable Filter," *QST*, April 1978.

ham radio

MORE FEATURES FROM ALLIANCE!



HD-73 HEAVY-DUTY ROTATOR

with exclusive Dual-Speed Control!

For antennas up to 10.7 sq. ft. of wind load area. Mast support bracket design permits easy centering and offers a positive drive no-slip option. Automatic brake action cushions stops to reduce inertia stresses. Unique control unit features DUAL-SPEED rotation with one five-position switch. SPECIFICATIONS: Max. wind load bending moment—10,000 in.-lbs. (side-thrust overturning); Starting torque — 400 in.-lbs.; Hardened steel drive gears; Bearings — 100-3/8" diameter (hardened); Meter — D'Arsonval, taut band (backlighted). There's much, much more — so get the whole story!

Mail this coupon for complete details!

YES! Send me complete details on the HD-73!
 Give me the name of my nearest dealer!

NAME _____

ADDRESS _____

CITY _____

STATE _____

ZIP _____



The ALLIANCE Manufacturing Co., Inc., Alliance, Ohio 44601
A NORTH AMERICAN PHILIPS COMPANY

Maker of the famous Antenna Rotator . . . Alliance Tenna-Rotor® . . . "TV's Better Color Getter!"

© 1978 The Alliance Mfg. Co., Inc.

HF Cushcraft 3-band antennas
may be imitated, but their
performance won't be duplicated.

18-foot (5.5m) boom uses 2 1/8" (5.4cm) OD
hard-drawn 6083-T382 aluminum tubing for
maximum strength. No external bracing is
required. Weatherproof end caps are
provided.

Feedpoint connections and trap
fasteners are stainless steel for
long life.

Element-to-boom brackets use 1/4" (6mm)
thick aluminum mounting plates and
hardware, and are designed to reduce stress
at this critical point. Use of double
thickness aluminum tubing elements at the
boom-mounting point contributes to the
high wind survival rating of the antenna.

Heavy-duty mast-mounting bracket has been
carefully engineered for maximum strength and
minimum weight. Use of bright zinc-plated
hardware eliminates problems with rust and
corrosion. A 2" (5cm) OD heavy-wall mast is
recommended.

SPECIFICATIONS

Model	ATB-34
Gain 20 meters	7.5 dBd
15 meters	7.5 dBd
10 meters	7.5 dBd
Front-to-back ratio	
20 meters	30 dB
15 meters	22 dB
10 meters	18 dB
3dB Beamwidth	~ 62°
Normal Input Impedance	50 Ω
Power Handling	2000 watts PEP
Boom length	18' (5.5m)
Longest Element	32'8" (9.95m)
Turning radius	18' 9" (5.7m)
Wind area	5.4 ft ² (0.5 m ²)
Weight (assembled)	42 lbs (19.1 kg)
Maximum mast OD	2.5" (6.3 cm)



cushcraft
CORPORATION

P.O. Box 4680, 48 Perimeter Road
Manchester, N. H. 03108

ATB-34[®]

THE COMPLETE 3-BAND ANTENNA




Elements are manufactured from high-strength hard-drawn aluminum tubing for maximum durability and long life. The element diameter tapers from 1 1/4" (3.2cm) OD at the center down to 5/8" (1.6cm) OD at the end to reduce sag and minimize wind resistance. Weatherproof end caps are provided for all elements.

Exclusive low-profile high-Q traps provide automatic bandswitching on 10, 15, and 20 meters. Unique design allows each trap to be individually tuned at the factory. Weatherproof covers ensure low SWR performance under all weather conditions.

10-15-20 METERS

The Cushcraft ATB-34[®] 3-band antenna offers the no-compromise performance of a single-band Yagi on 10, 15, and 20 meters and represents the best in state-of-the-art antenna design — a nonsense combination of precision electrical engineering, skillful mechanical layout, and modern manufacturing techniques. The antenna's rugged construction, broad bandwidth, and four active elements give superb performance and outstanding front-to-back ratio on all three bands. Quality workmanship and the use of the best available materials give an estimated wind survival rating of 90 mph.

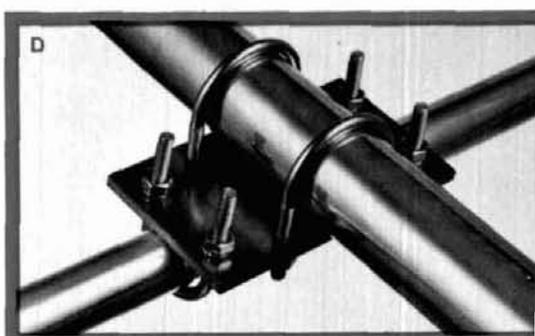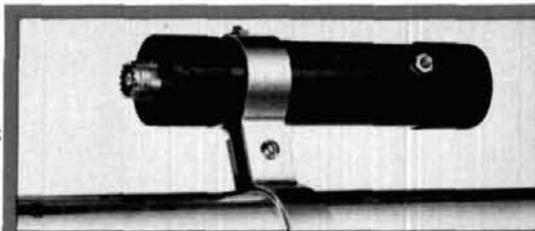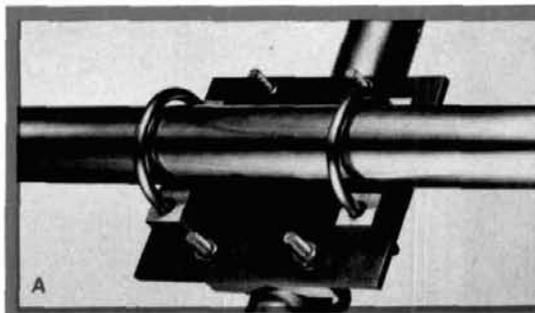The ATB-34[®] gives better performance than most single-band beams, yet is easier to install and keep in the air than larger, heavier beams. Forward gain of the ATB-34[®] is 7.5 dBd on all bands; front-to-back ratio is nominally 30 dB on 20 meters; 22 dB on 15 meters; and 18 dB on 10 meters. Nominal input impedance is 50 ohms; VSWR is 1.5:1 or less at resonance.





A. Heavy-duty mast-mounting bracket for Cushcraft 3-band antenna uses solid aluminum pillow blocks and bright zinc-plated steel hardware for maximum strength and reliability.

B. High-Q coaxial traps are wound with no. 10 aluminum wire (epox coated) on filament-wound fiberglass forms and have extremely low ohmic losses for longer, full performance elements rated at 2000 watt PEP. Weatherproof covers are provided.



C. Cushcraft 3-band antennas are factory adjusted for a 50-ohm coaxial feedline and come complete with a low-loss, high-performance 1:1 balun which takes a PL-259 connector.

D. Rugged element-mounting brackets are designed with thick aluminum plates and zinc plated steel hardware to reduce stress and provide trouble-free operation in severe weather. Elements and boom use high-strength hard-drawn 6063-T832 bright-finish aluminum tubing.



20 METERS

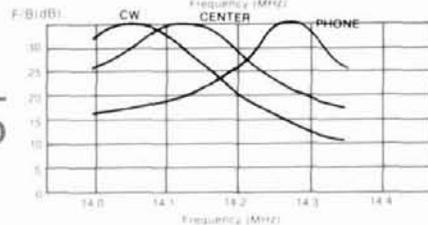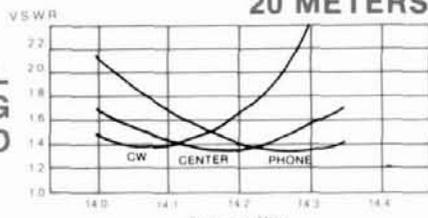

15 METERS

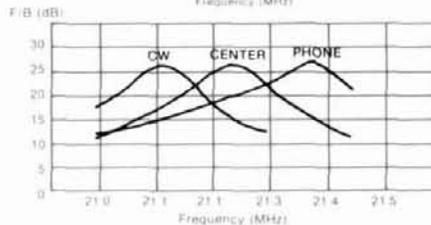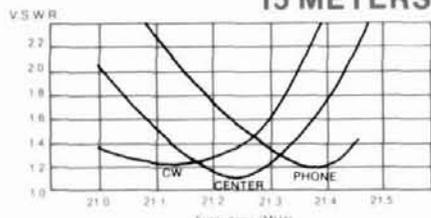

10 METER

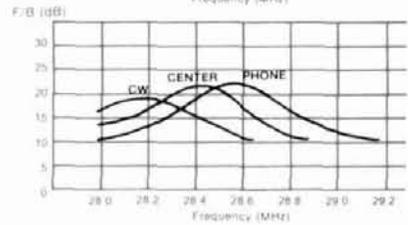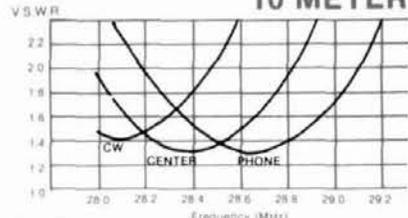

TYPICAL
VSWR

FRONT-TO-
BACK RATIO

split-frequency operation

with the Drake R-4B receiver and the TR-4 transceiver

Modifications
you can make
to your Drake receiver
and transceiver
to enhance
operating convenience
and versatility

This article describes how I increased the versatility of my Drake TR-4 transceiver for split-frequency operation using a Drake R-4B receiver as an external VFO.

I purchased a used R-4B receiver, and the thought kept passing through my mind that it would sure help if I could use it to control the TR-4 transmit frequency (as in the R-4 TX-4 combination).

analysis

The Drake R-4 receiver and the TR-4 use different i-fs; therefore there's no direct interface as with the TX-4. After studying the circuit diagrams, it occurred to me that it should be very easy to duplicate the control circuit of the Drake RV-4 remote VFO and

make use of only the VFO portion of the R-4B to control the TR-4.

The control circuit described was built and minor modifications were made to the R-4B to interface with the TR-4. The R-4B can be used as a separate receiver, then switched to remote VFO operation.

Circuit modifications don't interfere with R-4B normal operation. The added components can be removed in a few minutes at resale time to restore the receiver to its original condition.

The main problem in the project is the fact that there's a 45-kHz difference in VFO operating frequency between the TR-4 and R-4B. This is apparently because of the 50-kHz second i-f of the R-4B. There's no reason why the VFO frequency can't be decreased 45 kHz to match the TR-4 VFO output; then the crystals in the premixer oscillator can be changed to oscillate 45 kHz higher to compensate for the VFO downward shift. I breadboarded the circuits to test the idea and everything worked as planned.

control circuit

I duplicated the control circuit of the RV-4 (fig. 1) and mounted it in a small minibox. This minibox sits on top or alongside the TR-4 to interface the R-4B. Only two critical items are in the control circuit. One is peaking coil L1 at the grid of V1 (12AU7); it must match the coax cable from the VFO to the 12AU7 grids.

The diagram in my manual didn't give a value for L1 so I experimented a bit. I reclaimed a vhf coil form from some surplus gear and wound 70 turns of no. 30 (0.25 mm) enamel wire on the 6.5-mm (1/4-inch) slug-tuned form. Too few or too many turns would not peak the 5-MHz signal, so the number of turns must be adjusted. A scope is a great aid in tuning L2.

The other critical item is the four-position special switch, A1. After tracing the functions of the Drake switch, I discovered that a standard four-position, five-pole switch would do the job. These parts could be ordered from Drake, but I used all junkbox parts.

By William P. Winter, Jr., WB8JCO, O'Higgins 3168 Buenos Aires, Argentina

From **Vlf**
to **Uhf...**

R.L. Drake systems advance the technology
of worldwide
radio communications...



with innovative system engineering that offers you
a number of "first in the world" features.

The Drake 7-line system:

Drake TR-7: The first amateur transceiver in the world to offer full general coverage (0-30 MHz) reception capability, 1.8 to 30 MHz transmission capability, and synthesized "up-conversion" design techniques. It's ready now for future band expansions, MARS, and other services.

Drake R-7: The first amateur receiver in the world to combine full general coverage (0-30 MHz) reception and synthesized "up-conversion" design techniques, with transceive capability, full passband tuning, notch filter and dual receive antenna circuitry.

The Drake UV-3 system:

Drake UV-3: The first amateur fm transceiver in the world to offer 3 fully synthesized bands (144-220-440 MHz) in a single transceiver, and bandswitched from the front panel. A remote mounting kit, PS-3 matching ac supply and 1525EM pushbutton microphone round out the system.

For a FREE Drake Full Line Catalog contact your favorite Drake Dealer.

R. L. DRAKE COMPANY



540 Richard St., Miamisburg, Ohio 45342
Phone: (513) 866-2421 • Telex: 288-017

The 1-mH rf choke from TR1 collector is from an old TV set. Any coil will work as long as it has a good number of turns. Transistor TR1 turns the VFO B+ on and off through the rf choke and the coax line going to the R-4B receiver.

control switching

Position 1, separate receive. The 330-kilohm resistor in fig. 1 is connected through S1D to B+, turning TR1 on, causing its collector to saturate. Thus TR1 collector goes low, pulling the 10-Vdc B+

TR-1 off, thus allowing the VFO B+ to rise to normal. This allows the VFO in the R-4B to operate on transceive.

Position 4, transmit. During transmit only, the 330-kilohm resistor is connected to ground through S1C and pin 3 of the Jones plug to the transmit cathode. TR1 is cut off allowing the VFO B+ to rise, enabling the R-4B VFO. During receive, the transmit cathode goes high, turning on TR1, which pulls the VFO B+ down so that the R-4B VFO can't operate.

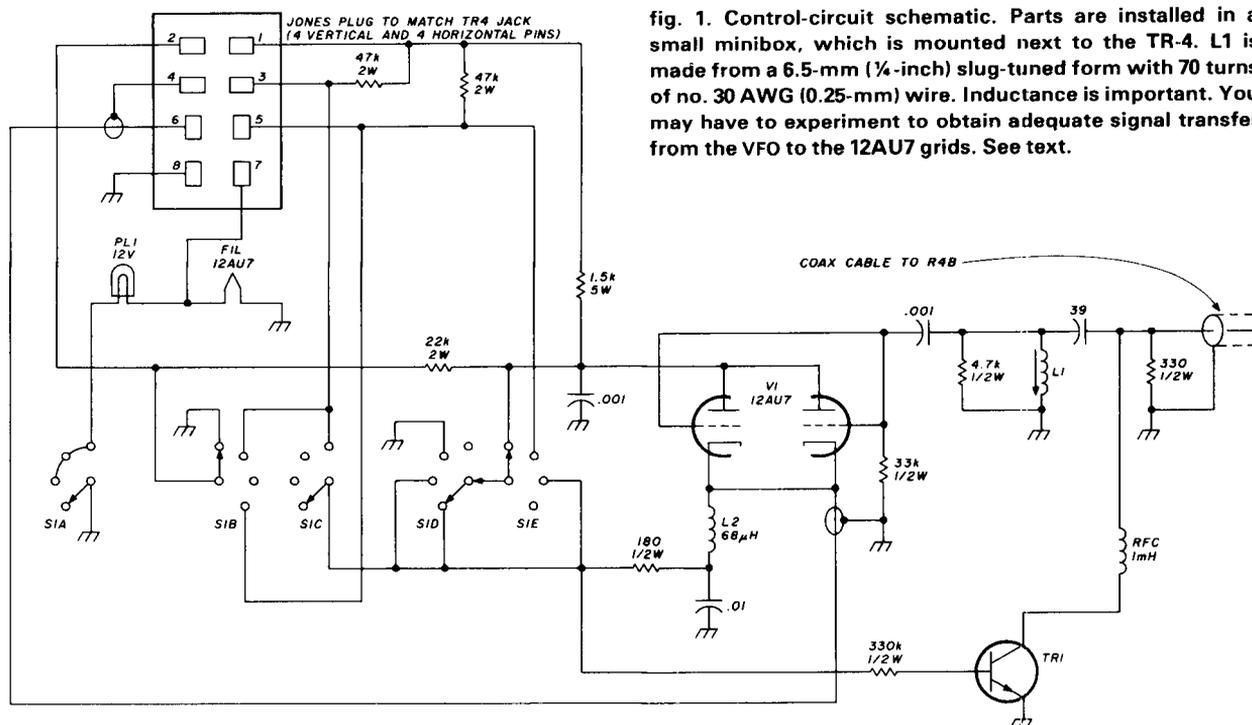


fig. 1. Control-circuit schematic. Parts are installed in a small minibox, which is mounted next to the TR-4. L1 is made from a 6.5-mm (¼-inch) slug-tuned form with 70 turns of no. 30 AWG (0.25-mm) wire. Inductance is important. You may have to experiment to obtain adequate signal transfer from the VFO to the 12AU7 grids. See text.

line to the R-4B VFO toward zero, which turns the VFO off. The slide switch on the side of the R-4B must be forward to disconnect the control unit, thus defeating the above action. The VFO output is now sent to V8 (premixer) cathode. The R-4B operates normally.

Position 2, receive. The 330-kilohm resistor is connected through S1D and S1E to pin 5 of the Jones plug. This is receive cathode ground. During receive TR1 base goes low, cutting it off, and the B+ to the VFO goes high, which allows the VFO in the R-4B to operate during receive only. During transmit the receive cathode goes high, turning the R-4B VFO off. Note that the slide switch on the side of the R-4B must be toward the rear to switch the VFO output from V8 mixer to the control unit.

Position 3, transceive. The 330-kilohm resistor is connected through S1D and S1E to ground, turning

The 12AU7 is a cathode follower with both sections in parallel. It functions as an impedance transformer giving a low impedance output to feed the TR-4. At the same time, the 12AU7 acts as a switch to disconnect the signal from the remote VFO. The cathode is switched high or low at the appropriate time according to the switch position and the TR-4 transmit-receive relay.

control-circuit layout

Nothing is critical about the control-circuit layout, since it is primarily composed of dc switching lines. However, some attention should be paid to the rf components related to the 12AU7 grid. Leads should be short, and accepted rf-wiring practice should be used.

Transistor TR1 can be any silicon npn device with a voltage rating of about 40 volts. The coax cable from the R-4B to the control unit, and the cables

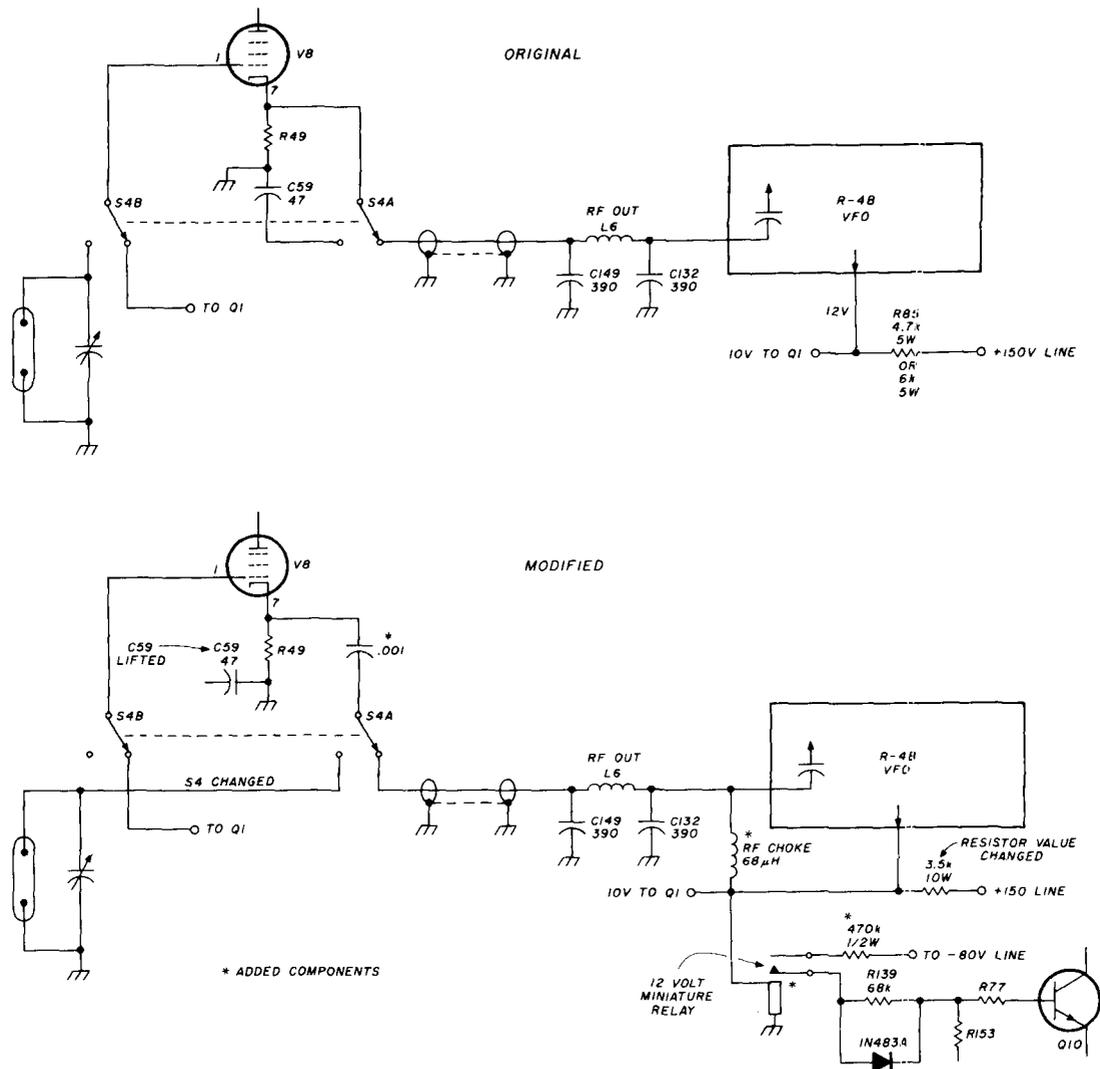


fig. 2. Before and after mods to the Drake R-4B receiver.

from the control unit to the Jones plug, should be as short as possible. *Caution:* Do not insert or remove the Jones plug in the TR-4 while the rig is on; otherwise the TR-4 transistors may be damaged.

R-4B modifications

Of the five modifications described, only the first two are needed to make the R-4B receiver function as a remote VFO. Modifications 3 through 5 are optional. The modifications to be described involve:

1. Changing the value of power resistor R85
2. Changing the position of three wires on S4
3. Adding four components to switch the neon VFO indicator lamp
4. Changing the VFO dial
5. Changing the crystals and adding padding capacitors if desired

Fig. 2 shows the R-4B circuit before and after modification.

Modification 1. Provide VFO output from the fixed-channel crystal jack on the side of the R-4B by following these steps:

1. Lift C59 from S4A. Bend C59 so that it doesn't touch anything. Leave it there for restoration at resale time.
2. Locate the jumper that comes from the fixed-channel crystal jack to S4B. Lift the connection from S4B and solder it to the lug on S4A where C59 was removed.
3. Locate the wire that comes from V8 pin 7. Lift it from S4A middle lug.
4. Lift VFO output coax center conductor from S4A and move it to S4A middle lug (vacated in step 3 above).

5. Place a small 0.001- μ F ceramic capacitor in series with the wire removed in 3 above. Solder the other lead of the capacitor to S4A where the coax formerly was connected. This blocks the 10-Vdc control voltage, which we will place on the VFO output line, from reaching V8.

We have now modified S4 to provide the following switchings: Forward: regular R-4B receive mode. Back: VFO output to crystal jack, receiver disabled. The fixed-frequency crystal socket is now the VFO output jack. A length of RG-59 carries the R-4B VFO signal from this jack to the control box. I soldered the pins of a defunct crystal to the ends of the coax so I could plug the coax into the crystal socket.

Modification 2. Dc switching of the R-4B VFO is accomplished from the control unit by placing an rf choke from the 10-volt VFO B + line to the rf output line from the VFO. A convenient spot is between the two solder tabs on the circuit board just behind the audio gain control. I used a 68- μ H choke from my junk box. The value isn't critical as long as it presents a high reactance at 5 MHz. Check that resistor R85 can handle the additional dissipation when the 10-volt line is shorted to ground by the control box. R85 must drop the entire 150 volts from the +150-volt line. The control unit now enables the TR-4 to turn the R-4B VFO on and off in the same manner as in the remote RV-4 VFO.

Modification 3. Switching the neon VFO indicator lamp is optional but enhances operating convenience. I purchased a surplus 12-Vdc, 10-mA miniature relay and mounted it on a long bolt, which I installed where the audio output transformer is mounted. Your mounting will depend on what relay you have available. (See the comments on relay selection.) The following steps are necessary for this modification:

1. Connect the relay coil from the +10 volt line to ground.
2. Place a 470-kilohm resistor from the normally open contact (normally open with coil energized) to the -80 volt line. A convenient spot is the solder tab that has a white wire with a green stripe (on my R-4B). This is the negative lead of C91, which is the 8- μ F, 150-volt filter of the -80 volt line. It's located on a small vertical board behind the notch-depth control, which is mounted on the right-side panel.
3. Locate the board containing Q10. It's mounted below the VFO and just behind the front panel. Connect the other relay contact to the junction of R139 (68k) and D15 anode.

The relay functions as follows. When the TR-4 control box is set to inhibit a signal from R-4B VFO, the +10 Vdc line goes low (3 volts or lower). This action de-energizes the relay just installed, connect-

ing negative cutoff bias to transistor Q10, which causes NE2 to be extinguished.

4. R85, 4.7-kilohm, 5 watts, should be changed to a 3.5-kilohm, 10-watt resistor if you use a 10-mA relay as I did. Extreme care should be used here. With the original 4.7-kilohm resistor, the additional current drain caused the normal 10-Vdc regulated voltage to drop below the zener regulation point. Reducing the value of R85 allows an additional 10 mA of current to be drawn, and the zener will still regulate at 10 Vdc. Do not operate the VFO with the lower resistance value without the relay coil connected, as the additional current will probably blow the 250-mW, 10-volt zener mounted inside the VFO enclosure. Easy does it!

If you use a relay with a coil other than 10 mA, 12 Vdc, adjust the value of R85 accordingly or perhaps provide a separate supply to drive the relay by a transistor. An alternative method would be to put a pre-regulator on the line (12 to 15 volts) with a zener of enough power-handling capability to do the job.

Modification 4. If you wish dial calibration on the R-4B identical to that on the TR-4, it will be necessary to order a TR-4 dial from Drake. (The price in June of 1978 was \$2.00, plus \$1.00 handling, plus postage.) It's installed in the following manner:

1. Remove all front-panel knobs (some slip on; others have a set screw).
2. Remove nut on the function selector switch.
3. Remove four screws at corners of the front panel. Be careful to catch the fiber spacers behind the panel (they're hard to find when they fall and roll across the floor).
4. Remove the two screws holding the metal shield over the neon bulb. Be extremely careful *not* to bend the neon-bulb leads, because they break very easily; many standard replacement neon bulbs will not fit. I had to cut a hole in the shield to allow the end of the bulb to stick out.
5. Very carefully remove the front panel without unduly bending the neon-bulb leads. Lay aside the clear Plexiglas sheet with the red line. Do not lose the pressure washer. Note how it came off so it can be replaced in the same way.
6. Remove two screws holding the pilot light shield mounted behind the panel.
7. Remove the two C-rings from the VFO shaft. You'll need a C-ring tool; it can be purchased in auto parts shops. Be careful! The C-rings are tight and are hard to remove. (I broke my tool and had to use a wheel puller to remove the first C-ring). The second C-ring wasn't so tight. *Important:* Note the position of these C-rings so they can be replaced in the exact spot.

8. Locate, identify, (make a drawing), and remove the three leads coming out of the VFO.
9. Remove the three nuts holding the VFO in place. Lift and remove the VFO assembly from the R-4B.
10. Turn the VFO shaft to find the final stop. Noting *exactly* where it was positioned (pencil mark),

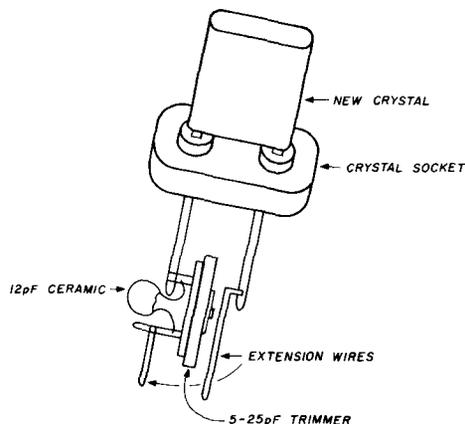


fig. 3. Construction of the crystal paddler, which plugs into the R-4B receiver crystal socket.

remove the dial by removing the large C-ring. Place the TR-4 dial in the same position.

11. Reassemble, following the steps above in reverse order.

Modification 5. To track the VFO for TR-4 use and separate receiver use, I ordered new crystals that are 45 kHz higher in frequency than the originals. For the 20-meter band to tune backward, as in the TR-4, I substituted a crystal frequency (14.645 MHz), which is added, rather than subtracted, to the VFO output to obtain the proper injection frequency.

This, by the way, is the same crystal needed for 80 meters. Therefore, by installing an appropriate jumper and one other change, the same crystal can be used for both 20- and 80-meter operation.

To keep expenses down I ordered only three crystals (my cost locally was \$20.00 for the three crystals): one for 80 meters, which doubles for 20 meters; one for 15 meters, and one to receive WWV on 15 MHz. Thus I've covered my needs at the present. For the same crystal to be used for both 80 and 20 meters, the following steps are required:

1. Find C53 (68 pF) in parallel with R47 (1.5 kilohms). This network is the collector load for Q1 at 25.1 MHz. Lift these two components from S5F and dress them

out of the way so they don't touch anything but are handy for replacement at resale time.

2. Place a jumper from C55 (68 pF) to the switch tab vacated above. Solder the connections.
3. Place an insulated jumper wire from the 14.6-MHz crystal jack to the 25.1-MHz jack. (The 25.1-MHz crystal will no longer be used.) Put it away so it will be handy at restoration time.* The jumper should be placed in the holes toward the front panel. The new crystal, 16.645 MHz, can now be plugged into the 14.1-MHz jack. Eighty-meter operation is as normal; 20-meter operation now tunes backward, as in the TR-4.

crystal padding

I found it necessary to put a trimmer in series with the new crystals to trim the R-4B receive frequency to exactly the same dial calibration as when using the R-4B as a remote VFO. I used a 12-pF ceramic cap in parallel with a small 5-25 pF variable, which I removed from some surplus equipment (see fig. 3). The cap is smaller than the standard-size trimmer and will fit between the solder tabs of a standard-size crystal socket. The capacitors are in series with one lead of a crystal socket adapter, which is plugged into the main crystal socket.

dial calibration

Dial calibration is as follows:

1. Calibrate the TR-4 dial as usual, using the TR-4 internal crystal calibrator.
2. Switch the control unit to receive from external VFO. Calibrate the external VFO dial (R-4B dial) in the same manner as the TR-4.
3. Switch the control unit to separate receive (don't forget to throw the slide switch for separate receive). The R-4B should now operate normally. Adjust the trimmer mounted below the new crystal to zero beat.

summing up

Now you can receive a station on the R-4B and then switch immediately to transceive on the same frequency by simply selecting transceive on the control box and moving the slide switch on the side of the R-4B. You're now transmitting with R-4B VFO control. It's a good idea to check the dial calibration from time to time to make sure that everything is still calibrated, otherwise you'll have a small frequency offset when switching to transmit from the R-4B.

You have greatly increased the versatility of the TR-4/R-4B combination, and, if your experience is like mine, you'll also have greatly increased your operating pleasure.

ham radio

*The steps in these modifications should be kept in a file with your equipment literature. Appropriate annotations to the steps will come in handy when you decide to restore your radio for resale. Editor.

Introducing Kantronics' Field Day

TRADEMARK

Morse Code/teletype reader and code speed display:

Kantronics' Field Day Morse Code/teletype reader and code-speed display reads code signals right off the air. Its powerful microcomputer system picks out signals, computes their speed, and reads even sloppy copy up to 80 words per minute!

1. Flies through the air with the greatest of ease.

Field Day is simple to use. You plug it into your station receiver just as you would a set of headphones.

Code and teletype conversations are converted from dots and dashes to standard alphanumeric text. The text advances across 10 big half-inch displays, and lab tests show that even the fastest CW is easily readable.

Field Day displays incoming or outgoing code speeds for you at the touch of a button. An accurate code speed-sampling program shows the speed right on the front panel. Everything is enclosed in a single, lightweight package that's small enough to fit in with the rest of your station.

2. Pay a little, get a lot.

In addition to a highly superior code-reading program and unique "on-board" speed display, **Field**

Day has the specifications that make it a truly great code reader.

Modes: CW, RTTY and speed display. **Speed Range:** 3-80 WPM. **RTTY Speeds:** 60, 67, 75 and 100 baudot. **Code Display:** 10 alphanumeric displays. **Special Characters:** AS, AR, SK, BT, /, ? (.), ", comma, period, colon, semicolon, "understood," "attention," and "error." **Filtering:** Active, 750 Hz center, 200 Hz bandwidth. **Input Impedance:** 1,000 ohms. **Power Requirements:** 117 Vac, 20 watts. **Dimensions:** HWD 3.44" by 8.50" by 9.25". **Warranty:** Limited, one year parts and labor. **Price:** \$449.95 Shipments after 3/1/79.

3. C'mon, take a test drive.

Check with these Authorized **Kantronics** dealers for more information on the **Field Day** Morse Code/teletype reader and code-speed display:

Associated Radio/Kansas City, **Barry**/New York, **Bill's**/Carbondale, IL, **Brodie**/Moore, OK, **Burghardt**/Watertown, SD, **Burstein-Applebee**/Kansas City, **Cohoon**/Trenton, KY and Austintown, OH, **Fontana Electronics**/Fontana, CA, **H-E-P**/Aurora, CO, **Hirsch**/Williamsville, NY, **Long's**/Birmingham, **Madison**/Houston, **MidCom**/St. Louis, **Omar**/Durand, MI, **Omaha Radio Center**/Omaha, **Queen City**/Cincinnati, **Radio World**/Oriskany, NY, **Spectronics**/Oak Park, IL, **Tracy**/Fort Worth.

 **KANTRONICS**
The Lightweight Champs.

(913) 842-7745
1202 East 23rd Street
Lawrence, Kansas 66044

Our Smart Machine

TRADEMARK

reads sloppy copy.

COMPACT ENCLOSURE.

In inches, **FIELD DAY** is only 3.44 high by 8.50 wide by 9.25 deep!

SPEED DISPLAY.

Special program computes received and transmitted code speeds.

RTTY COPY.
Control functions in back for copying all the standard baudot speeds.

ON-BOARD CODE DISPLAY.
No need to tote around a TV set to copy code.



MOVABLE SUPPORT ARM.
Tilts to different viewing angles.

SMART CODE-EDITOR.
Copy sent by sloppy lists is edited before display.
Reads good code too!



Puts the World at Your Fingertips

Get your antenna high enough with a TRI-EX tower and bring the world to you.

Receive signals which you have never heard before.

Send your call to other HAMS who have never heard you.

A TRI-EX tower will give you listening power...calling power...and stay-up power that means durability.

Durability comes from TRI-EX's 25 years of building quality towers. These years of experience combined with the latest engineering knowledge and materials are used to design and build towers which stay up under the antenna loads and wind speeds specified. After manufacture our steel towers are hot dipped in molten zinc (galvanizing). All exposed steel is covered inside and out — including the inside of tubing.

Our aluminum towers are self-resistant to corrosion. TRI-EX TOWERS makes them all: GUYED TOWERS, CRANK-UP TOWERS, FREE STANDING TOWERS, STACKED TOWERS.

And we will install a tower on your site, upon request.


Call, or write TRI-EX now for information on the right TRI-EX tower for you. We will send you our complete list of prices, delivery dates, installation information and the name of your nearest dealer. Call TOLL FREE.

Call our New Number
1-800-528-6050, Extension 1025

In Arizona, dial:
1-800-352-0458, Extension 1025



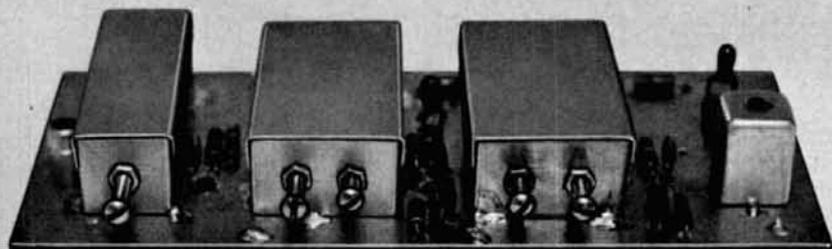7182 Rasmussen Avenue, Visalia, California 93277



high-performance 432-MHz converter

Complete construction details
for a 432-435 MHz
receiving converter
that is easy to build
and tune up


The 432-MHz receiving converter described here is the result of several month's work. As anyone who has attempted to build solid-state uhf gear knows, layout and construction technique is vital, not only to coming up with a good basic design, but also to building a converter that works properly.

Now that economically priced solid-state equipment and devices are available for use above 432 MHz, the cost of building uhf equipment has been reduced considerably. This converter uses three transistors (six if you build the oscillator chain for copying Oscar 8). Three Texas Instruments dual-gate 3CT225A mosfet transistors are used in the converter (90 cents each in small quantities). The 3CT225A transistors are rated at 900 MHz with a 4-dB noise factor; at 432 MHz with 12 Vdc drain voltage and 4 volts on gate 2, gain will be about 22 dB with a noise factor of 2 dB or less. These transistors, and the stripline tuned circuits, makes this a very good converter for weak-signal reception.

Two versions of the converter were built using coils in the tuned circuits, but the results were far below that achieved with striplines. A local-oscillator chain was not built on the converter board because the 404-MHz injection frequency was coupled from the oscillator chain in my 432-MHz transmitting converter. However, a diagram of an easy-to-build oscillator chain will also be described. I use it with the converter to copy Oscar 8 Mode J.

layout and construction

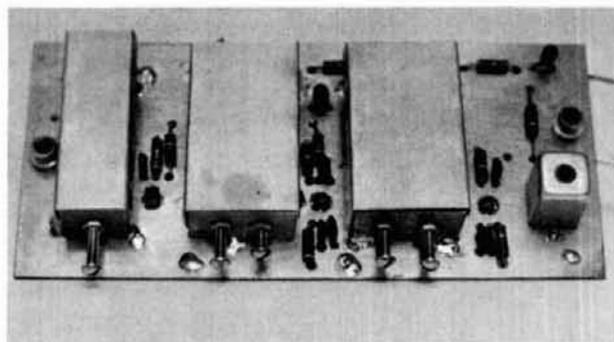Component arrangement, component spacing, and wiring have been optimized for best results, based on several earlier versions. The spacing between the tuned circuits in the amplifier and mixer



Top view of the 432-435 MHz converter showing placement of the enclosures with the tuned lines. Input is to the left, output to the right. Transformer T1 is in the shield can near the output connector.

By C. H. Robinson, N9KD, 89 Nottingham Road, Springfield, Illinois 62074


was laid out to provide satisfactory interstage coupling without the use of capacitors.

The circuit boards I used are glass epoxy. The oscillator board has foil on one side; the converter board has copper on both sides. Anyone can make the circuit boards, even if he has never etched boards before. Start by cutting the boards to size; clean the boards with steel wool and paint the copper. I used *Rustoleum* gray primer in a spray can — it protects the copper while in the etching solution, and it is easy to remove when you scribe the lines. After the painted boards have dried, using the pattern, trace out the lines; since there are no curved lines, scribing is very easy.

Use a small jeweler's screwdriver to scribe the lines. You can paint a spare piece of circuit board and practice getting the lines the right width; about 1/16 inch (1.5 mm) is best. Put the scribed boards in etching solution and agitate once in a while to speed up the etching process. After all the necessary copper has been etched off, thoroughly clean the boards with soap and water using steel wool. A final cleaning with abrasive household cleanser is recommended to remove any last traces of the etchant solution.


tuned-circuit construction

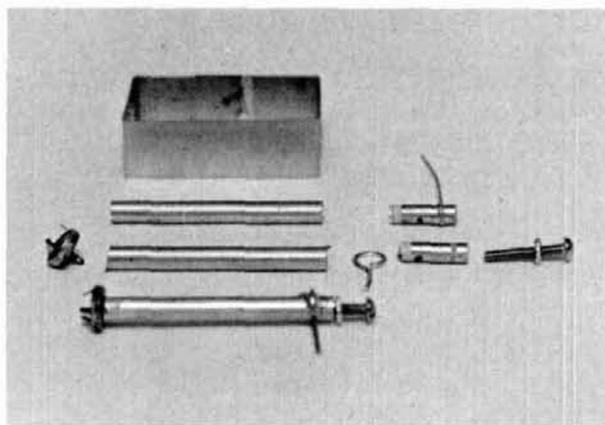The enclosures for the striplines are made from brass strips 0.065 inch (1.5 mm) thick, 3/4 inch (19 mm) wide, and 12 inches (30 cm) long. These strips



Finished components for one of the tuned stripline circuits. The button mica capacitor is soldered to the bottom of the line; the piston capacitor is inserted in the top and soldered in place (see text).

and the 1/4-inch (6.5 mm) brass tubes can be purchased in many hobby shops. The dimensions for the second rf and the mixer stages are 1-1/4 × 2-1/4 × 3/4 inches (32 × 57 × 19 mm); the first rf stage is 2-1/4 × 3/4 × 3/4 inches (57 × 19 × 19 mm). These are inside dimensions, so, when bending, allow for the bend angle. One way is to mark off the first bend, bend in a vise, then mark the second bend, and so on. One side must be longer than the other so it laps and can be soldered. The spacing between the tuned lines is 1/4 inch (6.5

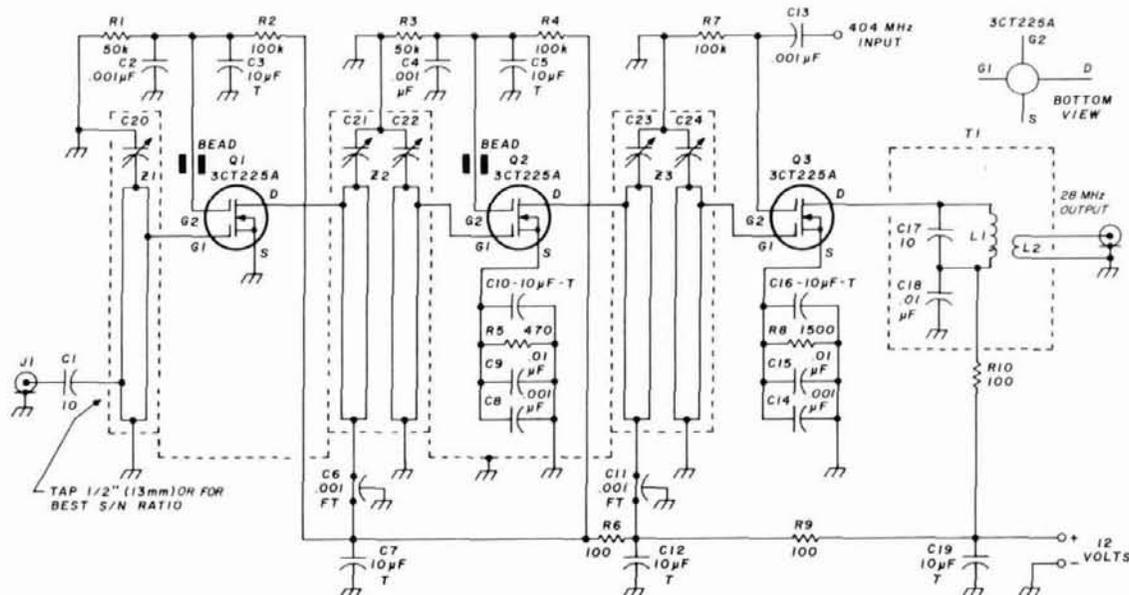


C20-C24 1.5-10 pF ceramic piston capacitors (Centralab 829-10)

T1 Hamtronics 7807 coil form and shield. L1 is 22 turns no. 26 (0.4 mm) close-wound; L2 is 4 turns no. 26 (0.4 mm) on bottom of L1


fig. 1. Schematic diagram of the high-performance converter for 432-435 MHz; companion local-oscillator chain is shown in fig. 2. Capacitors marked with FT are button mica feedthrough types; capacitors marked with T are tantalum; all other capacitors are disc ceramic. Z1, Z2, and Z3 designate the stripline circuits.

mm) and 1/4 inch (6.5 mm) from the side of the enclosure.

The tubes for the tuned lines are 2-1/8 inches (54 mm) long; this allows 1/8 inch (3 mm) clearance between the end of the tube and the enclosure where the trimmer is mounted. Solder tin the inside of the tube about 1/2 inch (13 mm) down. Remove the wire pigtail from the trimmer, and insert the trimmer in the tube; you may have to apply heat with the soldering iron to get it in. About 1/8 inch (3 mm) of the

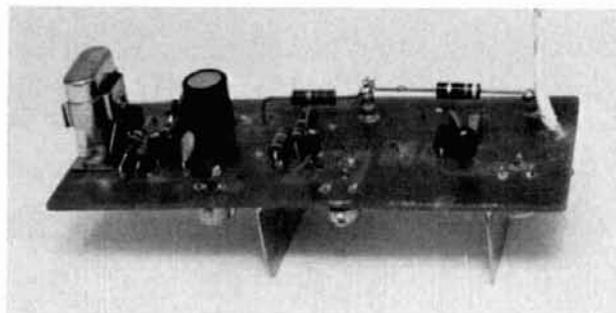

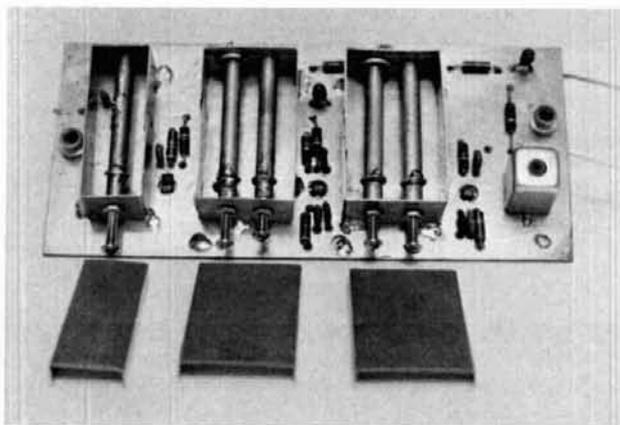Construction of the 404-MHz local-oscillator chain. Printed-circuit layout is shown in fig. 4.



Top view of the converter with the enclosure covers removed to show the placement of the tuned lines. Note the holes in the board for mounting the transistors.

trimmer should protrude beyond the tube. Apply heat to the tube and sweat solder the trimmer in place.


Two of the tuned lines have dc blocking capacitors mounted at the ends; these are mounted like the trimmers, but the tubes will be shorter by the thickness of the capacitor. Form the piece of wire that

connects the tuned lines to the PC board, but do not solder yet; this will be done later when the tuned lines are placed in the enclosures.

mounting and components

If you don't have a 404-MHz oscillator chain for injection, build the oscillator chain first. I built the oscillator board one circuit at a time, drilling the holes for the components as I went, testing each stage before starting the next. The schematics and photographs show all the details. After the oscillator board is complete and tested, lay it aside and start construction on the converter board.

Wiring the converter is straightforward; if you study the photographs and schematic you should have no problems. However, there's one precaution: Since the converter board has copper foil on both sides, the foil around the component holes on top of the board must be cleared to prevent shorts. To do this use a 1/8-inch (3-mm) drill and flatten the angle of the point so it will cut the copper from around the top hole but not touch the copper on the bottom of

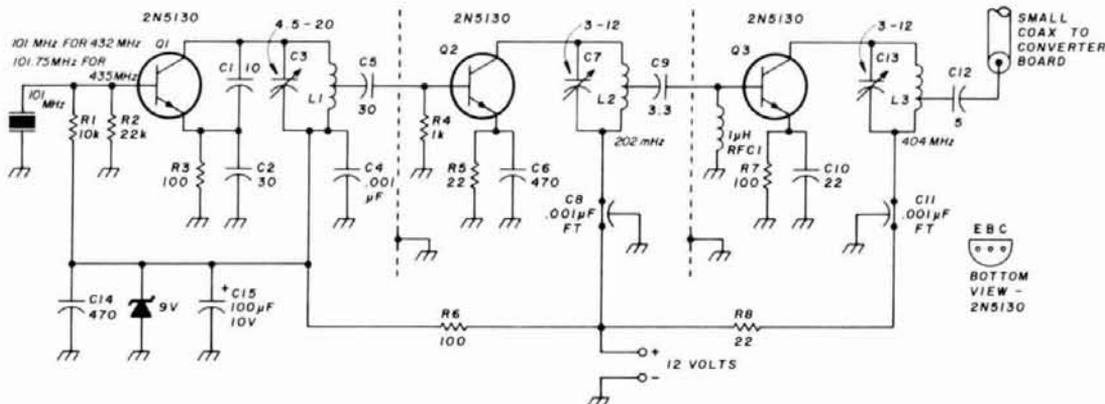

- L1 6 turns no. 16 (1.3-mm) wire, 1/4-inch (6.5-mm) diameter, 3/4 inch (19 mm) long, tapped at one turn
- L2 3 turns no. 16 (1.3-mm) wire, 1/4-inch (6.5-mm) diameter, 3/4 inch (19 mm) long, tapped at 1-1/2 turns
- L3 1 turn no. 16 (1.3-mm) wire, 1/4-inch (6.5-mm) diameter, with 1/2-inch (13-mm) leads

fig. 2. 404-MHz local-oscillator chain for the 432-435 MHz converter. Capacitors marked with FT are feedthrough types; except for the electrolytic (C15), all other capacitors are disc ceramic.

Two kinds of experts appreciate Rockwell-Collins equipment: People who buy it, and people who sell it.

Every Rockwell-Collins Distributor is a real pro at answering questions and solving problems.

He'll show you how to operate specific equipment, discuss peripheral gear, check everything out when you get it, even help with installation. And he'll be there to support your needs for years to come.

Get in touch with the distributor in your area. (And ask for a copy of the Rockwell-Collins Amateur Equipment Catalog.) Or contact Collins Telecommunications Products Division, Rockwell International, Cedar Rapids, Iowa 52406. Telephone 319/395-4493.

CALIFORNIA

Anaheim — *Ham Radio Outlet
 Anaheim — *Henry Radio Co., Inc.
 Burlingame — ** *Ham Radio Outlet
 Los Angeles — ** *Henry Radio Co., Inc.
 San Jose — *Quement Electronics

COLORADO

Denver — *C. W. Electronic Sales Co.

FLORIDA

Miami — *Amateur Radio Center, Inc.
 Miami Springs — ** *Argon Electronics Co.

Orlando — *Amateur Electronic Supply

GEORGIA

Atlanta — ** *ACK Radio Supply

HAWAII

Honolulu — ** *Honolulu Electronics

ILLINOIS

Peoria — *Klaus Radio Inc.

INDIANA

Terre Haute — ** *Hoosier Electronics, Inc.

KANSAS

Overland Park — ** *Associated Radio Communications Inc.

LOUISIANA

Metairie — ** *Thomas J. Morgavi Elec.

MARYLAND

Wheaton — ** *Electronics Int'l Service Corp.

MINNESOTA

Minneapolis — ** *Electronic Center, Inc.

MISSISSIPPI

Jackson — ** *Coker Electronic Service

MISSOURI

Butler — *Henry Radio Company
 St. Louis — ** *Ham Radio Center
 St. Louis — ** *Midcom Electronics Inc.

NEBRASKA

Potter — ** *Western Nebraska Electronics

NEW HAMPSHIRE

Concord — *Evans Radio, Inc.

NEW JERSEY

Maple Shade — ** *Communications Service Company

NEW YORK

Amsterdam — *Adirondack Radio Supply Inc.
 Farmingdale — ** *Harrison Radio Corp.

New York — ** *Barry Electronics Corp.
 Valley Stream — *Harrison Radio Company

NORTH CAROLINA

Otto — ** *Slep Electronics Company

OHIO

Cleveland — *Amateur Electronic Supply
 Columbus — ** *Central Communications

OKLAHOMA

Ponca City — ** *Starks Avionics & Communications Service

OREGON

Portland — ** *Portland Radio Supply Co.

PENNSYLVANIA

Drexel Hill — *Kass Electronic Distributors
 Tevose — ** *Hamtronics

TEXAS

Dallas — ** *Electronic Center, Inc.
 Garland — ** *Teco, Inc.
 Houston — ** *Madison Electronics Supply

WASHINGTON

Seattle — ** *ABC Communications
 Spokane — ** *HCJ Electronics
 Tacoma — *C & G Electronic Company

WISCONSIN

Milwaukee — ** *Amateur Electronic Supply

* DEALER ONLY
 ** SERVICE AGENCY ONLY
 *** DEALERS /SERVICE AGENCIES



...where science gets down to business

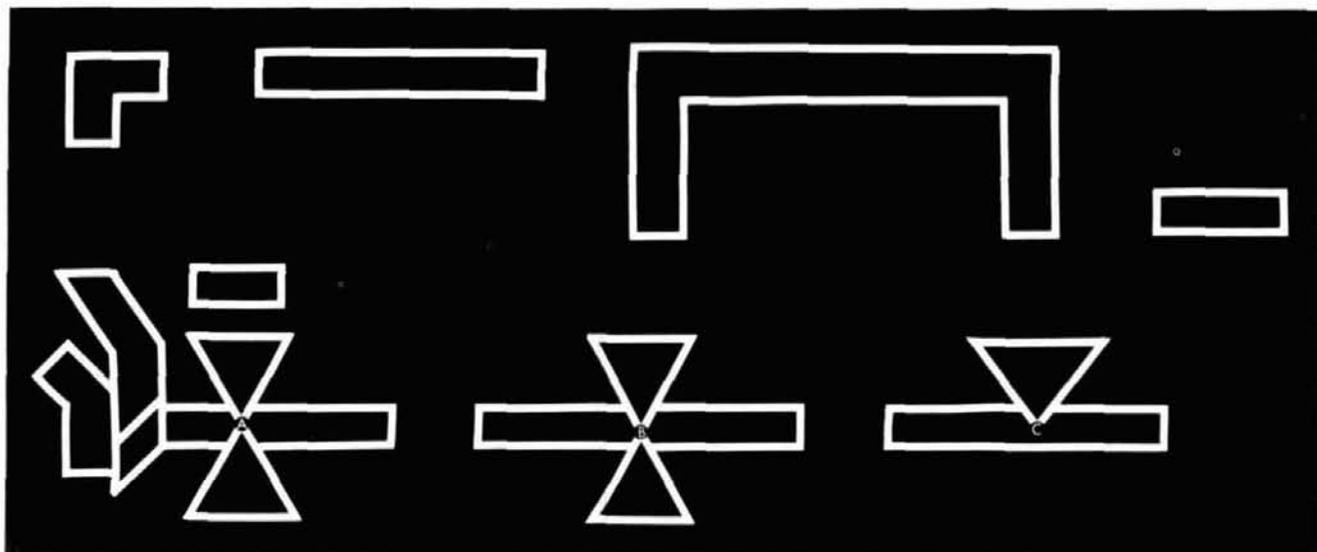


fig. 3. Full-size printed-circuit layout for the 432-435 MHz converter. Component placement for the converter is shown in the photograph. Transistor mounting holes marked A, B, and C are 5/16 inch (8 mm) diameter.

the board. Use an emery wheel to shape the drill bit for this task.

After the mixer wiring has been completed, connect the output of the oscillator to gate 2 of Q3 in the converter board with small coax cable; apply 12 Vdc and common to both boards. You should be able to receive the third harmonic of a two-meter transmitter that tuned to 144 MHz, or a weak-signal source if you have one. There are two excellent articles on weak-signal generators in past issues of *ham radio*.^{1,2} When the mixer is working properly, proceed with the other two stages — testing as you complete each one.


You may be able to build the converter without using the 10- μ F tantalum capacitors, but they do

tune up

If a commercial signal generator is available, use it; if not, use a weak-signal source. You may find that the test signal will leak into the converter from places other than the antenna! Take the weak signal outside, as far away from the antenna as possible, or until you can't pick up the signal with the antenna disconnected. With the antenna connected you should receive the weak signal at S-5 or better. You can now peak everything up for optimum performance.


With my weak-signal source about 100 meters from the antenna I receive it at S-9 using a Kenwood TS-520. After the circuits have been tuned for maxi-

fig. 4. Printed-circuit layout for the 404-MHz local-oscillator chain. Component mounting and shield placement is shown in the photograph.

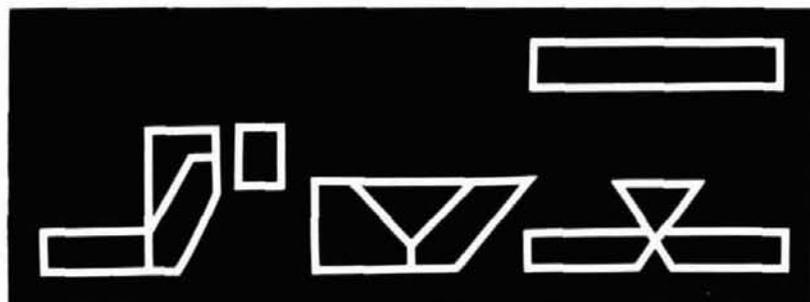


much to stabilize the circuits so they are well worth the extra cost. You may have noticed that on the schematic diagram ferrite beads are shown on gate 2 of each rf stage; the photograph shows only one on the first stage — my error, use the bead to improve stability.

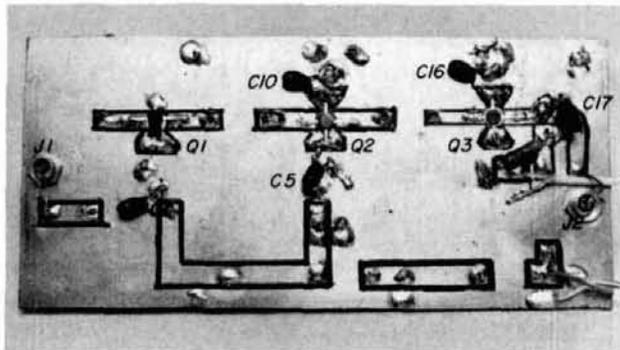mum signal, tune away from the signal and check the noise level as indicated on the receiver's S-meter. The objective is to obtain the greatest signal-to-noise ratio. You can also adjust the converter for lowest noise figure if you have equipment for noise figure measurements.^{3,4}



Component placement on the converter board (see fig.3). In this view the input is to the left, output to the right. Designated capacitors are mounted on the bottom of the board. Small coax cable near C17 couples 404-MHz injection to the converter.

When using this converter with a TS-520 transceiver and no 28-MHz preamp, I have consistently maintained schedules on 432 MHz with stations over 100 miles (160 km) away, with reports ranging from S-4 to 20 dB over S-9 depending upon conditions. During band openings many stations have been heard 700-800 miles (1100-1300 km) out with S-meter readings over S-9. I have also used this converter to copy Oscar 8 and hear the spacecraft signals around S-6 without any special antennas. I

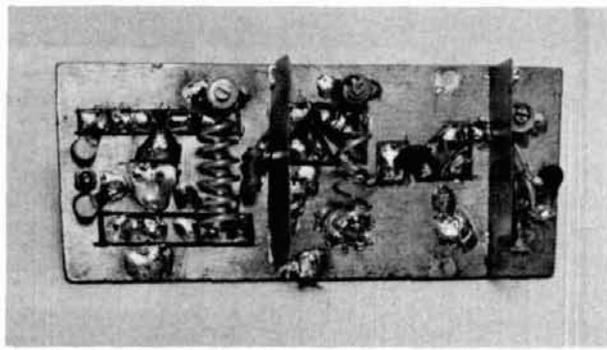

Component placement on the circuit board for the 404-MHz local-oscillator chain.

have built several 432-MHz converters from handbooks, magazine articles, and commercial kits, but this converter tops them all.

references

1. James Brannin, K6JC, "A Stable Small-Signal Source for 432 MHz," *ham radio*, March, 1970, page 58.
2. Bruce Clark, K6JYO, "A Stable Variable Output Weak-Signal Source," *ham radio*, September, 1971, page 36.
3. Louis Anclaux, WB6NMT, "Accurate Noise-Figure Measurements for VHF," *ham radio*, June, 1972, page 36.
4. Robert Stein, W6NBI, "Automatic Noise-Figure Measurements," *ham radio*, August, 1978, page 40.

ham radio

NEW FROM LUNAR

Modular Erectable Towers

- Ideal for ground or roof mounts
- One man can assemble and erect
- Lightweight
- High quality aluminum alloy
- High stability
- Modular and portable
- Extremely rugged

These unique antenna towers can be installed on the ground or roof. Since they're easily transported and site erected, they're a natural for field and portable operations.

Constructed of sturdy aluminum alloy, they're sturdy enough to handle large size HF beams and

EME arrays as well. Also available with optional stainless steel hardware for harsh environments.


Base is approximately 60" high and weighs 28 pounds. Tower sections are 72" high and weigh 21 pounds.

LUNAR'S NEW MODEL 2M 10-150 LINEARIZED AMP



Now ready and being shipped. We held off on announcing it until it was right...

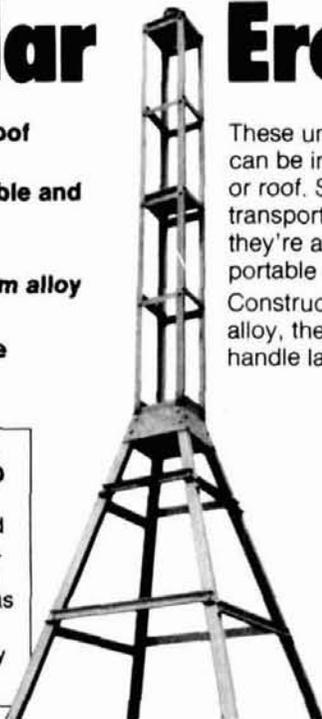Ready now. Order today from your Lunar dealer.



Louis Anclaux
WB 6NMT



2785 KURTZ STREET • SUITE 10
SAN DIEGO, CA 92110 • (714) 299-9740

impedance measurements

using an swr meter

The simple SWR meter and a handheld calculator can be used to measure complex relationships involving impedance in tuned circuits

An SWR measurement can indicate when an rf source is properly matched to a load, but often it's desirable to know the actual impedance values for the load. Once these values are determined, it's then possible to design matching circuits or transformers to translate the load impedance to the desired impedance.

For example, as more solid-state broadband transmitters come into use, a matched load impedance becomes more desirable. While the high SWR of an antenna may not damage transistors rated to withstand that SWR, the output power may be reduced because of an improper load impedance. The lack of tuning and load adjustments prohibits rematching the load impedance to the final output stage for the rated transmitter performance.

Another example of the requirement for knowing the load impedance can be seen for a typical installation with an antenna cut for the 75-meter phone band, but with an occasional trip down in frequency to check into an 80-meter CW net. When an antenna tuner isn't available it's possible to construct a matching circuit so the transmitter still sees a load

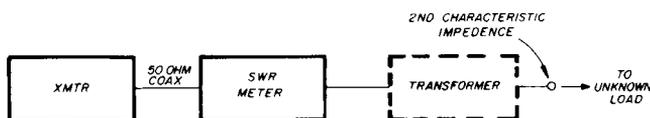


fig. 1. System for measuring characteristic impedances other than 50 ohms. The transformer can be a lumped-constant element, broadband transformer, or a transmission line such as a quarter-wavelength of 75-ohm coaxial cable at the frequency of interest.

impedance within its rated SWR, even though the actual antenna SWR is somewhat higher. Knowing the actual impedance values of the 75-meter antenna while using it at 80 meters will yield a starting point for construction of such a circuit.

measurement procedure

Many instruments are available to measure impedance values, but only a few fortunate Amateurs have them. An instrument that is available, or at least not too expensive or difficult to construct, is an SWR meter.

Once the SWR of an impedance is known, half the battle is over. If the reflection coefficient electrical angle, θ , is known, the impedance can be quickly determined by using a Smith chart. (This is discussed later.)

Information that's available is the SWR based on a characteristic impedance, Z_{01} , of 50 ohms. This means the source, usually a transmitter, looks like a 50-ohm source, and the SWR meter has a 50-ohm characteristic impedance. However, the use of a Smith chart isn't the only method of determining an impedance when the SWR and the reflection coefficient electrical angle are known. The impedance can be calculated outright by knowing the SWR, the reflection coefficient electrical angle, and the characteristic impedance of the measuring system.¹

If another SWR measurement could be made with a different characteristic-impedance-measurement system, Z_{02} , the same impedance values would be found. Of course a different SWR reading would exist, as well as a different reflection coefficient electrical angle. But the impedance values of the load will not have changed.

Since the impedance is constant for the two measurements, the equations relating SWR, Z_{01} , and θ , are set equal to each other, yielding:

$$(\tan \theta_1) (\tan \theta_2) = \frac{\left[\left(\frac{Z_{02}}{Z_{01}} \right) (swr_1) - swr_2 \right]}{\left[\left(\frac{Z_{02}}{Z_{01}} \right) (swr_2) - swr_1 \right]} \quad (1)$$

$$\frac{\tan \theta_1}{\tan \theta_2} = \frac{\left(\frac{Z_{02}}{Z_{01}} \cdot swr_1 \cdot swr_2 \right) - 1}{(swr_1 \cdot swr_2) - \frac{Z_{02}}{Z_{01}}} \quad (2)$$

The SWR is a measured value, and Z_{01} is known

By Ben Lowe, K4QF, Hytop Star Route, Box 66B, Scottsboro, Alabama 35768

from the characteristic impedance of the test equipment.

This means that a second characteristic-impedance-SWR-measurement system must be devised. Such a system is easily obtainable by using the existing 50-ohm source and an SWR meter and transforming this impedance to some other impedance, as shown in **fig. 1**. The transformer can be a lumped-element, broadband transformer^{2,3} or a transmission-line-type, such as a quarter-wavelength of 75-ohm coax at the frequency of interest. (This quarter-wavelength transformer results in a characteristic impedance of 112.5 ohms.)

The procedure is as follows. It's simpler to perform than to describe. Using the 50-ohm system, measure and record the SWR of an unknown impedance. This measurement yields swr_1 and $Z_{01} = 50$ ohms. Then connect the transformer at the output, or antenna side, of the SWR meter. Connect the unknown load

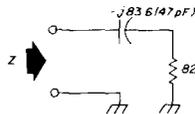


fig. 2. Impedance test circuit.

to the output port of the transformer. Again, measure the SWR. This measurement yields swr_2 and Z_{02} . These four values, swr_1 , Z_{01} , swr_2 and Z_{02} , are substituted in **eqs. 1** and **2**, resulting in two equations and two unknowns. The two unknowns are $\tan \theta_1$, and $\tan \theta_2$, where θ_1 and θ_2 , are the reflection-coefficient electrical angles.

Unfortunately, more than one solution exists, giving more than one value for $\tan \theta_1$, and $\tan \theta_2$. But the resulting impedance calculations yield the same reactance magnitude using either values; whether the reactance is inductive or capacitive can't be determined directly. Another test must be conducted to make this determination; such tests are described later.

From the measurements, all the information necessary to calculate the actual impedance has been found. Substituting swr_1 , $\tan \theta_1$, and Z_{01} into **eq. 3** gives the impedance. Likewise, substituting swr_2 , $\tan \theta_2$, and Z_{01} into **eq. 4** gives the same impedance:

$$Z = Z_{01} \left[\frac{1 - j(swr_1) \tan \theta_1}{swr_1 - j \tan \theta_1} \right] \quad (3)$$

or

$$Z = Z_{02} \left[\frac{1 - j(swr_2) \tan \theta_2}{swr_2 - j \tan \theta_2} \right] \quad (4)$$

test results and example

To test this procedure, I constructed a test load using an 82-ohm resistor in series with a 47-pF capacitor. A randomly selected piece of 75-ohm cable was

found to look like a quarter wavelength at 40.5 MHz. At this frequency the resistor and capacitor look like $82 - j83.6$ ohms (**fig. 2**).

The reactance of the 47-pF capacitor is found from:

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(40.5 \times 10^6)(47 \times 10^{-12})} = -j83.6$$

The one-quarter wavelength of 75-ohm coax transforms the 50-ohm source impedance to 112.5 ohms:

$$\frac{Z_L^2}{Z_1} = Z_2 = \frac{(75)^2}{50} = 112.5 \text{ ohms} \quad (5)$$

Now the two SWR measurements are made. Using the 50-ohm system ($Z_{01} = 50$ ohms), swr_1 of the capacitor and resistor in series is measured as 4:1. The quarter-wavelength, 75-ohm transformer is inserted between the SWR meter and the unknown impedance, and another SWR reading, swr_2 , is measured as 2.5:1; Z_{02} is 112.5 ohms. These values are now substituted into **eqs. 1** and **2** to determine the values of $\tan \theta_1$ and $\tan \theta_2$. Note that calculating the values of θ_1 and θ_2 isn't necessary unless the reflection coefficient electrical angle is desired; only the $\tan \theta_1$ and θ_2 values are needed. These calculations yield:

$$(\tan \theta_1) (\tan \theta_2) = \frac{\left(\frac{112.5}{50}\right)(4) - 2.5}{\left(\frac{112.5}{50}\right)(2.5) - 4} = 4 \quad (6)$$

$$\frac{\tan \theta_1}{\tan \theta_2} = \frac{\left(\frac{112.5}{50} \cdot 4 \cdot 2.5\right) - 1}{(4 \cdot 2.5) - \frac{112.5}{50}} = 2.77 \quad (7)$$

Eq. 7 yields: $\tan \theta_1 = 2.77 \tan \theta_2$. Substituting into **eq. 6** yields:

$$2.77 \tan^2 \theta_2 = 4$$

$$\tan \theta_2 = \pm 1.2$$

Solving for $\tan \theta_1$ by substituting the value of $\tan \theta_2$ into **eq. 7** yields:

$$\tan \theta_1 = 2.77 (\pm 1.2) = \pm 3.32$$

The positive value for $\tan \theta_1$, Z_{01} , and swr_1 are now substituted into **eq. 3** to give Z , the unknown impedance:

$$Z = 50 \left[\frac{1 - j(4)(3.32)}{4 - j3.32} \right]$$

$$= 50 [2.56 \angle -46^\circ]$$


$$Z = 50 [1.78 - j1.84] = 89 - j92.1$$

This gives the resistance as 89 ohms and the

capacitive reactance as $-j92.1$ ohms, resulting in a capacitor value at 40.5 MHz of:

$$C = \frac{1}{2\pi f x_c} = \frac{1}{2\pi(40.5 \times 10^6)(92.1)} = 42.7 \text{ pF}$$


The measured circuit is then:

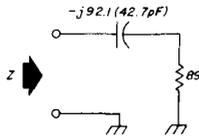

This compares favorably with the component values used in the circuit of **fig. 2**.

Two pertinent factors should be noted here. The values for Z_{02} , swr_2 , and $\tan \theta_2$ could just as easily have been substituted into **eq. 4** to obtain the same impedance. The negative values for $\tan \theta$ could have been used, giving a positive value for the impedance reactive component. Often, observation of the circuit can indicate the proper sign of the reactive component. If this isn't possible a second measurement can be made at another frequency, and the direction of change for the reactive component can be observed. For instance, a higher frequency should yield a lower capacitive reactance. If the reactance is inductive, the higher frequency should yield a higher value of reactance.

Another method of determining the sign of the reactance would be to insert a known reactance value in series with the measured impedance and make another measurement. For the example given above, an inductor of approximately $+j92$ ohms at 40.5 MHz ($0.36 \mu\text{H}$) would cancel the $-j92$ ohm reactance, leaving only a real component of 80 ohms. If the reactance happened to be positive in the first place, the second measurement would yield:

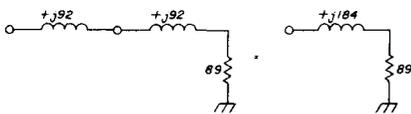

Actually, a second calculation isn't necessary, since it can quickly be seen that $89 + j0$ would yield a much lower SWR than $89 + j184$.

theory

The derivation of this concept follows directly by equating **eqs. 3** and **4**. This is reproduced here for reference:

$$Z = Z_{01} \left[\frac{1 - j(sw r_1) \tan \theta_1}{sw r_1 - j \tan \theta_1} \right] = Z_{02} \left[\frac{1 - j(sw r_2) \tan \theta_2}{sw r_2 - j \tan \theta_2} \right]$$

$$(1 - j sw r_1 \tan \theta_1) (sw r_2 - j \tan \theta_2) =$$

$$\frac{Z_{02}}{Z_{01}} (1 - j sw r_2 \tan \theta_2) (sw r_1 - j \tan \theta_1)$$

Equating the real and imaginary terms yields:

$$(A) sw r_2 - sw r_1 \tan \theta_1 \tan \theta_2 =$$

$$\frac{Z_{02}}{Z_{01}} (sw r_1 - sw r_2 \tan \theta_1 \tan \theta_2)$$

$$(B) sw r_1 sw r_2 \tan \theta_1 + \tan \theta_2 =$$

$$\frac{Z_{02}}{Z_{01}} (\tan \theta_1 + sw r_1 sw r_2 \tan \theta_2)$$

From A,

$$\left[\left(\frac{Z_{02}}{Z_{01}} \cdot sw r_2 \right) - sw r_1 \right] \tan \theta_1 \tan \theta_2 =$$

$$\left(\frac{Z_{02}}{Z_{01}} \cdot sw r_1 \right) - sw r_2$$

$$\tan \theta_1 \tan \theta_2 = \frac{\left[\left(\frac{Z_{02}}{Z_{01}} \right) (sw r_1) \right] - sw r_2}{\left[\left(\frac{Z_{02}}{Z_{01}} \right) (sw r_2) \right] - sw r_1}$$

From B,

$$\tan \theta_1 \left[(sw r_1 \cdot sw r_2) - \left(\frac{Z_{02}}{Z_{01}} \right) \right] =$$

$$\tan \theta_2 \left[\left(\frac{Z_{02}}{Z_{01}} \cdot sw r_1 \cdot sw r_2 \right) - 1 \right]$$

$$\frac{\tan \theta_1}{\tan \theta_2} = \frac{\left[\left(\frac{Z_{02}}{Z_{01}} \right) (sw r_1) (sw r_2) \right] - 1}{\left[(sw r_1) (sw r_2) \right] - \frac{Z_{02}}{Z_{01}}}$$

Exactly what transpires can readily be seen by looking at the Smith chart shown in **fig. 3**. The first SWR measurement, $sw r_1 = 4$, yields a reflection coefficient, ρ_1 , of 0.6. The electrical angle of the reflection coefficient, θ_1 , is found from $\tan \theta_1 = \pm 3.32$. Therefore, $\theta_1 = \pm 73.2^\circ$. Using only the positive value and knowing that the total distance around the Smith chart is 180° , one-half wavelength, the ratio of 73.2° to 180° gives a reflection coefficient at 0.203λ . This is shown as Z_1 and corresponds to the normalized impedance of $1.78 - j1.84$ for the 50-ohm measurement system. When the 112.5-ohm system is employed, $sw r_2 (2.5)$ results in a value of $\rho_2 = 0.43$. The reflection coefficient electrical angle, θ_2 , is 50.2° , found from $\tan \theta_2 = 1.2$. For this system the reflection coefficient in wave-lengths is 0.14λ . These values are also plotted on the Smith chart, but it must be remembered that the center of the chart represents 112.5 ohms $+ j0$. This normalized impe-

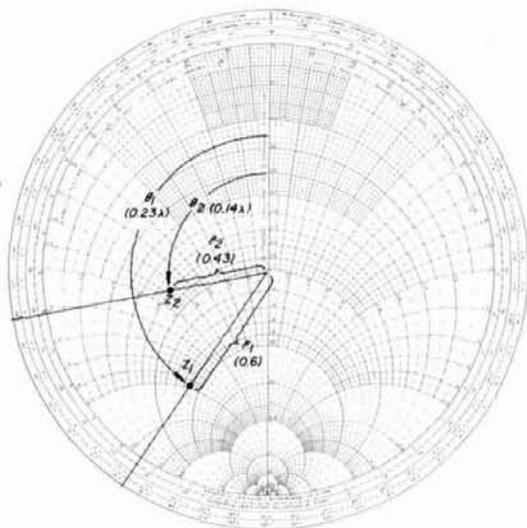


fig. 3. Test results shown on a Smith chart for the example described in the text.

dance is $0.79 - j0.82$ and is shown as Z_2 . Actually, both impedances, Z_1 and Z_2 , are equal; only the characteristic impedance of the measurement system is different.

One other point should be mentioned. Suppose the load is actually $82 - j83.6$, but a matching circuit is designed to match the source impedance to the measured value of $89 - j91.1$. How suitable is this? A new reflection coefficient must be determined from:

$$\Gamma = \rho \angle \theta = \frac{Z - Z_0}{Z + Z_0} \quad (8)$$

$$\text{where } Z_0 = 82 - j83.6, Z = 89 - j92.1$$

Making these substitutions yields a reflection coefficient of $\rho = 0.045$, which results in an SWR of 1.09:1.

conclusion

While there are many methods of measuring impedance, the procedure described is straightforward and requires only one simple instrument, the SWR meter. Also, since so many handheld calculators are available, the calculations using the measured values can be accomplished very quickly. Other means of calculating can be employed, although more time is required. The results are acceptable for most practical applications.

references

1. *Reference Data for Radio Engineers*, International Telephone and Telegraph Co., 4th edition, page 587.
2. Ben Lowe, K4VOW, "A 15-Watt Output Solid-State Linear Amplifier for 3.5 to 30 MHz," *QST*, December 1971, page 11.
3. *The Radio Amateur's Handbook*, ARRL, Newington, Connecticut, April 1975, page 581.

ham radio

State
of the art



by

K.V.G.

CRYSTAL FILTERS and DISCRIMINATORS

9.0 MHz FILTERS

XF9-A	2.5 kHz	SSB TX	\$40.65
XF9-B	2.4 kHz	SSB RX/TX	\$55.10
XF9-C	3.75 kHz	AM	\$59.30
XF9-D	5.0 kHz	AM	\$59.30
XF9-E	12.0 kHz	NBFM	\$59.30
XF9-M	0.5 kHz	CW (4 pole)	\$41.50
XF9-NB	0.5 kHz	CW (8 pole)	\$73.45

9.0 MHz CRYSTALS (Hc25/u)

XF900	9000.0 kHz	Carrier	\$4.75
XF901	8998.5 kHz	USB	\$4.75
XF902	9001.5 kHz	LSB	\$4.75
XF903	8999.0 kHz	BFO	\$4.75
F-05	Hc25/u	Socket Chassis	.50
F-06	Hc25/u	Socket P.C. Board	.50

Export
Inquiries
Invited

Shipping
\$1.50
per filter

VHF and UHF FILTERS

ELIMINATE IMD "BIRDIES"	144 MHz	PSf144	\$79.95
FROM YOUR RECEIVER.	432 MHz	PSf432	\$43.95
CLEAN UP YOUR TRANS-	1296 MHz	PSf1296	\$43.95
MITTER OUTPUT. Shipping	\$3.50		

OSCAR-J FILTERS



Suppress 2m Tx Third Harmonics. Low 2m loss (0.5dB typ.). High loss at 435 MHz (30/40dB).

MMf200-5
30 dB min. atten. \$29.95

MMf200-7
40 dB min. atten. \$39.95

Shipping \$2.50

LINEAR AMPLIFIERS

COMPATIBLE WITH OUR LOW
POWER TRANSVERTERS.

10W DRIVE, 50Ω IN/OUT

EDL432, 50W (ILLUS.) \$144.95

EDL432P, INCL. POWER SUPPLY/CABINET \$329.95

UPS Shipping at Cost



432 MHz SSB TRANSVERTERS

Use your HF Transceiver on the 432 MHz band with the addition of the MMt432 linear Transverter. The MMt432 operates on all modes; SSB, CW, AM, FM. It contains BOTH the linear transmit up-converter and the receive down-converter. An internal PIN diode T/R connects to your Transceiver T/R line. The MMt432 is FT101 and similar HF rig compatible. Add the 70/MBM4B MULTIBEAM and operate direct into OSCARS 7 & 8. Write for application note.

Specifications:

Output Power	10 W PEP
Drive, 10 Meters	1/2 W max
Receiver N.F.	3.0 dB typ
Receiver gain	30 dB typ
Prime Power	12 V D.C.

Shipping: \$3.50

MMt432-28S	\$309.95
MMt432-50	\$310.00
MMt438-ATV	\$330.00
MMt432-144	\$365.00



MMt144-28	\$239.95
Also Available:	
FMt440-146	\$175.00
QMt432-144	\$175.00

Send 30¢ (2 stamps) for full details of KVG crystal products and all your VHF & UHF equipment requirements.

Pre-Selector Filters	Amplifiers	SSB Transverters
Varactor Triplers	Crystal Filters	FM Transverters
Decade Pre-Scalers	Frequency Filters	VHF Converters
Antennas	Oscillator Crystals	UHF Converters



si

Spectrum
International, Inc.
Post Office Box 1084
Concord, Mass. 01742, USA

RF Transformer



- New! Broadband antenna matching.
- Convenient switch selection of impedance taps.
- For verticals and mobile whip antennas.
- Taps at 8, 12.5, 16, 22, 32 and 50 ohms.
- Full 500 watt capability. No time limit.

Here is the answer to the matching problem for vertical antennas and mobile whips. A broadband transformer that really works. Plenty of taps to match your 50 ohm transmitter to any short vertical.

And with no tuning or other adjustment. The 500 Watt RF Transformer is completely broadbanded 1-30 MHz (1-10 MHz below 20 ohms). So when you change frequency within a band you need only retune the antenna loading coil to resonance; not fiddle with a matching network.

Also, more power goes into your antenna. The 500 Watt RF Transformer is more efficient than a matching network or tuner — less than .1 db loss.

As always, when you buy Palomar Engineers you get the best; large ferrite toroid core, teflon insulated wire, rugged ceramic switch, heavy die cast aluminum case, full 500 watt CW capability.

Free descriptive brochure on request.

Improve your mobile operation. Simplify your tuneup. Get better results with the new Palomar Engineers 500 Watt RF Transformer.

Order yours now! Price \$35.00 plus \$2 shipping/handling U.S. & Canada. Calif. residents add sales tax.

Palomar Engineers

Box 455, Escondido, CA. 92025 • Phone: [714] 747-3343

THIS IS IT

WATT



MODEL 4431 THRULINE®

RF DIRECTIONAL WATTMETER
with VARIABLE RF
SIGNAL SAMPLER — BUILT IN
IN STOCK FOR PROMPT DELIVERY

AUTHORIZED DISTRIBUTOR

Webster
associates

115 BELLARMINE
ROCHESTER, MI 48063

CALL TOLL FREE

800 — 521-2333

IN MICHIGAN 313 — 375-0420

GILFER'S "BEST SELLER" SHORTWAVE BOOKS



Just Released 1979 Edition

CONFIDENTIAL FREQUENCY LIST
Identifies those thousands of HF stations (SSB, CW, FAX) between 4 and 26 MHz. \$6.95 ppd.

Just Released 33rd Edition

WORLD RADIO TV HANDBOOK
The "bible" of the shortwave listener — most comprehensive directory of stations plus last-minute info on skeds, new band allocations, best bands due to sunspots. \$14.95 ppd.

SPECIAL COMBO OFFER:


Both books only \$20 ppd.

**NEW FREE GILFER
SHORTWAVE CATALOG**

• Receivers • Antennas • Preselectors
• Tuners • Headphones • Clocks • Calibrators
• AM, FM & TV Directories • Logs and QSL Albums • Report Forms

GILFER SHORTWAVE
Dept. HR4, Box 239, Park Ridge, NJ 07656

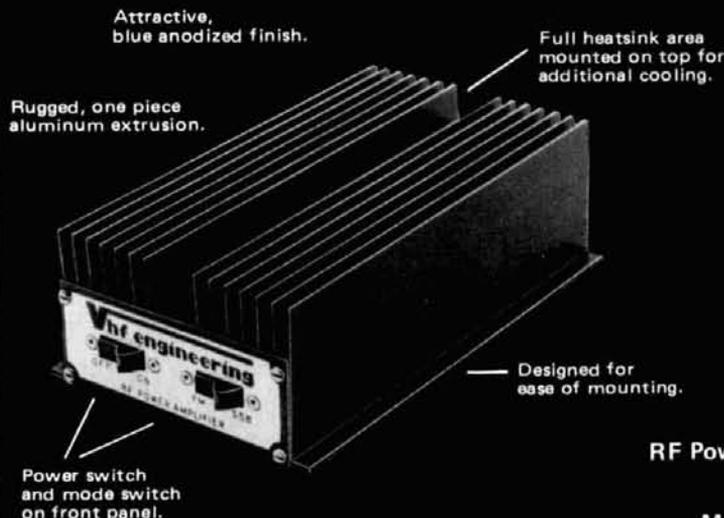Don't depend on your antenna to do all the work...



EXTEND YOUR RANGE
and improve weak signal area performance
with
Vhf engineering
BLUE LINE AMPLIFIERS

RF Power Amp, Wired & Tested, Emission — CW-FM-SSB/AM

FEATURES

- High efficiency means low current drain.
- Broad band design (no tuning).
- Direct 12 volt DC operation.
- Indicator lamps for On/Off and FM/SSB.
- Relay switching (allows you to put amplifier in or out of circuit at the flip of a switch).
- Insertion loss of less than 1 dB.
- 90 day limited warranty on parts and labor.

Model	BAND	Power Input	Power Output	Price
BLC 10/70	144 MHz	10W	70W	149.95
BLC 2/70	144 MHz	2W	70W	174.95
BLC 10/150	144 MHz	10W	150W	269.95
BLC 30/150	144 MHz	30W	150W	249.95
BLD 2/60	220 MHz	2W	60W	164.95
BLD 10/60	220 MHz	10W	60W	169.95
BLD 10/120	220 MHz	10W	120W	269.95
BLE 10/40	420 MHz	10W	40W	159.95
BLE 2/40	420 MHz	2W	40W	189.95
BLE 10/80	420 MHz	10W	80W	289.95

AVAILABLE ONLY AT THESE AUTHORIZED DEALERS

CALIFORNIA

C & A Electronic Enterprises, Carson, CA 90745, Ph. 213-834-5868
Tele Com Electronics, San Jose, CA 95121, Ph. 408-274-4479
Zackit Corporation, Vallejo, CA 94590, 707-644-6676

COLORADO

A.E.S. Communications, Wes-Com, Colorado Springs, CO 80909,
Ph. 303-475-7050

FLORIDA

Amateur Electronic Supply, Orlando, FL 32803, Ph. 305-894-3238
N & G Distributing, Miami, FL 33126, Ph. 305-592-9685
VHF/JAX, Orange Park, FL 32073, Ph. 904-264-7176

GEORGIA

Creative Electronics, Marietta, GA 30065, Ph. 404-971-2122

ILLINOIS

Klaus Radio, Peoria, IL 61614, Ph. 309-691-4840
Spectronics, Oak Park, IL 60304, Ph. 312-848-6777

IOWA

Bob Smith Electronics, Fort Dodge, IA 50501, Ph. 515-576-3886

MASSACHUSETTS

Tufts Radio Electronics, Medford, MA 02155, Ph. 617-395-8280

MICHIGAN

Adams Distributing, Detroit, MI 48228, Ph. 313-584-4640
The Ham Shack, Kentwood, MI 49508, Ph. 616-531-1976

MINNESOTA

PAL Electronics, Minneapolis, MN 55412, Ph. 612-521-4662

MISSOURI

Alpha Electronic Labs, Columbia, MO 65201, Ph. 314-449-1362

NEBRASKA

Communications Center, Lincoln, NE 68504, Ph. 402-466-3733

NEVADA

Communications Center West, Las Vegas, NV 89106, Ph. 702-647-3114

NEW YORK

Barry Electronics, New York, NY 10012, Ph. 212-925-7000
Delmar Electronics, W. Babylon, LI, NY 11704, Ph. 516-420-1234
VHF Communications, Jamestown, NY 14701, Ph. 716-664-6345

OHIO

Universal Amateur Radio, Reynoldsburg, (Columbus) Ohio 43068
Ph. 614-866-4267

OKLAHOMA

Derrick Electronics, Broken Arrow, OK 74012, Ph. 918-251-9923

PENNSYLVANIA

LaRue Electronics, Scranton, PA 18509, Ph. 717-343-2124

SOUTH DAKOTA

Burghardt Amateur Center, Watertown, SD 57201, Ph. 605-886-7314

TEXAS

AGL Electronics, Dallas, TX 75234, Ph. 214-241-6414
Madison Electronics Supply, Houston, TX 77002, Ph. 713-658-0268

VIRGINIA

Radio Communications, Roanoke, VA 24016, Ph. 703-342-8513

WASHINGTON

A-B-C Communications, Seattle, WA 98155, Ph. 206-364-8300

WISCONSIN

Amateur Electronic Supply, Milwaukee, WI 53216, Ph. 414-442-4200


CANADA

Bytown Marine Ltd., Ottawa, Ontario, Can. K2H 7V1, Ph. 613-820-6910
Traeger Distributors, Richmond, BC, Can. V6X 2A7, Ph. 604-278-1541

Vhf engineering

DIVISION OF BROWNIAN ELECTRONICS CORP.

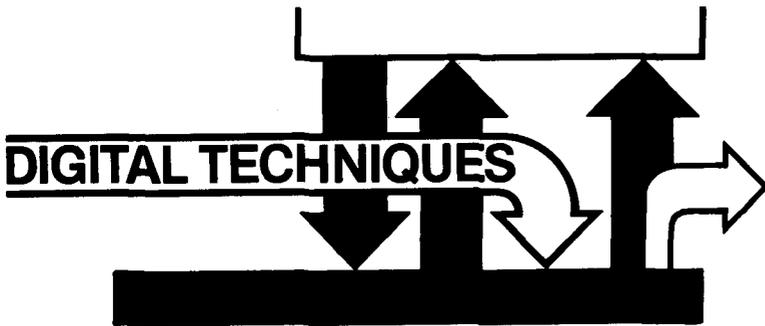Prices and specifications subject to change without notice.



flip-flop internal structure

Previous parts of this series have shown the three basic flip-flops, the latch, and clocked flip-flops JK and D. Only the RS latch has been examined for timing. Timing is crucial in proper operation of JK and D flip-flops, so it's worthwhile to examine some typical internal structures for timing relationships.

Fig. 1 shows a NAND-gate equivalent of a master-slave flip-flop with waveforms and "1 and 0" state notation. The master-slave term comes from using one latch (G3 and G4) to control the other latch (G7 and G8). State feedback makes each latch dependent on the other. The 1 and 0 notation is useful for scratchpad state analysis, and the state is that of each gate after the clock edge has passed.

JK flip-flops are commonly found in master-slave form, and fig. 1 has both J and K control inputs held high for a divide-by-two function. A negative clock edge will change output state, so the symbol would use an inversion bubble at the clock pin.

Initial conditions assume all inputs high and Q low. Master latch G3, G4 could be in either state but is chosen with G3 initially high. All gate states are stable in the left-hand 1 and 0 notation.

The first negative clock forces G1 high. G5 then goes low since both inputs are high (the *NAND RULE*) and forces G7 (Q output) high which, in turn, makes G8 (\bar{Q} output) low. Waveform arrows show the sequential state change. The other four gates remain in the same state as long as the clock is low.

Returning the clock high doesn't affect output but

will set up conditions for the next negative clock edge. G2 goes low and forces intermediate latch G3 and G4 to change state. G5 returns to a high, and output latches G7 and G8 remain stable (both G5 and G6 are now high).

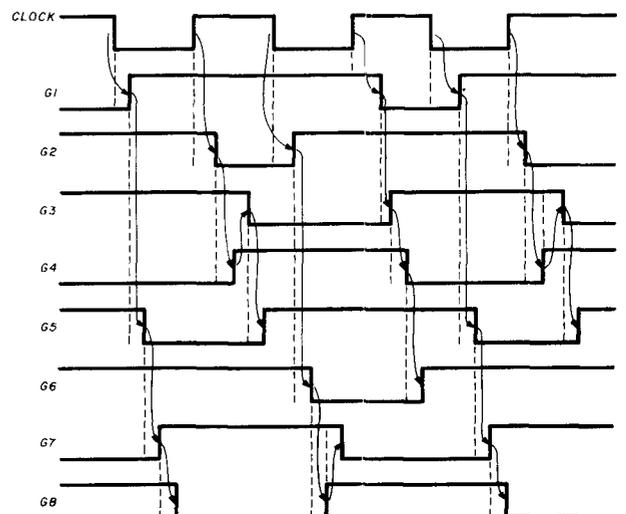
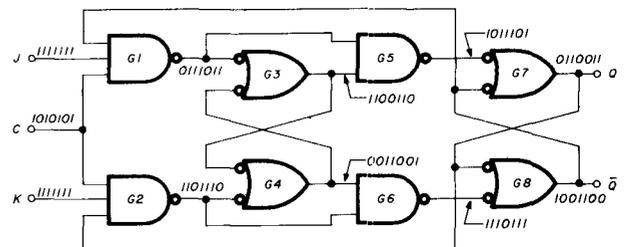


fig. 1. Master-slave flip-flop with J and K inputs held high.

A second negative clock will make G2 high. G6 now goes low and flips the output latch. Q output changes state. Returning the clock high will flip the intermediate latch and set up conditions for another output state change.

An important thing to note is that both clock edges affect internal states and that each edge causes a sequence of four gate state changes with attendant delays. A high clock level must persist long enough to set up conditions for an output change. A low clock level must persist for a time sufficient to ripple-through state changes to toggle the output. Each time will limit maximum clock frequency.

changing control inputs

Fig. 2 has the same circuit but input K is held low and only J is changed. Initial conditions have Q low and J low. Since K is low, G2 will always remain high. Note that if both J and K were held low, there would be no output change at all since input gates G1 and G2 would be held high constantly. The intermediate latch has G3 low.

The first low clock does nothing. Returning it high has no effect either, since J is held low. When J goes high with the clock high, the intermediate latch flips from the low state of G1. G6 goes high and the flip-flop is set up for an output change.

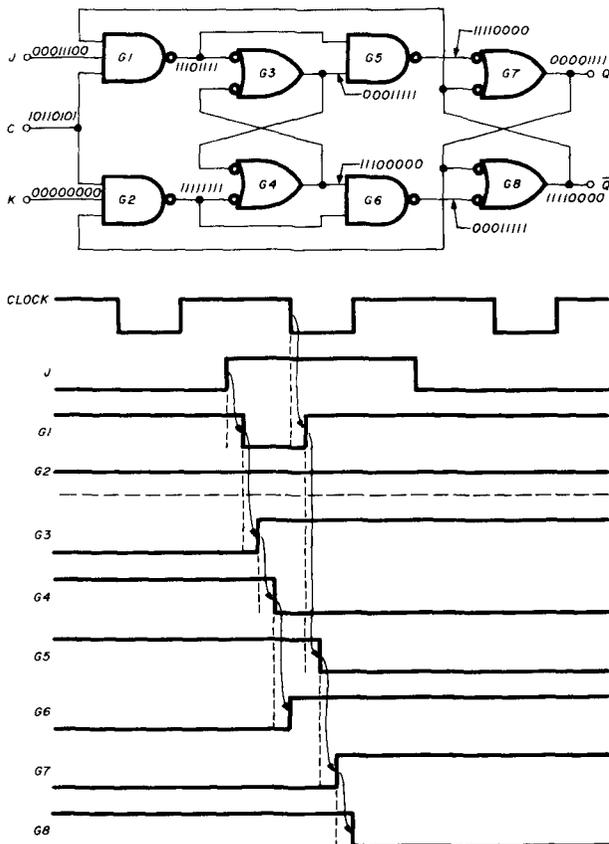


fig. 2. Master-slave flip-flop with K held low and J input switched.

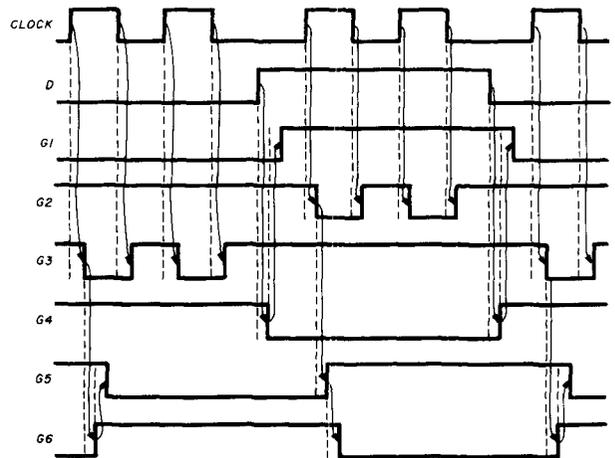
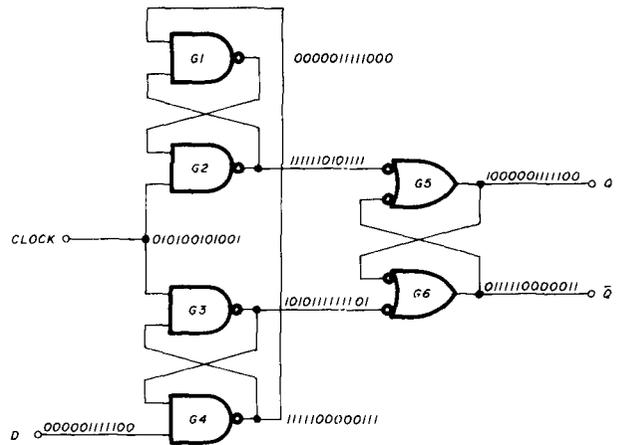


fig. 3. Type-D flip-flop.

The second low clock, while J is held high, will return G1 high and make G5 low. The output latch flips and Q goes high, matching the J input state. Again, four gate delays are required for both set-up and hold.

Once Q has toggled high, neither J nor the clock will have any effect. Why? The answer lies in state feedback from G8 (Q) to G1 input. The low G8 state will inhibit any inputs from changing G1 (the *NAND RULE* again).

Holding J low and changing only K will result in similar action, except that Q will eventually go low and remain in that state. Try this out on some scratchpaper.

type D flip-flop

A NAND gate equivalent is given in fig. 3. This version changes output on a *positive* clock edge. Gates G1 through G4 are "almost" latches with an *AND* symbol shape; their action is best observed by following input changes.

Initial state has Q high and D low. With both D input and clock low, G2 through G4 are held high. G1 is held low by state feedback from G4. Output latch

G5, G6 remains stable since all inputs (from G2 and G3) are high.

The first high clock will force G3 low; its other input from G4 is also high. G3 then forces G6 (Q) high to flip the output latch. Clock return to low will change only G3, as does a second clock input. G3 stays high on a low clock.

Changing D input high while the clock is low will force G4 low, which, in turn, forces G1 high. Input gates are now set up to change the output. A third positive edge clock will make G2 low and flip the output latch to a Q high state. As long as D remains high, further clocks will not change Q.

Returning D low while the clock is low will force G4 high, then G1 low to finish a setup. The cross connections of G1, G2, and G3, G4 appear to make two latches. These, plus G4 to G1 connection, make one large latch, not two, with G1 and G4 acting as inhibits for G2 and G3.

This structure is faster than the master-slave JK. Setup requires only two gate delays, output change only three.

direct set and reset

A direct set or reset will override the clock and any

control inputs. The master-slave JK may be modified by increasing the latch gate inputs from two to three. A SET (active low) is connected to both G3 and G7. A RESET (again, active low) is connected to both G4 and G8.

The D flip-flop is also modifiable for active-low set or reset but is more complex. A RESET is made to G2, G4, and G6, a SET made to only G1 and G5. The number of gate inputs must be increased for either.

Actual devices may have direct set and reset (sometimes called preset and clear, respectively) either active low or active high. Check for inversion bubbles. Some dual devices have either or both common. Check the spec sheet. In any situation an unused set or reset must be made inoperative. An unused active low should be tied high; unused active high tied low.

Removing a set or reset will restore a JK or D to normal clocked operation. Some time is required for this restoration, similar to setup and hold times. The spec sheet for a particular device should be checked for this and proper time allotted in circuit operation.

The next part of this series will go into interfacing analog signals and present one-shots.

ham radio

NEW — NEW — NEW from DATA SIGNAL

TOUCH TONE[®] MICROPHONE DataCoder 5



\$39⁰⁰

JUST LOOK AT THESE FEATURES:

- Tough "Mobile Environment" Microphone
- Positive-Action Tactile Keys
- High-Impedance Ceramic or 500-ohm Dynamic Cartridge
- Adjustable Tone Balance and Output Level
- "Positive Hold - Easy Lift" Hanger
- For Vehicle or Hand-held Portable Use
- Complete . . . Not a Kit . . . \$39.00

*Touch-Tone is a registered trade name of AT&T

MINIATURE ENCODERS DTM



MODEL DTM — Completely self-contained miniature encoder for hand-held portables. Only 5/16" thick. Three wire connection. Automatic PTT keying optional. With your choice of 12- or 16-digit Digitran keyboard.

Price DTM - \$39.00, DTM-PTT - \$49.00

SUB-MINIATURE ENCODERS



MODEL SME-1: Smallest available crystal-controlled Touch-Tone encoder, only 0.2" h x 0.5" w x 1.8" d. Complete with all connecting wires, mounts inside portable. **MODEL SME-2:** Only 1" square, mounts directly to pins on 12- or 16-digit Digitran keyboards. Price of either unit \$29.00 with choice of keyboards. SME-1 or SME-2 encoder only (less keyboard) \$24.00.

ds

DATA SIGNAL, INC.

2403 COMMERCE LANE
ALBANY, GEORGIA 31707, 912-883-4703



Be sure to ask about
our new keyers and CW
memory for CW buffs.

THERE IS A DIFFERENCE IN QUARTZ CRYSTALS

For more than a quarter century, International Crystal Mfg. Co., Inc. has earned a reputation for design and capability in manufacturing and marketing precision electronic products.


The market for International crystals is world wide. With a full range of types and frequencies available, International is a major supplier to the commercial and industrial crystal market.

International's leadership in crystal design and production is synonymous with quality quartz crystals from 70 KHz to 160 MHz. Accurately controlled calibration and a long list of tests are made on the finished crystal prior to shipment.

That is why we guarantee International crystals against defects, material and workmanship for an unlimited time when used in equipment for which they were specifically made.

Orders may be placed by Phone: 405/236-3741 • TELEX: 071-347 • CABLE: Incrystal • TWX: 910-831-3177 • Mail: International Crystal Mfg. Co., Inc., 10 North Lee, Oklahoma City, Oklahoma 73102.

Write for information.

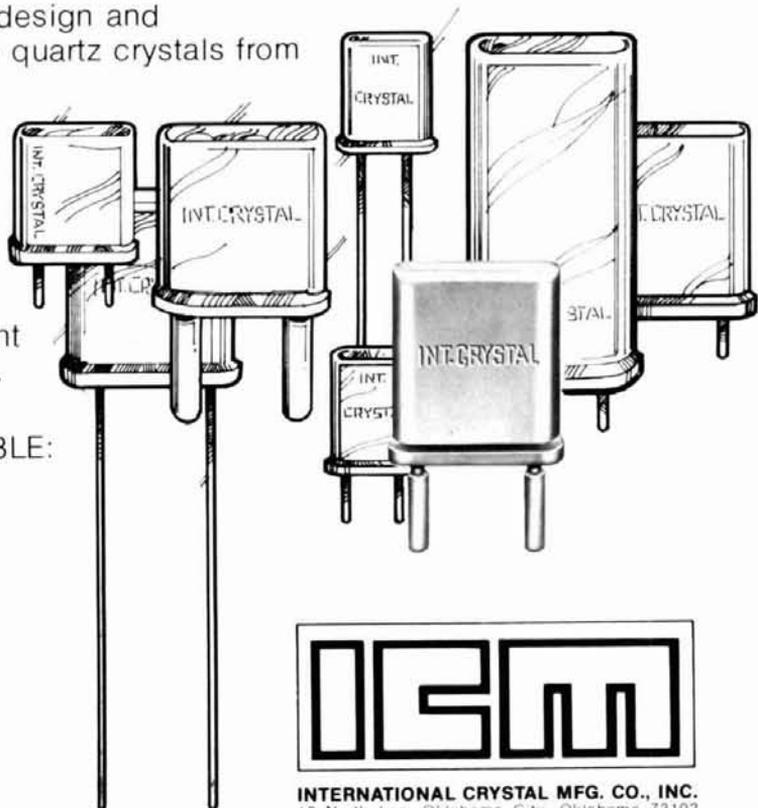

INTERNATIONAL CRYSTAL MFG. CO., INC.
10 North Lee, Oklahoma City, Oklahoma 73102

THE **NEW!** **ALDA 105:**
TRANSCEIVER

5-BAND HF SSB/CW COVERS 80 THROUGH 10 METER BANDS
BASE PRICE \$595. WITH CAL., NB, MIKE & MOBILE BRACKET: \$673.80

We also have

- ANTENNAS FOR HF & UHF
- ROTORS
- TOWERS
- REPEATERS
- MICROPHONES
- KEYS & KEYERS
- TUBES and much, much more

JUST CALL OR
WRITE FOR THE
BARRY PRICE;
BETTER STILL . . .
STOP IN!!

Yes, we have
EIMAC Tubes
& Chimneys,
and YAESU
Replacement
Tubes in stock!
Repair lab
on premises.

WE STOCK THESE FAMOUS NAME BRANDS

- | | | |
|-------------|------------|-------------|
| AEA | DRAKE | ROBOT |
| ALDA | EIMAC | ROHN |
| ANTENNA | E-Z WAY | STANDARD |
| SPECIALISTS | HY-GAIN | SWAN |
| ATLAS | ICOM | TEMPO |
| B & W | KDK | TEN-TEC |
| BIRD | KLM | TRI-EX |
| COLLINS | MFJ | VHF |
| CUSHCRAFT | MIRAGE | ENGINEERING |
| DSI | MOSLEY | WILSON |
| DENTRON | NEWTRONICS | YAESU |

BARRY ELECTRONICS

512 BROADWAY
NEW YORK, N. Y. 10012

(212) 925-7000

Now from J. W. Miller DAIWA CORPORATION Communications Essentials



RF Speech Processor Model RF-440

Increases talk power with splatter free operation. RF clipping assures low distortion. Simply install between microphone and transmitter.

Talk Power: Better than 6 dB
Clipping Threshold: Less than 2 mV at 1 KHz
Bandwidth: 2200 Hz at 6 dB down
Frequency Response: 300-3000 Hz at 12 dB down
Distortion: Less than 3% at 1 KHz, 20 dB clipping
Output Level: More than 50 mV at 1 KHz
Power Requirement: 115 VAC, 60 Hz, 1.4 W,
or 13.5 VDC, 55 mA
Dimensions: 150 x 70 x 150 mm, 6 x 2.5 x 6 in.



CN-720




CN-620

SWR & Power Meters Models CN-720 and CN-620

Simultaneous direct reading SWR,
Forward Power and Reflected Power

Frequency Range: 1.8-150 MHz
SWR Detection Sensitivity: 5 Watts Min.
Power: 3 Ranges (FWD 20/200/1000 Watts)
(REF 4/40/200 Watts)

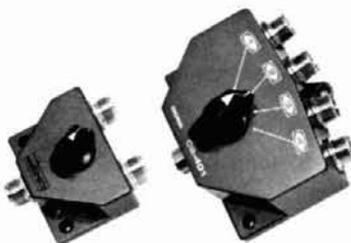Input/Output Impedance: 50 Ohm
Dimensions: 180 x 120 x 130 mm;
7 x 4.75 x 5 in.
165 x 75 x 97 mm;
6.5 x 3 x 4 in.



Coaxial Switches

2 Position/Model CS-201
4 Position/Model CS-401

Professionally engineered cavity
Construction: High Isolation
Power Rating: 2.5 kW PEP, 1 kW CW
Impedance: 50 Ohm
Insertion Loss: less than 2 dB
VSWR: 1:1.2
Maximum Frequency: 500 MHz
Isolation: Better than 60 dB at 300 MHz;
better than 45 dB at 450 MHz adjacent
terminal

Connectors: SO-239

**Exclusive USA agent for these units;
inquiries invited.**

Write for literature.



J. W. Miller Division BELL INDUSTRIES

19070 REYES AVE. ■ P.O. BOX 5825
COMPTON, CALIFORNIA 90224

SEE US AT THE
DAYTON HAMVENTION

90 **7th** april 1979

SYNTHESIZERS

We have the worlds largest selection of synthesizers for receivers, transmitters and transceivers. For complete details see our 1/3 page ad in the April 1976 issue of this magazine or call or write for additional information. Phone orders accepted between 9 AM and 4 PM EDT. (212) 468-2720

VANGUARD LABS

196-23 JAMAICA AVENUE
HOLLIS, N. Y. 11423



HAM REPEATER AUTOPATCH

Offer your club **COMPLETE**
emergency communications

Commercial quality, gold plated contacts, plug in, epoxy glass PC boards. 12 volt DC or 115 volt AC operation - Power supply included. Four digit access - Single digit releases - field programmable. Hybrid network - No switching required. FCC certified telephone line coupler. Auxiliary "In Use" contacts supplied. Land line "call-in" signalling control contacts provided. Price complete \$498 + \$3 shipping & handling. Master Charge, Bank money order, or certified check acceptable.

Accessories: CES-300 powered tone pad - \$59 BUS-COM Soft-touch® telephone powered mike/pad element - \$34.95.



MONROE ELECTRONICS, INC.
410 Housel Ave., Lyndonville, N.Y. 14098



FREQUENCY COUNTER KIT

Outstanding Performance

Incredible Price

\$89⁹⁵

CT-50

The CT-50 is a versatile and precision frequency counter which will measure frequencies to 60 mHz and up to 600 mHz with the CT-600 option. Large Scale Integration, CMOS circuitry and solid state display technology have enabled this counter to match performance found in units selling for over three times as much. Low power consumption (typically 300-400 ma) makes the CT-50 ideal for portable battery operation. Features of the CT-50 include: large 8 digit LED display, RF shielded all metal case, easy pushbutton operation, automatic decimal point, fully socketed IC chips and input protection to 50 volts to insure against accidental burnout or overload. And, the best feature of all is the easy assembly. Clear, step by step instructions guide you to a finished unit you can rely on.

Order your today!

- CT-50, 60 mHz counter kit **\$89.95**
- CT-50WT, 60 mHz counter, wired and tested **159.95**
- CT-600, 600 mHz scaler option, add **29.95**

- CB-1, Color TV calibrator-stabilizer **\$14.95**
- DP-1, DC probe, general purpose probe **12.95**
- HP-1, High impedance probe, non-loadier **15.95**

SPECIFICATIONS:

Frequency range: 6 Hz to 65 mHz, 600 mHz with CT-600
 Resolution: 10 Hz @ 0.1 sec gate, 1 Hz @ 1 sec gate
 Readout: 8 digit, 0.4" high LED, direct readout in mHz
 Accuracy: adjustable to 0.5 ppm
 Stability: 2.0 ppm over 10° to 40° C, temperature compensated
 Input: BNC, 1 megohm, 20 pF direct, 50 ohm with CT-600
 Overload: 50VAC maximum, all modes
 Sensitivity: less than 25 mv to 65 mHz, 50-150 mv to 600 mHz
 Power: 110 VAC 5 Watts or 12 VDC @ 400 ma
 Size: 6" x 4" x 2", high quality aluminum case, 2 lbs
 ICS: 13 units, all socketed

CAR CLOCK



The UN-KIT, only 5 solder connections

Here's a super looking, rugged and accurate auto clock which is a snap to build and install. Clock movement is completely assembled—you only solder 3 wires and 2 switches, takes about 15 minutes! Display is bright green with automatic brightness control photocell—assures you of a highly readable display, day or night. Comes in a satin finish anodized aluminum case which can be attached 5 different ways using 2 sided tape. Choice of silver, black or gold case (specify)

- DC-3 kit, 12 hour format **\$22.95**
- DC-3 wired and tested **\$29.95**
- 110V AC adapter **\$5.95**

Under dash car clock



12, 24 hour clock in a beautiful plastic case features 6 jumbo RED LEDs, high accuracy (1min. mo.), easy 3 wire hookup, display blanks with ignition, and super instructions. Optional dimmer automatically adjusts display to ambient light level

- DC-11 clock with mtg. bracket **\$27.95**
- DM-1 dimmer adapter **2.50**

PRESCALER



Extend the range of your counter to 600 mHz Works with any counter. Includes 2 transistor pre-amp to give super sens., typically 20 mv at 150 mHz. Specify +10 or +100 ratio

- PS-1B, 600 mHz prescaler **\$59.95**
- PS-1BK, 600 mHz prescaler kit **49.95**

OP-AMP SPECIAL

- 741 mini dip **12/\$2.00**
- B1-FET mini dip 741 type **10/\$2.00**

VIDEO TERMINAL

A completely self-contained, stand alone video terminal card. Requires only an ASCII keyboard and TV set to become a complete terminal unit. Two units available, common features are: single 5V supply, XTAL controlled sync and baud rates (to 9600), complete computer and keyboard control of cursor. Parity error control and display. Accepts and generates serial ASCII plus parallel keyboard input. The 3216 is 32 char. by 16 lines, 2 pages with memory dump feature. The 6416 is 64 char. by 16 lines, with scrolling, upper and lower case (optional) and has RS-232 and 20ma loop interfaces on board. Kits include sockets and complete documentation.

- RE 3216, terminal card **\$149.95**
- RE 6416, terminal card **189.95**
- Lower Case option, 6416 only **13.95**
- Power Supply Kit **14.95**
- Video /RF Modulator, VD-1 **6.95**
- Assembled, tested units, add **60.00**

CALENDAR ALARM CLOCK

The clock that's got it all! 6-5" LEDs, 12, 24 hour snooze, 24 hour alarm, 4 year calendar battery backup, and lots more. The super 7001 chip is used. Size 5x4x2 inches. Complete kit, less case (not available)

- DC-9 **\$34.95**

30 Watt 2 mtr PWR AMP

Simple Class C power amp features 8 times power gain. 1 W in for 8 out, 2 in for 15 out, 4 W in for 30 out. Max. output of 35W incredible value, complete with all parts, less case and T-R relay

- PA-1, 30 W pwr amp kit **\$22.95**
- TR-1, RF sensed T-R relay kit **6.95**

FM MINI MIKE KIT



A super high performance FM wireless mike kit! Transmits a stable signal up to 300 yards with exceptional audio quality by means of its built in electret mike. Kit includes case, mike, on-off switch, antenna, battery and super instructions. This is the finest unit available

- FM-3 kit **\$12.95**
- FM-3 wired and tested **16.95**

CLOCK KITS



our Best Seller your Best Deal

Try your hand at building the finest looking clock on the market. Its satin finish anodized aluminum case looks great anywhere, while six 4" LED digits provide a highly readable display. This is a complete kit, no extras needed, and it only takes 1-2 hours to assemble. Your choice of case colors: silver, gold, bronze, black, blue (specify)

- Clock kit, 12, 24 hour, DC-5 **\$22.95**
- Clock with 10 min. ID timer, 12, 24 hour, DC-10 **27.95**
- Alarm clock, 12 hour only, DC-8 **24.95**
- 12V DC car clock, DC-7 **27.95**

For wired and tested clocks add \$10.00 to kit price

Ramsey's famous MINI-KITS

FM WIRELESS MIKE KIT

Transmits up to 300' to any FM broadcast radio, uses any type of mike. Runs on 3 to 9V. Type FM-2 has added sensitive mike preamp stage

- FM-1 kit **\$2.95**
- FM-2 kit **\$4.95**

VIDEO MODULATOR KIT

Converts any TV to video monitor. Super stable, tunable over ch. 4-6. Runs on 5-15V, accepts std. video signal. Best unit on the market!

- Complete kit, VD-1 **\$6.95**

SUPER SLEUTH

A super sensitive amplifier which will pick up a pin drop at 15 feet! Great for monitoring baby's room or as general purpose amplifier. Full 2 W rms output, runs on 6 to 15 volts, uses 8-45 ohm speaker

- Complete kit, BN-9 **\$5.95**

COLOR ORGAN/MUSIC LIGHTS

See music come alive! 3 different lights flicker with music. One light for low-range for the mid-range and one for the highs. Each channel individually adjustable, and drives up to 300W. Great for parties, band music, nite clubs and more

- Complete kit, ML-1 **\$7.95**

tone DECODER

A complete tone decoder on a single PC board. Features: 400-5000 Hz adjustable range via 20 turn pot, voltage regulation, 567 IC. Useful for touch-tone decoding, tone burst detection, FSK, etc. Can also be used as a stable tone encoder. Runs on 5 to 12 volts.

- Complete kit, TD-1 **\$5.95**

POWER SUPPLY KIT

Complete triple regulated power supply provides variable 6 to 18 volts at 200 ma and +5V at 1 Amp. Excellent load regulation, good filtering and small size. Less transformers, requires 6 3V @ 1 A and 24 VCT.

- Complete kit, PS-3LT **\$6.95**

LED BLINKY KIT

A great attention getter which alternately flashes 2 jumbo LEDs. Use for name badges, buttons, warning panel lights, anything! Runs on 3 to 15 volts.

- Complete kit, BL-1 **\$2.95**

WHISPER LIGHT KIT

An interesting kit, small mike picks up sounds and converts them to light. The louder the sound! the brighter the light. Completely self-contained, includes mike, runs on 110VAC, controls up to 300 watts

- Complete kit, WL-1 **\$6.95**

SIREN KIT

Produces upward and downward wail characteristic of a police siren. 5W peak audio output, runs on 3-15 volts, uses 3-45 ohm speaker

- Complete kit, SM-3 **\$2.95**

Hard to find PARTS

LINEAR ICs	REGULATORS	
301	78MG	\$1.25
324	723	.50
380	309K	.85
380-8	7805	.85
555	78L05	.25
556	7905	1.25
566	7812	.85
567	7912	1.25
1458	7815	.85
3900	50	
4011	20	
4013	35	
4046	185	
4049	40	
4518	125	
5369	175	
CMOS ICs	TTL ICs	
2N3904 type	74500	.35
2N3906 type	7447	.65
NPN 30W Pwr	7475	.50
PNP 30W Pwr	7490	.50
2N3055	74196T1	1.35
UJT 2N2646 type	SPECIAL ICs	
FET MPF102 type	11C90	13.50
UMF 2N5179 type	10116	1.25
MRF-238 RF	4511	2.00
	5314	2.95
	5375AB	2.95
	7001	6.50
	4059-N	9.00
	7208	17.95
	LEDs	
	Jumbo red	8 1.00
	Jumbo green	6 1.00
	Jumbo yellow	6 1.00
	Mini red	8 1.00
	Micro red	8 1.00
	BiPolar	75
	FERRITE BEADS	
	With info, specs	15 1.00
	6 hole balun	5 1.00

ramsey electronics

PHONE ORDERS CALL (716) 271-6487

TERMS: Satisfaction guaranteed or money refunded. COD, add \$1.50. Minimum order \$6.00. Orders under \$10.00, add \$.75. Add 5% for postage, insurance, handling. Overseas, add 15%. NY residents, add 7% tax.

the ham notebook

external frequency programmer

The beauty of the IC-22S is that it offers precise frequency selection by programming with low-cost silicon diodes, rather than crystals with trimmers. This advantage though becomes overshadowed when channel selections need to be changed; out comes the soldering iron to redo the diode matrix. To solve this problem, I built an external programmer containing eight switches, eight diodes, and a zero-center microammeter for discriminator output readings.

The internal speaker was disconnected from the external speaker jack and reconnected directly to the audio output. The discriminator output was then connected to the external speaker jack. The eight diode/cathode connections and the 9-volt common pad of channel 22 on the



External frequency programmer enclosed in a Ten-Tec style box. The connections to the transceiver are made via nine-conductor ribbon cable.

matrix board were connected to the nine pins of the accessory socket via a nine-conductor ribbon cable (see fig. 1).

The external programmer was built in a Ten-Tec cabinet. The discriminator meter was connected via a shielded cable and miniplug. Nine-conductor ribbon cable was used to

connect the programmer to the accessory plug.

With the programmer, any frequency can be selected at the flip of a switch and at a considerable savings over the cost of a fully programmable 2-meter rig.

Hugh Pearl, WB9VWM

using the IC-22S below 146 MHz

As it turns out, the IC-22S is not restricted to 146.01 MHz and above. The IC-22S is, in fact, usable without modification from 145.350 MHz through 147.990 MHz. That's an additional 44 free channels! These additional channels do accommodate some of the new repeater frequencies as well as five Oscar frequencies. By keying the push-to-talk line you can also enjoy the excitement of Oscar 7 and Oscar 8.

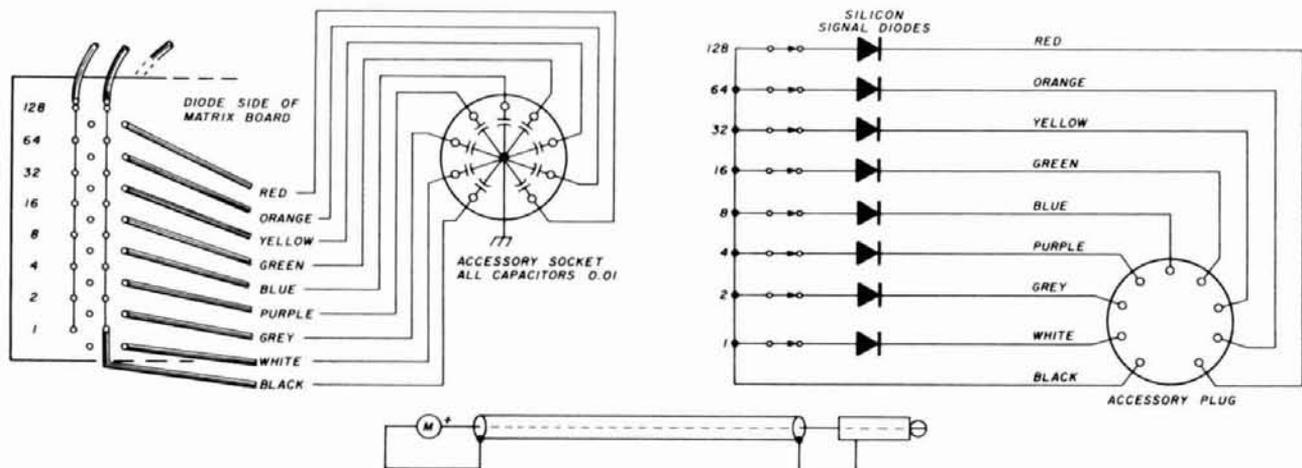


fig. 1. Diagram of the connections to the diode matrix board and switch connections for the external frequency programmer. The discriminator meter is connected to the rewired external speaker jack.

table 1. Diode programming matrix for frequencies below 146 MHz.

frequency MHz	total N	diode insert positions								frequency MHz	total N	128 D7	64 D6	32 D5	16 D4	8 D3	4 D2	2 D1	1 D0
		128 D7	64 D6	32 D5	16 D4	8 D3	4 D2	2 D1	1 D0										
145.350	64	*								145.680	86	*						*	*
145.365	65	*							*	145.695	87	*		*			*	*	*
145.380	66	*							*	145.710	88	*		*			*	*	*
145.395	67	*							*	145.725	89	*		*	*		*	*	*
145.410	68	*						*	*	145.740	90	*		*	*	*	*	*	*
145.425	69	*						*	*	145.755	91	*		*	*	*	*	*	*
145.440	70	*						*	*	145.770	92	*		*	*	*	*	*	*
145.455	71	*						*	*	145.785	93	*		*	*	*	*	*	*
145.470	72	*						*	*	145.800	94	*		*	*	*	*	*	*
145.485	73	*						*	*	145.815	95	*		*	*	*	*	*	*
145.500	74	*						*	*	145.830	96	*		*	*	*	*	*	*
145.515	75	*						*	*	145.845	97	*		*	*	*	*	*	*
145.530	76	*						*	*	145.860	98	*		*	*	*	*	*	*
145.545	77	*						*	*	145.875	99	*		*	*	*	*	*	*
145.560	78	*						*	*	145.890	100	*		*	*	*	*	*	*
145.575	79	*						*	*	145.905	101	*		*	*	*	*	*	*
145.590	80	*		*				*	*	145.920	102	*		*	*	*	*	*	*
145.605	81	*		*				*	*	145.935	103	*		*	*	*	*	*	*
145.620	82	*		*				*	*	145.950	104	*		*	*	*	*	*	*
145.635	83	*		*				*	*	145.965	105	*		*	*	*	*	*	*
145.650	84	*		*				*	*	145.980	106	*		*	*	*	*	*	*
145.665	85	*		*				*	*	145.995	107	*		*	*	*	*	*	*

The programming of the IC-22S diode matrix is governed by the equation:

$$\text{programmed number (N)} = \frac{\text{desired frequency} - 144.39}{.015}$$

The resulting number must be an integer (no fractional part). The decimal number computed from the equation is then translated into a binary number and programmed accordingly into the diode matrix. For convenience, table 1 presents the

additional frequencies and the corresponding diode positions in a format similar to that in the instruction manual. The simplex-offset switch functions the same as for other frequencies below 147 MHz.

Steven Holzman, W1IBI

75S () CW sidetone

The CW sidetone provided by my 32S-1 transmitter is of sufficient amplitude to give an adequate monitoring level while using headphones. Even when low-impedance headphones (stereo types with the sections paralleled) were used, no prob-


lems were encountered here.

In an attempt to increase the sidetone level while using a speaker, the value of R99 (2.2 meg ohms) was altered. This change proved insufficient, and, if carried too far, vox operation on ssb was hampered. The best balance between speaker, head-

phones, overall receiver volume, and CW sidetone level was obtained in the following manner.

Remove the two wires connected to the SIDETONE jack on the receiver rear lip, solder them together, and insulate. Using a piece of shielded wire (RG-174/U in my case), connect one end to the SIDETONE jack and the other end to the center (wiper) terminal of the AF GAIN control. The cable should be neatly routed around the chassis following the path of the existent harness. Refer to fig. 2 for the complete wiring changes. The result is a sufficient sidetone level for both speaker and phones.

fig. 2. Sidetone modification for the 75S() series receivers. In this case, the level of the sidetone is controlled by the AF GAIN, providing a better balance between signal and sidetone levels. The heavy line indicates the added shielded cable.

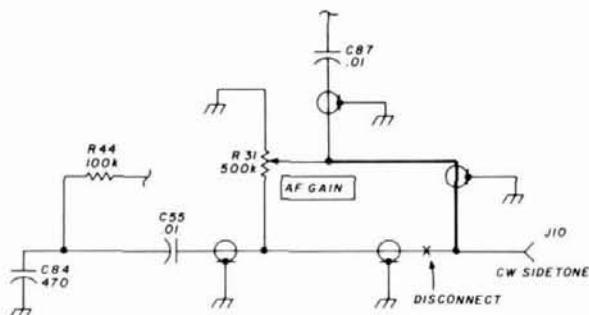

Paul Pagel, N1FB

SST-4

ULTRA TUNER DELUXE



ULTRA TUNER DELUXE. Matches any antenna—coax fed or random wire on all bands (160-10 meters). Tune out the SWR on your antenna for more efficient operation of any rig. Home, mobile, portable—only 9" x 2 1/2" x 5 1/2" • 300 watt RF output capability • SWR meter with 2-color scale • Antenna Switch selects between two coax fed antennas, random wire, or tuner bypass • Efficient Airwound inductor • 208 pf. 1000V. Capacitors • Attractive bronze finished enclosure.

only \$64.95

SST-2 ULTRA TUNER

Tunes out SWR on any antenna—coax fed or random wire (160-10 meters). Any rig—up to 200 watts RF output. Rugged, yet compact: 5 1/4" x 2 1/4" x 2 1/2".



only \$37.95

SST-3 MOBILE IMPEDANCE TRANSFORMER

Matches 52 ohm coax to the lower impedance of a mobile whip. Taps between 3 and 50 ohms, 3-30 MHz, 300 watts output. 2 1/4" x 2" x 2 1/4".



only \$19.95

SST-1 RANDOM WIRE ANTENNA TUNER

All bands (160-10 m.) with any wire • 200W output • Any transceiver • Home or portable • Neon tune-up indicator.



only \$29.95

SST DL-1 KIRBY DUMMY LOAD, 1000W PEP 1.5:1 1-225 MHz. Scaled, 3-1/8" x 4-3/8".

only \$17.95

SST CL-1 24 HR. CLOCK. Giant red LED numerals. Month and day also at push of button. Beautiful for your desk. 110VAC.

only \$22.95

SST B-1 BALUN for balanced lines, 300W.

only \$5.00

Call (213) 376-5887 to order C.O.D., VISA, or Master Charge.

To Order:

Send a check or money order—or use your M.C. or VISA. Add 8% shipping and handling. Calif. residents, add sales tax.

Guarantee: All SST products are unconditionally guaranteed for 1 year. In addition, they may be returned within 10 days for a full refund (less shipping) if you are not satisfied for any reason.

SSS
ELECTRONICS
P.O. BOX 1 LAWDALE, CALIF.
90260 (213) 376-5887

SPRING SPECIALS

KLM 144-148 - 13 lb	\$ 59.95	8214 RG8 Foam	0.25
OMNI-J & heavy duty magnet mount complete	49.95	8237 RG8	0.21
TRIEX W-51 FT self-support tower (Reg \$825)		8267 RG213	0.25
Your cost (FOB California)	725.00	Amphenol Silver Plate PL259	0.59
Tonna F9FT Antennas 144/16 el.	79.95	Times 1/2" Foam Hardline \$0.65/ft. —	
RIW 432 19 el	59.95	Connectors, ea	15.00
Klitzing VHF-UHF Amplifiers		7/8" Hardline \$1.50/ft. —	
2M 10W in - 100W Out	198.00	Connectors, ea	25.00
432 10W in - 50W Out	198.00	Berktek RG8X, 52 ohm, KW per ft	0.16
Bird 43 and slugs. UPS paid in USA	stock	Consolidated HD-18 Ga Galv Tower, 10' section	29.95
Microwave Modules 432-28S	329.95	Robot "Slow Scan" Now in Stock	Call
Deluxe Amp 432-100W output	398.00	Alliance HD73 Rotor	109.95
Telrex TB5EM, in stock	415.00	Teletow'r self support:	
NEW Palomar Engr. Transceiver		55 ft/w breakover	499.00
Preamp	89.50	40 ft/w breakover	349.00
Bencher Paddles — \$39.95 Chrome	49.95		
ETO 76 Amplifiers	stock		
Lunar 6M-2M-220 In Line Preamps	49.95		
Lunar 2M Amp 10-80 w/Preamp.			
UPS paid USA	198.00		
Janel QSA-5	41.95		
CDE Ham-3 — \$129.95; Ham-X — \$209.95			
NEW Ham-4	157.50		
VHF Engrs. blue line amps	stock		
Cetron 572B	29.50		
Motorola HEP 170	0.29		
Mallory 2.5A/1000 PIV Epoxy Diode	0.19		
Aerovox 1000PF/500V Feed thru	1.95		
GE6146B or 8950	7.95		
Technical Books, Ameco, ARRL, Sams, Tab. Rider Radio Pub., Callbook, Cowan, etc.	Call		
NEW Belden 9405 (2#16)X(6#18) 8 wire rotor cable, heavy duty for long runs.			
per ft.	0.26		
8448 std. 8 wire rotor, per ft.	0.16		
9888 double shield RG8 Foam, per ft.	0.39		

THIS MONTH'S SPECIALS:

Icom IC280 — \$395.00
Dentron GLA 1000 Amp. — \$319.00
Bearcat 250 — \$299.00

All prices fob Houston except where indicated. Prices subject to change without notice, all items guaranteed. Some items subject prior sale. Send letterhead for Dealer price list. Texas residents add 6% tax. Please add postage estimate \$1.00 minimum.

MADISON

ELECTRONICS SUPPLY, INC.

1508 McKINNEY

HOUSTON, TEXAS 77002

713/658-0268

RTTY for ALL Systems



ELECTROCOM® "SERIES 400" FREQUENCY SHIFT CONVERTERS

Professionally engineered for outstanding performance, stability, and reliability, the Electrocom® Models 400 and 402 add new dimensions of compatibility between radio and teletypewriter systems. Manufactured to highest quality standards—an Electrocom tradition for nearly two decades—these units are ideal for military, government, commercial, civil defense and amateur applications. The Model 400 front panel digital knob accurately selects shifts up to 1000 Hz, while two such knobs on the Model 402 independently set the mark and space frequencies. Both models may also be preset with any tone pair between 1000 and 3200 Hz.

Optimum performance with FSK or AFSK

systems is assured by matched filters, precision linear detectors, baud rate selector, bias compensation, and semi-diversity circuitry. Operation is enhanced by a CRT monitor, autostart with solid-state motor switching, antispacer, markhold, EIA/MIL output voltages, and a constant current loop supply. In addition, various options are available including rack mounting and polar current output.


Write or call us for complete product details and specifications. Learn why Electrocom® "400" Converters are designed not only for today's communication environment, but ultimately to fulfill RTTY requirements for years to come.

Electrocom® INDUSTRIES

1105 N. IRONWOOD DRIVE, SOUTH BEND, INDIANA 46615

Telephone: (219) 232-2743

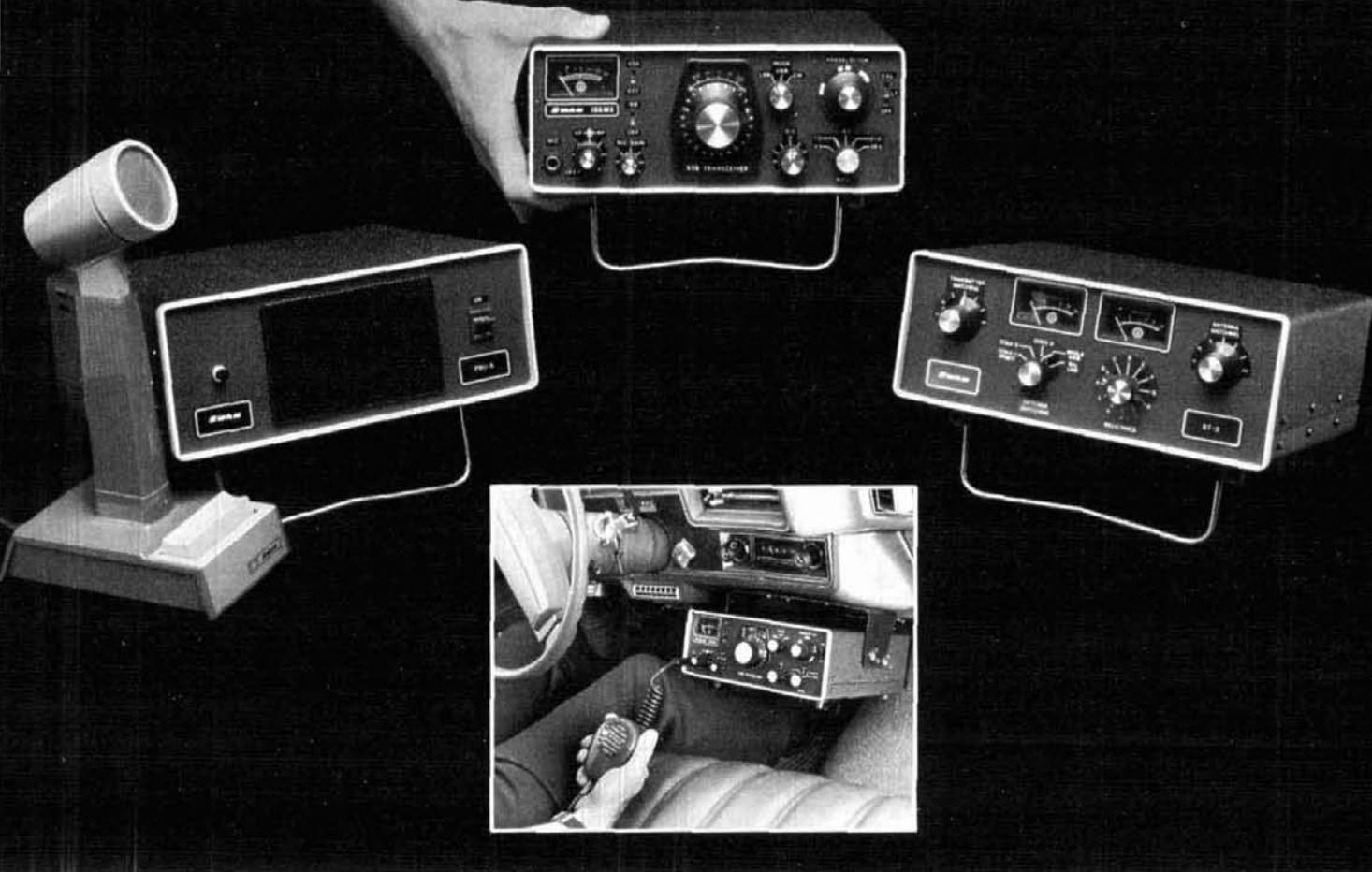BREAKS THROUGH EVERY HF SOUND BARRIER --INSIDE AND OUT!



**The revolutionary Swan 100 MX: 100% new, 100% solid state,
100% portable from home station to mobile!**

Introducing a superb "get up and go" transceiver, superbly designed for 100% mobility and control, as only new Swan space-age technology could do it!

100% solid state 100 MX: the compact HF unit you can take seriously — anywhere you choose to operate.

At home, set into Swan's unique new style-coordinated station, with *matching* antenna tuner and power supply.

Or on the road — it's easy to relocate 100 MX. Instantly. Just two simple connections on the back panel: snap out, snap in... and run!

100% improved audio quality: home or mobile, transmit or receive. 100 MX electronics cut through SSB sound barriers —

producing a natural clarity reported comparable to AM!

Your most-wanted extras, 100% built-in: like noise blanker and VOX. Like a preselector to optimize signals. Like a real RF GAIN control, and CW sidetone.

Swan includes the RIT control (± 1.5 kHz) you'd like too. Plus, for stability, a permability tuned oscillator with 1Kc readout.

A powerful package, delivering a *minimum* 100 watts PEP output on all bands, 10-80 meters.

Setting a 100% new state of art: 100 MX and our matched-station units. Ready for check out today at your Swan dealer, the first major breakthrough in Swan's new program dedicated to changing the face — and performance — of ham equipment 100%...inside and out!

Available only through authorized Swan dealers.

Please rush full specs on Swan's all-new 100 MX home/mobile transceiver.

Name _____

Address _____

City _____

State _____ Zip _____

 **SWAN**
ELECTRONICS

a member of the Cubic Corporation family of companies

305 Airport Road, Oceanside, CA 92054
(714) 757-7525

Swan's continuing commitment to product improvement may affect specifications and prices without notice

Heavy Duty Power Supplies

from **ASTRON**
High Quality • Rugged • Reliable

SPECIAL FEATURES

- SOLID STATE ELECTRONICALLY REGULATED
- FOLD-BACK CURRENT LIMITING Protects Power Supply from excessive current & continuous shorted output.
- CROWBAR OVER VOLTAGE PROTECTION on Models RS-7A, RS-12A, RS-20A, & RS-35A.
- MAINTAIN REGULATION & LOW RIPPLE at low line input Voltage.
- HEAVY DUTY HEAT SINK • CHASSIS MOUNT FUSE
- THREE CONDUCTOR POWER CORD
- ONE YEAR WARRANTY • MADE IN U.S.A.

PERFORMANCE SPECIFICATIONS

- INPUT VOLTAGE: 105 - 125 VAC
- OUTPUT VOLTAGE: 13.8 VDC \pm 0.05 volts (Internally Adjustable: 11-15 VDC)
- RIPPLE: Less than 5mv peak to peak (full load & low line)
- REGULATION: \pm .05 volts no load to full load & low line to high line




ASTRON 12 AMP REGULATED POWER SUPPLY Model RS-12A

9 Amps continuous
12 Amps ICS*
4" (H) \times 8" (W) \times 9" (D)
Shipping Weight 13 lbs.
Price..... \$72.95

Other popular POWER SUPPLIES also available: (Same features and specifications as above)

Model	Continuous Duty (amps)	ICS* (amps)	Size (in.) H \times W \times D	Shipping Wt. (lbs.)	Price
RS-35A	25	35	5 \times 11 \times 11	29	\$136.95
RS-20A	16	20	5 \times 9 \times 10½	20	\$94.95
RS-7A	5	7	3¼ \times 6 \times 7½	7½	\$49.95
RS-4A	3	4	3¼ \times 6 \times 7½	5	\$39.95

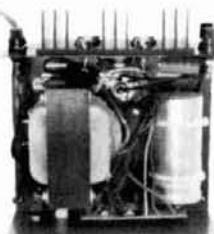*ICS — Intermittent Communication Service (50% Duty Cycle)
If not available at your local dealer, please contact us directly.



Inside View — RS-12A

ASTRON CORPORATION

1971 SOUTH RITCHEY ST., SANTA ANA, CA 92705 (714) 835-0682

JAN CRYSTALS

HOLD THE FREQUENCY

- CB
- CB standard
- 2 meter
- Scanners
- Amateur Bands
- General Communication
- Industry
- Marine VHF
- Micro processor crystals

Send 10¢ for our latest catalog. Write or phone for more details.

easy to charge

2400 Crystal Drive
Ft. Myers, Florida 33907
all phones (813) 936-2397

STEP UP TO TELREX

WITH A

TELREX "BALUN" FED—"INVERTED-VEE" KIT
THE IDEAL HI-PERFORMANCE

INEXPENSIVE AND PRACTICAL TO INSTALL LOW-FREQUENCY
MONO OR MULTIPLE BAND, 52 OHM ANTENNA SYSTEM



Telrex "Monarch" (Trapped) I.V. Kit
Duo-Band / 4 KWP I.V. Kit \$63.50
Post Paid Continental U.S.

Optimum, full-size doublet performance, independent of ground conditions! "Balanced-Pattern", low radiation angle, high signal to noise, and signal to performance ratio! Minimal support costs, (existing tower, house, tree). A technician can resonate a Telrex "Inverted-Vee" to frequency within the hour! Minimal S/W/R is possible if installed and resonated to frequency as directed! Pattern primarily low-angle, Omnidirectional, approx. 6 DB null at ends! Costly, lossy, antenna tuners not required! Complete simplified installation and resonating to frequency instructions supplied with each kit.

For technical data and prices on complete Telrex line, write for Catalog PL 7 (HRH)



ALUMA TOWERS

40 Ft. Crank-Up Ham Model T-140
60 Ft. Ham Crank-Up Model T-60-H

HIGHEST QUALITY

MADE IN ALUMINUM

- ★ TELESCOPING (CRANK UP)
- ★ GUYED
- ★ TILT OVER MODELS

QUALITY MADE

Excellent for

HAM COMMUNICATIONS

MANY MODELS MFG.

Towers to 100 feet. Specials designed & made. See dealer or send for free catalog.

ALUMA TOWER CO.
BOX 2806HR
VERO BEACH, FLA. 32960
PHONE (305) 567-3423

SAVE \$25.00

Model 8100 Frequency Counter Kit

- Range: 20Hz to 100MHz
- High Sensitivity
- Resolution to 0.1Hz



Now you can forget about price/performance trade-offs when you select a frequency counter. In Sabtronics' Model 8100 kit you get all the characteristics of superior performance at a low, affordable price.

This frequency counter, employing LSI technology, has the performance and input characteristics you demand: guaranteed frequency range of 20Hz to 100MHz (10 Hz to 120MHz typical); selectable hi/lo impedance; superior sensitivity; selectable resolution and selectable attenuation. Plus an accurate time base with excellent stability.

An 8-digit LED display features gate activity indicator, leading zero suppression and overflow indicator. You would expect to find all these features only on high-priced instruments — or from Sabtronics' advanced digital technology.

BRIEF SPECIFICATIONS:

- Frequency Range: 20Hz to 100MHz guaranteed. (10Hz to 120MHz typical) • Sensitivity: 15mV RMS, 20Hz to 50MHz (10mV typical); 25mV RMS, 50MHz to 100MHz (20mV typical)
- Selectable Impedance: 1M Ω /25pF or 50 Ω • Attenuation: X1, X10 or X100 • Accuracy: \pm 1Hz plus time base accuracy • Aging Rate: \pm 5ppm/yr. • Temperature Stability: \pm 10ppm, 0 $^{\circ}$ C to 40 $^{\circ}$ C
- Resolution: 0.1Hz, 1Hz, 10Hz selectable • Display: 8-digit LED, overflow indicator, gate activity indicator • Overload Protection
- Power Requirement: 9-15 VDC @ 330mA



Model 2000, 3 1/2 Digit DMM Kit

- 5 Functions, 28 Ranges
- Basic DCV Accuracy: 0.1% \pm 1 Digit

The amazing Sabtronics 2000 is the choice of both professionals and hobbyists. It's the only portable/bench DMM that offers so much performance for such an astonishing low price.

You get basic DCV accuracy of 0.1% \pm 1 digit; 5 functions giving 28 ranges; readings to \pm 1999 with 100% overrange; overrange indication; input overload protection; automatic polarity; and automatic zeroing.

The all-solid-state Model 2000 incorporates a single LSI circuit and high-quality components. Our clear, step-by-step manual simplifies assembly. Complete kit includes a rugged high-impact case ideal for both test-bench and field use.

BRIEF SPECIFICATIONS:

- DC volts in 5 ranges: 100 μ V to 1kV • AC volts in 5 ranges: 100 μ V to 1kV • DC current in 6 ranges: 100 nA to 2A • AC current in 6 ranges: 100 nA to 2A • Resistance: 0.1 Ω to 20M Ω in 6 ranges
- AC frequency response: 40 Hz to 50kHz • Display: 0.36" (9.1mm) 7-segment LED • Input Impedance: 10M Ω • Size: 8"W \times 6.5"D \times 3"H (203 \times 165 \times 76 mm) • Power requirement: 4.5-6.5 VDC-4 "C" cells (not included).

By Popular Demand! SPECIAL OFFER extended through April 30, 1979.

SEE YOU AT DAYTON!

Special Offer! Save \$25.00*

If you order both the frequency counter and DMM kits now, you pay only \$144.90 including shipping and handling. You save \$25.00 off the combined regular low price of \$169.90. Order both kits now. This special offer good for a limited time only.

*Special offer good in USA only.

Making performance affordable.

sabtronics


13426 Floyd Circle • Dallas, Texas 75243
Telephone 214/783-0994

Sabtronics International Inc. 13426 Floyd Circle Dallas Tx 75243		HR-4
<input type="checkbox"/> Yes, I want to take advantage of your special \$25.00-off offer.*		
Please send	Model 8100 and Model 2000 kit(s) for only \$144.90 total including shipping and handling	\$
Please send	Model 8100 Frequency Counter kit(s)	@ \$89.95 ea \$
	Shipping and handling	\$ 5.00/unit*
Please send	Model 2000 DMM kit(s)	@ \$69.95 ea \$
	Shipping and handling	\$ 5.00/unit*
	Texas residents add sales tax	\$
	Total enclosed	\$
<input type="checkbox"/> Check	<input type="checkbox"/> Money Order	<input type="checkbox"/> Charge my Master Charge
	Acc. No.	Visa Exp. Dt.
Name		
Address		
City	State	Zip
*USA only. CANADA: \$6.50. FOREIGN: \$19.00 AIRMAIL.		

PSI-AMP

"IT SPEAKS FOR ITSELF"

- MORE EFFECTIVE THAN OTHER PROCESSORS (INCLUDING RF) IN ON-THE-AIR TESTS.
- L.E.D. LEVEL METER AIDS SETTING MIKE LEVEL FOR OPTIMUM A.G.C. AND CLIPPING.
- "Under less favorable noise conditions the prefiltered clipped speech yields significantly higher intelligibility scores than does unmodified speech, when the two are presented to the listener at the same average power level."*
- 3 position high pass prefiltering control selects optimum intelligibility with low distortion (1050Hz) for adverse conditions or naturalness for more favorable conditions (750Hz or 550Hz).
- Selectable A.G.C. with 35dB dynamic range.
- Adjustable clipper, 0-20dB, increases average talk power.
- Output level adjustable from 0-125mV.
- Mike level control on front panel.
- P.T.T. line feed through.
- Heavy anodized aluminum RF tight case.
- Processor is bypassed in the "off" position.
- Slim package, 7" x 7" x 3/4", fits under, on top of, or along side any rig.
- MIKE SQUELCH TURNS OFF BACKGROUND NOISE BETWEEN PHRASES.
- Design based on research reported in the Journal of the Audio Engineering Society.*
- Up to 50% more intelligible at OdB signal-to-noise ratio than unprocessed speech.*

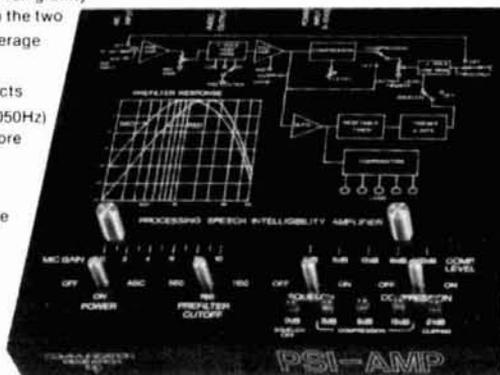

*Journal of the Audio Engineering Society, October 1978, article on speech intelligibility by Thomas and Niederjohn.

COMMUNICATION RESEARCH INC. • \$149.95 including power supply, cable and shipping
CONN. RESIDENTS ADD 7% SALES TAX
90 DAY WARRANTY
External power supply included
internal 9V battery optional.

3 GREAT PASTURE ROAD
W. REDDING, CT 06896
(203) 938-2273



NEW FROM GLB

A complete line of **QUALITY 50** thru 450 MHz **TRANSMITTER AND RECEIVER KITS**. Only two boards for a complete receiver. 4 pole crystal filter is standard. Use with our **CHANNELIZER** or your crystals. Priced from \$69.95. Matching transmitter strips. Easy construction, clean spectrum, **TWO WATTS** output, unsurpassed audio quality and built in **TONE PAD INTERFACE**. Priced from \$29.95.

SYNTHESIZER KITS from 50 to 450 MHz. Prices start at \$119.95.

Now available in **KIT FORM** — **GLB Model 200 MINI-SIZER**.

Fits any HT. Only 3.5 mA current drain. Kit price \$159.95 Wired and tested. \$239.95

Send for **FREE 16 page catalog**. We welcome Mastercharge or VISA

GLB ELECTRONICS
1952 Clinton St., Buffalo, N. Y. 14206

RESETTABLE TO EXACT FREQ.--BASE TUNED WITH LOG

ANTECK, INC.

Box 415 — Rt. 1
Hansen, Idaho 83334
208-423-4100



The model MT-1 Mobile Antenna tunes 3.5 to 30 MHz inclusive. 750 WATTS for HAM BANDS, MILITARY, MARS, MARINE, and C-B. Center Loaded for high efficiency. EXACT RESONANCE FULL OUTPUT from Finals. Base tuned with logging scale and correlation chart from logging scale to Freq. Max. length-116 inches at 3.5 MHz. Min. length-92.5 inches at 30 MHz. 3/8" X 24 Std Mt.

SEE AT YOUR LOCAL DEALER OR ORDER DIRECT \$119.95 EA.

DEALERS--(Inquiries invited)

Clegg Communications Lancaster, Pennsylvania	Conley Radio Billings, Montana
Quement Electronics San Jose, California	Radio World Oriskany, New York
Ross Distributing Preston, Idaho	C-Comm Seattle, Washington
Omar Electronics Durand, Michigan	Colville Amateur Supply Colville, Washington
Burghardt Amateur Center Watertown, So. Dakota	Cohon Amateur Supply Santa Maria, California

LESS THAN 1.5 VSWR (ENTIRE TUNING RANGE)

STAINLESS STEEL WHIP--FIBERGLASS LOADING COIL--PATENT APPLIED

NO COILS TO CHANGE--NO TUNERS REQUIRED--POSITIVE TUNING LOCK

QUARTZ CRYSTALS



"IN A HURRY"
SINCE 1970

CRYSTALS AVAILABLE FOR:

- CB — Synthesizers
- Amateur - HF, VHF, UHF
- Industrial
- Scanner
- Marine — LB & VHF
- Conversion Crystals
- Special Attention to R & D.
- Micro-processor Types.

DISCOUNTS AVAILABLE TO DEALERS & MANUFACTURERS

CALL "BONNIE" FOR PRICES & DELIVERY

VISA & MASTER CHARGE credit cards accepted.



CAL CRYSTAL LAB, INC.
1142 N. Gilbert Street
Anaheim, CA 92801
(714) 991-1580



MICROWAVE MODULES LTD.

432 Mhz Linear Transverter

UP YOUR FREQUENCY!



Put your 28Mhz Transceiver to work at 432Mhz!!

- EXTRA RANGE (434-436 Mhz) for Satellite operation.
- 10 Watts RMS output power.
- Simple Frequency Range Selection Using Toggle Switches.
- Highly Stable Regulator Controlled Crystal Oscillator Stages
- 30 dB Receiver Gain.
- Better than 3.0dB Noise Figure.
- Antenna Changeover Achieved by Low Loss Pin Diode Switch.
- 50 Mhz and 144 Mhz I.F.'s Available.

MMT432/28-S — PRICE: \$329.95 INCLUDING SHIPPING

144 Mhz Linear Transverter

Join the Fun on 2 Meter Sideband — using your 28Mhz Transceiver.

- 10 WATTS RMS OUTPUT POWER
- 30dB RECEIVER GAIN
- BETTER THAN 2.5dB NOISE FIGURE
- 50 Mhz I.F. AVAILABLE



MMT 144/28 — PRICE: \$259.95 INCLUDING SHIPPING

432 Mhz LINEAR AMPLIFIER 100 WATTS OUTPUT

ALL MODE



- 100% DUTY CYCLE RATED
- RFOVX
- 10dB MINIMUM GAIN

- FULLY PROTECTED VSWR, OVERHEATING, REVERSE POLARITY

MML432/100 — PRICE: \$449.95

INCLUDING SHIPPING

432-436 Dual Range Receiving Converter



- OSCAR, MODE J RECEPTION
- 30dB GAIN
- BETTER THAN 3.0dB NOISE FIGURE
- I.F.'s AVAILABLE: 28-30Mhz, 144-146Mhz

MMC 432/28-S — PRICE: \$95.95

INCLUDING SHIPPING

GUARANTEE

ALL MICROWAVE MODULES PRODUCTS ARE GUARANTEED FOR 1 YEAR. IN ADDITION, THEY MAY BE RETURNED WITHIN 10 DAYS FOR A FULL REFUND IF YOU ARE NOT SATISFIED FOR ANY REASON.

TEXAS RF DISTRIBUTORS IS THE EXCLUSIVE IMPORTER OF MICROWAVE MODULES PRODUCTS, AND WE SUPPLY A COAST-TO-COAST DEALER NETWORK. WRITE OR PHONE FOR DETAILS OF THESE PRODUCTS AND THE OTHER VHF AND UHF MICROWAVE MODULES PRODUCTS WHICH WE STOCK.

TEXAS RF DISTRIBUTORS, INC.

JOE - WA5HMK

CARL - W5UPR



Exclusive U.S.A. Distributors of Microwave Modules Products

4800 WEST 34TH STREET • SUITE D12A
HOUSTON, TEXAS 77092
PHONE 713/680-9797 • TELEX 791322

Need a 3rd hand?

Here it is!

PANAVERSE
ELECTRONICS VISE

Now when you need your circuit board positioned just a bit differently, it's a snap with the ELECTRONICS VISE! Tilt, turn and rotate your PC board to any position and keep it there. Movement and placement angles controlled by a single variable-pressure star knob on the base. This multi-purpose vise features a black oxide finished head reducing glare and eye fatigue. Neoprene jaws with molded grooves to firmly grip PC boards.

After you discover the convenience of ELECTRONICS VISE — you'll wonder how you ever lived without it, indeed, a 3rd hand.



\$24.50

(plus \$2.00 shipping & handling.)

Include 2 First Class Postage stamps and we'll rush you the most complete source for hard-to-find parts.

Or Call **(603) 673-7724**

**SEND FOR FREE
HARD-TO-FIND ELECTRONIC'S
PARTS CATALOG**

Whitehouse Co.

10 NEWBURY DRIVE, AMHERST, NH 03031

Regency Scanner

BRINGS
YOU THE
NEWS
WHILE ITS
HAPPENING



10 channels covering
all 5 bands. AC/DC operation.

SAVE \$40 \$89.95
LIST-\$129.95

1,000's OF CRYSTALS



- H25C Case Scanner Monitor
- 10.7 Amateur Ham
- 2 Meter, CB, Standard

1 to 9 10 to 49 50 and UP
\$3.70 \$3.00 \$2.50

CRYSTAL BANKING SERVICE
P.O. BOX 683
LYNNFIELD, MASS. 01940

ARE YOU HAVING CONTROL PROBLEMS ??

Help solve them with one
of "Creative Electronics"
Repeater Control and Timer Boards
or Tone Pad Decoder Board !



RCT 101 - REPEATER CONTROL & TIMER

- PROGRAMMABLE ANALOG TONE DECODERS
- CONTROL LOGIC
- ADJUSTABLE TIME LIMIT
- ADJUSTABLE DELAYED DROP OUT
- OPERATES ON FROM 8 - 20 VOLTS D.C.

COMPLETE KIT \$ 59.95
ASSEMBLED UNIT \$ 79.95

TPD 204 - TONE PAD DECODER

- 8 ANALOG TYPE FILTER TONE DECODERS
- FULL 4 X 4 MATRIX
- INDIVIDUAL TTL LOGIC OUTPUT FOR EACH TONE
- INDIVIDUAL TTL LOGIC OUTPUT FOR EACH DIGIT
- TTL BCD OUTPUT FOR DIGITS 0 - 9 INCLUDING STROBE
- SEVEN SEGMENT DISPLAY OF BCD OUTPUT

PRICES SUBJECT TO CHANGE

GA. RESIDENTS ADD 3% TAX SHIPPING EXTRA

COMPLETE KIT \$ 109.95
ASSEMBLED UNIT \$ 139.95



"creative electronics"

P.O. BOX 7054

MARIETTA, GEORGIA 30065

PHONE 404 971-2122 outside ga. 800 241-4547

WE ACCEPT



TEST EQUIPMENT

All equipment listed is operational and unconditionally guaranteed. Money back if not satisfied. Prices listed are FOB Monroe.

Boonton 190A Q mtr 20-260MHz	
Q 5 1200	395
GR 1001A Stand sig gen 5kHz	
-50MHz calib atfn	255
HP170A (USM140) 30mHz scope with	
reg horiz, dual trace vert plugs	475
Tek565 Dual beam 10mHz scope	
less plug-ins (3 series)	625
URM25 Stand Sig Gen 10kHz-50MHz	
calib atfn	225
Weinschel 70 Prec RF atfn DC	
1GHz 0.60db, 1db steps 4w	395

Lists outdated. Write specifying test equipment needs. Quick response assured.

GRAY Electronics

P.O. Box 941, Monroe, Mich. 48161
Specializing in used test equipment.

"RUBBER DUCKIES"

FROM

g & c Communications

A MUST FOR 2-METER HAND HELDS

Model	Description	Price
GC-1	5/16" Knurled Stud. Fits Icom, Motorola and many others	\$ 6.50
GC-2	BNC Connector	\$ 9.98
GC-3	TNC — Connector for Wilson 1405	\$13.98
GC-4	PL-259 Connector	\$ 6.50
GC-5	Type F Connector fits Wilson 1402 and Tempo	\$ 9.50

Equipment made in USA by OEM MFRS

Send to:
G & C COMMUNICATIONS
730 Cottonwood, Lincoln, NE 68510
Add \$1.00 for handling and shipping.
(Dealer and OEM RFO's Welcome)

SUBSCRIBE AND SAVE!



Get every exciting issue, every month, and save dollars, too.

News! New ideas! Excitement! It's happening every day in electronics, the most exciting, fastest-growing field in the world. So make sure you get every idea-packed issue of the world's best electronics magazine — Radio - Electronics. You get projects to build, test reports on new equipment, servicing tips, com-

puter technology, and more. You find all the news, all the features, and you find them first in Radio-Electronics. Plus, you get specialized columns in every issue: *Computer Corner*, *Hi-Fi Lab Test Reports* by Len Feldman, *Jack Darr's Service Clinic*, *Hobby Corner*, and the *State-of-Solid-State*, all written by experts, the outstanding authorities in the field.

Don't miss a single issue. Have Radio-Electronics delivered to your door, every month. Subscribe to Radio-Electronics today, and be assured of getting your

copy of each issue before it runs out on the newsstands. Save money too. When you choose one of the subscription offers listed on the coupon below you can save up to \$14.50 off the newsstand price of Radio-Electronics. You save time, you save money, and you get the most interesting, most exciting and authoritative reporting of electronics news you'll find in any magazine. Pick the plan you like best, and use the coupon right now to make sure you get all of the best—every issue of Radio-Electronics—every month.

Mail to: Radio-Electronics SUBSCRIPTION DEPT., P.O. BOX 2520, BOULDER, COLO. 80322

Save almost 1/2 off the newsstand.
Indicate the offer you prefer:

1 Year—12 issues ONLY \$7.77

(Save \$7.23 on newsstand or \$2.21 off basic subscription price.)

2 Years—24 issues ONLY \$15.50

(Save \$14.50 on newsstand or \$3.50 off basic subscription price.)

(please print)


Name		
Address		
City	State	Zip Code

4HRA

- Payment enclosed Bill me
 Check here if this is a new subscription.
 Check here if you are extending or renewing your subscription.

Extra Shipping: Canada \$3.00 per year, all other countries \$5.00 per year.

flea market

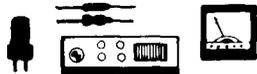

RATES Non-commercial ads 10¢ per word; commercial ads 60¢ per word both payable in advance. No cash discounts or agency commissions allowed.

HAMFESTS Sponsored by non-profit organizations receive one free Flea Market ad (subject to our editing). Repeat insertions of hamfest ads pay the non-commercial rate.

COPY No special layout or arrangements available. Material should be typewritten or clearly printed (not all capitals) and must include full name and address. We reserve the right to reject unsuitable copy. **Ham Radio** cannot check each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue.

DEADLINE 15th of second preceding month.

SEND MATERIAL TO: Flea Market, Ham Radio, Greenville, N.H. 03048.

TRI-EX W-67 TOWER, motorized extension from 22 ft. (nested) to 67 feet. Also Drake remote antenna selector, Ham III rotator and Wilson 10/15 meter beam. Sell only complete package for \$1995.00 or write and ask for details on complete QTH. Write: F. Moller, Cathedral Rd. Rindge, N. H. 03461.

VERY in-ter-est-ing! Next 3 issues \$1. "The Ham Trader", Sycamore, IL 60178.

QUALITY NEW COMPONENTS: 1/4 and 1/2 watt carbon film resistors; electrolytic, mylar, tantalum, disc capacitors; trim pots; miscellaneous other items including chassis and enclosures. Enclose 15¢ stamp for catalogue. Midnight Engineering Group, P.O. Box 349, Galesburg, IL 61401.

STAR-TRONICS monthly picture flyer is full of parts and pieces for the builder. Cheap. Quality. U.S. only. Star-Tronics, Box 683, McMinnville, OR 97128.

WANTED: Used Hy-Quad, also Ham II. All response answered. Frank 12552 West Mississippi Ave., Lakewood, CO 80228.

Foreign Subscription Agents for Ham Radio Magazine

Ham Radio Austria
F. Bassl
Hauptplatz 5
A-2700 Wiener Neustadt
Austria

Ham Radio Belgium
Stereohouse
Brusselssesteenweg 416
B-9218 Gent
Belgium

Ham Radio Canada
Box 114, Goderich
Ontario, Canada N7A 3Y5

Ham Radio Europe
Box 444
S-19404 Upplands Vasby
Sweden

Ham Radio France
Christiane Michel
F-89117 Paray
France

Ham Radio Germany
Karin Ueber
Postfach 2454
D-7850 Loerrach
West Germany

Ham Radio Holland
MRL Electronics
Postbus 88
NL-2204 Delft
Holland

Ham Radio Italy
STE. Via Maniagio 15
I-20134 Milano
Italy

Ham Radio Switzerland
Karin Ueber
Postfach 2454
D-7850 Loerrach
West Germany

Ham Radio UK
P.O. Box 63, Harrow
Middlesex HA3 6HS
England

Holland Radio
143 Greenway
Greenside, Johannesburg
Republic of South Africa

6 METER KW STATION. Drake TR6, Excellent, Raytrack KW Amp Excellent, 26-60 Universal Foldover Tower 130' RG 17U Cable. Mast rotor and cable. \$2000.00 Firm. (316) 686-6288. 9229 Lincoln Ct., Wichita, KS 67207.

MOBILE IGNITION SHIELDING provides more range with no noise. Available most engines. Many other suppression accessories. Literature, Estes Engineering, 930 Marine Dr., Port Angeles, WA 98362.

2M REPEATER — New Spectrum Communications SCR-1000/PL. Purchased as back-up station. \$1,000. Also, Cushcraft 8-pole antenna system, 12 dB off-set — 9 dB Omni add \$125. Anytime. WAZCEB. Dennis. (716) 648-4450.

RECONDITIONED TEST EQUIPMENT for sale. Catalog \$3.50. Walter, 2697 Nickel, San Pablo, Ca. 94806.

ADDS 980 CRT — less than 50 hrs run time, all manuals — graphics — editing, etc. Also KIM I (\$75) and HT220 synthesizer kit (\$50). Make offer or will consider trades. Dave WA4IWA, 944 Hazel Court, Lilburn, GA 30247. (404) 972-6459 (after 6 PM).

SST ANTENNA TUNERS — your best buy. SST Electronics, Box 1, Lawndale, CA 90260.

ROHN TOWERS — Buy wholesale direct from distributor. 20G sections \$28.82 each, 25G sections \$37.62 each, 45G sections \$57.20 each — 100 foot tower kit complete \$646.02 — 40 foot free standing BX tower \$179.45 — 48 foot 25G foldover, freight paid \$565.00 — Hill Radio, 2503 G.E. Road, Bloomington, IL 61701, (309) 663-2141.

QSL CARDS 500/\$10. 400 Illustrations, sample. Bowman Printing, Dept. HR, 743 Harvard, St. Louis, MO 63130.

WWVB RECEIVER. The ElemeK Model LXX receiver receives the 60 kHz WWVB signal and provides the following outputs: 60 kHz and 100 kHz, phase locked to WWVB carrier, and the demodulated WWVB time code. Send for brochure describing the receiver to ElemeK, Inc., 6500 Joy Rd., East Syracuse, N.Y. 13057.

ELECTRONIC BARGAINS, CLOSEOUTS, SURPLUS! Parts, equipment, stereo, industrial, educational. Amazing values! Fascinating items unavailable in stores or catalogs anywhere. Unusual FREE catalog. ETCO-012, Box 762, Plattsburgh, N.Y. 12901. SURPLUS WANTED.

WANTED: Hilltop property near Pollock Pines, California. WA6COA, 4 Ajax Place, Berkeley, CA 94708.

FOR SALE: One G.E. Master Pro in outdoor cabinet with duplexer. B. M. Ellison, III, 222 Bramblewood, Summerville, SC 29483.

REPLACE RUSTED ANTENNA bolts with stainless steel. Small quantities, free catalog. Elwick, Dept. 324, 230 Woods Lane, Somerdale, N.J. 08083

EZ deals are the best! Try me and see for Yaesu, Drake, KLM, Swan, Cushcraft, DenTron, VHF Eng., ICOM, CDE, Hustler, Wilson and more. Call, see or write W0EZ. Bob Smith Electronics, RFD 3, Hwy 169 & 7, Fort Dodge, IA 50501. (515) 576-3886.

TEFLON CIRCUIT BOARD, double-sided 1 oz. copper. Approximately 3.5" x 5". .01 (thick) \$5.00 ea., .032 (thick) \$6.00 ea. postage paid. Master Charge, VISA, or check. S. S. Enterprises, 4335 e. 5th Anchorage, AK 99504. (907) 333-7367.

RTTY PARTS AND MACHINES: Model 28RO's, KSR's, ASR's, typing reperfs, TD's. Gears — all machines. Underdome reperf for 28ASR, single-speed, \$285.00 PP. Auto CR-LF non-overline kit for M28, \$12.75 PP. M28 stand-alone TD, single-speed, \$170.00 PP. Model 15 covers, gears, etc. 14TD, \$50.00 PP. M14 keyboard typing reperf, \$95.00 PP. Much more. Send SASE for complete list machines and parts. Lawrence R. Pflieger, K9WJB, 1715 E. McPherson St., Kirksville, MO 63501.


DRAKE 2B RECEIVER and matching speaker. Good condition — \$125.00. Drake TV 1000 low pass filter. \$10.00. Heath Kit Ione patch \$25.00. SBE 3 transceiver mint condition \$150.00. Leon Fry WB6JTR, 239 61st Street, Newport Beach, CA 96223. (714) 642-3573.

RM-300 RTTY Modem, the complete TU and AFSK generator on one board. This modem featured Sept '78 Ham Radio. Complete documentation \$2.00. RM-300 Modem or RP-400 Power Supply board just \$21.25. Complete RM-300 or RP-400 kit less PROM \$71.25. PROM programmed with your call \$7.00. WA6DNR Eclipse Communications, 5 Westwood Drive, San Rafael, CA 94901.


FERRITE BEADS: w/specification and application sheet - 12/\$1.00. Assorted PC pots - 10/\$1.00. Miniature mica trimmers, 3-4 pF. - 5/\$1.00. Postpaid. Includes latest catalog. Stamp for catalog alone. CPO Surplus, Box 189, Braintree, MA 02184.

WANTED: Motorola KXN 1024 and KXN 1052 channel elements. WA6COA, 4 Ajax Place, Berkeley, CA 94708.

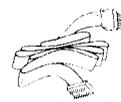14 Pin DIP extender cable. 36" long with MOLDED plug each end. Highest quality \$2.00 ea.



6 for \$10.00

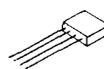

Molded bridge rectifier. 100 volt PIV @ 2 amps. 45¢ ea. or 5 for \$2.00 ppd.

Photocell — first quality plastic encapsulated. Dark resistance 100 megohm; Lite resistance 150 ohms. 20¢ ea. 6 for \$1.00 ppd.



Single RCA type jack. High quality factory new. 15¢ ea. 8 for \$1.00

7 segment display FND type. Cosmetic rejects. Common anode .5 high. Real nice. 75¢ each



Jumbo LEDs. .2 inch diameter. Color-Red. Prime factory units. Not seconds or retests. 20¢ ea. ppd.



4PDT Relay, 12 VDC coil, Potter Brumfield, 5 amp contacts, factory new of course, a beauty. Also available with 24 VDC coil. \$1.90 ea. ppd.



Vertical Mount Trimmer Pots — All highest quality. No junk. 100 - 1000 - 2000 - 5000 - 10K - 20K - 25K - 50K - 250K - 500K Ohms. All have thumbscrew adjust. Your choice 5 for \$1.00 ppd.



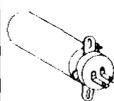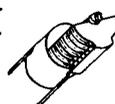Highest Quality E. F. Johnson Trimmer Caps. Hard-to-find P.C. board mount. .5-11 mmfd. No junk. 90¢ each; 10 for \$7.50 ppd.



SUPER-BUY — 5000 mfd. @ 40 volt electrolytic cap. factory new and complete w/all hardware. \$1.35 ea. ppd.

Just arrived — thousands of ICs. Removed from sockets on new P.C. boards. All marked with standard numbers and in the 7400 series. Examples of nos. are 7486-7495-7496 etc. Chance of a lifetime. Sorry no choice of numbers. We mixed them up. 50 for \$7.50 ppd. 100 for \$12.50 ppd.

Transformer: 115V AC Primary, Secondary 17-0-17V @ 7 Amps. We tested and find good for 10 Amps intermittent duty. Ideal for 2M rigs! \$8.00 ea. ppd.

ALL ITEMS PPD USA

SEND STAMP FOR LIST OF BARGAINS
PA RESIDENTS ADD 6% SALES TAX
FONE 412-863-7006



Full Electronics

12690 ROUTE 30
NORTH HUNTINGDON, PA. 15642

RADIO AMATEUR CALLBOOKS



Respected worldwide as
the only complete authority
for radio amateur
QSL and QTH information

The U. S. Callbook has nearly 350,000 W & K listings. It lists calls, license classes, names and addresses plus the many valuable back-up charts and references you come to expect from the Callbook.

Specialize in DX? Then you're looking for the Foreign Callbook with almost 285,000 calls, names and addresses of amateurs outside of the USA.

U.S. Callbook \$15.95

Foreign Callbook \$14.95

(Plus Shipping)

Order from your favorite electronics dealer or direct from the publisher. All direct orders add \$1.75 for shipping. Illinois residents add 5% Sales Tax.

RADIO AMATEUR
callbook INC
Dept. E 925 Sherwood Drive
Lake Bluff, Ill. 60044

MOBILE HF ANTENNA, 3.5-30 MHz inclusive, 750 watts PEP, center loaded coil, tuned from the base, eliminating coil changing or removing from mount. Less than 1.5 to 1 VSWR on all ham bands. \$119.95 each — contact your local dealer or order from Anteck, Inc., Box 543, Jerome, Idaho 83338. (208) 324-3400. Master Charge and VISA cards accepted. Dealer inquiries invited.

TELETYPE EQUIPMENT for beginners and experienced operators. RTTY machines, parts, supplies. Beginner's special: Model 15 Printer and demodulator \$139.00. Dozen black ribbons \$6.50; case 40 rolls 11/16 perf. tape \$17.50 FOB. Allantic Surplus Sales, 3730 Nautilus Ave., Brooklyn, N. Y. 11224. Tel: (212) 372-0349.

FOR SALE OR TRADE — like new in original cartons. 1 HAL-RVD-1005 visual display unit; 1 HAL-ST-6 RTTY Terminal Unit (with AK-1 AFSK-OSC); 1 HAL-RKB-2010 Key Board with 128 key extended memory key strokes Dual Mode for CW; 1 MD-12 Modified Page Printer — Automatic Carriage Return; 1 Oscilloscope for Tuning; 1 Complete set of technical manuals. All for good video tape recorder outfit — Zeb Deville K5ISY — Box 4007, Alexandria, LA 71301. (318) 640-0234.

RTTY — Bandpass active filter 2125/2295 Hz. Kit \$11.95, W/T \$16.95 ppd. SASE for info. Nat Stinnette Electronics, Tavares, FL 32778.

RTTY AFSK Modulator PC board. See Feb. 79 Ham Radio. Drilled \$5.00. F.E. Hinkle, 12412 Mossy Bark, Austin, TX 78750.

FREQUENCY ALLOCATION CHART. See how the entire radio spectrum is used. 2 kHz to 200 GHz. Send \$3.00. Collins Chart Co., Box 935, Coronado, CA 92118.

REPEATERS — Factory Built VHF Engineering. 4 uhf, 1 with P.L. Two in unopened boxes. 1 220 MHz, 2K Takes all. WA6COA, 4 Ajax, Berkeley, CA 94708.

THE MEASUREMENT SHOP has used/reconditioned test equipment at sensible prices; catalog, 2 West 22nd St., Baltimore, MD 21218.

WANTED — Instructor Ham Radio. N.Y.S. Co-ed Children's Sleep-Away Camp. Write: Camp Kinder Ring, 45 East 33rd Street, New York, N.Y. 10016.

HAMS requesting our famous "SHOOT THE BULL" QSL Card, send yours & SASE K4NBN, Box 23413, Jacksonville, FL 32217.

MANUALS for most ham gear 1937/1970. Send 25¢ for "Manual Catalog." Hi, Inc., Box H864, Council Bluffs, Iowa 51502.

AUTHORIZED DISTRIBUTOR F9FT Antennas, Microwave Modules, RIW Products' new tandem reflector, 19 element, 432 MHz Yagi — Radio Clinic — N2MB (formerly WA2BIT) 212-327-4952.

WANTED: 2 sets, TG5A Army field telegraph, Paul Amber, 3807 Crooks Rd., Royal Oak, MI 48073.

CLUB CALL PINS 3 lines 1 1/4 x 3 3/4 \$1.55 each. Call, first name and club. Colors — black, blue or red with white letters. (Catalog) Arnold Linzner, 2041 Linden Street, Ridgewood, N. Y. 11227.

ICOM 211 Mint Condition. \$700. W4DGA (703) 273-8278.

SELL — Boonton 202D Signal Generator, Reconditioned, \$50 plus transp. W6LGO, 34 Laurel Ave., Petaluma, CA 94952.

PORTA PAK — Make your FM mobile a self-contained portable. Models in stock for most popular makes. 4.5 amp hr model \$67.50. 9 amp hr \$88.00. Charger included, shipping extra. P.O. Box 67, Somers, WI 53171.

WANTED — Radio transcription discs. Any size or speed. Larry, W7FIZ. Box 724, Redmond, Washington 98052.

TECH MANUALS for Govt. surplus gear — \$6.50 each: SP-600JX, URM-25D, OS-8A/U, TS-173/UR. Thousands more available. Send 50¢ (coin) for 22-page list. W3IHD, 7218 Roanne Drive, Washington, DC 20021.

TEST EQUIPMENT CATALOG listing used Tektronix, HP and GR equipment at bargain prices. PTI, Box 8699, White Bear Lake, MN 55110. Price \$1.00 refundable with first order.

STOP LOOKING for a good deal on amateur radio equipment — you've found it here — at your amateur radio headquarters in the heart of the Midwest. We may not have a toll free number but we'll save you more in the long run! We are factory-authorized dealers for Kenwood, Drake, Yaesu, Collins, Wilson, Ten-Tec, Atlas, ICOM, DenTron, MFJ, Tempo, Regency, Hy-Gain, Mosley, Alpha, CushCraft, Swan, and many more. Write or call us today for low quote and try our personal and friendly Hoosier service. HOOSIER ELECTRONICS, P.O. Box 2001, Terre Haute, Indiana 47802. (812) 238-1456.

CURTIS LSI's help you



speaking MORSE

- ★ 8044; Keyer-On-A-Chip* (Replaces 8043) . \$14.95
- ★ Apr '75 HR, Feb '76 OST, Radio Hdbk '75, Apr Hdbk '77-78
- ★ 8044-3; IC, PCB, Socket, Manual 24.95
- ★ 8044-4; Semi-Kit 54.95
- ★ 8045; Morse Keyboard-On-A-Chip IC . . . 59.95
- ★ 8045-1; IC, PCB, FIFO, Sockets, Manual . . 89.95
- ★ 8045-2; Semi-Kit 159.95
- ★ 8046; Instructokeyer-On-A-Chip IC . . . 49.95
- ★ 8046-1; Semi-Kit 79.95
- ★ 8047; Message Memory-On-A-Chip IC . . . 39.95
- ★ 8047-1; IC, PCB, RAM, Sockets, Manual . . 69.95

(add \$1.75 on above for postage and handling)

EK-430; CMOS Keyer* (Feb '76 OST) 124.95

IK-40A; Instructokeyer* (Mar '76 OST) 224.95

*now with dash memory as standard

System 4000 Ham Computer (see Jan '78 OST) (write)

Curtis Electro Devices, Inc.
Dept. H (415) 964-3136
Box 4090, Mountain View, CA 94040



You can build a better organ than you can buy!

A magnificent Schober Electronic Organ

What a marvelous way to put your special talents to work! With our Schober Electronic Organ Kits and your skill, you can build yourself some very special satisfaction, and a lifetime of great music!

Schober Organs are literally far superior to comparably-priced "ready-made" units. You could actually pay twice as much and get no better organ — and miss the fun of assembling it yourself. A PC board at a time, component by component, you'll assemble your own "king of instruments." And when you're done, you'll wish there was more to do. And there is! For then, Schober will help you learn to play, even if you've never played a note before!

Schober Organ Kits range from \$650 to \$2850, and you can purchase in sections to spread costs out... or have two-year time payments.

Just send the coupon for the fascinating Schober color catalog (or enclose \$1 for a record that lets you hear as well as see Schober quality.)


The Schober Organ Corp., Dept. HA-2
43 West 61st Street, New York, N.Y. 10023

- Please send me Schober Organ Catalog
- Enclosed please find \$1.00 for 12-inch L.P. record of Schober Organ music

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

CALL TOLL FREE

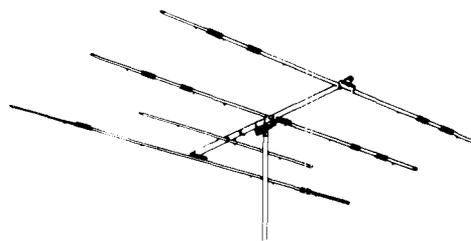1-800-228-4097
Communications Center
 443 N 48th Street
 Lincoln, Nebraska 68504
 In Nebraska Call (402)466-8402



Antenna Sale!

HY-GAIN

		Regular	Special			Regular	Special
TH6DXX	Super Thunderbird	\$299.95	\$239.95	18HT	Hy-Tower 80-10M vertical	299.95	239.95
TH3MK3	3 el. 10-15-20M beam	229.95	179.95	18AVT/WB	80-10M Trap vertical	99.95	79.95
TH3JR	3 el. 10-15-20M beam	149.95	129.95	14AVQ/WB	40-10M Trap vertical	69.95	57.00
Hy-Quad	2 el. 10-15-20M Quad	229.95	179.95	12AVQ	20-10M Trap Vertical	39.95	32.95
205BA	5 el. "Long John" 20M beam	289.95	229.95	14RMQ	Roof Mounting kit (verticals)	33.95	29.95
155BA	5 el. "Long John" 15M beam	169.95	139.95	5BDQ	80-10M Trap doublet	89.95	69.95
105BA	5 el. "Long John" 10M beam	119.95	99.95	2BDQ	80-40M Trap doublet	49.95	39.95
204BA	4 el. 20M beam	219.95	179.95	66B	6 el. 6M beam	119.95	99.95
204MK5	5 el. conversion kit	99.95	79.95	203	3 el. 2M beam	15.95	
153BA	3 el. 15M beam	79.95	69.95	205	5 el. 2M beam	17.95	
103BA	3 el. 10M beam	54.95	44.95	208	8 el. 2M beam	25.95	
402BA	2 el. 40M beam	209.95	169.95	214	14 el. 2M beam	31.95	
BN-86	Balun for beam antennas	15.95	15.95	LA-1	Deluxe lightning arrester	59.95	49.95
TH2MK3	2 el. 10-15-20M beam	149.95	119.95				

MOSLEY

		Regular	Special
Classic 33	3 el. 10, 15, 20 Mtr. beam	304.75	209.95
Classic 36	6 el. 10, 15, 20 Mtr. beam	392.75	269.95
TA-33	3 el. 10, 15, 20 Mtr. beam	264.00	189.95
TA-36	6 el. 10, 15, 20 Mtr. beam	392.75	269.95
TA-33 Jr.	3 el. 10, 15, 20 Mtr. beam	197.00	149.95
TA-40KR	40 Mtr. Add On	119.95	89.95

CUSHCRAFT

		Regular	Special
ATB-34	4 ele. 10, 15, 20 Mtr. beam	289.95	219.95
ATV-4	10, 15, 20, 40 Mtr. Vertical	89.95	69.95
ATV-5	10, 15, 20, 40, 80 Mtr. Vertical	109.95	89.95
ARX-2	2 Mtr. Ringo Ranger	39.95	32.95
AR-6	6 Mtr. Ringo	36.95	32.95
ARX-220	220 Mhz. Ringo Ranger	39.95	32.95
ARX-450	435 Mhz. Ringo Ranger	39.95	32.95
A144-11	11 ele. 144-146 Mhz. beam	36.95	30.95
A147-11	11 ele. 146-148 Mhz. beam	36.95	30.95
A147-22	22 ele. Power Pack	109.95	89.95
A144-10T	2 Mtr. "Twist" 10 ele.	42.95	34.95
A144-20T	2 Mtr. "Twist" 20 ele.	62.95	52.95
A147-20T	2 Mtr. beam	62.95	52.95
A430-11	432 Mhz. 11 ele. beam	34.95	29.95
A432-20T	430-436 Mhz. Beam	59.95	49.95

HUSTLER

3-TBA	3 ele; 10, 15, 20 Mtr. beam	259.95	189.95
4-BTV	10-40 Mtr. Vertical	99.95	79.95
5-BTV	10-80 Mtr. Vertical	134.95	99.95
RM-75	75 Meter Resonator	16.95	14.50
RM-75S	75 Meter Super Resonator	31.95	27.50
G6-144B	2 Mtr. Base Colinear	79.95	59.95
G7-144	2 Mtr. Base Colinear	119.95	89.95

WILSON

System One	5 ele. 10, 15, 20, Mtr. Beam	274.95	229.95
System Two	4 ele. 10, 15, 20 Mtr. Beam	219.95	179.95
System Three	3 ele. 10, 15, 20 Mtr. Beam	179.95	149.95
WV-1	10-40 Mtr. Vertical	79.95	69.95

ROTORS

Ham III \$125.00 T2X Tailtwister \$199.95 Alliance HD 73 \$109.95

Call for prices on rotor cable, Coax, Towers, and Accessories. All prices do not include shipping.

**We carry all major brands of ham radios
 AT DISCOUNT PRICES**

Yaesu — Kenwood — Drake — ICOM — Dentron —
 Ten-Tec — Swan — Tempo — Midland — E.T.O. — Wilson



18HT



CONNECTORS		2N5589 CASE HT-72 \$2.95	
BNC M/UHF-F UG-255U \$3.00		2N5590 CASE TO-117 \$4.95	
BNC F/UHF-M UG-273U \$2.50		LED JUMBOS	
BNC F/BNC-F UG-914U \$2.00		10 FOR \$1.00 100 FOR \$7.95	
UHF F/UHF-F PL-258 \$1.50		USED FANS	
UHF F/BNC-M UG-349U \$3.75		100 CFM 115VAC 4.5" X 1.5" GUARANTEED \$6.95	
'N' M/UHF-F UG-146U \$4.75		NYLON CABLE TIES	
'N' F/UHF-M UG-83BU \$4.75		4 INCH 100EA \$1.50 6 INCH 100EA \$2.50	
RGB Adapter UG-175 \$.25		TOGGLE SWITCH	
BNC M-CABLE UG-88 \$1.35		PC MOUNT OR PANEL MINI SP DT SWITCH \$1.00 10/\$8.00	
BNC F-PANEL UG-1094 \$1.00		25¢	
"N" M CABLE UG-21B \$2.95		2200UF 16VDC	
"N" F PANEL UG-58 \$2.25		1N4007 10¢	
SO-239 65¢ PL-259 65¢ 10/\$6.00 MIX & MATCH		5V. DIP RELAY	
Computer Grade capacitors		Touch-Tone Housing. BLACK only...\$3.25	
10,000uf 50v \$2.95 23,200uf 50v 3.50 100,000uf 10v 1.75		50 ohm COAX	
50 ohm COAX		25A 200 PIV \$1.75	
RG 174 U 50 FT. \$2.75		coax relay	
12 VDC SP DT 100 WATTS RF. .8GHZ. 2 RCA CONNECTORS, 1 50239, PLUS SP ST, 20A CONTACT. ALL IN AN EN- CLOSED HOUSING. LIST \$49.95 OURS \$6.95		1 OHM 5 WATT RESISTORS	
NICAD PACK 'NEW'		5 FOR \$1.00	
10 'C' CELLS. RATED AT 12VDC. 1.2 AH. A1 10 HR. RATE. \$14.95		50 OHM 200 WATT	
NICAD		\$2.50 EA.	
NICAD		HIGH VOLTAGE SUPPLY	
NICAD		20K V. @ 30 WATTS. \$9.95	
NICAD		MJ3000 \$2.25	
POWER SUPPLY MODULE		RATED AT 12V @ 2.5A. CAN BE MODIFIED BY CHANGING THE ZENER. PARTS: 4-3A DIODES, 1-2.5A FUSE, 1-2200MF @ 35V CAP. 1-12V ZENER, 1-PASS TRANS. WITH HEAT SINK. \$4.95	
M P J A		MARLIN P JONES & ASSOC.	
M P J A		PO BOX 9023	
M P J A		RIVIERA BEACH, FLORIDA	
M P J A		33404	
M P J A		(305) 848-8236	
M P J A		*Fla. residents add 4% sales tax.	
M P J A		*MC & VISA accepted, please include expiration date and signature as on card.	
M P J A		*Add \$1.00 for order under \$10.00.	
M P J A		*Canada & Foreign orders please add sufficient postage.	
M P J A		**USA orders please add 5% postage.	

BUY-SELL-TRADE: Send \$1.00 for catalog. Give name, address and call letters. Complete stock of major brands new and reconditioned amateur radio equipment. Call for best deals. We buy Collins, Drake, Swan, etc. Associated Radio, 8012 Conser, Overland Park, KS 66204 (913) 381-5900.

DESK TOP CONSOLES, ultimate operating convenience. Free brochure. Thompson Electronics, P.O. Box 363, Westfield, IN 46074.

Coming Events

ILLINOIS: 13th Annual Rock River Radio Club hamfest, Sunday, April 22, Lee County 4-H Center, South of Dixon. Advance, \$1.50; Gate, \$2.00. Indoor facilities, camping area, free coffee & donuts 7:30 to 8:30 AM. Food available, prizes. Talk-in 146.52 simplex or WR9ADG Repeater 146.37-146.97. Advance tickets: RRRR Hamfest, Chuck Randall, W9LDU, 1414 Ann Ave., Dixon, IL 61021.

NEW YORK STATE QSO party, sponsored by the University of Buffalo Amateur Radio Club, WA2NPQ, from 1700Z May 6 to 0500Z May 7 and 1200-2359Z May 7. Stations may be contacted once on phone and once on CW on each band. NY stations may work each other. Mobile/portables changing counties may be reworked. Exchange consists of report, serial number starting with 001, and QTH (counties for NY, state/province for others). Suggested frequencies: CW, 1810 3560 7060 1460 2160 28060; Phone, 3900 7275 14285 21375 28550; Novice, 3725 7125 21125 28125. Score one point per QSO times the number of multipliers: states, provinces, countries and NY counties for NY stations; and NY counties for others (maximum of 62). This is the first time NY stations may include counties in the multiplier total. Number the first contact for each new multiplier. A check sheet is required for stations making more than 100 contacts. Awards. Logs must be received by June 16 to qualify and entrants desiring results please send #10 SASE. Please also include your name, address and county (if NY). Send all entries to Michael Bergman, WD2AJS, 45 Swartson Ct., Albany, NY 12209.

RADIO EXPO '79 September 15th and 16th, 1979, Lake County Fair Grounds, Routes 120 and 45, Grays Lake, Illinois. Manufacturers' displays, flea market, seminars, ladies programs. Advance tickets \$2.00. Write EXPO, P.O. Box 305, Maywood, IL 60153. Exhibitors inquiries: EXPO Hotline (312) 345-2525.

FLORIDA: The Daytona Beach Amateur Radio Association's First Hamfest, May 12 and 13, Holiday Inn Surfside, Daytona Beach. Advance registration: \$3.00 per family, \$3.50 at door. Indoor, air-conditioned facilities. "Drive-on" ocean beach, nearby Bellair Shopping Plaza. For info: David Rusler, WA4ZTT, 1725 Hope Drive, Ormond Beach, FL 32074, (904) 672-9536.

WASHINGTON: Pacific Northwest Hamfest, July 14 & 15, HAM Inc., Box 78442, Seattle, WA 98178.

NEW YORK: MARAC — ICHN convention, May 4, 5, 6, 1979 in Albany, New York, and hosted by Russ Sawyer, W2UJ; Bruce Jacobs, K2QK; Cliff Miller, N2FN and Jerome Walsh, WA2LSU. The purpose of the convention is to meet club members face-to-face and to raise funds for donation to a national charity. For information, write: Jerry Walsh, WA2LSU, R.F.D. #1, P.O. Box 197B, Hudson, New York 12534.

SHIP ISLAND! The Magnolia DX Group with the support of the Mississippi Coas A.R.A. plans to operate WN5IJZ from Ship Island during the 1979 CQWW-WPX Contest. This is the first ever operation from Ship Island, 12 miles south of Gulfport, Mississippi in the Gulf of Mexico, and the home of historic Fort Massachusetts. Operation will be multi-single on 80 through 10 meters. Commemorative QSL to all stations worked. Manager: N5FG/WB5HVY, Floyd Gerald, 4706 Washington Avenue, Gulfport, Mississippi 39501. S.A.S.E. please!

ROCHESTER Hamfest & NY State ARRL Convention, May 25-27. Add your name to mailing list. Send QSL to Rochester Hamfest, Box 1388, Rochester, NY 14603. Phone (716) 424-1100.

INDIANA: Hamfest! Indiana's friendliest and largest hamfest. Wabash County Amateur Radio Club's 11th annual hamfest will be held Sunday, May 13, 1979, rain or shine, at the Wabash County 4-H Fairgrounds in Wabash. Large flea market (no set-up charge), technical forums, bingo, free overnight camping, plenty of free parking, good food at reasonable prices. Only one ticket to buy. Donation is \$2.50 for advance tickets — \$3.00 at the gate. Children under 12 years old free. For more information or advance tickets, write: Dave Nagel, WD9BDZ, 555 Valley Brook Ln., Wabash, IN 46992, S.A.S.E. Required.

FAST SCAN ATV

ALL YOU NEED IN ONE BOX



Show the shack, home movies, computer games, etc. Connect to the ant. terminals of any TV set, add a good 450 antenna, a camera, and you are there...

- 10 Watts peak RF output. Specify 434.0 or 439.25 MHz
- Subcarrier sound with plenty of mic gain for distance pick-up
- 8 MHz bandwidth, high resolution necessary for computer alphanumeric and color.
- Tuneable converter covers 420 to 450. (Covers CH 2, 3)
- Contains AC to 12VDC regulated 3 AMP power supply.
- Only \$399.00 direct mail. Check, Money Order, VISA. Send S.A.S.E. for catalog of ATV Modules and PC Boards.



HITACHI HV-62U TV CAMERA \$239 ppd.
• Better than 500 line resolution. 7 watts on 117VAC.
• Small 4x25/8x8 inches. Can run on 12vdc @ 230ma.
• 10,000:1 automatic light compensation. Lens included.
Send SASE for catalog of ATV and UHF products VISA or MC orders call (213) 447-4565.

P.C. ELECTRONICS

Maryann WB6YSS 2522 PAXSON Tom W6ORG
ARCADIA, CA 91006



July 28 thru August 10, 1979

Have trouble finding time to study for Upgrading?

Do it on your vacation at the
OAK HILL ACADEMY
AMATEUR RADIO SESSION

20 years of successful teaching

Two weeks of intensive code and theory starting at your level.

Classes from Novice thru Amateur Extra

- Expert instructors
- Friendly surroundings
- Excellent Accommodations

C. L. PETERS, K4DNJ, Director
Oak Hill Academy Amateur Radio Session
Mouth of Wilson, Virginia 24363

Name _____ Call _____

Address _____

City/State/Zip _____

Transistor Checker



— Completely Assembled —
— Battery Operated —

The ASI Transistor Checker is capable of checking a wide range of transistor types, either "in circuit" or out of circuit. To operate, simply plug the transistor to be checked into the front panel socket, or connect it with the alligator clip test leads provided. The unit safely and automatically identifies low, medium and high-power PNP and NPN transistors. Size: 3 1/2" x 6 1/2" x 2". "C" cell battery not included.

Trans-Check \$29.95 ea.

Custom Cables & Jumpers



DB 25 Series Cables			
Part No.	Cable Length	Connectors	Price
DB25P-4-P	4 ft.	2-DP25P	\$15.95 ea.
DB25P-4-S	4 ft.	1-DP25P/1-25S	\$16.95 ea.
DB25S-4-S	4 ft.	2-DP25S	\$17.95 ea.

Dip Jumpers			
Part No.	Length	Pin Configuration	Price
DJ14-1	1 ft.	1-14 Pin	\$1.59 ea.
DJ16-1	1 ft.	1-16 Pin	1.79 ea.
DJ24-1	1 ft.	1-24 Pin	2.79 ea.
DJ14-1-14	1 ft.	2-14 Pin	2.79 ea.
DJ16-1-16	1 ft.	2-16 Pin	3.19 ea.
DJ24-1-24	1 ft.	2-24 Pin	4.95 ea.

For Custom Cables & Jumpers, See JAMECO 1979 Catalog for Pricing

CONNECTORS

25 Pin-D Subminiature

DB25P (as pictured)	PLUG (Meets RS232)	\$2.95
DB25S	SOCKET (Meets RS232)	\$3.50
DBS122S-1	Cable Cover for DB25P or DB25S	\$1.75

PRINTED CIRCUIT EDGE-CARD

156 Spacing 1-in Double Row Out - Buffered Contacts - Pins 094 to 019 P.C. Core	Price
15/30	PINS (Solder Eyelet) \$1.95
18/36	PINS (Solder Eyelet) \$2.49
22/44	PINS (Solder Eyelet) \$2.95
50/100 (100 Spacing)	PINS (Wire Wrap) \$6.95
50/100 (125 Spacing)	PINS (Wire Wrap) R681-1 \$6.95

Solar Cells 2x2cm

- 0.4 volts
 - 100mA
 - 41 MW
- Can be added in series for higher voltage or parallel for higher current.
- #SC 2x2 \$1.95 ea. or 3/\$5.00

Magnetically Activated Switch

The 9250 0002 is a single pole normally closed switch. When the magnet is engaged, the circuit is open. This switch is only suitable for use in non-magnetic doors and windows.


#9250-0002 2/\$1.00

AC Wall Transformer



Part No.	Input	Output	Price
AC 250	117V/60Hz	12 VAC 250mA	\$3.95
AC 500	117V/60Hz	12 VAC 500mA	\$4.95

REMOTE CONTROL TRANSMITTER & RECEIVER

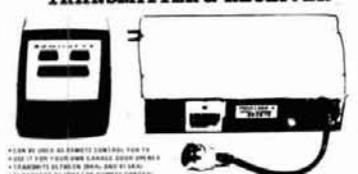

PLUG IN YOUR REMOTE CONTROL NOW TO FIND OUT HOW YOUR NEW REMOTE CONTROL WORKS!
* TRANSMITTER IS FOR TV, VCR, STEREO, AND MORE!
* TRANSMITTER IS ONLY FOR REMOTE CONTROL APPLICATIONS!
* TRANSMITTER USES A 1.5V BATTERY!
* REMOTE CONTROL ONLY!
\$19.95

INSTRUMENT/CLOCK CASE

This case is an injection molded unit that is ideal for uses such as DVM, COUNTER, or CLOCK cases. It has dimensions of 4 1/2" in length by 4" in width by 1-9/16" in height. It comes complete with a red bezel.

PART NO: IN-CC \$3.49 each

MICROPROCESSOR COMPONENTS

8080/8085 SUPPORT DEVICES		MICROPROCESSOR MANUALS	
8080A CPU	\$ 9.95	M-Z80 User Manual	\$7.50
8212 8-Bit Input/Output	7.75	M-COP1802 User Manual	7.50
8214 Priority Interrupt Control	3.95	M-Z8000 User Manual	5.00
8216 8-Directional Bus Driver	3.49		
8224 Clock Generator/Driver	3.95		
8226 Bus Driver	3.49	25132(140) Character Generator (upper case)	\$9.95
8228 System Controller/Bus Driver	5.95	25132(201) Character Generator (lower case)	9.95
8238 System Controller	5.49	2516 Character Generator	10.95
8251 Prog. Control 1.0 (LSI/ART)	14.95	MMS320N 2048-Bit Read-Only Memory	1.95
8253 Prog. Interval Timer	7.95		
8255 Prog. Parallel I/O (PPI)	9.95		
8257 Prog. DMA Control	19.95		
8259 Prog. Interrupt Control	19.95		

8080/8085 SUPPORT DEVICES		MICROPROCESSOR CHIPS—MISCELLANEOUS	
MC6800 MPU with Clock and Ram	\$14.95	7801/7802 CPU	\$19.95
MC6810MPU 128K Static Ram	24.95	Z80A/7801-1 CPU	24.95
MC6821 Peripheral Adapt (MC6820)	5.99	COP1802 CPU	19.95
MC6828 Priority Interrupt Controller	7.49	2650 MPU	19.95
MC6830L 1024X8 Bit ROM (MC68A30-B)	14.95	8035 8-Bit MPU w/clock, RAM, I/O lines	19.95
MC6850 Asynchronous Comm. Adapter	7.99	PN85 CPU	19.95
MC6862 Synchronous Serial Data Adapter	9.95	TMS9903L 16-Bit MPU w/hardware multiply & divide	49.95
MC6860 0-600 bps Digital MODEM	12.95		
MC6862 2400 bps Modulator	14.95		
MC6868A Quad 3-State Bus Trans. (MC68726)	7.25		

MICROPROCESSOR CHIPS—MISCELLANEOUS		SHIFT REGISTERS	
7801/7802 CPU	\$19.95	MM5009H Dual 35 Bit Dynamic	5.50
Z80A/7801-1 CPU	24.95	MM5009H Dual 30 Bit Dynamic	5.00
COP1802 CPU	19.95	MM5009H Dual 16 Bit Static	5.00
2650 MPU	19.95	MM5009H Dual 100 Bit Static	5.00
8035 8-Bit MPU w/clock, RAM, I/O lines	19.95	MM5104H Dual 64 Bit Accumulator	5.00
PN85 CPU	19.95	MM50512H 500-512 Bit Dynamic	3.99
TMS9903L 16-Bit MPU w/hardware multiply & divide	49.95	1024 Dynamic	2.95
		2527 Dual 132 Bit Static	2.95
		2524 512 Static	2.95
		2525 1024 Dynamic	2.95
		2527 Dual 256 Bit Static	2.95
		2528 Dual 250 Static	2.95
		2529 Dual 740 Bit Static	2.95
		2532 Quad 80 Bit Static	2.95
		2533 1024 Static	2.95
		3341 Flip	6.95
		74LS670 4X4 Register File (TriState)	1.95

UART'S		PROM'S	
A-Y-5-1013 30K BAUD	5.95	7802A 2048 FAMOS	55.95
		7802B 16K* EPROM (Intel 2716)	49.95
		7802C 16K* EPROM (Intel 2716)	49.95
		7802D 16K* EPROM (Intel 2716)	49.95
		7802E 16K* EPROM (Intel 2716)	49.95
		7802F 16K* EPROM (Intel 2716)	49.95
		7802G 16K* EPROM (Intel 2716)	49.95
		7802H 16K* EPROM (Intel 2716)	49.95
		7802I 16K* EPROM (Intel 2716)	49.95
		7802J 16K* EPROM (Intel 2716)	49.95
		7802K 16K* EPROM (Intel 2716)	49.95
		7802L 16K* EPROM (Intel 2716)	49.95
		7802M 16K* EPROM (Intel 2716)	49.95
		7802N 16K* EPROM (Intel 2716)	49.95
		7802O 16K* EPROM (Intel 2716)	49.95
		7802P 16K* EPROM (Intel 2716)	49.95
		7802Q 16K* EPROM (Intel 2716)	49.95
		7802R 16K* EPROM (Intel 2716)	49.95
		7802S 16K* EPROM (Intel 2716)	49.95
		7802T 16K* EPROM (Intel 2716)	49.95
		7802U 16K* EPROM (Intel 2716)	49.95
		7802V 16K* EPROM (Intel 2716)	49.95
		7802W 16K* EPROM (Intel 2716)	49.95
		7802X 16K* EPROM (Intel 2716)	49.95
		7802Y 16K* EPROM (Intel 2716)	49.95
		7802Z 16K* EPROM (Intel 2716)	49.95

CSC CONTINENTAL SPECIALTIES PROTO BOARDS

Proto Board 203

Model Number: PB-6
L x W x H (inches): 6.0 x 4.5 x 1.4
Price: \$15.95

Proto Board 203A

Model Number: PB-102
L x W x H (inches): 7.0 x 4.5 x 1.4
Price: \$26.95

BK PRECISION 3 1/2-Digit Portable DMM

Model 2800 \$99.95

CSC 100 MHz 8-Digit Counter

Model 100-100 \$134.95

CSC Mini-Max 6 Digit 50MHz Frequency Counter

Model 100-100 \$89.95

Accessories for Mini-Max:

Part No.	Description	Price
MM-A4	Antenna	\$ 3.95
MM-CS	Carrying case	5.95
MM-IPC	Input cable with clip leads	3.95
MM-AC2	110V adapter	9.95
MM-AC3	220V adapter	9.95

The Incredible "Pennywhistle 103"

\$139.95 Kit Only

The Pennywhistle 103 is capable of recording data to and from audio tape without critical speed requirements for the recorder and it is able to communicate directly with another modern and terminal for telephone, telex, and communications. In addition, it is free of critical adjustments and is built with non-precision, readily available parts.

Maximum Data Rate: 300 Baud
Data Format: Asynchronous Serial (return to mark level required between each character)
Receive Channel Frequencies: 2025 Hz for space, 2225 Hz for mark
Transmit Channel Frequencies: Switch selectable. Low (normal) — 1070 space, 1270 mark, high — 805 space, 2225 mark
Receive Sensitivity: -46 dbm acoustically coupled
Transmit Level: -15 dbm nominal. Adjustable from -6 dbm to -20 dbm
Receive Frequency Tolerance: Frequency reference automatically adjusts to allow for operation between 1800 Hz and 2400 Hz
Digital Data Interface: (EIA RS-232C or 20 mA current loop receiver is optional and non-polar)
Power Requirements: 120 VAC, single phase, 10 Watts
Physical: All components mount on a single 5" x 9" printed circuit board. All components included.
Requires a VOM, Audio Oscillator, Frequency Counter and/or Oscilloscope to align

TRS-80 16K Conversion Kit

Expand your 4K TRS-80 System to 16K. Kit comes complete with:

- * 8 each UPD416 (16K Dynamic Rams)
- * Documentation for conversion

TRS-16K \$115.00

Special Offer - Order both your TRS-16K and the Sup'R' MOD II Interface kit together (retail value \$144.95) for only \$139.95

COMPUTER CASSETTES

• 6 EACH 15 MINUTE HIGH QUALITY C-15 CASSETTES
• PLASTIC CASE INCLUDED
• 12 CASSETTE CAPACITY
• ADDITIONAL CASSETTES AVAILABLE @ C-15-\$2.50 ea

CAS-6 \$14.95
(Case and 6 Cassettes)

SUP 'R' MOD II

UHF Channel 33 TV Interface Unit Kit

Wide Band B/W or Color System

- * Converts TV to Video Display for home computers, CCTV camera, Apple II, works with Cromecor Dazler, SOL-20, TRS-80, Challenger, etc.
- * MOD II is pretuned to Channel 33 (UHF)
- * Includes coaxial cable and antenna transformer

MOD II \$29.95 Kit

RS-232 CONTROL CENTER

Plug in your modem, computer, prom programmer, terminal, printer, etc. and selectively control data flow.

- Same Control as "Pennywhistle 103"
- Totally self contained
- Includes 2 master ports and 3 slave ports

PART NO. RS-232CC \$89.95 kit only

CASSETTE CONTROLLER

Model 100-100 \$29.50

The CC100 controls cassette motor functions, monitors tape location with its internal speaker and requires no power. Eliminates the plugging and unplugging of cables during computer loading operation from cassette.

63-Key Unencoded Keyboard

This is a 63-key, terminal keyboard newly manufactured by a large computer manufacturer. It is unencoded with SPST keys, unattached to any kind of PC board. A very solid molded plastic 13 x 4" base suits most application. IN STOCK **\$29.95/each**

Hexadecimal Unencoded Keypad

19-key pad includes 4-10 keys, ABCDEF and 2 optional keys and a shift key. **\$10.95/each**

\$10.00 Minimum Order — U.S. Funds Only
California Residents — Add 6% Sales Tax

NEW 1979 Catalog

Jameco ELECTRONICS

MAIL ORDER ELECTRONICS — WORLDWIDE
1021 HOWARD AVENUE, SAN CARLOS, CA 94070
ADVERTISED PRICES GOOD THRU APRIL

PHONE ORDERS WELCOME (415) 592-8097

CALL TOLL FREE

For the best deal on

- AEA • Ameco • ASP • Atlas
- Belden • Bencher • Bird
- CDE • CIR • CES • Cushcraft
- DenTron • Drake • Hy-Gain
- Icom • KLM • Kenwood
- Larsen • MFJ • Midland
- Mosley • NPC • Newtronics
- Nye • Palomar • Regency
- Shure • Swan • Standard
- Tempo • Ten-Tec • Tonna
- Transcom • Wilson • Yaesu

NEAR CHICAGO?

COME IN AND SEE US!



Tim WB8SBL and Mike WN9AN
serving you!



CALL TOLL FREE
FOR THE ERICKSON PRICE!

OUTSIDE ILLINOIS: (800) 621-5802



Hours:

9:30-5:30 Mon., Tues., Wed. & Fri.

9:30-9:00 Thursday

9:00-3:00 Saturday

ERICKSON

COMMUNICATIONS, INC.

5456 N. MILWAUKEE AVE

CHICAGO, IL 60630 (312) 631-5181

ILLINOIS: Kishwaukee Radio Club and DeKalb Co. Amateur Repeater Club's 21st annual indoor/outdoor hamfest, Sunday, May 6, 8:00 AM to 3:00 PM, Notre Dame School, Gurler Road, DeKalb. Tickets \$1.50 advance, \$2.00 door. Indoor tables available, own tables free, outdoor setup free. Talk-in 146.13/73 and 94 simplex. For info: SASE to Howard WA9TXW, P.O. Box 349, Sycamore, IL 60178.

ILLINOIS: The Moultrie Amateur Radio Klub's 18th annual hamfest, April 22, Moultrie County 4-H Center Fairgrounds, Cadwell Road, Mattoon. Indoor/outdoor flea market. Talk-in 146.94 and 146.055/655. For info: M.A.R.K., Box 327, Mattoon, IL 61938.

INDIANA: The Cass County Amateur Radio Club's second annual hamfest, Sunday, May 6, from 7:00 AM to 4:00 PM, at the 4-H Fairgrounds, Rain or Shine. Go North to Logansport on Highway 25, turn right at road 100, follow QSY signs. Advance tickets \$1.50, \$2.00 at gate. Outside setup free, undercover \$1.00. Bring your own tables. Free overnight camping, plenty of refreshments. Talk-in: 146.52 and Logansport Repeater: 147.78-18. Write to: K9DVL Dave Rothermel, RR 4, Box 146 G, Logansport, IN 46947.

CALIFORNIA: The 37th Annual Fresno hamfest, May 11-13, Sheraton Inn, Clinton and Hiway 99. Technical talks, swap tables, flea market, transmitter hunt on 2 meters (146.52), QLF contest, exhibits, prizes. Prime rib banquet. Registration with eligibility for pre-registration prize, \$17.00 before April 27. \$19.00 and no pre-reg prize after that date. Talk-in on 146.34/146.94. For info: Fresno Amateur Radio Club, P.O. Box 783, Dept. HF, Fresno, CA 93712.

KENTUCKY HAM-O-RAMA — Sunday, May 20, at Boone County Fairgrounds, Burlington, Kentucky, 10 miles South I-75 of Cincinnati, Ohio. Major and hourly door prizes included with \$3.00 gate ticket. Info: N.K.A.R.C., Box 31, Ft. Mitchell, KY 41017.

MASSACHUSETTS: South Shore Repeater Association's 4th annual Ham Auction, Saturday, April 21, Central Junior High School, Broad Street, Weymouth. 12 Noon. Doors open 9 AM. Club share 10%, refreshments, door prizes. For info: South Shore Repeater Ass., Town Hall Annex, 402 Essex St. Weymouth, MA 02188.

MASSACHUSETTS: Central Mass. Amateur Radio Association's auction and flea market, April 27, 7:30 PM. Doors open 6:00 PM. Main South American Legion Post 341, Main Street at Webster Square, Worcester. Auction rates — 15% to CMARA, Flea Market tables \$5.00. Door prizes, raffles, refreshments. Talk-in 146.37-146.97 and .52 direct. For info: Rene Brodeur, WA1LEA (617) 753-7480 and Dave Penttila, K1COW, (617) 885-4995.

MASSACHUSETTS: The Wellesley Amateur Radio Society's annual auction, Saturday, April 7, 11:00 AM (doors open 10:00 AM), Wellesley High School Cafeteria, Rich Street, Wellesley. Talk-in on 96/36, 63/03, 04/64 and 52. Contact: Kevin P. Kelly, WA1YHV, 7 Lawnwood Place, Charlestown, MA 02129.

MASSACHUSETTS: The Hampden County Radio Association's annual flea market, Friday, May 4, Feeding Hills Congregational Church, intersection of Routes 57 and 187, west of Springfield. \$2.00 per table, no admission fee. Doors open 7:00 PM. Refreshments available. For info: Andy Bouchard, WB1BZW — (413) 786-2301.

MICHIGAN: South Eastern Michigan Amateur Radio Association's 21st annual hamfest, April 8, 8:00 AM to 3:00 PM EST, South Lake High School, 21900 E. Nine Mile Road at Mack Avenue, St. Clair Shores. For info: SEMARA, Mark C. Wilke, W8BRDA, 171 Merriweather Rd., Grosse Pointe Farms, MI 48236.

MICHIGAN: The Wexauke ARA's 19th annual Swap and Shop, Saturday, May 19, 9:00 AM - 4:00 PM, National Guard Armory, 415 Haynes St., Cadillac. Tickets \$2.00, free parking. Talk-in on 146-3797. Info from W8RZL.

MISSISSIPPI: The Jackson Amateur Radio Club's annual hamfest, April 21 and 22, Manhattan Academy gymnasium, 5055 Manhattan Rd., Jackson. For info: JARC, Box 8371, Jackson, MS 39204 or call MS. Sideband Net daily, 3987.5, 2345 GMT.

MISSOURI: Central Missouri Radio Association's fourth annual hamfest, April 7, Cosmo Recreation Center, 1507 Business Loop 70 West, Columbia. FCC exams, forums, ladies' programs, flea market, prizes. Open for exhibitors April 6, 7-9 PM, April 7, 6:30 AM. Reserved commercial space, \$15.00 per table. For info write: C.M.R.A., P.O. Box 283, Columbia, Missouri 65201.

MISSOURI: The P.H.D. Amateur Radio Association's tenth annual hamfest, Saturday and Sunday, April 21, 22, Kansas City Trade Mart, Kansas City Downtown Airport, free parking. Display booth space, \$15.00 single, \$25.00 double. 11:00 AM to 5:30 PM Saturday, 10:00 AM to 5:00 PM Sunday. Set up beginning 9:00 AM Saturday. PHD ARA, P.O. Box 11, Liberty, MO 64068.

SECURITRON CW IDENTIFIERS



MODEL 97812

PREPROGRAMMED MEMORY ID'ers

MODEL 97812 — multi-mode MCW ID'er • adjustable audio level • programmable code speed, tone & repeat interval • manual, auto & semi-auto modes • for repeater, base or mobil operation • 1.8" x 3.6" PCB. \$44.95/kit*, \$64.95/assembly*

MODEL 11764 — continuous MCW ID'er with PTT control • adjustable audio level • programmable code speed, tone & repeat interval • 1.7" x 3" PCB. \$34.95/kit*, \$49.95/assembly*

MODEL 97710 — manual CW ID'er • programmable code speed • ID's upon request • ideal for contesting or low band CO's • 1.5" x 2.2" PCB. \$29.95/kit*, \$39.95/assembly*

MODEL 11765 — beacon CW ID'er • programmable code speed • great for 1750 meter band • 1.3" x 2" PCB. \$24.95/kit*, \$34.95/assembly*

[254 bit memory, standard on above ID'ers. 510 bit memory version on Models 97812E & 97710E. \$15.00 additional. Additional pre-programmed memory elements available. Commercial ID'ers available.]

MODEL 12751 — field programmable auto MCW ID'er • 110 bit memory • closeout on remaining stock. \$29.95/kit* — only.

*Include \$3 shpg/hdng., \$5 foreign. CA res. add 6% tax. CODs accepted. Send check or MO, allow 3 weeks on personal checks. Write for additional information.
Phone (408) 294-8383

SECURITRON CO.
P. O. Box 24899
San Jose, Ca 95154

DAMES COMMUNICATION SYSTEMS

Ham Gear

Collins 51J4, general coverage receiver	\$595
Collins 516 F2 power supply, new, in box	\$275
Collins KWM2A transceiver, exc. rnd.	\$1375
Collins 75A4 ham receiver, vy good	\$425
Collins 312B4, Sta Cntl, rd, exc	\$250
Collins 312B5, Vfo Console, exc	\$250
Collins 75S3C, rnd, exc	\$1250
Collins 180S1, antenna tuner	\$295
Collins 30L1, vy gd	\$595
Collins 516F2, power supply	\$175
Collins R-390A rcvrs, overhauled exc cond	call for quote

Collins 51S1, 2-30 MHz rcvr	Special
Hammarlund SP-600JX, rcvr	\$395
Collins CP-1 Crystal Pack	\$195
Racal 6217E, .5-30 MHz receiver	\$1350
Collins 32S3 ham transmitter, vy gd	\$650
Harrison 0-20 volt/1.5 amp lab pwr supplies, ea.	\$45
Johnson 2kw Matchbox w/swr meter	\$195

Test Gear

HP-302A wave analyzer	\$375
Boonton Radio 225A sig. gen., 10-500 MHz	\$495
HP-200CD wide-range oscilloscope	\$150
Measurements Model 80, 2-400 MHz	\$295
Measurements Model 65B signal generator	\$295
HP-202H 54-216 MHz AM/FM sig gen	\$695
HP-608D 10-420 MHz sig gen	\$550
Tek 564 storage 'scope, w/plug ins	\$695
Tek 545 30-MHz 'scope	\$395
Tek 531A 'scope, exc	\$350
Tek 851 digital tester new, w/access	call for quote

We stock Amateur and Professional equipment from manufacturers such as Collins, Hewlett-Packard, etc.

All equipment sold checked and realigned
Write for free catalog.

201-998-4256
10 SCHUYLER AVENUE
NORTH ARLINGTON, N. J. 07032

**NOT FOR
BEGINNERS**

"HOT" NEW BOOKS FOR MICRO-COMPUTER PROS!

The latest in micro-computer books that people waited in line to buy!



TV Typewriter Cookbook
By D. Lancaster

Covers tvl terms, principles, configurations, memories, system design, cursor & update circuitry & techniques, hard copy, color graphics, keyboards & encoders. 256 pgs. #21313... \$9.95



8080/8085 Software Design
By C. Titus, P. Rony, D. Larsen & J. Titus

Offers basic & advanced instructions for assembly language programming. Covers mathematical manipulations, number-base conversions, decoders, arrays, etc. 336 pgs. #21541... \$9.50



CMOS Cookbook
By D. Lancaster

What CMOS is, how it works, & how to power, use, test & interface it, etc. With minicatalog of over 100 devices. 416 pgs. #21398... \$10.50



Getting Acquainted with Microcomputers
By L. Frenzel

Explains basic concepts, definitions, organization, architecture, operation, software, programming & personal computing. With experiments for self-education. 288 pgs. #21486... \$8.95



Design of OP-AMP Circuits, with Experiments
By H. Berlin

The fundamentals of operational amplifier devices (e.g., 741 & 3900) in linear amps, differentiators, filters & nonlinear amps. 35 experiments. 224 pgs. #21537... \$7.95



Z-80 Microcomputer Handbook
By W. Barden, Jr.

All about the Zilog Z-80, a very sophisticated microprocessor: its hardware, its software, and microcomputers built around it. 304 pgs. #21500... \$8.95



Design of Phase Locked Loop Circuits, with Experiments
By H. Berlin

Details the design of the basic PLL circuits, detector, phase comparator & voltage-controlled oscillator circuits. 15 experiments. 256 pgs. #21545... \$8.95



The Cheap Video Cookbook
By D. Lancaster

A complete guide to super-low-cost alphanumeric & graphic microprocessor-based video displays, with construction details on a seven IC circuit—and much more! 256 pgs. #21524... \$5.95



555 Timer Applications Sourcebook, with Experiments
By H. Berlin

Deals with the many uses of the 555 timer "chip"—for timing, signal generation, voltage regulation, control, sequencing. 15 experiments. 160 pgs. #21538... \$5.95



Design of Active Filters, with Experiments
By H. Berlin

An intro to the theory, design & use of active filter circuits using the 741 op-amp chip—and no complex math. Many experiments, examples. 240 pgs. #21539... \$7.95



TTL Cookbook
By D. Lancaster

Explains what transistor-transistor logic is, how it works & how to use it—for a digital counter & display system, electronic stopwatch, digital tachometer, voltmeter, etc. 336 pgs. #21035... \$9.50

**AVAILABLE FOR THE
FIRST TIME BY MAIL!**

**NO RISK
OFFER!**

**YOURS TO EXAMINE
AT NO RISK
FOR 15 DAYS**

Clip Out—Mail Today!

YES—Please send me the book(s) indicated below. If I'm not completely satisfied, I may return any or all within 15 days of receipt for full credit or refund. Add sales tax where applicable.

- | | | |
|--------------------------------|--------------------------------|--------------------------------|
| <input type="checkbox"/> 21313 | <input type="checkbox"/> 21539 | <input type="checkbox"/> 21538 |
| <input type="checkbox"/> 21486 | <input type="checkbox"/> 21541 | <input type="checkbox"/> 21035 |
| <input type="checkbox"/> 21500 | <input type="checkbox"/> 21537 | <input type="checkbox"/> 21398 |
| <input type="checkbox"/> 21524 | <input type="checkbox"/> 21545 | |

I have checked 3 or more titles and deducted my 10% savings.

Name _____ (Please Print)

Address _____

City _____ Total: \$ _____

State _____ Zip Code _____

Check Money Order Master Charge

Visa/BankAmericard

Exp. Date _____

Account No.: _____

Interbank No.: _____ (Master Charge only) MN 5 2

3 17

Signature: _____

Minimum credit card purchase: \$10.00

MAIL TO:
Howard W. Sams & Co., Inc.
4300 W. 62nd St.
Indianapolis, IN 46206

Prices subject to change 6 months after issue date

CAREER OPPORTUNITY

We are a leading manufacturer of automated material handling systems, and presently have openings for technicians and field service engineers having a good working knowledge of electronics and mechanics. Will be working with servo control, guidance systems and microprocessors. Good benefits and more. Call (312) 272-2300 or write to:

BARRETT ELECTRONICS CORP.

630 Dundee Road
Northbrook, Illinois 60062
Attn: Wally Mitchell WA9EQP

SIGNAL GENERATORS

RECONDITIONED AND LAB CALIBRATED

AN/URM-25, 10 KHZ THRU 50 MHZ, AM/CW MODULATION 400 & 1 KHZ, RF OUTPUT 0-2V OR 0-1V PRECISION 50 OHM STOP ATTENUATOR \$285.00
 TS-497/URR, 10 KHZ THRU 50 MHZ, AM/CW 0-100,000 MV, 2 THRU 400 MHZ, MILITARY VERSION OF MEASUREMENTS MODEL 80 225.00
 TS-510A/U RANGE 10 MHZ THRU 420 MHZ OUTPUT VOLTAGE .5V to 1V, MODULATION 400, 1000 HZ BUILT-IN CALIBRATOR, AM, CW, PULSE 425.00
 SG-12/U, RANGE 20 MHZ THRU 100 MHZ IN 5 RANGES, BUILT-IN FM MODULATION, CALIBRATED OUTPUT METER AND DEVIATION, CRYSTAL MARKERS 185.00
 SG-3/U RANGE 50 THRU 400 MHZ IN 3 BANDS, RF OUTPUT .1V, VARIABLE 50 OHM ATTENUATOR, FM DEVIATION 0-150 KHZ IN 3 RANGES 385.00
 SG-24/TRM-3 SWEEP SIGNAL GENERATOR, RANGE 15 THRU 400 MHZ, FM, AM, CW OUTPUT, FM DEVIATION, BUILT-IN OSCILLOSCOPES FOR OBSERVING WAVEFORMS, CRYSTAL MARKERS 265.00
 COLLINS 479T-2 VOR/ILS, RANGE 108-135.9 MHZ AND 329.3 TO 335 MHZ OUTPUT SIGNALS INCLUDE VOR, LOC, GLIDESLOPE AND 1000 CPS, OPERATES FROM 28 VDC AIRCRAFT OR BENCH POWER SUPPLY 225.00
 TS-621/URM-52 RANGE 3.8 THRU 7 GHZ, SAME AS HP618B, CW, PULSE, FM, SQUARE WAVE 285.00
 TS-403/URM-61 RANGE 1800 THRU 4000 MHZ, FM, CW, PULSE, SQUARE WAVE, MILITARY VERSION OF HP616A 285.00
 TS-418/URM-49, RANGE 400 THRU 1000 MHZ AM, CW OR PULSE 145.00
 TS-419/URM-64, RANGE 900 THRU 2100 MHZ CW OR PULSE EMISSION 165.00
 SG-66/ARM-5, VOR GENERATOR RANGE 108 THRU 132 MHZ, MILITARY VERSION ARC H-14A 285.00
 SATISFACTION GUARANTEED OR MONEY REFUNDED. SEND CHECK, M. C. OR VISA, FOB OTTO, N. C., PHONE BILL SLEP (704) 524-7519.

SLEP ELECTRONICS  CO.

P.O. BOX 100, HWY. 441, DEPT. HR
OTTO, NORTH CAROLINA 28763

NEW ENGLAND: The Hosstraders Net will hold its Sixth Annual Tailgate Swapfest, Saturday, May 12, at the Deerfield, New Hampshire, Fairgrounds (covered buildings in case of rain). Admission: one dollar, no percentage or commission, commercial dealers welcome at same rate. Excess revenues benefit Boston Burns Unit of Shriners' Hospital for Crippled Children. Last year we donated \$1140.50. Talk-in .52 and 146.40-147.00. Questions about New England's biggest flea market? SASE to Joe DeMaso K1RQG, Star Route Box 56, Bucksport, ME 04416, or Norm Blake, WA1IVB, P.O. Box 32, Cornish, ME 04020.

NORTH CAROLINA: The Raleigh Amateur Radio Society's 7th annual hamfest, April 22, 9:00 AM, Crabtree Valley Mall, US 70 West, Raleigh. \$3.00 admission. Many prizes. First prize: Kenwood TS520S or ICOM 211 and others. Covered flea market, nearby motels and restaurants, hospitality room Saturday night. Talk-in Saturday and Sunday, WR4ACF (146.04/146.64) and WR4AOE (146.28/146.88). For info: RARS Hamfest, P.O. Box 17124, Raleigh, NC 27609.

NORTH CAROLINA: The Durham F.M. Association's annual Durhamfest, Saturday and Sunday, May 19 and 20, South Square Mall, Durham. Prizes, exhibits, programs. Shopping malls for XYLs. Sunday, ladies's bingo. Free tailgating spaces, covered flea market. \$3.00 general ticket. Vendors and dealers included. Harmonics and unlicensed XYL's free. Power available. Talk-in 147.825-225, 146.34-94, 222.34-3.94. For info: DFMA, Box 8651, Durham, NC 27707.

OHIO: F.M. B*A*S*H, Dayton, April 27, 1979, Friday night of DAYTON HAMVENTION. Social evening for hams and friends, 8 PM til midnight, Dayton Convention Center, Main at Fifth Street. Admission free. Sandwiches, snacks and C.O.D. bar available. TV personality Rob Reider, WA8GFF, and his group will present a super show and there will be drawings for many fabulous prizes including a complete Drake UV-3 with 144, 220 and 440 MHz synthesized modules, power supply, encoder mike and antenna. For further information contact: Miami Valley F.M. Assn., P.O. Box 263, Dayton, Ohio 45401.

OHIO: The Dayton Amateur Radio Association's Hamvention, April 27, 28 and 29, Dayton Hara Arena and Exhibition Center. Prizes, contests, banquets. "Radio Amateur of the Year" award. Flea market hours: Saturday — 6 AM to 5 PM. Sunday — 6 AM to 4 PM. Own tables. Space: \$10.00 ea. advance, \$12.00 ea. door. Maximum four spaces. For additional information, reservations, accommodations: Dayton Hamvention, P.O. Box 44, Dayton, OH 45401. (513) 293-0459.

PENNSYLVANIA: Fifth Annual Northwest PA hamfest, Saturday, June 9, 1979, Crawford County Fairgrounds, Meadville, PA. Note date change. Gates open at 8:00 AM. Bring your own tables. \$2.00 in; \$1.00 out to display. \$2.00 admission. Hourly door prizes, refreshments, commercial displays welcome. Talk-in 04/64, 81/21, 63/03. Details C.A.R.S., P.O. Box 653, Meadville, PA 16335. Attention: Hamfest Committee.

PENNSYLVANIA: The Annual Reading Radio Club hamfest, Sunday, May 27, 9:00 AM, Hamburg Field House, Hamburg. Door prizes, food, tailgate sales, dealer space available, rain or shine. Talk-in on 31/91 and 146.52. For info: Reading Radio Club, P.O. Box 124, Reading, PA 19603.

PENNSYLVANIA: The Penn Wireless Association's Tradefest '79, April 1, 8:00 AM. (7:00 AM for setup), National Guard Armory, Southampton Road and Roosevelt Blvd., Philadelphia. Display space \$3.00 ea. includes one chance towards prizes.

PENNSYLVANIA: The Warminster Amateur Radio Club's Fifth Annual Ham-Mart Flea Market and Auction, Sunday, May 6, 9:00 AM - 4:00 PM, William Tennent Intermediate High School, Street Road (Route 132) Warminster, Bucks County. Registration: \$1.00 per car (includes one door prize ticket). Tailgating: \$2.00 add. Indoor tables: \$3.00 ea. Talk-in on 146.16/76 and 146.52 MHz. For info: Horace Carter, K3KT, 38 Hickory Lane, Doylestown, PA 18901. (215) 345-6816.

PUERTO RICO: The Radio Club de Puerto Rico's annual convention and hamfest, April 28 and 29, Condado Holiday Inn Hotel, San Juan. For details: GPO, Box 693, San Juan, PR 00936.

WASHINGTON: The Skagit Amateur Radio Club's 27th annual convention, April 20, 21 and 22, Bryant Grange Center near Seattle. For info: Norman G. Ray, Program Chairman, 14005 - 132nd Avenue N.E., Kirkland, WA 98033.

WISCONSIN: 3-F Amateur Radio Club's annual Swapfest, Saturday, May 5, 8 AM to 3 PM, Neenah Labor Temple, 157 South Greenbay Rd., Neenah. Large parking, indoor swap areas, free auction. Refreshments available. Tickets: \$1.50 advance, \$2.00 door; tables \$1.50 advance, \$2.00 door. Reservations to: Mark Michel, W9OP, 339 Naymut St., Menasha, WI 54952.

MILO ASSOCIATES

BOX 2323 • INDIANAPOLIS, INDIANA 46206

ICOM
SUBSTITUTES
COMPONENTS
MATERIALS

PHONE: 317-871-5519

VISA	HAMS SERVING HAMS	Master Charge
COAXIAL CONNECTORS		
	PL259's 10/\$5 \$40/C	
	SO239's 10/\$5 \$40/C	
	UG83's (1" N/UHF) \$4.50	
	UG146U (UHF/N) \$4.50	
	PL258 Barrel \$1.25	
	PL259PO Push-on \$1.50	
	UG1094 BNC F \$1.00	
	UG8B BNC M \$1.25	

WE STOCK ALL TYPES!!!

	76477	SOUND EFFECT IC
CERAMIC TRIMMERS		
3-9pf	5-5-18pf	How you can easily make ANY custom, complex type sounds you desire! 2pin wonder-THE LATEST!
3-10pf	10-60pf	\$3.50 EA. 3/\$10!
4.5-20pf	30-90pf	16 page manual only 50c
MIX/MATCH	10/\$5	

BRIDGES	HEAT SLIPS
IR #30DB4P-NEW!	
400V @ 3AMP	HEAT SLIP-TOUCH
Stock up NOW!	For TO-18 Cases
\$1 ea. 6/\$5	\$1 ea. 6/\$5

ELECTROLYTIC'S	SEE US AT THE DAYTON Hamvention
	OR
FACTORY FRESH RADIALS!	SEND STAMP FOR FLYER!
1mf @ 25v 8/51.00	
100 @ 25v 6/31.00	
2200 @ 16v 1/31.00	

ITS EASY TO ORDER!

Use Visa; Master Charge; Check; M.O.; C.O.D. Telephone orders welcome. Allow for shipping - excess quickly refunded. Minimum order of \$5.00 please! Indiana residents add 4% tax. Prices good through cover month.

HI-Q BALUN

- For dipoles, yagis, inverted vees, doublets & quads
- For full legal power & more
- Puts power in antenna
- Broadbanded 3-40Mhz.
- Small, light, weather-proof
- 1:1 Impedance ratio
- Replaces center insulator
- Helps eliminate TVI
- Fully Guaranteed



Van Gorden Engineering
\$9.95 PPD U.S.A.
BOX 21305, S. EUCLID, OHIO 44121



Instant

Identity

The time has come for all amateurs to unite on sight. We must know each other as do other fraternal organizations. The ability to recognize each other on any occasion is a true mark of fraternal brotherhood. Group III, (WB2LCK, KB2DX and KB2DZ) designed this 10 karat gold ring to portray our great and proud fraternity. This exquisite ring is made exclusively for you by Josten's (world famous for their quality achievement rings) with your call letters prominently displayed. For detailed information and reusable ring size... Write: Group III Sales Co., Dept. 35 P.O. Box 259 Little Neck, N.Y. 11362

No Obligation

DIODES/ZENERS

QTY.	1N914	100v	10mA	.05
	1N4005	600v	1A	.08
	1N4007	1000v	1A	.15
	1N4148	75v	10mA	.05
	1N4733	5.1v	1 W Zener	.25
	1N753A	6.2v	500 mW Zener	.25
	1N758A	10v	"	.25
	1N759A	12v	"	.25
	1N5243	13v	"	.25
	1N5244B	14v	"	.25
	1N5245B	15v	"	.25

SOCKETS/BRIDGES

QTY.	8-pin	pcb	.20	ww	.35
	14-pin	pcb	.20	ww	.40
	16-pin	pcb	.20	ww	.40
	18-pin	pcb	.25	ww	.95
	20-pin	pcb	.35	ww	.95
	22-pin	pcb	.35	ww	.95
	24-pin	pcb	.35	ww	.95
	28-pin	pcb	.45	ww	1.25
	40-pin	pcb	.50	ww	1.25
	Molex pins	.01	To-3 Sockets		.25
	2 Amp Bridge		100-prv		.95
	25 Amp Bridge		200-prv		1.50

TRANSISTORS, LEDS, etc.

QTY.	2N2222	(2N2222 Plastic .10)	.15
	2N2222A		.19
	2N2907A	PNP	.19
	2N3906	PNP (Plastic Unmarked)	.10
	2N3904	NPN (Plastic Unmarked)	.10
	2N3054	NPN	.45
	2N3055	NPN 15A 60v	.60
	T1P125	PNP Darlington	1.95
	LED Green, Red, Clear, Yellow		.15
	D.L.747	7 seg 5/8" High com-anode	1.95
	MAN72	7 seg com-anode (Red)	1.25
	MAN3610	7 seg com-anode (Orange)	1.25
	MAN82A	7 seg com-anode (Yellow)	1.25
	MAN74	7 seg com-cathode (Red)	1.50
	FND359	7 seg com-cathode (Red)	1.25

9000 SERIES

QTY.	9301	.85	9322	.65
	9309	.35	9601	.20
	9316	1.10	9602	.45

MICRO'S, RAMS, CPU'S, E-PROMS

QTY.	8T13	1.50	2107B-4	4.95
	8T23	1.50	2114	9.50
	8T24	2.00	2513	6.25
	8T97	1.00	2708	10.50
	74S188	3.00	2716 D.S.	34.00
	1488	1.25	2716 (5v)	59.00
	1489	1.25	2758 (5v)	23.95
	1702A	4.50	3242	10.50
	AM 9050	4.00	4116	11.50
			6800	13.95
	MM 5314	3.00	6850	7.95
	MM 5316	3.50	8080	7.50
	MM 5387	3.50	8212	2.75
	MM 5369	2.95	8214	4.95
	TR 1602B	3.95	8216	3.50
	UPD 414	4.95	8224	3.25
	Z 80 A	22.50	8228	6.00
	Z 80	17.50	8251	7.50
	Z 80 PIO	10.50	8253	18.50
	2102	1.45	8255	8.50
	2102L	1.75	TMS 4044	9.95

C MOS

QTY.	4000	.15
	4001	.15
	4002	.20
	4004	3.95
	4006	.95
	4007	.20
	4008	.75
	4009	.35
	4010	.35
	4011	.20
	4012	.20
	4013	.40
	4014	.75
	4015	.75
	4016	.35
	4017	.75
	4018	.75
	4019	.35
	4020	.85
	4021	.75
	4022	.75
	4023	.20
	4024	.75
	4025	.20
	4026	1.95
	4027	.35
	4028	.75
	4029	1.15
	4030	.30
	4033	1.50
	4034	2.45
	4035	.75
	4037	1.80
	4040	.75
	4041	.69
	4042	.65
	4043	.50
	4044	.65
	4046	1.25
	4048	.95
	4049	.45
	4050	.45
	4052	.75
	4053	.75
	4066	.55
	4069/74C04	.35
	4071	.25
	4081	.30
	4082	.30
	4507	.95
	4511	.95
	4512	1.10
	4515	2.95
	4519	.85
	4522	1.10
	4526	.95
	4528	1.10
	4529	.95
	MC 14409	14.50
	MC 14419	4.85
	74C151	1.50

LINEARS, REGULATORS, etc.

QTY.	MCT2	.95	LM323K	5.95	LM380 (8-14 Pin)	1.19
	8038	3.95	LM324	1.25	LM709 (8-14 Pin)	.35
	LM201	.75	LM339	.75	LM711	.45
	LM301	.45	7805 (340T5)	.95	LM723	.40
	LM308	.65	LM340T12	.95	LM725	2.50
	LM309H	.65	LM340T15	.95	LM739	1.50
	LM309K (340K-5)	1.50	LM340T18	.95	LM741 (8-14)	.35
	LM310	.85	LM340T24	.95	LM747	1.10
	LM311D	.75	LM340K12	1.25	LM1307	1.25
	LM318	1.75	LM340K15	1.25	LM1458	.65
	LM320H6	.79	LM340K18	1.25	LM3900	.50
	LM320H15	.79	LM340K24	1.25	LM75451	.65
	LM320H24	.79	LM373	2.95	NE555	.45
	7905 (LM320K5)	1.65	LM377	3.95	NE556	.85
	LM320K12	1.65	78L05	.75	NE555	.95
	LM320K24	1.65	78L12	.75	NE566	1.25
	LM320T5	1.65	78L15	.75	NE567	.95
	LM320T12	1.65	78M05	.75		
	LM320T15	1.65				

- T T L -

QTY.	7400	.10	7482	.75	74221	1.00	74LS02	.30
	7401	.15	7483	.75	74367	.95	74LS04	.30
	7402	.15	7485	.55	75108A	.35	74LS05	.35
	7403	.15	7486	.25	75491	.50	74LS08	.35
	7404	.10	7489	1.05	75492	.50	74LS09	.35
	7405	.25	7490	.45	74H00	.15	74LS10	.35
	7406	.25	7491	.70	74H01	.20	74LS11	.35
	7407	.55	7492	.45	74H04	.20	74LS20	.30
	7408	.15	7493	.35	74H05	.20	74LS21	.35
	7409	.15	7494	.75	74H08	.35	74LS22	.35
	7410	.15	7495	.60	74H10	.35	74LS32	.35
	7411	.25	7496	.80	74H11	.25	74LS37	.35
	7412	.25	74100	1.15	74H15	.45	74LS38	.45
	7413	.25	74107	.25	74H20	.25	74LS40	.40
	7414	.75	74121	.35	74H21	.25	74LS42	.75
	7416	.25	74122	.55	74H22	.40	74LS51	.45
	7417	.40	74123	.35	74H30	.20	74LS74	.45
	7420	.15	74125	.45	74H40	.25	74LS76	.50
	7426	.25	74126	.35	74H50	.25	74LS86	.45
	7427	.25	74132	.75	74H51	.25	74LS90	.65
	7430	.15	74141	.90	74H52	.15	74LS93	.65
	7432	.20	74150	.85	74H53	.25	74LS107	.50
	7437	.20	74151	.65	74H55	.20	74LS123	1.20
	7438	.20	74153	.75	74H72	.35	74LS151	.85
	7440	.20	74154	.95	74H74	.35	74LS153	.85
	7441	1.15	74156	.70	74H101	.75	74LS157	.85
	7442	.45	74157	.65	74H103	.55	74LS160	.95
	7443	.45	74161	.55	74H106	.95	74LS164	1.20
	7444	.45	74163	.85	74L00	.25	74LS193	1.05
	7445	.65	74164	.60	74L02	.20	74LS195	.95
	7446	.70	74165	1.10	74L03	.25	74LS244	1.70
	7447	.70	74166	1.25	74L04	.30	74LS367	.95
	7448	.50	74175	.80	74L10	.20	74LS368	.95
	7450	.25	74176	.85	74L20	.35	74S00	.35
	7451	.25	74180	.55	74L30	.45	74S02	.35
	7453	.20	74181	2.25	74L47	1.95	74S03	.25
	7454	.25	74182	.75	74L51	.45	74S04	.25
	7460	.40	74190	1.25	74L55	.65	74S05	.35
	7470	.45	74191	1.25	74L72	.45	74S08	.35
	7472	.40	74192	.75	74L73	.40	74S10	.35
	7473	.25	74193	.85	74L74	.45	74S11	.35
	7474	.30	74194	.95	74L75	.85	74S20	.25
	7475	.35	74195	.95	74L93	.55	74S40	.20
	7476	.40	74196	.95	74L123	.85	74S90	.20
	7480	.55	74197	.95	74LS00	.30	74S51	.25
	7481	.75	74198	1.45	74LS01	.30	74S64	.15
							74S74	.35
							74S112	.60
							74S114	.65
							74S133	.40
							74S140	.55
							74S151	.30
							74S153	.35
							74S157	.75
							74S158	.30
							74S194	1.05
							74S257 (8123)	1.05
							8131	2.75

INTEGRATED CIRCUITS UNLIMITED

7889 Clairemont Mesa Blvd., San Diego, California 92111

24 Hour Toll Free Phone 1-800-854-2211

(714) 278-4394 California Residents 1-800-542-6239

CABLE ADDRESS ICUSD

CUSTOMER NAME _____

STREET ADDRESS _____

CITY _____ STATE _____ ZIP _____

PHONE _____ CHARGE CARD # _____ AE Visa BA MC _____ EXP. DATE _____

C.O.D. _____ WILL CALL _____ UPS _____ POST _____ NET 10th OF THE MONTH _____ PO # _____

ALL ORDERS SHIPPED PREPAID - NO MINIMUM - COD ORDERS ACCEPTED - ALL ORDERS SHIPPED SAME DAY
OPEN ACCOUNTS INVITED - California Residents add 6% Sales Tax. PRICES SUBJECT TO CHANGE WITHOUT NOTICE.

We accept American Express / Visa / BankAmericard / Master Charge

SPECIAL DISCOUNT

Total Order	Deduc
\$35-\$99	10%
\$100-\$300	15%
\$301-\$1000	20%



Ham Radio's guide to help you find your local

Alaska

RELIABLE ELECTRONICS

3306 COPE STREET
ANCHORAGE, AK 99503
907-279-5100
Kenwood, Yaesu, DenTron, Wilson,
Atlas, ICOM, Rohn, Tri-Ex.

Arizona

HAM SHACK

4506-A NORTH 16TH STREET
PHOENIX, AZ 85016
602-279-HAMS

Serving all amateurs from beginner
to expert. Classes, sales & service.

KRYDER ELECTRONICS

5520 NORTH 7TH AVENUE
NORTH 7TH AVE. SHOPPING CTR.
PHOENIX, AZ 85013
602-249-3739

Your Complete Amateur Radio Store.

California

C & A ELECTRONIC ENTERPRISES

22010 S. WILMINGTON AVE.
SUITE 105

P. O. BOX 5232
CARSON, CA 90745
800-421-2258

213-834-5868 - Calif. Res.
Not The Biggest, But The Best —
Since 1962.

JUN'S ELECTRONICS

11656 W. PICO BLVD.
LOS ANGELES, CA 90064
213-477-1824 Trades
714-282-8682 San Diego
The Home of the One Year
Warranty — Full Service.

SHAVER RADIO

3550 LOCHINVAR AVE.
SANTA CLARA, CA 95051
408-247-4220
Atlas, Kenwood, Yaesu, KDK,
Icom, Tempo, Wilson, Ten-Tec.

Connecticut

THOMAS COMMUNICATIONS

95 KITTS LANE
NEWINGTON, CT 06111
800-243-7765
203-667-0811

Call us toll free - See our full
page ad in this issue.

Delaware

DELAWARE AMATEUR SUPPLY

71 MEADOW ROAD
NEW CASTLE, DE 19720
302-328-7728

Delaware's largest stock of amateur
radio equipment & accessories.

Florida

AGL ELECTRONICS, INC.

1800-B DREW ST.
CLEARWATER, FL 33515
813-461-HAMS

West Coast's only full service
Amateur Radio Store.

AMATEUR RADIO CENTER, INC.

2805 N.E. 2ND AVENUE
MIAMI, FL 33137
305-573-8383

The place for great dependable
names in Ham Radio.

RAY'S AMATEUR RADIO

1590 US HIGHWAY 19 SO.
CLEARWATER, FL 33516
813-535-1416

West coast's only dealer:
Drake, Icom, Cushcraft, Hustler.

Illinois

AUREUS ELECTRONICS, INC.

1415 N. EAGLE STREET
NAPERVILLE, IL 60540
312-420-8629

"Amateur Excellence"

ERICKSON COMMUNICATIONS, INC.

5456 N. MILWAUKEE AVE.
CHICAGO, IL 60630
Chicago - 312-631-5181
Illinois - 800-972-5841

Outside Illinois - 800-621-5802
Hours: 9:30-5:30 Mon, Tu, Wed &
Fri.; 9:30-9:00 Thurs; 9:00-3:00 Sat.

SPECTRONICS, INC.

1009 GARFIELD STREET
OAK PARK, IL 60304
312-848-6777

One of America's Largest
Amateur & SWL Stores.

Indiana

KRYDER ELECTRONICS

GEORGETOWN NORTH
SHOPPING CENTER
2810 MAPLECREST RD.
FORT WAYNE, IN 46815
219-484-4946

Your Complete Amateur Radio Store.
10-9 T, TH, F; 10-5 W, SAT.

Kansas

REVCOM ELECTRONICS

6247 N. HYDRAULIC
WICHITA, KS 67219
316-744-1083

New - Used HF, VHF, & Microwave
Gear. Manufacturing & Sales.

Maryland

THE COMM CENTER, INC.

9624 FT. MEADE ROAD
LAUREL PLAZA, RT. 198
LAUREL, MD 20810
800-638-4486

R. L. Drake, Ten-Tec, ICOM, Wilson,
Tempo, DenTron, Mosley, Cushcraft.

Massachusetts

TEL-COM, INC.

675 GREAT RD. RT. 119
LITTLETON, MA 01460
617-486-3040

The Ham Store of New England
you can rely on.

TUFTS RADIO ELECTRONICS

209 MYSTIC AVENUE
MEDFORD, MA 02155
617-395-8280

New England's friendliest
ham store.

Michigan

ELECTRONIC DISTRIBUTORS

1960 PECK STREET
MUSKEGON, MI 49441
616-726-3196

Dealer for all major amateur
radio product lines.

Dealers: YOU SHOULD BE HERE TOO!
Contact Ham Radio now for complete details.

Amateur Radio Dealer

Minnesota

PAL ELECTRONICS INC.
3452 FREMONT AVE. NO.
MINNEAPOLIS, MN 55412
612-521-4662
Midwest's Fastest Growing Ham
Store, Where Service Counts.

Missouri

HAM RADIO CENTER, INC.
8340-42 OLIVE BLVD.
ST. LOUIS, MO 63132
800-325-3636
For Best Price and Fast Delivery
Call toll free 1-800-325-3636

Nebraska

COMMUNICATIONS CENTER, INC.
443 NORTH 48TH ST.
LINCOLN, NE 68504
800-228-4097
Lowest Prices in the USA
on Ham Equipment.

Nevada

COMMUNICATIONS CENTER WEST
1072 RANCHO DRIVE
LAS VEGAS, NV 89106
800-634-6227
Kenwood, Yaesu, Drake and more
at discount prices.

New Hampshire

EVANS RADIO, INC.
BOX 893, RT. 3A BOW JUNCTION
CONCORD, NH 03301
603-224-9961
Icom, DenTron & Yaesu dealer.
We service what we sell.

New Jersey

ATKINSON & SMITH, INC.
17 LEWIS ST.
EATONTOWN, NJ 07724
201-542-2447
Ham supplies since "55".

BARGAIN BROTHERS ELECTRONICS
216 SCOTCH ROAD
GLEN ROC SHOPPING CTR.
WEST TRENTON, NJ 06828
609-883-2050
A million parts - lowest prices
anywhere. Call us!

METUCHEN RADIO
216 MAIN STREET
METUCHEN, NJ 08840
201-494-8350
New and Used Ham Equipment
WA2AET "T" Bruno

RADIOS UNLIMITED
P. O. BOX 347
1760 EASTON AVENUE
SOMERSET, NJ 08873
201-469-4599
New Jersey's Fastest Growing
Amateur Radio Center.

New York

AM-COM ELECTRONICS INC.
RT. 5
NORTH UTICA SHOPPING CTR.
UTICA, NY 13502
315-732-3656
The Mohawk Valley's Newest &
Largest Electronics Supermarket.

GRAND CENTRAL RADIO
124 EAST 44 STREET
NEW YORK, NY 10017
212-682-3869
Drake, Atlas, Ten-Tec, Midland,
Hy-Gain, Mosley in stock

HAM-BONE RADIO
3206 ERIE BLVD. EAST
SYRACUSE, NY 13214
315-446-2266
We deal, we trade, all major brands!

RADIO WORLD
ONEIDA COUNTY AIRPORT
TERMINAL BLDG.
ORISKANY, NY 13424
Toll Free 800-448-7914
NY { 315-337-2622
Res. { 315-337-0203
New & Used Ham Equipment.
See Warren K2IXN or Bob WA2MSH.

Ohio

AMATEUR RADIO
SALES & SERVICE INC.
2187 E. LIVINGSTON AVE.
COLUMBUS, OH 43209
614-236-1625
Antennas and Towers for
All Services.

Oklahoma

KRYDER ELECTRONICS
5826 N.W. 50TH
MacARTHUR SQ. SHOPPING CTR.
OKLAHOMA CITY, OK 73122
405-789-1951
Your Complete Amateur Radio Store

Pennsylvania

ELECTRONIC EXCHANGE
136 N. MAIN STREET
SOUDERTON, PA 18964
215-723-1200
Demonstrations, Sales, Service
New/Used Amateur Radio Equip.

"HAM" BUERGER, INC.
68 N. YORK ROAD
WILLOW GROVE, PA 19090
215-659-5900
Delaware Valley's Fastest Growing
Amateur Radio Store

HAMTRONICS, DIV. OF
TREVOSE ELECTRONICS
4033 BROWNSVILLE ROAD
TREVOSE, PA 19047
215-357-1400
Same Location for 30 Years.
Call Toll Free 800-523-8998.

LaRUE ELECTRONICS
1112 GRANDVIEW STREET
SCRANTON, PENNSYLVANIA 18509
717-343-2124
ICOM, Bird, Cushcraft, CDE,
Ham-Keys, VHF Engineering,
Antenna Specialists.

South Dakota

BURGHARDT
AMATEUR RADIO CENTER, INC.
P. O. BOX 73
WATERTOWN, SD 57201
605-886-7314
"America's Most Reliable
Amateur Radio Dealer".

Texas


AGL ELECTRONICS
3068 FOREST LANE, SUITE 309
DALLAS, TX 75234
214-241-6414 (within Texas)
Out-of-State, Call our toll-free
number 800-527-7418.

HARDIN ELECTRONICS
5635 E. ROSEDALE
FT. WORTH, TX 76112
817-461-9761
Your Full Line Authorized
Yaesu Dealer.

NEW CoaxProbe* NEW

Coaxial RF Probe for Frequency Counters and Oscilloscopes That Lets You Monitor Your Transmitted Signal Directly From the Coax Line.

Only **\$12.95**
plus .50 postage

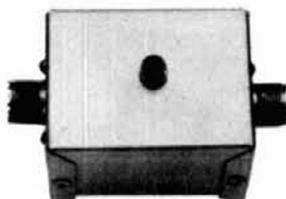

FINALLY! A RF PROBE that lets you connect into your coax cable for frequency measurements and modulation waveform checks directly from the transmitter.

JUST CONNECT THE CoaxProbe* into your transmission line and plug the output into the frequency counter or oscilloscope. Insertion loss is less than .2db so you can leave it in while you operate.

A NECESSITY IN ANY WELL-ORGANIZED HAM SHACK, the CoaxProbe* eliminates "jerry-rigging" and hassles when tapping into the coax line is desired.

A SPECIAL METHOD OF SAMPLING keeps output relatively constant with a wide variation of power. Power output of 8 watts gives .31v out, while 800 watts will give 1.8v out. (rms 3-30 khz.) 2000 watts PEP rating too!

*Trademark of CoaxProbe Co. for rf sampling device.
© 1978 by CoaxProbe Co.

USE IT ON 2 METER RIGS TO ADJUST FREQUENCY. The CoaxProbe* has a range of 1.8 to 150 mhz.

MONITOR YOUR MODULATION WAVEFORM. With an oscilloscope of proper bandwidth, you can check your modulation for flat-topping, etc. Ideal for adjusting the speech processor.

NOW YOU CAN MONITOR SIGNALS when connected to the dummy load, eliminating unnecessary on-the-air radiation.

AVAILABLE FOR THE FIRST TIME TO AMATEURS. Try it for 10 days. If not satisfied, send it back for refund (minus shipping charges).

Order today from:

CoaxProbe Co.
P.O. Box 426, Portage, MI 49081
Michigan Res. Add 4% Sales Tax

VOICE BAND EQUALIZER



Vbe
\$69.95
ppd USA

clean crisp audio

Xmit audio passband equalizer — gives punch without distortion — best on dx, yl's, problem voices — lo, mid, hi, ranges adj + 12db made in usa — performance guaranteed specify rig, mike plug or universal

P.O. Box 144, Hannacroix, N.Y. 12089
The Electronic Farm

Duns #01-048-6066

Cash plus shipping paid for clean late model Motorola GE, RCA mobiles. Base Stations, Accessories. We also sell used and reconditioned equipment. For further information contact:

Jesse La Fleur
The Communications Center
1629 Wyoming
El Paso, Texas 79902
(915) 545-1133

Call for cash quotation 16 years of fair dealing

8-POLE 350-Hz FILTER FOR SIGNAL/ONE TRANSCEIVERS \$120.00

Finally! Superior 8-Pole CW Selectivity for Drake TR-4, TR-4C, TR-4Cw

350 Hz at -6db, 850 Hz at -60db, Cuts QRM. More selective than 6-pole CW filter in new TR-4Cw which is 500 Hz at -6db, and 2000 Hz at -60db. CF-350/B \$100.00. Switch and mounting kit \$10.00

At Last! Superior 8-Pole CW Selectivity for Kenwood TS-820

MINIMAL LOSS HI SET GOOD SIGNAL-TO-NOISE. 350 Hz at 6db, 850 Hz at 60db. Cuts QRM. More selective than standard YG-BBC 6-pole CW filter which is 500 Hz at 6db, and 1800 Hz at 60 db. CK-350/B \$100.00

600 Hz 6-Pole First-IF Filter for Drake R-4C

Improve the early-stage selectivity. Eliminate those high-pitched beat notes from signals that leak around the switchable second-IF filter. Minimize the chance of strong signals overloading the second mixer, causing intermodulation and desensitization. Both the existing filter and our CF-600/B can be mounted in the receiver and relay switched to retain phone capabilities. CF-600/B \$80.00 Relay switch kit \$33.00

125 Hz 8-Pole Second-IF Filter for Drake R-4C

Still sharpest available! 300 Hz at -60db! Cuts QRM. Ideal for DX and contest work. Unexcelled under crowded band conditions. Does what no audio filter can do. More selective than audio filters. Pure selectivity in AGC loop. Unlike with audio filters, receiver gain not reduced by QRM outside passband. Yet works well with an audio filter to improve receiver performance. Plugs directly into an accessory filter socket of the R-4C. CF-125/B \$130.00

CW Operators!
Attention:
These crystal filters are for you!

All filters contain specially-treated high-Q crystals.

Sherwood Engineering Inc.
1268 South Ogden St.
Denver, Colo. 80210
(303) 722-2257

Money back if not satisfied

Add \$3 per order shipping;
\$6 overseas air

Dealer Inquiries Welcome



BUILD-IT-YOURSELF AVIONICS FOR HAM PILOTS

Free catalogue describes high technology, low cost avionics and test equipment offered in kit form. Product line includes audio panel, aircraft band two-channel transceiver, digital chronometer, navigation and communications test equipment, bench power supply, and more. Shoot us the coupon for details.

Name _____
Address _____
City _____ State _____ Zip _____

(916)
272-2203

Radio Systems Technology, Inc.

RR 5, GRASS VALLEY, CA 95945

Radio World

CENTRAL NEW YORK'S FASTEST GROWING HAM DEALER



Featuring Yaesu, Icom, Drake, Atlas, Ten-Tec, Swan, DenTron, Pace, Palomar, Alda, Midland, Wilson, KDK, MFJ, Microwave Module, Standard, Tempo, Astron, KLM, Hy-Gain, Mosley, Larsen, Cushcraft, Hustler, Mini Products, Universal and Tristao Towers. We service everything we sell! Write or call for quote. **You Won't be Disappointed.**

We are just a few minutes off the NYS Thruway (I-90) Exit 32

ONEIDA COUNTY AIRPORT TERMINAL BUILDING
ORISKANY, NEW YORK 13424

Warren
K2IXN
Call Toll Free: 1-800-448-7914

Bob
WA2MSH

New York State Residents Call: 315-337-2622 or 315-337-0203

DIGITAL READOUT

for your HAM II or III

Kit MM-1 includes key components necessary to make conversion described in article by K1DG, *Ham Radio*, January 1979, p. 54.

- AD 2020
- 10-turn pot 5K
- F9374
- 10-turn pot 1K

Allow three weeks for delivery. Send check or M.O. for \$28.95.

SUNSET ELECTRONICS
44 SUNSET DRIVE
FRAMINGHAM, MA 01701

TOP QUALITY MOBILE ANTENNAS

FROM G & C Communications

- Stainless Steel Radiator
- Heavy Nickel-Chrome Plated Brass Base and Fittings
- Mounts Come with 17' RG-58AU and PL-259 Connectors.
- Compatible with Motorola TAD and TAE Mounts.

When ordering, suffix "T" indicates complete antenna assembly with trunk lid mount. Suffix "M" indicates for hole mounting.

BM-2700T — 27-31 MHz $\frac{1}{2}$ wave base-loaded 200 watt rating. Covers 10 meters or CB. Great mobile antenna for converted CB rigs. 49" at lowest frequency and is approximately 42" when cut for ten meters. Complete with trunk lid mount assembly. **\$29.95**

BM-MATH — Extra whip (Cut one for 10 and one for CB) ... **\$5.00**

BM-4700T — Same assembly except for 47-54 MHz **\$29.95**

BM-5800T — 144-174 MHz $\frac{1}{2}$ wave gain antenna. 200 watt rating. Complete **\$29.95**

BM-MAT 58 or BM-MAT 22 — $\frac{1}{2}$ matching coils (these coils with whips allow same mounting assembly to be used on different bands) **\$14.95**

BM-5822 — 220-225 MHz $\frac{1}{2}$ wave gain antenna **\$ 29.95**

Note: Deduct \$4.00 from "T" price for "M" assemblies

Additional Information On Other Antenna Models Available

G & C Communications
Dept. HH, 730 Cottonwood
Lincoln, NE 68510

ERC PROMISES UP TO THE MINUTE STATE-OF-THE-ART DESIGN AND PERFORMANCE WE'VE DONE IT FOR 1979

FOUR SIMULTANEOUS FILTERS IN ONE FOR UNPARALLELED QRM FREE RECEPTION (SSB & CW) *PLUS A SPECIAL PATENTED CW PROCESSOR*



SL-56
AUDIO ACTIVE FILTER
(3.5 x 5.5 x 7.5 INCHES)

THE BRAND NEW SL-56 AUDIO ACTIVE FILTER SUPERCEDES OUR SL-55 IN BOTH CONCEPT AND PERFORMANCE. CONSOLIDATION OF MANY COMPONENTS HAS ALLOWED US TO MAKE 16 OPERATIONAL AMPLIFIERS (COMPARED TO 6 IN THE SL-55) INTO A FILTER GUARANTEED TO OUTPERFORM ANY OTHER AT A COST ONLY SLIGHTLY HIGHER THAN THE SL-55. THE FEATURES OF THE SL-56 ARE SO ADVANCED FROM ITS PREDECESSOR THAT CALLING IT THE SL-55A IS NOT JUSTIFIED. UNLIKE OTHER FILTERS THAT SIMPLY OFFER A CHOICE OF ONE OR TWO FILTER TYPES AT A TIME (NOTCH, BANDPASS, ETC.) SL-56 PROVIDES WHAT IS REALLY NEEDED --- THE SIMULTANEOUS ACTION OF A 6 POLE 200 HZ FIXED HIGH-PASS FILTER AND A 6 POLE 1600 HZ FIXED LOWPASS FILTER WITH A 60 DB NOTCH WHICH IS TUNABLE OVER THE 200-1600 HZ RANGE. THIS 3 FILTER COMBINATION IS UNBEATABLE FOR THE ULTIMATE IN QRM FREE SSB RECEPTION. ADJACENT CHANNEL QRM IS ELIMINATED ON THE HIGH AND LOW SIDES AT THE SAME TIME AND DOES NOT INTRODUCE ANY HOLLOWNESS TO THE DESIRED SIGNAL. ON CW THE SL-56 IS A DREAM. THE LOWPASS, HIGHPASS AND NOTCH FILTERS ARE ENGAGED ALONG WITH THE TUNABLE BANDPASS FILTER (400-1600 HZ) PROVIDING THE NEEDED ACTION OF 4 SIMULTANEOUS FILTER TYPES. THE BANDPASS MAY BE MADE AS NARROW AS 14 HZ (3dB). ADDITIONALLY, A SPECIAL PATENTED CIRCUIT FOLLOWS THE FILTER SECTIONS WHICH ALLOWS ONLY THE PEAKED SIGNAL TO "GATE ITSELF" THROUGH TO THE SPEAKER OR HEADPHONES (4-2000 OHMS). RECEIVER NOISE, RING AND OTHER SIGNALS ARE REJECTED. THIS IS NOT A REGENERATOR, BUT A MODERN NEW CONCEPT IN CW RECEPTION. THE SL-56 CONNECTS IN SERIES WITH THE RECEIVER SPEAKER OUTPUT AND DRIVES ANY SPEAKER OR HEADPHONES WITH ONE WATT OF AUDIO POWER. REQUIRES 115 VAC. EASILY CONVERTED TO 12 VDC OPERATION. COLLINS GRAY CABINET AND WRINKLE GRAY PANEL.

WARRANTED ONE YEAR FULLY RFI PROOF FULLY WIRED AND TESTED AVAILABLE NOW
\$75.00 POSTPAID IN THE USA AND CANADA. VIRGINIA RESIDENTS ADD 4% SALES TAX.

ATTN SL-55 OWNERS: THE CIRCUIT BOARD OF THE SL-56 IS COMPLETELY COMPATIBLE WITH THE SL-55 CHASSIS. OUR RETROFIT KIT IS AVAILABLE AT \$35.00 POSTPAID.



ERC INTRODUCES A BRAND NEW CONCEPT IN THE MEASUREMENT OF VSWR AND POWER ACCEPTED BY THE LOAD

REQUIRES 115 VAC AT LESS THAN 1/16 AMP.

COLLINS GRAY CABINET.
WRINKLE PANEL - BRIGHT RED LED DIGITS (.33").
DECIMAL POINT IS THE PILOT LIGHT.



1.8-30 MHz

TWO SO-239 COAX CONNECTORS ARE AT THE REAR PANEL.

DIMENSIONS 3.5 x 5.5 x 7.5 INCHES.

WEIGHT IS 2 POUNDS.

THE MODEL SL-65* (20-2000 WATTS) AND THE QRP MODEL SL-65A* (0.2-20 WATTS) DIGITALLY INDICATE ANTENNA VSWR UNDER ANY TRANSMISSION MODE -- SSB, CW, RTTY, AM Etc. THERE IS NO CALIBRATION REQUIRED AND NO CROSSED METER NEEDLES TO INTERPRET. SIMPLY LOOK AT THE READOUT AND THAT IS THE VSWR. SPEAKING NORMALLY INTO A SSB TRANSMITTER MIC. INSTANTLY CAUSES THE VSWR TO BE DISPLAYED THROUGHOUT YOUR ENTIRE TRANSMISSION. REVERSING THE POSITION OF A FRONT PANEL TOGGLE SWITCH AND THE DISPLAY INDICATES THE NET POWER (FORWARD LESS REFLECTED) THAT IS ACCEPTED BY THE ANTENNA. THE PEAK OF THE NET PEP IS DETECTED AND DISPLAYED WITHOUT FLICKER FOR ANY MODULATION TYPE. DISPLAY UPDATE IS CONSTANT YET FLICKER FREE AS YOU MAY CHANGE THE POWER ACCORDING TO YOUR VOICE. THERE IS NOTHING LIKE THIS QUALITY INSTRUMENT AVAILABLE ANYWHERE ELSE. IT IS THE ONLY VSWR-NET POWER INDICATOR THAT LETS YOU KNOW THE STATE OF YOUR ANTENNAS AND TRANSMITTED POWER AT ALL TIMES WHILE TRANSMITTING. EITHER MODEL IS A SOPHISTICATED DEVICE CONTAINING FOUR CIRCUIT BOARDS AND THIRTEEN INTEGRATED CIRCUITS.

SL-65
VSWR INDICATOR

WARRANTY ONE YEAR

SL-65
NET POWER INDICATOR

- TWO DIGIT DISPLAY SHOWS VSWR TO AN ACCURACY OF .1 FOR VALUES FROM 1.0 AND 2.2. ACCURACY IS TO .2 FOR VALUES FROM 2.3 TO 3.4 AND TO .3 FROM 3.4 TO 4.0. FROM 4.1 TO 6.2 THE INDICATION MEANS THAT VSWR IS VERY HIGH.

- THE POWER DISPLAYED IS THE DETECTED PEAK OF THE PEP FOR ANY MODULATION. THIS IS THE POWER THAT THE TRANSMITTER IS "TALKED" UP TO. DISPLAY DECAY TIME IS ABOUT ONE SECOND.

- FOR VSWR VALUES NEAR 1.0, THE POWER RANGE FOR A VALID READING IS 20 - 2000 WATTS OUTPUT. FOR HIGHER VALUES THE UPPER POWER LIMIT FOR A FLICKER FREE VALID READING IS SOMEWHAT LESS (35 - 1000 WATTS FOR VSWR AT 2.0).

- THE POWER DISPLAYED IS THAT WHICH IS ACCEPTED BY THE ANTENNA (FORWARD LESS REFLECTED).

- POWER IS DISPLAYED ON THE SAME TWO DIGITS AS VSWR IN TWO AUTORANGING SCALES. 20 TO 500 WATTS AND 500 TO 2000 WATTS. TRIPOVER AT THE 500 WATT LEVEL IS AUTOMATIC EX: A READING OF 1.2 COULD MEAN 120 OR 1200 WATTS. YOU MUST KNOW WHICH RANGE YOU ARE IN.

- DIVIDE THE ABOVE POWER LEVELS BY 100 TO OBTAIN THE PERFORMANCE OF THE SL-65A QRP MODEL.

- ACCURACY IS TO 10 WATTS IN THE LOWER RANGE AND 100 WATTS IN THE UPPER RANGE. DIVIDE POWER SPECS BY 100 FOR SL-65A.

SPECIAL AUDIO VERSION AVAILABLE FOR THE SIGHTLESS • WRITE FOR DETAILS •

PRICE: \$189.50 POSTPAID IN USA & CANADA. VA. RESIDENTS ADD 4% SALES TAX.

BOOKLET AVAILABLE AT \$2.00 REDEEMABLE TO-WARD PURCHASE.
* PATENT PENDING.

ELECTRONIC RESEARCH CORP. OF VIRGINIA
P. O. BOX 2394
VIRGINIA BEACH, VIRGINIA 23452

TELEPHONE (804) 463-2669

D & V RADIO PARTS

VARIABLE & TRIMMER CAPACITORS-RF CHOKES-AIRED WOUND COILS-TOROIDS-FEED THRU'S-TUBULAR TRIMMERS-KNOBS-WIRE-COUPPLINGS-TRANSMATCH COMPONENTS.

No minimum order-low cost shipping.
First class stamp for complete flyer.
12804 W. SARLE, FREELAND, MICHIGAN 48623

DX OPERATORS

CUSTOM CALCULATED, PERSONALIZED BEAM HEADING AND DISTANCE CHART TO OVER 330 FOREIGN CALL AREAS AND COUNTRIES BASED ON YOUR EXACT QTH. UP TO DATE FOR 1979. SEND CALL SIGN AND \$5.95 TO WILLCOMP, INC., P.O. BOX 86, SOUTH SALEM, N. Y. 10590. N. Y. RESIDENTS ADD 5% SALES TAX.

MILITARY SURPLUS WANTED

Space buys more and pays more. Highest prices ever on U.S. Military surplus, especially on Collins equipment or parts. We pay freight. Call collect now for our high offer. 201 440-8787. SPACE ELECTRONICS CO. div. of Military Electronics Corp. 35 Ruta Court, S. Hackensack, N.J. 07606

DIPOLE ANTENNA CONNECTOR

HYE-QUE (HQ-1) dipole connector has coax SO-239 socket molded into glass filled plastic body to accept coax PL-259 plug on feedline. Drip cap keeps coax fittings dry. Instructions included. Guaranteed. At your dealers or \$4.95 postpaid. Companion insulators 2/\$.99.

BUDWIG MFG. Co. PO Box 829, Ramona, CA 92065

SQ

S-f Amateur Radio Services

(213) 837-4870

4384 KEYSTONE AVE., CULVER CITY, CA. 90230

the W6TOG* RECEIVER MODIFICATION KITS

INCREASE SELECTIVITY • IMPROVE SENSITIVITY
LOWER INTERNAL NOISE
IMPROVE NOISE BLANKER OPERATION
COMBAT BLOCKING FROM LOCAL SIGNALS

TS-520 KIT	\$27.50	FT-101 SERIES KIT	\$32.50
TS-520S KIT	32.50	FR-101 SERIES KIT	34.50
TS-820 & 820S KIT	34.50	FT-301 SERIES KIT	34.50
R-599 A/D KIT	27.50	FT-901 SERIES KIT	34.50

EXPLICIT INSTRUCTIONS MAKE MODIFICATION A CINCH

IT'S MAGIC... IT'S "MAGICOM" PROCESSOR MODIFICATION KIT IMPROVES AUDIO PUNCH IMPROVES PROCESSED SPEECH QUALITY

Converts TS-820/820S speech processor from RF compressor to RF clipper \$27.50

RF speech processor for TS-520/520S \$42.50

The "MAGICOM" RF processor module provides up to

6 dB increase in output with smooth, clean,

non-distorted audio and more penetration for those pile-ups.


ENDORSED BY W6TOG AND BIG GUN DXers WORLD WIDE

*WELL KNOWN DXer WITH OVER 300 COUNTRIES CONFIRMED

All prices postpaid - in Calif. add 6% sales tax - Mastercharge & Visa accepted

SATISFACTION GUARANTEED OR MONEY REFUNDED

WANTED FOR CASH

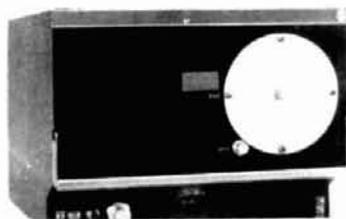

490-T Ant. Tuning Unit
(Also known as CU1658
and CU1669)



618-T Transceiver
(Also known as MRC95,
ARC94, ARC102,
or VC102)

Highest price paid for these units. Parts purchased. Phone Ted, W2KUW collect. We will trade for new amateur gear. GRC106, ARC105, ARC112 and some aircraft units also required.

We stand on our long term offer to pay ~~3%~~ ^{25%} more than any other bonafide offer.

DCO, INC.

10 Schuyler Avenue
(201) 998-4246

No. Arlington, N.J. 07032
Evenings (201) 998-6475

TR7400A "KENWOOD" OWNERS: SCANNER KIT

• Installs completely inside rig. No obtrusive external connections • Scans the complete band or only the portion you select on the MHz switch of your rig (e.g. 144-148 or 146-148 MHz) • Scan frequency is displayed on digital readout • Two miniature toggle switches supplied with kit (scanner: on-off, scan-lock may be mounted externally or on the top or bottom cover of the rig) • In the scanner OFF mode the TR-7400A behaves normally. In the scanner ON mode the scanner locks up on an occupied frequency, pauses for a preset time (3-30 seconds) and then resumes scanning. This means you can eavesdrop all over the band without lifting a finger. When you hear something interesting you flip the switch to the lock mode and the rig is ready to transmit • Scans at the rate of 50 kHz per second • Complete with detailed instructions (even for the beginner)

Introductory Offer
KIT \$39.95

Preassembled \$59.95
add \$1.50 postage and handling

FT-227 "MEMORIZER" OWNERS: SCANNER KIT

• Selectable sweep width (up to full band) • Scans only the portion of band you select • Scans at the rate of 200 kHz per second • Switch modification on mike allows you to scan past, or lock on, any occupied frequency • Complete kit with detailed instructions • Installs inside rig; no obtrusive external connections • Rig can easily be returned to original condition whenever desired • Scans to preset limits and reverses • Automatic bypass of locked frequency in 3-1/2 seconds unless you press lock-on switch • You can eavesdrop all over the band without lifting a finger.

KIT \$34.95

Preassembled and tested \$54.00
add \$1.50 postage and handling

IC-22S SCANNER KITS

also available
Kit \$34.95; \$54.00 Assembled add \$1.50 postage and handling

dealer inquiries invited

AED ELECTRONICS

750 LUCERNE RD., SUITE 120, MONTREAL, QUEBEC, CANADA H3R 2H6
TEL. 514-737-7293

THE BIG SIGNAL

UNADILLA "W2AU" Baluns

DEMANDED BY
PROFESSIONALS
WORLD-WIDE
OVER 12 YEARS

- The Original Lightning Arrest
- 650# Strength
- Stainless Hardware
- Sealed
- GUARANTEED



FULL-POWER, QUALITY HAM ANTENNA PARTS

AT YOUR DEALER

- BALUNS · TRAPS · INSULATORS
- QUAD PARTS · ANTENNA KITS
- BOOM / MAST MOUNTS · WIRE
- CABLE · CONNECTORS

WRITE FOR FULL CATALOG
[Enclose 30c Stamps]

MICROWAVE FILTER UNADILLA/REYCO DIVISION [Dept. HR]
JFC COMPANY INC.
8743 KINNE STREET EAST SYRACUSE NEW YORK 13217

DEALERS WANTED - OVER 300 WORLD-WIDE

NEW THE DRY WET CELL


A 12 volt lead-acid battery that doesn't care what position it's in - new from Portable Communications. Sealed, small, powerful, rechargeable, and convenient, this battery may be just the answer you've been looking for. Look -

- 2.5 ampere hours
- 70% of full capacity after 150 days at 25°C.
- rechargeable with most home charging units or power supplies
- only 8" x 3 3/8" x 1 1/2" (approximate outside dimensions)
- weight approximately 2 3/4 lbs.
- 1 year warranty

So whether you're converting mobile equipment to portable, looking for long-lived, trouble-free power for repeaters, or back-up power for your equipment, at \$49.95, this battery could be your best investment. Send your check (add \$1.50 postage), or ask for our free brochure. (Conn. residents add sales tax.)

Portable Communication
Supply, Inc. P.O. Box 345,
Trumbull, CT. 06611

TOUCH-TONE® DECODER MODULE

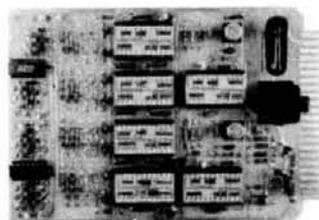

MODEL DTMF-8
4.5" x 6.5"

- Excellent building block for amateur control systems
- Hybrid active filters throughout. No PLL's!
- 40db dynamic range
No gain adj. necessary
- Min. 20db twist allowable
- Std. AT&T tones
- Decodes all 8 touch-tone frequencies
- 8 open collector outputs supplied to interface with any logic system
- 10K Ohm transformer isolated input stage
- 11-15 VDC operation

ONLY

\$179.95 post paid
CA Res. Add 6% Sales Tax



Call or write
for detailed
specification sheet



ABLETRONICS

8131 FOOTHILL BLVD.
CUCAMONGA, CA 91730
714/981-3473

SEE
HAM
MART
THIS ISSUE FOR
YOUR LOCAL
DEALER!

More Details? CHECK — OFF Page 118

ALL BAND TRAP ANTENNAS!



PRETUNED - COMPLETELY ASSEMBLED - ONLY ONE NEAT SMALL ANTENNA FOR UP TO 6 BANDS! EXCELLENT FOR CONGESTED HOUSING AREAS - APARTMENTS LIGHT - STRONG - ALMOST INVISIBLE!

FOR ALL MAKES & MODELS OF AMATEUR TRANSCEIVERS - TRANSMITTERS - GUARANTEED FOR 2000 WATTS SSB 100 WATTS CW. FOR NOVICE AND ALL CLASS AMATEURS!

COMPLETE AS SHOWN with 90 ft. RG58U-52 ohm feedline, and PL259 connector, insulators, 30 ft. 300 lb. test dacron end supports, center connector with built in lightning arrester and static discharge - molded, sealed, weatherproof, resonant traps 1"X6" - you just switch to band desired for excellent worldwide operation - transmitting and receiving! WT. LESS THAN 5 LBS.

160-80-40-20-15-10 bands 2 trap--149 ft. with 90 ft. RG58U - connector - Model 777BU ... \$59.95
80-40-20-15-10 bands 2 trap --- 102 ft. with 90 ft. RG58U - connector - Model 998BU ... \$54.95
40-20-15-10 bands 2 trap --- 54 ft. with 90 ft. RG58U coax - connector - Model 1001BU ... \$53.95
20-15-10 bands 2 trap --- 26 ft. with 90 ft. RG58U coax - connector - Model 1007BU ... \$52.95

SEND FULL PRICE FOR POST PAID INSURED DEL. IN USA. (Canada is \$5.00 extra for postage - clerical - customs - etc.) or order using VISA Bank Americard - MASTER CHARGE - AMER. EX-PRESS. Give number and ex. date. Ph 1-308-236-5333 9AM - 6PM week days. We ship in 2-3 days. PRICES MAY INCREASE SO - ORDER NOW AND SAVE! All antennas guaranteed for 1 year. Money back trial! Made in USA. FREE INFO. AVAILABLE ONLY FROM.

WESTERN ELECTRONICS

Dept. AR-4

Kearney, Nebraska, 68847



CRYSTAL FILTERS The Heart of your Set Get the BEST for Less!

ONLY
\$5.50
MOST TYPES

YAESU — KENWOOD — HEATH — and now DRAKE (R-4C)!

FOX-TANGO continues to expand its quality-line of 8-pole filters, made up entirely of specially-treated, high Q crystals. Custom-made for each set with ultimate rejection of over 80 dB and superior shape factors, these filters are unavailable from other sources. Only FOX-TANGO gives owners of the most popular brands of ham gear a choice of drop-in filters closer to their needs than the limited number of 6-pole (or less) units offered as extra-cost options by most manufacturers. In addition, for the Yaesu and Kenwood lines we offer specially designed Diode Switching Boards which permit inboard mounting of up to two filters more than those for which the manufacturer provides room. Thus, either now or in the future, a set could be provided with a sharp (250 Hz) and/or standard (500 Hz) CW filter, and/or a narrow (1800 Hz) SSB in addition to the regularly supplied SSB filter — all switch selectable. This provides superior variable bandwidth selection without the need for buying an expensive new model to provide it. In these inflationary times, it is sound economics to up-grade your present set. FOX-TANGO makes it easy — and relatively inexpensive. Order with confidence: satisfaction is guaranteed on a money-back basis. Incidentally even our current line of filters will fit many other brands of home-brew rigs. Check the specifications or write us about custom-built units for most rigs. (COMING: YF455 F250 — 250 Hz CW for 75S-3B/C — order yours now for fastest delivery)

FOX-TANGO CRYSTAL FILTER SPECIFICATIONS

	FILTER NO. YF-	USED FOR	CENTER FREQUENCY kHz	BANDWIDTH — Hz		INSERTION LOSS dB	TERMINAL Z (IN-OUT) Ω/pF	CASE SIZE SEE BELOW	SEE NOTE	
				-6 dB	-60 dB					
YAESU	FT-101 FR-101	31H250	CW-N	3179.3	250 ± 50	< 750	< 9	500Ω	A	1
		31H500	CW	3179.3	500 ± 50	< 1200	< 7	500Ω	A	2
		31H1.8	SSB-N	3180	1800 ± 100	< 3500	< 6	500Ω	B	3
		31H2.4	SSB-F	3180	2400 ± 100	< 4200	< 6	500Ω	B	4, 6
		31H6.0	AM	3180	6000 ± 500	< 11K	< 6	500Ω	A	5
	FT-301 FT-7	91H250	CW-N	8999.3	250 ± 50	< 750	< 10	500Ω	C	1
	91H500	CW	8999.3	500 ± 50	< 1400	< 8	500Ω	C	2	
	90H1.8	SSB-N	9000	1800 ± 100	< 3500	< 6	500Ω	C	3	
	90H2.4	SSB-F	9000	2400 ± 100	< 4200	< 6	500Ω	C	6	
	FT-901 FT-101Z	89H250	CW-N	8988.3	250 ± 50	< 750	< 10	500Ω	C	1
		89H500	CW	8988.3	500 ± 50	< 1400	< 8	500Ω	C	2
KENWOOD	TS-520 R-599	33H250	CW-N	3395	250 ± 50	< 750	< 9	4.7K/33pF	B	1
		33H400	CW	3395	400 ± 50	< 1200	< 8	4.7K/33pF	B	7
		33H1.8	SSB-N	3395	1800 ± 100	< 3500	< 6	4.7K/33pF	B	3
TS-820	88H250	CW-N	8830.7	250 ± 50	< 750	< 10	470/5pF	D	1	
	88H400	CW	8830.7	400 ± 50	< 1400	< 9	470/5pF	D	7	
	88H1.8	SSB-N	8830	1800 ± 100	< 3500	< 6	470/5pF	D	3	
HEATH	All Except SB/HW 104	33H250	CW-N	3395.4	250 ± 50	< 750	< 9	2KΩ	E	1
		33H400	CW	3395.4	400 ± 50	< 1200	< 8	2KΩ	E	8
		33H2.1	SSB	3395	2100 ± 100	< 3500	< 6	2KΩ	E	9
DRAKE	R-4C	56H8.0	CW/SSB	5645 ± 150	8000 ± 500	< 13K	< 3	500Ω	F	10, 11
		56H800	CW	5645 ± 150	800 ± 100	< 1800	< 5	500Ω	C	10, 12
		56H125	CW-N	5695	125 ± 50	< 350	< 13	50Ω	G	10, 12

All filters, except Drake, are \$55 each. For Drake prices, see ad page 43. Prices include airmail postpaid to U.S., Canada and Mexico. For overseas airmail, add \$3.

CASE SIZES

(LWH in mm)
A 45 x 23 x 28
B 50 x 25 x 25
C 40 x 20 x 21
D 50 x 18 x 18
E 57 x 24 x 25
F 57 x 24 x 18
G 57 x 24 x 21

NOTES

- 1 Sharp CW Filter for DX and Contest work
- 2 Use instead of optional 600 Hz (6 pole) unit
- 3 For narrow SSB to reduce QRM
- 4 Use instead of XF-30A (6 pole) in early units
- 5 Superior to XF-30B (6 pole) AM unit
- 6 Used in G3LLL RF Speech Processors
- 7 Use instead of optional 500 Hz (6 pole) unit
- 8 Use instead of optional 400 Hz (4 pole) unit
- 9 Superior replacement for standard SSB unit
- 10 For detailed description and prices see ad page 43
- 11 Also known as GUF-1
- 12 Also known as GUF-2S

VISA & MASTER CHARGE Accepted

Dealer Inquiries Welcomed

Florida residents add 4% (sales tax)
See our other ad page 43 this issue



FOX-TANGO CORP.
Box 15944, W. Palm Beach, FL 33406

Advertisers check-off

... for literature, in a hurry — we'll rush your name to the companies whose names you "check-off"

Place your check mark in the space between name and number. Ex: Ham Radio 234

INDEX

AED _____ 710	Kantronics * _____
Abletronics _____ 770	Kenwood * _____
Alliance _____ 700	Long's _____ 468
Aluma _____ 589	Lunar _____ 577
Antek _____ 733	MFJ _____ 082
Astron _____ 734	Madison * _____
Atlas _____ 198	Microwave Filter _____ 637
Barrett * _____	J. W. Miller _____ 745
Barry * _____	Milo _____ 736
Bauman _____ 017	Monroe _____ 715
Budwig _____ 233	Oak Hill Acad. A.R.S. * _____
Bullet _____ 328	P.C. Elec. _____ 766
Cal Crystal _____ 709	Palomar Eng. * _____
CoaxProbe _____ 726	Port. Comm. Sup. _____ 769
Communications Center _____ 534	Callbook _____ 100
Comm. Research _____ 753	Radio Elec. _____ 767
Comm. Spec. _____ 330	Radio Sys. Tech. _____ 422
Creative Elec. _____ 751	Radio World * _____
Crystal Banking _____ 573	Ramsey _____ 442
Curtis Electro _____ 034	Rockwell Collins _____ 258
Cushcraft * _____	S.F.A.R.S. _____ 640
D&V Radio * _____	SST _____ 375
DCO _____ 324	Sabtronics * _____
DSI _____ 656	Howard W. Sams _____ 104
Dames Comm. _____ 551	Schober Organ _____ 762
Data Signal _____ 270	Securitron _____ 461
Drake * _____	Sherwood _____ 435
E.T.O. * _____	Slep _____ 232
Electrocom _____ 663	Space _____ 107
Electronic Farm * _____	Spec. Int. _____ 108
Elec. Research Virginia * _____	Sunset Elec. _____ 768
Erickson * _____	Swan _____ 111
Fox-Tango _____ 657	TPL _____ 240
G & C Comm. _____ 754	Telrex _____ 377
GLB _____ 552	Ten-Tec * _____
GL Enterprises * _____	Texas RF Distr. _____ 763
Gilfer _____ 207	The Communication Center * _____
Gray _____ 055	Thomas Comm. _____ 730
Gregory * _____	Tri-Ex _____ 116
Group III _____ 701	VHF Eng. _____ 121
Gull _____ 635	Van Gorden _____ 737
Hal * _____	Vanguard Labs _____ 716
Hal-Tronix _____ 254	Varian _____ 043
H. R. B. _____ 150	Webster _____
Heath _____ 060	Assoc. _____ 423
Henry _____ 062	Western * _____
Hy-Gain _____ 064	Whitehouse * _____
Icom _____	Willcomp _____ 764
Integ. Circuits _____ 518	Wilson _____ 123
Int. Crystal _____ 066	Yaesu _____ 127
Jameco _____ 333	
Jan _____ 067	
Jones _____ 626	

*Please contact this advertiser directly.
Limit 15 inquiries per request.

April, 1979

Please use before May 31, 1979

Tear off and mail to
HAM RADIO MAGAZINE — "check off"
Greenville, N. H. 03048

NAME _____


CALL _____

STREET _____

CITY _____

STATE _____ ZIP _____

MADISON APRIL SHOWERS

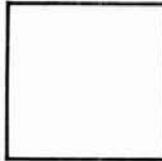

% WRITE IN
YOUR
BEST QUOTE
FROM THE
"800 GANG."

NOW, LIST THE EQUIPMENT YOU WANT IN THE SPACES PROVIDED BELOW, CUT OUT THIS AD, AND SEND IT TO US WITH YOUR NAME, ADDRESS AND TELEPHONE NUMBER. WE WILL WRITE OR CALL (CHECK ONE) YOU BACK AS SOON AS POSSIBLE WITH THE MADISON QUOTE.

(HINT: DON'T GO BELOW OUR COST).

WE HAVE AN IN-DEPTH STOCK AND LARGE INVENTORY OF MAJOR LINES AND ACCESSORIES.

PLEASE QUOTE ON:

1. _____

2. _____

3. _____

4. _____

NAME _____

ADDRESS _____

TELEPHONE _____

ZIP _____

TERMS: ALL PRICES FOB HOUSTON. PRICES SUBJECT TO CHANGE WITHOUT NOTICE. ALL ITEMS GUARANTEED. SOME ITEMS SUBJECT TO PRIOR SALE. SEND LETTERHEAD FOR AMATEUR DEALER'S PRICE LIST. TEXAS RESIDENTS ADD 6% TAX. PLEASE ADD POSTAGE ESTIMATE.

MADISON ELECTRONICS SUPPLY, INC.

1508-D McKINNEY HOUSTON, TEXAS 77002
713/658-0268 NITES 713/497-5683

Advertisers iNdex

AED Electronics	116
Abletronics	117
Alliance Mfg. Company	63
Aluma Tower Co.	96
Antek, Inc.	98
Astron Corporation	96
Atlas Radio	31
Barrett Electronics	110
Barry Electronics	90
R. H. Bauman Sales Co.	102
Budwig Mfg. Co.	115
Bullet	102
Cal Crystal Lab, Inc.	98
CoaxProbe Co.	114
Communications Center	105
Communication Research, Inc.	98
Communications Specialists	10, 11
Creative Electronics	100
Crystal Banking Service	100
Curtis Electro Devices	104
Cushcraft	64, 65
D & V Radio Parts	115
DCO, Inc.	102, 116
DSI Instruments	54, 55
Dames Communications Systems	108
Data Signal, Inc.	88
Drake Co., R.L.	67
Ehrhorn Technological Operations	119
Electrocom Industries	94
The Electronic Farm	114
Electronic Research Corp. of Virginia	115
Erickson Communications	108
Fox-Tango Corp.	43, 117
G & C Communications	100, 115
GLB	98
GL Enterprises	49
Gilfer Associates	84
Gray Electronics	100
Gregory Electronics	52
Group III Sales Company	110
Gull Electronics	103
Hal Communications Corp.	22
Hal-Tronix	25
Ham Radio's Bookstore	117
Heath Company	59
Henry Radio Stores	Cover II
Hy-Gain Electronics	1
Icom	5
Integrated Circuits Unlimited	111
International Crystal	89
Jameco Electronics	107
Jan Crystals	96
Jones, Marlin P. & Assoc.	106
Kantronics	72
Trio-Kenwood Communications, Inc.	7, 60, 61
Long's Electronics	120
Lunar Electronics	79
MFJ Enterprises	2
Madison Electronic Supply	43, 52, 94, 118
Microwave Filter, Inc.	116
J. W. Miller Division, Bell Industries	90
Milo Associates	110
Monroe Electronics, Inc.	90
Oak Hill Academy Amateur Radio Session	106
P. C. Electronics	106
Palomar Engineers	84
Portable Communications Supply	116
Radio Amateur Callbook	104
Radio Electronics	101
Radio Systems Technology, Inc.	114
Radio World	114
Ramsey Electronics	91
Rockwell International, Collins Division	77
S-F Amateur Radio Service	116
SST Electronics	94
Sabtronics International, Inc.	97
Howard W. Sams & Co., Inc.	109
Schober Organ Corp.	104
Securitron	108
Sherwood Engineering	114
Slep Electronics	110
Space Electronics	115
Spectrum International	83
Sunset Electronics	114
Swan Electronics	95
TPL Communications	49
Telrex Laboratories	96, 102
Ten-Tec	9
Texas RF Distributors	99
The Communication Center	114
Thomas Communications	44, 45
Tri-Ex Tower Corporation	73
VHF Engineering, Div. of Brownian	85
Van Gorden Engineering	110
Vanguard Labs	90
Varian, Eimac Division	Cover IV
Webster Associates	84
Western Electronics	117
Whitehouse, G.R. & Co.	100
Willcomp, Inc.	115
Wilson Electronics	53
Yaesu Electronics Corp.	Cover III

WHY WISH YOU'D BOUGHT ALPHA?



IS SOMETHING ELSE "JUST AS GOOD?"

New **ALPHA** owners often tell us, "I wish I'd saved my time and money and bought an **ALPHA** in the first place." Why not benefit from their experiences? Compare first!

TRY TO GET ANY OTHER MANUFACTURER TO TELL YOU - IN WRITING - THAT IT'S SAFE TO OPERATE HIS DESK TOP LINEAR AT A FULL D-C KILOWATT . . . SAY FOR 24 HOURS KEY-DOWN. OR, ASK HIM FOR A FULL YEAR WRITTEN WARRANTY. LOTS OF LUCK!

YOUR NEW ALPHA WILL HAPPILY AND COOLLY RUN THAT KILOWATT KEY-DOWN . . . FOR 24 DAYS IF YOU WISH. AND YOU'LL BE PROTECTED BY ETO'S UNMATCHED WARRANTY FOR TWO YEARS. WE PUT IT IN WRITING ALL THE TIME. IT'S THE WAY WE BUILD AND WARRANT EVERY ALPHA!

The new **ALPHA's** are the best we've ever built. Nothing else even approaches an **ALPHA's** combination of power, convenience, quality, and owner protection. The ETO/**ALPHA** two year limited warranty offers you eight times as much protection as the industry-standard 90 day warranty.

The new **ALPHA 374A** adds NO-TUNE-UP operation to all the other traditional **ALPHA** qualities and capabilities. You can hop instantly from one HF band to another, with full maximum legal power and with little or no amplifier tune-up at all! (If new amateur bands are added, you can manually adjust your **ALPHA** to work them, too.)

In 1974 the original **ALPHA 374** set a standard of high power convenience that has remained unmatched since. Despite its small size, not even one '374 owner ever burned out a power transformer. Impressive? The new '374A has an even huskier power supply. And it has ETO's ducted-air system with acoustically-isolated centrifugal blower to insure cool, whisper-quiet operation.

Before you get serious about any other brand of linear, compare its convenience and quality, its transformer heft, its cooling system efficiency and noise level - and its warranty - with the **ALPHA's**. Be sure to ask around about its reputation.

Call or write for detailed literature and thoroughly check out all the great new **ALPHA's** . . . so you don't make a mistake.

EHRHORN TECHNOLOGICAL OPERATIONS, INC.
BOX 708, CAÑON CITY, CO 81212 (303) 275-1613

MOBILE VALUES FROM LONG'S

1-800-633-3410



NEW!

KENWOOD TR-7625 25 watt 2m transceiver

Featuring: memory channel, mode switch for simplex or switching transmit freq. up or down, full 4 MHz coverage, 800 channels, 5 kHz offset switch, MHz selector switch, LED, unlock indicator.

425.00 Call for quote.



ICOM IC-211 2m transceiver

• 144 to 148 MHz coverage • Modes: SSB, CW, FM • LSI synthesizer PLL • 4-digit LED readout • Pulse-type noise blanker • VOX w/adjustable gain • SWR bridge • CW monitor • Automatic power control • AC/DC power supplies • Antenna impedance: 50 ohms unbalanced • TX output: 10W PEP.

899.00 Call for quote.



YAESU CPU-2500RK 2m FM transceiver

800 PLL channels, auto scan over entire 2m band, 4 memories, tone burst, 3/25 watts, fixed ± 600 KHz programmable offsets, 13.8 VDC at 8 amps continuous. Comes with keyboard mic for remote input, scanning control, aux. repeater split, and 2 tone input for auto patch or control link.

585.00 Call for quote.



YAESU FT-227RA The "Memorizer" transceiver

One knob channel selection for 800 channels, frequency 144-148 MHz, 4-digit LED readout, fully synthesized frequency control, selectable 10 watt Hi/1 watt Low output, 4 memories, touch control on mic for scanning, scan selectable for clear or busy channels.

399.00 Call for quote.



KENWOOD TS-700SP all mode 2m transceiver

Covers the entire 2 meter band. The features are SSB, CW, FM, AM and semi-break-in CW. Also side tone monitor digital freq. readout, receiver preamp and 600 KHz repeater offset op (144.5-145.5 Hz) 10 watts RF output, AC/DC pow. supply.

799.00 Call for quote.



TUCH COM 1215 encoding mic

500 ohm low impedance mic, needing no battery or modification to use with the ICOM 22S, 245, 211, 215, and 280.

49.00 Call for yours today!



CUSHCRAFT AMS-147 FM mobile 2m mag mount antenna

A $\frac{1}{2}$ wave length antenna with 3 dBi gain, low SWR operation over 146-148 MHz FM band. Move center freq. ± 1.5 MHz. Matched to 50 ohms. Built in connector takes PL-259.

34.95 Call for yours today.



ICOM IC-280 remotable 2m FM mobile

Frequency 143.90-148.11 MHz • Power: 10 watts Hi, 1 watt adj. Low • Power requirements: 13.8 VDC at 2.5 amps • Main PLL control head may be detached and remotely mounted • With micro-processor, stores 3 frequencies • Easy to read LED's.

480.00 Call for quote.



Long's Electronics



MAIL ORDERS: P.O. BOX 11347 BIRMINGHAM, AL 35202 • STREET ADDRESS: 2808 7TH AVENUE SOUTH BIRMINGHAM, ALABAMA 35233

Remember, you can Call Toll Free: **1-800-633-3410** in the U.S.A. or call **1-800-292-8668** in Alabama for our low price quote. Store hours: 9:00 AM til 5:30 PM, Monday thru Friday.

ALL NEW

FT-101ZD

HIGH-PERFORMANCE HF TRANSCEIVER

Today's technology, backed by a proud tradition, is yours to enjoy in the all-new FT-101ZD transceiver from YAESU. A host of new features are teamed with the FT-101 heritage to bring you a top-dollar value. See your dealer today for a "hands on" demonstration of the performance-packed FT-101ZD.


Cast front panel, plus heavy
/ case

1/2-in. fully adjustable, VOX
circuitry

1/2-in. RF speech processor
more "talk power" when you
speak

1/2-in. threshold adjustable,
sense blanker

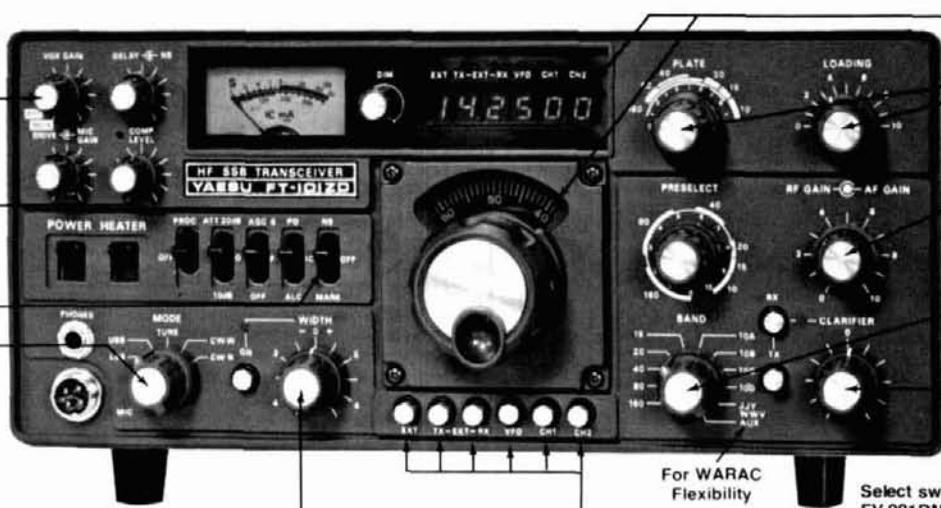Switched for SSB and CW
operation. Choice of wide or
narrow bandwidth for CW (with
optional CW filter installed)



Continuously variable IF band-
width: 300 Hz to 2.4 KHz

Digital plus analog frequency
readout. Digital display resolu-
tion to 100 Hz

Rugged 6146B final amplifier
tubes with RF negative feed-
back

RF and AF gain controls located
on concentric shafts for
operator convenience

Full band coverage: 160 through
10 meters, plus WWV/JJY
(receive only)

TX, RX, or transceive frequency
offset from main dial frequency

For WARAC
Flexibility

Select switches for use with
FV-901DM synthesized scan-
ning VFO (option). FV-901DM
provides scanners plus 40 fre-
quency memory bank.

SPECIFICATIONS

TRANSMITTER

PA Input Power:

180 watts DC

Carrier Suppression:

Better than 40 dB

Unwanted Sideband Suppression:

Better than 40 dB @ 1000 Hz, 14 MHz

Spurious Radiation:

Better than 40 dB below rated output

Third Order Distortion Products:

Better than -31 dB

Transmitter Frequency Response:

300-2700 Hz (-6 dB)

Stability:

Less than 300 Hz in first 30 minutes after 10

min. warmup; less than 100 Hz after 30 minutes

over any 30 min. period

Negative Feedback: 6 dB @ 14 MHz

Antenna Output Impedance:

50-75 ohms, unbalanced

GENERAL

Frequency Coverage:

Amateur bands from 1.8-29.9 MHz, plus

WWV/JJY (receive only)

Operating Modes:

LSB, USB, CW

Power Requirements:

100/110/117/200/220/234 volts AC,

50/60 Hz; 13.5 volts DC (with optional DC-DC

converter)

Power Consumption:

AC 117V: 75 VA receive (65 VA HEATER OFF)

285 VA transmit; DC 13.5V: 5.5 amps receive

(1.1 amps HEATER OFF), 21 amps transmit

Size:

345 (W) x 157 (H) x 326 (D) mm

Weight:

Approximately 15 kg.

COMPATIBLE WITH

FT-901DM ACCESSORIES

RECEIVER

Sensitivity:

0.25 uV for S/N 10 dB

Selectivity:

2.4 KHz at 6 dB down, 4.0 KHz at 60 dB down

(1.66 shape factor); Continuously variable be-

tween 300 and 2400 Hz (-6 dB); CW (with

optional CW filter installed); 600 Hz at 6 dB

down, 1.2 KHz at 60 dB down (2:1 shape factor)

Image Rejection:

Better than 60 dB (160-15 meters); Better than

50 dB (10 meters)

IF Rejection:

Better than 70 dB (160, 80, 20-10 m); Better

than 60 dB (40 m)

Audio Output Impedance:

4-16 ohms

Audio Output Power:

3 watts @10% THD (into 4 ohms)



Price And Specifications Subject To
Change Without Notice Or Obligation

YAESU The radio.



379X

YAESU ELECTRONICS CORP., 15954 Downey Ave., Paramount, CA 90723 ● (213) 633-4007
YAESU ELECTRONICS Eastern Service Ctr., 9812 Princeton-Glendale Rd., Cincinnati, OH 45246

Two EIMAC 3-500Zs provide the punch in Kenwood's new amplifier.


Kenwood chooses EIMAC for trouble-free service.

The new heavy-duty Kenwood TL-922A linear amplifier provides 2 kW PEP input for SSB service and 1 kW input for CW, RTTY, and SSTV operation.

Kenwood chose two EIMAC 3-500Z high-mu triodes to do the job. With a total of 1000 watts anode dissipation, the two 3-500Zs coast along to provide trouble-free, long-life service.

For more information

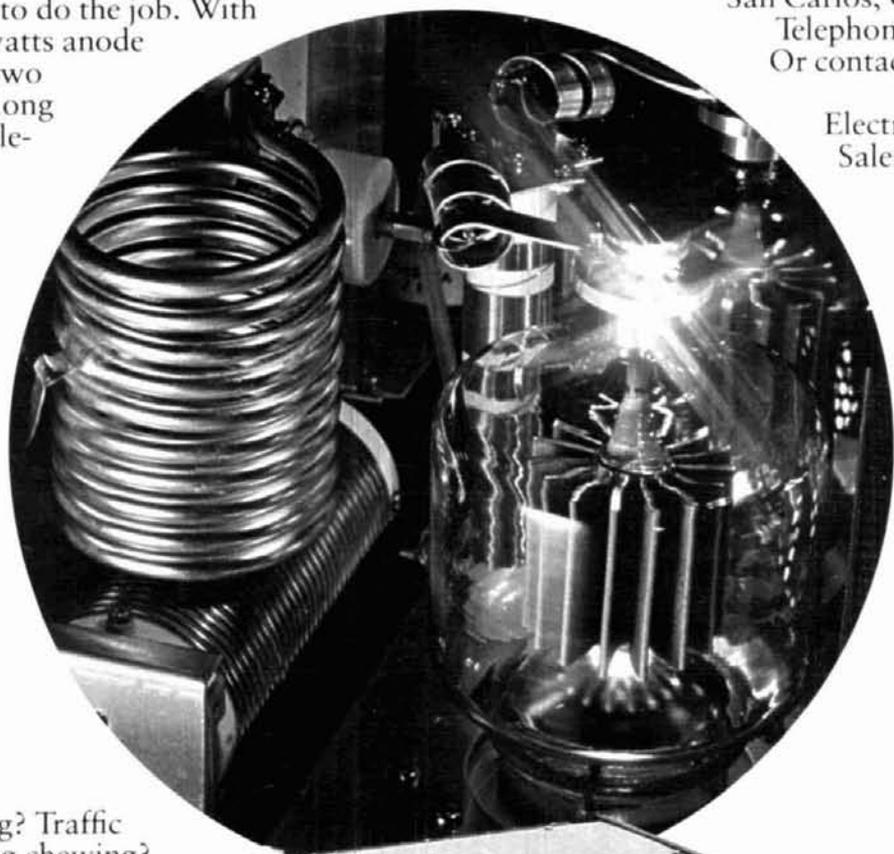Send for the EIMAC Quick Reference catalog covering the complete line of EIMAC products and for the 3-500Z Data Sheet. Learn why the important manufacturers of communication equipment choose EIMAC. Varian, EIMAC Division, 301 Industrial Way, San Carlos, California 94070. Telephone (415) 592-1221. Or contact any of the more than 30 Varian Electron Device Group Sales Offices throughout the world.



What's your pleasure?

DX chasing? Traffic nets? RTTY? Rag chewing? SSTV? The EIMAC 3-500Z provides the power when you need it, with ample safety margin. Value wise amateurs always look for the EIMAC power tube for reliability. And equipment manufacturers, such as Kenwood, choose EIMAC for leadership in power tube technology.



For new
ideas in
electronics
read
**Radio-
Electronics**



Save almost 1/2 off the newsstand on RADIO-ELECTRONICS, the magazine which keeps you up-to-date with the newest ideas and innovations in electronics. (If you already are a subscriber, do a friend a favor and pass this subscription card along to him.)

check offer preferred

- 1 Year—12 issues **ONLY \$7.77**
(Save \$7.23 on newsstand or \$2.21 off basic sub. price)
- 2 Years—24 issues **SAVE MORE \$15.50**
(Save \$14.50 on newsstand or \$3.50 off basic sub. price)
- Payment enclosed Bill Me Check here if you are extending or renewing your subscription
- Check here if this is a new subscription

Name _____

Company Name (If applicable) _____

Address _____

City _____ State _____ Zip _____

Extra Postage: Canada \$3.00
per year, all other countries \$5.00 per year.

IMPORTANT
HAM RADIO MAGAZINE
4HRC



NO POSTAGE
NECESSARY
IF MAILED
IN THE
UNITED STATES

BUSINESS REPLY MAIL

FIRST CLASS PERMIT NO. 597 BOULDER, COLORADO
POSTAGE WILL BE PAID BY ADDRESSEE

Radio-Electronics®

SUBSCRIPTION SERVICE

P.O. Box 2520

BOULDER, COLORADO 80321



For new
ideas in
electronics
read
**Radio-
Electronics**

