

MARCH • 1955



25 CENTS

Lawrence W. Dams

PF
PHOTOFACT[®]

REPORTER

for the Electronic Service Industry

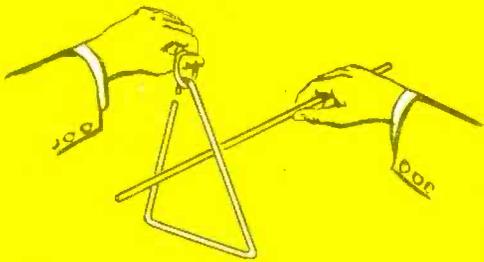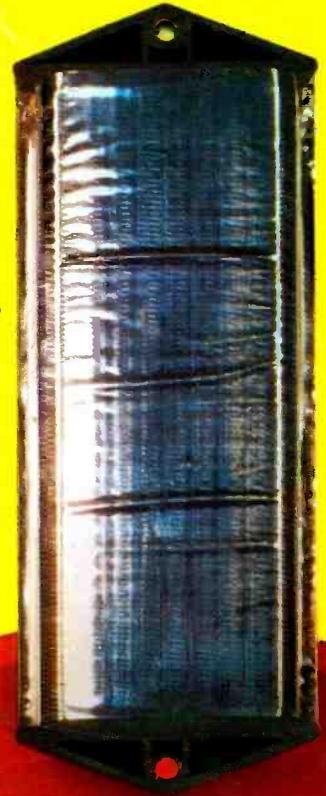


COLOR TV
TRAINING SERIES
(Part X)

ELECTROSTATIC SPEAKERS

see—

**EXAMINING
DESIGN FEATURES**

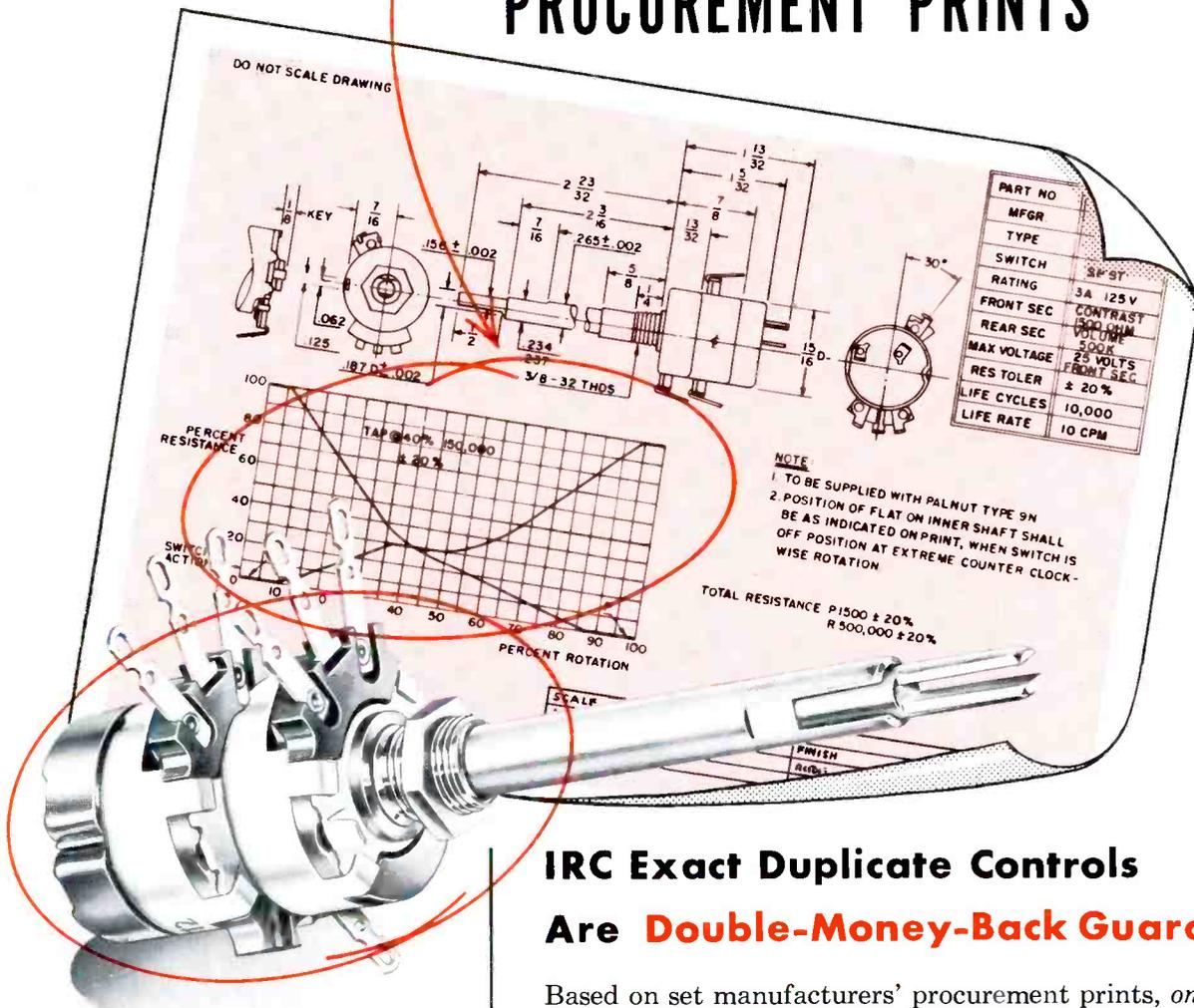ASSURED ELECTRICAL ACCURACY BASED ON MANUFACTURERS' PROCUREMENT PRINTS



**ONLY IRC GUARANTEES
ACCURATE ELECTRICAL OPERATION
AND SATISFACTORY MECHANICAL FIT
OR DOUBLE-YOUR-MONEY-BACK**

Electrical specifications of this typical manufacturer's procurement print are exactly duplicated by IRC's QJ-412 control (shown). CONCENTRIKIT assembly includes P1-206 and R1-223 shafts with B17-109 and B13-133X Base Elements and 76-1 Switch.

IRC Exact Duplicate Controls Are Double-Money-Back Guaranteed

Based on set manufacturers' procurement prints, *only* IRC Exact Duplicate Controls are double-money-back guaranteed for accurate electrical operation. This firm guarantee applies to both IRC factory-assembled Exact Duplicates *and* universal CONCENTRIKIT equivalents.

Set manufacturers' electrical specifications are closely followed. Resistance values are carefully selected to match. Tapers are watched carefully; IRC doesn't arbitrarily substitute tapers to obtain wide coverage. For exact duplicate controls of guaranteed accuracy, specify IRC. Most Service Technicians do.



Wherever the Circuit Says ~~~

INTERNATIONAL RESISTANCE CO.

423 N. Broad Street, Philadelphia 8, Pa.
In Canada: International Resistance Co., Ltd., Toronto, Licensee

the **one** line
 that has **everything**
C·D·R ROTORS

a model for
 every need

Powerful beyond any need!





featuring the
**SHARPEST TUNING
 AUTOMATIC ROTOR**

model AR-2 ... complete, automatic rotor with thrust bearing. Handsome modern design cabinet, uses 4 wire cable.

model AR-1 ... same as AR-2 without thrust bearing.

model TR-12
 ... a special combination value consisting of complete rotor, including thrust bearing. Handsome, modern cabinet with meter control dial, uses 4 wire cable.

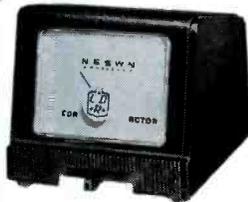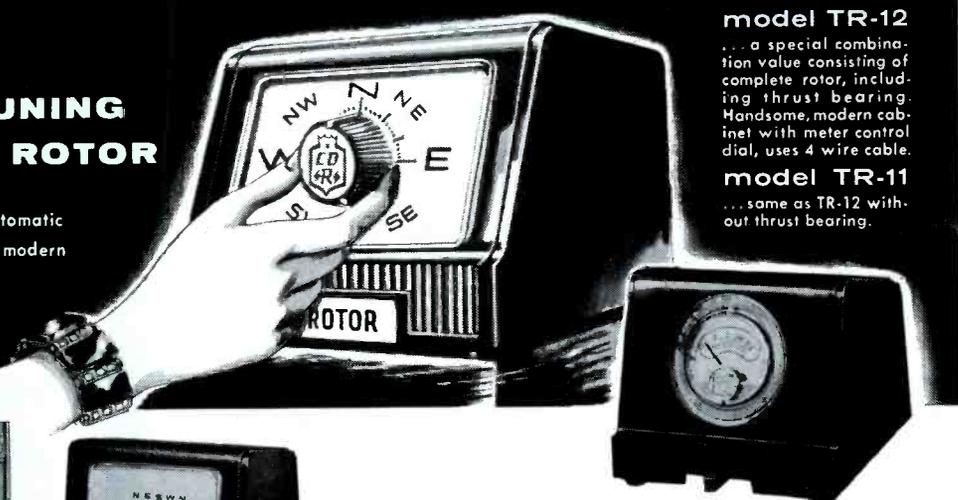model TR-11
 ... same as TR-12 without thrust bearing.



model TR-2
 ... the heavy-duty rotor with plastic cabinet featuring "Compass Control" illuminated perfect pattern dial, uses 8 wire cable.

model TR-4
 ... the heavy-duty rotor complete with handsome, new, modern cabinet with METER control dial, uses 4 wire cable.

Here is the one **COMPLETE** line of rotors... everything you need because there is a CDR rotor for every need! **SIX** skillfully engineered models... **ALL FIELD TESTED AND PROVEN** by thousands and thousands of satisfied users from coast to coast.



Pre-Sold to millions every week on TV stations across the nation.



CORNELL-DUBILIER
 SOUTH PLAINFIELD, N. J.




THE RADIART CORP.
 CLEVELAND 13, OHIO

NOW

New

SPRAGUE CERAMIKITS

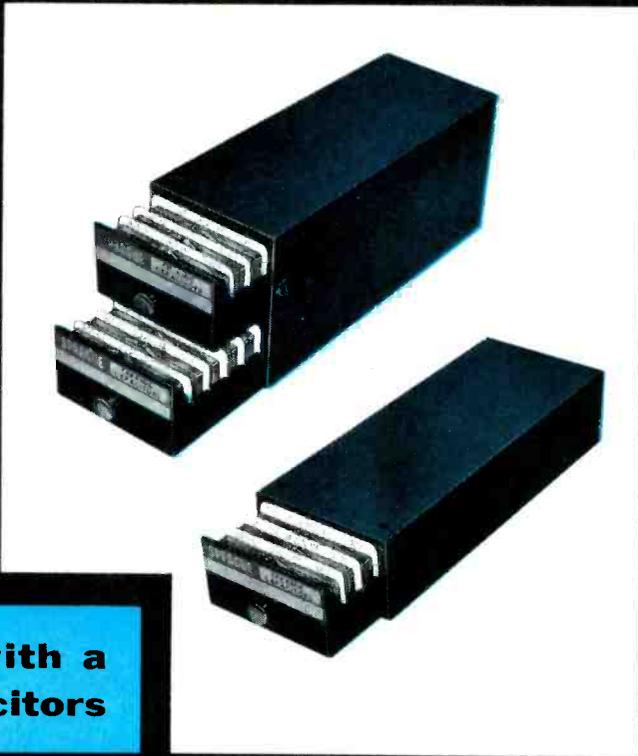

Get these cabinets FREE with a basic order of ceramic capacitors

- NOW . . . stock ceramics so you can find 'em when you want 'em . . . have your own neat and complete cabinet . . . at the cost of the capacitors alone.

- Sprague has pre-stocked these handsome, blue, heavy-gauge steel CERAMIKIT cabinets with its famous Ceramite capacitors. Ratings and quantities are based on popularity. No dogs! Stand-up indexes separate reusable plastic boxes in 12 different ratings. Catalog numbers and ratings can be seen at a glance.

- Whether you use many ceramics, or just a few, there's a Ceramikit sized and priced just right for you. Kit CK-2 is a two-drawer model holding 150 capacitors in 27 different ratings. Kit CK-3 is a single-drawer unit holding 75 capacitors in 12 different ratings. Remember there's not a dog in either Ceramikit.

- Kits interlock so You Can Build With Sprague as you buy your Ceramikits. Use the extra cabinets for handy indexed stocking of all your small parts.

- See your distributor *now* about Ceramikits, or request complete facts in Sheet M-711 from Sprague Products Co., 105 Marshall St., North Adams, Massachusetts.

CERAMIKIT CK-3

CONTENTS
3 1/2" x 9 1/4" x 2"
\$19.25 List

Quan.	Cat. No.	Quan.	Cat. No.
5	5GA-Q1	5	5GA-T47
5	5GA-Q22	5	5GA-T5
5	5GA-Q5	10	5GA-D1
10	5GA-T1	5	5GA-D2
5	5GA-T15	5	5MK-D5
5	5GA-T22	10	5MK-S1

CERAMIKIT CK-2

CONTENTS
3 1/2" x 9 1/4" x 4"
\$38.00 List

Quan.	Cat. No.	Quan.	Cat. No.
5	5GA-V5	5	5GA-T27
5	5GA-Q1	5	5GA-T33
5	5GA-Q15	5	5GA-T39
5	5GA-Q22	5	5GA-T47
5	5GA-Q33	5	5GA-T5
5	5GA-Q39	5	5GA-T68
5	5GA-Q47	10	5GA-D1
5	5GA-Q5	5	5GA-D15
5	5GA-Q68	5	5GA-D2
5	5GA-Q82	5	5GA-D33
10	5GA-T1	5	5GA-D4
5	5GA-T12	5	5MK-D5
5	5GA-T15	5	5MK-D5
5	5GA-T22	10	5MK-S1

don't be vague . . . major in

SPRAGUE®

YOU CAN BUILD WITH SPRAGUE

JAMES R. RONK
Editor

LESTER H. NELSON
Managing Editor

W. WILLIAM HENSLER
Technical Editor

GLEN E. SLUTZ
Asst. Technical Editor

Editorial Staff

GWEN BIGHAM
WILLIAM E. BURKE
HENRY A. CARTER
ROBERT B. DUNHAM
JAMES M. FOY
PHYLLIS J. HURLEY
GLENN M. McROAN
EVELYN S. MOUSER
MARGARET NEFF
C. P. OLIPHANT
VERNE M. RAY
PAUL C. SMITH
CALVIN C. YOUNG, JR.

ANTHONY M. ANDREONE
GLENN R. SMITH
Art Directors

ROBERT W. REED
Photography

ARCHIE E. CUTSHALL
DOUGLAS G. BOLT
HARRY A. MARTIN
Production

★

HOWARD W. SAMS
Publisher

Business Department:

Donald B. Shaw, V. P.
Treasurer

F. T. Dobbs, Secretary
Joe H. Morin, Sales Mgr.
Ann W. Jones, Advertising

Eastern Representatives

Paul S. Weil and
Donald C. Weil
39-01 Main Street,
Flushing 54, New York
Independence 3-9098

Western Representatives

Maurice A. Kimball Co., Inc.
2550 Beverly Blvd.
Los Angeles 57, Cal.
DUnkirk 8-6178

681 Market St.
San Francisco 5, Cal.
EXbrook 2-3365



VOL. 5 • NO. 3

MARCH • 1955

CONTENTS

Deflection Yokes	Calvin C. Young, Jr.	5
Color TV Training Series (Part X)	C. P. Oliphant and Verne M. Ray	7
Servicing the Transistor Radio	William E. Burke	11
Frequency Response in Magnetic Recording	Robert B. Dunham	13
In the Interest of Quicker Servicing	Henry A. Carter and Calvin C. Young, Jr.	15
Shop Talk	Milton S. Kiver	17
Notes on Test Equipment	Paul C. Smith	19
Examining Design Features	William E. Burke and James M. Foy	21
Radio Alignment	Paul C. Smith	23
Audio Facts	Robert B. Dunham	27
Dollar and Sense Servicing	John Markus	31
Photofact Cumulative Index No. 49		
Covering Photofact Sets—Nos. 1-270 Inclusive		85

SUBJECT REFERENCE

ANTENNAS AND ACCESSORIES	Shadow Mask and Viewing Screen, Curved Type	7
New Developments in Antennas	Three-Beam Tube Using Magnetic Convergence	7
AUDIO	COMONENTS	
Fairchild Model 260 Power Amplifier	Deflection Yokes	5
Frequency Response in Magnetic Recording	Transistors, Checking of	55
Philco Electrostatic Speaker	RADIO	
COLOR TV	Alignment Procedure	23
Convergence and Tilt Coils, Currents in	Superheterodyne Theory	23
Deflection Yoke for the Three-Beam Tube	Zenith Model R512R	81
Dynamic-Convergence Circuits in the Motorola Model 19CT1	SERVICING	
Dynamic-Convergence Circuits in the RCA Victor Model 21CT55	Deflection Yokes, Servicing and Installation of	76
Dynamic-Convergence Electromagnets for the Three-Beam Tube	Radio Alignment	23
Electron-Gun Assembly in the Three-Beam Tube	RF Tuner, Servicing of	61
Field-Neutralizing Devices for the Three-Beam Tube	TELEVISION	
Lateral-Correction Magnet for the Three-Beam Tube	Muntz Chassis 47A4	21
Magnetic Shielding for the Three-Beam Tube	TEST EQUIPMENT	
Purity Magnet	Authorized Multivolt Model 301	68
	Capacitance Checkers	19
	Polarity of Ohmmeter Leads	52
	RF Generator, Uses of	17
	Simpson Midgetester Model 355	69

Copyright 1955 by Howard W. Sams & Co., Inc.
No part of the PF REPORTER may be reproduced without written permission. No
patent liability is assumed with respect to the use of information contained herein.

The PF REPORTER is published monthly by Howard W. Sams & Co., Inc., 2201 East 46th Street, Indianapolis 5, Indiana. The PF REPORTER is on sale at 25¢ a copy at 1220 jobbers of Electronic Parts throughout the United States and Canada. (In Canada 30 cents.) When available, back numbers may be obtained by sending 35¢ for each copy desired. Entered as second class matter October 11, 1954, at the Post Office at Indianapolis, Indiana, under the Act of March 3, 1879.

SUBSCRIPTION DATA: For those desiring the convenience of delivery to their homes or shops, each issue of the REPORTER will be mailed direct, promptly upon publication. Rates: U. S. and its Possessions, one year \$3.00. Canadian subscriptions, one year \$3.60. All other countries \$12.00 per year in American money.



For Convenience and Safety

Standardize on BUSS FUSES

No matter what your fuse application may be — in television, radio, radar, avionics, instrument or controls — you can be sure there is a BUSS fuse to fit your exact needs.

Our complete line includes: standard type, dual-element (slow blowing), renewable and one-time types . . . in sizes from 1/500 ampere up, plus a companion line of fuse clips, blocks and holders.

You'll find that standardizing on BUSS fuses helps to simplify buying, stock handling and records.

And probably most important of all is your assurance that BUSS fuses will give dependable electrical protection under all service conditions. For every BUSS fuse normally used by the Electronic Industries is tested in a sensitive electronic device that makes sure the fuse is electrically and physically perfect.

Let BUSS fuses help protect your profits

Naturally, the "trouble-free" service of BUSS fuses means fewer kicks and call-backs. Your good-will, reputation and profits are safeguarded. That's why so many leading sales and service organizations refuse to take a chance with anything less than BUSS quality in fuses.

More information is available on BUSS and Fusetron small dimension fuses and fuse holders. Just write for bulletin SFB.

BUSSMANN Mfg. Co.

(Div. McGraw Electric Co.)

University at Jefferson St. Louis 7 Mo.



255

DEFLECTION YOKES

Types, Design Features, and General Servicing Hints

BY CALVIN C. YOUNG, JR.

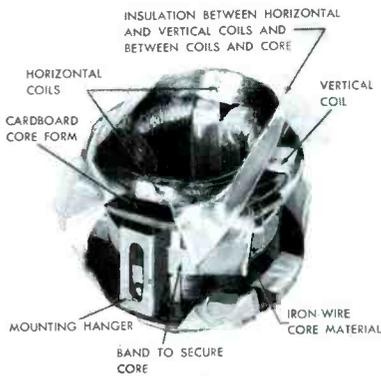


Fig. 1. Early Type 50-Degree Deflection Yoke.

A deflection yoke is an assembly of four coils of wire arranged to provide deflection in both a horizontal and a vertical plane when suitable driving signals are applied.

Fig. 1 is an illustration of one of the early types of deflection yokes with the outside cover removed. The horizontal coils, vertical coils, mounting bracket, and core may be seen in this photograph. The core is constructed of a number of turns of iron wire separated from the coils by a paper form and suitable insulation material, and it is tightly bound with a metal band.

Fig. 2A is a cross-sectional view of one pair of the deflection coils of an early type of yoke. The shaded sections form one of the coils, and the light sections form the other coil. The nonuniform magnetic field produced by a yoke of this design is illustrated in Fig. 2B. The distortion caused by this nonuniform field is illustrated by the elliptical spots in the outer portion of the field.

The cosine yoke is a product of research by engineers in their efforts to eliminate such distortion. The

yoke is called a cosine yoke because the distribution of the windings in any one coil is in proportion to the cosine of the angle between the deflection axis of that coil and the radial position of the windings in that coil. The drawing in Fig. 3 shows the location of the deflection axis of the horizontal coils and the radial position X of one winding. The angle θ is the radial angle between the axis and the windings at point X . The number of windings at point X is proportional to the cosine of the angle θ . The number of windings at any other point along the horizontal coil will also be in proportion to the cosine of the angle formed by the radius of that point and the deflection axis.

As the angle θ nears ninety degrees, the number of windings increases greatly. This follows the basic rule of mathematics which states that the cosine of an angle approaches infinity as the angle approaches ninety degrees.

The photograph in Fig. 4 is that of a modern cosine yoke that has been partially disassembled to show some of the construction details. The core in this yoke is made up of four sections of a ferrite material. These

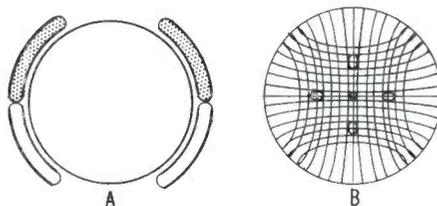


Fig. 2. (A) Cross-Sectional View of One Pair of Deflection Coils. (B) Nonuniform Field Produced by the 50-Degree Deflection Yoke.

four sections are cemented to the rest of the assembly and tightly encircled with the metal band. A suitable insulation material which is also shown in the photograph of Fig. 4 prevents short circuits between the core material and the deflection coils. The mounting lug is fastened to the metal band which secures the core.

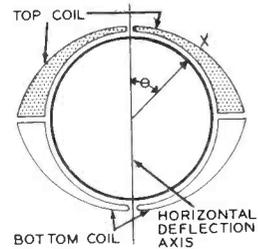


Fig. 3. Distribution of Windings in a Cosine Yoke.

Fig. 5A is an illustration of the cross-sectional view of the horizontal pair of deflection coils. You will notice that the coils are thick at the center and taper off very rapidly so that at the top they are very thin. This is the cosine distribution of the deflection-coil windings. The effect of this type of winding is to produce a uniform magnetic field with straight lines, as illustrated in Fig. 5B. Notice that the electron beam (illustrated by the small circles) is free from distortion at all parts of the magnetic field.

The uniform magnetic field produced by the cosine-distributed winding is responsible for the appearance of the bow in the top, bottom, and sides of the picture on flat-faced picture tubes. In receivers using the earlier type of deflection yoke, no pincushion effect was present because the nonuniform magnetic field had the effect of cancelling it. The pincushion effect produced by a cosine yoke may be corrected by positioning small magnets at the top and bottom of the bell of the picture tube near the neck. See Fig. 6 for an illustration of this placement. The pincushion effect at the sides is usually so small that no correction is required.

It has been found that by using a deflection yoke having cosine-squared distribution and by using a picture tube having a slightly curved face, the pincushion effect can be reduced to the point at which no correction is required. This cosine-squared distribution also provides a uniform magnetic field so that the electron beam will not be distorted. Cosine-squared distribution means that the distribution of the windings

* * Please turn to page 76 * *



HICKOK

MODEL 650C

VIDEO GENERATOR

- White-Dot generator and TV trouble shooter.
- The first instrument of its kind to quickly localize and accurately identify causes of TV receiver malfunction.
- Compatible for Color or Black and White.
- Ideal for accurate registration adjustment in color receivers.




MODEL 690

VHF-UHF MARKER GENERATOR

- Crystal controlled.
- Provides dual markers with any TV sweep generator.
- Non-parallax shadow-type dial greatly improves reading accuracy.
- Provides for 3.57 MC crystal for color burst, or any other crystal frequencies desired.

Newest Test Equipment
COMPATIBLE FOR
COLOR or BLACK and WHITE

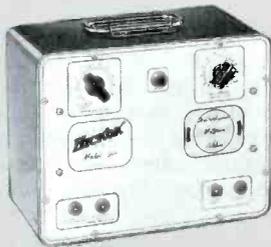

MODEL 691

HETERODYNED

MARKER ADDER

- Greatly simplifies TV alignment technique.
- Provides strong base line marker at all points including traps.
- Will not change in amplitude or distort response curve.



MODEL 695

ALL-ELECTRONIC

SWEEP-ALIGNMENT GENERATOR

- Absolutely linear sweep signal.
- Triple shielded.
- HICKOK design ALL-ELECTRONIC SWEEP.
- Signal attenuation from 3 to 300,000 microvolts.
- Channels 2-13, on fundamentals.

↓ It's Here! ↓

MODEL 655XC

The All New COLOR-BAR GENERATOR

Developed in cooperation with TV manufacturers to meet requirements for accurate color phase adjustments as well as provides for adjusting signals and gains in the matrix of color TV receiver.

THE HICKOK ELECTRICAL INSTRUMENT CO.

10566 DUPONT AVENUE • CLEVELAND 8, OHIO

COLOR TV

TRAINING SERIES

PART X THE COLOR PICTURE TUBE AND ASSOCIATED CIRCUITS

by C. P. Oliphant and Verne M. Ray

A general discussion of the three-beam color picture tube was presented in the last issue. It was pointed out that tubes of this type are divided into two categories; those that employ electrostatic methods of obtaining beam convergence and those that use a magnetic principle to obtain beam convergence. A detailed discussion of a tube which employs the electrostatic principle and of the associated components and circuits was concluded last month. This month, the data presented concerns a picture tube in the second category and also concerns the auxiliary components and circuits associated with this type of picture tube.

A THREE-BEAM TUBE EMPLOYING MAGNETIC CONVERGENCE

Actually, a tube which uses the magnetic principle of convergence is a later development than the tube which employs the electrostatic method. Although the viewing screen, the shadow mask, and the electron-gun assembly still constitute the major components of the three-beam tube, several changes in these components have been made. These changes have been incorporated in the tube which uses the magnetic method of obtaining beam convergence.

Shadow Mask and Viewing Screen.

One of the changes in the three-beam picture tube concerns the viewing-screen assembly. As shown in Fig. 9-28, this assembly in the earliest tubes consisted of a shadow mask, a phosphor-dot plate, a decorative mask, and the necessary mounting frames. It can be seen that the phosphor screen is not a part of the faceplate and that the screen and shadow mask are flat.

A later development of the shadow mask and viewing screen is shown in Fig. 9-29. In this arrangement

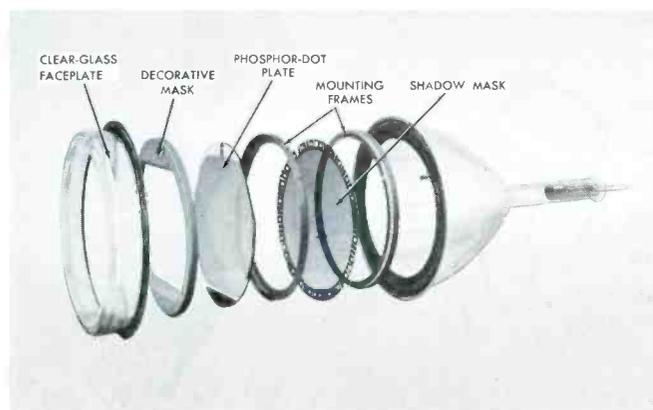


Fig. 9-28. Parts Used in an Early Commercial Color Picture Tube

the phosphor dots are applied directly to the inner surface of the curved faceplate. In addition, a simple mounting procedure allows a curved mask to be placed directly behind the faceplate so that the stringent requirements are maintained between the viewing screen and the mask. As shown in Fig. 9-30, the fact that the screen and mask are curved reduces the need for dynamic control of the beams. Although the curvature of the arc described by the points of convergence of the beams is still greater than the curvature of the mask and screen, a larger viewing surface can be used with a given amount of dynamic convergence force.

Electron-Gun Assembly.

Both the static control and the dynamic control of the three beams have been improved by changes in the design of the electron-gun assembly. A side view of the improved assembly is shown in Fig. 9-31. A close examination would reveal that each of the guns is tilted slightly so that each beam will be directed toward a common point. This is done with the intention of providing static convergence of the beams at the shadow mask; consequently, a convergence element such as that used in a tube which employs the electrostatic method of convergence is not necessary.

The expanded drawing of one of the guns shows that a gun is composed of a heater, cathode, control grid (grid No. 1), accelerating anode (grid No. 2), and a focusing anode (grid No. 3). The final anode which is grid No. 4 in Fig. 9-31 is located at the end of each gun and is electrically connected to the neck coating and to the shadow mask. The mask, coating, and grid No. 4 together form the ultor anode of the tube. The drawing in Fig. 9-31 shows a pair of pole pieces at the end of the final anode of each gun. Each pair of pole pieces is used in conjunction with a magnetic field from an external source.


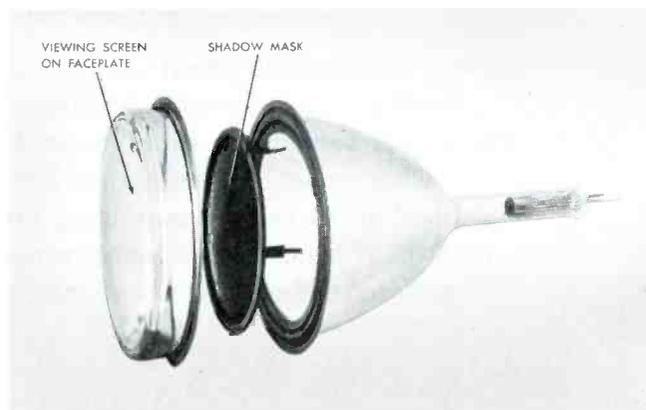


Fig. 9-29. Parts Used in a Later Commercial Color Picture Tube

OUR HATS

ARE OFF TO YOU...

MR. SERVICEMAN

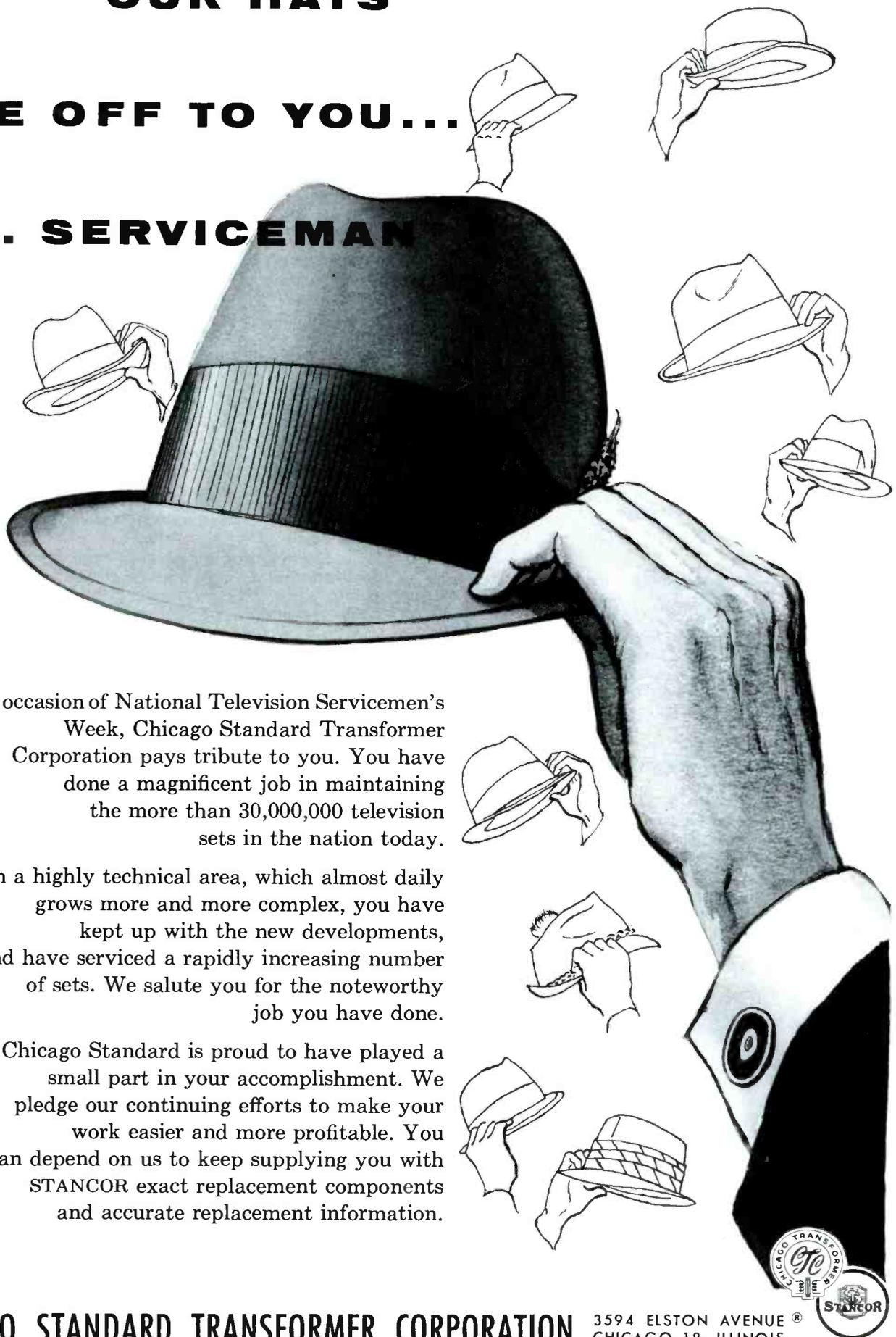

On the occasion of National Television Servicemen's Week, Chicago Standard Transformer Corporation pays tribute to you. You have done a magnificent job in maintaining the more than 30,000,000 television sets in the nation today.

In a highly technical area, which almost daily grows more and more complex, you have kept up with the new developments, and have serviced a rapidly increasing number of sets. We salute you for the noteworthy job you have done.

Chicago Standard is proud to have played a small part in your accomplishment. We pledge our continuing efforts to make your work easier and more profitable. You can depend on us to keep supplying you with STANCOR exact replacement components and accurate replacement information.

CHICAGO STANDARD TRANSFORMER CORPORATION

3594 ELSTON AVENUE®
CHICAGO 18, ILLINOIS



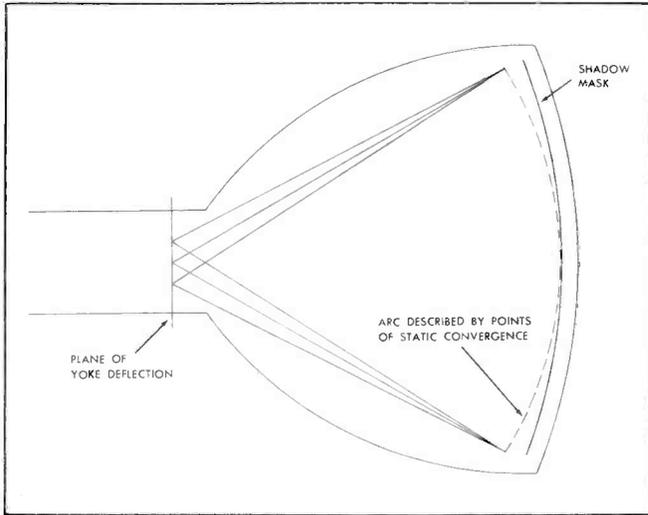


Fig. 9-30. A Curved Mask-and-Screen Assembly Reduces the Need for Dynamic Control of the Beams.

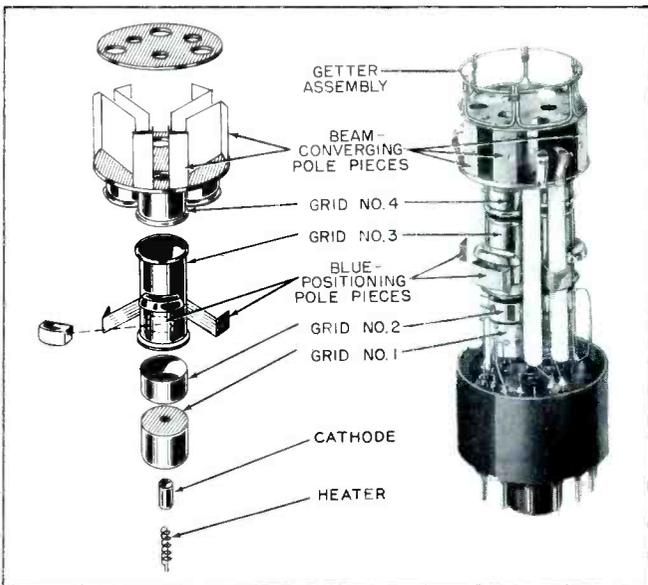


Fig. 9-31. Electron-Gun Assembly Used in a Tube Which Employs the Principle of Magnetic Convergence. (Photograph Courtesy of RCA.)

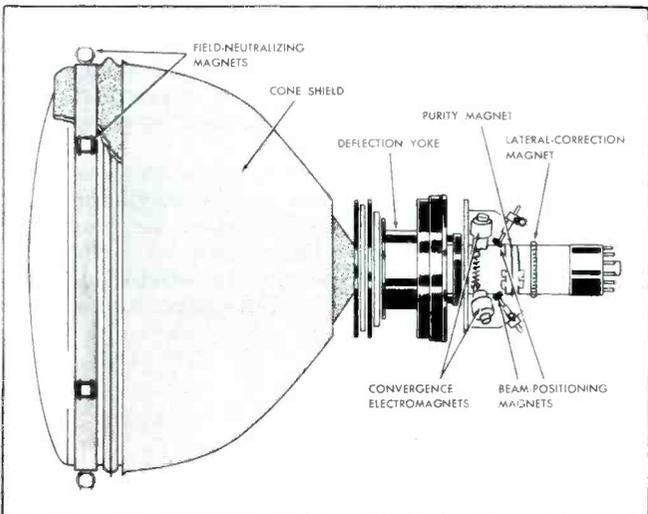


Fig. 9-32. Auxiliary Components Used With a Tube Which Employs the Principle of Magnetic Convergence.

This is done to provide a method of positioning each beam so that proper convergence will be achieved.

A special set of pole pieces associated with the source of the blue beam is also shown in Fig. 9-31. These pole pieces are constructed from magnetic material and are mounted on the focus electrode of the blue gun. A magnetic field from an external source is used with this set of pole pieces to aid in obtaining proper beam convergence.

AUXILIARY COMPONENTS

This section concerns auxiliary components as they are used with the three-beam tube that employs the magnetic method of convergence.

As pointed out in Part IX of this Color TV Training Series, an exacting relationship between the electron beams and the mask and screen must be maintained to obtain optimum performance from the three-beam tube. Even though close tolerances are observed in the manufacturing process, some variations exist. One such condition will result if the guns are not positioned properly in the gun assembly. A second variation exists when the axis of the gun assembly does not coincide with the central axis of the tube. Another kind of variation is caused when the gun assembly is turned slightly in the neck of the tube.

In order to minimize the errors which are produced by these variations, it is necessary to use certain auxiliary corrective devices to control the position of each beam with respect to the shadow mask and viewing screen. Other auxiliary components are used as a precaution against the effects of stray magnetic fields on the electron beams. Fig. 9-32 is a drawing that shows the outline of a three-beam tube which employs the magnetic method of obtaining beam convergence, and it also shows the auxiliary components used with a tube of this type. In the order of their positions starting from the tube base, the external components are the lateral-correction magnet, the purity magnet, the beam-positioning magnets, the convergence electromagnets, the deflection-yoke assembly, the cone shield, and the field-neutralizing magnets.

Color purity is achieved when each beam strikes only its respective set of color dots. The adjustment of the purity magnet, the position of the deflection yoke, the presence of the cone shield, and the setting of the field-neutralizing magnets play an important part in obtaining color purity.

The beam-positioning magnets and the lateral-correction magnet are used in conjunction with the convergence electromagnets to obtain beam convergence at all points on the shadow mask. By making the proper adjustment to the beam-positioning magnets and to the lateral-correction magnet and by applying the proper voltages to the convergence electromagnets, the points at which the three beams strike the shadow mask will coincide throughout the scanning process. Under these conditions, optimum convergence is obtained.

The Color-Purity Magnet.

The photograph in Fig. 9-33 shows that the purity magnet is similar to the centering device used with some types of monochrome picture tubes. Actually, this device uses two rings which are composed of magnetic material. The arrangement of the molecules in each ring is such that one half of each ring is a north pole and the opposite

* * Please turn to page 33 * *



9 1/2 OUT OF EVERY 10 BONDED DEALERS* SAY



**THE RAYTHEON BONDED PROGRAM
HELPS THEM MAKE MORE MONEY**

And chances are that the other half isn't half trying.


We say that because there's definite proof that wherever service dealers take full advantage of the Raytheon Bond — publicize the fact that their work and parts guarantee is bonded through one of America's largest insurance companies — they are making more money.

They tell customers about their bonded way of doing business with free displays, identification cards, ad mats, decals, etc. supplied by Raytheon — all de-

signed to create customer confidence in their shops and their men. And here's the most important fact of all. This Raytheon Bond that builds their business costs them *not one penny*.

If you can qualify for it, it won't cost you one cent, either. For further information on the Raytheon Bonded Electronic Technician Program, see your sponsoring Raytheon Tube Distributor or write direct to Department P, Raytheon Manufacturing Co., Receiving and Cathode Ray Tube Operations, 55 Chapel St., Newton 58, Mass.

*Based on a recent survey

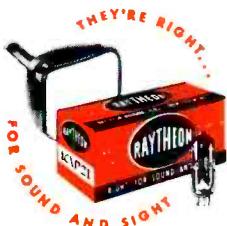


RAYTHEON MANUFACTURING COMPANY
 Receiving and Cathode Ray Tube Operations
 Newton, Mass. • Chicago • Atlanta, Ga. • Los Angeles, Calif.

Raytheon makes all these: Receiving and Picture Tubes • Reliable Subminiature and Miniature Tubes • Semiconductor Diodes and Transistors • Nucleonic Tubes • Microwave Tubes



SERVICING The TRANSISTOR RADIO

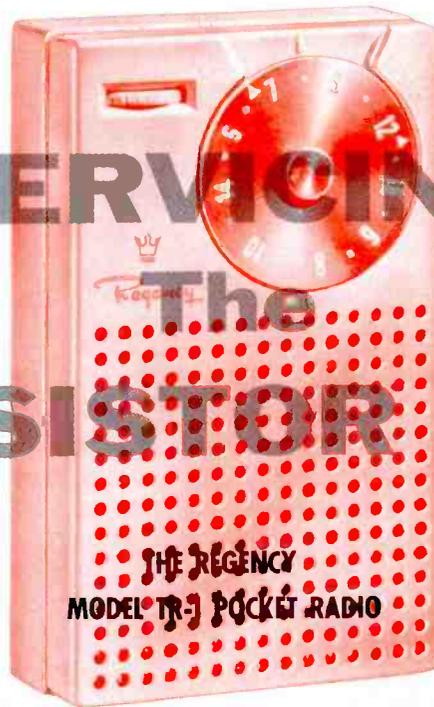

The introduction of the first transistor radio presents to the service technician new problems such as:

1. Will the printed wiring board need repairing?
2. How can transistors be tested?
3. Does normal servicing procedure apply to this receiver?

Because of the extremely small size of the receiver and because of the use of transistors, the technician is in "strange territory" as soon as he opens the case. A look at the back of the Regency Model TR-1 (with the cover removed) will reveal that the components are very closely spaced and that apparently no wiring points are accessible. With this article, we hope to present to the service technician

BY WILLIAM E. BURKE

a method of trouble shooting this receiver with the least expenditure of time and effort as well as methods of repair and replacement of components with the least possibility of damage to the delicate miniature components.

Battery Replacement

As with any piece of battery-operated equipment, the first suspect

when the receiver is inoperative is the battery. A voltage check of the battery is easy when the rear cover of the receiver is removed, since the battery clips are readily accessible. This measurement should be made with the receiver turned on and should read more than 15 volts. Any reading below this value indicates a defective battery which should be replaced.

Since it is usually not known whether the battery deteriorated through normal usage or through a defect in the receiver, an ohmmeter check should be made across the battery clips before a new battery is installed but after the old one is removed.

* * Please turn to page 52 * *

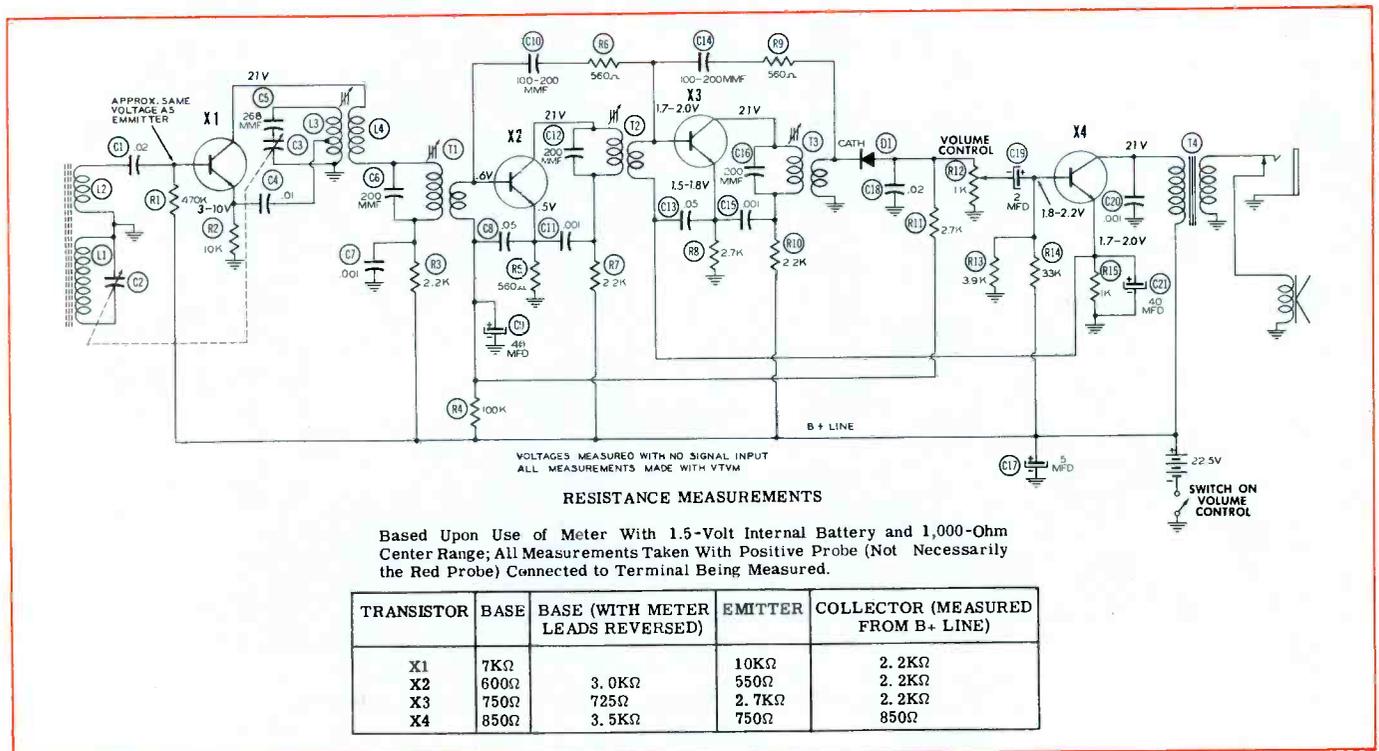


Fig. 1. Schematic Diagram of the Regency Model TR-1 Receiver.

QUIET...

Controls should be *adjustable* but not really variable. That's why Clarostat controls—composition-element and wire-wound alike—are designed, manufactured, and quality-controlled for QUIET operation, insuring maximum listening and viewing pleasure. Satisfy your customers with QUIET controls. • Details in latest Clarostat catalog.



All tapers, taps and choice of field-attached shafts and switches.



Popular $\frac{1}{4}$ " dia. size has become the universal replacement choice.



Dual controls in all types, combinations, single or concentric shafts.



CONTROLS and RESISTORS

CLAROSTAT MFG. CO., INC., DOVER, NEW HAMPSHIRE
In Canada: Canadian Marconi, Co., Ltd., Toronto 17, Ont.

FREQUENCY RESPONSE

IN

MAGNETIC RECORDING



The Fourth in a Series
of Articles Devoted to
the Principles of
Magnetic Recording

BY ROBERT B. DUNHAM

The smooth wide-range frequency response featured by most late-model tape recorders is one of the important reasons why most high quality recordings are recorded originally on tape. Advances in design and construction of tape recording and playback equipment, particularly of the recording and playback heads, and the improvements made in the tape have resulted in extended frequency response at comparatively slow tape speeds.

In common with other methods of recording and playback, some inherent characteristics of the magnetic tape recording and playback processes discriminate against certain frequency ranges. Consequently, compensation such as pre-emphasizing the high frequencies during the recording process and then boosting the low frequencies during playback must be employed because of these characteristics.

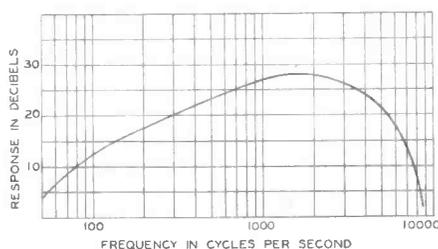


Fig. 1. Typical Response Curve Obtained When Signal Is Recorded and Played Back and There Is No Compensation.

A frequency response similar to the typical curve shown in Fig. 1 is obtained when a signal that is held at a constant current level throughout the frequency run is recorded without pre-emphasis and is played back without low-frequency boost. The subject of the compensation required to level out the response and how this compensation is obtained will not be discussed at this time. It will be taken up later when circuits are considered. Instead, we will look into the characteristics of magnetic recording to see why and how a response like that shown in Fig. 1 comes about.

The frequency response obtained with a tape recorder depends chiefly upon the width of the gap in the recording and playback heads, the magnetic characteristics of the tape used, and the speed at which the tape moves across the recording and playback heads. Of course, many things such as the amplifier circuits can affect frequency response; and correct mechanical and electrical adjustments must be maintained. But the important basic factors which influence frequency response are speed and the properties of the heads and the tape.

Recording and Playback Heads

The width of the gap in the playback head has more effect upon frequency response than does the width of the gap in the recording head. Output is reduced when the wavelength of the recorded signal is equal in size or smaller than the width of the gap in the playback head. Consequently, to extend the high-frequency response, the gap in the playback head is made very narrow. Gaps of .001 to .0005 inch or smaller are used in playback

heads; whereas, recording heads can and do use gaps measuring .001 to .002 inch in width. In any case, the effective width of the gap is wider than its physical size because the magnetic flux cannot be confined completely within the gap.

One reason for the playback gap being critical is that the signal output depends upon the time rate of change in magnetic flux as the recorded tape moves across the gap in the playback head. Remember, a playback head operates like a generator, and current flows when the magnetic lines of force cut through its coils. Output increases as frequency increases, at least in theory. Actually, during playback, the output increases at the rate of 6 db per octave at the lower frequencies; but at the higher frequencies, this increase in output is not achieved. The high frequencies suffer increasing loss, as frequency increases, because a narrower gap and a higher tape speed would be required to reproduce them properly.

This discussion of the effect of gap width upon frequency response would not be complete without directing attention to the importance of maintaining constant and uniform contact of the tape with the gap. Any change in pressure or in tension exerted upon the tape while it is moving across the head will cause the distance between the tape and the gap to vary and will cause variations in the frequency response.

The gap in the recording head need not be so narrow as that in the playback head, because the tape is magnetized as it leaves the gap during

* * Please turn to page 70 * *

P. R. MALLORY & CO. INC.
MALLORY
APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO. INC.
MALLORY
APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO. INC.
MALLORY
APPROVED PRECISION PRODUCTS



On electrolytics— FP means MALLORY!

Look for the two names—Mallory and FP—on the electrolytic capacitors you buy. They're your assurance of getting the genuine FP design, offering an exclusive combination of Mallory-developed features.

Famous for long life on the shelf and in service, they have true fabricated plate anodes... have been built for years to operate dependably at 85° C (185° F).

FP's handle high ripple currents. They're ideal for voltage doubler applications and for selenium rectifier circuits. Their twist prong mounting cuts installation time to seconds.

Don't accept substitutes. Always specify Mallory FP Capacitors to be sure of premium performance at no extra price.

BE SURE TO USE . . .



Mallory Pluscaps® . . . plastic tubular replacements with permanently secured leads . . . won't short out or open prematurely.




Subminiature Silverlytic* Capacitors . . . only 3/8" long and 1/32" in diameter . . . ideal for transistors and other miniature low-voltage circuits.

*Trademark

P. R. MALLORY & CO. INC.
MALLORY
APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO. INC.
MALLORY
CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
RECTIFIERS • POWER SUPPLIES • FILTERS • MERCURY BATTERIES
APPROVED PRECISION PRODUCTS
P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

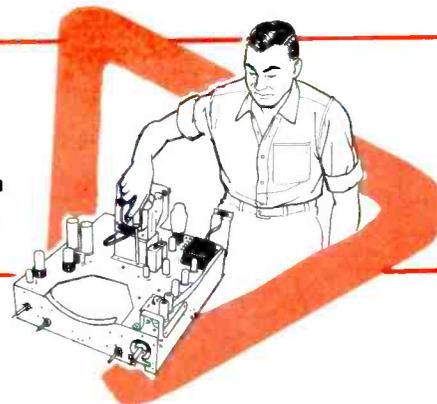In the Interest of . . . Quicker Servicing



by Henry A. Carter and Calvin C. Young, Jr.

IN THE HOME

New Antenna Developments

Since the freeze on construction permits for new television stations was removed by the Federal Communications Commission (FCC) in April of 1952, a great many of the larger cities over the country have acquired additional VHF television stations. This means that many cities which formerly had only one now have two or more in operation.

In most of these cities, the stations have their transmitting antennas located in different places in the city or in outlying areas. The city of Indianapolis, Indiana is a good example of this situation. The relative locations of three VHF stations which provide local reception are shown in Fig. 1. It can be seen from this illustration that it is very difficult within the city to orient a single antenna so that reception may be obtained from all three stations without ghosts or distortion.

To combat this problem in the residential areas, technicians have in many cases installed a DPDT

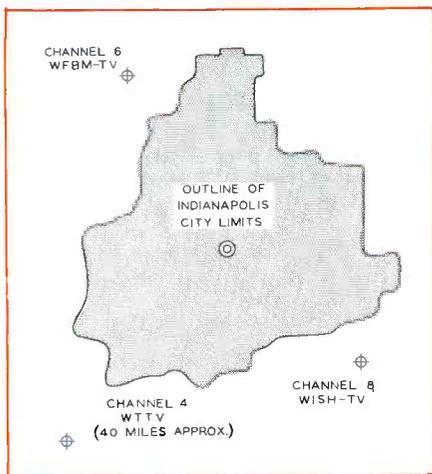


Fig. 1. Relative Locations of TV Transmitting Towers in Indianapolis, Indiana.

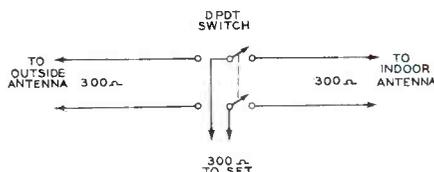


Fig. 2. Antenna-Switch Arrangement.

switch in the antenna lead, as illustrated in Fig. 2. In using this hookup, the outside antenna is turned for best reception on channel 4 and the indoor antenna provides a usable signal on channels 6 and 8. This method has proved to be very satisfactory where there is acceptable reception on channels 6 and 8 by means of indoor V-type antennas (rabbit ears).

There are other methods which may be employed in residential areas to receive all channels without ghosts or without other types of distortion caused by the antenna. A good grade of all-channel outdoor antenna may be used in conjunction with an antenna rotator. The antenna used in this type of installation should have a high front-to-back ratio and a sharp directivity pattern. Another method is to install an outdoor antenna for each channel to be received.

The Clear Beam Antenna Company has recently introduced in the Indianapolis area an antenna system which consists of a three-element Yagi for channel 4, another three-element Yagi for channel 6, a folded dipole with reflector for channel 8, a matching transformer, and a harness for connecting the two Yagis to the transformer. The harness is made up of 450-ohm open-wire line. A sketch of this antenna system is illustrated in Fig. 3. The matching transformer is mounted on the mast, the channel-4 and channel-6 Yagis are connected to the low-channel input of the transformer by means of the harness, and the channel-8 folded dipole is connected to the high channel input. The output of the transformer is connected to the receiver

through a single 300-ohm ribbon lead-in wire. Reception in this area with the Clear Beam unit just described has proved to be very satisfactory.

There will be cases, however, when reception problems will be a function of the location of the receiver and antenna system. Such may be the case in downtown areas, in large apartment buildings, in areas behind a hill or mountain, or even in areas directly behind a large building. If the reception problem in a downtown area consists of ghosts or multiple images, the installation of an antenna having very sharp directivity and a high front-to-back ratio will do much toward improving reception. For an installation in such a downtown area, an antenna which has no minor lobes in its directivity pattern is almost a necessity because ghost pickup may be a problem on an antenna which has several pickup lobes. See Fig. 4 for examples of a single-lobe directional pattern and a multiple-lobe pattern.

There will be occasions when ignition interference, interference from neon signs, and interference present on the AC power line may cause reception problems in the downtown area. Installing a high-pass filter in the antenna input circuit, twisting the antenna lead-in wire, and routing the lead-in wire as far away

* * Please turn to page 58 * *


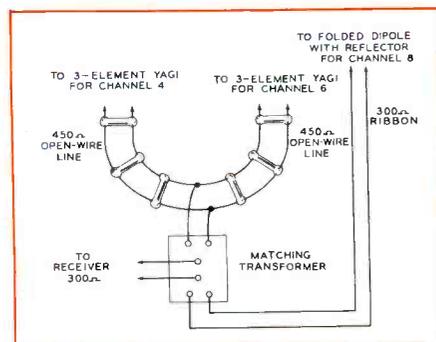


Fig. 3. Clear Beam Antenna System Designed for Indianapolis Area.

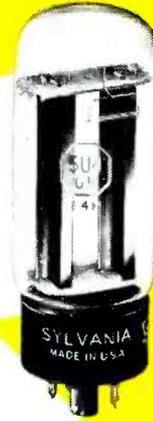

NEW 12AU7A

- shorter construction reduces intermittent scan and heater cathode failures.
- completely interchangeable with Type 12AU7.



NEW 5U4GB

- twin-wing plates provide greater heat dissipation.
- wafer stem strengthens construction. Increases ratings to 275 Ma at 44V drop with 1.0 amp. peak plate current.

Sylvania makes important NEW advances in

WAR ON CALL-BACKS

Six "double-duty" tubes designed to lick TV service's costliest problems. More to come!

Sylvania's war against callbacks began with the highly improved 5U4GB tube. Now Sylvania continues its fight against profit-grabbing callbacks and offers five more improved types for TV service.

These tubes score a direct hit on the most common "quick failures." Stronger winged-plate design and wafer-stem construction—sturdier welds and glass-to-metal seals; these plus a score of other mechanical and electrical improvements are incorporated to give trouble-free service.

Join the battle against callbacks! Use only Sylvania "double-duty" types! They're designed for servicing old as well as new sets.

NEW 1X2B

- all-nickel plates reduce electrolysis. Lower gas level results in higher breakdown voltage.
- longer life-test under conditions well above ratings.



NEW 6BQ6GTA

- folded-edge plate design avoids bulb bombardment.
- double-clearance between mount and bulb top eliminates the "pigtail" to grid shorts. Avoids bulb-puncturing electron bombardment.



NEW 1B3GT

- electrostatic shield-ring protects filament during high-voltage operation.
- Sylvania-developed top-cap alloy produces positive glass-to-metal seal
- high-voltage base makes tube interchangeable with coated types.



NEW 6SN7GTB

- oblique orientation of sections reduces microphonism.
- direct weld between stem pins and plates strengthens mount.



Look for the new "double-duty" types in this yellow-and-black carton. It's your calling card of quality.

SYLVANIA

Sylvania Electric Products Inc.
1740 Broadway, New York 19, N.Y.

In Canada: Sylvania Electric (Canada) Ltd.
University Tower Bldg., St. Catherine Street
Montreal, P. Q.

LIGHTING • RADIO • ELECTRONICS • TELEVISION • ATOMIC ENERGY

ShopTalk

MILTON S. KIVER

President, Television Communications Institute

Uses for the RF Generator

Normally, an RF generator is associated with alignment work, and that is its chief application; however, the RF generator also serves as a very fine localizer of defects, and those men who have never thought of using it in this way will be interested in the following discussion.

In last month's column, mention was made of an RF generator that was successfully used in locating an intermittent defect. Briefly, here is the procedure that was followed. The receiver was placed on the bench and tuned to one of the local channels. Then a VTVM was placed across the load resistor of the video detector. At the same time, an RF generator was loosely connected between grid and ground of the second video IF stage. The generator was set to the mid-frequency of the video IF range, and the amplitude of its output signal was modulated by its own 400-cycle audio note. Then its output control was slowly advanced until alternate black and white horizontal bars were just barely visible on the screen.

The set was left to operate. In time, the intermittent condition appeared and removed the picture and the sound; but it did not affect the horizontal bars produced by the RF generator. This meant that the cause of the intermittent condition was situated between the antenna terminals and the second video IF stage.

For the next step, the RF generator was shifted to the grid of the mixer tube. When the intermittent symptom once again appeared, all the signals left the screen. The inescapable conclusion was that the trouble was located between the mixer grid and the grid of the second video IF amplifier. By tapping the various capacitors, resistors, and tubes in these two stages, the technician found the defective component to be a bypass capacitor.

Fortunately for the health and welfare of the service technician, comparatively few of his jobs involve

intermittent receivers, but whether the trouble is persistent or elusive, an RF generator can be of great assistance in tracking it down. Here are some additional examples.

Stages which are completely dead are readily checked by an RF generator. In the video system following the second detector, only the audio modulating voltage of the generator is used. The signal is applied across the load resistor of the second detector, and the picture tube screen is observed for horizontal black and white stripes. See Fig. 1. Appearance of these stripes indicates that the audio signal is passing through the various video amplifier stages.

If there are several video amplifiers and you wish to obtain a relative indication of their amplifying power, the foregoing procedure can be modified as follows. Inject the audio signal at the signal element of the picture tube. Then reduce the level of the audio signal until the black and white bars are just barely visible on the screen. Shift the generator to the control grid of the final video amplifier. The bars, as seen on the screen, should appear considerably darker, indicating that the video stage has amplified them. If there is still another video amplifier, again the audio signal can be reduced until the bars are just visible on the screen. Then the input point is shifted from the grid of the final video amplifier to the grid of the preceding stage.



Fig. 1. Horizontal-Bar Pattern Produced on Screen Is Caused by Audio Modulation of RF Generator.

The increase in bar intensity is an indication that the video amplifier is amplifying the signal.

If desired, the actual numerical stage gain can be determined. Place the audio signal at the grid of a video amplifier, and increase the generator output until one volt of signal at the grid is indicated on the AC scale of a VTVM. Then move the meter to the plate of the tube, and note the value of the audio signal at that point. The ratio between the signal at the plate and the signal at the grid represents the gain of the video amplifier. The test can be carried out over the entire video amplifier section or any part of it; moreover, the gain checks which can be done in the video amplifier with the foregoing tests can also be carried out in the audio amplifier system.

In the IF system, all the tests are performed with the generator set to an appropriate IF frequency. If your instrument only goes up to 30 mc and the video IF in the receiver is in the 40-mc range, it is almost always possible to use the second harmonic of some frequency in the 20-mc range. The method of testing is similar to that described in the foregoing, with the exception that a modulated RF signal is used instead of an audio signal. Horizontal bars will again appear on the screen; and by their relative intensity, you will be able to judge whether or not a certain stage is amplifying the signal. At any point where the signal path is broken, the signal will disappear; and this will practically pinpoint the source of trouble. You can proceed stage by stage or jump several stages at a time. Either method is carried out readily with approximately the same service time.

Checking the gains of the video IF stages by means of an RF generator may seem a little involved at first, but it actually offers very little additional difficulty. There are two ways of making the measurements — one is by using an unmodulated RF


* * Please turn to page 72 * *

BATTERY BUSINESS IS BIG BUSINESS

here's how to win your share

Over 15 million portables in the USA today make this business of selling batteries a big business. Get your share by letting RCA give selling power to your battery selling plans. Remind your customers that RCA Batteries are radio-engineered for extra listening hours . . . manufactured to the highest performance standards of the greatest name in radio. Your RCA Battery Distributor is ready now to supply you with fresh, full-powered RCA Batteries. And, remember, when you place your order, ask about RCA's profit-building battery selling aids. They're available with your purchase of fast-selling RCA Batteries.

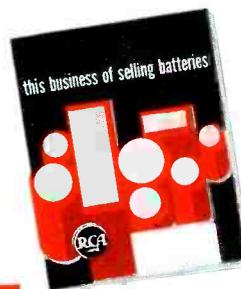FREE! "This Business of Selling Batteries" (Form 4F303), filled with business tips, selling hints, and promotional ideas. Get your free copy from your RCA Battery Distributor or write directly to RCA Commercial Engineering, Section C-33-N, Harrison, New Jersey.



**RADIO CORPORATION
of AMERICA**


RADIO BATTERIES HARRISON, N. J.



Notes On

TEST EQUIPMENT

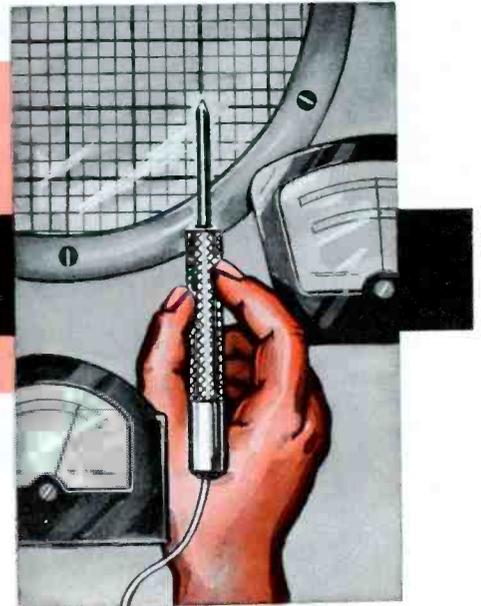Presenting Information on Application, Maintenance, and Adaptability of Service Instruments



by Paul C. Smith

CAPACITANCE CHECKERS

The service technician is interested in many characteristics of capacitors. The foremost of these characteristics is capacitance, but others also have a direct influence on the behavior of the capacitor. The technician may wish to know whether a capacitor is open, shorted, leaky, or intermittent; or he may be interested in the insulation resistance, power factor, or RF impedance. All this information can be obtained through the use of present-day capacitance checkers.

One of the simplest capacity checks may be performed with the use of an AC voltmeter. The capacitor is connected in series with a known resistance, and this series network is placed across an AC voltage source of known voltage and frequency. A part of this applied voltage will be developed across the capacitor in direct proportion to the reactance of the capacitor. A chart could be prepared to show capacitance corresponding to reactance at the frequency used, and the value of capacitance can be obtained directly from such a chart. Some VTVM's may include a circuit for this type of capacity checking, in which case the chart would be unnecessary because the VTVM is calibrated so that capacity may be read on the meter scale.

More accurate checks can be obtained with the use of a bridge, and the majority of capacitance checkers will be found to use any one of several types of bridge circuits. These types may range in complexity from the very simple general-purpose bridge

circuits to the more complex laboratory bridge circuits. The ones commonly encountered in capacitance checkers are kept fairly simple in operation.

Bridge Theory

A schematic diagram of an AC bridge circuit is shown in Fig. 1A. The bridge circuit consists of four arms and a detecting device connected at two opposite junctions. A source of AC signal is connected to the two remaining junctions. The detector may be an oscilloscope, a pair of earphones, an electron-eye tube, or some other device which will indicate the relative magnitude of the AC signal present across the detecting device. The arms are labeled as impedances because they may represent resistances, capacitances, inductances, or any combination thereof. The bridge is balanced when:

$$\frac{Z_a}{Z_b} = \frac{Z_c}{Z_d}$$

where

$Z_a, Z_b, Z_c,$ and Z_d = the impedances designated.

There will be no potential difference between the junction points y and z for this condition.

The bridge circuit of Fig. 1A can be modified to the form of Fig. 1B in which it is shown as a general-purpose bridge. Z_x is an unknown impedance, and Z_s is a standard impedance with which it is to be compared. Three conditions are

necessary in order for the bridge of Fig. 1B to be in balance:

$$Z_x = \frac{R_a}{R_b} (Z_s),$$

$$X_x = \frac{R_a}{R_b} (X_s),$$

$$R_x = \frac{R_a}{R_b} (R_s),$$

where

X = reactance,

x = unknown value,

Z_x = impedance of unknown,

R_a, R_b = resistances,

Z_s = standard impedance,

X_x = reactive component of Z_x ,

X_s = reactive component of the standard impedance,

R_x = resistive component of the unknown impedance,


R_s = resistive component of the standard impedance.

Both resistance and reactance, which are impedance components, must be considered in order to reach a balance. This fact is the basis for

* * Please turn to page 66 * *

...for leading TV receiver
manufacturers


...for you

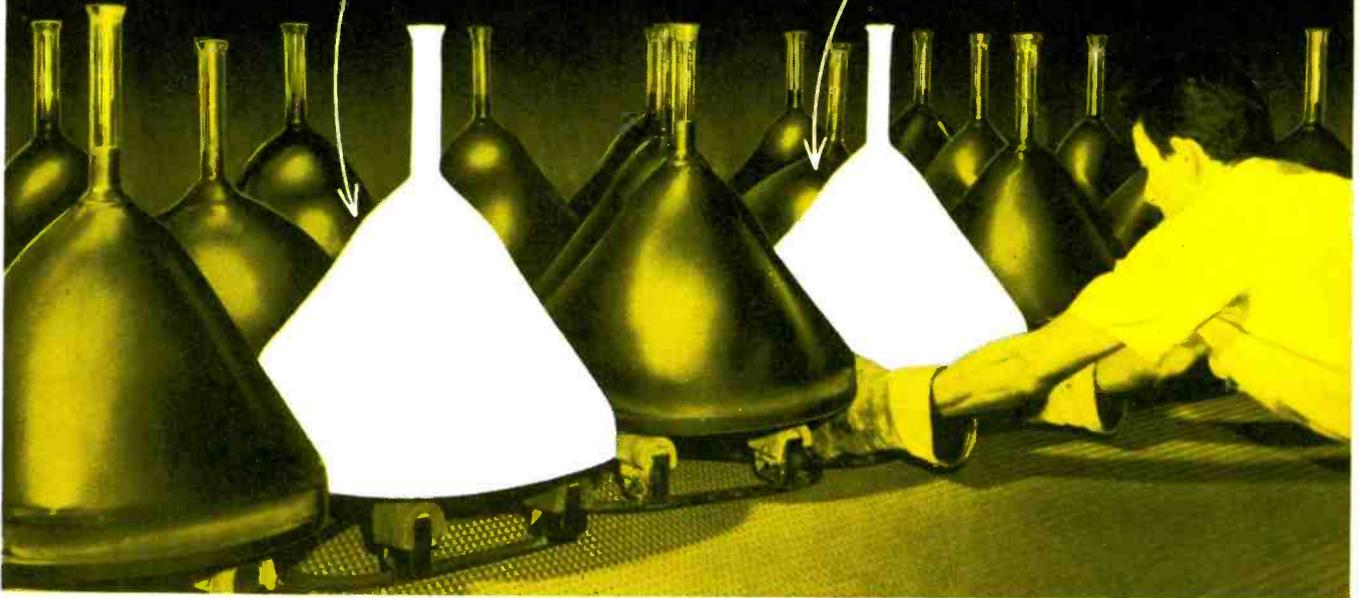

At Du Mont there is only one *Standard of Quality...*

You take no chances with quality when you use Du Mont picture tubes. *Every* Du Mont picture tube is manufactured to the same exacting quality standards

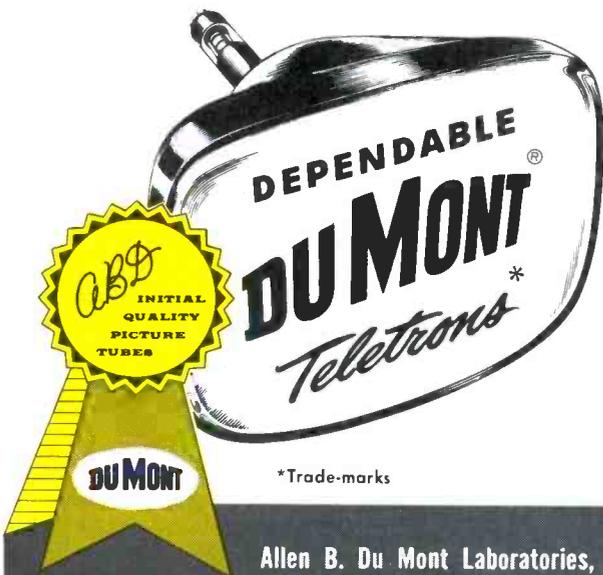— whether it's for a leading television receiver manufacturer to be used as initial equipment, or for you to be used as a replacement.




ADVERTISE QUALITY — FOR QUALITY PROFIT!

Look for the Initial Quality Picture Tube tag packed with every Du Mont picture tube. Use it to show your customers that you have provided the finest quality components with your service.



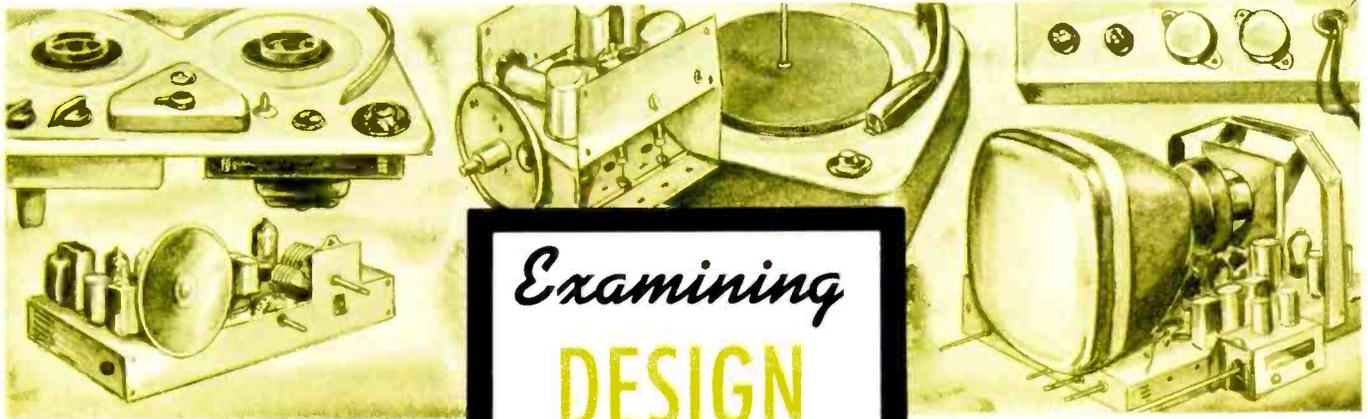Allen B. Du Mont Laboratories, Inc., Clifton, N. J. Replacement Sales, Cathode Ray Tube Division



Examining DESIGN Features

BY WILLIAM E. BURKE
and JAMES M. FOY

MUNTZ CHASSIS 47A4

The Muntz Chassis 47A4 shown in Fig. 1 is an example of the Muntz Industries' new line of TV receivers. The chassis has the newly popular vertical construction, and the receiver uses 14 tubes plus the 21-inch picture tube. The intermediate frequency is in the 40-mc range; the picture carrier is at 45.75 mc, and the sound carrier at 41.25 mc.

One side of the AC line is connected directly to the chassis; consequently, an isolation transformer is particularly recommended when servicing this receiver. The circuits employed in the receiver have some unusual features which will be covered in the following discussion.



Fig. 1. Muntz Chassis 47A4 Mounted in Cabinet.

A circuit of this type has the advantage that a tube change, with its accompanying capacity change, cannot alter the IF alignment because the small change in tube capacity is masked by the relatively large capacity of the trimmers.

Two 6AU6 tubes provide amplification in the first two IF stages, and the pentode section of a 6AM8 is used in the third IF stage. AGC voltage is applied to the control grids of the first two IF stages, and it is derived from the output of the video detector. The video detector and output stages use conventional circuitry, and the functions are provided by the diode section of a 6AM8 and the pentode section of a 6AU8 respectively.

Tuner.

The tuner is a turret type with 12 positions covering VHF channels 2 through 13. (UHF reception can be added to this receiver through the use of UHF turret strips, or an optional UHF tuner can be installed.) The RF signal is first amplified by a conventional pentode RF stage and is converted to the intermediate frequency by the pentode and triode sections of a 6AT8. These sections operate as the mixer and oscillator respectively. AGC voltage is applied to the grid of the RF tube.

Video IF.

The IF signal from the tuner is coupled to the grid of the first IF stage through a pi-network composed of coil L6 and capacitors C101 and C17. This network can be seen in the schematic of Fig. 2. The coil L6 and the plate coils of the three IF stages are tubular, impregnated with plastic, and have fixed inductance values. The necessary adjustments for the correct IF response are made by means of small, variable, ceramic trimmers. The coils and trimmer capacitors are identified in the photograph of the IF section in Fig. 3.

Sound.

The 4.5-mc sound IF signal is derived from the video output stage and is amplified by the pentode section of a 6U8 before being applied to the 6BN6 gated-beam detector. Since the detector provides amplification of the audio signal, that signal is fed from the detector through the volume control to the 25L6GT output tube. Filtering of the B+ voltage is supplied by a part of the primary of the audio output transformer.

* * Please turn to page 79 * *

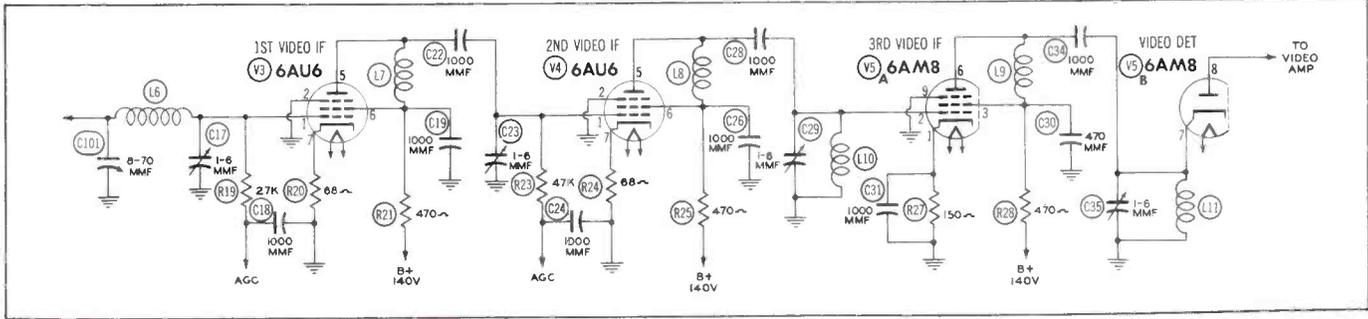


Fig. 2. Schematic Diagram of Video IF Strip in Muntz Chassis 47A4.

Editorially featured by **HOWARD SAMS Photofact Reporter***—

Feature "invisible" conversion for over

14,000,000

TV sets with Standard Coil tuners in use today.

Buy the set owners' goodwill and loyalty by selling them "invisible" conversion with Standard Coil UHF strips in their Standard Coil tuner.

Strip conversion is "designed in" conversion developed by the same engineers who designed the tuners used in the sets. And—no extra box, no extra wires, no extra tuning knobs—and the absolute minimum of interference.

And Standard Coil "invisible" conversion is simple to install and easy to align. Capitalize on the steady demand for UHF conversion. This is all that's needed for each channel converted (actual size).

*Vol. 3, No. 2—page 35 and following



BURTON BROWNE ADVERTISING

Standard—**COIL PRODUCTS CO., INC.**

CHICAGO • LOS ANGELES • BANGOR, MICH. • NO. DIGHTON, MASS.

Export Agent: *Rocke International Corporation, 13 E. 40th Street, New York City*

The alignment of a small radio is much simpler than that of a TV receiver. The latter involves video IF alignment (often accompanied by many trap adjustments), sound IF and sound detector alignment, and in some cases adjustment of the oscillator and RF stages. The radio alignment quite often consists of only three or four steps. With this great difference in the two alignments, it is probably a temptation for the service technician to view the radio alignment as something of much less importance — perhaps as something to be hurried over with the idea that almost any sort of alignment will do. The truth of the matter is that an excellent radio alignment takes very little or no more time than an indifferent one, and the improvement effected in some cases is quite easily noted by the owner when the receiver is returned.

If a technician has a receiver on the shop bench for a routine repair such as replacement of a filter capacitor or of an open or shorted bypass capacitor, it takes only a little more time for a quick check of the alignment; and he may feel justified in completing the alignment and charging for the added service if he sees that considerable improvement can be made. The very process of checking the alignment puts him partially through the alignment procedure so that not much extra time is involved. Quite often there will be sets which do not receive stations falling near the extremes of the broadcast band or which do so only at greatly reduced volume compared to the rest of the band. Another common occurrence is to find that a set will tune just to the edge of a station frequency that is at one extreme of the band, and the hiss and distortion which are characteristic of a mistuned superheterodyne receiver will result.

The symptoms or shortcomings just mentioned must be considered to be the result of poor tracking or misalignment, inasmuch as all standard AM receivers of recent design provide ample coverage of the broadcast band. Poor tracking and misalignment may be the result of gradual changes in component values over a period of time; they may come about because of vibration or rough handling during shipment; or they may even be the result of amateur "slug twisting." (A slug twister is the next step beyond a "knob twirler.")

A step-by-step alignment of a radio may range from something that is extremely simple in the case of small 4- or 5-tube AC-DC sets to a more complicated alignment for larger sets, for sets having several tuning ranges, and for sets having an

RADIO

ALIGNMENT

A DISCUSSION OF TRACKING, ALIGNMENT POINTS, IMAGE FREQUENCIES, AND OTHER FACTORS

BY PAUL C. SMITH

FM band. Alignment of auto radios also tends to be a little more elaborate than that of the simpler table-top model radios. A typical alignment procedure for a small radio is outlined in Chart I. Step 1 consists of peaking

the IF transformers for maximum response at the intermediate frequency. Step 2 calls for setting the tuning range at the high-frequency end of the band by means of the oscillator trimmer. Step 3 is a tracking operation to adjust for greatest response at a tracking point (1400 kc in this case). For this last operation, the antenna circuit is tuned by means of a trimmer on the antenna section of the tuning capacitor. The alignment procedure of Chart I is about as simple as any the technician is likely to encounter. Occasionally, a receiver which uses only one IF transformer is found; and in that case, fewer adjustments would be necessary. Normally, however, the set employs two or more IF transformers. Sometimes, an RF stage is added ahead of the converter, thus increasing the sensitivity and selectivity of the set.

Superheterodyne Theory


A brief review of the principles of operation of superheterodyne receivers may lead to a better understanding of some of the points to be made in the paragraphs which follow. The modulated carrier signal from the radio station is intercepted by the antenna system of the receiver; then this RF signal is applied to an RF stage for amplification, or it is passed directly to the converter stage of the receiver. A tuned circuit between the antenna and the converter stage provides for a certain amount of attenuation to all signals except the desired one. The RF signal is combined or heterodyned in the converter stage with an oscillator signal, and the result is a combination signal made up of each original signal plus the sum and difference frequencies.

Consider a case in which the RF or antenna circuits are tuned to accept a signal at 1000 kc and in which the oscillator is operating at 1455 kc. Frequencies of 1000 kc, 1455 kc, 2455 kc, and 455 kc will be present in the output of the converter. The IF stages are tuned to accept and pass only one of these signals and to reject the others. The accepted signal, which is 455 kc in this case, contains all the audio information impressed upon the RF carrier at the broadcasting station; but the carrier has been effectively changed from 1000 kc to 455 kc.

This system has several advantages not found in tuned radio frequency (TRF) receivers. The IF stages do not need to be designed for amplification at frequencies other than the intermediate frequency, and this permits simpler design and greater amplification. Because the IF signal is lower than the RF signal, the selectivity is improved and there

The *New* PRECISION

MODEL 88

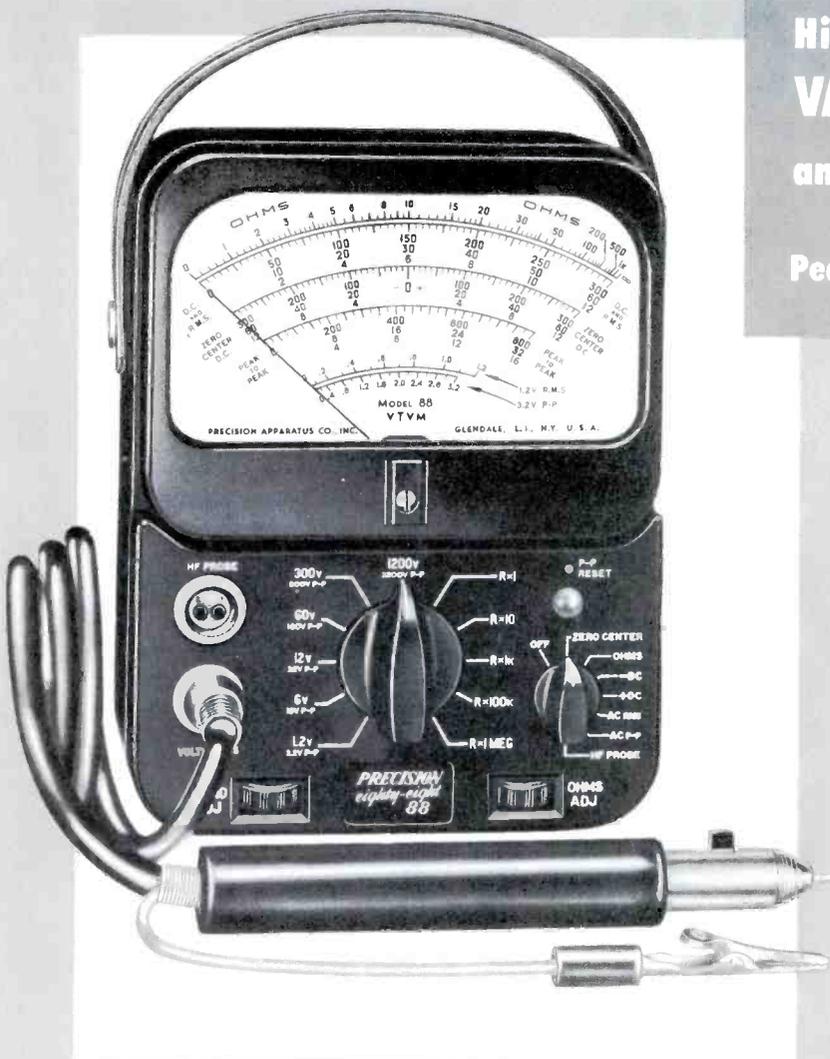

High Sensitivity VACUUM TUBE VOLTMETER and ELECTRONIC OHMMETER

Complete with 3-way Universal Test Probe.

Peak to Peak Voltage Ranges to 3200 volts

The Model 88 is a compact, wide range VTVM-Ohmmeter, for modern electronic circuit checking in the laboratory, on the production line and for general service-maintenance.

Its many advanced features include specially engineered Peak-to-Peak voltage ranges which afford a new high in P-P reading accuracy of pulsed wave-forms encountered in Color or Monochrome TV and similar applications.

THE MODEL 88 PROVIDES 7 DISTINCTLY SEPARATE FUNCTIONS 40 SELECTED, WIDE-SPREAD RANGES

- ▶ **TRUE-ZERO-CENTER DC VOLTAGE RANGES.** Eliminates need for test lead reversal or polarity switching: Constant 26 2/3 Megohms input resistance. 0 ±1.2 ±6 ±12 ±60 ±300 ±1200 volts.
- ▶ **5 ELECTRONIC OHMMETER RANGES.** Covers wide range of resistance values encountered in modern electronic circuits, AM-FM-TV: 0-1000-10,000 ohms. 0-1-100-1000 Megohms.
- ▶ **6 (-) MINUS DC VOLTAGE RANGES:** (Left-Hand-Zero) constant 13 1/3 Megs. input resistance. 0-1.2-6-12-60-300-1200 volts.
- ▶ **6 (+) PLUS DC VOLTAGE RANGES:** (Left-Hand-Zero) constant 13 1/3 Megs. input resistance. 0-1.2-6-12-60-300-1200 volts.
- ▶ **6 HIGH IMPEDANCE RMS AC VOLTAGE RANGES:**
0-1.2-6-12-60-300-1200 volts.
Input Characteristics: Up to 60V Range: - 3 Megohms, 90 mmfd.
300V Range: - 1 Megohm, 70 mmfd.
1200V Range: - 4 Megohms, 67 mmfd.
- ▶ **6 HIGH IMPEDANCE PEAK-TO-PEAK AC VOLTAGE RANGES:**
Engineered for more accurate measurement of symmetrical and pulsed voltages: 0-3.2-16-32-160-800-3200 volts.
Input Characteristics: Up to 160V Range: - 6 Megohms, 90 mmfd.
800V Range: - 1 Megohm, 70 mmfd.
3200V Range: - 4 Megohms, 67 mmfd.
- ▶ **5 SPECIAL HIGH FREQUENCY PROBE RANGES:** Extends AC RMS reading facility to 300 Mc. with minimized circuit loading:
0-1.2-6-12-60-300 volts RMS. (Requires optional PRECISION RF-10A HF Probe). Probe input capacity: - approximately 5 mmfd.

- **ONE UNIVERSAL, COAXIAL AC-DC VTVM PROBE** serves all functions other than high frequency probe ranges.
- **PEAK-TO-PEAK "RE-SET" PUSH-BUTTON** for rapid "zero" return of special, electronically damped test circuit.
- **LARGE 5 1/4" RUGGED PACE METER:** 200 microamperes sensitivity, ±2% accuracy. Manufactured in PRECISION'S own modern meter plant.
- **1% MULTIPLIERS and SHUNTS:** wire-wound and deposited-film types.
- **CUSTOM-MOLDED PHENOLIC CASE and PANEL:** Compact, efficient, laboratory instrument styling.

MODEL 88: complete with detachable AC line cord, internal ohmmeter battery, 3-way coaxial VTVM probe and detailed operating manual. Over-all case dimensions 5 3/8" x 7" x 3 1/8".
Net Price \$69.75

ACCESSORIES FOR THE MODEL 88

RF-10A High Frequency vacuum tube probe	\$14.40 net
TV-8 60 Kilovolt safety probe	14.75 net
ST-1 Snap-on foldaway tilt-stand	1.00 net

WILL COLOR TELEVISION MAKE PRESENT TEST EQUIPMENT OBSOLETE?

THE ANSWER IS NO! There is nothing in Color TV that will nullify good present-day monochrome equipment or render it obsolete. It will create even more uses for the **PRECISION** instruments you have always owned. Color servicing will merely require one or two special-purpose instruments . . . which you can rely on **PRECISION** to produce at the proper time . . . when field requirements are clearly defined.

As for V.T.V.M.'s — a volt is a volt, an ohm is an ohm and a mil is a mil . . . whether it is being measured in color TV, monochrome or plain ordinary radio!



PACE
THE METER OF PRECISION

PRECISION Apparatus Company, Inc.

70-31 84th STREET, GLENDALE 27, L. I., N. Y.

Export Division: 458 Broadway, New York 13, U.S.A. Cables: Morhanex
Canada: Atlas Radio Corp., Ltd., 560 King Street W., Toronto 2B

CHART I

AN EXAMPLE OF ALIGNMENT INSTRUCTIONS FOR A SMALL AM RADIO

Volume control should be at maximum position. Output of signal generator should be no higher than necessary to obtain an output reading. Use an insulated alignment screwdriver for adjusting.
 Loop should be maintained in same relative position to chassis as when receiver is in cabinet.
 To set pointer, turn tuning capacitor fully closed and set pointer parallel with base of dial.

DUMMY ANTENNA	SIGNAL GENERATOR COUPLING	SIGNAL GENERATOR FREQUENCY	RADIO DIAL SETTING	OUTPUT METER	ADJUST	REMARKS
1. .05MFD	High side to pin 7 (grid) of 12BE6 (V1). Low side to B-.	455KC (400%Mod)	Tuning gang fully open	Across voice coil	A1, A2, A3, A4	Adjust for maximum output. If isolation transformer is not used, reduce dummy antenna to .001MFD to reduce hum modulation.
2. "	"	1640KC	"	"	A5	"
3.	Loop	1400KC	Tune to 1400KC signal	"	A6	Fashion loop of several turns of wire and radiate signal into loop of receiver. Adjust for maximum output.

is less danger of feedback trouble between stages.

The amplified IF signal is applied to a conventional detector circuit for detection of the audio modulation. This is often called the second detector, since the action of the converter stage involves a detection process; therefore, the converter stage can be considered as the first detector. After any necessary amplification, the audio signal is applied to the speaker system of the receiver.

Tracking Principles

The IF stages are permanently tuned to the intermediate frequency during alignment, and the intermediate frequency should not be changed while the set is being operated; therefore, in order to make sure that this intermediate frequency will be obtained at the output of the converter stage whenever a signal is being received, the design of the receiver is such that the frequency of the oscillator can be maintained at a constant difference from the RF signal being tuned. The difference was 455 kc in the example described previously. To establish the 455-kc difference, the oscillator

and RF circuits are both tuned by separate sections of a ganged tuning capacitor. Both sections cannot have the same tuning effect, however. While the RF section is tuned from 535 to 1620 kc, the frequency of the oscillator section must vary from 990 to 2075 kc in order to maintain the intermediate frequency constantly at 455 kc.

The formula for the resonant frequency of a tuned circuit is:

$$f = \frac{1}{2\pi\sqrt{LC}}, \quad (1)$$

where

L = inductance in henrys,

C = capacitance in farads,

f = frequency in cycles per second.

By squaring both sides of equation 1, we obtain:

$$f^2 = \frac{1}{4\pi^2 LC}$$

where

L, C, and f are the only variables. If we double L or C, then f^2 will be halved. With a given value of inductance L, it is possible to calculate the capacitance range which we must have in order to tune through a given frequency range. For example, with the frequencies chosen in the preceding paragraph, the RF range from 1620 to 535 kc represents a frequency ratio of 3.03 to 1. To tune this range, capacitance C must vary through this ratio squared, which is about 9.2 to 1. In other words, the maximum capacity of C must be 9.2 times its minimum capacity. At the same time, the oscillator varies according to a frequency

ratio of 2.1 to 1, requiring a capacity ratio of 4.4 to 1.

Obviously, we cannot tune through capacity ratios of 9.2 to 1 and 4.4 to 1 by rotating the common tuning shaft unless the operation of one of the sections in the dual capacitor is modified. Some early radio receivers utilized a padder capacitor in series with the oscillator section, and this altered the tuning ratio in the proper manner. Theoretically, perfect tracking was obtained at two or three points of the range, and the tracking at other points was close enough to be satisfactory.

More recent models use what is termed a "cut rotor" in the oscillator section. This method accomplishes the same results and also saves materials, since no padder is needed and since the oscillator section of the capacitor is reduced in size. With proper design, this arrangement should track very closely across the entire tuning range. As a result of the advantages just mentioned, cut-rotor tuning is used almost exclusively in present-day superheterodynes.

Several circuit components may be made variable to permit the service technician to make necessary tracking adjustments. These include the small trimmer capacitors usually mounted on the ends of the stator plates of each section of the tuning gang; and in some cases, they include slug-tuned coils to obtain variable inductance.

Fig. 1 illustrates one type of loop antenna with a few turns which have been moved out of line at the factory for tracking purposes. Thus, the inductance of the loop as a whole has been lowered.

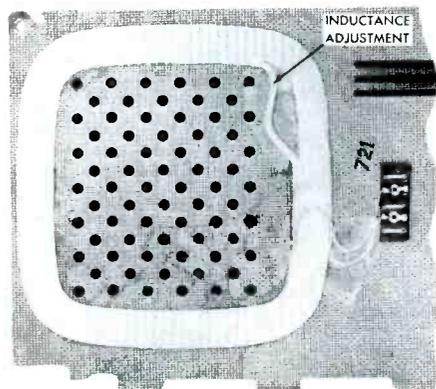


Fig. 1. Loop Antenna with Turns Moved in Order to Change Its Inductance.

* * Please turn to page 82 * *



**GENERAL CEMENT
RADIO CHEMICAL LABORATORY**
Save time and money, with this complete lab of 20 2-oz. G-C chemicals. Do all repairs to speakers, coils, dials, etc. Free metal rack included.
NO. 997 NET \$7.65



G-C ROOF-SEEL COMPOUND
Seal holes in roofs on roof-top antenna installations. Stop call-backs.
NO. 18-16 Pint can NET \$0.60



G-C LENS-TUBE CLEANER
Specially prepared to remove finger marks and spots on picture tube and lens.
NO. 216-2-2-oz. bottle NET \$0.36



G-C DE-OX-ID
Cleans and prevents oxidation on all sensitive circuit contacts, switches, etc.
NO. 19-2 2-oz. bottle NET \$0.96



G-C INSULATION AND DIPPING VARNISH
Treat field coils, chokes, noisy or buzzing transformers.
NO. 56-2 2-oz. bottle NET \$0.39



G-C SCRATCH REMOVER
Dark shade covers hairline scratches, renews appearance of TV set, furniture.
NO. 92-2 2-oz. bottle NET \$0.30



G-C DELUXE FELT-KOAT KIT
Complete flock finishing kit for applying to turntables, grilles, cabinets, etc.
NO. 180-0 NET \$2.25



G-C DIAL CORD DRESSING
Prevents dial cord slipping. Simply rub dressing stock on cord. Long lasting.
NO. 1212 NET \$0.15



G-C RADIO KNOB KIT
Kit contains 35 assorted walnut and ivory replacement knobs. Includes springs.
NO. 1140 NET \$2.82



G-C KNOB SPRING KIT
Kit of 100 knob springs in 12 different styles. Tempered spring steel.
NO. 1051 NET \$1.17




G-C TURNTABLE SPRING KIT
Kit of 50 assorted turntable springs for replacement on RCA, Philco, Zenith, etc.
NO. 6478 NET \$1.65



G-C WOOD CABINET GLUE
Repair TV and radio cabinets, furniture, etc. Fasten grill cloth, labels.
NO. 39-2 2-oz. bottle NET \$0.39

GENERAL

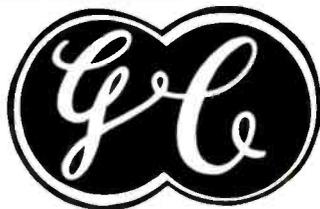

CEMENT

Ask For These
RADIO-TV SERVICE AIDS

... at Your Jobber



G-C RADIO-TV SPAGHETTI
Best grade varnished tubing in 20-ft. lengths. Fit No. 12-18 wire. Five colors.
NO. 499 NET \$1.11




G-C MIKE CONNECTOR
Single contact male type, completely shielded. Brass, bright chrome plated.
NO. 7940 NET \$0.30




G-C PHONO PLUG
Phono connector for RCA, Philco, Zenith and others. Use also for auto radio.
NO. 1742 NET \$0.06



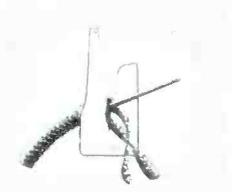
G-C STD. TERMINAL STRIPS
Bakelite insulation $\frac{1}{16}$ " thick, $\frac{3}{8}$ " spacing. Five lugs, others 1 to 12.
NO. 1785 NET \$0.072



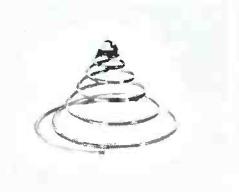G-C POCKET WIRE STRIPPER
Popular wire stripper is also scraper, cutter, screwdriver and wire winder.
NO. 757 NET \$0.30



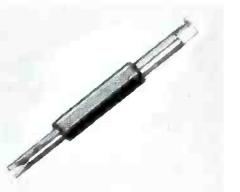G-C STATIC SPRING
Eliminates auto front wheel static noise. Riveted metal points for firm contact.
NO. 1058 NET \$0.03




G-C AUTO RADIO TUNER
Handy tuner tool for adjusting auto radio when chassis and cables are removed.
NO. 8285 NET \$0.27



G-C FAHNESTOCK CLIPS
Spring brass, $\frac{3}{4}$ " long x $\frac{3}{16}$ " wide. No. 6 mtg. hole. Box of 144. Medium Size.
NO. 6302-G NET \$2.46



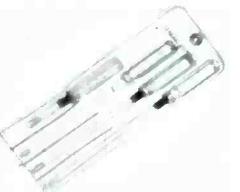G-C BANANA JACK
Standard jack, insulated $\frac{7}{16}$ " head. Mounts in $\frac{5}{16}$ " hole.
NO. 7741 Color Red NET \$0.132
NO. 7742 Color Black NET \$0.132




G-C TV ALIGNMENT KIT
Handy versatile alignment tool kit in plastic holder. Four basic tools.
NO. 8457 NET \$1.77




G-C HANDLE INSULATORS
Envelope of assorted sizes to insulate handles on pliers, cutters, etc. Neat appearing.
NO. 8118-E NET \$0.27



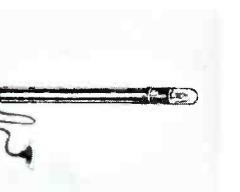G-C 6-PIECE "SLIP-ON" SET
Friction handle holds 5 plated hex sockets. Sizes: $\frac{1}{4}$ ", $\frac{3}{16}$ ", $\frac{1}{2}$ ", $\frac{3}{8}$ ", $\frac{7}{16}$ ".
NO. 715 NET \$1.35



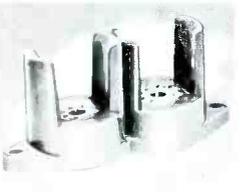G-C INSPECTION LIGHT
Service light where you want it. Ideal for production inspection. 110 v. AC-DC.
NO. 705 NET \$1.35



G-C PIN STRAIGHTENER
Straightens both miniature and jumbo-miniature tubes of both 7- and 9-pin types.
NO. 8655 NET \$1.50




G-C LIGHTNING ARRESTOR
Underwriters' approved, for all types of UHF-VHF lead-in lines. Easy to use.
NO. 8642 NET \$0.75



G-C 300-OHM CONNECTOR
Screw-type connector to splice 300-ohm twin line. Retains wire characteristics.
NO. 8095-E Env. of 2 NET \$0.27



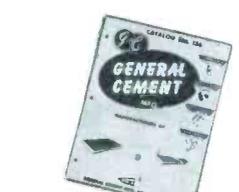G-C H. O. POWER SWITCH
D.P.S.T. toggle switch. Rated 12 amp. at 125 volts. For motors, appliances, etc.
NO. 1350 NET \$1.32



FREE!
Send postcard for your illustrated G-C Catalog.



GENERAL CEMENT MFG. CO.

903 Taylor Avenue • Rockford, Illinois

ASK YOUR JOBBER




SPECIALS OF THE MONTH

 G-C "KLEFFR LENS" LENS CLEANER NO. 9081 NET \$0.75	 G-C 3-WAY TV LINE KLIP NO. 9015 NET \$0.12	 G-C UNIV. UHF-VHF LIGHTNING ARRESTOR NO. 8642 NET \$0.75	 "MITY-V" ADJUSTABLE UHF-VHF ANTENNA NO. A-9098 NET \$2.25
---	---	---	---

Audio-Facts

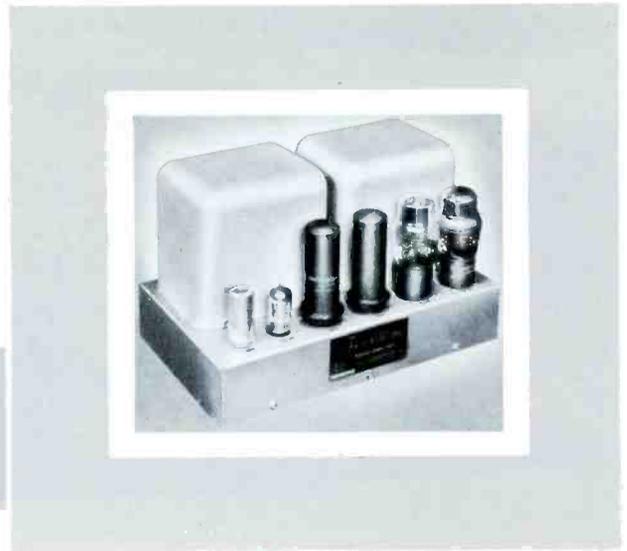A 50-Watt Power Amplifier Fairchild Model 260



The large number of amplifiers now available permits a prospective user to select one that will prove to be suitable for most any application. Although they are made in many shapes and sizes and most of them possess some special features, probably no amplifier is ever chosen without some consideration being given to whether or not its power capabilities will be adequate.

It is understood that the amplifier must develop enough power to drive the loudspeaker to reproduce the signal (music in most cases) properly. Just how varied and critical the power demands can be and how much power the amplifier must actually handle at times might surprise some users.

We discussed power requirements briefly in the article "A Small High Quality Amplifier" in the July-August 1953 issue of the PF INDEX. We mentioned how well the small

4-watt (maximum) amplifier, which was the subject of the article, performed under conditions found in the average home.

It is true that a small low-powered amplifier can provide very satisfactory results. The pleasing music that can be obtained from one of the many small high quality record players now available illustrates this fact. If the listening is done at low or very moderate levels, and if reproduction is good otherwise, the fact that extreme power output is not available does not detract from the pleasure of the average listener.

The subject of power capabilities of power amplifiers was brought to our attention at this time by some tests we have been making on the Fairchild Model 260 power amplifier. The Model 260 shown in Figs. 1, 2, and 3 is a 50-watt amplifier. Tests

were made with instruments to check specific ratings, and many listening tests were also made in an effort to form an opinion on the value and desirability of an amplifier with a power rating of 50 watts. These tests and experiments proved to be very interesting from several angles.

Before examining the circuit and features of the Model 260, we will continue the discussion about the amount of power which is required to reproduce music satisfactorily.

Most audio enthusiasts would probably voice the opinion at this point that there is no reason for having a 50-watt amplifier in a home. It is true that a sustained level of 50 watts will never be used when operating the typical home music system, but it is surprising how often peaks in the sound being reproduced can call for outputs approaching that amount.

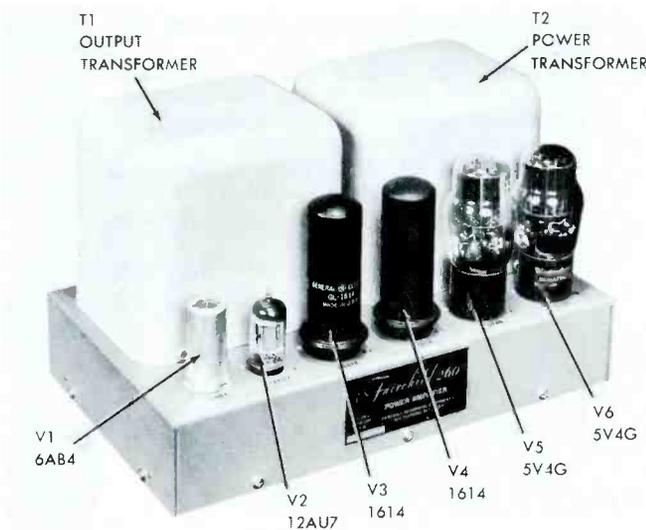


Fig. 1. Front View of Fairchild Model 260 Power Amplifier.

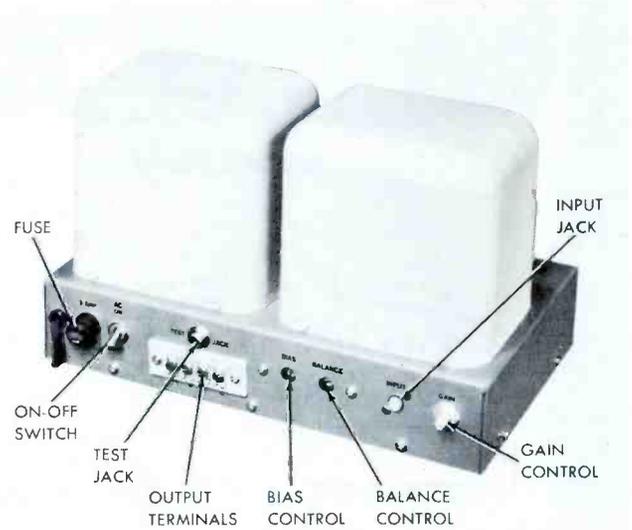


Fig. 2. Rear View of Fairchild Model 260.



SIDNEY C. SILVER, Managing Editor,
TECHNICIAN, CALDWELL-CLEMENTS, INC.
 says, "No service man will quarrel with the statement
 that properly designed, accurate test equipment is
 A must in the TV-Radio
 Repair Shop."

"An instrument of good quality can, when properly used, greatly speed up service work and boost service revenue. A unit with significant design faults, on the other hand, particularly faults (or limitations) poorly comprehended by the user can make a difficult service job out of a relatively simple one, and cause appreciable losses of time and money."

Reprints of Mr. Silver's complete article on test equipment are available at no cost from your parts jobber or Triplett Electrical Instrument Company, Bluffton, Ohio.



MODEL 3413A

TRIPLETT

TRIPLETT ELECTRICAL INSTRUMENT CO., Bluffton, Ohio

**Don't let your profit suffer
 from obsolete equipment!**

If you test 3 tubes a day
 Triplett Model 3413A will

Pay for itself in one year
 at the customary checking charge of 10 cents a tube
 you will write off the cost of only \$79.50 in actually
 less than a year. And you will have

**Faster,
 more accurate testing—Featuring:**

IMPROVED LEVER SWITCHING for complete control of each tube element. Gets at each tube pin to make an open and short check, exclusive with Triplett in this price range.

GREATER METER SENSITIVITY for the new type tubes with low cathode current.

TV PICTURE TUBE TESTS by means of the new BV adapter, without removing the tube from the receiver.

ILLUMINATED SPEED-ROLL CHART with test settings for over 700 tubes at the flick of a finger.

SPECIAL CIRCUIT FEATURE accurately compensates to provide correct voltage on each tube test.

SHORT TEST for each element by a simple flip of the switch.

BIG 6-INCH METER, direct reading "BAD-?-GOOD" dial.
TESTS NEW series filament tubes.

When mentioning audio enthusiasts, we should not overlook the group that prefers high-powered amplifiers (and probably high-powered cars); because they derive a great deal of satisfaction from knowing that they possess an outfit which can cope with any situation they are likely to encounter. In homes where music is used for background and consequently is not played at a high level, low power output is sufficient in most cases. This was particularly true not so long ago when radio broadcasts and recordings were subjected to much compressing. This caused the level to remain fairly constant with very little difference in volume between the softest and loudest passages of reproduced music.

Very little if any compression is used during most present-day FM broadcasts and during a recording process, since both processes now feature wide dynamic range. This wide range in signal level can be seen when an oscilloscope is connected across the output (speaker) terminals of the amplifier while a record is being played. It is not at all unusual to observe peaks 20 times the level which would be considered normal for the music being played.

An odd thing about the peaks is that the highest ones occur so often

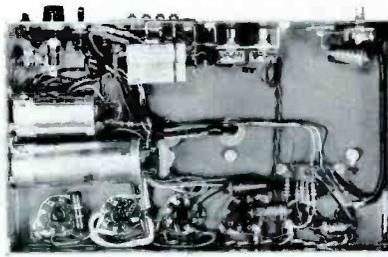


Fig. 3. Bottom View of Fairchild Model 260.

in passages in the music that do not sound so loud as other portions which the listener would judge to be the loudest. Such things fool the listener and can account for some baffling effects. Considerable power is required to reproduce the peaks properly and effectively.

To increase the output 3 db, the power must be doubled. For example, if the listening is being done at a level using one watt of power and the level is increased 3 db, the power output will have to be raised to 2 watts. Increasing the output 12 db above the original one-watt level would require 16 watts. A 15-db level would require 32 watts, and an 18-db level would call for 64 watts.

The increase from 15 db to 18 db might even pass unnoticed because

the sound level is already so high that the ear may not notice the difference. To increase the power output from 32 to 64 watts is really asking a lot from the equipment, thus it can be seen that power requirements pile up.

Of course, the value of a high-powered amplifier is unquestioned when sound is being reproduced in auditoriums, theaters, or for PA work. Driving a large speaker system for high quality reproduction of music for a large audience does require power, particularly for handling the peaks, and calls for a large margin of reserve.

Another application which requires power in excess of that furnished by the usual 20- or 25-watt amplifier is the cutting of disc recordings. Plenty of power is needed to drive a cutting head. This is especially true when cutting micro-groove recordings because of the pre-emphasis employed.

To return to the tests made on the Model 260, it was found that when some recent recordings of very high quality were played the reproduction of all high-level passages and sudden heavy chords was very clean and un-

* * Please turn to page 64 * *


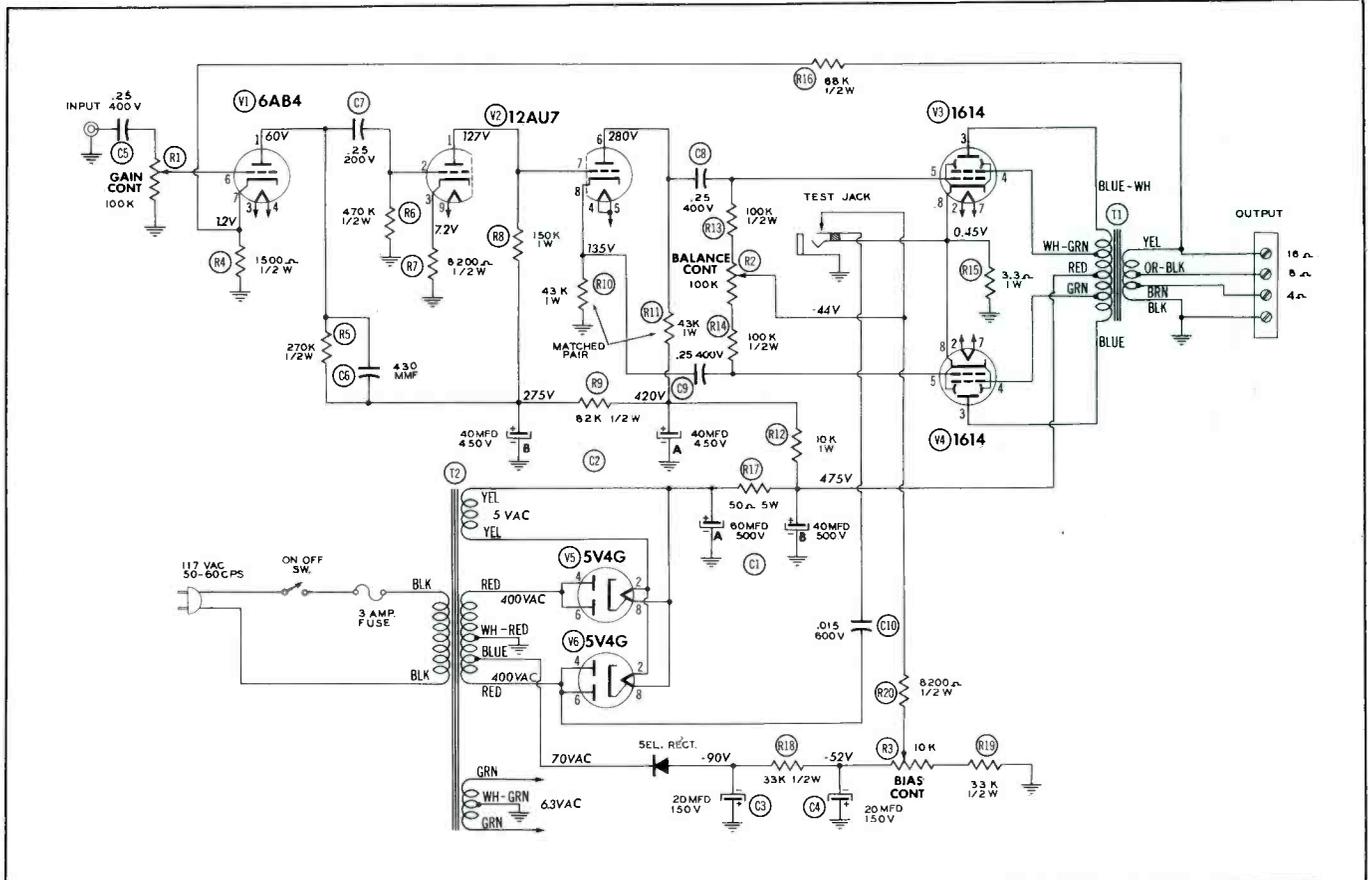


Fig. 4. Schematic of Fairchild Model 260.

150 field tests have proved to WARD jobbers:

- * Good VHF picture at as far as 200 miles on several channels
- * Excellent results at 100 miles
- * Good results in areas where no other antenna was able to bring in a picture
- * More compact—25%-75% less stacking distance
- * Channel 2-13 response as much as 40% better than any comparable antenna
- * Unique superior snap-lock bracket
- * Original WARD design all aluminum supplemented spring pressure bracket—eliminates possibility of intermittent contact

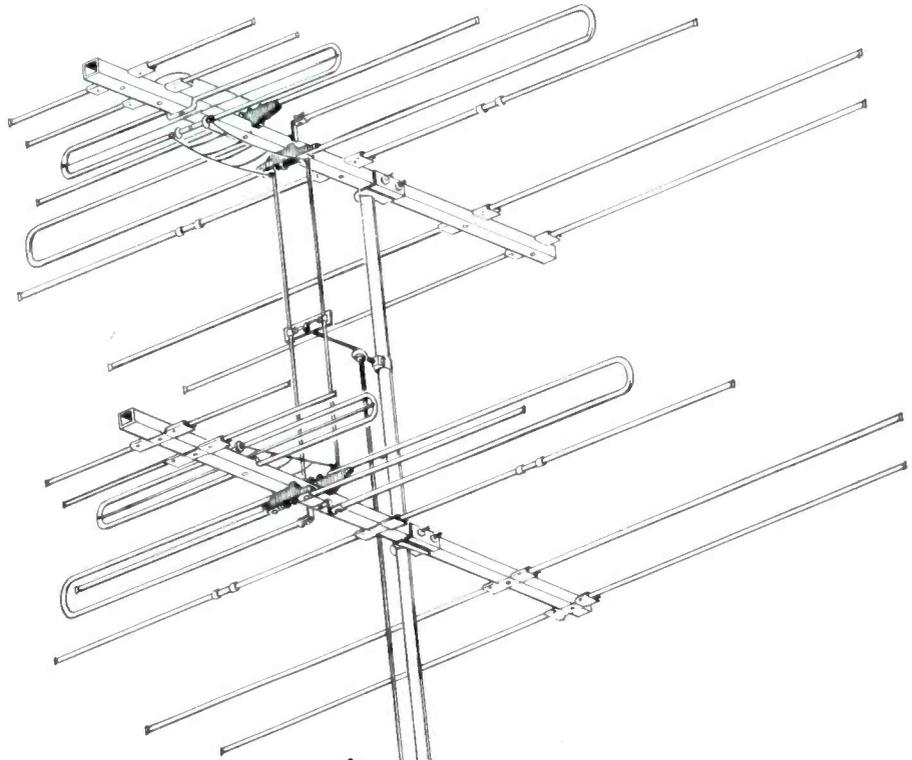

TRY ONE—you'll find why the Invader is superseding all fringe and super-fringe antennas.


WARD Model TVS 356 2 bay and stacking harness \$39.95 list

WARD Model TVS 357 4 bay stacking kit (feed harness only) \$3.95

THE INVADER* CONQUERS


sweeps all other fringe and super-fringe antennas before it

* an original WARD design

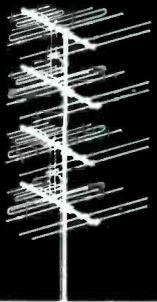

flat type Uni-plane Yagi for fringe area VHF and primary signal area UHF.

*Documental testimonials in our files

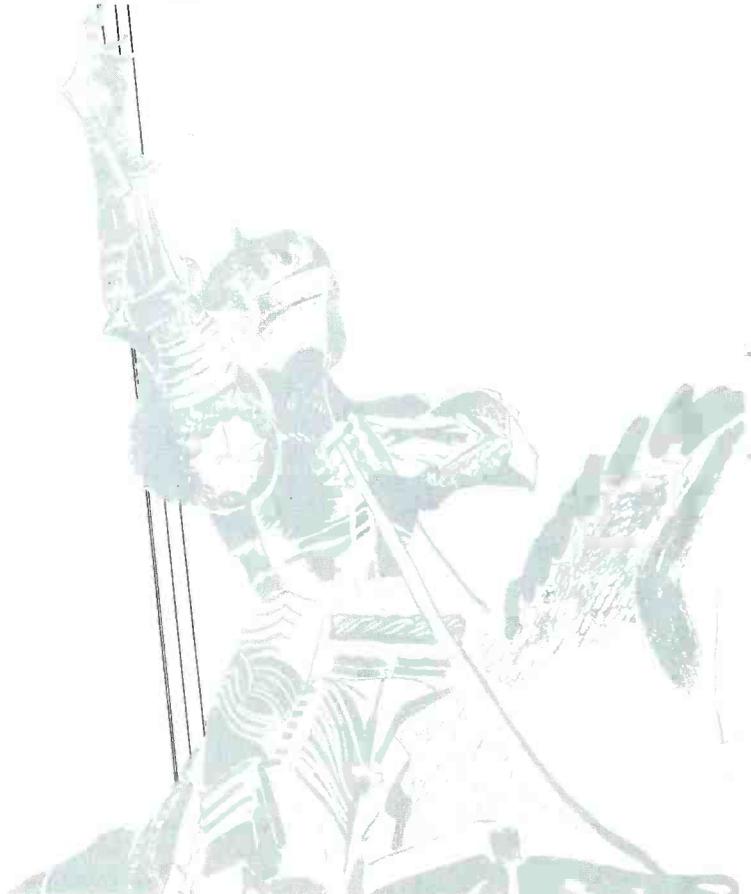

WARD PRODUCTS CORP., Cleveland 15, Ohio



Dollar and Sense Servicing

by *John Markus*

Editor-in-Chief, McGraw-Hill Radio Servicing Library

CALL BOX. When Clancy goes to a call box in Baltimore for his hourly check-in with police headquarters, he hears the latest information on robberies, stolen cars, and fugitives wanted. It's all done with Magnecord tape recorders at headquarters. The dispatcher acknowledges Clancy's call, then switches him over to a recorder that's continuously repeating the latest police news.

When new information comes in, it is recorded on a second machine and then added to the tape currently in use. After a message has been on the tape for about an hour so that it has been heard by every officer on duty, it is erased. Use of two machines eliminates any silent periods while adding or removing messages.

By eliminating time-consuming human repetition of this vital information, the electronic system has permitted cutting the police switchboard staff in half. The equipment has thus paid for itself in a matter of weeks and has already saved the department over \$50,000.

For tape-recorder salesmen, this is a dream setup — assuming they can coax the headquarters' staff to go pound the beats again so the saving can be realized.



FIRE DETECTION. In place of the forest ranger high up on those steel towers that dominate mountaintops in forest country, Raytheon proposes a rotating TV camera feeding a microwave relay transmitter aimed at a distant central location where a ranger can sit in comfort in front of a battery of monitor receivers yet see the first sign of smoke or fire just as quickly as if actually up in a tower.

TV ANTIQUES. Only 1.5 per cent of the TV sets now in use were made before July 1948, according to a nationwide spot-check survey by American Research Bureau Inc. This amounts to about 400,000 sets; therefore, you can just about let your tube stock run out on those special early TV tubes which had dropped out of use by mid-'48.



PICTUROLA. In the place where the speaker ought to be in one new phonograph, you see a brightly colored kaleidoscopic pattern that changes formations in time to music. It's called the Picturola, was built to order for Liberty Music Shop in New York City, sells for \$59.95 in console cabinet with 3-speed player, and is intended chiefly as a musical novelty for children.

A small projection lamp and lens throw a beam of light through a tiny kaleidoscope onto a frosted plastic screen. A small PM-speaker movement without cone is mounted alongside the kaleidoscope and connected in parallel with the voice coil of the regular speaker. A metal strip links the dust cap of this extra voice coil to the inch-cube kaleidoscope; consequently, the cube gets gently shaken on loud passages to produce a change of pattern. On soft steady music, the pattern quivers much like the needle of an output meter without changing color or shape.

The same idea can be used in other ways, such as for giving action to a grass-skirted cardboard hula dancer atop a radio (a sure traffic stopper for your shop window if you perch her atop a table radio to which she's connected), for jiggling the arms or legs of other cardboard figures, or for putting a wiggle into a furry toy mouse atop the radio. For the last, you might put up a price card: WALTZING MICE, \$9.95 each.

GETTING ACQUAINTED. After each orchestral selection at a recent concert in huge Constitution Hall in Washington, the audience heard the same number played back on high-fidelity equipment by a magnetic tape recorder. Purpose was to acquaint music fans with high-fidelity and to acquaint high-fidelity fans with good music, according to promotion by the sponsoring sound-equipment manufacturers and local radio station WGMS. To us, a still more important result would be acquainting high-fidelity fans with high fidelity; some get so familiar with screechy, improperly equalized hi-fi systems that live music sounds distorted to them.



SWEET MUSIC. Former radio service technician Burton Minshall of London, Ontario now heads a million-dollar business because his wife wanted an organ in 1935 and he couldn't afford such things on a \$25-a-week salary. Working in spare time for three years with around \$40 worth of radio parts, he produced an electronic organ that delighted Mrs. Minshall and brought demands for more. The second was sold to a funeral parlor for \$400 and the third to another funeral parlor for \$625. From that point, the business built up to the extent that his two firms — Minshall Organ Ltd., of Canada and Minshall Organ, Inc., of Brattleboro Vt. — built some 2,500 organs priced from \$995 to \$3,000.

Your own future may likewise lie in what you do in your spare time, evenings and weekends. As a suggestion, there's still a demand and need for a really good radio type of metal detector — one that's reliable, light in weight, has wide coverage and deep penetration (or an adjustment for attaining varying degrees of each), and can be waterproofed for working under water. Transistors may be the answer.


* * Please turn to page 49 * *

**FOR A LIMITED TIME
to introduce
the first NEW design of selenium rectifiers**

in OVER 20 YEARS

Koolseel rectifiers

for the price of

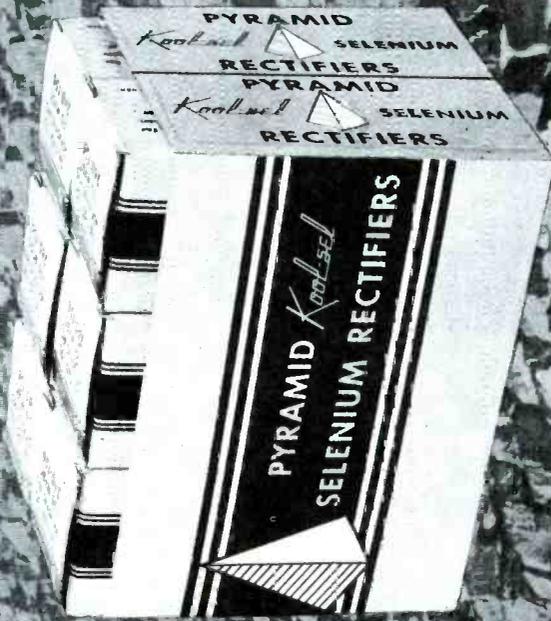

Service equipment will be better than new when you replace with a Koolseel rectifier by Pyramid.

No center mounting

Full air ventilation between plates

Light contact and constant assembly pressure

No center hot spots

Lightest weight per unit of output power

Lower initial forward resistance—better voltage regulation

Smaller overall size for each rating—cost no more

Better for all electrical and electronic equipment because of

• Improved convection cooling

• Simpler mounting

• Longer life and minimum aging

• Designed for more rugged service and rated for use in high ambient temperatures

In stock at your Pyramid jobber now.

PYRAMID



ELECTRIC COMPANY 145 Hudson Blvd., North Bergen, N. J.



STAR-HELIX

RAINBOW ANTENNA

A STAR IS BORN!



THE NEWEST STAR IN THE JFD RAINBOW ANTENNA GALAXY

It's out of this world! . . . A radical new departure in all-channel black and white or color performance—featuring the JFD Hi-Plex folded dipole system—the greatest antenna advance since the origin of the Inline Yagi.

MODEL		LIST
SX711	Single	\$25.50
SX711S*	Stacked	\$52.50

*Complete with Hi-Gain Stacking Transformers

-  **SUN** From JFD, the fountainhead of Antenna development
-  **MOON** As sensitive in signal attraction as the Moon
-  **VENUS** As beautiful as *Verus*
-  **MERCURY** As quick to install as *Mercury*
-  **SATURN** As spectacular as *Saturn*
-  **JUPITER** As outstanding as *Jupiter*
-  **MARS** As powerful as *Mars*

Look to JFD for Engineering Leadership!



THE MOST OUTSTANDING ANTENNA ADVANCE SINCE THE ORIGIN OF THE INLINE YAGI!



STAR-HELIX



RAINBOW ANTENNA

NOW—2 GREAT JFD HELIX RAINBOW ARRAYS TO CHOOSE FROM:

1. Jet-Helix featuring the new JFD Flat Plane Helical-Conical Concept.
2. Star-Helix featuring the new JFD Inline Helical-Yagi Concept.

TOMORROW'S COLOR ANTENNA — TODAY!

A giant in black and white performance. Flat microwave type helical section composed of individual non-linear additive collectors, each tuned separately for highest gain and sharpest directivity on one high band channel.

Revolutionary new Hi-Plex folded dipole design transforms low band collector into 3 half wave length antennas that develop highest in-phase current on high band. Result: sustained high signal magnitude on all low and high band channels — plus sharp forward unidirectional response.

A giant in color performance! Possesses consistently flat gain across the spectrum, uniformly high signal to noise ratio, narrow beam width, and close 300 ohm impedance match essential for fidelity color reception.

Special matching Booster Transformer permits close stacking for maximum high band response and electrical wide stacking for optimum low band response.

Inline designed for physically streamlined appearance. Maximum eye-appeal. Minimum wind resistance.

Completely preassembled. Just flip elements into place. New "Hi-Tension" aluminum brackets lock elements permanently in place. No tools. No screws.

Built for permanence — constructed of matchless aluminum by ALCOA.

300 ohm impedance for 100% signal transfer.

COMPARE THE PERFORMANCE OF THE STAR HELIX WITH ANY VHF ANTENNA YOU ARE NOW USING!

ANTENNA	CHANNELS												
	2	3	4	5	6	7	8	9	10	11	12	13	
"STAR-HELIX" SX711	4.75	5.	6.25	7.25	7.	14.5	14.	13.25	13.5	13.75	13.75	14.5	
"STAR-HELIX" SX711S	8.	8.5	9.	10.5	10.5	17.5	17.	15.75	16.	16.	16.	17.5	
"DODO" Screen Type REFLECTOR	4.75	4.5	7.2	7.1	7.	11.	11.2	11.8	11.5	11.1	12.1	12.	
"SUPER DODO" Screen Type REFLECTOR	6.3	6.8	8.8	7.8	7.5	9.5	11.2	11.8	12.	11.1	12.1	12.	
Broad Band Yagi with Phasing Stubs	4.3	5.7	4.5	7.1	9.	13.	14.	13.5	14.	13.	14.	15.	
Inline Yagi with Phasing Stubs	5.2	5.5	6.	8.	8.	11.5	9.5	10.	9.	11.	11.5	11.8	
Inline Yagi with Triple Dipole	5.25	6.25	7.	7.5	7.75	10.5	10.25	8.75	9.5	10.25	11.	11.75	
Super-Inline Yagi with Triple Dipole	6.75	7.	9.2	9.	10.	11.5	12.2	12.8	13.5	13.1	14.6	15.5	


Highest Front-to-Back Ratio ever in Broad Band design

Chan.	DB	Rel. Volt.
2	17.	7:1
3	22.	12.5:1
4	21.	11.5:1
5	20.	10:1
6	20.	10:1
7	10.5	3.5:1

Chan.	DB	Rel. Volt.
8	18.	8:1
9	19.	9:1
10	25.	18:1
11	22.	12.5:1
12	25.	18:1
13	13.	4.5:1


HERE'S HOW THE JFD HI-PLEX SYSTEM WORKS!

ON LOW BAND

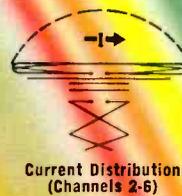


Full sized low band half wave folded dipole develops maximum in-phase current across its length on low band channels 2 to 6. Entire dipole length acts as effective capturing device because it operates totally on fundamental frequency unimpeded by additional radiating devices used in other broad band systems to raise high band gain.

ON HIGH BAND

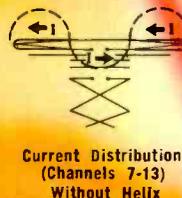

When operating on high band frequencies, JFD Hi-Plex phasers transform each low-band collector extremity into separate high band dipoles. These electrically isolated elements function as independent collectors operating on their fundamental frequency, each developing maximum in-phase current on channels 7 to 13. Out-of-phase voltage of center section of folded dipole is minimized and isolated from other high band dipoles by blocking action of two anterior high band phasing elements.

ON BOTH LOW AND HIGH BANDS

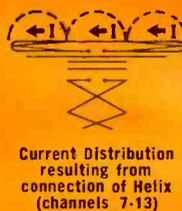

Special phasing harness feeds channel 7 to 13 energy produced by flat plane helix into Hi-Plex collector in same phase and magnitude of other 2 high band dipoles. Result in in-phase additive operation of 3 half-wave antennas balanced for increased high band gain and unlimited signal strength on low band channels — Plus 300 ohm impedance to assure 100% energy transfer.


65.6% S/N Figure of Merit*

*The S/N Figure of Merit sums up the major individual characteristics of an antenna in one concise value. Write for S/N Figure of Merit engineering folder No. 315 for complete details.

Gain Represents That Over 1/2 Wave Reference Folded Dipole


Up to 18 db on High Band*

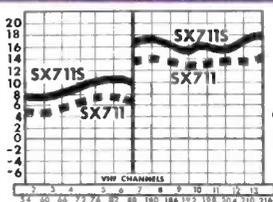*Tested in strict accordance with RETMA antenna measuring standards



Up to 11 db on Low Band*

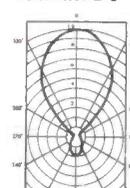Horizontal Pattern (Relative Voltage) Channel 2-6



Today's Fastest Installing Broad Band Antenna! As Easy to Handle as Power Steering. The Slowest Part Is Opening the carton! Remarkable new JFD Hi-Tension Aluminum Bracket Design Cuts Installation Time 250%. No tools or labor necessary. No screws or hardware to tighten. Just flip elements into place.

INTERNATIONAL DIVISION

15 Moore Street, New York 4, U. S. A.



MANUFACTURING CO., INC. Brooklyn 4, New York

Color TV Training Series

(Continued from page 9)

half is a south pole. The alignment of the molecules in the ring can be seen in Fig. 9-34.

Each of the magnetic rings in the color-purity device may be rotated 360 degrees. In this manner, the unlike poles of each ring may be placed adjacent to each other so that no appreciable field exists in the space at the center of the rings. By rotating one magnet slightly, a weak magnetic field is produced. This field becomes increasingly stronger as one ring is rotated with respect to the other, and the field reaches maximum strength when the like poles of the two rings are adjacent to each other.

The drawing in Fig. 9-35 shows the magnetic field produced in the space at the center of the purity device. This field is fairly uniform and exerts an equal force on all three beams. The force is at right angles to the direction of the magnetic field.

By adjusting the strength and direction of the purity field, the beams can be caused to enter the deflection field at the proper points. Fig. 9-36 shows a beam entering at the proper point as well as at an improper point in the deflection field. Only the red beam is shown in order to simplify the drawing. When the beam enters the deflection plane at point A, it will pass through the shadow mask at the proper angle throughout the scanning process and will produce a pure red raster.

If the beam enters the deflection plane at any other point, color impurity will result. Such a condition would occur if the red beam were to enter the deflection plane at point B in Fig. 9-36. Note that the dotted line from point B to the screen enters the shadow mask at a different angle than the line from point A to the screen. This condition can be corrected by the use of the purity magnet. The field of the magnet can be aligned so that the beam will enter the deflection plane at point A. The red beam is shown to be so aligned in the drawing.

The Deflection Yoke.

As previously stated, the position of the deflection yoke is a factor in obtaining color purity. This is also illustrated in Fig. 9-36. Assume that the position of the yoke along the neck of the tube is such that the red beam is deflected at point C. The dotted line from point C to the screen indicates the angle at which the beam would pass through the shadow mask. Since this angle is incorrect, color impurity would result. An improperly posi-



Fig. 9-33. Magnetic Rings Used in the Color-Purity Device. (Sample Courtesy of RCA.)

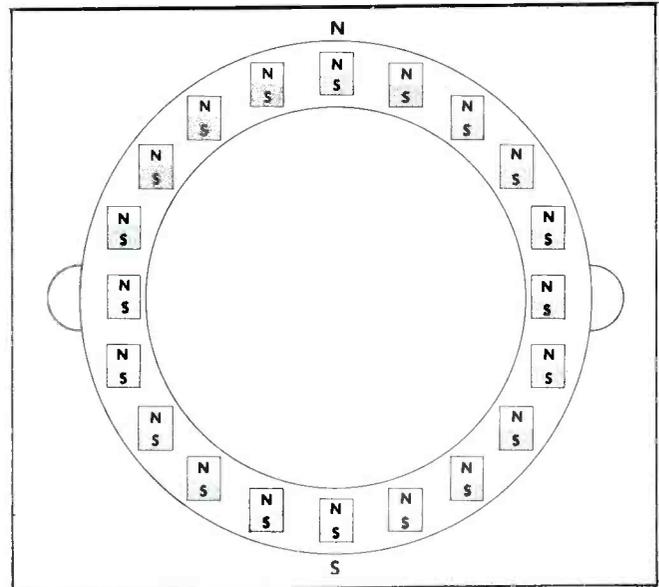


Fig. 9-34. Alignment of the Molecules in Either One of the Rings Used in the Purity Magnet.

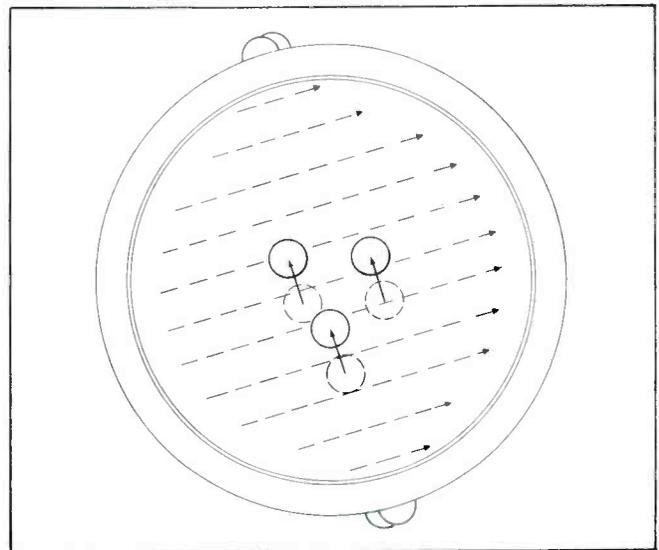


Fig. 9-35. The Field Produced by the Purity Magnet Exerts on Each Beam an Equal Force at Right Angles to the Direction of the Field.

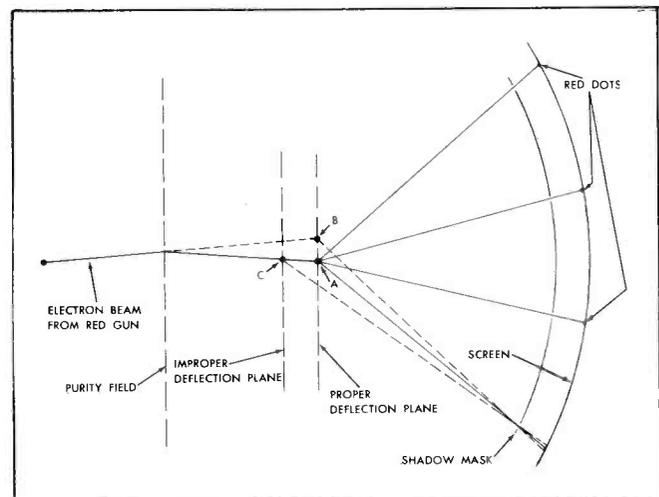


Fig. 9-36. Paths of the Red Beam As a Result of Proper and Improper Settings of the Purity Magnet and the Yoke Position.

LOOK TO THE LITTLE INDIAN  FOR

THE **BIGGEST** VALUE IN

MOLDED PAPER TUBULAR CAPACITORS

the Sangamo

Telechief[®]



The Telechief will outlive all other tubulars! Major manufacturers' test and stamp of approval prove that Telechiefs have longer life. They have a final insulation resistance value 10 to 15 times greater than any other paper tubular—because they're molded in HUMIDITITE!



The Telechief outperforms all other molded paper tubulars in moisture resistance... in high temperature operation... in holding its rated capacity under all conditions.



EXTRA VALUE AT NO EXTRA COST! This amazing new capacitor — that meets specifications so tough that no previously existing paper tubular could approach them — is a *premium* tubular at the price of an ordinary one. See your Sangamo Distributor today!

Those who know  *choose Sangamo*

SANGAMO ELECTRIC COMPANY

MARION, ILLINOIS

tioned deflection yoke will cause color impurity around the edges of the screen, since the error in the angle is greatest at those parts of the screen.

A discussion of the deflection yoke used with a three-beam picture tube was included in the data on tubes employing the electrostatic convergence principle. The yoke for a tube using magnetic convergence is different only in that special shielding techniques are required. These techniques are necessary to prevent the magnetic fields around the yoke from affecting the fields around the convergence assembly.

The photograph in Fig. 9-37 shows a yoke which employs special shields for this purpose. Note that a copper plate is placed directly behind the yoke assembly and that a ferrite ring is mounted a short distance behind the copper plate. These components prevent electrostatic and electromagnetic coupling between the yoke windings and the convergence magnets.

Field-Neutralizing Devices and Magnetic Shielding.

The earth's magnetic field and stray fields generated within the receiver can cause a severe misalignment of the three beams in the color picture tube. Unless certain precautions are taken to prevent this condition, poor image reproduction will result. For this reason, field-neutralizing components and magnetic shielding are commonly used as auxiliary devices for the three-beam tube.

The area in which the beams are most likely to be affected by stray fields extends from the plane of the deflection field to the viewing screen. A metal shield is placed around the bell of the tube to provide a path for the flux lines of these fields. The flux lines will follow the contour of the shield and are therefore prevented from extending into the beam paths.

The photograph in Fig. 9-38 shows that the cone shield does not extend beyond the welded joint between the main cone of the tube and the faceplate section. As a result, this shield does not protect the beams as they pass between the shadow mask and the viewing screen. The magnets shown around the rim of the faceplate section are used to counteract stray fields which would affect the positions of the beams in this area. In an earlier method of doing this, a field-neutralizing coil which encircled the faceplate section was employed. (The use of this device was described in Part IX of this Color TV Training Series.) Individual magnets for this application do the job better than a coil, since the strength and direction of the stray fields may not be the same at different points around the rim of the tube. Each magnet may be turned so that it neutralizes only the stray fields in its immediate area.

Another type of field-neutralizing magnet is shown in Fig. 9-39. The cylindrical magnet is polarized in a direction that is perpendicular to its axis. Several of these devices are mounted around the rim strap. Two adjustments can be made in conjunction with each magnet. One adjustment involves the movement of the magnet toward or away from the tube. The other adjustment is performed by rotation of the magnet so that the direction of its field is changed.

It was previously mentioned that beam-positioning magnets, a lateral-correction magnet, and convergence electromagnets were used to ensure beam convergence at all points on the shadow mask. The following discussion concerns these auxiliary components.

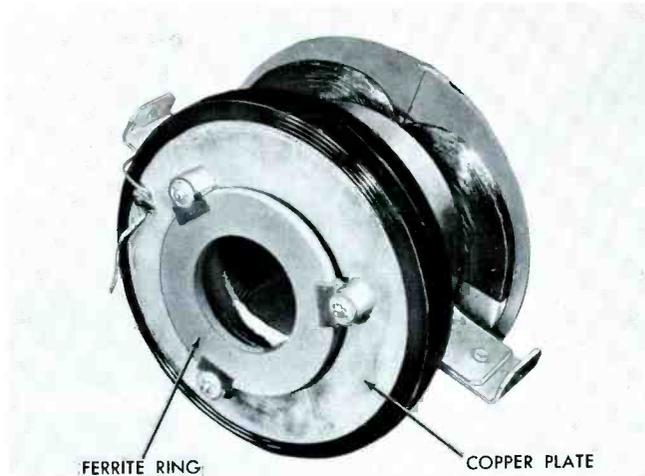


Fig. 9-37. Deflection Yoke Used With a Tube Which Employs the Principle of Magnetic Convergence. (Sample Courtesy of RCA.)

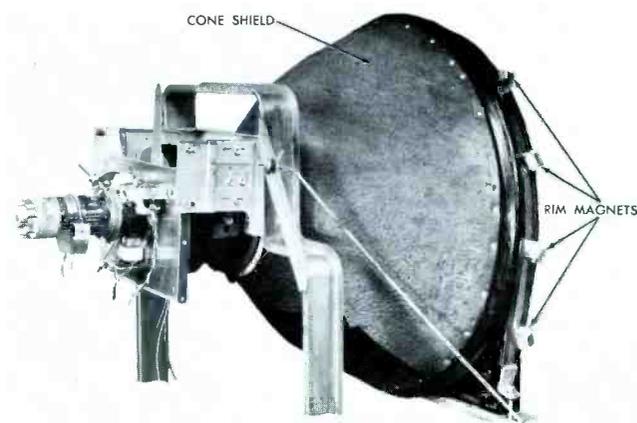


Fig. 9-38. Metal Shield and Rim Magnets Used in Motorola Model 19CT1.



Fig. 9-39. One of the Rim Magnets Used in the RCA Victor Model 21CT55.

Beam-Positioning Magnets.

The photograph in Fig. 9-40 shows the physical appearance of the beam-positioning magnets used in the Motorola Model 19CT1 color receiver. In the photograph, the magnets are spaced 120 degrees apart to correspond with the positions of the electron guns. These magnets are placed in a plane which is approximately perpendicular to the central axis of the picture tube and which intersects the three sets of pole pieces at the end of the gun assembly. The distance from any one of the magnets to the neck of the tube may be altered by loosening the thumbscrew and sliding the shaft through its mounting.

offer

MORE PROGRAMS

and you make

MORE SALES!

The public is buying entertainment. Radios are simply the means to that end. So, the more programs offered, the more sales. In FM areas, you can now offer such FM exclusives as hi-fi music, educational features, informative forums, farm co-op programs, etc., along with usual AM programs generally broadcast on FM as well. In UHF TV areas, you can offer the additional UHF programs.

GRANCO "Music Hall" FM RECEIVER

- The FM receiver that millions have been waiting for.
- Powerful six-tube chassis for high sensitivity and drift-free performance.
- Exclusive coaxial tuning—outstanding selectivity and stability.
- Amazing volume. Only table radio in its price class with a big, oval, 6" speaker.
- With built-in antenna. No installation required.
- Smart paragrid styling. Fits anywhere. In three colors. Blends with any decor. Ultra-compact.



Only \$29.95!

GRANCO Model LCU-A UHF CONVERTER

- Combining quality and price, and reflecting the outstanding "know-how" in UHF converters.
- Includes complete stage of amplification for greatest sensitivity over entire UHF band.
- Features a stage of preselection—a "must" in areas with two or more UHF or even VHF channels.
- Its unique coaxial tuner means continuous coverage of desired UHF channel.
- Outstanding eye appeal. Attractive plastic cabinet. Ultra-compact. Fits anywhere. Blends anywhere.

Only \$29.95!



Write, Wire, 'Phonel Get the merchandising story behind the Granco Line. Literature and sales details on request. Better still, send us that order for these fast-moving items.

Granco

LEADING MANUFACTURER OF UHF CONVERTERS AND FM RECEIVERS

GRANCO PRODUCTS, INC.
36-17 20th AVENUE LONG ISLAND CITY 5, N. Y.

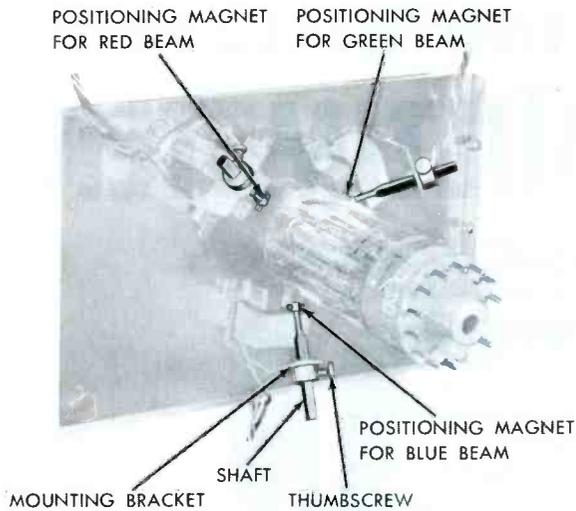


Fig. 9-40. Beam-Positioning Magnets Used in the Motorola Model 19CT1.

The drawing in Fig. 9-41 shows the three fields which are produced by the positioning magnets. The strengths of the fields produced between the pairs of pole pieces are dependent upon the settings of the magnets. The force exerted upon each beam is perpendicular to the direction of the magnetic field between the pole pieces associated with that beam. Thus, the beams are deflected in directions indicated by the solid arrows in Fig. 9-41. The amount of deflection on each beam is a function of the strength of the magnetic field between its associated pole pieces. Let us assume for the moment that the beams strike the shadow mask of a particular tube in the pattern shown in Fig. 9-42. The dots represent the centers of the beams. The arrows indicate the directions that the beams can be moved by the fields between the pole pieces. Note that any two of the three beams in this tube can be converged but that all three beams cannot be converged. This is an undesirable condition. In order to correct the error in convergence, a lateral-correction magnet is used.

The Lateral-Correction Magnet.

The lateral-correction magnet is used to provide a field which will move the blue beam in a horizontal direction. This device is placed on the neck of the picture tube so that its field intersects the special pole pieces mounted on the focus element of the blue gun. The magnetic field produced between these pole pieces and the direction of beam movement caused by this field can be seen in Fig. 9-43. Let us see how the lateral-correction device aids in obtaining convergence of all three beams.

Consider a condition in which the blue beam cannot be made to converge at the same point at which the red and green beams converge. Such a condition was described in connection with Fig. 9-42. Fig. 9-44 shows the points at which the beams can be made to strike the shadow mask by means of the positioning magnets. The dotted arrow shows the direction in which the blue beam can be moved through the use of the lateral-correction magnet. Note that a movement of the blue beam in a lateral direction will cause all three beams to be converged.

Two different types of lateral-correction devices are shown in Fig. 9-45. Both of these components will produce the same effect; therefore, either type may be used to obtain the desired result. The magnet in the device labeled A in Fig. 9-45 is contained in a circular plastic piece which can be revolved 360 degrees; thus, a means is provided for varying the strength and revers -

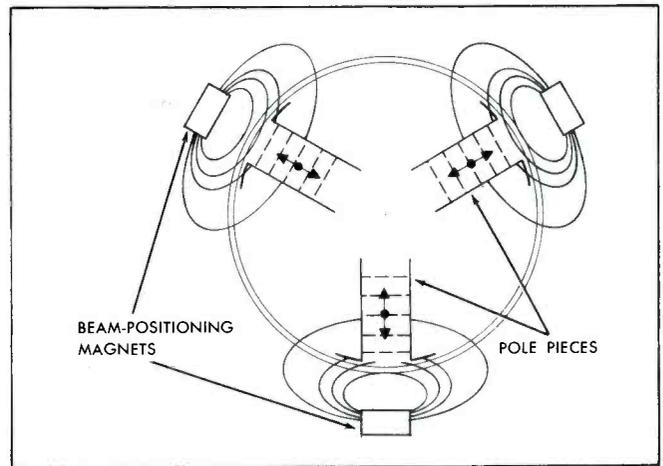


Fig. 9-41. Possible Directions of the Force Exerted Upon Each Beam by the Field of Its Associated Positioning Magnet.

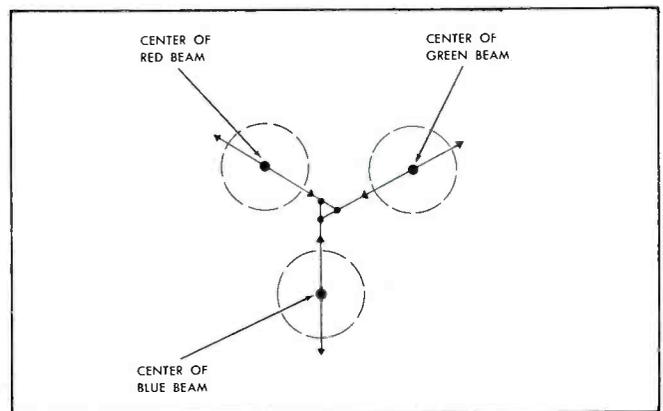


Fig. 9-42. Beams on the Shadow Mask and Possible Directions They Can Be Moved by Means of the Positioning Magnets.

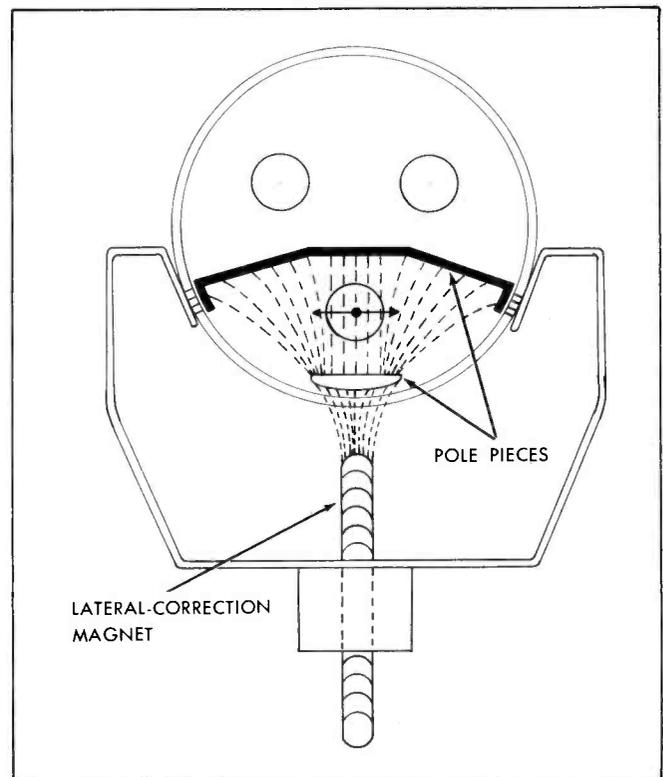


Fig. 9-43. The Field of the Lateral-Correction Magnet Deflects the Blue Beam in a Horizontal Direction.

the KEY to your problem

phastron "555" metal-cased MULTIMETERS

the NEW LOOK in



POCKET SIZE WITH A 4 7/8" LENGTH SCALE

WE LEAVE IT TO YOU

WOULD YOU BUY A PLASTIC-CASED WRIST WATCH . . .

if you could buy the finest movement in a magnetically shielded metal case?

Phastron, world famous manufacturer of ENVIRONMENT FREE PRECISION AIRCRAFT EQUIPMENT for Military and Industrial uses introduces a new concept in Multimeters. This magnetically shielded, metal-cased "555" compares with plastic-cased multimeters as a fine watch in a precious metal case would compare with a plastic wrist watch.

The shielded, shatterproof and anti-magnetic case insures continued accuracy and integrity of this instrument for years to come.

Phastron "555" Multimeter incorporates more ranges, including AC current, greater visibility, simplified and functional controls and the greatest value offered to date.


See the Phastron "555", note its many outstanding features, its beautiful satin chrome case, its compactness and light weight, and you will know why

"YOU CANNOT BUY BETTER"

AC CURRENT RANGES
SEPARATE RANGE & FUNCTION SWITCHES
ONLY 2 JACKS




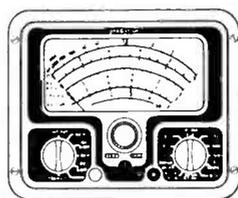COLOR CODED SCALES ARE RED, GREEN, BLUE & BLACK
ACCURACY 3% DC, 4% AC



PANEL MOUNTING ADAPTER \$1.50

GENUINE LEATHER CARRYING CASE
\$5.95

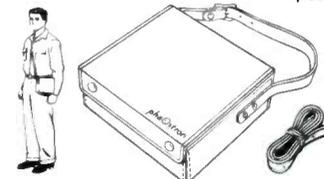

"555" MULTIMETER
complete with probes and batteries
at your **PARTS DISTRIBUTOR**

\$39.95

Manufactured by PHAOSTRON COMPANY • 151 Pasadena Avenue • South Pasadena, Calif., U.S.A.

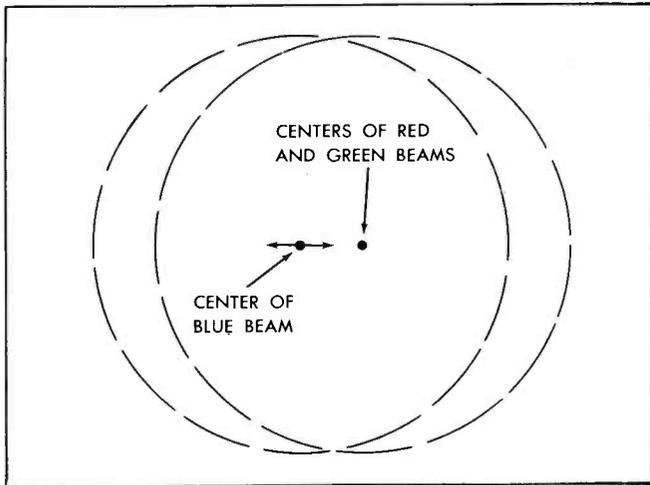


Fig. 9-44. Beams on the Shadow Mask and Possible Directions the Blue Beam Can Be Moved by Means of the Lateral-Correction Magnet.

ing the direction of the magnetic field. The magnet used in the device labeled B is threaded over its entire length so that the distance between the magnet and the neck of the tube may be varied as needed. If a reverse field is required, the magnet can be reversed in the assembly.

Dynamic-Convergence Electromagnets.

It has been pointed out that the distance the beams must travel from the plane of deflection to the shadow mask is greater at the edges than at the center of the screen. The convergence force must be varied during the scanning process if the beams are to converge at all points on the shadow mask. On the type of tube under discussion, an assembly of electromagnets is used to supply the dynamic convergence force. This assembly is positioned on the neck of the tube so that the field from each one of the electromagnets is coupled to the pair of pole pieces at the end of each electron gun.

As shown in Fig. 9-46, the forces exerted upon the beams are radial with respect to the axis of the tube. It may be recalled that this description also applies to the forces produced by the beam-positioning magnets; therefore, it can be said that the fields produced by the electromagnets aid or oppose the fields produced by the positioning magnets. Dynamic voltages at the horizontal and vertical-scanning frequencies are applied to each of the electromagnets. As a result, the field produced by a positioning magnet and the field produced by the associated electromagnet will aid each other when current through the electromagnet flows in one direction and will oppose each other when the current flow is reversed. This being the case, the beams can be independently di-



Fig. 9-45. Lateral-Correction Devices Used in (A) RCA Victor Model 21CT55 and (B) Motorola Model 19CT1.

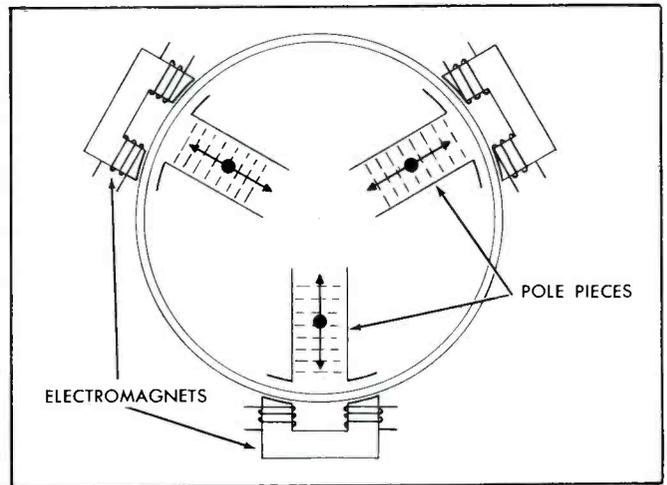


Fig. 9-46. Possible Directions of the Force Exerted Upon Each Beam by the Field of Its Associated Electromagnet.

rected so that they converge on the shadow mask at all times during the scanning process. Although earlier versions of color picture tubes employed a single element to provide dynamic convergence of all three beams simultaneously, it was found that a tube on which individual convergence adjustments could be made for each beam provided better over-all convergence. The tube under discussion is such a tube.

Again referring to Fig. 9-46, the reader will note that the electromagnets have horseshoe-shaped cores. These cores are constructed so that they can be aligned with the pole pieces in the tube. Two separate windings are found on each core. It is to these windings that the dynamic convergence voltages are applied. The nature of these voltages and their derivation will be discussed later in this section.

The photograph in Fig. 9-47 shows the electromagnets and their method of mounting in the Motorola Model 19CT1. This arrangement is typical in receivers which employ this type of picture tube.

DYNAMIC-CONVERGENCE CIRCUITS

Motorola Model 19CT1.

A schematic diagram of the dynamic-convergence circuits used in the Motorola Model 19CT1 color receiver

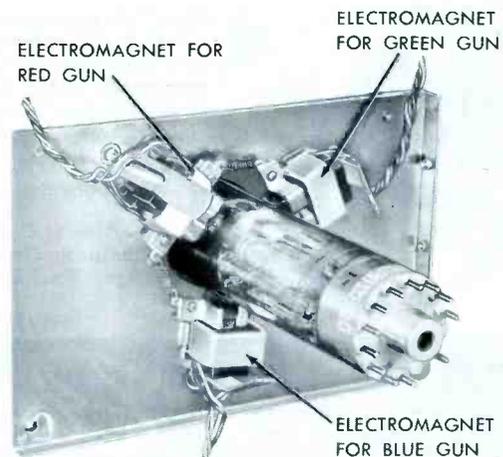


Fig. 9-47. Dynamic-Convergence Electromagnets Used in the Motorola Model 19CT1.

Ask "The Man on the Roof"
why he prefers

South River



Take **CHIMNEY BANDING** for instance...



Why take this?

The troublesome watchspring effect —Some servicemen have to put up with banding that has a tight spiral "set". Bands of this kind can easily be spotted by their reluctance to stay put. Placement around the chimney is difficult and time consuming.



You can have this?



This is the "free-opening" South River Band. Remove the retaining tape and you'll see it naturally unwinds for easy placement around the chimney. That's South River's way of making things easier for the man-on-the-roof.



NEW!

**Hi-Strength Aluminum Guy Cable Equivalent to 6-18 Steel Wire
Highly Resistant to Atmospheric Corrosion**



◀ This 7-strand aluminum guy cable of 17 ga. Alclad 56S alloy is specially made for TV guying purposes. It should not be confused with converted clothesline types of cable. Our particular cable has a "tight" twist that gives maximum strength, minimum wind resistance and ice load, does not "basket" when bent. Grey Alclad finish.

Available in 100 ft. coils individually boxed, or ten 100 ft. coils, interconnected and packed 1000 ft. to the box.

Also . . . for Lightning Protection; our EC Aluminum Ground Wire. High conductivity #8 gauge. Packaged 100 ft. per coil. ▶



WRITE FOR NEW 1955 CATALOG

South River

METAL PRODUCTS CO., INC.
South River, New Jersey

PIONEER MANUFACTURER AND OUTSTANDING PRODUCER OF THE FINEST LINE OF ANTENNA MOUNTING ACCESSORIES

is shown in Fig. 9-48. The coils in the assembly of electromagnets are designated as T10, T11, and T12. The diagram shows that a convergence coil and a tilt coil are used with each electromagnet. Generally speaking, it can be said that the field produced by the convergence coil on the electromagnet determines the maximum amount of dynamic-convergence correction obtained. The field produced by the tilt coil determines the time during vertical scanning when maximum correction is obtained. The term "tilt" is used because the action of the tilt coil produces an effect which makes a vertical row of colored dots slant to the right or left on a picture-tube screen as the amplitude of the voltage applied to the tilt coil is varied.

Let us first consider the action of the circuits with respect to the convergence coils. The horizontal-phase coil and the .01-mfd capacitor associated with each of the convergence coils form resonant circuits at the horizontal-oscillator frequency. A sine wave at the horizontal-scanning rate is developed across each of these resonant circuits by a pulse from a winding on the horizontal-output transformer. The convergence-coil circuits which are effective at the horizontal frequency are shown in Fig. 9-49. The .047-mfd capacitors and the vertical-amplitude controls in Fig. 9-48 have been eliminated in Fig. 9-49 because the reactances of the capacitors are negligible at the horizontal frequency.

The sine wave at the horizontal frequency is applied to each of the convergence coils through the horizontal-amplitude controls. Each control provides the means for changing the voltage across its associated convergence coil so that the strength of the field at the horizontal frequency around the convergence coil may be varied as needed. The core in each of the phase coils can be adjusted to shape the current waveform as required to obtain the best convergence in the horizontal plane.

Further examination of the circuit drawing in Fig. 9-48 will show that the saw-tooth current from the vertical-output stage passes through the three vertical-phase controls and through the 2-henry choke L56 to a B+ point at the junction of R148 and C3D. This saw-tooth current causes a parabolic voltage at the vertical-oscillator frequency to be developed across the parallel circuit formed by C14A and L56. This voltage is coupled to the convergence coils through C14B, the horizontal-phase coils, and the vertical-amplitude controls.

The equivalent convergence-coil circuit at the vertical frequency is shown in Fig. 9-50. The 100-mfd capacitor C14B and the horizontal-phase coils are not shown because the reactances of these components are negligible at 60 cycles. A parabolic voltage at the vertical-oscillator frequency is applied to each of the convergence coils through its respective amplitude control. Each control provides the means for changing the voltage at the vertical frequency across its associated coil so that the strength of the field around each coil may be varied as needed.

A saw-tooth voltage is developed across each of the vertical-phase controls as a result of the current from the plate of the vertical-output stage. The drawing in Fig. 9-50 shows that the center tap and rotor arm of each control are connected to opposite ends of an associated tilt coil. The amplitude and polarity of the saw-tooth voltage which is applied across any one of the tilt coils depend upon the relative position of the rotor arm on the associated phase control with respect to the center tap on that control.

Since the convergence and tilt coils are wound on the same core, the fields generated by these coils are

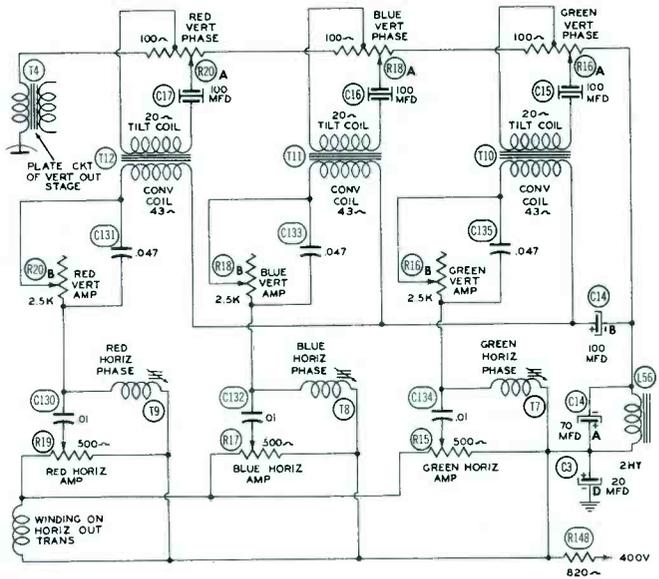


Fig. 9-48. Dynamic-Convergence Circuits Used in the Motorola Model 19CT1.

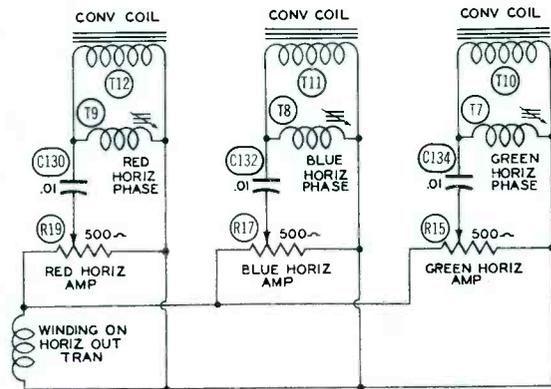


Fig. 9-49. Simplified Schematic of the Dynamic-Convergence Circuit at the Horizontal Frequency. (Motorola Model 19CT1.)

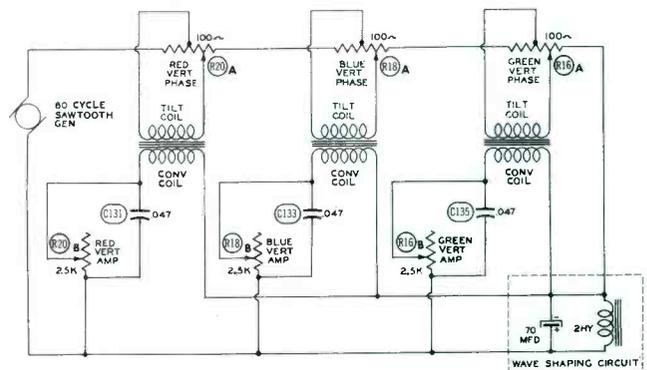


Fig. 9-50. Simplified Schematic of the Dynamic-Convergence Circuit at the Vertical Frequency. (Motorola Model 19CT1.)

combined and produce a resultant field. In order to obtain the best convergence in the vertical plane, the vertical-amplitude and vertical-phase controls can be adjusted as needed to control this resultant field.

Before analyzing the current waveforms in the convergence and tilt coils, let us investigate the circuitry of another color receiver which uses electromagnetic convergence.

TRIO

America's Top Quality Line...

is the Best Buy for the Money!




Behind every TRIO antenna is the RESEARCH—ENGINEERING—EXPERIENCE and CRAFTSMANSHIP that has made TRIO the leader in antenna development.



Sensational "INSTA-LOK" CLAMP

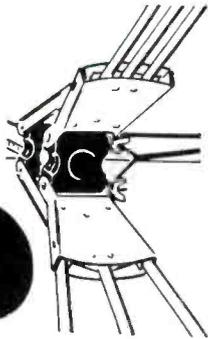
(Good-Bye Nuts)
 Revolutionary TRIO clamp employed on all TRIO antennas with parasitic elements. Permits instant flip-out assembly — permanent alignment and ultra-strength. Nothing stronger! Nothing faster!



New "Vari-Con" Head

Four hi-strength aluminum adjustable arms. Interlocking butterfly sections. Heavier snap-action spring assembly. Spring dampeners lessen vibration and breakage. Mycastyrene insulators. Used on the popular TRIO "88" and "Vari-Con" antennas.

COMPARE THESE FEATURES!

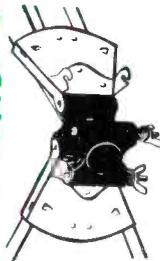

New Mini-Up Conical Head

Superior strength — with the new modern riveted construction. No shedding of elements as with doweled, friction held elements.



Heaviest Booms!

Thick-wall, extra sturdy 1 1/4" diameter booms used on ALL low band Yagis. Highest grade Alcoa aluminum for added strength.



THE TRIO "ARISTOCRAT"

America's Most Dependable Rotator Is Also America's Most Beautiful

Control unit available in four glorious colors.

TRIO — THE COMPLETE LINE
 YAGIS CONICALS "VARI-CONS"
 RADAR SCREEN TYPES COLINEAR ARRAYS
 UHF & REFLECTOR TYPES CONICAL — YAGIS

America's No. 1 Choice

The TRIO "88"

More DB gain per dollar cost. Completely pre-assembled, ready to unfold and install. New Mycastyrene insulators for greater strength and insulating qualities. Highest quality Alcoa aluminum elements and extra sturdy boom. Exclusive, sensational TRIO Jr. & Sr. "Insta-Lok" clamps combined with famous "Vari-Con" head gives the "88" all the plus features everyone wants. Rugged construction, completely pre-assembled, superior performance and low unit cost. The best buy on the market today! Available in single or two bay models.



NEWEST ADDITIONS TO THE TRIO LINE

The TRIO "99"

CHANNELS 3-13


A well-known broad band Yagi type featuring sturdier construction, higher quality materials and faster assembly. Improved forward gain with reduced side and rear pick-up as a result of TRIO engineering and research. Uses famous "Insta-Lok" clamps and all riveted construction as originally introduced by TRIO.



The TRIO "77"

CHANNELS 3-13

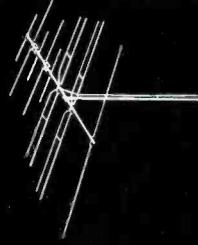High gain, broad band type now greatly improved as a result of TRIO engineering. Highest quality Alcoa elements and boom. Exclusive "Insta-Lok" clamps for easy, fast assembly. Designed for low wind resistance and balanced for rotator operation.



TRIO MANUFACTURING COMPANY • GRIGGSVILLE, ILLINOIS

Leader in Antenna Development

Copyright 1955 by TRIO MANUFACTURING CO.

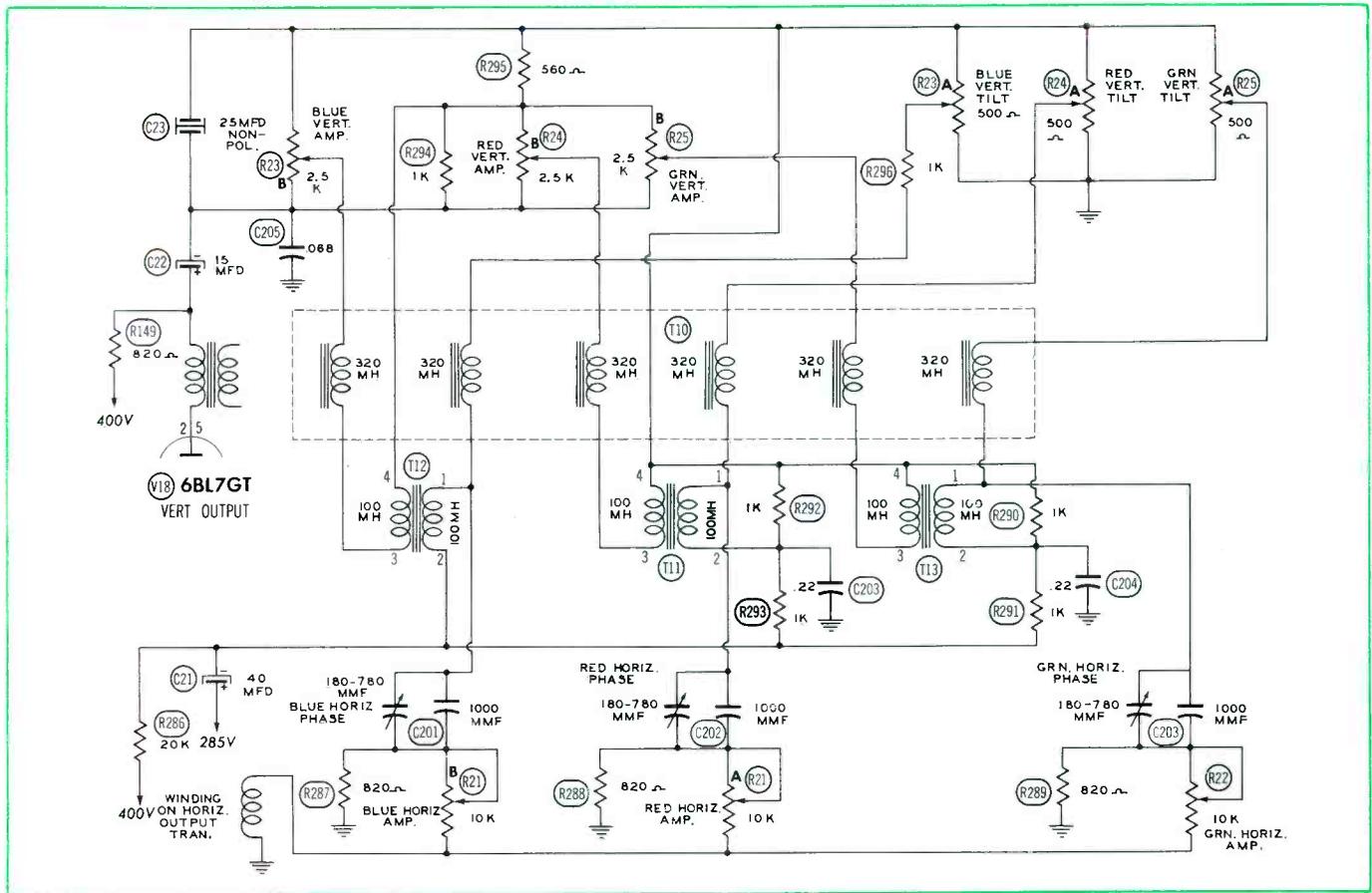


Fig. 9-51. Dynamic-Convergence Circuits Used in the RCA Victor Model 21CT55.

RCA Victor Model 21CT55.

The schematic diagram in Fig. 9-51 shows the dynamic-convergence circuits used in the RCA Victor Model 21CT55 color receiver. As in the circuit just discussed, two coils are used with each of the three electromagnets T11, T12, and T13. According to the schematic one might conclude that each pair of coils is connected to provide transformer action by which coupling is provided from one winding to another; but in the case of convergence electromagnets, energy is applied to both coils in order to produce a resultant field. The two coils are wound around adjoining sections of a ferrite core. As shown in Fig. 9-52, a horseshoe-shaped core is formed by the two sections. Since the core is common to both coils, the fields of the two coils will be combined.

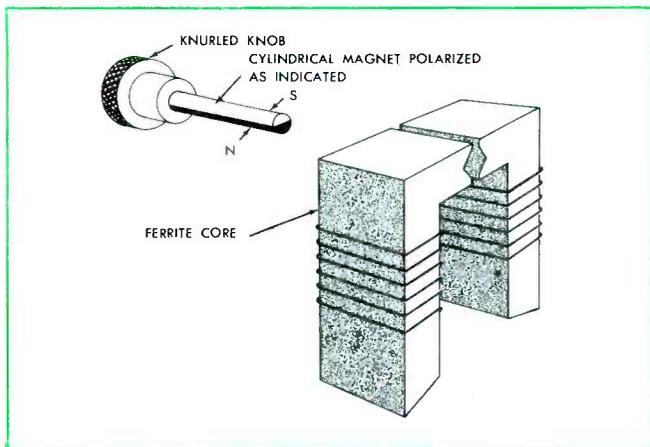


Fig. 9-52. Parts of an Electromagnet Used in the RCA Victor Model 21CT55.

Fig. 9-52 also shows that the beam-positioning magnets used in this receiver are cylindrical in shape and are mounted in the groove between the two sections of the ferrite core. Each magnet is polarized as indicated in the drawing and produces a static field within its associated electromagnet. The magnet may be rotated so that a static field of either polarity and of the desired strength will be produced.

In order to understand clearly the operation of the dynamic-convergence circuits in this receiver, let us use a simplified schematic for each individual circuit.

The simplified schematic in Fig. 9-53 shows the dynamic-convergence circuit which is effective at the horizontal frequency. The operation of this circuit is almost identical to the one used in the Motorola receiver. The main difference between the two is that in this circuit, trimmer capacitors are used to vary the phase of the sinusoidal voltages; whereas, in the other circuit, variable inductances are used for this purpose.


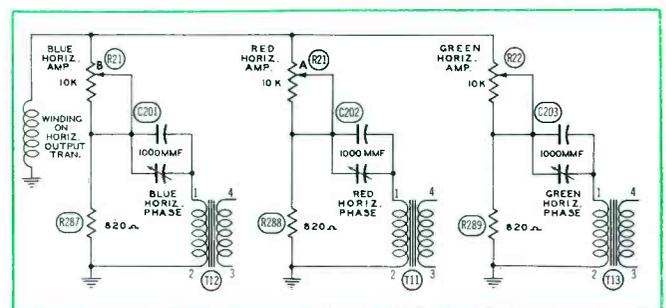


Fig. 9-53. Simplified Schematic of the Dynamic-Convergence Circuit at the Horizontal Frequency. (RCA Victor Model 21CT55.)

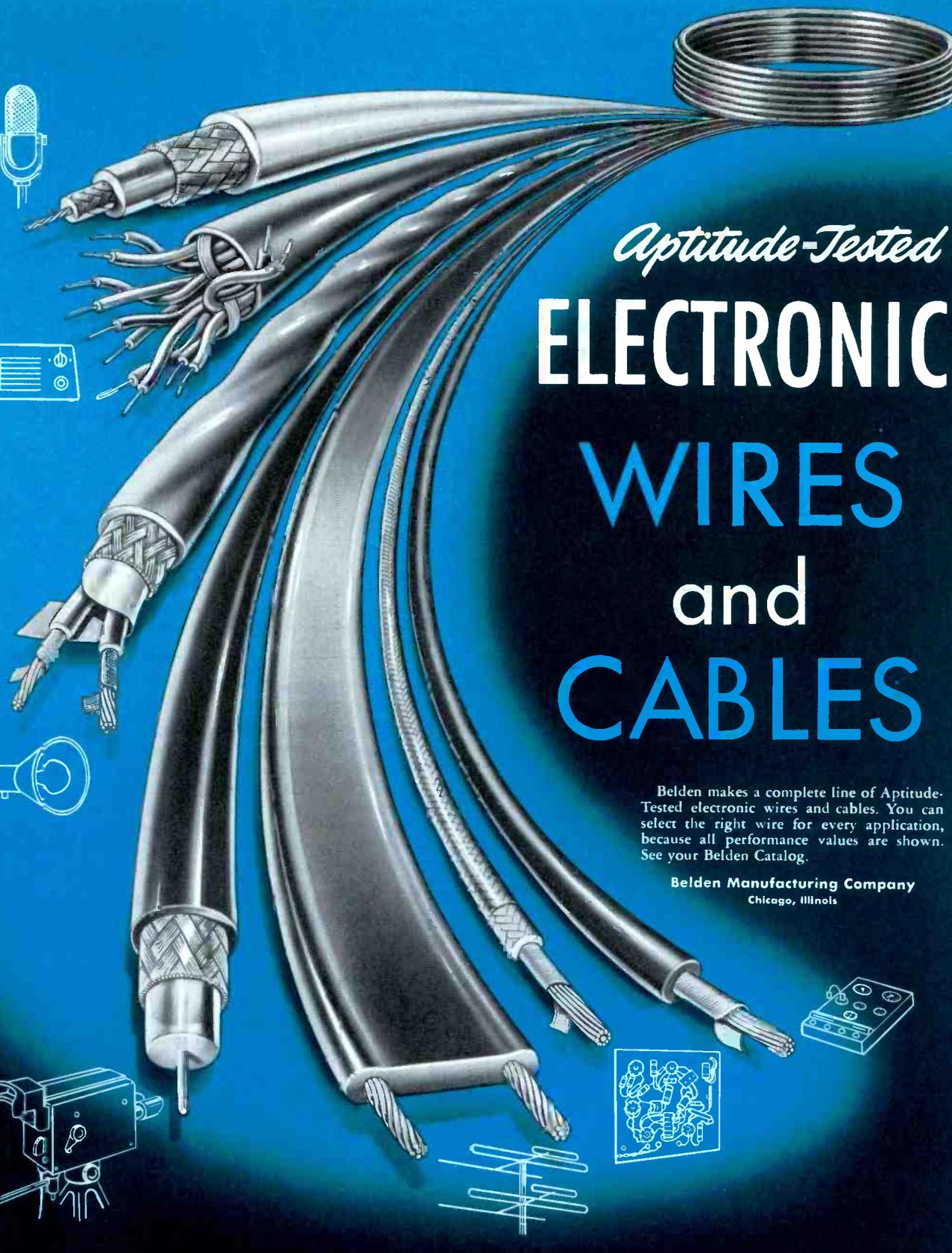

Aptitude-Tested
ELECTRONIC
WIRES
and
CABLES

Belden makes a complete line of Aptitude-Tested electronic wires and cables. You can select the right wire for every application, because all performance values are shown. See your Belden Catalog.

Belden Manufacturing Company
Chicago, Illinois

Belden

**WIREMAKER
FOR INDUSTRY**

Fig. 9-54 is a simplified schematic which shows the source for the dynamic convergence voltage at the vertical frequency. R1 represents the total resistance of the network (in Fig. 9-51) composed of R294, R295, and the three vertical-amplitude controls. R2 in Fig. 9-54 represents the total resistance of the three tilt controls shown in Fig. 9-51. A saw-tooth waveform of current flows from the vertical-output stage through the primary winding of the output transformer; however, the current waveform through R149 is parabolic because of the bypassing action of the parallel RC network composed of C22, R1, C23, and R2. See waveform W1 which represents the voltage waveform across R149.

The 15-mfd capacitor C22 blocks the DC component of waveform W1 and aids in shaping the voltage waveform across the remainder of the network. The voltage across the RC network formed by R1, R2, and C23 is shown by waveform W2. These components comprise a voltage-divider network. Capacitor C23 presents a low impedance to the high frequencies represented by the sharp voltage rise, but it presents considerable impedance to the low frequencies represented by the parabolic curve. The result is that the parabolic voltage shown by waveform W3 appears across R1 (which represents the vertical-amplitude controls in Fig. 9-51). The saw-tooth waveform of voltage shown by W4 appears across R2 (which represents the vertical-tilt controls in Fig. 9-51).

The simplified schematic in Fig. 9-55 represents only that portion of the circuit which supplies the vertical parabolic voltage to the convergence coil associated with the blue gun. R3 represents the total resistance afforded by the red- and green-amplitude controls and the 1K-ohm resistor R294 in Fig. 9-51. Keep in mind that the voltage waveform across C23 is W3 in Fig. 9-54. The amplitudes of the parabolic voltages developed across R295 and R3 in Fig. 9-55 are approximately the same, because the voltage division is approximately one to one.

When the rotor arm of the blue-amplitude control R23B is moved to a point somewhere near the center of the control, no voltage will be applied across the coil. Thus, no current will flow through the coil and no magnetic field will be produced. When the rotor arm of R23B is moved to the upper end of the control, the coil will be connected across R3. When the rotor arm of R23B is moved to the lower end of the control, the coil will be connected across R295. In the first case, point 4 of the coil will be connected to the lower side of R3; and in the second case, this point will be connected to the upper side of R295. The polarity of the voltage applied to the coil can be reversed by moving the arm of the control from one side of center to the other. The amplitude of the applied voltage will increase as the arm of R23B is moved farther from the center of the control.

The simplified schematic in Fig. 9-56 represents only that portion of the circuit which supplies the vertical parabolic voltage to the convergence coil associated with the red gun. R4 represents the combined resistance of the green-amplitude control and the 1K-ohm resistor R294 in Fig. 9-51. When the rotor arm of R24B in Fig. 9-56 is moved to the lower end of the control, the voltage drop across the coil will be at a minimum. Very little current will flow through the coil, and a weak magnetic field will be produced. As the rotor arm is moved toward the upper end of the control, the voltage applied to the coil will increase; consequently, the current flow through the coil and the strength of the electromagnetic field around the coil will increase. The field strength will be at its maximum when the rotor arm reaches the upper end of the control.

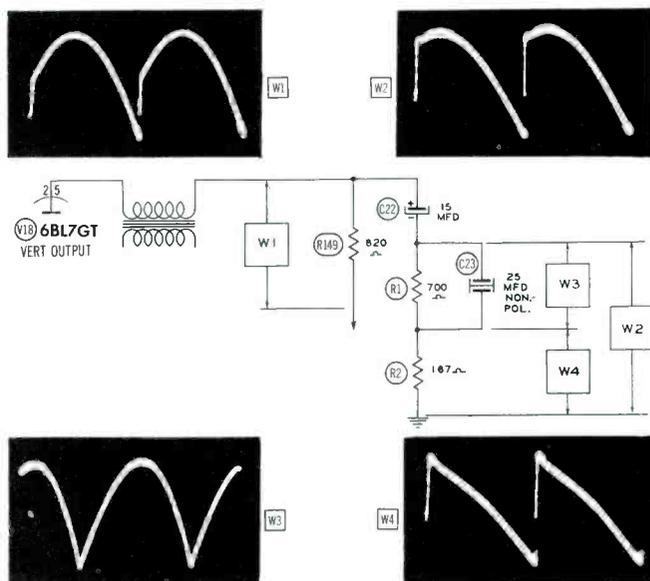


Fig. 9-54. Simplified Schematic of the Dynamic-Convergence Circuit at the Vertical Frequency. (RCA Victor Model 21CT55.)

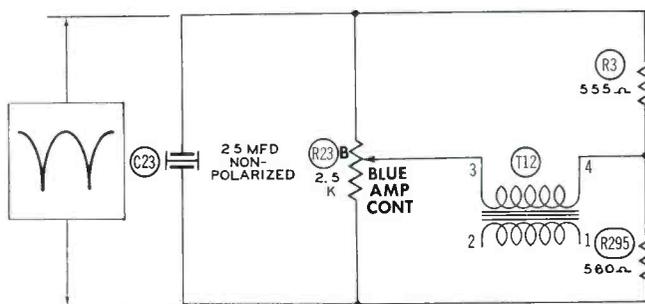


Fig. 9-55. Simplified Schematic of the Circuit Which Supplies the Voltage to the Convergence Coil for the Blue Gun. (RCA Victor Model 21CT55.)


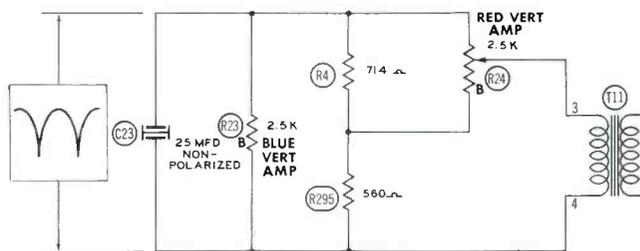


Fig. 9-56. Simplified Schematic of the Circuit Which Supplies the Voltage to the Convergence Coil for the Red Gun. (RCA Victor Model 21CT55.)

The operation of the circuit which supplies the vertical parabolic voltage to the convergence coil associated with the green gun is the same as the operation of the circuit shown in Fig. 9-56. It is interesting to note that the polarity of the parabolic voltages applied to the red- and green-convergence coils cannot be reversed in the same manner that the parabolic voltage applied to the blue-convergence coil can be reversed.

The circuits which supply the saw-tooth voltages to the electromagnets are shown in the simplified schematic diagrams in Fig. 9-57. Schematic A represents the blue-tilt circuit, and schematic B represents the red-tilt circuit. The coil shown in each of these circuits is the tilt coil and should not be confused with the convergence

"SATISFIED CUSTOMERS - NOT CALL BACKS."

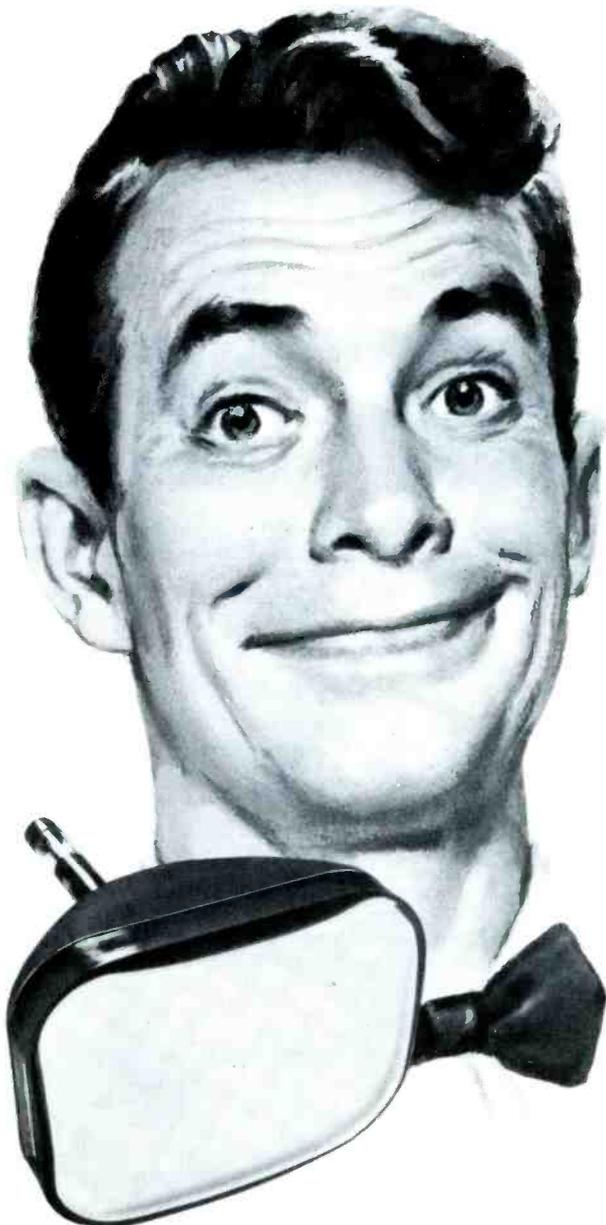

That's right. I rarely get a complaint callback when I've used Tung-Sol Tubes. That makes for a lot of happy customers. I've found Tung-Sol's regular line of tubes more uniform and more dependable than the so-called 'super' grades of tubes.

TUNG-SOL[®] dependable PICTURE TUBES

TUNG-SOL ELECTRIC INC., Newark 4, N. J. Sales Offices: Atlanta, Chicago, Columbus, Culver City (Los Angeles), Dallas, Denver, Detroit, Newark, Seattle.

coils shown in the previous simplified circuits. The input signal is that shown as waveform W4 in Fig. 9-54. Note that direct current flows through each of the coils in Fig. 9-57 from point 1 to point 2. This current flow results from the fact that each coil is connected across the power supply through a voltage-divider network. Direct current through the coils was provided in order to compensate for any slight misconvergence caused by variations in the line voltage. The green-tilt circuit is not shown in simplified form because it is identical to the red-tilt circuit.

The polarity of the saw-tooth voltage applied to the blue-tilt coil cannot be reversed; whereas, a saw-tooth voltage of either polarity may be applied to the other two tilt coils.

Summarizing the discussions that concern the circuits which supply the dynamic voltages at the vertical frequency, we can state that the voltage applied to the blue-tilt coil cannot be reversed in polarity but that the voltage applied to the blue-convergence coil can be reversed in polarity. In addition, we can state that the voltages applied to the red- and green-tilt coils can be reversed in polarity but that the voltages applied to the red- and green-convergence coils cannot be.

Now let us consider the function of a few components which are used in the circuit shown in Fig. 9-51 but which were not included in the simplified drawings. Refer back to Fig. 9-51, and note that T10 is comprised of six 320-millihenry chokes. The reactance of each choke is about 120 ohms at the vertical frequency and about 31.5K ohms at the horizontal frequency. As a result, the chokes can be considered as short circuits to the parabolic and saw-tooth voltages; however, these chokes present a considerable impedance to the sinusoidal voltages at the horizontal frequency and prevent these voltages from appearing across the vertical amplitude and tilt controls. The .068-mfd capacitor C205 in Fig. 9-51 presents a high impedance at the vertical frequency and a very low impedance at the horizontal frequency. That portion of the horizontal-frequency voltage which appears across the convergence coils because of transformer action will be bypassed to ground. This prevents a voltage at the horizontal fre-

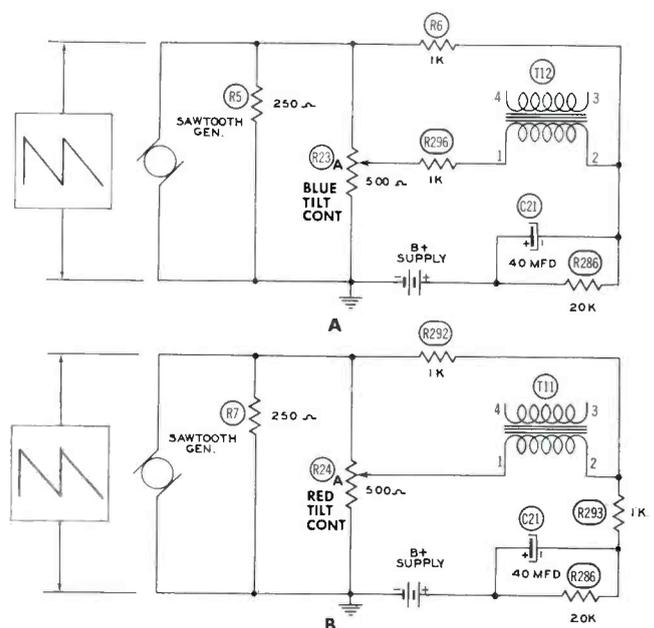


Fig. 9-57. Simplified Schematics of the Circuits Which Supply the Voltages to the Tilt Coils (A) for the Blue Gun; (B) for the Red Gun. (RCA Victor Model 21CT55.)

quency from appearing in the circuits which supply the parabolic and saw-tooth voltages at the vertical frequency. The .22-mfd capacitors C203 and C204 which are connected respectively at terminal 2 of T11 and at terminal 2 of T13 provide bypasses to ground at the horizontal frequency. C21 provides a bypass at this frequency from terminal 2 of T12 to a B+ source.

Currents in the Convergence and Tilt Coils.

At this point in the discussion of convergence circuits, let us consider the nature of the currents through the coils of each of the electromagnets. In both the RCA Victor Model 21CT55 and the Motorola Model 19CT1 receivers, a parabolic voltage at the vertical frequency is applied to one coil of each electromagnet, and a saw-tooth voltage at the same frequency is applied to the other coil. A sinusoidal voltage at the horizontal frequency is also applied across one of these coils. The parabolic voltage produces a parabolic current, the saw-tooth voltage produces a modified saw-tooth current, and the sinusoidal voltage produces a sinusoidal current.

It has been mentioned that the magnetic fields of the two coils used with each electromagnet will be combined because the coils have a common core. The resultant field of any one electromagnet is approximately the same as that which would be produced if the three voltages were combined and then applied across a single coil. If the waveforms of the parabolic and saw-tooth currents are plotted graphically, the algebraic sum of their values can be plotted to show the variation in the field strength during a vertical-scanning period. Then when the field produced by the sinusoidal current at the horizontal frequency is considered, it can be said that the vertical field is modulated by a sine wave at the horizontal frequency.

The waveforms of the parabolic and saw-tooth currents through the coils of the electromagnets and the resultant fields are shown in the drawings of Fig. 9-58. The circuits for all three electromagnets used in the Motorola Model 19CT1 receiver are identical, and only parts A and B of this figure are needed to illustrate the currents and resultant fields associated with this receiver. Parts A and B also illustrate the currents and fields which are associated with the electromagnets used with the red and green guns in the RCA Victor Model 21CT55 receiver. Parts C and D of the same figure pertain only to the currents and resultant fields for the elec-

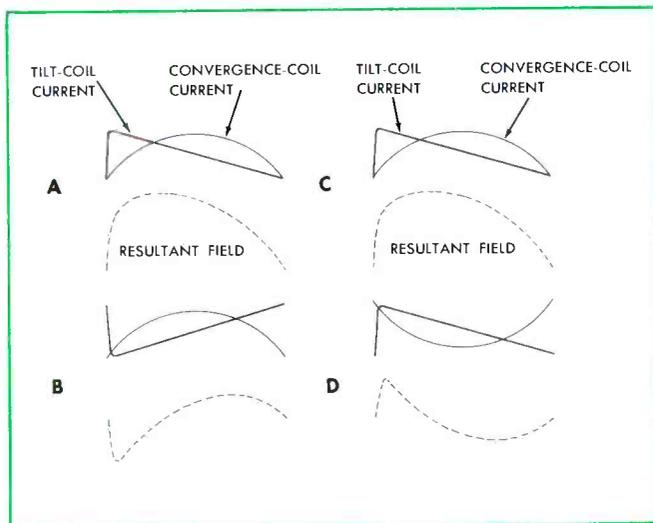


Fig. 9-58. Current Waveforms Through the Two Coils of an Electromagnet and the Resultant Fields Produced.

"SATISFIED? I SURE AM!"



I don't know anything about tubes, but I do know that the serviceman used Tung-Sol Tubes to fix my set and now it works as well as the day I got it.

TUNG-SOL[®]
dependable
TUBES-DIAL LAMPS



TUNG-SOL makes All-Glass Sealed Beam Lamps, Miniature Lamps, Signal Flashers, Picture Tubes, Radio, TV and Special Purpose Electron Tubes and Semiconductor Products.

what you want
when you want it

... use

ERIE

RESISTOR CORP.
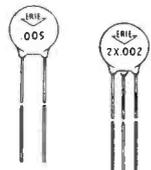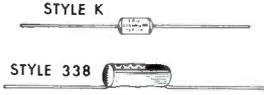
<p>ERIE CERAMICON and TUBULAR TRIMMERS</p>  <p>STYLE TD2A STYLE 532</p>	<p>ERIE FEED-THRU CERAMICONS</p>  <p>STYLE 362 STYLE 327</p>	<p>ERIE SWITCHES</p>  <p>STYLE 3612-01</p>
 <p>STYLE 557 STYLE TS2A</p>	<p>ERIE DISC and PLATE CERAMICONS</p>  <p>STYLE 005 STYLE 2X002</p> <p>STYLE 811 STYLE 812</p>	<p>ERIE STAND-OFF CERAMICONS</p>  <p>STYLE 325</p> <p>STYLE 326 STYLE 324</p> <p>STYLE 323</p> <p>STYLE 2336 STYLE 2322</p>
<p>ERIE UNIVERSAL 20KV CERAMICONS</p>  <p>STYLE 413</p>	<p>ERIE CERAMICONS</p>  <p>STYLE K</p> <p>STYLE 338</p>	
<p>ERIE BUTTON SILVER MICA CAPACITORS</p>  <p>STYLE CB STYLE FA</p>		

the most complete line of ceramic replacement capacitors

Leading builders of radio and TV sets and electronic equipment have approved ERIE components and have used them for many years.

Your requirements can be met without delay from your ERIE Distributors' vast and varied stock.

Most ERIE Distributors have in stock from 25,000 to 75,000 ERIE Ceramicons of various styles, types, and values.

Write for latest catalog and the name of your nearest ERIE Distributor.

ERIE
RESISTOR CORP.

ELECTRONICS DISTRIBUTOR DIVISION
ERIE RESISTOR CORPORATION
Main Offices: ERIE, PA.
Factories: ERIE, PA. • LONDON, ENGLAND • TRENTON, ONTARIO

tromagnet used with the blue gun in the RCA Victor Model 21CT55.

The resultant fields shown in parts A and B of Fig. 9-58 represent the possible extremes obtainable through adjustment of the tilt control, with the amplitude control set for maximum current in both cases. The tilt-coil current represented in part A is obtained with the tilt control set at one end of its rotation, and the tilt-coil current represented in part B is obtained with the tilt control set at the opposite end of its rotation. Note the difference in the shapes of the waveforms of the two resultant fields.

The difference in the waveforms of the resultant fields shown in parts C and D are obtainable by setting the amplitude control for maximum current and by setting the tilt control first at one extreme of its rotation and then at the other.

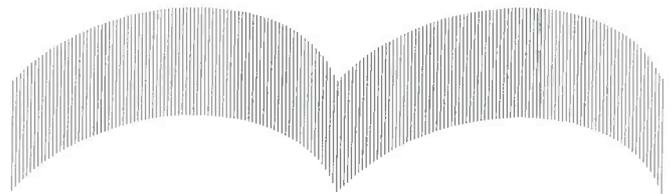


Fig. 9-59. The Strength of the Magnetic Convergence Field Varies at Both the Vertical and Horizontal Frequencies.

An infinite number of variations of waveforms of the resultant fields could be plotted, because the amplitudes of the currents through the convergence coil and tilt coil can be reduced individually or together. If the amplitude of the current of the convergence coil is reduced, the curvature of the waveform which represents the resultant field will decrease. As the amplitude of the current of the tilt coil is reduced, the waveform which represents the resultant field will approach the symmetry of the waveform of the convergence-coil current. These factors provide an infinite number of variations in the phase and amplitude of the vertical-convergence force applied to each of the electron beams.

When the dynamic voltages at both the horizontal and vertical frequencies are applied across the coils of each electromagnet, it may be stated that the dynamic-convergence field developed at the vertical rate will be modulated by the field developed at the horizontal rate. Fig. 9-59 shows a waveform which follows the variations of the strength of such an electromagnetic field over an interval of two vertical-scanning periods. By individually adjusting the controls which determine the amplitude and phase of each voltage applied to the coils of each electromagnet, the rasters of the three electron beams can be made to coincide on the shadow mask of the picture tube.

The next part of the Color TV Training Series will present the setup procedure for a receiver which uses a color picture tube of the electrostatic type.

In order to give the reader an opportunity to test himself on the material in this issue, we are including on the insert a few questions that are answered in this discussion.

C. P. OLIPHANT

and

VERNE M. RAY

Dollar and Sense Servicing

(Continued from page 31)

GUMPTION. Here's an old-fashioned word meaning what you have to have to get somewhere in life. The man who stands still or slips backward doesn't have it; however, without "gumption" he may well be a lot happier and healthier than those who're pushing their career like a wheelbarrow.

As we grow older and notice more closely the "big shots" who baby their ulcers with a milk diet, who land in the hospital with a nervous breakdown, or who just simply drop dead at their desk from an overworked heart, common sense begins to look much more desirable than gumption. Call it slipping or call it laziness if you will, but what good is gumption to you and your family when you're six feet under?



ELECTROFORMED WIRE. The wire that runs from the street telephone line to your house has two requirements - enough steel to hold when branches fall on it and enough copper to give the required conductivity. Western Electric formerly had to use copper-clad steel wire in which the copper was rolled around the steel by an intricate mechanical process. Now it has its own plant for putting the copper on the steel by plating, sometimes called electroforming. Some 25 wires at a time run through block-long plating baths, with electronic controls measuring the conductivity of each wire in turn and changing plating speed accordingly so that each wire gets the essential amount of copper.

In wartime, the same wire can be used for telephone lines strung over treetops by airplane or helicopter, to maintain jam proof and secret communication with advancing troops. Development of the electroforming process gives the needed second source of supply for this essential military requirement of strong conductive wire, so that if one plant is knocked out there'll still be wire for war.

Publication of details on how these new production techniques work means we can set up new plants quickly anywhere, no matter what an enemy does. That's why we get such a feeling of pride in our country and security in our future when going through little-known plants having terrific military value.

TRAPS. Practically all picture-tube manufacturers have gone to aluminized tubes now. Automatic equipment puts a layer of aluminum only a few molecules thick on the screen inside the tube.

The first aluminized coatings were heavy enough to stop ions, making ion traps unnecessary; with electronically controlled thin coatings currently being produced, ion traps are back again in many sets for added insurance against ion trouble.



PROP. When you're the boss of your own business, in effect you're president of the company. Traditionally, though, this title is used only for large businesses, chiefly those that are incorporated. The title of proprietor, abbreviated Prop., or Propr., has been widely used on business cards and in advertising to indicate who's head of a servicing business; but somehow this title sounds antiquated. How about just putting Owner after your name?



TRANSISTOR RADIO. The little Regency radio, first all-transistor design to hit the market in volume, is selling fine at \$49.95 list price at Liberty Music Shop in New York City, with no discounts given. People are amazed at its performance in the shop and even more so when they get it home in quieter surroundings where its tone quality can be appreciated.

Service manager Norman Platner at this shop says there've been very few troubles with these little sets. Practically 100 per cent of them work on arrival, and the occasional troublemaker has invariably had only a rosin joint due to trouble in dip-soldering. If the bad joint can't readily be localized, a quick dab at each joint with a small hot soldering iron will clear up the trouble.

It's hard to realize that bad joints can occur when all are soldered at once by dunking the chassis in liquid flux first, then in molten solder. Apparently some component leads acquire a grease or oxide film that doesn't come off in the flux. Be assured that all manufacturers are working on this dip-soldering problem. In the meantime, condition yourself to suspect joints first when a dip-soldered set acts up. Leave the transistors alone; they're the least likely to be the cause of trouble.

INCOME TAX. For real help in preparing your Federal income tax return, see pages 75 to 107 of "Successful Service Management," a book that is available from GE tube distributors. Among other things, this tells how to make out your deductions from your gross income in order to get credit if part of your residence is used for such business as keeping the books, handling correspondence, and handling business phone calls. Automobile expenses are also deductible to whatever extent the car is used for business, and the book gives detailed instructions for keeping the necessary logs and records to substantiate your claims if challenged.

An example is given for a five-room house in which one room is used for business; therefore, 20 per cent of the residence expense is deductible. The telephone is estimated to be used 50 per cent for business, and the automobile is estimated at 25 per cent for business. In this particular case then, the permissible deductions for adjusted gross income to report on your Federal tax return are:

	Total Cost	Business Deduction
Depreciation on house	\$250.00	\$ 50.00
Repairs to house	500.00	100.00
Interest on mortgage	450.00	90.00
Real estate taxes	400.00	80.00
Light and heat	200.00	40.00
Telephone	96.00	48.00
Auto depreciation cost $\left[\begin{array}{l} \$2,000 \\ 5 \text{ yrs.} \end{array} \right]$	400.00	100.00
Auto repairs, gas, oil	325.00	81.25
State gasoline taxes	8.00	2.00
Driver's license	5.00	<u>1.25</u>
Total		\$592.50

The book cautions that these percentage figures should not be used in your own return just because they are given in this example and gives specific instructions for figuring out your own values and percentages.

NOW AN EVEN BIGGER TURNER

VALUE

Popular miniature crystal mike...
level now only -54 db.

Turner Model 80... you can hide it in the palm of your hand



THE TURNER 80 CRYSTAL MICROPHONE

Response:
80—7,000 c.p.s. Sharp,
clean-cut performance within
its range.

Level:
-54 db. A further improve-
ment in this outstanding mike.

Case:
die-cast zinc alloy with lus-
trous satin chrome plating.
Total weight only 5 ounces.

Crystal:
bimorph moisture sealed. Blast
and mechanical shock proofed.

Cable:
7 ft. attached single conductor
shielded cable.

LIST PRICE \$15.95

Matching C-4 stand (as shown here):
\$5.75. Stand won't tip or slide. Pivots
mike in 135° arc.

THE TURNER COMPANY

Cedar Rapids, Iowa

IN CANADA:
Canadian Marconi Co.,
Toronto, Ont., & Branches

EXPORT:
Ad. Auriema, Inc., 89 Broad St.
New York 4, N. Y.

THE TURNER COMPANY

949 17th St., NE, Cedar Rapids, Iowa

For complete catalog on all TURNER mikes,
simply check TURNER number on Catalog
and Literature post card in rear of magazine.

Big new
catalog
FREE

TAPE RECORDERS. Year-end estimate by Electrical Merchandising magazine says 470,000 magnetic tape recorders were sold in 1954, as compared to 275,000 in 1953. They say three factors kept the sales from going still higher:

1. Production slowdowns due to lack of needed special components such as recording heads.

2. Failure of many recorder manufacturers to achieve mass distribution of their models.

3. Lack of merchandising. Too few dealers try as hard to sell recorders as they do other merchandise, and most of the manufacturers give their dealers little sales help other than through national advertising.

As a venture into a new branch of selling, service organizations might well consider taking on a good line of magnetic recorders and using service technicians to give on-the-spot demonstrations right in homes during service calls. Just plug in the machine loaded with the latest pre-recorded reel of taped background music, and let it run while working on the TV set. Even just one sale a week may put a decided boost in a service technician's take-home pay and in shop income.



FAR-SEEING EYES. Here are two interesting new uses for industrial television systems. On the West Virginia Turnpike, cameras are mounted on the ceiling of a tunnel to replace the guards formerly stationed at intervals in the tunnel to detect traffic jams. And out West, a parking lot operator mounted a camera high atop a post and put the monitor receiver in his shack to show at all times where the empty spaces were, if any, on the lot.



TRENDS OF THE TIMES. Console radios are fast vanishing these days, with universal AC-DC table-model radios taking over. Straight AC receivers with power transformers are also pretty much a thing of the past, along with tuning indicators and push-button tuning. Bets are still being taken on the battle between loop antennas and ferrite sticks for radios. But all bets are off on the TV-radio battle; it's evident to all now that these two will live happily together for many years to come.

UNDERWATER TV. The new United States supercarrier "Forrestal" will have underwater TV cameras designed to swing over the side to inspect the hull for battle damage. The new high-sensitivity camera tubes are even better than frogmen in the murky depths, because the cameras can see more than human eyes and bring the picture right up to the experts who must make the decisions in connection with the damage.

Another innovation on this carrier is a system of fixed cameras on the flight deck and at other key stations, with monitoring screens in below-deck control centers. This can well mean that the Navy will be looking for TV service technicians soon.



DISGUISE. A complete hearing aid concealed inside the frame of horn-rimmed glasses has been announced as ready for the market early this year, and it will sell at about \$265 plus the cost of the lenses. The three transistors used, each about the size of a match head, are made by CBS-Hytron especially for hearing aids. The battery is about the size of a dime, and all other parts are proportionally subminiature in size to fit inside the hollow earpieces. Manufacturer is Otarion Inc., Dobbs Ferry, New York.



FLUORESCENTS. For just about fifty bucks today, you can get a bench light that will serve every corner of a ten-foot bench, will ease eye strain, and will give the entire shop a new and modern look. Just order a plain white-enamel 8-foot fixture holding four 8-foot instant-starting fluorescent lights, and put it up against the ceiling right over the bench. It's worth every cent of the price.

Modern fluorescents radiate very little interference, but we know one service technician who prefers the noisy older fluorescents as an aid to high-speed servicing. He uses his as a handy noise generator for providing an indication of receiver sensitivity and AVC action. At the high end of the broadcast band, the noise can be used for peaking the high-frequency trimmers. At the low end of the band, a finger touching the stator of the antenna tuning section will furnish noise to indicate a dead oscillator.

CHOICE. Is it better to be a well man with a sick business — or a sick man with a well business?

All too often, those of us who are seldom sick forget that good health is a real blessing to be enjoyed and treasured. What good are business success and money when they are achieved by destroying your health?

Work hard when you work, but work just as hard at enjoying life. Spring is coming soon; make plans now for those early-morning fishing trips, for hikes in the woods, for going to ball games now and then, or for following whatever other hobby you have. This planning chiefly involves organizing your business to run itself while you're away for the half-day, day, or even week.

For a small business, part-time help may be the answer — chiefly for tending the shop and answering the phone so that customers won't think you're just ignoring them while you're having fun. Many a young wife, missing the excitement of her before-marriage job, would jump at the chance to work a half day now and then for the minimum legal wage rate per hour. Just run a small help-wanted classified ad in your local paper, and take your pick. In between handling customers, a part-time girl can also take care of correspondence, if you pick one who has been a stenographer. Even larger service organizations can profitably use part-time stenographers now and then.



TRADE-INS. What happens to the old TV sets that are traded in on new models? A recent survey made by Electrical Merchandising magazine gives the answer: 9.7 per cent of the trade-ins are junked, 16.0 per cent are resold as is, 62.7 per cent are rebuilt and resold, and 11.6 per cent are still on hand. These percentages are based on a study of records for about 18,000 sales which involved 4,000 trade-ins; this is an amply large sampling to justify use in future planning.

Assuming that the sets still on hand will eventually be disposed of, chiefly by junking, here are the rounded-off percentages you can apply to the trade-in picture in 1955: plan on junking 15 per cent, selling 20 per cent as is, and rebuilding 65 per cent for resale.

FLORIDA. In one Florida locality, it's a common sight to see people watering their TV antennas with the garden hose, according to Reader's Digest. Off-sea winds coat the antennas with salt, bridging across the insulators with a conductive coating and thus impairing reception — hence the need for washing off the antenna.

To tourists, the procedure is quite startling and generally results in questions that become a bit monotonous after the first few dozen tourists have asked them. At Pompano Beach, one housewife turned the tables on one group of tourists who'd just stopped, by turning toward them first and placing her hand palm down at the height of her knee. "Only used to be that big," she said; then she went on with her antenna watering.



SWAPPING TUBES. When things tighten up businesswise, be on the lookout for an epidemic of radios and even TV sets that have been tinkered with before reaching your shop. One of the favorite stunts of the home handyman is interchanging tubes. A few of these sets may come in during seasonal periods when owners are "broke," such as right after Christmas or right after vacation. It's hard to believe anyone would switch tubes around blindly, but they surely do.

For TV, the old paper bag is coming into use, just as for radio, even by those set owners who should know better. One chap we know had a set that had sound but no picture, so he "yanked" all the tubes, put them in a paper bag, and took them into a shop for testing. All checked good except the damper, for which he considerably bought a new tube from the shop owner. But putting the tubes back into the receiver just made things worse; the sound went out, and the picture was hopelessly out of sync. The service technician who was finally called had to replace two tubes that had somehow been ruined. In addition, he had difficulty with a few other things before the set was finally put in order again.

Anyway, the current do-it-yourself fad has one advantage — when people try to fix their own TV sets and fail, they appreciate the abilities of their service technicians more and pay the bill more cheerfully.

* * Please turn to page 64 * *



HIGH PASS FILTER eliminates TV interference

The model 114-330 High Pass Filter is an inexpensive accessory providing clearer, sharper pictures for any tv set.

It effectively rejects all signals at frequencies below 50 mc, including communication-type, diathermy and heat-transmitting interference, and industrial or ignition interference • Circuits are double-shielded in the 114-330 to prevent pick-ups of signals by the Filter itself. Mounting/grounding strap bleeds off rf interference direct to chassis ground.

Easily attached to chassis of any tv set.

Lists at only \$5.45!

AMERICAN PHENOLIC CORPORATION

chicago 50, illinois

In Canada: AMPHENOL CANADA LIMITED, Toronto



Servicing the Transistor Radio

(Continued from page 11)

Meter Precautions

It is important to point out at this time that some service ohmmeters utilize circuitry which necessitates an other-than-normal battery polarity inside the meter. With meters of this type, the red test lead has a negative potential and the black lead has a positive potential. The technician should investigate his meter to determine its polarity. This can easily be done by connecting a voltmeter across the ohmmeter test prods. When measuring circuits which are critical with regard to polarity (such as those containing electrolytic capacitors), the technician should keep in mind the polarity of the meter leads and should connect them accordingly. The positive lead, whether it is red or black, should be connected to the positive lead of the electrolytic capacitor. The transistors in this receiver would not be ruined if an ohmmeter were to be connected into the circuit in the reversed polarity, but the electrolytic capacitors would give incorrect readings because they would be measured backwards. It is also imperative not to use an ohms range which utilizes a battery of more than three volts (or two cells), because the transistors can be ruined if too much voltage is applied to them.

The resistance between the battery clips (with the battery removed and the receiver turned on) should be between 6K and 15K ohms for a normal receiver, as read by an ohmmeter with an internal battery of not more than three volts. A reading lower than 6K ohms will usually indicate a defective receiver which should be checked before the new battery is installed.

Checking Battery Current

Probably the easiest method of checking a receiver which has a low B+ resistance reading is to measure the battery current. This can be done very easily by holding the battery vertically with the negative terminal resting on the negative clip. The negative lead of a milliammeter is attached to the positive battery clip, and then the positive meter lead is touched to the positive terminal of the battery. Normal battery current should be between 3.5 and 4.8 milliamperes.

Trouble Shooting

The new battery can be inserted into the clips if the reading of the

CHART I

TROUBLE-SHOOTING PROCEDURE FOR THE REGENCY MODEL TR-1 RECEIVER

DEAD RECEIVER

A. Absolutely No Output.

1. Remove the battery and turn on the switch. Measure the resistance between the battery clips. (Make sure the positive meter lead is on the positive clip.) If the resistance is:

- a. Approximately 10K ohms, the B+ circuit is normal.
- b. Less than 2500 ohms, check the leads of capacitors C17 and C21, and make sure that they are not touching the battery clips or the frame of the output transformer. Check for a shorted condition in either C17 or C21. Measure the resistances from the top ends of R3 and R7 to ground. These should be 2200 ohms more than the reading across the battery clips.
- c. Infinity, check for an open switch.

2. Turn the volume control to maximum, and insert the battery. If a click or noise is heard from the speaker, check X4 by shorting its base to the frame of the output transformer. The audio stage is operating if a click is heard. If no click or noise is heard, proceed as follows:

- a. Check for an open or shorted jack. Indicative readings can be obtained by measuring the resistance from the fixed contact of the jack to ground. These readings are:

0 ohms	— Shorted jack.
2 ohms	— Normal.
15 ohms	— Jack is open, or the ground between the wiring board and chassis is open.

- b. Check for an open condition in the speaker or in the output transformer.
- c. Voltage at the base of X4 (about +2 volts normal).
- d. Voltage at the emitter of X4 (should measure approximately .15 volt less than the base voltage).

3. Check capacitor C19 by paralleling it with a capacitor known to be good.

4. Measure the voltage at the output of the diode D1 (should be approximately +.1 volt).

- a. If voltage is zero, check the resistance to ground with the positive meter lead on the output. This resistance should measure between 20 and 100 ohms. If the resistance is zero, check for a shorted condition in the diode circuit. If the resistance is 200 ohms or greater, check for an open in the diode circuit or for an open diode.
- b. If voltage is negative when the receiver is tuned to a station, move the tuning dial so that no station is received. The negative voltage should decrease.
- c. If voltage is negative by one volt or more and does not drop when the receiver is tuned off the station, the receiver is oscillating. Proceed to the section entitled "Oscillating Receiver."

5. Make voltage and resistance measurements in the IF stages.

B. Noise But No Signal.

1. Check the local oscillator in the receiver as follows: Tune another receiver to any station above 850 kc. On the receiver being serviced, rock the dial above and below a setting that is approximately 262 kc below the frequency of the station being received by the other receiver. If the local oscillator in the receiver being serviced is operating, a whistle will be heard from the other receiver

as the radiation from the oscillator beats with the station frequency.

- a. If the oscillator is dead, proceed as follows:

(1) Check the voltage at the base of X1. This should be between 3 and 10 volts.

(2) Check the voltage at the emitter of X1. This voltage should be within .1 volt of the base voltage.

(3) Check the voltage at the top end of R3. This should be measured from the B+ line, and it should be between .6 volt and 2 volts.

(4) If any of the voltages measured in the three preceding steps are incorrect, check for an open oscillator-coil primary or an open first IF transformer.

- (5) Check resistances of:

(a) The high side of the antenna coupling coil to ground (should be less than 1 ohm).

(b) The secondary of the oscillator coil (should be approximately 10 ohms).

(c) Stator of oscillator section of the tuning capacitor to ground (should be infinity).

WEAK OR DISTORTED OUTPUT

1. Turn volume control to maximum. Check capacitors C19 and C21 by paralleling a good capacitor across each.

2. Perform step 5 under section entitled "Dead Receiver."

3. Measure voltages at:

a. Base of X4 (should be approximately +2 volts).

b. Emitter of X4 (should be approximately .15 volt less than the base voltage).

c. Emitter of X3 (should be approximately .15 volt less than the voltage at the emitter of X4).

d. Top end of R11 (should be approximately -.5 volt when receiving a signal of average strength).

e. AVC line (should be from approximately 0 volts with signal to .5 volt with no signal).

f. Emitter of X2 (should be approximately .15 volt less than the AVC line).

4. Check the alignment of the receiver.

OSCILLATING RECEIVER

1. Measure the battery voltage. If it is below 15 volts, the battery should be replaced.

2. Check the local oscillator as in step 1 under the section entitled "Noise But No Signal."

3. Check capacitors C17, C9, and C21 by paralleling a good capacitor across each.

4. Check ground connection between wiring board and chassis. This connection is the twisted lug near the negative battery clip and is the only lug which has been soldered to the board. Measure between an IF transformer can and the metal chassis. These readings are:

0 ohms — Normal.

15 ohms — Ground lead is open.

63 RAM FLYBACKS replace the 551 Original Types made since TV began!

—save Servicemen lots of time, money, labor, call-backs!



"Even if I want
EXACT MECHANICAL & ELECTRICAL REPLACEMENTS?"
asks C. J. Lee of Los Angeles, California.

YES . . . Because 41 of the RAM units are **COMPOSITE FLYBACKS**. A RAM **COMPOSITE** replaces a related group of initial equipment flybacks, which may cover several manufacturers, because it combines the exact mechanical and electrical characteristics of that group.

Why does ONLY RAM make COMPOSITES?

RAM's many years of pioneering manufacture and know-how in design of initial TV Sweep Components give it the most extensive experience in the industry—put RAM way ahead of contemporaries. RAM's engineers have long concentrated on the Serviceman's needs for simplified replacement—finally came up with the exclusive concept of the **COMPOSITE FLYBACK!**

Are all flybacks in the RAM line COMPOSITES?

No . . . Some originals are extremely unusual in characteristics. For these, RAM makes **ORIGINAL SERVICE REPLACEMENTS** which specifically meet all initial equipment specifications.

For **FREE** listings of latest RAM COMPOSITES, write for Release PF-3.

RAM Sweep Components now listed in Sams' **PHOTOFACT FOLDERS**—assure you of the **BEST** replacement, always. Double proof of RAM quality and precision!

See your **RAM JOBBER** — he's your HQ for all TV Sweep needs.



RAM ELECTRONICS SALES CO.
IRVINGTON, NEW YORK

battery current is within the normal range. If the dead battery were the only trouble, the receiver should operate satisfactorily; however, there will presumably be many cases in which a new battery will not return the receiver to operating condition. For these receivers, a troubleshooting procedure is outlined in Chart I. This chart covers the basic methods of isolating and identifying the causes of the most common troubles.

Oscillations

There is one receiver condition which is not fully covered in Chart I. This is the condition wherein the receiver is oscillating and normal reception is impossible. As in most battery-operated receivers, the battery in the Model TR-1 is bypassed with an electrolytic capacitor C17 in order to present a low-impedance circuit for signal currents. Consult the schematic in Fig. 1 for the location of these components in the circuit. If this capacitor were to develop an open circuit, there would be a considerable amount of feedback along the B+ line to all stages; and the receiver would have general oscillations over the entire tuning range. A similar condition of general oscillations will exist when and if capacitor C9 develops an open circuit. Since C9 bypasses the audio voltages on the AVC line, its failure will allow the gain of the IF stages to vary at an audio rate; and oscillations will result.

An electrolytic capacitor of almost any value can be used to check an electrolytic capacitor that is suspected as being open. This can be accomplished by momentarily bridging the external capacitor across the suspected one while the receiver is turned on. The capacitor polarity should be observed when making this check.

Failure of capacitor C19 in the audio stage will cause a complete loss of audio output. An open condition in capacitor C21 will cause extreme degeneration in the audio stage. This will in turn cause the output of the receiver to be weak and distorted, and some IF oscillation will be encountered.

The information in Chart I lists most of the possible troubles in this receiver. Actually, the replacement of the battery and the electrolytic capacitors is expected to constitute the great majority of service operations in the field.

Circuit Checks

At first glance, it may seem that no points are available for volt-

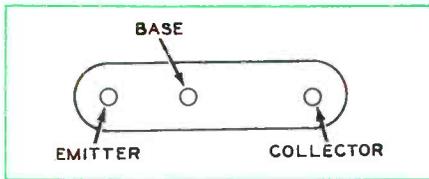


Fig. 2. Basing Diagram for the Transistors Used in the Regency Model TR-1 Receiver.

age or resistance checks of the circuit. Actually, the top end of each resistor in the receiver provides an important circuit point at which to make measurements. All but three of the transistor elements can be measured very easily from the rear, and those three (the collectors of X2, X3, and X4) could be checked by using some ingenuity. The transistors in this receiver use the basing illustrated in Fig. 2; and X2, X3, and X4 are mounted so that their collector leads are toward the outer edges of the circuit board. A small wire probe could be attached to the conventional meter probe and could be bent to reach under the transistor in order to touch the collector lead.

The voltage readings of an average receiver are shown on the schematic diagram. All of the readings were obtained from the rear of the receiver, and the receiver was not disassembled in any way. The photograph in Fig. 3 identifies each of the points at which these measurements were taken. The polarities of the leads of the electrolytic capacitors are also shown in Fig. 3.

Checking Transistors

The transistors are soldered onto the circuit board and must be checked in the circuit. Transistors are low-impedance devices; and unlike vacuum tubes, the input and output resistances can be measured directly with an ohmmeter. When checking the transistors, care must

be taken to ensure the correct polarity of the ohmmeter leads. The positive lead, whether it is red or black, must be connected to the base terminal for these transistors which are of the NPN type. The negative lead is then used to measure resistance at the emitter and collector terminals.

The transistor is a nonlinear device; therefore, different types of ohmmeters will give different values of resistance between the terminals of the transistor. The reading given by any one ohmmeter will depend upon the circuit in that meter, the range that is selected, and the voltage of the internal battery. Ohmmeters using an internal battery of 1.5 or 3 volts and having a 10-ohm midscale range will give the following resistance values:

Base to emitter — 2 to 10 ohms,

Base to collector — 5 to 200 ohms.

The junction transistor is a very stable device having exceptionally long life. Mishandling, mechanical damage, or application of improper voltages are the usual causes of transistor failure. Improper voltage and resistance measurements which are encountered at the transistor leads are in all probability the result of a fault in a component other than the transistor. Before any component (especially the transistor) is changed, the entire associated circuit should be checked thoroughly to determine which component is faulty.

Component Replacement

The replacement of small components such as resistors and capacitors can be accomplished without disassembling the receiver. The leads of a faulty capacitor can be cut close to the body of the component, thus leaving leads long enough to solder to the new component. Faulty resistors can be crushed with a pair

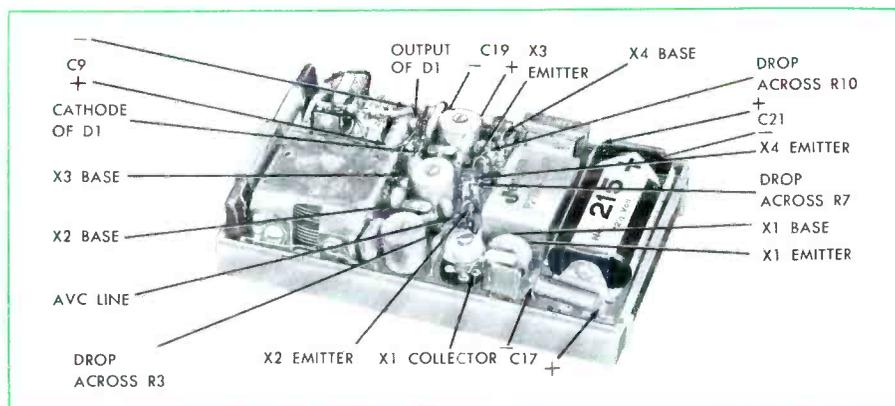


Fig. 3. Photograph Showing the Measuring Points in the Circuits of the Regency Model TR-1 Receiver.

no matter
how you look
at it...

INTERNATIONAL'S
Replacement
Rectifier...

is the
Replacement Rectifier
that's Right!

all types available from
your parts distributor

INTERNATIONAL
RECTIFIER
CORPORATION

El Segundo, Calif. ORegon 8-6281

NEW YORK CHICAGO

World's Largest Supplier of
Quality Industrial Rectifiers



IT'S IDEAL FOR . . .

Color

JACKSON CRO-2 FIVE-INCH OSCILLOSCOPE

And, this Jackson scope has been good for color even before color standards were approved. For Jackson "Service-Engineering" wisely provided four years ago this wide-band, high sensitivity oscilloscope to answer the need for a good television instrument that would not become obsolete. Now provided with new probes (easily attached to older models) the Jackson CRO-2 is the ideal service oscilloscope, used by servicemen and manufacturers. If you're thinking of buying a 'scope, check these features.

Wide Band Amplifier—Flat within 1 db from 20 cycles thru 4.5 MC. This feature is absolutely essential for evaluating color burst signal and Chrominance signal.

Vertical Deflection Sensitivity—Two ranges with three positions for each range. Has fully compensated attenuators. Excellent transient response. Each unit completely tested for "tilt" and "overshoot."

Sensitivity Ranges—With a band width of 20 cycles thru 100 KC, the sensitivity ranges are .018, .18, 1.8 RMS volts per inch. The wide band position 20 cycles thru 4.5 MC has sensitivity ranges of .25, 2.5, 25 RMS volts per inch.

Internal Horizontal Sync.—Positive or negative signal is available to provide excellent stability due to using the best available component of the waveform, such as the leading edge of the horizontal sync. pulse of the standard TV signal. Reversing pattern vertically will not interfere with sync.

Horizontal Sweep Expansion—Four times screen width—up to 20 inches of equivalent width. This feature is excellent for enlarging any small portion of the total waveform. For example, the color TV sync. pulse can be spread to easily observe the 3.58 MC color burst signal so that the individual cycles can be clearly viewed.

Horizontal Deflection Sensitivity—Push-

pull horizontal amplifiers have a sensitivity for all applications of 0.40 RMS volts per inch.

Vertical Input Impedance—1.5 megohms, shunted by 20 mmf. Direct to plates balanced 6 megohms, shunted by 11 mmf.

Horizontal Input Impedance—1.1 meg. **Linear Sweep Oscillator**—Sawtooth wave 20 cycles thru 50 KC per second in 5 steps. Sine wave sweep of 60 cycles also available. Provision for external sync.

Input Calibration—A standard voltage is provided to determine unknown voltages. Permits peak-to-peak measurements.

Vertical Polarity Reversal—By merely flipping a switch you can reverse the polarity of voltage to the vertical plates.

Return Trace Blanking—A new amplifier-timer combination for blanking return traces, providing a clearer, sharper image at all times. Prevents confusion in analysis.

Synchronizing Input Control—Four input control positions, Internal Positive—Internal Negative—External—60 cycle.

Deflection Plate Connections—Direct connections thru capacitors for AC only to deflection plates of CR tube by means of terminal block at back of instrument.

Intensity Modulation—Either 60 cycle internal intensity modulation or external intensity modulation through binding posts.

Accessories—Demodulation Probe, Model CR-P available for using scope as signal tracing instrument. Low Capacity Cathode Follower Probe, Model 10LCP with 2 to 1 attenuation ratio and not more than 8 mmf effective input capacitance. High Voltage Low Capacity Probe Model 3LCP with 10 to 1 attenuation ratio for use up to 1,000 volts.

Model CRO-2 Oscilloscope . . . \$225.00, net
 Model CR-P Probe . . . \$ 9.95, net
 Model 10LCP Probe . . . \$ 19.95, net
 Model 3LCP Probe . . . \$ 7.95, net

of pliers and the resistive material can be removed, again leaving leads long enough to solder to the new components. Access to the wiring side of the circuit board is not necessary for these replacements. A small 20- to 25-watt soldering iron is recommended for any repairs that have to be done. Repairs on the wiring board itself should not be attempted unless the technician has some general knowledge of printed-wiring repairs.

Disassembly of Receiver

The larger components, including the transistors, will have to be unsoldered before they can be removed from the board. To do this, the circuit board must be disassembled from the chassis. Disassembly should proceed as follows:

1. Rotate the tuning dial to the extreme counterclockwise position.

2. Loosen the knurled screw in the center of the dial, and remove the screw and dial.

3. Loosen and remove the one flat-head screw.

4. Remove the chassis from the receiver case.

5. Straighten the twisted lugs at three corners of the circuit board.

6. Unsolder the connections to the stator of the tuning capacitor and to the twisted lug projecting from the chassis.

7. Move the circuit board to a right-angle position with the chassis.

Alignment

The alignment of this receiver is very simple. Signal injection is accomplished by connecting the signal generator to a loop formed of several turns of wire and situated close to the antenna coil of the receiver. Set the generator to 262 kilocycles with 400-cycle modulation, and reduce the output to as low a value as is usable. Connect an output meter (with a .1-volt scale) across the voice-coil connections. (The high side of the voice coil is easily accessible at the spring of the phone jack.) Set the volume control in the receiver to maximum. Adjust each of the cores of the IF transformers for maximum indication on the output meter. Set the receiver dial to its maximum counterclockwise position, tune the generator to 535 kilocycles, and adjust the core of the oscillator coil for maximum output. Tune the generator to 1630 kilocycles, set the receiver dial to its maximum clock-

"Service Engineered"
 Test Equipment



16-18 S. Patterson Boulevard, Dayton 2, Ohio • In Canada: The Canadian Marconi Company

wise position and adjust the oscillator trimmer capacitor for maximum output. Repeat these last two adjustments alternately until no further improvement can be made. Then tune the generator to 1500 kilocycles, tune in this signal with the receiver dial, and adjust the antenna trimmer capacitor for maximum output. Turn the receiver dial to the high-frequency end, and determine whether or not the range extends to 1630 kilocycles. If not, the oscillator trimmer capacitor must be readjusted, and the alignment at 1500 kc must be repeated.

Transistor Replacement

The transistors in the two IF stages of this receiver have been carefully selected and matched so that the IF gain is held at an average value for all receivers. To accomplish this, there are three types of transistors that are used in these stages. These types are identifiable by the body (or top) color.

In addition, the transistors in the IF amplifier stages have been divided into several classifications according to their internal capacitances. The neutralizing capacitors C10 and C14 are selected during manufacture to neutralize effectively the specific internal capacitances of the transistors used.

To eliminate the confusion which could arise from this situation, the manufacturer has color-coded each transistor for internal capacity. When available, each replacement transistor will be supplied with its proper neutralizing capacitor. The neutralizing capacitor (either C10 or C14) must be replaced when X2 or X3 are changed, unless the new one is of the same value as the old.

Since the Regency TR-1 transistor receiver has been on the market only a short time, the special components are not yet available through parts distributors. Distribution of these components is planned by the manufacturer for a future date. Until such distribution has been made, the service technician should contact the manufacturer for information regarding the contemplated plan for factory service at a fixed price before attempting any component replacement; or the faulty receiver should be returned to the manufacturer for service.

EDITOR'S NOTE: For a discussion on the repair of printed wiring boards, refer to pages 70 to 72 in the January 1955 issue of the PF REPORTER.

WILLIAM E. BURKE

March, 1955 - PF REPORTER

TWO NEW COLOR BAR GENERATORS



For All Color
Circuit Checks in
Color TV Receivers

"Ideal for
COLOR"

Specifications—Model 700

Signal Outputs

1. Composite video of either polarity, adjustable amplitude to 1-volt across 90 ohms. Either luminance or chrominance can be eliminated from the composite signal.
2. Modulated R.F., channels 3, 4, or 5 of .1 volt across 300 ohms.
3. Horizontal sync., positive polarity, 1 volt across 200 ohms.
4. Crystal controlled color subcarrier (3.5795 MC), 40 Millivolts across 200 ohms at burst phase.

Synchronizing Signals

1. Color burst, crystal controlled (NTSC standards).
2. Standard horizontal sync. and blanking signals.

Color Bar Signals

1. Simultaneous bar display with luminance and chrominance levels held to plus or minus 10 percent, phase angles to plus or minus 5 degrees as follows:

Color	Relative Luminance	Chrominance
White	1.0	0
Yellow	0.89	0.44
Cyan	0.70	0.63
Green	0.59	0.59
Magenta	0.41	0.59
Red	0.30	0.63
Blue	0.11	0.44
Black	0	0

2. Color Difference Displays. Bars of zero luminance selectivity available as follows: (Phase angles within plus or minus 2 degrees):

Signal	Type of Display	Relative Chrominance
I	single bar	0.25
Q	single bar	0.25
I & Q	simultaneously	0.25
R-Y	single bar	0.25
B-Y	single bar	0.25
R-Y & B-Y	simultaneously	0.25

(Background for all color difference bars in black—relative chrominance zero)

3. Single Bars — Primary colors — red, green and blue—selectively available. Each bar is approximately 60% of screen width. Luminance 0.3, chrominance 0.5.

Crystal Controlled Sound Carrier—approximately 25% of peak picture carrier, placed 4.5 megacycles from picture carrier. Sound carrier may be turned off or on by panel control switch.

Panel Controls

1. R.F. Carrier Tuning—channels 3, 4 or 5.
2. Video Output Amplitude.
3. Horizontal Lock.
4. Sound On—Sound Off Switch.
5. Video Output Polarity Switch.
6. Power Switch.
7. Color Bar Selector Switch.
8. Horizontal Centering Control.
9. R.F. Attenuator.
10. Luminance-Chrominance Selector.

Internal Adjustments

1. Burst amplitude.
2. Color Sub-Carrier.
3. Modulation percentage.

Circuit Operation

1. Color sub-carrier and sound frequencies are determined by crystal oscillators.
2. All six color bars—yellow, cyan, green, magenta, red, blue, plus black and white are independently generated. No color mixing or matrixing is required.
3. Color phase angles are determined by an accurate, low impedance delay line.
4. Direct gating of proper chrominance phase is employed for each color bar to attain maximum stability and reliability rather than the usual methods which utilize quadrature encoders.
5. Luminance and Chrominance levels are reliable and stable. No multi-vibrators are employed in generating any bars.
6. No internal or external adjustments are required for proper phase angles, bar widths, luminance, or chrominance levels.

Specifications—Model 712

Provides similar signal outputs and Color Selection to model 700. Also includes crosshatch and white dot generators for convergence checks on 3-gun tubes. Cross-hatch pattern may also be used for linearity and tilt adjustments. Small dot size—about 1/4" on a 19" tube permits more positive convergence adjustment.

Accessories

Model 75C—Attractive Leatherette Covered Carrying Case with Velvet interior lining. For either Model 700 or 712.

Model 700—Shipping weight

30 pounds\$295.00 net

Model 712—Shipping weight

32 pounds\$395.00 net

Model 75C—Carrying Case—Shipping weight

12 pounds\$24.95 net

"Service Engineered"
Test Equipment



take
Deflecting
Yokes
for example



RCA Deflecting Yokes for RCA Victor TV receivers are specifically designed to save you time and money by fitting right—installing fast. Yokes are just one example of how every RCA Service Part is FACTORY-TAILORED to keep your servicing “on the go” profitably. Remember: RCA Service Parts are the only genuine replacement parts for RCA Victor TV receivers, radios, and phonographs.



**RADIO CORPORATION
of AMERICA**

SERVICE PARTS

HARRISON, N. J.

In the Interest of Quicker Servicing

(Continued from page 15)

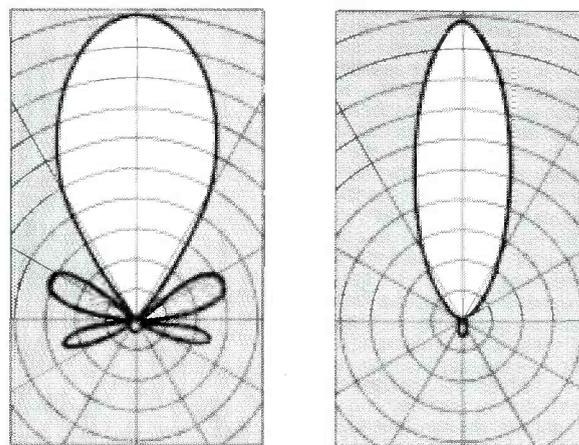


Fig. 4. Antenna Directivity Patterns.

(A) Single Lobe.

(B) Multiple Lobes.

as possible from the interference sources will do much toward minimizing ignition interference and other similar types of interference. The installation of a line filter of good quality between the TV receiver and the AC outlet will tend to eliminate such interference. The installation of a line filter will also prove to be of great value in large apartments, since

receivers will in some cases radiate spurious signals back through the AC power line. If this condition is suspected in an apartment, a line filter should be installed. These units are relatively inexpensive and are advisable to have in stock.

In an area behind an obstruction such as a large building or mountain, the signal may be very poor; in fact, there may not be sufficient signal to obtain a measurement with a field-strength meter. The only method to combat difficulties with dead spots in areas behind such obstructions is to locate the antenna so that satisfactory clearance of the obstruction is obtained. Feed the signal to the receiver with a suitable feed wire and install a booster amplifier if required. Good examples of this method are the community antenna systems which are located throughout the country.

The reception in large apartment buildings, especially those of concrete and steel construction, is often somewhat of a problem. Some of the recently built units have antenna distribution systems which were installed as the buildings were being built. When the distribution system is properly operating and the customers have their receivers connected to it, there is usually excellent reception on those channels for which the system is set up to operate.

In the older apartments or in ones which have no TV antenna distribution system, there are some problems which are difficult to overcome. The easiest method of securing satisfactory reception is to install a suitable outside antenna. This may not be possible in all cases because of the height of the building or the refusal of the property owner to grant permission to install an outside antenna. To overcome this problem, many technicians have installed folded



Fig. 5. RMS Model CL-2 Indoor Antenna.

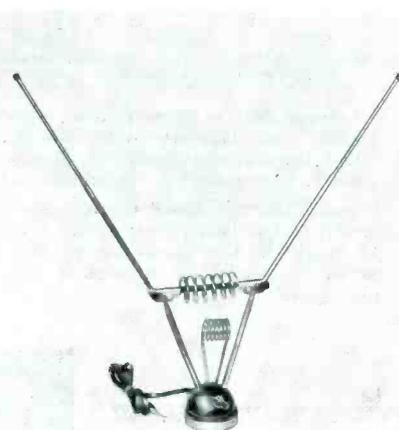


Fig. 6. K-G Model 6A Delta-Beam Antenna.



Fig. 7. Spico Model 501 Indoor Antenna.

dipoles made of 300-ohm ribbon lead-in wire under the rug or behind curtains, have constructed matching stubs of 300-ohm twin lead by using a cut-and-try method, or have gone to other elaborate and time-consuming means to secure a usable picture in these apartment buildings.

During the last few months, there have been placed on the market several indoor antennas which feature tuning stubs or other methods of tuning the antenna to provide proper impedance match between the antenna and receiver. Three of these antennas are illustrated in Figs. 5, 6, and 7. The RMS Model CL-2 shown in Fig. 5 is the deluxe model, and a similar unit without the clock assembly is available as RMS Model K-38. The internal switching arrangement of the RMS Model CL-2 antenna is shown in Fig. 8.

On the switch there are six different positions to enable the operator to select a variety of circuit connections from the two ears and the center stub to the output lead-in wire. It has been found that very good reception may be achieved by selecting the length of the ears, the angle at which they are spread, the correct switch position, and the proper orientation of the antenna.

The internal connections in the Delta-Beam indoor antenna produced by the K-G Electronics Corporation are very similar to those shown in

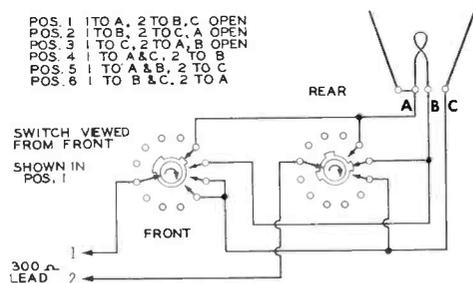


Fig. 8. Switch Connections in the RMS Model CL-2 Indoor Antenna.

OHMITE® REPLACEMENTS


WON'T boomerang
into call backs




NEW OHMITE FUSE RESISTOR

FOR REPLACEMENT IN ALL TELEVISION RECEIVERS

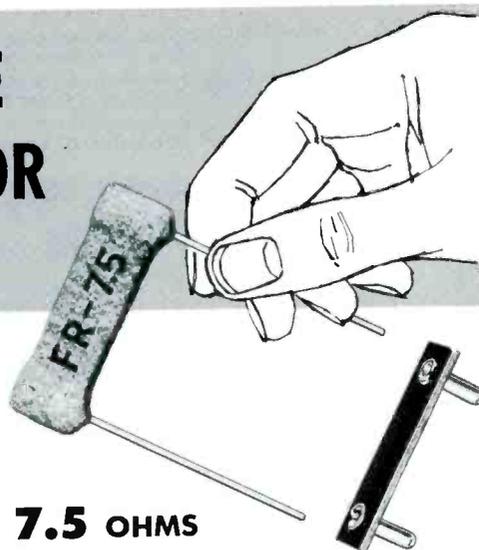The FR-7.5 Fuse Resistor is provided with 1½" tinned wire leads for easy installation directly in the circuit. Can also be soldered to the plug-in terminal strip which is provided.



7.5 OHMS

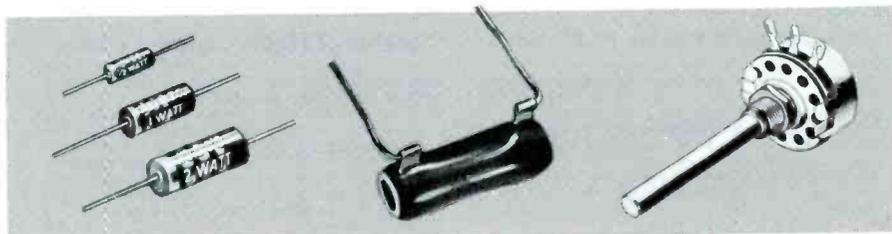

Little Devil® COMPOSITION RESISTORS

Tiny, yes . . . but what dependability, ruggedness, and stability! Rated at 70C rather than 40C. Completely sealed and insulated by molded plastic, they meet all MIL-R-11A requirements. Little Devils are available in ½, 1, and 2-watt sizes in all Standard RETMA values.

BROWN DEVIL® AND DIVIDOHM® RESISTORS

Brown Devil fixed resistors and Dividohm adjustable resistors are favorite vitreous-enamelled units! Resistance wire is welded to terminals. Brown Devils are available in 5, 10, and 20-watt sizes; Dividohm and fixed resistors, in 10 to 200 watts.

TYPE AB NOISE-FREE POTENTIOMETERS

Because the resistance material in these units is solid-molded—not sprayed or painted on—continued use has practically no effect on the resistance. Often, the noise-level decreases with use. They give exceptionally long service. Rated at 2-watts.

Be Right with
OHMITE®
 DEPENDABLE RESISTANCE UNITS

GET THEM FROM YOUR ELECTRONIC PARTS DISTRIBUTOR


Write for Stock Catalog No. 24



OHMITE MANUFACTURING CO.
 3644 Howard St., Skokie, Ill.
 (Suburb of Chicago)

STAY AHEAD IN TV!

these SAMS books show you how

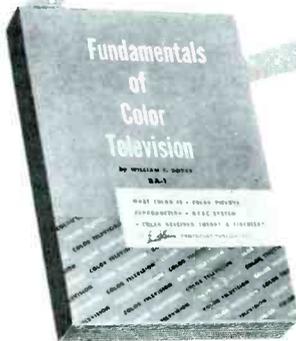

"Fundamentals of Color Television"

Written by William F. Boyce. A complete explanation of Color TV written so you can understand it. Tells you all you want to know in 5 great chapters: 1. What You Need to Know About Color TV (explains principles and terms); 2. Color Picture Reproduction (describes picture tube types and function); 3. Principles of NTSC Color System (describes color signal, methods of transmission and reception); 4. Color Receivers (theory of operation); 5. Circuit Analysis of Color Receivers (full description of circuits and special components). Complete, authoritative, fully illustrated. 224 pages. 5½ x 8½". **Order BA-1, only \$2.00**



"Photofact Television Course"

A complete, simple explanation of modern Television principles, operation and practice. Covers Cathode Beam Formation and Control; Beam Deflection Systems; Beam Modulation and Synchronization. Includes analysis of CR tube construction, camera tubes, voltage supplies, saw-tooth generators, sync circuits, control functions, receiving antenna circuits, RF input tuning systems, IF systems, AGC, etc. Fully illustrated. 208 pages, 8½ x 11". **Order TV-1, only \$3.00**

"Analyzing & Tracing TV Circuits"

Milton S. Kiver's new approach to television servicing. Shows you how to best utilize the data included on the schematic, so that you can speed up repairs and earn more. Shows how to trace specific sections of a TV receiver. The importance of properly analyzing voltages on the tube elements is stressed. Helps you solve the toughest TV service problems in the shortest time. Fully illustrated. 168 pages, 8½ x 11". **Order JA-1, only \$3.00**

"TV Servicing Time-Savers"

A new, extremely helpful book by Milton S. Kiver. Prepared in 5 sections presenting 51 "Time-saver Tips" showing causes and cures of common TV troubles. Shows how to improve reception; includes practical time-saving tips; covers alignment problems, etc. Any one of the 51 "tips" may save you more than the low cost of this book. 124 pages; illustrated, 5½ x 8½". **Order JC-1, only \$1.50**

"TV Service Data Handbook"

A compilation by Milton S. Kiver of the most frequently needed charts, tables and formulas required in TV servicing and installation. Includes charts and tables on fuses, color codes, attenuator pads. A section on trouble shooting lists nearly all TV trouble symptoms along with suggestions for locating the defective component. Includes valuable mathematical constants and electrical formulas. 112 pages, 5½ x 8½". **Order JB-1, only \$1.50**

"Telecasting Operations"

Here, in one complete, easy-to-understand volume, Harold E. Ennes tells the whole fascinating story of the equipment and techniques used in Telecasting. Covers such subjects as: The TV Camera; The TV Control Room; Fundamentals of Studio Lighting; Network Program Relay Systems; Maintenance Practices; Technical Production; Field Equipment and Microwave Relays, plus hundreds of other subjects. 600 pages; fully illustrated; 6 x 9". **Order OH-1, only \$7.95**

"Servicing TV in the Customer's Home"

Provides practical, proved help for technicians and outside TV service calls. (New enlarged edition, including advance data on Color TV receivers.) Saves time, work and chassis hauling — shows how to make successful repairs on the spot by using a VTVM and capacitor probe to trace trouble; by "tube-pulling" to diagnose audio and picture trouble; by performance tests through analysis of the picture test pattern; etc. 128 pages; illustrated; 5½ x 8½". **Order TC-1, only \$1.75**

"TV Servicing Short-Cuts"

This helpful book describes a series of actual TV service case histories, each presenting a specific problem about a specific receiver. The symptoms of the trouble are outlined and then followed by a step-by-step explanation of how to solve it. Finally there is a discussion of how this particular trouble can be tracked down and solved in any TV set. 98 pages; 5½ x 8½". **Order TK-1, only \$1.50**

"TV Test Instruments"

Provides basic explanations of how each test instrument operates; describes functions of each control and shows their proper adjustment. Covers: Vacuum Tube Voltmeters, AM Signal Generators, Sweep Signal Generators, Oscilloscopes, Video Signal Generators, Field Intensity Meters, Voltage Calibrators. Describes use in actual servicing. 180 pages; illus.; 8½ x 11". **Order TN-1, only \$3.00**

Look for the SAMS "BOOK TREE" at your Parts Distributor



Make it a habit to browse at the "Book Tree." It's loaded with the time-saving, profit-building books you want and need to keep ahead in every phase of Radio and TV servicing. Get these and other Howard W. Sams Publications at your Electronic Parts Distributor.

HOWARD W. SAMS & CO., INC.

ORDER THESE OUTSTANDING BOOKS FROM YOUR

PHOTOFACT DISTRIBUTOR

OR WRITE TO

HOWARD W. SAMS CO., INC.

2201 E. 46th STREET

INDIANAPOLIS 5, INDIANA

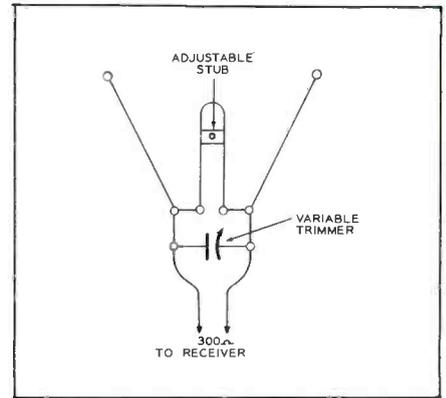


Fig. 9. Connections in the Spico Model 501 Indoor Antenna.

Fig. 8. The connections in the Spico Model 501 antenna are shown in Fig. 9. There are many more of these improved indoor antennas which cannot be shown here because of limited space; but it will be found that all of the indoor models which feature some method of tuning will provide improved reception almost without exception. This is not only true of installations in apartment buildings but also in residential areas, since the impedance match between antenna and receiver is of prime importance in achieving satisfactory reception.

CBS-Hytron Four-Way Tool

The CBS-Hytron four-way tool shown in Fig. 10 is a pocket tool which was designed to contain in one unit all of the tools normally needed to remove the back cover and the high-voltage cover of a receiver.

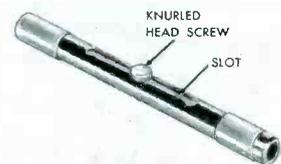


Fig. 10. CBS Four-Way Tool.

To those who like multipurpose tools, this small handy unit should be of interest. The tool has 1/4-inch and 5/16-inch hexagonal sockets at opposite ends. Inside, it has a standard screwdriver and a Phillips-head screwdriver. Either can be used by first loosening the knurled thumb-screw, then by slipping the assembly to one end or the other of the slot, and by tightening the knurled thumb-screw.

IN THE SHOP

Tuner Troubles

Many technicians find that the TV tuner is the most difficult portion

of a receiver to service. This is understandable for three principal reasons.

The first and foremost of these reasons is brought about by the fact that there is a risk of throwing the tuner completely out of alignment when probing around the components or when moving them to get to other parts hidden beneath. Care should most certainly be taken when probing in the tuner.

Secondly, the signal level in the tuner is so weak that most test equipment will detune the circuit to such a degree that the signal is completely lost.

Third, but not least, is the fact that tuners are usually so crowded that the parts are very difficult to change without practically dismantling the tuner. This crowded condition also makes voltage and resistance checks difficult to do.

The favorite method of many technicians when servicing tuners is to attempt to align the tuner after substituting tubes. If there are any troubles in the tuner, such troubles will probably show up during alignment. The portion of the circuit in which the trouble lies can usually be detected by noting the adjustments which fail to provide the proper response. If the tuner will not pass a signal at all, there are two other methods which may be used for testing. Measuring the operating voltages will sometimes disclose a lot, as is true in any other part of the receiver. Since the voltage readings are difficult to obtain because of the crowded condition of the tuner circuits, a test-socket adapter can be used. The use of such an adapter permits the measurement of the voltages from the top of the chassis during operation. These adapters were discussed in the June 1954 issue of the PF INDEX on page 65.

In some tuners, however, test-socket adapters cannot be used for measuring the voltages of the oscillator because the added capacity, small as it may be, will sometimes throw the oscillator completely out of operation. If the oscillator voltages cannot be read from the underside of the chassis in such cases, the technician must rely upon resistance checks. These checks may be done from the top of the chassis at the tube sockets. It must be kept in mind when making measurements of any kind from the top of the chassis that the socket pins are numbered in a counterclockwise direction.

One of the most common troubles encountered in TV tuners using a cas-

code circuit is a cathode-to-heater short in the RF amplifier. This trouble very often causes much more damage to the set than is normally caused by a bad tube. A study of the partial and simplified schematic shown in Fig. 11 will indicate what happens when the second section of the RF amplifier becomes shorted between the cathode (pin 3) and filament (pin 5). Since one side of the filament is connected directly to ground, any element which touches the filament will naturally become grounded. If a heater-to-cathode short exists, the cathode which normally has a potential of approximately 105 volts with respect to ground will lose this voltage. The grid, which normally has a voltage of slightly under 105 volts, immediately starts to draw current. The grid voltage drops so that it is very close to the cathode voltage which is zero under these conditions. At the same time, the effective plate voltage on the second section of the tube is practically doubled; and much more than normal plate current is drawn. It was found by actual tests that the plate current increases to approximately 35 milliamperes when the cathode is shorted to ground. This current is three to four times the normal plate current for this tube.

If the receiver is allowed to operate for any length of time in this condition, the result will be burned-out resistors in the plate circuit. In the case of the tuner shown in Fig. 12, the resistors that would be damaged are R8 and R52. The plate current of the RF amplifier must pass through both of these resistors. With zero bias on the stage, R52 would have to withstand a dissipation of five and one-half watts. Since a one-watt resistor is usually used for R52, it naturally burns out. Since R8 is usually a one-watt resistor but of a much smaller resistance (470 ohms), it normally only becomes charred and increases in value instead of burning out.

It is sometimes rather comical (to a person not involved) the way we mortals jump to false conclusions at the slightest opportunity. These false

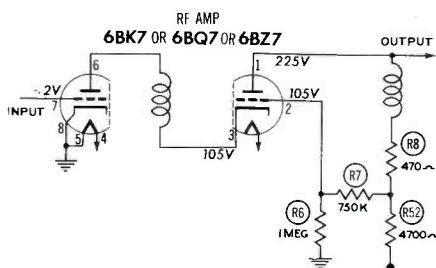


Fig. 11. Simplified Partial Schematic of Cascade-Coupled RF Amplifier.

conclusions are not funny, however, to those involved in the mistake; because all too often these mistakes cost us time, money, and loss of temper.

An example of this type of mistake is illustrated by the following incident. A television receiver was brought to a technician with the complaint from the customer that it had appeared to be on fire. Judging from the odor, it must have been.



By use of his sense of smell, the technician was very quickly able to trace the odor to the tuner. When he pulled the shield off the bottom of the tuner, he noticed that two resistors were burned. The symptoms were identical to those encountered in a receiver that had been repaired the previous week and which had been found to have a heater-to-cathode short in the 6BZ7A. With this in mind, he made one check. Using the tube tester, he checked the 6BZ7A duo-triode for short circuits. The tester showed a heater-to-cathode short. That was all he needed to know. He went straight to work replacing the resistors and the 6BZ7A tube. He then put the set back together and turned it on for adjustment, confident that he had fixed it; but after about a minute of waiting for the picture to come on, he noticed smoke coming out of the tuner. He quickly turned off the set and removed the bottom shield of the tuner. The resistors were again badly burned. The next logical step was to check the new tube to see if by chance it was also shorted between the heater and cathode. It was not; however, thinking that perhaps the tube was breaking down under load, he tried another tube. The resistors again showed signs of overheating.

By this time, the technician was beginning to suspect that perhaps the old tube had not caused the trouble in the first place. He retrieved the old tube; and using an ohmmeter, he started measuring for shorts between pins. He found a heater-to-cathode short, but it was between pin No. 8 and the filament instead of between pin No. 3 and the filament. This meant that the short was in the first section instead of in the second. Thus, the short could not have caused the trouble, because pin No. 8 was connected to ground. This meant that the trouble had to be caused by some other component in the circuit.

After closely examining the schematic diagram in Fig. 12, the technician decided that the trouble had to be a short in the plate decoupler C12. His conclusion was brought

ATR

INTRODUCES

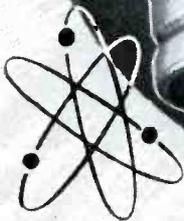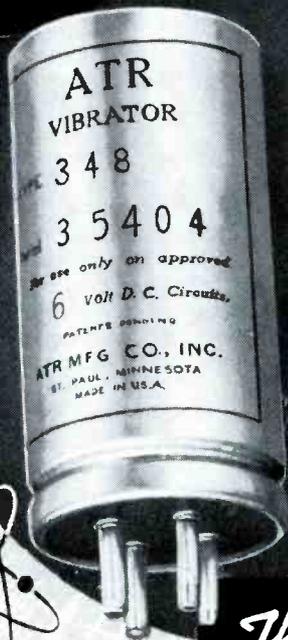

The World's Finest Communication VIBRATORS

featuring:

- CERAMIC STACK SPACERS
- 1/4" DIAMETER POWER CONTACTS
- DRIVER-TYPE COIL CONSTRUCTION
- SPECIAL REED HINGE and WIRING
- POWER CAPABILITY UP TO 15 AMPERES

A COMPLETE LINE OF REPLACEMENT

ATR VIBRATORS

FOR AUTOMOTIVE, HOUSEHOLD and TWO-WAY COMMUNICATION SETS

ATR VIBRATORS are proven units of the highest quality, engineered to perfection. They are backed by more than 23 years of vibrator design and research, development and manufacturing. ATR pioneered in the vibrator field.



FREE - Just off the Press!
1954 ATR VIBRATOR
MASTER MANUAL

See your jobber or write factory today
for complete information

ATR

AMERICAN TELEVISION & RADIO CO.

Quality Products Since 1931

SAINT PAUL 1, MINNESOTA - U. S. A.

about by the following manner of reasoning.

In order for R8 to become burned, the excessive current which had burned R52 would have to be passing through it, too. This meant that there had to be a short between ground and the junction of R8 and C12, or it meant that a high current had to be flowing through the tube. Therefore, the trouble could not be a short in either C28 or C81 because the high current which would have resulted, if either were shorted, would not flow through R8. C13 and C14 were also excluded as possibilities, because a short in one of them would probably have done damage to the mixer circuit instead of to the RF stage. If C11 became shorted, an increase in bias on the tube would result, and that would reduce the plate current rather than increase it. As a result, C11 was also eliminated.

On the other hand, if C12 were shorted, the full plate voltage would be placed on the grid and cause a very high plate current. This high current passing through R8 and R52 would surely burn them out.

The foregoing theory proved to give the solution to the problem; for when C12 was measured, it proved to be shorted. After C12 was replaced, operation returned to normal. Incidentally, the resistors R8 and R52 had to be replaced again because of the fact that the overheating caused by the high current resulted in an increase in their values.

Although this trouble with a shorted capacitor was rather difficult to locate and to eliminate, it need not have been if the technician had been more careful in his first tests. In other words, if he had noted which section of the tube had the heater-to-cathode short when he tested it, he would no doubt have found the trouble much sooner.

It is a recognized fact that in most instances, a dead tuner is much easier to repair than a tuner which is either intermittent or has low gain.

In the case of an intermittent condition, make sure that the trouble is in the tuner by first connecting a scope to the looker point which is provided on top of most tuners and by clamping the bias of the RF stage with an external battery. Then watch the scope to see if the amplitude of the signal changes during the intermittent operation. If it does, then you can be sure the tuner is at fault. Otherwise, it is probably not the tuner; and you can look elsewhere for the trouble in the receiver.

6 MORE NEW TRIAD *CORRECT REPLACEMENT FLYBACKS

These new flybacks are mechanically correct and electrically correct ruggedized versions of manufacturer's items—precisely engineered by TRIAD for specific makes and models—to give exceptionally high performance and long, trouble-free service.

D-45 List Price \$10.00
*Correct Replacement
for Zenith S-20908,
S-15911, S-15912,
S-16566, S-17130,
S-17140, S-17233,
S-17245, S-17265,
S-17435, S-17646,
S-17767, S-17811,
S-17927, S-18930.



D-46 List Price \$10.50
*Correct Replacement
for Muntz TO-0031
TO-0031-1, TO-0031-2.



D-47 List Price \$10.50
*Correct Replacement
for Muntz TO-0036,
TO-0036-1, TO-0036-2.




D-48 List Price \$8.25
*Correct Replacement
for Crosley 158481-1,
187820-5-1; Sentinel
20E995; Hallicrafter
55D251, 55D253.



D-49 List Price \$8.25
*Correct Replacement
for Admiral 79C60-2,
79C60-3, 79C60-5.



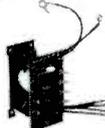D-55 List Price \$11.00
*Correct Replacement
for RCA 211T5.
Voltage doubler type.



WRITE FOR FREE LITERATURE
Triad *CR Transformers are
listed in Sams Photofact
folders and Counterfacts.



4055 Redwood Ave. • Venice, Calif.



Dollar and Sense Servicing

(Continued from page 51)

PEGBOARD. That new Sylvania tube and tool tender is a "honey" for home calls; be sure to look it over. Besides being a carrying case for tubes, it has pegboards and a supply of 100 special spring clips for holding the small tools used in servicing. The clips are far better than the wire inserts sold by lumber dealers for use in pegboards. There's even room for a multimeter, soldering gun, and mirror. The case opens up in such a way as to form a miniature equivalent of a workbench when placed on a chair or table. Wish we could buy those spring clips separately for use on our own workbench pegboard.



BILLIONS. This country paid out around \$1.7 billion to service technicians last year for replacing some 88 million receiving tubes; about 5 1/2 million picture tubes; and \$400 million worth of components, antennas, and accessories — according to an RCA estimate. This year should run a bit better, and by 1957 it is estimated that the servicing bill will hit an all-time high of \$2.7 billion. The rise is predicated on acceptance of color television with its increased servicing problems, because servicing income from radio and black-and-white TV is now well stabilized.



FINGERPRINTS. No matter how good a job you do on the roof, grimy fingerprints on the window sill near the TV lead-in are what the lady'll be thinking of when you present the bill. For just this situation, there's now a waterless on-the-job hand cleaner that comes in a squirt can of proper size to fit into the tool box. A touch of the button and out comes a blob of white foam that works like magic when rubbed over the hands. A cloth, paper towel, or piece of Kleenex completes the job. Distributors are now stocking this. Ask for a can of Handy at \$1.49, made by Planet Sales Corp., of Bloomfield, N. J.

JOHN MARKUS

Audio Facts

(Continued from page 29)

distorted. The conclusion was reached that on the many occasions when the loudspeaker had been overloaded, the breakup in sound had actually been due to distortion caused by peaks which exceeded the power capabilities of the inadequate amplifier being used at the time.

Tests verified the 50-watt rating of the Model 260. Our measurements revealed less than one per cent intermodulation distortion at 50-watt output.

The specifications supplied by the manufacturer are:

Power Output — 50 watts.

Controlled Frequency Response — within 0.5 db, 20 to 20,000 cps.

Input — full 50-watt output with input of 9.9 volts.

Intermodulation Distortion — under 0.5 per cent at 45 watts; under 2 per cent at 50 watts.

Harmonic Distortion — under 0.1 per cent at 45 watts; under 0.5 per cent at 50 watts.

Noise — in excess of 85 db below rated output.

Damping Factor — 9.

Dimensions — 12 inches wide by 7 inches deep by 7 1/4 inches high.

Weight — 27 pounds.

The specifications also state that the amplifier is guaranteed not to ring at any level because it is designed to be stable with a loudspeaker load. In our tests, no instability or ringing was detected at any time with a loudspeaker connected to the amplifier output, even when reproducing square waves. Ringing or oscillations at high or supersonic frequencies are prevented in the Model 260 by rolling off the high-frequency response, starting at about 20,000 cps.

The amplifier and its tube complement do not appear unusual, as can be seen in the illustrations (Figs. 1, 2, and 3) and in the schematic shown in Fig. 4. Much the same arrangement has been used in many amplifiers producing maximum outputs of only 15 to 25 watts; but the Model 260 makes use of an excellent output transformer tapped for screen connections, fixed bias, and an adequate power supply to achieve high power output.

The circuit, as mentioned previously, is conventional in most respects. The first stage using a 6AB4 tube designated as V1 is a voltage amplifier. Negative feedback is accomplished by connecting the feedback resistor R16 from the secondary of the output transformer to the cathode (pin 7) of V1. The 430-mmf capacitor C6 connected across the plate-load resistor R5 serves to roll off the extreme high frequencies and prevent oscillation (ringing) at super-sonic frequencies.

The first half of the 12AU7 tube designated as V2 is a voltage amplifier which is direct-coupled to the second section. This section is a split-load phase inverter. The screens of the 1614 tubes designated as V3 and V4 are connected to taps on the primary of the output transformer in a manner similar to that discussed in the article "The Williamson Amplifier, A Modified Design" in the February 1954 issue of the PF INDEX.

Fixed bias is employed in the output stage. The bias can be adjusted by plugging a DC voltmeter into the test jack by means of a phone plug and then by turning the bias control R3 until 0.45 volts are indicated on the meter.

The output stage can be balanced by inserting the phone plug (the meter need not be connected to the plug) into the test jack, with the 12AU7 tube V2 removed from its socket. The amplifier is then turned on, and the balance control R2 is turned until minimum hum is heard in the loudspeaker. This null indicates balance.

This convenient method of obtaining balance is made possible by the arrangement which places an AC voltage on the movable contact of the balance control R2. This voltage is fed to the control through C10 when the normally open contact of the test jack is closed by inserting the phone plug in the jack. The AC voltage is out of phase on the grids of the 1614 tubes and cancels out when perfect balance is reached.

The power supply, which uses two 5V4G rectifier tubes in the plate supply section and a selenium rectifier in the bias supply, is straightforward and needs no explanations.

The Model 260 is not large physically, but it is heavy for its size. Its 50 watts of power output make it a powerful performer but not beyond reason. This amplifier should satisfy the most critical listener. It has adequate reserve power and provides virtually distortion-free reproduction at normal as well as high levels.

ROBERT B. DUNHAM

March, 1955 - PF REPORTER

Smart Servicemen

Are Modernizing Current TV Sets

And...


*Making
dollars*



By Using

Conversion Chassis CC-1

And...

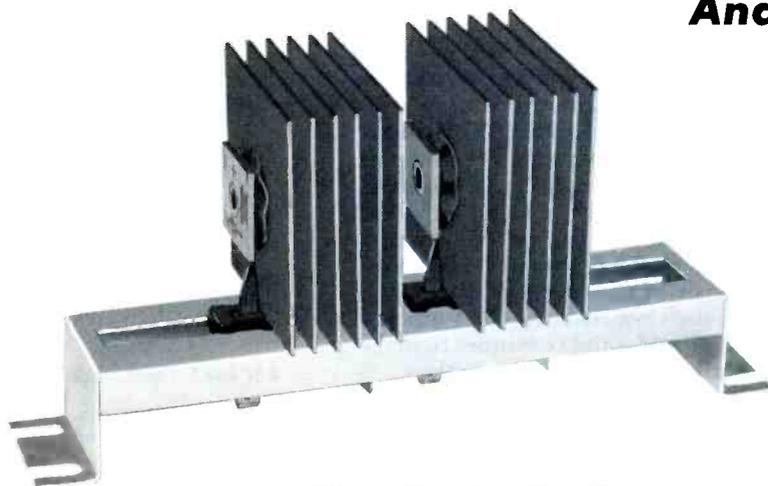

**...The Only Truly
Universal Plug-In* Replacement
Rectifier That Can Also Be
Bolted And Soldered**

* PATENT APPLIED FOR

*Get a copy of the latest Selenium Rectifier
Replacement Guide from your distributor*

**Sarkes
Tarzian**, INC.

RECTIFIER DIVISION

415 N. COLLEGE. DEPT. PF-1. BLOOMINGTON, IND.

*In Canada: 700 Weston Rd., Toronto 9, Tel. Murray 7535
Export: Ad. Auriema, Inc., New York City*

New PORTABLE DOUBLE-DUTY Money-Maker



Size only 11"x7 1/2"x5"

Spots the Trouble and Quickly Corrects it—without removing tube from set!


Now it's easy to save thousands of weak and inoperative TV picture tubes. As much as 80% of the troubles which arise in picture tubes may easily be repaired with the CRT. This amazing portable instrument creates new profitable picture tube repair business. Saves servicing time, speeds work. Assures more satisfied customers. Eliminates tube transportation. Saves money on trade-in reconditioning. And at such low cost, the CRT quickly pays for itself—and continues to make big profits for TV service-dealers.

See Your Distributor or
Write for Bulletin No. 102-R

TESTS and REPAIRS TV PICTURE TUBES

Amazing
Low Price **\$54.95** NET

No extra accessories necessary

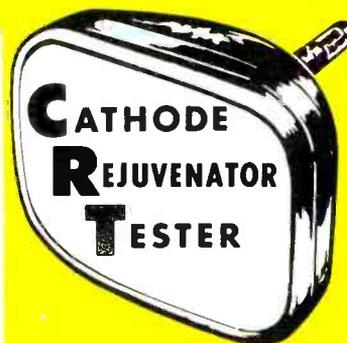

DOES ALL THIS

TESTS FOR Emission, Inter-Element Shorts, Leakage, Open Circuits, Grid Cut-Off, Gas Content, Probable Useful Life

RESTORES Emission and Brightness

REMOVES Shorts

REPAIRS Open Circuits

Less than one foot long.
Weighs only five pounds.

B&K MFG. CO. 3731 N. Southport · Chicago 13, Illinois

Notes on Test Equipment

(Continued from page 19)

power-factor checks when the bridge is set up to check electrolytic capacitors. The power factor of a capacitor is the result of an internal resistance effectively in series with its capacitance. This resistance can be balanced by the proper value of resistance in another arm of the bridge circuit. The potentiometer used to obtain this balance is calibrated to indicate the value of the power factor.

In most capacitor checkers, the final form of bridge circuit used to check electrolytic capacitors will be similar to that of Fig. 1C. The unknown capacitance is to be connected across the terminals at C_X . C_S is a standard capacitance to which the unknown capacitance is to be compared and is selected internally by a certain position of the operating controls of the tester. C_S and R_f are in series to form one arm of the bridge circuit. The two ratio arms R_a and R_b are combined in one resistance in the form of a potentiometer, and this potentiometer is the main operating control for adjusting for bridge balance. Adjustment of this control varies the ratio between the bridge arms R_a and R_b ; and at the same time, the pointer will indicate the proper capacitance value on the instrument dial.

Certain modifications of the basic bridge circuit make it adaptable for special applications; thus, one variation may make the bridge more suitable for measuring small capacitances, another may make it more suitable for reading inductances, and so on. These modifications will not be covered in detail in this article; a great many variations may be found in textbooks dealing with electrical measurements.

Shorted or Open Capacitors

The bridge test furnishes information about the amount of capacity or resistance involved, but there are still several quality checks that must be performed to obtain a complete picture of the condition of the component being tested. A shorted or open condition renders a capacitor useless for all normal applications; therefore, it is important to provide a check for these conditions.

It is sometimes found that a capacitance bridge will give no indication of balance for a given capacitor except at the extreme end of its range. If this indication occurs at the low-capacitance end, the capacitor is considered to be open; and if this indication occurs at the high capacitance end, the capacitor may be considered to be shorted. Some bridges

1440 pgs.

Fully catalogs
Radio-TV-
Electronic
parts &
equipment:
Tubes,
Trans-
mitters,
Test Equip-
ment, Comm.
Receivers,
Transformers,
Capacitors,
Antennas,
Resistors,
Coils & Relays,
Recording &
PA Systems,
Hardware,
Tools, etc., etc.
**OFFICIAL BUYING
GUIDE OF THE
INDUSTRY**

1440 page MASTER for everything in Electronics

Make rapid selections from one industry-wide MASTER CATALOG complete with SPECIFICATIONS, ILLUSTRATIONS, DESCRIPTIONS, DIAGRAMS, PRICES on thousands of Radio-TV-Electronic parts and equipment.


NEW! 1955 BUYING GUIDE

List \$6.50

As low as **\$1.95** • Over 85,000 • Fully indexed items • 8 1/2" x 11" • Over 8,500 illus. • Weighs 6 lbs.

From leading parts distributors or write to:

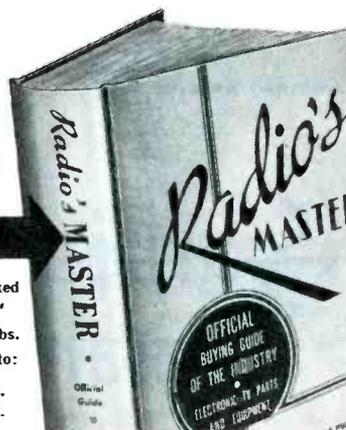UNITED CATALOG PUBLISHERS, INC.
110 Lafayette Street, New York 13, N. Y.



have the extremes of the dial marked in that manner. Others have a separate test for opens and shorts, and this test may take the form of a quick check that may be performed without the necessity of disconnecting the component from the rest of the circuit. At least one manufacturer has made this feature the basis for a separate instrument. (See the PF REPORTER for November 1954, page 72.)

Within certain limitations, an ohmmeter may be used to check for an open or shorted condition of a capacitor. To perform this check, set the ohmmeter to a high-resistance range; and watch the meter needle closely while the ohmmeter leads are touched across the capacitor. A momentary "kick" of the meter needle indicates that the capacitor is not open. If the capacitor is of a low value, the charging current may be too small to be noticeable on the meter. Some shorts will be shown by the meter test, but others may require a higher voltage than that furnished by the ohmmeter and therefore will not be detected.


Leakage or Insulation Resistance

Leakage is usually thought of as applying to electrolytic capacitors, and insulation resistance is thought of as applying to other types; however, both can be measured by the amount of current that a given DC voltage will force through the capacitor in question. In the case of insulation resistance, the meter is calibrated to read in megohms instead of current.

In a leakage test, a voltage of the proper polarity and magnitude is applied to the electrolytic capacitor; and the leakage current is read directly on the meter. This current value can be compared with standard values for new capacitors of similar voltage rating and capacity. Thus, a relative indication of the condition of the capacitor is obtained. It is important that this leakage be below certain values to avoid excess loading of any circuit involved. An excess of current will also cause heating of the capacitor and subsequent deterioration. Some capacitor checkers use a neon indicator to show a leakage condition. A slight amount of leakage is shown by a slow rate of flashing of the neon lamp. More leakage results in a faster rate of flashing; and if the leakage is great enough, the lamp glows brightly and continuously.

The nature of an electrolytic capacitor is such that both its capacity and leakage may change considerably if it is allowed to remain

Fig. 1. Evolution of a Capacitance Bridge. (A) Simple Alternating-Current Bridge. (B) Modification of Alternating-Current Bridge. (C) Final Form of Capacitance Bridge.

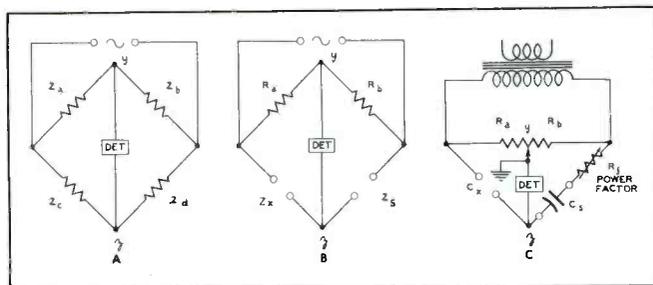

idle for a long period of time. A re-forming period will usually restore the capacitor to its original condition. This re-forming action can be supplied by the capacitor tester. In fact, if the change has not been great, it is usually corrected by performing a leakage test. During this test, the leakage becomes less and less and finally tapers off to a steady value. Any improvement in the condition of the capacitor is indicated by the instrument. As the leakage becomes less and less, the applied test voltage will rise a little so that a slight readjustment of this voltage may be needed.

The insulation resistance of paper, mica, and ceramic capacitors is much greater than that of electrolytic capacitors and is measured in terms of hundreds or thousands of megohms. It might seem that a resistance of 500 megohms would be an adequate figure for a coupling capacitor, but the following reasoning will show that this is not necessarily true. Fig. 2 shows such a capacitor used as a coupling to the grid of an amplifier stage having a 10-megohm grid resistor. This is not an uncommon value where grid contact potential is used for bias. The preceding stage is shown as having a plate voltage of 100 volts DC. The 500-megohm resistance of the capacitor is in series with the 10-megohm grid resistor, and 100 volts is applied across the total resistance of 510 megohms. The voltage developed across the grid resistor is 1/51 of 100 or approximately 2 volts. Moreover, the polarity of this voltage will be positive at the grid with respect to ground; and so this voltage will be subtracted from any value of grid bias developed by contact potential in the amplifier tube. It can therefore be seen that very high insulation resistances are required for some applications and that an insulation test is helpful in selecting capacitors for these applications or in locating troubles caused by low insulation resistance.

The usual procedure in setting up such a test is to adjust the instrument, before connecting it to the capacitor, until infinite resistance is indicated. Then when the capacitor is connected, it will charge because

of current flow through the internal resistance of the instrument; and the final value of insulation resistance can be read on the meter. For large values of capacitance, the charging rate is slow; consequently, an added control feature is sometimes provided for a quick charging rate. The operation of this control momentarily shunts a part of the charging circuit, allowing the capacitor to charge quickly.

A safety feature is usually provided to discharge any capacitor before it is removed from the capacitor checker. This removes any shock hazard which might be present after a test.

Testing Intermittent Capacitors

An intermittent condition of a capacitor will be indicated, as the capacitor is tapped, by a fluttering of the electronic eye or of the indicating device used. As was true with the shorts check, sometimes an intermittent condition will not be apparent unless the capacitor is subjected to higher applied voltages like those encountered in actual use. An intermittent condition of this type may prove difficult to locate.

RF Impedance

RF impedance is an important factor when considering the use of a capacitor as an RF bypass. If the capacitive reactance were the only consideration, any capacitance above a certain value ought to work well as a bypass since the reactance decreases with an increase in frequency. Therefore, it would seem reasonable

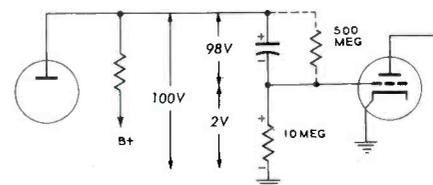


Fig. 2. Partial Schematic Showing Effect of Low Insulation Resistance. Contact Potential Is Reduced by Leakage Through the Capacitor.

to assume that all frequencies above a certain minimum would be effectively bypassed. Other factors enter into the case, however; and the RF impedance may actually increase at some higher frequencies. This increase in RF impedance of the electrolytic capacitor is due to such properties as: inductive value, characteristics of the electrolyte and film, and the disposition of the lead assembly. For this reason, we find circuit designs that use additional capacitors in parallel with some electrolytic bypass or filter

capacitors. These additional capacitors are nonelectrolytics of small value, and they serve to shunt the RF impedance of the electrolytic capacitor. A test of the RF impedance would be useful in selecting capacitors for special application or in tracing troubles caused by this RF impedance.

Most test-instrument manuals are well written and provide the service technician with complete instructions for operating a particular piece of equipment. A good

manual for a capacitor checker will probably contain, in addition to the operating instructions, several charts or tables giving pertinent information about capacitors. Normal insulation resistance and leakage, power factors of new electrolytic capacitors, and capacity tolerances are a few of the things these charts or tables may list. A good capacitance checker, together with a well-written manual, should make it easy for the technician to determine with speed and certainty the condition of any capacitor. This is more satisfactory than a cut-and-replace policy, as anyone will agree if he has struggled with a multi-section electrolytic only to find that the trouble was caused by some other component.

RECENT RELEASES

AUTHORIZED MULTIVOLTER MODEL 301



Fig. 3. Authorized Multivolter Power Supply.

The Authorized multivolter pictured in Fig. 3 is a product of Authorized Manufacturers Service Co., Inc., 919 Wyckoff Avenue, Brooklyn 27, N. Y. The instrument is a miniature power supply and is designed to furnish DC voltages from -135 volts through 0 to +135 volts and to furnish AC voltages from 0 to 135 volts. In addition, one ampere at 6.3 volts may be obtained for filaments from separate terminals. A neon-lamp indicator is lit during normal operation and is extinguished when an overload current of more than 20 ma is drawn.

The instrument is housed in a molded phenolic case of small size, 3 3/4 inches by 6 1/4 inches by 2 inches, and will fit easily into a tool box or tube caddy. The weight is 2 pounds. Other specifications include:

DC volts: no-load voltage is continuously variable from -135 to +135.

AC volts: no-load voltage is continuously variable from 0 to 135.

Output resistance: varies inversely as the output voltage varies.

Your Ideal **SECOND** Soldering Tool

This newest Weller Soldering Gun fills your need for an *extra* soldering tool. Its new, compact design includes *all* regular Weller Gun features, at a rating of over 100 watts. Its new, low price makes it as convenient to buy as it is to own!

SEE THE WELLER **Junior** AT YOUR DISTRIBUTOR NOW

Weller Junior SOLDERING GUN
827 Packer Street, Easton, Pa.

Power consumption: 15 watts.

Some possible uses listed by the manufacturer are for: source of AVC, AGC, or AFC bias; measurement of amplifier gain; source of bridge voltage; capacitor re-forming; development and testing of original models; component testing; source of calibration voltage; and power supply.

SIMPSON MIDGETESTER MODEL 355

The trend toward miniaturizing in the electronics field has spread to the design of test equipment. This fact is exemplified by the Simpson Midgetester Model 355 shown in Fig. 4. This meter measures 2 3/4 inches by 4 1/2 inches by 1 inch over-all and weighs just under 8 ounces complete with batteries and test leads.

Selection of the various ranges is made by inserting the test leads in the proper test sockets. Leads and sockets are threaded to fit so that once a lead has been properly inserted and good electrical contact is assured, there is no danger of the leads being accidentally removed. The act of inserting the black lead automatically closes a switch in the circuit for measuring DC volts, AC volts, or ohms, depending upon the function selected. The test lead does not make a direct connection between its tip and the switch, because a fiber insulator is interposed.

Measurement ranges offered by the instrument are: 0 to 3, 0 to 12, 0 to 60, 0 to 300, 0 to 1200 volts AC and DC. The total instrument resistance for both AC and DC voltage measurements is 10,000 ohms per volt. Meter-scale calibrations are 0 to 12, 0 to 60, and 0 to 300 volts.

DC resistance ranges are 0 to 10,000 ohms, 0 to 100,000 ohms, 0 to

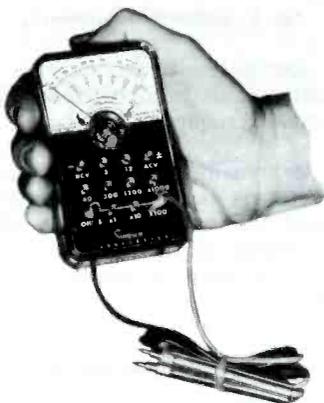


Fig. 4. Simpson Midgetester Model 355.

1 megohm, and 0 to 10 megohms. An adjusting knob labeled OHMS ZERO is provided at one side of the case in a small recessed opening which minimizes the possibility of accidental movement.

The test leads included with the instrument have an insulation rating of 5,000 volts. The probe ends of the leads have sharp conical tips to ensure good contact with the circuit under test. A shoulder on each tip permits the use of alligator clips, if this type of connection is desired.

The range of the instrument can be extended by the use of external multiplier resistors to measure high voltages. The Simpson Operator's Manual lists the values needed to extend the range to 6,000, 12,000, or 30,000 volts.

The Midgetester is housed in a smooth plastic case which surrounds the entire instrument. The face is of clear plastic, and the back cover is of black plastic.

PAUL C. SMITH

C-D's CUB BEST-BAR NONE



MOLDED TUBULAR CAPACITORS

The C-D "Cub" capacitor has proven itself the best on the market today—by out-lasting, out-performing, out-selling any other replacement capacitor for radio or TV. For consistent high quality—always rely on C-D, the only tubulars with the built-in extras required in servicing sets today. That's why distributors *who know*, carry the complete Cornell-Dubilier line.

Special! "Cub-Kit" with bonus plastic service dispenser.

Ask your C-D Distributor. He's listed in your local Classified Telephone Directory.

There are more C-D capacitors in use today than any other make



CONSISTENTLY DEPENDABLE CORNELL-DUBILIER CAPACITORS

PLANTS IN SOUTH PLAINFIELD, N. J.; NEW BEDFORD, WORCESTER AND CAMBRIDGE, MASS.; PROVIDENCE AND HOPE VALLEY, R. I.; INDIANAPOLIS, IND.; SANFORD AND FUGUAY SPRINGS, N. C.; SUBSIDIARY: THE RADIART CORPORATION, CLEVELAND, O.

Frequency Response in Magnetic Recording

(Continued from page 13)

the recording process. A recording head is an electromagnet, and its magnetic field varies with the signal current flowing through its coil. So, since the magnetic field of the head magnetizes the tape, the amount of signal current flowing through the coil of the recording head determines the strength of the magnetic patterns recorded on the tape. The magnetic

patterns are the recorded signal, and their strength is the level of the signal. This can be called constant-current recording because the level of the signal recorded on the tape is constant with respect to frequency.

Various things occur during the recording process to affect the frequency response. At high frequencies, the shunt capacity of the recording-head windings reduces the level of the recorded signal. Hysteresis and eddy-current losses in the core of the head can also cause the high-frequency response to fall off rapidly.

At high frequencies, the poles of the magnetic patterns formed on the tape are very close together and tend to demagnetize each other. This results in a loss of high-frequency response, and the loss increases with frequency and becomes very severe.


While discussing the influence that recording and playback heads have on frequency response, some things that have critical effects upon the operation of the heads should be mentioned.

Azimuth adjustment (the alignment of the gaps in the recording and playback heads so they are positioned at right angles to the direction of tape travel, as shown in Fig. 2) must be correct. Otherwise, the high frequency response will be reduced and excessive distortion will be produced.


OXFORD Speakers
Guarantee Quality Sound

Better sound from OXFORD SPEAKERS... complete line from 2" to 15"... for all replacement needs... ORDER TODAY!

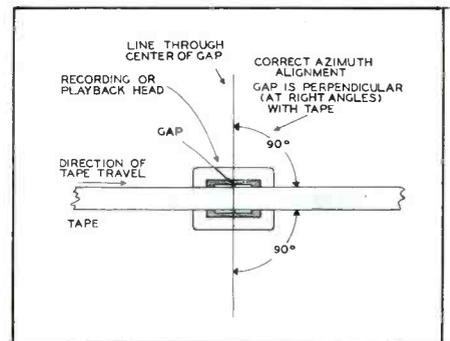
OXFORD ELECTRIC CORPORATION
 3911 South Michigan Avenue • Chicago 15, Illinois
 EXPORT — ROBURN AGENCIES, NEW YORK CITY IN CANADA — ATLAS RADIO CORP. LTD., TORONTO



(A) Correct.

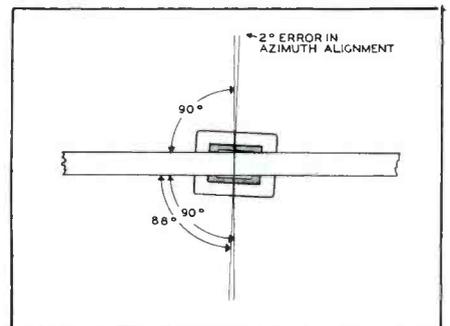

(B) Incorrect.

Fig. 2. Azimuth Adjustment.

Excessive bias current can partially erase the higher frequencies and impair frequency response.

Overloading during recording will saturate the recording head and increase the effective width of the gap. Overloading disturbs the frequency response and produces distortion.

Characteristics of Tape

Two magnetic characteristics of tape, its remanence and coercive

force, influence frequency response. Remanence, the ability of the tape to become magnetized and retain its magnetism when the magnetizing force is reduced to zero, determines how well the low frequencies will be recorded on the tape. Coercive force, the opposition of the tape to a magnetic force which tries to reduce the magnetism of the tape to zero, has a definite effect upon high-frequency response.

As mentioned previously, at high frequencies the poles of the magnetic patterns in the tape are very close together and losses are high because of self-demagnetization. So, a tape with high coercive force to oppose this demagnetization is desirable. But a tape which has a high coercive force has a low remanence or flux density and does not record well at low frequencies.

High coercive force is not important at low frequencies, because wavelengths are long and the self-demagnetization is negligible.

Since the characteristic which aids in low-frequency response causes a loss to occur in high frequencies and since the one that increases high-frequency response produces a loss in low frequencies, a compromise must be reached.

Most improved tapes possess a high coercive force because, in most cases, an extended high frequency response is desired.

Tape Speed

High-frequency response is greatly affected by tape speed; whereas, low-frequency response is nearly independent of speed.

As the speed of the tape increases, the poles of the magnetic patterns recorded on the tape are spread farther apart, resulting in decreased self-demagnetization and reduced losses. Since demagnetization losses are negligible at low frequencies, tape speed has very little effect upon low-frequency response.

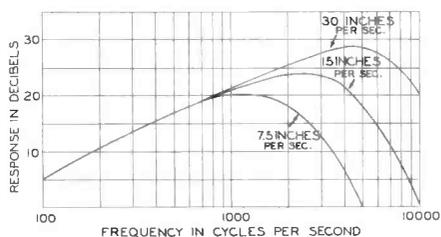


Fig. 3. Curves Showing the Effect of Tape Speed on Frequency Response.


The frequency of maximum response increases with tape speed. If the speed is doubled, the frequency of maximum response will increase one octave. The curves in Fig. 3 illustrate the change in frequency response with increase in speed. Increased tape speed, besides increasing high-frequency response, also increases signal-to-noise ratio.

For most purposes, tape speed has become fairly well standardized -- 3 3/4, 7 1/2, and 15 inches per

second are the most commonly used speeds. Thirty inches per second and higher are used for extended high-frequency response when making certain types of high quality recordings. One and seven-eighths inches per second and no doubt slower speeds are sometimes used when recording voice or material for which wide-frequency response is not required.


ROBERT B. DUNHAM

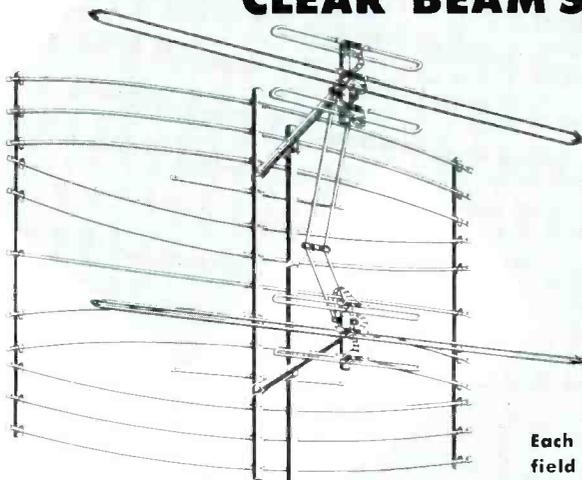HOTTEST IN THE FRINGES..NATION-WIDE! CLEAR BEAM'S **BIG**




Model TK1500

TRI-KING

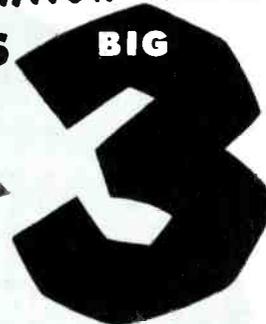

ALL-BAND FRINGE ANTENNAS

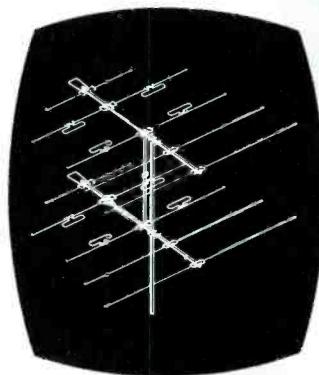
Each a peak performer in its field . . . a triple threat to any fringe problem . . . with more dollar-for-dollar construction value!



Clear Beam **HUNTER**

2 Bay Model MYH 50-2

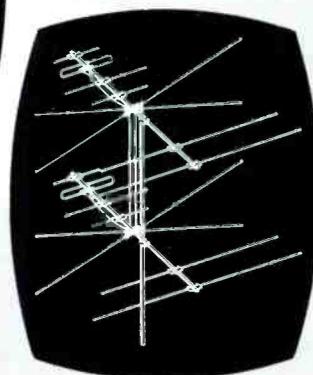New wave trap principle gives extremely high gain, sharp directivity, in-phase tuning on all channels. New, flat design for low wind resistance!



Clear Beam **BIG CHIEF**
2 Bay Model BC 12-2

An advanced conical-Yagi with element diameters varied for precision tuning, matched sensitivity and peak performance on high and low band!

B CLEAR ANTENNA CORP.
BEAM Canoga Park, Calif. • Chicago, Ill.
affiliated with TEMPO TV products

Warehouses in Seattle, Portland, San Francisco, Honolulu, Dallas, Kansas City, Chicago, Detroit, Baltimore

Shop Talk

(Continued from page 17)

carrier, the other by modulating the carrier with a 400-cycle note.

Whichever method is employed, it is necessary to substitute fixed bias for any AGC bias that may be used. This can be achieved by connecting a source of bias voltage between the AGC line and ground. A suitable voltage to use is approximately -2 to -3 volts, unless the manufacturer specifies some other value in his alignment instructions. Or, with a station tuned in and the controls set for a normal picture, measure the AGC bias; then use this value in the gain measurements.

Considering the unmodulated-carrier method first, here is how to proceed. Apply the output of the signal generator to the control grid of the final video IF amplifier. Place a VTVM across the load resistor of the second detector. The VTVM is set to read DC, and the lowest scale is generally chosen. Next, adjust the generator output so that the meter reads some small value, possibly about .5 volt or less. Two things are important in this test. Do not drive any of the stages to saturation or cut-

off, and be sure to employ readings which can be accurately read.

(When a vacuum-tube detector is employed in the receiver, a preliminary voltage measurement across the load resistor should be made with no station or generator signal applied. Any voltage, such as contact potential, should be subtracted from all subsequent voltage measurements made across the load resistor.)


Next, shift the generator signal to the control grid of the preceding IF stage. The meter reading will increase; and if this new value is divided by the initial reading, the amplification of the next-to-last stage will be obtained.

To determine the gain of the second stage from the end, reduce the generator output until the VTVM reading is again .5 volt. Then move the generator back one stage, and note the VTVM reading. This new value divided by the initial .5 volt will be the gain of this stage.

The best video IF value to use is the mid-frequency of the passband. For example, in the 40-mc IF range, 43.75 mc is a good frequency. In the

20-mc range, use 23.75 mc. In stagger-tuned systems, the choice of the signal frequency may have some bearing upon the gain. This may be noted by rotating the dial frequency on either side of the chosen mid-frequency and by noting its effect upon the VTVM reading. If there is a marked rise in gain at some other frequency, that frequency may be used in the measurement.

The reader will note that by the foregoing method, we did not measure the gain of the final video IF amplifier. (We used this stage to set up the initial VTVM reading.) If the technician has a demodulator probe for his VTVM, then the following method will give him a fairly accurate indication of the gain in the last video IF amplifier. Apply the signal from the generator to the grid of the first IF amplifier. Then, with the demodulator probe, measure the signal voltages at the plate and grid of the final video IF amplifier. The ratio of plate-to-grid values will represent the gain of this stage. If you wish, you can check the accuracy of this method by using it to measure the gain of another video IF stage. Check this gain figure with the figure obtained by the previous method. If the two gain values are close, then the demodulator results can be accepted

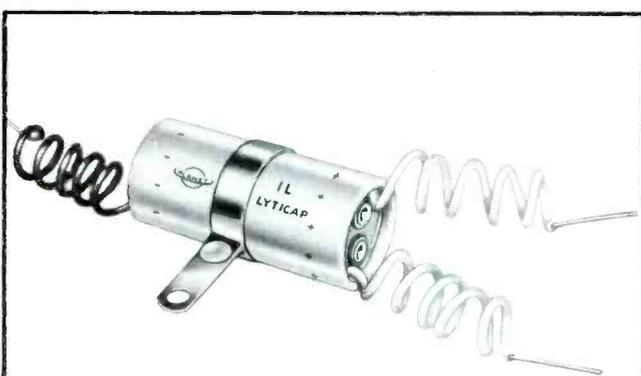

NEW DUAL SECTION ELECTROLYTIC CAPACITORS HERMETICALLY SEALED IN ALUMINUM TUBES WITH COMPLETELY FLEXIBLE INSULATED LEADS. By riveting the leads directly to the condenser end disc, Planet has eliminated the use of rigid terminal risers ordinarily used on this type construction. This allows Planet Type IL capacitors to fit into a smaller space and eliminates the possibility of lead breakage.



"ENGINEERED FOR QUALITY"
GUARANTEED FOR ONE YEAR

PLANET MANUFACTURING CORPORATION
225 BELLEVILLE AVENUE
BLOOMFIELD, N. J.

Write for Catalog 200—Lists Specifications on Stock Items

XCELITE Hand Tools
PREFERRED BY THE EXPERTS

**PROOF IT
PAYS TO
BUY THE BEST!**

**CAN XCELITE
SCREWDRIVERS
take it ?**

**WHILE WE
DON'T RECOMMEND**

this treatment for XCELITE tools, we do think it's a good example of how those Chrome Vanadium blades and tough XCELITE plastic handles can take it — how it pays and pays to buy the best. Have your supplier show you the complete XCELITE line of "lifetime" tools ready to make your day easier!

This R-3164 put in ten busy years in an aircraft plant — another four in a garage — is now "retired" to nightly service in an active workshop. Beaten, run over, burned and used for almost everything, it's still "good for another fifteen years" as its third owner says!

**TIP
NEVER
REGROUND**
(unretouched photo)

XCELITE, INCORPORATED
(formerly Park
Metalware Co., Inc.)
Dept. Q
Orchard Park, New York

For Originality
LOOK TO XCELITE

as obtained; however, if the demodulator value is higher or lower than the figure obtained by the other method, it should be corrected accordingly. For example, if you obtain a gain of 6 via the demodulator method, whereas the previous method indicated that the stage gain was 8, then any gain figures obtained using the probe should be multiplied by 8/6 or 4/3.

A second approach to video IF gain measurements is to use a modulated RF signal. In place of the VTVM, connect an oscilloscope across the load resistor of the second detector. By noting the changes in the peak-to-peak value of the 400-cycle wave as the input point of the RF signal is moved from plate to grid, we can determine the gain of an amplifier. This method requires some means of determining the peak-to-peak value of the 400-cycle wave developed on the scope screen.

In the RF stages, the signal generator can again provide a method of locating a stage with low gain or a break in the signal path. For convenience, a modulated RF signal is used and the horizontal-bar pattern is observed on the scope screen.

It might be supposed that there would be nothing that an RF generator could do in the sync-separator stages, but signal tracing is also possible in them. For this application, we resort to the 400-cycle note contained in the generator. This note will pass through the sync-separator stages and indicate whether a sync signal can get through these stages. For a detecting device, we can connect a jumper lead from the output of the sync-separator stages to the volume control. Any 400-cycle signal that passes through the sync-separator stage will then be heard from the loudspeaker. Absence of the signal indicates that it is not getting through the stage (or stages), and further point-by-point measurements are needed.

All in all, the RF generator is a very useful instrument to have around the shop; and the finer the instrument, the more reliable the results.

REVIEW

Commercial television is now in its ninth year, and many far-reaching advances have been made in design. For example, the average set of 1955 has fewer than 20 tubes, whereas the receivers of 1946 had 30 or more. Furthermore, over-all receiver sensitivity has increased considerably, and the equally important noise factor has gone down. Yet in spite of this substantial progress, antennas (par-

ticularly outside antennas) still are an important adjunct to the development of clear, noise-free pictures.

In a previous review (PF INDEX, June 1954), we discussed the corrective measures that should be taken after an antenna has been up for some time — generally about a year or so. Preceding this, however, is the initial problem of installing the antenna; and much of the subsequent maintenance which an array requires is directly related to the care taken when installation was first made.

An article containing an excellent summary of desirable installation practices appeared in the December 1954 issue of Radio & Television News magazine. The article is entitled "How Good Are Your TV Installations?" and was written by John B. Ledbetter.

Radio & Television News is published monthly by the Ziff-Davis Publishing Company, 366 Madison Ave., New York 17, N. Y. Subscription rates for the United States, its possessions, and Canada are \$4.00 per year. Single copies are priced at 35 cents.

Thirteen recommended installation pointers are discussed in the article. All are reviewed briefly in the following discussion, and it is suggested that the reader compare them with his own techniques to see whether there is any room for improvement.

1. Anchor the Mast Properly.

Do not use clamps or straps which will tend to rust or stretch. Pipe clamps and bracket mounts are suggested if the antenna mast is to be fastened to a wall or to one side of the house. For chimney mounting, straps or brackets may be employed, with brackets favored when the mast is heavy.


2. Use Guy Wires.

The damage which wind and snow storms have wrought on television antennas in recent months has emphasized the desirability of using guy wires when a mast extends higher than 5 to 8 feet. Mr. Ledbetter suggests three guy wires for masts 10 to 15 feet high, six for masts 15 to 25 feet high, and nine or more for greater heights.

In areas where the masts are subjected to high winds, self-supporting or guyed towers are suggested in place of the usual hollow mast. The initial cost is greater, but the former type of construction will give longer trouble-free life; and this is a factor

beyond a shadow of a doubt

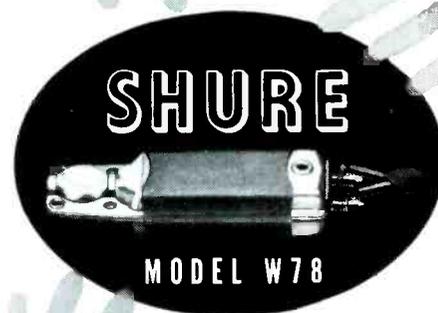the most versatile
78 rpm
crystal phono cartridge
of them all!



THIS DUAL-WEIGHT, DUAL-VOLT
PICKUP CARTRIDGE
REPLACES 149 DIFFERENT MODELS
OF 78-RPM CARTRIDGES!

The W78 Dual-Weight, Dual-Volt Phono Cartridge replaces 149 different steel and aluminum case cartridges currently found in 78 rpm equipment! This versatility shows beyond a shadow of a doubt that the W78 is the most useful crystal phono cartridge ever designed for 78 rpm cartridge replacement business! Actual sales to servicemen prove that the versatile W78 cartridge is a replacement sensation—prove indeed that the W78 fills a great need—here in one cartridge model is the answer to servicemen's inventory problems for 78 rpm cartridges!

MODEL NO.	TYPE	LIST PRICE	OUTPUT LEVEL	MIN. NEEDLE FORCE	RESPONSE TD	NET WT.	SHURE NEEDLE NO.
W78	Crystal	\$5.55	4.0V or 2.0V	1 oz.	6,000 c.p.s.	Dual-Weight 25 grams or 12 grams	None

†Dual-Weight, Dual-Volt Cartridge. Has weight slug secured by shrink-on band. With lead weight, net weight of cartridge is 25 grams. If 12 gram weight is desired, the shrink-on band can be cut off and the lead weight removed. In addition, Model W78 has capacitor, furnished as accessory. Without capacitor output is 4.0 volts; with capacitor output is 2.0 volts.

See your Shure Distributor or write the factory for Replacement Chart which lists the 149 crystal phono cartridges replaced by Model W78

SHURE *The Mark of Quality*


SHURE BROTHERS, INC. • 225 W. HURON ST. • CHICAGO 10

MAKE

\$44⁴⁰

PROFIT

PER WEEK

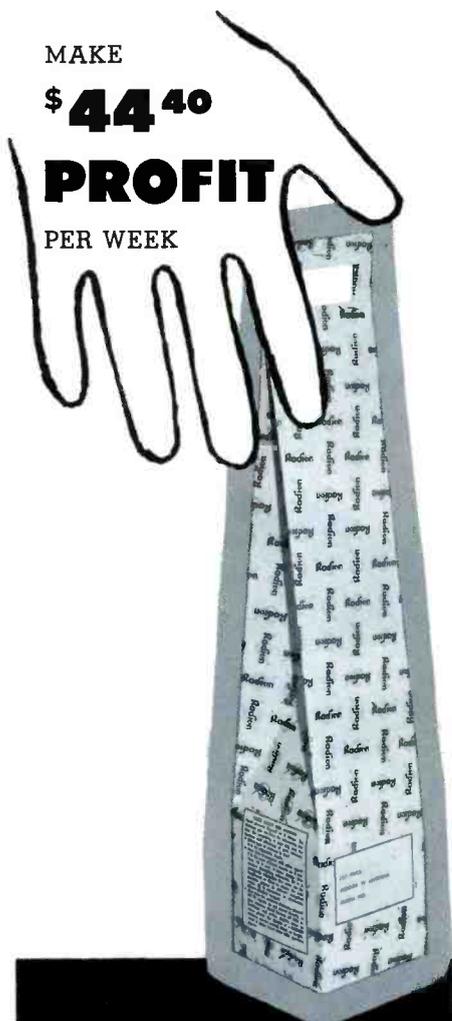

WITH THE NEW

**Radion
PROFIT-PAK**

CARTON



**SELL
only**

12

QTA-3 antennas in new self-merchandising carton. (\$3.70 minimum profit on each)

Contact your distributor today.



THE RADION CORPORATION
Dept. R, 1130 W. Wisconsin Ave., Chicago 14

which is beginning to carry greater weight with a good many customers.

For guy wires, the stranded type of No. 6 or No. 8 steel wire is recommended. It is frequently necessary to insert strain insulators in each guy wire to prevent the reradiation from these elements (which are, after all, equivalent to antennas) from producing ghost images on the receiver screen. There are those who recommend that the uninterrupted length of any guy wire should be made less than the shortest length of antenna; however, it is seldom necessary to break up a wire into this many sections. Your own experience will reveal how many insulators will be needed, but the number seldom exceeds one or two per wire.

3. Use Solid Anchor Points for the Guy Wires.

If the termination point is wood (such as beams or rafters), ordinary screw type anchors with an eye in one end will serve satisfactorily. For termination in brick, mortar, or concrete, some form of expansion bolt such as an Ackerman-Johnson is recommended. If the guy wire is terminated in the ground, specially constructed stakes having radiating spokes must be buried in the earth.

4. Use Ring Lugs.

Ring lugs, known also as solder or terminal lugs, should be clamped on the end of the lead-in wires before connecting the wires to the antenna terminals. This is a far more desirable practice than simply wrapping the lead-in wires around the antenna terminals and depending on the pressure of the terminal heads to hold the wires in place. Wires swing in the wind; and without a shake-free connection, they can be expected to work loose in a short time. By first clamping and then soldering a terminal lug onto the ends of the lead-in wires, the risk of the wires working loose is eliminated.

5. Secure the Lead-in.

A secure lead-in is a salient feature of every good installation and is one of the earmarks of a craftsman. Use a stand-off insulator every 4 or 5 feet on straight runs; use closer spacing, as required, when the direction of the lead-in is altered. The function of an insulator is to hold the line firmly in place. Do not crimp the line since this will alter its characteristics.

If separate lead-ins are employed for both UHF and VHF signals, use special stand-off insulators which act to prevent cross-coupling

LEARN COLOR UHF, MONOCHROME TELEVISION



Edward M. Noll

nationally known TV consultant, teacher and writer

MAKES IT EASY

in the new revised edition of his famous

TELEVISION FOR RADIOMEN

Complete course in one volume

All in one book—at much less cost than the average course of lessons—you'll get THOROUGH, practical training for the best jobs in TV. You'll know the fundamentals of both transmission and receiving; the practical techniques of installation, alignment, adjustment, trouble-shooting; the latest improvements, transistor circuits, UHF, color.

You'll UNDERSTAND TV; be able to handle service work expertly, efficiently; be well qualified for the hundreds of high-paid technical openings in TV today.

Easy to learn

Each step in theory is explained in clear non-mathematical terms and is applied to circuit set-up and operation so you see exactly how to use theory in practical work. Many schematics and how-to-do-it examples help you learn both theory and practical techniques easily and thoroughly. Study questions insure your understanding.


Prepares you fully for work on color TV, UHF

You'll learn each detail of the NTSC color system; the function of each circuit, the special installation and adjustment techniques, the service problems and how to handle them. You'll know the principles and all practical details of the intercarrier I-F system, the best antenna installations for UHF.

There is no better, more up-to-date, or more thorough book on television fundamentals.

HERE is your ticket to the best TV technical jobs today!

See it at your distributor or order from

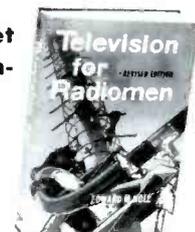

The Macmillan Company
60 FIFTH AVENUE, NEW YORK 11, N. Y.

TABLE I
TRANSMISSION-LINE LOSSES FOR VARIOUS
TEST FREQUENCIES AND LINE CONDITIONS

(In Decibels per 100 Feet)

TYPE OF LINE	100 MC		500 MC		1000 MC	
	Wet	Dry	Wet	Dry	Wet	Dry
	450-ohm open wire*	--	0.35	--	.78	--
300-ohm tubular wire	2.5	1.1	6.8	3.0	10.0	4.6
300-ohm flat wire	7.3	1.2	20.0	3.2	30.0	5.0
RF-59U cable	--	3.8	--	9.4	--	14.2
RF-11U cable	--	1.8	--	5.0	--	7.6

*Estimated values; unknown for wet conditions.

between lines. With UHF signals, it is particularly important that the line be kept as far away from building surfaces as possible.

6. Keep Twin-Lead Away From Metal.

Some metal surfaces most frequently encountered include drain pipes, downspouts, roof flashing, gutters, sheeting, vent pipes, and metal conduits. When a line is to be run over the edge of the roof, use enough insulators to prevent it from brushing up against the roof edge.

Also forbidden is the taping of twin lead-in lines to metal antenna posts. Finally, if shielding of the line is desirable, use coaxial cable. Do not run twin-lead through a pipe. The capacitance which the metal pipe shunts across the line may very well reduce signal strength below a usable level.

7. Protect Lead-in From the Weather.

In order to protect lead-ins from the weather, the following precautions should be taken:

a. Keep the horizontal runs in the lead-in as short as possible. A horizontal surface will permit rain or snow to collect, and the attenuation of a wet line is considerably higher than that of a dry line. A comparison of transmission-line losses in decibels per 100 feet is given in Table I. Note how sharply the attenuation of a 300-ohm flat line rises with moisture. The 300-ohm tubular line is considerably better in this respect and hence would be more desirable. Attenuation of open-wire lines is generally not appreciable, and shielded cables are

not affected at all by inclement weather.

b. Run transmission lines under eaves or straight down as much as possible.

c. If an antenna is mounted on a chimney and the chimney is never used, then the wire may be run down the center of the unit. Never do this when the chimney is to be used.

d. Mr. Ledbetter further suggests that if an antenna is chimney mounted, the array should be positioned so that it is least subject to the collection of soot, particularly across the antenna terminals.

8. Use a Good Ground.

For adequate protection, ground the antenna mast either to a cold-water pipe or by means of a wire to a ground. A rod with a diameter of 3/8 inch or more and a length of 4 to 6 feet will provide the proper low-resistance grounding if driven well into the earth. The grounding lead

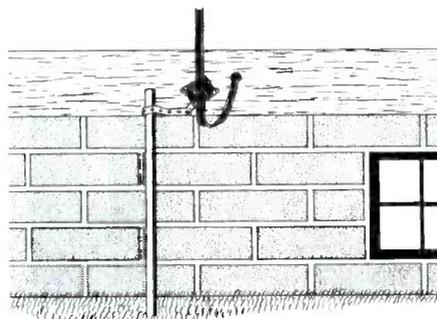


Fig. 2. The Best Position for a Lightning Arrester Is at the Point Where the Transmission Line Enters the House.

should be kept away from the building (if the construction is of wood or shingles). Use an insulated heavy wire, No. 10 or larger.

For those who ignore or pooh-poooh antenna grounding, reference should be made to the "Shop Talk" column in the February 1954 issue of the PF INDEX. The pictures there speak for themselves.

9. Use a Lightning Arrester With Twin-Lead.

In addition to the grounding protection afforded the antenna mast, similar protection in the form of a lightning arrester should be given the lead-in line and the receiver. The most common and the best place to install the arrester is the point where the lead-in line enters the house. See Fig. 2. The ground lead from the arrester may be run directly to its own earth ground, or it may be connected to the grounding lead of the antenna mast if the latter is convenient.

Coaxial transmission lines do not require special lightning arrestors so long as the precaution is taken to ground the outer shield securely. Doing this will afford adequate lightning protection and is sanctioned by the electrical code.

If more than one lead-in is used, install a separate lightning arrester for each line. Finally, clamp or bolt the ground-rod connections — never solder them.

10. Check Reception Before Securing Lead-in Permanently.

The reason for this pointer is so obvious that further discussion is unwarranted.

11. Check the Safety Features of the Antenna.

Safety features include the following: rigid mounting, keeping the antenna structure and lead-in lines away from power lines, and carefully inspecting the mounting surface (such as brick, concrete, or wood) to make certain the surface itself is secure.

The final two items in the article, Nos. 12 and 13, deal with special situations such as installing antennas on flat roofs, sun porches, or slate roofs. In all instances, be careful not to damage the roof. If mounting holes have to be made in the roof, cover these with pitch or caulking compound. On slate roofs, chimney mounting is your best bet.

MILTON S. KIVER

Deflection Yokes

(Continued from page 5)

is in proportion to the square of the cosine of the angle that is between the deflection axis of the coil and the radial position of the winding on the neck of the picture tube.

Service

Deflection yokes for the most part have the same general appear-

ance, size, and mounting feature; but there the similarity often stops. Deflection yokes come in different impedance combinations, deflection angles, insulation ratings, and have different damping networks. To provide sweep for the picture is only one function of the deflection yoke. The deflection yoke must also provide an accurate impedance match for the horizontal- and vertical-output stages so that no distortion will result from a mismatch. Troubles with deflection

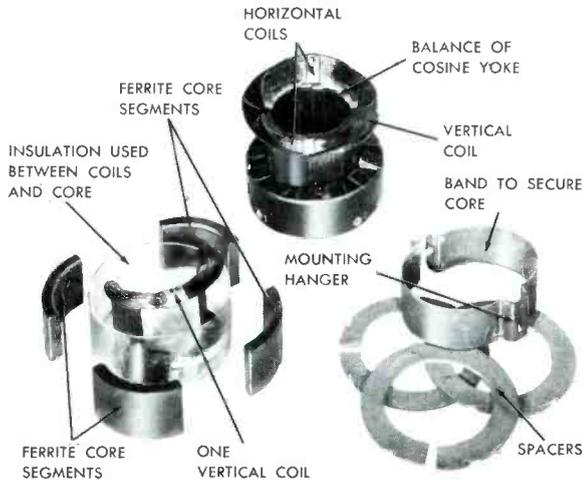


Fig. 4. Partially Disassembled View of a Cosine Yoke.

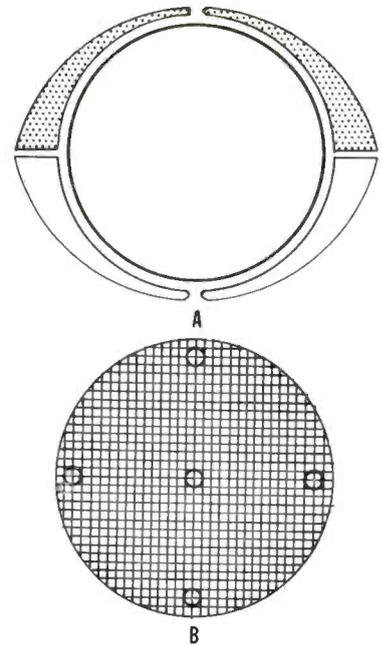


Fig. 5. (A) Cross-Sectional View of One Pair of the Deflection Coils of the Cosine Yoke. (B) Uniform Field Produced by a Cosine Yoke.

yokes will usually fall into one of five categories: (1) short circuits to the core, (2) shorted turns, (3) failure of the damping-network components, (4) open winding, and (5) short cir-

in TV fringe areas...

DON'T GIVE YOUR CUSTOMERS A SNOW JOB!

install a "De-Snow" Preamplifier

Here's your key to snow-free all-channel TV reception in hard-to-reach areas! The Jerrold "De-Snow" Preamplifier, mounted at the antenna, amplifies the *signal*—not the snow. 6BQ7A, 6AK5, and 6CB6 tubes in a new cascade circuit provide a whopping 25-db gain with a noise level of only 6 db (approaching the theoretical minimum). So, even with long cable runs, your customer receives the clearest picture attainable from his antenna.

Available in two models—channels 2-6 or 2-13. *Flat response for color.* See your parts distributor or write Jerrold for illustrated literature.

JERROLD ELECTRONICS CORP.

1405 S. 26th Street • Philadelphia 46, Pa.

JERROLD



Easier, Faster

INSTALLATIONS WITH THE

New LA-75 ARRESTER

LIST \$1.35
Pat. Pending



ANOTHER

Radion

FIRST

ANOTHER

Radion

FIRST

ANOTHER

Radion

FIRST

New twin-lead grip speeds connections.

Flame-proof, waterproof. All hardware included. UL Approved indoors or out. Carry one arrester to fit all needs. Ask your distributor now.

THE RADION CORP.

1130 W. Wisconsin Ave.,

Dept. R,

Chicago 14, Ill.

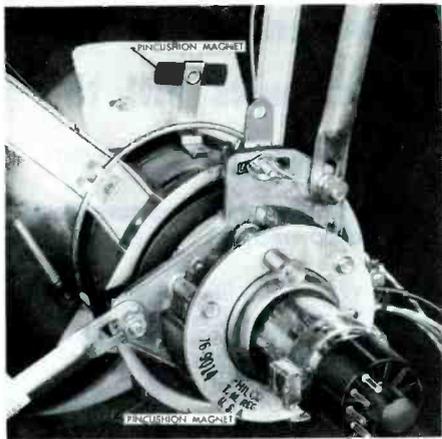


Fig. 6. Illustration Showing Installation of Magnets for Correcting Pincushion Effect.

uits between the horizontal and vertical coils.

Short circuits to the core and between the horizontal and vertical coils are usually characterized by excessive loading on the low-voltage power supply. Often, a shorted yoke will cause the plates of the low voltage rectifier tube to turn red or will cause the tube to fail completely. If the yoke connects to the receiver by a plug-in cable, the trouble may be quickly isolated by simply unplugging the yoke from its socket.

The location of faulty damping components requires that one end of each damping component should be unsoldered and checked with an ohm-meter or capacity checker as required. There are two methods of checking a deflection yoke for shorted turns: (1) substitution with a replacement yoke of known good quality, (2) checking the suspected yoke with one of the flyback and yoke testers such as the RCP Model 123 Flybacker which is manufactured by Radio City Products Company, Inc., Easton, Pa.

To locate an open coil in the vertical windings, it is necessary to disconnect one end of the deflection coil to be checked since the vertical coils are connected across the verti-

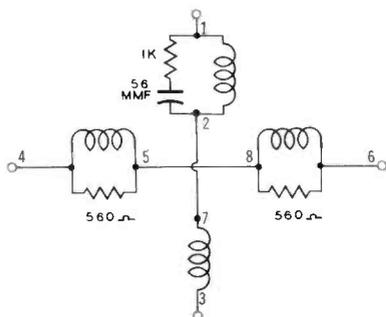


Fig. 7. Schematic of a Typical Deflection Yoke.

cal output transformer. The horizontal coils may be checked without disconnecting one end, provided that the receiver incorporates a coupling capacitor in the return lead from the horizontal coils. The schematic shown in Fig. 7 is representative of a good many of the deflection yokes now in use. The 1,000-ohm resistor in the horizontal-damping network is sometimes omitted.

Installation

Once it has been determined that the deflection yoke is defective, the next problem that arises is the proper installation and setup of the replacement yoke.

Replacement yokes of the different types may be supplied in one of three ways: (1) with the horizontal-damping components across either coil, (2) with the damping network components supplied but not connected, (3) without the damping network components. In order to make sure that the yoke will be installed properly, it should first be determined whether the horizontal-output transformer is of the isolated-secondary or autotransformer type. If the horizontal-output transformer is of the isolated-secondary type, the high side of the secondary winding should be connected to the horizontal coils of the deflection yoke at terminal 1, and the sweep-return lead should come from terminal 3. The damping network in this case should be connected across terminals 1 and 2 in the deflection windings.

If the horizontal-output transformer is of the autotransformer type, the high side of that portion of the autotransformer which serves as a source of deflection voltage should be connected to terminal 3 on the yoke, and the sweep-return lead should come from terminal 1. Again, the damping network should be connected from terminal 3 which is the point of highest AC potential to terminal 7 which is the center junction of the horizontal coils.

By using this procedure, the deflection yoke may be installed with the assurance that the picture will not be reversed in the horizontal plane and with the assurance also that the damping network will be located so that maximum reduction of ringing will be accomplished.

Since the damping resistor across each one of the vertical-deflection coils is the same, it is the usual procedure: (1) to connect the vertical coils temporarily; (2) to reverse the leads to the vertical coils, in case the picture should happen to be upside down; and (3) then to connect the vertical-deflection coils into the circuit permanently.



LOOK...

another chance
for you to sell

an RCA
**BROADBAND
AMPLIFIER**

Garden apartments, motels, small apartment houses, stores, small institutions... these and every new or old building where many television sets operate are your prospects for RCA Antenaplex* Broadband Amplifier sales.

Remember, this is the ideal amplifier for multiple TV distribution systems requiring from 2 to 50 outlets.

Point out to building owners that fees from tenants pay for the system, then add to profits... that the RCA Antenaplex Broadband Amplifier ends dangerous rooftop clutter... that it pulls finest sound and pictures in VHF or UHF, color or black and white... that this is RCA equipment, engineered by the world leader in electronics to give best performance longest.

It's smart to have business like RCA Antenaplex Broadband Amplifiers in the house. Your local RCA parts distributor has the components... you need no heavy inventory. You can plan selling so that installation keeps technicians busy in slack periods... and there's maintenance business in years ahead.

You have lots of RCA Antenaplex Broadband Amplifier customers. See your RCA distributor for parts, then see those prospects for profits!

*"ANTENAPLEX"®



**RADIO CORPORATION
of AMERICA**

ENGINEERING PRODUCTS DIVISION
CAMDEN 2, NEW JERSEY



YOU BUILD

EICO

**KITS
IN ONE
EVENING—
but they
last a lifetime...
and you
save 50%**

**38 Kits and 42 Instruments —
the Industry's most complete
line of MATCHED
TEST INSTRUMENTS**

1/4 - million EICO Instruments are now in use the world over! That's the proof of EICO's leadership in Value.

For latest precision engineering, finest components, smart professional appearance, lifetime performance and rock-bottom economy — see and compare the EICO line at your Jobber before you buy any higher-priced equipment! You'll agree with over 100,000 others that only EICO Kits and Instruments give you the industry's greatest values at lowest cost.

Prices 5% higher on West Coast.



Write NOW for FREE latest Catalog PF 3

EICO
Laboratory Precision at lowest cost

©1954

ELECTRONIC INSTRUMENT CO., Inc.
84 Withers Street, Brooklyn 11, N. Y.

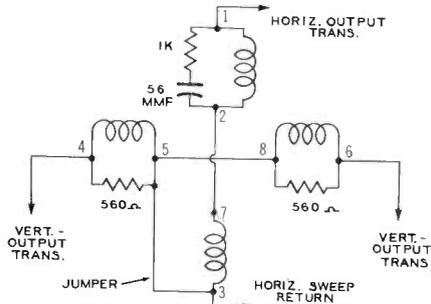


Fig. 8. Schematic of a Yoke in Which Boost Voltage Is Applied to the Vertical-Output Stage by Using Internal Connections in the Yoke.

In some direct-drive horizontal-output systems, high-impedance (30-millihenry) horizontal coils are used in combination with low impedance (3.5-millihenry) vertical coils in the deflection yoke. In this case, it is usually necessary to connect a 270-mmf or other small capacitor from a terminal at the center junction of the vertical coils to the one at the sweep-return end of the horizontal-deflection coils. The presence of this capacitor causes the center junction of the vertical coils to be at AC ground potential for horizontal-sweep frequencies and cancels the ringing which can be caused by inductive coupling between the horizontal and vertical coils.

In some late-model receivers, it has been the practice to apply boost B+ voltage to the vertical-output amplifier. This may be done by connecting the center junction of the vertical-deflection coils to the sweep-return end of the horizontal coils by means of a jumper within the yoke. This connection is shown in Fig. 8. When installing replacement yokes in receivers using this arrangement, always remember to add the jumper; otherwise, there will be no vertical sweep.

After the deflection yoke is properly installed so that the sweep is from left to right and from top to bottom, the yoke should be checked to see that it is as far forward on the neck of the picture tube as possible and that the scanning lines are exactly horizontal.

After replacing a deflection yoke, all the adjustments which are necessary for a proper picture should be made. These adjustment points include: the ion trap; the centering, focus, width, horizontal-linearity, and horizontal-drive devices; and the height and vertical-linearity controls. Careful adjustment of the receiver after any repair work has been done is very important because the customer is apt to be overly critical of the operation of the set after it has been repaired.

CALVIN C. YOUNG, JR.

Get more out of electronics with the Gernsback Library

RADIO-CONTROL HANDBOOK — No. 53

Howard G. McEntee, W2SI, gives you all the practical details (without the theory) on how to build R/C systems and the mechanical components to control model planes, boats, etc. 192 Pages. 175 illustrations. **\$2.25**



THE OSCILLOSCOPE—No. 52



A practical book that tells you how to use the scope to best advantage in all types of servicing. Gives you tips on use and warns about pitfalls to avoid. 192 Pages. Over 100 illustrations. **\$2.25**

\$2.25

TRANSISTORS—THEORY AND PRACTICE—No. 51

Rufus P. Turner explains transistors for the practical man. Gives applications in well-known circuits. Contains guide to characteristics of commercial transistors. 144 Pages. **\$2.00**



\$2.00

TV REPAIR TECHNIQUES—No. 50



Top technician-writers tell you how to recognize and correct quickly the tough servicing problems which stump even the experts. Will help you do a better job faster. 128 Pages. **\$1.50**

\$1.50

RADIO & TV TEST INSTRUMENTS —No. 49

How to build just about every modern TV-radio-audio servicing instrument, plus unique chapters on service bench and carrying case construction. 128 Pages. Over 100 Illustrations. **\$1.50**



\$1.50

See the complete library at your parts distributor's

Gernsback Publications, Inc.

Publishers of RADIO-ELECTRONICS

25 West Broadway

New York, N.Y.

Examining Design Features

(Continued from page 21)

Synchronization.

A composite video signal from the video output is coupled to the triode section of a 6AU8. The video is removed, and the sync pulses are further coupled to the sync clipper which is the triode section of a 6U8. The output from the cathode of this stage is applied to the vertical-sweep section; whereas, the output from the plate of the sync clipper is applied to the horizontal-sweep section.

Vertical Oscillator and Output Amplifier.

The Muntz Chassis 47A4 is unusual in that only one tube, a 25L6GT, is used for both the vertical-oscillator and vertical-output functions. A partial schematic and the waveforms in the circuit are shown in Fig. 4. The explanation of the operation of the circuit can best be made by following the sequence of events that take place in the circuit, beginning with the instant that the vertical sync pulse is applied.

Current is flowing through the tube until the negative sync pulse arrives from the cathode of the sync clipper. The sync pulse is applied to the screen of the 25L6GT and causes the plate current to decrease. The magnetic field which had been built up around the winding AB of transformer T2 suddenly begins to collapse, and a negative voltage is applied to the screen of the tube from winding CD. This voltage acts to decrease the plate current still further, and the action is cumulative until the tube is cut off. The cutoff of current through the tube takes place very rapidly; and immediately thereafter, ringing occurs in the circuits of the tube. A

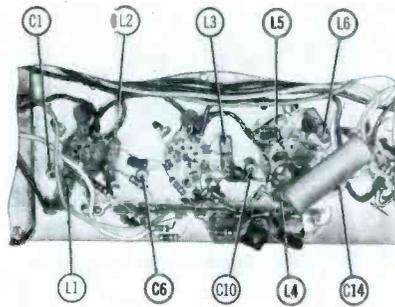


Fig. 3. Underchassis View of Video IF Strip in Muntz Chassis 47A4.

high positive pulse of voltage appears on the plate. This pulse is coupled to the grid of the tube through capacitors C57 and C56, but it is limited in amplitude by the flow of grid current which charges C56 to the polarity shown on the schematic of Fig. 4. Although the plate and control grid of the tube have positive voltages during this half cycle of ringing oscillation, the screen grid is highly negative; consequently, the tube cannot conduct, and ringing continues. The second half cycle of ringing causes a negative pulse on the plate and grid. When the grid voltage reaches the cutoff level at the conclusion of this pulse, the plate and screen are both positive; and the tube begins to conduct, and the next vertical scan begins. After conduction begins, ringing is immediately damped out; and the rate of rise in plate current is controlled by the rate of positive rise in control-grid voltage. The latter, in turn, is controlled by the discharge time of capacitor C56. Plate current flows until the next sync pulse arrives at the screen grid, and the sync pulse starts the cycle once again.

The vertical-linearity control R6 governs the amount of charge which is placed on C56 during retrace, and the vertical-hold control R5 fixes

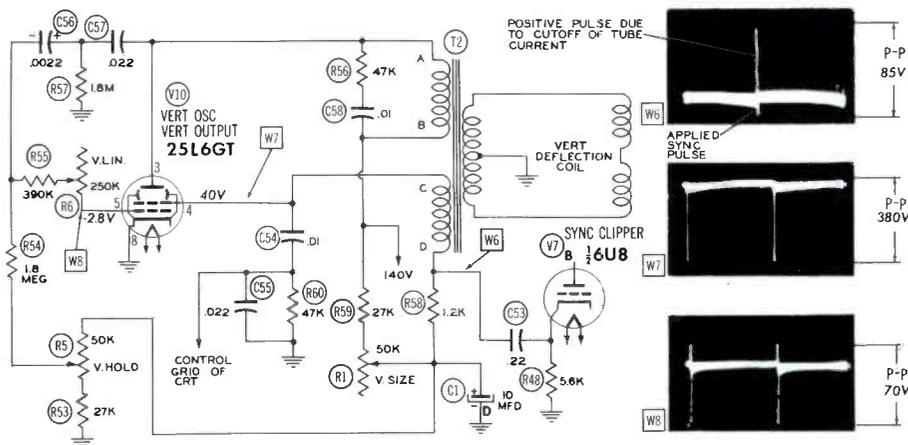


Fig. 4. Schematic Diagram of Vertical Oscillator and Output Circuit in Muntz Chassis 47A4.

*Just a touch
of Your Finger*

**OPENS and CLOSSES
YOUR GARAGE DOOR**



with the

**Perma-Power[®] ELECTRONIC
Remote Control
Garage Door Opener**



Press A Button
On The Dash

**OPEN AND CLOSE FROM
YOUR OWN CAR**

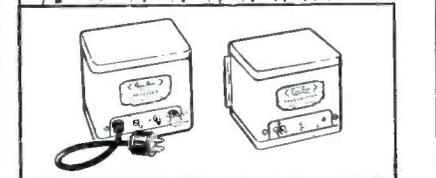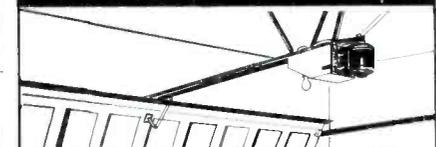

**Everyone can afford this
modern convenience!**

- * It's really simple to install . . . one man can do it easily!
- * Takes just an afternoon with common hand tools; no soldering.
- * Complete instructions assure professional-type installation.

Available from electronic parts distributors
Illustrated literature upon request

Perma-Power[®] COMPANY 4727 N. DAMEN AVE.
CHICAGO 25, ILL.
Manufacturers of electronic equipment since 1928

the bias on the control grid. This bias level influences the frequency of the oscillator. Vertical size is determined by the setting of R1 in the screen circuit of the tube.

Horizontal Sweep.

Control of the horizontal sweeping rate is provided by a 12AU7 in a pulse-width type of AFC system. A 25BQ6GA supplies the output power for the sweep and for the high voltage. The high-voltage rectifier is a 1X2B, and damping action is provided by a 25AX4GT.

Power Supply.

An autotransformer is used to raise the line voltage slightly. A selenium rectifier provides the direct current, and a filter choke smooths this current. The output from this selenium rectifier is 140 volts DC, and this is reduced to approximately 125 volts by the time it reaches the plates of the tubes. Since this is a rather low plate voltage, it should be noted that any change in the selenium rectifier will have an effect greater than usual upon the performance of the set.



Fig. 5. Philco Electrostatic Speaker.

PHILCO ELECTROSTATIC SPEAKER

The development of high-fidelity sound reproduction has resulted in a number of different arrangements for reproducing the higher audio fre-

quencies. Philco has reintroduced the electrostatic speaker for this function. The original electrostatic speakers were used quite a few years ago, but they were not widely used nor perfected to a high degree because of the lack of suitable dielectric materials.

The Philco Model 1758 radio-phonograph combination uses the electrostatic speaker shown in Fig. 5 for reproducing the frequencies between 7,000 and 20,000 cycles. Its construction is similar to that of a capacitor in that each has two plates separated by a dielectric. In the speaker, one plate is fixed in position and the other is movable to a very slight degree. The movable plate has a large area in order to move a sufficient quantity of air. This plate consists of a layer of gold deposited on a polyester plastic film which serves as the dielectric.

The layer of gold and the plastic film have practically no mass so that only a small electrostatic force is necessary to move them. The force is provided by an AC voltage which is derived from the plate of one of the output tubes, as shown in the schematic of Fig. 6. The AC voltage is superimposed upon a DC voltage, and the strength of the electrostatic field

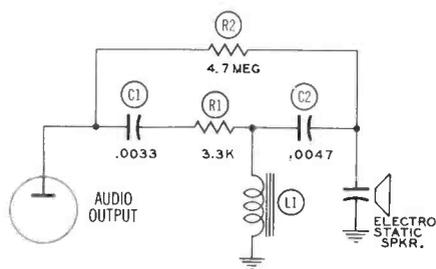


Fig. 6. Schematic diagram of Circuit Used With Electrostatic Speaker in Philco Receiver.

SUPERIOR'S NEW MODEL TV-40

C.R.T. TUBE TESTER



- ★ A complete picture tube tester for little more than the price of a "make-shift" adapter!!
- ★ Tests all magnetically deflected tubes . . . in the set . . . out of the set . . . in the carton!!

The Kinescope Tube (TV Picture Tube) compared to the standard receiving tube is a very complicated component. The complexity of its make-up makes it impractical to employ the same circuit used to test standard receiving tubes. On the other hand, the advantage of being able to use one socket for all C.R.T. tubes, and the fact that all such tubes use the same filament Voltage, has enabled us to design this relatively simple, yet extremely efficient tester.

EASY TO USE:

Simply insert line cord into any 110 volt A.C. outlet, then attach tester socket to tube base (Ion trap need not be on tube). Throw switch up for quality test . . . read direct on Good-Bad scale. Throw switch down for all leakage tests.

SPECIFICATIONS:

- Tests all magnetically deflected picture tubes from 7 inch to 30 inch types
- Tests for quality by the well established emission method. All readings on "Good-Bad" scale.
- Tests for inter-element shorts and leakages up to 5 megohms.
- Test for open elements.

\$15⁸⁵
NET

Model TV-40 C.R.T. Tube Tester comes absolutely complete — nothing else to buy. Housed in round, cornered, molded bakelite case.



"He goes into such ecstasies since we're using JENSEN NEEDLES, there's no holding him."



Write Dept. PF-3 for Catalog

SUPERIOR INSTRUMENTS CO.
2435 White Plains Road New York 67, N. Y.

**AT YOUR
RADIO PARTS
JOBBER**

ZENITH MODEL R512R



Fig. 7. Zenith Model R512R Push-Button Radio.

between the two plates varies in direct proportion to the audio modulation. The movable plate or diaphragm follows the variations in electrostatic force and reproduces the audio signal.

The Zenith Model R512R, a photograph of which is shown in Fig. 7, is an AC-DC portable that utilizes push-button tuning to cover the broadcast band from 540 to 1700 kc. With the exception of the automatic push-button controls, it employs a conventional circuit composed of a 12BE6 converter, a 12BA6 IF amplifier, a 12AT6 detector and audio amplifier, a 50C5 power amplifier, and a 35W4 rectifier.

The automatic-tuning assembly is shown in the schematic in Fig. 8 and is composed of the oscillator coils L8, L9, L10, L11, L12, and oscillator shunt coil L7, along with the antenna

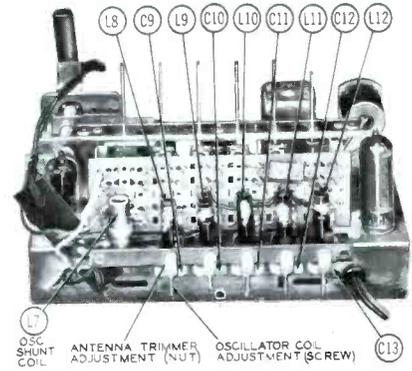


Fig. 9. Coils and Capacitors in Tuning Assembly of Zenith Model R512R.

trimmer capacitors C9, C10, C11, C12, and C13. The arrangement of these coils and capacitors on the chassis can be seen in the photograph shown in Fig. 9. For ease of identification, the coils are coded with colored dots. The dot on L8 (750 to 1700 kc) is white, on L9 (700 to 1500 kc) is blue, on L10 (650 to 1400 kc) is green, on L11 (600 to 1300 kc) is red, and that on L12 (540 to 1200 kc) is yellow. For push-button operation, a tuning-bar arrangement places the desired coil for the selected station in parallel with the oscillator coil L2. At the same time, the correct trimmer capacitor is placed in parallel with the antenna loop.

To adjust a particular automatic push button to the frequency of a specific station, first rotate the oscillator screw adjustment to the desired station, then rotate the antenna-trimmer adjustment for maximum sensitivity.

William E. Burke and James M. Foy

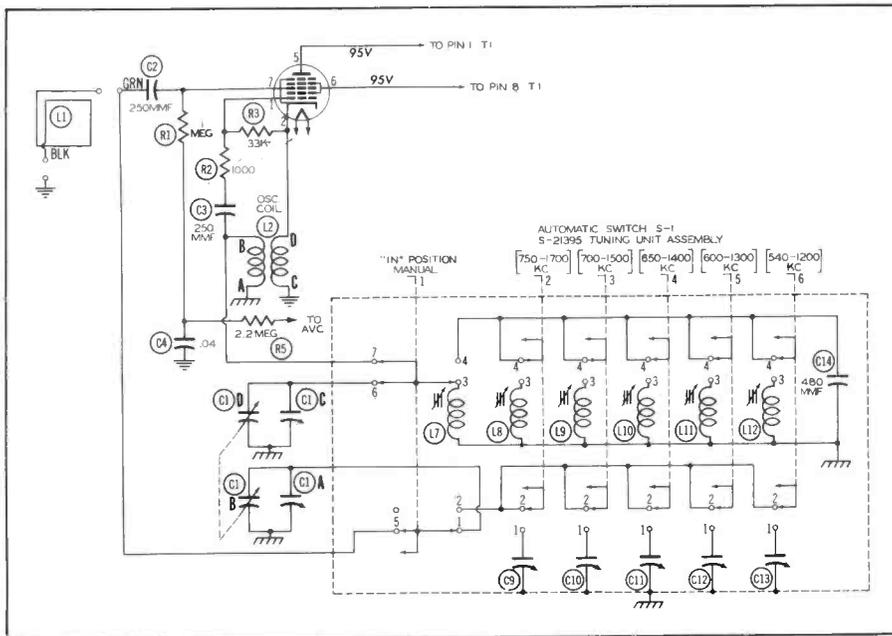


Fig. 8. Tuning Circuits in Zenith Model R512R.

Burton Brown Advertising



LIST PRICE \$19.95

PLAY YOUR TRUMP



Regency

...with high volume low-cost conversion using Regency RC-53 all channel UHF converter—the lowest price converter available which provides conversion to all UHF channels from a wide selection of VHF channels. Designed as a primary area converter, tests prove excellent performance in 80% of UHF locations.

Regency, world's leading manufacturer of TV accessories including VHF boosters, FM boosters, voltage boosters, UHF converters, remote TV control, high pass filters and a complete line of high fidelity equipment.

REGENCY DIVISION, I.D.E.A., INC.,
INDIANAPOLIS 26, INDIANA

NEW Columbia PACKAGING

- For easier selling
- For quicker inventory
- To save time and money



VHF-UHF FOAM POLYETHYLENE TV TRANSMISSION LINE

100 ft. of high quality VHF-UHF cable in an attractive multi-colored box for easy handling. Takes little space and is quickly identified. Installs as easy as flat T/V line.



NEW 300 OHM TELEVISION LINE PACKAGE

100 ft. of wire in printed, clear polyethylene package with the television line neatly coiled, banded, identified. Price lower than comparable packages.

EXCLUSIVE!

NEW "PERMALINE" 300 OHM POLYETHYLENE TV TRANSMISSION LINE

- Will outlast any 300 ohm line in use today
- Far superior . . . resists practically anything
- **NO DETERIORATION**

Write for your FREE SAMPLE TODAY!

"Columbia" products are available at recognized distributors.

Columbia
WIRE & SUPPLY CO.

2850 Irving Park Road, Chicago 18, Ill.

"America's Most Complete Wire Line"

Radio Alignment

(Continued from page 25)

Another tracking feature is the use of slotted rotor plates in the tuning capacitor. The terms "slotted

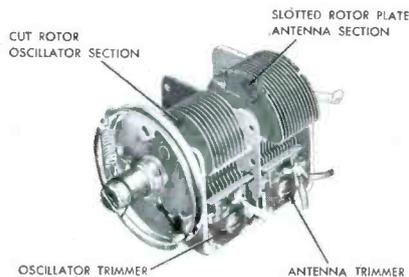


Fig. 2. Tuning Capacitor of a Small Radio Receiver. A Cut Rotor for the Oscillator Section and Slotted Plates for Antenna Tracking Adjustments Are Shown.

rotor" and "cut rotor" should not be confused. Both of these features are illustrated in Fig. 2. The cut rotor has already been mentioned and refers to rotor plates smaller than those used in the RF or antenna section of the tuning capacitor. The term slotted rotor describes the condition in which the outside plates of a rotor section are slotted to permit easy bending of portions of these plates. In this manner, the plates may be adjusted to give more or less capacity at certain parts of the tuning range.

General Alignment Procedure

Alignment of small radios usually assumes a more or less set procedure. The alignment technician attaches some measuring device to the receiver to indicate the relative strength of the detector output. This device may be an output meter or an AC meter across the voice coil. Some technicians like to use an oscilloscope as an AC indicator for the added sensitivity it affords, but it has a disadvantage in that difficulty is experienced in judging the point of maximum indication for small changes in amplitude.

A VTVM across the AVC line is favored by some as an indicating device; however, using a VTVM in this fashion also has its advantages and disadvantages. Among the advantages are: (1) no modulation is required for an indication and (2) the volume control may be turned down to eliminate the distraction caused by noise from the loudspeaker.

If the receiver employs delayed AVC, there is a disadvantage in using the VTVM across the AVC line. The input signal must be increased somewhat in order to overcome the delay in the AVC action; consequently, the



TUBE TESTER #625
KIT \$34.95 Wired \$49.95



More Servicemen buy EICO TUBE TESTERS — in KIT and wired form — than any others sold through distributors. Why? Because EICO gives you the MOST value at LOW-EST cost.

- Test all conventional & TV tubes and pilot lights.
- 10 individual lever-type element switches.
- Illuminated anti-backlash rollchart kept up-to-date by EICO's Engineering Dept.
- 4 1/2" meter, 3-color "Good-Bad" scale.
- Line-adjust control. Blank socket for new tubes. Protective overload bulb.

In stock at your local jobber. Write for free Catalog, P.T.-3 Prices 5% higher on West Coast.

ELECTRONIC INSTRUMENT CO., INC.
84 Withers Street • Brooklyn 11, N. Y.



QUIETROLE
Reg. U. S. Pat. Off.
The ORIGINAL
NON-INFLAMMABLE
NON-CONDUCTIVE
LUBRICANT CLEANER



CONTROLS & SWITCHES like new by the BASKETFUL for only a few PENNIES . . . that's what QUIETROLE can do for you, and only QUIETROLE will give that long lasting smooth, quiet operation . . . even new controls last longer and operate quieter when treated with QUIETROLE . . . the original and most reliable product of its kind.

THE CHOICE OF BETTER SERVICEMEN "EVERYWHERE"
Supplied in 2, 4, and 8 oz. sizes. Ask for it at your distributor.

manufactured by

**QUIETROLE
COMPANY**

Spartanburg, South Carolina



alignment will not be made at the point of most sensitive receiver operation. Another disadvantage in using the VTVM in this way is that sometimes the AVC line is not so readily accessible as the voice-coil terminals on the speaker. In other instances, however, the AVC line may be returned to the rotor plates of the antenna-tuning capacitor or to one terminal of the loop antenna. Either of these test points can be reached easily.

When using an output meter across the voice coil of the speaker, the volume control should be fully advanced and only enough signal input to obtain an indication should be used. This will avoid driving the AVC into operation, and a maximum sensitivity of response to any adjustment which might be made will be assured. It is common practice to start adjustments at the last IF stage and work toward the front. The IF signal used for alignment is commonly fed to the converter tube at the same point that receives the station signal from the RF stage or from the antenna of the receiver. It is good practice to use a blocking capacitor with the signal generator and to use an isolation transformer for supplying power to the receiver.

The oscillator adjustment can be made next with the alignment signal applied at the same point as that just mentioned for the IF alignment. Often, all alignment signals are introduced at the antenna input of small sets; and this fact simplifies the alignment procedure considerably.

The alignment instructions in Chart I give a convenient method of coupling the signal generator to the loop without a direct connection. This method ensures a minimum of detuning in the receiver circuits. The trimmer capacitor for the oscillator is adjusted with the receiver tuned to the high-frequency end of the band. This is the normal thing to do because the effect of the trimmer is greater at the high-frequency end of the band than at the low-frequency end. At the high end, the trimmer capacitance is a large percentage of the total capacitance which consists of trimmer capacitance, oscillator-tuning capacitance, and the distributed capacitances of coils and other circuit components. At the low-frequency end of the range, trimmer capacitances and distributed capacitances contribute less to the total tuning effect; therefore, any tracking adjustments at the low end of the range are usually made by altering the amount of inductance. When provision for changing the amount of inductance is not made, bending of the slotted rotor plates may compensate for

tracking deficiencies at either end or at the middle of the range.

After the adjustment of the oscillator, adjustment of the antenna trimmer is made for best tracking at one of the higher frequencies. Common choices of the designers are around 1400 kc or 1500 kc. The setting of the antenna trimmer adjusts the receiver for maximum sensitivity at the chosen frequency. Then it is customary to check the tracking near the 600-kc tuning point and to make any slight adjustments that will increase the sensitivity at that point. Any adjustment made at this lower frequency will affect the tracking at the high end; therefore, alternate adjustments for maximum sensitivity are recommended first at the high end then at the low end until no further improvement can be made. These adjustments should end with the one made at the higher frequency, because a slight adjustment of capacity has a greater effect at the high-frequency end.

With receivers having an RF stage, tracking adjustments for this stage usually follow the oscillator adjustment and are made in a manner similar to the antenna adjustment just described. Both antenna and RF tracking adjustments are usually performed at the same points on the tuning range.

FM and Multiple-Band AM Receivers

Much of the alignment procedure mentioned also applies to FM receivers and to multiple-band AM receivers. Addition of other bands to an AM receiver increases the number of necessary tracking adjustments but does not affect the IF alignment. Alignment of the RF sections of an FM receiver resembles that of an AM receiver in principle. Alignment of the IF stages can also be similar, but the FM detector requires its own individual treatment.

Two methods of alignment of the IF stages of an FM receiver may be used, or sometimes a combination of both may be used. One method is the use of an RF signal generator and a VTVM, and the other is the use of an RF sweep generator and an oscilloscope. The latter is called a visual-alignment procedure and is especially suited to FM detector alignment and to alignment of wide-band IF systems. It is also used for aligning AM receivers having wide-band IF stages. The sweep generator furnishes a signal which varies in frequency over a certain range on each side of a center frequency which is adjusted to equal the intermediate frequency. This variation occurs at an audio rate which may be 60, 120, or 400 cycles

per second. Thus, all the frequencies to which the IF stages ordinarily respond are covered repeatedly at the sweep rate; and the response of the tuned stages to these frequencies can be viewed on the oscilloscope.

Some form of detector is required in order to view the IF response of the FM receiver, because the intermediate frequency of most of these receivers is above the response range of general-purpose oscilloscopes. The necessary detector action may be obtained at the grid of the last limiter stage or across the FM detector itself.

Fig. 3 shows the response curves obtained during an FM alignment. The curve of Fig. 3A may be obtained at either the limiter grid or across the detector load resistor. In Fig. 3B, the output of the detector as applied to the audio amplifier is shown. This waveform is obtained when the sweep rates of the generator and the scope are the same. If the scope rate is twice that of the generator, the butterfly waveform of Fig. 3C is obtained.

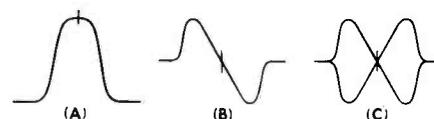


Fig. 3. Alignment Response Curves Obtained During the Alignment of FM Receivers. (A) At the Grid Load Resistor in the Limiter Stage. (B) At the Input to the Audio Stages with Scope Sweep Rate Equal to Generator Sweep Rate. (C) At the Input to the Audio Stages with Scope Sweep Rate Equal to Twice the Generator Sweep Rate.

The waveforms mentioned are really graphs traced by the oscilloscope, and they show the relative amplitude of the response of the circuit which is connected between the generator output and the scope input. The response is shown for all the frequencies covered by the sweeping action of the generator. These waveforms provide a means of checking the adjustments of the tuned circuits involved.


The use of markers enables the technician to pinpoint the response at any frequency on the response curve. The markers shown in Figs. 3A, 3B, and 3C indicate the intermediate frequency of the receiver. Typical alignment adjustments are made: (1) with the IF slugs in order to obtain at the last limiter stage the response of Fig. 3A, (2) with the slug in the primary of the discriminator transformer or in the primary of the ratio-detector transformer in order to obtain across the detector load the

Fen-tone Hi-Fi

MOTEK

TAPE TRANSPORT MECHANISM

(Without Amplifier)

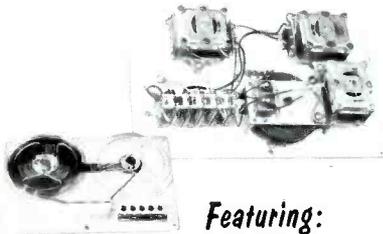

Featuring:

- ★ Three individual motors.
- ★ Speed: 7½ I.P.S., dual tracks.
- ★ Hi-Fi record/playback and erase heads.
- ★ Push button control.
- ★ Frequency response better than 50—10,000 C.P.S.
- ★ WOW and FLUTTER less than .3%.
- ★ Accommodates 1200' reels (7").

Ask for descriptive literature

See our "packaged" Audio System at your Hi-Fi Center featuring MOTEK Deck, Amplifier and PE REX Changer, only \$173.90 complete.

FENTON COMPANY

15 Moore Street • N. Y. 4, N. Y.
Tel. 80Wing Green 9-3445

FLY-BACK INTERVAL & INDUCTANCE CHECKER

AT A GLANCE!



**NO
DISCONNECTING
NECESSARY**

EXCLUSIVE

SECO

**FLY-BACK
INTERVAL
CHECKER**

MAKE THIS 3 WAY CHECK:

1. Fly-back interval (Exclusive Feature!)
2. Checks flyback transformers individually.
3. Checks yokes individually.

See your Jobber or write for literature and prices.

SECO MFG. CO. 5015 PENN. AVE. S.
MINNEAPOLIS, MINN.

response of Fig. 3A, and (3) with the slug in the secondary of either the discriminator or ratio detector transformer in order to obtain at the input to the audio stages the waveforms of either Fig. 3B or 3C.

Instead of being obtained by these curves, the same sort of information — that is, the amplitude and symmetry of response, the straightness of the linear portion of the curve, and the crossover point — could be obtained by using a VTVM and an RF signal generator; but this would involve much time and many VTVM readings.

Special Cases

Alignment of any particular receiver should follow the alignment instructions for that receiver very closely. In special cases, however, the technician may be justified in taking some liberties in order to obtain a compromise which seems best to him under the circumstances.

In some locations, a strong local station may broadcast on a frequency which is the second harmonic of the intermediate frequency of the receiver; and in that case, one may hear an interfering squeal when listening to that station. One example would be that of a station that is broadcasting on 910 kc and is being received by a radio having an intermediate frequency of 455 kc. By shifting the intermediate frequency slightly from 455 kc, the technician should be able to reduce this type of interference. If the shift is too great, he may experience trouble in making the receiver track across the band.

Another type of interference similar to the one just mentioned is the reception of image frequencies. Such interference results from the fact that two different frequencies may beat with the local oscillator to produce the intermediate frequency. Assume that a receiver is tuned to a station operating on 600 kc. The local oscillator is tuned to 1055 kc, and the 455-kc intermediate frequency is obtained as the difference beat. If another signal of 1510-kc frequency should beat with the oscillator, this signal will also result in a 455-kc difference and will interfere with the first signal. This sometimes happens when the second signal is very strong. The tuned circuit of the antenna will greatly reduce the response of the receiver at 1510 kc; but if the signal is very strong, some of it may reach the converter to cause the interference just mentioned. An RF stage preceding the converter will do much to reduce this type of interference. The 1510-kc frequency is called an "image frequency" of the 600-kc

frequency of the desired station because both are separated from the oscillator frequency by an equal amount, one above and the other below.

A choice of a high intermediate frequency reduces the number of image frequencies that can occur over the broadcast range. If image frequencies are troublesome, the technician may try to eliminate the interference by shifting the intermediate frequency slightly.

Another liberty that may be taken, if there is considerable mis-tracking and if it defies correction, is to adjust the tracking to favor the stations of the owner's choice or to favor a weak station in preference to a strong one.

Little has been said in this article concerning alignment of auto radios; therefore, it might be well to call attention to at least one feature. Alignment of an auto radio is usually not complete until the radio has been replaced in the automobile and the antenna trimmer has been adjusted. These steps in service literature usually read somewhat as follows: "Replace the radio in the car, extend the antenna fully, and adjust the antenna trimmer for maximum sensitivity on a weak signal near 1400 kc." This procedure is necessary because the capacity of the car antenna affects the tracking at the high frequencies and because the capacity may be different with each individual antenna.

All the aspects of alignment have not been covered in the foregoing discussion, but it can be seen that there are many fine points to radio alignment and that it requires more than just a "lick and a promise." The conscientious technician has plenty of opportunity to exercise his skill on the "lowly" radio, and the result will be a job that he can view with pride.

PAUL C. SMITH

ADDENDUM

The WALSCO PC-9 TV chassis distributed by Walsco Electronics Corporation of Los Angeles and Chicago is identical to the CALTECH chassis T1 described in the article "Examining Design Features" in the January 1955 issue of the PF REPORTER. The information given therein is therefore also applicable to the WALSCO PC-9.

1C. B & K (B & K Manufacturing Co.)

Bulletin No. 102-P tells how servicemen can make money and retain customers with new low-cost, portable CRT Cathode Rejuvenator. *See advertisement page 66.*

2C. CHICAGO STANDARD (Chicago Standard Transformer Corp.)

TV Library. Auto-Radio Transformer Replacement Guide. *See advertisement page 8.*

3C. CLEAR BEAM (Clear Beam TV Antenna Co.)

Descriptive Literature on "Big 3" All Bank Fringe Antennas. *See advertisement page 71.*

4C. DUMONT (Allen B. DuMont Laboratories, Inc.)

Cathode-Ray Tube Data Chart. (1955 Edition) Complete technical data on all TV picture tubes. Ideal for replacement information. *See advertisement page 20.*

5C. EICO (Electronics Instrument Co., Inc.)

1955 12-page EICO Catalog describing the complete EICO line of 38 Kits and 42 Wired Instruments. Tells how to save 50% on your test equipment. *See advertisement pages 78, 82.*

6C. ERIE (Erie Resistor Corp.)

Bulletin on Erie Suppressors. *See advertisement page 48.*

7C. FENTON (Fenton Company)

Literature on Vortexion tape recorder; Motek transport mechanism; Rex Record Changer; Adaphone; Pillowphone; Miniature Earsets; TUF-GUY guy wire; Twistube; Fentube-Air-spaced. *See advertisement page 84.*

8C. IRC (International Resistance Company)

Form S-052—New Power Resistors. *See advertisement 2nd cover.*

9C. JACKSON (Jackson Electrical Instrument Co.)

Complete Line Folder—4 pages of complete information and specifications on all Jackson "Service-Engineered" Test Equipment. *See advertisement pages 56, 57.*

10C. JERRCLD (Jerrold Electronics Corp.)

Catalog, Jerrold Multi-Outlet System. *See advertisement page 76.*

11C. JFD (JFD Manufacturing Co., Inc.)

"Roto-King" Rotator Brochure and "Star-Helix" TV Antenna Brochure. *See advertisement insert.*

12C. MACMILLAN (The Macmillan Company)

New 1955 Catalog of Technical & Business Books on TV, Radio and Electronics. *See advertisement page 74.*

13C. MALLORY (P. R. Mallory & Co., Inc.)

FP and WP Electrolytic Capacitor Replacements. *See advertisement page 14.*

14C. OHMITE (Ohmite Manufacturing Company)

Bulletin No. 146—Brief description of Ohmite Fuse Resistor, Stock No. FR-7.5. *See advertisement page 59.*

15C. OXFORD (Oxford Electric Corp.)

Speaker Catalog. *See advertisement page 70.*

16C. PHAOSTRON (Phaostron Company)

Information on the New Model "555" pocket size Multimeter. *See advertisement page 38.*

17C. SAMS (Howard W. Sams & Co., Inc.)

Spring 1955 Book List. *See advertisement page 64.*

18C. SHURE (Shure Brothers, Inc.)

General Catalog No. 55. Microphones, phono cartridges and magnetic recording heads. *See advertisement page 73.*

19C. SPRAGUE (Sprague Products Company)

M-711 Descriptive circular on Ceramikit cabinet assortments of disc ceramic capacitors built like miniature letter files. *See advertisement page 2.*

20C. TRIAD (Triad Transformer Corp.)

Catalog TV-55, Replacement TV Guide, listing Triad Correct Replacement Television Transformers. *See advertisement page 60.*

21C. TRIO (Trio Manufacturing Co.)

Four color brochure on New Trio "Aristocrat" rotator control units. Ask for Form No. 101. *See advertisement page 42.*

22C. TRIPLETT (Triplett Electrical Instrument Co.)

Test Equipment Catalog Featuring Model 631 Volt-Ohm-Milliammeter and Vacuumtube Voltmeter. *See advertisement page 28.*

23C. TUNG-SOL (Tung-Sol Electric, Inc.)

Broadside, Form T-1, showing all sales promotion and service aids for Tube Distributors and Service Dealers. *See advertisement pages 46, 47.*

24C. TURNER (The Turner Company)

Bulletin No. 966 describing Turner Model 57 Slender Dynamic Microphone. *See advertisement page 50.*

25C. UCP (United Catalog Publishers, Inc.)

Descriptive literature on THE MASTER—the official buying guide of the Radio-TV-Electronic parts industry, with list of distributors. *See advertisement page 66.*

26C. XCELITE (Xcelite, Inc.)

Revised catalogs and supplementary literature on complete lines of screwdrivers, nut drivers, combination kits and pliers. *See advertisement page 72.*

27C. BOGEN (David Bogen Co., Inc.)

Complete New Public Address System Catalog. (NOTE: Bogen ad appeared in January PF REPORTER. Listing was omitted through error.)

JUST CHECK AND MAIL THE CARD

1. Circle or check the corresponding numbers of literature you want to receive.
2. Fill in your complete name and address.
3. Detach and mail self-addressed card. No postage necessary.

Please send me the following literature checked below:

1C	2C	3C	4C	5C	6C	7C	8C	9C	10C	11C	12C	13C	
14C	15C	16C	17C	18C	19C	20C	21C	22C	23C	24C	25C	26C	27C

Print plainly or type below

Name _____
 Firm _____
 Firm Address _____
 City _____ Zone _____ State _____

**OFFER GOOD
ONLY UNTIL
MAY 1, 1955**

Has your address changed since you last wrote us No Yes

To guarantee receipt of literature please check one of boxes below:

- Independent Serviceman Dealer with Service Shop Student
 Other (Please explain) _____

COLOR TV TRAINING SERIES

QUESTIONS ON PART X

James W. Adams



REPORTER

INDEX TO ADVERTISERS
March, 1955

Part X of the Color TV Training Series, appearing in this issue, should be studied prior to reading the following questions.

The questions are presented to give the reader an opportunity to test himself on the color-television material in this issue.

1. Into what two categories may three-beam color picture tubes be divided?
2. With respect to the electron-gun assembly used in the later type tube, how are the guns positioned to aid in obtaining static convergence of the beams at the shadow mask?
3. What advantage with respect to convergence is gained by using a curved instead of a flat mask and screen?
4. What auxiliary components used with a tube employing the magnetic principle can be adjusted to obtain optimum color purity?
5. What auxiliary components are used to obtain beam convergence at all points on the shadow mask of this tube?
6. The color-purity magnet directs the red beam so that it will converge with the blue and green beams. True or false?
7. What is the purpose of the lateral-correction magnet?
8. What special precautions are taken with respect to the deflection yoke used with a tube employing the magnetic principle?
9. What is the nature of the voltages applied to the coils of the convergence electromagnets that are used with a tube of this type?
10. Where do these voltages originate?

C. P. O. & V. M. R.

Advertiser	Page No.
American Phenolic Corp.	52
American Television & Radio Co.	62
B & K Manufacturing Co.	66
Belden Manufacturing Co.	44
Bussmann Manufacturing Co.	4
Chicago Standard Trans. Corp.	8
Clarostat Mfg. Co., Inc.	12
Clear Beam Antenna Corp.	71
Columbia Wire & Supply Co.	82
Cornell-Dubilier Electric Corp.	69
DuMont Labs., Inc., Allen B.	20
Electronic Instrument Co., Inc. (EICO)	78, 82
Erie Resistor Corp.	48
Fenton Co.	84
General Cement Mfg. Co.	26
Granco Products, Inc.	36
Hickok Electrical Instr. Co., The	6
International Rectifier Corp.	55
International Resistance Co.	2nd Cover
Jackson Electrical Instr. Co.	56, 57
Jensen Industries, Inc.	80
Jerrold Electronics Corp.	76
JFD Manufacturing Co.	Insert
Littelfuse, Inc.	4th Cover
Macmillan Co., The	74
Mallory & Co., Inc., P. R.	14
Ohmite Mfg. Co.	59
Oxford Electric Corp.	70
Perma-Power Co.	79
Phaostron Co.	38
Planet Sales Corp.	72
Precision Apparatus Co.	24
Pyramid Electric Co.	32
Quietrole Co.	82
Radiart Corp. - Cornell-Dubilier Electric Corp.	1
Radio Corp of America	18, 58, 77, 3rd Cover
Radio Electronics	78
Radion Corp.	74, 76
Ram Electronics Sales Co.	54
Raytheon Mfg. Co.	10
Regency Div., I.D.E.A.	81
Sams & Co., Inc., Howard W.	60, 86
Sangamo Electric Co.	34
Seco Manufacturing Co.	84
Shure Bros., Inc.	73
South River Metal Products Co.	40
Sprague Products Co.	2
Standard Coil Products Co., Inc.	22
Superior Instruments Co.	80
Sylvania Electric Products Inc.	16
Tarzian, Inc., Sarkes	65
Triad Transformer Corp.	64
Trilo Manufacturing Co.	42
Triplett Electrical Instrument Co.	28
Tung-Sol Electric Inc.	46, 47
Turner Co.	50
United Catalog Pubs., Inc.	66
Ward Products Corp.	30
Weller Corp.	68
Xcelite, Inc.	72

FIRST CLASS
PERMIT No. 1076
(Sec. 34.9, P. L. & R.)
Indianapolis, Ind.

BUSINESS REPLY CARD

No Postage Stamp Necessary If Mailed in the United States

3¢ POSTAGE WILL BE PAID BY

PF REPORTER

Reader's Literature Service Dept.

2201 EAST 46TH STREET

INDIANAPOLIS 5, IND.



While every precaution is taken to insure accuracy, we cannot guarantee against the possibility of an occasional change or omission in the preparation of the REPORTER.

Cumulative Index

No. 49
MARCH-APRIL 1955

COVERING PHOTOFAC T FOLDER SETS 1 THRU 270

FIND THE FOLDER SET
YOU NEED AND GET
IT FROM YOUR
PHOTOFAC DISTRIBUTOR

THIS INDEX IS
YOUR ANSWER TO
SERVICE DATA
REQUIREMENTS

THIS INDEX CURRENT ONLY UNTIL MAY 15th, 1955

here's what makes **PHOTOFACT** the World's Best TV-RADIO SERVICE DATA

PHOTOFACT Service Data is the *only* service information based upon first-hand examination of the actual production-run receivers and equipment. It is authentic, uniform service data, based on actual study and analysis by service engineers in the Howard W. Sams' Laboratories. PHOTOFACT is the *only data* prepared from the practical point of view of the Service Technician.


Thousands of Service Technicians use PHOTOFACT daily for time-saving, profit-boosting service operations. If you've never used PHOTOFACT, you've never realized your full earning power. So get the proof for yourself. Try PHOTOFACT—use it on any job. Get the Folder Sets you need for any of the 17,000 TV and radio receivers, changers, recorders and amplifiers covered in PHOTOFACT. Once you use this great service, we know you'll want the complete PHOTOFACT Library.

32 Great Features Exclusive in PHOTOFACT...To Help You Earn More Daily


FULL SCHEMATIC COVERAGE

1. Famous "Standard Notation" uniform symbols are used in every schematic.
2. The same standard, uniform layout is used for each schematic.
3. Diagrams are clear, large, extremely easy to read.
4. Wave forms are shown right on the TV schematics for quick analysis by 'scope. 
5. Voltages appear on the schematics for speedy voltage analysis. 
6. Transformer lead color-coding is indicated on the schematic.
7. Transformer winding resistances appear on the schematic.
8. Schematics are keyed to photographs and parts lists.

FULL PHOTOGRAPHIC COVERAGE

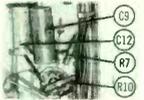9. Exclusive photo coverage of all chassis views is provided for each receiver. 
10. All parts are numbered and keyed to the schematic and parts lists.
11. Photo coverage provides quicker parts identifications and location.
12. Photo coverage helps identify burned-out or missing parts.

ALIGNMENT INSTRUCTIONS

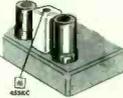
13. Complete, detailed alignment data is standard and uniformly presented in all Folders.
14. Alignment frequencies are shown on radio photos adjacent to adjustment number—all alignment adjustments are keyed to schematic and photos. 

TUBE PLACEMENT CHARTS

15. Top and bottom views are shown. Top view is positioned as chassis would be viewed from back of cabinet.
16. Blank pin or locating key on each tube is shown on placement chart. 
17. Tube charts include fuse location for quick service reference.

TUBE FAILURE CHECK CHARTS

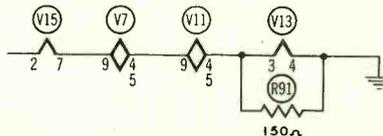18. Shows common trouble symptoms and indicates tubes generally responsible for such troubles.
19. Series filament strings are schematically presented for quick reference.



COMPLETE PARTS LISTS

20. A complete and detailed parts list is given for each receiver.
21. Proper replacement parts are listed, together with installation notes where required.
22. All parts are keyed to the photos and schematics for quick reference.

FIELD SERVICE NOTES

23. Each Folder includes time-saving tips for servicing in the customer's home.
24. Valuable hints are given for quick access to pertinent adjustments.
25. Includes tips on safety glass removal and cleaning.

TROUBLE-SHOOTING AIDS

26. Includes advice for localizing commonly recurring troubles.
27. Gives useful description of any new or unusual circuits employed in the receiver.
28. Includes aids, hints and advice for each specific chassis.

OUTSTANDING GENERAL FEATURES

29. Each and every PHOTOFACT Folder, regardless of receiver manufacturer, is presented in a standard, uniform layout.
30. PHOTOFACT, is a *current* service—you don't have to wait a year or longer for the service data you need. PHOTOFACT keeps right up with receiver production.
31. PHOTOFACT gives you complete coverage in both TV and Radio—to serve every Technician.
32. PHOTOFACT maintains an inquiry service bureau for the benefit of its Service Technician users.

**ONLY \$25 DOWN PUTS THE COMPLETE
PHOTOFACT SERVICE DATA LIBRARY IN YOUR SHOP**

ask your PHOTOFACT Distributor for details, or write us...

HOWARD W. SAMs & CO., INC. • 2201 E. 46th St., Indianapolis 5, Ind.

Cumulative Index to PHOTOFACT FOLDERS

No. 49 • Covering Folder Sets Nos. 1 through 270 • World's Finest Electronic Service Data

HOW TO USE THIS INDEX

To find the PHOTOFACT Folder you need, first look for the name of the receiver (listed alphabetically below), and then find the required model number. Opposite the model, you will find the number of the PHOTOFACT Set in which the required Folder appears, and the number of that Folder. The PHOTOFACT Set number is shown in bold-face type; the Folder number is in the regular light-face type.

IMPORTANT—1. The letter "A" following a set number in the Index listing, indicates a "Preliminary Data Folder." These folders were designed to provide immediate basic data on TV receivers. Many of these were later superseded by regular Photofact Folders. In those cases where short production runs and/or limited distribution prevented availability of a sample chassis the "A" designation has been retained.

2. Models marked by an asterisk (*) have not yet been covered in a standard Folder. However, regular PHOTOFACT Subscribers may obtain Schematic, Alignment Data or other required information on these models without charge by supplying make, model or chassis number and serial number. (When requesting such data, mention the name of the Parts Distributor who supplies you with your PHOTOFACT Folder Sets.)

3. Production Change Bulletins contain data supplementary to certain models covered in previously issued PHOTOFACT Folders, and are listed in this Index immediately preceding the listing of the original coverage of the model or chassis. These Bulletins should be filed with the Folders covering the models to which the changes apply.

Set Folder No. No.	Set Folder No. No.	Set Folder No. No.	Set Folder No. No.	Set Folder No. No.
ADAPTOL	ADMIRAL—Cont.	ADMIRAL—Cont.	ADMIRAL—Cont.	ADMIRAL—Cont.
CT-1 48-1	● Chassis 19G1 (See PCB 78—Set 219-1 or Ch. 19F1—Set 203-2)	● Models K2216A, K2217A (See Ch. 19M2)	Models 5G21, 5G21/15, 5G22, 5G22/15, 5G23, 5G23/15 (See Ch. 5G2)	● Model 16M12 (See Ch. 21X1)
ADMIRAL (Also see Record Changer Listing)	● Chassis 19H1, 19K1 (Also see PCB 112—Set 263-1) 210-2	● Models KA2216, KA2217 (See Ch. 19M2)	Models 5J21, 5J22, 5J23 (See Ch. 5J2)	● Models 16R11, 16R12 (See Ch. 21B1)
Chassis ULSK1 30-1	● Chassis 19L2, Z, 19M2 266-1	● Models KA2226, KA2227 (See Ch. 19Y1A)	Models 5K11, 5K12, 5K13, 5K14 (See Ch. 5K1)	● Models 17DX10, 17DX11, 17DX12 (See Ch. 17B1)
Chassis UL7C1 25-2	● Chassis 19N1 (See PCB 78—Set 219-1 and Ch. 19E1—Set 203-2)	● Models LA2215Z, LA2216Z, LA2217Z (See Ch. 19N2 and Ch. 20J1)	Models 5L21, 5L22, 5L23 (See Ch. 5L2)	● Models 17K11, 17K12 (See Ch. 21F1)
Chassis 1HF1 258-2	● Chassis 19O2, 19T1, 19T1C 266-1	● Models T1811, T1812 (See Ch. 19B1 or 19B1C)	Models 5M21, 5M22 (See Ch. 5M2)	● Models 17K21, 17K22 (See Ch. 21F1)
Chassis 3A1 2-24	● Chassis 19Q1, 19T2A (See PCB 112—Set 263-1 and Chassis 19B1—Set 210-2)	● Model T1822 (See Ch. 19B1, 19B1C)	Models 5R10 (See Ch. 5R1)	● Models 17M15, 17M16, 17M17 (See Ch. 21F1)
Chassis 3C1 (Also see PCB 15—Set 126-1) 117-2	● Chassis 19U1, A, B, C, 19Y1A 266-1	● Model T2211 (See Ch. 19F1B)	Models 5R11, 5R12, 5R13, 5R14 (See Ch. 5R1)	● Models 19A115, SN, 19A125, SN (See Ch. 19A11)
Chassis 3D1 266-1	● Chassis 20A1, 20B1 (Also see PCB 25—Set 140-1)	● Model T2211A (See Ch. 19T2A)	Model 5S21AN (See Ch. 5C3)	● Models 19A155, SN (See Ch. 19A1)
Chassis 4A1 3-31	● Chassis 20A2, 20A2Z 256-2	● Model T2212 (See Ch. 19F1A or 19F1B)	Model 5S23AN (See Ch. 5C3)	● Models 20X11, 20X12 (See Ch. 20X1)
Chassis 4B1 24-1	● Chassis 20D2 256-2	● Models T2216A, T2217A (See Ch. 20A2)	Model 5T12 (Ch. 5T1)	● Model 20X122 (See Ch. 20X1)
Chassis 4D1 49-1	● Chassis 20T1 (Also see PCB 15—Set 126-1 and PCB 26—Set 146-1)	● Model T2222 (See Ch. 19F1 or 19F1C)	Models 5W11, 5W12 (See Ch. 5W1)	● Model 20X136 (See Ch. 20Y1)
Chassis 4HF1 258-2	● Chassis 20V1 (Also see PCB 15—Set 126-1 and PCB 26—Set 146-1)	● Model T2236Z (See Ch. 19F1)	Models 5X11, 5X12, 5X13, 5X14 (See Ch. 5X1)	● Models 20X145, 20X146, 20X147 (See Ch. 20Y1)
Chassis 4H1 71-2	● Chassis 20X1, 20Y1 117-2	● Model T2237Z, T2239Z (See Ch. 22A3Z)	Models 5Y21, 5Y22, 5Y23 (See Ch. 5Y2)	● Model 22X12 (See Ch. 20Z1)
Chassis 4H1 AK1 77-7	● Chassis 20Z1 (Also see PCB 7—Set 110-1)	● Model T2242 (See Ch. 19K1)	Models 6A21, 6A22, 6A23 (See Ch. 6A2)	● Models 22X25, 22X26, 22X27 (See Ch. 20Z1)
Chassis 4L1 100-1	● Chassis 21A1 (Also see PCB 23—Set 140-1)	● Model T2242A (See Ch. 19K1)	Model 6C21 (See Ch. 6C1)	● Models 24A11, 24A12 (See Ch. 20A1)
Chassis 4R1 108-3	● Chassis 21B1 (Also see PCB 25—Set 144-1 and PCB 79—Set 220-1)	● Models TA1811, TA1812, TA1822 (See Ch. 19T1 or 19T1C)	Models 6C2A, A, 6C2B, A (See Ch. 6C2, A, 6C2B, A)	● Model 24A125 (See Ch. 20A1)
Chassis 4S1 100-1	● Chassis 21C1, 21D1 (Also see PCB 118-2 and PCB 25—Set 144-1)	● Models TA2211, TA2212 (See Ch. 19W1A or 19W1B)	Model 6C71 (See Ch. 10A1)	● Models 24A126, 24A127 (See Ch. 20A1)
Chassis 4T1 143-2	● Chassis 21E1 (See Ch. 21D1—Set 118-2 and PCB 25—Set 144-1)	● Models TA2215, TA2216, TA2217, TA2218 (See Ch. 19L2)	Models 6J21, 6J22 (See Ch. 6J2)	● Models 24C15, 24C16, 24C17 (See Ch. 20B1)
Chassis 4W1 143-2	● Chassis 21F1, 21G1 (Also see PCB 30—Set 156-2 and PCB 46—Set 180-1)	● Models TA2222 (See Ch. 19W1 or 19W1C)	Model 6M22 (See Ch. 6M2)	● Models 24R11, 24R12 (See Ch. 20T1)
Chassis 4X1 261-1	● Chassis 21H1, 21J1 (Also see PCB 25—Set 144-1)	● Model TA2226 (See Ch. 19W1)	Models 6N25, 6N26, 6N27 (See Ch. 6N2)	● Models 24X15, 24X16, 24X175 (See Ch. 20X1)
Chassis 5A3 191-2	● Chassis 21K1, 21L1 (Also see PCB 46—Set 180-1)	● Model TA2232Z (See Ch. 22G2Z)	Models 6P24B, 6P24C, 6P25 (See Ch. 6P)	● Models 25A15, 25A16, 25A17 (See Ch. 20A1)
Chassis 5B1 (See Model 6T02—Set 1-20)	● Chassis 21M1, 21N1 (See PCB 30—Set 156-2, PCB 46—Set 180-1 and Ch. 21F1—Set 135-2)	● Model TD11, 4D12, 4D13 (See Ch. 4D1)	Models 6R48, 6R49, 6R50 (See Ch. 6R)	● Models 26R11, 26R12 (See Ch. 21B1)
Chassis 5B1 Phono 4-24	● Chassis 21P1, 21Q1 (Also see PCB 30—Set 156-2 and PCB 46—Set 180-1)	● Models 4H15, 4H16, 4H17 (A or B) (See Ch. 20A1)	Models 6RT41, 6RT42, 6RT43 (See Ch. 5B1 Phono)	● Model 26R25 (See Ch. 24H1)
Chassis 5B1A 18-1	● Chassis 21R1, 21S1 (See PCB 62—Set 196-1 and Ch. 21W1—Set 177-2)	● Models 4H15A, 4H16, 4H17, 4H18, 4H19 (S or SN) (See Ch. 30B1)	Models 6RT44, 6RT45, 6RT46 (See Ch. 5B1A)	● Model 26R26 (See Ch. 24H1)
Chassis 5B1B 10-1	● Chassis 21T1, 21U1 (Also see PCB 177-2)	● Models 4H141, 4H19 (C or CN) (See Ch. 20B1)	Model 6T01 1-19	● Model 26R28 (See Ch. 24H1)
Chassis 5C1 197-2	● Chassis 21V1 177-2	● Models 4H126A, B, C, CN (See Ch. 21A)	Model 6T02, 6T04 1-20	● Model 26R35 (See Ch. 24H1)
Chassis 5D2 118-2	● Chassis 21Y1 177-2	● Model 4H126B (S or SN) (See Ch. 30B1)	Model 6T05 1-19	● Model 26R36 (See Ch. 24H1)
Chassis 5D3 256-3	● Chassis 21Z1, 21Z1A 177-2	● Models 4H137 (S or SN) (See Ch. 30B1)	Model 6T06, 6T07 (See Ch. 4A1)	● Model 26R37 (See Ch. 24H1)
Chassis 5E2 139-2	● Chassis 22A2, 22A2A 180-2	● Models 4H137A, B (See Ch. 21A)	Model 6T11 (See Model 6T02—Set 1-20)	● Model 26R38 (See Ch. 24H1)
Chassis 5E3 224-2	● Chassis 22A3, 22A3A, 22A3Z 266-2	● Models 4H145A, B (See Ch. 30B1)	Model 6T12 (See Ch. 4A1)	● Models 26X35, 26X36 (See Ch. 24D1)
Chassis 5F1 53-2	● Chassis 22B3Z, 22B3Z 260-2	● Models 4H145, SN (See Ch. 30B1)	Model 6T13 (See Ch. 4A1)	● Models 26X37, 26X38 (See Ch. 24D1)
Chassis 5G2 137-2	● Chassis 22C2 201-2	● Models 4H146A, B, C (See Ch. 20B1)	Model 6T14 (See Ch. 4A1)	● Models 26X39, 26X40 (See Ch. 24D1)
Chassis 5H1 26-1	● Chassis 22E2 201-2	● Models 4H146B, SN (See Ch. 30B1)	Model 6T15 (See Ch. 4A1)	● Models 26X41, 26X42 (See Ch. 24D1)
Chassis 5J2 136-2	● Chassis 22F2 222-2	● Models 4H147A, B (See Ch. 20B1)	Model 6T16 (See Ch. 4A1)	● Models 26X43, 26X44 (See Ch. 24D1)
Chassis 5K1 30-1	● Chassis 22G2 260-2	● Models 4H147S, SN (See Ch. 30B1)	Model 6T17 (See Ch. 4A1)	● Models 26X45, 26X46 (See Ch. 24D1)
Chassis 5L2 140-1	● Chassis 22H1 180-2	● Models 4H155A, B (See Ch. 20B1)	Model 6T18 (See Ch. 4A1)	● Models 26X47, 26X48 (See Ch. 24D1)
Chassis 5M2 157-2	● Chassis 22M2, 22P2 222-2	● Models 4H155S, SN (See Ch. 30B1)	Model 6T19 (See Ch. 4A1)	● Models 26X49, 26X50 (See Ch. 24D1)
Chassis 5N1 31-1	● Chassis 22N2 260-2	● Models 4H156A, B (See Ch. 20B1)	Model 6T20 (See Ch. 4A1)	● Models 26X51, 26X52 (See Ch. 24D1)
Chassis 5R1 59-1	● Chassis 22Y1 180-2	● Models 4H156S, SN (See Ch. 30B1)	Model 6T21 (See Ch. 4A1)	● Models 26X53, 26X54 (See Ch. 24D1)
Chassis 5R2 165-3	● Chassis 23A1 21-2	● Models 4H157A, B (See Ch. 20B1)	Model 6T22 (See Ch. 4A1)	● Models 26X55, 26X56, 26X57 (See Ch. 24D1)
Chassis 5X1 68-1	● Chassis 24E1, 24F1, 24G1 240-1	● Models 4H157S, SN (See Ch. 30B1)	Model 6T23 (See Ch. 4A1)	● Models 26X58, 26X59 (See Ch. 24D1)
Chassis 5W1 79-2	● Chassis 24H1 (Also see PCB 9—Set 114-1)	● Models 4H165A, B (See Ch. 20B1)	Model 6T24 (See Ch. 4A1)	● Models 26X60, 26X61 (See Ch. 24D1)
Chassis 5X2 204-2	● Chassis 30A1 57-2	● Models 4H165S, SN (See Ch. 30B1)	Model 6T25 (See Ch. 4A1)	● Models 26X62, 26X63 (See Ch. 24D1)
Chassis 5Y2 188-2	● Chassis 30B1, 30C1, 30D1, 71-2	● Models 4H166A, B, C, CN (See Ch. 20B1)	Model 6T26 (See Ch. 4A1)	● Models 26X64, 26X65 (See Ch. 24D1)
Chassis 6A1 (See Model 6T01—Set 1-19)	● Model C2216Z (See Ch. 20A2Z)	● Models 4H166B, SN (See Ch. 30B1)	Model 6T27 (See Ch. 4A1)	● Models 26X66, 26X67 (See Ch. 24D1)
Chassis 6A2 103-1	● Models C2225Z, C2226Z, C2227Z (See Ch. 22A3Z)	● Models 4H167A, B, C, CN (See Ch. 20B1)	Model 6T28 (See Ch. 4A1)	● Models 26X68, 26X69 (See Ch. 24D1)
Chassis 6B1 48-2	● Model C2236A (See Ch. 20A2)	● Models 4H167S, SN (See Ch. 30B1)	Model 6T29 (See Ch. 4A1)	● Models 26X70, 26X71 (See Ch. 24D1)
Chassis 6C1 53-1	● Model C2246 (See Ch. 19F1B)	● Models 4R11, 4R12 (See Ch. 4R1)	Model 6T30 (See Ch. 4A1)	● Models 26X72, 26X73 (See Ch. 24D1)
Chassis 6C2, 6C2A 252-3	● Models CA2215Z, CA2216Z, CA2217Z (See Ch. 19L2Z)	● Model 4T11 (See Ch. 4T1)	Model 6T31 (See Ch. 4A1)	● Models 26X74, 26X75 (See Ch. 24D1)
Chassis 6E1, 6E1N 6-1	● Models CA2236, CA2237 (See Ch. 19L2Z)	● Models 4X11, 4X12 (See Ch. 4X1)	Model 6T32 (See Ch. 4A1)	● Models 26X76, 26X77 (See Ch. 24D1)
Chassis 6E2 140-2	● Models CA2246 (See Ch. 19W1B)	● Models 4X18, 4X19 (See Ch. 4X1)	Model 6T33 (See Ch. 4A1)	● Models 26X78, 26X79 (See Ch. 24D1)
Chassis 6L1 146-2	● Models CU2225Z, CU2226Z, CU2227Z (Ch. 22B3Z)	● Models 5A32/12, 5A32/15, 5A32/16, 5A33/12, 5A33/15, 5A33/16 (See Ch. 5A3)	Model 6T34 (See Ch. 4A1)	● Models 26X80, 26X81 (See Ch. 24D1)
Chassis 6M1 25-1	● Models F2216Z, F2217Z, F2218Z (See Ch. 22A3Z)	● Models 5E21, 5E22, 5E23 (See Ch. 5E2)	Model 6T35 (See Ch. 4A1)	● Models 26X82, 26X83 (See Ch. 24D1)
Chassis 6M2 (See Ch. 6J2—Set 140-2)	● Model F2226 (See Ch. 20A2)	● Models 5E31, 5E32, 5E33 (See Ch. 5E3)	Model 6T36 (See Ch. 4A1)	● Models 26X84, 26X85 (See Ch. 24D1)
Chassis 6Q1 78-1	● Models HA2216Z, HA2217Z (See Ch. 19L2Z)	● Models 5F38, 5F39 (See Ch. 5F3)	Model 6T37 (See Ch. 4A1)	● Models 26X86, 26X87 (See Ch. 24D1)
Chassis 6R1 54-1	● Model HIF16, HIF17, HIF18 (Ch. 15HF1, 4HF1, 1HF1) 258-2	● Model 5F12 (See Ch. 5F1)	Model 6T38 (See Ch. 4A1)	● Models 26X88, 26X89 (See Ch. 24D1)
Chassis 6S1 107-1			Model 6T39 (See Ch. 4A1)	● Models 26X90, 26X91 (See Ch. 24D1)
Chassis 6V1 62-1			Model 6T40 (See Ch. 4A1)	● Models 26X92, 26X93 (See Ch. 24D1)
Chassis 6W1 71-1			Model 6T41 (See Ch. 4A1)	● Models 26X94, 26X95 (See Ch. 24D1)
Chassis 6Y1 75-1			Model 6T42 (See Ch. 4A1)	● Models 26X96, 26X97 (See Ch. 24D1)
Chassis 6Y2 18-2			Model 6T43 (See Ch. 4A1)	● Models 26X98, 26X99 (See Ch. 24D1)
Chassis 7C1 25-2			Model 6T44 (See Ch. 4A1)	● Models 26X100, 26X101 (See Ch. 24D1)
Chassis 7E1 75-1			Model 6T45 (See Ch. 4A1)	● Models 26X102, 26X103 (See Ch. 24D1)
Chassis 7G1 54-2			Model 6T46 (See Ch. 4A1)	● Models 26X104, 26X105 (See Ch. 24D1)
Chassis 8C1 (See Ch. 8D1—Set 67-1)			Model 6T47 (See Ch. 4A1)	● Models 26X106, 26X107 (See Ch. 24D1)
Chassis 8D1 67-1			Model 6T48 (See Ch. 4A1)	● Models 26X108, 26X109 (See Ch. 24D1)
Chassis 9A1 32-1			Model 6T49 (See Ch. 4A1)	● Models 26X110, 26X111 (See Ch. 24D1)
Chassis 9B1 49-2			Model 6T50 (See Ch. 4A1)	● Models 26X112, 26X113 (See Ch. 24D1)
Chassis 9E1 68-2			Model 6T51 (See Ch. 4A1)	● Models 26X114, 26X115 (See Ch. 24D1)
Chassis 10A1 3-30			Model 6T52 (See Ch. 4A1)	● Models 26X116, 26X117 (See Ch. 24D1)
Chassis 15HF1 258-2			Model 6T53 (See Ch. 4A1)	● Models 26X118, 26X119 (See Ch. 24D1)
● Chassis 19A1 (Also see PCB 5—Set 106-1)			Model 6T54 (See Ch. 4A1)	● Models 26X120, 26X121 (See Ch. 24D1)
● Chassis 19B1 (Also see PCB 112—Set 263-1) 210-2			Model 6T55 (See Ch. 4A1)	● Models 26X122, 26X123 (See Ch. 24D1)
● Chassis 19B1C (See PCB 112—Set 263-1 and Chassis 19B1—Set 210-2)			Model 6T56 (See Ch. 4A1)	● Models 26X124, 26X125 (See Ch. 24D1)
● Chassis 19C1 (Also see PCB 112—Set 263-1) 210-2			Model 6T57 (See Ch. 4A1)	● Models 26X126, 26X127 (See Ch. 24D1)
● Chassis 19E1 (Also see PCB 78—Set 219-1)			Model 6T58 (See Ch. 4A1)	● Models 26X128, 26X129 (See Ch. 24D1)
● Chassis 19F1, 19F1A (Also see PCB 112—Set 263-1) 210-2			Model 6T59 (See Ch. 4A1)	● Models 26X130, 26X131 (See Ch. 24D1)
● Chassis 19F1B, 19F1C (See PCB 112—Set 263-1 and Chassis 19B1—Set 210-2)			Model 6T60 (See Ch. 4A1)	● Models 26X132, 26X133 (See Ch. 24D1)

NOTE: PCB Denoter Production Change Bulletin. Production Change Bulletin Nos. 1 Through 63 Are All Contained in Set No. A-200. ● Denotes Television Receiver.

AIRLINE—Cont.

- 35GAA-970A 253-2
35GAA-3969A 227-1
35GDC-998A, B 259-1
35CHM-938A 250-4
35CHM-941C 252-4
35CHM-1073B, C 242-2
35CHM-1074A 243-2
35CHM-2012A 256-4
35CHM-2020A 256-4
35GMD-3309A (Early Version) Tel. UHF Conv. (Similar to Chassis) 194-7
35GMD-3309A (Late Version) Tel. UHF Conv. (Similar to Chassis) 194-8
35GSE-1555C (See Model 25GSE-1555A—Set 174-3)
35GSE-1556C (See Model 25GSE-1556A—Set 174-3)
35GSE-3074A (See PCB 72—Set 195-2) and Model 25GSE-3063A—Set 195-2
35GSE-3076A 238-3
35GSE-3078A 238-3
35GSE-3085A (See PCB 72—Set 195-2) and Model 25GSE-3063A—Set 195-2
35GSE-3087A (See PCB 72—Set 195-2) and Model 25GSE-3063A—Set 195-2
35GSE-3093A 238-3
35GSE-3097A 238-3
35GSG-2016A (See Model 35GSG-2016B—Set 225-2)
35GSG-2016B 225-2
35GSL-2770A 249-3
35GSL-3064A, B 218-3
35GSL-3083A, B 218-3
35WG-1570B, C, 35WG-1571B
35WG-1572B (See Model 25WG-1570A—Set 177-4)
35WG-1573B 228-1
35WG-2761C, D (See Model 15WG-2745C—Set 130-2)
35WG-2765F, G (See Model 15WG-2745C—Set 130-2)
35WG-3060B (See PCB 92—Set 237-1) and Model 25WG-3060A—Set 212-2
35WG-3070B (See PCB 92—Set 237-1) and Model 25WG-3070A—Set 212-2
35WG-3071D, E, F (See PCB 96—Set 240-1) and Model 25WG-3071A—Set 206-2
35WG-3073D, E, F (See PCB 96—Set 240-1) and Model 25WG-3073A—Set 206-2
35WG-3171A, B 222-3
35WG-3173A, B 222-3
35WG-3175A 222-3
35WG-3177A 222-3
35WG-3179A 222-3
45BR-3186A 256-6
54BR-1501A, 54BR-1502A 2-26
54BR-1503A, B, C, 54BR-1504A, B, C 3-4
54BR-1505A, B, 54BR-1506A, B 2-34
44WK-1209A, B 1-2
44WG-1801A, 54WG-1801B 4-33
54WG-2500A, 54WG-2700A 4-15
61-6780 (Similar to Chassis) 147-2
61-6781 (Similar to Chassis) 147-2
61-6782 (Similar to Chassis) 146-3
61-6783 (Similar to Chassis) 173-4
61-6784 (Similar to Chassis) 173-4
61-6787 256-6
61-6788 264-2
61-6789 260-5
61-6792 237-2
61-6794 236-2
61-6795 242-3
61-12601 241-3
64BR-916A 3-34
64BR-916B (See Model 74BR-916B—Set 17-5) 10-1
64BR-917A (See Model 64BR-917A—Set 10-1) 10-1
64BR-917B (See Model 64BR-917A—Set 10-1) 10-1
64BR-1051A (See Model 64BR-1051A—Set 2-32) 2-32
64BR-1051B (See Model 64BR-1051A—Set 2-32) 2-32
64BR-1205A, 64BR-1206A 10-3
64BR-1208A 16-4
64BR-1503B, 64BR-1504B (See Model 54BR-1503A—Set 3-4) 3-4
64BR-1513A, B, 64BR-1514A, B 24-4
64BR-1808A 16-4
64BR-2200A 16-4
64BR-7000A 51-2
64BR-7100A, 64BR-7110A, 64BR-7120A 57-5
64BR-7300A, 64BR-7310A, 64BR-7320A 54-8
64WG-7810A, 64WG-7820A 53-3
64WG-1050A 10-2
64WG-1050B, C, D (See Model 64WG-1050A—Set 10-2) 9-2
64WG-1052A (See Model 64WG-1052A—Set 9-2) 9-2
64WG-1207B 18-5
64WG-1511A, 64WG-1511B, 64WG-1512A, 64WG-1512B 5-5
64WG-1801C 4-33
64WG-1804A 4-27
64WG-1804C (See Model 64WG-1804A—Set 4-27) 4-27
64WG-1807A, 64WG-1807B 5-4
64WG-1809A, B 5-5
64WG-2007A, 64WG-2007B 5-6
64WG-2009A, 64WG-2009B 6-2
64WG-2010B 18-6
64WG-2500A (See Model 54WG-2500A—Set 4-15) 4-15
64WG-2700A, B (See Model 54WG-2700A—Set 4-15) 4-15
64WG-2704A, B (See Model 74WG-2704A—Set 28-1) 28-1
64WG-2704B, C (See Model 74WG-2704A—Set 28-1) 28-1
64WG-2705A, B (See Model 74WG-2705A—Set 18-7) 18-7
64WG-2709A 26-5
64WG-2711A (See Model 74WG-2709A—Set 18-7) 26-5
84BR-1815B, 84BR-1816B 55-3
84CAA-3967A 91-3
84GDC-925A 52-2
84GDC-963B 51-3
84GDC-987A 53-4
84GDM-926B 55-4
84GSE-2730A, 84GSE-2731A 70-1
84GSE-3011A 82-1
84HA-1527A, 84HA-1528A (See Model 84HA-1527C—Set 67-3) 67-3
84HA-1529A, 84HA-1530A 85-2
84HA-1810A (See Model 84HA-1810C—Set 69-2) 69-2
84HA-1810C 69-2
84HA-3002A, 84HA-3002B 99-3
84HR-1501A, B, C (Also see PCB 11—Set 118-1) 94-2
84KR-1520A 56-4
84KR-2511A 68-4
84WG-1060A 42-1
84WG-1060C (See Model 84WG-1060A—Set 42-1) 42-1
84WG-2015A 38-1
84WG-2506 (See Model 84WG-2721A—Set 46-3) 46-3
84WG-2506B 58-5
84WG-2712A 43-2
84WG-2712B (See Model 84WG-2712A—Set 43-3) 43-3
84WG-2714A 36-2
84WG-2714F, G, H, J 56-5
84WG-2718A, 84WG-2718B, 84WG-2718C 45-3
84WG-2719A, B 46-3
84WG-2724A 45-5
84WG-2728A (See Model 84WG-2718A—Set 45-5) 45-5
84WG-2732A, B (See Model 84WG-2718A—Set 45-5) 45-5
84WG-2734A (See Model 84WG-2718A—Set 45-5) 45-5
84WG-3006, 84WG-3008, 84WG-3009 (See Model 94WG-3006A—Set 72-4) 88-1
94BR-1527A, 94BR-2741A, B 89-1
94BR300A, C, 94BR300S, C 91A-3
94BR-3017A 89-2
94BR-3017B (See PCB 7—Set 110-1) and Model 94BR-3017A—Set 87-3
94CAA-3654A 95-1
94GCB-1064A 96-2
94GCB-3023A, B, C 116-2
94GDM-934A 167-3
94GSE-2735A, 94GSE-2736A 72-3
94GSE-3008, B (See Model 84GSE-3011A—Set 82-1) 82-1
94GSE-3015A 107-2
94GSE-3018A 93A-2
94HA-1527C, 94HA-1528C 67-3
94HA-1529A, 94HA-1530A 85-2
94WG-1059A 75-6
94WG-1804D 86-2
94WG-1811A 99-4
94WG-2742A, C, D 71-5
94WG-2745A 76-4
94WG-2746A, B, 94WG-2747A 71-5
94WG-2748A, 94WG-2749A 90-1
94WG-2748C (See Model 94WG-2748A—Set 90-1) 90-1
94WG-2749A 90-1
94WG-3006A 72-4
94WG-3006B 85-3
94WG-3008A, 94WG-3009A 72-4
94WG-3009B 85-3

AIRLINE—Cont.

- 74BR1812B 22-2
74BR-2001A (See Model 74BR-2001B—Set 23-2) 23-2
74BR-2001B 23-2
74BR-2701A 24-5
74BR-2702A (See Model 74BR-2702B—Set 25-3) 25-3
74BR-2702B 25-3
74GSG-8400A, 74GSG-8700A 60-3
74GSG-8810A, 74GSG-8820A 52-2
74HA-8200A 58-4
74KR-1210A 41-1
74KR-2706B 35-1
74KR-2713A 43-2
74WG-925A 24-6
74WG-1050C, D (See Model 64WG-1050A—Set 10-2) 10-2
74WG-1052B (See Model 64WG-1052A, B—Set 9-2) 9-2
74WG-1054A 22-1
74WG-1054B (See Model 74WG-1054A—Set 22-1) 22-1
74WG-1056A 29-1
74WG-1057A 32-2
74WG-1207B 18-5
74WG-1509A, 74WG-1510A 27-1
74WG-1511B, 74WG-1512B (See Model 64WG-1511A—Set 5-5) 5-5
74WG-1802A 25-4
74WG-1803A (See Model 74WG-1802A—Set 25-4) 25-4
74WG-1804C (See Model 64WG-1804A—Set 4-27) 4-27
74WG-1807A, B (See Model 64WG-1807A—Set 5-4) 5-4
74WG-2002A 26-4
74WG-2004A 27-2
74WG-2007B, 74WG-2007C 5-6
74WG-2009B (See Model 64WG-2009A—Set 6-2) 6-2
74WG-2010A (See Model 74WG-2010B—Set 18-6) 18-6
74WG-2010B 18-6
74WG-2500A (See Model 54WG-2500A—Set 4-15) 4-15
74WG-2504A 28-1
74WG-2504B, C (See Model 74WG-2504A—Set 28-1) 28-1
74WG-2700A, B (See Model 54WG-2500A—Set 4-15) 4-15
74WG-2704A 28-1
74WG-2704B, C (See Model 74WG-2704A—Set 28-1) 28-1
74WG-2705A, B (See Model 74WG-2705A—Set 18-7) 18-7
74WG-2709A 26-5
74WG-2711A (See Model 74WG-2709A—Set 18-7) 26-5
84BR-1815B, 84BR-1816B 55-3
84CAA-3967A 91-3
84GDC-925A 52-2
84GDC-963B 51-3
84GDC-987A 53-4
84GDM-926B 55-4
84GSE-2730A, 84GSE-2731A 70-1
84GSE-3011A 82-1
84HA-1527A, 84HA-1528A (See Model 84HA-1527C—Set 67-3) 67-3
84HA-1529A, 84HA-1530A 85-2
84HA-1810A (See Model 84HA-1810C—Set 69-2) 69-2
84HA-1810C 69-2
84HA-3002A, 84HA-3002B 99-3
84HR-1501A, B, C (Also see PCB 11—Set 118-1) 94-2
84KR-1520A 56-4
84KR-2511A 68-4
84WG-1060A 42-1
84WG-1060C (See Model 84WG-1060A—Set 42-1) 42-1
84WG-2015A 38-1
84WG-2506 (See Model 84WG-2721A—Set 46-3) 46-3
84WG-2506B 58-5
84WG-2712A 43-2
84WG-2712B (See Model 84WG-2712A—Set 43-3) 43-3
84WG-2714A 36-2
84WG-2714F, G, H, J 56-5
84WG-2718A, 84WG-2718B, 84WG-2718C 45-3
84WG-2719A, B 46-3
84WG-2724A 45-5
84WG-2728A (See Model 84WG-2718A—Set 45-5) 45-5
84WG-2732A, B (See Model 84WG-2718A—Set 45-5) 45-5
84WG-2734A (See Model 84WG-2718A—Set 45-5) 45-5
84WG-3006, 84WG-3008, 84WG-3009 (See Model 94WG-3006A—Set 72-4) 88-1
94BR-1527A, 94BR-2741A, B 89-1
94BR300A, C, 94BR300S, C 91A-3
94BR-3017A 89-2
94BR-3017B (See PCB 7—Set 110-1) and Model 94BR-3017A—Set 87-3
94CAA-3654A 95-1
94GCB-1064A 96-2
94GCB-3023A, B, C 116-2
94GDM-934A 167-3
94GSE-2735A, 94GSE-2736A 72-3
94GSE-3008, B (See Model 84GSE-3011A—Set 82-1) 82-1
94GSE-3015A 107-2
94GSE-3018A 93A-2
94HA-1527C, 94HA-1528C 67-3
94HA-1529A, 94HA-1530A 85-2
94WG-1059A 75-6
94WG-1804D 86-2
94WG-1811A 99-4
94WG-2742A, C, D 71-5
94WG-2745A 76-4
94WG-2746A, B, 94WG-2747A 71-5
94WG-2748A, 94WG-2749A 90-1
94WG-2748C (See Model 94WG-2748A—Set 90-1) 90-1
94WG-2749A 90-1
94WG-3006A 72-4
94WG-3006B 85-3
94WG-3008A, 94WG-3009A 72-4
94WG-3009B 85-3

AIRLINE—Cont.

- 94WG-3016A, B, C (See Set 110-2) and Model 94WG-9006A—Set 72-4
94WG-3022 85-3
94WG-3026A 85-3
94WG-3028A (See Model 94WG-3006A—Set 72-4) 85-3
94WG-3029A 85-3
ALDENS
114G, 116G, 117G, 120G (Similar to Chassis) 162-7
ALGENE
AR5U 22-3
AR6U 22-4
ALLIANCE
AB-3 (TV Booster) 254-2
BB2 (TV Booster) 253-3
ALLSTATE
6263 (Ch. 528.6263) 269-3
6284 (Ch. 528.6284) 228-2
6284 (Ch. 528.6286-4) 225-3
6287 (Ch. 528.6287-4) 225-3
6295-6 (Ch. 528.6295-6) 229-2
ALTEC LANSING
ALC-101 84-2
ALC-205, ALC-206 105-3
A323B 66-2
A323C 84-2
A-333A 165-5
A-433A 165-5
303A 166-4
AMBASSADOR
AM17C, CB, CIM, PT, TIM 171-2
AM20C, T 171-2
A17CS, A17TS (See Model 20PC—Set 178-3)
A20CS (See Model 20PC—Set 178-3)
A21QDCS (See Model 20PC—Set 178-3)
A24QDCS (See Model 20PC—Set 178-3)
A-9121-A, -AX (See Model 21C2A—Set 191-4)
CD2020 175-2
C1720 175-2
C2020 175-2
C2050 (See Model C1720—Set 175-2)
C2052 (See Model T1853—Set 197-3)
C2150 (See Model C1720—Set 175-2)
C2152, A (See Model T1853—Set 197-3)
C2155 (See Model T1853—Set 197-3)
C2420 175-2
P17CB, CG, PG, TM 171-2
T1720 175-2
T2020 175-2
14MC, MT 162-2
14MT (2nd Prod.), 14MTS 173-2
16MC, MT, MXC, MXCS, 162-2
16MT (2nd Prod.), MTS 173-2
17MC, MT, MXC, MXCS, MXT, MXTS 162-2
17MC (2nd Prod.), MCS, MT (2nd Prod.), MTS 173-2
17PC, 17PCS (See Model 20PC—Set 178-3)
17PT, 17PTS (See Model 20PC—Set 178-3)
20C 171-2
20MC, MCS, MT, MTS 173-2
20PC, 20PCS, 20PCS2 173-3
20PT, 20PTS, 20PTS (See Model 20PC—Set 178-3)
21C2DA, B (See Model 21C2A—Set 191-4)
21C2A, 21C2AL0 191-4
23P 171-2
921 (See Model 21C2A—Set 191-4)
9120, LO 191-4
9121, M, LO, XB (See Model 21C2A—Set 191-4) 191-4
AMC (AIMCEE)
1C23 (Similar to Chassis) 139-11
1C72 (Similar to Chassis) 126-8
1171 (Similar to Chassis) 126-8
17C, CB (Similar to Chassis) 126-8
17CC, 17C3 (Similar to Chassis) 149-13
17T (Similar to Chassis) 126-8
17TG (Similar to Chassis) 149-13
17T20 (Similar to Chassis) 139-11
20CD (Similar to Chassis) 149-13
20CD2A, 1 (See Model 20C2A—Set 188-3)
20CD2B (Early) (See Model 20C2A—Set 188-3)
20CD2B (Late) 252-2
20C1 (Similar to Chassis) 149-13
20C2A (See Model 20C2A—Set 188-3)
20C2B (Early) (See Model 20C2A—Set 188-3)
20C2B (Late) 252-2
20C22 (Similar to Chassis) 139-11
20D, DB (Similar to Chassis) 139-11
20TG (Similar to Chassis) 149-13
20T2A, 1 (See Model 20C2A—Set 188-3)
20T2B (Early) (See Model 20C2A—Set 188-3)
20T2B (Late) 252-2
20T21 (Similar to Chassis) 139-11
21C2DA (Early) (See Model 20C2A—Set 188-3)
21C2DA (Late) 252-2
21C2A (Early) (See Model 20C2A—Set 188-3)
21C2A (Late) 252-2
24T2A, 1 (See Model 20C2A—Set 188-3)
114C, 114T (Similar to Chassis) 111-3
116C, 116CD, 116T (Similar to Chassis) 111-3
125P 3-27
126 16-1

AMPEX (See Recorder Listing)

- AMPLIFIER CORP. OF AMERICA
ACA-100DC, ACA-100GE 63-2
AMPLIPHONE
10 21-1
20 21-12
AMPRO (See Recorder Listing)
ANDREA
BC-VL17 (Ch. VL17) (See Model C-VL17—Set 152-1)
BT-VK12 76-5
BR-VL17 (Ch. VL17) (See Model C-VL17—Set 152-1)
CO-U15 27-3
CO-VK15, COVK16 (Ch. VK1516) [Also see PCB 8—Set 112-1] 103-4
COVK-125 76-5
COVK-16 (Ch. VL16) 125-3
CO-VL19 (Ch. VL19) 168-4
CO-VN21 (Ch. VN21) 204-3
CO-VK19 (See PCB 8—Set 112-1) and Model COVK15—Set 103-4
CVK-126 76-5
CVL-16 (Ch. VL16) 125-3
CVL-17 (Ch. VL17) 152-1
CV-M21 (Ch. VM-21) 204-3
CV-VN21 (Ch. VN21) 246-2
P-163 (Ch. 163) 18-8
T16 21-2
T-U16 21-3
T-VK12 76-5
TVK-127B, M 76-5
TVL-12 123-3
TVL-16 (Ch. VL-16) 125-3
T-VL17 (Ch. VL17) 152-1
T-VN21 (Ch. VN21) 204-3
2C-VL17 (Ch. VL17) 152-1
2C-VL20 (Ch. VL-20) 175-3
2C-VN21 (Ch. VN21) 204-3
2C-VN21 (Ch. VN21) 246-2
Ch. VK1516 (See Model CO-VK15)
Ch. VL16 (See Model CO-VL16)
Ch. VL17 (See Model CO-VL17)
Ch. VL19 (See Model CO-VL19)
Ch. VL20 (See Model 2C-VL20)
Ch. VN21 (See Model C-VN21)
Ch. VN21 (See Model C-VN21)
ANSLEY
32 5-27
41 (Paneltone) 4-38
50 24-8
701 71-6
APEX
485 37-2
192A 17-6
817, 920, 924 181-3
9120, 9121 181-3
9820, 9820B, 9821 181-3
APPROVED ELECTRONIC INSTRUMENT CORP.
FM Tuner 41-2
A-600AC 175-4
A710 177-5
A-800 176-2
A-850 175-5
ARC
601 25-5
ARCADIA
37D14-600 9-3
ARIA
554-1-61A 7-2
ARLINGTON
30T14A-056 (Similar to Chassis) 119-3
38T12A-058 (Similar to Chassis) 109-1
317T3 (Similar to Chassis) 72-4
318T4 (Similar to Chassis) 85-3
318T4S (Similar to Chassis) 85-3
318T4-B72 (Similar to Chassis) 85-3
318T6A (Similar to Chassis) 85-3
318T6A-950 (Similar to Chassis) 85-3
318T9A-900 (Similar to Chassis) 78-4
321MS31C (Similar to Chassis) 182-5
321MS39A (Similar to Chassis) 226-11
318T6A (Similar to Chassis) 85-3
318T9A-918 (Similar to Chassis) 78-4
318T10A-916 (Similar to Chassis) 78-4
2318T6A-954 (Similar to Chassis) 85-3
2318T9A-912 (Similar to Chassis) 85-3
321MS39A (Similar to Chassis) 226-11
ARTHUR ANSLEY
HE7 263-2
LP-2, LP-3 62-4
LP-4A 82-2
LP-5 (See Model P-5—Set 108-4) 136-5
LP-6, LP-6S 136-5
LP-7 134-3
P-5 108-4
R-1 200-2
SP-1 60-4
TP-1 173-3
ARTONE
AR14L, AR17L 172-3
AR21 205-3
AR71 205-3
AR-23TV-1 80-1
ARC21 205-3
ARC71 205-3
AR221 170-4
AST12, AST14 170-4
14TR, 16TR 170-4
17CD (1st Prod.) 170-4
17CD (2nd Prod.) 172-3

ARTONE—Cont.

- 17CRR (1st Prod.) 170-4
17CRR (2nd Prod.) 172-3
17ROG (1st Prod.) 170-4
17ROG (2nd Prod.) 172-3
20CD (1st Prod.) 170-4
20CD (2nd Prod.) 172-3
20TR 170-4
112X 170-4
203D (1st Prod.) 170-4
203D (2nd Prod.) 172-3
312 170-4
524 76-7
819 170-4
1000, 1001 172-3
3163CR 170-4
8163CR, 8193CR 170-4
ARVIN
15-550KB-UHF 262-2
21-550KB, KM, 21-551TB, TM, 21-552KB, KM, 21-553TB, TM (Ch. TE383) 266-2
21-550KB, KM, 21-551TB, TM, 21-552KB, KM, 21-553TB, TM (Ch. TE383) 266-2
21-554KM, KMU (Ch. TE383 'E' Series, TE386-UHF 'E' Series) 264-3
21-555TG, TGU, TM, TAU (Ch. TE383 'E' Series, TE386-UHF 'E' Series) 264-3
21-557TM, TMU (Ch. TE383 'E' Series, TE386-UHF 'E' Series) 264-3
140P (Ch. RE-209) 25-6
150-TC, 151-TC (Ch. RE-28) 25-7
150TC, 151TC (Ch. RE-28) 152F (Ch. RE-233) 33-1
153T (See Model 152T—Set 33-1) 160T, 161T (Ch. RE-232) 49-5
182TFM (Ch. RE-237) 32-3
240-P (Ch. RE-243) 42-2
241P (Ch. RE-244, RE-254, RE-255, RE-256, RE-259) 47-3
242T, 243T (Ch. RE-251) 52-3
244P (Ch. RE-244, RE-254, RE-255, RE-256, RE-259) 47-3
250-P (Ch. RE-248) 43-4
253T, 254T, 255T, 256T (Ch. RE-252) 53-5
264T, 265T (Ch. RE-265) 64-2
280TFM, 281TFM (Ch. RE-253) 44-2
341T (Ch. RE-274) 84-3
350P (Ch. RE-267) 69-3
350-PB (Ch. RE-267-1) 100-4
350PL (Ch. RE-277-2) 100-4
351P (Ch. RE-267) 69-3
351-PB (Ch. RE-267-1) 100-4
351-PL (Ch. RE-267-2) 100-4
352-PL, 353-PL (Ch. RE-267-2) 100-4
355T (Ch. RE-213) (See Model 356T—Set 78-2) 78-2
356T, 357T (Ch. RE-273) 78-2
358T (Ch. RE-233) (See Model 152T—Set 33-1) 117-4
360TFM, 361TFM (Ch. RE-260) 70-2
440T (Ch. RE-278) 96-3
441T (Ch. RE-278) (See Model 440T—Set 96-3) 34-2
442 (Ch. RE-91) 1-3
444, 444A (Ch. RE-200) 1-3
444AM, 444M (Ch. RE-200M) 23-3
446P (Ch. RE-280) 106-2
450T, 451T (Ch. RE-281) 110-3
460T, 461T (Ch. RE-284) 107-3
462-CB, 462-CM (Ch. RE-281) 116-3
480TFM, 481TFM (Ch. RE-277, RE-277-1) 107-4
482CFB, 482CFM (Ch. RE-288-1) 117-4
540T (Ch. RE-278) 143-4
542T (See Model 440T—Set 96-3) 1-7
544A, 544M (Ch. RE-201) (See Model 544A—Set 1-7) 42-3
547A (Ch. RE-242) 154-2
551T (Ch. RE-297) 134-2
552AN, 552N (Ch. RE-231) 13-9
553 (Ch. RE-308) 159-4
554CCB, 554CCM (Ch. RE-306) 153-3
555, A (Ch. RE-202) 13-16
558 (Ch. RE-204) 13-16
580TFM (Ch. RE-313) 152-2
581TFM (Ch. RE-333) 227-2
582CFB, 582CFM (Ch. RE-310) 156-4
652-P (Ch. RE-292) (See Model 650-P—Set 175-6) 175-6
654-P (Ch. RE-292) (See Model 650-P—Set 175-6) 175-6
655 (Ch. RE-323) 251-3
655 SWT (Ch. RE-327) 187-2
657 (Ch. RE-342) 233-3
664, 664A (Ch. RE-206) 3-23
664, 664A (Ch. RE-206-1) 29-2
665 (Ch. RE-229) 18-10
740T (Ch. RE-278) (See Model 540T—Set 143-4) 225-4
741T (Ch. RE-352) 225-4
746P, 747P (Ch. RE-347) 225-5
751TB (See Model 551T—Set 154-2) 220-2
753T (Ch. RE-348) 220-2
758T (Ch. RE-350) 221-3
760T (Ch. RE-342) 223-3
780TFM (Ch. RE-333) 227-2
840T (Ch. RE-278-1) 263-3
848T, 849T (Ch. RE-369) 259-2
850T (Ch. RE-375) 262-3
851T (Ch. RE-377) 266-3
852P (Ch. RE-372) 258-3
853T (Ch. RE-345) 62-3
854P (Ch. RE-372) 258-3
855T (Ch. RE-377) 266-3
858T, 859T (Ch. RE-374) 261-2
2120CM (Ch. TE289-2, TE289-3) [Also see PCB 20—

ARVIN-BENDIX

ARVIN-Cont.

- 2122TM (Ch. TE-289) ... 97A-1
- 2123TM (Ch. TE-289-2, TE289-3) (Also see PCB 20—Set 134-1) ... 120-3
- 2124CCM (Ch. TE289-2, TE289-3) (Also see PCB 20—Set 134-1) ... 120-3
- 2126CM (Ch. TE289-2, TE289-3) (Also see PCB 20—Set 134-1) ... 120-3
- 2160, 2161, 2162, 2164 (Ch. TE-290) ... 126-3
- 2410P (Ch. RE-244, RE-254, RE-255, RE-256, RE-259) ... 47-3
- 3100TB, 3100TM, 3101CM, 3120-TM, 3121TM (Ch. TE-272-1, TE-272-2) ... 80-2
- 3160CM (Ch. TE-276) ... 93-2
- 4080T (Ch. TE282) ... 104-2
- 4081T (See Model 4080T—Set 104-2) ... 104-2
- 4162CM (Ch. TE-286) ... 130-3
- 5170CB, CM, 5171TM, 5172CB, CM (Ch. TE-302, -1, -2, -3, -4, -5A, -6) (Also see PCB 50—Set 184-1) ... 142-5
- 5173TM (Ch. TE-302) (See Model 5170CB) ... 179-3
- 5175, 5176 (Ch. TE320) ... 179-3
- 5204CM, 5206CM (Ch. TE-300) ... 149-3
- 5210, 5211, 5212 (Ch. TE-315, -1, -2, -3, -4, -5) (Also see PCB 37—Set 166-1 and PCB 50—Set 184-1) ... 151-5
- 5213TM (Ch. TE334) ... 191-5
- 5213TM (Ch. TE331-3, -4, -5) (See PCB 66—Set 203-1, PCB 92—Set 237-1 and Model 6175TM—Set 181-4) ... 181-4
- 6173TM-UHF (Ch. TE332, -1, -2, -3, -4) (Also see PCB 88—Set 231-1) ... 208-2
- 6175TM (Ch. TE-331, -1, -2, -3, -4) (Also see PCB 66—Set 203-1) ... 181-4
- 6175TMA-A (Ch. TE331-5) (See PCB 66—Set 203-1, PCB 92—Set 207-1 and Model 6175TM—Set 181-4) ... 181-4
- 6179TM (Ch. TE-331, -1, -2, -3, -4) (Also see PCB 66—Set 203-1) ... 181-4
- 6213TB (Ch. TE-319, -1, -2) (See PCB 67—Set 204-1 and Model 6213TM—Set 195-4) ... 195-4
- 6213TB-UHF (Ch. TE330, -1, -2, -3, -4, -5, -6) (Also see PCB 88—Set 231-1) ... 208-2
- 6213TM (Ch. TE-319, -1, -2) (Also see PCB 67—Set 204-1) ... 195-4
- 6213TM-UHF (Ch. TE330, -1, -2, -3, -4, -5, -6) (Also see PCB 88—Set 231-1) ... 208-2
- 6215CB (Ch. TE-319, -1, -2) (Also see PCB 67—Set 204-1) ... 195-4
- 6215CB-UHF (Ch. TE330, -1, -2, -3, -4, -5, -6) (Also see PCB 88—Set 231-1) ... 208-2
- 6215CM (Ch. TE-319, -1, -2) (Also see PCB 67—Set 204-1) ... 195-4
- 6215CM-UHF (Ch. TE330, -1, -2, -3, -4, -5, -6) (Also see PCB 88—Set 231-1) ... 208-2
- 6640 (Ch. RE-206-2) ... 29-2
- 7210CB (Ch. TE337, -1, -2, -3, -4, -5) (Also see PCB 93—Set 238-1) ... 189-3
- 7210CB-UHF (Ch. TE341, -1, -2, -3, -4, -5, -6, -41) (Also see PCB 63—Set 197-1 and PCB 94—Set 239-1) ... 188-4
- 7210CM (Ch. TE337, -1, -2, -3, -4, -5) (Also see PCB 93—Set 238-1) ... 189-3
- 7210CM-UHF (Ch. TE341, -1, -2, -3, -4, -5, -6, -41) (Also see PCB 63—Set 197-1 and PCB 94—Set 239-1) ... 188-4
- 7212CFP (Ch. TE337, -1, -2, -3, -4, -5) (Also see PCB 93—Set 238-1 and Model 7210CM—Set 189-3) ... 189-3
- 7212CFP-UHF (Ch. TE341, -1, -2, -3, -4, -5, -6, -41) (Also see PCB 63—Set 197-1 and PCB 94—Set 239-1) ... 188-4
- 7212MEA-UHF (Ch. TE341, -1, -2, -3, -4, -5, -6, -41) (Also see PCB 63—Set 197-1 and PCB 94—Set 239-1) ... 188-4
- 7214CM (Ch. TE337, -1, -2, -3, -4, -5) (Also see PCB 93—Set 238-1) ... 189-3
- 7214CM-UHF (Ch. TE341, -1, -2, -3, -4, -5, -6, -41) (Also see PCB 63—Set 197-1 and PCB 94—Set 239-1) ... 188-4
- 7216CB (Ch. TE-337-1) (See Model 7210CM—Set 189-3) ... 189-3
- 7216CB-UHF (Ch. TE341, -1, -2, -3, -4, -5, -6, -41) (Also see PCB 63—Set 197-1 and PCB 94—Set 239-1) ... 188-4
- 7218CB (Ch. TE337, -1, -2, -3, -4, -5) (Also see PCB 93—Set 238-1) ... 189-3
- 7218CB-UHF (Ch. TE341, -1, -2, -3, -4, -5, -6, -41) (Also see PCB 63—Set 197-1 and PCB 94—Set 239-1) ... 188-4
- 7218CM (Ch. TE337, -1, -2, -3, -4, -5) (Also see PCB 93—Set 238-1) ... 189-3
- 7218CM-UHF (Ch. TE341, -1, -2, -3, -4, -5, -6, -41) (Also see PCB 63—Set 197-1 and PCB 94—Set 239-1) ... 188-4
- 7276CB-UHF (Ch. TE340, -1, -2) ... 231-3
- 7279CM-UHF (Ch. TE340, -1, -2) ... 231-3
- 8171TM (Ch. TE331-6) (See PCB 66—Set 203-1, PCB 92—Set 237-1 and Model 6175TM—Set 181-4) ... 181-4

ARVIN-Cont.

- 8171TM-UHF (Ch. TE332-5) (See PCB 88—Set 231-1 and Model 6175TM-UHF—Set 208-2) ... 208-2
- 8179TM (Ch. TE331-5) (See PCB 66—Set 203-1, PCB 92—Set 237-1 and Model 6175TM—Set 181-4) ... 181-4
- 8179TMA (Ch. TE332-4) (See PCB 88—Set 231-1 and Model 6173TM-UHF—Set 208-2) ... 208-2
- 8211TB (Ch. TE319-3) (See PCB 67—Set 204-1, PCB 89—Set 233-1 and Model 6213TM—Set 195-4) ... 195-4
- 8211TB-UHF (Ch. TE330-7) (See PCB 88—Set 231-1 and Model 6213TB-UHF—Set 208-2) ... 208-2
- 8213TM (Ch. TE319-3) (See PCB 67—Set 204-1, PCB 89—Set 233-1 and Model 6213TM—Set 195-4) ... 195-4
- 8213TM-UHF (Ch. TE330-6) (See PCB 88—Set 231-1 and Model 6213TB-UHF—Set 208-2) ... 208-2
- 8213TMA (Ch. TE319-21) (See PCB 67—Set 204-1, PCB 89—Set 233-1 and Model 6213TM—Set 195-4) ... 195-4
- 8213TMA-UHF (Ch. TE330-61) (See PCB 88—Set 231-1 and Model 6213TB-UHF—Set 208-2) ... 208-2
- 8215CB (Ch. TE319-3) (See PCB 67—Set 204-1, PCB 89—Set 233-1 and Model 6213TM—Set 195-4) ... 195-4
- 8215CB-UHF (Ch. TE330-6) (See PCB 88—Set 231-1 and Model 6213TB-UHF—Set 208-2) ... 208-2
- 8215CM (Ch. TE319-21) (See PCB 67—Set 204-1, PCB 89—Set 233-1 and Model 6213TM—Set 195-4) ... 195-4
- 8215CM-UHF (Ch. TE330-6) (See PCB 88—Set 231-1 and Model 6213TB-UHF—Set 208-2) ... 208-2
- 8215CMA (Ch. TE319-21) (See PCB 67—Set 204-1, PCB 89—Set 233-1 and Model 6213TM—Set 195-4) ... 195-4
- 8215CMA-UHF (Ch. TE330-61) (See PCB 88—Set 231-1 and Model 6213TB-UHF—Set 208-2) ... 208-2
- 8218CB (Ch. TE319-3) (See PCB 67—Set 204-1, PCB 89—Set 233-1 and Model 6213TM—Set 195-4) ... 195-4
- 8218CB-UHF (Ch. TE330-7) (See PCB 88—Set 231-1 and Model 6213TB-UHF—Set 208-2) ... 208-2
- 9210CB (Ch. TE358, -1, -2, -3) ... 238-4
- 9210CB-UHF (Ch. TE-363, -1, -2, -3) ... 238-4
- 9210CM (Ch. TE358, -1, -2, -3) ... 238-4
- 9210CM-UHF (Ch. TE363, -1, -2, -3) ... 238-4
- 9211TM (Ch. TE355) ... 248-2
- 9211TM-UHF (Ch. TE-362) ... 248-2
- 9212CFP (Ch. TE358, -1, -2, -3) ... 238-4
- 9212CFP-UHF (Ch. TE363, -1, -2, -3) ... 238-4
- 9212MEA (Ch. TE358, -1, -2, -3) ... 238-4
- 9212MEA-UHF (Ch. TE363, -1, -2, -3) ... 238-4
- 9213TM (Ch. TE-355) ... 248-2
- 9213TM-UHF (Ch. TE-362) ... 248-2
- 9215CM (Ch. TE-355) ... 248-2
- 9215CM-UHF (Ch. TE-362) ... 248-2
- 9216CB (Ch. TE358, -1, -2, -3) ... 238-4
- 9216CB-UHF (Ch. TE363, -1, -2, -3) ... 238-4
- 9218CB (Ch. TE358, -1, -2, -3) ... 238-4
- 9218CB-UHF (Ch. TE363, -1, -2, -3) ... 238-4
- 9218CM (Ch. TE358, -1, -2, -3) ... 238-4
- 9218CM-UHF (Ch. TE363, -1, -2, -3) ... 238-4
- 9219CM (Ch. TE358, -1, -2, -3) ... 238-4
- 9219CM-UHF (Ch. TE363, -1, -2, -3) ... 238-4
- 9240CB (Ch. TE364, -1) ... 235-2
- 9240CB-UHF (Ch. TE359, -1) ... 235-2
- 9240CM (Ch. TE364, -1) ... 235-2
- 9240CM-UHF (Ch. TE359, -1) ... 235-2
- 9243CM-UHF (Ch. TE373) ... 247-3
- Ch. RE-200 (See Model 442) ... 14-5
- Ch. RE-200M (See Model 444M) ... 14-5
- Ch. RE-201 (See Model 544) ... 14-5
- Ch. RE-202 (See Model 558) ... 14-5
- Ch. RE-206 (See Model 664) ... 14-5
- Ch. RE-206-1, 206-2 (See Model 664 Late) ... 14-5
- Ch. RE-209 (See Model 140P) ... 14-5
- Ch. RE-228 (See Model 150TC) ... 14-5
- Ch. RE-228-1 (See Model 150TC) ... 14-5
- Ch. RE-229 (See Model 665) ... 14-5
- Ch. RE-231 (See Model 552AN) ... 14-5
- Ch. RE-232 (See Model 160T) ... 14-5
- Ch. RE-233 (See Model 152T) ... 14-5
- Ch. RE-237 (See Model 182TFM) ... 14-5
- Ch. RE-242 (See Model 547A) ... 14-5
- Ch. RE-243 (See Model 240P) ... 14-5
- Ch. RE-244 (See Model 241P) ... 14-5
- Ch. RE-248 (See Model 250P) ... 14-5

ARVIN-Cont.

- Ch. RE-251 (See Model 242T) ... 14-5
- Ch. RE-252 (See Model 253T) ... 14-5
- Ch. RE-253 (See Model 280TFM) ... 14-5
- Ch. RE-254, 255, 256, 259 (See Model 241P) ... 14-5
- Ch. RE-261 (See Model 360TFM) ... 14-5
- Ch. RE-265 (See Model 264T) ... 14-5
- Ch. RE-267 (See Model 350P) ... 14-5
- Ch. RE-267-1, RE-267-2 (See Model 350-PB) ... 14-5
- Ch. RE-273 (See Model 356T) ... 14-5
- Ch. RE-274 (See Model 341T) ... 14-5
- Ch. RE-277, RE-277-1 (See Model 480TFM) ... 14-5
- Ch. RE-278 (See Model 540T) ... 14-5
- Ch. RE-278-1 (See Model 840T) ... 14-5
- Ch. RE-280 (See Model 446P) ... 14-5
- Ch. RE-281 (See Model 450T) ... 14-5
- Ch. RE-284 (See Model 460T) ... 14-5
- Ch. RE-287-1 (See Model 442-CB) ... 14-5
- Ch. RE-288-1 (See Model 482CFB) ... 14-5
- Ch. RE-292 (See Model 650-P) ... 14-5
- Ch. RE-297 (See Model 551T) ... 14-5
- Ch. RE-306 (See Model 554CCB) ... 14-5
- Ch. RE-307 (See Model 557T) ... 14-5
- Ch. RE-308 (See Model 553C) ... 14-5
- Ch. RE-310 (See Model 582CFB) ... 14-5
- Ch. RE-313 (See Model 580TFM) ... 14-5
- Ch. RE-323 (See Model 651T) ... 14-5
- Ch. RE-327 (See Model 655SWT) ... 14-5
- Ch. RE-333 (See Model 585FM) ... 14-5
- Ch. RE-342 (See Model 740T) ... 14-5
- Ch. RE-347 (See Model 746P) ... 14-5
- Ch. RE-348 (See Model 753T) ... 14-5
- Ch. RE-350 (See Model 758T) ... 14-5
- Ch. RE-352 (See Model 741T) ... 14-5
- Ch. RE-369 (See Model 848T) ... 14-5
- Ch. RE-372 (See Model 852P) ... 14-5
- Ch. RE-374 (See Model 858T) ... 14-5
- Ch. RE-375 (See Model 850T) ... 14-5
- Ch. RE-377 (See Model 851T) ... 14-5
- Ch. TE-272-1, -2 (See Model 3100TB) ... 14-5
- Ch. TE-276 (See Model 3160CM) ... 14-5
- Ch. TE-282 (See Model 4080T) ... 14-5
- Ch. TE-286 (See Model 4162CM) ... 14-5
- Ch. TE-289 (See Model 2122TM) ... 14-5
- Ch. TE-289-2, TE-289-3 (See Model 2120CM) ... 14-5
- Ch. TE-290 (See Model 2160) ... 14-5
- Ch. TE-300 (See Model 5204) ... 14-5
- Ch. TE-302, -1, -2, -3, -4, -5, -5A, -6 (See Model 5170CB) ... 14-5
- Ch. TE-315, -1, -2, -3, -4, -5, -5A, -6 (See Model 5210) ... 14-5
- Ch. TE-319, -1, -2 (See Model 6213TM) ... 14-5
- Ch. TE-319-3 (See Model 8211TB) ... 14-5
- Ch. TE-319-21 (See Model 8213TMA) ... 14-5
- Ch. TE-320 (See Models 5175, 5176) ... 14-5
- Ch. TE330, -1, -2, -3, -4, -5, -6 (See Model 6213TB-UHF) ... 14-5
- Ch. TE330-6 (See Model 8213TM-UHF) ... 14-5
- Ch. TE330-7 (See Model 8211TB-UHF) ... 14-5
- Ch. TE-331, -1, -2, -3, -4 (See Model 6175TM) ... 14-5
- Ch. TE 331-5 (See Model 6173TM) ... 14-5
- Ch. TE 331-6 (See Model 8171TM) ... 14-5
- Ch. TE332, -1, -2, -3, -4 (See Model 6173TM-UHF) ... 14-5
- Ch. TE332-4 (See Model 8179TM-UHF) ... 14-5
- Ch. TE332-5 (See Model 8171TB-UHF) ... 14-5
- Ch. TE-334 (See Model 5213TM) ... 14-5
- Ch. TE 337-1, -2, -3, -4, -31 (See Model 7210CB) ... 14-5
- Ch. TE340, -1, -2 (See Model 7276CB-UHF) ... 14-5
- Ch. TE 341, -1, -2, -3, -4, -5, -6, -41 (See Model 7210CB-UHF) ... 14-5
- Ch. TE355 (See Model 9211TM) ... 14-5
- Ch. TE-358, -1, -2, -3 (See Model 9210CB) ... 14-5
- Ch. TE 359-1 (See Model 9240CB-UHF) ... 14-5
- Ch. TE362 (See Model 9211TM-UHF) ... 14-5
- Ch. TE 363, -1, -2, -3 (See Model 9210CB-UHF) ... 14-5
- Ch. TE 364, -1 (See Model 9240CB-UHF) ... 14-5
- Ch. TE373 (See Model 9245CM-UHF) ... 14-5
- Ch. TE-379 (See Model 21-550KBU) ... 14-5
- Ch. TE382 (See Model 21-550KB) ... 14-5
- Ch. TE-393 "E" Series (See Model 21-554KMU) ... 14-5
- Ch. TE-386-UHF "E" Series (See Model 21-554KMU) ... 14-5

ASTATIC

- CB-1 Tel. UHF Conv.-Booster 224-3
- 9HM (Tel. UHF Conv.) ... 264-4

ASTORIA

- A-21, A-72, A-73L (Similar to Chassis) ... 182-3

ASTROSONIC

- (Also see Pentron) ... 121-4
- T-3 ... 748
- 748 ... 53-6

ATLAS

- AB-45 ... 14-5

AUDAR

- AV-7T ... 166-6
- MAS-4 "Bingo Amp" ... 26-6
- P-1A ... 5-10
- P-4A ... 19-3
- P-5 ... 5-11
- P-7 ... 4-3
- PR-6 ... 13-10
- PR-6A ... 19-4
- RE-8A ... 25-8
- Telvar SW-25, BMP-25 ... 2-5
- Telvar FM-12 ... 3-5
- Telvar RER-9 ... 6-2
- WC-7T ... 166-6

AUDIO DEVELOPMENT (ADC)

- 71-F ... 128-3

AUTOMATIC

- Tom Boy ... 27-4
- Tom Thumb Buddy ... 53-7
- Tom Thumb Camera-Radio ... 49-6
- Tom Thumb Jr. ... 26-7
- Tom Thumb Personal ATP ... 60-5
- B-44 ... 178-4
- C-51 ... 186-2
- C-54 ... 5-20
- C-60 ... 24-10
- C-60X (See Model C-60X—Set 24-10) ... 24-10
- C300 ... 102-1
- C-351 ... 148-4
- CL-152B, M ... 192-3
- CL-164B ... 192-3
- CM-333 ... 230-3
- D200 ... 104-3
- D-251 ... 174-4
- DM-132 ... 228-3
- F-100 ... 103-6
- F-151 ... 147-2
- F-790 ... 23-5
- M-86 ... 34-3
- M-90 ... 207-3
- MM-430 ... 229-3
- P-651 ... 173-4
- PM-236 ... 226-2
- S-551 ... 146-3
- TR-12 ... 228-4
- TV-P490 ... 81-3
- TV-707, TV-709, TV-710 ... 81-3
- TV-712 (See Model TV-707—Set 60-6) ... 60-6
- TV-1205 (See PCB 5—Set 106-1 and Model TV-1249—Set 103-5) ... 103-5
- TV-1249, TV-1250 ... 103-5
- TV-1294 (See PCB 5—Set 106-1 and Model TV-1249—Set 103-5) ... 103-5
- TV-1605 (See Model TV-1249—Set 103-5) ... 103-5
- TV-1615 (See Model TV-1249—Set 103-5) ... 103-5
- TV-1649, TV-1650, TV-1651 ... 143-5
- TV-1654 (See Model TV-1249—Set 103-5) ... 103-5
- TV-5006 ... 145-4
- TV-5020 ... 134-4
- TV-5061 ... 145-4
- TV-5077 ... 145-4
- TV-5116R ... 134-4
- TV-5160 ... 134-4
- TVX313 (See Model TV-707—Set 60-6) ... 60-6
- TVX404 (See Model TV-707—Set 60-6) ... 60-6
- 601, 602 (Series A) ... 13-11
- 601, 602 (Series B) ... 22-5
- 612X ... 1-34
- 613X (See Model 612X—Set 1-34) ... 1-34
- 614X, 616X ... 8-2
- 620 ... 12-3
- 640, 641 ... 22-6
- 660, 662, 666 ... 22-6
- 677 ... 22-7
- 720 ... 21-4

AVIOLA (Also see Record Changer Listing)

- 509 ... 7-3
- 601 ... 15-3
- 608 ... 15-3
- 612 ... 16-6
- 618 ... 16-6

BELL-AIR

- PL17C (Similar to Chassis) ... 149-13
- PL20C (Similar to Chassis) ... 149-13

BELL SOUND SYSTEMS

- B-23 ... 75-4
- PA3710A-P3 (Above Serial No. 78000) ... 225-6
- PA2915-B ... 249-4
- PA3725-B ... 244-3
- PA3750-B ... 250-5
- RC-47 (RE-CORD-O-FONE) ... 30-3
- RT-65 ... 130-4
- RT-65, B ... 171-3
- 3D ... 256-7
- 350 ... 148-5
- 352 ... 149-4
- 3745S ... 151-6
- 420 ... 150-4
- 440L, 440S "Belfone" ... 25-9
- 2075 ... 10-5
- 2122 ... 77-3
- 2122A, 2122AR ... 153-1
- 2122B ... 199-2
- 2122R ... 76-7
- 2145, A ... 161-2
- 2150, 2150R ... 256-8
- 2195, 2195MG ... 134-1
- 2199 ... 228-5
- 2200 ... 207-1
- 2210 ... 269-4
- 3706-M ... 227-3
- 3710A (Above Serial No. 78000) ... 225-6
- 3715 ... 22-8
- 3715-B ... 249-4
- 3717-MB, 3717MB3 ... 238-5
- 3723-MB, -MB3 ... 224-4
- 3724-B ... 272-9
- 3725-B ... 244-3
- 3728M ... 24-11
- 3728MB ... 235-3
- 3750 ... 31-5
- 3750-B ... 250-5

BELLTONE

- 500 ... 5-33

BELMONT (Also see Raytheon)

- A-6D10 ... 17-7
- 6A7A ... 10-7
- 6B7A ... 2-27
- 753F, M, W (Ch. C-19) ... 199-3
- 847-B ... 27-5
- 847-S "Facto-Meter" ... 28-3
- 951, 951W ... 136-6
- 1217, 1217B, 1217D ... 29-4
- 1217D (Late) ... 46-5
- 1518, 1519 ... 37-3
- 1521 ... 42-4
- 1524, 1525 ... 37-3
- 1531, 1533 ... 34-3
- 2001, 2002 ... 84-4
- 2020, 2021 ... 84-4

BENDIX

- CMBT21CS (Ch. T14-7) (See Model FB21CU—Set 213-2) ... 213-2
- CMBT21CU (Ch. T14-4) (See Model FB21CU—Set 213-2) ... 213-2
- CMTM21CS (Ch. T14-7) (See Model FB21CU—Set 213-2) ... 213-2
- CMTM21CU (Ch. T14-4) (See Model FB21CU—Set 213-2) ... 213-2
- C172 ... 134-5
- C174 (See Model 2051—Set 111-3) ... 111-3
- C176, B

CAPEHART-CORONADO

CAPEHART-Cont.

337RM (Ch. CT-39) [Ch. Series CX-33DX] (For TV Ch. only see Ch. CT-27-Set 160-2)

338X (Ch. CT-45) [Ch. Series CX-33DX] (See Ch. CT-45-Set 160-2)

339MX (Ch. CT-38) [Ch. Series CX-33DX] (See Ch. CT-38-Set 160-2)

340X, 341X (Ch. CT-45) [Ch. Series CX-33DX] (See Ch. CT-45-Set 160-2)

413P, 414P 67-6

461P, 462P 87-2

501P, 502P, 504P (For TV Ch. see Model 461P-Set 87-2, for Radio Ch. see Model 35P7-Set 135-4)

610P, 651P, 661P 95A-1

1002F, 1003M, 1004B (Ch. P-8) 135-4

1005B, M W (Ch. C-296) 132-5

1006B, M W (Ch. C-287) 132-5

1007AM (Ch. C-318) 150-5

3001, 3002 (Ch. C-272) [Ch. Series CX-30] 99A-1

3001, 3002 (Ch. C-272) [Ch. Series CX-30A-2] 99A-2

3004-M (Ch. C-268) [Ch. Series CX-31] (See Ch. CX-31-Set 93A-5)

3005 (Ch. C-268) [Ch. Series CX-32] (See Ch. CX-32-Set 93A-5)

3006-M (Ch. C-274) [Ch. Series CX-31] (See Ch. CX-31-Set 93A-5)

3007 (Ch. C-276) [Ch. Series CX-30] 99A-2

3008 (Ch. C-297) [Ch. Series CX-32] (See Ch. CX-32-Set 93A-5)

3011B, M, 3012B, M (Ch. C-281) [Ch. Series CX-33] 112-3

4001-M (Ch. C-268) [Ch. Series CX-31] (See Ch. CX-31-Set 93A-5)

4002-M (Ch. C-274) [Ch. Series CX-31] (See Ch. CX-31-Set 93A-5)

Ch. C-268 (See Model 3004-M)

Ch. C-272 (See Model 3001)

Ch. C-274 (See Model 3006-M)

Ch. C-276 (See Model 3007)

Ch. C-279 (See Model 3008)

Ch. C-281 (See Model 3012)

Ch. C-285 (See Model 327M)

Ch. C-286 (See Model 323M)

Ch. C-287 (See Model 1006B)

Ch. C-289 (Ch. Model 320)

Ch. C-292 (See Model 337M)

Ch. C-296 (See Model 336C)

Ch. C-297 (See Model TC-20)

Ch. C-298 (See Model 1177M)

Ch. C-299 (See Model 328)

Ch. C-303 (See Model 2120)

Ch. C-312 (See Model 10)

Ch. C-318 (See Model 1007AM)

Ch. CA-135 (See Model RP154B)

Ch. CR-36 (See Model TC-101)

Ch. CR-71 (See Model TC-62)

Ch. CR-76 (See Model T-522)

Ch. CR-79 (See Model RP153)

Ch. CR-85 (See Model P-213)

Ch. CR-93 (See Model CA)

Ch. CR-129 (See Model RP154B)

Ch. CR-147 (See Model RP254)

Ch. CR-148 (See Model 1P55)

Ch. CR-150 (See Model 3T55E)

Ch. CR-154 (See Model 2T55)

Ch. CT-27 (Ch. Series CX-33DX) (See Ch. CT-27-Set 160-2)

Ch. CT-37 (Ch. Series CX-33DX) (See Ch. CT-27-Set 160-2)

Ch. CT-38 (Ch. Series CX-33DX) 160-2

Ch. CT-39 (Ch. Series CX-33DX) (See Ch. CT-27-Set 160-2)

Ch. CT-45 (Ch. Series CX-33DX) 160-2

Ch. CT-47 (Ch. Series CX-33DX) (See Ch. CT-27-Set 160-2)

Ch. CT-52 (Ch. Series CX-36) (See Model 1T172M)

Ch. CT-57 (Ch. Series CX-36) (See Model 3C212B)

Ch. CT-58 (Ch. Series CX-36) (See Model 11W212M)

Ch. CT-74 (See Model 12F272M)

Ch. CT-75 (Ch. Series CX-37) (Also See PCB 113-Set 264-1 and Ch. CT-75-Set 203-4)

Ch. CT-77 (Ch. Series CX-37) (Also See PCB 113-Set 264-1 and Ch. CT-75-Set 203-4)

Ch. CT-99 (Ch. Series CX-37) (Also See PCB 113-Set 264-1 and Ch. CT-75-Set 203-4)

Ch. CT-108 (Ch. Series CX-37) (Also See PCB 113-Set 264-1 and Ch. CT-75-Set 203-4)

Ch. CT-110 (Ch. Series CX-37) (Also See PCB 113-Set 264-1 and Ch. CT-75-Set 203-4)

Ch. CT-112 (Ch. Series CX-37) (Also See PCB 113-Set 264-1 and Ch. CT-75-Set 203-4)

Ch. CT-115 (Ch. Series CX-37) (Also See PCB 113-Set 264-1 and Ch. CT-75-Set 203-4)

Ch. CT-116 (Ch. Series CX-37) (Also See PCB 113-Set 264-1 and Ch. CT-75-Set 203-4)

Ch. CT-121 (Ch. Series CX-37) (Also See PCB 113-Set 264-1 and Ch. CT-75-Set 203-4)

Ch. CT-122 (Ch. Series CX-37) (Also See PCB 113-Set 264-1 and Ch. CT-75-Set 203-4)

Ch. CT-123 (Ch. Series CX-37) (Also See PCB 113-Set 264-1 and Ch. CT-75-Set 203-4)

Ch. CT-124 (Ch. Series CX-37) (Also See PCB 113-Set 264-1 and Ch. CT-75-Set 203-4)

Ch. CT-126 (Ch. Series CX-37) (Also See PCB 113-Set 264-1 and Ch. CT-75-Set 203-4)

CAPEHART-Cont.

Ch. CT-127 (Ch. Series CX-37-1) (Also See PCB 113-Set 264-1 and Ch. CT-75-Set 203-4)

Ch. CT-128 (Ch. Series CX-37) (Also See PCB 113-Set 264-1 and Ch. CT-75-Set 203-4)

Ch. CT-129 (Ch. Series CX-37-1) (Also See PCB 113-Set 264-1 and Ch. CT-75-Set 203-4)

Ch. CT-130 (Ch. Series CX-37) (Also See PCB 113-Set 264-1 and Ch. CT-75-Set 203-4)

Ch. CT-131 (Ch. Series CX-37-1) (Also See PCB 113-Set 264-1 and Ch. CT-75-Set 203-4)

Ch. CT-134 (Ch. Series CX-37-1) (Also See PCB 113-Set 264-1 and Ch. CT-75-Set 203-4)

Ch. CT-143 (Ch. Series CX-37) (Also See PCB 113-Set 264-1 and Ch. CT-75-Set 203-4)

Ch. CT-144 (Ch. Series CX-37-1) (Also See PCB 113-Set 264-1 and Ch. CT-75-Set 203-4)

Ch. CT-146 (Ch. Series CX-37-1) (Also See PCB 113-Set 264-1 and Ch. CT-75-Set 203-4)

Ch. CTR-68 (See Model 10W212M)

Ch. P-7 (See Model 35P7)

Ch. P-8 (See Model 1002F)

Ch. Series CX-30, A (See Model 3001)

Ch. Series CX-30-A-2 (See Model 3001)

Ch. Series CX-31 (See Model 3004-M)

Ch. Series CX-32 (See Model 3005)

Ch. Series CX-33 (See Model 325F)

Ch. Series CX-33F (See Model 323M)

Ch. Series CX-33L (See Model 326-M)

Ch. Series CX-33DX (See Ch. CT-27)

Ch. Series CX-36 (See Model 1T172M)

Ch. Series CX-37 (See Ch. CT-75)

CAPITOL

D-17 30-4

T-13 28-5

U-24 29-6

CARDWELL, ALLEN D.

CE-26 14-6

ES-1 (Tel. UHF Conv.) 263-5

CAVENDISH (See Bell Air)

CAVALIER

4P3 266-4

5AT1 241-4

5B1 238-6

5C1 242-4

5R1 265-4

6A2 265-5

CBS-COLUMBIA (Also see Air King)

17C18 (Ch. 817, -1) 188-5

17C18 (Ch. 817-2) (See Model 18C18-Set 214-2)

17M06 (Ch. 750-3) (See Model 18C18-Set 214-2)

17M18 (Ch. 817, -1) 188-5

17M18 (Ch. 817-2) (See Model 18C18-Set 214-2)

17T18 (Ch. 817, -1) 188-5

17T18 (Ch. 817-2) (See Model 18C18-Set 214-2)

18C18 (Ch. 817-6) 214-2

18L18 (Ch. 817-6) (See Model 18C18-Set 214-2)

18M08 (Ch. 817-2) (See Model 18C18-Set 214-2)

18M08 (Ch. 817-6) 214-2

18M28 (Ch. 817-6) (See Model 18C18-Set 214-2)

18M28 (Ch. 817-6, -8) 255-3

18M38 (Ch. 817-6, -8) (See Model 18C18-Set 214-2)

18T18 (Ch. 817-6) 214-2

18T28 (Ch. 817-6) (See Model 18C18-Set 214-2)

18T28 (Ch. 817-6, -8) 255-3

20M18 (Ch. 820, -1) 188-5

20M28 (Ch. 820-2) (See Model 18C18-Set 214-2)

20T18 (Ch. 820-2) (See Model 18C18-Set 214-2)

21C11, B (Ch. 1021) 199-4

21C18 (Ch. 821) (See Model 17C18-Set 199-4)

21C21 (Ch. 1021) 199-4

21C31 (Ch. 1021) 199-4

21C41 (Ch. 1021) 199-4

21T11 (Ch. 1021) 199-4

22C06 (Ch. 751-3) (See Model 18C18-Set 214-2)

22C08 (Ch. 821-6, -6A) 214-2

22C11, B (Ch. 1021) (See Model 21C11-Set 199-4)

22C18 (Ch. 821-6, -6A) 214-2

22C21 (Ch. 1021) (See Model 21C11-Set 199-4)

22C28 (Ch. 751-3) (See Model 18C18-Set 214-2)

22C38 (Ch. 821-6, -6A) 214-2

22C38 (Ch. 1021) (See Model 21C11-Set 199-4)

22C38 (Ch. 751-3) (See Model 18C18-Set 214-2)

22C38 (Ch. 821-6, -6A) 214-2

22C38 (Ch. 822-1, -2, -3, -4, -10) 255-3

22C41 (Ch. 1021) 199-4

22C41 (Ch. 1021) 199-4

22C48, B (Ch. 821-4) (See Model 18C18-Set 214-2)

CBS-COLUMBIA-Cont.

22C48, B (Ch. 822-1, -2, -3, -4, -10) 255-3

22C58 (Ch. 822-1, -2, -3, -4, -10) 255-3

22C58 (Ch. 821-4) (See Model 18C18-Set 214-2) 230-5

22C68 (Ch. 1021-2) 230-5

22C68, B (Ch. 822-1, -2, -3, -4, -10) 255-3

22C68, B (Ch. 821-4) (See Model 18C18-Set 214-2) 230-5

22C78, B (Ch. 821-4) (See Model 18C18-Set 214-2) 230-5

22C88, B (Ch. 822-1, -2, -3, -4, -10) 255-3

22K38 (Ch. 821-20 and Radio Ch. 2A1) 255-3

22L18 (Ch. 821-6, -6A) 214-2

22M08, 22M18 (Ch. 821-6, -6A) 214-2

22M28 (Ch. 821-4) (See Model 18C18-Set 214-2) 230-5

22M38 (Ch. 821-4) (See Model 18C18-Set 214-2) 230-5

22M38 (Ch. 822-1, -2, -3, -4, -10) 255-3

22T11 (Ch. 1021) (See Model 21C11-Set 199-4) 199-4

22T18 (Ch. 821-6, -6A) 214-2

22T28, B (Ch. 821-4) (See Model 18C18-Set 214-2) 230-5

22T28, B (Ch. 822-1, -2, -3, -4, -10) 255-3

22T38, B (Ch. 822-1, -2, -3, -4, -10) 255-3

27C31 (Ch. 1027-1) 231-4

515A, 516A, 517A 223-4

525, 526 223-4

540, 541 211-4

545, 546 (See Model 540-Set 211-4) 207-2

2001 Tel. UHF Conv. 207-2

5220 261-5

Ch. 2A1 (See Model 22K38)

Ch. 750-3 (See Model 17M06)

Ch. 751-3 (See Model 22C06)

Ch. 817, -1 (See Model 17C18)

Ch. 817-2 (See Model 17C18)

Ch. 817-6 (See Model 18C18)

Ch. 817-6 (See Model 18M28)

Ch. 817-6 (See Model 18B28)

Ch. 820, 820-1 (See Model 20M18)

Ch. 820-2 (See Model 20M18)

Ch. 821 (See Model 21C18)

Ch. 821-3 (See Model 22C38)

Ch. 821-4 (See Model 22C48)

Ch. 821-6, -6A (See Model 22C08)

Ch. 821-20 (See Model 22K38)

Ch. 822-1, -2, -3, -4 (See Model 22C38)

Ch. 822-10 (See Model 22C38)

Ch. 1021 (See Model 21C11)

Ch. 1027-1 (See Model 27C31)

CENTURY (Also see Industrial Television)

226, 326 (Ch. IT-26R, IT-35R, IT-39R, IT-46R) 99A-7

721, 821, 921, 1021 (Ch. IT-21R) 97A-8

CENTURY (20th)

100X, 101, 104 12-5

200 21-5

300 21-6

CHALLENGER

CCB 63-4

CC18 67-7

CC30 68-6

CC60 70-3

CC618 66-4

CC64 65-4

HFB 257-3

20R 69-5

60R 62-7

200 69-5

600 62-7

CHANCELLOR (Also see Radionic)

35P 30-25

CHEVROLET

985792 6-5

985793 19-6

986067 19-6

986146 28-6

986240 75-5

986241 58-7

986388 104-5

986443 189-4

986515 149-5

986516 150-5

986668 219-2

986669 224-6

986771 262-4

CHRYSLER (See Mopar)

CISCO

1A5 37-4

9A5 20-3

CLARION

C100 1-5

C101 5-9

C102 9-6

C103 6-6

C104 1-4

C105 (See Model C-104-Set 1-4)

C105A 6-7

C108 (Ch. 101) 5-8

11011 17-8

11305 18-11

11411-N 30-5

11801 23-6

11802-V (See Model 11801-Set 23-6)

12110M 54-5

12310-W 31-6

12708 41-5

12801 61-5

CLARION-Cont.

13101 46-7

13201, 13203 62-8

14601 60-9

14965 66-5

16703 102-2

CLARK

PA-10 12-6

PA-10A 18-12

PA-20 13-2

PA-20A 18-13

PA-30 19-7

CLEARSONIC (See U. S. Television)

COLLINS AUDIO PRODUCTS

FMA-6 99-6

45-D 72-6

COLLINS RADIO

51J-3 260-6

75A-1 34-4

75A-2 171-4

COLUMBIA RECORDS

202 219-3

360 Series "B" 215-5

COMMANDER INDUSTRIES

Commander 3 Tube Record Player CD61P 19-9

CONCERTONE (See Recorder Listing)

CONCORD

IN434, IN435, IN436 (Similar to Chassis) 98-5

IN437 (Similar to Chassis) 121-2

IN549 (Similar to Chassis) 38-5

IN551 (Similar to Chassis) 38-6

IN554, IN555 (Similar to Chassis) 55-10

IN556, IN557 (Similar to Chassis) 109-7

IN559 (Similar to Chassis) 90-7

IN560 (Similar to Chassis) 109-7

IN561, IN562 (Similar to Chassis) 97-8

IN563 (Similar to Chassis) 136-10

IN819 (Similar to Chassis) 69-7

6C518 19-8

6C519 19-8

6F26W 19-10

6R3ARC 21-7

6T61W 22-11

7G26C 20-5

7R3APW 21-7

1-402, 1-403 45-6

1-441 48-5

1-501 (See Model 6E51B-Set 20-4)

1-504 55-6

1-509, 1-510 (See Model 6C518-Set 19-8) 49-7

1-516, 1-517 49-7

1-601, 1-602, 1-603 (See Model 7G26C-Set 20-5) 45-7

1-608 (See Model 6F26W-Set 19-10) (See Model 6T61W-Set 19-8) 22-11

1-611 46-8

1-1201 55-7

2-105 (See Model 315W-Set 53-8) 54-6

2-104 21-6

2-200, 2-201, 2-218, 2-219, 2-232, 2-235, 2-236, 2-237, 2-238, 2-239, 2-240 62-9

315WL, 315 WM 53-8

325WL, 325 WN (See Model 2-106-Set 54-6) 62-7

CONRAC

10-M-36, 10-W-36 (Ch. 36) (See Ch. 36) 36

11-B-36 (Ch. 36) (See Ch. 36) 36

12-M-36, 12-W-36 (Ch. 36) (See Ch. 36) 36

13-B-36 (Ch. 36) (See Ch. 36) 36

14-M-36, 14-W-36 (Ch. 36) (See Ch. 36) 36

15-P-36 (Ch. 36) (See Ch. 36) 36

16-B-36 (Ch. 36) (See Ch. 36) 36

17-P-39 (Ch. 39) (See Ch. 39) 39

18-M-39, 18-W-39 (Ch. 39) (See Ch. 39) 39

20-M-39, 20-W-39 (Ch. 39) (See Ch. 39) 39

21-B-39 (Ch. 39) (See Ch. 39) 39

22-P-39 (Ch. 39) (See Ch. 39) 39

23-M-39, 23-W-39 (Ch. 39) (See Ch. 39) 39

24-M-36 (Ch. 36) (See Ch. 36) 36

25-W-36 (Ch. 36) (See Ch. 36) 36

26-M-36 (Ch. 36) (See Ch. 36) 36

27-M-40, 27-W-40 (Ch. 40) (See Ch. 40) 40

28-B-40 (Ch. 40) (See Ch. 40) 40

29-P-40 (Ch. 40) (See Ch. 40) 40

30-M-40, 30-W-40 (Ch. 40) (See Ch. 40) 40

31-P-40 (Ch. 40) (See Ch. 40) 40

32-W-44, 32-W-44 (Ch. 44) (See Ch. 44) 44

33-B-44 (Ch. 44) (See Ch. 44) 44

34-P-44 (Ch. 44) (See Ch. 44) 44

35-M-61, 35-W-61 (Ch. 61) (See Ch. 61) 61

36-B-61 (Ch. 61) (See Ch. 61) 61

37-P-61 (Ch. 61) (See Ch. 61) 61

38-B-61, 38-M-61 (Ch. 61) (See Ch. 61) 61

39-M-61 (Ch. 61) (See Ch. 61) 61

40-M-64, 40-W-64 (Ch. 64) (See Ch. 64) 64

41-B-64 (Ch. 64) (See Ch. 64) 64

42-P-64 (Ch. 64) (See Ch. 64) 64

43-B-64, 43-M-64 (Ch. 64) (See Ch. 64) 64

43-C-64 110-4

43-D-64 110-4

43-E-64 110-4

43-F-64 110-4

43-G-64 110-4

43-H-64 110-4

43-I-64 110-4

43-J-64 110-4

43-K-64 110-4

43-L-64 110-4

43-M-64 110-4

43-N-64 110-4

43-O-64 110-4

43-P-64 110-4

43-Q-64 110-4

43-R-64 110-4

43-S-64 110-4

43-T-64 110-4

43-U-64 110-4

43-V-64 110-4

43-W-64 110-4

43-X-64 110-4

43-Y-64 110-4

43-Z-64 110-4

CONTINENTAL ELECTRONICS (See Skyweight)

CONVERSA-FONE

MS-5 (Master Station) SS-5 (Sub-Station) 16-7

CO-OP

6AWC2, 6AWC3, 6A47WCR, 6A47-WT, 6A47WTR 56-8

CORONADO

FA43-8965 (See Model 43-8965-Set 86-3) 182-3

K-72 (43-9031) 182-3

K-731 (43-9030) 182-3

RA37-43-9855 227-5

RA33-9856D 264-5

OSRA1-43-7755A, OSRA1-43-7755B 101-2

OSRA1-43-7901A 101-2

OSRA2-43-8230A 162-3

OSRA2-43-8515A 110-5

OSRA4-43-9876A 103-7

OSRA33-43-8120A 110-6

OSRA33-43-8135 (See Model 94RA-33-43-8130C-Set 82-3) 102-5

OSRA37-43-8360A 142-3

OSTV1-43-8945A 145-5

OSTV1-43-9005A, OSTV1-43-9006A, OSTV1-43-9014A 128-4

OSTV2-43-8950A 141-4

OSTV2-43-9010A 146-5

OSTV2-43-9010B 153-2

15RA1-43-7654A 147-3

15RA1-43-7902A 134-6

15RA2-43-8230A 162-3

15RA4-43-9876C, 15RA4-43-9877 (See Model OSRA4-43-9876A-Set 103-7) 142-3

15RA33-43-8245A, 15RA33-43-8246A 174-5

15RA33-43-8365 169-4

15RA37-43

- EMERSON—Cont.**
- 627 (Ch. 120078)..... 76-11
 - 628 (Ch. 120098B)..... 108-5
 - 629 (Ch. 120148) (See Model 631) Set 93A-6
 - 629B, 629C (120120)..... 119-6
 - 629D (Ch. 120124B)..... 116-5
 - 630 (Ch. 120099B)..... 108-5
 - 631 (Ch. 120109)..... 93A-6
 - 632 (Ch. 120096B)..... 93A-7
 - 633 (Ch. 120114)..... 93A-6
 - 634B (Ch. 120107B)..... 112-1
 - 635 (Ch. 120108)..... 92-4
 - 636A (Ch. 120106A)..... 99-7
 - 637, B, BC, C (Ch. 120110, B, BC, C)..... 97-4
 - 637A (Ch. 120095-B)..... 95A-3
 - 638 (Ch. 120087D) (See Model 57) —Set 76-11
 - 639 (Ch. 120138) (Also see PCB 9—Set 114-1)..... 87-6
 - 640 (Ch. 120121)..... 93-5
 - 641B (Ch. 120125B)..... 120-5
 - 642 (Ch. 120117A)..... 98-3
 - 643A (Ch. 120114)..... 97-4
 - 644, B, BC, C (Ch. 120113, B, BC, C)..... 91-4
 - 645 (Ch. 120115)..... 94-4
 - 646A (Ch. 120121A)..... 102-6
 - 646B (Ch. 120121B)..... 102-6
 - 647, B, BC, C (Ch. 120113, B, BC, C)..... 97-4
 - 648B (Ch. 120134B, G, H) (See PCB 48—Set 182-1) and Model 61B—Set 137-4
 - 649A (Ch. 120094A)..... 106-7
 - 650 (Ch. 120133C) (See Model 614—Set 97-4)
 - 650 [Ch. 120188]..... 113-2
 - 650B (Ch. 120188B) (See Model 650—Set 113-2)
 - 650D (Ch. 120123-B) (Also see PCB 48—Set 182-1)..... 109-3
 - 650F (Ch. 120138-B)..... 133-1A
 - 651B (Ch. 120120)..... 119-6
 - 651C (Ch. 120109)..... 93A-6
 - 651C (Ch. 120124)..... 116-5
 - 651D (Ch. 120124, B)..... 116-5
 - 652 (Ch. 120023B)..... 98-3
 - 653 (Ch. 120080B)..... 98-3
 - 653B (Ch. 120135-B)..... 159-5
 - 654 (Ch. 120188B)..... 113-2
 - 654B (Ch. 120188B) (See Model 654—Set 113-2)
 - 654D (Ch. 120123B) (Also see PCB 48—Set 182-1)..... 109-3
 - 654F (Ch. 120138B)..... 133-1A
 - 655B (Ch. 120123-B)..... 109-3
 - 655D (Ch. 120123B) (See Model 650D—Set 109-3)
 - 655F (Ch. 120138-B)..... 133-1A
 - 656B, 657B (Ch. 120122B)..... 111-5
 - 658B (Ch. 120124, B)..... 116-5
 - 658C (Ch. 120124, B) (See Model 629D—Set 116-5)
 - 660B (Ch. 120133B)..... 131-6
 - 661B (Ch. 120134B, G, H) (Also see PCB 48—Set 182-1)..... 137-4
 - 662B (Ch. 120127-B) (Also see PCB 18—Set 130-1)..... 125-6
 - 663B (Ch. 120138-B) (Also see PCB 18—Set 130-1)..... 125-6
 - 664B (Ch. 120133-B)..... 131-6
 - 665B (Ch. 120131-B and Radio Ch. 120130-B)..... 146-6
 - 666B (Ch. 120135B, G, H and Radio Ch. 120132B) (Also see PCB 27—Set 148-1)..... 133-5
 - 667B, 668B (Ch. 120134B, G, H) (Also see PCB 48—Set 182-1)..... 137-4
 - 669B (Ch. 120129B, D) (Also see PCB 24—Set 142-1 and PCB 47—Set 181-1)..... 126-5
 - 671B (Ch. 120137-B)..... 118-6
 - 671D (Ch. 120137D) (See Model 671B—Set 118-6)
 - 672B (Ch. 120078B)..... 131-7
 - 673B (Ch. 120133-B)..... 131-6
 - 674B (Ch. 120134B, G, H) (Also see PCB 48—Set 182-1)..... 137-4
 - 675B (Ch. 120129B, D) (Also see PCB 24—Set 142-1 and PCB 47—Set 181-1)..... 126-5
 - 676B (Ch. 120148, G, H) (Also see PCB 48—Set 182-1)..... 138-4
 - 676F (Ch. 120143B) (Also see PCB 50—Set 184-1)..... 148-6
 - 677B, 678B (Ch. 120134B, G, H) (Also see PCB 48—Set 182-1)..... 137-4
 - 679B (Ch. 120116-B)..... 142-7
 - 680B (Ch. 120144-B, G, H) (Also see PCB 48—Set 182-1)..... 138-4
 - 680D (Ch. 120140B)..... 128-6
 - 680D (Ch. 120144B, G, H) (See PCB 48—Set 182-1 and Model 676D—Set 138-4)
 - 681B (Ch. 120140B)..... 128-6
 - 681D (Ch. 120144B, G, H) (Also see PCB 48—Set 182-1)..... 138-4
 - 681F (Ch. 120140B, H) (Also see PCB 50—Set 184-1)..... 148-6
 - 684B, 685B (Ch. 120134B, G, H)..... 137-4
 - 686B (Ch. 120144B, G, H) (Also see PCB 48—Set 182-1)..... 138-4
 - 686D (Ch. 120140B, H) (Also see PCB 50—Set 184-1)..... 148-6
 - 686F (Ch. 120143B, H) (Also see PCB 50—Set 184-1)..... 148-6
 - 686L (Ch. 120142B) (Also see PCB 50—Set 184-1)..... 148-6
 - 687B (Ch. 120144B, G, H) (Also see PCB 50—Set 184-1)..... 148-6
 - 687L (Ch. 120142B) (Also see PCB 50—Set 184-1)..... 148-6
 - 688B, 689B, 690B (Ch. 120129B) (Also see PCB 47—Set 181-1)..... 126-5
 - 691B (Ch. 120145-B)..... 160-3
 - 692B, 693B, 694B (Ch. 120129B, D) (See PCB 24—Set 142-1, PCB 47—Set 181-1 and Model 669B—Set 126-5)

- EMERSON—Cont.**
- 695B (Ch. 120146-B)..... 162-5
 - 696B (Ch. 120144B, G, H) (See PCB 48—Set 182-1 and Model 676D—Set 138-4)
 - 696F (Ch. 120143B, H) (Also see PCB 50—Set 184-1)..... 148-6
 - 696L (Ch. 120142B) (Also see PCB 50—Set 184-1)..... 148-6
 - 697B (Ch. 120129B, D) (See PCB 24—Set 142-1, PCB 47—Set 181-1 and Model 669B—Set 126-5)
 - 698B (Ch. 120127B) (See PCB 18—Set 130-1 and Model 662B—Set 125-6)
 - 699D (Ch. 120160-B)..... 165-1A
 - 700B (Ch. 120153-B)..... 169-6
 - 700D (Ch. 120158-B)..... 166-9
 - 701B (Ch. 120153-B)..... 169-6
 - 701D (Ch. 120158-B)..... 166-9
 - 701F (Ch. 120143B) (See PCB 50—Set 184-1 and Model 676F—Set 148-6)
 - 702B (Ch. 120136-B)..... 159-5
 - 703B (Ch. 120097-B)..... 160-4
 - 704 (Ch. 120154-B)..... 184-6
 - 705A, B (Ch. 120155A, B)..... 208-4
 - 706B, 707B (Ch. 120156-B)..... 178-5
 - 708B (Ch. 120165-B) (See Model 706B—Set 178-5)
 - 709A (Ch. 120162-A)..... 167-6
 - 710B (Ch. 120146-B) (See Model 695B—Set 162-5)
 - 711B (Ch. 120164-B)..... 183-6
 - 711F (Ch. 120169-B)..... 206-4
 - 712B (Ch. 120164B)..... 183-6
 - 712F (Ch. 120169B)..... 206-4
 - 713B (Ch. 120156-B) (See Model 706B—Set 176-5)
 - 714B (Ch. 120153-B) (See Model 700B—Set 169-6)
 - 716D (Ch. 120163-D)..... 190-2
 - 716F (Ch. 120168-D) (See PCB 61—Set 195-1, PCB 71—Set 211-1 and Model 716D—Set 190-2)
 - 717D (Ch. 120163-D)..... 190-2
 - 717F (Ch. 120168-D) (See PCB 61—Set 195-1, PCB 71—Set 211-1 and Model 716D—Set 190-2)
 - 718B (Ch. 120150-B)..... 191-7
 - 719D (Ch. 120163-D)..... 190-2
 - 719F (Ch. 120168-D) (See PCB 61—Set 195-1, PCB 71—Set 211-1 and Model 716D—Set 190-2)
 - 720B (Ch. 120164-B)..... 183-6
 - 720D (Ch. 120169B)..... 206-4
 - 720F (Ch. 120169-D)..... 206-4
 - 721D (Ch. 120166-D) (Also see PCB 65—Set 202-1 and PCB 77—Set 218-1)..... 197-5
 - 722D (Ch. 120163-D)..... 190-2
 - 724B (Ch. 120151B)..... 209-2
 - 725A (Ch. 120149A)..... 209-2
 - 727D (Ch. 120168D) (See PCB 61—Set 195-1, PCB 71—Set 211-1 and Model 716D—Set 190-2)
 - 728B (Ch. 120166-D) (Also see PCB 65—Set 202-1 and PCB 77—Set 218-1)..... 197-5
 - 728D (Ch. 120166-D) (Also see PCB 65—Set 202-1 and PCB 77—Set 218-1)..... 197-5
 - 729B (Ch. 120170-B)..... 251-6
 - 731D (Ch. 120167-D and Radio Ch. 120152-B) (See PCB 65—Set 202-1 and Model 721D—Set 197-5)
 - 732B (Ch. 120169B)..... 206-4
 - 732D (Ch. 120164-B) (See Model 711B—Set 183-6)
 - 733F (Ch. 120169F and Radio Ch. 120152F)..... 206-4
 - 732G (Ch. 120185-B)..... 243-4
 - 734B (Ch. 120169B)..... 206-4
 - 736B (Ch. 120171-B) (See PCB 65—Set 202-1, PCB 77—Set 218-1 and Model 721D—Set 197-5)
 - 737A, B (Ch. 120172A, B)..... 207-3
 - 738B (Ch. 120150-B) (See Model 711B—Set 183-6)
 - 740D (Ch. 120173-D) (See PCB 65—Set 202-1, PCB 77—Set 218-1 and Model 721D—Set 197-5)
 - 741D (Ch. 120168-D) (See PCB 61—Set 195-1, PCB 71—Set 211-1 and Model 716D—Set 190-2)
 - 741F (Ch. 120182-D) (Also see PCB 103—Set 249-1 and PCB 117—Set 269-1)..... 235-5
 - 742B (Ch. 120169B)..... 206-4
 - 742E (Ch. 120185-B)..... 243-4
 - 743A (Ch. 120171-B) (See Model 736B)
 - 743B (Ch. 120171-B) (See PCB 65—Set 202-1, PCB 77—Set 218-1 and Model 721D—Set 197-5)
 - 744B (Ch. 120175-B)..... 231-6
 - 745B (Ch. 120176-B)..... 227-7
 - 746B (Ch. 120177-B)..... 228-9
 - 747 (Ch. 120178)..... 234-8
 - 748B (Ch. 120179-B)..... 263-7
 - 748C (Ch. 120203-B)..... 263-7
 - 750D (Ch. 120166-D) (See PCB 65—Set 202-1, PCB 77—Set 218-1 and Model 721D—Set 197-5)
 - 751D (Ch. 120168-D) (See PCB 61—Set 195-1, PCB 71—Set 211-1 and Model 716D—Set 190-2)
 - 752A, B (Ch. 120174-B)..... 243-4
 - 753D (Ch. 120180-D)..... 243-4
 - 753F (Ch. 120198-D)..... 243-4
 - 754D (Ch. 120176-B) (See Model 745B—Set 227-7)
 - 755A, B (Ch. 120174-B)..... 243-4
 - 756B (Ch. 120125-B) (See Model 641B—Set 120-5)
 - 757D (Ch. 120182-D) (Also see PCB 103—Set 249-1 and PCB 117—Set 269-1)..... 235-5
 - 757F (Ch. 120194-D) (See PCB 61—Set 195-1, PCB 71—Set 211-1, and Model 716D—Set 190-2)
 - 757I (Ch. 120168-D) (See PCB 61—Set 195-1, PCB 71—Set 211-1, and Model 716D—Set 190-2)
 - 758F (Ch. 120182-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)

- EMERSON—Cont.**
- 759C (Ch. 120195-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 785K—Set 235-5)
 - 760D (Ch. 120194-D)..... 243-4
 - 760F (Ch. 120194-D) (See PCB 61—Set 195-1, PCB 71—Set 211-1, and Model 716D—Set 190-2)
 - 760M (Ch. 120182-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 761C (Ch. 120180-D)..... 243-4
 - 762D (Ch. 120191-D)..... 243-4
 - 762F (Ch. 120190-D)..... 243-4
 - 764F (Ch. 120166-D) (See PCB 65—Set 202-1, PCB 77—Set 218-1 and Model 721D—Set 197-5)
 - 765D (Ch. 120173-D) (See Model 740D)
 - 766D (Ch. 120210-D)..... 243-4
 - 767A, B (Ch. 120192-B)..... 243-4
 - 767C (Ch. 120169-B) (See Model 711F—Set 206-4)
 - 768A (Ch. 120193-D)..... 243-4
 - 768C (Ch. 120197-B) (See Model 752A—Set 243-4)
 - 769F (Ch. 120173-D) (See Model 740D)
 - 770C (Ch. 120209-D)..... 243-4
 - 771A, B (Ch. 120192-B)..... 243-4
 - 771F (Ch. 120169-B) (See Model 711F—Set 206-4)
 - 771D (Ch. 120192-D)..... 243-4
 - 772A (Ch. 120193-B)..... 243-4
 - 773A (Ch. 120192-B)..... 243-4
 - 774A (Ch. 120193-B)..... 243-4
 - 775A, B (Ch. 120192-F and Radio Ch. 120181-B) (See Model 775A—Set 243-4)
 - 777B (Ch. 120204-B)..... 263-7
 - 778B (Ch. 120199B)..... 248-6
 - 779B (Ch. 120197-B)..... 243-4
 - 780A (Ch. 120171-B) (See Model 736B)
 - 781A, B (Ch. 120196-B) (Also see PCB 103—Set 249-1 and PCB 117—Set 269-1)..... 235-5
 - 781E (Ch. 120206-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 782D (Ch. 120166-D) (See Model 721D)
 - 783B (Ch. 120200B)..... 252-7
 - 784A (Ch. 120174-B)..... 243-4
 - 784E (Ch. 120197-B) (Also see PCB 103—Set 249-1 and PCB 117—Set 269-1)..... 235-5
 - 784G (Ch. 120197-D) (Also see PCB 103—Set 249-1 and PCB 117—Set 269-1)..... 235-5
 - 784K (Ch. 120197-B) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 784E—Set 235-5)
 - 784M (Ch. 120211-D) (See PCB 103—Set 249-1 and Model 741F—Set 235-5)
 - 785C, E (Ch. 120198-D)..... 243-4
 - 785K (Ch. 120198-D) (Also see PCB 103—Set 249-1)..... 243-4
 - 787A (Ch. 120179-B)..... 263-7
 - 787B (Ch. 120203-B)..... 263-7
 - 788B (Ch. 120201-B)..... 250-8
 - 789B (Ch. 120207-B)..... 258-6
 - 790B (Ch. 120147-B)..... 252-5
 - 791D (Ch. 120210-D)..... 243-4
 - 792D (Ch. 120206-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 793E (Ch. 120211-F) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 794A (Ch. 120193-B) (See Model 768A—Set 243-4)
 - 795C (Ch. 120192-B)..... 243-4
 - 796C (Ch. 120203-B)..... 263-7
 - 797B (Ch. 120204-B)..... 263-7
 - 797C (Ch. 120203-B)..... 263-7
 - 798B (Ch. 120205-B)..... 263-7
 - 799E (Ch. 120209-F)..... 243-4
 - 800B (Ch. 120159-B)..... 267-3
 - 801 (Ch. 120154-B) (See Model 704—Set 184-6)
 - 802B (Ch. 120159-B)..... 267-3
 - 802B (Ch. 120202D)..... 260-7
 - 809A (Ch. 12021-A)..... 266-5
 - 810B (Ch. 12022-B)..... 268-6
 - 1000C (Ch. 120206-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1001E (Ch. 120208-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1001G (Ch. 120211-E) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1002C (Ch. 120206-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1002D (Ch. 120206-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1002F (Ch. 120225-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1003 (See Model 1002—Set 16-14)
 - 1003E (Ch. 120208-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1003F (Ch. 120208-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1003G (Ch. 120211-F) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)

- EMERSON—Cont.**
- 1004C (Ch. 120206-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1004F (Ch. 120225-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1005E (Ch. 120208-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1005F (Ch. 120208-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1005G (Ch. 120211-F) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1006C (Ch. 120206-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1006F (Ch. 120225-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1007E (Ch. 120208-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1007G (Ch. 120211-F) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1008C (Ch. 120206-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1008E (Ch. 120206-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1008F (Ch. 120225-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1009E (Ch. 120208-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1009G (Ch. 120211-F) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1010C (Ch. 120206-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1011C (Ch. 120208-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1011G (Ch. 120211-F) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1012D (Ch. 120182-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1012F (Ch. 120223-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1013C (Ch. 120195-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1014D (Ch. 120182-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1015C (Ch. 120195-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 785K—Set 235-5)
 - 1018C, D (Ch. 120206-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1022C, D (Ch. 120206-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1023E (Ch. 120211-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1024C (Ch. 120206-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1025E (Ch. 120211-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1026C (Ch. 120206-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1027E (Ch. 120211-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1028C (Ch. 120206-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 10297C (Ch. 120211-F) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1036F (Ch. 120225-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1040D (Ch. 120182-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1040F (Ch. 120225-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1041E (Ch. 120211-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1042D (Ch. 120225-D) (See PCB 103—Set 249-1, PCB 117—Set 269-1 and Model 741F—Set 235-5)
 - 1044F (Ch. 120225-F

ESPEY—GENERAL ELECTRIC

ESPEY—Cont.

6611, 6612, 6613, 6614, 6615, 6630, 6631, 6632, 6634, 6635 (Ch. 97A) 15-16
7541 (Ch. FJ97) [See Model 651—Set 9-14] 90-7
7552 90-7

ESQUIRE

60-10, 65-4 14-11
511 157-3
517 [See Model 520—Set 1-13] 63-5
520 163-5
550 177-6

FADA

DL121T 200-5
DL121T8 [See Model 215C—Set 200-5]
G-925 89-6
HD821T [See Model UH21T—Set 228-10]
H212C [See Model UH21T—Set 228-10]
H218C [See Model UDL2100T—Set 228-10]
H274T, H276T 247-5
H321T [See Model UDL2100T—Set 228-10]
H421T [See Model UH21T—Set 228-10]
H442C 247-5
H522C 247-5
H621T [See Model UH21T—Set 228-10]
P80 27-9
P82 21-10
P100 27-10
P11 178-6
P130 13-7
P130 13-7
RC15, RC25 158-3
R-1025 114-4
R-1050 114-4
54C20 142-8
54C40 142-8
54T15 142-8
54T30 142-8
56C55 134-7
56C70 134-7
56T65 134-7
57C20, 57C30 [See Model 56C55—Set 134-7]
57C70 134-7
57T65 134-7
59C10 134-7
520T20 [See Model 56C55—Set 134-7]
51015 109-4
51020 109-4
51030 109-4
51055, 51055X 134-7
51060 134-7
51065 134-7
V230 74-3
UDL2100T 228-10
UH21T 228-10
U1700CD 244-4
2100C 228-10
21030C 228-10
V21T [See Model 215C—Set 200-5]
V21T6 [See Model 215C—Set 200-5]
V211CD 257-5
V213CD 257-5
V217C [See Model DL121T—Set 200-5]
V219C [See Model 215C—Set 200-5]
V271T, V273T 259-5
7C42 179-5
7C52 179-5
7T32 179-7
1774 204-4
1779 204-4
20C22 180-3
20T12 180-3
21C2 200-5
21T 200-5
21T3 [See Model DL121T—Set 200-5]
21T4 [See Model 215C—Set 200-5]
24C4, 24C5 259-5
24T2 200-5
24T10 180-3
173T, 175C, 177CD 200-5
215C 200-5
602 14-12
605, 606 Series 1-13
609, 610 Series 1-15
633 17-13
637 17-14
652 Series 1-23
700 32-7
711 28-10
740 177-7
775T [See Model 7T32—Set 177-7]
790 64-6
795 36-7
799 74-3
830 97-5
845 97-6
855 97-6
880 95A-5
899 74-3
925 89-6
930, 940 74-3
965 89-6
1000 Series 1-17
1001 17-15

FAIRMONT

30T14A-056 (Similar to Chassis) 119-3
38T12A-058 (Similar to Chassis) 109-1
317T3 (Similar to Chassis) 72-4
318T4 (Similar to Chassis) 85-3
318T4S (Similar to Chassis) 85-3
318T4-872 (Similar to Chassis) 85-3
318T6A (Similar to Chassis) 85-3
318T6A-950 (Similar to Chassis) 85-3
318T9A-900 (Similar to Chassis) 78-4
518T6A (Similar to Chassis) 85-3
518T9A-918 (Similar to Chassis) 78-4

FAIRMONT—Cont.

518T10A-916 (Similar to Chassis) 78-4
2318T6A-954 (Similar to Chassis) 85-3
2318T9A-912 (Similar to Chassis) 78-4

FARNSWORTH (Also see Record Changer Listing)

EC-260 7-15
EK-081, EK-082, EK-083, 26-13
EK-242, EK-243, E-263WL, E-264BL, EK-264WL, EK-265 7-15
EK-681 26-13
ET-060, ET-061, ET-063 6-11
ET-064, ET-065, ET-066 4-7
GK-100, GK-102, GK-103, GK-104 23-8
GK-111, GK-112, GK-114, GK-115 60-11
GK-140, GK-141, GK-142, GK-143, GK-144 24-18
GT-050, GT-051, GT-052 35-5
GT-060, GT-061, GT-064, GT-065 35-6
K-267, K-669 [See Model EC-260—Set 7-15]
Ch. 150 [See Model ET-060]
Ch. 152, 153 [See Model EC-260]
Ch. 156, 157 [See Model EK-081]
Ch. 159 [See Model ET-064]
Ch. 162 [See Model EC-260]
Ch. 170 [See Model GK-100]
Ch. 193 [See Model EK-081]
Ch. 194, 201, 216 [See Model GK-100]

FEDERAL MFG. CO.

104 (Select-A-Call) 18-17
135 (Select-A-Call) 11-7

FEDERAL TEL. & RADIO CORP.

102T1 [See Model 1030T—Set 8-13]
103T1, 1032 [See Model 1030T—Set 8-13]
1040T 23-9
1040T8 [See Model 1040T—Set 23-9]
1540T 8-13

FEDWAY

321MS39A (Similar to Chassis) 226-11
2321MS39A (Similar to Chassis) 226-11

FERRAR

C-81-B 17-16
T-61B 39-4
WR-11 15-10

FIRESTONE (AIR CHIEF)

4-A-2 (Code No. 297-6-LMMU-143) 14-4
4-A-3 (Code No. 297-6-LMFU-134) 4-10
4-A-10 (Code No. 297-7-RN228) 28-11
4-A-11 (Code No. 188-8-4A11) 41-7
4-A-12 (Code No. 213-8-8370) 49-8
4-A-15 (Code 177-7-4A15) 36-7
4-A-17 (Code No. 213-7-7170) 35-7
4-A-20 (Code 5-5-9000-A) 15-11
4-A-21 (Code No. 5-5-9001-A) 11-19
4-A-22X (Code No. 5-5-9001B) 11-19
4-A-23 (5-5-9003-A) 2-29
4-A-24 (Code 291-6-566) 13-5
4-A-25 (Code 291-6-572) 13-6
4-A-26 (Code 307-6-9030-A) 33-5
4-A-27 28-12
4-A-31 (Code No. 177-5-4A31) 11-20
4-A-37 (Code 177-5-4A37) 13-7
4-A-41 (Code 291-7-576) 52-8
4-A-42 (Code No. 177-7-4A42) 30-9
4-A-60 (Code No. 307-8-9047A) 38-6
4-A-61 (Code No. 332-8-1372T) 48-7
4-A-62, 4-A-63 67-10
4-A-64, 4-A-65 68-9
4-A-66 (Code No. 177-8-4A66) 74-4
4-A-68 (Code No. 332-8-143653) 53-11
4-A-69 (Code No. 155-8-85) 61-8
4-A-70 136-8
4-A-71 (Code 291-8-628) 59-9
4-A-78, 4-A-79 117-5
4-A-85 118-7
4-A-86 129-6
4-A-86 (Late) 144-4
4-A-87 119-7
4-A-88 132-6
4-A-89 118-7
4-A-92 154-4
4-A-95 144-4
4-A-96 [See Model 4-A-87—Set 119-7]
4-A-97, 4-A-98 147-5
4-A-101, 4-A-102 181-7
4-A-108 (Code 297-2-361) 191-8
4-A-110 215-6
4-A-112 [See Model 4-A-92—Set 154-4]
4A-113, 4A-114 224-8
4-A-115 219-5
4-A-118 (See Model 4-A-92—Set 154-4)
4-A-121, 4-A-122 244-5
4-A-127, 4-A-128 259-7
4-A-133 266-6
4-A-135, 4-A-136 266-7
4-B-1 (Code 7-6-PM15) 7-1
4-B-2 (Code 7-6-PM14) 18-18
4-B-6 (Code No. 177-7-PM18) 29-8
4-B-56 133-6
4-B-57 124-4
4-B-58 135-8
4-B-60 153-5

FIRESTONE (AIR CHIEF)—Cont.

4-B-61 155-6
4-B-62 152-6
4-B-63 (Similar to Chassis) 173-4
4-B-67 (Code 120-2-F152) 187-6
4-B-69 235-6
4-B-71 222-6
4-B-72 223-7
4-B-74 268-7
4-B-75 267-4
4-C-3 19-17
4-C-5 (Code 291-7-574) 19-17
4-C-6 31-6
4-C-13 (Code 332-8-140623) 66-9
4-C-16, 4-C-17 120-6
4-C-18 110-8
4-C-19, 4-C-20 170-7
4-C-21 (Code 120-2-C51-U) 15-7
4-C-22 247-6
4-C-24 250-6
13-G-3 86-5
13-G-4 (Code 347-9-2498) 73-5
13-G-5 (Code 291-9-651) 83-3
13-G-6 133-6
13-G-46, 13-G-47 140-6
13-G-48 143-6
13-G-51, 13-G-52 (Code 307-1-9202A, AA, B, BA) 193-4
13-G-56 152-7
13-G-57 158-4
13-G-107, 13-G-108 (Code 105-2-700100) 197-6
13-G-109, A (Code 105-2-700100, 105-2-700104) 197-6
13-G-110 (Code 334-2-MS29A) 180-4
13-G-110A (Code 334-2-MS31CA) 182-5
13-G-111, 13-G-112 (Code 334-2-MS31CA) 182-5
13-G-114, A (Code 105-2-8170) (Ch. 817) 198-6
13-G-115, 13-G-116 (Code 334-2-MS31CA) 182-5
13-G-117 (Code 105-2-8170) (Ch. 817) 198-6
13-G-119, 13-G-120 (Code 334-2-MS31CA) 182-5
13-G-121 (Code 105-2-8170) 194-1 and PCB 76—Set 217-11
13-G-122 (Code 105-2-700140) 197-6
13-G-124 (Code 105-2-82000) (See Model 13-G-107—Set 197-6)
13-G-125 (Code 105-2-8170) (See Model 13-G-107—Set 197-6)
13-G-127 (Code 334-3-MS31D) (See PCB 60—Set 194-1, PCB 76—Set 217-11 and Model 13-G-110A—Set 182-5)
13-G-128, 13-G-129, 13-G-130 230-6
13-G-132 230-6
13-G-134 (Code 105-4-82203) 250-9
13-G-145, 13-G-146 230-6
13-G-150 256-9
13-G-153 (See Model 13-G-155—Set 241-8)
13-G-155 241-8

FISHER

50-A 229-6
50-CB, -CM (50C Series) (C-50CH) 209-2
50-F 262-7
50-PR 262-8
50R, 50RT 231-7
70-A 263-8
70T 258-7

FLEETWOOD

600 209-4
610 248-7
700 243-5
710 246-5

FLUSH WALL

5P 26-14
5P (Revised) 252-8

FORD

FAC-18805-A 175-10
FAC-18805-A1 184-7
FAC-18805-B 167-7
FAC-18805-C (See Model M4A or Model 3MF) 208-6
FAD-18805-D 215-7
FAE-18805-A 255-6
FDA-18805-A1 255-6
FDA-18805-B1 236-5
FDA-18805-B-2 250-10
GF890, E (OA-18805-B) 109-5
M-1 (BA-18805-A1) 46-4
M-1A (OA-18805-A1) [See Model M-1—Set 46-4]
M-1A-1 (OA-18805-A1) 106-8
M-2 (1A-18805-A1) 132-7
M-4 (FAC-18805-A1) 184-7
M-4A (FAC-18805-C) [See Model M4—Set 184-7]
M-4B (FDA-18805-B1) 236-5
OA-18805-A1 (See Model M-1A or Model M-1A-1) 106-8
OA-18805-A2 135-9
OA-18805-B1 109-5
OBF (OA-18805-A1 [Serial No. 150,000 and below] [See Model M1—Set 46-4])
OBF (OA-18805-A1) [Serial No. 150,001 and up] [See Model M1A—Set 184-7]
OCF751-1 (1A-18805-D) 157-4
OMF (OA-18805-A2) 135-9
OZF (OA-18805-B) [See Model GF890—Set 109-5]
1A-18805-A1 132-7
1A-18805-A2 131-8
1A-18805-B (See Model ICF743—Set 132-7 or Model ICF743-1—Set 158-5)
1A-18805-D 157-4
1A-18805-E 157-4
1BF (1A-18805-A1) [See Model M-2—Set 132-7]
ICF743 (1A-18805-B) 133-7
ICF743-1 (1A-18805-B) 158-5
ICF751-2 (1A-18805-G) 157-4
1MF (1A-18805-A2) 131-8

FORD—Cont.

1SFT751-2 (1A-18805-G) [See Model ICF751-2—Set 157-4]
2BF (FAC-18805-A1) [See Model M4—Set 184-7]
2CF754 (FAC-18805-B) 167-7
2MF (FAC-18805-A) 175-10
3BF (FAD-18805-C) [See Model M-4—Set 184-7]
3MF (FAD-18805-C) 206-5
3MF1T (FAE-18805-A) 208-6
3SF755 (FAD-18805-D) 207-7
4BF (See Model M4B—Set 236-5)
4MF (FDA-18805-B-2) 250-10
4SF765 (FDA-18805-A) 255-6
6MF080 (51A-18805-A1) (Ch. 6CA1) 10-18
6MF780 (51A-18805-A1) 62-12
6MF780-E (51AF-18805) [See Model 6MF780—Set 62-12]
8A-18805 83-4
8A-18805-A 44-4
8A-18805-A1 46-4
8A-18805-A2 [See Model 9AF] 47-9
8A-18805-B (See Model 8MF980—Set 42-12 or Model 8MF980—Set 61-9)
8A-18805-B1 83-4
8C-18805-B 47-9
8C-18805-B1 (BA-18805B) 42-12
8MF881 (8C-18805B) 61-9
8MF980 (8A-18805B) 61-9
8MF983 (8A-18805-B1) [8MF983-E (BA-18805)] 83-4
8ZT (8C-18805-B) [See Model 8MF881—Set 47-9]
9BF (BA-18805-A1) [See Model M-1—Set 46-4]
9DF (8A-18805-A) [See Model 8072—Set 44-4]
9MF (8A-18805-A3) [See Model 8072—Set 44-4]
9ZT (8A-18805-A1) [See Model 8MF983—Set 83-4]
51A-18805-A1 [See Model 6MF080—Set 10-18 or Model 6MF780—Set 62-12]
51A-18805-B2 45-10
51AF-18805 (See Model 6MF780-E) 45-10
51B (8A-18805-B2) 44-4

FREED EISEMAN

46 54, 55, 56, 68 (Ch. 1620C) 113-1A
717 269-6

GALVIN (See Motorola)

GAMBLE-SKOGMO (See Coronado)

GAROD (Also see Majestic)

4A1, 4A-2 29-9
4B-1 45-6
5A-1 25-15
5A-2 5-28
5A-3 44-5
5A-4 40-6
5A-5 15-12
5D-3, 5D-2 12-12
5D-3A 10-16
5D-4, 5D-5 33-7
5RC-1 36-8
6A-2 28-13
6AU-1 5-29
6BU-1A "The Senator" 15-18
6DPS 6DPS-A 12-13
10T21, 10T22, 10T23, 10T24 60-12
10T25 10T25
10T220, 10T221, 10T222, 10T223 95A-4
11FMP 38-7
12T21, 12T22, 12T23, 12T24, 12T25, 12T26A, 12T27A, 12T27B, 12T27C, 12T27D 95A-4
15T26, 15T27 60-12
15T224, 15T225, 15T226, 15T227 95A-4
16CT4, 16CT5 (See Majestic Model 16CT4—Set 133-8)
19C6, 19CT (See Majestic Model 19C6—Set 133-8)
628 29-10
608 50-8
900TV, 910TV 50-7
1000TV, 1010TV 50-7
1042G, 1043G (See Majestic Model 12C4—Set 108-7)
1042T, 1043T 93A-7
110TVP, 1110TVP 93A-7
1200TV, 1210TVP 50-7
1244G, 1245G (See Majestic Model 12C4—Set 108-7)
1244T, 1245T 93A-7
1546G, 1547G (See Majestic Model 12C4—Set 108-7)
1546T, 1547T 93A-7
1548G, 1549G (See Majestic Model 12C4—Set 108-7)
1671 (98 Series) 97A-3
1671, 1672, 1673, 1674 (See Majestic Model 1671—Set 133-8)
1974, 1975 (See Majestic Model 1974—Set 133-8)
2042T, 2043T 93A-7
2546T 93A-7
2549T 93A-7
3912 TVFMP, 3915 TVFMP 95A-6

GARRARD (See Record Changer Listing)

GENERAL (Mutual Buying Syndicate)

17CG1, 17TV (Similar to Chassis) 149-13
12C101, 12C102, 12C108, 12C109, 12C109B, 12C109C 125-7
12K1 95A-6
18T1 96-4
12T3, 12T3B, 12T4, 12T4B 125-7
12T7 99A-5
14 35-8
14C102, 14C103 123-4
14T2, 14T3 123-4
16C103 123-4
16C104, 16C111 123-4
16C113 123-4
16C115, 16C116, 16C117 123-4
16T1, 16K2 161-1A
16T1, 16T2, 16T3, 16T4 123-4
16T5 [See Model 16T4—Set 123-4]
17C101, 17C102 123-4
17C103, 17C104, 17C105 [Also see PCB 32—Set 158-1] 141-6
17C107, 17C108, 17C109 [Also see PCB 32—Set 158-1] 141-6
17C110, 17C111 (Early "D" and "W" Versions) 180-5
17C112 [See PCB 32—Set 158-1 and Model 17C103—Set 141-6]
17C113 166-10
17C114 [See PCB 32—Set 158-1 and Model 17C103—Set 141-6]
17C115 166-10
17C117 [See Model 17C113—Set 166-10]
17C120 166-10
17C125 [See PCB 64—Set 201-1 and Model 21C201—Set 209-5]
17C126 [See PCB 64—Set 201-1 and Model 21C201—Set 209-5]
17C127 [See PCB 97—Set 242-1 and Model 21C115—Set 229-7]
17T1, 17T2, 17T3 [Also see PCB 32—Set 158-1] 141-6
17T4, 17T5, 17T6 [See PCB 32—Set 158-1 and Model 17C103—Set 141-6]
17T7 [See Model 17C113—Set 166-10]
17T10 [See Model 17C113—Set 166-10]
17T11 [See Model 17T10—Set 196-3]
17T11-UHF (For TV Ch. see Model 17T10—Set 196-3, for UHF Conv. see Model UHF-103—Set 209-5)
17T12 [See Model 17T10—Set 196-3]
17T12-UHF (For TV Ch. see Model 17T10—Set 196-3, for UHF Conv. see Model UHF-103—Set 209-5)
17T15, 17T17 [See PCB 32—Set 242-1 and Model 21C11—Set 229-7]
17T20 265-6
19C101 99A-6
20C103, 20C106 176-3
20C107 [See PCB 64—Set 201-1 and Model 21C201—Set 194-2]
20C107-UHF (For TV Ch. see PCB 64—Set 201-1 and Model 21C201—Set 194-2, for UHF Conv. see Model UHF-103—Set 209-5)
20C150, 20C151 153-6
20T2 176-3
21C103, 21C104 265-6
21C105 (See Model 17T20—Set 265-6)
21C114 [See PCB 97—Set 242-1 and Model 21C15—Set 229-7]
21C115 [See PCB 97—Set 242-1 and Model 21C15—Set 229-7]
21C117 [See PCB 97—Set 242-1 and Model 21C15—Set 229-7]
21C120, 21C121 [See PCB 97—Set 242-1 and Model 21C15—Set 229-7]
21C200 176-3
21C201 [Also see PCB 64—Set 201-1] 194-2
21C201-UHF (For TV Ch. see PCB 64—Set 201-1 and Model 21C201—Set 194-2, for UHF Conv. see Model UHF-103—Set 209-5)
21C202 [Also see PCB 64—Set 201-1] 194-2
21C202-UHF (For TV Ch. see PCB 64—Set 201-1 and Model 21C201—Set 194-2, for UHF Conv. see Model UHF-103—Set 209-5)
21C204 [Also see PCB 64—Set 201-1] 194-2
21C206 [Also see PCB 64—Set 201-1] 194-2
21C206-UHF (For TV Ch. see PCB 64—Set 201-1 and Model 21C206—Set 194-2, for UHF Conv. see Model UHF-103—Set 209-5)
21C208 [Also see PCB 64—Set 201-1] 194-2
21C208-UHF (For TV Ch. see PCB 64—Set 201-1 and Model 21C208—Set 194-2, for UHF Conv. see Model UHF-103—Set 209-5)
21C208U (See PCB 64—Set 201-1 and Model 21C208—Set 194-2)
21C208U-UHF (For TV Ch. see PCB 64—Set 201-1 and Model 21C208—Set 194-2, for UHF Conv. see Model UHF-103—Set 209-5)
21C210 [See PCB 64—Set 201-1 and Model 21C201—Set 194-2]
21C210-UHF (For TV Ch. see PCB 64—Set 201-1 and Model 21C201—Set 194-2, for UHF Conv. see Model UHF-103—Set 209-5)
21C214 [Also see PCB 64—Set 201-1] 194-2
21C214-UHF Tel. Rec. (For TV Ch. see PCB 64—Set 201-1 and Model 21C214—Set 194-2, for UHF Conv. see Model UHF-103—Set 209-5)
21C225, 21C226, 21C227, 21C228, 21C229, 21C230, 21C231, 21C232, 21C233 237-7

GENERAL ELECTRIC—Cont.

12C101, 12C102, 12C108, 12C109, 12C109B, 12C109C 125-7
12K1 95A-6
18T1 96-4
12T3, 12T3B, 12T4, 12T4B 125-7
12T7 99A-5
14 35-8
14C102, 14C103 123-4
14T2, 14T3 123-4
16C103 123-4
16C104, 16C111 123-4
16C113 123-4
16C115, 16C116, 16C117 123-4
16T1, 16K2 161-1A
16T1, 16T2, 16T3, 16T4 123-4
16T5 [See Model 16T4—Set 123-4]
17C101, 17C102 123-4
17C103, 17C104, 17C105 [Also see PCB 32—Set 158-1] 141-6
17C107, 17C108, 17C109 [Also see PCB 32—Set 158-1] 141-6
17C110, 17C111 (Early "D" and "W" Versions) 180-5
17C112 [See PCB 32—Set 158-1 and Model 17C103—Set 141-6]
17C113 166-10
17C114 [See PCB 32—Set 158-1 and Model 17C103—Set 141-6]
17C115 166-10
17C117 [See Model 17C113—Set 166-10]
17C120 166-10
17C125 [See PCB 64—Set 201-1 and Model 21C201—Set 209-5]
17C126 [See PCB 64—Set 201-1 and Model 21C201—Set 209-5]
17C127 [See PCB 97—Set 242-1 and Model 21C115—Set 229-7]
17T1, 17T2, 17T3 [Also see PCB 32—Set 158-1] 141-6
17T4, 17T5, 17T6 [See PCB 32—Set 158-1 and Model 17C103—Set 141-6]
17T7 [See Model 17C113—Set 166-10]
17T10 [See

GENERAL ELECTRIC—Cont.

● 21C240, UHF, 21C241, UHF, 21C242, UHF, 21C243, UHF, 21C244, UHF 264-7

● 21T1 (Also see PCB 64—Set 201-1) 194-2

● 21T1-UHF (For TV Ch. see PCB 64—Set 201-1 and Model 21T1—Set 194-2, for UHF Conv. see Model UHF-103—Set 209-5)

● 21T1U (See PCB 64—Set 201-1 and Model 21T1—Set 194-2)

● 21T1U-UHF (For TV Ch. see PCB 64—Set 201-1 and Model 21T1—Set 194-2, for UHF Conv. see Model UHF-103—Set 209-5)

● 21T2 196-3

● 21T3 (See Model 21T1—Set 194-2)

● 21T3-UHF (For TV Ch. see PCB 64—Set 201-1 and Model 21T1—Set 194-2, for UHF Conv. see Model UHF-103—Set 209-5)

● 21T4, 21T5 184-8

● 21T6 (See Model 21T1—Set 194-2)

● 21T6-UHF (For TV Ch. see PCB 64—Set 201-1 and Model 21T1—Set 194-2, for UHF Conv. see Model UHF-103—Set 209-5)

● 21T7, 21T8 225-10

● 21T11, 21T12 (See PCB 97—Set 242-1 and Model 21C115—Set 229-7)

● 21T14 (Also see PCB 97—Set 242-1)

● 21T20, 21T21 237-7

● 21T22, 21T23, 21T24, 21T25 265-6

● 21T26, UHF, 21T27, UHF 264-7

● 21T34 (See Model 17T20—Set 265-6)

● 24C101 152-8

41, 42, 43, 44, 45 32-8

50 7-16

60, 62 36-9

64, 65 98-4

66, 67 76-12

100, 101 6-13

102, 102W 41-8

103, 105 6-13

106 8-14

107, 107W 41-8

113 51-7

114, 114W, 115, 115W 41-8

118, 119M, 119W 39-7

123, 124 97-7

131 (See Model 118—Set 39-5)

135, 136 81-8

140 30-10

143 75-9

145 66-13

150 56-11

160 56-12

165 89-7

180 20-11

186-4 57-7

200, 201, 202, 203, 205, 205M 13-15

210, 211, 212 51-8

218, 218 "H" 121-5

219, 220, 221 4-1

226 91-5

230 (See Kaiser-Frazer Model 200001—Set 35-13)

250 4-13

254 32-9

260 15-13

262 23-10

280 18-19

304 32-10

321 3-24

324 64-7

326 30-11

328 64-7

329, 330 (See Model 324—Set 64-7)

354, 355 33-9

356, 357, 358 37-6

376, 377, 378 45-11

400, 401 118-8

404, 405 121-6

408 116-6

409 176-4

410 121-6

411 118-8

412 189-9

412F 211-6

417 175-11

414F 211-6

415 175-11

415F 211-6

416F 211-6

417 16-15

419 231-8

422, 423 154-5

424, 425 233-2

427, 428, 429 270-5

430 175-11

431 241-9

431A (See Model 431—Set 241-9)

432 241-9

432A (See Model 432—Set 241-9)

440 246-6

442, 443, 444 270-5

450, 451, 452 (See Model 424—Set 233-2)

500, 501 98-4

502 35-9

505, 506, 507, 508, 509 98-4

510, 511 120-7

510F, 511F, 512F, 513F 23-7

514 198-7

515F, 516F, 517F, 518F 143-7

521, 522 114-5

521F, 522F 143-7

530 98-4

535 151-7

542, 543 198-7

546, 547, 548, 549 191-9

551, 552 201-4

555, 555G, 556 250-11

557, 558, 559 (See Model 560—Set 249-7)

560, 561 249-7

564, 565, 566 251-7

580, 581, 582 270-6

600 109-6

601, 603, 604 115-3

605, 606 145-6

GENERAL ELECTRIC—Cont.

607, 608 (See Model 605—Set 145-6)

610, 611 147-7

612, 613 231-9

614, 615 199-6

620, 621, 622 262-9

625, 626 (See Model 612—Set 231-9)

630, 631, 632 261-7

640, 641 (See Model 614—Set 199-6)

740 101-3

741 157-6

752, 753 123-3

754 167-8

755 130-6

756 167-8

757 (See Model 755—Set 130-6)

● 800A, B, C, D (See Model 805—Set 78-7)

● 802 91A-7

● 803 97A-4

● 805, 806, 807, 809 Series 78-7

● 810 53-12

● 811 63-9

● 814 69-9

● 815 97A-5

● 817 78-7

● 818 95A-7

● 821 40A 122-4

● 830 Early 81-9

● 835 Early 81-9

● 840 81-9

● 901 97A-5

● 910 97A-5

GENERAL IMPLEMENT 37-7

9A5

GENERAL INDUSTRIES (See Changer and Recorder Listings)

GENERAL INSTRUMENT (Also see Recorder Changer Listing)

63A, 64 Tel. UHF Conv. 232-7

GENERAL MOTORS CORP. (GMC) 93-6

2233029

GENERAL TELEVISION

1A5, 2A5, 3A5, 5A5 (Ch. 1-1) [2-21]

485 27-11

585G, 585Y 98A5 36-10

9A5F 3-21

15A5 (Ch. 1-1) 1-21

17A5 5-22

19A5 (Ch. 1-1) 1-21

21A4 12-14

22A5C 13-19

23A6 14-14

2486 37-8

2585 26-15

2685 29-11

27C5 36-11

GIFILLAN

56A, 56B 1-27

56BC1, 56BCR (See Model 56A—Set 1-27)

56C, 56D 1-27

56E (See Model 56A—Set 1-27)

58M, 58W 45-12

64A, 66AM 8-16

64B "The Overland" 8-17

66D, 66DM 8-16

66P, 66PM "El Dorado" 9-15

68B-D 46-10

68F 46-11

68-48 61-10

86C, 86P, 86U (86 Series) 26-16

108-48 59-40

GLOBE

58P1 18-20

64B1 20-12

6D1 20-13

6P1 20-12

6U1 20-13

7CP-1 28-14

51 19-18

62C 19-19

85 49-9

454 40-9

456 41-7

457 39-7

500 21-18

517 21-18

551 16-16

552 27-13

553 28-15

559 20-18

GODFREY

6AD 28-17

65M 28-17

GONSET

3-30 Meter Converter 61-11

10-11 Meter Converter 31-9

ATB-3 70-5

NSA-20 73-6

B. F. GOODRICH (Also see Mantola)

92-523, 92-524, 92-525, 92-526, 92-527, 92-528 148-7

GOTHAM

● 319 209-6

● 323 251-8

GRANCO

CTU UHF Conv. 217-6

LCU UHF Conv. 251-9

ATU (Tel. UHF Conv.) 265-7

W. T. GRANT (See Grantline)

GRANTLINE

300 (Series B) 9-16

500, 501 (Series A) 9-17

501 9-17

504-7 21-19

508-7 34-8

GRANTLINE—Cont.

510-A 24-19

605, 616 2-17

641 12-15

651 11-9

5610 35-11

6547 11-10

GROMMES

LJ-2 260-8

50PG, 51PG 263-6

50PG2 206-6

100BA 189-10

517PS 190-3

205PA 191-10

205PA 192-10

210PA 260-3

215BA 198-8

HALLICRAFTERS (Also see Echophone)

A-84 (Run 1) 209-7

ATCL-10, -11 (Run 1) 225-11

CA-2, CA-2A 30-12

CA-4 36-13

S-38 3-7

S-38B 121-7

S-38C (Run 2) 190-4

S-42 2-19

S-40A 33-10

S-40B 122-4

S-41W, S-41W 10-19

S-47 46-12

S-51 40-8

S-52 48-9

S-53 39-8

S53A, AU 171-5

S-55, S-56 55-9

S-58 57-8

S-59 58-10

S-72 82-6

S-72L 173-6

S-76, S-76U 143-9

S-77 146-7

S-78 124-5

S-78A (Run 1) 180-6

S-80 162-6

S-81 164-11

S-82 167-9

ST-74 125-8

ST-83 218-5

SX-42 44-6

SX-43 45-13

SX-52 61-12

SX-71 111-6

● T-54 (Early) 48-10

● T-54 (Late) 91-6

● T-60 63-10

● T-61, T-64, T-67 (Also see PCB 32—Set 158-1) 65-7

● T-68 123-10

TW-25 (Runs 1 and 2) 224-9

TW-500 (Runs 1 and 2) 251-10

TW-600 (Runs 1 and 2) 251-10

TW-1000 (Run 1) 221-5

SR10 130-7

SR10A (Run 1) 155-7

SR10A (Run 4) [See Model SR10A (Run 1)—Set 155-7]

SR11, SR12, SR13, SR14 129-7

SR18, SR19, SR20, SR21, SR22 (See Model SR11—Set 129-7)

SR2 168-7

SR30, A, SR31, A, SR32, A, SR33, A, SR34, 170-8

SR50, SR51, SR52 179-6

SR100A (Run 4) [See Model SR10A (Run 1)—Set 155-7]

SR230, SR231, SR232 (Run 1) 127-8

BR40, BR40C 181-7

● 17T3108, M, W (Ch. A1600D) 253-7

400, 406, 409, 410, 411, 412 48-10

● 505 (Early) 48-10

505 (Late) [See Model T-54 (Late)—Set 91-6]

● 506 (Early) [See Model 505 (Early)—Set 48-10]

● 506 (Late) 91-6

● 509, 510 (Also see PCB 32—Set 158-1) 65-7

● 511 96-5

● 512C, 513 80-7

● 514 91-6

● 515 80-6

● 518, 519, 520 92-3

● 520E 80-7

● 521 92-3

● 521E 80-7

● 524 80-7

● 600, 601, 602, 603, 604, 605, 606 107-5

611, 612 250-12

● 680, 681 113-3

● 690 113-3

● 715, A 113-3

● 716 (See Model 680—Set 113-3)

● 730, 731 (Run 1) [See Model 680—Set 113-3]

● 740, 741 (Run 1) [See Model 680—Set 113-3]

● 745 105-4

750, 751 105-4

760, 761 105-4

805, 806 136-9

● 810 136-9

● 810A 124-6

● 810C (See Model 805—Set 136-9)

● 811 124-6

● 815 124-6

● 818, 820 124-6

● 821 (See Model 810A—Set 124-6)

● 822 124-6

● 832, 833 121-1A

● 860, 861 124-6

● 870, 871 (See Model 810A—Set 124-6)

● 880 (See Model 810A—Set 124-6)

● 1000 (Ch. W1000D) 180-7

● 1001 (Ch. F1100D) [See Model 1002—Set 169-7]

● 1002, 1003, 1004 (Ch. F1100D) 169-7

● 1005, 1006 (Ch. A1100D) 177-8

● 1007 (Ch. F1100D) 169-7

● 1008 (Ch. X1000D) 180-7

● 1010P (Ch. A-1200D, K1200D, W1200D) 188-6

HALLICRAFTERS—Cont.

● 1012P (Ch. A-1200D, K1200D, W1200D) 188-6

● 1013C (Ch. F1200D) 188-6

● 1015, 1016, 1017, 1018, 1019 (Ch. A1100D) 177-8

● 1019 (Ch. X1000D) 180-7

● 1021P (Ch. D1200D, L1200D, X1200D) 188-6

● 1022C (Ch. G1200D) 188-6

● 1025 (Ch. C1000D) 172-4

● 1026P (Ch. D1200D, L1200D, X1200D) 188-6

● 1027C (Ch. G1200D) 188-6

● 1050, A (Ch. A11200D) (Also see PCB 81—Set 222-1) 211-7

● 1051P, 1052P (Ch. P1200D) (See PCB 75—Set 216-1 and Model 1010P—Set 188-6)

● 1053P, 1054P (Ch. R1200D) (See PCB 75—Set 216-1 and Model 1010P—Set 188-6)

● 1055C, 1056C (Ch. T1200D) (See PCB 75—Set 216-1 and Model 1010P—Set 188-6)

● 1060C, 1061C (Ch. T1200D) (See PCB 75—Set 216-1 and Model 1010P—Set 188-6)

● 1062C, 1063C (Ch. J1200D) (See PCB 75—Set 216-1 and Model 1010P—Set 188-6)

● 1072 (Ch. AG1200D) 211-7

● 1072A (Ch. AR1200D) 211-7

● 1074 (Ch. AG1200D) 211-7

● 1074A (Ch. AR1200D) 211-7

● 1074AT (Ch. AY1200D) (Also see PCB 81—Set 222-1) 211-7

● 1075 (Ch. AG1200D) 211-7

● 1075A (Ch. AR1200D) 211-7

● 1075AT (Ch. AY1200D) (Also see PCB 81—Set 222-1) 211-7

● 1077 (Ch. AH1200D) 211-7

● 1078 (Ch. AG1200D) 211-7

● 1078A (Ch. AR1200D) 211-7

● 1078AT (Ch. AY1200D) (Also see PCB 81—Set 222-1) 211-7

● 1081, A (Ch. AJ1200D) (Also see PCB 81—Set 222-1) 211-7

● 1081B (Ch. AZ1200D) (See PCB 81—Set 222-1 and Model 1050—Set 211-7)

● 1081C (Ch. BA1200D) (See PCB 81—Set 222-1 and Model 1050—Set 211-7)

● 1081D (Ch. AZ1200D) (See PCB 81—Set 222-1 and Model 1050—Set 211-7)

● 1081E (Ch. AZ1200D) (See PCB 81—Set 222-1 and Model 1050—Set 211-7)

● 1085A (Ch. AJ1200D) (Also see PCB 81—Set 222-1) 211-7

● 1085B (Ch. AZ1200D) (See PCB 81—Set 222-1 and Model 1050—Set 211-7)

● 1085C (Ch. BA1200D) (See PCB 81—Set 222-1 and Model 1050—Set 211-7)

● 1085D (Ch. AZ1200D) (See PCB 81—Set 222-1 and Model 1050—Set 211-7)

● 1085E (Ch. BA1200D) (See PCB 81—Set 222-1 and Model 1050—Set 211-7)

● 1088A (Ch. AJ1200D) (Also see PCB 81—Set 222-1) 211-7

● 1088B (Ch. AZ1200D) (See PCB 81—Set 222-1 and Model 1050—Set 211-7)

● 1088C (Ch. BA1200D) (See PCB 81—Set 222-1 and Model 1050—Set 211-7)

● 1088D (Ch. AZ1200D) (See PCB 81—Set 222-1 and Model 1050—Set 211-7)

● 1092 (Ch. AZ1200D) (See PCB 81—Set 222-1 and Model 1050—Set 211-7)

● 1111P (Ch. A1200D) 188-6

● 1113P (Ch. D1200D) 188-6

1621, 1622 (Run 1) 253-8

● 14808 (Ch. R900D) 167-10

● 17804C 155-8

● 17810A 155-8

● 17811-H 156-6

● 17812, 17813, 17814, 17815-H 155-8

● 17816, 17817 156-6

● 17819 (Ch. Set 222-1) 155-8

● 17824 155-8

● 17824-A 165-6

● 17825 (See Model 17804C—Set 155-8)

● 17829 (Ch. F1100D) [See Model 1000—Set 169-7]

● 17838 155-8

● 17848, 17849, 17850 155-8

● 17860-H, 17861-H 156-6

● 17905 (See Model 17810—Set 152-9)

● 17906 165-6

● 17908 (See Model 17824—A—Set 165-6)

● 17922 (See Model 17824—A—Set 165-6)

● 17930, 17931, 17932, 17933, 17934 165-6

● 20823 (Ch. M900D) 167-10

● 20823B (Ch. 900D) 167-10

● 20823C 165-6

● 20882 155-8

● 20990, 20990S, 20994 154-6

● 21923 165-6

● 21928 165-6

● 21940 165-6

● 21981 165-6

Ch. A1100D [See Model 1005]

Ch. A1200D [See Model 1010P]

Ch. A1600D [See Model 17T3108]

Ch. AG1200D [See Model 1072]

Ch. AH1200D [See Model 1077]

Ch. AJ1200D [See Model 1081]

Ch. AL1200D [See Model 1050]

Ch. AR1200D [See Model 1072A]

Ch. AX1200D [See Model 1092]

Ch. AY1200D [See Model 1074AT]

Ch. AZ1200D [See Model 1081B]

Ch. BA1200D [See Model 1081C]

Ch. D1200D [See Model 1021P]

Ch. F1200D [See Model 1013C]

HALLICRAFTERS—Cont.

Ch. G1200D [See Model 1022C]

Ch. J1200D [See Model 1062C]

Ch. K1200D [See Model 1010P]

Ch. L1200D [See Model 1021P]

Ch. P1200D [See Model 1051P]

Ch. R1200D [See Model 1053P]

Ch. T1200D [See Model 1055C]

Ch. W1000D [See Model 1000]

Ch. W1200D [See Model 1010P]

Ch. X1000D [See Model 1008]

Ch. X1200D [See Model 1021P]

Ch. X1200D [See Model 1019]

HAMILTON ELECTRONICS (See Olympic)

HAMMARLUND

HQ-129-X 8-18

SP-400-X 10-20

HARVEY-WELLS

AT-3B-6, AT-3B-12 32-11

ATR-3-6, ATR-2-12 36-14

HEATH

HBR-5 24-20

HOFFMAN

A-200 (Ch. 103) 4-23

A-201 (Ch. 119) 11-11

A-300 4-41

A-309 (Ch. 119) 11-11

A-401 (Ch. 102) 11-12

A-500 (Ch. 107) 4-35

A-501 (Ch. 108ST) 3-34

A-700 (Ch. 1105) 12-16

B-400 17-17

B-1000 20-14

C-501 48-19

C-502 51-9

C-503 30-9

C-504 (Ch. 123) 47-10

C-506, C-507 49-10

C-511 48-11

C-512 51-9

C-513 50-9

C-514 47-10

C-515 61-13

C710 (Ch. 133) 54-9

C1006, C1007 54-9

● CT-800, CT-801, CT-900, CT-901 63-11

● 7B104 (Ch. 190, B) 201-5

● 7B1108 (Ch. 210, M) 205-5

● 7B1109 (Ch. 190, B) 205-5

● 7B1138 (Ch. 212, M) 194-4

● 7B128 (Ch. 212) [See Model 7B1138—Set 194-4]

● 7B141, U (Ch. 300-17) [Also see PCB 108—Set 256-1] 236-6

● 7B157 (Ch. 306-17) 254-6

● 7B303 (Ch. 190, B) 201-5

● 7M103 (Ch. 190, B) 201-5

● 7M109 (Ch. 200) 205-5

● 7M109B (Ch. 210, M) 205-5

● 7M112 (Ch. 202) 205-5

● 7M113 (Ch. 212, M) 194-4

● 7M127 (Ch. 212) [See Model 7B1138—Set 194-4]

● 7M140, U (Ch. 300-17) [Also see PCB 108—Set 256-1] 236-6

● 7M156, U (Ch. 301-17) 254-6

● 7M302 (Ch. 190, B) 201-5

● 7M303 (Ch. 190, B) 201-5

● 7P1118 (Ch. 210, M) 205-5

● 7P1148 (Ch. 212, M) [See Model 7B1138—Set 194-4]

● 7P304 (Ch. 190, B) 201-5

● 208102 (Ch. 183T) 168-8

● 208103 (Ch. 183T) 168-8

● 208501 (Ch. 183T) 168-8

● 20M101 (Ch. 183T) 168-8

● 20M101F (Ch. 194) 201-5

● 20M500 (Ch. 183T) 168-8

● 20P534 (Ch. 183T) 168-8

● 218107 (Ch. 191, B) 201-5

● 218116 (Ch. 196, M) 195-8

● 218122 (Ch. 211, M) 194-4

● 218134 (Ch. 211) [See Model 218122—Set 194-4]

● 218135 (Ch. 194) [See Model 218116—Set 195-8]

● 218144, U (

HOFFMAN-LEAR

HOFFMAN-Cont.
21B911 (Ch. 375-21) [See PCB 108-Set 256-1 and Model 21B144-Set 236.6]
21M106 (Ch. 191, B) 201-5
21M115 (Ch. 196, M) 194-8
21M121 (Ch. 211, M) 194-9
21M133 (Ch. 211) [See Model 21B122-Set 194.4]
21M136 (Ch. 196) [See Model 21B116-Set 195.8]
21M143, U (Ch. 300-21) [Also see PCB 108-Set 256-1]
21M146, U (Ch. 401-21) 249-8
21M153, U (Ch. 301-21) 254-6
21M160, U (Ch. 406-21) 250-13
21M160A, U (Ch. 406-21) [See Model 21M160-Set 250-13]
21M163, U (Ch. 301-21) [See Model 21B154-Set 254.6]
21M163X, U (Ch. 301X-21) [See Model 21B154-Set 254.6]
21M166, U (Ch. 302) 254-6
21M166A, U (Ch. 302) [See Model 21M166-Set 254.6]
21M300 (Ch. 211, B) 201-5
21M305 (Ch. 211, B) 205-5
21M305B (Ch. 211, M) 194-4
21M308 (Ch. 196M, T) 195-8
21M314 (Ch. 211T) [See Model 21B122-Set 194.4]
21M317, U (Ch. 300-21) [Also see PCB 108-Set 256-1]
21M320, U (Ch. 400-21) 249-8
21M330, U (Ch. 406-21) 250-13
21M333, U (Ch. 406-21) 250-13
21M336, U (Ch. 301-21) 254-6
21M336P, U (Ch. 302) 254-6
21M339, U (Ch. 406-21) 249-8
21M339, U (Ch. 406-21) [See Model 21B16-Set 250-13]
21M503 (Ch. 191, B) 201-5
21M506 (Ch. 211, M) 194-4
21M509 (Ch. 196) [See Model 21B116-Set 195.8]
21M700 (Ch. 196, M) 201-5
21M700 (Ch. 196M, T) 195-8
21M715 (Ch. 211T) [See Model 21B122-Set 194.4]
21M718, U (Ch. 300-21) [Also see PCB 108-Set 256-1]
21M721, U, 21M722, U (Ch. 400-21) 249-8
21M900 (Ch. 192) (TV Ch. only) 201-5
21M903 (Ch. 213, M) 211-8
21M906 (Ch. 199, M, T and Radio Ch. 182) 221-6
21M910 (Ch. 375-21) [See PCB 108-Set 256-1 and Model 21B144-Set 236.6]
21P108 (Ch. 191, B) 201-5
21P117 (Ch. 196, M) 195-8
21P122 (Ch. 211, M) 194-4
21P145, U (Ch. 301-21) [Also see PCB 108-Set 256-1]
21P148, U (Ch. 401-21) 249-8
21P168, U (Ch. 302) 254-6
21P307B (Ch. 211, M) 194-4
21P310 (Ch. 196M, T) 195-8
21P322, U (Ch. 402-21) 249-8
21P332, U (Ch. 405-21) 250-13
21P338P, U (Ch. 302) 254-6
21P505 (Ch. 191, B) 201-5
21P508 (Ch. 211, M) 194-4
21P511 (Ch. 196) [See Model 21B116-Set 195.8]
21P702 (Ch. 191, B) 201-5
21P702 (Ch. 196M, T) 195-8
21P717 (Ch. 211T) [See Model 21B122-Set 194.4]
21P720, U (Ch. 300-21) [Also see PCB 108-Set 256-1]
21P724, U (Ch. 400-21) 249-8
21P902 (Ch. 192) (TV Ch. only) 201-5
21P905 (Ch. 213, M) 211-8
21P908 (Ch. 199, M, T and Radio Ch. 182) 221-6
21P912 (Ch. 375-21) [Also see PCB 108-Set 256-1]
24B151, U (Ch. 402-24) 257-7
24B707 (Ch. 187, B, C) 159-6
24B726, U (Ch. 402-24) 257-7
24M150, U (Ch. 402-24) 257-7
24M708 (Ch. 187, B, C) 159-6
24M725, U (Ch. 403-24) 257-7
24P152, U (Ch. 403-24) 257-7
24P727, U (Ch. 403-24) 257-7
27M709 (Ch. 197) 219-6
600 (Ch. 154) 95A-8
601 (Ch. 155) 95A-8
610 (Ch. 140) 97A-6
612 (Ch. 142) 97A-6
613 (Ch. 149) 97A-6
630, 631 (Ch. 170) 150-7
632, 633, 634, 635 (Ch. 171) 150-7
634A, 635A (Ch. 173) 150-7
636, 637 (Ch. 183) 141-7
636B, 637B (Ch. 183 B) 168-8
638, 639 (Ch. 180) 144-5
826, 827, 828 (Ch. 43) 95A-8
830, 831 (Ch. 151) 97A-6
832 (Ch. 151) [See Model 830-Set 97A.6]
836, 837 (Ch. 153) 93A-8
840 (Ch. 153) 93A-8
846 (Ch. 151) [See Model 830-Set 97A.6]
847, 848, 849 (Ch. 156) 97A-7
860, 861, 862 (Ch. 157) 97A-7
866, A, 867, A, 868, A (Ch. 173) 78-4
870, 871, 872 (Ch. 170) 150-7
876, 877, 878 (Ch. 171) 150-7
876A, 877A, 878A (Ch. 173) 150-7
880, 881, 882, 883, 884, 885, 886, 887 (Ch. 183) 147-7
886B, 887B (Ch. 183B) 168-8
890, 891, 892 (Ch. 175) 150-7
893, 894, 895, 896, 897 (Ch. 185) 141-7
896B, 897B (Ch. 183T) 168-8
902 (Ch. 141, Radio Ch. 137) 150-7
912, 913 (Ch. 147) 95A-8
914, 915 (Ch. 150) 97A-6
917, 918 (Ch. 152) 97A-6

HOFFMAN-Cont.
920 (Ch. 152) [See Model 830-Set 97A.6]
946, 947, 948 (Ch. 164) 97A-7
950, 951, 952 (Ch. 172), 950A, 951A, 952A (Ch. 172) 127-6
953, 954, 955 (Ch. 164) 141-7
960, 961, 962 (Ch. 176) 127-6
963, 964, 965 (Ch. 186) 141-7
Ch. 102 [See Model A401]
Ch. 103 [See Model A200]
Ch. 107 [See Model A500]
Ch. 108ST [See Model A501]
Ch. 1105 [See Model A700]
Ch. 114 [See Model B1000]
Ch. 119 [See Model A202]
Ch. 123 [See Model C504]
Ch. 137 [See Model 902]
Ch. 140 [See Model 610]
Ch. 141 [See Model 902]
Ch. 142 [See Model 612]
Ch. 143 [See Model 826]
Ch. 147 [See Model 826]
Ch. 149 [See Model 613]
Ch. 150 [See Model 914]
Ch. 151 [See Model 830]
Ch. 152 [See Model 917]
Ch. 153 [See Model 836]
Ch. 154 [See Model 600]
Ch. 155 [See Model 601]
Ch. 156 [See Model 847]
Ch. 157 [See Model 840]
Ch. 164 [See Model 946]
Ch. 170, 171 [See Model 630]
Ch. 172 [See Model 950]
Ch. 173 [See Model 634A]
Ch. 174 [See Model 950A]
Ch. 175 [See Model 890]
Ch. 176 [See Model 960]
Ch. 182 [See Model 21M907]
Ch. 183 [See Model 636]
Ch. 183B, 183M, 183T [See Model 636B]
Ch. 186 [See Model 963]
Ch. 187, B, C [See Model 24B707]
Ch. 190, B [See Model 78104]
Ch. 191, B [See Model 21B107]
Ch. 192 [See Model 21B901]
Ch. 194 [See Model 20B102F]
Ch. 196, M [See Model 21B116]
Ch. 197 [See Model 21B701]
Ch. 197 [See Model 27M709]
Ch. 199 [See Model 21B907]
Ch. 200 [See Model 7B1108]
Ch. 201 [See Model 21M305]
Ch. 202 [See Model 7B113]
Ch. 210, M [See Model 7M109B]
Ch. 211, M [See Model 21B122]
Ch. 211T [See Model 21B315]
Ch. 212, M [See Model 7B113B]
Ch. 213, M [See Model 21B904]
Ch. 214, M [See Model 7B141, U]
Ch. 300-21 [See Model 21B14, U]
Ch. 301-17 [See Model 7B157]
Ch. 301-21 [See Model 21B154]
Ch. 301X-21 [See Model 21B164X]
Ch. 302 [See Model 21B167]
Ch. 375-21 [See Model 21B911]
Ch. 400-21 [See Model 21B321]
Ch. 401-21 [See Model 21B147]
Ch. 402-24 [See Model 24B151]
Ch. 403-24 [See Model 24B726]
Ch. 405-21 [See Model 21B331]
Ch. 406-21 [See Model 21B161]
HOWARD
472AC, 472AF, 472C, 472F 31-14
473 32-12
474 32-12
475TV Photofact Servicer 84
481AC, 481M 67-11
482, 482A 48-12
901A-E, -H, -J, -M, -W [See Model 901A Series-Set 1-8]
901A Series T-8
901AP 10-21
906, 906C 17-18
909M 25-15
920 5-7
HUDSON (Auto Radio)
D847 (Fact. No. 6MH089) 25-16
D888 (Fact. No. 6MH89) 39-9
225908 (Early) 149-6
225908 (Late) (Ch. 749-1) 167-11
229403 (Ch. 749-2) 167-11
236476 (SH759) 215-8
236486 (SH758) 214-4
238060 (SH758) 214-4
HUDSON (Dept. Stores)
30T14A-056 (Similar to Chassis) 119-3
38T12A-058 (Similar to Chassis) 109-1
317T3 (Similar to Chassis) 72-9
318T4 (Similar to Chassis) 85-3
318T4S (Similar to Chassis) 85-3
318T4-872 (Similar to Chassis) 85-3
318T6A (Similar to Chassis) 85-3
318T6A-950 (Similar to Chassis) 85-3
318T9A-900 (Similar to Chassis) 78-4
321MS31C-A (Similar to Chassis) 182-5
321MS39A (Similar to Chassis) 21-11
518T6A (Similar to Chassis) 85-3
518T9A-918 (Similar to Chassis) 78-4
518T10A-916 (Similar to Chassis) 78-4
2318T6A-954 (Similar to Chassis) 85-3
2318T9A-912 (Similar to Chassis) 78-4
2321MS39A (Similar to Chassis) 226-11
HUDSON ELECTRONICS
RPM-71 186-6
3W 191-11
11 194-5
39HB 186-6
3100 190-5
312H 194-5
324H 198-9
332H 123-6
347BL 121-8

HUDSON ELECTRONICS-Cont.
350 126-6
374H 188-7
388 191-12
HYDE PARK
AR14L 169-8
AR17L 169-8
MS12, MST14 168-9
14TR, 16TR 168-9
17CD (1st Prod.) 168-9
17CD (2nd Prod.) 169-8
17CRR (1st Prod.) 169-8
17CRR (2nd Prod.) 169-8
17ROG (1st Prod.) 169-8
17ROG (2nd Prod.) 169-8
20CD (2nd Prod.) 169-8
20TR 168-9
112X 168-9
203D (1st Prod.) 168-9
203D (2nd Prod.) 169-8
312 168-9
819 168-9
1001 174-7
3163CR 168-9
8163CR 168-9
8193CM 168-9
INDUSTRIAL ELECTRONIC CORP. (See Simplon)
INDUSTRIAL TELEVISION (Also see Century)
IT-40R, IT-42R (Ch. IT-26R, IT-35R, IT-39R, IT-46R) 99A-7
721, 821, 921, 1021 (Ch. IT-21R) 97A-8
INTERNATIONAL ELECTRONICS (See Recorder Listing)
JACKSON
DP-51 156-7
JP-20 173-7
JP-30 153-7
JP-50 155-9
JP-200 171-6
JP-300 174-7
JP-400 171-6
10C, 10T 132-8
12C, 12T 132-8
14C, 14T 132-8
16C, 16T 132-8
17XC, 17XT [See Model 10C-Set 132-8]
20XC, 20XT [See Model 10C-Set 132-8]
150 130-8
153 [See Model 150-Set 130-8]
214A, 217A, B, C, 220A, B, 221A, 242 179-7
254 173-8
255 179-7
312 132-8
316 132-8
350 132-9
412 132-8
416 132-8
1400T [See Model 10C-Set 132-8]
1700, T [See Model 10C-Set 132-8]
2000C [See Model 10C-Set 132-1]
5000, 5050 88-5
5200, 5250 88-5
5600, 5650 88-5
Ch. 114H 162-7
Ch. 116H, 117H 162-7
Ch. 120H 162-7
Ch. 317-B, -D 226-3
Ch. 321-B, -D 226-3
JEFFERSON-TRAVIS
MR-28 10-22
MR3 17-19
JEWEL
17C9, 17T9, 17T7 187-7
21C9, 21T9 187-7
300 12-11
304 15-12
500A, B, C, 501A, B, C; 502A, B, C; 503A, B, C; 504A, B, C; 505A, B, C
505 "Pin-Up" 18-21
801 (Trixite) 45-14
814 170-9
910 99-8
915 99-8
920A 55-10
921 [See Model 920-Set 55-10]
935, 936 [See Model 920-Set 55-10]
949 105-5
955 98-5
956 144-6
960 97-8
960U, 961 [See Model 960-Set 97-8]
985 99-8
5007 183-7
5010 111-7
5020 136-10
5020U [See Model 5020-Set 136-10]
5040 160-5
5050 128-7
5057U 109-7
5100, E, U 159-7
5125U 217-7
5200 294-6
5205 196-4
5250 206-7
5310 225-12
KAISER-FRAZER
100170 128-8
100205 139-6
100330 [See Model 100170-Set 128-8]
200001 35-13
200002 56-13
KAPPLER
102T 54-10
KARADIO
M80B 233-3
80C 66-10
1275, 1275A 85-7
1276 115-4

KAYE-HALBERT
C-024 (Ch. 253) [For TV Ch. only See PCB 63-Set 197-1 and Model 014-Set 146-8]
012 (Ch. 243) 169-9
014 (Ch. 253) [Also see PCB 63-Set 197-1] 146-8
024 (Ch. 253) [Also see PCB 63-Set 197-1] 146-8
033, 034, 035, 036, 037 (Ch. 242) 139-7
044, 045, 046 (Ch. 253) [Also see PCB 63-Set 197-1] 146-8
074, 076, 077 (Ch. 253) [Also see PCB 63-Set 197-1] 146-8
104, 114 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
104 (Ch. 243) [See Model 012-Set 169-9]
114 (Ch. 243) [See Model 012-Set 169-9]
114DX (Ch. 253DX) [Also see PCB 63-Set 197-1] 170-9
122 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
122 (Ch. 243) [See Model 012-Set 169-9]
124 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
138 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
138 (Ch. 243) [See Model 012-Set 169-9]
144, 145, 146 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
144, 145, 146 (Ch. 243) [See Model 012-Set 169-9]
146 (Ch. 253) [See Model 014-Set 146-8]
146 (Ch. 253DX) [See PCB 45-Set 179-1 and Model 114DX-Set 169-9]
154, 164 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
154 (Ch. 243) [See Model 012-Set 169-9]
164 (Ch. 243) [See Model 012-Set 169-9]
174 (Ch. 243) [See Model 012-Set 169-9]
231, 232, 233, 234, 235, 236, 237, 238, 239, 240, 241 (Ch. 231, 242, 243) 139-7
314 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
314 (Ch. 253DX) [See PCB 45-Set 179-1 and Model 114DX-Set 169-9]
322 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
322 (Ch. 253DX) [See PCB 45-Set 179-1 and Model 114DX-Set 169-9]
324 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
324 (Ch. 253DX) [See PCB 45-Set 179-1 and Model 114DX-Set 169-9]
338 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
338 (Ch. 253DX) [See PCB 45-Set 179-1 and Model 114DX-Set 169-9]
344 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
344 (Ch. 253DX) [See PCB 45-Set 179-1 and Model 114DX-Set 169-9]
354 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
354 (Ch. 253DX) [See PCB 45-Set 179-1 and Model 114DX-Set 169-9]
356 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
356 (Ch. 253DX) [See PCB 45-Set 179-1 and Model 114DX-Set 169-9]
385 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
385 (Ch. 253DX) [See PCB 45-Set 179-1 and Model 114DX-Set 169-9]
394, 395, 396 (Ch. 263) [See Ch. 263-Set 217-8]
424, 425, 426 (Ch. 253) [Also see PCB 63-Set 197-1] 146-8
425, 426 (Ch. 253DX) [See PCB 45-Set 179-1 and Model 114DX-Set 169-9]
426 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
426 (Ch. 243) [See Model 012-Set 169-9]
428 (Ch. 253DX) [See PCB 45-Set 179-1 and Model 114DX-Set 169-9]
714 (Ch. 253) [Also see PCB 63-Set 197-1] 146-8
72 (Ch. 253) [Also see PCB 63-Set 197-1] 146-8
731, 733 (Ch. 231, 242) 139-7
734, 735, 736, 737 (Ch. 242) 139-7
744, 745 (Ch. 253) [Also see PCB 63-Set 197-1] 146-8
777 (Ch. 253) [Also see PCB 63-Set 197-1] 146-8
914 (Ch. 253) [Also see PCB 63-Set 197-1] 146-8
924 (Ch. 253) [See PCB 63-Set 197-1 and Model 014-Set 146-8]
KAYE-HALBERT-Cont.
Ch. F-243 [See Model 104]
Ch. 231 [See Model 231]
Ch. 242 [See Model 033]
Ch. 243 [See Model 012]
Ch. 253 [See Model 014]
Ch. 253DX [See Model 114DX]
KAY MUSICAL INSTRUMENT CO.
5 Tube Radio 6-14
KNIGHT (Also see Recorder Listing)
SK6727 244-6
SK10722 [See Model 722-Set 240.4]
SK11719 246-7
SK14721 252-9
SK19170 248-8
4D-50 40-9
4G-40 30-13
5A150, 5A152, 5A154 12-17
5A-190 14-15
5B-160 20-15
5B-175, 5B-176 20-16
5B-185 22-17
5C-90 30-13
5D-250, 5D-251 55-11
5D-555 34-9
5E-250, 5E-251 [Similar to Chassis] 36-25
5E-457 [Similar to Chassis] 53-23
5F-525, 5F-526 53-13
5F-565 55-12
5G-563 [Similar to Chassis] 97-1
5H-570 143-10
5H-571 [See Model 5H-570-Set 143-10]
5H-605 131-10
5H-607, 5H-608 [Similar to Chassis] 97-15
5H-678, 5H-679 [Similar to Chassis] 109-7
5H-700 123-7
5J-705 174-8
5K715 219-2
6A-122 9-18
6A-125 9-19
6A-192 16-19
6B-122 [See Model 6A-122-Set 9-18]
6B-127 [See Model 6A-127-Set 9-19]
6C-225 30-14
6C-225, 6D-226 [See Model 6C-225-Set 30-14]
6D-235 54-11
6D-300 39-10
6G-400 [See Model 449-Set 83-5]
6H-580 126-7
6K718 217-9
7B-220 27-14
7D-405 21-12
8B-210 20-17
8D-340 46-13
8G-200, 8G-201 128-9
89V-101 78-8
10B-249 42-14
11C-300 29-12
11D-302 57-9
12H-610 176-5
14F-490, 14F-495, 14F-496 63-12
15H-609 [See Model 511B-Set 125-9]
19F492, 19F497, 19F498 58-11
20H611 164-4
93X321 255-7
93-017 31-5
93-024 32-13
93-103 31-16
93-146 31-16
93-155 37-10
93-191 38-8
93-320 74-5
93-330 99-9
93-350 76-13
93-360 38-9
93-370 75-10
93-380 90-8
93-431 167-12
96-279 160-6
96-326 137-5
96-354 [Similar to Chassis] 38-9
97-870 78-19
449 83-5
511B 125-9
LAFAYETTE
FA15W, FA15Y 15-15
J62, J62C 16-21
MC10B, MC10Y 14-16
MC11 28-18
MC12 27-15
MC13 15-16
MC16 27-16
P564 [Similar to Chassis] 38-5
IN434, IN435, IN436 [Similar to Chassis] 98-5
IN437 [Similar to Chassis] 121-2
IN549 [Similar to Chassis] 139-12
IN551 [Similar to Chassis] 38-6
IN554, IN555 [Similar to Chassis] 55-10
IN556, IN557 [Similar to Chassis] 109-7
IN559 [Similar to Chassis] 90-7
IN560 [Similar to Chassis] 109-7
IN561, IN562 [Similar to Chassis] 97-8
IN819 [Similar to Chassis] 69-7
IP184 [Similar to Chassis] 149-13
IP185, IP186 [Similar to Chassis] 149-13
IP187 [Similar to Chassis] 149-13
IP188 [Similar to Chassis] 149-13
IP189 [Similar to Chassis] 149-13
IP282 [Similar to Chassis] 149-13

LEARADIO

RM-402C (Learnavian)	42-15
561, 562, 563	1-26
563, 565BL, 566, 567, 568	9-20
1281-PC (Ch. 78)	49-11
6610PC, 6611PC, 6612PC	9-21
6614, 6615, 6616, 6619	3-18
6617PC	16-22
Chassis R-971	51-11

LEE (See Royal)

LEE TONE

AP-100	16-23
--------------	-------

LEWITT

615A	11-13
711	42-16

LEXINGTON

6545	13-20
------------	-------

LIBERTY

A6K, A6P, 6K	20-18
507A	20-19

LINCOLN (Auto Radio)

FAA-18805	167-7
FAG-18805-A	214-5
FDD-18805-A, B	246-8
GL892 (OL-18805-A) [See PCB 105	
Set 252-1 and Ford Model	
GF890 (OA-18805-B) — Set	
109.5]	
1CH748 (1H-18805) [See Ford Mod-	
el 1C743—Set 133-7]	
1CH748-1 (1H-18805)	158-5
1H-18805 [See Model 1CH748 or	
1CH748-1]	

2CH753 (FAA-18805-A)	167-7
35H756 (FAG-18805-A)	214-5
45H764 (FDD-18805-A), 45H766	
(FDD-18805-B)	246-8
5EH-18805-A	66-11
5EH-18805-B	66-11
7M1080 (5EH-18805-A), 7M1081	
(5EH-18805-B)	66-11
8H-18805	83-4
8H-18805-A (See Model 8M1882Z—	
Set 44-7 or 8M1985Z—Set 83-4)	
8L-18805-A (See Model 8M1882Z—	
Set 44-7 or 8M1985Z—Set 83-4)	
8L-18805-B	83-4
8M1882 (8L-18805-A), 8M1882Z	
(8H-18805-A) (Ch. 8E82) 44-7	
8M1985 (8L-18805-A), 8M1985E	
(8L-18805-B), 8M1985Z (8H-	
18805-A), 8M1985ZE (8H-18805-	
B)	83-4

LINCOLN

S131-B	2-10
--------------	------

LINCOLN (Allied Radio Corp.)

5A-110	5-34
--------------	------

LINDEX CORP. (See Swank)

LIPAN (See Supreme)

LULLABY (See Mitchell)

LYMAN

CM10, CM20	44-8
------------------	------

LYRIC (Also see Reuland)

5467, 5467Y, 5467W	7-17
--------------------------	------

MAGIC TONE

500, 501	5-40
504 (Bottle Receiver)	22-18
508 (Keg Radio)	38-9
510	52-10
900	38-9

MAGNAVOX

CP251M (Chassis AMP-128A, B,	
AMP-129)	254-7
252M (Chassis CR700 and AMP132)	
)	260-9

● 104 Series (Ch. CT301 thru CT314)	
.....	161-4
● 108, 108A Series	239-6
● 108B Series	240-5
● 300 Series	263-9

Chassis AMP-101A, AMP-101B	
.....	43-12

Chassis AMP-108A, AMP-108B	
.....	41-10

Chassis AMP-111A, B, C	68-10
------------------------------	-------

Chassis AMP-128A, B	254-7
---------------------------	-------

Chassis AMP-129	254-7
-----------------------	-------

Chassis AMP-131A, B	249-9
---------------------------	-------

Chassis AMP132	260-9
----------------------	-------

● Chassis CMU401AA, CMU402AA,	
CMU403AA, CMU404AA, CMU405AA,	
CMU406AA, CMU407AA (108, 108A	
Series)	239-6

● Chassis CMU410AA (108, 108A	
Series)	239-6

● Chassis CMU413AA (108, 108A	
Series)	239-6

● Chassis CMU418AA, CMU419AA,	
CMU420AA (108, 108A Series)	
.....	239-6

● Chassis CMU401BB, CMU402BB,	
CMU403BB, CMU404BB, CMU405BB,	
CMU406BB, CMU407BB (108B	
Series)	240-5

● Chassis CMU410BB (108B Series)	
.....	240-5

● Chassis CMU413BB (108B Series)	
.....	240-5

● Chassis CMU418BB, CMU419BB,	
CMU420BB (108B Series)	240-5

● Chassis CMU422BC (300 Series)	
.....	263-9

● Chassis CMU410AA, (108, 108A	
Series)	239-6

● Chassis CMU413AA, (108, 108A	
Series)	239-6

● Chassis CMU418AA, CMU419AA,	
CMU420AA (108, 108A Series)	
.....	239-6

● Chassis CMU401BB, CMU402BB,	
CMU403BB, CMU404BB, CMU405BB,	
CMU406BB, CMU407BB (108B	
Series)	240-5

● Chassis CMU410BB (108B Series)	
.....	240-5

● Chassis CMU413BB (108B Series)	
.....	240-5

● Chassis CMU418BB, CMU419BB,	
CMU420BB (108B Series)	240-5

● Chassis CMU422BC (300 Series)	
.....	263-9

CP251M (Chassis AMP-128A, B,	
AMP-129)	254-7

Chassis CR-188 (155B Regency Sym-	
phony)	18-22

Chassis CR190A, CR190B	46-14
------------------------------	-------

Chassis CR-192A, CR-193B	41-11
--------------------------------	-------

Chassis CR-197C	37-11
-----------------------	-------

Chassis CR-198A, B, C (Hepple-	
white, Modern Symphony)	17-20

Chassis CR-199	63-13
----------------------	-------

Chassis CR-200A, B, C, D, E, F	
.....	44-9

MAGNAVOX—Cont.

Chassis CR-207A, B, C, D	41-12
Chassis CR-208A, CR-208B	54-11
Chassis CR-210A, CR-210B	52-11
Chassis CR-211A, B	68-10
Chassis CR300AA-1	268-8
Chassis CR700	260-9

● Chassis CT-214, CT-218	62-13
--------------------------------	-------

● Chassis CT-219, CT-220	62-7
--------------------------------	------

● Chassis CT-221	62-13
------------------------	-------

● Chassis CT-222	82-7
------------------------	------

● Chassis CT-224	97A-8
------------------------	-------

● Chassis CT-232	93A-9
------------------------	-------

● Chassis CT-235	97A-8
------------------------	-------

● Chassis CT-236	93A-9
------------------------	-------

● Chassis CT-237, CT-238 (See Set	
95A-9 and Ch. CT219—Set 82-7)	

● Chassis CT239	93A-9
-----------------------	-------

● Chassis CT244, CT245, CT246	
.....	93A-9

● Chassis CT250, CT251	135-1A
------------------------------	--------

● Chassis CT252, CT253	95A-9
------------------------------	-------

● Chassis CT257, CT258, CT259,	
CT260	119-1A

● Chassis CT262, CT263, CT264,	
CT265	155-10

● Chassis CT266, CT267, CT269	
.....	131-1A

● Chassis CT-270, CT-271, CT-272,	
CT-273, CT-274, CT-275, CT-276,	
CT-277, CT-278, CT-279, CT-280,	
CT-281, CT-282	148-8

● Chassis CT283	155-10
-----------------------	--------

● Chassis CT284, CT285	131-1A
------------------------------	--------

● Chassis CT286	155-10
-----------------------	--------

● Chassis CT287, CT288	131-1A
------------------------------	--------

● Chassis CT289	155-10
-----------------------	--------

● Chassis CT290	131-1A
-----------------------	--------

● Chassis CT291, CT293	155-10
------------------------------	--------

● Chassis CT294	131-1A
-----------------------	--------

● Chassis CT295	155-10
-----------------------	--------

● Chassis CT301 thru CT314	161-4
----------------------------------	-------

● Chassis CT331 thru CT349 (105	
Series)	168-10

● Chassis CT350 thru 357 (105 Series)	
[See Ch. CT351—Set 168-10]	

● Chassis CT358A (107 Series)	226-4
-------------------------------------	-------

● Chassis CT358AA, AB, BA, BB, CB	
(107 Series) [See Ch. CT358—Set	
226-4]	

● Chassis CT362, CT363 (105L, M,	
N Series)	205-6

● Chassis CT372, CT373 (105L, M, N	
Series)	205-6

● Chassis CT374 (105N Series)	205-6
-------------------------------------	-------

● Chassis CT385AA, AB, BA, BB, CB	
(107 Series) [See Ch. CT-358—	
Set 226-4]	

● Chassis CT385CB, DC (107 Series)	
[See Ch. CT358—Set 226-4]	

● Chassis CT386AA, AB, BA, BB, CB	
(107 Series) [See Ch. CT358—	
Set 226-4]	

● Chassis CT401AA, CT402AA,	
CT403AA, CT404AA, CT405AA,	
CT406AA, CT407AA (108, 108B	
Series)	239-6

● Chassis CT410AA (108, 108B Series)	
.....	239-6

● Chassis CT418AA, CT419AA,	
CT420AA (108, 108A Series)	
.....	239-6

● Chassis CT401BB, CT402BB,	
CT403BB, CT404BB, CT405BB,	
CT406BB, CT407BB (108B	
Series)	240-5

● Chassis CT410BB (108B Series)	
.....	240-5

● Chassis CT413BB (108B Series)	
.....	240-5

● Chassis CTA418BB, CTA419BB,	
CTA420BB (108B Series)	240-5

● Chassis CT8422BC (300 Series)	
.....	263-9

● Chassis CU401AA, CU402AA,	
CU403AA, CU404AA, CU405AA,	
CU406AA, CU407AA (108, 108A	
Series)	239-6

● Chassis CU410AA (108, 108A	
Series)	239-6

● Chassis CU413AA (108, 108A	
Series)	239-6

● Chassis CU418AA, CU419AA,	
CU420AA (108, 108A Series)	
.....	239-6

● Chassis CU401BB, CU402BB,	
CU403BB, CU404BB, CU405BB,	
CU406BB, CU407BB (108B	
Series)	240-5

● Chassis CU410BB (108B Series)	
.....	240-5

● Chassis CU413BB (108B Series)	
.....	240-5

● Chassis CU418BB, CU419BB,	
CU420BB (108B Series)	240-5

● Chassis MCT228	95A-9
------------------------	-------

MAGNECORD (See Recorder Listing)

MAGUIRE (Also see Record Changer Listing)

500B1, 500BW, 500D1, 500DW	
.....	6-15

561B1, 561BW, 561D1, 561DW	
.....	6-16

571B1, 571BW, 571D1, 571DW	
.....	6-10

661, 661A	12-18
-----------------	-------

700A	7-18
------------	------

700E	15-17
------------	-------

MECK—MOTOROLA

MECK—Cont.
●JM720T (Ch. 9032) 186-9
●JM720TU (Ch. 9021) 148-11
●JM721C, CD (Ch. 9032) 186-9
●JM721C, D (Ch. 9040) 220-4
●M616C, T (Ch. 9023) [See Model JM717C—Set 148-11]
●M620C, T (Ch. 9023) [See Model JM717C—Set 148-11]
●MM510T, MM512T, MM516C, MM516T 110-9
●MM614C, T (Ch. 9018) [Also see PCB 12—Set 120-1]
●MM616C, T (Ch. 9018) [Also see PCB 12—Set 120-1]
●MM617C, T (Ch. 9032) [See Model JM717C—Set 186-9]
●MM617C, T (Ch. 9032) [See Model JM717C—Set 186-9]
●MM619C (Ch. 9018) [Also see PCB 12—Set 120-1]
●MM-620C, T (Ch. 9032) [See Model JM-717C—Set 186-9]
●MM621C (Ch. 9040) 220-4
●MM621RPT, RPTB (Ch. 9040) 220-4
PM-5CS-DW10 2-4
PM-5CS-DW10 21-19
RC-5CS-P 1-9
RC-6A7-P6 31-18
SA-10, SA-20 101-4
●XA-701 61-16
●XF-705 [See Model XA-701—Set 61-16]
●XL750 76-14
●XN-752 101-5
●XOB 110-9
●XP-775 101-5
●XQ-776 101-5
●XQA 110-9
●XQA-776 101-5
●XQR 110-9
●XR-777 101-5
●XRA, XRP 110-9
●XS-786 101-5
●XSA 110-9
●XSB (Ch. 9018) [Also see PCB 12—Set 120-1]
●XSC, XSD (Ch. 9018) [See Model MM614C—Set 117-8 and PCB 12—Set 120-1]
●XST 110-9
●XT-785 101-5
●XTA, XTR 110-9
●XX900 110-9
4C7 35-14
5A7-P11, 5A7-PB11 31-18
5D7/WL18 11-26
6A6-W4 16-26
●514C, T (Ch. 9018) [See Model MM614C—Set 117-8 and PCB 12—Set 120-1]
●614C, 614T (Ch. 9022) [See Model JM717C—Set 148-11]
●616C, T (Ch. 9018) [See Model MM614C—Set 117-8 and PCB 12—Set 120-1]
●617C, 617T (Ch. 9022) [See Model JM717C—Set 148-11]
●619C, T (Ch. 9018) [See Model MM614C—Set 117-8 and PCB 12—Set 120-1]
9030 228-11
Ch. 9018 [See Model MM614C]
Ch. 9021 [See Model JM717C]
Ch. 9022 [See Model JM717C]
Ch. 9023 [See Model MM614C]
Ch. 9032 [See Model JM717C]
Ch. 9040 [See Model JM717C]
MEDCO (See Telesonic)
MITSNER
●TV-1 (Ch. 24TV) 56-15
4E 172-5
5A [See Maguire Model 57]—Set 44-10
6H [See Maguire Model 66]—Set 12-18
8BT 161-5
8C 37-12
9A 123-9
9-1065 3-15
9-1091A, 9-1091B 3-15
9-1091C 116-8
9-1093 55-13
9-1160 257-9
16A 105-6
●24TV [See Model TV1—Set 56-15]
57A [See Maguire Model 57]—Set 44-10]
661 [See Maguire Model 66]—Set 12-18]
2961 Series 27-19
MERCURY (Automobile)
FAB-1880S-A 167-7
FAB-1880S-A 214-5
FDC-1880S-A 246-8
GM891 (OM-1880S-A) [See PCB 105—Set 252-1 and Ford Model CF890 (OA-1880S-B)—Set 109-5]
OM-1880S-A [See Model GM891]
1CM747-1 (1M-1880S) [See Ford Model 1CF743—Set 133-7]
1CM747-1 (1M-1880S) 158-5
1M-1880S [See Model 1CM747 or 1CM747-1]
2CM752 (FAB-1880S-A) 167-7
3SM757 (FAB-1880S-A) 214-5
4SM767 (FDC-1880S-A) 246-8
6MM790 (59A-1880S-A1) 62-12
6MM790-E (59AF-1880S) 62-12
8MM890 (Ch. BE90) (8M-1880S-B) 49-13
8MM890 (8M-1880S-B) 69-10
8MM991 (8M-1880S-B), 8MM991-E, (8M-1880S) 83-4
8M-1880S-B [See Model 8MM890 or 8MM990 or 8MM991]
59AF-1880S 62-12
59A-1880S-A1 62-12
MERCURY (Pacific-Mercury)
●2013 (Ch. 150-2) [Also see PCB 57—Set 191-1] 172-6
●2080 (Ch. 150-2) [See PCB 57—Set 191-1 and Model 2013—Set 172-6]
●2081 (Ch. 150-4 and Radio Ch. 155) 198-11
●2113, 2115 (Ch. 150-11, -8) [Also see PCB 57—Set 191-1] 172-6
●2116, 2117 (Ch. 150-8) [See PCB 57—Set 191-1 and Model 2013—Set 172-6]
●2181 (Ch. 150-31, -61 and Radio Ch. 155) 198-11
●2217, 2218, X (Ch. 200-11) 216-8
●2224 (Ch. 200-11) 216-8
●2241 (Ch. 200-11) 216-8
●2401 (Ch. 150-5, -51) [Also see PCB 57—Set 191-1] 172-6
●2424 (Ch. 201-34) 254-9
●2701 (Ch. 201-553, Audio Amp. Ch. 159-1 and Radio Ch. 160-1) 254-9
●4120 (Ch. 150-2) [Also see PCB 57—Set 191-1] 172-6
●4220 (Ch. 150) [Also see PCB 57—Set 191-1] 172-6
●4317 (Ch. 150-9) 172-6
●4320 (Ch. 150-2, -15) [Also see PCB 57—Set 191-1] 172-6
●4421 (Ch. 150-81) [See Model 2013—Set 172-6 and PCB 57—Set 191-1]
Ch. 150-2 [See Model 2013]
Ch. 150-4 [See Model 2081]
Ch. 150-5 [See Model 2401]
Ch. 150-9 [See Model 4317]
Ch. 150-11 [See Model 2113]
Ch. 150-12 [See Model 4317]
Ch. 150-15 [See Model 4320]
Ch. 150-31 [See Model 2181]
Ch. 150-51 [See Model 2401]
Ch. 150-61 [See Model 2181]
Ch. 150-81 [See Model 2113]
Ch. 155 [See Model 2081]
Ch. 159-1 [See Model 2701]
Ch. 160-1 [See Model 2424]
Ch. 200-11 [See Model 2217]
Ch. 201-34 [See Model 2241]
Ch. 201-553 [See Model 2701]
MIDLAND
M68 2-30
MIDWEST
P6, PB-6 14-19
R-12, RG-12, RT-12 (Ch. RGL-12) 44-12
R-12, RG-12, RT-12 (Ch. RGT-12) 44-13
R-16, RG-16, RT-16 (Ch. RGT-16) 45-16
S8, ST-8 (Ch. STM-8) 15-19
S-12, SG-12, ST-12 (Ch. SGT-12) 21-23
S-16, SG-16, ST-16 (Ch. SGT-16) 21-24
TM-8 (Ch. STM-8) 15-19
716, A [See Model S-16—Set 21-24]
Ch. KD-16 263-10
Ch. RN-16 263-10
MILWAUKEE ERWOOD (See Record Changer Listings)
MINERVA
L-702 12-20
L-728 11-15
W-177, Tropic Master 11-15
W-107-3 11-14
W-112B 12-20
W-710, W710A (W119) 5-25
W-728 11-15
410, 411 41-14
702B, 72H-1 30-18
729 (Partapal) 23-14
MIRRORTONE (Also see Meck)
●A-17C, T (Ch. 9040) 216-4
●A-21C, CB, T, TB, X, Z (Ch. 9040) 216-4
●A24C (Ch. 9049, 9051) 247-6
●14MTS 163-7
●16MC, MT, 17MC, MT, MZ-C, MZ-T 163-7
●17PC (Ch. 9025) (Series 'P') [See Model 20PC—Set 175-12]
●17PCSB, 17PCW 204-5
●17PT (Ch. 9025) (Series 'P') [See Model 20PC—Set 175-12]
●17PTE 204-5
●20NC, MT, MZ-C, MZ-T 163-7
●20PC 175-12
●20PCSB, 20PCW 204-5
●20PTCS [See Model 20PC—Set 175-12]
●20PTE, 20PTS, 20PTSB, 20PTW 204-5
●20PRSB 204-5
●21PCS 204-5
●21QDCS 204-5
●24QDCS 204-5
Ch. 9040 [See Model A-17C]
Ch. 9047 251-11
Ch. 9048 250-14
Ch. 9049 247-6
Ch. 9050 250-14
Ch. 9051 247-6
Ch. 9053, 9054 250-14
Ch. 9055 251-11
MITCHELL
●T16-B, -M, T16-2KB, T16-2KM, T17-2B, T17-2M, T17-2MM 154-8
●T12-B, T12-M, T12-2M 189-11
●T121-B, -M 190-9
3D 251-12
1250, 1251 55-14
1252, 1253 155-12
1254, 1255 159-8
1256 156-8
1258, 1259 264-11
1261, 1262 259-8
1263, A, 1264, A 259-9
1266 124-7
1267 158-7
1268 127-11
1271, 1272, 1273 260-11
1274, 1275 257-10
1276, 1277 250-15
1278 265-8
1279, 1280 279-10
1281 264-11
1283, 1284 263-11
1287 267-6
MOLDED INSULATION Co. (Also see Viz)
MR-6 (Wiretone) 41-15
MONITOR
M-403 (Fact. No. 470-2) 22-20
M-502 (Fact. No. 475) 23-15
M-510 (Fact. No. 472) 23-15
M-3070 29-15
RA-50 24-23
TA56M, TW56M 6-18
MONITORADIO (Radio Apparatus)
AR-1 164-5
AR-3 175-13
DRS-1 261-8
DR-200 261-8
MR-32 233-5
M-51A 162-8
M-101 159-9
MONTGOMERY WARD (See Airline)
MOPAR
602 (671A) 19-20
603 65-9
604 106-9
606 133-9
607 170-11
608 207-4
609 252-11
610T 220-5
611T [See Model 610T—Set 220-5]
612 [See Model 609—Set 201-6]
802 (C-4608) 18-24
802 (C-4608) (Revised) 42-19
903 (PD-4908) 66-17
809 66-12
805 (C-4908) 71-11
806, 807 [See Model 803—Set 66-12]
808 107-6
809 (C-5009) [See Model 805—Set 71-11]
810 (C-5010) [See Model 805—Set 71-11]
812 (P-5106) 139-8
813 (D5107) 139-8
814 137-8
815 (C-5109) 139-8
816 (C-5110) 139-8
817 (C-5111) 139-8
819 (P-5206) 202-3
820 (D-5207) 202-3
821 204-6
824 (C-5209) 202-3
828 (D-5407) [See Model 820—Set 202-3]
829 247-7
830 (C-5409) 249-10
831 [See Model 830—Set 249-10]
MOTOROLA (Also see Record Changer Listings)
AR-96-23 (M-5) 11-16
BKO-A [See Ch. 10A—Set 106-10]
BK2A (Ch. 2A and P6-2 or P8-2) 197-7
BK2M (Ch. 2M and P6-2 or P8-2) 197-7
BK3A6 (Ch. R-15A6 and P6-2 or P8-2) 256-10
BK-6 10-23
BK-8, X [See Ch. 8A—Set 46-16]
BK3A6 (Ch. R17A6 and P6-2 or P8-2) 263-13
CR-6 20-24
CR-76 25-21
CTA3 230-7
CTM3 255-9
CTC [See Model CT-9—Set 82-8]
CT1 [See Ch. 1A—Set 134-8]
CT1M 143-11
CT2A (Ch. 2A and P6-2 or P8-2) 197-7
CT2A6 (Ch. R-15A6 and P6-2 or P8-2) 256-10
CT2M (Ch. 2M and P6-2 or P8-2) 197-7
CT-6 8-21
CT8 [See Ch. 8A—Set 46-16]
CT8-A [See Ch. 10A—Set 106-10]
FD-6 7-20
FD7 [See Model FD-6—Set 7-20]
FD8 [See Ch. 8A—Set 46-16]
GMOT [See Ch. 10A—Set 106-10]
GM2A (Ch. 2A and P6-2 or P8-2) 263-13
GM2M (Ch. 2M and P6-2 or P8-2) 197-7
GM3A6 (Ch. R-15A6 and P6-2 or P8-2) 256-10
GM3A6 (Ch. R17A6 and P6-2 or P8-2) 263-13
GM9T [See Ch. 8A—Set 46-16]
GM9T-A [See Ch. 10A—Set 106-10]
HJ2A (Ch. 2A and P6-2 or P8-2) 197-7
HJ2M (Ch. 2M and P6-2 or P8-2) 197-7
HJ3A6 (Ch. R-15A6 and P6-2 or P8-2) 256-10
HNO [See Ch. 10A—Set 106-10]
HN2A (Ch. 2A and P6-2 or P8-2) 197-7
HN2A6 (Ch. R-15A6 and P6-2 or P8-2) 256-10
HN2M (Ch. 2M and P6-2 or P8-2) 197-7
HN3A6 (Ch. R-15A6 and P6-2 or P8-2) 256-10
HN4A6 (Ch. R17A6 and P6-2 or P8-2) 263-13
HN8, HN9 [See Ch. 8A—Set 46-16]
HT3A6 (Ch. R-15A6 and P6-2 or P8-2) 256-10
IL2TC [See Ch. 1A—Set 134-8]
IL2TC [See Ch. 1A—Set 134-8]
IL2T2 [See Ch. 1A—Set 134-8]
KR1 [See Ch. 1A—Set 134-8]
KR2A (Ch. 2A and P6-2 or P8-2) 197-7
KR2M (Ch. 2M and P6-2 or P8-2) 197-7
KR3A6 (Ch. R-15A6 and P6-2 or P8-2) 256-10
MOTOROLA—Cont.
KR8, KR9 [See Ch. 8A—Set 46-16]
KR9A [See Ch. 10A—Set 106-10]
NHIC 139-9
NH2AC [See Nash Model AC-152—Set 184-9]
NH3C [See Nash Model NH3C—Set 216-6]
NH4AC [See Nash Model AC-154—Set 264-13]
NH6 9-24
NH8 [See Ch. 8A—Set 46-16]
OE1 [See Ch. 10A—Set 106-10]
OE2 [See Ch. 8A—Set 46-16]
OE2A (Ch. 2A and P6-2 or P8-2) 197-7
OE2A6 (Ch. R-15A6 and P6-2 or P8-2) 256-10
OE2M (Ch. 2M and P6-2 or P8-2) 197-7
OE6 8-21
OE8, OE9 [See Ch. 8A—Set 46-16]
PCO [See Ch. 10A—Set 106-10]
PC2 [See Ch. 8A—Set 46-16]
PC2A (Ch. 2A and P6-2 or P8-2) 197-7
PC2A6 (Ch. R-15A6 and P6-2 or P8-2) 256-10
PC2M (Ch. 2M and P6-2 or P8-2) 197-7
PC6 8-21
PC8, PC9 [See Ch. 8A—Set 46-16]
PC9A [See Ch. 10A—Set 106-10]
PD2A (Ch. 2A and P6-2 or P8-2) 197-7
PD3A6 (Ch. R-15A6 and P6-2 or P8-2) 256-10
PD2M (Ch. 2M and P6-2 or P8-2) 197-7
PD2A6 (Ch. R-15A6 and P6-2 or P8-2) 256-10
SROB (Ch. OB) 105-7
SR18 [See Ch. 1B—Set 136-11]
SR2A (Ch. 2A and P6-2 or P8-2) 197-7
SR2A6 (Ch. R-15A6 and P6-2 or P8-2) 256-10
SR2M (Ch. 2M and P6-2 or P8-2) 197-7
SR9A [See Ch. 10A—Set 106-10]
SR52A6 (Ch. R17A6 and P6-2 or P8-2) 263-13
TK-101, B Tel. UHF Conv. 194-6
TK-17M Tel. UHF Conv. 193-5
TK-19M Tel. UHF Conv. 193-5
TK-19ME Tel. UHF Conv. [See Model TK17M—Set 193-5]
TK-20M Tel. UHF Conv. 193-5
TK-22M Tel. UHF Conv. 193-5
TK-23M Tel. UHF Conv. 193-5
TK-24M Tel. UHF Conv. 193-5
TK-24ME Tel. UHF Conv. [See Model TK17M—Set 193-5]
TK-31M Tel. UHF Conv. [See Model TK17M—Set 193-5]
TK-33M Tel. UHF Conv. [See Model TK17M—Set 193-5]
●VF102, A, C (Ch. TS-7 and Radio Ch. HS-317) 51-14
●VF103, VF103M (Ch. TS-8) 73-8
●VK101, B, M (Ch. TS-5 and Radio Ch. HS-108) 51-14
●VK106 (Ch. TS-9D) Photofact. Servicer 82
●VK106, B, M (Ch. TS-9, A, B, C) 67-13
●VK106, VK107 [Ch. TS-9E, TS-9E1] 77-6
●VT71B, M-A (Ch. 4B through J) 55-16
●VT-73, VT-73A (Chassis TS-4) Lote 71-12
●VT101 (Ch. TS-3) 51-14
●VT105 (Ch. TS-9D) Photofact. Servicer 82
●VT105, VT105M (Ch. TS-9, TS-9A, TS-9B, TS-9C) 67-13
●VT107 (Ch. TS-9D) Photofact. Servicer 82
●VT107, B, M (Ch. TS-9, A, B, C) 67-13
●VT121 (Ch. TS-15) 91A-9
VTK-17M, ME Tel. UHF Conv. [See Model TK17M—Set 193-5]
WR6 (Ch. HS-18) 5-2
WR7, WR8 [See Model WR6—Set 5-2]
WS1C [See Willlys Model 677012—Set 156-14]
WS2C [See Willlys Model 679517—Set 172-12]
●Y17K17, A, AB, B (Ch. TS-402Y) [Also see PCB 106—Set 253-1] 237-8
●Y17T15A, AE (Ch. VTS-402Y) [Also see PCB 106—Set 253-1] 237-8
●Y17T16, B, W (Ch. TS-402Y) [Also see PCB 106—Set 253-1] 237-8
●Y17T20B, E, M (Ch. VTS-418Y) 269-9
●Y21C2 (Ch. TS-502Y) [Also see PCB 106—Set 253-1] 237-8
●Y21C2A, AB (Ch. VTS-502Y) [See PCB 106—Set 253-1 and Model Y17K17—Set 237-8]
●Y21C2B (Ch. TS-502Y) [Also see PCB 106—Set 253-1] 237-8
●Y21F5, B (Ch. TS-502Y, QTS-502Y and Radio Ch. HS-403) [Also see PCB 106—Set 253-1] 237-8
●Y21K12A, AB, AW (Ch. VTS-502Y) [Also see PCB 106—Set 253-1] 237-8
●Y21K12C, CB, CW, D, DB, DW (Ch. VTS-502Y) [See PCB 106—Set 253-1 and Model Y17K17—Set 237-8]
●Y21K12G (Ch. RTS-502Y) [See PCB 106—Set 253-1 and Model Y17K17—Set 237-8]
●Y21K13 (Ch. TS-502Y) [Also see PCB 106—Set 253-1] 237-8
●Y21K13A, AB (Ch. RTS-502Y) [See PCB 106—Set 253-1 and Model Y17K17—Set 237-8]
●Y21K14 (Ch. TS-502Y, QTS-502Y) [Also see PCB 106—Set 253-1] 237-8
●Y21K14A, AB (Ch. RTS-502Y) [See PCB 106—Set 253-1 and Model Y17K17—Set 237-8]
●Y21K14B (Ch. TS-502Y, QTS-502Y) [Also see PCB 106—Set 253-1] 237-8
●Y21K15A (Ch. RTS-502Y) [See PCB 106—Set 253-1 and Model Y17K17—Set 237-8]
●Y21K16 (Ch. TS-502Y, QTS-502Y) [Also see PCB 106—Set 253-1] 237-8
●Y21K17 (Ch. TS-502Y) [Also see PCB 106—Set 253-1] 237-8
●Y21K17A (Ch. VTS-502Y) [See PCB 106—Set 253-1 and Model Y17K17—Set 237-8]
●Y21T8A, AE (Ch. VTS-502Y) [Also see PCB 106—Set 253-1] 237-8
●Y21T11, B (Ch. VTS-524Y) [See PCB 106—Set 253-1 and Model Y17K17—Set 237-8]
●Y21T11E (Ch. TS-507Y) [See PCB 106—Set 253-1 and Model Y17K17—Set 237-8]
●Y21T15 (Ch. VTS-518YA-02) 269-9
●Y21T16, B, E (Ch. VTS-518Y) 269-9
●Y21T17, Y21T17B (Ch. VTS-518Y) 269-9
●Y24K1, B, Y24K2, B, Y24K3, W (Ch. TS-602Y) 233-6
●Y27K2, B, Y27K3 (Ch. TS-602Y) 233-6
2MF [See Ford Model 2MF—Set 175-10]
3MF [See Ford Model 3MF—Set 206-6]
3MFT [See Ford Model 3MFT—Set 215-7]
5A1 (Ch. HS-6) 2-11
5A5 (Ch. HS-15) 3-11
5A7 (Ch. HS-62), 5A7A (Ch. HS-62A) 116-9
5C1 (Ch. HS-228) 116-9
5C2 (Ch. HS-258) 116-9
5C3 (Ch. HS-262) 116-9
5C4 (Ch. HS-270) 116-9
5C5 (Ch. HS-271) [See Model SC1—Set 116-9]
5C6 (Ch. HS-272) [See Model SC1—Set 116-9]
5H11U, 5H12U, 5H13U (Ch. HS-224) 117-9
5J1 (Ch. HS-250), 5J1U (Ch. HS-224) 100-7
5J2 (Ch. HS-250) [See Model 5J1—Set 100-7]
5J2U (Ch. HS-224) [See Model 5J1—Set 100-7]
5L1 (Ch. HS-250), 5L1U (Ch. HS-224) 100-7
5L2 (Ch. HS-250) [See Model 5J1—Set 100-7]
5L2U (Ch. HS-224) [See Model 5J1—Set 100-7]
5M1, 5M1U, 5M2, 5M2U (Ch. HS-249, HS-223) 101-7
5R11, 5R12, 5R13, 5R14A, 5R15A, 5R16A (Ch. HS-280) [See Model 5R11U—Set 115-6]
5R11U, 5R12U, 5R13U, 5R14U, 5R15U, 5R16U, [Ch. HS-242] 115-6
5X11U, 5X12U, 5X13U (Ch. HS-243) 114-7
5X21U, 5X22U, 5X23U (Ch. HS-259) 120-9
6F11, 6F11B (Ch. HS-264) 117-10
6L1, 6L2 (Ch. HS-226) 102-7
6X11U, 6X12U (Ch. HS-245) 112-5
7F11, 7F11B (Ch. HS-265) 113-5
7V11, 7V12, 7V15 (Ch. TS-18) 83-6
8FDT [See Ch. 8A—Set 46-16]
8FM21, 8FM21B (Ch. HS-147) 121-9
8GM1T [See Ch. 8A—Set 46-16]
9FM21, 9FM21B (Ch. HS-246) 114-8
●9T1 (Ch. TS-18, A) [See Model 7V11—Set 83-6]
●9V11, 9V15 (Ch. TS-18, A) 83-6
10T2 (Ch. TS-148) 92-4
10VK9 (Ch. TS-9E, TS-9E1) 77-6
10VK12 (Ch. TS-14, A, B) 92-4
10VK22 (Ch. TS-14, A, B) 92-4
10V13 (Ch. TS-9E, TS-9E1) 77-6
10V10 (Ch. TS-14, A, B) 92-4
10V12A (Ch. TS-14, A, B) 92-4
12K1, B (Ch. TS-23B) 92-4
12K1, B (Ch. TS-23) [See Model 12K2—Set 115-7]
12K2, B (Ch. TS-23) 92-4
12K2, B (Ch. TS-53) 115-7
12K3, B (Ch. TS-53) [See Model 12K2—Set 115-7]
12T1, B (Ch. TS-23B) 92-4
12T1, B, 12T2, B (Ch. TS-53) [See Model 12T3—Set 115-7]
12T3 (Ch. TS-53) 115-7
12VF4B, R, R-C (Ch. TS-23, A and Radio Ch. HS-190) 92-4
NOTE: PCB Denotes Production Change Bulletin. Production Change Bulletin Nos. 1 Through 63 Are All Contained in Set No. A-200. ● Denotes Television Receiver.

MERCURY—Cont.
●2081 (Ch. 150-4 and Radio Ch. 155) 198-11
●2113, 2115 (Ch. 150-11, -8) [Also see PCB 57—Set 191-1] 172-6
●2116, 2117 (Ch. 150-8) [See PCB 57—Set 191-1 and Model 2013—Set 172-6]
●2181 (Ch. 150-31, -61 and Radio Ch. 155) 198-11
●2217, 2218, X (Ch. 200-11) 216-8
●2224 (Ch. 200-11) 216-8
●2401 (Ch. 150-5, -51) [Also see PCB 57—Set 191-1] 172-6
●2424 (Ch. 201-34) 254-9
●2701 (Ch. 201-553, Audio Amp. Ch. 159-1 and Radio Ch. 160-1) 254-9
●4120 (Ch. 150-2) [Also see PCB 57—Set 191-1] 172-6
●4220 (Ch. 150) [Also see PCB 57—Set 191-1] 172-6
●4317 (Ch. 150-9) 172-6
●4320 (Ch. 150-2, -15) [Also see PCB 57—Set 191-1] 172-6
●4421 (Ch. 150-81) [See Model 2013—Set 172-6 and PCB 57—Set 191-1]
Ch. 150-2 [See Model 2013]
Ch. 150-4 [See Model 2081]
Ch. 150-5 [See Model 2401]
Ch. 150-9 [See Model 4317]
Ch. 150-11 [See Model 2113]
Ch. 150-12 [See Model 4317]
Ch. 150-15 [See Model 4320]
Ch. 150-31 [See Model 2181]
Ch. 150-51 [See Model 2401]
Ch. 150-61 [See Model 2181]
Ch. 150-81 [See Model 2113]
Ch. 155 [See Model 2081]
Ch. 159-1 [See Model 2701]
Ch. 160-1 [See Model 2424]
Ch. 200-11 [See Model 2217]
Ch. 201-34 [See Model 2241]
Ch. 201-553 [See Model 2701]
MIDLAND
M68 2-30
MIDWEST
P6, PB-6 14-19
R-12, RG-12, RT-12 (Ch. RGL-12) 44-12
R-12, RG-12, RT-12 (Ch. RGT-12) 44-13
R-16, RG-16, RT-16 (Ch. RGT-16) 45-16
S8, ST-8 (Ch. STM-8) 15-19
S-12, SG-12, ST-12 (Ch. SGT-12) 21-23
S-16, SG-16, ST-16 (Ch. SGT-16) 21-24
TM-8 (Ch. STM-8) 15-19
716, A [See Model S-16—Set 21-24]
Ch. KD-16 263-10
Ch. RN-16 263-10
MILWAUKEE ERWOOD (See Record Changer Listings)
MINERVA
L-702 12-20
L-728 11-15
W-177, Tropic Master 11-15
W-107-3 11-14
W-112B 12-20
W-710, W710A (W119) 5-25
W-728 11-15
410, 411 41-14
702B, 72H-1 30-18
729 (Partapal) 23-14
MIRRORTONE (Also see Meck)
●A-17C, T (Ch. 9040) 216-4
●A-21C, CB, T, TB, X, Z (Ch. 9040) 216-4
●A24C (Ch. 9049, 9051) 247-6
●14MTS 163-7
●16MC, MT, 17MC, MT, MZ-C, MZ-T 163-7
●17PC (Ch. 9025) (Series 'P') [See Model 20PC—Set 175-12]
●17PCSB, 17PCW 204-5
●17PT (Ch. 9025) (Series 'P') [See Model 20PC—Set 175-12]
●17PTE 204-5
●20NC, MT, MZ-C, MZ-T 163-7
●20PC 175-12
●20PCSB, 20PCW 204-5
●20PTCS [See Model 20PC—Set 175-12]
●20PTE, 20PTS, 20PTSB, 20PTW 204-5
●20PRSB 204-5
●21PCS 204-5
●21QDCS 204-5
●24QDCS 204-5
Ch. 9040 [See Model A-17C]
Ch. 9047 251-11
Ch. 9048 250-14
Ch. 9049 247-6
Ch. 9050 250-14
Ch. 9051 247-6
Ch. 9053, 9054 250-14
Ch. 9055 251-11
MITCHELL
●T16-B, -M, T16-2KB, T16-2KM, T17-2B, T17-2M, T17-2MM 154-8
●T12-B, T12-M, T12-

MOTOROLA-PACKARD

MOTOROLA-Cont.

Table listing Motorola models and their specifications, including model numbers like 107F31, 107F31B, 309, 400, 401, 402, 403, 404, 405, etc.

MOTOROLA-Cont.

Table listing Motorola models and their specifications, including model numbers like Ch. HS-246, Ch. HS-247, Ch. HS-249, Ch. HS-250, etc.

MOTOROLA-Cont.

Table listing Motorola models and their specifications, including model numbers like Ch. TS-418Y, Ch. TS-501A, Ch. TS-501Y, etc.

MUNTZ-Cont.

Table listing Muntz models and their specifications, including model numbers like 2461-A, 2763A, 2764A, 2765A, etc.

OLYMPIC-Cont.

Table listing Olympic models and their specifications, including model numbers like TV-944, TV-945, TV-946, etc.

NOTE: PCB Denotes Production Change Bulletin. Production Change Bulletin Nos. 1 Through 63 Are All Contained in Set No. A-200. * Denotes Television Receiver.

RCA VICTOR—Cont.

Swathmore (See Model 27D32, U) Taltbot (See Models 16T152, 21S36ZC, GU, M, MU) Wayne (See Model 17T301) Westland (See Model 21T242) Whitfield (See Model 17T154) Winston (See Model 7T132) York (See Model 9T57, 9T105) Yorktown (See Model 21D327, U)

RME

DB-22A 50-14
HF10-20 49-17
VHF 2-11 79-14
VHF-152A 51-18
45 13-25
84 14-13
200 Tel. UHF Conv. 219-8

RADIOLA

61-1, 61-2, 61-3 (Ch. RC-1011) 14-25
61-5 (Ch. RC-1023) 12-25
61-6, 61-9 (Ch. RC-1034) 27-21
61-10 (Ch. RC-1023B) 12-35
62-2 (See RCA Model 65U-1)—Set 14-23
732U (Ch. RC-1063A) 36-19
752X1, 762X12 (Ch. RC-1058, RC-1058A) 36-20
Ch. RC-1011 (See Model 61-1)
Ch. RC-1023, RC-1023B (See Model 61-5)
Ch. RC-1023B (See Model 61-10)
Ch. RC-1034 (See Model 61-8)
Ch. RC-1058, RC-1058A (See Model 762X11)
Ch. RC-1063A (See Model 752U)

RADIO CRAFTSMEN

(Also see Craftsmen)
C400 186-11
RC-1 (Tuner), RC-2 (Audio Amp.) 39-19
"Kitchenaire" 6-14
RC-8 66-13
RC-10 110-12
RC100 96-9
RC-100A (Also see PCB 39—Set 170-2) 117-11
RC101 142-10
RC200 (Also see PCB 40 —Set 172-1) 140-9
RC201 151-10
2 176-8
10 184-13
202 184-13
500 164-8
800 204-8

RADIO DEVELOPMENT & RESEARCH CO.
(See Magic-Tone)

RADIOETTE 50-15
PR-2

RADIONIC
(Also see Chancellor)

Y62W, Y728 26-22

RADIO MFG. ENGINEERS
(See RME)

RADIO RECEPTOR

C-1709-P Tel. UHF Conv. 222-12

RADIO WIRE TELEVISION
(See Lafayette)

RANGER

118 28-27
RAULAND
BA21 87-10
BAU21 211-10
W-819-A 43-16
1801A 251-15
1805A 251-5
1810 179-10
1814 99-13
1820 100-10
1821, 1822 59-17
1825 97-14
1826 (1801A, 1805) 251-15
1835 58-19
1841 140-10
1904 229-12
1932 148-14
1940 208-9
1960 212-4
2100 (Sub-station) 39-20
2101-A (Master Station) 39-20
2105 (Master Station) 36-21
2106-F, 2106H-F 236-11
2112-F, 2112H-F 236-11
2206, 2206H, 2212, 2212H, 2218, 2218H, 2224, 2224H 80-13
2306, 2312, 2324 87-10
2400 Series 33-12
3406, H 210-6
3412, H 210-6
3424, H 210-6

RAY ENERGY

AD 7-24
AD4 7-25
SRB-1X 13-26

RAYTHEON (Also see Belmont)

●A-7DX22P (See Model 7DX21—Set 81-13)
●A-10DX24, B-10DX22 (Also see PCB 1—Set 103-19) 75-14
CR-41, CR-42, A, CR-43, A (Ch. 4D16-A) 212-5
●C1102 (Ch. 12AX22) (Also see PCB 3—Set 105-1) 94-8
●C1104 (Ch. 12AX22) (Also see PCB 3—Set 105-1) 94-8
●C-1104B (Ch. 12AX26, 12AX27) 141-11
●C-1401 (Ch. 14AX21) 123-12
●C-1602, A, B, C (Ch. 16AX23, 25, 26) 99-14
●C-1602, Series 2 (Ch. 16AX29) (See PCB 16—Set 126-1 and Model C-1602—Set 99-14) 124-8
●C-1614A (Ch. 16AY21) (See PCB 19—Set 132-1 and Model C-1615A—Set 124-8)

RAYTHEON—Cont.

●C-1614B (Ch. 16AY28) (See PCB 19—Set 132-1 and Model C-1615B—Set 124-8)
●C-1615A (Ch. 16AY21), C-1615B (Ch. 16AY28) (Also see PCB 19—Set 132-1) 124-8
●C-1616A (Ch. 16AY21), C-1616B (Ch. 16AY28) (Also see PCB 19—Set 132-1) 124-8
●C-1714A (Ch. 17AY24) (See PCB 19—Set 132-1 and Model C-1715A—Set 124-8)
●C-1714B (Ch. 17AY21) (Also see PCB 19—Set 132-1) 124-8
●C-1715A (Ch. 17AY24), C-1715B (Ch. 17AY21) (Also see PCB 19—Set 132-1) 124-8
●C-1716A (Ch. 17AY24), C-1716B (Ch. 17AY21) (Also see PCB 19—Set 132-1) 124-8
●C-1724A (Ch. 17AY21) (See PCB 19—Set 132-1 and Model C-1615A—Set 124-8)
●C-1729, C-1731A (Ch. 17AY21A) 176-10
●C-1735A, C-1736A (Ch. 17T1) (Also see PCB 87—Set 230-1) 189-14
●C-1739A, C-1741A (Ch. 17T4) (See PCB 87—Set 230-1 and Model C-1735A—Set 189-14)
●C-2001A, C-2002A (Ch. 20AY21) (Also see PCB 43—Set 177-1) 149-9
●C-2006A (Ch. 20AY21) (Also see PCB 43—Set 177-1) 149-9
●C-2103A, C-2105A (Ch. 21AY21) 173-1A
●C-2108A (Ch. 21T1) (Also see PCB 87—Set 230-1) 189-14
●C-2109A (Ch. 21T2) (For TV Ch. See PCB 87—Set 230-1 and Model C-1735A—Set 189-14, For UHF Tuner See Model UHF-100—Set 207-8)
●C-2110A, C-2111A (Ch. 21T1) (Also see PCB 87—Set 230-1) 189-14
●C-2112A, C-2113A, C-2114A, C-2115A, C-2116A, C-2118A (Ch. 21T3) (Also see PCB 87—Set 230-1) 202-7
●C-2127A, C-2129A (Ch. 21T5) (See PCB 87—Set 230-1 and Model C-1735A—Set 189-14)
●C-2137A, C-2138A (Ch. 21T1) 244-8
●C-2401A, C-2402A (Ch. 24T3) 246-9
FR81A, FR82A (Ch. 9AF25A) 232-6
●M701 (Ch. 10AX22) (Also see PCB 3—Set 105-1) 94-8
●M1101, M1103, M1105 (Ch. 12AX-22) (Also see PCB 3—Set 105-1) 94-8
●M1105X, M-1106, M-1107 (Ch. 12AX26, 12AX27) 141-11
●M-1402, M-1403, M-1404 (Ch. 14AX21) 123-12
●M-1601 (Ch. 16AX23, 25, 26) 99-14
●M-1611A (Ch. 16AY21), M-1611B (Ch. 16AY28) (Also see PCB 19—Set 132-1) 124-8
●M-1612A (Ch. 16AY21), M-1612B (Ch. 16AY28) (Also see PCB 19—Set 132-1) 124-8
●M-1613A (Ch. 16AY21), M-1613B (Ch. 16AY28) (Also see PCB 19—Set 132-1) 124-8
●M-1626 (Ch. 16AY21) 165-2A
●M1711A (Ch. 17AY24), M1711B (Ch. 17AY21) (Also see PCB 19—Set 132-1) 124-8
●M-1712A (Ch. 17AY24), M-1712B (Ch. 17AY21) (Also see PCB 19—Set 132-1) 124-8
●M-1713A (Ch. 17AY24), M-1713B (Ch. 17AY21) (Also see PCB 19—Set 132-1) 124-8
●M1725A (Ch. 17AY21) (See PCB 19—Set 132-1 and Model M-1711B—Set 124-8)
●M-1726 (Ch. 17AY21), (See PCB 19—Set 132-1 and Model M-1711B—Set 124-8)
●M-1726A, M-1728A (Ch. 17AY21A) 176-10
●M-1733A (Ch. 17T1) (Also see PCB 87—Set 230-1) 189-14
●M-1733A, A, mA (Ch. 17T1) (See PCB 87—Set 230-1 and Model C-1735A—Set 189-14)
●M-1734A (Ch. 17T2) (For TV Ch. See PCB 87—Set 230-1 and Model C-1735A—Set 189-14, For UHF Tuner See Model UHF-100—Set 207-8)
●M-1737, iA, mA (Ch. 17T4) (See PCB 87—Set 230-1 and Model C-1735A—Set 189-14)
●M-1750A, C, G, K, M-1751D, F, M-1752E, M-1753H, 261-13
●M-2007A, M-2008A (Ch. 20AY21) (See PCB 43—Set 177-1 and Model C-2001A—Set 149-9)
●M-2101A (Ch. 21AY21) (See Model C-2103A) 173-1A
●M-2107A (Ch. 21T1) (Also see PCB 86—Set 230-1) 189-14
●M-2107bA, iA, mA (See PCB 87—Set 230-1 and Model C-1735A—Set 189-14)
●M-2125A, mA (Ch. 21T5) (See PCB 87—Set 230-1 and Model C-1735A—Set 189-14)
●M-2131A (Ch. 21T1) 244-8
●M-2160A, C, G, K, M-2160D, F, M-2161E, L (Ch. 21T19) 261-13
PR-501 (See Model 7DX21—Set 81-13)
PR-51, A (Ch. 4P12, A) 218-9
●RC-1405 (Ch. 14AX21) (For TV Ch. only see Model C-1401—Set 123-12)
●RC-1618A (Ch. 16AY21), RC-1618B (Ch. 16AY28) (Also see PCB 19—Set 132-1) 124-8
●RC-1619A (Ch. 16AY21) (Also see PCB 19—Set 132-1) 124-8

RAYTHEON—Cont.

●RC-1619B (Ch. 16AY28) (Also see PCB 19—Set 132-1) 124-8
●RC-1718A (Ch. 17AY24) (See PCB 19—Set 132-1 and Model M-1711B—Set 124-8)
●RC-1718B (Ch. 17AY21) (Also see PCB 19—Set 132-1) 124-8
●RC-1719A (Ch. 17AY24) (See PCB 19—Set 132-1 and Model M-1711A—Set 124-8)
●RC-1719B (Ch. 17AY21) (Also see PCB 19—Set 132-1) 124-8
●RC-1720A (Ch. 17AY27) 147-9
●RC-2005A (Ch. 20AY21) (See PCB 43—Set 177-1 and Model C-2001A—Set 149-9)
●RC-2117A (Ch. 21T3) (Also see PCB 89—Set 233-1) 202-7
●RC-2121A, RC-2122A, RC-2123A (Ch. 21T3) (See PCB 89—Set 233-1 and Model C-2112A—Set 202-7)
●UC-1735A, UC-1736A (Ch. 17T2) (For TV Ch. See PCB 87—Set 230-1 and Model C-1735A—Set 189-14, For UHF Tuner See Model UHF-100—Set 207-8)
●UC-1740A, UC-1742A (Ch. 17T5) (For TV Ch. See PCB 87—Set 230-1 and Model C-1735A—Set 189-14, For UHF Tuner See Model UHF-100—Set 207-8)
●UC-2109A, UC-2110A (Ch. 21T2) (For TV Ch. See PCB 87—Set 230-1 and Model C-1735A—Set 189-14, For UHF Tuner See Model UHF-100—Set 207-8)
●UC-2128A, UC-2130A (Ch. 21T6) (For TV Ch. See PCB 87—Set 230-1 and Model C-1735A—Set 189-14, For UHF Tuner See Model UHF-100—Set 207-8)
●UC-2403A, UC-2404A, UC-2405A, UC-2406A (Ch. 24T2) 237-9
●UM-1734B, iA, mA (Ch. 17T2) (For TV Ch. See PCB 87—Set 230-1 and Model C-1735A—Set 189-14, For UHF Tuner See Model UHF-100—Set 207-8)
●UM-1738iA, mA (Ch. 17T5) (For TV Ch. See PCB 87—Set 230-1 and Model C-1735A—Set 189-14, For UHF Tuner See Model UHF-100—Set 207-8)
●UM-2107bA, iA, mA (Ch. 21T2) (For TV Ch. See PCB 87—Set 230-1 and Model C-1735A—Set 189-14, For UHF Tuner See Model UHF-100—Set 207-8)
●UM-2125A, mA (Ch. 21T5) (For TV Ch. See PCB 87—Set 230-1 and Model C-1735A—Set 189-14, For UHF Tuner See Model UHF-100—Set 207-8)
●7DX21, 7DX22P 81-13
●10AXF23 (Also see PCB 3—Set 105-1) 75-14
●10AXF44 (See Model C-1102—Set 94-8 and Model A-10DX24—Set 75-14)
●10DXK1, 10DXK2 (Also see PCB 3—Set 105-1) 75-14
●10DXK4 (See Model A-10DX24—Set 75-14)
●18DX21A 81-13
Ch. 4D16-A (See Model CR-41, A)
Ch. 4P12, A (See Model PR-51, A)
Ch. 8AF25A (See Model FR81A)
Ch. 10AX22 (See Model M701)
Ch. 12AX22 (See Model C1102)
Ch. 12AX26, 12AX27 (See Model C-1104B)
Ch. 14AX21 (See Model C-1401)
Ch. 16AX23, 25, 26 (See Model C-1602)
Ch. 16AY28 (See Model C-1615B)
Ch. 16AY21 (See Model C-1615A)
Ch. 1711B (Also see PCB 19—Set 132-1)
Ch. 16AY212 (See Model M-1626)
Ch. 17AY21 (See Model C-1714B)
Ch. 17AY21A (See Model C-1729)
Ch. 17AY24 (See Model C-1715A)
Ch. 17AY27 (See Model RC-1720A)
Ch. 17T2 (See Model C-1735A)
Ch. 17T2 (See Model M-1734A)
Ch. 17T4 (See Model C-1741A)
Ch. 17T5 (See Model UC-1740A)
Ch. 17T18 (See Model M-1750A)
Ch. 20AY21 (See Model C-2001A)
Ch. 21AY21 (See Model C-2103A)
Ch. 21T1 (See Model C-2108)
Ch. 21T2 (See Model C-2109A)
Ch. 21T3 (See Model C-2112A)
Ch. 21T5 (See Model C-2127A)
Ch. 21T6 (See Model UC-2128A)
Ch. 21T8 (See Model UC-2139A)
Ch. 21T11 (See Model C-2137A)
Ch. 21T19 (See Model M-2160A)
Ch. 24T2 (See Model UC-2403A)
Ch. 24T3 (See Model C-2401A)

RECORDIO (Wilcox-Gay)

1B10 149-10
1C10 146-9
1J10 (Ch. 1J1) 128-12
2A10 163-10
6A10, 6A20 (Ch. 6A) 10-27
6B10, 6B20, 6B30, 6B32 8-27
7D42, 7D44 (Ch. 7D1) 52-18
7E40, 7E44 47-20
9C10, 9I50 62-17
9C10 91-10
9H40M, 9G42 86-9
9H40M 89-13
Ch. 1J1 (See Model 1J10)
Ch. 6A (See Model 6A10)
Ch. 7D1 (See Model 7D42)

RELEST
(See Recorder Listing)

REGAL (TOK-FONE)

Tok-Fone (20-watt Amp.) 13-27
AP40, ARP400, ARP450 15-26
BP48 49-18
C473 217-12
C-527 182-9
●CD31 (See Model 16T31—Set 80-14)
CR761 50-16
CR762 195-11
CR871 238-11
FM78 68-14
L-74 17-8
P-175 183-12
W700 (See Model W800—Set 14-26)
W800, W801 14-26
W900, W901 13-28
●16T31 80-14
●17HD31, 17HD36 147-10
●17T22, 17T22DX 143-13
●19C31, 19C36 147-10
●19D31, 19D36 147-10
●20C22, 20C22DX 143-13
●20C31, 20C36 143-13
●20D22, 20D22X 147-10
●20D31, 20D36 147-10
●20HD31, 20HD36 147-10
●20T22, 20T22DX 143-13
●22D17, 22D17DX, 22D19, 22D19DX 143-13
205 26-23
208 (See Model W800—Set 14-26)
271 210-7
472 217-12
575 210-8
747 27-22
777 53-27
●1007 83-9
1030, 1031 80-14
1049 17-28
1107 41-19
●1207, 1208 83-9
●1230 80-14
●1300 38-10
●1607 83-9
●1708, 1708DX 143-13
1749 28-29
1877 182-10
●2217, 2217DX, 2219, 2219DX 143-13
7152 70-8
7162 69-12
7163 66-14
7251 40-16

REGENCY

HF-150 265-10
RC-53 Tel. UHF Conv. 266-12
RC-600 Tel. UHF Conv. 200-8

REMBRANDT

●721, 1606, 1606-15, 1950 65-11
MP5-5-3 8-28
5300B, 5300B1, 53001 23-18
5310 40-17
5400, 5410 44-19
5500 "Scottie Pup" 27-23
5505 "Scottie Pup" (See Model 5500—Set 27-23)
5510 "Scottie Pup" 27-23
5515 "Scottie Pup" (See Model 5500—Set 27-23)
5520, 5530 "Scottie Junior" 27-23
6000 77-9

RENNARD

L-1A, PT-1A, 185T-1 9-28

REVERE (Also See Recorder Listing)

400 269-13

ROLAND

4P2 266-13
4T1 213-7
SC1 225-14
SC2 223-13
SP2 233-9
SP4 205-8
ST1E 208-10
ST2A 204-10
ST3 231-14
ST4 238-12
ST5 234-11
5K1, 5X2 217-3
5K3, 5X4 236-12
6P2 236-12
6T1M 216-9
8FT1M 211-9
8XF1, 8XF2 249-13
8XF3-M, 8XF4-M 249-14
10TF1

ROYAL (Lee)

AN150, AN160 179-11
●20CP, 20TW (Similar to Chassis) 149-13

SCOTT (E. H.)

Musical 44-20
Music Control, Dynamic Noise Suppressor 46-21
●"Raventwood" 150-11
●6T11, 6T11A (Also see PCB 45—Set 105-2) 52-19
16A 40-18
310 154-11
●400 (See PCB 4—Set 105-2 and Model 6T11—Set 52-19)
510 103-14
515 165-11
●710, 710A, 710X 150-11
800-B 14-27
●800BT (For TV Ch. see PCB 4—Set 105-2 and Model 6T11—Set 52-19, for Radio Ch. see Model 800C—Set 14-27)
●817C (Ch. 9029, 9031) (See Model 820C—Set 178-9)
●817C (Ch. 9036, 9037, 9038, 9039) 217-14
●817C (Ch. 9043) 234-12
●817C (Ch. 9029, 9031) (See Model 820C—Set 178-9)
●817T (Ch. 9029, 9031) (See Model 820C—Set 178-9)

SCOTT (E. H.)—Cont.

●817T (Ch. 9036, 9037, 9038, 9039) 217-14
●817T (Ch. 9043) 234-12
●817TU (Ch. 9029, 9031) (See Model 820C—Set 178-9) 178-9
●820C 178-9
●820CU 178-9
●820T, 820TU (See Model 820C—Set 178-9) 178-9
●821C (Ch. 9036, 9037, 9038, 9039) 217-14
●821C (Ch. 9043) 234-12
●821CB (Ch. 9036, 9037, 9038, 9039) 217-14
●821CB, CH (Ch. 9043) 234-12
●821D (Ch. 9036, 9037, 9038, 9039) 217-14
●821D, DB, DBH, DM, DMH (Ch. 9043) 234-12
●821RC, RCH (Ch. 9043) 234-12
●821TC (Ch. 9036, 9037, 9038, 9039) 217-14
●821T (Ch. 9043) 234-12
●821TU (Ch. 9036, 9037, 9038, 9039) 217-14
●821TB, TH, TU (Ch. 9043) 234-12
●824C, CH, DB, DBH, DM, DMH (Ch. 9045) 242-9
●910 150-11
●924W 176-11
●924XW (Ch. 9045) 242-9
1000 180-8
1510 181-11
2000 229-13
2510 233-10
Ch. 9029, 9031 (See Model 817C)
Ch. 9036, 9037, 9038, 9039 (See Model 817C)
Ch. 9043 (See Model 817C)
Ch. 9045 (See Model 824C)
Ch. 9052 265-12

SCOTT (H. H.)

99-A 267-17
111-B 143-14
112-B 144-8
120-A 183-13
121-A 265-11
210-A 79-15
210-B 145-8
214-A (120-A, 220-A) 81-13
220-A 183-13

SEARS-ROEBUCK
(See Allstate or Silvertone)

SEEBURG
(See Record Changer Listing)

SENTINEL

1U-284GA 22-25
1U-284NA, 1U-284NI 1-2
1U-284W 6-27
1U-285P 29-29
1U-293CT 1-14
1U-2931, 1U-293T, 1U-293W 1-14
1U-2941, 1U-294N, 1U-2941 1-11
1U-315G, 1U-312PW 103-5
1U-3131, 1U-313W 39-21
1U-314E, 1U-314I, 1U-314W 38-21
1U-316PM, 1U-316PT 48-22
1U-335PG, PL, PM, PW 105-9
1U-338L, 1U-338R, 1U-338W 122-9
1U-339K 111-12
1U-340-C 129-10
1U-342K 155-14
1U-343 212-6
1U-344 211-12
1U-345P 183-14
1U-346 209-11

SENTINEL—SILVERTONE

SENTINEL—Cont.

- 1U-532, A 239-8
• 1U-542, A 239-8
• 1U-552, 1U-554 239-8
• 1U-562, 1U-564 239-8
• 1U-581, 1U-582 240-7
• 1U-581, 1U-585 240-7
• 1U-600 (See PCB 97—Set 242-1 and Model 1U-500—Set 226-8)
• 1U-610, 1U-612 (See PCB 97—Set 242-1 and Model 1U-510—Set 226-8)
• 1U-620, 1U-622 (See PCB 97—Set 242-1 and Model 1U-520—Set 226-8)
• 1U-701 262-11
• 1U-711 262-11
• 1U-714 262-11
• 1U-721 262-11
• 1U-724 262-11
• 1U-752 262-11
• 1U-755 262-11
• 1U-758 262-11
• 1U-762 262-11
• 1U-765 262-11
• 1U-768 262-11
• 1U-791 262-11
L-2841, L-284NA, L-284NI, L-284NR, L-284W 23-19
284GA 22-25
284I 1-2
284NA, 284NI 1-2
285P 6-27
286P, 286PR 23-20
289T 6-28
292K 16-30
293 Series 1-14
293-CT 29-22
293I, 293T, 293W 1-14
294 Series 1-11
294I, 294N, 294T 1-11
295-T 22-26
296B, 296M 46-22
302-1, 302-T, 302-W 33-23
305-1, 305-I-3, 305-W, 305-3P 3-24
309-1, 309-N, 309-R, 309-W 28-30
312PG, 312PW 103-15
313-1, 313-W 39-21
314-E, 314-I, 314-W 38-21
315-1, 315-W 40-19
316PM, 316PT 48-22
332 (See Model 313-1—Set 39-21)
333 (See Model 315-1—Set 40-19)
335PG, PI, PM, PW 105-9
338-1, 338-R, 338-W 122-9
339-K 11-12
340-C 129-10
342K 155-14
343 212-6
344 211-12
345P 183-14
346 209-11
• 400TV 73-11
• 401, 402 Series 70-9
• 405TVM 73-11
• 405 Series 70-9
• 406 Series 70-9
• 407 Series *
• 409 Series *
• 411 Series (See Model 401 Series—Set 70-9)
• 412, 413, 414, 415 (Series YA, YB, YC, YD, YE, YF) (Also see PCB 4—Set 105-2) 100-11
• 416 117-12
• 419, 420 115-9
• 420B 124-9
• 421, 422 (See PCB 16—Set 126-1 and Model 412—Set 100-11)
• 423, 424 (Also see PCB 19—Set 132-1) 132-11
• 423B, 423-17 (See PCB 19—Set 132-1 and Model 423B—Set 124-9)
• 424 (Also see PCB 19—Set 132-1) 124-9
• 424-17 (See PCB 19—Set 132-1 and Model 424—Set 124-9)
• 425 127-10
• 428 127-10
• 429, 430, 431 (See PCB 25—Set 144-1 and Model 1U-420B—Set 124-9)
• 432 (Also see PCB 21—Set 136-1) 127-10
• 435 (See PCB 21—Set 136-1 and Model 425—Set 127-10)
• 438, 439, 440, 441, 443, 444 (Series *XD, XGD, XGD, 2XD) 157-9
• 446 (Series *XD, XGD, 2XD) (See Model 438—Set 157-9)
• 452, 453 (See Model 1U-447-A—Set 178-10)
• 454, 455, 456, 457 (Also see PCB 63—Set 197-1) 191-17
• 458, 459, 460, 461 (See Model 1U-458—Set 199-10)
• 462, 463 (Ch. 2WA) 205-9
• 464, 465, 466 (See Model 1U-454—Set 191-17)
Ch. 2WA (See Model 462)

SETCHEL-CARLSON

- A53, A531, A533, A5301, A5302, A-5303 (Ch. 153) 243-8
• 53 (Ch. 152) 209-12
• 150-9 144-9
• 151-A17, 151-A17-LR, 151-B17, 151-B17-LR, 151-B20, 151-B20-LR, 151-C20, 151-C20-LR 155-15
416 2-14
427 21-29
437 39-22
447 40-20
458-RD 106-13
469 99-15
• 531 (Ch. 152) 209-12
570 97-15
• 2500, 2500LP 144-9
• 5301, 5302 (Ch. 152) 209-12
Ch. 152 (See Model 53)
Ch. 153 (See Model A53)

SHAW

- Ch. 224 (Runs 301, 302, 303, 304, 304-1, -2, 305, 305-2) 202-8

SHERATON

- (Also See Video Products)
• C308, M 176-13
• C3082A, C30M2A 176-13
• C-2125 (Ch. 250XL Series) 218-10
• T30M 176-13
• T-155 (Ch. 250XL Series) 218-10
• T-2155 (Ch. 250XL Series) 218-10
• 17M20 (Ch. 530DX Series) 210-9
• 17M20T (Ch. 530DX-A) (See PCB 89—Set 203-1 and Model 17M20T—Set 210-9)
• 21B10 (Ch. 530DX Series) 210-9
• 21BC10 (Ch. 530DX-A) (See PCB 89—Set 203-1 and Model 17M20T—Set 210-9)
• 21BD10 (Ch. 530DX Series) 210-9
• 21BD10 (Ch. 530DX-A) (See PCB 89—Set 203-1 and Model 17M20T—Set 210-9)
• 21BT10 (Ch. 530DX Series) 210-9
• 21BT10 (Ch. 530DX-A) (See PCB 89—Set 203-1 and Model 17M20T—Set 210-9)
• 21MC10 (Ch. 530DX Series) 210-9
• 21MC10 (Ch. 530DX-A) (See PCB 89—Set 203-1 and Model 17M20T—Set 210-9)
• 21MD10 (Ch. 530DX Series) 210-9
• 21MD10 (Ch. 530DX-A) (See PCB 89—Set 203-1 and Model 17M20T—Set 210-9)
• 21MT10 (Ch. 530DX Series) 210-9
• 21MT10 (Ch. 530DX-A) (See PCB 89—Set 203-1 and Model 17M20T—Set 210-9)
• 21T10 (Ch. 530DX Series) 210-9
• 21T10 (Ch. 530DX-A) (See PCB 89—Set 203-1 and Model 17M20T—Set 210-9)
• 25 530DX (See Model 17M20T)
Ch. 530DX-A (See Model 17M20T)

SHERIDAN ELECTRONICS

(See Vogue)

SIGNAL

- AF252 37-19
141 44-21
241 33-25
341-A 39-23
341-T 25-25

SILVERLINE (See General Instrument)

SILVERTONE (Also see Changer and Recorder Listing)

- 1 (Ch. 132.878) 101-10
1 (Ch. 132.878-1) (See Model 1—Set 101-10)
2 (Ch. 132.878) 101-10
2 (Ch. 132.878-1) (See Model 2—Set 101-10)
5, 6 (Ch. 132.881) 144-10
10, 11 (Ch. 132.896) 144-11
15, 16 (Ch. 132.884, -1, -2) 141-12
18 (Ch. 132.877) 140-11
20 (Ch. 132.877) 140-11
25, 27 (Ch. 478.238) 161-10
33 (Ch. 548.363) 111-13
41, 41A (Ch. 135.245) 107-11
43, A (Ch. 135.245) (See Model 41—Set 101-11)
51, 53 (Ch. 132.887) 112-8
54, 56 (Ch. 132.888) 115-10
64, 65 (Ch. 101.859-2) 113-8
67 (Ch. 101.859-1, -2) (See Model 64—Set 113-8)
67B (Ch. 101.859-2) (See Model 64—Set 113-8)
69 (Ch. 100.201) 162-10
72 (Ch. 134.111) 142-11
• 101 (Ch. 549.100) 102-12
• 101A (Ch. 549.100-1) 102-12
• 102A (Ch. 549.100-3, -7) 161-9
• 106, 107 (Ch. 132.889-2) 149-12
• 108 (Ch. 549.100) 102-12
• 108A (Ch. 478.303, A) (See Model 125—Set 104-10)
• 112 (Ch. 478.289) 118-9
• 114 (Ch. 478.302) (See Model 125—Set 104-10)
• 115 (Ch. 110.499-7A, B, 8A, B) 124-9
• 116, 116A (Ch. 110.700-1, -10) 139-13
• 120 (Ch. 478.311) 115-11
• 125 (Ch. 478.257) 104-10
• 131, 131A (Ch. 110.700-1, -10) 139-13
• 132 (Ch. 110.499-1) (See Model 9123—Set 79-16)
• 133 (Ch. 100.107-1 and Radio Ch. 100.043) 156-12
• 135 (Ch. 110.499-7A, B, 8A, B) 124-9
• 137 (Ch. 549.100-1 and Radio Ch. 101.831-1) (For TV Ch. see Model 101—Set 102-12, for Radio Ch. see Model 8127—Set 41-20)
• 138 (Ch. 549.100-3 and Radio Ch. 101.831-1) (For TV Ch. see Model 102A—Set 161-9, for Radio Ch. see Model 8127—Set 41-20)
• 141 (Ch. 132.889-2) 149-12
• 143 (See Model 143A—Set 121-12)
• 143A (Ch. 100.111) 121-12
• 144 (Ch. 478.312 and Radio Ch. 478.240) 160-11
• 149 (Ch. 100.107-1) (See Model 133—Set 156-12)
• 150-14 (Ch. 478.338) 142-12
• 151-16, 151-17 (Ch. 528.630-1) 102-2
• 152-16, 16A (Ch. 549.102, 549-102-2) 115-11
• 159 (Ch. 478.309) 115-11
• 160-12 (Ch. 549.100-4) 97A-12
• 161-16 (Ch. 100.112) 99A-10
• 162-17 (Ch. 110.700-10) 139-13
• 163-16 (Ch. 478.319) 157-10
• 164-14 (Ch. 478.313) 144-12
• 165-16 (Ch. 100.120) 144-12
• 166-16 (Ch. 478.339) 144-12
• 166-17 (Ch. 478.339-A) 144-12
• 167-16, 167-16A (Ch. 549.101, -1) 102-2
• 168-16 (Ch. 549.100-3) 161-9
• 169-16 (Ch. 549.102, 549-102-2) 206, 206I (Ch. 101.861, -1)

SILVERTONE—Cont.

- 170-16 (Ch. 549.102, 549.102A) 203-9
• 173-16 (Ch. 110.700-10) 139-13
• 175-16, A (Ch. 549.100-5, -8, -9) 161-9
• 176-19 (Ch. 549.100-6) 161-9
• 177-19 (Ch. 110.700-40) 139-13
• 179-16, 180-16 (Ch. 132.890) 130-12
• 185-16 (Ch. 549.101-2) *
• 187-16 (Ch. 188-16) (Ch. 110.700-10) (See Model 116—Set 139-13)
• 189-16 (Ch. 110.700-1, -10) 139-13
• 194-16, 195-16 (Ch. 132.890) 130-12
210 (Ch. 132.880) 109-22
215 (Ch. 528.174) 117-13
217, 218 (Ch. 528.174) (See Model 215—Set 117-13)
220 (Ch. 528.173) 110-13
222, 223, 224 (Ch. 528.173) (See Model 220—Set 110-13)
225 (Ch. 528.171-1) 107-8
237 (Ch. 488.237) 145-10
238 (Ch. 548.360-1, 548.361) (See Model 239—Set 115-12)
239 (Ch. 548.360-1, 548.361) 111-12
245 (Ch. 548.358-1) 107-9
246 (Ch. 137.906) 111-14
249 (Ch. 548.360-1, 548.361) 115-12
1017, 1018 (Ch. 528.210, -1, -2) 182-11
1032 (Ch. 528.196) 183-16
1035-A (Ch. 528.195, -1, -2) 215-12
1038 (Ch. 528.219) (See Model 1040—Set 181-12)
1040, 1045 (Ch. 528.194) 181-12
1040C (Ch. 528.194-1) (See Model 1040—Set 181-12)
1045A (Ch. 528.194-1) (See Model 1040—Set 181-12)
1052 (Ch. 132.011) 174-10
1052A (Ch. 132.011-1) (See Model 1052—Set 174-10)
1053 (Ch. 132.011) 174-10
1053A (Ch. 132.011-1) (See Model 1053—Set 174-10)
1054 (Ch. 132.012) 173-12
1054A (Ch. 132.012-1) (See Model 1054—Set 173-12)
1055 (Ch. 132.012) 173-12
1055A (Ch. 132.012-1) (See Model 1055—Set 173-12)
1058, 1059 (Ch. 101.860) 162-11
1062, 1063 (Ch. 101.860) 162-11
1066 (Ch. 100.202) 162-10
• 1117-17 (Ch. 110.700-10) 201-8
• 1130-17, 1130A-17 (Ch. 110.700-100, -104) 201-8
• 1141-20 (Ch. 110.700-120) 201-8
• 1145-20 (Ch. 110.700-140) 201-8
• 1150-14 (Ch. 478.361, A) 101-10
• 1161-17 (Ch. 110.702-10) 205-10
• 1162-17 (Ch. 110.700-100, -104) 201-8
• 1166-17 (Ch. 478.339-B) 201-8
• 1171-17 (Ch. 110.702-10, -50) 205-10
• 1172-17 (Ch. 110.700-100, -104) 201-8
• 1173-20 (Ch. 110.700-140) 201-8
• 1176-21 (Ch. 100.208) 165-12
• 1181-20 (Ch. 110.700-120) 201-8
• 1182-21 (Ch. 110.700-150) 201-8
• 1184-20 (Ch. 528.631, -1) 181-13
• 1186-21 (Ch. 100.208) 165-12
• 1188-20 (Ch. 110.700-140) 201-8
1239 (Ch. 488.237) (See Model 239—Set 115-12)
• 1260 (Ch. 456.150, -2, -6, -15) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
• 1261 (Ch. 456.150, -2, -21) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
• 1266 (Ch. 456.150, -2, -6, -15) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
• 1268 (Ch. 456.150, -1, -11, -81) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
• 1270, 1271 (Ch. 456.150-1, -11) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
• 1272 (Ch. 456.150-1, -11, -81) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
• 1273, 1274, 1275 (Ch. 456.150-1, -11) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
• 1297, 1298 (Ch. 456.150-3) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
• 1299 (Ch. 456.150-7, -9, -17) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
• 1300 (Ch. 319.200), 1300-1 (Ch. 319.200-1) 90-10
1301 (Ch. 319.190) 91-11
2001, 2002 (Ch. 132.878) (See Model 1—Set 101-10)
2003, 2004, 2005, 2006 (Ch. 757-201) 198-12
2007 (Ch. 757.100) 198-12
2009, 2010, 2011, 2012, 2013 (Ch. 132.022) 196-14
2014, 2015, 2016 (Ch. 132.021) 196-15
2018, 2019 (Ch. 757.100-1) 266-4
2022 (Ch. 132.027) 197-11
2023, 2024, 2025, 2026, 2027 (Ch. 132.896-1) (See Model 10—Set 144-11)
2028 (Ch. 528.230) 203-8
2035A (Ch. 528.195, -1, -2) 215-12
2041 (Ch. 528.235) 208-11
2041 (Ch. 528.235-1) (See Model 2041—Set 208-11)
• 2054 (Ch. 132.026-3) 207-9
2060, 2061 (Ch. 101.861, -1)

SILVERTONE—Cont.

- 2063, 2064 (Ch. 101.860, -1) (See Model 1058—Set 162-11)
2068 (Ch. 100.202) (See Model 1066—Set 162-10)
• 2100 (Ch. 110.700-100, -104) 201-8
• 2100A (Ch. 110.817-1) 217-15
• 2105 (Ch. 132.024, -1, -2) 198-13
• 2105A (Ch. 132.024-3) 311
• 2110A, 2111 (Ch. 528.631, -1, Ch. 528.632, -1, -2, -3, -4, -5, Ch. 528.632A, -1, -2, -3, -5) 212-7
• 2115B (Ch. 528.631, -1, Ch. 528-632, -1, -2, -3, -4, -5, Ch. 528-632A, -1, -2, -3, -5) 212-7
• 2130 (Ch. 100.210, -1, -3) 207-10
• 2140 (Ch. 110.817-1) 217-15
• 2145 (Ch. 132.024, -1, -2) 198-13
• 2145A (Ch. 132.024-3) 311
• 2145B (Ch. 132.024-4) 198-13
2150 (Ch. 110.700-140) 201-9
• 2150A (Ch. 110.820-11) 217-15
• 2150B (Ch. 528.631, -1, Ch. 528-632, -1, -2, -3, -4, -5, Ch. 528-632A, -1, -2, -3, -5) 212-7
• 2160, 2162 (Ch. 528.631, -1, Ch. 528.632, -1, -2, -3, -4, -5, Ch. 528.632A, -1, -2, -3, -5) 212-7
• 2170-C (Ch. 100.209) 193-10
• 2170-D, -E (Ch. 100.210, -1, -3) 207-10
• 2172 (Ch. 100.210, -1, -3) 207-10
• 2174 (Ch. 132.035) (See PCB 99—Set 220-1 and Model 3174—Set 206-11)
• 2195-21 (Ch. 100.208-1 and Radio Ch. 100.202-1) (See PCB 59—Set 193-1 and Model 1176-21—Set 165-12 for TV Ch. and Model 1066—Set 162-10 for Radio Ch.)
2200, 2202, 2203 (Ch. 528.229) 201-9
2210 (Ch. 132.880) (See Model 210—Set 109-12)
2215, 2217, 2218 (Ch. 528.238) 225 (Ch. 528.233) 208-12
2243 (Ch. 137.914, -1, -2, -3) 201-9
2246 (Ch. 137.914, -1, -2, -3) 230-9
2249, 2250 (Ch. 137.915) 259-14
• 2260 (Ch. 456.150-6, -15) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
• 2264, 2265, 2266 (Ch. 456.150-11 and Model 2276—Set 230-10)
• 2276, 2277 (Ch. 456.150-11, -14 and Radio Ch. 456.155) 230-10
• 2278, 2279 (Ch. 456.150-11, -81 and Radio Ch. 456.860-1) (For TV Ch. see PCB 118—Set 270-1 and Model 2276—Set 230-10)
• 2280 (Ch. 456.150-6, -13) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
• 2286, 2287 (Ch. 456.150-6, -15) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
• 2289 (Ch. 456.150-9, -12, -17) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
• 2290 (Ch. 456.150-9, -17) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
• 2297, 2298 (Ch. 456.150-81) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
3001, 3002 (Ch. 132.054) 239-9
3004 (Ch. 757.130) 231-15
3007, 3008, 3009 (Ch. 757.120) 226-9
3025, 3026, 3027 (Ch. 132.066) 249-15
3032 (Ch. 528.252) 219-10
3035A (Ch. 528.195, -1, -2) 215-12
3040 (Ch. 528.253) 225-16
3040A (Ch. 528.311) 270-13
3041 (Ch. 528.235-1) (See Model 2041—Set 208-11)
3045, 3046 (Ch. 528.254) 216-10
3052, 3053 (Ch. 132.053) 225-15
3054, 3055 (Ch. 132.056) 250-18
3058, 3059 (Ch. 101.860-3) 240-8
3061, 3062 (Ch. 101.861-1) (See Model 2060—Set 203-9)
3063, 3064 (Ch. 101.860-3) 240-8
3067 (Ch. 101.860-3) 240-8
3068 (Ch. 100.174) 270-14
• 3100 (Ch. 110.817-1) (See Model 2100A—Set 217-15)
• 3100A (Ch. 110.817-1, -3) (See Model 2100A—Set 217-15)
• 3101 (Ch. 110.817-1) (See Model 2100A—Set 217-15)
• 3102X (Ch. 528.271, -1, -2, -3, -4, -5) (See Model 4108—Set 245-6)
• 3103A (Ch. 528.290-2) 253-12
• 3104A (Ch. 528.271-3, -4) 245-6
• 3105 (Ch. 132.024-5, -6, -7, -8) (Also see PCB 117—Set 198-13)
• 3106 (Ch. 132.045, -1, -2, -3, -4, -5) (Also see PCB 90—Set 235-1) 199-11
• 3109 (Ch. 528.264) 227-12
• 3110 (Ch. 528.248, -1, -2) 220-7
• 3110A (Ch. 528.242, -1, -2) 220-7
• 3110B (Ch. 528.264-1, 2) 227-12
• 3112A (Ch. 528.256) (See Model 3112B—Set 227-12)
• 3112B (Ch. 528.263, -1, -2) 227-12
• 3112C (Ch. 528.258) 247-10
• 3112X (Ch. 528.292, -1, -2, -3, -4) (See Model 4113A—Set 245-6)

SILVERTONE—Cont.

- 3115 (Ch. 528.248, -1, -2) 220-7
• 3115A (Ch. 528.242, -1, -2) 220-7
• 3127 (Ch. 100.210, -1, -3) 207-10
• 3140 (Ch. 110.817, -1) (See Model 2100A—Set 217-15)
• 3145 (Ch. 132.024-5, -6, -7, -8) (Also see PCB 117—Set 269-1) 198-13
• 3146 (Ch. 132.045-2, -3, -4, -5) (See PCB 90—Set 235-1 and Model 3106—Set 199-11)
• 3150 (Ch. 110.820-1, -3) (See Model 2100A—Set 217-15)
• 3150L (Ch. 528.264, -1, -2) 227-12
• 3151A (Ch. 528.256) (See Model 3151B—Set 227-12)
• 3151B, C (Ch. 528.263, -1, -2) 227-12
• 3160 (Ch. 528.248, -1, -2) 220-7
• 3160A (Ch. 528.242, -1, -2) 220-7
• 3170 (Ch. 528.239) 207-10
• 3170B (Ch. 100.210, -1, -3) 207-10
• 3170C (Ch. 528.249, -1) 218-11
• 3170D (Ch. 528.261) 227-12
• 3171A (Ch. 528.247, -1) 217-16
• 3174 (Ch. 132.035-2) 206-11
• 3175 (Ch. 132.044-1) 203-10
• 3177 (Ch. 100.210, -1, -3) 207-10
• 3177A, (Ch. 100.400) 244-10
• 3187 (Ch. 100.210, -1, -3) 207-10
• 3187A (Ch. 100.400) 244-10
• 3195 (Ch. 100.210-2 and Radio Ch. 100.202-1) (See PCB 91—Set 236-1 and Model 2130—Set 207-1 for TV Ch. and Model 1066

SILVERTONE—Cont.

- 4116 (Ch. 526.266) 227-12
- 4116W (Ch. 101.662-11, 12-13, 21, 22, 23) (See PCB 109—Set 257-1 and Model 3376—Set 225-16)
- 4117 (Ch. 528.266) 227-12
- 4117W (Ch. 101.662-11, 12-13, 21, 22, 23) (See PCB 109—Set 257-1 and Model 3376—Set 225-16)
- 4118 (Ch. 528.263-1, 2) 227-12
- 4118B (Ch. 528.292-1, 2) 245-6
- 4118C (Ch. 528.303-1) 245-6
- 4118W (Ch. 456.200-11, 12, 13, 21, 22, 23) (See PCB 109—Set 257-1 and Model 3376—Set 225-16)
- 4119 (Ch. 528.263-2) 227-12
- 4119A (Ch. 528.303-1) 245-6
- 4119W (Ch. 456.200-11, 12, 13, 21, 22, 23) (See PCB 109—Set 257-1 and Model 3376—Set 225-16)
- 4120 (Ch. 456.150-2) (See PCB 118—Set 279-2 and Model 2276—Set 230-10)
- 4124 (Ch. 528.290-1, 2) 253-12
- 4125 (Ch. 528.271-1, 2, 3, 4) 245-6
- 4126 (Ch. 528.264-1, 2) 227-12
- 4126A (Ch. 528.297) 253-12
- 4126B (Ch. 528.291, 2) 253-12
- 4126D (Ch. 528.302) 253-12
- 4127 (Ch. 528.263-1, 2) 227-12
- 4127A (Ch. 528.268) 247-10
- 4127C (Ch. 528.292-1) 245-6
- 4127D (Ch. 528.303-1) 245-6
- 4127W (Ch. 456.200-11, 12, 13, 21, 22, 23) (See PCB 109—Set 257-1 and Model 3376—Set 225-16)
- 4128 (Ch. 528.264-2) 227-12
- 4128A (Ch. 528.291) 253-12
- 4128B (Ch. 528.292) 253-12
- 4128C (Ch. 528.293) 253-12
- 4129A (Ch. 528.292-1) 245-6
- 4129B (Ch. 528.303-1) 245-6
- 4129W (Ch. 456.200-11, 12, 13, 21, 22, 23) (See PCB 109—Set 257-1 and Model 3376—Set 225-16)
- 4131 (Ch. 528.263-1) 227-12
- 4132 (Ch. 528.291-2) 253-12
- 4132B (Ch. 528.291-3) (See Model 4111A—Set 253-12)
- 4133 (Ch. 528.292-2, 3) 245-6
- 4133B (Ch. 528.292-1, 2, 3, 4) (See Model 4118B—Set 245-6)
- 4135 (Ch. 528.292-1, 3) 245-6
- 4135B (Ch. 528.292-2, 3, 4) (See Model 4113A—Set 245-6)
- 4139 (Ch. 528.270) 227-12
- 4139A (Ch. 528.299) 253-12
- 4140 (Ch. 528.247-1) 217-16
- 4140D (Ch. 528.266-1) 227-12
- 4140E (Ch. 528.300-1, 2, 3) 245-6
- 4142 (Ch. 528.299-2, 3) 253-12
- 4142H (Ch. 528.32000, 528.32001) 267-13
- 4143 (Ch. 528.247-1) 217-16
- 4143D (Ch. 528.266-1) 227-12
- 4144 (Ch. 528.299-2, 3) 253-12
- 4145 (Ch. 528.247-1) 217-16
- 4145D (Ch. 528.266-1) 227-12
- 4149 (Ch. 528.299-2, 3) 253-12
- 4149E (Ch. 528.32000, 528.32001) 267-13
- 4150 (Ch. 528.247-1) 217-16
- 4150D (Ch. 528.266) 227-12
- 4150E (Ch. 528.300-2, 3) 245-6
- 4152H (Ch. 528.32001) 267-13
- 4153 (Ch. 528.247-1) 217-16
- 4153D (Ch. 528.266) 227-12
- 4153E (Ch. 528.300-3) (See Model 4140E—Set 245-6)
- 4155 (Ch. 528.247-1) 217-16
- 4155E (Ch. 528.286) 227-12
- 4155E (Ch. 528.300-2, 3) 245-6
- 4200 (Ch. 757.140) 262-13
- 4204 (Ch. 132.067) 255-13
- 4206 (Ch. 132.067) 255-13
- 4225 (Ch. 528.303-1) 245-6
- 4242 (Ch. 548.401-A) 258-11
- 5100 (Ch. 528.31300, 528.31301) 264-17
- 5106 (Ch. 528.31700, 528.31701) 264-17
- 5110 (Ch. 528.31400, 528.31401) 264-17
- 5110A (Ch. 528.32800, 528.31801) 5126A—Set 264-17
- 5111 (Ch. 528.302-1) 253-12
- 5113 (Ch. 528.303-1) (See Model 4118C—Set 245-6)
- 5114 (Ch. 528.31800, 528.31801) 264-17
- 5116 (Ch. 528.31800, 528.31801) 264-17
- 5118 (Ch. 528.31900, 528.31901) 267-13
- 5126 (Ch. 528.31400, 528.31401) 264-17
- 5126A (Ch. 528.32800) 264-17
- 5132 (Ch. 528.31900, 528.31901) 267-13
- 5139 (Ch. 528.32000, 528.32001) 267-13
- 5149 (Ch. 528.32001) 267-13
- 6002 (Ch. 132.818) 5-35
- 6011 (Ch. 132.816), 6012 (Ch. 132.816A) 15-27
- 6016 (Ch. 132.820) 27-24
- 6050 (Ch. 132.825-4) 15-28
- 6051 (Ch. 110.451), 6052 (Ch. 110.452) 13-29
- 6052A (Ch. 110.452-1) (See Model 6051—Set 13-29)
- 6071 (Ch. 132.826-1) 15-29
- 6072 (Ch. 110.454) 13-30
- 6092 (Ch. 101.672-1B), 6093 (Ch. 101.672-1C) 10-28
- 6100 (Ch. 101.660-1A) 6-29
- 6104 (Ch. 101.662-2D) (See Model 6105—Set 7-26)

SILVERTONE—Cont.

- 6105 (Ch. 101.622-2B) 7-26
- 6106A (Ch. 101.662-4E) 29-23
- 6111 (Ch. 101.662-3C) 7-26
- 6111A (Ch. 101.662-5F) 29-23
- 6200A (Ch. 101.800-1) 9-29
- 6200A (Ch. 101.800-3) 65-12
- 6203 (Ch. 101.800A) (See Model 6200A—Set 9-29)
- 6220, 6220A (Ch. 101.801, 101.801-1A) 9-30
- 6230 (Ch. 101.802) 11-21
- 6230A (Ch. 101.802-1) 11-21
- 6235A (Ch. 101.666-1B) 20-28
- 6286 (Ch. 528.6286-1) 3185-12
- 6287 (Ch. 528.6287-1) 3185-12
- 6290 (Ch. 101.677-8) 20-29
- 6293 (Ch. 528.6293-2) 99-16
- 6295 (Ch. 528.6295) 98-12
- 6685 (Ch. 139.150, Ch. 139.150-1) 15-30
- 6950 (Ch. 725.101-1) Tel. UHF Conv. 235-11
- 7020 (See Model 7021—Set 16-31)
- 7021 (Ch. 101.807, 101.807A) 16-31
- 7025 (Ch. 132.807-2) 16-31
- 7054 (Ch. 101.808) 15-31
- 7070 (Ch. 101.817) 30-26
- 7080 (Ch. 101.809) 16-32
- 7080, 7080A (Ch. 101.809-2) 58-20
- 7085 (Ch. 101.814) 30-27
- 7086 (Ch. 101.814) 27-25
- 7090 (Ch. 101.810) 15-32
- 7095 (Ch. 101.826) (See Model 7115—Set 16-31)
- 7100 (Ch. 101.811) 17-29
- 7102 (Ch. 101.814-1A) 30-27
- 7103 (Ch. 110.466-1) 27-25
- 7111 (Ch. 434.140) 30-28
- 7115 (Ch. 101.825), 7116 (Ch. 101.825-1A), 7117 (Ch. 101.825-1B) 16-33
- 7119 (Ch. 101.825-2C) 62-18
- 7125 (Ch. 436.200-1) 253-12
- 7148 (Ch. 431.188), 7148A (Ch. 431.188-1) 23-22
- 7152 (Ch. 109.626) 25-26
- 7153 (Ch. 109.627) 26-30
- 7165 (Ch. 101.823-A, 1A) 10-29
- 7166 (Ch. 101.823, 101.823-1) 10-29
- 7210 (Ch. 101.820) 32-20
- 7220 (Ch. 101.801-2C) (See Model 6220—Set 9-30)
- 7226 (Ch. 101.819A) 31-28
- 7230 (Ch. 101.802-2A) (See Model 6230—Set 11-21)
- 7300 (Ch. 435.240) 45-22
- 7350 (Ch. 435.410) 38-22
- 7353 (See Model 7350—Set 38-22)
- 8000 (Ch. 132.838) 31-29
- 8003 (Ch. 132.818-1) 53-22
- 8004 (See Model 8003—Set 53-22)
- 8005 (Ch. 132.839) 33-26
- 8010 (Ch. 132.840) 40-21
- 8011 (See Model 8010—Set 40-21)
- 8020 (Ch. 132.841) 43-17
- 8021 (Ch. 132.868) 70-10
- 8024, 8025 (Ch. 478.206-1) 80-15
- 8050 (Ch. 101.813) 33-27
- 8051 (Ch. 101.839) 49-19
- 8052 (Ch. 101.808-1C) 68-15
- 8053 (Ch. 101.808-1D) (See Model 8052—Set 68-15)
- 8070 (Ch. 101.817-1A) (See Model 7070—Set 30-26)
- 8072 (Ch. 101.834) 34-19
- 8073 (Ch. 135.243) 84-9
- 8080 (Ch. 101.852) 52-20
- 8083, 8083A (Ch. 101.809-1A) 58-20
- 8084, 8084A (Ch. 101.809-1B) 58-20
- 8086 (Ch. 101.814-5C) 61-18
- 8086A, 8086B (Ch. 101.814-6C) 61-18
- 8099 (Ch. 101.821) 49-20
- 8099 (Ch. 101.825-3G) (See Model 8115—Set 62-18)
- 8097A (Ch. 101.825-4) 62-18
- 8100 (Ch. 101.829) 51-19
- 8101, 8101A, 8101B, 8101C (Ch. 101.809-3C) 58-20
- 8102 (Ch. 101.814-2B) 61-18
- 8102A (Ch. 101.814-3B) 61-18
- 8102B (Ch. 101.814-2B) 61-18
- 8103 (Ch. 110.473) 56-21
- 8104 (See Model 8086—Set 61-18)
- 8105, 8105A (Ch. 101.833) 35-20
- 8106, A, B, C (Ch. 101.833-1A) (See Model 8105—Set 35-20)
- 8107A, 8108, 8108A (Ch. 101.851), 8109 (Ch. 101.851-1) 64-10
- 8112, 8113 (Ch. 101.851) (See Model 8107A—Set 64-10)
- 8115 (Ch. 101.825-3D) 62-18
- 8115, A, B, C (Ch. 101.825-4) 62-18
- 8115D (Ch. 101.825-4) (See Model 8115A—Set 62-18)
- 8117 (Ch. 101.825-3E) 62-18
- 8118 (Ch. 101.825-3F) 62-18
- 8118 A, B, C (Ch. 101.825-4) 62-18
- 8118D (Ch. 101.825-4) (See Model 8118A—Set 62-18)
- 8124, 8125, 8126 (Ch. 101.831A, 101.831) (See Model 8127—Set 41-20)
- 8127, A, B, C (Ch. 101.831A), 8128, A, B, C (Ch. 101.831), Wire Recorder Amp. (Ch. 101-773) 41-20
- 8127CX (Ch. 101.831A) Wire Recorder Amp. 101-773) (See Model 8127—Set 41-20)
- 8130 49-21
- 8132 (Ch. 101.854) 66-15
- 8133 (Ch. 101.829-1, Ch. 101.846) 66-15
- 8144 (Ch. 431.199) 32-21
- 8145 (Ch. 109.631) 45-23
- 8148 (Ch. 109.632) 48-23
- 8149 (Ch. 109.633) 48-23
- 8150 (Ch. 109.634) 32-22
- 8152 (Ch. 109.635) (See Model 8153—Set 42-22)

SILVERTONE—Cont.

- 8153 (Ch. 109.635), 8153A (Ch. 109.635-1) 42-22
- 8155 (Ch. 463.155) 57-17
- 8160 (Ch. 109.636A) 50-17
- 8168 (Ch. 109.638) 46-23
- 8168—Set 46-23) (See Model 8200 (Ch. 101.800-2B) (See Model 6200A—Set 65-12)
- 8201 (See Model 6200A—Set 65-12)
- 8210 (Ch. 101.820-1A) 71-13
- 8220, 8221 (Ch. 101.801-3D) (See Model 6220—Set 9-30)
- 8222 (See Model 6220—Set 9-30)
- 8230 (Ch. 101.835) 59-18
- 8231 (See Model 8230—Set 59-18)
- 8260 (Ch. 101.823-2B) (See Model 7145—Set 10-29)
- 8270 (Ch. 101.822), 8270A (Ch. 101.822A) 57-18
- 9000 (Ch. 132.875) 65-13
- 9005, 9006 (Ch. 132.858) 72-11
- 9022 (Ch. 132.871) 76-17
- 9023 (Ch. 101.849) 63-16
- 9073, 9073A (Ch. 135.244) 9073B (Ch. 135.244-1) 83-10
- 9073C (Ch. 135.243-1) (See Model 9073—Set 83-10)
- 9082 (Ch. 135-245) 101-11
- 9084 (Ch. 135-245) (See Model 4191—Set 101-11)
- 9101 (Ch. 101.809-3C) (See Model 7080—Set 58-20)
- 9102 (See Model 7080—Set 58-20)
- 9105 (Ch. 132.875) 89-14
- 9107 (Ch. 101.859-1) (See Model 64-10)
- 9107A (Ch. 101.851-1) (See Model 8107A—Set 64-10)
- 9107B (Ch. 101.859-2) (See Model 64-10)
- 9108 (Ch. 101.859-1) (See Model 64-10)
- 9109 (Ch. 110.491) (See Model 9123—Set 79-16)
- 9112 (Ch. 110.499-1) (See Model 9124—Set 79-16)
- 9113 (Ch. 110.499) (See Model 9123—Set 79-16)
- 9114 (Ch. 110.499-1) (See Model 9124—Set 79-16)
- 9115 (Ch. 478.224), 9116 (Ch. 478.221) 97-16
- 9116 (Ch. 478.221) 97-16
- 9119, 9120 (Ch. 101.865) 97-16
- 9120 (Ch. 101.862-1) *
- 9121 (Ch. 101.867) *
- 9122 (Ch. 101.864) (See Model 8132—Set 66-15)
- 9122A (Ch. 101.868) *
- 9123 (Ch. 110.499) 79-16
- 9124 (Ch. 478.252) 79-16
- 9125 (Ch. 478.252) 79-16
- 9125A (Ch. 478.253) 104-10
- 9125B (Ch. 478.253-1) *
- 9126 (Ch. 100.499-2) (See Model 9126—Set 104-10)
- 9126A (Ch. 101.868) *
- 9129 (Ch. 110.499) (See Model 9123—Set 79-16)
- 9130 (Ch. 110.499-1) (See Model 9124—Set 79-16)
- 9131 (Ch. 478.210) 84-10
- 9132 (Ch. 110.499-1) (See Model 9124—Set 79-16)
- 9133, 9134 (Ch. 101.866 and Radio Ch. 101.859) 95-5
- 9139, 9140 (Ch. 110.499-1) (See Model 9124—Set 79-16)
- 9151 (Ch. 478.253) 67-16
- 9161 (Ch. 548.358) 88-10
- 9260 (Ch. 101.850) 51-20
- 9270 (Ch. 547.245) 82-11
- 9280 (Ch. 528.168) 94-9
- 5126B (Ch. 528.32800) (See Model 5126A—Set 264-17)
- 5128, 5130 (Ch. 528.31800, 528.31801) 264-17
- 41102 (Ch. 528.32800) (See Model 5126A—Set 264-17)
- Ch. 100.043 (See Model 133)
- Ch. 100.107 (See Model 691)
- Ch. 100.107-1 (See Model 149)
- Ch. 100.111 (See Model 143A)
- Ch. 100.112 (See Model 161-16)
- Ch. 100.120 (See Model 165-16)
- Ch. 100.174 (See Model 306B)
- Ch. 100.202 (See Model 691)
- Ch. 100.202 (See Model 1066)
- Ch. 100.202-1 (See Model 2195-21 or 3195)
- Ch. 100.208 (See Model 1176-21)
- Ch. 100.208-1 (See Model 2195-21)
- Ch. 100.209 (See Model 2170-C)
- Ch. 100.210, 1 (See Model 2130)
- Ch. 100.210-2 (See Model 3195)
- Ch. 100.210-3 (See Model 3130)
- Ch. 100.400 (See Model 3177A)
- Ch. 101.660-1A (See Model 6100)
- Ch. 101.662-1A (See Model 6105)
- Ch. 101.662-2D (See Model 6105)
- Ch. 101.662-3C (See Model 6111)
- Ch. 101.662-4E (See Model 6106A)
- Ch. 101.662-5F (See Model 6111A)
- Ch. 101.666-1B (See Model 6285A)
- Ch. 101.672-1A (See Model 6093)
- Ch. 101.672-1B (See Model 6092)
- Ch. 101.677B (See Model 6290)
- Ch. 101.733 (See Model 8127)
- Ch. 101.800-1, -1A (See Model 6200A, Ch. 101.800-1, 1A)
- Ch. 101.800-3 (See Model 6200A, Ch. 101.800-3)
- Ch. 101.801, -1A (See Model 6230)
- Ch. 101.802, -1 (See Model 6230)
- Ch. 101.807, A (See Model 7021)
- Ch. 101.808 (See Model 7054)
- Ch. 101.808-1 (See Model 8052)
- Ch. 101.808-10 (See Model 8053)
- Ch. 101.809 (See Model 7080, Ch. 101.809)
- Ch. 101.809-1A (See Model 8083)
- Ch. 101.809-1B (See Model 8084)
- Ch. 101.809-2 (See Model 7080, Ch. 101.809-2)
- Ch. 101.809-3C (See Model 8101)
- Ch. 101.810 (See Model 7090)

SILVERTONE—Cont.

- Ch. 101.811 (See Model 7100)
- Ch. 101.813 (See Model 8050)
- Ch. 101.814 (See Model 7085)
- Ch. 101.814-1A (See Model 7102)
- Ch. 101.814-2B (See Model 8102)
- Ch. 101.814-3B (See Model 8102A)
- Ch. 101.814-5C (See Model 8086A)
- Ch. 101.814-6C (See Model 8086A)
- Ch. 101.817 (See Model 7070)
- Ch. 101.819A (See Model 7226)
- Ch. 101.820 (See Model 7210)
- Ch. 101.821 (See Model 8090)
- Ch. 101.822 (See Model 8270)
- Ch. 101.822A (See Model 8270A)
- Ch. 101.823, -1 (See Model 7166)
- Ch. 101.823-A, -1A (See Model 7165)
- Ch. 101.825 (See Model 7115)
- Ch. 101.825-1 (See Model 7116)
- Ch. 101.825-1B (See Model 7117)
- Ch. 101.825-2C (See Model 7119)
- Ch. 101.825-3E (See Model 8115)
- Ch. 101.825-3F (See Model 8117)
- Ch. 101.825-3G (See Model 8097)
- Ch. 101.825-4 (See Model 8097A)
- Ch. 101.829 (See Model 8100)
- Ch. 101.829-1 (See Model 8133)
- Ch. 101.831 (See Model 8128)
- Ch. 101.831A (See Model 8127)
- Ch. 101.831-1 (See Model 8124)
- Ch. 101.833 (See Model 8105)
- Ch. 101.834 (See Model 8072)
- Ch. 101.835 (See Model 8230)
- Ch. 101.839 (See Model 8051)
- Ch. 101.846 (See Model 8133)
- Ch. 101.849 (See Model 9054)
- Ch. 101.850 (See Model 9260)
- Ch. 101.851 (See Model 8107A)
- Ch. 101.851-1 (See Model 8109)
- Ch. 101.852 (See Model 8080)
- Ch. 101.854 (See Model 8132)
- Ch. 101.859 (See Model 9133)
- Ch. 101.859-2 (See Model 67)
- Ch. 101.859-2 (See Model 64)
- Ch. 101.860 (See Model 1058)
- Ch. 101.860-3 (See Model 3058)
- Ch. 101.861, -1 (See Model 2060)
- Ch. 101.864 (See Model 2060)
- Ch. 101.865 (See Model 9119)
- Ch. 101.865-1 (See Model 9120A)
- Ch. 101.866 (See Model 9133)
- Ch. 101.867 (See Model 9121)
- Ch. 101.868 (See Model 9122A)
- Ch. 109.626 (See Model 7132)
- Ch. 109.631 (See Model 7133)
- Ch. 109.631 (See Model 8145)
- Ch. 109.632 (See Model 8148)
- Ch. 109.633 (See Model 8149)
- Ch. 109.634 (See Model 8150)
- Ch. 109.635 (See Model 8153)
- Ch. 109.635-1 (See Model 8153A)
- Ch. 109.636 (See Model 8160)
- Ch. 109.636A (See Model 8160A)
- Ch. 109.638 (See Model 8168)
- Ch. 110.451 (See Model 6051)
- Ch. 110.452 (See Model 6052)
- Ch. 110.454 (See Model 6072)
- Ch. 110.466 (See Model 9125A)
- Ch. 110.466-1 (See Model 7103)
- Ch. 110.473 (See Model 8103)
- Ch. 110.499 (See Model 9123)
- Ch. 110.499-1 (See Model 9124)
- Ch. 110.499-2 (See Model

SILVERTONE-STEWART-WARNER

SILVERTONE-Cont.

Ch. 528.300, -1, -2, -3 (See Model 4140E)
Ch. 528.303, -1 (See Model 4112)
Ch. 528.304, -1 (See Model 4041, B)

SIMPLON

CA-5 22-27
WV2 17-30

SKY KNIGHT (See Air Knight)

SKYRIDER (See Helicopters)

SKYROVER
NS-RD-250 (9022-N), NS-RD-251 (9022-H) 6-31
NS-RD295 (Ch. 5A7) 21-30

SKY WEIGHT

B18 20-30
82 13-13

SONOGRAPH

BL100 122-10
BW100 (See Model BL100-Set 122-10)

SONORA

RB-176 5-31
RB-207 (See Model RB-176-Set 5-31)
RCU-208 5-30
RDU-209 3-29
RET-110 24-24
RGMF-212, RGMF-230 27-26
RKRU-215 (Ch. RKRU) 23-23
RMR-219 19-28
RMR-220, RMR-245 (See Model RMR-219-Set 19-28)
RQU-222 8-23
RWFU-238 23-24
RX-223 23-23
WAU-243 27-27
WBRU-249 32-23
WCU-236 36-22
WDU-233 25-27
WOU-249 37-20
WEU-262 33-28
WGFU-241, WGFU-242 24-25
WJU-252 36-23
WKRU-254A 34-20
WLRU-219A 37-21
WLRU-220A (See Model WLRU-219A-Set 17-21)
WLRU-245A (See Model WLRU-219A-Set 37-21)
YB-299 112-9
100 41-21
101 48-24
102 23-13
103 23-13
104 109-13
105 109-13
106 86-10
107 174-11
108 174-11
109 108-11
110 253-13
111 174-11
112 174-11
113 174-11
114 253-13
115 253-13
116 253-13
200 253-13

SONORA-Cont.

402F (See Model WLRU-219A-Set 37-21)
413, 414, 415, 416 (For TV Ch. Only, See Model 421-Set 221-10)
421, 422, 423, 424, 425, 426, 428, 429 221-10
441, 442 253-13
458, 459 253-14
464, 465, 466 249-17
467 254-10
470A 249-16
477, 478 253-13

SOUND, INC.

"Intersound" 7-27
MB6P3, MB6P6, MB6P30, MB6R4 35-21
MB7E3 28-31
MB7E8 26-24
5R2 28-32

SPARKS-WITHINGTON

(See Spartan)

SPARTON (Also see Record Changer Listing)

4AW17 (Ch. 417) 50-18
4AW17 (Ch. 417A) 49-22
5A10 (Ch. 516) 30-29
5A106, 5A106 (See Model 5AW06-Set 4-17)
5AM26-PS (Ch. 5-26-PS) 5-17
5AW06 (Ch. 5-06) 4-17
5AW16 (Ch. 5-16) 30-29
6AM06 (Ch. 6-06) 34-21
6AW26 (See Model 6AW26PA-Set 15-33)
6AW26PA (Ch. PC5-6-26) 15-33
6-66A (Ch. 666A) 51-21
7AM46 (Ch. 7-46) 1-31
7AM46PA, 7BM46PA, 7BW46PA (See Model 7AM46-Set 1-31)
8AM46 (Ch. 8-46) 1-31
10AB76-PA, 10AM76-PA, 10BM76-PA (See Model 10BW76-PA-Set 15-34)
10BW76-PA (Ch. 10-76PA) 15-34
1121 (Ch. 23U21) 255-14
12A20A (Ch. 23U21A) 255-14
12A210 (Ch. 23U21A) 255-14
14A20A (Ch. 23U21A) 255-14
100, 101 (Ch. 5A7) 38-23
102, 103, 104 (See Model 100-Set 38-23)
121 (Ch. 819) 57-19
122 (See Model 121-Set 57-19)
130, 132, 135, 139 (Ch. 5A10) 94-10
141 (See Model 121-Set 57-19)
145 (Ch. 5A10, A) 210-10
141XX, 142XX (Ch. 8W10) 126-12
142 (See Model 121-Set 57-19)
150, 151, 152, 155 (Ch. 4E10) 91-12
230 (Ch. 5A10, A) 210-10
232 (Ch. 5A10, A) 210-10
301, 305, 309 (Ch. 4E3) 222-13
320C, 321C (Ch. 583C) 237-10
325C (Ch. 583C) 237-10
329C (Ch. 583C) 237-10
342, 345, 347 (Ch. 5C3) 220-9
350, 351 (Ch. 613) 197-12
1000, 1001, 1003 (Ch. 1217) 60-18
1005, 1006, 1007, 1008 (Ch. 8-57) 29-25
1010 (Ch. 717) 35-22
1015 (See Model 10BW76PA-Set 15-34)
1020, 1021, 1023 60-18
1030, 1030A (Ch. 618) 37-22
1031, A (See Model 1030-Set 37-22)
1036, 1035A, 1036, 1036A, 1037, 1037A, 1039, 1040, 1041 (Ch. 918) 62-19
1040XX, 1041XX (Ch. 8W10) 126-12
1051, 1052 (Ch. 689) 58-21
1058, 1059, 1060, 1061, 1064 (Ch. 918) 61-11
1071 (See Model 121-Set 57-19)
1072 (Ch. 819) 57-19
1080 (Ch. 918A) (See Model 4900-TV-Set 64-11)
1080A, 1081 (Ch. 810) (See Model 141A-Set 92-6)
1081 (Ch. 918A) (See Model 4900-TV-Set 64-11)
1081A (Ch. 810) (See Model 141A-Set 92-6)
1085, 1086 (Ch. 8W10) 126-12
1090, 1091 (Ch. 8W10) 126-12
1210, 1211 (Ch. 8W10) (See Model 141XX-Set 126-12)
1300, 1301 (Ch. 613) 197-12
4900TV (Ch. 24TV9C, 3TV9C, 918A)
4916, 4917, 4918 (Ch. 24T10, 3T10, 6S10) 164-9
4920, 4921, 4922 (Ch. 24T10) 164-9
4935 (Ch. 23T10) 133-1A
4937, 4938, 4939, 4941 (Ch. 24TV9, 3TV9) 64-11
4942 (Ch. 23T10) 133-1A
4944, 4945 (Ch. 3T810, 24T810)
4951, 4952 (See Model 4900TV-Set 64-11)
4954 (Ch. 23T10) 133-1A
4960 (Ch. 23T10) 133-1A
4964, 4965 (Ch. 23T810) 157-11
4970, 4971, 4972 (Ch. 8510) 92-6
5002, 5003 (Ch. 23T10) 102-13
5006, 5007 (Ch. 23T10) 102-13
5006X (Ch. 25T10A) 12-13
5007X (Ch. 25T10A) 12-13
5010, 5011 (Ch. 19T510, A) 104-11
5014, 5015 (Ch. 19T510, A) 104-11
5025 (Ch. 2655160) 128-13
5025BA (See PCB 22-Set 138-1 and Model 5025-Set 128-13)
5026 128-13
5029, 5030 (Ch. 265D160) 128-13
5035, 5036, 5037 (Ch. 2655160L) 128-13

SPARTON-Cont.

5052 (Ch. 24T10, 3TR10) 97A-13
5056, 5057 (Ch. 19T510, A) 104-11
5064, 5065 (Ch. 23T810) 157-11
5068, 5069 (Ch. 24TV9C) (See Model 4900TV-Set 64-11)
5071, 5072 (Ch. 19T510, A) 104-11
5075BA (See PCB 22-Set 138-1 and Model 5025-Set 128-13)
5076 (Ch. 2655160, B) 128-13
5076BA (See PCB 22-Set 138-1 and Model 5076-Set 128-13)
5076BB 128-13
5077 128-13
5077BA (See PCB 22-Set 138-1 and Model 5077-Set 128-13)
5078B 128-13
5079 128-13
5079B (See PCB 22-Set 138-1 and Model 5079-Set 128-13)
5080 128-13
5080C (See PCB 22-Set 138-1 and Model 5080-Set 128-13)
5082, 5083 (Ch. 265D160, 265D170) (For TV Ch. see Set 128-13, for Radio Ch. see Model 141XX-Set 126-12)
5082, 5083 (Ch. 265D170X, XP) (For TV Ch. see PCB 22-Set 138-1 and Model 5082-Set 128-13, for Radio Ch. see Model 141XX-Set 126-12)
5085, 5086 (Ch. 2RD190, 25RD190) 139-14
5088, 5089, 5090 (Ch. 265D160, 265D170 and Radio Ch. 8W10) (For TV Ch. see Set 128-13, for Radio Ch. see Model 141XX-Set 126-12)
5101, 5102, 5103 (Ch. 2655170, P) (See PCB 22-Set 138-1 and Model 5025-Set 128-13)
5104, 5105 (Ch. 2655170D, P) (See PCB 22-Set 138-1 and Model 5025-Set 128-13)
5152, 5153, 5154 (Ch. 2655170, P) (See PCB 22-Set 138-1 and Model 5025-Set 128-13)
5155, 5156, 5157 (Ch. 265D170X, XP) (See PCB 22-Set 138-1 and Model 5025-Set 128-13)
5158 (Ch. 265D170, P) (See PCB 22-Set 138-1 and Model 5025-Set 128-13)
5165X, 5166X (Ch. 265D171) 166-13
5170, 5171 (Ch. 255D201, 25D201) 147-11
5175X (Ch. 265D171) 166-13
5178X (Ch. 265D171) 166-13
5182, 5183, 5188, 5189 (Ch. 265D170, P and Radio Ch. 8W10) (For TV Ch. see Model 5A116)
5182 and Model 5025-Set 128-13, for Radio Ch. see Model 141XX-Set 126-12)
5191, 5192 (Ch. 255D201, 25D201) (See Model 5170-Set 147-11)
5207, 5208 (Ch. 2655172, A) 167-14
5210 (Ch. 2655172B) 167-14
5212 (Ch. 215172) 174-12
5220 (Ch. 265D172C) 167-14
5225, 5226 (Ch. 265D172C) 167-14
5240, 5241 (Ch. 215172) 201-10
5250, 5252, 5253 (Ch. 215172) 174-12
5262, 5263 (Ch. 2655172, A) 167-14
5265 (Ch. 265D172, A) 167-14
5267, 5268 (Ch. 265D172, A) 167-14
5270 (Ch. 265D172C) 167-14
5271 (Ch. 265D172C) (See Model 5207-Set 167-14)
5272, 5273 (Ch. 265D172C) 167-14
5280, 5281 (Ch. 215172) 201-10
5288, 5289 (Ch. 25CD202) 178-11
5290 (Ch. 25CD202) 178-11
5291, 5292, 5293, 5294, 5295 (Ch. 25CD202) 178-11
5296A, 5297A (Ch. 26CD202) 178-11
5296, 5297 (Ch. 25CD202) 178-11
5298 (Ch. 25CD202) 178-11
5299 (Ch. 25CD202) (See Model 5298-Set 178-11)
5301 (Ch. 215173-D) 201-10
5323 (Ch. 25D173A) 222-14
5324 (Ch. 25D173A) 222-14
5326 (Ch. 25D173A) 222-14
5326A (Ch. 27D173) 222-14
5340, 5341 (Ch. 215213) 201-10
5342 (Ch. 25D213) (See PCB 104-Set 210-11 and Model 5342A-Set 210-11)
5342A (Ch. 27D213) 210-11
5343 (Ch. 25D213) (See PCB 104-Set 250-1 and Model 5342A-Set 210-11)
5343A (Ch. 27D213) 210-11
5343B (Ch. 27D213A) 222-14
5343C (Ch. 27D173) 222-14
5363 (Ch. 25D173A) 222-14
5363A (Ch. 27D173) 222-14
5380, 5381 (Ch. 215213) 201-10
5382 (Ch. 25D213) (See PCB 104-Set 250-1 and Model 5342A-Set 210-11)
5382A (Ch. 27D213) 210-11
5382B (Ch. 27D213A) 210-11
5383 (Ch. 25D213) (See PCB 104-Set 250-1 and Model 5342A-Set 210-11)
5383A (Ch. 27D213) 210-11
5383B (Ch. 27D213A) (See Model 5382B-Set 210-11)
5384 (Ch. 25D213) (See PCB 104-Set 250-1 and Model 5342A-Set 210-11)
5384A (Ch. 27D213) 210-11
5385 (Ch. 25D213) (See PCB 104-Set 250-1 and Model 5342A-Set 210-11)
5386 (Ch. 27D213) 210-11

SPARTON-Cont.

5386B (Ch. 27D213A) (See Model 5382B-Set 210-11)
5387B (Ch. 27D213A) (See Model 5382B-Set 210-11)
5390 (Ch. 25D213) (See PCB 104-Set 250-1 and Model 5342A-Set 210-11)
5391 (Ch. 25D213) (See PCB 104-Set 250-1 and Model 5342A-Set 210-11)
1032 (Ch. 27D213 and Radio Ch. 8W10) (For TV Ch. see Set 210-11, for Radio Ch. see Model 141XX-Set 126-12)
10352A (Ch. 27D213A and Radio Ch. 8W10) (For TV Ch. see Model 5382B-Set 210-11, for Radio Ch. see Model 141XX-Set 126-12)
10353 (Ch. 27D213 and Radio Ch. 8W10) (For TV Ch. see Set 210-11, for Radio Ch. see Model 141XX-Set 126-12)
11322, 11324 (Ch. 215213A) (See Model 5240-Set 201-10)
14342 (Ch. 27D213A and Radio Ch. 8W10) (For TV Ch. see Model 5382B-Set 210-11, for Radio Ch. see Model 141XX-Set 126-12)
15312, 15314 (Ch. 215213A) (See Model 5240-Set 201-10)
22312, 22313 (Ch. 29U213) 232-8
23322, 23323 (Ch. 29U213) 232-8
24542 (Ch. 29U273) 224-13
25544 (Ch. 29U273) 224-13
26542 (Ch. 27D273) 224-13
26544 (Ch. 27D273) 224-13
Ch. PC-5-6-26 (See Model 6AW26-PA)
Ch. 2RD190 (See Model 5085)
Ch. 25D201 (See Model 5170)
Ch. 3T810 (See Model 4944)
Ch. 3T110 (See Model 4916)
Ch. 3T190 (See Model 5052)
Ch. 3TV9, 3TV9C (See Model 4900-TV)
Ch. 4E3 (See Model 301)
Ch. 4E10 (See Model 100)
Ch. 5A7 (See Model 100)
Ch. 5-06 (See Model 3AW06)
Ch. 5A10 (See Model 130)
Ch. 5A10, A (See Model 230)
Ch. 583C (See Model 342C)
Ch. 5C3 (See Model 320)
Ch. 5-16 (See Model 5A116)
Ch. 5-26PS (See Model 5AM26PS)
Ch. 689 (See Model 1051)
Ch. 613 (See Model 350)
Ch. 618 (See Model 1030)
Ch. 6-06 (See Model 6AM06)
Ch. 617 (See Model 101)
Ch. 7-46 (See Model 7AM46)
Ch. 819 (See Model 121)
Ch. 8L10 (See Model 141A)
Ch. 8510 (See Model 4970)
Ch. 8W10 (See Model 141XX)
Ch. 8A46 (See Model 8A46)
Ch. 8-57 (See Model 1005)
Ch. 918 (See Model 1035)
Ch. 918A (See Model 4900TV)
Ch. 10-77PA (See Model 10BW76PA)
Ch. 12L7 (See Model 1000)
Ch. 19T510, 19T510A (See Model 5010)
Ch. 215172 (See Model 5212)
Ch. 215173-D (See Model 5301)
Ch. 215212 (See Model 5240)
Ch. 215213 (See Model 5340)
Ch. 21523A (See Model 11322)
Ch. 23T810 (See Model 496A)
Ch. 23T10 (See Model 4935)
Ch. 23U214 (See Model 11T210)
Ch. 23T10 (See Model 5002)
Ch. 24T810 (See Model 4944)
Ch. 24T10 (See Model 4916)
Ch. 24T10 (See Model 4920)
Ch. 24T10 (See Model 5052)
Ch. 24TV9 (See Model 4939TV)
Ch. 24TV9C (See Model 4900TV)
Ch. 25CD202 (See Model 5288)
Ch. 25D173A (See Model 5323)
Ch. 25D213 (See Model 5342)
Ch. 25D190 (See Model 5085)
Ch. 25D201 (See Model 5170)
Ch. 25D202 (See Model 5290)
Ch. 25T10A (See Model 5062)
Ch. 265D160 (See Model 5025)
Ch. 265D170P (See Model 5182)
Ch. 265D170X, XP (See Model 5082)
Ch. 265D171 (See Model 5165X)
Ch. 265D172 (See Model 5267)
Ch. 265D172C (See Model 5220)
Ch. 2655160, B (See Model 5076)
Ch. 2655160L (See Model 5035)
Ch. 2655170 (See Model 5101)
Ch. 2655170D, P (See Model 5104)
Ch. 2655172, A, B (See Model 5270)
Ch. 27D173 (See Model 5325A)
Ch. 27D213 (See Model 5342A)
Ch. 27D213-A (See Model 5382B)
Ch. 27D273 (See Model 26542)
Ch. 29U273 (See Model 24542)
Ch. 417 (See Model 4AW17)
Ch. 417A (See Model 5AW17A)
Ch. 666A (See Model 6-66A)

STARRETT

Gotham 101-12
Henry Hudson, Henry Parks 92-7
John Hancock 96-10
Nathan Hale 87-12

STARRETT-Cont.

Robert E. Lee 92-7
A17CG-1 (Ch. 1751) (See Ch. 1751-Set 165-2A)
A17TG-1 (Ch. 1751) (See Ch. 1751-Set 165-2A)
A20C-2 (Ch. 1851) (See Ch. 1851-Set 165-2A)
A20CD-1 (Ch. 1851) (See Ch. 1851-Set 165-2A)
A20TG (Ch. 1851) (See Ch. 1851-Set 165-2A)
17BA1 (Ch. 1251) 149-13
20BA1 (Ch. 1551) 149-13
27BA1 (Ch. 1251) 149-13
29A1 (Ch. 1451) 149-13
30BA1 (Ch. 1551) 149-13
37B1 (Ch. 1251) 149-13
39A1 (Ch. 1451) 149-13
Ch. 1251 (See Model 17BA1)
Ch. 1451 (See Model 29A1)
Ch. 1551 (See Model 20BA1)
Ch. 1751 165-2A
Ch. 1851 165-2A

STEELEMAN

AF100 180-9
BE-20, BE-21, BE-22 247-11
5E2 257-15
3AR 217-17
3AR3 243-10
3A2 250-20
3A4 253-15
3A5 244-11
30D2 (See Model 30D5-Set 245-8)
30S, 306 245-8
3E1 251-17
3R1 210-12
3R3 238-13
352 247-11
102 184-14
107 178-12
151M 223-11
200 23-25
215 165-13
303 19-31
327 182-13
330 186-12
350, 351 178-12
351 (Lote) 227-14
357 178-13
450, 451 178-14
487 182-14
517 179-12
597 164-10
601 177-12
602 185-13
4000 176-12
5000 186-13
5122 163-11
6000 163-11

STEWART-WARNER

AVCI (Code 9054B), AVC2 (Code 9054AC), AVTI (Code 9054-A)
AS11 (Code 9020-A), A-5112 (Code 9020-B), A5113 (Code 9020-C), A5114 (Code 9020-D) 17-32
A61CR1 (Code 9034-C), A61CR2 (Code 9034-D), A61CR3 (Code 9034-E), A61CR4 (Code 9034-F) 39-25
A61PI (Code 9036-A), A61P2 (Code 9036-B), A61P3 (Code 9036-C) 42-23
A7211 (Code 9026-A), A7212 (Code 9026-B), A7213 (Code 9026-C), A7214 (Code 9026-D) 32-24
AP2CR3, AP2CR5 (Code 9028-C), AP2CR6, AP2CR6S (Code 9028-F) 29-26
B511T, B511T2, B511T3 (Code 9044-A) 58-22
B61T1, B61T2 (Code 9046-A, B) 59-19
B72CR1 (Code 9038A) 47-22
B92CR1, B92CR2, B92CR3, B92CR4, B92CR8, B92CR9, B92CR10 (Codes 9043-A, B, C, D, K, L) 65-14
C51T1 (Code 9054-A), C51T2 (Code 9054-B) 41-22
T-711 (Code 9031-A) 95A-12
T-711A (Code 9031-AM) 95A-12
T-712 (Code 9031-B) 95A-12
T-713 (Code 9031-C) 95A-12
17C-9380A 245-9
21C-9210C (Series "A, B, C, D, E") 192-8
21C-9211D, E, F, G (Series A, B, C) 206-9
21C-9300E, F, G, K, B, L, LB, M, MB, P (Series A thru T) 223-12
21C-9325F, G 258-12
21C-9340E, K, B, L, LB, M, MB, P 258-12
21T-9210A (Series "A, B, C, D, E") 192-8
21T-9210B (Series "A, B, C, D, E") 192-8
21T-9211B (Series A, B, C) 200-9
21T-9211C (Series A, B, C) 200-9
21T-9300A, AA, B, D, H, HA, R, RB, S, T (Series A thru T) 223-12
21C-9360A, AB (Series A, AB) 245-12
24C-9370A, AB (Series A, AB) 254-11
27C-9212A (Series A, B, C) 211-15
27C-9310A, AB (Series A, AB) 254-11
27C-9350A, AB (Series A, AB) 254-11
51T46 (Code 9024B), 51T56 (Code 9024-C) 39-24
51T126 (Code 9018-C), 51T136 (Code 9018-F), 51T146 (Code 9018-H), 51T176 (Code 9018-B) 15-35
61T16 (Code 9022-A), 61T26 (Code 9022-B) 6-6
62T16 (Code 9023-C), 62T16 (Code 9023-E) 6-6
62T36 (Code 9023-F) 2-21
72CR16, 72CR26 18-28
9000-B 11-22
9001-C, D, E, F, G 8-29

SYLVANIA—TRUETONE

SYLVANIA—Cont.

Ch. 1-510-2, -4 (See Model 120BU)
 Ch. 1-512-1 (See Model 386B)
 Ch. 1-512-2 (See Model 386BU)
 Ch. 1-513-1 (See Model 331 Series)
 Ch. 1-513-2 (See Model 331 "U" Series)
 Ch. 1-513-3 (See Model 331 Series)
 Ch. 1-513-4 (See Model 331 "U" Series)
 Ch. 1-514-1, -3 (See Model 105-14 Series)
 Ch. 1-514-4 (See Model 105-14 "U" Series)
 Ch. 1-514-5 (See Model 301 Series)
 Ch. 1-514-6 (See Model 301 "U" Series)
 Ch. 1-518-1 (See Model 175-18 Series)
 Ch. 1-518-2 (See Model 175-18 "U" Series)
 Ch. 1-518-3 (See Model 175-18 Series)
 Ch. 1-518-5 (See Model 372 Series)
 Ch. 1-518-6 (See Model 372 "U" Series)
 Ch. 1-520-0 (See Model 326 Series)
 Ch. 1-520-1, -3 (See Model 120-20 Series)
 Ch. 1-520-4 (See Model 120-20 "U" Series)
 Ch. 1-520-5 (See Model 321 Series)
 Ch. 1-520-6 (See Model 321 "U" Series)
 Ch. 1-520-7 (See Model 326 Series)
 Ch. 1-520-8 (See Model 326 "U" Series)
 Ch. 1-530-1 (See Model 410 Series)
 Ch. 1-530-2 (See Model 410 "U" Series)
 Ch. 1-601-1 (See Model 518B)
 Ch. 1-601-2 (See Model 518B)
 Ch. 1-601-3 (See Model 563B)
 Ch. 1-602-1 (See Model 541B)
 Ch. 1-602-2 (See Model 543)
 Ch. 1-602-3 (See Model 593)
 Ch. 1-603-1 (See Model 178B)
 Ch. 1-604-1 (See Model 434BR)
 Ch. 1-606-1 (See Model 454BR)

SYMPHONETTE
 45-KA-37 263-15

TAPMASTER
 (Also see Recorder Listings)
 PA-1 186-14

TECH-MASTER
 1930 Tel. Rec. 159-14

TELECHRON
 8H67 "Musalarm" 44-23

TELECOIN
 M5TS4 25-28

TELECAST
 ●30T14A-056 (Similar to Chassis) 119-3
 ●38T12A-058 (Similar to Chassis) 109-1
 ●317T3 (Similar to Chassis) 72-4
 ●318T4 (Similar to Chassis) 85-3
 ●318T4-872 (Similar to Chassis) 85-3
 ●318T6A (Similar to Chassis) 85-3
 ●318T6A-950 (Similar to Chassis) 85-3
 ●318T9A-900 (Similar to Chassis) 78-4
 ●321MS39A (Similar to Chassis) 226-11
 ●518T6A (Similar to Chassis) 85-3
 ●518T9A-918 (Similar to Chassis) 78-4
 ●518T10A-916 (Similar to Chassis) 78-4
 ●2318T6A-954 (Similar to Chassis) 85-3
 ●2318T9A-912 (Similar to Chassis) 78-4
 ●2321MS39A (Similar to Chassis) 226-11

TELE-KING
 ●K21 (Ch. TVJ) 177-13
 ●K72 (Ch. TVJ) 177-13
 ●K73 (Ch. TVJ) 177-13
 ●K-74 (Ch. TVJ-Revised) 257-17
 ●K21 (Ch. TVJ) 177-13
 ●K21 (Ch. TVJ) 177-13
 ●KD21M (Ch. TVJ) 177-13
 ●KD28 (Ch. TVJ) 177-13
 ●KD71 (Ch. TVJ) 177-13
 ●KD78 (Ch. TVJ) 177-13
 RK41 (Ch. RD-1) 203-11
 RK51A 202-9
 RKP-53-A 230-12
 ●T-516 (See Model 114—Set 141-13)
 ●16CD3CR (For TV Ch. only see Model 162—Set 129-12)
 ●114 141-13
 ●116, 116C 141-13
 ●117, 117C, 117LO 141-13
 ●117CA, CAF (For TV Ch. only see Model 117—Set 141-13)
 ●162 129-12
 ●172 (Ch. TVG) (See Model 201—Set 131-16)
 ●174 (Ch. TVG) (See Model 201—Set 131-16)
 ●201, 202 131-16
 ●203 (Ch. TVG) (See Model 201—Set 131-16)
 ●410 88-12
 ●416 (See Model 162—Set 129-12)
 ●510 (See Model 410—Set 88-12)
 ●512 88-12
 ●516 (See Model 114—Set 141-13)
 ●612 88-12
 ●710 88-12
 ●712 (See Model 410—Set 88-12)
 ●716 129-12
 ●816-3CR (For TV Ch. only see Model 162—Set 129-12)
 ●916C 129-12
 ●916CAF (For TV Ch. only see Model 162—Set 129-12)
 ●919C 141-13

TELE-KING—Cont.

●919CAF (For TV Ch. only see Model 114—Set 141-13)
 ●920 (Ch. TVG) (See Model 201—Set 131-16)
 ●1014 (Ch. TVG) (See Model 201—Set 131-16)
 ●1016 (Ch. TVG) (See Model 201—Set 131-16)
 Ch. RD-1 (See Model RK41)
 Ch. TVG (See Model 201)
 Ch. TVJ (See Model K21)
 Ch. TVJ (Revised) (See Model K-74)

TELEQUIP
 5135, 5136, 5140A 11-24

TELESONIC (Medco)
 1635 20-22
 1636 21-33
 1642 20-23
 1643 21-34

TELE-TONE
 ●TV140 56-22
 ●TV-170 83-12
 ●TV-208 90-11
 ●TV208TR 95-6
 ●TV-209 (See PCB 21—Set 136-1 and Model TV-249—Set 57-21)
 ●TV-210 (See PCB 21—Set 136-1 and Model TV-249—Set 57-21)
 ●TV-229 95-6
 ●TV-249 (Also see PCB 21—Set 136-1) 57-21
 ●TV-250 91-13
 ●TV-254 91-13
 ●TV-255, TV-256 (Ch. TS) 101-13
 ●TV-259 (See Model TV-249—Set 57-21) 71-14
 TV-282 (See Model TV-285—Set 87-13)
 ●TV-284 87-13
 ●TV-285 87-13
 ●TV-286, 287, 288 93-10
 ●TV-300, TV-301 (Ch. TAA, TAB) 99A-12
 ●TV-300, TV-301 (Ch. TW) 107-10
 ●TV-304, TV-305 (Ch. TAA, TAB) 99A-12
 ●TV-304, TV-305 (Ch. TX) 107-10
 ●TV-306, TV-307 (Ch. TV, TZ) 104-12
 ●TV-308 (Ch. TAC) 109-14
 ●TV-314 (Ch. TAJ) 125-12
 ●TV-315 (Ch. TAA, TAB) 115-13
 ●TV-316 (Ch. TAH) 135-13
 ●TV-318 (Ch. TAM) 124-11
 ●TV-322, TV-323 (Ch. TAM) 124-11
 ●TV-324, TV-325, TV-326 (Ch. TAP, TAP-1, TAP-2) 127-12
 ●TV-329 (See Model TV-324—Set 127-12)
 ●TV-330, TV-331, TV-332, TV-333 (Ch. TAO) 145-11
 ●TV-335, TV-336 (Ch. TAP, TAP-1, TAP-2) 127-12
 ●TV-340 (Ch. TAP, TAP-1, TAP-2) 127-12
 ●TV-345 (Ch. TAP, TAP-1, TAP-2) 127-12
 ●TV-348, TV-349 (Ch. TAP-2) (See Model TV-324—Set 127-12)
 ●TV-355 (Ch. 8001, 8002, 8003) 145-11
 ●TV-357 (Ch. 8001, 8002, 8003) 145-11
 ●TV-358, TV-359 (See Model TV-324—Set 127-12)
 ●TV-360, TV-365 (Ch. 8001, 8002, 8003) 145-11
 ●TV-374 (Ch. 8001, 8002, 8003) (See PCB 35—Set 164-1 and Model TV-330—Set 145-11)
 100, 100-A, 101, 109 (Ch. Series A) 39-26
 109 (Ch. Series) 8-30
 110 (See Model 117-A—Set 1-35) 111, 113 39-26
 117-A (Ch. Series "D") 35 119, 120 (See Model 117-A—Set 1-35) 122, 123 39-26
 124 (See Model 117-A—Set 1-35) 125 39-26
 126 (See Model 117-A—Set 1-35) 127, 130, 131 39-26
 132 (See Model 117-A—Set 1-35) 133 11-25
 134 13-32
 135 14-29
 138 (Ch. Series N) 23-27
 139, 140, 141 (Ch. Series "H") (See Model 135—Set 14-29) 142, 143, 144 (See Model 145—Set 23-28)
 145 (Ch. Series "R") 23-28
 148 (Ch. Series "S") 24-26
 149 (Ch. Series "H") (See Model 135—Set 14-29)
 150 (Ch. Series "T") 38-25
 151 (Ch. Series "S") (See Model 148—Set 24-26)
 152 (Ch. Series "R") (See Model 145—Set 23-28)
 156 (Ch. Series U) 35-23
 157 (Ch. Series "H") (See Model 135—Set 14-29)
 157 (Ch. Series AE) 49-24
 158 (Ch. Series AT) 59-20
 159 (Ch. Series AA) 38-26
 160 (Ch. Series Y) 36-24
 161, 162 (Ch. Series T) 38-25
 163, 164 (Ch. Series "H") (See Model 135—Set 14-29)
 165 (Ch. Series AG) 50-20
 166 (Ch. AE) 49-24
 167, 168, 171 (Ch. Series T) 38-25
 172 (Ch. Series U) 35-23
 174 (Ch. Series T) 38-25
 176 (Ch. Series U) 35-23
 177 51-22
 183 53-24
 185 (Ch. Series AH) 52-21
 190 (Ch. Series AZ) 61-19
 195 (Ch. Series BH) 71-15
 198 59-20

TELE-TONE—Cont.

200 (Ch. Series "AZ") (See Model 190—Set 61-19)
 201 (Ch. Series AX) 74-9
 205 (Ch. Series BD) 73-12
 206 127-11
 214 (Ch. Series "AZ") (See Model 190—Set 61-19)
 215 (Ch. Series BD) 73-12
 228 (Ch. BL) 144-13
 232 (Ch. Series "BP") (See Model 205—Set 73-12)
 235 (Ch. BO) 141-14
 Ch. Series A (See Model 100)
 Ch. Series AA (See Model 159)
 Ch. Series AE (See Model 157)
 Ch. Series AG (See Model 165)
 Ch. Series AH (See Model 185)
 Ch. Series AT (See Model 158)
 Ch. Series AX (See Model 201)
 Ch. Series AZ (See Model 190)
 Ch. Series BD (See Model 205)
 Ch. Series BH (See Model 195)
 Ch. BL (See Model 228)
 Ch. BO (See Model 235)
 Ch. Series C (See Model 134)
 Ch. Series CA (See Model 133)
 Ch. Series D (See Model 117A)
 Ch. Series H (See Model 135)
 Ch. Series J (See Model 109)
 Ch. Series N (See Model 148)
 Ch. Series R (See Model 135)
 Ch. Series S (See Model 148)
 Ch. Series T (See Model 150)
 Ch. TAA, TAB (See Model TV-315)
 Ch. TAC (See Model TV-308)
 Ch. TAH (See Model TV-316)
 Ch. TAJ (See Model TV-314)
 Ch. TAM (See Model TV-318)
 Ch. TAO (See Model TV-330)
 Ch. TAP, TAP-1, TAP-2 (See Model TV-324)
 Ch. TS (See Model TV-255)
 Ch. TW, TX (See Model TV-300)
 Ch. TY, TZ (See Model TV-306)
 Ch. Series U (See Model 156)
 Ch. Series Y (See Model 160)
 Ch. 8001, 8002, 8003 (See Model TV-335)

TELE-VOGUE (See Muntz)

TELEVOX
 RP 22-29
 27B-2W 20-32
 27K-W 20-33
 27P-T 22-28

TELE-VAR (See Audar)

TEMPLE
 E-301 21-35
 E-510 2-3
 E-511 11-26
 E-512, E-514 (See Model E-510—Set 2-3) 2-3
 E-519 2-3
 F-202 12-26
 F-611 9-32
 F-616 5-38
 F-617 12-27
 G-410 27-28
 G-415 43-18
 G-418, G-419 26-25
 G-513 23-29
 G-515 17-34
 G-516 18-31
 G-518 29-27
 G-521 28-33
 G-522 26-26
 G-529 22-30
 G-622 44-24
 G-721 (See Model G-722—Set 24-27) 27-27
 G-722 24-27
 G-723 (See Model G-722—Set 24-27) 27-27
 G-724 38-27
 G-725 34-23
 G-1430 43-19
 G-4108 (See Model G-418—Set 24-25) 24-25
 G-7205 (See Model G-722—Set 24-27) 47-23
 H-411 47-23
 H-521 (See Model G-521—Set 28-32) 44-24
 H-727 (See Model G-725—Set 34-26) 26-21
 ●TV-1776, TV-1777, TV-1778, TV-1779 66-16

TEMPOTONE
 500 E Series 2-8

TEMPLETON (See Temple)

THORDARSON
 T-30W08A 8-31
 T-31W10A 30-30
 T-31W10-AX 57-22
 T-31W25A 9-33
 T-31W50A 20-34
 T-32W00, T-32W10 76-18

THORENS (See Record Changer Listing)

TRAD
 ●C-2020, C-2420, CD2020 173-14
 ●T-20, A 133-14
 ●T-20-E 165-17A
 ●T-1720 173-14
 ●T-1853, A 200-10

TRANSVISION
 ●Ch. Model A 107-11
 ●Ch. A-3 130-15
 ●Ch. A-4 192-10
 ●WRS-3 112-10

TRANSVUE
 ●17XC, 17XT (Similar to Chassis) 132-8
 ●20XC, 20XT (Similar to Chassis) 132-8
 ●601 (Ch. 16AX23, 25, 26) (Similar to Chassis) 99-14

TRANSVUE—Cont.

●610 (Ch. 16AX23, 25, 26) (Similar to Chassis) 99-14
 ●1400T (Similar to Chassis) 132-8
 ●1700C (Similar to Chassis) 132-8
 ●2000C (Similar to Chassis) 132-8

TRAV-LER (Also see Record Changer Listing)

●10T 86-11
 ●12L50, A 108-13
 ●12T 86-11
 14850, A, 14C50, A 108-13
 ●16S50, 16T50A 108-13
 ●16T (Also see PCB 31—Set 156-3) 86-11
 ●20A50 146-11
 ●62R50, 63R50 150-13
 ●64R50, 64R50-1, 64R50-2 146-11
 ●65G50, -1, -2 (See Model 20A50—Set 146-11)
 ●75A50, 75A50-1, 75A50-2 146-11
 ●114-1A, -2 (Ch. 32A1) 150-13
 ●117-3, -4, -6 (Ch. 32A1) 150-13
 ●119-5 (Ch. 32A1) 150-13
 ●217, -10, -11, -12, -14 (Ch. 32A2) 171-11
 ●217-15, 217-16 (Ch. 34A2) (Also see PCB 116—Set 268-1 and Model 217-15—Set 170-14)
 ●217-27 (Ch. 35B2) (See Model 217-15—Set 170-14)
 ●217-32, 217-33 (Ch. 36A2) (See PCB 116—Set 268-1 and Model 217-15—Set 170-14)
 ●217-37 (Ch. 36A2) (See PCB 116—Set 268-1 and Model 217-15—Set 170-14)
 ●217-331 (Ch. 36B2) (See PCB 116—Set 268-1 and Model 217-15—Set 170-14)
 ●217-371 (Ch. 36B2) (See PCB 116—Set 268-1 and Model 217-15—Set 170-14)
 ●219-8A, 219-8B (Ch. 11A2) 162-14
 ●220-9, -9A, -9B (Ch. 33A2) 171-11
 ●220-22, 220-23 (Ch. 34A2) (See PCB 116—Set 268-1 and Model 217-15—Set 170-14)
 ●220-34, 220-35 (Ch. 36A2) (See PCB 116—Set 268-1 and Model 217-15—Set 170-14)
 ●221-24 (Ch. 34A2) (See PCB 116—Set 268-1 and Model 217-15—Set 170-14)
 ●221-27 (Ch. 35B2) (See PCB 116—Set 268-1 and Model 217-15—Set 170-14)
 ●221-36 (Ch. 36A2) (See PCB 116—Set 268-1 and Model 217-15—Set 170-14)
 ●317-33 (Ch. 36A3) (See PCB 116—Set 268-1 and Model 217-15—Set 170-14)
 ●317-44, A (Ch. 46B3) 240-10
 ●317-40, (Ch. 46A3) 240-10
 ●317-60, 317-62 (Ch. 36A3) (See PCB 116—Set 268-1 and Model 217-15—Set 170-14)
 ●320-35 (Ch. 36A3) (See PCB 116—Set 268-1 and Model 217-15—Set 170-14)
 ●321-36 (Ch. 36A3) (See PCB 116—Set 268-1 and Model 217-15—Set 170-14)
 ●321-44, 321-48 (Ch. 46A3) 240-10
 ●321-43 (Ch. 36A3) (See PCB 116—Set 268-1 and Model 217-15—Set 170-14)
 5000 (See Model 50001—Set 11-27) 11-27
 5002 Series (Ch. 109) 12-28
 5007, 5008, 5009 (Ch. 104) 1-36
 5010, 5011, 5012 (Ch. 105) 2-5
 5015 36-25
 5019 23-30
 5020 (Ch. 800) 11-28
 5021 20-30
 5022 101-14
 5027 31-30
 5028 34-24
 5029 33-29
 5030, 5031 32-25
 5034 34-19
 5049 45-24
 5051 32-26
 5054 36-26
 5056-A 90-12
 5060, 5061 116-11
 5066 42-24
 5091 252-12
 5170 163-13
 5180B, M 260-14
 5182-B, -M 263-16
 5300 223-13
 5301 223-15
 5305 260-15
 5310 243-12
 5372 246-10
 6040 49-25
 6050 56-23
 6053 (See Model 6050—Set 56-23) 56-23
 7000, 7001 59-21
 7003 (Ch. 501) 12-29
 7014 59-21
 7016, 7017 84-11
 7023 83-13
 7036 112-11
 7056 262-14
 9051, 9052 265-14
 9060, 9061 265-14
 Ch. 11A2 (See Model 219-8A)
 Ch. 32A1 (See Model 62R50)
 Ch. 34A2 (See Model 217-15)
 Ch. 34A2 (See Model 217-15)
 Ch. 35B2 (See Model 217-27)
 Ch. 36A2 (See Model 217-32)
 Ch. 36A3 (See Model 317-33)
 Ch. 36B2 (See Model 217-331)

TRAV-LER—Cont.

Ch. 46A3 (See Model 317-47)
 Ch. 46B3 (See Model 317-44)
 Ch. 104 (See Model 5007)
 Ch. 105 (See Model 5010)
 Ch. 109 (See Model 5002)
 Ch. 501 (See Model 7002)
 Ch. 800 (See Model 5021)

TRELA
 HW301 14-28

TRUETONE
 D1034A, B, C (See Model D1046A—Set 102-15)
 D1046A 102-15
 D1046B, C, D (See Model D1046A—Set 102-15)
 ●D1092 (Similar to Chassis) 108-7
 D-1234A, B 189-15
 D1240A 187-12
 D1435A, D1436A 239-10
 D1612 28-34
 D1644 12-30
 D-645 (Factory 26A76-650) 64-33
 D1747, D1748 32-27
 D1752 (Factory 7901-14) 34-25
 D1835 (Factory Model 25A86-85) 44-26
 D1836, D1836A (Factory 26A85-856) 45-25
 D1842 (Fact. No. 138PCXM) 46-24
 D1845 31-31
 D1846A, B, C 40-23
 D1850 (Series A) 51-23
 D1949 60-20
 D1950, D1951 (See Model D1850—Set 51-23)
 ●D1952 (See Model D1949—Set 60-20)
 ●D1990 (Factory No. 74F22) 69-13
 ●D1991, B 77-11
 ●D1992 (Factory No. 74F22) 69-13
 ●D1993, B 77-11
 ●D1994 77-11
 ●D1996 (See Model D2983—Set 68-18)
 D2017, D2018 101-15
 D2020 106-15
 D2025A (Fact. Mod. 26A95-906) 93-14
 D2027A 97-18
 D2102A, B 200-11
 D2103A, B 200-11
 D2108A, D2109A 199-14
 D2145 201-12
 D2205 201-12
 D2214A 204-10
 D2226 196-16
 D2237A 182-15
 D2235 197-14
 D2263 190-14
 D2270 211-6
 D2325 A 205-11
 D2383 199-15
 D2385 266-17
 D2386, D2387, D2388 230-13
 D2389 95-16
 D2410A, D2411A, D2412A, D243A 225-19
 D2418A, D2419A, D2420A 257-18
 D2483 261-14
 D2603 (Factory No. 461) 13-33
 D2604 95-14
 D2605 (Factory Model 2A2W) 9-34
 D2606 65-15
 D2612 (Cade SW-9022-G) 3-9
 D2613 13-37
 D2615 (Factory Model 6D110) 2-18
 D2616 (Factory Model 6D117) 10-32
 D2616-B 31-32
 D2619 (Factory No. 2701) 27-29
 D2620 1-28
 D2621 4-32
 D2622 14-30
 D2623 35-29
 D2624 (Factory 27D14-600) 2-6
 D2626 (Fact. No. 457-2) 52-22
 D2630 (Factory 27D14-602 Issue A) 1-10
 D2634 12-31
 D2640 (Factory No. 459) 19-13
 D2642 12-32
 D2644 (Factory No. 101C) 11-30
 D2645 4-39
 D2661 (Factory 4B19) 2-23
 D2663 (Ch. 4C1) 11-31
 D2665 (Factory 4B14 Series A) 22-31
 D2692 39-28
 D2709 (Factory No. 470) 27-30
 D2710 (Factory No. 24D22-6308R) 23-31
 D2718 (Factory No. 227D14-6381U) 23-32
 D2743 25-29
 D2745 (See Model D1645—Set 6-33)
 D2748 (Ch. 7156) 26-27
 D2806, D2807 (Factory Model 181) 19-13
 D2810 (Factory No. 24D24-7308B) 36-27
 D2815 48-25
 D2819 (Factory No. 26A82-738) 38-28
 D2851 35-21
 D2906 (Factory No. 189) 69-14
 D2907 69-14
 D2910 65-16
 D2919 (Fact. No. 60F21) 59-22
 D2963 17-13
 ●D2983 68-18
 ●D2985 70-11
 ●D2987 69-13
 D3120A 203-12
 D3130A, B 203-13
 D3161 190-14
 D3350 189-14
 D3300 225-20
 D3351, D3352, D3353 224-16
 D3490 267-14
 D3615 (Factory 25B2D-606) 18-32
 D3619 (Factory 5P110) 10-33
 D3630, D3630N 19-33
 D3720 24-29
 D3721 (Factory 1108X) 32-28
 D3722 (Fact. No. 472) 51-24
 D3809 (Factory No. 178) 43-22

NOTE: PCB Denotes Production Change Bulletin. Production Change Bulletin Nos. 1 Through 63 Are All Contained in Set No. A-200. ● Denotes Television Receiver.

TRUE-TONE—Cont.

- D3810 39-27
D3811 (Fact. No. 114BXH) 47-24
D3840 49-26
D3910 (Fact. Model 140611) 74-10
D4118, B 209-12
D4124 142-14
D4320 227-15
D4320B 247-13
D4321, A 229-16
D4620 (Factory No. 5C12) 26-28
D4730 (Factory 26C9) 7-28
D4818 (Fact. No. 134DX) 45-26
D4832 (Fact. No. 25C22-82) 47-25
D4842 (Fact. No. 26C21-81) 50-21
2D1088A 105-11
2D1088B 145-1A
2D1089A 113-10
2D1089B 136-14
2D1091 161-10
2D1093A, 2D1094A 119-12
2D1095 134-11
2D1185A (See Model 2D1185B—Set 154-13)
2D1185B 154-13
2D1185C (See PCB 43—Set 177-1, and Model 2D1185B—Set 177-13)
2D1185E (See PCB 43—Set 177-1, PCB 46—Set 180-1 and Model 2D1185B—Set 154-13)
2D1190A, B 147-12
2D1194A 151-11
2D1230B 185-14
2D1230C, D, E (See PCB 98—Set 243-1 and Model 2D1230B—Set 185-14)
2D1230B (Also see PCB 59—Set 193-1)
2D1235A (Ch. 17M5345) 188-13
2D1235B, C, D, E (See PCB 74—Set 215-1 and Model 2D1235A—Set 188-13)
2D1303A 207-11
2D1315A 204-11
2D1315B (See PCB 117—Set 269-1 and Model 2D1315A—Set 204-11)
2D1316A 224-17
2D1325A 204-11
2D1325B (See PCB 117—Set 269-1 and Model 2D1325A—Set 204-11)
2D1326A 224-17
2D1330A (See PCB 98—Set 243-1 and Model 2D1330B—Set 185-14)
2D1331A, B 233-11
2D1331C (See Model 2D1331A—Set 233-11)
2D1336A 238-14
2D1344A, B (Ch. 21M536C) 210-13
2D1352A 242-10
2D1353A (Series A Thru M) 244-12
2D1354A (Ch. 9210P) 194-13
2D1358A 242-10
2D1359A (Series A, C, D, E) 248-10
2D1415A (Ch. 2116) 249-19
2D1416A (Ch. 2116A) 249-19
2D1426A (Ch. 2116A) 249-19
2D1430A (See PCB 98—Set 243-1 and Model 2D1230B—Set 185-14)
2D1430B (See Model 2D1430A)
2D1430C 261-15
2D1431A 261-15
2D2043A 161-10
2D2047B 161-10
2D2052 134-11
2D2053 120-11
2D2149A (Ch. 17A7212) 177-14
2D2152A (Ch. 17AY26)
2D2215A (Ch. 21AY21A)
2D2219A 179-13
2D2223A (Ch. 21AY21A)
2D2301A, 2D2302A 229-17
2D2312A 204-11
2D2312B (See PCB 117—Set 269-1 and Model 2D2312A—Set 204-11)
2D2313A 224-17
2D2313C (Ch. 1775) 249-19
2D2314A 204-11
2D2314B (See PCB 117—Set 269-1 and Model 2D2314A—Set 204-11)
2D2315A 224-17
2D2321A 204-11
2D2321B (See PCB 117—Set 269-1 and Model 2D2321A—Set 204-11)
2D2333A, B 203-14
2D2414A (Ch. 2111A) 249-19
2D2415A (Ch. 2111AA) 249-19
2D2422A (Ch. 1778) 249-19
2D2422B (Ch. 1774) 249-19
2D2423A, 2D2424A, B, 2D2425A, 2D2426A 265-15
2D2433A (See PCB 98—Set 243-1 and Model 2D1230B—Set 185-14)
3D6000 Tel. UHF Conv. 221-12
TURNER
TV-3 Tel. UHF Conv. 231-17
ULTRADYNE
L-46 4-21
ULTRATONE
400 253-16
UNITED MOTORS SERVICE (See Delco or Buick, Cadillac, Chevrolet, Oldsmobile and Pontiac)
U. S. TELEVISION
C16030 99A-12
C19031 99A-12
T-10823 89-15
T16030 99A-12
T19031 99A-12
5A16, 5B16, 5C16 (See Model 5C66—Set 17-9)

U. S. TELEVISION—Cont.

- 5A66, 5B66, 5C66, 5D66MPA 24-30
5C66 (Dumbarton) 17-9
8-16M (Ely) 26-29
UNITONE
88 5-26
UNIVERSAL CAMERA (See Record Changer Listing)
UTAH (See Record Changer Listing)
V-M (Also see Record Changer Listing)
110 191-19
121 242-11
150 139-15
150A 213-9
151 231-20
160 187-13
555-M, O 235-13
556 270-17
560-B, -M 269-15
570 159-15
970 203-11
975 165-16
980 138-12
985 166-16
986 247-14
990 248-11
1001-A 10-34
VAN-CAMP
576-1.6A 7-29
VIDEO CORP. OF AMERICA (See Videola)
VIDEODYNE
10FM, 10TV, 12FM, 12TV 69-15
VIDEOLA
VS-160, VS-161 92-9
VS-165, VS-166, VS-167, VS-168 92-9
VIDEO PRODUCTS (Also see Sheraton)
630-DX Series 213-10
630-DXC 176-13
630-DX24C 176-13
630-K3C 176-13
630-K24C 176-13
VIEWPOINT, RRC-201 11-32
VIC-201A, VIC-201 11-32
VISION MASTER
14MC, MT (Similar to Chassis) 117-8
16MC, 16MT, 16MXC, 16MXCS, 16MXT, 16MXTS (Similar to Chassis) 117-8
17MC, 17MT, 17MXC, 17MXCS, 17MXT, 17MXTS (Similar to Chassis) 117-8
VIZ
RS-1 14-31
VOCATRON
CC-20 (D) 246-11
CC-45 247-15
VOGUE
532 A-P 11-33
Ch. Models 533R, 554R 8-32
WALSLO
2000 (Tel. UHF Conv.) 261-16
WARWICK (See Clarion)
WATTERSON
ARC-4591A 16-36
PA-4585, APA-4587 3-2
RC-4581 16-35
4581 3-32
4582 4-34
4583 249-12
4790 16-34
4800 43-23
WAVEFORMS
A-20 191-20
C-5 191-20
WEBCOR (See Webster-Chicago)
WEBSTER-CHICAGO (Also see Changer and Recorder Listings)
B-123-1 204-12
B-124-1 203-16
B-134-1 205-12
B-135-1 210-14
B-136-1 207-12
D-300-1 255-16
F-123-1 204-12
F-134-1 205-12
F-137-1 205-12
T-136-1 207-12
66-1A 34-26
100-608 121-14
100-621 113-11
129-1, 129-2 215-10
130-1 113-11
161-1 55-23
166 159-16
181-1R 221-13
288 117-14
333-1, 333-2 250-22
362 105-12
760 112-12
762 105-12
1024 (See Model B-124-1—Set 203-16)
1024-1 (See Model B-134-1—Set 205-12)
1035 (See Model B-135-1—Set 210-14)
1036 (See Model B-136-1—Set 207-12)

WEBSTER ELECTRIC (Also see Recorder Listing)

- RFM-1, -2, -3 263-17
WCM-1, WCM5-1 268-15
81-15, 81-15A 142-15
82-25, 82-25A, 83-25 143-15
84-25 145-12
85-25 144-14
605M, S, 606M, S 260-17
610M, S 260-17
906 231-18
1105M 226-10
WEBSTER (Telephone)
W606M 56-24
604M 57-23
WELLS-GARDNER
WG-30A8-A-496 246-12
317G534C-218 (Also See PCB 84—Set 225-1) 195-12
317G534C-220 (Also See PCB 84—Set 225-1) 195-12
317G534C-278 (Also See PCB 84—Set 225-1) 195-12
321GM44-A-462, -464, 321GM44-A-466 266-18
321GM47-486 268-16
321MS31C-222, -224 194-14
321MS31C-227, -274, -276 194-14
321MS31C-280, -282, -284 194-14
321MS39-322 226-11
321MS39-327 226-11
321MS39-376.1 226-11
1321MS31C-296 194-14
2321GM47-488 268-16
2321MS39-324 226-11
2321MS39-370 226-11
2321MS39-396.1 226-11
WESTERN AUTO (See Truetone)
WESTINGHOUSE (Also see Record Changer Listing)
H-104, H-105 4-11
H-104A, H-105A, H-107A, H-108A (See Set 21-36 and Model H-104—Set 4-11)
H-107, H-108, H-110, H-111 4-19
H-113, H-114, H-116 (See Model H-117—Set 11-34)
H-117, H-119 11-34
H-122 6-35
H-122A, B (See Model H-122—Set 6-35)
H-125, H-126 3-19
H-130 6-35
H-133 14-24
H-137 (See Model H-138—Set 6-36)
H-138 6-36
H-147 31-33
H-148 15-37
H-148A (See Model H-148—Set 15-37)
H-153, H-153A (Ch. V-2103) 35-25
H-154 (See Set 21-36 and Model H-104—Set 4-11)
H-155 35-25
H-156 (See Model H-153—Set 35-25)
H-157 (Ch. V-2122) 33-31
H-161 (Ch. V-2118) 34-27
H-162 (See Model H-117—Set 11-34)
H-164 (Ch. V-2119-1) 36-28
H-165 32-29
H-166, H-167 36-28
H-168, H-168A, H-168B (Ch. V-2118) 34-27
H-169 (Ch. V-2124-1) 37-24
H-171 (Ch. V-2103) 35-25
H-171A, C (Ch. V-2103) (See Model H-153—Set 35-25)
H-178 (Ch. V-2123) 35-26
H-182 (Ch. V-2128, V-2128-1) 53-25
H-183, H-183A 48-26
H-184 (See Model H-153—Set 35-25)
H-185 (Ch. V-2131, V-2131-1) 54-20
H-186M, H-187 (Ch. V-2132) 60-21
H-188 (Ch. V-2133) 51-25
H-190, H-191, H-191A (Ch. V-2134) 59-23
H-195 54-20
H-196 65-17
H-196A (Ch. V-2130-1) (See Model H-196—Set 65-17)
H-196A (DX) (Ch. V-2130-1)DX or V-2130-12X) 84-3
H-198 (Ch. V-2137-2) 67-15
H-199 (Ch. V-2137-1) 69-16
H-202 (Ch. V-2182-2) 50-22
H-203 (Ch. V-2137) 62-21
H-204 50-22
H-207A (Ch. V-2130-1, V-2130-1A) 65-17
H-207A (DX) (Ch. V-2130-1)DX or V-2130-12DX and Radio Ch. V-2137) 84-13
H-207B (DX) (Ch. V-2130-1)DX or V-2130-12DX and Radio Ch. V-2137) 84-13
H-210, H-211 (Ch. V-2144, V-2144-1) 61-20
H-212 (Ch. V-2137) 62-21
H-214, H-214A (Ch. V-2103-3) 75-16
H-216, H-216A (Ch. V-2146-05, V-2146-45, V-2149-1) 97A-14
H-217 (Ch. V-2146-11)DX, V-2149, V-2149 (See Set 99A-14 and Model H-217B—Set 91-14)
H-217B (Ch. V-2146-35DX, V-2137, V-2149) 91-14
H-220 59-23
H-223 (Ch. V-2150-01, V-2150-02) 78-14
H-225 (DX) (Ch. V-2130-31)DX or V-2130-32DX) 84-17
H-226 (Ch. V-2146-21DX, -25DX, V-2149) (See Model H-217B—Set 91-14)
H-231 (Ch. V-2150-51 and V-2137-3 or V-2137-3S, V-2149-2) 99A-14
H-242 (Ch. V-2150-31) 97A-14

WESTINGHOUSE—Cont.

- H-251 (Ch. V-2150-81, -82, -84) (See 99A-14 and Model H-60911—Set 95-7)
H-300T5, H-301T5 (Ch. V-2148) 88-14
H-302P5 (Ch. V-2151-1) 91-15
H-303PA, H-304PA (Ch. V-2153) 89-16
H-307T7, H-308T7 (Ch. V-2136) 100-13
H-309P5, H-309P5U (Ch. V-2156) 101-16
H-310T5, H-310T5U, H-311T5, H-311T5U (Ch. V-2161, V-2161U) 99-18
H-312PA, H-312PAU, H-313PA, H-313PAU, H-314PA, H-314PAU, H-315PA, H-315PAU (Ch. V-2153-1) 98-13
H-316C7 (Ch. V-2136-1) 112-13
H-317C7 (Ch. V-2136-1) (See Model H-316C7—Set 112-13)
H-318T5, U (Ch. V-2157, U) 117-15
H-320T5, U (Ch. V-2157, U) 117-15
H-321T5, U, H-322T5, U (Ch. V-2157-1, U) 117-15
H-323T5, U (Ch. V-2157-2, U) 117-15
H-324T7, H-325T7, U (Ch. V-2136-2) 113-13
H-326C7 (See Model H-316C7—Set 112-13)
H-3276U (Ch. V-2157-3U) 126-14
H-328C7, U (Ch. V-2136-4) 137-15
H-331PA, U (Ch. V-2164, U) (Also see PCB 52—Set 186-1) 171-12
H-332PA (See Model H-331PA—Set 171-12)
H-333PA, U (Ch. V-2164, U) (Also see PCB 52—Set 187-1) 171-12
H-334T2U, H-335T2U (Ch. V-2136-5U) 142-16
H-334T7UR (Ch. V-2136-5R) 149-14
H-336T5U, H-337T5U (Ch. V-2157U) 134-12
H-338T6 (Ch. V-2157-4U) 140-13
H-341T5U (Ch. V-2157-4U) 140-13
H-342P5U, H-343P5U (Ch. V-2156-U) 138-13
H-345T5, H-346T5 (Ch. V-2157-4U) (See Model H-338T5U—Set 140-13)
H-348P5, H-349P5 (Ch. V-2156-U) (See Model H-342P5U—Set 138-13)
H-350T7, H-351T7 (Ch. V-2180-1) (Also see PCB 52—Set 186-1)
H-354C7 (Ch. V-2180-2) 158-13
H-355T5, H-356T5 (Ch. V-2157-5) 161-11
H-357C10 (Ch. V-2180-5) 161-12
H-359T5, H-360T5 (Ch. V-2186-1) 158-15
H-361T6 (Ch. V-2181-1) 187-16
H-365T5, H-366T5 (Ch. V-2157-7) 185-15
H-367T5 (Ch. V-2157-8) 189-17
H-368P5, H-369P5 (Ch. V-2156-U) (See Model H-342P5U—Set 138-13)
H-370T7, H-371T7 (Ch. V-2180-8) 186-16
H-372PA, H-373PA, H-374-1 and H-377 Optional Pwr. Supply 188-14
H-374T5, H-375T5 (Ch. V-2157-9) 189-17
H-376PA (Ch. V-2182-1 and H-377 Optional Power Supply) 188-14
H-377 (Power Supply) (See Set 188-14 or Set 233-12)
H-378T5, H-379T5, H-380T5, H-381T5 (Ch. V-2184-1) 211-17
H-382T5, H-383T5 (Ch. V-2157-10) 215-14
H-384T5 (Ch. V-2157-10) (See Model H-382T5—Set 215-14)
H-385T5, H-386T5 (Ch. V-2157-11) 204-13
H-387T5 (Ch. V-2157-11) (See Model H-385T5—Set 204-13)
H-388T5 (Ch. V-2157-12) 215-15
H-391T5, H-392T5 (Ch. V-2157-14) 219-19
H-393T6 (Ch. V-2181-2) 210-15
H-397T5, H-398T5 (Ch. V-2184-2) 232-10
H-400PA, H-401PA, H-402PA, H-403PA (Ch. V-2164-2) 205-13
H-405P5, H-406P5 (Ch. V-2156-2) 266-19
H-405T5 (Ch. V-2157-14) (See Model H-391T5—Set 231-19)
H-409PA, H-410PA, H-411PA (Ch. V-2185-1 and H-377 Optional Power Supply) 233-12
H-414PA, H-415PA (Ch. V-2182-2) 257-19
H-417T5, H-418T5 (Ch. V-2186-1) 239-11
H-420T5, H-421T5 (Ch. V-2157-13) 264-18
H-422PA, H-423PA, H-424PA, H-425PA (Ch. V-2188-1) 245-11
H-431T5, H-432T5, H-433T5, H-434T5 (Ch. V-2184-1) (See Model H-378T5—Set 211-17)
H-457T6, H-458T6, H-459T6, H-460T6 (Ch. V-2229-1) 269-16
H-461PA, H-462PA, H-463PA, H-464PA (Ch. V-2182-2) 257-19
H-465R6, H-466R6 (Ch. V-2229-2) 269-16
H-467R6, H-468R6 (Ch. V-2229-3) 269-16
H-475T5, H-476T5, H-477T5, H-478T5 (Ch. V-2236-1) 266-20
H-479PA (Ch. V-2182-2) 257-19
H-600T16 (Ch. V-2150-61, A, B) 98-14
H-601K12, H-602K12 (Ch. V-2150-41) 98-14
H-603C12 (Ch. V-2152-01 and V-2149-3) 100-14

WESTINGHOUSE—Cont.

- H-604T10, A (Ch. V-2150-91A, -94, -94A) (See Set 99A-14 and Model H-604T10—Set 95-7)
H-605T12 (Ch. V-2150-101) 97-19
H-606K12 (Ch. V-2150-111, A) 120-12
H-607K12 (Ch. V-2150-111, A) 120-12
H-608C12 (Ch. V-2152-01, V-2149-3) (See Model H-603C12—Set 100-14)
H-609T10 (Ch. V-2150-94C) 95-7
H-610T12 (Ch. V-2150-136) 105-13
H-611C12 (Ch. V-2152-16) 112-14
H-613K16 (Ch. V-2150-146) 107-12
H-614T12 (Ch. V-2150-136) 105-13
H-615C12 (Ch. V-2152-16) 112-14
H-617T12 (Ch. V-2150-176, U-177U) (Also see PCB 10—Set 116-1) 103-17
H-618T16 (Ch. V-2150-186, A, C, CA) (Also see PCB 10—Set 116-1) 103-17
H-619T12, U (Ch. V-2150-176, U-177U) (Also see PCB 10—Set 116-1) 103-17
H-620K16 (Ch. V-2150-186, A, C, CA) (Also see PCB 10—Set 116-1) 103-17
H-622K16 (Ch. V-2150-186, A, C, CA) (See PCB 10—Set 116-1 and Model H-617T12—Set 103-17)
H-625T12 (Ch. V-2150-197) 114-11
H-626T16 (Ch. V-2150-197) 116-13
H-627T16 (Ch. V-2171) 116-13
H-628K16, H-629K16 (Ch. V-2171) 116-13
H-630T14 (Ch. V-2176) 116-13
H-633C17 (Ch. V-2176) 116-13
H-636T17 (Ch. V-2175) 127-13
H-637T14 (Ch. V-2177) 116-13
H-638K20 (Ch. V-2178) 129-13
H-639T17 (Ch. V-2192, -1) 133-15
H-640T17 (Ch. V-2175-3, -4, H-640T17A) (Ch. V-2192, -1, -2, -3, -4, -5, -6) (Also see PCB 28—Set 150-1) 133-15
H-641K17 (Ch. V-2175-1, -5), H-641K17A (Ch. V-2192, -1, -2, -3, -4, -5, -6) (Also see PCB 28—Set 150-1) 133-15
H-642K20 (Ch. V-2178) 129-13
H-642K20A (Ch. V-2194, V-2194A, V-2194-1) 137-16
H-643K16 (Ch. V-2179, V-2179-1) 127-13
H-646K17 (Ch. V-2192) 133-15
H-647K17 (Ch. V-2175-3) 133-15
H-648T20 (Ch. V-2201-1) (Also see PCB 42—Set 176-1) 154-15
H-649T17 (Ch. V-2200-1) (Also see PCB 42—Set 176-1) 154-15
H-649T17 (Ch. V-2192-4) (See Model H-639T17—Set 133-15)
H-650K21 (Ch. V-2192-4) (See Model H-639T17—Set 133-15)
H-650T17 (Ch. V-2200-1) (Also see PCB 42—Set 176-1) 154-15
H-652K20 (Ch. V-2194-2, -3) (See PCB 31—Set 157-3 and Model H-642K20A—Set 137-16)
H-652K20 (Ch. V-2201-1) (Also see PCB 42—Set 176-1) 154-15
H-653K24 (Ch. V-2202-2, V-2210-1) (Also see PCB 35—Set 164-1) 160-13
H-654T17 (Ch. V-2175-3, -4, V-2192-4) 133-15
H-655K17, H-656K17, H-657K17 (Ch. V-2200-1) (Also see PCB 42—Set 176-1) 154-15
H-657K17 (Ch. V-2192-4, -5, -6) (See PCB 28—Set 150-1 and Model H-639T17—Set 133-15)
H-658T17 (Ch. V-2192, -1) (See PCB 28—Set 150-1 and Model H-639T17—Set 133-15)
H-659T17 (Ch. V-2204-1) (Also see PCB 42—Set 176-1) 154-15
H-660C17, H-661C17 (Ch. V-2203 and Radio Ch. V-2180-3) (Also see PCB 46—Set 180-1) 157-12
H-662K20 (Ch. V-2201-1) (Also see PCB 42—Set 176-1) 154-15
H-663T17 (Ch. V-2192-2) (See PCB 28—Set 150-1 and Model H-639T17—Set 133-15)
H-663T17 (Ch. V-2204) (Also see PCB 42—Set 176-1) 154-15
H-664K17 (Ch. V-2200-1) (Also see PCB 42—Set 176-1) 154-15
H-665T16 (Ch. V-2206-1) (See PCB 42—Set 176-1 and Model H-648T20—Set 154-15)
H-667T17, H-668T17 (Ch. V-2216) (Also see PCB 40—Set 172-1) 167-15
H-673K21 (Ch. V-2217-1) (See Model H-667T17—Set 167-15)
H-676T21 (Ch. V-2217-1) (See Model H-667T17—Set 167-15)
H-678K17, H-679K17 (Ch. V-2216-1, -2, -3) (Also see PCB 40—Set 172-1, PCB 45—Set 179-1 and PCB 52—Set 186-1) 167-15
H-681T17 (Ch. V-2150-11) (See PCB 45—Set 179-1, PCB 52—Set 186-1 and Model H-667T17—Set 167-15)
H-689K24 (Ch. V-2219-1) (Also see PCB 52—Set 186-1) 174-14
H-689T16 (Ch. V-2184-1) (See PCB 40—Set 172-1, PCB 58—Set 195-1 and Model H-667T17—Set 167-15)
H-690K21, H-691K21 (Ch. V-2217-1) (See Model H-667T17—Set 167-15)
H-692T21 (Ch. V-2217-2, -3) (See PCB 43—Set 177-1, PCB 52—Set 186-1 and Model H-667T17—Set 167-15)

NOTE: PCB Denotes Production Change Bulletin. Production Change Bulletin Nos. 1 Through 63 Are All Contained in Set No. A.200. * Denotes Telephone Receiver.

ZENITH

ZENITH—Cont.

Ch. 4140 (See Model J402)
 Ch. 4160T (See Model J420T)
 Ch. 4K01 (See Model K412G)
 Ch. 4K40 (See Model K401)
 Ch. 4102 (See Model S-9010)
 Ch. 4103 (See Model L2281)
 Ch. 4140 (See Model L401)
 Ch. 4141 (See Model L403F)
 Ch. 4142 (See Model L406F)
 Ch. 5C01, 5C01Z (See Model 50011)
 Ch. 5C02, 5C02Z (See Model 50011)
 Ch. 5C04 (See Model 5R080)
 Ch. 5C40 (See Model 5G003)
 Ch. 5C40Z (See Model 5G003Z)
 Ch. 5C40Z2 (See Model 5G003Z2)
 Ch. 5C51 (See Model 5G036)
 Ch. 5E02 (See Model 5D810)
 Ch. 5C01 (See Model G511)
 Ch. 5G02 (See Model G510)
 Ch. 5G03 (See Model G516)
 Ch. 5G40 (See Model G500)
 Ch. 5G41 (See Model G503)
 Ch. 5H01 (See Model H511)
 Ch. 5H40 (See Model H500)
 Ch. 5H41 (See Model H503)
 Ch. 5J03 (See Model J514)
 Ch. 5J41 (See Model J504)
 Ch. 5K02 (See Model K510)
 Ch. 5K03 (See Model K518)
 Ch. 3K04 (See Model K526)
 Ch. 5I03 (See Model I518)
 Ch. 5I06 (See Model I518)
 Ch. 5I07 (See Model I520)
 Ch. 5I08 (See Model I566)
 Ch. 5I09 (See Model I565E)
 Ch. 5I41 (See Model I505F)
 Ch. 5I42 (See Model I507)
 Ch. 5M02 (See Model M510G)

ZENITH—Cont.

Ch. 5R01 (See Model R511F)
 Ch. 6C01 (See Model 6D014)
 Ch. 6C05, Z (See Model 6D015)
 Ch. 6C06 (See Model 7R070)
 Ch. 6C21 (See Model 6R084)
 Ch. 6C22 (See Model 6R087)
 Ch. 6C40 (See Model 6G001)
 Ch. 6C41 (See Model 6G004R)
 Ch. 6C50 (See Model 6G038)
 Ch. 6E02 (See Model 6R886)
 Ch. 6E05 (See Model 6D815)
 Ch. 6E40 (See Model 6G801)
 Ch. 6G01 (See Model G660)
 Ch. 6G05 (See Model G615)
 Ch. 6G05Z1 (See Model H615Z1)
 Ch. 6G20 (See Model G2957)
 Ch. 6H01 (See Model H661E)
 Ch. 6H02 (See Model H664)
 Ch. 6J02 (See Model J644)
 Ch. 6J03 (See Model J616)
 Ch. 6J05 (See Model J615)
 Ch. 6K02 (See Model K666R)
 Ch. 6K03 (See Model K622)
 Ch. 6I03 (See Model L622)
 Ch. 6I20 (See Model L677E)
 Ch. 6L40 (See Model L600)
 Ch. 6R40, 6R41 (See Model 1600)
 Ch. 7E01 (See Model 7H820)
 Ch. 7E02 (See Model 7H822)
 Ch. 7E02Z (See Model 7H822WZ)
 Ch. 7E22 (See Model 7R887)
 Ch. 7F01 (See Model 7H920)
 Ch. 7F02 (See Model 7H922)
 Ch. 7F03 (See Model 7H918)
 Ch. 7F04 (See Model 7H921)
 Ch. 7G01 (See Model G725)
 Ch. 7G01Z (See Model H725)
 Ch. 7G02 (See Model G724)
 Ch. 7G04 (See Model G723)
 Ch. 7H02 (See Model H724)

ZENITH—Cont.

Ch. 7H02Z (See Model H724Z)
 Ch. 7H02Z1 (See Model H724Z1)
 Ch. 7H02Z2 (See Model H724Z2)
 Ch. 7H04 (See Model H723)
 Ch. 7H04Z (See Model H723Z)
 Ch. 7H04Z1 (See Model H723Z1)
 Ch. 7H04Z2 (See Model H723Z2)
 Ch. 7J03 (See Model J733)
 Ch. 7K01 (See Model K725)
 Ch. 7K20 (See Model K777E)
 Ch. 7L05 (See Model L721)
 Ch. 8C01 (See Model 8H023)
 Ch. 8C20 (See Model 8H032)
 Ch. 8C21 (See Model 9H079)
 Ch. 8C40 (See Model 8C005Y)
 Ch. 8C40T(21) [See Model 8G005-YT (21)]
 Ch. 8C40T (22) [See Model 8G005-YT (22)]
 Ch. 8E20 (See Model 8H832)
 Ch. 8G20 (See Model G881)
 Ch. 8G20/22 91A-13
 Ch. 8H20 (See Model H880RZ)
 Ch. 8H20 Revised (See Model H880)
 Ch. 8H20Z (See Model J880)
 Ch. 8I20 (See Model L880 or L2285R)
 Ch. 8I21 (See Model L8458)
 Ch. 9E21 (See Model 9H811)
 Ch. 9E21Z (See Model 9H995)
 Ch. 9F22 (See Model 9H984)
 Ch. 10H20 (See Model H3467R)
 Ch. 10H20Z (See Model H3273E)
 Ch. 10I20 (See Model L1083E or L2592R)
 Ch. 11C21 (See Model L2H090)
 Ch. 11M20 (See Model HFM1184E)
 Ch. 13D22 (See Model 14H789)
 Ch. 19K20 (See Model K1815E)
 Ch. 19K20-3 (See Model K1820E-3)

ZENITH—Cont.

Ch. 19K22 (See Model K1812E)
 Ch. 19K22-3 (See Model K1812E-3)
 Ch. 19K23 (See Model K2299R)
 Ch. 19K23-3 (See Model K2235E-3)
 Ch. 19K24 (See Model K2229E)
 Ch. 19K24-3 (See Model K2229E-3)
 Ch. 19L25, U (See Model L1846E, EU)
 Ch. 19L26, U (See Model L1812E, EU)
 Ch. 19L27, U (See Model L2236E, EU)
 Ch. 23G22 (See Model G2322)
 Ch. 19L28, U (See Model L2229E, EU)
 Ch. 19I30, U (See Model L2250E)
 Ch. 19I33, U (See Model L2228R, RU)
 Ch. 19I34, U (See Model L1800R, RU)
 Ch. 19M20 (See Model M1800E)
 Ch. 19M20U (See Model M1800EU)
 Ch. 19M20Z (See Model M1800EZ)
 Ch. 19M21 (See Model M2228R)
 Ch. 19M21U (See Model M2228RU)
 Ch. 19M21UZ (See Model M2250-RUZ)
 Ch. 19M21Z (See Model M2228RU)
 Ch. 19R20, U (See Model R1800E, EU)
 Ch. 19R21, U (See Model R2229E, EU)
 Ch. 19R22, U (See Model R2257E, EU)
 Ch. 20H20 (See Model H2029R)
 Ch. 20J21 (See Model J2027E)
 Ch. 20J22 (See Model J2026R)
 Ch. 20M20 (See Model M2237R)
 Ch. 20M20U (See Model M2237EU)
 Ch. 20M20Z (See Model M2237EZ)

ZENITH—Cont.

Ch. 21J20 (See Model J2127E)
 Ch. 21J21 (See Model J2127R)
 Ch. 21K20 (See Model K-2230E)
 Ch. 21K20-3 (See Model K2260R-3)
 Ch. 21L21, U (See Model L2259E, EU)
 Ch. 22H20 (See Model H2226R)
 Ch. 22H21 (See Model H2229R)
 Ch. 22H22 (See Model H2242E)
 Ch. 22L20, U (See Model L2571R, RU)
 Ch. 23G22 (See Model G2322)
 Ch. 23G23 (See Model G2957)
 Ch. 23G24 91A-13
 Ch. 23G24Z1 (See Model G2322Z1)
 Ch. 23H22, 23H22Z (See Model H-2328E)
 Ch. 24G20 (See Model G2420E)
 Ch. 24G20-OX (See Model G2420-EOX)
 Ch. 24G21 (See Model G2454R)
 Ch. 24G21-OX (See Model G2454-R-OX)
 Ch. 24G22/24 (See Model G2441R)
 Ch. 24G23/25 (See Model G3059R)
 Ch. 24G24 (See Model G2441)
 Ch. 24G26 91A-12
 Ch. 24G26Z1 (See Model G2441Z1)
 Ch. 24H20 (See Model H2437E)
 Ch. 24H21 (See Model H2445R)
 Ch. 27F20 (See Model 27T965R)
 Ch. 28F20 (See Model 28T960E)
 Ch. 28F20Z (See Model 28T960E-Z)
 Ch. 28F21 (See Model 28T961E)
 Ch. 28F22 (See Model 28T962E)
 Ch. 28F23 (See Model 28T964R)
 Ch. 28F25 (See Model 28T962E)
 Ch. 28K20 (See Model K2827R)
 Ch. 29G20 (See Model G2951)

RECORD CHANGERS

(CM-1) indicates service data also available in Howard W. Sams 1947 Record Changer Manual. (CM-2) indicates service data available in Howard W. Sams 1948 Record Changer Manual. (CM-3) indicates service data available in Howard W. Sams 1949, 1950 Record Changer Manual. (CM-4) indicates service data available in Howard W. Sams 1951, 1952 Record Changer Manual. (CM-5) indicates service data available in Howard W. Sams 1953 Record Changer Manual.

ADMIRAL

RC-150 (CM-1) 26-31
 RC160, RC160A, RC161, RC161A
 (See Model RC200—Set 9 and
 Model RC160—Set 21-37)
 RC-170, RC-170A (CM-1) 31-2
 RC-180, RC181 (CM-2) 76-1
 RC-182 (See Model RC-181—Set
 76-1 and Supplement—Set 76-2)
 (CM-2)
 RC-200 (CM-1) 9
 RC-210, RC211, RC212 (CM-3)
 72-1
 RC-220, RC-221, RC-222, RC-320,
 RC-321, RC-322 [See Set 79-1
 and Changes in Set 108-2 (CM-3)]
 RC400 (CM-4) 104-1
 RC500 (CM-4) 132-2
 RC-550 (See Model RC-500—Set
 132-2 (CM-4) and Model RC-550
 —Set 185-2 (CM-5))
 RC600 (CM-5) 218-2
AERO
 46A (CM-1) 19-34
 47A (CM-2) 77-2
AVIOLA
 100 (CM-1) 33-32
BELMONT
 C-9 (CM-2) 34-21
COLLARO
 RC-521, RC-522 (CM-5) 205-4
 3RC-521, 3RC-522 (CM-5) 205-4
 3RC-531, 3RC-532 237-4
COLUMBIA
 104 124-2
CRESCENT
 C-200 (CM-1) 20-37
 6 Series (CM-3) 89-4

CRESCENT—Cont.

250 Series (CM-2) 78-5
 350 Series (CM-2) 80-3
 500 Series (CM-5) 197-4
FARNSWORTH
 P-51, P56 (CM-1) 13-36
 P-72, P73 (CM-2) 75-8
GARRARD
 RC-60 (CM-2) 81-7
 RC-80 (CM-4) 157-5
 RC90 258-8
GENERAL ELECTRIC
 P6 (CM-2) 79-8
GENERAL INDUSTRIES
 RC130L (CM-1) 22-33
GENERAL INSTRUMENT
 204 (CM-1) 23-34
 205 (CM-1) 10
LEAR
 PC-206A (CM-1) 18-33
MAGUIRE
 ARC-1 (CM-1) 7
MARKEL
 70, 71 (CM-2) 84-8
 74, 75 [See Set 91-7 (CM-3) and
 Supplement—Set 131-11]
MILWAUKEE ERWOOD
 10700 (CM-1) 16-37
 11200 (CM-2) 86-6
 11600 (CM-3) 73-7
 12300 (CM-4) 138-5
MOTOROLA
 B24RC, B25RC, B27RC, B28RC
 6 Series (CM-1) 12-35

MOTOROLA—Cont.

RC30 (CM-2) 80-9
 RC36, A (CM-4) 147-8
 RC36C [See Model RC36—Set
 147-8)
 RC37 (CM-4) 141-8
 RC40 [See Model RC37—Set 141-8
 (CM-4)]
OAK
 6666 (CM-1) 19-35
 9201 (CM-3) 111-10
PHILCO
 D10, D10A (CM-1) 14-21
 M-4 (CM-1) 25-30
 M-7 (CM-1) 28-35
 M-8 (CM-2) 83-7
 M-9C (CM-2) 74-7
 M-12C (CM-3) 109-9
 M-20 (CM-3) 103-11
 M-22 (CM-4) 140-6
RCA
 RP168 (CM-3) 72-10
 RP-176 (CM-1) 25-31
 RP-177 (CM-2) 44-27
 RP-178 (CM-2) 79-12
 RP-190 Series (CM-4) 144-7
SEEBURG
 K (CM-1) 11-36
 L (CM-1) 24-34
 M (CM-1) 32-19
 S, SQ (CM-2) 78-12
SILVERTONE
 101.761-2, 101.762-2
 (CM-2) 77-10
 101.761-3, 101.762-3
 (CM-2) 83-11
 101.762, 101.763 (CM-2) 88-11
 488.218 (CM-2) 243-9
 488.219 (Late) 244-9

SPARTON

C48 (CM-2) 87-11
THORENS
 CD-40 (CM-1) 39-29
 CD43 222-15
TRAVLER
 A (CM-3) 72-13
UNIVERSAL CAMERA
 100 (CM-1) 36-30
UTAH
 550 (CM-1) 8
 650 (CM-1) 22-34
 700 (CM-1) 27-31
 7001 (CM-2) 83-15
V-M
 200-B (CM-1) 15-36
 400 (CM-1) 26-33
 400 (Late) (CM-2) 90-13
 402, 400C (CM-2) 82-12
 402D, 400D (CM-2) 87-14
 404 [See Model 405—Set 73-14
 (CM-3)]
 405 (CM-3) 73-14
 406, 407 (CM-3) 102-6
 800 (CM-1) 21-38
 800-D (CM-2) 84-12
 802 (CM-3) 77-12
 910 (CM-3) 95-14
 925, 936 252-13
 950 [See Set 107-13 (CM-3) and
 Supplement—Set 131-17]
 950, 951 (Late) (CM-5) 216-11
WEBSTER-CHICAGO
 50 (CM-1) 24-35
 56 (CM-1) 17-36
 60 (CM-1) 29-28
 77 (CM-4) 137-14
 100 (CM-4) 135-14

WEBSTER-CHICAGO—Cont.

106 (CM-4) 146-12
 121, 122, 123, 124, 125 (CM-5) 206-12
 126, 127, 129 (CM-5) 208-13
 133 (CM-2) 82-13
 148 (CM-2) 86-12
 246 (CM-2) 74-11
 256 (CM-2) 88-13
 346 (CM-3) 100-12
 356, 357 (CM-3) 106-16
WESTINGHOUSE
 V4914 (CM-2) 47-26
 V4944 (CM-2) 86-13
 V6235 134-13
 V6676 136-15
ZENITH
 S11478 (CM-1) 23-35
 Series 700R (CM-2) 91-8
 S11680 (CM-1) 27-32
 S14001 (CM-2) 75-17
 S13675, S-14002, S14006, S14008
 (CM-2) 85-15
 S14004, S14007 (CM-2) 79-18
 S14012, S14014 (CM-3) 110-14
 S14022 (CM-3) 112-15
 S14023 (CM-3) 105-14
 S14024, S14025 (CM-3) 112-15
 S14026 (CM-3) 105-14
 S14027 (CM-3) 112-15
 S-14028, S-14029, S-14030, S-
 14031 (CM-4) 145-13
 S-14036 (CM-4) 145-13
 S-14053, S-14054, S-14056,
 S-14057 226-13
MISCELLANEOUS
 Series 700F (CM-2) 89-9
 Series 700F 33/45 (CM-3) 75-11
 Series 700FLP (CM-2) 101-6
 Series 700FS (CM-2) 104-8

RECORDERS

AMPEX

400A, 401A (CM-5) 213-1
AMPRO
 730 (CM-4) 133-4
 731 (For electrical unit see Folder
 166-5; for mechanical unit see
 Folder 133-4)
 731-R (See Model 731)
 755, 756 262-1
BRUSH SOUND MIRROR
 BK-401 (CM-1) 42-25
 BK-403 (CM-2) 78-3
 BK-416 (CM-2) 81-4
 BK-437, BK-437S, BK-441, BK-442,
 BK-443P (CM-5) 164-3
 BK-455P 245-2
BRUSH MAIL-A-VOICE
 BK-501, BK-502, BK-503 (CM-1)
CONCERTONE
 1401 (401) (CM-4) 155-4
CRESCENT
 H-1A (CM-4) 130-5
 H-2A1 Series (CM-3) 119-4
 H-19 Series "Steno"
 (See Model H22A1)—Set
 125-4)
 H-22A1 125-4
 H2000 Series (CM-4) 120-4

CRESCENT—Cont.

M-2001 Series (CM-4) 120-4
 M-2500 Series (CM-4) 120-4
 M-3000 Series (CM-4) 120-4
 M-3001 Series (CM-4) 120-4
 M-3500 Series (CM-4) 120-4
 900 Series 239-3
 1000 Series (CM-2)
 1000 Series Revised (CM-2) 77-4
CRESTWOOD
 CR-201 (CM-3) 118-4
 400 Series (401, 402) 251-5
DUKANE
 11A55FF, 11B55 (CM-5) 187-5
 11A75 248-5
EICOR
 230 223-6
 400 235-4
 1000 (CM-3) 90-4
EKOTAPE (WEBSTER-ELECTRIC)
 101-4, 5, 102-4, 5, 103-4, 5
 104-4, 5 (CM-3) 116-12
 101-8, 101-9, 102-9, 103-8
 (CM-5) 170-6
 109, 110, 111, 112 (CM-4) 152-5
 114, 115, 116, 117 (CM-5) 189-8
 205, 206 228-8
FEDERAL
 37-B 259-6

GENERAL INDUSTRIES

R70, R90 (CM-1) 35-28
 R90L [See Model R90—Set 35-28
 (CM-1)]
 250 (CM-4) 143-8
INTERNATIONAL ELECTRONICS
 PT3 (CM-2) 88-4
KNIGHT
 96-144 (CM-4) 158-6
 96-485 (CM-5) 183-8
 96-499 (CM-4) 158-6
 96-590 240-3
 96RX676 269-7
LEAR DYNAPORT
 WC-311-D (CM-2) 80-8
MAGNECORD AUDIAD
 AD-1R (CM-2) 84-7
 PT6, A, AH, AHX, AX (CM-5) 190-6
 PT63-A, AH, AHX, AX (CM-5) 190-6
MASCO
 DC37R (CM-4) 148-9
 D37 (CM-4) 148-9
 D37R (CM-4) 148-9
 LD37, LD37R (CM-4) 148-9
 52, 52C, 52CR, 52L, 52LR, 52R
 (CM-5) 214-6
 375 (CM-3) 117-7


MITCHELL

1290 263-12
PENTRON
 HT-225, TR-4 267-9
 PB-A2, PB-1 (CM-5) 184-11
 9T-3 (CM-4) 153-10
 9T-3C (CM-4) 162-9
RCA
 MI-12875 (CM-2) 85-12
 SRT-301 (M1-15910) 224-11
RECORDIO (See Wilcox Gay)
RELEST
 CIA (CM-4) 123-13
REVERE
 T-100 (CM-4) 149-11
 T-500 [See Model T-100—Set 149-
 11 (CM-4)]
 TR-200, TR-600 (For electrical unit
 see Folder 165-10; for mechani-
 cal unit see Folder 149-11)
 T-70153, T-70157, T-70163, T-
 70167, T-70253, T-70257, T-
 70263, T-70267, T-77153, T-
 77157, T-77163, T-77167, T-
 77253, T-77257, T-77263, T-
 77267 (CM-5) 193-9
SILVERTONE
 70 (Ch. 567, 230, 577, 231)
 (CM-4) 121-11
 771 (CM-1) 26-32
 101.774-2, 101.774-4
 (CM-3) 114-10

ST. GEORGE

1100 Series (CM-1) 40-24
TAPE MASTER
 PT-121 (CM-5) 186-14
 PT-125 (CM-5) 198-15
 PT-150 [For Mechanical Unit Only
 See Model PT-125—Set 198-15
 (CM-5)]
TELECTRO-TAPE
 A 254-12
TDC
 130 (Stereo) 256-13
WEBSTER-CHICAGO
 79-80 (CM-1) 37-26
 178 (CM-3) 113-12
 210 (CM-4) 159-17
 228 (CM-4) 156-13
 2010 [See Model 210—Set 159-17
 (CM-4)]
WEBSTER ELECTRIC
 (See Ekotape)
WILCOX GAY
 2A10, 2A10B, 2A11, 2A11B180-10
 3A10, 3A11 (CM-5) 200-13
 3C10 (CM-5) 215-17
 3F10 (CM-5) 220-11
 4A10 255-18
WIRE RECORDING CORP.
 WP (CM-2) 76-19

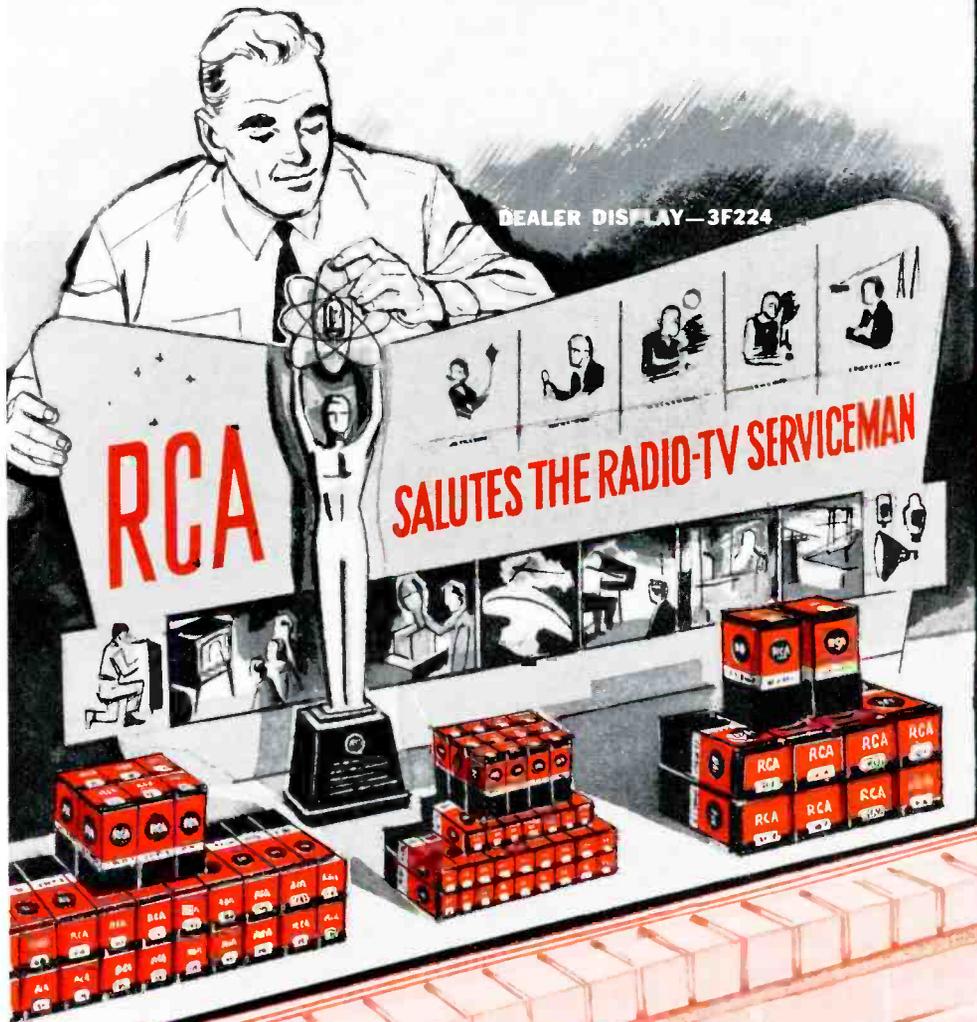GET READY FOR . . . NATIONAL TELEVISION SERVICEMEN'S WEEK MARCH 7-12



DEALER DISPLAY—3F224

Television dealers and service technicians all over the country are preparing to tie-in with a great promotional event. It's National Television Servicemen's Week, March 7-12, sponsored by the RCA Tube Division and registered officially with the Chamber of Commerce of the United States.

You can use this unique merchandising plan right in your own neighborhood to meet and sell more television service prospects than ever before. Your RCA Tube Distributor offers you excellent promotional materials to help you identify yourself and your store with this nationwide consumer promotion.

Plan an active participation in National Television Servicemen's Week now. Act today! See your RCA Tube Distributor for full details.



RADIO CORPORATION of AMERICA
ELECTRON TUBES HARRISON, N.J.


Use These Promotional
Materials



ELECTRONIC STATUETTE
(3F220)



PROMOTION KIT (3F223)

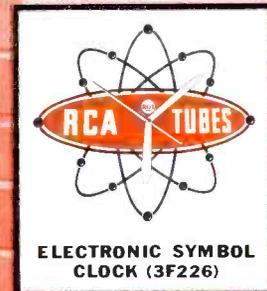


ELECTRONIC SYMBOL
CLOCK (3F226)



TV SERVICE SIGN
(3F230)






TEST EQUIPMENT
AWARDS

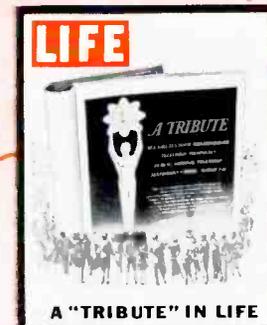

A "TRIBUTE" IN LIFE

THE RIGHT FUSE

AT HAND: TIME SAVED: YOUR PROFIT

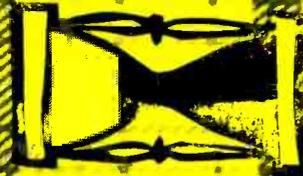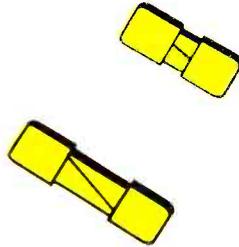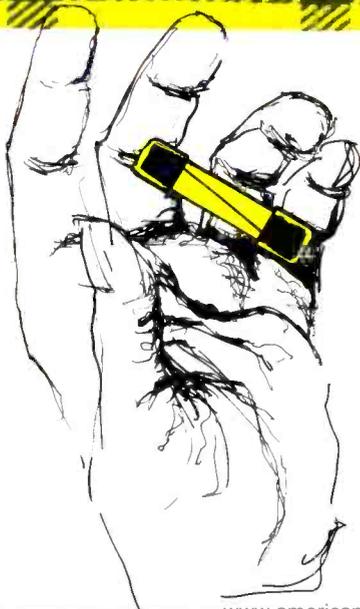

LITTELFUSE



YOUR BENCH BOX

For the average TV-radio service operation this box provides the perfect container for the right number of fuses you should keep on hand. Supplied to you as a service by your distributor. The cover lists the fuses most widely used in TV, radio and communications service. You or your distributor salesman can replenish your stock quickly by checking what is in the box against the listing on the lid.

Ask your distributor today for full information on these time-saving money-making service aids. Littelfuse also provides illustrated price sheets, cross-reference sheets and fuse guides. For your convenience Littelfuse products are listed and cross-referenced in all Howard Sams Photofact folders.



FUSE DISPENSER

Ideal where your service turnover is greater. A revolving drum with self-dispensing channels to hold the individual boxes of fuses. No time lost in looking for the proper fuse—no time lost taking inventory of your stock—no time lost because you do not have the right fuse.



ONE CALL KIT

One call is all. This kit provides the fuse you need for 94% of all TV fuse service calls. A real service, the perfect assortment in the perfect container for your portable tool box.