
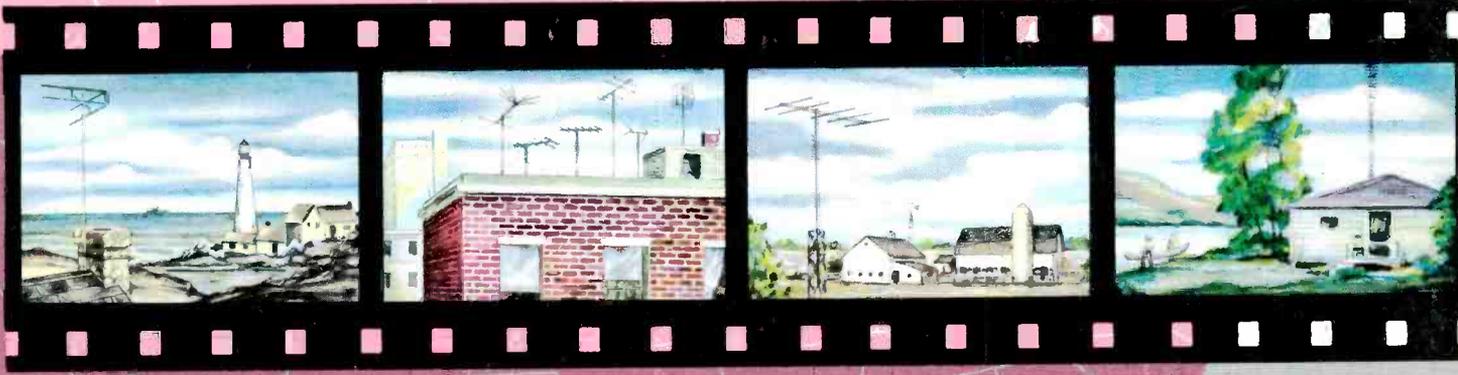


Lewis W. Dams

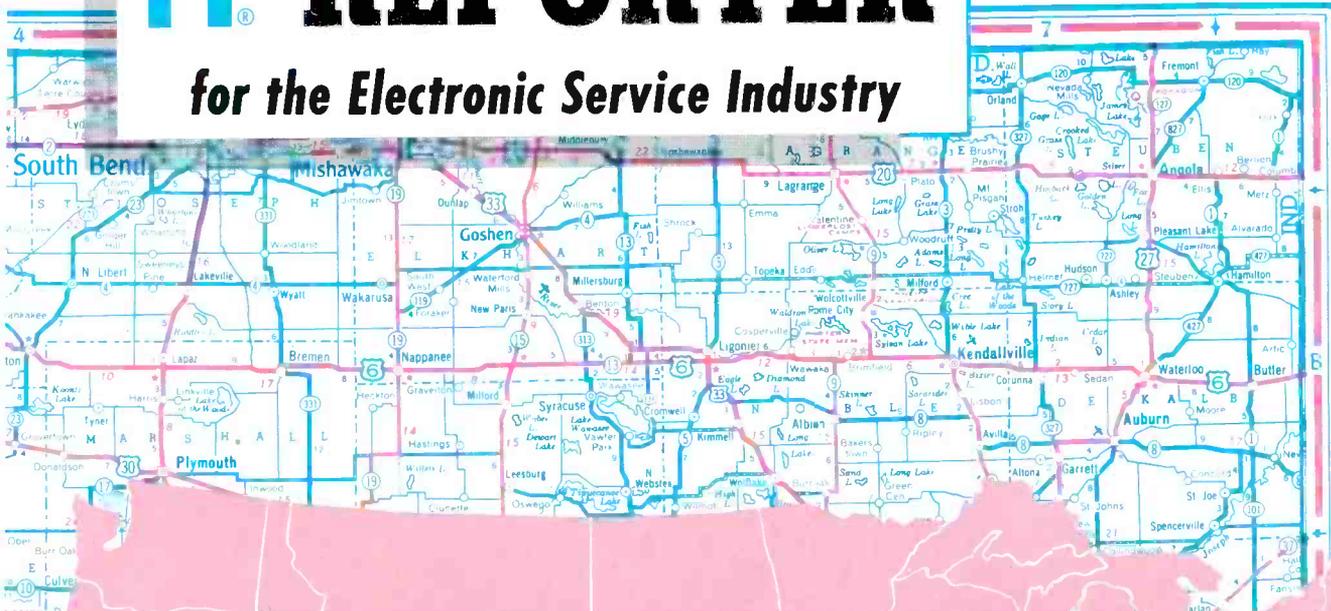

REPORTER


for the Electronic Service Industry



**COLOR TV
TRAINING SERIES
Part XVI**

...ANTENNAS...
...TEST EQUIPMENT...
...SERVICING...

Preferred for modern set servicing

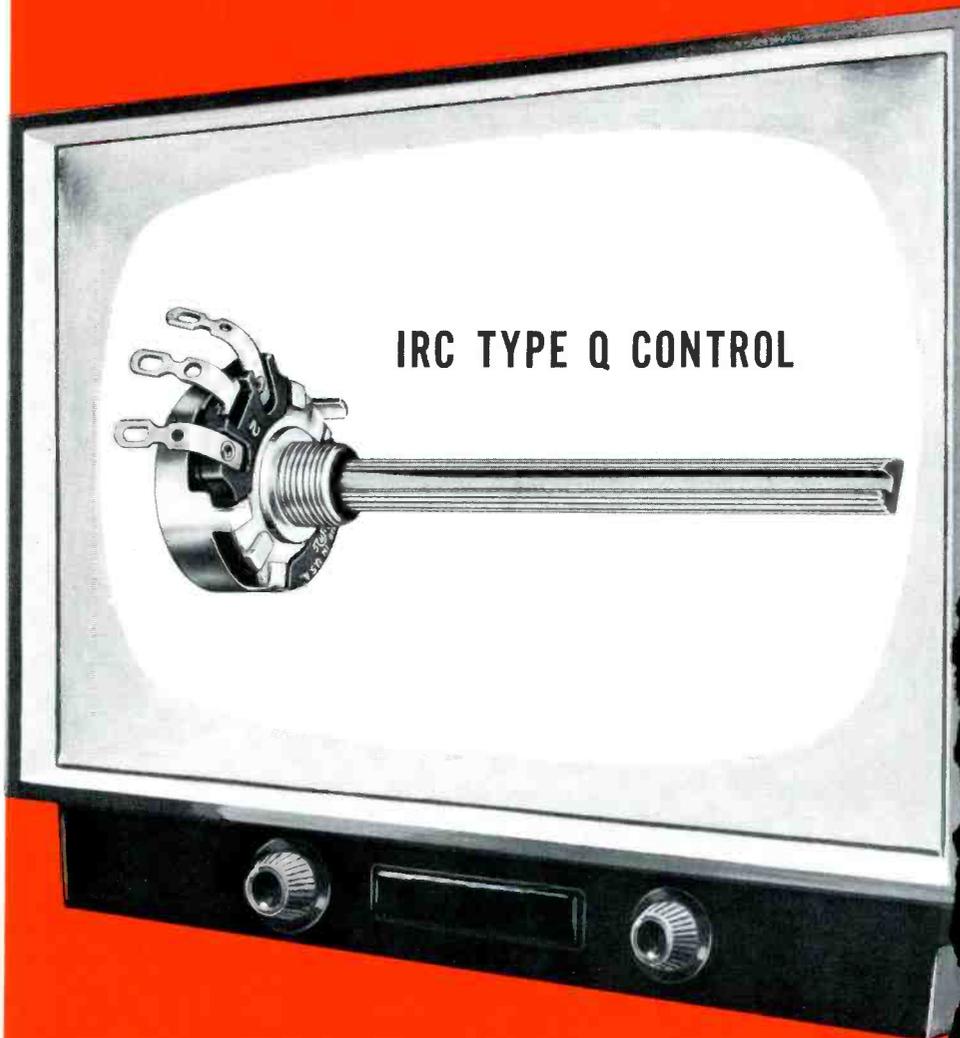

Service technicians get greater coverage with less investment; more practical service features; and easier, faster installation with the IRC Type Q Control. Here's a dependable, basic control that is directly designed for modern set servicing. For appearance, performance and price . . . there's none better. So why settle for less? Tell your Distributor you want Q Controls . . . most servicemen do.



Wherever the Circuit Says 



This 8 page catalog gives you all the facts . . . Send for your free copy now—

INTERNATIONAL RESISTANCE CO.

Dept. 363, 401 N. Broad St., Phila. 8, Pa.

In Canada: International Resistance Co., Ltd., Toronto, licensee

KNOBMASTER FIXED SHAFT

Q Control standard shaft is knurled, flatted and slotted —fits most knobs without alteration.

INTERCHANGEABLE FIXED SHAFTS

Exclusive IRC convenience feature—provides fast conversion to "specials", with FIXED shaft security. 15 types available.

1/4" LONG BUSHING

Accommodates all small sets, yet handles large set needs perfectly.

7 STANDARD TAPERS

Full coverage of all taper requirements is provided in the Q Control.

94 RESISTANCE VALUES

For TV, AM and FM coverage, 94 values of plain and tapped controls are furnished.

QUALITY APPEARANCE

The handsome professional appearance of IRC Q Controls lets you point to your work with pride.

CUSHIONED TURN

The smooth, quality of "feel" of a Q Control contributes to customer confidence.

TYPE 76 SWITCHES

Either of two type IRC switches attached as quickly and easily as a control cover—meets all your requirements.

JAMES R. RONK
Editor

LESTER H. NELSON
Managing Editor

W. WILLIAM HENSLER
Technical Editor

GLEN E. SLUTZ
Asst. Technical Editor

Editorial Staff

GWEN BIGHAM
WILLIAM E. BURKE
HENRY A. CARTER
LESLIE D. DEANE
ROBERT B. DUNHAM
PHYLLIS J. HURLEY
THOMAS A. LESH
GEORGE B. MANN
GLENN A. McROAN
EVELYN S. MOUSER
MARGARET NEFF
C. P. OLIPHANT
VERNE M. RAY
PAUL C. SMITH
CALVIN C. YOUNG, JR.

ANTHONY M. ANDREONE
GLENN R. SMITH
Art Directors

ROBERT W. REED
Photography

ARCHIE E. CUTSHALL
DOUGLAS G. BOLT
Production

★

HOWARD W. SAMS
Publisher

Business Department:

Donald B. Shaw, V. P.
Treasurer

F. T. Dobbs, Secretary

Joe H. Morin, Sales Mgr.

Ann W. Jones, Advertising

Eastern Representatives

Paul S. Weil and
Donald C. Weil
39-01 Main Street,
Flushing 54, New York
Independence 3-9098

Western Representatives

Maurice A. Kimball Co., Inc.
2550 Beverly Blvd.
Los Angeles 57, Cal.
DUnkirk 8-6178

681 Market St.
San Francisco 5, Cal.
EXbrook 2-3365



Howard W. Sams

for the Electronic Service Industry

VOL. 5 • NO. 9

SEPTEMBER • 1955

CONTENTS

Antennas—the Eyes of TV Receivers	George B. Mann	5
Color TV Training Series (Part XVI)	C. P. Oliphant and Verne M. Ray	7
Shop Talk	Milton S. Kiver	11
Diagrams for Setting Up Test Equipment	Paul C. Smith	13
In the Interest of Quicker Servicing	Calvin C. Young, Jr.	17
Notes on Test Equipment	Paul C. Smith	19
Audio Facts	Robert B. Dunham	21
The Triode Phase Detector	Thomas A. Lesh	23
Examining Design Features	Leslie D. Deane	25
Troubles in Video IF and Detector Systems	Leslie D. Deane and Calvin C. Young, Jr.	29
Dollar and Sense Servicing	John Markus	33
PHOTOFACT Cumulative Index No. 52 Covering Photofact Sets Nos. 1-289 Inclusive		87

SUBJECT REFERENCE

ANTENNAS AND ACCESSORIES	Replacing Tubes in the Tube Caddy	57
Comparisons Between Antennas and the Human Eye	Routing Service Calls	57
AUDIO	Symptoms and Troubles in Video IF and Detector Systems	29
Care and Handling of Records	Ways to Improve Service	59
COLOR TV	TELEVISION	
Loss of Color Synchronization	General Electric Model 21T17, Phase Detector in	78
Reference Patterns for Trouble Shooting	Motorola Model 21T21E, Phase Detector in	23
Troubles With Color Purity	TEST EQUIPMENT	
Troubles With Convergence	Authorized Model 101F Cathode-Ray Tube Tester and Rejuvenator	70
GENERAL THEORY	Diagrams for Setting Up Test Equipment	13
Triode Phase Detector, Operation of	Hickok Model 770 Oscilloscope	71
RADIO	Hycon Model 614 VTVM	69
Raytheon Transistorized Radio (Chassis 8RT1)	Hycon Model 617 Oscilloscope	19
SERVICING	RCP Model 780 Sweep Generator	73
Alignment Setup Diagrams	Raytronic Cathode Beamer, Gas Test With	75
Gas in Picture Tubes, Quick Check for	Test Equipment for Rapid Checks	11
Line-Voltage Variations		

Copyright 1955 by Howard W. Sams & Co., Inc.
No part of the PF REPORTER may be reproduced without written permission. No
patent liability is assumed with respect to the use of information contained herein.

The PF REPORTER is published monthly by Howard W. Sams & Co., Inc., 2201 East 46th Street, Indianapolis 5, Indiana. The PF REPORTER is on sale at 25¢ a copy at 1401 jobbers of Electronic Parts throughout the United States and Canada. (In Canada 30 cents.) When available, back numbers may be obtained by sending 35¢ for each copy desired. Entered as second class matter October 11, 1954, at the Post Office at Indianapolis, Indiana, under the Act of March 3, 1879.

SUBSCRIPTION DATA: For those desiring the convenience of delivery to their homes or shops, each issue of the REPORTER will be mailed direct, promptly upon publication. Rates: U. S. and its Possessions, one year \$3.00. Canadian subscriptions, one year \$3.60. All other countries \$12.00 per year in American money.

TV CAPACITOR SERVICING DATA

For Every Manufacturer from A to Z

FREE FROM SPRAGUE

These two pocket-size manuals are the hottest radio-TV servicing guides ever produced. Both contain the most complete—and the most up-to-date—capacitor replacement information available ANYWHERE!

Keep them both handy and you'll never have to thrash around for the right capacitor replacement information. Sprague makes them all, Sprague lists them all, and Sprague distributors know them all—all to help you handle every capacitor job right every time.


What's more, you don't have to pay a red cent for these valuable, expensive-to-prepare, expensive to keep up-to-date manuals. You can get them both FREE from Sprague distributors located in every sales area in the United States. We'll be glad to send you the name of the one nearest you. Or, for 10c to cover postage and mailing, we'll gladly send you the manuals direct from Sprague Products Co., 105 Marshall St., N. Adams, Mass.

DON'T BE VAGUE...INSIST ON

SPRAGUE®

WORLD'S LARGEST CAPACITOR MANUFACTURER

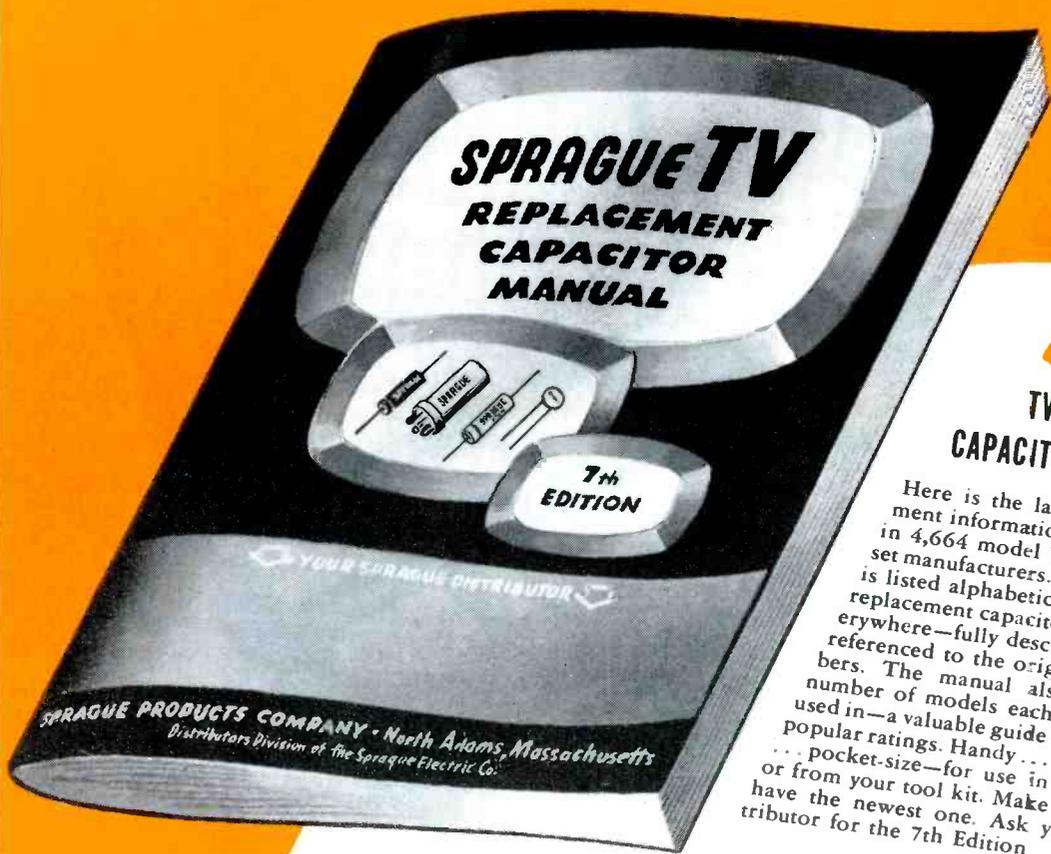Sprague Products Co. is the Distributors' Division of the Sprague Electric Co.




FREE!
TV REPLACEMENT
CAPACITOR MANUAL K-101

Here is the latest capacitor replacement information for every capacitor in 4,664 model TV sets made by 85 set manufacturers. Every manufacturer is listed alphabetically, with Sprague replacement capacitors—available everywhere—fully described and cross-referenced to the original part numbers. The manual also shows the number of models each capacitor is used in—a valuable guide for stocking popular ratings. Handy... convenient... pocket-size—for use in the shop or from your tool kit. Make sure you have the newest one. Ask your distributor for the 7th Edition

FREE!
CERAMIC CAPACITOR
REPLACEMENT MANUAL K-200

This handy little guide is the most informative, the most complete manual of its kind ever published. Pocket-size, like Sprague's TV replacement Capacitor Manual K-101, it lists every conceivable ceramic capacitor and printed circuit replacement... for every television set made... during the past five years. All told, more ceramic capacitor values than can be found in any other manufacturer's line, including discs and tubulars. And each capacitor or printed circuit listed is one you can depend on for a no-call-back replacement. Ask your distributor for it today. It's new!

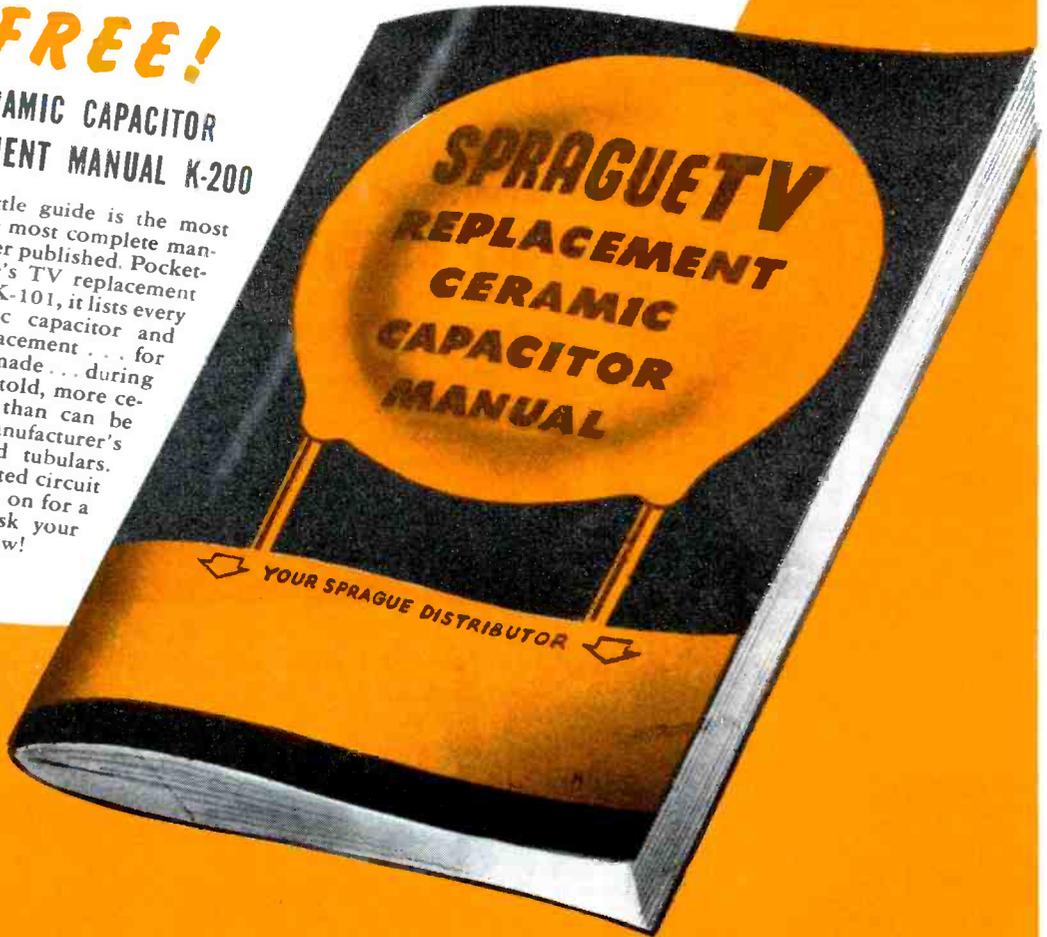

Always at your fingertips...

TV WIRE-WOUND CONTROLS

thanks to the

CLAROSTAT PD-1 PACKAGE

Here's a versatile assortment of wire-wound controls with a selection of the most popular Pick-A-Shaft field-attached shafts, packaged in an attractive, convenient, hinge-cover box.

The PD-1 includes eight different values of the well-known Clarostat Series A10 (4-watt) wire-wound controls, eight Pick-A-Shaft* shafts (two each of the four most popular types); and a handy mounting-nut wrench.

For focus controls alone, the assortment services over 2000 TV set models! Also provides for other functions such as width, linearity, balance and gain. Included is a data sheet listing TV manufacturers' part numbers with proper replacements from this assortment.

And of course the controls may be used in various test equipment, radios, hi-fi systems, industrial electronics, etc.



CLAROSTAT
FUZOHM[†]
12-1-7.5 ohms
List Price \$0.75 ea



and don't overlook those
CLAROSTAT RESISTOR CARDS!

GK-1	20 most popular 10-watt wire-wounds	(1 ohm to 25K)
GK-2	32 most popular 2-watt wire-wounds	(5 to 2000 ohms)
GK-3	36 most popular 5-watt wire-wounds	(1 to 4000 ohms)
GK-4	54 most popular 5-watt wire-wounds	(1 ohm to 10K)
GK-5	50 most popular 10-watt wire-wounds	(1 to 9000 ohms)
GK-6	45 most popular 10-watt wire-wounds	(5 ohms to 50K)
GL-1	12 "Fuzohm" [†] 7.5-ohm fuse-type resistors	

Order Your PD-1 Package Today!

Clarostat distributors have it waiting for you. Take advantage of this time- and money-saving assortment. Ask for latest Clarostat Catalog—or write us.

[†]Trade-mark.

*Reg. U. S. Pat. Office



Controls and Resistors

CLAROSTAT MFG. CO., INC., DOVER, NEW HAMPSHIRE

In Canada: Canadian Marconi, Co., Ltd., Toronto 17, Ont.

antennas

the EYES of
TV
RECEIVERS

by GEORGE B. MANN

The eye is one of the most important sense organs in the human body. Its function can be likened in many ways to that of a simple type of television antenna. The eye receives light waves; whereas, the antenna receives radio-frequency waves.

Limitations

Both the eye and the antenna have limitations in what they can do. The human eye can perceive only a limited range of light frequencies. This frequency range extends from red at the low end of the visible spectrum to violet at the high end. One might say that the eye is "tuned" to this range of light frequencies in much the same manner that a television antenna may be tuned to a certain band of television frequencies. The RF response curve of a simple type of television antenna closely resembles the light-frequency response curve of the human eye.

Another limitation of human eyes and antennas is the inability to isolate a weak source of energy in the presence of strong sources of energy. An example of this, in the case of the human eye, is the fact that a neon sign will appear dim in the daytime. Although the neon sign is the same brilliance day or night, the surrounding light has reduced the apparent brilliance to a very low level and the eye has difficulty in seeing the neon sign. A simple form of television antenna also has difficulty in isolating a signal in the presence of high-level atmospheric noise and strong local interference. It

might be said that the antenna is blinded by the interference.

Another limiting factor associated with the eye and the antenna is the amount of receiving area presented to the incoming wave. The total receiving area which the eye presents to the incoming light is very small. If the light intensity is very low, the amount of light striking the retina in the eye will not be great enough to cause a response which the human brain can interpret. Similarly, the simple television antenna presents a limited area to the incoming radio wave. If the incoming wave is weak, the receiver will detect the signal but it will be unable to produce a usable picture.

Another comparison between human eyes and television antennas is the limited range of direction from which maximum energy can be received at any one instant. When looking straight ahead at a certain object, there is a circular field of clear vision around this object. As the eye is shifted, the field moves; and as this field of clear vision moves farther away from the object, the object becomes less distinct. The field in front of the eye is analogous to the field directly in front of the antenna. As the antenna is turned away from the energy source, the amount of energy which the antenna can receive becomes less. This characteristic of a television antenna is referred to as directivity.

These limits are imposed upon the human eye because of the basic

make-up of the eye. The human eye as a receiving element cannot be changed to accommodate other frequency ranges or wider bandwidths. In contrast to this, the antenna receiving element can be designed for any particular range of radio frequencies and can also be designed for a certain bandwidth. This allows us to obtain greater versatility in antenna performance.

An example of this versatility is in overcoming the limitations of bandwidth. A receiving element composed of thin conductors like those shown in Fig. 1A has a narrow bandwidth. This means that the response to signals drops off rapidly at either side of the resonant frequency. A tuned element can be made

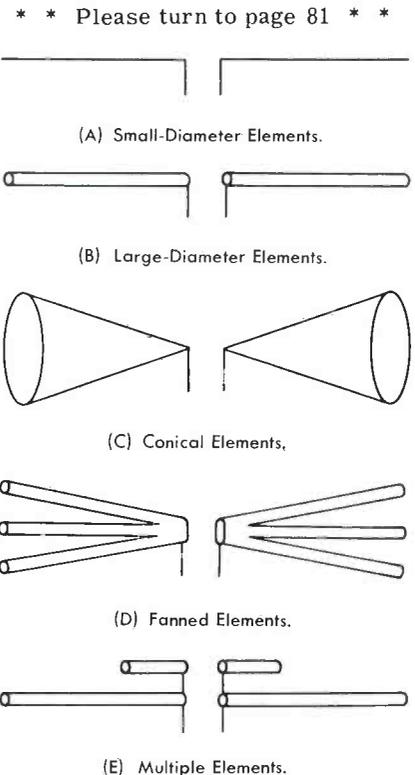


Fig. 1. Receiving Elements Showing Methods of Increasing Bandwidth.

*If you want
 "Trouble-Free"
 fuses in all
 sizes and
 types —*
**TURN
 TO BUSS!**

You can depend on BUSS fuses to operate properly under all service conditions. This means that BUSS fuses will open and prevent further damage to your customers' equipment when there is trouble on the circuit.



And just as important, BUSS fuses won't blow when trouble doesn't exist. Users are not annoyed with useless shutdowns caused by needless blows.

To make sure of this "trouble-free" operation — every BUSS fuse normally used by the Electronic Industries is tested in a sensitive electronic device. Any fuse not correctly calibrated, properly constructed and right in all physical dimensions is automatically rejected.

A complete line of fuses is available. Made in dual-element (slow blowing), renewable and one time types . . . in sizes from 1/500 ampere up — plus a companion line of fuse clips, blocks and holders.

When it's a fuse you need — think first of BUSS. You will be protecting both the product and your good name against troubles and complaints often caused by use of poor quality fuses.

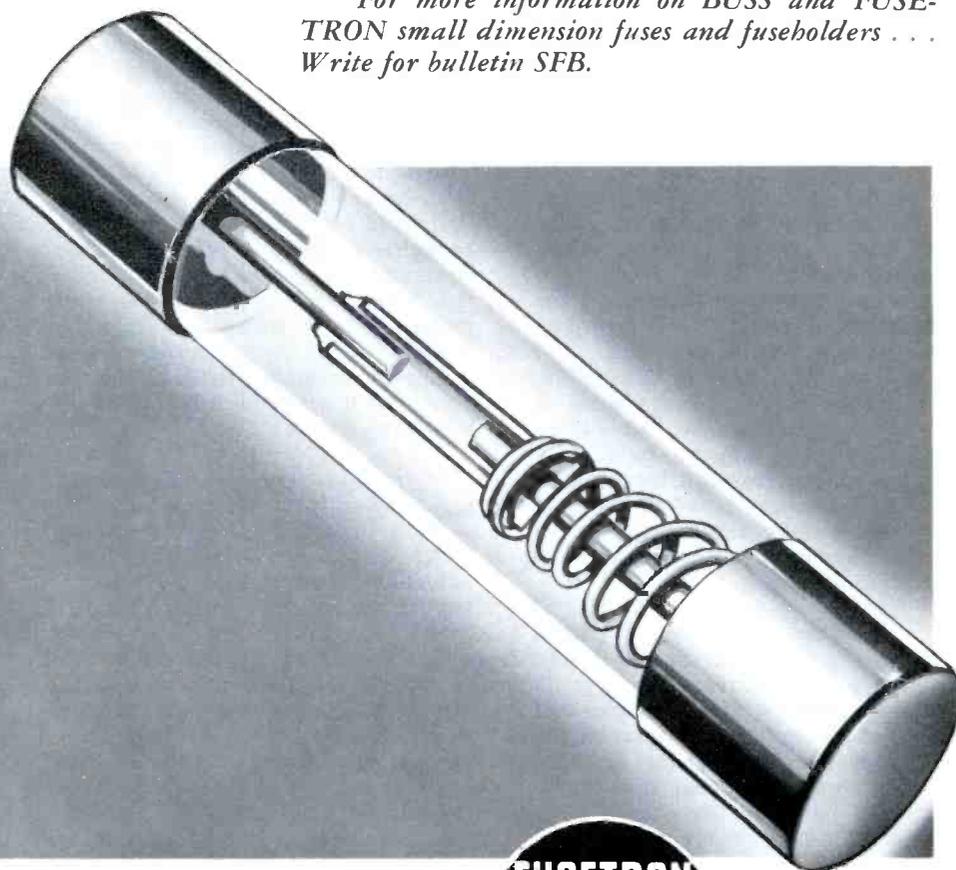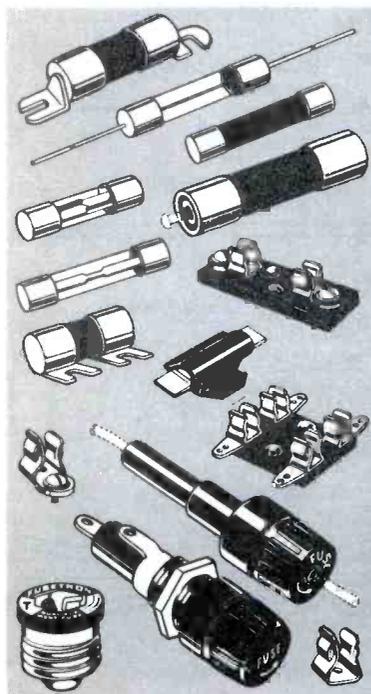For more information on BUSS and FUSE-TRON small dimension fuses and fuseholders . . . Write for bulletin SFB.



Makers of a complete line of fuses for home, farm, commercial, electronic, automotive and industrial use.

BUSSMANN MFG. CO.

University at Jefferson

FUSETRON

TRUSTWORTHY NAMES IN
ELECTRICAL PROTECTION

BUSS

Div. McGraw Electric Co.

St. Louis 7, Mo.

COLOR TV TRAINING SERIES

PART XVI TROUBLE SHOOTING

by C. P. Oliphant and Verne M. Ray

In Part XV of this Color TV Training Series, trouble-shooting procedures were discussed for the condition of hum in the monochrome picture and for the condition of wrong colors. In this part, the subject of trouble shooting will be concluded by a coverage of the troubles which cause loss of color synchronization and those which affect purity and convergence.

Loss of Color Synchronization

Whenever the chrominance and reference signals are arriving at the color demodulators, the chrominance signal will be demodulated and color will be reproduced, provided that the circuits which accomplish demodulation and those which handle the color signals after demodulation are operating properly. It has been shown in previous discussions that if either the chrominance or the reference signals are absent at the inputs of the demodulators, the receiver will not reproduce color. It has also been shown that the colors will not be right unless the chrominance and reference signals have the correct amplitudes and phase relationships.

When the frequency of the reference signals is incorrect, loss of color synchronization will be experienced. This trouble will be indicated on the screen by horizontal or diagonal stripes of variegated colors. The stripes may be either in motion or stationary. If the oscillator is operating at a random frequency, the stripes will be in motion. Fig. E1 of the Color Plate shows the appearance of the screen when the 3.58-mc oscillator is not operating at the correct frequency. As indicated by the small number of diagonal stripes, the frequency of the oscillator is only slightly off. If the oscillator were operating at a frequency that is far from correct, there would be a large number of horizontal or diagonal stripes.

The circuit of a color-sync section is shown in Fig. 12-22. This circuit is employed in the RCA Victor Models CT-100 and 21-CT-55 color receivers. Let us briefly review the operation of this type of circuit.

The output of the 3.58-mc oscillator is amplified, then a portion of it is fed back to the phase detectors where it is compared with the color-burst signal. If the

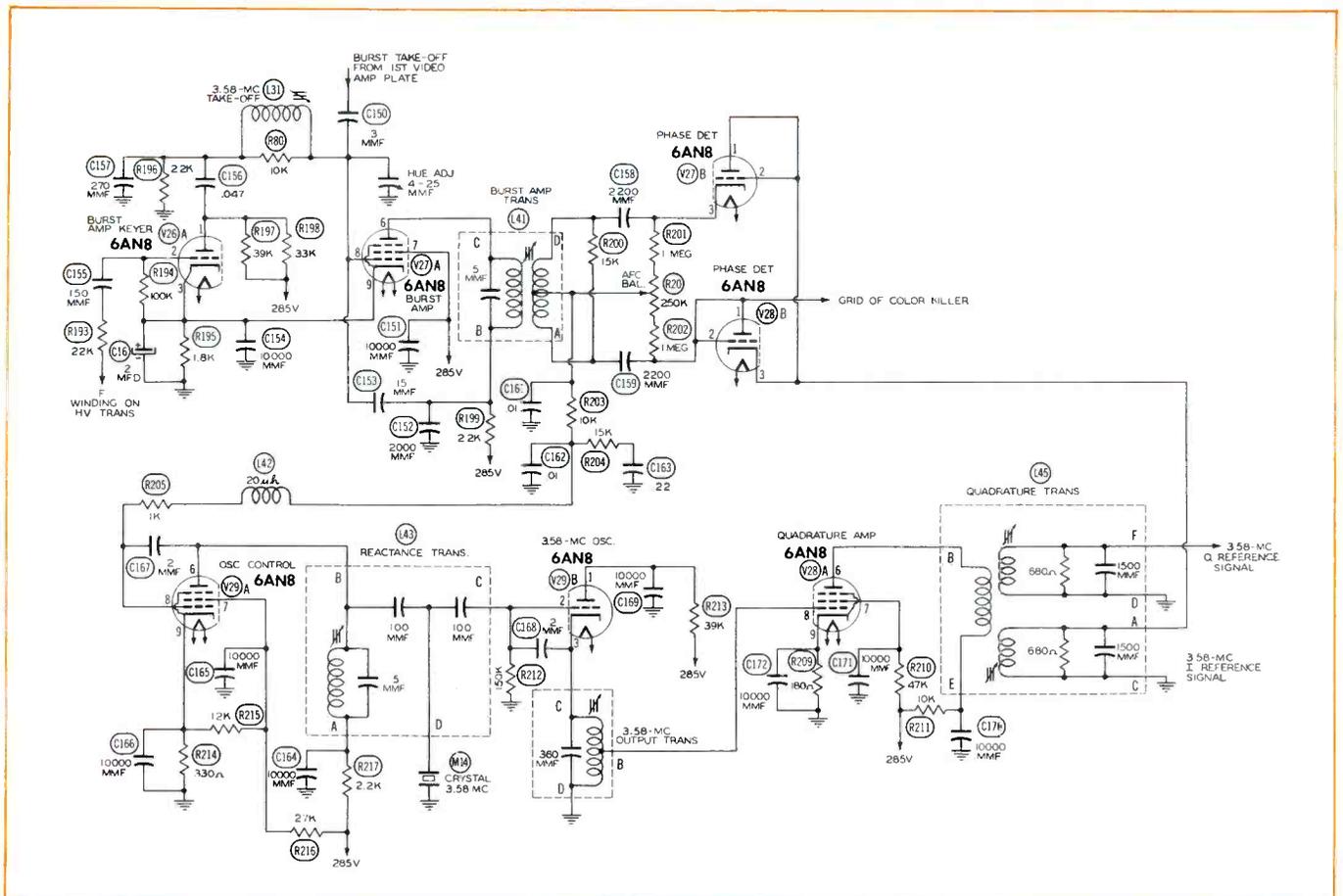


Fig. 12-22. Color-Sync Circuit Employed in RCA Victor Model CT-100 Color Receiver.

oscillator signal is not of the correct phase and frequency, a DC correction voltage will be developed by the phase detectors. This correction voltage is applied to the grid of the control stage which will then add more or less capacitive reactance to the grid circuit of the oscillator. The frequency and phase of the oscillator are closely controlled in this manner.

When the reference signal begins to lag behind the burst signal, the following events occur. Phase detector V28B conducts more than V27B. The negative DC correction voltage which is developed is added to the bias of the control stage. The gain of the control tube is reduced, and the amount of capacitance in the grid circuit of the oscillator is effectively decreased. The frequency and phase of the oscillator will tend to advance until the oscillator is in step with the color-burst signal.

If the reference signal begins to lead the burst signal, a positive correction voltage is developed and opposite events occur. For a more detailed discussion concerning the operation of the color-sync section, refer to Part VI of the Color TV Training Series in the November 1954 issue of the PF REPORTER.

If anything should happen in the color-sync circuit to interrupt or change the value of the DC correction voltage, the reference signal would be caused to change and would be thrown out of step with the incoming burst signal. When color synchronization is lost, the cause of the trouble will be located in some circuit ahead of the 3.58-mc oscillator.

If the pattern on the screen appears like that shown in Fig. E1 of the Color Plate and if the color-sync circuit under consideration is of the type shown in Fig. 12-22, the first thing to check is the control tube V29A. This is the only tube that can cause loss of color synchronization in this receiver. If the burst amplifier or either of the phase detectors were inoperative, the color killer would be allowed to conduct, in which case the bandpass amplifier would be biased to cutoff. The chrominance signal would be absent at the color demodulators, and the condition of no color would exist.

In a receiver which does not employ a color killer, it would be necessary to check the tubes in the burst amplifier and phase detector because color synchronization would be lost if one of these tubes were inoperative.

If replacement of tubes does not cure the trouble, a check of the circuit is in order. When checking the circuit, the best place to begin is in the oscillator-control stage. By making a voltage check, the technician can determine whether the operating voltages in this stage are correct or not. With abnormal plate or screen voltages at the control tube, the oscillator will drop out of synchronization.

If the plate and screen voltages are found to be normal, the next place to check is at the control grid of the oscillator-control tube. The voltage at this point should be approximately one volt positive. With a defective component in the circuit ahead of this point, the voltage at the control grid will be affected. For instance, if capacitor C162 were to develop a short to ground, the voltage on the control grid would go to zero and loss of color synchronization would result.

With capacitor C158 open or capacitor C159 shorted, the voltage at the grid of the control tube would drop below 15 volts negative. This amount of negative voltage places the control stage below cutoff. The control tube no longer governs the operation of the oscillator; therefore, the reference signal drops out of synchronization with the

burst signal. If resistor R201 becomes open, the same thing will happen. The grid voltage will drop to approximately 40 volts negative.

A voltage check at the phase detectors can be very helpful. For instance, if capacitor C158 should become open, the voltage at the cathode of phase detector V27B would drop far below normal. Under normal operation, the voltage at the cathode of V27B and the voltage at the plate of V28B are equal in amplitude but of opposite polarity. If these voltages are found to be unbalanced, the cause of the trouble will often be found in the circuit of the phase detector.

If the operating voltages at the control stage are found to be normal, the tuning of coil L43 in the plate circuit of the control stage should be checked. If this coil were misadjusted, color synchronization would be lost.

Troubles With Color Purity

Improper color purity is noticeable when there is color contamination in parts of a reproduced monochrome picture or test pattern. It is also noticeable when the colors in various portions of a color picture are not pure. It signifies that the beams are not striking the correct sets of phosphor dots on the portions of the screen where the contamination is present. In order to obtain correct purity, the beam from the red gun must be striking only the phosphor dots which emit red light, the beam from the blue gun must strike only the phosphor dots which emit blue light, and the beam from the green gun must strike only the phosphor dots which emit green light.

Whenever color contamination is present, the adjustments of the purity devices associated with the picture tube should first be checked. The procedure for making these adjustments was outlined in previous sections of this Color TV Training Series. This adjustment procedure concerning the electrostatic picture tube appeared in the April 1955 issue, and the procedure concerning the electromagnetic picture tube appeared in the May 1955 issue. If adjustment of the purity devices does not correct the contamination, the purity circuits and the devices will need to be checked for defects.

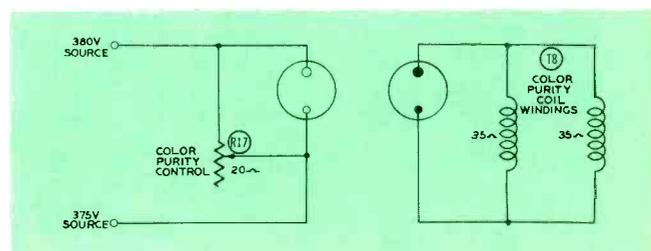


Fig. 12-23 Color-Purity Coil and Control Circuit Used in RCA Victor Model CT-100 Color Receiver.

For the electrostatic type of picture tube, there are three devices which affect purity. These are the purity coil, the deflection yoke, and the field-neutralizing coil. If any one of these units should become defective, the achievement of satisfactory purity would not be possible.

The circuit of the purity coil and its control is shown in Fig. 12-23. If purity adjustment is unsuccessful, first check the voltages at the input of this circuit. If they are normal, check the purity control and the purity coil. Direct replacement of the purity coil is the surest method

* * Please turn to page 41 * *

REFERENCE PATTERNS FOR TROUBLE SHOOTING

COLOR TV TRAINING SERIES



Fig. E1. Color-Bar Pattern Indicating Loss of Color Synchronization.



Fig. E2. Pattern Produced When Purity Coil Is Open.

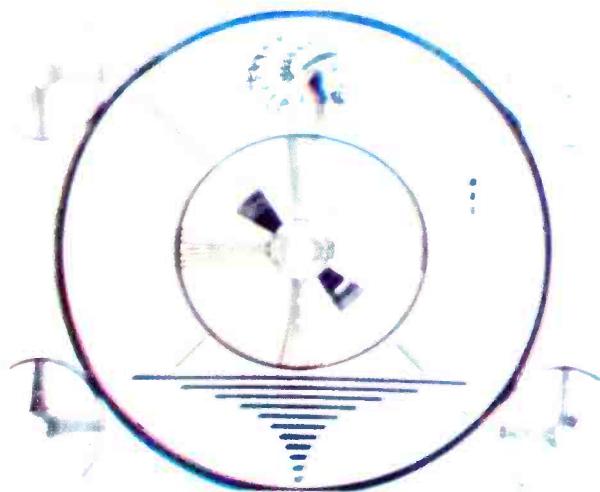


Fig. E3. Test Pattern Indicating Poor Vertical Dynamic Convergence.

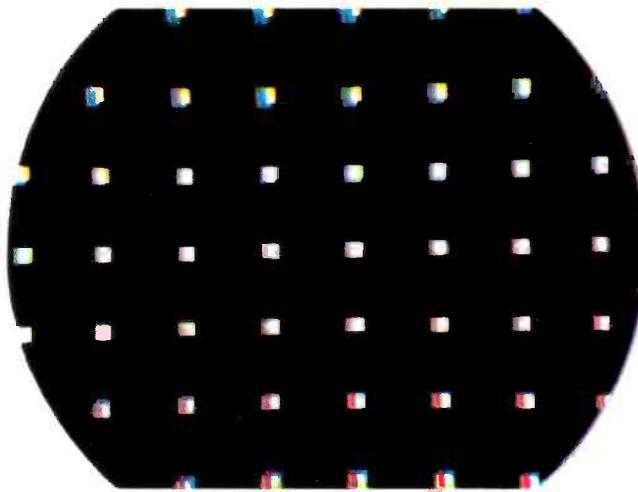


Fig. E4. White-Dot Pattern Indicating Poor Vertical Dynamic Convergence.

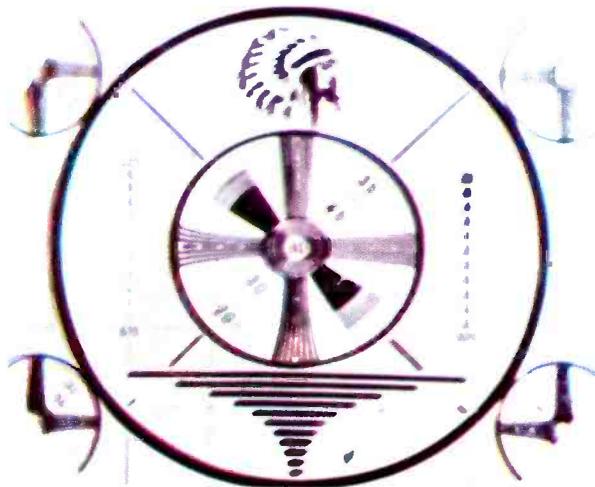


Fig. E5. Test Pattern Indicating Poor Horizontal Dynamic Convergence.


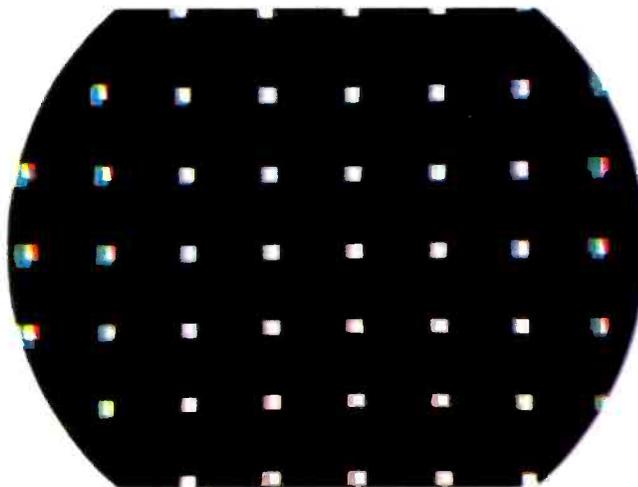


Fig. E6. White-Dot Pattern Indicating Poor Horizontal Dynamic Convergence.

P. R. MALLORY & CO. INC.
MALLORY
APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO. INC.
MALLORY
APPROVED PRECISION PRODUCTS

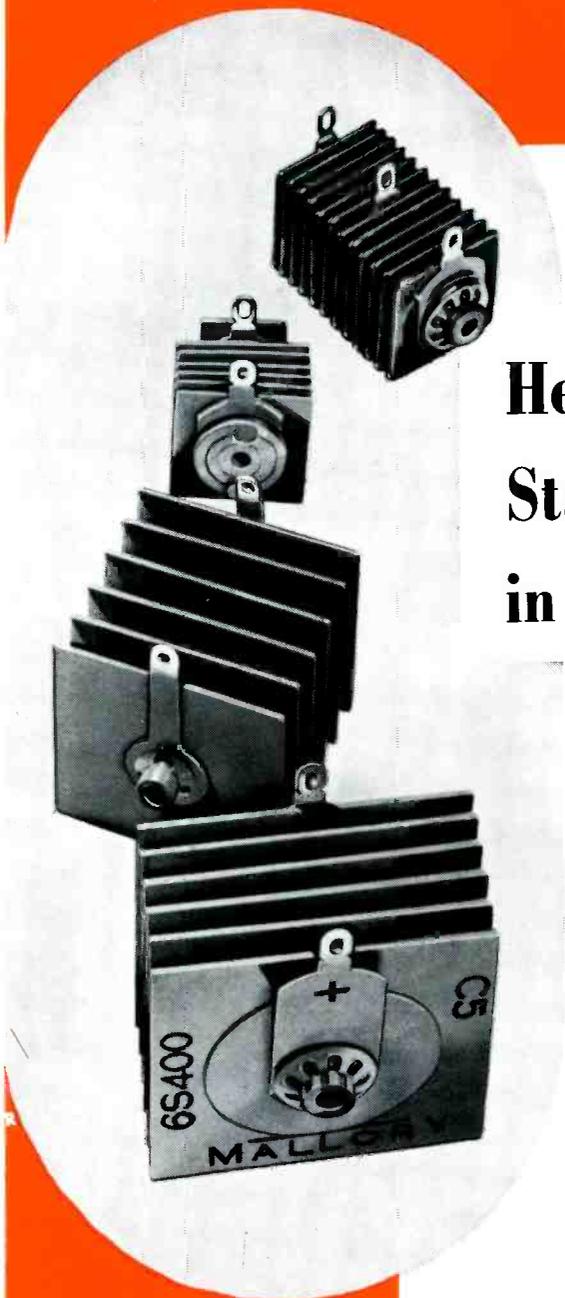P. R. MALLORY & CO. INC.
MALLORY
APPROVED PRECISION PRODUCTS



Here's the **NEW** Standard of Performance in Selenium Rectifiers

A completely new line of Mallory selenium rectifier stacks now gives you *performance that equals or surpasses* original equipment specifications to a degree of uniformity never before attained.

The secret is new Mallory designs and manufacturing methods developed to produce superior characteristics... and to maintain these standards on *every* stack.

The new Mallory stacks are noted for unusually long service. Exceptionally low forward voltage drop gives them high efficiency throughout their long, dependable life.

Make sure you use these new rectifiers on all your replacement jobs. You can connect them and forget them... with the assurance that *every* stack will turn in long, reliable service.

A complete selection of values, all conservatively rated, is available to fit every possible application. Ask your Mallory distributor to send you the stock you need.

P. R. MALLORY & CO. INC.
MALLORY
APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO. INC.
MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
RECTIFIERS • POWER SUPPLIES • FILTERS • MERCURY BATTERIES
APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

Shop Talk

MILTON S. KIVER

President, Television Communications Institute

Test Equipment for Rapid Checks

Parts replacement occupies a considerable amount of the service technician's time. It is not unusual to have to unsolder and resolder a half-dozen components during the course of any ordinary service job. Since the service technician is always working against the clock whether he is in business for himself or is an employee of someone else, it is very clear that anything which will reduce the amount of time used in finding and changing defective components will definitely be advantageous.

A further reason for paying attention to the problem of reducing service time stems from the increased use of printed circuits which, as anyone who has worked with them knows, are set up in such a way that changing the parts is not an easy task. Considerable care must be exercised not only to see that adjacent portions of the circuitry are undisturbed but also to see that no damage will come to the wiring, components, or baseboard of the section being serviced. You want to be absolutely certain that the part is truly defective when you decide to change a component.

There have appeared in recent months a number of test instruments which tend to ease the service technician's job because they enable him to check the condition of a component while it is still wired into the circuit. Among the most important of these instruments are those which reveal whether a capacitor is open, shorted, leaky, or intermittent. Other instruments enable the technician to check the condition of horizontal-output transformers, yokes, and other inductive components such as width and linearity controls. For the latter, some unsoldering of leads may be required although a substantial amount of time is still saved by this method when compared to the substitution method.

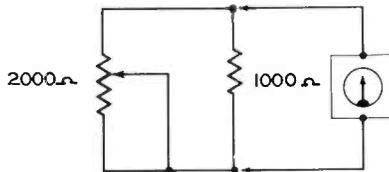


Fig. 1. The Measured Value of This Parallel Combination Depends Upon the Setting of the Potentiometer.

The common resistor is an other item in plentiful supply in every receiver. Ordinarily, resistor values can be checked directly without unsoldering of leads. If two resistors are connected in parallel, as shown in Fig. 1, the technician can still check them by comparing their measured value with their computed value. The total value of two resistors in parallel may be computed by using the equation:

$$R \text{ (resultant)} = \frac{R_1 \times R_2}{R_1 + R_2}$$

If the arm of the variable resistor in Fig. 1 is set at the bottom of the control so that both resistors will be fully in the circuit, the values of 1000 and 2000 ohms can be substituted in the foregoing equation.

$$R = \frac{1000 \times 2000}{3000} = 667 \text{ ohms.}$$

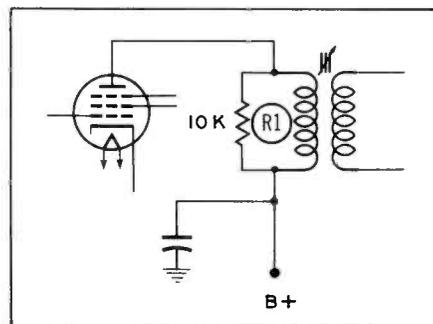


Fig. 2. Typical Circuit in Which Resistor Must Be Unsoldered Before Being Measured.

When the arm of the variable resistor has been moved to the top, the value of the parallel combination is zero ohms.

If you find that these computations are too difficult to do, then you would have to unsolder one end of one of the resistors and measure each unit individually. If you find the computations easy to do, then you do not need to go to the trouble of unsoldering a component to find out whether it is defective or not.

If you meet a condition such as that shown in the drawing in Fig. 2 and feel that the resistor may have changed value, then you would need to do some unsoldering; but it need not involve the resistor. The physical layout of the circuit may be such that it is easier to unsolder one end of the coil. A moment's inspection, while comparing the schematic diagram with the receiver, may save you a little time.

This preoccupation with time-saving methods, while of interest to all, is probably pursued with greatest vigor by the larger servicing outfits. This writer has had occasion to sit in on many such conferences at Central Television Service, Chicago, an organization that employs nearly a hundred men. Some of the time-saving devices and procedures instituted by this company would not be suitable for smaller firms, but one recently developed device designed and manufactured by the B & K Manufacturing Company is currently being made available to other service firms.

The need for this instrument, a simplified tube checker, arose because of two problems that Central encountered. One stemmed from the length of time it took to check tubes in the home on a conventional tube

* * Please turn to page 35 * *

**MR. SERVICE DEALER:
you're ridin' high, wide
an' handsome**

in this **RAYTHEON**

LIFE ad

September 12th



**It takes a heap of
Know-How to ride herd
on 36,000,000 TV Sets**

In only a few short years, America has created a new guild of skilled craftsmen... the electronic technicians who service the nation's 36 million television receivers. It's a big job—one that calls for a high order of technical know-how and a substantial investment in training and equipment.

Your neighborhood radio and television serviceman takes pride in his ability to serve you with skill and integrity.

He takes special pride when he has qualified as a member of the select group of Raytheon Bonded Electronic Technicians. As such he displays the Raytheon Bonded Seal and adheres to this Code of Ethics:

1. Guarantee all radio and television repair work for 90 days.
2. Use only parts of recognized quality.
3. Charge not over established prices for parts.
4. Test customer's tubes as accurately as possible.
5. Keep labor charges at a reasonable level.
6. Perform only such work as is necessary.
7. Maintain proper equipment for good repair work.
8. Maintain the highest quality service.

He has the ability and equipment to solve your TV service problems, whatever the make or model of your sets. His work is made or noted through one of America's largest insurance companies and his standing as a Raytheon Bonded Electronic Technician is your guarantee of satisfaction.



LOOK FOR THIS SEAL
It's the symbol of Satisfactory Service

RAYTHEON MANUFACTURING COMPANY, Receiving and Cathode Ray Tube Operations
NEWTON CHICAGO ATLANTA LOS ANGELES



Excellence in Electronics

MAKE THE MOST OF IT!

Once again, Raytheon is telling your story, this time to the 26,450,000 readers of LIFE Magazine (September 12 issue) and, once again, you have a golden opportunity to cash in on this great, national promotion. All you need to do is tie in with this dramatic, colorful, full page advertisement. Use Raytheon decals, blow-ups of the ad, displays and local advertising to show customers you are the capable service dealer we're talking about. You'll increase your volume and profit and boost your neighborhood prestige to an all-time high.

Your Raytheon Tube Distributor will be happy to help you plan a tie-in campaign that will prove most effective. Call him today.



**HOT OFF THE PRESS!
The Sensational New RAYTHEON
TRANSISTOR APPLICATIONS BOOK**

116 pages — over 50 practical applications — complete how-to-do-it instructions. Available from your Raytheon Tube Distributor or send 50¢ to Department P7, Raytheon Manufacturing Company, Newton 58, Massachusetts.

DIAGRAMS FOR SETTING UP TEST EQUIPMENT

INTRODUCTION

The following diagrams are designed to show methods of application of test instruments that the technician can use in servicing radio and TV receivers. Reading matter has been kept to a smaller amount than usual, and an attempt has been made to convey as much information as possible through the use of diagrams.

A complete alignment procedure for a TV receiver has been selected as an operation which brings into use several of the more important test instruments that the service technician may use in a single project. These instruments include the sweep signal generator, RF marker generator, oscilloscope, and VTVM.

Obtaining a Response Curve

Diagram No. 1

*NOTE 1. Some form of detector is almost always used when a response curve is being obtained, although a response indication can be obtained without a detector if the sweep frequencies applied do not go above the response characteristics of the vertical amplifier of the oscilloscope. Typical receiver points which give detection are the mixer grid of the tuner, the video detector, the sound-limiter grids, and the ratio detectors or discriminators. If a detector that is external to the receiver circuits is used, it is usually in the form of an RF detector probe.

*NOTE 2. Oscilloscope controls are set to the horizontal-input position.

Marking a Response Curve

Diagram No. 2

Sound IF Detector Alignment Using the VTVM and the RF Generator

Diagram Nos. 3 and 4

*NOTE. A blocking capacitor should be used if the generator is connected at a point where considerable DC voltage is present or where any current drain would upset the circuit operation. The capacitor also serves to protect the generator. The termination network found at the output of most generators has characteristics of low impedance and low wattage. If this network is connected directly to a voltage source, it may draw enough current to damage the low-wattage resistors.

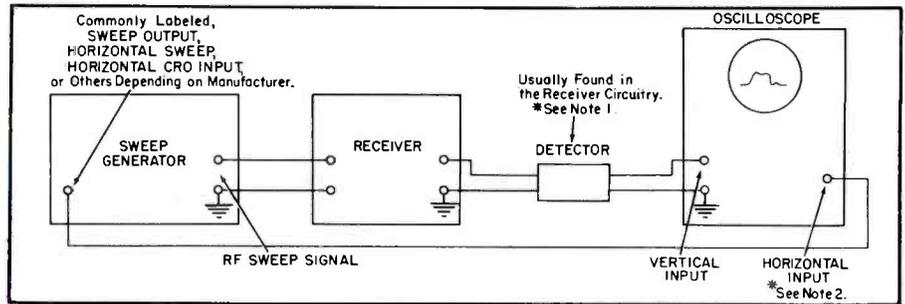


Diagram No. 1. Minimum Equipment Necessary to Obtain a Response Curve.

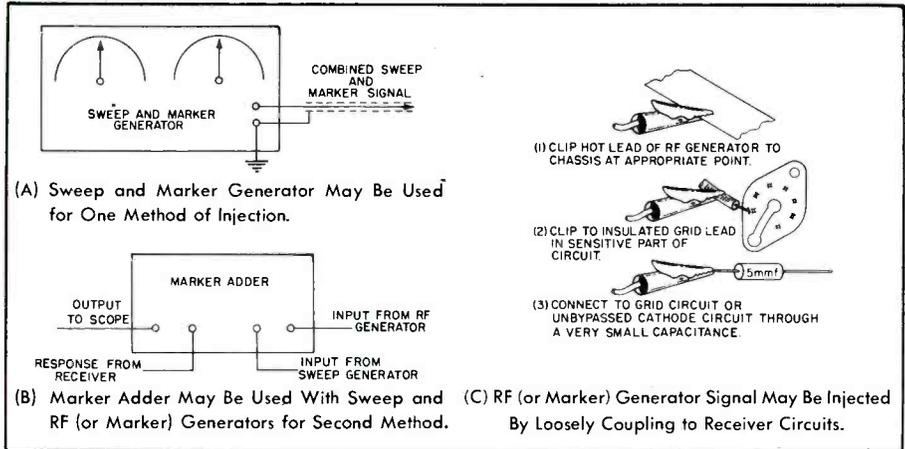


Diagram No. 2. Marker-Injection Methods.

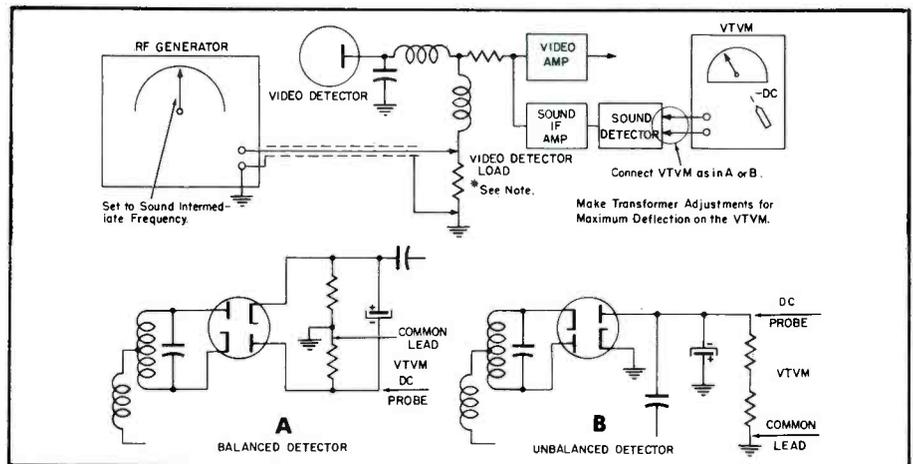


Diagram No. 3. Equipment Setup Used for Adjustment of Sound IF Transformers and of Primary of Sound-Detector Transformer.


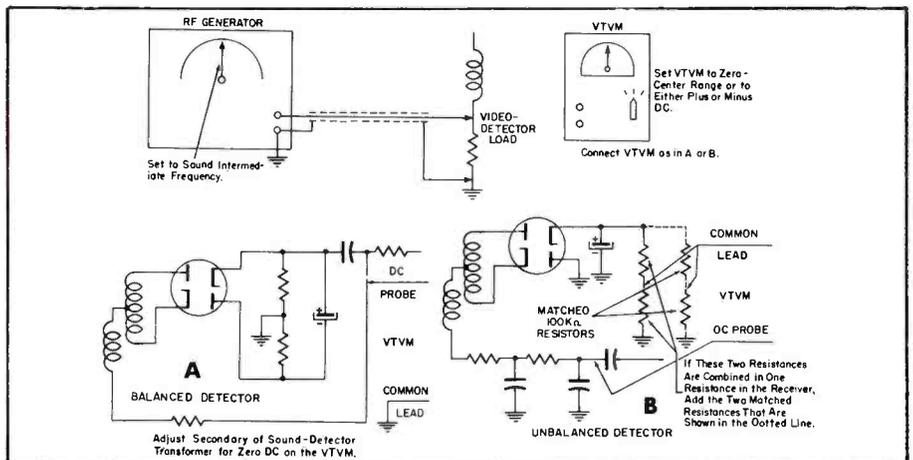


Diagram No. 4. Equipment Setup for Adjustment of the Secondary of Sound-Detector Transformer.

RCA announces a NEW line of...

"UNIVERSAL"-TYPE SELENIUM RECTIFIERS

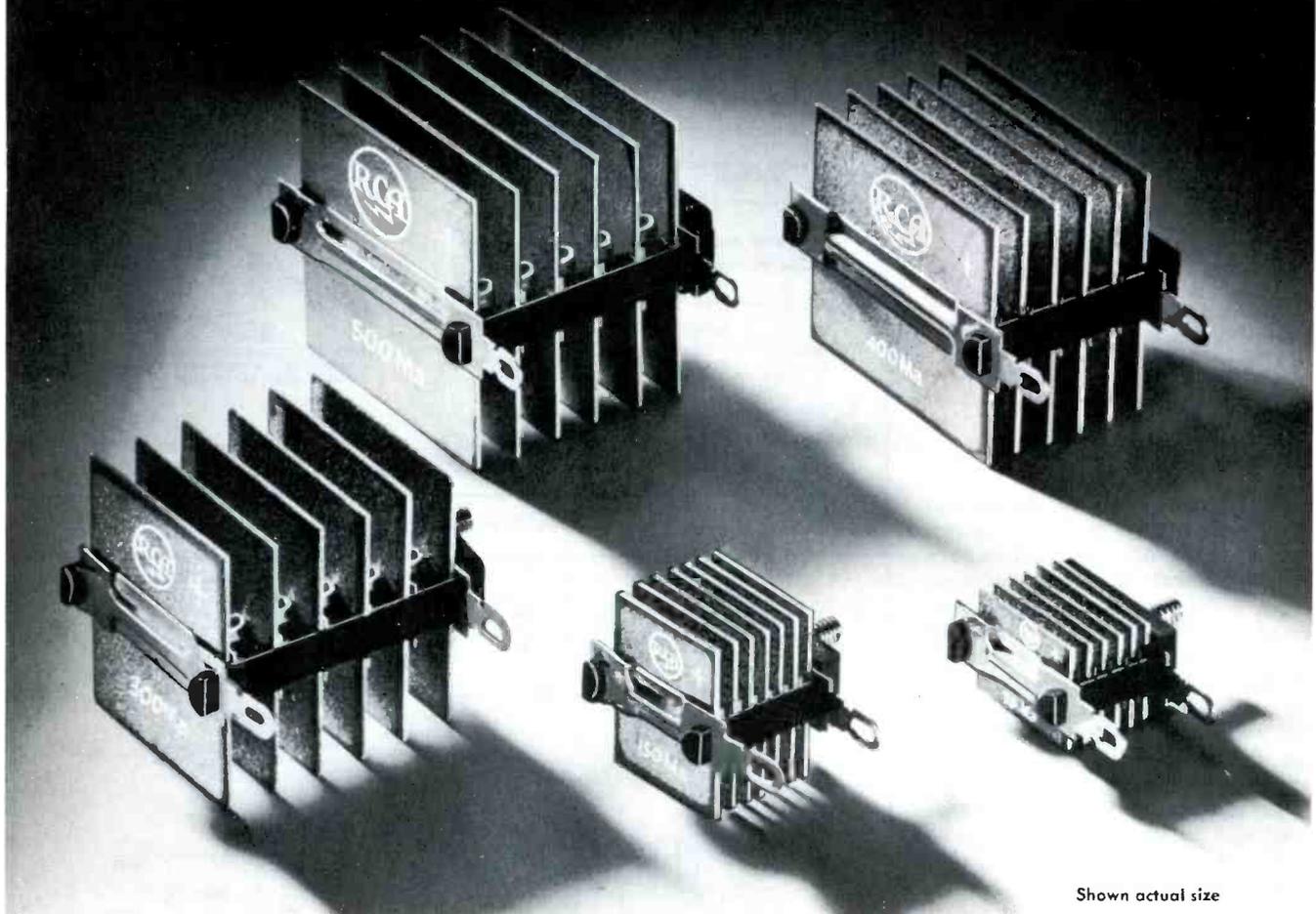

Shown actual size

**Just 5 types meet virtually all replacement requirements
... in TV, radio receivers, and phonographs!**



Look at the "wide-open" design of RCA Selenium Rectifiers. Benefits: Maximum cooling, dependable performance.

Again, RCA sets the pace—with an *all-new* line of "Universal"-type selenium rectifiers.

NEW—Improved heat dissipation . . . "Wide-open" design permits maximum air circulation.

NEW—Smaller size . . . For any given current, they are smaller than other types (installation is a "snap").

NEW—Versatility . . . Only five types needed to cover the range from 50 to 500 milliamperes.

Always replace with an RCA Selenium Rectifier — for *consistently* good performance, faster customer service! Order RCA All-New Selenium Rectifiers from your RCA Distributor TODAY. Stock up on new, RCA "Universal"-type Selenium Rectifiers, — competitively priced for profitable, fast turnover.

5 Types Cover Your Replacements			
RCA Type Number	Max. Output Current	Max. Input Volts	Suggested List Price
200 G1	75 MA	130V	\$1.85
201 G1	150 MA	130V	2.25
202 G1	300 MA	130V	3.30
203 G1	400 MA	130V	4.25
204 G1	500 MA	130V	4.40



RADIO CORPORATION of AMERICA
ELECTRONIC COMPONENTS
HARRISON, N. J.

Sound IF and Detector Alignment Using an Oscilloscope and FM Generator

Diagram Nos. 5 and 6

Video IF Alignment

Diagram No. 7

*NOTE 1. It is desirable to disable the oscillator section of the mixer stage so that there will be fewer confusing indications on the VTVM. A good way of doing this is to substitute another mixer-oscillator tube which has had the plate pin of the oscillator section removed.

*NOTE 2. Trap adjustments are made for minimum deflection on the VTVM at the trap frequency. The other adjustments are normally made to obtain maximum deflection at the frequency indicated for each adjustment.

Video IF Response Check

Diagram No. 8

*NOTE 1. A bias supply is usually connected at some point on the AGC line. This is for the purpose of maintaining the gain of the video IF stages as nearly as possible to that obtained when a station signal is being received. The value of bias and the point for application may vary somewhat and are usually given in the alignment instructions.

*NOTE 2. Connect leads from the generator in the same manner as that shown in Diagram No. 7. Moreover, the oscillator in the tuner should be disabled in the manner described in Note 1 for Diagram No. 7.

Tuner Alignment

Diagram No. 9

*NOTE 1. Many generators do not include a termination network or matching pad at the end of the output cable. In some cases, such a termination is advisable in order to eliminate distortion caused by standing waves on the output cable. The matching pad is designed to present an input impedance which matches the characteristic impedance of the output cable and to present an output impedance which matches the input impedance of the receiver.

*NOTE 2. The looker point is one of the points previously mentioned as affording a detector action; consequently, no detector is needed at the oscilloscope. Only one or two stages are normally found between the antenna and the looker point; therefore, maximum output from the generator and maximum gain of the oscilloscope are usually necessary to obtain a usable response curve. For the same reason, bias is seldom applied to the stages during alignment because the gain would be reduced as a result of such application.

PAUL C. SMITH

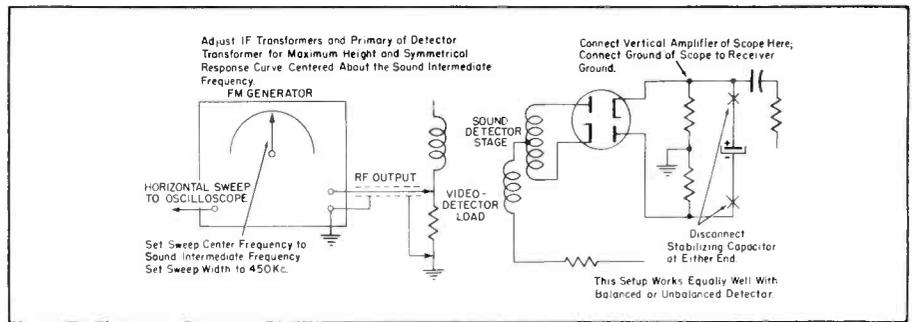


Diagram No. 5. Connections to Be Made for Adjustment of Sound IF Transformers and of Primary of Detector Transformer.

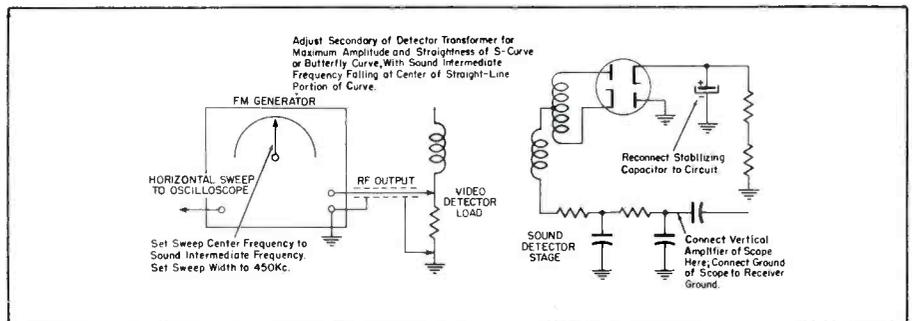


Diagram No. 6. Connections to Be Made for Adjustment of Secondary of Detector Transformer.

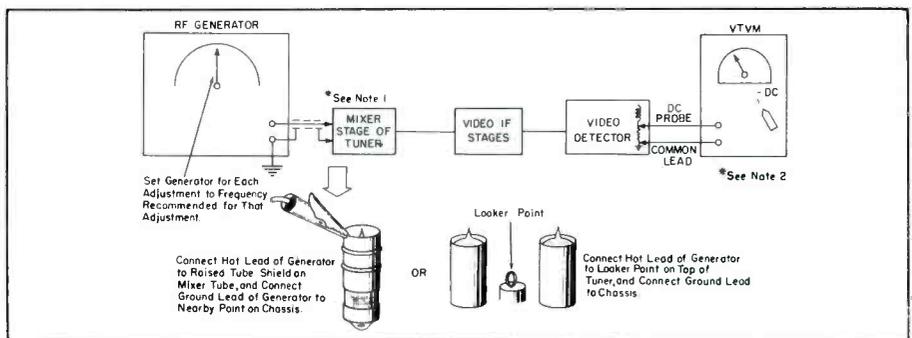


Diagram No. 7. Equipment Setup for Video IF Alignment Using RF Generator and VTVM.

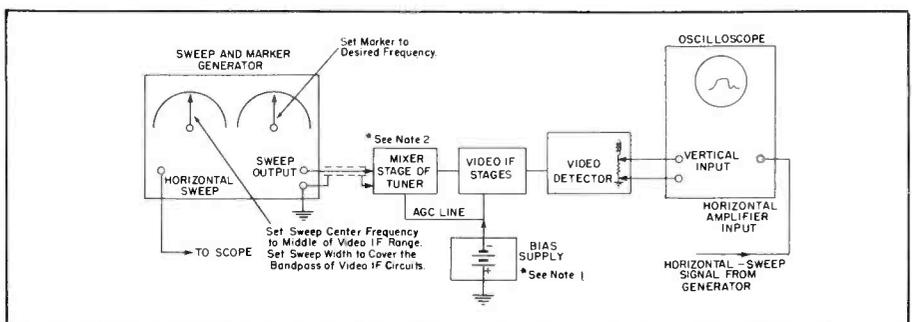


Diagram No. 8. Equipment Setup for Video IF Response Check.

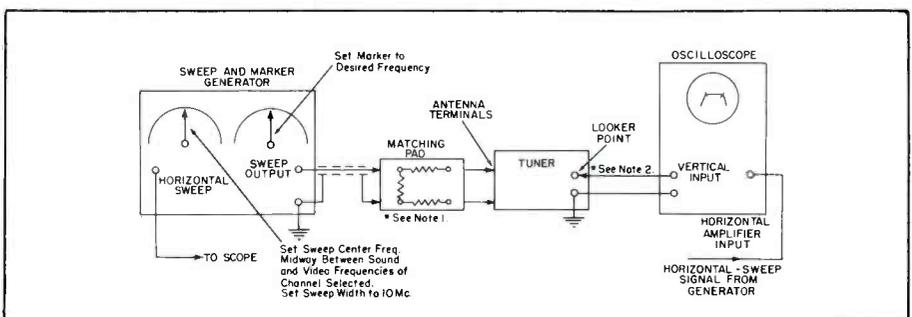


Diagram No. 9. Equipment Setup for Tuner Response Check and Alignment.

**How to
hand
yourself
more
business**

Whenever you replace a tube, it's smart to hand the lady the CBS carton . . . and yourself more business.

It's smart because CBS tubes are advertised to *women* in Life, Good Housekeeping and on Arthur Godfrey's Talent Scouts.

And it's good business for you because *women* have greater confidence in CBS tubes . . . the tubes with the Good Housekeeping Guaranty Seal.

There are no better tubes made than CBS tubes.




CBS-HYTRON, Danvers, Massachusetts

A DIVISION OF COLUMBIA BROADCASTING SYSTEM, INC.



In the Interest of . . . Quicker Servicing

by Calvin C. Young, Jr.

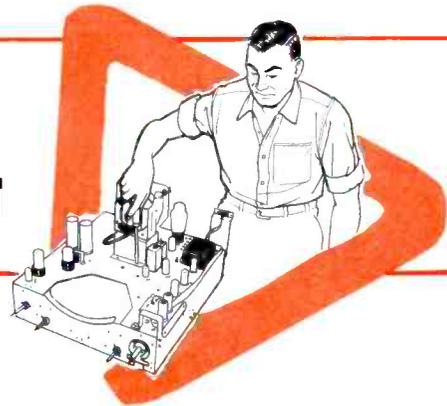

LINE-VOLTAGE VARIATIONS

Television receivers are designed to operate with power-line voltages of approximately 115 to 117 volts AC. These units will operate, however, at 105 to 125 volts AC; but certain troubles may occur at these extreme voltages. At 105 volts, a set may operate with reduced efficiency; and at 125 volts, the tubes and other components in a set may have a tendency to fail more rapidly.

Low line voltages are most often encountered in the city where the power lines are heavily loaded, and high line voltages are most often encountered in certain rural areas where the power lines are not heavily loaded. There are also localities in which the line voltage may be satisfactory during the day but may fall to a low value at night. In some extreme cases, the voltage may even vary from a value that is too high to one that is too low during a 24-hour period.



Fig. 2. Acme Electric Model T-8394M Manual Voltage Adjustor.

To combat these various line-voltage conditions, it would obviously be desirable to have a device which when installed between the power line and the receiver would maintain

a constant 117-volt AC output regardless of the input voltage. Such units or devices are available; but, unfortunately, they are very expensive. For monetary or practical reasons, therefore, a unit which may be manually adjusted to compensate for low or high voltages is desirable. These units should provide some means for the user to check the output voltage so that the correct voltage can be maintained.

Shown in Figs. 1 and 2 are two of the many different makes of adjustable line-voltage transformers. The unit shown in Fig. 1 is representative of a type that uses two neon bulbs to reveal the approximate value of the output voltage. The unit which is pictured is the Regency Model VB-1 voltage booster made by I.D.E.A., Inc. The neon bulbs can reveal three conditions:

1. Output voltage too low — neither bulb is lit.

* * Please turn to page 56 * *

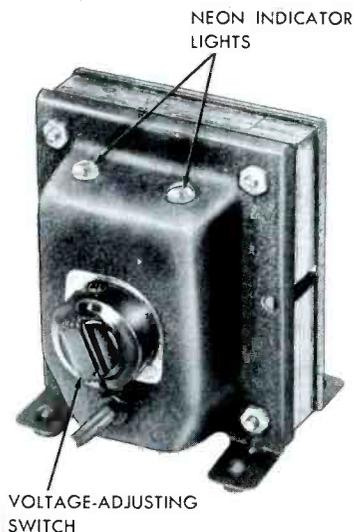


Fig. 1. Regency Model VB-1 Voltage Booster.

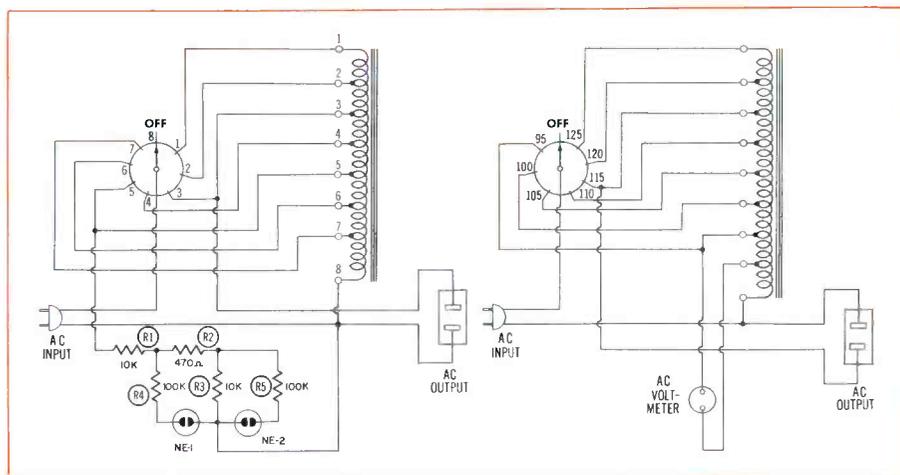


Fig. 3. Schematic Diagrams of Two Typical Voltage-Booster Transformers.

this TV serviceman uses

STANCOR

EXACT REPLACEMENT TRANSFORMERS



There are now 59 Stancor exact replacement flybacks covering all major TV set manufacturers and many private label brands.

The latest units include 6 new Zenith replacements that give you

**71% ZENITH
EXACT REPLACEMENT
FLYBACK COVERAGE**

and 6 new General Electric replacements that give you

**79% G. E.
EXACT REPLACEMENT
FLYBACK COVERAGE**

You too can take life easy and have time to spare when you use Stancor exact replacements. No changing of circuits, no drilling of holes . . . you just take out the defective unit and replace it with a Stancor Transformer that exactly duplicates the original.

FREE The New Stancor TV Transformer Replacement Guide, listing accurate replacement data on almost 8500 TV models and chassis of 116 manufacturers. If you haven't received your copy see your Stancor distributor or write Chicago Standard Transformer Corporation.

CHICAGO STANDARD TRANSFORMER CORPORATION


3594 ELSTON AVENUE
CHICAGO 18, ILLINOIS

Export Sales:

Roburn Agencies, Inc.
431 Greenwich Street
New York 13, N. Y.



this is
going to
make your
rotor sales

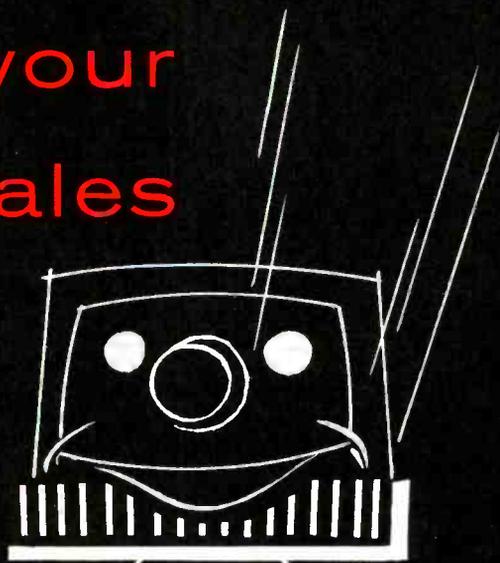

jump up

BIGGEST

n in Our History

work for you

rotors

featuring

C·D·R

automatic

ROTORS

An outstanding group of rotors . . . three proven and tested models . . . **ALL 40% SHARPER TUNING** than ANY other automatic rotor. Handsome cabinet . . . dependable performance . . . proven and tested by thousands and thousands of satisfied users.

to
millions of
TV viewers
every week

We are going to make this the **BIGGEST** rotor year you've ever had! The **CDR ROTOR** line is **COMPLETE** in every detail . . . featuring **SEVEN MODELS** . . . **A TYPE FOR EVERY NEED!** And backing up this is the **BIGGEST** and most extensive consumer campaign in all our history! Millions of TV viewers will see the **CDR rotor** announcements on TV, preselling them for you. And a complete promotional kit of dealer aids to help you sell and feature **CDR ROTORS!** Plan now . . . for the **BIGGEST CDR ROTOR** year ever!


and

BIGG

TV Spot Campaign
is going to v

pre-selling...

C·D·R·R·C
TV antenna

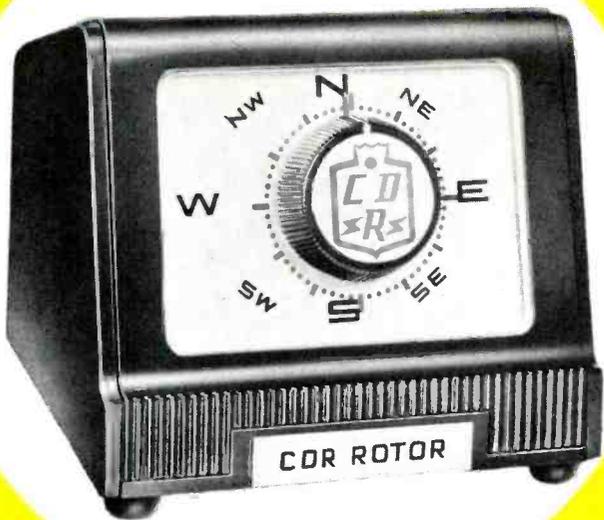

AR-1

AR-2



fea

AR-22



CORNELL-DUBILIER
SOUTH PLAINFIELD, N.J.



THE RADIART CORP.
CLEVELAND 13, OHIO

the complete line . . .

a model for every need

C.D.R. Rotors



TR-4 the heavy duty rotor complete with handsome modern cabinet with METER control dial, uses 4 wire cable.



TR-11 same as TR-12 without thrust bearing.



TR-2 the heavy duty rotor with plastic cabinet featuring "compass control" illuminated perfect pattern dial, uses 8 wire cable.



TR-12 a special combination value consisting of complete rotor, including thrust bearing. Handsome new modern cabinet with meter control dial, uses 4 wire cable.



CORNELL-DUBILIER
SOUTH PLAINFIELD, N. J.




THE RADIART CORP.
CLEVELAND 13, OHIO

Notes On

TEST EQUIPMENT

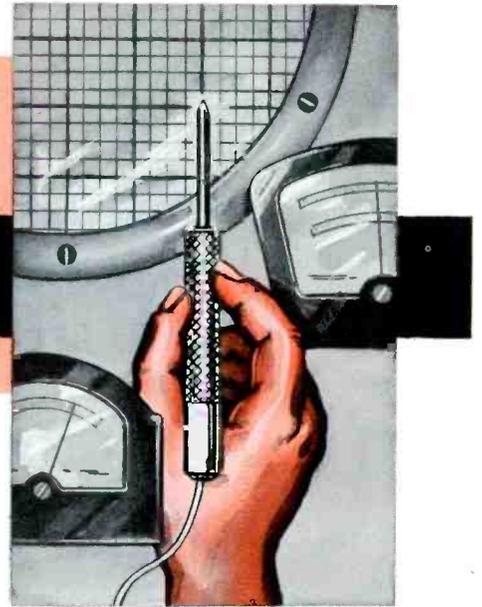Presenting Information on Application, Maintenance, and Adaptability of Service Instruments



by Paul C. Smith

HYCON MODEL 617 OSCILLOSCOPE

Recently, we obtained a Hycon Model 617 oscilloscope. We have had occasion to use this instrument a number of times, and we would like to pass along to our readers some information which may be of interest.

One of the features that was first noticed was the relatively small size of this oscilloscope. When measured, it proved to be 8 1/2 inches wide, 11 inches high, and 10 3/4 inches deep. This small size is an advantage if bench space is at a premium. For a further saving of space, the case and handle are designed to permit stacking with other Hycon test instruments.

The oscilloscope is equipped with a 3RP1A cathode-ray tube. The face of the tube is fitted with a green filter to ensure maximum contrast of the trace. Horizontal and vertical lines are ruled on the filter so that it may also be used for calibration purposes.

An interesting method is used to illuminate the calibration graph. A small lamp has been mounted so that its light strikes the edge of the plastic filter disc. In this manner, only the ruled lines are illuminated. The lines have an orange-red hue which can be easily seen against the green background of the filter. The operator has full control of the degree of illumination by means of a front-panel knob. This knob also controls the operation of the ON-OFF switch of the oscilloscope when the knob is turned to its extreme counterclockwise position.

The sensitivity of the vertical amplifier is 10 millivolts rms per inch, and the vertical bandwidth is from 6 cycles to 4.5 megacycles per second plus or minus 1 db. The input impedance (less probe) is 1 megohm shunted by 30 micromicrofarads plus or minus 2 micromicrofarads. The sensitivity and high-frequency response of the vertical amplifier were checked and found to be well up to the manufacturer's specifications. The low-frequency response was beyond the reach of the signal sources at hand and was not checked.

The sensitivity of the horizontal amplifier is 75 millivolts rms per inch, and the horizontal bandwidth is 6 cycles to 500 kilocycles per second plus or minus 3 db. The input impedance of the horizontal amplifier is 1 megohm shunted by 35 micromicrofarads.

Sawtooth sweeps ranging from 15 cycles per second to 100 kilocycles per second are provided in four ranges. Two additional positions of the sweep-range switch furnish automatic sweep rates of 30 and 7,875 cycles per second. These are the sweep rates which the technician commonly uses for viewing the vertical- and horizontal-deflection waveforms in TV receivers.

A 60-cycle sinusoidal sweep is provided for use in alignment procedures or wherever such a sweep is desirable. The phase of the sinusoidal sweep may be varied by means of a phasing control on the oscilloscope panel. The phasing control acts as an amplitude control for the synchronizing signal when the horizontal-selector

switch is in either the INT (internal), LINE, or EXT SYNC position.

The oscilloscope trace is blanked during retrace time. When the internal sawtooth sweep is used, this oscilloscope provides for three types of synchronization: (1) INT (internal), during which a portion of the vertical-input signal is applied to the sync section; (2) LINE, during which a signal at the line frequency is applied to the sync section; and (3) EXT (external), during which an external signal can be applied to the sync section. The sync-amplifier section also functions as a sync limiter in order to prevent distortion

* * Please turn to page 69 * *



Fig. 1. Hycon Model 617 Oscilloscope.

5 Megacycles Bandwidth 10 Millivolts per Inch Sensitivity

in the NEW **PRECISION** **ES-550**

5 inch OSCILLOSCOPE



Engineered to cover a wide range
of modern electronic applications including
MONOCHROME and COLOR TELEVISION

The Model ES-550 is the **PRECISION** answer to laboratory, industrial and technician requirements for a rugged, dependable instrument for broad coverage of modern electronic oscillograph applications, INCLUDING COLOR TV. It provides a new and unparalleled standard of high sensitivity with single, overall wideband frequency response, plus other special performance features—at most sensible selling price.

- ★ **Push-Pull, Wide-Band Vertical Amplifier:** 10 MV/inch sensitivity. Input Characteristics: 2 Megohms, 22 mmd. Response: One DB from 10 cps. to 3.5 MC—3 DB at 5 MC. Attenuator: 3 step freq. compensated plus a continuously variable gain control in cathode follower circuit.
- ★ **Direct Reading, Peak to Peak Voltage Calibrator**
- ★ **Vertical Pattern Reversal Switching Facility**
- ★ **Push-Pull, Wide-Range Horizontal Amplifier:** 100 MV/inch sens. Input Characteristics: 2 Megohms, 25 mmd. Response: One DB from 10 cps. to 1.0 MC—3DB at 2 MC. Attenuator: 3 step, freq. compensated, plus a continuously variable gain control in cathode follower circuit.
- ★ **Linear, Multi-vibrator Sweep Circuit:** 10 cycles to 100 KC plus automatically synchronized 30 cycles and 7875 cycles sweep for TV sync-pulse analysis. Amplified sweep retrace blanking.
- ★ **Amplified Auto-Sync Circuit** active on all internal sweep ranges.
- ★ **Four Way Sync. Selector Switch** provides for Internal Negative, Internal Positive, External and Line Synchronization.
- ★ **3,000 Volt Intensifier Power Supply** assures utmost visibility of 'scope traces. Essential to high frequency and pulsed waveform analysis.
- ★ **"Z" Axis Input Terminal** for blanking, timing and marking.
- ★ **Built-in 60 cps Phasing and Blanking Controls** especially designed for more convenient FM, Monochrome and Color TV alignment and sync pulse analysis.
- ★ **All 4 Deflection Plates Available** with full beam centering facilities.
- ★ **Tube Complement:** 12AV7 "V" Cathode Follower-Amplifier, 6U8 "V" Amplifier-Phase Splitter, Two 6CL6 Push-Pull "V" Drivers, 6U8 "H" Cathode Follower-Amplifier, 6C4 "H" Phase Splitter, Dual 12BH7 Push-Pull "H" Driver, 12AV7 Linear-Sweep Multi-vibrator, 6BH6 Auto-Sync Amplifier, 12AU7 Sweep Retrace Blanking Amplifier, OA2 Voltage Regulator, 5V4 Low Voltage Rectifier, Two 1V2 High Voltage Rectifiers, 5CP1/A CR Tube.
- ★ **High Contrast, Filter Type, Removable Calibrating Screen**

Model ES-550 Deluxe: (Illustrated) In custom-styled, blue-grey ripple finished steel cabinet; 2 color satin-brushed aluminum panel and contrasting dark blue control knobs. Case Dimensions 8¼ x 14½ x 18½ inches. Complete with all tubes, including 5CP1/A CR tube. Comprehensive Instruction Manual. Net Price: \$215.00

Model ES-550 Standard: Electrically Identical to above but in standard black cabinet with black anodized aluminum panel. Case dimensions 8¼ x 14½ x 18½ inches. Complete as above. Net Price: \$210.00

MODEL SP-5 OSCILLOSCOPE TEST PROBE SET

for TV Signal Tracing, Alignment, Trouble-Shooting and Waveform Analysis

Engineered for use with all **PRECISION** Cathode Ray Oscillographs, Models ES-500, ES-500A, ES-520 and ES-550. Model SP-5: in vinyl carrying case, complete with four different detachable probe heads, universal coaxial cable, and operating instructions. Net Price: \$23.50



PRECISION Apparatus Company, Inc.

70-31 84th Street, Glendale 27, L. I., N. Y.

Export: 458 Broadway, New York 13, U. S. A. Cables: Morhanex
Canada: Atlas Radio Corp., Ltd., 50 Wingold Ave., Toronto 10

Audio-Facts

CARE and HANDLING of RECORDS

by ROBERT B. DUNHAM

reproduction and the extended useful life to be obtained from records as the result of using and handling them with care should surely point out the value of a discussion of the measures to be observed.


Most present-day records are 33 1/3-rpm and 45-rpm microgroove disks played with a 1-mil (.001-inch) stylus. Some manufacturers have discontinued production of 78-rpm (3-mil) records. Microgroove records are made of plastic and are termed unbreakable, but the small and delicate grooves in the playing surface can be damaged. Any small scratch, if it cuts into the wall of a groove, will be heard as a tick or pop from the loudspeaker when the record is played. The loudness will depend upon the depth and size of the scratch. Dirt, dust, grit, or any other foreign matter in the grooves can cause noise as the stylus moves through the contaminated grooves. Furthermore, such foreign matter can cause permanent damage when forced against the walls of the grooves by the stylus as the record is played. The damaged record cannot be repaired when the grooves become deformed by being gouged, scored, or imbedded with grit.

Handling

A record, when not in use on a turntable, should be kept in its protective container. Many types of containers are used with records. These include boxes, envelopes, and various types of jackets and sleeves. It is now becoming a common practice to use some form of lightweight paper or plastic envelope or sleeve on the record inside the heavier outer container for added protection.

The manner in which a record is removed from its protective cover

* * Please turn to page 65 * *

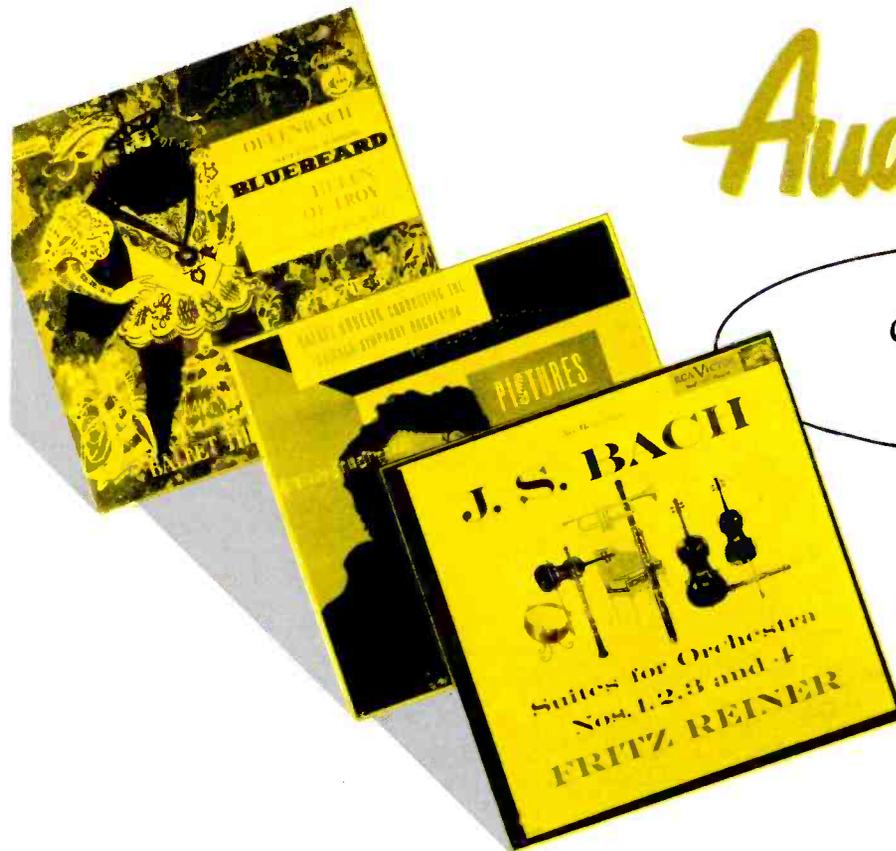

Good music for listening pleasure is the primary reason for having a high quality audio system in the home. This fact has been mentioned several times in these columns and is the reason why we usually use the term "home music system."

If we are to obtain high quality reproduction of music from an audio system, no weak links can be tolerated. Every unit or section of the system must do its part and do it well. The program material, obtained from records in most cases, must be considered as a critical part of the system because any faults or undesirable effects will be reproduced as well as the desired portions. In fact, the undesirable things are often more disturbing when heard from the loudspeaker of a high quality system which reproduces everything faithfully than they would be if reproduced by a mediocre outfit.


Anyone not acquainted with the effect produced by defective or damaged records is usually amazed to find just how severe the disturbance can be. An example is the recent experience of an owner when he turned on his audio system in his newly constructed home and operated a high quality music system for the first time. The writer was requested by the perplexed owner to come and find out what was wrong with the outfit. He said it seemed there were

many high-pitched sounds coming out of the loudspeakers. As was suspected, the disturbing sounds were found to be ticks and pops caused by damaged records.

The records were new but had been removed from their protective jackets and subjected to handling in the unprotected state. The interior of the house was not completely finished, and most surfaces were covered with a film of dust and grit from sawing and sanding. The records had been laid on bookshelves; consequently, they had received many small scratches and were more or less covered by the dust and grit. The resulting ticks and pops were very noticeable and disturbing when heard in the large rooms which were still empty.

The owner was relieved to learn that the system was operating satisfactorily but was surprised to find that the care and handling of records is so important and critical. He was convinced by the satisfactory reproduction obtained from clean and undamaged records.

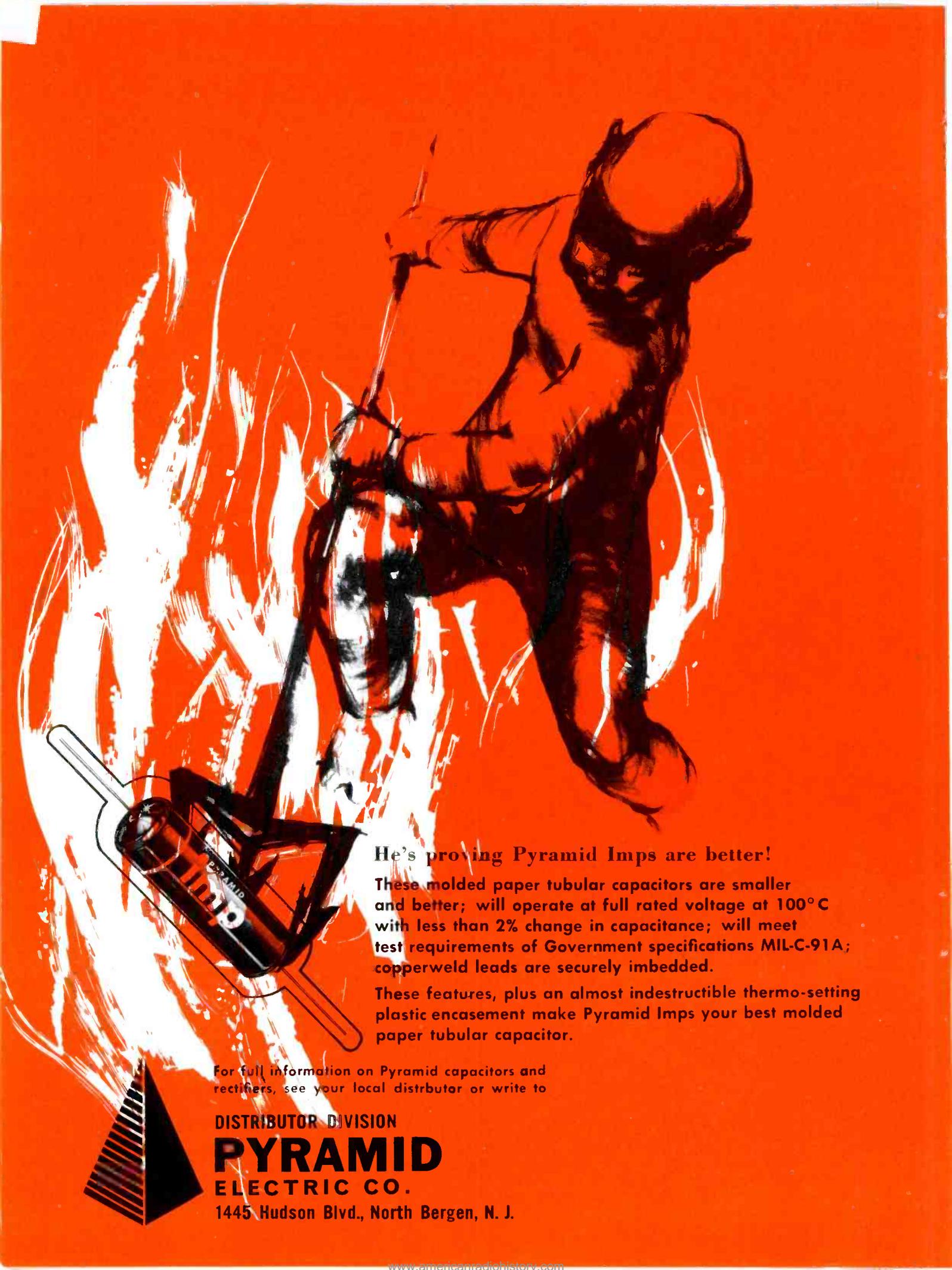Proper care and handling of records are so important that correct methods should be understood and used by everyone who uses or handles records. The satisfactory



He's proving Pyramid Imps are better!

These molded paper tubular capacitors are smaller and better; will operate at full rated voltage at 100°C with less than 2% change in capacitance; will meet test requirements of Government specifications MIL-C-91A; copperweld leads are securely imbedded.

These features, plus an almost indestructible thermo-setting plastic encasement make Pyramid Imps your best molded paper tubular capacitor.

For full information on Pyramid capacitors and rectifiers, see your local distributor or write to


DISTRIBUTOR DIVISION

PYRAMID
ELECTRIC CO.

1445 Hudson Blvd., North Bergen, N. J.

THE TRIODE PHASE DETECTOR

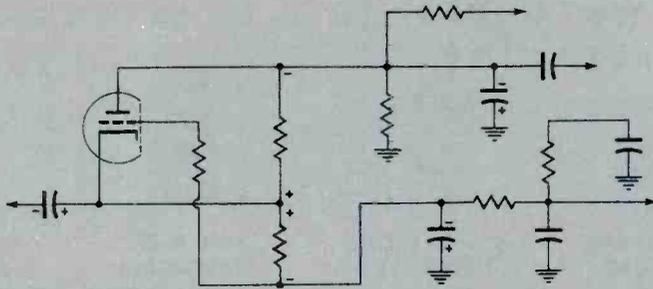Theory of Operation With Waveform Illustrations



by THOMAS A. LESH

The phase detector, one type of circuit used to supply horizontal AFC in television receivers, commonly employs a dual diode such as the 6AL5. Occasionally, the technician will find sets which have a modified circuit using a triode.

The function of both types of phase detectors is to compare two voltages — sync pulses from the incoming signal and a sawtooth voltage developed usually by integration of a pulse from the horizontal-output transformer of the receiver. If the voltages are not in phase, a correction voltage is applied from the phase detector to the horizontal oscillator in order that the frequency and phase of the oscillator will be the same as the frequency and phase of the sync signal. The oscillator that is teamed with the phase detector is usually either a cathode-coupled multivibrator or a combination of a sine-wave oscillator and a reactance tube. In the first case, the correction voltage is fed to one grid of the multivibrator tube; and in the second case, it

is placed on the grid of the reactance tube.

Dual Diode

A review of the operation of a phase detector using a dual diode should be helpful in explaining how the triode circuits differ from the diode circuits. Fig. 1A is a schematic diagram of one arrangement of a diode type of circuit. Sync pulses of two polarities are taken from a phase-inverter stage. Positive sync pulses are applied to the plate of V1A, and negative pulses are applied to the cathode of V1B. The sawtooth wave is applied to the cathode of V1A and to the plate of V1B.

If the oscillator is on frequency and in phase with the sync pulses, the pulses will occur at instants when the value of the sawtooth voltage is zero. The pulses, which are of equal amplitudes, cause the diodes to conduct equally and to charge C1 and C2 in the polarities shown on the diagram. Between pulses, C1 discharges

through R5 and R7; at the same time, C2 discharges through R4 and R7. The voltages developed across R7 by these discharge currents are opposite in polarity, and they are equal because the capacitors were equally charged and because the resistances in the discharge paths are equal. The resultant output voltage taken from the top of R7 is zero.

The sawtooth wave causes some conduction in addition to that caused by the sync pulses, but this conduction is equally divided in the two diodes. The voltage produced by the sawtooth wave has an average value of zero, when measured across R7, no matter what the phase of the sawtooth wave may be.


Production of a correction voltage is the result of an unbalanced condition in which one diode conducts more than the other during a sync-pulse interval. When the oscillator associated with the circuit shown in Fig. 1A is running too fast, the sawtooth voltage reaches a positive value by the time the sync pulse arrives. The diodes are therefore biased in such a manner that V1B conducts more heavily than V1A, and C2 is given a greater charge than C1.

The resultant voltage across R7 is positive. A voltage of this polarity is needed to slow the oscillator used with this phase detector. If the oscillator tends to run at a reduced rate, V1A conducts more heavily than V1B and the correction voltage is negative.


Triode in Motorola Model 21T21E

There are some similarities between the diode phase detector and one type of triode phase detector. A circuit in the Motorola Model 21T21E is shown in Fig. 1B. The triode receives the same input sig-

* * Please turn to page 76 * *

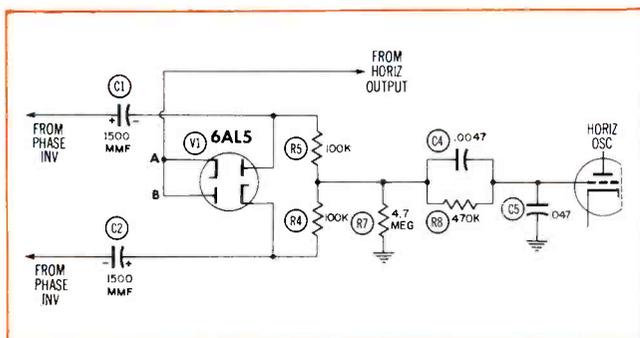

(A) Dual-Diode Circuit.

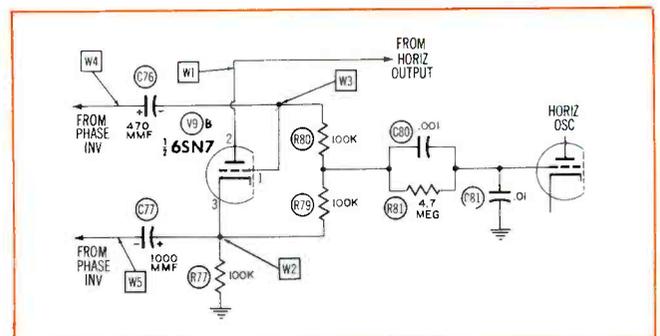

(B) Triode Circuit in Motorola Model 21T21E.

Fig. 1. Typical Phase Detectors for Horizontal AFC.



G-C CRT DUO-DECAL TEST SOCKET ADAPTER
For top-of-chassis tests.
No. 9251 NET \$1.95



G-C GRILLE CLOTH ASSORTMENT
Various sizes and patterns.
No. 9114 NET \$0.99



G-C HIGH-VOLT TEST LEADS
Heavy duty TV leads; phone tips.
No. 9100 NET \$3.00




G-C POCKET HEX KEY WRENCH SET
Seven sizes .050" to 3/16"; case.
No. 9124 NET \$1.65



G-C PRINT-KOTE SILICONE RESIN
Protects printed circuit repairs.
No. 14-2 NET \$1.17



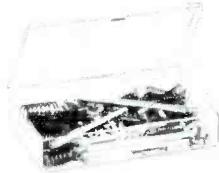
G-C "99" RUBBER GROMMET ASSORTMENT
Many types & sizes; plastic box.
No. 9121 NET \$0.99



G-C "99" SPRING ASSORTMENT
Styles and sizes for all repairs.
No. 9118 NET \$0.99



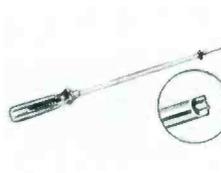G-C "99" WASHER ASSORTMENT
Metal & fiber washers, all types.
No. 9119 NET \$0.99



G-C SCREW-STARTER SCREW DRIVER
Starts screws in tight spots.
No. 9148 NET \$2.10



G-C SPRAY-KOTE TUBE-KOTE
Touchups scratched picture tubes.
No. 49-12 NET \$2.17



G-C K-27 PRINT-KOTE
Pressure-spray silicone resin.
No. 14-6 NET \$2.17



G-C SPRAY-KOTE HAMMER-KOTE
Brown hammer finish, air dries.
No. 83-12 NET \$1.83



G-C DUAL SPEAKER SWITCH ASSEMBLY KIT
Wired, ready to use.
No. 9188 NET \$1.17

GENERAL



Ask For These


RADIO-TV SERVICE AIDS

... at Your Jobber

CEMENT



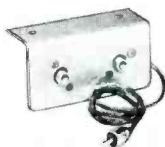G-C SPRAY-KOTE APPLIANCE WHITE
Snow white finish for ranges, etc.
No. 9113 NET \$1.30



G-C PHONE DUPLEX JACK AND PLUG
For hi-fi and audio, ready-wired.
No. 9226 NET \$0.90



G-C ALL-STEEL SERVICEMAN'S KIT
Large, roomy kit with 7 tools.
No. 9052 NET \$8.10




G-C KLEEN-TEX CLEANER
Safe, slow-burning, inexpensive.
No. 11-G NET \$2.10



G-C HORIZONTAL BAR GENERATOR
Simple, accurate TV alignment.
No. 9149 NET \$1.95



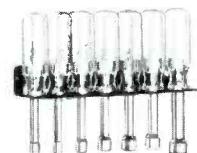G-C NUT & HEXHEAD SCREW STARTER
For 1/4" & 3/8" hex nuts, screws.
No. 9147 NET \$1.50



G-C 7-PIECE NUT DRIVER SET
Sizes 3/16" to 1/2"; wall rack.
No. 9208 NET \$3.60



G-C TV PICTURE TUBE BOOSTER
5-wire type, half-moon socket.
No. 9136 NET \$1.50



G-C PRINT-KOTE SOLVENT
Solvent for silicone resin.
No. 13-2 NET \$0.33



G-C TV-RADIO IRON CORE KIT
7 types, for 90% replacements.
No. 9141 NET \$0.57



G-C STANDARD TUNER SLUGS
Envelope of 3 replacements.
No. 9095-E NET \$0.30



G-C DELUXE TV ALIGNMENT TOOL KIT
Roll-type case with 16 tools.
No. 8280 NET \$7.74



G-C 7-PIN MIN. TEST SOCKET ADAPTER
Saves time on chassis tests.
No. 9247 NET \$1.65



G-C 9-PIN MIN. TEST SOCKET ADAPTER
Use with alligator clips or prods.
No. 9249 NET \$1.85



G-C MOTOROLA TV DIAL BELT
Genuine replacement for tuners.
No. 196 NET \$0.30




FREE!

Complete, illustrated G-C Catalog. New service aids. Send postcard today.



GENERAL CEMENT MFG. CO.

903 TAYLOR AVENUE • ROCKFORD, ILLINOIS

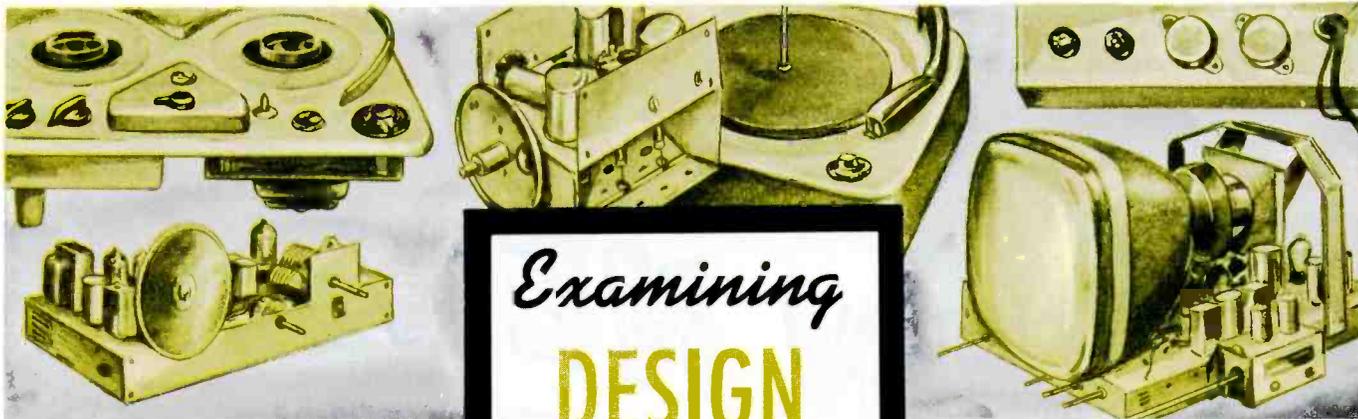

Examining DESIGN Features

by **LESLIE D. DEANE**

Raytheon Transistorized Radio With Chassis 8RT1

The receiver pictured in Fig. 1 is an example of Raytheon's new portable transistorized radio. There are very few transistorized radios on the market at the present time; but what the future holds for this new field, only time can tell.

The Raytheon receiver shown in Fig. 1 incorporates Chassis 8RT1. The physical locations of some of the components in the Raytheon transistorized radio are indicated in the photograph of Fig. 2. A schematic diagram of this chassis is given in Fig. 3. The unit employs eight transistors which actually replace the vacuum tubes that would normally be employed in a conventional portable AM radio. The transistors used in the RF, IF, and detector stages are the CK760 type made by Raytheon. The ones used in the audio stages are the CK721 or the CK722 type and are also produced by Raytheon. These types are shown in the photograph of Fig. 4.

The antenna, which is attached to the chassis, consists of a coil wound on a long ferrite rod. This type of antenna provides a rather high Q for the input circuit. The tuning capacitor is of the conventional ganged type, and the receiver has a frequency range from 540 to 1,600 kilocycles.

The signal from the antenna is inductively coupled to the base circuit of the mixer which is a CK760 transistor having a relatively low input impedance. Another CK760 transistor is employed as the oscillator.

A superheterodyning action takes place at the mixer because of the oscillator injection voltage which is coupled through the oscillator coil L2 to the emitter circuit of the mixer. The IF transformer L3, which also has a low input impedance, allows

the proper intermediate frequencies to pass from the mixer to the first IF stage. The intermediate frequency is 455 kilocycles; and the IF transformers L3, L4, and L5 are all single-tuned units. The first and second IF transistors operate in a similar manner to that of triode RF amplifiers and therefore require neutralization. Capacitors C12 and C17 function as neutralizing components, and they feed back a portion of the output signal to the input of each IF stage.

A negative AVC voltage is fed back from the detector to the base connection of each IF transistor in order to control the gain of each IF stage. Resistors R13 and R18 develop the proper bias voltages required for

* * Please turn to page 61 * *



Fig. 1. Raytheon Transistorized Portable Radio Using Chassis 8RT1.

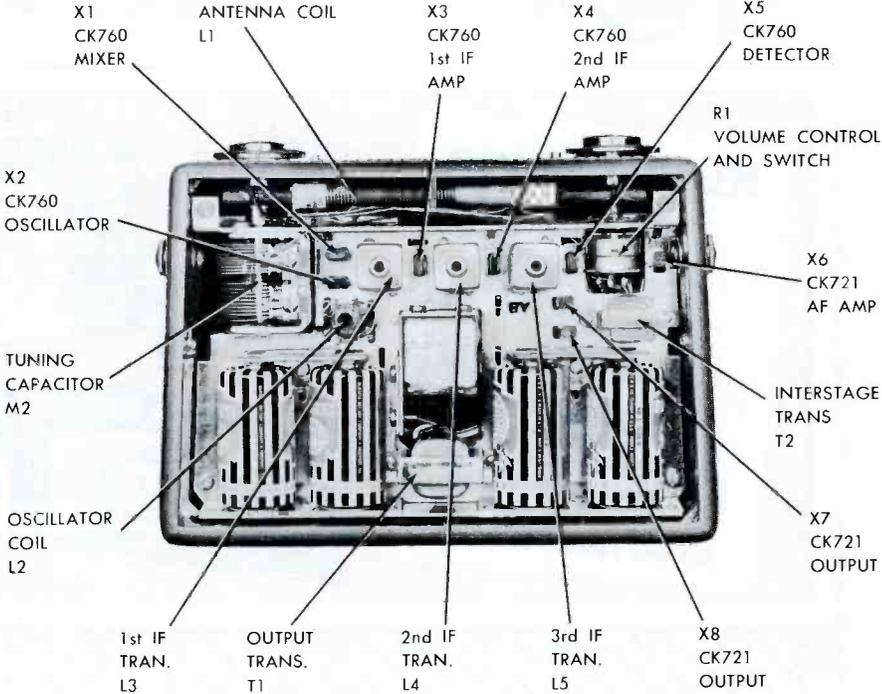


Fig. 2. Rear View of Raytheon Transistorized Radio With Cover Removed.

WIN NEW CUSTOMERS WEEK AFTER WEEK!

10 NEW PRIZES—EVERY WEEK
10 NEW WINNERS—EVERY WEEK

It's easy for you to take part—

- Window Displays,
- Streamers,
- Counter Cards,
- and Entry Blanks—

Identify you with Sylvania's big, new business-building prize promotion.
 "See your Sylvania Distributor."





**OFFER THEM A CHANCE TO
WIN VALUABLE
"BEAT THE CLOCK"
PRIZES AT HOME**

**It's easy for your customers to win... nothing to write
nothing to buy...but every entry
blank must be endorsed by you**

**Weekly
CONTEST
PRIZES
for home viewers
include:**

**TV CONSOLES
TV TABLE MODELS
HI FI PHONOGRAPHS
CLOCK RADIOS
TABLE RADIOS**

Nothing to write—nothing to buy—and everything to win. Sylvania's big, new "Beat the Clock" prize contest for home viewers is as easy as that. Every week, week after week you can create new contacts with the TV families in your community who want to play "Beat the Clock" at home and win one of 10 valuable prizes given away each week. How do you do it? Just see that they get an official entry blank endorsed by you.

It's the greatest business-building opportunity you've ever had. Make it work two ways for you. Bring new customers to your shop by displaying "Beat the Clock" prize promotion material. Tie in window and counter displays with the Sylvania products you sell.

Bring your service into new customers' homes by mailing entry blanks to your TV community. Tie in the "Silver Screen 85" consumer booklet and other Sylvania direct mail material with your TV service.

Remember, never before has the TV Service Dealer had such a concrete part in a national TV program. Make Sylvania's "Beat the Clock" prize contest click for you. See your Sylvania Distributor for your promotion package.

SYLVANIA ELECTRIC PRODUCTS INC.
1740 Broadway, New York 10, N. Y.
In Canada: Sylvania Electric (Canada) Ltd.,
University Tower Bldg., Montreal

 **SYLVANIA®**

LIGHTING • RADIO • ELECTRONICS • TELEVISION • ATOMIC ENERGY

New! SELENIUM

TV REPLACEMENT RECTIFIER

Bonus Pack!

4 TV Replacement Rectifiers . . .
a PAIR and a SPARE PAIR in every pack!

You can't miss with International's New "BONUS PACK"! You'll get the *best* in TV replacement rectifiers. Each BONUS PACK contains a pair for immediate use, and a spare pair for your next job—PLUS a Nylon TV Alignment Tool worth \$1—ABSOLUTELY FREE!



GET THE BEST...SPECIFY

International

THE WIDEST RANGE
OF QUALITY REPLACEMENT
RECTIFIERS IN THE
INDUSTRY

Makes a World of Difference



International Rectifier

C O R P O R A T I O N

1521 EAST GRAND AVENUE • EL SEGUNDO, CALIFORNIA • OREGON 8-6281
IN CANADA: Atlas Radio Corp., 50 Wingold Ave. W., Toronto, Ontario
WORLD'S LARGEST SUPPLIERS OF INDUSTRIAL METALLIC RECTIFIERS

Here's Why International Rectifiers Are Your Best Bet!

HIGH QUALITY International, through its advanced designs and precision production, consistently meets—or exceeds—the highest government and trade standards for all types of rectifiers. These high standards are maintained on *all* International products, assuring *you* a better product.

THE WIDEST RANGE IN THE INDUSTRY! . . . more than 10,000 types! International TV-Radio rectifiers are available in *all* sizes and types. This complete line of selenium and germanium products also includes industrial rectifiers, replacement diodes and a wide range of photo-cells and sun batteries.

SPECIFY INTERNATIONAL RECTIFIERS for long, dependable performance. Best for you . . . Best for your service customers!

Ask your distributor for details about
International's "Bonus Pack" today!

TROUBLES in VIDEO IF and DETECTOR SYSTEMS

A Servicing Guide Arranged by Symptoms

BY LESLIE D. DEANE
and CALVIN C. YOUNG, JR.

The video IF strip, including the video detector, forms the link between the RF tuner and the video-amplifier stages. The IF amplifier stages use tubes which may be dual purpose and which may function in other sections of the receiver.

The video IF strip has three main purposes. The first is to amplify the signal from a station after that signal has been converted to intermediate frequencies, the second is to reject all other signals, and the third is to detect the video signal so that it may be applied to the video-amplifier stages. Even though different IF strips may tune to widely different frequencies, the problems associated with each are very similar.

The troubles usually encountered in a video IF strip are generally associated with certain symptoms either in the sound, in the picture, or in both. The following list contains many of these symptoms.

1. Raster, no picture, and no snow.
2. Snowy picture.
3. Ringing in picture.
4. Poor vertical synchronization.
5. Pulling in picture.
6. Lack of picture contrast.
7. Intercarrier buzz in sound.
8. Negative picture.
9. Hum in picture.
10. Intermittent troubles.
11. Smeared picture.
12. Overloading in picture.

detector stages along with a few general servicing hints will be presented at this point. It is hoped that this general discussion will better equip the service technician to trouble shoot these stages of the television receiver.

There are two major classifications for video IF circuits. One is the split-sound system in which the video IF and sound IF signals are amplified separately. The other is the intercarrier system in which both the sound and video IF signals are amplified through one common IF strip. In the split-sound system, the sound IF signal is extracted from the composite IF signal at some point ahead of the video detector. In the intercarrier system, the sound IF signal is permitted to pass through the video IF stages; however, its amplification is held to only about 5 per cent of that of the video IF signal. The majority of television receivers now in the field incorporate the intercarrier system.

General Discussion

A brief review of the different designs employed in the video IF and

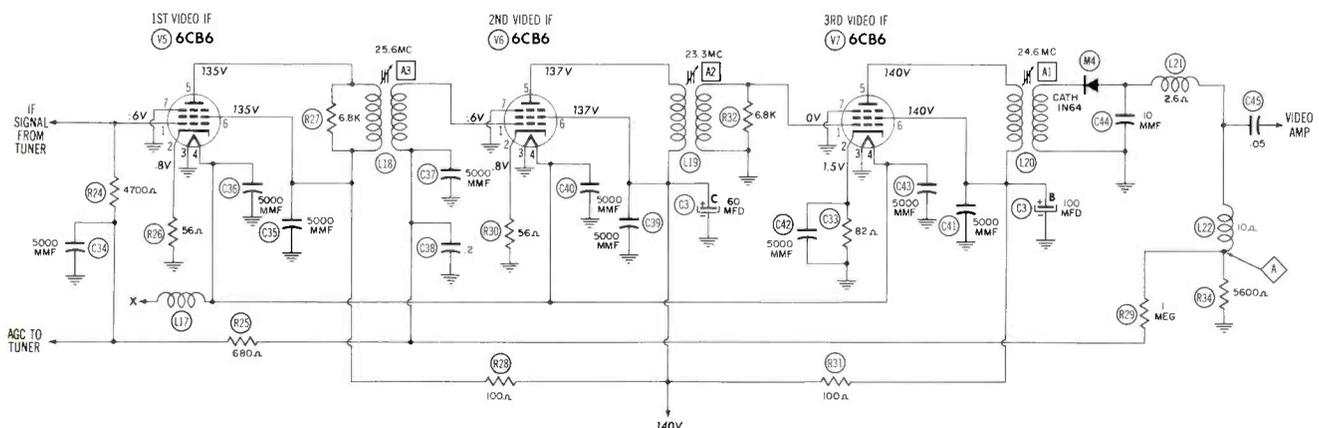


Fig. 1. Video IF and Detector System Which Employs a Crystal Detector and Transformer Coupling Between Stages.

P. R. MALLORY & CO. INC.
MALLORY
APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO. INC.
MALLORY
APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO. INC.
MALLORY
APPROVED PRECISION PROD

Exact Duplicate DUAL CONTROLS available TWO ways

DO you prefer ready-to-use dual controls? Or would you like a small stock of control sections, switches and shafts that you can assemble quickly for the combination you need? Either way, with Mallory, you can be sure of duplicating the exact electrical characteristics of the controls in practically any popular TV set.


Either way, with Mallory, you can equal or exceed the performance of the original equipment control. You can count on accurate resistance values, smooth tapers, quiet operation and long life.

Either way, with Mallory, you can be sure the job is right the first time . . . without profit-cutting "come backs."

Either way, your Mallory distributor has what you need. Call him today!

Exact duplicate, ready-to-use, dual control . . . factory-made with all the resistance values, tapers, taps, switches and shaft lengths needed for most of the popular TV sets.

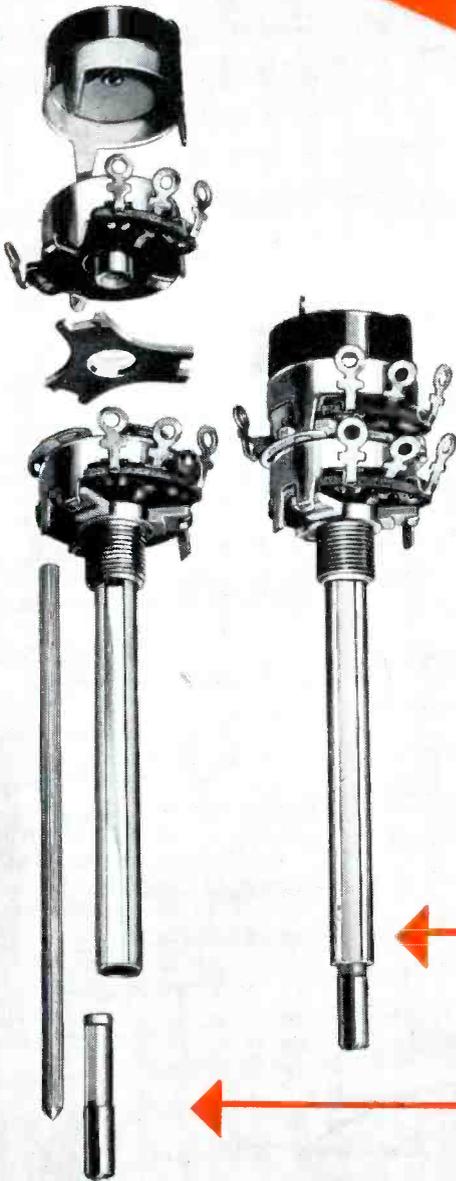Exact duplicate, dual control kits. With a small stock of factory-assembled control sections, you can make 10,000 different combinations. No soldering or special tools required. Assembly takes less than five minutes.



APPROVED PRECISION

APPROVED PRECISION

P. R. MALLORY & CO. INC.
MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
RECTIFIERS • POWER SUPPLIES • FILTERS • MERCURY BATTERIES
APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

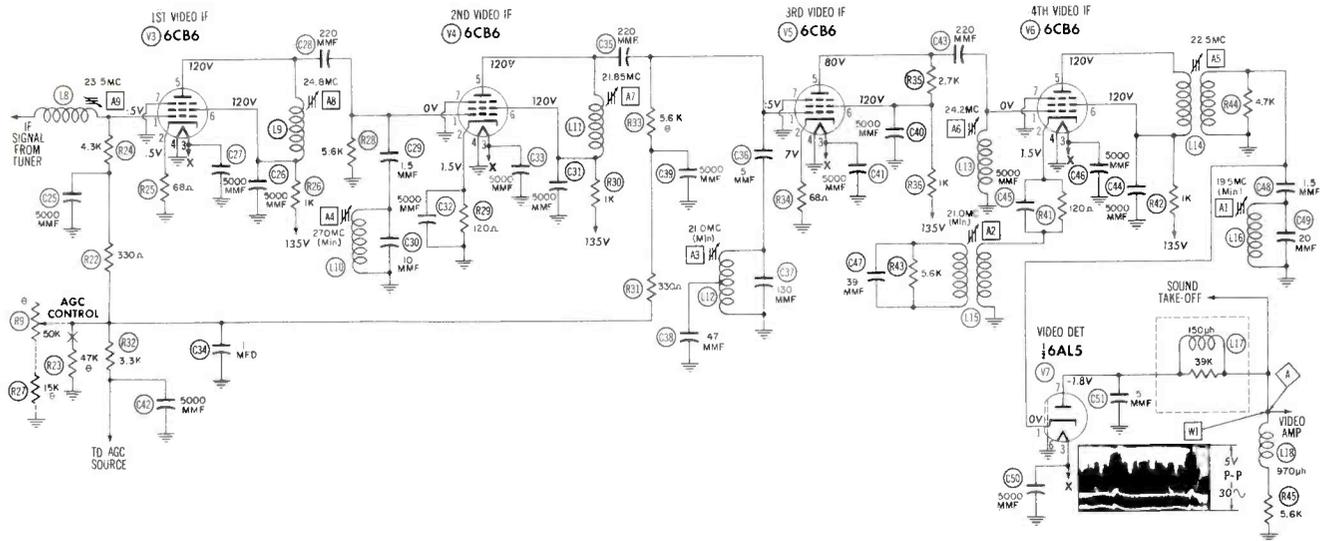


Fig. 2. Video IF and Detector System Which Employs a Diode Detector and Capacitive Coupling Between Stages.

The resonant circuit employed in the majority of IF stages consists of a coil or transformer in combination with the associated capacity of the circuits. Adjustment is provided by movable metal cores, and the stages may be overcoupled or stagger-tuned in either the intercarrier or split-sound systems.

The number of IF stages in a TV receiver will vary from two to four, and the stages may employ a wide selection of high-gain tubes. At the present time, the two IF ranges most commonly used in TV sets are the ranges between 21 and 26 megacycles and between 41 and 46 megacycles.

The video-detector stage will employ either a crystal diode or a vacuum tube connected in a series or shunt arrangement. The detected output signal from this stage will either be positive or negative, depending upon the polarity required by the video-output stage. The detector stage is sensitive to stray pickup and therefore requires adequate shielding.

The IF signal is usually inductively or capacitively coupled through the IF strip. A schematic diagram of a typical IF section which is transformer coupled is shown in Fig. 1. This circuit also employs a 1N64 crystal as a video detector. The schematic of Fig. 2 illustrates another typical IF strip; however, it utilizes capacity coupling and a 6AL5 tube as a detector. These schematics will be referred to from time to time in connection with the possible causes of each symptom.

Proper operation of the video IF strip depends upon three basic voltages: (1) the RF signal voltage

supplied by the tuner, (2) the B+ voltage which is usually furnished directly from the low-voltage power supply or indirectly from the audio-output stage, and (3) the AGC voltage which automatically controls the gain of one or more of the IF amplifiers. The AGC voltage is usually derived from the video-detector stage or from a keyed AGC circuit.

A trouble symptom that may point to an inoperative IF strip can often be caused by a defective component in another section of the receiver if the trouble affects one or more of the three voltages mentioned in the previous paragraph. The B+ and AGC voltages applied to the IF section can be checked with an ordinary voltmeter. If these voltages appear to be incorrect, it may be necessary to make a resistance check of the components in the B+ and AGC circuits.

It is rather difficult to formulate one universal trouble-shooting procedure to cover all symptoms that may develop because of a faulty video IF or detector stage; therefore, only a general procedure for localizing the defective section will be presented.

Isolating the trouble to the RF, IF, or video-output circuits may be accomplished by tracing the signal with the aid of an oscilloscope. One of the first logical steps would be to check the signal at the video-detector load. If a normal signal is present, it usually indicates that the trouble exists in the video-output stage or that the picture tube is defective. If a normal signal is not encountered across the video-detector load, then the trouble is probably in the RF or IF stages.

The next step would be to check the tuner. One method to determine if the signal is getting through the tuner is to connect an RF signal generator across the antenna terminals. A signal modulated with 400 cycles should be used. Two resistors of about 100 ohms each should be placed in series with the generator leads. The oscilloscope detector probe may then be placed at the grid of the first IF stage, and a 400-cycle pattern will be observed if the tuner is passing the input signal. The 400-cycle signal can also be traced on through the IF stages. A more detailed procedure for trouble shooting the IF section is outlined under symptom No. 1.

In trouble shooting an IF system, a check of the IF alignment is often very helpful. This check can help to determine two conditions: (1) the frequency response and (2) the relative gain of the IF strip. The frequency response of the IF strip is represented by the shape of the IF response curve as seen on the face of the scope. The relative gain is represented by the height of the curve.

In order to be able to evaluate relative gain, it is necessary for the technician to be familiar with his particular alignment equipment and also to be familiar with the approximate gain of an IF strip that is operating normally. These things can both be obtained by checking the IF response and gain of several receivers that are operating normally and by maintaining the same gain settings on the generator and oscilloscope. A check on the frequency response of the IF strip can be had by comparing the response pattern obtained on the oscilloscope face with

* * Please turn to page 47 * *

NEW!

NOISELESS!


ELECTRONIC!



Thompson Products


Automatic

Superotor.

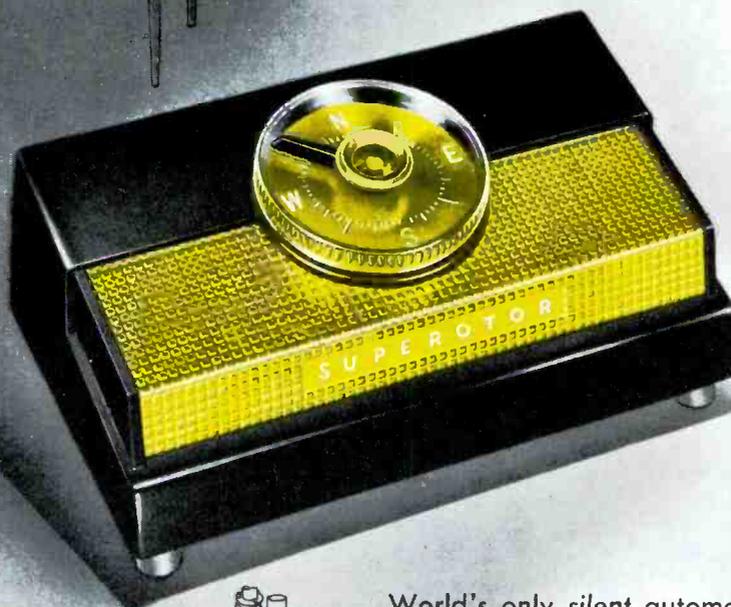

INTERCHANGEABLE ROTORS

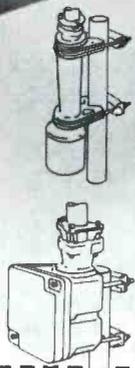Famous time-proved Superotor models "100" and "500" have both been adapted for automatic operation!



World's only *silent* automatic antenna rotator! No gears, no click, no clatter. Electronic fingertip VP* tuning. Antenna rotation and control is smooth, not in "steps" like ordinary automatics — provides a new standard of tuning accuracy for Fringe, UHF and Color reception. Write today for specifications.

*VP (Vernier Precision)

**OTHER THOMPSON PRODUCTS
ELECTRONIC AFFILIATES**

- Bell Sound Systems • Dage Television • Ramo-Wooldridge Corp. • Pacific Semi-Conductors, Inc.


ELECTRONICS DIVISION

Thompson Products, Inc.



2196 CLARKWOOD ROAD • CLEVELAND 3, OHIO

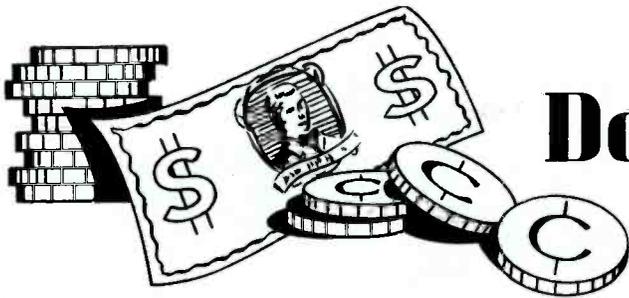Available in Canada thru Atlas Radio Corp., Ltd., 50 Wingold Ave., Toronto



Dollar and Sense Servicing

by *John Markus*

Editor-in-Chief, McGraw-Hill Radio Servicing Library

SURVIVAL. The secret "White House" outside Washington will be linked by a closed-circuit survival TV network with several other retreats to be occupied by government officials in the event of enemy attack. There will also be facilities for linking to commercial networks for reporting to the nation.



BLOOD. With an arm around each combatant at a boxing match, the referee adds an afterthought to his routine instructions: "... and, oh yes, one more thing — this is color television! So, bleed a little." Saw this in Walt Ditzen's FANFARE cartoon strip recently.

Wonder how many other TV programs will be affected by color. Will girls have to learn to blush all over again as they did in the gay nineties?

At least, we know that commercials adjacent to or within regularly scheduled NBC color programs will have to be in color; the notice went out to all advertisers. After Sept. 1 on WRCA-TV in New York and WNBQ in Chicago, advertisers will either use color at \$500 extra per 20 seconds or lose their place to some other client who will. It makes sense, too; in those first few minutes after a fine color program, any black-and-white commercial would look pretty sick.

Here's something to keep you up nights. Suppose that each tone of color was represented by a specific shade of gray in the range from white to black. Then, with a camera to translate colors into equivalent grays, color could be transmitted as a black-and-white program for reception on black-and-white sets, provided that we had something to change the grays back to their colors for color viewing. Well, one firm claims to have done exactly this; you watch the receiver

with binocularlike eyeglasses that convert the grays back into the original colors. The operating principle involves color temperatures in some way. Until we see a demonstration, though, we'll continue rooting for compatible color.



SURVEY. Checkup by General Electric of 150 models of 1954 and 1955 TV sets showed 119 different types of receiving tubes in a total of 2,950 sockets for an average of about 20 tubes per set. The new RCA color TV line thus has only 6 more tubes per set than the average for black and white.



TAPED TUTORING. A classified ad in Tape Recording magazine may well be indicative of a new way of learning by mail. A professor offers correspondence courses on tape in five different languages. You state your knowledge level and objective, and he outlines your program and gives the price.

Many types of courses could be offered on tape, with associated booklets of diagrams when necessary. Music, languages, dramatics, public speaking, and singing are just a few courses that come to mind. Completed lessons on tape could be returned in trade for the next, thus keeping down costs. Practice assignments could be recorded on separate tape by the student for analysis by the instructor, and the latter's comments and advice could in turn be recorded for the student.

In the same magazine, there is another unique use for magnetic recording. The Baltimore YMCA has

three automatic announcement machines hooked to its telephone lines. When their number is called, one of the machines answers automatically with a 30-second recorded message of inspiration. A newspaper announcement of the service resulted in some 6,000 completed calls and over 16,000 "busies" during a 24-hour period, with all three machines running. Here's a typical message:

"Hello — we're glad you called! A wise man knows what to do next; a skilled man knows how to do it; and a successful man does it. God giveth to man that which is good in His sight — wisdom, and knowledge and joy. (Eccles. 2:26) Your YMCA reminds you that families that worship together are happy families. — Thank you!"



TRANSISTORS. Pointing up the reliability of transistors, General Electric has increased the warranty period on its units from 90 days to a full year.



LAMPLIGHTERS. The arrival of the arc lamp for street lighting put our dad out of work back in the days when dogs lay waiting to nip him as he trudged the streets with his flaming torch to light the gas lamps at twilight. Then in turn the guy who replaced the carbon pencils of the arc lamps lost his job when they changed over to Edison's incandescent invention. And now the switch-thrower for these "gets the gate." In Manhattan and the Bronx, they're putting phototransistors right on the lamps to turn them on and off automatically. Or will the switch-thrower be put back on the beat to replace phototransistors as they go bad?

* * Please turn to page 54 * *

INTRODUCING THE

New **GEOMATIC** TV ANTENNAS

(pat. pend.)

BY **FINCO**®

with exclusive **Fidelity Phasing***


* Dictionary: the highest degree of accuracy in the reproduction of a signal




Model B-1
Metropolitan
and Suburban




Model B-2
Suburban and
Semi-Fringe Area

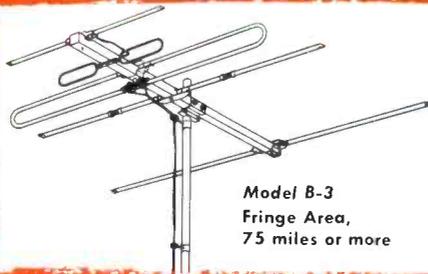

Model B-3
Fringe Area,
75 miles or more

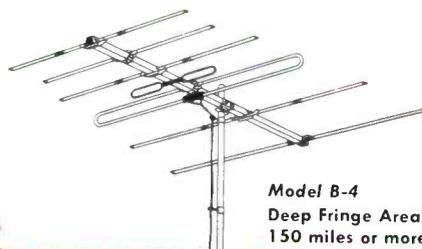

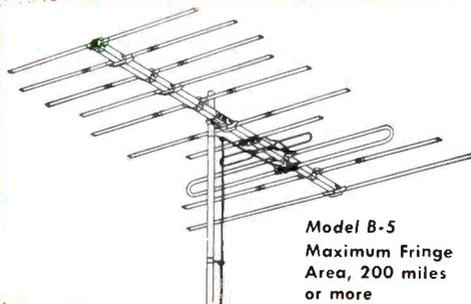Model B-4
Deep Fringe Area,
150 miles or more



Model B-5
Maximum Fringe
Area, 200 miles
or more

Here are the antennas they said could never be developed — combining the finest features of an impedance matching, driven folded dipole on low-band with super-gain of a 3-element colinear on high-band (without the use of matching harness) to produce the — **GREATEST BROAD-BAND ANTENNAS EVER BUILT!** In addition, the new **GEOMATIC** Series features extremely high **FRONT - TO - BACK RATIO!** Models range from "in-town" types to super-fringe area antennas.

GEOMATIC

 means
customized for your locality

Now For The First Time —

Regardless of channels, distance from station, or terrain **FINCO** can deliver a model that is perfectly suited for your area — at no extra cost!

Write, wire or phone

The FINNEY Company

Henderson 2-2150 4612 ST. CLAIR AVENUE
Dept. pf-95 CLEVELAND 3, OHIO

Copyright, 1955
The Finney Company

Now

YOUR TV PICTURE TUBE INSTALLATIONS FINANCED BY GENERAL ELECTRIC


YOU can sell G-E picture tubes to your service customers on the *instalment plan!* First national tube credit program to be handled direct by a leading manufacturer!

- You tie up no capital—endorse no notes. You are reimbursed immediately for the full amount of your bill covering tubes, parts, and labor.
- You sell high-profit tubes and

service where cash isn't available to your customers. You open the door wide to new business—more business! And those repaired TV sets piling up on your shelves which customers can't pay for, now will move out from your shop *FAST.*

- You have no collections or record-keeping to worry about. Credit arrangements with your customers are made quickly and easily.

GENERAL  ELECTRIC

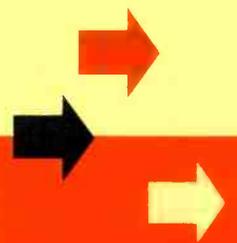

It's easy as 1-2-3

to sell new G-E picture tube installations on credit

1.




You find that your customer hasn't the cash on hand to pay for the new G-E picture tube that's needed, plus other General Electric tubes, also parts and labor. So . . .

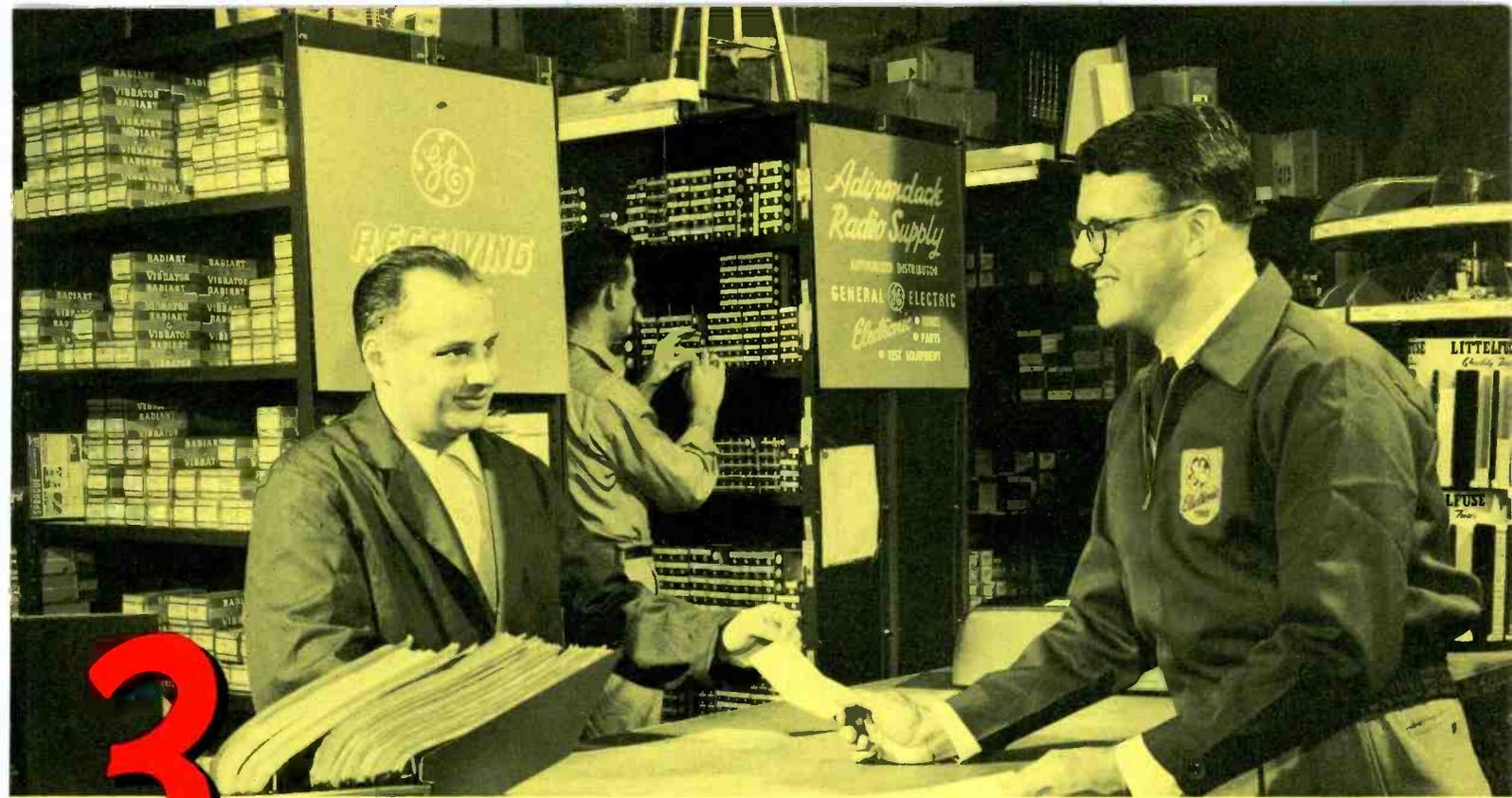2.



You explain G.E.'s easy payment terms. The customer welcomes the opportunity to sign the contract. You then proceed to make the installation, and put your customer's TV in tip-top shape.

One call to your G-E tube distributor will bring full



Next day you turn over the contract to your G-E tube distributor, who reimburses you for the complete installation job, including labor.

READ HOW YOU CAN USE THIS GREAT NEW GENERAL ELECTRIC CREDIT PLAN!

OFTEN the price of a new picture tube keeps customers from having their TV sets serviced properly. They are forced to get along with an inferior picture, or no picture at all, while you lose a profitable repair job.

Now G.E. gives you a way to turn these lost jobs into service dollars. No longer need your customers pay cash in full. You can give them as long as six months to pay out of income, with a down payment as low as \$5.

Yet you get reimbursed immediately by your G-E tube distributor. Furthermore, you endorse no notes, have no collections to make. That part is handled by the General Electric Credit Corporation in cooperation with your distributor.

Act today! Ask your G-E tube distributor to show you how to obtain . . . on easy credit terms . . . picture tube installation jobs you've never been able to sell before! *Tube Department, General Electric Company, Schenectady 5, N. Y.*

GENERAL  ELECTRIC


AND BE THE FIRST TO OFFER...

instructions, forms, and advertising-promotion helps!

A New Look FOR OLD TV's

Choice of 10 decorator colors and patterns

"STIX" is its name, and it works wonders on old TV receivers. Your customers can quickly and easily change cabinets to blonde, or to 9 other desired colors or patterns. That TV receiver which has outgrown its living-room usefulness, can be made over into a second set that matches the decoration of den, rumpus-room, or nursery. "Stix"—made of Firestone Velon, and available from your General Electric tube distributor—is another big reason why your customers will want to have their television sets repaired . . . by *you*, who offer them new TV appearance along with new and better performance—a new set inside and out!

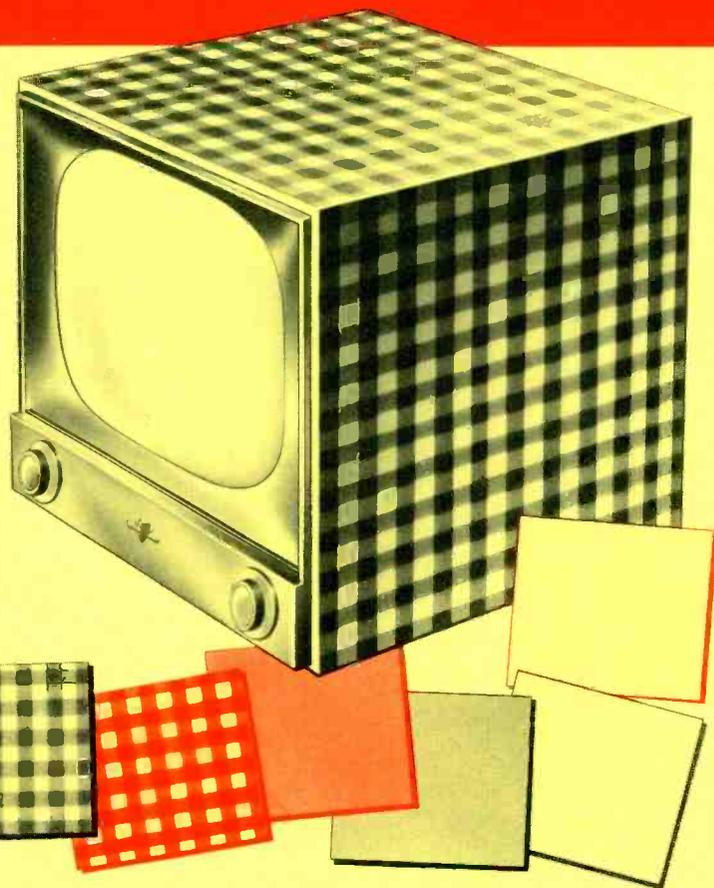

NINE OUT OF TEN TV OWNERS right in your neighborhood will read about the sensational new G-E picture tube credit plan—and about the new decorator coverings for old TV's

. . . in every Sunday newspaper supplement—
and TV Guide—reaching 46,500,000 homes.

. . . in colorful posters, displays, and other promotion
material G.E. is providing for your local use.



GENERAL  ELECTRIC

Shop Talk

(Continued from page 11)

tester (whether it is a gm or emission type). To check even as few as five tubes would take between 7 and 10 minutes because of the various controls that had to be set before the value test could be made. To do a thorough service job, it is frequently desirable to check more than 5 tubes, and the time required would be increasingly longer. This is valuable time to the technician and his organization. The longer each job takes, the fewer the calls that can be made. Time is also important to the customer because he is being charged on a time basis. Anything that would reduce this checking time and still provide the necessary information would thus be beneficial to both the technician and his customer.

That was the first consideration, but there was a second problem which apparently was not unrelated. Central found that when the low-voltage rectifier tube was replaced in a set, one or more tubes went bad soon afterward. This happened often enough to make it significant. The customer would call and lodge a complaint. Since this trouble occurred shortly after the service call, the customer felt that the set had not been repaired properly the first time. Trying to assure these customers that this was not the case seldom evoked any understanding, and it is not difficult to appreciate their reasoning. Even if the customer had complete confidence in the service organization, it would still seem suspicious that the set would fail so

soon after a service call. What makes the evidence even more conclusive in their eyes is the fact that the set had worked for "umpteen" months before the call. If the job had been properly performed, they conclude that it should certainly take more than a week or two before the set should go bad again.

When you stop to think of counterarguments to this reasoning, you readily see that they concern technical matters which the customer cannot understand; therefore, in 7 out of 10 cases you end by losing a customer unless you forego the charge for the second call. This generosity might wipe out any profit you may have made on the original call.

This is a problem that happened often enough to warrant special consideration. The reasons for the subsequent tube failures after the power tubes had been replaced were felt to be the increased stresses produced by the higher voltages that the new rectifier tubes developed and the fact that the other tubes were near the end of their useful lives anyway. A verification of this supposition was not made because the conditions under which the failures occurred did not lend themselves to individual examination. The manner in which the problem was solved seemed to substantiate the assumptions made.

After examining the various aspects of such a situation, the conclusion was reached that more extensive tube testing during a service call should be required. The ideal condition would be to test all the

tubes in a set, since this would essentially constitute an over-all preventive maintenance check. All tubes that checked weak would then be called to the set owner's attention, and failure to replace them would then become his responsibility. From past experience, it was felt that the set owner would approve replacement of these tubes.

As the reader will immediately note, the one drawback to this solution was that it only tended to aggravate the first problem, namely, the time required to test tubes. It was apparent that a checker was needed to test tubes rapidly, and a project to develop one along these lines was started.

The result of this development program was the instrument shown in Fig. 3. This is a tube tester which incorporates a large number of sockets instead of the few sockets and numerous switches found on conventional testers. There are 30 sockets, and each is wired to accommodate only the specific tubes which are indicated for that socket. This arrangement permits 400 of the most widely used tubes to be checked. At the bottom of the instrument, there are two controls — one marked "Heater" and one marked "Sensitivity."

To test a tube, first locate its appropriate socket from the socket listings. The same listing also indicates the proper settings for the two controls. After the controls are set, the tube is inserted into the socket. By means of a test switch, the condition of the tube is revealed on a built-in meter.

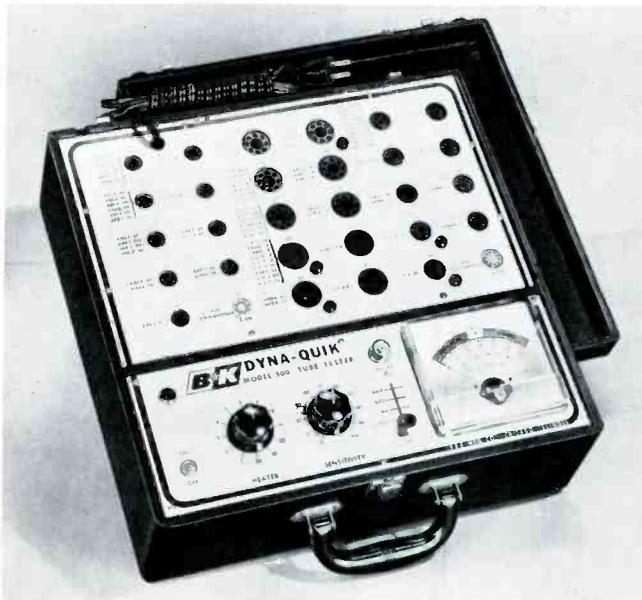


Fig. 3 B & K DYNA-QUIK Model 500 Tube Tester.



Fig. 4. Another Tube Checker for Rapid Testing.


150 field tests have proved to
WARD jobbers:

- * Good VHF picture at as far as 200 miles on several channels
- * Excellent results at 100 miles
- * Good results in areas where no other antenna was able to bring in a picture
- * More compact—25%-75% less stacking distance
- * Channel 2-13 response as much as 40% better than any comparable antenna
- * Unique superior snap-lock bracket
- * Original WARD design all aluminum supplemented spring pressure bracket—eliminates possibility of intermittent contact

TRY ONE—you'll find why the Invader is superseding all fringe and super-fringe antennas.

WARD Model TVS 356 2 bay and stacking harness \$39.95 list

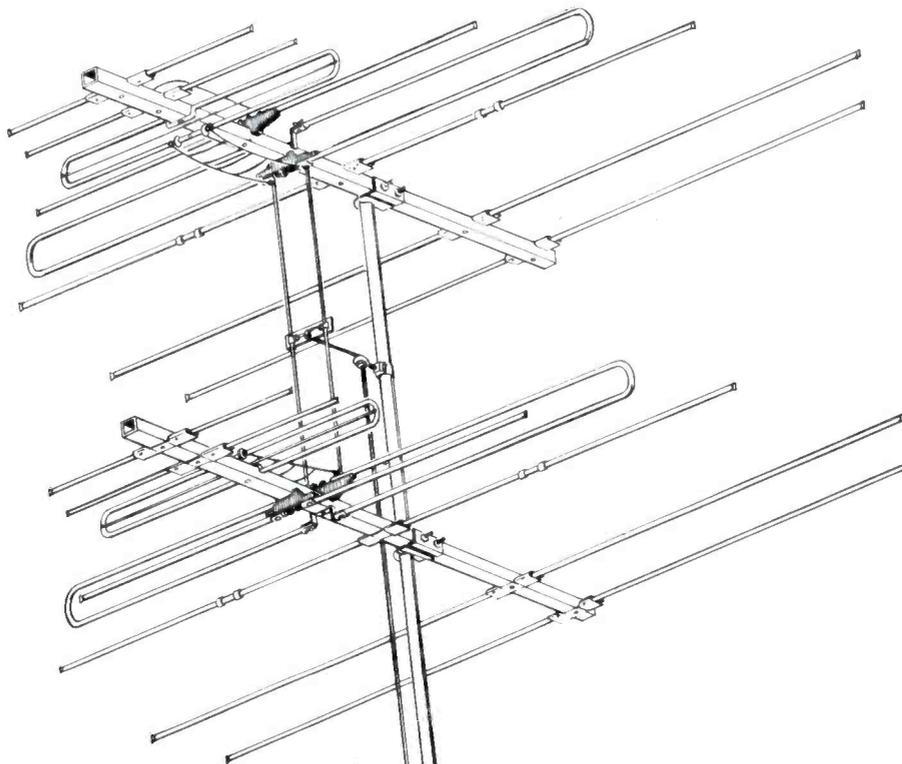
WARD Model TVS 357 4 bay stacking kit (feed harness only) \$3.95



THE INVADER* CONQUERS

sweeps all other fringe and super-fringe antennas before it

* an original WARD design

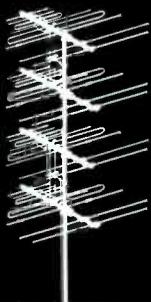

flat type Uni-plane Yagi for fringe area VHF and primary signal area UHF.

*Documental testimonials in our files

WARD PRODUCTS CORP., Cleveland 15, Ohio

With this newly developed tester, a complete set of tubes for an average TV set can be checked in 12 minutes. If fewer tubes are tested, the time is correspondingly less. In addition, the tube-testing facility is complemented by a number of features which are desirable, as experience has indicated. For example, the instrument will indicate tube shorts and do this before the g_m test is made. It also possesses a life-test feature which indicates the ability of a tube to operate when its filament voltage is reduced. (The reader will recall that mention of such a test was made in last month's column.) It contains a sensitive check designed to reveal whether a tube contains gas, a contaminated grid, or grid-to-cathode leakage.

The idea for a quick-check tube tester is not new. One unit that has been available for some time is the TeleTest instrument shown in Fig. 4. This checks tube emission under loaded conditions; and it will reveal gas, grid emission, or interelectrode shorts. Undoubtedly, there are other such instruments on the market; and as their worth is recognized, more will appear.

The trend toward the development of instruments which enable a service technician to carry out his test procedures in less time than before is a healthy one that is indicative of a vigorous and expanding field. The customer will benefit by

the lower charges, and the saving of time will aid the technician by permitting him to do more and better work in the same length of time. A number of worthless gadgets will appear along with the desirable instruments, and caution will be needed to "separate the wheat from the chaff." The criterion which every test instrument must satisfy is: "Does this enable me to do a job better and faster than I am doing it with my present equipment?" If the answer is yes, the instrument is worth while. If the answer is no, then the instrument may be nice to have; but from a business standpoint, it certainly would not be needed.

REVIEW

Auto-radio repair generally poses no more of a problem insofar as circuitry is concerned than any home receiver. Actually, the biggest difficulty that one encounters with this type of servicing is either in gaining access to the chassis or in removing the set from its mounting. Once these have been accomplished, 75 per cent of your work is completed.

Circuitwise, only a few of all the possible causes are responsible for more than 90 per cent of the troubles found in auto radios. Once the technician has become familiar with these, he may perhaps find it profitable to pay more attention to

repairing auto radios and thus open up a new potential source of income.

An article that discusses the major troubles that befall auto radios appeared in the March 1955 issue of Radio and Television News Magazine. The article was entitled, "Servicing Automobile Radios." It was written by I. Silverstein.

Radio and Television News Magazine is published monthly by the Ziff-Davis Publishing Company at 366 Madison Avenue, New York 17, N. Y. Subscription rates are \$4.00 per year for the United States, its possessions, and Canada.

The schematic diagram of a typical auto-radio receiver is shown in Fig. 5. It contains a 6BD6 RF amplifier; a 6BE6 converter; a 6BD6 IF amplifier; a 6AT6 detector, 1st AF amplifier, and AVC stage; and a 6AQ5 audio-output amplifier. Thus far, with the possible exception of the RF amplifier (which most home sets do not have), the circuit differs in no important respect from the AM radios that the technician sees every day. The significant difference between auto and home receivers is in the power supply. In the auto radio, we find a vibrator and either a gaseous or a vacuum-tube rectifier. The vibrator converts the applied DC voltage to pulsating DC which is stepped up to a high AC voltage by a transformer and then converted by the rectifier into a DC voltage suitable for use in the receiver.

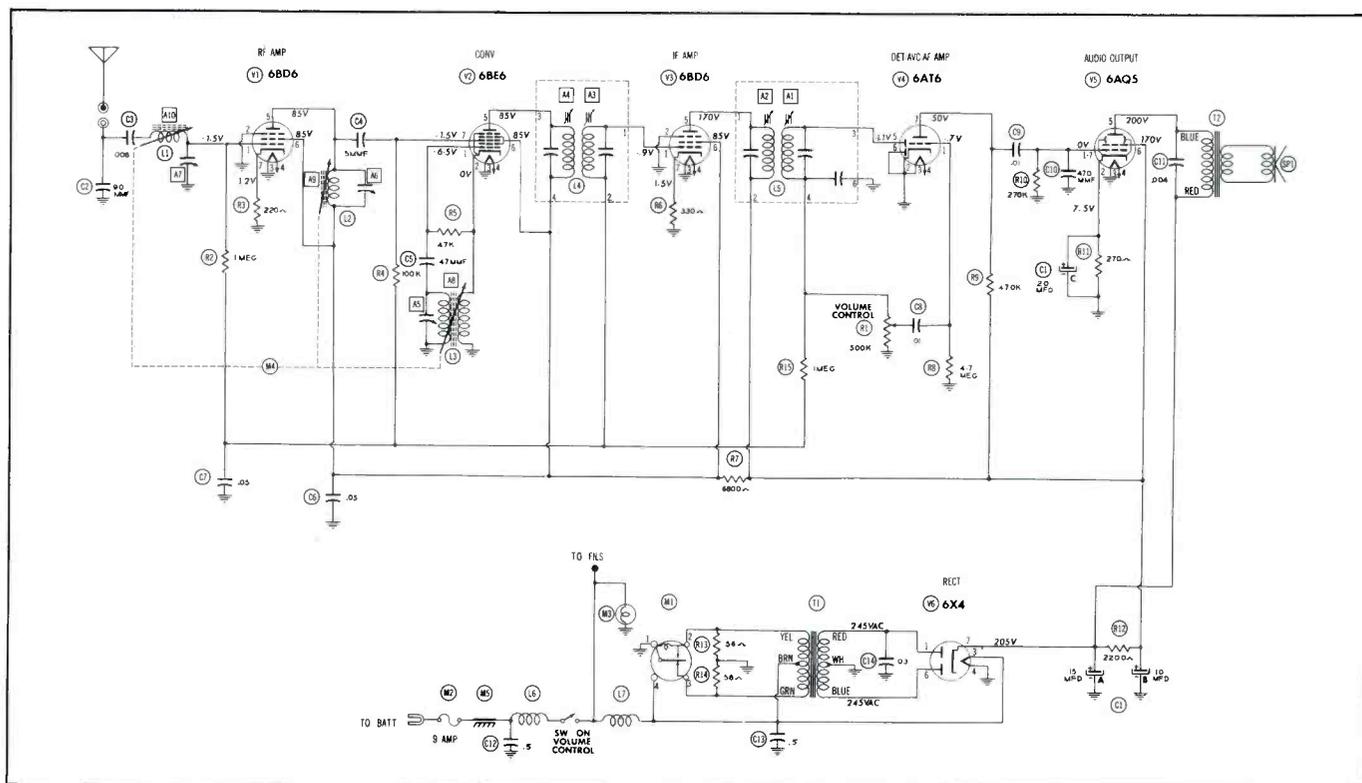


Fig. 5. Schematic Diagram of a Typical Auto-Radio Receiver.

TUNG-SOL "Magic Mirror"

ALUMINIZED

PICTURE TUBE

**BRIGHTER-SHARPER
MORE DETAIL
MORE CONTRAST**




The "Magic-Mirror" Aluminized Picture Tube creates the brightest, most realistic TV picture you can bring into the homes of your customers. The "Magic-Mirror" tube effectively utilizes *all* the light generated by the phosphor screen.

Tung-Sol has developed a unique "fogging" method of backing up the phosphor screen with a mirror-like aluminum reflector. This reflector prevents light radiating uselessly back into the tube. It brings out all the detail of which the receiver circuit is capable. So smooth and true is the Tung-Sol aluminum reflector that mottling, streaks, swirls, "blue-edge", "yellow-center" and other objectionable irregularities are eliminated.

Tung-Sol pin-point-focused electron gun assures a steady, brilliant picture—free from alternate fading and overlighting. Tung-Sol's exacting standards of quality control, manufacture and testing further guarantee the high uniformity and maximum performance of the "Magic-Mirror" TV Picture Tube.

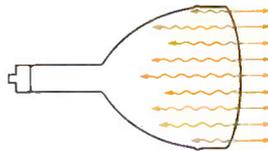
For further details, including Tung-Sol's sales aids and advertising support, call your Tung-Sol supplier today.



ORDINARY TUBE—Only *half* the light produced by the phosphor screen is utilized in the picture. Other half radiates wastefully back into tube.



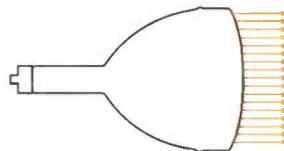RESULT—A light background within the tube which reduces picture contrast.



MAGIC-MIRROR ALUMINIZED TUBE—Aluminized reflector allows electron beam through. Blocks wasted light from backing up into tube. Reflects *all* the light into picture.



RESULT—Pronounced increase in contrast to make a bright, clear, more realistic picture.

TUNG-SOL ELECTRIC INC., Newark 4, N. J.

Sales Offices: Atlanta, Chicago, Columbus, Culver City (Los Angeles), Dallas, Denver, Detroit, Montreal (Canada), Newark, Seattle.

Tung-Sol makes All-Glass Sealed Beam Lamps, Miniature Lamps, Signal Flashers, Aluminized Picture Tubes, Radio, TV and Special Purpose Electron Tubes and Semiconductor Products.

It is in the power-supply section that a high percentage of the troubles arise in auto radios. Mr. Silverstein lists three that he says affect 49 out of every 50 sets.

1. Bad rectifier.

Until just before 1950, the gaseous OZ4 tube was in general use; but since then the 6X4 vacuum tube has largely taken over (although OZ4's are still in use). Behavior of the 6X4, when it is going defective, is similar to that of other vacuum-tube rectifiers. It may become completely inoperative all at once, or the receiver volume may decrease gradually as the tube emission decreases. Intermittent conditions that persist are not frequently encountered. In the case of the gaseous rectifier, intermittent operation is more prevalent.

2. Bad vibrator.

The second item that is responsible for a high percentage of trouble is the vibrator. When it is operating, a mechanical buzz will be heard. This does not necessarily mean that the unit is functioning satisfactorily, because a buzzing vibrator can still be defective. On the other hand, when a vibrator does not buzz at all, then it is not operating. The trouble may lie in the vibrator, or the radio fuse may have blown so that no power is reaching the receiver. Common reasons for vibrator failure are: pitted points (which may tend to stick) or metal fatigue in the vibrating arms. Under these conditions, replacement with a new unit is the only desirable solution. Occasionally, a technician will try filing pitted points. This affords only temporary relief, and the unit will soon become defective again.

3. Defective buffer capacitor.

The third major source of trouble in auto-radio sets is the buffer capacitor across the secondary of the power transformer. The current drain of the car radio rises 20 per cent or more when this capacitor is bad, and the trouble may even cause the vibrator or the power transformer to fail or the fuse to blow. In replacing this buffer capacitor, use one having the same capacitance value. This particular precaution cannot be stressed too strongly because a capacitor of the wrong value can reduce the life of a vibrator by as much as 50 per cent. Also pay particular attention to the voltage rating of the buffer capacitor, and never install one of a lower rating.

A desirable check to run on every auto-radio receiver before it

leaves the shop is measurement of its current drain. This value should be within one ampere of the figure established by the manufacturer as normal. If it exceeds this limit, additional troubles exist in the set. Excessive current drain is not only detrimental to the car battery; but when the extra drain is through the power supply, the vibrator arms may lose temper and possibly stick. Bad buffer and electrolytic capacitors are the most frequent causes of excessive current through the power supply.

While we are on the subject of current drain, it should be noted that the current used by an auto radio goes through three circuits: the tube heaters, the vibrator power supply, and the dial lights. Excessive current drain may stem from any one of these paths; but the most frequent offender is the power supply or a circuit which draws current from the power supply.

While the three troubles outlined are responsible for most breakdowns of auto radios, they are not the only ones. For example, a common complaint is weak volume. For this, the most likely causes are a weak tube (or tubes) or an open or partially shorted antenna. To shield the auto receiver from the electrical disturbances generated in the motor and also to protect it physically, the entire receiver is encased in a metal container. This shield prevents reception of any signals except those which are brought in by the antenna. Consequently, an auto radio is much more dependent upon its antenna than a home radio, and any factor which interferes with or otherwise weakens this signal path will have a marked effect on speaker output. A car antenna is connected to the receiver through a low-loss lead — a very thin wire designed to reduce capacitance in this circuit. Excessive movement of this lead will frequently cause it to break. A continuity check between the antenna and the receiver

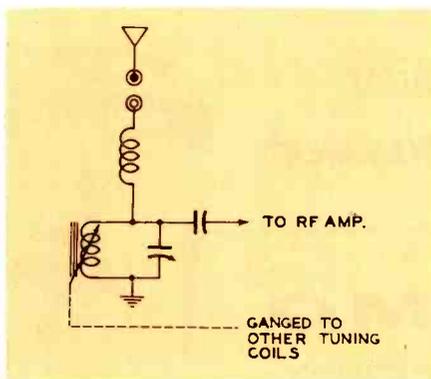


Fig. 6. The Antenna Input Circuit of Some Auto-Radio Receivers.

end of the cable will reveal any open circuit. An intermittent connection can also be uncovered by tapping the antenna and noting whether the ohmmeter needle is affected.

A continuity check between the antenna and the car chassis is also useful for uncovering short circuits. Before making this test inspect the circuit diagram to see whether the set has a low-resistance circuit connected between the antenna input and ground. See Fig. 6. If it does, remove the antenna plug from the set and make the same measurement. The circuit should be open.

For a quick method of localizing other troubles, the author suggests the old stand-by system of tube pulling. Start with the power-output stage, and remove the tube from its socket. If the stage is operative, a click will be heard in the loudspeaker. If a push-pull arrangement is employed, try both tubes. Then proceed to work back through the set, stage by stage, until you reach the point where a click does not appear. This is the section on which to concentrate.

There are additional troubles that may afflict a receiver. Intermittent operation is among the more common of these. Before the set is taken out of the automobile, make certain the trouble is not due to the antenna. Wiggle the antenna back and forth, and check to make sure that no intermittent grounding condition exists. Check the plug at the input terminal of the receiver to make certain that a good connection is being made. Poorly soldered connections or breaks may be found by moving the lead-in wire back and forth.

Once you are certain the trouble is not in the antenna system, the set may be removed from the car and taken into the shop where the search follows closely the procedure employed with home sets, except that there exists a greater possibility of broken connections or loose components because of the physical vibrations to which auto receivers are subjected.

Mr. Silverstein has chosen to concentrate only on those troubles which account for the majority of servicing of auto radios. Within these limits, the information is valuable; however, if extensive auto-radio service work is contemplated, additional reading along these lines would be advisable.

BY MILTON S. KIVER

Sangamo wire lead mica capacitors



Now packaged for your convenience!

Save time—do away with the cluttered mess of tangled wire leads. Use Sangamo Mica Capacitors, now mounted on space-saving cards.

These high quality mica capacitors are the finest available anywhere—at any price. They are fabricated with carefully selected premium grade India Ruby mica and are molded in Humidite for unequalled moisture resistance.

You can depend on these wire leads for completely trouble-free TV replacements.

Each card of five capacitors has rating and wvdc clearly marked. Each card shows the new RTMA Standards and the new MIL-C-5-A color code.

Stock up now—see your Sangamo distributor, or write us.

*High quality wire lead micas
for troublefree TV replacements*

SANGAMO
ELECTRIC COMPANY
MARION, ILLINOIS



Color TV Training Series

(Continued from page 8)

of determining whether or not the coil is functioning properly.

Fig. E2 of the Color Plate illustrates the appearance of the screen when the purity control has become open. With this control open, excessive current is allowed to flow through the purity coil. This current produces a very strong magnetic field around the coil. The central axis of the three beams is greatly displaced from the central axis of the tube by this strong magnetic force. As a result, the center of the raster moves away from the center of the screen and becomes greatly contaminated with color.

The circuit and control of the field-neutralizing coil is shown in Fig. 12-24. This circuit is used to obtain color purity at the edges of the screen. After a pure red

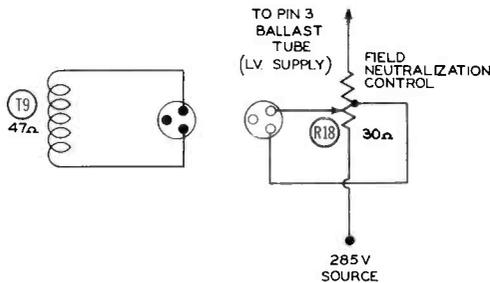


Fig. 12-24. Field-Neutralizing Coil and Control Circuit Used in RCA Model CT-100 Color Receiver.

screen (except at the edges) has been obtained during the setup procedure, the field-neutralizing control is adjusted to obtain purity at the edges. If this cannot be achieved, check the circuit in Fig. 12-24. If the voltage at the input of the circuit is correct, check the control and the coil for defects.

The electromagnetic type of picture tube employs neither a purity coil nor a field-neutralizing coil to obtain color purity. Instead, permanent magnets are used. The purity magnet, which is similar to the centering device used with some types of monochrome picture tubes, is placed around the neck of the tube. It has two rings which can be rotated when purity adjustments are made. If one or both of these rings loses its magnetism, correct purity cannot be achieved. The condition of the purity magnet is checked by direct replacement.

The field-neutralizing device in an electromagnetic tube consists of a series of permanent magnets mounted around the rim of the face plate of the picture tube. All the magnets can be positioned individually to obtain purity at the edges of the screen. A magnet should be replaced if very little or no effect is noticed when the position of that magnet is altered.

Convergence Troubles


Shown in Fig. 12-25 is the convergence circuit employed in the RCA Victor Model CT-100 color receiver. This circuit supplies the vertical and horizontal voltages used to obtain dynamic convergence of the beams.

Whenever it is noticed on the screen that the beams are not converging properly, the adjustments of the convergence controls should first be checked. The setup procedure for obtaining beam convergence was discussed in Part XI of the Color TV Training Series in the April 1955 issue.

By close examination of a monochrome picture on the screen, it can be determined in which portions of the screen the beams are misconverged. Shown in Fig. E3 of the Color Plate is one example of misconvergence. Notice that along a horizontal line through the center of the test pattern there is very little misconvergence. Along the top and bottom of the test pattern, it can be seen that the convergence is very poor. This is signified by color fringing on the edges of the black lines in these areas of the test pattern.

Fig. E4 of the Color Plate shows how the same condition appears when a white-dot pattern is being viewed. The dots in the horizontal center row are converged properly, but those in the vertical center row are not. By examination of the appearance of the screen, it can be determined that the cause of the trouble is in the vertical-convergence circuit. First, the controls for vertical amplitude and phase are adjusted. If this does not cure the trouble, then the circuit is checked. In the circuit of Fig. 12-25, a vertical-convergence amplifier is employed. This tube should be checked before other components are tested. If the tube is found to be good, the circuit can be checked by using an oscilloscope.

The waveform at the grid of the first half of V19 should be like that shown in Fig. 12-26. This is the pulse that is derived from the vertical-output stage. If the pulse is found to be abnormal at the first grid of the amplifier, check the circuit between this point and the point where the pulse is obtained at the vertical-output stage.

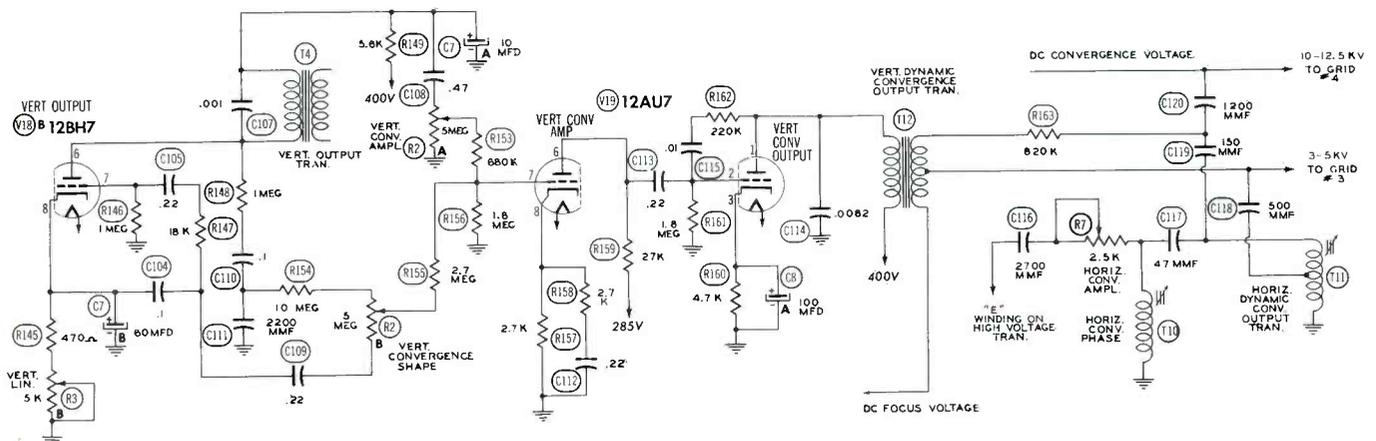

FREE 10-DAY TRIAL

**ON THE SYLVANIA TEST EQUIPMENT
OF YOUR CHOICE...**

then after you decide to buy

Pay as you earn!



▲ —Type 403 7" Television Service Oscilloscope—\$269.50
—incorporating advanced features of models priced much higher



◀ —Type 302 Deluxe Polypolymer—\$129.50
—stabilized against calibration errors due to changing line voltage

▶ —Type 620 New Tube Tester—\$149.50
—equipped to test 600 ma series string tubes as well as all other conventional tubes.



Experience without expense

Sylvania offers you an opportunity to experience the pleasure and profit of using high-quality test equipment, without being obligated to buy. Ask your Distributor to let you take the Sylvania Test Equipment you want back to your shop so you can use it for 10 days. If you're not completely convinced that your Sylvania Test Equipment is accurate and efficient to use, take

it back to your Sylvania Distributor. That's all there is to it.

Painless payment plan

If you decide to buy, your Sylvania Distributor will arrange easy payment terms. After a small down payment, you can take up to 18 months to pay on easy credit terms. Your new Sylvania equipment will bring extra profits which will more than pay for itself as you use it.

This offer is limited so see your Sylvania Distributor right away. He'll demonstrate the outstanding features of the Sylvania Test Equipment you need.

For the complete line of Sylvania Test Equipment you can buy on these new terms, write for the complete Test Equipment Brochure, Address Dept. E 35T.

Write for the
Complete Test Equipment Brochure

**SYLVANIA
ELECTRIC PRODUCTS, INC.**

Department E 31 T

1740 Broadway New York 19, N. Y.



SYLVANIA

Sylvania Electric Products Inc., 1740 Broadway, New York 19, N. Y.
In Canada: Sylvania Electric (Canada) Ltd., University Tower Bldg., Montreal

LIGHTING • RADIO • ELECTRONICS • TELEVISION • ATOMIC ENERGY

The waveform at the second grid of V19 should appear like that shown in Fig. 12-27. If it has been found that the signal is normal at the first grid but is abnormal at the second grid, the cause of the trouble is located between these two points. The defective component can then be located by making a voltage and resistance check. If the waveform at the second grid is found to be normal, the cause of the trouble is between this point and the output of the vertical-convergence circuit.

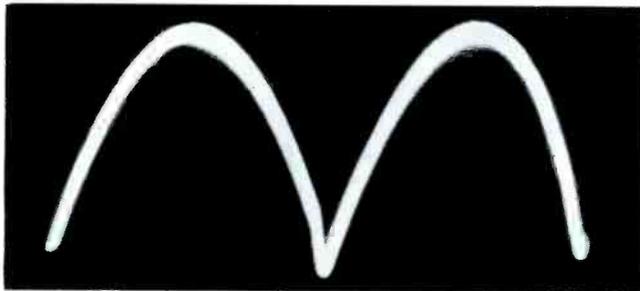


Fig. 12-26. Waveform of Signal at Pin No. 7 of V19 in Fig. 12-25.

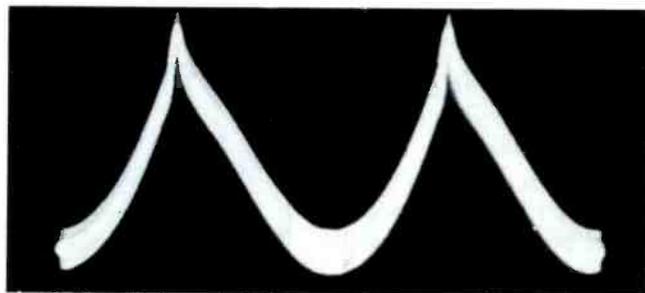


Fig. 12-27. Waveform of Signal at Pin No. 2 of V19 in Fig. 12-25.

Fig. E5 of the Color Plate shows the appearance of a test pattern when misconvergence is present in the horizontal direction. Notice that convergence of the beams is correct through the vertical center of the test pattern. On the left and right sides of the test pattern, convergence is very poor. This indicates that the horizontal dynamic convergence is not correct but that the vertical dynamic convergence is all right. The white-dot pattern for the same condition is shown in Fig. E6 of the Color Plate.

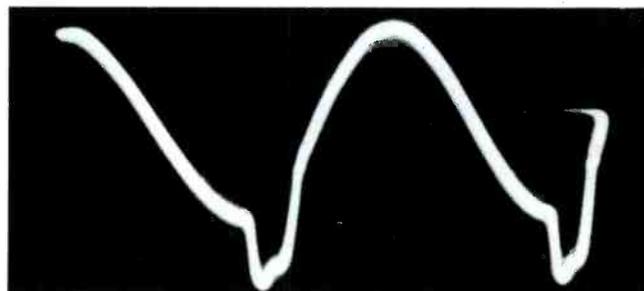


Fig. 12-28. Waveform of Signal at Junction of R7 and T10 in Fig. 12-25.

The convergence trouble is known to be in the circuit for horizontal convergence.

If it is not possible to obtain proper convergence in the horizontal direction by adjustment of the controls for horizontal amplitude and phase, check the appearance of the waveform at the junction of the horizontal-phase control T10 and the horizontal-amplitude control R7. This waveform should appear like the one in Fig. 12-28. If the waveform at this point is correct, the trouble is located after this point. If the waveform is incorrect, the trouble is located before this point.

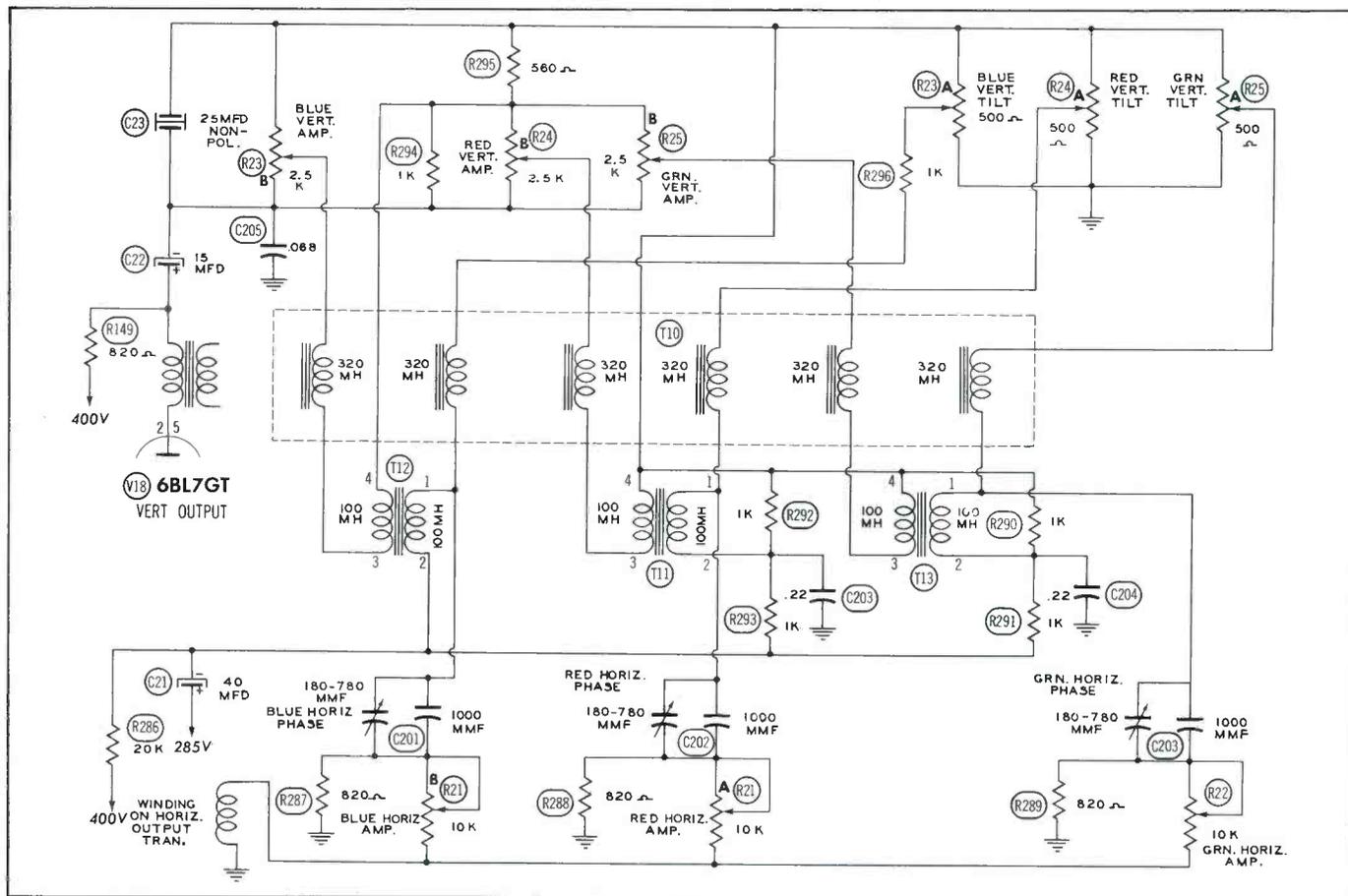


Fig. 12-29. Dynamic-Convergence Circuits Used in RCA Victor Model 21-CT-55 Color Receiver.

HOW TO MAKE MONEY IN HIGH FIDELITY WITH Jensen *Authentic* HIGH FIDELITY LOUDSPEAKERS



G-613 *Triaxial*



H-539 coaxial



H-520 coaxial



H-222 coaxial



K-310A coaxial



K-210 coaxial



PR-100 *Imperial*



RS-100
Laboratory Standard




TP-200 *TRI-Plex*



CT-100 *Concerto*



DU-500 TV *Duetto*

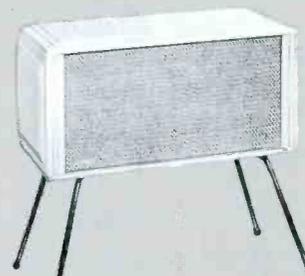

DU-300 *Duetto*
Treasure Chest

Have you been wondering how to **get in the High Fidelity business**—but find you can't compete under the established distribution and pricing system?

Now you *can* compete—at a Profit! If you are an established dealer, you can buy Jensen Authentic High Fidelity loudspeakers—the complete line—sell at prevailing prices and make a normal profit. You buy out of stocks in your area from a Jensen High Fidelity Wholesaler, selected for his experience and ability to help you with promotional material and sales counsel.

Why not **get the story now**—and be ready to get *your* share of the big high fidelity market? Just ask for "How To Make Money in High Fidelity"—on your letterhead, please.

Louis W Selsor

Louis W. Selsor
Distributor Sales Manager



DU-202
Duetto Portable



DU-201 *Duetto*

Jensen MANUFACTURING COMPANY 6601 S. Laramie, Chicago 38, Ill.
Division of The Muter Company • In Canada: Copper Wire Products, Ltd., Licensee

WORLD'S QUALITY STANDARD FOR MORE THAN A QUARTER CENTURY

Beam convergence in the electromagnetic type of picture tube is achieved through the use of electromagnets mounted around the neck of the picture tube. By control of the current through the coils associated with the electromagnets, the beams can be made to converge properly.

Shown in Fig. 12-29 is the dynamic-convergence circuit employed in the RCA Victor Model 21-CT-55 color receiver. The setup procedure for obtaining beam convergence in the electromagnetic type of tube was presented in Part XII of this Color TV Training Series in the May 1955 issue.

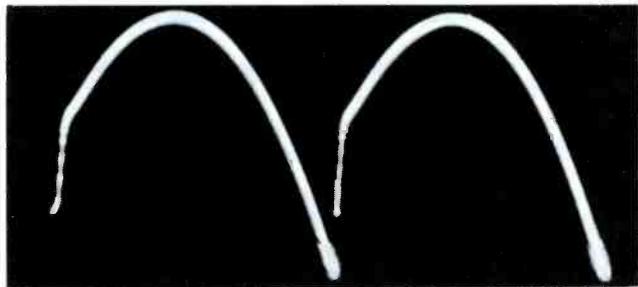


Fig. 12-30. Waveform of Signal at Junction of R149 and C22 in Fig. 12-29.

When trouble shooting the type of convergence circuit shown in Fig. 12-29, the same procedure should be followed as that for the convergence circuit used with the electrostatic type of picture tube.

If it is shown on the screen that misconvergence is present in the vertical direction only, the controls for vertical convergence are first adjusted to see if the trouble can be corrected. When making convergence adjustments, it must be remembered that a signal from a white-dot generator must be used.

If adjustment of the controls for vertical convergence does not cure the trouble, use the oscilloscope to make sure that the pulse from the vertical-output stage is being applied to the input of the circuit. This waveform, shown in Fig. 12-30, can be observed at the junction of R149 and C22 in the circuit of Fig. 12-29.

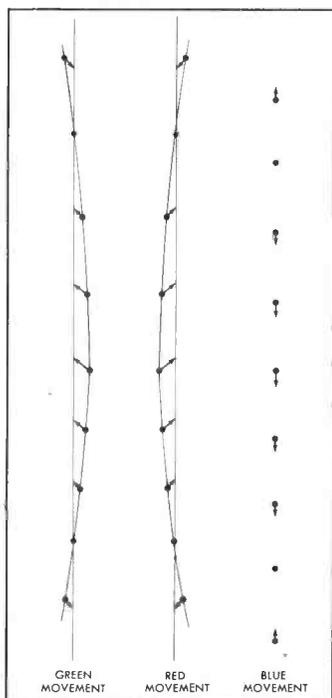


Fig. 12-31 Dot Movements Caused by Adjusting the Vertical-Amplitude Controls.

In the circuit of Fig. 12-29, there is associated with each convergence coil a control for vertical amplitude and one for vertical tilt. By adjusting each control while observing a dot pattern on the screen, the technician can determine which portion of the circuit is not functioning properly. Fig. 12-31 shows the directions in which the vertical center rows of dots should move when the amplitude controls are adjusted. Fig. 12-32 shows the directions in which the dots should move when the tilt controls are adjusted. When it has been determined which control is not functioning properly, a voltage and resistance check of the circuit associated with that particular control should reveal the cause of the trouble.

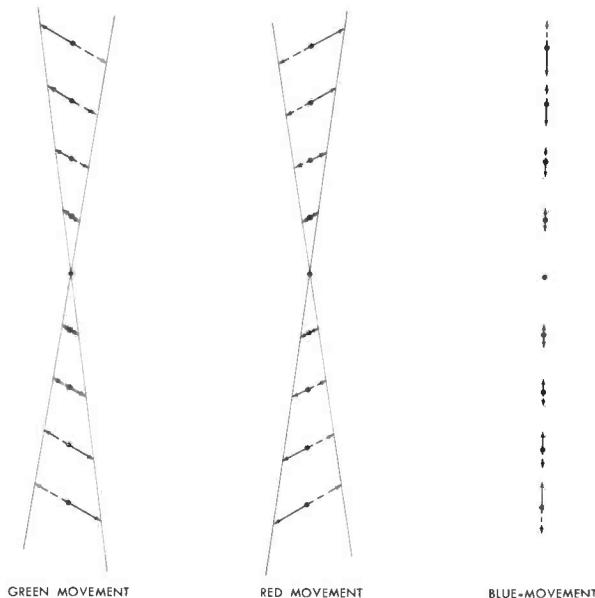


Fig. 12-32. Dot Movements Caused by Adjusting the Vertical-Tilt Controls.

If the beams are misconverged in the horizontal direction but are properly converged in the vertical direction, only the horizontal-convergence circuit needs to be checked. The same trouble-shooting procedure as that for the vertical-convergence circuit can be followed. First, make sure that the horizontal pulse from the horizontal-output transformer is being applied to the convergence circuit. Associated with each convergence coil, there is a control for horizontal amplitude and one for

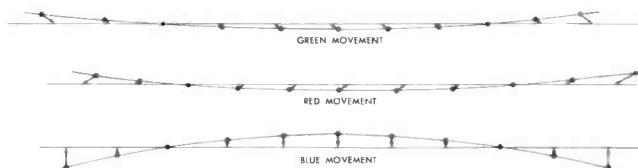


Fig. 12-33. Dot Movements Caused by Adjusting the Horizontal-Amplitude Controls.

horizontal phase. The directions in which the dots should move when the controls for horizontal amplitude are adjusted are shown in Fig. 12-33. If the dots do not move correctly when a control is adjusted, a voltage and resistance check of the circuit associated with that particular control should reveal the cause of the trouble.

In order to give the reader an opportunity to test himself on the material in this issue, we are including on the insert a few questions that are answered in this discussion.

C. P. OLIPHANT

BLACK AND WHITE TV

COLOR TV

TRANSISTOR RADIOS
FM RADIOS

AM RADIOS

AMPLIFIERS AND TUNERS
AUTO RADIOS

RECORD CHANGERS



WHAT'S YOUR SERVICE PROBLEM?

PHOTOFACT HELPS YOU SOLVE IT

FASTER, EASIER, BETTER, MORE PROFITABLY!

**THE WORLD'S
FINEST SERVICE DATA**



THESE GREAT FEATURES ARE EXCLUSIVE IN PHOTOFACT—THEY HELP YOU EARN MORE DAILY, HELP INSURE CUSTOMER SATISFACTION

PHOTOFACT Service Data is the *only* service information based upon first-hand examination of the actual production-run receivers and equipment. It is authentic, uniform data developed through actual study and analysis by service engineers in the Howard W. Sams Laboratories. PHOTOFACT is the *only data* prepared from the practical point of view of the Service Technician.

Thousands of Service Technicians use PHOTOFACT daily for time-saving, profit-boosting service operations. If you've never used PHOTOFACT, you've never realized your full earning power—you've never given such complete customer satisfaction. So get the proof for yourself. Try PHOTOFACT—use it on any job. Your Parts Distributor has the Folder Sets you need for any of the 17,000 TV and radio receivers, changers, recorders, etc., covered in PHOTOFACT. Once you use this great service, we know you'll want the complete PHOTOFACT Library.

EASY-PAY PLAN TO FIT YOUR BUDGET

Ask your PHOTOFACT Distributor . . . he'll show you how you can now own the PHOTOFACT Library through a unique Easy-Pay Plan that exactly fits your needs. Pays for itself as you EARN MORE.

IT'S EASY TO SOLVE YOUR SERVICE PROBLEMS

See the PHOTOFACT Cumulative Index, page 88 and following

It is your guide to virtually any model ever to come into your shop; helps you locate the proper PHOTOFACT Folder you need to solve any service problem on any model. Once you have the make and chassis number, it takes just 60 seconds to find the applicable PHOTOFACT Folder.

Get the required Folders from your parts distributor and you are all set for faster, easier, better, more profitable work.

HOWARD W. SAMS & CO., INC. • Indianapolis 5, Indiana

FULL SCHEMATIC COVERAGE

1. Famous "Standard Notation" uniform symbols are used in every schematic.
2. The same standard, uniform layout is used for each schematic.
3. Diagrams are clear, large, easy to read, easy to handle.
4. Wave forms are shown right on the TV schematics for quick analysis by 'scope.
5. Voltages appear on the schematics for speedy voltage analysis.
6. Transformer lead color-coding is indicated on the schematic.
7. Transformer winding resistances appear on the schematic.
8. Schematics are keyed to photos and parts lists.

FULL PHOTOGRAPHIC COVERAGE

9. Exclusive photo coverage of all chassis views is provided for each receiver.
10. All parts are numbered and keyed to the schematic and parts lists.
11. Photo coverage provides quicker parts identifications and location.

ALIGNMENT INSTRUCTIONS

12. Complete, detailed alignment data is standard and uniformly presented in all Folders.
13. Alignment frequencies are shown on radio photos adjacent to adjustment number—adjustments are keyed to schematic and photos.

TUBE PLACEMENT CHARTS

14. Top and bottom views are shown. Top view is positioned as chassis would be viewed from back of cabinet.
15. Blank pin or locating key on each tube is shown on placement chart.
16. Tube charts include fuse location for quick service reference.

TUBE FAILURE CHECK CHARTS

17. Shows common trouble symptoms and indicates tubes generally responsible for such troubles.
18. Series filament strings are schematically presented for quick reference.

COMPLETE PARTS LISTS

19. A complete and detailed parts list is given for each receiver.
20. Proper replacement parts are listed, together with installation notes where required.
21. All parts are keyed to the photos and schematics for quick reference.

FIELD SERVICE NOTES

22. Each Folder includes time-saving tips for servicing in the customer's home.
23. Valuable hints are given for quick access to pertinent adjustments.
24. Tips on safety glass removal and cleaning.

TROUBLE-SHOOTING AIDS

25. Includes advice for localizing commonly recurring troubles.
26. Gives useful description of any new or unusual circuits employed in the receiver.
27. Includes hints and advice for each specific chassis.

OUTSTANDING GENERAL FEATURES

28. Each and every PHOTOFACT Folder, regardless of receiver manufacturer, is presented in a standard, uniform layout.
29. PHOTOFACT is a *current* service—you don't have to wait a year or longer for the data you need. PHOTOFACT keeps right up with receiver production.
30. PHOTOFACT gives you *complete* coverage on TV, Radio, Amplifiers, Tuners, Phonos, Changers.
31. PHOTOFACT maintains an inquiry service bureau for the benefit of its customers.

HELPS YOU EARN MORE DAILY

Troubles in Video IF and Detector Systems

(Continued from page 31)

the pattern given in the alignment instructions.

The IF strip should always be clamped with a negative 3-volt battery for these checks. By always clamping the AGC at -3 volts, by always setting the gain control of the oscilloscope at the same point, and by adjusting the output control of the signal generator to produce a pattern of the same height, a basis for obtaining a relative-gain characteristic is reached. That is to say, by noting the difference between the settings of the output control of the signal generator, a relative-gain reading can be obtained. The gain of different IF strips will vary; but after checking several strips, the permissible range of this variation will become apparent.

When replacing a crystal detector, the technician must make sure that it is connected in the proper polarity. The crystals are coded to show the polarity of voltage that should be applied to the terminals in order to obtain maximum current flow. The cathode end of a germanium crystal may be painted green or marked with a negative sign (-). The anode terminal will be coded with a positive sign (+) or in some cases with no marking at all. When the crystal is schematically illustrated, the anode is shown as an arrowhead and the cathode as a bar.

In order to establish a reference for the photographs showing the various trouble symptoms, a normal test pattern is illustrated in Fig. 3.

Common Symptoms

1. Raster, No Picture, and No Snow.

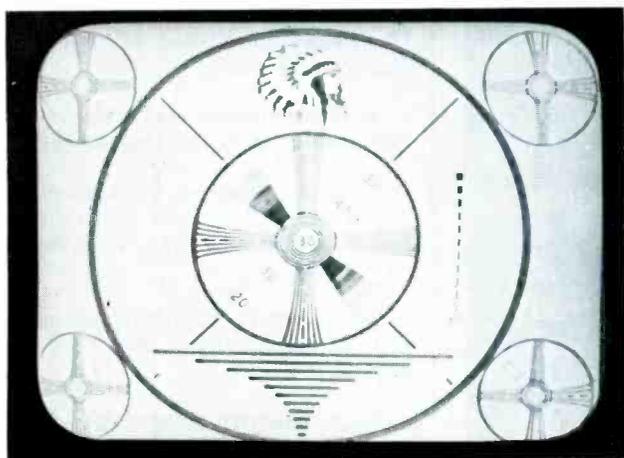


Fig. 3. Normal Test Pattern.

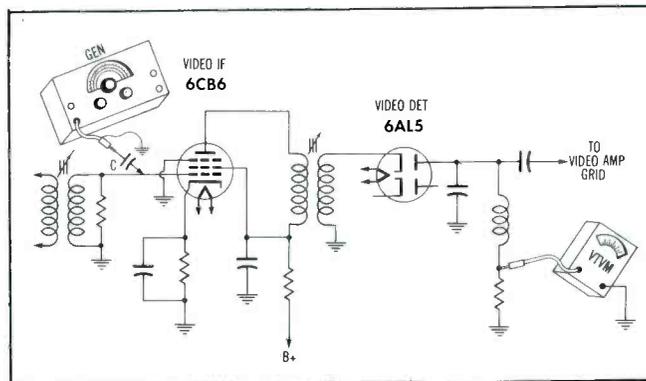


Fig. 5. Setup for Checking Operation of Last Video IF Amplifier and Video Detector.

Fig. 4 shows the condition in which there is a raster on the screen but there is no video signal nor snow reaching the picture tube. This symptom and the loss of sound in receivers employing an intercarrier sound system may be caused by an inoperative video IF or video-detector stage. In the split-sound type of receiver, a trouble in the video IF section may not affect the sound; and the sound can be used as a guide for tuning in a strong operating channel. When the sound is normal in any receiver, it is a good indication that the RF and IF stages up to the sound take-off point are operating.

In the process of isolating the trouble to a certain section of the receiver, the obvious symptoms can often aid in pin-pointing the fault. The absence of snow in the raster usually indicates that the trouble exists somewhere after the mixer stage; however, in a few cases, a faulty tuner could also produce this condition.

In rare instances, receivers of the intercarrier type will produce weak sound with no picture when the trouble is in the video IF or video-detector stages. A small portion of the combined video and sound carriers will be coupled through the defective stage, and the small amount of the

4.5-mc beat frequency developed at the detector will be sufficient to produce some sound from the speaker even though the video frequencies will be too low in amplitude to produce a picture. When trouble shooting for a dead video IF or video-detector stage, the signal-substitution method can prove very helpful. The use of a VTVM and of a signal generator which has an output in the IF range of the receiver can quickly isolate the defective circuits.

The VTVM is placed across the detector load resistor, and the output from the signal generator is connected to the grid of the last video IF amplifier in the manner shown in Fig. 5. By varying the generator frequency through the IF range of the receiver, a frequency will be found that will produce a reading on the VTVM. This reading will be of a relatively low DC voltage of either polarity.

If the signal is able to pass through the last IF stage, the other stages can then be checked by applying the generator signal to the grid of each preceding stage. In some cases, the defective stage may not lie in the IF strip; consequently, a further check of the video-detector circuit is necessary. Trouble in this stage can be located by injecting a strong signal

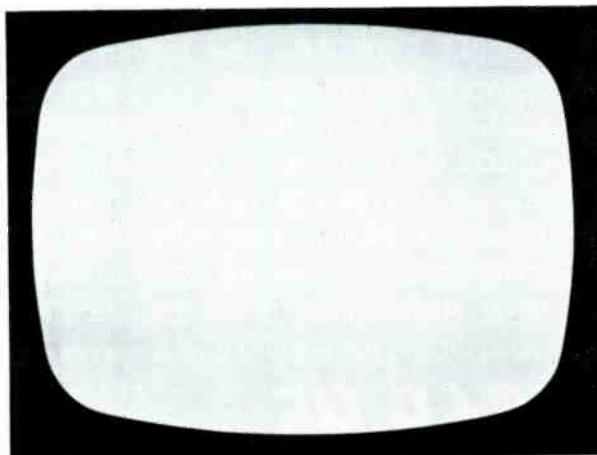


Fig. 4. Raster, No Picture, and No Snow.

your KEY
TO EXCELLENCE

phastron

"777"

NEW!



The MODEL "777" VTVM is a completely self-contained, ready-to-use test instrument. Its accessories and the HF co-ax cable, DC Probe, AC line cord and instruction book all fit in the genuine California Saddle Leather carrying case that is furnished with the instrument.

- ✓ 42 UNDUPLICATED RANGES
- ✓ ILLUMINATED DIAL (5000 hour self-contained lamps)
- ✓ DIE CAST CHROME FINISHED BEZEL
- ✓ METAL CASE—unbreakable, ultra compact
- ✓ DOUBLY SHIELDED, time proven 200 microamp movement
- ✓ PERMANENT ACCURACY . . . 3% DC, 5% AC
- ✓ LARGE, EASY TO READ SCALES 4-7/8" LONG
- ✓ COLOR CODED SCALES: green-ohms; black-AC, DC; red-P. to P.
- ✓ 2 ZERO CENTER SCALES for FM DISCRIMINATOR ALIGNMENT
- ✓ SEPARATE RANGE and FUNCTION SWITCHES
- ✓ ONLY 2 JACKS for ALL MEASUREMENTS
- ✓ NEW HIGH STYLE, EASY-TO-USE CHROME BAR KNOBS
- ✓ DUAL PURPOSE HANDLE also serves as AC line cord reel

\$69.95

"777" VTVM complete with
Coaxial Cables DC Probes and Leather Case
at your PARTS DISTRIBUTOR

PHASTRON COMPANY • 151 PASADENA AVE. • SOUTH PASADENA, CALIF., U.S.A.

from the generator into the receiver at the input to the detector and by observing the indication on the VTVM.

If the signal generator can be internally modulated at 400 cycles or some other audio frequency, a pattern of horizontal bars will appear on the picture-tube screen and the VTVM can be eliminated. The bars serve as an indication of proper operation for each stage tested. A sweep generator can also be used in conjunction with an oscilloscope to isolate a dead video IF stage. First connect the oscilloscope across the video-detector load, and then inject the signal from the generator into each stage, as described in the signal generator and VTVM method. The IF response curve will appear on the scope if the stage under test is functioning.

In the majority of television receivers in the field today, there is little trouble with the video-detector stage, except for tube failure. The reason for this is the fact that in most designs no high supply voltages are required for this circuit, and longer life for the components usually results. Crystal diode detectors, however, are being used to a great extent in many of the new vertical-chassis TV receivers. These crystals are sensitive to heat and moisture; and when one is defective, it may produce an intermittent condition or a complete loss of sound and picture.

Possible causes for a raster with no picture and no snow are:

- a. Tube failure.
- b. Shorted plate and screen decoupling capacitor. (See C35, C39, C41, or C3B in Fig. 1; C26, C31, C40, or C44 in Fig. 2.)
- c. An open decoupling resistor or one of too high a value. (See R28 or R31 in Fig. 1; R26, R30, R36, or R42 in Fig. 2.)
- d. Short circuits caused in video IF stages by pieces of solder or foreign material.
- e. Tube pins not making good contact with their respective sockets.
- f. Open coupling capacitors between video IF stages or to the detector stage. (See C28, C35, or C43 in Fig. 2.)
- g. An open primary or secondary of an IF transformer. (See L18, L19, or L20 in Fig. 1.)
- h. A defective crystal detector.
- i. Shorted bypass capacitor in B+ line.

j. Shorted or leaky coupling capacitor. (See C28, C35, or C43 in Fig. 2.)

k. Open cathode resistor in a video IF stage. (See R26, R30, or R33 in Fig. 1; R25, R29, R34, or R41 in Fig. 2.)

The most common cause of failure in the video IF section is a defective tube. Shorted elements in a tube will often affect other circuit components. In the case of a shorted plate or screen grid within a tube, the decoupling resistor of the stage may become overheated and it may open or increase in value. In a few receivers, heater-to-cathode leakage in the first IF stage may result in no picture, no sound, and no hum bars.

In some strong-signal areas, an open IF transformer or coil will produce a weak picture and a slight amount of sound; however, the same trouble in a weaker-signal area will result in the complete loss of both picture and sound.

The coupling capacitor from the last IF stage to the video-detector input may become leaky because of the B+ voltage present on the IF amplifier plate. This leakage may upset the proper functioning of the detector stage and result in a loss of the video signal.

Crystal detectors may develop a low output because of a change in the ratio between the forward and backward resistance. If a germanium diode becomes defective but it is still able to produce a picture, the picture will have a washed-out appearance and the contrast control will have little or no effect. One quick check of this type of detector is a resistance reading across the disconnected crystal. If the test prods are placed with the proper polarity across the unit, a

reading in excess of 10K ohms is normal. By reversing the test prods, a decreased reading that is usually less than 500 ohms should result. If reversal of the test prods reveals no great difference between the two readings, the crystal should be replaced.

2. Snowy Picture.

A snowy picture with weak or noisy sound is caused by a loss of signal amplification in stages that precede the sound take-off point. A test pattern that contains snow content is shown in Fig. 6.

In order to receive weak signals with a minimum of snow, it is very necessary to utilize the maximum available gain of both the IF and tuner sections. Generally speaking, when a snowy picture with weak or noisy sound is caused by trouble within the IF section, it will be more noticeable on the weak signals. This is true since the AGC voltage applied to the IF strip is much higher when the set is receiving a strong signal; thus the IF strip is prevented from operating at maximum gain. The IF strip is not allowed to operate at maximum gain on strong signals because this would cause severe overloading, and distortion of the signal would result.

In receiving a strong signal such as one from a local station, a serious loss of signal amplification in a stage of the IF strip usually causes a degraded picture rather than a snowy one.

Possible causes of a snowy raster with weak or noisy sound are:

a. Defective video IF or detector tubes.

b. Defective detector crystal (if used).

c. Open plate coils in IF stages. (See L18, L19, L20 in Fig. 1; L9, L11, L14, L15 in Fig. 2.)

d. Low plate or screen voltage applied to IF tubes.

e. Open screen-grid bypass capacitors. (See C35, C39, C41 in Fig. 1; or C26, C31, C40, C44 in Fig. 2.)

f. Open cathode-bypass capacitors. (See C42 in Fig. 1; or C32, C45 in Fig. 2.)

g. Open RF bypass capacitor (detector filter network). (See C44 in Fig. 1; or C51 in Fig. 2.)

h. Open input grid coil. (See L8 or L13 in Fig. 2.)

i. Excessive AGC voltage applied to IF strip.

Remember that, in receivers which employ a split-sound system and in which the sound (as well as the picture) is affected, the trouble is located in one of the stages that precede the sound take-off point.

An investigation of the alignment and relative gain (as discussed) can be very helpful in restoring the gain of the receiver. In any alignment procedure, the tubes should be checked and all defective and weak ones should be replaced. All voltages should be normal before the alignment procedure is started.

3. Ringing in Picture.

The distortion that is evident in the picture illustrated in Fig. 7 represents either a severe case of ringing or a condition in which there are multiple images produced by a faulty video IF circuit. A distortion of this nature should not be mistaken for ghosts produced by any condition

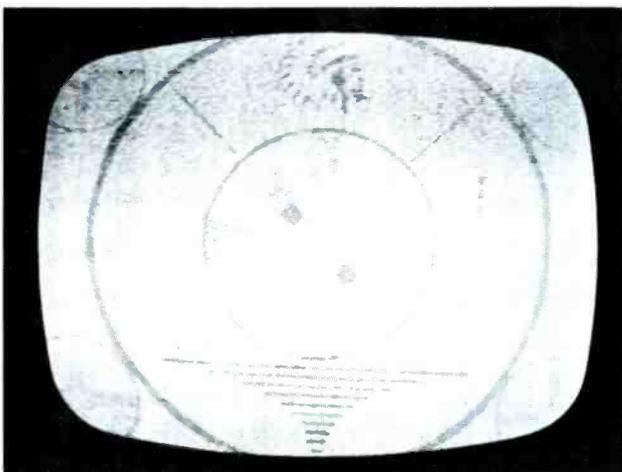


Fig. 6. Snowy Picture.

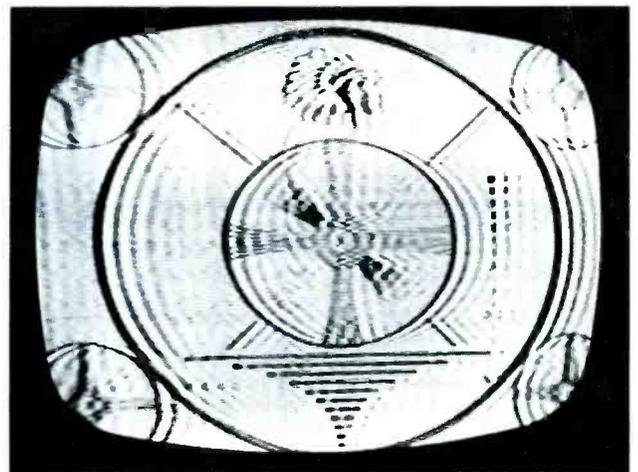


Fig. 7. Ringing in Picture.

Here's a pair
You can bet on!



ROTOR QUEEN

ANTENNA ROTATORS

Exclusive! Signal Pilot Light
(ON during operation,
DIMS near end of rotation)

Model R-55 1995 LIST
LOWEST PRICE
QUALITY ROTATOR ON
THE MARKET TODAY

Model M-55 2665 LIST
SAME SUPERIOR QUALITY AS
R-55 WITH ADDED DELUXE
• Directional Meter Indicator

OPTIONAL!
Model TB-2
Universal
Thrust Bearing
\$4.95 List

POWERFUL RMS
CONSUMER ADVERTISING
WORKS FOR YOU!
FREE mats
on request.

RMS
RADIO
MERCHANDISE
SALES, Inc.
New York 62, N. Y.

DEAL YOURSELF . . .
NEW CUSTOMERS . . .
FASTER SALES . . . BIGGER PROFITS

with this winning pair of Rotor Queens. Both models feature the latest engineering advances, and are designed to satisfy the most demanding requirements of ALL your customers. They assure the sharpest, clearest pictures on every TV channel for every home.

ONLY the RMS ROTOR QUEEN gives
you all these quality features!

- Instant braking action
- Full 370 degree rotation, right or left
- Direct gear drive for high torque—no worm gears
- Step-down transformer . . . safe 24 volts to drive unit
- Lifetime oilite bronze side thrust bearing
- Die-cast zinc weather sealed housing
- Flagpole type base for easy installation
- Guy wire supports • All parts rustproof
- Full 1 year RMS guarantee against defective workmanship and materials.

ORDER TODAY and watch the chips roll in!

LOOK for the RMS man for your best buy in
Outdoor Antennas • Indoor Antennas • Rotors • Intercoms • TV Antenna Accessories.

external to the receiver. When a trouble within the receiver causes ringing, it should be noticed that the images will appear equally spaced from one another and weaker as they depart from the normal pattern. These multiple images will usually be affected by changing the position of the fine-tuning control. If the control is varied, the images may increase or decrease in number and change from a negative to a positive picture, or vice versa.

Because of the use of high-gain amplifier tubes in the video IF section, only a small amount of stray coupling between stages is sufficient to produce trouble. Coupling between the grid and plate leads can easily produce instability and in some cases can produce oscillation which results in picture ringing.

Misalignment in the video IF section is one of the most common causes that produce ringing in the picture; however, if a receiver is found to be out of alignment, this situation may be a result of some defective component. If the AGC or B+ voltages applied to the video IF stages are not at the proper level, the alignment will appear to be off. It is recommended that a thorough and complete trouble-shooting process should be undertaken before receiver alignment is attempted.

Possible causes of ringing in the picture are:

- Defective tube in the video IF section.
- Misalignment.
- Improper placement of the leads or components in the video IF stages.
- Open IF plate and screen decoupling capacitor. (C35, C39, or C41 in Fig. 1; C26, C31, C40, or C44 in Fig. 2.)
- Shorted AGC filter capacitor. (C38 in Fig. 1 or C34 in Fig. 2.)
- Defective video IF transformer.
- An open cathode bypass capacitor in one of the video IF stages. (C42 in Fig. 1; C32 or C45 in Fig. 2.)
- Improper shielding of the IF and detector stages.
- Defective filament-bypass capacitor. (C36, C40, or C43 in Fig. 1; C27, C33, C41, C46, or C50 in Fig. 2.)

The RC decoupling network in each IF stage isolates each amplifier from the effects of the other stages

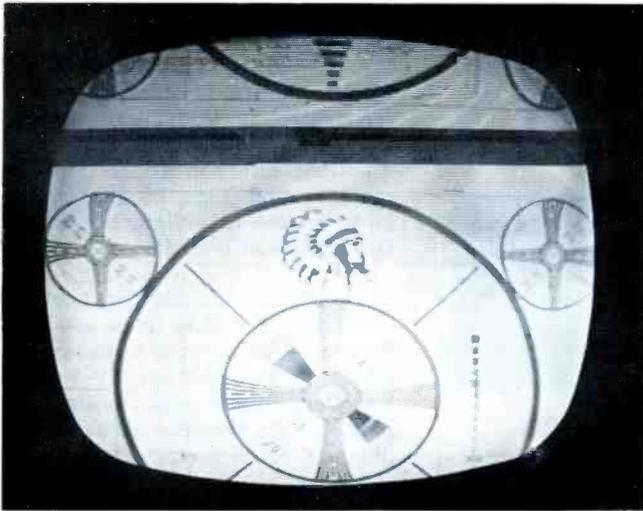


Fig. 8. Poor Vertical Synchronization.

by eliminating direct connections through the B+ line to the other stages. An open bypass capacitor in either the cathode or screen circuit of an IF stage is capable of producing regeneration or ringing with an accompanying decrease in signal strength. In cases of this kind, the fine-tuning control tends to have little effect on the tuning of the sound signal. A shorted AGC filter capacitor will produce ringing, but it is generally accompanied by an overloading condition which may also disrupt the synchronization. Many receivers employ tube shields for the IF and detector stages and for the IF circuitry under the chassis. If these shields are not in place or grounded properly in an overly critical IF strip, ringing may result.

If any component is replaced in the video IF section, the physical position and lead dress for each wire should be carefully noted. Keep all leads as direct and as short as possible, unless a special lead dress is plainly called for in the original circuit design. By following these

servicing hints when replacing a component, such as an IF transformer, a troublesome ringing condition may be prevented.

4. Poor Vertical Synchronization.

Problems concerning vertical synchronization are usually associated with the sync and vertical-oscillator sections. Some of these troubles can, however, be traced to the IF system. When such is the case, it will usually be noted that the receiver has a tendency to synchronize in such a way that the sync bar shows on the screen or the receiver has a tendency to trigger on noise pulses. In Fig. 8, a test pattern with a visible sync bar is shown. Notice also that the contrast is somewhat weak.

Possible causes of poor vertical synchronization are:

- a. Hum modulation caused by heater-to-cathode leakage in an IF tube.
- b. Low plate or screen voltage applied to an IF stage.

c. Low bias applied to an IF stage.

d. Open screen-grid bypass capacitor. (See C35, C39, C41 in Fig. 1; C26, C31, C40, C44 in Fig. 2.)

e. Overloading caused by excessive signal applied to a stage.

f. Gassy tubes.

Hum caused by heater-to-cathode leakage in an IF amplifier tube can produce a loss of synchronization because the hum has the same frequency that the vertical-sync signal has. This type of trouble most often affects the vertical synchronization; but when the hum is severe enough, it can cause a loss of horizontal synchronization as well.

A low value of plate or screen voltage applied to an IF stage would have the same effect on a strong signal that a low value of bias would have. That is to say, a strong signal would overdrive a stage if the stage were operating with low bias, low plate voltage, or low screen voltage. This overdriving action by the large signal may cause distortion or complete elimination of the sync pulses.

Open screen-bypass capacitors can cause poor vertical synchronization because, in cases where the screen-grid bypass capacitor is open, a signal is present on the screen grid. This signal has a degenerating effect on the plate signal and can cause distortion in the sync-pulse portion of the video signal.

By causing a stage to have excessive gain, a gassy tube can be the source of sync trouble. This excessive gain within one stage can amplify the signal to such magnitude that a following stage is overloaded. This signal overloading can cause compression of the sync pulses.

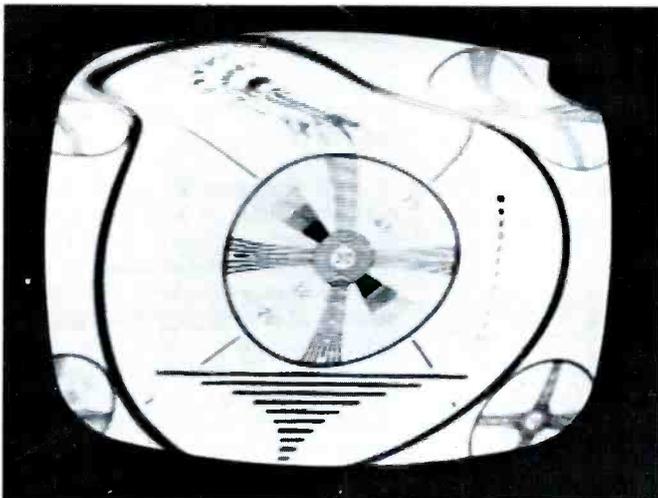


Fig. 9. Pulling in Picture..



Fig. 10. Pulling in Picture With Brightness Modulation.


Dealers

PROMOTE

Plus Profits

with

AMPHENOL

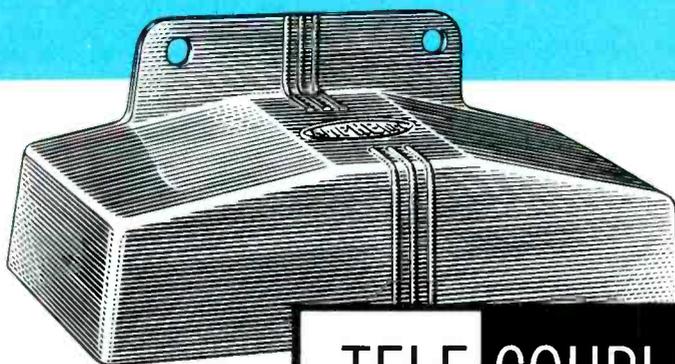

TELE-COUPPLERS

Are you a dealer in television sets? If you are you have already spotted the trend toward the two set family. *You can promote plus profits on the sale of the second set with AMPHENOL Tele-Couplers!* These small accessories effectively couple two, three or four tv sets to a single antenna lead-in. Tele-Couplers are easy to sell for they save the customer the expense of an additional antenna installation.

To help you merchandise Tele-Couplers AMPHENOL has prepared an attractive counter display carton containing 12 Tele-Couplers. On your counter this display may help stimulate your customers into the purchase of that second tv set! A small folder describing the Tele-Couplers is also available—to give additional facts and to give additional impetus to your sales of tv and AMPHENOL Tele-Couplers.

114-088 2 Set Tele-Coupler List \$3.75
114-090 4 Set Tele-Coupler List 5.75



See Your Amphenol Distributor!

AMPHENOL

5. Pulling in Picture.

A pulling or horizontal bending of the picture is encountered very frequently in television servicing. The photograph of Fig. 9 illustrates a pulling effect near the top of the picture, and Fig. 10 represents a severe case of pulling accompanied by brightness modulation.

Picture pulling or horizontal bending can result from any one of a number of defects in several different sections of the TV receiver; however, this discussion deals primarily with troubles situated in the video IF and detector stages.

Two checks are useful in isolating a defect which is causing picture pulling or raster bending. First, observe the edge of the raster by using the centering mechanism to bring it into view. If there is no bending in the raster, the defect is ahead of the horizontal oscillator. In those sets in which the sync take-off point is after the stage employing the contrast control, the amount of picture pulling will vary when the contrast control is varied. If the setting of the contrast control is decreased and if the pulling tends to decrease, the trouble is probably in the video IF section or in the tuner. If the pulling tends to increase, the trouble is in the sync stages or in the video amplifier.

Another symptom which often occurs with picture pulling is brightness modulation. This modulation will appear as a dark area horizontally across the screen. This dark hum bar which may accompany picture pulling usually indicates a defective tube. One of the more common causes of this type of distortion is heater-to-cathode leakage in the RF or IF tubes. The presence of the 60-cycle voltage in the video signal usually results in brightness modulation; however, if only one tube has a very slight amount of leakage, the picture may tend to pull but the modulation will not always be noticeable on the screen.

If the trouble is not due to a defective tube, it will be necessary to remove the chassis from the cabinet in order to determine the reason for the picture pulling. In some instances, unstable vertical synchronization will accompany the pulling condition. This often indicates that the receiver has a poor low-frequency response. In order to make a quick check of the low-frequency response, turn up the brightness control and adjust the vertical-hold control until the vertical-blanking signal appears on the screen of the picture tube. The

vertical sync pulse should be darker than the darkest portion of the picture. If it is not, the sync pulses are too low in amplitude because of poor low-frequency response or the signal is being limited somewhere in the video section.



Fig. 11. Horizontal Blanking Pedestal and Sync Pulse. (A) Normal; (B) Distorted Because of Poor Low-Frequency Response.

The waveform shown in Fig. 11A represents a normal horizontal blanking pedestal and sync pulse. The waveform in Fig. 11B shows the distorted shape of the same signal after passing through an amplifier having a poor low-frequency response. The sync pulse is usually completely lost, and the horizontal oscillator will attempt to synchronize to the leading edge of the blanking pedestal. This condition is often accompanied with poor vertical synchronization because the loss in low-frequency response will also affect the vertical sync pulses. Before attempting any video IF alignment, the adjustment of the local oscillator should be checked to make sure that the picture carrier is properly situated on the video IF response curve.

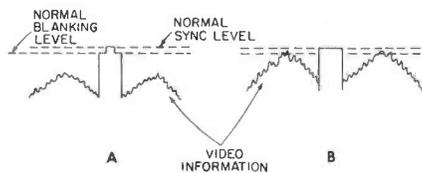


Fig. 12. Composite Video Signal. (A) Normal; (B) Sync Pulse Missing Because of Clipping Action.

Another form of distortion in the horizontal-sync pulse is shown in Fig. 12. A normal video signal in Fig. 12A illustrates the correct sync-pulse amplitude with respect to the video information. Fig. 12B represents the signal after it has undergone a limiting or clipping action in the last IF amplifier or in the video-output stage. In the latter drawing, the top of the sync pulse has been clipped; however, the video information has been amplified and some portions reach the same level as the sync pulses. Under these conditions, the video information tends to trigger the horizontal oscillator and severe picture stretching often occurs.

Excessive gain in the video IF stages may be caused from a defective

TACO TRAPPERS



FAST
Positive tension booster design



DRY-CLEANED
No greasy hands or clothing

MAKE YOUR JOB PROFITABLE

RESULTS — Excellent gain for better pictures on all channels.	SHARP — Trappers eliminate unwanted signals, give higher signal-to-noise level.	BROAD — Patented phase reversing traps for better response —black and white or color.	RUGGED — Tops in ruggedness. Finest aluminum alloy, shock absorbers and fiberglass used in all Trappers.

In every respect, Taco Trapper antennas make your job easier and more profitable. Streamlined, modern design plus extra features save you time, trouble and give greater user acceptance.

These Trapper designs were originated and patented by Taco engineers.* Improved Staying-Power, so important in distorted signal areas, is derived from multiple driven elements and Penta-Phase tuning.

Stacking lines, close spaced and wide spaced, are available to meet any area requirement. Use a Trapper for that next installation and find out for yourself, how much easier and more profitable your work can be.

*U. S. Patent 2,705,283

1890 SUPER TRAPPER
A superior 1/2" element design for fringe to wide-fringe installations.

1880 TRAPPER
An efficient 3/16" element design for medium to fringe area installations.

1870 TRAPPER

870 TRAPPER JR.
A compact 3/8" element design for attic or prime service installations.

*Working elements on low-band and high-band

TECHNICAL APPLIANCE CORPORATION • SHERBURNE, N. Y.
In Canada: Hackbusch Electronics, Toronto 4, Ont.

SAVE WITH THE NEW



ERIE
DISC and GP
CERAMICON®
Kits

ORDER
Now
 from your
ERIE
DISTRIBUTOR

Here's **WHAT YOU GET**

- 1** 100 High Stability ERIE Disc or Tubular Ceramicons
- 2** 18 Popular Values
- 3** Handy, Convenient 18 Section Plastic Storage Case
- 4** Exceptional Value

Here's **WHAT YOU SAVE**

REGULAR PRICE

100 ERIE Disc or Tubular
 Ceramicons \$15.00

18 Section Plastic Case 1.75

Total Value \$16.75

YOU PAY \$10.65

YOU SAVE \$6.10

ERIE
electronics

ERIE ELECTRONICS DISTRIBUTOR DIVISION
ERIE RESISTOR CORPORATION
 Main Offices: ERIE, PA.
 Factories: ERIE, PA. • LONDON, ENGLAND • TRENTON, ONTARIO

AGC circuit. If the AGC voltage is found to be normal, the grid voltage of each IF stage should be checked with a VTVM. A leaky or gassy tube may develop a positive grid voltage and cause the stage to overload.

Possible causes of picture pulling are:

- a. Defective IF amplifier tubes.
- b. Strong signal applied to the IF section causing an overloading condition.
- c. Poor low-frequency response as a result of misalignment.
- d. Shorted or open AGC filter capacitor. (C38 in Fig. 1; C34 in Fig. 2.)
- e. Open decoupling or bypass capacitor. (C35, C39, C41, or C3B in Fig. 1; C26, C31, C40, or C44 in Fig. 2.)
- f. Interference caused by improper shielding of the IF strip.
- g. Poor alignment as a result of incorrect component placement or improper lead dress.

If picture pulling is a result of heater-to-cathode leakage in more than one of the video tubes, all of the defective tubes must be replaced to cure the condition completely. In receivers employing a series-filament system, leakage or shorts within a tube can sometimes affect the operation of one or more other tubes in different sections. This situation may result in freak symptoms which are often misleading to the service technician.

When the low-frequency response of a receiver is poor and the trouble is not due to a component failure, a complete RF and IF alignment may be required in order to correct this difficulty; however, adequate alignment data for the receiver should be obtained before attempting this operation.

Symptoms Nos. 6 through 12, which were listed at the beginning of this article, are still to be covered. This will be done in a second installment of "Troubles in Video IF and Detector Systems."

LESLIE D. DEANE
 and
CALVIN C. YOUNG, JR.

Dollar and Sense Servicing

(Continued from page 33)

COLOR PROGRAMS. Playing down of color programs, to the extent that the "compatible color television" announcement is made only at the end of the show, has actually resulted in many owners watching a program on their color sets with the controls set for black and white because they didn't know it was in color. Few newspapers list the color programs because of the limited number of color sets that have been sold.

Color TV booster W. C. Moore, large Motorola distributor in Dayton, Ohio, runs co-op ads with restaurant and tavern owners of color sets on the days of big color shows. These help the night spots and promote color TV as well. In addition, he mails printed programs about once a month to all owners of Motorola color sets. These programs can be put up right alongside the sets. On superspectaculars such as the Peter Pan telecast, he used larger advertising space to list the locations of all color sets available to the public.

PAINTING. If you have a favorite dish or cup for painting yet hate to clean it out after each job, try lining it with aluminum foil inside and out. The foil can then be thrown away when you finish, and the dish will be clean. How about trying it on a paint job some cool evening to put new life into the shop. Color is the thing these days. To pick the pair of colors that'll bring your shop in step with the times, just watch the new cars roll by.



FUTURE. Etched-wiring boards mean fewer factory errors and greater reliability of receivers once manufacturers obtain experience in molten-solder dunking to make all joints at once. Time, temperature, solder, and flux are the four factors that must be kept consistently in balance to achieve good dip soldering.

Most users of etched-wiring boards are doing the dip soldering by hand, sometimes with a timer and bell to signal the end of the 8- to 10-second immersion interval. Automatic soldering machines are used by Westinghouse, DuMont, and a few other firms in order to mechanize this operation; but at present, all of these machines are loaded and unloaded by hand.

Automatic assembly machines are already inserting parts in wiring boards at RCA, Admiral, and Emerson plants, though bulky and odd-shaped parts still have to be inserted by hand. When insertion heads have been developed for these, the boards can go right on into the dip-soldering machine, untouched by human hands. Look for this step in mechanization sometime in 1956.

Most plants use a single dip in solder, but RCA consistently uses two solder pots side by side. The operator dunks the board in one for a few seconds, lifts it out, wipes a cake of beeswax across the solder in the second pot, then dunks the board in that pot to complete the job. The wax is claimed to give neater filleted joints and fewer shorts between wiring strips.



DATES. For tax-deductible business trips, consider the National Electronics Conference at the Hotel Sherman in Chicago Oct. 3-5, the Audio Fair at the Hotel New Yorker in New York Oct. 12-15, or the RETMA Radio Fall Meeting at the Hotel Syracuse in Syracuse, New York.

SURPRISES. One nice thing about servicing is its variety of problems. You never know what'll show up next in a TV set. Now we have side and top controls, the vertical chassis, printed circuits, and even flashlight tuning. Next year, there'll be entire stages crammed into little modules or blocks; for replacement of these your bill to the customer may read, "Replace Horizontal Sync Stage \$9.75."

Both DuMont and Emerson are considering the use of some modules next year. Aerovox just took over a factory for making these things, too. It's the original Project Tinkertoy machine setup of the National Bureau of Standards.

Transistors are still the dark horse in the picture; no one knows yet what they'll do to the appearance of a TV set. Another question is what they'll do to servicing. If some 75 percent of the troubles today concern tubes, if transistors don't fail in use, if wiring and soldering achieve perfection through printed circuitry, and if resistor and capacitor makers likewise turn out failure-proof products, we'll have a TV set that's as trouble-free as the modern electric refrigerator. But don't start looking for a new business yet — all this is a long long way off, and there's color television coming up fast to put cash in the till.



BOOMERANG. Trapped by the radar that he invented, Sir Robert Watson-Watt recently plunked out \$12.50 for a speeding ticket in Canada.

Our local police just bought radar equipment and expect it to pay for itself in a few months, even at special bargain rates of \$1 per mile over the speed limit. People have stopped challenging the accuracy of the electronic gadget, and they pay up and shut up to get out of its range.



LOOK — NO SOLDER. Interconnections among the five etched-wiring boards in RCA TV sets are made without solder by using a Keller wire-wrapping tool to wind the stripped wire around each rectangular terminal. Tests show these joints to be electrically and mechanically equal or superior to conventional soldered joints. Once loosened for repair, however, they have to be soldered; human hands just can't wind wire tightly and evenly enough to get the required fusion of metals by pressure.

CASTLE. Human guides have disappeared from the famous castle of Langeais in France. At the entrance to each of the 12 halls through which tourists are conducted is a small knob. When turned by the supervisor accompanying the visitors, it starts a tape recorder that gives carefully worded historical information. At appropriate points in the commentary, pulses recorded on the tape actuate control circuits to turn on special illumination aimed at the piece of furniture or tapestry being described.



FILING. In place of EENY, MEENEY, MINY, MO for your file drawers, reader Eugene Olney suggests RADIO, AUDIO, VIDEO, FIASCO. Take your pick.



SUBMINIATURIZING. Motorola Vice President Dan Noble recently demonstrated a golf ball having a built-in transistorized transmitter and dime-size battery. It puts out a signal strong enough to be picked up by a portable radio receiver used as a direction finder. No more lost balls!

Hearing aids are rapidly approaching invisibility these days. One make is built right into eyeglass frames, and now Philco announces a unit no larger than a packet of matches.

Be assured that these refinements in miniaturizing are also going into military electronic developments. Next thing we know, machine-gun bullets will have built-in electronic target seekers that make every shot count. Our son doesn't agree, so we just read to him those lines from Tennyson:

"For I dipt into the future, far as human eye could see,
Saw the Vision of the world, and all the wonder that would be;
Saw the heavens fill with commerce, argosies of magic sails,
Pilots of the purple twilight, dropping down with costly bales;
Heard the heavens fill with shouting, and there rain'd a ghastly dew
From the nations' airy navies grappling in the central blue; . . ."

The fifth line takes on a new significance this year. Could Tennyson actually have been thinking of radio-active fallout, way back in 1843?

JOHN MARKUS

for servicing **color**

YOU NEED SOMETHING EXTRA

For instruments actually *ahead* of today's circuitry ... ready for the day when color TV becomes as general as today's black-and-white sets... look at the Hycon line, designed with the electronic serviceman in mind. Accurate enough for critical work in the shop, you'll also find these test instruments rugged, compact, lightweight... just what you need for those money-making house calls.

MODEL 616 COLOR-BAR/DOT GENERATOR

... for adjusting and testing color receivers and transmitting equipment by manufacturer, station or serviceman. Features: Seven output forms of bars, dots, cross-hatch, phase and color-difference signals, including NTSC color bars. **PANEL PRESENTATION SHOWS ACTUAL COLOR AND SEQUENCE OF GENERATOR OUTPUT. \$415⁰⁰**



MODEL 614 VTVM

Convenience at unprecedented low cost sums up this rugged, serviceable instrument. Hycon *plus* features include: 21 ranges (28 with peak-to-peak scales); large 6½" meter; 3% accuracy on DC and ohms, 5% on AC; AC frequency response to 250 mc (auxiliary probe extra) **AND TEST PROBES STOW INSIDE CASE, READY TO USE. \$87⁵⁰**



MODEL 617 3" OSCILLOSCOPE

Designed both for color TV servicing and laboratory requirements. Features high deflection sensitivity. (.01 v/in rms); 4.5 mc vertical bandpass, flat within ±1 db; internal 5% calibrating voltage. Small, lightweight... but accurate enough for the most exacting work. **SPECIAL FLAT FACE 3" CRT PROVIDES UNDISTORTED TRACE EDGE TO EDGE. \$269⁵⁰**



See these latest Hycon money-makers — all in matching, bench-stacking cases — at your local electronic parts jobber.

Hycon Mfg. Company

2961 East Colorado Street
Pasadena 8, California

"Where accuracy counts"

ORDNANCE · ELECTRONIC TEST INSTRUMENTS
ELECTRONIC SYSTEMS · AERIAL SURVEYS
BASIC ELECTRONIC RESEARCH · AERIAL CAMERAS
GO NO-GO MISSILE TEST SYSTEMS

In the Interest of Quicker Servicing

(Continued from page 17)

2. Output voltage correct — one bulb is lit.

3. Output voltage too high — both bulbs are lit.

A switch is provided to adjust the output voltage to the correct value.

The unit shown in Fig. 2 is representative of a type that has a meter which indicates the output voltage. The unit which is pictured is the Acme T-8394M voltage adjuster made by Acme Electric Corporation. A switch is used to adjust the output voltage to the correct value. Schematic diagrams of two typical voltage regulators, one of each type, are shown in Figs. 3A and 3B.

Adjustable line-voltage transformers are best described as devices which prevent trouble because, through their use, the voltage to the receiver can be maintained at a normal value. This will ensure that the voltages applied throughout the receiver are correct, and component failures which could be caused by excessive voltages will be minimized.

Some indications of a possible need for an adjustable line transformer are as follows:

1. Narrow picture.
2. Short tube life (in the output stages).
3. Filaments that burn out frequently.
4. Lack of focus on some receivers.

A good check to make when trying to determine the need for an adjustable line-voltage transformer is to measure the line voltage during the time of day when the receiver is usually operated the most. A reading that is too high or too low would show a definite need for an adjustable transformer.

For best results in using a variable line-voltage transformer, the voltage should be checked and readjusted each time the receiver is turned on. The indicating device on the transformer should be checked at intervals after that to make sure that the correct voltage is being maintained.

Sensational!

Retract-O-Matic

—the new, foolproof replacement

Pickup



Even if you drop it... or slide it...


Retract-O-Matic protects records and needles from damage!

WEBSTER ELECTRIC proudly offers the new, exclusive RETRACT-O-MATIC—the sensational crystal pickup that provides positive protection to record and needle, *even when it is dropped or slid* across the record surface.

Retract-O-Matic is priced to make it a *practical replacement* for installation on any manual record player.

THE DOME ABSORBS THE SHOCK

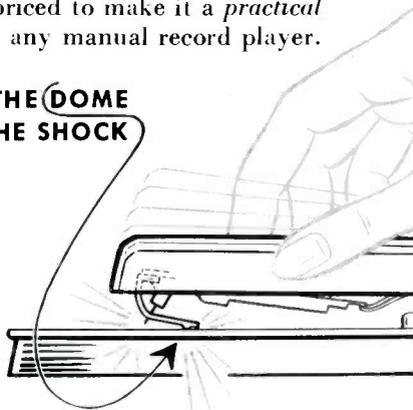The unique spring-mounted construction gives absolute insurance against damage to cartridge, needle, or record. The slightest pressure on the arm automatically lifts the needle from the record's surface, and lets Retract-O-Matic's rounded "dome" absorb the shock.



A BIG PROFITABLE MARKET

Retract-O-Matic is a "natural" as a pickup replacement for record players, children's and portable phonographs. List price of complete assembly (tone arm, cartridge, arm rest and all parts needed for installation) is only \$6.95—little more than the price of the cartridge alone. Order a stock today. Step up your sales with Retract-O-Matic!

WEBSTER  **ELECTRIC**
RACINE WISCONSIN

reserved to the technician assigned to that area. If that technician is working near one boundary or corner of his area and a call from the opposite side of that area is received, the routing system should be flexible enough so that the technician working the closest to the call should answer it even though he may be assigned to a different area. Obviously, any system that finds two men scheduled to make calls within one or two blocks of one another is not making maximum use of the advantages of a routing system unless both technicians have several calls in the immediate area. Such cases could exist if the dividing line between two sections ran through the center of a heavily populated area.

In all cases, the service calls should be routed in a logical order so that the distance to be traveled by each technician is kept at a minimum. This will ensure that a minimum amount of time will be spent in travel and will therefore make it possible for each technician to make a maximum number of calls. Shown in Fig. 7 is a sample routing sheet. This sheet contains practically all of the data necessary to operate a successful routing system.

The technician assigned to an area should be thoroughly familiar with it if possible. It is very desirable that a man be assigned to an area in which he lives because he may be personally acquainted with many of the people in that area and thus might know better how to deal with them. In fact, assigning a technician to service his own neighborhood may even result in an increase in business from that area.

Deliveries

The delivery of repaired receivers should be interspersed among the service calls. The delivery of the repaired receiver should always be made by the technician who removed the receiver. He will be in a better position to answer to the customer's satisfaction any questions which may be asked. In anticipation of such questions, the technician delivering a repaired receiver should always know exactly what steps were taken in the shop in repairing the receiver. When the technician did not repair the receiver himself, he can get the necessary information by asking the technician who actually performed the work.

Calling the Shop

Some arrangement should be made for the service technician to

call the shop for a briefing and to take care of any additional service calls in his area. One way is to have the technician phone after each service call or after every other call. The service technician should phone his shop before leaving one home en route to another in a remote area. A call at this particular time is most important because it could save returning to the same area to service another set.

OTHER WAYS TO IMPROVE SERVICE

Service the Same Day

It is always the best policy to give service as soon as possible. Always complete a call the same day it is received or by the next day at the latest. This is very important, especially if your organization deals in service only. The customer who has to wait three or four days to see a service technician then has to have his receiver taken to the shop for several more days is not going to be too eager to call the same organization for service the next time his receiver needs it.

Customer Not Home

The first thing for the technician to ask himself when he gets no response to his knock is: Is the customer really not at home? Maybe he is upstairs, in the basement, or in the back of the house. In some cases, he may even be in the back yard or in a garage workshop. To avoid having to make a return call, ring the bell for a few seconds to make sure that it could be heard. If there is no doorbell, be sure to knock loud and often enough to be heard. A walk to the side of the house or along the driveway should reveal if the customer is in the yard or garage. In any case, a period of 2 or 3 minutes should be given the customer to appear. In some cases, an even longer wait is advisable.

Not-Home Card

If it is finally determined that the customer is definitely not at home, a "Not-Home Card" should be left. This card should be in the form of a tag that is fastened to the doorknob so that the customer will be sure to get it. A sample card is shown in Fig. 8. It has most of the pertinent data which should be included on such a card. Notice that the time of the call is very bold and prominent. Also notice that the "NOT AT HOME" is in the largest lettering on the card so that there will be no possibility of missing it. The entire card should be a bright



Fig. 8. Example of Not-Home Card.

color, or the letters should be a bright color so that the customer will be sure to see it when he returns. In size, the card should be large enough to be seen easily and to contain the necessary data. The printer can help in the determination of the size because it may be less expensive to have certain sizes printed.

Free Return Calls

There are several factors which may have caused the customer to be away from the home when the technician called, and not all of them are the customer's fault. Some of these are:

1. Technician arriving later than the appointed time.
2. Emergency trip to a doctor's office.
3. Unexpected business in town.
4. Washing clothes in the basement and did not hear the knock or doorbell.
5. In the back yard and did not hear the knock or doorbell.
6. Forgot service technician was coming.

In any case, a return call results in a loss of time which means fewer calls can be made, a fact which means that less money will be taken in by the technician that day. Therefore, anything which can be done to eliminate a call back is desirable. There are two things that

the technician and service organization can do to help eliminate these return calls which become necessary because the customer is away from home:

1. Give the customer a good idea of the time the service technician will arrive; then be there at the appointed time.
2. Make an honest effort to locate the customer after ringing the doorbell.

The technician can also reduce the number of return calls by making sure that he has sufficient money to cash the largest denomination of bill which he may expect to receive.

Speed and Traffic

Besides being a violation of the law, speeding or any form of reckless driving is not the way to give fast efficient service. It may also cause the customer to take his service elsewhere. This is caused by the fact that people resent having their children endangered by speeding vehicles, and rightly so. Another thing to be considered is that being picked up for traffic violations is a gross waste of time. It could also result in having the police on a constant lookout for any type of violation by your service vehicles, and this can be harrasing.


Day and Evening Service Calls

It is a common practice for most service organizations to make both day and evening service calls. This was made necessary by the fact that many people work and can only be at home in the evening. In addition to this, the television receiver is in use mostly during the evening; and therefore more troubles develop then.

It is good business to give service as soon as possible after the customer calls, preferably on the same day or evening. This type of same-day service is the best advertising a TV service company can get.

Some special problems must be considered if evenings calls are to be made with the same efficient dispatch with which day calls are made. Parking is one of the prime problems, especially in areas where there are large apartment buildings. Whenever possible, the service vehicle should be parked in the customer's driveway since it may be necessary to remove the TV chassis and take it to the shop for repair.

Tops The Field . . .

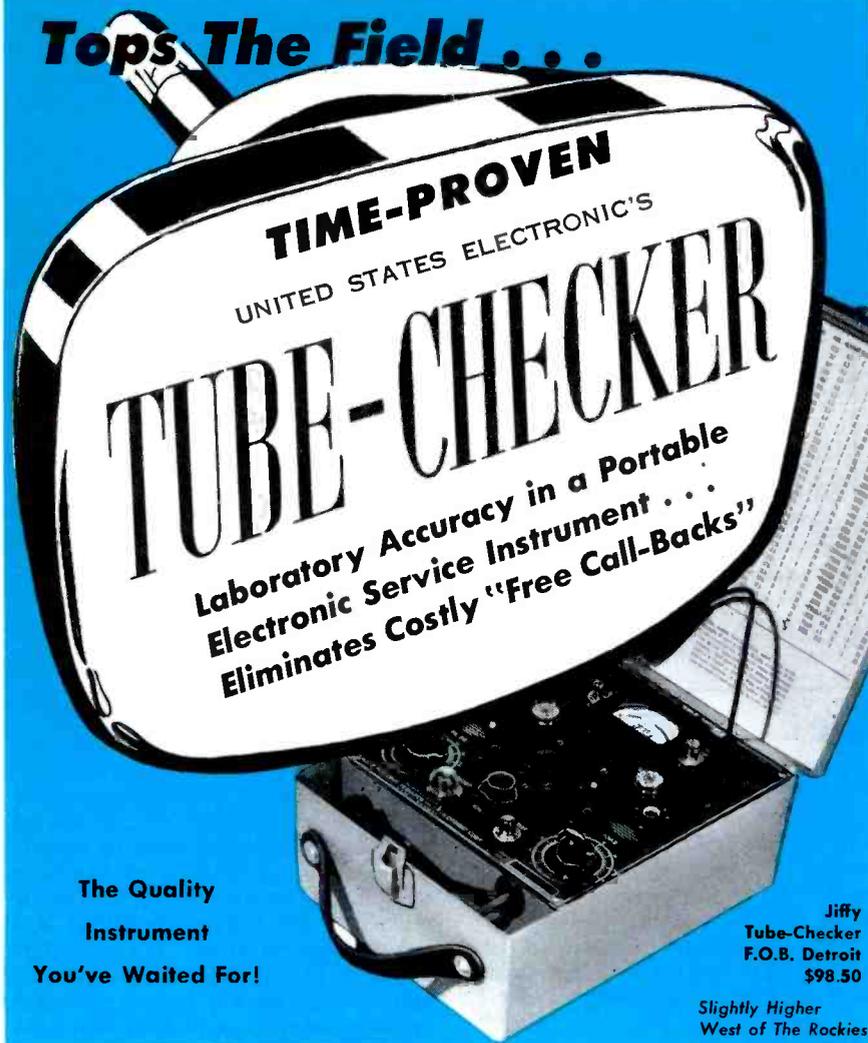

TIME-PROVEN
UNITED STATES ELECTRONIC'S

TUBE-CHECKER

Laboratory Accuracy in a Portable
Electronic Service Instrument . . .
Eliminates Costly "Free Call-Backs"

The Quality
Instrument
You've Waited For!

Jiffy
Tube-Checker
F.O.B. Detroit
\$98.50

Slightly Higher
West of The Rockies

MUTUAL CONDUCTANCE AND EMISSION CHECKER

Accurately checks Picture and Circuit Tubes for filament Continuity, Emission, Gas, Shorts and Leakage under load conditions—in 20 seconds time!

Built to TV Servicemen's specifications, tested in the field and now endorsed by leading service organizations as the leading Tube-Checker! This revolutionary quality product increases sales, develops customer confidence and puts money in the serviceman's pocket! Amazing "on-the-job" instrument eliminates doubt, proves conclusively any need for replacement of tubes right in your CUSTOMER'S HOME! Built for rugged daily usage, the 6½-lb. steel-cased Tube-Checker fits in the serviceman's caddy. Get the best . . . and reap profits for your organization!

- No complicated controls—No re-setting for Duo-Purpose Tubes
- Built-in leakage sensitivity to detect hot and cold leakage to 15 meg.
- Perfect Companion to 7 lb. Jiffy Ren-O-Lyzer

**UNITED STATES ELECTRONIC
RESEARCH & DEVELOPMENT CORP.**

1605 W. Lafayette Detroit, Mich. Woodward 3-4498

Write for further details and address of your nearest dealer.

955PF
955PJ

Locating the correct address also poses a problem because house numbers that are visible in daylight sometimes are almost impossible to see at night. In addition, it is often difficult to see the street signs even with the help of a spotlight. For this reason, it is important that the service technician be thoroughly familiar with the area. Directions are very important in routing evening calls because it is much easier to become confused after dark. The directions should route each call via the nearest through street.

Uniforms

In making calls after dark, technicians wearing uniforms which have the company's name on them will usually have less trouble gaining entrance to the customer's home when the customer has never seen the technician before. If it becomes necessary to remove the chassis for shop service, less difficulty is met in getting the customer's permission. This problem of customer distrust has arisen from the actions of a few unscrupulous operators; consequently, uniforms can help somewhat. Fair dealing, good service, and courteous manners complete the picture for obtaining good customer relations.

The major objective of any service organization should be the improvement of its service to the customer. Some of the ways to do this are as follows:

1. Establish a fast and efficient routing system.
2. Return repaired chassis immediately.
3. Make a service call the same day that the customer calls in.
4. Notify the customer the approximate time that the service technician will arrive.
 - a. When the customer is not at home, use a not-home card.
 - b. Make efforts to reduce the number of free return calls.
5. Technicians should drive carefully to avoid loss of time.
6. A proper uniform should be worn.

If the many different phases of these main ideas are kept in mind, an efficient and fast servicing system can be maintained.

CALVIN C. YOUNG, JR.

Examining Design Features

(Continued from page 25)

the emitters in the IF transistors. Resistor R13 returns to a negative 1.5-volt DC source; whereas, R18 is returned to chassis ground.

The detector stage also utilizes a CK760 transistor having a grounded emitter. The AVC voltage is tapped off at the detector output where it is filtered by C1 and is reduced to the proper DC level by R23. The audio signal from the detector stage is coupled to the volume control through the electrolytic capacitor C2. The resistors R24 and R30 have been added in later productions to improve the quality of the audio system in the receiver.

The audio amplifier stage employs a CK721 or a CK722 transistor connected in a grounded-emitter circuit. Bias for the emitter circuit is derived from the series resistor R27, and capacitor C4 acts as an RF bypass. The base connection of the AF amplifier transistor obtains bias from a divider network formed by resistors R25 and R26. The audio output from the collector circuit of this stage goes into the primary of transformer T1. The secondary of this interstage transformer is center tapped and develops two out-of-phase signals which are required for the operation of the push-pull output circuit.

The output stage consists of two CK721 or two CK722 transistors connected as push-pull amplifiers. These units are connected in grounded-emitter circuits. The bias for the base connections is provided by the voltage dividers R28 and R29, and C5 serves as a decoupling capacitor. The impedance of the center-tapped primary of the audio output transformer T2 matches the collector impedance of the output transistors. A .15-mfd capacitor C25 has been connected across the primary of this transformer in later productions in order to improve the impedance match and thus reduce audio distortion. The secondary of the output transformer drives a 3 1/2-inch PM speaker. The secondary of the transformer and the voice coil of the speaker are matched in impedance. The impedance is 16.8 ohms. The small speaker employed in this radio provides a reasonable amount of volume and fidelity. The manufacturer of the receiver rates the power output at 100 milliwatts.

All input power required to operate this relatively small receiver

Tops The Field...

UNITED STATES ELECTRONIC'S
REN-O-LYZER
Electronically Analyzes and
CORRECTS Picture Tube Trouble
in 2 Minutes!
90.1% PICTURE TUBES RECOVERED
ARE STILL IN USE AFTER ONE YEAR!

Jiffy Ren-O-Lyzer
F.O.B. Detroit \$115
Slightly Higher
West of The Rockies

The Quality
Instrument
You've Waited For!
Write or Wire for Demonstration

ONLY THE REN-O-LYZER FORECASTS REPAIRABILITY

**Cleans Picture Tube Elements, Burns Off Oxygen,
Welds Open Cathodes and Filaments Electronically . . .**

Proven results with the quality-built REN-O-LYZER assure the TV serviceman increased income and satisfied customers! Thousands of service organizations all over the country are earning \$9.95 per service call with the revolutionary REN-O-LYZER . . . and they are averaging \$120.00 increased income per week on each REN-O-LYZER unit in use! Their customers are amazed at the immediate and lasting picture tube recovery—recommend the services to others. Extremely simple to operate—no complicated controls. Write or wire for a demonstration of this amazing electronic instrument!

- Service Charge is just \$9.95 to the customer!
- Service May be Sold with a Minimum Guarantee!
- 12 Service Calls and the REN-O-LYZER is Paid For!

955PJ
955PF

**UNITED STATES ELECTRONIC
RESEARCH & DEVELOPMENT CORP.**
1605 W. Lafayette Detroit, Mich. Woodward 3-4498

Write for further details and address of your nearest dealer.



Big bargain for two bits!

Handy, 4 drawer steel stock cabinet
— complete with generous supply of blank labels.



\$2.50 value
yours for only
25¢ plus **40** identification labels from envelopes containing **Centralab Ceramic Capacitors**

Gives you a place to keep loose capacitors after you've opened an envelope


To get this handy cabinet, you buy capacitors just as you usually do to meet your needs — making sure to get Centralab Ceramic Capacitors.

Every envelope of five Centralab Ceramic Capacitors contains a small folder. At each end of this folder, there's a green identification label. One of these labels has this same identification printed on its reverse side, only in black. This is the label you tear off and save.

After you have 40 of these identification labels, send them with a quarter (for postage and handling) — and your name and address (printed clearly) — to Centralab, A Division of Globe-Union Inc., 942F E. Keefe Avenue, Milwaukee 1, Wisconsin.

Save **40** labels like this

green on one side, black on the other

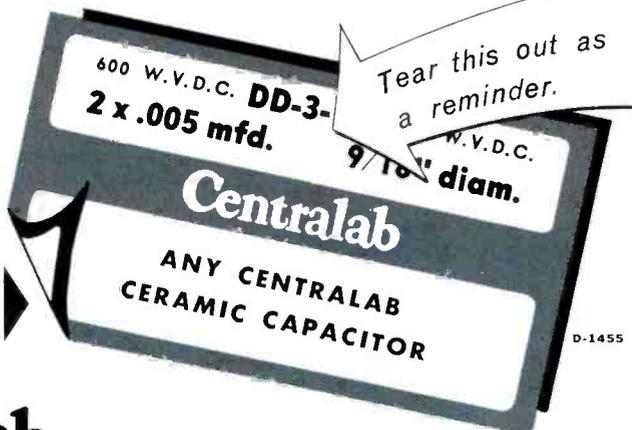

Centralab A DIVISION OF GLOBE-UNION INC.

is furnished by four 1 1/2-volt, size D batteries connected in series. The current drain from this power supply is approximately 15 milliamperes, and the life expectancy of ordinary flashlight batteries in this application is about 500 hours. If mercuric-oxide batteries are employed, their life expectancy will be as much as 2,500 hours depending upon the duration and frequency of operation.

The transistors used in the circuit are of the p-n-p type; therefore, the positive terminal of the battery series is connected to the chassis, and the supply voltage becomes a negative 6 volts DC. The transistor pictured in Fig. 4A has the pins keyed to fit the socket, and the middle pin is placed closer to one end than it is to the other. The transistor in Fig. 4B has the pins equally spaced; however, they may be bent to fit the socket, as shown in this photograph. If a transistor is suspected of being faulty, the only reliable check is by means of substitution. When replacing the type shown in Fig. 4B, it may be noticed that one end is coded with a red dot. This indicates that the collector pin is located near the dot end of the transistor. The drawing of Fig. 5 illustrates the connections of a transistor socket.

KENCO KATE SAYS

"NO INSTALLATION PROBLEMS when you use KENCO MOUNTS"




KENCO 6" and 12" Aluminum Snap-In Wall Brackets

Made of heavy gauge high strength aluminum alloy. Snap-in feature eliminates holding of mast while applying hardware. Carriage bolts throughout for easy installation. Full thread hex head lag screws permit use of ratchet or speed wrench.

Available with Stainless Steel Hardware (optional at slight extra cost).

For information on the complete Kenco line write Dept. R.J.

KENWOOD ENGINEERING CO., INC.
Kenilworth, New Jersey

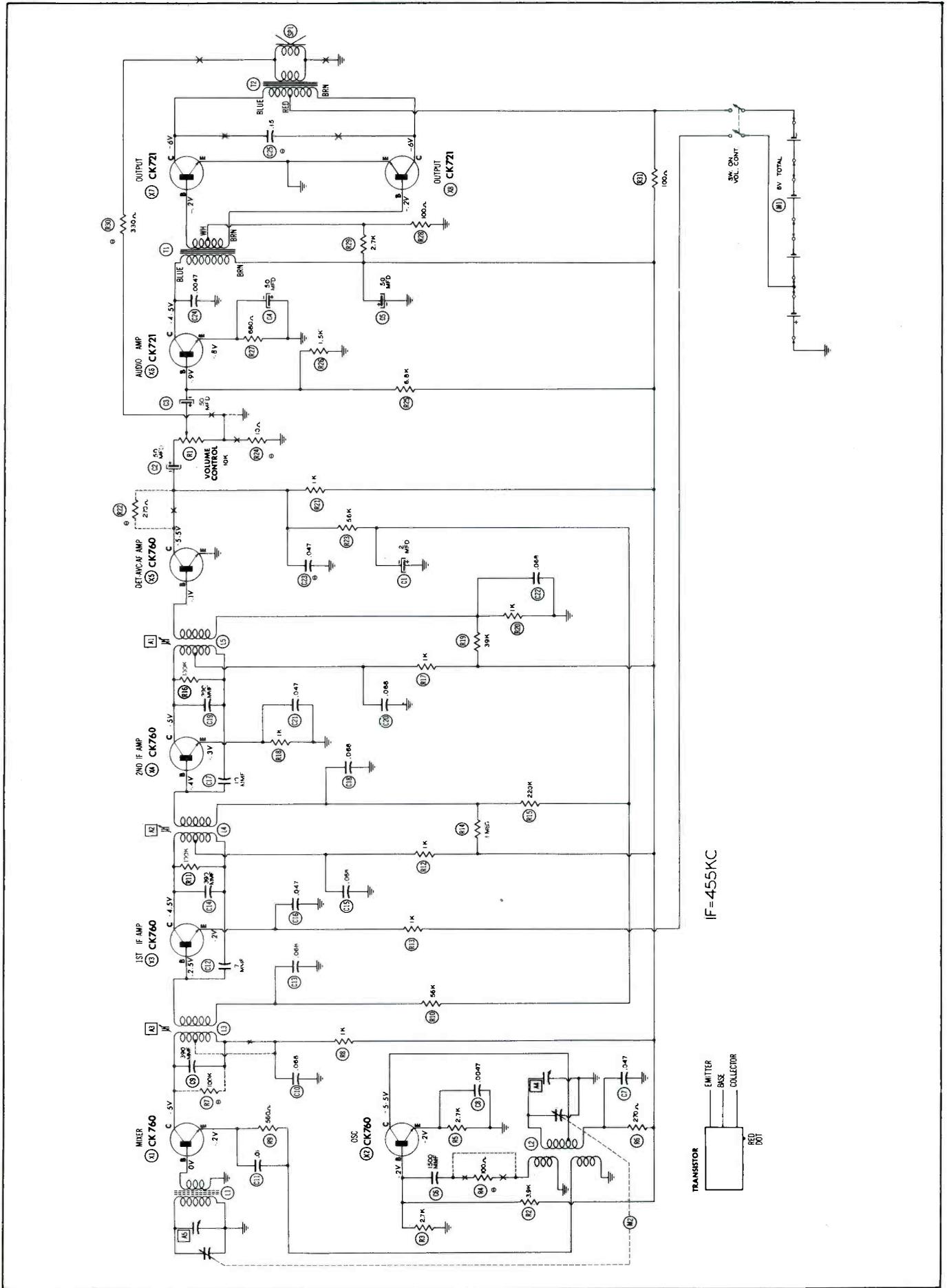


Fig. 3. Schematic Diagram of Raytheon Chassis 8RT1.

only vokar vibrators give you

VOKAR VIBRATORS—preferred by leading manufacturers of auto radios.

NEW SAHARA-PACK!

ALL-WEATHER, LOW-VOLTAGE STARTS! New dry-air canning developed by Vokar reduces moisture inside vibrator during manufacture. Moisture cannot condense on tungsten points causing corrosion during shipping or storage.

NEW VAPOR-BLOCK COATING!

NO EARLY-LIFE FAILURES! Applied to points by hand, Vapor-Block Coating eliminates pitting and arcing during vital first hours of vibrator operation. Result: Sure Starts! Longer Life! Higher Output!


NEW SWING-SUSPENSION!

SUPER-SILENT PERFORMANCE! Noise level is reduced to absolute minimum — whisper quiet! No hum to affect radio performance. Swing-Suspension design also means less hash, less heat!

VOKAR QUALITY BRAND VIBRATORS*

Produced under the same quality conditions that made Imperial quality famous!

*Unpackaged

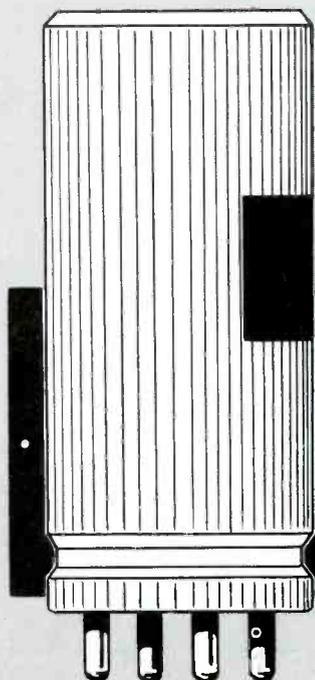

In order to simplify the replacement of this type of transistor, note the location of the red dot and bend the pins of the new unit to duplicate those of the original. In some later production runs of this chassis, the manufacturer has wired and soldered the transistors directly to their respective circuits.



(A) For RF, IF, and Detector Stages.



(B) For Audio Stages.

Fig. 4. Plug-in Type Transistors Employed in Raytheon Chassis 8RT1.

Interchanging the transistors from one stage to another in the receiver is not recommended. In some instances, realignment will be required after substituting a new transistor unit in the RF stages.

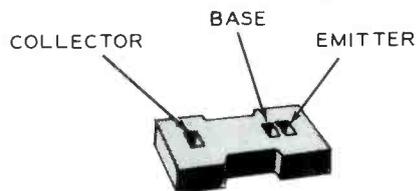


Fig. 5. Transistor Socket Showing Connections.

The transistor should always be removed before replacing a component which is soldered to its socket because excessive heat is capable of damaging the transistor permanently. When servicing a receiver of this design, remember that transistors should be removed before accurate readings of resistance through other components can be made and that the voltage at the terminals of the meter leads should not exceed the normal operating voltage of the circuit under test.

LESLIE D. DEANE

PF REPORTER, September 1955

Audio Facts

(Continued from page 21)

is important, and certain precautions should be taken. As shown in Fig. 1, a record jacket should be pressed on its edges so its sides will be bowed away from the playing surfaces of the record. The record is then grasped with the thumb at the edges and with the finger tips on the label surface and withdrawn from the jacket. In this way, dust or grit that might be clinging to the inner surfaces of the jacket or to the surface of the record will not be rubbed across the record and will not damage the playing surfaces of the record.

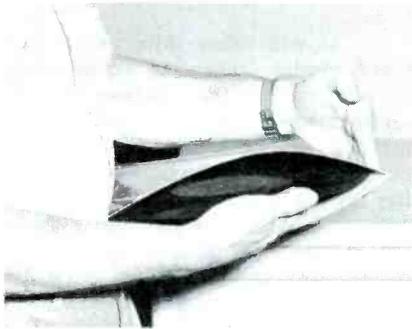


Fig. 1. Removing Record From Jacket.

The record should only be handled by the edge and the label surfaces. The fingers should never be placed on a playing surface. Fingers will usually leave prints which will at the least have a tendency to hold dust. Of course, if any dust, grit, or other foreign material is present on the fingers, it will be deposited in the grooves where it can cause damage eventually, if not at the time of handling.

The important things to remember are that records should never be handled by the playing surfaces and should never be laid on any surface that might scratch them or deposit dirt on them. Keep them in their protective containers when not in use, and keep them clean.

We must not forget that the turntable must also be kept clean and free of dust.

Importance of Stylus

Before proceeding further, we should mention that one of the most common causes of damage to records is the use of a worn, damaged, or improperly used stylus. A stylus which has become worn from normal usage or has been broken can do great damage to the grooves subjected to its cutting and gouging action. If

64% of all Electronic Engineers

USE

HICKOK

Dynamic Mutual Conductance TUBE TESTERS



- ★ **FASTER**
- ★ **MORE ACCURATE**
- ★ **DEPENDABLE**
- ★ **LONGER LIFE...**

... are only a few reasons why more engineers prefer HICKOK than all other makes of tube testers combined.

NEW DESIGN FEATURES FOR MODEL 750 SHOWN

- Micromho ranges on the dial of the large, HICKOK 5" Meter: 0-1500, 0-3000, 0-6000, 0-15,000, 0-30,000 Micromhos. Also, two "Replace-Good" ranges.
- Tests voltage regulator (VR) tubes in accordance with any manufacturer's handbook data or by use of the up-to-date roll chart furnished.
 - A. Accurate DC Voltmeter readings up to 200 volts.
 - B. Accurate DC Milliammeter Measurements up to 100 milliamperes.
(Both on the Micromho Meter).
- Two DC plate and screen voltages provided—Normal and Low—controlled by a Selector Switch. The Low Range is for use with sub-miniature tubes and for other tubes requiring a low range of plate and screen volts.
- New 0-1500 Micromhos range for increased accuracy in testing sub-miniature tubes.
- Four AC signal voltages provided—as low as .25 volt.
- Two "red-green" ranges on the Micromho Meter scale offer easier customer readings.
- Quick and easy scale selection—The Chart identifies the range to be read by the letters from "A" through "H" inclusive. A simple selector switch carries the same letters and identifies the various ranges.
- Short test—Recent HICKOK engineering and achievements have provided a highly accurate short test which will show up even the slightest heater cathode leakage condition of a vacuum tube.
- Line adjust knob automatically indicates whether the line voltage is low or high.
- Permits matching of tubes such as 6SN7 when used in critical circuits.
- Forecasts the future life of the tube under test. Tests the gas content of the tube. Tests for tube noise.
- Bias and line fuses prevent accidental damage. Chart arrangement makes for quickest tube selection. The tube's location on the chart is indicated by a key type number stamped beneath the chart openings.

TESTS THE NEW SERIES HEATER-STRING (600 M. A.) Tubes

ALSO TESTS GERMANIUM DIODES AND SELENIUM RECTIFIERS

THE HICKOK ELECTRICAL INSTRUMENT COMPANY

10566 Dupont Avenue • Cleveland 8, Ohio

INSURE CUSTOMER SATISFACTION . . .

OHMITE®



Little Devil® COMPOSITION RESISTORS

Provide an
**EXTRA MARGIN
OF SAFETY**



● You can eliminate "call-backs" and insure customer satisfaction by standardizing on Ohmite "Little Devil" composition resistors. These tiny units provide an *extra margin of safety* on your repair jobs. For example, they are rated at 70C instead of the usual 40C . . . and they meet all test requirements of MIL-R-11A, including salt water immersion and high humidity tests without wax impregnation. Ohmite "Little Devil" resistors are available in ½, 1, and 2-watt sizes ($\pm 5\%$ or $\pm 10\%$ tolerance) in all RETMA values. Order from your distributor, today.

Other Dependable OHMITE Products



Type AB Noise-Free Potentiometers



BROWN DEVIL Wire-Wound Resistors

Be Right with
OHMITE®

DEPENDABLE RESISTANCE UNITS



Write for
Stock
Catalog

OHMITE MANUFACTURING CO.
3644 Howard Street, Skokie, Illinois
(Suburb of Chicago)

the stylus is not aligned properly and leans to one side or the other or if the turntable is not level, the grooves can be distorted and damaged. Excessive stylus pressure or the use of the wrong stylus, such as a 3-mil stylus for a microgroove record, can cause irreparable damage.

Cleaning Records

Dust has a tendency to settle on all surfaces; but since microgroove records are made of plastic, they accumulate a static charge and attract dust to their surfaces. When dust settles on a record, the record should be cleaned before it is played or returned to its protective container.

As with other things connected with audio, there is no absolute agreement on the virtues of the methods used to clean records. Most methods are both recommended and condemned, with the opinion depending on the individual. Some claims are made that the damage done to the record during cleaning exceeds by far any good derived from the process. These claims may be valid in cases in which proper precautions are not taken and in which the cleaning is not done with care, but any reasonable method which will at least remove the most of the grit and foreign material should prove worth while. It would seem that a knowledge of how and what to do and the use of some common sense could be the answer to any controversy on the subject.

Included among the notes on some record jackets is the suggestion that "before the enclosed record is played, it should be wiped carefully with a moist soft cloth to remove any accumulation of dust." This seems to be a reasonable suggestion because a lint-free soft cloth when moistened and used with a gentle circular motion on the surface of the record will pick up dust and also dissipate some of the static charge on the record for at least a short time.

Microgrooves are very small and narrow but do have depth, consequently some difficulty is encountered when attempts are made to remove dust, grit, or any other foreign particles from them. The opinion that such material will be pushed deeper into the grooves rather than be removed appears logical. For this reason, the use of a suitable brush seems appropriate.

A two-inch paint brush with very fine soft bristles was used by the writer for many years to remove



Fig. 2. Kral Rek O Klean Brush in Use.

dust from 78-rpm records while they were spinning on the turntable prior to being played. This practice was carried over to microgroove records and seemed to be very satisfactory. The brush had to be kept clean because it certainly did pick up a great deal of dust and lint.

Several styles of brushes are supplied for this purpose. Some very small ones are designed for mounting on the pickup arm with the bristles riding in the record grooves in front of or adjacent to the stylus. This type is not so popular at the present time, probably because of the lightweight pickups used with microgroove recordings. A larger brush which mounts or stands on the turntable mounting board is adjusted to allow the tips of the bristles to ride on the playing surfaces of the record. One is shown in Fig. 2. This type can only be used with a single-play turntable and must be moved aside when a record is changed. This model will automatically return to its correct position on the record. A special brush which neutralizes the static charge as it cleans the record will be discussed in a later paragraph.

A record can also be cleaned by washing it in a stream of running water from a tap. Of course, this cannot be done recklessly. Hot water and too much force cannot be used because labels can be washed off very easily.

Removing Static Charge From Records

Dust can be removed from the playing surfaces of a record; but if the static charge is not removed from the disk, more dust will soon collect on the surfaces again. This static condition is more severe when the humidity is low and is aggravated by motion and friction. A spinning record can accumulate a heavy charge, and rubbing with a cloth or using a brush can increase the charge to a degree that will attract additional dust and lint.

Various static removers have been developed for use with records. These are available in the form of liquids, sprays, prepared cloths, and special brushes all of which are to be

used directly on the records. There are also some small attachments that mount on the pickup arm near the stylus and never touch the record.

Several manufacturers supply liquid antistatic solutions. The liquid is applied and used according to the directions accompanying that particular brand. In most cases, a few drops are applied to the playing surface of the record and then spread with a soft clean cloth. Manufacturers of certain brands of records recommend that enough liquid should be applied to saturate the surface of the record; whereas, others say that only a very small amount is required. In any event, a clean cloth must be used and the record should be clean. If the record is not clean when the liquid is applied, even though the static is eliminated, the dirt and foreign particles will be rubbed into the grooves. An antistatic solution can also be sprayed on the record instead of being poured.

Antistatic cloths are impregnated and prepared in such a way that they dissipate the static when they are rubbed over the record in a prescribed manner. These are convenient because no liquid is required. The same rules of cleanliness must be observed; and of course, the cloth must be kept clean.

The static-eliminating brush (Fig. 3) derives its powers from the polonium strip located in its ferrule. When the record is brushed, the dust is removed and at the same time the static charge is neutralized by the radioactive polonium in the strip. The polonium strip is effective for one or two years. When necessary, the brush can be returned to the manufacturer for replacement of the strip to renew its static-neutralizing properties.

Some small, very lightweight attachments which clip to the pickup arm near the stylus, as shown in Fig. 4, remove the static charge by the neutralizing action of a small bit of radioactive material held close to the record surface. As the record revolves, the radiation scans the record grooves and removes the static charge. If any particles of dust or grit have been clinging to the



Fig. 3. Staticmaster (Hi-Fi Model) Record Brush.

record, they will be released and be free on the surface. These small attachments seem to do a good job of keeping the records uncharged so that the records would apparently remain neutralized for an indefinite period.

How long records will remain in the uncharged state will depend on how often they are played, how they are handled, and how and where they are stored. If a record is static free and clean when it is returned to its protective container, it should be in excellent condition when removed to be played in the future.

We read and hear objections to the application of any kind of solution to the playing surfaces of a record. One objection is that if the solution is allowed to accumulate, the grooves might have a tendency to become filled with a sludge. We have also heard the opinion expressed that an excess amount of some of the solutions would have a deteriorating effect upon damping material and protective membranes associated with the stylus of certain cartridges. No doubt there is some truth to these claims if some solutions are used in excessive amounts; but if discretion and common sense are used in following specified procedures, the benefits should outweigh any damage.



Fig. 4. Eby Stati-Mute Installed on General Electric "Baton" Arm.

NOW! TEST TUBES IN SECONDS! MAKE NEW PROFITS *in MINUTES!*



on every
service call



B&K NEW PORTABLE
DYNA-QUIK MODEL 500
DYNAMIC MUTUAL CONDUCTANCE TUBE TESTER

ONLY
\$109⁹⁵
NET

Now you can easily cut servicing time—make more on-the-spot tube sales—prevent costly call-backs—and give a better service guarantee! DYNA-QUIK—the new top quality, low cost, portable tester quickly locates all weak and in-operative tubes—and easily does the complete job with laboratory accuracy right in the home! You create greater customer confidence because your customer sees for himself the true tube condition. Easy to operate—in just a few minutes you can quickly check all the tubes in a TV set. You can depend upon DYNA-QUIK because it tests under the dynamic heavily loaded conditions that are the actual operating conditions of the set. At such low cost DYNA-QUIK quickly pays for itself—and continues to make money for you every day!

DYNA-QUIK DOES IT FASTER, EASIER, MORE ACCURATELY

- Makes complete tube test in as little as 12 seconds per tube—faster than any other tester!
- One switch tests everything! No multiple switching—no roll chart.
- Laboratory accuracy right in the home! Large 4½" plastic meter has two scales calibrated 0-6,000 and 0-18,000 micromhos.
- Shows customer true tube condition and life expectancy on "Good-Bad" scale!
- Automatic line compensation! Special bridge continuously monitors line voltage.
- 7-pin and 9-pin straighteners mounted on panel!
- Never Obsolete! New overlay panels with up-to-date markings available from factory, when required.

TESTS 99%

OF ALL TUBES*
in use today for:

DYNAMIC
MUTUAL CONDUCTANCE
SHORTS
GRID EMISSION
GAS CONTENT
LEAKAGE
LIFE EXPECTANCY

*Including new 600 mil series tubes.

PORTABLE—CAN BE USED ANYWHERE

Handsome, rugged, luggage style carrying case, covered in durable, black leatherette. Removable slip-hinged cover. Size: 15½ x 14½ x 5¾ in. For 105-125 volts, 60 cycle, A.C. Net wt. 12 lbs.

SEND FOR BULLETIN 500

Made by the makers of
the famous CRT 350



B&K MANUFACTURING CO.
3726 N. SOUTHPORT, CHICAGO 13

We must admit that there is a wide disparity between the recommendation that enough of a certain brand of solution should be used to saturate the surface of the record because of the lubrication afforded the grooves and the one that warns against using any type of fluid including water. Probably the moral to be gained from all this is that a record should be kept clean and static free with a minimum of manipulation.

Storage of Records

The storage of records involves only a few basic precautions. The most troublesome problem encountered when large numbers of records are to be stored seems to be the difficulty of finding a suitable cabinet shelf or some such container which will fit into the surroundings.

Records should be clean and stored vertically (on edge) in their original jackets. Suitable plastic envelopes that afford added protection from dust and handling are available from several suppliers. If the jacket or container is flat, if no distorting pressure is applied, and if the temperature is not excessively high, the stored records should remain flat and not become warped. Because of the accumulated weight, records can become warped and deformed in a very short time if they are stored horizontally (flat), particularly if they are placed in stacks of many records.

Records should be clean, should be stored in a vertical position in protective jackets, and should not be subjected to excessive pressure or high temperature. This seems to cover the story of record storage.

ROBERT B. DUNHAM

**DON'T JUST SAY
CAPACITORS**

Ask For Sprague By
Catalog Number

Know what you're getting . . . get exactly what you want. Don't be vague . . . insist on Sprague. Use complete radio-TV service catalog C-610. Write Sprague Products Company, 105 Marshall Street, North Adams, Massachusetts.

SPRAGUE
WORLD'S LARGEST CAPACITOR MANUFACTURER

Notes on Test Equipment

(Continued from page 19)

caused by application of too great a sync signal.

A calibration voltage is provided internally. When the CAL (calibrate) button on the front panel is pressed, a square-wave signal with an amplitude of .05 volt peak to peak is applied to the vertical section of the oscilloscope. The calibrating voltage is kept constant by means of a voltage-regulating circuit.

This voltage is applied at a point after the step-attenuator section so that the calibration may be used for all positions of the step attenuator once the calibration has been made. To calibrate the oscilloscope, the operator presses the CAL button; then he adjusts the V-GAIN (vertical amplifier gain) control until the height of the square wave is equal to the distance between the two horizontal calibration lines on the screen. The switch of the vertical attenuator is marked at each position with the peak-to-peak voltage that is represented by the distance between the calibration lines when the oscilloscope has been set up in this manner.

Two input connections to the vertical amplifier are provided on the front panel of the oscilloscope. One is a binding post, and the other is an Amphenol connector for cables such as the one shown in Fig. 1. The probe and cable assembly shown is the Hycon Model 6211 oscilloscope probe having an impedance of 10 megohms and 15 micromicrofarads. Two binding posts for ground connections are provided, and there is one for horizontal input and another for Z-axis modulation. All of the binding posts will accept banana plugs, and they are also spaced on 3/4-inch centers to accommodate General Radio 274-MB plugs. The vertical and horizontal step attenuators are frequency compensated for best frequency response at all positions.

HYCON MODEL 614 VTVM

Another Hycon test instrument which we have had an opportunity to use is the Model 614 VTVM pictured in Fig. 2. This meter is designed to measure a wide range of resistances and voltages (both AC and DC). DC voltages are measured with the use of a probe having a built-in isolating resistor. AC measurements are made with the use of a low-impedance probe or a crystal-diode probe.

The Hycon Model 614 VTVM matches other Hycon equipment in

outward appearance. The meter is housed in a green steel case, and the instrument can be stacked vertically with other Hycon instruments. An interesting and convenient feature is that storage compartments are provided in one side of the case where the cables and probes that are permanently attached may be kept when not in use.

A small circular groove has been cut around the tips of both the AC-OHMS probe and the DC probe. It was noticed during the use of this VTVM in our laboratories that this groove was of great aid in keeping

the probe from slipping off the test point.

The size of the case is 8 1/2 inches wide, 11 inches high, and 7 1/2 inches deep. Weight of the instrument is approximately 10 pounds. The large 6 1/2-inch meter dial contains seven photo-printed scales and is illuminated by dial lamps.

There are four front-panel controls: (1) an input-selector switch, (2) a range-selector switch, (3) a zero-adjust control, and (4) an ohms-adjust control. The input-selector switch has five positions:

now 2 B&K CRT Money-Makers

TEST and REPAIR TV PICTURE TUBES



NEW DELUXE CRT 400 with 4 1/2" Plastic Meter

This portable Cathode Rejuvenator Tester quickly locates and corrects picture tube troubles in a few minutes, right in the home, without removing tube from set! Restores emission, stops leakage, repairs inter-element shorts and open circuits. Life-test checks gas content and predicts remaining useful tube life. Grid Cut-Off reading indicates picture quality customer can expect. Earns servicing dollars in minutes. Cuts operating costs, eliminates tube transportation. Saves money on TV set trade-in reconditioning. Pays its way from the very first day.

Weighs only 5 lbs. mounted in rugged, luggage style, carrying case covered with handsome, durable leatherette. Size: 11 x 7 1/2 x 5".

Model 400. Net \$5495

Over 20,000 CRT'S NOW IN DAILY USE ACROSS THE NATION



NEW ECONOMY CRT 200

A quick profit maker priced low enough for every serviceman to cash in on picture tube repairs. Performs most of the functions of the CRT 400. Has 3" meter. In leatherette carrying case. Size: 11 x 7 1/2 x 5". Weighs 5 lbs.

Model 200. Net \$3995




Send for Bulletin 104

B & K MANUFACTURING CO.
3726 N. Southport Ave. • Chicago 13, Illinois



It's as EASY as This

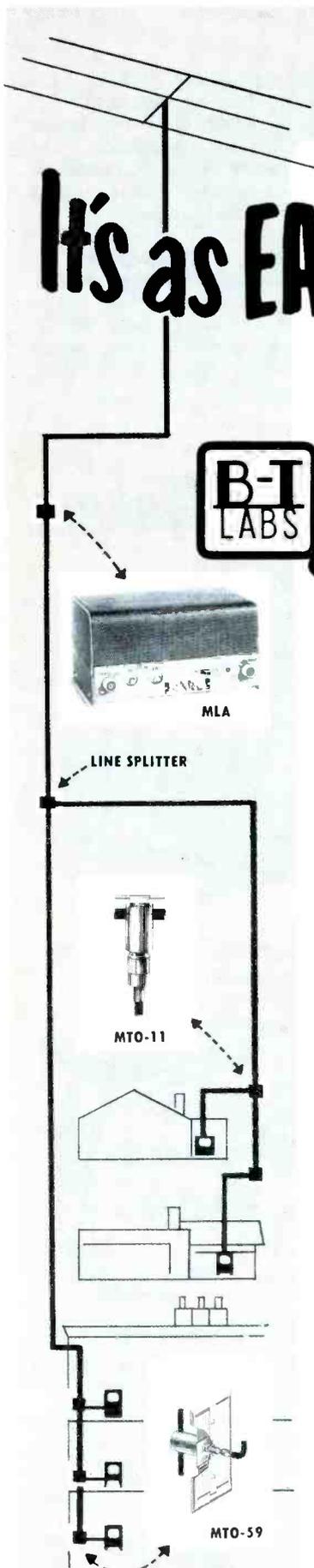TO INSTALL A MASTER TV SYSTEM WITH Masterline UNITS



A Connect the antenna line to the INPUT of your Masterline MLA Line Amplifier. The signal is now amplified 37db (70 times).

B Connect a line splitter or line coupler to the OUTPUT of the MLA. You now have 2 or more branch lines for feeding to TV receivers.

C Where the branch line is run out-of-doors, connect a Masterline MTO-11 (outdoor tap-off) wherever a TV set feed line is required.

D Where the branch line serves as a riser inside a building, connect a Masterline MTO-59 (wall-plate tap-off) wherever an antenna outlet is required.

This is only one example of a Master TV System, to show the flexibility of Blonder-Tongue distribution equipment. There are many more, all covered in the new B-T INSTALLATION MANUAL.

Write for your Free copy to Dept. FJ-13

BLONDER-TONGUE LABORATORIES, INC.
WESTFIELD, NEW JERSEY

Manufacturers of TV Cameras, TV Amplifiers, Boosters, Converters, Accessories and Originators of the Masterline and 'Add-A-Unit' Master TV Systems.



Fig. 2. Hycon Model 614 VTVM.

OFF, -VOLTS, +VOLTS, AC VOLTS, and OHMS. The range-selector switch has seven positions. For voltages, the positions are marked as follows: 1.5V, 5V, 15V, 150V, 500V, and 1500V. For resistances, the positions are marked as follows: R x 1, R x 10, R x 100, R x 1K, R x 10K, R x 100K, and R x 1MEG.

The meter dial is calibrated so that DC and AC rms voltages may be read for the voltage ranges just mentioned. The instrument responds to peak-to-peak AC voltages, and separate scales that are marked in red are provided for these ranges.

The input impedance is 11 megohms for all DC ranges, and the accuracy is ± 3 per cent of full scale. The input impedance on AC ranges is 1 megohm shunted by 60 micromicrofarads. The frequency response is 30 cycles per second to 3 megacycles with the direct probe, and it is 50 kilocycles to 250 megacycles with a crystal probe. Accuracy is ± 5 per cent of full scale on all AC ranges.

AUTHORIZED MODEL 101F CATHODE-RAY TUBE TESTER AND REJUVENATOR

In the February 1955 issue of the PF REPORTER, mention was made in this column of the Authorized Model 101 cathode-ray tube tester. A more recent model, the Authorized Model 101F, has some added features to increase its range of applications over that of the previous model.

The general appearance of both instruments is similar. The Model 101F is shown in Fig. 3. The push button which was in the lower left corner of the earlier model has been replaced by a three-position switch marked READ - SET - REJUVENATE.



Fig. 3. Authorized Model 101F Cathode-Ray Tube Tester and Rejuvenator.

This switch adapts the instrument for use in rejuvenating cathode-ray tubes which give a low emission reading on the tester. It is claimed that the rejuvenation process will not injure grid structures and that the instrument will indicate whether or not the rejuvenation has proceeded to the necessary degree.

In addition, the emission scale has been recalibrated to give a true indication of beam current in microamperes.

HICKOCK MODEL 770 OSCILLOSCOPE

A new addition to the line of test instruments manufactured by the Hickok Electrical Instrument Co., Cleveland, Ohio, is the Model 770 oscilloscope which is shown in Fig. 4.

The Model 770 is a general-purpose oscilloscope having high deflection sensitivity and a wide-band frequency response. It is suitable for a great number of applications by the service technician. Although this oscilloscope is classed by the manufacturer as a general-purpose type, its appearance suggests that it is



Fig. 4. Hickok Model 770 Oscilloscope.

more of a laboratory type because of the number and variety of functions which it offers.


Some of the features of the Hickok Model 770 are not usually found in general-purpose oscilloscopes. These features are: DC amplifiers for both vertical- and horizontal-deflection circuits, balanced input to the vertical amplifier, and a driven sweep.

A driven sweep (sometimes called "triggered sweep") depends upon an applied signal to initiate the trace, whereas the usual recurrent


sweep does not depend upon such a signal. The recurrent sweep will operate at a free-running rate if no sync signal is applied; however, if no sync signal is applied to the driven sweep, it will not operate at all. In the Model 770, the triggering signal can be taken from the vertical-input signal if the sync selector is in the INT (internal) position; or it can be taken from some external source if the sync selector is in the EXT (external) position.

We have had occasion to use a driven sweep at various times in our laboratories; and we find that under

in ceramics

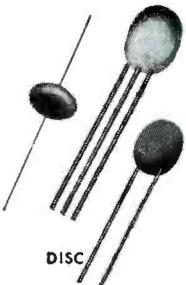

DISC

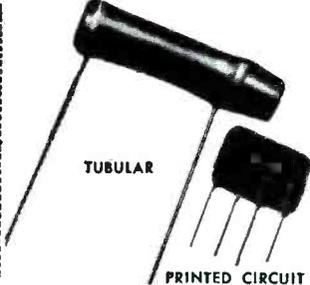

TUBULAR



PRINTED CIRCUIT


you can see why C-D is always the leader

THE ONLY CERAMIC WITH THE MILLION-DOLLAR BODY

C-D Ceramic Capacitors are made from beginning to end under one roof in a huge plant devoted completely to ceramic capacitor production. Every process . . . every ingredient is under constant control. You can see the reasons for C-D's outstanding superior quality.

And to help you, C-D Ceramic Capacitors are packaged in compact, crystal-clear, easy to handle and always usable plastic boxes (no extra charge). That's why Distributors who know carry the complete C-D line. See your C-D Distributor today. He's listed in your local Classified Telephone Directory.

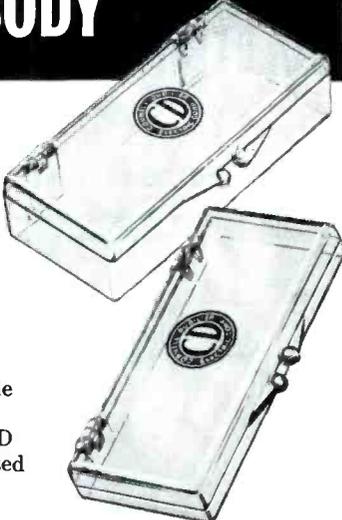There are more C-D capacitors in use today than any other make.





CONSISTENTLY DEPENDABLE

CORNELL-DUBILIER CAPACITORS

PLANTS IN SOUTH PLAINFIELD, N. J.; NEW BEDFORD, WORCESTER AND CAMBRIDGE, MASS.; PROVIDENCE AND HOPE VALLEY, R. I.; INDIANAPOLIS, IND.; SANFORD AND FUQUAY SPRINGS, N. C.; SUBSIDIARY THE RADIART CORPORATION, CLEVELAND, O.

difficult synchronization conditions, it may offer a more stable synchronization than the use of a recurrent sweep. A change of setting of the vernier sweep control does not appear to disturb the synchronization greatly. A driven sweep may be used in such a manner as to result in a greatly expanded sweep if the sweep is set to a much higher rate than the repetition rate of the observed signal and if a synchronization signal of the same rate as the observed signal is used. In this manner only a portion of a cycle will be observed; but the detail of that portion will be shown in a stretched or expanded form.

Front-panel controls and switches are provided for the following functions: focusing; phasing; calibration; sync selection; adjustment of beam intensity, sweep stability, scale illumination, and sync amplitude; selection of type of sweep and vertical-amplifier bandwidth; coarse and fine adjustment of sweep rate; vertical and horizontal positioning and attenuation.

The calibration signal may be .1, 1, 10, or 100 volts peak to peak, depending upon the position of the calibration switch.

The vertical- and horizontal-gain controls are vernier controls, and the vertical attenuator is governed by a four-position switch. The vertical attenuator is frequency compensated. The LOCKING (or sync-amplitude) control will select either polarity of the sync signal.

A sweep range of 2 cycles to 30 kilocycles is covered by the coarse-frequency switch and is obtained by means of six of the switch positions. Two other positions are for frequencies of 30 and 7,875 cycles per second. These positions are useful when viewing vertical and horizontal signals in TV receivers. Another switch position is marked EXT. CAP.; and when this position is used, an external capacitor can be connected between the ground and the horizontal DC terminals in order to extend the sweep rate below 2 cycles per second.

The type of sweep used is governed by the position of the horizontal selector switch. This is a five-position switch. Two of the positions provide for feeding an external deflection signal to the input of the horizontal amplifier. The signal is fed directly to the amplifier when the switch is in the X1 position, and it is fed through an attenuator in the X10 position. The third position is for a recurrent sweep, the fourth is for a driven sweep, and the fifth is for a sine-wave sweep at line frequency.

The sync-selector switch is a four-position switch marked EXT, INT, LINE, and 2X LINE.

The DC balance controls for the vertical and horizontal amplifiers are accessible through the front panel as screwdriver adjustments. Binding posts are provided for:

LOOK FOR THIS LABEL



TO BE SURE OF THIS SOLDERING PERFORMANCE



5 SECOND HEAT

Weller was first to design and patent a fast-heating soldering gun. All Weller models heat in 5 seconds.

TRIGGER CONTROL

Fingertip control brings heat instantly on— instantly off. There's no need to unplug . . . no wasted time or current.




PERFECT BALANCE

The exclusive streamlined design of Weller Guns permits easy access to tight places, comfortable handling and precision soldering.

EXCLUSIVE TIP-GRIP

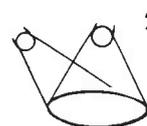Wiping action of tip-fastening nuts eliminates contact resistance and oxidation. Full, constant heat is assured.



2 SPOTLIGHTS

Pre-focused dual spotlights eliminate shadows and illuminate the work. Lights and heat come on simultaneously.

LONG-LIFE TIPS

Low cost Wellertips give long service, are designed for maximum heat transfer and can be changed in seconds.



Weller

ask your distributor for a demonstration

ELECTRIC CORP.

827 Packer Street, Easton, Pa.

DON'T JUST SAY CAPACITORS

Ask For Sprague By Catalog Number

Know what you're getting . . . get exactly what you want. Don't be vague . . . insist on Sprague. Use complete radio-TV service catalog C-610. Write Sprague Products Company, 105 Marshall Street, North Adams, Massachusetts.

SPRAGUE

WORLD'S LARGEST CAPACITOR MANUFACTURER

All input signals to the horizontal and vertical amplifiers.

An output signal at line frequency.

A sawtooth output signal.

An input signal for intensity modulation.

An external sync signal.

The manufacturer's specifications for the deflection sensitivity and frequency range of the Hickok Model 770 are as follows:

Deflection Sensitivity

First vertical amplifier — .010 volt rms per inch with the bandwidth switch in NARROW position.

Second vertical amplifier — .035 volt rms per inch with the bandwidth switch in WIDE position.

Horizontal amplifier — .075 volt rms per inch.

Frequency Ranges

First vertical amplifier — 0 to 2.5 megacycles (flat within 3 decibels) with the bandwidth switch in NARROW position.

Second vertical amplifier — 0 to 5 megacycles (flat within 3 decibels) with the bandwidth switch in WIDE position.

Horizontal amplifier — 0 to 500 kilocycles (flat within 3 decibels).

The size of the Hickok Model 770 is 12 by 14 by 18 inches. The weight is 50 pounds.

RCP MODEL 780 SWEEP GENERATOR

The RCP Model 780 electronic sweep generator is made by the Radio City Products Company and is pictured in Fig. 5. This sweep generator is designed to provide a sweep signal within a frequency range from 3 to 1200 megacycles. Six frequency bands are employed to cover this range. The signals on bands A, B, C, and D are at fundamental frequencies; and the signals on bands D₁ and D₂ are harmonics.

The sweep-generating portion of the instrument is entirely electronic

in operation, depending for its action upon a tank circuit which has the property of variable reluctance. The sweep action is in one direction only and starts at the frequency indicated on the dial, sweeping upward in frequency an amount that is dependent upon the setting of the width control and upon the band selected.

According to the manufacturer, the sweep width may be as high as 30 megacycles on band D. The WIDTH control is calibrated with 90 equal divisions from 10 to 100, and a table in the instruction manual gives the different sweep widths obtained for

(Advertisement)

MODEL 648		MODEL 715/115		MODEL 715/115-7	
TUBE TYPE	FIL.	CIRCUIT	PLATE TEST	FIL. X. PLATE YZ	YZ
3BZ6	3.0	AC1234	5B7	3.0	26 3JKMQ
4BC8	4.2	A123	A45	4.2	17 2LR 4NR
5BE8	5.0	A127	A89	5.0	17 4NR 47NPS 3KR
6A28	6.3	A123	AC45	6.3	30 21JQ 6PR
6BA8	6.3	A128	AC345	6.3	20 9LR 71OR
6BC8	6.3	A128	679	6.3	17 2LR 4NR
6CM7	6.3	A123	A45	6.3	18 2OR 4NR
		126	A45		30 4NR

Latest Chart Form 648-13



tape-o-matic® tape recorder

Here's What You Have to Offer . . .

- TOP FEATURES — many not found on models selling for up to \$500.00!
- DUAL TRACK
- DUAL SPEED
- PRECISION TAPE INDEX TIMER
- "RECORD READY" LIGHT
- AUTOMATIC SHUT-OFF
- MONITOR SWITCH
- PAUSE BUTTON
- DUAL INPUT AND OUTPUT JACKS
- PROFESSIONAL QUALITY MICROPHONE
- PUSH-BUTTON CONTROLS
- SAFETY SWITCH
- "OFF" "TREBLE" "BASS" CONTROLS

— and a cinch to sell!

Many Hi-Fi installation and service jobs can lead right into a plus-profit sale when you demonstrate the versatile V-M tape-o-matic to your customers! A Voice of Music tape-o-matic "rounds out" their installation . . . is remarkably flexible for a wide variety of uses.

See your V-M Distributor Salesman. Stock and sell the Voice of Music Model 700 tape-o-matic for plus profits! They're yours for the taking!



V-M MODEL 1200
4-speed Record Changer for precision-engineered hi-fi response . . . at a "never-before" price! Easy to install. Trouble-free. Only \$46.50*



*Slightly higher in the west.

V-M CORPORATION, BENTON HARBOR 7, MICHIGAN

WORLD'S LARGEST MANUFACTURER OF PHONOGRAPHS AND RECORD CHANGERS

various settings of the WIDTH control, BAND switch, and TUNING control.

The six ranges provided by the BAND switch are as follows (in megacycles):

Band A — 3.0 to 8.4.

Band B — 9 to 25.

Band C — 28 to 72.

Band D — 72 to 200.

Band D₁ — 216 to 600.

Band D₂ — 435 to 1200.

No external blanking signal is required inasmuch as blanking is provided internally by the action of a gating internal.

A HORZ SCOPE OUTPUT jack is provided so that a horizontal-deflection voltage may be applied to the horizontal-input terminals of an oscilloscope when it is desired to view a response curve. The phase of the horizontal-deflection voltage may be varied through 180 degrees by means of the PHASING control of the generator. The knob of this control also operates the ON-OFF switch of the instrument.

The SWEEP OUTPUT cable is permanently attached to the instrument and is terminated at the opposite end with a 50-ohm resistor. An unusual feature of the instrument is the attenuator system that is operated by five push buttons. The attenuator is of the step or ladder type and is calibrated directly in decibels. The attenuation range is from 0 to 78 decibels. It is obtained in 32 steps, and no two successive steps are separated by an amount greater than 3 decibels. Any attenuation ratio within the range can be selected by the proper combination of push buttons. Each section of the attenuator is completely shielded and terminated for low leakage and constant impedance over the entire range of attenuation.

An internal detector circuit is connected to the DET/COMP (detector/comparator) OUTPUT jack, and



Fig. 5. Radio City Products Model 780 Sweep Generator.

this circuit provides a means for checking the output signal of the sweep generator. A marker can be applied to the MARKER INPUT jack, and this marker will appear in the detector-comparator output. The sweep limits can be determined in this manner. The marker will also be present in the SWEEP-OUTPUT signal fed to the circuit under observation.

An AGC circuit is used to provide a regulated output signal.

The RCP Model 780 is supplied with three cables — one for sweep output, one for horizontal output, and one for detector-comparator output. The size of the instrument is 9 1/2 by 9 1/4 by 12 1/2 inches. The weight is 16 1/2 pounds.

*Sure-
Cure
for
Replacement
Headaches:*



Replace with the **BEST**

OXFORD SPEAKERS

"No more worrying after you've completed your replacement jobs" . . . that's the saying of more and more servicemen every day because they've switched to OXFORD REPLACEMENT SPEAKERS.

We GUARANTEE you products that are built to be replacement speakers. We stand behind each and every speaker with a 100% guarantee against any mechanical or electrical defects for one full year.

OXFORD Replacement Speakers undergo a rigid inspection to make certain that they are as good or better than the original speaker. That's why more servicemen are switching to OXFORD . . . the replacement speakers for a better job.

OXFORD ELECTRIC CORPORATION

3911 SOUTH MICHIGAN AVENUE
CHICAGO 15, ILLINOIS
EXPORT — ROBURN AGENCIES, NEW YORK CITY
IN CANADA — ATLAS RADIO CORP. LTD., TORONTO

Illustrated literature is available without obligation.

. . . at better jobbers!



GAS TEST WITH RAYTRONIC CATHODE BEAMER

The Raytronic Laboratories, Inc., of Cincinnati, Ohio, have included facilities for a critical gas test in their latest model of the Raytronic Beamer CB-54A. Other testing and repair operations remain the same as in previous models except for the removal of the toggle switch which controlled the burn current during removal of a cathode-to-grid short. The space formerly occupied by this switch is now occupied by the gas-test switch. This gas-test feature is designed to provide the service technician with a means for accurate determination of the gas content of a picture tube. Knowing this content, the technician will then be better able to advise either replacement or repair of the picture tube as he sees fit.

The manufacturer of the Raytronic Beamer states that no attempt should be made to rejuvenate a tube showing indications of more than 1 microampere of ion current (gas) per milliampere of beam current.

Their field tests indicate that a gas content in excess of this amount

will lower the life expectancy of the tube even though the emission can be increased by rejuvenation. If the gas content is less than this amount (1 microampere), then other factors such as the thickness of the barium coating on the cathode will govern the life expectancy of the tube.

The action of the Cum-A-Tron circuit, as it is called by the manufacturer, will be described briefly. The gas test is made with the master selector switch of the Raytronic Beamer in the GRID position. (The technician should first make sure that the tube is not defective. This means that the tube should have grid control, good emission characteristics, and should not be shorted.) The GAS-TEST switch is then set to the METER SET position, and the grid-control potentiometer is adjusted until the meter needle is at the red calibration mark. Then the GAS-TEST switch is set to GAS CONTENT, POS 1; and the position of the meter needle is noted. At this setting of the controls of the instrument, the meter is registering a current which is the sum of the plate current in the amplifier tube of the instrument, the ion current (gas) in the picture tube, and the interelement leakage.

In the next position, GAS CONTENT, POS 2, the cathode-ray tube is biased to cutoff so that the meter indicates the sum of the plate current and the interelement leakage. The difference between these two readings for POS 1 and POS 2 is the indication of gas content. This difference can be measured in the number of the smallest scale divisions between the two meter-needle positions. If this number exceeds 10 (15 in some models of the instrument), the tube should be rejected as too gassy for rejuvenation. At these control settings, 10 divisions (or 15 in some models) indicate a gas-ion current of 1 microampere which is the limit previously mentioned.

An accurate indication of the gas content of a picture tube will help the technician to decide whether to repair or replace. This will save him some wasted time in repairing tubes which would fail at an early date because of high gas content. It will also do much to prevent customer dissatisfaction from cases of early failure after rejuvenation.

PAUL C. SMITH




URANIUM. A small California appliance shop reports selling \$3,200 worth of Geiger counters in less than a month. A big department chain expects to sell \$2,000,000 worth of uranium-finding equipment this year, 40 per cent of it east of the Mississippi. Yes, uranium hunting is becoming big business.

Radio and television shops are logical market places for this equipment, because of its technical nature. Because so many dealers are showing interest, one manufacturer of radiation instruments (Technical Associates, Burbank, California) has issued a brochure of advice: "Cashing In on the Big Uranium Boom."

They say, among other things, that Geiger counters are fine for pinpoint prospecting and for making rough ore assays but are strictly for shoe-leather prospecting. The more expensive scintillation counters, on the other hand, have much higher sensitivity and are nondirectional; they can easily detect bodies of hidden ore and can be used while moving at good speeds on a jeep or other vehicle.

For information about prospecting areas in your vicinity, write the Atomic Energy Commission in Grand Junction, Colo. For a good booklet, order "Prospecting for Uranium" from the Supt. of Documents, U. S. Govt. Printing Office, Washington 25, D. C., at 25 cents.

MARKUS • • Dollar and Sense Servicing

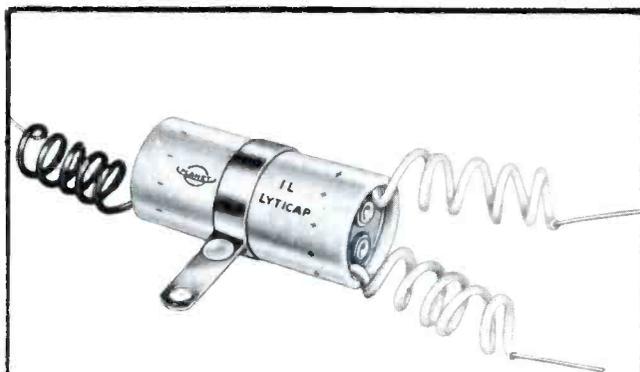

NEW DUAL SECTION ELECTROLYTIC CAPACITORS HERMETICALLY SEALED IN ALUMINUM TUBES WITH COMPLETELY FLEXIBLE INSULATED LEADS. By riveting the leads directly to the condenser end disc, Planet has eliminated the use of rigid terminal risers ordinarily used on this type construction. This allows Planet Type IL capacitors to fit into a smaller space and eliminates the possibility of lead breakage.




"ENGINEERED FOR QUALITY"
GUARANTEED FOR ONE YEAR

PLANET MANUFACTURING CORPORATION
225 BELLEVILLE AVENUE
BLOOMFIELD, N. J.

Write for Catalog 200—Lists Specifications on Stock Items

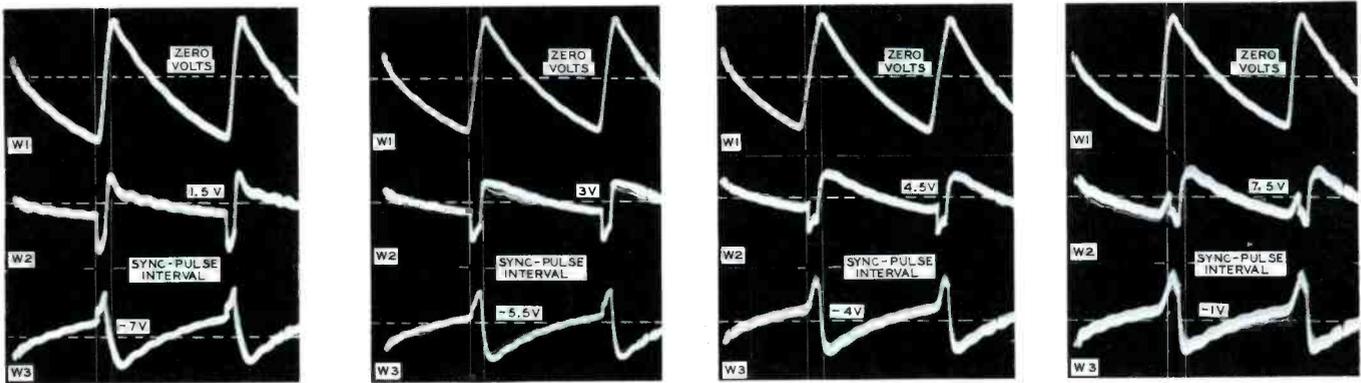The Triode Phase Detector (Continued from page 23)



(A) With Oscillator Tending to Run at a Reduced Rate.

(B) With Oscillator Tending to Run at a Slightly Reduced Rate.

(C) With Oscillator Tending to Run at Correct Frequency.

(D) With Oscillator Tending to Run Fast.

• Fig. 2 Waveforms Observed in Circuit of Fig. 1B.

nals as the dual diode; but the negative sync pulse is applied to the cathode, the positive pulse goes to the grid, and the sawtooth wave is fed to the plate of the triode. The correction voltage is taken from the junction of two equal resistors, R79 and R80. These resistors form a voltage-divider network so that the value of the correction voltage is midway between the grid and cathode potentials.

The series of waveforms in Fig. 2 shows how the voltage relationships in the Motorola phase detector change when the horizontal oscillator tends to drift off frequency. In each group of pictures, W1 is the sawtooth waveform on the plate; W2 is the negative pulse on the cathode; and W3 is the positive pulse on the grid.

While the waveforms were being taken, the oscilloscope was

synchronized externally to a voltage obtained by clipping a lead to the insulation on one of the leads to the horizontal windings of the yoke. In this manner, the true phase relationships between each of the waveforms could be observed. The distance between the two vertical lines in each group of waveforms represents the duration of the sync pulse. The sawtooth voltage W1 applied to the plate maintains an average value of

XCELITE Hand Tools
PREFERRED BY THE EXPERTS

Yes, they're
SUPERREAMERS!

Just what you've wanted!

- SUPER size!
... ream 1/8" to 3/8"
- SUPER tough ...
rust resistant
CHROME FINISH!

No. 38 fixed in full-size XCELITE handle ... **\$2.15**
List, less your discount

No. 99-38 to fit the big 99-1 handle in your versatile 99PR nut driver-screwdriver kit (there's a pocket to hold it!) ... **\$1.85**
List, less your discount

ASK YOUR JOBBER TODAY!

XCELITE, INCORPORATED
Dept. Q
Orchard Park,
New York

For Originality
LOOK TO XCELITE

Now! TEST A COUPLING CONDENSER
FOR LEAKAGE

...without disconnecting
from circuit!

TeleTest
CapaciTester



Model CT 355
\$44⁹⁵

- Eliminates unsoldering or clipping of coupling condenser from circuit
- Tests for leakage up to 40 megohms
- Also tests for opens, shorts, and intermittents
- Also detects leakage between any points in a circuit where leakage may occur
- All leakage tests are performed dynamically, under load
- Includes Wien bridge for measurement of capacity from 10 mmf to 50 mfd.

The greatest impact of the CapaciTester will be realized in trouble-shooting printed wire or printed circuit equipment. It does away with delicate, time-consuming, and often damaging operations. See it at your jobber or write for information.

TELETEST
INSTRUMENT CORP.

31-01 Linden Place,
Flushing, New York

approximately zero volts with respect to ground at all times.

In Fig. 2C, the free-running frequency of the horizontal oscillator is about the same as the frequency of the sync pulses. Note that the sawtooth voltage crosses its AC axis during the sync-pulse interval. The sync pulses are negative on the cathode and positive on the grid; and there is a flow of grid current from the cathode side of C77, through the tube, and on to the grid side of C76. Capacitors C76 and C77 become charged in the polarities shown in Fig. 1B. The charges leak off slightly between pulses but are re-established during every sync-pulse interval.

Because of the flow of grid current during each sync pulse, the potential on the grid side of C76 with respect to the potential on the cathode side of C77 is dependent upon the sync amplitude which is almost constant for a given signal. Since the difference between these potentials is essentially the bias on the tube, the bias remains practically constant.

The cathode voltage with respect to ground will vary, however, depending upon the average amount of tube conduction; and the tube conduction will vary depending upon the instantaneous plate voltage during the sync-pulse interval. The voltage at the junction of R79 and R80 together with the grid voltage on the tube will vary in step with the cathode voltage.

The DC levels which were observed in the Motorola circuit under the conditions of Fig. 2 are given in Table I. It can be observed in Table I that the difference of DC potential between the cathode and the grid stays constant regardless of the amount of conduction through the tube; therefore, the potential across R79 maintains a steady value. The output voltage measured from the

junction of R80 and R79 to ground is really the result of the combined voltages across R77 and R79. Since the average potential of the grid is more negative than the cathode voltage, the grid end of R79 is negative with respect to the cathode. The cathode, however, is positive with respect to ground. The circuit is designed in such a way that the voltage developed across R77 is equal to that which appears across R79 when the free-running frequency of the oscillator is approximately the same as the frequency of the sync pulses. Cancellation takes place, and no correction voltage is produced.

If the oscillator tends to run fast, the sawtooth voltage reaches a positive value by the time the sync pulses arrive. See waveform W1 in Fig. 2D. Since the plate voltage is positive, conduction is heavier through the tube during the pulse time and the average cathode voltage becomes more positive. The grid voltage is also less negative than it was in Fig. 2C, but the grid constantly maintains the same DC potential with respect to the cathode.


Since the negative voltage across R79 has not changed and the positive voltage across R77 has increased, the correction voltage from the phase detector is positive. This correction voltage serves to decrease the frequency of the cathode-coupled multivibrator which is used as the horizontal oscillator.

If the oscillator tends to run at a reduced rate, the sawtooth voltage on the plate of the triode is negative during pulse time and conduction through the tube is reduced. See Figs. 2A and 2B. The voltage across R77 is lower, and the potential across R79 is as great as before. The output, which is the algebraic sum of these two voltages, is negative.

The incoming sync pulse shown in waveform W4 of Fig. 3 is distorted

TABLE I
DC LEVELS IN MOTOROLA CIRCUIT

Figure No.	On Cathode (volts DC)	On Grid (volts DC)	At Junction of R79 and R80 (volts DC)
2A	1.5	-7.0	-3.0
2B	3.0	-5.5	-1.5
2C	4.5	-4.0	0.0
2D	7.5	-1.0	3.0

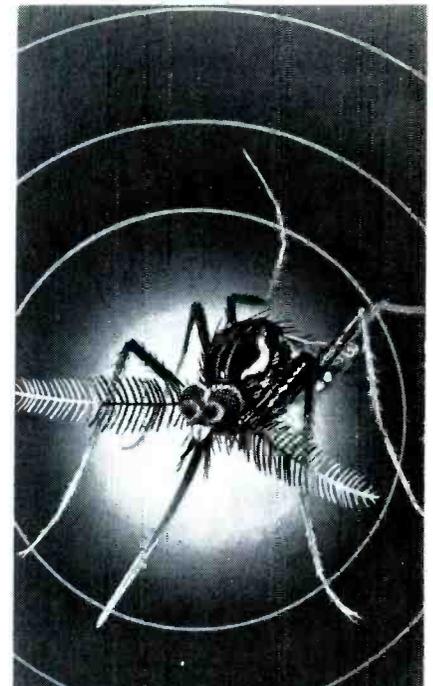

No Antenna Problem Here!

(it came as original equipment)

YOUR antenna problems however may not be so easily solved. That's where we come in—specializing in antennas for automotive and mobile communications uses. Proof of our quality workmanship—such fine accounts as Motorola, Zenith, Lear, RCA, GE, Bendix, and Crosley. Whatever your needs, The Antenna Specialists Company will be pleased to serve you.

Our latest sensation — the Telescopic Auto "Baseball" Antenna in triple chrome, or 6 baked-on automotive colors. Also, the "Double Header" Twin-tail antennas in chrome or color. In self-displaying units, these QUALITY antennas are a SELLING sensation.

Write today for catalog sheets on communication, automotive or special antenna requirements.



the
antenna
specialists
co.

12435 Euclid Ave., Cleveland 6, Ohio
CANADA | ACTIVE RADIO & TV DISTRIBUTOR
REPS | 58 SPADINA AVE., TORONTO, ONT.



YOU BUILD



**KITS
IN ONE
EVENING—
but they
last a lifetime...
and you
save 50%**

**38 Kits and 42 Instruments —
the Industry's most complete
line of MATCHED
TEST INSTRUMENTS**

1/2-million EICO Instruments are now in use the world over! That's the proof of EICO's leadership in Value.

For latest precision engineering, finest components, smart professional appearance, lifetime performance and rock-bottom economy — see and compare the EICO line at your Jobber before you buy any higher-priced equipment! You'll agree with over 100,000 others that only EICO Kits and Instruments give you the industry's greatest values at lowest cost.


Prices 5% higher on West Coast.



Write NOW for FREE latest Catalog PF-8



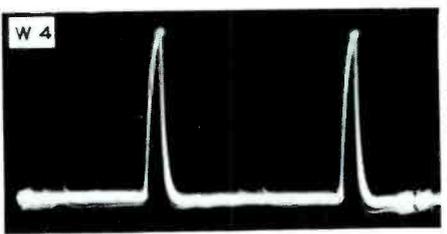ELECTRONIC INSTRUMENT CO., Inc.
84 Withers Street, Brooklyn 11, N. Y.



(A) Positive Pulse to the Grid.



(B) Negative Pulse to the Cathode.

Fig. 3. Input Pulses to the Phase Detector of Fig. 1B.

into the shape of waveform W3 of Fig. 2. The incoming sync pulse shown in W5 of Fig. 3 is distorted into the shape of W2 of Fig. 2. This distortion is caused by the action of the circuit of the phase detector. The gradual rise in grid voltage and the gradual fall in cathode voltage between pulses are caused by the discharge of C76 and C77.

Triode in General Electric Model 21T17


Fig. 4 is a schematic diagram of another phase detector using a triode. This circuit, which is found in the General Electric Model 21T17, requires only one sync pulse — a negative one from the cathode of the phase-inverter stage. A sawtooth voltage taken from the output of the horizontal-deflection system is applied to the plate of the phase detector.

The output voltage of the phase detector is developed across R71, R73, and R75 in series and is measured between ground and the junction of R71 and R78. This voltage is applied to one grid of a cathode-coupled multivibrator where it is superimposed upon a small negative bias which is already present on that grid. A more detailed description of this same multivibrator is included in the article, "Grid Emission and Gas in Vacuum Tubes" in the August 1955 issue of the PF REPORTER.

Fig. 5A shows the waveform W6 which appears on the cathode of the phase detector, Fig. 5B shows the amplified view of the waveform W7 produced on the grid of the phase detector by conduction through the tube, and Fig. 5C shows the sawtooth waveform W8 which appears on the plate.

The sync pulse is much greater in amplitude than the sawtooth wave.

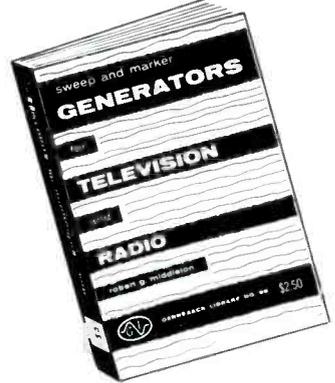**NEW—
middleton
on sweep
and marker
generators**



Bob Middleton, well known author-engineer, takes you behind the dials and shows you how and why sweep and marker generators operate. In the same free and easy style in which he speaks to thousands of technicians all over the country, he clarifies all the fundamental concepts which are frequently misunderstood.

For more efficient servicing

Sweep and marker generators are standard servicing tools today, and unless you understand fully how they work, you're not getting all you can out of them. This book will give you confidence in your instruments and show you how to put them to uses you never before thought possible. No service technician can afford to be without this book — especially with color TV on the way!

SWEEP AND MARKER GENERATORS FOR TELEVISION AND RADIO.
No. 55. By Robert G. Middleton. 224 Pages. Over 200 illustrations. Paper cover. \$2.50

- 10 BIG CHAPTERS**
- The sweep generator signal.
 - Generating a sweep signal.
 - Attenuating the output.
 - Shielding the output.
 - Aspects of sweep output.
 - Marker generators.
 - Marker signal generation.
 - Marker signal calibration.
 - Receiver alignment.
 - Visual-alignment methods.

ON SALE AT PARTS DISTRIBUTORS
GET THE COMPLETE GERNSBACK LIBRARY

- PROBES — \$2.50
- RADIO-CONTROL HANDBOOK — \$2.25
- THE OSCILLOSCOPE — \$2.25
- TRANSISTORS — THEORY AND PRACTICE — \$2.00
- TV REPAIR TECHNIQUES — \$1.50
- RADIO & TV TEST INSTRUMENTS — \$1.50
- HIGH-FIDELITY—Design, Construction, Measurements — \$1.50
- RADIO & TV HINTS — \$1.00
- TELEVISION TECHNOTES — \$1.50
- RADIO TUBE FUNDAMENTALS — \$1.00
- BASIC RADIO COURSE — \$2.25
- MODEL CONTROL BY RADIO — \$1.00
- HIGH-FIDELITY TECHNIQUES — \$1.00
- PUBLIC-ADDRESS GUIDE — 75¢
- PRACTICAL DISC RECORDING — 75¢

Gernsback Publications, Inc.
Publishers of RADIO-ELECTRONICS
25 West Broadway New York, N.Y.

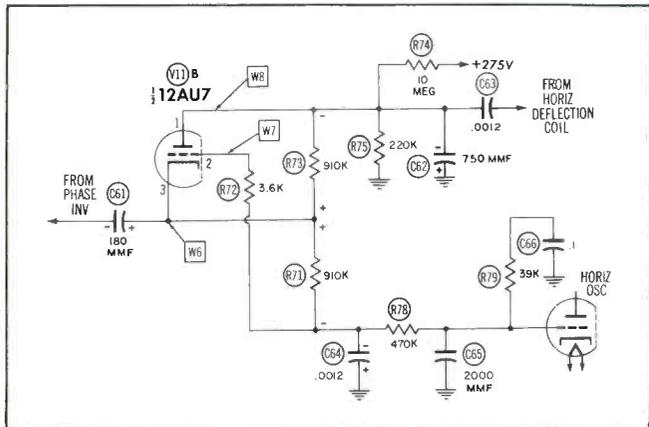


Fig. 4. Phase Detector in General Electric Model 21T17.

When this strong negative pulse is applied to the cathode of the phase detector, the tube conducts. During pulse time, both the grid and plate are positive with respect to the cathode; and both draw current. The operation of this circuit depends upon the proportion between the current drawn by the grid circuit and that drawn by the plate circuit.

At the end of the pulse, C62 and C64 are charged in the polarity shown in Fig. 4. The cathode side of C61 is positively charged. Between pulses, the capacitors discharge as follows. The discharge path in the plate circuit is from the top of C62 through R73, C61, the phase inverter, ground, and back to the bottom of C62. The discharge path in the grid circuit is from the top of C64 through R71, C61, the phase inverter, ground, and back to the bottom of C64. The time constant of each discharge path is long.

Between pulses, the voltage developed across R71 is opposite in polarity to that across R73; and the values of the components in the phase

detector are chosen so that these voltages will be equal if the free-running frequency of the oscillator is the same as that of the sync signal.

When the oscillator frequency is too low, the sawtooth wave lags behind the sync pulses. The tube conducts at a time when the sawtooth wave is at a value more negative than normal. The grid voltage during the sync pulse is approximately the same as normal. Since plate current in a triode is proportional to plate voltage, provided that the grid voltage is constant, the proportion of cathode current going to the plate is reduced. The charge on C62 is lower than it is when the oscillator frequency is correct. The voltage developed across R73 between pulses is lower than that across R71; therefore, the resultant correction voltage is negative, and the speed of the multivibrator increases.


The sequence of events is exactly the opposite when the oscil-

**DON'T
JUST SAY
CAPACITORS**

Ask For
Sprague
By Catalog
Number

Know what you're getting . . . get exactly what you want. Don't be vague . . . insist on Sprague. Use complete radio-TV service catalog C-610. Write Sprague Products Company, 105 Marshall Street, North Adams, Massachusetts.

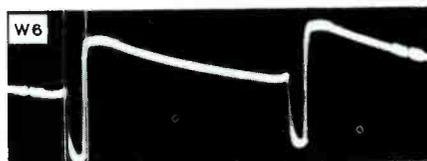SPRAGUE
WORLD'S LARGEST
CAPACITOR MANUFACTURER



(A) On Cathode.



(B) On Grid.



(C) On Plate.

Fig. 5. Waveforms Observed in the Circuit of Fig. 4.

RCA SERVICE PARTS • FACTORY-TAILORED TO SAVE YOU TIME AND MONEY

take
**RECORD
CHANGER**
PARTS
for
example



RCA Service Parts for RCA Victor record-changers and "Victrola"® phonographs are specifically designed to save you time and money by fitting right, installing fast. Record-changer parts are an especially important example of how every RCA Service Part is factory-tailored to keep your servicing "on the go" profitably. Remember: RCA Service Parts are the only genuine replacement parts for RCA Victor phonographs, record-changers, radios, and TV receivers.

RCA RADIO CORPORATION
of AMERICA
SERVICE PARTS HARRISON, N. J.

BE *Sure* with



TV
antenna cable and
tubular twin-lead
Made from Virgin
POLYETHYLENE



Famous for Quality and Performance since the very beginning of commercial radio! CORNISH TV Antenna Cables and Tubular Twin-lead are packaged now, so that your customers just can't miss them. They'll be looking for these brilliant orange-and-black displays . . . the countersign of superior service.

Write for Complete Illustrated Catalog of Radio-TV Products

"MADE BY ENGINEERS FOR ENGINEERS"

CORNISH WIRE CO., INC.
50 Church Street New York 7, N. Y.



lator tends to run at a frequency faster than that of the sync signal. The charge on C62 is higher than usual, the voltage across R73 is greater than that across R71, and the correction voltage is positive.

The value of the positive correction voltage that can be supplied is limited because the grid of the multivibrator will draw current and some of the positive voltage will be neutralized when the bias of the multivibrator is reduced beyond a certain point.

The circuit found in the General Electric Model 21C106 has a phase detector which includes a slight modification of the system used in the Model 21T17. Resistor R72 has been removed, and R71 has been replaced with a potentiometer and a small fixed resistor. The circuit has been modified to accommodate the characteristics of the 5U8 tube used as the phase detector and to permit the inclusion of the potentiometer which is called the phase-balance control.

If there is synchronization at only one extreme of the horizontal-hold control or if there is unstable horizontal synchronization, the technician should not immediately look for defective components in the phase detector and horizontal oscillator. The input signals to the phase detector should be checked first with an oscilloscope to make sure that the proper waveforms are arriving and that stray noise pulses are being kept out.

The horizontal-oscillator coil may need adjustment, especially if a new tube has been installed. To make this adjustment, the technician should follow the instructions given in the service notes for the set concerned.

Component deterioration short of actual failure will tend to have a considerable effect on phase detectors. Leakage in a capacitor, gas in a tube, or any change in the value of a resistor will have a more marked effect in phase-detector circuits than in many other applications.

THOMAS A. LESH

MASKS. In a Dick Rogers cartoon in *Electrical Merchandising*, one lady has just taken a 7-inch mask off a TV console to reveal a 10-inch mask framing the picture while explaining to the other lady, "I bought a 21-inch set last week and I'm breaking the news to my husband gradually."

MARKUS • • Dollar and Sense Servicing

**NEW
IMPROVED**

Senco FILAMENT CHECKER



Now ONLY \$2.75
DEALER NET
With Leads \$2.95


COMPLETELY NEW **MORE VERSATILE LOWER COST**

- Automatically checks ALL TUBES including locals and pix tube.
- Continuity and voltage tester—no switches, merely plug in test leads.

Ask your Jobber to see the New Senco Checker.

SERVICE INSTRUMENTS CO. ADDISON, ILLINOIS
"ADDISON INDUSTRIAL DISTRICT"

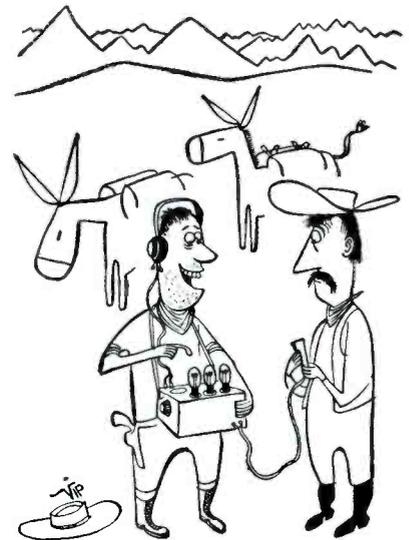Insert Leads in Pins 1 & 12 of Pix Tube Socket



*"This bulb indicates gold.
This one lights up for Uranium
—and this one spots
JENSEN NEEDLES."*

**Joe
Serviceman
says:**



**"You can't get somethin'
for nothin', especially
Quality and Reliability"**

QUIETROLE

TRADE MARK REG. U.S. PAT. OFF.



the original lubricant and cleaner for quieting noisy controls and switches, costs little more than the cheapest imitations, but the name assures you are getting the best.

INSIST ON QUIETROLE

"The Choice of Better Service Dealers Everywhere"




manufactured by
**QUIETROLE
COMPANY**

Spartanburg, South Carolina

ask the
"Man-on-the-Roof"
why he prefers

South River

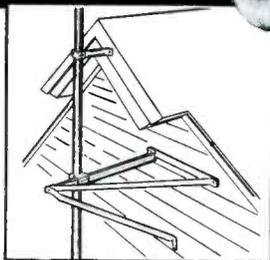

COMBINATION STEEL ADJUSTABLE WALL BRACKET—Model ST3-18A

All steel construction; Hot-Dip galvanized to prevent corrosion. 18" lower bracket featuring embossed steel bracing leg, is adjustable for vertical mast mounting under eave. 3" embossed steel top bracket with "reversed" U bolt and clamp permits use of Spintite for nut tightening.

Write for 1955 Catalog

**SOUTH RIVER
METAL PRODUCTS CO., INC.**
South River, New Jersey

pioneer & outstanding producer of finest line of antenna mounts


Antennas— the Eyes of TV Receivers

(Continued from page 5)


to respond to a wider range of frequencies if the diameter of the receiving elements is increased. See Fig. 1B.

A cone-shaped receiving element like that shown in Fig. 1C will also increase the frequency coverage, but this shape presents a high resistance to wind; therefore, it has been supplanted by the fan shape shown in Fig. 1D. An antenna with the latter shape is referred to as a conical antenna.

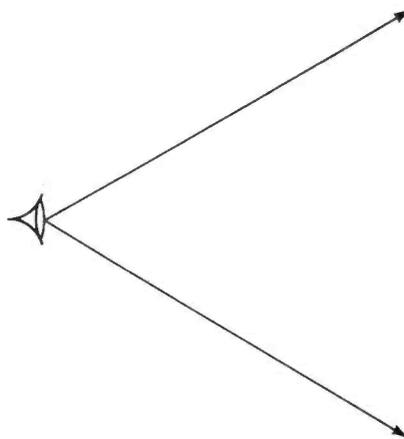
Still another method of obtaining wide-band operation is by using multiple receiving elements. See Fig. 1E. This antenna makes use of more than one receiving element, each tuned




(A) Field of Vision With Unaided Eye.

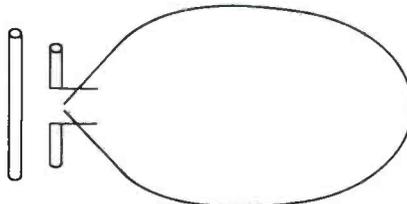

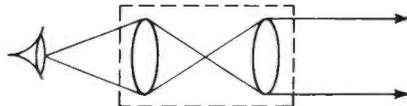(B) Field Pattern of Antenna Without Directors.



(C) Field of Vision With Telescope.

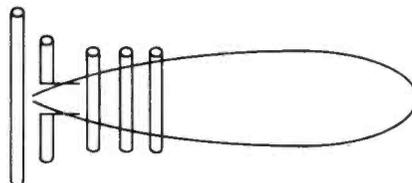

(D) Field Pattern of Antenna With Directors.

Fig. 2. Fields of Vision Compared to Field Patterns of Television Antennas.

3 * CR MORE NEW TRIAD * CORRECT REPLACEMENT FLYBACKS

These three new flybacks are mechanically correct and electrically correct, ruggedized versions of manufacturer's items — precisely engineered by TRIAD for specific makes and models — to give exceptionally high performance and long, trouble-free service.

		
D-52 List Price \$7.15 *Correct Replacement for RCA 75519, 75585, 76381.	D-53 List Price \$7.45 *Correct Replacement for RCA 76501, 76672.	D-56 List Price \$9.50 *Correct Replacement for Airking, CBS, Silver- tone, 10104, 10107, 10108, 10110, 10126, 10135.



** COMPOSITE REPLACEMENT

Triad flybacks wherever possible are COMPOSITE items designed to provide correct electrical and mechanical characteristics for as many television chassis as possible.

Ask your distributor, or write, for Catalog TV-155C



Triad *CR Transformers are listed in Sams Photofact folders and Counter-Facts.

4055 Redwood Ave. • Venice, Calif

the VITAMETER

AN INSTRUMENT DESIGNED TO MAINTAIN, IMPROVE and VITALIZE OPERATION OF CATHODE RAY TUBES



10,000 In Active Use

IT'S PORTABLE

WEIGHT ONLY 10 LBS.

Unique reactivator function is accomplished by dynamic sweep between cathode and grid . . . removing gas ions and stale emitting material from surface of cathode tube.

the VITAMETER

- analyzes performance characteristics
- locate and remove inter-element shorts
- repairs open elements
- welds open filaments
- restores or improves emission quality
- estimates tube life expectancy

only \$6995

At your distributor or write for bulletin.

The VITAMETER is handsomely designed and housed in rugged steel case to insure long and dependable service. It is light, compact, portable and therefore can be used on picture tube while it is still in the cabinet. Just plug in and attach instrument socket to C.R. Tube . . . easy to read indicators tells the whole accurate story at a glance. VITAMETER repairs tubes right-on-the-spot.

ELECTRONIC TEST INSTRUMENT CORP. 13224 LIVERNOIS AVENUE DETROIT 38, MICHIGAN

to a different frequency range and connected or coupled in such a manner that signals can be received over a wide range of frequencies.

The human eye, by reason of its unchangeable design, responds only to a limited range of light frequencies from red to violet. On the other hand, the frequencies to which an antenna responds can be changed by lengthening or shortening the elements. As the element length is increased, the frequencies to which an antenna responds become lower; and as the element length is decreased, the frequencies to which it responds become higher. For this reason, we can choose an antenna which will respond to any frequencies we wish to receive.

Improving Performance

Once the receiving element has been decided upon for a particular range of frequencies, we then have a similarity to the human eye. In the case of the human eye, improvements upon its operation depend upon the addition of a system of lenses and mirrors; whereas, improvements upon the abilities of the receiving element of the antenna are dependent upon the addition of directors and reflectors.

When directors and reflectors are used in a manner similar to the use of lenses and mirrors, they are sometimes referred to as parasitic elements. These elements are not electrically connected to the receiving element, and their action is dependent entirely upon mutually induced fields created by the incoming radio wave. Hence, the name "parasitic" elements is derived. The parasitic elements play a large part in shaping the field pattern of the television antenna.

The normal field of vision of the human eye is changed when lenses are placed in front of the eye, as shown in Figs. 2A and 2C. An example is the telescope which creates a narrow field of vision. Directors can be thought of as lenses which act upon the radio waves arriving from the forward direction to a greater degree than on signals arriving from other angles. The director is placed in front of and parallel to the receiving element. The receiving element then makes use of the director to look down a narrow field of receptivity in much the same manner that a telescope is used by the eye to look at a distant point. Figs. 2B and 2D show field patterns of antennas with and without directors.

Let us refer back to the example of strong surrounding light

PERMO'S SALES INDEX

A factor of the relative national rate of movement of each type of needle to other types

Permo Needle Number	Unit Price	Dealer Unit Price	Dealer Unit Price	Index	Type of Needle	Permo's % Material & Size
A-300	\$2.50	\$1.50	\$1.47	7.9	33 1/2 & 45	Shielded Jewel .001
A-304	1.50	.90	.88	2.3	33 1/2 & 45	Permo Metal .001
B-310	1.00	.50	.49	136.3	33 1/2, 45 & 78	Permo Metal .002
A-318	1.50	.90	.88	1.3	33 1/2 & 45	Permo Metal .001
C-320	1.50	.90	.88	17.9		Permo Metal .001
B-334	2.50	1.50	1.47	6		Shielded Jewel .001
C-340	25.00	15.00	14.70	0		Diamond
C-360	2.50	1.50	1.47	0		
C-360D	25.00	15.00	14.70	11.6		
A-311	1.50	.90	.88	7.3	33 1/2 & 45	Permo Metal .001
A-312	1.50	.90	.88	30.2	33 1/2 & 45	Permo Metal .001
C-312	25.00	15.00	14.70	7.8	33 1/2 & 45	Permo Metal .001
AC-313	3.00	1.80	1.76	4.7	33 1/2 & 45	Permo Metal .001
AC-312D3	26.50	15.90	15.58	1.4	33 1/2 & 45	Shielded Jewel .001

DEALER PRICE

Keeps you from being "STUCK" with once-a-year sellers . . .

PERMO PHONO NEEDLES

PERMO, INC. CHICAGO 26

NOW! Service Dealers can offer the finest in on an investment of only \$495**

HI-FI

TRANSVISION Lifetime MATCHED HI-FI UNITS enable you to undersell ALL competition at a good profit! You get full Dealer Price Protection—and more!

**How? Ask your distributor or write for details about our "Dealer Hi-Fi Program."

FOR The Finest MASTER AMPLIFIED AND COMMUNITY TV ANTENNA SYSTEMS-

— Send Us Your Problem for FREE Engineering Advice.

FREE: Important Technical Manual for Community and Master TV Systems

Ask your distributor or write to:

TRANSVISION, INC.

NEW ROCHELLE, N. Y. NE 6-6000

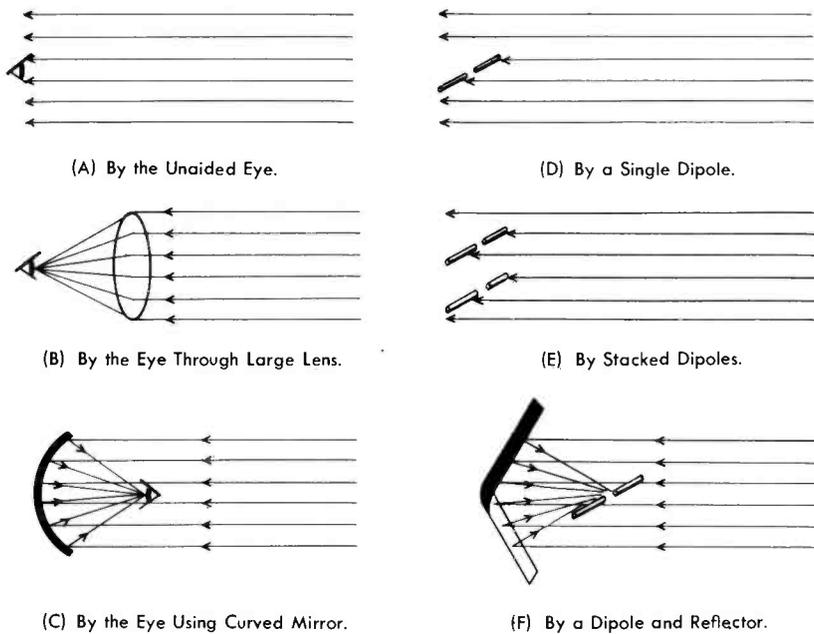


Fig. 3. Amounts of Energy That Are Intercepted.

blinding the eye. One method of looking at a neon sign in the daylight would be to cup the hands over the eyes to shield them from the bright light. The antenna cannot be shielded in the same manner from interference, but a large screen can be mounted in back of the receiving element. This screen will reduce the interference from the back side. In addition, a system of directors will narrow the field pattern and reduce the amount of interference picked up by the receiving element. The reflector and directors will allow clearer reception of the television signal. This is similar to using a telescope or long tube to narrow the field of vision and to reduce the strong interfering light so that a distant neon sign will appear clearer and brighter.

The problem of the limited receiving area of the human eye, as shown in Fig. 3A, has been solved by increasing the sizes of the lenses and mirrors that are used with the eye.

In Fig. 3B, a large lens intercepts more of the arriving light waves for the eye to use. In Fig. 3C, a large curved mirror collects light and directs it upon the eye. The 200-inch mirror used at the observatory on Mt. Palomar to collect light from the stars is the best example of this method of increasing the amount of light available to the eye.

Fig. 3E shows an array of stacked antennas which present a large receiving area and intercept more of the incoming radio waves in comparison with the amount intercepted by the single antenna in Fig. 3D. The broadside and collinear arrays are examples of this method of increasing the receiving area presented to radio waves. A curved reflector is used in Fig. 3F. The radio waves striking the large area of the reflector are directed back upon the receiving element, and the strength of the received signal is increased.


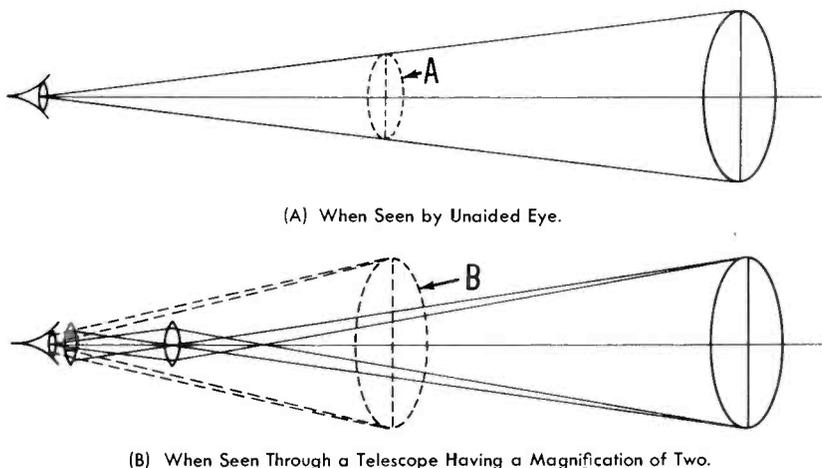


Fig. 4. Apparent Size of an Object.

WANTED

FOR VALUE

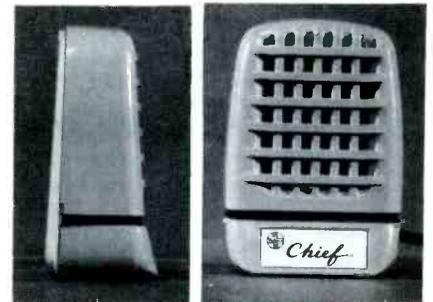An amateur, P. A. and tape recording microphone known to be in the vicinity of the price people want to pay



TURNER

MODEL 808 CRYSTAL

Response: 60—7,000 c.p.s.
Level: -49 db.

ALIAS

MODEL 807 CERAMIC

Response: 80—7,000 c.p.s.
Level: -57 db.

ALIAS

MODEL 809 MAGNETIC

Response: 100—8,000 c.p.s.
Level: -52 db.

ALIAS

THE CHIEF

Subject microphone has been seen in desk, stand and hand use where quality was demanded, accompanied by compact size and low cost. By virtue of its good looks and versatility, the Chief is sought by the public for economical amateur use, public address and paging, and is ideal original or replacement equipment for tape recorders. Chief Model 808 has moisture sealed crystal, is wind and blast proof. Ruggedness, good performance and resistance to high humidity and heat are characteristic of Chief Model 809 with magnetic interior. Chief Model 807 with ceramic interior has heat and humidity resistance at a lower cost.

For complete information, write today to



949 17th Street, N. E.,
Cedar Rapids, Iowa

For full details see Literature Service Insert following page 86.

1st with all prices

Dave Rice's Official Pricing Digest answers a need long-felt by Servicemen—List or resale prices for every replacement part or component at your fingertips.

Over 300 pages; covers more than 60,000 items

Compiled like a telephone book (1) Alphabetical by Manufacturer (2) Alphabetical by Product Category (3) Numerical by Part Number. Price and identify any replacement item in seconds—as easy as 1-2-3.

1st handy sized reference in the industry

9 3/4" long by 3 3/4" wide . . . convenient for counter, pocket, tool box or tube caddy.



1st completely revised four times each year

Publication dates are October, January, April and July. Prices will be current on each publication date.

1st in savings

Time and money savings—no wasted effort—no calls to your distributor to check prices. No undercharges—no overcharges when you price your tubes and parts from the Official Pricing Digest.

1st issue October, 1955

PRICE \$2.50 PER COPY—will pay for itself many times over by giving you CORRECT PRICES where and when you need them.

available exclusively thru your parts distributor

See him now and place your order for the first issue.

Electronic Publishing Co., Inc.
180 North Wacker Drive
Chicago 6, Illinois

Directors and reflectors may be combined with the receiving element to produce a variety of antenna arrays which can then be used singly or grouped together to form more complex arrays.

In any antenna array, there are three important characteristics to be considered. These are the directivity, the gain, and the terminal impedance. Similarly, in an optical system, three factors are of importance: the field of vision, the amount of amplification, and the ability to focus over the entire visible frequency spectrum.

Directivity

Let us consider the field of vision of a pair of binoculars. A pair with a very narrow field angle would be used to look at a single distant object. If these binoculars were used to watch a number of objects, the narrow angle would cut off some of the objects from view. A wide-angle pair of binoculars might allow you to see all of the objects.

An analogy to this would be a highly directive antenna being used in a location where signals are to be received from more than one direction. A highly directive antenna has the ability to receive a signal from one direction while rejecting signals from others. In this case, the signal arriving from a direction other than from the front would be rejected or at best would be received very poorly.

Gain

The second characteristic to be considered is gain. In a telescope, this is rated according to the amount of image amplification realized. Fig. 4 shows a comparison between the image A as seen by the eye and the enlarged image B as seen through a telescope. A magnification of two has the effect of bringing the object halfway toward you. The area of the object will then appear four times as big. The latter effect is analogous to antenna gain.

To describe the gain of an antenna, a reference point must be established. In most cases, the signal strength measured at the terminals of a dipole is used for this reference point. This dipole is called a reference dipole and is designed to be resonant at the frequency of the test signal. Assume that a signal strength of 100 microvolts is measured at the terminals of the dipole receiving element, as in Fig. 5A. The dipole is then replaced by an antenna array. The signal present at the terminals of the receiving element of the array


nothing...
no, **NOTHING!**



by the makers of
GEMCO Re-Fractors



Great Eastern M'fg Co.
B'klyn 12, N. Y.

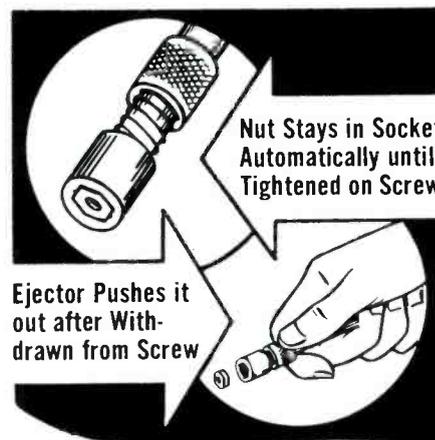

The Radio-TV Serviceman Will Save Time and Effort with this NEW

Ejection-Grip NUT DRIVER

Eliminates last nuts, screws or bolts. Specially designed to speed intricate assembly work. The internal tapered socket takes care of all size variations in nuts, bolts and screws. Non-magnetic. Non-jamming. Unconditionally guaranteed.

SET YOUR SIGHT ON

See Your Jobber

AMALITE inc.
1884 PITKIN AVENUE, BROOKLYN 12, N. Y.

is 400 microvolts. Refer to Fig. 5B. This is four times the signal received on the dipole, or the gain of the antenna array is four.


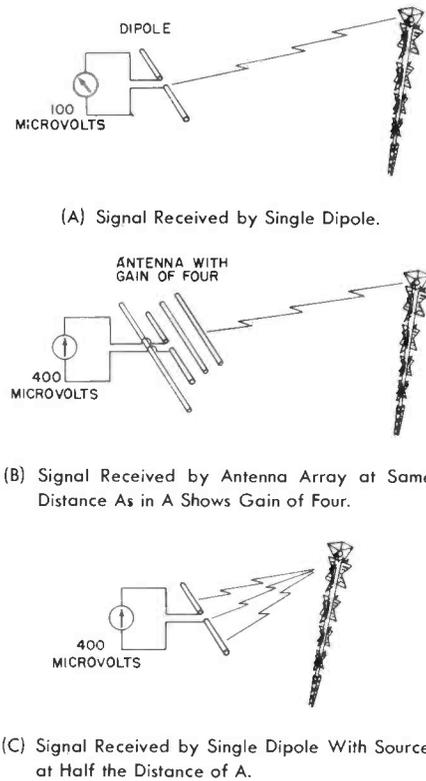


Fig. 5. Drawings Which Illustrate Antenna Gain.

The signal of 100 microvolts is received on the dipole from the signal source. If the signal source were closer by one half the distance, a signal of 400 microvolts would be received. Refer to Fig. 5C. This is the same amount of signal received on the antenna array. The addition of parasitic elements to the receiving element has effectively brought the transmitter closer to the receiving element.

Impedance

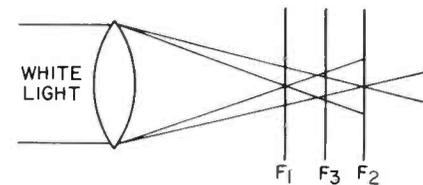The third important factor to consider is impedance. This is the



(A) Focus Points Have Different Positions for Different Light Frequencies.



(B) Impedance Values Are Different for Different Radio Frequencies.

Fig. 6. Plain Lens Compared to Dipole With Small-Diameter Elements.

most difficult of the antenna characteristics to explain. To form an analogy to antenna impedance, we will consider the ability of a lens to focus properly throughout the visible frequency spectrum.

A plain glass lens bends the high-frequency or violet light to a greater degree than it bends the low-frequency or red light. A beam of white light is directed through this lens in Fig. 6A. The violet light or high frequencies will focus at point F_1 ; the red light or low frequencies will focus at point F_2 . A compromise point at F_3 can be used for the focal plane, and both red and violet light will be slightly out of focus. At one frequency between the red and violet, the focus will be correct. The condition is known as chromatic aberration.

A similar situation exists in an antenna with a small-diameter receiving element. See Fig. 6B. At the resonant frequency, the impedance will be 72 ohms; and at frequencies off resonance, it will be more than 72 ohms. The maximum transfer of energy to a 72-ohm transmission line takes place when the terminal impedance of the dipole is 72 ohms; therefore, at frequencies other than the resonant frequency, the transfer of energy to the transmission line will be less.

Fig. 7A shows two lenses composed of two types of glass cemented together to form a single lens which causes all light frequencies in the visible spectrum to focus at point F_3 . Similarly, the dipole can be made to retain an impedance match of 72 ohms over a given frequency band by increasing the diameter of the receiving elements, as in Fig. 7B.

In the design of a broad-band antenna, it is important that the impedance variation be as small as possible over the entire range of frequencies being received. A large variation in impedance at any frequency will result in a signal reduction at that frequency.

Let us review the three important characteristics of television antennas.

1. Directivity of an antenna is its ability to receive a signal from one direction and to reject simultaneously signals arriving from other directions.

2. The gain of an antenna is the ratio between the signal voltage

AVAILABLE through all jobbers!

AT NO EXTRA COST

All packaged "Columbia" 300 ohm line now has open spade terminals securely attached to one end of line for perfect antenna attachment . . . PLUS 2 loose terminals for set attachment . . . AT NO EXTRA COST.

A wonderful time saver for the serviceman . . . 60 ft., 75 ft., and 100 ft. coils of high quality 300 ohm television line. Terminals slide easily under screw heads in seconds. Loose terminals are easily attached with a pair of pliers.

Television line and terminals are packed in a heat sealed, clear polyethylene bag, insuring a clean, dry, dust free item until used.



ORDER this money and time-saver TODAY!

WIRE & SUPPLY CO.

2850 Irving Park Road • Chicago 18, Ill.



Columbia

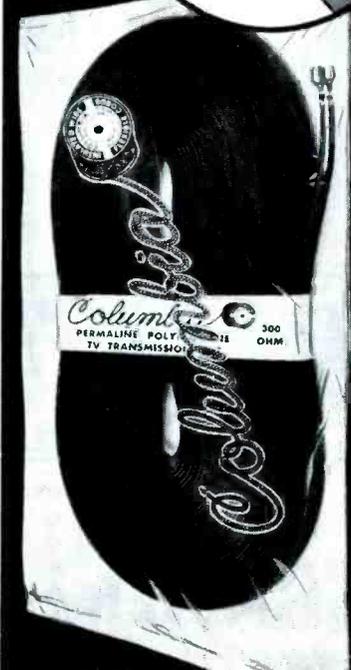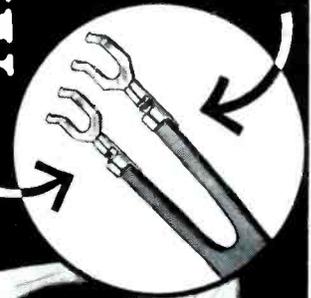

Have you received your FREE COPY of "Columbia's" newly enlarged 36-page catalog?

Now IN YOUR DISTRIBUTOR'S STOCK

GRAMER-Halldorson REPLACEMENTS FOR...

44 EXACT REPLACEMENT FLYBACKS
with **19** MOUNTING-STYLES
"BETTER THAN ORIGINALS"

☆ Exclusive PLASKOIL process virtually encapsulates vital windings . . . ☆ Permits safer, heat-resistant operation . . . ☆ Guards against flash-overs and breakdowns . . . ☆ Corona-resistant . . . ☆ Non-hygroscopic . . . protects from moisture . . . ☆ Structurally stronger . . . will not chip or crack . . .


You are assured of complete customer satisfaction when using GRAMER-HALLDORSON Flybacks, Deflection Yokes and other components as replacements.

ADMIRAL
AIR KING
AIRLINE
AMBASSADOR
APEX
BRUNSWICK
CAPEHART
CBS-COLUMBIA
CROSLY
CROYDON
DUMONT
EMERSON
FIRESTONE
GENERAL ELECTRIC
HALLICRAFTERS
HOFFMAN
LAFAYETTE
MAGNAVOX
MAJESTIC
MECK
MOTOROLA
MUNTZ
OLYMPIC
PACKARD BELL
PHILCO
RCA
RAYTHEON
SENTINEL
SHERATON
SILVERTONE
SPARTON
STARRETT
STROMBERG-CARLSON
SYLVANIA
TRUETONE
VIDEO PRODUCTS
WELLS - GARDNER
WESTINGHOUSE
ZENITH
(and many others)


write FOR CATALOG **G-24**
listing the sweep components and transformers. Send name of your nearest distributor

available at the terminals of the test antenna and the signal voltage which would be developed at the terminals of a reference dipole.

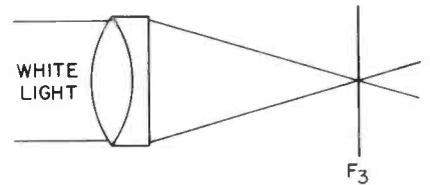3. The terminal impedance of an antenna is the reactance in ohms at the antenna terminals. When the antenna is connected to a resistor having a resistance equal to the terminal impedance, maximum energy will be transferred from the antenna to the resistor. This maximum transfer of energy will also occur if the antenna is connected to a transmission line having a characteristic impedance equal to the terminal impedance of the antenna.



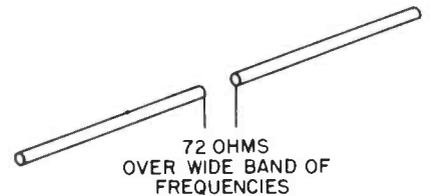(A) Focus Point Is Fixed for All Visible Light Frequencies.



(B) Impedance Value Is Constant for Wide Band of Radio Frequencies.

Fig. 7. Composite Lens Compared to a Dipole With Large-Diameter Elements.

In presenting the analogy between antennas and the human eye, we have attempted to create a different viewpoint from which to look at the television antenna and its characteristics.

The television antenna plays an important part in television reception. Its application and installation should be given the consideration that a person gives his own eyes when he purchases a pair of eyeglasses.

All types of television antennas will receive a television signal. Many types will give good results, but one antenna which is chosen for a particular area and properly installed will give the best results.

All Gramer-Halldorson Replacement parts are listed in Howard W. Sams Photofact Service.

GRAMER Halldorson **TRANSFORMER CORPORATION**
2734 NORTH PULASKI ROAD · CHICAGO 39, ILLINOIS

GEORGE B. MANN

PF REPORTER

CATALOG and LITERATURE SERVICE

valuable manufacturers' data available to our readers

- 1J. B & K (B & K Manufacturing Co.)**
Bulletin No. 500 describing DYNA-QUIK, Model 500, a new dynamic mutual conductance tube tester that completely tests, with laboratory accuracy, 99% of all tubes; and Bulletin 104 describing two new B & K Cathode Rejuvenator Testers—the CRT 400 and the CRT 200. *See advertisements pages 68, 69.*
- 2J. CBS (CBS-Hytron, a Division of CBS, Inc.)**
Flyer describing CBS tube promotion kit tying in with advertising on Arthur Godfrey's Talent Scouts and in Good Housekeeping Magazine. *See advertisement page 16.*
- 3J. CENTRALAB (Centralab, a Division of Globe-Union, Inc.)**
Information on how to obtain the Centralab "Pick-Ur-Pak" 4-drawer metal cabinet for storing capacitors and other small parts. *See advertisement page 62.*
- 4J. CLAROSTAT (Clarostat Manufacturing Co., Inc.)**
Precision Potentiometer, Series 42-900, Form No. 753793010. *See advertisement page 4.*
- 5J. CORNELL-DUBILIER (Cornell-Dubilier Electric Corp.)**
Vibrator Replacement Guide (VC). *See advertisement page 71.*
- 6J. EICO (Electronic Instrument Co., Inc.)**
Free EICO Catalog HS-9 describes complete line of 46 Kits and Wired Instruments, including oscilloscope, VTVM's, signal generators, tube testers, flyback testers, etc. *See advertisement page 78.*
- 7J. ELECTRONIC TEST (Electronic Test Instrument Corp.)**
Brochure on Vitameter. *See advertisement page 82.*
- 8J. FINNEY (The Finney Co.)**
Combined catalog and technical data sheet; engineering data folder; both on new GEOMATIC series antenna. *See advertisement page 34.*
- 9J. GENERAL CEMENT (General Cement Mfg. Co.)**
G-C No. S-57 New Products Supplement and Printed Circuit Service Manual. *See advertisement page 24.*
- 10J. GERNSBACK (Gernsback Publications, Inc.)**
Descriptive literature on the Gernsback Library Books. *See advertisement page 78.*
- 11J. HICKOK (The Hickok Electrical Instrument Co.)**
New 8-page Radio-TV Test Equipment catalog. *See advertisement page 65.*
- 12J. HYCON (Hycon Mfg. Co.)**
Catalog sheets on 616 Color Bar Generator, Model 622 5" Oscilloscope, 614 VTVM, and Model 617 3" Oscilloscope. *See advertisement page 56.*
- 13J. IRC (International Resistance Company)**
Form S-031, Auto Radio Control Replacements. *See advertisement 2nd cover.*
- 14J. JENSEN (Jensen Industries, Inc.)**
Jenselector (guide to correct needle) Wall Chart, (list of needles and cartridges); Catalog; Jenseedler, (guide to salespeople new in the needle field). *See advertisement page 80.*
- 15J. OHMITE (Ohmite Mfg. Co.)**
Bulletin No. 147 describes the line of Ohmite Axial Lead Vitreous Enameled All-Welded Construction Resistors. Includes tables of resistance values carried in stock with list prices. *See advertisement page 66.*
- 16J. PHAOSTRON (Phaostron Company)**
"777" VTVM. *See advertisement page 48.*
- 17J. RADIART (The Radiart Corp.)**
F-925 Vipower Catalog. *See advertisement insert.*
- 18J. SOUTH RIVER (South River Metal Products Co.)**
Complete catalog of Antenna Mounting Accessories. *See advertisement page 81.*
- 19J. SYLVANIA (Sylvania Electric Products, Inc.)**
Test Equipment Free Trial and Time Payment Plan. *See advertisement pages 26, 27, and 42.*
- 20J. TACO (Technical Appliance Corp.)**
Catalog 5010 on "Heavy-Duty" fully welded broad-band Yagi Antennas for communications. *See advertisement page 53.*
- 21J. TRANSVISION (Transvision, Inc.)**
Electronic Components Catalog (instruments, parts, kits, master antennas); "Hi-Fi" Catalog (speakers, cabinets, etc.). *See advertisement page 82.*
- 22J. TRIAD (Triad Transformer Corp.)**
New Triad TV Replacement Guide, TV-155, listing Triad correct replacement transformers for television use showing recommended Triad items for more than 100 television manufacturers and over 5800 models. *See advertisement page 81.*
- 23J. TURNER (The Turner Co.)**
Bulletin No. 969 describing the Turner Chief crystal, ceramic or magnetic microphone. *See advertisement page 83.*
- 24J. XCELITE (Xcelite, Inc.)**
Folder describing new, larger chrome plated hand reamers; also catalog on complete line of screwdrivers, nut drivers, pliers, kits. *See advertisement page 76.*

Please send me the following literature checked below:

1J	2J	3J	4J	5J	6J	7J	8J	9J	10J	11J	12J
13J	14J	15J	16J	17J	18J	19J	20J	21J	22J	23J	24J

Print plainly or type below

Name

Firm

Firm Address

City Zone State

Has your address changed since you last wrote us No Yes

To guarantee receipt of literature please check one of boxes below:

Independent Serviceman Dealer with Service Shop Student

Other (Please explain)

**OFFER GOOD
ONLY UNTIL
NOV. 1, 1955**

JUST CHECK AND MAIL THE CARD

1. Circle or check the corresponding numbers of literature you want to receive.

2. Fill in your complete name and address.

3. Detach and mail self-addressed card. No postage necessary.

COLOR TV TRAINING SERIES

QUESTIONS ON PART XVI

Part XVI of the Color TV Training Series appears in this issue and should be studied prior to reading the following questions.

These questions are presented to give the reader an opportunity to test himself on the color-television material discussed in this part.

1. What is the appearance of the screen when color synchronization is lost?
2. What is the best stage in which to begin the trouble-shooting procedure for the loss of color synchronization?
3. If the receiver employs a color killer, which tube is the only one that can cause loss of color synchronization?
4. What would be the result if the DC correction voltage applied to the oscillator-control stage were lost or had an incorrect value?
5. What indication on the screen points to improper color purity?
6. What circuits and components should be checked when improper color purity is present?
7. What indications in a monochrome picture point to misconvergence of the beams?
8. If the beams converge properly in the horizontal direction but not in the vertical direction, what is the procedure to follow for finding the cause of the trouble?

C.P.O. & V.M.R.

Lawrence H. Sams

RF
PUBLICATION

REPORTER


INDEX TO ADVERTISERS
September, 1955

Advertiser	Page No.
Amalite, Inc.	84
American Phenolic Corp.	52
Antenna Specialists Co., The	77
B & K Manufacturing Co.	68, 69
Blonder-Tongue Labs., Inc.	70
Bussmann Manufacturing Co.	6
CBS-Hytron	16
Centralab Div. of Globe-Union, Inc.	62
Chicago Standard Trans. Corp.	18
Clarostat Mfg. Co., Inc.	4
Columbia Wire & Supply Co.	85
Cornell-Dubilier Electric Corp.	71
Cornish Wire Co., Inc.	80
Electronic Instrument Co., Inc. (EICO).	78
Electronic Pub. Co., Inc.	84
Electronic Test Instrument Corp.	82
Erie Resistor Corp.	54
Finney Co., The	34
General Cement Mfg. Co.	24
General Electric Co.	Insert
Gernsback Publications, Inc.	78
Gramer-Halldorson Trans. Corp.	86
Great Eastern Mfg. Co.	84
Hickok Electrical Instrument Co.	65
Hycon Mfg. Co.	56
International Rectifier Corp.	28
International Resistance Co.	2nd Cover
Jackson Electrical Instr. Co.	73
Jensen Industries, Inc.	80
Jensen Mfg. Co.	44
Kenwood Engineering Co., Inc.	62
Littelfuse, Inc.	4th Cover
Mallory & Co., Inc., P. R.	10, 30
Ohmite Mfg. Co.	66
Oxford Electric Corp.	74
Permo, Inc.	82
Phaotron Co.	48
Planet Sales Corp.	75
Precision Apparatus Co.	20
Pyramid Electric Co.	22
Quietrole Co.	81
Radiart Corp. -Cornell Dubilier Electric Corp.	Insert
Radio Corp. of America	14, 79, 3rd Cover
Radio Merchandise Sales, Inc.	50
Raytheon Mfg. Co.	12
Sams & Co., Inc., Howard W.	46
Sangamo Electric Co.	40
Service Instruments Co.	80
South River Metal Products Co.	81
Sprague Products Co.	2 & 3, 68, 72, 79
Sylvania Electric Products Inc.	26 & 27, 42
Technical Appliance Corp.	53
Teletest Instruments Corp.	76
Thompson Products, Inc.	32
Transvision, Inc.	82
Triad Transformer Corp.	81
Tung-Sol Electric Inc.	38
Turner Co.	83
U. S. Electronic Research & Development Corp.	60, 61
V-M Corp.	73
Vokar Corp.	64
Ward Products Corp.	36
Webster Electric Co.	58
Weller Corp.	72
Xcelite, Inc.	76

FIRST CLASS
PERMIT No. 1076
(Sec. 34.9, P. L. & R.)
Indianapolis, Ind.

BUSINESS REPLY CARD
No Postage Stamp Necessary If Mailed in the United States

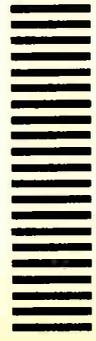3¢ POSTAGE WILL BE PAID BY
PF REPORTER
Reader's Literature Service Dept.
2201 EAST 46TH STREET
INDIANAPOLIS 5, IND.



While every precaution is taken to insure accuracy, we cannot guarantee against the possibility of an occasional change or omission in the preparation of the REPORTER.

Cumulative Index to PHOTOFAC FOLDERS

No. 52 • Covering Folder Sets Nos. 1 through 289 • World's Finest Electronic Service Data

HOW TO USE THIS INDEX

To find the PHOTOFAC Folder you need, first look for the name of the receiver (listed alphabetically below), and then find the required model number. Opposite the model, you will find the number of the PHOTOFAC Set in which the required Folder appears, and the number of that Folder. The PHOTOFAC Set number is shown in bold-face type; the Folder number is in the regular light-face type.

IMPORTANT—1. The letter "A" following a set number in the Index listing, indicates a "Preliminary Data Folder." These folders were designed to provide immediate basic data on TV receivers. Many of these were later superseded by regular Photofac Folders. In those cases where short production runs and/or limited distribution prevented availability of a sample chassis the "A" designation has been retained.

2. Models marked by an asterisk (*) have not yet been covered in a standard Folder. However, regular PHOTOFAC Subscribers may obtain Schematic, Alignment Data or other required information on these models without charge by supplying make, model or chassis number and serial number. (When requesting such data, mention the name of the Parts Distributor who supplies you with your PHOTOFAC Folder Sets.)

3. Production Change Bulletins contain data supplementary to certain models covered in previously issued PHOTOFAC Folders, and are listed in this Index immediately preceding the listing of the original coverage of the model or chassis. These Bulletins should be filed with the Folders covering the models to which the changes apply.

Set Folder No. No.	Set Folder No. No.	Set Folder No. No.	Set Folder No. No.
ADAPTOL	ADMIRAL—Cont.	ADMIRAL—Cont.	ADMIRAL—Cont.
CT-1..... 48-1	● Chassis 19A1 (Also see PCB 5—Set 106-1)..... 59-2	● Chassis 22F22 (Also See PCB 121—Set 275-1)..... 260-2	● Model T1822 (See Ch. 19B1, 19B1C)
ADMIRAL (Also see Record Changer Listing)	● Chassis 19A2, A, AZ, Z..... 271-1	● Chassis 22G2, 22G2Z (Also See PCB 121—Set 275-1)..... 260-2	● Model T2211 (See Ch. 19F1B)
Chassis UL5K1..... 30-1	● Chassis 19B1 (Also see PCB 112—Set 263-1)..... 210-2	● Chassis 22M1..... 180-2	● Model T2211A (See Ch. 19F2A)
Chassis UL7C1..... 25-2	● Chassis 19B1C (See PCB 112—Set 263-1 and Chassis 19B1—Set 210-2)	● Chassis 22M2, 22P2..... 222-2	● Model T2212 (See Ch. 19F1A or 19F1B)
Chassis 1HF1..... 25-2	● Chassis 19C1 (Also see PCB 112—Set 263-1, A, AZ, Z..... 271-1)	● Chassis 22N2 (Also See PCB 121—Set 275-1)..... 260-2	● Models T2215, T2216, T2217, T2218, T2219 (See Ch. 19A2)
Chassis 3A1..... 2-24	● Chassis 19D1 (Also see PCB 112—Set 263-1, A, AZ, Z..... 271-1)	● Chassis 22O1..... 180-2	● Model T2216A, T2217A (See Ch. 20A2)
Chassis 3C1 (Also see PCB 15—Set 126-1)..... 117-2	● Chassis 19E1 (Also see PCB 78—Set 219-1)	● Chassis 23A1..... 211-2	● Model T2222 (See Ch. 19F1 or 19F1C)
Chassis 3D1..... 266-1, 271-1	● Chassis 19E2, A..... 203-2	● Chassis 24D1, 24E1, 24F1, 24G1, 24H1 (Also see PCB 9—Set 114-1)..... 103-2	● Model T2226 (See Ch. 19F1)
Chassis 3G1..... 284-3	● Chassis 19F1, 19F1A (Also see PCB 112—Set 263-1, A, AZ, Z..... 271-1)	● Chassis 30A1..... 57-2	● Model T2232 (See Ch. 22F2)
Chassis 4A1..... 3-31	● Chassis 19F1B, 19F1C (See PCB 112—Set 263-1 and Chassis 19B1—Set 210-2)	● Chassis 30C1, 30D1..... 114-1	● Model T2236, T2237 (See Ch. 22A3)
Chassis 4E2..... 24-1	● Chassis 19F2AZ, Z..... 271-1	● Model C2215, C2216, C2217 (See Ch. 19A2)	● Model T2236Z (See Ch. 22A3Z or 22A3AZ)
Chassis 4D1..... 49-1	● Chassis 19H1, 19K1 (Also see PCB 112—Set 263-1)..... 210-2	● Model C2216Z (See Ch. 20A2Z)	● Model T2239Z (See Ch. 22A3Z)
Chassis 4HF1..... 258-2	● Chassis 19J1, A..... 271-1	● Model C2225, C2226, C2227 (See Ch. 22A3Z)	● Model T2239 (See Ch. 22A3)
Chassis 4H1..... 71-2	● Chassis 19K2AZ, Z..... 271-1	● Model C2225Z, C2226Z, C2227Z (See Ch. 22A3Z)	● Model T2242 (See Ch. 19K1)
Chassis 4J1, 4K1..... 77-1	● Chassis 19L1..... 271-1	● Model C2236, C2237 (See Ch. 19A2)	● Model T2301Z, ZN, T2302Z, ZN (See Ch. 18XP4BZ)
Chassis 4L1..... 100-1	● Chassis 19M2, 19M2Z..... 266-1	● Model C2236A (See Ch. 20A2)	● Models T2316Z, T2317Z, T2318Z, T2319Z (See Ch. 21A3Z)
Chassis 4R1..... 108-3	● Chassis 19N1 (See PCB 78—Set 219-1 and Ch. 19E1—Set 203-2)	● Model C2246 (See Ch. 19F1B)	● Models T2326Z, ZN, T2327Z, ZN (See Ch. 18XP4BZ)
Chassis 4S1..... 100-1	● Chassis 19N2Z..... 266-1	● Model C2246Z (See Ch. 19F1B)	● Models TA1811, TA1812, TA1822 (See Ch. 19W1)
Chassis 4T1..... 143-2	● Chassis 19P1..... 271-1	● Model C2316Z, C2317Z, C2319Z (See Ch. 21A3Z)	● Models TA2215, TA2216, TA2217, TA2218 (See Ch. 19L2)
Chassis 4W1..... 143-2	● Chassis 19Q1..... 271-1	● Model C2326Z, C2327Z (See Ch. 21A3Z or 21A3AZ)	● Model TA2222 (See Ch. 19W1 or 19W1C)
Chassis 4X1..... 261-1	● Chassis 19R1..... 271-1	● Model C2362Z, C2367Z (See Ch. 21G3Z)	● Model TA2226 (See Ch. 19W1)
Chassis 4Z1 (See Model 4Z1)..... 100-1	● Chassis 19S2, 19T1, 19T1C..... 266-1	● Model CA2215Z, CA2216Z, CA2217Z (See Ch. 19L2Z)	● Model TA2242 (See Ch. 19S2)
Chassis 5A3..... 191-2	● Chassis 19T2, 19T2A (See PCB 112—Set 263-1 and Chassis 19B1—Set 210-2)	● Model CA2236, CA2237 (See Ch. 19L2)	● Model TS2301Z, ZN, TS2302Z, ZN (See Ch. 18S4BZ)
Chassis 5B1 (See Model 6T02—Set 1-20)..... 4-24	● Chassis 19W1, A, B, C, 19Y1A..... 266-1	● Model CU2215, CU2216, CU2217 (See Ch. 19B2)	● Model TS2326Z, ZN, TS2327Z, ZN (See Ch. 18S4BZ)
Chassis 5B1A..... 18-1	● Chassis 20A1, 20B1 (Also see PCB 23—Set 140-1)..... 77-1	● Model CU2225, CU2226, CU2227 (See Ch. 22B3)	● Model TU1811, TU1812 (See Ch. 19S1)
Chassis 5B2..... 100-1	● Chassis 20A2, 20A2Z..... 256-2	● Model CU2225Z, CU2226Z, CU2227Z (See Ch. 22B3Z)	● Model TU1822 (See Ch. 19S1)
Chassis 5C3..... 197-2	● Chassis 20D2..... 256-2	● Model CU2225Z, CU2226Z, CU2227Z (See Ch. 22B3Z)	● Model TU2215, TU2216, TU2217, TU2218, TU2219 (See Ch. 19B2)
Chassis 5D2..... 118-2	● Chassis 20T1 (Also see PCB 15—Set 126-1 and PCB 26—Set 146-1)	● Model CU2236, CU2237 (See Ch. 19B2)	● Model TU2222, TU2226 (See Ch. 19J1)
Chassis 5D3..... 256-3	● Chassis 20V1 (Also see PCB 15—Set 126-1 and PCB 26—Set 146-1)	● Model F2216Z, F2217Z, F2218Z (See Ch. 22A3Z)	● Model TU2232 (See Ch. 22G2Z)
Chassis 5D3A (See Ch. 5D3—Set 256-3)..... 139-2	● Chassis 20X1, 20Y1..... 100-1	● Model F2216Z, F2217Z, F2218Z (See Ch. 22A3Z)	● Model TU2236, TU2237 (See Ch. 22B3)
Chassis 5E2..... 224-2	● Chassis 20Z1 (Also see PCB 7—Set 110-1)..... 100-1	● Model F2226Z (See Ch. 20A2Z)	● Model TU2236Z, TU2237Z (See Ch. 22B3Z)
Chassis 5E3..... 57-1	● Chassis 21A1 (Also see PCB 23—Set 140-1)..... 77-1	● Model F2226Z (See Ch. 20A2Z)	● Model 3G18 (See Ch. 3G1)
Chassis 5G2..... 137-2	● Chassis 21A2 (Also see PCB 23—Set 140-1)..... 77-1	● Model F2226Z (See Ch. 20A2Z)	● Models 4C26, 4C27, 4C28 (See Ch. 4D1)
Chassis 5H1..... 26-1	● Chassis 21A3AZ..... 275-2	● Model F2226Z (See Ch. 20A2Z)	● Models 4H15, 4H16, 4H17 (A or B) (See Ch. 20A1)
Chassis 5J2..... 30-1	● Chassis 21A3Z..... 275-2	● Model F2226Z (See Ch. 20A2Z)	● Models 4H15, 4H16, 4H17, 4H18, 4H19 (S or SN) (See Ch. 30B1)
Chassis 5K1..... 160-1	● Chassis 21B1 (Also see PCB 25—Set 144-1 and PCB 79—Set 220-1)	● Model F2226Z (See Ch. 20A2Z)	● Models 4H18, 4H19 (C or CN) (See Ch. 30B1)
Chassis 5L2..... 157-2	● Chassis 21C1 (Also see PCB 25—Set 144-1)..... 118-2	● Model F2226Z (See Ch. 20A2Z)	● Models 4H115, 4H116, 4H117 (S or SN) (See Ch. 30B1)
Chassis 5M3..... 282-2	● Chassis 21C2 (Also see PCB 25—Set 144-1)..... 118-2	● Model F2226Z (See Ch. 20A2Z)	● Models 4H126A, B, C, CN (See Ch. 21A1)
Chassis 5N1..... 39-1	● Chassis 21C3..... 275-2	● Model F2226Z (See Ch. 20A2Z)	● Models 4H126 (S or SN) (See Ch. 30B1)
Chassis 5R1..... 165-3	● Chassis 21D1 (Also see PCB 25—Set 144-1)..... 118-2	● Model F2226Z (See Ch. 20A2Z)	● Models 4H137 (S or SN) (See Ch. 30B1)
Chassis 5R3..... 272-1	● Chassis 21E1 (See Ch. 21D1—Set 118-2 and PCB 25—Set 144-1)	● Model F2226Z (See Ch. 20A2Z)	● Models 4H137A, B (See Ch. 21A1)
Chassis 5S3..... 272-1	● Chassis 21F1, 21G1 (Also see PCB 30—Set 156-2 and PCB 46—Set 180-1)..... 135-2	● Model F2226Z (See Ch. 20A2Z)	● Models 4H145A, B, C, CN (See Ch. 20B1)
Chassis 5T3..... 68-1	● Chassis 21G2..... 275-2	● Model F2226Z (See Ch. 20A2Z)	● Models 4H155A, B (See Ch. 30B1)
Chassis 5T3..... 275-1	● Chassis 21H1, 21J1 (Also see PCB 25—Set 144-1)..... 118-2	● Model F2226Z (See Ch. 20A2Z)	● Models 4H155S, SN (See Ch. 30B1)
Chassis 5W1..... 79-2	● Chassis 21K1, 21L1 (Also see PCB 46—Set 180-1)..... 135-2	● Model F2226Z (See Ch. 20A2Z)	● Models 4H156S, SN (See Ch. 30B1)
Chassis 5X1..... 76-3	● Chassis 21M1, 21N1 (See PCB 30—Set 156-2, PCB 46—Set 180-1 and Ch. 21F1—Set 135-2)	● Model F2226Z (See Ch. 20A2Z)	● Models 4H157A, B (See Ch. 20B1)
Chassis 5Y2..... 204-2	● Chassis 21P1, 21Q1 (Also see PCB 30—Set 156-2 and PCB 46—Set 180-1)..... 135-2	● Model F2226Z (See Ch. 20A2Z)	● Models 4H157S, SN (See Ch. 30B1)
Chassis 5Y2..... 188-2	● Chassis 21R1, 21X2 (See PCB 62—Set 196-1 and Ch. 21W1—Set 177-2)	● Model F2226Z (See Ch. 20A2Z)	● Models 4H165A, B (See Ch. 20B1)
Chassis 6A1 (See Model 6T01—Set 1-19)..... 103-1	● Chassis 21Y1..... 177-2	● Model F2226Z (See Ch. 20A2Z)	● Models 4H165S, SN (See Ch. 30B1)
Chassis 6A2..... 48-2	● Chassis 21Z1, 21Z1A..... 177-2	● Model F2226Z (See Ch. 20A2Z)	● Models 4H175S, SN (See Ch. 30B1)
Chassis 6B1..... 53-1	● Chassis 22A2, 22A2A..... 180-2	● Model F2226Z (See Ch. 20A2Z)	● Models 4H181, 4H182 (See Ch. 19B1 or 19B1C)
Chassis 6C1..... 252-3	● Chassis 22A3, 22A3AZ, 22A3Z (Also see PCB 121—Set 275-1)..... 260-2	● Model F2226Z (See Ch. 20A2Z)	
Chassis 6E1, 6E1N..... 140-2	● Chassis 22B3, 22B3AZ, 22B3Z (Also see PCB 121—Set 275-1)..... 260-2	● Model F2226Z (See Ch. 20A2Z)	
Chassis 6J2..... 26-2	● Chassis 22C2..... 201-2	● Model F2226Z (See Ch. 20A2Z)	
Chassis 6L1..... 25-1	● Chassis 22E2..... 201-2	● Model F2226Z (See Ch. 20A2Z)	
Chassis 6M1..... 25-1	● Chassis 22F2..... 222-2	● Model F2226Z (See Ch. 20A2Z)	
Chassis 6M2 (See Ch. 6J2—Set 140-2)..... 78-1		● Model F2226Z (See Ch. 20A2Z)	
Chassis 6Q1..... 54-1		● Model F2226Z (See Ch. 20A2Z)	
Chassis 6R1..... 107-2		● Model F2226Z (See Ch. 20A2Z)	
Chassis 6V1..... 62-1		● Model F2226Z (See Ch. 20A2Z)	
Chassis 6W1..... 71-1		● Model F2226Z (See Ch. 20A2Z)	
Chassis 6Y1..... 75-1		● Model F2226Z (See Ch. 20A2Z)	
Chassis 7B1..... 18-2		● Model F2226Z (See Ch. 20A2Z)	
Chassis 7C1..... 25-2		● Model F2226Z (See Ch. 20A2Z)	
Chassis 7E1..... 36-1		● Model F2226Z (See Ch. 20A2Z)	
Chassis 7G1..... 54-2		● Model F2226Z (See Ch. 20A2Z)	
Chassis 8C1 (See Ch. 8D1—Set 67-1)..... 67-1		● Model F2226Z (See Ch. 20A2Z)	
Chassis 8D1..... 32-1		● Model F2226Z (See Ch. 20A2Z)	
Chassis 9A1..... 49-2		● Model F2226Z (See Ch. 20A2Z)	
Chassis 9E1..... 68-2		● Model F2226Z (See Ch. 20A2Z)	
Chassis 10A1..... 3-30		● Model F2226Z (See Ch. 20A2Z)	
Chassis 15HF1..... 258-2		● Model F2226Z (See Ch. 20A2Z)	
● Chassis 18X4BZ, 18X4EZ, 18X4FZ, 18X4GZ, 18X4HZ, 18X4JZ, 18X4KZ, 18X4LZ, 18X4MZ, 18X4NZ, 18X4OZ, 18X4PZ, 18X4QZ, 18X4RZ, 18X4SZ, 18X4TZ, 18X4UZ, 18X4VZ, 18X4WZ, 18X4XZ, 18X4YZ, 18X4ZZ..... 280-2		● Model F2226Z (See Ch. 20A2Z)	

NOTE: PCB Denotes Production Change Bulletin. Production Change Bulletin Nos. 1 Through 63 Are All Contained in Set No. A-200 • Denotes Television Receiver. Production Change Bulletin Nos. 64 Through 104 Are All Contained in Set No. A-250

ADMIRAL—Cont.

- Model 7C62A (See Ch. 6M1)
Models 7C63, 7C63-UL (See Ch. 7C1)
Model 7C63A (See Ch. 7C1)
Models 7C65B, 7C65M, 7C65W (See Ch. 7E1)
Model 7C73 (See Ch. 9A1)
Models 7G11, 7G12, 7G14, 7G15, 7G16 (See Ch. 7G3)
Models 7P32, 7P33, 7P34, 7P35 (See Ch. 5H1)
Model 7R741, 7R742, 7R743 (See Ch. 6L1)
Models 7T01, 7T01M-UL, 7T04, 7T04-UL (See Ch. 5N1)
Model 7T06 (See Ch. 4B1)
Model 7T10 (See Ch. 5K1)
Model 7T12 (See Ch. 4B1)
Models 7T14, 7T15 (See Ch. 5K1)
Models 8C11, 8C12, 8C13 (See Ch. 30A1 and Ch. 8C1)
Models 8C14, 8C15, 8C16, 8C17 (See Ch. 8C1)
Models 8D15, 8D16 (See Ch. 8D1)
Model 8R46 (See Ch. 3A1)
Models 9B14, 9B15, 9B16 (See Ch. 9B1)
Models 9E15, 9E16, 9E17 (See Ch. 9E1)
Models 12X11, 12X12 (See Ch. 20Z1)
Model 14R11, 14R12 (See Ch. 20T1)
Model 14R16 (See Ch. 20T1)
Model 15K21 (See Ch. 20T1)
Model 16M12 (See Ch. 20X1)
Models 16R11, 16R12 (See Ch. 21B1)
Models 17D1X10, 17D1X11, 17D1X12 (See Ch. 19B1)
Models 17K11, 17K12 (See Ch. 21F1)
Model 17K16 (See Ch. 21F1)
Models 17K21, 17K22 (See Ch. 21F1)
Models 17M15, 17M16, 17M17 (See Ch. 21F1)
Models 17D1X11, 17D1X12 (See Ch. 19S1)
Models 19A11S, SN, 19A12S, SN (See Ch. 19A1)
Models 19A15S, SN (See Ch. 19A1)
Models 20X11, 20X12 (See Ch. 20X1)
Model 20X122 (See Ch. 20X1)
Model 20X136 (See Ch. 20Y1)
Models 20X145, 20X146, 20X147 (See Ch. 20Y1)
Model 22X12 (See Ch. 20Z1)
Models 22X25, 22X26, 22X27 (See Ch. 20Z1)
Models 24A11, 24A12 (See Ch. 20A1)
Model 24A125 (See Ch. 20A1)
Model 24A125AN (See Ch. 20X1)
Models 24A126, 24A127 (See Ch. 20A1)
Models 24C15, 24C16, 24C17 (See Ch. 20B1)
Models 24R11, 24R12 (See Ch. 20T1)
Models 24X15, 24X16, 24X17S (See Ch. 20X1)
Models 25A15, 25A16, 25A17 (See Ch. 20A1)
Models 26R11, 26R12 (See Ch. 21B1)
Model 26R25 (See Ch. 24H1)
Model 26R25A (See Ch. 21B1)
Model 26R26 (See Ch. 24H1)
Model 26R26A (See Ch. 21B1)
Model 26R26S (See Ch. 24H1)
Model 26R26SA (See Ch. 21B1)
Model 26R36 (See Ch. 24H1)
Model 26R36A (See Ch. 21B1)
Model 26R37 (See Ch. 24H1)
Model 26R37A (See Ch. 21B1)
Models 26X35, 26X36 (See Ch. 24D1)
Models 26X36AS, S (See Ch. 21E1)
Model 26X37 (See Ch. 24D1)
Models 26X45, 26X46 (See Ch. 24H1)
Models 26X55, 26X56, 26X57 (See Ch. 24D1)
Models 26X55A, 26X56A, 26X57A (See Ch. 21D1)
Models 26X65, 26X66, 26X67 (See Ch. 24D1)
Models 26X65A, 26X66A, 26X67A (See Ch. 21D1)
Models 26X75, 26X76 (See Ch. 24D1)
Models 26X75A, 26X76A (See Ch. 21D1)
Models 27K12 (See Ch. 21F1)
Models 27K15, A, B, 27K16, A, B, 27K17, A, B (See Ch. 21F1)
Models 27K25, A, B, 27K26, A, B, 27K27, A, B (See Ch. 21F1)
Models 27K35, A, B, 27K36, A, B (See Ch. 21F1)
Models 27K46, A, B (See Ch. 21F1)
Models 27K85, 27K86, 27K87 (See Ch. 21F1)
Model 27M12 (See Ch. 21X2)
Models 27M25, 27M26, 27M27 (See Ch. 21F1)
Models 27M35, 27M36 (See Ch. 21F1)
Models 29X15, 29X16, 29X17 (See Ch. 24F1)
Model 29X25 (See Ch. 24F1)
Model 29X25A (See Ch. 21H1)
Model 29X26 (See Ch. 24F1)
Model 29X26A (See Ch. 21H1)
Model 29X27 (See Ch. 24F1)
Models 30A12, 30A13 (S or SN) (See Ch. 30A1)
Models 30A14, 30A15, 30A16 (See Ch. 30A1)
Models 30B15S, SN, 30B16S, SN, 30B17S, SN (See Ch. 30B1)
Models 30C15S, SN, 30C16S, SN, 30C17S, SN (See Ch. 30C1)
Models 30F15, A, 30F16, A, 30F17, A (See Ch. 20A1)
Models 32X15, 32X16 (See Ch. 20Z1)

ADMIRAL—Cont.

- Models 32X26, 32X27 (See Ch. 20Z1)
Models 32X35, 32X36 (See Ch. 20Z1)
Models 34R15, A, 34R16, A (See Ch. 20V1)
Model 36R37 (See Ch. 21C1)
Models 36R45, 36R46 (See Ch. 21C1)
Models 36X35, 36X36, 36X37 (See Ch. 24E1 and Ch. 5B2)
Models 36X35A, 37X36A, 36X37A (See Ch. 24E1 and Ch. 5B2)
Model 37F15, A, B, 37F16, A, B (See Ch. 21G1 or Ch. 21Q1 and Ch. 5D2)
Models 37F27, A, B, 37F28, A, B (See Ch. 21G1 or Ch. 21Q1 and Ch. 5D2)
Models 37F35, A, B, 37F36, A, B (See Ch. 21G1 or Ch. 21Q1 and Ch. 5D2)
Models 37F55, 37F56, 37F57 (See Ch. 21G1 or Ch. 21Q1 and Ch. 5D2)
Models 37K15, A, B, 37K16, A, B (See Ch. 21G1 or Ch. 21Q1 and Ch. 3C1)
Models 37K27, A, B, 37K28, A, B (See Ch. 21G1 or Ch. 21Q1 and Ch. 3C1)
Models 37K35, A, B, 37K36, A, B (See Ch. 21G1 or Ch. 21Q1 and Ch. 3C1)
Models 37K55, 37K56, 37K57 (See Ch. 21G1 or Ch. 21Q1 and Ch. 3C1)
Models 37M15, 37M16 (See Ch. 21G1 or Ch. 21Q1 and Ch. 3C1)
Models 37M25, 37M26, 37M27 (See Ch. 21Z1A)
Models 39X16, A, 39X17, A (See Ch. 24G1 and Ch. 5B2)
Models 39X16B, 39X17B (See Ch. 24G1 and Ch. 5D2)
Model 39X17C (See Ch. 21J1)
Models 39X25, 39X26 (See Ch. 24F1 and Ch. 5D2)
Models 39X25A, 39X26A (See Ch. 21J1)
Models 39X35, 39X36, 39X37 (See Ch. 21J1 and Ch. 3C1)
Models 47M15, A, 47M16, 47M17 (See Ch. 21Z1A)
Models 47M35, 47M36, 47M37 (See Ch. 21Z1)
Models 52M15, 52M16, 52M17 (See Ch. 21Y1)
Models 57M10, 57M11, 57M12 (See Ch. 21Z1A)
Model 121DX10 (See Ch. 19C1)
Model 121DX11 (See Ch. 19F1A)
Model 121DX12 (See Ch. 19C1)
Model 121DX12A (See Ch. 19C1 or 19F1)
Model 121DX16 (See Ch. 19C1)
Model 121DX16A (See Ch. 19C1 or 19F1)
Model 121DX16L (See Ch. 19K1)
Model 121DX17 (See Ch. 19C1)
Model 121DX17A (See Ch. 19C1 or 19F1)
Model 121DX17L (See Ch. 19K1)
Models 121K15, 121K16, 121K17 (See Ch. 21M1)
Models 121K15A, 121K16A, 121K17A (See Ch. 22M1)
Model 121M10 (See Ch. 22M1)
Models 121M11, 121M12 (See Ch. 21M1)
Models 121M11A, 121M12A (See Ch. 22M1)
Model 121UDX12 (See Ch. 19J1)
Models 121UDX16L, 121UDX17L (See Ch. 19L1)
Model 122DX12 (See Ch. 22F2)
Model 122DX12 (See Ch. 22G2)
Model 122DX15 (See Ch. 19C1)
Model 122DX15A (See Ch. 19C1 or 19F1)
Model 122DX15L (See Ch. 19K1)
Model 122DX16 (See Ch. 19C1)
Model 122DX16A (See Ch. 19C1 or 19F1)
Model 122DX16L (See Ch. 19K1)
Model 122DX17 (See Ch. 19C1)
Model 122DX17A (See Ch. 19C1 or 19F1)
Model 122DX17L (See Ch. 19K1)
Models 122DX26 (See Ch. 19C1)
Model 122DX26L (See Ch. 19K1)
Model 122DX38 (See Ch. 19C1)
Model 122DX38A (See Ch. 19C1 or 19F1)
Models 221K16, A (See Ch. 21K1)
Model 221K26 (See Ch. 21K1)
Models 221K35, 221K36 (See Ch. 21K1)
Models 221K45, 221K46, 221K47 (See Ch. 21M1)
Models 221K45A, 221K46A, 221K47A (See Ch. 22M1)
Models 221M26, 221M27 (See Ch. 21K1)
Models 221UDX15L, 221UDX16L, 221UDX17L (See Ch. 19L1)
Model 222DX15 (See Ch. 19H1)
Model 222DX15B (See Ch. 22M2)
Model 222DX15S (See Ch. 22C2)
Model 222DX16B (See Ch. 22M2)
Model 222DX17 (See Ch. 22C2)
Model 222DX17B (See Ch. 22M2)
Models 222DX26, 222DX27 (See Ch. 22C2)
Model 222DX27B (See Ch. 22M2)
Models 222DX48, 222DX49 (See Ch. 22C2)
Models 222DX15, 222DX16, 222DX17 (See Ch. 22N2)
Models 22BDX16, 22BDX17 (See Ch. 23A1)
Model 320R17 (See Ch. 21J1)
Models 320R25, 320R26 (See Ch. 21J1)
Models 321DX15, 321DX16, 321DX17 (See Ch. 19E1)

ADMIRAL—Cont.

- Models 321DX15A, 321DX16A, 321DX17A (See Ch. 19E1 or Ch. 19G1)
Models 321DX15L, 321DX16L, 321DX17L (See Ch. 19N1)
Model 321DX25B (See Ch. 19E1 or Ch. 19G1)
Model 321DX26 (See Ch. 19E1)
Model 321DX26B (See Ch. 19E1 or Ch. 19G1)
Model 321DX27B (See Ch. 19E1 or Ch. 19G1)
Models 321F15, 321F16 (See Ch. 21I1 and Ch. 5D2)
Model 321F18 (See Ch. 21I1 and Ch. 5D2)
Model 321F27 (See Ch. 21I1 and Ch. 5D2)
Models 321F35, 321F36 (See Ch. 21I1 and Ch. 5D2)
Models 321F46, 321F47 (See Ch. 21I1 and Ch. 5D2)
Model 321F49 (See Ch. 21I1 and Ch. 5D2)
Models 321F66, 321F66, 321F67 (See Ch. 21I1 and Ch. 5D2)
Models 321K15, 321K16 (See Ch. 21I1 and Ch. 3C1)
Model 321K18 (See Ch. 21I1 and Ch. 3C1)
Model 321K27 (See Ch. 21I1 and Ch. 3C1)
Models 321K35, 321K36 (See Ch. 21I1 and Ch. 3C1)
Models 321K46, 321K47 (See Ch. 21I1 and Ch. 3C1)
Model 321K49 (See Ch. 21I1 and Ch. 3C1)
Models 321K65, 321K66, 321K67 (See Ch. 21I1 and Ch. 3C1)
Models 321M25, 321M26, 321M27 (See Ch. 21Y1)
Models 321M25A, 321M26A, 321M27A (See Ch. 22Y1)
Models 321UDX15L, 321UDX16L (See Ch. 19H1)
Model 322DX16 (See Ch. 22E2)
Model 322DX16A (See Ch. 22P2)
Model 322DX16S (See Ch. 22R2)
Models 421M15, 421M16 (See Ch. 21Y1)
Models 421M15A, 421M16A (See Ch. 22Y1)
Models 421M35, 421M36, 421M37 (See Ch. 22Y1)
Models 520M11, 520M12 (See Ch. 22A2A)
Models 520M15, 520M16, 520M17 (See Ch. 22A2)
Models 521M15, 521M16, 521M17 (See Ch. 21Y1)
Models 521M15A, 521M16A, 521M17A (See Ch. 22Y1)
AERMOVIVE
181-AD 12-1
AERO (See Record Changer Listing)
AIMCEE (See AMC)
AIRADIO
SU-41D 11-1
SU-52A, B, C (Receiver) 13-2
TRA-1A, B, C (Transmitter) 13-1
641 15-1
651 17-1
652 A25, 652 A35 169-2
552.3A65.1 268-2
652.3 268-2
652.5C1M, V 260-3
652.5T3M, V 246-1
652.5T5E, V 260-4
652.5X5 286-2
652.6T1E, V 205-2
652.8T1 250-2
652.3275A 210-3
652.4875 218-2
652.505 168-2
659.511, 659.513 167-2
659.520E, 158-4
738.8300, UL 250-2
782.5C1, 782.5R1 287-2
91.51, W 129-2
935 128-2
9631, W, 965K1, W (See Model 913-35, Set 129-2)
1400C, 1400T 140-3
1700C, 1700T 140-3
2000C 140-3
3170 (For TV Ch. See Set 140-3, for Radio Ch. See Set 150-3, Set 126-2)
4170 (For TV Ch. See Set 140-3, for Radio Ch. See Set 350-3, Set 136-4)
5000, 5001 16-2
5002 19-1
5003, 5004, 5005, 5006 20-1
5008, 5009 46-1
5010, 5011, 5012 (Ch. 110) 13-4
5015.1 118-3
5020 14-3
5022 125-2
5024 45-1
5025 24-2
5027 49-3
5028 44-1
5029 46-2
5035 51-1
5036 72-2
5044 121-2
5050 48-4
5052 45-2
5055A 15-2
6054 61-1
6050 74-1
6053 97-1
6514 18-4
6541 17-2
6544 (See Model 6541—Set 17-2)
6547 17-2
6611, 6612, 6613, 6630, 6631 15-2
6632, 6634, 6635 14-3
7000, 7001 19-2
7004 19-2
G50-5101A 57-3
7015 Early 47-2
7553 45-3

AIRCATTLE—Cont.

- 416 (See Model 14C—Set 140-3)
472.8P24, 472.8P25 (See Model 472.MP25—Set 168-1)
472.MP24 (See Model 472.MP25—Set 168-1)
472.MP25 168-1
472-053VM 163-2
472.17XUCM, 472.XUCM.1 (Ch. 21Z1) 223-2
472.17XUCM.2, 472.XUCM.3, 472.17XUCM.4, 472.17XUCM.5 (Ch. 317-D) 223-2
472.17XUCO, 472.17XUCO.1 (Ch. 317-B) 223-2
472.17XUT.1, 472.17XUT.2, 472.XUT.3 (Ch. 21Z8) [See Model 20XUT—Set 185-3]
472.17XUT.4, 472.17XUT.5 (Ch. 317-B) 223-2
472.17XUT.6, 472.17XUT.7, 472.17XUT.8 (Ch. 317-D) 223-2
472.20XUC (Ch. 220B) [See Model 20XUT—Set 185-3]
472.20XUT, 472.20XUT.1, 472.20XUT.2 (Ch. 220B) [See Model 20XUT—Set 185-3]
472.21XUC (Ch. 321-B) 223-2
472.21XUCO (Ch. 321-B) 223-2
472.21XUCO.1, 472.21XUCO.2 (Ch. 321-D) 223-2
472.21XUT, 472.21XUT.1 (Ch. 321-B) 223-2
472.21XUT.2 (Ch. 321-D) 223-2
472.217C, 472.217C.1 (Ch. 317-D) 223-2
472.217T, 472.217T.1 (Ch. 317-D) 223-2
472.221XC (Ch. 321-D) 223-2
472.221XT, 472.221XT.1 (Ch. 321-D) 223-2
472.254 215-2
568 141-1
568.205 141-2
568.205-1 [See Model 200—Set 139-3]
568.305 141-2
572 55-1
594.935 [See Model 935—Set 128-2]
602-182144 114-2
603-PR-8.1 133-2
603.880 230-2
604 53-2
606.400WB 119-2
607.299 177-3
607.314, 607.315 122-2
607.316, -1, 607.317, -1 138-2
610.A67 247-2
610.C35 174-2
610.C1152B, M 221-1
610.CM-333 (Similar to Chassis) 230-3
610.PM-236 (Similar to Chassis) 226-2
610.D200 142-3
610.F100 133-3
610.F151 172-2
610.FE153 244-2
610.H400 178-2
610.P-651.1 179-2
610.S500 184-2
610.W-100 249-2
621 (Ch. F1-91) 14-2
626 18-3
641 17-1
651 15-1
652 A25, 652 A35 169-2
552.3A65.1 268-2
652.3 268-2
652.5C1M, V 260-3
652.5T3M, V 246-1
652.5T5E, V 260-4
652.5X5 286-2
652.6T1E, V 205-2
652.8T1 250-2
652.3275A 210-3
652.4875 218-2
652.505 168-2
659.511, 659.513 167-2
659.520E, 158-4
738.8300, UL 250-2
782.5C1, 782.5R1 287-2
91.51, W 129-2
935 128-2
9631, W, 965K1, W (See Model 913-35, Set 129-2)
1400C, 1400T 140-3
1700C, 1700T 140-3
2000C 140-3
3170 (For TV Ch. See Set 140-3, for Radio Ch. See Set 150-3, Set 126-2)
4170 (For TV Ch. See Set 140-3, for Radio Ch. See Set 350-3, Set 136-4)
5000, 5001 16-2
5002 19-1
5003, 5004, 5005, 5006 20-1
5008, 5009 46-1
5010, 5011, 5012 (Ch. 110) 13-4
5015.1 118-3
5020 14-3
5022 125-2
5024 45-1
5025 24-2
5027 49-3
5028 44-1
5029 46-2
5035 51-1
5036 72-2
5044 121-2
5050 48-4
5052 45-2
5055A 15-2
6054 61-1
6050 74-1
6053 97-1
6514 18-4
6541 17-2
6544 (See Model 6541—Set 17-2)
6547 17-2
6611, 6612, 6613, 6630, 6631 15-2
6632, 6634, 6635 14-3
7000, 7001 19-2
7004 19-2
G50-5101A 57-3
7015 Early 47-2
7553 45-3

AIRCATTLE—Cont.

- 90081, 9008W 99-2
90091, 9009W 97-2
90101, 9012W 94-1
10002-1 54-1
10003-1 46-2
10005 62-3
10021-1, 10022-1 59-3
10023 58-1
10024 58-2
108014, 108504 57-4
12104 73-1
12124 61-2
127084 55-2
131504 60-2
132904 75-1
138104 64-1
138124 64-1
139114 (See Model 139144—Set 59-4)
147114 56-3
149654 71-4
150084 71-4
159144 (See Model 139144—Set 59-4)
Ch. 217B (See Model 472.17XUT)
Ch. 220B (See Model 472.20XUC)
Ch. 317-B (See Model 472.17XUCO)
Ch. 317-D (See Model 472.17XUCO.2)
Ch. 321-B (See Model 472.21XUT)
Ch. 321-D (See Model 472.21XUT.2)
AIR CHIEF (See Firestone)
AIR KING
A-400 (Ch. 470) 23-1
A-403 20-2
A-410 34-1
A-410 (Revised) 40-2
A-426 43-1
A-510, A-502 (Ch. 465.4) 31-3
A-510 24-3
A-511, A-512 30-2
A-520 49-4
A-600 26-3
A-601 81-2
A-625 50-3
A-650 45-4
A-1000, A-1001 58-3
A1010A 75-2
A1016 91-2
A2000, A2001 40-2
2002 (See Model A2000—Set 75-2)
A2010 75-2
A2012 (See Model A1001A—Set 75-2)
12C1 (Ch. 700) (See Model 16C1—Set 121-3)
12C2, 12C3 (Ch. 700) (See Model 16C1—Set 121-3)
14T1 (See Model 16C1—Set 121-3)
16C1, 16C2, 16C3 (Ch. 700-1) 121-3
16M1 (Ch. 700-1) 121-3
16T1 121-3
16T1B (See Model 16C1—Set 121-3)
17C2 (Ch. 700-96) 151-2
17C5, B (Ch. 700-96) 151-2
17C7 (Ch. 700-96) 151-2
17K1 (Ch. 700-96) 151-2
17K1C (Ch. 700.110, 700.130) 150-2
17M1 (Ch. 700-96) 151-2
17T1 (Ch. 700-96) 151-2
19C1 121-3
20C1, 20C2 (Ch. 700-93) 151-2
20K1 (Ch. 700-93) 151-2
20M1 (Ch. 700-93) 151-2
718R 121-3
800 66-1
2017R 111-2
4601 (See Model 4609—Set 11-2)
4603 3-26
4604 4-25
4704A (See Model 4604—Set 4-25)
4607, 4608 3-1
4609, 4610 (Early) (See Model 4607—Set 3-1)
4609, 4610 (Late) 11-2
4625 13-8
4700 39-1
4704 12-2
4705, 4706 (See Model 4704—Set 12-2)
4708 (See Model 4704—Set 12-2)
Ch. 465 (See Model A-501)
Ch. 470 (See Model A-400)
Ch. 700 (See Model 12T1)
Ch. 700-1 (See Model 16C1)
Ch. 700-93 (See Model 20C1)
Ch. 700-95 (See Model 20K1)
Ch. 700-96 (See Model 17C2)
Ch. 700.110 (See Model 17K1C)
Ch. 700.130 (See Model 17K1C)
AIR KNIGHT (SKY KNIGHT)
CA-500 17-4
CB-500P 17-31
NS-RD291 17-3
AIRLINE
BR-3082A, BR-3084A [See Model 35BR-3158A—Set 221-2]
BR-3091A [See Model 35BR-3158A—Set 221-2]
BR-3182A [See Model 35BR-3158A—Set 221-2]
BR-4000A, BR-4001A, BR-4003A, BR-4005A [Also See PCB 125—Set 282-1]
GSE-1077A, GSE-1078A 250-3
GSE-3176A, B [See PCB 102—Set 248-1 and Model 35GSE-3076A—Set 238-3]
GSE-3178A, B [See PCB 102—Set 248-1 and Model 35GSE-3078A—Set 238-3]
GSE-3195A [See PCB 102—Set 248-1 and Model 35GSE-3095—Set 238-3]
GSE-3197A [See PCB 102—Set 248-1 and Model 35GSE-3097—Set 238-3]
GSE-5001A 269-2
GSE-5004A 269-2
GSE-5101A 269-2
GSE-5104A 269-2
GSL-1581A, GSL-1582A 280-3

NOTE: PCB Denotes Production Change Bulletin. Production Change Bulletin Nos. 1 Through 63 Are All Contained in Set No. A-200 Production Change Bulletin Nos. 64 Through 104 Are All Contained in Set No. A-250

D Denotes Television Receiver.

AIRLINE—APEX

AIRLINE—Cont.

Table listing various model numbers and their corresponding page numbers under the AIRLINE—Cont. section.

AIRLINE—Cont.

Table listing various model numbers and their corresponding page numbers under the AIRLINE—Cont. section.

AIRLINE—Cont.

Table listing various model numbers and their corresponding page numbers under the AIRLINE—Cont. section.

AIRLINE—Cont.

Table listing various model numbers and their corresponding page numbers under the AIRLINE—Cont. section.

AMBASSADOR—Cont.

Table listing various model numbers and their corresponding page numbers under the AMBASSADOR—Cont. section.

NOTE: PCB Denotes Production Change Bulletin. Production Change Bulletin Nos. 1 Through 63 Are All Contained in Set No. A-200. Denotes Television Receiver.

APPROVED ELECTRONIC INSTRUMENT CORP.

FM Tuner 41-2
A-600AC 175-4
A710 177-5
A-800 176-2
A-850 175-5

ARC

440T (Ch. RE-278) 96-3
441T (Ch. RE-278) (See Model 440T) 96-3
—Set 96-3

ARCADIA

37D1A-600 9-3

ARIA

554-1-61A 7-2

ARLINGTON

●30T14A-056 (Similar to Chassis) 119-3
●38T12A-058 (Similar to Chassis) 109-1
●317T3 (Similar to Chassis) 72-4
●318T4 (Similar to Chassis) 85-3
●318T4S (Similar to Chassis) 85-3
●318T4-872 (Similar to Chassis) 85-3
●318T6A (Similar to Chassis) 85-3
●318T6A-950 (Similar to Chassis) 85-3
●318T9A-900 (Similar to Chassis) 85-3
●321MS31C (Similar to Chassis) 182-5
●321MS39A (Similar to Chassis) 226-1
●318T9A-918 (Similar to Chassis) 78-4
●318T9A-918 (Similar to Chassis) 78-4
●318T10A-916 (Similar to Chassis) 78-4
●2318T6A-954 (Similar to Chassis) 85-3
●2318T9A-912 (Similar to Chassis) 78-4
●2321MS39A (Similar to Chassis) 226-1

ARTHUR ANSLEY

HF7 263-2
LP-2, LP-3 82-4
LP-4A 82-4
LP-5 (See Model P-5—Set 108-4)
LP-6, LP-6S 136-5
LP-7 134-3
P-5 108-4
R-1 209-2
Sp-1 60-4
TP-1 173-3

ARTONE

●AR14L, AR17L 172-3
●AR17 205-3
●AR71 205-3
●AR-23TV-1 80-1
ARC21 205-3
ARC71 205-3
●AR02 205-3
●AST12, MST14 170-4
●14TR, 14TR 170-4
●17CD (1st Prod.) 172-4
●17CD (2nd Prod.) 170-4
●17CCR (1st Prod.) 170-4
●17CCR (2nd Prod.) 172-3
●17ROG (1st Prod.) 170-4
●17ROG (2nd Prod.) 172-3
●20CD (1st Prod.) 170-4
●20CD (2nd Prod.) 172-3
●20TR 170-4
●112X 170-4
●203D (1st Prod.) 170-4
●203D (2nd Prod.) 170-4
●312 170-4
524 76-7
●819 170-4
●1000, 1001 172-3
●8163CR, 8193CM 170-4

ARVIN

●15-550KB-UHF 262-2
●21-550KB, 21-551TB, TM 21-552-2
KB, KM, 21-553TB, TM (Ch. TE-382, TE-382-1) (Also See PCB 127—Set 286-1) 266-2
●21-550KBU, KMU, 21-551TBU, TMU, 21-552KBU, KMU, 21-553TBU, TMU (Ch. TE-379, TE-379-1) (Also See PCB 127—Set 286-1) 266-2
●21-554KMU, KMU (Ch. TE383 "E" Series, TE386-UHF "E" Series) 264-3
●21-555TG, TGU, TM, TMU (Ch. TE-383 "E" Series, TE-386-UHF "E" Series) 264-3
●21-557TM, TMU (Ch. TE-383 "E" Series, TE-386-UHF "E" Series) 264-3
140P (Ch. RE-209) 25-6
150TC, 151TC (Ch. RE-228) 25-7
150TC, 151TC (Ch. RE-228-1) Late 39-2
152T (Ch. RE-233) 33-1
153T (See Model 152T—Set 33-1)
160T, 161T (Ch. RE-232) 45-5
182TFM (Ch. RE-237) 32-3
240-P (Ch. RE-243) 42-2
241P (Ch. RE-244, RE-254, RE-255, RE-256, RE-259) 47-3
242T, 243T (Ch. RE-251) 52-3
244P (Ch. RE-244, RE-254, RE-255, RE-256, RE-259) 47-3
250-P (Ch. RE-248) 43-4
253T, 254T, 255T, 256T (Ch. RE-252) 53-5
264T, 265T (Ch. RE-265) 64-2
280TFM, 281TFM (Ch. RE-253) 44-2
341T (Ch. RE-274) 84-3
350P (Ch. RE-267) 69-3
350P-B (Ch. RE-267-1) 100-4
350PL (Ch. RE-277-2) 100-4
351P (Ch. RE-267) 69-3
351-PB (Ch. RE-267-1) 100-4
351-PL (Ch. RE-267-2) 100-4
352-PL, 353-PL (Ch. RE-267-2) 100-4

ARVIN—Cont.

355T (Ch. RE-213) (See Model 356T) Set 78-2
356T, 357T (Ch. RE-273) 78-2
358T (Ch. RE-233) (See Model 152T) —Set 33-1
360TFM, 361TFM (Ch. RE-260) 79-3
440T (Ch. RE-278) 96-3
441T (Ch. RE-278) (See Model 440T) —Set 96-3
442 (Ch. RE-91) 34-2
444, 444A (Ch. RE-200) 1-3
444AM, 444AM (Ch. RE-200M) 23-3
446P (Ch. RE-280) 136-2
450T, 451T (Ch. RE-281) 110-3
460T, 461T (Ch. RE-284) 107-3
462CB, 462CM (Ch. RE-287-1) 116-3
480TFM, 481TFM (Ch. RE-277) 107-4
482CFB, 482CFM (Ch. RE-288-1) 117-4
540T (Ch. RE-278) 143-4
542T (See Model 440T—Set 96-3)
544, 544A (Ch. RE-201) 1-7
544AR, 544AR (Ch. RE-201) (See Model 544—Set 1-7)
547A (Ch. RE-242) 42-3
551T (Ch. RE-297) 154-2
552AN, 552N (Ch. RE-231) 13-9
553 (Ch. RE-308) 159-4
554CCB, 554CCM (Ch. RE-306) 155-3
555, A (Ch. RE-202) 13-9
558 (Ch. RE-204) 3-16
580TFM (Ch. RE-313) 152-2
581TFM (Ch. RE-333) 227-2
582CFB, 582CFM (Ch. RE-310) 156-4
652-P (Ch. RE-292) (See Model 650-P—Set 175-6)
654-P (Ch. RE-292) (See Model 650-P—Set 175-6)
650-P (Ch. RE-292) 175-6
651T (Ch. RE-323) 251-3
655 SWT (Ch. RE-327) 187-2
657-T (Ch. RE-307) 168-5
664, 664A (Ch. RE-206) 3-23
664, 664A (Ch. RE-206-1) 29-2
665 (Ch. RE-229) 18-10
740T (Ch. RE-278) (See Model 540T—Set 143-4)
741T (Ch. RE-352) 225-4
746P, 747P (Ch. RE-347) 225-5
751TB (See Model 551T—Set 154-2)
753T (Ch. RE-348) 220-2
758T (Ch. RE-350) 221-3
760T (Ch. RE-342) 223-3
780TFM (Ch. RE-333) 227-2
840T (Ch. RE-278-1) 263-3
848T, 849T (Ch. RE-369) 251-2
850T (Ch. RE-375) 262-3
851T (Ch. RE-377) 266-3
852P (Ch. RE-372) 258-3
853T (Ch. RE-375) 262-3
854P (Ch. RE-372) 258-3
855T (Ch. RE-377) 266-3
857T (Ch. RE-378) 227-3
858T, 859T (Ch. RE-374) 261-2
●2120CM (Ch. TE289-2, TE289-3) (Also See PCB 20—Set 134-1) 120-3
●2121TM (Ch. TE289-2, TE289-3) (Also See PCB 20—Set 134-1) 120-3
●2122TM (Ch. TE-289) 97A-1
●2123TM (Ch. TE-289-2, TE289-3) (Also See PCB 20—Set 134-1) 120-3
●2124CCM (Ch. TE289-2, TE289-3) (Also See PCB 20—Set 134-1) 120-3
●2126CM (Ch. TE289-2, TE-289-3) (Also See PCB 20—Set 134-1) 120-3
●2160, 2161, 2162, 2164 (Ch. TE-290) 126-3
2410P (Ch. RE-244, RE-254, RE-255, RE-256, RE-259) 47-3
●3100TB, 3100TM, 3101CM, 3120-TE, 3121TM (Ch. TE-272-1, TE-272-2) 80-2
●3160CM (Ch. TE-276) 93-2
●4080T (Ch. TE282) 104-2
●4081T (See Model 4080T—Set 104-2)
●410CM (Ch. TE-286) 130-3
●5170CB, CM, 5171TM, 5172CB, CM (Ch. TE-302, -1, -2, -3, -4, -5A, -6) (Also see PCB 50—Set 184-1) 142-5
●5173TM (Ch. TE-302) (See Model 5170CB) 179-3
●5175, 5176 (Ch. TE320) 179-3
●5176CM-E (Ch. TE-320-1) (See PCB 126—Set 284-1 and Model 5176—Set 179-3)
●5204CM, 5206CM (Ch. TE-300) 149-3
●5210, 5211, 5212 (Ch. TE-315, -1, -2, -3, -4, -5) (Also see PCB 37—Set 166-1 and PCB 50—Set 184-1) 181-4
●5213TM (Ch. TE334) 91-5
●6173TA (Ch. TE331, -4, -5) (See PCB 66—Set 203-1, PCB 92—Set 237-1) and Model 6175TM—Set 195-4
●6173TM-UHF (Ch. TE332, -1, -2, -3, -4) (Also see PCB 81—Set 231-1) 208-2
●6175TA (Ch. TE-331, -1, -2, -3, -4) (Also see PCB 66—Set 203-1) 181-4
●6175TA-A (Ch. TE331-5) See PCB 66—Set 203-1, PCB 92—Set 237-1 and Model 6175TM—Set 181-4
●6179TM (Ch. TE-331, -1, -2, -3, -4) (Also see PCB 66—Set 203-1) 181-4
●6213TB (Ch. TE-319, -1, -2) (See PCB 67—Set 204-1 and Model 6213TM—Set 195-4)
●6213TB-UHF (Ch. TE330, -1, -2, -3, -4, -5, -6) (Also see PCB 81—Set 231-1) 208-2
●6213TA (Ch. TE-319, -1, -2) (Also see PCB 67—Set 204-1) 195-4

ARVIN—Cont.

●6213TM-UHF (Ch. TE330, -1, -2, -3, -4, -5, -6) (Also see PCB 81—Set 231-1) 208-2
●6215CB (Ch. TE-319, -1, -2) (Also see PCB 67—Set 204-1) 195-4
●6215CB-UHF (Ch. TE330, -1, -2, -3, -4, -5, -6) (Also see PCB 81—Set 231-1) 208-2
●6215CM (Ch. TE-319, -1, -2) (Also see PCB 67—Set 204-1) 195-4
●6215CM-UHF (Ch. TE330, -1, -2, -3, -4, -5, -6) (Also see PCB 81—Set 231-1) 208-2
●6640 (Ch. RE-206-2) 29-2
●7210CB (Ch. TE337, -1, -2, -3, -4, 31) (Also see PCB 93—Set 238-1) 189-3
●7210CB-UHF (Ch. TE341, -1, -2, -3, -4, -5, -6, -41) (Also see PCB 93—Set 197-1 and PCB 94—Set 239-1) 188-4
●7210CM (Ch. TE337, -1, -2, -3, -4, -31) (Also see PCB 93—Set 197-1) 189-3
●7210CM-UHF (Ch. TE341, -1, -2, -3, -4, -5, -6, -41) (Also see PCB 93—Set 197-1 and PCB 94—Set 239-1) 188-4
●7212CFP (Ch. TE337, -1, -2, -3, -4, -31) (See PCB 93—Set 238-1 and Model 7210CM—Set 189-3)
●7212CFP-UHF (Ch. TE341, -1, -2, -3, -4, -5, -6, -41) (Also see PCB 93—Set 197-1 and PCB 94—Set 239-1) 188-4
●7212MEA-UHF (Ch. TE341, -1, -2, -3, -4, -5, -6, -41) (Also see PCB 93—Set 197-1 and PCB 94—Set 239-1) 188-4
●7214CM (Ch. TE337, -1, -2, -3, -4, -31) (Also see PCB 93—Set 238-1) 189-3
●7214CM-UHF (Ch. TE341, -1, -2, -3, -4, -5, -6, -41) (Also see PCB 93—Set 197-1 and PCB 94—Set 239-1) 188-4
●7216CB (Ch. TE-337-1) (See Model 7210CM—Set 189-3)
●7216CB-UHF (Ch. TE341, -1, -2, -3, -4, -5, -6, -41) (Also see PCB 93—Set 197-1 and PCB 94—Set 239-1) 188-4
●7218CB (Ch. TE337, -1, -2, -3, -4, -31) (Also see PCB 93—Set 238-1) 189-3
●7218CB-UHF (Ch. TE341, -1, -2, -3, -4, -5, -6, -41) (Also see PCB 93—Set 197-1 and PCB 94—Set 239-1) 188-4
●7218CM (Ch. TE337, -1, -2, -3, -4, -31) (Also see PCB 93—Set 238-1) 189-3
●7218CM-UHF (Ch. TE341, -1, -2, -3, -4, -5, -6, -41) (Also see PCB 93—Set 197-1 and PCB 94—Set 239-1) 188-4
●7218CM-UHF (Ch. TE341, -1, -2, -3, -4, -5, -6, -41) (Also see PCB 93—Set 197-1 and PCB 94—Set 239-1) 188-4
●7219CM-UHF (Ch. TE341, -1, -2, -3, -4, -5, -6, -41) (Also see PCB 93—Set 197-1 and PCB 94—Set 239-1) 188-4
●7276CB-UHF (Ch. TE340, -1, -2) 231-3
●7279CM-UHF (Ch. TE340, -1, -2) 231-3
●8171TM (Ch. TE331-6) (See PCB 66—Set 203-1, PCB 92—Set 237-1 and Model 6175TM—Set 181-4)
●8171TM-UHF (Ch. TE332-5) (See PCB 88—Set 231-1 and Model 6173TM-UHF—Set 208-2)
●8179TM (Ch. TE331-5) (See PCB 66—Set 203-1, PCB 92—Set 237-1 and Model 6175TM—Set 181-4)
●8179TM-UHF (Ch. TE332-4) (See PCB 88—Set 231-1 and Model 6173TM-UHF—Set 208-2)
●8211TB (Ch. TE319-3) (See PCB 67—Set 204-1, PCB 89—Set 233-1 and Model 6213TM—Set 195-4)
●8211TB-UHF (Ch. TE307-7) (See PCB 88—Set 231-1 and Model 6213TB-UHF—Set 208-2)
●8211TM (Ch. TE319-3) (See PCB 67—Set 204-1, PCB 89—Set 233-1 and Model 6213TM—Set 195-4)
●821TM-UHF (Ch. TE330-7) (See PCB 88—Set 231-1 and Model 6213TB-UHF—Set 208-2)
●8213TA (Ch. TE319-2) (See PCB 67—Set 204-1, PCB 89—Set 233-1 and Model 6213TM—Set 195-4)
●8213TA-UHF (Ch. TE330-6) (See PCB 88—Set 231-1 and Model 6213TB-UHF—Set 208-2)
●8213TMA (Ch. TE319-21) (See PCB 67—Set 204-1, PCB 89—Set 233-1 and Model 6213TM—Set 195-4)
●8213TMA-UHF (Ch. TE330-61) (See PCB 88—Set 231-1 and Model 6213TB-UHF—Set 208-2)
●8215CM (Ch. TE319-21) (See PCB 67—Set 204-1, PCB 89—Set 233-1 and Model 6213TM—Set 195-4)
●8215CM-UHF (Ch. TE330-6) (See PCB 88—Set 231-1 and Model 6213TB-UHF—Set 208-2)
●8215CMA (Ch. TE319-21) (See PCB 67—Set 204-1, PCB 89—Set 233-1 and Model 6213TM—Set 195-4)
●8215CMA-UHF (Ch. TE330-61) (See PCB 88—Set 231-1 and Model 6213TB-UHF—Set 208-2)
●8218CB (Ch. TE319-3) (See PCB 67—Set 204-1, PCB 89—Set 233-1 and Model 6213TM—Set 195-4)

ARVIN—Cont.

●8218CB-UHF (Ch. TE330-7) (See PCB 88—Set 231-1 and Model 6213TB-UHF—Set 208-2)
●8218CM (Ch. TE319-3) (See PCB 67—Set 204-1, PCB 89—Set 233-1 and Model 6213TM—Set 195-4)
●8218CM-UHF (Ch. TE330-7) (See PCB 88—Set 231-1 and Model 6213TB-UHF—Set 208-2)
●9210CB (Ch. TE358, -1, -2, -3) 238-4
●9210CB-UHF (Ch. TE-363, -1, -2, -3) 238-4
●9210CM (Ch. TE358, -1, -2, -3) 238-4
●9210CM-UHF (Ch. TE363, -1, -2, -3) 238-4
●9211TM (Ch. TE355) 248-2
●9211TM-UHF (Ch. TE-362) 248-2
●9212CFP (Ch. TE358, -1, -2, -3) 238-4
●9212CFP-UHF (Ch. TE363, -1, -2, -3) 238-4
●9212MEA (Ch. TE358, -1, -2, -3) 238-4
●9212MEA-UHF (Ch. TE363, -1, -2, -3) 238-4
●9213TM (Ch. TE-355) 248-2
●9213TM-UHF (Ch. TE-362) 248-2
●9213CM (Ch. TE-353) 248-2
●9213CM-UHF (Ch. TE-362) 248-2
●9216CB (Ch. TE358, -1, -2, -3) 238-4
●9216CB-UHF (Ch. TE363, -1, -2, -3) 238-4
●9218CB (Ch. TE358, -1, -2, -3) 238-4
●9218CB-UHF (Ch. TE363-1, -2, -3) 238-4
●9218CM (Ch. TE358, -1, -2, -3) 238-4
●9218CM-UHF (Ch. TE363, -1, -2, -3) 238-4
●9219CM (Ch. TE358, -1, -2, -3) 238-4
●9219CM-UHF (Ch. TE363, -1, -2, -3) 238-4
●9240CB (Ch. TE364, -1) 235-2
●9240CB-UHF (Ch. TE364, -1) 235-2
●9240CM (Ch. TE364, -1) 235-2
●9240CM-UHF (Ch. TE359, -1) 235-2
●9245CM-UHF (Ch. TE373) 247-3
Ch. RE-91 (See Model 442) 238-4
Ch. RE-200 (See Model 444) 238-4
Ch. RE-200M (See Model 444M) 238-4
Ch. RE-201 (See Model 544) 238-4
Ch. RE-202 (See Model 555) 238-4
Ch. RE-204 (See Model 558) 238-4
Ch. RE-205 (See Model 564) 238-4
Ch. RE-206-1, 206-2 (See Model 664 Late) 238-4
Ch. RE-209 (See Model 140P) 238-4
Ch. RE-228 (See Model 150TC) 238-4
Ch. RE-228-1 (See Model 150TC Late) 238-4
Ch. RE-229 (See Model 665) 238-4
Ch. RE-231 (See Model 552AN) 238-4
Ch. RE-232 (See Model 160T) 238-4
Ch. RE-233 (See Model 152T) 238-4
Ch. RE-237 (See Model 182TFM) 238-4
Ch. RE-242 (See Model 545) 238-4
Ch. RE-243 (See Model 240P) 238-4
Ch. RE-244 (See Model 241P) 238-4
Ch. RE-248 (See Model 250P) 238-4
Ch. RE-251 (See Model 242T) 238-4
Ch. RE-252 (See Model 253T)
Ch. RE-253 (See Model 280TFM)
Ch. RE-254, 255, 256, 259 (See Model 241P)
Ch. RE-260 (See Model 360TFM)
Ch. RE-265 (See Model 264T)
Ch. RE-267 (See Model 350P)
Ch. RE-267-1, RE-267-2 (See Model 350-PB)
Ch. RE-273 (See Model 356T)
Ch. RE-274 (See Model 341T)
Ch. RE-277, RE-277-1 (See Model 480TFM)
Ch. RE-278 (See Model 540T)
Ch. RE-278-1 (See Model 840T)
Ch. RE-280 (See Model 446P)
Ch. RE-281 (See Model 450T)
Ch. RE-284 (See Model 460T)
Ch. RE-287 (See Model 545) 452-CB
Ch. RE-288-1 (See Model 482CFB)
Ch. RE-292 (See Model 650-P)
Ch. RE-297 (See Model 551T)
Ch. RE-306 (See Model 554CCB)
Ch. RE-307 (See Model 657T)
Ch. RE-308 (See Model 523T)
Ch. RE-310 (See Model 582CFB)
Ch. RE-313 (See Model 580TFM)
Ch. RE-323 (See Model 651T)
Ch. RE-327 (See Model 655SWT)
Ch. RE-333 (See Model 581TFM)
Ch. RE-342 (See Model 740T)
Ch. RE-347 (See Model 746P)
Ch. RE-348 (See Model 753T)
Ch. RE-350 (See Model 758T)
Ch. RE-352 (See Model 741T)
Ch. RE-359 (See Model 840T)
Ch. RE-372 (See Model 852P)
Ch. RE-374 (See Model 858T)
Ch. RE-375 (See Model 850T)
Ch. RE-377 (See Model 851T)
Ch. RE-378 (See Model 857T)
Ch. TE-272-1, -2 (See Model 3100TB)
Ch. TE-276 (See Model 3160CM)
Ch. TE282 (See Model 4080T)
Ch. TE-286 (See Model 4162CM)
Ch. TE-289 (See Model 2122TM)
Ch. TE-289-2, TE-289-3 (See Model 2120CM)
Ch. TE-290 (See Model 2160)
Ch. TE-300 (See Model 5204)
Ch. TE-302, -1, -2, -3, -4, -5A, -5A, -6 (See Model 5170CB)
Ch. TE-315, -1, -2, -3, -4, -5, -5A, -6 (See Model 5210)
Ch. TE-319, -1, -2 (See Model 6213TM)
Ch. TE-319-3 (See Model 8211TB)
Ch. TE319-21 (See Model 8213TMA)

ARVIN—Cont.

Ch. TE-320 (See Models 5175, 5176)
Ch. TE-320-1 (See Model 5176CM-E)
Ch. TE330, -1, -2, -3, -4, -5, -6 (See Model 6213TB-UHF)
Ch. TE330-6 (See Model 8213TM-UHF)
Ch. TE330-7 (See Model 8211TB-UHF)
Ch. TE330-61 (See Model 8215CMA-UHF)
Ch. TE-331, -1, -2, -3, -4 (See Model 6175TA)
Ch. TE 331-5 (See Model 6173TM)
Ch. TE 331-6 (See Model 8171TM)
Ch. TE332, -1, -2, -3, -4 (See Model 6173TM-UHF)
Ch. TE332-5 (See Model 8171TB-UHF)
Ch. TE 334 (See Model 5213TM)
Ch. TE 337-1, -2, -3, -4, -31 (See Model 7210CB)
Ch. TE340, -1, -2 (See Model 7276CB-UHF)
Ch. TE 341, -1, -2, -3, -4, -5, -6, -41 (See Model 7210CB-UHF)
Ch. TE355 (See Model 9211TM)
Ch. TE-358, -1, -2, -3 (See Model 9210CB)
Ch. TE 359-1 (See Model 9240CB-UHF)
Ch. TE362 (See Model 9211TM-UHF)
Ch. TE 363, -1, -2, -3 (See Model 9210CB-UHF)
Ch. TE 364, -1 (See Model 9240CB)
Ch. TE373 (See Model 9245CM-UHF)
Ch. TE-379, TE-379-1 (See Model 21-550KBU)
Ch. TE-382, TE-382-1 (See Model 21-550KB)
Ch. TE-383 "E" Series (See Model 21-554KMU)
Ch. TE-386-UHF "E" Series (See Model 21-554KMU)
ASTATIC
CB-1 Tal. UHF Conv.-Booster 224-3
UHf (UHF Conv. Cn.) 264-4
ASTORIA
●A-21, A-72, A-73L (Similar to Chassis) 182-3
ASTRASONIC (Also see Pentron)
T-3 121-4
748 53-6
ATLAS
AB-45 14-5
AUDAR
AV-7T 166-6
MAS-4 "Bingo Amp" 26-6
P-1A 5-10
P-4A 19-3
P-5 4-1
P-7 4-1
PR-6 13-10
PR-6A 19-4
RE-8A 25-8
Telvor BM-25, BMP-25 62-5
Telvor BC-12 35-2
Telvor HER-9 65-2
WC-2T 166-6
AUDIO DEVELOPMENT (ADC)
71-F 128-3
AUTOMATIC
Tom Boy 27-4
Tom Thumb Buddy 53-7
Tom Thumb Camera-Radio 49-6
Tom Thumb Jr. 26-7
Tom Thumb Personal ATTP 23-4
B-44 60-5
C51 178-4
C-54 186-2
C-60 5-20
C-60X (See Model C-60X—Set 24-10)
C300 102-1
C-351 148-4
CL-132B, M 192-3
CL-149 192-3
CM-333 230-3
D200 104-3
D-251 174-4
DM-132 228-3
F-151 103-6
F-790 23-5
M-86 34-3
M-90 69-4
MM-430 227-3
P-651 173-4
PM-236 226-2
S-551 146-3
TR-12 228-4
●TV-P490 81-3
●TV-707, TV-709, TV-710 60-6
●TV-712 (See Model TV-707—Set 60-6)
●TV-1205 (See PCB 5—Set 106-1 and Model TV-1249—Set 103-5)
●TV-1249, TV-1250 103-5
●TV-1294 (See PCB 5—Set 106-1 and Model TV-1249—Set 103-5)
●TV-1605 (See Model TV-1249—Set 103-5)
●TV-1615 (See Model TV-1249—Set 103-5)
●TV-1616, TV-1650, TV-1651 143-5
●TV-1694 (See Model TV-1249—Set 103-5)
●TV-3003 145-4
●TV-5020 134-4
●TV-5061 145-4
●TV-5077 145-4
●TV-5116R 134-4
●TV-5160 134-4
●TVX313 (See Model TV-707—Set 60-6)
●TVX404 (See Model TV-707—Set 60-6)
601, 602 (Series A) 131-11

CHEVROLET—CROSLEY

CHEVROLET—Cont.
986443 189-4
986515 149-5
986516 150-6
986668 219-2
986669 224-6
986771 224-4
987066 276-3
987087 284-6
987088 278-3

CHRYSLER (See Mopar)

CISCO

1A5 37-4
9A5 20-3

CLARION

C100 1-5
C101 5-9
C102 9-6
C103 6-6
C104 1-4
C105 (See Model C-104—Set 1-4)
C105A 6-7
C108 (Ch. 101) 5-8
11011 17-8
11305 18-11
11411-N 30-5
11801 23-6
11802V-M (See Model 11801—Set 23-6)
12100M 54-5
12310-W 31-6
12708 41-5
12801 61-5
13101 46-7
13201, 13203 62-8
14601 60-9
14965 66-5
16703 102-2

CLARK

PA-10 12-6
PA-10A 18-12
PA-20 13-12
PA-20A 18-13
PA-30 19-7

CLEARSONIC (See U.S. Television)

COLLINS AUDIO PRODUCTS

FMA-6 99-6
45-D 72-6

COLLINS RADIO

511-3 260-6
75A-1 37-4
75A-2 171-4

COLUMBIA RECORDS

202 219-3
312 287-4
318 281-4
324 279-2
326 275-5
360 Series 'B' 215-5

COMMANDER INDUSTRIES

Commander 3 Tube Record Player 17-10
CD61P 19-9

CONCERTONE (See Recorder Listing)

CONCORD

IN434, IN435, IN436 (Similar to Chassis) 98-5
IN437 (Similar to Chassis) 121-2
IN549 (Similar to Chassis) 38-5
IN551 (Similar to Chassis) 38-6
IN554, IN555 (Similar to Chassis) 55-10
IN556, IN557 (Similar to Chassis) 109-7
IN559 (Similar to Chassis) 90-7
IN560 (Similar to Chassis) 109-7
IN561, IN562 (Similar to Chassis) 97-8
IN563 (Similar to Chassis) 136-10
IN819 (Similar to Chassis) 69-7
6C518 19-8
6C519 19-8
6E518 20-4
6F26W 19-10
6R3ARC 21-7
6T61W 22-11
7G26C 20-5
7R2A9W 21-7
1-402 1-403 45-6
1-411 48-5
1-501 (See Model 6E518—Set 20-4)
1-504 55-6
1-509, 1-510 (See Model 6C518—Set 19-8)
1-516, 1-517 49-7
1-601, 1-602, 1-603 (See Model 7G26C—Set 20-5)
1-608 45-7
1-608 (See Model 6F26W—Set 19-10)
1-609 (See Model 6T61W—Set 22-11)
1-611 46-8
1-1201 55-7
2-105 (See Model 315WL—Set 53-8)
2-106 54-6
2-200, 2-201, 2-218, 2-219, 2-232, 2-235, 2-236, 2-237, 2-238, 2-239, 2-240 62-9
325WL, 315 WM 53-8
325WL, 325 WN (See Model 2-106—Set 54-6)

CONRAC

10-M-36, 10-W-36 (Ch. 36) (See Ch. 36)
11-B-36 (Ch. 36) (See Ch. 36)
12-M-36, 12-W-36 (Ch. 36) (See Ch. 36)
13-B-36 (Ch. 36) (See Ch. 36)
14-M-36, 14-W-36 (Ch. 36) (See Ch. 36)
15-P-36 (Ch. 36) (See Ch. 36)
16-B-36 (Ch. 36) (See Ch. 36)
17-P-39 (Ch. 39) (See Ch. 39)

CONRAC—Cont.

18-M-39, 18-W-39 (Ch. 39) (See Ch. 39)
20-M-39, 20-W-39 (Ch. 39) (See Ch. 39)
21-B-39 (Ch. 39) (See Ch. 39)
22-39 (Ch. 39) (See Ch. 39)
23-M-390, 23-W-390 (Ch. 39) (See Ch. 39)
24-M-36 (Ch. 36) (See Ch. 36)
25-W-36 (Ch. 36) (See Ch. 36)
26-B-36 (Ch. 36) (See Ch. 36)
27-M-40, 27-W-40 (Ch. 40) (See Ch. 40)
28-B-40 (Ch. 40) (See Ch. 40)
29-P-40 (Ch. 40) (See Ch. 40)
30-M-40, 30-W-40 (Ch. 40) (See Ch. 40)
31-P-40 (Ch. 40) (See Ch. 40)
32-M-44, 32-W-44 (Ch. 44) (See Ch. 44)
33-B-44 (Ch. 44) (See Ch. 44)
34-P-44 (Ch. 44) (See Ch. 44)
35-M-61, 35-W-61 (Ch. 61) (See Ch. 61)
36-B-61 (Ch. 61) (See Ch. 61)
37-P-61 (Ch. 61) (See Ch. 61)
38-B-61, 38-M-61 (Ch. 61) (See Ch. 61)
39-M-61 (Ch. 61) (See Ch. 61)
40-M-64, 40-W-64 (Ch. 64) (See Ch. 64)
41-B-64 (Ch. 64) (See Ch. 64)
42-P-64 (Ch. 64) (See Ch. 64)
43-B-64, 43-M-64 (Ch. 64) (See Ch. 64)
Ch. 36 110-4
Ch. 39 110-4
Ch. 40 Series 140-4
Ch. 44 (See PCB 27—Set 148-1 and Ch. 40—Set 140-4)
Ch. 61, 64 Series 185-5

CONTINENTAL ELECTRONICS (See Skyweight)

CONVERSA-FONE

MS-5 (Master Station) SS-5 (Sub-Station) 16-7

CO-OP

6AWC2, 6AWC3, 6A47WCR, 6A47-WT, 6A47WTR 56-8

CORONADO

FA43-8945 (See Model 43-8945—Set 86-3)
K-21 (43-9041) 182-3
K-72 (43-9031) 182-3
K-73L (43-9030) 182-3
RA37-43-9240A 282-4
RA37-43-9240A 282-4
RA37-43-9855 227-5
RA42-9850A 274-4
TV1-9017A, B (Also See PCB 130—Set 289-1) 276-5
TV1-9017A, B (Also See PCB 130—Set 289-1) 276-5
TV2-9157A 285-7
TV2-9157A, TV2-9160A, TV2-9161A, TV2-9162A 285-7
OSRA1-43-7755A, OSRA1-43-7755B 101-2
OSRA1-43-7901A 115-2
OSRA2-43-8230A 162-3
OSRA2-43-8515A 110-5
OSRA3-43-8120A 110-6
OSRA3-43-8125 (See Model 94RA-33-43-8130C—Set 82-3) 102-3
OSRA37-43-8360A 102-3
OSTV1-43-905A, OSTV1-43-9006A, OSTV1-43-9005A, OSTV1-43-9006A, OSTV1-43-9014A 128-4
OSTV2-43-8950A 141-4
OSTV2-43-9010A 146-5
OSTV2-43-9010B 153-2
15RA1-43-7654A 147-3
15RA1-43-7902A 134-6
15RA2-43-8230A 162-3
15RA4-43-9876C, 15RA4-43-9877 (See Model OSRA4-43-9876A—Set 10-2) 174-5
15RA33-43-8245A, 15RA33-43-8246A 174-5
15RA33-43-8365 169-4
15RA37-43-9230A 175-5
15TV1-43-9057A, B 162-6
15TV1-43-9058A, B (Also See PCB 34—Set 162-1) 161-3
15TV1-43-9015A, B, 15TV1-43-9061A, B 162-4
15TV1-43-9020A, B, 15TV1-43-9021A, B (Also See PCB 34—Set 162-1) 161-3
15TV2-43-9025A, B, 15TV2-43-9026A, B 144-3
15TV2-43-9101A, 15TV2-43-9102A 152-4
15TV4-43-8948A, 15TV4-43-8949A 175-7
25TV2-43-9022A 183-4
25TV2-43-9022B (See PCB 65—Set 202-1 and Model 25TV2-43-9022A—Set 183-4)
25TV2-43-9022C (See PCB 65—Set 202-1, PCB 72—Set 212-1 and Model 25TV2-43-9022A—Set 183-4)
25TV2-43-9045A, B 199-5
25TV2-43-9045C (See PCB 66—Set 205-1 and Model 25TV2-43-9045A—Set 199-5)
25TV2-43-9060A 199-5
25TV2-43-9060B (See PCB 68—Set 205-1 and Model 25TV2-43-9060A—Set 199-5)
35RA2-43-5101A 214-3
35RA4-43-9856A 221-4
35RA33-43-8125 217-5
35RA33-43-8145 224-7
35RA33-43-8225 219-4
35RA37-43-8355 225-9
35RA40-43-8247A 236-3

CORONADO—Cont.

35TV2-43-9022C (See PCB 65—Set 202-1, PCB 72—Set 212-1 and Model 25TV2-43-9022A—Set 183-4)
35TV2-43-9023A 234-4
35TV2-43-9045D (See PCB 68—Set 205-1, PCB 71—Set 211-1 and Model 25TV2-43-9045E—Set 199-5)
35TV2-43-9045E (See Model 35-1V2-43-9045D)
35TV2-43-9050C (See PCB 66—Set 205-1, PCB 71—Set 211-1 and Model 25TV2-43-9060A—Set 199-5)
35TV2-43-9060D (See Model 35-1V2-43-9060C)
35TV2-43-9061A 237-5
43-2027 11-3
43-5005 28-36
43-6301 7-4
43-6451 10-10
43-6452 16-9
43-730 (See Model 43-8685—Set 11-4)
43-7401 (See Model 43-7601B—Set 10-11)
43-7601B 10-11
43-7602 (See Model 43-7601B—Set 10-11)
43-7651 9-7
43-7652 (See Model 43-7651—Set 9-7)
43-7851 47-5
43-7852 (See Model 43-7851—Set 47-5)
43-8101 (See Model 94RA31-43-8130C, 43-8131C (See Model 94RA33-43-8130C—Set 82-3) 43-8177 (See Model 43-8178—Set 21-8)
43-8178 21-8
43-8180 10-12
43-8190 19-11
43-8201 (See Model 43-8178—Set 21-8)
43-8213 7-5
43-8240, 43-8241 12-8
43-8305 8-3
43-8312A 8-4
43-8330 19-12
43-8351, 43-8352 28-7
43-8353, 43-8354 28-7
43-8420 24-13
43-8470 8-3
43-8471 8-4
43-8576B 9-8
43-8685 11-4
43-8965 86-3
43-9030 182-3
43-9031 182-3
43-9041 182-3
43-9056 14-35
43-9201 24-14
43-9841A (See Model 94RA31-43-9841A—Set 79-3) 232-3
45RA1-43-7666A 232-3
45RA1-43-7910A, 45RA1-43-7911-2 (See Model 15RA1-43-7902A—Set 134-6) 219-4
45RA33-43-8126 (See Model 35-RA33-43-8146—Set 217-5) 43-8146 (See Model 35-RA33-43-8146—Set 224-7)
45RA33-8222 45RA33-8226 45RA33-8227 45RA33-8228 (See Model 35RA33-43-8225—Set 219-4)
45RA33-43-8355 (See Model 35-RA37-43-8356—Set 225-9)
45RA37-43-8355 (See Model 35-RA37-43-8355—Set 225-9)
45TV2-43-9023B 234-4
45TV2-43-9045F (See Model 35TV2-43-9045D)
45TV2-43-9050B (See Model 35TV2-43-9050A—Set 237-5)
45TV2-43-9060E (See Model 35TV2-43-9045D)
45TV2-43-9061B 237-5
45TV2-43-9064A 237-5
45TV1-43-9027A, 45TV1-43-9028A (Series XT-100) 262-5
45TV11-43-9085A, 45TV11-43-9086A, 45TV11-43-9088A, 45TV11-43-9089A, 45TV11-43-9090A, 45TV11-43-9091A, 45TV11-43-9092A, 45TV11-43-9093A, 45TV11-43-9094A, 45TV11-43-9095A, 45TV11-43-9096A, 45TV11-43-9097A, 45TV11-43-9098A (Series XT-100) 262-5
45TV11-43-9130A, 45TV11-43-9131A (Series XT-100) 262-5
45TV13-43-9038A 252-5
45TV13-43-9081A 252-5
94RA1-43-6945A 69-6
94RA1-43-7605A 65-5
94RA1-43-7656A, 94RA1-43-7657A 73-2
94RA1-43-7751A 87-3
94RA1-43-8510A, 94RA1-43-8511-1A 71-7
94RA1-43-8510B, 94RA1-43-8511-2A 75-6
94RA2-43-8230A 162-3
94RA4-43-8129A 94RA4-43-8130A, 94RA4-43-8130B, 94RA4-43-8131A, 94RA4-43-8131B, 94RA4-43-8132A (See Model 94RA4-43-8129A—Set 62-10) 94RA31-43-8115A, B, 94RA31-43-8116A 81-5
94RA31-43-9841A 79-3
94RA33-43-8130C, 94RA33-43-8131C 82-3
94TV2-43-8970A, 94TV2-43-8971-A, 94TV2-43-8972A, 94TV2-43-8973A, 94TV2-43-8974A, 94TV2-43-9313A, 94TV2-43-9314A

DEWALD—EMERSON

DEWALD—Cont.

- DT-190 118-5
- DT-190D (Also see PCB 58—Set 192-1) 136-7
- DT-1020, DT-1020A 100-6
- DT-1030, DT-1030A 100-6
- DT-X-160 100-6
- E-520 274-6
- E-522 141-5
- ET-140, ET-141 118-5
- ET-140R, ET-141R (Also see PCB 58—Set 192-1) 136-7
- E-170, ET-171 (Also see PCB 58—Set 192-1) 136-7
- ET-171-20 208-3
- ET-172 (Also see PCB 58—Set 192-1) 136-7
- ET-190D, R (Also see PCB 58—Set 192-1) 136-7
- ET-190D (Revised) 208-3
- F-404 181-5
- F-405 198-5
- F-523 170-5
- FT-200 (See PCB 58—Set 192-1 and Model DT-162R—Set 136-7)
- FT-200 (Revised) 208-3
- FT-201 (See PCB 58—Set 192-1 and Model DT-162R—Set 136-7)
- G-174 208-3
- G-201 208-3
- G-210, G-211 208-3
- G-408 220-3
- H-300 UHF Conv. 250-7
- H-410 264-6
- H-527 239-5
- H-528 234-5
- H-533 248-4
- H-537 266-4
- 511 71-9

DODGE (See Mopar)

DORN'S (See Bell Air)

DOUGLAS

- 327 (Ch. S-103, T-103) 246-4

DREXEL (Mutual Buying Syndicate)

- 17CG1, 17TW (Similar to Chassis) 149-13

DUKANE

- 1A45-A 184-5
- 1A300, 18300 189-6
- 1U325 185-6
- 4A100 186-5
- 4B100 (See Model 4A100—Set 186-5)
- 4C25 Flexiphone 187-4
- 4C100 200-4

DUMONT

- RA-103 (Also see PCB 6—Set 108-1) 90-3
- RA-103D (Also see PCB 9—Set 114-1) 93-4
- RA-104A (Also see PCB 9—Set 114-1) 93-4
- RA-105 (Also see PCB 6—Set 108-1) 72-8
- RA-105B 95-3
- RA-106 (Supp. to RA-105, Set 72-8) (Also see PCB 6—Set 108-1) 99A-4
- RA-108A 95-3
- RA-109A-FAS (See PCB 54—Set 188-1 and Model RA-109—Set 110-7)
- RA-109-A1, -A2, -A3, -A5, -A6, -A7 (Also see PCB 14—Set 124-1) 110-7
- RA-110A (Also see PCB 9—Set 114-1) 93-4
- RA-111-A1, -A2, -A3, -A5 106-6
- RA-112-A1, -A2, -A3, -A4, -A5, -A6 (Also see PCB 38—Set 170-1) 119-5
- RA-113-B1, -B2, -B3, -B4, -B5, -B6, -B7, -B8 (Also see PCB 38—Set 170-1) 119-5
- RA-116A 131-5
- RA-117-A1, -A3, -A5, -A6, -A7 131-5
- RA-119A 156-5
- RA-120 (See PCB 51—Set 185-1 and Model RA-113—Set 119-5)
- RA-130A (See PCB 54—Set 188-1 and Model RA-109—Set 110-7)
- RA-147A (See PCB 49—Set 183-1 and Model RA-117A—Set 131-5)
- RA-140, -A1 (Also see PCB 55—Set 189-1) 179-4
- RA-162, -B1, -B4, -B5, -B6, -B7, -B21 through 26 (Also see PCB 55—Set 189-1) 179-4
- RA-164, -A1 (Also see PCB 69—Set 194-1 and PCB 69—Set 206-1) 189-7
- RA-166, RA-167, RA-168, RA-169, RA-170, RA-171 216-2
- RA-301, RA-301-A1, RA-302 270-4
- RA-306, RA-307 241-6
- RA-321, RA-322 287-6
- Andover Model RA-117-A6 (See Model RA-117A)
- Andover Model RA-147A (See Model RA-147A)
- Ardmore Model RA-112-A1, -A4 (See Model RA-112A)
- Banbury Model RA-162-B4 (See Model RA-162)
- Banbury Model RA-162-B21 through 826 (See Model RA-162)
- Beverly Model RA-165-B2 (See Model RA-165)
- Bradford (See Model RA-108A)
- Bradford Models RA-306, RA-307 (See Model RA-306)
- Bristol Models RA-306, RA-307 (See Model RA-306)

DUMONT—Cont.

- Brookville Model RA-113-B1, -B2 (See Model RA-113) 82
- Burlington Model RA-113-B5, -B6 (See Model RA-113) 82
- Cambridge Model RA-103 (See Model RA-103) 82
- Carlton Model RA-117-A3 (See Model RA-117A) 82
- Chatham (See Model RA-103) 82
- Chatham Model RA-166 (See Model RA-166) 82
- Chatham Model RA-168, RA-169 (See Model RA-168) 82
- Chester (See Model RA-147A) 82
- Clinton Model RA-164-A1 (See Model RA-164) 82
- Club 20 (See Model RA-106A) 82
- Colony (See Model RA-105A) 82
- Devon Model RA-160-A1 (See Model RA-160) 82
- Dynasty (See Model RA-162) 82
- Essex Model RA-167 (See Model RA-167) 82
- Fairfield (See Model RA-110A) 82
- Flinders Model RA-162-B5 (See Model RA-162) 82
- Glendale (See Model RA-321) 82
- Guilford Model RA-112-A2, -A5 (See Model RA-112A) 82
- Hampton Model RA-306, RA-307 (See Model RA-306) 82
- Hanover Model RA-109-A2, -A6 (See Model RA-109A) 82
- Hanover (See Model RA-109A-FAS) 82
- Hanover Model RA-162 (See Model RA-162) 82
- Hanover II Model RA-170 (See Model RA-170) 82
- Hanover II Model RA-171 (See Model RA-171) 82
- Harford Models RA-306, RA-307 (See Model RA-306) 82
- Hastings (See Model RA-104A) 82
- Lynwood Model RA-167 (See Model RA-167) 82
- Lynwood Model RA-169 (See Model RA-169) 82
- Manchu (See Model RA-106A) 82
- Mansfield (See Model RA-108A) 82
- Meadowbrook Model RA-103 (See Model RA-103) 82
- Meadowbrook II (See Model RA-147A) 82
- Millford Model RA-165-B1 (See Model RA-165) 82
- Mt. Vernon Model RA-112-A3, -A6 (See Model RA-112A) 82
- Newbury (See Model RA-162) 82
- Newbury II Model RA-170 (See Model RA-170) 82
- Newbury II Model RA-171 (See Model RA-171) 82
- Newport Models RA-306, RA-307 (See Model RA-306) 82
- Oxford Model RA-167 (See Model RA-167) 82
- Park Lane Model RA-117-A7 (See Model RA-117A) 82
- Parklane (See Model RA-147A) 82
- Putnam Model RA-111-A1, -A4 (See Model RA-111A) 82
- Revere Model RA-113-B3, -B4 (See Model RA-113) 82
- Ridgewood Model RA-165-B4 (See Model RA-165) 82
- Ridgewood "41" Model RA-167 (See Model RA-167) 82
- Royal Sovereign (See Model RA-119A) 82
- Rumson (See Model RA-103D) 82
- Rutland Models RA-306, RA-307 (See Model RA-306) 82
- Savoy (See Model RA-103) 82
- Sheffield (See Model RA-103D) 82
- Sheffield Models RA-306, RA-307 (See Model RA-306) 82
- Shelburne Model RA-165-B5 (See Model RA-165) 82
- Sutton Model RA-167 (See Model RA-167) 82
- Sherbrooke Models RA-109-A3 -A7 (See Model RA-109A) 82
- Sherbrooke (See Model RA-109A-FAS) 82
- Sherbrooke (See Model RA-130A) 82
- Somerset (See Model RA-162) 82
- Somerset II Model RA-170 (See Model RA-170) 82
- Somerset III Model RA-171 (See Model RA-171) 82
- Stratford (See Model RA-105A) 82
- Strathmore Model RA-117-A5 (See Model RA-117A) 82
- Sumter Model RA-117-A1 (See Model RA-117A) 82
- Sussex (See Model RA-105B) 82
- Sutton Model (RA-103 (See Model RA-103) 82
- Tarrytown Models RA-113-B7, -B8 (See Model RA-113) 82
- Tarrytown (See Model RA-120) 82
- Wakefield Model RA-165-B3 (See Model RA-166) 82
- Wakefield "41" Model RA-167 (See Model RA-167) 82
- Warren Models RA-306, RA-307 (See Model RA-307) 82
- Warwick Models RA-306, RA-307 (See Model RA-306) 82
- Wellington (See Model RA104A) 82
- Westport Model RA-306, RA-307 (See Model RA-306) 82
- Westbury (See Model RA-105A) 82
- Westbury II (See Model RA-109A-FAS) 82
- Westerly Model RA-112-A2, -A5 (See Model RA-112A) 82
- Whitehall (See Model RA-105A) 82
- Whitehall II (See Model RA-130A) 82
- Whitehall III (See Model RA-162-B7 (See Model RA-162) 82
- Wickford Model RA-162-B1 (See Model RA-162) 82
- Wimbledon Model RA-162-B6 (See Model RA-162) 82
- Windsor Models RA-306, RA-307 (See Model RA-306) 82
- Winstow (See Model RA-109A-FAS) 82

DUMONT—Cont.

- Winstow Model RA-109-A1, -A5 (See Model RA-109A) 82
- Winthrop Model RA-103 (See Model RA-103) 82

DUOSONIC

- K1, K2 19-15
- K3, K4 19-16

DYNAVOX

- AP-514 (Ch. AT) 28-9
- H-510 15-8
- Swingmaster 27-7
- 3-P-801 36-3

ECA

- 101 (Ch. AA) 1-25
- 102 14-7
- 104 13-14
- 105 16-11
- 106 7-10
- 108 3-6
- 121 13-15
- 131 16-12
- 132 45-9
- 201 15-9
- 202 32-5

ECHOPHONE (Also see Hallcrafters)

- EC-113 3-13
- EC-306 14-18
- EC-403, EC-404 22-14
- EX-600 4-18
- EX-102, EX-103 64-5
- EX-306 (See Model EC-306—Set 14-8) 14-8

EDWARDS

- Fieldtuner 33-4

EICOR (Also see Recorder Listing)

- 15 135-6

EKOTAPE (See Recorder Listing)

ELCAR

- 602 5-19

ELECTONE

- T5T53 12-34

ELECTRO

- B-20 14-9

ELECTROMATIC

- APH301-A, APH301-C 7-11
- 660A, 607A 5-32

ELECTRO-TONE

- 555 13-17
- 706, 712 (See Model 555—Set 13-16) 13-16

ELECTRO-VOICE

- A-20C 285-10
- 3300 Tel. UHF Conv. 222-5

ELECTRONIC CORP. OF AMERICA (See ECA)

ELECTRONIC SPECIALTY CO. (See Ranger)

E/L (ELECTRONIC LABS.)

- 75 (Sub-Station) 20-6
- 76E, K, W (See Model 2701—Set 4-28) 20-6
- 76RU ("Radio-Utiliphone") 20-6
- 710B, 710M, 710T, 710W, Orthosonic (Ch. 2875) 20-7
- 710PB, 710PC Orthosonic (Ch. 2887) 24-16
- 2660 "Master Utiliphone" 4-28
- 2701 4-28
- 3000 Orthosonic 31-10

EMERSON

- 501, 502 (Ch. 120000, 120029) 2-1
- 503 (Ch. 120000, 120029) 1-18
- 504 (Ch. 120000, 120029) 2-1
- 505 (Ch. 120002) 8-9
- 505 (Ch. 120041) (See Model 523—Set 5-27) 5-27
- 506 6-9
- 507 8-10
- 508 (Ch. 120008) 7-12
- 509 8-10
- 510, 510A (Ch. 120000, 120029) 5-36
- 511 8-10
- 511 (Ch. 120010) (See Model 541—Set 16-23) 9-12
- 512 (Ch. 120006) 24-11
- 512 (Ch. 120056) 24-11
- 514 (Ch. 120007) 27-8
- 515, 516 12-11
- 515, 516 (Ch. 120056) 26-11
- 517 (Ch. 120010) (See Model 541—Set 16-13) 8-10
- 518 30-7
- 519 (Ch. 120030) 8-10
- 520 (Ch. 120000, 120029) 2-1
- 521 (Ch. 120013, 120031) 7-13
- 522 8-10
- 523 5-37
- 524 17-12
- 525 20-8
- 528 (Ch. 120038) 21-13
- 529, 529-9 (Ch. 120028) 18-15
- 530 (Ch. 120006, Ch. 120056) 32-6
- 531, 532, 533 27-8
- 534 (Ch. 120007) 20-9
- 535 20-9
- 536 (Ch. 120036) 21-14
- 536A 24-17
- 537 23-7
- 538 (Ch. 120051) (See Model 549—Set 26-12) 9-13
- 539 9-13
- 540A (Ch. 120042) 20-10
- 541 16-13
- 542 (See Model 521—Set 7-13) 19-30
- 543, 544 (Ch. 120046) 63-8

EMERSON—Cont.

- 545 (Ch. 120047) Photofact Servicer 82
- 546 (Ch. 120049) 21-15
- 547A (Ch. 120050) 25-13
- 548 (Ch. 120051) 30-8
- 549 (Ch. 120051) 26-12
- 550 (Ch. 120006) (See Model 512—Set 9-12) 26-11
- 550 (Ch. 120056) 24-17
- 551A 25-9
- 552 24-17
- 553A 70-4
- 556, 557 (Ch. 120018B) 43-10
- 557B (Ch. 120048B) 31-11
- 558 (Ch. 120058) 31-12
- 559A (Ch. 120059) 25-14
- 560 (Ch. 120061) 73-4
- 561 (Ch. 120001B) 73-4
- 563 (Ch. 120063B) 73-4
- 564 (Ch. 120027) (See Model 540A—Set 20-10) 70-4
- 565 (Ch. 120018B) 70-4
- 566 (Ch. 120051) (See Model 549—Set 26-12) 567 (Ch. 120016) (See Model 560—Set 25-14) 567 (Ch. 120042) (See Model 540A—Set 20-10) 58-9
- 568A (Ch. 120070A) 42-10
- 569A (Ch. 120062A) 97-3
- 570 (Ch. 120064) 46-25
- 571 (Ch. 120066) 76-11
- 571 (Ch. 120086B) (See Model 540A—Set 20-10) 42-11
- 573B (Ch. 120039B) 97-3
- 574 (Ch. 120064) 85-6
- 575 (Ch. 120068A, 120068B) 40-5
- 576A (Ch. 120069A) 41-6
- 578 (Ch. 120050) (See Model 547A—Set 25-13) 61-6
- 579A (Ch. 120034A) 97-3
- 580 (Ch. 120064) 68-7
- 581 (Ch. 120014A, B) 30-8
- 582 (See Model 547A—Set 25-13)
- 583 (See Model 573B—Set 42-11)
- 584 (See Model 558—Set 31-11) 61-7
- 585 (Ch. 120025B) 72-9
- 586 (Ch. 120023B, 120083B) 71-10
- 587 (Ch. 120033A, B) 71-10
- 588 (See Model 547A—Set 25-13)
- 590 (Ch. 12001A, B) 67-9
- 591 (Ch. 120055A) 73-4
- 593 (Ch. 120063B) 68-7
- 594, 595 (Ch. 120071A) 61-6
- 596 90-5
- 597 (Ch. 120073B) 69-8
- 599 (Ch. 120075B) 87-6
- 600 (Ch. 120103-B) (Also see PCB 9—Set 114-1) 69-8
- 601 (Ch. 120075B) 56-10
- 602 (Ch. 120072A, 120082A) 73-4
- 603 (Ch. 120063B) 60-5
- 604A (See Model 576A—Set 40-5)
- 605 (Ch. 120076B) 46-25
- 606 (Ch. 120066) 76-11
- 606 (Ch. 120086B-D) 76-11
- 607 (Ch. 120068) 90-5
- 607 (Ch. 120074) 84-6
- 608A (Ch. 120089B) 90-6
- 609 (Ch. 120084-B) 71-10
- 610 (Ch. 120100A, B) 76-11
- 611, 612 (Ch. 120087B-D) 76-11
- 613A (Ch. 12005A, B) 97-4
- 614, B, BC, C (Ch. 120110, B, BC, C) 97-4
- 614D (Ch. 120095-B) 63-7
- 615 (Ch. 120001B) 71-10
- 616 (Ch. 120100A, B) 76-11
- 617 (Ch. 120092D) 76-11
- 620 (Ch. 120091D-QD) 76-11
- 621 (Ch. 120098B) 108-5
- 622 (Ch. 120098P) 87-5
- 623 (Ch. 120101A, B) 76-11
- 624 (Ch. 120087B-D) 102-6
- 625 (Ch. 120108) 84-6
- 626 (Ch. 120104B, 120104B) 84-6
- 627 (Ch. 120107B) 108-5
- 628 (Ch. 120098B) 84-6
- 629 (Ch. 120114B) (See Model 631—Set 93A-6) 116-5
- 629B, 629C (Ch. 120120) 116-5
- 629D (Ch. 120124B) 108-5
- 630 (Ch. 120099B) 93A-6
- 631 (Ch. 120109) 93A-6
- 632 (Ch. 120098B) 93A-6
- 633 (Ch. 120114) 111-4
- 634B (Ch. 120097B) 92-1
- 635 (Ch. 120108) 97-4
- 636A (Ch. 120106A) 84-6
- 637, B, BC, C (Ch. 120110, B, BC, C) 97-4
- 637A (Ch. 120095-B) 93A-6
- 638 (Ch. 120087D) (See Model 571—Set 76-11) 87-6
- 639 (Ch. 120103B) (Also see PCB 9—Set 114-1) 120-5
- 640 (Ch. 120112) 120-5
- 641B (Ch. 120125B) 98-3
- 642 (Ch. 120117A) 91-4
- 643A (Ch. 120111A) 97-4
- 644, B, BC, C (Ch. 120113, B, BC, C) 97-4
- 645 (Ch. 120115) 102-6
- 646A (Ch. 120121A) 102-6
- 646B (Ch. 120121B) 102-6
- 647, B, BC, C (Ch. 120113, B, BC, C) 97-4
- 648B (Ch. 120134B, G, H) (See PCB 48—Set 182-1 and Model 661B—Set 137-4) 106-7
- 649A (Ch. 120094A) 614
- 650 (Ch. 120113C) (See Model 614—Set 97-4) 113-2
- 650 (Ch. 120118B) 133-1A
- 650B (Ch. 120118B) (See Model 650—Set 113-2) (Also see PCB 48—Set 182-1) 133-1A
- 650F (Ch. 120138-B) 119-6
- 651B (Ch. 120120) 93A-6
- 651C (Ch. 120109) 116-5
- 651C (Ch. 120124) 116-5

EMERSON—Cont.

- 652 (Ch. 120032B) 98-3
- 653 (Ch. 120080B) 98-3
- 653B (Ch. 120136B) 113-2
- 654B (Ch. 120118B) 113-2
- 654B (Ch. 120118B) (See Model 654—Set 113-2) 116-5
- 654D (Ch. 120123B) (Also see PCB 48—Set 182-1) 109-3
- 654E (Ch. 120138B) 131-1A
- 655B (Ch. 120123-B) 109-3
- 655D (Ch. 120123B) (See Model 650D—Set 109-3) 133-1A
- 655F (Ch. 120138-B) 111-5
- 656B, 657B (Ch. 120122B) 113-1A
- 658B (Ch. 120124, B) 116-5
- 658C (Ch. 120124) (See Model 629D—Set 116-5) 131-6
- 660B (Ch. 120138B) 131-6
- 661B (Ch. 120134B, G, H) (Also see PCB 48—Set 182-1) 137-4
- 662B (Ch. 120127-B) (Also see PCB 48—Set 182-1) 125-6
- 663B (Ch. 120128-B) (Also see PCB 18—Set 130-1) 131-6
- 664B (Ch. 120133-B) 131-6
- 665B (Ch. 120131-B and Radio Ch. 120130-B) 146-6
- 6660B (Ch. 120135B, G, H, and Radio Ch. 120132B) (Also see PCB 27—Set 148-1) 133-5
- 667B, 668B (Ch. 120134B, G, H) (Also see PCB 48—Set 182-1) 137-4
- 669B (Ch. 120129B, D) (Also see PCB 24—Set 142-1 and PCB 47—Set 181-1) 126-5
- 671B (Ch. 120137-B) 118-6
- 671D (Ch. 120137D) (See Model 671B—Set 118-6) 131-7
- 672B (Ch. 120097B) 131-6
- 673B (Ch. 120133-B) 131-6
- 674B (Ch. 120134B, G, H) (Also see PCB 48—Set 182-1) 137-4
- 675B (Ch. 120129B, D) (Also see PCB 24—Set 142-1 and PCB 47—Set 181-1) 126-5
- 676B (Ch. 120140B) 128-6
- 676D (Ch. 120144B, G, H) (Also see PCB 48—Set 182-1) 138-4
- 676F (Ch. 120143B) (Also see PCB 50—Set 184-1) 148-6
- 677B, 678B (Ch. 120134B, G, H) (Also see PCB 48—Set 182-1) 137-4
- 679B (Ch. 130116-B) 142-7
- 680B (Ch. 120144-B, G, H) (Also see PCB 48—Set 182-1) 138-4
-

EMERSON—Cont.
717D (Ch. 120163-D) 190-2
717F (Ch. 120168-D) [See PCB 61]
Set 195-1, PCB 71—Set 211-1
and Model 716D—Set 190-2
718B (Ch. 120150-B) 191-7
719D (Ch. 120151-B) 190-2
719F (Ch. 120168-D) [See PCB 61]
Set 195-1, PCB 71—Set 211-1
and Model 716D—Set 190-2
720B (Ch. 120164-B) 183-6
720D (Ch. 120169B) 206-4
720F (Ch. 120169B) 206-4
721D (Ch. 120166-D) [Also see PCB 65]
Set 202-1 and PCB 77—Set 218-1
197-5
722D (Ch. 120163-D) 190-2
724B (Ch. 120151-B) 208-5
725A (Ch. 120149A) 209-2
727D (Ch. 120168-D) [See PCB 61]
Set 195-1, PCB 71—Set 211-1
and Model 716D—Set 190-2
728D (Ch. 120166-D) [Also see PCB 65]
Set 202-1 and PCB 77—Set 218-1
729B (Ch. 120170-B) 251-6
731D (Ch. 120167-D and Radio Ch. 120152-B) [See PCB 65]
Set 202-1 and Model 721D—Set 197-5
732B (Ch. 120169B) 206-4
732D (Ch. 120164-B) [See Model 711B—Set 183-6]
733F (Ch. 120169F and Radio Ch. 120152F) 206-4
732G (Ch. 120185-B) 206-4
734B (Ch. 120169B) 243-4
736B (Ch. 120171-B) [See PCB 65]
Set 202-1, PCB 77—Set 218-1
and Model 721D—Set 197-5
737A, B (Ch. 120172A, B) 207-3
738B (Ch. 120150-B) [See Model 718B—Set 191-7]
740D (Ch. 120173-D) [See PCB 65]
Set 202-1, PCB 77—Set 218-1
and Model 721D—Set 197-5
741D (Ch. 120168-D) [See PCB 61]
Set 195-1, PCB 71—Set 211-1
and Model 716D—Set 190-2
741F (Ch. 120182-D) [Also see PCB 103]
Set 249-1 and PCB 117—Set 269-1
742B (Ch. 120169B) 206-4
742E (Ch. 120185-B) 243-4
743A (Ch. 120171-B) [See Model 738B]
743B (Ch. 120171-B) [See PCB 65]
Set 202-1, PCB 77—Set 218-1
and Model 721D—Set 197-5
744B (Ch. 120175-B) 231-6
745B (Ch. 120175-B) 227-7
746B (Ch. 120178-B) 238-9
747A (Ch. 120178-B) 234-8
748B (Ch. 120179-B) 263-7
748C (Ch. 120203-B) 263-7
750D (Ch. 120166-D) [See PCB 65]
Set 202-1, PCB 77—Set 218-1
and Model 721D—Set 197-5
751D (Ch. 120168-D) [See PCB 61]
Set 195-1, PCB 71—Set 211-1
and Model 716D—Set 190-2
752A, B (Ch. 120174-B) 243-4
753D (Ch. 120180-D) 243-4
753F (Ch. 120176-B) [See Model 745B—Set 227-7]
755A, B (Ch. 120174-B) 243-4
756B (Ch. 120125-B) [See Model 641B—Set 120-5]
757D (Ch. 120182-D) [Also see PCB 103]
Set 249-1 and PCB 117—Set 269-1
757F (Ch. 120194-D) [See PCB 61]
Set 195-1, PCB 71—Set 211-1,
PCB 86—Set 229-1 and Model 716D—Set 190-2
758F (Ch. 120182-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
759C (Ch. 120195-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 785C—Set 235-5
760D (Ch. 120193-D) 243-4
760F (Ch. 120194-D) [See PCB 61]
Set 195-1, PCB 71—Set 211-1,
PCB 86—Set 229-1 and Model 716D—Set 190-2
760M (Ch. 120192-D) 243-4
760J (Ch. 120168-D) [See PCB 61]
Set 195-1, PCB 71—Set 211-1,
PCB 86—Set 229-1 and Model 716D—Set 190-2
760M (Ch. 120182-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
761C (Ch. 120180-D) 243-4
762D (Ch. 120191-D) 243-4
762F (Ch. 120190-D) 243-4
764F (Ch. 120166-D) [See PCB 65]
Set 202-1, PCB 77—Set 218-1
and Model 721D—Set 197-5
765D (Ch. 120173-D) [See Model 740D]
766D (Ch. 120210-D) 243-4
767A, B (Ch. 120192-B) 243-4
767C (Ch. 120169-B) [See Model 711F—Set 206-4]
768A (Ch. 120193-D) 243-4
768C (Ch. 120174-B) [See Model 752A—Set 243-4]
769F (Ch. 120173-D) [See Model 740D]
770C (Ch. 120209-D) 243-4
771A, B (Ch. 120192-B) 243-4
771C (Ch. 120169-B) [See Model 711F—Set 206-4]
771D (Ch. 120192-D) 243-4
772A (Ch. 120193-B) 243-4
773A (Ch. 120192-B) 243-4
774A (Ch. 120193-B) 243-4
775A, B (Ch. 120192-F and Radio Ch. 120184-B) 243-4
776A (Ch. 120193-F and Radio Ch. 120184-B) [See Model 775A—Set 243-4]

EMERSON—Cont.
777B (Ch. 120204-B) 263-7
778B (Ch. 120199B) 248-6
779B (Ch. 120170-B) 251-6
780A (Ch. 120171-B) [See Model 736B]
781A, B (Ch. 120196-B) [Also see PCB 103]
Set 249-1 and PCB 117—Set 269-1
781E (Ch. 120206-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
782D (Ch. 120166-D) [See Model 707D]
783B (Ch. 120200B) 252-7
784A (Ch. 120174-B) 243-4
784E (Ch. 120197-B) [Also see PCB 103]
Set 249-1 and PCB 117—Set 269-1
784G (Ch. 120197-D) 235-5
784C (Ch. 120197-B) [See PCB 103]
Set 249-1 and PCB 117—Set 269-1
784K (Ch. 120197-B) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 784E—Set 235-5
784M (Ch. 120211-D) [See PCB 103]
Set 249-1 and Model 741F—Set 235-5
785C, E (Ch. 120198-D) 243-4
785K (Ch. 120195-D) [Also see PCB 103]
Set 249-1, PCB 117—Set 269-1
787A (Ch. 120179-B) 235-5
787B (Ch. 120203-B) 263-7
788B (Ch. 120201B) 250-8
789B (Ch. 120207-B) 258-6
790B (Ch. 120147-B) 255-5
791D (Ch. 120210-D) 243-4
792D (Ch. 120206-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
793E (Ch. 120211-F) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
794A (Ch. 120193-B) [See Model 768A—Set 243-4]
795C (Ch. 120192-B) 243-4
796C (Ch. 120203-B) 263-7
797B (Ch. 120204-B) 263-7
797C (Ch. 120205-B) 263-7
798B (Ch. 120203-B) 263-7
799C (Ch. 120209-F) 243-4
800B (Ch. 120159-B) 263-7
801 (Ch. 120154-B) [See Model 704—Set 184-6]
802B (Ch. 120159-B) 267-3
805B (Ch. 120202D) 260-7
806, 807 275-7
808B (Ch. 120189-B) 275-7
809A (Ch. 120221-A) 266-5
810B (Ch. 120222-B) 268-6
811B (Ch. 120228-B) 274-8
812B (Ch. 120229-B) 272-6
813B (Ch. 120230-B) 272-6
816A (Ch. 120201-B) [See Model 788B—Set 250-8]
818B (Ch. 120159-B) [Revised] [See Model 800B—Set 267-3]
822B (Ch. 120232-B) 274-8
823B (Ch. 120250-B) [See Model 641B—Set 120-5]
825B, 826B (Ch. 120243-B) 287-7
828B (Ch. 120207-B) [See Model 789B—Set 258-6]
836B (Ch. 120159-B) [Revised] [See Model 800B—Set 267-3]
1000C (Ch. 120206-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1001E (Ch. 120208-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1001G (Ch. 120211-E) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1001I (Ch. 120211-F) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1002C (Ch. 120206-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1002D (Ch. 120206-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1002F (Ch. 120225-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 785C—Set 235-5
1003 (Ch. 120206-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1003E (Ch. 120208-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1003F (Ch. 120208-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1003G (Ch. 120211-F) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1004C (Ch. 120206-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1004F (Ch. 120225-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1005E (Ch. 120208-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1005F (Ch. 120208-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1005G (Ch. 120211-F) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1006C (Ch. 120206-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1006F (Ch. 120225-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1007E (Ch. 120208-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1007G (Ch. 120211-F) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1008C (Ch. 120206-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5

EMERSON—Cont.
1008E (Ch. 120206-D) [See PCB 103]
Set 249-1 and Model 741F—Set 235-5
1008F (Ch. 120225-F) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1009E (Ch. 120208-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1009G (Ch. 120211F) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1010C (Ch. 120211-F) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1011C (Ch. 120208-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1011G (Ch. 120211-F) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1012D (Ch. 120182-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1012F (Ch. 120223-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1013C (Ch. 120195-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1014D (Ch. 120182-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1015C (Ch. 120195-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 785K—Set 235-5
1018C, D (Ch. 120206-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1022C, D (Ch. 120206-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1023E (Ch. 120211-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1024C (Ch. 120206-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1025E (Ch. 120211-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1026C (Ch. 120206-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1027E (Ch. 120211-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1028C (Ch. 120206-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1029E (Ch. 120211-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1030D, 1032D (Ch. 12020-D) 275-7
1036F (Ch. 120225-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1040D (Ch. 120225-F) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1040F (Ch. 120225-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1041E (Ch. 120211-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1042D (Ch. 120225-D) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1044F (Ch. 120225-F) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
1058B, 1060D, 1062D, 1064D (Ch. 120239-D) 275-7
1074F (Ch. 120225-F) [See PCB 103]
Set 249-1, PCB 117—Set 269-1
and Model 741F—Set 235-5
120025B (See Model 585)
Ch. 120047 (See Model 545)
Ch. 120066 (See Model 571)
Ch. 120084B (See Model 609)
Ch. 120085B (See Model 571)
Ch. 120078B (See Model 511)
Ch. 120088B (See Model 585)
Ch. 120089B (See Model 608A)
Ch. 120091D-QD (See Model 620)
Ch. 120092D (See Model 619)
Ch. 120094A (See Model 642A)
Ch. 120095-B (See Model 614)
Ch. 120096B (See Model 632)
Ch. 120098B (See Model 621)
Ch. 120098P (See Model 622)
Ch. 120099B (See Model 630)
Ch. 120103B (See Model 600)
Ch. 120104B (See Model 600)
Ch. 120104B, BJ (See Model 626)
Ch. 120107B (See Model 627B)
Ch. 120109 (See Model 631)
Ch. 120110, B, BC, C (See Model 614, B, BC, C)
Ch. 120110E (See Model 648B)
Ch. 120113, B, BC, C (See Model 644, B, BC, C)
Ch. 120114 (See Model 633)
Ch. 120118B (See Model 650)
Ch. 120120 (See Model 629B, C)
Ch. 120123B (See Model 650D)
Ch. 120124 (See Model 651C)
Ch. 120125-B (See Model 629D)
Ch. 120127-B (See Model 622B)
Ch. 120128-B (See Model 663B)
Ch. 120129B (See Model 669B)
Ch. 120131-B (See Model 665B)
Ch. 120132B (See Model 660B)
Ch. 120134B, G, H (See Model 661B)
Ch. 120135B, G, H (See Model 666B)
Ch. 120136-B (See Model 653B)
Ch. 120138-B (See Model 650F)
Ch. 120140B (See Model 678B)
Ch. 120142B (See Model 6861)

EMERSON—Cont.
Ch. 120143B, H (See Model 676F)
Ch. 120144B, G, H (See Model 676D)
Ch. 120147-B (See Model 790B)
Ch. 120149A (See Model 725A)
Ch. 120150-B (See Model 718B)
Ch. 120151-B (See Model 724B)
Ch. 120152-B (See Model 731D)
Ch. 120152-F (See Model 733F)
Ch. 120153-B (See Model 700B)
Ch. 120154-B (See Model 704)
Ch. 120155A, B (See Model 705A, B)
Ch. 120158-B (See Model 700D)
Ch. 120159-B (See Model 800B)
Ch. 120160-B (See Model 699D)
Ch. 120162A (See Model 709A)
Ch. 120163-D (See Model 716D)
Ch. 120164-B (See Model 711B)
Ch. 120166-D (See Model 721D)
Ch. 120167-D (See Model 731D)
Ch. 120168-D (See Model 716F)
Ch. 120169-B (See Model 711F)
Ch. 120169-D (See Model 716F)
Ch. 120169-F (See Model 733F)
Ch. 120170-B (See Model 729B)
Ch. 120171-B (See Model 736B)
Ch. 120172A, B (See Model 737A, B)
Ch. 120173-D (See Model 740D)
Ch. 120174-B (See Model 752A)
Ch. 120175-B (See Model 744B)
Ch. 120176-B (See Model 745B)
Ch. 120177-B (See Model 746B)
Ch. 120178 (See Model 747)
Ch. 120179-B (See Model 749B)
Ch. 120180-D (See Model 753D)
Ch. 120182-D (See Model 741F)
Ch. 120184-B (See Model 775A)
Ch. 120185-B (See Model 732G)
Ch. 120189-B (See Model 800B)
Ch. 120190-B (See Model 740B)
Ch. 120191-D (See Model 760D)
Ch. 120192-B (See Model 767A)
Ch. 120192-D (See Model 771D)
Ch. 120192-F (See Model 775A)
Ch. 120193-B (See Model 768A)
Ch. 120193-D (See Model 776A)
Ch. 120194-B (See Model 776A)
Ch. 120195-D (See Model 785K)
Ch. 120196-B (See Model 781A)
Ch. 120197-B (See Model 784E)
Ch. 120197-D (See Model 784G)
Ch. 120198-D (See Model 759F)
Ch. 120199-B (See Model 797C)
Ch. 120200-B (See Model 783B)
Ch. 120201-B (See Model 788B)
Ch. 120202-D (See Model 805B)
Ch. 120203-B (See Model 748C)
Ch. 120204-B (See Model 777B)
Ch. 120205-B (See Model 797C)
Ch. 120206-D (See Model 781E)
Ch. 120207-B (See Model 789B)
Ch. 120208-D (See Model 1001E)
Ch. 120209-D (See Model 770C)
Ch. 120209-F (See Model 810B)
Ch. 120210-D (See Model 766D)
Ch. 120211-D (See Model 784M)
Ch. 120211-F (See Model 793E)
Ch. 120220-D (See Model 1030D)
Ch. 120221-A (See Model 809A)
Ch. 120222-B (See Model 810B)
Ch. 120223-D (See Model 1012F)
Ch. 120225-D (See Model 1002F)
Ch. 120225-F (See Model 1044F)
Ch. 120228-B (See Model 811B)
Ch. 120229-B (See Model 812B)
Ch. 120230-B (See Model 813B)
Ch. 120239-D (See Model 1058D)
Ch. 120243-B (See Model 825B)
Ch. 120250-B (See Model 823B)

FADA
DL21T 200-5
DL21T8 (See Model 215C—Set 200-5)
G-925 89-6
H821T (See Model UH21T—Set 218-1)
H21C (See Model UH21T—Set 228-10)
H21CB (See Model UDL2100T—Set 228-10)
H274T, H276T 247-5
H321T (See Model UDL2100T—Set 228-10)
H421T (See Model UH21T—Set 228-10)
H442C 247-5
H542C 247-5
H521T (See Model UH21T—Set 228-10)
P80 27-9
P82 21-6
P100 27-10
P111 178-6
P130 135-7
R7C15, R7C25 158-3
R-1025 114-4
R-1050 114-4
S4C20 142-8
S4C40 142-8
S4T15 142-8
S4T30 142-8
S6C55 134-7
S6C70 134-7
S6T65 134-7
S7C20, S7C30 (See Model S6C55—Set 134-7)
S7C70 134-7
S7T65 134-7
S9C10 134-7
S20T20 (See Model S6C55—Set 134-7)
S1015 109-4
S1020 109-4
S1030 109-4
S1055, S1055X 134-7
S1060 134-7
S1065 134-7
S1930 74-3
U1700CD 244-4
U1720CD 244-4
U2150C 228-10
UDL2100T 228-10
UH21T 228-10
V21T (See Model 215C—Set 200-5)
V21T8 (See Model 215C—Set 200-5)
V211CD 257-5
V213CD 257-5
V217C (See Model DL21T—Set 200-5)
V219C (See Model 215C—Set 200-5)
V2218M 281-3
V221T, V223T 259-5
V7C42 179-5
V7C52 179-5
V732 177-7
V732C 177-7
V732D 177-7
V732E 177-7
V732F 177-7
V732G 177-7
V732H 177-7
V732I 177-7
V732J 177-7
V732K 177-7
V732L 177-7
V732M 177-7
V732N 177-7
V732O 177-7
V732P 177-7
V732Q 177-7
V732R 177-7
V732S 177-7
V732T 177-7
V732U 177-7
V732V 177-7
V732W 177-7
V732X 177-7
V732Y 177-7
V732Z 177-7
V733 177-7
V733A 177-7
V733B 177-7
V733C 177-7
V733D 177-7
V733E 177-7
V733F 177-7
V733G 177-7
V733H 177-7
V733I 177-7
V733J 177-7
V733K 177-7
V733L 177-7
V733M 177-7
V733N 177-7
V733O 177-7
V733P 177-7
V733Q 177-7
V733R 177-7
V733S 177-7
V733T 177-7
V733U 177-7
V733V 177-7
V733W 177-7
V733X 177-7
V733Y 177-7
V733Z 177-7
V734 177-7
V734A 177-7
V734B 177-7
V734C 177-7
V734D 177-7
V734E 177-7
V734F 177-7
V734G 177-7
V734H 177-7
V734I 177-7
V734J 177-7
V734K 177-7
V734L 177-7
V734M 177-7
V734N 177-7
V734O 177-7
V734P 177-7
V734Q 177-7
V734R 177-7
V734S 177-7
V734T 177-7
V734U 177-7
V734V 177-7
V734W 177-7
V734X 177-7
V734Y 177-7
V734Z 177-7
V735 177-7
V735A 177-7
V735B 177-7
V735C 177-7
V735D 177-7
V735E 177-7
V735F 177-7
V735G 177-7
V735H 177-7
V735I 177-7
V735J 177-7
V735K 177-7
V735L 177-7
V735M 177-7
V735N 177-7
V735O 177-7
V735P 177-7
V735Q 177-7
V735R 177-7
V735S 177-7
V735T 177-7
V735U 177-7
V735V 177-7
V735W 177-7
V735X 177-7
V735Y 177-7
V735Z 177-7
V736 177-7
V736A 177-7
V736B 177-7
V736C 177-7
V736D 177-7
V736E 177-7
V736F 177-7
V736G 177-7
V736H 177-7
V736I 177-7
V736J 177-7
V736K 177-7
V736L 177-7
V736M 177-7
V736N 177-7
V736O 177-7
V736P 177-7
V736Q 177-7
V736R 177-7
V736S 177-7
V736T 177-7
V736U 177-7
V736V 177-7
V736W 177-7
V736X 177-7
V736Y 177-7
V736Z 177

FAIRMONT—GENERAL ELECTRIC

FAIRMONT—Cont.

●231876A-954 (Similar to Chassis) 85-3
 ●231879A-912 (Similar to Chassis) 78-4

FARNSWORTH (Also see Record Changer Listing)

EC-260 7-15
 EK-081, EK-082, EK-083 26-13
 EK-262, EK-263BL, E-263WL 7-5
 EK-264BL, EK-264WL, E-265 7-15
 EK-681 26-13
 ET-060, ET-061, ET-063 6-11
 ET-064, ET-065, ET-066 4-2
 GK-100, GK-102, GK-103, GK-104 23-8
 GK-111, GK-112, GK-114, GK-115 60-11
 GK-140, GK-141, GK-142, GK-143, GK-144 24-18
 GT-050, GT-051, GT-052 35-5
 GT-060, GT-061, GT-064, GT-065 35-6
 K-267, K-669 (See Model EC-260—Set 7-15)

Ch. 150 (See Model ET-060) 7-15
 Ch. 152, 153 (See Model EC-260) Ch. 156, 157 (See Model EK-081) Ch. 158, 159 (See Model ET-064) Ch. 162 (See Model EC-260) Ch. 170 (See Model GK-100) Ch. 193 (See Model EK-081) Ch. 194, 201, 216 (See Model GK-100)

FEDERAL MFG. CO.
 104 (Select-A-Call) 18-17
 135 (Select-A-Call) 11-7

FEDERAL TEL. & RADIO CORP.
 1021 (See Model 1030T—Set B-13) 10301 8-13
 1031, 1032 (See Model 1030T—Set B-13) 8-13
 1040T 23-9
 1040TB (See Model 1040T—Set 23-9) 23-9
 1540T 8-13

●231M539A (Similar to Chassis) 226-11
 ●231M539A (Similar to Chassis) 226-11

FERRAR

C-81-B 17-16
 T-618 15-10
 WR-11 15-10

FIRESTONE (AIR CHIEF)

4-A-2 (Code No. 297-6-LMMU-143) 14-4
 4-A-3 (Code No. 297-6-LMFU-134) 31-13
 4-A-10 (Code No. 297-7-RN228) 28-11
 4-A-11 (Code No. 188-8-4A11) 41-7
 4-A-12 (Code No. 213-8-8270) 41-7
 4-A-15 (Code 177-7-4A15) 36-7
 4-A-17 (Code No. 213-7-7270) 35-7
 4-A-20 (Code 5-5-9000-A) 15-11
 4-A-21 (Code No. 5-5-9001A) 11-19
 4-A-22X (Code No. 5-5-9001B) 11-19
 4-A-23 (5-5-9003-A) 2-29
 4-A-24 (Code 291-6-566) 13-5
 4-A-25 (Code 291-6-572) 33-6
 4-A-26 (Code 307-6-9030-A) 28-12
 4-A-27 23-5
 4-A-31 (Code No. 177-5-4A31) 11-20
 4-A-37 (Code 177-5-4A37) 13-7
 4-A-31 (Code 291-7-576) 52-8
 4-A-42 (Code No. 107-7-4A42) 30-9
 4-A-60 (Code No. 307-8-9047A) 38-6
 4-A-61 (Code No. 332-8-1372T) 48-7
 4-A-62, 4-A-63 67-10
 4-A-64, 4-A-65 68-9
 4-A-66 (Code No. 177-8-4A66) 74-4
 4-A-68 (Code No. 332-8-14363) 53-11
 4-A-69 (Code No. 155-8-85) 61-8
 4-A-70 136-8
 4-A-71 (Code 291-8-628) 59-9
 4-A-78, 4-A-79 117-5
 4-A-85 118-7
 4-A-86 129-6
 4-A-86 (Late) 144-4
 4-A-87 119-7
 4-A-88 132-6
 4-A-89 118-7
 4-A-92 154-4
 4-A-95 144-4
 4-A-96 (See Model 4-A-87—Set 119-7) 119-7
 4-A-97, 4-A-98 147-5
 4-A-101, 4-A-102 181-7
 4-A-108 (Code 297-2-361) 191-8
 4-A-110 215-6
 4-A-112 (See Model 4-A-92—Set 154-4) 154-4
 4-A-113, 4-A-114 224-8
 4-A-115 219-5
 4-A-118 (See Model 4-A-92—Set 154-4) 154-4
 4-A-120 273-6
 4-A-121, 4-A-122 244-5
 4-A-127, 4-A-128 259-7
 4-A-131 279-4
 4-A-133 266-4
 4-A-135, 4-A-136 266-7
 4-A-136, 4-A-137 271-3
 4-B-1 (Code 7-6-PM15) 7-1
 4-B-2 (Code 7-6-PM14) 18-18
 4-B-6 (Code No. 177-7-PM18) 29-8
 4-B-56 133-6
 4-B-57 124-4
 4-B-58 135-8
 4-B-60 153-5
 4-B-61 155-6

FIRESTONE (AIR CHIEF)—Cont.

4-B-62 152-6
 4-B-63 (Similar to Chassis) 173-4
 4-B-67 (Code 120-2-F152) 187-6
 4-B-69 233-6
 4-B-71 222-6
 4-B-72 223-7
 4-B-74 268-7
 4-B-75 267-4
 4-C-3 19-17
 4-C-5 (Code 291-7-574) 33-6
 4-C-6 19-17
 4-C-13 (Code 332-8-140623) 66-9
 4-C-16, 4-C-17 120-6
 4-C-18 110-8
 4-C-19, 4-C-20 170-7
 4-C-21 (Code 120-2-C51-U) 185-7
 4-C-22 246-2
 4-C-24 257-6
 ●13-G-3 86-5
 ●13-G-4 (Code 347-9-249B) 73-5
 ●13-G-5 (Code 291-9-651) 83-3
 ●13-G-33 108-6
 ●13-G-46, 13-G-47 140-5
 ●13-G-51, 13-G-52 (Code 307-1-9202A, AA, B, BA) 193-4
 ●13-G-56 152-7
 ●13-G-57 158-4
 ●13-G-107, 13-G-108 (Code 105-2-70010) 197-6
 ●13-G-109, A (Code 105-2-700100, 105-2-700104) 197-6
 13-G-110 (Code 334-2-MS29A) 180-4
 ●13-G-110A (Code 334-2-MS31CA) (Also see PCB 60—Set 194-1 and PCB 76—Set 217-1) 182-5
 ●13-G-114, A (Code 105-2-8170) (Ch. 817) 198-6
 ●13-G-115, 13-G-116 (Code 334-2-MS31CA) (Also see PCB 60—Set 194-1 and PCB 76—Set 217-1) 182-5
 ●13-G-117 (Code 105-2-8170) (Ch. 817) 198-6
 ●13-G-119, 13-G-120 (Code 334-2-MS31CA) (Also see PCB 60—Set 194-1 and PCB 76—Set 217-1) 182-5
 ●13-G-122 (Code 105-2-700140) 197-6
 ●13-G-124 (Code 105-2-82000) (See Model 13-G-107—Set 197-6) 197-6
 ●13-G-125 (Code 105-2-81700) (See Model 13-G-107—Set 197-6) 197-6
 ●13-G-127 (Code 334-3-MS31D) (See PCB 60—Set 194-1, PCB 76—Set 217-1 and Model 13-G-110A—Set 182-5) 182-5
 ●13-G-128, 13-G-129, 13-G-130 (See Model 13-G-107—Set 197-6) 197-6
 ●13-G-132 230-6
 ●13-G-134 (Code 105-4-82203) 250-9
 ●13-G-134 (Code 105-4-82210) 277-4
 ●13-G-145, 13-G-146 230-6
 ●13-G-147 (Code 105-4-75301) 277-4
 ●13-G-148 (Code 105-4-82204) 277-4
 ●13-G-150 256-9
 ●13-G-153 (See Model 13-G-155—Set 241-8) 241-8
 ●13-G-156 (Code 105-4-81786) 277-4
 ●13-G-161, 13-G-162 (Code 105-4-82209) 277-4
 ●13-G-163 (Code 105-4-82210) 277-4
 ●13-G-165 (Code 280-4-17118) 282-7
 ●13-G-166 (Code 280-4-21119) 282-7
 ●13-G-167 (Code 280-4-21119AGH) 286-5
 ●13-G-168, 13-G-169 (Codes 334-4-AM57A, 334-4-AS57A) 283-5
 ●13-G-172, 13-G-173 (Codes 334-4-AM57A, 334-4-AS57A) 283-5
 ●13-G-174 (Code 334-4-AM51A) 279-5
 ●13-G-178, 13-G-179 (Code 334-4-AM51A) 279-5

FISHER

FM-80 277-5
 50-A 209-6
 50-BC, .CM (50C Series) (Ch. 209) 209-6
 50-CB 262-7
 50-PR 262-8
 50R, 50RT 231-7
 70-A 263-8
 70RT 258-7

FLEETWOOD

●600 209-4
 ●610 248-7
 ●610 243-5
 ●710 246-5

FLUSH WALL

5P 26-14
 5P (Revised) 252-8

FORD

FAC-18805-A 175-10
 FAC-18805-A1 184-7
 FAC-18805-B 167-7
 FAC-18805-C (See Model M4A or Model 3MF) 209-6
 FAD-18805-D 208-6
 FAE-18805-A 215-7
 FDA-18805-A 255-6
 FDA-18805-B1 48-6
 FDA-18805-B-2 250-10
 FDH-18805-A2 289-4
 FDH-18805-B1 286-6
 FDH-18805-B2 281-4
 GF890, E (OA-18805-B) 109-5
 M-1 (OA-18805-A1) 46-4
 M-1A (OA-18805-A1) (See Model M-1—Set 46-4) 46-4
 M-1A-1 (OA-18805-A1) 106-8
 M-2 (1A-18805-A1) 132-7
 M-4 (FAC-18805-A1) 184-7

FORD—Cont.

M-4A (FAC-18805-C) (See Model M-4—Set 184-7) 184-7
 M-4B (FDA-18805-B1) 236-5
 OA-18805-A1 (See Model M-1A or Model M-1A-1) 135-9
 OA-18805-A2 109-5
 OBF (OA-18805-A1) (Serial No. 150,000 and below) (See Model M-1—Set 46-4) 46-4
 OBF (OA-18805-A1) (Serial No. 150,001 and up) (See Model M-1A-1—Set 106-8) 106-8
 OCF751-1 (1A-18805-D) 157-4
 OMF (OA-18805-A2) 135-9
 OF890 (FAC-18805-B) (See Model GF890—Set 109-5) 109-5
 1A-18805-A1 132-7
 1A-18805-A2 131-8
 1A-18805-B (See Model 1CF743—Set 157-5) 157-5
 1A-18805-C 157-4
 1B (1A-18805-A1) (See Model M-2—Set 132-7) 132-7
 1CF743 (1A-18805-B) 133-7
 1CF743-1 (1A-18805-B) 133-7
 1CF751-2 (1A-18805-G) 57-4
 1MF (1A-18805-A2) 131-8
 1SF751-2 (1A-18805-G) (See Model 1CF751-2—Set 157-4) 157-4
 2B (FAC-18805-A1) (See Model M-4—Set 184-7) 184-7
 2CF750 (FAC-18805-B) 167-7
 2MF (FAC-18805-A) 175-10
 3BF (FAD-18805-C) (See Model M-4—Set 184-7) 184-7
 3MF (FAD-18805-C) 206-5
 3MF1 (FAE-18805-A) 215-7
 3SF750 (FAD-18805-D) 208-6
 4BF (See Model M4B—Set 236-5) 236-5
 4MF (FDA-18805-B-2) 250-10
 4SF765 (FDA-18805-A) 255-6
 5BF (FDH-18805-B1) 286-6
 5MF (FDH-18805-B2) 281-4
 5MF8 (FDH-18805-F) 289-4
 6MF080 (51A-18805-A1) (Ch. 6CA1) 10-18
 6MF780 (51A-18805-A1) 62-12
 6MF780-E (51AF-18805) (See Model 6MF780—Set 62-12) 62-12
 8A-18805-A 83-4
 8A-18805-A 44-4
 8A-18805-A3 (See Model 9MF) 46-4
 8A-18805-B (See Model 8MF880—Set 61-9) 61-9
 8A-18805-B1 83-4
 8C-18805-B 47-9
 8MF880 (8A-18805B) 42-12
 8MF881 (8C-18805B) 47-9
 8MF890 (8A-18805B) 47-9
 8MF893 (8A-18805B-1) (8MF983-E (8A-18805) 83-4
 8ZT (8C-18805-B) (See Model 8MF-881—Set 47-9) 47-9
 9BF (8A-18805-A1) (See Model M-1—Set 46-4) 46-4
 9DF (8A-18805-A) (See Model 8072—Set 44-4) 44-4
 9MF (8A-18805-A3) (See Model 8072—Set 44-4) 44-4
 9ZF (8A-18805-B1) (See Model 8MF983—Set 83-4) 83-4
 51A-18805-A1 (See Model 6MF080—Set 10-18 or Model 6MF780—Set 62-12) 62-12
 51A-18805-B2 45-10
 51AF-18805-1 (See Model 6MF780-E) 45-10
 7070 (51A-18805-B2) 45-10
 8072 (8A-18805-A) 44-4

FREED EISEMANN

46 11-8
 ●54, 55, 56, 66 (Ch. 1620C) 113-1A
 717 269-6

GALVIN (See Motorola)

GAMBLE-SKOGMO (See Coronado)

GAROD (Also see Majestic)

4A1, 4A-2 29-9
 4B-1 51-6
 5A-1 22-15
 5A-2 24-5
 4A-3 44-50CH
 5A-4 40-6
 5-AP1-Y 'The Companion' 15-12
 5D, 5D-2 12-12
 5D-3, 5D-3A 22-16
 5D-4, 5D-5 33-7
 5RC-1 36-8
 6A-2 28-13
 6AU-1 5-29
 6BU-1A 'The Senator' 13-18
 6DPS, 6DPS-A 12-13
 ●10T21, 10T22, 10T23, 10T24, 10T25 60-12
 ●10T220, 10T221, 10T222, 10T223 95A-4
 11FP 38-7
 ●11T21, 11T22, 11T23, 11T24, 11T25, 11T26, 11T27A, 60-12
 ●11T220, 11T221, 11T222, 11T223 95A-4
 ●15T26, 15T27 60-12
 ●15T224, 15T225, 15T226, 15T227 95A-4
 ●16CT4, 16CT5 (See Majestic Model 16CT4—Set 133-8) 133-8
 ●19C6, 19C7 (See Majestic Model 19C6—Set 133-8) 133-8
 62B 29-10
 608 48-6
 ●900TV, 910TV 50-7
 ●1000TV, 1010TV 50-7
 ●1042G, 1043G (See Majestic Model 12C4—Set 108-7) 108-7
 ●1042T, 1043T 93A-7
 ●1100TVP, 1110TVP 50-7
 ●1200TVP, 1210TVP 50-7
 ●1244G, 1245G (See Majestic Model 12C4—Set 108-7) 108-7
 ●1244T, 1245T 93A-7

GAROD—Cont.

●1546G, 1547G (See Majestic Model 12C4—Set 108-7) 108-7
 ●1546T, 1547T 93A-7
 ●1548G, 1549G (See Majestic Model 12C4—Set 108-7) 108-7
 ●1671 (98 Series) 97A-3
 ●1671, 1672, 1673, 1674 (See Majestic Model 1671—Set 133-8) 133-8
 ●197A, 1975 (See Majestic Model 197A—Set 133-8) 133-8
 ●2042T, 2043T 93A-7
 ●2546T 93A-7
 ●2549T 93A-7
 ●3912 TVFMP, 3915 TVFMP 95A-6

GARRARD (See Record Changer Listing)

GENERAL (Mutual Buying Syndicate)

●17CG1, 17TW (Similar to Chassis) 149-13
 ●17CG1 (See Model 17CG1—Set 149-13) 149-13

GENERAL ELECTRIC (Also see Record Changer Listing)

A1-200 243-6
 A1-300 238-8
 UHF-103 Tel. UHF Conv. 209-5
 YRB-60-1, YRB-60-2, YRB-60-12 33-8
 ●10C101, 10C102 96-4
 ●10T4, 10T5, 10T6 96-4
 ●12C101, 12C102, 12C105 96-4
 ●12C107, 12C107B, 12C108, 12C-108B, 12C109, 12C109B 125-7
 ●12K1 95A-6
 ●12T1 94-4
 ●12T3, 12T3B, 12T4, 12T4B 125-7
 ●12T7 95A-5
 14 35-8
 ●14C102, 14C103 123-4
 ●14T2, 14T3 123-4
 ●16C103 123-4
 ●16C11, 16C111 123-4
 ●16C113 123-4
 ●16C115, 16C116, 16C117 123-4
 ●16K1, 16K2 161-1A
 ●16T1, 16T2, 16T3, 16T4 123-4
 ●16T5 (See Model 16T4—Set 123-4) 123-4
 ●17C101, 17C102 123-4
 ●17C103, 17C104, 17C105 (Also see PCB 32—Set 158-1) 141-6
 ●17C107, 17C109 (Also see PCB 32—Set 158-1) 141-6
 ●17C110, 17C111 (Early, 'D' and 'W' Versions) 180-5
 ●17C112 (See PCB 32—Set 158-1 and Model 17C103—Set 141-6) 141-6
 ●17C113 166-10
 ●17C114 (See PCB 32—Set 158-1 and Model 17C103—Set 141-6) 141-6
 ●17C115 166-10
 ●17C117 (See Model 17C113—Set 166-10) 166-10
 ●17C125 (See PCB 64—Set 201-1 and Model 21C201—Set 194-2) 194-2
 ●17C125-UHF (For TV Ch. see PCB 64—Set 201-1 and Model 21C201—Set 194-2, for UHF Conv. See Model UHF-103—Set 209-5) 209-5
 ●17C127 (See PCB 97—Set 242-1 and Model 21C115—Set 229-7) 229-7
 ●17T1, 17T2, 17T3 (Also see PCB 32—Set 158-1) 141-6
 ●17T4, 17T5, 17T6 (See PCB 32—Set 158-1 and Model 17T103—Set 141-6) 141-6
 ●17T7 (See Model 17C113—Set 166-10) 166-10
 ●17T10 196-3
 ●17T10-UHF (For TV Ch. see Model 17T10—Set 196-3, for UHF Conv. See Model UHF-103—Set 209-5) 209-5
 ●17T11 (See Model 17T10—Set 196-3) 196-3
 ●17T11-UHF (For TV Ch. see Model 17T10—Set 196-3, for UHF Conv. See Model UHF-103—Set 209-5) 209-5
 ●17T12 (See Model 17T10—Set 196-3) 196-3
 ●17T12-UHF (For TV Ch. see Model 17T10—Set 196-3, for UHF Conv. See Model UHF-103—Set 209-5) 209-5
 ●17T15, 17T17 (See PCB 97—Set 242-1 and Model 21C11—Set 229-7) 229-7
 ●17T20 295-6
 ●19C101 69A-6
 ●20C105, 20C106 176-3
 ●20C107 (See PCB 64—Set 201-1 and Model 21C201—Set 194-2) 194-2
 ●20C107-UHF (For TV Ch. see PCB 64—Set 201-1 and Model 21C201—Set 194-2, for UHF Conv. See Model UHF-103—Set 209-5) 209-5
 ●20C150, 20C151 153-6
 ●20T2 176-3
 ●21C103, 21C104 265-6
 ●21C105 (See Model 17T20—Set 265-6) 265-6
 ●21C114 (See PCB 97—Set 242-1 and Model 21C115—Set 229-7) 229-7
 ●21C115 (Also see PCB 97—Set 242-1) 229-7
 ●21C116, 21C117 (See PCB 97—Set 242-1 and Model 21C115—Set 229-7) 229-7
 ●21C210, 21C211 (See PCB 97—Set 242-1 and Model 21C115—Set 229-7) 229-7
 ●21C200 176-3
 ●21C201 (Also see PCB 64—Set 201-1) 194-2
 ●21C201-UHF (For TV Ch. see PCB 64—Set 201-1 and Model 21C201—Set 194-2, for UHF Conv. See Model UHF-103—Set 209-5) 209-5
 ●21C202 (Also see PCB 64—Set 201-1) 194-2
 ●21C202-UHF (For TV Ch. see PCB 64—Set 201-1 and Model 21C201—Set 194-2, for UHF Conv. See Model UHF-103—Set 209-5) 209-5
 ●21C204 (Also see PCB 64—Set 201-1) 194-2

GENERAL ELECTRIC—Cont.

●21C206 (Also see PCB 64—Set 201-1) 194-2
 ●21C206-UHF (For TV Ch. see PCB 64—Set 201-1 and Model 21C206—Set 194-2, for UHF Conv. See Model UHF-103—Set 209-5) 209-5
 ●21C208 (Also see PCB 64—Set 201-1) 194-2
 ●21C208-UHF (For TV Ch. see PCB 64—Set 201-1 and Model 21C208—Set 194-2, for UHF Conv. See Model UHF-103—Set 209-5) 209-5
 ●21C208U (See PCB 64—Set 201-1 and Model 21C208—Set 194-2) 194-2
 ●21C210-UHF (For TV Ch. see PCB 64—Set 201-1 and Model 21C208—Set 194-2, for UHF Conv. See Model UHF-103—Set 209-5) 209-5
 ●21C210 (See PCB 64—Set 201-1 and Model 21C201—Set 194-2) 194-2
 ●21C210-UHF (For TV Ch. see PCB 64—Set 201-1 and Model 21C201—Set 194-2, for UHF Conv. See Model UHF-103—Set 209-5) 209-5
 ●21C214 (Also see PCB 64—Set 201-1) 194-2
 ●21C214-UHF (For TV Ch. see PCB 64—Set 201-1 and Model 21C214—Set 194-2, for UHF Conv. See Model UHF-103—Set 209-5) 209-5
 ●21C225, 21C226, 21C227, 21C228, 21C229, 21C230, 21C231, 21C232, 21C233 237-7
 ●21C242, UHF, 21C243, UHF, 21C244, UHF 264-7
 ●21C347, 21C348, 21C349, 21C350, 21C351 ('J' Line) 275-8
 ●21T1 (Also see PCB 64—Set 201-1) 194-2
 ●21T1-UHF (For TV Ch. see PCB 64—Set 201-1 and Model 21T1—Set 194-2, for UHF Conv. See Model UHF-103—Set 209-5) 209-5
 ●21T1U (See PCB 64—Set 201-1 and Model 21T1—Set 194-2) 194-2
 ●21T1U-UHF (For TV Ch. see PCB 64—Set 201-1 and Model 21T1—Set 194-2, for UHF Conv. See Model UHF-103—Set 209-5) 209-5
 ●21T2 196-3
 ●21T3 (See Model 21T1—Set 194-2) 194-2
 ●21T3-UHF (For TV Ch. see PCB 64—Set 201-1 and Model 21T3—Set 194-2, for UHF Conv. See Model UHF-103—Set 209-5) 209-5
 ●21T4, 21T5 184-8
 ●21T6-UHF (For TV Ch. see PCB 64—Set 201-1 and Model 21T1—Set 194-2, for UHF Conv. See Model UHF-103—Set 209-5) 209-5
 ●21T7, 21T8 225-10
 ●21T11, 21T12 (See PCB 97—Set 242-1 and Model 21C115—Set 229-7) 229-7
 ●21T14 (Also see PCB 97—Set 242-1) 229-7
 ●21T20, 21T21 229-7
 ●21T22, 21T23, 21T24, 21T25 265-6
 ●21T26, UHF, 21T27, UHF 264-7
 ●21T30, 21T31 ('J' Line) 275-8
 ●21T34 (See Model 17T20—Set 265-6) 265-6
 ●24C101 152-8
 41, 42, 43, 44, 45 32-8
 50 7-16
 60, 62 36-9
 64, 65 98-4
 100, 101 6-13
 102, 102W 41-

HOFFMAN-LEAR

HOFFMAN-Cont.
• 21M700TU, U (Ch. 196M, T) [See PCB 124-Set 280-1 and Model 21M700-Set 905]
• 21M715 (Ch. 211T) [See Model 21B122-Set 194-4]
• 21M718, U (Ch. 300-21) [Also see PCB 108-Set 256-1]
• 21M721, U (Ch. 400-21)
• 21M728L, LU (Ch. 408-21)
• 21M728N, NU (Ch. 408-21N)
• 21M728U (Ch. 408-21)
• 21M900 (Ch. 192) [TV Ch. only]
• 21M903 (Ch. 213, M)
• 21M906 (Ch. 199, M, T and Radio Ch. 182)
• 21M910 (Ch. 375-21) [See PCB 108-Set 256-1 and Model 21B144-Set 236-6]
• 21P108 (Ch. 191, B)
• 21P117 (Ch. 195, M)
• 21P123 (Ch. 211)
• 21P145, U (Ch. 300-21) [Also see PCB 108-Set 256-1]
• 21P148, U (Ch. 401-21)
• 21P168, U (Ch. 302)
• 21P180, L, LU, N, NU, U (Ch. 207-21, L)
• 21P307B (Ch. 211, M)
• 21P310 (Ch. 196M, T) [See PCB 124-Set 280-1 and Model 21P310-Set 195-8]
• 21P322, U (Ch. 405-21)
• 21P338P, U (Ch. 302)
• 21P353, U (Ch. 408-21)
• 21P353L, LU (Ch. 408-21)
• 21P353N, NU (Ch. 408-21N)
• 21P505 (Ch. 191, B)
• 21P508 (Ch. 211, M)
• 21P511 (Ch. 196) [See Model 21B116-Set 195-8]
• 21P702 (Ch. 191, B)
• 21P702 (Ch. 196M, T)
• 21P717 (Ch. 211T) [See Model 21B122-Set 194-4]
• 21P720, U (Ch. 300-21) [Also see PCB 108-Set 256-1]
• 21P724, U (Ch. 400-21)
• 21P730, U (Ch. 408-21)
• 21P731, LU (Ch. 408-21)
• 21P731N, NU (Ch. 408-21N)
• 21P902 (Ch. 192) [TV Ch. only]
• 21P905 (Ch. 213, M)
• 21P908 (Ch. 199, M, T and Radio Ch. 182)
• 21P912 (Ch. 375-21) [Also see PCB 108-Set 256-1]
• 21U208, U (Ch. 408-21B)
• 21U208N, NU (Ch. 408-21N)
• 24B151, U (Ch. 402-24)
• 24B707 (Ch. 187, B, C)
• 24B726, U (Ch. 402-24)
• 24B732, U (Ch. 410-24)
• 24M150, U (Ch. 402-24)
• 24M354, U (Ch. 410-24)
• 24M708 (Ch. 187, B, C)
• 24M725, U (Ch. 403-24)
• 24P152, U (Ch. 402-24)
• 24P310, U (Ch. 410-24)
• 24P727, U (Ch. 403-24)
• 24P733, U (Ch. 410-24)
• 24U-211, U (Ch. 410-24B)
• 27M709 (Ch. 197)
• 600 (Ch. 154)
• 601 (Ch. 155)
• 610 (Ch. 140)
• 612 (Ch. 142)
• 613 (Ch. 149)
• 630, 631 (Ch. 170)
• 632, 633, 634, 635 (Ch. 171)
• 634A, 635A (Ch. 173)
• 636, 637 (Ch. 183)
• 636B, 637B (Ch. 183 B)
• 639, 639 (Ch. 180)
• 826, 827, 828 (Ch. 143)
• 830, 831 (Ch. 151)
• 832 (Ch. 151) [See Model 830-Set 97A-6]
• 836, 837 (Ch. 153)
• 840 (Ch. 153)
• 846 (Ch. 151) [See Model 830-Set 97A-6]
• 847, 848, 849 (Ch. 156)
• 860, 861, 862 (Ch. 157)
• 866, A, 867, A, 868, A (Ch. 173)
• 870, 871, 872 (Ch. 170)
• 876, 877, 878 (Ch. 171)
• 876A, 877A, 878A (Ch. 173)
• 880, 881, 882, 883, 884, 885, 886, 887 (Ch. 183)
• 886B, 887B (Ch. 183B)
• 890, 891, 892 (Ch. 175)
• 893, 894, 895, 896, 897 (Ch. 185)
• 896B, 897B (Ch. 183T)
• 902 (Ch. 141, Radio Ch. 137)
• 912, 913 (Ch. 147)
• 914, 915 (Ch. 150)
• 917, 918 (Ch. 152)
• 920 (Ch. 152) [See Model 830-Set 97A-6]
• 946, 947, 948 (Ch. 164)
• 950, 951, 952 (Ch. 172)
• 951A, 952A (Ch. 174)
• 953, 954, 955 (Ch. 184)
• 960, 961, 962 (Ch. 176)
• 963, 964, 965 (Ch. 186)
• Ch. 102 [See Model A400]
• Ch. 103 [See Model A201]
• Ch. 107 [See Model A500]
• Ch. 108ST [See Model A501]
• Ch. 110S [See Model A700]
• Ch. 114 [See Model B1000]
• Ch. 119 [See Model A202]
• Ch. 123 [See Model C504]

HOFFMAN-Cont.
Ch. 137 [See Model 902]
Ch. 140 [See Model 610]
Ch. 141 [See Model 902]
Ch. 142 [See Model 612]
Ch. 143 [See Model 826]
Ch. 147 [See Model 826]
Ch. 149 [See Model 613]
Ch. 150 [See Model 914]
Ch. 151 [See Model 830]
Ch. 152 [See Model 917]
Ch. 142 [See Model 836]
Ch. 154 [See Model 600]
Ch. 155 [See Model 601]
Ch. 156 [See Model 847]
Ch. 157 [See Model 860]
Ch. 164 [See Model 946]
Ch. 170, 171 [See Model 630]
Ch. 172 [See Model 950]
Ch. 173 [See Model 634A]
Ch. 174 [See Model 950A]
Ch. 175 [See Model 890]
Ch. 176 [See Model 960]
Ch. 180, 181 [See Model 21M907]
Ch. 183 [See Model 636]
Ch. 183B, 183M, 183T [See Model 636B]
Ch. 186 [See Model 963]
Ch. 187, B, C [See Model 24B707]
Ch. 191, B, C [See Model 21B104]
Ch. 191, B, C [See Model 21B107]
Ch. 192 [See Model 21B901]
Ch. 194 [See Model 20B102F]
Ch. 196, M [See Model 21B116]
Ch. 196T [See Model 21B701]
Ch. 197 [See Model 21M909]
Ch. 199 [See Model 21B907]
Ch. 200 [See Model 7B110B]
Ch. 201 [See Model 21M305]
Ch. 202 [See Model 7B113]
Ch. 210, M [See Model 7M109B]
Ch. 211, M [See Model 21B122]
Ch. 211T [See Model 21B315]
Ch. 212, M [See Model 7B113B]
Ch. 213, M [See Model 21B904]
Ch. 300-17 [See Model 7B141, U]
Ch. 300-21 [See Model 21B144, U]
Ch. 400, B [See Model 7B157]
Ch. 301-21 [See Model 21B154]
Ch. 301X-21 [See Model 21B164X]
Ch. 302 [See Model 21B167]
Ch. 375-21 [See Model 21B911]
Ch. 400-21 [See Model 21B321]
Ch. 401, B [See Model 21B147]
Ch. 402-24 [See Model 24B151]
Ch. 403-24 [See Model 24B726]
Ch. 405-21 [See Model 21B331]
Ch. 406-21 [See Model 21B161]
Ch. 407-21, L, N [See Model 21B179]
Ch. 408-21, B, L, N [See Model 21B352]
Ch. 410-24, B [See Model 24B732]
HOWARD
472AC, 472AF, 472C, 472F 31-14
474 31-14
• 475TV Photofac Servicer 84
481B, 481C, 481M 67-11
482, 482A 48-12
901A, E, H, I, M, W [See Model 901A Series-Set 1-8]
901A Series 1-8
901AP 10-21
906, 906C 17-18
909M 25-15
920 5-7
HUDSON (Auto Radio)
DB47 (Fact. No. 6MH089) 25-16
DB84B (Fact. No. 6MH089) 39-9
225908 (Early) 149-6
225908 (Late) (Ch. 749-1) 167-11
229403 (Ch. 749-2) 167-11
236476 (SH759) 215-8
236486 (SH758) 214-4
238060 (SH758) 214-4
HUDSON (Dept. Stores)
• 30T14A-056 (Similar to Chassis) 119-3
• 38T12A-058 (Similar to Chassis) 109-1
• 317T3 (Similar to Chassis) 72-4
• 318T4 (Similar to Chassis) 85-3
• 318T45 (Similar to Chassis) 85-3
• 318T4-872 (Similar to Chassis) 85-3
• 318T6A (Similar to Chassis) 85-3
• 318T6A-950 (Similar to Chassis) 5007
• 318T9A-900 (Similar to Chassis) 78-4
• 321M531C-A (Similar to Chassis) 182-5
• 321M539A (Similar to Chassis) 226-11
• 518T6A (Similar to Chassis) 85-3
• 518T9A-918 (Similar to Chassis) 78-4
• 518T10A-916 (Similar to Chassis) 78-4
• 2318T6A-954 (Similar to Chassis) 85-3
• 2318T9A-912 (Similar to Chassis) 78-4
• 2321M539A (Similar to Chassis) 226-11
HUDSON ELECTRONICS
RPM-71 186-6
3W 191-11
309B 194-5
310R 190-5
312H 194-5
324H 198-9
332H 123-6
347BL 121-8
350-6 126-6
374H 188-7
388 191-12
HYDE PARK
• AR14 169-8
• AR14 169-8
• MST12, MST14 168-9
• 14TR, 16TR 168-9
• 17CD (1st Prod.) 168-9
• 17CD (2nd Prod.) 169-8

HYDE PARK-Cont.
• 17CCR (1st Prod.) 168-9
• 17CCR (2nd Prod.) 169-8
• 17ROG (1st Prod.) 168-9
• 17ROG (2nd Prod.) 168-9
• 20CD (1st Prod.) 168-9
• 20CD (2nd Prod.) 169-8
• 20TR 168-9
• 112X 168-9
• 203D (1st Prod.) 168-9
• 203D (2nd Prod.) 168-9
• 812 168-9
• 819 168-9
• 1000, 1001 168-9
• 3163CR 168-9
• 8163CR 168-9
• 8193CR 168-9
INDUSTRIAL ELECTRONIC CORP. (See Simplon)
INDUSTRIAL TELEVISION (Also see Century)
• IT-40R, IT-42R (Ch. IT-26R, IT-35R, IT-39R, IT-46R) 99A-7
• 721, 821, 921, 1021 (Ch. IT-21R) 97A-8
INTERNATIONAL ELECTRONICS (See Recorder Listing)
JACKSON
DP-51 156-7
JP-20 173-7
JP-30 153-7
JP-50 155-9
JP-200 171-6
JP-300 174-7
JP-400 171-6
• 10C, 10T 132-8
• 12C, 12T 132-8
• 14C, 14T 132-8
• 16C, 16T 132-8
• 17X, 17XT [See Model 10C-Set 132-8]
• 20XC, 20XT [See Model 10C-Set 132-8]
150 130-8
153 [See Model 150-Set 130-8]
214A, 217A, B, C, 220A, B, 221A, B 171-7
254 173-8
255 179-7
312 132-8
314 132-8
350 131-9
412 132-8
416 132-8
• 1400T [See Model 10C-Set 132-8]
• 1700, 1700T [See Model 10C-Set 132-8]
• 2000C [See Model 10C-Set 132-8]
5000, 5050 88-5
5200, 5250 88-5
5600, 5650 88-5
Ch. 114H, 117H 162-7
Ch. 120H 162-7
Ch. 127, B, D 226-3
Ch. 321, B, D 226-3
JEFFERSON-TRAVIS
MR-28 10-22
MR-3 17-19
JEWEL
• 170C, 1779, 177W 187-7
• 17C, 2119 187-7
• 17C, 2119 23-11
300A, 300B 35-12
500A, B, C, 501A, B, C, 502A, B, C, 503A, B, C, 504A, B, C, 505A, B, C 15-4
505 "Pin-Up" 18-21
801 (Trixie) 45-14
814 51-10
815 99-8
910 99-8
915 99-8
920A 55-10
921 [See Model 920-Set 55-10]
935, 936 [See Model 920-Set 55-10]
949 105-5
950 98-5
955 144-6
956 97-8
960U, 961 [See Model 960-Set 97-8]
985 99-8
5007 183-7
5010 111-7
5020 136-10
5020U [See Model 5020-Set 136-10]
5040 160-5
5050 128-7
5057U 109-7
5100, E, U 159-7
5125U 217-7
5200 194-6
5205 196-4
5250 206-7
5310 225-12
KAISER-FRAZER
100170 128-8
100205 139-6
100330 [See Model 100170-Set 128-8]
200001 35-13
200002 56-13
KAPPLER
102T 54-10
KARADIO
M80B 233-3
80C 66-10
1275, 1275A 85-7
1276 115-4
KAYE-HALBERT
• C-024 (Ch. 253) (For TV Ch. only See PCB 63-Set 197-1 and Model 012-Set 146-8)
• 012 (Ch. 243) 169-9
• 014 (Ch. 253) [Also see PCB 63-Set 197-1]
• 024 (Ch. 253) [Also see PCB 63-Set 197-1]
• 17C (2nd Prod.) 169-9

KAYE-HALBERT-Cont.
• 033, 034, 035, 036, 037 (Ch. 242) 139-7
• 044, 045, 046 (Ch. 253) [Also see PCB 63-Set 197-1]
• 074, 075, 077 (Ch. 253) [Also see PCB 63-Set 197-1]
• 104, 114 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
• 104 (Ch. 243) [See Model 012-Set 169-9]
• 114 (Ch. 243) [See Model 012-Set 169-9]
• 114DX (Ch. 253DX) [Also see PCB 45-Set 179-1]
• 122 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
• 122 (Ch. 243) [See Model 012-Set 169-9]
• 124 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
• 124 (Ch. 243) [See Model 012-Set 169-9]
• 138 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
• 138 (Ch. 243) [See Model 012-Set 169-9]
• 144, 145, 146 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
• 144, 145, 146 (Ch. 243) [See Model 012-Set 169-9]
• 146 (Ch. 253) [See Model 014-Set 146-8]
• 146 (Ch. 253DX) [See PCB 45-Set 179-1 and Model 114DX-Set 170-9]
• 154, 164 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
• 154 (Ch. 243) [See Model 012-Set 169-9]
• 164 (Ch. 243) [See Model 012-Set 169-9]
• 174 (Ch. 243) [See Model 012-Set 169-9]
• 231, 232, 233, 234, 235, 236, 237, 238, 239, 240, 241 (Ch. 231, 242) 139-7
• 314 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
• 314 (Ch. 253DX) [See PCB 45-Set 179-1 and Model 114DX-Set 170-9]
• 322 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
• 322 (Ch. 253DX) [See PCB 45-Set 179-1 and Model 114DX-Set 170-9]
• 324 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
• 324 (Ch. 253DX) [See PCB 45-Set 179-1 and Model 114DX-Set 170-9]
• 324 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
• 338 (Ch. 253DX) [See PCB 45-Set 179-1 and Model 114DX-Set 170-9]
• 344 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
• 344 (Ch. 253DX) [See PCB 45-Set 179-1 and Model 114DX-Set 170-9]
• 354 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
• 354 (Ch. 253DX) [See PCB 45-Set 179-1 and Model 114DX-Set 170-9]
• 356 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
• 356 (Ch. 253DX) [See PCB 45-Set 179-1 and Model 114DX-Set 170-9]
• 385 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
• 385 (Ch. 253DX) [See PCB 45-Set 179-1 and Model 114DX-Set 170-9]
• 394, 395, 396 (Ch. 263) [See Ch. 263-Set 217-8]
• 424, 425, 426 (Ch. 253) [Also see PCB 63-Set 197-1]
• 425, 426 (Ch. 253DX) [See PCB 45-Set 179-1 and Model 114DX-Set 170-9]
• 426 (Ch. F-243) [See PCB 96-Set 241-1 and Model 012-Set 169-9]
• 426 (Ch. 243) [See Model 012-Set 169-9]
• 428 (Ch. 253DX) [See PCB 45-Set 179-1 and Model 114DX-Set 170-9]
• 714 (Ch. 253) [Also see PCB 63-Set 197-1]
• 724 (Ch. 253) [Also see PCB 63-Set 197-1]
• 731, 733 (Ch. 231, 242) 139-7
• 734, 735, 736, 737 (Ch. 242) 139-7
• 744, 745 (Ch. 253) [Also see PCB 63-Set 197-1]
• 777 (Ch. 253) [Also see PCB 63-Set 197-1]
• 914 (Ch. 253) [Also see PCB 63-Set 197-1]
• 924 (Ch. 253) [See PCB 63-Set 197-1 and Model 014-Set 146-8]
Ch. F-243 [See Model 104]
Ch. 241 [See Model 231]
Ch. 242 [See Model 033]
Ch. 243 [See Model 012]
Ch. 253 [See Model 014]
Ch. 253DX [See Model 114DX]
• Ch. 263 217-8

KAY MUSICAL INSTRUMENT CO.
77 42-13
KEENEY (J. H.) (See Croydon)
KITCHENAIRE
5 Tube Radio 6-14
KNIGHT (Also see Recorder Listing)
SX8L727 244-6
SX10L722 [See Model 722-Set 240-4]
SK11L719 246-7
SK14L721 252-9
SX19L720 248-8
4G-450 40-9
4G-420 88-6
5A150, 5A152, 5A154 12-17
5A-190 14-15
5B-150 20-15
5B-175, 5B-176 20-16
5B-185 22-17
5C-290 30-13
5D-250, 5D-251 55-11
5D-355 97-11
5E-250, 5E-251 (Similar to Chassis) 36-25
5E-455 (Similar to Chassis) 53-23
5F-525, 5F-526 53-13
5F-565 55-12
5G-563 (Similar to Chassis) 97-11
5H-570 143-10
5H-571 [See Model 5H-570-Set 143-10]
5H-605 131-10
5H-607, 5H-608 (Similar to Chassis) 97-15
5H-678, 5H-679 (Similar to Chassis) 109-7
5H-700 123-7
5J-705 174-8
5K715 215-9
6A-122 9-19
6A-127 16-19
6A-195 16-19
6B-122 [See Model 6A-122-Set 9-18]
6B-127 [See Model 6A-127-Set 9-19]
6C-225 30-14
6D-225, 6D-226 [See Model 6C-225-Set 30-14]
6D-235 54-11
6E-360 39-10
6G-400 [See Model 449-Set 83-9]
6H-580 217-9
6K718 27-14
7B-220 27-14
7D-405 39-11
8B-210 20-17
8C-340 20-17
8G-300, 8G-201 128-9
• 9V-101 78-8
10B-249 42-14
11C-300 29-12
12H-610 176-5
14F-490, 14F-495, 14F-496 63-12
15H-609 [See Model 5118-Set 125-9]
19F492, 19F497, 19F498 58-11
20H611 164-4
935X321 288-5
935X321 255-7
93-017 31-15
93-024 32-13
93-103 31-16
93-146 26-15
93-155 37-10
93-191 38-8
93-320 74-5
93-330 99-9
93-350 76-13
93-360 79-9
93-370 75-10
93-380 90-8
93-431 167-12
94S445 287-10
94S728 289-5
95-279 160-6
96-326 137-5
96-354 (Similar to Chassis) 139-15
97-870 78-9
449 83-5
5118 125-9
LAFAYETTE
FA15W, FA15Y 15-15
J62, J62C 16-21
MC10B, MC10Y 14-16
MC11 28-18
MC12 27-15
MC13 15-16
MC16 21-16
P564 (Similar to Chassis) 3B-5
IN434, IN435, IN436 (Similar to Chassis) 98-5
IN437 (Similar to Chassis) 121-2
IN549 (Similar to Chassis) 38-5
IN551 (Similar to Chassis) 38-6
IN554, IN555 (Similar to Chassis) 55-10
IN556, IN557 (Similar to Chassis) 109-7
IN559 (Similar to Chassis) 90-7
IN560 (Similar to Chassis) 109-7
IN561, IN562 (Similar to Chassis) 97-8
IN819 (Similar to Chassis) 69-7
• IP184 (Similar to Chassis) 149-13
• IP185, IP186 (Similar to Chassis) 149-13
• 17B4M1 (Similar to Chassis) 149-13
• 20CP (Similar to Chassis) 149-13
• 27B4M1 (Similar to Chassis) 149-13
LAMCO
1000 16-20
LEAK
TL/12 166-12
RC/PA/U 166-12
LEAR (See Record Changer Listing)

NOTE: PCB Denotes Production Change Bulletin. Production Change Bulletin Nos. 1 Through 63 Are All Contained in Set No. A-200. Production Change Bulletin Nos. 64 Through 104 Are All Contained in Set No. A-250. • Denotes Television Receiver.

LEARADIO

RM-402C (Learnovian) 42-15
561, 562, 563, 564, 565, 566, 567, 568 9-20
1281-PC (Ch. 78) 49-11
6610PC, 6611PC, 6612PC 9-21
6614, 6615, 6616, 6619, 3-18
6617PC 16-22
Chassis R-971 51-11

LEE (See Royal)

LEE TONE
AP-100 16-23

LEWYTT
615A 11-13
711 42-16

LEXINGTON
6545 13-20

LIBERTY
A6K, A6P, 6K 20-18
507A 20-19

LINCOLN (Auto Radio)

FAA-18805 167-7
FAG-18805-A 214-5
FDD-18805-A, B 246-8
GL892 (OL-18805-A) [See PCB 105
—Set 252-1 and Ford Model
GF890 (OA-18805-B) —Set
109-]
1CH748 (1H-18805) [See Ford Model
1C743—Set 133-7]
1CH748-1 (1H-18805) 158-5
1H-18805 (See Model 1CH748 or
1CH748-1)
2CH757 (FAA-18805-A) 167-7
3SH756 (FAG-18805-A) 214-5
4SH764 (FDD-18805-A), 4SH766
(FDD-18805-B) 246-8
5EH-18805-A 66-11
5EH-18805-B 66-11
7M10801 (5EH-18805-A), 7M10802
(5EH-18805-B) 66-11
8H-18805 83-4
8H-18805-A (See Model 8M1882Z—
Set 44-7 or 8M1985Z—Set 83-4)
8L-18805-A (See Model 8M1882Z—
Set 44-7 or 8M1985Z—Set 83-4)
8L-18805-B 83-4
8M1882 (8L-18805-A), 8M1882Z
(8H-18805-A) (Ch. 8E82) 44-7
8M1985 (8L-18805-A), 8M1985E
(8L-18805-B), 8M1985Z (8H-
18805-A), 8M1985ZE (8H-18805-
B) 83-4

LINCOLN

S13L-B 2-10

LINCOLN (Allied Radio Corp.)

5A-110 5-34

LINEX CORP. (See Swank)

LIPAN (See Supreme)

LULLABY (See Mitchell)

LYMAN

CM10, CM20 44-8

LYRIC (Also see Rauland)

546T, 546TY, 546TW 7-17

MAGIC TONE

500, 501 5-40
504 (Bottle Receiver) 22-18
508 (Keg Radio) 52-10
510 900 38-9

MAGNAVOX

CP251M (Chassis AMP-128A, B,
AMP-129) 254-7
252M (Chassis CR700 and AMP132)
260-9

• 104 Series (Ch. CT301 thru CT314)
161-4

• 108, 108A Series 239-6

• 108B Series 240-5

• 250 Series 278-5

• 300 Series 263-9

• 300 Series 287-11

Chassis AMP-101A, AMP-101B 43-12

Chassis AMP-108A, AMP-108B 41-10

Chassis AMP-111A, B, C 68-10

Chassis AMP-128A, B 254-7

Chassis AMP-129 254-7

Chassis AMP-131A, B 249-9

Chassis AMP132 260-9

Chassis AMP-135 288-6

• Chassis CMU401AA, CMU402AA,
CMU403AA, CMU404AA,
CMU405AA, CMU406AA,
CMU407AA, 108, 108A Series)
239-6

• Chassis CMU410AA, (108, 108A
Series) 239-6

• Chassis CMU413AA, (108, 108A
Series) 239-6

• Chassis CMU418AA, CMU419AA,
CMU420AA (108, 108A Series)
239-6

• Chassis CMU401BB, CMU402BB,
CMU403BB, CMU404BB,
CMU405BB, CMU406BB,
CMU407BB (108B Series)
240-5

• Chassis CMU410BB (108B Series)
240-5

• Chassis CMU413BB (108B Series)
240-5

• Chassis CMU418BB, CMU419BB,
CMU420BB (108B Series)
240-5

• Chassis CMU427CE (300 Series)
287-11

• Chassis CMU435AA, CMU436AA
(Series 250) 278-5

• Chassis CMU422BC (300 Series)
263-9

• Chassis CMU426CE (300 Series)
287-11

CP251M (Chassis AMP-128A, B,
AMP-129) 254-7

MAGNAVOX—Cont.

Chassis CR-188 (1558 Regency Sym-
phony) 18-22
Chassis CR190A, CR190B 41-11
Chassis CR-192A, CR-192B 41-11
Chassis CR-197C 37-11
Chassis CR-198A, B, C (Hepple-
white, Modern Symphony) 17-20
Chassis CR-199 63-13
Chassis CR-200A, B, C, D, E, F,
G 44-9
Chassis CR-207A, B, C, D 41-12
Chassis CR-208A, CR-208B 43-13
Chassis CR-210A, CR-210B 52-11
Chassis CR-211A, B 68-10
Chassis CR300AA-1 268-9
Chassis CR700 260-9
Chassis CR-702A, B (260M Series)
271-6

• Chassis CT-214, CT-218 62-13

• Chassis CT-219, CT-220 82-7

• Chassis CT-221 62-13

• Chassis CT-222 82-7

• Chassis CT-224 97A-8

• Chassis CT-232 93A-9

• Chassis CT-235 93A-9

• Chassis CT-236 93A-9

• Chassis CT-237, CT-238 (See Set
95A-9 and Ch. CT219—Set 82-7)

• Chassis CT239 93A-9

• Chassis CT244, CT245, CT246
93A-9

• Chassis CT250, CT251 135-1A

• Chassis CT252, CT253 95A-9

• Chassis CT257, CT258, CT259,
CT260 119-1A

• Chassis CT262, CT263, CT264,
CT265 155-10

• Chassis CT266, CT267, CT269
131-1A

• Chassis CT-270, CT-271, CT-272,
CT-273, CT-274, CT-275, CT-276,
CT-277, CT-278, CT-279, CT-280,
CT-281, CT-282 148-8

• Chassis CT283 155-10

• Chassis CT284, CT285 131-1A

• Chassis CT286 155-10

• Chassis CT287, CT288 131-1A

• Chassis CT289 155-10

• Chassis CT290 131-1A

• Chassis CT291, CT293 155-10

• Chassis CT294, CT295 131-1A

• Chassis CT297 155-10

• Chassis CT301 thru CT314 161-4

• Chassis CT331 thru CT349 (105
Series) 168-10

• Chassis CT350 thru 357 (105 Series)
(See Ch. CT331—Set 168-10)

• Chassis CT358 (107 Series) 226-4

Chassis CT358AA, AB, BA, BB, CB,
DC (107 Series) (See Ch. CT358—
Set 226-4)

• Chassis CT359AA, AB, BA, BB, CB
(107 Series) (See Ch. CT358—Set
226-4)

• Chassis CT362, CT363 (105L, M
Series) 205-6

• Chassis CT372, CT373 (105L, M, N
Series) 205-6

• Chassis CT374 (105N Series)
205-6

• Chassis CT385AA, AB, BA, BB, CB
(107 Series) (See Ch. CT358—
Set 226-4)

• Chassis CT385CB, DC (107 Series)
(See Ch. CT358—Set 226-4)

• Chassis CT386AA, AB, BA, BB, CB
(107 Series) (See Ch. CT358—
Set 226-4)

• Chassis CT401AA, CT402AA,
CT403AA, CT404AA, CT405AA,
CT406AA, CT407AA (108, 108B
Series) 239-6

• Chassis CT410AA (108, 108B Series)
239-6

• Chassis CT418AA, CT419AA,
CT420AA (108, 108A Series)
239-6

• Chassis CT401BB, CT402BB,
CT403BB, CT404BB, CT405BB,
CT406BB, CT407BB (108B Se-
ries) 240-5

• Chassis CT410BB (108B Series)
240-5

• Chassis CT413BB (108B Series)
240-5

• Chassis CT418BB, CT419BB,
CT420BB (108B Series) 240-5

• Chassis CT427CE (300 Series)
287-11

• Chassis CT435AA, CT436AA (Se-
ries 250) 278-5

• Chassis CT422BC (300 Series)
263-9

• Chassis CTD426CE (300 Series)
287-11

• Chassis CU401AA, CU402AA,
CU403AA, CU404AA, CU405AA,
CU406AA, CU407AA (108, 108A
Series) 239-6

• Chassis CU410AA (108, 108A Se-
ries) 239-6

• Chassis CU413AA (108, 108A Se-
ries) 239-6

• Chassis CU418AA, CU419AA,
CU420AA (108, 108A Series)
239-6

• Chassis CU401BB, CU402BB,
CUA 403 B B, CUA 404 B B,
CUA 405 B B, CUA 406 B B,
CUA407BB (108B Series)
240-5

• Chassis CUA410BB (108B Series)
240-5

• Chassis CUA413BB (108B Series)
240-5

• Chassis CUA418BB, CUA419BB,
CUA420BB (108B Series) 240-5

• Chassis MCT228 95A-9

MAGNECORP. (See Recorder Listing)

MAGUIRE (Also see Recrd Changer Listing)

500BI, 500BW, 500DI, 500DW 6-15
561BI, 561BW, 561DI, 561DW 6-16
571 44-10

MAGUIRE—Cont.

601, 601A 12-18
700A 7-18
700E 15-17

MAJESTIC

• G-614 133-8
• G-614 133-8
• G-624 133-8
• G-614 133-8
411 270-7
4P1 276-6
5A410 (Ch. 4501), 5A430 (Ch.
4504) 1-30
5A445, 5A445R 23-12
5A471 27-17
5AK731, 5AK780 (Ch. 5805A)
28-19

5C-2, 5C-3 169-10

5LA5, 5LA6 130-9

5LA7, 5LA8 132-9

5M1 270-8

6FM714 (Ch. 6802D) 50-10

6FM773 (Ch. 6811D) 57-10

78K758 (See Model 7J777R—Set
27-18)

7C432 (Ch. 4706) 14-17

7C432 (Ch. 4707) (See Model
7C432—Set 14-17)

7FM877, 7FM888 (Ch. 7C11D)
56-14

7JK777R (Ch. 4708R) 27-18

7JL866 (Ch. 7C25A) 60-14

7P420 (Ch. 4705) 26-17

75433, 75450, 75470 (Ch. 4702,
4703) 22-19

7YR752 (Ch. 7804A) 29-13

7YR753 (Ch. 7809A-1), 7YR772
(Ch. 7809A) 42-17

8FM744 (Ch. 8804D) 30-15

8FM775 (Ch. 8808D), 8FM776 (Ch.
8807D) 29-14

8FM889 (Ch. 8C07D) 54-12

8JL885 (Ch. 4810B) 47-11

85452, 85473 (Ch. 4810) 8-19

10FM981 (Set 65-8) 108-7

• 12C4, 12C5 108-7

• 12FM475, 12FM778, 12FM779 (Ch.
41201) 28-20

• 12FM895 (Ch. 12C22E) 59-11

• 12T1, 12T2 108-7

• 12T6 (See Model 12C4—Set 108-7)

• 14C4 (See Model 12C4—Set 108-7)

• 14C7A 133-8

• 14T2 (See Model 12C4—Set 108-7)

• 16C4, 16C5 108-7

• 16C7A, 16C7S 133-8

• 16T2, 16T3 108-7

• 17C42, 17C43 (Series 112, 112-2)
(See Series 112—Set 233-4)

• 17C62, 17C64, 17C65 (Series 106)
(See PCB 43—Set 177-1 and Model
70—Set 153-8)

• 17DA (Ch. 101) 127-7

• 17GA, 17HA (Ch. 101) 127-7

• 17TA6A, 17TA81 (Series 106) (See
Model 70—Set 153-8 and PCB 43
—Set 177-1)

• 17TA6, 17TA7 (Series 112, 112-2)
(See Series 112—Set 233-4)

• 17T62 (Series 106) (See PCB 43—
Set 177-1 and Model 70—Set
153-8)

• 19C2, 19C7 133-8

• 20C2, 20C83, 20C84 (Series 108)
(See PCB 43—Set 177-1 and
Model 70—Set 153-8)

• 20FP88, 20FP89 (Series 109)
170-10

• 20F82, 20F83 (Series 108) (See PCB
43—Set 177-1 and Model 70—
Set 153-8)

• 20F85, 20F86, 20F87 (Series 108)
(See PCB 43—Set 177-1 and
Model 70—Set 153-8)

• 20F811 (Series 108) (See PCB 43—
Set 177-1 and Model 70—Set
153-8)

• 20T82, 20T83, 20T84 (Series 108)
(See PCB 43—Set 177-1 and
Model 70—Set 153-8)

• 21C30, 21C31 (Series 108) (See
PCB 43—Set 177-1 and Model 70—
Set 153-8)

• 21C36, 21C37, 21C38, 21C39 (Se-
ries 116) 280-5

• 21D40, 21D41 (Series 108) (See
PCB 43—Set 177-1 and Model 70—
Set 153-8)

• 21D50, 21D51 (Series 108) (See
PCB 43—Set 177-1 and Model 70—
Set 153-8)

• 21D56, 21D57, 21D58, 21D59 (Se-
ries 116) 280-5

• 21F86, 21F87 (Series 108) (See
PCB 43—Set 177-1 and Model 70—
Set 153-8)

• 21F88, 21F89 (Series 108-5) (See
PCB 43—Set 177-1 and Model 70—
Set 153-8)

• 21P62, 21P63 (Series 110, 111)
221-7

• 21T20, 21T21 (Series 108) (See
PCB 43—Set 177-1 and Model 70—
Set 153-8)

• 21T22, 21T23 (Series 116) 280-5

• 22 thru 35 Series 106-5) (See PCB
43—Set 177-1 and Model 70—
Set 153-8)

• 70, 72, 73 (Series 106) (Also see
PCB 43—Set 177-1) 153-8

• 80FP27 137-6

• 120-1, 121, 121B (Ch. 99) (Also see
PCB 37—Set 166-2) 127-7

• 141, 141B (Ch. 100), 141C (Ch.
101), 142, 142B (Ch. 100)
127-7

• 143 (See PCB 37—Set 166-2 and
Model 17DA—Set 127-7)

• 160, 160B, 162, 163 (Ch. 101)
127-7

• 170 (Ch. 101) 127-7

• 173 (See PCB 37—Set 166-2 and
Model 17DA—Set 127-

MOTOROLA-OAK

MOTOROLA-Cont.

52R11U, 52R12U, 52R13U, 52R-14U, 52R15U, 52R16U (Ch. HS-31) 177-1

MOTOROLA-Cont.

107F31, 107F31B (Ch. HS-87) 33-14

MOTOROLA-Cont.

Ch. HS-244 (See Model 5H11U) Ch. HS-245 (See Model 4X11U)

MOTOROLA-Cont.

Ch. TS-325, A, TS-326, A (See Model 17F12)

MUNTZ-Cont.

Ch. TS-325, A (Ch. 1782) (See Ch. 1782-Set 163-8)

NOTE: PCB Denotes Production Change Bulletin. Production Change Bulletin Nos. 1 Through 64 Are All Contained in Set No. A-200

OLDSMOBILE

- 982375 20-25
982399 59-14
982420 57-12
982421 87-7
982454 87-7
982543 157-7
982544, 982573 96-7
982579 157-7
982697, 982698 (See Model 982544—Set 96-7)
982699, 982700 150-10
982990 225-13
983004 235-8
983090 267-10
983091 261-10
983024 (See PCB 123—Set 277-1 and Model 983090—Set 267-7)
983205 (See PCB 122—Set 277-1 and Model 983091—Set 261-1)

OLYMPIC

- DX 214, DX-215, DX-216 106-11
DX-619, DX-620, DX-621, DX-622 106-11
DX-931, DX-932 106-11
DX-950 106-11
HF500 256-11
RTU-3H (Duplicator) 62-15
TV-104, TV-105 67-15
TV-106, TV-107, TV-108 (See Model TV-104—Set 67-15)
TV-246 (See Model TV-946—Set 67-15)
TV-247 (See Model TV-947—Set 85-10)
TV-248 (See Model TV-948—Set 67-15)
TV-922 58-14
TV-922L 67-15
TV-928 (See Model TV-922—Set 58-14)
TV-944, TV-945 67-15
TV-946 (See Model TV-104—Set 67-15)
TV-947 85-10
TV-948 (See Model TV-104—Set 67-15)
TV-949, TV-950 85-10
XL-210, XL-211 109-8
XL-612, XL-613 109-8
6-501, 6-502, 6-502-P, 6-503 4-10
6-501W, U (See Model 6-501W—U—Set 3-20)
6-501W-U, 6-502-U 3-20
6-504, 6-504L 3-25
6-601W, 6-601V, 6-602 8-24
6-604 Series 22-21
6-604V-110, 6-604V-220, 6-604AV-110, 6-604V-150, 6-604 220 (See Model 6-604 Series—Set 22-21)
6-606 4-36
6-606-A 11-17
6-606-U 11-18
6-617 4-7
6-617U (See Model 6-617—Set 4-7)
7-421V, 7-421W, 7-421X 57-13
7-435V, 7-435W 34-13
7-526 30-21
7-532W, 7-532V 32-15
7-537 37-13
7-622, 7-638 34-14
7-724 (See Model 7-724—Set 29-19)
7-925, 7-934, 7-936, 7-939 31-22
8-451 48-15
8-533V, 8-533W 57-14
8-618 35-16
8-925, 8-934, 8-936 45-19
9-435V, 9-435W 152-11
17C (See Model 752—Set 124-11)
17C24 182-7
17C44 (Ch. TK17) 196-9
17C57 (Ch. TM-17) 216-7
17C70 (See Model 752—Set 124-11)
17K31, 17K32 182-6
17K41, 17K42 (Ch. TK17) 196-9
17K50 (Ch. TK17) 196-9
17K55 (Ch. TM-17) 216-7
17T20 182-6
17T33 196-9
17T40 (Ch. TK17) 196-9
17T48 (Ch. TK17) 196-9
17T56 (Ch. TM-17) 216-7
17T71 (Ch. TM-17) (See Model 17C57—Set 216-7)
17T75 (Ch. TM-17) (See Model 17C57—Set 216-7)
17T83 (Ch. TM-17) (See Model 17C57—Set 216-7)
17T85 (Ch. TM-17) (See Model 17C57—Set 216-7)
17T89, 17T91 (Ch. 'R') 267-8
17TW27 (Ch. W) 288-7
20C22 (See Model 967—Set 139-11)
20C45 (Ch. TL20) 196-9
20C52, 20C53 (Ch. TL20) 196-9
20D (See Model 967—Set 139-11)
20D49 (Ch. TL20) 196-9
20K43 (Ch. TL20) 196-9
20K51 (Ch. TL20) 196-9
20T21 (See Model 967—Set 139-11)
20T46, 20T47 (Ch. TL20) 196-9
21C28 182-7
21C65, 21C68 (Ch. TN-21) 214-7
21C72, 21C73 (Ch. TN-21) 214-7
21C80, 21C81, 21C82 (Ch. TN-21) (See Model 21C65—Set 214-7)
21C89, 21C90, 21C91, 21C92 (Ch. TN-21) (See Model 21C65—Set 214-7)
21C512, 21C518 (Ch. 'S') 267-8
21CUI5, 21CUI6 (Ch. 'U') 267-8
21CX29 (Ch. X) 288-7
21D29 182-7
21D60, 21D64 (Ch. TN-21) 214-7
21K26 182-7
21K61, 21K62, 21K63 (Ch. TN-21) 214-7
21K101 (Ch. TN-21) (See Model 21C65—Set 214-7)
21KS22 (Ch. 'S') 267-8
21T27 182-7

OLYMPIC—Cont.

- 21T58 (Ch. TN-21) 214-7
21T69, 21T70 (Ch. TN-21) 214-7
21T74 (Ch. TN-21) 214-7
21T88 (Ch. TN-21) (See Model 21C65—Set 214-7)
21T511, 21T517 (Ch. 'S') 267-8
21TUI4 (Ch. 'U') 267-8
21TX28 (Ch. X) 288-7
22D100 through 22D109 (Ch. TN-21) (See Model 21C65—Set 214-7)
22D111 (Ch. TN-21) (See Model 21C65—Set 214-7)
22D113 through 22D117 (Ch. TN-21) (See Model 21C65—Set 214-7)
51-421W 151-9
51-435-W (See Model 9-435V—Set 152-11)
402 286-8
445 264-15
489 154-9
505 505B
572B, W 257-11
752, 752U, 753, 753U 126-8
754 (See Model 752—Set 126-8)
755, 755U 126-8
757 (See Model 752—Set 126-8)
758 (See Model 752—Set 126-8)
762 139-11
764, 764U 126-8
765, 766 (See Model 752—Set 126-8)
767 126-8
768, 769, 773 (See Model 752—Set 126-8)
783 139-11
785 (See Model 762—Set 139-11)
791, 792 (See Model 752—Set 126-8)
967, 968, 970 139-11
971, 972, 973 (See Model 967—Set 139-11)
Ch. 'R' (See Model 17CR20)
Ch. 'S' (See Model 21C512)
Ch. 'W' (See Model 17TW27)
Ch. 'U' (See Model 21CUI5)
Ch. 'X' (See Model 21CX29)
Ch. TK17 (See Model 17T40)
Ch. TL20 (See Model 20C45)
Ch. TM-17 (See Model 17C57)
Ch. TN-21 (See Model 21C65)

OPERADIO

- 1A30 34-15
1A35 33-15
1A45 48-16
1A65 52-14
1A70-A 47-16
1A140 46-17
4A25-E 101-8
4A30-A 102-9
4A35 100-9
4A50-A, 4A51-A 102-9
4A55 100-9
4M25C 99-11
11A55 113-6
530, 531, 1335 'Soundmaster' 37-14

ORTHOSONIC (See Electronic Labs.)

PACIFIC MERCURY (See Mercury)

PACKARD

- PA-382042 20-26
PA-393607 57-15
416387 160-7
416394 145-8
439279 (See PCB 104—Set 250-1 and Model 416387—Set 140-7)
439310 (See PCB 104—Set 250-1 and Model 416387—Set 140-7)
439338, 439339 229-8
439661 (See PCB 104—Set 250-1 and Model 416387—Set 140-7)
439663 (See PCB 101—Set 247-1 and Model 439338—Set 229-8)
439665 (See PCB 104—Set 250-1 and Model 416387—Set 140-7)
439666 (See PCB 101—Set 247-1 and Model 439338—Set 229-8)

PACKARD-BELL

- CI362 12-21
CI461 12-22
5D4 16-29
5D8 44-15
5F9 1-29
100 53-16
261 1-28
471 30-22
531 231-11
532 232-4
541 270-12
543 270-12
553 27-7
551-D (See Model 551—Set 2-7)
561 2-35
563 (See Model 561—Set 2-35)
576 (See Model 551—Set 2-7)
568 19-24
571 (See Model 572—Set 22-22)
572 22-22
581 (See Model 581—Set 44-15)
621 181-8
631 256-12
632 266-11
651 44-42
661 8-25
662 13-22
673A, 673B 46-18
682 54-16
683 44-16
684 17-23
687 31-23
880, 880A 46-16
881-A, 881-B 47-17
884, 892 74-7
1052, 1052A 8-26
1043 13-23
1046 18-25
1181, 1181A 75-12
1273 46-19
1472 48-17
1841, 1842 (Ch. 1840) 260-12
1941, 1942 (Ch. 1840) 260-12

PACKARD-BELL—Cont.

- 2001TV, 2002TV 98-8
2041, 2042, 2043, 2044 (Ch. 2040) 233-8
2101, 2102 123-10
2102, 2105A 123-10
2115, 2116 (Ch. 2115-2) 195-9
2117 (Ch. 2117) 195-9
2118 204-7
2141, 2142, 2133, 2144 (Ch. 2040) 233-8
2202, 2204 123-10
2291TV, 2292TV, 2293TV, 2294TV, 2295TV, 2296TV 82-10
2297-TV De Luxe, 2297-TV Standard 82-10
2298-TV 126-9
2301-TV 126-9
2302 (See Model 2301—Set 182-10)
2311 161-6
2421, 2422, 2423 187-9
2601-TV 122-6
2602 123-10
2622, 2622 (Ch. 2621-2) 196-10
2692-TV 122-7
2721, 2722 (Ch. 2720) 207-6
2723, 2724 (Ch. 2710) 207-6
2742, 2743 (Ch. 2740) 238-10
2801-TV, 2801A-TV 126-9
2803TV 129-8
2811A 161-6
2841 (Ch. 2840) 242-7
2842, 2843, 2844 (Ch. 2740) 238-10
2846, 2847 (Ch. 2840) (See Model 2841—Set 242-7)
2921, 2922 213-4
2941 (Ch. 2940-1) 238-10
2942 (Ch. 2840) 242-7
2946, 2947 (Ch. 2840) (See Model 2841—Set 242-7)
2991TV 94-6
3041 (Ch. 2940-1) 238-10
3042 (Ch. 3040-1) 242-7
3142 (Ch. 3040-1) 242-7
31701, U, 1710A, U (Ch. T-10) 274-11
21102, U (Ch. T-10) 274-11
21103, U (Ch. T-1) 282-11
21201, U (Ch. T-10) 274-11
21202, U (Ch. T-1) 282-11
21204, U (Ch. T-10) 274-11
21206, U (Ch. T-10) (See Model 17101—Set 274-11)
21401, U (Ch. T-1) 282-11
21402, U (Ch. T-10) (See Model 17101—Set 274-11)
Ch. T-1 (See Model 21103)
Ch. T-10 (See Model 17101)
Ch. T-1840 (See Model 1841)
Ch. 2040 (See Model 2041)
Ch. 2115-2 (See Model 2115)
Ch. 2117 (See Model 2117)
Ch. 2621-2 (See Model 2621)
Ch. 2740 (See Model 2723)
Ch. 2742 (See Model 2742)
Ch. 2840 (See Model 2841)
Ch. 2940-1 (See Model 2941)
Ch. 3040-1 (See Model 3042)

PARKVIEW

- 17X 185-9

PATHE (Similar to Chassis) 127-12

PEDERSEN

- PCP-20 289-7

PENTRON (Also see Recorder Listings)

- AFM 264-16
AM-T 183-11
F-100 184-10
HFP-1 253-10
MM4 178-8

PHILCO (Also see Recorder Listing)

- A-T1814, A-T1816, L (Code 123) (Ch. 81, H-1, H-1A) (See PCB 83—Set 224-1 and Model 53-T1824—Set 201-7)
A-T1816 (Code 129) (Ch. 81A, D-81) (Also See PCB 115—Set 267-1)
A-T1817, HM (Code 123) (Ch. 81, H-1, H-1A) (See PCB 83—Set 224-1 and Model 53-T1824—Set 201-7)
A-T1856, HM, L, W (Code 123) (Ch. 81, H-1, H-1A) (See PCB 83—Set 224-1 and Model 53-T1824—Set 201-7)
A-T1856W (Code 129) (Ch. 81A, D-81) (Also See PCB 115—Set 267-1)
A-T1858 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2230, L (Code 123) (Ch. 81, H-1, H-1A) (See PCB 83—Set 224-1 and Model 53-T1824—Set 201-7)
A-T2232 (Code 129) (Ch. 81A, D-81) (Also See PCB 115—Set 267-1)
A-T2274, W (Code 123) (Ch. 81, H-1, H-1A) (See PCB 83—Set 224-1 and Model 53-T1824—Set 201-7)
A-T2274, W (Code 123) (Ch. 81, H-1, H-1A) (See PCB 83—Set 224-1 and Model 53-T1824—Set 201-7)
A-T2275 (Code 129) (Ch. 81A, D-81) (Also See PCB 115—Set 267-1)
A-T2277, L (Code 123) (Ch. 81, H-1, H-1A) (See PCB 83—Set 224-1 and Model 53-T1824—Set 201-7)
A-T2278 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2279 (Code 129) (Ch. 81A, D-81) (Also See PCB 115—Set 267-1)
A-T2282, L (Code 123) (Ch. 81, H-1, H-1A) (See PCB 83—Set 224-1 and Model 53-T1824—Set 201-7)
A-T2283 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2289 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1, and Model 53-T1853—Set 185-10)
A-T2291 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2292 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2293 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2294 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2295 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2296 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2297 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2298 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2299 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2300 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2301 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2302 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2303 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2304 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2305 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2306 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2307 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2308 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2309 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2310 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2311 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2312 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2313 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2314 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2315 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2316 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2317 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2318 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2319 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2320 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2321 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2322 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2323 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2324 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2325 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2326 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2327 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2328 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2329 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2330 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2331 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2332 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2333 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2334 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2335 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2336 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2337 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2338 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2339 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2340 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2341 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2342 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2343 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2344 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2345 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2346 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2347 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2348 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2349 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2350 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2351 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2352 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2353 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2354 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2355 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 185-10)
A-T2356 (Code 128) (Ch. 91A, J-2) (See PCB 66—Set 203-1, PCB 82—Set 223-1 and Model 53-T1853—Set 1

RAYTHEON-SHERIDAN ELECTRONICS

RAYTHEON-Cont.

- M-1612A (Ch. 16AY21), M-1612B (Ch. 16AY28) [Also see PCB 19—Set 132-1] 124-8
M-1613A (Ch. 16AY21), M-1613B (Ch. 16AY28) [Also see PCB 19—Set 132-1] 124-8
M-1626 (Ch. 16AY21) 165-2A
M-1711A (Ch. 17AY24), M-1711B (Ch. 17AY21) [Also see PCB 19—Set 132-1] 124-8
M-1712A (Ch. 17AY24), M-1712B (Ch. 17AY21) [Also see PCB 19—Set 132-1] 124-8
M-1713A (Ch. 17AY24), M-1713B (Ch. 17AY21) [Also see PCB 19—Set 132-1] 124-8
M-1725A (Ch. 17AY21) [See PCB 19—Set 132-1 and Model M-1711B—Set 124-8] 124-8
M-1726 (Ch. 17AY21), [See PCB 19—Set 132-1 and Model M-1711B—Set 124-8] 124-8
M-1726A, M-1728A (Ch. 17AY21A) 174-10
M-1733A (Ch. 17T1) [Also see PCB 87—Set 230-1] 189-14
M-1733b, IA, mA (Ch. 17T1) [See PCB 87—Set 230-1 and Model C-1735A—Set 189-14] 189-14
M-1734A (Ch. 17T1) [For TV Ch. See PCB 87—Set 230-1 and Model C-1735A—Set 189-14, For UHF Tuner See Model UHF-100—Set 207-8] 189-14
M-1737, IA, mA (Ch. 17T4) [See PCB 87—Set 230-1 and Model C-1735A—Set 189-14] 189-14
M-1750A, C, G, K, M-1751D, F, M-1752E, L (Ch. 17T18), 261-3
M-2007A, M-2008A (Ch. 20AY21) [See PCB 43—Set 177-1 and Model C-2001A—Set 149-9] 173-1A
M-2101A (Ch. 21AY21) [See Model C-2103A] 173-1A
M-2107A (Ch. 21T1) [Also see PCB 87—Set 230-1] 189-14
M-2107b, IA, mA [See PCB 87—Set 230-1 and Model C-1735A—Set 189-14] 189-14
M-2125A, mA (Ch. 21T5) [See PCB 87—Set 230-1 and Model C-1735A—Set 189-14] 189-14
M-2131A (Ch. 21T11) 244-8
M-2160A, C, G, K, M-2160D, F, M-2161E, L (Ch. 21T9), 261-3
P-301 [See Model 7DX21—Set 81-13] 81-13
P-51, A, (Ch. 4P12, A) 218-9
RC-1405 (Ch. 14AX21) [For TV Ch. only see Model C-1401—Set 123-12] 123-12
RC-1618A (Ch. 16AY21), RC-1618B (Ch. 16AY28) [Also see PCB 19—Set 132-1] 124-8
RC-1619A (Ch. 16AY21) [Also see PCB 19—Set 132-1] 124-8
RC-1619B (Ch. 16AY28) [Also see PCB 19—Set 132-1] 124-8
RC-1718A (Ch. 17AY24) [See PCB 19—Set 132-1 and Model M-1711A—Set 124-8] 124-8
RC-1718B (Ch. 17AY21) [Also see PCB 19—Set 132-1] 124-8
RC-1719A (Ch. 17AY24) [See PCB 19—Set 132-1 and Model M-1711A—Set 124-8] 124-8
RC-1719B (Ch. 17AY21) [Also see PCB 19—Set 132-1] 124-8
RC-1720A (Ch. 17AY27), 147-9
RC-2005A (Ch. 20AY21) [See PCB 43—Set 177-1 and Model C-2001A—Set 149-9] 173-1A
RC-2117A (Ch. 21T3) [Also see PCB 87—Set 230-1 and Model C-1735A—Set 189-14, RC-2122A, RC-2123A (Ch. 21T3) [See PCB 87—Set 230-1 and Model C-2112A—Set 202-7] 202-7
UC-1736A, UC-1736A (Ch. 17T2) [For TV Ch. See PCB 87—Set 230-1 and Model C-1735A—Set 189-14, For UHF Tuner See Model UHF-100—Set 207-8] 207-8
UC-1740A, UC-1740A (Ch. 17T5) [For TV Ch. See PCB 87—Set 230-1 and Model C-1735A—Set 189-14, For UHF Tuner See Model UHF-100—Set 207-8] 207-8
UC-2109A, UC-2110A (Ch. 21T2) [For TV Ch. See PCB 87—Set 230-1 and Model C-1735A—Set 189-14, For UHF Tuner See Model UHF-100—Set 207-8] 207-8
UC-2128A, UC-2130A (Ch. 21T6) [For TV Ch. See PCB 87—Set 230-1 and Model C-1735A—Set 189-14, For UHF Tuner See Model UHF-100—Set 207-8] 207-8
UC-2139A, UC-2141A, UC-2142A, UC-2144A, UC-2145A (Ch. 21T8) 239-7
UC-2403A, UC-2404A, UC-2405A, UC-2406A (Ch. 24T2), 237-9
UM-1734b, IA, mA (Ch. 17T2) [For TV Ch. See PCB 87—Set 230-1 and Model C-1735A—Set 189-14, For UHF Tuner See Model UHF-100—Set 207-8] 207-8
UM-1738IA, mA (Ch. 17T5) [For TV Ch. See PCB 87—Set 230-1 and Model C-1735A—Set 189-14, For UHF Tuner See Model UHF-100—Set 207-8] 207-8
UM-2107b, IA, mA (Ch. 21T1) 189-14
UM-2107b, IA, mA (Ch. 21T1) 189-14
UM-2136A (Ch. 21T8), 239-7
UHF-100 (UHF Tuner) 207-8
7DX21, 7DX22P 81-13

RAYTHEON-Cont.

- 10AXF23 [Also see PCB 3—Set 105-1] 75-14
10AXF44 [See Model C-1102—Set 94-8 and Model A-10DX24—Set 71-4] 71-4
10DX21, 10DX22 [Also see PCB 3—Set 105-1] 75-14
10DX24 [See Model A-10DX24—Set 75-14] 75-14
18DX21A (See Model C-81-13) Ch. 18AY24 (See Model C-81-13) Ch. 4P12 A (See Model PR-51, A) Ch. 8AF25A (See Model FR81A) Ch. 10AX22 (See Model M701) Ch. 12AX22 (See Model C1102) Ch. 12AX26, 12AX27 (See Model C-1102B) Ch. 14AX21 (See Model C-1401) Ch. 16AX23, 25, 26 (See Model C-1602) Ch. 16AY28 (See Model C-1615B) Ch. 16AY211 (See Model C-1615A) [Also see PCB 19—Set 132-1] Ch. 16AY12 (See Model M-1626) Ch. 17AY21 (See Model C-1714B) Ch. 17AY21A (See Model C-1729) Ch. 17AY24 (See Model C-1715A) Ch. 17AY27 (See Model RC-1720A) Ch. 17T1 (See Model C-1735A) Ch. 17T2 (See Model M-1734A) Ch. 17T4 (See Model C-1741A) Ch. 17T5 (See Model UC-1740A) Ch. 17T18 (See Model M-1750A) Ch. 20AY21 (See Model C-2001A) Ch. 21AY21 (See Model C-2103A) Ch. 21T1 (See Model C-2108) Ch. 21T2 (See Model C-2109A) Ch. 21T3 (See Model C-2112A) Ch. 21T5 (See Model C-2127A) Ch. 21T6 (See Model UC-2128A) Ch. 21T8 (See Model UC-2139A) Ch. 21T9 (See Model M-2160A) Ch. 21T19 (See Model M-2160A) Ch. 24T2 (See Model UC-2403A) Ch. 24T3 (See Model C-2401A) 149-10
1810 149-10
1C-10 146-9
1J10 (Ch. 1J1) 128-12
2A10 163-10
6A10, 6A20 (Ch. 6A) 10-27
6B1, 6B2, 6B3, 6B32, 8-27
7D42, 7D44 (Ch. 7D1) 52-18
7E40, 7E44 47-20
8J10, 8J50 62-17
9G10 91-10
9G40M, 9G42 86-9
9H40M 89-13
Ch. 1J1 (See Model 1J10) Ch. 6A (See Model 6A10) Ch. 7D1 (See Model 7D42) 149-10
REELIST (See Recorder Listing)
REGAL (TOK-FONE) Tok-Fone (20-watt Amp.) 13-27 AP40, ARP400, ARP450 15-26 BR418, BR419 49-18 C473 217-12 C-527 182-9 CD31 [See Model 16T31—Set 80-16] 80-16 CR761 195-8 CR871 238-11 FM78 68-14 L-7 5-18 P-125 183-12 W700 [See Model W800—Set 14-26] W800, W801 14-26 W900, W901 13-28 16T31 80-14 17HD31, 17HD36 147-10 17T2, 17T2DX 143-13 19C31, 19C36 147-10 19D31, 19D36 147-10 20C22, 20C2DX 143-13 20C31, 20C36 147-10 20D22, 20D2DX 143-13 20D31, 20D36 147-10 20HD31, 20HD36 147-10 20T22, 20T2DX 143-13 22D17, 22D17DX, 22D19, 22D19DX 143-13 205 26-23 206 [See Model W800—Set 14-26] 271 210-7 472 217-12 575 210-8 747 27-22 777 83-9 1007 83-9 1030, 1031 80-14 1049 17-28 1107 41-19 1207, 1208 83-9 1500 38-19 1607 83-9 1708, 1708DX 143-13 1731, 1736 (See Model 17HD31—Set 147-10) 1736 28-29 1877 182-10 1931, 1936 (See Model 17HD31—Set 147-10) 2031, 2036 (See Model 17HD31—Set 147-10) 2217, 2217DX, 2219, 2219DX 143-13 7152 70-8 7162 69-12 7163 66-14 7251 40-16
REGENCY HF-80 272-12 HF-150 265-10 HF-200 285-13 HF-350A 271-11 HF-350P 278-11 RC-53 Tel. UHF Conv. 266-12 RC-600 Tel. UHF Conv. 200-8 TR-1 283-10

REMBRANDT

- 721, 1606, 1606-15, 1950. 65-11
REMLER HF-5-3 8-28 5308, 5308B1, 53001 23-18 5310 40-17 5400, 5410 44-19 5500 "Scottie Pup" (See Model 5505 "Scottie Pup" (See Model 5500—Set 27-23) 27-23 5515 "Scottie Pup" (See Model 5500—Set 27-23) 27-23 5520, 5530 "Scottie Junior" 27-23 6000 77-9
RENARD L-1A, PT-1A, 185T-1 9-28
REVERE (Also See Recorder Listings) 400 269-13
ROLAND 4P2 266-13 4C1 213-7 511 215-11 5C2 225-14 5P2 231-13 5P4 233-9 5T1E 205-8 5T1V 208-10 5T2M 204-9 5T3 231-14 5T4 238-2 5T5 234-11 5X1, 5X2 217-13 5X3, 5X4 247-9 6P2 236-12 6T1M 216-9 8F1M 214-9 8XF1, 8XF2 211-11 8XF3-M, 8XF4-M 249-13 10TF1 249-14 10XF1 280-10
ROYAL (Lee) AN150, AN160 179-11 20CP, 20TP (Similar to Chassis) 149-13
SCOTT (E. H.) Musicale 44-20 Music Control, Dynamic Noise Suppressor 46-21 "Ravenswood" 150-11 6T11, 6T11A [Also see PCB 4—Set 105-2] 52-19 6T12 52-19 310 154-11 400 [See PCB 4—Set 105-2 and Model 6T11—Set 52-19] 52-19 510 103-14 510B 165-11 1000, 710A, 710K 124-12 800B7 (For TV Ch. see PCB 4—Set 105-2 and Model 6T11—Set 52-19, For Radio Ch. see Model 800B-8) 817C (Ch. 9029, 9031) [See Model 820C—Set 178-9] 178-9 817C (Ch. 9036, 9037, 9038, 9039) 217-14 817C (Ch. 9043) 234-12 817C (Ch. 9029, 9031) [See Model 820C—Set 178-9] 178-9 817T (Ch. 9029, 9031) [See Model 820C—Set 178-9] 178-9 817T (Ch. 9036, 9037, 9038, 9039) 217-14 817T (Ch. 9043) 234-12 817TU (Ch. 9029, 9031) [See Model 820C—Set 178-9] 178-9 820C 178-9 820TU [See Model 820C—Set 178-9] 178-9 821C (Ch. 9036, 9037, 9038, 9039) 217-14 821C (Ch. 9043) 234-12 821CB (Ch. 9036, 9037, 9038, 9039) 217-14 821CB (Ch. 9043) 234-12 821D (Ch. 9036, 9037, 9038, 9039) 217-14 821D, DB, DBH, DM, DMH (Ch. 9043) 234-12 821RC, RCH (Ch. 9043) 234-12 821T (Ch. 9036, 9037, 9038, 9039) 217-14 821T (Ch. 9043) 234-12 821TB (Ch. 9036, 9037, 9038, 9039) 217-14 821TB (Ch. 9043) 234-12 824C, CH, DB, DBH, DM, DMH (Ch. 9045) 242-9 910 150-11 924W 176-11 924XW (Ch. 9045) 242-9 1000 180-8 1510 181-11 2000 229-13 2510 233-10 Ch. 9029, 9031 (See Model 817C) Ch. 9036, 9037, 9038, 9039 (See Model 817C) 217-14 Ch. 9043 (See Model 817C) Ch. 9045 (See Model 824C) Ch. 9052 265-12
SCOTT (H. H.) 99-A 267-17 111-B 143-14 112-B 144-8 120-A 183-13 121-A 265-11 210-A 79-15 210-B 145-9 211-A 81-14 214-A (120-A, 220-A) 183-13 220-A 183-13 232, 232A 272-13
SEARS-ROEBUCK (See Allstate or Silvertone)
SEEBURG (See Record Changer Listing)

SENTINEL

- 1U-284GA 22-25 1U-284I, 1U-284NA, 1U-284NI, 1U-284W 1-2 1U-285P 6-27 1U-293CT 29-29 1U-293I, 1U-293T, 1U-293W 1-14 1U-294I, 1U-294N, 1U-294T 1-11 1U312PG, 1U312PW 103-15 1U-313I, 1U-313W 39-21 1U-314E, 1U-314I, 1U-314W 38-21 1U-316PM, 1U-316PT 48-22 1U-335PG, PI, PM, PW, 105-9 1U338-I, 1U338-R, 1U338-W 122-9 1U339-K 111-12 1U340-A 129-10 1U342K 155-14 1U-343 212-6 1U-344 211-2 1U345P 183-14 1U346 209-11 1U-357, 1U-358 111-12 1U416 115-9 1U419, 1U420 115-9 1U420B 124-9 1U421, 1U422 (Series "YA") 124-9 PCB 16—Set 126-1 and Model 412-29 (See 100-11) 1U423 [Also see PCB 19—Set 132-1] 124-9 1U423B, 1U423-17 (See PCB 19—Set 132-1 and Model 1U423—Set 124-9) 124-9 1U424 [Also see PCB 19—Set 132-1 and Model 1U424—Set 124-9] 124-9 1U424-17 (See PCB 19—Set 132-1 and Model 1U424—Set 124-9) 124-9 1U-425 127-10 1U428 127-10 1U429, 1U430, 1U431 (See PCB 25—Set 124-9) and Model 1U420B—Set 124-9) 124-9 1U-432 [Also see PCB 21—Set 136-1] 127-10 1U435 (See PCB 21—Set 136-1 and Model 1U425—Set 127-10) 127-10 1U438, 1U439, 1U440, 1U441, 1U-442, 1U444 (Series "XD, XDD, 2XD") 157-9 1U446, 1U447 (Series "XD, XDD, 2XD") [See Model 1U438—Set 157-9] 157-9 1U447-A, 1U448-A, 1U449-A, 1U-450-A, 1U451-A 178-10 1U448, 1U-449, 1U-450 (Series "XD, XDD, 2XD") [See Model 1U-438—Set 157-9] 157-9 1U-454, 1U-455, 1U-456, 1U-457 [Also see PCB 63—Set 197-1] 191-17 1U-458, 1U-459, 1U-460, 1U-461 199-10 1U462, 1U463 (Ch. 2WA) 205-9 1U500 22-8 1U510, 1U511, 1U512, 1U513 226-8 1U515 226-8 1U-520 226-8 1U-520B [See PCB 97—Set 242-1 and Model 1U-520—Set 242-1] 242-1 1U-521 [See PCB 97—Set 242-1 and Model 1U-521—Set 226-8] 226-8 1U-522 226-8 1U-522B [See PCB 97—Set 242-1 and Model 1U-522—Set 242-1] 242-1 1U-523 226-8 1U525 226-8 1U-532, A 239-8 1U-542, A 239-8 1U-552, 1U-554 239-8 1U-562, 1U-564 239-8 1U-581, 1U-582 240-7 1U-584, 1U-585 240-7 1U-600 [See PCB 97—Set 242-1 and Model 1U-500—Set 226-8] 226-8 1U-610, 1U-612 [See PCB 97—Set 242-1 and Model 1U-510—Set 226-8] 226-8 1U-620, 1U-622 [See PCB 97—Set 242-1 and Model 1U-520—Set 226-8] 226-8 1U-701 262-11 1U-711 262-11 1U-714 262-11 1U-721 262-11 1U-724 262-11 1U-752 262-11 1U-755 262-11 1U-758 262-11 1U-762 262-11 1U-765 262-11 1U-768 262-11 1U-791 262-11 1U-901 275-14 1U-911, 1U-914 275-14 1U-921, 1U-924 275-14 1U-991 275-14 L-284I, L-284NA, L-284NI, L-284R, L-284W 23-19 284C, L-284W 22-25 284I 1-2 284NA, 284NI 1-2 285P 6-27 286P, 286PR 23-20 289T 28-29 292K 16-30 293 Series 1-14 293-CT 29-22 293I, 293T, 293W 1-14 294 Series 2-11 294I, 294N, 294T 22-6 295-1 46-22 296B, 296M 33-23 302-1, 302-T, 302-W 33-23 305-I, 305-I-3, 305-W, 305-W-3 3-24 309-I, 309-N, 309-R, 309-W 23-30 312PG, 312PW 103-15 313-I, 313-W 39-21 314-E, 314-I, 314-W 38-21 315-I, 315-W 40-19 316PM, 316PT 48-22 332 (See Model 313-I—Set 39-21) 333 (See Model 315-I—Set 40-19) 335PG, PI, PM, PW 105-9 338-I, 338-R, 338-W 122-9

SENTINEL-Cont.

- 339-K 111-12 340-C 129-10 342K 155-14 343 212-6 344 211-2 345P 183-14 346 209-11 400TV 73-11 401, 402 Series 73-11 403TV 73-11 405 Series 70-9 406 Series 70-9 407 Series 70-9 409 Series 70-9 411 Series (See Model 401 Series—Set 70-9) 70-9 412, 413, 414, 415 (Series YA, YB, YC, YD, YE, YF) [Also see PCB 4—Set 105-2] 100-11 416 117-12 419, 420 115-9 420B 124-9 421, 422 (See PCB 16—Set 126-1 and Model 412—Set 100-11) 124-9 423, 424 (Also see PCB 19—Set 132-1) 124-9 423B, 423-17 (See PCB 19—Set 132-1 and Model 423—Set 124-9) 124-9 424 [Also see PCB 19—Set 132-1] 124-9 424-17 (See PCB 19—Set 132-1 and Model 424—Set 124-9) 124-9 425 127-10 425B 127-10 429, 430, 431 (See PCB 25—Set 144-1 and Model 1U-420B—Set 124-9) 124-9 432 [Also see PCB 21—Set 136-1] 127-10 435 (See PCB 21—Set 136-1 and Model 425—Set 127-10) 127-10 438, 439, 440, 441, 443, 444 (Series "XD, XDD, 2XD") 157-9 446 (Series "XD, XDD, 2XD") [See Model 438—Set 157-9] 157-9 452, 453 (See Model 1U-447-A—Set 178-10) 178-10 454, 455, 456, 457 [Also see PCB 63—Set 197-1] 191-17 458, 459, 460, 461 [See Model 1U-458—Set 199-10] 199-10 462, 463, 466 [See Model 1U-454—Set 191-17] 191-17 2911 [See PCB 128—Set 287-1 and Model 1U-901—Set 275-14] 275-14 2914 [See PCB 128—Set 287-1 and Model 1U-901—Set 275-14] 275-14 21011B [See PCB 128—Set 287-1 and Model 1U-901—Set 275-14] 275-14 21017B [See PCB 128—Set 287-1 and Model 1U-901—Set 275-14] 275-14 Ch. 2WA (See Model 462) 462
SETCHALL-CARLSON A53, A531, A533, A5301, A5302, A-5303 (Ch. 153) 243-8 53 (Ch. 152) 209-12 150 144-9 151-A17, 151-A17-LR, 151-B17, 151-B17-LR, 151-B20, 151-B20-LR, 151-C20, 151-C20-LR 155-15 416 2-14 427 21-29 437 39-22 447 46-30 458-RD 106-13 469 99-15 531 (Ch. 152) 209-12 551, 552, 553 (Ch. 155) 276-9 570 97-15 2500, 2500LP 209-12 5301, 5302 (Ch. 152) 209-12 5501, 5502, 5503 (Ch. 155) 276-9 Ch. 152 (See Model 53) Ch. 153 (See Model 551) Ch. 155 (See Model 551)
SHAW Ch. 224 (Runs 301, 302, 303, 304, 304-1, -2, 305, 305-2) 202-8
SHERATON (Also See Video Products) C30B, M 176-13 C30B24, C30M24 176-13 C-2125 (Ch. 250XL Series) 218-10 T300M 176-13 T-1755 (Ch. 250XL Series) 218-10 T-2155 (Ch. 250XL Series) 218-10 17MT20 (Ch. 530DX Series) 210-9 17MT20 (Ch. 530DX-A) (See PCB 89—Set 233-1 and Model 17MT20—Set 210-9) 210-9 21BC10 (Ch. 530DX Series) 210-9 21BC10 (Ch. 530DX-A) (See PCB 89—Set 233-1 and Model 17MT20—Set 210-9) 210-9 21BD10 (Ch. 530DX Series) 210-9 21BD10 (Ch. 530DX-A) (See PCB 89—Set 233-1 and Model 17MT20—Set 210-9) 210-9 21AC10 (Ch. 530DX Series) 210-9 21AC10 (Ch. 530DX-A) (See PCB 89—Set 233-1 and Model 17MT20—Set 210-9) 210-9 21MD10 (Ch. 530DX Series) 210-9 21MD10 (Ch. 530DX-A) (See PCB 89—Set 233-1 and Model 17MT20—Set 210-9) 210-9 21MT100 (Ch. 530DX Series) 210-9 21MT100 (Ch. 530DX-A) (See PCB 89—Set 233-1 and Model 17MT20—Set 210-9) 210-9 Ch. 250XL (See Model C2125) Ch. 530DX (See Model 17MT20) Ch. 530DX-A (See Model 17MT20)
SHERIDAN ELECTRONICS (See Vogue)

NOTE: PCB Denotes Production Change Bulletin. Production Change Bulletin Nos. 1 through 63 Are All Contained in Set No. A-200. Production Change Bulletin Nos. 64 Through 104 Are All Contained in Set No. A-250. Denotes Television Receiver.

SIGNAL

- AF252 37-19
141 44-21
241 33-25
341-A 39-23
341-T 25-25

SILVERLINE (See General Instrument)

SILVERTONE (Also see Changer and Recorder Listing)

- PC-5100 (Ch. 456.31300) (See Model 5100—Set 264-17)
PC-5101 (Ch. 456.31500) (See Model 5101—Set 279-14)
PC-5106 (Ch. 456.31700) (See Model 5106—Set 264-17)
PC-5107 (Ch. 456.31500) (See Model 5101—Set 279-14)
PC-5110 (Ch. 456.31400) (See Model 5100—Set 264-17)
PC-5110A (Ch. 456.32800) (See Model 5126A—Set 264-17)
PC-5112 (Ch. 456.31600) (See Model 5101—Set 279-14)
PC-5115 (Ch. 456.31600) (See Model 5101—Set 279-14)
PC-5117 (Ch. 456.31600) (See Model 5101—Set 279-14)
PC-5126 (Ch. 456.31400) (See Model 5126—Set 264-17)
PC-5126A (Ch. 456.32800) (See Model 5126A—Set 264-17)
PC-5127 (Ch. 456.31600) (See Model 5101—Set 279-14)
PC-5129 (Ch. 456.31600) (See Model 5101—Set 279-14)
PC-5131 (Ch. 456.31600) (See Model 5101—Set 279-14)
PC-5139 (Ch. 456.31600) (See Model 5101—Set 279-14)
PC-41102 (Ch. 456.32800) (See Model 5126A—Set 264-17)
1 (Ch. 132.878) 101-10
2 (Ch. 132.878-1) (See Model 1—Set 101-10)
2 (Ch. 132.878-1) (See Model 2—Set 101-10)
5, 6 (Ch. 132.881) 144-10
10, 11 (Ch. 132.896) 144-11
15, 16 (Ch. 132.884, -1, -2) 141-12
18 (Ch. 132.877) 140-11
20 (Ch. 132.877) 140-11
25, 27 (Ch. 478.238) 101-13
33 (Ch. 549.100-1) 111-13
41, 41A (Ch. 135.245) 101-11
43, A (Ch. 135.245) (See Model 41—Set 101-11)
51, 53 (Ch. 132.887) 112-8
54, 56 (Ch. 132.888) 115-10
57PC143B, W (Ch. 456.200-21) (See PCB 109—Set 257-1 and Model 3376—Set 225-16)
64, 65 (Ch. 101.859-2) 113-8
67 (Ch. 101.859-1, -2) (See Model 64—Set 113-8)
67B (Ch. 101.859-2) (See Model 64—Set 113-8)
69 (Ch. 100.201) 162-10
72 (Ch. 134.111) 142-11
101 (Ch. 549.100-1) 102-12
101A (Ch. 549.100-1) 102-12
102A (Ch. 549.100-3, -7) 161-9
106, 107 (Ch. 132.889-2) 149-12
108 (Ch. 549.100) 102-12
110, A (Ch. 478.303, A) (See Model 110—Set 118-9)
112 (Ch. 478.289) 118-9
114 (Ch. 478.302) (See Model 125—Set 104-10)
115 (Ch. 110.499-7A, B, 8A, B)
116, 116A (Ch. 110.700-1, -10) 139-13
120 (Ch. 478.311) 115-11
125 (Ch. 478.257) 104-10
131, 131A (Ch. 110.700-1, -10) 139-13
132 (Ch. 110.499-1) (See Model 9123—Set 79-16)
133 (Ch. 549.100-1 and Radio Ch. 101.831-1) 156-12
135 (Ch. 110.499-7A, B, 8A, B)
137 (Ch. 549.100-1 and Radio Ch. 101.831-1) (For TV Ch. See Model 101—Set 102-12 and Radio Ch. See Model 8127—Set 41-20)
138 (Ch. 549.100-3 and Radio Ch. 101.831-1) (For TV Ch. See Model 102A—Set 161-9 and Radio Ch. See Model 8127—Set 41-20)
141 (Ch. 132.889-2) 149-12
143 (See Model 143A—Set 121-12)
143A (Ch. 100.111) 121-12
144 (Ch. 478.312 and Radio Ch. 478.240) 160-11
149 (Ch. 100.107-1) (See Model 139—Set 156-12)
150-14 (Ch. 478.338) 142-12
151-16, 151-17 (Ch. 528.630-1)
152, 16, 16A (Ch. 549.102, 549-102-2) 115-11
159 (Ch. 478.309) 115-11
160-12 (Ch. 549.100-4) 97A-12
161-16 (Ch. 100.111) 99-10
162-17 (Ch. 110.700-10) 139-13
163-16 (Ch. 478.319) 157-10
164-14 (Ch. 478.313)
165-16 (Ch. 100.120) 144-12
166-16 (Ch. 478.339)
166-17 (Ch. 478.339A)
167-16, 167-16A (Ch. 549.101, -1)
168-16 (Ch. 549.100-3) 161-9
169-16 (Ch. 549.102, 549.102-2)
170-16 (Ch. 549.102, 549.102A)
173-16 (Ch. 110.700-10) 139-13
175-16, A (Ch. 549.100-5, -8, -9) 161-9
176-19 (Ch. 549.100-6) 161-9
177-19 (Ch. 110.700-40) 139-13
179-16, 180-16 (Ch. 132.890) 130-12

SILVERTONE—Cont.

- 185-16 (Ch. 549.101-2)
186-19 (Ch. 549.101-3)
187-16, 188-16 (Ch. 110.700-10)
189-16 (Ch. 110.700-1, -10)
194-16, 195-16 (Ch. 132.890)
210 (Ch. 132.890)
215 (Ch. 528.174)
217, 218 (Ch. 528.174) (See Model 215—Set 117-13)
220 (Ch. 528.173)
222, 223, 224 (Ch. 528.173)
225 (Ch. 528.171)
237 (Ch. 488.237)
238 (Ch. 548.360-1, 548.361) (See Model 239—Set 115-12)
239 (Ch. 548.360-1, 548.361)
245 (Ch. 548.358-1)
246 (Ch. 137.906)
249 (Ch. 548.360-1, 548.361)
1017, 1018 (Ch. 528.210, -1, -2)
1032 (Ch. 528.196)
1035, A (Ch. 528.195, -1, -2)
1038 (Ch. 528.219) (See Model 1040—Set 181-12)
1040, 1045 (Ch. 528.194) 181-12
1040A (Ch. 528.194-1) (See Model 1040—Set 181-12)
1045A (Ch. 528.194-1) (See Model 1040—Set 181-12)
1052 (Ch. 132.011) 174-10
1052A (Ch. 132.011-1) (See Model 1052—Set 174-10)
1053 (Ch. 132.011) 174-10
1053A (Ch. 132.011-1) (See Model 1053—Set 174-10)
1054 (Ch. 132.012) 173-12
1054A (Ch. 132.012-1) (See Model 1054—Set 173-12)
1055 (Ch. 132.012) 173-12
1055A (Ch. 132.012-1) (See Model 1055—Set 173-12)
1058, 1059 (Ch. 101.860) 162-11
1062, 1063 (Ch. 101.860) 162-11
1064 (Ch. 100.202) 162-10
1117-17 (Ch. 110.700-100, -104)
1130-17, 1130A-17 (Ch. 110.700-100, -104)
1141-20 (Ch. 528.194-1) 201-8
1145-20 (Ch. 110.700-140) 201-8
1145-14 (Ch. 478.361, A)
1161-17 (Ch. 110.700-10) 205-10
1162-17 (Ch. 110.700-100, -104)
1166-17 (Ch. 478.339-B)
1171-17 (Ch. 110.700-10, -50)
1172-17 (Ch. 110.700-100, -104)
1173-20 (Ch. 110.700-140) 201-8
1176-12 (Ch. 100.208) 165-12
1181-20 (Ch. 110.700-10) 201-8
1183-21 (Ch. 110.700-150) 201-8
1184-20 (Ch. 528.631, -1) 181-13
1186-21 (Ch. 100.208) 165-12
1188-20 (Ch. 110.700-140) 201-8
1239 (Ch. 408.237) (See Model 237—Set 145-10)
1260 (Ch. 456.150, -2, -6, -15) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
1261 (Ch. 456.150, -2, -21) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
1266 (Ch. 456.150, -2, -6, -15) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
1268 (Ch. 456.150, -1, -11, -81) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
1270, 1271 (Ch. 456.150-1, -11) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
1272, 1274, 1275 (Ch. 456.150-1, -11) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
1297, 1298 (Ch. 456.150-3) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
1299 (Ch. 456.150-7, -9, -17) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
1300 (Ch. 319.200), 1300-1 (Ch. 319.200-1) 90-10
1301 (Ch. 319.190) 91-11
2001, 2002 (Ch. 132.878) (See Model 1—Set 101-10)
2003, 2004, 2005, 2006 (Ch. 757-10)
2007 (Ch. 757.100) 211-13
2009, 2010, 2011, 2012, 2013 (Ch. 132.022) 196-14
2014, 2015, 2016 (Ch. 132.021) 196-15
2018, 2019 (Ch. 757.100-1) 211-13
2022 (Ch. 132.027) 197-11
2023, 2024, 2025, 2026, 2027 (Ch. 132.896-1) (See Model 10—Set 144-11)
2028 (Ch. 528.230) 203-8
2035A (Ch. 528.195, -1, -2) 215-12
2041 (Ch. 528.235) 208-11
2041 (Ch. 528.235-1) (See Model 2041—Set 208-11)
2056 (Ch. 132.026-3) 207-9
2060, 2061 (Ch. 101.861, -1, -2) 203-9
2063, 2064 (Ch. 101.860, -1) (See Model 1058—Set 162-11)
2068 (Ch. 100.202) (See Model 1066—Set 162-10)
2100 (Ch. 110.700-100, -104)
2100A (Ch. 110.817-1) 217-15
2105 (Ch. 132.024, -1, -2) 198-13

SILVERTONE—Cont.

- 2105A (Ch. 132.024-3, -31) 198-13
2110A, 2111 (Ch. 528.631, -1, -1) (Ch. 528.632A, -1, -2, -3, -5) 212-7
2115B (Ch. 528.631, -1, Ch. 528.632, -1, -2, -3, -4, -5, Ch. 528.632A, -1, -2, -3, -5) 212-7
2130 (Ch. 100.210, -1, -3) 207-10
2130A (Ch. 110.820-1, -2) 217-12
2145 (Ch. 132.024, -3) 198-13
2145A (Ch. 132.024-3, -31) 198-13
2145B (Ch. 132.024-4) 198-13
2150 (Ch. 110.700-140) 201-8
2150A (Ch. 110.820-1) 217-15
2150B (Ch. 528.631, -1, Ch. 528.632, -1, -2, -3, -4, -5, Ch. 528.632A, -1, -2, -3, -5) 212-7
2160, 2162 (Ch. 528.631, -1, Ch. 528.632, -1, -2, -3, -4, -5, Ch. 528.632A, -1, -2, -3, -5) 212-7
2170A (Ch. 100.210) 207-10
2170-D, -E (Ch. 100.210, -1, -3) 207-10
2172 (Ch. 100.210, -1, -3) 207-10
2174 (Ch. 132.035) (See PCB 79—Set 206-1 and Model 3174—Set 206-1)
2195-21 (Ch. 100.208-1 and Radio Ch. 100.202-1) (See PCB 59—Set 193-1 and Model 1176-21—Set 165-12 for TV Ch. and Model 1066A—Set 162-10 for Radio Ch.)
2200, 2202, 2203 (Ch. 528.229) 201-9
2210 (Ch. 132.880) (See Model 210—Set 207-10)
2215, 2217, 2218 (Ch. 528.238)
2225 (Ch. 528.233) 208-12
2243 (Ch. 137.914, -1, -2, -3) 230-9
2246 (Ch. 137.914, -1, -2, -3) 230-9
2249, 2250 (Ch. 137.915) 269-14
2260 (Ch. 456.150-6, -15) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
2262, 2265, 2266 (Ch. 456.150-1, -81) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
2276 (Ch. 456.150-9, -14, -18 and Radio Ch. 456.155) (Also See PCB 118—Set 270-1)
2278, 2279 (Ch. 456.150-11, -81) (For and Radio Ch. 456.860-1) (Also See PCB 118—Set 270-1 and Model 2276—Set 230-10)
2280 (Ch. 456.150-6, -13) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
2282, 2287 (Ch. 456.150-6, -15) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
2289 (Ch. 456.150-9, -12, -17) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
2290 (Ch. 456.150-9, -17) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
2297, 2298 (Ch. 456.150-81) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
3001, 3002 (Ch. 132.054) 239-9
3003 (Ch. 757.100-1) 211-15
3007, 3008, 3009 (Ch. 757.100) 226-9
3025, 3026, 3027 (Ch. 132.066) 249-15
3032 (Ch. 528.252) 219-10
3035A (Ch. 528.195, -1) 215-12
3040 (Ch. 528.253) 221-9
3040A (Ch. 528.311) 270-13
3041 (Ch. 528.235-1) (See Model 2041—Set 208-11)
3045, 3046 (Ch. 528.254) 216-10
3052, 3053 (Ch. 132.053) 225-15
3054, 3055 (Ch. 132.056) 250-18
3058, 3059 (Ch. 101.860-3) 240-8
3061, 3062 (Ch. 101.861-1) (See Model 3064—Set 203-9)
3063, 3064 (Ch. 101.860-3) 240-8
3067 (Ch. 101.860-3) 240-8
3068 (Ch. 100.174) 270-14
3100 (Ch. 110.817-1) (See Model 2100A—Set 217-15)
3100A (Ch. 110.817, -3) (See Model 2100A—Set 217-15)
3101 (Ch. 110.817-3) (See Model 2100A—Set 217-15)
3102X (Ch. 528.271, -1, -2, -3, -4, -5) (See Model 4108—Set 245-6)
3103A (Ch. 528.290-2) 253-12
3104A (Ch. 528.271-3, -4) 245-6
3105 (Ch. 132.024-5, -6, -7, -8) (Also See PCB 117—Set 269-13)
3106 (Ch. 132.045, -1, -2, -3, -4, -5) (Also See PCB 90—Set 235-1) 199-11
3109 (Ch. 528.264) 227-12
3110 (Ch. 528.248, -1, -2) 220-7
3110A (Ch. 528.242, -1, -2) 220-7
3110B (Ch. 528.264, -1, 2) 227-12
3112 (Ch. 528.256) (See Model 3112B—Set 227-12)
3112B (Ch. 528.263, -1, -2) 227-12
3112C (Ch. 528.258) 247-10
3112X (Ch. 528.292, -1, -2, -3, -4) (See Model 4113A—Set 245-6)
3115 (Ch. 528.248, -1, -2) 200-7
3115A (Ch. 528.242, -1, -2) 220-7
3127 (Ch. 100.210, -1, -3) 207-10
3136 (Ch. 100.425-2, -4, -6, -8) 281-6
3140 (Ch. 110.817-1, -3) (See Model 2100A—Set 217-15) 245-6

SILVERTONE—Cont.

- 3145 (Ch. 132.024-5, -6, -7, -8) (Also See PCB 117—Set 269-1) 198-13
3146 (Ch. 132.045-2, -3, -4, -5) (See PCB 117—Set 269-1 and Model 3106—Set 199-11) 217-12
3150 (Ch. 110.820-1, -3) (See Model 2100A—Set 217-15)
3150L (Ch. 528.264, -1) 227-12
3151A (Ch. 528.256) 227-12
3151B (Set 227-12)
3151B, C (Ch. 528.263, -1, -2) 227-12
3160 (Ch. 528.248, -1, -2) 220-7
3160A (Ch. 528.242, -1, -2) 220-7
3170 (Ch. 528.239)
3170-B (Ch. 100.210, -1, -3) 207-10
3170C (Ch. 528.249, -1) 218-11
3170D (Ch. 528.261) 217-12
3171A (Ch. 528.247, -1) 217-16
3174 (Ch. 132.035-2) 206-11
3175 (Ch. 132.044) 203-10
3177 (Ch. 100.210, -1, -3) 207-10
3177A (Ch. 100.400) 244-10
3181, 3185 (Ch. 100.425-2, -4) 281-6
3187 (Ch. 100.210, -1, -3) 207-10
3187A (Ch. 100.400) 244-10
3195 (Ch. 100.210-2 and Radio Ch. 100.202-1) (See PCB 91—Set 236-1 and Model 2130—Set 207-10 for TV Ch. and Model 1066—Set 162-10 for Radio Ch.)
3200 (Ch. 528.259) 224-12
3202, 3203 (Ch. 528.259) 224-12
3210 (Ch. 528.241) 220-8
3215 (Ch. 528.265) (See Model 3217—Set 227-13)
3217 (Ch. 528.265) 227-13
3218 (Ch. 528.265) (See Model 3217—Set 227-13)
3247 (Ch. 548.400, -1) 281-7
3260, 3261 (Ch. 456.150-19, -81) 255-16 (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
3263 (456.150-16) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
3268 (Ch. 456.150-19, -81) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
3271, 3272, 3273, 3274, 3275 (Ch. 456.150-19, -81) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
3276, 3277 (Ch. 456.150-22, -61) (For and Radio Ch. 456.155) (Also See PCB 118—Set 270-1)
3280 (Ch. 456.150-19, -81) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
3289, 3290 (Ch. 456.150-16) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
3295, 3296, 3297 (Ch. 456.150-19, -81) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
3298, 3299 (Ch. 456.150-16) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
3360, 3361 (Ch. 456.200-11, -12, -13, -21, -22, -23) (See PCB 109—Set 257-1 and Model 3376—Set 225-16)
3364, 3365, 3366 (Ch. 456.200-11) (See PCB 109—Set 257-1 and Model 3376—Set 225-16)
3368 (Ch. 456.200-11, -12, -13, -21, -22, -23) (See PCB 109—Set 257-1 and Model 3376—Set 225-16)
3371, 3372, 3373, 3374, 3375 (Ch. 456.200-11, -12, -13, -21, -22, -23) (See PCB 109—Set 257-1 and Model 3376—Set 225-16)
3376, 3377 (Ch. 456.200-11, -12, -13, -21, -22, -23) (See PCB 109—Set 257-1 and Model 3376—Set 225-16)
3378, 3379 (Ch. 456.200-11, -12, -13, -21, -22, -23) (See PCB 109—Set 257-1 and Model 3376—Set 225-16)
3399 (Ch. 456.200-1) (See PCB 109—Set 257-1 and Model 3376—Set 225-16)
3399A, 3399B (Ch. 456.200-1) (See PCB 109—Set 257-1 and Model 3376—Set 225-16)
3399C (Ch. 456.200-1) (See PCB 109—Set 257-1 and Model 3376—Set 225-16)
4016, 4017 (Ch. 757.100) 267-11
4022 (Ch. 757.300) 262-12
4032 (Ch. 757.300) 267-12
4035 (Ch. 528.305) 266-15
4041, B (Ch. 528.304, -1) 268-12
4045A, B, C, 4046A, B, C (Ch. 528.312, -1) 270-15
4056, 4057 (Ch. 132.026-6) 255-12
4068A (Ch. 100.176) 271-12
4103 (Ch. 528.34700) (See PCB 122—Set 276-1 and Model 5100—Set 264-17)
4107 (Ch. 528.290, -1) 253-12
4107A (Ch. 528.290-1, -2) 253-12
4108 (Ch. 456.200-1, -2, -3) (See PCB 109—Set 257-1 and Model 3376—Set 225-16) 245-6
4108 (Ch. 528.271) 281-6
4108A (Ch. 528.271, -1, -2, -3, -4) 281-6
4109 (Ch. 528.34800) (See PCB 122—Set 276-1 and Model 5100—Set 264-17)
4109A (Ch. 528.34801) (See PCB 122—Set 276-1 and Model 5100—Set 264-17)
4110 (Ch. 528.302) 253-12
4110B (Ch. 132.08400) 271-13
4111 (Ch. 528.264-1, -2) 227-12
4111A (Ch. 528.291, -1) 253-12
4112 (Ch. 528.303, -1) 245-6
4112B (Ch. 132.08500) 271-13
4113 (Ch. 528.263-1, -2) 227-12
4113A (Ch. 528.292-1) 245-6
4113B (Ch. 528.303, -1) 245-6
4114 (Ch. 528.264-2) 227-12
4114A (Ch. 528.291) 253-12
4114B (Ch. 528.291, -2) 253-12
4114C (Ch. 528.302) 253-12
4114W (Ch. 456.150-19, -81) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
4115 (Ch. 528.270) 227-12
4116 (Ch. 528.266) 227-12
4116W (Ch. 456.200-11, -12, -13, -21, -22, -23) (See PCB 109—Set 257-1 and Model 3376—Set 225-16)
4117 (Ch. 528.266) 227-12
4117W (Ch. 456.200-11, -12, -13, -21, -22, -23) (See PCB 109—Set 257-1 and Model 3376—Set 225-16)
4118 (Ch. 528.292-1, -2) 227-12
4118B (Ch. 528.292-1, -2) 227-12
4118C (Ch. 528.303, -1) 245-6
4118W (Ch. 456.200-11, -12, -13, -21, -22, -23) (See PCB 109—Set 257-1 and Model 3376—Set 225-16)
4119 (Ch. 528.263-2) 227-12
4119A (Ch. 528.303, -1) 245-6
4119W (Ch. 456.200-11, -12, -13, -21, -22, -23) (See PCB 109—Set 257-1 and Model 3376—Set 225-16)
4120 (Ch. 456.150-16) (See PCB 118—Set 270-1 and Model 2276—Set 230-10)
4124 (Ch. 528.290-1, -2) 253-12
4125 (Ch. 528.271-1, -2, -3, -4) 245-6
4126 (Ch. 528.264-1, -2) 227-12
4126A (Ch. 528.297) 253-12
4126B (Ch. 528.291, -2) 253-12
4126D (Ch. 528.302) 253-12
4127 (Ch. 528.263-1, -2) 227-12
4127 (Ch. 456.200-21) (See PCB 109—Set 257-1 and Model 3376—Set 225-16)
4127A (Ch. 528.268) 247-10
4127C (Ch

SILVERTONE

SILVERTONE-Cont.

- 4283 (Ch. 456.200-21) (See PCB 109-Set 257-1 and Model 3376 -Set 225-16)
4285 (Ch. 456.200-21) (See PCB 109-Set 257-1 and Model 3376 -Set 225-16)
5036 (Ch. 528.32400) ... 283-11
5038 (Ch. 528.32401) (See Model 5036-Set 283-11)
5041 (Ch. 528.304-2) (See Model 4041-Set 268-12)
5042 (Ch. 528.34000) ... 283-11
5042A (Ch. 528.32501) (See Model 5042-Set 283-11)
5045, 5046 (Ch. 528.34900)
5061, 5062, (Ch. 101.861-1) (See Model 2060-Set 203-9)
5100 (Ch. 528.31300, 528.31301) ... 264-17
5100A, AA (Ch. 528.33000) (See PCB 122-Set 276-1 and Model 5100-Set 264-17)
5101 (Ch. 528.31300) (See PCB 122-Set 276-1 and Model 5100-Set 264-17)
5101C (Ch. 528.31500) ... 279-14
5101A (Ch. 528.33800) ... 279-14
5106 (Ch. 528.31700, 528.31701) ... 264-17
5106-2 (Ch. 549.16002, 549.16004) ... 289-10
5106A, AA, B (Ch. 528.33100) (See PCB 122-Set 276-1 and Model 5100-Set 264-17)
5107 (Ch. 528.31500) ... 279-14
5107A (Ch. 528.33800) ... 279-14
5107B (Ch. 528.33800) (See Model 5101-Set 279-14)
5110 (Ch. 528.31400, 528.31401) ... 264-17
5110A (Ch. 528.32800) (See Model 5126A-Set 264-17)
5110C, CC (Ch. 528.34100) (See PCB 122-Set 276-1 and Model 5110-Set 264-17)
5111 (Ch. 528.302, -1) ... 253-12
5111B (Ch. 132.08400) ... 271-13
5112 (Ch. 528.31600) ... 279-14
5112A (Ch. 528.33900) ... 279-14
5112C (Ch. 528.34200) ... 279-14
5113 (Ch. 456.200-43) (See PCB 109-Set 257-1 and Model 3376 -Set 225-16)
5113 (Ch. 528.303-1) (See Model 4118C-Set 245-6)
5113B (Ch. 132.08500) ... 271-13
5114 (Ch. 528.31800, 528.31801) ... 264-17
5114-2, 5114-2W (Ch. 549.16000, 549.16002, 549.16003) ... 289-10
5114B (Ch. 528.32900) (See PCB 122-Set 276-1 and Model 5100-Set 264-17)
5114C (Ch. 528.34500) (See PCB 122-Set 276-1 and Model 5100-Set 264-17)
5114D (Ch. 528.34501) (See PCB 122-Set 276-1 and Model 5100-Set 264-17)
5115 (Ch. 528.31600) ... 279-14
5115A (Ch. 528.34200) ... 279-14
5115B (Ch. 528.33900) ... 279-14
5115C (Ch. 528.34600) ... 279-14
5115D (Ch. 528.34601) ... 279-14
5116 (Ch. 528.31800, 528.31801) ... 264-17
5116-2 (Ch. 549.16000, 549.16002, 549.16003) ... 289-10
5116B (Ch. 528.32900) (See PCB 122-Set 276-1 and Model 5100-Set 264-17)
5116C (Ch. 528.34500) (See PCB 122-Set 276-1 and Model 5100-Set 264-17)
5116D (Ch. 528.34501) (See PCB 122-Set 276-1 and Model 5100-Set 264-17)
5117 (Ch. 528.31600) ... 279-14
5117A (Ch. 528.34200) ... 279-14
5117B (Ch. 528.33900) ... 279-14
5117C (Ch. 528.34600) ... 279-14
5117D (Ch. 528.34601) ... 279-14
5118 (Ch. 528.31900, 528.31901) (Also See PCB 124-Set 280-1) ... 267-13
5119 (Ch. 456.200-21) (See PCB 109-Set 257-1 and Model 3376 -Set 225-16)
5119 (Ch. 528.32100) ... 282-14
5119A (Ch. 528.34100) (See PCB 122-Set 276-1 and Model 5100-Set 264-17)
5124 (Ch. 528.34000) (See PCB 122-Set 276-1 and Model 5100-Set 264-17)
5125 (Ch. 528.34200) ... 279-14
5126 (Ch. 528.31400, 528.31401) ... 264-17
5126A (Ch. 528.32800) ... 264-17
5126B (Ch. 528.32800) (See PCB 122-Set 276-1 and Model 5126A-Set 264-17)
5126C, CC (Ch. 528.34100) (See PCB 122-Set 276-1 and Model 5100-Set 264-17)
5127 (Ch. 528.31600) ... 279-14
5127A, B (Ch. 528.33900) ... 279-14
5127C (Ch. 528.34200) ... 279-14
5128 (Ch. 528.31800) (See PCB 122-Set 276-1 and Model 5100-Set 264-17)
5128B (Ch. 528.32900) (See PCB 122-Set 276-1 and Model 5100-Set 264-17)
5128C, D (Ch. 528.34500, 528.34501) (See PCB 122-Set 276-1 and Model 5100-Set 264-17)
5129 (Ch. 528.31600) ... 279-14
5129A (Ch. 528.34200) ... 279-14
5129B (Ch. 528.33900) ... 279-14
5129C (Ch. 528.34600) ... 279-14
5129D (Ch. 528.34601) ... 279-14
5130 (Ch. 528.31801) (See PCB 122-Set 276-1 and Model 5100-Set 264-17)
5130B (Ch. 528.32900) (See PCB 122-Set 276-1 and Model 5100-Set 264-17)

SILVERTONE-Cont.

- 5130C, D (Ch. 528.34500, 528.34501) (See PCB 122-Set 276-1 and Model 5100-Set 264-17)
5131 (Ch. 528.31600) ... 279-14
5131A (Ch. 528.34200) ... 279-14
5131B (Ch. 528.33900) ... 279-14
5131C (Ch. 528.34600) ... 279-14
5131D (Ch. 528.34601) ... 279-14
5132 (Ch. 528.31900, 528.31901) (Also See PCB 124-Set 280-1) ... 267-13
5133 (Ch. 456.200-21) (See PCB 109-Set 257-1 and Model 3376 -Set 225-16)
5133 (Ch. 528.32100) ... 282-14
5139 (Ch. 528.32000, 528.32001) ... 288-8 (Also See PCB 124-Set 280-1) ... 267-13
5140 (Ch. 456.200-21) (See PCB 109-Set 257-1 and Model 3376 -Set 225-16)
5140 (Ch. 528.32200) ... 282-14
5149 (Ch. 528.32001) (Also See PCB 124-Set 280-1) ... 267-13
5150 (Ch. 528.200-21) (See PCB 109-Set 257-1 and Model 3376 -Set 225-16)
5150 (Ch. 528.32202) ... 282-14
5155 (Ch. 528.33300) ... 89-11
5227 (Ch. 101.800-1) ... 9-29
6002 (Ch. 132.8181) ... 5-35
6011 (Ch. 132.8181), 6012 (Ch. 132.8181A) ... 15-27
6016 (Ch. 132.820) ... 27-24
6050 (Ch. 132.825-4) ... 15-28
6051 (Ch. 110.451), 6052 (Ch. 110.452) ... 13-29
6052A (Ch. 110.452, -1) (See Model 6051-Set 13-29)
6056, 6057 (Ch. 101.861-1) (See Model 2060-Set 203-9)
6071 (Ch. 52.826-1) ... 15-29
6072 (Ch. 110.454) ... 13-30
6092 (Ch. 101.672-1B), 6093 (Ch. 101.672-1A) ... 10-28
6100 (Ch. 101.660-1A) ... 6-29
6104 (Ch. 101.662-2D) (See Model 6105-Set 7-26)
6105 (Ch. 101.622-2B) ... 7-26
6106A (Ch. 101.662-4E) ... 29-23
6111 (Ch. 101.662-3C) ... 7-26
6111A (Ch. 101.662-5F) ... 29-23
6200A (Ch. 101.800-3) ... 9-29
6200B (Ch. 101.800-3) ... 65-12
6203 (Ch. 101.800A) (See Model 6200A-Set 9-29)
6210 (Ch. 528.308) (See Model 4210-Set 272-14)
6220 6220A (Ch. 101.801, 101.801A) ... 9-30
6230 (Ch. 101.802) ... 11-21
6230A (Ch. 101.802-1) ... 11-21
6285A (Ch. 101.866-1B) ... 20-28
6286 (Ch. 528.6286, -1, -3) 185-12
6287 (Ch. 528.6287, -1, -3) 185-12
6290 (Ch. 101.677-8) ... 20-29
6293 (Ch. 528.6293-2) ... 99-16
6295 (Ch. 528.6295) ... 98-12
6685 (Ch. 139.150, Ch. 139.150-1) ... 15-30
Power Shifter (Ch. 725.101-1) Tel. UHF Conv. ... 235-11
7020 (See Model 7021-Set 16-31)
7021 (Ch. 101.807, 101.807A) ... 16-31
7025 (Ch. 132.807-2) ... 29-23
7054 (Ch. 101.808) ... 15-31
7070 (Ch. 101.817) ... 30-26
7080 (Ch. 101.809) ... 16-32
7080, 7080A (Ch. 101.809-2) ... 30-27
7085 (Ch. 101.814) ... 58-20
7086 (Ch. 101.466) ... 27-25
7090 (Ch. 101.810) ... 15-32
7095 (Ch. 101.826) (See Model 7115-Set 16-33)
7100 (Ch. 101.811) ... 17-29
7102 (Ch. 101.819A) ... 30-27
7103 (Ch. 110.466-1) ... 27-25
7111 (Ch. 434.140) ... 30-28
7115 (Ch. 101.825), 7116 (Ch. 101.825-1A), 7117 (Ch. 101.825-1B) ... 16-33
7119 (Ch. 101.825-2C) ... 62-18
7145 (Ch. 436.200) ... 23-21
7148 (Ch. 431.188), 7148A (Ch. 431.188-1) ... 23-22
7152 (Ch. 109.626) ... 25-26
7153 (Ch. 109.630) ... 26-30
7165 (Ch. 101.823-A, 1A) ... 10-29
7166 (Ch. 101.823, 101.823-1) ... 10-29
7210 (Ch. 101.820) ... 32-20
7220 (Ch. 101.801-2C) (See Model 6220-Set 9-30)
7226 (Ch. 101.819A) ... 31-28
7230 (Ch. 101.802-2A) (See Model 6230-Set 11-21)
7300 (Ch. 435.240) ... 45-22
7330 (Ch. 435.410) ... 38-22
7353 (See Model 7350-Set 38-22)
8000 (Ch. 132.838) ... 31-29
8003 (Ch. 132.818-1) ... 53-22
8004 (See Model 8003-Set 53-22)
8005 (Ch. 132.839) ... 33-26
8010 (Ch. 132.840) ... 40-21
8011 (Ch. 132.841) ... 40-21
8020 (Ch. 132.841) ... 43-17
8021 (Ch. 132.868) ... 70-10
8024, 8025 (Ch. 478.206-1) ... 80-15
8050 (Ch. 101.813) ... 33-27
8051 (Ch. 101.839) ... 49-19
8053 (Ch. 101.808-1C) ... 68-15
8055 (Ch. 101.808-1D) (See Model 8052-Set 68-15)
8070 (Ch. 101.817-1A) (See Model 7070-Set 30-26)
8072 (Ch. 101.834) ... 34-19
8073 (Ch. 135.243) ... 84-9
8080 (Ch. 101.852) ... 52-20
8083, 8083A (Ch. 101.809-1A) ... 58-20
8084, 8084A (Ch. 101.809-1B) ... 58-20
8086 (Ch. 101.814-5C) ... 61-18
8086A, 8086B (Ch. 101.814-6C) ... 61-18
8090 (Ch. 101.821) ... 49-20

SILVERTONE-Cont.

- 8097 (Ch. 101.825-3G) (See Model 8115-Set 62-18)
8097A (Ch. 101.825-4) ... 62-18
8100 (Ch. 101.829) ... 51-19
8101 (Ch. 101.814, 8101B, 8101C) (Ch. 101.809-3C) ... 58-20
8102 (Ch. 101.814-2B) ... 61-18
8102A (Ch. 101.814-3B) ... 61-18
8102B (Ch. 101.814-2B) ... 61-18
8103 (Ch. 110.473) ... 56-21
8104 (See Model 8086-Set 61-18)
8105, 8106 (Ch. 101.833) 35-20
8106, A (Ch. 101.833-1A) (See Model 8105-Set 35-20)
8107A, 8108, 8108A (Ch. 101.851), 8109 (Ch. 101.851-1) ... 64-10
8110 (Ch. 101.813) (Ch. 101.851) (See Model 8107A-Set 64-10)
8115 (Ch. 101.825-3D) ... 62-18
8115, A, B, C (Ch. 101.825-4) ... 62-18
8115D (Ch. 101.825-4) (See Model 8115A-Set 62-18)
8115A-Set 62-18)
8117 (Ch. 101.825-3E) ... 62-18
8118 A, B, C (Ch. 101.825-4) ... 62-18
8118D (Ch. 101.825-4) (See Model 8118A-Set 62-18)
8124, 8125 (Ch. 101.831A, 101.831A-1) (See Model 8127-Set 41-20)
8127, A, B, C (Ch. 101.831A), 8128, A, B, C (Ch. 101.831), Wire Recorder Amp. (Ch. 101.773)
8127CX (Ch. 101.831A) and Wire Recorder Amp. (101.773) (See Model 8127-Set 41-20)
8130 (Ch. 101.854) ... 49-21
8132 (Ch. 101.829-1, (Ch. 101.846) ... 66-15
8133 (Ch. 101.829-1, (Ch. 101.846) ... 66-15
8144 (Ch. 431.199) ... 32-21
8145 (Ch. 109.631) ... 45-23
8148 (Ch. 109.632) ... 44-22
8150 (Ch. 109.633) ... 48-23
8150A (Ch. 109.634) ... 32-22
8152 (Ch. 109.635) (See Model 8153-Set 42-22)
8153 (Ch. 109.635), 8153A (Ch. 109.635-1) ... 42-22
8155 (Ch. 463.155) ... 57-17
8160 (Ch. 109.636A) ... 50-17
8168 (Ch. 109.638) ... 46-23
8169 (Ch. 109.638) (See Model 8168-Set 46-23)
8200 (Ch. 101.800-2B) (See Model 6200A-Set 65-12)
8201 (See Model 6200A-Set 65-12)
8210 (Ch. 101.820-1A) ... 71-13
8220, 8221 (Ch. 101.801-3D) (See Model 6220-Set 9-30)
8228 (See Model 6220-Set 9-30)
8230 (Ch. 101.835) ... 59-10
8231 (See Model 8230-Set 59-10)
8260 (Ch. 101.823-2B) (See Model 7165-Set 10-29)
8270 (Ch. 101.822), 8270A (Ch. 101.822A) ... 57-18
9000 (Ch. 132.857) ... 65-13
9005, 9006 (Ch. 132.858), 72-11
9022 (Ch. 132.871) ... 76-17
9054 (Ch. 101.849) ... 63-16
9078, 9078A (Ch. 135.244) ... 907-8
(Ch. 135.244, -1) ... 83-10
9073C (Ch. 135.243-1) (See Model 9073-Set 83-10)
9082 (Ch. 135.245) ... 101-11
9084 (Ch. 135.245) (See Model 41-22)
9101 (Ch. 101.809-3C) (See Model 7080-Set 58-20)
9102 (See Model 7080-Set 58-20)
9105 (Ch. 132.875) ... 89-14
9107 (Ch. 101.859-1) (See Model 64-Set 113-81)
9107A (Ch. 101.851-1) (See Model 8107A-Set 64-10)
9107B (Ch. 101.859-2) (See Model 64-Set 113-81)
9108 (Ch. 101.859-1) (See Model 9107-Set 113-81)
9111 (Ch. 110.499) (See Model 9123-Set 79-16)
9112 (Ch. 110.499-1) (See Model 9124-Set 79-16)
9113 (Ch. 478.221) (See Model 9123-Set 79-16)
9114 (Ch. 110.499-1) (See Model 9124-Set 79-16)
9115 (Ch. 478.224), 9116 (Ch. 478.221) ... 97-16
9116 (Ch. 478.221) ... 97-16
9120A (Ch. 101.862-1) *
9121 (Ch. 101.867) *
9122 (Ch. 101.864) (See Model 8132-Set 66-15)
9122A (Ch. 101.868) (See Model 8132-Set 66-15)
9123 (Ch. 110.499) ... 79-16
9124 (Ch. 110.499-1) ... 79-16
9125 (Ch. 478.252) ... 104-10
9125A (Ch. 478.253) ... 104-10
9125B (Ch. 478.253-1) ... 79-16
9126 (Ch. 110.499-2) (See Model 9126-Set 79-16)
9128A (Ch. 101.868) *
9129 (Ch. 110.499) (See Model 9123-Set 79-16)
9130 (Ch. 110.499-1) (See Model 9124-Set 79-16)
9131 (Ch. 478.210) ... 84-10
9132 (Ch. 110.499-1) (See Model 9124-Set 79-16)
9133, 9134 (Ch. 101.866 and Radio Ch. 101.859) ... 95-5
9139, 9140 (Ch. 110.499-1) (See Model 9124-Set 79-16)
9153 (Ch. 435.417) ... 67-16
9161 (Ch. 548.358) ... 88-10
9260 (Ch. 101.850) ... 51-20
9270 (Ch. 547.245) ... 82-11

SILVERTONE-Cont.

- 9280 (Ch. 528.168) ... 94-9
41102 (Ch. 528.32800) (See Model 5126A-Set 264-17)
41102A (Ch. 528.34100) (See PCB 122-Set 276-1 and Model 5100-Set 264-17)
41122, A (Ch. 528.33900) 279-14
41282A (Ch. 528.32900) (See PCB 122-Set 276-1 and Model 5100-Set 264-17)
41292 (Ch. 528.34200) ... 279-14
41292A (Ch. 528.33900) ... 279-14
41302A (Ch. 528.32900) (See PCB 122-Set 276-1 and Model 5100-Set 264-17)
41312 (Ch. 528.34200) ... 279-14
41312A (Ch. 528.33900) ... 279-14
42471 (Ch. 548.400, -1) ... 281-7
Ch. 100.043 (See Model 133)
Ch. 100.07 (See Model 133)
Ch. 100.107-1 (See Model 149)
Ch. 100.111 (See Model 143A)
Ch. 100.112 (See Model 161-16)
Ch. 100.120 (See Model 165-16)
Ch. 100.174 (See Model 306B)
Ch. 100.176 (See Model 468A)
Ch. 100.201 (See Model 69)
Ch. 100.202 (See Model 1066)
Ch. 100.202-1 (See Model 2195-21 or 3195)
Ch. 100.208 (See Model 1176-21)
Ch. 100.209-1 (See Model 2195-21)
Ch. 100.209 (See Model 2170-C)
Ch. 100.210, -1 (See Model 2130)
Ch. 100.210-2 (See Model 3195)
Ch. 100.210-3 (See Model 3130)
Ch. 100.400 (See Model 3177A)
Ch. 100.425-2, -4, -7, -8 (See Model 3136)
Ch. 101.660-1A (See Model 6100)
Ch. 101.662-2B (See Model 6105)
Ch. 101.662-2D (See Model 6105)
Ch. 101.662-3C (See Model 6111)
Ch. 101.662-4E (See Model 6106A)
Ch. 101.662-5F (See Model 6111A)
Ch. 101.666-1B (See Model 6285A)
Ch. 101.672-1A (See Model 6093)
Ch. 101.672-1B (See Model 6092)
Ch. 101.678 (See Model 6290)
Ch. 101.733 (See Model 8127)
Ch. 101.800-1, -1A (See Model 6200A)
Ch. 101.800-3 (See Model 6200A, Ch. 101.800-3)
Ch. 101.803-1 (See Model 6230)
Ch. 101.802, -1 (See Model 6230)
Ch. 101.807, A (See Model 7021)
Ch. 101.808 (See Model 7054)
Ch. 101.808-1C (See Model 8052)
Ch. 101.808-1D (See Model 8053)
Ch. 101.809 (See Model 7080)
Ch. 101.809-1A (See Model 8084)
Ch. 101.809-2 (See Model 7080)
Ch. 101.809-3C (See Model 8101)
Ch. 101.810 (See Model 7090)
Ch. 101.811 (See Model 7080)
Ch. 101.813 (See Model 8050)
Ch. 101.814 (See Model 7085)
Ch. 101.814-1A (See Model 7102)
Ch. 101.814-2B (See Model 8102A)
Ch. 101.814-3B (See Model 8102A)
Ch. 101.814-4C (See Model 8086)
Ch. 101.814-6C (See Model 8086A)
Ch. 101.817 (See Model 7070)
Ch. 101.819A (See Model 7226)
Ch. 101.820 (See Model 7210)
Ch. 101.821 (See Model 8090)
Ch. 101.822 (See Model 8270)
Ch. 101.822A (See Model 8270A)
Ch. 101.823, -1 (See Model 7166)
Ch. 101.823-A, -1A (See Model 7165)
Ch. 101.825 (See Model 7115)
Ch. 101.825-1A (See Model 7116)
Ch. 101.825-2C (See Model 7119)
Ch. 101.825-2D (See Model 8115)
Ch. 101.825-3E (See Model 8117)
Ch. 101.825-3G (See Model 8118)
Ch. 101.825-3G (See Model 8097)
Ch. 101.825-4 (See Model 8074)
Ch. 101.829 (See Model 8100)
Ch. 101.829-1 (See Model 8133)
Ch. 101.831 (See Model 8128)
Ch. 101.831A (See Model 8127)
Ch. 101.831-1 (See Model 8124)
Ch. 101.833 (See Model 8105)
Ch. 101.834 (See Model 8072)
Ch. 101.835 (See Model 8230)
Ch. 101.839 (See Model 8051)
Ch. 101.846 (See Model 8133)
Ch. 101.849 (See Model 9054)
Ch. 101.850 (See Model 9260)
Ch. 101.851 (See Model 8107A)
Ch. 101.851-1 (See Model 8109)
Ch. 101.852 (See Model 8080)
Ch. 101.854 (See Model 8132)
Ch. 101.859 (See Model 9133)
Ch. 101.859-1 (See Model 67)
Ch. 101.859-2 (See Model 64)
Ch. 101.860-3 (See Model 1058)
Ch. 101.860-3 (See Model 3058)
Ch. 101.861-1 (See Model 2060)
Ch. 101.864 (See Model 9122)
Ch. 101.865 (See Model 9119)
Ch. 101.865-1 (See Model 9120A)
Ch. 101.866 (See Model 9133)
Ch. 101.867 (See Model 9118)
Ch. 101.868 (See Model 9122A)
Ch. 109.626 (See Model 7152)
Ch. 109.627 (See Model 7153)
Ch. 109.632 (See Model 8145)
Ch. 109.633 (See Model 8149)
Ch. 109.634 (See Model 8150)
Ch. 109.635 (See Model 8153)
Ch. 109.635-1 (See Model 8153A)
Ch. 109.636 (See Model 8160)
Ch. 109.636A (See Model 8160A)
Ch. 109.638 (See Model 8168)
Ch. 110.451 (See Model 6051)
Ch. 110.452 (See Model 6052)
Ch. 110.454 (See Model 6072)
Ch. 110.466 (See Model 7086)

SILVERTONE-Cont.

- Ch. 110.466-1 (See Model 7103)
Ch. 110.473 (See Model 8103)
Ch. 110.499 (See Model 9123)
Ch. 110.499-1 (See Model 9124)
Ch. 110.499-2 (See Model 9126)
Ch. 110.700-1 (See Model 116)
Ch. 110.700-10 (See Model 116)
Ch. 110.700-40 (See Model 117)
Ch. 110.700-40 (See Model 117-19)
Ch. 110.700-100 (See Model 117-17)
Ch. 110.700-120 (See Model 1181-20)
Ch. 110.700-140 (See Model 1145-20)
Ch. 110.700-150 (See Model 1183-21)
Ch. 110.702-10, -50 (See Model 1171-17)
Ch. 110.817-1 (See Model 2100A)
Ch. 110.817-3 (See Model 3100A)
Ch. 110.820-3 (See Model 2150A)
Ch. 110.820-3 (See Model 3150)
Ch. 132.011 (See Model 1052)
Ch. 132.011-1 (See Model 1053A)
Ch. 132.012 (See Model 1054)
Ch. 132.012-1 (See Model 1054A)
Ch. 13

SILVERTONE-Cont.

- Ch. 456.31600 (See Model PC-5112)
Ch. 456.31700 (See Model PC-5106)
Ch. 456.32800 (See Model PC-5126A)
Ch. 463.155 (See Model 8155)
Ch. 478.206-1 (See Model 8024)
Ch. 478.210 (See Model 9131)
Ch. 478.221 (See Model 9116)
Ch. 478.224 (See Model 9115)
Ch. 478.238 (See Model 25)
Ch. 478.240 (See Model 144)
Ch. 478.252 (See Model 9125)
Ch. 478.253 (See Model 9125A)
Ch. 478.253-1 (See Model 9125B)
Ch. 478.257 (See Model 125)
Ch. 478.289 (See Model 112)
Ch. 478.302 (See Model 114)
Ch. 478.303, A (See Model 110)
Ch. 478.309 (See Model 159)
Ch. 478.311 (See Model 120)
Ch. 478.312 (See Model 144)
Ch. 478.313 (See Model 164-14)
Ch. 478.319 (See Model 163-16)
Ch. 478.338 (See Model 150-14)
Ch. 478.339 (See Model 166-16)
Ch. 478.339-A (See Model 166-17)
Ch. 478.339-B (See Model 1166-17)
Ch. 478.361, A (See Model 1150-14)
Ch. 488.237 (See Model 237)
Ch. 488.22000 (See Model 4243)
Ch. 488.1600 (See Model 9280)
Ch. 528.171-1 (See Model 225)
Ch. 528.173 (See Model 220)
Ch. 528.174 (See Model 215)
Ch. 528.194 (See Model 1040)
Ch. 528.195, -1, -2 (See Model 1035)
Ch. 528.196 (See Model 1032)
Ch. 528.210, -1 (See Model 1017)
Ch. 528.219 (See Model 1038)
Ch. 528.229 (See Model 2200)
Ch. 528.230 (See Model 2028)
Ch. 528.233 (See Model 2225)
Ch. 528.235 (See Model 2041)
Ch. 528.238 (See Model 2215)
Ch. 528.239 (See Model 2165)
Ch. 528.241 (See Model 3210)
Ch. 528.242, -1, -2 (See Model 3110A)
Ch. 528.247, -1, -2 (See Model 3171A)
Ch. 528.248, -1, -2 (See Model 3110)
Ch. 528.249, -1 (See Model 3170C)
Ch. 528.252 (See Model 3040)
Ch. 528.253 (See Model 3032)
Ch. 528.254 (See Model 3045)
Ch. 528.256 (See Model 3112A)
Ch. 528.258 (See Model 3112C)
Ch. 528.259 (See Model 3200)
Ch. 528.261 (See Model 3170D)
Ch. 528.263, -1, -2 (See Model 3112B)
Ch. 528.264 (See Model 3109)
Ch. 528.264-1, -2 (See Model 3110B)
Ch. 528.265 (See Model 3217)
Ch. 528.266 (See Model 3115)
Ch. 528.268 (See Model 4127A)
Ch. 528.270 (See Model 4115)
Ch. 528.271, -1, -2, -3, -4 (See Model 4108A)
Ch. 528.286 (See Model 4150D)
Ch. 528.290, -1 (See Model 4103)
Ch. 528.290-2 (See Model 4107A)
Ch. 528.291, -1, -2 (See Model 4111A)
Ch. 528.292, -1, -2, -3 (See Model 4118B)
Ch. 528.297 (See Model 4126A)
Ch. 528.299-3 (See Model 4142)
Ch. 528.300, -1, -2, -3, -4 (See Model 4140E)
Ch. 528.303, -1 (See Model 4112)
Ch. 528.304, -1, -2 (See Model 4041-B)
Ch. 528.305 (See Model 4035)
Ch. 528.306, -1, -2 (See Model 4025)
Ch. 528.307, -1 (See Model 4225)
Ch. 528.308 (See Model 4210)
Ch. 528.311 (See Model 3040A)
Ch. 528.312, -1 (See Model 4045A)
Ch. 528.630, -1 (See Model 151-16)
Ch. 528.631, -1 (See Model 2110A)
Ch. 528.632, -1, -2, -3, -4, -5 (See Model 2110A)
Ch. 528.632A, -1, -2, -3, -5 (See Model 2110A)
Ch. 528.6286, -1, -3 (See Model 6286)
Ch. 528.6287, -1, -3 (See Model 6287)
Ch. 528.6293-2 (See Model 6293)
Ch. 528.6295 (See Model 6295)
Ch. 528.31300, 528.31301 (See Model 5100)
528.31400, 528.31401 (See Model 5110)
Ch. 528.31500 (See Model 5101)
Ch. 528.31600 (See Model 5112)
Ch. 528.31700, 528.31701 (See Model 5106)
Ch. 528.31800, 528.31801 (See Model 5114)
Ch. 528.31900, 528.31901 (See Model 5118)
Ch. 528.32000, 528.32001 (See Model 5142)
Ch. 528.32100, 528.32101 (See Model 5119)
Ch. 528.32200 (See Model 5150)
Ch. 528.32201 (See Model 5155)
Ch. 528.32202 (See Model 5150)
Ch. 528.32800 (See Model 5126A)
Ch. 528.32900 (See Model 5114B)
Ch. 528.33000 (See Model 5100A)
Ch. 528.33100 (See Model 5106A)
Ch. 528.33101 (See Model 5106A)
Ch. 528.33200 (See Model 5227)
Ch. 528.33800 (See Model 5101A)

SILVERTONE-Cont.

- Ch. 528.33900 (See Model 5112A)
Ch. 528.34000 (See Model 5148)
Ch. 528.34001 (See Model 5148)
Ch. 528.34100 (See Model 5110C)
Ch. 528.34101 (See Model 5110C)
Ch. 528.34200 (See Model 5112C)
Ch. 528.34500, 528.34501, 528-34502, 528.34503, 528.34504 (See Model 5114C)
Ch. 528.34600 (See Model 5115C)
Ch. 528.34601 (See Model 5115D)
Ch. 528.34602, 528.34603 (See Model 5115C)
Ch. 528.34700 (See Model 4103)
Ch. 528.34800, 528.34801 (See Model 4109)
Ch. 528.34900 (See Model 5045)
Ch. 547.245 (See Model 9270)
Ch. 548.358 (See Model 9161)
Ch. 548.358-1 (See Model 245)
Ch. 548.360-1 (See Model 239)
Ch. 548.361 (See Model 239)
Ch. 548.363 (See Model 33)
Ch. 548.400, -1 (See Model 3247)
Ch. 548.401-1 (See Model 4242)
Ch. 549.100 (See Model 101)
Ch. 549.100-1 (See Model 101A)
Ch. 549.100-3 (See Model 102A)
Ch. 549.100-4 (See Model 160-12)
Ch. 549.100-5, -6, -7, -8, -9 (See Model 175-16)
Ch. 549.102, -2 (See Model 169-16)
Ch. 549.16000, 549.16001, 549-16002, 549.16003, 549.16004 (See Model 5106-2)
Ch. 725.101-1 (See Model 6950)
Ch. 757.100 (See Model 2007)
Ch. 757.100-1 (See Model 2018)
Ch. 757.110 (See Model 2003)
Ch. 757.120 (See Model 3007)
Ch. 757.130 (See Model 3004)
Ch. 757.140 (See Model 4200)
Ch. 757.150 (See Model 4064)
Ch. 757.300 (See Model 4032)
Ch. 757.421 (See Model 4212)

SIMPLON

- CA-5 22-27
WV2 17-30

SKY KNIGHT (See Air Knight)

SKYRIDER (See Hallcrafters)

SKYROVER

- NS-RD-250 (9022-N), NS-RD-251 (9022-H) 6-31
NS-RD295 (Ch. 5A7) 21-30

SOUND, INC.

- "InterSound" 7-27
MB6P3, MB6P6, MB6P30, MB6P4 3-21
MB7E3 28-31
MB7E8 26-24
SR2 28-32

SPARKS-WITHINGTON (See Sparton)

SPARTON (Also see Record Changer Listing)

- 4AW17 (Ch. 417) 50-18
4AW17-A (Ch. 417A) 49-22
5A116 (Ch. 5-16) 30-29
5AH06, 5A106 (See Model 5AW06) 4-17
5AW26-PS (Ch. 5-26-PS) 5-17
5AW06 (Ch. 5-06) 4-17
5AW16 (Ch. 5-16) 30-29
6AM06 (Ch. 6-06) 34-21
6AM26 (See Model 6AW26PA) 15-33
6AW26P (Ch. PC-5-6-26) 15-33
6-66A (Ch. 6-66A) 53-21
7AM46 (Ch. 7-46) 1-31
7AM46PA, 7BAM46PA, 7BW46PA (See Model 7AM46) 1-31
8AM46 (Ch. 8-46) 1-31
10AB76-PA, 10AM76-PA, 10BM76-PA (See Model 10BW76-PA) 15-34
10BW76-PA (Ch. 10-76PA) 15-34
11T210 (Ch. 23U214) 255-14
12A204 (Ch. 23U214) 255-14
12A210 (Ch. 23U214) 255-14
14A204 (Ch. 23U214) 255-14
17A203, 17A204 (Ch. 22V214B, 23U214B) 288-9
18A203, 18A204 (Ch. 22V214B, 23U214B) 288-9
19A203, 19A204 (Ch. 22V214B, 23U214B) 288-9
19A209, 19A210 (Ch. 22V214B, 23U214B) 288-9
20T203, 20T204 (Ch. 22V214B, 23U214B) 288-9
20T209, 20T210 (Ch. 22V214B, 23U214B) 288-9
20T403, 20T404 (Ch. 22V214B, 23U214B) 288-9
21T203, 21T204 (Ch. 22V214B, 23U214B) 288-9
22A403, 22A404 (Ch. 22V214B, 23U214B) 288-9
24T201, 24T202 (Ch. 22V174B, 23U174B) 288-9
24T301 (Ch. 22V174B) 288-9
100, 101 (Ch. 5A7) 38-23
102, 101, 104 (See Model 100) 38-23
121 (Ch. 8L9) 57-19
122 (See Model 121) 57-19
130, 132, 135, 139 (Ch. 5A10) 94-10
141 (See Model 121) 57-19
141 (Ch. 8L10) 92-6
141XX, 142XX (Ch. 8W10) 126-12
142 (See Model 121) 57-19
150, 151, 152, 155 (Ch. 4E10) 91-12
230 (Ch. 5A10, A) 210-10
232 (Ch. 5A10, A) 210-10
329 (Ch. 5A10, A) 210-10
301, 305, 309 (Ch. 4E3) 222-13
320C, 321C (Ch. 5B3C) 237-10
325C (Ch. 5B3C) 237-10
329C (Ch. 5B3C) 237-10
342, 345, 347 (Ch. 5C3) 222-13
350, 351 (Ch. 6L3) 197-9
1000, 1001, 1003 (Ch. 12L7) 60-18
1005, 1006, 1007, 1008 (Ch. 8-57) 41-28
1010 (Ch. 717) 29-25
1015 (See Model 10BW76PA) 15-34
1020, 1021, 1023 60-18
1030, 1030A (Ch. 6L8) 37-22
1031, A (See Model 1030) 37-22
1035, 1035A, 1036, 1036A, 1037, 1037A, 1039, 1040, 1041 (Ch. 9L8) 62-19
1040XX, 1041XX (Ch. 8W10) 126-12
1051, 1052 (Ch. 6B9) 58-21
1058, 1059, 1060, 1061, 1064 (Ch. 8L9) 57-19
1071 (See Model 121) 57-19
1072 (Ch. 9L8) 62-19
1080 (Ch. 9L8A) (See Model 4900-TV) 64-11
1080A (Ch. 8L10) (See Model 141A) 92-6
1081A (Ch. 8L10) (See Model 141A) 92-6
1085, 1086 (Ch. 8W10) 126-12
1090, 1091 (Ch. 8W10) 126-12
1210, 1211 (Ch. 8W10) (See Model 141XX) 126-12
1300, 1301 (Ch. 6L3) 197-12
4900TV (Ch. 24TV9C, 31TV9C, 918A) 64-11
4916, 4917, 4918 (Ch. 24T10, 31T10, 6510) 161-9
4920, 4921, 4922 (Ch. 24T10) 161-9
4935 (Ch. 23T10) 133-1A
4939TV, 4940TV, 4941TV (Ch. 24TV9, 31TV9) 64-11
4942 (Ch. 23T10) 133-1A
4944, 4945 (Ch. 31T10, 24T10) 86-10
4951, 4952 (See Model 4900TV) 64-11
4954 (Ch. 23T10) 133-1A
4960 (Ch. 23T10) 133-1A
4964, 4965 (Ch. 23T10) 157-11
4970, 4971, 4972 (Ch. 8510) 92-6
5002, 5003 (Ch. 23T10) 102-13
5006, 5007 (Ch. 23T10) 102-13
5006X (Ch. 25T10A) 121-13
5007X (Ch. 25T10A) 121-13
5010, 5011 (Ch. 19T510, A) 104-11
5014, 5015 (Ch. 19T510, A) 104-11

SPARTON-Cont.

- 5025 (Ch. 26S510) 128-13
5025BA (See PCB 22) 138-1 and Model 5025-Set 128-13
5026 128-13
5029, 5030 (Ch. 26S510D) 128-13
5035, 5036, 5037 (Ch. 26S5160L) 128-13
5052 (Ch. 24T10, 31T10) 97A-13
5056, 5057 (Ch. 19T510, A) 104-11
5064, 5065 (Ch. 23T10) 157-11
5068, 5069 (Ch. 24TV9C) (See Model 4900TV) 64-11
5071, 5072 (Ch. 19T510, A) 104-11
5075BA (See PCB 22) 138-1 and Model 5075-Set 128-13
5076 (Ch. 26S5160, B) 128-13
5076BA (See PCB 22) 138-1 and Model 5076-Set 128-13
5076BB 128-13
5077 128-13
5077BA (See PCB 22) 138-1 and Model 5077-Set 128-13
5078 128-13
5079 128-13
5079B (See PCB 22) 138-1 and Model 5079-Set 128-13
5080 (See PCB 22) 138-1 and Model 5080-Set 128-13
5082, 5083 (Ch. 26S5160, 26SD-170) (For TV Ch. see Model 141XX) 126-12
5082, 5083 (Ch. 26S5170X, XP) (For TV Ch. see PCB 22) 138-1 and Model 5082-Set 128-13
5083, 5086 (Ch. 2RD190, 25RD190) 139-14
5088, 5089, 5090 (Ch. 26S5160, 26SD170 and Radio Ch. 8W10) (For TV Ch. see Set 128-13, for Radio Ch. see Model 141XX) 126-12
5101, 5102, 5103 (Ch. 26S5170, P) (See PCB 22) 138-1 and Model 5025-Set 128-13
5104, 5105 (Ch. 26S5170D, P) (See PCB 22) 138-1 and Model 5025-Set 128-13
5152, 5153, 5154 (Ch. 26S5170, P) (See PCB 22) 138-1 and Model 5025-Set 128-13
5155, 5156, 5157 (Ch. 26SD170X, XP) (See PCB 22) 138-1 and Model 5025-Set 128-13
5158 (Ch. 26S5170, P) (See PCB 22) 138-1 and Model 5025-Set 128-13
5165X, 5166X (Ch. 26S5170) 166-13
5170, 5171 (Ch. 25SD201, 25D-201) 147-11
5175X (Ch. 26S5171) 166-13
5178X (Ch. 26S5171) 166-13
5182, 5183, 5189 (Ch. 26SD-170, P and Radio Ch. 8W10) (For Ch. 8W10 (See Model 5116) and Model 5025-Set 128-13, for Radio Ch. see Model 141XX) 126-12
5191, 5192 (Ch. 25SD201, 25D201) (See Model 5170) 147-11
5207, 5208 (Ch. 26S5172, A) 167-14
5210 (Ch. 26S5172B) 167-14
5212 (Ch. 21S172) 174-12
5220 (Ch. 26S5172C) 167-14
5225, 5226 (Ch. 26S5172C) 167-14
5240, 5241 (Ch. 21S212) 201-10
5250, 5252, 5253 (Ch. 21S172) 174-12
5262, 5263 (Ch. 26S5172, A) 167-14
5265 (Ch. 26S5172, A) 167-14
5267, 5268 (Ch. 26S5172, A) 167-14
5270 (Ch. 26S5172C) 167-14
5271 (Ch. 26S5172C) (See Model 5207) 167-14
5272, 5273 (Ch. 26S5172C) 167-14
5280, 5281 (Ch. 21S212) 201-10
5288, 5289 (Ch. 25CD202) 178-11
5290 (Ch. 25SD202) 178-11
5291, 5292, 5293, 5294, 5295 (Ch. 25CD202) 178-11
5296A, 5297A (Ch. 26CD202) 178-11
5296, 5297 (Ch. 25SD202) 178-11
5298 (Ch. 25CD202) 178-11
5299 (Ch. 25CD202) (See Model 5298) 178-11
5301 (Ch. 21S212) 201-10
5325 (Ch. 25D173A) 222-14
5325A (Ch. 27D173) 222-14
5326 (Ch. 25D173A) 222-14
5326A (Ch. 27D173) 222-14
5340, 5341 (Ch. 21S213) 201-10
5342 (Ch. 25D173) (See PCB 104) 222-14
5343 (Ch. 27D173) 222-14
5344 (Ch. 27D173) 222-14
5345 (Ch. 27D173) 222-14
5494 (Ch. 27D173) 222-14
5495 (

SPiegel (See Aircraft)

Table with 2 columns: Model number and price. Includes STARK 40-22, 410, 1010, 1020.

STARRETT

Table with 2 columns: Model number and price. Includes Gotham, Henry Hudson, John Hancock, etc.

STEELMAN

Table with 2 columns: Model number and price. Includes AF1100, BE20, BE21, BE22, etc.

STEWART-WARNER

Table with 2 columns: Model number and price. Includes AS1T1, A61CR1, A61CR2, etc.

STEWART-WARNER-Cont.

Table with 2 columns: Model number and price. Includes 27C-9310A, 27C-9350A, 51146, etc.

ST. GEORGE

Table with 2 columns: Model number and price. Includes 916, 917, 920, 921, etc.

STRATOVOX

Table with 2 columns: Model number and price. Includes 579-58A.

STROMBERG-CARLSON

Table with 2 columns: Model number and price. Includes AM-43, AM-48, AM-49, etc.

STROMBERG-CARLSON-Cont.

Table with 2 columns: Model number and price. Includes TV-125, IX1P22, IX2P22, etc.

SYLVANIA-Cont.

Table with 2 columns: Model number and price. Includes 1-177, 1-197, 1-97-1, etc.

SYLVANIA-Cont.

Table with 2 columns: Model number and price. Includes 172K, 172KU, 172M, etc.

NOTE: PCB Denotes Production Change Bulletin.

Production Change Bulletin Nos. 1 Through 63 Are All Contained in Set No. A-200

Denotes Television Receiver.

TRAV-LER—WESTINGHOUSE

TRAV-LER—Cont.

- 217-331 (Ch. 36B2) [See PCB 116—Set 268-1 and Model 217-15—Set 170-14]
- 217-371 (Ch. 36B2) [See PCB 116—Set 268-1 and Model 217-15—Set 170-14]
- 219-8A, 219-8B (Ch. 11A2) 162-14
- 220-9, 9A, 9B (Ch. 33A2) 171-11
- 220-22, 220-23 (Ch. 34A2) [See PCB 116—Set 268-1 and Model 217-15—Set 170-14]
- 220-26 (Ch. 34A2) [See PCB 116—Set 268-1 and Model 217-15—Set 170-14]
- 220-34, 220-35 (Ch. 36A2) [See PCB 116—Set 268-1 and Model 217-15—Set 170-14]
- 221-24 (Ch. 34A2) [See PCB 116—Set 268-1 and Model 217-15—Set 170-14]
- 221-27 (Ch. 35B2) [See PCB 116—Set 268-1 and Model 217-15—Set 170-14]
- 221-36 (Ch. 36A2) [See PCB 116—Set 268-1 and Model 217-15—Set 170-14]
- 317-33 (Ch. 36A3) [See PCB 116—Set 268-1 and Model 217-15—Set 170-14]
- 317-37 (Ch. 36A3) [See PCB 116—Set 268-1 and Model 217-15—Set 170-14]
- 317-44, A (Ch. 46B3) 240-10
- 317-47 (Ch. 46A3) 240-10
- 317-47, 47D, 47UC, 47U9 (Ch. 46A4, 46A4A, 47A3, 48A3, 48A4) [See PCB 129—Set 288-1 and Model 317-44—Set 240-10]
- 317-56 (Ch. 510A4) [See PCB 129—Set 288-1 and Model 317-44—Set 240-10]
- 317-60, 317-62 (Ch. 36A3) [See PCB 116—Set 268-1 and Model 217-15—Set 170-14]
- 317-67 (Ch. 36A3) [See PCB 129—Set 288-1 and Model 317-44—Set 240-10]
- 320-35 (Ch. 36A3) [See PCB 116—Set 268-1 and Model 217-15—Set 170-14]
- 321-36 (Ch. 36A3) [See PCB 116—Set 268-1 and Model 217-15—Set 170-14]
- 321-R45, -46, -46UC, -46U9 (Ch. 46A3, 46A4A, 47A3, 48A3, 48A4) [See PCB 129—Set 288-1 and Model 317-44—Set 240-10]
- 321-46, 321-48 (Ch. 46A3) 240-10
- 321-48-48U, -48UC, -48U9 (Ch. 46A4, 47A3, 48A3, 48A4, 49A4) [See PCB 129—Set 288-1 and Model 317-44—Set 240-10]
- 321-54, -54UC, -54U9 (Ch. 46A3, 46A4, 48A3, 48A4, 49A4) [See PCB 129—Set 288-1 and Model 317-44—Set 240-10]
- 321-55, -55UC, -55U9 (Ch. 46A3, 46A4, 48A3, 48A4, 49A4) [See PCB 129—Set 288-1 and Model 317-44—Set 240-10]
- 321-63 (Ch. 36A3) [See PCB 116—Set 268-1 and Model 217-15—Set 170-14]
- 321-75, -76 (Ch. 511A4) [See PCB 129—Set 288-1 and Model 317-44—Set 240-10]
- 321-460, -460UC, -460U9 (Ch. 46A3, 46A4, 46D4, 48A4, 49A4, 49D4) [See PCB 129—Set 288-1 and Model 317-44—Set 240-10]
- 321-480, -480UC, -480U9 (Ch. 46A3, 46A4, 46D4, 48A4, 49A4, 49D4) [See PCB 129—Set 288-1 and Model 317-44—Set 240-10]
- 321-540, -540UC, -540U9 (Ch. 46A3, 46A4, 46D4, 48A4, 49A4, 49D4) [See PCB 129—Set 288-1 and Model 317-44—Set 240-10]
- 321-770 (Ch. 511A4) [See PCB 129—Set 288-1 and Model 317-44—Set 240-10]
- 324-49 (Ch. 46C3, 46C4) [See PCB 129—Set 288-1 and Model 317-44—Set 240-10]
- 517-56 (Ch. 510A4) [See PCB 129—Set 288-1 and Model 317-44—Set 240-10]
- 517-67 (Ch. 510A4) [See PCB 129—Set 288-1 and Model 317-44—Set 240-10]
- 521-75, -76, -77, -78 (Ch. 511A4) [See PCB 129—Set 288-1 and Model 317-44—Set 240-10]
- 3210-60-60UC, -60U9 (Ch. 46A4, 46D4, 48A4, 49A4, 49D4) [See PCB 129—Set 288-1 and Model 317-44—Set 240-10]
- 3210-61, -61UC, -61U9 (Ch. 46A4, 46D4, 48A4, 49A4, 49D4) [See PCB 129—Set 288-1 and Model 317-44—Set 240-10]
- 5000 [See Model 50001—Set 11-27]
- 5001
- 5002 Series (Ch. 109) 12-28
- 5007, 5008, 5009 (Ch. 10A) 1-36
- 5010, 5011, 5012 (Ch. 105) 2-5
- 5015 36-25
- 5019 23-30
- 5020 (Ch. 800) 11-28
- 5021 43-20
- 5022 101-14
- 5027 31-30
- 5028 34-24
- 5029 33-29
- 5030, 5031 32-25
- 5036 54-19
- 5049 45-24
- 5051 32-26
- 5054 36-26
- 5056-A 90-12
- 5066 42-24
- 5091 25-12
- 5170 163-13
- 5180B, M 260-14
- 5182-B, -M 263-16

TRAV-LER—Cont.

- 5300 223-13
- 5301 224-15
- 5305 260-15
- 5310 243-12
- 5372 246-10
- 6040 49-25
- 6045 56-23
- 6053 (See Model 6050—Set 56-23)
- 7000, 7001 59-21
- 7003 (Ch. 501) 12-29
- 7014 59-21
- 7016, 7017 84-11
- 7023 83-13
- 7036 112-11
- 7053 262-14
- 9051, 9052 265-14
- 9060, 9061 265-14
- Ch. 11A2 (See Model 219-8A)
- Ch. 32A1 (See Model 62R50)
- Ch. 33A2 (See Model 217-15)
- Ch. 34A2 (See Model 217-15)
- Ch. 35B2 (See Model 217-27)
- Ch. 36A2 (See Model 217-32)
- Ch. 36A3 (See Model 317-33)
- Ch. 36B2 (See Model 217-33)
- Ch. 46A3 (See Model 317-47)
- Ch. 46A4 (See Model 317-47)
- Ch. 46B3 (See Model 317-44)
- Ch. 46C3, 46C4 (See Model 324-49)
- Ch. 46D4 (See Model 317-47)
- Ch. 47A3 (See Model 317-47)
- Ch. 48A3, 48A4 (See Model 317-47UC)
- Ch. 49A4, 49D4 (See Model 317-47U9)
- Ch. 104 (See Model 5007)
- Ch. 105 (See Model 5010)
- Ch. 109 (See Model 5002)
- Ch. 501 (See Model 7003)
- Ch. 510A4 (See Model 317-56)
- Ch. 511A4 (See Model 321-75)
- Ch. 800 (See Model 5021)

TRELA

- HW301 14-28

TRUETONE

- D1034A, B, C (See Model D1046A—Set 102-15)
- D1046A 102-15
- D1046B, C, D (See Model D1046A—Set 102-15)
- D1092 (Similar to Chassis) 108-7
- D123AA, B 189-15
- D123AB 187-12
- D1435A, D1436A 239-10
- D1612 28-34
- D1644 12-30
- D1645 (Factory 26A76-650) 6-33
- D1740 (D1748) 32-27
- D1752 (Factory 7901-14) 34-25
- D1835 (Factory Model 25A86-856) 46-24
- D1836, D1836A (Factory 26A85-856) 45-25
- D1840 (Fact. No. 138PCXK) 46-24
- D1845 31-31
- D1846A, B, C 40-23
- D1850 (Series A) 51-23
- D1949 60-20
- D1950, D1951 (See Model D1850—Set 51-23)
- D1952 (See Model D1949—Set 60-20)
- D1990 (Factory No. 74F22) 69-13
- D1991, B 77-11
- D1992 (Factory No. 74F22) 69-13
- D1993, B 77-11
- D1994, B 77-11
- D1996 (See Model D2983—Set 68-18)
- D2017, D2018 101-15
- D2020 106-15
- D2025A (Fact. Model 26A95-906) 83-14
- D2027A 97-18
- D2102A, B 200-11
- D2103A, B 200-11
- D2104A, D2109A 199-13
- D2145 197-13
- D2205 201-12
- D2214A 204-10
- D2226 196-16
- D2237A 196-15
- D2245 197-14
- D2263 190-14
- D2270 211-16
- D2325-A 205-11
- D2383 199-15
- D2385 206-27
- D2386, D2387, D2388 230-13
- D2389 231-16
- D2410A, D2411A, D2412A, D2413A, D2410B, D2411B, D2412B, D2413B 227-15
- D2418A, D2419A, D2420A 257-18
- D2483 261-14
- D2552A, D2553A 283-13
- D2556A 274-14
- D2560A 280-11
- D2562A, D2563A 287-15
- D2582 275-16
- D2603 (Factory No. 461) 13-33
- D2604 13-34
- D2605 (Factory Model 2AW2) 9-34
- D2606 65-15
- D2612 (Code SW-9022-G) 3-9
- D2613 13-37
- D2615 (Factory Model 6D110) 2-18
- D2616 (Factory Model 6D117) 2-18
- D2616-B 10-32
- D2619 (Factory No. 2701) 27-29
- D2620 4-28
- D2621 4-32
- D2622 14-30
- D2623 11-29
- D2624 (Factory 27D14-600) 2-6
- D2626 (Fact. No. 457-21) 52-22
- D2630 (Factory 27D14-602 Issue A) 1-10
- D2634 12-31
- D2640 (Factory No. 459) 43-21
- D2642 12-32
- D2644 (Factory No. 101C) 11-30
- D2645 4-39

TRUETONE—Cont.

- D2661 (Factory 4B19) 2-23
- D2663 (Ch. 4C1) 11-31
- D2665 (Factory 4B114 Series A) 22-31
- D2692 39-28
- D2709 (Factory No. 470) 27-30
- D2710 (Factory No. 24D22-6308) 23-31
- D2718 (Factory No. 227D14-638U) 23-32
- D2743 25-29
- D2745 (See Model D1645—Set 6-33)
- D2748 (Ch. 7156) 26-27
- D2806, D2807 (Factory Model 181) 44-26
- D2810 (Factory No. 24D24-7308B) 36-27
- D2815 48-25
- D2819 (Factory No. 26A82-738) 35-24
- D2851 38-28
- D2906 (Factory No. 189) 69-14
- D2907 69-14
- D2910 65-16
- D2919 (Fact. No. 6DF21) 59-22
- D2963 73-13
- D2983 68-18
- D2985 70-11
- D2987 69-13
- D3120A 203-12
- D3130A, B 203-13
- D3210A 190-15
- D3265A 189-16
- D3300 225-20
- D3311, D3352, D3353 224-16
- D3490 267-14
- D3503A, D3504A 282-15
- D3615 (Factory 25B22-606) 18-32
- D3619 (Factory SP110) 10-33
- D3630, D3630N 19-33
- D3720 26-29
- D3721 (Factory 1108X) 32-28
- D3722 (Fact. No. 472) 51-24
- D3809 (Factory No. 178) 43-22
- D3810 39-27
- D3811 (Fact. No. 1148X) 47-24
- D3840 49-26
- D3910 (Fact. Model 140611) 74-10
- D4118, B 200-12
- D4142A 142-14
- D4320 227-15
- D4320B 247-13
- D4321, A 29-16
- D4370 (Factory No. 5C12) 26-28
- D4730 (Factory 26C19-61) 7-28
- D4818 (Fact. No. 134DX) 45-26
- D4832 (Fact. No. 25C22-82) 47-25
- D4842 (Fact. No. 26C21-81) 50-21
- D1088A 105-11
- D21088B 145-14
- D21089A 113-10
- D21089B 136-14
- D21091 161-10
- D21093A, D21094A 19-12
- D21095 134-11
- D21185A (See Model D21185B—Set 154-13)
- D21185B 154-13
- D21185C, D (See PCB 43—Set 177-1 and Model D21185B—Set 154-13)
- D21185E (See PCB 43—Set 177-1 and Model D21185B—Set 154-13)
- D21190A, B 147-12
- D21192A 185-14
- D21230B 185-14
- D21230C, D, E (See PCB 98—Set 243-1 and Model D21230B—Set 185-14)
- D21230B (Also see PCB 59—Set 193-1) 185-14
- D21235A (Ch. 17MS345) 188-13
- D21235B, C, D, E (See PCB 74—Set 215-1 and Model D21235A—Set 188-13)
- D21303A 207-11
- D21315A 204-11
- D21315B (See PCB 117—Set 269-1 and Model D21315A—Set 204-11)
- D21316A 224-17
- D21325A 204-11
- D21325B (See PCB 117—Set 269-1 and Model D21325A—Set 204-11)
- D21326A 224-17
- D21330A (See PCB 98—Set 243-1 and Model D21230B—Set 185-14)
- D21331A, B 233-11
- D21331C, D (See Model D21331A—Set 233-11)
- D21336A 238-14
- D21344A, B (Ch. 21MS36C) 210-13
- D21352A 232-9
- D21353A (Series A Thru M) 244-12
- D21354A (Ch. 9210P) 194-13
- D21358A 242-10
- D21359A (Series A, C, D, E) 248-10
- D21411A, B, D 287-16
- D21415A (Ch. 21T16) 249-19
- D21416A (Ch. 21T16A) 249-19
- D21426A (Ch. 21T16A) 249-19
- D21430A (See PCB 98—Set 243-1 and Model D21230B—Set 185-14)
- D21430B (See Model D21430A) 260-16
- D21430C 260-16
- D21431A 260-15
- D22043A 161-10
- D22047B 161-10
- D22052 134-11
- D22053 120-11
- D22149A (Ch. 17AY212) 177-14
- D22152A (Ch. 17AY216) *
- D22215A (Ch. 21AY21A) 179-13
- D22219A 179-13
- D2222A (Ch. 21AY21A) 229-17
- D22301A, D22302A 204-11
- D22312A 204-11
- D22312B (See PCB 117—Set 269-1 and Model D22312A—Set 204-11)
- D22313A 224-17

TRUETONE—Cont.

- D22313C (Ch. 17T15) 249-19
- D22314A 204-11
- D22314B (See PCB 117—Set 269-1 and Model D22314A—Set 204-11)
- D22315A 224-17
- D22321A 204-11
- D22321B (See PCB 117—Set 269-1 and Model D22321A—Set 204-11)
- D22322A (For TV See PCB 117—Set 269-1 and Model D21315A—Set 204-11) For UHF Tuner See Model 3D6000—Set 221-12
- D22322B (See PCB 117—Set 269-1 and Model D21315A—Set 204-11)
- D22333A, B 203-14
- D22334A 233-11
- D22414A (Ch. 21T14) 249-19
- D22415A (Ch. 21T14A) 249-19
- D22422A (Ch. 17T8) 249-19
- D22422B (Ch. 17T4) 249-19
- D22423A, B, D22425A, D22426A 265-15
- D22431C 271-16
- D22433A (See PCB 98—Set 243-1 and Model D21230B—Set 185-14)
- 3D6000 Tel. UHF Conv. 221-12

ULTRADYNE

- TV-3 Tel. UHF Conv. 231-17

ULTRATONE

- L-46 4-21
- 400 253-16

UNITED MOTORS SERVICE (See Delco or Buick, Cadillac, Chevrolet, Oldsmobile and Pontiac)

U. S. TELEVISION

- C16030 99A-12
- C19031 99A-12
- T-10823 89-15
- T16030 99A-12
- T19031 99A-12
- 5A16, 5B16, 5C16 (See Model 5C66—Set 17-9)
- 5A66, 5B66, 5C66, 5D66MPA 24-30
- 5C66 Early 17-9
- 8-16M (Dumbarton) 26-29

UNITONE

- 88 5-26

UNIVERSAL CAMERA (See Record Changer Listing)

UTAH (See Record Changer Listing)

V-M (Also see Record Changer Listing)

- 110 191-19
- 121 242-11
- 121 243-14
- 150 139-15
- 150A 213-9
- 151 231-20
- 160 187-13
- 555-M, -O 235-13
- 560-B, -M 270-17
- 970 269-15
- 972 159-15
- 975 203-15
- 980 165-16
- 985 138-12
- 986 247-14
- 990 248-11
- 1001-A 10-34

VAN-CAMP

- 576-1-6A 7-29

VIDEO CORP. OF MARYLAND (See Videole)

VIDEODYNE

- 10FM, 10TV, 12FM, 12TV 69-15

VIDEOLA

- VS-160, VS-161 92-9
- VS-165, VS-166, VS-167, VS-168 92-9

VIDEO PRODUCTS (Also see Sheraton)

- 530-DX Series 213-10
- 630-DXC 176-13
- 630-DX2AC 176-13
- 630-K3C 176-13
- 630-K24C 176-13

VIEWTONE

- RC-201A, RRC-201 11-32

VISION MASTER

- 14MC, MT (Similar to Chassis) 117-8
- 16MC, 16MT, 16MXX, 16MXCS, 16MXT, 16MXTS (Similar to Chassis) 117-8
- 17MC, 17MT, 17MXX, 17MXCS, 17MXT, 17MXTS (Similar to Chassis) 117-8

VIZ

- RS-1 14-31

VOCATRON

- CC-20 (D) 246-11
- CC-45 247-15

VOGUE

- 532 A-P 11-33
- Ch. Models 533R, 554R 8-32

WALSICO

- 2000 (Tel. UHF Conv.) 261-16

WARWICK (See Clarion)

WATTERSON

- ARC-4591A 16-36
- PA-4585, APA-4587 3-2
- RC-4581 16-35
- 4581 3-32
- 4582 6-34
- 4784 24-31
- 4790 16-34
- 4800 43-23

WAVEFORMS

- A-20 191-20
- C-5 191-20

WEBCOR (See Webster-Chicago)

WEBSTER-CHICAGO (Also see Changer and Recorder Listings)

- B-123-1 204-12
- B-124-1 203-16
- B-134-1 205-12
- B-135-1 207-12
- D-300-1 255-16
- F-123-1 204-12
- F-134-1 205-12
- F-136-1 207-12
- F-136-1 207-12
- 666-1A 34-26
- 100-608 121-14
- 100-621 113-11
- 129-1, 129-2 215-13
- 130 119-13
- 166 55-22
- 181-1R 221-13
- 288 117-14
- 333-1, 333-2 250-22
- 362 105-12
- 760 112-12
- 762 105-12
- 1024 (See Model B-124-1—Set 203-16)
- 1034 (See Model B-134-1—Set 205-12)
- 1035 (See Model B-135-1—Set 210-14)
- 1036 (See Model B-136-1—Set 207-12)

WEBSTER ELECTRIC (Also see Recorder Listing)

- RFM-1, 2 263-17
- WCMI-1, WCS1-1 268-15
- 81-15, 81-15A 142-15
- 82-25, 82-25A, 83-25 143-15
- 84-25 145-12
- 85-25 144-14
- 6054, S, 606M, S 260-17
- 610M, S 260-17
- 906 231-18
- 1105M 226-10

WEBSTER (Telephone)

- W606M 56-24
- 604M 57-23

WELLS-GARDNER

- WG-30A8-A-496 246-12
- 317G534C-218 (Also See PCB 84—Set 225-11) 195-12
- 317G534C-220 (Also See PCB 84—Set 225-11) 195-12
- 317G534C-278 (Also See PCB 84—Set 225-11) 195-12
- 321AM49-A-436 278-13
- 321AM49-A-470 278-13
- 321AM51-A-432, 321AM51-A-486 278-13
- 321GM44-A-462, -464, 321GM44-B-462, -464 266-18
-

WESTINGHOUSE—ZENITH

WESTINGHOUSE—Cont.

- H-866T21B [Ch. V-2313-15, -25, -35] (Also See PCB 127—Set 286-1) (See Model H-270-18)
H-866T21A [Ch. V-2323-101, -122, -124, -201, -301] (Also See PCB 127—Set 286-1) (See Model H-270-18)
H-866T21A [Ch. V-2273-32] (See Model H-769T21—Set 253-17)
H-866T21B [Ch. V-2323-101, -122, -124, -201, -301] (Also See PCB 127—Set 286-1) (See Model H-270-18)
H-867T21 [Ch. V-2313-15, -25, -35] (Also See PCB 127—Set 286-1) (See Model H-270-18)
H-867T21B [Ch. V-2312] 281-10
H-867T21C [Ch. V-2323-101, -122, -124, -201, -301] (Also See PCB 127—Set 286-1) (See Model H-270-18)
H-868T21 [Ch. V-2313-15, -25, -35] (Also See PCB 127—Set 286-1) (See Model H-270-18)
H-868T21A [Ch. V-2322] 281-10
H-868T21B [Ch. V-2323-101, -122, -124, -201, -301] (Also See PCB 127—Set 286-1) (See Model H-270-18)
H-869K24 [Ch. V-2314-15, -25] 274-16
H-869K24 [Ch. V-2324-203] 274-16
H-870K24 [Ch. V-2314-15, -25] 274-16
H-870K24 [Ch. V-2324-203] 274-16
H-871T21 [Ch. V-2313-15, -25, -35] (Also See PCB 127—Set 286-1) (See Model H-270-18)
H-871T21 [Ch. V-2323-101, -122, -124, -201, -301] (Also See PCB 127—Set 286-1) (See Model H-270-18)
H-872T21 [Ch. V-2313-15, -25, -35] (Also See PCB 127—Set 286-1) (See Model H-270-18)
H-872T21A [Ch. V-2323-101, -122, -124, -201, -301] (Also See PCB 127—Set 286-1) (See Model H-270-18)
H-873T21 [Ch. V-2313-15, -25, -35] (See Model H-838K21B—Set 270-18)
H-873T21A [Ch. V-2263-35] (See Model H-769T21—Set 253-17)
H-873T21B [Ch. V-2323-101, -122, -124, -201, -301] (See Model H-838K21B—Set 270-18)
H-873T21A [Ch. V-2273-32] (See Model H-769T21—Set 253-17)
H-875T24, A, C [Ch. V-2314-15, -25] 274-16
H-875T24, B [Ch. V-2324-203] 274-16
H-876T24 [Ch. V-2314-15, -25] 274-16
H-876T24, A [Ch. V-2314-15, -25] 274-16
H-877T24, A [Ch. V-2314-15, -25] 274-16
H-877T24, A [Ch. V-2324-203] 274-16
H-878K24, B [Ch. V-2314-15, -25] 274-16
H-878K24, B [Ch. V-2324-203] 274-16
H-879T21 (S), (V) [Ch. V-2312] 281-10
H-879T21 (S), (V) [Ch. V-2322] 281-10
H-880T21 (S), (V) [Ch. V-2312] 281-10
H-880T21 (S), (V) [Ch. V-2322] 281-10
H-881K24 [Ch. V-2314-15, -25] 274-16
H-881K24 [Ch. V-2324-203] 274-16
H-1251 [Ch. V-2102 (See Model H-104)
Ch. V-2102-1 (See Model H-138)
Ch. V-2103 (See Model H-153)
Ch. V-2103-3 (See Model H-214)
Ch. V-2107 (See Model H-313)
Ch. V-2118 (See Model H-161)
Ch. V-2119-1 (See Model H-164)
Ch. V-2120 (See Model H-165)
Ch. V-2122 (See Model H-157)
Ch. V-2123 (See Model H-178)
Ch. V-2124-1 (See Model H-169)
Ch. V-2127 (See Model H-183)
Ch. V-2128, V-2128-1 (See Model H-182)
Ch. V-2128-2 (See Model H-202)
Ch. V-2130-1 (See Model H-196)
Ch. V-2130-11DX (See Model H-196A (DX))
Ch. V-2130-21DX, -22DX [See Model H-207A (DX)]
Ch. V-2130-31DX, -32DX [See Model H-225 (DX)]
Ch. V-2131, V-2131-1 (See Model H-185)
Ch. V-2132 (See Model H-186M)
Ch. V-2133 (See Model H-188)
Ch. V-2134 (See Model H-190)
Ch. V-2136 (See Model H-3077)
Ch. V-2136-1 (See Model H-316C7)
Ch. V-2136-2 (See Model H-3247)
Ch. V-2136-4 (See Model H-328C7)
Ch. V-2136-5R (See Model H-3347UR)
Ch. V-2137-5U (See Model H-3347UR)
Ch. V-2137 (See Model H-203)
Ch. V-2137-1 (See Model H-199)
Ch. V-2137-2 (See Model H-198)
Ch. V-2137-3, V-2137-3S [See Model H-234]
Ch. V-2144, V-2144-1 (See Model H-210)
Ch. V-2146-05 (See Model H-216)
Ch. V-2146-11DX (See Model H-217)
Ch. V-2146-21DX, -25DX [See Model H-224]
Ch. V-2146-35DX (See Model H-217B)
Ch. V-2146-45 (See Model H-216)
Ch. V-2148 (See Model H300T5)
Ch. V-2149 (See Model H-217B)
Ch. V-2149-1 (See Model H-216)
Ch. V-2149-2 (See Model H-231)

WESTINGHOUSE—Cont.

- Ch. V-2149-3 (See Model H-603C-12)
Ch. V-2150-01, V-2150-02 (See Model H-223)
Ch. V-2150-31 (See Model H-242)
Ch. V-2150-41 (See Model H-601K-12)
Ch. V-2150-51 (See Model H-231)
Ch. V-2150-61, A, B (See Model H-600T16)
Ch. V-2150-81, -82, -84 (See Model H-215)
Ch. V-2150-91A (See Model H-604-T10)
Ch. V-2150-94C (See Model H-609T10)
Ch. V-2150-101 (See Model H-605T12)
Ch. V-2150-111, A (See Model H-606K12)
Ch. V-2150-136 (See Model H-610T12)
Ch. V-2150-146 (See Model H-613K16)
Ch. V-2150-176, U (See Model H-617T12)
Ch. V-2150-177U (See Model H-617T12)
Ch. V-2150-186, A, C, CA (See Model H-618T16)
Ch. V-2150-197 (See Model H-625T12)
Ch. V-2151-1 (See Model H-302P5)
Ch. V-2152-01 (See Model H-603C-12)
Ch. V-2152-16 (See Model H-611C12)
Ch. V-2153 (See Model H303P4)
Ch. V-2153-1 (See Model H-312P4)
Ch. V-2156 (See Model H-309P5)
Ch. V-2156-1U (See Model H-342-PSU)
Ch. V-2156-2 (See Model H-405P5)
Ch. V-2157, U (See Model H-318T5)
Ch. V-2157-1, -1U (See Model H-321T5)
Ch. V-2157-2, -2U (See Model H-323T5)
Ch. V-2157-3U (See Model H-327U6)
Ch. V-2157-4U (See Model H338-T5U)
Ch. V-2157-5 (See Model H-355T5)
Ch. V-2157-6 (See Model H-359T5)
Ch. V-2157-8 (See Model H-367T5)
Ch. V-2157-9 (See Model H-374T5)
Ch. V-2157-10 (See Model H-382T5)
Ch. V-2157-11 (See Model H-385T5)
Ch. V-2157-12 (See Model H-388T5)
Ch. V-2157-13 (See Model H-420T5)
Ch. V-2157-14 (See Model H-391T5)
Ch. V-2161, V-2161U (See Model H-310T1)
Ch. V-2164, U (See Model H-331P4)
Ch. V-2164-2 (See Model H-400P4)
Ch. V-2171 (See Model H-627K16)
Ch. V-2172 (See Model H-626T16)
Ch. V-2173 (See Model H-633C17)
Ch. V-2175 (See Model H-636T17)
Ch. V-2175-1 (See Model H-641-K17)
Ch. V-2175-3, -4 (See Model H-640T17)
Ch. V-2175-5 (See Model H-641K17)
Ch. V-2176 (See Model H-630T14)
Ch. V-2177 (See Model H-637T14)
Ch. V-2178, -1, -3 (See Model H-638K20)
Ch. V-2180-1 (See Model H350T7)
Ch. V-2180-2 (See Model H-354C7)
Ch. V-2180-3 (See Model H-660C17)
Ch. V-2180-5 (See Model H-357C10)
Ch. V-2180-8 (See Model H-370T7)
Ch. V-2180-9, -10 (See Model H-730T11)
Ch. V-2180-13 (See Model H-669R12)
Ch. V-2181-1 (See Model H-361T6)
Ch. V-2181-2 (See Model H-393T6)
Ch. V-2182-2 (See Model H-414R4)
Ch. V-2184-1 (See Model H-378T5)
Ch. V-2184-2 (See Model H-447T4)
Ch. V-2184-4 (See Model H-471T5)
Ch. V-2184-6 (See Model H-499T5)
Ch. V-2185-1 (See Model H-409P4)
Ch. V-2186-1 (See Model H-417T5)
Ch. V-2188-1 (See Model H-422P4)
Ch. V-2189-2 (See Model H-434T5)
Ch. V-2189-4 (See Model H-443T5)
Ch. V-2192, -1 (See Model H-639T17)
Ch. V-2192, -3, -4, -5, -6 (See Model H-640T17A)
Ch. V-2194, V-2194A, V-2194-1 (See Model H-642K20A)
Ch. V-2194-2, -3 (See Model H-652K20)
Ch. V-2200-1 (See Model H-651-K17)
Ch. V-2201-1 (See Model H-652-K20)
Ch. V-2202-2 (See Model H-653K20)
Ch. V-2203-1 (See Model H-660C17)
Ch. V-2204-1 (See Model H-659T17)
Ch. V-2206-1 (See Model H-665T16)
Ch. V-2207-1 (See Model H-705T16)
Ch. V-2210-1 (See Model H-653K24)
Ch. V-2214-1 (See Model H-689T16)
Ch. V-2215-1 (See Model H-681T17)
Ch. V-2216-1 (See Model H-667T17)
Ch. V-2216-2, -3 (See Model H-678K17)
Ch. V-2216-4, -5 (See Model H-704T17)

WESTINGHOUSE—Cont.

- Ch. V-2217-1 (See Model H-673K21)
Ch. V-2217-2, -3 (See Model H-692T17)
Ch. V-2217-4, -5 (See Model H-71044RZ)
Ch. V-2218-1, -2, 11 (See Model H-730C21)
Ch. V-2218-1 (See Model H-688K24)
Ch. V-2220-1 (See Model H-708K20)
Ch. V-2220-2 (See Model H-718K20)
Ch. V-2220-3, -11 (See Model H-708T20)
Ch. V-2227-1 (See Model H-738T17)
Ch. V-2227-2 (See Model H-739T17)
Ch. V-2229-5 (See Model H-482PR5)
Ch. V-2232-2 (See Model H-737T17)
Ch. V-2233-1 (See Model H-740T17)
Ch. V-2233-2 (See Model H-751T17)
Ch. V-2233-3 (See Model H-750T17)
Ch. V-2233-4 (See Model H-746K21)
Ch. V-2235-1 (See Model H-469R12)
Ch. V-2236-1 (See Model H-475T5)
Ch. V-2236-2 (See Model H-486T5)
Ch. V-2250-1 (See Model H-795R21)
Ch. V-2250-4 (See Model H-815T24)
Ch. V-2263-11, -12, -13, -14 (See Model H-830K21)
Ch. V-2263-15 (See Model H-827T21)
Ch. V-2263-22 (See Model H-834K21)
Ch. V-2263-35 (See Model H-836T21)
Ch. V-2273-111, -122, -124, -132, -134 (See Model H-830K21)
Ch. V-2273-222 (See Model H-834K21)
Ch. V-2273-322 (See Model H-836T21)
Ch. V-2273-324 (See Model H-833T21)
Ch. V-2284-15 (See Model H-840C15)
Ch. V-2310 (See Model H-799T17)
Ch. V-2312 (See Model H-867T21)
Ch. V-2313-15, -25, -35 (See Model H-838K21B)
Ch. V-2314-15, -25 (See Model H-853K24)
Ch. V-2320 (See Model H-799T17)
Ch. V-2322 (See Model H-867T21)
Ch. V-2323-101, -122, -124, -201, -301 (See Model H-833K21B)
Ch. V-2324-203 (See Model H-853K24)
Ch. V-11213 (See Model H-802)
Ch. V-11900-1, -2, -3, -4, -5 (See Model H-802)
WILCOX-GAY (Also see Majestic) (Also see Recordio)
G-306, G-402, G-403, G-404 (See Model H-1272—Set 108-7)
G-414 (See Majestic Model G-414—Set 133-8)
G-426, G-427 (See Majestic Model 1272—Set 108-7)
G-614, G-624 (See Majestic Model G-614—Set 133-8)
G-914 (See Majestic Model G-414—Set 133-8)
OD-446M (OD Series) 101-17
OF439-1-C (Ch. OF Series) 98-13
OD Series (See Model OD-446M)
400A, B, C 242-12
WILLYS-OVERLAND
8032 (670777) 50-23
670777 (See Model 8030—Set 50-23)
677012 156-14
679517 172-12
WILMAK
W-446 "DENchum" 21-11
WIRE RECORDING CORP. (See Recorder Listing)
WOOLAROC
3-1A (Ch. 6-9022-J), 3-2A (Ch. 6-9022-K) 6-37
3-3A (Code 7-9002-D) 6-38
3-5A 22-32
3-6A/5 24-32
3-9A, 3-10A 7-30
3-11A (Ch. 56A76) 23-33
3-13A, 3-14A, 3-15A, 3-16A 34-28
3-17A, 3-18A 34-29
3-20A 24-33
3-29A 7-31
3-61A (See Model 3-71A—Set 36-29)
3-70A 31-34
3-71A 36-29
ZENITH (Also see Record Changer Listing)
G500 (Ch. 5G40) 83-16
G503 (Ch. 5G41) 99-19
G510, G510Y (Ch. 5G02) 84-14
G511, G511W, G511Y (Ch. 5G01) 85-15
G516 (Ch. 5G03) 86-14
G615, G615W, G615Y (Ch. 6G05) 86-14
G660, G663, G665 (Ch. 6G01) 96-12
G723 (Ch. 7G04) 104-13
G724 (Ch. 7G02) 103-18
G725 (Ch. 7G01) 101-18
G881, G882, G883, G884, G885 (Ch. 8G20) 98-16
G-2322 (Ch. 23G22) 98-17
G-2322Z (Ch. 23G24) (See Ch. 23G24—Set 91A-13)


ZENITH—Cont.

- G-2322Z (Ch. 23G24Z1) (See Ch. 23G24—Set 91A-13)
G-2327Z (Ch. 23G24) (See Ch. 23G24—Set 91A-13)
G-2340RZ (Ch. 23G24) 98-17
G-2340Z (Ch. 23G24) (See Ch. 23G24—Set 91A-13)
G-2340Z1, G-2340Z2 (Ch. 23G24Z1) (See Ch. 23G24—Set 91A-13)
G-2346R (Ch. 23G22) 98-17
G-2350RZ, Z (Ch. 23G24) (See Ch. 23G24—Set 91A-13)
G-2353EZ (Ch. 23G24) (See Ch. 23G24—Set 91A-13)
G-2353EZ1 (Ch. 23G24Z1) (See Ch. 23G24—Set 91A-13)
G-2356EZ (Ch. 23G24) (See Ch. 23G24—Set 91A-13)
G-2420E (Ch. 24G20) 93-11
G-2420-EOX (Ch. 24G20-OX) 93-11
G-2420R (Ch. 24G20) 93-11
G-2420-ROX (Ch. 24G20-OX) 93-11
G-2437RZ, G-2438RZ, Z, G-2439RZ (Ch. 24G26) (See Ch. 24G26—Set 91A-12)
G-2441 (Ch. 24G24) 98-17
G-2441R (Ch. 24G22/24) 98-17
G-2441RZ, Z (Ch. 24G26) (See Ch. 24G26—Set 91A-12)
G-2441RZ1, G-2441RZ2 (Ch. 24G26-Z1) (See Ch. 24G26—Set 91A-12)
G-2442E, R (Ch. 24G22/24) 98-17
G-2442RZ (Ch. 24G26) (See Ch. 24G26—Set 91A-12)
G-2442E1, G-2442R1 (Ch. 24G-26Z1) (See Ch. 24G26—Set 91A-12)
G-2448R (Ch. 24G22/24) 98-17
G-2448RZ (Ch. 24G26) (See Ch. 24G26—Set 91A-12)
G-2448RZ1 (Ch. 24G26Z1) (See Ch. 24G26—Set 91A-12)
G-2454R (Ch. 24G21) 93-11
G-2454-ROX (Ch. 24G21-OX) 93-11
G-2854A OX (Ch. 28F20) (See Model 28T96—Set 64-15)
G-2951, R, OX, ROX, G-2952, R, ROX (Ch. 29G20, -OX) 95-8
G-2957, R (Ch. 23G23 and Radio Ch. 6G20) 98-17
G-2958R (Ch. 23G23 and Radio Ch. 6G20) 98-17
G-3059R (Ch. 24G23/25 and Radio Ch. 6G20) 98-17
G-3062 (Ch. 24G23/25 and Radio Ch. 6G20) 98-17
G-3157RZ, Z (Ch. 23G24 and Radio Ch. 8G20/22) (See Ch. 23G24 and Ch. 8G20/22—Set 91A-13)
G-3157Z1, G-3157Z2 (Ch. 23G24Z1 and Radio Ch. 8G22) (See Ch. 23G24 and Ch. 8G20/22—Set 91A-13)
G-3158RZ (Ch. 23G24 and Radio Ch. 8G20/22) (See Ch. 23G24 and Ch. 8G20/22—Set 91A-13)
G-3158RZ1 (Ch. 23G24Z1 and Radio Ch. 8G22) (See Ch. 23G24 and Ch. 8G20/22—Set 91A-13)
G-3173RZ, Z, G-3174RZ (Ch. 23G24 and Radio Ch. 8G20/22) (See Ch. 23G24 and Ch. 8G20/22—Set 91A-13)
G-3259RZ (Ch. 24G26 and Radio Ch. 8G20/22) (For TV Ch. see Ch. 24G26—Set 91A-12, For Radio Ch. see Ch. 8G20/22—Set 91A-13)
G-3259RZ1 (Ch. 24G26Z1 and Radio Ch. 8G22) (For TV Ch. see Ch. 24G26—Set 91A-12, For Radio Ch. see Ch. 8G20/22—Set 91A-13)
G-3262Z (Ch. 24G26 and Radio Ch. 8G20/22) (For TV Ch. see Ch. 24G26—Set 91A-12, For Radio Ch. see Ch. 8G20/22—Set 91A-13)
G-3262Z1 (Ch. 24G26Z1 and Radio Ch. 8G22) (For TV Ch. see Ch. 24G26—Set 91A-12, For Radio Ch. see Ch. 8G20/22—Set 91A-13)
G-3275RZ (Ch. 24G26 and Radio Ch. 8G20/22) (For TV Ch. see Ch. 24G26—Set 91A-12, For Radio Ch. see Ch. 8G20/22—Set 91A-13)
H401, G (Ch. 4H40) 156-15
H500 (Ch. 5H40) 152-12
H503, Y (Ch. 5H41) 151-12
H511, H511W, H511Y (Ch. 5H01) 147-13
H615 (Ch. 6G05) 140-14
H615Z1 (Ch. 6G05Z1) 178-16
H661E, H661R (Ch. 6H01) 125-13
H664 (Ch. 6H02) 149-15
H665, R, Z (Ch. 6H01) 152-13
H723 (Ch. 7H04) 122-12
H723Z (Ch. 7H04Z) 134-14
H723Z1 (Ch. 7H04Z1) (See Model H724Z1—Set 163-14)
H723Z2 (Ch. 7H04Z2) 146-15
H724 (Ch. 7H02) 126-15
H724Z (Ch. 7H02Z) (See Model H723Z—Set 134-14)
H724Z1 (Ch. 7H02Z1) 163-14
H724Z2 (Ch. 7H02Z2) 178-17
H725 (Ch. 7G01Z) 135-15
H880, H880R (Ch. 8H20 Revised) 127-14
H880RZ (Ch. 8H20) 114-12
H1083E (Ch. 10H20) (See Model H3467R—Set 120-13)
H1086R, H-1087R (Ch. 10H20) (See Model H3467R—Set 120-13)
H2029R, H2030E, H2030R (Ch. 20H20) 144-15
H2041R (Ch. 20H20) 144-15
H-2052R, H2053E (Ch. 20H20) 144-15
H2226E, R, H2227E, H2227R (Ch. 22H20) 114-13
H2229R, H2230E, R (Ch. 22H21) 151-13
H2242E, R (Ch. 22H22) 151-13
H2250R (Ch. 22H20) 114-13
H2252R, H2253E (Ch. 22H21) 151-13
H2254R (Ch. 22H22) 151-13
H2255E (Ch. 22H20) 114-13
H2328E, EZ, R, RZ (Ch. 23H22, Z) 118-11
H2329R, RZ (Ch. 23H22, Z) (See Model H2328EZ—Set 118-11)
H2330E, R (Ch. 23H22) (See Model H2328E—Set 118-11)
H2341R (Ch. 23H22) (See Model H2328E—Set 118-11)
H2352R, RZ, H2353E, EZ, Ch. 23H22, Z 118-11
H2436G (Ch. 24H21) (See Model H3477R—Set 120-13)
H2437E, H-2438R, H-2439R (Ch. 24H20) 120-13
H2443R (Ch. 24H20) (See Model H3477E—Set 120-13)
H2445R (Ch. 24H21) 120-13
H2447R (Ch. 24H21) 120-13
H2449E (Ch. 24H20) 120-13
H2868R (Ch. 20H20 and Radio Ch. 8H20Z) (For TV Ch. see Model H-2029R—Set 144-15, For Radio Ch. see Model H2229R—Set 151-13, For Radio Ch. see Model H880—Set 168-14)
H3074 (Ch. 20H20 and Radio Ch. 10H20Z) (For TV Ch. see Model H2229R—Set 144-15, For Radio Ch. see Model H2229R—Set 151-13)
H3168R (Ch. 23H22 and Radio Ch. 8H20) (For TV Ch. see Model H2328E—Set 118-11, For Radio Ch. see Model H880RZ—Set 114-12)
H3267, R (Ch. 24H20 and Radio Ch. 8H20) (For TV Ch. see Set 120-13, For Radio Ch. see Model H880RZ—Set 114-12)
H3273E, H3274R (Ch. 22H21 and Radio Ch. 10H20Z) 151-13
H3284R (Ch. 22H22 and Radio Ch. 10H20Z) 151-13
H3467R (Ch. 24H20 and Radio Ch. 10H20Z) 151-13
H3477E (Ch. 24H20 and Radio Ch. 10H20Z) (See Model H3467R—Set 120-13)
H3477E (Ch. 24H21 and Radio Ch. 10H20Z) 120-13
H3478E (Ch. 24H21 and Radio Ch. 10H20Z) 120-13
H3478E (Ch. 24H21 and Radio Ch. 10H20Z) 120-13
H3490EQ (Ch. 24H21 and Radio Ch. 10H20Z) (For TV Ch. see Model H2445R—Set 120-13, For Radio Ch. see Model H3273E—Set 151-13)
HF1A, E (Ch. 3M02) 270-19
HF15E, R (Ch. 3M02) 270-19
HFMI184E (Ch. 11M20) 267-15
HM18190R (Ch. 11M20) 267-15
HFRI1A, E (Ch. 3M02) 270-19
HFRI1E, E (Ch. 3M02) 270-19
HFR-20E (Ch. 5R20) 272-16
HFR-21R (Ch. 5R20) 272-16
HFR1283E (Ch. 12R20) 281-11
HFR1284E (Ch. 12R21) 281-11
HFR1286R (Ch. 12R20) 281-11
HFR1290R (Ch. 12R21) 281-11
J402 (Ch. 4J40) 178-18
J420T (Ch. 4J60T) 185-16
J504 (Ch. 5J41) 176-12
J514 (Ch. 5J03) 176-14
J615, F, G, W, Y (Ch. 6J05) 182-16
J616 (Ch. 6J03) 179-14
J644, J665E, R (Ch. 6J02) 172-13
J733, G, R, Y (Ch. 7H02) 186-17
J880, J880R (Ch. 8H20Z), 168-14
J1083E, EZ (Ch. 10H20Z) (See Model H3273E—Set 151-13)
J1086, R, RZ (Ch. 10H20Z) (See Model H2273E—Set 113-13)
J1087, Z (Ch. 10H20Z) (See Model H3273E—Set 151-13)
J2026E (Ch. 20J21) 159-18
J2027E, R, J2029E, R, J2030E, R (Ch. 20J21) 159-18
J2031R (Ch. 20J21) (See Model J2026E—Set 159-18)
J2032R (Ch. 20J21) (See Model J2051E—Set 159-18)
J2040E, J2042R, J2043R, J2044E, R (Ch. 20J21) 159-18
J2049R (Ch. 20J21) (See Model J2027E—Set 159-18)
J2050R (Ch. 20J21) (See Model J2027E—Set 159-18)
J2051E, J2053R, J2054R, J2055R (Ch. 20J21) 159-18
J2126R (Ch. 21J21) 159-18
J2127E, R, J2129E, R, J2130E, R (Ch. 21J20) 159-18
J2140E, J2142R, J2143R, J2144E, R (Ch. 21J20) 159-18
J2151E, J2153R, J2154R, J2155R (Ch. 21J21) 159-18
J2868R (Ch. 20J21 and Radio Ch. 8H20Z) (For TV Ch. see Set 159-18, For Radio Ch. see Model H880—Set 168-14)
J2968R (Ch. 21J20 and Radio Ch. 8H20Z) (For TV Ch. see Set 159-18, For Radio Ch. see Model H880—Set 168-14)
J3069E (Ch. 20J21 and Radio Ch. 10H20Z) (For TV Ch. see Set 159-18, For Radio Ch. see Model H3273E—Set 151-13)
J3169E (Ch. 21J20 and Radio Ch. 10H20Z) (For TV Ch. see Set 159-18, For Radio Ch. see Model H3273E—Set 151-13)

ZENITH—Cont.

- H2226E, R, H2227E, H2227R (Ch. 22H20) 114-13
H2229R, H2230E, R (Ch. 22H21) 151-13
H2242E, R (Ch. 22H22) 151-13
H2250R (Ch. 22H20) 114-13
H2252R, H2253E (Ch. 22H21) 151-13
H2254R (Ch. 22H22) 151-13
H2255E (Ch. 22H20) 114-13
H2328E, EZ, R, RZ (Ch. 23H22, Z) 118-11
H2329R,

How to "tame" a TV Sync Circuit *FAST*

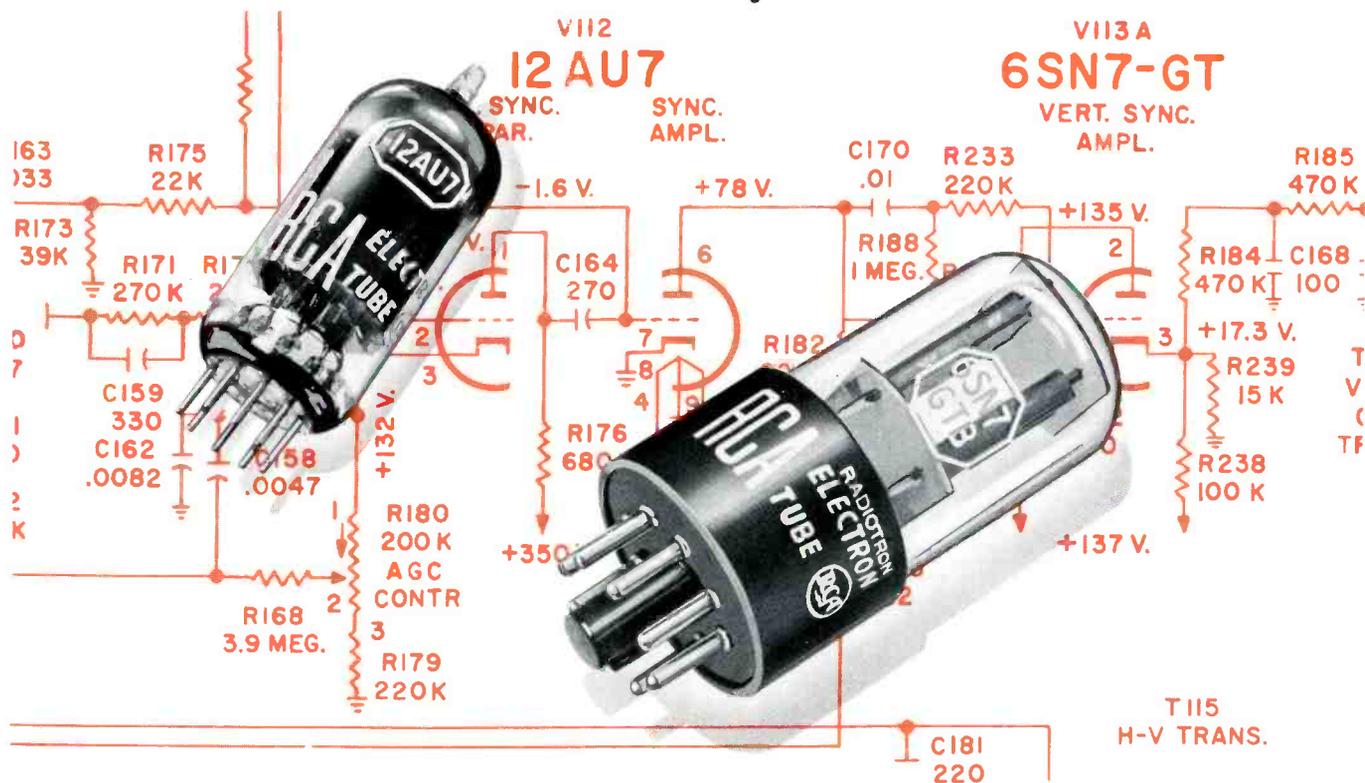


Use RCA Tubes with Built-In Quality!

For instance, RCA-12AU7's and 6SN7-GTB's are known for their close manufacturing tolerances. Microphonics are minimized. Plate current cutoff is closely controlled. Result: High tube stability—even during variations in heater voltages!

It's a fact—you can rely on RCA Tubes to give your customers stable TV pictures. That's because RCA Tubes are designed and manufactured specifically to meet the close tolerance requirements of TV circuitry.

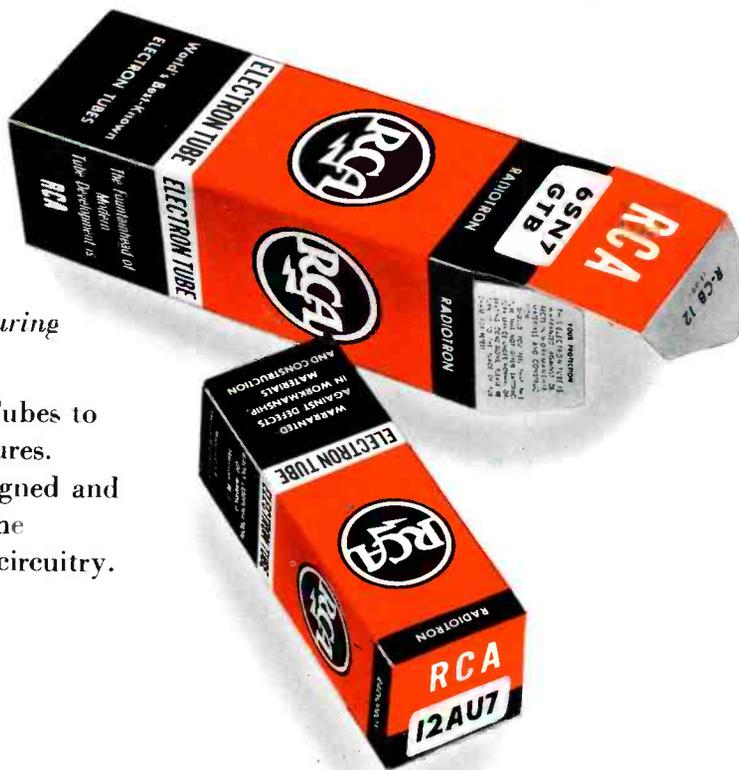
So, insist on RCA Receiving Tubes for *all* your service work.




RADIO CORPORATION of AMERICA
ELECTRON TUBES

HARRISON, N.J.

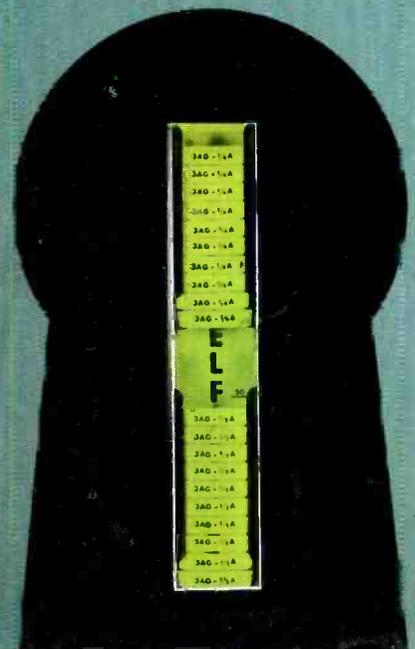
First Choice for TV Circuits... dependable RCA Tubes




IT'S NO SECRET

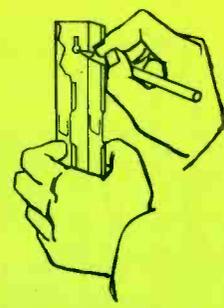

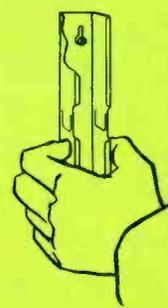
1. Determine the most handy location above or near your work bench. Using one channel as a guide locate the position of the screws for the number of channels required — single, double or triple bank.



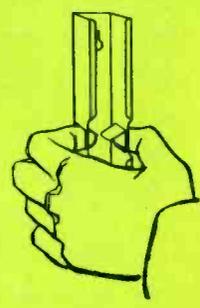2. Insert screws in position—do not turn all the way down. Slide channel down, letting screw head come through large part of keyhole slot. Slip narrow part of slot behind the screw head and tighten.



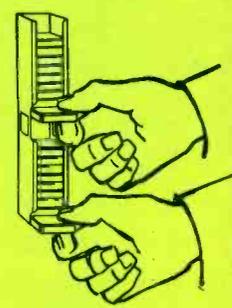3. Each channel can be made to dispense two types of fuses simply by folding in the tabs cut out in the middle of the channel.



4. Fuses now dispense from the middle or the bottom of the channel.

To serve you . . .
to increase your profits

LITTLEFUSE Again streamline your fuse service operation with a program that makes sure you have the right fuse at your fingertips at all times—time saved, effort saved, build up your service profits. ASK YOUR JOBBER about the Littlefuse Single Channel Fuse "Stocked Package": 10 single (double dispensing) fuse channels, 10 boxes (50) 3 AG 1/4 fuses and 10 boxes (50) 3 AG 1/2 fuses in our complete package FOR THE COST OF TWO FUSES ALONE.