


APRIL, 1959 35 CENTS



**PH**  
PHOTOFACT

# REPORTER

Including **Electronic Servicing**

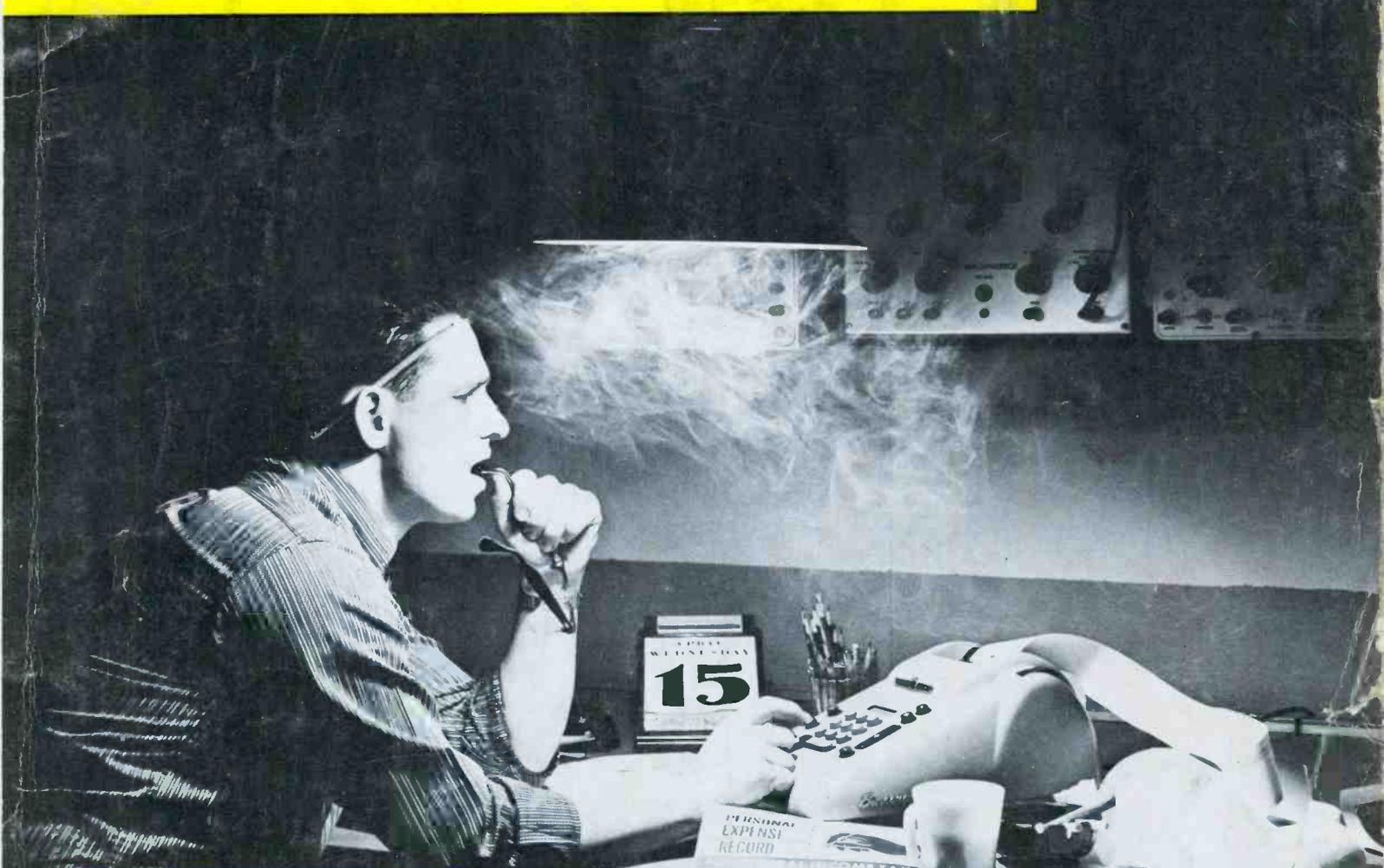

### This Month's Highlights

**Bench Servicing  
New Sets**



**Room  
Air-Conditioner  
Maintenance**



**Printed Circuit  
Components**

JA BM 635 1260E  
WM R DAVIS  
118 RIVERSIDE AVE  
CANNON CITY COLO

**G-C CEMENT SAMPLER KIT**  
Contains 14 different cements for every application.  
No. 345 ..... List \$9.95



**G-C ELECTRONIC OIL KIT**  
Complete assortment of 6 special oils in vial dispensers.  
No. 9400  
List \$3.50



**G-C SPRA-KLEEN**  
Spray away radio-TV control noises.  
6 oz. can.  
No. 8666 ..... List \$1.20



**G-C MASTER PRINTED CIRCUIT REPAIR KIT**  
Everything for printed circuit repairs, plus instructions.  
No. 683  
List \$13.25



**G-C TOP 12 TV ALIGNMENT TOOL KIT**  
Contains 12 basic tools in plastic fitted container.  
No. 5040 ..... List \$10.95



**G-C TINNEMAN NUT REMOVER**  
Removes large or small Tinnermans with simple twist.  
No. 9355 ..... List \$1.47



**G-C PHONO TURNTABLE STAND**  
The easy way to make repairs on all turntable sizes and types.  
No. 5212  
List \$12.50



**G-C SPEED-O-MATIC WIRE STRIPPER**  
No wire crushing with this handy tool. 12 models for all wire sizes.  
No. 766 (A to N)  
List \$9.90



**G-C KLIPZOM CRYSTAL PROD**  
Completely insulated prop snaps on and holds.  
No. 5638—Red ..... List \$3.06  
No. 5639—Black ..... List \$3.06



**G-C DIAL CABLE**  
Nylon with fiberglass core treated to prevent slipping and stretching.



**G-C AMC MINIATURE TUBE PULLER**  
A tube puller that prevents burnt fingers and tube breakage.  
No. 5093—7-Pin Tubes ..... List \$1.80  
No. 8106—9-Pin Tubes ..... List \$1.80



**G-C UNIVERSAL TYPE TEST LEADS**  
Interchangeable tips and 50" leads. Complete set of tips.  
No. 8463 ..... List \$3.00



**G-C RADIO-TV SERVICE CEMENT**  
For all kinds of repairs. 2-oz. bottle, brush in cap.  
No. 30-2 ..... List \$2.75



**G-C Z-5 SILICONE COMPOUND**  
Transfers heat from transistors to chassis, prevents damage.  
No. 8101 ..... List \$2.25



**G-C DE-OX-ID**  
Efficient electrical contact cleaner in 6-oz. spray can.  
No. 19-6 ..... List \$3.50



**G-C FLEX-SOL SPRAY-CAN EXTENSION**  
Fits all spray cans, puts spray where you want it.  
No. 9344 ..... List \$1.49



**G-C ZERO MIST CIRCUIT COOLER**  
Circuits cooled instantly. Intermittent components isolated.  
No. 8667 ..... List \$2.17



**G-C MINIATURE TUBE PIN STRAIGHTENERS**  
Precision-constructed steel dies in 2 sizes.  
No. 5191 (for 7-pin tubes) ..... List \$1.25  
No. 8105 (for 9-pin tubes) ..... List \$1.25

**EVERYTHING UNDER THE SUN!**



## Electronic Products

The newest and latest items, as well as those you need year after year... the best you can find, as well as the most economically priced—that's what you get in the big G-C ELECTRONIC PRODUCTS line. Your favorite jobber has them. Always look for G-C... the sign of Good-Components!



**WRITE TODAY!**

for your FREE G-C Catalog. Send postcard.

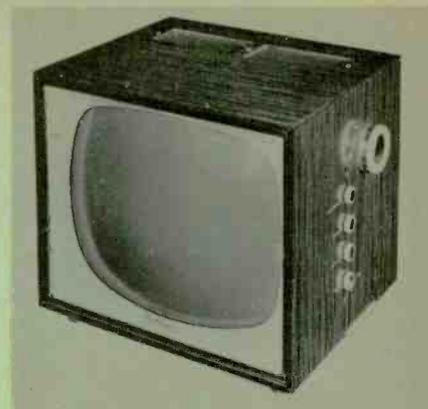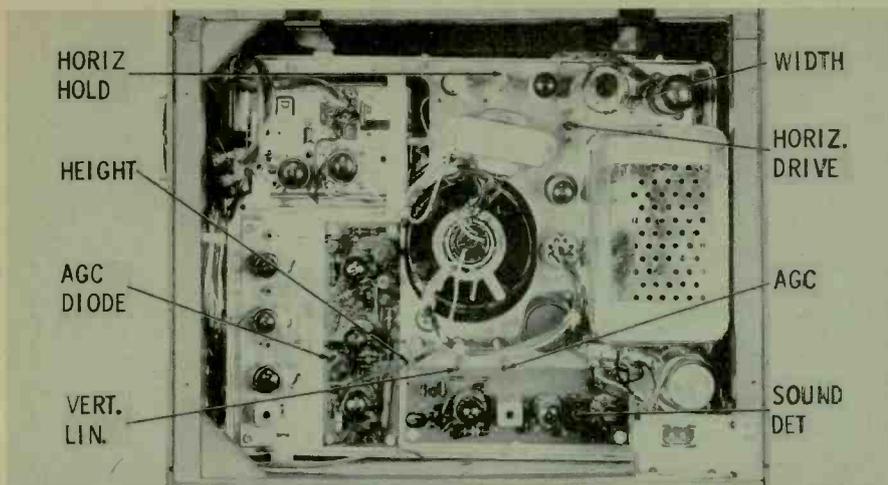**GENERAL CEMENT MFG. CO.**

division of G-C Textron Inc.

Western Plant: Los Angeles 18, Calif.  
Main Plant: ROCKFORD, ILLINOIS, U.S.A.






**Hoffman Model M1277  
Chassis 335**

*Pacoima* is the trade name for this new 17" VHF portable, which features a short neck 110° picture tube. Two strips of printed wiring are used in the make-up of the vertically-mounted chassis—one for the sound section and the other containing the video, AGC, sync, and vertical-oscillator circuits. Tube heaters are all in series, and one side of the AC line is connected to chassis ground. A 6BJ8 dual-diode/triode is employed in the horizontal-AFC and sync phase-inverter stages. The remaining tube types are fairly conventional, except perhaps the 12DT5 output tube in the vertical circuit. The AGC diode pointed out in the rear cabinet photo is a small crystal used to clamp the AGC voltage for the RF amplifier. Since this component is found on the printed board containing the video amplifier stage, one might conclude that it functions as the video detector; however, the diode section of a 5AM8 is actually used for this purpose.

Powering the chassis are two silicon rectifiers mounted in polarized clips on the bottom side of the high-voltage cage. Connected in a voltage-doubler circuit, each unit is rated at 500 ma. The supply is protected by a 7.5-ohm fusible resistor located on the wiring side of the chassis directly behind the audio-output transformer. Chassis removal involves taking out two bottom bolts and two screws holding the brackets on the upper rear of the cabinet. After removing the interlock panel and disconnecting the necessary leads, the chassis slips out the back without the picture tube.

Adjustment of the RF oscillator is accomplished by removing the channel-selector and fine-tuning knobs and tuning each operating channel slug as the turret is rotated. The front of the tuner is covered with a fibre insulating board having a single adjustment hole as shown. Incidentally, you'll find that the control panel (mounted on the side of the cabinet) has long leads and will not necessarily require removal to work on the chassis.

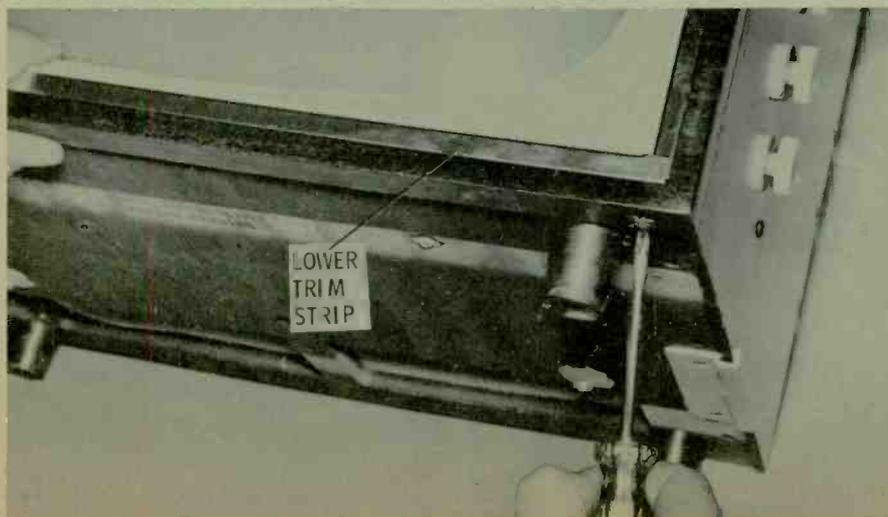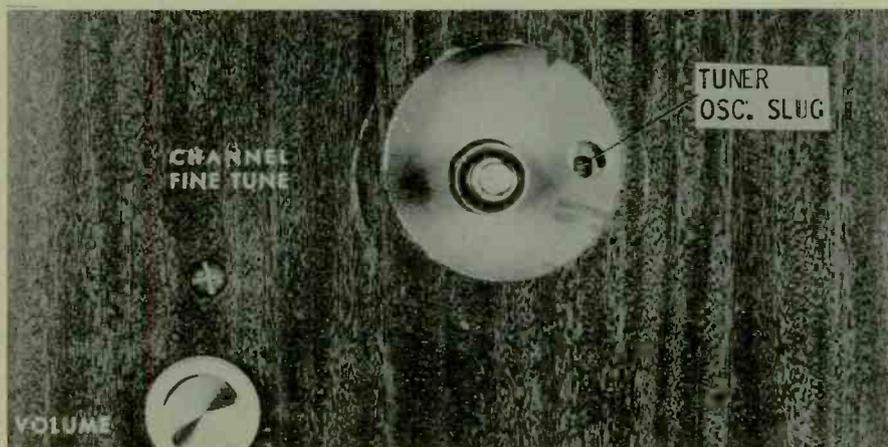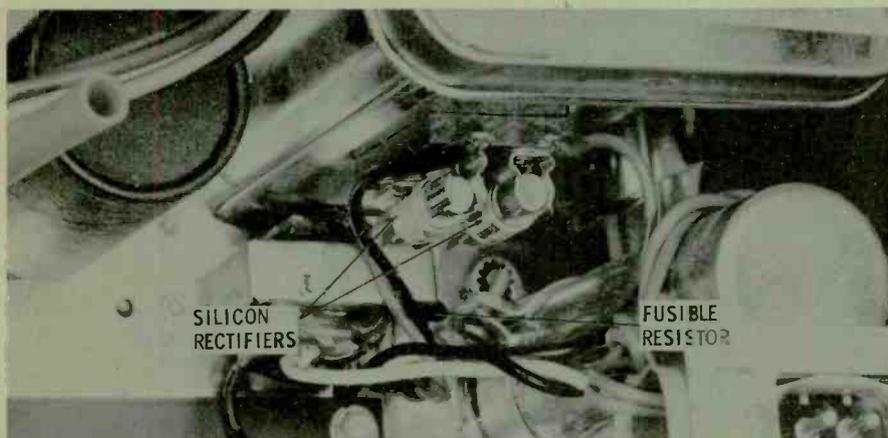To clean the screen on this model, remove the two Phillips-head screws securing the lower trim-strip under the front edge of the cabinet, pull the glass assembly out at the bottom and remove.





**Magnavox  
Model 2MV-147L  
Chassis V30-05AA**



The vertical chassis in this console is powered by a transformer, and mounts in the center section of the cabinet with a 21" picture tube. On each side, an 8" woofer and a 4" tweeter reproduce sound (four speakers in all), while the tuner and power-tuning unit mount to one side as shown. Be careful not to mistake the AC jumper plug above the power transformer for a horizontal-AFC diode. The jumper, fashioned as a plug-in dual diode, is merely a connecting device used in the primary circuit of the power transformer. If line voltage is normal, the plug should be placed in the socket with its "117V" marking on top. If voltage is higher than normal, the "127V" marking should be up.



You'll find vertical-linearity, height, and horizontal-frequency adjustments near the bottom of the chassis pan between the high-voltage cage and the power transformer. Although the tube lineup is not revolutionary, the audio output stage employs a 6DG6GT (6W6GT), and a 6BF6 is used for half the vertical multivibrator and the AGC clamper. The other section of the multivibrator uses a 6DT5.

Positioned on the chassis just to the left of the yoke is a three-connection terminal strip. The lead from the focus anode of the picture tube should be connected to the terminal producing best picture focus. The 1/4-amp fuse shown in the photograph is a slow-blow unit which protects the horizontal-output and flyback components. A length of #24 un-insulated wire fuses the filament circuit.

The remote hand unit is a small plastic case with a suction cup on one end and a combination pushbutton switch and volume control on the other. The switch enables the operator to select channels automatically and to turn the set on. If one channel of the tuner (such as the UHF position) is set up for automatic shut-off, power can also be turned off with this switch.

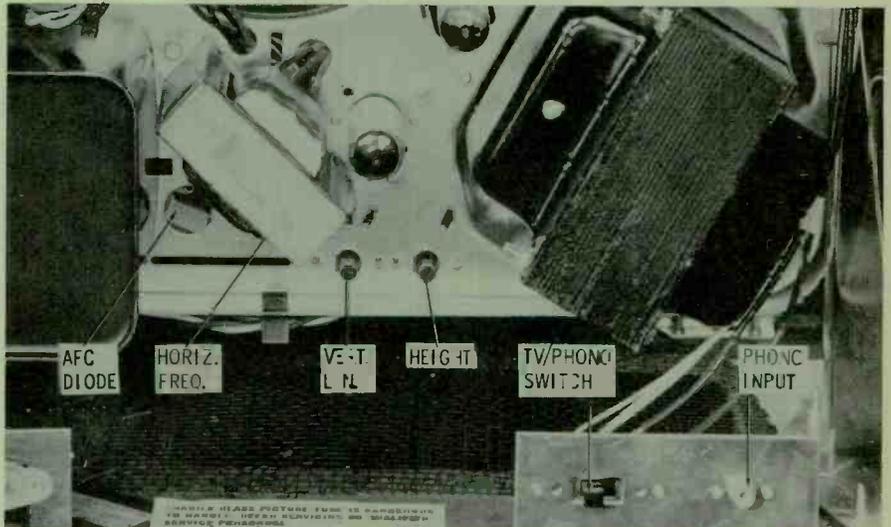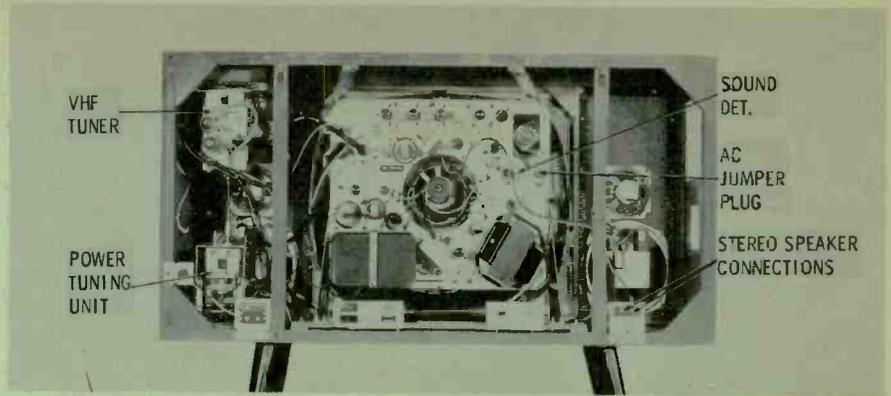Set-up adjustments for indexing the powered tuner are located under the cabinet. The *set* control (nearest side of cabinet) selects channels for automatic tuning by pulling out or down on the knob. When this control is rotated clockwise in the *out* position, the associated channel is then set up for automatic shut-off. Pushing in on the *clear* control bypasses undesired channels.



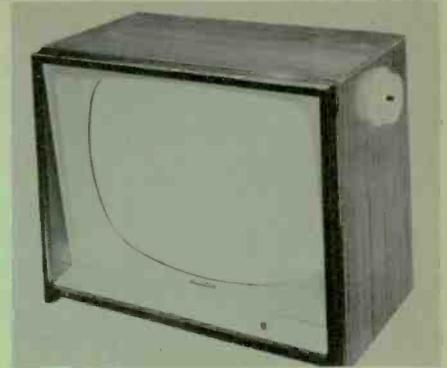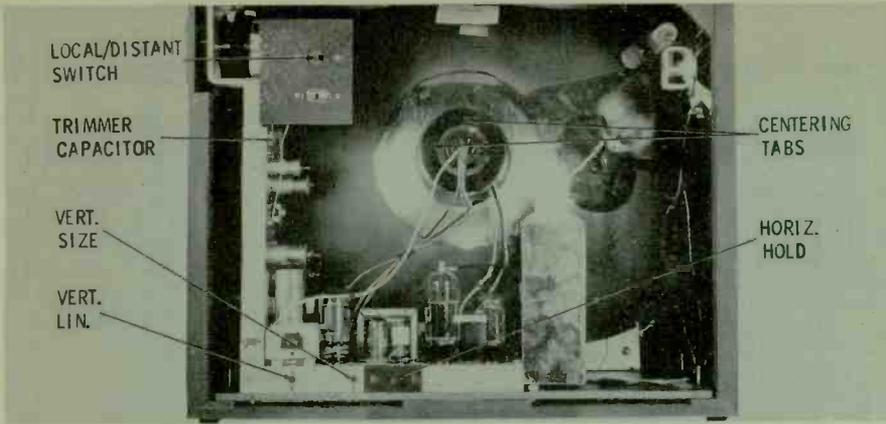

**Muntz Model 21TM  
Chassis "J"**



A little different from the Muntz portable design, this new table model has all its operating controls on the side. Also featured are a 21" 110° picture tube and a local-distant switch for selection of the proper AGC range.


When you remove the back cover, you'll find a narrow "L" shaped chassis with one of the new Sarkes Tarzian *Hot-Rod* tuners positioned on top of the vertical section. Incidentally, the tuner is not positioned directly behind the group of control knobs, but is offset and operated via a gear arrangement. The trimmer capacitor pointed out in the photo is an alignment adjustment located in the grid circuit of the first IF stage. Remember this so you won't mistake it for a horizontal-AFC or drive control.

Five separate operating controls, including contrast, fine tuning, brilliance, volume with on-off switch, and vertical hold, are confined within the large channel-selector knob. To remove the knobs prior to pulling the chassis, the circular control plate, which is held by four Phillips-head screws, must be removed. The large screw below and to the right of the controls is part of the mounting hardware for the tuner assembly. Chassis and picture tube are attached to a single mounting board, which is removable from the rear of the cabinet.

Alignment of the horizontal oscillator is accomplished by tuning in a normal signal, shorting out the ringing coil, grounding the AFC voltage at pin 2 of the 5BW8 phase detector, and adjusting the hold control until a single picture is obtained. Next, remove the jumper across the ringing coil and adjust the coil slug with a hex-ended tool. Screw the slug up into the winding until a single picture is again obtained. Then, turn it back about 1/4 turn, remove the short from the AFC diodes, and observe the picture to see if it snaps into sync. To check AFC action, measure the voltage on pin 2 of the 6CG7 oscillator tube. A normal reading should be from 0 to .2 volts DC.

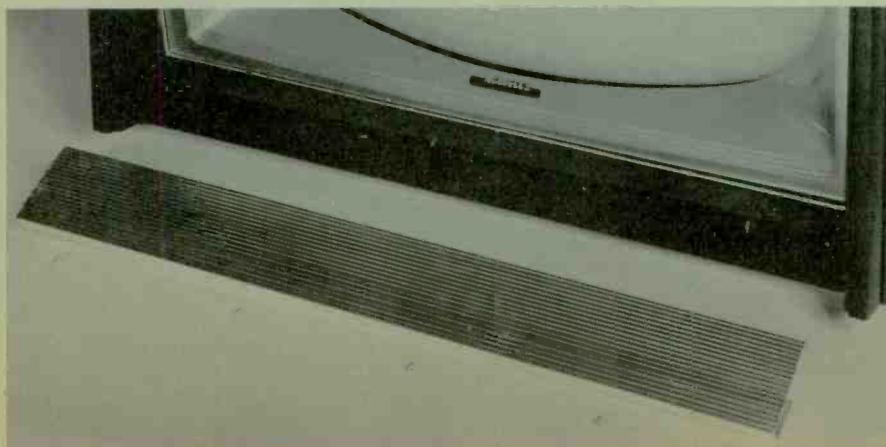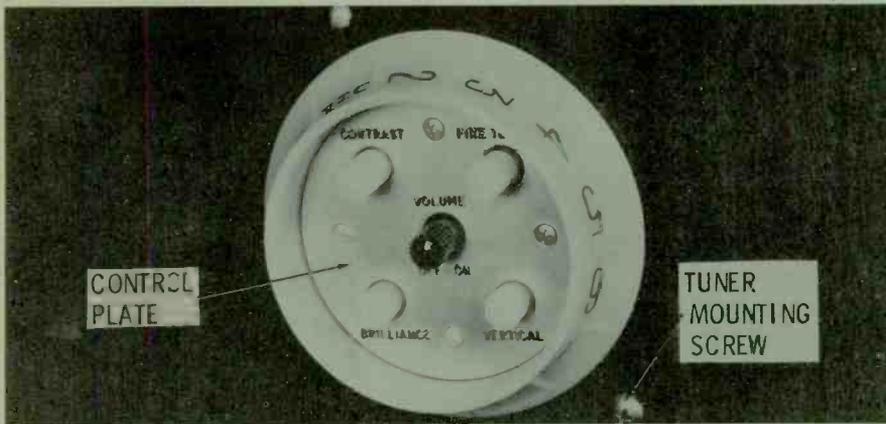To take the safety glass out from the front, you'll find four Phillips-head screws under the lower trim-strip. With the strip removed as shown, tilt the cabinet forward until the glass swings out at the bottom; then slip it down and out of the top retainer.



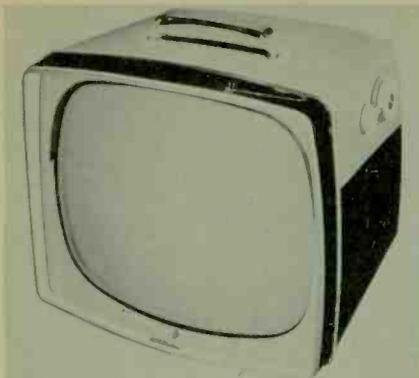

**RCA Model 21PT9095  
Chassis KCS 117A**




This large-screen portable has all operating controls on the side of its metal cabinet, with horizontal hold, brightness, and vertical hold in a small hidden compartment below the contrast, volume, and tuner knobs. Although not shown, the set also has a "V" or rabbit-ear antenna attached to the rear cover.

The chassis is of the vertical style positioned around the neck of a 21" 110° tube. A VHF tuner, which incidentally uses a 6CQ8 converter tube, mounts right on the chassis in the upper left corner. The transformer-powered set, featuring almost all printed wiring, introduces another newcomer to your tube caddy—a 6EM5 serving the vertical multivibrator-output section. The fusible resistor, located on the chassis just to the left of the yoke cut-out, is a special 9-ohm unit, and should be replaced by an original type. This component guards the B+ supply against damage from shorts, while three separate lengths of copper wire protect the heater circuits.

All tubes and service adjustments are easily reached, with the exception of the height and vertical linearity controls. These two pots are screwdriver adjustments mounted on a printed board recessed from the chassis surface. Horizontal adjustments (drive, waveform, and width) are near the left side of the chassis.

You'll find a thermal cut-out device fastened to the side of the high-voltage cage directly behind the AC interlock. This combination switch and resistive unit offers automatic protection for the low-voltage supply, breaking the circuit when current drawn by the receiver becomes excessive. The AGC control located below the interlock should be adjusted while the strongest signal is being received. If adjusted with a weak signal as a guide, the set may overload when a stronger signal is tuned in.

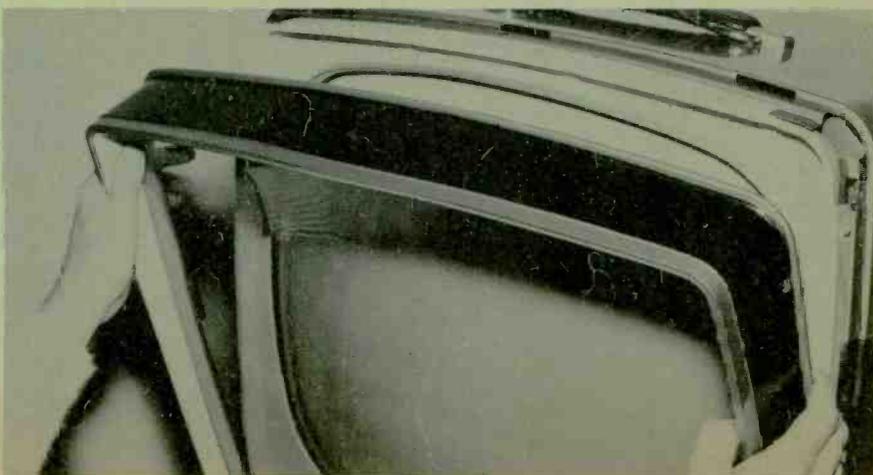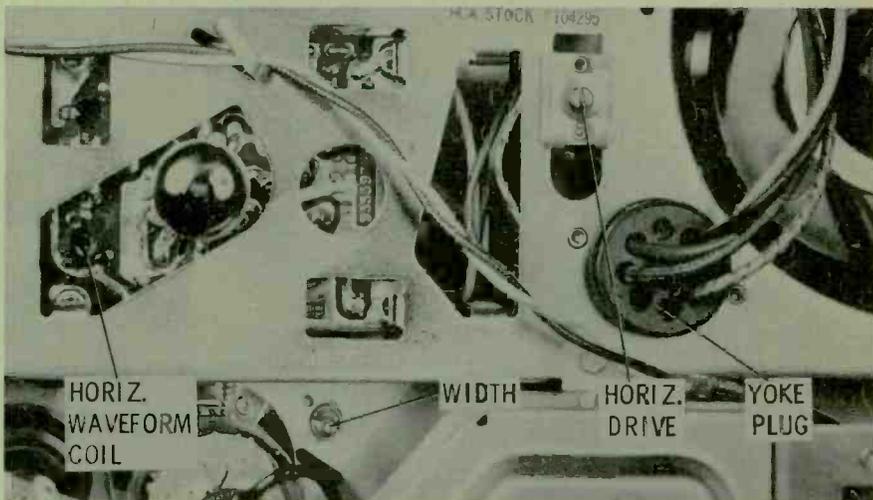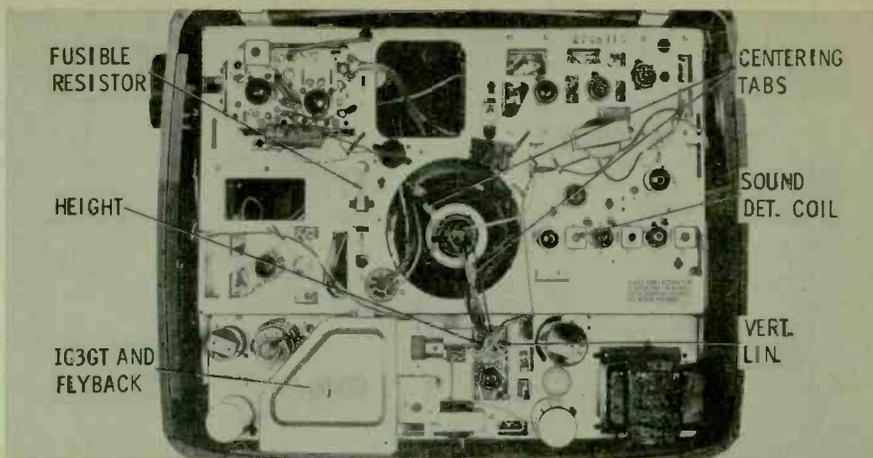The picture tube and safety glass on this model can be separated for cleaning by removing the entire front mask assembly. To free the bezel, remove the two Phillips-head screws from each side of the cabinet, and two screws from the bottom. There are actually four screws under the front section of the cabinet, but you need only remove the two back ones.



Wherever You Go... There are Radio Sales




For the first Time

Regency

the first name in transistor radios

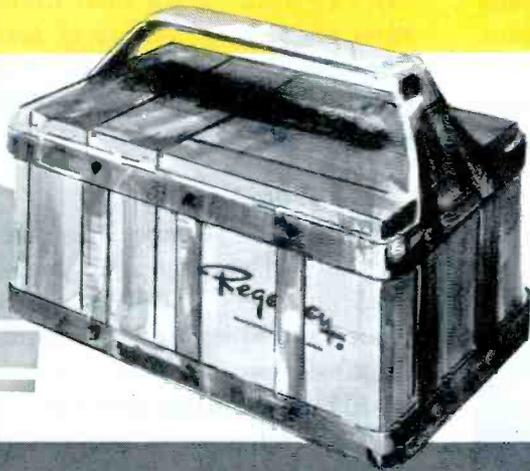makes it easy for you to go to your sales  
and take your profits with you



The  
New Regency  
Radio Caddy

6 Leading Regency Transistor Radios in all price categories from \$14.95 to \$49.95 plus a Regency transistorized portable record player.

On your service calls:

Sell up from a radio repair—more profit less labor.

Pick up sales from the people who already want a transistor

radio but haven't gotten around to a store.

Pick-up impulse sales—from people who have never actually heard a transistor radio at home.

Anything can happen if you have Regency radios with you. The Regency Caddy can be yours at no cost—see your Electronic Parts Distributor—today.



NEW! Model TR-22 \$29.95

NEW! Model RF-3 \$29.95



Sales Proved  
Model TR-7 \$39.95

Sales Proved Model XR-2A \$14.95



Regency

First in Transistor Radios

DIVISION, I. D. E. A., INC.,  
INDIANAPOLIS 26, INDIANA


Burton Browne Advertising

# NEW DIFILM<sup>®</sup> BLACK BEAUTY<sup>®</sup> MOLDED CAPACITORS
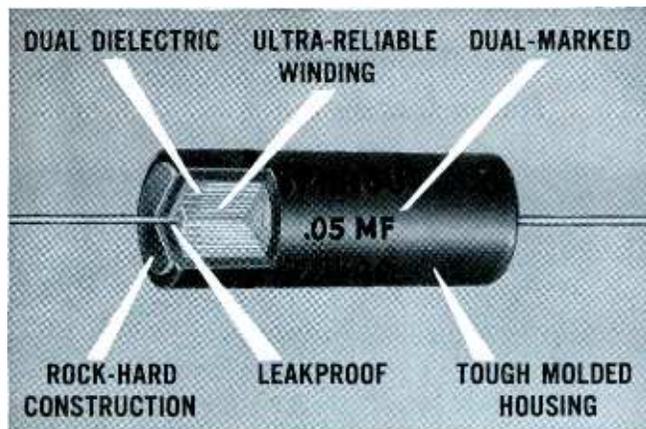
# BEAT THE HEAT AND HUMIDITY!

Now Sprague's new DIFILM BLACK BEAUTY MOLDED CAPACITORS have taken the steam out of heat and humidity problems. These capacitors are so good you can *boil 'em* for 24 hours without affecting their performance.

Unlike straight polyester film tubulars, these capacitors operate in a 105°C environment *without derating*.



Look for the RED markings on the black case.

And the heart of these new DIFILM capacitors can't be beat. It's a dual dielectric which *combines the best advantages of both Mylar\* polyester film and the highest grade of paper dielectric*. A rock-hard solid impregnant fills voids and pin-holes in the film.

Talk about *reliability!* . . . these capacitors have it. DIFILM capacitors are actually low cost versions of the Sprague capacitors now being used in every modern military missile. The basic reliability and outstanding performance of missile-type Sprague capacitors are all yours in this outstanding new development. Why take chances when you can get the best—DIFILM BLACK BEAUTY MOLDED TUBULARS . . . at regular prices.

*For the complete DIFILM BLACK BEAUTY story, write for Bulletin M-759 to Sprague Products Company, 105 Marshall St., North Adams, Mass.*

\*DuPont trademark

The major capacitor improvements  
come from



SPRAGUE RESEARCH IS CONSTANTLY PRODUCING NEW AND BETTER CAPACITORS FOR YOU

**publisher**  
Howard W. Sams  
**general manager**  
Mal Parks, Jr.  
**editor**  
Verne M. Ray  
**associate editors**  
Leslie D. Deane  
Thomas A. Lesh  
Calvin C. Young, Jr.  
**consulting editors**  
William E. Burke  
Robert B. Dunham  
George B. Mann  
C. P. Oliphant  
Paul C. Smith

**art director**  
Don W. Bradley  
**editorial assistant**  
Georgeanna Caldwell  
**production manager**  
Robert N. Rippy  
**adv. production**  
Bertie Johnson  
**circulation fulfillment**  
Pat Tidd, Mgr.  
Ann Mathews, Ass't.  
**photography**  
Robert W. Reed  
**advertising sales offices**

**Midwestern**  
PF REPORTER  
2201 East 46th Street, Indianapolis 6, Ind.  
Clifford 3-6441

**Eastern**  
Paul S. Weil and Donald C. Weil  
30-01 Main Street, Flushing 54, New York  
Independence 3-9098

**Western**  
The Maurice A. Kimball Co., Inc.  
2550 Beverly Blvd., Los Angeles 57, Calif.  
Dunkirk 8-6178; and 681 Market Street,  
San Francisco 5, Calif. Exbrook 2-3365

Address all correspondence relating to circulation and editorial to PF REPORTER, 2201 East 46th Street, Indianapolis 6, Indiana

Copyright 1959 by Howard W. Sams & Co., Inc. No part of the PF REPORTER may be reproduced without written permission. No patent liability is assumed with respect to use of information herein. As a magazine devoted to public service to the entire electronics industry, it is the obligation of PF REPORTER with Electronic Servicing to present to its readers all legitimate advertising in this field. Acceptance of advertising does not in any manner signify the products, policies and services so advertised have been approved, endorsed, or recommended by this magazine.

## NEXT MONTH

### Aligning and Calibrating Communications Sets

Another "mecty" feature by expert Jack Darr, following up the "Getting Acquainted" article under his byline in the March issue. The title tells you what to expect.

### Question and Answers on Deflection Yokes

Are you lost when it comes to deflection problems? For answers to the most-often asked questions, along with numerous picture symptoms to help you isolate yoke troubles more quickly, be sure to read this down-to-earth presentation in the May issue.

### Using a Crosshatch Generator to Align Chroma Circuits

This one is particularly for the numerous readers who have urged us to put in more color TV coverage, but it will also be a great help to those who want to cut a few corners and take on some color work.



**PF**  
PHOTOFACT

# REPORTER

including Electronic Servicing

VOLUME 9, No. 4

APRIL, 1959

## CONTENTS


|   |    |
|---|----|
| <b>Previews of New Sets</b>   | 1  |
| Data for in-the-home servicing of '59 sets.   |    |
| <b>Video Speed Servicing</b>  | 5  |
| Servicing hints for DuMont and Philco chassis.  |    |
| <b>Letters to the Editor</b>  | 18 |
| <b>Across the Bench</b> Stan Prentiss   | 22 |
| More on the RCA KCS47 and Capehart CX-33 chassis.   |    |
| <b>Printed Circuit Components</b>   | 24 |
| Schematic diagrams plus component-test and cross-reference data for the most popular types.                         |    |
| <b>Audio Facts</b> Alan Andrews   | 26 |
| Tracking down troubles in preamps and equalizers.   |    |
| <b>Bench Servicing New Sets</b> Thomas A. Lesh  | 28 |
| How to "approach" the Philco 9L37 "Predicta" model.   |    |
| <b>Room Air-Conditioner Maintenance</b> Joseph Derman & Harold Seaman   | 30 |
| Part 1—Operational theory of modern units and how to locate electrical component failures.                          |    |
| <b>Quicker Servicing</b> Calvin C. Young, Jr.   | 32 |
| New connectors for your VTVM; obtaining special temperature coefficients; Sencore "Electro-Sub"; bench "Auto tray." |    |
| <b>Dollar &amp; Sense Servicing</b>   | 40 |
| <b>Tips for Techs</b> John A. Comstock  | 44 |
| <b>Notes on Test Equipment</b> Les Deane  | 48 |
| Hickok 810 transistor-radio tester; Precision Apparatus "Electronamic" tube tester.                                 |    |
| <b>Stock Guide for TV Tubes</b>   | 58 |
| <b>The Troubleshooter</b>   | 60 |
| <b>Product Report</b>   | 82 |
| <b>Free Catalog &amp; Literature Service</b>  | 84 |
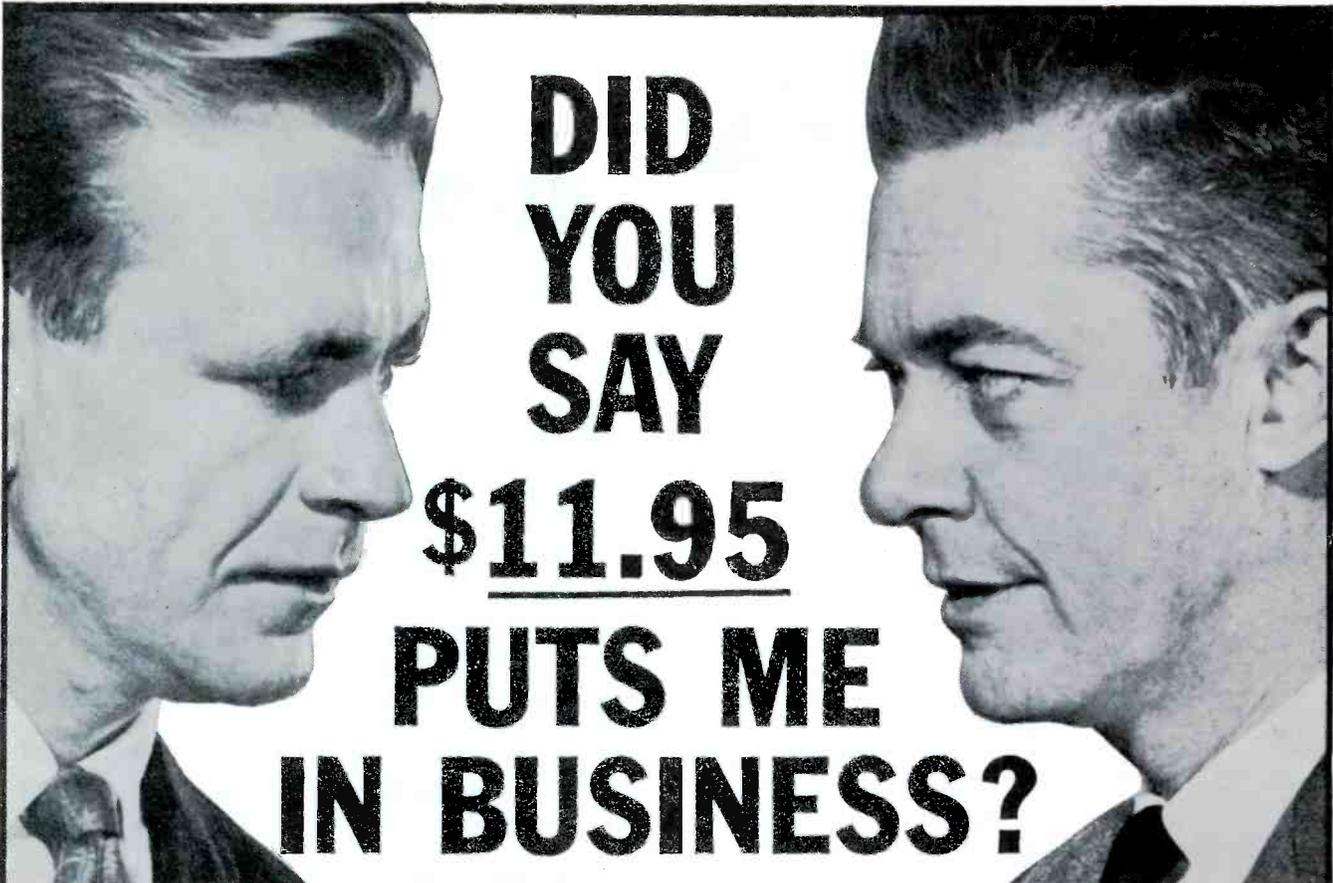
## ABOUT THE COVER

Like so many of us, our cover serviceman has been too busy repairing sets to file his federal income tax report. Now he's scrambling to beat the midnight deadline. Doesn't look like April 16th will be a good day to have a set fixed.



USE HANDY CARD AT BACK TO ENTER YOUR SUBSCRIPTION



# DID YOU SAY \$11.95 PUTS ME IN BUSINESS?

## Yes, \$11.95 Puts You in the BOOMING EXACT REPLACEMENT PORTABLE ANTENNA BUSINESS!

You bet. Only \$11.95 earns you a king-sized share of today's 4 million dollar portable TV antenna replacement market. That's the amazingly low price for the new JFD Exact Replacement Portable TV Antenna Merchandising Kit that sets you up overnight in this thriving new business.

### Look at what you get:

5 top-selling Exact Replacement antennas that cover 85% of portable TV's in use... the 1959 JFD edition listing every portable TV set by make, model, and antenna... a traffic-stopping window streamer... and a comprehensive portable antenna business building plan.

As a Portable TV Antenna Service Specialist, you can forget about competition with drug stores, auto accessory stores and the like, too. *You* make a handy profit on every sale.

Makes sense, doesn't it, to stop at your JFD distributor today for your Exact Replacement Portable TV Antenna Merchandising Kit?



### JFD Exact Replacement Portable TV Antenna Merchandising Kit

No. PA500      Contents:      **\$11.95 Dealers Net**

| No. | JFD Antenna Model | Exact Replacements for     | List                      |
|-----|-------------------|----------------------------|---------------------------|
| 1   | TA154             | Admiral-Westinghouse       | \$10.95                   |
| 1   | TA155             | Zenith-Admiral             | 11.50                     |
| 1   | TA359             | RCA, Motorola, Magnavox    | 12.95                     |
| 1   | TA360             | GE, Hotpoint, Westinghouse | 11.75                     |
| 1   | TA442             | Emerson, GE, Olympic       | 10.95                     |
|     |                   |                            | <b>Total List \$58.10</b> |

- 1 1959 catalog of all Portable TV Sets by brand, model and JFD Exact Replacement Indoor Antenna.
- 1 "Exact Replacement Portable TV Antenna Headquarters" streamer.
- 1 Outline of complete dealer sales promotion plan.

Pioneers in Electronics since 1929

**JFD ELECTRONICS CORP.**  
6101 Sixteenth Avenue      Brooklyn 4, New York

**JFD CANADA LTD.      JFD INTERNATIONAL**  
51 McCormack Street      15 Moore Street  
Toronto, Ontario, Canada      New York, N.Y.

# NOW... AN *Electro-Voice*<sup>®</sup> PUBLIC ADDRESS SPEAKER FOR ANY APPLICATION

For SUPERIOR SOUND . . . CONTROLLED COVERAGE

See Electro-Voice public address projectors. They offer perfect voice penetration and full-range "musicasting." They're weatherproof, splashproof and blastproof.



Model 844 30-Watt Paging Unit. Compact, economical unit for quality, high-efficiency voice reproduction.

**\$34.50**  
LIST



The New Electro-Voice Musicaster. Rugged, weatherproof high-fidelity speaker system for high-quality music reproduction.

**\$80.00**  
LIST

**\$75.00**  
LIST

Model 848LT Long Throw CDP\* (With 1000-cycle concentrating horn). For projecting intelligible, extended-range sound over great distances.

\*CDP (Compound Diffraction Projection) Design Patent 169,904. Additional Patent Pending.



Model 848 30-Watt CDP. For wide-angle coverage and extended range. Standard of the industry.

**\$75.00**  
LIST



Model 847 25-Watt CDP. Smaller version of Model 848.

**\$46.33**  
LIST



Model LS-12. For interior installations requiring full-range response.

**\$32.50**  
LIST



Model LS-8. Smaller version of Model LS-12.

**\$30.00**  
LIST

THESE ELECTRO-VOICE MICROPHONES ARE  
ESPECIALLY OUTSTANDING FOR PUBLIC ADDRESS



**\$85.00**  
LIST

Model 664 Cardioid Dynamic. Broadcast-quality for every public address installation.



**\$49.50**  
LIST

Model 951 Cardioid Crystal. Excellent, wide-range, all-purpose microphone.

The Sound of Electro-Voice . . . Assures Superior Installations, Customer Satisfaction, Your Reputation!

**Electro-Voice**<sup>®</sup>

ELECTRO-VOICE, INC.  
BUCHANAN, MICH.

In Canada: E-V of Canada Ltd., 73 Crockford Blvd., Scarborough, Ontario  
Cables: ARLAB



SAVE THE EASY WAY  
BUY U.S. BONDS  
ON PAYROLL-SAVING



Raytheon M  
Distri  
Feb. 16, 1959

Manufacturing Company  
Division  
Massachusetts

Raytheon Manufacturing Company  
Distributor Products Division  
Newton 58, Massachusetts

Gentlemen,


You claim your Raytheon TV and  
Radio tubes are the best... but every  
maker makes the same claim.  
It's very confusing. I sure wish  
someone could prove theirs best.  
Can you?

Sincerely  
Frank

Raytheon grids  
are made of  
gold or silver.  
Important  
because grid  
is heart of tube.



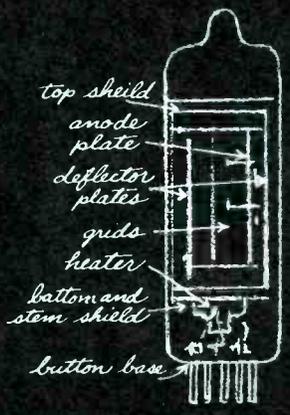Imported getter  
is circular...  
holds more  
power... creates  
better vacuum



all made by Raytheon



RAYTHEON MANUFACTURING COMPANY

DISTRIBUTOR PRODUCTS DIVISION

55 CHAPEL STREET • NEWTON 58, MASSACHUSETTS • BIGELOW 4-7500

Dear Frank:

How can I prove Raytheon Tubes are superior to all others? A good question and I'm going to try and give you an honest answer!

First, we believe that what we put in Raytheon TV and Radio Tubes . . . and the way we make them . . . are the real reasons why they are best. Pictures of quality control, manufacturing processes, might help convince you, but would they actually prove the end result is a quality product?

You still wouldn't be sure that the Raytheon replacement Tube you put in your customer's set was as good as or better than the original and would outlast it in saving you all those no-charge repeat calls.

To be sure, Frank, we could give you a long list of how we make all our own tube parts—use imported getters, special grids, ceramic insulated multiple fold heaters, and many, many others—but do you really care about these things?

You know, of course, that Raytheon is the world's largest exclusive manufacturer of Electronic Components. Raytheon Tubes and Components which go into 21 of our nation's missiles have to be better than normal. They don't just have to be good!

Honestly, Frank, maybe we can't prove superiority . . . but you can! You and thousands of men like yourself are proving it every day. I would suggest that as long as there is a doubt in your mind, why don't you find out for yourself by using Raytheon Tubes as others have done? I don't know of any other way.

Thanks for your letter . . . let's hear from you again real soon. I know you're going to be convinced.

Sincerely,

RAYTHEON MANUFACTURING COMPANY

*Ray Raytheon*

P.S. I'll be talking to you again next month.


Excellence in Electronics

*TV Technician Bing Longton says . . .*
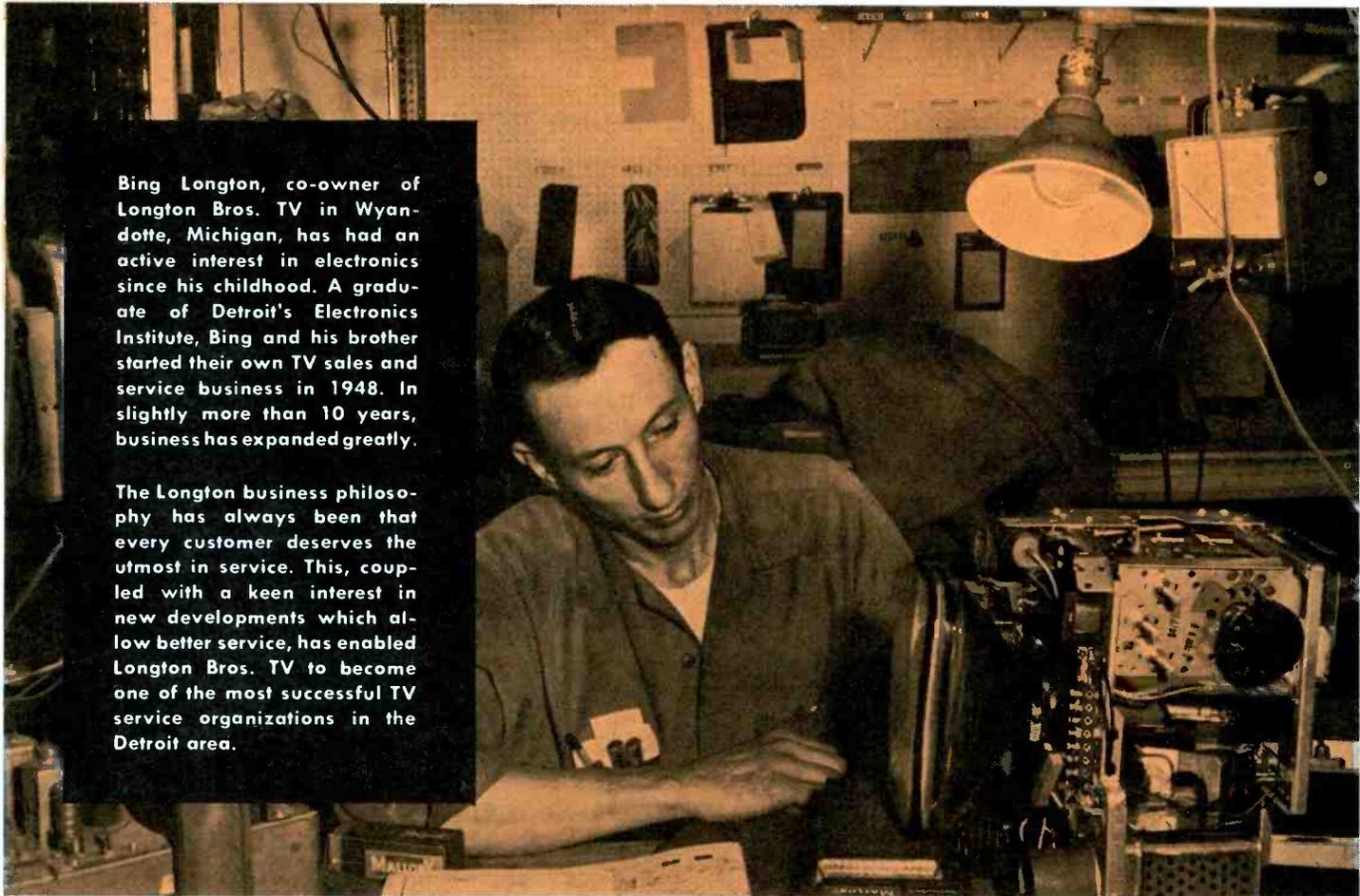
# “We Can’t Gamble With Customer

Bing Longton, co-owner of Longton Bros. TV in Wyandotte, Michigan, has had an active interest in electronics since his childhood. A graduate of Detroit's Electronics Institute, Bing and his brother started their own TV sales and service business in 1948. In slightly more than 10 years, business has expanded greatly.

The Longton business philosophy has always been that every customer deserves the utmost in service. This, coupled with a keen interest in new developments which allow better service, has enabled Longton Bros. TV to become one of the most successful TV service organizations in the Detroit area.



*Put an end to call-backs with these quality Mallory products . . .*



## GEMS

5 rugged, moistureproof, Mallory “Gem” tubular capacitors in an easy-to-use dispenser that keeps your stock fresh and clean—easy to find—no more kinks in lead wires. They’re your best bet for outstanding service in buffer, by-pass or coupling applications.



## RMC DISCAPS®

Are a product of the world's largest producer of ceramic disc capacitors. Long the original equipment standard, Mallory RMC Discaps are now available for replacement. They come in a handy 3" x 5" file card package . . . easy to stock, simple to use.

®A registered trade mark of Radio Materials Company, a division of P. R. Mallory & Co. Inc.



## FP ELECTROLYTICS

The Mallory FP—the original 85°C. capacitor—now has improved shock-resistant construction and leakproof seal. Its etched cathode construction—standard in all FP's—assures hum-free performance. High ripple current ratings fit the toughest filter circuits.

# Satisfaction . . . We Use Mallory Components for Replacement”

“Customers demand quality repair service, and at Longton TV the customer is *king*. We figure the best way to keep him happy . . . and protect our own profits, too . . . is to prevent complaints before they happen. So we give him the best in service and the best in replacement parts—that means MALLORY components. We’ve used them ever since we started in business, because we know

we can always depend on MALLORY.”

Whether you need capacitors, controls, resistors, silicon rectifiers or batteries, you get the highest quality components at sensible prices. The Mallory line is the widest in the industry, and Mallory “service-engineering” assures you fewer call-backs and more satisfied customers. See your Mallory distributor for a full selection of the parts you need.

Get TC capacitors at your distributor from this handy merchandise display.



## STA-LOC\* CONTROLS

New Sta-Loc design enables your distributor to custom build, in just 30 seconds, any of 38,000 combinations—eliminates waiting for out-of-stock controls. You can replace the line switch by itself, without unsoldering control connections.



## GOLD LABEL VIBRATORS

On critical auto radio servicing, use the Mallory Gold Label Vibrator. It gives longer, trouble-free service life. Mallory Gold Label Vibrators feature Mallory exclusive buttonless contact design.

*\*Trade Mark*




## TC TUBULAR ELECTROLYTICS

Economically priced electrolytic filter capacitors with a reputation for doing an excellent job. They have been proved in performance and are backed by years of Mallory experience. Also special TCX type available for  $-55^{\circ}\text{C}$ .

by  
every  
test



is BEST!

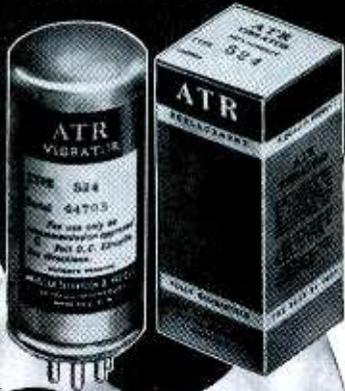

**ATR** AUTO  
RADIO  
VIBRATORS

Have Ceramic Stack Spacers

A COMPLETE LINE  
OF VIBRATORS

Designed for Use in Standard  
Vibrator-Operated Auto Radio  
Receivers. Built with Precision  
Construction, featuring Ceram-  
ic Stack Spacers for longer  
lasting life. Backed by more  
than 27 years of experience in  
Vibrator Design, Develop-  
ment, and Manufacturing.

Free

"A" Battery Eliminators, DC-AC  
Inverters, Auto Radio Vibrators



**ATR**

NEW MODELS

NEW DESIGNS

NEW LITERATURE

See your jobber or write factory

**AMERICAN TELEVISION & RADIO CO.**

Quality Products Since 1931

SAINT PAUL 1, MINNESOTA—U. S. A.

## Letters to the EDITOR

Dear Editor:

Please enter our order for your "Homeowner's TV Antenna Handbook."

We have been anticipating setting up a special division for the sales and service of antenna systems, and are anxious to try out the handbooks. We feel they will help us gain a considerable amount of business.

E. W. THIESS

Livingston, N. J.

Dear Editor:

When I came across the "Homeowner's TV Antenna Handbook" in your February issue, I was very much impressed.

I plan to open a new TV service center on March 1st, and can't think of better direct-mail advertising material than the handbook.

Many thanks for your past help and the splendid articles on electronics.

VICTOR SAULTER

Bloomington, Ind.

We knew the "Handbook" was good, but we didn't know how good until orders started pouring in.

Please bear with us if your order is delayed slightly. We're doing our best to keep up with the demand.—Ed.

Dear Editor:

In your Homeowner's TV Antenna Handbook, I noticed no reference to the use of a preamplifier or amplifier for improving signals from a TV antenna. There is mention, and rightfully so, of amplifiers for use with multiple outlets or for distribution systems—but no mention of them as an aid to single-set reception.

SELMAN M. KREMER

Jerrold Electronics Corp.  
Philadelphia, Pa.

Take heed, you guys out there in the fringe!—Ed.

Dear Editor:

The information you gave me about the puckered raster on a Westinghouse set (Troubleshooter, February) was very helpful. I'm writing to let you know how I made out.

I'd already tried changing the filter capacitors one at a time, without success; but, when I bridged all filters at the same time (two triple-section units and one double) the defect was cured.

Even after the filters were repaired, the set would receive only one station. I checked the tuner and found that lightning had damaged the set.

JIM PHILLIPS

Lavonia, Ga.

Always glad to help our readers with a "dog." Incidentally, Jim didn't have to wait until the data he wanted was published. A personal reply, with suggestions

for curing the trouble, is given immediately in all such cases.—Ed.

Dear Editor:

To prevent squeals while servicing the Philco E670 series chassis, as discussed in the February Quicker Servicing column, I always connect a jumper from the minus terminal of the filter capacitor to the frame. I also make sure the volume control is secured to the frame with its own Parker screw. The set can then be serviced with the shield removed.

JOHN WIZEMANN

Jackson Heights, N. Y.

Good idea, John, but watch out for shock hazards! And don't forget to restore isolation between B minus and chassis before returning the set. We can't defend you in a lawsuit!—Ed.

Dear Editor:

While driving between Ottumwa and Bloomfield, Iowa, we saw a sight that startled us—a TV antenna already in place on what appeared to be the unfinished frame of a new house. When we drove on around to the other side of the hill, we could see that people were already living in the basement of the house.

R. L. KURTZ

Des Moines, Iowa



This incident serves to emphasize the sacrifices some people make to have TV. It should also point out that, as long as people feel this way, it isn't necessary to repair sets at cut rates.—Ed.

Dear Editor:

I'd like to get a copy of your "Cross Reference Guide on Fusible Resistors." Why don't the set manufacturers state the value of this resistor on the tube chart they mount inside the receiver cabinet? To me, that is just as important as the tube type numbers.

WALTER A. RINDY

Mayville, N. D.

Perhaps they haven't realized what a problem it's been, Walter. Let's hope publication of the "Guide" and knowledge of the tremendous demand we've had for reprints will serve as a gentle hint. Your copy is on its way.—Ed.

Dear Editor:

The absence of cartoons in your February issue makes me very, very unhappy.

Every month, after the men in our shop have read the PF from kiver to kiver, I am allowed to (1) file the "Previews of New Sets," (2) make note of the latest tube test data, and (3) send for the "literature circled below." Then, and only then, may I cut out the little cartoons and paste them on the walls of our shop. We and our customers are used to

*designed by and for the technician*

**NEW  
1959  
EDITION  
\$1.85**



This new Handbook was designed especially for the technician. Planned for on-the-job use, it is compact, handy, rugged . . . lies flat when open. Its modern styling permits quick, easy reference. And, of course, it is up-to-the-minute, complete in one volume . . . with data for receiving, special and picture tubes as well as semiconductors. Get your copy today from your CBS-Hytron distributor.

*Reliable products through Advanced-Engineering*

**CHECK THESE FEATURES**

- 550 pages
- 1050 receiving tubes
- 390 TV picture tubes
- 270 special-purpose tubes and semiconductors
- Comprehensive data, popular types
- Reference data, seldom-used types
- Appendix especially for technicians



**Engineer's Handbook**

**NOW TWO VOLUMES . . . . . \$10.00**

**Additional hard-cover binders:  
\$3.00 for 1, \$5.50 for 2.**

This modern Handbook has expanded into two volumes. It includes receiving, special and picture tubes and semiconductors. Features are: Complete EIA engineering design data on current tubes • tabulated quick-reference data for seldom-used types • 375 two-color design curves • over 700 pages, two colors • handy 8¼ by 9½ inches • sturdy hard covers • 16-ring metal binders • appendix • supplement service available. Order direct.

**CBS-HYTRON, Danvers, Massachusetts**  
A Division of Columbia Broadcasting System, Inc.



**"LOOK, BUSTER! ... WHY DON'T YOU  
GET OFF THAT BEADS AND TRINKETS  
KICK AND BRING US SOME  
WEBSTER STEREO-CERAMICS"**

Aborigines, audiophiles — everyone would be *demanding* Websters if they knew these Stereo-Ceramics play those cherished 78's, standard LP's and new stereo disks with an *extra* measure of high quality reproduction. So tell 'em and install 'em every chance you get. And be sure you carry a good stock of all Stereo-Ceramics on hand — load up your service kit, too.

Extra profits for you in stereo conversion — check the "Service Center" at your jobber.



**SC-3D Stereo turn-under** —  
Frequency response,  
30 - 15,000; Output, 0.5V;  
Compliance, 2x10 cm/dyne;  
Channel separation, 20 db;  
Stylus, .7 mil diamond,  
3 mil sapphire. **\$21.00\***



**SC-2D Stereo single needle**  
— Frequency response,  
30 - 15,000; Output, 0.5V;  
Compliance, 2x10 cm/dyne;  
Channel separation, 20 db;  
Stylus, .7 mil diamond.  
**\$18.50\***



**MC-2 78 rpm single  
needle** — Frequency  
response, 30 - 15,000;  
Output, 0.5V;  
Compliance, 2x10 cm/  
dyne; Stylus, 3 mil  
sapphire. **\$7.50\***

\*List price complete with bracket — standard discounts apply

**ELECTRONICS DIVISION**  
**WEBSTER ELECTRIC**  
our **50**th year  
**RACINE - WIS**

franklin adv. Y-135

this procedure, and YOU have upset our amusing way of life.

MRS. C. E. MANLEY

San Jose, Calif.

*Cheer up! We have no intention of doing away with cartoons. It's just that we have to omit one here and there to make room for an article which runs a little longer than anticipated. We must, so to speak, finish all the "meat" before we can have any dessert. We're firmly committed to using cartoons, however, having built up a stockpile big enough to keep you chuckling for at least a year.* —Ed.

Dear Editor:

I note with regret the discontinuance of the *Subject Reference Index* that used to be found at the bottom of the contents page. This was very useful for quickly locating data. In fact, I wish you'd carry this idea further and print a subject index on the *outside front cover* so that a serviceman could search a file of PF REPORTERS in a hurry for specific data.

J. J. HANCOCK

Keokuk, Iowa

*Information in past issues can be located most quickly with our annual Subject Reference Index, which has been published as a separate pamphlet for the last couple of years. Copies are free simply for the asking.*

*If you'd rather refer to the cover, why not make appropriate notes as you read each issue. These can be neatly typed and pasted on the front of the magazine.*—Ed.

Dear Editor:

I think your magazine is the best printed; you just can't beat it. Keep up the good work.

DONALD ELLWOOD

Detroit, Mich.

*Thanks for the kind words, Donald (also, the 3-year subscription renewal). Modesty keeps us from saying more.*—Ed.

Dear Editor:

The day after I received your December issue, I had a service call on a Sylvania Chassis 1-537-1, the same one you described in *Video Speed Servicing* that month. It had a complete loss of vertical sweep, and the trouble was a short in the .001-mfd capacitor from the oscillator grid to ground—just as described in your article.

Then, about a month later, I serviced a twin to this set. The trouble was exactly the same, and so I replaced the .001-mfd capacitor in this case also. To my astonishment, this did not remedy the trouble. I got busy with the VTVM. Checking pins 7 and 6 of the 10DE7 oscillator tube, I found no voltage at either place. Finally, I changed a .22-mfd capacitor wired from pin 6 (the oscillator plate) to ground; this replacement restored the raster and got the set operating normally again.

I thought this experience might be of interest to someone else who might run into the same thing.

EUGENE BEST



Schenectady, N. Y.

# SAVE $\frac{1}{2}$ THE TIME

## Make Twice The Profit!

### in TV Trouble-Shooting

**THIS EASY  
SIGNAL INJECTION  
POINT-TO-POINT  
DIRECT VIEWING  
WAY**

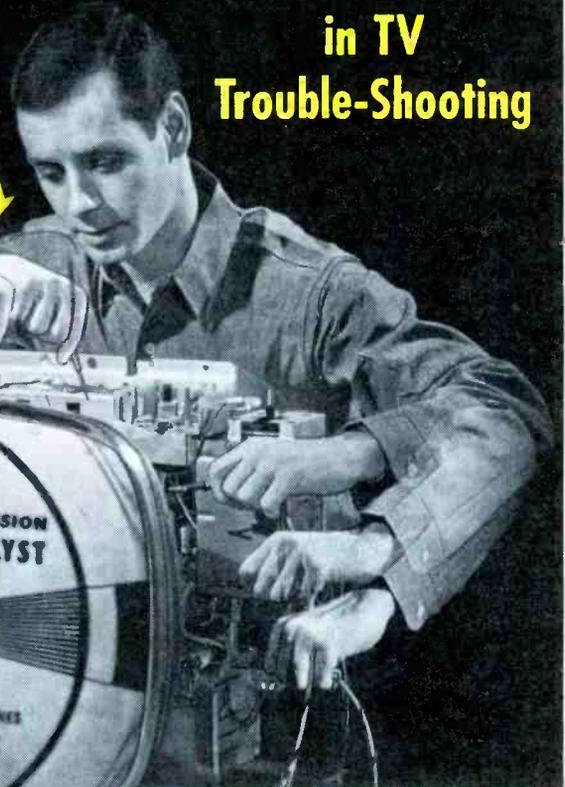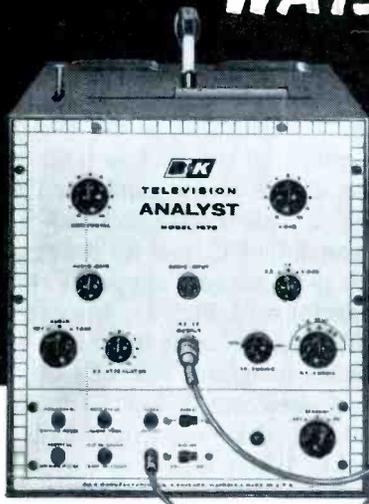

**MODEL 1075**



# TELEVISION ANALYST


### New Technique Makes TV Servicing Easier, Faster, More Profitable

Thousands of service technicians already save thousands of hours every day with the amazing B&K TELEVISION ANALYST. Enables you to inject your own TV signal at any point and watch the resulting test pattern on the picture tube itself. Makes it quick and easy to isolate, pin-point, and correct TV trouble in any stage throughout the video, audio, r.f., i.f., sync, and sweep sections of black & white and color television sets—including intermittents. Makes external scope or wave-form interpretation unnecessary. Enables any serviceman to cut servicing time in half, service more TV sets in less time, really satisfy more customers, and make more money. Color generator provides both rainbow pattern and color bars.

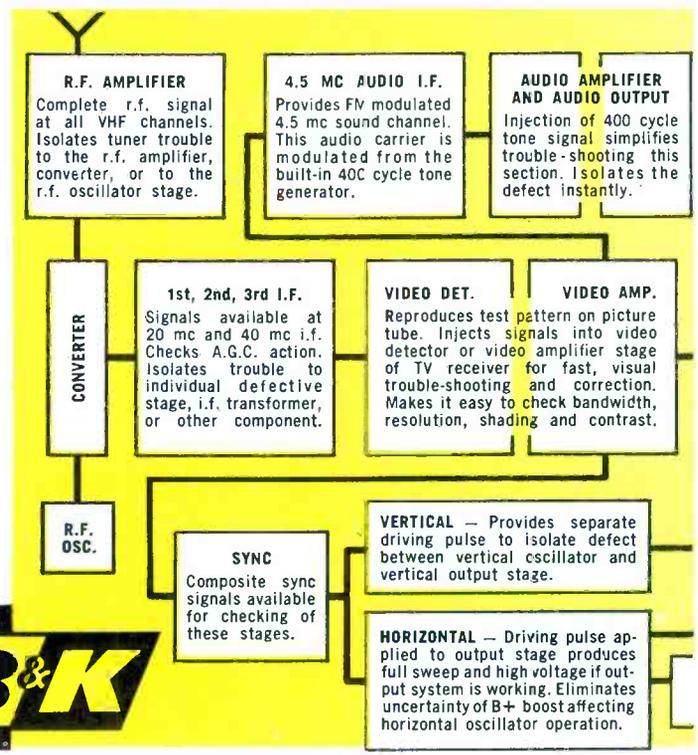**MODEL 1075 TELEVISION ANALYST.** Complete with standard test pattern, white dot, white line, and color-bar slide transparencies, and one clear acetate. Net, **\$259<sup>95</sup>**

See your B&K Distributor or Write for Bulletin ST21-R

**B & K MANUFACTURING CO.**  
3726 N. Southport Ave. • Chicago 13, Illinois  
Canada: Atlas Radio Corp., 50 Wirgold, Toronto 10, Ont.  
Export: Empire Exporters, 458 Broadway, New York 13, U.S.A.



# across the

# BENCH

by Stan Prentiss

In December and February, I described two series of receivers—the Capehart CX-33 and the RCA KCS47. A healthy percentage of these sets are still playing an important part in home entertainment, and since space didn't permit telling their stories completely, the remaining notes and waveforms for both these receivers comprise this month's column. As an added attraction, there are some waveforms taken between several points with rather large differences in DC potentials, demonstrating the practical use of DC amplifiers in an oscilloscope. In future installments, more instrument techniques will be described to help you make sure that "old TVs never die."

## Updating the Capehart CX-33DX

Just recently, I obtained one of these excellent receivers for the modest sum of \$25.00. It had a beautiful cabinet, but also some minor electrical defects that, confided the owner, consisted of merely a "bad vertical condenser in the tuner." Happily, the high and low voltage supplies were just what they should be. IF, sync, and AGC voltages were restored to normal by re-

and *No-Noise*. Replacing the channel strips, I air-checked the receiver on all local stations. Response was uniform and there was signal strength to spare. After a few minutes of operation, however, there was noticeable vertical jitter in the picture. This, obviously, was the real difficulty. The only trouble in the tuner had been tarnished contacts.

## Oscilloscope to the Rescue

With the receiver connected to the shop antenna, the first waveform I took (Fig. 1) was at the end of the PC-100 integrator network. Instead of the normal 25 volts peak-to-peak, its amplitude was hardly 6 volts. This meant the trouble was either ahead of or in the integrator circuit itself. Since the DC supply had already been inspected and found adequate, the signal circuits were obviously responsible. Switching the oscilloscope cable to the DC input, I compared the relative positions of the signals across capacitor C60 in Fig. 2. This initial check indicated a substantial DC level for the signal at the plate of sync clipper V14 (top waveform of Fig. 3); however, the difference in levels for it and signal on the integrator side of C60 (bottom waveform of Fig. 3) made me suspect that capacitor C60 was leaky. While replacing C60, I also replaced C59 (the .01 mfd to ground). Now, the DC-level separation between the two waveforms appeared as in Fig. 4.

The next point of inspection was on either side of C63, the coupling capacitor from the plate of the vertical multivibrator (Fig. 5) to the grid of the vertical output. Considering the differences in their DC potentials to ground (-85V and +275V), the spacing of the waveforms was again a little too close (Fig. 6), and their negative portions

• Please turn to page 66

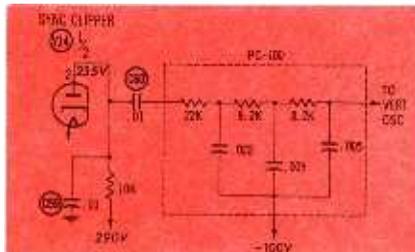


Fig. 2. Partial schematic showing the location of sync coupling capacitor C60.

placement of some resistors and capacitors, plus a tube. Handling of the horizontal-sync discriminator, horizontal-oscillator and discharge, damper, and horizontal-output circuits was routine; I simply replaced all the paper coupling and bypass capacitors and checked the values of individual resistors. This is the best way I know to insure that these highly critical circuits keep operating for a long, long time. I also checked tubes very carefully for Gm and leakage.

When these circuits were all in good order, I turned to the task of tackling that "bad vertical condenser in the tuner." I first tested the RF and oscillator-mixer tubes, then removed most of the oscillator and RF channel strips and measured the value of the RF plate-load resistor. Following this, the tuner was carefully cleaned with pressurized *Hush*

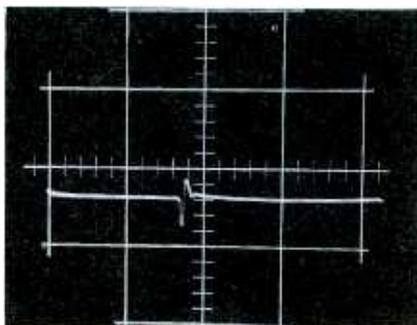


Fig. 1. Defective waveform at the output of the vertical integrator assembly.

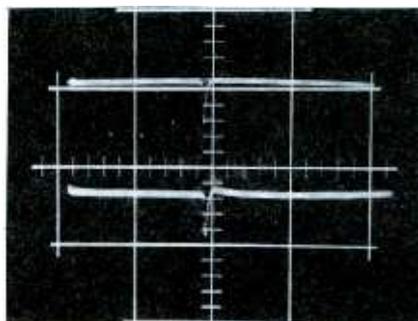


Fig. 3. Lack of separation between waveforms indicates leakage in C60.

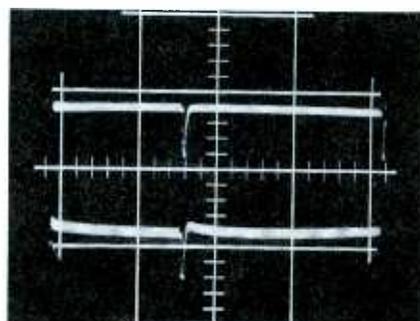


Fig. 4. Normal separation between the waveforms when C60 has no leakage.

Top Name in Portable Radio Battery Sales!



**BURGESS BATTERIES**

WITH

*"Lasting Freshness!"*

FOR **ALL** RADIOS

*Powerize* **YOUR SALES!**



BURGESS BATTERIES supply you with a complete line of the finest portable radio batteries available. Powerful Burgess Batteries are fresher when you get them, fresher when you sell them. You make more initial sales, plus pulling increased repeat business. Burgess — always the best in batteries for tube model portable radios — now leads the field with the finest batteries for transistor type radios!

*Depend on BURGESS the Complete Line!*

*More Selling Power to You!*

**1959 BURGESS PORTABLE RADIO BATTERY PROMOTION AIDS**



MOTION DISPLAY  
Brand New in '59



STEEL FLOOR STAND



WIRE COUNTER RACK




FLOOR STAND



PANEL DISPLAY



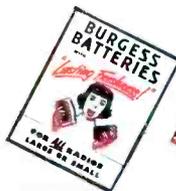**NEW!**  
"Lasting Freshness"  
WINDOW BANNER



**NEW!**  
COUNTER  
CARD



NEW 6 PAGE  
CATALOG



NEW SUGGESTED  
DEALER PRICE LIST



Brand New **ANOTHER BURGESS FIRST IN '59**  
COMPLETE POCKET REFERENCE MANUAL


Contact Your **BURGESS** Distributor For Full Details Today!

**BURGESS BATTERIES**

**BURGESS BATTERY COMPANY**  
FREEPORT, ILLINOIS  
DIVISION OF SERVEL, INC.
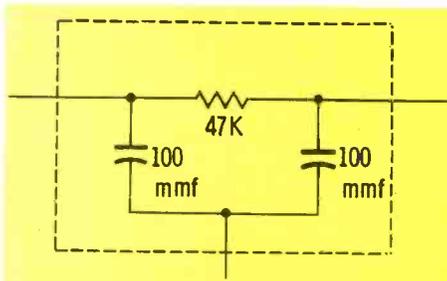
## DIODE FILTER

By using the service scope and signal generator, components in a diode filter can be checked without unsoldering any leads. Set the scope to sweep at about 60 to 100 cps and connect the vertical input leads to the output of the filter. Apply a tone-modulated signal to the IF stage ahead of the filter and check for the presence of a detected signal. A signal indicates that the resistor isn't open and the capacitors aren't shorted. Switch off the modulation and change the scope's sweep frequency to 100-250KC. Also check for the presence of RF signal at the output of the detector. No signal means the capacitors are good. If the unit is out of the circuit and you desire to test the capacitors for value, simply connect the outer leads together and test for total capacity between this junction and the center lead.



AEROVOX PA - 97  
CENTRALAB PC - 50  
C D 111TM1  
ERIE 1403 - 01  
SPRAGUE D - 1

# PRINTED CIRCUIT COMPONENTS

Assemblies of multiple electronic components, encapsulated in a thermo-setting plastic and equipped with either spear-like terminals or wire leads, are to be found in almost every radio and TV receiver manufactured in the past couple of years. Greater application of printed wiring boards has resulted in increased use of these assemblies; some TV receivers employ as many as 6 to 10. This pictorial coverage will acquaint the serviceman with the characteristics of the


most often used units.

Generally speaking, resistors used in packaged units are rated at  $\frac{1}{8}$  to  $\frac{1}{4}$  watt with value tolerances of  $\pm 20\%$ , while capacitors are rated at 500 WVDC with value tolerances of  $+50$  and  $-20\%$ . Some of the least critical capacitors, such as audio couplers, are rated  $+80$  and  $-20\%$ . When testing these units with ohmmeters or capacitance bridges, be sure to consider tolerance ranges.
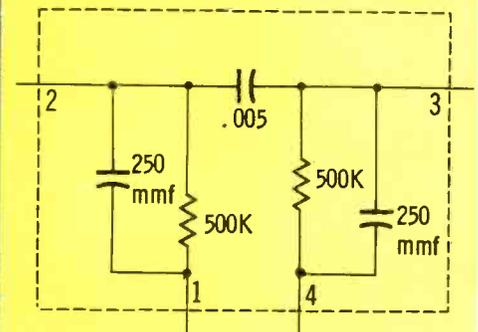
## TRIODE COUPLING

This four-lead network contains all of the components that link the audio-power and voltage-amplifier stages in many AC-DC radios. Checking this unit involves, in addition to the scope and signal generator, a VTVM plus duplicates of the tubes used at both ends. Lead 2 normally connects to the plate of the voltage amplifier, lead 1 to B+, lead 4 to B-, and lead 3 to the grid of the power amplifier. First of all, measure the voltage at leads 2 and 3. The reading at 2 should be lower than B+, while the reading at 3 should be 0 volts. If you get a reading at lead 3, replace the output tube and check the reading again. The presence of voltage indicates a leaky coupling capacitor or an open grid resistor—the ohmmeter section of your VTVM will quickly tell you

AEROVOX PA - 112 - 1  
CENTRALAB PC - 70  
C D 112 TM1  
ERIE 1406 - 01  
SPRAGUE T3  
TOBE 112TM1




which. A lack of voltage on lead 2 can be caused by a defective tube or an open plate resistor. Check the resistor with an ohmmeter to tell which. If open or increased in value, it can be replaced with an external unit of correct size, providing all other components check good. Apply

an audio signal to lead 2 to test the balance of the unit. Sound from the speaker is a good sign; install the external plate-load resistor and check circuit operation. A check at lead 2 with the scope will tell you if the RF bypass capacitors are still doing their job.
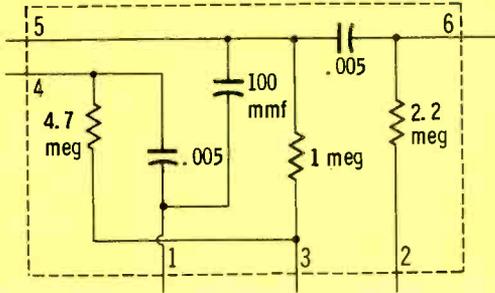
## PENTODE COUPLING

This unit is used in a good many portable radios and is very similar to the triode unit. It has two more leads (6 instead of 4 for the triode unit) to accommodate the screen grid circuit of the pentode audio amplifier. The screen-grid bypass capacitor can be checked by applying an audio signal to the control grid of the pentode and checking for the presence of an audio signal at lead 4. No signal indicates a good capacitor. Check the balance of the network as outlined for triode units.



AEROVOX  
CENTRALAB  
C D  
ERIE  
SPRAGUE  
TOBE


PA - 117  
PC - 91  
114TM2  
1407-03  
P - 2  
114TM2

## DE-EMPHASIS NETWORK

The de-emphasis network in the FM detector output circuit of a TV receiver frequently appears in encapsulated form. The original may be a three-terminal type (omit terminal 3) or in the form shown. Install the type shown if terminal 3 is used in detector alignment procedures. To test this network, apply a tone-modulated FM signal to a stage and check network as specified under "Diode Filter."


AEROVOX  
CENTRALAB  
SPRAGUE

PA - 425  
PC - 186  
V - 17

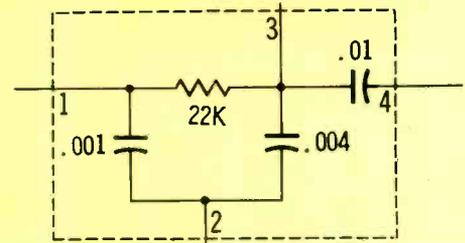
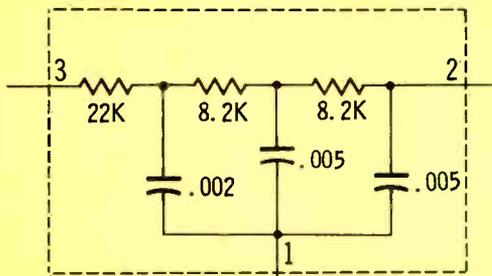
## VERTICAL INTEGRATOR

This three-lead unit, having been used in at least 175 different models (well over 7 million sets), can be considered the standard of the industry. No shop should be without at least one in the stock room. To check these units, operate the set, disable the vertical oscillator, and check the output for a signal that is roughly  $\frac{3}{4}$  of the amplitude of the signal applied to the integrator. To test the three filter capacitors and the DC blocking unit for leakage, remove power, disconnect lead 2 and measure from it to chassis. The reading should be infinite even on the highest range of your ohmmeter. If the DC blocking capacitor is in the output network, disconnect lead 3 and measure from there to chassis. Again, the reading should be infinite. A resistance check between leads 2 and 3 should produce a reading of 38.4K ohms  $\pm 20\%$ .



AEROVOX  
CENTRALAB  
C D  
ERIE  
SPRAGUE  
TOBE


PA - 110  
PC - 100  
115TM1  
1405 - 01  
V1  
115TM1


## RETRACE SUPPRESSION

This is a familiar network to the serviceman working on Admiral sets—not that they are prone to fail too often, but simply because, outside of vertical integrators, this was about the first printed assembly used in TV receivers. Two quick checks with a scope and one with a VTVM can tell you all about this little unit. The signal at lead 2 should be about half that at lead 1 when checking with the scope. The VTVM should indicate zero volts on lead 2. Any voltage here indicates a shorted or leaky coupling capacitor. The checks just outlined should be made when you have high voltage but no raster, and they should be made before you try to sell the customer a new CRT.

CENTRALAB  
SPRAGUE

PC - 314  
RS - 3

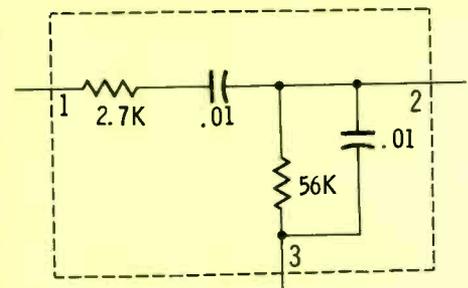

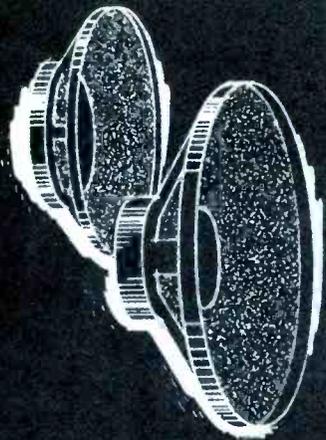

## AUDIO FACTS

servicing

# HIFI

equipment  
part 4

### Equalizers and Preamps

The output signal of a magnetic phono cartridge is very low in amplitude, often no more than 6 to 15 millivolts. This low-level signal must be amplified considerably before it can be applied to a power-output stage. Because of noise considerations, the first stage of amplification must be a high-gain, low-noise circuit called a preamplifier. It is desirable to use a very short signal lead between this initial stage and the magnetic cartridge; for this reason, the preamp is sometimes built on a separate chassis complete with power supply and mounted in the same cabinet with the turntable or changer. However, because there are several controls which must be adjusted for optimum playback, the

preamp stage is most often included with tone-control and equalization stages in a single unit called a *Pre-amplifier, Tone Control Amplifier, Master Audio Control*, etc.

### Why Equalization?

Signal output from a phono cartridge is a function of needle velocity — the greater the velocity, the greater the output voltage. This means that for a given output, groove excursions must be greater at low frequencies than at high frequencies. If a record were cut so that low-frequency signals had the same amplitude as high-frequency signals, the width of record grooves would have to be much wider than they now are, and it wouldn't be possible to get several musical selections on a single 10" or 12" record. In addition, low-level, high-frequency signals are more prone than any other to noise pickup. It is desirable to increase the amplitude of high-frequency signals to overcome this tendency. Records are cut with reduced low-frequency groove excursions to conserve record space, and increased high-frequency groove excursions to minimize noise pickup. This is accomplished by decreasing the amplitude of low-frequency signals and increasing the amplitude of high-frequency signals before applying them to the recording cutter. For correct playback, therefore, the cartridge output signal must undergo a reversed version of this amplification difference. This is done by the equalizer circuits in the pre-amplifier stage.

All recording companies do not use the same amount of treble boost and bass attenuation. As a result, some form of variable equalizer must be used. The equalizer may be a separate unit inserted between the phono cartridge and the preamp, or it may be part of the preamp. It consists of resistors and capacitors, with a switch for the selection of various combinations. In every position, basic functions are the same—boost the lows and attenuate the highs. The only differences are in the degree of amplitude change and the frequencies at which the change starts.

### Bass Boost

Bass playback equalizers boost the lower frequencies using a cir-

cuit resembling the one shown in Fig. 1A. R3 and C1 are selected by switching, and determine the frequency at which bass boost begins (called *turnover frequency*). The combination of R2, R3 and C1 determines the degree of boost. As signal frequency decreases, Xc increases, causing an increase in the output voltage and effectively giving bass boost. In some variations of the circuit, R1, R2, or R3 may be omitted. None of these changes, however, alter the basic action of the circuit.

If R1 or R2 is open, or if C1 is shorted, there is no boost. In the

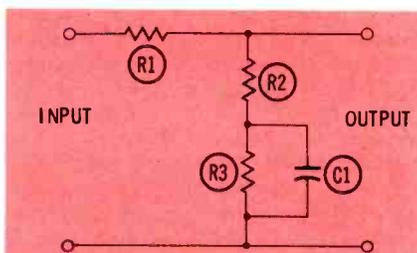


Fig. 1A. Typical bass-boost circuit.

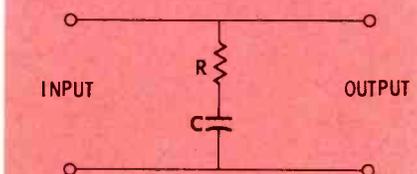


Fig. 1B. Circuit for treble attenuation.

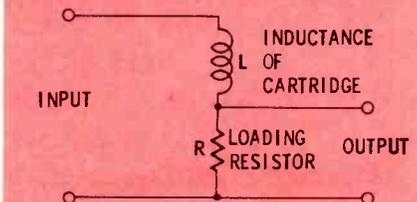


Fig. 1C. Roll-off provided by L and R.

latter case, however, signal amplitude is decreased below its normal level. If C1 is open, the impedance across the output is considerably higher, resulting in greater voltage output, but there is a loss of bass boost. If R3 should open, boost will be excessive and hum level will increase.

### Treble Attenuation

A basic circuit for treble attenuation (called *roll-off*) is shown in Fig. 1B. R and C may be in parallel, but results are similar. The value of C governs the frequency at which roll-off begins, and R determines the amount of roll-off. For each setting, R and C have different values.

• Please turn to page 74

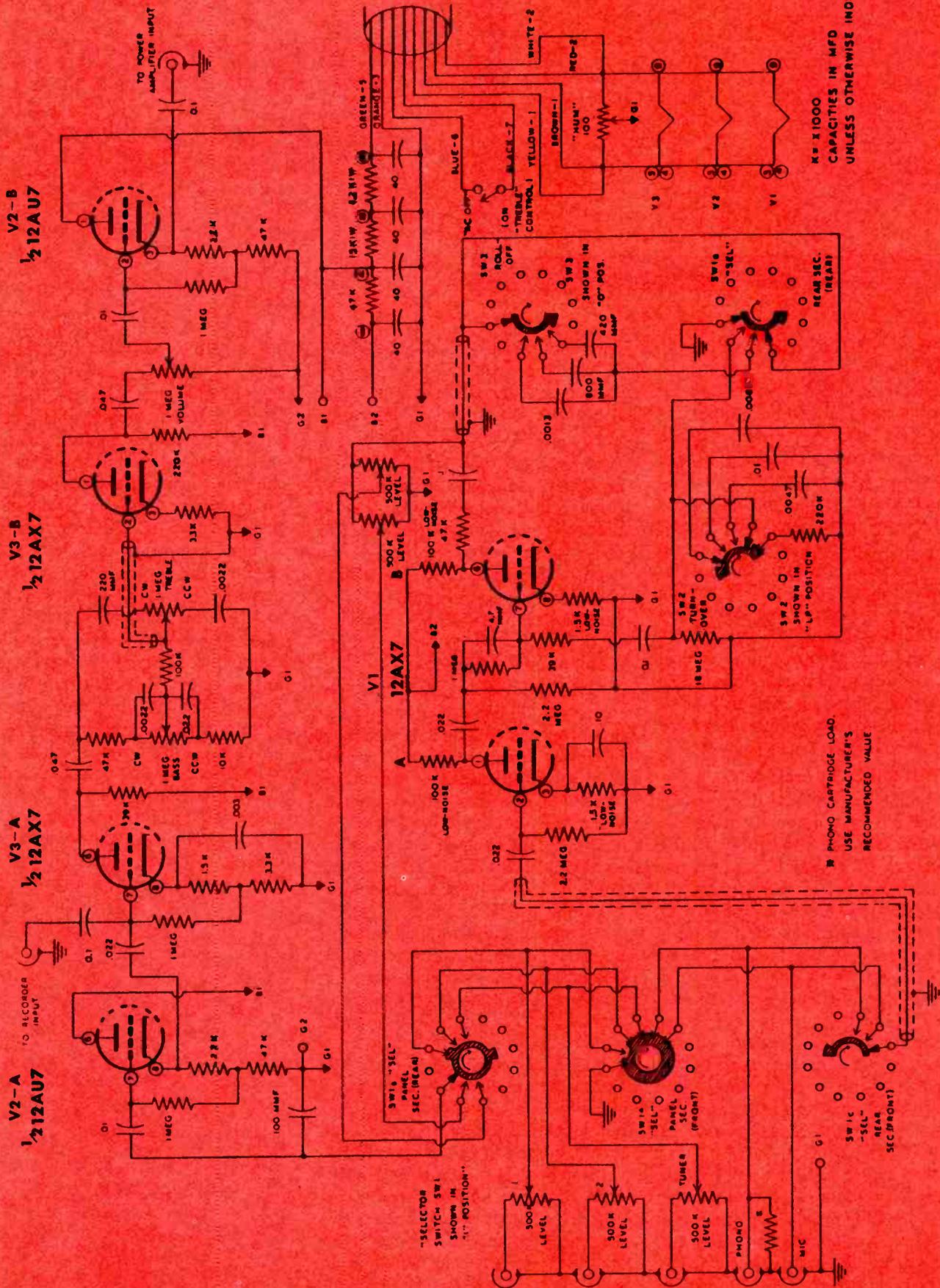


Fig. 2. Typical Hi-Fi preamp has switched inputs and cathode-follower output.

# BENCH SERVICING NEW SETS

by Thomas A. Lesh



Fig. 1. *Predicta* table model has picture tube fastened to top of cabinet.

When you are disassembling an unfamiliar TV set and getting the chassis ready for bench work, it usually takes a certain amount of trial and error to figure out the answers to questions such as the following: Are there any unseen "catches" to cause complications while you are pulling the chassis? How should you place the chassis on the bench for maximum stability?

To save you some time in solving problems like these, we took a few of the 1959-model TV sets into the lab and put them through typical bench-setup procedures. This article reports the results of our analysis of one of the new Philco models; future articles will cover other new sets.

## Philco Chassis 9L37

The Philco *Predicta* design, with the picture tube mounted outside the cabinet, represents the most drastic change in TV styling in many years. Servicemen are naturally curious to know how these sets compare with conventional receivers from a servicing standpoint. We'll provide many of the answers as we explore the table model shown in Fig. 1 (Chassis 9L37), reported to be the best-selling set in the *Predicta* series. Coverage on another model, the *Tandem* (with picture tube connected to chassis by a long cable) is scheduled for the May *Previews of New Sets* department.

With its 21" CRT looming above a small, fragile-looking cabinet, the receiver in Fig. 1 appears somewhat top-heavy — especially to someone who knows that a picture tube is a pretty hefty object. This impression is misleading. The set is actually quite stable because the cabinet is

considerably heavier than it looks. If you approach this set from the front when lifting it, you'll find that it is easier to carry than many conventionally-styled table models.

If you have to do some shop work on this model, you'd be better off to bring in the whole set rather than to pull the chassis. It's not practical to use a substitute picture tube on the bench; standard 110° tubes and check tubes are not compatible with Philco's "semi-flat" 21EAP4 picture tube, which has a heater-voltage rating of only 2.35 volts.

Considering the shape of the cabinet, it should come as no surprise to learn that the chassis is horizontally mounted. The rear panel of the cabinet can be taken off to permit removal of the chassis. Only two screws are employed to fasten the chassis to the cabinet, and both are located just inside the rear cover; you'll find no bolts or screws underneath the set. To prepare the chassis for removal, pull off all control knobs; also, reach inside the cabinet and unfasten the retaining clips that hold two long leads against the right side. (One is for the front-mounted speaker and the other for video signal input to the CRT.) Once the wires are freed from these clips, all interconnecting leads will have ample slack to allow the chassis to be taken all the way out of the cabinet.

From reading preliminary descriptions of this receiver when it was first introduced, we somehow got the idea that the chassis might be mounted on rollers traveling in tracks or guides. No such arrangement is used, however; the chassis is simply hauled out of its resting

place with a rearward pull, helped along by sled-like runners. Only one minor snag stands in the way—a length of plastic tubing, which serves as a socket for the built-in antenna, projects inward from the left wall of the cabinet, where the control panel on the chassis will run afoul of it. To cope with this situation, pull the antenna completely out of the socket; then the tubing will be flexible and can be bent out of the way.

After you have pulled the chassis, rest its front edge on the rear sill of the cabinet for greatest convenience in servicing topside components. (CAUTION! This is a "hot" chassis, and an isolation transformer should be used.) Power supply filters and other heavy-duty components underneath the chassis can be checked while the receiver is operating, if you carefully swing the chassis up into the position shown in Fig. 2. The chassis is not self-supporting

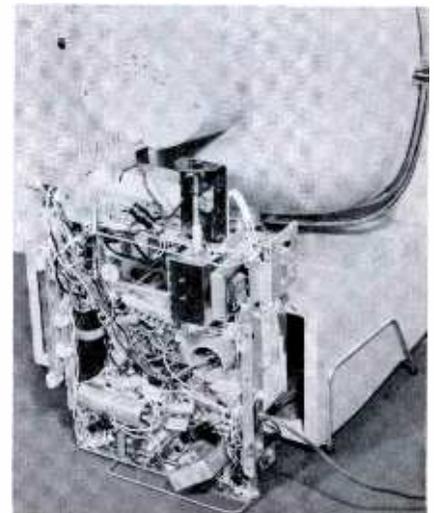


Fig. 2. Chassis can be operated while upended on bench behind the cabinet.

when raised up on end, but it can be safely leaned against the "dog-house" on the back of the CRT housing.

No extension leads are necessary to operate the receiver when it is arranged as in Fig. 2. Extensions *would* be required if you wanted to get the chassis into a position that would permit you to reach the top and bottom sides with equal ease—but there is no particular advantage to such a hookup. Recent Philco chassis are laid out so that troubleshooting can be done with a minimum of back-and-forth neck-craning. For example, the printed wiring boards in *Predicta* sets are mounted above a solid metal chassis pan and are designed to be worked on from one side only. Parts such as resistors and capacitors should be removed by clipping the pigtail leads close to the component body, and then using the lead stubs that remain on the chassis as points of attachment for the leads of the replacement component. Printed-circuit components with multiple leads, which are widely used in the 9L37 chassis, can be removed by either clipping or heating the leads on the top side of the board. Leads on these parts are relatively easy to remove from above, since they are not crimped underneath the board.

One thing is clear: For efficient servicing of this chassis, the practice of disconnecting and testing individual parts must be held to an absolute minimum. This means you'll have to *use your noodle* and obtain most of the needed information by analyzing the results of in-circuit checks such as voltage and waveform readings. Philco has attempted to make these tests as convenient as possible. A number of lugs around the edges of the wiring boards serve as handy test points; in addition, all tube sockets on these boards are constructed so that the tube pins can be reached with a test prod from the top side. The latter feature, in particular, is extremely helpful—as long as you remember that the pin numbers run *counterclockwise* around the socket when you are looking at it from above.

Some of the most important test points on top of the chassis are indicated in Fig. 3. The colors of the attached leads are listed to help you locate the correct points on an actual

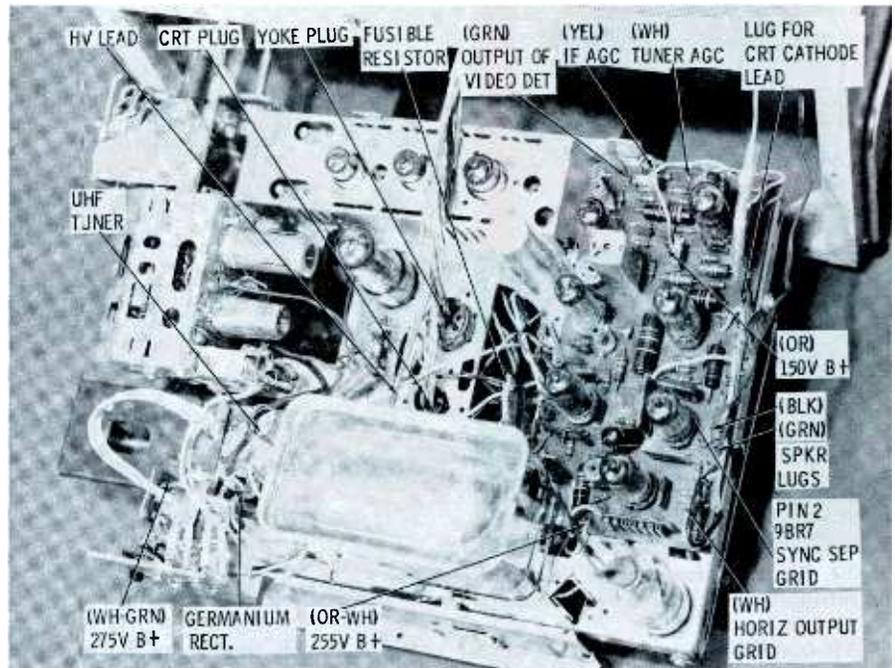


Fig. 3. Topside view of Philco Chassis 9L37 showing important test points.

chassis.

If you are familiar with other recent Philco models, you will recognize the 9L37 chassis as being practically the same as the 9L35 used in the "Advanced '59'er" receivers. This earlier chassis was mounted vertically inside a more-or-less conventional cabinet. When adapted for use in the *Predicta* table model, the VHF tuner and operating controls were moved to new locations and the "doughnut hole" in the center of the chassis was covered with a metal panel to provide for yoke and CRT socket mountings.

Voltages and waveforms on the base pins of the picture tube can be checked by inserting a sharp-pointed prod into test jacks in the CRT base socket. Boost B+ can be conveniently measured at the accelerating anode (pin 6), and the vertical retrace-blanking pulses can be viewed at the control grid (pin 3). The tube base is accessible when a small trapdoor in the rear cover of the CRT housing is removed.

The high-voltage anode lead is plugged into a hole on the top side of the high-voltage rectifier tube socket. To gain access to this plug-in connection, pry off the "cocoa can" lid of the high-voltage cage.

The IF strip is hidden under a shield at the front of the chassis. To perform service work (other than alignment) in this section of the receiver, remove a half-dozen ¼" hex-head screws from the shield and

lift it off. To reach the screws at the end of the shield, you must first remove two ¼" mounting screws from the control panel and swing it out of the way as demonstrated in Fig. 4.

Note the white plastic grommet in the photo. There are two of these on the front edge of the chassis; their purpose is to mate with two projections on the inside front wall of the cabinet, thereby anchoring the chassis in the correct position.

#### Lead Dress Precautions

Before reinserting the *Predicta* chassis into the cabinet, make sure that everything on the underside is in its proper place. A number of long leads pass below the chassis pan—some across the full width of the front border, and others diagonally across the chassis to the area-selector switch on the rear of the set. If these leads are allowed to hang below the bottom edge of the chassis, they are likely to become

• Please turn to page 78

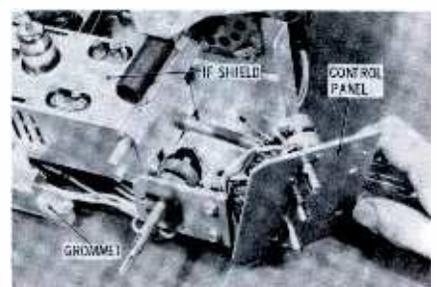


Fig. 4. When removing IF shield, loosen control panel for access to screw.

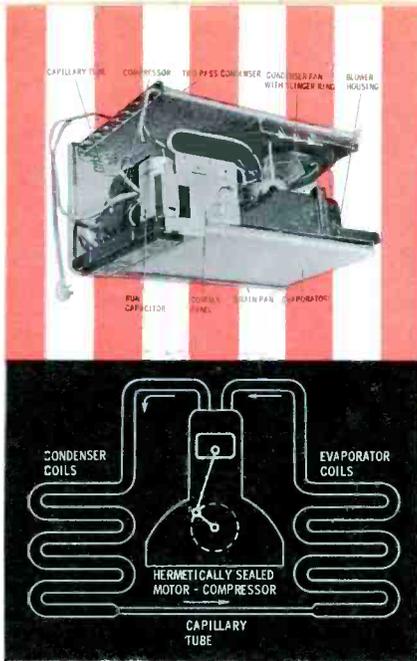


Fig. 1. Diagram showing the flow path of refrigerant used in air-conditioners.

Air-conditioning is assured of a permanent place in our modern electronic-appliance industry. To the consumer, air-conditioning represents a basic requirement for everyday physical comfort; to the technician, it is an opportunity for profitable service.

This article is the first of a two-part series on the operation, repair, maintenance, and installation of the room air-conditioner. Incidentally, the room air-conditioner, or the so-called window unit, is a self-contained, factory-assembled, packaged piece of equipment. It requires only an external electrical supply to be able to cool, dehumidify (remove moisture), circulate, and clean the air in a confined space. Complete air-conditioning may require the addition of heat and/or moisture; how-

# ROOM AIR-CONDITIONER MAINTENANCE

*The first of a two-part series on installing and repairing self-contained units*

*by Joseph Derman and Harold Seaman*

ever, we will touch on these items only briefly, since air-conditioning has primarily come to mean the practical manipulation of summer air to achieve personal comfort.

## How It Works

Cooling is achieved because a chemical, called *Freon*, flows around a mechanical circuit. Briefly, the action is as follows (see Fig. 1): A restrictive element, called the capillary tube, permits liquid *Freon* to vaporize (and expand) at a pre-assigned rate in the evaporator, which is located in the room or output side of the air-conditioner. During this evaporation process, room heat is absorbed by the *Freon*. The compressor, which is driven by a direct-coupled induction motor, draws the *Freon* vapor from the

evaporator, compresses it, and directs it to the condenser. The condenser is located *outside* the space to be conditioned; thus, the gas, hot and compressed, liberates its heat outdoors and thereby becomes a liquid again, completing the cycle. In the succeeding article, we will develop this phase in greater detail.

## The Electrical System

Most air-conditioning units are furnished with power cords having plugs that use a ground connection, as shown at bottom left in Fig. 2. It is recommended that a licensed electrician provide a suitable wall receptacle if one is needed. Some local communities permit the use of an adapter between the three-prong plug and the standard two-element wall outlet. In this case, the ground

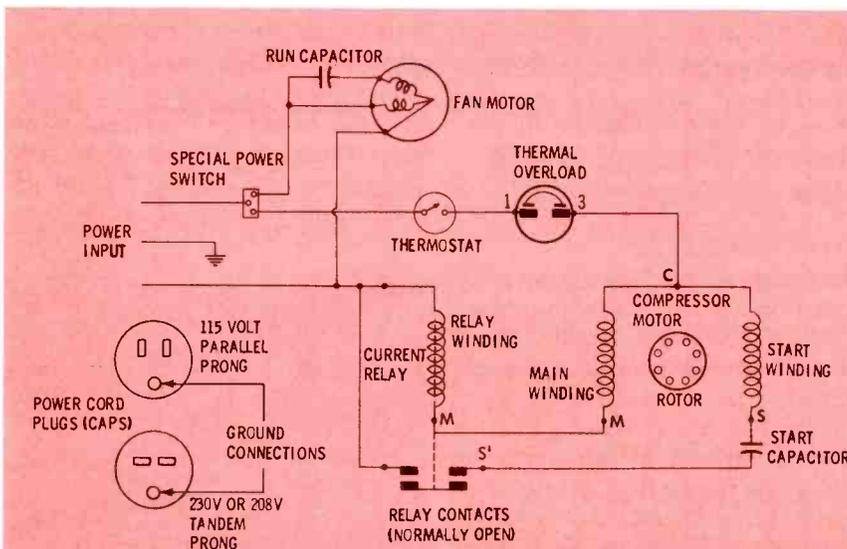


Fig. 2. Electrical circuit for a conventional room air-conditioning unit.

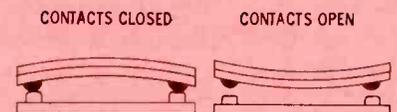


Fig. 3. Thermal overload uses a temperature-sensitive, bimetal-disc breaker.

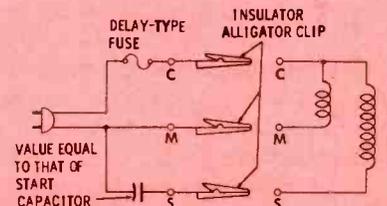


Fig. 4. Test harness for use on standard capacitor start and run circuits.

wire of the adapter must be electrically connected to the wall receptacle. (Be sure to scrape the paint from the screw that secures the adapter wire to the receptacle!)

Obviously, if the prongs of the power plug do not make contact at the receptacle, or the plug is otherwise defective, power will not reach the unit. A voltmeter check at a point beyond the plug is conclusive evidence that power is available. Make sure you have a good ground connection at the receptacle.

#### The Thermostat

As the drawing in Fig. 2 indicates, the thermostat is a make-and-break device. Action depends on the pressure in a vapor-filled tube called the sensing element. If room (ambient) temperature is high, increased pressure will close the contacts, thus causing the compressor to operate. Conversely, when ambient temperature drops, the contacts will open.

Most thermostats are designed so that the customer can control the actuating temperature and choose his own comfort level. In addition, the serviceman can also set the low-temperature operating point by adjusting a screw on the mechanism. (Do not give this screw more than a few turns.) NOTE: It is possible to set some thermostats for "continuous operation"; that is, to keep the contacts closed irrespective of ambient temperature. This position must be used with care, however, as will be explained in the second article.

A simple continuity check (with

power cord removed) can show the effectiveness of the thermostat. Note, however, that the unit must call for cooling before the contacts of the thermostat are actually closed. Grasp the sensing element (bulb) in your hand; body heat will then simulate room temperature and the contacts will close. Make sure the sensing element is in a free air stream and not up against any metal members of the chassis.

#### Thermal Overload

Every compressor is protected against current overload by an automatic resetting device (located on the compressor shell). Fig. 2 illustrates use of the two-terminal, disc-type overload (also see Fig. 3). At a predetermined current level, depending on the particular compressor, the bimetal curved disc will alter its curvature to open the contacts and break the circuit. After the disc cools (and the overload condition has been removed), it assumes its original position with contacts closed. Of course, if the disc continues to break the circuit again and again, the cause of such cycling must be determined.

The compressor should never be operated for any length of time without the thermal overload device. Normally, the thermal overload should show continuity and permit power to reach the compressor. Every time the contacts open, the compressor is being safeguarded against excessive current; if there is no continuity across the overload, it must be replaced.

#### Compressor Motor

The compressor motor is perhaps the most critical, and is certainly the most expensive item in the air-conditioner. It is directly coupled to the compressor and, as previously stated, forces the Freon about the mechanical circuit. As seen in Fig. 2, the compressor motor has a main-winding circuit and an auxiliary (start) circuit which includes the start capacitor. The magnetic field of the main winding and the out-of-phase magnetic field developed by the start circuit are both required for sufficient torque to initiate motor operation. (AC power is connected directly to these stationary or stator windings.) When the rotor reaches a certain speed, current in the relay winding will have decreased sufficiently to permit the start-circuit relay contacts to open. The main winding alone then maintains rotation.

#### Fan Motor

The fan motor may be of the shaded-pole or the permanent split-capacitor type used in Fig. 2. The shaded-pole type has no capacitor; starting is achieved by special internal construction. The motor shown is the induction type and operates in practically the same manner as the compressor motor; there is no relay, however. The fan motor will function if the windings and the capacitor are satisfactory and suitable voltage reaches the motor.

#### Power Source Requirements

The full load voltage *must be* within  $\pm 10\%$  of the rated nameplate voltage. This is most important because, if the voltage is insufficient, the compressor motor will start up too slowly or not at all. In such a situation, current drain will be excessive, the overload device will be actuated and/or the line fuse will blow.

In most dwellings, one or more convenience (wall) receptacles are supplied by a single branch circuit. Each branch has a very definite current limitation, usually 15 amps, or 20 amps if the wiring is more recent. The air-conditioner load (operating, not surge) plus other loads on the same branch circuit must not exceed this limitation. Where the air-con-

• Please turn to page 79

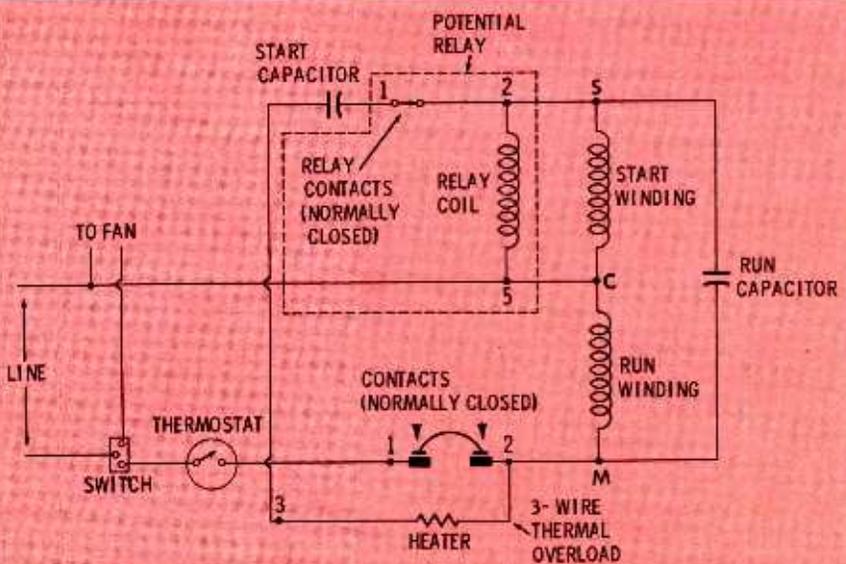


Fig. 5. Alternate circuit using potential relay and 3-terminal overload.

# BRAND NEW!

Another **DOSS** Instrument  
designed to save you time!



## The Pioneer 250 Horizontal Systems Analyzer

Systematically isolates horizontal sweep system troubles in minutes! No need for chassis removal—unit plugs directly into damper and horizontal-output tube sockets. With the set operating, the following in-circuit tests can be made:

- Checks boost filter capacitor
- Checks output-tube screen resistor
- Checks output-tube cathode resistor
- Checks output-tube filament voltage
- Checks damper tube filament voltage
- Checks B+ supply voltage
- Checks B+ boost voltage
- Checks horizontal output tube
- Checks output-tube screen voltage
- Checks screen-bypass capacitor
- Checks output-grid coupling capacitor
- Checks output-tube cathode current
- Checks output-tube cathode voltage
- Checks cathode-bypass capacitor
- Checks output-tube bias
- Checks grid-drive signal
- Checks oscillator frequency in cps
- Checks flyback transformer for defects
- Checks horizontal yoke for defects
- Checks inductance of horizontal yoke

**ONLY \$109.00 net**

Fill in this handy coupon. Order will be credited our distributor in your area.

**DOSS**

**ELECTRONIC RESEARCH, INC.**  
820 Baltimore, K.C. 5, Missouri

**ORDER NOW ON A 30-DAY  
MONEY-BACK GUARANTEE**

If for any reason I am not satisfied with my PIONEER 250, I may return it within 30 days for a full refund.

- Enclosed is remittance of \$109.00  
 Please ship C.O.D.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_



# SERVICING

By Calvin C. Young, Jr.

## Improve Your VTVM

If your VTVM is one of the older models (before uniprobos) and employs pin or banana jacks for common and AC-ohms leads, you probably find yourself reinserting the leads in the jacks more often than you care to admit. Worn banana plugs seem to pop out of their jacks at the slightest provocation. This situation can be remedied in a very simple way — replace the banana jacks and plugs with miniature microphone connectors such as Amphenol 75-1 and 75-3 or Switchcraft 5501F and 5501MF — the latter unit being the male panel connector.

Installation details are shown in Fig. 1. The fiber shoulder washer originally used with the banana jacks can be reused in most cases. The leads that previously soldered to each of the banana jacks must be connected to the center terminals of the new connectors. The finished job should look as shown in Fig. 2.

## Negative Temperature Coefficient

If your experiences have been like mine, you haven't had too much

luck obtaining capacitors with special temperature characteristics from your local distributor. About the only ones I've been able to get consistently are zero and N750 types.

While plowing through a maze of capacitor catalogs, I came across a system for combining zero and N750 units to produce any negative characteristic that might be required. The method is simple, involving only the parallel connection of a zero type and a N750 type. To determine the value of the N750 unit, divide the product of the desired capacity and the desired temperature coefficient by 750. To determine the value of the zero unit, subtract the value of the N750 unit from the desired capacity.

Thus, if you wanted to assemble a 220-mmf unit with a N220 temperature coefficient, you would calculate the value of the N750 component as follows:

$$\frac{220 \times 220}{750} = \frac{48,400}{750} = 64 \text{ mmf}$$

Since 62 mmf is the nearest standard value, subtract 62 mmf from 220 mmf, and you'll find you need a 158-mmf capacitor with zero coefficient. The nearest standard

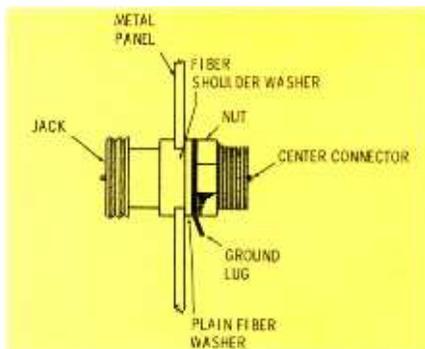


Fig. 1. Installation of miniature microphone connectors improves VTVM value.


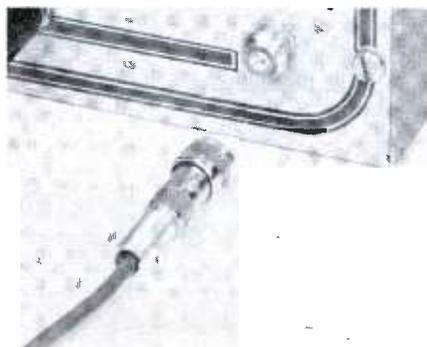


Fig. 2. Finished installation on VTVM showing the AC-OHM lead connectors.

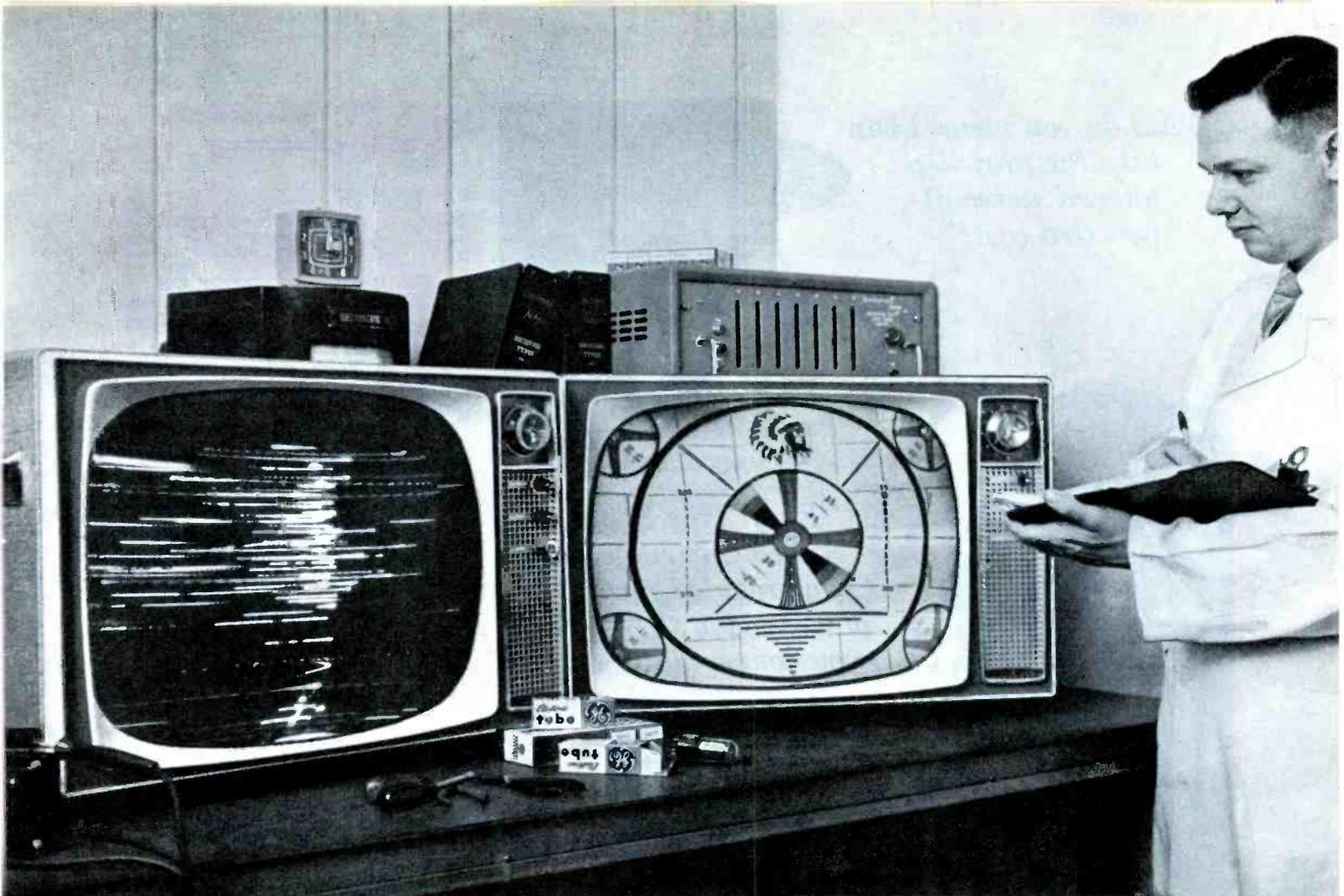

## CUT DAMPER-TUBE ARCING!

Have steady, dependable pictures with the new Service-Designed General Electric 6AX4-GTA (right)!

Side-by-side receiver tests show how prototype horizontal-damper tube occasionally will arc, cathode-to-plate (screen at left), whereas the new General Electric 6AX4-GTA continues to do its job reliably. The reason: a new, 15% larger cathode, with more emission area, consequently a lower operating temperature requirement.

New 6AX4-GTA also has faster warm-up, tapered pins, other improvements. Install this advanced tube to promote customer satisfaction, reduce callbacks. Service-Designed quality through and through! See your G-E tube distributor! *Distributor Sales, Electronic Components Division, General Electric Co., Owensboro, Ky.*

*Progress Is Our Most Important Product*

GENERAL  ELECTRIC

2-111-202

*"What do you mean I can take the first step toward stereo at no extra cost?"*



*"Easy. This Sonotone Stereo Cartridge plays your regular records now...plays stereo when you convert later on."*



## Sonotone Stereo Cartridges

give brilliant performance on *both* stereo and regular discs...and cost the same as regular cartridges.

### Specify Sonotone...here's why you'll hear the difference:

1. Extremely high compliance...also means good tracking, longer record life.
2. Amazingly clean wide-range frequency response.
3. First-quality jewel styli tips—correctly cut and optically ground for minimum record wear.
4. Rumble suppressor greatly reduces vertical turntable noise.

Prices start at \$6.45 (including mounting brackets).

Get details on converting to stereo. Send for free booklet: "Stereo Simplified," Sonotone Corp., Dept. CP-49, Elmsford, N. Y.

**Sonotone** ® © 1959

Electronic Applications Division, Dept. CP-49

ELMSFORD, NEW YORK

In Canada, contact Atlas Radio Corp., Ltd., Toronto

Leading makers of fine ceramic cartridges, speakers, microphones, tape heads, electron tubes.

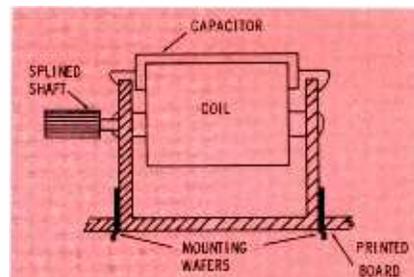


Fig. 3. Mounting details for the horizontal-oscillator coil in Sylvania TV.

value is 150 mmf; thus, you would use this value and select a higher value for the N750 unit, say 68 mmf. Connected in parallel, these two values give you a total capacity of 218 mmf at very near the desired temperature characteristic (within 10% and close enough for all practical purposes). Other values and characteristics would be calculated in the same manner.

### Service Hint on Sylvania 21P101A

The customer had originally complained that this set was completely dead. None of the tubes had open filaments, and the AC switch wasn't defective, leaving as the only suspect a large dropping resistor in the filament circuit. In the shop, a 51-ohm, 30-watt resistor cured the trouble. Everything seemed okay, so the set was placed in the outgoing rack.


Even though it was below zero the next day, the serviceman checked with the customer and made arrangements to deliver the set. In the customer's home, with the chassis back in the cabinet and all the knobs in place, the serviceman found he couldn't get the horizontal oscillator to lock in. In fact, the hold control didn't seem to have any effect at all. In the course of events that followed, the serviceman found that tapping the shaft of the control (connected to a slug in a coil) would cause the picture to pop in and out of sync.

Because the set had already been shop-tested and the balance of the circuits were operating nicely, the chassis wasn't pulled again. Instead, only the suspected coil was removed. A vigorous shake confirmed the previous suspicion; the core was definitely broken, so it was taken to the shop to serve as a guide in obtaining a replacement.

Checks with local parts distribu-
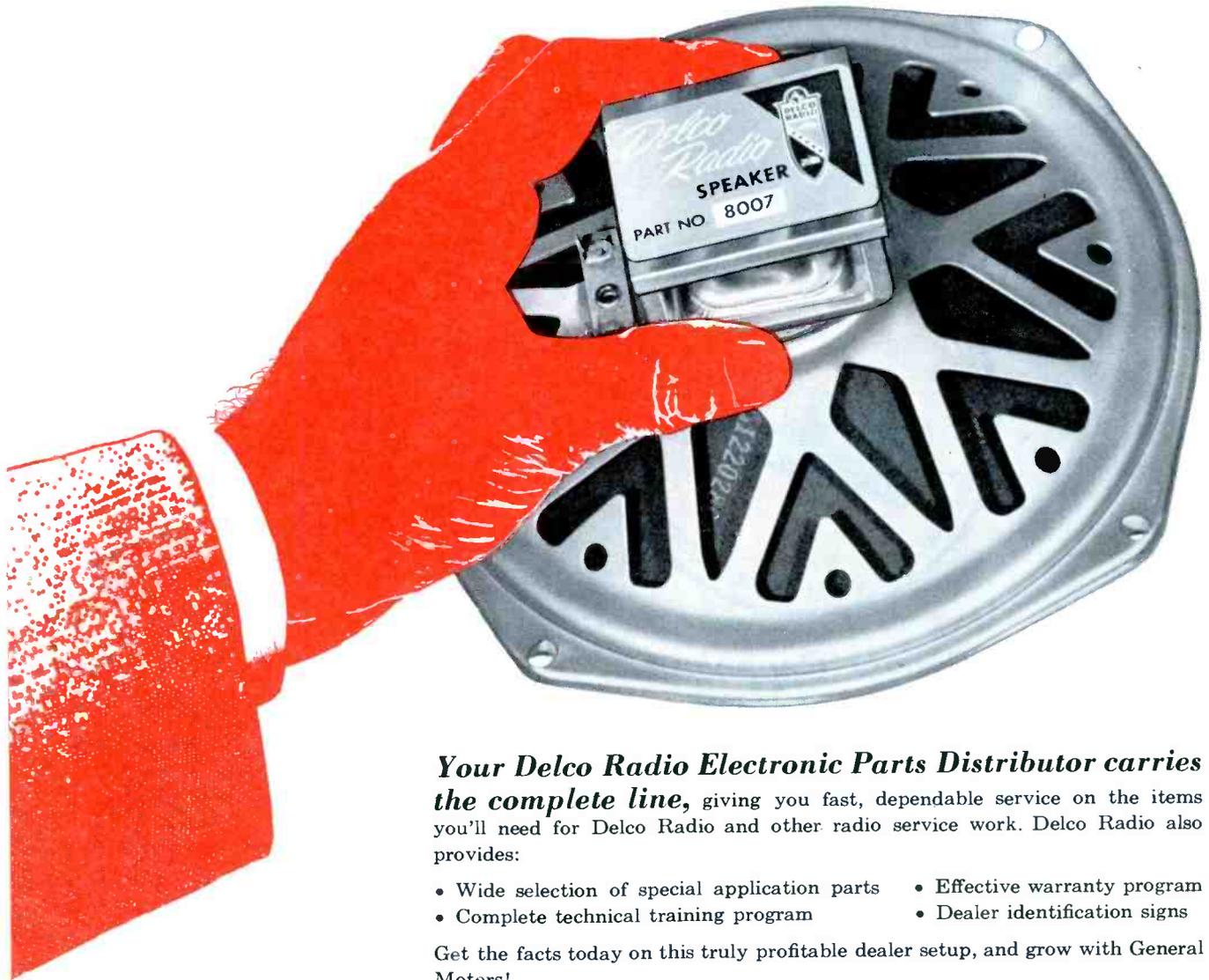
# Use Delco Radio Service Parts!

8-inch "Hi-Fi" speaker, No. 8007 offers the most highs, the most lows, the most watts in a medium-price speaker. Designed for replacement use and high fidelity audio systems.



*Your Delco Radio Electronic Parts Distributor carries the complete line,* giving you fast, dependable service on the items you'll need for Delco Radio and other radio service work. Delco Radio also provides:

- Wide selection of special application parts
- Complete technical training program
- Effective warranty program
- Dealer identification signs




Get the facts today on this truly profitable dealer setup, and grow with General Motors!

Available everywhere through Electronic Distributors associated with ...



## DELCO RADIO

DIVISION OF GENERAL MOTORS, KOKOMO, INDIANA
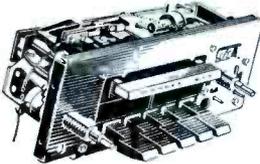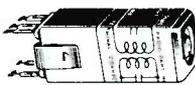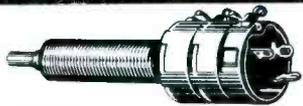
|   |  |  |  |
|---|--|--|--|
|  <p><b>TRANSISTORS</b></p> |  <p><b>TUNER PARTS</b></p>  <p><b>TRANSFORMERS</b></p> |  <p><b>TUBES</b></p>  <p><b>COILS</b></p>  <p><b>VIBRATORS</b></p> |  <p><b>IRON CORES</b></p>  <p><b>RESISTORS</b></p>  <p><b>CAPACITORS</b></p>  <p><b>CONTROLS</b></p> |
|---|--|--|--|



*Bypass Capacitor  
you can use!*

## AEROVOX TYPE V84C

*\*Aerofilm (†Mylar) Tubulars*

The best bypass capacitor on the market today at a price no higher than conventional units. All the technical advantages of Mylar dielectric, so widely used in premium-priced capacitors, are yours in a superior bypass tubular that virtually eliminates call-backs. Combining performance-proved, humidity resistant white ceramic cases with Mylar dielectric makes these capacitors superior to anything previously offered. These remarkable units will stand-up in those high humidity areas where other types have failed!

**Only Aerovox Type V84C  
gives you these plus features...**

**SMALLER SIZES** than conventional tubulars.  
**85°C 150°C** operating temperatures (with voltage derating).  
**LOW DIELECTRIC ABSORPTION**, lower than oil-impregnated types.  
**OUTSTANDING STABILITY**, little temperature change over normal operating range.  
**HIGHEST INSULATION RESISTANCE**  
**PREMIUM QUALITY** at prices no higher than conventional units.

**BUY 'EM  
BY THE KIT...**

two Mylar Tubular Kits (AK-100 & AK-101HS) in handsome 4-drawer metal cabinets are now available at your local Aerovox Distributor. Buy the capacitor assortment kit and get the cabinet FREE!



\* Aerovox trademark † DuPont trademark.

# AEROVOX CORPORATION

DISTRIBUTOR DIVISION

NEW BEDFORD, MASS



Fig. 4. "Electro-Sub" provides 10 popular capacitance values at 450 WVDC.

tors failed to locate a suitable replacement; therefore, a man was dispatched to the Sylvania distributor to obtain the correct part which, by the way, was 132-0019. The capacitor pointed out in Fig. 3 was transferred to the new coil which was then installed. This restored the set to normal operation and helped produce another satisfied customer.

Since the chassis had been operated in various positions while it was in the shop, the technician was sure the defect had developed after the set left the shop. The only possible explanation for the broken core is that the relatively warm core, when taken outside into the frigid weather, had broken due to the rapid temperature change.

### Shop Service Aid

The Sencore Model ES-102 Electro-Sub shown in Fig. 4 not only provides ten of the most-often-needed capacitance values at 450 WVDC, but also includes a 3-position switch and a 500-ohm resistor for capacitor surge protection and automatic discharge. Red and black test leads are permanently connected into the test switch circuit as illustrated in Fig. 5.

The three-position switch is spring-loaded for automatic return to position 1. As the switch is moved

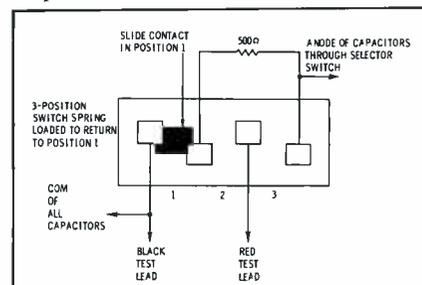


Fig. 5. Slide switch automatically provides surge protection for capacitors.



## Electronic Wire for Every Application

Service Rated—Quality Controlled  
Every Electronic Wire you need  
in easy-to-use packages.

- |                              |                          |
|------------------------------|--------------------------|
| Aircraft and Auto Radio Wire | Magnet Wire              |
| Antenna Rotor Cables         | Microphone Cables        |
| Broadcast Audio Cables       | Mil-Spec Hook-Up Wires   |
| Bus Bar Wire                 | RG/U Cables              |
| Community TV Cables          | Shielded Power Cables    |
| Cords                        | Shielding                |
| Hi-Fi and Phono Cables       | Sound and PA Cables      |
| Hook-Up Wires                | Strain Gauge Cables      |
| Intercom Cables              | Transmission Line Cables |
|                              | TV Camera Cables         |


**Ask Your Belden Jobber**

One Wire Source for Everything  
Electrical and Electronic



Magnet Wire • Lead Wire • Power Supply Cords,  
Cord Sets and Portable Cord • Aircraft Wires  
Electrical Household Cords • Electronic Wires  
Welding Cable • Automotive Wire and Cable

08A03J8

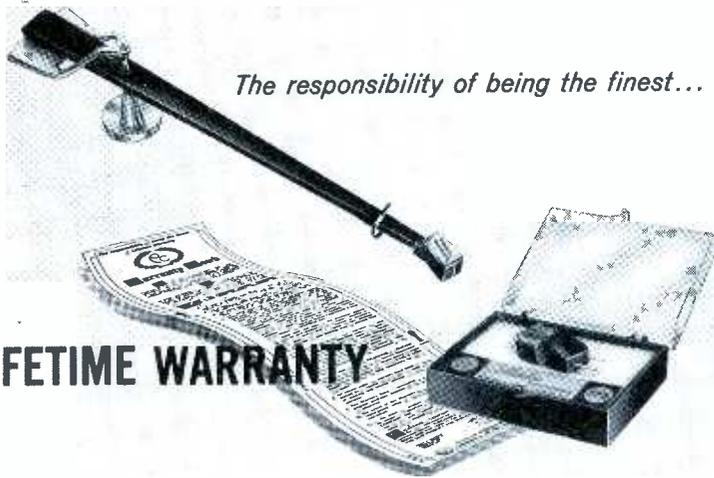

The responsibility of being the finest...

## A LIFETIME WARRANTY

FLUXVALVE AND T-GUARD ARE TRADEMARKS USED TO DENOTE THE QUALITY OF PICKERING & COMPANY INVENTIONS.

Truly the finest stereo pickup ever made... the STANTON Stereo FLUXVALVE is hermetically sealed in lifetime polystyrene with all of the precision that has made Pickering a quality leader in the field of high fidelity for more than a dozen years.

For instance... only the STANTON Stereo FLUXVALVE has the "T-GUARD" stylus assembly—so safe and easy to handle... so obedient and responsive to every musical nuance in the stereo groove.

Only the STANTON Stereo FLUXVALVE has the parallel reproducing element contained in the "T-GUARD"... assuring the proper angle of correspondence between recording and playback styli for maximum Vertical Tracking Accuracy.

And... because of this the STANTON Stereo FLUXVALVE reproduces music with magnificent sound quality... from both stereophonic and monophonic records... with negligible wear on record and stylus.

In plain truth... the STANTON Stereo FLUXVALVE is by far the finest stereo pickup made... backed by a Lifetime Warranty\*, assuring you a lifetime of uninterrupted, trouble-free performance—with a quality of reproduction no other pickup can equal.

We suggest you visit your Pickering Dealer soon —drop in and ask for a personal demonstration.

NEWLY REVISED—"IT TAKES TWO TO STEREO"— ADDRESS DEPT. T49 FOR YOUR FREE COPY

\*Excluding wear and tear of the diamond stylus tip and parts of the related moving system in the "T-GUARD" assembly.



For those who can hear the difference FINE QUALITY HIGH FIDELITY PRODUCTS BY PICKERING & COMPANY, INC., Plainview, N. Y.

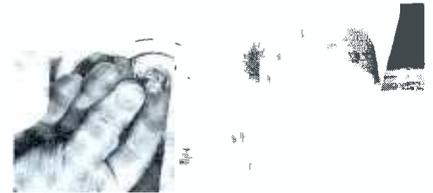


Fig. 6. Installing an auto snack tray on the underside of the servicing bench.

away from its resting position, the slide contact connects the red test lead through the 500-ohm resistor to the anode of the capacitor previously chosen by the rotary selector. As the slide connector is moved further, the 500-ohm resistor is dropped out of the circuit and the red test lead is connected directly to the anode of the capacitor. Releasing the switch labeled "Surge Protector — Push to Test" automatically removes the red test lead from the circuit and discharges the capacitor.

Capacitances offered by this unit (as seen in the photo) are 4 through 350 mfd in 10 steps and, while the voltage rating of all units is 450 volts, any of them can be used at lower voltages without any effect on capacitance value.

### "Autotray" Becomes Service Aid

Are you troubled with small screws, washers and nuts falling to the floor — not to mention a miniature tube sometimes rolling off the bench? If so, a suggestion sent in by H. Leeper of Canton, Ohio, may save you time and trouble. The *Autotray* shown is designed to swing under a car's dash when not in use. It may be attached to the underside of your bench or table with the bracket furnished (see Fig. 6.)

The tray is about 12" x 6½" and has two openings which are about 3" in diameter and about 2" deep. Paper drinking cups may be placed in the openings as shown in Fig. 7 to hold miniature tubes taken from a radio or TV being repaired. The tray can be swung out of sight and out of the way when not in use. ▲



Fig. 7. Paper cup holders are handy for holding stray tubes used at the bench.

## PROFESSIONAL technicians

use *Dave Rice's* OFFICIAL ORDER BOOKS for every TV-RADIO service call

This is the businesslike approach to service record keeping. Triplicate forms serve as order form, invoice and office record, with spaces for complete information on every job. Separate listings for receiving tubes, pix tube, parts, serial numbers, labor and tax charges, signatures, etc. 75c a book, \$6.50 for dust-proof box of 10. In stock at your distributor.

Write for your free folder describing Dave Rice's OFFICIAL ORDER BOOKS, including an actual size sample copy of the handy order form.

\*\*\*\*\*

For customer's prices on every replacement part, plus flat rate and hourly service charge data, regional and national, Dave Rice's OFFICIAL PRICING DIGEST, listing over 63,000 items. \$2.50.

ELECTRONIC PUBLISHING CO., INC. 180 N. WACKER DRIVE CHICAGO 6, ILLINOIS

## RADIO AND TV SERVICEMEN

Here's the perfect companion to any tester!



### Model GCT-8 GRID CIRCUIT TUBE TESTER

(U.S. Pat. No. 2,784,372)

Quickly spots grid errors and leakage

Here's the perfect accessory for every serviceman! Checks critical "Control-Grid" condition of vacuum tubes faster, more accurately than any other tester! As many as eleven simultaneous checks—automatically! Stops guessing, substitution checking, and costly rechecks. Electron-eye tube indicates following faults at a glance: Control Grid Emission Excl., Grid-to-Cathode Shorts, Gaseous Condition, Cathode-to-Heater Shorts, Grid-to-Heater Shorts, Grid-to-Plate Shorts, Plate-to-Heater Shorts, Grid-to-Screen Shorts, Screen-to-Heater Shorts, Heater-to-Suppressor Shorts, Grid-to-Suppressor Shorts.

Truly portable—may be stored and carried anywhere. Complete, easy-to-assemble kit \$19.95 net

Wired and factory tested.. \$29.95 net




Write today for free literature MANUFACTURING CO. 5015 Penn Ave. So., Mpls., Minn.


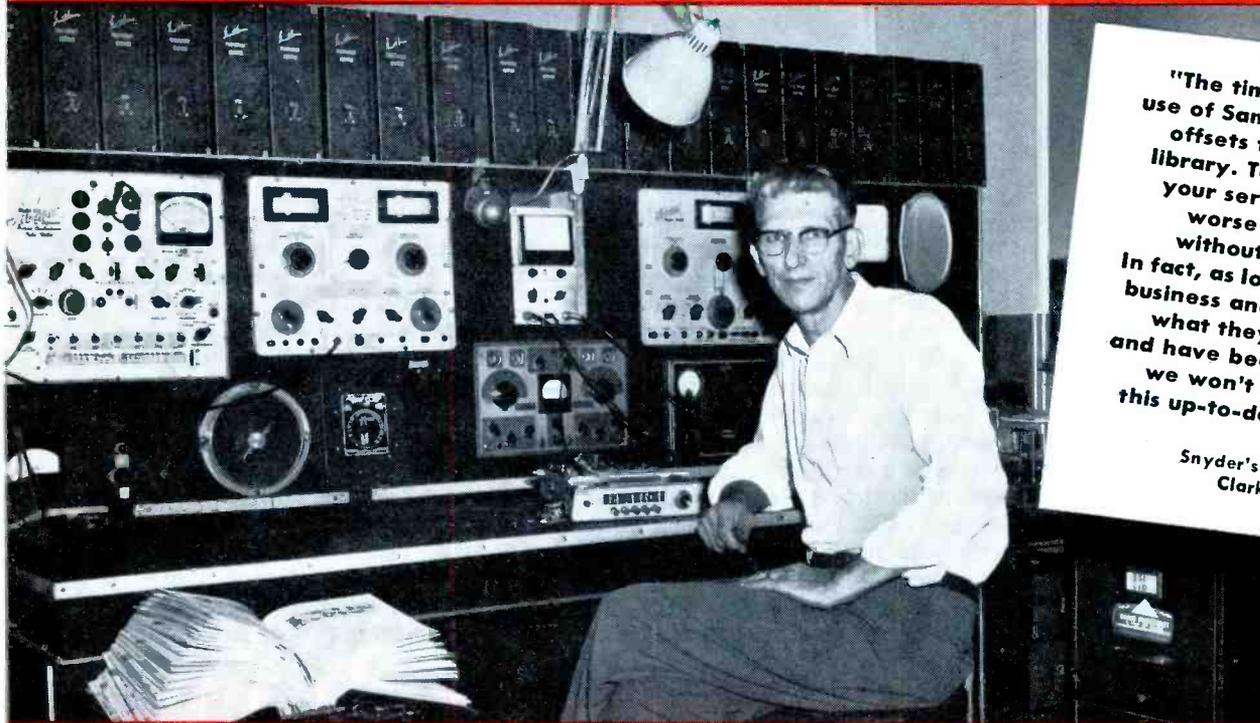
# ownership of a **PHOTOFACT** SERVICE DATA LIBRARY SPELLS SUCCESS FOR SERVICE TECHNICIANS

here's actual proof from the men who know



"The time saved by the use of Sams more than offsets the cost of the library. To do without your service would be worse than operating without a V.T.V.M. In fact, as long as we are in business and Sams remain what they are today and have been in the past, we won't be without this up-to-date service."

—Frank Snyder,  
Snyder's Sales & Service,  
Clarksburg, West Va.

## HERE'S MORE PROOF...FROM COAST-TO-COAST

### ARIZONA

"I would not take anything for my valuable collection of Sams PHOTOFACT."

—Charles S. Cook,  
Winslow, Arizona

### IDAHO

"My PHOTOFACT library is an indispensable source of service information on the . . . TV sets serviced in our shop. Without this information, the time required to complete many repair jobs would be prohibitive."

—Richard Huntley,  
Craigmont, Idaho

### WISCONSIN

"With the PHOTOFACT file to back us, we have complete confidence that we can handle any service problem brought to the shop."

—Howard R. Olds,  
Darlington, Wis.

### TEXAS

"I don't see how anyone can run a shop without a set of PHOTOFACT. I would be lost without mine. They are a must on any bench job. You can do a faster job with the information in PHOTOFACT."

—A. Hopkins,  
Quannah, Texas

### OHIO

"PHOTOFACT speeds up my service on repairs and the file cabinets help dress up the shop."

—Ed Rahm, Toledo, Ohio

### MASSACHUSETTS

"PHOTOFACT has been one of the mainstays in my service business. The PHOTOFACT library has cut my service time well in half and has more than paid for itself already. In the best words—PHOTOFACT kept my new business in the black."

—Benjamin L. Hall,  
Edgarton, Mass.

### PENNSYLVANIA

"They are just great. Cuts service time to a minimum."

—Virgil Franceschini,  
Barnesboro, Pa.

These are just a few of the hundreds of "Success with PHOTOFACT" letters in our files. Service Technicians everywhere are enjoying the profit-making advantages of a

complete PHOTOFACT Library. If you're not among them, see your Sams Distributor today, or write direct to Howard W. Sams for full details. Use coupon below.

**NEW EASY-BUY PLAN!** It's the money-saving way to build your complete profit-making PHOTOFACT Library!

NO INTEREST—NO CARRYING CHARGE—AS LITTLE AS \$10 DOWN

**FREE!** Valuable steel file cabinets for PHOTOFACT monthly subscribers and Library purchasers.



Valuable booklet shows you how PHOTOFACT boosts your profit-capacity

**FREE!**

Send for it!



**HOWARD W. SAMS & CO., INC.**

2201 E. 46th St., Indianapolis 6, Ind.



- Send me Free booklet "Your Guide To Maximum Profits"  
 I'm a Service Technician:  full-time;  part-time

My Distributor is: \_\_\_\_\_

Shop Name \_\_\_\_\_

Attn. \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_



An  
exclusive  
service  
by

**Amperex®**  
distributors:

## VALVO RECEIVING TUBES

for replacement in  
European radios

Many European radios and hi-fi components now popular in this country utilize the European-made VALVO tubes, which have thus far had no American distribution. As a special service to the trade, VALVO tubes are now being stocked by all franchised Amperex distributors. Replacement of the original tubes with completely identical types will assure optimum results in the repair and servicing of these European sets.



ask **Amperex**  
for the name and address  
of your nearest distributor

**Amperex Electronic Corp.**  
230 Duffy Avenue Hicksville, L.I., N.Y.



**Greetings.** As a means of expanding your customer list, have you ever thought of spending some of your ad budget for participation in a local *Welcome Wagon* service? You might introduce yourself to every new family in the neighborhood by offering to check their TV set (without charge) to make sure it survived moving day without damage. Another appropriate offer would be a credit of so many dollars toward the labor charge on the first service call. This invitation, along with your name and address, could be printed on a card and slipped into the basket of gifts that the *Welcome Wagon* delivers to newcomers.

You are charged a small fee (exact sum varies) for each such call made. In a medium-sized city, this organization visits hundreds of families per month — drumming up more potential business than you could ever handle. Fortunately, they are willing to offer partial coverage; for example, they might present only 50 or 60 of your cards per month to families who have moved into your immediate locality.



**They're In The Bag.** *Electrotex*, a parts distributor in Texas, imprints common paper bags in two colors with a message headed, "Your Troubles Are In The Bag." These are offered to service technicians at a low bulk rate for use in delivering bad parts to customers after completion of shop jobs.

This jobber reports the bags have been a rousing success in his area. Perhaps an idea along this line would work well for you, too.

Returning defective parts along with the set is recognized as a wise practice, since it lets the customer see what he's getting for his money. However, he will accept a loose collection of grimy TV tubes and diseased-looking tubular capacitors

about as eagerly as a handful of dead bugs. Hand over the decrepit parts in a neat bag, however, and the average customer will follow a simple three-step procedure: Read the good-will message on the outside, peer gingerly inside, and then fling the whole mess into the trash can. This last gesture signifies he is satisfied with the job you've done.

Besides its usefulness as a neat bit of public relations, the bag also helps you keep track of all parts removed from the set during repair. This cuts down on the number of capacitors and resistors absent-mindedly donated to the cause of getting the set in proper working order.



**Limping Along.** We'll bet that you are putting up with a number of nagging little defects in things which belong to you — for instance, a lock on one door of your truck that can't be operated from the outside, or a zipper on your jacket that won't zip up all the way. It seems to be human nature to live with such faults as long as the object can still be used. Why don't you get them fixed? Simply because you never get exasperated enough to fix them yourself or to hunt up a professional repairman. Yet, if someone came along and convinced you that he could take care of these little things with minimum cost and inconvenience, you'd most likely be willing to let him do it. You might even agree to have your storm windows repaired in July.

People have the same sort of minor defects in their radio and TV sets—burned-out dial lights, broken contrast-control knobs, dirty safety glass, or minor circuit defects which don't prevent use of the set. These annoyances will frequently be tolerated until some major trouble develops, unless some considerate serviceman takes the trouble to correct them. Like so many of life's

# 1ST TIME IN RESISTOR HISTORY

**COMPLETE**

10-WATT POWER RESISTOR

**COVERAGE**

IN JUST ONE  
POCKET CASE!



**HERE'S THE SECRET!**

*With the new IRC*

**MULTI-RANGE RESISTOR**

ONLY **5** TYPES

COVER

**200**

VALUES


10-watt ranges from 1/2 to 50K ohms

The first new approach to power resistors in 25 years. 4 separate elements sealed in a single, steatite case. Axial lead design speeds replacement. Steatite case provides superior insulation.

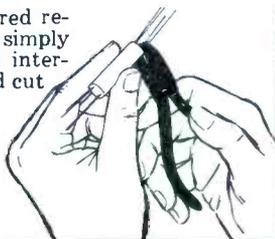**QUICK, SIMPLE TO ADAPT!**

Only 10 basic terminal interconnections... all with axial leads. Connection diagrams in each Handy-Pak.

For the required resistance value, simply solder desired interconnection and cut off unwanted terminals.



New! Compact! Efficient!

## IRC MULTI-RANGE RESISTOR KIT!

ASSORTMENT #55

CONTAINS **5** HANDY-PAKS

10 Type MR Resistors

**\$6.60**  
dealer net

Here's super-convenience on power resistors. Have complete 10-watt coverage right at your fingertips... in a stock so compact it fits in the palm of your hand. No delays for odd values... no costly inventories of slow-movers.

- Kit gives complete 10-watt coverage of 200 values.
- Contains 5 Handy-Paks—2 of each Type MR resistor—10 Multi-Range units.
- Rigid, clear-plastic box with hinged lid.
- Measures only 5 1/4 x 1 1/4 x 3 1/2".

Available Now From Your  
IRC Distributor. Order  
Yours Today!

**INTERNATIONAL RESISTANCE CO.**

Dept. 364, 401 N. Broad St.,  
Philadelphia 8, Pa.

In Canada: International Resistance Co.,  
Ltd., Toronto, Licensee



For Quality of international reputation


Economies that guarantee extra profits

FAMOUS

# HITACHI

## RECEIVING TUBES

Exclusively through **E.U.C.**

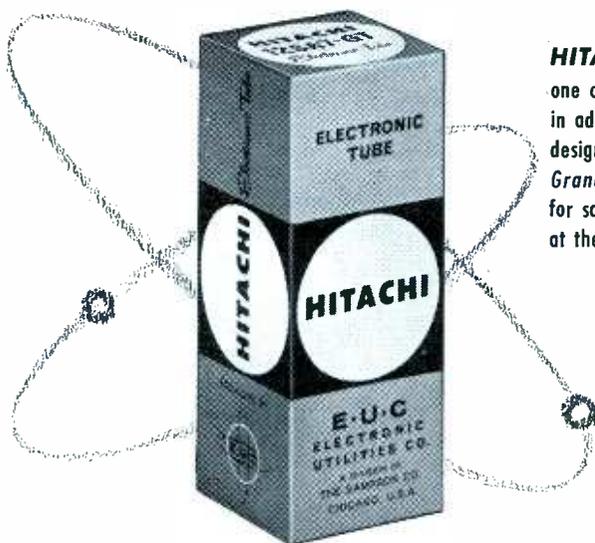


**HITACHI, LTD.,**  
one of the world's leaders  
in advanced electronics  
design and manufacture...  
*Grand Prix* Award winners,  
for scientific equipment,  
at the Brussels World's Fair.

HITACHI TUBES, CHOICE AS ORIGINAL  
EQUIPMENT BY MANUFACTURERS IN THE U.S.  
AND ABROAD

**SELL—SERVICE—SATISFY**—with dependable, EUC-guaranteed Hitachi tubes. Performance-proved around the world, Hitachi tubes are made the quality-controlled American way to fully meet *top American standards*. And, important cost savings assure you of profits not normally obtainable with tubes of this high calibre. Most popular types available.

**Behind the EUC symbol...** Electronic Utilities Co., a division of The Sampson Company, makes these tubes and other selected electronic components from abroad available to original equipment manufacturers and replacement parts distributors... on a *localized, prompt-delivery* basis. In addition, EUC has its own resident representatives and engineers abroad, maintaining quality of product in strict accordance with U. S. requirements.

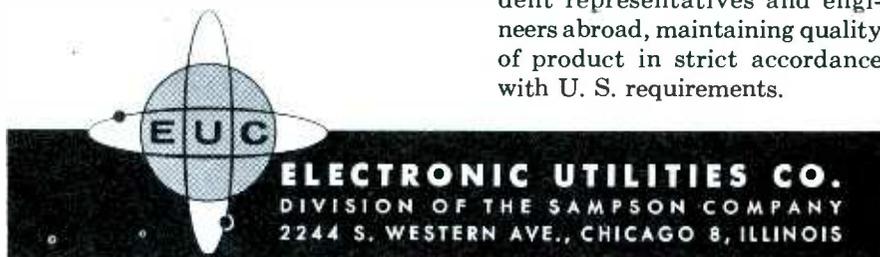

See your EUC Distributor now, or write for CATALOG NO. 558-R



A complete line of Quality Electronic Components:

Capacitors • Miniature Transistor Transformers • Variable Condensers  
Carbon Resistors • Tone Arms and Cartridges • Transistor Radio Earphones

small comforts, these little improvements are really appreciated; so they're well worth performing as routine "extras" on your calls. You could even work up a direct-mail or radio-spot advertising campaign to let people know that you take care of small repair needs.

**\$ & C**

**More Sets—More Business.** The theme. "Two or More TV Sets in Every Home," is expected to appear often in TV manufacturers' advertisements during the coming season. The consumer products division of EIA is currently cooperating with individual manufacturers to build a coordinated program of new-set promotion around this idea.

The multiple-set campaign should be regarded as more than just an effort to sell new TV sets. It will also serve to increase the total number of sets in use, thus providing opportunities for the ambitious serviceman to increase his volume of business. Besides creating more service work, an increase in multiple-set homes will open up new chances to install antennas, two-set couplers, and antenna distribution systems.

Here's another encouraging note: If the average customer warms up to the suggestion that he should own an extra TV set or two, dealers may be able to solve the problem of what to do with trade-ins. After all, the second or third set in a home doesn't have to be new! Perhaps this year's new-set buyer will be more easily talked into keeping his old set instead of having the dealer haul it away. Sales of reconditioned used sets may perk up, too.

**\$ & C**

**Edible Resistors.** Ohm's Law has been put to use for cooking hot dogs! In a new "Dog-O-Matic" appliance, electrodes are attached to wieners at both ends — thus literally "plugging them in" across the AC line. The electrical resistance of a hot dog is high enough to prevent blowing a line fuse when the current is turned on. Like an ordinary resistor, however, it will heat up; in about 90 seconds, it's cooked to perfection.

Need an expendable power resistor for an electronic experiment? Don't rummage around in your parts box — raid the refrigerator! Then enjoy a snack afterward, too!


# Quick as a Wink!



## THE RIGHT CARBON CONTROL COMBINATION

There's no fuss, no muss, when it comes to getting the **exact** carbon control you want—when you ask for Clarostat. You get your choice of shaft—13 types to select from—and with just a light tap, the shaft is permanently attached. Also, pick your switch, and in a moment you have the **exact** combination you need. Ask your Clarostat distributor for the new, bigger, 1958 Catalog.

### SHAFT

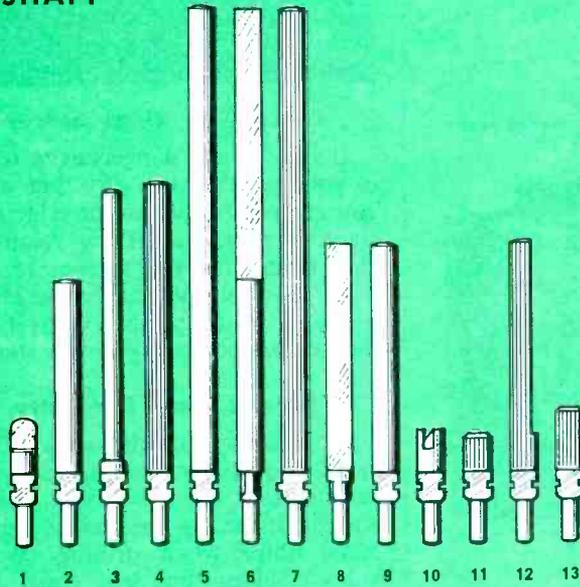

- 1  $\frac{3}{8}$ " long male for female fitting.
- 2 2" round shaft.
- 3 3" round shaft,  $\frac{3}{16}$ " dia.
- 4 3" knurled split shaft.
- 5 5" round shaft.
- 6 5" flatted shaft.
- 7 5" knurled split shaft.
- 8 3" flatted shaft.
- 9 3" round shaft.
- 10  $\frac{1}{2}$ " double-flatted Philco-type shaft.
- 11  $\frac{1}{4}$ " fine knurled shaft.
- 12 3" knurled flatted shaft.
- 13  $\frac{1}{2}$ " fine knurled flatted shaft.

### CONTROLS



Series A 47:  $\frac{1}{2}$ -watt,  $\frac{1}{16}$ " diameter controls. 500 ohms to 10 megohms.



Series A 47F:  $\frac{1}{2}$ -watt,  $\frac{1}{16}$ " diameter controls, with taps located at 30%, 50% or 70% of rotation, depending upon resistance value. 50K to 3 megohms.



Series AD 47:  $\frac{1}{2}$ -watt,  $\frac{1}{16}$ " diameter dual controls for audio, radio, TV and industrial uses. Various taps available. 50K to 5 megohms.

### SWITCH



Choice of five switch types including SPST and DPST, for various power ratings. UL approved.

**CLAROSTAT MFG. CO., INC.**

Headquarters for **RESISTORS, CONTROLS, and RESISTANCE DEVICES**

DOVER, NEW HAMPSHIRE, U.S.A.

In Canada: CANADIAN MARCONI CO., LTD., Toronto 17, Ont.

# MORE OF EVERYTHING YOU WANT IN A TUBE and TRANSISTOR CHECKER

1. *Electronamic*® Tube Performance Checker
  2. Comprehensive Transistor Checker
  3. Complete Crystal Diode Tester
  4. CR Tube Beam Current Tester
  5. Functional VR Tube Tester
  6. Direct Reading Gas Tester
- ... plus Free Tube and Transistor Test Data Subscription Service for one full year!



... AT  
**A PRICE THAT  
MAKES SENSE**  
THE  
**PRECISION  
MODEL 10-60**

1. Positive, all-inclusive tube performance testing ... not limited to mutual conductance alone.
2. Widespread  $I_{c60}$  ranges cover all types of transistors—low, medium and high power n-p-n and p-n-p types.
3. Crystal diode tests: 22 selected DC voltages for forward and reverse current tests.
4. Cathode ray tubes tested for true beam current.
5. Tests voltage regulator tubes for regulation at manufacturer's specified current limits.
6. Special gas test circuit indicates troublesome gas content directly on sensitive  $5\frac{1}{2}$ " meter.

**Model 10-60:** Complete with 5 window hi-speed geared roller chart unit and technical manual. . . . Net Price \$195.00

**Model 10-40:** Physically and electrically similar to the Model 10-60 but without transistor and crystal diode testing facilities. . . . Net Price \$149.50


► Available and on display at leading electronic parts distributors. Write for complete *PRECISION* catalog.

► *PRECISION* Test Equipment carries a full year warranty!



# TIPS

# for TECHS

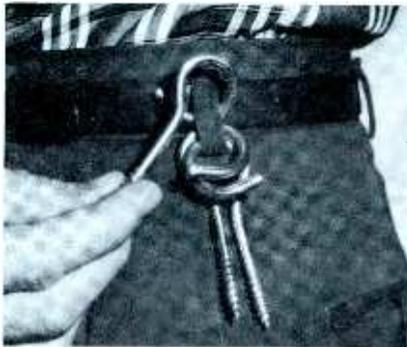

### Carry Guy Rings Safely

It's downright dangerous to reach in your pocket for a guy ring when you are poised out on the edge of a slanting roof, but it's a relatively easy matter for you to remove one from your belt loop as shown. Hook a supply of rings on a convenient loop before you go up on the roof.

### Service Uses for Putty


Extra-sticky calking-strip putty (available at hardware stores) is a helpful item for the service bench. Among its many uses are catching metal chips when drilling chassis holes, picking up drill chips and small bits of solder, removing metal filings from pole pieces of PM speakers, or holding parts on the bench when soldering or testing.

### Shockless AC-DC Servicing

Have you ever received a jolt while servicing an AC-DC set on the bench? Chances are, you completed a circuit between the chassis and a grounded object. If you want to avoid such unpleasant shocks, cover an area about 2' square at one end of your bench with a piece of fine-mesh copper screen or sheet metal and ground it through a neon lamp. Place the AC-DC set on the screen or plate and turn the set on. If the lamp lights, just reverse the line plug in the outlet.
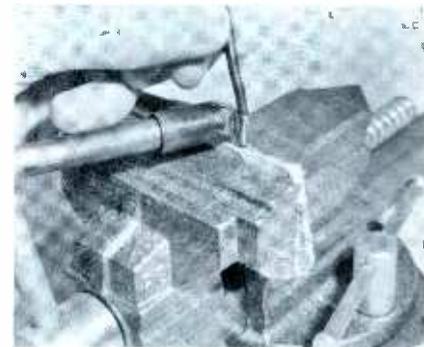
### Ladder Measures Lead-In

To simplify the measurement of lead-in wire used on antenna installation jobs, mark the length of your service ladder with different-colored daubs of paint at foot and half-foot intervals. Then you can charge the customer for exactly the amount of wire used.



### Asbestos Facilitates Soldering





Ever try soldering small parts while they are clamped in a vise? Chances are you found the task a difficult one because the heavy metal jaws dissipated the heat so rapidly that you had to resort to some other way to hold the work. Next time this happens, pad the jaws with some pieces of asbestos. This will eliminate the undesirable heat dissipation and make efficient soldering much easier.

### Magnetic Schematic Holder

Do Your PHOTOFAC service folders lay around on your bench and become torn by tools and soiled with solder and dirt? This can't possibly happen if you keep the folder you are using attached to the wall near the service bench. Fasten a magnetic knife rack (or a strong magnet from a PM speaker) to the wall, put your service folder up to it, and lay a small piece of iron such as a flat file against the folder. This will hold it securely in place without harming it in any way. You can turn it over easily to view the opposite side, too.
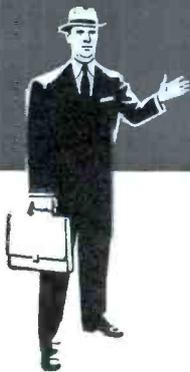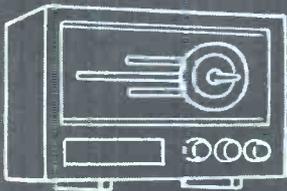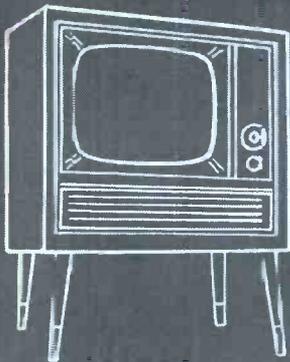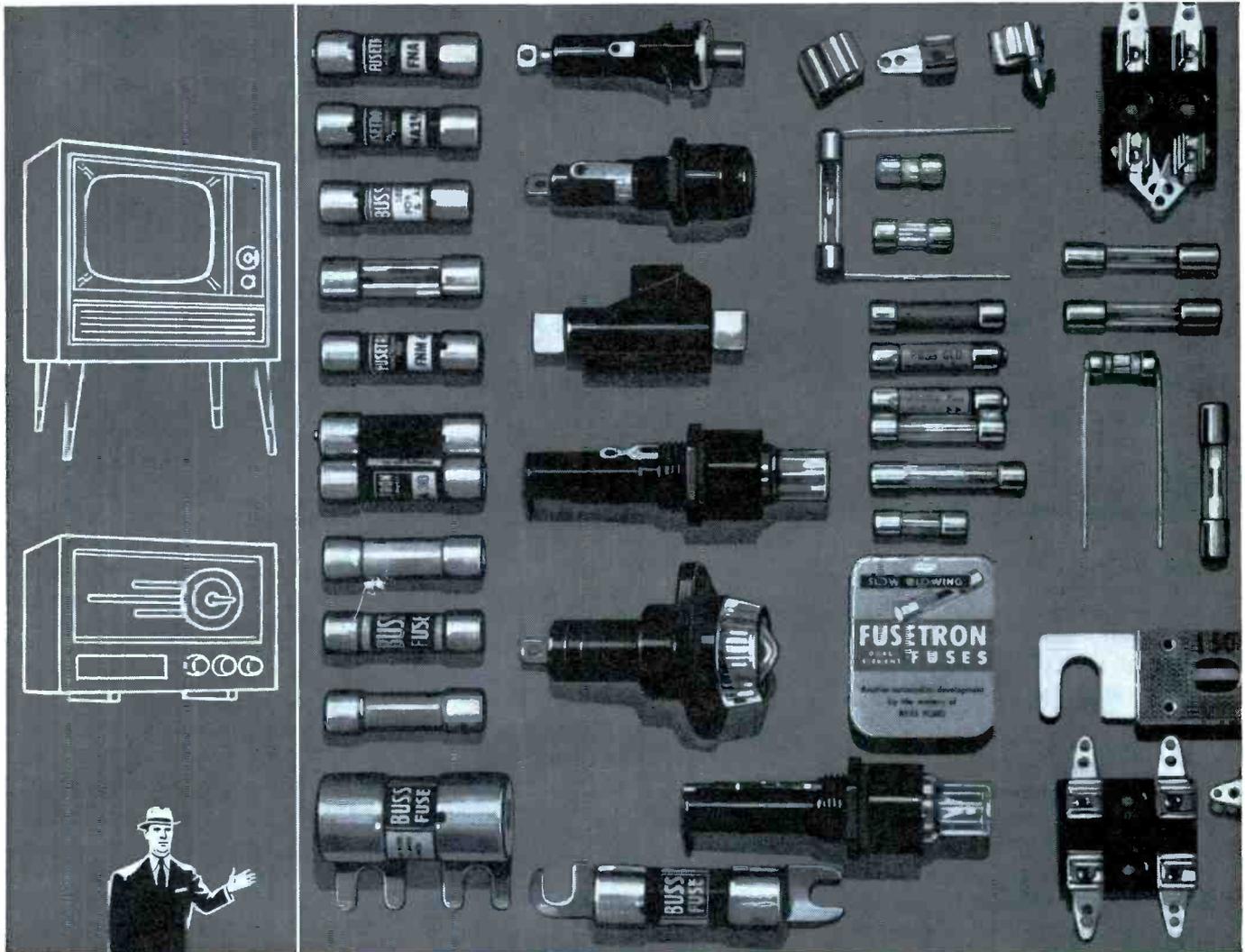
### Parts Bin for Shop

If you have some vacant space on your shop wall that isn't being put to good use, why not take a few spare moments to build a wall-mounted parts bin? If you keep most-often-needed pieces of hardware or parts in a bin made from some  $6\frac{1}{2}$ " three-quarter discs and a length of 6" stovepipe, parts selection will be fast and efficient. In case you don't have enough space left on your shop wall for such a bin, mount it on one end of the bench.



## Why it is more profitable to handle only BUSS Fuses!

BUSS fuses stay sold—customers stay satisfied because, BUSS fuses are made to protect, not to blow needlessly.

Every BUSS fuse you sell or install is tested in a sensitive electronic device that automatically rejects any fuse not properly constructed, correctly calibrated and right in all physical dimensions.

### Your customers know and prefer BUSS fuses

The ready acceptance of the BUSS trademark as standing for fuses of unquestioned high quality is built upon the millions upon millions of BUSS fuses that have provided dependable protection in homes, farms and industry over the past 44 years.

Selling and installing KNOWN, 'trouble-free' BUSS fuses, saves you

time and trouble and helps protect your reputation for service and reliability.

For more information on BUSS and FUSETRON Small Dimension fuses and fuseholders, write for BUSS bulletin SFB.

**BUSSMANN MFG. DIVISION,**  
McGraw-Edison Co.  
University at Jefferson, St. Louis 7, Mo.

459

*BUSS fuses are made to protect - not to blow, needlessly.*

*BUSS makes a complete line of fuses for home, farm, commercial, electronic, electrical, automotive and industrial use.*





"It's really just a pizza pie, but of course a JENSEN NEEDLE makes *anything* sound better."



**SUITS NEED PRESSING—  
MERIT DEFLECTION YOKES  
DO NOT!**


Merit deflection yokes are cosine wound TO FORM, not pressed. Pressing can lead to distortion and poor focusing. Pressing after winding frequently causes breakdown.

**MERIT COILS AND TRANSFORMERS  
HAVE "BUILT-IN" ADVANTAGES.**



Each Merit yoke is  
100% LIVE TESTED

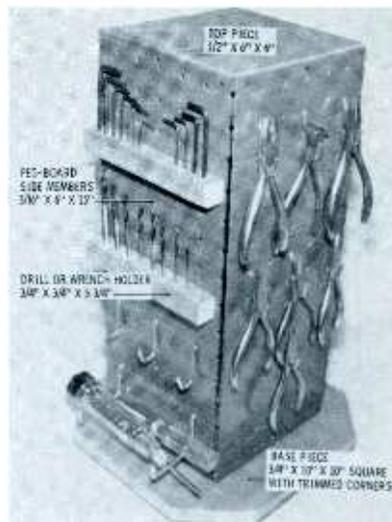**COMPARE IT WITH  
MERIT**  
MERIT COIL AND TRANSFORMER CORP.  
MERIT PLAZA • HOLLYWOOD, FLORIDA



**Tool "Tree"**

A convenient and orderly arrangement of tools on the service bench contributes much to the efficiency and money-making ability of any electronic service shop. This tool "tree" puts your most often needed tools within arm's reach. It should take you only a little longer than an hour to build. The four side members are cut from Marlite pre-finished pegboard and attached to the top and bottom pieces with small nails. A bolt with two washers, inserted through holes drilled in the middle of the bottom and base pieces, serves as a pivot and allows the tree to be rotated "Lazy-Susan" fashion. The threaded end of the bolt is recessed into the base piece and the nut locked in place with solder.

The tool fasteners are of the type normally used with pegboards. The holders for hex and spline wrenches and drill-bits are simply blocks of wood with holes drilled in them.



**Prod Adapted To Fit Clip**

To adapt a pointed test prod to fit the sleeve of an alligator clip, wind a medium-size paper clip into a small, tight-fitting coil and place it around the prod as shown. Now, whenever you need to clip one prod to chassis ground or to a terminal, merely slip the coil over the prod and insert it into the barrel of the clip.

**SAVE TIME! SAVE TUBES!**

**New Vis-U-All  
Picture Tube  
Reactivator  
ends guesswork . . .  
"magic eye" tells  
when to stop!**



Model Y200 10" high, 6" wide, 5" deep

Now test and reactivate all types of picture tubes, including 110°, quickly, efficiently, without worry or guesswork. Vis-U-All's exclusive, time-saving, tube-saving "magic eye" shows you tube's reaction to voltage as it's applied, tells you when to stop reactivating to prevent ruining with overdose. And for accurate test of tube, it measures *second* anode beam current. Convenient AC interlock included. Compact, easy-to-carry steel cabinet with instructions inside door.

See your distributor or write for literature

**Only  
\$59.95**

Slightly higher in West

**VIS-U-ALL PRODUCTS COMPANY** 303 Fuller Ave., N.E.  
Grand Rapids, Mich.

# The new *duallette*<sup>W</sup> by SYLVANIA



✓ MORE THAN A PORTABLE    ✓ MORE THAN A TABLE MODEL


*The set a serviceman can recommend to his best friend*

- powerful fringe area performance
- long-life GERMANIUM OR SILICON RECTIFIERS
- exclusive "LIFETIME ENGRAVED CIRCUIT"
- shockproof, HIGH IMPACT STYRENE CABINET

*for years of dependable reception*


**And, if service is ever necessary  
TWO QUICK STEPS OPEN THE DOOR FOR ALL SERVICE JOBS**

## STEP 1

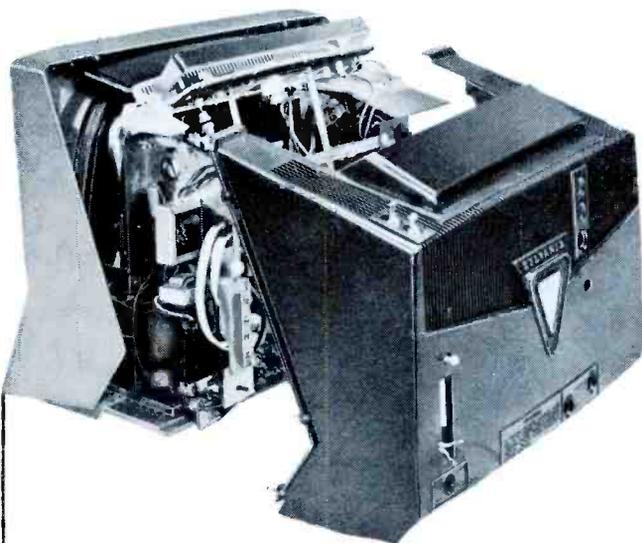

Take out only 8 screws to remove the back cover! All check points and tubes are accessible. A burned-out tube can be located in seconds! 90% of all service jobs and adjustments can be made without even removing the chassis!

## STEP 2

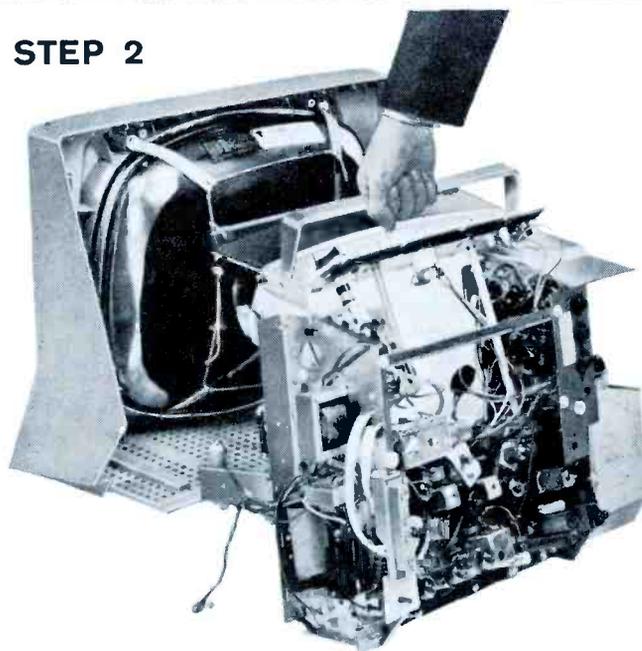

Just two more screws remove the entire chassis! If it ever becomes necessary to pull the chassis, simply remove two more screws and lift it out. The duallette carrying handle becomes a carrying handle for the chassis!

**Recommend SYLVANIA TV  
—every set has a "LIFETIME ENGRAVED CIRCUIT"**



## NOTES on test equipment

informative reports from the lab

by Les Deane

### New Radio Troubleshooter

Keeping pace with the ever-expanding electronic servicing field, Hickok Electrical Instrument Co. of Cleveland has recently introduced a new bench instrument specifically for troubleshooting transistor radios. Doing one of the jobs it was designed for in Fig. 1, the Model 810 Transistor-Radio Tester is actually a signal generator, an AM receiver substitute, and a transistor checker all rolled into one neat package.

Applications of the tester are not necessarily limited to transistor radios, however, and it may also be used in servicing tube-type receivers as well as auto radios.

Specifications and features are:

1. Power Requirements—105/125 volts, 50/70 cps; power consumption approximately 25 watts.
2. RF Output—audio modulated or unmodulated frequency ranges of 200 to

600 kc and 500 to 1600 kc; output impedance 180 ohms.

3. Radio Substitute—tuned receiver covering an IF band of 500 to 1600 kc; and an RF band of 500 to 1600 kc; cathode-follower probe provided; input impedance 5 megohms shunted by approximately 4 mmf; sensitivity 200 uv.
4. Audio Output — 600-cycle sawtooth, variable from 0 to 2 volts p-p across 180-ohm load; modulation switch provided on panel.
5. Audio Substitute—AF amplifier with cathode-follower input and built-in speaker; input probe resistance 5 megohms.
6. Transistor Test — checks both p-n-p and n-p-n transistors for leakage and relative gain when used with low-range milliammeter.
7. Size and Weight—9" x 11¼" x 7", 11¼ lbs.

One can probably visualize many uses for the Model 810 from the specifications alone, but to really become acquainted with a new instrument of this type, you should

understand its operating principles. When I first examined this piece of equipment and took a look at the function selector, I immediately wanted to find out how it worked.

Although the tester is basically a service instrument for transistorized equipment, its circuitry employs four vacuum tubes — one 6AB4, two 6AU8's, and a 6X4 power rectifier. This complement represents six separate stages; however, certain stages are used for more than one application, depending on the setting of the function selector.

The function switch has six positions. In one, labeled 500-1600 KC REC., the instrument operates as a complete AM radio, covering the standard broadcast band and reproducing sound on a built-in 4" speaker. Stages involved in this arrangement are shown in the block diagram of Fig. 2A.

The input to this substitute receiver consists of a cathode-follower triode stage housed in a probe at the end of the input cable. The probe may be connected to the RF circuits of a radio under test or, with the use of a 3' length of wire, used as an antenna itself. A gain control is also found in the output of this first stage.

The two RF amplifiers (V2A and V3A) are plate-tuned over a range from 500 kc to 1600 kc by varying the tuning dial on the front panel. Since an intermediate frequency is not used, the circuit operates as a simple TRF receiver.

Audio detection is accomplished by a 1N34 crystal diode which, in turn, supplies a grid signal to the AF amplifier V3B. In the final stage, an attenuator control located on the front panel varies the output signal to the tester's built-in speaker. For this function, the modulation switch is placed in its off position, automatically connecting the speaker across the output circuit.

Turning the function switch to the position marked 200-600 KC REC., the instrument is again operated as a TRF receiver, except that the plate circuits of V2A and V3A (Fig. 2A) are tuned to a range covering the two common IF radio frequencies of 262 kc and 455 kc. Incidentally, with the tester operating in this manner, you can also pick up aircraft weather signals, which are transmitted in this frequency band.

Selecting another function of the



Fig. 1. Signal-tracing, substitution, and alignment of transistor radios is easy with Hickok's Model 810, which also features a test circuit for transistors.




Model 810, I placed the switch in its 500-1600 KC OSC. position, operating the unit as an RF generator. Making use of the stages shown in Fig. 2B, tube sections V2A and V3A form a multivibrator-type RF oscillator. The output frequency is made variable by employing the same tuned circuits used in the TRF receiver setup. The dial on the panel thus selects the generated signal, which is then coupled to the output cable by way of the cathode follower V2B. If desired, the RF output can be modulated with a 600-cycle tone by merely flipping the MOD. switch

to its on position. I will describe this modulation source presently.

With the function selector in the position designated as 200-600 KC OSC., the generator circuit of Fig. 2B automatically falls into a tuning range covering the intermediate radio frequencies. This signal, too, can be modulated or unmodulated and used for either signal injection or IF alignment purposes.

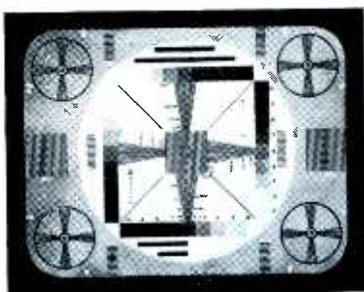The block diagram of Fig. 2C represents operating circuits of the tester when set up as an audio amplifier. In this case, the function switch is in the AUDIO AMPL. po-



## TV TIPS FROM TRIAD

NO. 2 IN A SERIES

The voice on the phone was painfully familiar. "No picture again," it said. The PTM (short for Professional Television Man) realized he was indeed on rather intimate terms with this particular receiver. Since installing a power transformer 8 months ago he had put in three 6CU6's, and two "exact replacement" flybacks.

"This is a blot on my escutcheon," said the PTM, who always used big words when talking to himself. "I'll fix it or buy it."

On the bench, the receiver revealed one flat 6CU6 and one flyback cooked to a turn.

First the PTM checked out the low voltage B+. Finding it excessive by 40 volts, he referred to the secondary rating and found it normal (660 volts where schematic called for 650).

"This can't be," he said, among other things. An outside salesman, attracted by the picturesque language, immediately presented the PTM with Triad's new Replacement Guide. "Check page 15," said the salesman, who was apparently blessed with total recall.

Here they find the rating that counts for the serviceman is the B+ he gets under actual conditions in the receiver; whether the set has one or two 5U4's; and, regardless, how fully loaded the circuit is. Actually the same power transformer can vary from 340 volts at 70% load with two 5U4 rectifiers to 285 volts with one 5U4 at 100%.

A Triad Service Aid called "Taking The Heat Off Flybacks" provides some additional information: "An increase of only 20 volts B+ can shorten tube and flyback life by 80%."

Better to fix the cause of the trouble than keep fighting the results. So the PTM looked up the current and voltage rating and selected the item that delivered it from his rectifier system. The picture was just as good but the whole set cooled down well below the boiling point.

**MORAL:** Too little information is a dangerous thing. Extra specifications—such as those you get from Triad—avoid callbacks. If you'd like to receive Triad Service Aids, communicate with **Triad Transformer Corp.**, 4055 Redwood Ave., Venice, Calif.

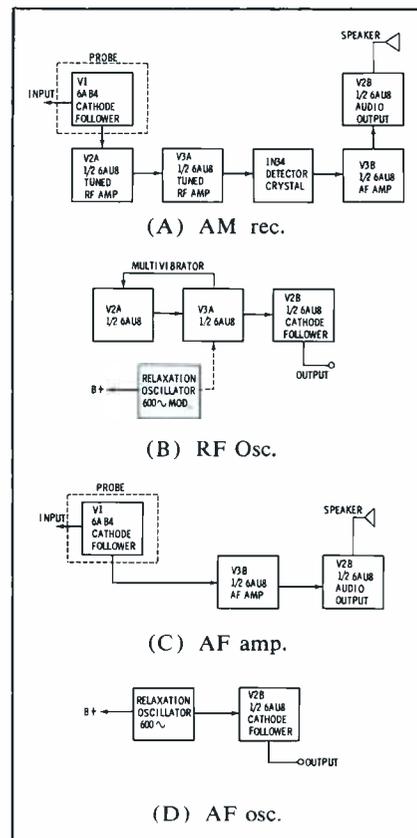


Fig. 2. Block diagrams of Model 810.

sition, and the modulation switch is turned off. This functional arrangement is used for complete signal tracing of the audio section of a radio, or as an auxiliary amplifier in itself. An input signal of 10 millivolts or more will normally produce a good aural indication from the instrument's speaker.

Placing the function switch in its one remaining position, namely 600 CPS AUDIO, I discovered that the unit operated as a simple audio oscillator or generator. The stages involved are shown in the block diagram of Fig. 2D. The relaxation oscillator, operating from the B+ supply, consists basically of an NE2 neon bulb, a .002-mfd charging capacitor, and a 5.6-megohm limiting resistor. The fixed frequency of the oscillator is 600 cycles, and its out-


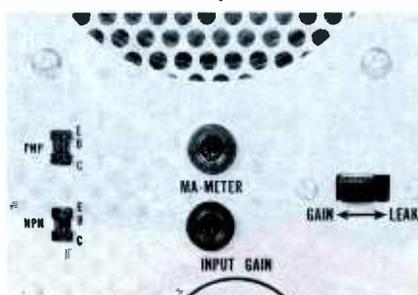


Fig. 3. Front panel provisions of the Hickok tester for checking transistors.

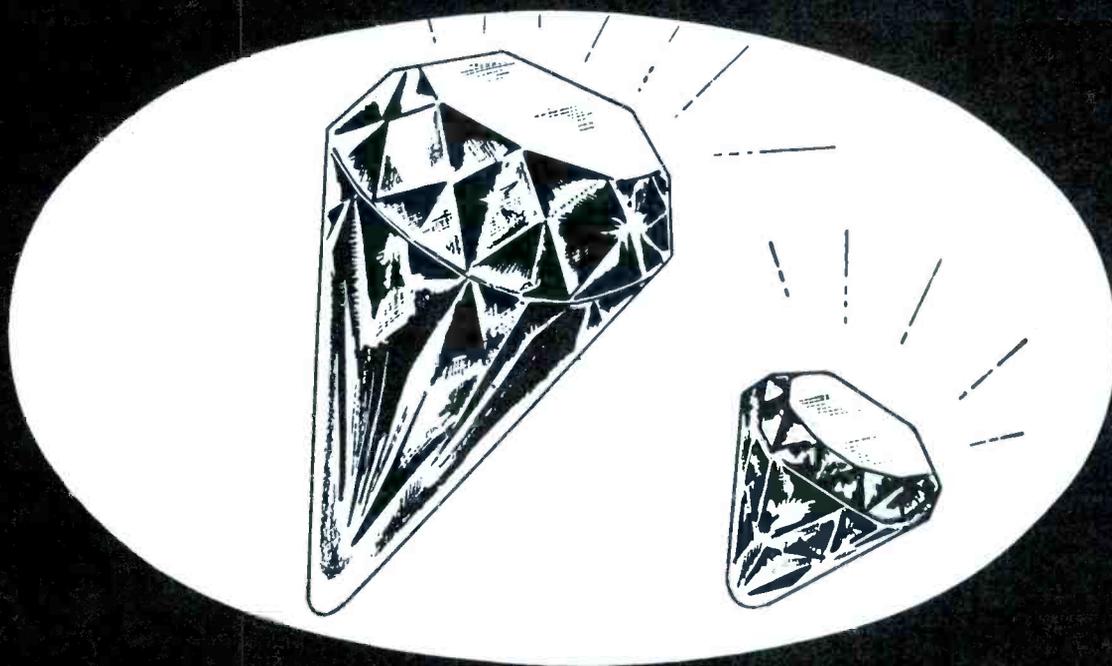

**WHICH  
WOULD  
YOU  
CHOOSE?**

**DUOTONE GUARANTEES THE WHOLE DIAMOND NEEDLE FOR EITHER MONOPHONIC OR STEREOHONIC REPRODUCTION, AT NO EXTRA COST**

What do we mean by the *whole* diamond needle?

There are two kinds of diamond needles now on the market. One is the *whole* diamond; the other is a diamond chip welded on a steel shaft. The overall length of both is the same. With the welded chip diamond the entire amount of diamond is visible on top of the steel shaft, and should there be a bubble resulting from heat or gas during the welding, the slightest jar can result in instant loss of the diamond. With the *whole* diamond needle, only 1/3 of the total diamond is visible and the remaining 2/3 is deeply embedded, crimped and cemented into the metal holder — thus making it impossible to shear off the point by any jarring or dropping of the tone arm.


What are the additional advantages of a Duotone Diamond Needle?

All Duotone diamond tips are hand ground and polished to a mirror finish, hand radiused to the exact required specifications, and hand set in perfect alignment to the record grooves. None of these delicate hand operations can weaken a weld that does not exist in a *whole* diamond. The constant observance under microscopic inspection plus Duotone's exacting quality standards eliminate every possibility of imperfection — permitting Duotone's 100% guarantee of the diamond needle itself, better reproduction and longest life possible for the needle.

One more important feature of your Duotone Diamond Needle.

No diamond needle will last forever. Only Duotone Diamond Needles give you the "needle that remembers" service and warns you when the Company Technicians know that needle wear is getting dangerous for your record collection.

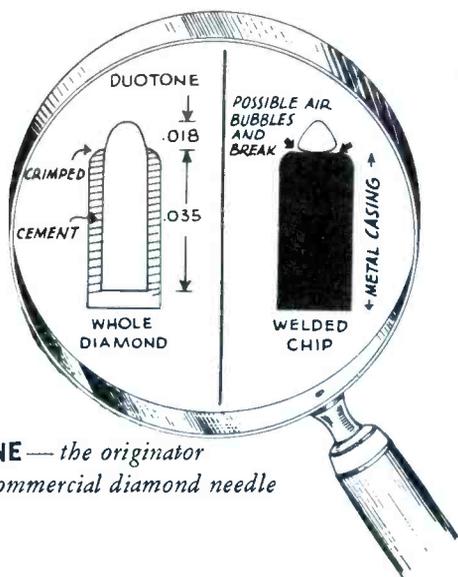All this at no extra cost over ordinary diamond needles.



**DUOTONE** — *the originator of the commercial diamond needle*

**DUOTONE**

**KEYPORT, NEW JERSEY**

*In Canada: Charles W. Pointon, Ltd., Toronto*

# NEW


from

## Tarzian


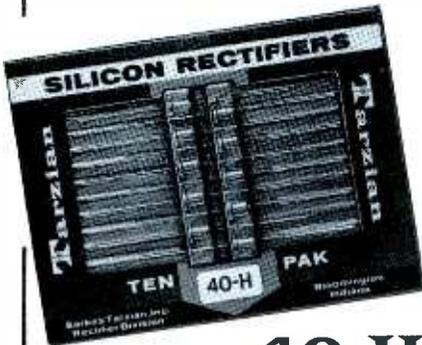
### F-4

Lowest priced 750 mil. silicon rectifier available . . . Ten in a handy pack—rated at 0.75 amps. dc, 400 P.I.V. . . . For use in radio, television and electronics.



### 40-H

Industry standard top hat hermetically sealed silicon rectifier rated at 0.75 amps. dc, 400 P.I.V.

Send for prices and complete information

**Sarkes Tarzian, Inc.**  
RECTIFIER DIVISION  
DEPT. PF-3, 415 N. COLLEGE AVE.  
BLOOMINGTON, INDIANA

IN CANADA: 700 WESTON RD., TORONTO 9  
TEL. ROGER 2-7535  
EXPORT: AD AURIEMA, INC., NEW YORK CITY

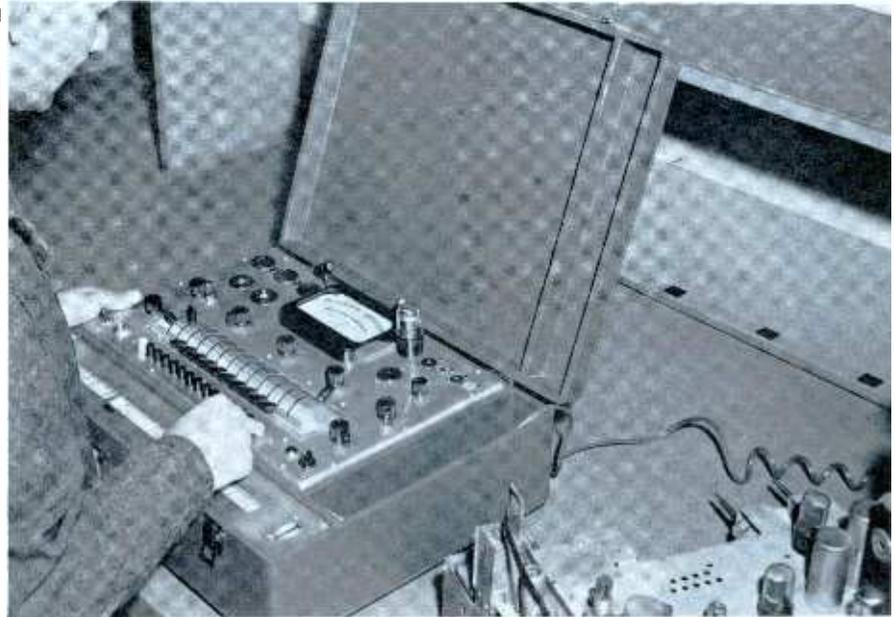


Fig. 4. Making use of Precision's *Electronamic* tube tester in the laboratory.

put waveform is sawtooth in nature.

For this phase of operation, I also found it necessary to place the MOD. switch in its "on" position, thus applying B+ to the oscillator circuit and shorting out the instrument's speaker at the same time. As shown in Fig. 2B, this same relaxation oscillator is used to modulate the output frequency when the instrument is used as an RF or IF signal generator. The cathode follower V2B offers a low-output impedance, which makes it suitable for driving transistor circuits.

Aside from the signal-tracing and signal-injection functions of the Model 810, it also provides a test circuit for transistors. As shown in Fig. 3, two test sockets, a positive and negative meter jack, and a leakage-gain switch are located on the front panel directly below the speaker grille. In addition to the test circuits, a separate milliammeter

must be plugged into the panel jacks and used as an indicating device. The instrument's manual gives step-by-step instructions for checking transistors, as well as general hints on servicing transistor receivers.

### "Electronamic" Tester

Pictured in Fig. 4 is the new Model 10-40 *Electronamic* Tube Tester developed by Precision Apparatus Co., Inc., Glendale, L. I. Featuring a special quality test for all amplifier tubes, the instrument is designed to meet the realistic needs of today's radio and TV service profession.

In addition to checking all receiving tubes for shorts, quality, and gas, the Model 10-40 can also be used to test picture tubes with the use of special accessory adapters. As you can see in the photo, the instrument comes in a leatherette carrying case with side compartment for adapters

Save Time with

## SENCORE

### LEAKAGE CHECKER

Check these outstanding New Features

The LC3 provides all these new improved features in addition to those employed in earlier leakage or "grid circuit" testers. A must for any TV service technician.

- ★ Checks 156 different tube types—more than any other "grid circuit" type checker. Includes UMF and latest type tubes.
- ★ Checks picture tubes without removing tube from cabinet or chassis.
- ★ New Roll Chart prevents obsolescence—just dial the tube type and save time. Chart is easily replaced at no extra cost.
- ★ Provides instant filament checks on "Fl-Check" position—no need to carry a second filament checker. ★ Capacitor checks simplified.
- ★ Two spare preheating sockets to cut down testing time.

In stock at your local parts distributor.

**Model LC-3**  
**\$289.95**

DEALER NET  
Really Whips  
Tough Deals

Service Instruments Corp., 121 Official Road, Addison, Ill.

*Mr. Service Dealer...  
Look what I've got for you!*



**OUR NEW 1959 PHILCO ELECTRONIC PARTS CATALOG IN 5 SEPARATE SECTIONS**

**A PROGRAM OF COMPLETENESS**  
*...All year 'round*

**The finest and most complete in the industry!**

The Philco Electronics Catalog is a complete service reference library for electronic parts and accessories. The data covers all Philco models and most models produced by other manufacturers.

- |   |  |  |   |  |
|---|--|--|---|--|
| <p><b>1 Quick Reference Data for Radio and TV Products.</b></p> <p>Knobs, Cabinets, TV Safety Windows, Parts Lists for TV and Radio, Service Substitution Data and Suggested List Prices.</p> | <p><b>2 Television Antennas and Accessories.</b></p> <p>Outdoor TV Antennas, Indoor TV Antennas, Heavy Duty Rotors, Antenna Installation Accessories, Transmission Line.</p> | <p><b>3 Electronic Components.</b></p> <p>Electronic and CR Tubes, Transistors, Diodes, Crystals, Rectifiers, Speakers, Batteries, Auto Radio Parts and Accessories, Test Equipment.</p> | <p><b>4 Needles, Cartridges and Phono Accessories.</b></p> <p>Universal Full Fidelity Needles for all Phono Makes, Cartridges, Spindles, Motors, Tone Arms, Changers and Accessories, and Recording Tape.</p> | <p><b>5 Universal Television Components and Transformers.</b></p> <p>Listed by Manufacturer's Model and Chassis Numbers. Cross-Referenced by Manufacturer's Part Number. Easy to read code selector.</p> |
|---|--|--|---|--|

We have just received copies of the new Philco Electronics Catalog and it's the finest we have ever seen. The five separate sections make it easy to

find anything you need. Come in and get your copy. You'll find that it will save you time, increase your profits and make your service jobs much easier.

*See me... your local Philco Distributor... Today!*


# 3

## Type SMT SUB-MINIATURE the BEST in ELECTROLYTIC CAPACITOR DESIGN

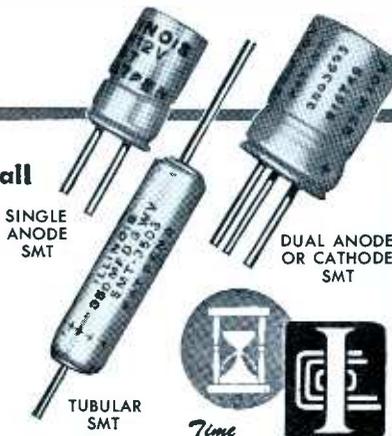**A complete line of capacitors for all miniaturized transistor circuits.**

The best in sub-miniature capacitors for replacement, development and original equipment. Outstanding features include patented construction, hermetically sealed in aluminum cases for long life; low leakage; stable through a wide temperature range and voltages.

Available from leading parts distributors everywhere. Illustrated catalog upon request.



TWX: CG3149

Telephones: EVerglade 4-1300

**ILLINOIS**

**CONDENSER COMPANY**

1616 N. Throop Street Chicago 22, Illinois

Export Department, 15 Moore Street, New York City, New York; Cable, Minthorne, New York

or tools and a detachable lid.

Specifications and features are:

1. Power Requirements—110/125 volts, 50/60 cps; power consumption approximately 15 watts in stand-by condition; all test circuits isolated from line.
2. Shorts Test—shorts indicated by neon bulb on front panel; individual push buttons provided for each tube element; test rapidly made before setting up lever switches.
3. Quality Test — separate loads and voltages applied to each tube element; indications given directly on 3-colored meter scale labeled REPLACE-?-GOOD; linear scale provided for comparison purposes.
4. Gas Test—VTVM measurement taken in grid circuit of tube; meter gives direct indication on special 0 to 20 ua scale.
5. CRT Test—shorts and beam current testing of all picture tubes with use of adapter cables; separate quality scale provided on meter.
6. Other Tests — voltage regulators, diodes, gas rectifiers, thyratrons, tuning eyes, certain foreign tubes, ballast units, pilot lamps, and a special contact potential test for 12-volt auto radio tubes.
7. Panel Features—built-in pin straighteners; 11 test sockets; large double-jeweled meter, accuracy within 2%; filament selector providing 24 individual voltages; roll chart with 3 viewing windows; line fuse and ON indicator.

In checking out one of these new tube testers in the lab, I first read over the operating instructions and then proceeded to test all of the tubes in both an old and a new TV chassis. Although the two chassis are generally kept in good working order for experimental purposes, I still ran across one tube that checked weak, and another that indicated excessive gas content. I then compared readings of the Model 10-40 with those obtained on an elaborate lab-type tester, and confirmed my findings.

Referring to the front panel shown in Fig. 5, you'll notice that the test sockets include standard octal; 7- and 9-pin miniatures; loctal; 7- and 8-pin subminiatures; 4, 5, 6, and 7-prong types; and also a special 12-prong socket for direct access to all twelve tube-testing circuits. The position of switch A selects the load and plate voltage applied to the tube under test. Switch B is used to complete the heater circuit. Control C, in the center of the panel, varies the input grid potential for different tubes. The control labeled D is adjusted to a precise value given on the roll chart, and accurately calibrates

**BERNS PERFECT PIN-CRIMPER**

**Picture-Tube Repair Tool**

*Eliminates that hard soldering job.*

**only \$1.25**

**Fix loose pin connections in seconds. Pays for itself in time saved on one job alone. 3" long.**

Intermittent operation of picture tubes due to defective solder connections at socket pins is easily corrected through the use of the Berns Perfect Pin Crimper. Actually a 3-in-1 tool that can also be used as a channel-selector wrench and screwdriver, it serves to notch pins and element leads to provide solid electrical connections. Pin keeps its original form.

**IT'S DANDY . . . IT'S HANDY**  
*"you'll like it"*

Available at your parts distributor.  
Another fine product from:

**BERNS Mfg. Co.**  
9853 Chalmers,  
Detroit 13, Mich



you'll find  
the right replacement  
faster in the

### '59 MASTER

Complete descriptions, illustrations, prices for more profitable TV-radio-audio-industrial servicing. You can buy, sell and bill direct from the **MASTER**—world's largest electronic catalog at your jobber . . . only **\$3.50**. \$4.50 in Canada

**FREE** — 24-page **PANEL LAMP CHART** at your jobber, or send 10c to:

**THE RADIO-ELECTRONIC MASTER**  
65 SEWELL ST. • HEMPSTEAD, N. Y.

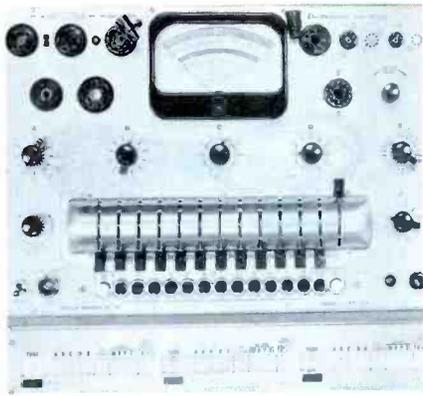


Fig. 5. Model 10-40 panel has easy-to-read meter and 3-window roll chart.

the meter for the particular tube tested. Switch E, on the far right, selects any standard filament voltage from .75 to 117 volts.

The bank of lever switches across the center of the panel enables the operator to connect individual tube elements into the test circuit. With the numbered levers in row "W", the tube element is open; in row "X", it's in the screen grid position; in "Y", the plate circuit; "Z", as control grid; and in "Normal", the element remains at a reference test potential. The line of pushbuttons just above the roll chart are used when checking for shorts and leakage as well as for a rapid continuity test of tube filaments. It's interesting to note that both these and the lever switches are numbered to represent the tube pin numbers standardized by EIA.

Switch F and the control knob opposite it on the far left are used for gas and picture tube testing. A line-voltage adjustment is located above switch E, while the neon short indicator is down in the lower left section of the panel. Leads for both grid- and plate-cap tubes are found at the top of the instrument on each side of the meter.

Operation of an amplifier tube depends on a number of characteristics such as electron emission, amplification factor, plate resistance, mutual conductance, plate current, power output, etc., and this instrument is designed to sum up these characteristics in a single quality test.

Examining the test procedure, I found that the instrument evaluates tube performance by monitoring output voltage or power while the tube input signal is dynamically swept over a wide range of characteristic curves. The results of this *Electronamic* test are integrated and

You're only doing half a servicing job if you're not checking the TV Antenna



One out of every two antennas is over three years old, worn out and defective



This means that half your servicing calls need a replacement TV Antenna



Why do half a job at half the profits when it's so easy to carry Clear Beam "top quality" antennas on your truck. Clear Beam "Do It Yourself" Kits, install yourself or sell kits outright.

Complete installation kits for every popular antenna... Conicals, Arrows, Yagis, Inlines.



Write for Complete Sales Aid Kit... Today



**CLEAR BEAM**

TV ANTENNAS • TELESCOPING MASTS • ACCESSORIES

• CANOGA PARK, CALIF. •

PROVED  
in over  
**500,000** installations!

ONLY AMPHENOL PROVIDES A CHOICE OF PROVED TELEVISION SET COUPLERS. THE TELECOUPLER, INTRODUCED IN 1954, AND THE COLORCOUPLER, INTRODUCED IN 1956, HAVE BEEN USED IN OVER A HALF-MILLION INSTALLATIONS!



## TELECOUPLERS

performance-proved designs

Telecoupler has an improved distributed line parameter of bifilar coiled transmission lines which isolate the signals and distribute them equally to each set with near-perfect impedance matching. Telecouplers are available at 2 set model 114-088 and 3 & 4 set model 114-090; suggested list prices are \$3.75 and \$5.75 respectively.



## COLORCOUPLERS

Colorcoupler employs balanced resistive networks to accomplish excellent impedance matching, flat signal response, low loss and effective isolation. Colorcouplers can be mounted vertically or horizontally and have built-in twin lead strain relief. Available as 114-097 (2 set), 114-098 (3 set) and 114-099 (4 set) models; suggested list prices are \$2.95, \$3.95 and \$4.95 respectively.

For sales action over your counter and for proved customer satisfaction stock and sell AMPHENOL Telecouplers and Colorcouplers!

**AMPHENOL** distributor division

AMPHENOL-BORG ELECTRONICS CORPORATION  
chicago 50, illinois



(A) Mod. PTA



(B) Mod. PAA


Fig. 6. CRT adapters for Precision unit.

expressed in terms of REPLACE—?—GOOD on the plate-circuit meter. With an output indication resulting from a sinusoidal voltage applied to the control grid, one can see that the test is actually based on more than emission or mutual conductance alone.

Adapter cables for testing picture tubes on the Model 10-40 are shown in Fig. 6. To check standard-base tubes having a deflection angle up to 90°, the Model PTA adapter of Fig. 6A is used; for the newer 110° types, the adapter pictured in Fig. 6B is also required. This latter cable (Model PAA) features two separate sockets on one end. The one visible in the photograph accommodates 110° tubes having a miniature base designated as the *small button Eightar* style. The one on the other end of the dual-socket is employed on 110° tubes having the medium-size base designated as the *small Seven Pin* type.

The plug end of the Model PTA cable fits into the octal test socket on the panel of the tester. The plug end of the Model PAA cable, on the other hand, attaches to the standard base socket of the Model PTA. Using the VTVM indicating circuit of the instrument, picture tubes are tested by measuring beam current. This has a direct relationship to picture brightness, and is usually preferred over standard emission tests. ▲

# FREE!

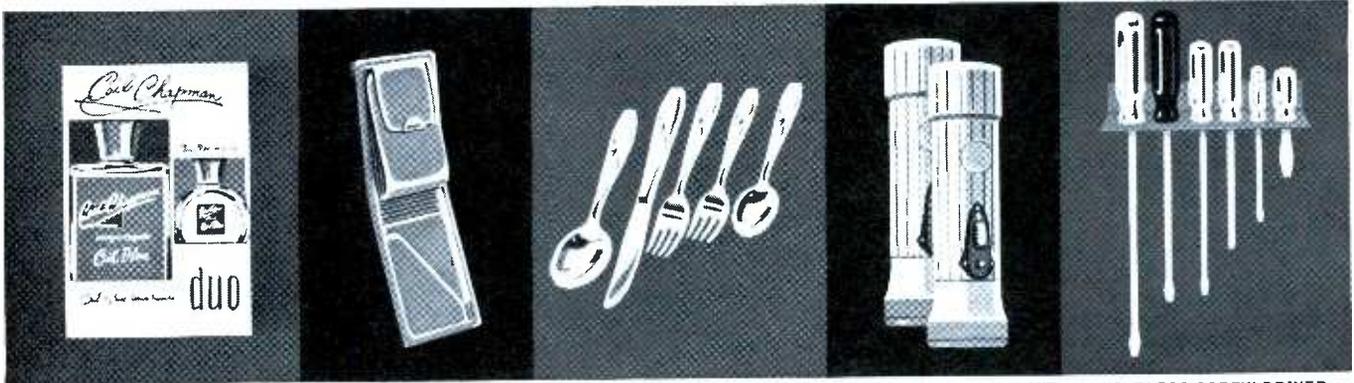

**CEIL CHAPMAN DUO.** Glamorous Ceil Chapman Parfum and Cologne in a gold and blue gift package. It will delight the wife or girl friend... a welcome gift for any occasion.

**WALLET TOP GRAIN COWHIDE WALLET.** A first quality man's wallet with pass case, zipper closing bill compartment, plus a secret section to hide your last twenty dollars.

**STAINLESS STEEL FLATWARE.** A five piece place setting of Wallace Stainless Steel tableware in the beautiful Northern Star pattern. Complete with lifetime guarantee.

**POLYETHYLENE FLASHLIGHT SET.** Not one, but two unbreakable flashlights made of lightweight, flexible polyethylene, the new miracle plastic. Use in the car and in your caddy.

**PEERLESS SCREW DRIVER SET WITH WALL HOLDER.** Six magnetized, alloy steel screw drivers in all the needed sizes. Complete with shockproof amber handles and handy wall holder.

## YOUR CHOICE OF THESE 5 GIFTS

(Worth up to \$4<sup>95</sup>!) when you order the

# Westinghouse "TOP PROFIT FIFTY"

## Electronic Tube Handi-Pak

Any one of these valuable gifts is yours when you order a "Handi-Pak" of the Top Profit Fifty Westinghouse Electronic Tubes—the types you'll need for 8 out of every 10 TV and radio service jobs. These pre-tested tube types were selected for fastest turnover and highest profit, and packaged in a special Handi-Pak you can take along on service calls. And don't forget: these are the tubes that are still standing up under the rugged Locked TV "Torture Test"—proving they work better and last longer to cut call-backs!

**PLACE YOUR ORDER AND SELECT YOUR FREE GIFT TODAY!**



**HERE ARE THE TUBES YOU GET IN THE TOP PROFIT FIFTY!**

| QUANTITY | TYPE    | QUANTITY | TYPE   |
|----------|---------|----------|--------|
| 10       | 5U4GB   | 3        | 6AU6   |
| 10       | 6SN7GTB | 3        | 6U8A   |
| 8        | 6CB6A   | 2        | 6BZ7   |
| 6        | 6BQ7A   | 3        | 6AX4GT |
| 3        | 12AU7A  | 2        | 1B3GT  |

**YOU CAN BE SURE...IF IT'S** **Westinghouse**  
Electronic Tube Division Elmira, New York

# STOCK GUIDE

## for tv tubes

The tube types listed on this page should account for at least 95% of your tube stock requirements. Figures in the chart indicate the number of tubes of each type that you might expect to find among a group of 1,000 tubes taken at random from all TV sets now in service. A figure "1" is listed if the frequency of usage is at least 1 in 2,000. If a tube is used less often than this, but is found in at least one out of every 4,000 sockets, the type number is listed with a dash in place of a figure.

About 75 of the rarest types, with a

frequency-of-use figure of less than 1 per 4,000, have been omitted from the chart. Most of these are new designs that have not yet become well established. A forthcoming article will list the circuit applications of these tubes and the brands of receivers in which they are used.

The information in the chart is purely statistical, so it should not be considered as a recommendation to stock a specific number of tubes of each type. However, you can combine the statistics with your own experience and come up with information tailor-made to your own needs.

Be sure to consider the following:


1. Relatively high failure rate of certain types such as RF amplifiers and power output tubes, requiring that larger stocks of these types be kept than a literal reading of the chart would indicate.
2. Specialization in particular makes of sets, such as regionally-popular brands. As a national publication, PF REPORTER necessarily gives nationwide averages based on all brands of receivers.

It's much easier to maintain an up-to-date tube stock when you are well informed about trends toward increased or decreased use of particular tube types. Keep posted on this subject by comparing the current Stock Guide chart with previous editions. The most recent ones were published in the April and October, 1958 issues.

### Notes on Using the Chart:

1. Redesignated "A" and "B" versions of tubes can almost always be used in place of their prototypes.
2. All type numbers (or "A" or "B" suffixes) marked with an asterisk are 450-ma series-string tubes.

| TUBE TYPES | NO. OF UNITS | TUBE TYPES      | NO. OF UNITS |
|------------|--------------|------------|--------------|------------|--------------|------------|--------------|-----------------|--------------|
| 1AX2       | —            | 5CG8       | 2            | 6BA8A      | 2            | 6CS6       | 3            | *8AW8A          | 1            |
| 1B3GT      | 39           | 5CL8       | 2            | 6BC5       | 4            | 6CS7       | 1            | 8CX8            | 1            |
| 1G3GT      | 3            | 5CQ8       | —            | 6BC8       | 2            | 6CU5       | 1            | 10DE7           | 1            |
| 1J3        | 2            | 5CZ5       | 1            | 6BE6       | 5            | 6CU6       | 2            | 12AT7           | 7            |
| 1K3        | —            | 5DH8       | —            | 6BF5       | —            | *6CU8      | 1            | 12AU7/-A        | 25           |
| 1V2        | 1            | 5EA8/5U8   | 1            | 6BG6GA     | 3            | 6CX8       | 1            | 12AV5GA         | 1            |
| 1X2A/-B    | 9            | 5J6        | 1            | 6BH8       | 2            | 6CY5       | 1            | 12AV7           | 2            |
| 2BN4       | 2            | 5T8        | 2            | 6BK4       | —            | 6CY7       | 1            | 12AX4GTA        | 8            |
| 2CY5       | 2            | 5U4GB      | 40           | 6BK5       | 2            | 6CZ5       | 2            | 12AX7/<br>ECC83 | 4            |
| 3A3        | 1            | 5U8        | 5            | 6BK7A/-B*  | 6            | 6DA4       | —            | 12AZ7           | 1            |
| 3AL5       | 1            | 5V3        | 1            | 6BL7GT     | 5            | 6DB5       | —            | 12B4A           | 1            |
| 3AU6       | 4            | 5X8        | 1            | 6BN4       | 2            | 6DC6       | —            | 12BH7A          | 10           |
| 3AV6       | —            | 5Y3GT      | 1            | 6BN6       | 7            | 6DE6       | 4            | 12BK5           | —            |
| 3BC5       | 1            | 6AB4       | 1            | 6BN8       | 1            | 6DE7       | —            | 12BQ6GTB        | 1            |
| 3BN6       | 3            | 6AC7       | 3            | 6BQ5/EL84  | 1            | 6DG6GT     | 1            | 12BR7           | —            |
| 3BU8       | 2            | 6AG5       | 4            | 6BQ6GTB    | 15           | 6DK6       | 1            | 12BV7           | —            |
| 3BZ6       | 9            | 6AG7       | 1            | 6BQ7A      | 14           | 6DN7       | 1            | 12BY7A          | 11           |
| 3CB6       | 11           | 6AH4GT     | 2            | 6BS8       | 1            | 6DS5       | 1            | 12C5/-CU5       | 2            |
| 3CF6       | —            | 6AH6       | 4            | 6BU8       | 2            | 6DQ6A      | 9            | 12CA5           | 1            |
| 3CS6       | 1            | 6AK5       | 2            | 6BW8       | —            | 6DT6       | 3            | 12CU6           | 1            |
| 3DK6       | 1            | 6AL5       | 48           | 6BX7GT     | —            | 6EA8/6U8A* | 1            | 12D4            | 2            |
| 3DT6       | 3            | 6AM8/-A*   | 4            | 6BY6       | 3            | 6EB8       | —            | 12DB5           | 1            |
| 4BC8       | 1            | 6AN8/-A*   | 5            | 6BY8       | 1            | 6EW6       | —            | 12DQ6A          | 6            |
| *4BN6      | —            | 6AQ5/-A*   | 19           | 6BZ6       | 11           | 6J5        | 2            | 12DQ7           | —            |
| 4BQ7A      | 2            | 6AR5       | —            | 6BZ7       | 3            | 6J6        | 17           | 12L6GT          | 3            |
| *4BU8      | —            | 6AS5       | 3            | 6C4        | 5            | 6K6GT      | 5            | 12R5            | —            |
| *4BZ6      | 1            | 6AS6       | —            | 6CB5A      | —            | 6S4A       | 1            | 12SN7GTA        | 3            |
| *4CB6      | —            | 6AS8       | 1            | 6CB6/-A    | 100          | 6SL7GT     | 1            | 12W6GT          | 1            |
| 5AM8       | 2            | 6AT6       | 2            | 6CD6GA     | 2            | 6SN7GTB    | 51           | *17AX4GT        | —            |
| 5AN8       | 1            | 6AT8/-A*   | 2            | 6CF6       | 3            | 6SQ7       | 2            | *17DQ6A         | —            |
| 5AQ5       | 4            | 6AU4GTA    | 6            | 6CG7       | 21           | 6T8        | 12           | 19AU4/-A        | 2            |
| 5AS4       | 1            | 6AU6/-A    | 77           | 6CG8/-A*   | 2            | 6U8/-A*    | 16           | 25AX4GT         | 1            |
| 5AT8       | 1            | 6AU8       | 3            | 6CK4       | —            | 6V3A       | 2            | 25BK5           | —            |
| 5AV8       | —            | 6AV5GA     | 2            | 6CL6       | 2            | 6V6GT/-A*  | 11           | 25BQ6GTB        | 3            |
| 5AU4       | —            | 6AV6       | 12           | 6CL8/-A*   | 1            | 6W4GT      | 14           | 25CD6GB         | 1            |
| 5AW4       | —            | 6AW8A      | 11           | 6CM6       | 1            | 6W6GT      | 8            | 25DN6           | 1            |
| 5B8        | 1            | 6AX4GTA    | 15           | 6CM7       | 4            | 6X8        | 6            | 25L6GT          | 3            |
| 5BK7A      | —            | 6AX5GT     | 1            | 6CN7       | 2            | 6Y6G       | —            | 25W4GT          | 1            |
| 5BR8       | 1            | 6BA6       | 5            | *6CQ8      | 3            | 7AU7       | 3            |                 |              |

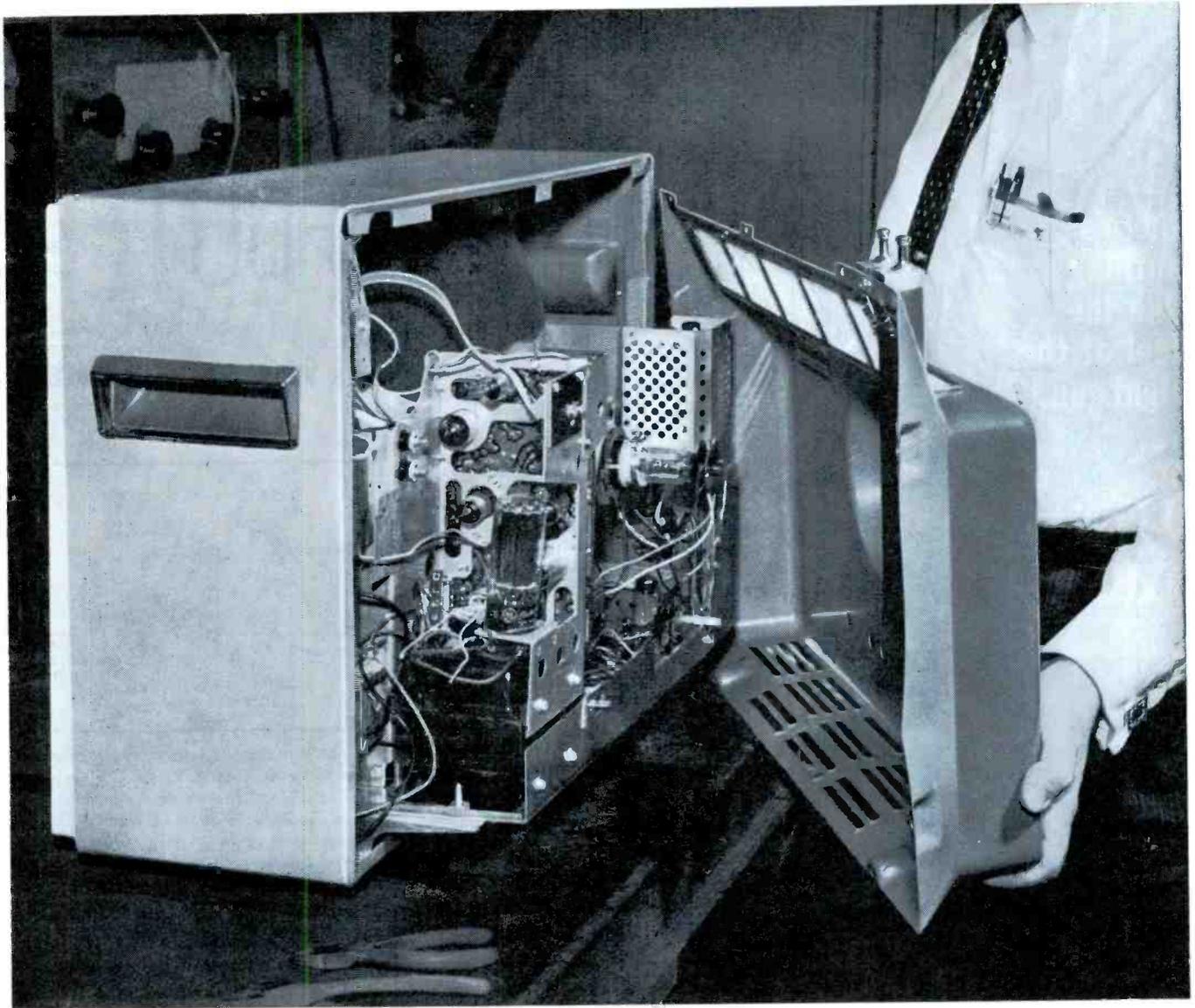

Take the back off the General Electric "Designer" TV set and you can **do 85%-90% of service jobs without pulling the chassis**

*You cut your time-per-repair by up to 40% . . . make more calls—and money—in the same amount of time!*

Take off the back and there you are—in easy reach of up to 90% of service jobs. Look at the chart!

**Look inside!** Both sides of the reliable printed circuit boards are easy to reach for service.

No series string filaments—no extension cables needed . . . the new "Designers" are certainly the easiest-to-service sets in all television. You'll wish every set was a General Electric "Designer."

*Progress Is Our Most Important Product*

**GENERAL  ELECTRIC**

| TEN TYPICAL JOBS THAT CAN BE DONE WITHOUT REMOVING THE CHASSIS |                |       |       |       |
|--|----------------|-------|-------|-------|
| JOB  | G-E "Designer" | Set A | Set B | Set C |
| Replace most resistors   | yes            | no    | no    | no    |
| Replace most capacitors  | yes            | no    | no    | no    |
| Replace deflection yoke  | yes            | no    | no    | no    |
| Replace video detector   | yes            | yes   | no    | no    |
| Replace audio detector   | yes            | no    | no    | yes   |
| Replace horizontal phase detector                              | yes            | no    | yes   | yes   |
| Replace power rectifier  | yes            | no    | no    | yes   |
| Adjust tuner oscillator  | yes            | no    | yes   | yes   |
| Replace inter-stage transformers                               | yes            | no    | no    | no    |
| Replace size and linearity controls                            | yes            | no    | yes   | yes   |

General Electric Co., Television Receiver Dept., Syracuse, N. Y.

there's  
nothing  
like the  
feel of the  
right gun...

or  
the right  
TOOL!

**WEN**

**POWER TOOLS**  
are "job-matched" for

easier handling, trustier performance!

Pick up a Wen tool. It fits in your hand like it grew there! Lightweight, streamlined Wen designs are extra easy-handling . . . quality-engineered to do the job right. Ask any Wen tool user. Your best dollar-for-dollar buy, too!



**2-SPEED POWER DRILL**  
3/8" capacity in steel, up to 3/4" in hardwood. Smooth easy speed change, high torque motor. **\$29<sup>95</sup>**



**TOTE KIT**  
Perfect supplement to drill. 35 pieces including drill holder, Tote Box with tray. A whole workshop, only **\$9<sup>95</sup>**



**SOLDERING GUN KIT**  
Includes 4 tips for wide variety of uses, solder. "Quick-Hot" gun heats in only 2 1/2 seconds. A buy at **\$9<sup>95</sup>**

See complete line of Wen power tools at your favorite dealer!

**WEN PRODUCTS, INC.**

5810 Northwest Highway • Chicago 31, Illinois

# THE TROUBLESHOOTER

ANSWERS YOUR SERVICE PROBLEMS

## Danger — Tube Out!

I am studying TV repair and have acquired a Bendix Model TS-17C for experimentation. One thing puzzles me about this set: When I remove the sync clipper-vertical oscillator tube (a 6SN7) while the set is on, the 2200-ohm, 2-watt plate load resistor of the vertical output tube overheats and begins to smoke. What causes this condition?

PAULMER L. WILLIAMS

Trout, W. Va.

The resistor gets hot because the output tube draws excessive plate current. The reason for this behavior is that the grid of the output tube receives no drive signal when the oscillator is disabled. As a rule, both horizontal and vertical output stages of TV sets depend on the presence of a normal input signal from their respective oscillators in order to maintain sufficient bias for operation at safe plate-current levels. "Loss of drive" usually has more severe consequences in the horizontal section, where it can cause the plate of the output tube to glow red from excessive current; but, as you have discovered, the same condition can also cause trouble in the vertical output stage.


## Resistor With a Fever

I recently serviced a Mirrortone Chassis 9034A which had no raster or high voltage. The AFC feedback resistor R77 was burned to a crisp. I replaced it with a 1-watt unit; this restored the raster, but the new R77 runs quite hot. The DC voltage drop across it is 8 volts, and I measure 450 volts AC across the coil to which R77 is connected. B+ voltage on the 135-volt line measures only 115 volts. Even though the receiver has been running OK for more than 100 hours, I wonder if there is still some trouble which might be causing the resistor to run abnormally hot.

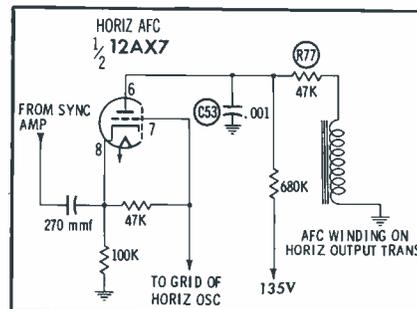A. V. ROUSE

Tonawanda, N. Y.

R77 couples a feedback signal from the flyback transformer to the horizontal AFC stage, and it also works in combination with C53 to reshape the signal into sawtooth form. Under normal conditions, R77 will run relatively hot because considerable pulse voltage is developed across it. You stated that the amplitude



of the signal at the transformer winding was 450 volts p-p. R77 and C53 in series act as a load across this winding; and, since the impedance of C53 at 15,750 cps (in ohms) is equal to only about one-fifth of the ohmic value of R77, about four-fifths of the pulse voltage will appear across the resistor.

A leaky condition in C53 would tend to make R77 run hotter than normal, besides pulling down the voltage on the 135-volt line. Just to be sure that the repair is completed to your satisfaction, you might replace this capacitor.

## Record Changer Shutoff

With the rising interest in stereo, I have been called on to convert several hi-fi installations to stereophonic operation. This sometimes calls for a new four-pole motor to reduce hum pickup in the magnetic stereo cartridge which I prefer to use. As a result of these modifications, a problem has cropped up. The automatic shutoff at the completion of a stack of records makes a loud snap in the speakers, and this is a source of great annoyance to my customers.

This problem may be shared by other servicemen doing stereo conversion work. Has anyone come up with a squelching circuit to eliminate this switch snap?

FRED A. SIEBOLD

Portland, Ore.

You are probably aware that the "pop" in the speakers is due to a transient pulse voltage of high peak amplitude which is produced when the contacts of the automatic shutoff switch are opened. This pulse interference reaches the audio amplifier by way of the power-supply circuits. One simple way to reduce or eliminate the snapping noise is to connect a .01-mfd, 1-kv capacitor across the con-

tacts of the shutoff switch in order to suppress the transients. This sort of arrangement is used in several commercial phonographs, and capacitors are sometimes connected across TV components such as damper tubes and silicon rectifiers for a similar purpose.

A high-voltage ceramic capacitor should be well suited for this application. Wire it directly to the switch terminals if possible; in any event, try to place it as close to the switch as you can.

#### Vertical Foldover

A white bar appears at the bottom of the raster on an Admiral Chassis 21F1 when the height control is adjusted to fill the screen. I was able to remove it by changing the vertical oscillator and output tubes, but it returned after about a month. I have been informed that several servicemen have worked on this set for the same trouble.

L. J. KELLER

Chicago, Ill.

The white bar indicates you have vertical foldover, a condition appearing when the vertical output tube is driven into saturation on positive peaks of the vertical sweep signal. This symptom could be caused by driving the output stage too hard or operating it with insufficient bias.

In a great many cases, the 100-mfd cathode bypass capacitor is the source of the trouble. If this unit loses capacitance, the gain of the stage is reduced. This makes it impossible to obtain normal raster height unless the input signal at the grid is made strong enough to cause fold-over.

You may find that the grid voltage is not as negative as it should be; if so, the coupling capacitor between the oscillator and output stages may be leaky.

Another conceivable cause of your trouble is abnormally low plate voltage, which could be due to a faulty plate-load circuit.

#### Persistent Burnout

What causes the 12BY7A video amplifier tube in a Westinghouse Chassis V-2342-24 to develop an open filament? I've replaced three of these tubes (besides the original one) in less than three years, the latest one lasting only five weeks.

BEN DIGENNARO

Willow Grove, Pa.


We have a Westinghouse TV Model H-950T24, Chassis V-2343, which repeatedly burns out 12BY7 tubes. We're unable to find the trouble.

WARREN L. GLENN

Burley, Idaho

We're receiving an unusually large number of reports from the field about this particular trouble. A Westinghouse field service technician informs us that the 12BY7A tube socket in the above-named chassis tends to develop leakage between the heater pins and ground as the receiver ages. Because of the series-string hookup used in these chassis, this leakage places enough voltage across the heater of the 12BY7A to burn it out. Replacement of the socket is reported to be the only effective cure.
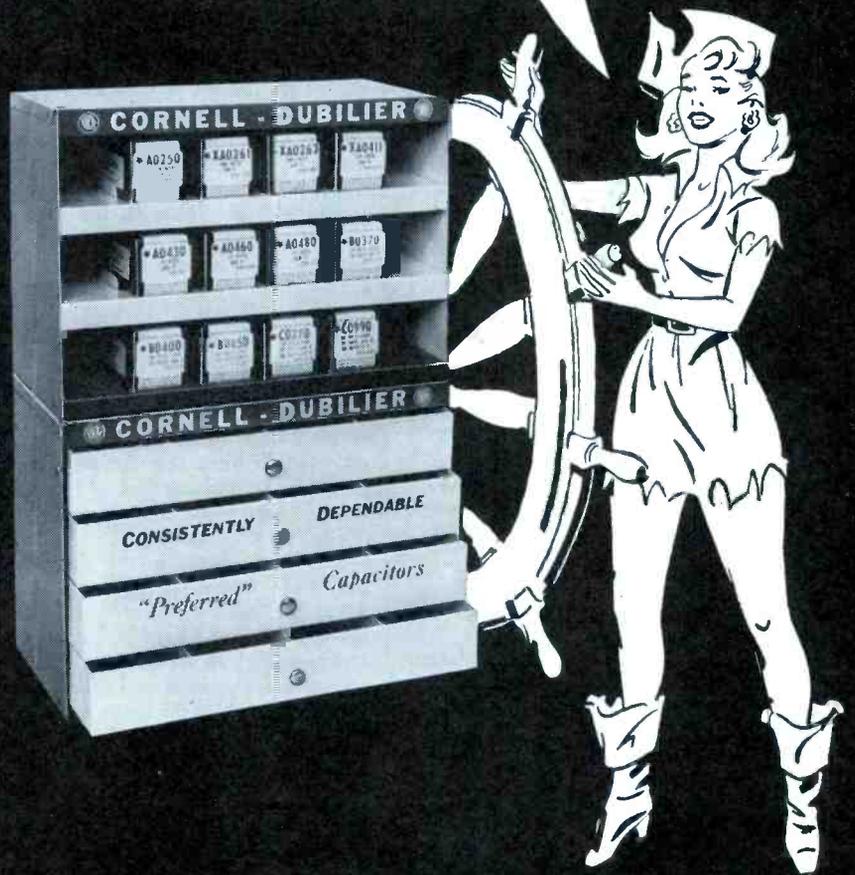
## THERE'S GOLD IN THIS C-D TREASURE CHEST



### The modern way to stock and sell the world's most wanted capacitors.

This efficient shop-chest tells you what's in stock and exactly where it is. No more digging for misplaced units. You get an assortment of the most popular C-D "Preferred" type twist-prongs, "Blue Beavers," and Mylar Tubulars—in handsome metal cabinets. Makes you look more efficient...makes work efficient! Best of all they're FREE with your purchase of capacitors.

See the "Treasure Chest" at your C-D distributor or write for Bulletins to Cornell-Dubilier Electric Corporation, South Plainfield, N.J.



Consistently Dependable  
**CORNELL-DUBILIER**  
SERVICE CAPACITORS



*Silicon Rectifier...* ... 1N2078

## NEW Tung-Sol 1N2078 designed and made for simple, speedy TV replacement!

Tung-Sol's new 1N2078 diffused junction silicon rectifier possesses distinct advantages the service industry will welcome. Optimum physical and electrical characteristics combine to make 1N2078 convenient to handle and install, and assure your TV and radio service customers the high-grade performance they want and appreciate.

**Small size, easy to install.** Tung-Sol's 1N2078 is smaller than most semiconductor devices, at no sacrifice in efficiency. Long

flexible leads can be quickly soldered to existing connections with no additional hardware. This is especially suited to printed circuitry.

**Long life.** Negligible voltage drop that remains stable over lengthy operation promotes long life. 1N2078 virtually unaffected by high current surges . . . maintains high B+ over full-length operation.

**Special insulated case.** Special case insulates against chassis shorts to further ease replacement. Also, 1N2078 dissipates its own heat . . . needs no heat sink . . . yet never requires derating. Only leads get hot.

You can replace any other device and, in some cases, rectifier tubes, with the new, high-quality Tung-Sol 1N2078. For complete information . . . to stock up, contact your distributor or: Tung-Sol Electric Inc., Newark 4, New Jersey.

### 1N2078 Maximum ratings (100°C) capacitive load:

(Similar types available with Peak Inverse Voltages ranging from 50 up to 500)

|   |                 |
|---|-----------------|
| Peak Inverse Voltage . . . . .                              | 400 Volts       |
| Continuous D. C. Reverse Working Voltage . . . . .          | 400 Volts       |
| Average D. C. Output Current . . . . .                      | 500 mAdc        |
| Peak Recurrent Forward Current . . . . .                    | 5 Amps.         |
| ½ Cycle Surge Current . . . . .                             | 30 Amps.        |
| Full Load Voltage Drop @ 25°C . . . . .                     | 1.1 Volts       |
| RMS Input Voltage . . . . .                                 | 130 Volts       |
| Minimum Series Resistance (for capacitive filter) . . . . . | 5 ohms, 10 watt |

 TUNG-SOL<sup>®</sup>

You can now **guarantee reliability** if you join Pyramid's

# GOLD RUSH



BURTON BROWNE, New York

affect the time it takes for plate current to reach saturation, they will have some bearing on oscillator frequency. Be especially wary of defects in C94, C95 and C96. In addition, a breakdown in the transformer or feedback network can also throw the oscillator off frequency.

## Vertical Hold

The picture on a Silvertone Model 5160 rolls vertically whenever it is locked into horizontal sync. The rolling can be stopped by counterclockwise rotation of the horizontal hold knob, but then the horizontal sync is lost!

Realignment of the pulse-width AFC and oscillator circuit improved the horizontal stability but did not affect the vertical trouble. Replacement of sync and video tubes made only a slight improvement. Voltages and waveforms in the sync and sweep circuits all seem to be within tolerance, except that the vertical sync pulses are lacking from the input and output waveforms of the sync amplifier at times when the picture is in horizontal sync.

LEE A. HUTCHINS

Cape Porpoise, Maine

*At first thought, it might seem logical to blame this trouble on the coupling circuit between the sync amplifier and the horizontal AFC stage; but experience with similar cases leads me to suspect that the horizontal hold control may be affecting vertical sync by a more round-about route.*

*For instance, we might start by assuming that a lack of AGC voltage is the cause of the vertical trouble. Considering that this receiver has a keyed AGC system, we can reconstruct a logical series of events to explain the whole situation.*

*As you know, the AGC tube will produce a normal output only when the keying pulses applied to the plate coincide in time with the horizontal sync pulses arriving at the grid. If the plate pulses were either speeded up or delayed for any reason, the keying tube would conduct less heavily than normal, and the AGC output voltage would be reduced. This would tend to cause overloading of some IF or video stage, which is a common cause of compression or clipping of the vertical sync pulses.*

*The most probable reason for incorrect timing of the AGC pulses would be a shift in the phase of the horizontal sync signal at some point between the horizontal oscillator and the flyback transformer. You can compensate for this phase shift by slightly adjusting the horizontal oscillator, but then you lose horizontal sync!*

*To test this theory, you might try checking the DC voltage on the AGC line. If it changes in a negative direction when you adjust the horizontal oscillator for good vertical sync (!) the keying tube is likely to be receiving improperly-timed pulses for the reason described.*

*You might expect the horizontal AFC circuit to be capable of compensating for any phase shift in the sweep signal. However, the pulse-width AFC circuit in this*

## Pyramid's New "Gold Standard" $\pm 10\%$ Mylar® Capacitors

Imagine, capacitors that "absolutely guarantee reliability"! Pyramid's new "Gold Standard" capacitors, designed to give a critical tolerance of  $\pm 10\%$  with non-hygroscopic Mylar dielectric, plus high resistance to moisture and high insulation resistance. Standard capacity values! Standard voltage ratings! Standard tolerance of  $\pm 10\%$ ! Previously made only on special order and at premium prices, new "Gold Standard" capacitors are now available to servicemen at a price competitive with ordinary paper capacitors.

For reliability assurance, insist on Pyramid "Gold Standard" capacitors from your distributor. Catalog available.



# PYRAMID

Pyramid Electric Company, North Bergen, N. J.

receiver gets most of its feedback from the input side of the horizontal output tube rather than from the flyback circuit itself; therefore, some phase shifting could be taking place in the output stage without affecting the AFC. A gassy output tube has been known to produce symptoms similar to those you have described.

### Shades of 15,750!

Picture contrast on a Philco Model 5311827 is normal along the right edge of the screen, but becomes progressively lighter toward the left and washes out almost completely at the extreme left edge.

Tubes have all been checked and several bad ones replaced.


ERWIN WHITE

Clare, Mich.

A spurious 15,750-cps sawtooth signal is evidently modulating the electron beam of the picture tube. It is probably being fed into the CRT cathode circuit from the screen grid of the horizontal output tube through the series-connected brightness and width controls (see schematic). The purpose of this unusual hookup is to counteract the raster's tendency to decrease in width when the brightness is turned up.

Higher brightness is obtained by moving the arm of R1B closer to ground. As a result of this action, a smaller proportion of R1B is shunted by R57; thus, the total resistance between the top of R1B and ground becomes greater. This change in resistance produces an increase in the voltage drop across R1B, with a consequent increase in the positive voltage at the arm of R4. A higher screen voltage is then applied to the horizontal output tube, and raster width increases.

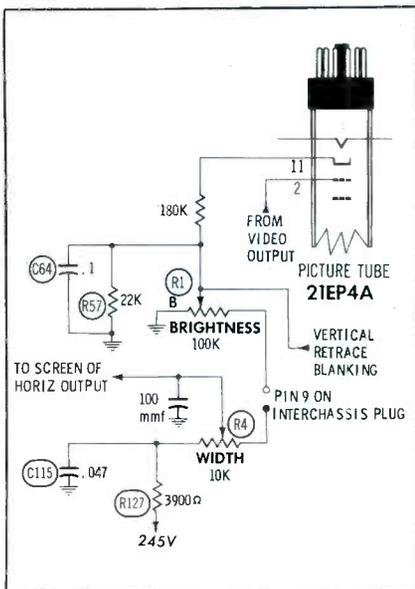Since the screen grid is bypassed by only 100 mmf, proper filtering of the voltage in the width-and-brightness circuit depends mostly upon the condition of C64 and C115. One of these capacitors—especially C64—could well be the root of your trouble.



## best buys in . . . custom hi-fi... **EICO**<sup>®</sup>

- praised by the experts
- beautifully styled
- priced right for you
- lifetime guarantee



### FM Tuner HFT90

with precision "eye-tronic" tuning  
Wired \$65.95\* Kit \$39.95\*  
Cover \$3.95.  
\*Less Cover, FET included  
"One of the best buys you can get."—AUDIOCRAFT.



### STEREO Dual Amplifier-Preamplifier HF81

Wired \$109.95 Kit \$69.95  
"Excellent"—SATURDAY REVIEW;  
and HI-FI MUSIC AT HOME.



### STEREO Dual Preamplifier HF85

Wired \$64.95 Kit \$39.95

### Omni-directional Speaker System HFS2

completely factory-built: 36" h, 15 1/4" w, 11 1/2" d.  
Mahogany or Walnut \$139.95. Blonde \$144.95  
"Eminently musical"—HIGH FIDELITY  
"Fine for stereo"—MODERN HI-FI

Also: Bookshelf 2-Way Speaker System HFS1  
complete with factory-built cabinet, \$39.95



Plus: POWER AMPLIFIERS (14, 22, 30, 35, 50 and 60-watts) from \$23.50.  
INTEGRATED AMPLIFIERS (12, 20, 32 and 50 watts) from \$34.95.

## best buys in test instruments... **EICO**<sup>®</sup>



COLOR & Monochrome DC to 5 MC Lab & TV Oscilloscope #460  
Wired \$129.50  
Kit \$79.95



TV-FM Sweep Generator & Marker #368  
Wired \$119.95  
Kit \$69.95



DYNAMIC CONDUCTANCE Tube & Transistor Tester #666  
Wired \$109.95  
Kit \$69.95

IN STOCK at over 2000 neighborhood distributors coast to coast  
Send for free catalog



PEAK-to-PEAK VTVM #232 & Unit-Probe  
Wired \$49.95  
Kit \$29.95  
(PAT. PEND.)

EICO, 33-00 Northern Blvd., L. I. C. 1, N. Y. PF 4  
Show me how to save 50% on top-quality:  Hi-Fi  
 Test Instruments  Ham Gear. Send free catalog and name of neighborhood EICO supplier.

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

ADD 5% IN THE WEST

At Your Service...  
at big savings

# arkay

Hi-Precision  
**TEST INSTRUMENTS**  
Kits and Wired

Designed and engineered in the Arkay tradition of highest professional quality at lowest cost.

**NEW!** ARKAY VT-10 6-INCH  
MULTI-PURPOSE  
VACUUM TUBE VOLTMETER



Advanced design and precision features make the Arkay VT-10 a truly sensational buy, unmatched at this price. You get exclusive larger 6-INCH 400 ua meter movement, within 2% accuracy, and edge-lighted for easier reading. 1% precision multiplier resistors are used throughout the range switch. There are 7 AC (RMS) and DC ranges, 0 to 1500 volts; also 7 AC (peak-to-peak) ranges, 0 to 2000 volts. Resistance of 0 to 1000 megohms, db and other essential ranges also included. Circuitry features 12AU7 for DC ranges, 6AL5 for AC, meter diodes rectifiers, and transformer operated selenium rectifier. Handsome durable plastic case.

Easy-to-build Kit **\$25.95**  
Wired and tested \$47.95



**ARKAY AV-20 6-INCH  
AUDIO VTVM  
PRE-AMPLIFIER**

An Audio Vacuum Tube Voltmeter of extreme sensitivity, engineered for accurate measurements of RMS voltages.

Easy-to-build Kit **\$29.95**  
Wired and tested \$49.95



**ARKAY AW-30 6-INCH  
DIRECT READING  
AUDIO WATTMETER**

Measures Audio Power Output with speed and precision, 0 to 500 watts in 6 ranges. For laboratory and general use.

Easy-to-build Kit **\$29.95**  
Wired and tested \$49.95



**ARKAY CAP-40 6-INCH  
DIRECT READING  
CAPACITY METER**

1% precision calibration capacitors and 6-inch 200 ua meter movement provide accurate readings. 0 to 1 mfd. in 6 ranges.

Easy-to-build Kit **\$29.95**  
Wired and tested \$49.95



**ARKAY MT-50 6-INCH  
20,000 OHMS  
PER VOLT METER**

A completely portable multimeter of high accuracy. Sensitivity is 20,000 ohms per volt DC, 5,000 ohms per volt AC.

Easy-to-build Kit **\$29.50**  
Wired and tested \$42.95

All prices 5% higher west of Mississippi

See ARKAY completely wired Test Instruments at your dealer. Write for detailed specifications and catalog. Dept. PF

**arkay**



88-06 Van Wyck Expressway Richmond Hill 18, N.Y.

Across the Bench (Continued from page 22)

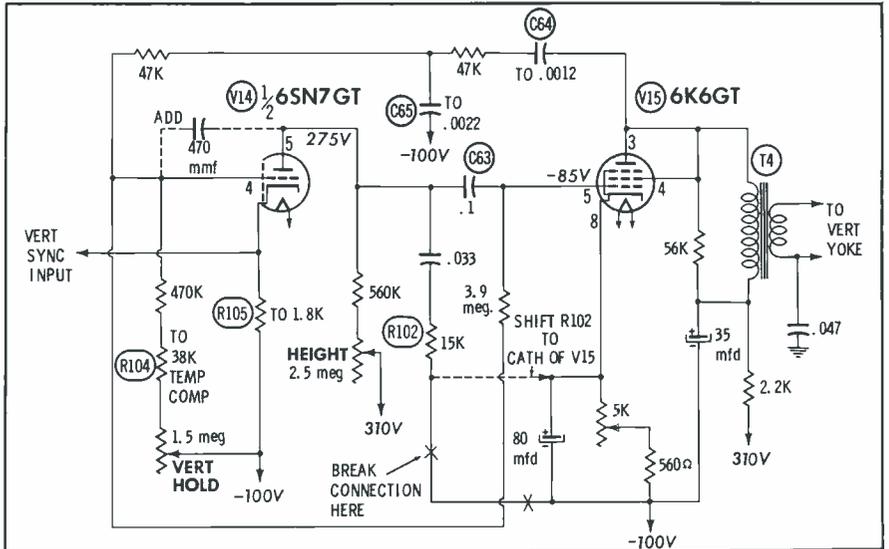


Fig. 5. Schematic of the vertical oscillator and output circuits showing the various changes that should be made to improve operation of the vertical circuit.

were oddly shaped. A capacitance checker showed C63 to be leaky.

**Circuit Improvements**

If you're really conscientious, like to have steady customers, and want that extra buck, here's the *pièce de resistance!* Bring this vertical circuit up to date by including all the changes made in the final production run. Add a 470-mmf mica capacitor between the plate and grid (pins 4 and 5) of vertical multi-

brator V14, change the value of C65 from .0047 to .0022, change R105 from 2.7K to 1.8K, disconnect the end of R102 (15K) from the -100V line and connect it to the cathode (pin 6) of the vertical multivibrator, change C64 in the plate circuit of V15 to .0012 mfd, 1,000V, and make sure that R104 is a 38K temperature-compensating resistor. These changes will produce both better vertical interlace and more stable vertical sync lock. The new

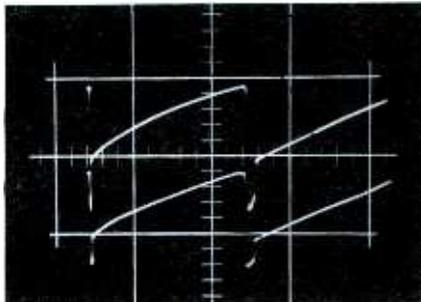


Fig. 6. Spacing of waveforms on either side of C63 indicate leakage in C63.

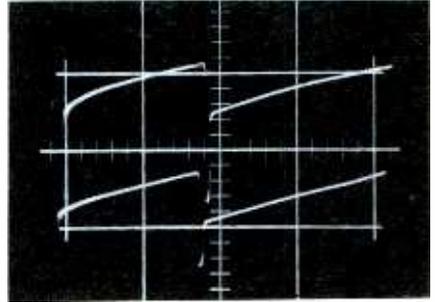


Fig. 7. Normal spacing between the waveforms when C63 has no leakage.

**SAVE TIME with SENCORE**

**SENCORE Handy "36"**

**R C-Substitution Unit**

"36"—Most Often Needed Components at YOUR Fingertips!

3 Pole, 12 position switch individually selects one of the "36" components for direct substitution.

Contains:

- ★ 12—1 watt 10% resistors from 10 ohms to 5600 ohms
- ★ 12—½ watt 10% resistors from 10K ohms to 5.6 megohms
- ★ 10—600 volt capacitors from 100-mmf. to .5 mfd.
- ★ 1—10 mfd., 450V Electrolytic ★ 1—40 mfd., 450V Electrolytic

★ For Shop, Lab, or outside service

Service Instruments Corp., 121 Official Road, Addison, Ill.

ONLY **\$12.95**  
DEALER NET

Model H-36

Completely Isolated Available at all Parts Distributors

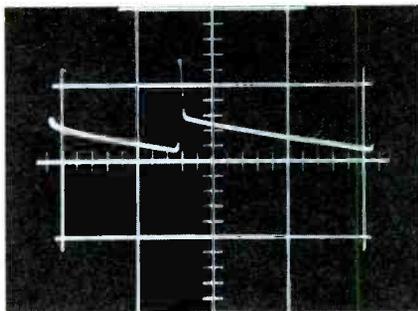


Fig. 8. Vertical-output plate signal should be 1200 volts peak-to-peak.

waveforms—DC amplifier and all—will appear on either side of the new C63 as in Fig. 7. The plate waveform of the vertical-output tube should have an amplitude of 1,200 volts as shown in Fig. 8.

If you aren't weary by this time, here's a bit more you might do. On receivers with the pentode RF stage (production run 2), the following changes will improve its over-all performance:

To cancel background "hiss", remove C50, C52, and R48 (Fig. 9) in the plate circuit of the AF amplifier and AGC clamper V9. Replace with a .0047 mfd (tied to the plate) in series with an 18K, ½-watt resistor to ground. C51 is still the coupling capacitor to the audio output and remains in the circuit. Change capacitor C53 from .0022 mfd to .01 mfd.

To remove IF harmonic feedback in the video detector, add a 2.7-uh choke between the secondary of L13 and the -100V supply (see Fig. 10). Disconnect C39 from ground and reconnect it to the junction of the new choke and the secondary of L13. Completely remove C40 from the circuit.

Should your customer be fortunate enough to have a receiver with a cascode 6BQ7 RF amplifier (production run 4 or 5), you might check the following changes to be sure it's completely up to date:

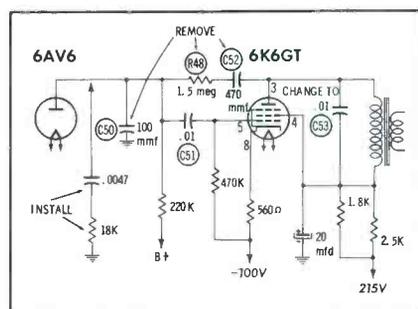


Fig. 9. Schematic of audio circuit showing changes to remove background hiss.

General Instrument has  
the **RIGHT RECTIFIER**  
for every **TV** set



**AUTOMATIC**  
**PT5 Silicon**  
**RECTIFIERS**

**RADIO RECEPTOR**  
**Selenium**  
**RECTIFIERS**



Don't be fooled by an "all or nothing at all" approach. Selenium and Silicon rectifiers both have a place in today's TV sets . . . and General Instrument supplies the very best!

Radio Receptor "Safe Center" selenium rectifiers have proved their reliability and long life in millions of circuits through the years. When your replacement calls for *selenium* there is no better rectifier.

AUTOMATIC PT5 Silicon rectifiers are the first choice of leading TV set manufacturers switching to silicon in their new models. When replacing or converting to *silicon*, install the PT5 for maximum performance and picture brightness.

Both these outstanding rectifiers are brought to you by GENERAL INSTRUMENT, your finest source of semiconductor components!

General Instrument Distributor Division  
**RADIO RECEPTOR COMPANY, INC.**  
Subsidiary of General Instrument Corporation  
240 Wythe Avenue, Brooklyn 11, N. Y. EVergreen 8-6000



# Precision cutting... a simple job


with the new

## Centralab

### SK-2

### SHAFT-KUT

### TOOL

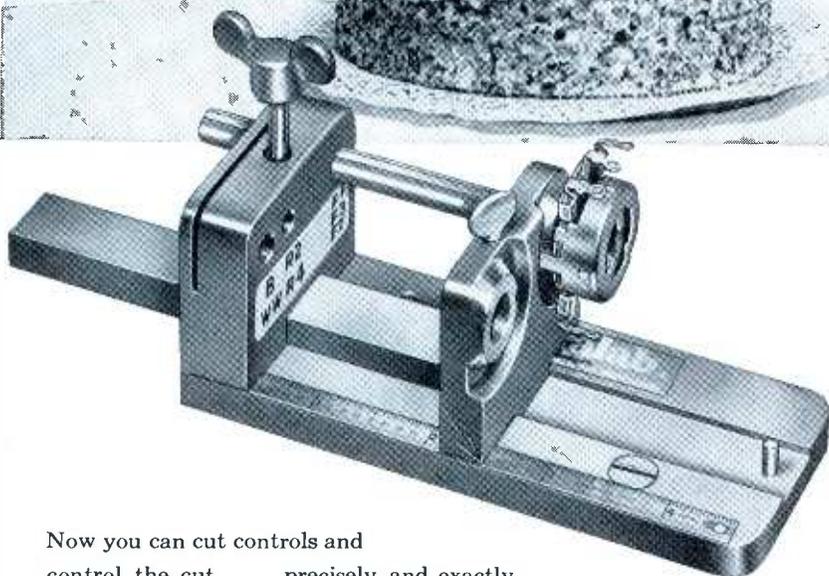

Now you can cut controls and control the cut . . . precisely and exactly. CENTRALAB'S Shaft-Kut Tool is a precision instrument, *guaranteed* to make a really simple job of cutting shafts to the exact size you need.

With this tool you can cut any single or dual control . . . or switch shaft, and get cuts that are accurate to  $\frac{1}{64}$ th of an inch! The tool and calibrated jig are made of case hardened tool steel, designed to last a lifetime.

You can't make a wrong cut with the CENTRALAB Shaft-Kut Tool! And the price is less than half what you'd expect to pay for a precision device of this kind . . . a low \$4.95 dealer net. Ask your distributor to show you how easy it is to use this new tool.

# Centralab

B-5931

A DIVISION OF GLOBE-UNION, INC.  
942D E. KEEFE AVE. • MILWAUKEE 1, WIS.  
IN CANADA: 804 Mt. Pleasant Rd. • Toronto 12, Ont.

CONTROLS • ROTARY SWITCHES • CERAMIC CAPACITORS  
PACKAGED ELECTRONIC CIRCUITS • ENGINEERED CERAMICS

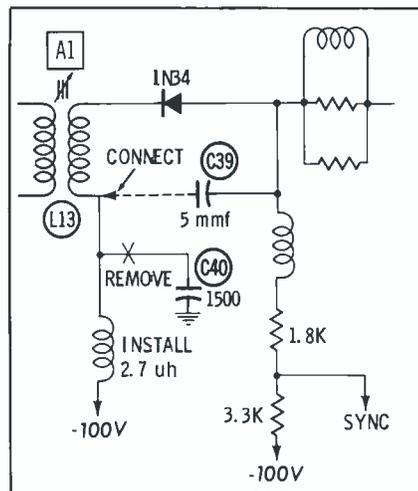


Fig. 10. Video-detector circuit showing changes to prevent harmonic feedback.

To remove bends (flagwaving) at top of pix, connect a 10K,  $\frac{1}{2}$ -watt resistor in series with a .22-mfd capacitor between the junction of C70 and C71 in the cathode circuit of the horizontal-sync discriminator and ground (see Fig. 11).

To improve sync stability, a 47K,  $\frac{1}{2}$ -watt resistor is now connected between the screen grid (pin 6) of V11, the 1st sync amplifier, and the 115V line as shown in Fig. 12. Also connect a 10-mfd, 450-WVDC electrolytic capacitor (+ terminal) to the screen of V11 and (- terminal) to the -100V line. Resistors R54 and R55 should be changed from 100K to 47K each. Also, change R66 and R67 in the plate circuit of the 2nd sync amplifier to 100K, 1-watt units.

In the AGC circuit (Fig. 13), C56 should be changed to .047 mfd and R58 to 470K. Also, in the cathode network of the AGC amplifier, R65 is changed to 8.2K, R63 and R64 are deleted, and R61 and R62 are changed to 220K, 1 watt.

What does a job like this cost? All right, here are the figures: It

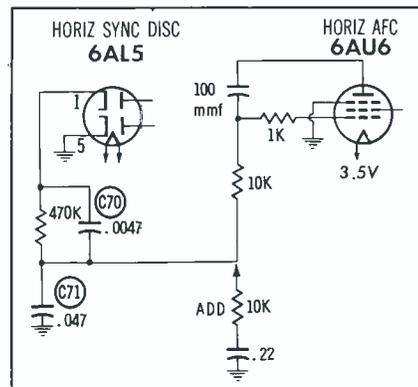


Fig. 11. Horizontal-AFC circuit showing changes to prevent bend in picture.

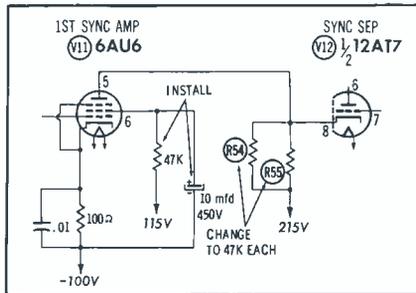


Fig. 12. Schematic showing sync-circuit changes to improve picture stability.

took approximately 10 hours of labor, a new 17BP4-B aluminized picture tube, 28 capacitors (8 of which were OK and within tolerance, 14 leaky, and 6 out of tolerance), 8 resistors (only 4 were actually defective), 6 receiving tubes, and one set of tuner strips. Cash money (net), about \$45. Results? One of the prettiest pictures in television!

### More on the RCA KCS47

Beginning with the 8TV321 RCA manufactured in 1947, the pulse-width AFC system survived almost unchanged through the KCS60A originated in 1950. With only slight modifications in the value of some components and a revamping of the horizontal-output stage, it is still a very popular circuit.

An oscilloscope with a low-capacitance probe is an absolute must for troubleshooting this sort of circuit. In fact, I also recommend using a 10 to 1 low-capacitance probe when investigating video amplifier, AGC, or sync circuits. It adds to the scope's input impedance, is welcome isolation between receiver and test instrument, and permits almost unlimited use of the scope's DC amplifiers.

### Pulse-Width Horizontal Sync System

This system was developed so

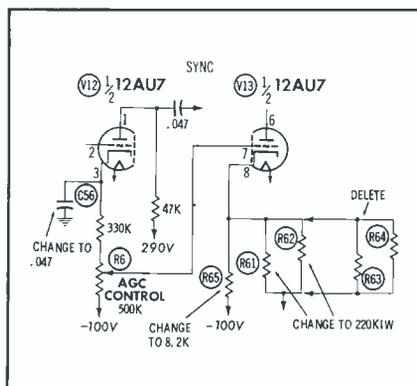


Fig. 13. Schematic showing the changes necessary to update the AGC circuit.

## a real sweet combination... the new FASTATCH FDK-100 Dual Control Kit

with the  
**Centralab** SK-2  
Shaft-Kut Tool  
**FREE!**



If you have a birthday *any time this year*, CENTRALAB has a present for you NOW... a real money-saving offer that gives you a \$41.90 value for only \$32.70.

This \$9.20 saving is yours when you buy the new CENTRALAB Fastatch FDK-100 Dual Control Kit and SK-2 Shaft-Kut Tool combination. The handy kit contains 24 controls and 9 switches—that let you quickly snap together any of 720 different dual control combinations.

The Shaft-Kut Tool assures you of *precise* control or switch shaft length... accurate to  $\frac{1}{64}$ th of an inch. It is available separately, at \$4.95, actually less than half the price you would expect to pay for it.

So don't waste any more time with special trips to your distributor when you need a dual-concentric. Have the control you need at your fingertips with this wonderful kit-and-tool combination. But don't delay... *this money-saving offer is for a limited time only!*

**Centralab**  
B-5940

| HERE'S WHAT YOU GET   | REGULAR PRICE  |
|---|----------------|
| 24 controls and 9 switches...<br>all factory assembled and tested | \$32.70        |
| Sturdy steel cabinet.....   | 4.25           |
| Shaft-Kut Tool.....   | 4.95           |
| <b>Actual value</b>   | <b>\$41.90</b> |

**You get all this for \$32.70—the cost of the controls alone! The Shaft-Kut Tool and steel cabinet are FREE!**

A DIVISION OF GLOBE-UNION, INC.  
942D E. KEEFE AVE. • MILWAUKEE 1, WIS.  
IN CANADA: 804 Mt. Pleasant Rd. • Toronto 12, Ont.

**CONTROLS • ROTARY SWITCHES • CERAMIC CAPACITORS  
PACKAGED ELECTRONIC CIRCUITS • ENGINEERED CERAMICS**




# "Call Backs"

ARE APPRECIATED  
BY SHOW FOLKS . . .

.. but **NOT** by  
**TV Servicemen!**

You will appreciate the time-saving economy and flexibility of MOSLEY Premium Quality TV Accessories. Low loss MOSLEY accessories provide neat, efficient TV installations resulting in satisfied customers . . . fewer call backs!

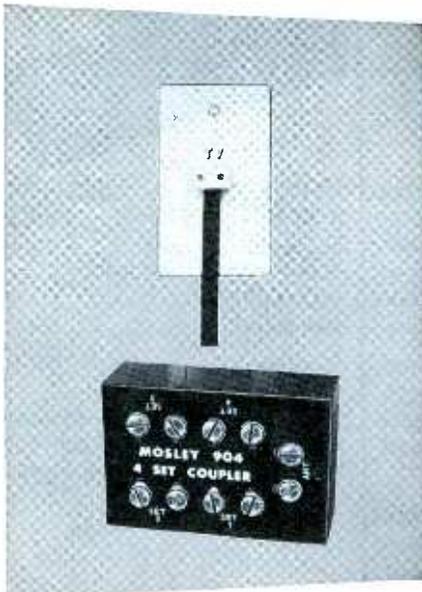**PROFIT-WISE SERVICEMEN  
USE MOSLEY  
TV ACCESSORIES**



Install MOSLEY TV Accessories . . . your customers will appreciate it, too!

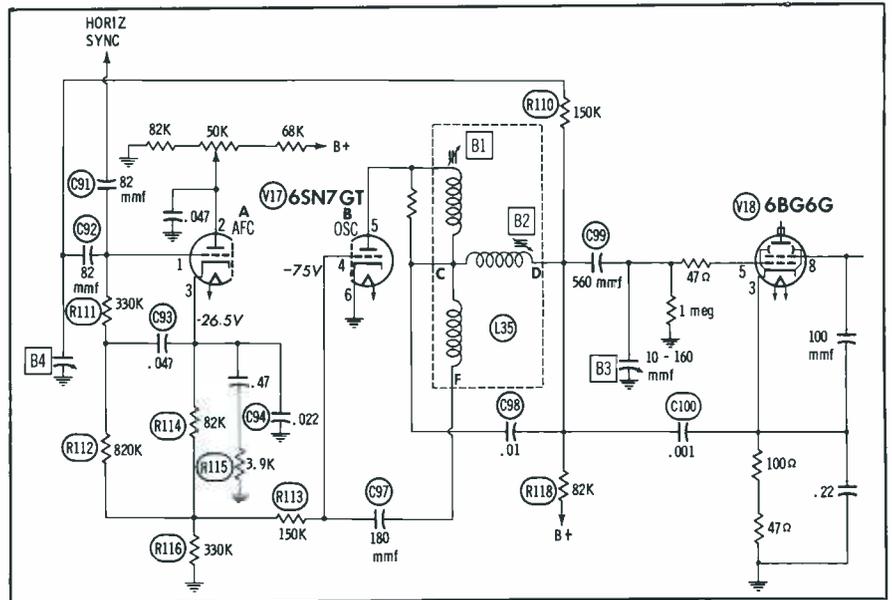


Fig. 14. Schematic of the pulse-width AFC and blocking-oscillator circuits.

that a single 6SN7 (now 6CG7) might develop a corrective voltage from comparison of the sync and horizontal - oscillator frequencies, and also act as the oscillator itself. The windings of L35 (Fig. 14) constitute a blocking-oscillator transformer. It operates in conjunction with the B section of V17 which, in its free-running state, oscillates at approximately 15,750 cps.

A sawtooth signal from the oscillator is fed back to the control grid of horizontal - AFC tube V17A through R110 and C92. Simultaneously, horizontal sync pulses are applied to the grid of the AFC stage through 82-mmF capacitor C91. Horizontal lock-in capacitor B4 is adjusted so that the peak of the sawtooth voltage is just below the cutoff point of V17A. Neither sawtooth nor sync-pulse signal alone is strong enough to cause the tube to conduct. However, when both reach their positive peaks simultaneously,

V17A conducts and a proportionate amount of voltage is developed across cathode-load resistors R114 and R116.

In order to understand how AFC action occurs, you must first know the factors which influence oscillator frequency. Using the simplest possible explanation, let's say that oscillator frequency is determined by the time it takes the charge on C97 (accumulated through grid conduction of the oscillator tube) to leak off through R113 and R116. Further, if the voltage on C97 is increased or decreased, its discharge time will increase or decrease proportionately.

The AFC and oscillator circuits are designed so that the oscillator will operate at the correct frequency when horizontal sync and feedback signals at the grid of the AFC tube coincide, as shown at the top of Fig. 15. If, however, the frequency of the oscillator tends to be lower

## SERVICEMEN KNOW!

Here they pay less and get the best

### HUSH®

Chemically-Electronically, engineered for Tuners and Switching Mechanisms.

When New HUSH is applied it will wash-away that dirt, leaving clean and positive contacts protected by a lasting lubricant. New HUSH is made from the finest solvents and it contains Electro-Silicone oils.

Also available—2 oz., 8 oz., 32 oz. containers 6 oz. Spray can **\$2.25** net

### EVER-QUIET®

Since 1949

VOLUME CONTROL AND CONTACT RESTORER

EVER-QUIET is a free-flowing liquid that leaves no powder residue. Scientifically designed to seep around the shaft and penetrate the control or potentiometer, cleaning the contacts and leaving a safe protecting film. Harmless to metals, wire or carbon.

Also available—32 oz. containers 6 oz. Spray can **\$1.59** net

2 oz. Bottle & dispenser **79c** net

**CHEMICAL ELECTRONIC ENGINEERING, INC. Manawan, New Jersey**



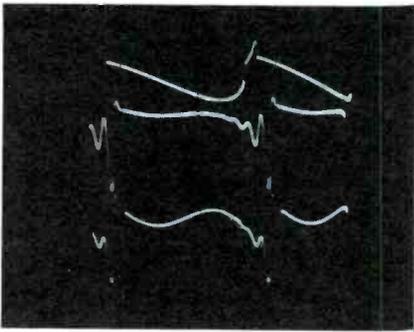


Fig. 15. Simultaneous display of signals in horizontal-AFC and oscillator stages.

than that of the incoming sync pulses, more of each sync pulse will ride high on the sawtooth, causing the AFC tube to conduct for a longer period. This increases the charge across C94 and C95 and the voltage across R116. In turn, the bias on the oscillator is decreased, so it begins conducting a little earlier. Oscillator frequency is thus increased. If, on the other hand, the oscillator is running too fast, most of the sync pulse rides down the steeper slope of the sawtooth, thus reducing the period of AFC tube conduction. This reduces the voltage across R116 and increases the bias on the oscillator. Oscillator frequency decreases because C97 will have to discharge to a lower level before a new cycle can start.

Capacitors C94 and C95, along with resistor R115, filter the AFC tube's current pulses, providing a DC control voltage proportional to conduction time. C95, along with R115, also has another duty, that of providing an "anti-hunt" circuit to prevent overcontrol of the oscillator. Incidentally, if C95 or R115 fails, you'll notice a "flagwaving" at the top of the picture. Should the grid-to-cathode capacitor C93 short, you'll have a narrow picture and lose horizontal sync. The values of all resistors in the AFC circuit are quite critical; they should be disconnected


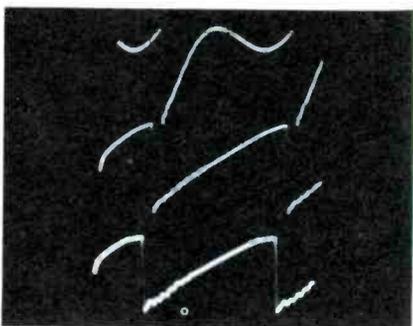


Fig. 16. Key waveforms at oscillator transformer and output control grid.

## TOBE SERVICE CAPACITORS

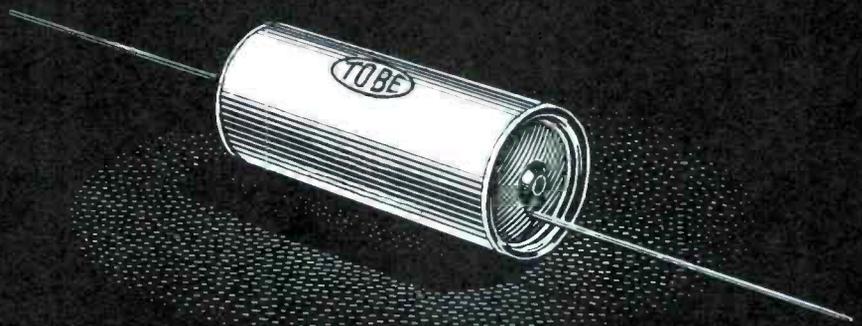

### Designed exclusively for service

Tobe Service Capacitors are the only capacitors literally "designed from the ground up" to meet the exacting requirements of modern radio and TV servicing. Before a capacitor was ever produced, Tobe engineers determined the ideal characteristics—then borrowed from their 36 years experience in the design and manufacture of high-quality commercial and industrial types. Result: capacitors like the plastic-sleeved streamlined "Jets" that stand up in the toughest circuits.


You owe it to yourself to try Tobe Service Capacitors on your next job. The line is complete—and they cost no more! See your Tobe Distributor today for full details or write Tobe Deutschmann Corporation: Distributor Division, 2900 Columbia Ave., Indianapolis 5, Ind.



**TOBE**  
RADIART  
CAPACITORS

*Old Hands at Dependability*

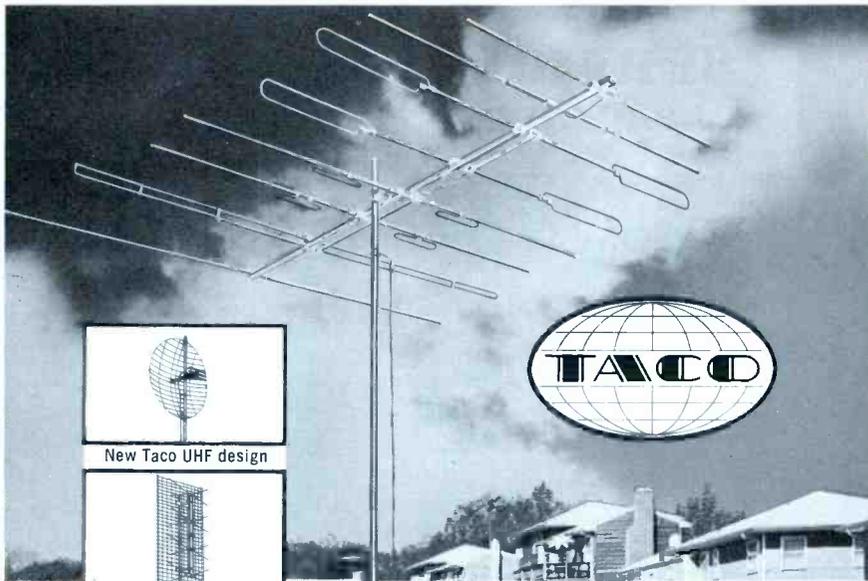
[www.americanradiohistory.com](http://www.americanradiohistory.com)



New Taco UHF design



Popular Taco Bowtie

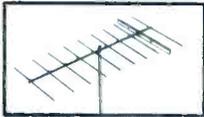

Taco area-sized antennas

THE **TV-riffic** ANTENNAS

TECHNICAL APPLIANCE CORPORATION, Sherburne, New York.

## Use the best— TO BE THE BEST—

Back up your skills and reputation with the best—always use a Taco antenna to assure top-notch performance and lasting satisfaction. You'll find Taco antennas go up easier and work better—and you make more money!

*Write for complete details*

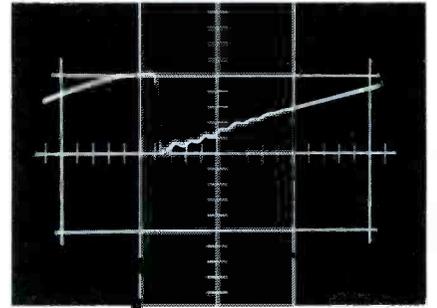


Fig. 17. Expanded waveform at grid of horizontal-output tube shows transients.

from the circuit during value checks.

### Horizontal Oscillator

Each time the oscillator tube conducts, the oscillator transformer is pulsed. The familiar sine-wave portion of the waveform (Fig. 16A) is generated at point C of L35 by the resonant circuit comprised of coil section C-D and C98. The required sawtooth signal (Fig. 16B), is developed at terminal D of L35 because of the charge and discharge of C100. Feedback to sustain oscillation is furnished by coil section C-F and is coupled through C97 to the oscillator grid. Oscillator frequency is affected primarily by the values of C97, R113, R116, C98, C99, C100, and R118. Leakage in C98 is often the cause of instability; C97 is the usual culprit when the oscillator goes wild (Christmas-tree effect). Proper circuit operation can be obtained only if B1, B2, B3, and B4 are properly adjusted.

### Horizontal System Transients

Now, let's discuss the waveform at the grid of the horizontal-output tube (Fig. 17). Frankly, this is about the worst drive signal I've ever seen; but, believe it or not, there are no bad components in the circuit. It's simply that this receiver has developed more oscillatory transients than usual. Look at the waveform in Fig. 18 and you'll have much of the answer before you. This

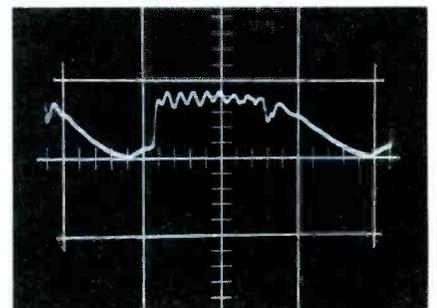


Fig. 18. Transients in the signal at screen grid of horizontal-output tube.

**SUBSTITUTE PARTS  
WITH-OUT SOLDERING**  
Quickly with **E-Z-Hook** "SUB" Connectors. Easily Has 1001 Uses!

**NEW** E-Z-Hook "SUB" Connectors

Connect a speaker, or

Substitute a

- transformer
- capacitor
- resistor, or

In Seconds!!

- ★ Makes connections instantly!
- ★ Won't pull off!
- ★ Insures positive contact!

Saves time, money and parts in servicing, experimenting, instructing and production.

**E-Z-HOOK SUB**  
No. 71-1...SUB... Only 69¢ ea.

Six Colors! - for Easy Lead Identification  
Canadian Rep.: Len Finkler & Co., Toronto, Ontario

ORDER THROUGH YOUR PARTS DISTRIBUTOR  
E-Z-HOOK TEST PRODUCTS  
Dept. F, 1536 Woodburn Ave  
Covington, Ky.

**E-Z-HOOK TEST PRODUCTS**  
SAFE • FAST • SURE

**Grips the screw!**  
Drives it too!

**Quick-Wedge  
SCREW-HOLDING  
SCREWDRIVER**

2" to 14" blades, 4 bit sizes.  
Available with shockproof plastic covered tubing  
Unconditionally guaranteed

**ASK FOR IT AT YOUR DEALER**  
Kedman Co., 233 South 5th W.,  
Salt Lake City, Utah

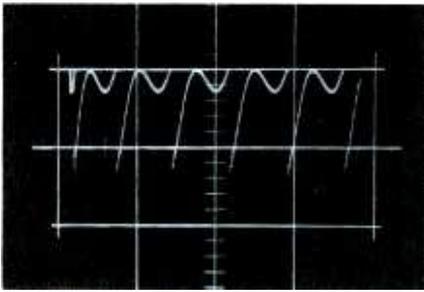


Fig. 19. Setting of the hold control must not affect waveform at terminal C.

is the screen waveform of the horizontal output tube. Varying the width control changes its amplitude almost 100 volts.

Take comfort, however, in several convenient conditions. Of the 63-microsecond trace and retrace period, 10 microseconds are utilized for blanking the return trace. This, coupled with the fact that 5 to 10% overscan is usually employed, results in most of the transients not being seen because they occur during blanking, or when the beam is past visible portions of the screen. In addition, the output tube doesn't begin significant conduction until approximately half way up the positive portion of the rising sawtooth waveform.

#### What To Do

In a situation like this, where there are no defective components, you can reduce the condition by carefully selecting a new horizontal-output tube, and by carefully adjusting the width and drive controls. But whatever you do, don't forget that for proper alignment of the horizontal-oscillator transformer, the waveform at junction C *must* look like Fig. 19, and must not change even when the horizontal-hold control is varied across its entire range. Only then will you have successfully repaired the horizontal oscillator of these pulse-width television receivers! ▲


### Planning To Move?

If so, notify us by the 15th of the month to assure uninterrupted delivery of PF REPORTER.


Be sure to include both your old and new address. (Or better yet, enclose a current mailing label with your new address.) Send to:

**PF REPORTER**  
Circulation Dept.  
2201 E. 46th Street  
Indianapolis 6, Ind.

# Next time you replace a...

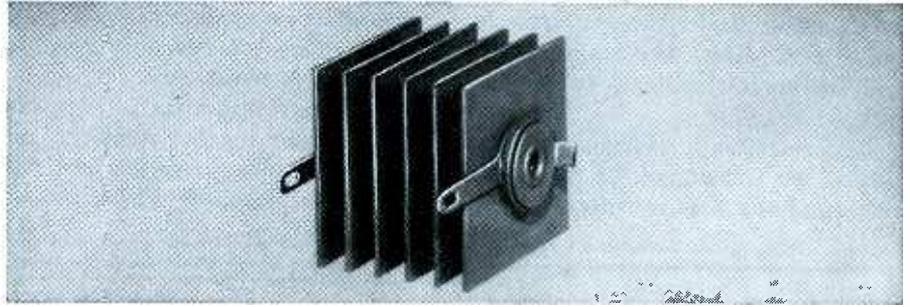

## with a

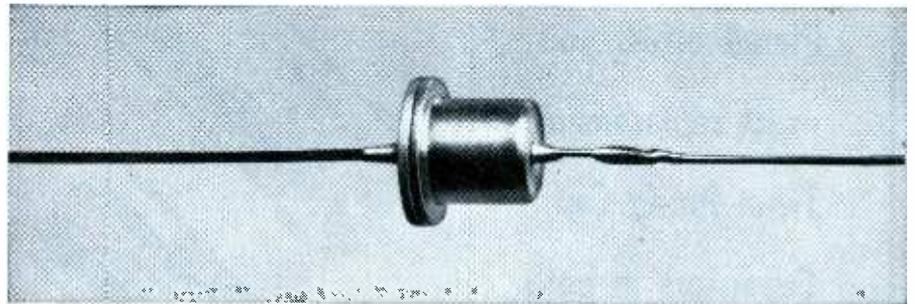

## ask for...



With just two Sylvania silicon rectifier types, SR200 and SR500, you can replace over 83 selenium rectifier types made by 5 different manufacturers. Type SR200 with a maximum rating of 200ma, 300 v is intended for low-voltage general purpose applications. Type SR500 with a maximum rating of 500ma, 400 v is designed for medium-power rectifier applications. Both types are in stock at your authorized Sylvania distributor. Get your free copy of Sylvania's Selenium Rectifier Replacement Guide from your Sylvania Distributor or write Sylvania direct—1100 Main St., Buffalo, N. Y.



# SYLVANIA

SYLVANIA ELECTRIC PRODUCTS INC.  
1740 Broadway, New York 19, N. Y.  
In Canada: P. O. Box 1190, Station  
"O", Montreal 9.

LIGHTING • TELEVISION • RADIO • ELECTRONICS • PHOTOGRAPHY • CHEMISTRY-METALLURGY

## Audio Facts

(Continued from page 26)

As signal frequency increases, the reactance of C decreases, giving a smaller total impedance and hence lower output voltage.

If either component opens, signal amplitude increases, giving too much treble and excessive scratch noise. If C shorts, the entire signal will be greatly reduced in amplitude.

For variable - reluctance cartridges, the inductance of the cartridge and the loading resistor pro-

vide roll-off as shown in Fig. 1C; bass boost is provided elsewhere. As frequency increases, inductive reactance increases, leaving less signal across R, thus providing proper roll-off. A load resistor which is open or increased in value would cause excessive treble and surface noise. It is imperative that the load resistor have the correct value for the cartridge being used.

Frequency response troubles often originate in the equalizer, in which case switch contacts are the most likely suspects. These should

be checked if the fault is traced to the equalizer. Poor switch contacts and cold solder joints comprise virtually all equalizer troubles.

## The Preamplifier Unit

The preamp unit is not too different from other audio amplifiers. It uses single-ended amplifier circuits, RC coupling, and in some cases feedback and cathode followers. However, preamps do have circuitry not found in other audio equipment; i.e., switching circuits, equalizers, and tone controls. In addition, they are designed to handle extremely low-level signals. We will concentrate on these in our tests and measurements.

Fig. 2 is the complete schematic of a typical hi-fi preamp. Five separate inputs are available through selector switch SW1. Three of these are for signals greater than 0.1 volt, and can be used for tuner, tape recorder, TV, etc. The other two are for magnetic phono cartridge and microphone, which have smaller signal levels. Each input has its own 500K level control.

Low-level input signals are first amplified by stages V1A and V1B, then by the other four stages. High-level signals bypass the first two stages. The output signal is taken from the cathode-follower stage V2B, providing a low-impedance output and allowing the use of almost any length of connecting lead. B+ and heater voltages are obtained from the power amplifier chassis. In addition to bass, treble, and volume, front-panel controls include input selector switch SW1, SW2 for selecting the turnover frequency, and SW3 for roll-off.

Should preliminary tests indicate trouble in the preamp, it can be localized by the methods described in previous installments of this series. If the trouble exists for all inputs, one of the last stages in the preamp must be at fault. Trouble for phono input, however, does not necessarily mean that the phono is at fault, because stages V1A, V1B, or the equalizing circuits could be defective.

It is important to remember that in the low-level stages of a preamp, even a trivial fault can be serious. Shielding, lead dress, component replacement, and soldering are just as

Now . . .

**Planet offers you  
exact replacement  
Twist Prong Can  
Capacitors in both  
Solder Lug and  
Printed Board  
Construction**



Planet Twist Prong Can Electrolytics are the choice of many top TV and electronic equipment makers. These firms use Planet "TP's" because of uniform quality, workmanlike construction and freedom from field troubles. Now Planet is making these same values and sizes available to you, the men who service this equipment. Ask for Planet "TP's" by name at your parts distributor.

We will send you our catalog listing upon request.

**PLANET SALES CORPORATION**

**BLOOMFIELD, NEW JERSEY**

critical as in TV tuners.

Because signal level is so low, even small amounts of hum or noise are objectionable. Suppose, for example, that 1 millivolt of hum were introduced at the preamp input. If the input signal is 10 millivolts, hum is down only 20 db. This same amount of hum or noise introduced in a later stage would not be nearly as objectionable. If signal level were 10 volts, the difference between it and 1 millivolt would be 80 db. For proper results, signal and hum levels should be at least 60 to 70 db apart.

### Switching

Switching troubles in preamps are not uncommon, especially when the switches are handled roughly. The major troubles encountered are open and dirty contacts. A certain amount of signal tracing is usually required to find the trouble.

In Fig. 2, the input selector switch SW1 is shown in the No. 1 position, connecting the top high-level input (as seen in the diagram) to the input of V2A through the top portion of the switch. The middle section of SW1 grounds the unused inputs. The bottom section is used only to apply phono or microphone signals to the first low-level stage V1A.

Usually, several input devices (phono, tuner, microphone, etc.) are connected to the various input jacks. When operating the system on phono, an extra signal coming through is due to an ungrounded contact on the middle section of SW1. When signal is not getting to the amplifier stages at all, check the signal path through SW1 with an ohmmeter. Open contacts can usually be remedied by bending the stationary sections so that normal contact again occurs. Noisy switching is caused by dirty contacts, which can be cleaned with carbon-tet or other suitable contact cleaner. Hum and noise can be caused by open or partly open contacts; for locating the guilty ones, the schematic diagram is a most valuable aid.

### Frequency Response

Frequency response limits are largely determined by the preamp. If the customer complains of low-end or high-end distortion, be sure to check the preamp first. As a

first step, make sure the customer is using the controls properly. Mis-adjusted tone and/or equalizer controls could be responsible for all the trouble.

In measuring response of pre-amplifier circuits, it's wise to apply the audio signal to the phono or microphone jack to check all stages at once. Naturally, tone controls and equalizers should all be set to flat. The simplest way to measure response (described in a previous article) is to vary the input fre-

quency over the audio range and check the output voltage across the range. A more accurate method of checking frequency response is shown in Fig. 3. Here, the same VTVM is used to measure both input and output signal voltages, thereby reducing errors due to meter inaccuracy.

The calibrated attenuator is a variable resistance which can be adjusted to provide a wide range of attenuation. It is designed so that, at any setting, the input and output re-

**SAVE TIME**  
with  
**SENCORE**

**New! Improved!**  
**TRANSISTOR CHECKER**

*America's newest, most popular test instrument*

Simple to Operate. Controls are accurately set for each transistor by referring to replaceable set-up chart on rear. Test leads or socket provides for fast hook-up.



**NOW CHECKS:**

- ★ **Transistors** for opens, shorts, leakage and current gain. Only tester that tests power transistors as used in car radio outputs.
- ★ **Crystal Diodes** checks forward to reverse current ratio on all diodes.
- ★ **Selenium Rectifiers** checks forward and reverse currents.

**Service Instruments Corp., 121 Official Rd., Addison, Ill.**


**MODEL TRC4**  
**\$17.95**  
DEALER NET

Cannot become obsolete. Approved by leading manufacturers.

See other SENCORE ads in this issue.

# XCELITE PLIERS

have a ...

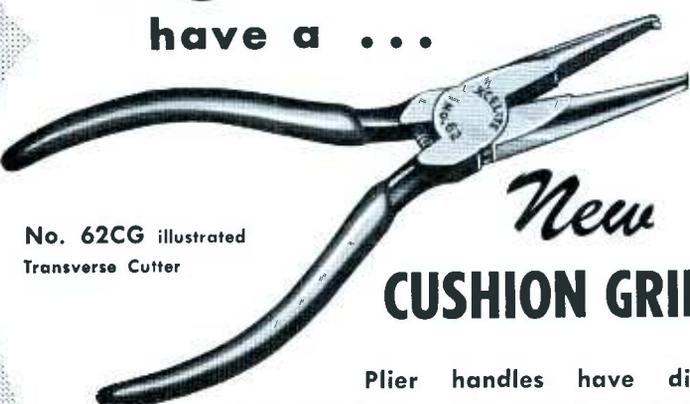

**No. 62CG illustrated**  
Transverse Cutter

*New*  
**CUSHION GRIP!**

Plier handles have dipped plastic coating ... permanent, comfortable.  
Heads polished and buffed to a "mirror finish".  
All pliers available ... See Your Distributor!

Gives pliers a "Feel" that inspires Craftsmanship!

**XCELITE, INCORPORATED**  
ORCHARD PARK, NEW YORK  
Canada: Charles W. Pointon, Ltd., Toronto

**XCELITE**  
*Quality Hand Tools*  
PREFERRED BY THE EXPERTS

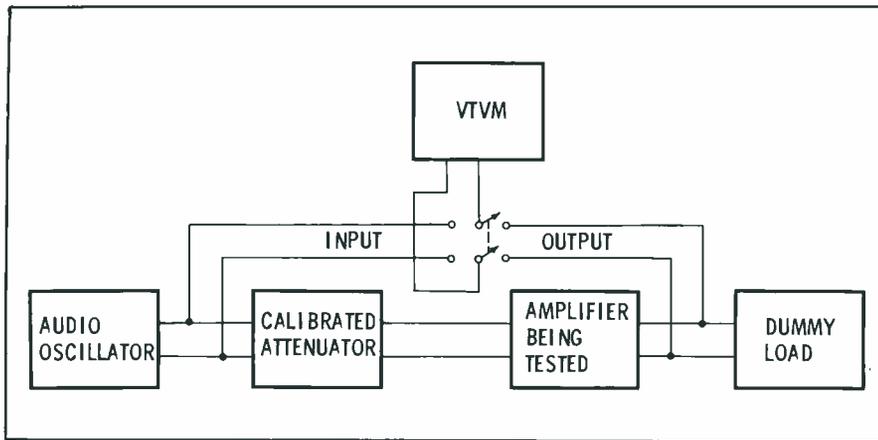


Fig. 3. Setup for testing frequency response employs a calibrated attenuator.

sistances of the unit are the same. One such unit gives attenuation from 0.1 to 100 db. The amount of attenuation is easily read from the front-panel control.

To measure frequency response, adjust the oscillator output to a predetermined voltage level as indicated on the VTVM (about two-thirds the maximum voltage output of the amplifier). Then, insert maximum attenuation, switch the meter to measure output, and adjust the attenuator so that the meter reads the same as the input. Gain of the amplifier is then equal to the loss offered by the attenuator. To make the test more accurate, it is wise to take readings at several different signal levels, and to observe the output on a scope. Good frequency response is not of much value if the output signal is distorted.

#### Testing Tone Controls

Separate bass and treble controls (both one megohm pots) are located between stages V3A and V3B. In testing these controls, a frequency response curve can be plotted. Applying an input signal to one of the high-level input jacks, the tone controls are adjusted until gain is the same at three different frequencies — 50, 1,000 and 12,000 cycles can be used for most amplifiers. Equal gain at these frequencies corresponds to flat response — zero boost and zero droop in both bass and treble circuits. Without changing the bass control setting, response at the high end can be checked with the treble control at maximum, then at minimum. Returning the treble control to the previously determined flat position, response curves can be observed with the bass at maximum, then at minimum. By converting the voltage changes to decibels, the differences can be compared with published values. In this preamp, the bass control should have a total deviation of about 30 db ( $\pm 15$  db), the treble control about 32 db ( $\pm 16$  db). If interaction between controls is suspected, curves can be run with both controls at maximum, then with both at minimum. These can then be compared to the curves run previously.

Locating troubles in these circuits is easier when you understood the purpose of the components. The

# new instruments from Jackson

## Peak-To-Peak and RMS VTVM

- Large 7" Meter and Hairline Pointer for greatest accuracy.
- Fast warm up time — complete accuracy in less than 5 minutes.
- Single probe for all measurements.
- Accurate AC voltage readings from 20 cycles to 2 mc.
- All-new tube and silicon diode circuitry.
- Factory calibrated for guaranteed accuracy.

**\$6995 NET**

RANGES: DC Volts ( $\pm$ ), AC volts, 1, 5, 10, 50, 100, 500, 1000 volts full scale. Separate 1V RMS Peak-To-Peak, and Zero-Center DC scales. Ohms: RX1: 10, 50, 100, 1k, 10k, 100k and 1 meg. Center of RX1 Scale, 10 ohms. Accuracy, DC and Ohms, 3% full scale; AC volts, 5% full scale.



MODEL 590



MODEL 591

## Wide Range Capacitance Tester

- Tests capacity from 10 uuf to 1000 uf in 4 ranges.
- Color-coded range push-buttons match scale colors.
- Graduated leakage tests for polarized or non-polarized capacitors.
- Low voltage leakage test for transistor-type capacitors.
- Graduated Power Factor test, 0 to 60%.
- Electron Ray Tube Indicator for all tests.
- Factory Wired and calibrated for guaranteed accuracy.

**\$6495 NET**

Coming Soon From Jackson — More New "Service-Engineered" Test Equipment

See Your Distributor or Write Today for Literature



16-18 S. Patterson Boulevard  
Dayton 2, Ohio

IN CANADA: The Canadian Marconi Company

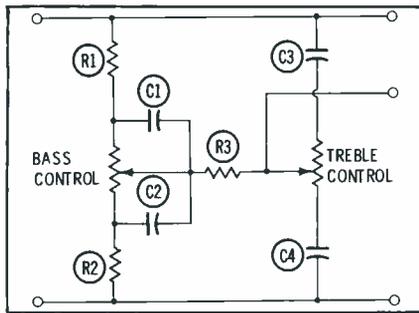


Fig. 4. Tone control circuit provides bass and treble boost and attenuation.

tone control circuit shown in Fig. 4 is very often used. R1 and R2 limit the range of the bass control, C1 controls bass cut, C2 bass boost. R3 provides isolation and prevents interaction between bass and treble controls. C3 controls treble boost, C4 treble cut. Troubles can usually be traced to one of these four capacitors, or to dirty controls.

Suppose, for example, that there is no boost, and over-all gain is increased. It is likely that C3 is shorted, or else quite leaky. However, if gain was not changed appreciably, then C4 would probably be open. Similar troubles could occur for the bass-circuit capacitors.

#### Signal Tracing

That the audio generator can be very useful in signal tracing is illustrated by this typical service case. The complaint is "excessive distortion" at any volume level for any input source. This places the trouble in the sections handling all signals and rules out stages V1A and V1B. Tube replacement does not remedy the trouble, and measurement of the high B+ (at B1 in Fig. 2) shows it to be close to the published value of 180 volts, so other tests must be made. The signal generator is set to 1,000 cps, and about one volt of signal is applied to a high-level input. Touching the oscilloscope lead

to the grid terminal (pin 7) of stage V2A reveals that a sine wave exists at that point, as well as at pin 8 of the same stage. However, at the grid of V3A (pin 7), a slight flattening of the positive portion of the signal is noticed. A check at the plate of the same stage shows the negative alternation clipped. Evidently the distortion is being introduced between the cathode of V1A and the grid of V3A.

Voltage measurement shows +8 volts at pin 7, whereas +2 volts is normal. This points to a leaky cou-

pling capacitor between pins 8 of V2A and pin 7 of V3A; its replacement cures the trouble. In signal tracing this amplifier, notice that the cathodes of V2A and V2B are signal elements, while the plates of these stages are not.

This same test can be used to locate hum, noise, or the point at which the signal is lost entirely. The use of systematic servicing procedures, along with intelligent application of test equipment, should eliminate most of the problems in pre-amp servicing. ▲

There are many reasons why you should use

**QUAM**

*Adjust-a-Cone®*

**SPEAKERS**

but it all comes down to this...


- Adjust-a-Cone® Suspension
- U-Shaped Pot
- Heavier Magnetic Structures
- Factory packaged
- Universal Mounting Brackets
- Baked Aluminum Finish
- Listed in Counterfacts and Photofacts

ask for QUAM, the quality line,  
for all your speaker needs

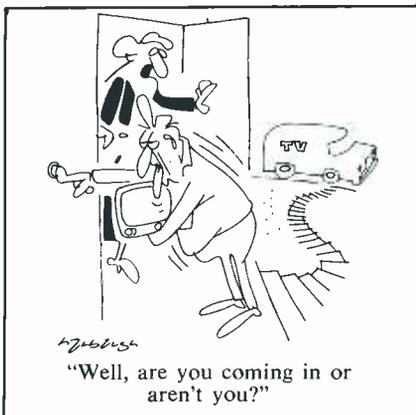**QUAM-NICHOLS CO.**

234D East Marquette  
Chicago 37, Illinois

Your customer  
can hear  
the Quality  
that is built  
into every  
Quam Speaker



## Bench Servicing

(Continued from page 29)  
snagged or pinched during installation. Runners on both sides (Fig. 3) normally serve to protect the under-chassis components from being struck or scraped by the rear sill of the cabinet while the chassis is being removed or replaced.

Electrically, the most important lead-dress problem concerns the CRT cathode lead. This long wire, which conveys a signal from a conventional high-impedance video output circuit to the base of the picture tube, is carefully routed to avoid spurious signal pickup from the yoke leads and other sources. When the chassis is returned to the cabinet after a service job, all slack in this lead should be gathered up and tucked under the retaining clip on the right wall of the cabinet.

### Picture-Tube Replacement

One man can safely replace the CRT without separating the support assembly from the cabinet. The first step in taking apart the picture-tube housing is the removal of a small ornamental plate just under the tube

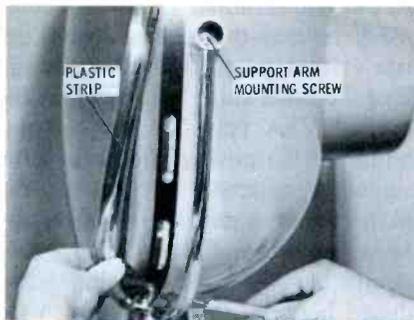


Fig. 5. To disassemble CRT housing, pry off plastic strip around its rim.

face. (Incidentally, the entire housing is designed to pivot on its base so that the picture tube can be rotated up to 45° in either direction from the straight-ahead position.) When the trim has been removed, you can pry off the strip of metalized plastic that encircles the rim of the housing. This is held in place by a tension spring at the bottom—like a dial cord spring, but larger and stronger. Your best bet is to pry the plastic strip outward and slip it off to one side, as in Fig. 5. Start near the bottom and work all the way around. The whole process is something like removing an automobile tire from a wheel.

Underneath the plastic is a metal band which grips a series of cleats on the two halves of the housing, thus fastening them together. Release the band by taking out two screws at the base; then lift off the front of the housing. To free the rear section, remove the ornamental support arm from each side as follows: Take out the screw indicated in Fig. 5, give the arm a quarter turn downward, and pull it loose. (These arms are mainly "appearance items" and seem to furnish only a minor amount of bracing.) As a final touch, remove two small screws along the bottom inside border of the housing—and there's your picture tube, like a hickory nut fresh out of the shell.

The tube is fastened to the swivel base by metal straps. Unfasten these at the sides, peel them off, and take away the tube. You'll find a small supporting cradle underneath it. This is equipped with two sturdy projecting tabs that will help you to hold the replacement tube steady while you retighten the mounting straps. To put the housing back together, follow the disassembly procedure in reverse order. ▲

## THE TOP 2 ANTENNAS TODAY FROM THE LEADER... RMS!

RMS HAS THE MOST MASSIVE, HEAVY DUTY CONSTRUCTED CONICALS DESIGNED TO WITHSTAND THE SEVEREST WEATHER!

### HURRICANE SPECIAL VFA SERIES CONICALS


- 1/2" Aluminum Elements
- Mammoth 5" x 3 1/2", 1/2" solid, 1/2 lb. Stress Proof Bakelite Insulator
- Extra Large stress Proof Reflector Bracket
- New Mast Gripping U-Bolt Assembly
- Quick-Rig Snap-Lock Design

Available stacked for additional gain

THE MAXIMUM ANTENNA FOR ALL AREAS!

### MAXIMUM CONSTRUCTION


### 1000 SERIES ANTENNAS

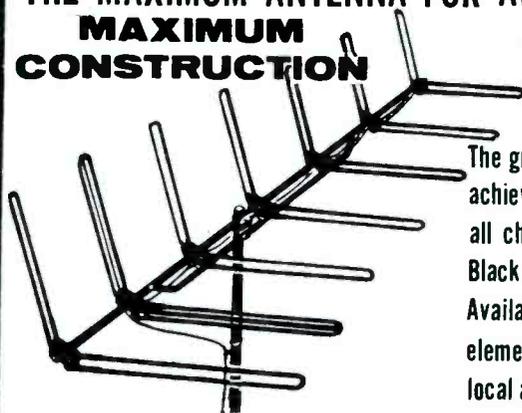

The greatest gain ever achieved for maximum all channel Color and Black and White TV. Available in 3, 5, and 7 element models for all local and fringe areas.
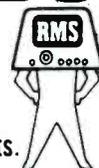
## WAVEBOOSTER

New bridged stress proof Super high impact Styrene Plastic insulators. Extra reinforced sleeved elements.



Licensed under United States Pat. Nos. 2,691,730 and 2,817,085 and 2,821,711 of Channel Master Corp.

SEE THE COMPLETE RMS LINE AT THE ELECTRONIC PARTS SHOW

CONRAD HILTON HOTEL CHICAGO MAY 18-20, 1959

• DISPLAY ROOM 657

for complete details and free catalog write to DEPT. P. F.

**Radio Merchandise Sales Inc.**  
New York 62, N. Y.

## Air Conditioning

(Continued from page 31)

ditioner load is more than 7½ amps, it is not wise—in fact, usually not permitted—to have any other outlet on the same branch circuit.

A most significant current characteristic of the induction motor is that the initial current surge is four to six times the steady or running current requirement. The line fuse used to protect the air-conditioner must, therefore, have similar delay characteristics, such as the thermal-delay type (*Fusetron* or equal).

### Servicing

It is a simple matter to check the current relay. An open coil, for example, would give no indication of continuity when checked with an ohmmeter. The relay contacts are normally open, but close when the coil is energized. A jumper placed momentarily across the relay contacts will energize the start circuit. If the compressor starts, the relay is defective. When checking the relay off the unit, orient it as originally mounted to permit gravity to act on the plunger. It is wise to replace the start capacitor when changing the relay.

If the supply voltage is proper (within ± 10% of rating); if the selector switch, the overload, and the relay are satisfactory; if the thermostat calls for cooling and if there are no breaks in the wiring, then the compressor motor should operate. If it doesn't, either the main (also called the run) winding or the start winding may be defective. Check continuity of the windings by connecting an ohmmeter across the compressor terminals. The resistance values are low—on the order

of 2 ohms for the run winding, 10 ohms for the start winding. An open or shorted start capacitor will prevent motor operation because the out-of-phase starting current is not developed. An ohmmeter test will usually provide a pretty fair indication of the capacitor's condition; direct substitution should be tried if there is any doubt.

Another defect that would keep the motor from operating is a short between the compressor shell and either winding. There must be no indication of continuity between any compressor terminal and the compressor shell. Be sure to unplug the power cord when testing for this condition.

Another possibility, although infrequent, is a stuck compressor, which in turn prevents the rotor from turning over. Such a compressor must be removed—an operation which cannot be performed in the customer's home.

The test harness shown in Fig 4 can be used to make a straightforward test for compressor operation. In putting it to use, disconnect all wires from the compressor terminals, apply *main* and *common* connections, and then—only momentarily (one or two seconds)—apply the *start* lead. Use a start capacitor having the exact value required for the motor under test. If the compressor motor is satisfactory, the power applied to the main winding will be sufficient to keep the compressor operating. We will see in the next article that the compressor may operate and yet be ineffective.

### Circuit Variations

The use of the three-terminal

NEW!

ON THE SPOT CHECK OF HORIZONTAL OUTPUT CIRCUIT!

—ends most common cause of callbacks!



**SECO HC-6 CURRENT CHECKER**

- PLACE IN CIRCUIT IN SECONDS — NO DISCONNECTING OF CATHODE
- FAST, ACCURATE WAY TO ADJUST HORIZONTAL DRIVE AND LINEARITY

This new, low-cost current checker provides a positive, on-the-spot method of checking and adjusting TV horizontal output circuits — eliminates one of the most common causes of callbacks. Can be placed in circuit in seconds — without disconnecting cathode — immediately indicates whether horizontal output tube cathode current is within manufacturer's recommended limits. Insures proper picture focus, width, and stability with minimum cathode current — helps prevent premature failure of horizontal output transformer and in some cases failure of power transformer and rectifiers. HC-6 is valuable as a fast, accurate indicating device when adjusting horizontal drive and linearity. A "must" on all TV horizontal tube, transformer, or yoke replacement jobs — may also be used to balance hi-fi audio output tubes. Compact — inexpensive — easy to use — the HC-6 is a time-saving, money-making addition to your service kit. **\$12.95** Complete, ready to use. NET

See your distributor ... or write to:

**SECO SECO MANUFACTURING CO.**  
5015 Penn. Ave. S., Mpls., Minn.



## INJECTORALL

THE NEEDLE DOES THE JOB!



**TUNER CLEANER AND LUBRICANT**

with ... INJECTOR NEEDLE

The leak-proof steel Injectorrall Needle lubricates where you need it ... you can reach hard-to-get at Wafer's without pulling Tuners apart, or even removing Chassis.

The BEST CLEANER on the market today!

**INJECTORALL CO.** Brooklyn 14, New York

SENCORE "Distributor of the Month"

WARREN RADIO CO.

The April Distributor of the Month is Warren Radio Company, Peoria, Illinois. Elmer Harding and Jim Alexander agree that "SENCORE is one of the top lines we have. Both counter men and outside salesmen have less trouble selling SENCORE than any other line."

The Terrific sales record of Warrner Radio Company, of Peoria, merits their being named "Distributor of the Month."



Save Time with SENCORE

Leading Distributors Feature SENCORE

SERVICE Instruments Corp., 121 Official Road • Addison, Ill.

"...worth their weight in gold and will do much more than you claim..."



*Ernest L. Walker*  
Ernest L. Walker TV Service  
Espanola, New Mexico



**Here's why this low cost DC POWER SUPPLY can also earn extra dollars for you . . .**

*. . . more power, less ripple to handle more jobs.*

*. . . services all these without hum: Transistor auto and portable radios, "hybrid" auto and marine radios.*

*. . . and does all this, too: Operates relays, phone circuits. Battery charging. Electroplating. Laboratory work. Other low voltage operations.*

**2 ranges:** 0-20 volts for transistor circuits; 0-16 volts for 12/6 volt tube and "hybrid" auto radios.

**0.15% ripple** up to 75 milliamperes. 0.5 ripple up to 5 amperes.

**Separate milliammeter** detects variations in transistor current.

**Separate fuse** in secondary circuit offers transistor protection.

**Patented conduction cooling** lowers cost per ampere output.

**Compare with others — see how much more Electro gives you**

**MODEL PS-2 \$49<sup>95</sup>**

at your Parts Jobber

**ALSO AVAILABLE—Model KPS-2 Kit version . . . . . \$39.95**

Send for detailed literature



**ELECTRO PRODUCTS LABORATORIES**

4501-R Ravenswood, Chicago 40  
Canada: Atlas Radio Ltd., Toronto

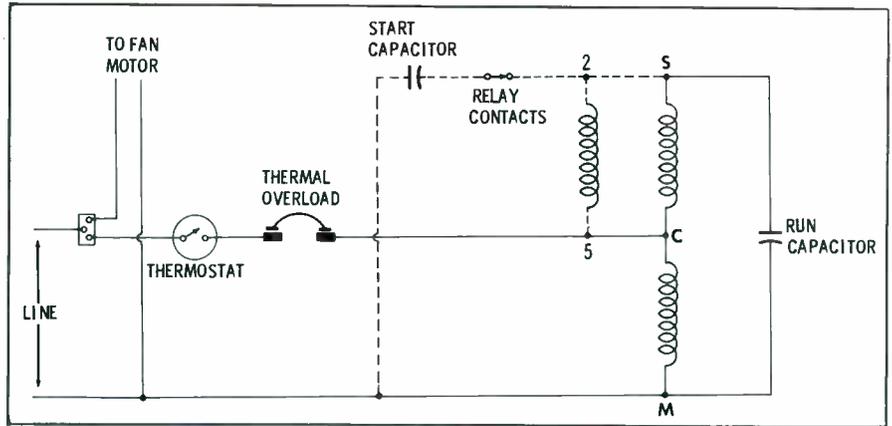


Fig. 6. Permanent split-capacitor motor does not need special start circuit.

thermal overload and a potential relay are shown in Fig. 5. Operation is as follows: The overload uses the disc contacts to protect the motor as described above. In addition, to afford extra protection for the start winding, the heater element assists in promoting disc action. Initially, the relay contacts are closed, enabling the starting components to develop the out-of-phase field for motor starting. During motor operation, an increasing voltage is induced across the closed circuit consisting of the start winding and the relay coil. At rated speed, current through the relay coil is great enough to hold the relay contacts open, effectively removing the start capacitor.

The run capacitor and the start winding are in series across the line (connected in the same manner as the start capacitor); consequently, the run capacitor aids in creating the initial starting torque. The run capacitor also improves the power factor of the air-conditioner, which means the same work is done with less current drain on the line.

Fig. 6 illustrates the use of the

PSC (permanent split-capacitor) type of compressor motor. Normally, this more recently engineered unit utilizes only the motor windings and a permanently connected external capacitor. No start capacitor or relay is necessary.

Occasionally, however, either because of manufacturing tolerances or because of lower line voltage, the PSC motor will fail to start. It will then be necessary to use the additional components shown by the broken-line circuit in Fig. 6. The air-conditioner manufacturer will recommend the necessary component values.

### Trouble Checks

1. The line voltage under load at point of use must be within  $\pm 10\%$  of rated voltage for the line fuse not to blow. Use a delay-type line fuse (*Fusetron* or equal) rated for the recommended line current.

2. If the fuse blows repeatedly, check to see if the branch circuit is not otherwise loaded excessively. Is there a short in the unit? Is start-circuit action satisfactory? Does the

**New!**

SAVE TIME with

**Model ES-102**  
ONLY \$15<sup>95</sup> DEALER NET

Load this tester for the individual capacitors. Carry it anywhere — measures only 4 3/4" H x 4 3/4" W x 2 1/4" D

SENCORE Electro-Sub

Check all ELECTROLYTIC CAPACITORS in Seconds!

Merely select the electrolytic and substitute it. 10 big electrolytics from 4 to 350 Mfd. to safely substitute in any circuit from 2 to 450 volts.

- ... COMPLETELY SAFE—no arc or spark when connecting or disconnecting.
- ... AUTOMATIC CAPACITOR DISCHARGE—within seconds after releasing test switch by unique surge protector circuit.
- ... NO CAPACITOR HEALING—surge protector circuit prevents accidental healing of capacitor being "bridged" in service work.

SENCORE SERVICE INSTRUMENTS CORP. 121 Officelot Rd. • Addison, Ill.

compressor start?


3. If voltage reaches the fan motor but the motor does not operate, check associated start and/or run capacitors; also, check for continuity of windings or a short to chassis. (Note: If capacitor is shorted, the fan will operate in either direction when started by hand.) With the power cord removed, examine for physical obstruction of fan blades. Is the shaft frozen? Does the motor need oil? Is the capacitor wired properly?

4. If the compressor is dead, is the selector switch satisfactory? Does the thermostat call for cooling? Is the overload defective? Test continuity of the windings directly, first removing all terminal wires. Use the test harness on standard compressors as previously explained. On PSC types, no start capacitor is to be used. Place the run capacitor across the main (or run) and start terminals, and apply line voltage across common and main terminals. Note: Sealed-system failures, such as defective compressors, cannot be replaced or repaired in the home.



5. If compressor operation is satisfactory, but does not start properly, the relay and/or start capacitor may be defective. These, or any other components, may be tested by the direct substitution method.

6. The run capacitor aids in starting the compressor motor and reduces the current drain of the entire unit. Where a wattmeter is available, its use will indicate that the capacitor may be defective if current drain of the unit is excessive.

In the June article, we will see how purely mechanical conditions can cause electrical trouble symptoms. The final summary will interrelate all causes and effects. ▲

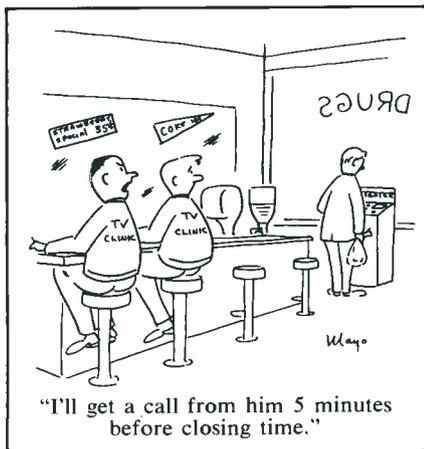

MODEL 12-C11

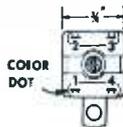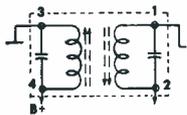

EXPORT REPRESENTATIVE:  
Roburn Agencies, Inc., N.Y. 13, N.Y.  
CANADIAN REPRESENTATIVE:  
Atlas Radio Corp., Ltd., Toronto 10, Ont.

**J. W. MILLER COMPANY**  
5917 S. Main St., Los Angeles 3, Calif.

## new MILLER 455 kc IF transformer

- an exact replacement for  
G. E. RTL-143 and RTL-163  
- at your MILLER distributor

Here's the IF transformer used in a broad line of G.E. clock and table radios—available from any Miller distributor. It comes to you complete with schematic and base layout, to speed installation. List price: \$2.30

This unit is one of many miniature IF transformers designed for replacement in "personal" radio receivers. The line includes:

| MODEL | ITEM                      |
|-------|---------------------------|
| 12-H1 | 262 KC Input I.F. Trans.  |
| 12-H2 | 262 KC Output I.F. Trans. |
| 12-C1 | 455 KC Input I.F. Trans.  |
| 12-C2 | 455 KC Output I.F. Trans. |
| 6203  | 4.5 Input or Interstage   |
| 6205  | 4.5 Ratio Detector        |

Write for the Miller general catalog, and the TV replacement guide, or get them at your distributor.

**ANOTHER HUNTER FIRST!**

**THE ATOM**

**3 NUT DRIVERS in 1**  
IN 3 POPULAR SIZES  
1/4" • 5/16" • 3/8"

**FREE!**  
32 PAGE TOOL CATALOG

**SLUG RETRIEVERS...**

**Magic-Tip SCREW HOLDING SCREWDRIVERS**

**NOW IN 14 PROVEN SIZES!**

951 ALBURTIS AVE.  
SANTA FE SPRINGS, CALIFORNIA

**SAMS PHOTOFAC INDEX**

sent direct to your shop

**FREE**

SEND FOR IT!

Yes, now you can have the valuable SAMS MASTER INDEX TO PHOTOFAC FOLDERS and Index Supplements sent direct to your shop at no cost to you! Just mail coupon below and you'll be sure to receive regularly your handy guide to the world's finest service data covering over 33,000 TV, Radio, Amplifier, Tuner Tape Recorder and Changer models. Send for it—it's FREE!

**MAIL COUPON**

**Howard W. Sams & Co., Inc.**  
2201 East 46th St., Indianapolis 6, Ind.

Put me on your mailing list to receive the Sams Photofact Master Index and Supplements

I'm a Service Technician: \_\_\_\_\_ full time; \_\_\_\_\_ part time

My Distributor is:

Shop Name: \_\_\_\_\_

Attn: \_\_\_\_\_


Address: \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

# PRODUCT report


For further information on any of the following items, circle the associated number on the Catalog & Literature Card.

## Offset-Mounted FM Antenna (No. 41C)

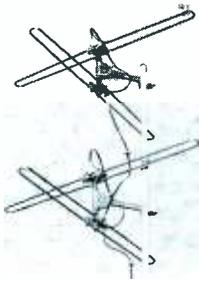

An omnidirectional "turnstile" antenna for FM radio reception, the Winegard Model FM3T, is equipped with an offset-type mounting bracket for convenient clamping to the mast of an existing TV antenna. Up to four bays can be stacked together using standard 300-ohm line. Elements are of gold-colored anodized aluminum. List price is \$11.95 per bay.

## Stereo Radio Tuner (No. 42C)

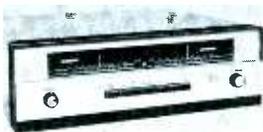

The Harman-Kardon *Madrigal* high-fidelity tuner (Model ST350) has completely separate AM and FM sections to permit stereo simulcast reception. If a multiplex adapter (MA350) is added, the unit can receive stereo signals transmitted by the Crosby multiplex method. All switches are operated by push buttons. Price is \$199.95.

## Dual-Heat Soldering Gun (No. 43C)



The latest addition to the Weller line of soldering guns is the 8200K, a dual-heat model rated at 90 and 125 watts. Features include a trigger-type switch, single spotlight, and a copper tip plated with iron for greater durability. The new gun is sold as part of a \$7.95 kit that also includes a soldering aid, a wire brush, and a spool of solder.

## Speaker Systems (No. 44C)



The new Audio Component Div. of JFD has announced a *Mardi Gras* line of high-fidelity loudspeaker systems to be marketed from distributors through service dealers. The speakers require a driving power of 5 to 15 watts and are equipped with 4-, 8-, and 16-ohm impedance taps. Two versions are available: Model ALC1 (18" x 10" x 10"; \$45 audiophile net), and Model ALC2 (14" x 10" x 10"; \$30 audiophile net).


## 12" Woofer (No. 45C)

An input of 4 watts at 16 cps produces a voice-coil excursion of 1" in the Cletron Model C-12-RW woofer. The ceramic *Indox* magnet of this 12" speaker weighs 2 lb. and has a strength of 10,000 gauss. The "flex-edge" peripheral portion of the cone is made of specially treated cloth, and the gasket ring is of a composition cork material 1/2" thick. Peak power is 35 watts, and impedance is 16 ohms.


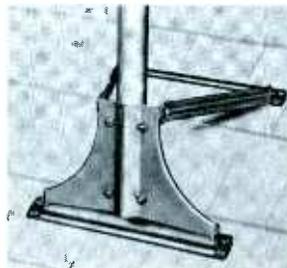
## Antenna Mount (No. 46C)

Vokar, a well-known maker of auto radio vibrators, has branched out into antenna accessories with a new *Fast Mount* steel base for roof installations. Fastened in place with self-tapping screws, it can be mounted at any convenient point on the roof — regardless of pitch. This bracket will securely hold antenna masts up to 6' tall without guy wires. List price is \$4.95.



## Tube and Transistor Tester (No. 47C)

A new portable tube tester of the dynamic mutual conductance type, Hickok Model 800, is similar to an earlier model (600A) but has several new features including circuits for leakage and gain tests of transistors and crystal diodes, a quick heater-continuity check, and improved tests for interelement leakage and grid current in tubes. Price is \$159.50.



## Stereo Channel Isolation (No. 48C)

A ground loop is created in a stereo system if the two amplifier channels have a common ground at any point and a three-wire cartridge is used. Objectionable feedback often results. The Triad A-210P, an isolation transformer with a 1:1 impedance ratio, remedies this problem when connected in series with the signal lead from the cartridge to one pre-amp. List price is \$16.50.




## Tone Arm With Cartridge (No. 49C)

The Shure *Studio Dynetic*, a combination of a moving-magnet phono cartridge and a transcription-type tone arm, is now being supplied in a stereo version priced at \$89.50. Tracking pressure is adjustable between 1 1/2 and 2 1/2 gm. Output voltage at 1000 cps is 5 mv per channel across the recommended load impedance of 50K ohms. Compliance is 8.0 x 10<sup>-6</sup> cm/dyne in both vertical and lateral directions.




**Stereo Cartridges (No. 50C)**

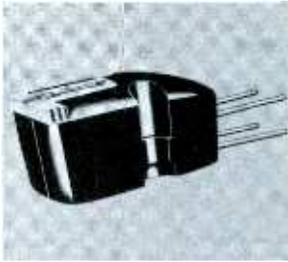

A new Pickering magnetic cartridge, the *Stanton 45X45 Stereo Fluxvalve* (Model 371) is designed for a tracking force of 3 to 6 gm. Frequency response within the stereo recording range is flat within 2 db when a load resistance of 27K to 47K ohms is used. The unit fits tone arms with 1/2" mounting centers. Price, including .7-mil diamond stylus, is \$29.85.

**Tiny Ceramic Capacitors (No. 51C)**

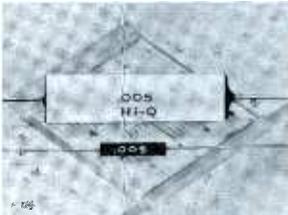

Ultra-miniaturized Aerovox *Cerafil* ceramic capacitors are available in capacitance values from 10 to 100,000 mmf at working voltages of either 30 or 100 WVDC. The photo illustrates the comparative size of one of the new units and an ordinary-sized ceramic tubular *Hi-Q* capacitor.

**Stereo Amplifier (No. 52C)**



The Arkey CS-28 incorporates dual 14-watt stereo amplifiers and a pair of control preamplifiers, all on a single chassis. A reverse-stereo switch (for interchanging channels) and a balance control are included. Output taps are provided for speaker impedance of 4, 8, 16 and 32 ohms. Price is \$64.95 (kit) or \$99.95 (wired).

**Transistorized Intercoms (No. 53C)**



1500 Series Fanon intercom systems are fully transistorized, and can be powered by either batteries or AC line current. Master stations are available with a choice of 6 or 12 connections for remote stations. A two-station, all-transistor system is also available, listing at \$74.95 including 50' of connecting cable.

**Automatic Antenna Rotator (No. 54C)**




The Alliance Model U-98 *Tenna-Rotor* is an automatic unit that shuts itself off after turning the antenna to the direction indicated on the dial. Although similar in design to an earlier automatic model (the U-83), the new rotator includes numerous new features to eliminate arcing and insure more positive action of the escapement mechanism.

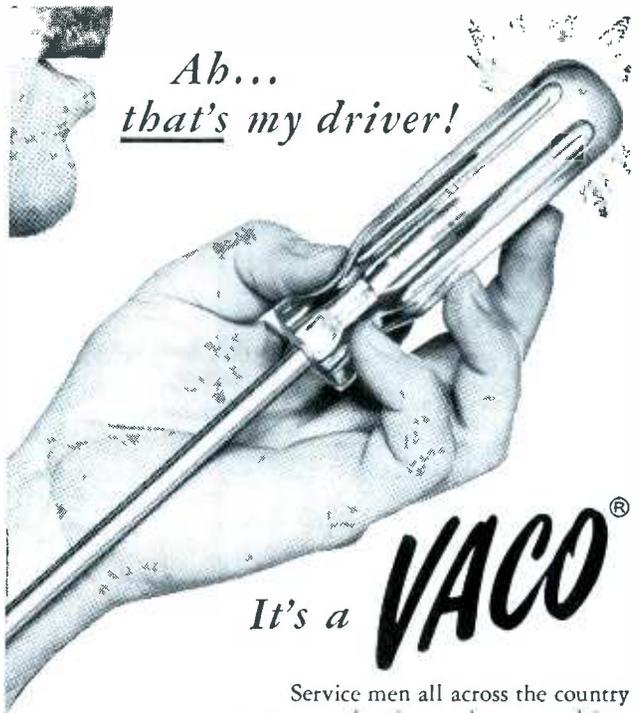**Stereo Record Changer (No. 55C)**



A built-in gauge on the United Audio *Dual-1006* four-speed stereo record changer shows stylus pressure in grams. Records of all sizes from 5" to 12" can be intermixed. Noise produced by spurious vertical stylus motion during monophonic operation is suppressed by the STEREO-MONO switch circuit.



Service men all across the country agree... there's no other screw driver or nut driver with the built-in comfort of the VACO "comfordome" handle. Makes service work easy! Enjoy the luxury grip of a VACO... the driver that gives plenty of power, yet is always kind to hands. Next time choose a VACO and *feel the difference!*

Manufactured and Unconditionally Guaranteed by  
**VACO PRODUCTS CO., 317 E. Ontario St., Chicago 11, Ill.**  
 In Canada: ATLAS RADIO CORP., Toronto 19, Ontario

**SO SAFE!**



**ARROW STAPLE GUNS** can't damage wire or cable because driving blade automatically stops staple at right height! That's why Arrow Staple Guns are proved safer on jobs all over the country. And Arrow staples have tremendous holding power because they're rosin-coated, have diverging points that lock into wood.

- T-25 (shown) for wires up to 1/4" in diameter. (Hi-Fi wire, radiant heating, bell, thermostat, telephone, inter-com, etc.) tapered striking edge gets into tight corners. Uses 3/8", 1/2", and 5/8" staples. List \$15
- T-25B For burglar alarm wiring. Drives staples flush... List \$15
- T-75 For non-metallic sheathed cable, Romex cable or any other object (such as copper tubing) up to 1/2" in diameter. Uses 3/8", 1/2", and 5/8" Arrow staples... List \$15

**ARROW FASTENER COMPANY, INC.**  
 1740 E. NEW YORK AVE., BROOKLYN 12, N. Y.

Aerovox Corp. 36  
 American Television & Radio Co. (ATR) 18  
 Ampere Electronic Corp. 40  
 Amphenol-Borg Electronic Corp. 56  
 Arkay Radio Kits, Inc. 66  
 Arrow Fastener Co., Inc. 83  
 B & K Mfg. Co. 21  
 Belden Mfg. Co. 37  
 Berns Mfg. Co. 54  
 Burgess Battery Co. 23  
 Bussmann Mfg. Co. 45  
 CBS-Hytron 19  
 Centralab, a Div. of Globe-Union, Inc. 68  
 Chemical Electronic Engineering, Inc. 70  
 Clarostat Mfg. Co., Inc. 43  
 Clear Beam Antenna Corp. 55  
 Cornell-Dubilier Electric Corp. 61  
 Delco Radio Div., General Motors Corp. 35  
 Doss Electronic Research, Inc. 32  
 Duotone Co., Inc. 51  
 EICO 65  
 E-Z-Hook Test Products 72  
 Electro Products Laboratories, Inc. 80  
 Electro-Voice, Inc. 13  
 Electronic Publishing Co. 38  
 General Cement Mfg. Co. 2nd Cover  
 General Electric Co. Electronic Components Div. 33  
 General Electric Co. Television Receiver Div. 59  
 General Instrument Distributor Div. 67  
 Hunter Tool Co. 81  
 Illinois Condenser Co. 54  
 Injectorall Co. 79  
 International Resistance Co. (IRC) 41  
 JFD Electronics Corp. 12  
 Jackson Electrical Instrument Co. 76, 84  
 Jensen Industries, Inc. 46  
 Kedman Co. 72  
 Littelfuse, Inc. 4th Cover  
 Mallory & Co., Inc., P. R. 16, 17  
 Merit Coil & Transformer Corp. 46  
 Miller Co., J. W. 81  
 Mosley Electronics, Inc. 70  
 Philco Corp.—Accessory Div. 53  
 Pickering & Co., Inc. 38  
 Planet Sales Corp. 74  
 Precision Apparatus Co. 44  
 Pyramid Electric Co. 64  
 Quam-Nichols Co. 77  
 RCA Electron Tube Div. 3rd Cover  
 Radio Merchandise Sales, Inc. 78  
 Raytheon Mfg. Co. 14, 15  
 Regency Div., I.D.E.A., Inc. 9  
 Sampson Co.—Electronic Utilities Div. 42  
 Sams & Co., Inc., Howard W. 39, 62, 81  
 Sarkes Tarzian, Inc. 52  
 Seco Mfg. Co. 38, 79  
 Service Instruments Corp. (Sencore) 52, 62, 66, 75, 79, 80  
 Sonotone Corp. 34  
 Sprague Products Co. 10  
 Sylvania Electric Products, Inc.—Semiconductor Div. 73  
 Sylvania Electric Products, Inc.—Television Rec. Div. 47  
 Technical Appliance Corp. (TACO) 72  
 Tobe Deutschmann Corp. 71  
 Triad Transformer Corp. 50  
 Triplett Electrical Instrument Co. 49  
 Tung-Sol Electric, Inc. 63  
 United Catalog Publishers, Inc. 54  
 Vaco Products Co. 83  
 Vis-U-All Products Co. 46  
 Webster Electric Co. 20  
 Wen Products, Inc. 60  
 Westinghouse Electric Co. 57  
 Xcelite, Inc. 75

ANTENNA SYSTEMS

- 1C. CLEAR BEAM — Complete information on how you can profit by stocking and selling antenna kits. See ad page 55.
- 2C. CORNELL-DUBILIER — Catalog and brochure entitled "All About Antenna Rotors." See ad page 61.
- 3C. TACO — Catalog on UHF antennas including the new Translator models. See ad page 72.

AUDIO AND HI-FI

- 4C. ARKAY—16-page booklet entitled "Let's Talk About Stereo" gives practical information about stereo, including recommended home installations. See ad page 66.
- 5C. SONOTONE—"Stereo Simplified" completely explains stereo reproduction for the layman; also, new catalog page on Ceramike, adaptable to existing tape recorder and PA systems. See ad page 34.

CAPACITORS

- 6C. ILLINOIS CONDENSER — Literature on all types of capacitors, including radio, TV, motor start, Philco flash, miniature, subminiature, military, computer, paper, audio crossover network, and tantalum. See ad page 54.
- 7C. SPRAGUE — M726 Cerami-Chart, large wall chart of standard ceramic capacitor color codes with circuit application data for various types. See ad page 10.
- 8C. TOBE DEUTSCHMANN — Capacitor catalog No. 5701. See ad page 71.

CARTRIDGES AND NEEDLES

- 9C. ELECTRO-VOICE — Bulletin No. 267 features new totally-compatible stereo cartridges. Offers two series—the Magnaromic for magnetic inputs and the standard ceramic for ceramic inputs. See ad page 13.
- 10C. GENERAL ELECTRIC — 16-page booklet entitled "Application Considerations in the Use of Stereo Cartridges." See ads pages 33, 59.
- 11C. JENSEN INDUSTRIES — 1959 cross-reference booklet on phono needles. See ad page 46.

COMPONENTS (MISC.)

- 12C. AMPEREX — Condensed catalog including a list of all company products. See ad page 40.
- 13C. CLAROSTAT — Catalog No. 59 of resistor and control products. See ad page 43.
- 14C. GENERAL CEMENT — Catalog sheet for Sav-A-Tube unit. See ad 2nd cover.
- 15C. IRC—Catalog on S505 Handy-Pak carbon composition resistors. See ad page 41.
- 16C. MALLORY — Capacitor catalog, Form No. 9-140; silicon rectifier catalog, Form No. 9-152. See ad pages 16, 17.
- 17C. J. W. MILLER—Data sheet gives schematic and base layout on IF transformer replacement for two GE models. See ad page 81.
- 18C. TRIAD — Data on new series of transformers for transistor power supplies; 6, 12, or 28 volt DC mobile supply inputs provide wide range of DC outputs. See ad page 50.
- 19C. UNITED CATALOG PUBLISHERS — List of distributors who have the 1959 edition of The Radio-Electronic MASTER, 1536-page standard parts catalog containing descriptions of over 150,000 items. See ad page 54.

FUSES

- 20C. BUSSMANN—Bulletin SFH-6 describes new space-saving fuse and fuseholder combination for circuit protection at 300 volts or less. See ad page 45.

POWER SUPPLIES

- 21C. ATR—Descriptive literature on battery eliminators, DC-AC inverters, tube protectors, and other products. See ad page 18.

SERVICE AIDS

- 22C. BERNS — Circular on the perfect pin-crimping picture-tube repair tool that eliminates hard soldering jobs. See ad page 54.
- 23C. E-Z-HOOK—Convenient reference sheet titled "How to Build the Five Most Useful Scope Probes," with schematics, mechanical component layouts, etc. See ad page 72.
- 24C. SERVICE INSTRUMENTS — Mailer describing the 10 most popular Sencore timesavers. See ads pages 52, 62, 66, 75, 79, 80.

TECHNICAL PUBLICATIONS

- 25C. CBS-HYTRON—Catalog sheet No. PA-528 describing 1959 editions of "Technician's Handbook" and "Engineer's Handbook." See ad page 19.
- 26C. PHILCO — "1959 Service Dealer Handbook" covers the business side of service and provides a day-by-day business record. See ad page 53.
- 27C. HOWARD W. SAMS—Descriptive literature on all Howard W. Sams books covering servicing of TV, radio, hi-fi, etc. Includes data on latest books, "101 Ways to Use Your Oscilloscope" and Volumes 3 and 4 of the "Hi-Fi Servicing" series. See ads pages 39, 62, 81.

TEST EQUIPMENT

- 28C. AEROVOX—Literature on Model 97 LC checker for in-circuit capacitor tests. See ad page 36.
- 29C. DOSS—Flyer describing latest troubleshooting instruments. See ad page 32.
- 30C. EICO—20-page 1959 2-color catalog describes 65 models of professional test instruments—hi-fi, and "ham" gear in both kit and factory-wired form—shows how to save 50%. See ad page 65.
- 31C. JACKSON — Catalog sheet on hi-fi, stereo, and audio test equipment. See ads pages 76, 84.
- 32C. SECO—New 2-color folder showing complete line of test equipment and service aids. See ads pages 38, 79.
- 33C. TRIPLETT—Flyer on new true dynamic mutual conductance tube tester, Model 3444. See ad page 49.

TOOLS

- 34C. HUNTER — Literature describing complete subminiature tool bar—first ever offered. See ad page 81.
- 35C. KEDMAN — Catalog sheet describing 4 screwdriver displays and specifications on 14 kinds of screwdrivers in company's line. See ad page 72.
- 36C. WELLER — Bulletin No. 017 describes new soldering kit combining dual-heat 90/125-watt gun for the tool kit with temperature-controlled 40-watt Magnastat iron for the bench.
- 37C. WEN — Free 50c 32-page booklet, "101 Ways to Use Small Electric Power Tools." See ad page 60.
- 38C. XCELITE—Latest catalog on complete line of tools for the electronic serviceman. See ad page 75.

TUBES

- 39C. TUNG-SOL — 30-page flip-style chart supplies electrical and physical characteristics for most important industrial, special-purpose and military tubes. See ad page 63.
- 40C. WESTINGHOUSE — Colorful comic book, "A Rescue Job for Tony," describing details of tube manufacturing. See ad page 57.



| MODEL 648 |                 | MODEL 115/715/561 |              |
|-----------|-----------------|-------------------|--------------|
| TUBE TYPE | FIL. D. CIRCUIT | FIL. D. CIRCUIT   | PLATE        |
| 6B85      | 6.3 A234        | 567 34YZ          | 22 2JMCR     |
| 19DE7 19  | 126 A127        | A89 65V           | 20 21LR      |
|           |                 | A45 35VW          | 30 4NR       |
| 25D4 25   | 234 6 15W       | 25.F              | 8 4S         |
| 25D7S 25  | 129 B946        | 50VW 25           | 4 10 7JKS    |
| TUBE TYPE | SEC. A.         | M. MODEL 49       | CATH. SHORTS |
| 6B85      | P 6.3 3         | 1X 256            | 7 30         |
| 19DE7     | T 19 4          | 2X 13             | 9 30         |
|           | T 19 4          | 2 67              | 8 9          |
| 25D4      | D 25 7          | - 5               | 3 4          |
| 25D7S     | P 25 4          | 6 139             | 7 5          |

Latest Chart Form 648-21, 115/715/561-11, 49-4

RCA  
pre-sells  
for you  
...with  
these  
hard  
hitting  
ads!

## How to make sure you get what you pay for in TV Picture Tubes!

If the time ever comes to replace the picture tube in your TV set, you should know these important facts:

### All Tubes Are Not New!

One out of every two replacement picture tubes sold are made of used or reconditioned parts. In fact, many rebuilt picture tubes are sold as new. Until now, you and even many TV Technicians could not tell the difference.

### RCA Takes the Guess-Work Out of It!

With RCA, you know what you're getting... and you get what you pay for. For all RCA Picture Tubes are now clearly labeled ALL-NEW or RE-BUILT—right!

## How can you be sure you're getting a brand new picture tube?

Complete For the best picture  
A picture Rebuilt factory  
Both tube card. Check virtually



Do you know that many TV picture tubes are made with reconditioned materials? Can you tell the difference between a new and a rebuilt picture tube? How can you be sure you are getting what you ask and pay for? The answer is simple! RCA now manufactures two lines of picture tubes—all-new Silverama and factory-rebuilt Monogram. Each is clearly labeled as

either new or rebuilt. Each is warranted for one full year. Each is priced accordingly. And both fit virtually every make and model TV set. All guess work is eliminated. You're sure you're getting an all-new factory-fresh TV picture tube when you ask for RCA Silverama—or the finest rebuilt picture tube made when you ask for RCA Monogram.

**All-New, Premium RCA Silverama®**  
Finest picture tube model  
Completely new, glass and all parts. For the brightest, sharpest, clearest picture your TV set can deliver!

\$49.00\*



**Factory-Rebuilt RCA Monogram**  
Finest rebuilt picture tube model  
A picture tube for the budget-minded. Reprocessed and tested in the same factory as RCA's premium picture tubes.

\$36.00\*



RADIO CORPORATION OF AMERICA Electron Tube Division, Harrison, N. J.  
\*Optional list prices for a popular 21" tube. Monogram prices slightly higher for West.




These ads are typical of the big advertising program for RCA SILVERAMA and RCA MONOGRAM Picture Tubes. You'll see these messages in TV GUIDE, LIFE, and the SATURDAY EVENING POST... on such leading TV shows as Steve Allen, Dave Garroway's Today, and Jack Paar.

Cash in! Make sure you're identified with this program. Your authorized RCA Distributor will tell you how. Contact him today!



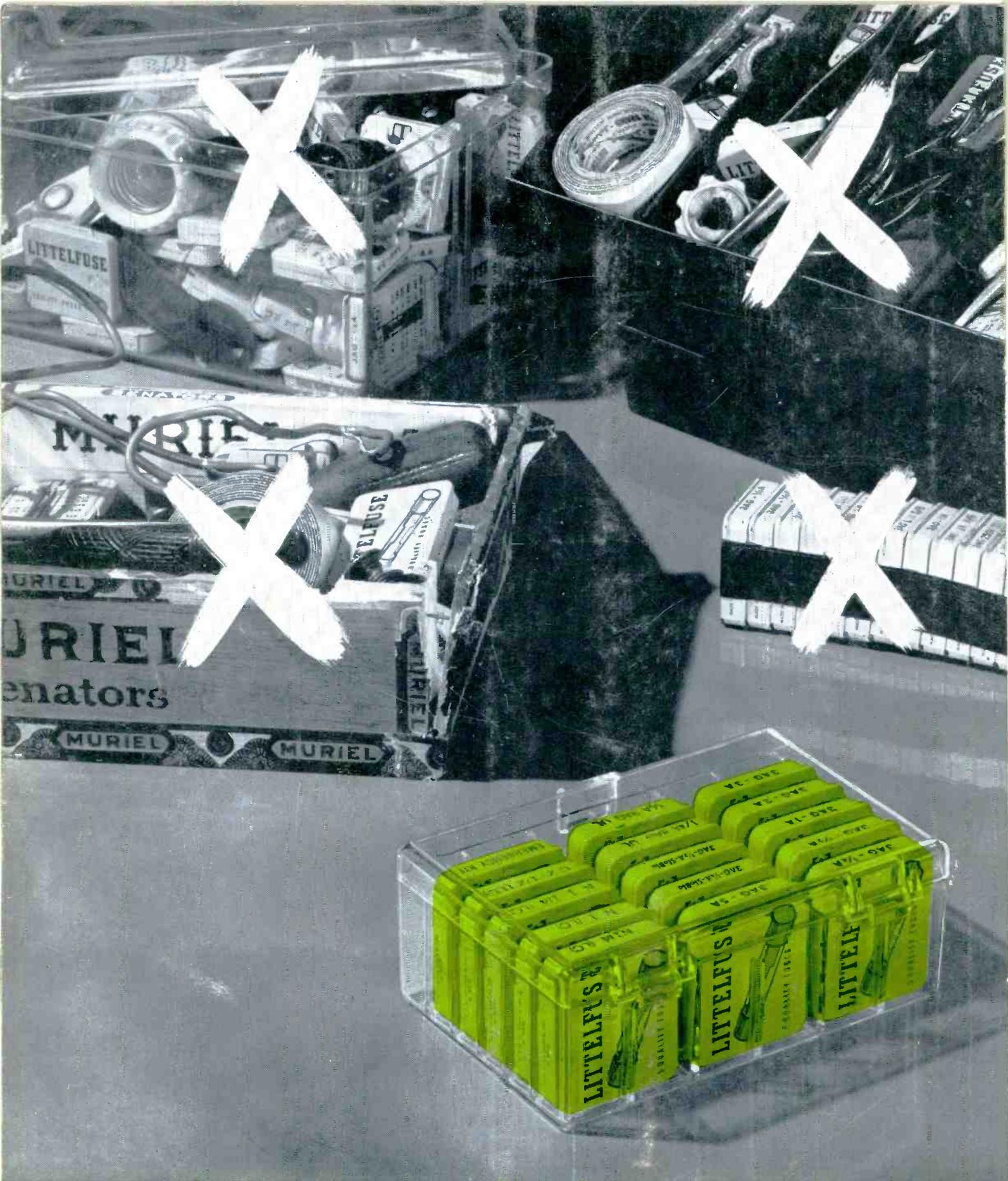**RADIO CORPORATION OF AMERICA**  
Electron Tube Division Harrison, N. J.



Burton Brown advertising

## THERE'S ONLY ONE RIGHT WAY

A *fuse caddy* for your *tube caddy*: 18 individual compartments for fingertip selection. The fuse caddy is complete with the 15 boxes of fuses required to service 93% of all TV sets. Three spare compartments are provided for additional fuses of your own selection.

**LITTELFUSE** Des Plaines, Ill.