

Radio-Electronics

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

DIGITAL WIPER DELAY

Build it and add it to your car. Provides intermittent windshield wiper operation and is programmed automatically. Turn to page 60.

AUDIO BREAKTHROUGH

New metal-particle tape for recording promises ultra-performance in the near future. For the complete story, turn to page 49.

VIDEO TANK GAME

Use your cannon to destroy your opponent first but watch out for the barriers. Construction starts on page 52.

CAPACITANCE METER


Part 2: 4-digit display reads out between 1 pF and 9999 μ F. Turn to page 67.

COVER STORY UNUSUAL TELEPHONE

Built into a stylish handset is a complete telephone and amplifier. To see how it's done, turn to page 37.

PLUS

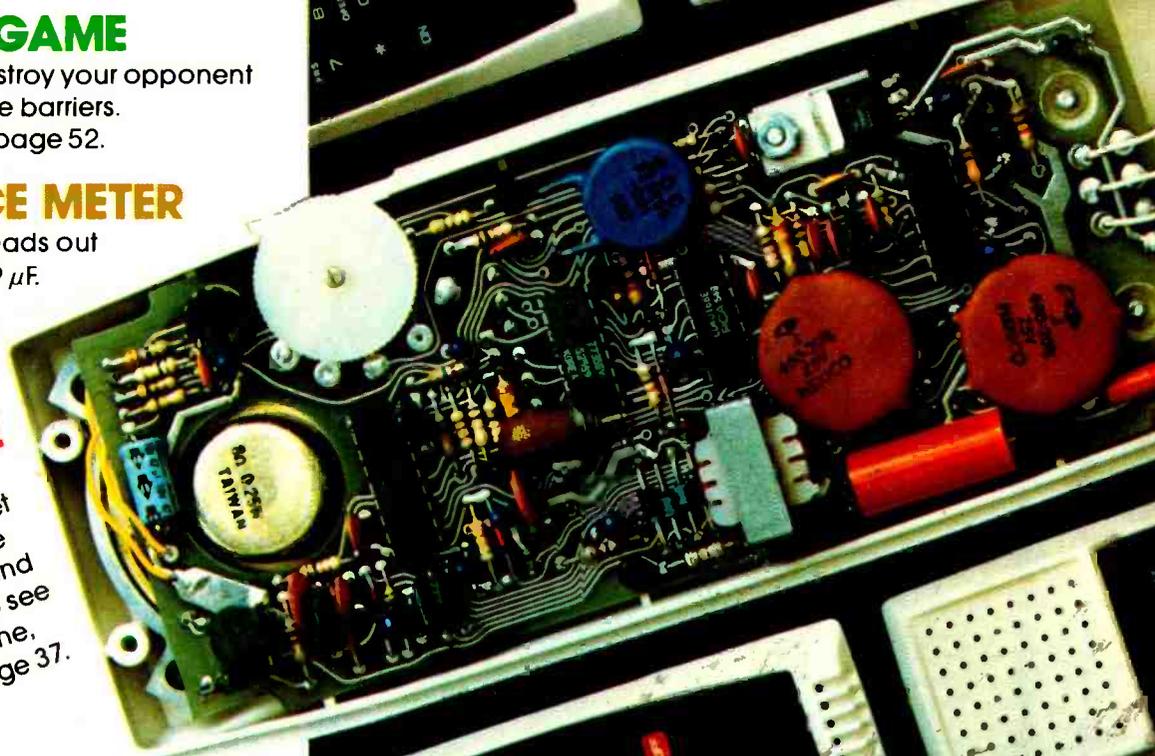- ★ Digital Crib Sheets
- ★ Computer Corner
- ★ Hobby Corner
- ★ Service Clinic



BERNSBACK



562024 OLS B005N66 14 A OCT80
 K06816012
 H. M. DELSCHLAGER
 BX 5
 NEW EGYPT
 NJ

600 MHZ. FREQUENCY COUNTER ±0.1 PPM TCXO

OPTO-8000.1



This new instrument has taken a giant step in front of the multitude of counters now available. The Opto-8000.1 boasts a combination of features and specifications not found in units costing several times its price. Accuracy of ± 0.1 PPM or better — *Guaranteed* — with a factory-adjusted, sealed TCXO (Temperature Compensated Xtal Oscillator). **Even kits require no adjustment for guaranteed accuracy!** Built-in, selectable-step attenuator, rugged and attractive, black anodized aluminum case (.090" thick aluminum) with tilt bail. 50 Ohm and 1 Megohm inputs, both with amplifier circuits for super sensitivity and both diode/overload protected. Front panel includes "Lead Zero Blanking Control" and a gate period indicator LED. AC and DC power cords with plugs included.



OPTOELECTRONICS, INC.

5821 NE 14 Avenue
Ft. Lauderdale, FL 33334
Phones: (305) 771-2050 771-2051
Phone orders accepted 6 days, until 7 p.m.



SPECIFICATIONS:

Time Base—TCXO ± 0.1 PPM GUARANTEED!
Frequency Range—10 Hz to 600 MHz
Resolution—1 Hz to 60 MHz; 10 Hz to 600 MHz
Decimal Point—Automatic
All IC's socketed (kits and factory-wired)
Display—8 digit LED
Gate Times—1 second and 1/10 second
Selectable Input Attenuation—X1, X10, X100
Input Connectors Type —BNC
Approximate Size—3" h x 7 1/2" w x 6 1/2" d
Approximate Weight—2 1/2 pounds
Cabinet—black anodized aluminum (.090" thickness)
Input Power—9-15 VDC, 115 VAC 50/60 Hz
or internal batteries
OPTO-8000.1 Factory Wired **\$299.95**
OPTO-8000.1K Kit **\$249.95**

ACCESSORIES:

Battery-Pack Option—Internal Ni-Cad Batteries and charging unit **\$19.95**
Probes: P-100—DC Probe, may also be used with scope **\$13.95**
P-101—LO-Pass Probe, very useful at audio frequencies **\$16.95**
P-102—High Impedance Probe, ideal general purpose usage **\$16.95**

VHF RF Pick-Up Antenna—Rubber Duck w/BNC #Duck-4H **\$12.50**
Right Angle BNC adapter #RA-BNC **\$ 2.95**

FC-50 — Opto-8000 Conversion Kits:

Owners of FC-50 counters with #PSL-650 Prescaler can use this kit to convert their units to the Opto-8000 style case, including most of the features.


FC-50 — Opto-8000	Kit \$59.95
*FC-50 — Opto-8000F	Factory Update \$99.95
FC-50 — Opto-8000.1 (w/TCXO)	Kit \$109.95
*FC-50 — Opto-8000.1F	Factory Update \$149.95

*Units returned for factory update must be completely assembled and operational

TERMS: Orders to U.S. and Canada, add 5% to maximum of \$10.00 per order for shipping, handling and insurance. To all other countries, add 10% of total order. Florida residents add 4% state tax. C.O.D. fee: \$1.00. Personal checks must clear before merchandise is shipped.

CIRCLE 18 ON FREE INFORMATION CARD

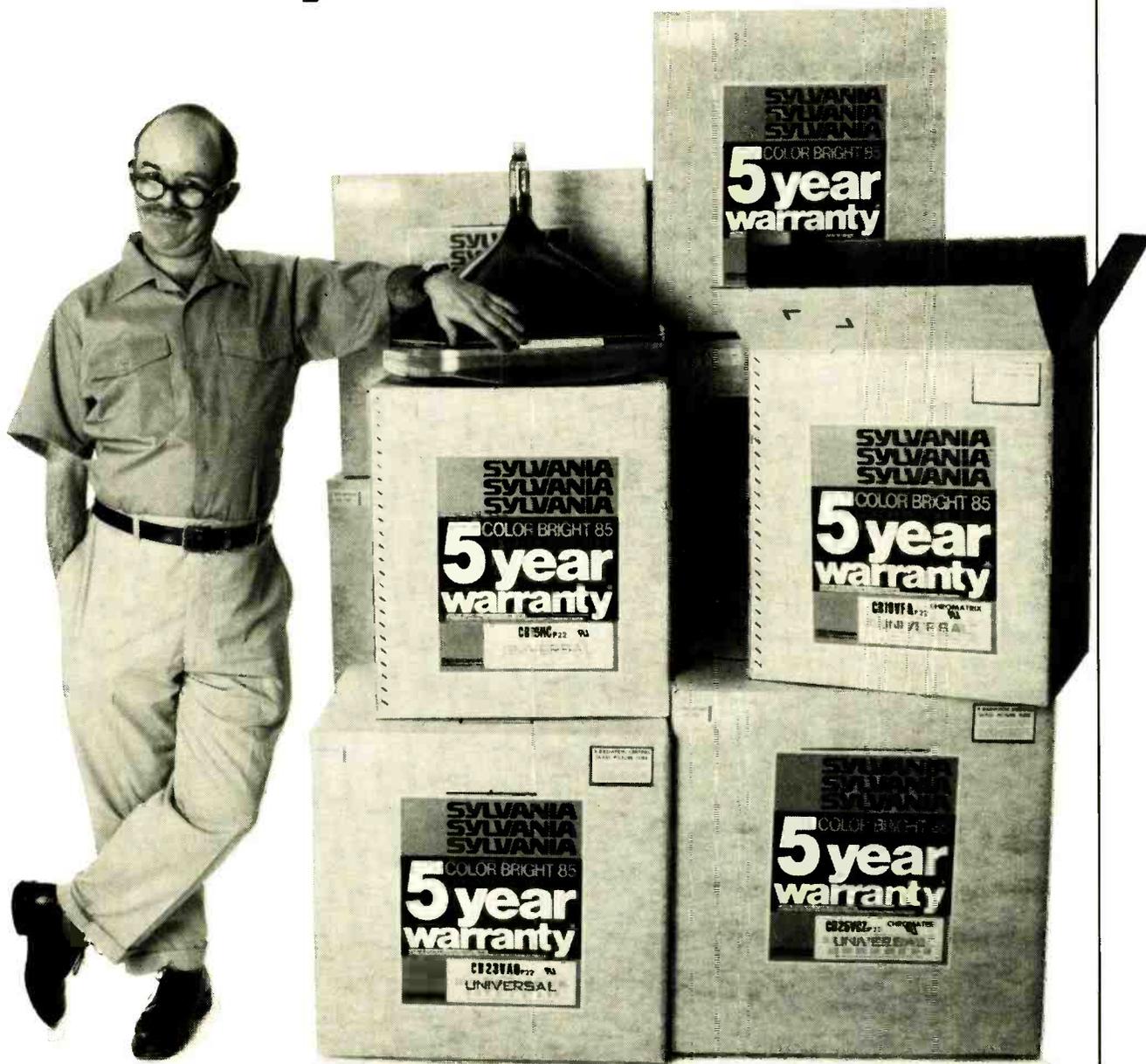Only eight TV tubes can make a warehouse out of your backroom.



*Limited warranty. Labor not included.

To offer fast replacement for 385 different TV tubes, you'd have to open a warehouse. Or, you could open eight Sylvania picture tube cartons.

Our eight Universal Color Bright tubes are designed as

direct replacements for 385 bonded safety plate picture tubes. And they're designed so well that they're offered with a five-year limited warranty.*

Call your Sylvania distributor to stock up on Color

Bright tubes. Then, you won't have to wait days for your customer's new tube to be delivered.

You can order a Color Bright for immediate delivery right from your own backroom.

SYLVANIA

CIRCLE 68 ON FREE INFORMATION CARD

Electronic
Components

GTE

We didn't have to make a better 2 track than our RS-1500. So we made a 4 track. Introducing the RS-1506.



Ingenuity is truly rare. Repeated ingenuity is true genius. Like the Technics 4-track RS-1506. It offers twice the program time of our 2-track RS-1500.

It also offers the award-winning RS-1500's "Isolated Loop" tape transport with a quartz-locked, phase-controlled, direct-drive capstan.

By isolating the tape from external influences we minimized tape tension to a constant 80 mgs. Providing extremely stable tape transport and low head wear. While reducing modulation noise and wow and flutter to a point where they are barely measurable on conventional laboratory equipment.

Electronically, too, Technics RS-1506 provides the same level of professional control as its predecessor. A separate microphone amplifier. Mixing amplifier. And separate three-position bias/equalization switches. While IC full-log function permits absolute freedom in switching modes. Also available is an optional full-feature infrared wireless remote control (RP-070). It lets you operate

all transport functions and record from up to 20 feet.

For the same performance as the RS-1506 with the convenience of auto reverse, there's the RS-1700.

Compare specifications. Even with the best 2-track decks. TRACK SYSTEM: 4-track, 2-channel recording, playback and erase. 2-track, 2-channel playback 4-head system. **FREQ. RESP.:** 30-30,000Hz, ± 3 dB (-10 dB rec. level) at 15ips. **WOW & FLUTTER:** 0.018% WRMS at 15ips. **S/N RATIO:** 57dB (NAB weighted) at 15 ips. **SEPARATION:** Greater than 50dB. **RISE TIME:** 0.7 secs. **SPEED DEVIATION:** $\pm 0.1\%$ with 1.0 or 1.5mil tape at 15ips. **SPEED FLUCT.:** 0.05% with 1.0 or 1.5mil tape at 15ips. **PITCH CONTROL:** $\pm 6\%$.

Technics 4-track RS-1506 and auto-reverse RS-1700. A rare combination of audio technology. A new standard of audio excellence.

Technics
Professional Series

CIRCLE 57 ON FREE INFORMATION CARD

Radio-Electronics®

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS
 Electronics publishers since 1908

NOVEMBER 1978 Vol. 49 No. 11

BUILD ONE OF THESE

- 52 **Tank!**
A dedicated TV battle game. Use your cannon to destroy your opponent, but watch out for the land mines.
- 60 **Automatic Wiper Delay**
Digital system for your car provides intermittent windshield wiper operation and is programmed automatically.
- 64 **2 to 200,000-Hz Function Generator**
Part 2: Build it around the latest state-of-the-art waveform generator IC.
- 67 **Digital Capacitance Meter**
Part 2: 4-digit display reads out between 1 pF and 9999 μF.
- 71 **Frequency Counter In A Probe**
Part 2: Self-contained in a probe this 6-digit counter makes a worthwhile project.

DIGITAL ELECTRONICS

- 41 **Digital Troubleshooting Is A Cinch**
A look at typical faults, troubleshooting techniques, and test equipment to speed the job.
- 45 **Digital Logic Charts**
4-pages of tear-out reference sheets that are chock full of logic circuit information.
- 77 **Circuit Ideas**
A nifty way to generate sinewaves digitally.
- 82 **Computer Corner**
How to use the 8085 with an A/D converter to monitor eight analog channels.

GENERAL ELECTRONICS

- 4 **Looking Ahead**
Tomorrow's news today.
- 14 **Guest Editorial**
Science for journalists.
- 37 **New! All-In-One Speakerphone**
Standard phone and speakerphone in a single compact ultra-modern package. Here's the circuitry and how it works.
- 80 **Hobby Corner**
Where to get parts, substituting parts and wiring prototype projects.

HI-FI STEREO

- 49 **New Breakthrough In Audio Tape**
Metal-particle tape for audio recording provides increased output level, reduced distortion, added high-frequency response and improved signal-to-noise ratio.

TELEVISION

- 78 **CET Test**
Test your knowledge. Another in this continuing series of CET practice guides.
- 84 **Jack Darr's Service Clinic**
Locating replacement parts for orphan sets.
- 84 **Service Questions**
R-E's Service Editor solves reader problems.

EQUIPMENT REPORTS


- 26 **Data Precision Model 1350 Digital Multimeter**
- 32 **Simpson Model 452 Dual-Trace Scope.**
- 34 **Radio-Shack TRS-80 Computer System**
- 36 **Electra Bearcat Model 250 Programmable Scanner**

DEPARTMENTS


- | | |
|-------------------------------------|---------------------------|
| 134 Advertising Index | 105 Market Center |
| 14 Advertising Sales Offices | 6 New & Timely |
| 98 Books | 99 New Literature |
| 94 Computer Products | 88 New Products |
| 135 Free Information Card | 96 Stereo Products |
| 16 Letters | |

ON THE COVER

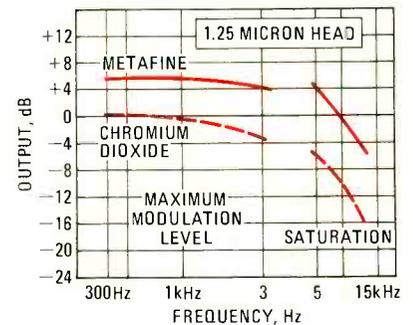That brick wall is made up of a large number of very special telephones. Take a look at the circuitry and how it works. Just turn to page 37.



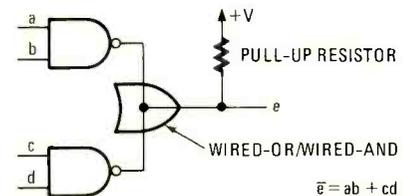NEW METAL-PARTICLE TAPE promises higher output levels with lower distortion. Story starts on page 49 and presents full details.



WIRED-OR/WIRED-AND is just one kind of digital circuit covered in digital troubleshooting story on page 41.

Radio-Electronics, Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Phone: 212-777-6400. Second-class postage paid at New York, NY and additional mailing offices. One-year subscription rate: U.S.A. and U.S. possessions, \$9.98, Canada, \$12.98. Other countries, \$14.98. Single copies \$1.25. © 1978 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

Subscription Service: Mail all subscription orders, changes, correspondence and Postmaster Notices of undelivered copies (Form 3579) to Radio-Electronics Subscription Service, Box 2520, Boulder, CO 80322.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

As a service to readers, Radio-Electronics publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, Radio-Electronics disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

Looking ahead

Projection TV: Three-tube projection TV is now in the lines of several major-brand TV manufacturers. Advent's new Model 760 has a 72-inch screen and a horizontal in-line-tube arrangement permitting a long, low projector which does added duty as a cocktail table. (Please don't spill your drinks on the electronics.) Panasonic and Quasar both have different versions of 60-inch one-piece sets—the optics are the same but electronics and furniture are different. Mitsubishi (MGA) has a two-piece 72-inch projection system and a one-piece 50-inch system. Sharp has a 72-inch two-piece system similar to Mitsubishi's. Sony has two one-piece units, with 50- and 70-inch screens, each with three tubes and two lenses. GE has the rear-view unit described in the July 1978 issue of **Radio-Electronics**. All the three-tube major-brand systems sell for more than \$3,000. The GE single-tube unit is \$2,800.

New feud? Remember hand wiring vs. printed circuits? We may be getting ready for a new RCA-vs.-Zenith dispute over set construction, but this one is much tougher to call. In introducing its 1979 color TV models, RCA quietly inaugurated a new chassis in two high-end 19-inch sets, and company spokesmen indicated that this indeed is RCA's chassis of the future. What's so special about it? Well, it's all one piece—not modular. RCA officials explain that the modular chassis has performed its function by introducing technicians to solid-state TV circuits. They said that 20% of modules returned to RCA for servicing have tested good, with no defects, and presumably the problem was in the connections. The new chassis reduces physical connections by 75% (to 30), wires from 150 to 40, hand-solder joints from 200 to 75. RCA concedes that it might cost a little more to repair the new set than its modular predecessors, but says repairs should be required less frequently.

So the very next week, what does Zenith do? Why, it introduces a brand spanking-new modular chassis, that's what. Well, the chassis has been quietly in use for some months, but now it's got a name (*Triple-Plus*). It has eight modules and low-cost Zenith-developed connectors that are claimed to compare favorably with military specs. Zenith's argument for modular: "The cost saving of the unitized chassis is not enough to give up the service advantages . . . This 100% modular chassis permits virtually 100% in-home repair."

More metal tapes: Although criticized by some competitors, 3M's introduction of its revolutionary metal-alloy audio tape (see **Radio-Electronics**, September 1978) may have established a standard of sorts. Fuji already has announced it will be next on the market with a metal tape, and company spokesmen indicated that it would be compatible with the 3M *Metafine* tape. Next to come in line has been BASF, which announced it had distributed samples to Japanese equipment manufacturers, with coercivity levels of both 950 and 1,100 oersteds. However, BASF suggested that any industry coercivity standard not exceed 1,000 oersteds. TDK also has a metal-particle tape and has provided samples to hardware manufacturers.

Videodisc boxscore: As the time draws nearer for the first U.S. consumer marketing of home videodiscs and players (at press time it was still scheduled for December or January in three or four introductory cities), more new systems are showing up. For the record, here's a summary of what has surfaced to date: **Ted**—developed by German Telefunken, British Decca and a joint subsidiary called Teldec, this mechanical system uses a flexible one-sided 8¾-inch discs which play for up to 10 minutes each. It has been marketed in Germany and Japan, is now principally used for education and training purposes. **Philips/MCA**—an optical system which will be marketed to consumers initially by Magnavox, later also by Universal-Pioneer of Japan. It uses 12-inch reflective double-sided discs. These play for up to 30 minutes-per-side and revolve at 1800 rpm while longer-playing discs (up to 60 minutes-per-side) revolve at a speed varying from 600 to 1800 rpm. The pickup never touches the disc. **RCA**—this is a capacitance needle-in-groove system that plays for up to one hour-per-side of each two-sided disc, revolving at 450 rpm. RCA hasn't yet made a commitment for marketing. **Thomson-CSF**—this French system, like Philips/MCA, is a laser-read optical system, but the discs are transparent rather than reflective. Two-sided discs are possible. Discs demonstrated have played for up to 30 minutes-per-side. The disc revolves at 1500 rpm for the PAL color system, 1800 rpm for NTSC.

A few units are being produced for demonstration and industrial-institutional uses. **MDR**—Magnetic disc recorder, originated in Germany and demonstrated in various forms, both records and plays back using an oxide-coated plastic disc. **Visc**—Mechanical system developed by Matsushita, playing 30 minutes or 60 minutes-per-side of a 12-inch disc, depending on version used, revolving at 450 rpm. Smaller seven-minute disc is the size of a 45-rpm audio disc and revolves at 720 rpm. No announced plans for commercialization. **Sony**—Reflective optical disc, laser-read, similar to the Philips/MCA development except that it revolves at 900 rpm. Provides up to one hour-per-side of two-sided 12-inch disc. No announced plans for commercialization. **JVC**—Capacitance system using ungrooved disc revolving at 900 rpm, claimed to have many advantages of optical systems but lower costs because of elimination of necessity to use laser pickup. No known plans for commercialization.

Color, China and USSR: The U.S. may be officially tilting toward China in its foreign policy, but in color TV technology it's dealing more closely with the Soviet Union. RCA, Owens-Illinois Glass and several Japanese firms have received contracts, estimated to total more than \$100 million, to provide the USSR with color tube manufacturing equipment and technology. Meanwhile, Hitachi and Toshiba are understood to have negotiated contracts with China to build a color tube plant and an IC development and manufacturing facility, respectively, with a total value of about \$245 million.


DAVID LACHENBRUCH
CONTRIBUTING EDITOR

TUNER SERVICE



CORPORATION

**SAME DAY
SERVICE**

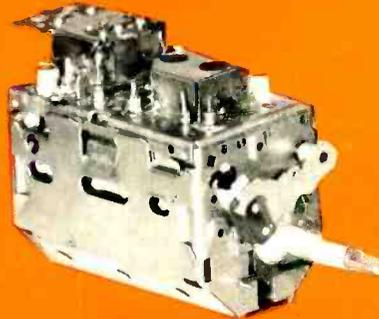

**ONE YEAR
GUARANTEE**

The Company of Independent Professionals

Better Quality — Personal Attention — Faster Service

TSC PROVIDES YOU WITH A COMPLETE
SERVICE FOR ALL YOUR TELEVISION
TUNER REQUIREMENTS




SUBSTITUNER

TUNER REPAIRS

EXACT
REPLACEMENT

UNIVERSAL
REPLACEMENT

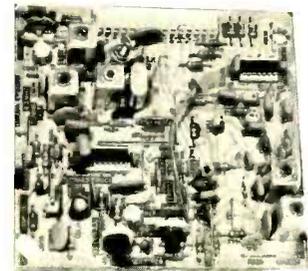

MODULES

HEADQUARTERS.....	BLOOMINGTON, INDIANA 47401.....	537 South Walnut Street.....	Tel. 812 / 334-0411
ALABAMA.....	BIRMINGHAM, ALABAMA 35212.....	5623 1st Avenue N.....	Tel. 205 / 592-9150
ARKANSAS.....	LITTLE ROCK, ARKANSAS 72204.....	4200-C Asher Avenue.....	Tel. 501 / 661-0393
CALIFORNIA.....	MODESTO, CALIF. 95351.....	123 Phoenix Avenue.....	Tel. 209 / 521-8051
	NATIONAL CITY, CALIF. 92050.....	117 East 8th Street.....	Tel. 714 / 477-8746
	NORTH HOLLYWOOD, CALIF. 91601.....	10654 Magnolia Boulevard.....	Tel. 213 / 769-2720
	SAN MATEO, CALIF. 94402.....	600 South Amphlett Boulevard.....	Tel. 415 / 348-3292
FLORIDA.....	TAMPA, FLORIDA 33606.....	1505 Cypress Street.....	Tel. 813 / 253-0324
	FT. LAUDERDALE, FLORIDA 33309.....	3516 N.W. 10th Avenue.....	Tel. 305 / 566-4882
GEORGIA.....	ATLANTA, GEORGIA 30310.....	646 Evans Street S.W.....	Tel. 404 / 758-2232
ILLINOIS.....	URBANA, ILLINOIS 61801.....	908 East Main Street.....	Tel. 217 / 384-2052
	SKOKIE, ILLINOIS 60076.....	5110 West Brown Street.....	Tel. 312 / 675-0230
INDIANA.....	INDIANAPOLIS, INDIANA 46204.....	112 West St. Clair Street.....	Tel. 317 / 632-3493
	SOUTH BEND, INDIANA 46619.....	2010 Western Avenue.....	Tel. 219 / 288-8918
KENTUCKY.....	LOUISVILLE, KENTUCKY 40217.....	#7 Dahlem Center, 826 Eastern Parkway.....	Tel. 502 / 452-1191
LOUISIANA.....	SHREVEPORT, LOUISIANA 71104.....	2423 Southern Avenue.....	Tel. 318 / 221-3027
MASSACHUSETTS.....	SPRINGFIELD, MASS. 01109.....	144 Boston Road.....	Tel. 413 / 788-8206
MISSOURI.....	ST. LOUIS, MISSOURI 63132.....	9577 Page Avenue.....	Tel. 314 / 429-0633
NEVADA.....	LAS VEGAS, NEVADA 89102.....	1114 South Casino Center Blvd.....	Tel. 702 / 384-4235
NEW JERSEY.....	TRENTON, NEW JERSEY 08638.....	1139 Pennsylvania Avenue.....	Tel. 609 / 393-0999
	JERSEY CITY, NEW JERSEY 07307.....	454 Central Avenue.....	Tel. 201 / 792-3730
NEW YORK.....	ROCHESTER, NEW YORK 14606.....	25 Howard Road.....	Tel. 716 / 647-9180
NORTH CAROLINA.....	GREENSBORO, N. CAROLINA 27405.....	2914 East Market Street.....	Tel. 919 / 273-6276
OHIO.....	CLEVELAND, OHIO 44109.....	4525 Pearl Road.....	Tel. 216 / 741-2314
OREGON.....	PORTLAND, OREGON 97210.....	1732 N.W. 25th Ave., P.O. Box 10141.....	Tel. 503 / 222-9059
PENNSYLVANIA.....	PITTSBURGH, PENNSYLVANIA 15209.....	515 Grant Avenue.....	Tel. 412 / 821-4004
TENNESSEE.....	MEMPHIS, TENNESSEE 38111.....	3158 Barron Avenue.....	Tel. 901 / 458-2355
TEXAS.....	DALLAS, TEXAS 75218.....	11540 Garland Road.....	Tel. 214 / 327-8413
CANADA.....	ST. LAURENT, QUEBEC H4N-2L7.....	305 Decarie Boulevard.....	Tel. 514 / 748-8803
	CALGARY, ALBERTA T2H-1Y3.....	P.O. Box 5823, Station "A".....	Tel. 403 / 243-0971

If you want to branch out into the TV Tuner Repair Business write to the
Bloomington Headquarters about a franchise.

CIRCLE 26 ON FREE INFORMATION CARD

www.americanradiohistory.com

Bell Labs designs communications system for the disabled

Bell Laboratories, together with the Telephone Pioneers of America (a voluntary industrial organization), has designed *Unix*, an experimental computer-based communications system for severely handicapped persons, such as cerebral palsy victims.



BELL LABS COMMUNICATIONS SYSTEM, *Unix*, contains a large keyboard with recessed keys that can be used by severely handicapped persons. Here a cerebral-palsied child uses a cap pointer to type a message on the keyboard.

The *Unix* system uses a special oversized keyboard coupled to a computer that is connected to a TV set and a page printer. The keys are large recessed pushbuttons that can be pressed either by a finger or by a pointer attached to a cap worn by the user that is controlled by head motion. Pressing the buttons with the pointer causes the "typed" message to appear immediately on the screen; two other push-buttons can be pressed for a copy of the message.

For simplicity and to reduce the amount of typing to a minimum, abbreviations are used for words, word endings and phrases. For example, "GH" stands for "I want to go home," and "gb" means "goodbye." A standard list of abbreviations has been preprogrammed by Bell, and instructions for adding more abbreviations are being developed.

The *Unix* system is designed so that up to three persons can share it; it also lets the computer perform store, retrieve, process and control tasks simultaneously.

Best record of 1978 receive audio awards

The 1978 Audio Excellence Record Awards were recently presented by Audio-Technica U.S., Inc., for discs in three categories: classical music, rock/pop and special-interest recordings.


The winner in the classical music category is a British recording of Tchaikovsky's Six Symphonies and Manfred performed

by the London Philharmonic conducted by Mstislav Rostropovich (EMI ELS 5099) and produced by David Mottley. For rock/pop, the top record was Steely Dan's "Aja," produced by Gary Katz (ABC AA 1006). In the special-disc category, the award was given to a direct-to-disc recording by Harry James and His Big Band, produced by Doug Sax and Lincoln Mayorga (Sheffield Lab 6).

TI's quarter-million-bit magnetic bubble memory due in late '78

Some time in the last quarter of 1978, TI will release its new quarter-million-bit magnetic bubble memory IC, the TIB0303, with a family of interface and control circuits available in 1979.

The bubble IC is composed of a gadolinium-gallium garnet substrate on top of which is superimposed a layer of magnetic epitaxial film. Permalloy metal patterns placed on the film determine the way the 3-micron-diameter bubble domains move when they are exposed to a rotating magnetic field, provided by two orthogonal coils. When the magnetic field rotates, the bubble domains move under the permalloy patterns similar to shift registers.

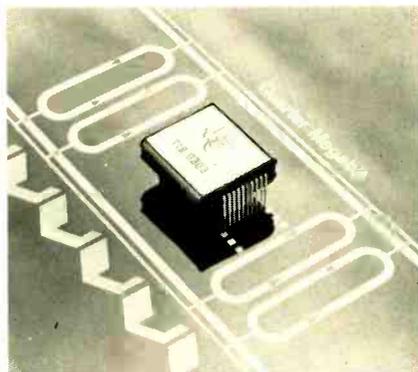

TI'S MAGNETIC BUBBLE MEMORY is a quarter-million-bit device. The advantages of bubble memory technology include storage density and nonvolatile characteristics.

The TIB0303 has a 7.2-ms average access time (for the first bit of the 224-bit page), a 0.9-watt power consumption, a read-data rate of 100K bits-per-second, and an operating temperature of 0° to 50°C. It comes in a 20-pin dual-in-line package and measures 1.2 × 1.2 × 0.4 inches; the package includes the IC, the magnetic coils, a permanent magnet set and magnetic shielding, and costs \$500.


Connecticut to receive first off-track betting/entertainment center

By the fall of 1979, New Haven, CT, will be the site of Teletrack, the very first off-track betting and entertainment center in a

theatre environment. The center will use a closed-circuit TV system to provide betting customers with on-track events and pad-dock activities as they occur.

Teletrack was developed by General Instrument Corporation, manufacturer of electronic systems and components, and built by AmTote, a subsidiary of the company, as part of the state's off-track betting system. Microwave transmissions will bring the track events into the betting center, where they will be displayed on giant 24-foot by 32-foot screens, as well as on strategically placed monitor screens. Customers will place their bets through TIM 300 ticket-issuing machines, insuring the efficiency of the betting operations.

TV MODULE SERVICING AIDS

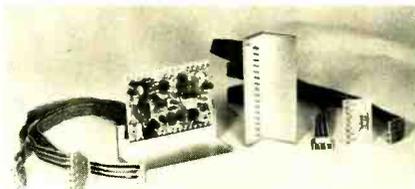

GTE-SYLVANIA CHEK-A-BOARD CABLE kits make it possible for technicians to service solid-state TV sets without removing the chassis. The *Chek-A-Board* kits, designed for use with RCA and Zenith modular sets, contain cables with female connectors on one end for modules, and mating chassis connectors on the other end. The two-foot cables, composed of stranded multilead ribbon wire, feature plated-alloy conductors on acrylic plastic PC boards. The side of each cable bears a different color for ease in orientation.

1978 mid-year VTR sales to dealers exceed 1977 figures

According to the Marketing Services Department of EIA, total U.S. market sales of home videotape recorders to dealers increased in June 1978, and showed an upward trend in the first six months of the year—in contrast to sales for a similar period in 1977. During the first 26 weeks of 1978 VTR sales to dealers amounted to 142,490 units and the June VTR sales came to 31,339.

Fotomat offers new film-to-videotape service

Fotomat Corporation is now offering a special service at all its 3400 stores in the U.S.: it will transfer your film and/or slide photography to a videotape cassette.

How it works is this: You take your film (either 8-mm or Super 8-mm) and/or 35-mm or 126-mm color slides to your Fotomat dealer who will transfer the material to either 1/2-inch Beta or VHS-format videotape. All you have to do is inform Fotomat what type of VTR you own so that the correct cassette format can be chosen.

continued on page 12

Now NRI makes it TV/Audio home

Side-by-side equipment comparison of NRI and two other leading schools shows what you get for what you pay. When you have to pay as much as \$985 more for another school's course, you should carefully consider your tuition investment.

When you sit down and try to pick out the school that's best for you, it gets

to be a problem. Catalogs are radically different and some are not too clear as to what you actually get for your money. So NRI has done a lot of the work for you. And put the prices right up front so you can make your own judgment.

Of course, we can't compare everything. Lesson clarity and content vary. What one covers here, another covers there...or not at all. The material one school breaks down into eight lessons may be four at another. And the qualifications and abilities of instructors are another question.

One Million Students, Over 60 Years' Experience

So we can only tell you what NRI has to offer. We've been in education since 1914, starting as a radio school six years before commercial broadcasting was even on the scene. Since then, we've kept right up with the times, improving techniques, adding material, creating new courses to help people improve their skills and income.


Early on, we learned to keep our lessons compact...thoroughly covering a subject, but not so much that students would be overwhelmed. We call them "bite-size" lessons because they're easy to digest.

Learn by Doing with "Hands-on" Training

And, we pioneered the concept of "hands-on" training. NRI goes far beyond theory and textbooks to give our students actual bench experience and prepare them for the realities of electronic servicing. Every piece of equipment in our Master Course in TV and Audio Servicing is designed for learning. As you assemble the kits we supply, you build a highest-quality, up-to-date 25" (diagonal) color TV, a 4-channel amplifier and tuner with speakers, your own oscilloscope,

	NRI	SCHOOL A	SCHOOL B
COURSE TITLE	Master Course in TV, Audio, and Video System Servicing	Master Course in Color TV Servicing	Electronics Technology and Advanced Troubleshooting I & II
CASH PRICE (terms available)	\$1295	\$1539	\$2280
TV SET	NRI designed-for-learning kit. Dual speaker 25" (diagonal) color TV with cabinet	Heathkit GR-2001 25" (diagonal) color TV (cabinet extra)	Zenith model G4020W 19" (diagonal) color TV (fully assembled)
OSCILLOSCOPE	NRI designed-for-learning kit. 5" (8 x 10 cm) triggered sweep	Heathkit IO-4541 5" (8 x 10 cm) triggered sweep (not given until after graduation)	Heathkit IO-4541 5" (8 x 10 cm) triggered sweep
COLOR BAR GENERATOR	NRI designed-for-learning kit. 10 patterns	Elenco SG-200 (kit) 10 patterns	Elenco SG-200 (fully assembled) 10 patterns
FREQUENCY COUNTER	NRI designed-for-learning kit. Complimentary metal oxide semiconductor digital type		
METER	NRI designed-for-learning kit. Transistorized AC/DC volt-ohm meter	Heathkit (part of TV kit) DC only; 1K Ohm/volt	Private label multimeter
AUDIO	NRI designed-for-learning kit. Four-channel high-fidelity AM/FM tuner with speakers	Private label pocket transistor AM radio kit and AM-FM-SW solid-state portable radio kit	
TRAINER	NRI Discovery Lab	Breadboard	Experimental Electronics Lab
MISCELLANEOUS EQUIPMENT		EICO Digital Logic Probe	

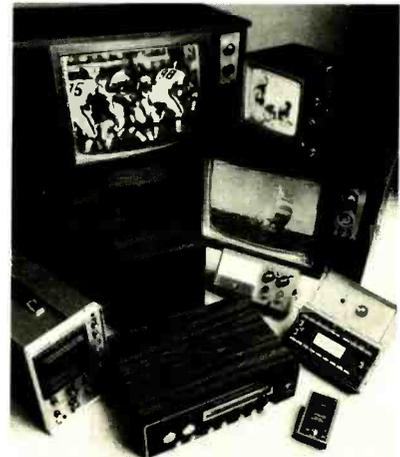All data as shown in each school's catalog as of September 1, 1978.



Learn as you build with "hands-on" training.

easy to compare study courses.

digital frequency counter, and other instruments you'll use in your course, use later to earn good money as a TV/ Audio technician.

The point is, none of this equipment is hobby-kit or commercial assembly line units with lessons "retro-fitted" to what was at hand. NRI has designed each so you get invaluable training and experience you just can't get any other way. As you build, you study operation of circuitry, see how sections interact, perform "power-on" experiments only possible with NRI. This total training is exclusive with NRI...no other school, home study or resident, offers it.

Instructors Who Know Their Business

NRI instructors are thoroughly qualified, with both technical and educational experience. Most of them helped develop NRI courses, lessons, and equipment, so they really know what they're talking about. They're interested in their students, always ready to help with a question, a problem...give good advice to help you reach your goals.

It's instructors and training like this that have made NRI the choice of professional TV servicemen who have taken home study courses. As a national survey shows (summary on request), they recommend NRI by a majority of three to one over any other school.

So how does NRI give you all this and still cost so little? We keep costs down by designing our own training kits, eliminating the middleman's profit on hobby kits or commercial units. And by offering our training by mail only. We have no sales force, no commissions to pay. You make up your mind in your own time, without pressure, let the facts speak for themselves. We pass these savings on to you in the form of lower tuitions, more equipment, carefully designed courses and effective lessons.

Send for Free Catalog, No Salesman Will Call

Send for our free catalog today and get all the details. See every piece of equipment and kit you get...a complete listing of fully described lessons...explanations of each and every experiment you perform. Read about NRI's background and qualifications...career opportunities...what NRI graduates say about their training...costs and monthly payment plans for the courses that interest you. Then compare NRI value and results and make your decision. Like the million that have gone before you, we think you'll choose NRI. Send the card today.



Build and keep 2-meter transceiver, test equipment for a communications career.


Or check out NRI value-training in Computer or Communications/CB Equipment Servicing.

If you're interested in learning how to service and maintain digital computers, check out our NRI course. You learn at home, in your spare time, and actually build a programmable, integrated circuit, digital computer with expanded memory. Or maybe your interest is CB or the expanding world of communications...mobile radio, microwave,

TV broadcasting, and much more. NRI can help you there, too, as you build and experiment with your own digitally synthesized 2-meter transceiver. For these and other NRI home study courses, just check the postage-paid card and mail today. If card is missing, write to:



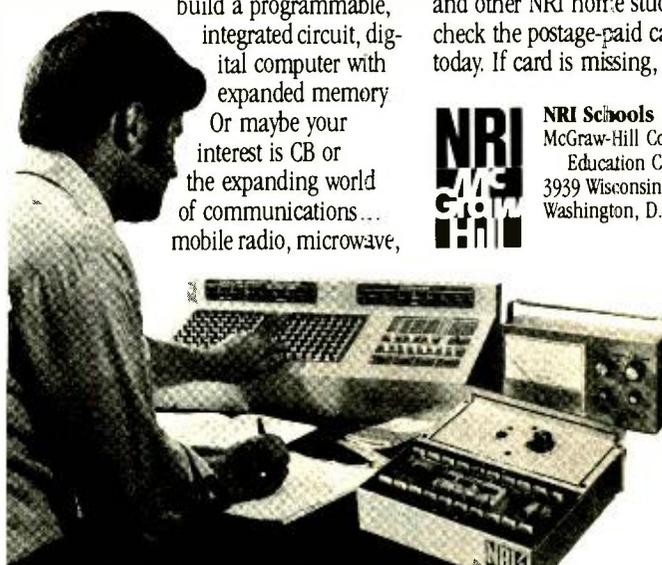NRI Schools
McGraw-Hill Continuing
Education Center
3939 Wisconsin Avenue
Washington, D.C. 20016



new & timely

continued from page 6

It is expected that this new service will benefit most those with an enormous backlog of already developed but rarely viewed movies and slides, as well as in the development and creation of new film and slide libraries. Sound narration or music to accompany a previously transferred movie or slide can be added by merely plugging in a mike or an audio input into the jack on the front of a VTR. In addition to home applications, Fotomat also sees possible future use for the new service in business, medical and educational fields.

The videotape cassette offered in Fotomat stores as an adjunct to the new service will cost the same as those presently being offered in the Fotomat drive-in stores. The cost of transferring a 400-foot roll of Super 8-mm film, plus the videotape cassette, is \$14.95 (for the 1-hour format).

NESDA/ISCET INSPECTS AND RATES RCA CHASSIS



In Las Vegas recently, a NESDA/ISCET inspection team looked over and rated three RCA TV chassis: the CT 92A, CTC 93D and CTC 88AC. The CT 92A was rated as "good," and the CTC 93D and CTC 88AC were each given an "excellent." The inspection forms used were developed by the serviceability committee from information supplied by manufacturers and from the service industry. Shown from left to right are CET members Don Winchel, Dean Mock, Jack Lang, R. E. Eddy, Hal Robbins, Frank Grabiec (ISCET vice-chairman) and Edward Burroughs.

NRBA approves proposed law to deregulate radio

The National Radio Broadcasters Association (NRBA) has approved proposed new legislation to deregulate the radio industry. The Communications Act (HR 13015) has as one of its primary objectives the release of radio from government restrictions. While not all the Act's proposals received the NRBA blessing, the association believes it will insure the continued growth and diversity of the radio industry in a competitive free marketplace, and that this will best serve the public interest. It is hoped that there will be enough input to the subcommittee from industry representatives and private individuals that the pro-

posed legislation will be passed, or at the very least that appropriate amendments will be made to the Communications Act of 1934.

Service-profits rise revealed by retail association survey


The National Association of Retail Dealers of America (NARDA) has published a cost-of-doing-business Survey that reveals that in 1977 service operations showed a 5.8% net profit (as against total sales) plus a 4.7% after-taxes profit.

Referring to a 9.5% increase in overall sales, John Gooley, manager of the NARDA service division, cautioned that "it should be kept in mind that the increase is among actual participants in the survey," and adds that the service industry volume may have declined due to a corresponding decline in the incidence of failure (in equipment). Labor income, however, was greater than parts income—the result of the gross margin on labor income being greater than that on parts. The Survey also indicates that inventories continued to rise during 1977, with 18.5% more inventory on hand at the end of the year than at the beginning.

The figures listed in the Survey are all percentages, making it possible to compare them with data from earlier years. The Survey costs \$25 (\$10 to NARDA members), and can be obtained from NARDA, 2 North Riverside Plaza, Chicago, IL 60606.

Programmable VCR provides up to 4-hour recording capability

RCA has designed a programmable video cassette recorder, the *SelectaVision 400* (model VCT400), that can be preprogrammed to record up to four TV shows simultaneously on different channels over a seven-day period. The unit is microprocessor-based, has a varactor tuner and two switch-selectable speeds: the long play setting provides a four-hour-per-cassette recording time; the standard play setting

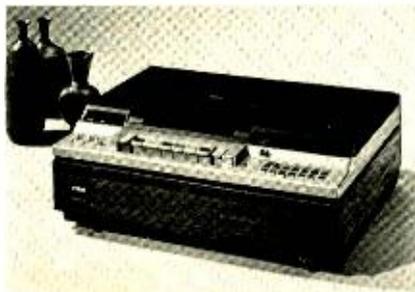

PROGRAMMABLE VCR can be preprogrammed to record up to four TV programs on different channels over a seven day period. In addition, the RCA VCT-400 has a 14-channel varactor tuner and a program indexing feature that lets you find the starting point of a recorded program.

provides a two-hour-per-cassette recording time.

To preset the VCR to record up to a full week's programs in advance, all that's needed is to store into memory the day, time, length and channel of the program you want taped. Other features include an electronic indexing capability, tape counter with memory switch, remote pause control, a tracking control (to correct distortions) and 14 channel selector switches that receive all UHF/VHF channels in any desired sequence. The *SelectaVision 400* carries a suggested retail price of \$1275.

IHF installs hi-fi systems in the White House

The Institute of High Fidelity, Inc. (IHF) was instrumental in selecting and assembling two complete high-fidelity systems for the White House—one for the President's living quarters, the other for the White House solarium.

Leonard Feldman, IHF technical director, selected the components and accessories from a list of IHF member companies whose names, in turn, had been drawn by Chip Carter.

Mr. Feldman said that the IHF intent in selecting the individual components for both systems was that they be representative of typical hi-fi equipment enjoyed by American families. The 14 manufacturers chosen to supply the White House are U.S. Pioneer, JVC America, Shure, Kenwood, Koss Corporation, Altec, Sony, Jensen Sound Labs, TDK Electronics, Sansui, B.I.C./Avnet, Pickering & Company, TEAC Corporation of America, and Maxell. The Institute also has the responsibility of reviewing the systems and replacing the components with new, more technologically up-to-date units as the need warrants.

TI awarded Japanese patent for miniature calculator

In August 1978, over the objections of several Japanese calculator companies, the Japanese Patent Office issued a patent to Texas Instruments covering the manufacture of practically all minicalculators incorporating their circuitry in a single IC. The Japanese patent is based on U.S. patent 3,819,921 originally filed in 1967 and granted TI in 1974.

The calculator described in the 1967 patent was the first to provide the computational capability of larger machines. The heart of the TI minicalculator was an integrated circuit that performed four basic arithmetic functions. It measured 4¼ × 6½ × 1¼ inches, and featured a small 18-pushbutton keyboard and a thermal printer to display up to 12 digits.

Nineteen other countries to date have issued patents to TI for manufacturing minicalculators. R-E

BEARCAT® SCANNERS ANNOUNCE AMERICA'S ONLY 50-CHANNEL, MICRO PROCESSOR CONTROLLED SCANNER. IT SEARCHES, STORES, REMEMBERS AND ALL BUT THINKS FOR YOU.

The new *Bearcat* 250. An unbelievable advancement in no-crystal scanning.

Bearcat's new, 250 is fully synthesized for punch-in programming. It searches, stores, and recalls every bit of programming, on a vast, 50-channel spectrum. Automatically. Unbelievable? Read and believe.



CRYSTAL-LESS.

Micro processor controlled. Brings in every local frequency, automatically, without a crystal.

50 CHANNELS. Scans up to 50 channels in banks of 10 each. Scans any combination of banks at the touch of a button.

SEARCH/STORE. Seeks out and stores up to 64 active local public service frequencies automatically.

SEARCH/RECALL. Retrieves stored frequencies for simple entry into scan program.

PRIORITY CHANNEL. Samples a designated priority frequency on channel 1 every two seconds.

DIGITAL CLOCK. A genuine, LED quartz crystal digital clock. Shows hours, minutes, seconds.

5-BAND COVERAGE. Low, high, UHF, UHF-T. Plus 2 meter amateur ham band, and other UHF frequencies.

COUNT. Transmissions on each frequency counted automatically to determine which are most active.

SCAN/SEARCH LOCKOUT. A unique feature. Not only locks out channels while scanning, it also eliminates unwanted frequencies while searching.

AND MUCH MORE!

Selective Scan Delay. Direct Channel Selection. Scan Speed Control. Automatic Squelch. Track Tuning Circuitry. Front-Mounted Speaker. Decimal Display. Quality Construction. AC/DC. UL listed. FCC Certified.

THE INCREDIBLE, NEW BEARCAT® 250 SCANNER.

LEADING THE WAY TO REAL EXCITEMENT.

Copyright 1978. Masco Corporation of Indiana.

CIRCLE 36 ON FREE INFORMATION CARD

www.americanradiohistory.com

guest editorial

SCIENCE FOR JOURNALISTS

Journalism students often explain their choice of profession by saying that they want to write. One caustic observer noted that this statement is tantamount to a medical student wanting to study surgery so that he can operate.

The point is that the surgeon's goal is not to cut but to cure. Likewise, the aim of the journalist should not be to "write" but rather to communicate. And there is much evidence that journalists are not communicating well.

The reason, according to some experts, is that journalism graduates today simply are not well educated. Whether dealing with history, economics, government, or science, they often demonstrate a poor grasp of principles, confusion over issues, or an inability to weigh the significance of events.

Science, in particular, gets apathetic coverage by the press. Shortly after NASA placed a probe on the surface of Mars, a poll by the *Indianapolis News* indicated that its readers regarded the event as one of the top ten news stories of the year. Surprisingly, a poll of the editors of that newspaper failed to place the Mars landing on the list. Editors subordinated this outstanding achievement to such events as a Korean border conflict and the outbreak of Legionnaires disease.

Other cases demonstrate befuddlement of technical concepts, sometimes with an amusing twist. When the roof of the Hartford Civic Center collapsed last winter, *Newsweek* magazine reported that the structure had been "designed by a computer." A perceptive reader noted that a statement such as that could appear only in an article written by a typewriter.

Even some of the most respected periodicals downplay important technical aspects of a story. When Chrysler introduced its Omni and Horizon automobiles, the event was covered extensively in *The Wall Street Journal*. The report dwelt at length on the price of the cars and their competitive posture with respect to other compact automobiles. Only in the last sentence did it mention what is perhaps the most significant facet of the introduction—that the cars are the first U.S. built compacts with front-wheel drive.

All of this would amount to mere nit-picking if it were not for a worrisome aspect. The public, which relies heavily on the consumer press for information, is increasingly asked to support political decisions on technical matters ranging from the energy crisis to the neutron bomb. Journalists who are either confused by or indifferent to technology can hardly be counted on to provide meaningful information.

We don't have a ready solution to the problem. But it is encouraging to note that one liberal arts college has recently required its students to take courses in mathematics. The purpose, according to the college provost, "is to emphasize quantitative and logical ways of thinking."

Perhaps that avenue, or some other form of "science-appreciation" curriculum, should also be considered by journalism schools.

RON KHOL
Managing Editor
Machine Design

Reprinted from *MACHINE DESIGN*, July 6, 1978.
Copyright, 1978, by Penton/IPC, Inc., Cleveland, Ohio.

Radio-Electronics®

Hugo Gernsback (1884-1967) founder
M. Harvey Gernsback, editor-in-chief and publisher
Larry Steckler, KTX-3644, CET, editor
Arthur Kleiman, KTZ-3288, managing editor
Robert F. Scott, CET, W2PWG, KXX-8533, technical editor
Sonia Greenbaum, copy editor
Jack Darr, CET service editor
Leonard Feldman, contributing high-fidelity editor
Karl Savon, semiconductor editor
David Lachenbruch, contributing editor
Earl "Doc" Savage, K4SDS, hobby editor
Vincent P. Cicenja, production manager
Ellen Celnik, production assistant
Harriet I. Matysko, circulation director
Sheila Wertling, circulation assistant
Arline R. Bailey, advertising coordinator

Cover design by Louis G. Rubsamen
Cover photo by Mel Small

Radio Electronics is a member of the *Institute of High Fidelity* and is indexed in *Applied Science & Technology Index* and *Readers Guide to Periodical Literature*.

Gernsback Publications, Inc.
200 Park Ave. S., New York, NY 10003
(212) 777-6400
President: M. Harvey Gernsback
Vice President: Larry Steckler
Treasurer: Carol A. Gernsback
Secretary: Bertina Baer

ADVERTISING SALES

Paul McGinnis
Director of Marketing

EAST

Stanley Levitan
Radio-Electronics
200 Park Ave. South
New York, NY 10003
(212) 777-6400

MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen
The Ralph Bergen Co.
540 Frontage Road—Suite 361-A
Northfield, Illinois 60093
(312) 446-1444

PACIFIC COAST

Mountain States
Jay Eisenberg
J.E. Publishers Representative Co.,
8732 Sunset Blvd.,
4th Floor,
Los Angeles, CA 90069
(213) 659-3810
Sales Mart Building
1485 Bayshore Blvd., Box 140
San Francisco, CA 94124
(415) 467-0125

SOUTHEAST

J.E. Publishers Representative Co.,
214-387-2424



How to listen to Moscow, Russia... Moscow, Idaho and your good buddy, Max Moscow.



Panasonic introduces the Command Series.™

Tune in. Sit back. And travel the world with Panasonic's short wave radios—the Command Series. Set your itinerary by simply setting the dial. Stop off in London for a concert with the London Philharmonic. Be in Peking when they announce the new pecking order. Or visit old friends in the old country. Any old country. Even the good ol' U.S.A.

There are thousands of overseas and domestic short wave transmissions* you can tune in. And with an optional outside antenna, you'll get incredible accuracy with the RF-2800 (shown above). Because Panasonic's LED Digital Frequency Display is so precise, it's accurate to within 1 kHz. That's the kind of tuning that used to cost twice the price. That was up until the Panasonic RF-2800.



And if you want to hear more than short wave, the RF-2800 gives you more. Like SSB (single sideband) amateur radio. All 40 CB channels. Ship to shore. Even Morse communications. And, of course there's AM and FM.

And like more expensive short wave receivers, the RF-2800 has an RF-Gain Control to enhance weak, distant stations or to prevent overload distortion from overstrong stations.

The Command Series from Panasonic. Now you can travel the world without ever leaving home.

*Short wave reception will vary with weather conditions, operator's geographic location and other factors.

Panasonic
just slightly ahead of our time.

CIRCLE 16 ON FREE INFORMATION CARD

letters

CRYSTAL OSCILLATOR PROJECT

The Hobby Corner article in the July 1978 issue states it is often desirable to change the frequency coverage of a receiver with a converter, the main part of which is a crystal oscillator.

The next paragraph is disappointing in that it does not explain how to use the oscillator to change receiver frequency, or a typical converter circuit.

I found the remainder of the article very clear and interesting. Was a paragraph left out; does R-E plan a follow-up article; could you send instructions on using the oscillator to change receiver frequency?

H. WOODS
Brentwood, NY

No, a paragraph was not omitted. There was no intention to go into further detail on frequency converters at that time.

Often the topic of a Hobby Corner column is some basic circuit that has many uses. In such cases, it is quite impossible to delve into all the possible applications.

Only a limited number can be discussed in the space available. Other uses can only be mentioned in passing.

It is our hope that readers will be stimulated to look further into circuit applications. I am indeed glad that the converter idea aroused your interest. Perhaps in the future such applications can be discussed in Hobby Corner, but I am sure you will not want to wait that long.

So that you can follow up on your interest, here are a couple of references:

ARRL Radio Amateur's Handbook, and Solid State Design for the Radio Amateur, published by the American Radio Relay League, Newington, CT 06111. Each publication has sections on frequency converters plus a great deal more. You can probably obtain them from the publishers or from the public library.

EARL "DOC" SAVAGE

TRS-80 PROGRAM ERROR

Congratulations to your typesetter for being so accurate in exactly copying my

TRS-80 Investment Evaluation Program listing (August 1978 issue). He even copied an error I made in the manuscript I sent you! In line 170, instead of the PRINT statement (P.) at the beginning of the line, it should be INPUT (IN.). It must have been another typesetter that misspelled my name in the byline.

FRED BLECHMAN


COSMAC NEWSLETTER

Readers of **Radio-Electronics** may be interested to know that a new RCA COSMAC 1802 computer newsletter has been published by Quest Electronics, entitled *Questdata*. Owners of Elf, Super Elf, Elf II, COSMAC VIP, COSMAC Development System or Homebrew 1802 systems will find programs, applications and experiments supporting their RCA 1802 COSMAC. The newsletter will feature complete instruction sets; how to set up programs for graphics, control, games, and business applications; plus sections on Tiny BASIC, Elf expansion possibilities, light pens, reader

ATTACH GROUND-STRAP



PLACE INSERTER OVER I.C.

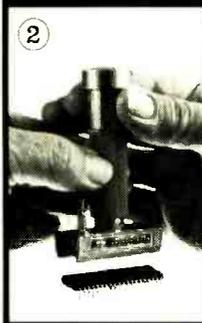

LOCK INSERTER



IC INSERTION TOOL 36-40 PIN CMOS-SAFE

Unique new insertion tool. Also aligns bent-out pins. A twist of the handle compresses the pins to proper .600 inch spacing and locks the IC into the tool. Then simply place the tool on the socket and depress the plunger for instant and accurate insertion. Features heavy chrome plating throughout for reliable static dissipation. Includes terminal lug for attachment of ground strap.


\$795
EACH

MINIMUM BILLING \$25.00 ADD SHIPPING CHARGE \$1.00
NEW YORK STATE RESIDENTS ADD APPLICABLE TAX




OK MACHINE & TOOL CORPORATION
3455 CONNER ST., BRONX, N.Y. 10475 U.S.A.
TELEX 125091


INSERT I.C.

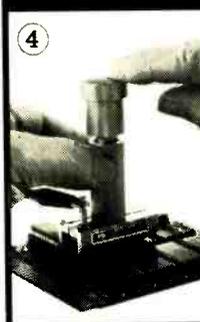

REMOVE INSERTER

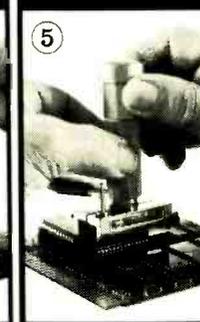

"LOADED" P.C. BOARD

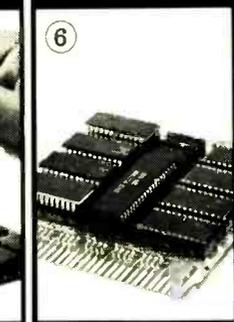

questions and music programs. The subscription cost is \$12; foreign subscriptions are \$18 (to cover postage). Write *Questdata*, P.O. Box 4430, Santa Clara, CA 95054.
BILL HASLACHER
 Editor
Santa Clara, CA

DeFOREST NOT EDISON

I've been a reader since the early Thirties when I subscribed to *Radio-Craft*.

You pulled a boo-boo in your September issue. In the article on "Pioneers in Radio," you show a picture of Lee DeForest holding the audion tube which, because of the added *grid* to the diode, started radio broadcasting. And he is not even mentioned in the article—you named him Thomas Alva Edison!

JOE BERO
Newark, DE

Boo-boo is right! The picture on page 46 of the September issue indeed shows Lee DeForest and not Thomas Alva Edison. The editorial staff of Radio-Electronics extends their deepest apology for this most unfortunate and careless error—Editor.

HOME COMPUTERS

You've done it again! First, you want to know where all the designers have gone (June 1978 editorial); now you want to know where the home computers are coming from (August 1978 editorial).

It seems that pretty much for the 20 years I've been working with computers, the computer has been a solution looking for a problem.

But, suppose the computer has utility as a home appliance, where will that utility emerge? Let me suggest the three E's: Entertainment, Education and Economics. (A fourth E, Environment, can be identified separately or included under the Economics category.)

Using home computers in entertainment and education applications should be self-explanatory. By economics, I mean supporting the household as an economic unit. This leads to a peculiar wrinkle: the value of a computer as an education and economics instrument only makes sense to households that are already pretty self-reliant in those areas. It is foolish, I agree, to expect a family to use a computer for things that no one's already eager to do. Given existing motivation, the computer operates as an amplifying device. But you can't amplify what isn't there.

With that viewpoint, I can see a market for the home computer but certainly not one comparable to that for, say, color television. Even by sneaking a computer into the house for entertainment purposes, a way of opening up the other possibilities, I don't see how that market can be substantially increased. We need another 15-20 years.

I do not believe that the foreseeable home computer market is inconsequential. I do believe that present computer systems are inadequate, with no immediate solution to compatibility and software problems. The *convenience* of computing just isn't there yet. The purchaser also need strong protection from obsolescence. System upgrading instead of replacement seems indispensable.


continued on page 22

JUST \$495 GETS YOU THIS DUAL TRACE GOULD SCOPE PLUS TWO X10 PROBES.

You know that's a great price. Especially when you consider the outstanding performance you get with this Gould OS245A oscilloscope.

And you get clear, bright displays. 5mV/div. sensitivity and exceptionally versatile trigger performance. It's ideal for TV or general electronic service work; perfect for hobbyists and educational institutions. You can rely on Gould to live up to these specs:

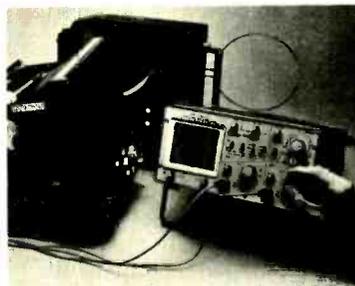- DC to 10 MHz; dual trace
- Trigger performance in excess of 15 MHz
- TV trigger facilitates solid synchronization with TV signals



- Portable; weighs just 11 lbs.
- Carries full two year warranty on all parts and labor excluding normal calibration, fuses and minor maintenance.


Just one phone call gets you action.

Don't miss out on this bargain. Pick up the phone now and call us toll-free at 800-325-6400. (In Missouri call 800-342-6600). We'll rush you free literature and ordering information on the OS245A as well as other Gould oscilloscopes applicable to your needs. Gould Inc., Instrument Systems Division, 3631 Perkins Avenue, Cleveland, Ohio 44114.



CIRCLE 83 ON FREE INFORMATION CARD

You gotta shop around.

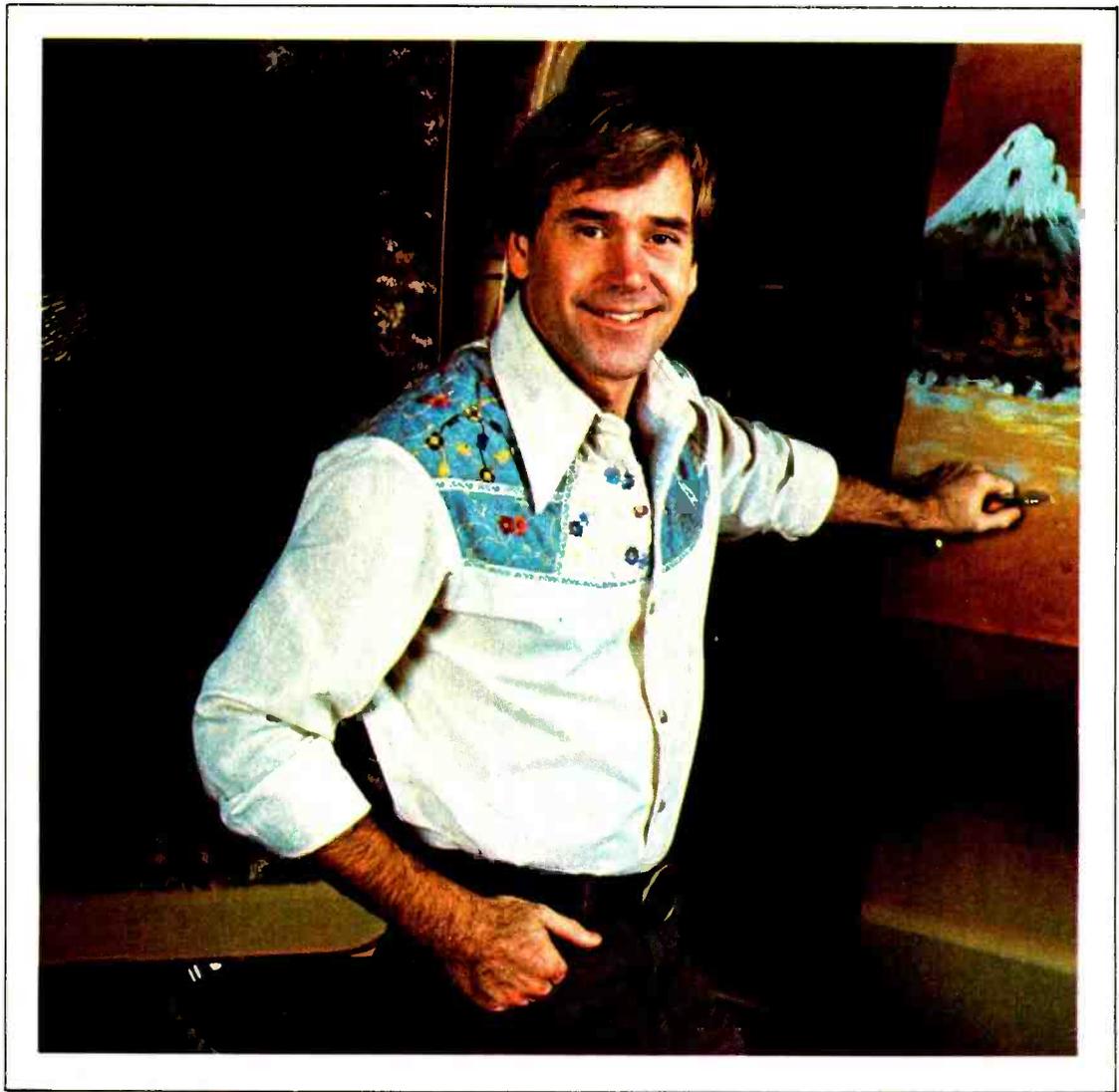

**When you do, you'll probably pick CIE.
You can't afford to settle for
less when it comes to something like
electronics training that could
affect your whole life.**

When you shop around for tires, you look for a bargain. After all, if it's the same brand, better price — why not save money?

Education's different. There's no such thing as "same brand." No two schools are alike. And, once you've made your choice, the training you get stays with you for the rest of your life.

So, shop around for your training. Not for the bargain. For the best. Thorough, professional training to help give you pride and confidence.

* * *

If you talked to some of our graduates, chances are you'd find a lot of them shopped around for their training. They pretty much knew what was available. And they picked CIE as number one.

Why you should shop around yourself.

We hope you'll shop around. Because, frankly, CIE isn't for everyone.

There are other options for the hobbyist. If you're the ambitious type — with serious career goals in electronics — take a close look at what we've planned for you at CIE.

What you should look for first.

Part of what makes electronics so interesting is it's based on scientific discoveries — on ideas! So the first thing to look for is a program that starts with ideas and builds on them!

That's what happens with CIE's Auto-Programmed® Lessons. Each lesson takes one or two principles and helps you master them — before you start using them!

How practical is the training?

This is the next big important question. After all, your career will be built on what you can do — and on how well you do it.

Here are ways some of CIE's troubleshooting programs help you get your "hands-on" training...

With CIE's Experimental Electronics Laboratory...




you learn and review the basics — perform dozens of experiments. Plus, you use a 3-in-1 precision Multimeter to learn testing, checking, analyzing!



When you build your own 5 MHz Triggered-Sweep, Solid-State Oscilloscope you take your first real professional step. You use it as a doctor uses an X-ray machine — to "read" waveform patterns... lock them in... study, understand and interpret them!

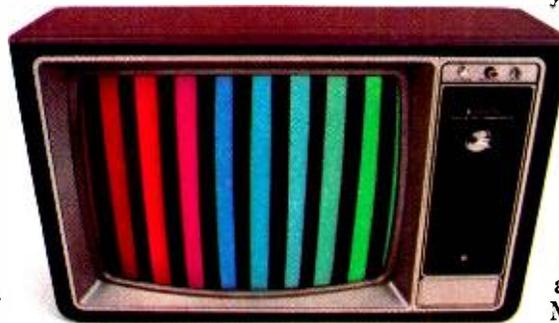When you get your Zenith 19-inch Diagonal Solid-State Color TV you



Pattern simulated.

apply your new skills to some real on-the-job-type troubleshooting! You learn to trace signal flow... locate malfunctions... restore perfect operating standards — just as with any sophisticated electronics equipment!



When you work with a completely Solid-State Color Bar Generator — actually a TV signal transmitter — you study up to ten different patterns on your TV screen... explore digital logic circuits... observe the action of a crystal-controlled oscillator!

Of course, CIE offers a more advanced training program, too. But the main point is

simply this:

All this training takes effort. But you'll enjoy it. And it's a real plus for a troubleshooting career!

Do you prepare for your FCC License?

Avoid regrets later. Check this out before you enroll in any program.

For some troubleshooting jobs, you must have your FCC License. For others, employers often consider it a mark in your favor. Either way, it's government-certified proof of specific knowledge and skills!

More than half of CIE's courses prepare you for the government-administered FCC License exam. In continuing surveys, nearly 4 out of 5 CIE graduates who take the exam get their Licenses!

Shop around... but send for CIE's free school catalog first!

Mail the card. If it's gone, cut out and mail the coupon. If you prefer to write, mention the name and date of this magazine. We'll send you a copy of CIE's FREE school catalog — plus a complete package of independent home study information! For your convenience, we'll try to have a representative contact you to answer your questions. Mail the card or coupon — or write: CIE, 1776 East 17th St., Cleveland, OH 44114.

CIE Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114
Accredited Member National Home Study Council

YES... I'm shopping around for the **right** kind of career training in electronics troubleshooting — and CIE sounds well worth looking into. Please send me my FREE CIE school catalog — including details about troubleshooting courses — plus my FREE package of home study information! **RE-48**

Print Name _____

Address _____ Apt. _____

City _____

State _____ Zip _____

Age _____ Phone _____
(area code)

Check box for G. I. Bill information:
 Veteran Active Duty

Mail today!

LETTERS

continued from page 17

That these problems can be solved is practically an article of faith among computer buffs. Whether these problems will be resolved, and when, remains to be seen. I hardly dare suggest that it will take more than five years, although it's hard to see how it might happen sooner.

In the meantime, digital processing will cover the Earth in microprocessor chips and a few of our neighbors will become BASIC freaks.

DENNIS E. HAMILTON
System Design Consultant
Penfield, NY

Your editorial certainly hit the mark. I, too, see little use for a home computer. Even as one of the people who helped start the spread of hobby computers, I don't expect to have one at home doing book-keeping, inventory or burglar alarming.

The home computer can be used to teach programming and have fun with, but my wife can keep track of the foods we need better than a computer. Who expects a housewife to "key-in" each item she uses just so she can have a computer-output shopping list? It's easier to keep this information in your head.

Simple controllers can be used to manage energy use, air conditioning, swimming pool heating, etc. Home computers just aren't needed.

This all reminds me of the tunnel diode, which was touted as the answer to many, many electronic problems. It's still the answer, it's just that no one has any questions.

JONATHAN A. TITUS
Tychon, Inc.
Blacksburg, VA

WHERE ARE THE ELECTRONIC DESIGNERS?

In your June 1978 editorial, you speak of design as if hooking up IC's is not design. Where do you draw the line? Any new device is designed (even if you modify your Heathkit). You may be an expert in capacitors but not know how to use them to couple IF stages. You may understand the quantum mechanics of PN junctions but not how to build a good FM tuner. We are all extremely specialized . . . some persons are good at designing corporate organizations, though ignorant of the skills and knowledge of those they organize.

The advent of IC's has lightened the burden for us all, and, yes, it has allowed some of us to design with devices we do not understand fully. How many engineers who use a calculator could design one (or even a slide rule)? The history of technical progress is marked with mechanisms that allow the designer to move to higher levels without worrying about details and trivia.

Yes, making a device smaller and less expensive is not the same as making a novel device. However, remember that the cost and performance of devices has traditionally been more important than their novelty. For instance, who would have bought a TV set in 1950 when the cost was so high? Mass production and production engineering are important fields. Design is where you find it and the injection of human energy with a foundation of education more often than not comprises the creation of things that are new, different, cheaper, etc.

One final word on the state of electronics: There are few colleges or universities which can keep faculty that is knowledgeable about the latest advances in such a fast-moving field as electronics. As you'd expect, the persons who have the latest information are out making a lot of money using that knowledge. Most of the latest data comes to us via the media (such as **Radio-Electronics**). It is an important service that you render and a contribution to technical progress.

DION L. JOHNSON
Santa Cruz, CA

SHOT-PUT EXPERIMENT

Were W. Cochran and **Radio-Electronics** promoting a religious revival in the June 1978 issue (see "Free Energy," Letters, p. 22)? None of the laws I ever alluded to can be found in my Bible.

Also, where did we come by this lossless spring and who needs it? If you place a shot-put on top of a helical car spring and push down on the shot-put until there is 600 lb of tension in the spring, the shot will receive much more kinetic, potential and heat energy when released than any heat loss in the spring. Caution: Do not attempt this experiment indoors unless you have a very high ceiling.

JOHN ECKLIN
Alexandria, VA

R-E

How To Be Sure You're Getting The REAL THING

That trademark tells you you're getting the ORIGINAL. The real thing. The tongue-'n-groover with smooth working, machined, undercut mating parts (1) that can't slip. The one with the reinforcing flange (2) that practically eliminates stress breakage. First of its kind and still best of its kind. Be sure you get the genuine CHANNELLOCK. Look for the trademark on the handle. Sizes from midget 4 1/2" to giant 16".

CHANNELLOCK, INC. • Meadville, Pa. 16335

CHAN NEL LOCK

The ORIGINAL Tongue-'N-Groover


Send For Our Free Catalog

An Extraordinary Offer to introduce you to the benefits of Membership in

ELECTRONICS BOOK CLUB

take any **4** of these 22 unique electronics books (values to \$65⁸⁰) for only **49¢** each

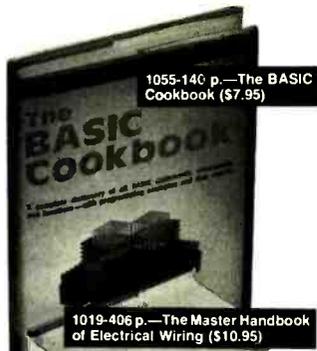with a Trial Membership in the Book Club that guarantees to save you 25% to 75% on a wide selection of electronics books



1055-140 p.—The BASIC Cookbook (\$7.95)




1019-406 p.—The Master Handbook of Electrical Wiring (\$10.95)



BUILD YOUR OWN WORKING ROBOT
BY ROY L. HEISLERMAN
841-238 p.—Build Your Own Working Robot (\$8.95)



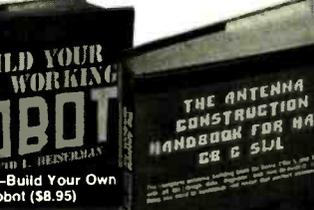1011-270 p.—How to Repair Movie & Slide Projectors (\$12.95)



1054-238 p.—The Antenna Construction Handbook for Ham, CB & SWL (\$9.95)



101-416 p.—Electronic Circuit Design Handbook (\$17.95)



1070-406 p.—Interfacing with an Analog World (\$12.95)



1260-308 p.—303 Dynamic Electronic Circuits (\$9.95)



678-276 p.—Modern Communications Switching Systems (\$17.95)



811-280 p.—The Complete Handbook of Videocassette Recorders (\$9.95)



1028-270 p.—How to Repair Video Games (\$9.95)




1088-322 p.—Illustrated Dictionary of Microcomputer Terminology (\$12.95)



1864-336 p.—How to Design, Build, & Test Complete Speaker Systems (\$10.95)



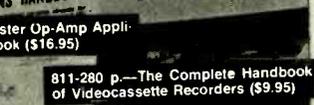
856-476 p.—Master Op-Amp Applications Handbook (\$16.95)



919-434 p.—Color TV Troubleshooting Factbook (\$9.95)



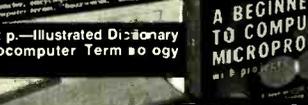966-272 p.—The Complete Handbook of Public Address Sound Systems (\$10.95)



1015-328 p.—A Beginner's Guide to Computers & Microprocessors (\$5.95)



800-602 p.—Master Handbook of 1001 Practical Electronic Circuits (\$12.95)



300-420 p.—Dictionary of Electronics (\$18.95)



929-322 p.—Solid-State Motor Controls (\$12.95)



1023-148 p.—A Beginner's Guide to Designing & Building Transistor Radios (\$7.95)



874-392 p.—Master Handbook of Digital Logic Applications (\$12.95)

May we send you your choice of 4 of these practical time-and-money-saving books as part of an unusual offer of a Trial Membership in Electronics Book Club?

Here are quality hardbound volumes, each especially designed to help you increase your know-how, earning power, and enjoyment of electronics. Whatever your interest in electronics, you'll find Electronics Book Club offers practical, quality books that you can put to immediate use and benefit.

This extraordinary offer is intended to prove to you through your own experience, that these very real advantages can be yours...that it is possible to keep up with the literature published in your areas of interest, and to save substantially while so doing. As part of your Trial Membership, you need purchase as few as four books during the coming 12 months. You would probably buy at least this many anyway, without the substantial savings offered through Club Membership.

To start your Membership on these attractive terms, simply fill out and mail the coupon today. You will receive the 4 books of your choice for 10-day inspection. YOU NEED SEND NO MONEY. If you're not delighted, return the books within 10 days and your Trial Membership will be cancelled without cost or obligation.

ELECTRONICS BOOK CLUB, Blue Ridge Summit, Pa. 17214

Facts About Club Membership

- The 4 introductory books of your choice carry publisher's retail prices of up to \$65.80. They are yours for only 49¢ each (plus postage/handling) with your Trial Membership.
- You will receive the Club News, describing the current Selection, Alternates and other books, every 4 weeks (13 x a year).
- If you want the Selection, do nothing; it will be sent to you automatically. If you do not wish to receive the Selection, or if you want to order one of the many Alternates offered, you simply give instructions on the reply form (and in the envelope) provided, and return it to us by the date specified. This date allows you at least 10 days in which to return the form. If, because of late mail delivery, you do not have 10 days to make a decision and so receive an unwanted Selection, you may return it at Club expense.
- To complete your Trial Membership, you need buy only four additional monthly Selections or Alternates during the next 12 months. You may cancel your Membership anytime after you purchase these four books.
- All books—including the Introductory Offer—are fully returnable after 10 days if you're not completely satisfied.
- All books are offered at low Member prices, plus a small postage and handling charge.
- Continuing Bonus: If you continue after this Trial Membership, you will earn a Dividend Certificate for every book you purchase. Three Certificates plus payment of the nominal sum of \$1.99 will entitle you to a valuable Book Dividend of your choice which you may choose from a list provided Members.

ELECTRONICS BOOK CLUB

Blue Ridge Summit, Pa. 17214

Please open my Trial Membership in ELECTRONICS BOOK CLUB and send me the 4 books circled below. I understand the cost of the books I have selected is only 49¢ each, plus a small shipping charge. If not delighted, I may return the books within 10 days and owe nothing, and have my Trial Membership cancelled. I agree to purchase at least four additional books during the next 12 months, after which I may cancel my membership at any time.

101 300 678 800 811 841 856 874
919 929 966 1011 1015 1019 1023
1028 1054 1055 1060 1064 1070 1088

Name _____ Phone _____

Address _____

City _____

State _____ Zip _____

(Valid for new Members only. Foreign and Canada add 10%) RE-118

CIRCLE 29 ON FREE INFORMATION CARD

www.americanradiohistory.com



PHILIPS

HICKOK



DORIC



Non-Linear Systems



C-Meter: MODEL 130 A precision, autoranging, capacitance meter

Autoranging
10 ranges are automatically selected from full scale values of 200 picofarads to 200,000 microfarads, with a maximum resolution of 0.1 picofarads.

Accurate
The C-meter achieves 0.1% (±1 count) up to 200 microfarads and 1% from 200 microfarads to 200,000 microfarads. It is accurate on all ranges at temperatures from 15° to 35°C. (S_P to 95%_R).

DORIC **\$325.**

FLUKE DIGITAL MULTIMETERS



- Measures AC/DC Volts, Current and Resistance
- True RMS on all AC Functions
- Diode Test
- In-Circuit Resistance Measurement
- Overload Protection on all Functions
- Functional Self Check

Model 8020A is a 3 1/2 digit six-function hand-held multimeter with features that qualify it as an excellent field service and troubleshooting instrument. Measurement functions include AC voltage, DC volts, AC current, resistance and diode test. Each function, with the exception of diode test, has five selectable ranges for a total of 25 ranges. (Look range for diode test.) True RMS conversion technology offers high accuracy for noise and other distorted waveforms. AC coupling rejects dc bias during ac voltage measurements. DC coupling is used on the ac current ranges to provide the ac and dc capability necessary for measuring power supply and SCR regulator currents. An optional resistance measurement can be made using the normal resistance ranges. Parallel semi-conductor junctions are measured by injecting 1 mA into 200 mV ranges. The unknown resistance.

SPECIFICATIONS

	AC Volts	DC Volts	DC Current	AC Current	Ohms	Diode Test
Range	0.7-1100V	0.2-750V	200-10A	200-10A	200-∞/1000Ω	0-2000 mV
Resolution	100-μV	100-μV	100-μA	100-μA	0.1Ω	0.2-1V
Accuracy	±0.1-1%	±0.5-2%	±0.5-1%	±1-2%	±0.2-1%	±0.2-1%

8010A **\$239.**

8020A

- 26 Ranges—5 Functions plus New Conductance Function for up to 10,000 MΩ Leakage Measurements
- Extensive Overload and Transient Protection
- Rugged Construction—1 Year Warranty
- Hi/Low Power Ohms for In-Circuit Resistance and Diode Testing
- 10 MΩ AC/DC Input Impedance Doesn't Load Circuit
- 200 Hour, 9V-Battery Life—Low Battery Indicator
- Large LCD Readout—2000 Counts
- 1 Year Calibration Cycle—Only 3 Adjustments
- One Hand Operation
- Complete with Battery and Test Leads

The 8020A has been designed with the user in mind and features exclusive one hand operation. Full service measurements, the 8020A has a ruggedized case and extensive overload/transient protection backed up by a 1 year warranty. Long term stability (1 year calibration cycle) is excellent with only three cal. adjustments. Up to 200 hours of continuous operation can be expected from a single 9V alkaline battery.

BASIC SPECIFICATIONS

	DC Volts	AC Volts	DC Current	AC Current	Other	Conductance
Range	0.2-1000V	0.2-750V	200-10A	200-10A	200-∞/1000Ω	200-∞
Resolution	100-μV	100-μV	1-μA	1-μA	0.1Ω	0.1K5
Accuracy	±0.2-1%	±0.5-2%	±0.5-1%	±1.5-2%	±0.2-1%	±0.1-1%

8020A **\$169.**

New Low Distortion Function Generator



MODEL 3010

- Generates sine, square and triangle waveforms
- Variable amplitude and fixed TTL waveforms
- 0.1 Hz to 1 MHz in six ranges
- Push button range and function selection
- Typical sine wave distortion under 0.5% from 0.1 Hz to 100 kHz
- Variable DC offset for engineering applications
- VCO external input for sweep-frequency oscillator (TCO)

\$144.95

Regular price \$175.



MODEL 1850

- 5Hz to 500 MHz reading guaranteed—100 MHz typical
- Gate time from 10ms to 10 ns
- Full period measurement capability
- 50 mV root sensitivity at 500 MHz
- Operates from 115 or 230 VAC, or 12 VDC
- Well protected input circuitry
- Temperature compensated crystal oscillator (TCO)

\$379.95

Regular price \$450.

520 MHz Frequency Counter



MULTIFUNCTION COUNTERS

DISTINCTIVE PERFORMANCE FEATURES YOU CAN USE

The 1910A, 911A And 1912A Family

Precise, rapid determination of frequency, period and period-average, coupled with totalize capability, repeat superior accuracy and performance in the Fluke 1910A, 911A and 1912A multimeters. Here are the features and benefits that distinguish these hard working counters from all others in their price range.

Multifunction

The family does the work of counters costing much more. They measure frequencies to 125 MHz (1910A), 250 MHz (911A), and 500 MHz (1912A) over a period of signal frequencies to 2 MHz.

Automatic Clean Dropout

The 1911A and 1912A Channel-B input has a circuit which automatically monitors the input and gives you instant warning in the form of zero reading whenever the input signal level falls below the sense threshold of the trigger circuit. When the signal level returns to an acceptable level, the counter locks on for a correct reading. *What you get a reading, you know it's right.*

Sensitivity

A basic sensitivity of 15 mV, backed by Fluke's conservative design margin, guarantees you not just reliable, solid readings every time. In practice, a typical sensitivity of 10 mV will be experienced.

Auorescent

This automatic feature is activated every time you select a new range of functions, which means you never have to wait for a second reading, the first one in the new measurement sequence is always correct. *Auorescent saves time and reduces errors.*

Autorange

Full autoranging is supplemented by selectable four-range manual operation. In autorange, the display is automatically fixed to a maximum 7-digit reading.

Input Signal Conditioning

All three counters offer trigger level and attenuate controls which operate over the dynamic range of the input to permit accurate readings in the presence of noise.

SPECIFICATIONS

Input Characteristics

Model	Channel	Operating Range		Sensitivity
		Frequencies	Period	
1910A	A	5 Hz - 125 MHz	500 ns - 0.2s (15 Hz - 2 MHz)	15 mV rms, 5 Hz - 100 MHz 25 mV rms, 100 MHz - 125 MHz
		50 MHz - 250 MHz	15 mV rms, 50 MHz - 175 MHz 30 mV rms, 175 MHz - 250 MHz	
1911A	A	5 Hz - 125 MHz	500 ns - 0.2s (15 Hz - 2 MHz)	15 mV rms, 5 Hz - 100 MHz 25 mV rms, 100 MHz - 125 MHz
		50 MHz - 250 MHz	15 mV rms, 50 MHz - 175 MHz 30 mV rms, 175 MHz - 250 MHz	
1912A	A	5 Hz - 125 MHz	500 ns - 0.2s (15 Hz - 2 MHz)	15 mV rms, 5 Hz - 100 MHz 25 mV rms, 100 MHz - 125 MHz
		50 MHz - 500 MHz	25 mV rms, 50 MHz - 500 MHz	



125 MHz	1910A	\$395
250 MHz	1911A	\$495
520 MHz	1912A	\$620



LCR-740 Transistorized LCR Bridge

- Highly accurate 3 digit readout.
- Measures Inductance (L), Capacitance (C) and Resistance (R) within ±0.5% accuracy.
- Range expandable — built-in 10% over range.
- Loss Factor scale (D).
- Battery, or AC adapter operation.

\$279.95

Regular price \$319.

LCG-395 SOLID STATE VIDEO COLOR SIGNAL SOURCE



- Provides staircase, window, convergence and white purity adjustments.
- Multi-purpose applications for CATV, MATV, CCTV, VTR and NTSC testing.
- Segment display information provides data details for every color check requirement.
- Exclusive convergence check facility gives hzt and vert lines and dots within 80% safety margin.
- 5-step staircase signal for checking modulation levels in 20% segments from 0 (black) to 100% (white).
- Window and noiseless white raster position.
- 10 gated windows, plus 3 gated color bars, plus overall rainbow pattern.
- Return trace blanking for vert hzt signals.
- 2 switch selectable RF chan. frequencies.



\$199.95 \$299.95

Regular price

Simpson

TRIPLETT


BK PRECISION

VIZ formerly **RCR**

LEADER

DATA PRECISION

Dual-Trace 5' 30MHz Triggered Scope...

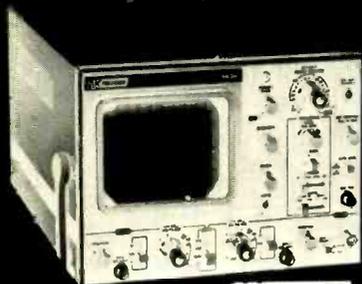


- MODEL 1474**
- Rise time 11.7 ns or less
 - Built-in digital delay line permits time of arrival (TOA) or time delay (TID) measurements
 - Frequency response up to 30 MHz
 - Lock-in for narrow band signals
 - Multiple channel operation
 - Wide area CHOP with ALTIMATE for zero charge transfer loss
 - Channel input impedance, 100 ohms, including ECL
 - High accuracy low-noise vertical sync separator
 - Flat response with smooth roll-off past 30 MHz
 - PDA CRT with 3000 lines
 - Built-in high-level sine wave filter
 - Maintains calibration accuracy from over 100 to 1000 VAC and 2000 Hz
 - 50 control lines - 62.5 μ sec - 0.15 sec

\$729.95

BK PRECISION

Probes not included in price

LBO-520
30MHz, Fixed Delay

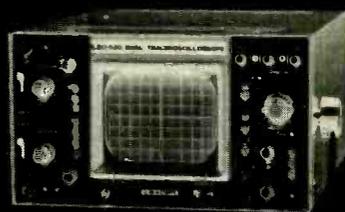


LEADER
Instruments Corp.

- Dual trace, 30MHz bandwidth.
- 5mV/cm Vertical Sensitivity
- Fixed delay facilitates hi-speed readings of the leading edge of a pulse or pulse train.
- Add, subtract, alternate selection, chopped and from panel X-Y modes broaden areas of application.
- T-V and TV-H sync. for both CH-1 & 2

\$849.95

Regular price \$1,050.

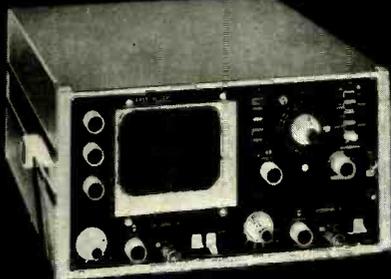Model 517
Dual-Trace
15 MHz
Triggered
Cscilloscope



HICKOK

\$589.95

Regular price \$695.

- 15 MHz response flat within 3dB for all signal levels. Excellent pulse response
- Minimizes overshoot and ringing.
- 5mV/cm sensitivity, useful for solid state work.
- Frequency triggering to 27 MHz (30 MHz typical).
- X-Y operation for vector scope measurements.
- Trigger & 10 cm display.
- Auto mode triggering provides baselines for recurrent wave operation.
- CHOP with ALTIMATE mode automatically selected as sweep time is changed for scope setup.

- Algebraic sum and difference capability
- Differential input capability
- Digital logic circuit capability, including CMOS.
- Switches to AM and OLS waveforms
- TV sync separator built in
- Regulated power supply maintains amplifier gain with changes in line voltage from 105 to 125 volts.

LBO-508
20MHz, Dual Trace



LEADER
Instruments Corp.

- Add, subtract modes on CH-1 & CH-2 facilitate easy check-out for simultaneous pulses, signal levels, distortion & noise cancelling.
- Front panel X-Y operation useful for phase shift measuring, sweep alignment, vector scope service
- 175nSec rise time.
- Automatic chop and alternate selection for low acc. high frequency checks.
- Automatic trigger for CH-1 or 2 includes TV sync.
- 10mV, 0.2CV/cm Vertical Sensitivity 11 steps.
- 0.2 μ Sec to 200m/cm sweep speed, 18 steps, XE magnification.


\$614.95

Regular price \$769.

SUPER SPECIALS

Shipping not included in price. Sale ends Dec. 31, 1978


New 15MHz portable 3" dual-trace scope

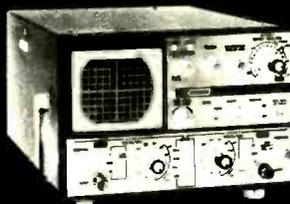

- MODEL 1432**
- 15MHz bandwidth with smooth (optional) usable response as wide as beyond 30MHz
 - 2mV/div. vertical sensitivity
 - Operates on 117VAC, 24 VAC, 15VDC or optional internal battery
 - Fully regulated high- and low-voltage supplies
 - Algebraic addition and subtraction of Channel A and B input signals
 - Nonlinear collapsed sweep ranges cover 0.1 microsecond to 1 second
 - TTL Compatible Z-stimulus
 - Collapsed sweep measures only 0.1 to 1.0 μ sec
 - Includes two 2mm lead 10:1 direct probes and connectors
 - Built-in sync separator

BK PRECISION

\$629.95 Regular price \$780.

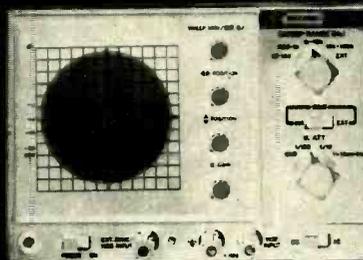

5MHz Solid State 3" Cscilloscope

- MODEL 1403A**
- 5 MHz with high sensitivity
 - Full production lines, schools, field use work, laboratory
 - CD reproduction monitor
 - Ultra-compact and lightweight: 10.5" x 10.5" x 10.5"
 - Like the 1402A to release more important signals from nonrepeating applications
 - Vertical sensitivity of 10mV/division
 - High brightness CRT and leaded-glass graticule

BK PRECISION

\$209.95
Regular price \$250.

3-1/2 Digit DMM with .5% Accuracy



BK PRECISION

MODEL 2810

\$109.95

Regular price \$130.

- 3 1/2 digit easy to read LED display
- 0.5% DC accuracy typical
- 1000 μ sec resolution
- 10 μ sec range and control to remote test fixture
- Sensitivity-high Low-Z input ohms on low range
- Auto reading
- Completely overload protected on all DC ranges
- 1000 overrange reading to 2000 counts full scale
- Protected against RF interference
- Completely portable

THE TEST EQUIPMENT SPECIALISTS

TOLL FREE HOT LINE
800-223-0474

54 West 45 Street, New York, N.Y. 10036 212-687-2224

ADVANCE ELECTRONICS

equipment reports

Data Precision Corp. Model 1350 DMM



CIRCLE 106 ON FREE INFORMATION CARD

THE DATA PRECISION CORP. (AUDUBON ROAD, Wakefield MA 01880) specializes in digital multimeters and they have introduced a new one. They call it a General Purpose Multimeter, and it is. It's designed for any kind of electronic/electrical work. It is a 3.5-digit instru-

ment and has a basic accuracy of 0.1%. It has a tough plastic case with a handle that doubles as a bench rest. The readouts are LED's, large enough (0.43 in.) to see quite a way off.

DC voltages can be read from $\pm 100 \mu\text{V}$ to a full 1200 volts. AC volts from $100 \mu\text{V}$ to 1000 volts RMS. The input impedance is 10.0 megohms on all ranges. Six pushbuttons are used for range switching on all functions—volts, ohms and mA. The ranges are set up in the simple 1-10-100-1000 sequence (the lowest range is $100 \mu\text{V}$) and all but the top range have 100% overrange capability. With 100% overrange, a 0-10 range will read up to 19.9. If the 100% overrange capability is exceeded, it is indicated by the display being blanked except the left-hand digit that displays a "1" and the decimal point. Resistance ranges start at 0-100 ohms, and go up to a 10.0-megohm range. Same overrange as the others; the 10.0 megohm will actually read 19.99 megohms. Either high-ohms with 2.8 volts on the prods or low ohms with only 300 mV can be selected on all resistance ranges by a pushbutton.

The panel is plain and simple. The functions are chosen by 4 pushbuttons and ranges by 6 pushbuttons, all along the bottom of the panel. Input jacks are at the right side, out of the way. A separate jack is used for current readings only. I like this approach better; it eliminates the chance of accidentally connecting the meter across a voltage with the switch on mA!

Early DMM's suffered from overload accidents. The *model 1350* is well protected on every range. It will take 1200 volts on any range, including resistance, and it will handle a 6000-volt spike on any voltage input for 500 ns, with no damage. The current ranges are protected by 2A 250-volt fuses. The AC frequency response is specified up to 10 kHz, except for the two highest current ranges that are specified up to 2 kHz.

The *model 1350* is all IC's with the exception of a couple of transistors used as voltage regulators. Even the DC power supply uses an IC regulator. The basic circuitry has the beauty of simplicity. A couple of op-amps and an

continued on page 32

Double your capability.

The VIZ Supplysts™ Power supplies with built-in circuit testing capability.

Only the VIZ Supplysts let you power equipment and circuits *and* test dc voltage points, all with the same instrument.

The Supplysts speed your work, help cut down bench clutter, and free VOMs for other jobs. And even with their extra testing capability, they cost less than most quality fully-regulated power supplies.



Single 0-50Vdc, 0-2A supply with two 0-99.9V DC voltmeters
WP-705 \$240.00



Single 0-25Vdc, 0-4A supply with two 0-99.9V DC voltmeters
WP-706 \$240.00



Dual Supplyst
Two 0-25Vdc, 0-2A supplies with two 0-99.9V DC voltmeters
WP-707 \$299.00



Triple Supplyst
Two 0-20Vdc, 0-2A supplies
One 5Vdc (to 4A) fixed-output supply with two 0-99.9V DC voltmeters
WP-708 \$333.00



The Circuit Tester line
Accuracy and stability assured

VIZ

VIZ Test Instruments Group 335 E. Price St. Philadelphia, PA 19144

CIRCLE 44 ON FREE INFORMATION CARD

The whole team wondered what Ron Brown was up to in his basement.

Word has it he was up to something mighty special. And when he didn't show up for bowling practice one Wednesday night, the Lucky Strikers (that was the name of his neighborhood team) began to wonder, too.

So it was that a bunch of the boys decided to pay their "star" a visit, and talk him out of his secret project and back into action. It didn't happen that way, though.

Matter of fact, it was Ron Brown who talked the Lucky Strikers out of their bowling night and down into his workshop. What was it ... what could be exciting enough to keep a bunch of ten-pin tigers from their favorite pas-time? One of the most fascinating learn-at-home programs in the world, that's what!

Actually build and experiment with a new big-screen color TV in ASI's fascinating learn-at-home program. It will help you develop new skills as an electronics troubleshooter.

You'll set up your own electronics laboratory to discover first-hand the technology behind the most exciting innovations in the world of home entertainment electronics.

In fact, as part of the program, you'll actually build and experiment with a beautiful, integrated circuit 100% solid state color TV.

But most important of all will be the new skills you'll develop all along the way... the kind of skills that could lead you in exciting new directions. For example, like many of ASI's 140,000 graduates, once you complete the program you could use your training:

1. To provide part-time income
2. To start a business of your own
3. To seek out a job in the electronics industry
4. To upgrade your current job
5. As a foundation for advanced programs in electronics

Go exploring at home, in your spare time. No traveling to class. No lectures. No one breathing down your neck.

ASI wants to make it easy for you to get to know the exciting world of home entertainment electronics. You'll be able to develop new skills in your own home on whatever days and hours you choose. So you don't have to give up your present job or paycheck just because you want to prepare yourself for some future opportunities.

What's more, we believe that when you're exploring a field as fascinating as home entertainment electronics, reading about it is just not enough. That's why you'll get lots of "hands on" training experience with some of the most impressive electronic training tools you've ever seen!

No Electronics Background Necessary

That's one of the advantages of this program. We start you off with the basics and help you work your way up, one step at a time. You'll start right off using your hands as well as your head. That's because ASI firmly believes that one of the best ways to develop skills is the exciting "hands on" way.

Each time you receive new materials you will assemble and experiment with the kind of fascinating electronic equipment that will guide you with tests and experiments and will help you become familiar with operations and applications. With ASI you BUILD, EXPERIMENT, and KEEP:

- Signal Generator—This important tool helps you explore AM alignment and signal injection. This is a source of modulated or unmodulated signals. It provides a wide range

of frequencies for use in AM, FM, TV, LW and SW broadcast bands.

- Transistorized Radio Receiver—Build your radio in a spread out format directly on a large schematic diagram. You will learn how transistors, capacitors, resistors and other parts work together to receive radio signals and convert them into sound.
- VTVM (Vacuum Tube Voltmeter)—Build and troubleshoot measurements of DC+, DC-, AC rms and peak-to-peak voltages.
- Solid State Triggered Sweep Oscilloscope—See the heartbeats of tiny integrated circuits with one of the most universal of all testers. You'll experiment with displays of voltage waveforms found in audio devices, television receivers, transmitters and other electronic equipment.
- Vectorscope—Patterns for converging, adjusting and troubleshooting color television receivers. Solid state circuitry and integrated circuits are used for accuracy, stability and reliability since this will be a key instrument for troubleshooting and servicing color television receivers.
- Color Television Set—As you build, you explore automatic fine tuning, plug-in circuit boards, the cathode ray tube and all the components and circuitry used in the late model color receivers.

Besides these, you will also receive a pre-wired and assembled multi-tester plus a professional quality set of electronic hand tools and tool box.

And Only ASI Offers Audio/Visual Aids Tool

You will receive a filmstrip projector, filmstrips and records that SHOW and TELL you the proper way to perform some of the fascinating tests and experiments you'll do in the program. Only ASI offers this exciting way to combine theory with practice... and our graduates tell us that these aids are some of the most helpful and interesting parts of the program.

We try to give more personal attention than other learn-at-home programs.

1. Toll-free phone-in assistance. Should you ever run into a rough spot, we'll be there to help. While many schools make you mail in your questions, we have a toll-free line for questions that can't wait.
2. Every student is assigned a Personal Technical Advisor. He'll follow your progress and be available whenever you want to "talk shop" or bounce around an idea or two.

Send for free details today—for a more secure tomorrow.

Whether your goal is higher-paid job skills... extra income from part-time work... being your own boss in your own business... or simply to become your own electronics expert and experience the comfortable confidence that comes with having another marketable skill to fall back on, in case of hard times... ASI can help you reach it.

Mail postpaid card today for free course outline and sample lesson.

No cost or obligation of any kind.
APPROVED FOR VETERANS BENEFITS
WHEN TAKEN FOR VOCATIONAL PURPOSES.

If card has been removed—write to:



advance schools, inc.
5900 NORTHWEST HIGHWAY • CHICAGO, ILLINOIS 60631

101



"Our whole family helped assemble this wonderful Schober Organ... now we all play it!"



Talk about real *family* fun! We all worked together, for a few hours almost every day. Almost too soon, our Schober Organ was finished. Our keen-eyed daughter sorted resistors. Mom soldered transistor sockets, although she'd never soldered anything before. And it did our hearts good to see the care with which our son—he's only 12—installed the transistors. Me? I was the quality control inspector—they let me do the final wiring. And when it came time to finish the beautiful walnut cabinet the easy Schober way, we all worked at it!

Now, we gather around our Schober Organ every evening to play and sing together. Some of us play better than the others, but we're all learning—with the help of the easy Schober Organ playing courses. I might add that I'm especially pleased with all the money we saved. Our completed Schober Organ compares favorably with a "ready-made" one costing twice as much! (The five models range from \$650 to \$2850.) And we didn't even need to pay the whole amount all at once, because we were able

to buy Schober Kits a component at a time, to spread costs out. Or we could have had two-year time payments!

Families like ours have been building Schober Organs for 20 years. How about your family? You can have all the details, without cost or obligation. Just send the coupon for the fascinating Schober color catalog (or enclose \$1 for a 12-inch LP record that lets you hear as well as see Schober quality). Clip the coupon right now—and mail it **TODAY!**

The *Schober* Organ Corp., Dept. RE-180
43 West 61st Street, New York, N.Y. 10023

- Please send me Schober Organ Catalog
 Enclosed please find \$1.00 for 12-inch L.P. record of Schober Organ music

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

CIRCLE 45 ON FREE INFORMATION CARD

EQUIPMENT REPORTS


continued from page 26

A/D converter do all of the work.

The instrument carries a full one-year warranty, and you get a certificate of conformance that traces its accuracy to NBS Standards. Calibration is needed only at one-year intervals. When calibration is necessary, only two adjustments are required.

An attractive feature of the *model 1350* is its price—\$169.00 complete with test leads, operating manual, certificate and even a spare fuse. This is getting it down to the point where the typical shop can have instruments of laboratory accuracy and stability that are also rugged enough for everyday use. **R-E**

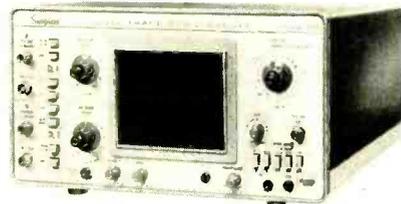Simpson Model 452 Dual-Trace Oscilloscope



CIRCLE 107 ON FREE INFORMATION CARD

THE SIMPSON ELECTRIC COMPANY, 853 DUNDEE Avenue, Elgin, IL 60120, has been making high-quality test instruments for a long time. Their latest introduction, the *model 452* dual-trace triggered-sweep oscilloscope, is an all-solid-state unit with many applications: lab work, production-line testing, design, or any kind of consumer electronics work. It is especially useful for color TV applications of any kind.

The *model 452* has all the regular features. Its two channels are identical: DC to 15 MHz and AC from 2 Hz to 15 MHz. The high-impedance inputs are 1.0 megohm shunted by 25 Pf, and handle a maximum input of 500 volts DC plus AC peak.

Calibrated vertical step attenuators give a deflection sensitivity from 5 mV-per-centimeter (.005 volt) up to 10 volts-per-centimeter with a direct probe. The attenuator switch uses the 1-2-5 sequence. A continuously variable control allows fine adjustment if needed; simply turn the control fully clockwise for calibration. The inputs can be switched to AC or DC. A total of 11 positions are used for the volts-per-centimeter selector switch.

Channel selection and other functions are handled by well-spaced push-push controls that lock in on the first push and release on the second. All pushbuttons are very plainly marked so that you know where you are all the time. Channel A or Channel B can each be used by itself if you want a single trace. Just press the Channel A button, leaving Channel B off; or move the Channel B trace up off the screen using the vertical position control. For a dual trace, the sweep is automatically chopped, at a rate of 200 kHz, for sweeps from 1 ms-per-centimeter and slower. For all higher speeds, the two traces are scanned alternately. There is no perceptible flicker in either one.

Other pushbuttons allow other types of testing: One adds the signals in Channel A and Channel B and then displays the sum waveform. Another pushbutton inverts the Channel

continued on page 34

U.S. & foreign patents

SAY GOODBYE to old manual wire wrapping tools!



**NEW P184
SLIT-N-WRAP**
tool with Tefzel
wire makes
connections as
reliable as
other wrap tools.

Now you can wrap
thick insulated wire
4 TIMES FASTER
with
NO pre-cutting
NO pre-stripping
DAISY CHAIN
RUNS.

P184, with
100' of 28
gage Tefzel
wire, \$29.50.

Insulation is slit
open before
wrapping on post,
not between
posts. No unwanted
cut-thru.

P184-4T with batteries and recharger, \$89.50 (includes P184).
P184-4T1 110V AC, \$99.50 (includes P184). Tefzel wire, 28 gage, various
colors, \$4.18/100 ft. If not available locally, factory order—add \$2 handling charge.

Prices subject to change without notice

Vector

ELECTRONIC COMPANY, INC., 12460 Gladstone Av., Sylmar, CA 91342
phone (213) 365-9661, twx 910-496-1539
571177

CIRCLE 52 ON FREE INFORMATION CARD

EQUIPMENT REPORTS

continued from page 32

B waveform. This control performs all kinds of tricks. For instance, when you make the standard input-output tests on any amplifier stage, the output waveform is inverted. You can press the Channel B INVERT pushbutton, adjust the traces to the same amplitude, and then superimpose one trace on the other. This will display instantly any significant differences, phase shifts and distortion.

By pressing the Channel B INVERT and ADD pushbuttons, you can subtract Channel A from Channel B. This test is used for comparing differential voltages between two points in a circuit, etc.

The model 452 dual-trace scope is indispensable for testing digital circuitry. Since we're going to be dragged kicking and screaming into digital work (at least I am!) we might as well have the right tools for it. Timing relationships are vital; pulses must arrive at the right place at exactly the right time (and *exactly* means just that!).

The model 452 manual shows a good typical example using a set of waveforms produced by the Simpson model 7016 frequency counter to show the exact timing. In only one case, the reset pulse, using its negative edge, triggers a control flip-flop. By hooking the scope up to observe the reset pulse on one channel and the flip-flop output on the other, this can be checked with the greatest of ease! This applies to any other type of digital circuitry.

The model 452 manual gives a very complete description of how to take phase readings

on any kind of signal—sinewave, pulse, square-wave, etc. After a simple calibration, the phase angle is very easy to read. After setup, just push the X5 magnification switch and the display expands (the sweep speed goes up). If the original resolution was, say, 40°-per-division, pressing this switch brings it to only 8°-per-division, which can easily be read to a close tolerance. You can also make Lissajous figures, which are shown in the manual.

In hi-fi audio applications, you can use the scope to read the phasing of the inverse feedback. If the phase is off far enough, it can cause the feedback to become regenerative instead of degenerative, and force the amplifier into violent oscillation. In color TV, you can easily check to make sure that the gating pulse and color burst are in precisely the correct phase (timing) relation. If the pulse arrives too soon or too late, the burst finds the gate slammed in its face!

Five trigger selector switches are on the right-hand side of the panel below the trigger-level control. These switches let you select Channel A, Channel B or external trigger signals using either positive or negative going slopes; and also switch to normal or auto (to display a trace on the screen without triggering if you need it). The last switch changes the Channel B input so that it becomes the horizontal amplifier. This feature is used in sweep alignment, vectorscope display, Lissajous figures, etc. The Channel B gain controls adjust the trace horizontally.

Vertical interval test signals (VITS) are very handy for quick IF/RF response and alignment tests. However, since the patterns are broadcast on only two lines of the vertical blanking

interval, they are not very easy to pick out and lock on to. (I know, I've tried it!)

The model 452 TIME/CM selector switch has three extra positions: TVV, TVH and VITS. The instruction manual shows a simple method for picking the VITS signal out of the video, locking onto it, then displaying it. Again, just press the X5 magnification switch, and the display opens up so that the VITS signal is easy to observe. All you do is *look* at the multiburst part of the VITS signal, which consists of several short bursts of video at a gradually increasing frequency.

If the IR/RF stages are working properly, these burst frequencies will all be amplified equally, and the top of the multiburst will be flat. If it slopes in either direction (becomes wedge-shaped) this indicates there is either a loss of high-frequency or low-frequency response somewhere ahead of the video detector. If a good flat top is displayed, just dig into the video stages to locate the source of your trouble.

The test probes used with the model 452 are 10:1 divider types; they use the popular miniature spring-loaded hook design. Special tips can be pushed on for testing IC's and several other types of components.

The DC power supply is regulated to within an inch of its life. I counted *seven* separate voltage regulators, and I may have missed one or two. The patterns are therefore very stable and the calibration remains accurate during variations of the AC line voltage.

The model 452 is a lot of instrument, and its price (\$635) is well within the ballpark for an instrument of its capabilities and construction. *continued on next page*

Today's most exciting automotive accessory, AUTOCOMP, is actually three complete instruments in one — each operated by electronic microprocessor control. AUTOCOMP is a digital clock, which may be programmed to read elapsed time or correct time in hours and minutes. AUTOCOMP is also a true MPG meter, utilizing a patented flowsensor and a speedsensor to compute instantaneous miles-per-gallon or average miles-per-gallon as you drive. And AUTOCOMP is a complete trip computer. It will display the amount of fuel your vehicle has used since last fill-up or beginning of trip and it will display the distance your vehicle has traveled since the last reset. AUTOCOMP mounts easily in or on your dash and provides large LED readouts of these functions by pushbutton control. With this valuable data at your fingertips, you can significantly reduce fuel bills by monitoring and improving your driving habits. You will know precisely how changes in acceleration, speed, weight, wind, hills, etc., affect fuel economy. You can also tell when your engine is burning extra gas by not running at peak performance. AUTOCOMP will allow you to operate your vehicle more efficiently, saving you dollars, not only in fuel bills, but also by helping you avoid the costly repairs of a major breakdown. In one year's operation you can easily save the cost of AUTOCOMP in fuel and repairs. AUTOCOMP can be installed on most American and Japanese make autos and vans except those with fuel injection, and is supplied with all necessary components and hardware, as well as clear illustrated instructions, that make it easy for a do-it-yourselfer to install. AUTOCOMP is covered by a 1 year Manufacturer's Limited Warranty.

3 Automotive instruments in 1

DIGITAL CLOCK

Press the TIME button and the LED display reads the correct time (in hours and minutes). The clock may instead be used to display ELAPSED TIME.

MPG METER

Press the INST MPG button and read how many miles per gallon your vehicle is attaining at each moment. Press the AVE MPG button, and read the average miles per gallon the vehicle has attained since the last reset (up to 200 MPG).

TRIP COMPUTER

Press the FUEL button and read the amount of fuel the vehicle has used since last reset (up to 1000 gallons). Press the DIST button and read the distance the vehicle has traveled since last reset (up to 1000 miles).



PRICE REDUCED! **\$99.95**

FOR ORDERS ONLY
CALL TOLL FREE ANYTIME!
1-800-423-2355 Ext. 601
In California 1-800-232-2175 Ext. 601
For more information call 805-965-1015

SPACEKOM-AUTOCOMP
212 E. Gutierrez Street
Santa Barbara, CA 93101



Please send me _____ AUTOCOMP(s) at \$99.95 ea. (California residents must add 6% sales tax.)

Car on which AUTOCOMP will be installed _____
Make _____ Model _____ Year _____

Factory Cruise Control? Yes No

Total enclosed (Cal. res. add tax) \$ _____

USE YOUR CHARGE CARD!

BankAmericard (VISA)
 Master Charge (Interbank # _____)

Charge # _____ Exp. Date _____

Signature _____

PRINT NAME _____

ADDRESS _____

CITY _____

STATE _____ ZIP _____

CIRCLE 75 ON FREE INFORMATION CARD

B&K-PRECISION'S new digital probe offers more than logic



Model DP-50

- Reveals pulse presence to 50MHz
- Priced at only \$50
- Multi-family, compatible with TTL, DTL, RTL, CMOS, MOS, and HINIL
- Clearly displays in-circuit logic activity
- Memory mode to "freeze" pulse display
- Pulse mode to "stretch" short pulses
- 2 megohm input impedance
- Typically detects pulses to 10 nanoseconds
- Overload and reverse polarity protected

The new B&K-PRECISION DP-50 50MHz digital probe simplifies the troubleshooting and analysis of all digital circuits by clearly displaying in-circuit logic activity and pulse presence.

This compact instrument includes every important logic probe feature and more. Three bright LED indicators display pulse presence and high- and low-logic states. Unlike ordinary logic probes, the DP-50 digital probe will continue to indicate pulse presence to 50MHz.

Available for immediate delivery at your local distributor.

B&K PRECISION
DYNASCAN
CORPORATION

6460 West Cortland Street
Chicago, Illinois 60635 • 312/889-9087
In Canada: Atlas Electronics, Ontario

CIRCLE 58 ON FREE INFORMATION CARD

Radio Shack Model TRS-80 Computer



CIRCLE 110 ON FREE INFORMATION CARD

SPECIFICATIONS

Z-80 based CPU; 4K bytes RAM; BASIC in 4K ROM; integrated 53-key ASCII keyboard; 500 baud cassette interface; 12-inch monitor displays 16 lines X 64 characters (32 characters selectable); interspersed graphics (128 horizontal by 48 vertical); 21 general commands with 14 functions, plus special commands including array and strings. Price: \$599.95.

THE TANDY CORPORATION (1400 ONE TANDY Center, Fort Worth, TX 76102) appears to have become a serious competitor in the field of small computer systems. The Radio Shack model TRS-80 (based on the popular Z-80 microprocessor) is rapidly becoming a standard item in homes and offices. Educators are also finding it both affordable and practical for instructing students in basic computer programming.

The model TRS-80 is available either with Level 1 BASIC with 4K RAM (\$599.95), or with Level 2 BASIC and 16K RAM (\$789). Included are such accessories as a 12-inch video monitor, cassette recorder and an easy-to-follow user's manual. A game tape (*Blackjack* and *Backgammon*) is also included.

The operator's manual itself is impressive—the style is witty, comprehensive, informative, and an excellent introduction to the world of computer programming.

Although the complete three-piece model TRS-80 package is recommended as a system, the keyboard terminal alone is available for \$400. Its video output can be fed to any video monitor (even a simply converted TV set), and data can be transferred into a good-quality portable cassette recorder. The video display provides 16 lines of 64 characters each.

The modular construction of the model TRS-80 system allows for future expansion as peripheral equipment becomes available. The keyboard terminal circuit board is designed to accommodate 16K RAM and Level 2 BASIC to handle more involved computer requirements, such as advanced string manipulation and peripheral control.

In the home, the Level 1 BASIC system would be ideal for recipes, bookkeeping, filing and even games (many already available from other sources). For educators, the system's applications could include keeping records of grades, familiarizing students with how a computer operates and for visual instruction.

Small business applications for the model

TRS-80 include record- and inventory-keeping.

With Level 2 BASIC, data exchange with the cassette is faster, and the system provides for more flexible software for alphanumeric data handling and improved graphics. Level 2 BASIC is required for such peripheral equipment as a printer or floppy-disc recorder.

Using the TRS-80

As uncrated from the box, the model TRS-80 Level 1 system is ready-to-go in minutes. The three units (keyboard, video monitor and cassette player) are interconnected with cables (provided), and initial starting and testing instructions are simple to follow.

By following the instructions, it soon became apparent that the sample system was in excellent working order. The keyboard is especially responsive and comfortable.

The 16-line, 64-character-per-line video display is bright and sharply defined. The 12-inch video monitor makes the characters quite readable even at a considerable distance, an advantage for classroom instruction.

After an extended period of familiarization, we developed an involved program to test the computer: It performed flawlessly. Occasionally, in the interval between commanding the computer to transfer data to the cassette and commanding the cassette to return the data to memory, a small glitch developed—the information did not always return. This usually caused no particular problem, however, since a blinking video signal constantly alerts you as to the status of the data transfer. If the blinking stops, this means a bit error has occurred and the transfer must be repeated.

If the error occurs during a data transfer from the terminal to the tape, you will not realize it until you attempt to reload the cassette data back into memory; this process will also erase the program presently in the memory. Thus, it is advisable to record the data on two or three tapes first before reloading the computer memory to check the tape. This routine precautionary step will prevent much anguish later if for any reason (including power-line spikes, incorrect cassette volume-control playback settings, loose connections, or operator error) the data did not transfer.

All things considered, the Level 1 model TRS-80 appears to be an excellent computer system; and, as system needs grow, the model TRS-80 can grow with them. **R-E**

Electra Bearcat model 250 Programmable Scanner



CIRCLE 111 ON FREE INFORMATION CARD

THE MODEL BC-250 BEARCAT IS THE LATEST addition to the programmable, frequency-

continued on page 36

SAVE \$9



AND RECEIVE 3 YEARS OF RADIO-ELECTRONICS AT HOME.

The option is yours! You can have the next 12, 24 or 36 excitement-packed issues of Radio-Electronics delivered to your door each month, and save up to \$9 of the newsstand price while enjoying the convenience of home delivery. And you'll enjoy all the news of electronics you get in Radio-Electronics: projects to build, new-equipment test reports, computer technology, servicing tips, and all your favorite columnists on solid state, hobbies, hi-fi, servicing and computers. Check out the money-saving subscription offers on the coupon below, and check off the one that suits you best. It's the best move you can make today, or for the next three years.

Mail to: Radio Electronics

SUBSCRIPTION DEPT., P.O. BOX 2520
BOULDER, COLO. 80323

(please print)

Name			
Address			
City	State	ZIP	

Indicate the offer you prefer:

- 1 Year—12 issues ONLY \$9.98
(You save \$2.02 off newsstand price.)
- 2 Years—24 issues ONLY \$19.00
(Save More! \$5.00 off newsstand price.)
- 3 Years—36 issues ONLY \$27.00
(Save Even More! Save \$9.00 off newsstand price.)
- Payment enclosed (Send one extra issue)
- Bill me
- Check here if this is a new subscription.
- Check here if you are extending or renewing your subscription.

Extra Shipping: Canada \$3.00 per year, all other countries \$5.00 per year. 40L8

INTRODUCING

Recon XK[®]

NEW
FROM
KITMASTER



A sophisticated X & K band radar detector kit for \$69.95!

You've always heard that high price equals high performance?

NOT ANY MORE! The new Recon XK[®] multi-channel radar monitor offers all the features of other units that start at \$149.95.

Our price? \$69.95!

Compare these outstanding features:

- X-BAND SENSITIVITY UP TO 5 MILES* AT 10.525 GHz.
- K-BAND SENSITIVITY INCLUDES "HANDHELD" RADAR AT 24.150 GHz.
- SOPHISTICATED ELECTRONIC FILTER CIRCUIT REDUCES FALSE SIGNALING.
- WARNING LIGHTS & ADJUSTABLE CONTROLS FOR X & K BANDS AND POWER INDICATOR.
- ADJUSTABLE ON-OFF/VOLUME CONTROL FOR AUDIBLE TONE WARNING.


- BLACK MILITARY CONTROL PANEL
- ALUMINUM CASE & 2-WAY "ALL PURPOSE" MOUNTING BRACKET.
- EXCLUSIVE EUROPEAN SPORTS STYLING

*Reception varies according to terrain, traffic and weather conditions.

If you compare the Recon XK[®] with other radar detectors, you will find only the most expensive units offering similar features. A simple glance will also reveal the difference in styling that Kitmaster[®] engineers have effected.

Now, as a result of superior design and production technology, **YOU CAN ASSEMBLE THIS ADVANCED RADAR DETECTOR — AT HOME — USING BASIC TOOLS AND OUR DETAILED INSTRUCTION**

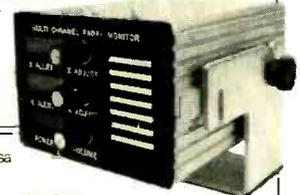GUIDE. Order your Recon XK[®] Kit today — at less than half its list price value!



— 10-DAY MONEY BACK GUARANTEE —

TO Dallas Electronic Products, Inc.
RECON XK[®] KIT OFFER Kitmaster[®] Division
Dept. RE
P.O. Box 225238, Dallas, TX 75265

Bill my Master Charge Visa

Please send

Recon XK[®] Kits \$69.95 ea
(PLUS \$2.00 SHIPPING U.S.A.)
Attached is my check or money order for \$

Card No. _____ Exp. Date _____

Name _____

Address _____

City _____ State _____ Zip _____

Signature _____

TEXAS RESIDENTS ADD \$3.50 SALES TAX EACH UNIT. CANADA \$6.75 SHIPPING. OTHER COUNTRIES \$19.25.


WE ACCEPT TELEPHONE ORDERS • 214-528-9900 • CREDIT CARD ORDERS ONLY

CIRCLE 36 ON FREE INFORMATION CARD

NOVEMBER 1978


35

ACCURACY MADE EASY

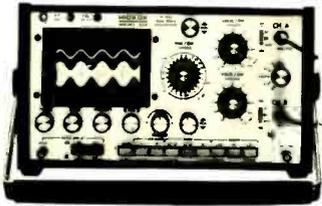


\$995

DUAL TRACE MODEL 532 - 30 MHz

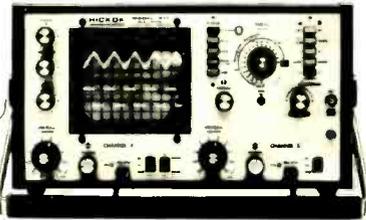

\$695

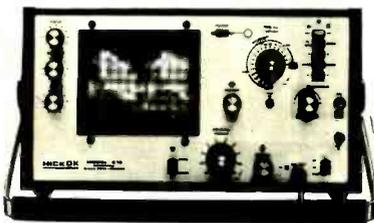DUAL TRACE MODEL 517 - 15 MHz
USABLE TO 27 MHz



\$495

SINGLE TRACE MODEL 515 - 15 MHz

Put Hickok Scope reliability on your side and get things done easier, faster, better and with complete assurance that you're doing them right.

Economically priced Hickok push-button-triggered Scopes are quick and easy to set up and use. A color-coded front panel speeds up and simplifies operation. Triggering is practically fool-proof, well in excess of the MHz rating. And excellent pulse responses virtually eliminate overshoot and ringing.

Call your nearby Hickok distributor and set up a demonstration today. See for yourself how a modestly priced Hickok single or dual trace 15 MHz, or dual trace 30 MHz, Scope will save you time and exasperation.

If you're outside of Ohio, call us toll free at 800-321-4664 for the name of your nearest Hickok distributor.

HICKOK

the value innovator

INSTRUMENTATION & CONTROLS DIVISION
THE HICKOK ELECTRICAL INSTRUMENT CO.
10514 Dupont Avenue • Cleveland, Ohio 44108
(216) 541-8060 • TWX: 810-421-8286
CIRCLE 77 ON FREE INFORMATION CARD

EQUIPMENT REPORTS

continued from page 34

synthesized VHF/UHF scanners already on the market. It is manufactured by Electra Company (300 South on East County Line Rd., Cumberland, IN 46229) the pioneer of scanning receivers.

At first glance, the BC-250 looks nearly identical to the popular *model BC-210*, but a closer look at the keyboard reveals the differences.

A custom-designed microprocessor IC greatly expands the flexibility of this scanner: It has 50-channel scanning capability; it counts the number of times any (or all) of the 50 channels have been heard in use while scanning; and it can search through any of its frequency ranges for unknown frequencies (up to 64) and store them for later display during recall.

The nonvolatile memory retains its frequency and instruction programming even if the unit is unplugged while it is operating, or if a power failure occurs; there is no battery to replace every few months.

The 50 channels are programmed into the scanner by a keyboard and stored in five banks of 10 channels each. The banks can be individually or collectively selected in or out of the scanning sequence. Thus, the frequency blocks of such agencies as fire and police departments, ambulances, etc., can be selected in and out of scanning at will.

The squelch control can be adjusted manually or rotated to an automatic position at which it is activated only when a received signal exceeds a preset level above the background noise. Plus any one of the 50 channels can be manually selected at random without having to step in sequence through the scanning order.

A delay feature places a two-second hold on any channels after a signal is received before scanning or searching is resumed. This feature allows you to hear a reply to an intercepted transmission from a simplex operation. The delay feature is not necessary for monitoring repeaters, since they have their own built-in delay for incoming signals.

Both scanning speed and search speed can be slowed down or speeded up at the touch of a button (a choice of 5 or 15 channels-per-second). The unit has a lockout feature which when activated, prevents unwanted signals from stopping the scan or search sequence.

A priority channel is also provided; no matter what function the monitor is presently executing, the priority channel overrides it and can be heard when it is active. In addition, an automatic 12-hour clock display appears when the receiver is switched off, and can also be read with the receiver on without disabling any receiving function.

The rear apron of the *model BC-250* provides an audio output for an external speaker or recorder, plus a control circuit to activate an external device such as a tape recorder. The quality of the audio sound is voice-tapered . . . crisp and clean.

Specifications

The manufacturer's specifications for the *model BC-250* show a noticeable improvement over those of earlier scanners. Naturally, published specifications are average, and will vary somewhat among individual receivers.

SPECIFICATIONS

Frequency range: 32-50, 146-174, 420-512 MHz
Sensitivity (12-dB SINAD): .6 μ V, low and high band; .9 μ V UHF
Adjacent-channel rejection: better than 50 dB
Audio output: 1.5 watts
Power requirements: 120 VAC or 13.5 VDC
Size: 10 $\frac{1}{2}$ " W \times 3" H \times 7 $\frac{1}{8}$ " D
Weight: 5 lb

Lab tests

To avoid strong signal overload in metropolitan area monitoring, Electra recommends the use of the small telescoping antenna provided with the *model BC-250*. We couldn't resist using a rooftop monitoring antenna. Distant weak signals came in surprisingly well, and problems with intermodulation and images were less than expected. A major metropolitan area is a beehive of signal activity, and only the better receivers can endure the signal overload presented by an outside antenna! Still, with the internal antenna provided, distant signals were very readable due to the *model BC-250's* improved sensitivity.

The automatic search feature, with search-lockout for unwanted signals, is a pleasure to use. The ability to recall active channels discovered during search, and the automatic capability to count transmissions intercepted on scan are very handy. A modest spectrum study of active channels in an area can be quickly accomplished using the *BC-250*.

Expected delivery for the new scanner was tentatively set for mid-summer, 1978, at a suggested retail price of \$399.95. **R-E**

Radio-Electronics®

is available in

MICROFILM

UNIVERSITY MICROFILMS

300 N. Zeeb Road

Ann Arbor, Michigan 48106

and

MICROFICHE

MICROCARD EDITIONS

A Division of

Information Handling Services

P.O. Box 1154

Englewood, Colorado 80110

BELL & HOWELL CO.

Micro Photo Division

Old Mansfield Road

Wooster, Ohio 44691

Attn.: Mr. Splers

Please write
for complete information

New All-In-One Speaker- phone



*It's a standard telephone
and speakerphone housed in a
compact ultra-modern package.
Here's a look at the circuitry
and how it works.*

HANS R. CAMENZIND*

IF YOU HAVE EVER USED A SPEAKERPHONE, OR IF YOU HAVE ever talked to somebody who was using a speakerphone, it is immediately apparent because it sounds as if the call is being made from inside a large wine barrel, a quite annoying phenomenon. Also, all except some of the most expensive speakerphones (\$300 and up) tend to drop off a word or a syllable here or there. And, if you happen to have a bad connection with much background noise, your speakerphone may not work at all. For all these reasons, speakerphones are almost exclusively used for group conversations. The much-advertised "hands-free" feature is really more of a nuisance than a valuable asset.

In attempting to design a speakerphone that eliminated, or at least greatly reduced, these shortcomings, the first and most serious problem encountered was the barrel sound that is caused by room acoustics. For example, if you place a tape recorder microphone in the middle of a room and speak into it from a few feet away, the sound bounces off the walls and you get a noticeable echo effect. In a face-to-face conversation, you do not notice this echo at all because your ears are stereophonic and the brain does a marvelous job of signal processing.

When you move a microphone to within about 18 inches from your mouth, the echo starts disappearing. At this distance, or even shorter distances, the direct sound becomes so much stronger than the reflected sound that the echo is no longer a factor.

There is at present no electronic solution to the echo problem. It is possible to process the signal so that the gain is reduced for a period of time after a sound peaks. This method works well for tone bursts, but it makes a conversation less intelligible. In addition, the time it takes for the echo to arrive at the microphone varies with room size. This means that the suppression time would have to be adjusted for each room.

The best solution to this problem is to design the speakerphone so small and light that the person using it would naturally

move it closer. This design choice was influenced by the electronic calculator: When you use a calculator you draw it close to you because it is small and handy.

A calculator-sized speakerphone also solves the problem of the noise interference on the line. If the connection is very bad, you simply pick the speakerphone up and hold it to your ear. The Tridar speakerphone contains a mercury switch that senses the angle at which the phone is being held. When it is tilted more than 45°, the gain is automatically reduced, and the speakerphone becomes a normal telephone.

This latter feature also has another advantage. Suppose you have been holding a hands-free conversation. Somebody walks into your office and you would rather continue the conversation privately. You simply pick up the phone.

Two other features are built into the Tridar speakerphone. One is a volume control to adjust the varying amplitude on the phone line and to make the speakerphone useful for a group conversation as well. The other control is a HOLD pushbutton to shut off the microphone so that the group can speak in private, or allow you to leave temporarily.

The most difficult problem to solve in the circuit design was the delay, which can chop off a part of the speech. Unlike a regular telephone, the microphone and the speaker in the speakerphone cannot be on simultaneously; otherwise the speaker feeds into the microphone, the signal is amplified and a portion of it returns to the speaker, creating the howling sound sometimes heard in public address systems.

The simplest solution here is to sense the microphone level. When the level exceeds a preset threshold, the speaker is turned off. However, since this threshold cannot be set very low (otherwise it would be triggered by room noise, e.g., a typewriter clicking), part of the first syllable is lost. To minimize the effect, typical low-cost speakerphones turn the speaker on with a delay of about 1 second so that the microphone channel is held on continuously for the entire sentence.

*Tridar Corporation.

But such relatively unsophisticated circuitry used in low-cost speakerphones has the disadvantage that comments interjected by the conversation partner can be missed. Especially if the other party in the conversation is long-winded, it becomes impossible to get a word in edgewise!

To avoid this delay a rather complex voice-level sensing scheme was designed. This is the main reason that high-performance speakerphones are rather bulky and heavy. Therefore, to provide this complexity in a small and light package, custom-designed integrated circuits were used. In fact, using custom IC's not only allowed the Tridar phone to be designed in a very small package, it reduced the cost to less than that of a design using components and standard IC's.

There is a great deal of misconception about custom IC's. Most designers feel that a custom IC is only economically feasible for very large quantities because of the enormous tooling cost and that you should design a product with standard, off-the-shelf components first. However, neither of these assumptions is quite true.

Semicustom IC's require little extra expense or added time for the development. And, especially for this speakerphone, a design using off-the-shelf components would have made no sense at all, since the end product would have been of the size of a normal telephone and weighed at least two pounds.

Basic design

Figure 1 shows the block diagram of the Tridar speakerphone. The most important feature that is responsible for the high performance of the speakerphone is the peak detector/comparator circuit. Its design represents a drastic departure from older speakerphone designs.

The most difficult task in designing a speakerphone is to devise a circuit that decides who is talking at any given moment. You cannot simply assume that if there is a signal in the microphone channel, it is the person at the speakerphone end that is talking. What makes this assumption wrong is the fact that the speakerphone's speaker also talks into the microphone.

At the other end—the telephone line—the distinction between the voices of the two parties is also unclear. On the telephone line itself the two signals are completely mixed and, supposedly, of equal amplitude so you cannot distinguish between the two. The connection to the phone line is usually made through a hybrid transformer, in which the two directions

can be separated somewhat. In the Tridar speakerphone, the hybrid circuit is an active circuit to reduce space and weight.

The separation of the two signals in even the best hybrid circuits is only about 10 dB, the reason being the telephone line impedance. If the impedance were 600 ohms, as specified, the hybrid circuit could be matched to the line and a separation of at least 30 dB would be possible. In reality, both impedance and phase vary wildly between 300 Hz and 3 kHz and depend on the length of the line.

How then can you tell which channel should be open? The information is there but just barely. The signal from the phone line coming from the hybrid circuit is slightly stronger even after the limited separation afforded by the hybrid circuit.

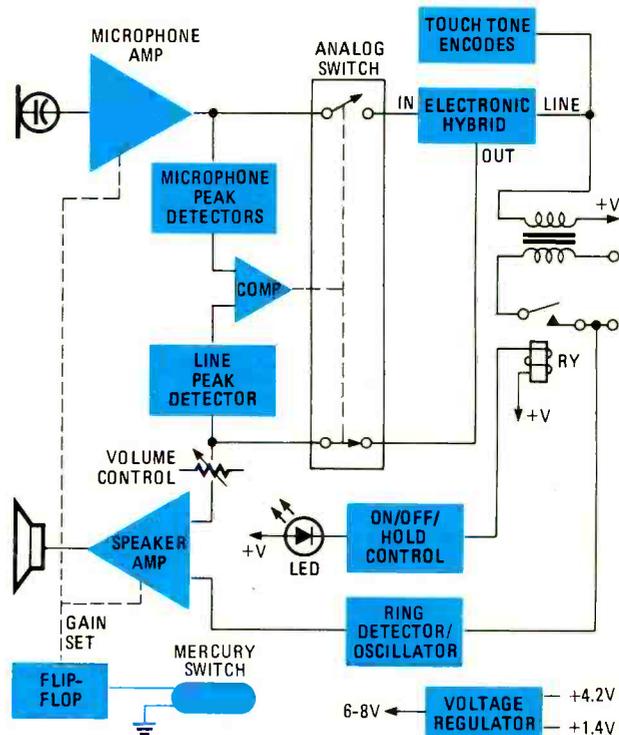


FIG. 1—PEAK DETECTORS AND COMPARATOR determine which party is talking. This represents a drastic departure from earlier designs.

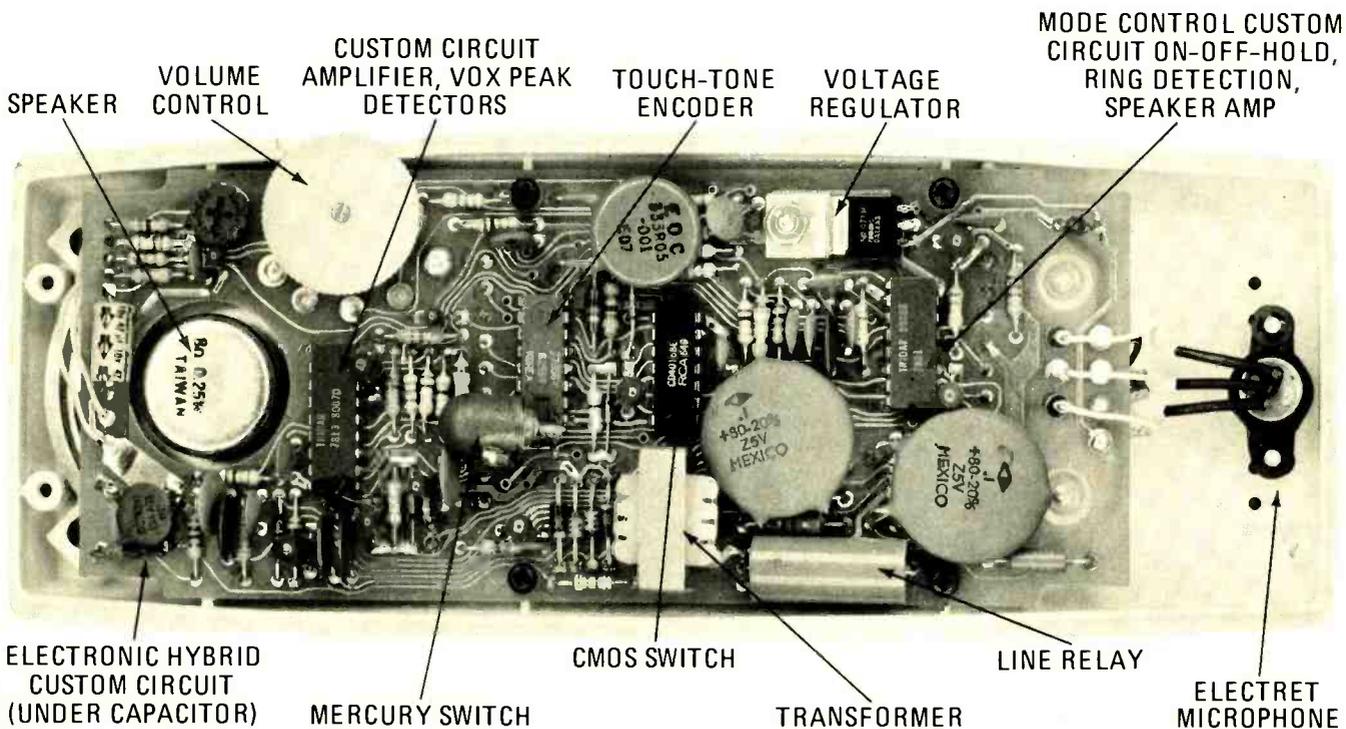


FIG. 2—CUSTOM IC's and careful layout result in a compact circuit.

Speaking directly into the microphone does result in a slightly larger amplitude than the indirect sound produced by the loudspeaker if the microphone is pointed away from the loudspeaker. In the Tridar design, the amplitudes of these two signals are converted into DC voltages in the peak detectors and then compared (see Fig. 1). If the microphone channel is louder, the upper section of the analog switch is closed and the lower one is opened; thus, the microphone sound will go to the line and the speaker channel is cut off.

During each pause in the microphone signal—even between words—the comparison is made again, i.e., the signal from the line is connected. To allow this, the time constant of the microphone peak detector is quite short.

Two factors help here. First, when you are talking, you cannot really hear anything. You shut off the other person's voice in your brain. You may be aware that he or she wants to say something, but you cannot understand it. Second, even segments of the other person's voice in this instance tell you what you need to know, namely that you are about to be interrupted and that you had better stop talking and start listening.

This is precisely what was built into this design. During each pause in the microphone signal, however short, the speaker channel is opened up. Thus, if the other person has been talking, a part of his speech is heard on the speakerphone.

If the user of the speakerphone continues to talk (despite the fact that sound is coming through) another effect takes place. The other person automatically raises his voice. This increases the level of the line peak detector, and the line signal begins to outweigh the microphone signal, thus opening the speaker and shutting off the microphone.

The entire speakerphone contains 465 components, of which 410 are contained in three custom IC's (not counting the touch-tone encoder, which is a standard, off-the-shelf IC). Figure 2 shows a view of the PC board. Here are some highlights of some of the important circuit blocks.

The hybrid circuit

The function of the hybrid circuit is to separate the two signals on the telephone line. In an ordinary telephone, this is accomplished with a rather bulky differential transformer. In the Tridar speakerphone, this function is duplicated in one of the custom IC's.

Figure 3 is the schematic diagram of the hybrid circuit. The

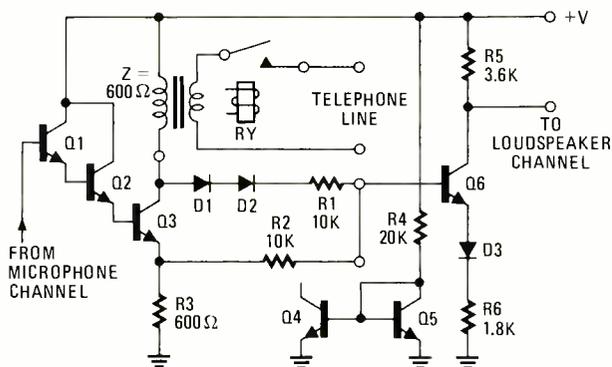


FIG. 3—ELECTRONIC HYBRID CIRCUIT duplicates function of bulky transformer used in ordinary telephone.

telephone line is connected to the phone through a small simple transformer to meet the FCC's 2000-volt isolation specification. The signal is then obtained at the secondary and arrives at the base of Q6 through D1, D2 and R1. Note that the signal cannot go through Q3 because transistor Q2 blocks the signal applied to Q3's base.

A signal coming from the microphone is buffered by Q1, Q2 and Q3. The impedance of the telephone line is nominally 600 ohms, and with a 1:1 ratio in the transformer, the collector load impedance of Q3 is the same as its emitter resistance. Thus, the signal going into the transformer has the same amplitude as the signal at the emitter of Q3, but the opposite phase. These two

signals are summed at the junction of R1 and R2. Since R1 and R2 are equal, the microphone signal cancels exactly at the base of Q6 so that only the line signal appears at this point. This, however, is true only if the line impedance is, in fact, 600 ohms. In reality, the line impedance can vary considerably and the cancellation at the base of Q6 is about 10 dB. This performance is identical to that of a hybrid transformer.

Diodes D1, D2 and D3 are used for DC level-shifting only; their influence on the gain and cancellation is minimal.

Mike amplifier and peak detectors

Figure 4 shows the diagram of the microphone amplifier. The

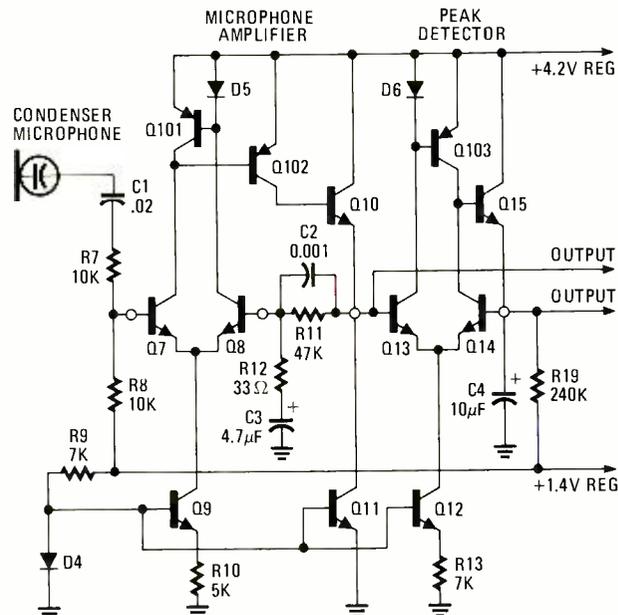


FIG. 4—MICROPHONE AMPLIFIER and peak detector features a differential input stage.

input is biased at 1.4 volts through R8. Transistors Q7 and Q8 form a differential pair with an active load D5/Q101. This active load is a diode-biased current source. The collector current of Q8 flows into D5. The internal base-emitter diode of Q101 is connected across D5. Therefore, as the current through D5 increases, the collector current of Q101 increases by the same amount. At the collectors of Q7 and Q101 there is a push-pull effect: When, with a signal at the input, one collector current increases, the other decreases by the same amount, resulting in a large amount of gain. Note, however, that this configuration can only be used in IC's since it requires a near perfect matching of the components.

The signal is then further amplified in Q102 and buffered by Q10. At this point there is an open-loop gain of several thousand that is then reduced to 140 with feedback resistors R11 and R12.

The operating current of the differential stage and the output is derived from D4. Diode D4 and the base-emitter diode of Q11 are identical in size; therefore, the collector current of Q11 will be similar to that of D4, or 100 μA. The current of Q9 and Q12 is reduced by emitter resistors.

The microphone-amplifier output is fed into both the analog switch (CMOS) and the peak detectors. The configuration of the peak detector is almost identical to the amplifier. However, there is no load current at the emitter of Q15. The positive peaks of the signal charge up capacitor C4 at the output. The only discharge path for C4 is R19. These two elements then set the time constant of the peak detectors.

Loudspeaker amplifier

Approximately 250 mW of audio power is required for a speakerphone, which can easily be integrated on a bipolar IC chip. The loudspeaker amplifier uses two of the four high-current (200-mA) NPN transistors contained in a linear IC.

Figure 5 is the schematic of the speaker amplifier. Coming from the volume control, the telephone line signal is first amplified in a differential pair with an active load. A diode string (D9-D11) and resistor R21 are biased through D8/Q107 at a

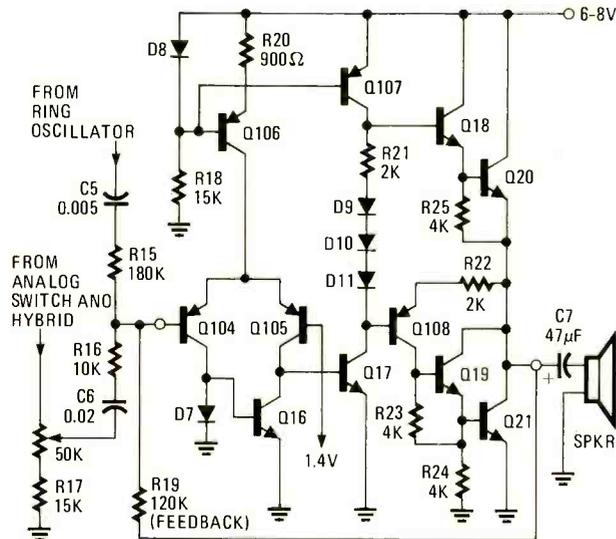


FIG. 5—SPEAKER AMPLIFIER circuit generates 250 mW of power.

current of 500 μ A. These four elements match the internal base-emitter diodes of Q18/Q20 and Q108/R22, so that the idling current of the output stage Q is also 500 μ A. The signal is fed into the diode string through Q17 and is amplified in the output stage. The closed-loop gain is set at approximately 5 by R19 and the input impedance.

Ring detectors and oscillators

The final circuit causes a ringing sound in the loudspeaker

Oscilloscopes gaining worldwide acceptance in computer field

As the mechanical design, layout and circuitry of oscilloscopes have improved so has their worldwide marketability. Hans Toorens, oscilloscope product manager for Philips Test & Measuring Instruments, Inc., believes that the broader range of applications and functions for an oscilloscope in computer servicing, as well as in other areas, has caused the market to expand both in the U.S. and abroad. He also believes oscilloscopes are destined to become the "workhorse" of the computer-service industry.

Purchasers of test equipment such as oscilloscopes have become increasingly sophisticated in their requirements—they use more precise parameters in judging an oscilloscope, looking for electronic measurement capability, cost reliability and its effectiveness both on the bench and in the field.

Connecticut judge dismisses radar-detector case


The city of Waterbury, CT, has probably experienced its last arrest for possession of a radar detector. This past June, Judge Norman Buzaid dismissed charges against Dr. Howard Rofsky who had been arrested for possession of a detector. Judge Buzaid termed the 1962 state ruling against radar detectors "ridiculous."

Most Connecticut courts have been reluctant to prosecute such cases, and Dr. Rofsky's case was only one of several lesser-known incidents. However, the Connec-

ticut decision came only days after the Supreme Court of the State of Virginia struck down a portion of that state's anti-radar law, declaring that a presumption of guilt in the statute was unconstitutional. The law will still be on the books, but police will now have a hard time proving the detector in the car was being used illegally. Virginia is the only state in the country to have a law against radar detectors.

The charge-coupled device, an idea come of age

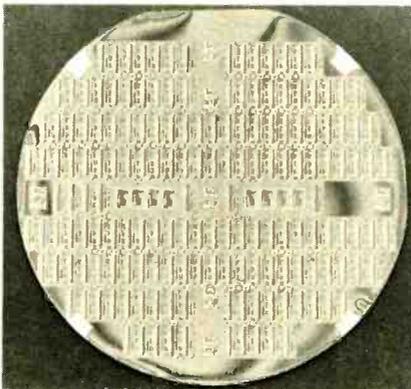In 1969 Bell Labs scientists Willard S. Boyle and George E. Smith devised the charge-coupled device (CCD), an invention that since then has inspired a great many technical papers but has now finally come of age.



CCD WAFER has a 3-inch diameter and contains 169 CCD devices.

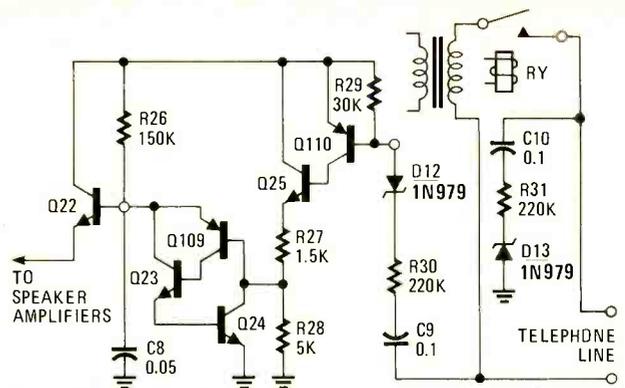


FIG. 6—RING DETECTOR AND OSCILLATOR generates a 1-kHz tone that varies between 60 and 150 volts P-P at a 20-Hz rate.

that eliminates the need for the bell. As shown in Fig. 6, the ring signal is picked up directly at the telephone line through a combination of Zener diodes, capacitors and resistors. In direct contrast to the voice signal, the ring signal has a very large amplitude that varies between 60 and 150 volts peak-to-peak at 20 Hz.

When the negative peak of the ring signal exceeds the Zener diode breakdown, Q110 and Q25 turn on. This powers up the relaxation oscillator made up of Q23/Q24 and Q109 through voltage divider R27/R28. The frequency of the relaxation oscillator is set by R26 and C8 at 1 kHz. The 1-kHz sound signal, which is modulated by 20 Hz, is fed into the speaker amplifier.

One large custom IC contains three of the four circuits discussed plus part of the control circuitry. As a result of using this type of IC, the Tridar speakerphone is smaller than the smallest telephone now offered and weighs less than the handset of a desk telephone. The custom integrated circuit is making its presence felt in consumer electronics. **R-E**

Scientists Boyle and Smith arrived at the idea for the CCD almost accidentally. They were looking for a semiconductor device that could control and handle data similar to magnetic bubble devices. (Bubbles store data in a very small space, making possible high-density data storage.) While at that time bubbles were fairly new devices, the semiconductor was well-known; the resulting invention was the CCD—a result of applying the principles of bubble devices to a semiconductor.

The CCD has three layers—one layer made of metallic electrodes, another of silicon crystal, and an insulating layer of silicon dioxide. Standard MOS processing techniques can be used to manufacture a CCD, which can then be used to perform many electronic functions now performed by larger, more complicated IC's.

Negatively charged electrons in the CCD can be moved about. The information (in the form of electrical charge packets) is stored in small areas or "wells" on the surface. Applying the desired voltage results in data transfer from one well to another. Since the amount of charge in a well can be varied continuously, this makes the CCD an analog device that can be used in analog communications transmissions. When the charge packets are digitized (i.e., the wells are either empty or full), the CCD can be used as a digital memory. If the charge packets are introduced *optically*, instead of electronically, with an image focused on the silicon surface, an imaging device results. It can then be used as an image sensor in an all solid-state television camera. **R-E**

How To Troubleshoot Digital Circuits

Isolating a fault in a digital circuit can be both difficult and time consuming if you don't know how to go about it. Here's an in-depth look at the faults, the right troubleshooting procedures and the test equipment to make it easier.

L. STEVEN CHEAIRS

MOST PROTOTYPE INSTRUMENTS HAVE A few design or fabrication bugs, and any system can malfunction due to a defective component. Unfortunately, these problems do not generally announce themselves in a way that makes them easy to identify. This is because a defect in the system can affect many other components and produce a number of secondary faults. This article will try to present a method that the average hobbyist can use to debug his own prototype or to repair malfunctioning logic circuits.

A list of digital troubleshooting equipment will be included. For each unit, we will try to outline when and where it should be used, noting its limitations. The reader will be led step-by-step through a few typical problems and we'll show various methods of obtaining the data required to pinpoint the fault. Since most of you only come into contact with TTL, CMOS and MOS devices, only these technologies will be covered.

Test equipment

Traditionally, when the individual components of a circuit were accessible, you could perform relatively simple tests to verify proper operation of each component by using a signal generator, voltmeter, ohmmeter, diode tester, transistor tester, tube tester, or an oscilloscope. All this equipment is defined as traditional troubleshooting equipment.

Now that a circuit element must be viewed as a little "black box," where the components are not accessible, a new troubleshooting philosophy must be adopted. Simply the IC must be tested for a complete circuit operation rather than just for a few characteristics such as capacitance, inductance, resistance and turn-on voltages. Note also that now we must observe complex digital signals, rather than simple circuit characteristics, to determine if the IC is functioning correctly. Complicating the situation further, you must consider a large number of inputs and outputs and compare the relationship of incoming signals to outgoing signals. This requires an intricate knowledge of many complex circuits. However,

I am not trying to scare you off but just trying to show why a new variety of test equipment was developed.

Multimeter and oscilloscope

The only two pieces of traditional test equipment that you will find some use for in digital troubleshooting are your *multimeter* and *oscilloscope*. With the multimeter you can check the power-supply voltage of a malfunctioning circuit. An oscilloscope can also find much use, especially if it is a dual-trace unit with triggered sweep. However, the older scopes will be next to useless because both time and frequency measurements cannot be made, and the amplitude, the Y-axis, is not generally calibrated, therefore preventing threshold measurements.

When viewing logic levels, absolute amplitudes are unimportant. A digital signal has three states. Only two of these states are used to convey information; they are logic 1 and logic 0 (the third state is designated as undefined). These states are defined by the threshold levels of the logic family; for TTL (*Transistor-Transistor Logic*) the low threshold is 0.4 volt and the high threshold is 2.4 volts. When the amplitude of the signal is less than 0.4 volt, it is considered to be at a logic 0 level; when it is above 2.4 volts it is at a logic 1 level; and when the amplitude is between 0.4 volt and 2.4 volts, the output is undefined. *Therefore, when you use an oscilloscope, all signals must be checked in order to determine if the data is at a valid logic level!* I have seen technicians spend days troubleshooting a circuit only to discover a problem that had been staring at them all along because they were only looking at waveforms and not logic levels.

Logic clip and probe

Two logic test instruments that almost anyone who works with logic has become familiar with are the *logic clip* and *logic probe*—both overcome the oscilloscope problem. When observing static or low-frequency data, the logic clip and logic probe function quite well; many units have a pulse stretcher and/or memory to

enable short pulses to be observed. The clip is simply piggybacked onto the IC; it will find its own power. If pin-to-pin contact is good, then the LED's will indicate the logic levels (where LED on = logic 1 and LED off = logic 0).

To use the logic probe, connect the two wires that exit from the end opposite the tip to the power supply (the red wire is positive and the black is negative). Some probes only have one indicator light; thus, a lit indicator is a logic 1 and an unlit indicator is a logic 0. Other probes may have two or more indicator lights; for instance, a light for the logic 1 state, another for the logic 0 state, and yet another light connected to a pulse stretch circuit or memory. To use the probe, simply touch a PC card run or the pin of one of the IC's and observe the indicators. The logic probe can detect pulses of short duration that have low repetition rates; these pulses would be difficult for an oscilloscope to detect. The probe should be used in one of two ways: First, you can let the circuit operate at its normal clock rate and monitor only key signal lines. Second, you can slow the system clock down using a low-frequency clock source so the logic changes are slow enough for the probe (or clip) to be useful.

Unfortunately, when you slow the clock down, the circuit will probably react differently—due to propagation delay. Many design problems that occur are due to the delaying of parallel signals; the glitches produced by propagation delays in two or more logic paths; or because of PC track inductance and capacitance (both of these are frequency sensitive).

The solution to these problems was provided by two instruments, the *logic comparator* and the *logic analyzer*. The logic comparator is a small hand-held unit having a cord protruding from one end, a 16-LED display and a cradle for a reference IC. The end of the cord contains an IC clip. The instrument has two modes of operation: First, connecting the IC clip to an IC and observing the LED provides you with a simple logic clip (when no reference IC is used and the mode switch is set to the clip position); second, insert-

ing the known good reference IC and setting the mode switch to the comparator position gives you a tester that will detect operational differences in the two IC's.

Since the reference IC is known to be good, it is assumed that any fault must be due to a bad IC; however, this is not always the case. Problems can occur when say a flip-flop or counter is being tested and the two IC's are not synchronized. The solution here is to use a logic pulser to reset the devices before testing. When testing memories or shift registers, attach the comparator for a long enough period for both IC's to acquire the same data.

The comparator does have some serious problems, however; it will not function properly with IC's that have a TTL input and a non-TTL output. Sometimes it will detect a problem that may not be caused by the test IC but by another IC, a bad clip connection, or a faulty circuit board. The worst problem the comparator has, and it shares this problem with all the other logic tools (with the exception of the current tracer), is that it cannot test any wired-OR/wired-AND connections. Thus, the whole set of open-collector IC's are unstable.

The logic analyzer is probably one of the most useful digital test instruments. Very simply, it monitors one or more signal lines until it observes a preprogrammed qualifier that is user-programmed. After detecting the qualifier, it loads its internal memory at a sample rate that is also user-determined; the rate may be synchronous or asynchronous to the data lines. It is also possible to wait a predetermined number of clock pulses (or amount of time) before or after the qualifier. The data is then displayed on a CRT screen as waveforms or truth tables. The logic analyzer also has difficulties testing wired-OR/wired-AND configurations.

The best solution to the wired-OR/wired-AND problem (as well as shorts and opens in the PC card) is to use a current tracer. This probe can be obtained in two forms. The first resembles a logic probe; one end has power leads and the other has a tip. The tip is not used to make electrical contact as with the logic probe; instead it contains a magnetic sensor used to monitor the field produced by current flow. Also, the probe can only detect low-impedance faults.

To detect a wired-OR/wired-AND fault, simply place the probe near the pull-up resistor and adjust the gain control until the indicator lamp lights up (see Fig. 1). Next, place the probe to each output pin of the open-collector gates—only the defective gate will cause the indicator to light up. Also, when a low-impedance fault exists between two gates, the current tracer and a logic pulser can be used as quick diagnostic tools (the logic pulser should be used on all faults responsible for abnormal current flow if the current

flow does not provide enough stimulation to use the current tracer). If a signal line between IC's is shorted to ground, place the logic pulser on the foil trace midway between the IC's. Next, use the current

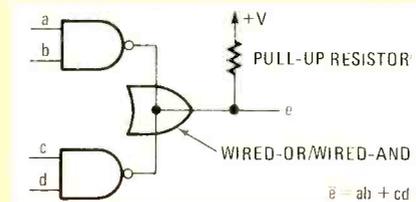


FIG. 1—WIRED-OR/WIRED-AND configuration is formed by connecting the outputs from open-collector gates and connecting a pull-up resistor.

tracer to follow the current to the defective component. A solder bridge may also be detected using the current tracer. Start with the gate that is sourcing the current and follow the current flow until you find the short. Another useful application is when a buffer is driving numerous inputs and one input is shorted to ground. Adjust the current tracer at the output of the buffer and then touch the probe to each input; the one that causes the indicator to light is the defective gate.

Logic pulser

A logic pulser is simply a pulse generator that provides either a single-pulse or a continuous-pulse stream. To use a logic pulser, place the tip of the pulser to the input of the suspected logic element. Next, press the trigger button and the logic element will be forced into its opposite logic state. With most conventional signal generators, either circuit compo-

nents have to be unsoldered and/or the foil trace has to be cut. Most pulsers will provide around 700 mA of current, which is more than sufficient to force the IC to change states. The pulser must generate a very narrow pulse to prevent any IC damage that might be caused by applying too much current. The pulser, as should all other test equipment, should have a high-impedance input to prevent adversely affecting normal circuit operation while using it.

Beyond this collection of equipment all you need is a set of IC test clips and jumper wires. It should also be emphasized that all the equipment described above will be required in any single application. The scope is a general-purpose instrument that can be used in almost any application, whereas the voltmeter may find use only in specific cases—such as checking the power supply. The logic clip should only be used for checking static or low-frequency signals. The logic probe also works best at low-frequency levels, but can be used on higher-frequency circuits if it is used just to monitor key control lines. The IC comparator is useful only for testing a restricted number of the available IC types (because of the need for a reference IC). Both the pulser and current tracer are very valuable troubleshooting tools. The logic analyzer is unquestionably a valuable tool—especially when used with systems that have parallel information, such as synchronous counter strings, address buses, data buses, etc.

IC technologies

To troubleshoot effectively, a knowledge of the individual IC's and the logic

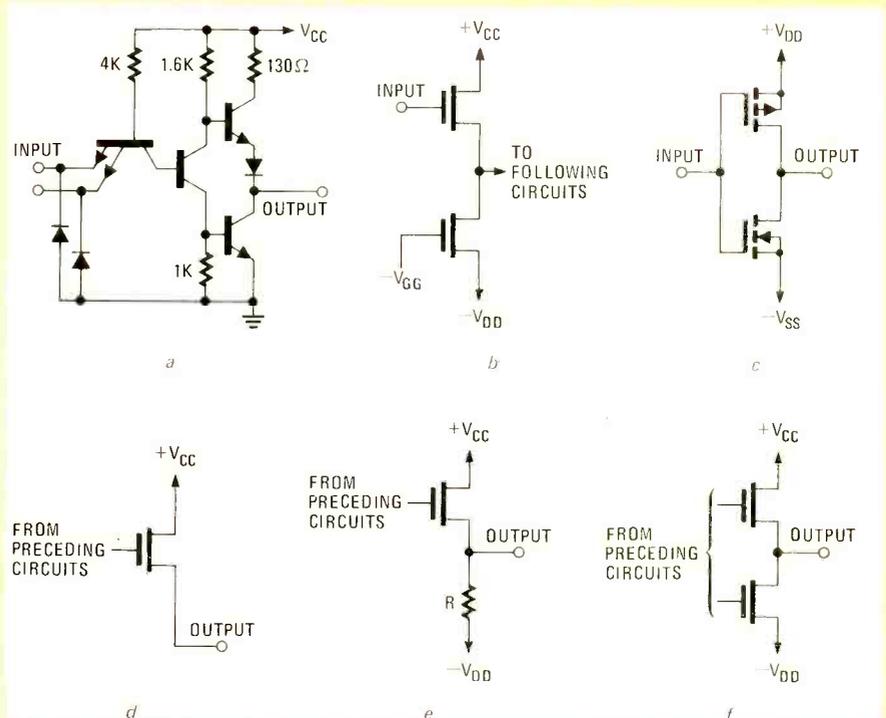


FIG. 2—INPUT AND OUTPUT CIRCUITRY FOR TTL, PMOS, CMOS and MOS logic families. Input circuitry for a 2-input TTL NAND gate is shown in a. Input of PMOS gate is shown in b. Circuit of a CMOS inverter is shown in c. Open-drain MOS output circuit is shown in d. Resistor pull-down MOS output circuit is shown in e. Push-pull MOS output circuit is shown in f.

family associated with them is required. Thus, the troubleshooter must have a library containing the pinouts and functional truth tables for all the common IC's, plus some not so common ones. Also, a firm understanding of the IC's input and output characteristics for the logic family is required. Figure 2 shows the input and output circuitry associated with TTL, CMOS and MOS logic families.

This article will not discuss such design characteristics as propagation delays, set-up times, power supplies, filtering, bypassing, fan-in/fan-out, etc. When discussing specific logic families, only threshold levels and failure modes will be examined. Furthermore, emphasis will be placed upon poor PC layout, with less emphasis on defective components. This is because more than 90% of the problems are a result of design and fabrication failures and less than 10% a result of faulty components. Of course, the exception to this rule is the digital circuit that experiences a logic failure after proving itself in operation for an extended period. In this case, the odds are in favor of a defective component.

I will assume that you have access to IC pinout information and description of all the IC functions. If not, such information is available from many sources. The most common IC's used by hobbyists are of the MOS, CMOS, or TTL technologies. For the MOS types—NMOS and PMOS—you should consult the individual components data sheet for switching-threshold levels. For most MOS/CMOS IC's that are TTL-compatible, the maximum low-level output, V_{OL} , with no noise at the input and assuming only capacitive loading, is given as $V_{OL} = V_{SS} + 0.01$ volts. The minimum high-level output, V_{OH} , for the same conditions, is given as $V_{OH} = V_{DD} - 0.01$ volts. For optimum performance, the high-level input should equal V_{DD} and the low-level should equal V_{SS} . Due to the high DC noise immunity of MOS/CMOS devices, an acceptable logic 1 is $V_{DD} - 0.3(V_{DD})$ and a logic 0 is $V_{SS} + 0.3(V_{DD})$. Therefore, as a worst case, V_H may equal 3.5 volts, and V_L may equal 1.5 volts, using a 5-volt power supply. Also, variations in the power-supply potential, V_{DD} , will directly affect the threshold point.

Transistor-Transistor Logic (TTL or T²L) can be subdivided into five families—regular, low-power, low-power Schottky, Schottky and high-speed. Table 1 shows threshold-level comparisons of each type. In this table, both the absolute and typical levels are shown; when testing use only the absolute levels. Thus, for standard TTL the low-level threshold is 0.4 volt and the high-level threshold is 2.4 volts (the area between 0.4 volt and 2.4 volts is undefined).

The failure modes for these logic families are similar, although some logic families may be more prone to one particular

type of failure. Basically, there are only five kinds of failure: (1) failure of the internal logic; (2) the input/output is shorted to ground; (3) the input/output is shorted to V_{CC} ; (4) the input/output is open; and (5) there is a short between two or more of the IC pins.

The first failure, that of internal logic, results in erratic circuit operation. Therefore, the output of the IC will not be predictable. This failure will block normal signal flow and most assuredly has a catastrophic effect upon circuit operation.

The second and third failure modes, the input/output being shorted to ground or to V_{CC} , do not qualify as catastrophic

will perform normally, but when they are driven into alternate states, the output will go low. Note that since the outputs must dissipate more power under these conditions, at some point a catastrophic failure may occur due to excessive heat buildup.

A troubleshooting example

Whenever you troubleshoot, it is mandatory to narrow the problem down as much as possible by observing the symptoms. By using the controls and displays provided on the front panel of the malfunctioning equipment, isolate the problem to as few circuits as possible. Obtain all the written information available, such

TABLE 1—THRESHOLD LEVELS for TTL logic families. Values are given in volts.

	Logic Level	7400	74L00	74LS00	74S00	74H00
V_L	Typical	0.2	0.2	0.35	0.35	0.2
	Maximum	0.4	0.4	0.5	0.5	0.4
V_H	Typical	3.4	3.2	3.4	3.4	3.4
	Minimum	2.4	2.4	2.7	2.7	2.4

failures since in many cases normal circuit operation continues with only occasional circuit malfunctions. In most cases, however, some expected system operations will not exist and thus can manifest themselves as catastrophic failures. The actual effect of this type of fault is that an input/output will be held high or low, depending upon the failure, and thus prevent normal circuit operation.

The fourth failure, open input/output, generally will be due to a bad internal wire bond between the IC pin and the silicon wafer. When the problem is due to an open input bond, then no signal will be delivered to the silicon wafer. Thus, the input will float at some undefined level. Note also that there will be no effect upon the signal source driving this input. An open bond on an output will cause the IC inputs being driven by that output to float (high in the case of TTL). For both TTL and DTL, a floating input drifts to about 1.4 volts to 1.5 volts. Therefore, an open bond on an output (for TTL or DTL) forces all corresponding inputs to a logic 1 level (even though this is below the valid logic 1 level).

The final failure, a short between two pins, is one of the harder cases to analyze. When two pins are shorted, two outputs that drive those lines are placed in opposition; i.e., they both will attempt to pull the other high or low. These outputs may be on the bad IC (when two outputs are shorted) or external to the IC (when two inputs are shorted), or there may be only one output on the IC (when an output and input are shorted together). In the case where one output attempts to go high and the other tries to go low, excessive current will be drawn through both outputs. The end result is that the short will pull both outputs to a low state. Therefore, when both outputs are driven low or high simultaneously, the circuit

as service manuals, operator's manuals and schematics. *Look and think before touching!* Remember you have enough problems now, do not create any more by hasty actions. A well-written service manual can provide information about key signals that may aid in isolating the failure to a single circuit.

When troubleshooting a complex system, such as a computer that contains hundreds of IC's, the first step is to isolate the malfunction to as few IC's as possible. Most of your time will be spent searching for the problem, not fixing it. Next, by using key signals and the proper test equipment, zero in on the faulty IC.

Let's look at a typical circuit containing a few problems. To enhance your skills for both general-purpose repair work and prototype testing, two separate troubleshooting paths will be followed: The first is to assume that the circuit has only one failure at a time and it will be due to a faulty component (this is basically what we see when a proven circuit fails); second, in order to simulate design, layout and fabrication problems, several concurrent problems are shown to exist.

The circuit is shown in Fig. 3 This circuit is one-half of the logic used in building a limited graphic terminal that uses subjective color. Subjective color, unlike standard color, can be displayed on a black-and-white monitor screen—if you stay within its limitations. The circuit board contains the video-output amplifier, sync generation circuits, composite blanking circuit, character generator, subjective color circuits, and the computer I/O circuits.

The schematic (see Fig. 3) shows six circuit failures. The first is an open circuit at the output of the video multiplexer. The symptom observed on the monitor is: No picture, with a white raster being displayed. This immediately

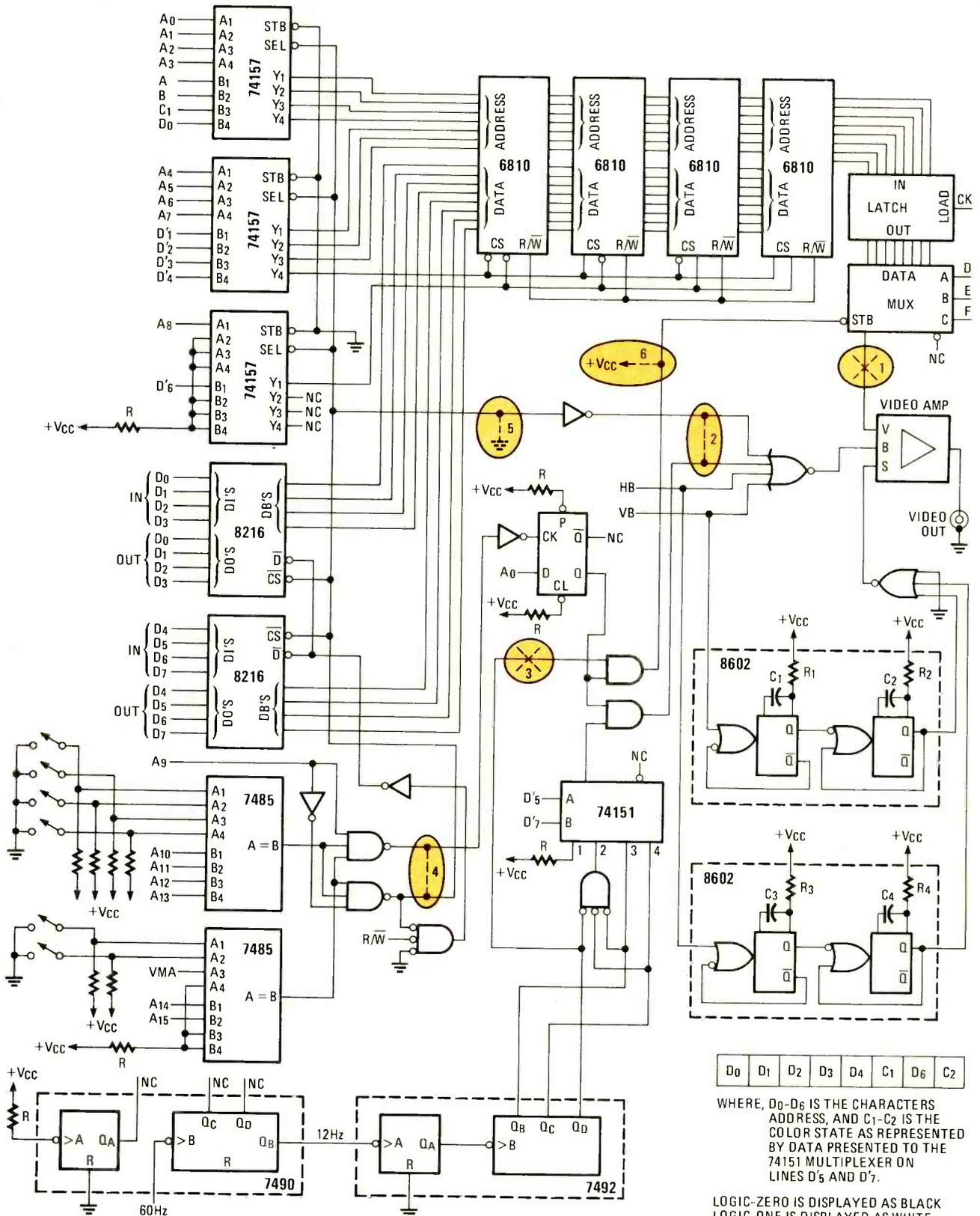


FIG. 3—LOGIC CIRCUIT showing six possible malfunctions.

suggests you should check the signal path between the video amplifier and the multiplexer, because both blanking and sync seem to be working. Since this is a high-frequency signal with only one line, use the oscilloscope. If there is no signal on that line, check the strobe input using a logic probe (this input should be a logic 0 or be checked at a low frequency). Since

this input checks OK, next use the logic analyzer or oscilloscope to verify that the 8-bit data lines and 3-bit control lines are active—they should be. After verifying these inputs, the only possible problem could be an open bond inside the multiplexer on the output.

The second fault is between two input pins of the composite summing circuit;

this fault causes the color-blanking and computer-access blanking outputs to be tied together. The symptoms of this failure are (1) the color cannot be observed, and (2) erratic images are displayed during computer access. During normal non-color operation when the computer is not loading a new character pattern into the

continued on page 87

BOOLEAN ALGEBRA RULES

▲ symbol indicates a logic variable. This can be either a logic 0 or a logic 1 level.

1	$0 + \Delta = \Delta$
2	$1 + \Delta = 1$
3	$\Delta + \Delta = \Delta$
4	$0 + \bar{\Delta} = \bar{\Delta}$
5	$0 \cdot \Delta = 0$
6	$1 \cdot \Delta = \Delta$
7	$\Delta \cdot \Delta = \Delta$
8	$\Delta \cdot \bar{\Delta} = 0$
9	$\overline{(\bar{\Delta})} = \Delta$
10	$\Delta + Y = Y + \Delta$
11	$\Delta \cdot Y = Y \cdot \Delta$
12	$\Delta + (Y + Z) = (\Delta + Y) + Z$
13	$\Delta (YZ) = (\Delta Y) Z$
14	$\Delta (Y + Z) = \Delta Y + \Delta Z$
15	$\Delta + \Delta Z = \Delta$
16	$\Delta (\Delta + Y) = \Delta$
17	$(\Delta + Y) (\Delta + Z) = \Delta + YZ$
18	$\Delta + \bar{\Delta} Y = \Delta + Y$

BOOLEAN SIMPLIFICATION

Simplify $P + X + \bar{X}$. Using Rule 4 from above table, $P + X + \bar{X}$ reduced to $P + 1$. Using Rule 2 reduced $P + 1$ to 1. Therefore, $P + \bar{X} + X$ is always equal to a logic 1.

Simplify $PQ\bar{Q}L$. By Rule 8 of above table, $Q \cdot \bar{Q} = 0$. Therefore, $PQ\bar{Q}L = P \cdot 0 \cdot L$. By Rule 5, $P \cdot 0 \cdot L = 0$. Therefore, $PQ\bar{Q}L = 0$.

Simplify: $\bar{M} + C\bar{S} + F$. Use Rule 8: $C\bar{S}$; $\bar{C}\bar{C} = 0$. Use Rule 5: $0 \cdot S = 0$. Expression becomes $\bar{M} + 0 + F$, which reduces to $\bar{M} + F$. Note we should not apply Rule 4 of boolean table $\bar{M} + F$ because variables are not identical. The answer is $\bar{M} + F$ or an OR gate with inputs \bar{M} and F .


LAW OF PRODUCTS

The law of *Products* is also called the law of *Intersection*. This law explains the behavior of an AND gate. It follows Rules 5 and 6 from the above table.




According to Rule 6 ($1 \cdot \Delta = \Delta$), if we apply a logic 1 and the variable Δ to the input of an AND gate, the output will be equal to the variable Δ . According to Rule 5 ($0 \cdot \Delta = 0$), if we set the variable Δ equal to a binary 1, the output of an AND gate is still 0.

For a pulsed input:

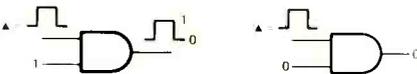


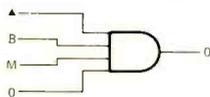Consequently for a four input AND gate, applying Rule 5 of the boolean algebra table:



$\Delta \cdot B \cdot M \cdot 0 = 0$. It is obvious that in the preceding AND gate expression if any of the variables is a logic 1 level, but either of the inputs is zero, the output will be 0.

If the input 0 becomes 1, then:

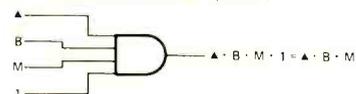


THE LAW OF UNIONS

This law pertains to the OR gate and is related to Rule 1 and 2 of the boolean table.



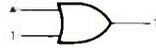
According to Rule 1 ($0 + \Delta = \Delta$), if one of the inputs of an OR gate is 0 and we apply the variable Δ to the other input, the output will be the variable Δ . According to Rule 2 ($1 + \Delta = 1$),



if we apply a 1 and the variable Δ to the inputs of an OR gate, the output will be 1.

LAW OF TAUTOLOGY

The known *Law of Tautology* applies to Rules 3 and 7 of the boolean table. Rules 3 and 7 apply to AND gates and OR gates. Using this law, simplification of long algebraic expressions becomes simple. The rules merely state that equal variables in an equation should be omitted. Example: Simplify the equation ($M = \Delta + \Delta + K + L$). It is obvious that the variable Δ repeats twice. By Rule 3, the equation simplifies to $M = \Delta + K + L$.

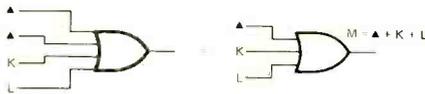

THE LAW OF COMPLEMENTS

If a logic signal and the complement of this logic signal is applied to a logic gate the resulting output is 1 or 0 depending on the logic gate being used. The law of the complement is stated in Rules 4 and 8 of the boolean table. Let's apply this rule to an OR gate.




According to Rule 4 ($\Delta + \bar{\Delta} = 1$), if one of the inputs of the OR gate is logic 1 ($\Delta = \bar{\Delta}$) and the other input is 0 ($0 = \bar{\Delta}$) the output will be 1. Example: Pulsed



According to Rule 8 ($\Delta + \Delta = \Delta$), if one input to an AND gate is variable Δ and the other input is 0, the output of the gate will be 0.

THE LAW OF DOUBLE NEGATION

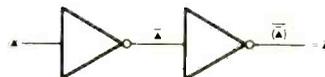The Law of Double Negation is expressed by Rule 9 of the boolean algebra table. This law states that feeding the negation of a variable through an inverter produces the original variable.



Complementing a signal an even number of times produces the original signal.


FLIP-FLOPS

A digital logic circuit able to memorize by storing logic levels. A flip-flop has two stable

states: It will remain in either set or reset state until its state is changed by external signals. The data stored in a flip-flop can be quickly checked by using an oscilloscope or meter to detect the state of its output. There are three basic types of flip-flops.

- 1 The RS
- 2 The D type
- 3 The JK

The logic symbol for an RS flip-flop is

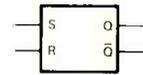


The inputs are S and R. The outputs are Q and \bar{Q} . Application of a logic 1 level on the S input will make the Q output go to a logic 1 level and the \bar{Q} output go to a logic 0 level. If the logic 1 level is applied to the R input, the output levels are reversed. The unused input must be held at a logic 0 level.

INPUTS		OUTPUTS	
R	S	Q	\bar{Q}
High	Low	Low	High
Low	High	High	Low
Low	Low	Unchanged	
High	High	Not Permitted	

When the S input is 1 and the R is 0 the flip-flop is reset. When the S is 0 and R is 1, it is set. All the other input combinations produce ambiguous or race states.


The D-type flip-flop logic symbol.

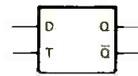

The D-type flip-flop generally behaves like the RS flip-flop but the main difference is that a low-to-high transition must be applied to the T input for the D flip-flop to toggle and store information.

INPUT		OUTPUT	
D	T	Q	\bar{Q}
Low	Low	Previous state	
Low	High	Low	High
High	Low	Previous state	
High	High	High	Low


The JK flip-flop symbol

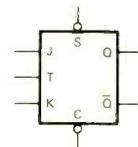


The S and C inputs presets the JK flip-flop to a desired state before another operation is begun. The S and C inputs are referred to as asynchronous inputs because they don't require a transition on the T input. The J and K inputs only affect the Q and \bar{Q} outputs when a transition occurs on the T or clock input. If the J input is 1 and the K input is 1, the flip-flop will reset from the previous state in the presence of a low-to-high transition on the T input. To set the JK flip-flop, apply a 1 to the J input and a 0 to the K input, then apply a low-to-high transition (clock pulse) to the T input. This operation is referred as synchronous with the clock operation.

THE NOR GATE

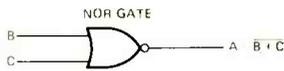A logic circuit with two or more input capable of resolving the equation $A = \overline{B + C}$. The NOR gate is a combination of an OR logic gate followed by an inverter.



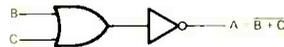The NOR gate could be constructed using an OR gate followed by an inverter.




The operation of a NOR gate is represented in the following truth table.


Input		Output
B	C	$A = \overline{B + C}$
0	0	1
0	1	0
1	0	0
1	1	0

Notice that the NOR table is the exact opposite or complement of the OR truth table. Summary: The 2 input NOR gate produces an output when both of the inputs are logic 0 level. If either of the inputs is 1, the output is always a logic 0 level.

Pulse Behavior

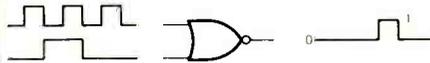

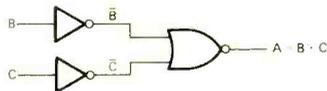A NOR gate using inverters in the input will act as an AND gate.



Truth Table for inverted input NOR gate shown above.

B	C	\overline{B}	\overline{C}	A
1	0	0	1	0
0	1	1	0	0
0	0	1	1	0
1	1	0	0	1

DUALITY OF LOGIC GATES

Gates can provide different functions depending on the assumed reference logic level applied to the input. There are two widely used types of combinational logic levels used in present logic circuits. These are known as *positive logic* and *negative logic*.

POSITIVE LOGIC LEVELS

Input	Output
Logic 1 = +5 volts	+5 volts
Logic 0 = 0 volts to +0.2 volts	0 volts to +0.2 volts

The logic 0 is relatively close to the 0 or ground reference level but in practical gate design the 0 reference is usually a few tenths of a volt above ground level.

NEGATIVE LOGIC LEVELS

Input	Output
Logic 1 = 0 volts to +0.2 volts	0 volts to +0.2 volts
Logic 0 = +5 volts	+5 volts

Truth Table for Positive Logic 2-input AND gate

Voltage Table

Input		Output
B	C	A
0V	0V	0V
0V	+5V	0V
+5V	0V	0V
+5V	+5V	+5V

Truth Table

Input		Output
B	C	A
0	0	0
0	1	0
1	0	0
1	1	1

Compare above Truth Table with Truth Table below for a negative logic 2-input AND gate.

Negative Logic AND gate.

Voltage Table

Input		Output
B	C	A
0V	0V	0V
+5V	0V	0V
0V	+5V	0V
+5V	+5V	+5V


Truth Table

Input		Output
B	C	A
1	1	1
0	1	1
1	0	1
0	0	0

Notice that the Truth Table for the negative logic AND gate is exactly opposite to the Truth Table for the positive logic AND gate. The negative logic AND gate acts as a positive logic OR gate.


Consequently an AND gate can provide the OR function and an OR gate can provide the AND function by selecting positive or negative logic level assignments.

Positive logic AND gate

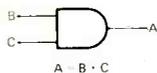


$$A = B \cdot C$$

Negative logic equivalent of AND gate.

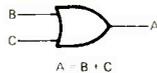


$$A = B + C$$

Positive logic OR gate

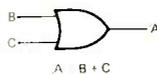


$$A = B + C$$

Negative logic equivalent of OR gate.

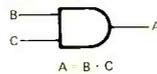


$$A = B \cdot C$$

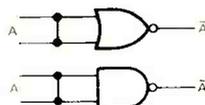Flexibility in implementation of the basic gate functions. NOR gates and NAND gates can be used to implement any of three basic logic functions. Example: By connecting all the inputs of a NOR or NAND gate together we can implement an inverter.



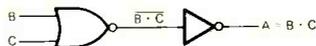By connecting an inverter in the output of a NOR gate, we can implement an OR gate. (Same applies for a NAND gate.)



BOOLEAN ALGEBRA


Is the mathematical method of analyzing logic circuits. Boolean equations describe the operation and provides the mathematical tool for the manipulation of logic circuits. For example, draw the logic circuit that solves the boolean equation $A = (B+C) + (M+D)$: The expression indicates that there are two OR gates being OR'ed by another single OR gate: Analysis: Draw the symbol for the first member of the equation. $(B+C)$:



Then draw the symbol for the second member of the equation $(M+D)$.



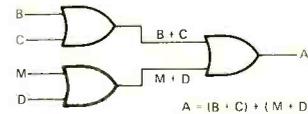Use a single OR gate to combine the two OR gate outputs as required by the indicated + symbol.




Draw symbol for the second term of the equation $(M+D)$.


Draw the logic circuit to solve the boolean equation $A = (B+C) \cdot (M+D)$.

The first term $(B+C)$ of the equation indicates an OR gate with inputs B and C.

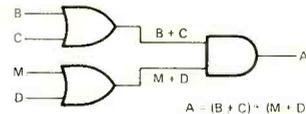Combine the two OR gate outputs using a single AND gate as required by the multiplication.




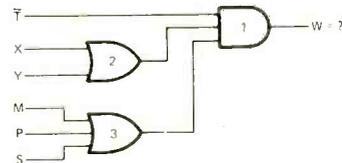Write the boolean algebraic expression from the given logic circuit.



First write the expression describing the output of gate 2. This is an OR gate, therefore, the expression is $X+Y$. Secondly write the output equation for gate 3. This is another OR gate, so the expression is $M + P + S$. Notice that the algebraic expressions are being AND'ed by gate 1. Consequently the output expression so far is $(X+Y) \cdot (M+P+S)$. Input T could have been included anywhere in the equation because it is being AND'ed by gate 1 with the other two equations. The complete output equation is: $W = (X + Y) (M + P + S) \overline{T}$.

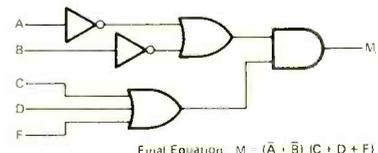
Write the boolean equation for the logic diagram.



Final Equation $M = (\overline{A} \cdot \overline{B}) (C + D + F)$

AND GATE

Logic circuits with two or more inputs and a single output capable of resolving an output with combinations of input variables. The two-input AND gate resolves the equation $A = BC$. The output (A) is expressed in terms of the two variables (B) and (C). The expression $A = BC$ does not imply multiplication but rather (A) is the result of quantity (B) AND quantity (C) presented at the input. AND gate symbol

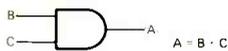

The operation of the AND gate is better represented by the use of a Truth Table that indicates the output for the various input combinations.

Truth Table for 2-input AND gate:


IN		OUT
B	C	A
0	0	0
1	0	0
0	1	0
1	1	1

The AND gate performs binary multiplication.

MULTIPLICATION TABLE	
0	0 = 0
1	0 = 0
0	1 = 0
1	1 = 1

The total number of possible input combinations for a gate with an even number of inputs is given as (inputs)² = outputs. For a two input AND gate; 2² = 4. The truth table then contains 4 possible input combinations. Summary: A two-input AND gate gives an output only when both inputs are logic 1.

For a pulse input:

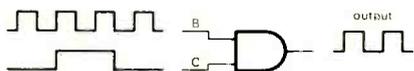

Notice that the AND gate produces 2 output pulses out of 4 input pulses arriving at the B input because the duration of pulse C is exactly twice the total duration of input pulses B.

Algebraic equations. Example: For $A = W \cdot TX \cdot MPS$. Using AND gate




THE INVERTER

A digital gate that inverts the input signal. It is also known as a complementary gate because the output is inverted in relation to the input. The inverted output is written with a bar over the inverted variable.




The inverter has only one input connection and one output connection.

For a pulse input:

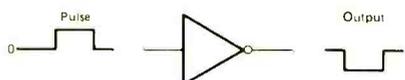

CASCADED INVERTERS

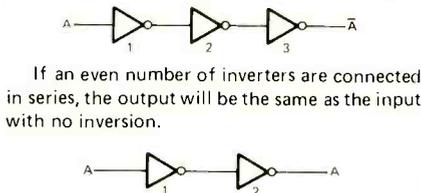If an odd number of inverters are connected in series, the output will always be the negation of complement or the input variable.



THE OR GATE

Logic circuit with two or more inputs that provides an output when any input is a logic (1). The two input OR gate resolves the equation $A = B + C$. The output is expressed in terms of either variable B or C acting on the input. The expression $A = B + C$ does not imply addition but rather A is the result of either B or C acting on the input.



The operation of the OR gate is better represented by the use of a Truth Table that indicates the output when the inputs are modified by (1) or (0):

2 INPUT OR GATE

INPUT		OUTPUT
B	C	A
0	0	0
0	1	1
1	0	1
1	1	1

Below is a 3-input OR gate Truth Table.

INPUT			OUTPUT
A	B	C	D
0	0	0	0
1	0	0	1
1	1	0	1
1	1	1	1
0	0	1	1
0	1	1	1
0	1	0	1
1	0	1	1

The number of inputs determines the number of combinations in the same manner as for the AND gate: input = combinations - 1. Example: 3² - 1 = 8.


Note: The equation; inputs² = combinations - 1; is for an ODD number of inputs. Use inputs² = combinations for an EVEN number of inputs. Example: An OR gate with 2 inputs has 2² = 4 possible input combinations. An OR gate with 5 inputs has 5² = 25 - 1 = 24 possible input combinations.

The OR gate equation satisfies the rule of binary addition.


LOGICAL ADDITION TABLE

0 + 0 = 0
1 + 0 = 1
0 + 1 = 1
1 + 1 = 1

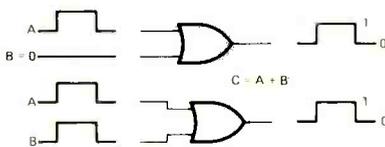Note: Binary addition and logical addition are not EQUAL. Summary: The OR gate gives an output when any input is a logic one. Output is zero when all inputs are zero.



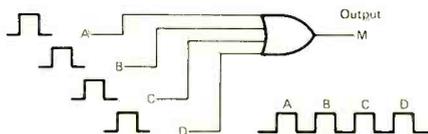The OR GATE preserves the individual characteristics of pulses arriving at the input.



Note: Each output pulse has the same time interval at the output as it had in the input. If there is time coincidence at the input, the output pulse will be equivalent to the longest pulse at the input. Example:




THE NAND GATE

The NAND (NOT-AND) gate is the combination of an AND gate and inverter. The operation of a NAND gate is represented by the equation $A = \overline{B \cdot C}$ and is read A is the result of B and C operating at the input of the NAND gate but inverted at the output. The solid bar over $B \cdot C$ means inversion.



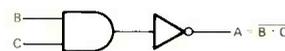
The NAND gate could be constructed by using an AND gate followed by an inverter.



The operation of a 2-input NAND gate is easily represented by a truth table form.

INPUT		OUTPUT
C	B	A = B · C
0	0	1
1	0	1
0	1	1
1	1	0

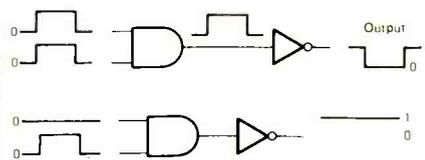
Note: The NAND gate truth table is the complement of the AND gate truth table. Both inputs must be at a logic 1 level to produce a logic 0 output. Pulse behavior:



Non-coincident input pulses have no effect on the output of a NAND gate. The output always stays at logic 1 level. Coincidence at input of logic 1 level pulses produces a negative going pulse at the output.



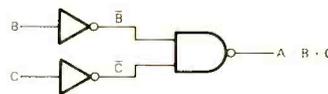A NAND gate with inverters connected to the inputs will act as an OR gate.



New Breakthrough In Audio Tape

New metal particle tape for recording provides increased output level, reduced distortion, added high-frequency response and improved S/N ratio.

LEN FELDMAN
CONTRIBUTING HI-FI EDITOR

THE HISTORY OF CASSETTE TAPE RECORDING has been marked by many minor and a few major technological breakthroughs. When the cassette format was originally introduced in 1964 by the Philips Company of the Netherlands, it was not much more than a tape recording medium suitable for low-fi voice recording. Over the years, there have been improvements both in tape hardware (i.e., better electronics, more efficient tape heads, smaller tape-head gaps and such noise-reduction techniques as Dolby and dbx) and, equally significantly, in tape software.

Initially all tapes used ferric-oxide particles suspended in a binder and coated onto a plastic base material. Later on, chromium dioxide (CrO₂) and other particles (such as cobalt-doped ferric oxide)

appeared. These formulations primarily improved high-frequency performance, but also the signal-to-noise capability of the cassette recording medium, since they could produce higher maximum-output levels at high frequencies before reaching magnetic saturation.

To understand how these improved tapes worked, it is necessary to examine a typical hysteresis loop associated with magnetic recording. Figure 1 shows such a hysteresis loop. Coercivity, plotted along the horizontal axis, demonstrates how difficult it is to magnetize (or demagnetize) a given tape formulation. Remanent magnetization (also known as remanence) indicates how strong such a magnetization can be. The area shown in the upper-left quadrant of Fig. 1 helps us in judging any particular tape formulation.

If the area in the upper-left quadrant is redrawn with what magnetic tape engineers call "frequency load lines," two things become apparent (see Figs. 2 and 3). In Fig. 2 typical load lines were drawn for 20 kHz and 200 Hz. The lower partial hysteresis curve might be considered typical of ferric-oxide-particle tape; the upper curve could typify the characteristics of chrome tape or one of the treated ferric compounds. Note that increasing the remanent magnetization has a profound effect upon high-frequency performance but little effect upon performance at lower frequencies.

Conversely, Fig. 3 shows that if the coercivity of a given formulation is improved compared with a reference tape, the tape's low-frequency performance is improved significantly while its high-frequency performance remains virtually the same. Clearly, then, an ideal tape is

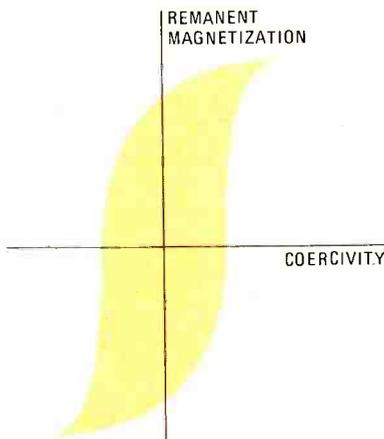


FIG. 1—HYSTERESIS LOOP is obtained by plotting remanence versus coercivity.

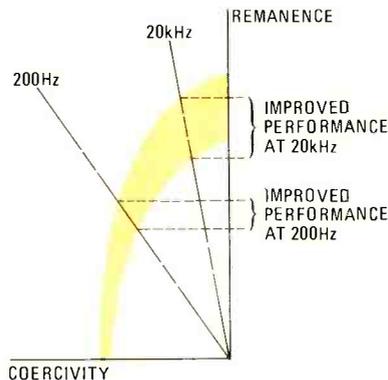


FIG. 2—INCREASING REMANENCE improves high-frequency performance.

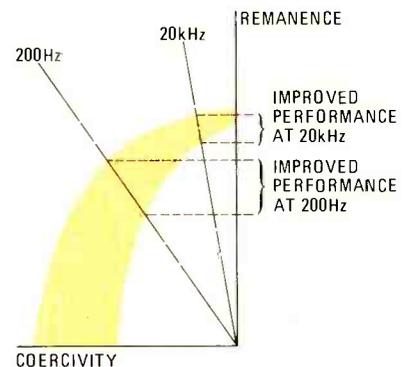


FIG. 3—INCREASING COERCIVITY improves low-frequency performance.

one in which both the remanence and the coercivity are greater than in any of the standard tapes.

Thirteen years of research

In 1965, barely more than a year after the cassette tape format was introduced commercially, the 3M Company, a leading magnetic tape manufacturer, began a long-term research project in search of a better magnetic tape medium. The project centered around using fine metal particles as the magnetizing medium rather than metal-oxide particles. Seven years later, in 1972, samples of a tape then known as XRM-4 were distributed to several tape equipment manufacturers. Between 1972 and 1976, the performance capabilities of the new tape were verified by many manufacturers, but problems related to its economical mass production prevented it's being marketed. There were also other problems. Available state-of-the-art tape recorders could not take full advantage of the new tape's capabilities. Existing record and erase tape heads were incapable of recording program material onto the new tape.

By 1976, 3M Company licked some of the production problems, and became convinced that the metal-particle tape had economic possibilities. At that point, the name of the tape was changed to *Metafine*, a name that is 3M's own registered trademark for the new tape. In 1977, adequate recording and erase heads were developed for use with Metafine tape, and recording heads became commercially available by the end of the year. By late 1977 and early 1978, equipment manufacturers were able to build prototype tape decks to fully demonstrate the capabilities of Metafine tape.

By the end of 1978, at least one tape-deck manufacturer (Tandberg of America, Inc.), and quite possibly several others, will be marketing stereo cassette decks that can handle both conventional oxide-particle tapes as well as the new metal-particle tapes.

There are indications that many other tape manufacturers have the capability for making pure metal-particle tapes. Fuji, for example, recently announced that they had come up with a metal-particle tape and would be able to produce it if they perceive a demand and greater availability of machines that can use the tape. Though TDK has not officially announced marketing dates for any metal-particle tape, they are quick to admit that they, too, know how to make the tape and could bring it to dealers' shelves just as soon as they saw a demand for it. Maxell, on the other hand, has indicated that they have no plans to market a metal-particle tape at this time. They maintain that the looming digital tape recording techniques would more than offset any advantages in the use of metal-particle tape. BASF is also in no rush to introduce metal-particle tape (though a spokesman for the compa-

ny says that the technology for producing such tape is well within the skills and experience of this German-based company), citing lack of standardization as one of the reasons for their reticence.

Indeed, lack of standardization may well be one of the things which impedes the proliferation of metal-particle tape. While 3M has proposed that 70-microsecond playback equalization be used for the new tape, others feel that a 50-microsecond standard would take best advantage of the new tape's capabilities. Nor is there complete agreement regarding the



FIG. 4—METAFINE TAPE will be packed in C-60 and C-90 cassettes.

other parameters, such as coercivity and retentivity. Unless manufacturers of tape, worldwide, can agree upon standards for the new tape (and thereby enable tape deck manufacturers to proceed in an orderly development of equipment suitable for use with the new tape), metal-particle tape may run into the same sort of resistance that consumers showed with respect to the multiplicity of 4-channel

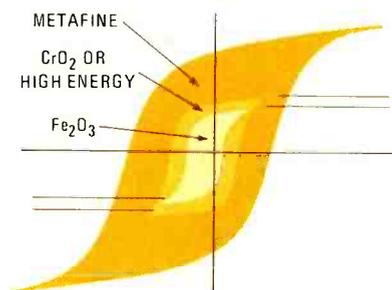


FIG. 5—HYSTERESIS CURVES for Metafine, chromium-dioxide, and ferric-oxide tapes are superimposed.

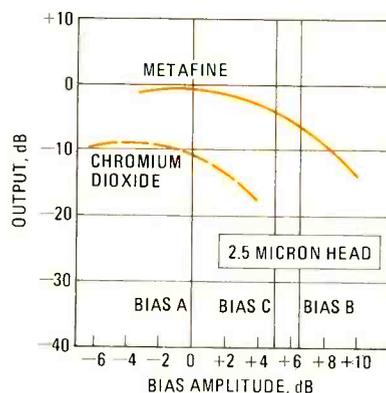


FIG. 6—OUTPUT LEVEL of Metafine versus chromium-dioxide tape.

recording systems that were popular just a few years ago. The 3M Company must nevertheless be credited with being first to announce the availability of metal-particle tape for use in cassette tape recording. The tape packaging will be similar to that used in 3M's other popular cassette tape formulations (see Fig. 4), and tape lengths will be in the popular C-60 and C-90 packages.

Comparing Figs. 2 and 3 with Fig. 5 gives you some idea of Metafine tape's tremendous improvement in performance and output levels. Figure 5 shows three hysteresis curves; the curve for Metafine tape is superimposed on that for chromium-dioxide or "high-energy" oxide tapes, as well as on a smaller curve representing the practical limits of earlier ferric-oxide tapes. The dramatic increase in the upper-left quadrant area of Fig. 5 indicates the performance capabilities of Metafine tape. Note that both coercivity and a remanent magnetization have been widely increased, indicating that both low-frequency and high-frequency output can be much higher than that obtained from any previous tape formulation.

According to 3M, in typical applications the Metafine cassettes delivered maximum outputs of 5 dB to 10 dB greater than typical chromium-dioxide tapes and 3 dB to 7 dB greater than 3M's own premium *Scotch Master II* cassettes. This means that the maximum output was double that of the other tapes or

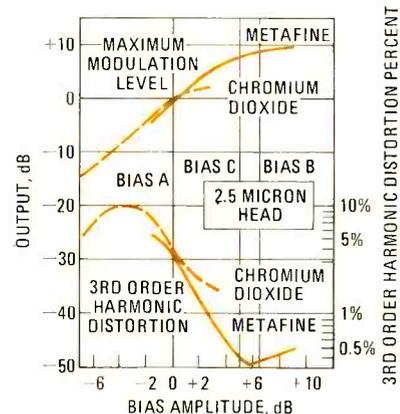


FIG. 7—MAXIMUM MODULATION level and harmonic distortion of Metafine versus chromium dioxide.

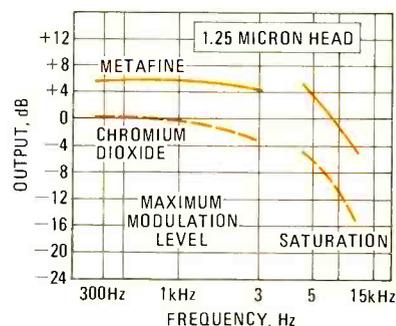


FIG. 8—OUTPUT versus frequency of Metafine and chromium-dioxide tape. For mid-frequencies, the maximum modulation level takes into account distortion. For high frequencies, saturation limits output.

more, depending upon the frequency.

Exact increases in performance characteristics will depend, in part, upon the benefits that home recording equipment manufacturers build into future tape recorders. Lower distortion, added high-frequency response, improved signal-to-noise ratio, increased maximum recorded output, etc., are all benefits that the new generation of recorders can provide (in various degrees) with the new metal-particle tapes.

Figure 6 shows the comparative output levels for Metafine and chromium-dioxide tape. Maximum output level (saturation) at 12.5 kHz is approximately 7-dB higher for the Metafine tape when each tape is biased optimally. (Bias A is the optimum bias level for chromium dioxide, Bias B is set for minimum distortion for Metafine, while Bias C is set for the flattest frequency response.) Note, however, that optimum bias for the Metafine tape is between 5 dB and 6.5 dB greater than for chromium-dioxide tapes whose bias is already several dB greater than that required for ferric-oxide tapes. This is one of the problems of compatibility.

Figure 7 shows the maximum modulation and harmonic-distortion level as a function of bias for Scotch Metafine tape and for chromium-dioxide tape. Maximum modulation level (the recording level that produces 3% third-order harmonic distortion at a 333-Hz test frequency) is up to 9-dB higher for the metal-particle tape. Distortion for the Metafine tape is more than 20-dB lower (when optimally biased) compared with optimally biased chromium-dioxide tape.

Both Figs. 6 and 7 show results for a record head having a 2.5-micron gap. Such a wide gap is typical of that used in three-head cassette tape decks, since the record head and play head can be optimized separately and the record-head gap will be more efficient at this width. Less expensive cassette decks generally use record-play combination heads, however, in which the gap must be made narrower for high-frequency reproduction.

Figure 8 shows the maximum output (at optimal bias) plotted against frequency for *Scotch Master II* chromium-dioxide tape, and the new Scotch Metafine tape, using a two-head tape deck in which the combination record-play head has a 1.25-micron gap. Under these conditions, the Metafine tape had a consistently higher output.

Compatibility/incompatibility

Present audio cassette decks having 70- μ s equalization (now required for playing back chromium-dioxide and treated ferric tapes such as *Scotch Master II*, TDK-SA, Maxell UD-XL-II and others) can play prerecorded cassette tapes without requiring any modifications in the playback electronics or the tape heads. However, most stereo cassette deck owners are more interested in being able to record

TABLE 1—PERFORMANCE SPECIFICATIONS

Recording Head Gap		1.25 Micron (2-head type)		2.5 Micron (3-head type)		
Tape	Chrome	Master II	Metafine	Master II	Metafine	
Bias reference point	0	0	+6	+1.3	+6½ ¹	+5 ²
Sensitivity, dB						
S _L -333 Hz	0	+3	+2½	+3	+3	+3
S _H -12.5 kHz	0	+2½	+2½	+2	+½	+3
Maximum Modulation Level (MML) at 333 Hz, in dB						
	0	+2½	+5½	+5½	+10	+9
Maximum Output Level (MO_H) at 12.5 kHz, in dB						
	0	+4	+11	+3	+5	+7
Distortion Level (HDL₃), in dB						
	0	-6½	-10	-11½	-23½	-21

1. Biased for minimum distortion ("B" on graph).
2. Biased for flat-frequency response ("C").

TABLE 2—TAPE SPECIFICATION COMPARISONS

	Typical Chrome	Scotch Master II	Metafine
Retentivity (gauss)	1400	1500	3400
Remanence (lines-per-¼ inch)	0.43	0.60	0.8
Coercivity (Oersteds)	550	550	1000

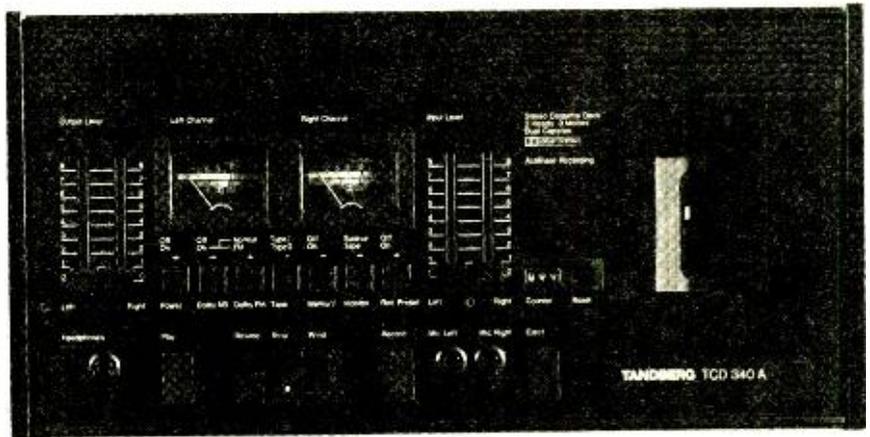


FIG. 9—TANDBERG MODEL TCD-340-AM cassette recorder can handle the new Metafine tape.

their own programs from records, tapes, FM radio or live program sources. In this respect, present-day recorders are incapable of handling the new metal-particle tapes. Bias-current requirements are much higher for Metafine tape than for previously available cassettes. Erase current applied to the erase head must also be considerably higher. Many present-day record and erase heads cannot handle such high erase and bias currents. On the other hand, such tape head types as *Sendust* or *Sen-Alloy* are able to handle the necessary increased current providing that suitable electronic changes are made in cassette decks using these heads.


Almost coincident with 3M's announcement of the availability of Metafine tape, Tandberg of America, Inc., announced its *model TCD-340-AM* cassette recorder, which is claimed to be the

first production cassette deck offered for use with the new metal-particle tapes. The new deck is shown in Fig. 9. Undoubtedly, a tape-technology improvement such as metal-particle tape won't be allowed to flounder while the industry becomes involved in a "chicken-or-egg" debate.

Summary

Table 1 summarizes the values obtained from 3M Company's tests of Metafine tape and compares them with those of chromium dioxide and *Scotch Master II* tape. In the case of chromium-dioxide tape, 0-dB reference values were used for the parameters. These comparisons show that the Metafine tape clearly wins out in every single instance. Comparisons of typical tape specifications are given in Table 2.

R-E

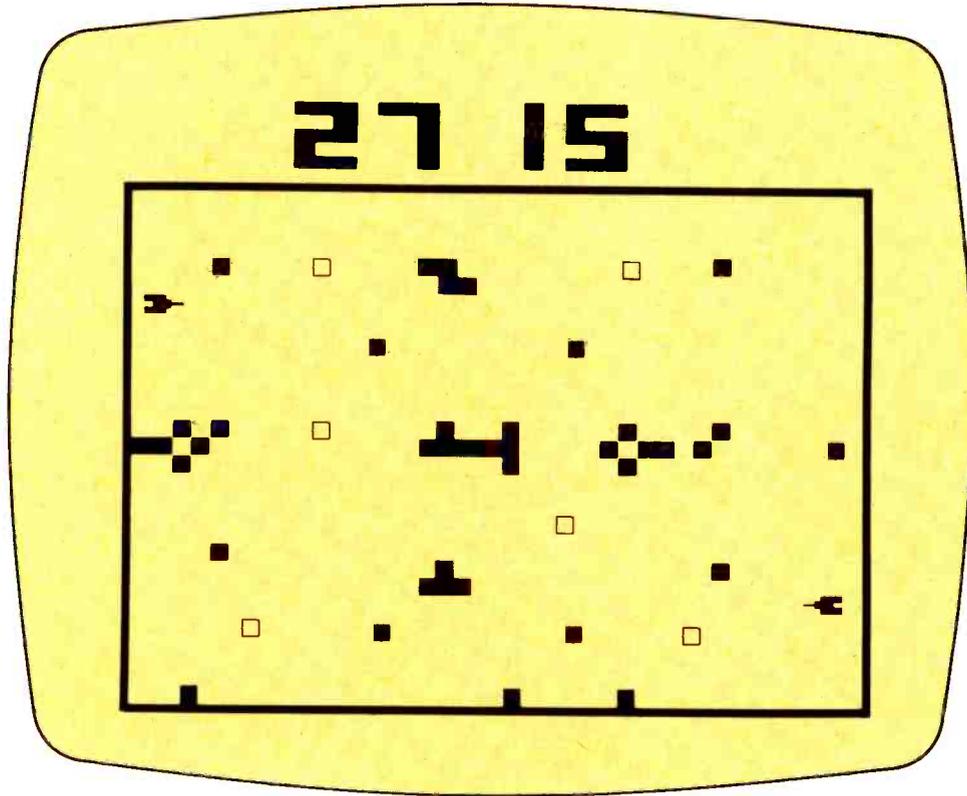

TANK

arcade quality TV game

Part 1. The object is to use your cannon to destroy your opponent first, but watch out for the land mines and anti-tank barriers. The circuit provides a composite video signal to your TV set and produces realistic sound effects.

L. STEVEN CHEAIRS

A FEW YEARS AGO I WAS AFFILIATED WITH a small repair company that specialized in video games. After the arcade pong-type games were retired from the market, they were replaced by road race and tank games. At that time, a pong game filled a 10-inch by 14-inch printed circuit board, with about 80 to 100 TTL, SSI and MSI IC's. The road race, baseball and tank games used two or three cards of that size and composition.

In the last few years, the arcade units have been improved by using newer LSI IC's; and the older pong games are now produced on a single LSI IC for home use, with a television set used as a display. It is interesting to note that many of the first arcade games used a converted black-and-white TV set as a monitor. In fact, the prototype of the game described in this article was tested on a TV set that was removed from a retired arcade pong game. Although the monolithic game IC's have permitted these games to be played at home, the quality has always been inferior to the arcade games. Now with the newer LSI IC's, the quality of the games has improved dramatically.

explosions—the illusion of battle is complete.

Playing the game

The game was designed to work into a standard domestic 525-line black-and-white receiver.


When the game is reset, the scores are cleared (to 0), all the mines reappear and the tanks are placed in their corners. The tanks remain in a stationary state until the control sticks are manipulated. These control sticks are single-pole double-throw (SPDT) center-off, momentary-contact-type switches. When the player pulls the control sticks toward himself the tank advances at a slow speed. If the control sticks are held back for another $\frac{1}{2}$ second, then the speed increases to medium. If the sticks are again held for another $\frac{1}{2}$ second, the tank switches to high speed. When the sticks are released, the tank remains at the selected speed.

If the control sticks are now momentarily pushed in the opposite direction, the tank will stop. When the sticks are pushed forward, the tank backs up. Again, the speed increases for each $\frac{1}{2}$

every four seconds is possible. The shell explodes when it hits an object or reaches the end of its range. If a shot is fired during a tank rotation, the shell follows a curved trajectory—in the direction of the tank rotation.

Twenty-two fixed-terrain antitank barriers are provided. These barriers can retard or help your progress in the game. They stop shells and tanks if the BARRIER INTERACTION switch is closed—for the AY-3-8710-1 IC only. This switch is not included in the prototype model designed around the AY-3-8700-1. Also, six mines are distributed over the battlefield area. When a tank hits one of these mines—the tank explodes and fragments momentarily, as it does when hit by a shell. When the tank image returns, it is stationary and the gun is inactive for about 2 to 4 seconds. The mine that was hit vanishes for the rest of the game. If you hit a mine a point is scored for the enemy's tank.

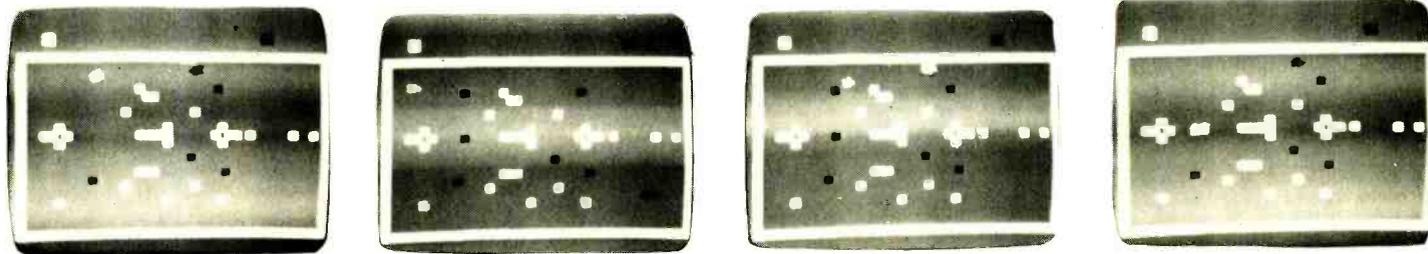Scoring is automatic. When a tank is hit by gunfire or it hits a mine, this increments the opponent's score. The game ends when a player's score indicates a total of 16 points; the score then flashes at



The leader in home monolithic game IC's is General Instruments Corporation's Microelectronics Group. This company is now producing an arcade-level single IC tank game. This single IC, the AY-3-8710-1, replaces the set of PC boards traditionally used in the arcade-type game that contained a couple of hundred TTL logic circuits and read-only memories (ROM's). This undoubtedly represents the start of a new generation of dedicated home video games.

To start the two-player tank game, you simply press the reset pushbutton. Two tanks, one white and one black, suddenly materialize in a battlefield of antitank barriers and mines. Realistic engine sounds, provided for each tank, help create the illusion of combat; four distinct sounds are produced, one for each of the motor speeds and one for the stationary condition. Next comes the sound of gunfire, coupled with shell bursts and tank

second the switches are closed, for a total of three speeds.

The tanks can be rotated by pushing one control stick forward and the other back. Rotation in the opposite direction occurs when the control sticks are reversed. Rotation may occur during all seven motion states—stationary, three speeds forward and three speeds backward. Rotation stops when the controls are returned to the normal standby position. A total of 32 rotation angles are provided.

The main gun is fired by pressing the SPST normally open pushbutton switch. A shell exits from the gun barrel and traverses the screen, unless it hits the enemy's tank or a barrier. The gun's range, if it is fired along the horizontal axis is about two-thirds of the TV screen; the range for the other directions varies with the angle. The switch must be depressed for each firing; only one shot

a 1-Hz rate and no further points are recorded. Of course, the object of the game is to maximize your score while minimizing your opponent's score.

The audio output is provided on five lines—one for each tank motor (plus bearing and track squeak), a gunfire envelope, an explosion envelope and a noise source. Figure 1 shows a typical waveform observed on the prototype tank game. In a typical system the tank motor sounds are summed. The noise and gunfire envelopes are gated with the noise output. These signals are summed with the motor noise. The composite audio signal then drives an audio-output amplifier that drives the speakers.

The circuit

The circuit described in this article is a modification of one shown in *Application Note Bulletin 104* developed by M. S. Sellars III, senior design engineer, Gen-

Train with NTS for the MicroComputers, digital the first name



The world of electronics is daily becoming more challenging. Technology is growing more specialized, and the importance of digital systems increases every day. Test instruments, home entertainment units and industrial control systems are all going digital. And now, NTS training programs include a wider choice of solid-state and digital equipment than ever before offered in any home study course: Advanced NTS/Heath digital color TV (25" diagonal with optional programming capability), NTS/Heath microcomputer, digital test equipment, digital stereo receiver (70 watts per channel), NTS compu-trainer, plus much more state-of-the-art equipment to make your training exciting and relevant.

The equipment you receive with NTS training programs is selected to provide you with a solid

background in electronic systems. Kits and lessons are designed to work together to demonstrate electronic principles and applications. The kit-building not only shows you how electronic hardware functions, but how various circuit designs accomplish different purposes. Your lessons guide you through any number of experiments associated with many projects. This is the Project-Method, and it works. Step-by-step, you learn how and why digital electronics has become a part of our world, and the even bigger role it is sure to play in the future.

Whether you are looking for training in Consumer, Commercial, or Industrial electronics, NTS offers fourteen courses, some basic, many advanced, in several areas of electronics. An all-new full-color NTS catalog shows you what each course covers,

electronics of the future.

systems and more...from
in home study.



and every piece of equipment included.
Send for it today, and see for yourself what's really
happening in electronics training technology at NTS.
Find out how much has changed, and what new
directions the field is taking. You'll probably want to
be a part of it.
It's free. Just mail the card or coupon. Today.

**NO OBLIGATION. NO SALESMAN WILL CALL.
APPROVED FOR VETERAN TRAINING.**

NATIONAL TECHNICAL SCHOOLS

TECHNICAL-TRADE TRAINING SINCE 1905
Resident and Home-Study Schools
4000 South Figueroa St., Los Angeles, Calif. 90037

NATIONAL TECHNICAL SCHOOLS Dept. 206-118
4000 South Figueroa Street, Los Angeles, California 90037

Please send FREE Color Catalog and Sample Lesson.

- Color TV Servicing
- B & W TV and Radio Servicing
- FCC License Course
- Electronic Communications
- Electronics Technology
- Audio Electronics Servicing
- Digital Electronics
- MicroComputers/MicroProcessors

Name _____

Address _____

Apartment Number _____ Age _____

City _____

State _____ Zip _____

- Check if interested in G.I. Bill information.
- Check if interested ONLY in classroom training in Los Angeles.

PARTS LIST

All resistors are 1/4 watt, 5%.

R1—180 ohms
 R2—510 ohms
 R3—470 ohms
 R4—1800 ohms
 R5—1000 ohms
 R6—270 ohms
 R7, R16, R19, R20, R23, R28—10,000 ohms
 R8—1600 ohms
 R9—2400 ohms
 R10—12 megohms
 R11—220 ohms
 R12—5000-ohm, PC-type potentiometer
 R13—2.2 megohms
 R14—2200 ohms
 R15, R21, R26—20 megohms
 R17, R22—3.9 megohms
 R18—22,000 ohms
 R24, R25—10 megohms

R27—30,000 ohms
 R29—15 ohms
 C1, C2—100 μ F, 50-volt electrolytic
 C3—2.7- μ F tantalum
 C4—C6, C13, C14—0.1- μ F disc
 C7, C8—30-pF disc
 C9, C10—0.01- μ F disc
 C11, C12—0.22 μ F
 C15, C16, C20—5 μ F
 C17—0.47 μ F
 C18—200 pF disc
 C19—100-pF disc
 C21—220- μ F, 15-volt electrolytic
 D1-D10—1N4148 or similar
 D11-D14—1N4005 or similar
 Q1—Q3—2N3904 or similar
 IC1—AY-3-8700-1 or AY-3-8710-1 LSI game
 game
 IC2, IC3—4001, CMOS quad NOR gates
 IC4—78M05, 5-volt regulator

J1—miniature open-circuit jack
 S1—S4—SPDT center-off, momentary-contact toggle switches
 S5—S7—SPST normally open pushbutton switch
 S8—SPST switch
 S9—SPST toggle switch
 T1—12VAC, 1A secondary transformer
 XTAL—4.090900-MHz crystal
 SPKR—8 ohms
 MISC.—12 X 7 X 3-inch aluminum chassis, line cord, hook-up wire, four 1/2 inch stand-off busings.

The following parts are available from Questar Engineering Company, McDonald Street, Mesa, AZ 85202:
 PC board, \$12.95; AY-3-8700-1 or AY-3-8710-1 (please specify), \$29.00; crystal, \$5.50; set of all switches, \$12.25. Kit of all parts, \$63.95.

eral Instruments Corporation, Microelectronics Group.

Figure 2 shows a block diagram of the tank game system and Fig. 3 is the sche-

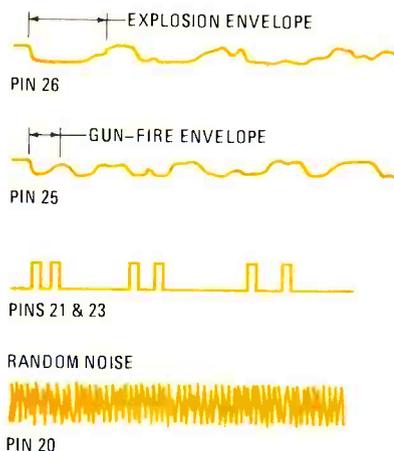


FIG. 1—TYPICAL AUDIO SIGNALS as they appear at the pins of the pins of the game IC.


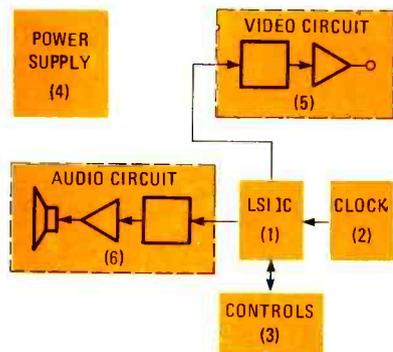


FIG. 2—BLOCK DIAGRAM of the tank battle game. Sections 5 and 6 are included on the LSI game integrated circuit.

matic diagram. Block one is the game IC, which, it is claimed, is more complex than most microprocessors. There are also two IC's, the AY-3-8700-1 and AY-8710-1. The two circuits are identical with the exception of one input pin: The AY-3-8710-1 has a barrier interaction select input, pin 22. If the pin is left floating,

the two IC's function identically. On the other hand, if the input pin is brought to the system ground potential, then the tanks cannot drive over the barricades.

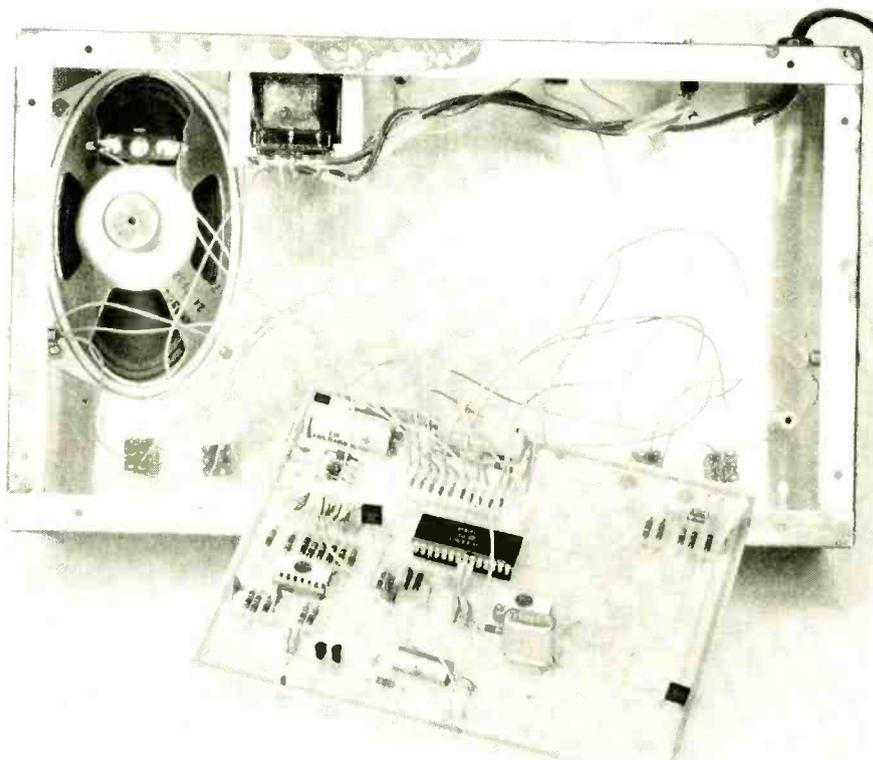Block two in Fig. 2 is a crystal-controlled clock. One inverter is used along with two resistors, two capacitors and a crystal to form a 4.0909-MHz oscil-



UNDER-SIDE VIEW of the tank game's chassis/enclosure. All components except the speaker, power transformer and switches are mounted on the printed-circuit board.

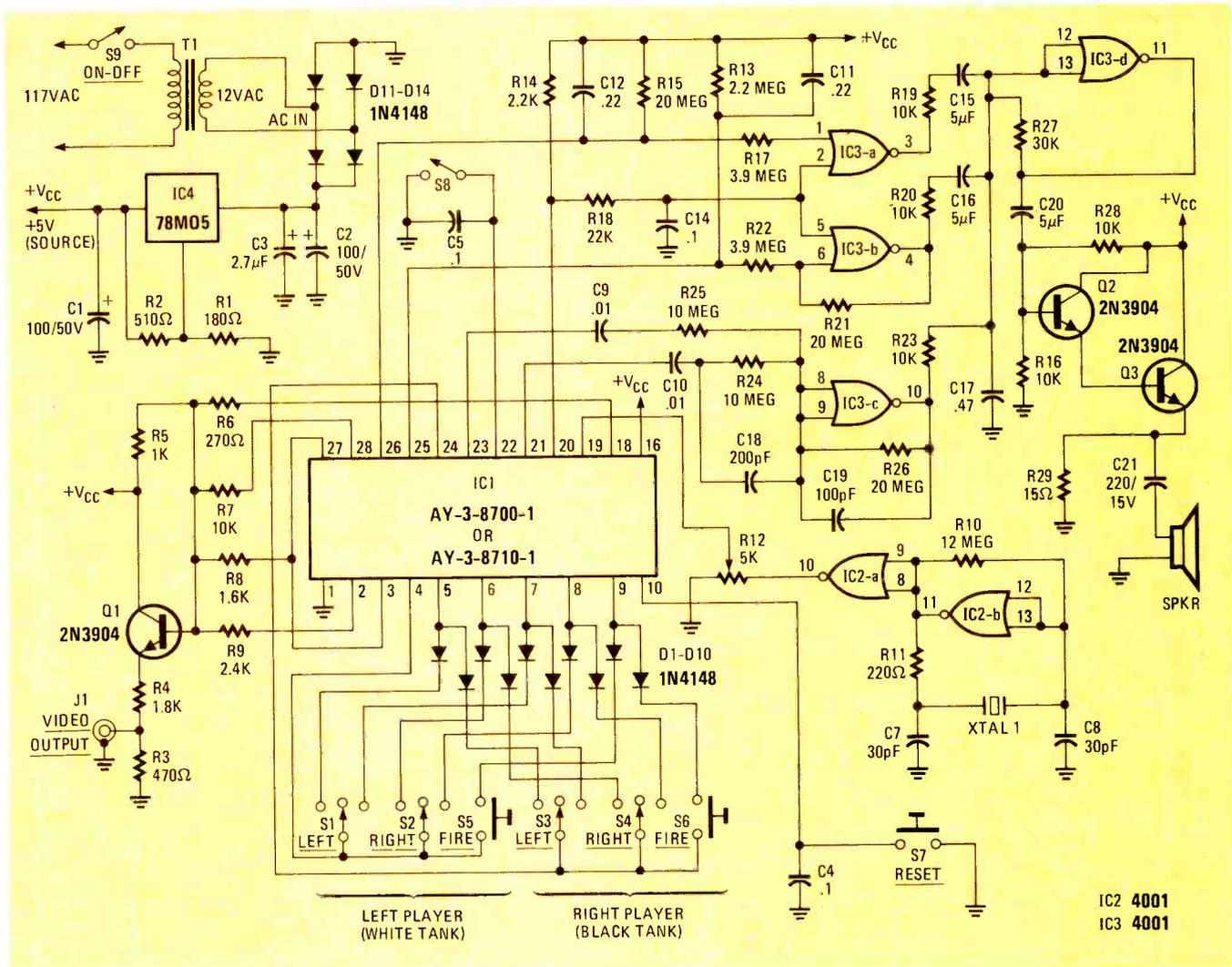


FIG 3—SCHEMATIC DIAGRAM of the tank battle video game. When using the AY-3-8700-1 IC, do not connect anything to pin 22.

lator. The output is isolated by passing the signal through another CMOS inverter. This inverter drives a 5,000-ohm potentiometer. This pot is adjusted so that the signal amplitude provided by this pot is between a 3.0-volt to 3.2-volt peak level.

The third block represents the controls. Eight switches, ten diodes and two capacitors are required. The four SPDT center-off momentary-contact switches are used to control the tank motions; the two SPST normally open pushbutton switches are used to fire the tank's main gun. The diodes provide isolation between these switches, thus allowing multiple closures. Reset is provided by an SPST normally open pushbutton and an 0.1- μ F capacitor; the capacitor provides for a small amount of debouncing. The last

switch, an SPST-type, and its capacitor select the barrier interaction.

Block four, the power supply, takes a 12-volt AC input and generates a 7-volt regulated DC output. Four 1-amp rectifiers convert the AC voltage into a pulsating full-wave DC voltage. Next, a filter capacitor smooths the ripple. The regulator is a 5-volt three-terminal unit. Two volts are dropped across the ground resistor. Another filter capacitor is used on the output.

Block five represents the video-summing and video-amplifier circuits. The passive summing circuit sets the luminance level (by the ratios of the resistors). Five outputs are provided: Sync; right tank/score/shells/shell burst/mines; left tank/score/shells/shell burst/mines; background; and blanking.

One tank is white, the other is black and the background is gray. The black video outputs and blanking are tied to a single resistor since the modulation levels are approximately equal. The video amplifier is formed using one NPN 2N3904 transistor and an emitter voltage divider. In Mr. Sellars' *Application Note*, this amplifier drove an Astec UM1082 RF modulator. If a different modulator is used, then the summing resistors and the emitter resistor may have to be adjusted. In the prototype version, the video signal was fed directly into the TV set's video amplifier; thus, no modulator was used.

Block 6 is the audio-output network. The speaker is driven by the emitter of a Darlington transistor amplifier via a DC blocking capacitor.

continued next month

Digital Windshield Wiper Delay



Most windshield-wiper pause controls require tedious trial-and-error adjustments each time they are turned on. Here's one that doesn't. Installation is easy with only six connections.

TOMMY N. TYLER

MOST VARIABLE-DELAY WINDSHIELD WIPER CONTROL CIRCUITS use a unijunction transistor or a 555 timer to periodically turn on the windshield wiper motor for one sweep of the blades. Invariably, a potentiometer is provided so that the driver of the vehicle can control the time delay between cycles.

This system has several disadvantages. Usually, when the wipers are first turned on, the delay control must be turned down all the way for a few cycles until windshield streaking has subsided. Then, you have to search for the right control setting to match the intensity of the rain. Even installing a delay control can be a headache as you search for a suitable spot on the dashboard to mount it.

This article describes a wiper-control system that eliminates these problems. First, installation is easier because no additional controls are required other than the existing windshield wiper switch. And you don't have to adjust the desired time between cycles by trial and error. When the wipers are first switched on, they run continuously in normal fashion. If the rain is only a light drizzle, the driver can select intermittent operation by switching the wipers off, then back on again when the windshield needs it. The control circuit "remembers" how long the wipers were switched off and repeats this delay between each successive cycle. The wipers continue to run intermittently at this rate until switched off.

If the rain changes intensity, you can easily readjust the delay by switching the wipers off and back on after the desired pause between the strokes. If continuous operation is needed, switching the wipers off and immediately back on (an almost instinctive reaction) in effect sets a zero delay between cycles. Whenever the wipers are left switched off for longer than 40 seconds (the maximum delay) the circuit resets itself.

Circuit description


Figure 1 shows the timing control assembly, in which gates IC1-a and IC1-b comprise a 50-Hz clock oscillator that drives address counter IC6 via IC1-c. Counter IC6 is a 12-stage binary

counter with the second through eleventh-stage outputs connected to the 10 address input pins of RAM IC7. The most significant bit, Q_{12} , is used to inhibit the counter via IC1-c when the address input to IC7 rolls over from 1023 to 0. The least significant bit, Q_1 , enables gate IC4-d and inhibits gate IC2-a so that proper timing is maintained between addressing, data input and the read/write control of the RAM.

When the wipers are switched on, the Q output of IC5-a goes high on the next clock pulse, and the Q output of IC5-b goes high on the clock pulse following. With the Q_{12} output of IC6 also high, IC4-a is enabled, keeping transistor Q2 turned on so that relay RY1 is energized. The contacts of RY1 are wired into the wiper motor circuit so that the motor runs continuously.

When the wipers are switched off, the Q outputs of IC5-a and IC5-b are clocked low in sequence, causing IC4-b to be enabled for one clock cycle to deliver a reset pulse to IC6 via IC4-c. The counter now starts measuring the prospective delay interval. With pin 2 of IC5-a high, the outputs of IC2-b and IC2-c are low, causing a 0 to be loaded into the RAM since the WRITE input to IC7 goes low momentarily following each change of address, as shown in Fig. 2. Note that the lowest-order address bit, Q_2 , changes on every odd clock cycle, and WRITE pulses occur on every even cycle. This causes a READ-WRITE-READ sequence at IC7 pin 3 for each new address input.

When the wipers are switched back on, outputs Q of IC5-a and IC5-b are clocked high sequentially, as before. This causes the IC2-b output to go high for one clock cycle so that a single 1 is written into the RAM. Since the output pin of the RAM continuously shows the data at the selected address, it goes high immediately. As the RAM is incremented to the next address (where a 0 is stored) its output goes low, triggering a 50-ms one-shot created by IC3-c and IC3-d. The output of this one-shot resets IC6 via IC4-c, and passes through a pulse stretcher consisting of C6, R8 and D3. The pulse stretcher energizes RY1 for about 3/4 second, long enough for the wiper motor to latch on and complete one cycle.

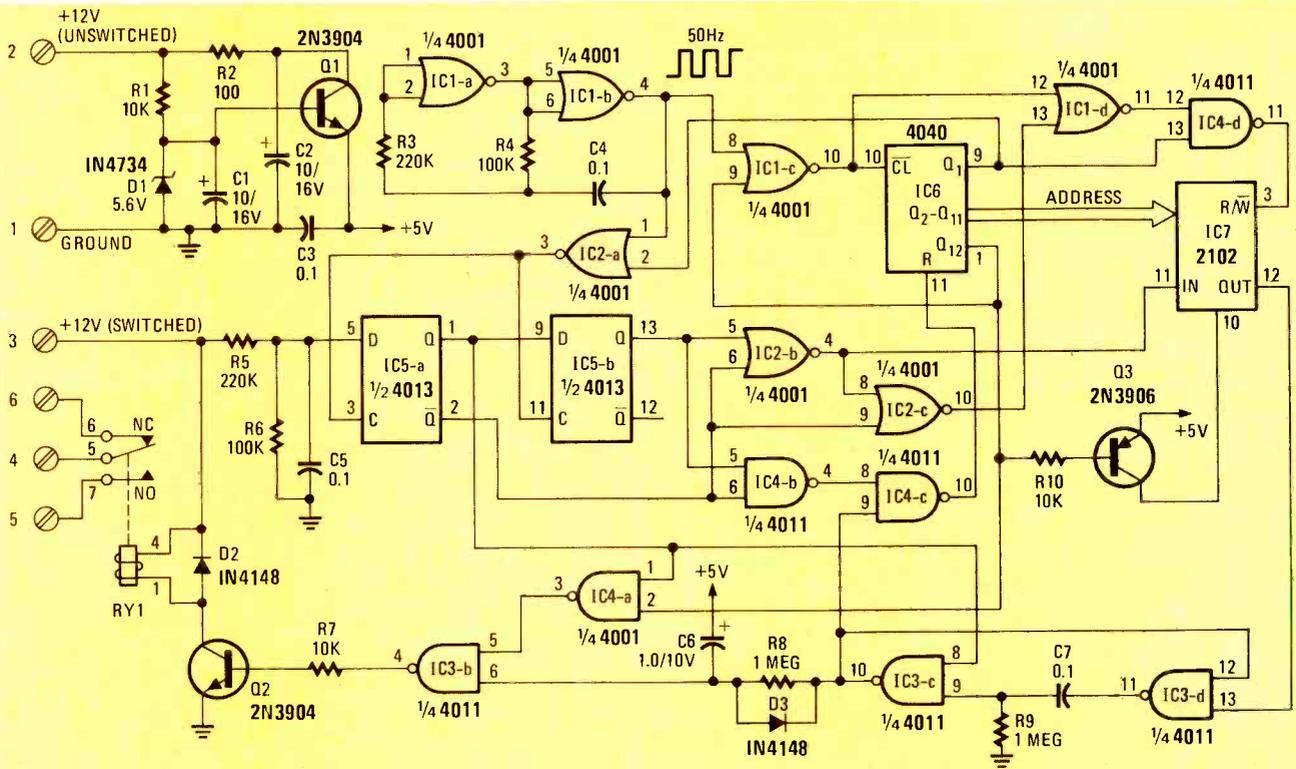

DEVICE	TYPE	+6.2V	COMMON
IC1, IC2	4001	PIN 14	PIN 7
IC3, IC4	4011	PIN 14	PIN 7
IC5	4013	PIN 14	PIN 4, 6, 7, 8, 10
IC6	4040	PIN 16	PIN 8
IC7	2102	—	PIN 9, 13

ADDRESS	IC6	IC7	ADDRESS	IC6	IC7
Q2	7	8	Q7	4	2
Q3	6	4	Q8	13	1
Q4	5	5	Q9	12	16
Q5	3	6	Q10	14	15
Q6	2	7	Q11	15	14

FIG. 1—SCHEMATIC of the windshield-wiper pause control. Circuit is simpler than it looks and is mounted on a perforated circuit board with point-to-point wiring.

PARTS LIST

All resistors 1/4 watt, 5%.

R1, R7, R10—10,000 ohms

R2—100 ohms

R3, R5—220,000 ohms

R4, R6—100,000 ohms

R8, R9—1 megohm

C1, C2—10 μ F, 16-volt electrolytic

C3—C5, C7—0.1 μ F, 50-volt ceramic disc

C6—1 μ F, 10-volt electrolytic

D1—Zener diode, 5.6 volts, 1N4734

D2, D3—1N914/4148

D4—1N4001, used in Fig. 13

RY1, RY2—relay, 12-volt coil, 3-amp contacts (Radio Shack 275-206 or equal)

Q1, Q2—2N3904

Q3—2N3906

IC1, IC2—CD4001

IC3, IC4—CD4011

IC5—CD4013

IC6—CD4040

IC7—2102 static RAM

Misc.—2 \times 4.8-inch glass-epoxy perforated board, 2 1/4 \times 2 1/4 \times 5-inch Minibox (Bud CU-3004-A or equal).

The system is now in its delay timer mode. The output of IC2-c is high, causing IC1-d to inhibit IC4-d so that no WRITE pulses can be applied to the RAM. Each time the address counter steps over the location where the 1 is stored in the RAM, the one-shot resets the counter and momentarily energizes the relay via the pulse stretcher. If the wipers are switched off to set a longer delay, the 1 previously stored in the RAM appears briefly at the RAM output before rewritten as a 0. However, this will not trigger the one-shot and reset IC6 because pin 8 of IC3-c is held low by output Q of IC5-a while the wipers are switched off. Any time the wipers are switched off and on quickly, RY1 remains energized to run the motor continuously, since the pulse stretcher blends the closely spaced output pulses from the RAM into one steady output.

The timer's performance is more than adequate for this application. The resolution of the delay interval is 1 address count, which is 2 clock cycles, or about 40 ms using the component values shown in Fig. 1. The maximum time interval is approxi-

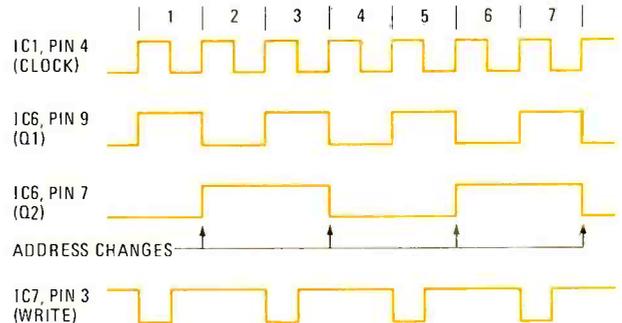


FIG. 2—TIMING DIAGRAM of the windshield-wiper pause control. A read-write-read sequence appears at pin 3 of IC7, a 2102 static RAM.

mately 40 seconds. This range can be modified easily by changing the value of C4 or R4 to speed up or slow down the system clock.

To minimize power consumption and prevent battery discharge during periods when the car is not being driven, the system uses CMOS IC's throughout except for the RAM, which needs about 30 mA at 5 volts. Since the RAM is needed only during actual operation, transistor Q3 shuts off its power when output Q₁₂ of IC6 goes high (standby condition) and the total current drain is then reduced to less than 1 mA. The power supply and logic connections are well filtered to protect the circuit from transient surges and noises within the vehicle's electrical system.

Construction

The circuit fits neatly on a 2.0- by 4.8-inch piece of glass-epoxy perforated board, as shown in Fig. 3. Use sockets for the IC's so they will not be damaged by static electricity during construction. Figure 4 shows a drilling layout of the holes in the

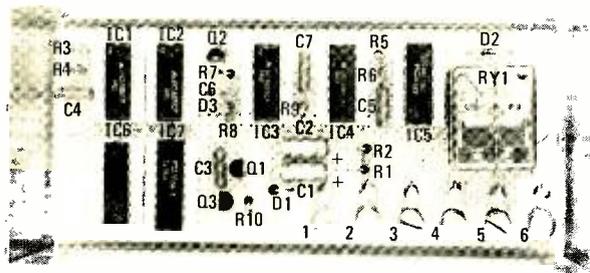


FIG. 3—INTERIOR VIEW shows positions of the various components on the perforated circuit board. Note that IC's are in sockets.

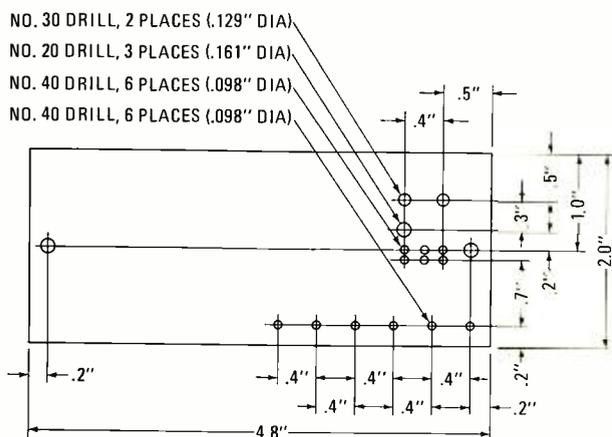


FIG. 4—DRILLING GUIDE shows locations and sizes of the 17 holes that must be drilled in the perforated circuit board.

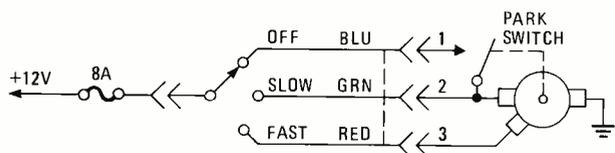


FIG. 5—THE BASIC two-speed windshield wiper.

perforated board that must be enlarged. Use several flat washers beneath the relay socket to prevent it from breaking or distorting the board when the mounting screw is tightened.

The termination points for external wiring are made by first securing flat solder terminal lugs to the top of the board with No. 6 by 1/4-inch-long, self-tapping sheet-metal screws, then anchor them in place with the component leads bent back up through the board from below and soldered. The self-tapping screws hold remarkably well in glass-epoxy material, and can be loosened and retightened to attach spade lugs or bare wires many times without any problem.

Mount the board assembly on threaded standoffs in a 2 1/4 × 2 1/4 × 5-inch metal utility box, as shown in the photograph. After checking the circuit operation, mount the box in a conven-

ient location beneath the dashboard and hook up the appropriate wires.

Installation

Since windshield wiper motor circuits are rarely standardized, for the details of your particular model you should refer to a shop manual or experiment. In some systems the positive supply to the motor circuit is switched, and in others it is on the ground side. Most automotive systems use permanent-magnet-field motors; but a few, including General Motors, use motors with series and shunt-field windings to obtain dual-speed operation. Let's look at a few of these circuits to determine how they can be modified to work with the wiper control circuit.

Figure 5 shows a simple dual-speed wiper circuit, such as is used on a '77 Jeep CJ model. The motor has a permanent-magnet field and uses different brush orientations to obtain slow and fast speed. If the wipers are switched off in the middle of a stroke, the motor continues to run slowly until the park switch opens when the blades are about five degrees from the bottom of their stroke. Figure 6 shows how the timing control is hooked up so that it is effective only in the SLOW position. Each time the control relay pulls in momentarily, it energizes the motor long enough for the park switch to close. When the relay opens,

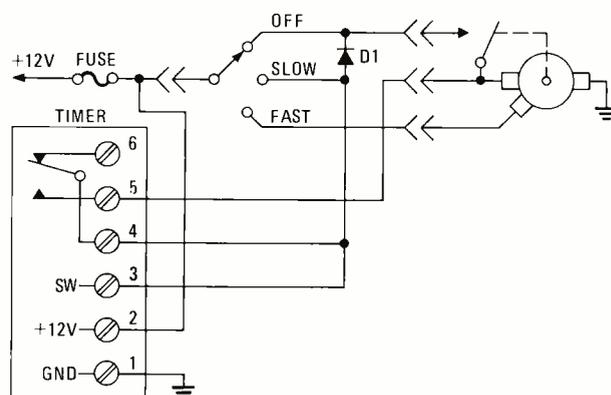


FIG. 6—HOW CONTROL IS ADDED to the two-speed windshield-wiper motor circuit.

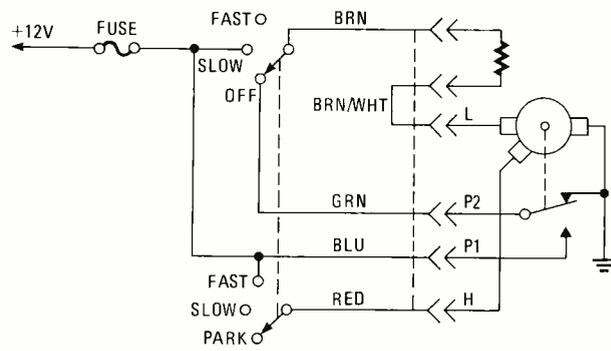


FIG. 7—WINDSHIELD-WIPER MOTOR with dynamic braking provided through the park switch.

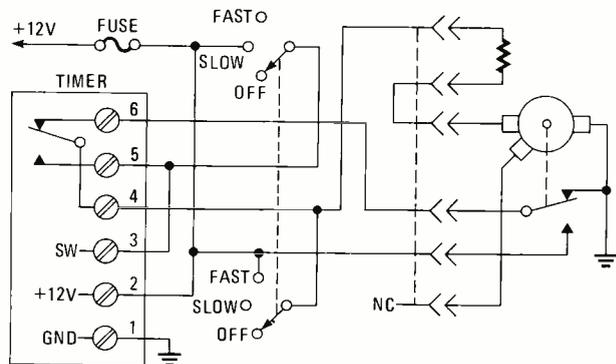


FIG. 8—CONNECTING THE CONTROLLER to the wiper motor. Fast position bypasses the timer and runs wiper continuously at slow speed.

current continues to flow through D1 until the motor completes one cycle. In this arrangement the FAST speed circuit is unaffected. This provides a backup in an emergency or a circuit failure.

Figure 7 shows the circuit for 2-speed nonconcealed wipers used on 1969–1973 Chrysler Motors vehicles. The same basic circuit, with minor switch modifications and elimination of the resistor, is used on the Volkswagen Dasher model. This circuit is similar to that in Fig. 6 except that the park switch shorts the armature when it removes power from the motor, stopping it abruptly by dynamic braking. This makes the park position more precise because it is less susceptible to variations in friction between the wiper blades and wet or dry glass. Figure 8

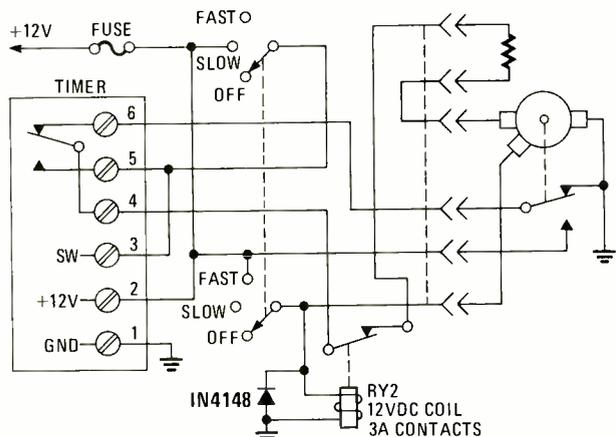


FIG. 9—INSTALLATION, with fast-speed operation made possible through addition of the relay.

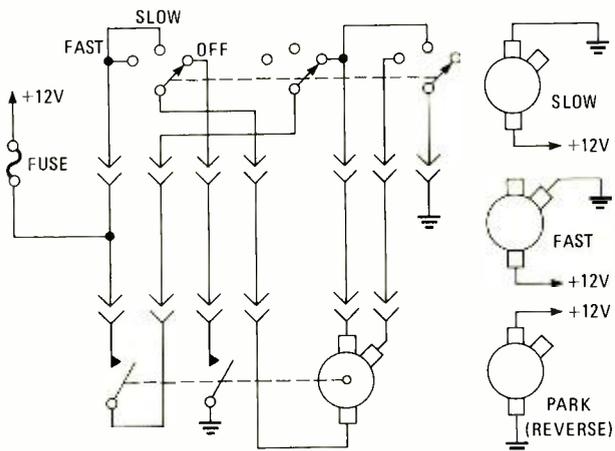


FIG. 10—REVERSIBLE MOTOR CONCEALS wiper blades in the park position when wiper is switched off.

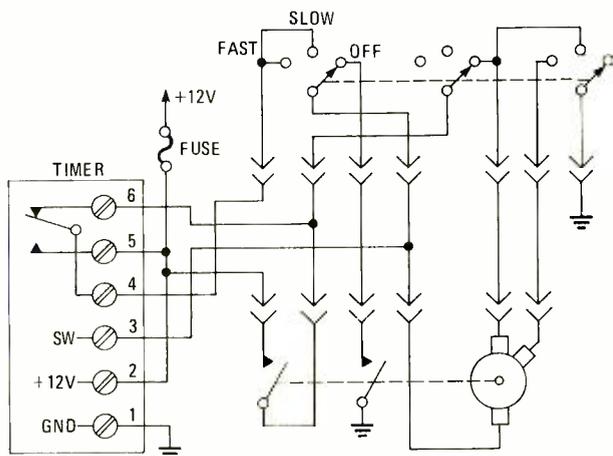


FIG. 11—TIMER IS EFFECTIVE at slow and fast speeds in this installation.

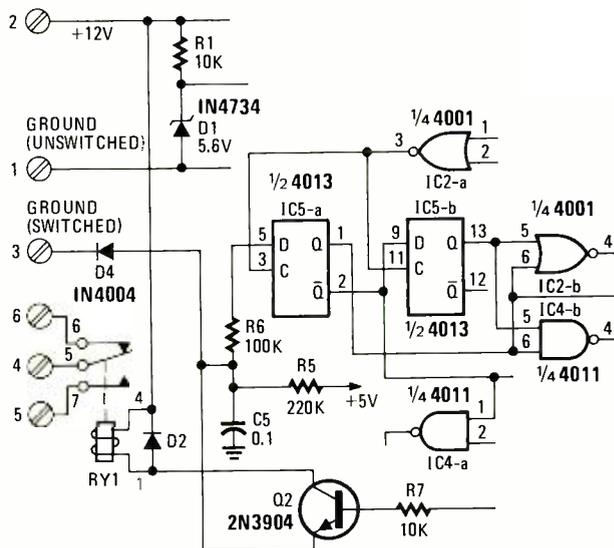


FIG. 12—BASIC CONTROL CIRCUIT modifications for use with windshield wiper motors that are controlled by switching in the grounded power lead.

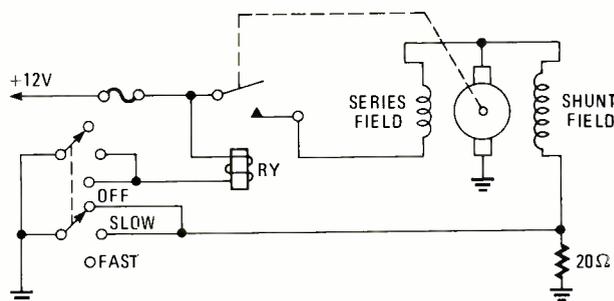


FIG. 13—TWO-SPEED circuit with switched ground is used in some GM automobiles.

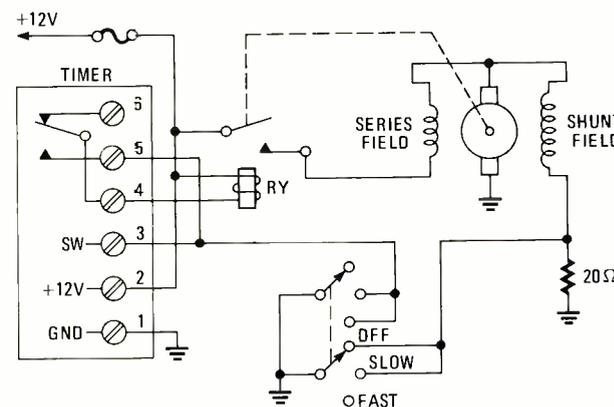


FIG. 14—TIMER CONTROL operates in either fast or slow-speed modes.

shows a method of attaching the control to this system. In this circuit the FAST position bypasses the timer and runs the motor continuously, but at slow speed. Figure 9 shows how to retain the fast speed by using an additional relay to disable the slow-speed circuit.

The wiper circuit of a '73 Ford with concealed blades in the park position is shown in Fig. 10. In this system the motor runs forward at either slow or fast speed for normal operation. When the wipers are switched off, the polarity of the motor is reversed to the slow-speed brushes. As the motor rotates backwards, it activates a mechanism that increases the stroke of the wiper arm and moves the blades down out of sight in the park position. Figure 11 shows how the wiper control can be interfaced to this type of circuit, with the timer effective in both slow and fast speed.

Figure 12 shows some slight modifications that allow the

continued on page 104

THIS FUNCTION GENERATOR IS DESIGNED around the 8038 waveform generator IC. Specifications, schematic, details of circuit operation and Len Feldman's Test Report on this versatile precision test instrument appeared last month.

Construction

Construction begins with the PC boards. Figure 2 is the foil pattern for the combined power supply and main circuit boards. Figure 3 shows the placement of components of the main board and Fig. 4 shows how parts are placed on the power supply section.

In an effort to minimize PC board-to-front panel wiring, all pots and switches (except S4 and S5) mount directly to the main PC board. The resulting assembly is then bolted to the chassis front panel and held in place by the threaded shafts of the pots and rotary switches. It is therefore important that the holes for the PC-mounted pots and switches accurately line up with the corresponding holes in the front panel. To do this the procedure outlined below should be followed.

After the circuit board has been etched and drilled, cut it along the indicated line. The smaller piece is the power supply board and the larger is the main board. Do not, however, begin mounting components in either board until after the drilling described below is done.

Using the LMB type 000-946 chassis, place the main PC board against the chassis' face; the foil side facing outward toward you, the component side resting against the chassis front. The drilling location for pots R5 and switch S1 will be on the chassis left-hand side while pots R23 and R33 and switch S3 are on the right-hand side. With this orientation, center the PC board so the hole location for switch S2 is exactly centered on the chassis' front-panel face (left-to-right, top-to-bottom). Using small scraps of PC board to protect the PC board's foil, tightly clamp the board in place using C-clamps. Repeat: tightly. Drill six $\frac{1}{16}$ -inch pilot holes in the PC board-chassis sandwich at the locations shown for pots R5, R23, R33 and switches S1, S2 and S3. Then drill out these holes to the diameter required by your switches and pots ($\frac{3}{8}$ -inch diameter is standard). Be careful that the PC board not slip due to the drilling torque, as you want perfect alignment between board and chassis holes.

Remove the clamps and set the PC board aside for now. Drill out the rest of the chassis front as shown in Fig. 5.

A standard $\frac{1}{2}$ -inch aluminum angle bar is used to heat sink the voltage regulators and to attach the power supply board to the chassis. Cut five 1-inch strips of the bar and drill out each as shown in Fig.

2-200,000 Hz Function Generator

Part 2—Construct your own function generator around the latest state-of-the-art waveform generator IC. Delivers sine, square and triangle waves with precision not possible with discrete components or IC's of a few years ago.

DOUG FARRAR

3-a. Take two of the pieces and position them on the power supply board as shown in Fig. 3-b, lining up each bar with the board's edges. Hold each in place with a C-clamp and then drill two $\frac{3}{64}$ -inch holes at the locations shown. Hold each in place with a 6-32 \times $\frac{1}{2}$ -inch bolt and nut.

The power supply board will be mounted on an angle bar bolted to the back edge of the chassis (Fig. 3-d). To line up and drill the two chassis mounting holes, place the board-angle bar network on the outside of the chassis rear panel, centering it left-to-right as close as possi-


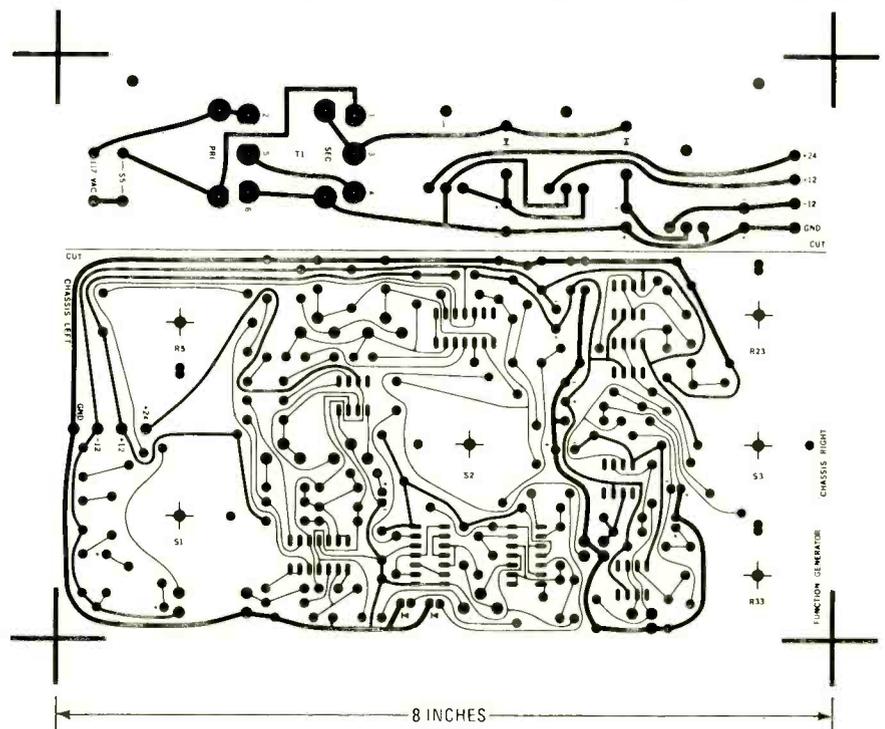


FIG. 2—FOIL PATTERNS for the main board and power supply. Cut boards apart along indicated line after etching and drilling.

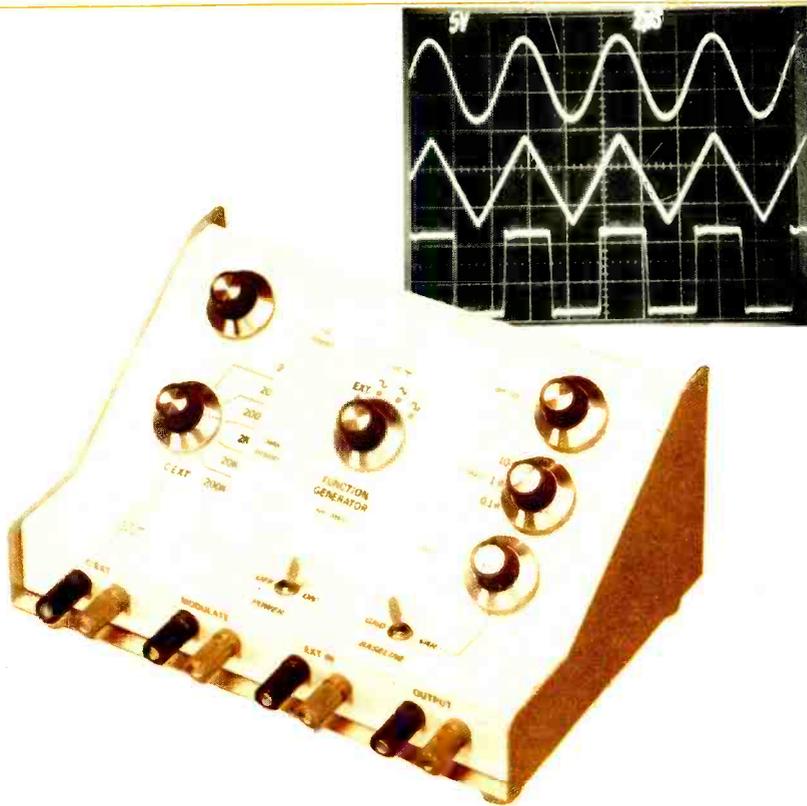

ble. With the bottom of the angle bar up $\frac{3}{8}$ inch from the bottom of the chassis, pencil in the location of the two holes on the chassis, and drill out each with a $\frac{1}{32}$ -inch drill. Remove all burrs. Lastly, drill out another hole in the chassis back for the power cord strain-relief. Center it

left-to-right, 2 inches up from the chassis bottom.

The chassis is now ready for painting and lettering. I found it difficult to get the dry transfer lettering to stick to the unit's baked enamel finish, so I applied three coats of flat white lacquer, followed

by two coats of flat clear lacquer. This surface, when thoroughly dry, is much more amenable to the lettering. When you've finished the lettering, apply three more coats of clear lacquer as a sealer.

You're now ready to begin component mounting and assembly. First, mount each of the heat-sink angle bars between the regulators and PC board as shown in Fig. 6-c. Use a small amount of silicone glue under each heat sink to prevent it from twisting loose.

Mount and solder the remaining components on the power supply board. The board can accept two different types of power transformers; either a 4-pin Radio Shack variety or a 6-pin Triad unit. Use whichever one is more convenient to locate.

Now assemble the main PC board, being careful to note the IC pin 1 locations. Trim all leads as close to the foil as possible, since the foil side will be held very close to the conducting chassis. If the leads are too long, shorts will occur. Mount trimmer pots R47 and R48 and remove R20 only if you have a distortion meter. Otherwise, omit the two trimmers and use only resistor R20. (In this case, pin 12 of IC8 goes to -12 volts through R20, pin 1 connects only to C8.) When all components are soldered in place, attach pots R5, R23 and R33 and switches S1, S2 and S3 to the board. These items mount to the component side of the board and are held in place on the foil side with a lockwasher and nut. Use short jumper wires to connect the terminals of the pots and switches to the board.

Take two 30-inch lengths of wire and twist them together with an electric drill. Cut four 4-inch wire pairs and solder them into the PC board pair locations labeled as D-E, F-G, O-P and Y-Z. Cut a 9-inch length of the twisted pair and solder it to the power supply PC board locations LL and MM. At the other end of this cable, solder switch S5. Now make a 4-inch 3-wire twisted cable and solder the wires to the locations called EE-FF-GG. To the other ends of these wires solder switch S4, making sure that PC board location GG connects to S4's center post.

Twist four 12-inch wires together, then connect the wires between the two boards' power connections. Be sure that +24 connects to +24, +12 to +12, etc. Use an ohmmeter for verification.

You're now ready for a preliminary debug. Place all trimmer potentiometers in their center positions. Set the now-interconnected PC boards on a non-conducting surface, plug in the power cord and turn switch S5 on. Be very careful at this point with the exposed 117-VAC wiring! With a voltmeter, verify

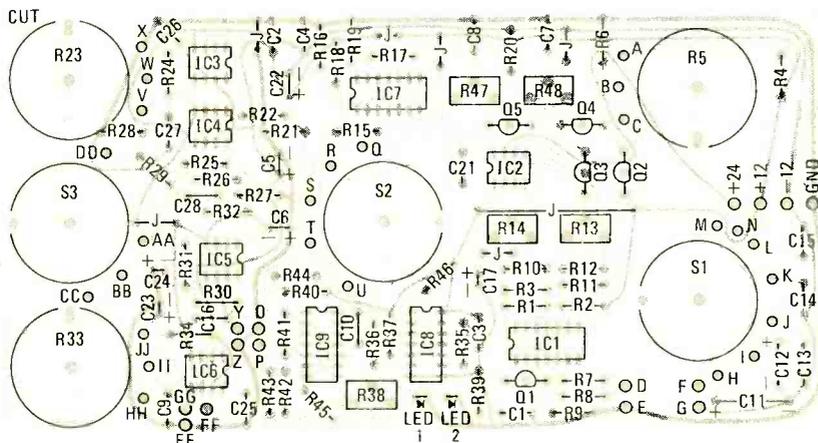


FIG. 3—PLACEMENT OF PARTS on the main PC board. Control shafts fasten this board to the front of the enclosure.

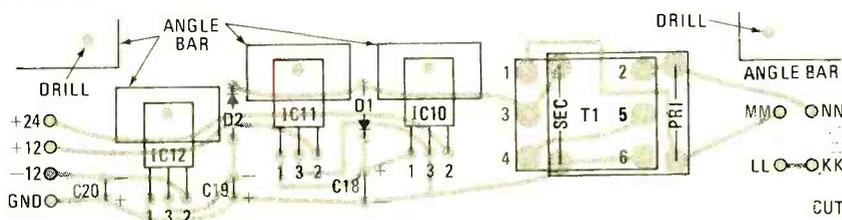


FIG. 4—MOUNTING BRACKETS and heat sinks for three regulator IC's are made from pieces of aluminum angle. These and other power supply components are placed on board as shown.

PARTS LIST

Resistors 1/4 watt, 5% unless otherwise noted

R1, R4—3300 ohms
 R2, R7, R8, R41, R42, R46—10,000 ohms
 R3—220 ohms
 R5—10,000 ohms, potentiometer, linear taper (Centralab HMP-10K)
 R6—470 ohms
 R9, R16, R30, R31, R44, R45—2000 ohms
 R10, R15, R22, R24, R29—1000 ohms
 R11, R17—2200 ohms
 R12, R25—1800 ohms
 R13—1000 ohms, printed circuit trimmer
 R14, R38—10,000 ohms, printed circuit trimmer
 R18—5600 ohms
 R19—1500 ohms
 R20, R40, R43—82,000 ohms
 R21, R28, R36, R37, R39—100,000 ohms
 R23—1000 ohms, potentiometer, linear taper (Centralab HMP-1000)
 R26—180 ohms
 R27—22 ohms
 R32, R34—56,000 ohms
 R33—100,000 ohms, potentiometer, linear taper (Centralab HMP-100K)
 R35—1 megohm
 R47, R48—100,000 ohms, printed circuit trimmer (optional, see text).

Capacitors

C1—C4, C7—C10, C21, C25—0.1 μ F, 50V, Mylar
 C5, C6, C20, C22—47 μ F, 35V, radial electrolytic
 C11—4.7 μ F, 25V, 10% tantalum
 C12—0.47 μ F, 25V, 10% tantalum
 C13—.047 μ F, 25V, 10% Mylar
 C14—.0047 μ F, 25V, 10% Mylar
 C15—470 pF, 25V, 10% ceramic
 C16, C26, C28—10 pF, 25V, ceramic
 C17, C23, C24—10 μ F, 25V, radial electrolytic
 C18—220 μ F, 50V, radial electrolytic
 C19—100 μ F, 50 V, radial electrolytic

D1, D2—1N4004, 100V, 1A diode
 IC1, IC9—LM324 quad op-amp
 IC2, IC6—LM341CN op-amp
 IC3—IC5—LM318CN high-speed op-amp
 IC7—8038 waveform generator (Intersil, Lithic Systems)
 IC8—4001 CMOS quad NOR gate
 IC10—LM340T-24, +24V regulator
 IC11—LM340T-12, +12V regulator
 IC12—LM320T-12, -12V regulator
 LED1, LED2—XC209 (or equal) LED lamp
 Q1—MPSA13, NPN Darlington

Q2—Q5—MPSA63, PNP Darlington
 S1—1-pole 6-position miniature rotary switch (CTS T-206)
 S2—1-pole 4-position miniature rotary switch (CTS T-206)
 S3—1-pole 3-position miniature rotary switch (CTS T-206)
 S4—SPDT miniature toggle switch
 S5—SPST miniature toggle switch
 T1—power transformer, 25.2-VAC 300-mA secondary, PC mount (Triad type F-148XP or Radio Shack 273-1386)
Miscellaneous—LMB 007-946 case, 1/2-inch aluminum angle bar, 6-32 \times 1/2" bolts with hex nuts 3/8" \times 32 nuts, 3/8" lockwashers. Binding posts (J1-J8), power cord, strain relief, hookup wire.

A complete kit of parts including all components, and undrilled and unlabeled cabinet is available for \$79.95. Etched, drilled and silk-screened PC boards \$11.00. Full-size photo-negative of PC pattern \$3.50. Available postpaid from Noveltronics, PO Box 4044, Mountain View, CA 94040. California residents add state and local taxes as applicable. Foreign readers add 5% for extra postage and handling.

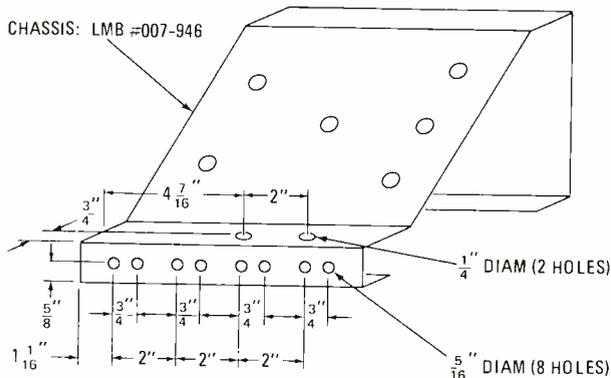


FIG. 5—FRONT PANEL has holes drilled in its three lower surfaces. The five holes for the switches and pots must be precise. See text.

that the three power supply voltages are arriving into the main board. Set pot R5 in its counterclockwise position, pots R23 and R33 in their clockwise positions. Place switch S1 in the "2—20"-Hz position, S2 in the TRIANGLE position, S3 in the "10" position and S4 in the VAR position. You should now be getting a 10-volt triangle waveform at the generator output. The low-frequency output can be observed with the voltmeter by probing at board locations Y-Z. The calibrator LED's should also be alternately blinking. Place function selector switch S2 in the square and sine positions and confirm their voltage excursions with the voltmeter. If anything is wrong at this point, remove power and locate the problem.


Calibration

Plug the power cord into an outlet and turn on power. Again keep your hands clear of the exposed line voltage at the power supply board's foil side. With a voltmeter, measure the +12-volt supply. Adjust trimmer R38 in the calibrator circuit until the voltage at pin 8 of IC9 is exactly half of the supply voltage.


Place FREQUENCY switch S1 in the "20—200"-Hz position with FINE FREQUENCY pot R5 in its fully clockwise position. Adjust trimmer R13 until both LED's are off. This is a very touchy adjustment, and you shouldn't expect the lights to remain off for any great length of time—thermal drift makes stability impossible. Now place S1 in the "200—2K"-Hz position and rotate R5 fully counterclockwise and adjust trimmer R14 until both LED's are off or just slightly glowing. Repeat this procedure one more time. The generator output will

NOTES:

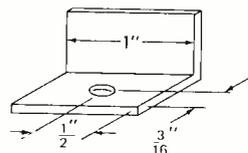
1. 1/2" ALUMINUM ANGLE BAR
2. FABRICATE 5 PIECES
3. DRILL HOLE TO 9/64" DIAM




a

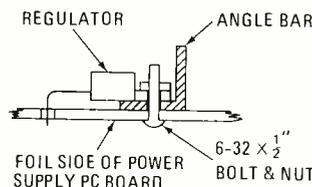

c

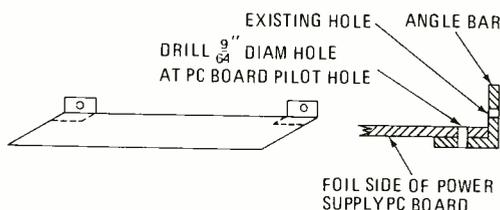

b

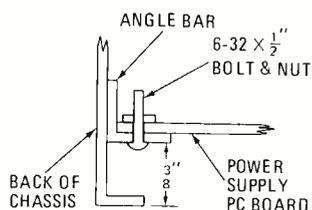

d

FIG. 6—ALUMINUM ANGLE STOCK is used to construct board mounting brackets and heat sinks for regulator IC's. See construction details for explanation.

now have a 50% duty cycle for any frequency setting.

If you're lucky (or rich) enough to have a distortion meter you can make one more distortion trimming. Set the generator for a 1-kHz sine wave and then adjust trimmers R47 and R48 for minimum distortion at the output. If you don't have such a meter then you shouldn't bother trying to make this adjustment; in fact, you should have omitted soldering the two trimmers to the board.

Operation

Using the function generator is fairly straightforward. Sine, triangle and square waveforms can be supplemented by any signal you may want to add at the external input. If you would like the output to be centered around a frequency different from that of the front panel, you can add an external timing capacitor at the C_{EXT} terminals. The swept frequency range (in Hertz) will be given by

$$10/C_{ext}(\mu F) \leq \text{frequency} \leq 100/C_{ext}(\mu F)$$

with about a 20% overlap on each side of the ranges.

There is a minimum capacitance that can be added at the C_{EXT} input of about 200 pF. Any value less than this causes gross signal distortion. The only limit on the maximum capacitance value is determined by the capacitor's leakage current.

By using the BASELINE OFFSET control, the waveform generator can be used as a digital pulse generator with a fixed 50% duty cycle. The output buffer will typically sink and source 25 mA, making it more than adequate for driving TTL and CMOS circuitry.

The function generator's frequency can be swept via the MODULATE INPUT. This input overrides the signal applied by FINE FREQUENCY pot R5. Its input impedance is 10,000 ohms. The net effect of the input is to force a frequency determined by this instantaneous voltage and the selected timing capacitor. Of course, if the input voltage is time-varying, then so is the output frequency. The exact relationship between input voltage, timing capacitor, and frequency is

$$\text{Frequency} = \frac{14 \times V_{in}}{C_{timing}(\mu F)}$$

Modulation voltage V_{in} should be kept between 0.4 and 9.1 volts for reliable operation. The upper sinusoidal AC limit for the modulated input is about 20 kHz, limited by op-amp frequency response.

Another potential use for the function generator is to measure capacitance. By switching S1 to the C_{EXT} mode, different output frequencies will be produced by different-valued capacitors. If you have an oscilloscope or a frequency meter, there will be an inverse relationship between frequency and capacitance. You thus have a new way to measure capacitance.

R-E

BUILD THIS

Digital Capacitance Meter

Part 2—A valuable addition to your workbench that lets you check the value of unmarked and suspected capacitors.

BILL WILSON AND BILL OWEN*

CAPACITOR VALUES FROM 1 pF TO 9,999 μF are easily measured using this digital capacitance meter. A quartz timebase, precision resistors and a premium IC timer yield 1% \pm count accuracy. Story begins in the September issue.

Construction

The *model CM-1000* is constructed using two double-sided plated-through glass-epoxy PC boards. The display board contains a complete four-digit counter and requires only power, ground, clock input, latch enable, and three decimal point connections. This arrangement greatly simplifies the building, testing and interfacing of the display and main counter boards. The remaining circuitry with the exception of the fuse and line cord is installed on the main counter board. The POWER/RANGE switch module solders directly to the main counter board eliminating almost all of the point-to-point wiring. The electronics assembly bolts in place in the custom black anodized heavy-gauge aluminum enclosure. The front panel is cut out for the push-button switch module and has a window with a high contrast lens for the LED digits. The front panel controls are labeled with a two-color silk screen. The instrument top is extended forward to protect the LED digits from direct overhead light and the instrument bottom has a tilt stand for angled viewing. Four machine screws recessed in each side allow easy removal of instrument covers.

*Product Engineers, Optoelectronics, Inc.



An exploded view of the meter assembly is in Fig. 3.

Begin construction with the two PC boards. Figures 4 and 5 are foil patterns for the bottom and top sides of the master board while Fig. 6 shows the component layout. Similarly, Figs. 7 and 8 are foil patterns for the display board while Fig. 9 shows parts placement. All components, with the exception of the POWER/RANGE switch and trimmer capacitor C2, mount on the component screened side of the PC board. Refer to Figs. 5 and 6 for component placement. Use a 20- to 25-watt small-tipped soldering pencil and small diameter solder. Be careful not to force solder through the plated-through holes as shorts can result from solder pools on the component side of the PC board. Do not install the IC's at this time.

The POWER/RANGE switch assembly is installed using No. 4 1/16-inch-thick fiber washers next to the PC board. See Fig. 3 for assembly details. Assemble the front and rear panels and side rails using hardware provided. Set the assembled PC boards in place on the chassis. The main counter board bolts to the side rails at four locations. When the two PC boards are aligned there are eight mating pairs of foil fingers that will be soldered to connect the two boards. Place a 1-inch piece of excess component lead in the hold in the third finger from each end of the display board. With the component lead wires centered in the display board as shown, solder to the foil finger and bend each side of both wires down to align with

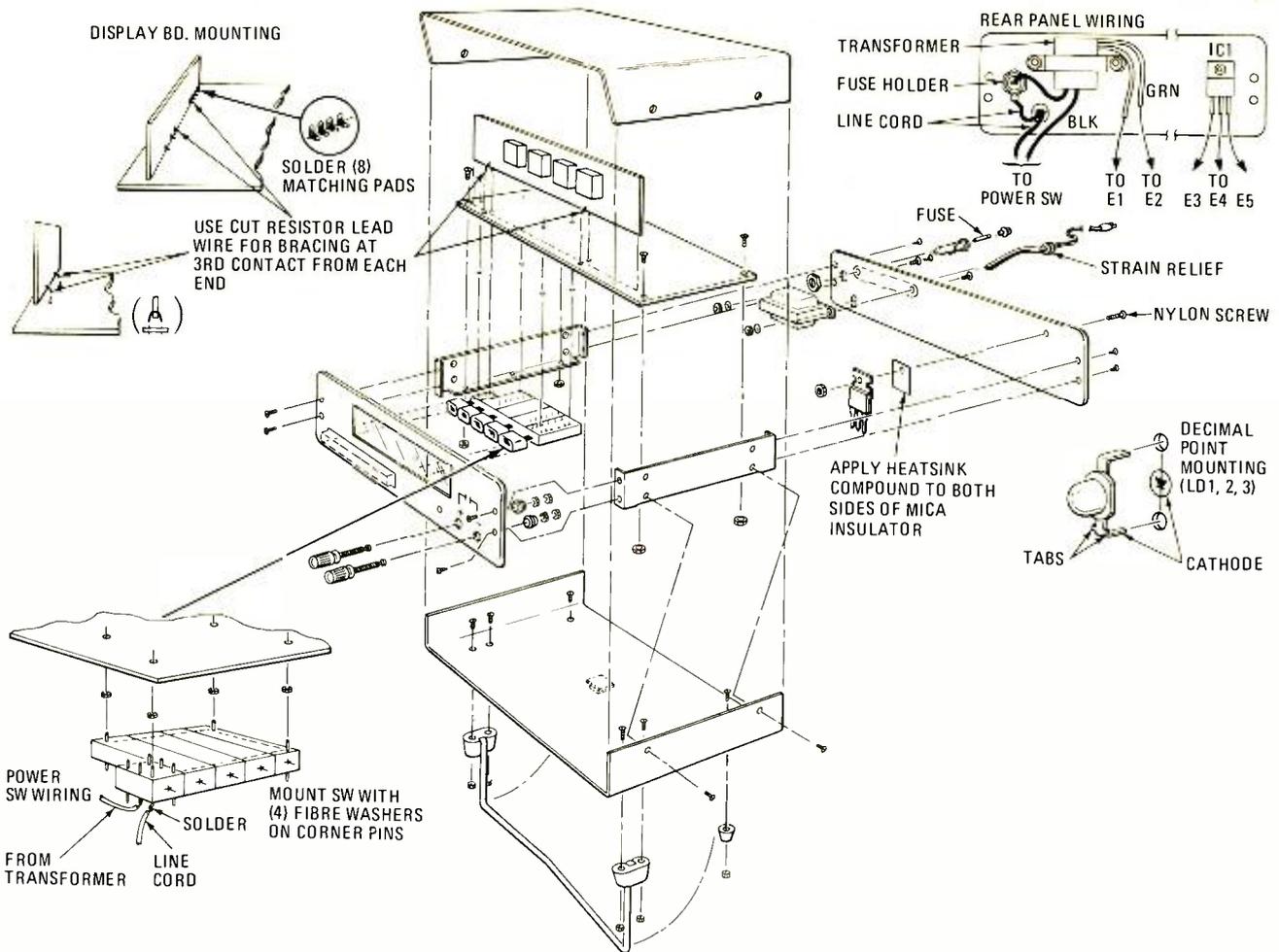


FIG. 3—EXPLODED VIEW of the model CM-1000 digital capacitance meter. Parts are as supplied in the kit. Use this as a guide if you build your meter from scratch.

PARTS LIST

Resistors are 10%, 1/4 watt unless otherwise noted

- R1—243,000 ohms, metal film, 0.25%, 1/8 watt
- R2—11,300 ohms, metal film, 0.25%, 1/8 watt
- R3—2430 ohms, metal film, 1%, 1/8 watt
- R4—220 ohms, 5%
- R5, R8, R21—100 ohms, carbon potentiometer, 1 watt
- R6—243 ohms, metal film, 1%, 1/8 watt
- R7—33 ohms, 5%
- R9, R11—10,000 ohms
- R10—3300 ohms
- R12, R14—330 ohms
- R13—6.8 megohms
- R15—8.2 megohms
- R16—180 ohms
- R17-R19—2200 ohms
- R20—1000 ohms
- R22—11 megohms
- R23-R26—100 ohms
- R27, R28—4700 ohms
- C1—47 pF NPO disc
- C2—15-60 pF, ceramic trimmer

- C3, C13, C19, C23—0.47 μ F, 50 volts
- C4, C5—3.3 μ F tantalum
- C6—.001 μ F
- C7, C8, C9, C11, C12, C14, C17, C20, C27, C28—0.1 μ F
- C10—.01 μ F
- C18—.02 μ F
- C21—3300 μ F, 16 volts, electrolytic
- C22—220 μ F, 25 volts, electrolytic
- C24—33 pF NPO disc
- C25—8.2 pF NPO disc
- C26—470 pF disc
- D1-D4—1N4002 silicon rectifier diode
- IC1—556 dual timer
- IC2-IC4, IC12, IC14, IC16, IC18—74LS90 decade counter/divider
- IC5—74LS73 flip-flop
- IC6—4001 quad NOR gate
- IC7—74LS04 hex inverter
- IC8, IC9—74LS00 quad 2-input NAND gate
- IC10—SE555 precision timer
- IC11—voltage regulator, 7805
- IC13, IC15, IC17, IC19—4511 BCD to 7-segment decoder/driver

- DIS1-DIS4—MAN-6680 7-segment LED display
- XTAL1—quartz crystal, 3.579 MHz
- S1-S5—5-gang SPST pushbutton switch
- T1—power transformer, 117 VAC primary, 10 VAC secondary
- J1, J2—insulated banana jack
- F1—120-volt, 125-mA fuse
- Miscellaneous: PC boards, 1 8-pin IC socket, 4 16-pin IC sockets, 14 14-pin IC sockets, line cord, hardware

The following parts are available from Optoelectronics, Inc., 5821 N.E. 14 Avenue, Fort Lauderdale, FL 33334.

CM-1000K Complete Kit	\$129.95
CM-1000WT Factory Wired & Tested	179.95
CM-1000 PC Boards Only	24.95
P-1000K Cap. Counter Probe Kit	3.95
P-1000 Assembled Probe	6.95

Add 5% shipping, handling and insurance, for foreign orders add 10%. Florida residents add 4% State Sales Tax.

holes in the main counter board. Insert the wire ends in their respective locations on the main counter board and push the display board down until the foil finger pairs touch. Check alignment to see that the display board is at right angles to the counter board and that the foil fingers are

perfectly aligned. Solder the wires to the main counter board and after rechecking alignment solder the matching foil fingers together.

Feed 6 feet of the AC line cord through the back panel and secure using plastic strain relief. Mount the transform-

er, fuse holder, using hardware provided on the back panel where indicated. Wire one side of the AC line through the power switch to the transformer primary as shown. The other side of the AC line runs to the other side of the transformer primary through the fuse holder.

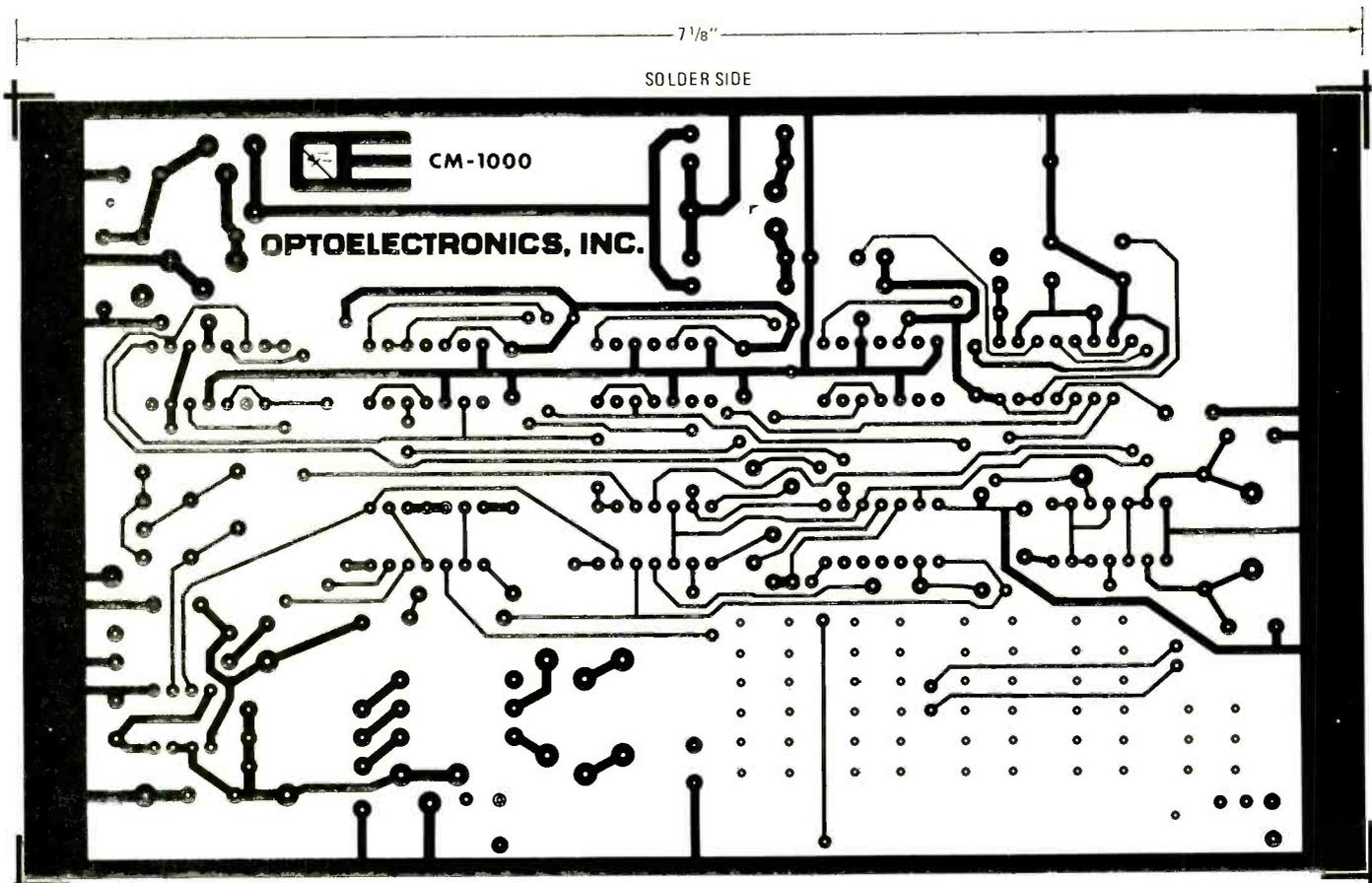


FIG. 4—FOIL PATTERN for the bottom (solder) side of the main board.


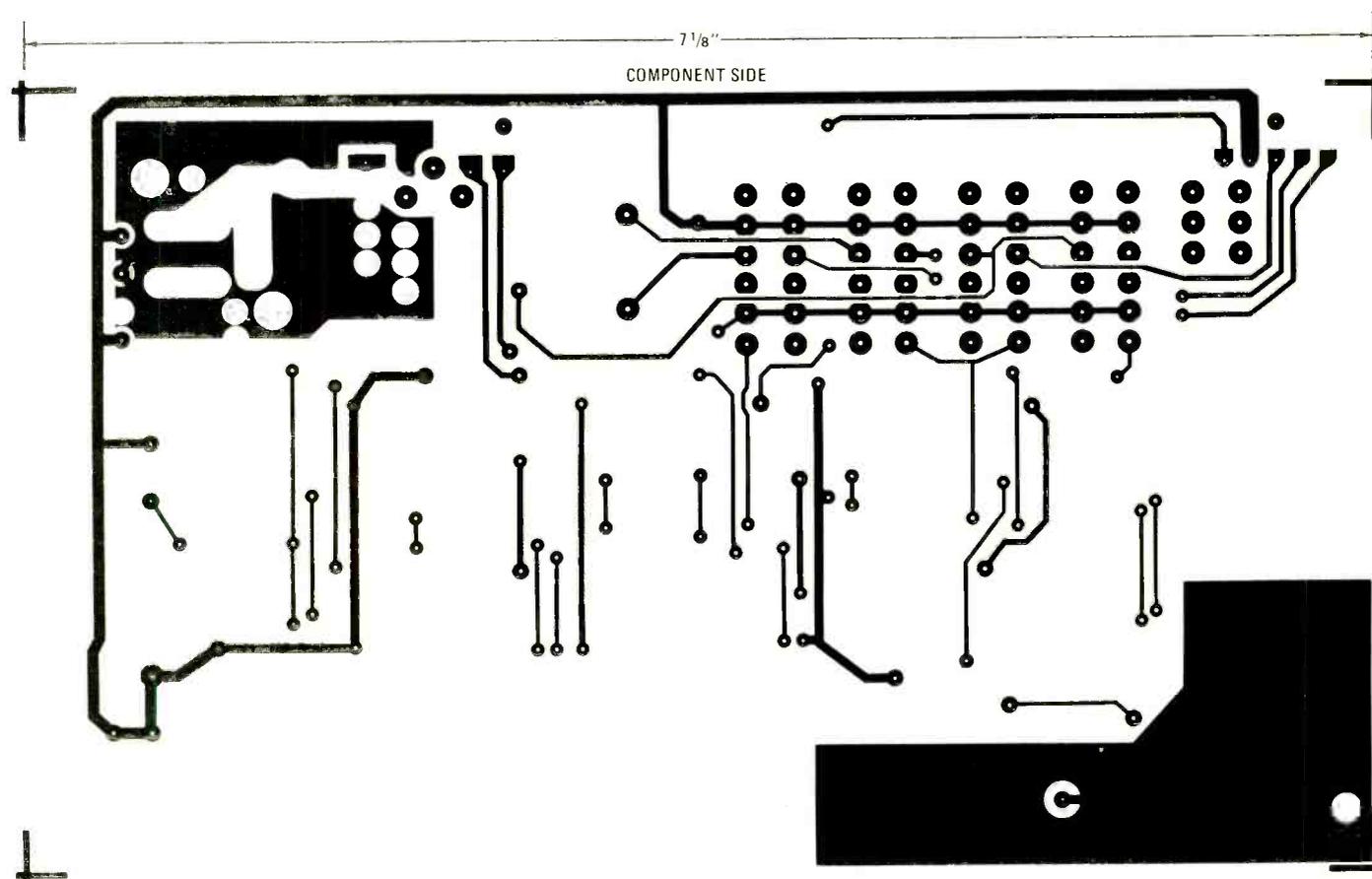



FIG. 5—COMPONENT-SIDE foil pattern. Board supplied in kit has plated-through holes. Compensate for lack of hole plating if you make your own boards.

Before installing IC's into sockets, perform a simple test by plugging in the AC power cord and depressing one of the range switches. Connect a voltmeter between the negative input terminal on the front panel and test point 1 (TP1). It

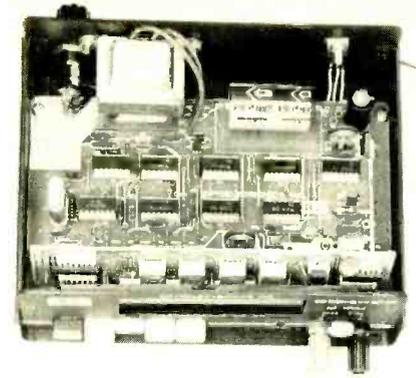should be possible to measure 5 volts DC by adjusting R21. If the voltage checks, then install all IC's in their sockets making sure that the notch on the IC is aligned with the outline on the printed-circuit board.



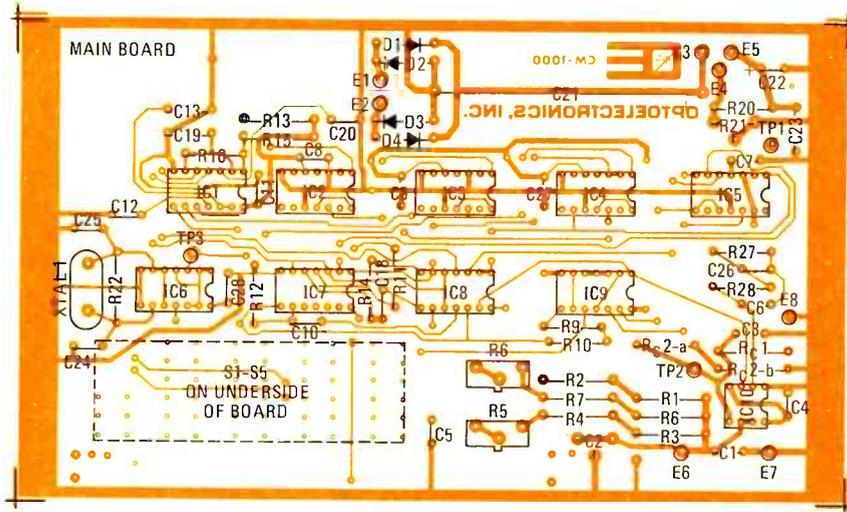INTERIOR VIEW of the Optoelectronics model CM-1000 digital capacitance meter.



Calibration

With IC's installed, reapply power and adjust TP1 for +5 volts referenced to ground. Depress the R1/PF switch and use a small bladed screwdriver to turn the ZERO ADJUST control (trimmer capacitor C2) until a reading of 0001 is observed. Continue to turn the control until the "1" turns to "0." **Do not adjust any further.**

The next step requires the use of an accurately known capacitor. The parts kit

FIG. 6—COMPONENT LAYOUT for the main board. Trimmer capacitor C2 is mounted on underside of board. See text on R₁ and R₂.

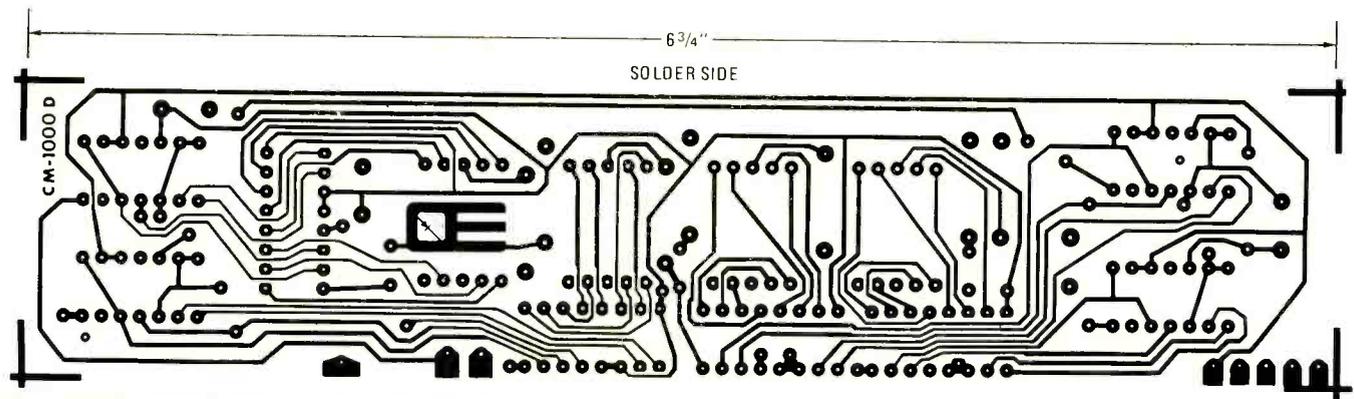


FIG. 7—BACK SIDE OF DISPLAY PANEL is etched with this foil pattern.

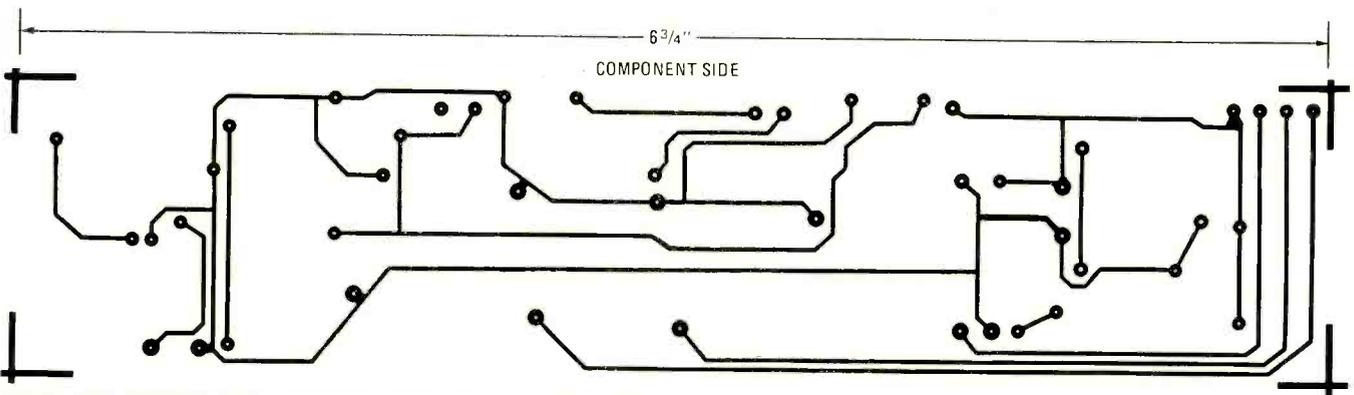


FIG. 8—FOIL PATTERN for the component (front) side of the display PC board.

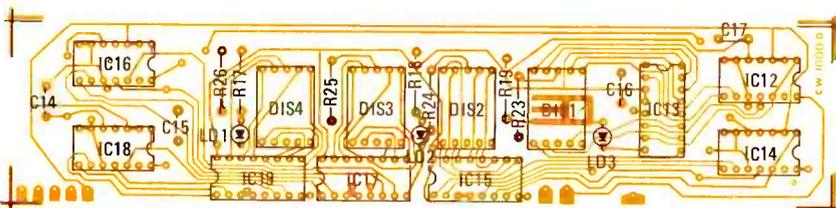


FIG. 9—DISPLAY BOARD components are laid out as shown. Decade counters and driver IC's are on board along with the LED displays and a few capacitors and resistors.

includes a calibrated capacitor with its value marked on the package. Connect this capacitor across the input terminals and depress the R3/μF switch. Adjust trimmer R5 to produce a reading equal to the value given.

Use a low-leakage capacitor between 10 and 22 μF to calibrate range R4/μF with trimmer R8 by comparing its reading to that observed on the previously calibrated R3/μF range. **R-E**

BUILD THIS

Frequency Counter In A Probe



Part 2—Completely self-contained in a handy probe, this frequency counter was constructed using a unique assembly method that makes possible an instrument that is rugged, compact and convenient to use.

WALTER T. CARDWELL, JR.

Beginning last month, this article describes an instrument that is constructed using an unusual technique (see "IC Bricklaying" in the December 1977 issue). Counter measures to 2.5 MHz with 10-Hz resolution.

Now build one

Figure 4 shows component placement using the "bricklaying" technique and keying of sockets S01 and S02. Glue a 12-pin socket on each end of the block of IC's, and a 1/16-inch acrylic plastic spacer between the socket pins. Then clip the socket flush with the spacer to allow 1/16-inch of space for soldering leads to the socket. Cut the sockets from an 80-pin PC-board edge connector.

The case is made from black opaque acrylic plastic. Glue a 1/8-inch-thick piece, as wide as the IC block, to the sides of the sockets at each end. On the front, glue a 1/16-inch black opaque piece of plastic to a 1/16-inch piece of transparent amber plastic; this strip is then glued to the front side with the transparent part placed over the readouts. Use cyanoacrylate glue, but don't get glue on the plastic surface.

Once the two sides are in place, file the top and bottom of the block flat using a metal file. You can curve the top to make it more comfortable to hold and easier to identify. When you file the block, bring the sides down as close to the IC's as possible to keep the overall size of the meter small. Be careful of the wires when you file. If the wiring is covered with tape, you are safe until the tape is marked by the file. You may have to add shims to the top of the sockets if the sockets are not as thick as the IC block. Once the top and bottom have been filed, glue two more pieces of 1/16-inch black plastic to the top and bottom. If you use cyanoacry-

late glue, you can open the case easily by inserting a razor blade along the seam.

The square block that plugs into the back is the battery pack and is made from 1/16-inch glass-epoxy double-sided PC board. The battery case is also made of black acrylic plastic. The meter is powered by 20 mA NiCad button cells. Also included in the power supply is a 2-volt reference, using an MC1403 IC and a 1000-ohm, 10-turn trimmer (see Fig. 5). This voltage reference will be used by certain meter accessories (still on the drawing board) that will plug into the front of the unit. You can use larger batteries if you don't find their weight and size objectionable.

The probe tip on the front contains the blocking capacitor, the X10 prescaler and hold switch. A CD4013 dual-D flip-flop generates the hold and X10 signals. The two dots on the top of the probe tip are two small copper nails inserted through a 1/4-inch black plastic strip and filed flush. These nails serve as a touch-control switch (S2) to select the X10 range. One side is connected to the +5-volt supply through a 100,000-ohm isolation resistor, as shown in Fig. 6-a. Placing your finger across the pins charges capacitor C2 through resistor R3 and the skin resistance. Diode D1 and capacitor C2 must be used to eliminate the 60-Hz charge that the body receives from the

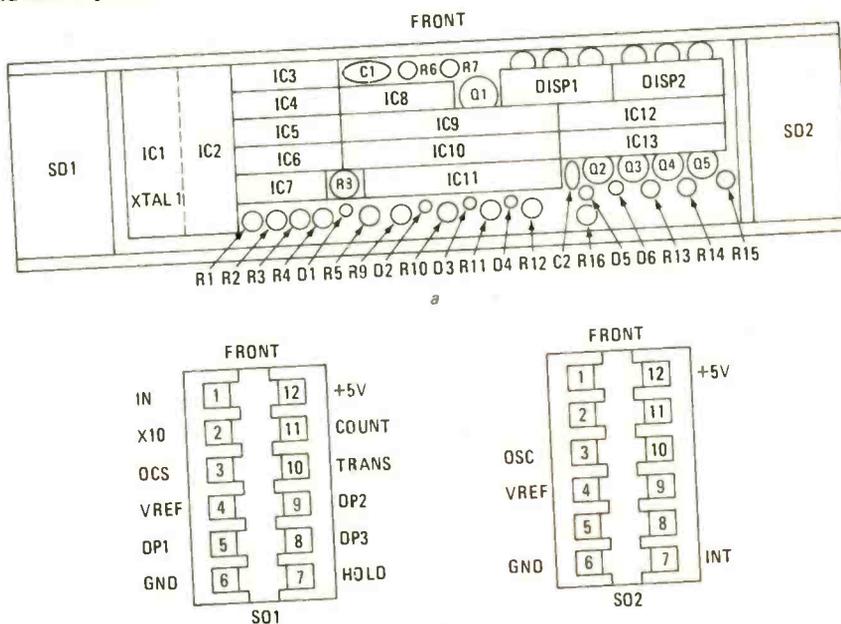


FIG. 4—INTERNAL LAYOUT of probe showing component placement. Location of signals on socket pins is shown in b.

F E C gi is fo tr: es cr yo va

power lines. Resistor R2 discharges capacitor C2. Charging C2 sets the dual-D flip-flop; the X10 input is high and the DP1-display is low. As soon as connector S goes low, output from the 3.57-MHz oscillator resets the flip-flop.

The clear plastic front holds momentary contact switch S1. Cut the front piece from 1/2-inch clear acrylic plastic, which you then glue to the front of the

completed black plastic back section of the unit. Sand both pieces with 100-grit sandpaper in a disc sander until you obtain the final shape (see Fig. 6-b). The drawings do not show dimensions since the size depends on the components used. Sand the probe tip with finer-grit paper, stopping at 400 grit.

Once the shape is roughed out, remove the clear plastic section with a razor

blade. Drill a 1/16-inch hole through the center to hold the wire probe tip, which is made from 1/8-inch piano wire ground to a point. Wrap AGC No. 10 copper wire once around the back end and silver-solder it using a propane torch. Then, file the copper until the tip resembles a long flathead nail.

The 1/8-inch hole in the clear acrylic plastic is drilled out from the back deep enough so that the SPST miniature push-button switch fits completely in the clear plastic section. Remove the pushbutton and metal section. Then, remove a white spacer on the red pushbutton to the end of the copper head on the probe tip. Room is hollowed out in the clear plastic to contain the switch lugs, which are bent at right angles to the switch body.

Solder two wires to the copper part of the probe tip. These wires must be flexible; we recommend phonograph pickup wires. Before assembling the switch, glue the clear plastic back on the probe front. Then, to restore the gloss on the plastic, polish the entire unit, using jewelers' rouge on a cloth buffing wheel. Be careful not to let the edges catch in the buffing wheel.

Calibration is the next step

After the probe tip is polished, you can assemble it. Unglue the clear plastic section again and file off the old glue from both sections. Push the probe tip through the 1/8-inch hole that was drilled in the clear plastic section. Insert first the spring and then the flat contact disc into the switch body. Place the switch assembly in the back of the clear plastic section and glue it in place. There should be sufficient room at the front of the switch body to allow the wires on the probe tip to move. Check the switch to make sure that it closes when the probe tip is pushed in. When the switch is finished, connect the wires to the switch, and the probe tip wires to the input capacitor. The clear plastic section is now glued to the front permanently. Any glue that appears on the surface can be removed with the buffing wheel. Be especially careful of the sharp point waiting to get you if it catches in the wheel!

When the tip is pushed in, the meter will convert until it is removed. The count will be held as long as the tip is not pushed in. When the prescalers are added you insert them between the probe tip and the meter body.

The usefulness of the basic frequency probe can be greatly expanded by accessories that plug into the main body. You can add a 5-volt calculator battery eliminator so that the meter can function off the AC power line. You can also construct a new front section so that you can use the probe as a normal bench meter. You can also add a 20-MHz to 125-MHz prescaler. Due to the construction of the main body, the number of accessories you can add is almost unlimited.

R-E

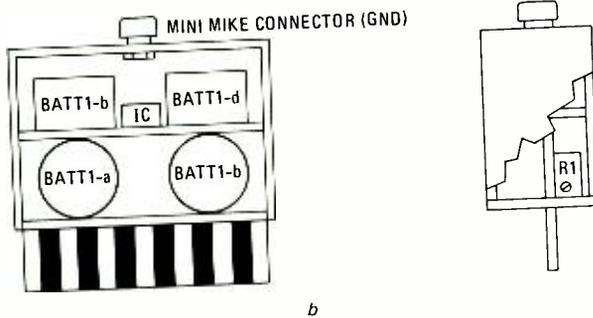
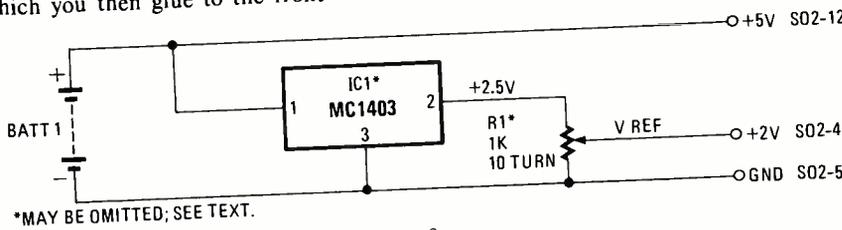


FIG. 5—POWER SUPPLY SCHEMATIC AND PARTS LAYOUT. The MC1403 voltage-regulator IC and the 1K pot are for a 2-volt source used as a reference for accessories not yet completed.


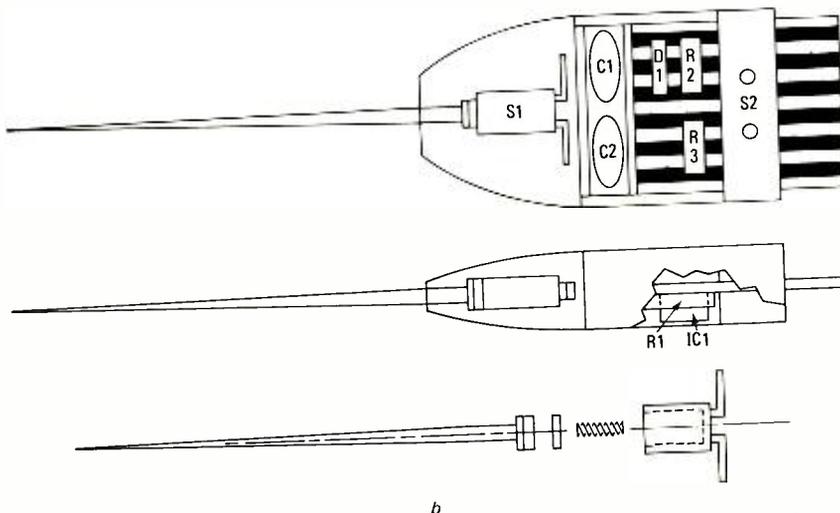


FIG. 6—CONSTRUCTION AND SCHEMATIC DIAGRAM of the probe front-end. The prescaler uses a CD4013 and is turned on by touch switch S2 consisting of two tiny nails.

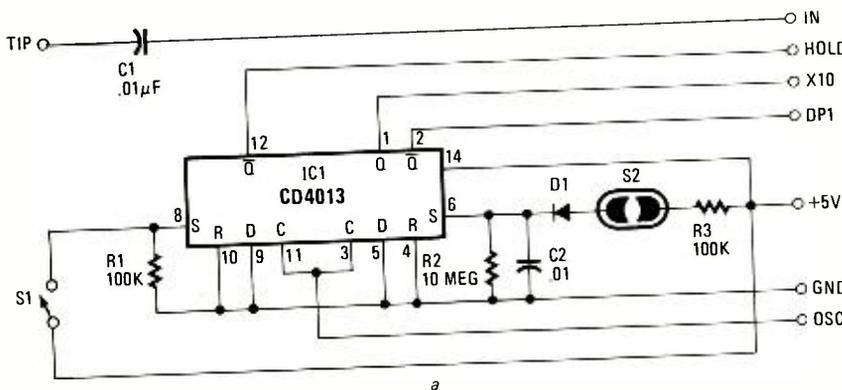

You Can

An installment of a continuing series
readiness to qualify as a

CHAPTER 4

TRY YOUR HAND AT THESE SAMPLE TEST questions on transistors and semiconductors. The answers to this month's and a new set of questions will appear in a future issue of **Radio-Electronics**. When you feel ready to take the CET Exam write to ISCET: 310½ Main St., Ames, IA 50010. Ask for the name and number of the nearest Certification Administrator, and take the CET exam.

Chapter 4 Questions, transistors and semiconductors

1. A good method of determining if the transistors are operating in a Class-A circuit, such as an audio amplifier, IF or RF amplifier, would be to check the:
 - () a. collector-base voltage
 - () b. bias voltage
 - () c. emitter-collector voltage
 - () d. base voltage
2. In a Class-A transistor amplifier cir-

cuit using a NPN silicon transistor, which of the following conditions would appear to be normal?

- () a. collector -5V; emitter 0V
 - () b. base -5V; collector -5.6V
 - () c. emitter -5V; base -5.6V
 - () d. collector -5V; emitter -10V
3. Which of the following statements regarding Zener diodes is true?
 - () a. a Zener diode will operate the same as any low-current solid-state diode if forward-biased
 - () b. a Zener diode will operate the same as any low-current solid-state diode if reverse-biased
 - () c. variations in the reverse-current flow in a Zener diode will cause similar variations in the Zener diode voltage level
 - () d. most Zener diodes are germanium

4. Which of the following statements is true regarding FET's (Field Effect Transistors)?
 - () a. the gate voltage necessary to cause the FET to cut off is called the "pinch-off" voltage
 - () b. the channel of a FET must be of 'N'-type material
 - () c. MOSFET's are immune to static charges
 - () d. the difference between a junction FET (JFET) and a MOSFET is that the JFET has an insulated gate to reduce reverse-bias gate current

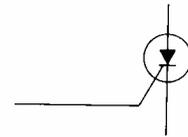


FIG. 1

Correct answers to Chapter 3 Questions on DC circuits

Here are the answers to the questions on DC circuits that appeared in the September 1978 issue.

1. **Correct answer is "d."** A scope calibrated for vertical deflection of 100 volts-per-inch will show about 3.3 inches of peak-to-peak deflection. An AC RMS meter would show 117 volts AC because the meter first rectifies the AC voltage and then reads the effective voltage, not the peak-to-peak voltage as the scope displays. Peak-to-peak voltage is 2.82 times RMS.
2. **Correct answer is "b."** High frequencies are bypassed to ground through the capacitors. Low frequencies (such as vertical-sync pulses (60 Hz) in TV sets) find the capacitive reactance high, while high frequencies

(such as the 15,750-Hz horizontal-sync pulses) find the capacitive reactance low, and are passed to ground—or filtered out—by the circuit. Low frequencies will appear at the output.

3. **Correct answer is "d."** The formula for impedance in a series LRC circuit is:

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

In this example X_C and X_L are equal and therefore would cancel. This leaves only the resistance as a factor, or a total of 10 ohms. The formula with X_C and X_L canceling would be: $Z = \sqrt{R^2}$. The square root of R_2 is

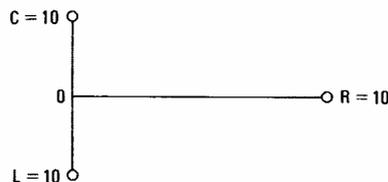


FIG. 3

ANSWERS TO

R, or 10 ohms. Figure 3 shows that L and C reactances are opposite each other, and ninety degrees from R. Being equal they cancel each other, which leaves only 10-ohms resistance as the effective impedance.

4. **Correct answer is "b."** Figure 4 can


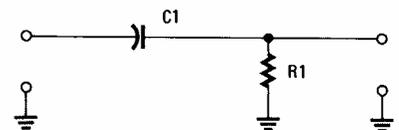


FIG. 4

be a differentiating circuit. Where it is used as such, the high-frequency response is good (the capacitor will charge quickly to a maximum value); the low-frequency response is poor (a squarewave will be reformed into a "peaky wave." See Fig. 5.)

5. **Correct answer is "d."** If X_L and X_C are equal, the frequency must be resonant. Higher frequencies will be

Be A CET

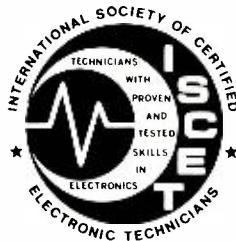

of questions aimed at checking your
Certified Electronic Technician

DICK GLASS

5. The symbol shown in Fig. 1 is a:
- () a. MOSFET
 - () b. thyatron
 - () c. tunnel diode
 - () d. SCR
6. A tunnel diode is most likely found in which location?
- () a. a power supply
 - () b. the horizontal or vertical oscillator circuits of a TV set
 - () c. a UHF tuner
 - () d. an audio detector
7. The gain-bandwidth product of a transistor can tell you:
- () a. the frequency at which the gain has decreased to 0.707 times the gain at 1000 Hz
 - () b. the frequency at which the gain has decreased 3 dB from the gain at 1000 Hz
 - () c. the frequency at which the gain has decreased to 1

- () d. none of the above
8. A frequency correction circuit using a transistor rather than a varactor uses which two elements as the variable capacitor?
- () a. collector-base
 - () b. emitter-collector
 - () c. all three elements must be connected
 - () d. emitter-base
9. What type of transistor is shown in Fig. 2?
- () a. a triac

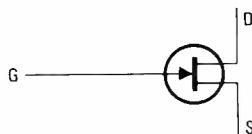


FIG. 2

- () b. an N-channel JFET
 - () c. a P-channel JFET
 - () d. a unijunction transistor
10. In most high power-output transistors used in radio, amplifiers and TV receivers:
- () a. the case is connected to the emitter
 - () b. the case is connected to the base
 - () c. the case is connected to the collector
 - () d. the case should be grounded for better shielding

Be sure to keep this month's issue of **Radio-Electronics** so you can check your answers in the next CET test. The new questions appearing in the next CET test will be on electronic components and circuits. **R-E**

PRIOR QUIZ

(September 1978)



FIG. 5

shunted through C, and the lower-than-resonance frequencies find L an easier path to ground. Only the resonant frequency finds X_L and X_C equal. The circuit responds to the resonant frequency, all others—higher or lower—to a lesser degree.

6. **Correct answer is "a."** Refer to discussion in answer 5 above.
7. **Correct answer is "d."** The time constant or R-C time for the cathode circuit is as follows:

$$t = R \times C$$

in which t is the time it takes for the capacitor to charge to 63% of full charge.

$$t = 4700 \times 1 \mu F$$

$$t = 4700 \times .000,001$$

$$t = .0047 \text{ seconds, or } 4.7 \text{ ms}$$

8. **Correct answer is "c."** A resistor in series with either leg of a parallel L-C circuit changes the resonant frequency. It therefore could be used to tune such a circuit. (Many practical technicians would instinctively select answer "b" as the correct one. However answer "c" is technically correct. The exact formula for the *natural resonant frequency* f_n is:

$$f_n = \frac{1}{2\pi} \sqrt{\frac{1}{L-C} - \frac{R^2}{L/L^2}}$$

When the value of R is small compared with $2\sqrt{L/C}$, natural resonant frequency f_n approaches resonant frequency f_o (when $R=0$) and is approximately equal to

$$\frac{1}{2\pi \sqrt{L-C}}$$

The resistance in an L-C circuit affects its Q, and, therefore, also its bandwidth. The circuit Q value must be less than 4 for f_n to differ from f_o by 1%. In the average practical circuit, the Q is at least 50. In this case, f_n and f_o differ by 1 part in 20,000. For further reading, see Terman's *Radio Engineering*, 3rd Edition, 1947, and *Radiotron Designers Handbook*, 3rd and 4th Editions.—RFS)

9. **Correct answer is "b."**
- $$X_L = 2\pi f_L$$
- $$X_L = 6.28 \times 15,750 \times 5$$
- $$X_L = 494,550 \text{ ohms}$$
10. **Correct answer is "b."** To reduce 27-MHz interference you would use a high-pass filter to shunt the 27-MHz signal, yet pass the desired 54-MHz to 216-MHz signals. **R-E**

HOBBY CORNER

Where to get parts, substituting parts and wiring prototype projects.

EARL "DOC" SAVAGE, K4SDS, HOBBY EDITOR

VERY OFTEN READERS OF HOBBY CORNER come up with some good questions of general interest. Then, also, some questions appear again and again, showing rather widespread problems. Here are a few that might include some answers you need.

1. Where do you get the components to build your projects? To be perfectly honest, most of the components come out of my "junkbox" (that's what hams call whatever holds their component inventory—a shoebox, cabinet, cigar box, shelf, etc.). So a better question might be: "Where do I get the stuff to put in the junkbox?" I do manage to keep a fairly good stock of many kinds of components, and I work at keeping the stock up as it is used. Here's how I do it.

Perhaps the best way to build up a stock of components is to buy mixed assortments of resistors, capacitors, LED's, coils, transistors, IC's, and so forth. Mixed assortments can usually be bought for a low unit cost, so you can save 50% to 90% over the cost of individual components. Then, if you use only half of them in the course of time, you are still ahead. Of course, you won't have a choice of size or value buying components this way, but remember, if you don't have any on hand as you build a project, you'll have to buy each one you need at full price.

My assortment purchases come from several sources but mainly from surplus mail-order suppliers. I read the ads carefully in the back of *Radio-Electronics* each month and keep the postman busy delivering the flyers, catalogs and parts I have ordered.

Another source of components is from sources offering small bulk purchases. When I discover a commonly used part (for example, a 2N2222 or 7400 or 1N4004) and the price is especially favorable, I order 10 or 25 or more, even though I have no immediate need for them—sooner or later they will be used. These bargains are found in catalogs but most often in ads as monthly specials.

Another source that bears watching is the local retail outlet if you have one nearby. Every few months they take inventory and order in an especially big shipment. Someone usually decides that

certain items should no longer be carried; then those parts go on a "bargain table." I have found that prices vary from store to store, but you can save from 25% to 50% when you find useful goodies on the bargain table.

As time goes by, you can build up a good stock from these and other sources. Another source you should not overlook, especially if you are just beginning to accumulate components, is old equipment. Anytime someone offers you a TV, radio, recorder, amplifier, or anything electronic, accept it! Very rarely does something like that come along that won't yield at least a few parts. I guess most of us started our junkboxes with *real* junk. You can find all sorts of components in those discarded sets—speakers, tubes, transistors, resistors, capacitors, transformers, dial lamps, sockets—they can be a real gold mine. (However, watch out for picture tubes—they can implode and cause severe damage!)

No matter how you go about it, however, you can't stock everything even if you try. Remember *Doc's law*: No project can be completed with just the components on hand! You'll always need something else to make it work.

At the start of a project when I discover something is missing, I try to find it locally to save time. I check the local retail stores, and then, if necessary, one or two of the wholesale distributors. As a final resort, I order the component and impatiently await its delivery.

In any case, I have found that time and money are saved by accumulating a stock of parts. I believe you will also find this useful.

2. I am a beginner in electronics and I want to build the projects you write about. Do I have to use exactly the same parts that you list? The answer to this is: Yes and no! There are times when you must use the exact value specified in a schematic. Fortunately, such instances are not frequent but you will experience them. You should always read very carefully both the text and any special schematic notes before starting any project.

In the Hobby Corner projects, I always try to indicate any parts that are critical in type or value; most other construction

project articles also do this. Of course, there are times when you just *know* it makes a difference. For example, in a coil-capacitor tuned circuit or a resistor-capacitor timing circuit, you know that a change of value changes the frequency.

Most of the time, however, component values simply are not critical. Usually, the next standard value up or down is sufficient. An even greater difference will often do the trick, too. In fact, marked values are normally 10% or even 20% tolerance.

We sometimes fall in the trap of thinking of values as absolute just because they are numbers. If a capacitor is marked .01, we think of it as *exactly* .01 even though the chances of that being true are pretty slim unless we pay a premium price for a precision (low-tolerance) capacitor. So, when a schematic calls for a 5000-ohm resistor, for example, and you put one in marked 5K, it could range from 4500 ohms to 5500 ohms, or more!

Now you can see why the next standard value almost always works—it may be closer to the specified value than one so marked. Note that the 5K 10% resistor could be 5500 while a 5.6K resistor could be 5040 ohms!

Let's take a look at a typical case. Figure 1 shows part of a transistor amplifier stage in which R1 and R2 form a

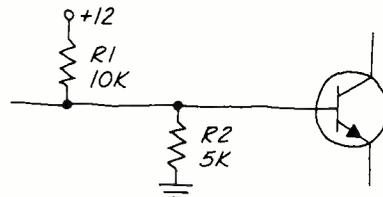


FIG. 1

voltage divider that is expected to provide +4 volts on the base of the transistor.

$$(12 \times R2) \div (R1 + R2) = 4.$$

But suppose R1 is 11K (10K + 10%) and R2 is 4.5K (5K - 10%). The base voltage would be 3.48, or if the resistors went the other way, the base voltage could be as much as 4.55.

The situation would be even more variable with 20% resistors (use some values in the formula to see just how much it would vary). The point is that unless 1% or 5% components are specified, the values range all over the countryside.

The next value up or even two greater

works just as well in most circuits. In substituting resistors and capacitors you should stay within the power and voltage ratings, however. If a 2-watt resistor is specified, you must use one that is 2 watts or larger. If a 16-volt capacitor is specified, make sure to use one that is rated 16 volts or more.

However, what do you do when you can't even come close to the specified value with the components you have on hand? Purchase what is needed or make them yourself if there is space in the project for one or two extra components. Note that I keep mentioning resistors, but the same principles apply to capacitors, inductors (coils) and other components.

You should always keep in mind the simple formulas for resistors and capacitors in series and in parallel. For example, suppose you need a 15K resistor. Do you have two 33K resistors to hook in parallel?

$$\frac{R1 \times R2}{R1 + R2} = \frac{33K \times 33K}{33K + 33K} = 16.5K.$$

Or how about two 6.8K resistors in series?

$$6.8K + 6.8K = 13.6K.$$

Or a 5.6K, an 8.2K and so on. Of course, capacitors work identically except that the series and parallel formulas are reversed.

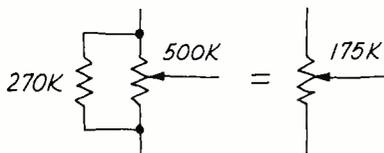


FIG. 2

This method of making your own components can also be quite handy with pots. A reader asked recently where he could obtain a 150K pot, stating he could only find values of 100K and 500K. I advised him to make the pot (see Fig. 2). The 500K pot in parallel with the 270K fixed resistor works similar to a 175K pot; this is close enough for most purposes. Actually, it's also possible to measure a handful of 20% resistors to find one at 200K, and that would yield the equivalent of a 153K pot!

With rectifier diodes, use substitutes that have an equal or higher Peak Reverse Voltage (PRV or PIV). A 50 or 100 PRV diode replaces a 25 PRV diode in almost any circuit—or two 25 PRV's can replace a 50 PRV (with equalizing resistors).

Most LED's have almost identical electrical values. They come in different sizes and colors and have different lenses, but one will serve as well as another in all but the most critical circuits.

The same holds true for most digital readouts, although if the ones you substitute differ greatly in size, you should check the current requirements. Of

course, you cannot interchange common-cathode and common-anode units without also making other circuit changes.

Transistors are hard to keep up with because there are so very many types. Most circuits work with *dozens* of different numbers. Usually it is a good idea to stay in the same transistor "families"—NPN, PNP, FET, audio, RF, silicon, germanium (even *this* list could go on forever!). Certainly you should have a transistor substitution book near your workbench.

There you have the parts story, or most of it at least. You seldom have to use the part exactly as specified. Use what you have that is in the right ball park and see how it works. I do it all the time as do all experienced builders. By the way, that's why I always run up a circuit on a solderless breadboard before building it permanently—I want to see if the circuit works properly with the components I have on hand.

3. What's the best way to wire a project? You came to the right place with that one! The truth is, I spend a lot of time trying to figure out the quickest and easiest way to build a project. I guess that's why I like the pencil wiring.

Over the years I must have tried every possible means of wiring. Of them all, I have settled on pencil wiring for most of my projects. It is effective and neat but, best of all, it is easy and *fast*.

You must understand that pencil wiring will not replace all the other wiring methods. I haven't given up wire-wrapping, PC boarding or even the old cut/strip/hook techniques—they still have their uses. However, most of my IC and transistor circuits are ideally suited to pencil wiring.

All you have to do is use a pencil-like device that also holds a roll of wire. As you move the point from place to place, just make a couple of loops around the components to be connected. Then go back and solder each joint—there's no need to scrape off the insulation because it vaporizes when it is touched with the hot iron.


I just finished wiring a project using Vector's new *model P178-1* wiring pencil (Vector Electronic Company, Inc., 12460 Gladstone Avenue, Sylmar, CA 91342). Vector's old model wiring pencil performed quite well, but this new slim one fits my hand better and gives me improved control. With its long metal snout, the wire can be laid exactly where you want it as you move quickly from one connection to the next. *What?* You've never done any pencil wiring? According to a once-popular expression, try it, you'll like it!

I hope these reader questions and answers have been interesting and helpful. If so, from time to time, we'll take a look at some more of them. **R-E**

Now you can safely plug away without the problems of overload or coming up short.

SGL WABER® MULTIPLE OUTLET STRIPS

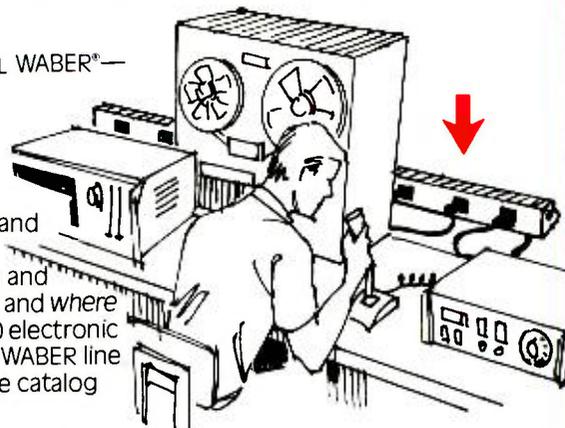You can do it thanks to SGL WABER®—the finest quality multiple outlet strip available! There are 240 versatile models—each unit exceeds National Electrical Code standards and is safety tested. Ideal for organizing your work area and having extra outlets *when and where* you need them. Over 2000 electronic distributors carry the SGL WABER line. Send for your free 24 page catalog today!



SGL WABER Electric

A division of SGL INDUSTRIES, INC.
Dept. H—300 Harvard Avenue
Westville, New Jersey 08093
(609) 456-5400

SGL Waber...THE POWER SOURCE IN ELECTRICAL OUTLET STRIPS

CIRCLE 25 ON FREE INFORMATION CARD

COMPUTER CORNER

8085 How to use the 8085 with an A/D converter to monitor eight analog channels.

P. RONY, D. LARSEN, C. TITUS AND J. TITUS*

THIS MONTH'S COLUMN WILL SHOW HOW to interface an 8085 microcomputer with an A/D converter so that eight analog channels can be monitored with the time period between measurements programmed by the user. It is assumed that all eight channels are monitored quickly with a long period between these quick samplings. The system's computer, the 8085, must have the following input/output (I/O) devices:

1. A fast 10-bit analog-to-digital (A/D) converter with an eight-channel multiplexer.
2. A set of thumbwheel switches to select the time period (1 second to 99 seconds).
3. A set of eight control on-off outputs that can be used to control the process being monitored.

The block diagram of Fig. 1 shows how we assigned I/O ports and bits to various I/O devices. One 8155 read/write memory and one 8355 read-only memory (ROM) device are used. Note that the six I/O lines of Port C on the 8155 have not been used. These I/O lines can be used for later expansion.

The 8355's I/O ports were chosen to control the A/D converter system because a combination of inputs and outputs was needed. The 8355's I/O ports can be assigned input or output functions on a bit-by-bit basis. The 8155 was used for the switch inputs and the control outputs since these were already prearranged in groups of eight lines each.

The bits of the I/O ports must first be assigned input or output functions. The eight bits at Port A are all input bits, while those at Port B are a combination of input and output bits. Thus, the following control words must be sent to the 8355's two port-control registers:

Port A Control = 00000000₂
 0 = Input Bit
 Port B Control = 11111000₂
 1 = Output Bit

*This article is reprinted courtesy American Laboratories. Dr. Rony, Department of Chemical Engineering, and Mr. Larsen, Department of Chemistry, are with the Virginia Polytechnic Institute & State University. Both Dr. C. Titus and Mr. J. Titus are with Tychon, Inc.

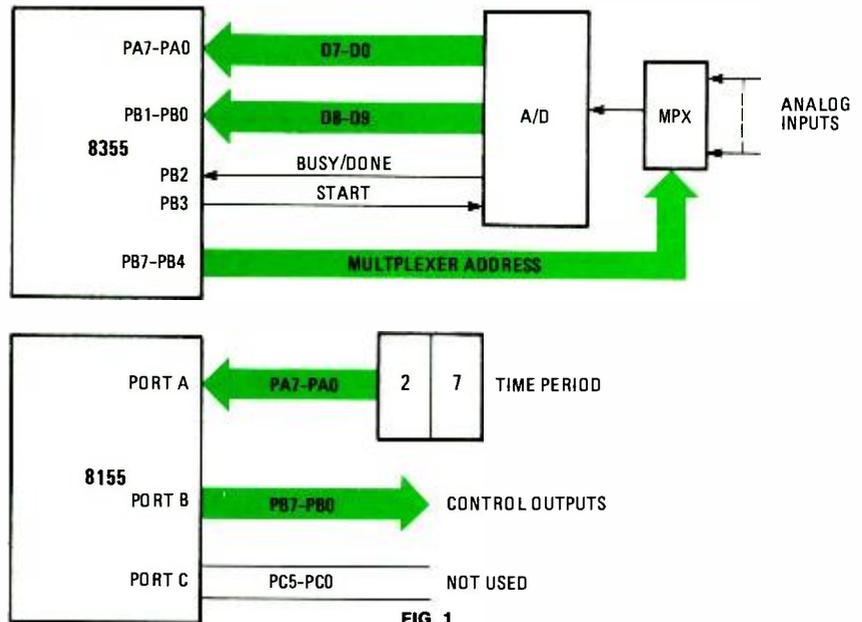


FIG. 1

```

START    MVI A, 000    /LOAD REG A WITH PORT A CONTROL WORD
          OUT 002    /OUTPUT IT TO THE 8355 CHIP
          MVI A, 370 /LOAD REG A WITH PORT B CONTROL WORD
          OUT 003    /OUTPUT IT TO THE 8355 CHIP
          NOP        /PROGRAM CONTINUES HERE
    
```

FIG. 2

```

/CONVERSION START PORTION OF THE PROGRAM
LDA STATUS    /GET THE STATUS WORD, BIT PB3 = START
OR 0          /SET THE START BIT TO A ONE
OUT 010       /OUTPUT IT
ANI 001       /CLEAR THE START BIT
OUT 367       /OUTPUT IT
NOP 001       /CONTINUE HERE

/MULTIPLEXER UPDATE, SWITCH TO THE NEXT CHANNEL
LDA STATUS    /GET THE STATUS WORD, BITS PB7 - PB4
AND 0        /ARE THE MULTIPLEXER CHANNEL ADDRESS
ADI 020       /ADD ONE TO MULTIPLEXER ADDRESS
OUT 001       /OUTPUT IT TO THE MULTIPLEXER
STA STATUS    /STORE THE NEW STATUS WORD BACK IN
              /ITS MEMORY LOCATION
NOP 0        /CONTINUE HERE
    
```

FIG. 3

```

/TIMER CONTROL PROGRAM FOR THE 8155 CHIP
MVIA      /PRESET THE 8 LSBS OF TIMER'S COUNT
020
OUT       /OUTPUT TO TIMER
204
MVIA      /OUTPUT THE 6 MSBS OF TIMER'S COUNT &
347      /THE 2 MODE CONTROL BITS, D6 & D7
OUT       /OUTPUT THEM TO THE TIMER
205
MVIA      /SET UP PORTS A & C FOR INPUT,
302      /PORT B FOR OUTPUT, AND START THE
OUT       /COUNTER
200
NOP       /CONTINUE HERE

```

FIG. 4

```

/RESTART 7.5 INTERRUPT SERVICE ENABLING STEPS
MVIA      /CLEAR ANY PREVIOUS RST7.5 INTERRUPTS
020
SIM       /SET INTERRUPT MASK
MVIA      /ENABLE RST7.5 INTERRUPTS
013
SIM       /SET INTERRUPT MASK

```

FIG. 5

The output of these control words is shown in Fig. 2.

When these control words are output to the control registers, the ports will be configured as required. It is wise to exercise some caution when you use Port B, since you want to control bit PB3 and bits PB7-PB4 independently. Therefore, when bit PB3 changes, bits PB7-PB4 must not be altered. Some careful thought must be applied to this problem so that the program does not start a conversion when all you want to do is


change the multiplexer's 4-bit address. A status word, stored in read/write memory, is used to tell the program the current status of the output lines. Individual bits can then be manipulated without affecting the other bits. Figure 3 shows two sections of the program, one indicating how the multiplexer is updated without affecting the converter, and the other showing how the converter is started without affecting the multiplexer. In fact, each routine can be treated as a subroutine.

The I/O ports on the 8155 are also easy to control. The bits at Port A are used as inputs and the bits at Port B are used as outputs; Port C is not used. Rather than using a software delay loop, we used the timer function in the 8155 to help time the 1-second period. Assume that the 8085 has a 1- μ s clock period. With a 14-bit counter this provides periods of up to 16.36 ms. In our example, we used a 10.00-ms time period, using a 14-bit binary count of 100111 00010000, which must be loaded into the counter. Since the timer will be used repeatedly, we used it in mode 3—automatic reload with a pulse at the end of each programmed period. Now it is necessary to initialize the 8155 to control Ports A and B plus the timer. The following sequence (see Fig. 4) initializes the system and starts the 10-ms clock period.

The timer's pulse output generates an interrupt (RST 7.5) whenever a 10-ms period "times out." To activate the RST 7.5 interrupt (on the 8085) the RST 7.5 interrupt mask must be enabled using the instruction steps shown in Fig. 5.


To initialize the I/O ports fully, only combine the steps from Figs. 2, 4 and 5. Remember also that you will have to establish a stack pointer before the interrupts can be used. In a future article, we will discuss the overall software integration necessary for this application. R-E

TUNERS•MODULES

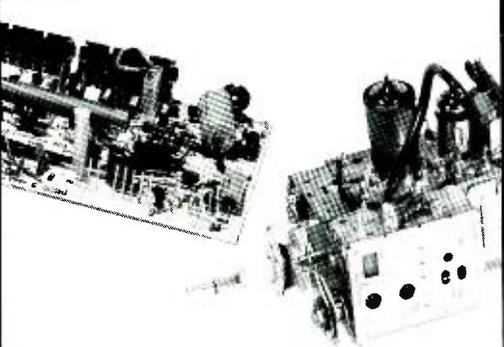

The next time you need a tuner repaired or module rebuilt:

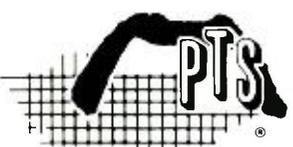- Remember **FAST SERVICE**
- Remember **PROFESSIONAL QUALITY**
- Remember **ONE-YEAR LIMITED WARRANTY**
- Remember **PTS ELECTRONICS**



PTS ELECTRONICS, INC.
SEE THE YELLOW PAGES FOR THE
PTS SERVICENTER LOCATION NEAREST YOU

CIRCLE 61 ON FREE INFORMATION CARD



Kleps 30
Kleps 40
Kleps 1
Kleps 10
Kleps 20
Prof 10



Kleps 10 - 20
Kleps 30
Kleps 40
Kleps 1
Prof 10

Clever Kleps

Test probes designed by your needs — Push to seize, push to release (all Kleps spring loaded).

- Kleps 10.** Boathook clamp-grips wires, lugs, terminals. Accepts banana plug or bare wire lead. 4¾" long. **\$1.59**
- Kleps 20.** Same, but 7" long. **\$1.69**
- Kleps 30.** Completely flexible. Forked-tongue gripper. Accepts banana plug or bare lead. 6" long. **\$1.99**
- Kleps 40.** Completely flexible. 3-segment automatic collet firmly grips wire ends, PC-board terminals, connector pins. Accepts banana plug or plain wire. 6¼" long. **\$2.89**
- Kleps 1.** Economy Kleps for light line work (not lab quality). Meshing claws. 4½" long. **\$1.09**
- Prof 10.** Versatile test prod. Solder connection. Molded phenolic. Doubles as scribing tool. "Bunch" pin fits banana jack. Phone tip. 5½" long. **\$.99**

All in red or black - specify. (Add 50¢ postage and handling). Write for complete catalog of - test probes, plugs, sockets, connectors, earphones, headsets, miniature components.

Available through your local distributor, or write to:



RYE INDUSTRIES INC.
129 Spencer Place, Mamaroneck, N.Y. 10543
In Canada: Rye Industries (Canada) Ltd.

CIRCLE 32 ON FREE INFORMATION CARD

service clinic

Locating replacement parts for orphan sets can be a real chore. For help, use your ingenuity and the part numbers.

JACK DARR, SERVICE EDITOR

IN THE ELECTRONICS SERVICE INDUSTRY we often find so-called "orphans" dumped on our doorstep. These are TV sets and radios sold by parent companies that have left town and cannot be located! In most cases, but specifically with the less costly imports, there's only one logical solution: Don't accept them! These sets lack service data and replacements, and are a lost cause.

With a few "brand-name" sets built by U.S. companies, there's some hope. One in particular is the Bradford line. This line appears to have been manufactured by a record number of companies, 16 in all! (This information was provided by the *Coil Replacement Guide No. 175*, published by the J. W. Miller Company of Compton, CA. This guide lists sets by brand and manufacturer.)

So far, in practically all cases, Bradford seems to use the original factory *part numbers*. Therefore, we have been able to trace them back and cross-reference them to the numbers used by the manufacturers in their own sets. Component numbers are often individual and identifiable. The Miller Company Guide lists only radio-stereo components. However, by checking the part number, you can identify the manufacturer, then use the TV transformer guides (such as those published by Thordarson, Triad, etc.) to find a replacement. We have done this in quite a few cases with good results.

Bradford is shown in the Miller Company Guide as having been manufactured by Admiral, Arvin, GE, RCA, Wells-Gardner and Westinghouse, as well as Sanyo, Aiwa, Matsushita, Mitsubishi and Toshiba. The American companies have distinctive part numbers. For example, an Admiral set will have flyback circuits numbered "79C187-1," and deflection yokes numbered "94C87-1." (Incidentally, the letter "C" in the number doesn't seem to be critical; it can also be a "D," etc.) Find the listing for Admiral and look for the same number; the chances are you will find the information you want.

Arvin uses five-digit numbers or seven-digit numbers with a suffix. For example, the numbers "68504-123" or "2002783-

2" are used for flyback circuits. Some components have letter-digit numbers, such as "TLF-413," which can also help. General Electric uses two letters, two digits, an "X" and more digits; "ET77X88" designates flyback circuits, "ET76X32" indicates yokes.

RCA uses six-digit numbers, usually without suffixes—"133640" (flybacks), "136642" (yokes), etc.

Wells-Gardner also uses an "X." However, there is a difference: "53X362C" is used for flyback circuits and "9A2403" for yokes. Flyback circuits, vertical-output transformers, audio transformers, etc., all seem to use numbers in the 50's. The designation for yokes and smaller coils starts with "9A."

A Westinghouse component is perhaps the easiest to identify at a glance since a typical number for a flyback circuit will be, say, "690V39H32." The "690" or "490" and the "V" are the key clues. All coils and transformers have that "V" in their number.

Of the imported sets, the larger ones may be in such quantities that the replacement-transformer companies manufacture parts. In any case, just cross-reference the component to a factory number for assistance. Sony, Panasonic (Matsushita), Mitsubishi and Toshiba all have parts centers around the country, and it is often easy to find the one you need. Some of these components are listed now in the transformer guides.

Service data on many Bradford sets is found in *Sams Photofacts*, in which the part numbers are listed. Many of the part numbers for other sets are also covered in this publication. Another company that has service data and parts for the Bradford line is the firm known as the Marcel Companies (57 Enfield Street, Enfield, CT 06082).

You can often discover some helpful information by accident. I once received a letter asking for data on a "XAM" D12BW74. I found that this used a Philco 3DL20 chassis (listed in *Sams No. 1277*). Another reader asked for data on a XAM 14CP74. I told him to research the Philco folders. He replied, "I looked all through the area you suggested (around

1200-1300 in *Sams Photofact*) and came up empty! A week later, a Philco C3052BWA came in. I took the back off and a light bulb lit up! It looks familiar! It turns out this one is a Philco 3CN20, *Sams No. 1414*." Thanks to Paul Fedison of Paul's TV in Jackson, NJ, for this help.

This cross-checking method works with other things as well. If you can find the part number, either from available data or the part itself, cross-check it to find a match. Once you can decode these numbers they can be *very* helpful. Good luck!

R-E

service questions

B+ VOLTAGES DOWN

This Sylvania model E-21 came in with no picture, raster, or sound. It showed about 15 kV on the high voltage and all the B+ voltages were low. I opened the B+ circuit between the rectifier and filter, and read only 240 mA. This should read 700 mA. I don't get it.—R. P., Bristol, VA.

In all solid-state TV sets, the value of the B+ voltage is critical. There are three things that can cause these symptoms you describe: excessive current, a weak supply, and a bad DC voltage regulator. You don't have a current overload, as you noted. Check the B+ voltage right out of the rectifier; this should read +145 volts. If so, check the output of the voltage regulator, which should read +112 volts. If it is quite low, check out the voltage-regulator circuit. Something in this circuit seems to be dropping the output voltage.

SHADED RASTER

The trouble with this Sony model SCC-64A is it has a shaded raster—dark on the left side, becoming gradually brighter to a whiteout on the right side. This shading tracks evenly with adjustment of the brightness control.—D. L., Battle Creek, MI.

This was the original letter. I suggested he check parts that are "common," such as the picture tube, grids, etc. This is his answer:

When I scoped the grids of the picture

tube with the gain cranked up as high as I could get it, I detected a 'very tiny sawtooth' waveform! Working my way back through the "Las Vegas Strip" (all those neon lamps!), I found that C707 was open. This is the filter capacitor for the +199-volt supply, and it comes from a winding on the flyback. Replacing the open capacitor with a new one cleared up the shading.

(Thanks to Darwin Lapham, Dar's TV, Battle Creek, MI.)

ERRATIC VOLTAGE SHUTDOWN

This Quasar model TT934HW would shut down after playing for some time. After tracing everything on the JA power-supply panel, I finally ordered a new power supply. The note included with it said if there was erratic voltage shutdown with the new panel, to install a beam current limiter kit. When I turned the set on, I had a very bright raster. I could not turn it down far enough and it shut down again. I then ordered the beam current limiter and installed it. This didn't help. I'm going in circles.—K.F., Darby, MT.



HIGH BLOOD PRESSURE
Treat it...and live.

The National High Blood Pressure Education Program,
U.S. Department of Health, Education, and Welfare.

Want to Switch to Land Mobile Servicing?

WE CAN HELP YOU SWITCH

... by providing professional HOME STUDY training for you and your technicians. MTI has been providing specialized training in land mobile servicing for 18 years. We would like to help you also. For more information, cut out this coupon.

NO SALESMAN WILL CALL!

Name _____
Address _____
City _____
State/Zip _____ YY3



Mobile Training Institute

Summerville, Pennsylvania 17093

CIRCLE 6 ON FREE INFORMATION CARD

So was I for a while! This is a *model 934*, but the chassis is No. 938. The Quasar service note states that this shutdown problem could be due either to a poor contact at pin 7 of plug P2, or to a poor contact where the +200-volt lead clips to the CA panel. Also, you could run a complete check of *all* the DC voltages and adjust any that are off. These voltages are all critical and can cause shutdown on low voltages as well as high.

TRANSISTOR IGNITION CUTOFF

The transistor ignition system on my car used to cut out on the highway. I've replaced the original TO-36 transistor with a 2N2527. Now it runs up to 50 mph at

highway speeds, but cuts out if I slow up for traffic. Any helpful ideas?—E. D., Tappan, NY.

I hope so. From the symptoms, the transistor is going into secondary breakdown and is not firing. This transistor is a germanium; germaniums can do this, then heal up when they cool off! The transistor is probably not getting sufficient cooling. (Try spraying coolant on it the next time it stops and see if this helps.)

If so, then add more heat-sink area. Make an auxiliary heat sink out of a big sheet of aluminum painted flat black. Also, place the unit in the car so that air does not get to it from the radiator but, rather directly from outside the car. In

NOW FROM LEADER . . .

The Basic LCR Bridge, Updated.

0.5% LCR Measurement Accuracy

Expandable Range
Built-in 10% Over-range.

Dissipation and 'Q' Measurements

3 Digit Readout

9V Battery or AC Adapter Operation

\$319⁹⁵ . . . includes 2 year warranty.

*Two years parts; 180 days labor;

Model LCR-740 . . . with accessories.

See your Distributor or Write for Details.

151 Dupont Street, Plainview, N.Y. 11803
(516) 822-9300

Regional Offices: Chicago & Los Angeles

When Quality Counts . . .

LEADER
Instruments Corp

CIRCLE 70 ON FREE INFORMATION CARD



FIND!

When you discover A P Products, you've got it made.

To electronics hobbyists, A P Products are a "find" every time. You'll see.

You'll find yourself building and testing your circuits faster and easier than you've been able to before. And with optimum electronic integrity.

Part of it is the practical, sensible, useful design of our solderless,

reusable breadboards and inter-connectors and testing devices.

The other part is quality. Superior materials. Superior manufacture. Everything pretested. You can truly depend on A P Products.

Item: Our connectors are molded onto the cable, not just crimped on. They just don't pull loose. Try one and see.

Where? Call (toll-free) 800-321-9668 for the name of your local A P store. And ask for our complete A P catalog, The Faster and Easier Book.



A P PRODUCTS INCORPORATED

Box 110 • 72 Corwin Drive
Painesville, Ohio 44077
Tel. 216/354-2101
TWX: 810-425-2250

Faster and Easier is what we're all about.


CIRCLE 84 ON FREE INFORMATION CARD

some cars, you can run a hose through the side of the radiator shell and place it so that it blows right on the transistor.

THIN VERTICAL LINE

I have problems now with a transistor TV I built while taking a course. Do you know where I can get a Sams schematic on the set? It's an HSK-T1. The problem is that all that appears on the screen is a thin white vertical line. I've replaced the horizontal driver, output and the driver transformers, with no result. This symptom indicates an open vertical deflection coil, but the continuity checks out! Help!—B. H., Orlando, FL.

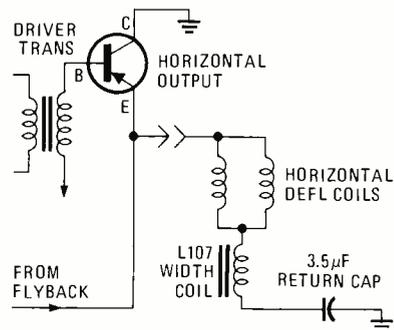Here are a couple of answers: First, you can't get a Sams schematic for anything but commercial TV sets. Second, let's recheck the cause of the problem.



A thin vertical line on the screen shows a loss of horizontal deflection, not vertical. In this set, as in many solid-state TV sets, the horizontal-deflection coil and the flyback are connected in parallel to the output of the horizontal-output transistor, which in this circuit is the emitter (see the diagram). If the horizontal-deflection circuit is open, there will be no sweep but there will be high voltage.

Check the horizontal yoke windings for continuity. Then follow the yoke-return circuit, which must be good. This circuit contains a width coil (L107) and a 3.5-µF capacitor to ground.

VERTICAL PROBLEM

This Motorola model TS-921 has a vertical problem. If a man is shown on the screen, his head is at his stomach level and his tie is over his head! There's not enough height, either. The voltages around the vertical stage are not too bad. Any ideas?—A.L., Dierks, AR.

You seem to have a simply massive foldover, plus other problems. Coupling capacitors can cause this problem, but you've tried these.

One thing that is easy to miss in this vertical circuit is the little 20-µF capacitor. This capacitor is actually in the vertical-output cathode circuit. It's located over on the pincushion circuit board, so it's easy to miss. Check this plus the 1500-ohm resistor across it. It can cause some odd problems.

(Feedback: "Bingo! The 20-µF shorted; the resistor was bad.")

R-E

TROUBLESHOOTING DIGITAL CIRCUITS

Continued from page 44

RAM, no problems are detectable. If color operation is chosen or the computer accesses the RAM, the screen is not blanked properly. In the case of color operation, the color is simply not displayed—since subjective coloring is an optical illusion and requires specific conditions to be observed.

Start the test by using the logic probe to check the counters and decoding circuits. Since they seem to work as designed, proceed to the AND gates; the video signal will blink the probe indicator at a low frequency. The blanking signal will be held low or in the undefined region. Since the output of that gate should have been pulsing at a low frequency, the problem exists on that line.

Using the current tracer (and pulser if required), follow the current into the NOR gate. Since the current flows from the AND gate into the NOR gate but is not pulsing, then either the input is shorted to ground, or another output is shorted to this line. Recalling that the blanking also malfunctions during computer access, this implies that the second case is true. Now, use the current probe to follow the flow into the inverter. Since these two lines only join at the NOR gate, the conclusion is simply that the two inputs are shorted together.

The third failure for the most part acts like and produces the same symptoms as the second failure, except that during computer access the blanking functions normally. The troubleshooting should begin and proceed in similar fashion. However, you will discover there is no output from the AND gate. Now, you should suspect a broken input wire bond in the AND gate. Use the logic probe on the output and place the pulser on the suspected input—there will be no signal. Next, place the pulser on the other input—you will receive a pulse. Since you have verified that the output, the other input and the power line connecting to that pin are all functioning, the only conclusion is an open input bond.

The fourth failure is due to two outputs being shorted together. During normal operation (computer is not accessing the circuit) both NAND gates are at a logic 1 state and normal operation continues. If the computer loads a new color command, then the character generator will be affected. Similarly, if a computer access to the RAM occurs, then the color circuits may be affected (depending upon the state of signal A_0). Use the same troubleshooting procedure used in the second failure case to locate the malfunction.

The fifth failure is due to an internal short, to ground, of the computer-access blanking signal. The obvious symptom is that the screen will always be blanked.

Start by checking the NOR gate—the computer-access blanking line is always high. Next, starting at the NAND gate (the gate that drives the chip selects pins of the data IC's) follow the logic pulser's signal using a logic probe. Since this line is shorted to ground, even the pulser cannot change its state. Again using the pulser to inject a signal, but this time using the current probe, follow the current flow into the inverter—the input of the inverter therefore must be shorted to ground.

The final circuit problem shows the effect of an input being shorted to V_{CC} . The symptoms are that color is not displayed (remember that a small percentage of people cannot observe subjective color, so be sure that you can). Again, starting with the color-counting circuit, proceed to the AND gates. The blanking signal will be OK, but the video line is held high. Again the pulser cannot change the state of the line. Furthermore, if the color circuits are not selected (the Q output of the D-type flip-flop is at a logic 0 level) then the current flows into the AND gate. This indicates that the input of the video multiplex is shorted to a logic high. R-E

Put Professional Knowledge and a
COLLEGE DEGREE
in your Electronics Career through

**HOME
STUDY**


**Earn Your
DEGREE**

by correspondence, while continuing your present job. No commuting to class. Study at your own pace. Learn from complete and explicit lesson materials, with additional assistance from our home-study instructors. Advance as fast as you wish, but take all the time you need to master each topic. Profit from, and enjoy, the advantages of directed but self-paced home study.

The Grantham electronics degree program begins with basics, leads first to the A.S.E.T. degree, and then to the B.S.E.E. degree. Our *free* bulletin gives complete details of the program itself, the degrees awarded, the requirements for each degree, and how to enroll. Write for *Bulletin R-79*,

Grantham College of Engineering
2000 Stoner Avenue
P. O. Box 25992
Los Angeles, CA 90025

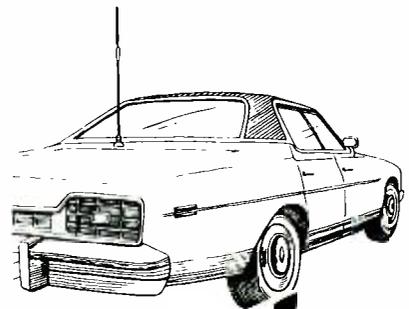Worldwide Career Training thru Home Study
CIRCLE 11 ON FREE INFORMATION CARD



NEW—
Antenna Hole Saw
for fast,
permanent
mounting!



Now you can cut time and cost in the installation of permanent mount mobile antennas. This new design cuts faster and requires no blade resharpening. Limits depth of hole to $\frac{1}{8}$ " to prevent damage to underlying headliner of cars. Special guide drill bit restricts walking of saw. Tool is available in $\frac{3}{4}$ " and $1\frac{5}{16}$ " sizes and designed for $\frac{3}{8}$ " or larger electric drill. Low-cost replaceable blades available. For fast, professional mounting jobs, this tool is indispensable. Write or call for literature and prices.




RIPLEY COMPANY, INC.
UTILITY TOOL DIVISION
CROMWELL, CT 06416 (203) 635-2200
CIRCLE 23 ON FREE INFORMATION CARD

How Can You Work Without it?

If you service electronic equipment, you've probably had more than one occasion where looking for a missing screw, nut, washer or other piece has wasted valuable time.

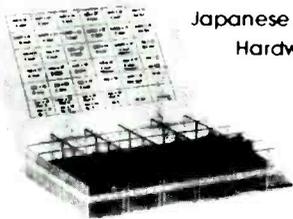FIND IT FAST
Japanese (Metric)
Hardware Kit



Used in the servicing of:

- CB Radio
- Car Stereo
- Tape Recorders
- Hi Fi Equipment
- Ham Gear
- Television
- Video Tape Rec.
- Test Equipment

And More

A MUST FOR EVERY TECHNICIAN, ENGINEER, HOBBYIST!!!

LOOK NO MORE FIND IT FAST
over 1,050 Pieces

METRIC (I.S.O.) (Japanese Standard)

- Round Head Screws
- Pan Head Screws
- E Rings
- Hex Nuts
- Spring Washers
- Chrome Screws
- Nylon Screws
- Solder Lugs

All packed in a shock resistant 36 compartment utility case

**NOT SOLD IN MOST
HARDWARE STORES!**

CALL TOLL FREE

(800) 423-5336

In California

(800) 382-3663

FREE Original Japanese Parts Catalog — Transistors, IC's, Capacitors, FETS and more

Be sure to send for this FREE Catalog!

Available from your distributor or send coupon to

ORA ELECTRONICS

7235 Canby Ave.
Reseda, CA 91335

Please send _____ea FIND IT FAST Hardware Pack
\$24.95 plus \$1.50 Shipping (Calif. Res. add 6% tax)

Enclosed _____

Name _____

Address _____


() I'd also like a Full-Line Catalog

CIRCLE 17 ON FREE INFORMATION CARD

new products

More information on new products is available from manufacturers of items identified by a Free Information number. Free Information Card is inside back cover.

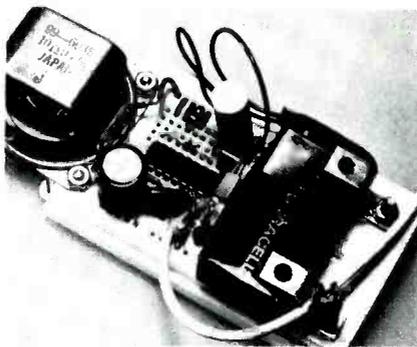SOLDERLESS BREADBOARD, Experimentor Socket, model EXP-350, permits youngsters learning electronics to simply plug a transistor or IC into the face of a wafer-shaped plastic block, add some components and wire to create a fascinating beeping, blinking, or ticking device. The model EXP-350 only requires a simple wire cutter



and stripper—no expensive tools—and necessary components for simple projects are inexpensive. Priced at \$3.50, the model EXP-350 can be used to design easy circuits obtainable from public libraries or electronic dealer sources.—Continental Specialties Corp., 70 Fulton Terrace, New Haven, CT 06509.

CIRCLE 112 ON FREE INFORMATION CARD

DUAL-TRACE OSCILLOSCOPE, model 1432, is a portable dual-channel, 15-MHz instrument that offers sweep ranges from 0.5 μ s to 1.5 seconds in 19 steps, with $\pm 3\%$ linearity. The unit has a 2-mV-per-division vertical sensitivity and 24-ns risetime. Features include a 3-inch CRT with internal graticule; $\times 5$ magnification; front-panel



X-Y operation. Vertical modes include Channel-A only, Channel-B only, A & B, A + B and A - B. Timebase automatically switches between chopped or alternate sweeps. Unit operates on 117 VAC, 234 VAC, 12 VDC; an optional rechargeable battery pack is also available for in-case mounting. Other options include a carrying case and demodulator probes. Provided with

10:1 direct probes and tips, the model 1432 weighs 18.3 lb. and measures 8.26 \times 5.5 \times 2.3 inches. Prices: model 1432, \$750; model BP-32 battery pack, \$50; model LC-132 carrying case, \$25; model PR-32 demodulator probes, \$18.—B&K Precision, Dynascan Corp., 6460 W. Cortland Ave., Chicago, IL 60635.

CIRCLE 113 ON FREE INFORMATION CARD


RADAR DETECTOR, model Bearfinder Two + Two, is the first to use two antennas to detect X- and K-bands that emanate from both moving radar and hand-held radar guns. Super-sensitive detector alerts driver both coming and going from signal emission point. Unit features "fail safe" indicator to warn of malfunction; sensitivity control dial; and a choice of either visual or audi-



tory alert signal. Bearfinder works on all 12-volt systems, can be plugged into car's cigarette lighter, requires no license to operate, and is guaranteed not to interfere with car radio performance or CB transceivers. The Bearfinder Two + Two comes in rugged heavy-gauge metal case and carries a 90-day warranty. Suggested retail price: \$149.95.—Bearfinder, Inc., 221 Crane St., Dayton, OH 45403.

CIRCLE 114 ON FREE INFORMATION CARD

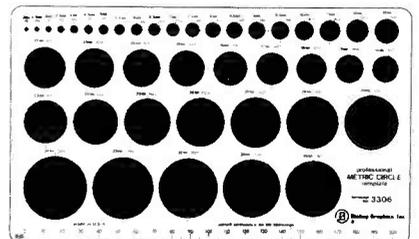GENERAL-PURPOSE TEMPLATES with metric dimensions together with their decimal equivalents include metric circles, large circles, squares, extra-large circles, pocket aids and sketch aids. Other templates featuring the standard U.S. deci-



mal measure include decimal circles, squares, arrowheads, brackets, combo ellipses, a free-hand lettering guide and more. Shapes and dimensions conform to MIL-STD 175 and the

Institute of Printed Circuits CM-770. Dual in-line templates are available in X1, X2 or X4 scale; logic symbols templates come in 1/4, 3/4, 1/2 and full sizes. Each template is tinted green and is .030-inch thick (freehand lettering guide is .040-inch thick) with a .025-inch pencil allowance. Information on all templates is provided in manufacturer's *Technical Bulletin No. 1020R*, available free.—**Bishop Graphics, Inc.**, 5388 Sterling Center Dr., Westlake Village, CA 91359.

CIRCLE 115 ON FREE INFORMATION CARD

WIDEBAND CABLE SPLITTER, model 1502A, provides a two-way split for 75-ohm cable lines. The unit can handle any audio or video signal; and has a nominal 6-dB loss and typical return



losses of 30 dB to 300 MHz and 25 dB to 890 MHz. Prices are available from the manufacturer.—**Extronix, Inc.**, 64 Gough Ave., Ivyland, PA 18974.

CIRCLE 116 ON FREE INFORMATION CARD

**For
faster
service**

**USE
ZIP
CODE**

**on
all
mail**

Our new test equipment catalog. Free!

With this catalog you can browse through one of the nation's largest electronics warehouses, packed floor to ceiling with the finest test instruments. Everything from probes to dual trace scopes; and everything at sensational savings made possible only by mail order selling. Volume pricing on orders over \$500 gives you even greater

savings. Every item is backed by a big brand name. Shipment is prompt from stock, always freight prepaid and there never is a handling charge on orders over \$200. Write today for the big free catalog of the big brands that offers you the big savings.




NORTH AMERICAN ELECTRONICS Dept. RE-178
1468 West 25th Street
Cleveland, Ohio 44113
Yes! Send me your big catalog.

Name _____
Address _____
City _____ State _____ Zip _____

CIRCLE 81 ON FREE INFORMATION CARD

Grandfather's Clock Was Never Like This!

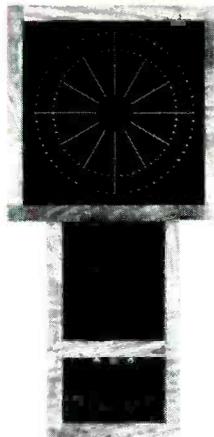

CL7402

If you love contemporary design and yet appreciate the more traditional, here's the perfect clock for you! Amelect has created their own version of the ever popular grandfather clock. Not only do the electronic eyes around the modern clock face light up displaying each second, minute, and hour, but our grandfather model includes a very novel and exciting electronic pendulum. There's even a shelf for displaying your prized treasures!

The upper section of the clock is 9³/₄" square with an overall length of 19¹/₄" all encased in beautiful, hand crafted hardwoods. Select from solid walnut, maple, mahogany, or cherry. This clock is covered by a 1 year warranty on material and workmanship.

As shown on R-E April '78 front cover and described by Fred Blechman.

Available completely assembled or in kit form.

CL7402 Assembled \$95.00
CL7402 Kit with Cabinet 71.50
CL7402 Kit less Cabinet 56.25
Shipping and Handling 3.50

To order write or call 219-297-3320

Indiana residents include 4% Sales Tax

AMELECT


INCORPORATED

P.O. Box 367 — 106 S. Newton St.
GOODLAND, INDIANA 47948

Allow 3 to 4 weeks for delivery

CIRCLE 82 ON FREE INFORMATION CARD

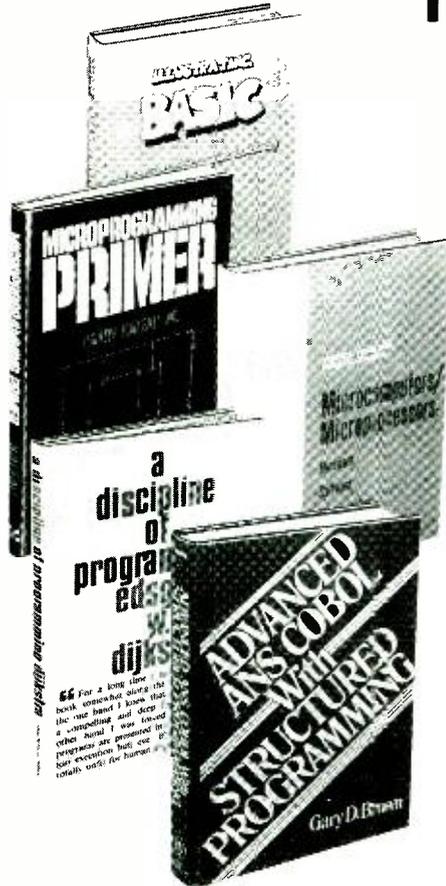Professional or not, the Computer the best books in the field...



PROGRAMMING LANGUAGES. By Allen B. Tucker, Jr. 439 pp., illus. Gives you not only the principles of design but the applications of six major programming languages so you can decide—among the special features of each—what best suits your operations. Shows you the languages' strengths and weaknesses through demonstrations of their use in solving various representative "benchmark" problems. Also provides programs using a variety of computers so you can evaluate languages and their compilers on a basis of uniform and meaningful criteria.
654/158 Pub. Pr., \$19.95 Club Pr., \$14.95

MICROPROCESSOR PROGRAMMING For Computer Hobbyists. By Neil Graham. 282 pp., with figures, tables, and samples. If you are a personal computer enthusiast or technician, this book will prove to be one of the most valuable and interesting investments you can make. It contains full details on programming—from the very basics to the state-of-the-art capabilities—and yet it is written so simply, and progresses in such a direct and logical manner, that any reader, no matter how inexperienced, can easily follow it.
783/56X Pub. Pr., \$12.95 Club Pr., \$10.95

A DISCIPLINE OF PROGRAMMING. By Edsger W. Dijkstra. 217 pp., with figures. Based on the author's conviction that a carefully chosen separation of concerns is essential for the design of high-quality programs, this book focuses on—and solves with fresh insight and originality—a separate problem of design in each chapter. Rather than choosing one of the existing programming languages to work with, he has designed a mini-language that helps to stress the more fundamental aspects of the task.
770/115 Pub. Pr., \$19.95 Club Pr., \$15.75

This title counts for two premium books

ENCYCLOPEDIA OF COMPUTER SCIENCE. Edited by Anthony Ralston and C. L. Meek. 1,500 pp., 60 illus., 100 charts, 7 x 10 format. This first and only in-depth coverage of the entire field of computer science in a single volume is utterly comprehensive and completely up to date. An invaluable reference work for specialists, nonspecialists, educators, students, general readers, and librarians, it provides answers to any computer science discipline question in minutes. In addition to covering every aspect of the discipline in five broad areas, each is broken down into some 500 articles, most of them containing bibliographic information to make intensive study of any one subject easier.
769/01X Pub. Pr., \$60.00 Club Pr., \$39.95

THE "COMPULATOR" BOOK: Building Super Calculators and Minicomputer Hardware with Calculator Chips. By R. P. Haviland. 320 pp., illus. Calculator chips are good for more than calculators—and here's the book to prove it. An imaginative, one-of-a-kind guide, it shows you how to use calculator chips in hundreds of innovative, practical ways, building bigger displays, designing better calculators, and creating exotic functions. Now experimenters can approach the full power of their own desktop minicomputers—multifunctioned, superbrained, and ready to do everything but get up and walk away!
783/578 Pub. Pr., \$10.95 Club Pr., \$9.30

THE 8080A BUGBOOK: Microcomputer Interfacing and Programming. By Peter R. Rony, David G. Larsen, and Jonathan A. Titus. 416 pp., with figures, charts, and tables, paperbound. Gives you the basic concepts of microcomputer interfacing and the associated microcomputer I/O programming so you can develop your own interfaces to other digital devices. For the 8080 user, this book will be invaluable, because the Intel 8080 is penetrating every facet of life today, creating new industries and threatening old ones, and this book teaches you the fundamental tasks of microcomputer interfacing.
783/845 Pub. Pr., \$9.95 Club Pr., \$8.45

MICROCOMPUTERS/ MICROPROCESSORS Hardware, Software, and Applications. By John L. Hilburn and Paul N. Julich. 372 pp., illus. This book was expressly created for people involved in the design, use, or maintenance of digital systems using microcomputers. The opening chapters provide needed background in digital logic and present well-organized discussions of number systems, arithmetic operations, and codes employed in microcomputers. The authors then describe the theory and workings behind microprocessor architecture, read-only memory (ROM), random-access memory (RAM), and input/output interfacing methods.
771/499 Pub. Pr., \$22.50 Club Pr., \$16.50

APPLYING MICROPROCESSORS New Hardware, Software, and Applications. Edited by Laurence Altman and Stephen E. Scrupski. 200 pp., illus., 8 1/2 x 11 format. A follow-up volume to Electronics magazine's recently published book, *Microprocessors*, this work takes you into the second- and third-generation devices rolling off semiconductor lines today. The collection of articles here is designed to smooth your way to mastery of new design methods, and it gives you both an overview of the state of the art and a wealth of design ideas, analyses, and applications.
191/603 Pub. Pr., \$16.95 Club Pr., \$13.25

BE SURE TO CONSIDER THESE IMPORTANT TITLES AS WELL—

GRAMMARS FOR PROGRAMMING LANGUAGES. By J. C. Cleaveland & R. C. Uzgalis. 783/594 Pub. Pr., \$18.95 Club Pr., \$12.75

GETTING INVOLVED WITH YOUR OWN COMPUTER A Guide for Beginners. By L. Solomon & S. Veit. 771/952 Pub. Pr., \$9.95 Club Pr., \$8.35

DIGITAL COMPUTER DESIGN. By R. Kline. 784/450 Pub. Pr., \$19.50 Club Pr., \$13.75

MINICOMPUTER SYSTEMS Organization and Programming. By R. H. Eckhouse Jr. 768/641 Pub. Pr., \$18.95 Club Pr., \$13.95

MICRO-ANALYSIS OF COMPUTER SYSTEM PERFORMANCE. By B. Beizer. 785/058 Pub. Pr., \$22.50 Club Pr., \$17.25


TOP-DOWN STRUCTURED PROGRAMMING TECHNIQUES. By C. L. McGowan & J. R. Kelly. 769/052 Pub. Pr., \$15.95 Club Pr., \$13.50

FUNDAMENTALS OF DATA STRUCTURES. By E. Horowitz & S. Sahni. 770/522 Pub. Pr., \$17.95 Club Pr., \$14.95

COMPUTER ARCHITECTURE. By C. C. Foster. 770/794 Pub. Pr., \$17.95 Club Pr., \$13.95

PROGRAMMING MICROPROCESSORS. By M. W. McMullan. 770/913 Pub. Pr., \$9.95 Club Pr., \$8.45

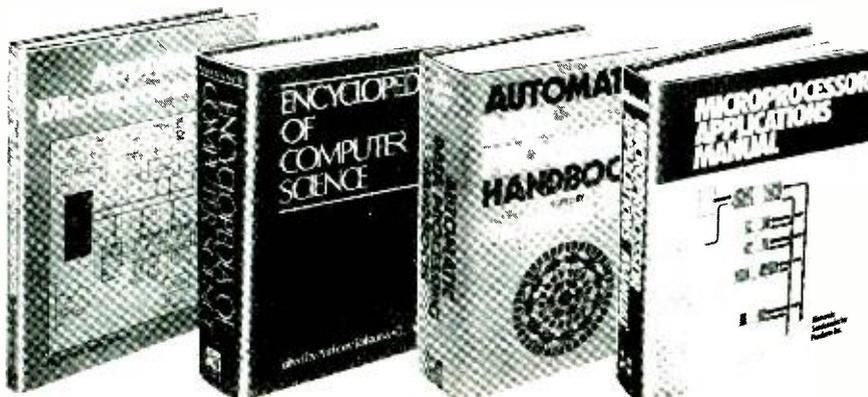MICROPROCESSOR/MICROPROGRAMMING HANDBOOK. By B. Ward. 768/749 Pub. Pr., \$9.95 Club Pr., \$8.45



Professionals' Book Club provides you with (and at great savings, too!)

AUTOMATIC DATA PROCESSING HANDBOOK. Edited by The Diebold Group. 976 pp., 269 illus. Written by a staff of internationally recognized authorities on ADP and sponsored by one of the nation's leading management consulting firms, this utterly comprehensive handbook explains and discusses computer systems, programming and languages, communications processes, and the design and installation of today's computers. 168/075 Pub. Pr., \$34.95 Club Pr., \$23.75

MICROPROGRAMMING PRIMER. By Harry Katzan, Jr. 254 pp., illus. An introductory how-to book that treats microprogramming and emulation topics, this volume assumes that readers are acquainted with basic concepts of computers. Discussions include the complex relationships between programs, computers, and modern methods of implementation. 333/874 Pub. Pr., \$20.95 Club Pr., \$15.70

DATABASE PROCESSING Fundamentals, Modeling, Applications. By David M. Kroenke. 408 pp., illus. An introduction to database-oriented systems, presenting material that covers the full spectrum of all activities involved. Physical representation, modeling, commercial systems, and implementation are discussed equally with no particular emphasis on one area to the neglect of any other. 769/931 Pub. Pr., \$16.95 Club Pr., \$12.95

MICROPROCESSOR APPLICATIONS MANUAL. By Motorola Semiconductor Products, Inc. 720 pp., illus., 8 1/2 x 11 format. With a nuts-and-bolts kind of practicality, this manual by the Motorola people (who should know) gives you detailed applications information on microprocessors and assumes no prior knowledge on your part about MPUs. It covers all the systems phases and explores such topics as architecture, the instruction set, addressing modes, interrupt structure, and other vital MPU features. 435/278 Pub. Pr., \$32.50 Club Pr., \$24.00

MINICOMPUTERS: Structure and Programming. By T. G. Lewis and J. W. Doerr. 282 pp., illus. This valuable handbook makes an outstanding introductory guide to both the hardware and software of today's minicomputers. Its broad coverage includes assembly language, machine architecture, and small machine algorithms. "Timely . . . a nice job on structure and content."—*Data Processing Digest*. 773/009 Pub. Pr., \$13.95 Club Pr., \$11.75

ILLUSTRATING BASIC: A Simple Programming Language. By Donald Alcock. 134 pp., illus. Completely handwritten by the author in a most unusual way, and containing an abundance of figures, diagrams, and drawings, this book was inspired by the need for a guide that would help readers who have to use computers but are terrified by them. 771/928 Pub. Pr., \$10.95 Club Pr., \$8.95

CHESS AND COMPUTERS By David Levy. 145 pp., illus. All over the world, great human effort and computer resources are being devoted to producing a program that can play chess as well as a master. This first comprehensive book on the subject shows why the project is worthwhile because the techniques employed in writing a strong chess program may be used to help solve other programs. 785/252 Pub. Pr., \$12.95 Club Pr., \$10.50

THE Z-80 MICROCOMPUTER HANDBOOK. By William Barden, Jr. 304 pp., illus., paperback. Sooner or later the Z-80 will have a successor. For the time being, this book gives you the entire "state of the art" in microcomputer technology today. Arranged in three convenient and logically developed sections, the book discusses architecture and interface signals, then the powerful interrupt sequences of Z-80 and interfacing examples of I/O memory devices. 784/914 Pub. Pr., \$8.95 Club Pr., \$7.60

ADVANCED ANS COBOL WITH STRUCTURED PROGRAMMING. By Gary D. Brown. 497 pp., illus. More and more people learn COBOL each year, increasing the number of active COBOL programmers. Having advanced beyond the introductory stages, they need a book that touches only lightly on the basics, and then goes into detail on both advanced programming techniques and advanced COBOL statements. This book begins where the basic manuals leave off. 772/118 Pub. Pr., \$19.95 Club Pr., \$15.95

COMPUTER ARCHITECTURE AND ORGANIZATION. By John P. Hayes. 512 pp., illus. Assuring you a far deeper understanding of computer design at the systems level, this comprehensive, in-depth volume gives you the broad coverage you need of computer architecture—and in a most rigorous but highly readable manner. It provides all the mathematics needed for analyzing computer performance, plus extensive references for additional reading. 273/634 Pub. Pr., \$21.50 Club Pr., \$16.50



Two Special premium books come to you with your first selection

MAIL THIS COUPON TODAY

COMPUTER PROFESSIONALS' BOOK CLUB
P.O. Box 582 Princeton Road, Hightstown, New Jersey 08520

Please enroll me as a member and send me the three books indicated. I am to receive the two bonus books at the introductory price of \$2.95 plus my first selection, plus tax, postage, and handling. If not completely satisfied, I may return the books within 10 days and request that my membership be cancelled. If I keep the books, I agree to take a minimum of three additional books during the next two years at special Club prices (guaranteed 15% discount, often more). I will receive the Club Bulletin 13 times a year. If I want to examine the featured selection, I need take no action. It will be shipped automatically. If, however, I want an alternate selection—or no book at all—I simply notify the Club by returning the convenient card always enclosed. I will always have a minimum of 10 days in which to return the card and you will credit my account fully, including postage, if this is not the case. Membership in the Club is continuous but cancellable by me at any time after the four-book purchase requirement has been filled. This order subject to acceptance by McGraw-Hill. Orders from outside the continental U.S. must be prepaid. Company, business or institutional tax exemption status is not applicable to purchases made through individual Club memberships. All prices subject to change without notice. Offer good for new members only. Postage and handling charges are added to all shipments. Members are billed when books arrive.

Write Code # of 1st premium book selection here	Write Code # of 2nd premium book selection here	Write Code # of 1st book selection here.
<input type="text"/>	<input type="text"/>	<input type="text"/>

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

EXTRA SAVINGS: Remit in full with your order, plus any local and state tax, and McGraw-Hill will pay all regular postage and handling charges. P 39349

COMPUTER PROFESSIONALS' BOOK CLUB saves you both time and money!

Here is a book club designed to meet all of your professional as well as hobbyist needs by providing practical books about computers on a regular basis at below publisher prices. If you're missing out on important technical literature—if today's high cost of reading curbs the growth of your library—here's the solution to your problem.

The Computer Professionals' Book Club was organized for you, to provide an economical reading program that cannot fail to be of value. Administered by the McGraw-Hill Book Company, all books are chosen by qualified editors and consultants. Their understanding of the standards and values of the literature of interest to you guarantees the appropriateness of the selections.

How the club operates: Thirteen times a year you receive free of charge The Computer Professionals' Book Club Bulletin. This announces and describes the Club's featured book as well as alternate selections available at special members' prices. If you want to examine the Club's feature, you do nothing. If you prefer one of the alternate selections—or if you want no book at all—you notify the Club by returning the card enclosed with each Bulletin.

As a Club member, you agree only to the purchase of four books (including your first selection) over a two-year period. Considering the many books published annually, there will surely be at least four you would want to own anyway. By joining the Club, you save both money and the trouble of searching for the best books.

CIRCLE 35 ON FREE INFORMATION CARD

THIS SIGN



ON YOUR DOOR
(wall, truck, or caddy)

TELLS YOUR CUSTOMERS
THAT YOU ARE THE P.R.I.D.E.
OF ELECTRONICS SERVICE


Your NESDA membership says you are
**Professional, Reliable, Industrious,
Dependable and Ethical**

Don't YOU want to
say nice things about
YOUR business?

JOIN NESDA

write for information to:
NESDA, 1715 Expo Lane
Indianapolis, IN 46224

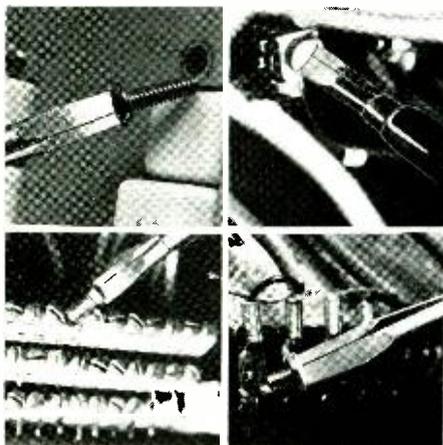**Use Quick Wedge to repair
a control panel, hook up a power
monitor, connect a power
supply, install a motor starter**



**They do all that ordinary
screwdrivers do, PLUS they
hold and start the screw**



QUICK-WEDGE 17 sizes
Screw-holding screwdrivers
Unconditionally guaranteed.

BUY A SET TODAY
See your dealer or write to:
Kedman Company, P.O. Box 25667,
Salt Lake City, Utah 84125

CIRCLE 15 ON FREE INFORMATION CARD

RADIO-ELECTRONICS


94

© 1977

computer products

*More information on new products is available from
manufacturers of items identified by a Free Information
number. Free Information Card is inside back cover.*

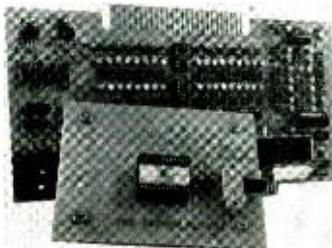COMPUTER, *Prom Setter*, assembled or in kit form, is designed to read/write 1720A and 2704/2708 EPROM's. The unit consists of an S-100 bus-compatible main module board and a low-insertion-force PROM socket unit, with no external power supplies needed. The main module functions as an I/O device using 4 consecutive



addresses out of 256 available segments. The *Prom Setter* can be used to read/write other EPROM's just by rearranging the main module's interconnecting cable to the 25 pin connectors. Adding a DPDT switch allows the unit to read/write different EPROM combinations; i.e., 1720A, 2704/2708 and TI's 2716. Changing to a 6-pole 3-throw switch, plus diode, Zener diode and 2 resistors, lets the unit read Intel's 2716. The *Prom Setter* comes complete with all hardware and software. It sells for \$210 (kit) and \$375 (assembled).—**Szerlip Enterprises**, 1414 W. 259th St., Harbor City, CA 90710.

CIRCLE 117 ON FREE INFORMATION CARD

GRAPHICS COMPUTER, *Compucolor II*, is available in five models, all with 13-inch, 8-color CRT; separate ASCII keyboard; 8080A CPU; all editing features (page/roll, erase line, etc.); and a built-in



minifloppy disc drive. The models range from one providing 4K RAM with a 16-line by 64-character per-line format to a top-of-the-line unit with 16K RAM, complete vector graphics, 32-line by 64-

character-per-line format and an expanded keyboard. The high-level language is BASIC 8001. Available software includes tutorial games, a checkbook balancing program and game programs for fun, such as *Star Trek*, *Chess* and *Biorhythm*. Suggested retail price: \$795-\$1995.—**Compucolor Corp.**, Box 569, Norcross, GA 30091.

CIRCLE 118 ON FREE INFORMATION CARD

HIGH-LEVEL LANGUAGE, *6800 Compiler*, is a fast 3-pass compiler providing a high-level disassembled language for 6800 computers having at least 16K RAM. The new language is called STRUBAL (*STR*uctured *BA*sic *L*anguage) and uses relocatable and linkable code. The software contains a full set of scientific functions, one- and two-dimensional arrays, 3 data types, structured programming modes, variable-length strings, embedded assembly language in the source program, and COMMON and DUMMY sections. The *6800 Compiler* is provided on floppy disc along with a user manual. Price: \$99.95.—**Hemenway Associates, Inc.**, 151 Tremont St., Suite 8P, Boston, MA 02111.

CIRCLE 119 ON FREE INFORMATION CARD

LOW-PROFILE KEYBOARD, *Touchcoder*, eliminates "double-strike" syndrome and produces 8-bit ASCII and other codes in any level or polarity without interfacing electronics. With the standard ASCII keyboard there is no restriction on the layout or number of keys; on the the standard cluster keyboard, the format is 10, 12, 16 digits.



Other specifications are: rise- and falltimes, less than 1 μ s; zero bounce; life, 100 million operations. Unit can either be flush-mounted or top-surface mounted. Price: \$35, OEM quantities.—**Computronics Engineering**, 7225 Hollywood Blvd., Los Angeles, CA 90046.

CIRCLE 120 ON FREE INFORMATION CARD

COMPUTER SOFTWARE, *Cosmac 1802 Simulator Program*, allows a 6502 microprocessor to execute the Cosmac 1802 instruction set. All Cosmac internal registers can be viewed in a single-step mode or in a trace mode. All Cosmac software is supported except for DMA (*D*irect *A*ccess *M*emory).


The software is in a KIM-1 mode that enables a KIM-1 to be a development and debugging tool for Cosmac software; no additional hardware or software are required. The simulator leaves two full pages of memory open for Cosmac programs;

alternative run mode provides an optional one-half page. The simulator program can be relocated in ROM and adapted to other 6502 systems.

Complete package contains KIM-1-format cassette tape, manual and assembly level source/object listing, priced at \$10, plus \$1.50 postage/handling (California residents add state and local taxes as applicable.)—**Dann McCreary**, Apt. 2R, 4758 Mansfield St., San Diego, CA 92116.

CIRCLE 121 ON FREE INFORMATION CARD

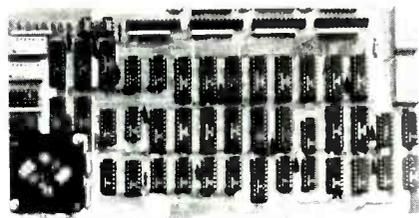PARALLEL INTERFACE is S-100 bus compatible and can be used with System 2 and System 3 computers. It provides 8 bidirectional 8-bit I/O ports that can be used singly or coupled together. For handshaking operations, I/O status flags can be grouped on one port and accessed with a single I/O statement.



Additional features include 8 sense switches, 8 LED's, 2 bits of opto-isolated input and 2 bits of relay-driven output. The board is available assembled for \$295, or in kit form for \$195.—**Cromemco, Inc.**, 280 Bernardo Ave., Mountain View, CA 94040.

CIRCLE 122 ON FREE INFORMATION CARD

Try this exciting new hobby!

Build your own electronic concert organ. It's easy. No technical knowledge required. Just follow the clearly pictured instructions of the famous Wersi do-it-yourself system. Choose from seven different models. Send \$2.00 (refundable) with coupon for colorful 104 page catalog.

WERSI



Wersi Electronics, Inc.
Dept. 42,
1720 Hempstead Road
Lancaster, PA 17601

Enclosed is \$2.00 for my copy of your 104 page catalog.

Name _____
Address _____
City _____ State _____ Zip _____

CIRCLE 30 ON FREE INFORMATION CARD



NATEAN catalog
Shopping center for small and precision tools

A fine selection of small tools, measuring instruments, hard-to-find items for shop, home and lab. Convenient one-stop shopping for technicians, engineers, craftsmen, hobbyists. Major credit cards accepted, satisfaction assured. Get your NATCAM catalog today.

National Camera, Inc.
2000 West Union Ave., Dept. GBF
Englewood CO 80110 USA

CIRCLE 16 ON FREE INFORMATION CARD

MATHEMATICS ELECTRONICS ENGINEERING MATHEMATICS ADVANCED MATHEMATICS DIGITAL TECHNOLOGY

These unusual courses are the result of many years of study and thought by the President of Indiana Home Study, who has *personally* lectured in the classroom to *thousands* of men, from all walks of life, on mathematics, and electrical and electronic engineering.

You will have to see the lessons to appreciate them!

WE ARE THIS SURE:—you order your lessons on a money-back guarantee.

In plain language, *if you aren't satisfied you don't pay*, and there are no strings attached.

Write today for more information and your outline of courses.

You have nothing to lose, and everything to gain!

The INDIANA HOME STUDY INSTITUTE

EASTERN DIVISION

P.O. BOX 1189

PANAMA CITY, FLA 32401

CIRCLE 13 ON FREE INFORMATION CARD

HOBBYISTS! ENGINEERS! TECHNICIANS! STUDENTS!

Write and run machine language programs at home, display video graphics on your TV set and design microprocessor circuits—the very first night—even if you've never used a computer before!



ELF II by NETRONICS

As featured in POPULAR ELECTRONICS

Shown with optional 4k Memory Boards, GIANT BOARD™ & Kluge Board.

ELF II featuring RCA COSMAC mini-COMPUTER \$99.95

Stop reading about computers and get your hands on one! With a \$99.95 ELF II and our *Short Course* by Tom Pittman, you master computers in no time at all! ELF II demonstrates all 91 commands an RCA 1802 can execute and the *Short Course* quickly teaches you to use each of the 1802's capabilities. ELF II also displays graphics on any TV set, including an exciting new target/missile gun game! Add-ons are among the most advanced available anywhere. You get massive computing potential. No wonder IEEE chapters, universities and major corporations all use ELF II to train engineers and students! Kit is easily assembled in a single evening and you may still have time to run your first programs before going to bed!

— SEND TODAY! —

NOW AVAILABLE FOR ELF II —

- Tom Pittman's *Short Course On Microprocessor & Computer Programming* teaches you just about everything there is to know about ELF II or any RCA 1802 computer. Written in non-technical language, it's a learning breakthrough for engineers and laymen alike. **\$5.00** postpaid!
- Deluxe metal cabinet with plexiglas dust cover for ELF II. **\$29.95** plus \$2.50 p&h.
- ELF II connects to the video input of your TV set. If you prefer to use your antenna terminals, order **RF Modulator**, **\$8.95** postpaid.
- GIANT BOARD™** kit with cassette I/O, RS 232-C TTY I/O, 8-bit P I/O, decoders for 14 separate I/O instructions and a system monitor/editor. **\$39.95** plus \$2 p&h.
- Kluge (Prototype) Board** accepts up to 36 IC's. **\$17.00** plus \$1 p&h.
- 4k Static RAM** kit. Addressable to any 4k page to 64k. **\$89.95** plus \$3 p&h.
- Gold plated **86-pin connectors** (one required for each plug-in board). **\$5.70** postpaid.
- Professional ASCII Keyboard kit with 128 ASCII upper/lower case set, 96 printable characters, onboard regulator, parity, logic selection and choice of 4 handshaking signals to mate with almost any computer. **\$64.95** plus \$2 p&h.

- Deluxe metal cabinet for ASCII Keyboard. **\$19.95** plus \$2.50 p&h.
- ELF II **Tiny BASIC** on cassette tape. Commands include SAVE, LOAD, GOTO, GOSUB, RETURN, END, REM, CLEAR, LIST, RUN, PLOT, PEEK, POKE. Comes fully documented and includes alphanumeric generator required to display alphanumeric characters directly on your TV screen without additional hardware. Also plays tick-tack-toe plus a drawing game that uses ELF II's hex keyboard as a joystick. 4k memory required. **\$14.95** postpaid.
- Tom Pittman's *Short Course on Tiny BASIC* for ELF II. **\$5** postpaid.
- Expansion Power Supply** (required when adding 4k RAM). **\$34.95** plus \$2 p&h.
- ELF-BUG™ Deluxe System Monitor** on cassette tape. Allows displaying the contents of all registers on your TV at any point in your program. Also displays 24 bytes of memory with full addresses, blinking cursor and auto scrolling. A must for the serious programmer! **\$14.95** postpaid.
- Coming Soon:** A/D, D-A Converter, Light Pen, Controller Board, Color Graphics & Music System...and more!

Call or write for wired prices!

Netronics R&D Ltd., Dept. RE-11
333 Litchfield Road, Phone
New Milford, CT 06776 (203) 354-9375

Yes! I want to run programs at home and have enclosed \$99.95 plus \$3 postage & handling for RCA COSMAC ELF II kit, \$4.95 for power supply (required), \$5 for RCA 1802 User's Manual, \$5 for *Short Course on Microprocessor & Computer Programming*.

I want mine wired and tested with power supply, RCA 1802 User's Manual and *Short Course* included for just **\$149.95 plus \$3 p&h!**

I am also enclosing payment (including postage & handling) for the items checked at the left:

Total Enclosed (Conn. res. add tax) \$ _____ Check here if

you are enclosing Money Order or Cashier's Check to expedite shipment
USE YOUR VISA Master Charge (Interbank # _____)


Account # _____ Exp. Date _____
Signature _____

PHONE ORDERS ACCEPTED (203) 354-9375

Name _____
Address _____
City _____
State _____ Zip _____

DEALER INQUIRIES INVITED.

CIRCLE 53 ON FREE INFORMATION CARD

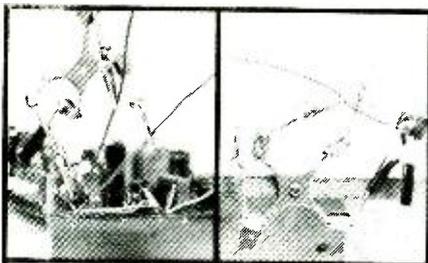

THE PORTABLE HAND

A holding device usable almost anywhere.

All angle ball and joint connections. Steel construction. Replaceable clips — Gluing, Soldering, Jewelry & Modelmaking.

Join clips together for grasping heavy objects.

clips will hook to any edge

12 inches overall

rust resistant

Made in U.S.A.


\$9.95

Add 75¢ shipping
Call, R.L. Add 6.4%

Spyderco

P.O. Box 3517 R

Redding, CA 96001

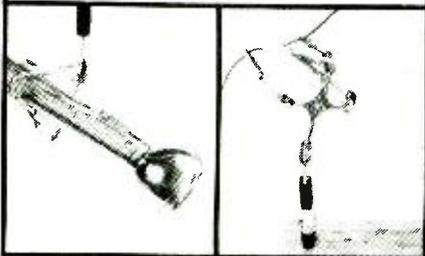

stereo products

More information on new products is available from manufacturers of items identified by a Free Information number. Free Information Card is inside back cover.

IN-DASH CAR STEREO UNITS, Series S600 8-track models and *Series T607* cassette models. Some units in the *Series S600* contain *Road-Rated Receiver* circuitry for increased performance when the automobile is in motion and a dial-in-door cartridge slot. Additional unit features are: for the *model S604*, repeat and separate bass/treble controls; *model S605*, LOC/DX and stereo indicator; *model S608*, repeat, separate bass/treble, FM muting, stereo matrix, LOC/DX; *model S682*, *Powerplay*, repeat, fast-forward, FM muting, LOC/DX; *model S683*, preset tuning, fast-forward, repeat, LOC/DX; *model S685* (shown), *Powerplay*, digital readout, clock, preset tuning switch, FM muting, LOC/DX, and power-off eject button. Price range: \$129.95-\$279.95.



Most units in the *Series T600* cassette format include the following features: *Road-Rated Receiver* circuitry, dial-in-door slot, FM muting, locking fast/forward rewind and LOC/DX. The *model T607* contains an auto-reverse switch and fader; *model T610*, stereo matrix and end-of-tape eject button; *model T611*, fader, power-off and end-of-tape eject buttons; *model T633*, preset tuning, fader, power-off and auto-eject buttons; *model T681*, *Powerplay*, power-off and end-of-tape eject buttons; *model T683*, auto-reverse, loudness and fader; *model T685*, digital readout, *Powerplay*, clock, preset tuning, auto-reverse and fader. Price range for the *Series T600* cassettes: \$114.95-\$299.95.—**Craig Corp.**, 921 W. Artesia Blvd., Compton, CA 90220.

CIRCLE 123 ON FREE INFORMATION CARD

PHONO RIBBON CARTRIDGE, model HV-9100, is fully handmade and assembled using ribbon technology to eliminate internal conductance problems. Designed to be used with the *model HA-9000* head amplifier, the *model HV-9100*




(shown) has the following specifications: a nominal frequency response of 20 Hz-30 kHz; channel balance within 1 dB at 1 kHz; 3-ohm impedance at 1 kHz; rated output voltage of 0.04 mV (4 mV with *model HA-9000* amplifier); stylus pressure of 1.6-1.8-grams and a solid diamond 0.4 X 0.8

elliptical stylus. The cartridge weighs 19 grams. Suggested retail prices: *model HV-9100* cartridge, \$220; *model HA-9000* amplifier, \$275.—**Nagatronics**, 2280 Grand Ave., Baldwin, NY 11510.

CIRCLE 124 ON FREE INFORMATION CARD

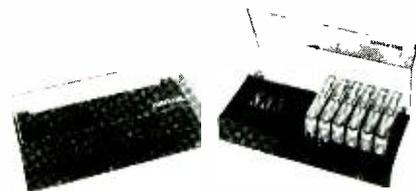CASSETTE STORAGE CASE. Large plastic case holds 12 cassettes along with insert cards and outer box, making it ideal for developing cassette



libraries. Retail price: \$5.95.—**Maxell Corp. of America**, 130 Commercial Way, Moonachie, NJ 07074.

CIRCLE 125 ON FREE INFORMATION CARD

AM/FM STEREO RECEIVER, model LR-120DB, is a top-of-the-line receiver that provides 120 watts-per-channel RMS into 8 ohms from 20 Hz to 20 kHz, with no more than 0.9% THD. The features include: dual tape monitors and dubbing, phono sensitivity switch, FM and audio muting switches, high-blend switch, high-cut and low-cut filter switches and stereo/mono switch, it also includes power output meters with dual ranges, built-in Dolby FM noise reduction and twin headphone jacks.



Specifications include: For the amplifier—a 15-Hz-40-kHz frequency response at 1 watt and a phono input sensitivity of 2.5 mV/5 mV/10 mV (switch-selectable); for the FM section—alternate channel selectivity, 80 dB; capture ratio, 1.3 dB; 1.8-μV sensitivity; 50-dB quieting, 14.1 dBf (mono) 36.8 dBf (stereo); frequency response, 30-Hz-15 kHz +0.5, -1.4 dB; S/N ratio, 74 dB (mono), 70 dB (stereo) without Dolby, 84 dB (mono) 80 dB (stereo) with Dolby; and IF rejection, 85 dB. The AM section provides an alternate channel selectivity of 32 dB at 1 MHz. The *model LR-120DB* measures 21½ W X 7 H X 17½-inches D and weighs 41 lb, 14 oz. Price: \$599.—**Lafayette Radio Electronics Corp.**, 111 Jericho Turnpike, Syosset, NY 11791.

CIRCLE 126 ON FREE INFORMATION CARD

FREE SWTP

CATALOG

Audio—Computers
Instruments
Kits & Assembled

COMPUTER
PRODUCTS
CATALOGUE



Southwest Technical Products Corporation

219 W. RHAPSODY

SAN ANTONIO, TEXAS 78216

CIRCLE 60 ON FREE INFORMATION CARD

TURNTABLE TONEARM, model MA-707, is incorporated in Micro Seiki turntables (models DQX-500, DQ-43 and DD-33) and is also available separately. A torsion bar system is used in the tonearm to provide optimum 10-Hz resonance. Specifications include: maximum tracking error less than 1.5 degrees/inch; tracking force adjustment of 0-3 grams; and a 315-mm overall length; a 4- to 12-gram-weight cartridge is recommended.



The model DQX-500 turntable is a direct-drive, quartz-locked manual unit, with a 5.75-lb platter and dustcover; the model DQ-43 turntable has a 3.33-lb aluminum platter with automatic lift and shutoff capability, and a rosewood base; and the model DD-33 features a servo-controlled motor and a 2-lb aluminum platter. Suggested retail prices: model MA-707 tonearm, \$200; model DQX-500, \$500; model DQ-43, \$450; model DD-33, \$350.—TEAC Corp. of America, 7733 Telegraph Rd., Montebello, CA 90640.

CIRCLE 127 ON FREE INFORMATION CARD



HIGH BLOOD PRESSURE.
Treat it...and live.

The National High Blood Pressure Education Program,
U.S. Department of Health, Education, and Welfare.

Includes
Functional
Tilt Stand!

**NEW EICO 270
3½ DIGIT DMM KIT
ONLY \$79.95**

Introductory Offer—FREE AC ADAPTOR

The first and only lab accuracy portable DMM Kit featuring MOS/LSI IC economy and reliability. Measures DC/AC Volts, Kilohms, DC/AC milliamps in 21 ranges. Polarity indicators and overload protection are provided, and 0.5 inch LED displays give easiest-to-read digital readout to 1999. The 270 features a basic 0.5% DC accuracy, 10 Megohm input impedance, low voltage drop in all current ranges and automatically flashing overrange indicator. **Assembled \$109.95**

FREE '78 EICO CATALOG

Check reader service card or send 50¢ for first class mail. See your local EICO Dealer or call (516) 681-9300, 9:00 a.m. - 5:00 p.m. EST. Major credit cards accepted.

EICO—108 New South Rd.
Hicksville, N.Y. 11801



CIRCLE 7 ON FREE INFORMATION CARD

**Cramped
for Antenna
space?**



The MCKAY DYMEK DA 100.

The DA 100 is a compact, wide dynamic range, broadband, untuned, omni-directional receiving antenna covering the frequency range of 50 kHz to 30 MHz.

The exterior module, a small weather-proof box with a 56 inch (142 cm) whip delivers the signal to the power supply unit through a supplied 50' coaxial cable.

The power supply locates near your general coverage receiver and attaches with a supplied patch cord.

The DA 100 antenna is small, but will equal or outperform a 100' long wire antenna, and is priced within reach of everyone!

Output Impedance - Attenuator Switch provided to match receiver input requirements and prevent overload.

Order factory Direct. Call toll free today! Money Back guarantee. Rent/Own Plan available. Specs and details on request.

Nationwide 800/854-7769
California 800/472-1783



MK McKay Dymek Co.
111 S. College Ave., PO Box 5000
Claremont CA 91711

CIRCLE 8 ON FREE INFORMATION CARD

**WANT BIGGER
PROFITS?**

More and more Servicemen are finding out how great Oneida's NuColor Picture Tube Restorer is! Not a Brightener, but a potential new way to put new life in many old, weak, colorless, picture tubes. Customer satisfaction now paves the way to a picture tube sale down the line. Get all the facts...see your Oneida dealer now or write us direct.

Oneida's

**NEW ...
TRIED AND TESTED
NU-COLOR®
PICTURE TUBE
RESTORER**




ONEIDA ELECTRONIC MFG. INC.
P.O. Box 678, Baldwin Street Ext., Meadville, Pa. 16335
Phone (814) 336-2125

CIRCLE 72 ON FREE INFORMATION CARD

Don't risk a \$20 IC chip

...be safe with **RN**

DIP SOCKETS costing pennies!

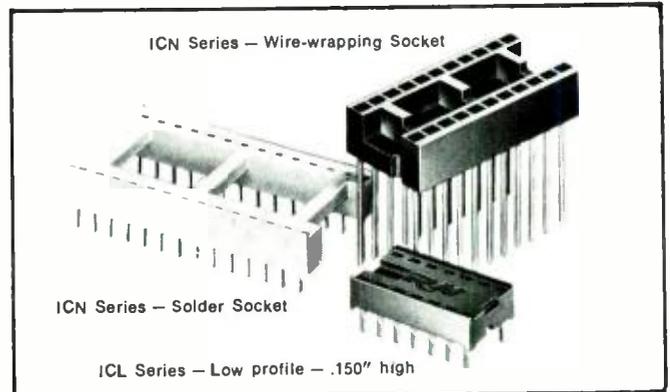

Don't damage an expensive IC chip with soldering iron heat! Simply solder an R-N DIP socket to your PC board, then insert IC chip into the socket. Changes in your microprocessor system are easy. Just remove the IC chip — and then take the low cost socket off of the board without harming the chip.

ORDER ROBINSON-NUGENT DIP SOCKETS FROM:

DIGI-KEY Corp.

Carries a full line of R-N IC Sockets
TOLL FREE—1-800-346-5144 In Minnesota—1-218-681-6674

ALLIED Electronics

Specify 906 Series IC Sockets
TOLL FREE—1-800-433-1570 In Texas—1-800-792-8760

The best speaker kit isn't a kit at all!



The best speaker kit is a system designed by Electro-Voice that allows you to choose your own level of performance; from a studio monitor to a modest bookshelf system, from a wide selection of woofers, tweeters, mid-range drivers and crossovers.

Then Electro-Voice provides detailed plans on how to construct the enclosures designed specifically for the drivers you chose.

Only Electro-Voice gives you all the options. But, then, Electro-Voice is known for their superb quality speakers - not for kits.

To get your component speaker catalog and construction plans package, just send \$1.00 to Electro-Voice Component Speaker Systems, 600 Cecil St., Buchanan, MI 49107.



600 Cecil Street, Buchanan, Michigan 49107

Electro-Voice Component Speaker Systems, 600 Cecil St., Buchanan, MI 49107.

Please send me E-V component speaker packages.

I have enclosed \$1.00 for each package ordered.

Name _____

Address _____

City State Zip _____

RE-11-78

RADIO-ELECTRONICS

books

A BEGINNER'S GUIDE TO MAKING ELECTRONIC GADGETS, by R. H. Warring. TAB Books, Blue Ridge Summit, PA 17214. 140 pp. 5 X 8 1/4 in. Softcover, \$4.95; hardcover, \$8.95.


This book uses easy-to-follow instructions and detailed diagrams to show you how to create 100 different kinds of circuits—from basic designs to more sophisticated projects—using readily available components. Proceeding from the basic circuits, the book teaches you how to couple them and to make such devices as metal detectors, burglar alarms, Morse code senders, electronic organs, temperature sensors, ohmmeters, etc.

MAKE PC BOARDS, by Edgar S. Young. Technical Workshop Publications, P.O. Box 368, Placentia, CA 92670. 64 pp. 5 1/2 X 8 1/4 in. Softcover \$4.98.

To produce high-quality PC boards requires sophisticated construction methods, three of which are discussed in detail in this book: the direct-transfer method, the polyester drafting film approach, and the photo film chemical method.

Each chapter starts with an outline of method procedure. The text is appropriately illustrated, and there is a handy Appendix in the back of the book.

PROFESSIONAL AIDS SHELF FILES

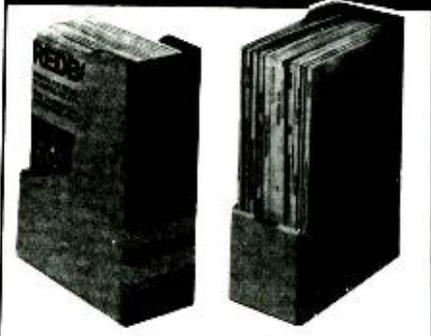

Eliminate the clutter of loose magazines, catalogs, etc. Find what you want, when you want it by utilizing these handy shelf or desk top files. Available in 6 sizes from Reader's Digest to newspaper size. Constructed of heavy duty fibreboard. Attractive front panel. Adhesive identification labels included. Popular letter size: 11 1/2 x 9 x 3/4



Store on Shelves

Organize Your Desk

ORDER DIRECT

10 for \$15.89 — 25 for \$28.97
Other sizes available — Request Catalog
Shipped pre-paid, Canada, add \$1.00

VISA & MASTER CHARGE ACCEPTED
ADVISE CARD NO. AND EXPIRATION DATE
PROFESSIONAL AIDS CO.
1 S. WACKER DR., SUITE RE 130
CHICAGO, ILL. 60606

CIRCLE 78 ON FREE INFORMATION CARD

Part of the money you give the American Cancer Society helps the International Association of Laryngologists help thousands of people to learn to talk again after their voice boxes have been removed. Give to the American Cancer Society. American Cancer Society.

Money Talks

EIGHT INSTRUMENTS IN ONE

- Out-of-Circuit Transistor Analyzer
- Dynamic In-Circuit Transistor & Radio Tester
- Signal Generator
- Signal Tracer • Voltmeter
- Milliammeter
- Battery Tester
- Diode Checker

Transistor Analyzer Model 212

Factory Wired & Tested — \$32.71
Easy-to-Assemble Kit — \$21.79

YOU DON'T NEED A BENCH FULL OF EQUIPMENT TO TEST TRANSISTOR RADIOS! All the facilities you need to check the transistors themselves — and the radios or other circuits in which they are used — have been ingeniously engineered into the compact, 6-inch high case of the Model 212. It's the transistor radio troubleshooter with all the features found only in more expensive units. Find defective transistors and circuit troubles speedily with a single, streamlined instrument instead of an elaborate hook-up.

Features:
Checks all transistor types — high or low power. Checks DC current gain (beta) to 200 in 3 ranges. Checks leakage. Universal test socket accepts different base configurations. Identifies unknown transistors as NPN or PNP.

Dynamic test for all transistors as signal amplifiers (oscillator check), in or out of circuit. Develops test signal for AF, IF, or RF circuits. Signal traces all circuits. Checks condition of diodes. Measures battery or other transistor-circuit power-supply voltages on 12-volt scale. No external power source needed. Measures circuit drain or other DC currents to 80 milliamperes. Supplied with three external leads for in-circuit testing and a pair of test leads for measuring voltage and current. Comes complete with instruction manual and transistor listing.

EMC, 625 Broadway, New York 12, N. Y.

Send me FREE catalog of the complete value-packed EMC line, and name of local distributor.

NAME _____ RE-11

ADDRESS _____

CITY _____ ZONE _____ STATE _____

EMC

ELECTRONIC MEASUREMENTS CORP.
625 Broadway, New York, N. Y. 10012



More information on new lit is available from the manufacturers of items identified by a Free Information number. Use the Free Information Card inside the back cover of this issue.

ELECTRONIC COMPONENTS CATALOG, 1978 Purchasing Manual 518, 88 pages offering a broad range of components, tools, hardware and equipment. The catalog features an extensive semiconductor line, LED's and lamps, SCR's and Triacs, plus hundreds of other components—from alligator clips to wire and cables. A handy order form is contained in the back, and a convenient quick index on the front cover.—**Mouser Electronics**, 11511 Woodside Ave., Lakeside, CA 92040.

CIRCLE 128 ON FREE INFORMATION CARD

COMPUTER PRODUCTS GUIDE, 1978 System Builders' Catalog, contains 48 pages of data on computers, peripherals and computer books and magazines, complete with descriptions and a comparison chart for over 1500 products. Included are Southeast Tech 6800, IMSAI 8080, Processor Tech Sol 20, IASIS 8080, Olivetti P6060, Intersil Intercept, Jr., Commodore Kim, RCA Cosmac, Motorola 6800 and National SC/MP computers.


There's also a wide choice of used equipment, including Centronics printers, Teletype and Olivetti teletypewriters, CRT terminals, video monitors, keyboards, modems, and many more. The back side of the catalog carries an additional 31 pages of used computers, memory and peripherals. The catalog is available for \$1.—**Computer Warehouse**, American Used Computer Corp., 584 Commonwealth Ave., Boston, MA 02215.

MICROCOMPUTER BROCHURE is a four-page roundup of manufacturer's line of computers, peripheral devices and software. Among the 18 products described is the *Memorite* video-based text-editing system incorporating the Vector-1 computer. Many S-100 bus-compatible boards are also included, as well as an assembler/editor program, a disassembler and a flexible-disc operating system.—**Vector Graphic, Inc.**, 790 Hampshire Rd., A + B, Westlake Village, CA 91361.

CIRCLE 129 ON FREE INFORMATION CARD

HEATH SCHLUMBERGER INSTRUMENTS, Catalog 811-25, contains 32 pages of assembled test instruments for hobbyists and service technicians. Some of the products featured are oscilloscopes, power supplies, signal and function generators, VOM's, DMM's, strip-chart recorders, and a complete line of accessories, including probes and connecting cables. Additionally, the catalog contains a list of self-instruction courses suitable for industrial training, covering such topics as AC and DC electronics, semiconductor devices and digital techniques.—**Heath Schlumberger Instruments**, Dept. 570-020, Benton Harbor, MI 49022.

CIRCLE 50 ON FREE INFORMATION CARD

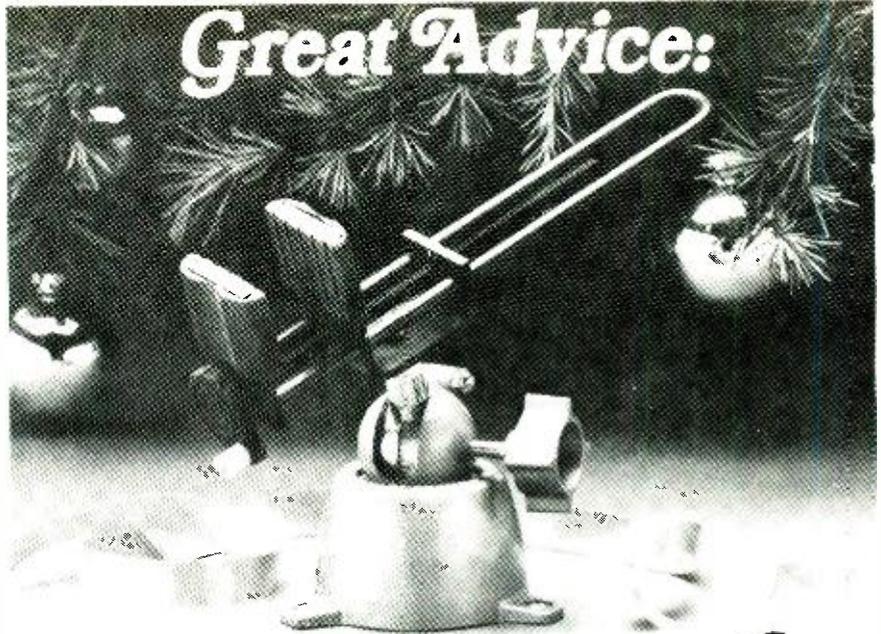

Give a Great Vise!

PanaVise ... a great gift idea. Everyone loves a PanaVise. It tilts, turns and rotates every which way to quickly and securely position electronic parts and PC boards exactly where wanted. Sturdy all metal construction. Model 396 PanaVise shown. Available at your electronic distributors, boxed ready to go, along with a variety of other PanaVise interchangeable bases, holders and accessories.

PANAVISE® Write for FREE brochure and distributor list.
Dept. CE5, 2850 29th Street, Long Beach, CA 90806
CIRCLE 47 ON FREE INFORMATION CARD

You Can Count On DAVIS!



NEW CTR-2A
500 MHz & 1 GHz COUNTERS
NOW WITH
PERIOD MEASUREMENT (Optional)
AND BUILT-IN PREAMP

- 8 Digit .3" LED Display
- High Stability TCXO Time Base
- Built-in VHF-UHF Prescaler & Preamp
- Period 1us to 1 sec. (optional)
- TCXO Std. ± 2 ppm
- Input Diode Protected
- 12V-DC Operation (optional)
- Oven Crystal ± .5 ppm (optional)
- Selectible Gate Times .1 sec. & 1 sec.

500 MHz kit CTR-2A-500K	\$249.95
500 MHz assembled CTR-2A-500A	349.95
1 GHz kit CTR-2A-1000K	399.95
1 GHz assembled CTR-2A-1000A	549.95

OPTIONS:	
(02) Oven Crystal	\$49.95
(03) .43" LED	10.00
(04) 12 V-DC	10.00
(05) 10 sec. Time Base	10.00
(06) Period Option	15.00




DAVIS ELECTRONICS
636 Sheridan Drive
Tonawanda, NY 14150
716/874-5848



CIRCLE 64 ON FREE INFORMATION CARD

ADVANCING the state of the art

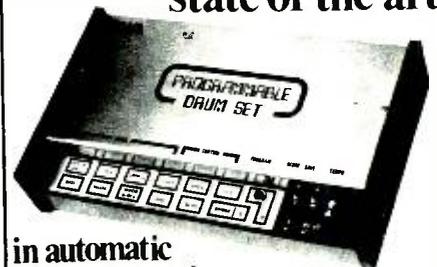

in automatic percussion units... the **PROGRAMMABLE DRUM SET** features: score editing, bridges, intro's, external sync to sequencers foot controls, memory save switch & much more.

Enter scores in seconds - **NO PROGRAMMING KNOWLEDGE IS REQUIRED!**

High Fidelity describes the 3750 as "an easy project... fun to do and yields delightful results... an excellent educational tool and versatile aid to the musician who can't afford a live rhythm section."

#3750 \$84.95... (+\$3 shipping)

Another Great Kit from: **DAI**

117 WEST WILSHIRE BLVD. OKLAHOMA CITY, OK 73116

- Send Programmable Drum Set Kit (\$84.95 + shipping enclosed)
- Factory assembled Programmable Drum Set (\$149.95 + \$3.00 shipping)

name: _____

address: _____

City: _____ State: _____ Zip: _____

SEND FREE CATALOG

CIRCLE 21 ON FREE INFORMATION CARD

FREE

World's biggest and best source of top-quality electronic kits!
Look at what's new in our new just-off-the-press catalog!

NEW

Computerized Weather Monitor



If you need weather information for ANY purpose, the ID-4001 is the way to get it! This microcomputer-based weather instrument displays — time of day in 12 or 24-hour format; wind direction and magnitude; indoor and outdoor temperature; barometric pressure; even wind chill factor! What's more, the computer's memory stores the highest and lowest data for each function so you can recall it for easy and accurate record keeping. Chart recorder and computer outputs provide even more versatility!

NEW

Rack-Mount Stereo Components



Heath has developed an entire new line of sophisticated audio equipment designed to offer the striking good looks and versatility of rack mounting combined with specifications and performance capabilities that are the equal of the finest components available today! The AA-1600 Stereo Power Amplifier features 125 watts, minimum RMS, per channel into 8 ohms, with less than 0.05% total harmonic distortion from 20-20,000 Hz. The AD-1700 provides a graphic LED display of power output to monitor system performance and help prevent overloads. Other components soon to come will be a versatile, low-distortion stereo preamplifier, and a deluxe digital FM-AM Stereo Tuner.

NEW

Digital Readout Car Clock with Trip Timer



Versatile clock/timer for any vehicle shows time in hours and minutes, has 24-hour timer that reads to nearest second. Bright, easy-to-read display, low-power circuit doesn't drain battery.

NEW

Deluxe Dual-Trace Oscilloscope



Low-priced dual-trace scope ideal for audio and TV servicing. Features outstanding sensitivity, extra-bright traces, selectable triggering, 7-position variable time base, DC to 5 MHz bandwidth.

NEW

Hand-Held 2-Meter Transceiver



Superb features specifications and a great low price make the VF-2031 a terrific buy in a hand-held two-meter transceiver. Features 8-channel simplex with ± 600 kHz offset using one crystal per channel, minimum 2 watts out, and 0.5 μ V sensitivity for 20 dB quieting. Includes built-in antenna, nickel-cadmium batteries and battery charger. An optional tone encoder and other accessories also available.

NO PREVIOUS EXPERIENCE NECESSARY

Thousands of people with no electronics experience whatsoever — people who have never handled a soldering iron before — have proved that you can build any Heathkit product you want — and enjoy every moment of it! Simple step-by-step manuals make it easy as 1-2-3, and every Heathkit product you build will be a source of pride and satisfaction for years to come as you say "I built it myself"!



Heath Company, Dept 020-470
Benton Harbor, Michigan 49022

HEATHKIT ELECTRONIC CENTERS* PROVIDE SALES AND SERVICE

ARIZONA — Phoenix, 85017, 2727 W. Indian School Rd. 602-279-6247.

CALIFORNIA — Anaheim, 92805, 330 E. Ball Rd. 714-776-9420; El Cerrito, 94530, 6000 Potrero Ave. 415-236-8870; Los Angeles, 90007, 2309 S. Flower St. 213-749-0261; Pomona, 91767, 1555 Orange Grove Ave. N. 714-823-3543; Redwood City, 94063, 2001 Middlefield Rd. 415-365-8155; Sacramento, 95825, 1860 Fulton Ave. 916-486-1575; San Diego, (La Mesa, 92041), 8363 Center Dr. 714-461-0110; San Jose (Campbell, 95008), 2350 S. Bascom Ave. 408-377-8920; Woodland Hills, 91364, 22504 Ventura Blvd. 213-882-0531.

COLORADO — Denver, 80212, 5940 W. 38th Ave. 303-422-3408.

CONNECTICUT — Hartford (Avon, 06001), 395 W. Main St. (Rte. 44) 203-678-0323.

FLORIDA — Miami (Hialeah, 33012), 4705 W. 16th Ave. 305-823-2280; Tampa, 33614, 4019 West Hillsborough Ave. 813-886-2541.

GEORGIA — Atlanta, 30342, 5285 Roswell Rd. 404-252-4341.

ILLINOIS — Chicago, 60645, 3462-66 W. Devon Ave. 312-583-3920; Chicago (Downers Grove, 60515), 224 Ogden Ave. 312-852-1304.

INDIANA — Indianapolis, 46220, 2112 E. 62nd St. 317-257-4321.

KANSAS — Kansas City (Mission, 66202), 5960 Lamar Ave. 913-362-4486.

KENTUCKY — Louisville, 40243, 12401 Shelbyville Rd. 502-245-7811.

LOUISIANA — New Orleans (Kenner, 70062), 1900 Veterans Memorial Hwy. 504-722-6321.

MARYLAND — Baltimore, 21234, 13 E. Joppa Rd. 301-661-4446; Rockville, 20852, 5542 Nicholson Lane. 301-881-5420.

MASSACHUSETTS — Boston (Peabody, 01960), 242 Andover St. 617-531-9330; Boston (Wellesley, 02181), 165 Worcester Ave. (Rt. 9 just west of Rt. 128) 617-237-1510.

MICHIGAN — Detroit, 48219, 18645 W. Eight Mile Rd. 313-535-6480; E. Detroit, 48021, 18149 E. Eight Mile Rd. 313-772-0416.

MINNESOTA — Minneapolis (Hopkins, 55343), 101 Shady Oak Rd. 612-938-6371; St. Paul, 55106, 1645 White Bear Ave. 612-778-1211.

MISSOURI — St. Louis (Bridgeton) 63044, 3794 McKelvey Rd. 314-291-1850.

NEBRASKA — Omaha, 68134, 9207 Maple St. 402-391-2071.

NEW JERSEY — Fair Lawn, 07410, 35-07 Broadway (Rte. 4) 201-791-6935; Ocean, 07712, 1013 State Hwy. 35. 201-775-1231.

* Units of Schlumberger Products Corporation. Retail prices on some products may be slightly higher.

Opening Soon:
Salt Lake City, Utah; Oklahoma City, Okla.

if you want quality...value...and pride of craftsmanship
 get the **NEW HEATHKIT® CHRISTMAS
 CATALOG!**



COAST-TO-COAST

NEW YORK — Buffalo (Amherst, 14226), 3476 Sheridan Dr. 716-835-3090; Jericho, Long Island, 11753, 15 Jericho Turnpike. 516-334-8181; Rochester, 14623, 937 Jefferson Rd. 716-244-5470; White Plains (North White Plains, 10603), 7 Reservoir Rd. 914-761-7690.

OHIO — Cincinnati (Woodlawn, 45215), 10133 Springfield Pike. 513-771-8850; Cleveland, 44122, 28100 Chagrin Blvd. 216-292-7553; Columbus, 43229, 2500 Morse Rd. 614-475-7200; Toledo, 43615, 48 S. Byrne Rd. 419-537-1887.

PENNSYLVANIA — Philadelphia, 19149, 6318 Roosevelt Blvd. 215-288-0180; Frazer (Chester Co.) 19355, 630 Lancaster Pike (Rt. 30) 215-647-5555; Pittsburgh, 15235, 3482 Wm. Penn Hwy. 412-824-3564.

RHODE ISLAND — Providence (Warwick, 02886), 558 Greenwich Ave. 401-738-5150.

TEXAS — Dallas, 75201, 2715 Ross Ave. 214-826-4053; Houston, 77027, 3705 Westheimer. 713-623-2090; San Antonio, 78218, 7111 Blanco Road. 512-341-8876.

VIRGINIA — Alexandria, 22303, 6201 Richmond Hwy. 703-765-5515; Norfolk (Virginia Beach, 23455), 1055 Independence Blvd. 804-460-0997.

WASHINGTON — Seattle, 98121, 505 8th Ave., N. 206-682-2172.

WISCONSIN — Milwaukee, 53218, 5215 W. Fond du Lac. 414-873-8250.

HEATH Schlumberger	Heath Company, Dept 020-470 Benton Harbor, Michigan 49022
Please send me my FREE Heathkit Catalog. I am not on your mailing list.	
Name _____	
Address _____	
City _____	State _____
Zip _____	
GX-354	
NOTE: This FREE Catalog Coupon can also be redeemed at any of the Heathkit Electronic Centers* nationwide. (See list at left)	

NOVEMBER 1978

CIRCLE 100 ON FREE INFORMATION CARD

INTERNATIONAL FM-2400CH

FREQUENCY METER FOR TESTING MOBILE TRANSMITTERS AND RECEIVERS

• Portable • Solid State • Rechargeable Batteries

The **FM-2400CH** provides an accurate frequency standard for testing and adjustment of mobile transmitters and receivers at predetermined frequencies.

The FM-2400CH with its extended range covers 25 to 1000 MHz.

The frequencies can be those of the radio frequency channels of operation and/or the intermediate frequencies of the receiver between 5 MHz and 40 MHz.

Frequency stability: $\pm .0005\%$ from $+50^\circ$ to $+104^\circ\text{F}$.

Frequency stability with built-in thermometer and temperature corrected charts: $\pm .00025\%$ from $+25^\circ$ to $+125^\circ$ (.000125% special 450 MHz crystals available).

- Tests Predetermined Frequencies 25 to 1000 MHz
- Extended Range Covers 950 MHz Band
- Pin Diode Attenuator for Full Range Coverage as Signal Generator
- Measures FM Deviation

FM-2400CH (meter only) Cat. No. 035320	\$595.00
RF crystals (with temperature correction)	24.90 ea.
RF crystals (less temperature correction)	18.90 ea.
IF crystals	catalog price

Write for catalog



INTERNATIONAL CRYSTAL MFG. CO., INC.
10 North Lee / Oklahoma City, Okla. 73102

CIRCLE 56 ON FREE INFORMATION CARD

DIGITAL WINDSHIELD WIPER DELAY

continued from page 63

control circuit to be used with wiper circuits having a switched ground connection. Note that the D input to IC5-a is normally high with the wipers switched off; therefore, the connections to pins 1 and 2 of IC5-a have been transposed. Rectifier D4 blocks +12 volts from any leakage paths in the wiper circuit. A wiper circuit with switched ground (used by General Motors) is shown in Fig. 13. When the wipers are switched on, the relay closes to energize the field winding in series with the armature. A secondary field winding shunts the armature in slow speed. In fast speed a 20-ohm resistor is placed in series with the shunt winding to minimize its effect. When the wipers are switched off, the relay is de-energized, but *its contact remains latched closed until released mechanically by the motor* when it reaches the park position. Figure 14 shows how to attach the control to this type of wiper circuit to affect both slow and fast speed.

The most difficult windshield wiper circuits to interface with are those having one fixed speed and one variable speed plus concealed blades; some even use three-pole and even four-pole selector switches. However, with a little patience, ingenuity, and perhaps using a supplementary relay or the second set of timer-relay contacts, you should be able to create a satisfactory arrangement. (Radio-Electronics would like to hear from anyone who feels he has developed an unusually clever circuit for attaching the control to a popular model car, and will consider publishing details in a future issue for the benefit of other readers.)

R-E

The WunderBuss™

End noise and cross-talk with our exclusive **Noiseguard™** system



Build your S-100 system on the WunderBuss™ 20-slot bus-board with Noiseguard™ and you'll get "textbook clean" signals.

The Noiseguard™ system's interlaced ground system shields all bus lines from cross-talk... and low-power active termination absorbs noise and signal reflections.

The printed circuit board is double-sided and (of course) has a solder mask. And there's 3 uncommitted

positions for peripheral power.

The incomparable WunderBuss™, by Morrow's Micro-Stuff, is now available for \$76 alone. With 10 edge connectors, \$120. With 20 edge connectors \$154. Add \$3 handling.

Thinker Toys™

1201 10th. St.
Berkeley, CA
94710

Order it at your local computer shop.
Or phone BAC/MC orders to (415) 524-5317

CIRCLE 49 ON FREE INFORMATION CARD

market center

CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services) **\$1.50 per word (no charge for zip code)** . . . minimum 15 words.

NONCOMMERCIAL RATE (for individuals who want to buy or sell personal items) **85¢ per word** . . . no minimum.

ONLY FIRST WORD AND NAME set in bold caps. Additional bold face (not available as all caps) at 10¢ per word. Payment must accompany all ads except those placed by accredited advertising agencies. 5% discount for 6 issues, 10% for 12 issues within one year, if paid in advance. All copy subject to publisher's approval. Advertisements using P.O. Box address will not be accepted until advertiser supplies publisher with permanent address and phone number. Copy to be in our hands on the 26th of the third month preceding the date of the issue (i.e., August issue closes May 26). When normal closing date falls on Saturday, Sunday or a holiday, issue closes on preceding working day.

FOR SALE

FREE catalog (anglais). IC's, semi's. **CORONET ELECTRONICS**, 649A Notre Dame W., Montreal, Que., Canada, H3C-1H8. US inquiries.

RADIO & TV tubes 36¢ each. One year guaranteed. Plus many unusual electronic bargains. Free catalog. **CORNELL**, 4217-E University, San Diego, Calif. 92105

BLITZ ZOINK ZATT: UNSCRAMBLE these fascinating police communications with our **CODE-BREAKER** and keep informed. Tunes all scramble frequencies, works with all scanners, and is factory built and guaranteed.



\$34.95PP. UNSCRAMBLER KIT: Latest Technology. 2 1/2" X 2 1/4" X 1 1/2" inch, complete instructions, only \$19.95PP. Thousands of satisfied customers. Catalog \$0¢. Order from **KRYSTAL KITS**, BOX 445, BENTONVILLE, ARK. 72712. COD orders. 501-273-5340.

NOTICE: RECORD RATERS WANTED

(No experience required) Each month you will receive nationally released albums to rate. THERE IS NO EXTRA CHARGE for the LP's you receive. You pay a small membership fee which covers all costs of the LP's. We pay postage. In return for your opinion, build your LP collection. "First come basis." For application write: **EARS. DEPT. RX** Box 10245, 5521 Center St., Milwaukee, WI 53210.

© 1975

SANKEN 50-watt power AMP 22.50 postpaid, 50-volt transformer for above 8.00 postpaid. **PRARIE SOUNDS**, P.O. Box 982, Champaign, IL 61820

RECORDS-TAPES! Discounts to 73%; all labels; no purchase obligations; newsletter; discount dividend certificates; 100% guarantees. Free details. **DISCOUNT MUSIC CLUB**, 650 Main St., Dept. 3-1178, New Rochelle, NY 10801

To run your own classified ad, put one word on each of the lines below and send this form along with your check for \$1.50 per word (minimum 15 words) to:

Radio-Electronics, 200 Park Avenue South, N.Y., N.Y. 10003

ORDER FORM

PLEASE INDICATE in which category of classified advertising you wish your ad to appear. For special headings, there is a surcharge of \$10.

() Plans/Kits () Business Opportunities () For Sale
() Education/Instruction () Wanted ()

Special Category: \$10

(PLEASE PRINT EACH WORD SEPARATELY, IN BLOCK LETTERS.)

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35

AUDIO modules 15W-60W X 2 under \$85.00. Free catalog: **AUDIOVISION**, Box 955, STN.B, Willowdale, Ont., Canada M2K 2T6

PRINTED CIRCUIT

Positive Acting Photo Resist; Carbide bits; Bubble etchers; Artwork; Epoxy Glass Boards.

Send stamp & address label for flyer

TRUMBULL

833 Balra Dr., El Cerrito, CA 94530

NEW electronic parts. Continuously stocked. Stamp brings catalog. **DAYATPRO ELECTRONICS**, 3029 Wilshire Ln., Dept. RE, Arlington Hts., IL 60004

SPEAKER INFORMATION KIT

Get 70 pages of speaker facts, specs, construction tips plus info on our raw speakers, crossovers and a line of 9 quality hi-fi speaker system kits. We'll send you our **full-color catalog**; plus **How to Hook Up Your System**, an exhaustive step-by-step treatise on hi-fi system installation; and our **Speaker Operating Manual**, chock full of facts on how to get the most from any speaker system. For only \$1.00. Even if you don't buy from us we want you to have the facts. That's how we got to be the world's largest manufacturer of speaker kits.

Send to:
Speakerlab, Dept. RE-H
735 N. Northlake
Seattle, WA 98103




TS-510A signal generator 10-420 MHz \$250.00, **USM-140C** dual-trace oscilloscope \$250.00. Stamp for catalog. **E. FRENCH**, Box 249, Aurora, IL 60507

PARTS! CORNELL TUBES!
FREE Send For FREE
CORNELL'S New Color Catalog
48 Pct. New Items IN LOTS OF 100
33¢ per tube
36¢ per tube
ORDER FREE IF NOT SHIPPED IN 24 HOURS
4215 E UNIVERSITY AVE. SAN DIEGO, CALIF. 92105

QUARTZ crystal-controlled clock movements \$14.95 . . . transistorized movements \$8.50 . . . use C battery . . . hands included. 60¢ shipping. **PEKO**, Box 1215, Studio City, CA 91604

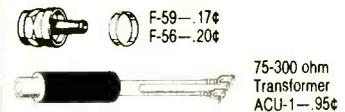TASCO offers reliable TV antenna system components below wholesale prices. Write for our **FREE** 32 page catalog full of great surplus bargains. Such bargains as:



F-59—17¢
F-56—20¢

75-300 ohm
Transformer
ACU-1—95¢


MS-2 2-Way Splitter—\$2.95
MS-4 4-Way Splitter—\$4.95



TEXAS ANTENNA SUPPLY CO.
P.O. BOX 30143
HOUSTON, TEXAS 77009


KITS • KITS • KITS

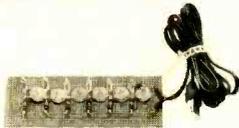Perforated Boards **NOT INCLUDED** w/100 Series



103 MINI-WINK NEON FLASHER. Random flash pattern. Interesting displays. 6 neon lamps. AC operated.

103	\$3.00
103A (103 w/PCB)	4.65
103B (103 w/PCB,CASE)	6.90

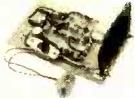

110 ELECTRONIC WHOOPER SIREN. Powerful wailing sound. Dual oscillator circuit. Use with any alarm circuit. Battery not included.

110	\$4.95
110A (110 w/PCB)	6.50
110B (110 w/PCB,CASE)	9.60



117 TUNABLE ELECTRONIC ORGAN. Tunable 7-note scale. Play sing-a-long favorites. Battery not included.

117	\$7.55
117A (117 w/PCB)	9.50
117B (117 w/PCB,CASE)	12.60



120 SIREN/CODE OSCILLATOR. Loud, piercing alarm. Practice Morse code. Battery not included.

120	\$4.20
120A (120 w/PCB)	5.55
120B (120 w/PCB,CASE)	8.65



104 VARIABLE STROBE LIGHT. Great for parties and photography. Variable flash rate. AC operated.

104	\$10.60
104A (104 w/PCB)	14.85
104B (104 w/PCB,CASE)	20.35



126 PROGRAMMABLE DOORBELL. Adjustable rate and pitch for 15 musical notes. Play favorite tunes. 6 IC's. Uses existing transformer and switch.

126	\$16.95
126A (126 w/PCB)	23.70
126B (126 w/PCB,CASE)	29.20

502 POWER SUPPLY. Switch from 6 to 9V DC. 100mA output. Filtered. Manual. Stepdown transformer. Insulated test clips.



\$6.95 Complete

540 BINARY CLOCK. Handcraft tomorrow's timepiece today. Watch constantly changing patterns of LED's as they display Binary Time. This unique clock project enhances the learning of Digital Logic and the Binary Coding System, as well as offering a beautifully styled conversation piece.

10 TTL INTEGRATED CIRCUITS • VOLTAGE REGULATOR • MANUAL TEACHES BINARY SYSTEM • FAST, SLOW AND HOLD CONTROLS • 115VAC 50 or 60Hz.



\$39.95 Complete

523 STROBE LITE. Create flashing light effects. Ideal for creating kaleidoscope effects for photography. Long life flash tube. PCB. Manual. Variable flash control. On-off switch. Silicon diodes. 117VAC 50-60 Hz.



\$22.95 Complete

536 8-TRANSISTOR AM RADIO. Experience jewel-like clarity in sound. The best superheterodyne kit circuit available. SEPARATE LOCAL OSCILLATOR for high sensitivity and excellent selectivity. Unique IF Transformer mounting system. Manual. 9V battery required (not included).



\$16.45 Complete

504 TRANSISTOR AMPLIFIER. 4 Transistors. Push-Pull output. Variable volume control. Requires one 9V battery (not included). PCB. Manual. 3 transformer stages for maximum gain. Power output 360mW. Can be operated with any 3.2 - 8 ohm speaker.



\$6.95 Complete

510 FIVE TUBE RADIO. Rediscover TUBES. This fun antique circuit offers high selectivity and sensitivity. 2 IF Transformers. Hi-Q Ferrite antenna. Manual. Superheterodyne circuit. Large PM speaker. For 110-120 VAC or DC.



\$34.95 Complete

401 TACHMETER. Know exactly when to shift. This fabulous Tach, with a range from 0-8 grand, will mount anywhere - dash, steering column, boat, motorcycle frame, etc. 250° wide sweep scale. Reading accuracy within 2% of full scale. PCB. Manual. Illuminated dial. For all cylinder engines.




\$27.95 Complete

Perforated Boards **NOT INCLUDED** w/100 Series



124 WARBLING SIREN. Two-tone oscillating siren. Loud and penetrating, 2 IC's. For automobile or other 12 volt systems.

124	\$5.65
124A (124 w/PCB)	7.10
124B (124 w/PCB,CASE)	10.20

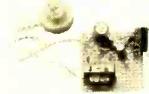


105 FISH CALLER. Clicking sound imitates distressed fish. Adjustable speed. Battery not included.

105	\$3.15
105A (105 w/PCB)	4.30
105B (105 w/PCB,CASE)	5.80



107 COLOR ORGAN CONTROL - 3 CHANNEL. Over 200W per channel. Separate sensitivity control. Hi-mid-lo frequency response. AC operated.

107	\$9.20
107A (107 w/PCB)	11.85
107B (107 w/PCB,CASE)	14.95

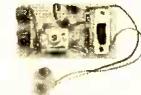

118 TV SCRAMBLER. Tunable to all VHF stations. 30 foot range. Battery not included.

118	\$1.95
118A (118 w/PCB)	2.90
118B (118 w/PCB,CASE)	4.40



122 COMPUTER SOUND EFFECTS GENERATOR. Produces weird, spacey sounds. 4 IC's. Control tone, rate and blip or glide. Battery not included.

122	\$14.95
122A (122 w/PCB)	19.40
122B (122 w/PCB,CASE)	22.75

We accept:
VISA,



MASTER CHARGE
BANKAMERICARD, CALL NOW TOLL FREE
800-824-5136

IN CALIFORNIA CALL 800-852-7631
ASK FOR OPERATOR 318

DO NOT SEND CASH • NO COD • ORDER BY PHONE OR MAIL


MINIMUM ORDER \$10.00. CALIF. RESIDENTS
ADD 6% SALES TAX.

WE PAY POSTAGE AND HANDLING
IN U.S.A. OVERSEAS COUNTRIES:
ADD 15% OF TOTAL FOR POSTAGE.

SEND CHECK OR
MONEY ORDER TO:

Graymark International, Inc.

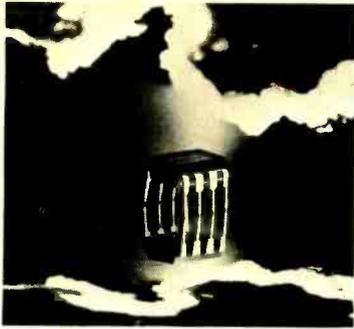1751 McGaw Avenue Dept. 11 Irvine, CA 92714 (714) 540-5480



THE NEW HOBBY WORLD CATALOG

Your source for factory prime, professional quality equipment. Computers, add-on boards, IC's, sockets, resistors, supplies, tools, test equipment,

books, and more. Shop your buy list at Hobby World. You'll find what you want, and at a solid savings. For example, look at this month's specials:

THE NEW ELENCO 3 1/2 DIGIT SOLID STATE MULTIMETER

The ultimate in performance: measures resistance to .01 ohms, voltage to 100 micro-volts, current to one micro-amp. Assembled and tested, with 2-Year warranty. Lists at \$99.95, **HOBBY WORLD PRICE ONLY \$74.95!**

16K MEMORY ADD-ON FOR APPLE OR TRS-80

HOBBY WORLD PRICE IS ONLY \$145.00 (specify when ordering)

WAHL ISO-TIP CORDLESS SOLDERING IRON

Includes ni-cad batteries and wall plug transformer. Lists at \$19.95, **BUT HOBBY WORLD HAS IT FOR \$14.95!**

SEND ME A FREE CATALOG!

Name _____
 Address _____
 City _____ State _____

Hobby World
 19355 Business Center Dr #6
 Northridge CA 91324

TELEPHONE ORDERS
Inside Cal 213 886 9200
Outside Cal 800 423 5387

RE-NOV

CIRCLE 74 ON FREE INFORMATION CARD

TAPE RECORDER!
 5 TRACK, 4 CASSETTE,
 EASILY MODIFIED TO PLAY ONE
 RECORD ANOTHER, ALL CONTROL
 SIGNALS ON EDGE CONNECTORS!
\$169.00 2000FT 1/4" TAPE/CASSETTE,
 PRINTED CIRCUIT MOTORS & TACH GEN; BALL BEARINGS, TOP
 QUALITY MFG! REQUIRES 12VOLT 5AMP DC;
 DATA BOOK & 1 CASSETTE FURNISHED; WT 85
 LBS SHIP'D COD. BOOK \$25, CASSETTE \$25.



STEPPING MOTOR

15°STEP, 28VOLT, LEAD SCREW SHAFT PRECISION BALL BEARING, 5 LEAD WINDING, \$4.95 WITH FOLLOWER & GUIDE \$9.50
 SHAFT .310 DIA 5 1/16 LG WORKING, MOTOR 1 7/16 DIA 2 15/16 LONG

NEW CATALOG! PLEASE SEND SELF ADDRESSED STAMPED ENVELOP FOR FREE COPY NOW!

DC MOTORS

SMALL SIZE 1 5/8" DIA 2 7/16 LG, SHAFT 1/8" DIA 1/2 LG, PM FIELD, BALL BEARING, 28 VOLT REMOVED FROM EQUIP. \$6.00 EACH
 HI TORQUE 3/16" DIA 3 3/4 LG SHAFT, PM FIELD W/MU-METAL SHIELD, B.B., 28VOLT, E.A. \$7.50 MOTOR & TACH GENERATOR, SET \$11.00
 TACH GENERATOR 1" DIA 1 3/4 LG, SHAFT 1/8" DIA 3/8" LONG, PM FIELD, WIRE LEADS, \$5.00
 ADD \$3.00 POSTAGE - BALANCE REFUNDED



CIRCUITBOARD

WIREWRAP, GOLD, 8-16PIN 32-14PIN, 8-26 PIN, 0.25 SQ. MALE RIBBON CONNECTORS, YOU STRIP, EACH \$10.00

NEW KLUGE BOARDS! EPOXY-GLASS, 2 SIDE COPPER, 1/16" X 7 1/2" X 10 1/2" DRILLED FOR 7-16PIN, 28-14PIN, 1-24PIN, & 4-28PIN SOCKETS, MANY THRU HOLES, EACH \$5.00 NO. 2 SAME EXCEPT HAS 13-16PIN, & 36-14PIN PATTERNS, YOU ETCH \$7.50 MIN ORDER \$10.00
J & E ELECTRONICS SALES
 PO BOX 4504, FT. WORTH, TX. 76106

CIRCLE 55 ON FREE INFORMATION CARD

Looking for Original Japanese Replacement Parts for CB, TV and Stereo ?

TYPE	25-up	10-24	1-9	TYPE	25-up	10-24	1-9	TYPE	25-up	10-24	1-9	TYPE	25-up	10-24	1-9	TYPE	25-up	10-24	1-9
ZSA 234	45	53	59	ZSC 372	.20	.27	.30	ZSC 1000BL	.35	.40	.45	ZSK 81	1.10	1.25	1.40	UHC005	5.00	5.20	5.80
ZSA 473	45	95	80	ZSC 373	.20	.27	.30	ZSC 1013	.50	.64	.70	ZSK 68	.40	.45	.50	UPC 20C	2.10	2.50	2.80
ZSA 484	1.90	2.10	2.40	ZSC 380	.20	.27	.30	ZSC 1014	.50	.64	.70	ZSK 22Y	1.40	1.60	1.80	UPC 563	1.90	2.10	2.40
ZSA 485	1.90	2.10	2.40	ZSC 381	.30	.40	.45	ZSC 1018	.30	.40	.45	ZSK 35	1.30	1.45	1.60	UPC579C	1.30	1.45	1.60
ZSA 489	1.10	1.25	1.40	ZSC 382	.30	.40	.45	ZSC 1030C	1.80	2.10	2.40	ZSK 37	1.80	2.10	2.40	UPC 576	1.10	1.20	1.40
ZSA 495	.25	.35	.40	ZSC 387A	.30	.40	.45	ZSC 1060	.70	.80	.90	ZSK 39	.90	1.10	1.20	UPC 592H2	.80	.90	1.00
ZSA 497	1.00	1.20	1.30	ZSC 394	.30	.40	.45	ZSC 1061	.70	.80	.90	ZSK 40	1.30	1.45	1.60	UPC 1001H	1.90	2.10	2.40
ZSA 509	.30	.35	.40	ZSC 458	.20	.27	.30	ZSC 1079	3.40	3.55	3.90	ZSK 41	1.30	1.45	1.60	UPC 1008C	5.00	5.30	5.90
ZSA 537A	1.50	1.70	1.90	ZSC 481	1.30	1.40	1.50	ZSC 1080	3.40	3.55	3.90	ZSK 45	1.30	1.45	1.60	UPC 1020H	1.90	2.10	2.40
ZSA 561	.30	.35	.40	ZSC 1166	.30	.40	.45	ZSC 1098	.45	.55	.60	ZSK 48	3.40	3.55	3.90	UPC 1025	.90	1.10	1.40
ZSA 562	.30	.35	.40	ZSC 482	1.10	1.25	1.40	ZSC 1098	.50	.64	.70	ZSK 49	1.30	1.45	1.60	UPC 1156	1.90	2.10	2.40
ZSA 634	.40	.45	.50	ZSC 485	1.30	1.40	1.50	ZSC 1111	2.10	2.50	2.90	AN 239	3.20	4.40	4.90	UPD 857C	8.00	8.40	9.50
ZSA 643	.30	.40	.45	ZSC 496	.45	.55	.60	ZSC 1114	4.20	4.40	4.90	AN 247	2.50	2.70	3.00	UPD 858C	8.00	8.40	9.50
ZSA 673	.30	.40	.45	ZSC 497	1.10	1.25	1.40	ZSC 1115	2.50	2.70	3.00	AN 274	1.50	1.75	1.95	PLL 01A	3.00	4.20	4.60
ZSA 683	.40	.53	.59	ZSC 509	.30	.40	.45	ZSC 1116	3.20	3.40	3.70	AN 315	1.80	2.00	2.25	PLL 02A	5.00	5.30	5.90
ZSA 684	.40	.53	.59	ZSC 517	3.00	3.20	3.40	ZSC 1116A	3.40	3.55	3.90	BA 511A	1.80	2.00	2.25	PLL 03A	7.60	8.00	8.80
ZSA 695	.40	.53	.59	ZSC 535	.30	.40	.45	ZSC 1124	.80	.90	1.00	BA 521	1.30	1.45	1.60	IS 84	.45	.55	.60
ZSA 699A	.50	.64	.70	ZSC 627	1.30	1.45	1.60	ZSC 1127	.80	.90	1.00	HA 1151	1.50	1.75	1.95	IS 188	.16	.18	.20
ZSA 706	.85	1.00	1.10	ZSC 696	1.00	1.20	1.30	ZSC 1162	.70	.80	.90	HA 1156	1.60	1.80	2.00	IS 332	.35	.40	.45
ZSA 719	.25	.35	.40	ZSC 710	2.80	2.7	3.00	ZSC 1172B	3.20	3.60	3.95	HA 1156W	2.00	2.20	2.50	IS 953	.16	.18	.20
ZSA 720	.25	.35	.40	ZSC 711	.20	.27	.30	ZSC 1173	.50	.64	.70	HA 1306	1.30	1.45	1.60	IS 1007	.35	.40	.45
ZSA 733	.20	.27	.30	ZSC 712	.20	.27	.30	ZSC 1178	11.00	12.60	14.00	HA 1309	2.30	2.40	2.65	IS 1209	.35	.40	.45
ZSA 744	4.20	4.40	4.90	ZSC 717	.35	.40	.45	ZSC 1209	.25	.35	.40	HA 1339	2.50	2.70	3.00	IS 1211	.35	.40	.45
ZSA 745R	3.00	3.20	3.40	ZSC 730	3.00	3.20	3.40	ZSC 1226	.50	.64	.70	HA 1392A	2.50	2.70	3.00	IS 1555	.20	.22	.25
ZSA 747	4.20	4.40	4.90	ZSC 732	.20	.27	.30	ZSC 1226A	.64	.70	.80	HA 1342A	2.50	2.70	3.00	IS 1588	.20	.22	.25
ZSA 847	.40	.53	.59	ZSC 733	.20	.27	.30	ZSC 1237	1.80	2.00	2.25	LA 4031B	1.30	1.45	1.60	IS 1885	.16	.18	.20
ZSB 54	.30	.40	.45	ZSC 734	.20	.27	.30	ZSC 1239	2.20	2.70	2.90	LA 4032P	.30	.40	.45	IS 2076	.20	.22	.25
ZSB 55	.40	.53	.59	ZSC 735	.20	.27	.30	ZSC 1306	1.30	1.70	1.90	ZSD 287	2.50	2.70	2.90	IS 2093	.35	.40	.45
ZSB 75	.30	.40	.45	ZSC 756A	1.50	1.80	2.00	ZSC 1307	2.20	2.70	2.90	ZSD 291	2.10	2.50	2.80	IS 2473	.16	.18	.20
ZSB 186	.20	.27	.30	ZSC 775	1.40	1.60	1.80	ZSC 1383	.30	.40	.45	ZSD 313	.60	.70	.80	IN 310	.12	.13	.15
ZSB 187	.30	.40	.45	ZSC 776	2.00	2.20	2.50	ZSC 1384	.30	.40	.45	ZSD 315	.60	.70	.80	IN 60	.25	.35	.40
ZSB 324	.25	.35	.40	ZSC 777	3.00	3.25	3.50	ZSC 1384	.30	.40	.45	ZSD 325	.60	.70	.80	TA 7045M	2.00	2.20	2.50
ZSB 367	1.10	1.25	1.40	ZSC 778	2.90	3.20	3.40	ZSC 1400	.30	.40	.45	ZSD 358	.70	.80	.90	TA 7055P	2.00	2.20	2.50
ZSB 495	.25	.35	.40	ZSC 781	2.00	2.20	2.50	ZSC 1403	3.20	3.40	3.70	ZSD 358	.70	.80	.90	TA 7060P	.90	1.10	1.20
ZSB 407	.70	.90	1.00	ZSC 784	.35	.40	.45	ZSC 1419	.60	.70	.80	ZSD 359	.80	.90	1.00	TA 7061P	.90	1.10	1.20
ZSB 434	.80	.90	1.00	ZSC 789	.80	.90	1.00	ZSC 1475	.70	.90	1.00	ZSD 381	.85	1.00	1.10	TA 7062P	1.10	1.25	1.40
ZSB 473	.70	.90	1.00	ZSC 793	2.00	2.20	2.50	ZSC 1567A	.60	.70	.80	ZSD 427	1.80	2.00	2.25	TA 7089P	2.00	2.20	2.50
ZSB 474	.70	.80	.90	ZSC 799	2.00	2.20	2.50	ZSC 1667	3.00	3.20	3.40	ZSD 525	.90	1.10	1.20	TA 7132P	1.00	1.30	1.50
ZSB 507	.70	.80	1.00	ZSC 828	.20	.27	.30	ZSC 1675	.25	.35	.40	ZSD 526	.60	.70	.80	TA 7203P	2.50	2.70	2.90
ZSB 511	.30	.40	.45	ZSC 829	.20	.27	.30	ZSC 1678	1.30	1.45	1.60	ZSK 198L	.45	.55	.60	TA 7204P	2.00	2.20	2.50
ZSB 536	1.00	1.20	1.30	ZSC 838	.35	.40	.45	ZSC 1687	.40	.45	.50	ZSK 200	.85	1.00	1.10	TA 7205P	1.50	1.80	2.00
ZSB 557	2.10	2.50	2.80	ZSC 839	.30	.40	.45	ZSC 1728	1.00	1.20	1.30	ZSK 200	.85	1.00	1.10	TC 5082P	3.40	3.55	3.90
ZSB 596	1.10	1.40	1.50	ZSC 867	3.20	3.40	3.70	ZSC 1730	.45	.53	.59	ZSK 33	.60	.70	.80	TBA 8105H	1.90	2.10	2.40
ZSB 596	1.10	1.40	1.50	ZSC 887	2.00	2.20	2.50	ZSC 1760	.90	1.10	1.20	ZSK 40	.50	.64	.70	TC 5080P	5.00	5.20	5.80
ZSB 600	5.00	6.00	6.60	ZSC 899	.20	.27	.30	ZSC 1875	.60	.70	.80	ZSK 40	.50	.64	.70	TC 5081P	3.00	3.20	3.40
ZSC 183	.40	.53	.59	ZSC 930	.20	.27	.30	ZSC 1816	1.50	1.75	1.95	ZSK 41	.40	.45	.50	UHC002	5.00	5.20	5.80
ZSC 184	.40	.53	.59	ZSC 945	.20	.27	.30	ZSC 1908	.25	.35	.40	ZSK 45	.40	.45	.50	UHC004	5.00	5.20	5.80
ZSC 281	.25	.35	.40	ZSC 959	1.00	1.20	1.30	ZSC 1909	2.20	2.70	2.90								

PRICES MAY CHANGE WITHOUT NOTICE COD ORDERS WELCOMED

Minimum order \$5.00 Ohio residents add 4% sales tax Add \$1.00 postage and handling
 Quantity discount prices Ask For Our Complete Price List Manufacturer Inquiries Welcomed
 ALL PARTS GUARANTEED FACTORY DEFECT

IMMEDIATE DELIVERY WITHIN 48 HOURS

ON ALL TRANSISTORS IN STOCK

TOLL FREE TELEPHONE

Nationwide 800/543-1607 LOCAL 513/874-0220
 Ohio 800/582-1630 874-0223
 Hours Mon Fri 10-7 Sat 11-5

FUJI-SVEA ENTERPRISE

a Division of Fuji Svesa Incorporated
 Dept.
 P.O. Box 40325 Cincinnati, Ohio 45240
 Telex 21-4732

Active Electronic Sales Corp.

1978 IC MASTER

Complete integrated circuit data selector. New 1978 edition (2200 pages) is twice as big as last year. Master guide to the latest IC's including microprocessors and consumer circuits.



Free quarterly updates.
\$24.95 \$19.95

Tremendous Opportunity. Subject to Prior Sale, Lowest Price Ever Offered Anywhere.

TTL LOW POWER SCHOTTKY PLASTIC DUAL-IN-LINE I.C.

Part No.	Price										
74LS00	15	74LS47	89	74LS123	79	74LS170	1.25	74LS258	75	74LS368	55
74LS01	15	74LS48	89	74LS124	99	74LS173	95	74LS259	1.45	74LS373	1.75
74LS02	15	74LS49	89	74LS125	59	74LS174	69	74LS260	29	74LS374	1.75
74LS03	15	74LS51	19	74LS126	59	74LS175	69	74LS261	1.85	74LS375	65
74LS04	19	74LS54	19	74LS132	79	74LS181	2.50	74LS266	39	74LS377	1.50
74LS05	19	74LS55	19	74LS133	29	74LS183	3.50	74LS273	1.65	74LS378	1.25
74LS08	19	74LS63	1.50	74LS136	39	74LS190	89	74LS275	4.50	74LS379	1.35
74LS09	19	74LS73	29	74LS138	64	74LS191	89	74LS279	59	74LS386	.49
74LS10	15	74LS74	35	74LS139	64	74LS192	95	74LS280	1.75	74LS390	1.50
74LS11	19	74LS75	49	74LS145	99	74LS193	95	74LS283	85	74LS393	1.25
74LS12	19	74LS76	39	74LS147	1.95	74LS194	75	74LS290	85	74LS395	1.50
74LS13	35	74LS78	39	74LS148	99	74LS195	66	74LS293	1.10	74LS396	1.70
74LS14	59	74LS83	79	74LS151	59	74LS196	1.09	74LS295	1.25	74LS398	2.65
74LS15	19	74LS85	99	74LS153	59	74LS197	1.09	74LS298	1.25	74LS399	1.50
74LS20	15	74LS86	35	74LS155	99	74LS221	1.25	74LS299	2.95	74LS424	4.50
74LS21	19	74LS90	59	74LS156	80	74LS240	1.95	74LS324	1.25	74LS445	1.25
74LS22	19	74LS91	99	74LS157	59	74LS241	1.95	74LS325	2.55	74LS447	1.25
74LS26	25	74LS92	59	74LS158	69	74LS242	1.95	74LS326	2.55	74LS490	1.95
74LS27	21	74LS93	49	74LS160	84	74LS243	1.95	74LS327	2.55	74LS668	.90
74LS28	21	74LS95	70	74LS161	84	74LS244	1.95	74LS347	1.25	74LS669	.90
74LS30	15	74LS96	99	74LS162	84	74LS245	1.95	74LS348	1.75	74LS670	2.00
74LS32	25	74LS107	39	74LS163	84	74LS247	1.25	74LS352	1.35		
74LS33	27	74LS109	32	74LS164	89	74LS248	1.25	74LS353	1.35		
74LS37	23	74LS112	32	74LS165	1.25	74LS249	1.25	74LS362	7.00		
74LS38	23	74LS113	39	74LS166	1.45	74LS251	85	74LS365	55		
74LS40	19	74LS114	39	74LS168	1.50	74LS253	85	74LS366	55		
74LS42	54	74LS122	50	74LS169	1.50	74LS257	60	74LS367	55		

Dual In-line Sockets



Finest Quality Sockets Available Anywhere

- PLUGGABLE SOCKET FOR IC PACKAGES WITH LEADS
- HIGH RELIABILITY GAS TIGHT JOINT.
- FULLY QUALIFIED TO MIL-S-88374
- COMPACT LOW PROFILE DESIGN
- NO WICKING WHEN SOLDERED TO PC BOARD
- FLAMMABILITY RATING: UL-94V-0

Stock level	Contacts	Price
14000	8 PIN	.11
345000	14 PIN	.13
156000	16 PIN	.15
33000	18 PIN	.19
18000	22 PIN	.27
84000	24 PIN	.28
25000	28 PIN	.36
46000	40 PIN	.48

All new major manufacturer production material offered. Largest variety of device types available anywhere.

UV EPROM

Stock level	Part No.	Price
7300	2708	7.99
6800	TMS 2716	24.95

3 power supply version, 16K pin for pin plug in replacement for 2708.

MOS Static RAM'S

Stock level	Part No.	Price
41400	2114	7.50
	4K (1K x 4) 450NS	
59500	2102LFPC	1.19
	1K 350NS (Low Power)	

MICROPROCESSOR CHIPS

Stock level	Part No.	Price
21600	8080A	3.95 5.50
2700	6800	8.95 7.95

GENERAL INSTRUMENT 1 Amp Rectifiers (Epoxy)

Stock level	Part No.	Price
1.7 Million	1N4001	50V .029
9 Million	1N4002	100V .039
5 Million	1N4003	200V .045
5.7 Million	1N4004	400V .049
1.6 Million	1N4005	600V .055
8 Million	1N4006	800V .065
1.8 Million	1N4007	1000V .07

1.5 AMP Single Phase Silicon Bridge Rectifiers

Stock level	Part No.	Price
29000	W02M	200V .28
57000	W04M	400V .32
390000	W06M	600V .34
80000	W08M	800V .39
7000	W10M	1000V .60

SWITCHING DIODES

Part No.	Price
1N914	(100V 4NS) .027
1N4148	(100V 4NS) .027

MOS Dynamic RAM'S

Stock level	Part No.	Price
21110	4K 4060	3.95
	300NS	
27550	16K 416-3	11.95
	200NS	
18650	16K 416-5	8.95
	300NS	

UART'S

Stock level	Part No.	Price
29000	AY5-1013A	4.95
9200	AY3-1015	5.95

1K CMOS RAM

Stock level	Part No.	Price
4400	5101	4.95
	450NS (Low Power)	

INTERFACE SUPPORT CIRCUITS

Stock level	Part No.	Price
1250	8212	1.98
1800	8214	4.95 3.95
11200	8216	1.98
1700	8224	2.75
2800	8226	1.98
1500	8228	4.75
1000	8238	4.75
4900	8251	5.95 4.95
500	8253	14.95
5200	8255	5.95
1100	8257	9.95
300	8259	14.95
1500	6810	3.95 3.50
1700	6820	4.95 3.95
1400	6821	4.95 3.95
2800	6850	5.95 4.95
700	6852	5.95 4.95



Z80-CPU	14.95	Z80-SIO/0	59.00
Z80A-CPU	24.95	Z80A-SIO/0	68.00
Z80-PIO	7.95	(common TX & RX clocks with DTRB)	
Z80A-PIO	11.95		
Z80-CTC	7.95	Z80-SIO/1	59.00
Z80A-CTC	11.95	Z80A-SIO/1	68.00
Z80-DMA	46.00	(separate TX & RX clocks without DTRB)	

P.O. BOX 1035 FRAMINGHAM, MASSACHUSETTS 01701



Active Electronic Sales Corp.

Over the counter sales, 12 Mercer Rd. Natick Mass 01760 Behind Zayres on Rte. 9 Telephone Orders & Enquires (617) 879-0077

IN CANADA 3 LOCATIONS

5651 FERRIER ST. MONTREAL, QUEBEC H4P 2K5 Tel: (514) 735-6425

4800 DUFFERIN ST. DOWNSVIEW, ONTARIO M3H 5S9 Tel: (416) 661-1115

BAKTER CENTRE 1050 BAKTER ROAD OTTAWA, ONTARIO K2C 3P2 Tel: (613) 820-9471

MINIMUM ORDER \$10.00 • ADD \$2.00 TO COVER POSTAGE & HANDLING • Canadian customers add 30% for exchange and handling. All federal and provincial taxes extra. Foreign customers please remit payment on an international bank draft or international postal money order in American dollars.



CIRCLE 37 ON FREE INFORMATION CARD

NAME brand test equipment. Up to 50% discount. Free catalog and price list. SALEN ELECTRONICS, P.O. Box 82, Skokie, IL 60076

PLANS & KITS

SCANNER users—build many useful accessories. Free kit catalog. **CAPRI ELECTRONICS**, Route 1R, Canon, GA 30520

CONSTRUCTION plans; over 100. From TV to telephone, from broadcasting to computers. Catalog air mailed \$1.00; includes year's subscription to Electronic Newsletter. **DON BRITTON ENTERPRISES**, PO Box G, Waikiki, HI 96815

HOBBYIST give your project the professional look. Printed circuit boards from your sketch or artwork. Affordable prices. Also fun kit projects. Rush free details. **DANOCINTHS**, Box 261, Westland, MI 48185

LINEAR AMPLIFIER: Ham only 2-30 MHz, 100 watt, solid-state. **FREQUENCY COUNTER:** 300 MHz, miniportable/mobile, memory! **VOX-COMPRESSOR:** Splatter-free modulation booster. Construction plans \$3.00 each. All \$7.50! Many others, catalog with order. **PANAXIS PRODUCTIONS**, Box 130-F11, Paradise, CA 95969

AMPLIFIER kits: Low TIM, Class A, BI-FET circuitry. Free 60-page manual. **MOONLIGHTER ELECTRONICS**, 117 Inverness, San Francisco, CA 94132

TESLA coil: simplified instructions, inexpensive parts easily obtained, plans \$3.00. **TOM ABRAMS**, 1359 Lakeland Drive, North Charleston, SC 29406

PROJECTION TV . . . Convert your TV to project 7-foot picture. Results equal to \$2,500 projector. Total cost less than \$20.00. Plans & lens \$16.00. Illustrated information free. **MACROCOMM**, Washington Crossing, PA 18977

GOVERNMENT SURPLUS

JEeps — \$59.30! — Cars — \$33.50! — 200,000 items! Government surplus—most comprehensive directory available tells how, where to buy—your area—\$2.00—moneyback guarantee—**GOVERNMENT INFORMATION SERVICES**, Department VA—10, Box 99249, San Francisco, CA 94109

BIORHYTHMS

PERSONALIZED biorhythms. Three month print-out only \$1.00, send birthdate. **BRIAN PETERSON**, Box 231, Northfield, MN 55057

BUSINESS OPPORTUNITIES

HIGHLY PROFITABLE ONE-MAN ELECTRONIC FACTORY

Investment unnecessary, knowledge not required, sales handled by professionals. Ideal home business. Write today for facts! **Postcard will do. Barta-RE-K, Box 248, Walnut Creek, CA 94597.**

MECHANICALLY inclined individuals desiring ownership of Small Electronics Manufacturing Business—without investment. Write: **BUSINESSSES**, 92-R, Brighton 11th, Brooklyn, NY 11235

MECHANICALLY INCLINED INDIVIDUALS —WANTED—

Assemble electronic devices in your home. Get started in spare time. Experience, Knowledge or Investment Not Necessary. Expect big profits: \$300 - \$600/Wk. Possible. Write for free literature telling how.

ELECTRONIC DEVELOPMENT LAB
Box 1535R, Pinellas Park, FL 33565



Delta Is Ready With The World's Best Bargains!

MOTION DETECTOR

When there is a new development in electronics, it takes some time before that development is available to hobbyists and experimenters, especially at surplus prices. This time we have reversed the trend, and announce a DELTA EXCLUSIVE: the DELTA MOTION DETECTOR. This device detects any motion or movement for a minimum distance of 4 ft. The secret is in the ultra-complex custom LSI chip, which combines the latest in linear & digital circuitry. The device is completely self-contained, in a case 6 x 3 x 2 1/4", and operates from four "AA" NiCad batteries. Nothing else is needed, for the device to perform its basic function, motion detection. When motion or movement is detected, a "whoop" alarm is sounded. The MOTION DETECTOR is designed to provide either an audible or silent alarm. The silent alarm is controlled by a timer, which delays the alarm up to 30 seconds. The silent alarm activates a relay, whose contacts are brought out to plug, and will activate ANY device, such as siren, horn, tape-recorder, telephone dialer, etc.

W-H-O-O-P!!
W-H-O-O-P!!
W-H-O-O-P!!

\$24.50

STEP UP/STEP DOWN ISOLATION TRANSFORMER

Hard-to-find step up or down isolation transformer. It will take either 208 or 230 volts, and give an output of 115 volts, or it will take an input of 115 volts and give an output of either 208 or 230 volts. Rating is 800 VA. **CRAMER** catalog shows a STANCOR with 500 VA rating for \$84.19. Wt. 23 lbs. **6592R** \$24.50 ea. (2 for \$47)

GOLD PLATED WIRE WRAP PROTOTYPE BOARDS

Wire wrap boards for prototyping or small run permanent work have been very expensive, with some boards running in excess of \$2000 for some of the medium size boards. We have come up with a fantastic board, that brings this highly desirable device within the price range of the hobbyist user. The board we have is 7 1/2" x 4 1/2" (four 24-pin LSI sockets). The LSI sockets are dual purpose, so that if not used, they may be used for 14 or 16 pin IC's. All the wire wrap pins are brought out to the top of the board, for simplicity in wire wrapping. The board has a ground plane, and a Vec plane, with pins from each plane at every socket. There are 50 gold plated contacts on each side of the board, for use with standard edge connector. The board is in 100% fiberglass, and each component is sealed in protective plastic. We just can't say enough about this board. **6592R** \$19.95 (2 for \$47)

FERRO RESONANT TRANSFORMER

Has 12V 4 amp winding & 26V CT @ 15A. For battery chargers, computers, lab power supplies, battery chargers. Brand new; designed for computer buffs. Complete with 6 mfd capacitor. Wt. 25 lbs. **6835R** \$24.95

VIDEO CUBE TV INTER FACE

The VIDEOCUBE is an RF Oscillator Modulator, which can take as its input a composite video signal, such as the output of a TV game, video camera, or video output of a micro or mini computer, and present it to the antenna terminals of a conventional h & w or color TV set, and displaying the information as if it was a monitor. The VIDEOCUBE comes with a 300 ohm output, and a selector switch for switching between TV and Videocube. Videocube: 5 to 12 VDC and draws about 10 mA. Meets all FCC requirements for this type of device, and is so certified. "Complete kit" contains all parts necessary to make an operating Videocube, which includes the p.c. board, the shield, the special switch, special capacitors, coils and inductance transformer, plus all resistors, capacitors and diodes. The "partial kit" contains all the hard-to-get parts, and you use your own resistors, capacitors & diodes, the kit comes with complete instructions, circuit diagram and assembly drawings, plus a reprint of the article by GLEN DASH, entitled, "THE VERSATILE VIDEOCUBE", appearing in Aug. Radio Electronics. **5500 Complete Kit of parts** \$13.95 (2 for \$26) **5500 Partial Kit of parts** \$11.95 (2 for \$22)

AMPEX TAPE

We have acquired an inventory of AMPEX 10 mil recording tape. These tapes have been used one time by government weather stations, and then we get them. On standard 7" AMPEX reel. **5588R** \$1.75 (4 for \$6)

SERIES SN74XX BENT PIN SPECIAL

Delta has a lot of SERIES SN74XX ICs, plus a few linears, which were removed from wire wrap boards. Included are just about every SN74XX in the book, plus op amps, phase locked loops, etc., and others found in a sophisticated computer system. Only defect is pins bent when removed from board. We are selling these in lots of 125 which will include a good cross-section of the mixture. Money back guarantee if not 100% satisfied. No choices at this price, but you will get a good working supply of these useful devices. **5491R 125-pc. set, SN74XX & linears** (3 for \$25)

Limited Quantities! 5V 75 AMP REGULATED POWER SUPPLY

By POWERTEC—worth over \$200. Can run a complete computer system! 16 x 15 x 4". Wt. 35 lbs. **5642R** \$89

FREE CATALOG



DELTA

ELECTRONICS
P.O. BOX 2, DEPT. 11R
7 OAKLAND ST.,
AMESBURY, MASS.
01913



When in our area, North-eastern Massachusetts or Southern New Hampshire, visit our new showroom, loaded with many desirable items that never get in the catalog or ads due to a limited quantity.

Atlanta, Georgia
DELTA ELECTRONIC HOBBIES
5151 BUFORD HWY, DORAVILLE, ATLANTA, GA.

Please enclose sufficient postage. Excess refunded.

Send for new catalog 19—120 pages of computer & electronic bargains... the best in the world!

CATCH-A-PULSE II LOGIC PROBE

10 Nsec SPEED AT 4 to 15V LEVELS



Compatible with DTL, TTL, CMOS, MOS, and Microprocessors using a 4 to 15V power supply. Thresholds automatically programmed. Automatic resetting memory. No adjustment required. Visual indication of logic levels, using LEDs to show high, low, bad level or open circuit logic and pulses. Highly sophisticated, shirt pocket portable (protective tip cap and removable coil cord). Eliminates need for heavy test equipment. A definite savings in time and money for engineer and technician.

ONLY \$44.95

- 10 Nsec pulse response
- Open circuit detection
- Replaceable tip & cord
- High input impedance
- Pulse stretching
- Multi-family

SPECIAL PAK-II \$51.95

Includes a standard coiled cord, coiled cord with micro hooks, adapter for using CATCH-A-PULSE on logic families whose power supply is 15V to 25V. Shipping add \$2.00 per probe.

AVR ELECTRONICS
Box 19299, San Diego CA 92119
(714) 447-1770

Radio Shack: No. 1 Parts Place

Low Prices and New Items Everyday!

Top-quality devices, fully functional, carefully inspected. Guaranteed to meet all specifications, both electrically and mechanically. All are made by well-known American manufacturers, and all have to pass manufacturer's quality control procedures. These are not rejects, not fallouts, not seconds. In fact, there are none better on the market! Always count on Radio Shack for the finest quality electronic parts!

Linear ICs

By National Semiconductor and Motorola — first quality

Type	Cat. No.	ONLY
301CN	276-017	49¢
324N	276-1711	1.49
339N	276-1712	1.49
386CN	276-1731	99¢
555CN	276-1723	79¢
556CN	276-1728	1.39
566CN	276-1724	1.89
567CN	276-1721	1.99
723CN	276-1740	69¢
741CN	276-007	49¢
741H	276-010	49¢
3900N	276-1713	99¢
3909N	276-1705	99¢
3911H	276-1706	1.99
4556CN	276-039	79¢
75491	276-1701	99¢
75492	276-1702	99¢
7805	276-1770	1.29
7812	276-1771	1.29
7815	276-1772	1.29


Hand-Held 6-Digit Frequency Counter

• Counts from 100 Hz to 45 MHz **9995**
• kHz and MHz Decimals

A high quality "pocket" counter with accuracy of 3ppm at 25°C or less than 30 Hz at 10 MHz! Overload-protected 1-meg input. Sensitivity, 30 mV up to 30 MHz. Lead-zero blanking. Just 3x4 1/2". With mini-rod antenna, leads, case, instructions. Requires 9V alkaline battery. **22-351 99.95**



Wire Wrapping Accessories

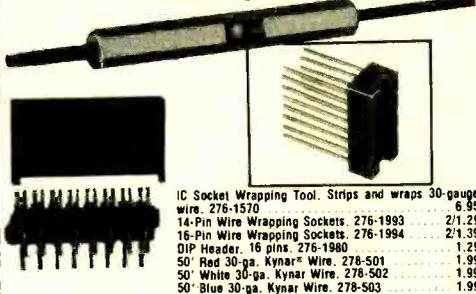

IC Socket Wrapping Tool. Strips and wraps 30-gauge wire. 276-1570 6.95
14-Pin Wire Wrapping Sockets. 276-1993 21.25
16-Pin Wire Wrapping Sockets. 276-1994 21.39
DIP Header, 16 pins. 276-1980 1.29
50' Red 30-ga. Kynar® Wire. 278-501 1.99
50' White 30-ga. Kynar Wire. 278-502 1.99
50' Blue 30-ga. Kynar Wire. 278-503 1.99

Computer Chip



8-Bit Data Bus, 16-Bit Address Bus
8080A Microprocessor. 100% prime CPU handles up to 65K bytes memory. **276-2510 12.95**

RAM Memory IC



Under 450 nS Access Time

2102 1K Static RAM. Low power version. 16-pin DIP. Buy 8 and save! **276-2501 2.49 Ea. or 8/14.95**

TTL and CMOS Logic ICs

Full-Spec Devices Direct from Motorola and National Semiconductor



Type	Cat. No.	ONLY
7400	276-1801	35¢
7402	276-1811	39¢
7404	276-1802	35¢
7406	276-1821	49¢
7410	276-1807	39¢
7413	276-1815	79¢
7420	276-1809	39¢
7427	276-1823	49¢
7432	276-1824	49¢
7441	276-1804	99¢
7447	276-1805	99¢
7448	276-1816	99¢
7451	276-1825	39¢
7473	276-1803	49¢
7474	276-1818	49¢
7475	276-1806	79¢
7476	276-1813	59¢
7485	276-1826	1.19
7486	276-1827	49¢
7490	276-1808	79¢
7492	276-1819	69¢
74123	276-1817	99¢
74145	276-1828	1.19
74150	276-1829	1.39
74154	276-1834	1.29
74192	276-1831	1.19
74193	276-1820	1.19
74194	276-1832	1.19
74196	276-1833	1.29
4001	276-2401	49¢
4011	276-2411	49¢
4013	276-2413	89¢
4017	276-2417	1.49
4020	276-2420	1.49
4027	276-2427	89¢
4049	276-2449	69¢
4050	276-2450	69¢
4511	276-2447	1.89
4518	276-2490	1.49

NEW IC Breadboard Sockets



Modular boards snap together and feature standard 0.3" center. Accepts 52 connections in 2 bus strips of 40 tie points each with 47 rows of 5 connected tie points. 2 1/2"x6". **276-174 9.95**

Ⓐ 550 connections in 2 bus strips of 40 tie points each with 23 rows of 5 connected tie points. 2 1/2"x3 3/4". **276-175 5.95**

Ⓑ Mini-Socket. 22 rows of 5 tie points each, plus 2 bus strips with 10 connections each. 2 1/2"x1 1/4". **276-176 3.95**

Low-Cost Power Transformers



• Primaries Designed to Operate from 120VAC, 60 Hz
• Solder Lugs for Easy Wiring or PC Board Mounting

Volts	Current	Cat. No.	Each	Volts	Current	Cat. No.	Each
6.3	1.2A	273-050	2.49	6.3 CT	3A	273-1510	3.99
6.3	300 mA	273-1384	1.99	12.6 CT	3A	273-1511	4.69
12	300 mA	273-1385	1.99	25.2 CT	2A	273-1512	4.99
24	300 mA	273-1386	2.49	12	5A	273-1513	8.95
24	1.2A	273-1480	2.99	18 CT*	4A	273-1514	8.95
12.6 CT	1.2A	273-1505	2.89	18 CT*	2A	273-1515	4.99

* Ideal for 5V (using CT) or 12V solid-state regulators

NEW 3-Amp 4PDT Relay



With Clear Protective Cover


Switch up to four different circuits! Contacts rated 3 amps at 125VAC. 12VDC coil, 160 ohms resistance. Solder terminals. Just 1 3/8"x1 1/2"x1 1/8". **275-214 4.99**

Radio Shack Reference Books



Digital Integrated Circuits. Complete specs. AC test circuits, waveforms. **62-1370 3.95**
Voltage Regulator Handbook. **62-1371 2.95**
Linear Integrated Circuits. Covers op-amps, voltage regulators, more. **62-1372 3.95**
Linear Applications. Fully indexed and cross-referenced. **62-1373 2.95**
Linear Applications, Vol. 2. The latest data sheets, applications. **62-1374 2.95**

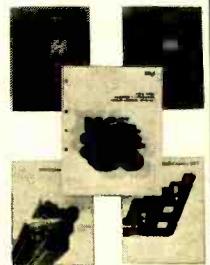CMOS Integrated Circuits. Covers 74C series, CD4000 with data specs. **62-1375 3.95**
Memory Data Book. **62-1376 3.95**
Intel® 8080/8085 Programming Manual. Uses Intel's assembly language. **62-1377 3.95**
Intel Memory Design Handbook. Companion to Data Catalog, below. **62-1378 3.95**
Intel Data Catalog. 928 pages of complete specs on most Intel standard devices. **62-1379 4.95**



Paddle Switches



NEW

Rated 6 Amps at 125VAC

Mounts in 3/4" round hole—no need to cut square opening.
SPST Black. 275-641 1.69
SPST Red. 275-642 1.89
DPDT Black. 275-643 2.19

Lighted DPDT Pushbutton Switch




NEW

Push-on/push-off switch rated 4A at 12VDC. Button glows red in "on" position. Mounts in 1/16" hole. U.L. listed. **275-675 4.69**


8-Rocker DIP Switch

Standard .100x.300" DIP

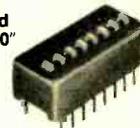

Designed for easy change of preset logic states in digital circuits. Fits 16-pin IC socket or mounts on PC board. **275-1301 1.99**

Epoxy-Glass Plug-In PC Boards

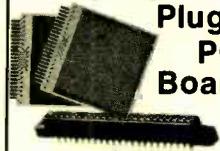

For 22-pin connectors. 4 1/2"x4 1/16" grid. 3 styles available.
Standard. 276-155 4.49
Digital. 276-156 4.49
Op-Amp. 276-157 4.49
22-Pin Dual Connector. 276-1551 2.99

WHY WAIT FOR MAIL ORDER DELIVERY?
IN STOCK NOW AT OUR STORE NEAR YOU!

Radio Shack®

A DIVISION OF TANDY CORPORATION • FORT WORTH, TEXAS 76102
OVER 7000 LOCATIONS IN NINE COUNTRIES

Prices may vary at individual stores and dealers

CABLE FM station. No experience required, excellent spare-time income, others operate for you. Details free. **BROADCASTING**, Box 130-F11, Paradise, CA 95969

WANTED: Manual for model MC-930 TV camera by Javelin Electronics. **DAN OGLE**, Box 84, Council, ID 83612

EDUCATION & INSTRUCTION

GRANTHAM's FCC License Study Guide—377 pages, 1465 questions with answers/discussions—covering third, second, first radiotelephone examinations. \$13.45 postpaid. **GSE PUBLICATIONS**, 2000 Stoner, Los Angeles, CA 90025

UNIVERSITY degrees by mail! Bachelors, Masters, Ph.D's . . . Free revealing details. **COUNSELLING**, Box 317-RE11, Tustin, CA 92680

F.C.C. EXAM MANUAL

PASS FCC EXAMS! Memorize, study—Tests—Answers for FCC 1st and 2nd class Radiotelephone licenses. Newly revised multiple choice questions and diagrams cover all areas tested in FCC exams, plus Self-Study Ability Test. \$9.95 postpaid. Money-back guarantee.


COMMAND PRODUCTIONS
RADIO ENGINEERING DIV

P.O. Box 26348 E
SAN FRANCISCO, CAL. 94126

TELEPHONE bugged? Don't be Watergated! Countermeasures brochure \$1.00. **NEGEYE LABORATORIES**, Box 547-RE, Pennsboro, WV 26415

Have regular medical check-ups.

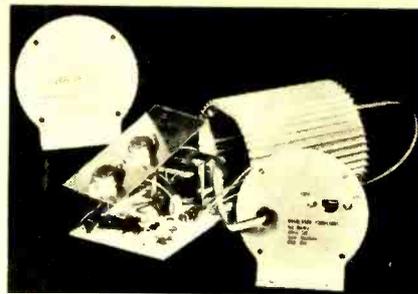American Heart Association
We're Fighting For Your Life



FROM KIT TO CAR IN 80 MINUTES!

Electronic ignition is "in." Update your car with the TOPS in power, efficiency and reliability — the TIGER SST capacitive discharge ignition (CD).

The TIGER delivers everything other CD's promise — and more: quicker starting, more power, more gas mileage, tune-ups eliminated, lifetime plugs and points, reduced repairs and pollution.

The TIGER can be built and installed in your car in 80 minutes. The TIGER is unique!

The TIGER comes with a switch for TIGER or standard ignition for 12V negative ground only.

Simpli-Kit \$21.95
POST PAID U.S.A.

WE ACCEPT:
Mastercharge or BankAmericard.
Send check or money order with order to:

Tri-Star Corporation

DEPT. FF, P.O. Box 1727
Grand Junction, Colorado 81501

CIRCLE 28 ON FREE INFORMATION CARD

YOU'RE UNDER SURVEILLANCE!!

A HOST OF PEOPLE, AGENCIES, AND COMPUTERS
ARE BUSY SPYING ON YOU AND YOUR BUSINESS
EVERY DAY, OFTEN ILLEGALLY. . . .

HOW TO STOP IT OR DO IT BACK!

THE BIG BROTHER GAME



A Large Format (8 1/2" x 11") Quality Paperback, 240 Pages

\$9.95

**BUGGING
WIRETAPPING
TAILING
OPTICAL AND
ELECTRONIC SURVEILLANCE
SURREPTITIOUS ENTRY
DETECTIVE TECHNIQUES
WEAPONS
COUNTERMEASURES**

"A VIRTUAL ENCYCLOPEDIA ON SURVEILLANCE
. . . EVERYTHING YOU'VE ALWAYS WANTED TO
KNOW ABOUT SPYING." —

PLAYBOY MAGAZINE

With Each Order You Receive Free Other Material And Literature
For Investigative Procedure \$9.95
Anarchist Cookbook \$9.95
CIA Improved Munitions Black Book \$9.95

QUIMTRONIX
Postpaid—P.O. Box 548-RE
Seattle, Washington 98111

CIRCLE 34 ON FREE INFORMATION CARD

Why is this the LARGEST SELLING low cost COUNTER KIT?

This counter is such a great seller because people like you have found that, feature for feature, the CT-50 gives you more for your money. Advanced LSI and CMOS circuitry has; lowered power consumption, increased performance, and reduced cost. Complete push button operation makes using the CT-50 a snap, and automatic decimal point positioning gives you quick, reliable readings. Battery operation is also possible because the CT-50 runs equally as well on 120VAC as it does on 110VAC. For ultra-accuracy we offer the CB-1 color burst adapter, it locks the CT-50's internal crystal to the television networks color standard for .001 ppm accuracy! Why sacrifice performance by using another counter when you can get professional quality at the unheard of price of **\$89.95**? Order yours today!



SPECIFICATIONS
Sensitivity: less than 10 mv.
Frequency range: 5 Hz to 60 MHz, typically 65 MHz
Gate time: 1 second, 1/10 second, with automatic decimal point positioning on both direct and prescale
Display: 8 digit red LED, 4" height
Accuracy: 2 ppm, internal TCXO standard
Input: BNC, 1 megohm direct, 50 Ohm with prescale, option
Power: 110 V ac 5 Watts or 12 V dc @ 300 400 ma
Size: Approx. 6" x 4" x 2", high quality aluminum case

CT 50, 60 MHz Counter Kit \$89.95
CT-50 wt 60 MHz Counter Wired & Tested \$159.95
CT-600, 600 MHz prescaler option for CT-50, add \$29.95

MINI-KITS

FM WIRELESS MIKE KIT
Transmit up to 300' to any FM broadcast radio, uses any type of mike. Runs on 3 to 9V. Type FM-2 has added super-sensitive mike preamp.
FM-1 \$2.95 FM-2 \$4.95

SUPER-SLEUTH AMPLIFIER
A super-sensitive amplifier which will pick up a pin drop at 15 feet! Great for monitoring baby's room or a general purpose test amplifier. Full 2 watts of output, runs on 6 to 12 volts, uses any type of mike. Requires 8-45 ohm speaker.
Complete Kit, BN-9 \$4.95

COLOR ORGAN/MUSIC LIGHTS
See music come alive! 3 different lights flicker with music or voice. One light for lows, one for the mid-range and one for the highs. Each channel individually adjustable, and drives up to 300 watts. Great for parties, band music, nite clubs and more.
Complete Kit, ML-1 \$7.95

TOPE DECODER KIT
A complete tone decoder on a single PC Board. Features: 400-5000 Hz adjustable frequency range, voltage regulation, 567 IC. Useful for touch-tone decoding, tone burst detection, FSK demod, signaling, and many other uses. Use 7 for 12 button touchtone decoding. Runs on 5 to 12 volts.
Complete Kit, TD-1 \$4.95

LED BLINKY KIT
A great attention getter which alternately flashes 2 Jumbo LEDs. Use for name badges, buttons, or warning type panel lights. Runs on 3 to 9 volts.
Complete Kit, BL-1 \$2.95

POWER SUPPLY KIT
Complete triple regulated power supply provides variable +15 volts at 200 mA and +5 volts at 1 Amp. 50 mV load regulation good filtering and small size. Kit less transformers. Requires 6-8V at 1 Amp and 18 to 30 VCT.
Complete Kit, PS-3LT \$6.95

SIREN KIT
Produces upward and downward wail characteristic of police siren. 5 watts audio output, runs on 3-9 volts, uses 8-45 ohm speaker.
Complete Kit, SM-3 \$2.95

VIDEO MODULATOR KIT
Converts any TV to video Monitor. Super stable tunable over Ch. 4-6. Runs on 5-15V, accepts std. video signal. Best unit on the market.
Complete Kit, VD-1 \$6.95

SIX DIGIT 12/24 HOUR CLOCK KIT

Here's a clock you can be proud of. The best looking, most complete kit on the market! Features include: time set push-buttons, jumbo, 4" readouts, and extruded aluminum case available in 5 colors. All parts included. Colors: gold, silver, bronze, black, blue (specify)



Clock Kit, DC-5 \$22.95 Alarm Clock, 12 Hr., DC-8 24.95
Mobile Clock, DC-7 25.95 Clock with HAM ID timer DC-10 25.95

Assembled and tested clocks available, add \$10.00 to Kit price.

600 MHz PRESCALER

Extend the range of your counter to 600 MHz. Works with all counters. Less than 150 mv sensitivity. Specify -10 or -100. Wired, tested,
PS-1 B \$59.95
Kit, PS-1 B \$44.95



CALENDAR ALARM CLOCK

Has every feature one could ever ask for. Kit includes everything except case, build it into wall, station or even car!

FEATURES:
• 6 Digits, 5" High LED • 12/24 Hour Format
• High Accuracy (1 minute/month)
• Calendar shows mo./day • Snooze button
• True 24 Hour Alarm • *7001 chip does all!
• Battery back-up with built-in on chip time base.

Complete Kit, less case
DC-9 \$34.95

TV TYPEWRITER KIT

A compact 5 x 10 inch PC card that requires only an ASCII keyboard and a TV set to become a complete interactive terminal for connection to your microprocessor asynchronous interface. Its many features are single 5-volt supply, crystal controlled sync and baud rates (up to 9600 baud), 2 pages of 32 characters by 16 lines, read to and from memory, computer and keyboard operated cursor and page ASCII display, block type, see thru cursor, keyboard/computer control backspaces, forward spaces, line feeds, rev. line feeds, home, returns cursor. Also clears page, clears to end of line, selects page 1 or 2, reads from or to memory. The card requires 5 volts at approx. 200 ma and outputs standard 15 ohm composite video.

TH3216 Kit \$149.50
TH3216, Assembled and Tested 239.95
VD 1 Video to RF Modulator Kit 6.95

ICs	LINEAR	REGULATOR	TRANSISTORS
5314 Clock \$2.95	555 \$5.50	78MG \$1.49	MRF-238 30W VHF \$11.95
7001 Clock 6.95	556 \$7.50	309K \$0.89	NPN 2N3904 type 10/\$1.00
5369 Cnos 7.95	566 \$1.49	309H \$0.99	PNP 2N3906 type 10/\$1.00
7447 \$5.67	567 \$1.49	340K-12 \$0.99	NPN Power Tab 40W 3/\$1.00
7473 \$.35	1458 \$0.50	7805 \$0.89	PNP Power Tab 40W 3/\$1.00
7475 \$.50	LED DRIVER 7812 \$0.89	FET MPF-102 type 3/\$2.00	
7490A \$.55	75491 \$0.78	UJT 2N2646 type 3/\$2.00	
74143 3.50	75492 \$0.50	2N3055 NPN Power 75	

ORDER BY PHONE OR MAIL
Satisfaction guaranteed or money refunded. Add 5% for shipping and insurance. C.O.D. add \$1.50. Orders under \$10.00, add \$1.75. NY residents add 7% sales tax. Minimum order \$6.00.

ramsey electronics

BOX 40728 ROCHESTER, NY 14610 (716) 271-6487

CIRCLE 42 ON FREE INFORMATION CARD

INTERNATIONAL ELECTRONICS UNLIMITED

LOW POWER SCHOTTKY - 74LS series
 Prime Motorola IC's Factory warranted
 Buy \$10.00 -any mix- deduct 10%
 Buy \$15.00 -any mix- deduct 10%

fall sale

LINEAR CIRCUITS
 All guaranteed functional
 Some items overmarked house numbers
 Buy \$10.00 -any mix- deduct 10%
 Buy \$15.00 -any mix- deduct 15%

74LS00	1.18	74LS54	1.18	74LS157	5.44	74LS251	5.66
74LS01	1.18	74LS55	1.18	74LS158	5.53	74LS252	6.66
74LS02	1.18	74LS56	1.18	74LS159	5.63	74LS253	6.66
74LS03	1.18	74LS57	1.18	74LS160	5.63	74LS254	6.66
74LS04	20	74LS58	71	74LS161	6.63	74LS255	4.4
74LS05	20	74LS59	30	74LS162	6.63	74LS256	6.66
74LS08	18	74LS60	42	74LS163	6.63	74LS257	6.66
74LS09	18	74LS61	43	74LS164	6.63	74LS258	6.66
74LS10	18	74LS62	43	74LS165	6.63	74LS259	6.66
74LS11	18	74LS63	74	74LS166	6.63	74LS260	6.66
74LS12	18	74LS64	74	74LS167	6.63	74LS261	6.66
74LS13	37	74LS65	74	74LS168	6.63	74LS262	6.66
74LS14	48	74LS66	74	74LS169	6.63	74LS263	6.66
74LS15	18	74LS67	74	74LS170	6.63	74LS264	6.66
74LS16	18	74LS68	74	74LS171	6.63	74LS265	6.66
74LS17	18	74LS69	74	74LS172	6.63	74LS266	6.66
74LS18	18	74LS70	74	74LS173	6.63	74LS267	6.66
74LS19	18	74LS71	74	74LS174	6.63	74LS268	6.66
74LS20	18	74LS72	74	74LS175	6.63	74LS269	6.66
74LS21	18	74LS73	74	74LS176	6.63	74LS270	6.66
74LS22	18	74LS74	74	74LS177	6.63	74LS271	6.66
74LS23	18	74LS75	74	74LS178	6.63	74LS272	6.66
74LS24	18	74LS76	74	74LS179	6.63	74LS273	6.66
74LS25	18	74LS77	74	74LS180	6.63	74LS274	6.66
74LS26	18	74LS78	74	74LS181	6.63	74LS275	6.66
74LS27	18	74LS79	74	74LS182	6.63	74LS276	6.66
74LS28	18	74LS80	74	74LS183	6.63	74LS277	6.66
74LS29	18	74LS81	74	74LS184	6.63	74LS278	6.66
74LS30	18	74LS82	74	74LS185	6.63	74LS279	6.66
74LS31	18	74LS83	74	74LS186	6.63	74LS280	6.66
74LS32	18	74LS84	74	74LS187	6.63	74LS281	6.66
74LS33	18	74LS85	74	74LS188	6.63	74LS282	6.66
74LS34	18	74LS86	74	74LS189	6.63	74LS283	6.66
74LS35	18	74LS87	74	74LS190	6.63	74LS284	6.66
74LS36	18	74LS88	74	74LS191	6.63	74LS285	6.66
74LS37	18	74LS89	74	74LS192	6.63	74LS286	6.66
74LS38	18	74LS90	74	74LS193	6.63	74LS287	6.66
74LS39	18	74LS91	74	74LS194	6.63	74LS288	6.66
74LS40	18	74LS92	74	74LS195	6.63	74LS289	6.66
74LS41	18	74LS93	74	74LS196	6.63	74LS290	6.66
74LS42	18	74LS94	74	74LS197	6.63	74LS291	6.66
74LS43	18	74LS95	74	74LS198	6.63	74LS292	6.66
74LS44	18	74LS96	74	74LS199	6.63	74LS293	6.66
74LS45	18	74LS97	74	74LS200	6.63	74LS294	6.66
74LS46	18	74LS98	74	74LS201	6.63	74LS295	6.66
74LS47	18	74LS99	74	74LS202	6.63	74LS296	6.66
74LS48	18	74LS100	74	74LS203	6.63	74LS297	6.66
74LS49	18	74LS101	74	74LS204	6.63	74LS298	6.66
74LS50	18	74LS102	74	74LS205	6.63	74LS299	6.66
74LS51	18	74LS103	74	74LS206	6.63	74LS300	6.66

TTL - 7400 - Full Spec
 Some items overmarked house numbers
 Buy \$10.00 -any mix- deduct 10%
 Buy \$15.00 -any mix- deduct 15%

LM300H	.49	LM340T (78XX)	LM566CN	1.19	ULN2208	.89
LM301CN	.20	5.6, 8, 12,	LM567CN	1.19	ULN2209	.89
LM302H	.45	15, 18, 24,	LM568CN	1.49	CA3046	1.19
LM304H	.80	LM370	LM703H	.59	CA3081H	1.49
LM305H	.45	LM372N	LM703CN	.39	CA3081H	1.49
LM307CN	.20	LM376CN	LM709H	.29	LM3900N	.35
LM307H	.30	LM377N	LM710N	.59	LM7524	.79
LM308H	.39	LM380N	LM711N	.35	LM7525	.79
LM309H	1.05	LM380-8CN	LM723N	.55	LM7535	.45
LM309K	1.05	LM381N	LM723N	.55	LM7535	.45
LM310CN	1.07	LM382N	LM733H	.59	75450AN	.35
LM311CN	.40	LM385K	LM739H	.65	75451CN	.25
LM311H	.50	LM386CN	LM741C(8)	.25	75452CN	.25
LM319N	1.13	LM387CN	LM741C(14)	.32	75453CN(351)	.25
LM320K	NE531V	1.90	LM741C	.35	75454CN	.35
5.5, 2, 12,	NE540L	1.90	LM747H	.79	75491N	.65
15	NE546A	1.09	LM747N	.65	75492N	.75
LM320T (79XX)	NE550A	.75	LM748CN	.25	XR202	1.19
5.1, 2, 15	LM555CN	.39	LM748CN	2.25	XR207	1.49
LM322N	LM556A	.85	LM1310N	1.29	XR2136	1.49
LM324N	LM5610N	2.95	LM1414N	.60	XR2567	1.49
LM339N	LM5620N	2.95	LM1456CN	1.29	XR4136	1.49
LM340K	LM5650N	.59	LM1496N	.89	XR4202	.69
5.6, 8, 12,	LM5654H	1.39	LM1800N	1.75	XR4212	.69
15, 18, 24,	LM5666H	1.39	LM1800N	1.75	XR4739	.69

CAPACITOR ASSORTMENT - All ±10%
 (10pf-820pf ceramic) .001uf-.47uf polyester)
 10pf/50V 82pf/50V 220pf/50V .001uf/100V .022uf/100V
 22pf/50V 82pf/50V 270pf/50V .0022uf/100V .047uf/100V
 33pf/50V 100pf/50V 470pf/50V .0033uf/100V .1uf/100V
 47pf/50V 150pf/50V 600pf/50V .0047uf/100V .2uf/100V
 56pf/50V 180pf/50V 820pf/50V .01uf/100V .47uf/100V
 100pf/50V .015uf/100V

TANTALUM CAPACITORS
 200µ solid dipped
 1-10 11-100 100-1000
 2.2u/35V 25 20 10u/16V 35 30
 .33u/35V 25 20 10u/20V 38 33
 1u/35V 25 20 15u/6.3V 38 33
 2.2u/20V 28 23 15u/20V 45 40
 2.2u/35V 30 25 22u/16V 45 40
 3.3u/35V 35 30 33u/10V 55 50
 4.7u/16V 30 25 47u/6V 55 50
 6.8u/6V 30 25 47u/20V 65 55
 6.8u/16V 30 25 56u/6V 75 65
 6.8u/50V 35 30 100u/20V 1.45
 cylindrical (axial)
 1-10 11-100
 .68u/15V 20 15
 15u/25V .40 .35

CERAMIC DISC CAPACITORS - 50V
 1pf 22pf 56pf 120pf 270pf 820pf .022uf .022uf
 5pf 27pf 68pf 180pf 470pf .001uf .030uf
 7pf 33pf 82pf 180pf 470pf .0047uf .050uf
 10pf 47pf 100pf 220pf 600pf .01uf .1uf
 1pf-.050u .1uf
 1-10 per value \$.10 \$.15
 11-100 .05 .08
 100-1000 .04 .08

CERAMIC CAPACITOR ASSORTMENT - 50V
 1pf 33pf 82pf 220pf 820pf .022uf
 5pf 27pf 68pf 180pf 470pf .001uf .030uf
 10pf 33pf 82pf 180pf 470pf .0047uf .050uf
 22pf 68pf 180pf 600pf .01uf .1uf
 10ea of above values.....\$11.95
 Supplied in steel cabinet with clear styrene drawers.....\$19.95
 Cabinet shipping chrg.....\$2.00
 (US & Canada).....\$2.00

TANTALUM CAPACITOR KIT
 solid dipped, 12 values, 5 each
 .1uf/35V 2.2/35 10/25 33/30 33/35
 33/35 4.7/16 15/20 55/50 55/50
 1/35 6.8/16 22/16 56/6
 capacitors only.....\$14.95

SUMMER CIRCUITS
 ELEKTOR 78
 Includes containing more than 100 circuits - such as high-perf. disc pre-amp, Audio control amp., LED level indicator, Car ammeter, Bibe speedometer, A/D converter and many more.
 with order \$3.00
 mag only 4.25

Carbon Film ± 5% 1/4 w or 1/2 w 15 ea. of 12 values:
 100, 220, 470, 1k, 1.5k, 3.3k, 4.7k, 6.8k, 10k, 33k, 100k, 1M.
 \$5.45

PRECISION RESISTOR PACKAGE
 Metal film, 1%, 1/4w, 50ppm
 240 resistors, 4 ea. from 10.5 - 464k
 \$27.95
 Supplied in steel cabinet with clear styrene drawers.....\$39.50
 Cabinet shipping chrg, US & Can. \$2.00

PRECISION RESISTOR PACKAGE
 Metal Film ± 1% 1/4 watt
 Starter kit - 2ea. 60 values
 120 Resistors 10.5 ohm-464k
 \$14.95
 Supplied in 15 Drawer 60 Comp. Cabinet - \$26.50 + \$2.00 Sh.


VECTOR BOARD - Phenolic
 169P44-062 (.1" spacing, .42" dia.)
 4-1/4" x 4-1/2" x .0625".....\$1.15 ea.

DL10A .27" Red CA LHD .79
 MAN66 .60" Red CA LHD 1.19
 DL338 2 Dig. 17" Red CC .29
 DL338 3 Dig. 17" Red CC .49
 NSN33 3 Dig. 17" Red CC .39
 MAN72 .30" Red CA LHD .59
 MAN74 .30" Red CC RHD .59
 NSN74R .30" Red CC RHD .59
 MAN82 .30" Yellow CA LHD .69
 OL302 .30" Red CC LHD .69
 HP7651 .5" Red CA RHD .79
 HP7653 .5" Red CC RHD .79
 HP3400 .8" Red CA LHD 1.25
 HP3405 .8" Red CC LHD 1.25
 MAN3620 .30" Orange CA LHD 7.99
 MAN3630 .30" Orange CA RHD 4.99
 MAN4610 .40" Orange CC RHD .59
 HP5082 5 dig. 11" mag. Red CC RHD .39
 HP5082 4 dig. 11" mag. Red CC RHD .39
 HP5082 5 dig. 11" mag. Red CC RHD .49

BEZELS - with red filters
 140-2 cut-out 1.125" x 2.375" max .062" panel thickness \$1.75
 140-4 cut-out 1.160" x 4.375" max .125" panel thickness \$2.75

MMS316 Clock Chip .95
 MMS370 Clock Chip 3.95
 MMS375AA Clock Chip 2.95

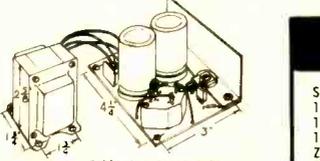POWER SUPPLY
 5 VOLT, 3 AMP - parts package



Includes following components:
 115/9V Transformer 2 - 3300uf/25V Caps.
 PC Board Diode Rectifier Terminal Block
 Power Transistor Heat sink Power cord
 V. Regulator Power cord
 Supplied with layout and schematic. \$22.95
 Shipping (US & Canada).....\$3.00

METAL FILM RESISTORS
 ± 1%, 1/4w, ± 50 PPM/OC
 Standard Decade Values 10.5 - 464k
 Qty. Ea. Min 10/value Min 100/value
 1-99 \$.20 \$.15
 100-999 .20 .10 \$9.00/100
 1000- 8.00/100

Carbon Film Resistors ± 5% 1/4w, 1/2w
 Qty. Ea. Min 10/value Min 100/value
 1-99 \$.10 \$.05
 100-999 .10 .04 \$3.00/100
 1000- 2.50/100

I C BREADBOARD
 Silver plated copper circuits holds 5 - 16 pin DIP IC's and interconnection holes. \$1.00

UNIVERSAL BREADBOARD
 Silver plated copper circuits fits any IC and related components. 2 triple rows of 27 holes for DIP. 3-3/16"x5-1/16" \$1.00

IC SPECIALS

LM311N, LM311CN Volt. comparator \$.29
 LM739N Dual hi perf op amp .59
 LM1414N Dual diff comp .49
 LM3900N Quad op amp .29
 XR4136N Op amp .79
 SL-5-4025 Dual 25bit shift reg. .50
 2510 Dual 100bit static shift register .50
 2511 Dual 200bit static shift register .65
 2513 64x8x5 Char gen upper case 3.95
 2513 64x8x5 Char gen lower case 3.95
 2516 64x6x8 Char gen ASC11 6.95
 F93410 256bit RAM bi-polar .95
 MAM82 256bit RAM tri-state 2.75
 745200 (82S16) 8 bit microprocessor 9.95
 LD110/111 set 3 1/2 digit A/D convert 17.95
 F7001 Calendar clock 4.95
 TR1602 UART 3.95

Silicon SW diode assorted 400 mw \$.05ea
 1N4148 (1N914) Silicon diode 400 mw .10
 1N3064 Silicon SW diode 400 mw .10
 1N4006 Silicon rect. diode 600V 400mw .10
 Zener diode 400 mw - 2.4V, 3.6V, 5.1V, 6.5V, 6.8V, 10V, 12V, 14.5V, 15V, 120V .15
 Germanium diode 400 mw .08

CERMET TRIMMER SPECIAL
 2ea of following values of Mecco 8014 - single turn
 500, 1k, 2k, 5k, 10k, 20k, 50k, 100k, 500k, 1M
 \$12.50

REGULATED POWER SUPPLY
 Plus & minus 5V 12V 15V

Uses 3 LM340T and 3 LM320T regulators, 115V/29V CT transformer plus PC board capacitors & diodes. All parts, schematic, instructions PS-29.....\$12.95 + \$1.00 Shppng.

COMPLETE SATISFACTION GUARANTEED. SHIPMENT TO US AND CANADA PREPAID UNLESS INDICATED OTHERWISE. OTHER COUNTRIES ADD 10% - EXCESS REFUNDED. ORDERS SHIPPED IN 3 WORKING DAYS FROM RECEIPT. MINIMUM ORDER \$10.00 CALIFORNIA RESIDENTS ADD SALES TAX. MINIMUM COD OR CHARGE ORDER \$15.00

IC SOCKETS
 Low Profile Solder Tail Wire Wrap
 8 pin \$16 24 pin \$.36 8 W pin .45
 14 pin .19 28 pin .44 14 pin .49
 16 pin .21 40 pin .61 16 pin .55
 18 pin .28

ELECTRONIC BUZZER
 Miniature, Solid State
 6V 15ma (4-9V oper.) \$1.29 ea.
 12V 15ma (8-20V oper.) \$1.29 ea.

CLOCK KIT - Mark I
 6 digit clock kit with one PC board. Accommodates MMS314 clock chip and 6 FND 359 displays contains all components except transformer. Includes 3 switches. Board has terminals for remote displays. \$10.95

BIMBOARD - BREADBOARD KIT
 Solderless breadboard section has 94 breadboard strips of 5 sockets each. 2 bus strips of 40 sockets each. Component bracket for switches lamp etc., accepts leads .01" to .035" diameter. \$11.95 ea.

TRIMPOT - Single Turn
 Mecco - Cermet 8014
 .5w, ± 100 PPM/OC ± 20%
 500 ohm, 2K, 10K, 20K, 50K, 100K, 500K, 1M.


1-9 10-99 100-999 1000-
 \$.75ea .69 .63 .57

TRIMPOT - 25 turn
 Bourns - Cermet 3299W
 PK Mount, vert. adj.
 2K, 10K, 20K
 1-9 10-999 100-
 \$1.65 1.50 1.35

FORDHAM BEST BUYS

HICKOK INSTRUMENTS

FREQUENCY COUNTERS

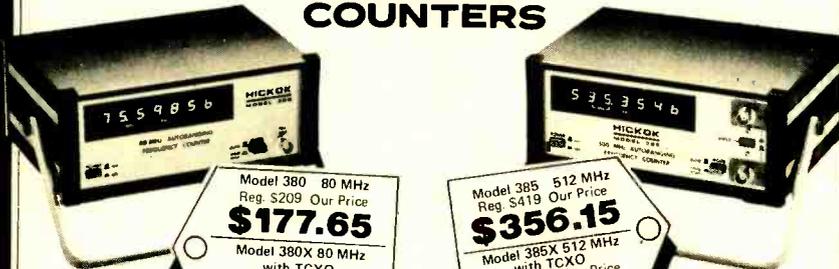

Model 380 80 MHz
Reg. \$209 Our Price
\$177.65
Model 380X 80 MHz
with TCXO
Reg. \$269 Our Price
\$228.65

Model 385 512 MHz
Reg. \$419 Our Price
\$356.15
Model 385X 512 MHz
with TCXO
Reg. \$499 Our Price
\$424.15

- 1 ppm TCXO time base on 380X/385X meets FCC regulations for most communications service.
- External time base input on 380/385.
- TCXO output on 380X, 385X will drive 4 other counters.
- Standard 10 ppm time base (380/385) meets FCC regulations for CB service.
- Built-in tilt stand/handle.
- Autodecimal in prescaled mode 385/385X • Display freeze (380/385).

SPECIFICATIONS:

380, 380X
Range: 1 Hz to 80MHz
Accuracy: ± 1 count ± time base uncertainty
Display: 7 LED digits, 3", auto decimal
Gate Times: autorangeing 1 sec., 0.1 sec., 1 sec. manual, 0.1 sec SPEED READ

Input
Impedance: 1MΩ, 25pF
Sensitivity: 100 mVrms from 1 Hz to 100 kHz increasing linearly to 25 mVrms from 1 MHz to 30 MHz decreasing linearly to 80 mVrms at 80 MHz

Time Base: 380, 385
Type: crystal oscillator
Frequency: 10 MHz
Stability: to ± 0.1 ppm
with line: 0.1 ppm for ± 10% line variation
with temp: 10 ppm from 0° C to 50° C
Aging Rate: 5 ppm/year
External Input: 1 MHz, 1 Vrms
Output:

385, 385X
Range: 1 Hz to 512 MHz
Accuracy: ± 1 count ± time base uncertainty
Display: 7 LED digits, 3", auto decimal
Gate Times: autorangeing 1 sec., 0.1 sec., 1 sec manual, 0.1 sec SPEED READ

Input
Impedance: 1 Hz to 80 MHz input: same as 380/380X
Sensitivity: 10 MHz to 512 MHz input: 50μV
25 mVrms 50 MHz to 100 MHz
50 mVrms to 300 MHz
100 mVrms to 400 MHz
300 mVrms to 512 MHz

Time Base: 380X, 385X
Type: temperature compensated crystal oscillator (TCXO)
Frequency: 10 MHz
Stability: to ± 0.1 ppm

0.1 ppm for ± 10% line variation
± 1 ppm from 0° C to 40° C
± 1 ppm/year

Buffered TCXO, 1 MHz, TTL level

General — ALL UNITS

Power: 105-125 Vac/210-250 vac. 50-400 Hz, 14 watts
Dimensions: 8-1/2" w X 4" h X 6" d (Not including handle)
Weight: 4 pounds

CB IN-LINE TESTER

- Seven-digit frequency — accurate to 10 ppm with 10 Hz resolution.
- Three-digit power output — two ranges — 10 watts or 100 watts with resolution to 0.1 watt.
- Four-digit SWR reading 1.00:1 to 20.00:1 — with exclusive "dynamic ratio" technique, one-step measurement — No Cal/Set required — continuously reads accurate SWR regardless of changing power level.
- Three digit % modulation readings 0% to 100% in 1% increments — also uses "dynamic ratio" technique — No Cal/Set required.
- Front panel counter input.
- External timebase input.
- TCXO timebase output (388X).
- AC or DC powered.



ALDELCO ELECTRONICS COMPANY

NEW IMPROVED DIGITAL ALARM CLOCK KIT
0.5 LED Display 12 hour format Snooze Feature Elapsed Timer Simulated Wood Grain or Black Leather Cabinet \$24.95
12 or 24 Hour Clock Kit. Similar to above but without Alarm or Timer features. Only \$23.95
Crystal Time Base Kit for 12 Volt DC use 4.95

DIGITAL MULTIMETER — THERMOMETER KIT 3 1/2 digit — 5 ranges on each. Functions: AC-DC. 2 to 2,000 Volts, 2 Micro Amps to 2 Amps, 2,000 Ohms to 2 Meg Ohms. Price \$49.95

VOLTAGE REGULATORS		CAPACITOR SPEC.
TO220 Package		25 for \$1.00
Positive	Negative	8pF 15pF 22pF
\$1.00	\$1.25	.01 20pF 47pF
7805	7905	.001 100pF 800pF
7806	7906	.01 Disc 30 volt 100 for \$3.50
7808	7912	500 for \$15.50
7812	7915	
7815	7918	
LM309H	\$1.10	
LM309K	1.10	
LM723	.55	

TURNER PTT Hand Mike
Model J360DM with 5 pin DIN. GOOD for Ham CB marine and aviation only \$10.95

Kit of parts for power supply
includes schematic
5 Volt, 6 Amp \$17.95
+15 and -15 2 Amp \$16.95

Special Electrolics
555 Timers 3MFD @12V 3/\$.25
3 for \$1.10
2200 MFD @16v 3/\$1.00

FETS 40673 1.55 We have transistors
MPF102 .55 Send stamp for catalog.

MA 1003 National Car Clock Module With 3 push button switches and filters \$19.95
New aluminum cabinet for MA 1003 \$6.95

MC14589 SPEC. Only .49
567 PLL \$1.10

Monsanto MV5053 Jumbo Red LED and LED Holder .25 each
Green, Yellow or Orange LEDs 5 for \$1.00

BRIDGE RECTIFIERS
2 Amp 200 Volt \$.50
2 Amp 400 Volt .95
3 Amp 200 Volt .85
25 Amp 200 Volt 2.50
25 Amp 400 Volt 4.00

FND 70 CC 0.3 Display LED .49
FND 500 CC 0.5 Display LED .89
FND 503 or FND 507 1.35
CLOCK FILTERS 2 1/2 x 5 1/2" Red, Blue, Green or Amber .60 ea

BLINKY-FLASHER-TIMER KIT
Includes 555, PC Board Parts & Instructions \$2.50

ACCUKEYER KIT. Uses TTL, includes IC's, sockets, Speaker, PC Board, instructions and all parts ONLY \$19.95
MEMORY KIT. Matches above & other accukeyer kits ONLY \$19.95


VARIABLE POWER SUPPLY KITS. 5 Amps 5-15 Volt DC \$6.95
add \$1.00 per kit shipping 5 Amps 12-28 Volt DC 6.95

Visit Our Store. Hours 9:00 AM to 6:00 PM Mon. to Fri. Sat. 9:00 AM to 2:00 P.M. Phone Orders accepted. Visa & Master Charge. ADD 5% FOR SHIPPING. ORDERS UNDER \$10.00 add \$1.00. Foreign Orders add 15% shipping (Except Canada & Mexico) send Certified Check or Money Order in USA funds.

ALDELCO

2281R BABYLON TURNPIKE, MERRICK, N.Y. 11566
(516) 378 4555

CIRCLE 33 ON FREE INFORMATION CARD

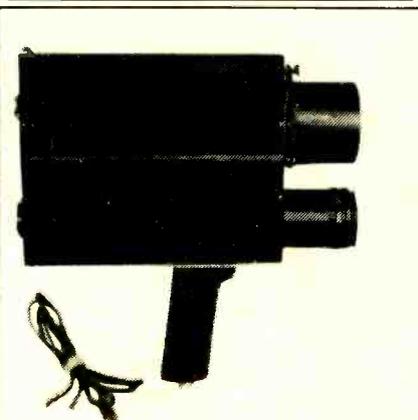

SEE IN THE DARK

IR viewer complete ready to operate. Guaranteed by the manufacturer. Portable, runs on lantern battery. New, see in total darkness. No shipments to Calif. Comes complete with built in IR source and adjustable focus lens. SPL-21 \$199.00

CHARACTER GENERATOR CHIP
Memory is 512X5 produces 64 five by seven ASCH characters. New by National, w/specs \$6.00

TOUCHTONE ENCODER CHIP
Compatible w/Bell system. Ideal for repeater work. W/specs \$6.00

HAWKEYE RADAR SPEED TRAP alarm
Plugs into cigar lighter outlet \$30

12 VOLT DC POWER SUPPLY 2 1/2 amps.
Runs CB's, tape decks in house. New in metal cabinet. \$14

customer pays all postage
MESHNA, PO BOX 62, E. Lynn Ma 01904

CIRCLE 39 ON FREE INFORMATION CARD

Immediate Delivery. . . To Place Your Order

Call TOLL FREE (800) 645-9518

N.Y. State call (516) 752-0050

FORDHAM RADIO SUPPLY CO. INC.
855R Conklin St.
Farmingdale, N.Y. 11735

YOUR ONE STOP DISCOUNT CENTER

Send for new 1978 catalog of over 3,000 items. 164 pages of test equipment. CB, tools, tubes, components and electronic supplies.


Mastercharge, BankAmericard, VISA and COD's accepted
ADD \$1.00 TO COVER SHIPPING, HANDLING & INSURANCE N.Y. Res. add 4.00% Sales Tax

FREE

CIRCLE 73 ON FREE INFORMATION CARD

30 MHz LOW COST FREQUENCY COUNTER KIT

- Features:**
- Frequency Range—100Hz to 30MHz min., resolution 100 Hz
 - All TTL Circuitry—No tears in the eyes when replacing ICs
 - FET Input Stage—Offers high input impedance
 - High Sensitivity—15mV typical
 - X'tal Time Base—0.001% 10MHz for better accuracy
 - On Board Regulator—No external power supply needed
 - All ICs Socketed—Easy to service
 - Easy to Operate—NO switches to flip
 - Tin Plated & Screamed Board—For easy assembly

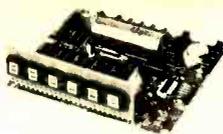

COMPARE and SAVE!
\$54.95

KIT # T-250-30A

KIT INCLUDES: Detailed Instructions (22 pages). All parts including transformer (case not available).

Plastic Molded Instrument Case

H—2 1/16" 3 1/16" W—8 3/4" D—9 1/4"
Adjustable heights to accommodate most needs. Available in tan & gray.
Model #CH-200 \$19.50



Instrument Case for Kit

H—2 1/16" W—6 1/16" D—6 1/4"
Ideal for many smaller projects
Similar to CH-200 less handle.
CM-6-225 \$9.40

6-DIGIT AUTO CLOCK KIT WITH ALARM

Features:
A. Fairchild 0.5" FND 500 Series Display
B. Display Board may be removed
C. X'tal time base
D. P.C. Boards, speaker, IC's and all parts.
E. Detailed Instructions
\$19.95
KIT # T-130Z

I.C. SOCKETS

	Lo-pro			Wire Wrap		
	5 pcs	10 pcs	100 pcs	5 pcs	10 pcs	100 pcs
8-pin	0.80	1.50	12.00	1.90	3.50	32.00
14-pin	0.95	1.75	15.00	2.10	3.90	36.00
16-pin	1.05	2.00	17.00	2.50	4.20	39.00
18-pin	1.40	2.50	23.00	3.20	6.00	55.00
20-pin	1.60	3.10	28.00	3.50	6.50	60.00
22-pin	1.80	3.40	32.00	3.75	7.00	65.00
24-pin	1.85	3.50	33.00	4.25	8.00	75.00
28-pin	2.20	4.20	39.00	4.75	9.00	85.00
40-pin	3.50	6.20	59.00	6.50	12.00	100.00

HAMMOND BREADBOARD KIT

BIMBOARD 1 \$9.95 ea.
Accepts DIP packages without adaptors or damaging component leads.
Contacts are double sided, nickel silver, current carrying capacity of 1 Amp with less than 10 milliohms contact resistance.
Total of 550 sockets (identified by a letter and number matrix for recording experiments)
Buss strip section runs up each side of board.
Component bracket (included with each board) will fit on any of the four edges or down the center.

FULLY ENCODED 74-key keyboard

manufactured by Micro Switch for Honeywell (Limited Qty) \$50.00 ea.

FREQUENCY COUNTER

LSI CHIPS
1CM7207 \$ 8.25
1CM7207 \$16.95
6.5536 MHz X'tal \$ 4.25
SAVE MORE BUY THEM ALL FOR \$28.00

STOP WATCH CHIP

1CM7205 \$18.50
3.2768 MHz X'tal \$ 4.75
Trimmer Cap \$ 0.50
ALL FDR JUST \$21.50

TRANSISTORS

Part No.	Power	Price
NPN Gen. Pur. 30V	10/51/100	
PNP Gen. Pur. 30V	10/51/10	
2N5458 Gen. Pur. FET	10/51/10	
2N5245 R F FET	10/55/100	
2N2222 Switching	10/51/75	
2N3055 150W Power	10/56/100	

POWER TRANSISTORS

Part No.	Power	Price
2N5062 0.8A 100V	30	
2N5064 0.8A 200V	45	
TIC 106B 5A 200V	45	
TIC 106D 5A 400V	55	
TIC 116A 8A 100V	1.00	
TIC 116B 8A 200V	1.20	
TIC 116D 8A 400V	1.50	
TIC 116E 8A 500V	1.80	
TIC 116F 8A 600V	2.10	
TIC 126A 12A 100V	1.35	
TIC 126B 12A 200V	1.50	
TIC 126D 12A 400V	1.90	
TIC 126E 12A 500V	2.25	
TIC 126F 12A 600V	2.55	

MINIATURE SLIDE SWITCH

DPDT 20 each
10 for \$1.75
100 for \$15.00

MINIATURE TOGGLE SWITCH

SPDT \$1.30 ea
DPDT \$1.50 ea

BIMBOARD 2 \$23.95

2 BIMboards and 2 component brackets
1 Aluminum base with 4 insulated Terminals

BIMBOARD 3 \$34.95

3 BIMboards and 3 component brackets
1 Aluminum base with 4 insulated terminals

BIMBOARD 4 \$43.

4 BIMboards and 4 component brackets
1 Aluminum base with 4 insulated terminals



0.2" L.E.D. Lamps

Color	20x	100/15.00
Red	20x	100/15.00
Green	20x	100/15.00
Yellow	20x	100/15.00
Amber	20x	100/15.00

L.E.D. Displays

Part No.	Price
END 503 C.C. 0.5"	75¢
END 510 C.A. 0.5"	75¢
1720R C.A. 1"	4.75
1723R C.C. 1"	4.75

JUMBO LED READOUT ARRAY

- 1.00 Inch High Characters
 - Common Cathode Connections
 - 3 1/2 Digits with Colons
 - Independent Segments
- LT1012 \$7.50

SOLDER

Quick solder remover
1/32" 5 ft.
1/16" 5
1/8" 5 1.40 ea.
1/4" 2 1/2

TANTALUM CAP AXIAL LEADS

Value	Price
1 10V 15¢	
1 35V 20¢	
3 35V 25¢	
10 50V 30¢	
22 35V 30¢	

DIP PLUGS

Pin Count	Price
5 pcs 10 pcs 100 pcs	
14-pin 3.25 6.00 55.00	
16-pin 3.50 6.50 60.00	
40-pin 9.50 18.00 150.00	

DIP TANTALUM

Value	Price
10u 20V	35¢
22u 15V	50¢
33u 15V	65¢
68u 10V	80¢
100u 10V	99¢

AUDIBLE TRANSDUCERS

Manufactured by "GULION INDUSTRIES" for producing audible sound. With a very simple one X'tal cut. Ideal for smoke detector & mouse code practice. \$1.75 ea. 10/51/14.00

TIME BASE MINI KIT

Includes MM5369 1.C.
3.5795 MHz X'tal
Trimmer Cap.
\$3.45

Wire Wrap Wire

Special Purchase
500 ft. roll @ 5.00
White only

WIRE-WRAP TOOLS

Hobby Wrap - 30
Hobby Wrap - BW-630
Battery UP. (less batt.)
\$30.95

ERIE MINI CERAMIC TRIMMER CAP.

Value	Price
10 - 40 p/F	10/\$4.50

SWITCHING DIODES IN4148

Value	Price
10 for 0.5u	
50 for 2.00	
100 for 3.50	

SPECIAL OF THE MONTH

AN214-4.5W Power IC with spec.	\$2.95 ea
MH0026-5MHz Clock Driver	\$1.95 ea
14-pin Lo-pro IC Socket	100/\$16.00
16-pin Lo-pro IC Socket	100/\$17.00
P.C. Mount X'tal. 24V 45A	\$1.95 ea
1,000uf 50V cap. Axial Lead	\$1.00 ea
C-60 Digital Cassette Tape	\$1.50 ea

MINIATURE CONSOLES

15" SLOPING PANELS


Panel	A	B	C	D	E	F
4.0 5.5 2.0 1.1 3.3 2.2 1-B	1-G	1-L	5.50	1-W	1-S	1-K
6.5 5.5 2.0 1.1 3.3 2.2 2-B	2-G	2-L	6.10	2-W	2-S	2-K
6.5 8.5 2.0 1.1 3.3 5.2 3-B	3-G	3-L	6.70	3-W	3-S	3-K
6.5 8.3 3.0 1.3 6.3 2.2 4-B	4-G	4-L	7.30	4-W	4-S	4-K
10.0 8.3 3.0 1.3 6.3 5.2 5-B	5-G	5-L	7.80	5-W	5-S	5-K
10.0 11.3 3.0 1.3 6.3 5.2 6-B	6-G	6-L	8.40	6-W	6-S	6-K
14.0 8.3 3.0 1.3 6.3 2.2 7-B	7-G	7-L	8.80	7-W	7-S	7-K
14.0 11.3 3.0 1.3 6.3 5.2 8-B	8-G	8-L	9.70	8-W	8-S	8-K

PANELS (tops)

Panel	A	B	C	D	E	F
4.0 5.5 3.0 1.1 3.7 2.2 9-B	9-G	9-L	5.50	9-W	9-S	9-K
6.5 5.5 3.0 1.1 3.7 2.2 10-B	10-G	10-L	6.10	10-W	10-S	10-K
6.5 7.2 4.0 1.1 5.7 2.2 11-B	11-G	11-L	6.70	11-W	11-S	11-K
10.0 5.5 3.0 1.1 3.7 2.2 12-B	12-G	12-L	7.30	12-W	12-S	12-K
10.0 7.2 4.0 1.1 5.7 2.2 13-B	13-G	13-L	7.80	13-W	13-S	13-K
10.0 10.2 4.0 1.1 5.7 2.2 14-B	14-G	14-L	8.40	14-W	14-S	14-K
14.0 7.2 4.0 1.1 5.7 2.2 15-B	15-G	15-L	8.80	15-W	15-S	15-K
14.0 10.2 4.0 1.1 5.7 2.2 16-B	16-G	16-L	9.70	16-W	16-S	16-K

30" SLOPING PANELS

Panel	A	B	C	D	E	F
4.0 5.5 3.0 1.1 3.7 2.2 9-B	9-G	9-L	5.50	9-W	9-S	9-K
6.5 5.5 3.0 1.1 3.7 2.2 10-B	10-G	10-L	6.10	10-W	10-S	10-K
6.5 7.2 4.0 1.1 5.7 2.2 11-B	11-G	11-L	6.70	11-W	11-S	11-K
10.0 5.5 3.0 1.1 3.7 2.2 12-B	12-G	12-L	7.30	12-W	12-S	12-K
10.0 7.2 4.0 1.1 5.7 2.2 13-B	13-G	13-L	7.80	13-W	13-S	13-K
10.0 10.2 4.0 1.1 5.7 2.2 14-B	14-G	14-L	8.40	14-W	14-S	14-K
14.0 7.2 4.0 1.1 5.7 2.2 15-B	15-G	15-L	8.80	15-W	15-S	15-K
14.0 10.2 4.0 1.1 5.7 2.2 16-B	16-G	16-L	9.70	16-W	16-S	16-K

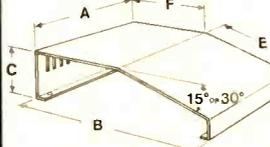

KEPCO Ferreroresant power supply.

Input 110V 3A
Output 24V 8A
Factory Price \$206
Our Price \$80

LAMBDA Precision Power Supply

Model LXS-EE-50V
5V 45A Factory Price \$600
Our Price \$100

THE KIM-1 MICROCOMPUTER SYSTEM

- 6502 - 8 bit MPU with powerful instruction set, 13 addressing modes, multiple interrupts, full 65K byte address range.
- 2 MCS 6530 chips each with 1024 bytes of ROM, 64K bytes of RAM, 15 I/O pins, and an interval timer.
- The Kim-1 monitor and operating programs are stored permanently in the 1048 ROM bytes provided.
- Comes with keyboard and alpha-numeric display.
- TTY and cassette interface
- Completely assembled and tested and documented.
- Including KIM-1 user manual, 6500 programming manual, and 6500 hardware manual.

ALL THESE FOR JUST \$235.00

TRINICO
2795-L West Lincoln Ave.
Anaheim, CA 92801
(714) 821-0234

Minimum order \$5.00. Please add \$2.00 postage and handling for out of States, \$1.00 inside California plus Tax. C.O.D. orders welcome (Min. Order \$20.00)

Store Hours 10 - 7, Mon. - Sat.
VISA MASTERCHARGE

KIM SUPPORT

6102	8.00
6502	11.95
6520	10.00
6522	9.25
6530	15.95
6530 002	15.95
6530 003	15.95
6530 004	15.95
6530 005	15.95

VHF Modulator

For TV Game or Computer
Modulates Video Input to RF output (ch. 3)
Supply voltage 5V
\$4.50 ea.

3815 5-DECADE COUNTER

The 3815 is a 5 Decade Counter which includes a memory with static latches for each counter digit and an output multiplexer. The 3815 is designed to drive a multiplexed display which has a Binary Coded Decimal output and five decoded outputs to strobe the display.
With Specification \$5.00 ea.

OUR BEST SELLER

5V 10A POWER SUPPLY KIT
Includes Extra large heat sink, power transistor, ICP regulator, P.C. board with OVP.
Kit, No T-500 \$14.95
With optional rectifiers and filtering cap. \$17.95

2-20V ADJ. POWER SUPPLY

KIT INCLUDES: Transformer, PC Board, Large heat sink, Large filtering capacitor and all parts with detailed instruction.
KIT # 1458 \$12.95

Car Battery Eliminator

KIT INCLUDES: Transformer, PC Board, Large heat sink, Large filtering capacitor
KIT#700 \$16.95

O.B.* 4 Digit Jumbo Display

Alarm Clock Kit
A. Fairchild 0.8" FSC8000 Display Array
B. Fairchild Super-Chip - F-3817PC
C. P.C. Board, Transformer, Speaker and all parts included (less case)
\$19.50
D. Detailed Instructions

Z-80 CPU BOARD/KIT

On board 2708 EPROM addressable to any 4K boundary above 32K. Power-on-jump to any 4K boundary above 32K, or the on board 2708. On board run-stop flip-flop and optional generation of Memory Write allow front panel-less operation.
BARE BOARD \$34.00
\$130.00 (2Mz) \$145.00 (4Mz)
ASSEMBLED & TESTED ADD \$50.00

8080 A CPU BOARD/KIT

With 8 level vector interrupt, CPU chip 8080 clock chip: 8224, crystal Freq: 18MHz, vector interrupt chip: 8214
BARE BOARD \$28.50 KIT \$95.00
Assembled and Tested \$145.00

REAL TIME CLOCK FOR S-100 BUSS

On board 1MHz Crystal Oscillator, two independent interrupts. 16 bit counter in 10 s steps, and decade steps from 100 s to 10 sec.
Kit #126 Assembled & Tested \$179.95
BARE BOARD \$24.00

8K STATIC RAM

Kit	450ns	350ns	250ns
-----	-------	-------	-------



NATIONAL EMERGENCY ALARM REPEATER
 UNIQUE DEVICE MADE FOR THE U.S. GOVERNMENT TO WARN OF NUCLEAR ATTACK. IT WAS TO BE PLUGGED INTO THE WALL OUTLET AND WAS TO SOUND OFF WHEN THE POWER COMPANY SWITCHED FROM 60 CYCLE TO 50 CYCLES. CONTAINS RELAY, TIMER/NOISE GENERATOR, RESISTORS, CAPACITORS, DIODE, REED SWITCH AND 50 CYCLE VIBRATING REED ALL IN AN ATTRACTIVE BLACK AND SILVER CASE. APPROX. SIZE: 3 7/8" x 3 2/8" x 2 1/4". AN EXPERIMENTOR'S DELIGHT! BRAND NEW IN BOXES. C22706 **\$3.95**

GE FAST CHARGE Nicad Pack
 CONTAINS 3 SERIES CONNECTED AA SIZE CELLS EACH RATED 1.2V AT 500MAH. CAN BE CUT APART OR USED AS A PACK. RECHARGE THESE IN AS LITTLE AS 3 HOURS! BRAND NEW. C23351 **\$2.95**

BISTABLE RELAY
 7 SEGMENT COMMON ANODE READOUT. CHARACTER HEIGHT .334". PRIME - SEALED PKG. 4 for **\$2.00**
SLA-1
 150 Watt Seconds STROBE TUBE C23443 **\$3.95**

PHOTOFLASH CAPS
 350 mf 330V 100
 720 mf 360V 150
 1600 mf 360V **\$2.25**
CALCULATOR BOARDS
 WITH DISPLAY LESS KEYBOARD AND CASE (AS IS) **\$1.50**

CARRYING CASE
 Small metal reflector with built-in horn. Also strobe tube requires 300VDC min. For electrodes. 2-4 KV for trigger. Excellent quality made for Honeywell. Approx size 1 1/2" x 1 1/2" x 1 1/2". C22864 **89¢**
STROBE TUBE & REFLECTOR ASSEMBLY
 Small metal reflector with built-in horn. Also strobe tube requires 300VDC min. For electrodes. 2-4 KV for trigger. Excellent quality made for Honeywell. Approx size 1 1/2" x 1 1/2" x 1 1/2". C22874 **\$2.25 ea**

2" ROUND Speaker
 C23068 **99¢**
V.O.X.
 Solid state Voice Operated Switch. Complete and assembled. With microphone. C21623 **99¢**
NONVIBRA
 PROJECTION LENSES 5" F/3.5 C23370 **\$3.95**

Crystal Oscillator 14.04 Mhz
 IC clock oscillator C22269 **\$1.98**
1003A SCR 200V 8 amp
 8 for **\$1.00**
GREEN NE2
 Same as NE2 but GREEN on 120V. 8 for **\$1.00**

LIMIT SWITCH
 MICRO-AMMETER
 LASER

MINIATURE 1 MF. 250V CAPACITOR
 SMALL SIZE. METAL CASE. LONG LEADS. 10 for **\$1**
LED PANEL MOUNTING KITS
 12 for **\$1** C22707
Hex Nuts
 Standard size hex nuts for pots, lamps. C22791 **\$0 for \$1**

Strobe Light Kit
 COMPLETE variable speed light kit. Contains all parts, including time cord, PC board and instructions. C22200 **\$7.50**
Electronic Warning Flasher Kit
 This battery operated device continuously flashes a series of intense light. Great safety device for bicycle riders, skiers, hikers, boat and campers. Comes complete of all electronic parts, quality glass-beep PC board & easy to understand instructions. Uses high output neon flash tube which flashes 1/2 second per second when batteries are fresh. Operates continuously for 12 hours on 2 alkaline "C" batteries. You need only to supply the batteries and, if needed, a 117VAC. C22307 **\$6.95**

STROBE TUBE ASST.
 Brand new factory prime strobe tubes. Assortment of 5 strobe tubes, w/ schematics. C23280 **\$3.00**
MINIATURE REFLECTOR
 Appx size: 1-7/16" L x 7/8" W x 3/4" D. C23227 **\$1.00**

AMAZING EARADIO
 THIS IS PROBABLY THE WORLD'S SMALLEST RADIO. IT WEIGHS ONLY 1/2 OUNCE AND IS WORN BEHIND THE EAR. CONTAINS AN IC AND SEVERAL DISCRETE DEVICES TO GIVE AN EQUIVALENT OF 12 TRANSISTORS. THE RADIO HAS A T.R.F. DESIGN OPERATING FROM 1 STANDARD SIZE 1.5V HEARING AID BATTERY (INCLUDED). IT PROVIDES GOOD VOLUME TO EARPHONE ON SEVERAL STATIONS IN METROPOLITAN AREAS. DOESN'T REQUIRE ANY ANTENNA, GROUND OR OTHER ADDITIONAL WIRES - FULLY SELF CONTAINED & TUNABLE. SIZE: 1 1/8" x 1 1/4" x 3/8". **\$5.95**

510V BATTERY
 EVEREADY No. 157 PHOTOGRAPHIC FLASH BATTERY PROVIDES 510V AND 180V. THESE ARE NEW UNITS IN THEIR ORIGINAL BOXES. C23459 **\$9.99**
WATER THIN COPPER CLAD GLASS EPOXY BOARD
 .035" 504 **\$1.50**
SOLID CARBIDE PC DRILL BITS
 .035" C21426 **\$1.50**
ULTRA MINIATURE ADJUSTABLE CAPACITOR
 3.5-11 PF 3 for **\$1.49**

100M PHOTOFLASH KIT
 SIMPLE TO ASSEMBLE KIT INCLUDES PRE-ASSEMBLED CIRCUIT BOARD, CAPACITOR, FLASH TUBE, REFLECTOR, SWITCH AND HOOKUP DIAGRAM. LESS CASE, BATTERY HOLDER, AND BATTERIES (OPERATES ON 2 AA CELLS). GUIDE #28 AT ASA 25. C23435 **\$2.95**

14" STROBE/MUTTER CORD
\$1

CHANEY electronics
 Minimum order \$5.00
 Please include \$1 for postage
 Visa, MC and COD accepted.
 Phone orders are welcome.

P.O. BOX 2703B, DENVER, CO. 80227 Ph: 303-781-5750

MULTI-TESTER

IT TESTS
TRANSISTORS AND LED'S
AS WELL!!

YX-360TR
TRANSISTOR TESTER
20K OHMS/VOLT



\$28.50

SPECIFICATIONS
 DCV 0.0 1.0 5.25 10 50 250 1000 120k Ω /V
 VI: 3% 25k (w/10V probe)
 DCA 0.50uA 0.25 2.5mA 0.0 25A (100mV & 250mV) 1.3%
 ACV 0.10 50 250 1000 (8k Ω /V) 1.4%
 Freq: 30Hz to 30kHz
 I: 1 x 10 1k x 10k (max. 20mA)
 Batt: 1.5V x 2 & 9V x 1
 dB -10 to +62
 ICEO 0.150uA 0.15 150mA -5%
 hFE 0.1000 1.3% (w/connector)
 150. 100.57 420p

SANYO HYBRID

Audio power amplifiers I.C.
Max. hi-fi output power, minimum ext. components needed.



15 Watts	STK-28	\$ 8.50
23 Watts	STK-054	\$13.50
30 Watts	STK-056	\$17.50
50 Watts	STK-050	\$26.50
10W + 10W (stereo)	STK-040	\$14.50
15W + 15W (stereo)	STK-041	\$25.50
20W + 20W (stereo)	STK-043	\$31.50

*data sheet comes with purchase

THE MOST POPULAR MM5314 CLOCK KIT

Features:
 * 12/24 Hours Display
 * 50/60 Hz Input
 * 6 Digits Bright Orange Readouts



Kit includes plastic case, MM 5314 I.C. One set transistor drivers, P.C. Board, gas discharge displays, all other electronic parts and transformer. Catalog no. DC-8SP

**SPECIAL PRICE
\$16.95 PER KIT**

COMPUTER GRADE CAPACITORS

All capacitors are Brand New U.S. made in standard size

9000MFD 50V	\$3.25 EA.
11000MFD 35V	\$3.20 EA.
14500MFD 40V	\$3.40 EA.
23000MFD 20V	\$3.00 EA.
58000MFD 20V	\$3.20 EA.
100,000MFD 6V	\$2.50 EA.

9 STEPS LED LEVEL INDICATOR KIT



for most stereo amplifiers
 This new project works as a pair of VU meter to indicate the output level of your amplifier from -20dB to +3dB. Kit includes all LED, transistors, electronic components, P.C. Board and instructions.
 Easy to build and fun to see.
ONLY \$9.90 EA.


ULTRA-SONIC REMOTE CONTROL SWITCH KIT

NEW

Kit includes the transmitter, the receiver, ultra sonic transducers, P.L.L. I.C., all other electronic parts and P.C. Boards. Ideal for control TV, light, fan or garage door. Case not included.

\$18.50 PER KIT

60W + 60W STEREO AMPLIFIER

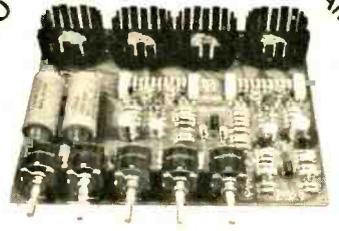

OCL pre amp. & power stereo amp. with bass, middle, treble 3-way tone control. Fully assembled and tested, ready to work. Total harmonic distortion less than 0.5% at full power. Output maximum is 60 watts per channel at 8 Ω . Power supply is 24 - 36V AC or DC. Complete unit

only **\$37.50 ea.**
\$7.50 ea.

Power transformer

DIP SWITCHES




(On-Off Contacts)

4 positions	\$1.50
5 positions	\$1.60
6 positions	\$1.70
7 positions	\$1.70
8 positions	\$1.80
10 positions	\$2.00

22W + 22W STEREO HYBRID AMPLIFIER KIT

It Works in 12V D.C. As Well! Kit includes 1 PC SANYO STK-024 stereo power amp. IC LM 1458 as pre amp, all other electronic parts, PC Board, all control pots and special heat sink for hybrid. Power transformer not included. It produces ultra hi-fi output up to 44 watts (22 watts per channel) yet gives out less than 0.1% total harmonic distortion between 100Mhz and 10KHz.

\$32.50 PER KIT

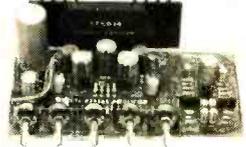

POWER TRANSFORMER \$6.50 EACH

SUPER 15 WATT AUDIO AMP KIT

Uses STK-015 Hybrid Power Amp

Kit Includes: STK-015 Hybrid IC, power supply with power transformer, front Amp with tone control, all electronic parts as well as PC Board. Less than 0.5% harmonic distortion at full power 1/2dB response from 20-100,000 Hz. This amplifier has QUASI-Complimentary class B output. Output max is watt (10 watt RMS) at 4Ω.

ONLY \$23.50 each



63 KEYS ASC11 DECODED COMPLETE KEYBOARD

by Honeywell
with dual color key tops, uses TMS 5000 decoder LSI. (Schematic data included)

SPECIAL \$56.50 NOT A KIT!



PROFESSIONAL CASE

for our 0-30V Power Supply. It is a nice looking metal cast case with giant 4" volt/amp meter; output blinding post and fuse holder, on/off switch and line cord!

ONLY \$21.50 EA.



CASE 030

FM WIRELESS MIC KIT



This new model FM wireless MIC kit uses 3 high freq. transistors, works in the FM range (88-108 MHz). It transmits the sound wave fidelity clearly over long distances (up to 250 ft.). Kit comes with all electronic parts, P.C. Board and mini microphone!


\$6.95 EACH KIT



WE FOUND THE CASE FOR THE FM MIC!
Small nice looking aluminum case size like a pack of cigarettes. It is an intercom. Audio amp inside with a mic jack, a mini toggle sw on top, can be used for many projects. We give you the circuit data as well!

VERY SPECIAL PRICE 2 for \$4.99

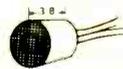Sub-Mini Size Condenser Microphone \$2.50 each



FET Transistor Built-in

FLUORESCENT LIGHT DRIVER KIT

12V DC POWERED

Lights up 8-15 Watt Fluorescent Light Tubes
Ideal for camper, outdoor



Auto or Boat
Kit includes high voltage coil, power transistor, heat sink, all other electronic parts and PC Board, light tube not included!

ONLY \$5.50 PER KIT

MANY SOUND DECISIONS!

Solid state sound indicator operating voltage 6V DC 30mA. Small size approximately 3/4" X 1 1/4".
Model EB2116 (Continuous)
Model EB2126 (Slow Pulse)
Model EB2136 (Fast Pulse)



\$3.60 EACH



Continuous



Slow pulse



Fast pulse

1Watt AUDIO AMP

All parts are pre assembled on a mini PC Board
Supply Voltage 6-9V D.C.
SPECIAL PRICE \$1.95 ea.



"FISHER" 30 WATT STEREO AMP

Kit includes 2 pcs. Fisher PA 301 Hybrid IC all electronic parts with PC Board, Power supply ± 16V DC (not included), Power band with (KF 1% ± 3dB). Voltage gain 33dB. 20Hz - 20KHz.
Super Buy Only \$18.50



5W AUDIO AMP KIT

2 LM 380 with Volume Control
Power Supply 6-18V DC
only \$5.00 ea.



TIMER KIT

Time Controlled from 1-100sec. Ideal to be used as timer delay unit for burglar alarm, photo service, and other purposes. Max. loading 110V, 2 AMP. Supply voltage 12-18V DC.
\$11.50 each



FT-90 ELECTRONIC IC TIMER

ELECTRONIC ALARM SIREN

COMPLETE UNIT
Ideal for use as an Alarm Unit or hookup to your car back up to make a reverse indicator.
Light Output up to 130dB
Voltage Supply 6-12V **\$7.50**



AU-999

SOUND ACTIVATED SWITCH

All parts completed on a PC Board
SCR will turn on relay, buzzer or trigger other circuit for 2-10 sec. (adjustable)
Ideal for use as door alarm, sound controlled toys and many other projects
Supply voltage 4.5V-9V D.C.
\$1.75 ea/2 for \$3.00



LINEAR SLIDE POT 500KΩ SINGLE

Metal Case 3" Long

2 FOR \$1.20



DIGITAL ELECTRONIC LOCK KIT

for auto ignition, entry door, burglar alarm, etc.
6.50 ea. 4 Digits Programmable to CMOS I.C. Any Combination
IN CIRCUIT
400A RELAY AND KEY PAD NOT INCLUDED



BATTERY POWERED FLUORESCENT LANTERN

FEATURES

- * Circuitry: designed for operation by high efficient, high power silicon transistor which enable illumination maintain in a standard level even the battery supply drops to a certain low voltage.
- * 9" 6W cool/daylight miniature fluorescent tube.
- * 6 X 1.5V UM-1 (size D) dry cell battery.
- * Easy sliding door for changing batteries.
- * Stainless reflector with wide angle increasing illumination of the lantern.



\$9.60 EACH MODEL 888 R

POWER SUPPLY KIT

0-30V D.C. REGULATED
Uses UA723 and ZN3055 Power TR output can be adjusted from 0-30V, 2 AMP. Complete with PC board and all electronic parts.
0-30V POWER SUPPLY **\$10.50 each**
Transformer for Power Supply, 2AMP 24V x 2 \$6.50
30V DC Panel Meter \$4.20



12V DC MINI RELAY

P.C. Board Solder Type



2AMP Contact SPDT \$1.30 EA
2AMP Contact DPDT \$1.75 EA
5AMP Contact 4PDT \$2.20 EA

12V D.C. AUTO DIGITAL CLOCK

Complete Unit
Not a Kit!



0.4" blue color 4 digits display. Turn off readouts when car is not running. X'tal controlled time base for time accuracy. Special designed case for easy mounting on top of your dashboard. Ideal for car, boat and campers.
SALE! ONLY \$28.50 ea. \$24.50

ELECTRONIC SWITCH KIT

CONDENSER TYPE
Touch On Touch Off uses 7473 I.C. and 12V relay
\$5.50 each



AUTO ALARM KIT




The Crimeflighter Auto Alarm is an electronic, self-controlled auto protection system, normally mounted within the glove box of an automobile. Two minutes after turning off the ignition, the alarm automatically turns itself "on". When auto is re-entered, the horn will sound after a 10-45 second entry delay. The automobile owner, by inserting the ignition key, will activate the alarm. Once activated, the alarm will sound for two minutes before automatically turning off. The alarm then resets and is ready to again protect the vehicle from unwanted entry.

FEATURES: Simple installation: 5 wires. Automatically turns on when auto is parked. Adjustable entry time. Extended exit time to allow for unflushed exit from vehicle. Numerous applications include protection of boats, campers, trailers, motorcycles, trucks, Cars. Cannot be deactivated by "hot wiring" an auto. Cannot be turned off without ignition key. Negative ground only.

ONLY \$14.00 PER KIT

AA SIZE NI-CD BATTERY

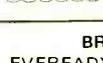
6 in a pack (1.2V)
X 6) 500 MA/HR
\$4.80 PER PACK



BRAND NEW EVEREADY CH15 AA size NI-CD 500 MA/HR. 4 for \$5.50
Only limited quantity available

Sub Mini Size PANEL METER 500 U.A. ONLY \$1.20 ea

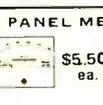PANEL METER (D.C. Type)
Size 60MM X 66MM
White Face Type
\$5.50 ea.
0-50 U.A. 0-30V
0-1MA 0-50V
0-5MA 0-100V



TRANSFORMERS

ALL 117 VOLT INPUT

30V 4AMP \$7.50 EA.
36V CT 3AMP \$6.50 EA.
48V CT 3AMP \$6.50 EA.
24V CT 3AMP \$6.50 EA.
24V CT 0.8AMP \$1.80 EA.
12V CT 0.8AMP \$1.80 EA.
12V CT 120MA \$1.25 EA.

AC POWER SUPPLY

Wall Type Transformer

12V AC Output 200MA \$2.75 EA.
16V CT AC Output 100MA \$2.10 EA.
6V DC Output 120MA \$1.90 EA.
12V DC Output 100MA \$1.90 EA.




WIDE ANGLE PANEL METER

1 3/4" X 3/8"
1MA Full Scale
(scale marks 0-100)
\$1.50 each



HOUR INDICATOR

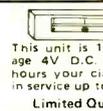This unit is 1 5/8" long operating voltage 4V D.C. will tell you how many hours your circuit or machine has been in service up to 100 hours.
Limited Quantity **ONLY \$1.75 ea.**



HEAVY DUTY CLIP LEADS



10 pairs - 5 colors
Alligator clips on a 22" long lead. Ideal for any testing.
\$1.85/pack

MINI-SIZED I.C. AM RADIO

Size smaller than a box of matches!
Receives all AM stations
Batteries and ear phone included

Only \$8.50



MINI-MINI TOGGLE SWITCH



Half size of submini toggle switch rated 3 amp 125V AC contact
1-9 10-99
MS 244 SPDT 1.00 0.90
MS 245 DPDT 1.20 1.10
LARGE QUANTITY AVAILABLE FOR OEM

SUBMINIATURES TOGGLE SWITCHES



Mini size Rocker Type
Also available at the same price

MINI SIZE REED RELAY



Approx. 1" square
SPST Normal Open
Contact rated 1AMP
Coil 6-12V DC
All brand new by AMF
3 for \$2.00

PUSH-BUTTON SWITCH



N/Open Contact
Color: Red, White, Blue, Green, Black, 4/\$1.00
N/Close also
Available 50¢ ea.
LARGE QTY. AVAILABLE

SOLID STATE ELECTRONIC BUZZER



Mini size 1" x 3/8" x 3/8"
Supply voltage 1.5V 12V
Ideal for Alarm or Tone Indicator
\$1.50 each

MINIMUM ORDER \$10.00. California residents add 6% sales tax and 10% shipping. Out of state add 15% of total purchase for shipping charges, out of USA and Overseas add 25% of total purchase. SEND CHECK OR MONEY ORDER TO:



FORMULA INTERNATIONAL INC.

12603 CRENSHAW BOULEVARD • HAWTHORNE, CALIFORNIA 90260

For more information please call (213) 973-1921, (213) 679-5162

STORE HOURS 10-7 Monday - Saturday

SEND \$1.00 FOR DETAILED CATALOG



TRS-80 memory SPECIAL

Our Conversion Kit upgrades TRS-80 mainframe from 4K to 16K, or populates Memory Expansion Module. With conversion instructions. Also works with APPLES. Only \$159 (3 kits/\$450) . . . and we back up our parts with a 1 year warranty.

HEATH H8 memory SPECIAL

Econoram VII™ brings 12K of Econoram quality to the H8 buss. Fully static. Regular price: \$235 for "unkit" (sockets, bypass caps pre-soldered in place); now, through cover month of magazine, buy 2 unkits for \$399.

SEE OUR PRODUCTS AT YOUR LOCAL COMPUTER STORE.

the S-100 ECONORAM™ family...

Our memories are recognized as outstanding buys, thanks to static design, compatibility with all S-100 machines, buffering, high speed/low power parts, conservative engineering and useful extras. Econoram II is 8K of cost-effective memory; kit \$135, assembled/tested \$155. The 16K Econoram IV costs \$279 for "unkit" (sockets, bypass caps soldered in place); \$314 assembled/tested; and \$414 for CSC qualified*. The top of the line 24K Econoram VII costs \$445 for "unkit"; \$485 assembled/tested; and \$605 CSC qualified*.

*Certified Systems Components board are assembled, tested, serial numbered, burned in for 200 hours, and guaranteed to run at 4 MHz over full temp range. Board exchanged if failure occurs within 1 year of invoice date.

MA1003 clock module \$16.50



Simple to apply; requires only 3 time-setting switches and 12V DC. Ideal for car, van, or other portable use thanks to built-in timebase. Four 0.3" blue-green fluorescent digits. Extra features (such as automatic dimming) included for car use. With applications data. \$16.50 ea., 3/\$46.

TERMS: Add 5% shipping, excess refunded. Cal res add tax. COD OK with street address for UPS. VISA®/Mastercharge® orders call 24 hrs (415) 562-0636. Thank you!

GODBOUT

BILL GODBOUT ELECTRONICS
BOX 2355, OAKLAND AIRPORT, CA 94614

CIRCLE 43 ON FREE INFORMATION CARD

AUDIO/ANALOG Experimenters

- VOLTAGE CONTROLLED SINEWAVE OSCILLATOR Basic™ w. sine & cosine outputs 10 vP P out, 10 Hz to over 16K Hz. Needs 15 VDC @ 20 mA. Easy to build \$49.00
- DC-DC CONVERTER: Outputs: 15 VDC @ 100 mA, for 15 VDC input. Ultra hi isolation, .05% reg'n. Only 2" sq. by .375" thick. An extremely unusual bargain \$19.00
- SYNTHESIZER (MUSICI) VCO: Sawtooth & trigger outs: 10 vP P 10:10KHz out, 1 volt per octave response (exponential), linear input. Needs 15 VDC \$17.95
- ANALOG DELAY IC: Identical to SAD 1024A. Produces real time audio delay w/data \$17.95
- ARTICLES & SYNTHESIS LITERATURE: "TECH NOTES" our own HiD newsletter. Featuring articles on building Active Filters, Audio Freq Shifters, VCO's, VCF's, Flangers, Synthesizers, & other Audio/electronic devices. \$19.50
- TECH NOTES Subscription 12 Issues \$8.95
- DUAL SEC. PWR TRANSFORMERS: 117 V Primary, output 2x 19V @ 1 amp. Hi quality \$4.95
- 5 VOLT, 50 WATT ZENER: TO-3 pkg. 10 amp capability. Unusual bargain \$4.95
- UNUSUAL IC: 14 pin DIP, generates pseudo-random motion sequence. A synthesizer-on-a-chip. Clear plastic pkg. also, senses motion VISUALLY. A unique buy \$7.95
- STATE VARIABLE FILTER IC: Hybrid, identical to the AF 100 IC, 4 on-board op amps. DC 10KHz. Hpass. Bandpass, Loppass, & Notch \$6.95
- "NON-LINEAR CIRCUITS HANDBOOK": By A.D. This is probably THE reference work for analog multipliers, dividers, logging, & anti-logging circuits. A WEALTH of unique information. Over 500 pages. \$9.95
- THE INVISIBLE IC: This clear plastic IC lets you peer into the inner workings of an integrated circuit. 14 pin DIP. Features gold wirebonding & BIG IC chip \$1.50
- TO-220 POWER TRANSISTORS: Complimentary pair, 10 amp ic, over 60 V, 5mhz \$1.95
- PREMIUM MINDIP OP AMPS: BB 3500, 10 noise, 1 bias, NE 531, Hi slew rate. Your Choice \$9.95
- DUAL 15 VOLT REGULATOR IC: Outputs +15 VDC @ over 50 mA, more with pass Xsistors. Balanced, tracking outputs with 5% reg'n or better w/data \$9.95
- AMPHENOL 9-PIN "Miniature Tube" CONNECTOR PLUG: Male plug w/gold plated pins. Fits standard 9 pin mini tube socket & includes rubber cover. 2/\$1.00
- MINDIP SOCKET: Solid nylon w/machined gold plated pins. Augur \$1.00
- 1 uF, 50 VDC CAPACITORS: Mylar construction, PC leads. Special price 12/\$1.00
- OP AMP SPECIALS
- CA 3140 mindip .79/ea LM 307 mindip .19/ea
SG ILM1308A mindip .79/ea LM 301A mindip .24/ea
CA 3401 DIP LM 3900L .49/ea LH 0024CH TO 99 hybrid .44/50
LM 313 TO 99 .89/ea UA 791 1 amp .54/50
- We have many unusual and unique bargains in our FREE FLYER CATALOG. Send us a stamp or 25¢ (for postage) for a FREE COPY and get on our mailing list.

CFR Associates, Inc.
Newton, N.H. 03858
1603382-5179

- Minimum order \$10.00
- Add \$2.00 for shipping
- MC, VISA, & C.O.D. accepted
- Phone orders are welcome

SATISFACTION GUARANTEED

CIRCLE 62 ON FREE INFORMATION CARD

NEW-TONE ELECTRONICS INTERNATIONAL

Specializing in Japanese Semiconductors, with THE LARGEST INVENTORY AND LOWEST PRICES ANYWHERE

AND YOU CAN ORDER TOLL FREE 800-631-1250

Check the prices in this partial list. Dealers - send for our complete volume discount price list.

INTEGRATED CIRCUITS	INTEGRATED CIRCUITS	INTEGRATED CIRCUITS	TRANSISTORS	INTEGRATED CIRCUITS	INTEGRATED CIRCUITS	TRANSISTORS	TRANSISTORS
AN115 2.25	MS1202 1.55	UPC574 1.20	2SC1429 1.49	UH1C004 5.60	2SB175 39	2SC1034 5.45	
AN228 4.65	MS3216P 1.80	UPC583C 3.30	2SC1452 1.40	UH1C005 5.60	2SB324 55	2SC1061 1.00	
AN272 3.90	MS3273P 1.60	UPC1028 1.80	2SC1474 79	UH1C006 6.40	2SB337 1.35	2SC1079 3.95	
AN313 4.85	MS8473P 7.90	UPC1031H 2.98	2SC1548 79	UPC20C 3.65	2SB370 62	2SC1096 75	
AN321 2.25	MB3710 2.95	UPC1032H 1.35	2SC1583 68	UPC355H 1.80	2SB405 45	2SC1166 40	
AN326 3.30	MB8719 7.70		2SC1622 49	UPC563H2 3.65	2SB407 1.20	2SC1172 4.80	
AN362 2.70	MN3006 5.90		2SC1630 3.60	UPC566H 1.15	2SB435 1.25	2SC1193 70	
AN366 2.49	MN3007 19.95		2SC1681 39	UPC575C2 2.35	2SB463 45	2SC1226A 70	
AN606 4.50	NP05107 14.95		2SC1682 39	UPC592H2 1.05	2SB474 85	2SC1237 2.15	
AN612 2.70	PL103A 14.95		2SC1761 1.58	UPC1001H2 3.40	2SB492 85	2SC1239 3.15	
BA401 1.50	SG264A 7.80		2SC1762 4.85	UPC1008C 5.75	2SC372 35	2SC1306 2.45	
BA402 2.50	SG609 4.50		2SC1775 54	UPC1025H 3.05	2SC373 35	2SC1307 3.85	
BA505 6.30	SG629 3.40		2SC1778 45	UPC1025H 2.85	2SC380 35	2SC1383 45	
BA612 2.40	SG6523 17.50		2SC1787 62	UPC1152H 3.25	2SC387A 45	2SC1384 55	
BA1310, 2.34	SI1010 6.90	2SA772 89	2SC1811 1.29	UPC1156H 2.80	2SC394 39	2SC1675 1.90	
HA1125 2.10	SI1020 13.95	2SA786 39	2SC1844 54	UPD857C 9.99	2SC458 45	2SC1678 1.00	
HA1329 2.45	SI1030 19.00	2SA811 54	2SC1885 79	UPD858C 7.20	2SC460 45	2SC1728 1.00	
HA1366W 3.30	SI1050 27.80	2SA818 1.05	2SC1906 48		2SC481 1.45	2SC1760 1.05	
HA1366WR 3.30	SM5104 8.90	2SA835 1.35	2SC1923 39		2SC482 1.35	2SC1909 2.75	
HA1388 3.35	SM5107C 11.95	2SA840 1.68	2SC1940 64		2SC495 79	2SC1957 95	
HA1406 1.20	STK013 11.25	2SA841 39	2SC1945 6.75		2SC509 45	2SC1973 55	
LA1222 1.59	STK014 11.85	2SA842 43	2SC1951 1.59		2SC517 3.25	2SC2028 74	
LA1365 2.20	STK041 8.22	2SA861 1.29	2SC1959 39		2SC535 35	2SC2029 3.35	
LA1368 3.42	STK075 6.75	2SA879 93	2SC1999 3.30		2SC627 1.35	2SC2091 2.40	
LA3101 3.75	STK113 6.50	2SA880 75	2SC2009 .85		2SC634A 45	2SC2092 3.10	
LA4220 2.55	TA7092P 3.60	2SA915 6.33	2SC2021 3.95		2SC710 37	2SC2098 3.40	
LA4430 2.70	TA7117P 7.77	2SA915 1.59	2SC2072 3.95		2SC730 3.95	2SD72 78	
LD3000 2.25	TA7206P 3.06	2SA922 3.98	2SC2120 2.65		2SC732 35	2SD92 1.75	
LD3080 2.70	TA7214P 5.15	2SA923 4.50	2SC2121 1.45		2SC735 35	2SD180 2.35	
LD3110A 3.75	TA7217AP 3.30	2SA940 96	2SC2213 1.45		2SC756A 2.40	2SD218 3.45	
LD3150 1.95	TA7222P 3.50	2SA991 58	2SC2214 2.95		2SC778 3.35	2SD234 80	
MS109P 3.30	TA7521M 3.55	2SB509 2.79	2SC2215 1.45		2SC781 2.50	2SD235 80	
MS112Y 6.70	TA7607P 9.90	2SB528 99	2SC2218 3.65		2SC784 45	2SD261 55	
MS118L 2.50	TA7609P 4.80	2SB549 79	2SD388 3.65		2SC789 85	2SD313 1.05	
MS130P 3.40	TA7609P 4.80	2SB567 2.30	2SD477 1.65		2SC793 2.45	2SD315 1.95	
MS135P 3.40	TA7610P 3.30	2SB618 2.65	2SD528 3.30		2SC828 35	2SD325 85	
MS142P 5.70	TA7610P 3.30	2SB632A 2.55	2SK9 4.45		2SC829 2.65	2SD330 85	
MS540P 1.55	TA7610P 3.30	2SB635 95	2SK107 1.85		2SC878 45	2SD335 85	
MS5930P 85	TA7610P 3.30	2SB635 95	2SK120 1.20		2SC899 85	2SD335 85	
MS5935P 1.20	TA7610P 3.30	2SB635 95	2SK121 1.20		2SC930 35	2SK33 85	
MS5946P 85	TA7610P 3.30	2SB635 95	2SK125 1.75		2SC945 35	2SK55 1.80	
MS5953P 2.55	TA7610P 3.30	2SB635 95	2SK125 1.75		2SC945 35	2SK22 89	
MS5962P 85	UPC572C 4.10	2SC1424 2.98	2SK133A 3.90		2SC1014 85	2SK40 2.10	
					2SC1018 85	2SK45 1.90	

N.J. Residents add 5% Sales Tax
We pay postage for prepaid orders of \$50.00 or more
under \$50.00 add \$1.00 Canada \$1.50

COD'S WELCOME
Hours - Daily 9 AM - 7 PM EST, Sat 9 AM - 5 PM
All prices are suggested retail prices. Excludes taxes.



NEW-TONE ELECTRONICS INTERNATIONAL
P.O. Box 1738 Bloomfield, N.J. 07003
New Jersey Phone 201/748-6171

CIRCLE 71 ON FREE INFORMATION CARD

Regency

SCANNER

4 Channels UHF

- POLICE
- FIRE

- Continuously Monitors 4-Channels
- Hear UHF (450-500MHz)
- Model ACT-C4U



Reg. ~~39⁹⁵~~

\$33

RA-214

RADAR DETECTOR

BEARFINDER

5555
AU-651



- Audible and Visual Indicator
- Detects Stationary and Moving Radar

* Ask about BEARFINDERS
Out of Warranty Special!

Reg. ~~89⁹⁹~~

RECORDER

"MESSAGE MINDER"

Reg. ~~7⁹⁹~~

499

RA-731

AS-IS



SWR METER

799

CB-067

INCLUDES ANTENNA



LOCKMOUNT

For Under Dash Mounting of CB's, Radios, etc.

99c

AU-149

Reg. ~~1⁹⁹~~




AM AUTO RADIO

Pushbutton Controls

Reg. ~~10⁹⁹~~


899

AU-580

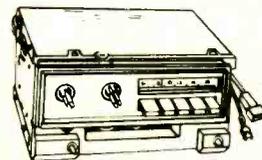

CASSETTE

30-Minute Blank

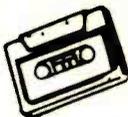

29c

TA-987

8-TRACK

40-Minute Blank
LIMIT 30

49c

TA-907

MULTIMETER

Olson 1000 Ohms/Volt

For Best CB Performance

899

TE-184

Reg. ~~12⁵⁰~~



AC ADAPTER

AC to 6, 7.5, 9 VDC

299

BA-159

Reg. 2 for \$11



8-TRACK TAPE DECK CHASSIS



799

RA-617

Reg. ~~9⁹⁹~~

Olson
electronics

Dept. LJ
260 S. Forge St.
Akron, Ohio 44327

NAME _____
ADDRESS _____
CITY _____
STATE _____ Zip _____

Qty.	Stk. #	Description	Price Ea.	Total

Tax _____
Postage _____
Total _____

FREE!

Please send me a free subscription to Olson Value Packed Catalog.

OLSON COMPUTERS

Commodore "PET"

Ohio Scientific
Challenger III

Challenger IIP

Videobrain



Olson - 8 8080



Write for FREE Computer Catalog


ELECTRONIC SUPERMARKET

Phone Orders:
(617) 532-2323
BA, MC or AE

Terms: Add postage. No C.O.D.'s. Phone Orders BA-MC-AE: (617) 532-2323.
Lynnfield, Massachusetts 01940 Dept. R-11 P.O. Box 619

REMOTE CONTROL SYSTEM

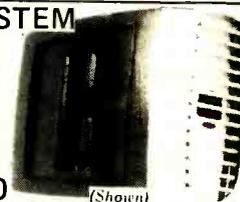This handy control was part of an Admiral remote control package for color TV. The original functions were: On-Off, Volume, VHF-UHF, and channel select. Receiver contains 3 relays and one-four position stepping relay. Also a complete 4 page data pkg. Use it to make all kinds of remote operating toys, alarms detectors, appliances, etc. Transmitter requires AA cell (not included). Qty. Ltd.



Sh. Wt. 1 lb. 8C30372 \$25.00
3 for \$69.88 8C30372 \$69.88/3

(Shown) Includes Transmitter & Receiver

AM/FM STEREO RECEIVER/AMP CHASSIS



"REPAIRMAN SPECIAL"

Surplus Brand-name receiver/amplifier chassis, including bulls-eye stereo light on tuning needle, slide controls, amp & tuner (no case). Mfr.'s "questionables", may need repair. You fix & save! Qty. is limited. AS IS (no returns). W/data. 5 Lbs. 8K3035 \$19.88 ea.

ALARM SYSTEM MOTION DETECTOR



New package system. A super close-out item. Protects your valuables; gun's, CB's, stereo equipment, test equipment, etc. . . . List Price \$22.88.
Sh. Wt. 1 lb. MD33 \$7.88
3 for \$22.88 MD33 \$22.88/3

ULTRASONIC

This alarm sensor fills the protected area with an energy screen that cannot be seen, felt or heard. Triggers your alarm whenever burglar moves through detector field. Mounts on ceiling, wall, desk, shelf etc. Optional delay mode, auto-reset. Operates on 12.5 VDC. A close-out that originally sold for \$179.00! 3 Lbs. Qty. Ltd. #8D30336. \$49.88

MICROPROCESSOR

The Viatron Data Management Station; Used, complete system. Running Condition. Sold "AS IS". Send for more information. Qty. Ltd. \$495.00

SEND FOR FREE CATALOGUE *CIRCLE FREE INFO. CARD* ea.

Visit our Retail Stores - 177R Washington St., Peabody, Mass. or our NEWEST store THE TOWNE DEPOT, INC. next to WOODCO. 777 So. Willow St., Manchester, New Hampshire.

70% OFF ON ALL ORDERS OVER \$10.00 FROM THIS AD.

CIRCLE 65 ON FREE INFORMATION CARD

INTEGRATED ELECTRONICS

540 Weddell Drive, #4, Sunnyvale, CA 94086 (408)734-8470

CMOS		74C08 .65		7427 .35		74161 1.00		8973 2.95		8334 4.00	
4000	.15	74C10	.25	7430	.15	74163 1.30	8974 2.95	8563 6.50			
4001	.20	74C20	.75	7432	.30	74164 1.45	8976 2.95	8556 3.25			
4002	.20	74C30	.26	7437	.44	74165 1.35	75107 3.25	8599 3.25			
4007	.20	74C32	.30	7442	.18	74166 1.20	75450 1.00				
4010	.36	74C42	1.40	7445	.70	74173 1.70	75451 .80				
4011	.20	74C48	2.75	7446	.70	74175 1.05	75452 .80				
4012	.20	74C73	1.25	7448	.70	74177 .90	75453 .80				
4013	.35	74C74	1.75	7450	.25	74191 1.20	75491 1.25				
4014	.80	74C86	1.00	7453	.25	74192 1.10	75492 1.40				
4015	.80	74C90	1.10	7451	.25	74193 1.35	75494 1.50				
4016	.35	74C93	1.25	7454	.35	74195 1.10	8214 8.50				
4017	.92	74C151	2.75	7460	.22	74196 1.10	8216 3.75				
4018	.92	74C154	3.00	7472	.40	74197 1.10	8224 4.75				
4019	.20	74C157	2.10	7473	.40	74199 2.25	8228 9.90				
4020	1.00	74C180	1.40	7474	.40	74367 .90	8228 11.50				
4022	.83	74C181	1.70	7475	.55		8228 11.50				
4023	.21	74C164	1.75	7476	.45		8228 11.50				
4024	.05	74C165	1.75	7483	1.05		8228 11.50				
4025	.20	74C174	1.50	7485	1.10		8228 11.50				
4027	.34	74C902	.85	7486	.43		8228 11.50				
4028	.79	74C904	.85	7489	2.00		8228 11.50				
4029	1.00	74C905	3.00	7492	.75		8228 11.50				
4030	.20	74C914	1.95	7493	.65		8228 11.50				
4035	.95			7495	.78		8228 11.50				
4040	1.00			7496	.78		8228 11.50				
4041	1.00	7400	.16	74121	.35		8228 11.50				
4042	.70	7401	.17	74122	.49		8228 11.50				
4044	.60	7403	.17	74123	.65		8228 11.50				
4049	.35	7404	.19	74126	.65		8228 11.50				
4051	1.10	7405	.40	74132	1.25		8228 11.50				
4056	.70	7407	.40	74141	1.15		8228 11.50				
4068	.40	7409	.25	74145	1.0		8228 11.50				
4069	.40	7410	.18	74148	1.20		8228 11.50				
4075	.20	7413	.78	74150	.90		8228 11.50				
4082	.23	7414	.68	74153	1.10		8228 11.50				
74C00	.25	7417	.38	74154	1.25		8228 11.50				
74C02	.45	7420	.18	74155	.75		8228 11.50				
74C04	.32	7421	.35	74157	1.00		8228 11.50				

* For more 74LSxx, refer to our ad in the June issue of this magazine.

SPECIAL DISCOUNT

OEM EDUCATORS AND SCHOOLS

For a low quote, send a list of your needs and, if possible, desired prices. No quantity is too small.

Minimum order \$5.00 US currency. Check or money order only. Add 5% to cover shipping and handling charges. Calif. residents add 6% sales tax. Santa Clara County residents add 6.5% sales tax.

CIRCLE 51 ON FREE INFORMATION CARD

BULLETT ELECTRONICS

P.O. BOX 19442R DALLAS, TEX. 75219
(214)823-3240

MC1351P FM-IF AMP AND DISCRIMINATOR

USED IN FM & TV SOUND CIRCUITS REQUIRES MINIMUM EXTERNAL COMPONENTS. 14 PIN DIP DIRECT REPLACEMENT FOR HEPC 6060, ECG 748 and MANY OTHERS. HOUSE # WITH SPECS 50c

MINI GRANDFATHER CLOCK KIT

Complete Electronics!
• Chimes the hour (1/3 times for 3 o'clock)
• Unique "swinging" LED pendulum
• Tick tock sound matches pendulum swing.
• Large 4 digit "5" LED readout
• All CMOS construction
• Complete electronics including transformer & speaker; drilled and plated PC boards measure 4.5" x 6.5"

BEAUTIFUL SOLID WALNUT
Custom case for above kit. Over 9" tall. 19.95

MJ900 - MJ1000

COMPLEMENTARY PNP, NPN DARLINGTON POWER TRANSISTORS, 8 AMPS. WE SUPPLY A SCHEMATIC TO BUILD A HIGH POWER (35W) LOW DISTORTION AUDIO AMP WITH ONLY ONE ADDITIONAL TRANSISTOR AND A DOZEN INEXPENSIVE COMPONENTS; TO-3 CASE STYLE. BUY A PAIR FOR \$3.00!

POWER SUPPLY METERS

Quality 3 1/2" meters for the P-14, 0-15VDC & 0-25A. Matched set, individually packaged. 12.95/set

LM3900 QUAD NORTON AMP

WE BOUGHT A LARGE QUANTITY OF THESE HOUSE NUMBERED PARTS AT A BARGAIN PRICE THAT ALLOWS US TO SELL THEM AT A LOW, LOW 39c

MK-05 MINI MOBILE CLOCK

The smallest and best priced mobile clock kit on the market. Designed to be a mobile clock from the ground up. There has been no compromise on quality.

FEATURES:
• Quartz crystal timebase
• Toroid & zener noise & overvoltage protection.
• Night face 15" 6 digit LED readout
• Complete with portable 24 hr. alarm
• 9-14 VDC @ 40 to 50 ma
• Readouts can be suppressed
• EASY QUICK ASSEMBLY
• All components required included (you supply the speaker)
• Top quality drilled and plated PC boards
• Clock board: 2 1/2" x 2 1/2"
• Readout board: 2 3/8" x 7 1/2"

12.95

FND510 69c

COMMON ANODE READOUT "I" CHARACTER
LIMIT 24 PER CUSTOMER!

CAPACITORS

SMALL SIZE!
2200 MFD @ 16 VDC RADIAL 3/1.00

POWER SUPPLY KIT PS-14

Better than 200MVA load and line regulation
• Foldback Current Limiting
• Short Circuit Protected
• Thermal Shutdown
• Adjustable Current Limiting
• Less than 1% ripple.
• 15 amps 11.5 to 14.5V
• All parts supplied including heavy duty transformer.
• Quality plated fiberglass PC board.

REVIEWED IN 7/78 73 MAG.
15A CONT. 20A INT. 42.95

ALL COMPONENTS 100% GUARANTEED

GA3011 WIDEBAND IF AMP w/specs	50c
2N3569 NPN 60KV 1W	6/1.00
741 OP AMP & PIN DIP	5/1.00
723 VOLTAGE REG. 14 PIN DIP	8/1.00
MP6530 PNP HOUSE #	8/1.00
725 OP AMP LOW NOISE HOUSE #	9/1.00
7815 15V 1A REGULATOR HOUSE #	6/1.00
LM3407-12 12V 1A VOLT. REG. w/specs	7/1.00
TC4430 QUAD OSCILLATOR w/specs	6/1.00
2N4343 P CHANNEL J FET	4/1.00
2N6111 PNP MED PWR 40W TO 220	3/1.00
2N6208 PROGRAMMABLE UNIJUNCTION w/specs	5/1.00
TRIAIC 200V 8A UNMARKED	3/1.00

UNIVERSAL SOUND EFFECTS BOARD

HAVE YOU EVER WISHED YOU COULD DUPLICATE THE SOUND OF A STEAM TRAIN OR A PHASOR GUN? HOW ABOUT GUNSHOTS, WHISTLES, SIRENS, BARKING DOGS AND OTHER SOUND EFFECTS? NOW YOU CAN WITH OUR PROGRAMMABLE SOUND EFFECTS KIT. IT USES THE NEW 28 PIN T.I. SOUND SYNTHESIZER CHIP, SM76477 AND SUPPORT CIRCUITRY. 5 TO 12VDC IS REQUIRED TO GIVE APPROX. 1/4 WATT OF AUDIO OUTPUT. WE PROVIDE THE P.C. BOARD, PARTS AND INSTRUCTIONS ALONG WITH A CHART TO PROGRAM SOME COMMON SOUNDS. USE YOUR IMAGINATION TO CREATE ORIGINAL SOUND EFFECTS. ORDER: SE-01 14.95 (Less Spkr.) 3/39.95

OVERVOLTAGE PROTECTION KIT 6.95

Provides cheap insurance for your expensive equipment. Trip voltage is adjustable from 3 to 30 volts. Overvoltage instantly fires a 25A SCR and shuts the line to protect equipment. Should be used on units that are fused. Directly compatible with the PS-12 and PS-14. All electronics supplied. Drilled and plated PC board. (Order OVP 1)

FANTASTIC SOUND EFFECTS CHIP

AVAILABLE ONLY FROM BULLETT!

WARBLE ALARM KIT

A fun EASY kit to assemble that emits an ear piercing 10 watt dual tone scream. Resembles European siren sound. Great for alarms or toys. Operates from 5-12VDC at up to 1 amp (using 12VDC 8 ohm speaker). Over five thousand have been sold. All parts including PC board, less speaker. 2.50 ORDER WB-02

CAPACITORS

.022	100VDC Mylar	8/1.00
.022	50VDC Mylar	6/1.00
1.5mfd	400VDC Mylar	4/1.00
1mfd	35V Tant Axial	6/1.00
4.7mfd	35V Tant Axial	6/1.00
2.2mfd	35V Tant Axial	5/1.00
22mfd	20V Dip Tant	4/1.00
33mfd	10V Dip Tant	4/1.00
220mfd	25V Alum Axial	7/1.00
500mfd	35V Alum Axial	5/1.00

HOUSE # PNP POWER

TO-3 IDENTICAL TO 2N3790

150 WATTS
80 VCEO
10 AMPS 1.00

IL-1 OPTO ISOLATORS

BY LITRONIX 6 PIN DIP STANDARD PINOUT LED-TRANSISTOR COMBINATION. 50c WHILE THEY LAST!

MK-03A CLOCK/TIMER KIT

Features 24 hour Zulu time and up to 24 hours of elapsed time on the same set of six 12VDC readouts. Totally independent operation of both functions. Clock has presettable alarm with 10 minute snooze. Timer has reset, hold, and count functions. Full noise and overvoltage protection. 24 hour only. Readouts has dimmer feature or they can be turned off without disturbing the clock or timer. Timebase included (0.1% accuracy). Because of the many options and mounting considerations the case and switches are not included. Switches are standard types. Will fit inside standard aircraft instrument case. 9-14VDC 28.95

* NO C.O.D.'S
* SEND CHECK M.O. OR CHARGE CARD NO.
* PHONE ORDERS ACCEPTED ON VISA AND MASTERCARD ONLY.

* ADD 5% FOR SHIPPING
* TX RES. ADD 5% STATE SALES TAX
* ORDERS OF \$50 & OVER TAKE 10% DISCOUNT
* FOREIGN ORDERS ADD 10% (20% AIRMAIL U.S. FUNDS ONLY.)

TOTAL SECURITY! Completely invisible ultrasonic (23KHz) sound beam works like a photoelectric beam but is unaffected by light, heat or noise. Separate Transmitter and Receiver can be used from 6 inches to 25 feet! A solid object breaking the beam causes an output to go low that will sink up to 150 MA to Drive a Relay, TRIAC, etc. Complete electronics are standard types. Works on 12VDC (unregulated) and draws less than 100 MA. Use it for burglar alarms, object counters, automatic door openers, automatic door bells, electronic rat trap! and more.
COMPLETE KIT LESS CASES 21.50
Optional entry delay and Alarm Timeout Circuit .95
Will source or sink up to 200 MA DC.

STUDENTS & TEACHERS
 WITH YOUR ORDER, SEND PROOF OF YOUR STATUS AND RECEIVE 5% OF YOUR PRESENT ORDER AS A CREDIT CERTIFICATE YOU CAN USE ON YOUR NEXT ORDER.

FREE SOCKETS WITH PURCHASE OF ANY OF THESE I.C.'S.

READ THE FINE PRINT AND SAVE!

THE FIRST MEMORY SPECIAL YOU WON'T FORGET

2102-2	650ns	8/9 ⁹⁵	32/37 ⁰⁰	64/71 ⁰⁰	128/135 ⁰⁰
2102-4	450ns	8/10 ⁹⁵	32/41 ⁰⁰	64/78 ⁰⁰	128/145 ⁰⁰
2114D	450ns	8/79 ⁰⁰	16/149 ⁰⁰	32/274 ⁰⁰	64/499 ⁰⁰

PRESCALER - 250 MHZ
complete \$23⁹⁵

PRESCALER - 650 MHZ
complete \$49⁹⁵

11C90 - PRESCALER CHIP
650 mc \$19⁹⁵

SOLID STATE RELAY
• 400 V at 3 AMPS • TTL COMPATIBLE
• MICRO REED ACTUATED TO MINIMIZE CHANCES OF AC POWER SPILLOVER INTO LOGIC CIRCUITS \$3⁹⁵

CHEAPER BY THE 100

LEDS - (HP AXIAL-RED)	100/8.95
LEDS - (MINI-RED)	100/9.95
LEDS - (JUMBO-RED)	100/13.95
LEDS - (DUAL COLOR)	100/59.00
1N4001 - (50V-1 AMP)	100/ 4.95
1N4148 - (SWITCHING DIODE)	100/ 3.95
2N4303 - (N-JFET)	100/21.95
2N3392 - (PRIME-NPN LDW NOISE)	100/ 9.95

AUDIO POWER AMPS

SINGLE		STEREO	
TDA-2020-20 Watt	\$9.95	STK433-5 Watts per channel	\$6.95
S11020H-20 Watt	\$10.50	STK437-10 Watts per channel	\$9.95
S11130H-30 Watt	\$12.50	STK439-15 Watts per channel	\$13.95
STK-50 50 Watt	\$18.95	STK441-20 Watts per channel	\$16.95

8080 SYSTEM

80804	5.95
8212	3.75
8214	8.95
8216	3.50
8224	4.80
8226	4.75
8228	7.25
8238	8.25
8251	9.45
8253	21.50
8255	10.75
8257	20.50
8259	20.50

OPTO ISOLATORS

- MCT2 \$.79
- MOC1000 \$.89
- 4N-26 \$.95
- CL1422

CLAIREX PHOTO MODULE (USE AS VOLTAGE VARIABLE RESISTOR—40 MEG OHM TO 40 OHM—MILLION TO ONE RATIO—OR USE AS VERY HIGH VOLTAGE OPTO ISOLATOR) \$1.49

REFLECTIVE PHOTO COUPLERS

TIL-139 LED INTO PHOTO TRANSISTOR \$2⁹⁵

ROC100 INCANDESCENT INTO CDS CELL—
20 MEG OHM OFF RESISTANCE \$1⁹⁵

9900 SYSTEM

9900	66.00
9901	23.75
9902	19.50
9980	54.00
9981	54.00

8080 SYSTEM

80804	5.95
8212	3.75
8214	8.95
8216	3.50
8224	4.80
8226	4.75
8228	7.25
8238	8.25
8251	9.45
8253	21.50
8255	10.75
8257	20.50
8259	20.50

Z-80 SYSTEM

3880	22.50
3881	12.50
3882	12.50
3883	49.00
3884	73.00

6800 SYSTEM

6800	16.95
6810	7.20
6820	7.95
6821	8.50
6850	8.95
6852	11.95
6860	9.95
6862	13.75

5500 SYSTEM

6502	14.95
6520	12.75
6522	12.50
6530	17.50

9900 SYSTEM

9900	66.00
9901	23.75
9902	19.50
9980	54.00
9981	54.00

8080 SYSTEM

80804	5.95
8212	3.75
8214	8.95
8216	3.50
8224	4.80
8226	4.75
8228	7.25
8238	8.25
8251	9.45
8253	21.50
8255	10.75
8257	20.50
8259	20.50

8080 SYSTEM

80804	5.95
8212	3.75
8214	8.95
8216	3.50
8224	4.80
8226	4.75
8228	7.25
8238	8.25
8251	9.45
8253	21.50
8255	10.75
8257	20.50
8259	20.50

8080 SYSTEM

80804	5.95
8212	3.75
8214	8.95
8216	3.50
8224	4.80
8226	4.75
8228	7.25
8238	8.25
8251	9.45
8253	21.50
8255	10.75
8257	20.50
8259	20.50

8080 SYSTEM

80804	5.95
8212	3.75
8214	8.95
8216	3.50
8224	4.80
8226	4.75
8228	7.25
8238	8.25
8251	9.45
8253	21.50
8255	10.75
8257	20.50
8259	20.50

RADIO SHACK® TRS-80™ COMPUTER SERVICE AND MODIFICATION

BE FIRST TO TURN YOUR TRS-80 INTO A SUPER MACHINE

- Keyboard and Video Mod**
ADD RAM FOR LOWER CASE CHARACTERS AND CLEAN UP HORIZONTAL SMEAR (SEND YOUR TRS-80 MICROCOMPUTER ONLY)
PARTS AND LABOR \$59⁰⁰
- Install 16K Memory**
JUST SEND US YOUR TRS-80 MICROCOMPUTER AND WE DO THE REST.
16K OF MEMORY AND LABOR \$189⁰⁰
- Level 2 plus 1 Mod**
WE INSTALL YOUR level 2 SO YOU KEEP LEVEL 1 AND CAN USE IT BY JUST FLIPPING A SWITCH. (SEND LEVEL 2 WITH YOUR TRS-80)
\$69⁰⁰
- Clock Mod**
INCREASE YOUR PROCESSING SPEED BY 30%. WITH THIS OPTION YOU CAN SWITCH-SELECT BETWEEN THE FASTER 2.66MHZ CLOCK RATE AND 1.77MHZ.
INSTALLATION, PARTS AND LABOR \$49⁰⁰
- Serial Printer Interface Mod**
OPERATE CRYSTAL CONTROLLED TTY WITH LEVEL 1 OR 2. WE INSTALL SWITCH SELECTABLE BAUD RATES OF 75, 110, 137.5, 150, 300, 600, 1200, 2400, 4800, 9600 OR EXTERNAL EIA RS232 AND CURRENT LOOP OUTPUT.
PARTS AND LABOR \$119⁰⁰
- Mini Floppy Mod**
YOU PROVIDE EXPANSION INTERFACE AND WE'LL INSTALL A PERTEC F D 200 MINI FLOPPY.
PARTS AND LABOR (PERTEC F D 200 MINI FLOPPY INCLUDED) FOR ONLY \$425⁰⁰

SPECIALS!! DO MORE THAN ONE MOD AND SAVE

MODS 1, 2, 3, 4 AND 5	\$449 ⁰⁰
MODS 1 AND 2	\$234 ⁰⁰
MODS 2 AND 3	\$243 ⁰⁰
16K OF MEMORY, PARTS AND INSTALLATION DATA.	\$159 ⁰⁰

ALL WORK GUARANTEED UNCONDITIONALLY FOR 1 YEAR

TERMS FOR TRS-80 WORK: WE ACCEPT ONLY TRS-80 MICROCOMPUTERS! SHIP YOUR TRS-80 MICROCOMPUTER TO US, INSURED AND SUITABLY PACKAGED AND WE WILL RETURN SAME FREIGHT COLLECT. ALL FACTORY SEALS MUST BE INTACT. ANY UNIT WHOSE SEALS HAVE BEEN TAMPERED WITH WILL BE SHIPPED BACK IMMEDIATELY. MODS 1, 2, 4 AND 5 SEND TRS-80 MICROCOMPUTER ONLY. MOD 3 SEND YOUR TRS-80 MICROCOMPUTER AND LEVEL 2. MOD 6 SEND TRS-80 AND EXPANSION INTERFACE. **NORMAL TURN AROUND TIME IS UNDER 10 DAYS WITH CERTIFIED FUNDS**

REPAIR—WE WILL REPAIR ANY ORIGINAL TRS-80 MICROCOMPUTER OR ONE OF OUR MODIFICATIONS.
ALL PARTS AND LABOR \$69⁰⁰

NOTE: THIS IS AN INDEPENDENT SERVICE EFFORT NOT AFFILIATED WITH RADIO SHACK® OR TANDY CORPORATION.

F. REICHERT SALES

1110 E. GARVEY AVE.
W. COVINA, CA 91790
(213) 967-3846

• \$20 MINIMUM ORDER
• FREE UPS DELIVERY ON U.S. ORDERS ONLY—OR BY SURFACE MAIL IF SPECIFIED.
• MONEY BACK GUARANTEE (MOS & LED DEVICES EXCLUDED)
• UNDER 8 HOUR PROCESSING ON MONEY ORDERS & CASHIER'S CHECK.

• SORRY! NO COD'S, P.O.'S OR CREDIT CARDS
• CALIF. RES. ADD 6% SALES TAX
• CANADA, PUERTO RICO & U.S. POSSESSIONS ADD U.S. \$3.50. ALL OTHERS ADD U.S. \$7.00.
• U.S. FUNDS ONLY.

DROP INTO ONE OF OUR LOCATIONS

LOS ANGELES (213) 967-4611 LMN ELECTRONICS 1042 E. GARVEY AVE. WEST COVINA, CA	PORTLAND (503) 646-4044 WIZARD OF PARTS 8225 S.W. CIRRUS DR. BEAVERTON, OREGON	DENVER (303) 573-5214 ELECTRONIC LOLLIPOP 5643 N. BROADWAY, DENVER (1-25 & 58th AVE.)
--	--	---

ALL ITEMS SUBJECT TO PRIOR SALE
CIRCLE 80 ON FREE INFORMATION CARD
www.americanradiohistory.com
PRICES SUBJECT TO CHANGE WITHOUT NOTICE

ASCII KEYBOARD KIT \$74.00



**Additional Improvements: Double Size Return Key
Control Characters Molded on Key Caps**

- Power: +5V 275mA
 - Upper and Lower Case
 - Full ASCII Set
 - 7 or 8 Bits Parallel Data
 - Optional Serial Output
 - Selectable Positive or Negative Strobe, and Strobe Pulse Width
 - 2 Key Roll-Over
 - 3 User Definable Keys
 - P.C. Board Size: 17-3/16" x 5"
- OPTIONS:**
- Metal Enclosure Painted Blue and White \$27.50
 - 18 Pin Edge Con. \$ 2.00
 - I.C. Sockets \$ 4.00
 - Serial Output Provision (Shift Register) \$ 2.00
 - Upper Case Lock Switch for Capital Letters and Nos. \$ 2.00
 - Assembled (on Sockets) and Tested \$90.00

Shipping: Keyboard \$3.50;

California residents add 6% sales tax

ELECTRONICS WAREHOUSE Inc.

1603 AVIATION BLVD.
REDONDO BEACH, CA. 90278
TEL. (213) 376-8005



WRITE FOR FREE CATALOG

Dept. R

CIRCLE 48 ON FREE INFORMATION CARD

WIRE WRAP

— PRECUT WIRE —
Why buy wire on rolls?

PRECUT & STRIPPED WIRE IS:

- Fast - No more cutting & stripping by hand
- Reliable - Good, clean, uniform strip
- Economical - Cheaper than using bulk wire

PRECUT WIRE BULK WIRE

100 pcs of 3' at \$1.82 3 1/4c/ft. 50 ft roll at \$1.99 4c/ft.
100 pcs of 6' at \$1.06 2c/ft. 100 ft roll at 2.95 3c/ft.
Wire Kit 1 at \$6.95 2 1/3c/ft.

30 Kynar stripped 1" on each end. Lengths are overall
Colors: Red, Blue, Green, Yellow, Black, Orange, White.
Wire packaged in plastic bags. Add 25% length for tubes.

	100	500	1000	5000
2' in	78	240	430/K	3.89/K
3' in	82	260	471/K	4.22/K
3' in	86	280	512/K	4.55/K
4' in	90	300	552/K	4.88/K
4' in	94	321	593/K	5.21/K
5' in	98	342	634/K	5.52/K
5' in	102	365	675/K	5.86/K
6' in	106	385	716/K	6.19/K
6' in	115	405	757/K	6.52/K
7' in	120	425	798/K	6.85/K
7' in	125	445	839/K	7.18/K
8' in	129	465	880/K	7.51/K
8' in	132	485	921/K	7.84/K
9' in	136	505	962/K	8.17/K
9' in	140	525	1003/K	8.50/K
10' in	145	551	1044/K	8.83/K
Additional	10	41	82/K	66/K

WIRE KITS

#1 \$6.95 #2 \$19.95

250 3'	100 4'	250 2'	250 4'	250 6'
250 3'	100 5'	500 3'	250 5'	100 6'
100 4'	100 6'	500 3'	100 5'	100 7'
		500 4'	1250 ft roll bulk	

Choose One Color or Assortment

WIRE WRAP SOCKETS

1-9 10-23 25-99 100-249 250-999 1K-5K

8 pin	35	33	31	29	25	23
14 pin	35	33	31	29	28	27
16 pin	37	35	33	31	30	29
18 pin	60	55	45	43	40	37
20 pin	84	78	71	63	59	54
22 pin	90	85	82	76	70	60
24 pin	91	84	78	68	64	59
28 pin	95	89	84	80	76	74
40 pin	150	140	130	120	105	90

Gold 3 Level Closed Entry Sockets
End & Side Stackable All prices include gold
2-Level Sockets Available

WIRE WRAP TOOLS



\$34.95

HOBBY WRAP
MODEL BW 630

With FREE Wire Kit #1
(\$6.95 Value)

Batteries & Charger	\$11.00
WSU 30 Hand Wrap-Unwrap Strip Tool	6.25
WSU 30M, for Modified Wrap	7.25
BT 30 Extra Bit	2.95

INTERCONNECT CABLES

Ribbon cable connectors for connecting boards to front panels, or board to board.

	SINGLE ENDED			DOUBLE ENDED		
	14 pin	16 pin	24 pin	14 pin	16 pin	24 pin
6'	1.24	1.34	2.05	2.24	2.45	3.37
12'	1.33	1.44	2.24	2.33	2.55	3.92
24'	1.52	1.65	2.63	2.52	2.76	4.31
48'	1.91	2.06	3.40	2.91	3.17	5.08

PAGE DIGITAL ELECTRONICS

135 E Chestnut St #5
Monrovia, California 91016
(213) 357-5005

ORDERING INFORMATION

- Orders under \$25 and COD's, add \$2
- All others, shipped Ppd in U.S. via UPS
- For Blue Label (Air) or 1st Class, add \$1
- We accept Visa & MasterCard
- Most orders shipped same day

DEALER INQUIRIES INVITED

CIRCLE 22 ON FREE INFORMATION CARD

EDLIE ELECTRONICS' TEST EQUIPMENT BONANZA.




EICO 272

Measures up to 1000 DC volts and up to 600 AC volts up to 1000 DC and AC milliamperes. Resistance in kilohms up to 1 meg, 3 digits .3 in four ranges 1(.999), 10(9.99) 100(99.9) 1000(999)
Accuracy: DC volts $\pm 0.5\%$ of reading. All other functions $\pm 1\%$ of reading. Automatic zero, automatic polarity
Reg. \$79.95. Our price \$67.95

B&K Dual-Trace Triggered 5" Scope

MODEL 1471B

Mode automatically shifts between CHOP and ALTERNATE as you change sweep time for fast set-up. Bright P31 blue phosphor. 18 calibrated sweeps—1 μ SEC/cm to .5SEC/cm. Sweep to 200nSEC/cm with 5X magnification. Front panel X-Y operation using matched vertical amps. Input grounding switches. TV sync separators. Check most digital logic circuitry including CMOS. Character display applications using TTL compatible Z-axis intensity modulation. Includes probes.
Reg. price \$599.00. Our price \$505.00

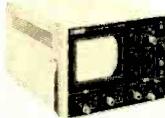

B&K 520 MHz Frequency Counter MODEL 1850

5Hz to 520 MHz reading guaranteed—600 MHz typical. Gate time from 10ms to 10 seconds. Full period measurement capability. 50 mV input sensitivity at 520MHz. Operates from 115 to 230 VAC, or 12 VDC. Well protected input circuitry. Temperature compensated crystal oscillator (TCXO).

APPLICATIONS RF frequency measurement to 520MHz, including business band, broadcast service, amateur radio, marine band, paging systems, mobile telephones and citizens band.
Reg. price \$450.00. Our price \$382.50

B&K Industrial Transistor Tester MODEL 520B

Now with HI/LO Drive. Works in-circuit when others won't. Identifies all three transistor leads. Random lead connection. Audibly and visually indicates GOOD transistor. Automatic NPN/PNP determination. Positive Si/Ge identification. Tests diodes, SCR's, FET's and Darlingtons.

The 520B with HI/LO Power Drive lets you test even more transistors and semiconductors in-circuit—with shunt resistances as low as 10 ohms and shunt capacitances up to 15 nF. A complete test can take less than nine seconds.
Reg. price \$175.00. Our price \$148.75



DE109 #22 GAUGE TWISTED PAIR (Solid); available in the following colors: Red and Black, Blue and Black, Yellow and Black.
100 ft. rolls Price only \$1.75 per roll
1000 ft. rolls Price only \$12.00 per roll



Back by popular demand. Mini speaker/dynamic mike element. 500Q impedance. Used for Hi-Fi, experimentation, or even digital.
Price now only 99c, 3 for \$2.65



Another EDLIE Super Tape Special. 1800 Quality Tape made by Scotch, Ampex or Soudcraft on 7" regular reels. They were bought surplus and are of excellent grade.
79c 3 for \$2.25 6 for \$3.99
100 for \$59.95

DE391 extra special!! 8" high compliance suspension speaker.

10 oz. magnet. Capable of handling the really heavy wattage Stereo & Hi-Fi Equipment. Really Exceptional Buy!! Only \$7.95



DE108 #20 WIRE STRANDED Red, White, Grey, Off-White (Clear), Orange, Black with White. Please Specify Color Desired.
100 ft. rolls Price only \$1.49 per roll
10 rolls assorted Price only \$12.95
1000 ft. rolls (1 color) \$10 per 1000
Buy 10,000 feet in any assortment or one color Price only \$75

EDLIE Electronics
2700 Hempstead Tpk.
Levittown, N.Y. 11756
Your one stop, full line
Electronic Discount Center
(516) 735-3330

WRITE FOR FREE VALUE PACKED CATALOG

Mastercharge
BankAmericard
VISA accepted



Terms: Minimum order \$10.00. Include postage. Either full payment with order or 30% deposit, balance C.O.D. F.O.B. Levittown, N.Y.

An EDLIE Super Special

DE944 Heavy Duty 6"x3" Air Suspension Speaker.
10 oz. magnet. 55-15,000 Hz. Price \$6.95 ea.



CIRCLE 38 ON FREE INFORMATION CARD

POLY PAKS® DISCOUNT ALLEY



WE'RE PUTTING "GREENBACKS" IN YOUR POCKET!

Poly Paks, originator of the world famous PENNY SALE, now brings you the best bargains available anywhere! For any \$15 ad, TAKE 10% DISCOUNT! Or, for any \$50 shipment of material from this ad, TAKE 25% DISCOUNT! NOBODY GIVES LIKE POLY PAKS!

300 CFM HIGH POWER BLOWER

Made by Fasco! For home, shop, industry! 115VAC, 2.2 Amps. Overall size 1/2" x 4 1/2" x 4 1/2". Wheel size 5/8" dia, 3" deep. Removed from new equipment. Wt. 12 lbs. Cat. No. 8185

\$12.50

NEW! DIGITAL CAPACITANCE METER KIT

5 Ranges! Measure any capacitor value from 100 pF to 10,000 uF! Five ranges: 0-1uF, 10uF, 100uF, 1000uF, 10000uF. Also tests leakage! Directly reads all types of capacitors at the touch of a button. Easy to assemble! Complete kit, nothing else required. With step-by-step instructions. Size 6" x 2 1/4" x 5 1/4" deep, vinyl covered wooden cabinet. Wt. 2 lbs.

Cat. No. 5238 Capacitance Meter Kit **\$69.95**
Cat. No. 5239 Capacitance Meter Wired **\$95**

• You've seen it at twice the price!

RIBBON CABLE AT THIN PRICES

Ultra Heat! 28 AWG

Cond	Size	Price	Order by Cat.
25	4 ft. \$1.99	40	3 ft. \$1.98
26	4 ft. \$1.98	50	2 ft. \$1.98
27	4 ft. \$1.98	60	2 ft. \$1.98

SANYO AUDIO AMPLIFIER MODULES

Easy to build a complete audio amplifier for hi-fi, tape, AM, FM, PA, and more! Response 20-20,000 Hz, less than .5% distortion at full power. Efficient heat radiating construction. Output 60ma. Size 3 1/2" x 2 1/2" x 1 1/2" deep. Approx. Wt. 8 oz. With instructions.

Cat. No.	Type	Watts-RMS	Sale
5350	STK-009	13	\$8.98
5351	STK-013	15	\$11.98
5352	STK-028	20	14.98
5353	STK-054	30	14.98
5354	STK-050	50	26.98
5355	STK-014	15x2	18.98

BARGAIN PRICED ONE-LINE SPECIALS

- ULTRASONIC TRANSDUCER, 42kHz, alarm, remote cont. (#5375) 1.49
- DYNAMIC MIKE, 500 ohm impedance, with stand. (#5330) 1.85
- LED RAY DIODES, emits coherent beam, 5-9W. (#3508) 6.88
- LED DRIVER IC'S, 18A contacts, SPDT, 700 ohms (#4032) 1.00
- RED DISC SPECIAL, Eris, mostly marked, pop value (#5341) 1.50 for 2.00
- LONG LEAD DISC CAPACITORS, pop values, asstd. (#2598) 100 for \$2.00
- TRANSISTOR LYTICS, asst. pop values, upright, axial. (#2747) 50 for \$2.00
- MOLEX IC SOCKET PINS, cut to any length. (#3144) 200 for \$2.00
- 5 VOLT BATTERY 500's, asst. pop values & capacitance (#3360) 40 for \$2.00
- JUMBO RED LEADS, 100% prime, long leads. (#3369) 15 for \$2.00
- LINE CORDS, 18ga, 2 cond, with plug, 5 ft. (#3843) 8 for \$2.00
- NCD DIMMER SURPRISE! screws, nuts, washers, and more. (#3987) 500 pc for \$2.00
- TUBULAR CAPACITORS, asst. values, 100 uF (#3821) 30 for \$2.00
- COILS AND CHOKES, RF, AF, osc. peaking, and more. (#35A227) 40 for \$1.00
- RCA PLUGS & JACKS, for audio, RF, etc. (#35A402) 18 for \$1.00
- SLIDE SWITCHES, pop types, from SPST up. (#1495) 20 for \$1.00
- 1N4148 SWITCHING DIODES, like 1N914, 100% prime. (#3000) 20 for \$1.00
- UTILITY AC OUTLET, ract mounting. (#3882) 8 for \$1.00
- 1 AMP CIRCUIT BREAKERS, glass, thermal. (#3905) 2 for \$1.00
- CAPACITOR SPECIAL, 1/2 watt, 100 uF (#2738) 100 for \$2.00
- VOLTAGE REGULATORS, hobby LM320, 340, TO-3 (#3330) 10 for \$2.00
- PANEL SWITCHES, slides, rotaries, med. etc. (#3288) 30 for \$2.00
- RESISTOR SPECIAL, 1/4 to 1W, carbon, metal (#3084) 200 for \$2.00
- WALF WATTERS, resistors, 1/4, 1/2, 1W (#3082) 200 for \$2.00
- NATIONAL IC BONANZA, linear, 7400s ROMS (#2860) 100 for \$2.00
- LM340T VOLTAGE REGULATORS, 5 to 24V, TO-220 (#2638) 18 for \$2.00
- POD YETI/TREME CAPS, asst'd values, voltage, hi-Q. (#2728) 100 for \$2.00
- BRIDGES, untested, 2, 4, 8, 16, 32, 64, 128, 256 (#2852) 20 for \$2.00
- MIXED READDUTS, hobby, untested, 127, 3, 5, etc. (#3618) 15 for \$2.00
- QUARTER WATTERS, resistors, metal film, marked (#3413) 180 for \$2.00
- PLASTIC TRANSISTORS, untested, TO-92 (#2604) 100 for \$2.00
- CONDENSER MIKES, 1/4, 1/2, 1W, 15k, 2k marked (#2428) 200 for \$2.00
- PRECISION RESISTORS, 1/4, 1/2, 1W, 15k, 2k marked (#2428) 200 for \$2.00
- DIPPED MYLARS, shiny finish, asst'd values (#2887) 60 for \$2.00
- VOLUME CONTROLS, audio, linear, asst'd values (#2421) 30 for \$2.00
- CONFORMER RESISTORS, 1/4, 1/2, 1W, 15k, 2k marked (#2428) 200 for \$2.00
- MMS262 2K RAMS, hobby, untested (#3940) 30 for \$2.00
- PUSH SWITCHES, push-to-break, spst, alarm (#3289) 10 for \$2.00
- CD-4000 SERIES CMOS, untested, 50% useable yield (#5284) 25 for \$2.00
- UNMARKED CAPACITORS, polystyrene, molded, pop values (#3805) 250 for \$2.00
- IC SOCKETS, 14, 16 pin, solder tail. (#3821) 8 for \$2.00
- PC TRIM POTENTIOMETERS, thumbwheel, screwdriver asst. (#3345) 30 for \$2.00
- UPRIGHT ELECTRY, asst'd values, dual, singles (#3087) 75 for \$2.00
- CRYSTALS, may include CB, Ham & more. (#250) 10 for \$2.00
- TERMINAL STRIPS, from 2 lugs up to (#3136) 100 for \$2.00
- NE-ZEON LAMPS, all 100% good (#2813) 30 for \$2.00
- COIL INDICATORS, 1 cond, mikes, phones. (#3877) 40 for \$2.00
- SOUND TRIGGER, sound trigger, asst. values (#5081) 3 for \$2.00
- VEEDER ROOP, counter, 000-999, retestable, panel mt. (#5081) 1 for 1.49
- DUAL GATE MOSFET, sim. to 3M200, 3M187, for RF & Mixer (#5101) 2 for 1.00
- UPRIGHT ELECTRY, asst'd values, dual, singles (#3087) 40 for \$2.00
- JOYSTICK, four 100K, 300K, 500K, 1M (#5195) 1 for 2.95
- ECD THUMBWHEEL SWITCH, BCD, 0-7 (#2870A) 1 for 1.49
- PLESSEY TV SIDE BAND FILTER, for chan. 3 or 4 (#3975) 1 for 1.95
- WET-CELL CHARGER PAK, plug-in, 125ma, 125 VAC pin (#4098) 2 for 1.49
- DATA ENTRY PUSH-BUTTONS, spst, norm open, for keyboard (#5278) 75 for \$2.00
- SN7400 TTL ICs, untested 50%+ yield, pop types (#2415) 75 for \$2.00
- MINI DIP ICs, linear, untested 80%+ yield, pop types (#3245) 100 for \$2.00
- LM340T ICs, 2 watts on-a-dip 50%+ yield (#5284) 30 for \$2.00
- LINEARS, OP AMPS, untested 50%+ yield, pop types (#3228) 75 for \$2.00
- LED WATCH GUTS, men's, how good? We don't know (#5287) 1 for 1.95
- SLIDE SWITCHES, asst pop styles (#1495) 10 for \$1.00
- PREFORMED DISC CAPACITORS, marked values, asst'd (#2605) 150 for \$2.00
- CALCULATOR KEYBOARDS, 20 keys up to (#5371) 10 for \$2.00
- ALARM WARNING STICKERS, for windows, 2 3/4" x 3" (#8338) 3 for 1.00
- IC SOCKET SWITCHES, SPST-M.O., asst'd, 4" sq. (#3524) 10 for \$1.00
- IT'S A DIGIT COUNTER, 110VAC, with mounting (#5382) 1 for 1.95
- 2M389 TRANSISTORS, NPN switch, like 2N2222. (#1992) 6 for 1.00
- FACTORY REJECT DIODES, geners, ract, signal, untested (#5369) 2000 for \$1.00

DISCRETE LED CLOSEOUT

6 for \$1

Cat. No.	Description
#2135	Jumbo Red
#2790	Jumbo Red Clear
#1944	Jumbo Yellow
#2134	Jumbo Green
#2793	Jumbo Amber
#2137	Micro Red
#1948	Micro Yellow
#2135	Micro Green
#2143	Micro Amber
#1788	Micro Top-hat Red
#1802	Micro single pin Red

Order in multiples of 6 of each type.

MOTOR SPEED CONTROL "BASIC" KIT

Controls up to 10 Amps, 1000 watt! Works with noninductive type motors and incandescent lights. Variety from 5K to 95% Wt. 10 oz. Cat. No. 5327

*Basic kits include all necessary electronic components, less PCB board, case, line cord, transformer, battery. Easy to breadboard, with instructions.

\$2.95

GIANT MINI TOGGLE SWITCHES

SALE! 3A 125VAC contacts or better!

Cat. No.	Contacts	Sale
4036	SPDT	89c
4037	DPDT	99c
5422	DPDT	1.29
5434	3PDT	1.49
5087	4PDT	1.95

*center off

1N4000 EPOXY RECTIFIERS

Cat. No.	Type	PIV	Sale
2377	1N4001	50	10 for .49
2378	1N4002	100	10 for .59
2379	1N4003	200	10 for .69
2380	1N4004	400	10 for .89
2381	1N4005	600	10 for 1.09
2382	1N4006	800	10 for 1.49

BLOCK FANS \$9.95

For cooling, flushing, heating and ventilating! Quiet & dependable! Lightweight, flame retardant, 3 blades or better (sorry, no choosing). Removed from new equipment. Ship wt. 1 1/2 lbs. Cat. No. 920198

*Famous USA Makers! - 4-11/16" sq. 1 1/2" deep.

30 WATT STEREO AMPLIFIER KIT \$24.95

Easy to build, assembles in minutes. Uses two 15 watt Hybrid Amplifier Modules with heat sink included! Power output 2 x 15W RMS, both channels into 8 ohms from 40-22,000 Hz. Total distortion less than 1%. Size: 6 1/2" x 3 1/2" x 1 1/2". Wt. 1 lb. Cat. No. 5408 Made For Fisher.

POCKET VOM \$8.88

1% precision resistors, D'Arsonval movement with burnout protection. Measures DC volts 0-15-150-1000, AC Volts 0-15-150-1000, DC Current 0-150mA; Resistance X1000 ohms. Sensitivity 1000 ohms per volt AC/DC. Uses AA penlight cell, not included. Size: 2 3/8" x 3 1/2" x 1 3/8". Wt. 6 oz. Cat. No. 3921

FREQUENCY COUNTER PRESCALER KIT \$24.95 kit

Fits inside our Frequency Counter Cabinet. Requires frequency counter! Works with all frequency counter! Extends range to 500 MHz!

Cat. No. 5215 PRESCALER **\$24.95** kit
Cat. No. 5225 PRESCALER **\$24.95** W/LED \$34.95

MICROPROCESSORS! MEMORIES! SUPPORT!

Order by Cat. No. 3459 and type

8008 7.95	8259 19.95
8080A 9.95	2102-L1 11.95
8212 3.50	1103 .79
8214 7.95	MM5260 .99
8216 3.50	MM5262 .39
8224 3.50	MM5280* 3.95
8228 6.95	MM4200P-11 3.95
8238 7.95	MM4096 3.95
8251 9.95	MM4116 19.95
8253 19.95	1702A 4.85
8255 19.95	MM5202 2.95
8257 19.95	2708 10.95

SOLAR ENERGY DISCS

Converts sunlight directly to electricity! All discs 0.5VDC. Add in series or parallel for higher voltages and amperages.

Cat. No.	Size	mA	Sale
6046	2"	500	3.95
8211	2 1/2"	500	8.50
3862	3"	1000	8.88
3078	3 1/2"	1500	10.95
5785	4"	1500	12.95

FULL WAVE BRIDGE RECTIFIERS

PIV	2 AMP	6 AMP	10 AMP	25 AMP
50	.59	.88	1.29	1.59
100	.99	.99	1.49	1.79
200	1.29	1.50	1.65	2.29
400	1.99	1.99	2.25	3.49
600	.99	1.75	2.25	3.79
800	1.19	1.95	2.90	4.90

8 DIGIT FREQUENCY COUNTER \$77

Easy to read 35' led digits, dependable MOS/LSI circuitry. Quartz crystal controlled for high accuracy! Displays internal frequency standard at the touch of a button. Built in power supply! Flip top black vinyl covered wooden cabinet for easy access.

• More features for the money!
• Easy to assemble and calibrate!

Specifications: SENSITIVITY: 25Hz to 35 MHz, 50 mV to 50 MHz. FREQ. RANGE: 10Hz to 30MHz. optional prescaler to 500 MHz. RESOLUTION: 1 Hz @ 1 sec, 10 Hz @ 10 sec. GATE TIMES: 1 and 0.1 sec. INTERNAL FREQUENCY STANDARD: 5.24288 MHz. Cat. No. 4049 COUNTER KIT... \$77. Cat. No. 4050 COUNTER WIRED & CALIBRATED... \$112. Cat. No. 8433 COUNTER WITH PRESCALER WIRED & CALIBRATED... \$150.

LINEAR "POP" OP AMPS

Type	Each	Price
LM300N	.49	#N556H .99
LM300	.49	#N556V .29
LM301V	.25	#N561H 1.99
LM301H	.25	#N565H .89
LM307V	.25	#N565V 1.20
LM308V	.29	#N567V 1.99
LM308H	.59	LM702H .39
LM309K	.99	LM704H .19
LM311V	.29	LM709H 1.99
LM312V	.49	LM710H .29
LM322N	.79	LM711H .39
LM322H	.59	LM723H .49
LM324H	.59	LM733H .59
LM339H	.99	LM741V .19
LM339V	.99	LM741H .18
LM340K-5V	.99	LM747H .39
LM340K-12V	.99	LM1304H .99
LM340K-15V	.99	LM709H 1.99
LM340K-18V	.99	MC1312H 2.48
LM340K-24V	.99	LM1414V .48
LM340T-5V	.99	LM1468V .29
LM340T-6V	.99	LM709H 1.99
LM340T-12V	.99	LM3028H .89
LM340T-15V	.99	LM3900H .29
LM340T-18V	.99	LM3909V .69
LM340T-24V	.99	LM3909H .69
LM350N	.75	78A51 .29
LM377N	1.49	78A53 .29
LM379S	5.50	75A91 .49
LM380H	.89	78A94 .69
NE531H	1.49	78A96 .69
PA283	2.50	PA283 .77
NE540H	2.50	DM8844 .99
NE555V	3.50	

Order by Type No. Case code: T-TO-220 Power Tab. V=Mini dip, K-TO-3, H=TO-5, N=DIP.

DIP SWITCHES

Cat. No.	Switches	Sale
3669	3	.77
3021	4	.99
2977	7	1.79
3672	8	1.99
3672	10	2.50

Send for new FREE 20 page catalog

including the best bargains on:

- SEMICONDUCTORS
- Computer Components
- Over 400 assortments
- Digital clocks and test equipment
- Hi-Fi stereos, speakers
- Solar Energy
- Fiber Optical
- Plus more-moral
- LED'S

SEND FOR YOURS NOW!

POLY PAKS®

CODES MAY BE PHONED!

P.O. BOX 942-R11
S.O. LYNNFIELD, MA 01940

Terms: Add Postage. Rated: Net 30
Phone: (617) 245-3828
Retail: 16-17 Del Carmine St.
MINIMUM ORDER: \$8 Wakefield, MA

ORDERING INSTRUCTIONS:
When ordering, always use catalog number, type no., the name of the magazine you are ordering from and the month.

SALE S-100 BUS EDGE CONNECTORS SALE

NLS MS-215 DUAL TRACE MINISCOPE \$435.00

NLS
1c SALE

LM3A 3 dig 1% DC \$134.00
LM3.5A 3 1/2 dig .5% DC \$158.50
LM40A 4 dig .1% DC \$209.00
LM4A 4 dig .03% DC \$250.00

- Rechargeable batteries and charger included
- Measures DC Volts, AC Volts, Ohms and Current
- Automatic polarity, decimal and overload indication
- Rechargeable batteries and charger
- Measures DC Volts, AC Volts, Ohms and Current
- Automatic polarity, decimal and overload indication
- No zero adjustment and no full-scale ohms adjust
- Battery-operated — NiCad batteries; also AC line operation.
- Large LED display for easy reading without interpolation
- Size: 1.9" H x 2.7" W x 4" D
- Parts & labor guaranteed 1 year
- Tilt stand option \$ 3.50
- Leather case \$20.00

Purchase any of the LM series Meters and buy the LEATHER CASE for 1c

NLS
\$318.

MS-15 MINISCOPE
With Rechargeable Batteries & Charger Unit

- 15 megahertz bandwidth
- External and Internal trigger
- Time base — 1 microsec. to 0.5 Sec/div - 21 settings ±3%
- Battery or line operation
- Automatic & line sync modes
- Power consumption < 15 watts
- Vertical Gain — 01 to 50 Divid - 12 settings ±3%
- Viewing area 1.1" x 1.25"
- Case Size 2.7" H x 6.4" W x 7.5" D, 3 pounds
- Parts & Labor guaranteed 1 year
- 100 to 10 meg probe
- Leather carrying case

PROBE 1c
PROBE 1c with the purchase of SCOPE and the MENTION of this MAGAZINE

MS-215 Dual Trace Version of MS-15 \$435.

3 LEVEL GOLD WIRE WRAP SOCKETS

	1-24	25-49	50-99	100-249	250-999	1K-5K
8 pin*	.41	.38	.35	.31	.27	.23
14 pin*	.39	.38	.36	.32	.29	.27
16 pin*	.43	.42	.39	.35	.32	.30
18 pin	.63	.58	.54	.47	.42	.36
20 pin	.80	.75	.70	.63	.58	.53
22 pin*	.90	.85	.80	.70	.61	.57
24 pin	.90	.84	.78	.68	.63	.58
28 pin	1.10	1.00	.90	.84	.76	.71
40 pin	1.50	1.40	1.30	1.20	1.04	.89

Sockets purchased in multiples of 50 per type may be combined for best price.

All sockets are GOLD 3 level closed entry * End and side stackable. 2 level, Solder Tail, Low Profile, Tin Sockets and Dip Plugs available. CALL FOR QUOTATION

SALE S-100 BUS EDGE CONNECTORS SALE

5100-WWG 50/100 Cont. 125 circ. 3 LEVEL WIRE WRAP 025 pin posts on 250 spaced rows. GOLD plated
 1-4 5-9 10-24
 \$4.00 \$3.75 \$3.50

\$100-STG 50/100 Cont. 125 circ. DIP SOLDER TAIL on 250 spaced rows for VECTOR and MASI motherboards. GOLD plated
 1-4 5-9 10-24
 \$4.00 \$3.75 \$3.50

R881-G 50/100 Cont. 125 circ. DIP SOLDER TAIL on 140 spaced rows for ALTAIR motherboards. GOLD plated
 \$6.00

R881-3 50/100 Cont. 125 circ. PERCED SOLDER EYELET TAIL
 GOLD \$7.35

R664-G 22/44 Cont. 156 circ. PERCED SOLDER EYELET TAIL. GOLD plated
 1-4 5-9 10-24
 \$3.00 \$2.75 \$2.50

R664-3 22/44 Cont. 156 circ. WIRE WRAP TAIL. GOLD
 \$4.71

Other Popular Edge Connectors

R664-G 22/44 Cont. 156 circ. PERCED SOLDER EYELET TAIL. GOLD plated
 1-4 5-9 10-24
 \$3.00 \$2.75 \$2.50

ATTN: OEM'S and Dealers, many other connectors available call or quotation.

8803 MOTHER BOARD FOR S100 BUS MICRO-COMPUTERS

• Kit includes: 12 bareboard capacitors for +5, +12, -12 buses and miscellaneous mounting spacers
 • Wiring side shown. Component side bare epoxy glass with white markings for component locations
 • 610 battery glass board with 2 ounce copper, solder plated and 138 jumper holes for leads
 • Solder mask with solder windows on critical circuits to avoid accidental shorts
 • Mounts 11 receptacles with 100 contacts (2 rows) - 125 entries with .250 row spacing. Vector part number R681-2; or mounts 10 receptacles plus interconnections to smaller mother board for expansion
 • Includes etched circuits and instructions for optional active pull up, or floating terminations
 • Large traces - 50 mil and 100 mil (10 AMP), 1/2 inch or 1/4 inch (1 AMP). Current ratings are per MIL-STD-275 with 10% rise
 • Fits in Vector case enclosure
 • Fits in IMSA1-8080 microcomputer as expansion board

Price: \$29.50

Vector

8800V Universal Microcomputer/processor plugboard, use with S-100 bus. Complete with heat sink & hardware. 5.3" x 10" x 1.16"

1-4	5-9	10-24
\$19.95	\$17.95	\$15.95

8801-1
Same as 8800V except plain; less power buses & heat sink.

1-4	5-9	10-24
\$14.95	\$13.46	\$11.96

Plugboards

3682 9.6" x 4.5"
\$10.97

3682-2 6.5" x 4.5"
\$9.81

Hi-Density Dual-In-Line Plugboard for Wire Wrap with Power & Grd. Bus Epoxy Glass 1/16" x 44 pin con. spaced .156

3677 9.6" x 4.5"
\$10.90

3677-2 6.5" x 4.5"
\$9.74

Gen. Purpose D.I.P. Boards with Bus Pattern for Solder or Wire Wrap Epoxy Glass 1/16" x 44 pin con. spaced .156

3662 6.5" x 4.5"
\$7.65

3662-2 9.6" x 4.5"
\$11.45

P pattern plugboards for IC's Epoxy Glass 1/16" x 44 pin con. spaced .156

3690-12 CARD EXTENDER
Card Extender has 100 contacts-50 per side on 125 centers-Attached connector is compatible with S-100 Bus Systems.....\$25.00
3690 6.5" x 22/44 pin .158 ctrs. Extenders.....\$12.00

1/16" Vector BOARD
.042 dia holes on 0.1 spacing for IC's

Phenolic

PART NO.	SIZE	1-9	10-19
64P44XXX	4.5x6.5"	\$1.49	1.34
169P44XXX	4.5x17"	\$3.51	3.16

Epoxy Glass

64P44	4.5x6.5"	\$1.70	1.53
84P44	4.5x8.5"	\$2.10	1.89
169P44	4.5x17"	\$4.30	3.87
169P84	8.5x17"	\$7.65	6.89

SLIT-N-WRAP
Wraps insulated wire on .025" square posts **FOUR TIMES FASTER** than regular manual wrap-post tools

P180
With two 100' spools of 28 ga. wire
\$24.50

P180-4C
Includes charger, wire, 100' spools
\$75.00

SLIT-N-WRAP WIRE
NO 28 GAGE INSULATED WIRE, 100' SPOOLS
W28-2-Pkg. 3. Green W28-2-C-Pkg. 3. Clear W28-2-B-Pkg. 3. Red W28-2-D-Pkg. 3. Blue

2708 8K 450 ns

EPROM FACTORY PRIME \$9.00 EA.
25 + Call For Price

14 & 16 PIN GOLD 3 LEVEL WIRE WRAP SOCKETS

14 - G3 100 for \$30.00
 16-G3 100 for \$30.00
 50 of each for \$32.00

Sockets are End & Side stackable, closed entry

LIQUID CRYSTAL DIGITAL CLOCK-CALENDAR

- For Auto, Home, Office
- Small in size (2x2 1/4 x 1 1/4)
- Push button for seconds release for date
- Clocks mount anywhere with either 3M double-sided tape or VELCRO, included.
- 2 MODELS AVAILABLE
- LCD-101, portable model runs on self-contained batteries for better than a year.
- LCD-102, runs on 12 Volt system and its back lighted.
- LCD-101 or LCD-102 your choice

\$34.95
\$2.00

• Clear desk stand for

LEDU MG 10A
List \$72. **SPECIAL \$44.95**

Perfectly balanced, fluorescent lighting with precision magnifier lens. For prof'l, techn' & hobbyist. Has die cast protective shade, inst. start 3 dioper lens, 42" reach.

\$44.95

With 10 fluorescent lamps (included)
 \$45.95
 Colors: Green or Black
 Chocolate Brown
 2 choice please

SC-5 With Rechargeable Batteries & Charger Unit \$98

Features include: • By using the new NLS SC-5 Prescaler, the range of the FM-7 Frequency Meter, which is 10 Hz to 50 MHz, may be extended to 512 MHz (the upper VHF & UHF frequency bands). • The FM-7 utilizes an LED readout, providing 7-digit resolution. • The FM-7 can be calibrated to an accuracy of 0.00001%. • The SC-5 is accurate to one part per million. • Each unit has 30 millivolt sensitivity, is battery powered and has a charger unit included. • Dimensions of each are 1.9" H x 2.7" W x 3.9" D. • The units may be obtained separately or as a "Frequency Duo." • Parts & Labor guaranteed 1 year.
 Tilt stand option \$ 3.50
 Leather case \$20.00

MICRO-KLIP
for .042 dia. holes (all boards on this page)
 T42-1 pkg. 100 \$ 1.50
 T42-1 pkg. 1000 \$11.00
 P-149 hand installing tool \$ 2.03

8" LED ALARM CLOCK
12 hr. LED Alarm Clock uses 3 1/2 digit 8" LED Display with AM/PM indicators and colons. Direct drive. PIN to PIN interface with **ST998A** I.C. Just add switches. AC Supply Alarm. Display and I.C. only.
\$7.95 or 2/\$15.00

Price Breakthrough! \$17.50

MA1003 CAR CLOCK
Bright Green Fluorescent Display Crystal Time Base Assembled, just add switches and 12 VDC.

SPECIAL
14CS2 100 for \$14.00
16CS2 100 for \$16.00
 14 pin CS2 10 for \$2.00
 16 pin CS2 8 for \$2.00

These low cost DIP sockets will accept both standard width plugs and chips. For use with chips, the sockets offer a low profile height of only .125" above the board. These sockets are end stackable.

PRIORITY ONE ELECTRONICS
 10031 S' Woodley Ave. Sepulveda CA. 91343

Terms: VISA, MC, BAC, check, Money Order, C.O.D., U.S. Funds Only. CA residents add 6% sales tax. Minimum order \$10.00. Orders less than \$75.00 include 10% shipping and handling, excess refunded. Just in case please include your phone no. **"Sorry, no over the counter sales."** GOOD THRU NOVEMBER 1978

Send for our latest brochure. phone orders welcome (213) 893-8202 OEM and Institutional inquiries invited.

24 PIN DIP PLUGS WITH COVERS
 3 / \$1.00
 40 / \$10.00

SALE S-100 BUS EDGE CONNECTORS SALE

Logic Probes and Digital Pulsers



LOGIC PROBES

CSC logic probes are the ultimate tool for breadboard design and testing. These hand-held units provide an instant overview of circuit conditions. Simple to use, just clip power leads to circuit's power supply, set logic family switch to TTL, DTL or CMOS (HTL). Touch probe to test node. Trace logic levels and pulses through digital circuits. Even stretch and latch for easy pulse detection. Instant recognition of high, low or inactive levels, open circuits and nodes. Simple, dual-level detector LEDs tell it quickly, correctly. HI (Logic "1"); LO (Logic "0"). Also incorporates blinking pulse detector, e.g., HI and LO LEDs blink on or off, tracking "1" or "0" states at square wave frequencies up to 1.5 MHz. Pulse LED blinks on for 1/4 second during pulse transition. Choice of three models to meet individual requirements: budget, project and speed of logic circuits.

MODEL LP-1

Hand-held logic probe provides instant reading of logic levels for TTL, DTL, HTL or CMOS. **Input Impedance:** 100,000 ohms. **Minimum Detectable Pulse:** 50 ns. **Maximum Input Signal (Frequency):** 10 MHz. **Pulse Detector (LED):** High speed train or single event. **Pulse Memory:** Pulse or level transition detected and stored.

CSC Model LP-1 Logic Probe—Net Each \$44.95

MODEL LP-2

Economy version of Model LP-1. Safer than a voltmeter. More accurate than a scope. **Input Impedance:** 500,000 ohms. **Minimum Detectable Pulse:** 300 ns. **Maximum Input Signal (Frequency):** 1.5 MHz. **Pulse Detector (LED):** High speed train or single event. **Pulse Memory:** None.

CSC Model LP-2 Logic Probe—Net Each \$24.95

MODEL LP-3

High speed logic probe. Captures pulses as short as 10 ns. **Input Impedance:** 500,000 ohms. **Minimum Detectable Pulse:** 10 ns. **Maximum Input Signal (Frequency):** 50 MHz. **Pulse Detector (LED):** High speed train or single event. **Pulse Memory:** Pulse or level transition detected and stored.

CSC Model LP-3 Logic Probe—Net Each \$89.95

DIGITAL PULSER

The ultimate in speed and ease of operation. Simply connect clip leads to positive and negative power, then touch DP-1's probe to a circuit node; automatic polarity sensor detects circuit's high or low condition. Depress the pushbutton and freeze an opposite polarity pulse into the circuit. Fast troubleshooting includes injected signals at key points in TTL, DTL, CMOS or other popular circuits. Test with single pulse or 100 pulses per second via built-in digital circuits. **Output:** Tristate. **Polarity:** Pulse-sensing auto-polarity. **Sync and Source:** 100 mA. **Pulse Train:** 100 pulses. **LED Indicator:** Flashes for single pulse; stays lit for pulse train.

CSC Model DP-1 Digital Pulser—Net Each \$74.95

PROTO-BOARD[®] UNITS

All the speed and convenience of QT Sockets and Bus Strips in both kits and preassembled units. Assemble, test and modify circuits literally as fast as you can think.

PROTO-BOARD 6 KIT

Contains one preassembled QT-47S socket, two preassembled QT-47B bus strips, four 5-way binding posts, metal ground/base plate, non-marring feet and all hardware. Ten minute assembly time. **Size:** 6" x 4.5" w. x 1.4" h. **Weight:** 7 ozs.

CSC Model PB-6 Kit—Complete. List Price \$15.95

PROTO-BOARD 100 KIT

Contains two preassembled QT-35S sockets, one preassembled QT-35B bus strip, four 5-way binding posts, metal ground/base plate, non-marring feet and all hardware. Ten minute assembly time. **Size:** 4.5" w. x 6" l. x 1.4" h. **Weight:** 7.5 ozs.

CSC Model PB-100 Kit—Complete. List Price \$19.95

PROTO-BOARD 101

Fully assembled breadboard contains two QT-35S sockets and four QT-35B bus strips mounted on metal ground/base plate with non-marring feet. Excellent for audio and small digital projects. **Size:** 5.8" l. x 4.5" w. x 1.4" h. **Weight:** 9 ozs.

CSC Model PB-101 Breadboard—Complete. List Price \$24.95

PROTO-BOARD 102

Fully assembled breadboard contains two QT-47S sockets, three QT-47B bus strips and one QT-35B bus strip on a metal ground/base plate with non-marring feet. Excellent for intermediate digital needs. **Size:** 7" l. x 4.5" w. x 1.4" h. **Weight:** 10 ozs.

CSC Model PB-102 Breadboard—Complete. List Price \$26.95

PROTO-BOARD 103

Fully assembled breadboard contains three QT-59S sockets, four QT-59B and one QT-47B bus strips, four 5-way binding posts on a metal ground/base plate with non-marring feet. Build calculators, interfaces, networks, etc. **Size:** 9" l. x 6" w. x 1.4" h. **Weight:** 1 1/4 lbs.

CSC Model PB-103 Breadboard—Complete. List Price \$59.95

PROTO-BOARD 104

Fully assembled breadboard contains four QT-59S sockets, seven QT-59B bus strips and four 5-way binding posts on a metal ground/base plate with non-marring feet. Build a CPU, encoder, complex display, etc. **Size:** 9.8" l. x 8" w. x 1.4" h. **Weight:** 1 1/2 lbs.

CSC Model PB-104 Breadboard—Complete. List Price \$54.95

PROTO-BOARD 203

Fully assembled breadboard contains built-in, short-proof, fused, 5 VDC at 1 amp, regulated power supply. In addition to three QT-59S sockets, four QT-59B bus strips, one QT-47B bus strip and four 5-way binding posts. Capacity for most digital and many analog projects. **Size:** 9.75" l. x 6.8" w. x 3.25" h. **Weight:** 5 lbs.

CSC Model PB-203 Breadboard—Complete. List Price \$75.00

PROTO-BOARD 203A

Provides all the features of Proto-Board 203 with additional +15 and -15 VDC at 0.5 amp power supplies with internally adjustable output voltages. **Size:** Same as PB-203. **Weight:** 5.5 lbs.

CSC Model PB-203A Breadboard—Complete. List Price \$124.95

LOGIC MONITOR 1

Trace signals through all types of digital circuits. Unit clips over any DIP IC up to 16 pins. Each of its 16 contacts connects to a single-bit level detector that drives a high-intensity, numbered LED readout activated when the applied voltage exceeds a fixed 2 V threshold. Logic "1" turns LED on; logic "0" keeps LED off. A power-seeking gate network automatically locates supply leads and feeds them to the LM-1's internal circuitry. Saves minutes, even hours in design, troubleshooting, debugging or equipment.

Voltage Threshold: 2 V ± 0.2 V. **Input Impedance:** 100,000 ohms. **Input Voltage Range:** 4-15 V max. across any two or more inputs. **Current Drain:** 200 mA at 10 V. **Size:** 4" l. x 2" w. x 1.75" d. when open. **Weight:** 3 ozs.

CSC Model LM-1 Logic Monitor—Complete. List Price \$59.95

LOGIC MONITOR 2

Provides greater versatility and precision in testing all types of digital circuits. The fully isolated power supply and selectable trigger threshold let you match the precise characteristics of the logic family under test, permitting more accurate measurements. The connector display unit clips over any DIP IC up to 16 pins. The power supply module contains the precision reference power supply and logic family selector switch. Operation is simple. Set the threshold switch to the proper logic family. Connect black clip lead to circuit ground. For CMOS circuitry, the red clip is connected to circuit positive or Vcc. The clip module is then clipped over the IC and the LED display instantly gives the logic states of all pins. **Logic Thresholds:** CMOS, 70% of circuit Vcc; TTL, 7.5 V; HTL, 2.4 V; DTL, 1.6 V; RTL, 1.2 V. **Maximum Visible Input Frequency:** 30 MHz at 50% duty cycle. **Size:** 4" l. x 2" w. x 1.75" d. when open. **Power Module:** 6" w. x 5.63" d. x 3" h. max. **Total Weight:** 20 ozs. **Power Required:** 117 VAC, 50/60 Hz, 10 W; also available for 220 VAC, 50/60 Hz at slightly higher price.

CSC Model LM-2 Logic Monitor—Complete. List Price \$129.95


MAX-100 PORTABLE FREQUENCY COUNTER

MAX-100 is a portable, high precision frequency counter that sets new standards in performance and value. In a compact, portable case, it gives you continuous readings from 20 Hz to a guaranteed 100 MHz, with 8-digit accuracy. Fast readings with 1/2-sec update and 1-sec. sampling rate. Precise readings, derived from a crystal-controlled time base with 3 ppm accuracy. High-sensitivity readings from signals as low as 30 mV, with diode overload protection up to 200 V peaks. Input signals over 100 MHz automatically flash the most significant digit, and to indicate low-battery condition and extend battery life, the entire display flashes at 1 kHz.

SPECIFICATIONS

Frequency Range: 20 Hz to 100 MHz guaranteed; 110 MHz typical. **Gate Time:** 1 sec. **Resolution:** 1 Hz. **Accuracy:** ±1 count + time base error. **Input Impedance:** 1 megohm shunted by 56 pF. **Coupling:** AC. **Sine Wave Sensitivity:** 30 mV RMS at 50 MHz. **Internal Time Base Frequency:** 3.579545 MHz crystal oscillator.

Digital IC Testers

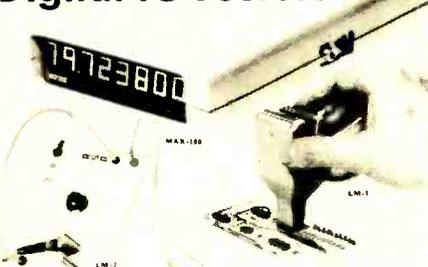

Stability: ±3 ppm at 25° C. **Temperature Stability:** Better than 0.2 ppm/°C, 0-50° C. **Max. Aging:** 10 ppm/year. **Display:** Eight 0.6" LED digits. **Lead-Zero Blanking:** Decimal point appears between 6th and 7th digit when input exceeds 1 MHz. **Overflow:** With signals over 99,999,999 Hz, most significant (left hand) digit flashes, allowing readings in excess of 100 MHz. **Display Update:** 1/4-sec. plus 1 sec. Gate time. **Low Battery Indicator:** When battery supply falls below 6.6 VDC, all digits flash at 1 Hz. **Power Required:** Internal, 6 "AA" cells; external, 110 or 220 VAC charger eliminator, auto cigarette lighter adapter or 7.2-10 VDC external supply. **Battery Charging:** 12-14 hrs. **Size:** 1.75" h. x 5.63" w. x 7.75" d. **Weight:** Less than 1.5 lbs., with batteries.

CSC Model MAX-100 Frequency Counter—Net Each \$134.95

MAX-100 ACCESSORIES

- Model 100-CLA Mobile charger/eliminator, Net Each \$ 3.95
- Model 100-CA1 110 VAC charger eliminator, Net Each 9.95
- Model 100-CA2 220 VAC charger eliminator, Net Each 9.95
- Model 100-IPC Input cable with clip leads, Net Each 5.95
- Model 100-LLC Low-loss tap-off, Net Each 14.95
- Model 100-MWA Mini-whip antenna, Net Each 3.95
- Model 100-CC Carrying case, Net Each 9.95

NEW VOLKSMETERS!

With LCD Display—Excellent Readability in Direct Sunlight!

0.5% 3 1/2 digits LM-350 \$144.00*



10% LM-300 Full three digits \$114.00*

FEATURES

- Measures DC volts, AC volts, ohms and current.
- Large LCD display for easy reading without interpolation.
- Automatic polarity, decimal and overload indication.
- Size 1.9" x 2.7" x 4.0" D.
- Parts and labor guaranteed for one year.

SPECIFICATIONS


MODE	RANGE	ACCURACY (1% Max)	RESOLUTION (1% Max)	INPUT IMPEDANCE	OPEN CIRCUIT VOLTAGE
VOLTS DC	10	±1%	0.1 mV	10 MΩ	10 mV
	100	±1%	0.01 mV	10 MΩ	100 mV
	1000	±1%	0.001 mV	10 MΩ	1 V
VOLTS AC	10	±1%	0.1 mV	10 MΩ	10 mV
	100	±1%	0.01 mV	10 MΩ	100 mV
	1000	±1%	0.001 mV	10 MΩ	1 V
RESISTANCE	10	±1%	1 Ω	10 MΩ	100 mA
	100	±1%	0.1 Ω	10 MΩ	10 mA
	1000	±1%	0.01 Ω	10 MΩ	1 mA
CURRENT	10 mA	±1%	100 μA	10 MΩ	100 mA
	100 mA	±1%	10 μA	10 MΩ	10 mA
	1 A	±1%	1 μA	10 MΩ	1 A

- * 1000-ohm or more of maximum resistance.
- * 100 Hz to 1000 Hz AC.
- * True Voltage RMS (1000 Hz Full Scale) 1% to 3% Full Scale, 1% to 3%.
- * LM-350 has 1000-ohm input impedance. Full scale readings are 0.999, 9.99, 99.9, etc.

- Tilt Stand Option: add \$ 3.50
- Leather Case \$ 20.00
- 3AA NiCad-Batteries & Charger \$ 12.00

Standard AA-size batteries provide up to 20 hours of operation. Rechargeable NiCad batteries and charger unit available as optional equipment. Batteries not included.

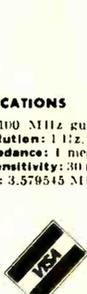Purchase any of the LM series Meters and buy the LEATHER CASE for 1C



PRIORITY ONE ELECTRONICS

10031 S. Woodley Ave., Sepulveda, CA, 91343

Terms: VISA, MC, BAC, check, Money Order, C.O.D., U.S. Funds Only. CA residents add 6% sales tax. Minimum order: \$10.00. Orders less than \$75.00 include 10% shipping and handling, excess refunded. Just in case please include your phone no. "Sorry, no over the counter sales."

Send for our latest brochure


phone orders welcome (213) 893-8202

OEM and Institutional Inquiries Invited.

GOOD NEWS

ETCO BARGAIN BLITZ!

FREE-GIFT!

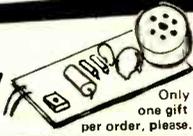

Only one gift per order, please.

WITH EVERY ORDER OF \$10 OR MORE - SOUND ACTIVATED SWITCH!

Intriguing surplus assembly. Microphone picks up sound and drives SCR switch. Ask for 039SU10 or you may order these at 99c each.

For UNUSUAL ITEMS not found in stores or catalogs anywhere, write for our NEW 32 PAGE No. BB BARGAIN IDEA BOOK!

ASSOCIATE DEALERS: Advertiser merchandise available at the following dealers prices may vary.

ETCO ELECTRONICS 183G Hymus Blvd. Pointe Claire, Quebec	ETCO ELECTRONICS 454 McGill St. Montreal, Quebec	ETCO ELECTRONICS Greenfield Park Shopping Center, Greenfield Park, Quebec
---	--	--

DEALERS WANTED: ETCO ELECTRONICS Dealer Division, North Country Shopping Center, Plattsburgh, N.Y. 12901

EVEREADY TRADE MARK
MALLYORY SPECIAL PURCHASE FALL SPECIAL!

ALKALINE PENCIL (SIZE "AA") BUYOUT!

39¢ Reg. 59c

37c ea./10 lots
33c ea./100 lots

Sensational ETCO Purchase - 14,000 in Stock! Mallyory Duracells and Eveready Alkalines! Every cell fully guaranteed. Selling below nationally advertised prices! (2 oz.) 039BA220

THIS IS DIFFERENT \$3.95 100 in stock!

ULTRASONIC HAND TRANSMITTER!

Made for Curtis Mathes, for TV remote control. Push button for burst of ultrasonic energy. Electronic transmitter powered by 9V battery (not included). A nice experimenter item. (8 oz.) 039SU321.

BUY OUT OF SYNCHRONEX RECORD-ONLY CASSETTE MACHINES! \$5.95

Our Reg. Catalog Price \$9.95! Factory Clear-out! Brand new. Intended for use with movie camera. With leather case. Convert to telephone recorder, etc. Uses standard cassettes-play back on any machine. (3 lb.) 039TR499

039TR254 - as above, factory warranty returns for parts value, sold as is. (3 lb.) \$3.95 ea.

4" COOLING FANS! \$1.99 SAVE!

4" fans - ventilate your hi-fi or other electronic equipment with this silent 110 VAC fan. Will prolong life of your gear. (2 lb.) 039ST062 (reg. \$2.95)

overaire COMPENSATED 2.675200 MHz CRYSTAL OSCILLATOR MODULE \$9.95 3/26.95

Very high precision (to Migo spec No. ICC30C122) Overaire No. 67-11-2 (2 oz.) 039SU318.

JUST ARRIVED! A few more of the LESLIE RATING TREMOLOR ORGAN SPEAKERS as advertised in the April 78 issue of Radio-Electronics - 039SP012 (15 lb.) \$49.95

LET'S GET ACQUAINTED

SPECTACULAR NOVEMBER SPECIALS!

039TR818 5" BASF plastic tape storage box (2 oz.)	39c
039JK117 2.5mm ultra mini closed circuit phone jack (1 oz.)	5c
039MS400 3.5mm mini closed circuit phone jack (1 oz.)	7c
039SW040 SP 3 position 3A appliance switch (2 oz.)	9c
039MS117 Silicon treated record cleaning cloth (1 oz.)	13c
039B8288 F15 T5 CW-15 photocoupler bulb (3 oz.)	29c
039SU091 33-transistor Nixie board assembly (3 oz.)	29c
039TE739 Mini vertical "S" meter (2 oz.)	79c
039MS037 Bell-pump "stick" pens (1 oz.)	4c
039MS050 Black marker pens (1 oz.)	9c
039OP120 Intriguing electronic camera shutter (6 oz.)	69c
039BB078 12-volt mini pigtail bulb (1 oz.)	5c
039HD054 Plastic telephone wall plates (4 oz.)	5c
039HP725 Home converter for car stereo c/w speakers (9 lb.)	\$12.95
039RL010 24 VDC SPDT Relay & Brumfield relay (2 oz.)	49c
039HP325 6 VDC 85ma. calculator power supply (10 oz.)	99c
039SU322 SWR meter assemblies - U fix (10 oz.)	\$2.99
039SU234 3 foot cable complete with stereo phone plug (3 oz.)	39c
039SU243 Thermostatic appliance switch (3 oz.)	18c
039SU305 Crazy incandescent digital clock assembly (1 lb.)	\$1.99
039SU308 12 VDC DPDT relay assembly (4 oz.)	\$1.49
039SW159 SPST "in-door" plunger switch (4 oz.)	29c
039TR731 Crazy - 1 minute Fidelity tape cartridge (7 oz.)	99c
039TR781 BASF cassette library storage box (3 oz.)	29c
039TT251 Record player single play turntables (3 lb.)	\$2.49
039PT252 6 ast. precision (marked) transmitting crystals (5 oz.)	99c
039PT214 10 ast. strip volume controls (8 oz.)	\$1.49
039PT124 10 assorted IF transformers (3 oz.)	39c
039PT087 10 assorted selenium rectifiers (2 lb.)	99c
039PT056 Nice assortment of spaghetti tubing (6 oz.)	39c
039PT017 20 assorted wirewound resistors (2 lb.)	69c
039PT011 25 assorted push-on plastic leads (12 oz.)	49c
039PT022 3 transistor audio amplifier (3 oz.)	49c
039MS027 S0239 single hole coaxial socket (2 oz.)	39c
039HP078 6 VDC 30ma. calculator power supply (5 oz.)	99c
039DS178 Philips No. ZC1050 trigger tube (2 oz.)	99c

TUBE SPECIALS!

5Y4	\$1.29	12A6	\$1.69	401A	\$2.89
6AK6	\$2.59	12X4	\$ 99	955	\$1.95
6AL4	\$1.49	274A	\$5.95	6661	\$3.99
6AG6	\$ 99	350B	\$5.95	9696	\$1.49

BARGAIN SCOOP! 4 INCH, 3.2 OHM REPLACEMENT SPEAKER! \$5.95

039SP004 (8 oz.) 10/\$4.99 100/\$42.88

PRICE BREAK! SENSATIONAL ETCO VALUE!

SANGAMO 1.950 - 2.050 H VARIABLE INDUCTANCE! \$9.95

Brand new factory surplus. Bears Sangamo No. CV-246-37800(7114). Permeability tuned variable inductor for PC board mounting. An interesting experimenter and builder item. 2.3mm dia. x 18mm high. (2 oz.) 039MS124.

SPECIAL PURCHASE OF ULTRASONIC ALARMS! \$39.95

Bookshelf design - 12VDC operation. For Rec vehicles. Use at home with battery eliminator. (requires 30 ma.) Operates on 31.5 KHz. Covers 1000 sq. ft. Features: Sensitivity control, normal/memory mode. Jack for remote key switch, output for alarm bell or siren, inputs for remote detector, heat/fire detectors, window/door switch, panic switch; (3 lb.) 039AL058.

3-CHANNEL ULTRASONIC REMOTE CONTROL SET! \$19.95

Regular \$29.95! Brand new factory surplus! Matched pair. Hand unit has 3 buttons, on/off, VHF/UHF channel. Uses 1.5V battery (not included). Receiver operates on 41.5, 40, 38.5 KHz. 110v operation. Ideal for experimenters-build all sorts of remote control devices. (3 lb.) 039SU323.

EXPERIMENTERS!

BURROUGHS GIANT 15-SEGMENT ALPHA NUMERIC TUBES! \$9.95

Reg. \$1.95! Display full alphabet plus numbers 0-9 Burroughs No. B7971. 2 1/2" high characters. Ultra long life. 170 volt operation. (6 oz.) 039DR377.

ETCO SPECIAL!

5" x 7" - 8 OHM REPLACEMENT SPEAKER \$2.99 SALE

039SP410 (1 lb.) \$2.49 ea./24 lot.

24 HOUR - 7 DAY A WEEK TELEPHONE ORDER SERVICE! Call in your CHARGE CARD Orders at Low Weekend and Evening Rates! Dial: 1-518-561-8700.

DEALER INQUIRIES INVITED

FREE

NOTE: If you have ordered from ETCO previously and your address remains unchanged, you will automatically receive all new catalogs.

BRAND NEW No. BB 32 page catalog packed with electronic bargains and unusual items! Write or circle the information card number below!

ETCO

LIQUIDATORS OF EXCESS ELECTRONIC INVENTORIES

Rush Your Order Today

ETCO ELECTRONICS, North Country Shopping Center, Route No. 9, Plattsburgh, N.Y. 12901.

MERCHANDISE SUBJECT TO PRIOR SALE. Full remittance with each order, please. Money order, Certified check, BANKAMERICARD, VISA, MASTERCHARGE, or CHARGEEX. Add 15% for UPS (or postage) and handling (we refund excess). Please try to bring your order total to \$10 or more. Worldwide export orders solicited. Open account to Government agencies, schools, institutions and triple "A" rated industrial & commercial accounts. Special quotes for quantities. Dealer inquiries invited. N.Y. state residents: Add 7% Sales tax.

7400 TTL

SN7400N	16	SN7473N	35	SN74160N	89
SN7401N	18	SN7474N	35	SN74161N	89
SN7402N	18	SN7475N	59	SN74162N	1.95
SN7403N	18	SN7476N	35	SN74163N	89
SN7404N	18	SN7477N	5.00	SN74164N	89
SN7405N	20	SN7480N	50	SN74165N	89
SN7406N	29	SN7482N	99	SN74166N	1.25
SN7407N	29	SN7483N	59	SN74167N	1.95
SN7408N	20	SN7484N	79	SN74170N	89
SN7409N	20	SN7486N	35	SN74172N	6.00
SN7410N	18	SN7488N	1.75	SN74173N	1.25
SN7411N	25	SN7490N	45	SN74174N	89
SN7412N	25	SN7491N	59	SN74175N	79
SN7413N	40	SN7492N	43	SN74176N	79
SN7414N	70	SN7493N	43	SN74177N	79
SN7415N	70	SN7494N	65	SN74178N	1.95
SN7417N	25	SN7495N	65	SN74180N	79
SN7420N	20	SN7496N	59	SN74181N	1.95
SN7421N	29	SN7497N	3.00	SN74182N	79
SN7422N	39	SN74100N	89	SN74183N	1.95
SN7423N	25	SN74107N	35	SN74185N	1.95
SN7425N	29	SN74109N	95	SN74186N	9.95
SN7426N	29	SN74119N	95	SN74187N	95
SN7427N	25	SN74121N	35	SN74190N	1.25
SN7429N	39	SN74122N	39	SN74191N	1.25
SN7430N	20	SN74123N	49	SN74192N	79
SN7432N	25	SN74125N	25	SN74194N	79
SN7437N	25	SN74126N	49	SN74196N	89
SN7438N	25	SN74132N	75	SN74195N	89
SN7439N	25	SN74136N	75	SN74199N	69
SN7443N	89	SN74141N	79	SN74197N	79
SN7441N	89	SN74142N	95	SN74198N	1.49
SN7442N	49	SN74143N	2.95	SN74199N	1.49
SN7443N	75	SN74144N	2.95	SN74200N	1.79
SN7444N	75	SN74145N	7.95	SN74201N	1.79
SN7445N	75	SN74146N	1.95	SN74202N	1.79
SN7446N	69	SN74148N	1.29	SN74203N	2.95
SN7447N	59	SN74150N	89	SN74204N	2.95
SN7448N	79	SN74151N	59	SN74205N	3.95
SN7449N	79	SN74152N	59	SN74206N	3.95
SN7450N	20	SN74153N	59	SN74207N	3.95
SN7451N	20	SN74154N	99	SN74208N	3.95
SN7452N	20	SN74155N	99	SN74209N	3.95
SN7453N	20	SN74156N	79	SN74210N	1.95
SN7454N	20	SN74157N	79	SN74211N	1.95
SN7455N	20	SN74158N	79	SN74212N	1.95
SN7456N	20	SN74159N	65	SN74213N	1.95
SN7457N	20	SN74160N	65	SN74214N	1.95

20% Discount 100 pcs combined order 25% - 1000 pcs combined order

C/MOS

CD4000	23	CD4070	55
CD4001	23	CD4071	23
CD4002	23	CD4072	1.39
CD4006	1.19	CD4073	89
CD4007	25	CD4074	1.19
CD4009	49	CD4075	49
CD4010	49	CD4076	99
CD4011	23	CD4077	23
CD4012	23	CD4078	23
CD4013	23	CD4079	23
CD4014	1.19	CD4080	1.19
CD4015	1.19	CD4081	1.19
CD4016	49	CD4082	1.19
CD4017	1.19	CD4083	1.19
CD4018	1.19	CD4084	1.19
CD4019	99	CD4085	99
CD4020	1.19	CD4086	1.19
CD4021	1.39	CD4087	1.39
CD4022	1.19	CD4088	2.95
CD4023	73	CD4089	95
CD4024	79	CD4090	79
CD4025	23	CD4091	23
CD4026	2.25	CD4092	2.25
CD4027	69	CD4093	45

74C00

74C00	35	74C163	3.00
74C01	55	74C164	3.25
74C02	75	74C165	2.60
74C03	75	74C166	2.60
74C04	75	74C167	3.49
74C05	75	74C168	2.75
74C06	75	74C169	2.95
74C07	3.00	74C170	2.95
74C08	65	74C171	2.95
74C09	74C09	74C172	14.95
74C10	74C10	74C173	11.95
74C11	74C11	74C174	11.95
74C12	74C12	74C175	2.15
74C13	74C13	74C176	3.25
74C14	74C14	74C177	1.50
74C15	74C15	74C178	1.50

LINEAR

LM3000	1.75	LM340T-6	1.25	LM714CN	35
LM3001CN	35	LM340T-8	1.25	LM717CN	79
LM3002	75	LM340T-12	1.25	LM718CN	79
LM3004	1.00	LM340T-15	1.25	LM719CN	79
LM3005H	60	LM340T-18	1.25	LM720CN	79
LM3007CN	35	LM340T-24	1.25	LM721CN	1.19
LM3080CN	1.00	LM350N	1.00	LM722CN	1.19
LM3090	1.19	LM35CN	1.00	LM723CN	1.19
LM3091	1.19	LM350N-1	85	LM724CN	1.19
LM3092	1.15	LM350N-2	85	LM725CN	1.19
LM311N	90	LM350N-3	85	LM726CN	1.19
LM312H	6.50	LM350N-4	85	LM727CN	1.19
LM318CN	1.50	LM350N-5	85	LM728CN	1.19
LM319N	1.30	LM350N-6	85	LM729CN	1.19
LM320K-5	1.35	LM350N-7	85	LM730CN	1.19
LM320K-12	1.35	LM350N-8	85	LM731CN	1.19
LM320K-15	1.35	LM350N-9	85	LM732CN	1.19
LM320K-18	1.35	LM350N-10	85	LM733CN	1.19
LM320K-24	1.35	LM350N-11	85	LM734CN	1.19
LM320K-30	1.35	LM350N-12	85	LM735CN	1.19
LM320K-36	1.35	LM350N-13	85	LM736CN	1.19
LM320K-42	1.35	LM350N-14	85	LM737CN	1.19
LM320K-48	1.35	LM350N-15	85	LM738CN	1.19
LM320K-54	1.35	LM350N-16	85	LM739CN	1.19
LM320K-60	1.35	LM350N-17	85	LM740CN	1.19
LM320K-66	1.35	LM350N-18	85	LM741CN	1.19
LM320K-72	1.35	LM350N-19	85	LM742CN	1.19
LM320K-78	1.35	LM350N-20	85	LM743CN	1.19
LM320K-84	1.35	LM350N-21	85	LM744CN	1.19
LM320K-90	1.35	LM350N-22	85	LM745CN	1.19
LM320K-96	1.35	LM350N-23	85	LM746CN	1.19
LM320K-102	1.35	LM350N-24	85	LM747CN	1.19
LM320K-108	1.35	LM350N-25	85	LM748CN	1.19
LM320K-114	1.35	LM350N-26	85	LM749CN	1.19
LM320K-120	1.35	LM350N-27	85	LM750CN	1.19
LM320K-126	1.35	LM350N-28	85	LM751CN	1.19
LM320K-132	1.35	LM350N-29	85	LM752CN	1.19
LM320K-138	1.35	LM350N-30	85	LM753CN	1.19
LM320K-144	1.35	LM350N-31	85	LM754CN	1.19
LM320K-150	1.35	LM350N-32	85	LM755CN	1.19
LM320K-156	1.35	LM350N-33	85	LM756CN	1.19
LM320K-162	1.35	LM350N-34	85	LM757CN	1.19
LM320K-168	1.35	LM350N-35	85	LM758CN	1.19
LM320K-174	1.35	LM350N-36	85	LM759CN	1.19
LM320K-180	1.35	LM350N-37	85	LM760CN	1.19
LM320K-186	1.35	LM350N-38	85	LM761CN	1.19
LM320K-192	1.35	LM350N-39	85	LM762CN	1.19
LM320K-198	1.35	LM350N-40	85	LM763CN	1.19
LM320K-204	1.35	LM350N-41	85	LM764CN	1.19
LM320K-210	1.35	LM350N-42	85	LM765CN	1.19
LM320K-216	1.35	LM350N-43	85	LM766CN	1.19
LM320K-222	1.35	LM350N-44	85	LM767CN	1.19
LM320K-228	1.35	LM350N-45	85	LM768CN	1.19
LM320K-234	1.35	LM350N-46	85	LM769CN	1.19
LM320K-240	1.35	LM350N-47	85	LM770CN	1.19
LM320K-246	1.35	LM350N-48	85	LM771CN	1.19
LM320K-252	1.35	LM350N-49	85	LM772CN	1.19
LM320K-258	1.35	LM350N-50	85	LM773CN	1.19
LM320K-264	1.35	LM350N-51	85	LM774CN	1.19
LM320K-270	1.35	LM350N-52	85	LM775CN	1.19
LM320K-276	1.35	LM350N-53	85	LM776CN	1.19
LM320K-282	1.35	LM350N-54	85	LM777CN	1.19
LM320K-288	1.35	LM350N-55	85	LM778CN	1.19
LM320K-294	1.35	LM350N-56	85	LM779CN	1.19
LM320K-300	1.35	LM350N-57	85	LM780CN	1.19
LM320K-306	1.35	LM350N-58	85	LM781CN	1.19
LM320K-312	1.35	LM350N-59	85	LM782CN	1.19
LM320K-318	1.35	LM350N-60	85	LM783CN	1.19
LM320K-324	1.35	LM350N-61	85	LM784CN	1.19
LM320K-330	1.35	LM350N-62	85	LM785CN	1.19
LM320K-336	1.35	LM350N-63	85	LM786CN	1.19
LM320K-342	1.35	LM350N-64	85	LM787CN	1.19
LM320K-348	1.35	LM350N-65	85	LM788CN	1.19
LM320K-354	1.35	LM350N-66	85	LM789CN	1.19
LM320K-360	1.35	LM350N-67	85	LM790CN	1.19
LM320K-366	1.35	LM350N-68	85	LM791CN	1.19
LM320K-372	1.35	LM350N-69	85	LM792CN	1.19
LM320K-378	1.35	LM350N-70	85	LM793CN	1.19
LM320K-384	1.35	LM350N-71	85	LM794CN	1.19
LM320K-390	1.35	LM350N-72	85	LM795CN	1.19
LM320K-396	1.35	LM350N-73	85	LM796CN	1.19
LM320K-402	1.35	LM350N-74	85	LM797CN	1.19
LM320K-408	1.35	LM350N-75	85	LM798CN	1.19
LM320K-414	1.35	LM350N-76	85	LM799CN	1.19
LM320K-420	1.35	LM350N-77	85	LM800CN	1.19

74LS00 TTL

74LS00	23	74LS139	4.49
74LS01	23	74LS151	69
74LS02	23	74LS152	69
74LS03	23	74LS153	69
74LS04	29	74LS154	69
74LS05	29	74LS155	69
74LS06	29	74LS156	69
74LS07	29	74LS157	69
74LS08	29	74LS158	69
74LS09	29	74LS159	69
74LS10	29	74LS160	69
74LS11	29	74LS161	69
74LS12	29	74LS162	69
74LS13	29	74LS163	69
74LS14	29	74LS164	69
74LS15	29	74LS165	69
74LS16	29	74LS166	69
74LS17	29	74LS167	69
74LS18	29	74LS168	69
74LS19	29	74LS169	69
74LS20	29	74LS170	69
74LS21	29	74LS171	69
74LS22	29	74LS172	69
74LS23	29	74LS173	69
74LS24	29	74LS174	69
74LS25	29	74LS175	69
74LS26	29	74LS176	69
74LS27	29	74LS177	69
74LS28	29	74LS178	69
74LS29	29	74LS179	69
74LS30	29	74LS180	69
74LS31	29	74LS181	69
74LS32	29	74LS182	69
74LS33	29	74LS183	69
74LS34	29	74LS184	69
74LS35	29	74LS185	69
74LS36	29	74LS186	69
74LS37	29	74LS187	69
74LS38	29	74LS188	69
74LS39	29	74LS189	69
74LS40	29	74LS190	69
74LS41	29	74LS191	69
74LS42	29	74LS192	69
74LS43	29	74LS193	69
74LS44			

SAVE

COMPUTER INTERFACES & PERIPHERALS

SAVE

For free catalog including parts lists and schematics, send a self-addressed stamped envelope.

APPLE II SERIAL I/O INTERFACE *

Part no. 2


Baud rate is continuously adjustable from 0 to 30,000 • Plugs into any peripheral connector • Low current drain. RS-232 input and output • On board switch selectable 5 to 8 data bits, 1 or 2 stop bits, and parity or no parity either odd or even • Jumper selectable address • SOFTWARE • Input and Output routine from monitor or BASIC to teletype or other serial printer • Program for using an Apple II for a video or an intelligent terminal. Also can output in correspondence code to interface with some electrics. Board only — \$15.00; with parts — \$42.00; assembled and tested — \$62.00.



T.V. TYPEWRITER

Part no. 106


• Stand alone TVT • 32 char/line, 16 lines, modifications for 64 char/line included • Paralle ASCII (TTL) input • Video output • 1K on board memory • Output for computer controlled cursor • Auto scroll • Non-destructive cursor • Cursor inputs: up, down, left, right, home, EOL, EOS • Scroll up, down • Requires +5 volts at 1.5 amps, and -12 volts at 30 mA • All 7400, TTL chips • Char. gen. 2513 • Upper case only • Board only \$39.00, with parts \$145.00

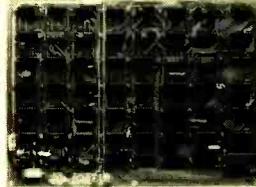

8K STATIC RAM

Part no. 300

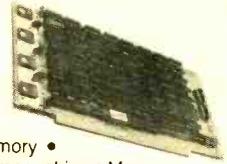
• 8K Altair bus memory • Uses 2102 Static memory chips • Memory protect • Gold contacts • Wait states • On board regulator • S-100 bus compatible • Vector input option • TRI state buffered • Board only \$22.50; with parts \$160.00




MODEM *

Part no. 109

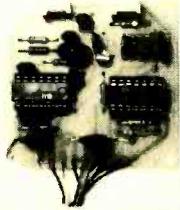• Type 103 • Full or half duplex • Works up to 300 baud • Originate or Answer • No coils, only low cost components • TTL input and output-serial • Connect 8 ohm speaker and crystal mic. directly to board • Uses XR FSK demodulator • Requires +5 volts • Board \$7.60; with parts \$27.50



TIDMA *

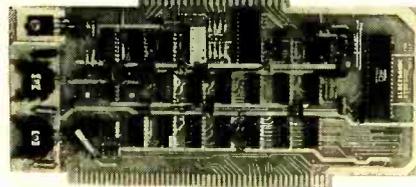

Part no. 112

• Tape Interface Direct Memory Access • Record and play programs without bootstrap loader (no prom) has FSK encoder/decoder for direct connections to low cost recorder at 1200 baud rate, and direct connections for inputs and outputs to a digital recorder at any baud rate. • S-100 bus compatible • Board only \$35.00; with parts \$110.00

RF MODULATOR *

Part no. 107

• Converts video to AM modulated RF, Channels 2 or 3. So powerful almost no tuning is required. On board regulated power supply makes this extremely stable. Rated very highly in Doctor Dobbs' Journal. Recommended by Apple. • Power required is 12 volts AC C.T., or +5 volts DC • Board \$7.60; with parts \$13.50



DC POWER SUPPLY *

Part no. 6085


• Board supplies a regulated +5 volts at 3 amps., +12, -12, and -5 volts at 1 amp. • Power required is 8 volts AC at 3 amps., and 24 volts AC C.T. at 1.5 amps. • Board only \$12.50; with parts excluding transformers \$42.50



RS 232/TTY * INTERFACE

Part no. 600

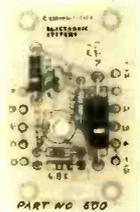• Converts RS-232 to 20mA current loop, and 20mA current loop to RS-232 • Two separate circuits • Requires +12 and -12 volts • Board only \$4.50, with parts \$7.00



TAPE INTERFACE *

Part no. 111


• Play and record Kansas City Standard tapes • Converts a low cost tape recorder to a digital recorder • Works up to 1200 baud • Digital in and out are TTL-serial • Output of board connects to mic. in of recorder • Earphone of recorder connects to input on board • No coils • Requires +5 volts, low power drain • Board \$7.60; with parts \$27.50



UART & BAUD RATE GENERATOR *

Part no. 101


• Converts serial to parallel and parallel to serial • Low cost on board baud rate generator • Baud rates: 110, 150, 300, 600, 1200, and 2400 • Low power drain +5 volts and -12 volts required • TTL compatible • All characters contain a start bit, 5 to 8 data bits, 1 or 2 stop bits, and either odd or even parity. • All connections go to a 44 pin gold plated edge connector • Board only \$12.00; with parts \$35.00 with connector add \$3.00

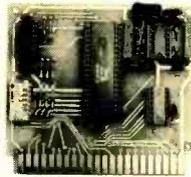

RS 232/TTL * INTERFACE

Part no. 232

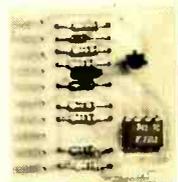• Converts TTL to RS-232, and converts RS-232 to TTL • Two separate circuits • Requires -12 and +12 volts • All connections go to a 10 pin gold plated edge connector • Board only \$4.50; with parts \$7.00 with connector add \$2.00



ELECTRONIC SYSTEMS

Dept. RE-9 P.O. Box 21638, San Jose, CA, USA 95151

To Order:

Mention part number and description. For parts kits add "A" to part number. In USA, shipping paid for orders accompanied by check, money order, or Master Charge, BankAmericard, or VISA number, expiration date and signature. Shipping charges added to C.O.D. orders. California residents add 6.5% for tax. Outside USA add 10% for air mail postage, no C.O.D.'s. Checks and money orders must be payable in US dollars. Parts kits include sockets for all ICs, components, and circuit board. Documentation is included with all products. All items are in stock, and will be shipped the day order is received via first class mail. Prices are in US dollars. No open accounts. To eliminate tariff in Canada boxes are marked "Computer Parts." Dealer inquiries invited. 24 Hour Order Line: (408) 226-4064



* Circuits designed by John Bell

DIGI-KEY CORPORATION

TOLL FREE 1-800-346-5444

QUALITY ELECTRONIC COMPONENTS

MINN., AK., HI. RESIDENTS 218-681-6674

DON'T FORGET OUR DISCOUNTS WHEN COMPARING PRICES

INTEGRATED CIRCUITS

TTL	741500	74C00	74S52	63	
7400	18	74C00N	25	75453	61
7401	18	74C01N	25	75461	61
7402	18	74C02N	25	75469	61
7403	18	74C03N	25	75477	61
7404	18	74C04N	25	75485	61
7405	21	74C05N	29	75493	1.09
7406	25	74C06N	35	75501	1.09
7407	25	74C07N	35	75509	1.09
7408	21	74C08N	29	75517	1.09
7409	21	74C09N	29	75525	1.09
7410	21	74C10N	29	75533	1.09
7411	21	74C11N	29	75541	1.09
7412	21	74C12N	29	75549	1.09
7413	25	74C13N	35	75557	1.09
7414	25	74C14N	35	75565	1.09
7415	25	74C15N	35	75573	1.09
7416	25	74C16N	35	75581	1.09
7417	25	74C17N	35	75589	1.09
7418	25	74C18N	35	75597	1.09
7419	25	74C19N	35	75605	1.09
7420	25	74C20N	35	75613	1.09
7421	25	74C21N	35	75621	1.09
7422	25	74C22N	35	75629	1.09
7423	25	74C23N	35	75637	1.09
7424	25	74C24N	35	75645	1.09
7425	25	74C25N	35	75653	1.09
7426	25	74C26N	35	75661	1.09
7427	25	74C27N	35	75669	1.09
7428	25	74C28N	35	75677	1.09
7429	25	74C29N	35	75685	1.09
7430	25	74C30N	35	75693	1.09
7431	25	74C31N	35	75701	1.09
7432	25	74C32N	35	75709	1.09
7433	25	74C33N	35	75717	1.09
7434	25	74C34N	35	75725	1.09
7435	25	74C35N	35	75733	1.09
7436	25	74C36N	35	75741	1.09
7437	25	74C37N	35	75749	1.09
7438	25	74C38N	35	75757	1.09
7439	25	74C39N	35	75765	1.09
7440	25	74C40N	35	75773	1.09
7441	25	74C41N	35	75781	1.09
7442	25	74C42N	35	75789	1.09
7443	25	74C43N	35	75797	1.09
7444	25	74C44N	35	75805	1.09
7445	25	74C45N	35	75813	1.09
7446	25	74C46N	35	75821	1.09
7447	25	74C47N	35	75829	1.09
7448	25	74C48N	35	75837	1.09
7449	25	74C49N	35	75845	1.09
7450	25	74C50N	35	75853	1.09
7451	25	74C51N	35	75861	1.09
7452	25	74C52N	35	75869	1.09
7453	25	74C53N	35	75877	1.09
7454	25	74C54N	35	75885	1.09
7455	25	74C55N	35	75893	1.09
7456	25	74C56N	35	75901	1.09
7457	25	74C57N	35	75909	1.09
7458	25	74C58N	35	75917	1.09
7459	25	74C59N	35	75925	1.09
7460	25	74C60N	35	75933	1.09
7461	25	74C61N	35	75941	1.09
7462	25	74C62N	35	75949	1.09
7463	25	74C63N	35	75957	1.09
7464	25	74C64N	35	75965	1.09
7465	25	74C65N	35	75973	1.09
7466	25	74C66N	35	75981	1.09
7467	25	74C67N	35	75989	1.09
7468	25	74C68N	35	75997	1.09
7469	25	74C69N	35	76005	1.09
7470	25	74C70N	35	76013	1.09
7471	25	74C71N	35	76021	1.09
7472	25	74C72N	35	76029	1.09
7473	25	74C73N	35	76037	1.09
7474	25	74C74N	35	76045	1.09
7475	25	74C75N	35	76053	1.09
7476	25	74C76N	35	76061	1.09
7477	25	74C77N	35	76069	1.09
7478	25	74C78N	35	76077	1.09
7479	25	74C79N	35	76085	1.09
7480	25	74C80N	35	76093	1.09
7481	25	74C81N	35	76101	1.09
7482	25	74C82N	35	76109	1.09
7483	25	74C83N	35	76117	1.09
7484	25	74C84N	35	76125	1.09
7485	25	74C85N	35	76133	1.09
7486	25	74C86N	35	76141	1.09
7487	25	74C87N	35	76149	1.09
7488	25	74C88N	35	76157	1.09
7489	25	74C89N	35	76165	1.09
7490	25	74C90N	35	76173	1.09
7491	25	74C91N	35	76181	1.09
7492	25	74C92N	35	76189	1.09
7493	25	74C93N	35	76197	1.09
7494	25	74C94N	35	76205	1.09
7495	25	74C95N	35	76213	1.09
7496	25	74C96N	35	76221	1.09
7497	25	74C97N	35	76229	1.09
7498	25	74C98N	35	76237	1.09
7499	25	74C99N	35	76245	1.09
7500	25	74C100N	35	76253	1.09

NEW! DIGI-KEY ONLY \$21.90

Part No. 5001K

• Trouble-free Mount!

• 270° Swivel Module!

• Inlaid Walnut Chrome Trim Bezel!

• Ideal for Car, Van or Boat!

• 3-5/8" x 2-3/16" Tall x 2-1/8" Deep!

• Quick and Easy To Install!



• AN MA1003 CLOCK MODULE BY NATIONAL SEMICONDUCTOR—Fully assembled, tested, and ready to run in 20 VDC this 3" fluorescent display is designed to replace those troublesome mechanical clocks. It is protected against automotive voltage transients and reversals with timekeeping maintained to 9 VDC. Automatic display brightness control logic blanks the display with the ignition off, reduces brightness to 33% with park or head lights and follows the dash lamp dimming control setting. Its crystal time base assures an accuracy of 7 seconds per day at 25°C and 5 seconds per day over the range of 25°C to 65°C.

• AN ATTRACTIVE INLAID WALNUT & CHROME TRIM BEZEL—Designed to be either flush mounted or used as a face plate for the enclosure. Its deep recessed display eliminates glare and reflection while its blue acrylic filter provides optimum display contrast.

• A NON-GLARE BLACK ENCLOSURE WITH A 270° SWIVEL BRACKET—Is made of ABS plastic and designed for mounting on under cabinet or ceiling dash or almost anywhere in your car, van or boat. Or use as a back box if you choose to flush mount the bezel. The enclosure-bezel combination can be flush mounted on paneling up to 5/16" thick and in addition is designed to fit between the ribs of most vans.

• 3 PUSH BUTTON SWITCHES—For quick and simple setting of hours, minutes, and display activation with the ignition off. These switches can be mounted directly on the bezel or enclosure or mounted remotely if you prefer.

• A SET OF EASY TO FOLLOW INSTRUCTIONS—To guide you step by step through the hardware included.

MA1003 Clock Module and Switches only 15.95
401 Bezel and Enclosure only 5.95
5001K Digi-Clock Kit (includes MA1003 and 401) 21.90

ELECTROLYTIC CAPACITORS

VALUE	RADIAL LEADS	AXIAL LEADS
47 50V	10 78 10 620 C	13 110 10 850 C
100 50V	10 78 10 620 C	13 110 10 850 C
220 50V	10 78 10 620 C	13 110 10 850 C
470 50V	10 78 10 620 C	13 110 10 850 C
1000 50V	10 78 10 620 C	13 110 10 850 C
2200 50V	10 78 10 620 C	13 110 10 850 C
4700 50V	10 78 10 620 C	13 110 10 850 C
10000 50V	10 78 10 620 C	13 110 10 850 C
22000 50V	10 78 10 620 C	13 110 10 850 C
47000 50V	10 78 10 620 C	13 110 10 850 C
100000 50V	10 78 10 620 C	13 110 10 850 C
220000 50V	10 78 10 620 C	13 110 10 850 C
470000 50V	10 78 10 620 C	13 110 10 850 C
1000000 50V	10 78 10 620 C	13 110 10 850 C
2200000 50V	10 78 10 620 C	13 110 10 850 C
4700000 50V	10 78 10 620 C	13 110 10 850 C
10000000 50V	10 78 10 620 C	13 110 10 850 C
22000000 50V	10 78 10 620 C	13 110 10 850 C
47000000 50V	10 78 10 620 C	13 110 10 850 C
100000000 50V	10 78 10 620 C	13 110 10 850 C
220000000 50V	10 78 10 620 C	13 110 10 850 C
470000000 50V	10 78 10 620 C	13 110 10 850 C
1000000000 50V	10 78 10 620 C	13 110 10 850 C
2200000000 50V	10 78 10 620 C	13 110 10 850 C
4700000000 50V	10 78 10 620 C	13 110 10 850 C
10000000000 50V	10 78 10 620 C	13 110 10 850 C
22000000000 50V	10 78 10 620 C	13 110 10 850 C
47000000000 50V	10 78 10 620 C	13 110 10 850 C
100000000000 50V	10 78 10 620 C	13 110 10 850 C
220000000000 50V	10 78 10 620 C	13 110 10 850 C
470000000000 50V	10 78 10 620 C	13 110 10 850 C
1000000000000 50V	10 78 10 620 C	13 110 10 850 C
2200000000000 50V	10 78 10 620 C	13 110 10 850 C
4700000000000 50V	10 78 10 620 C	13 110 10 850 C
10000000000000 50V	10 78 10 620 C	13 110 10 850 C
22000000000000 50V	10 78 10 620 C	13 110 10 850 C
47000000000000 50V	10 78 10 620 C	13 110 10 850 C
100000000000000 50V	10 78 10 620 C	13 110 10 850 C
220000000000000 50V	10 78 10 620 C	13 110 10 850 C
470000000000000 50V	10 78 10 620 C	13 110 10 850 C
1000000000000000 50V	10 78 10 620 C	13 110 10 850 C
2200000000000000 50V	10 78 10 620 C	13 110 10 850 C
4700000000000000 50V	10 78 10 620 C	13 110 10 850 C
10000000000000000 50V	10 78 10 620 C	13 110 10 850 C
22000000000000000 50V	10 78 10 620 C	13 110 10 850 C
47000000000000000 50V	10 78 10 620 C	13 110 10 850 C
100000000000000000 50V	10 78 10 620 C	13 110 10 850 C
220000000000000000 50V	10 78 10 620 C	13 110 10 850 C
470000000000000000 50V	10 78 10 620 C	13 110 10 850 C
1000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
2200000000000000000 50V	10 78 10 620 C	13 110 10 850 C
4700000000000000000 50V	10 78 10 620 C	13 110 10 850 C
10000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
22000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
47000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
100000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
220000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
470000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
1000000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
2200000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
4700000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
10000000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
22000000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
47000000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
100000000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
220000000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
470000000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
1000000000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
2200000000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
4700000000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
10000000000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
22000000000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
47000000000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
100000000000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
220000000000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
470000000000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
1000000000000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
2200000000000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
4700000000000000000000000000 50V	10 78 10 620 C	13 110 10 850 C
10000000000000000000000000000 50V	10 78	

SURPLUS SPECTACULAR!

2 METER MOBILE ANTENNA

\$12.95


BRAND NEW FACTORY BOXED ANTENNAS MADE BY WELL KNOWN TOP LINE MFR. FOR POLICE AND GOVT. AGENCIES. ORIGINAL COST IN HUGE QUANTITIES WAS TWICE OUR LOW PRICE.

Plus \$1 Shipping

FEATURES: -HIGHEST QUALITY; DESIGNED FOR USE WITH STATE & COUNTY POLICE VEHICLES. MOLDED FIBREGLASS HELICALLY WOUND WHIP (FLOURESCENT ORANGE), HEAVILY PLATED PARTS, SEALED MATCHING TRANSFORMER.
-SINGLE HOLE MOUNT (1/2" DIA) WITH ALL MOUNTING HARDWARE INCLUDING TRIM RINGS AND RUBBER SEALS. ALSO WORKS WITH MOST "CLAMP TYPE" ADAPTERS.
-TUNES FROM 140-176 MHz -- WHIP CUTTING CHART SHOWS WHIP LENGTH VS FREQUENCY. CUT FOR 2M HAM BAND, FIRE & POLICE BANDS (FOR SCANNERS) OR EVEN USE IN THE MARINE BAND!
-COMPLETE WITH ALL PARTS - WHIP, LOADING COIL (TRANSFORMER), HARDWARE, COAX (RG58A/U), PL259 CONNECTOR, AND COMPLETE INSTALLATION AND TUNING INSTRUCTIONS.

DOES IT GET OUT ? YOU BET !! 5/8 WAVE VERTICALS ARE MOST WIDELY USED IN COMMERCIAL AND 2 METER FM WORK BECAUSE OF THE LOW RADIATION ANGLE AND CONSIDERABLE GAIN OVER SHORTER VERTICAL WHIPS. BANDWIDTH IS GOOD, RESULTING IN LOWER SWR OVER A WIDER FREQUENCY RANGE. A LESSER DEPENDENCE ON A GROUND PLANE MEANS EASIER MOUNTING IN MANY CASES. (THESE ANTENNAS WERE USED ON POLICE MOTORCYCLES WITH EXCELLENT RESULTS -- GROUND PLANE ?) GIVE THEM A GOOD GROUND PLANE (LIKE A CAR ROOF) AND THEY'RE NEARLY UNBEATABLE !


LIMITED QUANTITIES

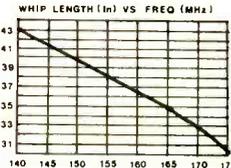

FREE CATALOG

CIRCLE 83 ON FREE INFORMATION CARD

LASER POWER SUPPLIES

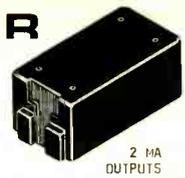

COMMERCIAL QUALITY SUPPLIES FEATURE 120 VAC INPUT, RECTIFIED AND FILTERED DC OUTPUT! THESE NEW UNITS ORIGINALLY COST THE MFR ABOUT \$30 EACH IN BIG QUANTITIES. USE FOR LASERS, BUG ZAPPERS, HIGH VOLTAGE EXPERIMENTS OF ALL SORTS. SUPPLIES ARE POTTED IN PLASTIC WITH THE RECTIFIERS ACCESSIBLE THROUGH A REMOVABLE PLATE.

12.500 Vdc 25 Watts L-1250

\$7.95 Plus \$2 Ship. (They are HEAVY!)

7.500 Vdc 15 Watts L-750

\$6.95 Plus \$1.40 shipping

CRYSTALS

HC-6 case tune w/18pf FRESH STOCK!
O-3125
3.579 MHz \$125
4.000 MHz \$150
4.194 MHz \$150

BEZELS

RED LENS BLACK FRAME VIEWING AREA 0.8" H x WIDTH GIVEN. NEW EASY MOUNT.
J-1200 2" Wide \$1.79
J-1300 3" Wide \$2.29
J-1400 4" Wide \$2.98

DIAMONDBACK ELECTRONICS COMPANY

PO BOX 194 SPRING VALLEY, IL 61362

OUR FIFTH YEAR!
FREE CATALOG
ALL MERCHANDISE 100% GUARANTEED MINIMUM ORDER \$5
ILL RESIDENTS ADD 5% SALES TAX PLEASE INCLUDE SUFFICIENT POSTAGE RATES QUOTED ARE CONTINENTAL US ONLY
PHONE ORDERS 815/664-5151

GREAT IDEAS FROM WEST SIDE ELECTRONICS

17 Digit, 10 Function Digital Clock Kit

The Ultimate Electronic Timepiece. 17 digits continuously read out the time, date, alarm setting, and timer 12/24 HR. AC/DC. crystal timebase. 3 mode timer, status LEDs, snooze, and more. Now with DIGISET™ thumbwheel preset option (see below). Featured in Radio-Electronics (Aug/Sept 1977)
MT1-C kit, less case \$129.95

Pink Noise Generator Kit \$13.95

NOW IMPROVED!! with 5% tolerance components
Allows proper set-up of graphic equalizer in a stereo system to achieve acoustically flat response. Uses latest MOS IC. See Jan. '78 Radio-Electronics.
PNG-2C Partial kit \$13.95
PNG-2K Complete kit with case \$19.95
PNG-2W Assembled and tested \$27.95

WRITE FOR DETAILS

DIGISET™ - Thumbwheel preset for MT1. Simply dial in alarm setting, timer, etc. and DIGISET™ does the rest. Also adds second ALARM feature. Will work with other 7001 based clocks.
APPLE II OWNERS: Real Time Clock plugs directly into any I/O slot. Crystal oscillator and AC supply (with battery backup) keeps clock running at all times.

16K MEMORY EXPANSION KIT \$130.00


Includes 8 MK4116 RAMs and instructions for Apple and TRS-80 Upgrade NOW at this LOW PRICE

WEST SIDE ELECTRONICS
P. O. Box 636, Chatsworth, CA 91311

We pay all shipping in Continental U.S.A. Others add 10%, California residents add 6% tax.

CIRCLE 67 ON FREE INFORMATION CARD

JUMBO LED READOUT ARRAY

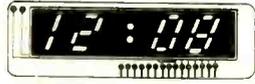

By Bowmar. .5 in. character common cathode. Designed for use with multiplexed clock chips 4 digits in 1 pack!

\$1.95 LIMITED STOCK

MICRO-MINI TOGGLE SWITCH




99¢ EACH

SPDT. By RAYTHEON. MADE IN USA! WITH HDWR.

6 FOR \$5

NATIONAL SEMICONDUCTOR JUMBO CLOCK MODULE

MA1008A BRAND NEW!

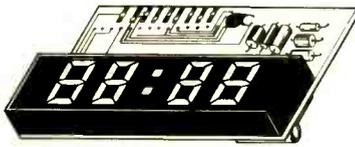

\$6.95

2 FOR \$13

(AC XFMR \$1.95)

- FEATURES:
- FOUR JUMBO 1/2 INCH LED DISPLAYS
 - 12 HR REAL TIME FORMAT
 - 24 HR ALARM SIGNAL OUTPUT
 - 50 OR 60 HZ OPERATION
 - LED BRIGHTNESS CONTROL
 - POWER FAILURE INDICATOR
 - SLEEP & SNOOZE TIMERS
 - DIRECT LED DRIVE (LOW RFI)
 - COMES WITH FULL DATA

ASSEMBLED! NOT A KIT!

ZULU VERSION!
We have a limited number of the 24 HR Real time version of this module in stock #MA1008D - \$9.95

PERFECT FOR USE WITH A TIMEBASE.

COMPARE AT UP TO TWICE OUR PRICE!

MANUFACTURER'S CLOSEOUT!

16K DYNAMIC RAM CHIP

16K X 1 Bits. 16 Pin Package. Same as Mostek 4116-4. 250 NS access. 410 NS cycle time. Our best price yet for this state of the art RAM. 32K and 64K RAM boards using this chip are readily available. These are new, fully guaranteed devices by a major mfg.

\$17.95 EACH

8 FOR \$129

EXPERIMENTER'S CRYSTAL



262.144KHZ. This frequency is 2 to the 18th power. Easily divided down to any power of 2, and even to 1HZ. New by CTS-Knight. A \$5 value!

\$1.25 each

SALE!
1N4148 DIODES
High speed switching diodes. Silicon. Same as 1N914. Brand New. Full Leads. Prime!
100 FOR \$2 1000 FOR \$17.50

FAIRCHILD JUMBO READOUTS
-.5 inch Char. High Efficiency!
FND-503-Common Cathode
FND-510-Common Anode
YOUR CHOICE 69¢
10 FOR \$5.75

DISC CAPACITORS
.1 MFD 16V. P.C. leads. Most popular value! By Sprague.
20 for \$1.00

Full Wave Bridge
4 Amp 200 PIV
69¢ ea. 10/5.75

MALLORY POWER SUPPLY CAPACITOR
1500 MFD 16 WVDC
3/\$1.00 10/\$2.95
FACTORY FRESH! SMALL SIZE

RECTIFIER SALE!
1N4006. Prime
New by ITT.
1 AMP. 800 PIV.
15 FOR \$1

FET SALE!
2N4304. Brand New
N Channel, Junction Fet.
BVG00-30V IDSS-15 MA Typ.
1500 uMOS TO-18 Plastic Case. Mfg. by Teledyne.
6 FOR \$1

Motorola PNP Power!
2N4905 TO-3 case. 90W.
VCEO-60. HFE-100 max. at 2.5A. Good mate for the 2N3055. PRIME!
75¢ ea. 4/\$2.50

COMPUTER CAPACITOR
By GE. 36,000 MFD 15W VDC
Small Size: 4 1/4 x 1 1/4 Inches.
SUPER DEAL! \$2.95 Each
3 FOR \$8

RCA MICRO-POWER OP AMP.
#CA3078T. Metal Can. Most OPAMPS require +15V to operate. But the CA3078 is designed to operate from -7.5 V to +6V!!! Perfect for battery use. Standby power as low as 700 NW! High Gain: 92 DB typical Open Loop Gain. Requires only one capacitor for compensation. See RCA Linear Data Book for more details. Similar to National LM112. Originally cost about \$2 each.
75¢ EACH 3 FOR \$2

Digital Research Corporation

(OF TEXAS)
P. O. BOX 401247B GARLAND, TEXAS 75040 • (214) 271-2461

TERMS: Add 30¢ postage, we pay balance. Orders under \$15 add 75¢ handling. No C.O.D. We accept Visa, MasterCard, and American Express cards. Tex. Res. add 5% Tax. Foreign orders (except Canada) add 20% P & H. 90 Day Money Back Guarantee on all items.

RADIO-ELECTRONICS

ADVANCED COMPUTER PRODUCTS

THE FIRST TO OFFER PRIME PRODUCTS TO THE HOBBYIST AT FAIR PRICES NOW LOWERS PRICES EVEN FURTHER!

- 1. Proven Quality** Factory tested products only, no re-tests or fallouts. Guaranteed money back. We stand behind our products.
- 2. Same Day Shipment** All prepaid orders with cashiers check, money order or charge card will be shipped same day as received.

\$100 PRODUCTS

LOGOS I 8K STATIC RAM

- ★ Low Power
- ★ Selectable Memory Protect
- ★ Totally Buffered
- ★ Battery Back-up
- ★ Address on 1K boundary
- ★ Requires no front panel
- ★ No wait states



ASSEMBLED & TESTED

250ns. 199.95
450ns. 179.95

WE OFFER GROUP DISCOUNTS

KIT

250ns. 149.95
450ns. 125.95

Bare PC Board w/Data \$21.95
Now over 1 year successful field experience
Special Offer Buy (4) 8K 450ns. Kits \$117.00 ea.

IMS 16K STATIC RAM

- ★ Memory mapping
- ★ Phantom
- ★ Address 16K Bound
- ★ Use with or w/o front panel
- ★ Power 2.1 amps typ.
- ★ Uses 2114

ASSEMBLED & TESTED ONLY
450ns. \$439.95 250ns. \$495.95

S-100 32K STATIC RAM

- ★ Address 32K Boundary
- ★ Power 450ns. 2.8 amps typ.
- ★ No wait states on 2MHz
- ★ Fully Buffered
- ★ Phantom can be added
- ★ 2114/TMS4045 or 9135

ASSEMBLED & TESTED KIT
250ns. \$849.00 250ns. \$790.00
450ns. \$769.95 450ns. \$625.00
Bare PC Board w/Data \$59.95
SPECIAL OFFER:
Kit without Memory only \$99.95
Add 2114 Memory for 8 @ \$7.50 ea.

PARATRONICS LOGIC S-100 ANALYZER KIT

MODEL 100A \$219.95
(analyzes any type of digital system)
Trigger Expander Model 10 \$229.00
Baseplate 9.95
Model 10 Manual 4.95
Model 150 Bus Grabber Kit 369.00

DC HAYES DATA COMMUNICATIONS ADAPTER

- ★ Telephone/TWX
- ★ S-100 compatible
- ★ Bell 103 freq
- ★ Originate & answer mode

Assembled & Tested \$279.95
Bare PC Board w/data \$49.95

DATABASES & MANUALS

NASC TTL Data	\$ 3.95	AMI MOS/LSI Data	3.95
NASC Linear Data	4.95	GI MOS/LSI Data	4.95
NASC APP/Note I	3.95	Osborne Intro to Micro Vol 0	7.50
NASC APP/Note II	3.95	Osborne Intro to Micro Vol II	7.50
NASC CMOS Data	2.95	Osborne 8080 Programming	7.50
NASC Audio Data	3.95	Osborne 8080 Programming	7.50
NASC Volt Reg Data	2.95	Osborne 8080 Programming	7.50
NASC Memory Data	3.95	Osborne Z80 Programming	7.50
NASC MOS/LSI Data	3.95	TI Power Sem's Data	7.50
NASC Power Transistors	2.95	TI TTL Data	7.50
Intel Databook	3.95	1 Transistors & Diodes	8.95
Intel MCS85 Manual	7.50	1 Memory Data	3.95
Intel MCS80 Manual	7.50	TI On-Chip Electronics	3.95
Intel MCS40 Manual	4.95	TI Linear Data	3.95
AMD 8080 Handbook	5.95	TI Bipolar Memory	3.95
AMD Linear Data	4.95	TI Interface Data	4.95
AMD Schottky Data	4.95	Motorola Sem's Data 1, 2, 3	9.95

Z-80/Z-80A CPU BOARD

- ★ On board 2708
 - ★ Power on Jump
 - ★ 2708 included (450ns.)
 - ★ completely socketed
- Assembled and tested \$185.00
Kit \$129.95
Bare PC Board \$34.95
★ For 4MHz Speed Add \$15.00

MICRODESIGN MR-8 2716 EPROM BOARD (MR-8 Also Available at same price)

- ★ Individual Prom Address
 - ★ Uses Low cost 16K TI EPROMS
 - ★ Optional 1K RAM ★ Phantom-control
- Assembled and Tested 174.95
Kit 99.50

SPECIAL SPECIAL SPECIAL

2708-6 Eprom 8 @ \$ 5.50 ea.
416 16K Ram 32 @ \$16.95 ea.
1771 01 Floppy 5 @ \$29.95 ea.
Pet Connector Set 5 @ \$ 7.95 ea.

BYTE USER 8K EPROM BOARD

- ★ Power on Jump
 - ★ Reset Jump
- Assembled & Tested 94.95
Kit 64.95
Bare PC Board 21.95

Special Offer: Buy 4 kits only \$59.95 each

NOTE: 2708-6 only \$5.95

TARBELL FLOPPY INTERFACE

- ★ S-100 Compatible
- ★ Uses CPM
- ★ Jumper Selectable
- ★ Persci, Shugart, etc

Assembled and tested \$269.95
Kit \$179.95
Bare PC Board \$39.95
NOTE: For CPM Add \$70.00
Documentation Add \$20.00

TRS 80 UPGRADE KIT

16K Memory with Jumpers and Instructions \$159.95
(Specify Level I or Level II)
APPLE II 16K UPGRADE KIT \$149.95

PET TO S-100 ADAPTER

Allows Pet to be interfaced to popular S-100 Bus
Kit \$189.95
Assembled \$269.95
For Low Cost 8 Slot Bus to expand your Pet only \$149.95 Kit

KEYBOARD ENCODERS

A5-2376	13.75
A5-3600	13.75
UR1628 (5V, 12V)	3.95
A5-5103 (5V, 12V)	5.50
A5-5104 (4A, 12, 15-14V)	6.95
A5-5105 (4A, 1863.5V)	6.95
TMS 6011 (5V, 12V)	5.50
IM6-02	9.95
IM6-03	9.95
2350 J58T	24.95
16719 Astros	9.95

SALE TR1472B \$9.95

DISKETTES

5" MINI	
★ Soft Sector	
★ 10 Sector	
★ 16 Sector	
4 \$4.50 each \$3.90/10	
NORTH STAR MINI	
4 \$4.95 each \$4.50/10	
8" STANDARD	
★ Hard	
★ Soft	
4 \$4.50 each \$4.10/10	

Hi PLOT LOW COST DIGITAL PLOTTER

- ★ RS 232
- ★ Plot Size 7" x 10"
- ★ Digitizer Avail. soon
- ★ High Resolution
- ★ 2.4"/sec Plot Speed

NEW
List: \$1085.00
OUR PRICE \$999.00

SPECIAL KEYBOARD BUY WHILE THEY LAST
"Clare Pender 62 Key ASCII w/26 Pin & 34 Pin Output Conn." \$54.95

SUPPORT DEVICES

AM9511A Arithmetic Processor	\$195.00
AM8517 DMA Controller	71.95
AM9519 Universal Interrupt	24.95
3881 (Z80 PIO)	10.45
3881-4 (4MHz)	14.95
3882 (Z80 CTC)	10.45
3882-4 (4MHz)	14.95
8205 (74AS138 Decoder)	2.95
8212 8 bit I/O	2.50
8214 Priority Int	3.95
8216 Bus Driver	2.50
8224 Clock Gen	3.95
8224-4 (4MHz)	9.75
8226 Bus Driver	2.95
8228 Bus Driver	2.95
8228 Sys Control	6.95
8238 Sys Cont	6.95
8251 Prog I/O	11.50
8253 Int Timer	11.50
8259 Prog I/O	19.50
8259 PPIO DMA	19.50
8259 Prog Int	19.50
8275 CRT Controller	74.95
8278 Keyboard	19.95
6810-1 128 x 8 RAM	4.75
6820 PIA	7.25
6821 PIA	7.25
6828 Priority Int	11.95
6834 1512 x 8 Eprom	7.20
6852 Serial Adapter	9.95
6852 1600 x 8 SGRAM Contr	29.95
6860 Modem	14.50
6862 Modem	14.50
6864 1.0MHz OSC	4.95
6875	8.25
2350 USRT	9.95
6880 Bus Driver	25.00
1821 16CD 1K RAM	25.00
1822 32CD 256 x 4 RAM	16.95
1823 64CD 32 x 8 RAM	9.95
1852 CD 8 bit I/O	10.95
1856 CD I/O	8.95
6878 CD I/O	6.95
6520 PIA	7.50
6522 Mult.	9.95
6530-002	15.50
6530-003	15.50
6530-004	15.50
3851 FB Prog Store	14.95
3853 FB Memory I/O	14.95

SOCKETS

8 Pin WW/32	8 Pin S/T 17
14 Pin WW/7	14 Pin S/T 20
16 Pin WW/38	16 Pin S/T 32
18 Pin WW/50	18 Pin S/T 31
20 Pin WW/90	20 Pin S/T 24
22 Pin WW/93	22 Pin S/T 35
24 Pin WW/145	24 Pin S/T 41
28 Pin WW/115	28 Pin S/T 49
40 Pin WW/149	40 Pin S/T 63

CONNECTORS

6 Pin Single S/E	1.49
1530 Dual S/E	1.95
1835 Dual S/E	1.25
2244 Dual S/E	2.95
4080 W/W	4.95
4386 Dual W/W/S/T	2.95
50100 IMSAI W/W	4.75
50100 IMSAI S/W	4.75
50100 Altair W/W/S/T	5.95
IMSAI Card Guides	4/1.00

NEW CTS DISPWITCHES

CTS206-4 \$175	CTS208-B \$195
CTS206-5 \$175	CTS209-B \$195
CTS206-6 \$175	CTS209-10 \$195

8080 USER'S IT'S HERE LIVERMORE BASIC

ON 65K ROM
"HARDWARE" ON ROM!!
OUR PRICE only \$95.00

PCG PROGRAMMABLE CHARACTER GENERATOR

The hottest version of PCG
8080/8085 compatible
S-100 compatible 2MHz kit
with complete code on tarbell or cpm \$169.95

NAKED PC BOARD SALES S-100

Z-80 CPU (ITHACA)	34.95
Z-80 CPU (TDL)	34.95
8080A CPU	34.95
8K Static Logos	21.95
8K Eprom Bytester	21.95
Vector 8080 Photo	59.95
Tarbell Floppy I/O	39.95
Tarbell Cassette	29.95
Vector 8080 Photo	19.95
ACP Photo Bd	24.95
Restoration w/conn	37.95
Restoration Clock	37.95
WMC 13 Slot Mother Bds	33.00
S-100 Bus Mother Bds	34.95
Vector 8081 1 Slot M Bd	29.95
SSM Video I/O	27.95
SSM I/O Parallel I/O	27.95

UV "Eprom" Eraser

Model US-11E \$219.95
Professional Industrial Model

ATTENTION KIM USERS

ATTENTION KIM USERS
M212 Coprocessor
2510A Shift Register
2519A Shift Register
MCM585 Shift Register
LM7600-1A Comparator
DS0025CN Clock Divider
DS0025CN Clock Divider
8720 Bidirect Register
1403AN Shift Register
9358B
Intel 8155 22 I/O w/DMA
Intel 1707 CPL 32 w/DMA

A/D CONVERTERS

8700 8 bit Binary	17.00
8710 10 bit Binary	23.00
8702 12 bit Binary	36.95
8705 12 bit IFS	42.95
8700 Volt to Freq Conv	7.25
8750 3 1/2 Digt BCD	13.95
8003 Multiplication	3.95
1408B 8 bit	1.95
1408B 8 bit	5.95
1408B 8 bit	11.95

INTERFACES

Pipe Viter	8.50
1-Video Interface	8.95
Packets & Trout TV Mod Kit	20.00
Multi-Channel	35.00
MAR Modulator	35.00

MICROPROCESSORS

Z-80	\$19.95
Z-80A	26.95
F-81850U	16.95
2102	24.95
CD1802	19.95
CD1802	19.95
SALE 8085	14.95
8085	14.95
2901	21.95
2901A	29.95
TMS 9900UL	69.95
4080 W/W	33.95
50100	19.95
50100	19.95
6800	18.95
6802P	32.95
8035	17.50

STATIC RAM HEADQUARTERS

21L02 450ns	1.24	25.99	100
21L02 250ns	1.30	12.95	115
21L02 250ns	1.59	15.95	145
21L02 250ns	1.15	11.50	125
21L11-1	1.75	16.50	150
21L11-1	4.10	39.50	350
21L12-1	3.75	36.50	350
21L12-1	4.25	40.00	395
21L12-1	4.10	39.50	350
21L01-1	3.95	37.50	365
21L12-1	2.90	27.00	255
2114-3 300ns	2.95	28.50	265
2114-4 450ns	7.95	75.00	550
TMS-044	9.95	95.00	825
TMS-045	9.95	95.00	825
EMM4200A	12.50	119.00	995
EMM4402	7.95	77.25	625
8101C	7.95	79.50	720
upd410 (4200)	10.95	105.25	925
AMD914041A	10.95	105.25	925
AMD913031	12.95	119.50	1025
F5C 460/46416K CCD Only \$195.00 Each			
7101	1.95	1.95	1.25
P2125-93425 (45 ns)	7.95	7.95	7.25
6508 1K x 1 CMOS	7.95	7.95	7.25
6518 1K x 1 CMOS	7.95	7.95	7.25
745189 64 bit Ram	3.95	3.25	2.50

WAVEFORM GENERATORS

8038 Function Gen	3.95
MC4024 VCO	2.45
LM566 VCO	1.75
XR2208 Function Generator	5.25

CHARGE COUPLED DEVICES

16K CCD - First time offered Farnich 480 CCD
16K Memory (now you can experiment with CCD technology at a reasonable price 17 page Additions are supplied with each order. Quantity limited)
\$18.95 each (reg. 43.00)

CRYSTALS

Frequency	Price	Frequency	Price
1.0MHz	\$1.85	5.0MHz	4.95
1.8432	4.95	6.144	4.95
2.0MHz	5.85	6.536	4.95
2.0MHz	5.85	10.0MHz	4.95
2.09152MHz	5.85	13.0MHz	4.95
2.475MHz	5.85	14.3168	4.95
3.579545MHz	5.85	10.0MHz	4.95
4.0MHz	4.95	19.32MHz	5.95

FIRST QUALITY CARBON RESISTOR KITS 1/4W

Each kit contains all the EIA designated 10% values from 2.2 ohms to 8.2 megohms. Your cost: Only \$.02 per resistor.



KIT A
1,000 Pcs. 19⁹⁵ ppd.
Includes FREE 9-drawer box (\$5.00 value)



KIT B
500 Pcs. 9⁹⁵ ppd.
Includes FREE compartmentalized box (\$2.00 value)



KIT C
250 Pcs. 4⁹⁵ ppd.
in Poly Bag

MANY OTHER KITS
Aluminum Electrolytic, Tantalum and Ceramic Capacitor Kits. Semiconductor Kits, too. Lamps also.

We have over 2,000 quality Receiving Tubes. Many hard-to-get types. All at 75% off list.

ORIGINAL JAPANESE SEMICONDUCTORS
Full range available to fill just about any requirement.

Send for complete catalog



TO ORDER:
Send check or Money Order—
N.Y. residents add appropriate tax.

STEVEN PRODUCTS

P.O. BOX 698, MELVILLE, N.Y. 11746

ADVERTISING INDEX

RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.

Free Information Number Page

37	Active Electronics	109
—	Advance Electronics	24,25
—	Advance Schools	28-31
3	Advanced Computer Products	133
33	Aldelco	114
—	AMC Sales	106
82	Amelect	89
4	American Antenna	Cov. 4
84	AP Products, Inc.	86
1	AVR Electronics	110
—	Karel Barta	110
85	Forest Belt's Training Workshop	27
58	B & K Precision Dynascan Co.	34
—	Bullett Electronics	120
—	Burdex Security Co.	106
62	C F R Associates	118
—	Chaney Electronics	116
69	Channelock	22
—	CIE-Cleveland Institute of Electronics	18-21
—	Command Productions	112
5	Continental Specialties	Cov. 3
—	Cornell Electronics	105
—	CREI-Div. of McGraw Hill Continuing Education	72-75
—	Dage Scientific Instruments	106
86	Dallas Electronic Products	35
64	Davis Electronics	99
54	Delta Electronics	110
83	Diamondback Electronics	132
59	Digi-Key	131
—	Digital Research Corporation	132
—	E.A.R.S., Inc.	105
38	Edlie Electronics	122
7	E I C O	97
36	Electra Company	13
—	Electro-Voice, Inc.	98
—	Electronic Development Lab	110
65	Electronic Supermarket	120
—	Electronic Systems	130
48	Electronic Warehouse	122
29	Electronics Book Club (Tab)	23
35	Electronics & Control Engineer's Book Club-McGraw Hill Book Div.	90-93
—	EMC-Electronics Measurements	98
41	Etco Electronics	127
73	Fordham Radio Supply	114
9	Formula International	116,117
—	Fuji-Svea	108
—	Gilfer Shortwave	106
43	Godbout Electronics	118
63	Gould	17
11	Grantham College of Engineering	87
10	Graymark International	107
68	G.T.E. Sylvania-Consumer Renewal	1
100	Heath	100-103
77	Hickok Electrical Instruments	36
74	Hobby World	108
13	Indiana Home Study	95
—	Information Unlimited	106
51	Integrated Electronics	120
56	International Crystal Mfg. Co.	104
14	International Electronics	113
20	James Electronics	128,129
55	J & E Electronics	108
15	Kedman	94
—	Krystal Kits	105
—	Lakeside Industries	106
70	Leader	85
80	LMN Electronics	121
8	McKay Dymek	97
39	Meshna	114
49	Morrow's Micro Stuff	104
6	M T I-Mobile Training Institute	84

16	National Camera Supply	95
—	National Radio Institute (NRI)	8-11
—	National Technical Schools	54-57
—	NESDA	94
53	Netronics	95
66	New-Tone Electronics	126
71	New-Tone Electronics International	118
81	North American Electronics	89
2	O.K. Machine & Tool	16
—	Olson	119
72	Oneida Electronics	97
18	Optoelectronics	Cov. 2
17	ORA Electronics	88
22	Page Digital	122
21	P A I A	99
57,19	Panasonic	2,15
47	Panavise	99
40	Poly Paks	123
—	Priority 1 Electronics	124,125
78	Professional Aids	98
61	PTS Electronics	83
46	Quest	106
34	Quimtronix	112
—	Radio Shack	111
42	Ramsey Electronics	112
23	Ripley Co.	87
—	Robinson Nugent	97
32	Rye Industries	83
—	Sabtronics	7
45	Schober Organ	32
25	S G L Waber	81
24	Solid State Sales	126
60	Southwest Technical Products	96
75	Spacekom	33
—	Speakerlab Inc.	105
—	Spyder Co.	96
—	A. F. Stahler Co.	106
31	Steven Products	134
—	Tasco	105
27	Trinico International	115
28	Tri-Star	112
—	Trumbull	105
26	Tuner Service	5
52	Vector	32
44	VIZ Mfg.	26
30	Wersi Electronics	95
67	West Side Electronics	132

MOVING?

Don't miss a single copy of **Radio-Electronics**. Give us:

Six weeks' notice

Your old address and zip code

Your new address and zip code

ATTACH LABEL HERE

name (please print)

address

city state zip code

Mail to: Radio-Electronics
SUBSCRIPTION DEPT., P.O. BOX 2520,
BOULDER, COLO. 80322

\$44.95 KNOW-IT-ALL

CSC's multi-family Logic Probe 1 with memory.
Already the industry standard for performance and value.

This compact, ergonomically versatile test and troubleshooting aid is like a pencil-sized scope at your fingertips. Simply connect its clip leads to the circuit's power supply, set a switch to the proper logic family, and touch the probe tip to the node under test.

LP-1's unique circuitry does the work of a level detector, pulse detector, pulse stretcher and memory. HI LED indicates logic "1," LO LED, logic "0," and all pulse transitions—positive and negative, as narrow as 50 nanoseconds—are stretched to 1/3 second and displayed on the PULSE LED. One-shot, low-rep-rate narrow pulses—nearly impossible to see even with a fast scope, are easily detectable and visible. And you can indefinitely store single-shot as well as low-rep-rate events.

At frequencies above 1 MHz, there is an additional indication with unsymmetrical pulses: duty cycles of less than 30% light the LO LED; over 70% the HI LED. In all modes and circuit states, LP-1's high input impedance virtually eliminates loading problems. The unit also features overvoltage and reverse-polarity protection, interchangeable probe tips, cables and other optional accessories.

Order today. Call 203-624-3103 (East Coast) or 415-421-8872 (West Coast): 9 a.m. - 5 p.m. local time. Major credit cards accepted. Or see your CSC dealer. Prices slightly higher outside USA.

Logic Family Switch—TTL/DTL or CMOS matches Logic "1" and "0" levels; CMOS position also compatible with HTL, HIN L and MOS logic.

PULSE/MEMORY Switch & LED—PULSE position detects and stretches pulses as narrow as 50 nanoseconds to 1/3 sec.; MEMORY stores single-shot and low-rep-rate events indefinitely; HI/LO LED's remain active.

HI/LO LED's—Display level (HI-logic "1", LO-logic "0") of signal activity.

Interchangeable probe tips—Straight tip supplied; optional alligator clip and insulated quick-connecting clip available. Optional input ground lead.

Plug-in leads—36" supplied, with alligator clips. Virtually any length leads may be connected via phono jack.

*Mfr.'s rec. resale. Slightly higher outside U.S.

© 1978 Continental Specialties Corporation

Specifications

Input impedance: 100,000Ω

Thresholds (switch selectable) DTL/TTL HTL/CMOS
logic "1" thresholds (HI-LED) 2.25V ± 15% 70% V_{CC} ± 10%
logic "0" thresholds (LO-LED) 0.60V ± 10% 30% V_{CC} ± 10%

Min. detectable pulse width 50nsec, guaranteed.

Pulse detector (PULSE LED) in PULSE position or PULSE/MEMORY switch 1/3-sec. pulse stretcher makes high-speed pulse train or single events (+ or - transitions) visible; in MEMORY position, first transition lights and latches LED.

Operating temperature 0-50°C





Physical size (l x w x d)

5.8 x 1.0 x 0.7" (1.47 x 25.4 x 17.8mm)

Weight 3oz. (0.085kg)

Power leads removable 36" (914mm) with color-coded insulated clips; others available

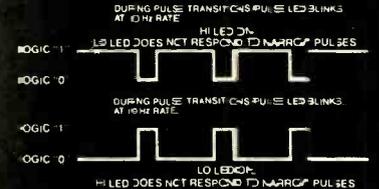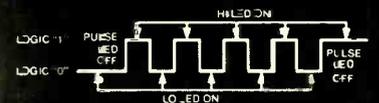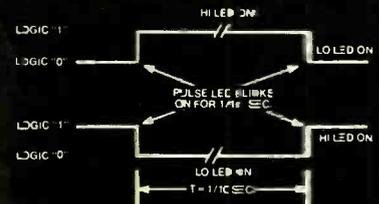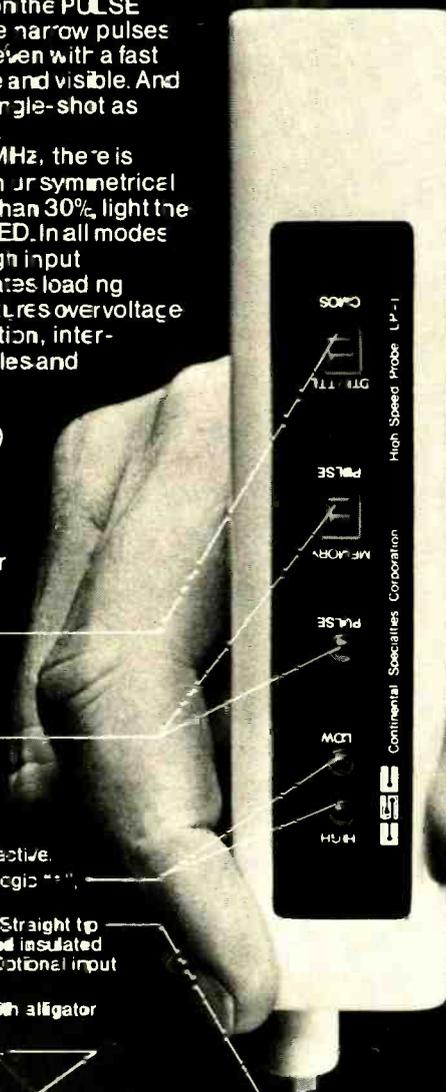Input protection overload, ± 50CV continuous; 117 VAC for less than 15 sec.; reverse polarity, 50V; power leads reverse-voltage protected.



70 Fulton Terrace, Box 1492, New Haven, CT 06509
203-624-3103 FAX 710-465-7227

WEST COAST: 351 California St., San Francisco, CA 94104,
415-421-8372 FAX 910-372-7992

GREAT BRITAIN: CSC UK LTD.

Spur Road, North Feltham Trading Estate,
Feltham, Middlesex, England.

01-850-0782 Int'l Telex: 851-831-3669
CANADA: Len Finkler Ltd., Ontario

CIRCLE 5 ON FREE INFORMATION CARD

NEW LP-1!

New, K40 Magnamount: Grips like a grapple, actually improves transmission.



We double guarantee it.*

Exclusive Octopole Construction.



That's eight magnets set in eight different directions to give you a magnetic seal so complete and powerful, your antenna would stay up there if you could squeeze between two semis passing each other at 180 miles an hour. That's magnetic octopower.

* GUARANTEE I

Placed on the roof of a vehicle; properly tuned, the K40 Magnamount is guaranteed to transmit a further distance than a standard K40 without the Magnamount or you will receive a prompt and full refund from your K40 dealer who installed and tuned the Magnamount K40 for you.

* GUARANTEE II

Materials and workmanship are guaranteed for a full 12 months. Any part that fails to perform satisfactorily will be replaced absolutely free.

Exclusive K40 Flux Harmonics for Greater Transmission.

The magnetic radiation pattern was designed to match the K40 antenna radiation for greater distance than the standard K40. See our guarantee.

The facts: Physics and Physical.

1. Magnamount is a bigger, stronger magnet—in fact it's 8 bigger, stronger, magnets.
2. It doesn't just hold the K40 antenna, it helps it transmit further.
3. Remember the law of reciprocity. The antenna that transmits better, receives better.
4. It provides a flatter, lower SWR because the Magnamount is capacitance grounded.
5. It puts your $\frac{5}{8}$ wave K40 antenna securely in place in the most advantageous place to work against a ground plane—high and free from obstruction. That's square in the middle, right up on top.

\$15.95 buys it.

(SUGGESTED RETAIL)

K40 Magnamount.

American Antennæ 1945 South Street Elgin, Illinois 60120

This professional CB equipment available only through Registered K40 Dealers!

CIRCLE 4 ON FREE INFORMATION CARD

www.americanradiohistory.com