## SI.25 SEPT. 1979 Radio De Electronics The magazine for new ideas in electronics

PerSyn

9

9

Build It Cover Story PERCUSSION SYNTHESIZER

HI-FI NOISE FILTER Build for 14-dB improvement

**PRINTED-CIRCUIT BOARDS** Which ones are best

ANTI-STATIC SPRAY Keeps discs dust free

GERNSBACK

TV VIA SATELLITE What's up there to watch

PROM PROGRAMMER You can build it

ALL ABOUT VCR CIRCUITS Video-signal processing

## \* HOBBY CORNER \* COMMUNICATIONS CORNER

0

0

0

PerSyn MODULATOR

00

FREQ

TRIG

-

0

OIRT

۹ 🕲

PERSYN

9

## A lot of signal. For a little cost.

We just set a new value standard. Twice.



#### Model 2001 Sweepable Function Generator.<sup>™</sup> \$149.95\*

Get the waveforms you need — 1 Hz to .1 MHz in five overlapping ranges: stable, low-distortion sine waves, fast rise/fall-time square waves, high linearity triangle waves — even a separate TTL square wave output. Plus high- and lowlevel main outputs.

An applied DC Voltage at the Sweep input can shift the 2001's frequency; or sweep up to 100:1 with an AC signal.

A pushbutton activates the DC Offset control, which shifts the output waveform up or down on command.

You'd expect to pay a lot more for all the 2001 can do!

#### Model 4001 Ultravariable Pulse Generator.<sup>™</sup> \$169.95\*

Here's a precision digital pulse generator with fast rise and fall times covering 0.5 Hz to 5 MHz in 5 overlapping ranges. With pulse width and pulse spacing each independently variable from 100 nsec to 1 sec for an amazing 10<sup>7</sup>:1 duty cycle range.

You'll find the 4001 delivers the pulse modes you need: Continuous, One-Shot, Triggered, Gated, Square Wave, even a Complement mode. The Trigger/Gate input, 50 Ohm variable output, TTL-level output and Sync output connectors are BNCs.

The 4001. Nothing does as much as well for anywhere near the price.

#### Smarter tools for testing and design.

CONTINENTAL SPECIALTIES CORPORATION

70 Fulton Terr New Haven CT 06509 (203) 624-3103 TWX 710-465-1227 OTHER OFFICES San Francisco (a15) 421-8872 TWX 910-372-7992 Europe CSC UK LTD Phone Salfrom-Walden 0799-21682 TLX 817477 Canada Len Finkier Ltd Dntano Call toll-free for details **1-800-243-6077** 

\* Suggested U.S. resale. Available at selected local distributors. Prices, specifications subject to change without notice. © Copyright 1979 Continental Specialities Corporation

CIRCLE 8 ON FREE INFORMATION CARD

## Don't take our word for it.

"We can heartily recommend the Superboard II computer system for the beginner who wants to get into microcomputers with a minimum of cost. Moreover, this is a 'real' computer with full expandability."

Popular Electronics March, 1979

"(Their) new Challenger 1P weighs in at \$349 and provides a remarkable amount of computing for this incredible price."

Kilobaud Microcomputing February, 1979

"Over the past four years we have taken delivery on over 25 computer systems. Only two have worked totally glitch free and without adjustment as they came out of the carton: The Tektronic 4051 (at \$7,000 the most expensive computer we tested) and the Ohio Scientific Superboard II (at \$279 the least expensive) . . . The Superboard II and companion C1P deserve your serious consideration."

Creative Computing January, 1979

"The Superboard II and its fully dressed companion the Challenger 1P series incorporate all the fundamental necessities of a personal computer at a very attractive price. With the expansion capabilities provided, this series becomes a very formidable competitor in the home computer area."

Interface Age April, 1979

"The graphics available permit some really dramatic effects and are relatively simple to program . . . The fact that the system can be easily expanded to include a floppy means that while you are starting out with a low-cost minimal system, you don't have to throw it away when you are ready to go on to more complex computer functions. Everything is there that you need; you simply build on to what you already have. You don't have to worry about trading off existing equipment to get the system that will really do what you want it to do. At \$279, Superboard II is a tough act to follow."

Radio Electronics June, 1979

Byte May, 1979

"The Superboard II is an excellent choice for the personal computer enthusiast on a budget."



\$279.00 The world's first complete computer system on a board including full keyboard, video display, audio assette interface, 8K BASIC-in-ROM and RAM. Expandable. Requires + 5V at 3 amp power supply.

INLLENGE

C1P \$349.00

Complete with enclosure and power supply. All features of Superboard II. Easy to expand to more memory and floppy disk.


C1P MF \$995.00 The first floppy disk based computer system the world has ever seen for under \$1,000. 8K BASIC-in-ROM, 12K RAM. Expandable to 32K RAM.





1333 S. CHILLICOTHE RD., AURORA, OHIO 44202 (216) 562-3101

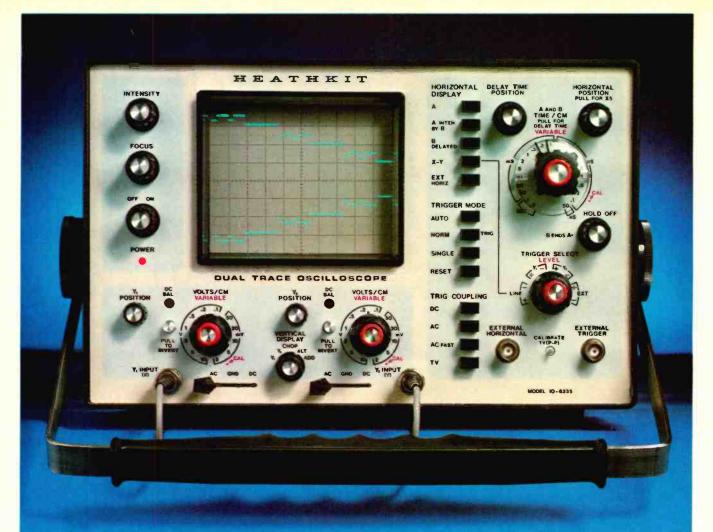See your Ohlo Scientific dealer for full details



#### LABORATORY QUALITY AT SERVICE BENCH PRICES

The most sophisticated scope ever offered in money-saving kit form: the new Heathkit **IO-4235!** Compare its features ...compare prices...and you'll move up to the IO-4235

- DC-35 MHz response with smooth roll-off beyond 50 MHz
- Dual trace study two signals simultaneously
- Delayed sweep observe any section of a waveform - magnified as needed
- Fast sweep speeds from 50 nS/cm to 0.2 sec/cm, plus X5 expansion for effective speed of 10 nS/cm at the highest sweep rate
- TV triggering for jitter-free display
- 2 mV/cm to 10 V/cm vertical sensitivity
- Algebraic ADD with ability to invert  $Y_{1}$  or  $Y_{2}$
- Internal graticule for parallax-free measurements



• 10 kV post-acceleration voltage - fastest, brightest display in any Heathkit oscilloscope ever All these features and more, in a scope that's surprisingly easy to build and maintain! Circuit boards swing out for easy access to components even while the scope is operating. You can make minor service adjustments quickly and

easily - should that ever be necessary. This Heathkit scope is one of the best values today...and for years to come! Kit IO-4235....just \$869.95 Also available factory assembled and tested .... \$1195.00

Prices are mail order net EO.B., Benton Harbor, Michigan. Prices and specifications subject to change without notice.

FREE HEATHKIT CATALOG!

Send for your FREE Catalog with full descriptions of the IQ-4235 and all the other exciting new Heathkit exclusives! Write to: Heath Company, Dapt. 020-570 GX-359 Benton Harbor MI 49022

## din-Electronics

#### THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

#### **Electronics publishers since 1908**

#### SEPTEMBER 1979 Vol. 50 No. 9

BUILD ONE	4 <mark>3</mark>	Cover Story Polytonic Percussion Synthes Easy-to-build modular system blocks and timpani. James J.	simula		
	54	Adaptive Noise Filter Part 2: Dynamic variable-cutol crackle and pop from records Tim Skormond & Gene Garris	and ta		
VIDEO	47	Home Reception Via Satellite What's up there that you migh channels of more television the Robert B. Cooper, Jr.	t want		
	63	VCR Video Signal Processing How the video is handled by V		d Betamax VCR's. Forest Belt	
	83	Service Clinic Those pesky electrolytics. Jac	k Darr		
	83	Service Questions R-E's Service Editor solves rea	ader pr	oblems.	
AUDIO	57	Antistatic Record Care Spray treatment stops static e Len Feldman	lectrici	ity problems permanently.	
	60	R.E.A.L. Sound Lab Tests Set Model RS-660 Stereo receiver			
TECHNOLOGY	4	Looking Ahead Tomorrow's news today. David	d Lach	enbruch	
	50	All About Printed Circuit Boa How to determine which board L. Steven Cheairs		st for your application.	
	68	PROM Programmer Application note tells how to b	ulid or	e. Fairchild Semiconductor	
	76	Hobby Corner The programmable calculator- Earl R. "Doc" Savage, K4SDS		nportant tool.	
	80	Communications Corner Electronic amplification for we Herb Friedman	ak sigr	nals is <mark>f</mark> easible.	
EQUIPMENT	26	ATV Research MVX-500 RF Modulator			
	32	American Antenna K-40 CB A	ntenn	a	
	34	Electra BC220 Programmable	Scan	ner	
	35	Motorola CM540 CB Transcei	ver		
DEPARTMENTS	114	Advertising Index	16	Letter	
	14	Advertising Offices	94	Market Center	
	90	Books	86	New Products	
	88	Communications Products	92	New Lit	
	14 115	Editorial Free Information Card	93	Stereo Products What's News	
	115	rise mormation card	0	WIIGI 3 140W3	

#### **ON THE COVER**

Fascinating percussion synthesizer simulates a variety of percussion instruments. Modular accessories make it even more valuable. Circuits are straightforward....construction is easy....equipment is inexpensive. Full details begin on page 43.



ommercial satellite TV receiving station uses uge dish and supersensitive receiver, but you an build your own. Story starts on page 47.



uild this adaptive noise filter to remove the nap, crackle and pop from your records and apes.

Nadio-Electronics, Published, monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York, VY 10003. Phone: 212-777-6400. Controlled Circulation ostage Paid at Concord, NH. One-year subscription ate: U.S.A. and U.S. possessions, 59-98, Canada, 512-98. Uher countries, 514.98. Single copies \$1.25. © 1979 by Sernsback Publications, Inc. All rights reserved. Printed p. U.S.A. U.S.A.

ubscription Service: Mail all subscription orders, hanges, correspondence and Postmaster Notices of indelivered copies (Form 3579) to Radio-Electronics iubscription Service, Box 2520, Boulder, CO 80322.

stamped self-addressed envelope must accompany all A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

As a service to readers, Radio-Electronics publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, Radio-Electronics disclaims any responsibility for the sate and proper functioning of reader-built projects based upon or from plans or information published in this magazine.



**TV sound:** With all of the 1980 TV models now introduced, It certainly can be said it's "the year of television sound." Last month reported approaches to better sound by RCA, Magnavox and Sylvania. Zenith is capitalizing on improved television audio transmission in several ways. A large percentage of its sets include audio output jacks for attaching to external amplifiers. Some consoles feature four speakers—two on each side. At the high end of the line are sets with separate 10-watt audio amplifiers, including bass and treble cut-boost controls. Quaser, which for several years has featured a pseudo-stereo system known as Audio Spectrum Sound, now extends that feature to several 19-inch sets and six consoles.

Among other trends in the new lines are an increased emphasis on microprocessor tuning systems that eliminate the need to adjust fine tuning even once, and more widespread use of the vertical interval reference (VIR) signal for color set adjusting, as well as comb filters for better color and higher resolution. Zenith has a random-access keyboard tuning system that can tune 105 channels-the standard VHF and UHF channels as well as midband and superband channels used for modern cable systems. Sony introduced the largest direct-view color sets ever offered in this country-with a 26-inch Trinitron picture tube that has a 341-square-inch picture as compared with 315 for a standard 25-inch tube. (The biggest color tube currently being offered commercially, also by Sony-but in Japanmeasures 30 inches in viewable diagonal, 32 inches overall. It isn't offered in a color receiver in the U.S.)

Car stereo fracas: Independent auto sound manufacturers have been up in arms about the tendency of car manufacturers to include radios as standard equipment in their new models, and their campaign against the practice is beginning to bear fruit. Aftermarket car sound manufacturers established an organization, the Custom Automotive Sound Association (CASA), to push their campaign. CASA's first major action was an anti-trust suit against General Motors which had indicated that all of its new "X" cars would be factory-equipped with AM radios. The suit never went to trial. In a settlement, GM agreed to allow dealers to delete the radios, not to force them to buy radio-equipped cars and not to make radios standard equipment before 1983. CASA then turned its sights on Toyota and Volkswagen, filing suits against both of them. Presumably reading the handwriting on the firewall, Honda voluntarily decided to delete radios as standard equipment on its 1980 models. CASA also plans to act on the legislative front, testifying before the Senate Anti-trust Subcommittee on the subject.

**Computers for everyman:** That all-purpose home computer for the non-technical consumer hasn't yet come to pass—but manufacturers still think it will. Texas Instruments has unveiled its long-awaited home computer, a \$1,150 self-contained unit with its own 13-inch color tube (procured from Zenith) with resident extended basic, a 16K RAM, 16-color graphics, a microphone jack, sound synthesizer and cartridges priced from \$10 to \$70 (game software cartridges at \$20 each will be supplied by Milton-Bradley).

RCA's new VIP-II home and business computer has a full keyboard, 8K RAM, 12K ROM, resident BASIC capability, but no monitor, at around \$400. APF introduced a "docking" computer system at \$500 for its video game with 10K RAM, 12K ROM, resident BASIC, color and sound capability for use with a color TV.

The hand-held "language translators" are rapidly evolving into portable computers. TI announced a language translator with a voice synthesizer for \$300, with \$60 modules containing 1,000 words, all words displayed on the readout and half of them pronounced. The translators offered by Craig and Lexicon increased their versatility with new non-language program modules, including made-toorder custom units. Matsushita announced that it would enter the hand-held computer market through agreement with Friends/Amis, which makes the Craig unit, and its American subsidiaries Quasar and Panasonic quickly said they'd market the units in the U.S. under their own brandnames.

**New VCR models:** More than 80 different models of home VCR's have now been introduced (including those already superseded by newer versions). Some of them are similar—even identical—except for the brandname, and all are still produced in Japan. For 1980, there are more manufacturers, more brandnames, longer playing time and a host of new features.


The two new brandnames in the U.S. are Akai and Sharp, both bringing in the first home video recorders produced in their own plants. Akai's is a two-hour-only VHS unit, designed for portable operation, lightweight (15 pounds with battery), but capable of home operation with a companion tuner-timer. The Sharp VHS unit records 6 hours per cassette and is programmable, for seven different recordings seven days in advance, and contains the video version of Sharp's Auto Program Locate Device (APLD) that can cue up to 99 different places on the tape for rapid access. Mitsubishi's first own-make recorder will debut under the MGA label, featuring five direct-drive motors, remote control of most functions, with freeze, fastforward and slow motion, also in the six-hour VHS mode. New Sony-made five-hour Beta models from Sony and Zenith also have complete remote-control systems and permit visible fast-forward and rewind for easy program location. Hitachi will have a portable similar to the one it's making for RCA. JVC, which had stuck with the two-hour single-speed concept in its VHS units, has come up with a new recorder containing four heads (a different pair for each speed), now playing in either the two- or six-hour mode. JVC says the four-head concept permits maximum fidelity in either speed. Its new model permits remotecontrol of freeze-frame, double- and triple-speed playback, infinitely variable slow-motion, is programmable for seven days. Sanyo and Toshiba both introduced programmable five-hour Beta models with visible fast-forward and reverse.

> DAVID LACHENBRUCH CONTRIBUTING EDITOR

## **On your newsstand September 18...**

## the single most exciting issue of any electronics magazine in the Twentieth Century.
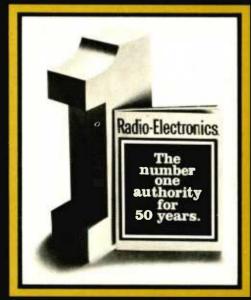
## October 1979 Radio-Electronics. 50th Anniversary Issue



From "Radio-Craft" in 1929 to Radio-Electronics today, and tomorrow, from the vacuum tube to the chip, from "wireless radio" to interplanetary communication—it's fifty years of history, experiments, and excitement from the pages of America's greatest newsstand electronics magazine, all in the most spectacular issue ever of any electronics magazine—October, 1979 Radio-Electronics.

Don't miss a word of this colorful, extra-special retrospective issue, bursting with all the excitement of all those years—or of our experts' fascinating projections and predictions for "The <u>Next</u> Fifty Years" of our lives.

It's October Radio-Electronics. On your newsstand September 18... but not for long. Don't miss it.

## what's news



#### Philips Shows Laser-Scanned 41/2-inch Audio Disc

Digital technology, combined with laseroptics, opened a new era in recorded sound at a two-day demonstration at New York's Plaza Hotel. The revolutionary Phillps Compact Disc system promises an unprecedented improvement in sound quality and realism of prerecorded material.

Combining videodisc technology with pulse-code-modulation and digital recording techniques; Philips showed a prototype system that puts one hour of extraordinary quality stereo sound on one side of a 4½inch diameter disc. The system is expected to ready for the marketplace in 1983. The home player is expected to be of the same size and cost as today's quality players.

The new system converts the original sound into high-density pulse-code-modulation and replaces the playback stylus with a low-power solid-state laser.

Compared to conventional LP and 45rpm audio discs, the Compact Disc (CD) provides a flatter frequency response; essentially flat from 20 to 20,000 Hz with stereo channel separation of 80 dB. Signalto-noise ratio and dynamic range are boosted to 85 dB—a substantial improvement over the 60 dB currently available.

An additional advantage is immunity to surface noise and hiss. Since there is no stylus riding in a groove, only a laser light beam touches the disc, there is no surface hiss, clicks, turntable rumble, room vibrations or pickup arm resonances to detract from the recorded sound.

To convert the analog signal into digital form in the CD system, the sound is sam-

pled 44,330 times each second, more than twice the audio bandwidth. These samples are then quantized and converted into binary 14-bit "words" through Pulse Code Modulation techniques.

Each hour-long CD recording is made up of 6-billion blts, encoded along a helical track of pits on this disc. This disc is quite sImilar to the Phillips videodisc described in **Radio-Electronics**, April 1979 issue. The helical track is tightly spaced—separation between tracks is only 1.66 microns and  $2\sqrt{2}$  miles of recording is fitted on each  $4\sqrt{2}$ inch diameter disc.

To retrieve the sound, the disc is inserted track-side down into the playback unit which permits automatic play or manual search for a specific selection. A miniature AlGaAs (Aluminum Gallium Arsenide) diode laser, located below the disc, is focused on the track and converts the encoded material back into an electronic signal. The track is scanned from the center of the record to the outer edge as the disc turns at speeds between 215 to 500 rpm to maintain a constant linear velocity between the disc and laser.

The Philips Compact Disc System is the first of it's kind to be designed for the audio market that looks like it may be able to destroy the "distance" (and the difference) between the recording studio and the listeners living room. It's the first to incorporate the digital decoding electronics in the playback unit and, with the laser scanner, it's the first to insure agaInst deterioration of the recorded material as it is played back.

#### **JVC Videodisc Shown**

Shown to the press for the first time during the Summer CES Show, JVC revealed their version of a capacitive video disc. It, like the RCA unit (Radio-Electronics, April 1979) uses a contact stylus. Unlike the RCA system it does not ride in a groove. Instead it rides over the surface of the disc. Victor claims that capacitive systems tend to be less expensive that optical disc systems.

The capacitive videodisc is made of an electroconductive plastic into which 54,000 spiral tracks consisting of pits in the base material are formed. During playback the stylus, mounted on the end of a cantilevered pick-up arm, is guided along the disc surface following the helical track. The stylus tip contains an electrode that receives information from the disc. It has an anticipated life of 2000 hours and as it wears down, new portions of the electrode are exposed.

The disc spins at 900 rpm, and with accessory optional equipment, can provide a still picture (maximum of one hour playing time), forward and reverse motion at normal speed, variable speed slow motion, variable speed fast motion, and high-speed search.

It is also possible to add on a randomaccess unit that permits accurate location



and retrieval of desired recorded material and automatic playback in any mode. JVC also demonstrated the ability to use their videodisc player for audio records. To use the player for this purpose a pulse-codemodulation (PCM) decoder is connected to the player. The random-access unit, when combined with the PCM feature provides retrieval of any music selection.

Like both the RCA and Philips videodisc systems a maximum of two hours of playback time, one hour on each side of the disc, is provided. The disc measures  $11^{-7/6}$  inches in diameter, is  $\frac{1}{10}$ -inch thick and Is scanned by a saphire stylus.

There has been much speculation about the possibility of JVC and RCA agreeing on a format for a capacitive videodisc, but to date this appears to be only speculation. As of this writing there is no such agreement and the two disc systems, while having some similarities, are not compatable, nor is either one compatable with the Phillps system.

JVC had no comment on when the players would be available.

llan **Confess.** 

### To sell an advanced DMM for under \$70 we had to cut corners.



And we sure did! First, we cut off the dealer's mark-up. Then we shaved off the overhead costs of national sales offices and warehouses. Finally, as if that wasn't enough, we even cut out the high labor costs of factory assembly lines.

All in all, we cut over \$100worth of corners! But not a single one that affected the quality and performance of our new DMM.

#### Don't let our low price fool you!

Because Sabtronics sells factory-direct – without all the hidden charges a dealer would track on – we can offer the superior 2010A DMM kit for a surprisingly low \$69.95. Surprising because you get the accuracy, features and performance you'd expect from the high priced units.

The 2010A offers you the long-term accuracy of a laser-trimmed resistor network, an ultrastable band-gap reference element and single chip LSI circuitry – all in a compact, rugged, human-engineered housing. With 31 ranges and 6 functions, you can measure AC and DC volts from 100  $\mu$ V to 1000V; AC and DC current from 0.1  $\mu$ A to a surprisingly high 10A; resistance from 0.1  $\Omega$  to 20 MΩ. Typical DCV and Ohms accuracy is 0.1% ± 1 digit. And you see these precise readings on a bright, 3½-digit

#### **Brief Specifications**


DC volts:  $100\mu V$  to 1000V in 5 ranges AC volts:  $100\mu V$  to 1000V in 5 ranges DC Current:  $0.1\mu A$  to 10 A in 6 ranges AC Current:  $0.1\mu A$  to 10 A in 6 ranges Resistance: 0.10 to 20 M $\Omega$  in 6 ranges Diode Test Current:  $0.1\mu A$ ,  $10\mu A$ , 1mAACV Frequency Response: 40Hz to 40kHzInput Impedance: 10 M $\Omega$  on ACV and DCV

Overload Protection: 1200 VDC or RMS on all voltage ranges except 250 VDC or RMS on 200mV and 2V AC ranges. Fuse protected on ohms and mA ranges.

Power Requirement: 4.5 to 6.5 VDC (4 "C" cells) optional NICd batteries or AC adapter/charger Display: 0.36" (9.2mm) Digits reading to ± 1999 Size: 8"W x 6.5"D x 3"H (203 x 165 x 76 mm) Weight: 1.5 lbs. (0.68kg.) excl. battery LED display with automatic decimal placement and large, 9mm numerals.

Of course, that's what you'd expect from a quality DMM. But we've even added more features for *extra* convenience, flexibility and reduction of human error.

- Unique X10 Multiplier Switch gives you convenient push-button selection to the next higher decade range. Hi-Lo Power Ohms capability gives you three high-ohms ranges that supply enough voltage to turn on a silicon junction for diode and transistor testing. For in-circuit resistance measurement without turning on a semiconductor junction, you use the three low-ohms ranges.
- Wide Frenquency Response 40Hz to 40kHz bandwidth lets you measure audio through ultra-sonic AC signals.
- Touch and Hold Capability with optional probe, retains readings for as long as you wish. You can make measurements in hard-

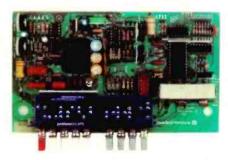

to-reach places without taking your eyes off the probe tip or stopping to record data.

 Plus More – Auto Polarity, Auto Zero, Overrange indication and fully overload protected on all ranges.

And, although designed for benchtop use, the sleek, compact 2010A is powered by 4 "C" cells (not included), bringing wide-range lab performance to the field when you need it.

#### You save either way.

Your 2010A DMM kit comes complete with easy-to-follow assembly instructions, all parts (including high-impact case), and test leads. You can complete assembly in a single evening. However, for a slight additional fee, Sabtronics will ship your 2010A factory-assembled and calibrated: at \$99.50 it's still an incomparable value!

Whether you're a professional or hobbyist, if quality and accuracy are important – and padded prices aren't – you should inspect the 2010A DMM for yourself. If you're not completely satisfied, return it in its original condition within 10 days for a prompt and courteous refund of purchase price. Call us with your MasterCharge or Visa order today, or simply fill out the convenient order form.

Making Performance Affordable



13426 Floyd Circle M/S 35 · Dallas, Texas 75243 Telephone 214/783-0994

To: Sabtronics International, Inc.	13426 Floyd Circle M/S 35, Dallas,	TX 75243
Please send me		
Model 2010A Digital Multimeter kit(s) @\$	69.95 plus \$4.00† shipping and handling each	. s
Model 2010A Digital Multimeter Assemble	ed @ \$99.50 plus \$4.00† shipping and handling each	h \$
# AC-115 AC adapter/charger(s) @\$7.50	0 each	\$
# NB-120 NiCd Battery set(s) @\$17.00/s	set	
# THP-20 Touch and Hold Probe(s) @\$1	8.00 each	s
For delivery In Texas, add 5% Sales Tax		s
l enclose 🗅 check 🛛 money order for	TOTA	L S
or, please charge to my Visa MasterCharg		
Account No.	Expiration Date:	
Name		
Street		_ Apt
City	State	Zin
Continental U.S. only. AK, HI & PR. \$5.00 Canada: 56.5		

#### Learn to service 2-way radio, microwave systems, AM/FM transmitters,

## with NRI's Complete

#### Learn installation and maintenance of commercial, amateur or CB communications equipment.

There are more than 25 million CB sets out there, millions more two-way radios, walkie-talkies, and other communications apparatus in use by business, industry, government, police and fire departments, and individuals. That means a lot of service and maintenance jobs...and NRI can train you at home to fill one of these openings. NRI's Complete Communications Course covers all types of two-way radio equipment...AM and FM transmission

and reception, television broadcasting, microwave systems, radar principles, marine electronics, mobile communications, and aircraft electronics. And NRI guarantees you will pass the exam for the commercial FCC Radiotelephone License you need to perform most servicing work, or your tuition will be refunded in full. This money-





back agreement is good for six months after completion of your course.

#### Learn on your own 2-meter, digitally synthesized VHF transceiver.

You'll learn to service all types of communications equipment as you assemble your own VHF transceiver. NRI engineers have designed it, not only as a commercial-quality, highperformance unit, but as a unique "power-on" training tool to give you actual bench experience with the principles needed to service commercial, CB, and amateur equipment.

#### Then we help you get your FCC Amateur License so you can go on the air.

The complete course includes 48 lessons, 9 special reference texts,

and 10 training kits. Included are your own electronics Discovery Lab,<sup>®</sup> antenna applications lab, CMOS digital frequency counter, and 7-scale AC/DC volt-ohm meter. You'll learn at home, at your own convenience, getting the training you need for your FCC License and the communications field of your choice.

### CB specialist course also offered.

If you prefer, you can concentrate on the big field of CB radio with NRI's special course in CB servicing. You get 37 lessons, 8 reference texts and plenty of "hands-on" training with your own 40-channel CB, AC power supply, and multimeter. Also included are 14 coaching units to make it easy to get your commercial Radiotelephone FCC License...required for you to test and service communications equipment.

## **Communications** Course.

## Orget into TV and audio servicing.

#### **NRI** instructor/engineers

Each NRI student is assigned his own course instructors, there to help you over any rough spots, explain problems, and give you the advice you need as you progress toward your future. And each one knows what he's talking about, because he was more than likely involved in the design of your course or some of the NRI equipment vou use. NRI instructors are practical, experienced people who really know their field and do their best to pass their knowledge on to you.

#### You get more for your money from NRI.

NRI employs no salesman, pays no commissions. We pass the savings on to you in reduced tuition, topquality professional equipment, and reliable testing instruments necessary for a successful career. You can pay hundreds of dollars more at other schools, but you can't get better training.

#### Free catalog... No salesman will call.

Get your free catalog and discover why NRI is the leader in home technical training. In 65 years of service, we've helped over a million students start to build new careers. Mail the card today and get started on your new future. If card has been removed. write to:



NRI SCHOOLS McGraw-Hill Continuing Education Center 3939 Wisconsin Avenue Washington, D.C. 20016

NRI can train you at home to service TV equipment and audio svstems. Choose from courses to meet your needs and budget, with our complete Master Course in TV/Audio/ Video Systems Servicing covering the entire field of electronic home entertainment. You learn to install and repair stereo systems, PA systems, car radios and tape players, musical instrument amplifiers, video tape and disc units, AM/FM radios, black and white and color TV. You get practical bench training as you build your own 25" (diagonal) solidstate color TV complete with computer tuning that lets you program an entire evening's entertainment. You also assemble your own solid-state stereo and professional test instruments.



It's the kind of training that's already helped thousands of pros. Send card for free catalog.

### Learn computer electronics.

#### Now! Build your own microcomputer as you train.

Train to become one of the new breed of computer technicians...at home with both the equipment hardware and the programming software. Over two years and one-half million dollars in development, the new NRI course in Microcomputers and Microprocessors covers this exciting new opportunity field thoroughly and

completely. As you learn, you get "hands-on" experience, building test instruments you use and keep, proving theory in the unique NRI Discovery Lab<sup>®</sup> and assembling the exclusive NRI designed-for-learning microcomputer. This unique "teaching" machine demonstrates and clarifies concepts from the very first stages of construction. Finished, it's a completely functional dual-language unit, ready to go to work as your personal microcomputer or basis for a commercial system. It's all part of the most

up-to-date, complete home study course ever offered. Mail the card for full facts.

## what's news



#### Heath Computer Kits—Heath Data Systems

the Heath Company. Now, in addition to their kit line, they've started a new division-Heath Data Systems. This division will market assembled computers through retail outlets such as computer stores.

Along with the announcement is an introduction of several new hardware items. Here's a quick rundown. Shown at the top of this column is the Heath H89 all-in-one computer, It's available in both kit form for \$1595. Wired and ready to use as model WH89, it costs \$2295. It puts into one package floppy disc storage, a smart video terminal, two Z80 microprocessors, 16K RAM expandable to 48K, professional keyboard and a numeric keypad.

The terminal and the computer each have their own Z80, so the terminal never shares processor power with the computer. This makes the terminal capable of a multitude of high-speed functions.

All terminal functions can be controlled by keyboard or softwear. Eight user-definable keys let your program your own special functions. Baud rates up to 19,200 are keyboard selectable. The 12-inch screen is formatted for 25 lines by 80 characters, upper and lower case, formed by 5X7 dot matrix. Lower case letters with decenders such as "g" use a 5×9 dot matrix. Direct cursor addressing permits inserting or deleting characters and lines anywhere on the screen and gives you line graphics capability from keyboard or computer.

The floppy is a Wangco 82 single-drive system. Each 51/4-inch diskette has more than 102K bytes of storage area.

Also introduced was the H19 Smart Video Terminal. It's \$675 as a kit, or \$995 as

Computers must be really doing a job for fully wired model WH19. The terminal interfaces with either the Heath H8 or H11 computers or with any RS-232 interface. It uses a Z-80 microprocessor. Like the H89 it works at baud rates up to 19,200 (keyboard selectable) and has 8 user-definable keys. Format on the 12-inch screen is 24 lines by 80 characters (with software controlled 25th line).

> Included in the products is the H14 line printer at \$595 in kit form and \$895 as an assembled WH14. It is microprocessor controlled and delivers a permanent hard copy printout. The unit prints the standard 96-character ASCII set (upper and lower case) with a 5×7 dot matrix print head. The impact printer uses readily available 1/2-inch wide nylon ribbon on 2-inch spools.

> Maximum Instantaneous print speed is 165 characters per second with a selectable line length of 80, 96 or 132 characters. Line spacing is 6-lines-per-inch with 8lines-per-inch software selectable. Baud rates are selectable from 110 to 4800. An adjustable width sprocket feeds allows the use of edge-punched fan-fold forms from 2.5 to 9.5-inches wide.

> Finally a modem, the WH13, is now available for \$195 wired. Use it to let your computer talk to other computers over ordinary telephone lines. Features selectable originate and answer modes. LED display of unit status and special acoustic self testina.

> That's the latest on computers from heath. They promise even more products to be added to the computer line in the months to come. It looks like Heath intends to keep computers as a major product line. That's good news indeed.

#### **Texas Instruments New Computer**


It has finally arrived. The TI-99/4; the home computer that Texas Instruments has been talking about for the last two years. The new machines using plug-in software modules as ready-made computer programs that provide a wide variety of user capabilities.

The computer consists of a console with 16K RAM, many sound effects, 16 colors for graphic display, extended BASIC as a programming language and a 13-inch color video monitor. The system is priced at




\$1150. Software modules cost between \$19.95 and \$69.95.

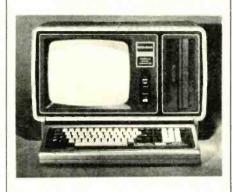Existing modules Include Demonstration, Home Financial Decisions, Household Budget Management, Video Chess, Investment Analysis, Early Reading, and Tax and Investment Recordkeeping.


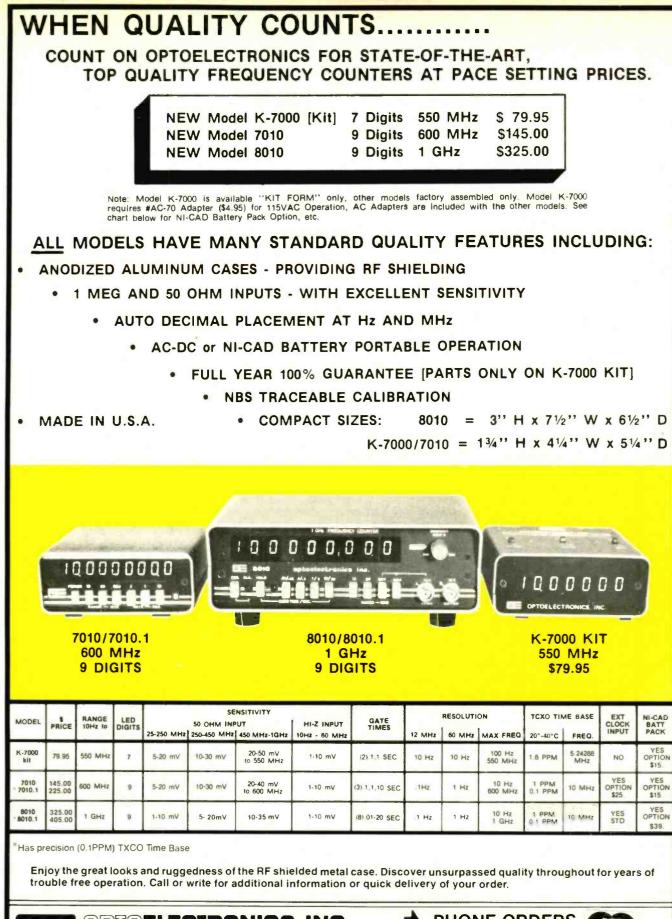
#### **TRS-80 Model II Announced**

The TRS-80 now has a bigger brother, the new Model II, designed to meet the needs of many users for more data storage, greater versatility and higher computing speed. The // has either 32 or 64K bytes of RAM and a built-in 8-inch floppy. It includes a 12-inch monitor that displays 24 lines of 80 characters either upper or lower case. The price will be \$3450.



OPTOELECTRONICS, INC. 5821 N.E. 14th Avenue, Fort Lauderdale, Florida 33334 PHONE ORDERS (305) 771-2050

TERMS: Drders to U.S. and Canada, add 5% for shipping, handling and insurance to a maximum of \$10.00. All other orders, add 10% C.O.D. collection, fee \$1.00. Orders under \$15.00 add extra \$1.00 handling. Regular checks must clear before order is shipped. Florida residents add 4% sales tax

VISA

## editorial

### The Fight Against Cancer—A Turn Towards Electronics!

If asked, we all pretty much agree that electronics is beneficial to mankind. We point to accomplishments in communications, data processing, energy conservation and generation, automation, entertainment, and on and on. We describe the roles of electronics in the industrial manufacturing process, collision avoidance, vehicular technology, navigation, etc. But strangely enough, most of us would probably overlook one important area—medical electronics.

A news item crossed my desk the other day and it made me feel proud just to be a part of this industry. The item described the use of RF energy in the fight against cancer. The treatment is called RF hyperthermia and is very much experimental. RF energy, ranging in frequency from several megahertz to the microwave area, is used to heat and thus destroy cancerous tumors. Cancer cells appear to be more susceptible to heat than normal cells. There are several theories, but it is more commonly accepted that cancer tumors have a limited blood supply and cannot disperse the heat as readily as normal tissue, making them more susceptible to the heat.

Hyperthermia is not new. Researchers have experimented with raising the temperature of the whole body instead of just the cancer site. They have also experimented with combining hyperthermia with radiation treatments, hoping that less radiation would be required. What is new, is using RF energy to perform the actual heating. By using RF energy, the researchers have much more precise control over temperature and localization.

It must be stressed that *the use of hyperthermia is experimental.* Some researchers argue that the increased blood flow around the heated tumor might actually have a cancer spreading affect. What is needed is far more research. The problem is that very little RF hyperthermia equipment actually exists. As a result, researchers are finding it difficult to experiment with it. For now, RF hyperthermia remains only as a treatment of last resort.

I do find it interesting though, that after all these years of surgery, chemotherapy and radiation treatments, researchers are turning towards electronics. If you are as proud as I am of being a part of this industry, you now have just cause for feeling prouder still.

# RADIO-ELECTRONICS

arthleiman

ART KLEIMAN MANAGING EDITOR

### Radio-Electronics .

Hugo Gernsback (1884-1967) founder M. Harvey Gernsback, editor-in-chief and publisher

Larry Steckler, KTX-3644, CET, editor

Arthur Kleiman, KTZ-3288, managing editor

Robert F. Scott, CET, W2PWG, KXK-8533, technical editor

Jack Darr, CET service editor

Leonard Feldman contributing high-fidelity editor

Karl Savon, semiconductor editor

Herb Freidman, communications editor

David Lachenbruch, contributing editor Earl "Doc" Savage, K4SDS, hobby editor

Ruby Yee, production manager

Robert A. W. Lowndes, production associate

Marie J. Stolfi, production assistant

Gabriele Margules, circulation director

Arline R. Bailey, advertising coordinator

Cover design by Louis G. Rubsamen Cover photo by Bob Lewis

**Radio Electronics** is a member of the *Institute of High Fidelity* and is indexed in *Applied Science & Technology Index* and *Readers Guide to Periodical Literature.* 

Gernsback Publications, Inc. 200 Park Ave. S., New York, NY 10003 (212) 777-6400 President: M. Harvey Gernsback Vice President: Larry Steckler Treasurer: Carol A. Gernsback Secretary: Bertina Baer

#### ADVERTISING SALES

Paul McGinnis Director of Marketing

#### EAST

Stanley Levitan Radio-Electronics 200 Park Ave. South New York, NY 10003 (212) 777-6400

#### MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen The Ralph Bergen Co. 540 Frontage Road—Suite 361-A Northfield, Illinois 60093 (312) 446-1444

#### PACIFIC COAST Mountain States

Jay Elsenberg J.E. Publishers Representative Co., 8732 Sunset Blvd., 4th Floor, Los Angeles, CA 90069 (213) 659-3810 Sales Mart Building 1485 Bayshore Blvd., Box 140 San Francisco, CA 94124 (415) 467-0125







**CIRCLE 29 ON FREE INFORMATION CARD** 

1979

SEPTEMBER

TEPS

RADAR JAMMER This is in response to your editorial comments concerning speed radar jammers in the December 1978 issue.

I recently received a flyer for a police radar calibrator ("illegal to use to jam police radar") that may be the device you refer to. Such a device can indeed cause a stationary Doppler radar to give a false reading if they are both in the same frequency band (X, K or whatever). However, consider this:

A moving oncoming police radar (for example, Kustom Signals' MR-7) probably will not be adversely affected by the steady tone that would jam a stationary radar. This is because internally the unit has two audio bands-a low Doppler band, representing the police-cruiser speed with respect to the road surface, and a high Doppler band within which the heterodyne signal from the oncoming vehicle will fall. The high-frequency band signal will represent the sum of the speeds of the cruiser and the target.

In real life this sum might be equal to 115 mph (cruiser, 50 mph; target, 65 mph).

In this example, in order to jam the radar, you would need to transmit an indicated speed of 105 mph. Suppose the cruiser slows down to 35 mph; you will pass him and indicate 70 mph. At 105 mph the stationary Smokey will just love you.

Such a moving radar can be jammed by using a glide tone passing through the high Doppler band. This must change at a rate indicating a speed change greater than 3.15 mph. This causes the internal verifier circuits to reject the Input. The effect of this technique on a stationary radar is unpredictable and not worth the risk.


There are also serious side effects in transmitting your own signal: 1) your own radar detector is overwhelmed and useless; 2) every detector in the oncoming traffice lanes will be set off, resulting in a mass slowdown. (A recent excursion down an interstate highway while testing a prototype microwave device, not a jammer, pointed

this out. No one could spot the Smokey, so everyone slowed down.)

A practical jammer is feasible, but It would need to be activated only when an Incoming signal is present and would have to transmit CW (Continuous Wave) at an offset from the police signal that would produce the desired heterodyne.

Passive methods are possible. Create a plasma screen large enough to hide your vehicle behind, then turn it on and off at the desired rate to modulate the returned microwave energy. A bank of neon or fluorescent tubes on the front would do it. A tuned cavity with a modulating device will return a jamming echo within 50 to 60 feet of a roadside radar. You could coat your vehicle with microwave absorber and then make them think you are a big fuzzy caterpillar.

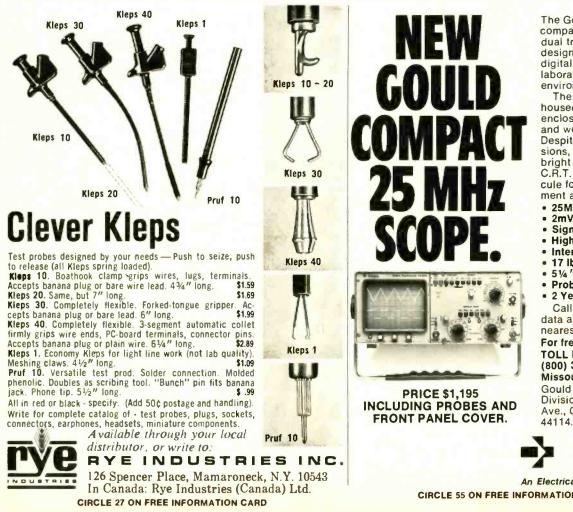If these so-called jammers proliferate, the only result will be increased confusion on the highways and the opportunity for government agencies to intrude further continued on page 22



The Gould OS1200 is a compact portable 25MHz dual trace oscilloscope designed for analog and digital applications in both laboratory and field service environments.


The oscilloscope is housed in a rugged metal enclosure only 51/4" high and weighing under 17 lbs. Despite its compact dimensions, the unit features a bright 5" rectangular C.R.T. with internal graticule for optimum measurement accuracy.

- 25MHz Bandwidth
- 2mV Sensitivity
- **Signal Delay** 
  - High Brightness C.R.T.
- Internal Graticule
- 17 lbs. Weight
- 51/4 " x 12" x 161/2" **Probes Included**
- 2 Year Warranty

Call today for complete data and location of your nearest distributor. For free brochure call: TOLL FREE NUMBER (800) 325-6400. In Missouri (800) 342-6600. Gould Inc., Instruments Division, 3631 Perkins Ave., Cleveland, Ohio

GOUL

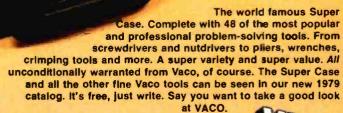An Electrical/Electronics Company CIRCLE 55 ON FREE INFORMATION CARD



Vaco Products Company, 1510 Skokie Blvd.,

**CIRCLE 37 ON FREE INFORMATION CARD** 



Northbrook, IL 60062 U.S.A.

lakeagood

ookatV


THE SUPER CASE 70260

## At CIE, you get electronics career training from specialists.

If you're interested in learning how to fix air conditioners, service cars or install heating systems – talk to some other school. But if you're serious about electronics, come to CIE – The Electronics Specialists.

the El

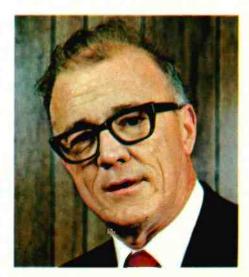Special Projects Director Cleveland Institute of Electronics



y father always told me that there were certain advantages to putting all your eggs in one basket. "John," he said, "learn to do one important thing better than anyone else, and you'll always be in demand."

I believe he was right. Today is the age of specialization. And I think that's a very good thing.

Consider doctors. You wouldn't expect your family doctor to perform open heart surgery or your dentist to set a broken bone, either. Would you?

For these things, you'd want a specialist. And you'd trust him. Because you'd know if he weren't any good, he'd be out of business.

#### Why trust your education and career future to anything less than a specialist?

You shouldn't. And you certainly don't have to.

FACT: CIE is the largest independent home study school in the world that specializes exclusively in electronics.

We have to be good at it because we put all our eggs in one basket: electronics. If we hadn't done a good job, we'd have closed our doors long ago.

### Specialists aren't for everyone.

I'll tell it to you straight. If you think electronics would make a nice hobby, check with other schools.

But if you think you have the cool – and want the training it takes – to make sure that a sound blackout during a prime time TV show will be corrected in seconds – then answer this ad. You'll probably find CIE has a course that's just right for you!

#### At CIE, we combine theory and practice. You learn the best of both.

Learning electronics is a lot more than memorizing a laundry list of facts about circuits and transistors. Electronics is interesting because it's based on some fairly recent scientific discoveries. It's built on ideas. So, look for a program that starts with ideas – and builds on them.

That's what happens with CIE's Auto-Programmed® Lessons. Each lesson uses world-famous "programmed learning" methods to teach you important principles. You explore them, master them completely... before you start to apply them!

But beyond theory, some of our courses come fully equipped with the electronics gear to actually let you perform hundreds of checking, testing and analyzing projects.

In fact, depending on the course you take, you'll do most of the basic things professionals do every day – things like servicing a beauty of a Zenith color TV set... or studying a variety of screen display patterns with the help of a color bar generator. Plus there's a professional quality oscilloscope you build and use to "see" and "read" the characteristic waveform patterns of electronic equipment.

#### You work with experienced specialists.

When you send us a completed lesson, you can be sure it will be reviewed and graded by a trained electronics instructor, backed by a team of technical specialists. If you need specialized help, you get it fast ... in writing from the faculty specialists best qualified to handle your question.

#### People who have known us a long time, think of us as the "FCC License School."

We don't mind. We have a fine record of preparing people to take ... and pass... the governmentadministered FCC License exams. In fact, in continuing surveys nearly 4 out of 5 of our graduates who take the exams get their Licenses. You may already know that an FCC License is needed for some careers in electronics – and it can be a valuable credential anytime.

#### Find out more: Mail this card for your FREE CATALOG today!

If the card is gone, cut out and mail the coupon.

I'll send you a copy of CIE's FREE school catalog, along with a complete package of independent home study information.

For your convenience, I'll try to arrange for a CIE representative to contact you to answer any questions you may have.

Remember, if you are serions about learning electronics... or building upon your present skills, your best bet is to go with the electronics specialists – CIE. Mail the eard or coupon today or write CIE (and mention the name and date of this magazine), 1776 East 17th Street, Cleveland, Ohio 44114.



Patterns shown on TV and oscilloscope screens are simulated.

CIE	Cleveland Institute of Electronics, Inc. 1776 East 17th Street, Cleveland, Ohio 44114
	1776 East 17th Street, Cleveland, Ohio 44114

Accredited Member National Home Study Council YES...John, I want to learn from the specialists in electronics-CIE.

Send me my FREE CIE school catalog – including details about troubleshooting courses – plus my FREE package of home study information. RE-71

Print Name	
Address	Apt
City	
State	Zip.
Age	Phone (area code)
Check box for G.I. Bill information Mail today:	: Veteran Active Duty


#### LETTERS continued from page 16

into our personal llves. Oh yes, the 55-mph limit has had one good effect: Look at the shot in the arm it gave the electronics industry! RICHARD L. PEARSON Pearson Electronics

Gastonia, NC
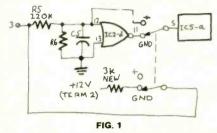
#### WIPER DELAY MODIFICATION


The following modifications (shown in the diagrams) to the Digital Windshield Wiper Delay described in the November 1978 issue of Radio-Electronics make it possible to operate the device on either switched + 12 volts or switched-ground circuits at the flip of a switch (see Fig. 1). I have also



provided an emergency bypass switch in case it (the device) fails (see Fig. 2). New components required are a 3K resistor, a DPDT switch and an SPDT switch.

(The diagram also shows the cathode of D2 was moved to + 12V at terminal 2.)

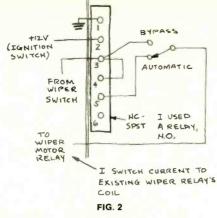I installed my unit in a '74 Ford Courier



(switched ground) and it works fine. I've used it in mist for one to two hours total so far. Thanks for the article. MILES ABERNATHY Austin, TX

#### **APRIL FOOLS**

When I received my April 1979 copy of Radio-Electronics, I was agreeably surprised at the three Special April Projects. The One Station Intercom is a must for every hermit. The Solar-Powered Night Light needs an on-OFF switch, otherwise a great deal of energy, which we need to conserve, is wasted.

I assume that Messrs. Weinstein and Gartman are proteges of those two widely known authors of previous years-Mr. Larson E. Rapp (WIOU of Amateur Fame) who wrote for QST such articles as "Negative

Modulation" (thus doubling the number of stations in a given spectrum), "Underground Antennas," Circular Hamband Theorem," etc.; and your own Mohammed Ulysses Phips who is no doubt best known for his 1962 article "An Electronic Shaver" (cordiess yet!). That one had a technician friend of mine actually accumulating the required components for three days until we pointed out that it was not a "construction" article!

I thoroughly enjoy Radio-Electronics, have for the past 20 or so years, and hope to continue for the next 20. Keep up the good work.

HERBERT M. PLUMMER Catharpin, VA

#### DIGITAL REFERENCE CHARTS

The Digital Reference Charts on page 45 of the November 1978 issue are guite informative. However, according to what I was taught in a digital course I took in college. the sample addition of the two binary numbers 111 and 111 are equal to 1110 and not 1010.

I enjoy your magazine very much. WILLIAM HAINER Hazelwood, MO

#### SOLAR CONTROLLER

With the current interest in solar energy, the article entitled "Solar Controller" (December 1978, page 35) should be of interest to many readers. Further articles on this topic would also be appreciated.

Probably many readers have noticed that the control, labeled "Hysteresis" in Figs. 5 continued on page 24



## ix it on the

SOAR's portable, battery-operated counters and multimeters are so light and convenient that you can take them anywhere your ham or CB equipment goes. Two models have been engineered specifically for the radio hobbyist and CB operator.

#### FC-841 MULTIFUNCTION FREQUENCY COUNTER

This seven-digit counter covers the entire ham and CB ranges from 10 Hz to 50 MHz. The tilt-view stand all-steel



case and the 3" high LED readout make troubleshooting easy no matter where you are. Supplied with four AA batteries, the counter can also be plugged into any AC outlet (AC adapter optional) or your car's cigarette lighter. Price: \$90.00



#### S-20 ANALOG MULTIMETER

At our price and for all its features, this instrument has no equal. The rugged d'Arsonval meter movement guarantees accuracy and sensitivity-30,000 ohms per volt DC. And let's not forget the five function modes-DCV, ACV, DCmA, Ohms, and dB-and the twenty measurement ranges. Price: \$35.00

Call or write TODAY to find out more about the FC-841 and S-20-and why not also inquire about our complete line of multimeters and frequency counters.



SOAR ELECTRONICS (U.S.A.) CORP. 200 13TH AVENUE RONKONKOMA, NEW YORK 11779 TEL. (516) 981-6444/TELEX 144638

CIRCLE 33 ON FREE INFORMATION CARD

## YOUCANGET TWICE AS BIG A DEAL AT GENERAL ELECTRIC.

### BUT ONLY DURING SEPTEMBER & OCTOBER.

Earning "pro plus" points by stocking up on GE receiving tubes, triplers and semiconductors was a big deal before. But now we've gone one better by <u>doubling</u> the deal!

That means you have twice as many reasons for saving those valuable tags, bags and flaps—and for submitting them to GE "pro plus" Award Headquarters before October 31. Each one will be worth twice its normal value in "pro plus" award points. Which means you can double the rate at which you earn that award or weekend-for-two trip you have in mind.

We cannot extend the time limit for this kind of double-dealing; but no one will ask questions if you decide to boost the size of your order. Just remember to save the tags & bags & flaps and turn 'em in during September and October. We want to be sure you get the big deal you deserve.

### WE'RE AT YOUR SERVICE.

Tube Products Department-Owensboro, Kentucky 42301



#### **LETTERS** continued from page 22

and 7, is actually a "Trip Point" setting and that the circuit has no hysteresis. A suitable hysteresis effect can be achieved with the addition of two resistors (see diagram).

For a hysteresis of 5°F to 10°F, the resistance ratio would be on the order of  $R_1 =$ 240  $R_2$ . The exact values can be determined in the experiment Mr. Kreuter describes on page 37. The 47-ohm resistor should be increased somewhat to insure that minimum turn-on minus hysteresis is greater than zero. A change in the value of hysteresis will affect the calibration of the trip point.

CYRUS W. ROTON China Lake, CA

#### **RADAR DETECTORS**

Radar detectors are, in my opinion, a good thing. I've been running a *Micronta* X-K (Radio Shack) detector for a little over nine months now, and I am well pleased.

I do not condone speeding; I just like to know where the police radar is. There are many times the police (all of whom I know personally) in my town will issue a traffic citation for going 37 mph in a 35 mph zone.

As for the miniradar transmitter you mentioned, it is a neat idea, but to be effective it would have to be in continuous operation what with the new radars now being in *moving* police cars. These police radars automatically deduct the speed of the po-

lice car, and register the speed of the clocked vehicle. The officer can turn off the radar until the suspicious car is just within range, turn it on, clock your speed and have you pulled over before you know what happened.

Some people I know have taken a 10,000-MHz amateur transcelver (a frequency range where pulse transmission is FCC-authorized) and modified them to work from 9320 MHz-9500 MHz (police X-band) or 10,500 MHz-10,750 MHz (approximate police K-band) with pulse transmission. Bear in mind that the normal police radar transcelver works at approximately 100-mW output from the transmitter, and the same amount comes back to the receiver. The modified amateur transcelver has output at either 1 watt or 10 watts, depending upon operator preference. The police radar does not stand a chance.

I guess we have only two alternatives. We can drive at the speed limit, or we can enter the countermeasure war, in which each side will have to spend huge sums of money to try to win. But if you have a detector and still get chased, don't blame the detector or the police—it is nobody's fault but your own.

ROBERT E. WILLIAMS Port Angeles, WA

Entering the "countermeasures war" by adding an illegal device, be it a transmitter or whatever, is not the answer. Many of us like to drive fast. But isn't it more important to have fuel available and drive slowly, than to have NO fuel available and be unable to drive at all! Or perhaps you believe that our crude oil supplies will last forever? Why not put the effort being expended on countermeasures into something productive, like a new fuel source or at least a more efficient power converter—Editor

#### **TECHNOLOGICAL PREDICTIONS**

It is true that technology is advancing at a staggering rate, but it is not "almost impossible to keep up with (it)." We are the masters; and whatever our needs, technology and human ingenuity will answer them.

The next 10 years will give us a magnitude of change equal to that of the past 100 years. We will see giant solid-state television panels that when switched off will display a mural or painting. We will see completely solid-state TV camera/receiver/recorder combinations that use no tape at all. Digital memories will store audio as well as video. There will be thousands of public communications and information channels. Medic-alert sensors will be built into our wrist calculator/watches that will be tied into central computer banks for cardiac monitoring. We will have central processing units capable of retrieving any type of information.

We will be limited only by our imaginations. But we must not become the slaves of technology; it is a tool for our survival and the key to our future. These are exciting times we live in. JOHN SOWERS, JR.

Petersburg, VA

OK, that takes care of tomorrow, but what about next week?—Editor R-E





## NEBS / SERVICE ORDER FORMS

#### "carbonless" SALES SLIP and Portable Register

Speeds sales handling - provides clean, clear copies without carbons to insert, position or throw away

Simplifies your paperwork - this one form serves as: Sales Slip, Charge Slip, Cash Receipt, Invoice, Service Order, etc.

Saves steps - have Portable Registers in several locations, on counter, by phone, in truck, etc. Cuts down customer waiting time.

Helps you collect your money - Promissory Note printed on back of all copies. Have doubtful accounts sign.



#### PORTABLE REGISTER

Compact, lightweight, easy-to-operate. Holds up to 75 "carbonless" Register Forms in duplicate or triplicate. Durable, virtually unbreakable made of silver-gray, high-impact Cycolac® plastic. Used copies

#925 — For 5½"×8½" "carbonless" Register Forms. Each. . .

SERIES 610 SALES SLIP REGISTER FORM - Size 52/2 X8½". Designed for use in NEBS Registers #925 and #927 or other Portable Registers for 5½" X8½" forms with two, ½" dia. round holes, 2¼" center-to-center. Duplicate sets have white original; canary copy. Triplicate sets are white, canary and pink. Prices include your heading printed in blue link and portabling authorized (bluege specify). consecutive numbering (please specify).

DUPLICATE 610-2		TRIPLIC	ATE 610-3
20,000	\$230.00	20,000	\$365.00
10.000	139.00	10,000	225.00
6.000	98.00	6,000	149.00
4,000	77.50	4,000	108.00
2.000	42.50	2,000	59.50
1.000	24.95	1,000	34.95
500	15.95	500	21.50
250	10.95	250	14.50

Prices for forms do not include Portable Register.

#### Save time and money with this 4 in 1 INVOICE-REPAIR TAG

8749

0 48749

C48749

CHECK

YOUR FIRM NAME HERE

YOUR FIRM NAME HERE

PERMANENT OFFICE **RECORD** – A carbon copy of all entries on customer invoice ... saves recopying

**CLAIM CHECK** - Printed with your heading and numbered consecutively.

**COMPLETE JOB** RECORD - Tag remains tied to article - space to list parts and labor.

CUSTOMER INVOICE -Δ Printed with your heading and numbered consecutively.

Provides quick, easy identification of work left for service - all parts consecutively numbered

Tags are pre-strung with extra long looped string - permits fast, secure attachment to merchandise.

Saves money — this one form serves as: Service Order, Claim Check, Identification Tag, Involce, Job Record, Office Record,

#### MONEY-BACK GUARANTEE

If for any reason you are not satis-fled, your money will be promptly refunded.

SINGLE TAG (#301-1) Heavy manila tag (no copies). DUPLICATE TAG (#300-2) White bond, heavy yellow tag. Carbons pasted in. TRIPLICATE TAG (#303-3) White & canary bond, heavy salmon tag. Carbons pasted in. All sizes 3%"×9" overall. Prices include: Firm name and address printed in red ink in two locations; consecutive numbering on all parts. (Note: Tags are pre-numbered, no specific starting numbers possible.)

QUANTI	ITY #301-1 SINGLE #300-2 DUP		#300-2 DUPL	ICATE	#303-3 TRIPLICATE
4,000 2,000 1,000 500		\$95.00 54.95 32.95 21.95	\$142.00 76.50 43.95 27.50		\$183.00 102.95 58.50 36.50
NEBS	OR Mas	ST SERVICE BY M. PHONE TOLL FRI ss. residents 500) 252-9226	EE 1 (800) 225	- <b>63</b> 80 DATE	CODE 6627
QTY.		ITEM NUMBER & DE		PRICE	CONSECUTIVE NUMBERING AT: NO. 1001 NO. DO NOT NUMBER
			JN TIEMS (Please	print or type	9)
ITY and STATE	E				ZIP CODE
HONE					
ILL AND SH	IIP TO	O (If different from abo	ve)		

AUTHORIZED SIGNATURE

PHONE NUMBER

New England Business Service, Inc. NEBS Townsend, Massachusetts 01470

SEPTEMBER 1979 25



ATV Research Model MVX-500 Micro-Verter RF Modulator



CIRCLE 101 ON FREE INFORMATION CARD

AS REPORTED IN THE AUGUST AND SEPTEMBER 1978 issues of Radio-Electronics, many video modulators are being offered for sale in kit

form and assembled. Frequently called RF modulators, these devices are used to convert a video signal from a computer, video game, video recorder or video camera into a modulated RF signal at a frequency that can be fed directly to the antenna terminals of a TV receiver. All the units described had an output in the low VHF range-Channels 2-6. However, most microcomputers radiate harmonics into this frequency range, causing interference and degradation of the TV picture. This is especially true in color systems, depending on the TV receiver or computer used, the placement of the cables and the RF modulator.

The model MVX-500 Micro-Verter (Computer Video to RF Interface) overcomes this problem by operating in the UHF frequencies well above the range of the computer generated harmonics. While specifically designed for use with the Apple II microcomputer to provide worm-free color displays, the Micro-Verter interfaces easily with other microcomputers and any color or monochrome TV receiver capable of tuning in the UHF channels above Channel 14. The Micro-Verter may



also be used with any standard NTSC-format video source.

This small  $(3\frac{1}{4} \text{ W} \times 2\frac{1}{2} \text{ H} \times 4 \text{ inches D})$ unit comes completely assembled (without batteries) in a black-wrinkle-finished steel cabinet with four rubber feet. The front and rear panels are silver with blue trim. The front panel contains an on-off toggle switch, while the rear panel has RCA-type video input and RF output jacks. The unit comes with a short, 1-cm (approximately 1/2-inch) stub coupler that plugs into the RF output jack, thus acting as a short-range antenna. The Micro-Verter comes with a 10-foot-long shielded cable with RCA-type plugs on each end. If your microcomputer is not an Apple II, or if you use the Micro-Verter with some other video source, a different connector or adapter at one end of this cable may be necessary.

Operation is simple. Just plug one end of the cable into the video input connector on the back of the Micro-Verter and connect the other end of the cable to your video source. Now, set the Micro-Verter on the TV receiver near the UHF loop antenna or UHF antenna terminals. The RF output is radiated from the stub coupler on the back of the unit, so no direct connection to the antenna terminals is necessary except in cases of high interference.

The Micro-Verter does not come tuned to a specific channel, but generally will be operating between Channel 15 and Channel 25. Tuning to a particular channel is accomplished with a screw adjustment that is accessible through a hole in the bottom of the case.

Unfortunately, a video input-level control is not included in the Micro-Verter. If the video output of your source is not adjustable and is too high, a small series resistor (typically from 15 ohms to 150 ohms) is needed in the video line to drop the signal to a level that will not overdrive the Micro-Verter.

The Micro-Verter is ruggedly constructed; no glue or double-sided tape is used, and everything is either bolted or soldered together. A small PC board holds all the working parts except for the switch, batteries and video-input bypass capacitor. Power is supplied by four AA penlight batteries mounted in a springloaded holder to provide 6 volts. The batteries will last for over 1000 hours of operation since the circuit draws less than 1 mA in use.

We tested the device using three video sources-a TRS-80 microcomputer, a blackand-white video camera and a color video recorder; in all cases, using both color and black-and-white TV receivers. When the camera or recorder were used, the TV pictures were as good as when using a typical directconnection video monitor. However, the computer image was still not as good as when a direct monitor connection was used. This is not surprising, since most microcomputers need a 6-mHz bandwidth to display all the characters and graphics sharply, and a TV front-end and continued on page 32

## no loose ends

### All-In-One: computer, floppy, I/O, 16K RAM. \$1595\*



#### New Heathkit<sup>®</sup> H89 All-In-One Computer

Heath takes the risk out of selecting a balanced computer system. Now, video terminal, floppy, keyboard and 8-bit computer are brought together in one self-contained, compact unit. Nothing hangs out.

#### Two Z80's

The personal computer has never been simpler. Or smarter. Two Z80 microprocessors mean terminal never shares power with computer, as do most desk-top units. So this terminal is capable of a multitude of high-speed functions, all controllable by keyboard or software.

#### 102K bytes storage

Built-in floppy disk system gives you fast access to programs and data. Each 5¼inch diskette has more than 102K bytes of storage area, enough to hold entire files. The All-In-One comes with 16K RAM, expandable to 48K.

### Hundreds of uses at home or work

The All-In-One Computer runs programs written in MICROSOFT<sup>™</sup> BASIC and ASSEMBLER Languages. And it accepts all current software written for the popular Heathkit H8 computer. You can choose from scores of practical programs for home and business.

#### Learn by building

What better way to learn about computers than to build one yourself? The All-In-One is available in easy-to-build kit form, as well as completely assembled. Like all Heath electronic kits, it comes to you with its own easy-to-follow assembly manual and a nationwide network of service centers to assure smooth sailing.

#### **FREE CATALOG**



For complete details on the Heathkit H89 All-In-One Computer and nearly 400 other electronic kits for your home, work or pleasure, send today for the latest Heathkit Catalog of values.


\*\$1195 without floppy. Mail order klt price, F.O.B. Benton Harbor, MI. Also available at Heathkit Electronic Centers at slightly higher prices. Prices subject to change without notice.

CP-165

HEATH COMPANY, DEPT. 020-570, BENTON HARBOR, MI 49022

## Train with NTS for the
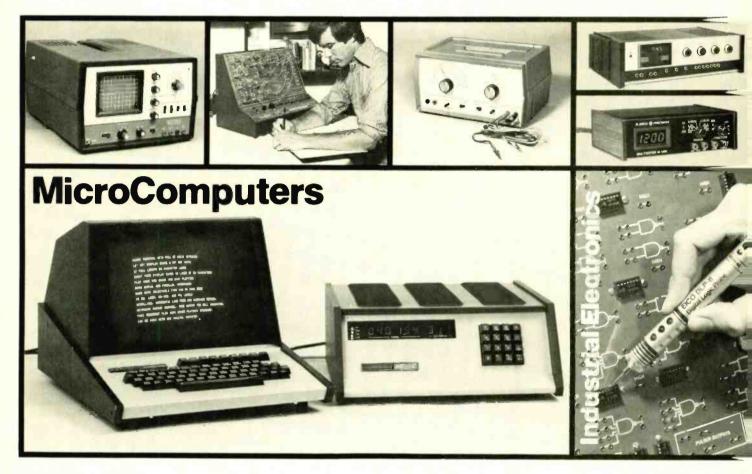
### MicroComputers, digital the first name



The world of electronics is daily becoming more challenging. Technology is growing more specialized, and the importance of digital systems increases every day. Test instruments, home entertainment units and industrial control systems are all going digital. And now, NTS training programs include a wider choice of solid-state and digital equipment than ever before offered in any home study course: Advanced NTS/Heath digital color TV (25" diagonal with optional programming capability), NTS/Heath microcomputer, digital test equipment, digital stereo receiver (70 watts per channel), NTS compu-trainer, plus much more state-of-the-art equipment to make your training exciting and relevant.

The equipment you receive with NTS training programs is selected to provide you with a solid

background in electronic systems. Kits and lessons are designed to work together to demonstrate electronic principles and applications. The kit-building not only shows you how electronic hardware functions, but how various circuit designs accomplish different purposes. Your lessons guide you through any number of experiments associated with many projects. This is the Project-Method, and it works. Step-by-step, you learn how and why digital electronics has become a part of our world, and the even bigger role it is sure to play in the future.

Whether you are looking for training in Consumer, Commercial, or Industrial electronics, NTS offers fourteen courses, some basic, many advanced, in several areas of electronics. An all-new full-color NTS catalog shows you what each course covers,

## electronics of the future.

## systems and more...from in home study.



and every piece of equipment included.

Send for it today, and see for yourself what's really happening in electronics training technology at NTS. Find out how much has changed, and what new directions the field is taking. You'll probably want to be a part of it.


It's free. Just mail the card or coupon. Today.





TECHNICAL-TRADE TRAINING SINCE 1905 Resident and Home-Study Schools 4000 South Figueroa St., Los Angeles, Calif. 90037

AATIONAL TECHNICAL 4000 South Figueroa Street, Lo	
Please send FREE Color Catal	log and Sample Lesson.
Color TV Servicing B & W TV and Radio FCC License Course Electronic Communi Electronics Technolo Audio Electronics Se	cations ogy
Digital Electronics MicroComputers/Mic	croProcessors
MicroComputers/Mic	croProcessors
MicroComputers/Mic	croProcessors
MicroComputers/Mic Name Address	

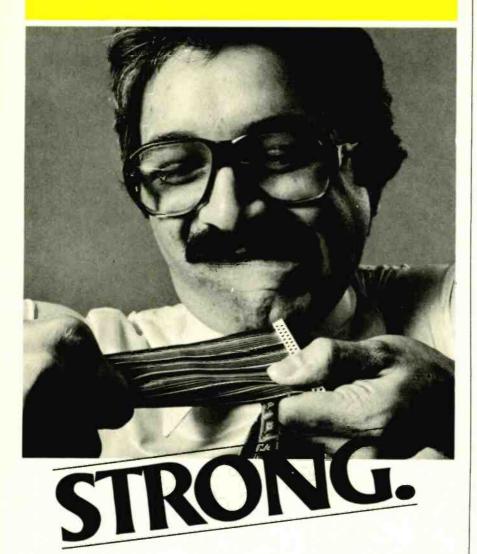

#### Your A P Jumper isn't just crimped, it's fused together for keeps.

You can't pull one of our assemblies apart on purpose, much less by accident. Not without tools.

It's because we don't just crimp them together like other jumper makers, we mold our connectors to the flat ribbon cable. And after they're fused together, we test each assembly to make sure it's in perfect working order.

All of this means you're not going

to be bugged by gaps or shorts. Not with A P Jumpers. Not even after repeated use. They're the world's most dependable way to jumper within PC boards and interconnect between PC boards, backplanes and motherboards.

If your application involves sockets, card edge or DIP connectors, you'll find your A P dealer has the contacts and lengths you need.

Who's your dealer? Phone (tollfree) 800-321-9668. And ask for the complete A P catalog, The Faster and Easier Book.



AP PRODUCTS

INCORPORATED Box 1108 • 72 Corwin Drive Painesville, Dhio 44077 Tel. 216/354-2101 TWX: 810-425-2250

#### Faster and Easier is what we're all about.

#### EQUIPMENT REPORTS

continued from page 26

IF section have only about a 4.5-mHz bandpass. However, no interference was noted—an improvement over the VHF modulators. Also, the coupling stub provides a very simple connection to the TV receiver. Unfortunately, the lack of a video input-level control was inconvenient, since a dropping resistor was needed with each source tested.

The detailed instruction sheet that accompanies the Micro-Verter has four lengthy paragraphs describing the FCC rules regarding Class I TV Devices, and the precautions to be followed in their use.

The model MVX-500 Micro-Verter sells for \$35 from ATV Research, Dept. R, 13th and Broadway, Dakota City, NE 68731 (postpaid in the U.S., Canada and Mexico). It is also available at many computer dealers nationwide. **R-E** 

#### American Antenna Model K-40 CB Antenna



CIRCLE 102 ON FREE INFORMATION CARD

PROBABLY FEW CB ANTENNA PRODUCTS HAVE has as much laboratory computer design and extensive field testing as the *model K-40* developed by American Antenna (1945 South Street, Elgin, IL 60120).

According to the manufacturer, an intensive two-year development period coupled with infield evaluation, preceded the product's appearance on the market. Over 700 active CB mobile operators participated in the in-field test, of which only about 5% reported no improvement over their present antennas. In contrast, the manufacturer claims 95% noted better performance over their present antennas.

The field tests confirmed the manufacturer's lab tests. The CB'ers reported an average 30% improvement in range over competitive antennas.

Much of the instrument's high performance can probably be attributed to its loading coil; it is carefully designed, wound over a hollow core (American Antenna calls it an "isolation chamber") and rigidly molded.

The adjustable steel whip has a rounded tip, making unnecessary the usual antistatic ball that is inevitably lost to a tree or low bridge! The hollow coil permits two inches of whip adjustment, allowing correction for a wide SWR range. The coil-and-whip assembly continued on page 34

### PLUG IT IN AND TAKE COMMAND







#### **NO WIRES NO HASSLES**

System X-10 requires no special wiring or complicated installation. Simply plug a Command Console into your wall outlet in any desired location in your home. Plug each Lamp or appliance into the appropriate module and then plug that module into any wall outlet. Any number of Command Consoles may be used in a single system.

#### TOTAL CONVENIENCE

With System X-10 you can operate almost every light and electrical appliance in your hom∋ without leeving the comfort of your easy chair. Imagine turning on a TV set or stereo, even dimming a light, in the next room without moving from your chair.

Think of the money you can save on electric bills with System X-10. Turn off heaters or appliances from any location in your home without a lot of running around.

#### DELUXE ULTRASONIC COMMAND SYSTEM

The Console controls all modules from its built-in keyboard, plus it completely controls all modules from ts wireless hand held ultrasonic control unit. Simply aim the hand held unit at the Console, press any appropriate Command button to turn on and off, dim and brighten lights, cr turn on and off appliances. Hand held unit operates at distances of up to thirty feet, line of sight of conscle (does not operate through walls). A worthwhile addition to any existing X-10 system or an excel ent way to begin.

#### STANDARD COMMAND CONSOLE

Fully controls all modules as above system, but will not respond to hand held remote unit commands - may be intermixed with the deluxe Command System or used separately to form independent control systems.

#### **MICROPROCESSOR BASED DESIGN**

The BSP X-10 System uses the latest digital techniques for trouble-free operation. Digital pulse codes are sent through the house power lines to assure reliable control throughout the system. Amazingly ocmpac; The Command Consoles measure only 434" X 31/2" X 31/2'

#### LAMP MODULE

Each module will control any incandescent lamp rated up to 300 watts from control signals received from the Command units. Functions include on and off, brighten and dim. UL listed.

#### APPLIANCE MODULE

Each module receives signals from the Command units to turn appliances on and off; such as TV, stereo, fan, etc. Maximum appliance ratings: Resistive load - 15 amps. Motor load -1/3 HP Incandescent lamp - 500 watts. UL listed.

#### WALL SWITCH MODULE

Receives signals from the Command units to control incandescent lamps normally operated by a wall switch up to 500 watts. Installs just like any normal wall switch. Functions include on and off by remote or local control and Ľ

brighten and dim by remote control. UL listed.

#### GETTING STARTED

Deluxe-Ultrasonic starter kit includes: 1-Deluxe Ultrasonic Command Console, 1-Hand Held Remote Unit, 2-Lamp Modules, 1-Appliance Module. Only \$112.95 Standard starter kit includes: 1-Standard Command Console, 2-Lamp Modules, 1-Appliance Module. Only \$87.95 Extra Lamp, Appliance or Wall Switch Modules only \$16.00 each

Extra Deluxe Ultrasonic Command Console with Hand Held Remote Unit, \$64.95.

Extra Standard Command Console \$39.95. Please include \$3.00 shipping and handling on all orders.

ADVANCE	To order — use this coupon or call
	TOLL FREE HOT LINE
ELECTRONICS	800-223-0474
54 West 45 Street New York N.Y. 10036	IN NEW YORK STATE 212-687-2224
Please send me BSR 5 piece Deluxe Ultrasonic starter kil BSR 4 piece Standard starter kil Lamp Mod Appliance Mod Deluxe Ultrasonic Console with Handhek Standard Command Console.	\$87.95 set           Wall Switch Mod.         \$16.00 each           Remote Lnit         \$64.95 each
	GE O VISA O RE-9
Acct. #	Exp. Date
Name	
Address	
City	StateZip
Add \$3.00 Shipping and Handling	o. N.Y.S. Res. add sales tax.

#### EQUIPMENT REPORTS

continued from page 32

quickly disconnects from the base. A springloaded bayonet system permits rigid contact while mounted, but the unit can be easily removed for storage, for a car wash, or as theft protection. The K-40 comes ready to mount on a trunk lip, hatch back, or through the roof.

The antenna has a double guarantee: a 1year warranty against defects, and a promise to perform *better* than any other mobile antenna (the antenna also comes with a full-length 9foot whip). An 18-foot length of low-loss RG-58A/U coaxial cable is provided that is terminated with a soldered (not crimped-on) PL-259 connector. And both the coaxial cable and chrome-plated mount meet military specifications.

The optional Uni-Mount universal mounting bracket allows the model K-40 to be attached to virtually any imaginable mobile fixture from mirrors to luggage racks. Another optional accessory is the Magna-Mount, an 8pole, 120-lb.-pull magnetic mount. Not only will this mount stay in place tightly under normal driving conditions, but, when used with the model K-40, it is guaranteed to outperform any mobile antenna, including the K-40 mounted without it!

So with all these boasted claims, we had to try one. A Cobra CB was connected through an SWR meter into a coaxial antenna switch. The switch, in turn, could select between the K-40 and another antenna, both of which were magnetically mounted. To prevent interaction between the antennas, only one antenna at a time was in place in the center of the roof of the vehicle.

A portable receiver with an S-meter was used to measure the relative signal strengths of the two antennas. When in place, the SWR on the *model K-40* was 1.5:1; that of the competitive antenna was 1.2:1. In theory, there should be little difference in performance if SWR were the only factor.

The results of our tests showed that, in three different positions of the monitoring receiver, the *model K-40* equaled or outperformed the competitive antenna. Apparently, American Antenna's advertising is not merely Madison Avenue showmanship.

Considering the performance, the workmanship and the price, we believe the *model K-40* is an excellent high-quality mobile CB antenna. Suggested retail prices are: The *model K-40* antenna, \$38.50; the Uni-Mount, \$8.95; the Magna-Mount, \$15.95. **R-E** 

#### Electra Model BC220 Programmable Scanner

ANOTHER PROGRAMMABLE SCANNER INNOVAtion has been released from Electra. The *model BC220* covers the VHF-low, VHF-high and UHF FM land mobile services. In addition, it can receive the VHF AM aircraft band, 118-136 MHz.

As with previous keyboard-entry scanners, it has a dual 120 VAC/12 VDC power supply. The unit's steel cabinet provides superior shielding. Accessory jacks are provided for an external speaker and antenna.

The BC220 provides 20 programmable channels. Similar to the BC250, these channels



#### CIRCLE 103 ON FREE INFORMATION CARD

can be selected or locked out in two banks of 10 channels each. Individual channels can also be locked out. Regardless of the setting of the channel band switch, when the receiver is turned on only the first bank will be operational

#### **Specifications**

The FM frequency ranges are: 32-50 MHz, 144-174 MHz and 420.450-512.450 MHz. Sensitivity is very good on the FM ranges:  $0.4\mu$ V on VHF and  $0.8 \mu$ V on UHF. Aircraft AM specifications display poor sensitivity: 1  $\mu$ V on the 118-136-MHz range. IF selectivity is a sharp 55-dB down  $\pm 25$  kHz.

An on-the-air evaluation of the compact model BC220 verified the aircraft band's low sensitivity; signals that were received quite strongly on a competitive receiver were noticeably weaker on the model BC220. Clearly, the design of the aircraft-band circuits is first-



generation, but it does work. Sensitivity should not be a problem for listeners near airports or aircraft flight patterns.

The greater improvement of this unit over all previous scanners is the virtual eradication of spurious signals. Reception is exceptionally clean of these phantom signals with no sacrifice in receiver sensitivity.

Scanning and search rates are slower than on previous Bearcat programmable scanners. A SPEED key selects between two speeds, which seems unnecessary since listeners would undoubtedly prefer to intercept communications as rapidly as possible.

A clever innovation in the model BC220 is the inclusion of a preprogrammed aircraft and marine-band search/limit feature. Simply press AIRCRAFT or MARINE key, and the unit starts searching either of those bands for signals. Another desirable provision is the inclusion of a hold feature (not shown in the photo). This feature permits you to stop the search mode at any point and remain on the frequency displayed until the SEARCH key is pressed again. On some previous Bearcat models, the only way the unit could be stopped on a particular frequency when no signal was present was by advancing the squelch control. This was a noisy inconvenience, and the relief is welcome!

A PRIORITY mode is also featured for the channel one position. As with previous Bearcat programmable scanners, a brief interruption every 3 seconds samples channel one when the priority channel is in use; this may be irritating to some listeners.

A key is also provided for delay/no delay. When no delay is desired, scan or search functions resume immediately upon the loss of the carrier signal. Unfortunately, even with delay, scanning resumes almost as fast-within 1 second. All scanners should provide a delay time of no less than 2 or 3 seconds. If not there is scarcely enough time for the listener to be distracted, look at the display, and register the frequency or channel number before the unit resumes its search or scan function.

Audio passband is crisp, enhancing good voice fidelity. Any channel, from 1 through 20, can be selected at random without your having to step through the sequence. Search-limit programming is simplified. The keyboard action is very positive; no contact bounce was apparent as observed with some other scanners. And the display itself provides thicker and brighter characters.

All tests considered, we liked the model BC220. It performs well by itself or as a receiving mainframe with outboard converters, such as a 220-400-MHz converter for the UHF/ AM military aircraft band. The model BC220 Bearcat has a suggested retail price of \$379.95 and is available from Electra Company, Cum-R-E berland, IN 46229

#### Motorola Model CM540 Electroscan CB Transreceiver

MOTOROLA, LONG A LEADER IN RADIO COMMUnications equipment, has released an advanced CB radio. Called the Electroscan, the Model CM540 40-channel transceiver has no fewer than 28 (count 'em, 28!) front panel and mikemounted pushbuttons, controls, and visual indicators.

In spite of the busy appearance of the rig, it does look more like a professionally-engineered piece of advanced communications



Own a powerful home computer system, starting for just 199.95-a price that gets you up and running the very first night with your own TV for a video display. \$99.95 ELF II includes RCA 1802 8-bit microprocessor addressable to 64k bytes with DMA, interrupt, 16 registers, ALU, 256 byte RAM, full hes keyboard. two digit hex output display, stable crystal clock for timing purposes, RCA 1861 video IC to display your programs on any video monitor or TV screen and 5-slot expansion bus fless connectors) to expand ELF II into a giant!

#### **ELF II Explodes Into A Giant!**

Master ELF II's 599.95 capabilities, then expand with GIANT BOARD KLUGE BOARD .4k RAM BOARDS TINY BASIC ASCII KEYBOARD. LIGHT PEN ELF BUG MONITOR COLOR GRAPHICS & MUSIC SYSTEM TEXT EDITOR ASSEMBLER DISASSEMBLER. VIDED DISPLAY BOARD

#### More Breakthroughs Coming Soon!

Soon to be introduced: ELF II special application kits that give you the hardware and software you need to use ELF II for specialized purposes such as a telephone dialer industrial controller home photography security sys tem police alert motor controller station output monitor on a conveyor bell assembly line and some new, super-fantastic games!

Also coming soon: PROM Programmer A.D. D.A. Converter Controller and more! Unlike some heavily advertised hobby computers. ELF II Board doesn't limit you to pre-recorded programs. With ELF II you learn computing from the ground up from machine language to assembly language to BASIC

in quick, clear and easy steps. ELF II is a powerful computing tool, but one that you can master with the same ease you once mastered a slide rule or pocket calculat

#### Master This Computer In A Flash!

Repardless of how minimal your computer background is now, you can learn to program an ELF II in almost no time at all. Dur Short Course On Micropro cessor & Computer Programming - written in non technical language - guides you through each of the RCA COSMAC 1802's capabilities, so you'll understand everything ELF II can do and how to get ELF II to do it! Don't worry it you've been stumped by computer books before. The Short Course represents a major advance in literary clarity in the computer field. You don't have to be a computer engineer in order to understand it Keyed to ELF II, it's loaded with hands on Illustrations. When you're linished with the Short Course, neither ELF II nor the RCA 1802 will hold any mysteries for you.

In fact, not only will you now be able to use a personal computer creatively. you'll also be able to read magazines such as BYTE INTERFACE AGE POPULAR ELECTRONICS and PERSONAL COMPUTING and fully understand the articles. And, you'll understand how to expand ELF II to give you the exact capabilities you need!

If you work with large computers. ELF II and the Short Course will help you nderstand what they're doing.

#### Get Started For Just \$99.95, Complete!

\$99.95 ELF fl includes all the hardware and software you need to start writing and running programs at home, displaying video graphics on your TV screen and designing circuits using a microprocessor -the very first night-even if you've never used a computer before.

ELF II connects directly to the video input of your TV set, without any additional hardware, Or, with an  $\$8.95~\rm RF$  modulator [see coupon below], you can connect ELF II to your TV's antenna terminals instead.

ELF II has been designed to play all the video games you want, including fascinating new largetimissile gun game that was developed specifically for ELF. II. But games are only the icing on the cake. The real value of ELF II is that it gives you a chance to write machine language programs—and machine language is the fundamental language of all computers. Of course, machine language is only a starting point. You can also program ELF II with assembly language and tiny BASIC. But ELF II's machine language capability gives you a chance to develop a working knowledge of computers that you can't get from running only

### Write and run programs-the very first night-even if you've never used a computer before!

You're up and running with video graphics for just \$99.95 then use low cost add-ons to create your own personal system that rivals home computers sold for 5-times ELF II's low price! pre recorded tape cassettes.

ELF II Gives You The Power To Make Things Happen! Expanded, ELF II can give you more power to make things happen in the real world than heavily advertised home computers that sell for a lot more money. Thanks to an ongoing committment to develop the RCA 1802 for home computer use, the ELF II products-being introduced by Netronics-keep you right on the outer fringe of today's small computer technology. It's a perfect computer for engineering, business, industrial, scientific and personal applications.

Plug in the GIANT BDARD to record and play back programs, edit and debug programs, communicate with remote devices and make things happen in the outside world. Add Kluge (prototyping) Board and you can use ELF II to solve special problems such as operating a complex alarm system or controlling printing press. Add 4k RAM Boards to write longer programs, store more information and solve more sophisticated problems.

ELF II add ons already include the ELF II Light Pen and the amazing ELF-BUG Monitor-two extremely recent breakthroughs that have not yet been duplicated by any other manufacturer

The ELF BUG Monitor lets you debug programs with lightening speed because the key to debugging is to know what's inside the registers of the microprocessor. And, with the ELF BUG Monitor, instead of single stepping through your programs, you can now display the entire contents of the registers on your TV screen. You find out immediately what's going on and can make any necessary changes

The incredible ELF II Light Pen lets you write or draw anything you want on a TV screen with just a wave of the "magic wand." Netronics has also introduced the ELF II Color Graphics & Music System-more breakthroughs that ELF II owners were the first to enjoy!

#### ELF II Tiny BASIC

Ultimately, ELF II understands only machine language-the fundamental coding required by all computers. But, to simplify your relationship with ELF II, we've introduced an ELF II Tiny BASIC that makes communicating with ELF II a hreeze

Tiny BASIC saves you the time of having to code your individual instructions in machine language for ELF II. Instead, you simply type instructions on a keyboard --PRINT, RUN, LOAD, ETC. Your Tiny BASIC program automatically translates them into machine language for ELF fl. Then it translates ELF fl's output back into simple words and symbols for you.

#### Now Available! Text Editor Assembler

#### Disassembler And A New Video Display Board!

The Text Editor gives you word processing ability and the ability to edit programs or text while it is displayed on your video monitor. Lines and Charac ters may be quickly inserted, deleted or changed. Add a printer and ELF II can type letters for you-error free-plus print names and addresses from your mailing list!

ELF II's Assembler translates assembly language programs into hexidecimal machine code for ELF II use. The Assembler features mnemonic abbreviations rather than numerics so that the instructions on your programs are easier to this is a big help in catching errors.

ELF II's Disassembler takes machine code programs and produces assembly language source listings. This helps you understand the programs you are working with and improve them when required.

The new ELF II Video Display Board lets you generate a sharp, professional 32 or 64 character by 16 line upper and lower case display on your TV screen or video monitor - dramatically improving your unexpanded \$99.95 ELF II. When you get into longer programs, the Video Orsplay Board is a real blessing!

#### Ask Not What Your Computer Can Do. But WHAT CAN IT DO FOR YOU?

Don't be trapped into buying an expensive dinosaur, simply because you can afford it. ELF II is more advanced and more fun to use than big name computers that cost a lot more money. With ELF II you learn to write and run your own programs. You're not just a keypunch operator. No matter what your interests are, ELF II is the fastest way to get into computers. Order from the coupon below!

SEPTEMBER 1979



equipment than a miniature pinball machine.

A large, bright LED channel indicator is easily visible. The S-meter serves also as a relative power output indicator and SWR meter. Separate IF and RF gain controls allow some reduction of background interference., A noise blanker effectively suppresses sharp pulse noise from nearby spark and ignition sources. A continuously variable ANL control allows various levels of noise suppression without distortion from harsh clipping.

Speaker audio is unusually good. Voice passband is emphasized from the speaker, and the loud audio available should be adequate for even the noisiest mobile environments. A PA switch allows the audio power to be put to use for public address applications.

The Electroscan feature refers to the builtin digital logic that provides a number of auto-



CIRCLE 104 ON FREE INFORMATION CARD

matic channel-searching functions. Pushbuttons on the microphone permit the user to step up or down, channel-by-channel, or switch channels rapidly. By using the built-in scan feature, the rig may automatically look for busy channels or open channels, at the user's discretion.

A memory feature permits up to ten chan-



CHANNELLOCK, INC. - Meadville, Pennsylvania 16335



Meet The Rest Of The Family. Send For Free Catalog.

nels to be memorized and scanned separately from the other thirty. Channel 9 will always be in memory unless it is purposely replaced by another tenth channel. When memorized channels are erased, channel 9 will remain in memory. Scan rate is rapid; all ten channels are sampled in less than one second.

The *Electroscan* is securely packaged. It includes a variety of mounting hardware and literature. Warranty/service booklets, FCC licensing information and applications, a complete set of operating instructions, and even a set of operational exercises to help you familiarize yourself with the *Electroscan* features are included. Additionally, a complete schematic diagram is provided.

In spite of the unusually-large selection of features, the Electroscan is no more difficult to install than any other CB transceiver. Simply mount the unit, connect power and an antenna, and you're on the air! Everything is self-contained.

Microphone audio is unusually crisp and natural. You may custom-adjust mike gain for your operating conditions with a thumbwheel control located on the mike.

Although the initial reaction of a new CB'er seeing all of those awesome controls might be fright, the *Electroscan* is really quite simple to operate. Virtually every control is independent of the others, and even the automatic features may be defeated at the touch of a button.


Sensitivity of the receiver is quite good. Although no specifications came with our sample, the unit seemed to perform as well as any we had previously tested. The two separate noise limiters proved to be very useful in combination. The variable ANL control allows adjustable suppression of moderate hash interference, with the Extender (noise blanker) switch reduces sharp impulse noise dramatically. Both controls worked efficiently without degrading the intelligibility of received signals.

A series of LED status lights provides visible indication of various transceiver functions. A modulation light flashes as the operator speaks into the microphone, providing a rough modulation level reference. Other LED's announce receive, memory, and scan modes operating at the moment.

Our sample unit had one apparent defect. Even with volume and all gain controls turned down, an annoying crackling sound issued constantly from the speaker. We assume that this was unusual, and not common to all radios of this series. If such a problem were encountered in the field, the user should exercise his warranty.

Although all of the features available on the *Electroscan* are not likely to be used by all operators, each has a legitimate application to CB communications. The Motorola *Electroscan* is well-engineered and thoughtfully designed for the serious CB user. For additional information about the model *CM540 Electroscan* CB transceiver, write Motorola, Inc., Automotive Products Division, 333 Northwest Avenue, Northlake, IL 60164.



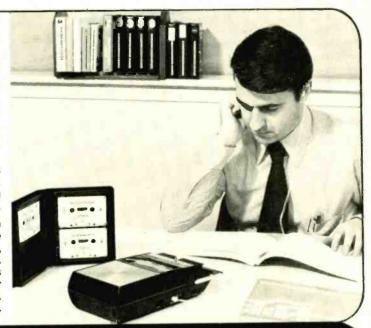

## The Most Complete MICROCOMPUTER Self-Study COURSES Available on Tape!

Now you or your company can hold self-study seminars at home or in the office. Whenever it's most convenient. Eliminate the need to, and cost of, sending corporate personnel to periodic seminars.

Choose one or more of the 10 cassette courses from the Sybex self-study library described below. Each course consists of a set of cassette tapes packaged in a durable, book-like case, and a guidebook for studying ease. The lectures are completely coordinated to the pages of the study books, and have been extensively used for personal study with positive results.

The tapes can be played on any standard cassette player.

#### TIME-EFFICIENT WAY TO LEARN.

STUDY

AT

HOME.

OFFICE **OR IN** 

YOUR

CAR.

CREDIT CARDS AND COMPANY P.O.S ACCEPTED

FOR FAST SERVICE CALL IN YOUR

ORDER TO (516) 829-5858

> I. I 1

\$29.95

\$29.95

\$21.95

\$69.95

#### INTRODUCTORY - SHORT COURSES (no technical background assumed)

Each course includes a special course book plus two cassettes (total course length 21/2 hours).

#### **S1 - INTRODUCTION TO MICROPROCESSORS**

S1 - IN INDUCTION TO MICHOPROCESSORS \$29.95 This seminar is intended for all non-specialists who wish to acquire a broad understanding of the basic concepts and advantages of microprocessors. It explains how microprocessors work and it stresses methods, costs, advantages and disadvantages for the most important application areas of each type of microprocessor. What is needed to implement a system, how to use it; the Impact of microprocessor-based systems; their evolution. Topics covered include: BASIC DEFINITIONS, SYSTEM COMPONENTS, MICROPROCESSOR APPLICATIONS, WHAT TO LOOK FOR, and IMPACT AND EVALUATION.

#### S2 - PROGRAMMING MICROPROCESSORS

52.95 This seminar describes the internal operation of a microprocessor system including how instructions are fetched and executed, how programs are written and executed in typical cases (arithmetic and input-output). The goal of this course is to provide an overall understanding of the basic concepts of microprocessor programming. Requires an understanding of the main concepts in the INTRODUCTION TO MICROPROCESSORS SEMINAR. It is recommended that these two seminars be laken together.

#### **S3 - DESIGNING A MICROPROCESSOR SYSTEM**

How to interconnect a standard microprocessor system, in detail: the ROM, RAM, PIO, UART, MPU, clock, Trade-offs in addressing techniques. Case studies (8080, 6085, others). You will learn in just 2,5 hours how to interconnect a complete system, wire by wire. The techniques are applicable to all standard microprocessors.

#### S10 - INTRODUCTION TO PERSONAL AND BUSINESS COMPUTING

Are you planning to buy or use a microcomputer system? This seminar will make you understand the choices and possibilities. A comprehensive description of what is needed and what is available; business computing; peripherals; selection; comparisons; costs; the future.

#### INTRODUCTORY - COMPREHENSIVE COURSES

Each course includes a 300-500 page seminar book and 7 to 8 C-90 cassettes.

#### SB1 - MICROPROCESSORS (12 hours)

GD I - MICHOFROCESSONS (12 HOURS) 300 The basic hardware course. It does not require any previous computer knowledge. It will provide you with a comprehensive and effective understanding of all the important aspects of microprocessors and systems. In two hours, you will know in complete detail how an MPU operates. In four hours, you will know all the chips. In ten hours you will know the complete interconnect of a system. At the end of the course, you will know all the assentias about microprocessors.

the essentials about microprocessors. CONTENTS: Technical Introduction / LSI Technologies / Internal Architecture of a Microprocessor / System Components / The Microprocessor Families / Microprocessor Programming / Applications of Microprocessors / Building a System / Product Development / Design Alds / Microprocessor Selection / Evolution and Perspectives.

#### SB2 - MICROPROCESSOR PROGRAMMING (10 hours) \$89.95

SEZ - MICHOPHOLESSOR PROGRAMMING (10 hours) \$69.95 The basic soltware course. It does not require any previous computer or programming knowledge. It will take you step by step through all the important aspects of microcomputer programming, at the assembly language level (with a survey of PL/M and BASIC). The techniques presented are applicable to all microprocessors. but the examples presented focus on the 8080 and the 6800. At the end of the course you will have understood the theory and should be ready for actual practice. CONTENTS: Microcomputers / Programming: Basic Concepts, Arithmetic, Subroutines / Inpui-Output: Putaes and Delays, Parallel and Serial Transfers. Peripherals. Polling and Inter-rupts / Microprogramming / Program Development: Procedure. Software. Equipment / PL / M / Costs and Summary.

SPECIALIZED COURSES Each course includes a 300-500 page workbook and 3 to 4 C-90 cassettes.

Level required: Basic understanding of microcomputers.

#### SB3 - MILITARY (SEVERE ENVIRONMENT) MICROPROCESSOR SYSTEMS (6 hours)

\$59.95

\$59.95

\$59.95

MICHOPHOCESSON SYSTEMS (6 nours) 582.50 A complete study of constraints, techniques, and systems available for severe-environmeni applications, including the Hugues, Raytheon, Actron, and other systems. CONTENTS: Technical Introduction / LSI Technologies / Milliarized Microprocessor Systems / Milliarized Microprocessors / Standardization / Building a System / Applications / Reliability / Testing / Summary and Perspective.

#### SB5 - BIT-SLICE (6 hours)

Source and the complete system will be built with bit-slices, in detail first a fast CPU, then the complete control section, using a PLA, a sequencer. PROM's and miscellaneous logic. Other innovative applications of slices are also examined.

togic, other innovative applications or sites are also examined. To follow this course, you must understand what a CPU is. In this course, you will learn how to build real systems, with careful performance optimization. CONTENTS: Brief History of CPU Design / Bit Sitee Principles / Bit-Sitee in Detait / Building with Bit-Sitee Devices / Survey of Bit-Sitee Devices / Applications Develop-ment Aids / Conclusions.

#### SB6 - INDUSTRIAL MICROPROCESSOR SYSTEMS (41/2 hours)

This course stresses actual industrial hardware and software techniques: the components, the programs, the cost. In particular: D/A conversion, filtering, tests, fall-soft, hardware

Interprograms, the Cost in purious Directory and the explorements of the programs, Industrial Constraints / Ruggedization / Input-Output / Digital-Analog Conversion / Industrial Components / Control Microprocessors / Industrial Case-Studies / System Development / Reliability and Testing / Evolution and Perspective.

#### SB7 - MICROPROCESSOR INTERFACING (6 hours) \$59.95

How to assemble, interface and interconnect a system. Assembling a complete CPU, Input-Output Techniques, Basic Interfacing, Connecting the Peripherals keyboard. LED teletype, printer, cassette, floppy-disk (including one-chip floppy controllers), CRT display, Communications Standard buses S100, RS232, CAMAC, IEEE 488. Evolution.

ORDER TODAY - SATISFACTION GUARANTEED

TECHNOLOGY TRENDS, INC. A division of CMP Publications, Inc. 333 East Shore Rd., Manhasset, NY 11030

	THE	
ehn	1.01	
PP.	nds	
	ing .	

E

I enclose che	ck or M.O. for	\$	NY State Residents please add sales	s tex
(in)	clude \$2.50 per	course for postage and	handling)	

Please mail me the courses O circled below.

Credit Card #				Exp. date	Mo.	Year
or please bill my Company-P.O.			(Sig	nature requi	red on all Ch	arges)
Ship to		-		_	_	
Company			_			
Address				_		-
City	-01	State			Zip	
	S1	S2	<b>S</b> 3	S10	SB1	SB2
DESIRED		B3 SI	B5 S	B6 SE	17	

1979 37

SEPTEMBER



## Professional or not, the Computer the best books in the field...

Programming Minicomputers

> PROGRAMMING LANGUAGES. By Allen B. Tucker, Jr. 439 pp., Illus. Gives you not only the principles of design but the applications of six major programming languages so you can decide—among the special features of each—what best suits your operations. Shows you the languages strengths and weaknesses through demonstrations of their use in solving various representative "benchmark" prob-lems. Also provides programs using a variety of computers so you can evaluate languages and their compilers on a basis of uniform and meaningful criteria.

#### 654/158 Pub. Pr., \$22.00 Club Pr., \$16,50 ADVANCED PROGRAMMING

TECHNIQUES: A Second Course in Programming Using FORTRAN. By Charles E. Hughes. Charles P. Peleeger, and Lawrence L. Rose. 287 pp., with figures. If you're a novice programmer who wants to become a professional-or if you've already made it and want to grow - here are the tools and techniques you need. Although the au-thors use FORTRAN as a basis for their presentation, much of what you will learn here applies to other languages. An ideal book for anyone with any experience in any procedure-oriented programming language

786/860 Pub. Pr., \$15.95 Club Pr., \$12,25 HOW TO DESIGN AND BUILD YOUR OWN CUSTOM TV GAMES. By David L. Heiserman. 544 pp. illus. This manual shows you how to concoct original games that are just as imaginative, complex, and tricky as you care to make them. It gives you a thorough course in game circuitry with detailed how-tobuild-it instructions and complete schema-tics-and it goes far beyond a mere description of game circuits to real-world design techniques and principles 786/585 Pub. Pr., \$14.95 Club Pr., \$11.95

INTRODUCTION TO PROGRAMMING: Pro-gramming Logic and Flowcharting. By G A

Pub. Pr. \$9.60

Club Pr., \$7.95

This title counts for two premium books

#### ENCYCLOPEDIA OF COMPUTER

ENCYCLOPEDIA OF COMPUTER SCIENCE. Edited by Anthony Ralston and C. L. Meek, 1,500 pp., 60 illus., 100 charts, 7 x 10 format. This first and only in-depth coverage of the entire field of computer science in a single volume is utterly comprehensive and completely up to date. An invaluable reference work for specialists, nonspecialists, educators work for specialists, nonspecialists, educators, students, general readers, and librarians, it provides answers to any computer science discipline question in minutes. In addition to covering every aspect of the discipline in five broad areas, each is broken down into some 500 articles, most of them containing bibliographic information to make intensive study of any one subject easier.

769/01X Pub. Pr., \$60.00 Club Pr., \$39.95

ERROR-DETECTING CODES, SELF-CHECKING CIRCUITS, AND APPLICA-TIONS. By JOHN WAKERLY. 321 pp. with figures and tables. Offers you the newest, most profitable uses of error-detecting codes in the design of logic circuits that check themselves. Combining a comprehensive treatment of the best codes for checking hardware errors in computers with the latest research results. this book is the first detailed study of self-checking circuits using the codes and their applications in computer design.

784/574 Pub. Pr., \$18,95 Club Pr., \$15.50

FORTRAN: A Structured, Disciplined Style. By GORDON B. DAVIS and THOMAS R. HOFFMANN. 372 pp., illus., 812x 11 format. Why another FORTRAN book? First, the 1977 changes in the American National Standard (ANS) FORTRAN made many existing texts obsolete. Second, recent developments in programming style and discipline made most existing works inappropriate. 159/017

Pub. Pr., \$12.95 Club Pr., \$10.50 PROGRAMMING FOR MINICOMPUT-ERS. By J. C. CLULEY 288 pp., illus. For practicing engineers, scientists, and students who must know the latest details and tech-niques of assembly level programming-particularly in the context of on-line operationshere is a book which covers the whole spectrum from the encoding of data and instruc-tions to the specific performance of systems software.

785/49X Pub. Pr., \$17.50 Club Pr., \$13.50

MICROPROCESSOR PROGRAMMING

For Computer Hobbyists. By Neil Graham. 282 pp., with ligures, tables, and samples. If you are a personal computer en-thusiast or technician, this book will prove to be one of the most valuable and interesting investments you can make. It contains full details on programming—from the very basics to the state-of-the-art capabilities—and yet it is written so simply, and progresses in such a direct and logical manner, that any reader, no matter how inexperienced, can easily follow it. 783/56X Pub. Pr., \$12.95 Club Pr., \$10.95 783/56X

**ELECTRONICS DICTIONARY.** Edited by JOHN MARKUS. 4th Ed., 768 pp., 1,173 illus. The indispensable, easy-to-use standard authority on the meaning of 17,090 terms that make up the language of today's electronics is now available in a revised, updated edition. With the vocabulary becoming more challenging and more complex every year, this latest edition is a real necessity for everyone in the electronics community-engineers, techni-cians, technical writers, students, and scientific and technical libraries 404/313

Pub. Pr., \$24.50 Club Pr., \$19.50



MICROPRO	OCESSOR/MICROP	ROGRAMMING		VOLVED WITH YO Guide for Beginners	
768/749	Pub. Pr. 59.95	Club Pr., \$8,45	S. Veit	Guide for Beginners	By L. Solomon &
PROGRAMA	ING MICROPROCE	SCORS D. M 14	771/952	Pub. Pr., \$9.95	Club Pr. \$8.35
McMurran				CESSOR AND MI	CROCOMPUTER
770/913	Pub. Pr., \$9.95	Ciub Pr., \$8.45	783/659	S. By G. V.Rao Pub. Pr., \$24.50	Club Pr., \$19,50
SOFTWARE tices. By G	RELIABILITY Prin	ciples & Prac-	MICROCON	APUTER-BASED DE	
769/885		Club Pr., \$15.75	man 491/380	Pub. Pr., \$26.50	Club Pr., \$18.95
MATHEMAT	TICAL ELEMENTS	FOR COMPUTER	DIGITAL CO	MPUTER DESIGN.	By B. Kline
GRAPHIC	S. By D F Rogers & J	A Adams	784/450	Pub. Pr., \$19.50	Club Pr., \$15.75

MATHEMATICAL ELEMENTS FOR COMPUTER GRAPHICS. By D F Rogers & J 535/272 Pub. Pr., \$12.95 Club Pr. 59.25

57 PRACTICAL PROGRAMS & GAMES IN BASIC. P 784/957 Pub. Pr., \$10.95 Club Ps. \$9.30

	and the second s		
Applya	INCYCLOPED	AUTOMAT	MICROPROCESSOR
MICTOP	OF OF THE D	DATA	APPLICATIONS
	ENCIOOPED OF COMPUTER SCIENCE	HANDBOC	
inter a second se		110740	
X			-
1	1 Identity total Constant		
			in the second seco

574/456

er&JB

BE SURE TO CONSIDER THESE IMPORTANT TITLES AS WELL

### Professionals' Book Club provides you with Values to \$76.95 (and at great savings, too!)

MINIPROCESSORS: From Calculators to Computers. By DAVID HEISERMAN. 195 pp., Illus. If you like to tinker with calculator circuits, this book shows you just how far you can push them. A lot of fun but with serious intentions, it is a machine-language hybrid calculator guide that you'll use for years Club Pr., \$8.45 Pub. Pr., \$9.95 784/71X

#### APPLYING MICROPROCESSORS

New Hardware, Software, and Applications. Edited by Laurence Altman and Stephen E. Scrupski. 200 pp., illus., 81/2 x 11 format. A follow-up volume to Electronics magazine's recently published book, Micro-processors, this work takes you into the second- and third-generation devices rolling off semiconductor lines today. The collection of articles here is designed to smooth your way to mastery of new design methods, and it gives you both an overview of the state of the art and a wealth of design ideas, analyses, and applications

191/603 Pub. Pr., \$19.50 Club Pr., \$15.50 MICROCOMPUTERS/

#### MICROPROCESSORS Hardware, Software, and

Applications. By John L. Hilburn and Paul N. Julich. 372 pp., Illus. This book was expressly created for people involved in the design, use, or maintenance of digital systems using microcomputers. The opening chapters provide needed background in digital logic and present well-organized discussions of number systems, arithmetic operations, and codes employed in microcomputers. The authors then describe the theory and workings behind microprocessor architecture, read-only mem ory (ROM), random-access memory (RAM), and input/output interfacing methods 771/499 Pub. Pr., \$22.50 Club Pr., \$16.50

#### THE 8080A BUGBOOK:

Microcomputer Interfacing and Pro-gramming. By Peter R. Rony, David G. Lar-sen. and Jonathan A. Titus. 416 pp., with figures, charts, and tables, paperbound. Gives you the basic concepts of microcomputer inter-facing and the associated microcomputer I/O programming so you can develop your own in-terfaces to other digital devices. For the 8080 user, this book will be invaluable, because the Intel 8080 is penetrating every facet of life today. creating new industries and threatening old ones, and this book teaches you the fundamental tasks of microcomputer interfacing 783/845 Pub. Pr., \$9.95 Club Pr., \$8.45

#### ANALOG SYSTEMS FOR MICROPROCESSORS AND

MINICOMPUTERS. By Patrick H. Garrett. 248 pp., illus. Explores all possibilities for ana log systems in one applications-oriented volume-with many specific examples. Analog topics presented in this outstanding reference support the growing emphasis on microprocessor and minicomputer applications for real-time data acquisition and control 786/496 Pub. Pr., \$18.95 Club Pr., \$14.95 MICROPROCESSOR

#### APPLICATIONS MANUAL. By Motorola Semiconductor Products. Inc. 720 pp., illus., $8\frac{1}{2} \times 11$ format. With a nuts-and-bolts kind of practicality, this manual by the Motorola people (who should know) gives you detailed applica-

tions information on microprocessors and assumes no prior knowledge on your part about MPUs. It covers all the systems phases and explores such topics as architecture, the instruction set, addressing modes, interrupt structure, and other vital MPU features.

Pub. Pr., \$38.00 435/278 Club Pr., \$26.50 ALGORITHMS + DATA STRUCTURES PROGRAMS. By NIKLAUS WIRTH. 366 pp. illus. Lucid, penetrating, and rigorous, this vol-

ume presents a very systematic and scientific approach to the fundamental techniques associated with data composition and program development. The basic principles discussed here are applicable to many scientific and engineering endeavors.

Pub. Pr., \$19.95 Club Pr., \$15.50 769/664

#### AUTOMATIC DATA PROCESSING

HANDBOOK. Edited by The Diebold Group. 976 pp., 269 illus. Written by a staff of Internationally recognized authorities on ADP and sponsored by one of the nation's leading man-agement consulting firms, this utterly comprehensive handbook explains and discusses computer systems, programming and lan-guages, communications processes, and the design and installation of today's computers. Pub. Pr., \$38.95 168/075 Club Pr., \$25,75 FUNDAMENTALS OF COMPUTER AL-GORITHMS. By ELLIS HOROWITZ and SARTAJ SAHNI. 626 pp. Illus. Some of the most useful, sophisticated, and beautiful al-gorithms that are known fill the pages of this book. But the skills you learn here are more important than just recreation. They give you a distinct advantage since you can apply them to your own work and the work of others 786/380 Club Pr., \$15.95 Pub. Pr., \$19.95

COMPUTER PROFESSIONALS' BOOK CLUB saves you both time and money!

Here is a book club designed to meet all of your professional as well as hobbyist needs by providing practical books about computers on a regular basis at below publisher prices. If you're missing out on important technical literature—if today's high cost of reading curbs the growth of your library-here's the solution to your problem.

The Computer Professionals' Book Club was organized for you, to provide an economical reading program that cannot fail to be of value. Administered by the McGraw-Hill Book Company, all books are chosen by qualified editors and consultants. Their understanding of the standards and values of the literature of interest to you guarantees the appropriateness of the selections. Books are selected from a wide range of publishers.

How the club operates: Thirteen times a year you receive free of charge The Computer Professionals' Book Club Bulletin. This announces and describes the Club's featured book as well as alternate selections available at special members' prices. If you want to examine the Club's feature, you do nothing. If you prefer one of the alternate selections - or if you want no book at all - you notify the Club by returning the card enclosed with each Bulletin.

As a Club member, you agree only to the purchase of four books (including your first selection) over a two-year period. Considering the many books published annually, there will surely be at least four you would want to own anyway. By joining the Club, you save both money and the trouble of searching for the best books.

any <u>two</u> of these great professional books for only

### values up to \$76.95

#### **Two Special** premium books come to you with your first selection

-- MAIL THIS COUPON TODAY -COMPUTER PROFESSIONALS' BOOK CLUB P.O. Box 582, Hightstown, New Jersey 08520

Please enroll me as a member and send me the three books indicated. I am to receive the two bonus books at the Introductory price of \$2.95 plus my first selection, plus tax, postage, and handling. If not completely satisfied, I may return the books within 10 days and request that my membership be cancelled. If I keep the books, I agree to take a minimum of three additional books during the next two years at special Club prices (guaranteed 15% dis-count, often more). I will receive the Club Bulletin 13 times a year. If I want to examine the featured selection, I need I take no action. It will be shipped automatically. If, however, I want an alternate selection—or no book at all—I simply notify the Club by returning the convenient card always enclosed. I will always have a minimum of 10 days in which to return the card and you will credit my account fully, including postage, if this is not the case. Membership in the Club is continuous but cancellable by me at any time after the four-book purchase requirement has been filled. This order subject to acceptance by McGraw-Hill. Or-ders from outside the continental U.S. must be prepaid. Company, business or institutional tax exemption status is not applicable to purchases inade through individual Club memberships. All prices subject to change without notice. Offer good for new members only Postage and handling charges are added to all shipments. Members are billed when books arrive.

Write Coo 1st premium selection	book	Write Code # of 2nd premium book selection here	Write Code 1st book selection here.	
NAME				
	ST/		ZIP	
		emit in full with your on v-Hill will pay all regular	postage and hai	

## ANNOUNCING **AMERKA'S ONLY** LAND, SEA AND AIR SCANNER.

Only the incredible, new, no-crystal Bearcat 220 Scanner tunes in all the real excitement of the entire AM aircraft band—plus every FM public service frequency—with pushbutton ease.

#### Now.

Tune in all the real excitement of the wild blue yonder, at the touch of a button.

The new, no-crystal Bearcat 220 Scanner searches and tunes in the entire aircraft band. Jets at 30,000 feet. All the tense tower talk. Everything is pre-programmed in space-age memory banks.

Only the 7-band Bearcat 220 Scanner also brings home every public service frequency, too. Pre-programmed Marine frequencies. Police action. Fire calls. Weather warnings. You name it.

The new Bearcat 220 has all the features and quality Bearcat Scanners are famous for. Track tuning. Decimal display readout. Automatic Search. Selective Scan Display. Automatic squelch and lockout. Priority. And much, much more.

After all, Bearcat invented Scanning. And we'll stop at nothing to bring you all the excitementof land, sea, and air.



VOLUME

SQUELCH

Electra. Copyright 1979 Electra Company • Division of Masco Corp. of Indiana • 300 East County Line Road, Cumberland, Indiana 46229

PI9dL 121 250

# BUILD THIS

# Polytonic Percussion Synthesizer

Even if you don't play a percussion instrument, you can have loads of fun simulating congas, bongos, wood blocks and timpani; either manually or with triggering from special circuits.


#### **JAMES J. BARBARELLO**

TECHNICALLY SPEAKING, PERSYN (PROnounced "Person") is a manually and/or automatically triggerable, polytonic percussion synthesizer. This fully electronic device contains three independent striking surfaces that, when struck, cause percussion sounds to be synthesized. Each striking surface controls its own percussion sound generator and each surface is adjustable as to the required striking force. Each sound generator is fully adjustable for frequency, envelope and volume of the sound synthesized. Each can also be automatically triggered (by way of the TRIG input/output jack) with a squarewave generator for automated or special effects. Any generator can be combined in the mixer with other signals or processed by special effects devices (such as a balanced modulator for gong and chime effects). Almost all standard percussion effects, such as conga, bongo, bell, wood block and timpani can be generated. The device can also be used with a special interface module (that will be described later) to allow triggering by the amplitude envelope of a conventional electrified instrument, such as an electric guitar.

PerSyn is powered by two 9-volt batteries, uses readily available parts and can be constructed for about \$60.00 (see parts list for complete kit availability).

#### How it works

Referring to the schematic diagram in Fig. 1, we see one of three identical

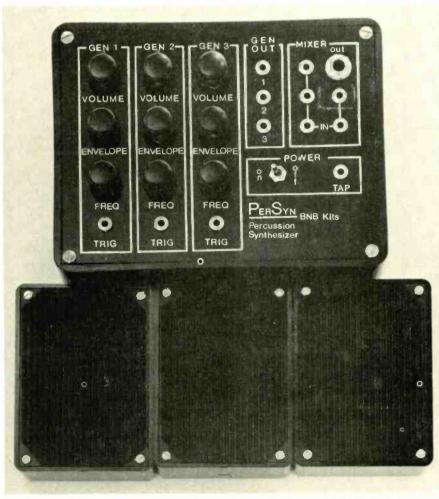

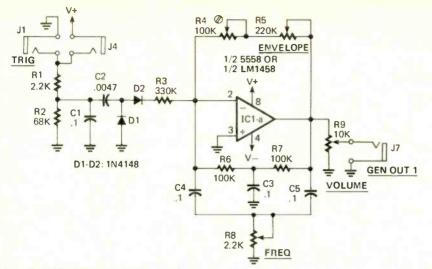


FIG. 1-SCHEMATIC of one of the three identical tone generators.

generator circuits built around two 5558 or 1458 dual op-amps (IC1 and IC2). (Table 1 compares the codes and IC pin connections of Generators 2 and 3 to Generator 2 in Fig. 1.) Using the IC1-a circuit as an example, we see that shorting J4 (or providing a positive voltage level to trigger jack J1) quickly charges C1 through R1. This positive transition is transmitted through C2 as a positivegoing pulse. Diode D2 clips the lower portion of the pulse. When the positive voltage provided by J1 or J4 is removed, C1 discharges through R2 and produces a negative-going pulse through C2. This negative pulse is blocked by D2 so that only a single trigger pulse is generated.

This pulse is applied through R3 to IC1-a, a high-gain inverting amplifier. Feedback loops R4-R5 and R6-R7-C3 and C4-C5-R8 (a twin-T notch filter) control the gain of the amplifier. The twin-T filter attenuates a specific frequency selected by R8. Therefore, if only the twin-T filter were used as a feedback loop, the amplifier would produce a continuous oscillation at the notch frequency. When R4-R5 feedback loop is added, the amplifier gain is reduced to the point where oscillation cannot be sustained. However, when the input trigger pulse is applied, it provides enough "kick" to create a damped oscillation. How long this oscillation lasts (envelope) is determined by the values of R4 and R5. With the values indicated, effects ranging from a short click to continuous oscillation are possible. A portion of the output signal is tapped off vOLUME control R9 and provided to J7 (GEN OUT 1).

The mixer (Fig. 2) circuit has IC2-b connected as a standard unity-gain inverting mixer with a very low output impedance (typically 75 ohms). This lowimpedance output can drive most any standard amplifier. Two transistor batteries (Fig. 2-b) provide  $\pm 9$  volts (that is also available at the TAP jack, J16).

#### Construction

We recommend constructing the cir-

cuit on a PC board, the layout and components placement for which are shown in Figs. 3 and 4. All controls, jacks and the power switch should be mounted in a suitable enclosure (see Fig. 5 for a



INTERIOR of the percussion synthesizer. See Fig. 6 for the hook-up of pots and jacks.

typical layout of components on the enclosure panel). Jack, control and power switch interwiring should be performed at this point as indicated in Fig. 6. Upon completion, the 21 wires from the PC board (identified as "A" through "U") are connected to the control plate. If solid wire is used, the PC board will be well

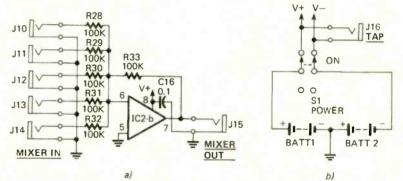


FIG. 2-DIAGRAM of the five-input mixer. Circuit uses an op-amp connected as a unity-gain inverter. The output impedance is approximately 75 ohms.

Generator 1	Generator 2	Generator 3	Value	
ICI-a	IC1-b	IC2-a		
R1	R10	R19	2.2K	
R2	R11	R20	68K	
R3	R12	R21	330K	
R4	R13	R22	100K trimme	
R5	R14	R23	200K pot	
R6	R15	R24	100K	
R7	R 16	R25	100K	
R8	R17	R26	2.2K pot	
R9	R18	R27	10K pot	
IC1-a	IC1-b	IC2-a	1/2 5558 or 1/2 LM1458	
DI	D3	D5	1N4148	
D2	D4	D6	1N4148	
C1	C6	C11	0.1	
C2	C7	C12	.0047	
C3	C8	C13	0.1	
C4	C9	C14	0.1	
C5	C10	C15	0.1	
J1	J2	J3		
J4	J5	J6		
J7	18	19		
V+		V+		
2 8	6	2 8		
IC1-a 1	IC1-b 7	IC2-a 1		
3	5	3 10248		
4		4		
V-	-	V-		

RADIO-ELECTRONICS

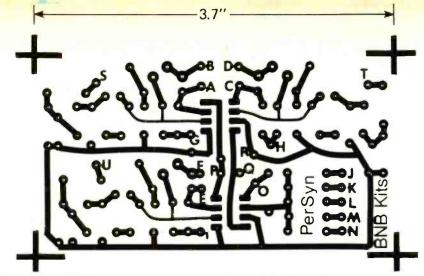


FIG. 3-FOIL PATTERN of the percussion synthesizer printed-circuit board. You can etch your own or get them in the complete kit of parts that is available.

supported by the interconnection wiring and no separate mounting is required.

The two 9-volt batteries (connected as in Fig. 2-b) should be mounted in the case. They can be held in place by a 1 by 3-inch piece of aluminum with a hole drilled in the center. By drilling a corresponding hole in the case bottom, a  $\frac{6}{32}$  X 1-inch screw can be passed through the case, between the batteries and through the aluminum plate. A nut tightened down will then keep the batteries from moving.

#### PARTS LIST FOR PERCUSSION **GENERATOR** (Figs. 1 and 2)

- Resistors 1/4 watt, 5% unless otherwise noted
- R1, R10, R19-2200 ohms
- R2, R11, R20-68,000 ohms
- R3, R12, R20-330,000 ohms
- R4, R13, R22-100,000 ohms, trimmer potentiometer
- R5, R14, R23-220,000 ohms, miniature potentiometer
- R6, R7, R15, R16, R24,
- R28-R33-100,000 ohms
- R8, R17, R26-2200 ohms, miniature potentiometer
- R9, R18, R27-10,000 ohms, miniature potentiometer
- Capacitors, disc ceramic, 10 volts or higher
- C1, C3-C6, C8-C11, C13-C16-0.1 µF
- C2, C7, C12-.0047 µF
- D1-D6-1N4148
- IC1, IC2-1458 or 5558 (8-pin DIP dual op-amp)
- J1–J14, J16—miniature phone jack
- J15-phone jack (full size)
- S1-DPDT switch
- BATT1, BATT2-battery, 9 volts

Note: A complete PerSyn kit, consisting of all required parts as listed above, all predrilled and marked enclosures and complete assembly instructions (Kit PS-1) is available for \$59.95 from BNB Kits, R.D. 1, Box 241H, Tennent Road, Englishtown, NJ 07726.

The above price includes U.S. postage and handling. Canadians add \$1.50 additional per order. New Jersey residents add 5% sales tax. No C.O.D. orders. Please allow 4 to 6 weeks for delivery.


#### Accessories


To fully use the capability of the device, three striking surface boxes should be constructed. The striking surface box contains a trigger switch assembly (see Fig. 7) and a thin plastic cover plate. (When assembled as shown, the adjusting screw can be rotated to force the PC board upward. This movement depresses the calculator switch to the point where a slight depression of the cover (striking surface) will close the switch contacts and generate a trigger pulse. The PC pattern is in Fig. 8a; Fig. 9 shows how the calculator switch goes on.)

The wires from the trigger switch assembly are connected to a phono jack or plug mounted in the case side (if the phono plug is used, the box can be plugged in directly to J4, J5 or J6). A piece of rubber should be used to cover the cover plate to lessen the noise when it is struck. The rubber can be secured with double-faced tape.

#### Initial adjustment and checkout

Place all controls and trimmers to midposition. Short J7 (GEN OUT 1) to J10 (MIXER IN) and connect J15 (MIXER OUT) to your amplifier. Place a phone plug in J4 and turn on the power. (Note: If you hear a continuous oscillation, proceed to

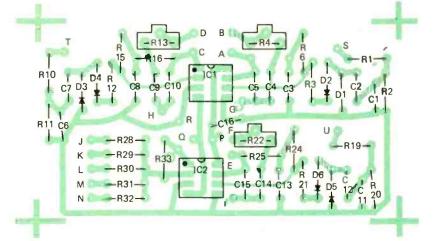

 

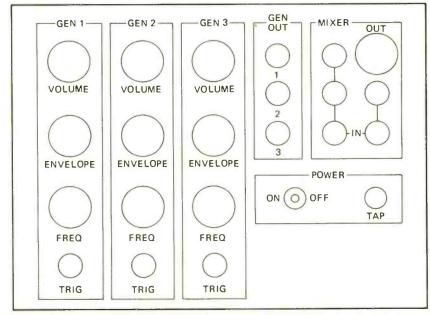


FIG. 5-TYPICAL LAYOUT for the components that are mounted on the front panel of the generator. Grouping of components makes the instrument easy to use.



#### JACK LEGEND NOTE: DPOINTS A-U CONNECT TO CORRESPOND-ING POINTS ON PC BOARD

2B1 & B2 ARE 9-VOLT TRANSISTOR BATTERY CONNECTORS.



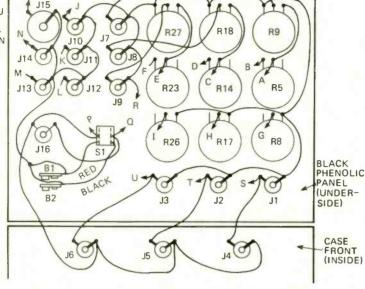


FIG. 6—INTERWIRING of the components on the control panel of the instrument. The points marked "A" through "U" are for making connections to the PC board.

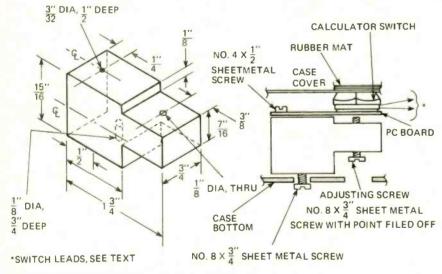

NOTE: DIMENSIONS SPECIFIED ARE FOR USE WITH KEYSTONE ELECTRONICS CASE NO. 703, BLACK PHENOLIC PANEL CATALOG NO. 2042 AND OAK CALCULATOR SWITCH NO. 7302.

FIG. 7—MECHANICAL CONSTRUCTION of the three striking blocks. Leads from the switches go to miniature phone plugs mounted on the end panels of the small enclosures.

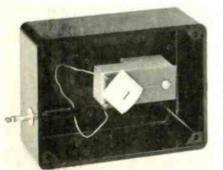


#### INSIDE THE STRIKING BLOCK. This particular block is on the right in lead photo.

the R4, R5 adjustment.) Momentarily short the contacts of the plug in J4 and note if an output is heard. Rotate R5 (EN- VELOPE) fully clockwise. Rotate trimmer R4 until a steady oscillation is heard. Back off R4 until the oscillation ceases, or to minimum resistance if oscillation does not cease. Reset R5 to midposition. Repeat this procedure for generator 2 (J5, J8 (GEN OUT 2), J11 (MIXER IN) trimmer R13 and R14 (ENVELOPE)) and generator 3 (J6, J9 (GEN OUT 3), J12 (MIXER IN), trimmer R22 and R23 (EN-VELOPE). Also use J13 and J14 (MIXER IN) to insure they are functioning.

Place a phone plug in J16 (TAP) and a phone plug in J1 (GEN 1 TRIG). Short the tips of the two plugs and note the presence of an output. Repeat this procedure using J2 (GEN 2 TRIG) and J3 (GEN 3 TRIG). If a voltmeter is available, measure approximately 18 volts between the phone plug tip and body in J16.

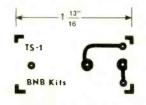Connect a striking surface box to J4. Rotate the adjusting screw clockwise until an output is generated. If nothing is heard, the screw may be advanced too far.



TRIGGER SWITCH P.C. BOARD FIG. 8—SIMPLE PC PATTERN for the striking block.

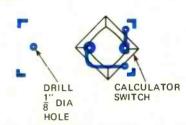


FIG. 9—CALCULATOR SWITCH positioned on the PC board. See photo on this page.

Back off the screw a few turns and begin again. After a sound is generated, back off the adjusting screw about a quarter turn. Tap the cover plate and note the presence of an output. Adjust the screw to obtain the sensitivity desired. Repeat this adjustment for the remaining two striking surface boxes.

#### Use

Once the initial adjustments have been completed as above, the basic operation of the device should be clear. Experiment with all controls and note their effect on the sounds created. When the unit is not being used, turn the power off to conserve battery life.

There are a few modifications you might like to make. The minimum setting of the frequency control may not produce a low enough frequency output to synthesize sounds such as a bass drum. If this is the case, you may wish to modify one or more of your generators in the following manner: Remove the three  $0.1-\mu f$  capacitors in the twin-t notch filter section (C3, C4 and C5 for generator 1) and replace them with  $0.2-\mu f$  units ( $0.2-\mu f$  units may be created by paralleling two  $0.1-\mu f$  capacitors). This modification should lower the complete frequency range.

There are several options that can increase the capability of the PerSyn. Among them are a pulse generator that will automatically trigger the PerSyn at a rate adjustable from around 1 Hz to 500 Hz. a balanced modulator for producing chimes and similar metallic sounds and a trigger interface for triggering the Per-Syn in step with the keying of another musical instrument. These options and details on their use and construction will be covered in the following issue. **R-E** 

# TELEVISION

LAST MONTH WE GOT A LOOK AT EARTH satellites and how they are used in domestic and world-wide communications. Now we'll conclude with a look at the "birds" that carry TV programming of interest.

#### 40-plus TV channels

Imagine you're sitting in your living room on a Sunday afternoon trying to decide what you want to watch. On local TV (or "terrestrial" as we'll call it from this point onward) there are a couple of network-selected regional professional football games, an old movie and a PBS program on how to prepare fall bulbs for planting. The two football games don't include any team you are really interested in, so, let's see what's on the satellites.

We'll start on the eastern edge of the active U.S./Canadian orbit belt with the WESTAR I at 99 degrees west:

Transponder 1 has a pro football game being relayed via satellite to who knows where; Transponders 2, 6 and 10 also feature football games, none of which are on terrestrial TV. Transponders 8, 9 and 11 present three separate PBS programs, one matching the local PBS channel. Transponder 12 is showing a professional soccer game originating in Minneapolis and relayed to Los Angeles. Next, ANIK III, the prime Canadian satellite, is stationed at 114 degrees. On Transponder 4 the CBC is running a "pre-network feed" for a program to be viewed on terrestrial TV later that evening in Canada. Transponder 8 shows a French language movie. Transponder 10 features a Canadian Football League football game, while Transponder 12 is showing a hockey game from Vancouver.

Moving on to RCA SATCOM F2 (at 119 degrees) Transponders 4, 10, 16 and 20 are showing more pro football games. One of these games is being shown on your local NBC affiliate; the other three are not available locally. On Transponder 8, there is an NBC network prefeed of Part 2—The conclusion of a story on domestic satellic communications and its use in distribution of TV programs.

SATELLITE

Reception

ROBERT B. COOPER, JR.

Home

that evening's Walt Disney program, beamed from Los Angeles to New York for network viewing several hours later. Transponder 18 has another prefeed for NBC; this one is a news report for the next day's "Today Show". On Transponder 22 a golf match is being relayed live from a South Carolina locale where it is being transmitted to major-market independent TV stations. Finally, Transpon-

via

der 23 is carrying a special program presented by the Alaskan Native's Federation being relayed via satellite to approximately 50 Alaskan "Bush Terminal" sites.

Our next stop is WESTAR II at 123.5 degrees west. Between WESTAR I and SATCOM II we've already run into eight professional football games. Eleven will be played that afternoon so we are not surprised to see engineers, technicians and announcers preparing for one more on transponder 3. Transponder 1 carries New York City's WOR-TV, (a highly rated independent station) which is being fed to cable systems, and is showing an old black-and-white Bogart film. On Transponder 4 Chicago's station WGN is showing Star Trek to cable systems. Transponder 7 shows a bullfight, direct from Mexico City's station XEW-TV. Transponder 7 carries an average of 12 hours of Spanish language programming per day, much of which is transmitted directly from Mexico City to a handful of U.S. Spanish language TV stations in Miami, San Antonio and Los Angeles. Way up on Transponder 12 station KTTV in Los Angeles, another independent station being fed to cable systems nationwide, is wrapping up the Dodgers' baseball season. Since this station televises around 100 live Dodger games each year, this broadcast of a Dodger game fits its format.

There's still "nothing to watch," so you head for "the big one," RCA's SAT-COM F1 (at 135 degrees west). You run through one of the three ATT/GT&E "telephone company" birds, COMSTAR I, at 128 degrees west. Normally, they don't have much video on them but you check anyway. There on Transponder 14 are a couple of people talking. It seems to be one-half of a conversation. Up on Transponder 18 you find the other half: a group of scientists in Honolulu are talking with politicians in San Juan.

You're not interested, so you now move the antenna round the last notch to SAT-COM F1. Surely here you will find something interesting to watch. After all, there are 20 separate almost full time video channels on F1!

On Transponder 1 station KTVU from San Francisco, another independent station, is showing a movie. Transponder 2 carries PTL, a 24-hour-per-day religiousbased family entertainment service. Transponder 3 is showing Chicago's WGN broadcast of Star Trek again. On Transponder 5 you find "Nickleodeon," a 13-hour-per-day Children's Television Network created by Warner (Brothers) Cable. Transponder 6 carries Atlanta's "Super Station" WTCG, with wrestling. On Transponder 7 "ESP," a New England regional service, is showing playbacks of the area's college football games. Then on Transponder 8 you tune into CBN (Christian Broadcasting Network) the original 24-hour-per-day, satellitetransmitted religious-family channel.

Transponder 9 gives you Knicks basketball game direct from Madison Square Garden (there are more than 1000 hours of Madison Square Garden events on this transponder per year). During the week and in the daytime, Transponder 9 televises U.S. House of Representatives sessions live from Washington, which also totals about 1000 hours per year. On Transponder 10 you find the West Coast feed for "Showtime," a 12-hourper-day movie and entertainment service; they are running a current children's (Grated) hit movie. Tuning to Transponder 11 you find Warner's "Star Channel," a 14-hour-per-day movie and entertainment service, showing a Tom Jones nightclub act from Las Vegas.

Transponder 12 gives you "Showtime's" East Coast channel and a Burt Reynolds movie. One nice thing about having an East and West Coast feed from SHOWTIME (and HBO) is that if you don't have the time to sit down and watch Burt Reynolds now you can come back in three hours and catch it on the West Coast channel at that time. Transponder 13 is running some engineering equipment tests. Transponder 14 also is showing the 24-hour-per-day religious channels-KTBN or Trinity Broadcasting. Only this channel, unlike PTL (Transponder 2) or CBN (Transponder 8), is a regular broadcast TV signal that happens to be sent out via satellite. (CBN and PTTL are special feeds created just for the satellite) On Transponder 16 you find, "Fanfare," a southwestern U.S. regional pay cable service specializing in late-release movies, nightclub and stage acts, and regional sports. Transponder 18 shows some digitally transmitted news from Reuters, on which, with a special receiver adapter, you can watch the latest world news. Transponder 20 is running a movie epic on oil exploration. Transponder 22 has the West Coast feed for HBO (Home Box Office), and as you tune in they are previewing the day's movie and

Are people actually watching all these programs? They sure are, and with their own backyard receiving systems.

They all must be millionaires, you might think. To be sure, a few had to be able to afford the prices being charged for "cable television grade receive terminals" back in 1977 or even early 1978. But let's back up a few steps again and take a look at some of the satellite specifications.

#### Microwave in the sky

A satellite is a combination of microwave electronics, solar-powered electronics and rocketry. Stripped of all of its mind-boggling exotic details, a satellite is nothing more than an unattended relay station. It has one set of antennas to receive the transmissions originating on earth (called uplink signals), and another set of antennas to retransmit those signals back to earth (called downlink signals). The uplink signals are between 5.9 GHz and 6.4 GHz (5900 MHz to 6400 MHz), and the downlink signals are between 3.7 GHz and 4.2 GHz (3700 MHz and 4200 MHz).

The uplink and downlink frequencies divided into (typically) 40-MHz-wide channels; and since the up and down frequency bands are 500 MHz wide, there is room for 12.5 such channels both up and down. This results in a maximum capacity of twelve 40-MHz-wide channels, plus some room for ground-to-satellite command signals, satellite-to-ground acknowledgment signals, and a couple of "beacons" to help ground control measure exactly where in space the satellite is located at any given moment. (See Fig.

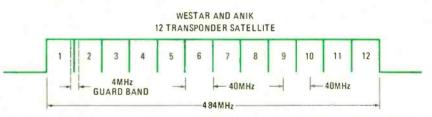


FIG 4--THE DOWNLINK BAND is 500 MHz wide from 3.7 to 4.2 GHz and is divided into 12 channels. Each channel is 40 MHz wide.

special fare. Transponder 23 has the HBO family-program service called "Take Two"; and a recently released Walt Disney movie. Finally, in the last transponder position, HBO's East-Coast feed service gives you the movie you wanted to watch. Decisions, decisions: Should you watch the movie now or catch it later on West Coast Transponder 22?

From Canadian hockey live from Vancouver to a bullfight telecast live from Mexico City, you have a choice of 11 professional football games, a motorcycle race from Houston or a soccer match from Minneapolis. These broadcasts are shown with such clarity and resolution that you almost feel compelled to reach out and touch the screen. That's what satellite TV means to those equipped to receive it. 4.) There can be more than 12 channels on a single satellite, however, and we'll see why that's possible in a later article.

The electronics inside most of today's satellites is fairly similar in design up to the output stages and the transmitting antennas. The uplink signals (between 5.9 GHz and 6.4 GHZ) are received via fairly wide-beam "sculptured" antennas that cover all the service area fairly efficiently. Being directional antennas, they have a pattern, and in satellites the center of the antenna pattern is called the "boresight point." The boresight point on the receive antenna is where maximum gain occurs, as well as on the downlink transmitting antenna. All received signals are processed by a broadband (5.9-6.4 GHz) front end. The signals are amplified and fed into a converter stage that translates

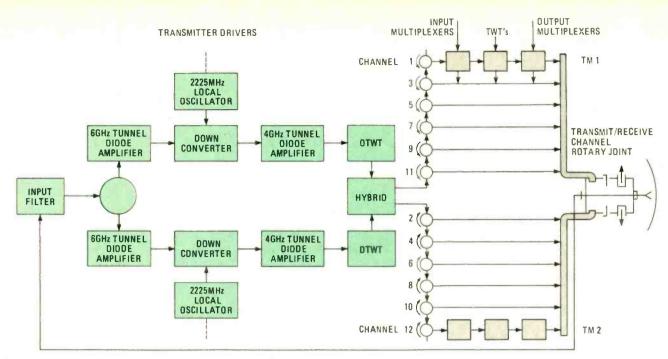


FIG. 5-12 CHANNEL SATELLITE designed by Hughes Aircraft.

their incoming frequency down directly to the appropriate area in the 3.7- to 4.2-GHz range.

Figure 5 is a block diagram of a typical 12-transponder satellite, in this case, the ANIK series. Note that the input side is redundant; this is a security measure in case something in this broadband circuit area should fail prematurely. Once the signals have been translated down to the 4-GHz range, they are fed into the appropriate output-amplifier stages; individual TWT (Traveling Wave Tube) outputamplifier stages are included for each transponder. The peak power at this point is 5 watts (+7 dBw, or decibels above 1 watt) and from there the 5 watts are coupled into the appropriate downlink transmit antennas. The transmit antennas have gain (with reference to a dipole or isotropic source) and the gain added by the directional transmit antenna measured in dB's is added to the poweroutput level of the TWT amplifier. This results in an effective radiated power (EIRP) for the downlink system. At boresight on the transmit antenna, the power generated is in the +34-dBw to + 37-dBw range; this varies slightly from satellite to satellite.

The ground-to-satellite signal path (in the 6-GHz range) requires substantial transmitter power (i.e., 1 kW to 3 kW) plus large antenna gains (50 dB to 60 dB) to saturate the input of the satellite with high-quality (noise-free) signals. Like any relay station, the signal quality returning to earth is only as good as that initially transmitted to the satellite. On the uplink path, free space loss approximates 198 dB.

Our primary interest is in the downlink path since that is where we can particpate. Figure 6 shows how the ANIK satellite views Canada:

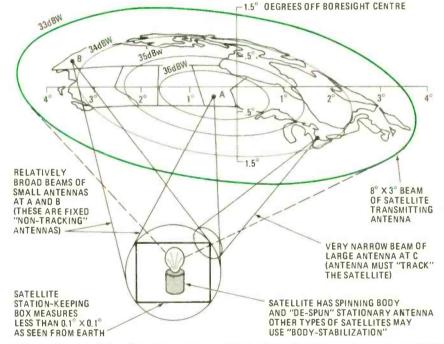


FIG. 6—TYPICAL COVERAGE of the earth's surface by a satellite. Two different approaches to receiving antennas are shown. Small antennas with a broad beam can be non-tracking while large antennas with a narrow beam must track the satellite.

#### **TVRO terminals**

TVRO (Tele Vision Receive-Only) terminals really came into being when satellite relay service was inaugurated for cable TV companies. Since September 1975 their development has followed closely the established criteria for the big (and expensive) Intelsat stations.

When the first cable TV use of satellites started the present gold rush in the sky, the FCC had no ready system for handling the explosion. Because Intelsat stations were more often than not both reception and transmission systems, they naturally required FCC licenses. Domestic terminals that were first installed by RCA, Western Union and (in Canada) by Telesat were both transmit and receive terminals. RCA, for instance, built ground-station terminals near major metropolitan centers and used terrestrial microwaves to link into and out of these centers. The New York City area is served from a location near Sussex, NJ, called Vernon Valley. This site (close to two other major uplink and downlink control sites) is the "first north-south valley location west of New York City where there is terrain shielding" from terrestrial microwave emissions.

This is important because the downlink frequency band in use (3.7 GHz to 4.2

GHz) is a shared band, that is, it is also used as the heavy microwave trunk route for the Bell Telephone Company (and other phone systems) throughout the U.S. Because the telephone company microwave circuits criss cross the country in the same frequency band as the downlink signals from the satellites, there exists a potential for interference. Fortunately, because of the highly directional characteristics of the parabolic antennas used in satellite reception (and the point-to-point "thin-line path" design of terrestrial telephone circuits) the two can operate closely without interference. What interference there is results from transmissions from the terrestrial circuits to the satellite-receive terminals since the latter do not transmit. (My own terminal is only 2.4 miles from a major Bell Company relay site, but we have never experienced any interference at our receiving TVRO.)

This does indicate however that occasionally a nearby terrestrial microwave transmitter, located either very close to you and to the side or out in front of you (i.e., on a line towards your satellite heading), could cause some interference with satellite reception. We'll look at solutions to this problem in a later article.

One of the manageable things about the satellite-to-earth system is its high degree of signal-level predictability. Between the excellent station keeping by the "flight engineers" and the well-known parameters of space loss between the satellite and earth, engineers with calculators or enthusiasts with TRS-80 computers can determine within 0.1 dB the type of signal level that can be expected at a given location. Adjusting to 0.1-dB signal-level steps is part of adjusting to satellite technology.

The satellite's signal is contained within a 36-MHz-wide frequency bandwidth. The video signal is frequency-modulated (FM) and the audio signal is also FM, being transmitted as a subcarrier signal at either 6.8 MHz or 6.2 MHz. Because this is an FM/FM system, several important factors must be considered that are not part of normal AM (terrestrial TV) transmission. The foremost factor is called "the FM threshold." Let's simplify what that is:

- 1. When an FM signal (on an FM set, a two-meter amateur radio, etc.) reaches "full quleting," all background noise is gone.
- As long as the signal stays above the "threshold of noise," you have no way of judging (without some complicated meter measurement) how close you are to the noise since in "full quieting" there is no noise.
- The signal may be far above quieting (into heavy limiting) or it may be simply right on the ragged edge (on the plus side) of noise; it all sounds the same.
- 4. However, when you fall out of full

quieting (that is, the signal level slips down in level and there is no limiting action) noise appears quite suddenly and often very dramatically.

This indicates that if the frequencymodulated satellite video signal could be maintained just above the noise threshold and if the satellite signal was very stable, you could get by with a "low-margin" (for fading) receive system that would to all normal eyeball testing give the same apparent picture quality as a signal that is many many dB stronger than full quieting. When you include in your calculations a parameter called the FM advantage (along with the other parameters of this particular system), a noise-free picture occurs when there is a 48-dB signalto-noise ratio, as measured at the baseband video signal. FM advantage derived from this type of service, with normal receivers, is around 37 dB (give or take a few tenths of dB's) If you subtract 37 dB (the FM advantage) from the noise free video signal-to-noise ratio (48 dB) this gives you the type of 4-GHz-range carrier-to-noise ratio your receiver must attain: in this case, 48 - 37 = 11 dB. Some fine tuning can be done with these values, but for now they are close enough.

When you go through all the system's mathematical components (satellite EIRP minus free-space loss minus receiver-noise value plus antenna gain) for 48 dB video signal-to-noise pictures, you need a 10-foot parabolic dish antenna with a 2.6-dB noise figure signal preamplifier, also called a low-noise amplifier (LNA). This is if you are within a 36-dBw contour and use a receiver with an adjusted IF bandwidth of 27 MHz.

Let's leave you with this bit of reassurance. If you sat down with an order form from established, reputable manufacturers selling hardware to the CATV (etc.) commercial users and bought everything you need for this type of reception already assembled (you would do the actual installation), you could buy everything necessary for 48-dB video signalto-noise-ratio reception for less than \$5500. And that includes a 24-channel tuneable receiver.

While a far cry from the \$100,000 early turnkey cable systems of 1975, it may still be too rich for your blood. So, let's add this postscript: If you built your own antenna and LNA, and assembled your own receiver from prewired and tested modules, it would cost about \$3000. Still too much? Here's the bottom line for this month: A California hobbyist assembled his own system for under \$1500, using lots of ingenuity and a good knowledge of surplus equipment. And a fellow in Sheffield, England, built his private terminal for under \$1000. We'll dig into all this with some enthusiasm in a future article. R-E

## HOBBY

#### L. STEVEN CHEAIRS

AS ELECTRONIC PROJECTS HAVE GROWN IN complexity, the problems of interconnecting the components have grown as well. When I first started building projects, point-to-point wiring was the most common method of interconnection. Today the most common interconnections are copper traces on a printed-circuit board. As the transition occurred, a number of "how-to" electronic hobbyist magazine articles were published. Unfortunately, none of the articles I have read ever discussed the topic of printed-circuit design; instead they dealt with PC fabrication or artwork generation. So, let' take a more general look at PC design starting with the choice of board material.

#### **Choosing PC stock**

There are seven general classes of copper-clad stock used today; three of them are a phenolic paper base and four are a type of glass epoxy. The first phenolic paper material has two subclasses—designated XXXP and XXXPC—where the only difference in their characteristics is that the XXXPC material must be punched in a temperature range of 73 °F to 140 °F (for a board-thickness range of  $\frac{1}{16}$  to  $\frac{1}{8}$  inch).

The PC board is made using a paperbase stock that is impregnated with phenolic resin. Generally, the material is opaque with a medium-brown color.

The second material is made of flameretardant paper phenolic and is designated FR-2. The color ranges from medium to dark brown.

The third paper-based material is FR-3 laminate impregnated with epoxy resin. There are two subclasses—PX and PH. This laminate is translucent (for <sup>1</sup>/16-inch or less thickness) and usually is a light yellow or white color. Epoxy paper is flame-retardant and self-extinguishing. The PX laminate is generally used when holes are cold-punched; the PH laminate on the other hand is hot-punched.

The remaining materials are of the glass-epoxy type. The first is G-10 stock which is the standard general-purpose grade. It is formed from a glass-base continuous-filament cloth that is then impregnated with an epoxy-resin binder. The board is semitransparent and is usually a medium-green color. The G-10 stock is used only in the range of normal ambient room temperature. It should not be used to mount heat sinks or in unventilated enclosures where heat is being generated or dissipated. There is hardly an electronic project designed today that does not have a printed-circuit board. If you design your own equipment, this story tells what you need to know to put it on PC boards.

The second is the G-11 material which is temperature-resistant grade. The material retains at least 50% of its roomtemperature flexural strength at an elevated temperature of 150 °C for one hour. The third glass-epoxy material is the FR-4 laminate which is a flame-retardant epoxy glass. This material is generally a yellow-green to medium-green color. Some manufacturers market dark opaque versions of varying colors.

The final type of laminate is of flameretardant and temperature-resistant glass-epoxy stock. Its NEMA (National Electrical Manufacturers Association) designation is FR-5. The material can be recognized by its semitranslucent brown to dark green color; some varying opaque colors are also manufactured. Now that you are familiar with what materials are available and how to identify them, we'll look at their individual characteristics.

#### **Physical characteristics**

An important featurTof any laminate is its capability to withstand deformation under load. It is this characteristic that defines how well components that are bolted or riveted to the board can withstand the board's tendency to deform and thus loosen the connection. Nowadays, voltage regulators are generally mounted on the board. When a TO-3-type case is used, two screws act as one of the electrical terminals; if they become loosened after assembly, then erratic operation of the complete assembly will surely result.

**B(0)** 

C BOAR

Another consideration is that the board acts as a shock amplifier. In this case the loosened bolts would leave the massive TO-3 case suspended by two pins. These pins are insulated from the package by glass seal rings—thus, one good-sized shock and you may need a new voltage regulator. If the laminate materials discussed above were subjected to 24 hours of a 4000 PSI load at 70 °C, the following deformation characteristics would be observed:

XXXP	1.7% deformed
FR-3	1.5% deformed
G-10	0.3% deformed
G-11	0.1% deformed
FR-4	0.2% deformed
FR-5	0.1% deformed

The modulus of elasticity is the amount of stress that a material can be subjected to without permanent deformation. The stress capability of the XXXP and the FR-3 materials is identical (about 1,300,000 PSI); that of the G-10 and FR-4 types is about twice that of the XXXP and FR-3; and the G-11 and FR-5 types are a bit more resistant yet. Flexural strength, or the load the laminate will stand without fracture, is about 12,000 PSI for the XXXP material. The FR-3 laminate is about twice as hard to break, and the glass epoxy is over twice the flexural strength of the FR-3 laminate.

The FR-3 copper-clad material resists delamination (the copper clad separating from the base material) for 5 seconds at 500 °F; the glass epoxies resist delamination at the same temperature for 20 seconds. The maximum continuous operating temperature of the XXXP and FR-3 materials is 120 °C; the G-10 and FR-4 glass-epoxy materials can operate at up to 130 °C; and the G-11 and FR-5 laminates can withstand 150 °C. The glass-epoxy materials can withstand fungus, the paper-phenolic types will not.

The remaining laminate characteristics are those that affect the electrical circuit. The dielectric strength (i.e., an insulator's capability to resist the passage of an electric current) is 740 volts-per-mil for XXXP; 550 volts-per-mil for FR-3; 510 volts-per-mil for G-10; 600 volts per mil for G-11; 500 volts-per-mil for FR-4; and 490 volts-per-mil for FR-5 stock. The dielectric breakdown for  $\frac{1}{10}$ -inch-thick material is 15 kV for XXXP; and 30 kV for FR-3, G-10, G-11, FR-4 and FR-5 materials.

The dielectric constant is the ratio of the capacitance of a capacitor with a given dielectric material to that of the same capacitor with air as a dielectric. The dielectric constant varies with temperature, humidity and frequency. The following data is shown for material tested at 1 MHz that has been preconditioned by being soaked in distilled water for a day at room temperature. The XXXP is 5.3, the FR-3 is 4.8 and the glass-epoxy boards are 5.4. The dissipation factor is the ratio of total power loss to the product of the voltage and current in a capacitor in which the laminate is used as a capacitor. The glass-epoxy materials have a dissipation factor of 0.035, the FR-3 materials, 0.040 and the XXXP material, 0.050.

#### **Drilling holes**

Holes are generally drilled in the PC board, as opposed to being die-punched, when low-production quantities are encountered or where higher quality with better tolerance is needed. The drill tolerances will be about -0.002 inch for all holes under  $^{3}/_{32}$  of an inch in diameter; the tolerance will be -0.003 inch for holes between  $^{3}/_{32}$ -inch and  $^{1}/_{4}$ -inch in diameter; and -0.004 inch for holes larger than  $^{1}/_{4}$ -inch in diameter.

For the paper-phenolic materials, almost any high-speed drill bits can be used. When drilling through paper phenolic, best results are obtained with a point angle around 70 degrees; however, burrs occur on the copper foil, so a compromise angle of 100 degrees is generally used.

Glass-epoxy laminate is another story—high-speed drill bits, chrome-plated or even nitrided drills, seem to melt away before your eyes. Solid-carbide drill bits are a must; these bits will produce from 10,000 to 30,000 holes (that is, if you don't break them) for G-10 and FR-4 materials. The FR-5 or G-11-type laminate will yield about 2000-5000 holes. Carbide drill bits are very brittle and easy to break. When drilling it is also recommended that you place a piece of board of same type as that being drilled under the PC board to keep the pressure on the bit constant.

#### **Electrical parameters**

A critical parameter of low-impedance circuits is the resistance of a printedcircuit trace. The TTL circuits and linear-voltage regulators that are commonly used by hobbyists are low-impedance circuits. If a conductive path becomes long—let's say it connects components on one side of an S-100 bus board to components on the other side—then close attention must be given to loads on that line or erratic operation may result. For 2-oz. copper stock, the resistance in ohms per linear inch, R, can be calculated as a function of line width (W, in inches) by the following equation:

$$R = \frac{0.000277}{W}$$

This calculation must be made for all power circuits and low-impedance logic arrays with long lead lengths.

If high-frequency circuits are to be constructed, then capacitance becomes very important. At high frequencies any distributed capacitance between conductors on opposite planes must be accounted for. A working guide can be obtained from

$$C = (0.00235) \frac{W d}{s}$$

where C is the capacitance in picofaradsper-inch, W is the conductor width in mils, d is the dielectric constant, and s is the thickness of the laminate in mils. The capacitance between parallel conductors on the same plane is a function of width, thickness, the spacing of the conductors, and the board material, as shown by the equation:

$$C = \frac{t}{3.23 \text{ W}} + \left(\frac{1+d}{4.35}\right)$$
  
g 10 $\left(1 + \frac{2 \text{ W}}{s} + 2 \times \text{ W} + \frac{\text{W}^2}{s^2}\right)$ 

where t is the conductor thickness in inches; all other symbols are the same as the previous equation.

10

Consideration should be given to any conductor located over a ground plane, since the entire length of the track is capacitance-coupled to the plane; as a result they are coupled to other lines with a similar relationship. It should be noted that for high frequency operation where critical circuits are involved, single-sided boards are unusable; ground planes and strip-line construction are mandatory. The ground plane significantly reduces the coupling between two adjacent single lines by as much as ten times.

One final electrical parameter that must be considered is the current flow with respect to temperature. Figure 1 shows a set of current vs. cross-sectional area curves, each of which represents the temperature rise above ambient. Therefore, it is possible for the designer to choose an acceptable temperature rise and the desired maximum current level for a PC trace and determine a crosssectional area. Next, you must find the minimum trace width by dividing by the copper-foil thickness (0.004 inch for 3oz. stock, 0.0027 inch for 2-oz. stock. 0.00135 inch for 1-oz., stock, and 0.00067 inch for 1/2-oz. stock). Using the above data assures having minimum conductor widths without sacrificing reliability. Trace spacing is a function of the printed-circuit process and breakdown voltage. For low-voltage logic circuits, traces can be placed within 15 mils or less


#### **Structural characteristics**

Earlier it was stated that a circuit board is a shock amplifier. This section discusses general PC mounting.

The two common board-mounting methods are: one end fixed, say, in an edge connector, with rails providing minimal support on the two sides; and a board clamped on both ends by rails or standoff insulators. The mechanical resonant frequency of the board depends upon the fastening method used and on its modulus of elasticity, its thickness, weight persquare-inch and length. The curve shown in Fig. 2 is a plot of board length vs. resonant frequency (where the modulus of elasticity equals 1,800,000 PSI; the thickness is 1/8-inch, and the board's weight per-square-inch is 0.016 PSI). Using the equation of Fig. 2, an S-100 bus board using G-10 glass epoxy would have a 101-Hz resonant frequency. If this board were clamped on the free end, its resonant frequency would become about 655 Hz. If paper-phenolic XXXP stock were used, the S-100 bus board (unclamped) would become resonant at about 70 Hz.

#### The vibration factor

Why is mechanical resonance so important? Most electronic equipment is subject to shock or vibration, even if only during shipping. A few decades ago when jet airplanes were just arriving on the scene, a new technology was discovered—

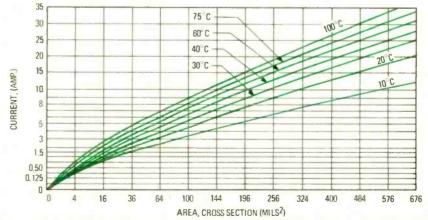



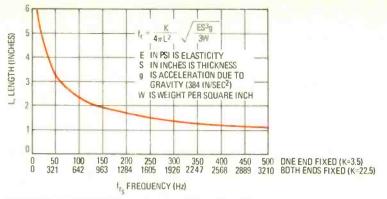


FIG. 2—RESONANT FREQUENCY as a function of board length.

the study of material fatigue. If your equipment is to be installed in a car, you should definitely give a thought to material fatigue. The best way to avoid problems is to design the resonant frequency of your board so that it is outside the band of vibration to which it will be subject. A ship or boat has a constant vibration of about one-third of a G between 0 Hz and 11 Hz; from 11 Hz-30 Hz it rises to about two-thirds of a G; throughout this frequency range, sporadic vibrations of just less than 1 G may occur. For aircraft a constant 1-G vibration between 0 and 50 Hz is observed; between 50 Hz and 300 Hz, vibrations of up to three G's are experienced; sporadic vibrations of two G's occur between 0 and 12 Hz; between 12 Hz-125 Hz, a linear curve ranging from 2 G's to 20 G's exists; and from 125 Hz to 300 Hz, sporadic vibrations with an amplitude of 20 G's occur.

Another fact to consider is that an electronic component mounted on a PC board may experience a higher G-force than the equipment as a whole. This G-level is determined by both the resonant frequency and the amplitude of the vibration. Since the G force is directly proportional to the amplitude of the vibration, if a vibration frequency is 0.9 times the resonant frequency, the G-level the component experiences is about  $5^{1/4}$  times greater then the G-level the equipment undergoes. This is expressed by

$$M = \frac{1}{1 - (f_v/f_r)^2}$$

where M is the amplitude multiplier transmitted to the component; f, is the frequency of the incoming vibration; and f, is the resonant frequency of the circuit board. The amplitude of the vibration transmitted to the component is the product of the amplitude of the vibration frequency and the value of M. Finally, several transmissibility-type functions may cascade, creating a supershock. For example, a circuit board may be mounted in a slot in a 19-inch card rack sitting in your lab area; a truck drives by, the building vibrates; this vibrates the rack, the card cage and, finally, the circuit board. Each vibration may increase in amplitude depending upon the individual resonant frequencies of each stage.

#### **Component layout**

One of the first steps in laying out a circuit board is to decide what its size will be and how many conductive layers are needed. If the circuit is simple and requires only a few interconnections, then a small single-sided board can be designed. But if it is a complex circuit with a mass of interconnections, a larger double-sided board is needed. It should be pointed out that the larger a board becomes, the fewer the connections to the board itself, but at the expense of warping or bowing (and also a lower resonant frequency is obtained).

The method I use for determining both predefined and undefined areas is to calculate the total area that will be taken up by all the components, and then multiply by a "cheat" factor. For example, if a circuit uses ten 14-pin IC's, three 16-pin IC's, fifteen <sup>1</sup>/4-watt resistors and fourteen bypass capacitors, the following equation would result:

 $A_{c} = 10 A_{ic_{14}} + 3 A_{ic_{16}} + 15 A_{R} + 14 A_{c}$ 

A<sub>c</sub> Since,  $A_{1C14} = 0.257$  sq. in.;  $A_{1C16} = 0.264$  sq. in.,  $A_R = 0.045$  sq. in., and  $A_C = 0.060$  sq. in., then  $A_C = 4.9$  square inches. Next, multiply by the interconnecting factor (1 use a value ranging from 3 to 5, depending on circuit complexity). If yours is a complex digital circuit with a large number of interconnections, use a factor of 5. This gives an area of  $24^{1/2}$  in.<sup>2</sup>; a board that is one-half the size of an S-100 bus is required. Another method would be to use a Bishop Graphics *Puppet* design kit; this contains scaled cutouts that, by intuition and trial-and-error, can be used to develop both conductor paths and board size.

Next, choose the laminate. Then, define the copper thickness—3 oz., 2 oz., 1 oz. or  $\frac{1}{2}$  oz.—which will depend upon the current requirements. The width of the conductors also depends on the current, but is limited by the board size. Keep the conductors less than  $\frac{1}{2}$ -inch wide since large areas may cause warpage or solderblistering. If wider conductors are needed use a ground plane. If space is no problem use 0.031-inch-wide conductors for lowvoltage logic paths and 0.050-inch-wide trace for power. Make sure the conductors are spaced far enough apart to withstand the peak voltage between them; when possible, leave 0.031 inch between all traces. If narrow conductors and spaces are used, then consider the error factor in your construction process.

Lay all components out along the horizontal and vertical axes; use a grid system to place all components and holes (a 0.1-, 0.05-, or 0.025-inch grid is recommended). First, using a well-drawn schematic, make a trial layout with the same parts proximity. Next, if there are some components that must be located at some particular point on the board due to mechanical requirements or because of signal input/output, move them to the required location. The closer you can make the layout look like the schematic the better, since this generally avoids unwanted couplings. Make sure that no physical interference exists between component bodies. Now, stop and look at your layout and consider the possibility of parasitic coupling between circuit elements; add any necessary bypass-circuit capacitors or move components about to reduce these effects.

Now, consider the routing of the conductors. Remember, however, that grounding the conductors is of the highest priority. Cross-talk is most often a ground problem. Try to generate a single ground at one point.

In order to reduce unwanted feedback, keep inputs and outputs of a device far apart. Another rule is to try to make conductor routes as short and direct as possible; in order to achieve this, some leads will become longer than desired. However, with a bit of thought these problems can be solved. Don't be afraid to use a jumper (for double-sided boards as well) because sometimes this results in a better-performing circuit than when a conductor has been routed all over a board in order to obtain a free path. If there's a noisy signal line near a low-level high-impedance line, try to run a ground line between them. Any ground planes should be formed using a striped or checkered pattern of 50-mil conductor (50% of the area must be nonconductive).

Although some designers lay out the conductors in smooth graceful lines, I prefer straight lines that change direction with sharp corners—between 90 and 135 degrees. Never use less than a 90-degree angle or delamination may occur. Another important point to consider when laying out your circuit is to leave test points at key circuit locations; you will be thankful you did.

Most boards require a number of different-size holes. Never space the holes closer than a distance equal to the board thickness. Never make overlapping holes—this is a good way to break expensive drill bits. A minimum hole-pad size should be 62 mils.

Every jumper, component lead or ter-Continued on page 91

## BUILD JHIS

# Adaptive Noise Filter

Part 2—Simple to build and operate, this dynamic variable-cutoff low-pass filter can be used to remove that annoying snap, crackle and pop from your records and tape.

#### TIM SKORMOND AND GENE GARRISON

LAST MONTH WE INTRODUCED THE Adaptive Noise Filter and discussed its operation. Now, we'll see how to put one together.

#### Construction

Printed-circuit construction techniques should be followed in the assembly of the filter and the associated bar-graph display. Two suitable printed-circuit boards are used; their patterns are shown in Figs. 7 and 8. Parts are placed as shown in Figs. 9 and 10. All components are mounted on the printed-circuit board with the exception of the sensitivity potentiometer, R19, the optional switches, jacks and the power transformer. Sockets or *Molex* strips will simplify IC installation.

The front panel may be drilled and punched to accommodate the bar-graph display and printed-circuit board. Mounting holes are provided at the four corners of the PC board for this purpose. The LED's are mounted on '/4-inch centers, with the hole diameter dependent upon the individual LED's used. The three switches and the sensitivity control are mounted on the front panel and eight phono jacks, J1–J8, on the rear panel.

Figure 11 shows a wiring format for the finished unit as seen looking down into the inside of the box. Switch S1 represents the POWER switch; S2, the PRE TAPE/BYPASS switch; and S3, the POST TAPE/BYPASS switch.

The jumpers across S2 and S3 should be wired before the boards or transformer

FIG. 7—FULL-SIZE FOIL pattern for the main board in the noise filter. The circuit on top half of board is for left channel; right channel is on lower half.

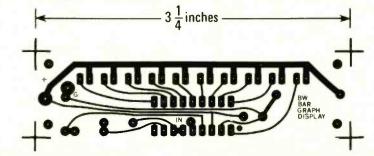


FIG. 8---THE BAR-GRAPH is made by mounting rectangular LED's in this PC board along with the IC that drives the individual elements.

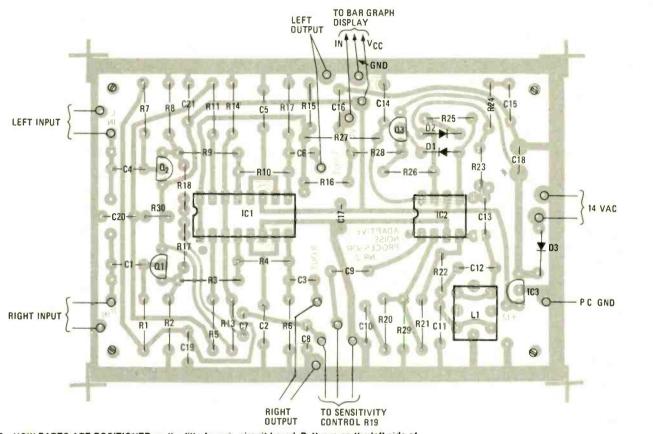


FIG. 9—HOW PARTS ARE POSITIONED on the filter's main circuit board. Patterns on the left side of board are almost mirror images because they are for right- and left-channel inputs.

are installed. These jumpers should be insulated wire but need not be shielded. The four wires to connect S2 and S3 to the PC board should be soldered to the switches and cut to length but not yet connected to the board; these wires should be shielded cable with the shield grounded at the PC board.

The eight connections to the rear-panel jacks may now be made using shielded wiring with the shields grounded at the jacks. The jacks are shown in Fig. 11. The "J" code numbers correspond to the numbers on the eight switch poles. These wires should be placed so that they will lie under the main board.

The PC boards and transformer may now be installed, and the AC line cord, fuse, power switch and transformer wiring connected. The SENSITIVITY pot is connected to the board through shielded cables with the shields grounded at the board. The three connections from the bar-graph display to the main board need not be shielded. Be sure to tie the ground for the jacks (chassis) to the board.

#### Using the filter

The Adaptive Noise Filter can now be connected in the tape monitor loop of a

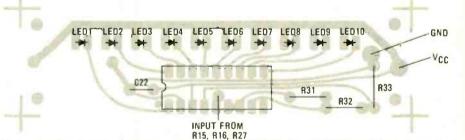


FIG. 10—COMPONENT LAYOUT for the display board. The rectangular LED's in the bar-graph protrude through a narrow slot that is cut in the front panel.

receiver or amplifier. The SENSITIVITY control, R19, should be turned down completely and the source material placed in an area with no musical content (between cuts, for instance).

All but the first LED should be off in this condition. The sensitivity control is then advanced until the next LED just begins to flicker. This is an indication that the filter is barely opening on the noise floor and is capable of reaching full bandwidth on musical information above this level. Alternatively, the control may be advanced until there is a barely perceptible increase in the noise level and then backed off very slightly.

The 19-kHz multiplex pilot tone pre-

sent in all stereo FM broadcasts is attenuated by L1 and C12. The presence of this pilot tone will limit the noise reduction capability since the noise filter will sense the level of the pilot tone rather than the level of the noise source.

The inductor provided with the kit of parts described in the parts list is pretuned and should not be altered. If, however, you purchase L1 separately, then it must be tuned to within about  $\pm 20$  Hz of the 19-kHz pilot tone. The simplest way to obtain this reference frequency is directly from the FM broadcaster. Tune your FM receiver and wait for a quiet (no audio signal) interlude. Tune L1 for minimum noise filter band-

#### PARTS LIST

All resistors 5%, 1/4 watt unless otherwise noted R1, R7-100.000 ohms R2, R6, R8, R12-3000 ohms R3, R4, R9, R10-22,000 ohms B5. B11-51.000 ohms R13-15,000 ohms R14, R26, R27-10,000 ohms R15-200,000 ohms R16-3900 ohms R17, R18-20,000 ohms R19-100,000 ohms, miniature pot, audio taper (Clarostat 389 N 100K-Z) R20, R32-3300 ohms R21-330,000 ohms R22, R25-100 ohms R23-1000 ohms R24-10 ohms R28-27 ohms R29-91,000 ohms R30-5100 ohms R31-750 ohms R32-360 ohms Capacitors C1, C4, C20-1 µF, 16 volts electrolytic, radial leads C2, C5-.0047 µF, 50 volts, Mylar, 10% C3, C6-5 µF, 10 volts, electrolytic, radial leads C7, C8-.001 µF, 50 volts, ceramic disc C9, C10-.01 µF, 50 volts, ceramic disc C11, C14, C15, C17, C21, 022-0.1 µF, 50 volts, Mylar C12-.015 µF, 50 volts, Mylar, 5% C13-.033 µF, 50 volts, Mylar C16-6.8 µF, 25 volts, tantalum, 10%, radial leads C18-470 µF, 25 volts, electrolytic, radial leads C19-10 µF, 10 volts, electrolytic, radial leads Semiconductors D1, D2-1N914 D3-1N4002 Q1, Q2, A3-2N4401 IC1-LM13600 dual operational transconductance amplifier (National) IC2-LM387N dual low-noise preamplifier (National) IC3-LM78L12CZ (National) IC4—LM3915N logarithmic bar-graph display driver (National) LED1-LED10-NSL57124 rectangular LED for bar graph (National) **Miscellaneous** S1-miniature SPST toggle switch S2, S3-miniature 4PDT toggle switch T1-power transformer, 14 VAC, 250 mA (Triad F-112X) L1-adjustable inductor, 4.7 mH, Q = 35 at 19 kHz (TOKO CLN20 740 HM) J1-J8-panel-mount RCA-type phono F1-1/4-amp slow-blow fuse Fuse holder, line cord, PC boards, control

knobs, hardware The following parts are available from Advanced Audio Systems, PO Box 24, Los Altos, CA 94022:

DX-244 (NR-2) complete kit including case—\$69.95

DX-245 (NR-2) main and display PC boards—\$19.95

DX-247 (NR-2) component kit; includes D1, D2, D3, IC1, IC2, IC3, IC4, Q1, Q2, Q3 and L1-\$27.50

California residents add state and local taxes, as applicable.


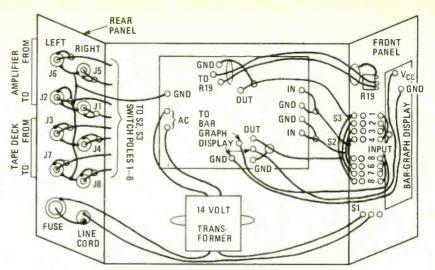


FIG. 11—WIRING LAYOUT shows connections between the main circuit board, the components on the back panel and the switches, pot and display board on the front panel.

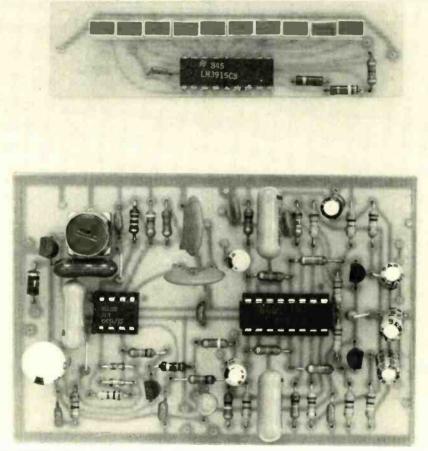

TOP VIEWS of the two circuit boards and their components. Translucent board material makes it easy to insert components in correct places and simplifies circuit tracing.

width as monitored on the LED display.

The bypass switch can be toggled between the BYPASS and FILTER positions to compare the action of the adaptive filter with that of a full system response. The difference should be quite dramatic, giving a subjective improvement in S/N of 12 to 14 dB. The action of the filter is most apparent between cuts where it removes nearly all of the annoying hiss.

You should be aware of a psychoacoustic effect that is common to all noisereduction systems. The addition of highfrequency noise (such as tape hiss) to a music signal will seem to increase the high-frequency content of the music. Thus, upon first auditioning the Adaptive Noise Filter using noisy source material, the user will seem to hear a degradation of the music's high-frequency content. The system's actual effect on the highfrequency information can be observed by using a source with a good initial S/Nand by switching the filter in and out.

It should be noted that the filter is designed for a 1-volt RMS average input level. Some tape decks are capable of much larger output levels at "0 VU" and should be attenuated accordingly to prevent overloading the filter inputs. **R-E** 

# HLELSTERED

# ANTISTATIC RECORD CARE

Electrostatic charges on phono records can be the direct and indirect causes of the "snap" and "crackle" that you hear. Here's word of an effective remedy.

#### LEN FELDMAN CONTRIBUTING HI-FI EDITOR

SOME MONTHS AGO, A REPRESENTATIVE OF a British-based company called Milty Products, Ltd., asked me if I would be willing to test a new antistatic product in my audio lab that his company had developed. The product, he claimed, would completely and permanently reduce static charges on phonograph records with a single application. While this seemed incredible to me, I agreed to perform the tests. Of course, I had no way of accurately measuring static charge on a record. The Milty representative agreed to lend me an instrument to measure electrostatic surface charge. This device is called a "field mill."

Figure 1 shows the field mill, a cleverly designed test instrument that features a motor-driven rotating blade in the front that effectively "chops up" the electrical field into a number of pulses, making it easy to measure the charge in volts-permeter or volts-per-centimeter using builtin alternating voltage detection and metering techniques.

The field mill's rear panel is equipped with a zero-centered meter, enabling the user to read both positive and negative charge voltages. In use the rotating-blade end of the device is held a few centimeters from a surface whose charge voltage is to be measured.

Since the meter is equipped with sensitivity scales  $\times 1$ ,  $\times 10$  and  $\times 100$ , fullscale maximum readings equal 10,000 volts. However, to arrive at a voltage-percentimeter reading, you must multiply the observed reading by the distance (in centimeters) from the surface being measured. Accordingly, holding the device at some 5 centimeters from the surface, you could measure charge voltages as high as 50,000!

Equipped with this field mill, I was astounded to find that in low-humidity conditions (such as are normally found in homes during the winter) merely removing a brand-new record from its protec-

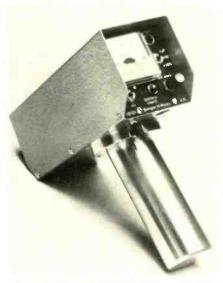


FIG. 1—FIELD MILL DEVICE measures electrostatic surface charge. Reading is in volts-percentimeter.

tive sleeve induces a charge of between 3,000 volts to 10,000 volts! The charges were found to be negative in all cases with vinyl LP records.

#### Effect of static charges

There are several undesirable effects that occur when highly charged records are played on a high-quality high-fidelity component system. When Shure Brothers, Inc. first introduced the *model V-15 Type IV* phono cartridge, we reported (Radio-Electronics, September 1978) on the unusual destaticizing and stabilizing carbon-filament brush on the cartridge, which, among other things, discharges the voltage on record surfaces. In connection with the cartridge, Shure had done a good deal of research into static voltage build-up on records.

For one thing, it was discovered that if the charge voltage exceeds a certain value, called the threshold voltage, pickups that have a grounded metal shield and a grounded stylus may cause "discharge" of the static voltage build-up, thus giving rise to crackling, popping or frying noises during playback. Such pickups were found to have threshold voltages ranging from 4000 to 5000, a voltage value that is often exceeded in dry weather on disc surfaces.

In addition, the electrostatic charge can actually increase stylus force, owing to the extra attraction of the cartridge to the record. It was found that a 4200-volt charge adds an extra <sup>3</sup>/<sub>8</sub> gram to the stylus force! This additional force can increase record wear or, at the very least, change the intended groove tracking conditions significantly.

Since the natural voltage charge on a record is not uniform over the entire surface, the added force can be cyclical in nature, causing the tracking angle of the stylus to vary cyclically with an attendant increase in apparent wow-and-flutter.

Perhaps the most serious effect created by electrostatic charges on records is that dust and dirt are attracted to the record surface, producing additional wear and playback noise.

#### Lab tests

The tests I conducted for Milty Products were not designed to prove that the company's antistatic product reduced static charges to zero. The company was perfectly capable of proving that to their own satisfaction. Rather, I was asked to investigate whether applying the antistatic product to a record surface in any way degraded the sonic or musical performance obtained *from* the record during playback.

The tests I conducted involved playing treated and untreated test records for a total of 100 plays, and measuring such specifications as harmonic distortion obtained from playback of test tones, frequency response, and any increase in background surface noise. I was able to report that with respect to any of the foregoing parameters, no deterioration of performance occurred. If anything, the treated record exhibited a somewhat lower surface noise level after 100 plays than the untreated control record.

As for the claimed permanency of the treatment, I have had the treated test record for over six months, and it still produces no electrostatic charge when pulled from its sleeve or played on a turn-table.

The Stanton Magnetics Company (101 Sunnyside Blvd., Plainview, NY 11803) recently agreed to become the American distributor for this product, which has been given the name *Permostat*. And, in a presentation, Stanton presented further dramatic evidence of the effectiveness of the antistatic compound.

Using an identical field mill to the one 1 used in my tests, Stanton confirmed that, no matter how hard you tried (including rubbing a record surface treated with *Permostat* with a silk handkerchief), no charge could be induced. Untreated records given the same test had induced charges as high as 15,000 volts.

Other antistatic devices have been available for some time, perhaps the most familiar being the so-called active ionizer, which is shaped like a pistol. Such destaticizers produce positive ions when the

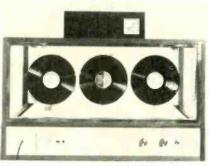


FIG. 2-DUST CHAMBER produces a dust storm that is used to demonstrate anti-static effectiveness.

trigger is pulled and negative ions when the trigger is released. As Shure Brothers had learned in earlier tests (and, as Stanton confirmed), the ion-gun is fairly effective for large charges, but it is difficult to avoid leaving residual charges of somewhat lower intensity on the record since there is no way of detecting the zero-charge condition (unless you own one of those sophisticated test instruments such as Stanton and I used in our tests). Even if the ion-gun does reduce the charge to virtually zero, the destaticized condition is temporary, and the record would have to be treated each time it is removed from its protective sleeve, and played.

To demonstrate the practical effectiveness of *Permostat*, Stanton unveiled a specially designed "dust chamber," shown in Fig. 2. Three records were suspended vertically within this chamber;



FIG. 3—PERMOSTAT LIQUID is applied directly to record surface via a hand pump.



FIG. 4—BUFFING PAD is used to evenly spread Permostat solution over record surface.

one was untreated (on the left), one was treated with an ion-gun destaticizer (center) and one was treated with *Permostat* (on the right). The method of treatment using *Permostat* is similar to applying *Sound Guard*, a record preservative. *Permostat* liquid is applied by a hand-spray pump (see Fig. 3). The fine spray is directed around the record; about 8 to 10 sprays are required to coat one side. It is essential that *both* sides of the record be treated for the *Permostat* to do its job effectively, even if only one side is to be played.

A buffing pad is then used to spread the solution evenly over the surface of the record and to remove any excess fluid. (See Fig. 4.) The dust chamber shown in Fig. 2 was equipped with electrically operated blower fans that injected simulated dust particles consisting of two oppositely charged fluorescent pigments having an average particle size of 2.5 microns to 3 microns. These particles were circulated within the test chamber parallel to the plane of the records. This created what amounted to a miniature dust storm. Once the dust had settled, the records were then examined for dust pickup.

Figure 5 clearly shows what happened to the untreated record, which previously had measured a static charge of 15,000 volts, readily attracted a considerable amount of dust. The record treated with the ion-gun registered much lower static charges but still attracted a significant amount of dust. Only the record treated with *Permostat* showed a zero static charge (as before) and picked up no dust.

Usually, leaving an untreated record exposed for a day or so in a normal envi-



FIG. 5—UNTREATED RECORD after being exposed in dust chamber.



FIG. 6—PERMOSTAT-TREATED RECORD after being exposed in dust chamber.

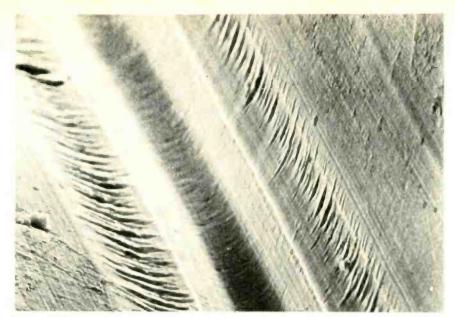


FIG. 7-SINGLE RECORD GROOVE of untreated record after 100 plays as viewed through electron microscope.

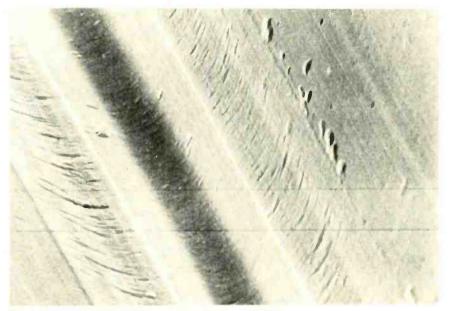


FIG. 8-PERMOSTAT-TREATED record groove after 100 plays.

ronment results in an appreciable collection of dust and debris on the disc surface. If such phonograph records are highly charged, it becomes extremely difficult to dislodge the dust. In the case of a record whose charge has been neutralized to zero volts, whatever dust does accumulate can be easily dislodged, often by merely shaking the record before playing or, at worst, by using a properly designed dry brush to lift off the nonadhering dust particles.

Figure 6 shows the Permostal treated disc, after their emergence from the dustchamber test. In the course of the demonstration conducted by Stanton, several pertinent questions were asked regarding the use of Permostat with other preparations, such as cleaning liquids and preservatives. We learned that Permostat is soluble in water. Thus, if a product such as Discwasher were used strictly as a record cleaner after a record had been

treated with Permostat, it would "wash off" the Permostat solution. The correct procedure would be to use such cleaners first and then treat the record with Permostat. The same holds true in applying record preservatives such as Sound Guard; apply them first, then apply Permostat

My earlier lab tests led me to the conclusion that applying Permostat also reduced record wear in some unknown manner. I reached these conclusions by measuring surface noise and distortion during multiple playback of treated and untreated discs. The reasons for the apparent decrease in record wear are not fully known. Obviously, if less dust is being attracted to the disc, then the stylus is less apt to grind such dust particles into record grooves with repeated playings; that, in and of itself, would reduce record groove wear. Furthermore, it is conceivable that the Permostat coating acts to


reduce overall friction between the pickup stylus and the record groove, thereby reducing record groove wear.

Regardless of the reasons, my results were directly derived from measuring playback performance of treated and untreated disc samples. Stanton's engineers were in a more advantageous position in that they own a scanning electron-beam microscope. The photo of Fig. 7 shows a highly magnified view of a single groove of an untreated record after being played 100 times with an elliptical stylus pickup using a 3-gram vertical tracking force. The serrations or breakup of the groove walls are evident. By contrast, Fig. 8, shows a magnified view of a single groove of a record that has been treated with the new product after 100 playings using the same pickup, stylus shape and vertical tracking force. While some damage to the groove is still visible, it is far less than that seen in Fig. 7. Figures 7 and 8 offer direct proof of reduced mistracking caused by the static charge.

The Permostat kit to be offered by Stanton is not inexpensive. It contains a 3-fluid-oz. bottle of fluid, a pump sprayer, a record buffing pad and record identification self-adhesive tabs so that you can identify discs that have been treated. The 3-oz. bottle of fluid is enough to treat both sides of about 25 records, 30 records if you are very careful and don't overuse the material. The complete kit carries a suggested retail price of \$19.95, with refills available for \$15.95. That amounts to about 67 cents-per-disc for the first 30 records, and 53 cents-perdisc once you start using the refills. This may seem a high price to pay for reducing static charges on records if you are a casual record collector and listener. But for many audiophiles who are fussy about their precious records and have been frustrated in their attempts to permanently de-staticize them, Permostat may be just what they have been waiting for. R-E



# REAL SOUND

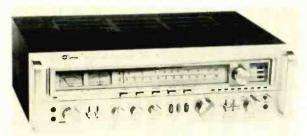

## Setton Model RS-660 Stereo Receiver

CIRCLE 106 ON FREE INFORMATION CARD

SETTON INTERNATIONAL, LTD. (60 REMINGTON Blvd., Ronkonkoma, NY 11779) is a relative newcomer to the high-fidelity field. The company's entry into the world hi-fi market has included no less than three receivers, a pair of stereo amplifiers, a separate preamplifier, a tuner, a turntable, a novel car stereo amplifier, and a three-way car speaker. The *model* RS-660 stereo receiver is their highest-powered and most expensive model.

This rugged-looking, integrated receiver, shown in Fig. 1, comes with a pair of integral carrying handles and a well-styled, threedimensional front panel with enough knobs, switches and lights to delight any controlhappy audiophile. The upper section of the panel has a softly illuminated dial area with signal-strength and center-of-channel tuning meters on the left., linearly calibrated FM and conventional AM dial scales in the center, an easy-to-grip tuning knob on the right and a "security panel" arrangement of three indicator lights that warn you when the amplifier is driven into clipping, when output circuits are overheating, or when the protection relay circuits have been activated. At turn-on, all lights illuminate briefly to show that they are working.

Centered just below the dial area are a series of oval-shaped pushbuttons for defeating the



#### MANUFACTURER'S PUBLISHED SPECIFICATIONS:

#### **FM TUNER:**

Usable Sensitivity: mono, 10.3 dBf; stereo, 18.0 dBf. 50-dB Quieting: mono, 16.0 dBf; stereo, 38 dBf. S/N Ratio: mono, 72 dB; stereo, 67 dB. Harmonic Distortion, 1 kHz: mono, 0.1%; stereo, 0.15%. Selectivity: 80 dB. Capture Ratio: 1.0 dB. IF Rejection: 95 dB. Image Rejection: 85dB. Spurious Rejection: 100 dB. Stereo Separation: 50dB at 1 kHz. Muting Threshold: 14 dBf. Subcarrier Rejection: 65 dB. Frequency Response: 30 Hz to 15 kHz, +0.5, -1.5 dB.

#### AM TUNER:

Usable Sensitivity: 25  $\mu$ V. Image Rejection: 60 dB. Selectivity: 45 dB. S/N Ratio: 45 dB. Frequency Response: -6 dB at 2.3 kHz.

#### AMPLIFIER AND CONTROL:

Power Output: 120 watts-per-channel into 8 ohms, 20 Hz to 20 kHz at 0.035% rated harmonic distortion. IM Distortion: 0.035%. Frequency Response: phono, N/A; auxiliary Inputs, 20 Hz to 20 kHz, ±0.5 dB. Damping Factor: 45. Input Sensitivity: phono, 2.5 or 5.0 mV; high level, 150 mV; mike, 6.0 mV. S/N Ratio: phono, referenced to 10 mV, "A"-weighted, 85 dB, high-sensitivity position; high level, 90 dB. Maximum Phono Input Voltage: high sensitivity, 180 mV. Bass Control Range: ± 10 dB at 62 or 125 Hz (depending upon turnover setting). Treble Control Range: ± 10 dB at 10 kHz or 20 kHz. (mid-Range: ± 6 dB at 1 kHz. Audio Muting: -20 dB. High-Cut Filter: 7 kHz or 12 kHz (-12 dB-per-octave). Low-Cut Filter: 15 Hz or 40 Hz (-12 dB-per-octave).

#### **GENERAL SPECIFICATIONS:**

Power Requirements: 110/130/220/240 volts (switchable), 50 to 60 Hz, 450 watts maximum. Dimensions:  $22.4 \text{ W} \times 6.7 \text{ H} \times 13.8$  inches D. Weight: 37 lb. Suggested Retail Price: \$879.95.



LEN FELDMAN

CONTRIBUTING HI-FI EDITOR


tone-control circuits, choosing bass or treble turnover frequencies (250 Hz or 500 Hz for the bass; 2.5 kHz or 5 kHz for the treble), selection of either the mono or the stereo mode, and selecting an external FM/Dolby circuit. An external adapter must be connected for Dolby FM decoding, but pressing the Dolby switch does introduce the required 25- $\mu$ s FM de-emphasis. To the right of these pushbuttons are a series of tiny indicator lights that denote program sources and speaker selection as well as stereo FM signal reception and activation of the Dolby FM switch. A matching power-on light is on the extreme left of the front panel.


The lower portion of the panel contains two phone jacks; a speaker selector switch (up to three sets of speakers can be connected to the model RS-660, with up to two sets operable at one time;) two high-cut and low-cut filter lever switches (each filter has two selectable cut-off frequencies); BASS, MID-RANGE and TREBLE detent-stepped tone controls; pushbuttons for FM muting, audio muting and loudness compensation; a dual concentric volume and balance control; lever switches for tape monitoring and dubbing; a program selector switch; and a stereo microphone input jack with a level control.

The rear panel of the *model RS-660*, shown in Fig 2, contains 300-ohm and 75-ohm FM/ AM antenna terminals, just below which are dual pairs of tape-output and tape-input jacks and a DIN connector for the Tape B input and output circuits. Alongside these jacks are the auxiliary (high level) and phono input jacks and a slide switch that varies phono input sensitivity to accommodate a wide variety of cartridges. The Dolby input and output jacks and preamplifier-output/main amplifier-input jacks are located near the center of the rear panel; below these jacks are the three sets of color-coded speaker terminals. The model RS-660 receiver can be used abroad thanks to a voltage selector switch located behind a cover plate and a separate power-cord receptable that can accept the different line cords required by each country. An AM-ferrite loopstick antenna and a chassis ground terminal complete the rear-panel layout. Auxiliary equipment that can be used includes three speaker systems, two tape decks and a Dolby adaptor.

#### **FM performance measurements**

Table 1 summarizes the measurements made for the FM section of the RS-660 receiver. Although harmonic distorion levels were a bit poorer than claimed at 1 kHz (the published specifications do not include figures for harmonic distortion at the other test points called for by the IHF Tuner Measurement Standards), they were nevertheless quite low and remained low at the more difficult 6-kHz test frequency, with readings of 0.12% for mono and 0.22% for stereo. What's more important, there was no evidence of "beats" when checking the recovered 6-kHz stereo waveforms. Frequency response in stereo FM is shown as the upper trace of Fig. 3, while separation is shown as the difference in dB between the upper and lower traces. Each

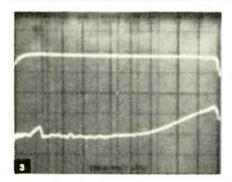

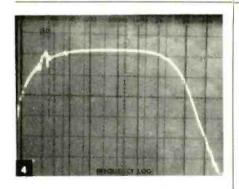

vertical division in this scope photo is equal to 10 dB.

Setton is one of the few manufacturers of stereo receivers that is willing to disclose the AM frequency response of their products. As it turns out, although the stated response range is nothing to be proud of, it was somewhat exceeded in our test sample as is shown in the response trace of Fig. 4. The -6-dB rolloff point actually turned out to be 3.0 kHz as opposed to the 2.3 kHz claimed. It should be noted that such limited frequency response range of AM is typical of most of today's stereo "high fidelity" receivers.

#### TABLE 1

#### RADIO-ELECTRONICS PRODUCT TEST REPORT


RADIO-ELECTRONICS PRODUC	T TEST REPORT	
Manufacturer: Setton International		Model: RS-660
FM PERFORMANCE MEAS	UREMENTS	
SENSITIVITY, NOISE AND FREEDOM FROM INTERFERENCE	R-E Measurement	R-E Evaluation
IHF sensitivity, mono (µV) (dBf)		
Sensitivity, stereo (µV) (dBf)		
50-dB quieting signal, mono (µV) (dBf)		
50-dB quietIng signal, stereo (µV) (dBf)		
Maximum S/N ratio, mono (dB) Maximum S/N ratio, stereo (dB)		
Capture ratio (dB)		
AM suppression (dB)		
Image rejection (dB)		
IF rejection (dB).		
Spurious rejection (dB)		
Alternate channel selectivity (dB)	81	Excellent
FIDELITY AND DISTORTION MEASUREMENTS		
Frequency response, 50 Hz to 15 kHz (±dB)		
Harmonic distortion, 1 kHz, mono (%)		
Harmonic distortion, 1 kHz, stereo (%)		
Harmonic distortion, 100 Hz, mono (%)		
Harmonic distortion, 100 Hz, stereo (%)		
Harmonic distortion, 6 kHz, stereo (%)		
Distortion at 50-dB quieting, mono (%).		
Distortion at 50-dB quieting, stereo (%).		
STEREO PERFORMANCE MEASUREMENTS		
Stereo threshold ( $\mu$ V) (dBf)	2.5 (13.2)	Superb
Separation, 1 kHz (dB)		
Separation, 100 Hz (dB)		
Separation, 10 kHz (dB)	30	Very good
MISCELLANEOUS MEASUREMENTS		
Muting threshold (µV) (dBf).	2.5 (13.2)	Excellent
Dial calibration accuracy (±kHz at MHz)	Perfect	Superb
EVALUATION OF CONTROLS, DESIGN AND CONSTRUCTION		
Control layout		
Ease of tuning		
Accuracy of meters or other tuning aids		
Usefulness of other controls		
Ease of servicing		
Evaluation of extra features, if any		
OVERALL FM PERFORMANCE RATING		
UVERALL FM PERFURMANCE KATING		very good

#### **Amplifier measurements**

Results of our amplifier measurements are summarized in Table 2. In general, the power amplifier circuitry exceeded published specifications by a wide margin and might well have been rated at 130 watts-per-channel for its rated harmonic distortion of 0.035%. At its presently rated output of 120 watts-per-channel, mid-frequency harmonic distortion was a very low 0.01% while IM distortion was almost as low, with readings of 0.027%. Dynamic Headroom (per the new IHF Amplifier Measurement Standards) was on the high side, with readings of 1.8 dB. This means that with short-term burst input signals, the amplifier can be expected to reproduce peaks of 180.0 watts without undergoing clipping.

Signal-to-noise and sensitivity measurements shown in Table 2 are in accordance with the new IHF Amplifier Measurement Standards, and will therefore not correlate with this manufacturer's published specifications. The measurements should therefore be judged on their own merits and should be compared with similarly obtained figures for competitive products.


Figure 5 depicts the range of the BASS and TREBLE tone controls when each is set to either of its available turnover frequency points. The availability of these alternate turnover settings

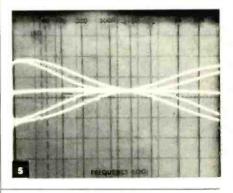



clearly provides increased tone control flexibility that is further augmented by the MID-range tone control whose maximum boost and cut range is shown in the scope photo of Fig. 6.

Figure 7 shows the response of the low-cut and high-cut filters. All slopes are at 12-dBper-octave as claimed. The scope display does not show the subsonic filter characteristic simply because our frequency sweep on this display extends only from 20 Hz to 20 kHz, whereas the subsonic filter cuts off at 15 kHz. Separate testing disclosed that it, was accurately designed and provides the same 12 dBper-octave slope below 15 Hz.

Figure 8 is a plot of the action of the loudness compensation circuitry, taken at various settings of the master volume control. Action begins at around 30 dB below the maximum

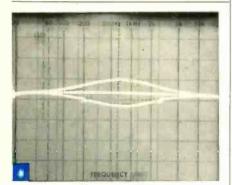

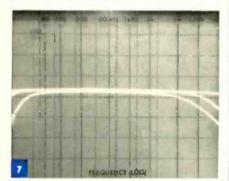

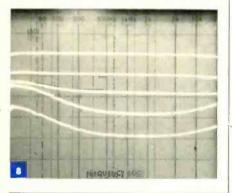

setting of the volume control and consists primarily of bass boost at that level. At lower settings of the volume control (-40 dB and)-50 dB), treble boost is also incorporated, though more moderately than the bass boost.

#### Summary

Table 3 provides an overall product evaluation of this high-powered receiver from Setton International, as well as our summary comments regarding its performance and ease of use. The RS-660 is, above all else, an extremely flexible and well-thought-out receiver that delivers enough clean power for just about any home high-fidelity requirements. Although phisically large, its depth has been kept reasonably short, permitting it to be used on a shelf as well as a table top-something that many highpowered receiver manufacturers seem to ignore these days. For its power output, control features, performance level and overall flexibility, the receiver seems to us to be fairly priced, and its features surpass those of many similarly priced receivers, not to mention separate components costing much more. R-E

#### TABLE 2

#### **RADIO-ELECTRONICS PRODUCT TEST REPORT**

#### Manufacturer: Setton International

AMPLIFIER PERFORMANCE MEASUREMENTS

Model: BS-660

Model: RS-660

	R-E	R-E
POWER OUTPUT CAPABILITY	Measurement	Evaluation
RMS power/channel, 8-ohms, 1 kHz (watts)	140.3	Excellent
RMS power/channel, 8-ohms, 20 Hz (watts)		
RMS power/channel, 8-ohms, 20 kHz (watts)		
RMS power/channel, 4-ohms, 1 kHz (watts)	N/A	
RMS power/channel, 4-ohms, 20 Hz (watts)	N/A	
RMS power/channel, 4-ohms, 20 kHz (watts)	N/A	N/A
Frequency limits for rated output (Hz-kHz)		
Dynamic Headroom (dB)	1.8	Excellent
DISTORTION MEASUREMENTS		
Harmonic distortion at rated output, 1 kHz (%)	0.01	Superb
Intermodulation distortion, rated output (%)		
Harmonic distortion at 1-watt output, 1 kHz (%)	0.0045	Superb
Intermodulation distortion at 1-watt output (%)	0.08	Very good
DAMPING FACTOR AT 8 OHMS, 50 Hz	44	Good
and the second		
PHONO PREAMPLIFIER MEASUREMENTS		
Frequency respons (RIAA ± dB).	+0.1 -0.8	Good
Maximum input before overload (mV) Hum/noise, "A" -weighted, referenced to 1W or 0.5V output,	160	Very good
for 5-mV input (dB)	77	Exections
		Excellent
HIGH LEVEL INPUT MEASUREMENTS		
Frequency response (Hz-kHz, ± dB)	. 8.5-94, 3.0	Superb
Hum/noise "A" -wt'd, re: 0.5 or 1W out, 0.5V in (dB)		Very good
Residual noise, "A" -wt'd, minimum volume, re 1W out (dB)		Good
TONAL COMPENSATION MEASUREMENTS		
Action of bass and treble'controls	See Fig. 5	Excellent
Action of secondary tone controls		
Action of high- and low-frequency filters	See Fig.7	Excellent
COMPONENT MATCHING MEASUREMENTS		
Input sensitivity, phono 1/phono 2, re: 1W or 0.5V out (mV)	0 22/0 44	Good
Input sensitivity, high level, re: 1W or 0.5V out (mV)		
Output level, tape outputs, at rated output (mV)		
Output level, headphone jack, at rated output (mV or mW)	90 mW	Good
EVALUATION OF CONTROLS.		
CONSTRUCTION AND DESIGN		
Adequacy of program source and monitor switching		Exections
Adequacy of input facilities		
Front panel layout		
Action of controls and switches		
Design and construction		
Ease of servicing.		
OVERALL AMPLIFIER PERFORMANCE RATING	·····	Excellent

#### TABLE 3

#### **RADIO-ELECTRONICS PRODUCT TEST REPORT**

Manufacturer: Setton International

#### **OVERALL PRODUCT ANALYSIS**

Retail price	\$879.95
Price category	High
Price/performance ratio	
Styling and appearance	Very good
Sound quality	Excellent
Mechanical performance	Excellent

Comments: The model RS-660 was obviously designed for the stereo receiver user who desires all of the flexibility of "separates" but has limited installation space and cannot afford the \$1200 to \$1500 that might have to be expended to acquire a separate amp and tuner having equal power capability and features. Not that the RS-660 is in any way miniaturized or compact. It is, very deliberately, a large unit for its rated power output, constructed in an extremely rugged manner, with careful attention paid to a logical layout of the front-panel controls, internal circuit board layout and long-term reliability. Individual components are top-grade. Intermodule wiring is kept to a minimum, and most of the potentiometers and switches on the front panel are directly mounted to their respective circuit boards. The three-way "security" light panel on the face of the receiver is a novel Idea that lets the user know that all is well with the internal circuits and even indicates when the amplifier is being driven into clipping levels

This conservatively rated 120-watt-per-channel receiver is not likely to go into clipping, however, even when driving relatively inefficient speaker systems such as those we used in our extended listening tests of the unit. The amplifier's performance is truly awesome, with reproduced sound extremely transparent and devoid of any audible transient intermodulation distortion, noise or other unwanted sonic coloration. The tuner section, while not quite as "state-of-the-art" as the amplifier and control sections, was nevertheless of high enough quality so that most of our FM listening evaluations were limited by the quality of broadcast signals rather than by any limitations of the tuner circultry itself.

ELEWSION

# Quickie Exercise Course in VCR Video

Although the results are similar, the video signal in the Beta and VHS systems is handled quite differently. Here's a look at the recording and playback video circuitry of these two systems.

#### FOREST BELT

YOU PROBABLY DO NOT NEED A lengthy discourse about television electronics. But VCR electronics does deserve some attention. Video may be video; yet it's not handled the same in video cassette recorders as in TV receivers.

The two popular video cassette formats—VHS and Beta—bear strong similarities, at least in their video. A brief familiarization should carry you through the video electronics in either kind of machine. You will see briefly how a color VCR processes luminance and chrominance signals in preparation for laying them down magnetically on a video tape. None of these processes are really very complicated.

You will note a considerable difference between how chroma is handled and how luminance is handled. They are treated separately, as individual functions, each in its own circuitry.

Chrominance, as it accompanies regular composite video, actually consists of various-phased 3.579545-MHz sidebands signals. For reasons we needn't go into here, it is impractical in video recording to keep the chroma at that frequency.

So conversion stages beat these sidebands down to much lower frequencies. In VHS machines, chroma ends up as 629.36-kHz sidebands. That's the frequency of the color signal that goes to the recording head and is impressed magnetically upon the tape. In Beta systems, conversion brings the chroma sidebands down to 688.362 kHz. In that form, chroma signals are impressed on the tape.

Luminance is handled differently—yet virtually alike in both machine formats. Composite video, minus color information, goes through a certain amount of frequency equalization. This is followed by clipping that prevents sync tips from reaching too far "black" and video from going toward "white" enough to compress or to overmodulate.

Video and sync then frequencymodulate an FM oscillator. The center frequency of the "luminance" oscillator is chosen so that, in VHS equipment, negative-going sync tips swing the frequency down to 3.4 MHz, while maximum video white raises it to 4.4 MHz. Beta systems permit a slightly greater modulation swing—from 3.5 MHz to 4.8 MHz.

These signal-handling techniques are called "color under." Summing them up: chrominance information goes on the tape as sidebands at 629 kHz or 688 kHz, depending on the VCR's format. Black-and-white video and sync are frequency-modulated, centered at a frequency of around 4 MHz. The exact frequency swing for 100% video modulation depends on the format.

In case you've been wondering, TV sound is not involved in either of these two processes. Sound is brought into the recorder electronics separately, is handled by itself, and then is recorded as one narrow track along the top of the tape. In all these respects, a VCR handles sound just like any audio cassette recorder.

The bottom of the video tape has another narrow track, used to record control pulses. These control signals operate the synchronizing and servo systems during playback.

#### Beta recording sections

The block diagram of Fig. 1 shows the major sections in a Beta format VCR that deal with luminance, sync and chrominance signals during the Record function. Some very complicated stages and circuits make up these sections. But the interrelationships among the sections are fairly simple.

Sections make a good level at which to start understanding a VCR. With a little study, you should be able to commit this entire diagram to memory. Doing so will greatly speed your thought processes later when you begin troubleshooting or diagnosing electronic malfunctions.

Composite video input signal comes from either a color camera (a monochrome camera omits chrominance) or from a video detector in the tuner/IF section of the VCR. (All consumer VCR's now have tuners and IF stages.)

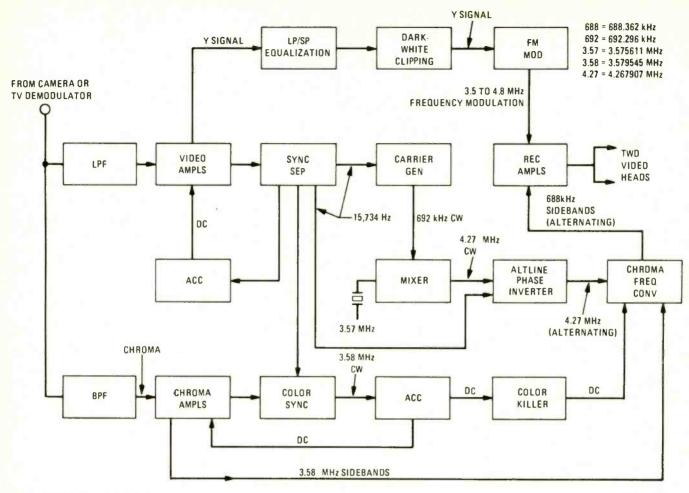


FIG. 1-BETA recording function

A bandpass filter separates out all 3.58-MHz burst and sideband signals and sends them to chroma amplifiers. A lowpass filter blocks the chroma, and sends video and sync signals to the video ampifiers.

Follow the video or luminance signal first since it is the simplest. Video from the video amplifier section goes through some equalization to prepare it for either standard-speed or long-play recording. In two-speed Beta format, this is the 1-hour/2-hour switch. (Long play, with a new 750-foot cassette, now gives 3 hours of Beta recording and playback time.)

A clipping section prevents sync from reaching too far black or the video from going too far white. This leveled luminance signal feeds an FM modulator. The 3.5- to 4.8-MHz FM signal goes to the recording amplifiers and from there to the video recording heads.

The signal back at the video amplifier section also goes to a sunc separator. Horizontal sync tips are used in an AGC system that controls gain in the video amplifiers.

The sync separator supplies 15,734-Hz signals to several other sections in the VCR. Instead of dealing with these sections at this point, save your study of each until you see its purpose. For now, just go back and follow what happens to the

3.58-MHz-chrominance (chroma) sidebands and burst signals.

A bandpass filter separates the color signals from the incoming composite signal and feeds them to a chrominance amplifier section. A color sync section recovers the burst. Horizontal sync from the sync separator gates this section only during the burst portion of the chroma signal. The 3.58-MHz burst thus separated out tightly controls a color oscillator inside the section. A phaselocked 3.58-MHz continous-wave (CW) signal feeds the automatic color control (ACC) section.

A DC voltage goes back from the ACC section to level out the gain of the chroma amplifiers. The ACC also puts out a sensing voltage to the color-killer section. The killer lets a frequency converter operate-or, in absence of a color signal, not operate.

Meanwhile, the chroma amplifier section amplifies 3.58-MHz sidebands. It then feeds them to the chroma frequency converter. There the color sidebands convert to sidebands of a 688-kHz signal.


To understand how this conversion occurs, you must go back to another group of sections. A carrier generator section takes a sample 15,734-Hz sync signal. Inside the carrier section, a control loop phase-locks a VCO at exactly 44 times the horizontal sync frequency. The output of this section is a signal tightly held at 692.296 kHz.

Next, this CW signal mixes with a crystal-controlled 3.575611-MHz signal in a mixer section. The additive heterodyne of the two makes 4.267907-MHz signal that also is CW (no modulation)

Meanwhile, another part of the signal from the sync separator triggers an alternate-line phase inverter. The entire function of this inverter section is to reverse the phase of the CW signal at intervals that correspond to every alternate horizontal line. The purpose lies in the way chroma signal must be laid down on the tape. Lines fit very closely together. The phase of chroma information is reversed for each line as it is laid down on the tape. This counters crosstalk between adjacent lines.

The inverter section alternately reverses the phase of the 4.27-MHz CW signal that is fed through it. This signal mixes subtractively with the 3.58-MHz chroma sidebands in the chroma frequency converter. In exact megahertz, 4.267907 minus 3.579545 equals 0.688362. The result, therefore, is 688.362-kHz sidebands reversed in phase for every alternate horizontal line.

This 688-kHz color sideband signal

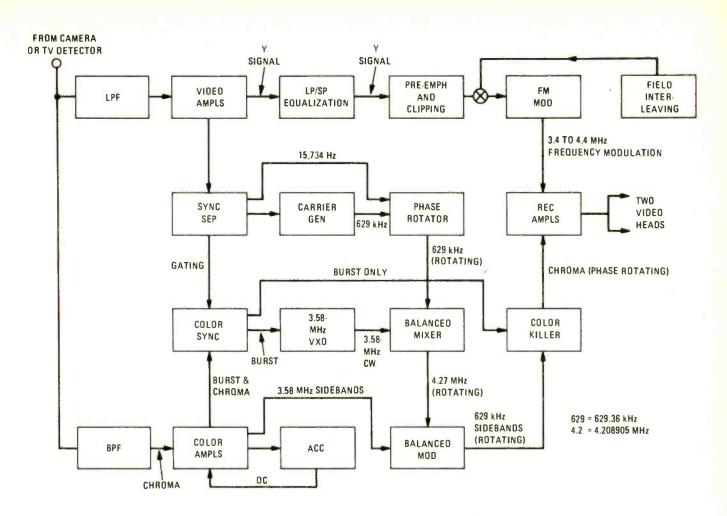

#### FIG. 2-VHS recording function

then goes to the recording amplifiers that matrix the FM signal and the 688-kHz sideband signal (this is linear mixing, with no heterodyning). The two recording heads lay both signals down on the tape.

This doesn't seem too complicated, does it? It really isn't, at this level of analysis. And this is the level at which you ordinarily begin your troubleshooting diagnosis.

#### **VHS** recording function

A VHS video cassette recorder uses similar electronics for recording. Figure 2 is the block diagram of the sections involved; you can just follow the analysis on this diagram.

A low-pass filter separates out the luminance or Y signal, and feeds it through a video amplifier section. Then, long-play/standard-play (2-hour/4hour) equalization is added, some preemphasis and the usual black/white clipping.

The only real difference in the luminance processing comes with the *field interleaving* that occurs before the video goes to the FM modulator. This locks the start of video in each field to the head/servo system. The frequencymodulated luminance signal proceeds through the amplifiers to the two video recording heads. A sync separator right after the video amplifiers does essentially the same thing as in a Beta-format tape deck. That is, it supplies gating and control pulses for other sections.

Chroma, pulled out by a bandpass filter, goes to a color amplifier section, where an ACC section controls the gain.

A color sync section uses horizontalrate gating from the sync separator to lift out the burst signal. Color sync controls a 3.58-MHz (actually, 3.579545-MHz) variable crystal oscillator (VXO). A colorburst-locked CW signal enters a balanced mixer.

Meanwhile, in a carrier generator section, a sync separator signal serves as reference to phase-lock a 2.51744-MHz VCO. A 4:1 down-counter divides the VCO signal. Output of the carrier generator therefore is 629.36 kHz, a CW signal that feeds a phase rotator.

Phase rotation accomplishes the same end as the alternate-line inverter does in the system described earlier—it reduces crosstalk. A unique phase-shifting system, slaved to the 15,734-Hz sync signal, rotates the vector (phase) of the 629-kHz CW signal. Coinciding with the start of each line, the CW signal phase rotates 90 degrees. At the next line-start time, the phase rotates again, and so forth.

At the start of each TV field, a phase

shifter also inverts the phase of the 629-kHz signal. This phase-switched signal goes to the balanced mixer to heterodyne with the color-burst-synchronized signal from the VXO. These signals together create an alternate-line-rotated and alternate-field-reversed CW signal at 4 208905 MHz.

This 4.2-MHz signal takes on the same phase-switched characteristics as the 629-kHz signal. The 4.2-MHz signal now goes to a balanced modulator. There it is modulated by the 3.58-MHz chroma sidebands. The result is the difference heterodyne: 4.208905 MHz minus 3.479545 MHz equals 629.36-kHz sidebands. In other words, the chroma signal has become 629.36-kHz sidebands, with the phase-rotating characteristics carried from the phase rotator/switcher.

This signal goes to the recording amplifiers and from there to the video heads. The color signals are laid down on the tape, oriented according to the phase conditions instituted by the signals. Video goes onto the tape simultaneously, but remember it is an FM signal that is confined between 3.4 MHz and 4.4 MHz.

#### Beta playback functions

Keeping in mind what happens to the signal during recording helps you know

what to expect during playback. Figure 3 shows the playback sections involved in a Beta-format machine. Try to memorize the signal-handling sequence:

The two spinning video heads pick up signals from the diagonal magnetic tracks on the video tape. Timing and positioning of the two heads is taken care of precisely by the control track and by the tape deck's servoelectronics. The heads pick up signals in a precisely synchronized pattern.

First, let's consider recovery of the luminance signal. The 3.5- to 4.8-MHz FM signal comes from the head amplifiers to a section called the *dropout compensator*. Slight oxide flaws in the tape cause specks to be seen during video playback. The compensator senses the dropped-out video and replaces the emptiness with whatever signal just precedes that spot on the line. The result is a more solid picture.

Next, the FM signal is demodulated. Recovered luminance video runs through de-emphasis according to the tape speed that the control track sets the machine to playing. Finally, the luminance (Y signal) goes to a Y-C matrix where it rejoins recovered chroma.

Before you get to the chroma recovery stage, note that the luminance signal at the Y-C matrix also goes to a sync separator section. The horizontal sync that accompanies the video is needed to control a number of color-recovery stages.

For example, it feeds horizontal sync pulses to the same carrier generator section used for recording. As you recall, the output is a steady 692.296 kHz (this is 44 times the horizontal sync frequency). The CW signal goes to a mixer.



RCA MODEL VCT400


Meanwhile, the sync separator also feeds a signal to a color-sync automatic phase control (APC) section. The output


of the APC section, a 3.579545-MHz signal that is phase-locked to the burst signal from the chroma amplifiers, goes to the mixer.

In the mixer, the 692.296-kHz signal and the 3.579545-MHz signal heterodyne to form a 4.271841-MHz signal. This CW signal goes through an alternate-line phase inverter that is also controlled by the sync separator. The signal phase reverses during the time of every other line. This alternate-linereversed 4.27-MHz signal is then fed to a frequency-conversion mixer. The same converter receives the 688-kHz colorsideband signal from the head amplifiers.

Remember that the 688-kHz signal was recorded in such a way that alternate lines are in opposite phase on the tape. Therefore, 688-kHz sidebands played back to the conversion mixer change phase every other line. Feeding an alternate-line-inverted 4.27-MHz signal to the frequency converter counters this. The 3.58-MHz signal heterodyned from the converter thus regains its original form. Going to the chroma amplifier are the original 3.58-MHz chroma sidebands.

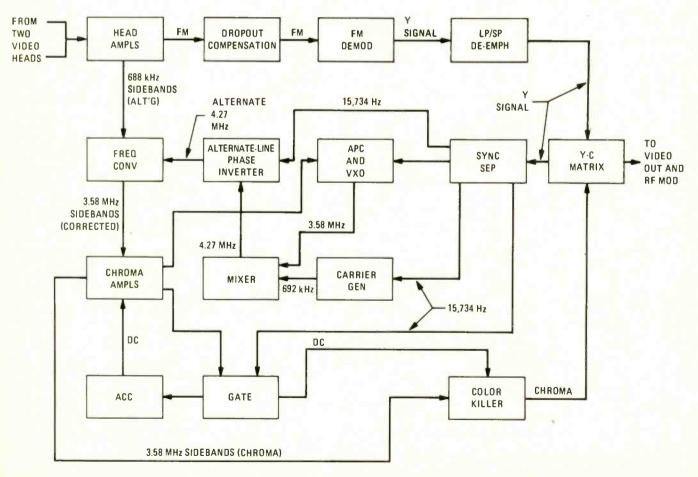Any jitter in the chroma signal appears also in burst signals that go to the APC section. An inverse jitter finds its way from the APC section to the frequency converter. This counteracts any tendency



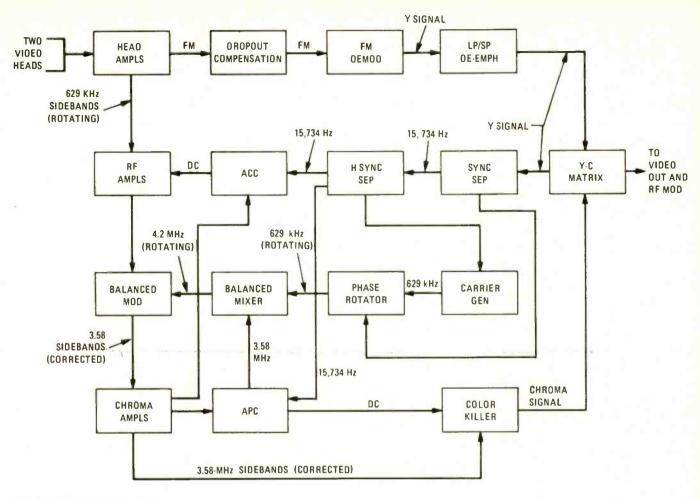

#### FIG. 4-VHS playback function

for the picture to jitter.

The sync separator also provides the gate signal to recover the burst from the chroma signal. One direction sends a burst signal to the automatic color control, just as in a TV receiver. Another direction opens the color-killer stage when color is present. This allows the chroma signal to reach the Y-C or luminance-chroma matrix. Of course, when no color burst is present, the killer blocks noise originating in the chroma amplifiers. The Y-C mixer feeds the video output jack and the RF modulator (for a TV set monitor).

The important thing to recognize here is that Playback processes the color and video signals virtually in mirror to the way they were processed when recording the tape. As soon as you recognize this fact, you can commit the whole record/playback system to memory.

#### **VHS playback sections**

Figure 4 shows a virtual reversal of the signal processing that took place during the VHS Record function.

Signals from the two video heads drive the playback amplifiers. The frequencymodulated Y signal and sync pass through a dropout compensator and demodulator. Video then finds deemphasis on its way to the Y- combiner. Video also goes to a sync separator. Meanwhile, the chroma, in the form of 629-kHz sideband signals, arrives at a balanced modulator whose job is to "modulate" a heterodyne with these sidebands.



SONY MODEL SL-5400

Horizontal sync, taken from Y video, controls a phase-rotation section that reverses the rotation applied during Record. The phase-corrected 629-kHz signal goes to a balanced mixer, along with a 3.58-MHz signal that has been locked by color burst in the APC (Automatic Phase Control) section. The sum of these signals forms a phasecorrecting 4.2-MHz signal. It is fed to the balanced modulator to mix with the phase-rotating 629-kHz chroma sideband signals coming from the tape through the head amplifiers.

Without the correcting rotation of the 4.2-MHz CW signal, color sidebands from the balanced modulator would contain the recorded phase rotation. But, as

it's processed here, the output of the balanced modulator consists of the phase-corrected original 3.58-MHz color-sideband signals.

This goes through chroma amplifiers. Some signal from the chroma amplifiers is fed back to an ACC section that is keyed by the horizontal sync separator. A DC voltage proportional to the burst-signal amplitude controls the gain in the 629-kHz RF section.

The chroma signal from the chroma amplifiers goes through a color-killer stage to the Y-C matrix—if the color killer doesn't block it. The color-killer section, operated from the APC, is open when the color burst is present. When the color burst is not present, the killer blocks noise coming from any of the chroma amplifier circuitry.

And, of course, the Y-C matrix sends color and luminance plus sync to the video-output jack or to the RF modulator in the tape deck.

Learning to understand and troubleshoot record and playback electronics of a VCR probably is the least of your worries with video cassette recorders. There are other functions that are more difficult to understand. They will be the subject of future "What You Need to Know" sections in **Radio-Electronics**. Watch for them in future issues. **R-E** 

# DIGITAI

# Prom. Programming

Programmable-read-only-memories can perform many logic functions and at the same time reduce circuit complexity. The key to using a PROM, however, is the ability to program it.

A read-only memory (ROM) is a random access memory in which data is mask-programmed during the manufacturing process. A programmable ROM, or PROM, is also a read-only memory; however, memory patterns are programmed into it by the user after manufacture. Read-only memories act as code converters that accept input codes and generate arbitrarily assigned output patterns. They are logically equivalent to truth tables in which the number of input variables equals the number of ROM address inputs and the number of output functions equals the number of ROM outputs. For example, an 8K PROM organized as 1024 x 8 bits implements the truth table for eight functions of ten variables.

Techniques for programming PROMs differ according to the technologies used to implement the devices. Certain types of MOS PROMS (EPROMs) can be erased and reprogrammed, but bipolar TTL PROMs can be programmed only once. In either case, the user can custom-program PROMs and, when necessary, make system changes without facing the substantial mask charges, manufacturing turn-around time, and need to maintain inventories of different patterns that are required by ROMs.

Bipolar TTL PROMs offer access times in the 25 ns to 50 ns range and ECL devices are available with access times in the 10 ns to 20 ns range, while MOS is slower than either type. Although MOS has historically been available in larger bit configurations than bipolar, advances in bipolar memory technology are narrowing the gap. Isoplanar Schottky PROMs, for example, offer densities between those of PMOS



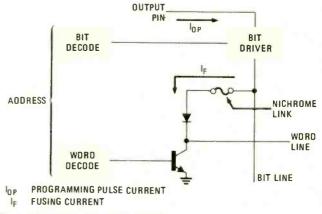


Fig. 1 Programming Current Path

and silicon-gate NMOS. They are also cost- and performance-competitive not only with ROMs, but also with standard TTL on a per-function basis.

Isoplanar Schottky PROMs in various sizes and configurations are available from Fairchild, with high performance guaranteed across both commercial and military temperature ranges. These devices include the 93417/93427 256 x 4bit, the 93436/93446 512 x 4-bit, the 93438/93448 512 x 8-bit, the 93452/93453 1024 x 4-bit, and the 93450/93451 1024 x 8bit PROMs. They are completely TTL compatible, include fully decoded addressing, and are available with open-collector or 3-state outputs. A 256 x 4-bit Isoplanar ECL PROM with a typical access time of 11 ns is also available.

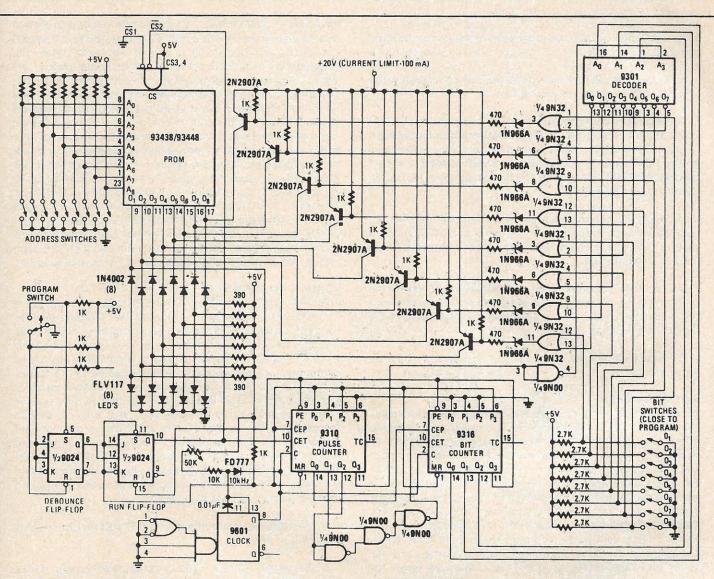


Fig. 2 PROM Programming Circuit

#### APPLICATIONS

Programmable ROMs are widely used today in microprogrammed computers ranging from the largest mainframe systems to microcomputers. They are also finding increased use as replacements for random logic in peripheral controllers, digital controllers, instruments, and terminals. Circuit applications include fixed data and instruction storage in computers, microprogrammed system control storage, lookup and decision tables, and address and priority mapping. Other applications include character/vector generation, encoding/decoding and sequential controllers. Many of these functions will, in time, be performed by field-programmable logic arrays (FPLAs); because of their large memory capabilities, however, PROMs will remain important elements in mass storage applications.

#### **PROGRAMMING TECHNIQUE**

The basic technique for programming a PROM having fusible links is to provide the amount of current necessary to permanently open the link associated with a selected bit, thereby programming the bit to a logic "0" or a logic "1", depending upon the circuit design. Several materials are used to provide the programmable links within bipolar PROMs, including nichrome, tungsten, titanium, and doped polysilicon. The nichrome fuse link is the most popular because of extensive past experience with this material, high programming yield, and reliability. In Fairchild PROMs, the fuse is a thin-film nichrome link with a small, square notch that concentrates the fusing energy in a central neck during programming, ensuring a wide, clean gap.

#### Fairchild Isoplanar Schottky TTL PROMs are manufactured with all bits in the HIGH, or logic "1", state. When a programming current pulse (IoP) is applied to an output pin, fusing current (IF) is driven through the selected bit, as shown in *Figure 1*. Because of careful device design, almost all of the fusing energy is delivered to the nichrome link, opening the link and programming the bit to a LOW, or logic "0", state. Minimal losses to leakage paths and intermediate circuits permit the link to open rapidly with a low-energy pulse, which improves reliability. The nichrome links actually program on the rise time of the pulse; this permits the reduction of programming pulse width for high-speed, low-energy device programming. *Table 1* gives programming specifications for Fairchild PROMs.

#### **PROGRAMMING PROCEDURE**

The following steps, performed with reference to Table 1, can be used to program one bit at a time:

1. Apply the proper power by supplying  $V_{CC} = +5$  V and ground.

2. Select the word to be programmed by applying the appropriate levels to the Address pins.

3. Select the chip for programming by disabling the outputs: apply a HIGH to the active LOW Chip Select inputs and a LOW to the active HIGH inputs, if present. All PROMs have active LOW Chip Select inputs; the 93438/93448 512 x 8-bit and 93450/93451 1024 x 8-bit PROMs have active HIGH Chip Select inputs as well.

4. Apply a programming pulse to the output pin associated with the bit to be programmed. The other outputs may be left open or tied to any HIGH. Note that only one output at a time can be programmed.

5. To verify a LOW in the bit just programmed, remove the pulse from the output pin and sense the pin after applying a LOW to the active LOW Chip Selects and a HIGH to the active HIGH Chip Selects, if any.

6. Repeat steps 2 through 5 as necessary for each bit to be programmed.

#### PROGRAMMERS

Most PROM programming is done with commercially available programmers. An alternative is simpler programmers with manual switches; for example, the circuit shown in *Figure 2*, designed for PROMs having eight outputs, is capable of sequentially programming all bits in words of up to 8bit length. The address of the word to be programmed is entered by the address switches, and the desired bit pattern for that word is set up on the bit switches. The contents of the PROM at the selected address are displayed on the eight FLV117 LEDs as long as the program switch is open. When the program switch is open, the PROM is enabled and, for every bit in the HIGH state, the associated LED is of; for every bit in the LOW state, the associated LED is off. Closing the program switch disables the chip and all of the LEDs are simultaneously turned on by current supplied through the 390  $\Omega$  resistors. The 1N4002 diodes isolate the LEDs from the 21 V programming pulse.

One-half of a 9024 dual JK flip-flop is used as a switch debouncer, while the other half is the run flip-flop. The 9601 one-shot is connected as a 10 kHz oscillator. When the program is initiated by closing the program switch, the switch debouncer sets; this clocks the other half of the flipflop into the run state and enables the pulse and bit counters to initiate programming pulses, preparing the PROM for programming. The pulse counter is preset to 5 to provide the requisite 20% duty factor, and the bit counter is preset to 8. To avoid overlap problems between the programming pulse, chip enable and scan, the bit counter advances when the pulse counter goes from state 3 to state 4. The bit to be programmed is decoded by the 9301 and wired-OR with the bit switch. The OR gate is a high-voltage driver that supplies the drive to the programming transistors upon selection by a closed bit switch. When the last bit has been programmed, the counter presets itself and resets the run flip-flop, completing the programming sequence for the selected word.

#### **BOARD PROGRAMMING**

It is often convenient to program PROMs mounted on a circuit board in wired-OR configurations. Fairchild devices are particularly convenient for board programming because only the Chip Select and output pins need to be accessed to program the part. *Figure 3* shows a circuit used for board programming. The programmer is connected to the output bus as shown and the Chip Selects are driven by a decoder with elevated voltage levels. Thus, all that is required for board programming is to raise VCC. VEE, and the Device Select inputs on the decoder to 7.6 V above their normal operating levels. The standard 21 V programming pulse then programs bits in the PROM having an active LOW Chip Select input of approximately 7.8 V, which is high enough to disable the PROM outputs. The following steps are used to program board-mounted PROMs with this circuit:

1. Connect the common output bus of PROMs 0 through n as shown in *Figure 3*.

2. On 93417, 93438, 93450, 93451, 93452, and 93453 PROMs, connect either  $\overline{CS}_1$  or  $\overline{CS}_2$  to 0 V. Connect the other active LOW Chip Select inputs to the active LOW outputs of the TTL decoder.

PARAMETER	SYMBOL	MIN	RECOMMENDED VALUE	MAX	UNITS	COMMENTS	
Power Supply Voltage	Vcc	4.75	5.0	5.25	V	Company and a set of the set of t	
Address Input	ViH	2.4	5.0	5.0	V	Do not leave inputs open	
Address input	VIL	0	0 99	0.4	V		
Chip Select	CS1. CS2	2.4	5.0	5.0	V		
omp select	CS3, CS4	0	0	0.4	V	Either or both	
Programming Pulse Voltage	VOP	20	21	21	V	Applied to output to be programmed	
Programming Pulse Current	IOP		1078	100	mA	If pulse generator is used, set current limit to this max value.	
Programming Pulse Width	tpw	0.05	0.18	50	ms		
Programming Pulse Duty Cycle			20	20	%	Maximum duty cycle to maintain t <sub>c</sub> < 85°C	
Programming Pulse Rise Time	tr	0.5	1.0	3.0	μS		
Number of Required Pulses		1	18 States	4		<b>网络马尔马尔东南部</b> 省中国马尔马马	
Case Temperature		Sec. Sec.	25	85	°C	a dina sina sana wakata ku ku ku	

3. On 93436 and 93446 PROMs, connect the Chip Select inputs to the TTL decoder outputs.

4. On 93438, 93448, 93450 and 93451 PROMs, connect the CS3 and CS4 inputs to a HIGH or leave them unconnected.


5. To program a bit in one of the PROMs, simultaneously raise the TTL decoder supply voltages to  $V_{CC} = 12.6$  V and  $V_{EE} = 7.6$  V and select the desired PROM via the TTL decoder Address inputs (HIGH = 10.0 V, LOW = 7.6 V).

6. Close the bit switch associated with the bit to be programmed and raise the programming pulse voltage to 21 V. The selected PROM, the active LOW Chip Select input of which is at approximately 7.8 V, programs. The active LOW Chip Select inputs of all other PROMs are at approximately 10.6 V; these PROMs remain deselected, and do not program.

7. To verify a LOW in the bit just programmed, remove the programming pulse and sense the PROM output bus after simultaneously lowering the TTL decoder supply voltages to  $V_{CC} = 5.0$  V and  $V_{EE} = 0$  V and lowering the TTL decoder Address inputs to their normal levels (HIGH = 2.4 V, LOW = 0.4 V).

8. Repeat the procedure for other bits, following the normal programming sequence.

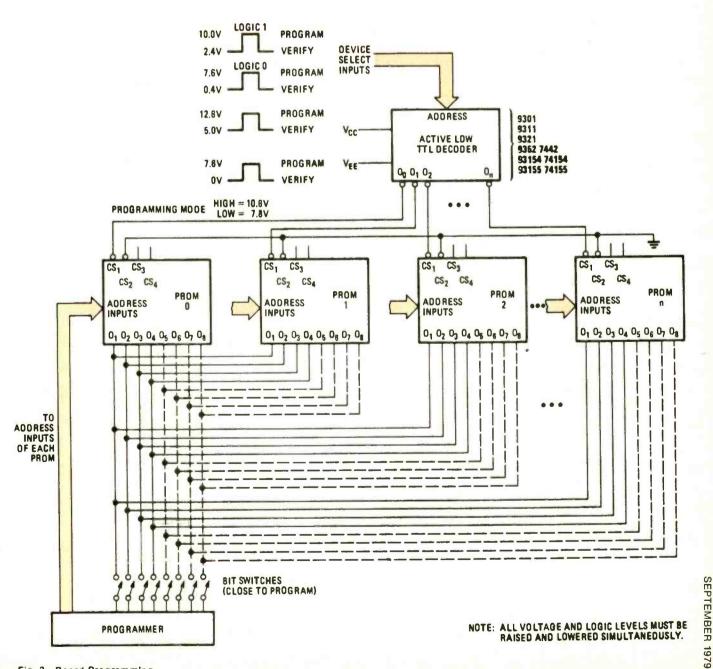9. To select a different PROM on the board, change the TTL decoder address.



# 

Think of it! A fully accredited college degree in electronics by studying at home.

#### At 18. things looked different

You remember-the most important thing was to get started working. Enough of books and classes! You wanted to make money. Maybe you had responsibilities. A family to take care of. Any further education would just have to wait.

But then you started noticing something: the guys with diplomas were getting first crack at good iobs and promotions. You were losing out. And it hurt.

#### Now you know: a degree opens doors

Government, defense contractors. large companies -they want good electronics and electrical specialists. But they also want credentials. A degree. Fortunately, even if you're working it's not too late to get one.

#### You don't have to commute, quit your job, conform to a class schedule

The Center for Degree Studies offers Associate in Specialized Technology degrees in electronics technology and electrical engineering technology.

These are no ordinary degree studies. Using guided independent study, a concept pioneered by ICS in 1890, you work at your own place and pace. No commuting to classes, no classroom pressures. You'll be supplied with clear, fully illustrated study materials including practice problems, quizzes and exams to evaluate your progress. In the final semester you'll have two weeks of on-campustraining at a leading engineering college or university.

You'll also receive valuable instruments and equipment when required, to make your course come alive. Equipment you can keep on using on the job.

#### Help is just a toll-free call away

You can call CDS/ICS from anywhere in the U.S. or Canada except Alaska and Hawaii, using our special toll-free Dial-A-Question® service.

#### CDS accreditation make your degree impressive

The Center for Degree Studies has been accredited by the Commission on Higher Education, Middle States Association of Colleges and Schools. This is the same body responsible for accrediting traditional colleges and universities of the Middle States region, including some of the nation's leading schools. So your degree from CDS means a great deal.

But maybe a degree isn't your goal. If you want career training that can help you move ahead in the exciting electronics/electrical field, ICS is the place to get it. Of course, no school can guarantee you a better job. But ICS can give you the first-rate training you need in areas like appliance servicing, TV servicing and repair, electronics, electrical contracting and more.

#### Here's what some of our students sav:

"My rotating shifts and three children made it impossible to get a degree the usual way. I did it at home through the Center for Degree Studies."

Frank Jones, Jr., East Brunswick, NJ "I started putting my knowledge to the test after only two months of training. I now have as many repair jobs as I can handle and guite a few satisfied Richard Stratton, Mastic, NY customers."

#### See what it's all about ... free

Just mail the coupon or card and we'll send you a catalog that includes a sample lesson and examination. Do it now. Don't let this second chance slip by.

#### Free facts about your electronics/electrical degree.

Mail to CDS/ICS Independent Study Programs, Scranton, PA 18515. There's no obligation and no salesman will call.

I want to know more about degree studies and career training in the electronics/electrical field

Name Address.

City, State, ZIP

Send me information about career training in the following fields:

- Electrical Motor Repair
- Electrical Appliance
- Servicing
- Electrical Contractor
- Electrical Engineering AST Degree in Electrical
- Engineering
- Electrical Fundamentals
- Electrician
- How to Install Electrical Wiring
- Industrial Electrical Technician
- Reading Electrical Blueprints Servicing Electrical
- Appliances Basic Electricity for
- Electronics

Electronics Fundamentals □ AST Degree in Electronics

XA230J

- Technology CDS-**First Semester** Electrical Troubleshooting
- Techniques □ Fundamentals of Electronics

Color Television Theory and

Troubleshooting

Electronics

- Communications Stereo Receiver & Component
- Troubleshooting Television Servicing



# HOBBY CORNER

### The programmable calculator can find many interesting applications in electronics.

#### EARL "DOC" SAVAGE, K4SDS, HOBBY EDITOR

THIS MONTH WE'RE GOING TO GET AWAY from the usual "how-to" info and talk a bit about an instrument that can be a great help in the "how-to" department. We all own soldering irons, VOM's and so on, but how about the forgotten programmable calculator?

The field of electronics is strange in many ways. Consider, for example, how microcomputers have captured the attention of hobbyists. This is quite understandable since they are awe-inspiring, and some of them can even talk!

However, the rush to microcomputers has overshadowed other electronic developments for many hobbyists; calculators are a case in point. A calculator was considered an impossible achievement just a few short years ago, and now it is practically ignored. I paid \$365 for my first book-sized "four-banger"; nowadays, dealers almost pay you to take them.

Calculators have become so commonplace that l, for one, can't even add 2 + 2without punching it out to find the answer. We all know that sophisticated calculators are available for a few tens of dollars. At this point, you may ask, so what? Well, something happened to calculators while you weren't looking.

What happened was the appearance of the scaled-up calculator—or strippeddown microcomputer, depending upon your point of view. The *programmable* calculator fits squarely between the two instruments and does not deserve to be forgotten.

#### **Programmable calculators**

Just what is a programmable calculator? It's a smart calculator that can learn; it is a dumb microcomputer that doesn't know the alphabet. If you stick with numbers, there is no limit (almost) to what it can do!

With just a few key-pushes, you can perform complex statistical analyses in a minute or two that would take hours or days on a conventional calculator. A programmable calculator can solve quadratic equations, multiple resistor networks, or inductor/capacitor frequency and impedance problems in *seconds*. It can also play a variety of games.

A programmable calculator makes it a snap to solve all kinds of involved problems. Equally important, it can perform simple or complex calculations repeatedly just by your punching in new values and then pressing the RUN key. Imagine the trial-and-error time you can save when you substitute values in a filter, for example.

If the programmable calculator doesn't already know how to do a particular job, it learns how just as quickly as you can press the keys. It is a *real* time-saver. As long as you stick with numbers, it performs as well as most microcomputers and better than some. Program it how to figure the bias resistors for one transistor and it will compute three or three hundred more resistors as fast as you can key in the conditions.

Programming it consists of nothing more than pressing a key labeled LEARN and then punching through the operational sequence of the problem. Of course, you should know how to do the problem in the first place. However, if you don't, programmable calculators come preprogrammed and/or with libraries of programs that have been figured out for you.

Let's take a look at several low-cost units that are currently available and find out what they can do for the electronics hobbyist. I have worked with three of these devices. You can find more sophisticated models, but they are definitely designed for mathematicians and engineers. In fact, even the least expensive one has capabilities (and programs) that are way over my head.

The model T1-58 (Texas Instruments, about \$130), and the models EC-4000 and EC-4001 (Radio Shack, \$60.00 and \$40.00, respectively) are three first-rate instruments. The most striking feature about them is that all three come with books of instructions.

It isn't that they are that difficult to use. The manufacturers simply don't want to leave *anything* out. They assume you don't know anything about them and proceed from there. In addition to *complete* instructions and numerous examples, the manuals provide libraries of programs (even the *model EC-4001* comes with 290 programs). If you can read, there is no way to go wrong.

The model T1-58 has several features not found on the other two. It contains connections for adding a printer. In addition, it incorporates a removable module containing 25 prerecorded programs that can be called up from the keyboard (other modules are also available).

The TI-58 provides more functions than the other two calculators. It contains 45 keys, 42 of which are dual-purpose, thus actually providing 87 keys. The model EC-4000 has 40 keys (27 of them are dual-purpose) for a total of 67 keys. The little model EC-4001 has only 19 keys, but 6 are double, 11 are triple and 1 is a four-purpose key; this gives an effective total of 50 keys.


Actually, the three calculators are much more alike than they are different. They are all battery- or AC-operated; capable of conditional and unconditional branching or looping programs; and can provide regular or scientific notation, log and trig functions, etc.

For an electronics hobbyist, perhaps the most practical difference between them is the number of memories and steps they have available for holding programs. Although they can be varied, the T1-58 normally has 20 memories and 320 potential program steps; the EC-4000 has 8 memories and 50 program steps; and the EC-4001 has 1 memory and 36 steps. In evaluating these figures, don't be misled. The number of problem steps to a solution can greatly exceed the maximum number of program steps. At first glance, this may seem impossible but it often happens through the proper and normal use of various types of branching. For example, in this manner the EC-4000 is not limited to calculations with 50 or fewer steps.

Overall, it seems unlikely that a hobbyist/experimenter would need the power and capacity of the *model TI-58*. However, if you are a student who is planning to go on to engineering or advanced math studies, the TI-58 (or better) would be the calculator to choose.

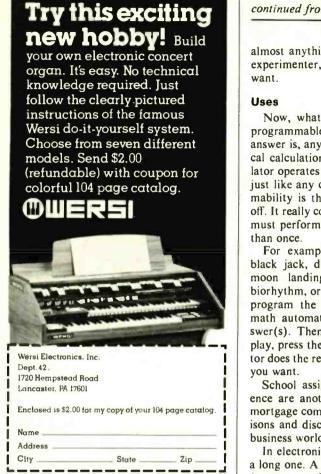However, don't get the idea that the EC-4000 and EC-4001 arc toys (remember the latter comes with 290 "canned" programs). These instruments will do Continued on page 78





CIRCLE 31 ON FREE INFORMATION CARD

#### HOBBY CORNER continued from page 76

almost anything an electronics hobbyist, experimenter, ham or CB'er will ever

Now, what can you and I do with a programmable calculator? The general answer is, anything that involves numerical calculations. A programmable calculator operates straight from the keyboard just like any calculator, but its programmability is the factor that makes it pay off. It really comes through whenever you must perform the same calculation more

For example, let's take any gameblack jack, dice-toss, number guessing, moon landing, submarine, cannonade, biorhythm, or whatever. In each case you program the calculator to perform the math automatically and display the answer(s). Then, you simply key in your play, press the RUN keys, and the calculator does the rest-over and over as long as

School assignments in math and science are another use. Bank statements, mortgage computations, interest comparisons and discounts are but a few of the business world applications.

In electronics the list of applications is a long one. A few examples are: in filters (power supply, audio, RF, bandpass, high-pass, low-pass); in networks (resistor, capacitor, inductor, combinations, tuned circuits); in antennas (dimensions, radiation, matching); and in transistor and tube-operating parameters.

Learning to use a programmable calculator provides a hidden advantage. Programming is simpler and easier to learn than for a microcomputer. Yet the principles are the same. If you become proficient in programming a calculator, you will be well ahead when you obtain your first microcomputer.

A hobbyist who builds slavishly from plans or an experimenter who sticks in different parts "just to see what will happen" doesn't need one; it would be only an interesting plaything. If you want to know why and how things operate, you have to dig a little deeper into circuits and a programmable calculator will help here. If you want to design and/or modify either simple or complex circuits, it can be as useful as meters and solder.

#### **Coming attractions**

If you've gotten the idea that I am "anti-microcomputer," it just ain't so. To prove it I'm preparing a rundown on a new, inexpensive microcomputer/controller, and we'll discuss it in a future "Hobby Corner." R-E

## Now, an automotive computer plus cruise control at your fingertips!

This is CompuCruise! The first true computer for your car, truck or RV. It's the most effective and functional cruise control ever designed, PLUS complete trip computing, an efficient fuel management system, and a split-second-accuracy quartz time system.

CompuCruise is a cruise control with a memory. A unique seek-and-hold capability makes highway driving easier and more enjoyable. Fully electronic, making it more accurate and reliable.

CompuCruise is a true computer, constantly reacting via automatic sensors to changing conditions, updating vital data for you every second. Just look at what CompuCruise gives you:

Time, E.T. Lap timing, Alarm Time, Distance, Fuel to arrival Time, Distance, Fuel to empty Time, Distance fuel on trip Current or average MPH, MPG, GPH Fuel used, Distance since fillup Inside, outside or coolant temp. Battery voltage English or Metric display


CompuCruise works on foreign or American cars (except Diesel and fuel-injected vehicles). It's priced for the budgetminded, and easily installable by you or your automotive outlet. Only \$199.95 with Cruise Control, \$159.50 without. Fully

warranted for 90 days from date of purchase. Delivered

complete with easy-to-follow installation guide. And backed by a 100% satisfaction guarantee. If not fully satisfied when you receive your unit, return it before installation and your money will be fully refunded without question.

For the name of your nearest dealer, call or write us right now: ZEMCO, 12907 Alcosta Blvd., San Ramon, CA 94583. Phone (415) 838-8060.

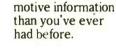Do it today-for a better cruise control and more auto-







Where do you find everything that's unique, everything that's new in electronics for home, hobby and business? Where else but in this exciting Heathkit<sup>®</sup> Catalog?...and it's



Dual

Wattmeter



Handheld Digital Multimeter









One-button Phone Dialer



#### BETTER ELECTRONICS BECAUSE YOU BUILD THEM BETTER

Some of the most exciting...and useful electronics kits you'll find anywhere. Easy to build, too! Heathkit instructions assure even a first-time builder of success. Imagine the pride as you tell family and friends, "I built it myself!" You'll save money, too, because each Heathkit manual's troubleshooting section helps you avoid costly repair bills. If you ever need help, though, it's as close as Heath's technical assistance phone line, or at 55 sales and service locations\* nationwide.

"Heathkit products are displayed, sold and serviced coast-to-coast at Heathkit Electronic Centers (Units of Schlumberger Products Corporation) listed In the white pages of your phone book.

If coupon is missing, write: Heath Company, Dept. 020-570, Benton Harbor, MJ 49022

#### send for yours TODAY!

The latest Heathkit Catalog's 104 pages contain pictures and descriptions of nearly 400 electronics kits you can build yourself...computers, color TV, amateur radio, test instruments, weather, radio control modeling, auto, boating and home products...and more. It's free.

HEATH Schlumberger	Heath Company, Dept. 020-570 Benton Harbor, MI 49022	
	e my FREE Heathkit Catalog. ntly receiving your catalogs.	
Address		
City	State	
CL-711	Zip	

CIRCLE 100 ON FREE INFORMATION CARD

**Digital Multimeter** 

Came Light

Educational Programs

R/C Gear

79

## communications corner

#### A new super-loop antenna system for DX'ing the broadcast band and a true SWR meter.

#### HERB FRIEDMAN, COMMUNICATIONS EDITOR

FOR MANY SWL'S THE REAL ACTION IS DX'ing on the broadcast band. But in today's world, between housing lots 60 X 100 feet or smaller, local ordinances against "transmitting" antennas, and crackpot neighbors who claim any visible wire radiates "eminations" that produce ghostly voices from their teeth, it's almost next to impossible to get up a longwire antenna that can really pull in the DX signals.


But there is a way to electronically boost the weak signals that can be picked up by a loop antenna, and at the same time "tune out" local stations that interfere with the DX. Fact is, with a Palomar Engineers Loop Antenna System you can tune your SW receiver to what appears to be a "dead" part of the broadcast band. and then make it spring to life with signals packed from end to end. And if a local broadcast gives you any trouble, you can simply tune it out. Sound fantastic? Well, it really does work. The Loop Antenna System consists of two sections that plug together. (See Fig. 1.) The base section contains a tuning capacitor, broadband amplifier, on/off switch, and a 9-volt "transistor" battery. Into the top of the cabinet you plug a loop antenna mounted on an unusually large, oversize, pivoting metal support. The support is calibrated to  $\pm 90^{\circ}$ , with  $0^{\circ}$  representing a horizontal loop position. The entire assembly can also be rotated through 360°, and the top of the cabinet has a 360° compass for reference.

The loop is tuned by the capacitor in the base section, so the circuit consists of a tuned loop followed by a broadband amplifier. The amplifier's output is fed through a short length of coax cable (any type) to your SW receiver.

Obviously, signals received by the loop will be "peaked" when the loop is tuned by the capacitor, and then amplified. What isn't obvious is that the loop is directional in the familiar figure-8 dipole pattern. If the loop is adjusted for maximum sensitivity, signals arriving  $\pm 90^{\circ}$ into the loop are sharply attenuated, so interference with the desired signal can he reduced

Next, imagine you can hear a weak DX

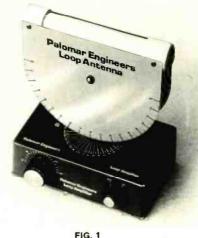signal but it's buried under a local broadcast. Now comes magic. Skip signals have no distinct polarization; reflections produce a combined vertical/horizontal wavefront. Groundwave signals, however-such as from a local station-are vertically polarized: there is essentially no horizontal component. By careful adjust-



ment of the rotational position (compass heading) and the tilt of the loop itself, it is possible to almost totally null out a local station. While this might reduce the reception of the DX signal, the signal will still be received if an adjacent or nearby local is sharply or completely nulled out.

So you have two options when it comes to the loop's position: either you can adjust for maximum received signal, or for nulling of local interference. (The null effect is very broad on skywaves-if at all-because of what is effectively dual polarization of the signal caused by sky/ ground reflections.)

The broadband amplifier is rated by Palomar Engineers at a nominal 20 dB gain. In comparison with a receiver having a built in broadcast band loop antenna, the Loop Antenna System produced a direct signal improvement of about 15 dB to 35 dB. The extra "gain" is explained by extra sensitivity of the high-Q loop/ tuning capacitor circuit in the Palomar Engineer's device.

The only limitation on use of the Loop

Antenna System is that the receiver used for broadcast band DX'ing must have external antenna terminals.

Obviously, if you have room, or some way to string a real longwire antenna, the Loop Antenna System offers little or no advantage, unless nulling of local signals is an important consideration. And if you have no way to string a longwire, the Palomar system is about the only way to bring a "dead band" to life.

You can get additional information by writing to Palomar Engineers at Box 455, Escondido, CA 92025.

#### SWR really means power

Though there is some mistvaue concerning SWR (Standing Wave Ratio), it is simply the antenna impedance divided by the transmission line impedance, or vice versa; the values being arbitrarily arranged to produce a value greater than 1. For example, if the antenna is 300 ohms and the line is 50 ohms the SWR is  $300 \div 50$  or 6:1 (the "1" being the reference value, and meaning the mismatch is 6:1). If the antenna was 50 ohms and the line 300 ohms we would rearrange the figures so again we get  $300 \div 50$ , or 6:1. There is no such thing as an SWR less than 1:1; we cannot have  $50 \div 300$  or 0.166:1.

Now the antenna to line ratio is all there is to antenna system SWR. There are no other considerations. Unfortunately, there is no convenient way to measure the antenna and line impedance where the two are connected together. Even if we had the instruments, how many of us are willing to climb to the top of a tower, or hang suspended from a wire dipole, to measure the impedance values?

Fortunately, there are other ways to accomplish the same end. If there is a line to antenna mismatch, some of the power fed into the line by the transmitter is not transferred to the antenna; it is reflected (Aha!) back towards the input end of the line, setting up standing voltage waves along the line. (There are no standing waves when the line is perfectly matched to the load as all power flows into the load.) It is easy to build a device that will measure the standing wave on the line. The device that measures voltage standing wave ratios is the VSWR meter. which is often mistakenly termed an "SWR meter". Switching is generally Continued on page 82

# Introducing the Troubleshooter.

Six functions and 24 ranges for \$129\*make the jump from Analog to Digital more affordable than ever.

We call our new hand-held 8022A DMM the Troubleshooter. It combines the basic performance features you want with all the advantages that give digital DMM's the edge over analog— 0.25% basic dc accuracy, a rugged, reliable design, a razor sharp 3½-digit LCD readout, small size and light weight.

**Measure** for measure you won't find a better value. Six functionshigh and low ohms, ac and dc voltage and current (24 ranges in all) make the Troubleshooter a 13 ounce (0.37 kg) package of excellent measurement value. This kind of value wasn't possible until our custom CMOS LSI single chip design made hand-held DMM's an affordable reality and Fluke the industry leader.

Here's something new that won't shock you. Fluke's exclusive probe design features finger guards on the probe and shrouded connections to discourage accidental contact with circuit voltages.

You won't find a more rugged or reliable hand-held DMM. There's a lot more to building a high-quality hand-held DMM than you might suspect. The case has to survive bumps, scrapes, and scuffs. The LCD readout must withstand the extremes of humid-\*U.S. Price Only ity, temperature, and vibration. Function switches need to perform reliably through thousands of cycles. And electrical circuitry must survive both physical shock and electrical overloads.

We built the 8022A to withstand all these tortures — with a rugged impact resistant plastic case, a custom LCD display, reliable push-buttons instead of rotary switches and over 20% of the components devoted to overload protection.

Take the next step. Contact the Fluke office, representative or authorized distributor in your area. In the U.S., CALL TOLL FREE (800) 426-0361. (For resi-

CIRCLE 44 ON FREE INFORMATION CARD

dents in Alaska, Hawaii, and Washington, the number is (206) 774-2481.)

In Europe, contact: Fluke (Holland) B.V., P.O. Box 5053, 5004 EB Tilburg, The Netherlands. Telephone (013)673973. Telex 52237.

Ask about the new 8022A. And while you're at it, check into the 8020A Analyst, the improved version of our \$169\* DMM. It boasts Fluke's exclusive conductance capability for high resistance measurements and 0.1% measurement accuracy. Both instruments are available at your distributor from stock. For immediate response, fill out the attached

John Fluke Mfg Co. Inc

coupon.

Mountlake Ter		oleshooter data
Please send	the 8020A	Analyst specs.
🗆 Please have	e a salesman	call.
Name		_
litle	Mail	Stop
Company		
Address		
City	State	Zip
	)	Ext.
lelephone (	/	

# See the logic of it all





DP-50 \$50

DP-100 \$80

Armed with only two portable instruments, you can now trace logic levels through the most popular types of logic circuitry...TTL, MOS, CMOS, even HTL and HiNIL.

The new B&K-PRECISION DP-100 is a digital pulser probe that's a great aid to fast analysis and debugging of integrated circuit logic systems. Sim ple to operate, the DP-100 can be used alone or with a logic probe or oscilloscope. It generates a "one shot" pulse train at a 5 Hz rate and senses circuit conditions to pull an existing high state to a low or a low state to a high.

The B&K-PRECISION DP-50 is the digital probe that offers more than logic. In addition to logic status, it actually displays pulse presence to 50 MHz. The intensity of its PULSE LED reveals the duty cycle of the signal observed.

Both the DP-50 and DP-100 are well protected against overload and accidental polarity reversal. You can see the logic of it all today! Contact your B&K-PRECISION distributor for immediate delivery.



**COMMUNICATIONS CORNER** continued from page 80

provided so we can set the *forward* voltage reading to full scale. The *reflected* voltage reading is then read, and a calibrated scale interpolates the meter pointer position into a VSWR or SWR value.

Now Ohms Law tells us that if we know the voltage and impedance values we can calculate current, or power. Fact is, professional forward/reverse indicators are calibrated in power, and the user employs a special chart to calculate SWR values. This might not seem important when you're using a 4-watt CB rig, but imagine a 300 kW TV transmitter with a 2:1 SWR. That's almost 10% of the forward power output, or 30 kW, coming back down the line that's got to go somewhere. Part of it is dissipated as heat in the transmission line; the remainder gets dissipated as heat in the transmitter's output circuit. Given a high enough SWR, you can literally burn up an output stage.

Imagine if you will, a 1 kW amateur radio linear or other final. With a 2:1 SWR you've got about 200 watts coming back down the line. When you think in terms of "200 watts" it becomes a little more unsettling than "a 2:1 SWR". You can afford to lose a little in the way of radiated signal, but can you afford to replace components that might burn up?

It is precisely for this reason that many commercial stations use meters that indicate the forward and reflected power, with the SWR calculated from special charts. To avoid the calculations, some stations employ a dual power meter consisting of two independent meter movements in a single case, with the movements located at each bottom corner. This causes the pointers to cross, and the scale is calibrated in SWR at the crossing location. In fact, the entire central area of the meter is calibrated in SWR so that regardless of the forward and reflected powers, and the meter pointer positions, they will always indicate the correct SWR value.

Formerly limited to commercial installations, the dual-purpose power/SWR meter (which dates back to the 1930's) is now available for amateur and low power commercial use as the DAIWA CN-720, distributed by the J. W. Miller Division of Bell industries (through your local amateur equipment distributor). Covering the frequency range of 1.8 to 150 MHz, with switch-selected full scale forward power ranges of 1kW, 200 W, and 20 W, and LED indicators visually indicating the selected power range, the CN-720 (and a smaller "junior" version, the CN-710) is designed for 50-ohm antenna systems employing coaxial cable transmission lines. A switch in the rear permits the output of the meter to be directed to the antenna or a dummy load

(I assume for calibration checks).

The photographs illustrate the actual operation of the CN-720 working into a deliberate mismatch producing an SWR of about 2.4:1. In Fig. 2 the transmitter is

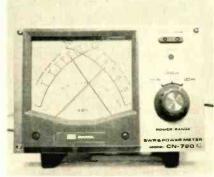


FIG. 1


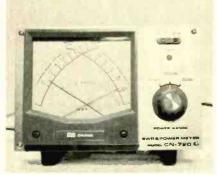


FIG. 2

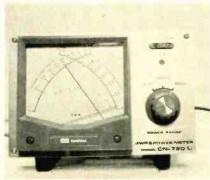

#### FIG. 3

delivering 10 watts forward power; there are about 1.5 watts reflected power. The pointers cross at about 2.4. In Fig. 3 the meter sensitivity has been upranged and the output power increased. Though the pointers indicate lower on the power scales, they still cross on a "line" representing an SWR of 2.4:1 (don't get confused by the pointers' shadows). Figure 4 shows the transmitter's 10-watt output being fed into an almost perfectly matched antenna system. The pointers now cross at about 1.2:1. Also note the almost unmeasurable reflected power that is causing the "low SWR" pointer crossing.

Best place for additional information on the CN-720 is your local amateur radio equipment distributor. If they can't help you write to the J. W. Miller Div., Bell Industries, 19070 Reyes Ave., Compton, CA. 90224. R-E

# INTERNATIONAL FM-2400CH FREGUENCY METER FOR TESTING MOBILE TRANSMITTERS AND RECEIVERS

Portable • Solid State • Rechargeable Batteries

The **FM-2400CH** provides an accurate frequency standard for testing and adjustment of mobile transmitters and receivers at predetermined frequencies.

The FM-2400CH with its extended range covers 25 to 1000 MHz.

The frequencies can be those of the radio frequency channels of operation and/or the intermediate frequencies of the receiver between 5 MHz and 40 MHz.

Frequency stability: ±.0005% from +50° to +104°F.

Frequency stability with built-in thermometer and temperature corrected charts:  $\pm$ .00025% from +25° to +125° (.000125% special 450 MHz crystals available).

- Tests Predetermined Frequencies 25 to 1000 MHz
- Extended Range Covers 950 MHz Band
- Pin Diode Attenuator for Full Range Coverage as Signal Generator
- Measures FM Deviation

FM-2400CH (meter only) Cat. No. 035320	\$627.72
RF crystals (with temperature correction)	26.26 ea.
RF crystals (less temperature correction)	19.93 ea.
IF crystals	catalog price



INTERNATIONAL CRYSTAL MFG. CO., INC. 10 North Lee / Oklahoma City. Okla. 73102 CIRCLE 67 ON FREE INFORMATION CARD

# Equip yourself with the best

#### PTS 8001 Component Analyzer



Solid state component tester works in or out of the circuit. Simple

hook-up to any standard oscilloscope. High, medium and low range switch for matching the impedance of the component being tested.

#### PTS DG-1 Digital Power Supply

External variable power supply for substituting voltages in televisions,



stereos, radios, computers, microprocessors, appliances, CB equipment, telephone equipment, electronic cash registers, security systems and other electronic devices.

#### PTS DG-4 Voltage Control Center/ Digital Power

Supply

Independently produces four variable DC supply voltages. Excellent for substituting critical control voltages for TV electronic/varactor



tuners. All units come In vinyl cabinet in optional walnut, black or blue and carry a one year limited warranty.

These products available from any PTS stocking distributor as well as PTS tuner/module servicenters. Check the yellow pages for the servicenter nearest you.



# service clinic

#### Vertical and convergence oriented problems can often be traced to a single capacitor. JACK DARR, SERVICE EDITOR

THERE ARE MANY PARTS IN TV SETS THAT cause frequent problems. However, my candidate for the most versatile and infuriating component is an easy winner. I've had problems with it for years, as have other technicians. The infuriating thing about this particular part is its ability to cause so many *different* kinds of problems.

You've probably guessed that I'm talking about the little  $50-\mu$ F or  $100-\mu$ F electrolytic capacitor found in the cathode circuit of the vertical-output tube of many color tube-type TV sets. Many different makes of sets use this circuit. So we run into problems in lots of sets from different manufacturers—all with the same cause.

Although at first glance this capacitor looks like a stock cathode-bypass capacitor, it really isn't. It has multiple functions, which is why it can cause so many different problems. It does serve as a cathode bypass, and also acts as a coupling capacitor. It feeds the parabolic pulses developed by this cathode circuit over into the convergence circuits.

So now we have the opportunity for all kinds of problems. If this "little monster" goes bad it can cause poor vertical linearity; loss of height; severe misconvergence; and in some cases a complete loss of convergence, and so on and on.

The actual problems depend on the type of defect. When they first appeared, low-voltage electrolytic capacitors weren't all that reliable. If the capacitor opens, this causes a complete loss of convergence. If it shorts, it upsets the impedance in the vertical-output cathode and results in loss of height, linearity or both. If the capacitor develops a highpower factor, this can cause many different troubles. If this happens you can't fix it by the old method of bridging it with a good capacitor! In all cases the surest method is to take the capacitor out and put in a new unit.

Very poor convergence or convergence drift can be due to leakage in the capacitor, to a high-power factor, or to many other causes. One quick check is to use a scope to display the waveform on the cathode. Normally, this waveform will be from 30-35 volts P-P with a parabolic shape that has the sharp points facing up. Follow this waveform through the capacitor to make sure that the signal is getting to the convergence board undistorted and with correct amplitude.

Reader Tom Davenport (Bellevue, OH) informs me that he had an RCA model CTC-63 with a terrible convergence problem. The picture was so far distorted that a vertical line pattern looked like a bunch of letter "C's" of different colors facing in opposite directions. The set's controls had no effect at all. He cured it by replacing this electrolytic capacitor; it was evidently completely open.

In many cases, I've told technicians to look for this capacitor to service and check it, and they couldn't find it! It is usually located on the chassis near the vertical-output tube; in quite a few sets it is mounted on the convergence board! If you trace the circuit from the convergerce board back to the vertical-output cathode, you'll find that it's in the usual place.

Finally, there is always a chance that the capacitor can be an intermittent! This can really run you up the wall unless you think of it. Intermittent loss of convergence or convergence drift can be a real headache. Always check or replace the electrolytic capacitor if you run into this problem. There's only one other component that can cause this, and I've seen it in only three sets: it's a thermal-convergence diode unit. It doesn't take long to check; just squirt coolant on it when the problem shows up. (Incidentally, this little component can also be thermal and go bad when it gets warmed up.) Most often however an electrolytic is the culprit since these capacitors love to develop intermittents when the contact between the terminal tab and the foil roll oxidizes or loosens up

This problem has been showing up ever since the development of the dry electrolytic capacitor way back in the year 5! (In the year 1, electrolytics were wet and about the size of a quart of oil. Had a nasty habit of getting the vent stopped up and exploding.)

To repeat, this is one of those oddball things that can be very simple to troubleshoot if you remember and so very hard when you forget! So, any weird problems that crop up anywhere in either the vertical or convergence circuitry, check out this capacitor. This may solve your whole problem. **R-E** 

# service questions

NO HIGH VOLTAGE, SOUND OK

This Sylvania model E40-3 plays for about 30 minutes, then loses the high voltage. The sound is still OK. After many tests, I found that pulling the high-voltage limiter, Q402, let the set work. When the high voltage goes, the + 125-volt supply jumps to + 185 volts. I then played the set for five hours with limiter Q402 removed. There were no apparent ill effects! However, I don't want to send it back like this. Any help would be appreciated.—C.L., Whitehall, PA.

Apparently, when the  $\pm 120$ -volt line goes up, this triggers high-voltage shutdown. From the voltages you show, this is what's happening (the high voltage is controlled by regulating the DC supply voltage).

Check the  $\pm 120$ -volt supply regulator, Q412, and its circuitry. Try plugging the set into a variable-voltage line transformer, and bringing the line up until the  $\pm 120$ -volt line shows exactly  $\pm 120$ . In the fault condition, see if the high-voltage adjust control is working. This control varies the bias on the base of Q410 and should control high voltage by setting the  $\pm 120$ -volt supply to the right value.

(Feedback: "Bingo! Regulator Q412 was leaky! I put a new regulator in; the set works perfectly!")

#### OHMMETER CAN TEST SCR'S

Several readers have written to ask if an SCR can be tested with an ohmmeter the same way that transistors can. Trying this test out showed that you can use an ohmmeter, at least with smaller SCR's. First, measure the SCR from the anode to the cathode. This should show an open circuit in both directions. Now, connect the positive lead of the ohmmeter to the anode and short the gate terminal to the anode. This should turn the SCR on. The larger SCR's won't latch on but will conduct when the gate is shorted to the anode. **R-E** 



Light years ahead

with information on software, hardware, simulations, circuit design, robotics, languages and compilers, computer games, custom systems design and a universe of applications.

Through each exciting issue of BYTE, the leading magazine in the personal computer field, you'll be kept informed of the latest fastpaced changes taking place within the everexpanding universe of microprocessors. You'll be way ahead with reports on home computer applications, tutorials, and computer product reviews.

BYTE's editorials explore in depth the

fun of using and applying computers for personal satisfaction in activities as wide ranging as electronic music, electronic mail, computer games, and practical personal business programs. Each monthly issue has authoritative yet easily read coverage of principles of hardware and software design, approaches to novel applications, and essential articles of interest to personal computer enthusiasts. Expand your mind with BYTE!

Read your first copy of BYTE. If it is everything you expected, honor our in-

> voice. If it isn't, just write cancel on the invoice and mail it back. You won't be billed, and the first issue is yours to keep at no charge.

-	BYTE® Subscription Dept. P.O. Box 590 Martinsville, N.J. 08836	>
AM and	United States  One year \$18 (12 issues) Two years \$32 Three years \$46 Canada or Mexico One year \$20 (12 issues) Two years \$36 Three years \$52	Thursday
TE Sub-	CHECK ENCLOSED (Entitles me to 13 issues for price of 12, North America only) Bill Visa Bill Master Charge Bill me (North America only)	hrough . Dial To U.S.)
ssing n. If you I all the By ment bety	Card Number Expires Signature Name (please print)	Monday t on Friday ntinental NH resi- 7217.
llow 6 to 8 eeks for proce our subscriptio ny questions, c rription Depart	Address         City       State/Province/Country         Code         Foreign Rates       (To expedite service, please remit in U.S. funds drawn on a U.S. bank)         Europe, one year, air delivered \$32       Other countries, one year, surface delivered \$32. Air delivery available upon request.	30 PM (ET), 1 nd until noon ree (within co 00-258-5485. ents dial 1-924-
S a v e S	RVTE Publications log 1979	4 0 L 0 P

The Small Systems Journal

CIRCLE 51 ON FREE INFORMATION CARD<sup>©</sup> BYTE Publications, Inc. 1979



## FREQUENCY OR TIME \_\_\_\_\_ USE THE BEST BUY JAN CRYSTALS

- CB
- CB standard
- 2 meter
- Scanners
- Amateur Bands
- General
   Communication
- Industry
- Marine VHF
- Micro processor crystals

Send 10° for our latest catalog. Write or phone for more details.

#### Jan Crystals



2400 Crystal Drive Ft. Myers, Florida 33907 all phones (813) 936-2397

easy

charge

# new products

More information on new products is available from manufacturers of items identified by a Free Information number. Free Information Card is inside the back cover.

AUTOMATIC DIAL PHONE, Freedom Dialer, replaces a conventional phone. In addition to providing 32-number automatic dialing capability, the unit features an LED clock, elapsed timer,



**CIRCLE 151 ON FREE INFORMATION CARD** 

month/date calendar and phone-number reminder. Also included are separate pushbuttons for dialing police and fire emergency numbers, plus an automatic redial function. Suggested retail price: \$199.95.—Royce Electronics, 1746 Levee Rd., North Kansas City, MI 64116.

DIGITAL POWER SUPPLY, model DG-1, can be used to substitute voltages in TV's, stereo systems, radios, computers, CB's, and many other electronic devices. The voltage meter provides a



#### CIRCLE 152 ON FREE INFORMATION CARD

0.05% accuracy and indicates to 0.1 volt. The unit is housed in a choice of walnut, black or blue vinyl. Dealer net price: \$114.95.—**PTS Electronics, Inc.,** Box 272, Bloomington, IN 47401.


12-MHZ SINGLE- AND DUAL-TRACE SCOPES, model 1021A, 1022A, are mini-sized instruments. Both units (model 1022A shown) have a rectangular CRT and internal graticule with  $8 \times 10$ -division display area. Unit specifications: a 5 mVper-division vertical sensitivity, display modes such as Channels 1 and 2, chopped, alternate and X-Y (model 1022A only); a continuously variable sweep speed from 100. ns-per-division to 100 ms-per-division; X 10 magnification; 36-ns risetime;  $\pm 3\%$  accuracy; internal and external triggering. Both units measure 8 W  $\times 7\%$  D  $\times 3\%$  inches H; weigh approximately 5 lbs., and operate on 10–16 VDC at less than 1A. Both models come with probes,  $\times 10/\times 1$  feature, 115 VAC adapter,



CIRCLE 153 ON FREE INFORMATION CARD

operator's manual, with other optional accessorles available. Prices: *model 1022A*, \$785; *model 1021A*, \$595.—Ballantine Laboratories, Inc., P.O. 97, Boonton, NJ 07005.

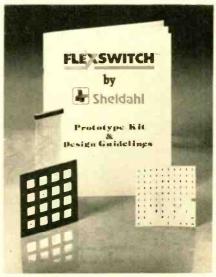FLAT SWITCHING PANEL KIT, Flexswitch, is a 16-position, nontactile switching control panel that can be trimmed to a 2- to 16-key water- and dust-resistant keyboard. Pressure-sensitive adhesive on panel back and press-on characters



**CIRCLE 154 ON FREE INFORMATION CARD** 

provide flexibility in control panel design. When ordering, specify short-to-ground or crosspoint clrcult. Comes with 8- or 17-position circuit connector, depending on circuit chosen. Price: *Flexswitch*, \$10 postpald by cash or check (no purchase orders).—Sheldahl, Inc., Dept. FSCP, Box 170, Northfield, MN 55057. R-E

CIRCLE 18 ON FREE INFORMATION CARD



#### SPECIFICATIONS

FREQUENCY RANGES:	Direct • 10 Hz to 60 MHz Prescaled • 10 MHz to 600 MHz
SENSITIVITY:	<15 mv at 30 MHz typical 25 mv at 150 MHz typical <50 mv at 450 MHz typical
TEMP. STABILITY:	.09 PPM/C° (± 1 PPM 20° to 40° typ.)
GATE TIMES:	Selectable — 1.0 second 0.1 second
RESOLUTION:	1 Hz - 10 Hz to 20 MHz 10 Hz - 10 MHz to 60 MHz 100 Hz 10 MHz to 600 MHz (Prescaled)
INPUT IMPEDANCE:	60 MHz - 1 Meg shunted by 20 pf 600 MHz - 50 ohm
INPUT PROTECTION:	Direct input — 100 V up to 10 MHz 50 V up to 60 MHz Prescaled input — 2 V max.
DECIMAL POINT:	Automatic placement
POWER REQUIRE- MENTS:	9 to 15 V AC or DC 300 ma.
BATTERIES:	4 each AA Ni-Cad.
SIZE:	3 ¾" H x 5" W x 5½2" D.
WEIGHT	1 Lb. 9 Oz. with batteries.

í



317-297-2717

**Completely Assembled** with a **1-Year Warranty** PACKAGE INCLUDES: TR-1000 freqcy. counter telescoping antenna AC power pack 4-AA nicad battery pack ALL FOR h

FOB Indianapolis, Ind. Indiana residents add 4% tax



# communications products

More information on communications products is available from manufacturers of items identified by a Free Information number. Free Information Card is inside the back cover.


MOBILE SCANNING RECEIVER, model SX-100, suitable for both mobile and home-base operation, is keyboard-programmable—most-used frequencies are entered into 16-channel memory for pushbutton retrieval. Other features include



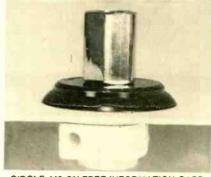**CIRCLE 111 ON FREE INFORMATION CARD** 

variable-speed scan-delay control; seek function to tune to and lock into next programmed channel; digital clock; volume and squelch controls; built-in speaker; and AC/DC operation. List price: \$489.95.—J.I.L., Dept. P, 737 West Artesia, Compton, CA 90220.

CB ANTENNA MOUNT, model 142, model 143, model 144. The model 142 is a heavy-duty root mount designed for mobile applications. Made of chrome-plated brass, mount accepts any <sup>3</sup>/<sub>1</sub>-inch



CIRCLE 112 ON FREE INFORMATION CARD

base antenna and fits a ½-Inch mounting hole. The model 143 is a flat ball-mount bracket, and the model 144 is a flat bracket bent 90° for vertical installation. Brackets accept most ball-type mounts and are corrosion-resistant. Suggested retail prices: model 142, \$5; model 143, \$7.50; model 144, \$8.—Valor Enterprises, Inc., 185 W. Hamilton St., West Milton, OH 45383.


SSB CB BASE TRANSCEIVER, model SB-5400, is a microprocessor-controlled transceiver that provides 5 programmable channel memories, automatic 2-speed 2-mode channel scannling (240 ms-per-channel, or 2 seconds-per-channel), and 15-pushbutton keyboard. The model SB-5400 also features PLL synthesizer, LED readout, 4digit LED clock, signal-strength and SWR meters, 40 AM/80 SSB channels, 4 operational modes (AM, USB, LSB, PA), 4-watt AM output, 12-watt PEP SSB, and 100% modulation. Dual-MOSFET receiver has  $0.5-\mu$ V AM and  $0.3-\mu$ V SSB sensitivity and -70 dB adjacent channel rejection. Other controls include dual clariflers, noise blanker and



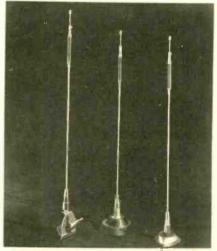**CIRCLE 113 ON FREE INFORMATION CARD** 

limiter, volume, squelch, RF gain, mike gain, SWR calibrate, and speaker and power switches. Builtin power supply provides 12 VDC or 117 VAC operation. Unit comes in simulated woodgrain vinyl-clad aluminum, and carries a list price of \$529.95—Robyn International, Inc., Northland Dr., P.O. Box 478, Rockford, MI 49341.

MOBILE ANTENNAS, *Monitennas*, is a line of mobile, four-band scanning antennas that operate on low- or high-VHF and two UHF bands. Each antenna is 24 Inches high, is constructed of stainless steel and brass, comes with hermetical-



CIRCLE 114 ON FREE INFORMATION CARD

ly sealed coils and RG-58/U coax cable (plugs attached). Retail prices: \$19.95-\$26.95.-Channel Master, Ellenville, NY 12428.

CIRCLE 56 ON FREE INFORMATION CARD

# ALL THE MOST WANTED FEATURES AT A MOST WANTED PRICE...

BIG ½" HIGH LCD DISPLAY USE INDOORS OR OUT 200 HOUR 9V BATTERY LIFE AUTO ZERO, POLARITY, OVERRANGE INDICATION 100 mV DC F.S. SENSITIVITY 19 RANGES AND FUNCTIONS



Removable cover stores test lead set furnished as part of the unit.



Available accessories include AC adapter, padded vinyl carrying case 40KV DC probe, 10 Amp DC shunt.



X10 DCV probe adapter available for protecting input up to 10KV.

CIRCLE 65 ON FREE INFORMATION CARD

TEMPERATURE: 0°-50°C

SPECIFICATIONS: DC VOLTS (5 RANGES): 0.1mV to 1000V; Accuracy ±0.5% rdg ±0.5% f.s.; Input imped: 10M Ω; Max. input 1kV except 500V on 200mV range. AC VOLTS (40Hz to 5kHz): 0.1V to 600V; Accuracy: ±1.0% rdg ±0.5% f.s. (-2dB max. at 5kHz); Max. input: 600V. RESISTANCE (6 LOW POWER RANGES): D.1Ω to 20MΩ; Accuracy: ±0.5% rdg ±0.5% f.s. (±1.5% rdg on 20MΩ range); input protected to 120VAC all ranges. DC CURRENT (6 RANGES):.01nA to 100mA; Accuracy: ±1.0% rdg ±0.5% f.s. DIMENSIONS AND WEIGHT; 5-778" x 3-3/8" x 1-3/4", 12 oz.; POWER: 9V batt. (not incl.) or Hickok AC adapter; READ RATE; 3/sec. OPERATING

HICKOK Y 303 DEE V/mA Ô ACY x1kV 600V ms max THE **R1**¥ 1000V ID TEON HEV de mai -198 TEL TH main () mA DCV COM ACV

\$74.95 HICKOK

> THE HICKOK ELECTRICAL INSTRUMENT CO. 10514 Dupont Avenue • Cleveland, Ohio 44108 (216) 541-8060 • TWX: 810-421-8286

Here is the handfull of accuracy you've been waiting for. Handsomely encased. Compact. Efficient. Only12ounces. Hickok's exciting, new LX 303, 31/2 digit Mini-Multimeter with high quality components, one year guarantee and rugged Cycolac® case offers features previously found only in expensive units. . .at a price under \$75.00! So why wait any longer? The amazing LX 303 is here. NOW! Another American made test equipment breakthrough from Hickok, The Value Innovator. Order today!


See your local Hickok distributor or order below

ADVANCE       TO ORDER CALL TOLL FREE 800-223-0474         St Wear 45th Street, New York, NY. 10036 212-687-2224       Image: Constraint of the street
Account # Exp. Date Name Address
CityStateZlp Add \$3.00 Postage and Handling, NY. residents add sales tax. RE0



Come on, treat yourself—and save money, too. Subscribe to Radio-Electronics today, and make sure you get all of the most interesting, most exciting and authoritative electronics reporting in any magazine, month after month. Don't miss a single one of the upcoming Issues jam-packed with new-equipment test reports, projects to build, servicing ideas, and news of solid state, computers, hi-fi, hobbles and everything electronic. Save money, too—as much as \$11 off the newsstand price when you subscribe to Radio-Electronics. Come on, you deserve it—check off the money-saving offer you prefer on the handy coupon, and start enjoying Radio-Electronics every month.

deserve it—check off the money-saving offer enjoying Radio-Electronics every month.		handy coupon, and start
Get The Authority—Every N	Aonth	4199
Address		
City	State	Zin Code
	Jiale	Zip Code
Indicate the offer you prefer:	Payment encl	osed (send one extra issue)
1 Year—12 issues ONLY \$9.98     (You save \$5.00 off newsstand price.)	Bill me	
2 Years—24 issues ONLY \$19.00 (Save Moret \$11.00 off newsstand price.)	Check here if subscription.	you are extending or renewing your
Extra Shipping: Canada \$3.00 pe		tries \$5.00 per year.
Mail to: Radio-Electronics SUBSCRIPTION DEPT., P.O. BOX 25	20 BOULDER. C	OLO. 80322
ODTOEL ECTDONIC		
OPTOELECTRONIC	WITH	CIRCUITS FASTER
EMICONDUCTORS:	VE	CTOR P178-1
	The state	7.95
28-PAGE		
LUTAUE	NEW IMPRO Makes sold	
CHOOSE	wrapped connection	ns 3 times
CHUUJE	faster than way.	usual
	Quick-melt	
& USE	insulation clean, fast	top A
	solder join with 759P	ts ///
GUIDE	iron.	
	Fast snap-i	n
RAGUE BOMALST IN TAIL	• Easy threa	ding
Describes highly di-	& finger	
verse line of optoelec-	tension & advance.	
tronic devices.	• SI m, light,	
Gives data on 77	• SIm, light, confort- able tis	A Canton
different visible light- emitting dlodes, alpha-	sangle.	
numeric light-emitting		
diode displays, infra- red emitters, photo	ŕ	NEW!
transistors, opto-isola-	l	better
tors plus mounting hardware.	EVERYONEL	
ncludes electrical & mechanical specifications	NER	23.
characteristic curves.	a B	and the
rovides handy cross-reference (other makes to	BBB	2011
gue Products).	If unavaila	ble locally, factory order. Add ping and handling charge.
for your copy	California	residents add 6% sales tax.
uide C-710 to gue Products SPRAGUE		ELECTRONIC COMPANY, Inc dstone Av., Sylmar, CA 91342
The Marshall St., THE MARK OF RELIABILITY	p	dstone Av., Sylmar, CA 91342 hone (213) 365-9661 twx 910-496-1539
Adama,     O1247. a subsidiary of GK Technologies		
CIRCLE 38 ON FREE INFORMATION CARD	CIRCLE 58	ON FREE INFORMATION CARD

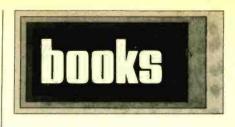

THE "COMPULATOR" BOOK—Building Super Calculators & Minicomputer Hardware with Calculator Chips, by R. P. Haviland. TAB Books, Blue Ridge Summit, PA 17214. 322 pp. 3 × 8¼ in. Softcover, \$7.95; hardcover, \$10.95.

This is a step-by-step guide to using calculator iC's to create more efficient calculators with sophisticated functions. All projects have been tested and include easy-to-follow instructions and circuit drawings. Some of the projects teach you how to create a computer interface for log and trig functions, an electronic lock, a *Teletype* interface, plus how to make glant displays, keep running totals, and many more. Other chapter topics include IC logic levels and voltage requirements, how keyboards operate and how digits are multiplexed. Chapter 10 contains instructions on how to build a tape-controlled calculator, Interfacing the calculator circuit to a *Teletype* terminal.

THE CMOS DESIGNERS' PRIMER AND HAND-BOOK, Second Edition, by Robert M. Glorioso and Jack Streater. E&L Instruments, Inc., 61 First St., Derby, CT 06418. 290 pp.  $6 \times 9$  in. Softcover, \$8.50.

This book is an expanded and revised guide to CMOS circuit design geared to engineers, hobbyists and designers. The introductory chapters outline and describe various basic CMOS devices and how to use them. A chapter on "How to Use CMOS Logic" covers power requirements, input protection, TTL interfacing and other topics. Other chapters include data on op-amps and microprocessors, and the reader has an opportunity to perform several experiments. The back of the book contains appendixes of characteristics and pinouts for more than 100 devices, plus a glossary of terms.

AN INTRODUCTION TO MICROCOMPUTERS, VOLUME II, SOME REAL PRODUCTS, by Adam Osborne, with Susanna Jacobson and Jerry Kane. Adam Osborne & Associates, Inc., P. O. Box 2036, Berkeley, CA 94702. 1208 pp. 5<sup>1</sup>/<sub>4</sub> × 8 in. Softcover, \$15.

This book is the companion volume to An Introduction to Microcomputers, Volume I, Basic Concepts, and deals with actual LSI circuits. Covered In this book are such devices as the 8080A, 8085, 8048, MC6800, Z80, 9440, MCS6500, PACE and SC/MP microprocessors. Only instruction set summaries are included, no actual programming descriptions. Each instruction set has two tables, with its own set of symbols, used for those tables alone. A short benchmark program is given to illustrate each program set and the text is augmented by many schematics and tables.

SEMICONDUCTOR REFERENCE AND APPLICATION HANDBOOK No. 276-4002. Radio Shack, Tandy Corp., 1400 One Tandy Center, Fort Worth, TX 76102. 144 pp. 8%  $\times$  11 pp. Softcover \$1.95.

This book contains replacement listings for over 46,000 transistors, diodes and other interchangeable devices. Data and schematic diagrams are also included on such IC's as counters, BCD decoders, op-amps, flip-flops, etc.; there is also a full description (plus schematic) of the 8080A microprocessor CPU. Other sections deal with soldering, case dimensions, and transistor testing; and a glossary of words and expressions is included in the back.

#### PC BOARDS

continued from page 53

minal must have its own hole. The circuit board can have one of two types of holes (or even both types at extra cost)plated-through and nonplated-through holes. The nonplated-through holes of course will not conduct from one side of the board to the other. These holes are drilled after plating (and quite often after etching). Plated-through holes are drilled before plating; during plating, a reliable interconnection is deposited between the layers on the inside walls of the hole. Since most hobbyists do not have the equipment to plate their own boards, we will only discuss nonplated-through holes

A nonplated-through hole should be drilled using the following equation:

$$D_{\min} = L_{\max} + T_{\min}$$

where D<sub>min</sub> is the minimum hole diameter, L<sub>max</sub> is the maximum lead diameter, and  $T_{min}$  is the tolerance of the drill. Always choose the next larger standard drill size if the calculated diameter falls between two sizes. The largest hole should never be over 20 mils greater in diameter than the lead to be inserted in it


#### Summary

Although this article has contained a good many facts and equations, PC de-




CIRCLE 47 ON FREE INFORMATION CARD

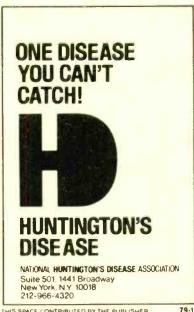sign does not have to be quite so formal. After you've worked with various materials and designed a few systems, you'll develop a certain intuitive expertise. This will reduce the amount of data required during design. Regardless of how the information is used, the procedure outlined in this article should be used if your design is to have any measure of reliabili-R-F ty.



THIS SPACE CONTRIBUTED BY THE PUBLISHER

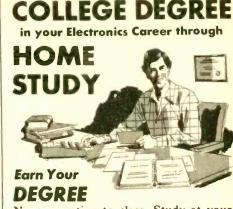

Put Professional Knowledge and a

No commuting to class. Study at your own pace, while continuing your present job. The Grantham home-study program leads first to the A.S.E.T. and then to the B.S.E.T. degree. Our free bulletin gives complete details. Write for Bulletin R-9.

Grantham College of Engineering 2500 S. LaCienega Blvd. Los Angeles, California 90034



The Grantham home-study package course for FCC license preparation consists of electronics technician studies slanted toward FCC license exams and final review materials to put you in top condition for the FCC exam just before you take it.

The electronics-technician studies consist of 91 lessons, bound in six lesson books, size 7 x 101/2, totaling 2062 pages. These lessons "begin at the beginning" and cover basic electricity, basic mathematics, electronic devices and circuits, electronic circuit analysis, radio and television systems, microwaves, etc.-all written in conversational easy-to-understand language, for home study. Included are detailed explanations, many diagrams and illustrations, many sample problems with solutions, 91 lesson-tests and 5 review-examinations. These lessons cover complete technical preparation for FCC radiotelephone exams.

The 91 lessons discussed above are followed by an additional volume of 377 pages, entitled Grantham FCC License Study Guide. This final volume of the package course covers FCC rules and regulations likely to appear on FCC exams and a complete technical review concentrated on the points most likely to appear on FCC exams. This study-guide volume consists of 1465 FCC-type multiple-choice questions, arranged by class of license in a total of 16 "pre-exams," with more than 65,000 words explaining the correct answers, with the explanations keyed to the questions.

#### 10-day free-examination money-back guarantee.

For this entire FCC License package course (everything you need to study for your FCC exam) sent postpaid upon receipt of your order, send \$99 cash in advance, or send \$39 down to be followed by two monthly payments of \$12 each. Please send payment with order (no C.O.D.s) to:

Home Study Publications P.O. Box 35499, Los Angeles, CA 90035 CIRCLE 45 ON FREE INFORMATION CARD 91

# Nobody does it better than **NIZ**

# NEW SUPPLYSTS DO TWO JOBS



... cost less than other power supplies alone!

Save money. Why buy a power supply and a voltmeter when a SUPPLYST will do both jobs. Every SUPPLYST is both a laboratory quality, fully regulated source of DC power and a dual digital voltmeter. That's real versatility!

As a power supply, a SUPPLYST can be set to your desired "voltage" and your "current limit" by convenient panel controls. Instant pushbutton reset. You can continuously monitor either voltage or current on a clear LED digital readout.

As a voltmeter, a SUPPLYST can be used to measure one or two external circuit voltages simultaneously-even while the unit is being used as a power supply!

SUPPLYSTS come with probe and one year parts and labor warranty. Available in four models-to meet a wide range of needs.

See your local VIZ distributor.



For faster service

USE

**ZIP** 

CODE

on

all

mail

THE GOVERNMENT CAN DO EVERYTHING THE UNITED WAY DOES ONLY THEY WRAP IT UP FOR YOU IN NICE RED RIBBON.

MILESAND MILES OF IT.

4 7

One of the best things about United Way is not what it does, but what it doesn't do. For instance, because United Way is run almost entirely by volunteers, it is able to return an amazing 89r of every dollar to people who need it. That means less than 11% goes for administrative costs.

administrative costs. So it doesn't waste

And because United

And because United Way is re-created each year with a combination of old' become over encumbered with huge staffs of people who might actually get in the way of progress. So it doesn't strangle you in red table

So it doesn't strangle you in red tape. All of which means that because of what United Way doesn't do. it can do a much better job at what it does do. Helping people.

Thanks to you it works, for all of us

United Way

your money.



More information on new lit is available from the manufacturers of items identified by a Free Information number. Use the Free Information Card inside the back cover of this issue.

SPEAKER SYSTEMS, 49-page catalog details characteristics of Speakerlab hi-fi speaker kits. Speakers are shown in full color and each system is described in detail, with technical specifications and prices. Some of the systems featured Include Speakerlab 30, Subwoofer Drive System 1000, and Speakerlab 1 (designed for inexpensive or low-powered receivers). Also included is a section on woofer design as well as lists of woofers, mid-range speakers, tweeters, enclosures, crossovers, accessories and publications. Two complete stereo systems are described with their specs and prices. A handy separate order form for your convenience comes with the catalog .-Speakerlab Inc., 735 N. Northlake Way, Seattle WA 98103 R-E

CIRCLE 141 ON FREE INFORMATION CARD

# Cramped for Antenna space?



#### The McKAY DYMEK DA 100.

The DA 100 is a compact, wide dynamic range, broadband, untuned, omni-directional receiving antenna covering the frequency range of 50 kHz to 30 MHz.

The exterior module, a small weather-proof box with a 56 inch (142 cm) whip delivers the signal to the power supply unit through a supplied 50' coaxial cable

The power supply locates near your general coverage receiver and attaches with a supplied patch cord.

The DA 100 antenna is small, but will equal or outperform a 100' long wire antenna, and is priced within reach of everyone!

**Output Impedance - Attenuator Switch** provided to match receiver input requirements and prevent overload

Order factory Direct. Call toll free today! Money Back guarantee. Rent/Own Plan available. Specs and details on request.

Nationwide 800/854-7769 California 800/472-1783




McKay Dymek Co. 111 S. College Ave., PO Box 5000 Claremont CA 91711

CIRCLE 36 ON FREE INFORMATION CARD



More information on stereo products is available from manufacturers of items identified by a Free Information number. Free Information Card is inside the back cover.

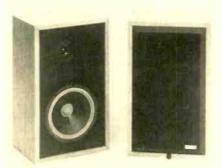SPEAKER SYSTEM, model CL 2, features acoustic suspension with a 10-inch woofer and 1-inch soft-dome tweeter. Its specifications include: frequency response, 52 Hz-22 kHz within 2 dB; crossover, 1200 Hz; nominal input Impedance, 8 ohms; minimum input impedance, 6 ohms; 60-



#### CIRCLE 131 ON FREE INFORMATION CARD

watt power-handling capacity; sensitivity, 9I.5 dB at 1 meter with a 1-watt "pink noise" input. The model CL 2 comes housed in either an oak or walnut-grain cabinet, with black or brown frontgrille panel. It measures 23½ H X 14 W X 10¾inches D. Suggested retail price, \$139.—KLH **Research & Development Corp.**, 145 University Ave., Westwood, MA 02090.

**POWER AMPLIFIER**, model 2300, has a rated output of 150 watts-per-channel minimum RMS, into 8 ohms, 20 Hz—20 kHz, 0.05% THD. Other features include toroidal transformer, thermal



#### CIRCLE 132 ON FREE INFORMATION CARD

protection, signal relays, overload protection, and LED indicators to monitor power output. Suggested retail price: \$700.—Scientific Audio Electronics, Inc., 701 E. Macy St., Los Angeles, CA 90012.

**CASSETTE TAPE DECK**, model M-T01, measures just  $10^{5/n} \times 5^{1/n} \times 9^{5/n}$  inches and weighs 17 lbs., 10 oz. The unit features a closed-loop dual-capstan system and Dolby noise reduction. Controls include peak-level meters, a multiplex filter, three-way bias and equalization switches, time-controlled record/playback functions, memory play/stop capability, line/mike mixing capability, an output-level control, and a mike jack. Specifi

cations: frequency response: (standard tape), 30 Hz-15 kHz; (ferrous and chrome tape), 30 Hz-17 kHz; S/N ratio, 64 dB (with Dolby); wow-and-flut-



CIRCLE 133 ON FREE INFORMATION CARD

ter, 0.045%. The *model M-T01* comes in a gold finish enclosure. Suggested retail price: \$560.— Mitsubishi, Melco Sales, Inc., 3030 E. Victoria St., Compton, CA 90221.

DIRECT-DRIVE TURNTABLES, Series 5000, Is a line of quartz-locked automatic, semiautomatic and manual turntables constructed of antiresonant material. The model SL-5100 (shown) is a manual turntable with a high-torque servomotor, an LED strobe light speed indicator, a manual pitch control and a 12-gram tonearm (includes diecast aluminum headshell with gimbal suspen-



#### CIRCLE 134 ON FREE INFORMATION CARD

sion). The model SL-5200 Is a semiautomatic unit with automatic tonearm return. LED Indicator and manual pitch control. The model SL-5300 has a high-torque servo-controlled motor to minimize ripple, cueing switch, on-off switch, two speed controls and manual pitch control, 12-gram tonearm; plus automatic single disc operation with Memo-Gram control that automatically repeats records up to 6 times. Specifications for the model SL-5300: speed drift, ±0.002%; wowand-flutter, 0.025%; rumble, 78 dB. The model SL-5350 is fully automatic; plays up to 6 records; and features Memo-Gram repeat control, LED Indicator light, manual pitch control and cueing switch (optional manual spindle available). Suggested retail prices: model SL-5100, \$240; model SL-5200, \$260; model SL-5350, \$340; model SL-5300, \$290 .- Technics, One Panasonic Way, Secaucus, NJ 07094. R-E

# You'll find more of what you need at the GC Chemical Center



Producing service chemicals is how we got our start half a century ago. Today, you'll find all the chemicals you want at your GC distributor:

- cements & glues
- "miracle" adhesives
- thinners & solvents
- Iubricants
- cleaners
- insulating chemicals
- printed circuit soldering chemicals
- circuit coolers
- special non-slip compounds

...all the different chemicals and cements you need for every kind of electronic repair or service.

Ask your distributor for the all-new GC 50th anniversary catalog of over 5000 products, for all your electronic needs.



93

400 S. Wyman Street, Rockford, IL 61101 815/968-9661

CIRCLE 66 ON FREE INFORMATION CARD

market center

CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services). \$1.50 per word (no charge for zip code) . . . minimum 15 words.

NONCOMMERCIAL RATE (for Individuals who want to buy or sell personal items) 85¢ per word . . . no minimum.

ONLY FIRST WORD AND NAME set in bold caps. Additional bold face (not available as all caps) at 10¢ per word. Payment must accompany all ads except those placed by accredited advertising agencies. 5% discount for 6 issues, 10% for 12 issues within one year, if paid in advance. All copy subject to publisher's approval. Advertisements using P.O. Box address will not be accepted until advertiser supplies publisher with permanent address and phone number. Copy to be in our hands on the 26th of the third month preceding the date of the Issue (i.e., August Issue closes May 26). When normal closing date falls on Saturday, Sunday, or a holiday, issue closes on preceding working day.

#### FOR SALE

FREE catalog (anglais). IC's, semi's. CORONET ELECTRONICS, 649A Notre Dame W., Montreal, Que., Canada, H3C 1H8. US inquiries.

RADIO & TV tubes 36¢ each. One year guaranteed. Plus many unusual electronic bargains. Free catalog. CORNELL, 4217-E University, San Dlego, Calit. 92105

TEST equipment catalog listing used Tektronix, HP and GR equipment at bargain prices. Price \$1.00 refundable with first order. PTI, Box 8699, White Bear Lake, MN 55110

NAME brand test equipment. Guaranteed discounts up to 50%. Free catalog. SALEN ELEC-TRONICS, Box 82-M, Skokle, IL 60077

SATELLITE Television-movies, sports, etc. Build or buy your own Earth Station. Send \$3.00 for information. SATELLITE TELEVISION, Box 140, Oxford, NY 13830 AUDIO noise reduction kit—318 silencer for tapes, records, FM. Free brochure. LOGICAL SYSTEMS, 3314 "H" St., Vancouver, Washington 98663.

TELEPHONES unlimited, equipment, supplies. All types, regular, keyed, modular. Free Catalog. Cali now toil free (800) 824-7888 in California, (800) 852-7777—Alaska, Hawaii—(800) 824-7919 ask for Operator 738

TUBE caddys: Just like the old favorite. . Only better! Free catalog: (800) 233-8851. JOHN AN-THONY TELEVISION, Box 13, Matamoras, PA 18336

FREE catalog of new merchandise, at great prices. IC's, semi's and more. KEY ELECTRON-ICS, Box 3506-RE, Schenectady, NY 12303

LED pen 6 function watch now only \$18.00, add \$1.50 for postage, regular price \$50.00. F J REYES, 12421 Racine St., Calumet Park, IL 60643

To run your own classified ad, put one word on each of the fines below and send this form along with your check for \$1.50 per word (minimum 15 words) to:

Radio-Electronics, 200 Park Avenue South, N.Y., N.Y. 10003

**ORDER FORM** 

PLEASE INDICATE in which category of classified advertising you wish your ad to appear. For special headings, there is a surcharge of \$10.

) Plans/Kits () Business Opportunities () For Sale ) Education/Instruction () Wanted ()

( ) Special Category: \$10

(PLEASE PRINT EACH WORD SEPARATELY, IN BLOCK LETTERS.)

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35



PRINTED-circuit boards, reasonable. Also, artwork, prototypes, designs, fabrication and testing. MICROCON INC., Box 43, Glenview, IL 60025

RCA, Zenith original TV parts. Dealer prices, fast service. Send part and model numbers. L.I. ELEC-TRONICS, 981 Sunrise Hwy., Bayshore, NY 11706, 516-666-7360

NEW. Meter solid-state isolated relay. Control 5 millivolts 5 microamperes 1000 ohms DC. Lead circuit 3 amperes 125 VAC. Write today for facts. EGYED ELECTRONICS, Box 92, Huntingdon Valley, PA 19006

SENSITIVE converter 1.6-2.4 GHz \$99.95 postpaid. Details for stamp. GW ELECTRONICS, POB 688, Greenwood, IN 46142

RECORDSAVER, poly-lined inner sleeves, ten cents each, postpaid, minimum 100. DEO INC., Box 452J, Glenview, IL 60025

#### **COMPUTER INFORMATION**

OSI 1P users. Solve some of the mysteries of your machine. Also some 1P orientated supplies. \$1.00 + S.A.S.E. gets sample info sheet and list. BILL'S MICRO SERVICES, c/o William Dirks, 44th USAAD, APO New York, NY 09221





\$89.95

29.95

B1-FET, minl dip, 741 type

RE 3216, terminal card RE 6416, terminal card

Lower Case option, 6416 only

Power Supply Kit Video/RF Modulator, VD-1

VIDEO TERMINAL

741 mini dip

**OP-AMP SPECIAL** 

A completely self-contained, stand alone video ter-minal card. Requires only an ASCII keyboard and TV set to become a complete terminal unit. Two units available, common features are: single 5V supply. XTAL controlled sync and baud rates (to 9600), complete computer and keyboard control of cursor. Parity error control and display. Accepts and gener-ates serial ASCII plus parallel keyboard input. The 3216 is 32 char. by 16 lines, 2 pages with memory dump teature. The 6416 is 64 char by 16 lines, with scrolling, upper and lower case (optional) and has RS-232 and 20ma loop interfaces on board. Kits include sockets and complete documentation. RE 3216. terminal card **\$149.95** 

easy assembly. Clear, step by step instructions guide you to a finished unit you can rely on Order your today! CB-1. Color TV çalibrator-stabilizer DP-1. DC probe, general purpose probe HP-1. High impedance probe, non-loadin

CT-50, 60 mHz counter kit CT-50WT, 60 mHz counter, wired and tested

CAR

CT-600, 600 mHz scaler option, add



Here's a super looking, rugged and accurate auto clock, which is a snap to build and install. Clock movement is completely assembled—you only solder movement is completely assembled—you only solder 3 wires and 2 switches, takes about 15 minutes! Display is bright green with automatic brightness control photocell—assures you of a highly readable display, day or night Comes in a satin finish an-odized aluminum case which can be attached 5 different ways using 2 sided tape. Choice of silver, black or goid case (specify). DC-3 kit, 12 hour tormat \$22.95 DC-3 wired and tested \$29.95 110V AC adapter \$5.95

#### **Under dash** car clock

12: 24 hour clock in a beau-tiful plastic case features 6 jumbo RED LEDS, high accuracy (1min mo), easy 3 wire hookup, display blanks with Ignition, and super instructions. Optional dimmer automatically adjusts display to ambient light level DC-11 clock with mtg. bracket \$27.95 2.50

DM-1 dimmer adapter

#### PRESCALER

**FM WIRELESS MIKE KIT** 

preamp stage

COLOR ORGAN/MUSIC LIGHTS

See music come alive! 3 different lights flicker with music. One light for lows, one for the mid-range and one for the highs. Each channel individually adjustable and drives up to 300W Great for parties, band music, nite clubs and more. Complete kit. ML-1 \$7.95

A great attention getter which alter-nately flashes 2 jumbo LEDs. Use for name badges, buttons, warning panel lights, anything! Runs on 3 to 15 volt

LED BLINKY KIT

15 volts

Transmits up to 300' to any FM broadcast

FM-1 kit \$2.95

radio. uses any type of mike Runs on 3 to 9V Type RM-2 has added senve mike

Extend the range of your counter to 600 mHz Works with any counter Includes 2 Iransistor pre-amp to give super sens. typically 20 mv at 150 mHz. Specify + 10 pr + 100 ratio. PS-1B, 600 mHz prescaler \$59.95 PS-1BK, 600 mHz prescaler kit

Art

\$2.95

ramsey electronics

BOX 4072, ROCHESTER, N.Y. 14610

FM-2 kit \$4.95



1-122

#### **Ramsey's famous MINI-KITS** VIDEO MODULATOR KIT

# Converts any TV to video monitor Super stable, tunable over ch. 4-6. Runs on 5-15V. accepts std. video signal. Best unit on the market! Complete kit, VD-1 \$6.95

## TONE DECODER

A complete tone decoder on a single PC board Features 400-5000 Hz adjustable range via 20 turn pot voltage regulation 567 IC Useful tortouch-tone decoding; tone burst detection, FSK etc Can aleo he used as a stable tone eff. also be used as a stable tone en-Complete kit TD-1 \$5.95

# WHISPER LIGHT KIT

An interesting kit small mike picks up sounds and converts them to light. The fouder the sound the brighter the light. Completely selfcontained, includes mike, runs on 110VAC, controls up to 300 watts plete kit. WL-1 \$6.95

## Assembled, tested units, add

#### CALENDAR ALARM CLOCK

The clock that's got if all, 6-5" LEDs, 12-24 hour, snooze, 24 hour, alarm, 4 year calendar, battery backup, and lots more. The super 7001 chip is used Size 5x4x2 inches Complete kit, less case (not available) \$34.95

DC-9

#### 30 Watt 2 mtr PWR AMP

Simple Class C power amp features 8 times power gain 1 W in for 8 out, 2 in for 15 out, 4 W in for 30 out, Max. output of 35 W, incredible value, complete with all parts, less case and T-R relay PA-1, 30 W pwr amp kit \$22.95 TR-1, RF sensed T-R relay kit 6 95

> SUPER SLEUTH JA A super sensitive an

#### A super sensitive am-plifier which will pick great for monitoring baby s room or as general purpose amplifier Full 2 W rms output runs on 6 to 15 volts. uses 8-45 ohm speaker. Complete kit, BN-9 \$5.95

POWER SUPPLY KIT

Complete triple regu-lated power supply pro-vides variable 6 to 18 volts at 200 ma and + 5V at 1 Amp Excellent load regu 244 Amp Excellent load regulation, good filtering and small size Less transformers, requires 6 3V (# 1 A load regulation and 24 VCT Complete kit, PS-3LT \$6.95

SIREN KIT

Produces upward and downward wail characteristic of a police siren 5 W peak audio output, runs on 3-15 volts, uses 3-45 ohm speaker Complete kit. SM-3 \$2.94

PHONE ORDERS CALL (716) 271-6487



minz Power: 110 VAC 5 Watts or 12 vDC (+ 400 ma Size: 6" x 4" x 2", high quality aluminum case, 2 lbs ICS: 13 units, all socketad

tional audio quality by means of its built in electret mike. Klt includes case, mike, on-off switch, antenna. battery and super instructions. This is the finest unit available \$12.95 EM-3 kit

FM-3 wired and tested

mHz

12/52.00

10/\$2.00

\$149.95 189.95

13.95

14 95

6.95

60.00

## CLOCK KITS

\$14.95 12.95

16.95

our Best Seller your Best Deal

Try your hand at building the linest lo	
clock on the market. Its satin finish and	
aluminum case looks great anywhere, while s	SIX 4"
LED digits provide a highly readable display. Th	his is a
complete kil, no extras needed, and it only tak	
hours to assemble Your choice of case of	
silver, gold, bronze, black, blue (specify).	
Clock kit, 12/24 hour, DC-5	522.95
Clock with 10 min. ID timer, 12/24 hour.	
DC-10	27.95
Alarm clock, 12 hour only: DC-8	24.95
12V DC car clock, DC-7	27.95
For wired and tested clocks add \$10,00 to kit	Drice

#### Hard to find PARTS

LINEAR ICS		REGULATORS	
301	\$ 35	78MG	\$1-25
324	1.50	723	.50
380	1 25	309K	85
380-8		7805	.85
555	.45	78L05 (1995)	25
556	.85	7905	1 25
566	1.15	7812	85
567	1.25	79 t 2	1 25
1458	.50-	7815	85
3900	.50	TTLICS	
CMOS ICs		74500	35
4011	20	7.447	65
4013	35	7475	.50
4046	1 85	7490	50
4049	40	74196TI	1.35
4518	1 25	SPECIAL ICs	
5369	1 75	11C90	13.50
TRANSISTORS		10116	1 25
2N3904 type	10/1 00	4514	2 00
2N3906 type.	10/1 00	5314	2 95
NPN 30W Par	3/1 00	5375AB	2 95
PNP 30W Pwr	3/1 00	7001	6 50
2N3055	.60	4059 + N	9 00
UJT 2N2646 typ	e 3/2.00	7208	17 95
FET MPF102 typ	e 3/2 00	LEDs	
UMF 2N5179 1yp	e 3/2.00	Jumbo red	8/1.00
MRF-238 RF	11.95	Jumbo green	6/1 00
SOCKETS		Jumbo yellow	6/1 00
8 pin	10/2.00	Mini red	8/1.00
14 pin	10/2.00	Micro red	8/1 00
16 pin	10/2.00	BiPolar	75
24 pin	4/2.00	FERRITE BEADS	
28 pin	4/2 002	With info, specs	15/1 00
40 pin	3/2 00	6 hole balun	5/1.00

TERM5: Satisfaction guaranteed or money retunded. COD, add \$1.50. Minimum order, 56.00. Orders under \$10.00, add \$.75. Add 5% for postage, insurance, handling. Over-seas, add 15%. NY residents, add 7% tax



## SpeakerGuts.

The absolute latest in advanced speaker techno-logy. Wave Aperature The Drivers, the Patented Nestrovic Woofer System." raw



their excellence. Horns, crossovers, subwooters, woofers, midranges, horn and dome tweeters. Over 30 in all. Build your own speaker system and we'll provide top quality speakers and design information. Send for FREE 48 page color catalog from the largest, most experienced speaker kit manufacturer in the world. DONT DELAY. Write today!



#### **BUSINESS OPPORTUNITIES**

MECHANICALLY inclined individuals desiring ownership of Small Electronics Manufacturing Business-without Investment, Write: BUSINESS-ES, 92-R, Brighton 11th, Brooklyn, NY 11235

LEARN to repair PLL or crystal synthesis CB for profit, 30 PLL's covered. Send \$12.95 for instruc-tion book. A.P. SYSTEMS, PO Box 488, Milford, PA 18337, Dept. RE

BECOME a consultant. Earn \$20-\$40/hr being in business for yourself. For detailed information on starting or expanding your own engineering con-sulting business write DR. S. TOMCZAK, ST & A, Dept RA, Box 480530, Los Angeles, CA 90048.

#### WANTED

LINEAR amplifier for SSB 1.6 to 23 MHz. Write: FERRO, 2933 Vauxhall, Vauxhall, NJ 07088



**PLANS & KITS** 

SCANNER users—build many useful accesso-ries. Free kit catalog. CAPRI ELECTRONICS, Route 1R, Canon, GA 30520

PRINTED circuit boards from your sketch or artwork. Affordable prices. Also fun kit projects. Free details. DANOCINTHS INC., Box 261, Westland, MI 48185

CONSTRUCTION plans for profitable business ideas. Catalog \$1.00. GARLING, 438 N. Garfield Street, Lombard, IL 60148

BUILD flyback and transformer checker under five dollars, Plans \$2.00, JACK ROSS, 6206 N. Francisco, Chicago, IL 60659

PROJECTION TV . . Convert your TV to project 7 foot picture. Results equal to \$2,500 projector. Total cost less than \$20.00. Plans & lens \$16.00. Illustrated information free. MACRICOMA, Washington Crossing, PA 18977

BUILD your own speaker system. Write for free catalogue. McGEE RADIO, 1901 McGee St., Kansas City, MO 64108

#### **GRAPHIC EQUALIZER**

TWELVE bands/channel \$100 kit still available: See May 1978 cover story. Complete instruc-tions, reprint review \$2.50. Free information. SYMMETRIC SOUND SYSTEMS, 1608 South Douglas, Loveland, CO 80537

#### **EDUCATION & INSTRUCTION**

TELEPHONE bugged? Don't be Watergated! Countermeasures brochure \$1.00. NEGEYE LA-BORATORIES, Box 547-RE, Pennsboro, WV 26415

UNIVERSITY degrees by mail! Bachelors, Masters, Ph'D's . . . Free revealing details. COUN-SELING, Box 317-RE9, Tustin, CA 92680

UNDERSTAND digital electronics. Programmed UNDERSTAND digital directionics, risg, learning courses, Design of Digital Systems, 6 volumes, only \$19.95, Digital Computer Logic, 4 volumes, \$14.95, Both \$29.95, Free details, GFM INDUSTRIES, Bidg. 7-20, 203 Loudon Road, Concord, NH 03301

EARN high school diploma, spare time. Collegerecognized. Credits given for previous courses, job experience. Low tultion. Exams repeated free. Individual counseling. State registered. CAM-BRIDGE ACADEMY, Dept. RE-2, 409 E. Osceola, Stuart, FL 33494, Toll-free 1-800-327-8103.

#### MECHANICALLY INCLINED INDIVIDUALS

Assemble electronic devices in your home. Invest ment, knowledge, or experience not necessary. Get started in spare time. Above average profits. \$300 \$600/wk. possible. Sales handled by others. Write for free details


ELECTRONIC DEVELOPMENT LAB Box 1560R, Pinellas Park, FL 33565

OUR PHO LS ON Record incoming and outgoing calls automatically with this all solid state unit connected to your telephone jack and tape recorder. Starts recording when phone is lifted. Stops when you hang up, making a permanent record. Easily installed. No extra monthly phone charges. FCC APPROVED 4 x 1-3/4 x 3/4 \$24.50<sup>4</sup> VOICE ACTIVATED 4 CONTROL SWITCH Self contained solid state. Excellent adjustable sensitivity. Recorder activated by voices other sounds. Uses recorder mike cr remote mike Great for home, business, etc. 524 951 MICRO MINI MIKE FCC APPROVED Among world's smallest, solid state, self contained WIRELESS MIKE. Mercury Bat, furn. Picks up most MINELESS MINE. MERCUTY Dat. Tuln. PICK up most sounds and transmits without wires up to 300 ft. thru FM Radio. Tyneable. Use as mike, ampf., alarm & alert system, baby silter, hot I ne, etc. I\*Plus S1.00 PAg. & Hdg.1 Money back guarantee. California residents add tax, Free data. Mail order. Visa, M/C, Cod to k. Quantity are data. Mail order. Visa, M/C, Cod to k. Quantity discount available. AMC Sales, Dept. 19, 9335 Lubec St., Box 928, Downey, Calif 90241 Phone (213) 869-8519

\$18.95\*

ECTRONICS RADIO-EL

When in our area, northeastern Mass, or southern N.H CIRCLE 9 ON FREE INFORMATION CARD

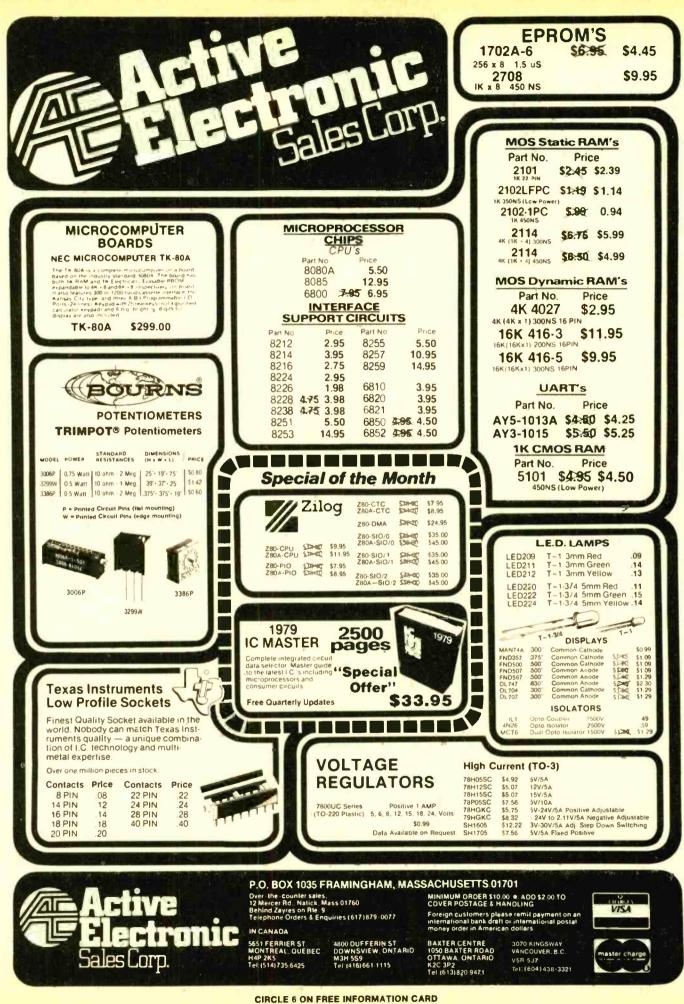

SEPTEMBER 1979

#### DIGITAL AUTO SECURITY SYSTEM

4 DIGITS PERSONAL CODE!!

proximity triggered

voltage triggered

mechanically triggered

#### **3-WAY PROTECTION!**

This alarm protects you and itself! Entering protected area will set it off, sounding your car horn or siren you add. Any change in voltage will also trigger the alarm into action. If cables within passenger compartment are cut, the unit protects itself by sounding the alarm.

SPECIAL \$19.95

ALL UNITS FACTORY ASSEMBLED AND TESTE

#### THE MOST ADVANCED TIMEPIECE OF ITS KIND IN THE WORLD!

LCD Quartz Alarm Chronograph with calendar and dual time zone!| Watch is the same as Seiko but you pay a lot more for the name! Features



- Chronograph counts up to 12 hrs., 59 mins. 59.9 sec. Precision of chrono up to
- 1/10 sec indicated by 10 moving arrows!!
- moving arrows!! Lap time (with chrono run-ning uninterrupied) Time displays by LCD for hour, min, sec, day, date of the week and AM/PM. Calendar gives out date-day Dual time zone for any two cities of the world at your.
- own choice.
- \* With light switch to allow you to see the time in the dark

\$55.50






play panell! This Mark III LED level indicator is a play panell! This Mark III LED level indicator is a new design PC board with an arc-shape 4 colors LED display (change color from red, yellow, green and the peak output indicated by rose red). The power range is very large, from -30dB to +5dB. The Mark III indicator is applicable to 1 wait – 200 watts amplifier operating voltage is 3V – 9V DC at max 400 MA. The circuit uses 10 LEDs per channel. It is very easy to connect to the am-plifier. Just hook up with the speaker output INK KLT ECORM \$18,50. IN KIT FORM \$18.50





 
densor microphone to allow you to have a better response in sound pick-up. Transmits up to 350 ft.! With an LED indicator to signal the unit is on



#### 100 W CLASS A POWER AMP KIT

Dynamic Bias Class "A" circuit design makes this unit unique in its class. Crystal clear, 100 watts power output will satisfy the most picky fans. A perfect combination with the TA-1020 low T.I.M. stereo pre-amp.

Specifications:

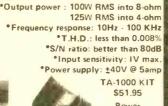

Power transformer \$15.00 each

#### LOW TIM DC STEREO PRE-AMP KIT TA-10 20

Incorporates brand-new D.C. design that gives a frequency response from 0Hz - 100KHz ±0.5dB! Added features like tone defeat and loudness control let you tailor your own fre-quency response. Independent I.C. regulated power supplies to eliminate power fluctuation! power supplies to eliminate power indications:  $0.1 \times 10.1$  km s = 0.05%  $^{\circ}$  Frequency response: DC to 100KHz  $\pm 0.5$ dB  $^{\circ}$  RIAA deviation:  $\pm 0.2$ dB  $^{\circ}$  S/N ratio: better than 700B  $^{\circ}$  Sensitivity: Phono 2MV 47K/Aux. 100MV 100K  $^{\circ}$ Output level: 1.3V \*Max output: 15V \*Tone control: bass ±10dB @ 50Hz/treble ±10dB @ 15Hz \*Power supply: ±24 D.C. @ 0.5A Kit comes with regulated power supply, all you need is a 48V C.T. transformer @ 0.5A ONLY \$44.50 X'FORMER

#### PROFESSIONAL FM WIRELESS MICROPHONE

TECT model WEM-16 is a factory assembled FM wireless microphonep powered by an AA size battery. Transmits in the range of 88-108MHz with 3 transistor circuits and an omni-directional electric conden-ser. Element built-in plastic tube type case; mike is 6%" long. With a standard FM radio, can be heard anywhere on a one-acre lot; sound quality was judged very good. \$16.50 -----

> sanua SPECIFICATIONS Hanges DC Voltage COMPACT -LIGHTWEIGHT -DC Current ULTRA-SLIM BATTERY CHECKER AC Voltage AC Current LED TESTER T-55D (w/o temp probe) S44 50 T-55THD (temp probe)

3½ digits display

oad Voltag \$66.50

HICKOK LX 303

DIGITAL LCD MULTIMETER

Decibels Batt Check LED Check (Available)

#### 250 mA (500 mV drop) 15V, 150V, 500V (9k Ω /V) 5 mA, 6A (2V and 55mV dro 10k Ω 100k Ω 1MΩ 5λ45 nan calbin] 00Ω 1kΩ 10kΩ 50kΩ (mid scele) 30mA 3mA 300mA 3V 3V 3V

-10 to +55d8 0.9 to 1.5V (10Ω toed) C and D: to +200 C IR.

150mV, 500mV, 1.5V, 5V, 15V, 50V, 250V, 1kV [A] 20k  $\Omega$  /V] 25kV \*Using HV probel 50µA, 25mA, 25mA, 250mA (1500mV 4 real Dimensions: 146 ± 97 ± 28 mm thick 240g

## **MARK IV 18 STEPS** LED POWER LEVEL

12.5% task. 12.5% task. 12.5% task. 12.5% task. Swer on 1.5V range: 15% task. Swer above 15V range: 13.5% task.

polied with BAtteries 1.5V (UM-3 or R61=2 500mA 250V

Transformer \$1.75

wer on 1.5v range: ±5% f.s.d. mperature: ±3% of arc

500mA 250V obe (T-55THD only)

**INDICATOR KIT** This new stereo level indicator kit consists of 36 4-color LED (18 per channel) to indicate the sound level output of your amplifier from  $36\mathrm{dB}$   $\sim$   $+3\mathrm{dB}$ . Comes with a well designed silk screen printed plastic panel and has a selector switch to allow floating or gradual output indicating. Power supply Is 6  $\sim$  12V D.C. with THG on board input sensitivity controls. This unit can work with any amplifier from

1W to 200W! Kit includes 70 pcs. driver transistors, 36 pcs. matched 4-color LED, all other electronic components, PC board and front panel.



S 8 50 ea


#### **30W + 30W STEREO HYBRID AMPLIFIER KIT**

It works in 12V D.C. as well! Kit includes 1 PC SANYO STK-043 stereo power amp. IC LM 1458 as pre amp, all other electronic parts, PC Board, all control pots and special heat sink for hybrid. Power transformer not included. It produces ultra hi-fi output up to 60 watts (30 watts per channel) yet gives out less than 0.1% total harmonic distortion between 100Mz \$32.50 PER KIT and 10KHz POWER TRANSFORMER \$6.50 EACH

**CIRCLE 11 ON FREE INFORMATION CARD** 

Power transformer



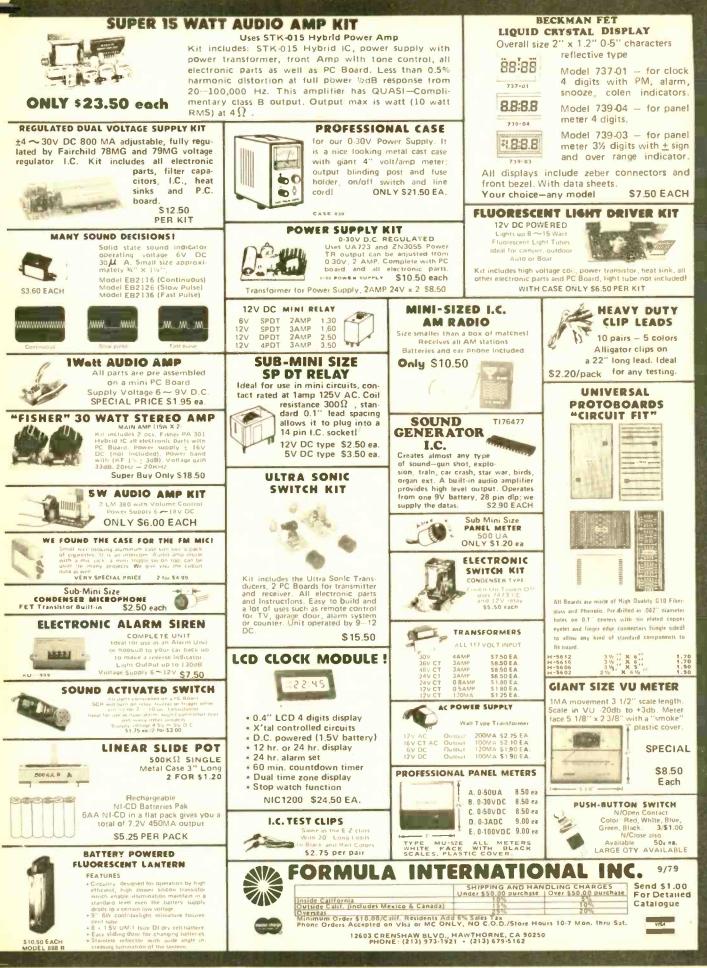

CIRCLE 12 ON FREE INFORMATION CARD

99

### **IS RADIO** CONTROL **YOUR HOBBY?**

Then here's the perfect opportunity to make your hobby your job. Mattel, the world's foremost toy manufacturer, is seeking enterprising people with experience in radio control systems, including linear experience up to 100Mhz. Selected applicants will work with the most advanced technology in radio control today

Degree in Electronics or Electrical Engineering is preferred. Start putting your skills and knowledge to work in an exciting new job - send us a resume or letter detailing your background and capabilities to:

**Dennis Marchand** Dept. RE MATTEL ELECTRONICS

5150 Rosecrans Ave. Hawthorne, CA 90250 Equal Opportunity Employer

...MORE SALE HOUSE MARKED HOUSE MARKED DARLINGTON DARLINGTON POWER TRANSISTOR Π 15 AMPS 60 VOLTS 150 WATTS SIMILAR TO \$1.50 MJ4030 PNP MJ4036 NPN each Part of preparing for the Fall is making SPECIFY 5 AMPS 65 WATTS room for a bunch of new products, so we're BO VOLTS SIMILAR TO TIP 121NPN 11P 126 PNP NPN Specily NPN clearing out some of our inventory at re-PNP OF PNP duced prices. Limited quantities 75' each HEAVY DUTY MA1003 CLOCK 12 VOLT RELAY \$13.20 west clock module. Internal use, fluorescent readouts that don't out, simple assembly (just add 2 time-set switches and + 12V DC), much more. Perfect for car, mobile use (documentation included). Match-ing asse with mounting hardware & optical filter add \$5.95. 16K MEMORY EXPA-CHIP SET Clear Plostic Enclosed
 S PD1 INDOOR-OUTDOOR 12 Amp Contacts PAGING \$3.00 each HORNS IO MEG POTS . 8" SIZE/30 WAT ndard 1/4 Wall Size \$24.95 • 3/8" Long Shaft 6" SIZE/15 WATT: \$17.95 • 5" SIZE/5 WATTS \$6.50 4 for \$1.00 SPRITE COOLING FAN 16K MEMORY EXPANSION CHIP SET 5499 \$87.20 20% off one of our all-time best sellers. For Radio Shack-80, Exidy Sorcerer, Apple computers. 250 ns access time, low power parts, DIP shunts included, 1 year limited warranty, and easy-to follow Instructions that make memory expansion a snap. WE BREAK THE SPECIAL SALE Used Bull Fully Tested 1000 MFD 16VDC • 115 vac 9 walts • 3 1/8 \* 3 1/8 • 1 5/8 \$8,00 each 4 lor \$1 00 P.N.P. GER. TRANSISTOR 2N1038 TO - 39 40 yolls 8 amos 20 watts MAGNETICALLY ACTUATED SWITCH \$1 00 each ALLIED CONTROL N D W/Magnet Engaged **1c/BYTE BARRIEK!!** We're offering low power 21L02 1K static memory chips, guaranteed to run with any 2 MHz system, at the very low price of 10/59.90...that's under to per byte! Stock up now, we can't predict Hole Miniature P.C. Belay MMPC - 4000 - 12VDC Magnet Included 10P1 12 VDC (m 960 MW 140 phms \$2.50 each 75¢ each ALCO MALLORY MINIATURE COMPUTER SWITCH GRADE narts available for sale 150,000 MFD 15VDC · 6 amps (a 125 volts 3" Dia 5 High 18V Surge \$3,50 each \$1.15 each order desk at (415) 562-0636 COD OK with s ALL ELECTRONICS CORP. SEND FOR OUR FREE FLIER 905 S. Vermont Ave. Quantities Lin Los Angeles. CA 90006 Min Order \$5.00 · Add \$150 Shipping USA (213) 380-8000 Calif. Res. Add 6%
 Same Day Shipping with Store & Warehouse Hours FREE FLYER: We have what you're looking for, end it's worth your while to send for our flyer. Just give us your name and ad dress, we'll take care of the rest. For 1st class mail, include 4 to 9 AM 5 PM Cert Check or M/C Monday thru Friday

-

**CIRCLE 48 ON FREE INFORMATION CARD** 

**CIRCLE 42 ON FREE INFORMATION CARD** 

Full Wave Bridges DIP SOCKETS TRANSISTOR SPECIALS PRINTED CIRCUIT BOARD C/MOS (DIODE CLAMPED \$ 1.95 \$ .75 \$ 1.00 \$ .75 \$ 1.00 \$ .75 \$ 1.00 \$ .75 \$ 1.00 \$ 1.00 8 PIN .17 24 PIN .35 14 PIN .20 28 PIN .40 ZA BA 25A MRF-8004 a CB RF Transistor NPN .4 35 00 27 27 30 27 27 30 27 90 75 2N1546 PNP GE TO-3 16 PIN 22 40 PIN .60 45 45 22 40 1.20 1.00 45 90 ,45 7 WATTLD-65 LASER DIODE IR \$8.95 1.04 1.65 3.30 18 PIN .25 95 95 97 85 85 .75 45 .10 45 2N3137 NPN SI RF .55 SANKEN AUDIO POWER AMPS 2N3919 NPN SI TO-3 RF 2N1420 NPN SI TO 5 2N3767 NPN SI TO 66 12646 UJT 50 GER DIODES . 3/\$ 1.00 \$ 70 5 · S 1 00 5 · S 1 00 2N3767 NPN SI TO 66 2N2222 NPN SI TO 18 ,50 1.30 50 95 MINIATURE MULTI-TURN TRIM POTS 100, 1K, 2K, 5K, 10K, 20K, 50K, 200K, 1Meg, 2Meg, 5,75 each 3/52 00 TANTULUM CAPACITORS 2N3904 NPN Si TO 92 2N3906 PNP Si TO 92 2N5296 NPN Si TO 92 6/\$ 6/\$ 1.00 .22UF 35V 5/\$1 00 .47UF 35V 5/\$1 00 .68UF 35V 5/\$1.00 6 8UI 
 .22UF
 35V
 5/51
 00
 0BUF
 35V
 4/51.00

 .47UF
 35V
 5/51
 00
 10UF
 10V
 5.25

 .68UF
 35V
 5/51
 00
 10UF
 10V
 5.25

 .68UF
 35V
 5/40
 22UF
 25.40
 5.40

 .1UF
 35V
 5/10.00
 15UF
 35V
 5.40

 .22UF
 25.40
 30UF
 6V
 5.40

 .23UF
 20V
 5/61.00
 30UF
 6V
 5/51.00

 .3.0F
 20V
 4/51.00
 150UF
 15V
 5.90

 .3.0F
 20V
 5/51.00
 58UF
 15V
 5.90
 watt Infra Red Pulse 1 SG 2006 equiv et included) RIPAX PC BOARD 5'S 1 00 4/\$ 1.00 
 PTODUC ISDRC Inter Influence
 321-33

 IPRAY PC BOARD
 321-33

 IPRAY PC BOARD
 \$12,94

 IPRAY PC BOARD
 \$12,94

 Inew Protoryphing is a ni density all "states"
 \$12,94

 Inew Protoryphing is a ni density all "states"
 \$12,94

 Is 10
 IPRAY PC BOARD
 \$12,94

 Is 10
 IPRO PHOTOLSOL
 \$12,94

 In dig Connector with 156" specing
 buses
 \$50

 PF 100 PHOTO TRANS
 \$50

 REO, YELLOW, GREEN
 \$75

 LARGE LED's. 2"
 .6/51,00

 TIL-118 0PTO-ISOLATOR
 \$80


 I WATT ZENERS
 3,3,4,7,51,56,91,10


 10,12,15,18 or 220
 .8/51,00

 MCM 6571A,7 x 9 cheracter gen
 \$10,75

 MUYERSAL 4xee MEMORP BOARD KIT
 \$10,75
 MPSA 13 NPN SI TTL IC SERIES CIRCUIT 1 05 1 05 1 41 87 82 82 1 20 82 1 20 82 1 27 1 42 1 80 1 47 8252) 875129 -A 15 1013 VART TR 1 6028 -RT03C TELEDYNE 75 75 .20 95 10 .70 AVAILABILITY & PRICING 370 377 380 382 UNIVERSAL 4Kx8 MEMORY BOARD KIT \$69.95 32-2102 1 fully buffared, 16 ac 386 87380 2.25 8834 2.25 8830 2.95 8837 2.25 F86K 8130 - 295 Silicon Power Rectifien 565 FOR 566 567 703 733 6 144 8 FLAT COLOR CODED MH2 8 000 MH 40 cont MH2 20.000 MH DATA CASSETTE ALAS TINGAN headers 1110 2 50 95 50 65 3 90 1 95 206-8 eight position dip switch 206-4 four position dip switch HT ACTIVATED SCR's to 18, 200 16/\$1 00, \$5.0 CLOCK CHIP 1458 RS232 DB 25P male CONNECTORS DB 25S female SILICON SOLAR CELLS NO 30 WIRE WRAP WIRE SINGLE \$10.0 TRIACS REGULATORS 340K - 12, 15 or 24 V. . . . \$ 1.50 340T - 5, 6, 8, 12 15, 18 or 24 V \$ 1.40 78 MG \$ . . . \$ 1.35 ND 359 C.C. 4" \$ .60 LED READOUTS 323K - 5V 3A \$ 5.75 \$ 1.60 35 A 1.5A DL-704 C.A DL 747 C.A HP3400 .8" MTA 44 48 .\$ .50 206 DPD1 723 3201 MTA 200 P-DPDT CENTER OFF MSD 206 P-DPDT CENTER OFF LEVER SWITCH 1.85 s 20 HP3405 8 5, 12, or 15 V 1.85 SOLID STATE SALES Money Order WE SHIP OVER 95% OF OUR ORDERS THE Send 25¢ for our catalog featuring Transistors and Rectifiers 145 Hampshire St., Cambridge, Mass. PO. BOX 740 DAY WE RECEIVE THEM SOMERVILLE, MASS. 02143 TEL. (617) 547-7053

**CIRCLE 28 ON FREE INFORMATION CARD** 

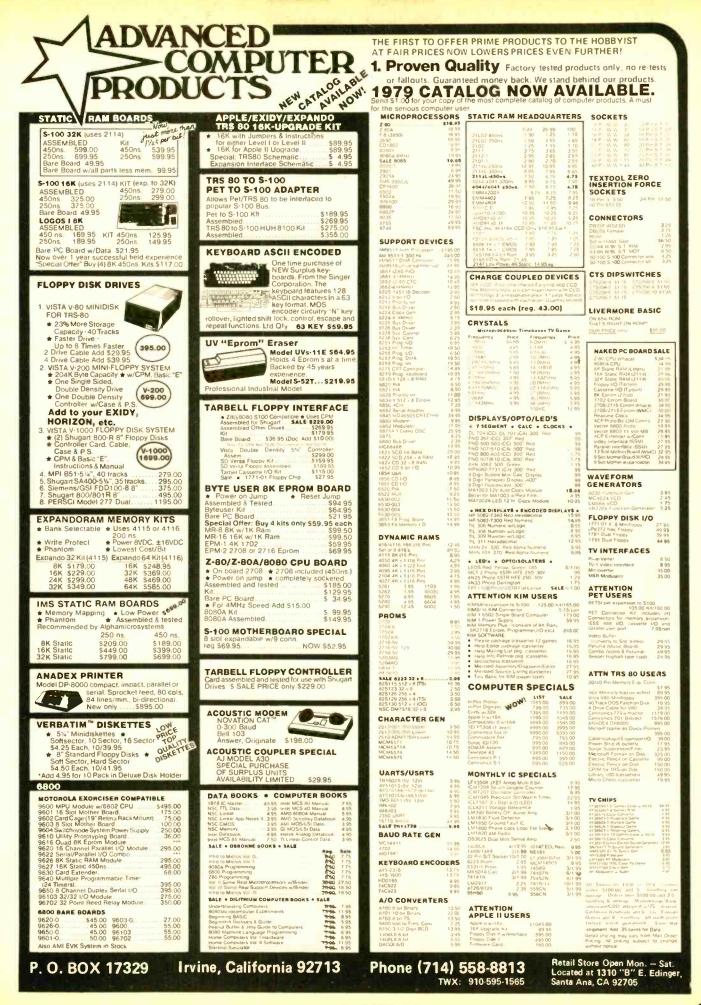

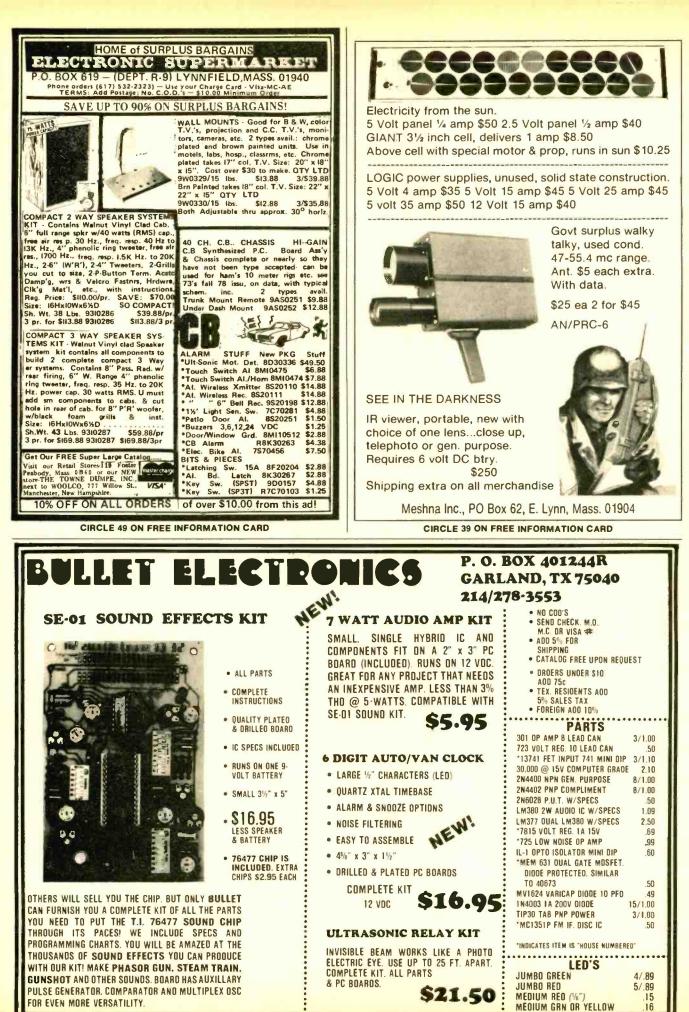

102

#### AVAILABLE NOW! AVAILABLE NOW! ONLYS3.95 Add \$1.00 for shipping JAPANESE TRANSISTOR SUBSTITUTION MANUAL

An involuable lapanese to lapanese substrution guide for approximately 3000 transitions \* Covers the 25A 25D 25C and 25D series \* Introduction includes a guide to understanding Japanese Mansistons \* A 90 page 812 by 11 solt

cover book

## PARTS PROCUREMENT PROBLEMS

FUJI-SVEA Has the Largest Inventory of Original Japanese Parts Anywhere







**CIRCLE 22 ON FREE INFORMATION CARD** 

	7400 TTL	-	EVOLUTINO NEW VITO	TELEPHONE/KEYBOARD CHIPS
( Numar	SN7470N 29	Napper 1	EXCITING NEW KITS Digital	AY-5-9100 Push Button Telephone Dialier \$14.95 AY-5-9200 Repertory Dialier 14.95
SN7400N 16 SN7401N 18 SN7402N 18	SN7472N .29 SN7473N 35 SN7474N 35 SN7474N 35 SN7475N .49	SN74160N 89 SN74161N 89 SN74162N 1 95	ENCODER KIT	AY-5-9500         CMOS Clock Generator         4.95           AY-5-2376         Keyboard Encoder (88 keys)         14.95           HD0165         Keyboard Encoder (16 keys)         7.95
SN7403N 18 SN7404N 18 SN7405N .20	SN7476N 35 SN7479N 5.00 SN7480N .50	SN74163N 89 SN74164N 89 SN74165N 89	FATURES     Full 8 Di lattered puput for merze- processor use     Juster 4**     Susser 4**     Susser 6 Deha kays with one beng bi-	74C922 Keyboard Encoder (16 keys) 5.95
SN7405N 29 SN7406N 29 SN7407N 29 SN7408N 20	SN7482N .99 SN7483N 59 SN7485N 79	5N74166N 1 25 5N74167N 1 95	3 User Deline kilys with one being bi- stable operation     0 Debunce oricetti provided for all 19	ICM7045 CM05 Precision Timer 24.95 ICM7205 CM05 LED Stopwatch/Timer 19.95 ICM7207 Oscillator Controller 7.50
SN7409N .20 SN7410N 18	SN7486N 35 SN7489N 1.75	SN74172N 6 00 SN7+173N 1 25	LED readout to verify entires - Easy interfacing with standard 16 pin	ICM7208 Seven Decade Counter 19.95 ICM7209 Clock Generator 6.95
SN7411N 25 SN7412N .25 SN7413N .40	SN7490N .45 SN7491N .59 SN7492N .43	SN74174N 89 SN74175N 79 SN74176N 79	Connector     Only +5VDC required for operations     door/outdoor or dual monitoring	NMOS READ ONLY MEMORIES           MCM6571         128 X 9 X 7 ASCII Shifted with Greek         13.50           MCM6574         128 X 9 X 7 Math Symbol & Pictures         13.50
SN7414N .70 SN7416N 25 SN7417N 25	SN7493N .43 SN7494N 65 SN7495N 65	SN74177N 79 SN74179N 195 SN74180N 79	Babos: 40°E to 100°C to 100°C	MCM6575 128 X 9 X 7 Alphanumeric Control 13.50 Character Generator
SN7420N .20 SN7421N 29 SN 422N 39	SN7496N .65 SN7497N 3.00 SN74100N 89	SN74181N 1 95 SN74182N 79 SN74184N 1 95	In a doo andoo and	MISCELLANEOUS TL074CN Quad Low Noise bi-let Dp Amp 2.49 TL494CN Swritching Regulator 4.49
SN7423N 25 SN7425N 29 SN 426N 29	SN74107N 35 SN74109N 59 SN74116N 1 95	SN74185N 1 95 SN74186N 9 95 SN74188N 3 95	seth LED readouts. Also included is a key entry strobe JE600\$59,95 JE300\$39,95	TL496CP         Single Switching Regulator         1.75           11C90         Divide 10/11 Prescaler         19.95           95H90         HI-Speed Divide 10/11 Prescaler         11.95
S 7427N 25 SN7429N 39 S 7430N 20	SN74121N .35 SN74122N .39 SN74123N .49	SN74190N 1 25 SN74191N 1 25 SN74192N 79	Hexadecimal Keypad only	4N33 Photo-Darlington Obto-Isolator 3.95 MK50240 Top Octave Fred, Generator 17.50 DS0026CH 5Min 2-phase MOS clock driver 3.75
SN7432N 25 SN7437N 25 SN7438N 25	SN74125N 49 SN74126N 49 SN74132N .75	SN74193N 79 SN74194N 89 SN74195N 69	xC556R red 5/\$1 .125 dia. LIQUID CRYSTAL DISPLAY CLASS II	TIL308 .27 red num. display winteg. logic chip 10.50 MM5320 4% Digit OPM Logic Biock (Special) 3.95
S 7439N .25 SH 7440N .20 S 7441N 89	SN74136N .75 SN74141N .79 SN74142N 2.95	SN74196N 89 SN7+197N 89 SN74196N 149	XC556G green 4/31 XC209R red 5/31 FIELD EFFECT XC556Y yellow 4/31 XC209G green 4/31	LD110/111 3½ Digit A/D Converter Set 25.00/set
SN7442N .49 SN7443N .75 SN7444N .75	SN74143N 2.95 SN74144N 2.95 SN74145N 79	SN74199N 1 49 SN74S200 4 95 SN74251N 1 79	.200° dia. XC226 red 5.\$1 XC5268 red 5.\$1	Photo Transistor Opto-Isolator (Same as MCL 2 or 4N25) Generales Complex Sounds
SN7445N .75 SN7446N .69 SN7447N 59	SN74147N 1 95 SN74148N 1 29 SN74150N	SN74279N 79 SN74283N 2.25 SN74284N 3.95	XC22Y yellow 4/\$1 XC526Y yellow 4/\$1 .170° dla. XC526C clear 4/\$1 4 DIGIT5" CHARACTERS	2/99¢ Low Power - Programmable 3.95 each
SN7448N 79 SN7450N 20 SN7451N 20	SN74151N 59 SN74152N 59 SN74153N 59	SN74285N 3 95 SN74365N 69 SN74366N 69	.085" dia	TV GAME CHIP AND CRYSTAL AY-3-8500-1 and 2 01 MHZ Crystal (Chip & Crystal includes score display, 6 games and select angles, etc. 7,95/set
SN7453N _20 SN7454N 20 SN7459A 25	SN74153N 59 SN74154N 99 SN74155N 79 SN74155N 79	SN74367N 69 SN74367N 69 SN74368N 69 SN74390N 1 95	INFRA-RED LED RC111G green 4751 1/8/rL1/Ark1/16/Tat //6/Tat XC111C clear 4/51 1/8/s1/Ark1/16/Tat XC111C clear 4/51	XR205 S8 40 FXAR XR2242CP 1.50 XR210 4.40 FXAR XR2264 4.25
SN7459A 25 SN7460N .20	SN74156N .79 SN74157N .65	SN74393N 195 SN74393N 195	DISPLAY LEDS	YR215 4 40 XR2556 3 20
CD4000 23 CD4001 23 CD4002 23	C/MOS	C04070 55 C04071 23 CD4072 49	MAN 1         Common Anode-red         270         2.95         MAN 6730         Common Anode-red ± 1         560         .99           MAN 2         5.x 7 Dot Matma-red         .300         4.95         MAN 6740         Common Cathode-red-D.D         .560         .99	XR555 .39 XR1800 3,20 XR4136 1.25 XR556 .99 XR2206 4,40 XR4151 2,85 XR567CP .99 XR2207 3,85 XR4194 4,95
CD4006 1 19 CD4007 .25 CD4009 .49	CD4029 1.19 CD4030 49 CD4035 99	CD4076 1 39 CD4081 23 CD4082 23	MAN         Common Cathode-red         125         .25         MAN 6730         Common Cathode-red         1560         99           MAN 4         Common Cathode-red         187         1.95         MAN 6760         Common Andde-red         560         99           MAN 7G         Common Andde-refen         300         1.25         MAN 6780         Common Andde-refen         560         99           MAN 7G         Common Andde-refen         300         1.25         MAN 6780         Common Andde-refen         300         99         U/D10         Common Andde-refen	XR567CT 1.25 XR2208 5.20 XR4202 3.60 XR1310P 1.30 XR2209 1.75 XR4212 2.05 XR1468CN 3.85 XR2211 5.25 XR4558 .75
CD4010 49 CD4011 23 CD4012 25	CD4040 1.19 CD4041 1.25 CD4042 99	CD4093 99 CD4098 2.49 MC14409 14.95	MAN /? Common Ander retow	XR1488 1.39 XR2212 4.35 XR4739 1.15 XR1489 1.39 XR2240 3.45 XR4741 1.47
CD4013 .39 CD4014 139 CD4015 119	CD4043 89 CD4044 89 CD4046 79	MC14410 14 95 MC14411 14 95 MC14419 4 95	Max         B2         Common Anade-real         Sol         4.9         DL724         Common Anade-real         600         1.25           MAN 84         Common Anade-real         6.00         .99         DL741         Common Anade-real         6.00         1.25           MAN 85/0         Common Anade-real         .30         .99         DL744         Common Anade-real         6.00         1.25           MAN 95/0         Common Anade-real         .30         .99         DL745         Common Anade-real         6.00         1.49           MAN 95/0         Common Anade-real         6.00         1.49         .30         .99         DL747         Common Anade-real         6.00         1.49	DIODES         TYPE         Vol.ts         W         PRICE           1%4002         100 Ptv 1 AMP         12/1 00         10/102         100 Ptv 1 AMP         12/1 00           1%745         3.3         400m         4/1.00         1%4004         400 Ptv 1 AMP         12/1 00
CD4016 49 CD4017 1 19 CD4018 .99	CD4047 2.50 CD4048 1.35 CD4049 .49	MC14433 19 95 MC14506 75 MC14507 99	MAN 3640         Common Camode orange         S00         99         DL249         Common Camode orange         500         1.49           MAN 4610         Common Camode orange         300         99         DL250         Common Camode red         600         1.49           MAN 4610         Common Camode red         300         99         DL250         Common Camode red         600         1.49           MAN 4640         common Camode red         300         99         DL250         Common Camode red         600         1.49           MAN 4640         common Camode red         300         39         DL238         Common Camode red         110         35.5	1N751 5.1 400m 4/1.00 1N4005 600 PIV 1 AMP 10/1 00 1N752 5.6 400m 4/1 00 1N4006 800 PIV 1 AMP 10/1 00
CD4019 .49 CD4020 1 19 CD4021 1 39	CD4050 49 CD4051 1,19 CD4053 1,19	MC14562 14 50 MC14583 3 50 CO4508 3 95	MAN 4710         Common Anode-red         100         39         FN070         Common Cathode         250         55           MAN 4730         Common Anode-red         400         99         FN0358         Common Cathode         35         59           MAN 4730         Common Anode-red         400         99         FN0358         Common Cathode         35         75	1N754 6.8 400m 4/1.00 1N3600 50 200m 6/1.00 1N757 9.0 400m 4/1.00 1N4148 75 10m 15/1.00
CD4022 1 19 CD4023 23 CD4024 79	CD4056 2 95 CD4059 9 95 CD4060 1 49	C04510 1 39 CD4511 1 29 CD4515 2 95	MAN 4810         Common Ander veillow         400         .99         FND533         Common Cathode (FND500)         500         .99           MAN 4810         Common Cathode (FND500)         S00         .99         FND507         Common Ander (FND500)         .500         .99           MAN 6610         Common Ander (FND500)         .500         .99         .502/7720         Common Ander (FND510)         .500         .99           MAN 6610         Common Ander (FND500)         .500         .99         .502/7720         Common Ander (FND510)         .500         .93	18959 8.2 400m 4/1.00 1N4305 75 25m 15/1.00 1N965 15 400m 4/1.00 1N4734 5.6 1w 28
CD4025 23 CD4026 2 25 CD4027 69	CD4066 79 CD4068 39 CD4069 45	CD4518 1 29 CD4520 1 29 CD4566 2 25	Max 6030         Common Andoe range 11         560         .99         H057-3400         Common Andoe range 13         560         210           MAX 6540         Common Andoe range 10         560         .99         H057-3400         Common Andoe range 10         800         210           MAX 6540         Common Cathode range 10         560         .99         H057-3403         Common Cathode red         800         210           MAX 6540         Common Cathode range 13         560         .99         H057-2300         4:         730         0         730         0         10         19         55	1M5232         5.6         500m         28         1M4735         6.2         1w         28           1M5234         6.2         500m         28         1M4736         6.8         1w         28           1M5235         6.8         500m         28         1M4738         8.2         1w         28
74C00 39 74C02 39	74C00	74C163 2 49	MAN 6660 Common Anode-orange 560 .99 5082-7302 4 # 7 Sgl Digit-LMDP .600 19 95	1N5236 7.5 500m 28 1N4742 12 1w 28
		740164 2 49	MAN 6680 Common Cathode-orange 560 .99 5082-7304 Overrange character (±1) 600 15.00	1N5242 12 500m 28 1N4744 15 1w 28 1N5245 15 500m 28 1N1783 50 PV 35 AMP 1.60
74C04 39 74C08 49 74C10 .39	74C85 2 49 74C90 1,95 74C93 1,95	74C164 2 49 74C173 2 60 74C192 2 49 74C193 2 49	MAN 6680         Common Catnose-cange         560         .99         5082-7304         Oversage disactor (L1)         600         15.00           MAN 6710         Common Antose-red D.D.         560         .99         5082-7304         Oversage disactor (L1)         600         15.00           RCA LINEAR         CALCULATOR         CLOCK CHIPS         MOTOROLA	14/5245         15         500m         28         14/1183         50 Ptv 35         AMP         1.60           14/456         25         40m         6/1.00         1N/184         100 Ptv 35         AMP         1.70           1A/458         150         7m         6/1.00         1N/1185         150 Ptv 35         AMP         1.70           1A/458         150         7m         5/1.00         1N/1185         150 Ptv 35         AMP         1.80
74004 39 74008 49 74010 39 74014 1,95 74020 39 74030 39	74C85 Z 49 74C90 1.95 74C93 1.95 74C95 1.95 74C107 1.25 74C151 Z.90	74C164 2 49 74C173 2 60 74C192 2 49 74C193 2 49 74C195 2 49 74C195 2 49 74C195 2 49 74C922 5 95 74C923 6 25	NAM 6680         Common Catthole-oninge         560         99         5082-7304         Oversnage dbacter (1,1)         600         15.00           RCA LINEAR         Catculator         Catculator         Catculator         Catculator         Catculator         Catculator         MotoRol         Catculator         MotoRol         MotoRol         Catculator         MotoRol         MotoRol         S75           CA3037         2.56         CA30319         2.06         CHP5/ORIVERS         MM3209         \$4.875         MotoRol         \$5.75         Mu5311         4.95         MotiAdelts         \$7.57           CA30357         2.56         CA30319         1.69         Mu5725         \$2.99         Mu5311         4.95         MotiAdelts         \$7.57	IN5245         15         500m         28         IN1183         50 PV 35 Au8P         1,00           IN456         25         40m         61,00         IN1184         100 PV 35 Au8P         1,70           IN455         150         7m         67,00         IN1185         150 PV 35 Au8P         1,70           IN485A         150         7m         67,00         IN1185         150 PV 35 Au8P         1,70           IN485A         180         10m         51,00         IN1186         200 PV 35 Au8P         1,70           IN485A         180         10m         51,00         IN1186         200 PV 35 Au8P         1,80           SCR AND FW BRIDGE RECTIFIERS         SCR         SCR         SCR         SCR         SCR
74004 39 74008 49 74010 39 74014 1.95 74020 39 74020 39 74020 39 74020 1.95 74020 2.49 74023 89	74C85         2         49           74C90         1.95         74C93         1.95           74C95         1.95         74C151         2.90           74C151         2.90         74C154         3.00           74C157         2.5         74C157         2.5           74C154         3.00         74C157         2.5	74C164 2 49 74C173 2 60 74C192 2 49 74C193 2 49 74C195 2 49 74C922 5 95 74C923 6 25 74C925 8 95 74C925 8 95 74C926 8 95	MAX 6800         Common Cattories enge tomme Anderer 40:0         560         99         5082-7304         Overanage disacter (1,1)         600         15:00           RCA         LINEAR         CALCULATOR         CALCULATOR         CLOCK CHIPS         Md3311         2:15         6430317         2:15         6430217         2:05         CALBOR         CALCULATOR         CLOCK CHIPS         Md5100         2:4 95           CA30217         2:15         64308017         2:00         CHIPS/ORIVERS         CLOCK CHIPS         Md5101         65         Md710810.5         57.95         57.96         Md5311         4:55         MG710810.5         57.95         2:95         Md5311         4:55         MG710810.5         2:95         Md5311         4:55         MG710810.5         2:95         Md5311         4:55         MG7108.5         2:95         Md5315         5:95         MG3017         2:95         Md5315         5:95         MG3016         7:35         Md5316 <td>IN5245         15         500m         28         111113         50 PV 35 AuP         1,00           IN456         25         40m         61,00         IN1184         100 PV 35 AuP         1,70           IN455         150         7m         67,00         IN1185         150 PV 35 AuP         1,70           IN455         150         7m         67,00         IN1185         150 PV 35 AuP         1,70           IN485A         160         00m         31,00         IN1186         160 PV 35 AuP         1,80           IN485A         100m         \$1,00         IN1184         400 PV 35 AuP         3,00           SCR         AND         FW 12/M         12/1.00         IN1184         400 PV 35 AuP         3,00           C36D         154 0# 400V         SCR(2N1949)         \$1,95         51,95         50           C38M         354 a# 600V         SCR(2N1949)         \$1,95         50         \$20           C38M         354 a# 600V         SCR         1,95         \$20         \$20           C38M         3.64 a# 300V         SCR         \$30         \$30         \$30</td>	IN5245         15         500m         28         111113         50 PV 35 AuP         1,00           IN456         25         40m         61,00         IN1184         100 PV 35 AuP         1,70           IN455         150         7m         67,00         IN1185         150 PV 35 AuP         1,70           IN455         150         7m         67,00         IN1185         150 PV 35 AuP         1,70           IN485A         160         00m         31,00         IN1186         160 PV 35 AuP         1,80           IN485A         100m         \$1,00         IN1184         400 PV 35 AuP         3,00           SCR         AND         FW 12/M         12/1.00         IN1184         400 PV 35 AuP         3,00           C36D         154 0# 400V         SCR(2N1949)         \$1,95         51,95         50           C38M         354 a# 600V         SCR(2N1949)         \$1,95         50         \$20           C38M         354 a# 600V         SCR         1,95         \$20         \$20           C38M         3.64 a# 300V         SCR         \$30         \$30         \$30
74004 39 74004 39 74010 39 74010 39 74020 39 74020 39 74020 39 74024 1.95 74024 1.95 74024 89 74024 89 74024 89 74024 89	74C85 2 99 74C90 1,95 74C93 1,95 74C93 1,95 74C107 1,25 74C107 1,25 74C151 2,90 74C154 3,00 74C157 2 15 74C160 2 49 74C161 2 49	74C163         2.49           74C173         2.60           74C192         2.49           74C193         2.49           74C193         2.49           74C195         2.49           74C195         2.49           74C95         6.25           74C925         8.95           74C925         8.95           74C925         1.50           80095         1.50           LM710N         79           LM710N         39	MAN 6800         Common Ander Hoto - oninge         560         99         5082-7304         Overange disacter (1,1)         600         15.00           RCA LINEAR         Calculator         Calculator         Calculator         Calculator         MotoRol         4 # 7 Set         Digit-Hexadecinal         600         25.00           RCA LINEAR         Calculator         CLOCK CHIPS         MotoRol         MotoRol         MotoRol         Konorol         Calculator           CA3037         2.56         CA3081N         1.60         Mis728         2.95         Mu5311         4.59         Mc14081/6         5.75           CA30357         1.64         CA3057         2.00         Mis728         2.95         Mu5311         4.59         Mc14081/6         5.75           CA30357         1.60         Mis728         2.96         Mu5311         4.95         Mc14081/6         5.75           CA30357         1.60         Mis728         2.96         Mu5314         4.95         Mc14081/6         2.95           CA30357         1.90         Mis864         2.00         Mis316         6.95         Mc327P         2.95	Scale         Soon         28         111183         So PV 35         Aug         1,00           11455         25         40m         61,00         111184         100 PV 35         1,70           11455         150         7m         67,00         111185         150 PV 35         Aug         1,70           114458         150         7m         67,00         11118         150 PV 35         Aug         1,70           114458         150         7m         67,00         11118         200 PV 35         Aug         1,80           114458         150         7m         127,00         11118         400 PV 35         Aug         3,00           SCR         AND         FW BRIDGE RECTIFIERS         51,95         1,34         50         1,35           C380         1,54 is 300v         5CR         1,54         3,00v         5CR         30           W63, 690-1         1,54 is 300v         5CR         30<
74004 39 74008 49 74008 49 74010 39 74014 1.95 74020 39 74021 39 74021 39 74021 39 74021 39 74021 39 74021 39 74021 49 74021 49 75 74021 49 75 74021 49 75 74021 49 75 74021 49 75 74021 49 75 74021 49 75 74021 49 75 75 76 76 76 76 76 76 76 76 76 76 76 76 76	74(25) 2.99 74(20) 1.95 74(20) 1.95 74(25) 1.95 74(25) 1.95 74(25) 2.95 74(25) 2.95 74(25) 2.95 74(25) 2.15 74(25) 2.49 74(25) 2.15 1.00 74(25) 2.15 74(25) 2.15 7	74C173 2 40 74C173 2 60 74C192 2 49 74C193 2 49 74C193 2 49 74C192 2 49 74C922 5 95 74C925 8 95 80C95 1 50 LM710N 79 LM711N 39 LM711N 39 LM723AH 10	MAK 6570         Common Anderen ange Emmon Anderen and D.         560         99         5082-7304         Overanage dualacter (1,1)         600         25         00         00         25         00         25         00         00         25         00         00	IN5245         15         500m         28         IN1193         50         PV 35         Aug         1,00           IN456         25         40m         6/1,00         IN1184         100         PV 34,00         1,70           IN455         150         7m         6/1,00         IN1184         150         PV 33, Aug         1,70           IN4854         150         7m         6/1,00         IN1184         150         PV 33, Aug         1,70           IN4854         150         7m         6/1,00         IN1184         600 PV 33, Aug         1,80           IN4801         50         PV1 1,4W         1271,00         IN1184         600 PV 33, Aug         3,00           SCAR         AND         FX         600V         SCR(2x11849)         51,95         3,00           C360         15A isi 400V         SCR         1,54         300V         SCR         50           PM2280         1,54 isi 300V         SCR         9106E REC         1,95         50           MDA 990 1         12A isi 200V         PW BHIDGE REC         1,95         1,95         1,90           C10661         50         TRANSISTORS         193,900         4/1,00         14/1,00
74004 39 74008 49 74008 49 74010 39 74014 195 74020 39 74024 195 74024 2, 49 74024 2, 49 74024 89 74024 89 74044 89 74044 89 74044 89 74044 89 74044 89 74044 89 74044 89 74044 80 74044 80 7404	74(25) 2 99 74(28) 1 95 74(28) 1 95 74(27) 1 95 74(27) 1 95 74(27) 2 95 74(27) 2 95 74(27) 2 99 74(27) 2 15 74(27) 2 99 74(27) 2 49 74(27)	746164         2.49           746173         2.49           746173         2.49           746193         2.49           746195         2.49           746195         2.49           746193         2.59           746925         5.95           746926         5.95           740926         9.95           60059         150           100597         1.50           1007304         10           10/73304         10           10/73304         10           10/747044         15           10/747044         16	MAK 6510         Common Anderer with 0.15         560         99         5082-7304         Overanage dusacter (1,1)         600         25         000         000         25         000         25         000	IN3245         15         500m         28         IN1183         50 PV 35 AuP         1.00           IN456         25         40m         6/1.00         IN1184         100 PV 35 AuP         1.70           IN458         150         7m         6/1.00         IN1184         150 PV 35 AuP         1.70           IN4858.1         150         7m         6/1.00         IN1184         150 PV 35 AuP         1.70           IN4858.1         10m         37.100         IN1186         50 PV 13 AuP         1.80           IN4858.1         10m         50 PV 1 AuP         127.00         IN1184         400 PV 35 AuP         3.00           SCR AND FW BRIDGE RECTIFIERS         50         50 PV 1 AuP         50 PV         50
74004 39 74008 49 74010 39 74014 195 74020 39 74024 195 74020 39 74024 195 74024 219 74024 219 74024 219 74024 25 74024 85 74024 85 740248	74(35) 2.95 74(38) 1.95 74(39) 1.95 74(37) 1.95 74(37) 1.95 74(37) 2.95 74(37) 2.95 74(37) 2.95 74(37) 2.15 74(37) 2.15 74(37) 2.15 74(37) 2.15 74(37) 2.15 74(37) 2.49 <b>LINEEAR</b> LM340(-72) 1.25 LM340(7-12) 1.25	746164 2.49 746173 2.49 746173 2.49 746179 2.49 746179 2.49 746179 2.49 746179 2.49 746179 2.49 746276 8.95 746285 8.95 74645 8.	MAK 6570         Common Anderen ange Emmon Anderen All DE         560         99         5082-7304         Overanage dual cert (1:1)         600         25 00           RCA         LINEEAR LINE         CAUCULATOR CHIPS/DRIVERS 1200337         Coverange dual cert (1:1)         600         15 00           RCA         LINE         CAUGUATOR CHIPS/DRIVERS 1200337         Coverange dual cert (1:1)         600         15 00           CAUSIT         215         GABBUN         2.00         CAUGUATOR CHIPS/DRIVERS         CUCK CHIPS         MM5209         94 95         MC1080L6         575           CAUGUST         1.60         MM5725         92 95         MM5311         4.55         MC1080L6         575           CAUGUST         1.60         MM5725         92 95         MM5316         4.60         MC1080L6         575           CAUGUST         1.30         DM8864         2.00         MM5316         4.60         MM5327         935           CAUGUST         2.00         CAUGUST         2.00         CAUGUST         2.00         CAUGUST         2.00           CAUGUST         2.00         CAUGUST         2.00         CAUGUST         2.00         CAUGUST         2.00         2.00         2.00         2.00         2.00	IN5245         15         500m         28         IN1193         50 PV 35 Aug         1,00           IN456         25         40m         61,00         IN1184         100 PV 35 Aug         1,70           IN455         150         7m         67,00         IN1185         150 PV 33 Aug         1,70           IN455         150         7m         67,00         IN1185         150 PV 33 Aug         1,80           IN485A         160         10m         51,00         IN1186         400 PV 33 Aug         1,80           IN4825A         150         PV 3 Aug         127,00         IN1184         400 PV 33 Aug         3,00           SCRAND FW BRIDGE RECTIFIERS         C36M         354 iii 600V         SCR (SCR 1989)         51,195           C38M         354 iii 600V         SCR         50         90         50         90           MDA 980 1         124 iii 200V         SCR         50         195         100         1160           MDA 980 3         124 iii 200V         PW BPIDGE REC         195         100         140         100         1159           MDA 980 3         124 iii 2055         100         240305         100         240305         100         100
74004 39 74008 49 74008 49 74014 195 74020 39 74024 195 74020 39 74024 29 74030 195 74030 195 740300 195 740000 195 74000000000000000000000000000000000000	74(25) 2 99 74(28) 1 95 74(28) 1 95 74(27) 1 95 74(27) 1 95 74(27) 1 95 74(27) 2 90 74(27) 2 90 74(27) 2 90 74(27) 2 99 74(27)	740161         2.49           740173         2.49           740173         2.49           740193         2.49           740193         2.49           740193         2.49           740193         2.49           740225         8.95           80030         1.50           80030         1.50           80030         1.50           80030         1.50           80031         1.50           80031         1.50           80031         1.50           80034         1.9           80035         1.9           80036         1.9           80037         1.50           80036         1.9           80037         1.50           80037         1.50           80037         1.50           80037         1.50           80038         1.9           80039         1.9           800439         1.9           8004480         1.9           80044808         1.9	MAK 6570         Common Andere manye         560         99         5082-7304         Overanage dusacter (1,1)         600         15 00           RCA         LINESAR         Calculation         Calculation         Club (1,1)         Clu	IN5245         15         500m         28         IN1193         50 PV 35 Aup         1.00           IN455         25         60m         60.00         IN1184         100 PV 35 Aup         1.70           IN455         150         7m         67.00         IN1185         150 PV 35 Aup         1.70           IN455         150         7m         67.00         IN1185         150 PV 35 Aup         1.70           IN4855         150         7m         67.00         IN1185         150 PV 35 Aup         1.80           IN4855         150         7m         67.00         IN1186         400 PV 35 Aup         1.80           C360         154 6# 400V         SCR(ZN1949)         51.95         200         200         200         200         200         200         200         200         200         200         200         200         200         200         200         20000         2000         2000
74004 39 74008 49 74010 39 74014 195 74020 39 74024 195 74020 39 74024 195 74024 2, 195 74024 2, 195 74024 2, 195 74024 89 74024 89 740448	74(25) 2 49 74(28) 1 55 74(28) 1 55 74(27) 1 55 74(27) 1 55 74(27) 1 55 74(27) 2 15 74(27) 2 15 74(27) 2 15 74(27) 2 49 <b>LINEEAR</b> LM3406-18 1 35 LM3407-2 1 35 LM3407-6 1,25 LM3407-6 1,25 LM3407-6 1,25 LM3407-1 1,	74C161         2.49           74C173         2.49           74C192         2.49           74C193         2.49           74C193         2.49           74C193         2.49           74C193         2.49           74C193         6.25           74C193         6.25           74C193         6.25           74C193         6.25           74C193         1.07           140236         6.25           140237         1.00           140237         1.00           140237         1.00           1407170         18           1477170         18           14774704         35           14774704         35           14774704         32           14774704         32           14774704         32           14774704         32           14774704         32           14774704         32           14774704         32           14774704         39           14774704         39           14774704         39           14780404         39           14780404 </td <td>MAK 6570         Common Andere wing         560         99         5082-7304         Overange duarter (1:1)         600         25         000</td> <td>IN3245         15         500m         28         IN1183         50 PV 35 AuP         1.00           IN456         25         40m         6/1.00         IN1184         100 PV 35 AuP         1.70           IN458         150         7m         6/1.00         IN1184         150 PV 35 AuP         1.70           IN4838.180         10m         50 PV 1.4W         12/1.00         IN1186         150 PV 35 AuP         1.70           IN4838.180         10m         51.70         6/1.00         IN1184         600 PV 35 AuP         1.80           IN4838.180         10m         52.71.00         IN1184         600 PV 35 AuP         3.09</td>	MAK 6570         Common Andere wing         560         99         5082-7304         Overange duarter (1:1)         600         25         000	IN3245         15         500m         28         IN1183         50 PV 35 AuP         1.00           IN456         25         40m         6/1.00         IN1184         100 PV 35 AuP         1.70           IN458         150         7m         6/1.00         IN1184         150 PV 35 AuP         1.70           IN4838.180         10m         50 PV 1.4W         12/1.00         IN1186         150 PV 35 AuP         1.70           IN4838.180         10m         51.70         6/1.00         IN1184         600 PV 35 AuP         1.80           IN4838.180         10m         52.71.00         IN1184         600 PV 35 AuP         3.09
74004 39 74008 49 74008 49 74010 39 74014 195 74020 39 74024 195 74020 39 74024 195 74024 2149 74024 49 74024 19 74024 19 75 74024 19 75 74024 19 75 75 75 75 75 75 75 75 75 75 75 75 75	74(25) 2.99 74(29) 1.95 74(29) 1.95 74(27) 1.95 74(27) 1.95 74(27) 1.95 74(27) 2.15 74(27) 2.15 74(27) 2.15 74(27) 2.15 74(27) 2.15 74(27) 2.15 74(27) 2.49 <b>LINEEAR</b> LM3404-78 1.25 LM3407-72 1.25 LM3407-15 1.25 LM3407-16 1.25 LM3407-18	74C161         2.49           74C173         2.49           74C173         2.49           74C193         2.49           74C193         2.49           74C193         2.49           74C195         2.49           74C195         2.49           74C195         6.95           74032         6.95           74037         6.95           74037         6.95           74037         1.90           LM77101         78           LM73194         10           LM73194         10           LM73194         10           LM73194         13           LM74114         39           LM74114         39           LM74144         13           LM74144         13           LM74144         13           LM1486K         13           LM1486K         15           LM1485K         175           LM1455K         175           LM1455K         175           LM1455K         175           LM145K         175           LM145K         175           LM145K         17	MAK 9510         Common Anderer with 10.5         560         99         5082-7304         Oversnage dualcerr (1.1)         600         15.00           RCA         LINDEAR         Calasta         Calasta <td>IN3245         15         500m         28         IN1193         50 PV 35 AuP         1.00           IN456         25         40m         61.00         IN1184         100 PV 35 AuP         1.70           IN455         150         7m         67.00         IN1185         150 PV 35 AuP         1.70           IN455         150         7m         67.00         IN1185         150 PV 35 AuP         1.70           IN4601         50 PV 1 AuP         127.00         IN1186         600 PV 35 AuP         3.00           SCER AND FW BRIDGE RECTREERS         50         50         50         1.90         50           C360         15.46 a 300V         5CR         1.95         50         70         70           20228         1.54 a 300V         SCR         1.95         50         70         70         70           20239         1.94 a 300V         SCR         1.95         50         70         70         70         70           MDA 990 1         12A 6r 30V         SCR         1.95         1.95         1.95         1.00         70         70         70         70         70         70         70         70         70         70         70</td>	IN3245         15         500m         28         IN1193         50 PV 35 AuP         1.00           IN456         25         40m         61.00         IN1184         100 PV 35 AuP         1.70           IN455         150         7m         67.00         IN1185         150 PV 35 AuP         1.70           IN455         150         7m         67.00         IN1185         150 PV 35 AuP         1.70           IN4601         50 PV 1 AuP         127.00         IN1186         600 PV 35 AuP         3.00           SCER AND FW BRIDGE RECTREERS         50         50         50         1.90         50           C360         15.46 a 300V         5CR         1.95         50         70         70           20228         1.54 a 300V         SCR         1.95         50         70         70         70           20239         1.94 a 300V         SCR         1.95         50         70         70         70         70           MDA 990 1         12A 6r 30V         SCR         1.95         1.95         1.95         1.00         70         70         70         70         70         70         70         70         70         70         70
74004 39 74008 49 74008 49 74014 195 74020 39 74024 195 74020 199 74024 199 74024 29 74074 89 74074 175 8 100709 175 100709 10 10 10 10 10 10 10 10 10 10 10 10 10 1	74(25)         2.49           74(26)         1.95           74(26)         1.95           74(26)         1.95           74(26)         1.95           74(26)         1.95           74(26)         2.90           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         1.25           LM340(-74)         1.25           LM340(-74)         1.25           LM340(-74)         1.25           LM340(-74)         1.25           LM340(-74)         1.25           LM320(-74)	740161         2.49           740173         2.69           740193         2.49           740193         2.49           740193         2.49           740193         2.49           740193         2.49           740202         8.25           740202         8.25           740202         8.25           740202         8.25           740202         8.25           740202         8.25           740202         8.25           740202         8.25           740203         8.25           740204         8.5           740304         9.5           740304         9.5           740304         9.5           740304         9.5           740304         9.5           107334         10           107334         10           107334         10           107334         10           1074344         13           1074444         13           10744444         13           10744444         13           10744444         13           10744444 <t< td=""><td>MAK 6510         Common Anote-eninge mark 6510         560         99         5082-7304         Overange dual cert (1)         600         15 00           RCA         LINE BAR         Calculations         Common Anote-eninge         500         99         5082-7304         Overange dual cert (1)         600         25 00         22 00         02 25           RCA         LINE BAR         CLOCK CHPS         MOTOBOLA         MOTOBOLA         MOTOBOLA           CA3011         2 15         CA30801         1.00         M3725         82 .98         MM3511         45 MOTOBOLA           CA30511         2 15         CA30801         1.00         M3725         82 .98         MM3511         45 MOTOBOLA           CA30511         2 15         CA30817         2 00         M3512         4 50         MOTOBOLA           CA30514         1 30         CA31007         1 30         M48587         1 00         M43316         6 50         MOTOBOLA           CA30610         3 25         CA31607         1 25         M48857         1 00         M43316         4 50         MC4024P         3 50           CA30610         2 30         CA30610         3 50         CA LED driver         1 50         M45316         4 50</td><td>IN3245         15         500m         28         IN1183         50 PV 35 AuP         1,00           IN456         25         40m         6/1,00         IN1184         150 PV 35 AuP         1,70           IN455         150         7m         6/1,00         IN1185         150 PV 35 AuP         1,70           IN455         150         7m         6/1,00         IN1185         150 PV 35 AuP         1,70           IN485A         160         0m         Y3,00         IN1186         150 PV 35 AuP         1,80           IN485A         160         Tom ST,00         IN1186         200 PV 35 AuP         30           SCRANDE         FW BRIDGE RECTIFIERS         C360         154 m 400V         SCR(x11849)         51.95           Z080         15.4 m 400V         SCR(x11849)         S1.95         50         90         90           M0A 980-1         12A m 50V         FW BRIDGE REC         195         90         140         100         141         100           IN591         51.00         274055         1,00         243905         41.00         1100         100         100         100         100         100         100         100         100         100</td></t<>	MAK 6510         Common Anote-eninge mark 6510         560         99         5082-7304         Overange dual cert (1)         600         15 00           RCA         LINE BAR         Calculations         Common Anote-eninge         500         99         5082-7304         Overange dual cert (1)         600         25 00         22 00         02 25           RCA         LINE BAR         CLOCK CHPS         MOTOBOLA         MOTOBOLA         MOTOBOLA           CA3011         2 15         CA30801         1.00         M3725         82 .98         MM3511         45 MOTOBOLA           CA30511         2 15         CA30801         1.00         M3725         82 .98         MM3511         45 MOTOBOLA           CA30511         2 15         CA30817         2 00         M3512         4 50         MOTOBOLA           CA30514         1 30         CA31007         1 30         M48587         1 00         M43316         6 50         MOTOBOLA           CA30610         3 25         CA31607         1 25         M48857         1 00         M43316         4 50         MC4024P         3 50           CA30610         2 30         CA30610         3 50         CA LED driver         1 50         M45316         4 50	IN3245         15         500m         28         IN1183         50 PV 35 AuP         1,00           IN456         25         40m         6/1,00         IN1184         150 PV 35 AuP         1,70           IN455         150         7m         6/1,00         IN1185         150 PV 35 AuP         1,70           IN455         150         7m         6/1,00         IN1185         150 PV 35 AuP         1,70           IN485A         160         0m         Y3,00         IN1186         150 PV 35 AuP         1,80           IN485A         160         Tom ST,00         IN1186         200 PV 35 AuP         30           SCRANDE         FW BRIDGE RECTIFIERS         C360         154 m 400V         SCR(x11849)         51.95           Z080         15.4 m 400V         SCR(x11849)         S1.95         50         90         90           M0A 980-1         12A m 50V         FW BRIDGE REC         195         90         140         100         141         100           IN591         51.00         274055         1,00         243905         41.00         1100         100         100         100         100         100         100         100         100         100
P4004         39           74008         49           74008         49           74008         49           74010         39           74021         39           74042         1.95           74042         1.95           74042         1.95           74042         1.95           74044         1.95           74044         1.95           74044         1.95           74044         1.95           74044         1.95           74044         1.95           74044         1.95           74044         1.95           74044         1.95           74044         1.95           74044         1.95           74044         1.95           7404044         1.00           7403044         1.00           7403044         1.00           7403044         1.00           7403044         1.00           7403044         1.00           7403044         1.00           7403044         1.00           7403044         1.00           7403044         1.00 <td>74(25)         2.95           74(26)         1.95           74(27)         1.95           74(27)         1.95           74(27)         1.95           74(27)         1.95           74(27)         2.5           74(27)         2.15           74(15)         2.49           242161         2.49           242161         2.49           243161         1.25           LM340K-18         1.25           LM3401-5         1.25           LM3401-1         1.25           LM3401-1         1.25           LM3401-2         1.25           LM3401-1         1.25           LM3401-1         1.25           LM3401-1         1.25           LM3401-2         1.25           LM3401-1         1.26      LM3401-1         1.20</td> <td>74C161         2.49           74C173         2.49           74C192         2.49           74C193         2.49           74C193         2.49           74C193         2.49           74C193         6.25           74C193         6.25           74C193         6.25           74C193         6.25           74C193         6.25           74C193         7.10           74037         6.25           740376         6.25           7470376         7.20           740376         7.20           740376         7.20           740376         7.20           740376         7.20           747070         7.20           747070         7.20           747070         7.20           747070         7.20           747070         7.20           747070         7.20           747070         7.20           747070         7.20           747070         7.20           747070         7.20           747070         7.20           774700         7.20           774700<!--</td--><td>MAK 6510         Common Ander eninge market         560         99         5082-7304         Overange dualater (±1)         600         15 00           RCA         LINESAB         CALCULATOR CHIPS/DRIVERS         CALCULATOR CHIPS/DRIVERS         CLOCK CHIPS         M010R0L           CA30317         2.15         GA308011         2.00         CALCULATOR CHIPS/DRIVERS         CLOCK CHIPS         M05309         4.4 / 7.5 git 150/1-Hexademain         M010R0L           CA30317         2.15         GA308011         2.00         CLIPS/DRIVERS         M05309         4.4 / 50         M010R0L         5.7 / 9.9           CA30347         2.40         CA30604         1.50         MM5732         2.96         MM5311         4.50         M010R0L         5.7 / 9.9           CA30464         1.30         CA31001         1.39         DM8865         2.00         MM5316         6.95         M40317         4.59         M40317         4.59         M40317         4.59         M40317         3.90         CA40074         3.90         CA40074         3.90         M43317         4.95         M40307         9.95         M40307         9.95         M40407474         3.90         M4337         9.95         M40407474         3.90         M4337         9.95         M40</td><td>IN3245         15         500m         28         IN1183         50 PV 35 AuP         1,00           IN456         25         40m         6/1,00         IN1184         150 PV 35 AuP         1,70           IN455         150         7m         6/1,00         IN1185         150 PV 35 AuP         1,70           IN455         150         7m         6/1,00         IN1185         150 PV 35 AuP         1,70           IN485A         160         0m         12/1,00         IN1186         150 PV 35 AuP         1,80           IN485A         160         TATA         12/1,00         IN1184         600 PV 35 AuP         3,90           C36D         154 m 400V         SCR(2N1849)         51.95         50         50         50           C38M         354 m 600V         SCR         1.95         50         50         50         50         50         50         70         50         70         70         71.95         50         70         70         71.90         71.90         71.90         71.90         71.90         71.90         71.90         71.90         71.90         71.90         71.90         71.90         71.90         71.90         71.90         71.90</td></td>	74(25)         2.95           74(26)         1.95           74(27)         1.95           74(27)         1.95           74(27)         1.95           74(27)         1.95           74(27)         2.5           74(27)         2.15           74(15)         2.49           242161         2.49           242161         2.49           243161         1.25           LM340K-18         1.25           LM3401-5         1.25           LM3401-1         1.25           LM3401-1         1.25           LM3401-2         1.25           LM3401-1         1.25           LM3401-1         1.25           LM3401-1         1.25           LM3401-2         1.25           LM3401-1         1.26      LM3401-1         1.20	74C161         2.49           74C173         2.49           74C192         2.49           74C193         2.49           74C193         2.49           74C193         2.49           74C193         6.25           74C193         6.25           74C193         6.25           74C193         6.25           74C193         6.25           74C193         7.10           74037         6.25           740376         6.25           7470376         7.20           740376         7.20           740376         7.20           740376         7.20           740376         7.20           747070         7.20           747070         7.20           747070         7.20           747070         7.20           747070         7.20           747070         7.20           747070         7.20           747070         7.20           747070         7.20           747070         7.20           747070         7.20           774700         7.20           774700 </td <td>MAK 6510         Common Ander eninge market         560         99         5082-7304         Overange dualater (±1)         600         15 00           RCA         LINESAB         CALCULATOR CHIPS/DRIVERS         CALCULATOR CHIPS/DRIVERS         CLOCK CHIPS         M010R0L           CA30317         2.15         GA308011         2.00         CALCULATOR CHIPS/DRIVERS         CLOCK CHIPS         M05309         4.4 / 7.5 git 150/1-Hexademain         M010R0L           CA30317         2.15         GA308011         2.00         CLIPS/DRIVERS         M05309         4.4 / 50         M010R0L         5.7 / 9.9           CA30347         2.40         CA30604         1.50         MM5732         2.96         MM5311         4.50         M010R0L         5.7 / 9.9           CA30464         1.30         CA31001         1.39         DM8865         2.00         MM5316         6.95         M40317         4.59         M40317         4.59         M40317         4.59         M40317         3.90         CA40074         3.90         CA40074         3.90         M43317         4.95         M40307         9.95         M40307         9.95         M40407474         3.90         M4337         9.95         M40407474         3.90         M4337         9.95         M40</td> <td>IN3245         15         500m         28         IN1183         50 PV 35 AuP         1,00           IN456         25         40m         6/1,00         IN1184         150 PV 35 AuP         1,70           IN455         150         7m         6/1,00         IN1185         150 PV 35 AuP         1,70           IN455         150         7m         6/1,00         IN1185         150 PV 35 AuP         1,70           IN485A         160         0m         12/1,00         IN1186         150 PV 35 AuP         1,80           IN485A         160         TATA         12/1,00         IN1184         600 PV 35 AuP         3,90           C36D         154 m 400V         SCR(2N1849)         51.95         50         50         50           C38M         354 m 600V         SCR         1.95         50         50         50         50         50         50         70         50         70         70         71.95         50         70         70         71.90         71.90         71.90         71.90         71.90         71.90         71.90         71.90         71.90         71.90         71.90         71.90         71.90         71.90         71.90         71.90</td>	MAK 6510         Common Ander eninge market         560         99         5082-7304         Overange dualater (±1)         600         15 00           RCA         LINESAB         CALCULATOR CHIPS/DRIVERS         CALCULATOR CHIPS/DRIVERS         CLOCK CHIPS         M010R0L           CA30317         2.15         GA308011         2.00         CALCULATOR CHIPS/DRIVERS         CLOCK CHIPS         M05309         4.4 / 7.5 git 150/1-Hexademain         M010R0L           CA30317         2.15         GA308011         2.00         CLIPS/DRIVERS         M05309         4.4 / 50         M010R0L         5.7 / 9.9           CA30347         2.40         CA30604         1.50         MM5732         2.96         MM5311         4.50         M010R0L         5.7 / 9.9           CA30464         1.30         CA31001         1.39         DM8865         2.00         MM5316         6.95         M40317         4.59         M40317         4.59         M40317         4.59         M40317         3.90         CA40074         3.90         CA40074         3.90         M43317         4.95         M40307         9.95         M40307         9.95         M40407474         3.90         M4337         9.95         M40407474         3.90         M4337         9.95         M40	IN3245         15         500m         28         IN1183         50 PV 35 AuP         1,00           IN456         25         40m         6/1,00         IN1184         150 PV 35 AuP         1,70           IN455         150         7m         6/1,00         IN1185         150 PV 35 AuP         1,70           IN455         150         7m         6/1,00         IN1185         150 PV 35 AuP         1,70           IN485A         160         0m         12/1,00         IN1186         150 PV 35 AuP         1,80           IN485A         160         TATA         12/1,00         IN1184         600 PV 35 AuP         3,90           C36D         154 m 400V         SCR(2N1849)         51.95         50         50         50           C38M         354 m 600V         SCR         1.95         50         50         50         50         50         50         70         50         70         70         71.95         50         70         70         71.90         71.90         71.90         71.90         71.90         71.90         71.90         71.90         71.90         71.90         71.90         71.90         71.90         71.90         71.90         71.90
74004         39           74008         49           74008         49           74008         49           74008         49           74008         49           7401         195           74020         39           7404         1.95           7402         1.95           7402         1.95           7402         1.95           7402         1.95           7402         1.95           7402         1.95           7402         1.95           7402         49           7402         49           7402         49           7402         49           7402         49           7402         49           7402         49           7402         49           7402         49           74024         49           74024         49           74024         49           74024         49           7403010000         1.00           143000000         1.25           143000000         1.35           1430200000	74(25) 2.99 74(28) 1.95 74(29) 1.95 74(27) 1.95 74(27) 1.95 74(27) 2.15 74(27) 2.15 74(27	740161         2.49           740173         2.69           740173         2.49           740173         2.49           740173         2.49           740173         2.49           740173         2.49           740173         2.49           740276         5.5           740326         5.6           740376         5.6           10007         1.50           LM7101         78           LM73104         1.9           LM73104         1.9           LM74111         35           LM74114         34           LM145004         75           LM145014         38           LM145014         39           LM145014         39           LM145014         39           LM145014         39           LM145014         39           LM145014         39           LM145014	MAK 6570         Common Anote-eninge market         560         99         5082-7304         Overange dual error (±1)         600         25           RCA         LINEGAR         CALCULATOR         CALCULATOR         CLOCK CHIPS         MM0TOBLA           CA3031         215         CA3080N         2.00         CALCULATOR         CLOCK CHIPS         MM0TOBLA         56         99         592.7304         CHERAR         MOTOBLA         56         99         5082.7304         0.00         25         50           CAUSIT         215         CA3080N         2.00         CALCULATOR         CLOCK CHIPS         MM53317         4.69         MC1408L7         54.95           CAUSIT         1.60         MM5725         82.99         M435317         4.69         MC1408L8         57.95           CAUSIT         1.20         CAUSIT         1.20         MM35318         9.95         MC0167/415         7.50           CAUGIN         3.25         CAUSIT         1.20         MA887         1.50         MM53318         9.95         MC0167/415         7.50           CAUGIN         2.50         CAUSIN         3.50         CAUCIN         1.50         MM3318         9.95         MC0167/415         7.50	IN3254         15         500m         28         1111133         50 PV3 35 AuP         1,00           IN455         25         40m         61,00         IN1184         100 PV 35 AuP         1,70           IN455         150         7m         67,00         IN1185         150 PV 35 AuP         1,70           IN455         150         7m         67,00         IN1185         150 PV 35 AuP         1,70           IN485A         160         10m         31,10         IN1186         200 PV 35 AuP         1,80           IN485A         100m         31,00         IN1184         400 PV 35 AuP         3,00           C36D         154 m 400V         SCR(2N1849)         31,95         30         202           C38M         354 m 600V         SCR         1,90         30         30         30         30         30         30         30         30         30         30         30         30         30         30         30         30         30         30         410         30         410         30         410         30         410         30         410         30         410         30         410         30         410         30 <t< td=""></t<>
74004         39           74008         49           74008         49           74008         49           74014         195           74020         39           74021         195           74023         39           74024         245           74036         245           74045         246           74046         245           74047         55           143004         80           LM3004         80           LM3004         100           LM30044         100           LM3007044         10           LM3007044         10           LM300704         15           LM310704         15	74(25)         2.49           74(26)         1.95           74(26)         1.95           74(26)         1.95           74(26)         1.95           74(26)         2.50           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         1.25           1.304(30)         1.25           1.304(30)         1.25           1.304(30)         1.25           1.304(30)         1.25           1.304(30)         1.25           1.302(70)         1.95           1.302(70)         1.95           1.303(70)         1.95           1.433(80)         1.25           1.433(80)         1.95           1.433(80)         1.95           1.433(80)         1.95           1.433(80)         1.95           1.435(80)         1.95 <td>74C161         2.49           74C172         2.49           74C192         2.49           74C193         2.49           74C193         2.49           74C193         2.49           74C193         6.25           74C193         6.25           74C92         5.95           74C93         6.25           74C93         6.25           74C93         1.97           147250         1.90           147270         1.91           1473140         1.92           14747444         1.92           14747444         1.93           14747444         1.93           14747444         1.93           14747444         1.94           14747444         1.94           14747444         1.94           14747444         1.94           147</td> <td>MAK 6510         Common Anote-eninge mark 6510         560         99         5082-7304         Operatinge dual cert [1:1]         600         15:00           RCA         LINDEAR         CALCULATOR CHIPS/DRIVERS         CALCULATOR 4:17 Set 05         CUDCC CHIPS         MOTOROLA           CA30311         2:15         CA30301         2:00         CAS0201         2:00         MOTOROLA         State         MOTOROLA           CA30311         2:15         CA30301         1:00         MOTOROLA         MOTOROLA         MOTOROLA           CA30311         2:15         CA30301         1:00         MOTOROLA         MOTOROLA         MOTOROLA           CA30311         2:15         CA30317         1:20         MOS311         4:50         MOTOROLA           CA30501         1:20         CA30517         1:20         MOS311         4:50         MOTOROLA           CA30501         1:20         CA30517         1:20         MOS317         4:50         MOTOROLA           CA30501         2:00         CA305017         1:20         MOS317         4:50         MOS317         4:50         MOS317           CA30501         2:00         CA30501         3:50         CA307017         50         MOTOROLA         MOTOR</td> <td>IN3254         15         500m         28         IN1183         50         PV3 54         Auf         1.70           IN455         25         40m         61.00         IN1184         100         PV 34.00         I.710           IN455         25         7m         67.00         IN1185         150         PV 33         Auf         I.70           IN4854         100m         27.100         IN1186         150         PV 33         Auf         I.70           IN4854         100m         27.100         IN1186         600 PV 33         Auf         I.70           IN4854         100m         27.100         IN1186         600 PV 33         Auf         I.70           IN4850         154         400         VS         SCR(2N1849)         31.15         I.76           C380         154         400V         SCR(2N1849)         31.95         I.70         M0         M0         I.76         1.95           C380         354         90V         VM BHDGE REC         1.95         I.70         1.94         1.70         1.75           MFSA05         17.00         M18295         1.00         243906         41.00         1.75         943905</td>	74C161         2.49           74C172         2.49           74C192         2.49           74C193         2.49           74C193         2.49           74C193         2.49           74C193         6.25           74C193         6.25           74C92         5.95           74C93         6.25           74C93         6.25           74C93         1.97           147250         1.90           147270         1.91           1473140         1.92           14747444         1.92           14747444         1.93           14747444         1.93           14747444         1.93           14747444         1.94           14747444         1.94           14747444         1.94           14747444         1.94           147	MAK 6510         Common Anote-eninge mark 6510         560         99         5082-7304         Operatinge dual cert [1:1]         600         15:00           RCA         LINDEAR         CALCULATOR CHIPS/DRIVERS         CALCULATOR 4:17 Set 05         CUDCC CHIPS         MOTOROLA           CA30311         2:15         CA30301         2:00         CAS0201         2:00         MOTOROLA         State         MOTOROLA           CA30311         2:15         CA30301         1:00         MOTOROLA         MOTOROLA         MOTOROLA           CA30311         2:15         CA30301         1:00         MOTOROLA         MOTOROLA         MOTOROLA           CA30311         2:15         CA30317         1:20         MOS311         4:50         MOTOROLA           CA30501         1:20         CA30517         1:20         MOS311         4:50         MOTOROLA           CA30501         1:20         CA30517         1:20         MOS317         4:50         MOTOROLA           CA30501         2:00         CA305017         1:20         MOS317         4:50         MOS317         4:50         MOS317           CA30501         2:00         CA30501         3:50         CA307017         50         MOTOROLA         MOTOR	IN3254         15         500m         28         IN1183         50         PV3 54         Auf         1.70           IN455         25         40m         61.00         IN1184         100         PV 34.00         I.710           IN455         25         7m         67.00         IN1185         150         PV 33         Auf         I.70           IN4854         100m         27.100         IN1186         150         PV 33         Auf         I.70           IN4854         100m         27.100         IN1186         600 PV 33         Auf         I.70           IN4854         100m         27.100         IN1186         600 PV 33         Auf         I.70           IN4850         154         400         VS         SCR(2N1849)         31.15         I.76           C380         154         400V         SCR(2N1849)         31.95         I.70         M0         M0         I.76         1.95           C380         354         90V         VM BHDGE REC         1.95         I.70         1.94         1.70         1.75           MFSA05         17.00         M18295         1.00         243906         41.00         1.75         943905
P4004         39           74C08         49           74C08         49           74C11         1.95           74C03         39           74C14         1.95           74C03         39           74C42         1.95           74C42         1.95           74C42         1.95           74C43         2.449           74C74         85           74C44         55           740074         100           14301744         100           14301744         100           14301744         100           14301744         105           14301744         105           14301744         105           14301744         105           14301744         105	74(25)         2.99           74(26)         1.95           74(27)         1.95           74(27)         1.95           74(27)         1.95           74(27)         1.95           74(27)         2.90           74(27)         2.50           74(27)         2.50           74(27)         2.50           74(27)         2.50           74(27)         2.49           24(21)         2.49           24(21)         2.49           24(21)         2.49           24(21)         2.50           24(21)         1.25           24(21)         1.25           24(21)         1.25           24(21)         1.25           24(21)         1.25           24(21)         1.25           24(21)         1.25           24(21)         1.25           24(21)         1.25           24(21)         1.25           24(21)         1.25           24(21)         1.25           24(21)         1.25           24(21)         1.25           24(21)         1.25           24(21) </td <td>7/40161 2,49 7/40173 2,64 7/40173 2,49 7/40193 2,49 7/40198 2,49 7/40196 2,49 7/40196 2,49 7/40276 6,25 8/0096 1,50 4/0097 1,50 M/1100 75 150 M/1100 75 150 150 150 150 150 150 150 15</td> <td>MAK 6510         Common Anote-eninge mark 6510         560         99         5082-7304         Operatinge dustrier (±1)         600         15:00           RCA         LINDEAR         CALCULATOR CHIPS/DRIVERS         CALCULATOR CHIPS/DRIVERS         CLOCK CHIPS         MOTOROLA           6433137         2:15         GA39877         2:00         CALCULATOR CHIPS/DRIVERS         CLOCK CHIPS         MOTOROLA           CAUGUS         2:00         CAUGUS         2:00         MM3513         4:65         MOTOROLA           CAUGUS         1:00         CAUGUS         2:00         MM3513         4:65         MOTOROLA           CAUGUS         1:00         CAUGUS         1:00         MM3516         6:50         MOTOROLA           CAUGUS         1:00         CAUGUS         1:00         MM3516         6:50         MOTOROLA           CAUGUS         2:00         CAUGUS         1:20         MM8567         1:00         MM3516         6:50         MMC3057         3:00           CAUGUS         2:00         CAUGUS         1:20         MM8687         1:00         MM3516         6:50         MMC3057         3:00         2:00         MM3516         6:50         MMC4024P         3:00         CAUGUS         4:50</td> <td>1152/5         15         500n         28         111113         50         713         54,44           11455         25         7m         67,00         111113         50         7m         57,100         11111           11455         25         7m         67,00         111113         100         12,700         111111         111111         11111</td>	7/40161 2,49 7/40173 2,64 7/40173 2,49 7/40193 2,49 7/40198 2,49 7/40196 2,49 7/40196 2,49 7/40276 6,25 8/0096 1,50 4/0097 1,50 M/1100 75 150 M/1100 75 150 150 150 150 150 150 150 15	MAK 6510         Common Anote-eninge mark 6510         560         99         5082-7304         Operatinge dustrier (±1)         600         15:00           RCA         LINDEAR         CALCULATOR CHIPS/DRIVERS         CALCULATOR CHIPS/DRIVERS         CLOCK CHIPS         MOTOROLA           6433137         2:15         GA39877         2:00         CALCULATOR CHIPS/DRIVERS         CLOCK CHIPS         MOTOROLA           CAUGUS         2:00         CAUGUS         2:00         MM3513         4:65         MOTOROLA           CAUGUS         1:00         CAUGUS         2:00         MM3513         4:65         MOTOROLA           CAUGUS         1:00         CAUGUS         1:00         MM3516         6:50         MOTOROLA           CAUGUS         1:00         CAUGUS         1:00         MM3516         6:50         MOTOROLA           CAUGUS         2:00         CAUGUS         1:20         MM8567         1:00         MM3516         6:50         MMC3057         3:00           CAUGUS         2:00         CAUGUS         1:20         MM8687         1:00         MM3516         6:50         MMC3057         3:00         2:00         MM3516         6:50         MMC4024P         3:00         CAUGUS         4:50	1152/5         15         500n         28         111113         50         713         54,44           11455         25         7m         67,00         111113         50         7m         57,100         11111           11455         25         7m         67,00         111113         100         12,700         111111         111111         11111
P4004         39           74C08         49           74C11         195           74C20         39           74C21         195           74C23         39           74C24         195           74C32         289           74C44         295           74C47         89           74C64         296           74C64         195           1M301CNrH         35           1M302CNrH         106           LM3041         100           LM304171         150           LM314171         195           LM314171         195           LM3142071         135           LM32071         135	74(25)         2.49           74(26)         1.95           74(26)         1.95           74(26)         1.95           74(26)         1.95           74(26)         2.50           74(15)         2.50           74(15)         2.50           74(15)         2.50           74(15)         2.50           74(15)         2.50           74(15)         2.49           74(15)         2.49           74(15)         2.49           74(15)         1.35           1.43(26)         1.25           1.43(26)         1.25           1.43(26)         1.25           1.43(26)         1.25           1.43(27)         1.25           1.43(27)         1.60           1.43(27)         1.60           1.43(27)         1.60           1.43(27)         1.60           1.43(27)         1.60           1.43(27)         1.60           1.43(27)         1.60           1.43(27)         1.60           1.43(27)         1.60           1.43(27)         1.60           1.43(28)         1.73 <td>740161         2.49           740173         2.69           740173         2.69           740193         2.49           740193         2.49           740193         2.49           740193         2.49           740205         5.29           740325         6.29           740325         6.29           740325         5.20           740337         1.50           00597         1.50           00597         1.50           1047110         73           11473140         73           11473141         73           114747044         73           114747044         73           114747044         73           114747044         73           114747044         73           114747044         73           114747044         73           114747044         73           114747044         74           114747044         74           11471804         74           11471804         74           11418040         74           11418040         74           1</td> <td>MMA 6510         Common Anote-eninge market (1)         560         99         5082-7304         Operange duscret (1)         600         15 00           RCA         LINEBAR         CALCULATOR CHIPS/DRIVERS         COLOR CHIPS         MOTOBOLA           240337         256         CABBAN         1.00         MM3725         87.95         MM3311         4.67         MOTOBOLA           240337         256         CABBAN         1.00         MM3725         87.95         MM3311         4.69         MOTOBOLA           240337         256         CABBAN         1.00         MM3725         87.95         MM3311         4.69         MUT18017         5.495           243337         1.30         CABBAN         1.20         MM3712         2.96         MM3316         6.96         MUT18017         3.90           CAMBON         3.20         CABBON         1.30         MM3318         9.95         MUC10167/4116         7.50           CAMBON         3.25         CABBON         9.97         MM8387         1.99         MUC10400F         4.50           CABON         3.20         CALED driver         1.50         MM3387         9.95         MUC1040F         4.50           CABON         3.20<td>IN3254         15         500m         28         IN1153         50 PV 35 AuP         1.70           IN455         25         40m         67.00         IN1185         150 PV 35 AuP         1.70           IN455         150         7m         67.00         IN1185         150 PV 35 AuP         1.70           IN455         150         7m         67.00         IN1185         150 PV 35 AuP         1.70           IN485A         160 Dm         32.10         IN1186         150 PV 35 AuP         1.80           SCR AND FW BRIDGE RECTIFIERS         C360         1.54 # 300V         SCR(X11493)         51.95           C380         35.4 # 60V         SCR         1.84         1.80         1.80           C081         3.5         TRANSISTORS         1.83         1.95           C081         3.5         TRANSISTORS         1.83         4.100           MPS05         1.00         2.84 90V         FW BRIDGE REC         1.95           T1597         ST1.00         2.84 90V         FW BRIDGE RC         1.95           MPS05         1.00         2.84 90V         FW BRIDGE RC         1.95           M140         1.75         PM3555         1.00         2.84 90V</td></td>	740161         2.49           740173         2.69           740173         2.69           740193         2.49           740193         2.49           740193         2.49           740193         2.49           740205         5.29           740325         6.29           740325         6.29           740325         5.20           740337         1.50           00597         1.50           00597         1.50           1047110         73           11473140         73           11473141         73           114747044         73           114747044         73           114747044         73           114747044         73           114747044         73           114747044         73           114747044         73           114747044         73           114747044         74           114747044         74           11471804         74           11471804         74           11418040         74           11418040         74           1	MMA 6510         Common Anote-eninge market (1)         560         99         5082-7304         Operange duscret (1)         600         15 00           RCA         LINEBAR         CALCULATOR CHIPS/DRIVERS         COLOR CHIPS         MOTOBOLA           240337         256         CABBAN         1.00         MM3725         87.95         MM3311         4.67         MOTOBOLA           240337         256         CABBAN         1.00         MM3725         87.95         MM3311         4.69         MOTOBOLA           240337         256         CABBAN         1.00         MM3725         87.95         MM3311         4.69         MUT18017         5.495           243337         1.30         CABBAN         1.20         MM3712         2.96         MM3316         6.96         MUT18017         3.90           CAMBON         3.20         CABBON         1.30         MM3318         9.95         MUC10167/4116         7.50           CAMBON         3.25         CABBON         9.97         MM8387         1.99         MUC10400F         4.50           CABON         3.20         CALED driver         1.50         MM3387         9.95         MUC1040F         4.50           CABON         3.20 <td>IN3254         15         500m         28         IN1153         50 PV 35 AuP         1.70           IN455         25         40m         67.00         IN1185         150 PV 35 AuP         1.70           IN455         150         7m         67.00         IN1185         150 PV 35 AuP         1.70           IN455         150         7m         67.00         IN1185         150 PV 35 AuP         1.70           IN485A         160 Dm         32.10         IN1186         150 PV 35 AuP         1.80           SCR AND FW BRIDGE RECTIFIERS         C360         1.54 # 300V         SCR(X11493)         51.95           C380         35.4 # 60V         SCR         1.84         1.80         1.80           C081         3.5         TRANSISTORS         1.83         1.95           C081         3.5         TRANSISTORS         1.83         4.100           MPS05         1.00         2.84 90V         FW BRIDGE REC         1.95           T1597         ST1.00         2.84 90V         FW BRIDGE RC         1.95           MPS05         1.00         2.84 90V         FW BRIDGE RC         1.95           M140         1.75         PM3555         1.00         2.84 90V</td>	IN3254         15         500m         28         IN1153         50 PV 35 AuP         1.70           IN455         25         40m         67.00         IN1185         150 PV 35 AuP         1.70           IN455         150         7m         67.00         IN1185         150 PV 35 AuP         1.70           IN455         150         7m         67.00         IN1185         150 PV 35 AuP         1.70           IN485A         160 Dm         32.10         IN1186         150 PV 35 AuP         1.80           SCR AND FW BRIDGE RECTIFIERS         C360         1.54 # 300V         SCR(X11493)         51.95           C380         35.4 # 60V         SCR         1.84         1.80         1.80           C081         3.5         TRANSISTORS         1.83         1.95           C081         3.5         TRANSISTORS         1.83         4.100           MPS05         1.00         2.84 90V         FW BRIDGE REC         1.95           T1597         ST1.00         2.84 90V         FW BRIDGE RC         1.95           MPS05         1.00         2.84 90V         FW BRIDGE RC         1.95           M140         1.75         PM3555         1.00         2.84 90V
P4004         39           P4008         49           P4008         49           P4008         49           P4008         49           P4011         195           P40214         195           P4024         195           P4024         195           P4024         49           P4044         50           LM3064         100           LM3064         100           LM3064         100           LM31644         50<	74(25)         2.99           74(26)         1.95           74(27)         1.95           74(27)         1.95           74(27)         1.95           74(27)         1.95           74(27)         1.5           74(15)         2.90           74(15)         2.90           74(15)         2.49           24(16)         2.49           24(16)         2.49           24(16)         1.25           24(16)         1.25           24(16)         1.25           24(16)         1.25           24(16)         1.25           24(16)         1.25           24(16)         1.25           24(16)         1.25           24(16)         1.25           24(16)         1.25           24(16)         1.25           24(16)         1.25           24(16)         1.25           24(16)         1.25           24(16)         1.25           24(16)         1.25           24(17)         1.25           24(17)         1.25           24(17)         1.25           24(17) <td>74C161         2.49           74C173         2.49           74C173         2.49           74C193         2.49           74C193         2.49           74C193         2.49           74C193         2.49           74C193         6.25           74C193         6.25           74C193         6.25           74C193         6.25           74C193         7.10           740376         6.25           7470376         6.25           7470376         7.50           1407170         7           1407170         7           1407304         10           1407304         10           1407304         13           140747044         13           140747044         13           140747044         13           140747044         13           140747044         13           140747044         13           140747044         13           140747044         13           140747044         13           140747044         13           140747044         13           14</td> <td>MMA 6910         Common Another energy (MMA 6710         Sold (MMA 6710)         Centraling efficiency (MMA 6710)         Centraling efficiency (MMA 6710)         Centraling efficiency (MMA 6710)         Control (MMA 6710)         C</td> <td>IN3254         15         500m         28         IN1193         50         PV3 54 AUP         1.00           IN455         25         40m         61.00         IN1185         150         PV3 54 AUP         1.70           IN455         25         7m         67.00         IN1185         150         PV3 54 AUP         1.70           IN455         150         7m         67.00         IN1185         150         PV3 54 AUP         1.70           IN4854         160         TAT         127.10         IN1186         150         PV3 54 AUP         1.80           SCR         AND         FW         BAUD         SCR         1.90         1.91           CABD         154         04         VD         SCR(2V11494)         31.95           CABD         1.54         040V         SCR         1.95         1.95           SM2285         1.64         00V         SCR         1.95         1.95           SM24390         1.22         0.90         FW BHDDE REC         1.95           MPSA05         71.00         PV1350         .85         2.8305         4.10.00           MPSA05         71.00         PV13505         .85         2</td>	74C161         2.49           74C173         2.49           74C173         2.49           74C193         2.49           74C193         2.49           74C193         2.49           74C193         2.49           74C193         6.25           74C193         6.25           74C193         6.25           74C193         6.25           74C193         7.10           740376         6.25           7470376         6.25           7470376         7.50           1407170         7           1407170         7           1407304         10           1407304         10           1407304         13           140747044         13           140747044         13           140747044         13           140747044         13           140747044         13           140747044         13           140747044         13           140747044         13           140747044         13           140747044         13           140747044         13           14	MMA 6910         Common Another energy (MMA 6710         Sold (MMA 6710)         Centraling efficiency (MMA 6710)         Centraling efficiency (MMA 6710)         Centraling efficiency (MMA 6710)         Control (MMA 6710)         C	IN3254         15         500m         28         IN1193         50         PV3 54 AUP         1.00           IN455         25         40m         61.00         IN1185         150         PV3 54 AUP         1.70           IN455         25         7m         67.00         IN1185         150         PV3 54 AUP         1.70           IN455         150         7m         67.00         IN1185         150         PV3 54 AUP         1.70           IN4854         160         TAT         127.10         IN1186         150         PV3 54 AUP         1.80           SCR         AND         FW         BAUD         SCR         1.90         1.91           CABD         154         04         VD         SCR(2V11494)         31.95           CABD         1.54         040V         SCR         1.95         1.95           SM2285         1.64         00V         SCR         1.95         1.95           SM24390         1.22         0.90         FW BHDDE REC         1.95           MPSA05         71.00         PV1350         .85         2.8305         4.10.00           MPSA05         71.00         PV13505         .85         2
P4004         39           74008         49           74008         49           74008         49           74008         49           74011         195           74020         39           74030         1.95           74030         39           7404         1.95           74030         1.95           7404         2.49           7404         89           7404         75           7404         75           7404         75           74040         80           74040         75           7403010000         80           74030100000         80           74030100000         1.00           740301000000         1.00           7403010000000000000000         1.00           740300000000000000000000000000000000000	74(25)         2.90           74(26)         1.95           74(26)         1.95           74(27)         1.95           74(27)         1.95           74(27)         1.95           74(27)         1.5           74(15)         2.90           74(15)         2.15           74(15)         2.49           74(15)         1.35           1.430(47)         1.35           1.430(47)         1.25           1.430(47)         1.25           1.430(47)         1.25           1.430(47)         1.25           1.430(47)         1.25           1.430(47)         1.25           1.430(47)         1.25           1.430(47)         1.25           1.430(47)         1.25           1.430(47)         1.25           1.430(47)         1.25           1.430(47)         1.55           1.431(47)         1.55           1.431(47)         1.55           1.431(47)         1.55           1.431(47)         1.55           1.431(47)         1.55           1.431(47)         1.55           1.431(47)	740161 2 49 740173 2 49 740173 2 49 740173 2 49 740173 2 49 740178 2 49 740178 2 49 740178 2 49 740178 2 49 740278 49 10 10 10 10 10 10 10 10 10 10 10 10 10	MMA 6910         Common Another energy (MMA 6910)         Sold (MMA 6910)         Contractions and (MMA 6910) <thcontractions (mma="" 691<="" and="" td=""><td>IN3254         15         500m         28         IN1183         50 PV 35 AuP         1.00           IN455         25         40m         6/1.00         IN1185         150 PV 35 AuP         1.70           IN455         150         7m         6/1.00         IN1185         150 PV 35 AuP         1.70           IN455         150         7m         6/1.00         IN1185         150 PV 35 AuP         1.70           IN485A         160         10m         12/1.00         IN1186         00 PV 35 AuP         1.80           SCR         AND         FW BRIDGE RECE         FISH         50         1.93         1.93         1.93           C380         154 # 600V         SCR(PH1849)         T.1.95         50         1.95         50         1.95         50         1.95         50         1.95         50         1.95         50         1.95         50         1.95         50         1.95         1.95         50         1.90         1.93         50         1.90         1.93         50         1.90         1.93         50         1.90         1.90         1.90         1.90         1.90         1.90         1.90         1.90         1.90         1.90         1.90</td></thcontractions>	IN3254         15         500m         28         IN1183         50 PV 35 AuP         1.00           IN455         25         40m         6/1.00         IN1185         150 PV 35 AuP         1.70           IN455         150         7m         6/1.00         IN1185         150 PV 35 AuP         1.70           IN455         150         7m         6/1.00         IN1185         150 PV 35 AuP         1.70           IN485A         160         10m         12/1.00         IN1186         00 PV 35 AuP         1.80           SCR         AND         FW BRIDGE RECE         FISH         50         1.93         1.93         1.93           C380         154 # 600V         SCR(PH1849)         T.1.95         50         1.95         50         1.95         50         1.95         50         1.95         50         1.95         50         1.95         50         1.95         50         1.95         1.95         50         1.90         1.93         50         1.90         1.93         50         1.90         1.93         50         1.90         1.90         1.90         1.90         1.90         1.90         1.90         1.90         1.90         1.90         1.90
P4004         39           74008         49           74008         49           74008         49           74008         49           74011         195           74020         39           74021         195           74033         245           74046         246           74046         246           74046         195           141064         95           141064         95           141064         95           141064         95           141064         95           141064         95           141064         95           141064         100           141064         100           141064         100           141067         100           141067         100           141067         100           141067         100           141067         100           141077         100           1410777         100           1410777         100           1410777         100           1410777         100	74C35         2.49           74C30         1.95           74C30         1.95           74C30         1.95           74C30         1.95           74C35         2.90           74C151         1.33           1.43407-18         1.25           1.43407-17         1.25           1.43407-18         1.25           1.43407-18         1.25           1.43407-19         1.25           1.43407-19         1.26           1.43407-19         1.26           1.43407-19         1.25           1.43407-19         1.25           1.43407-19         1.26           1.43407-19         1.26           1.43407-19         1.26           1.43407-19         1.26           1.43407-19 <td< td=""><td>74C161         2.49           74C172         2.49           74C192         2.49           74C193         2.49           74C193         2.49           74C193         2.49           74C192         2.49           74C192         5.29           74C192         6.29           74C192         6.29           74C192         6.29           74C193         6.25           74C92         5.00           00597         150           00597         150           1473104         10           147314         10           147314         10           147314         10           147314         10           14747144         13           14747144         13           14747144         13           14747144         13           14747144         13           14747144         13           14747144         13           14747144         13           14747144         13           14747144         13           14747144         13           14747144</td><td>MMA 6910         Common Another enging         560         99         5082-7304         Overange dustart (1)         600         15 00           RCA         LINESA         CALCULATOR         CALCULATOR         CLOCK CHPS         MOTOROLA           CA30211         2.15         GA308011         2.00         CALCULATOR         CLOCK CHPS         MOTOROLA           CA30211         2.15         GA308011         2.00         CALSCHATOR         CLOCK CHPS         MOTOROLA           CA30317         2.18         CAJOBEN         2.00         CALCULATOR         CLOCK CHPS         MOTOROLA           CA30317         2.18         CAJOBEN         2.00         MMS728         2.96         MMS311         4.50         MC10817         2.95           CA3064N         1.30         CAJABEN         2.00         MM8578         2.00         MMS311         4.50         MC300167         3.90           CA3064N         3.20         CAJABEN         3.90         CAJABE</td><td>1152/25         15         500m         28         111/153         50 PV 35 AuP         1.00           114/55         150         7m         6/1.00         111/153         10 PV 35 AuP         1.70           114/55         150         7m         6/1.00         111/153         150 PV 35 AuP         1.70           114/55         150         7m         6/1.00         111/153         150 PV 35 AuP         1.70           114/65         150         PV 1 AuP         12/1.00         111/164         400 PV 35 AuP         3.00           SCR AND FW BRIDGE RECTIFIERS           C360         154/19/40V         SCR         1.54           C4810         3.54         600V         SCR         1.55           20429         204         PW BHDDE REC         1.95           11526         1.54         600V         SCR         1.95           11636         30         PAROSE         1.95         2.93         41 00           MPSA05         31         2.84 92         AV         9.94         9.10         1.95           1100         2.93 89         1.10         2.94 393         41 00         1.95         1.95           1100         <t< td=""></t<></td></td<>	74C161         2.49           74C172         2.49           74C192         2.49           74C193         2.49           74C193         2.49           74C193         2.49           74C192         2.49           74C192         5.29           74C192         6.29           74C192         6.29           74C192         6.29           74C193         6.25           74C92         5.00           00597         150           00597         150           1473104         10           147314         10           147314         10           147314         10           147314         10           14747144         13           14747144         13           14747144         13           14747144         13           14747144         13           14747144         13           14747144         13           14747144         13           14747144         13           14747144         13           14747144         13           14747144	MMA 6910         Common Another enging         560         99         5082-7304         Overange dustart (1)         600         15 00           RCA         LINESA         CALCULATOR         CALCULATOR         CLOCK CHPS         MOTOROLA           CA30211         2.15         GA308011         2.00         CALCULATOR         CLOCK CHPS         MOTOROLA           CA30211         2.15         GA308011         2.00         CALSCHATOR         CLOCK CHPS         MOTOROLA           CA30317         2.18         CAJOBEN         2.00         CALCULATOR         CLOCK CHPS         MOTOROLA           CA30317         2.18         CAJOBEN         2.00         MMS728         2.96         MMS311         4.50         MC10817         2.95           CA3064N         1.30         CAJABEN         2.00         MM8578         2.00         MMS311         4.50         MC300167         3.90           CA3064N         3.20         CAJABEN         3.90         CAJABE	1152/25         15         500m         28         111/153         50 PV 35 AuP         1.00           114/55         150         7m         6/1.00         111/153         10 PV 35 AuP         1.70           114/55         150         7m         6/1.00         111/153         150 PV 35 AuP         1.70           114/55         150         7m         6/1.00         111/153         150 PV 35 AuP         1.70           114/65         150         PV 1 AuP         12/1.00         111/164         400 PV 35 AuP         3.00           SCR AND FW BRIDGE RECTIFIERS           C360         154/19/40V         SCR         1.54           C4810         3.54         600V         SCR         1.55           20429         204         PW BHDDE REC         1.95           11526         1.54         600V         SCR         1.95           11636         30         PAROSE         1.95         2.93         41 00           MPSA05         31         2.84 92         AV         9.94         9.10         1.95           1100         2.93 89         1.10         2.94 393         41 00         1.95         1.95           1100 <t< td=""></t<>
P4004         39           74008         49           74008         49           74008         49           74008         49           7401         195           74020         39           74042         1.95           7400         39           7404         1.95           7400         39           7404         1.95           7406         1.75           14106         99           74074         89           74074         89           74074         89           74074         89           74074         75           1403010000         1.05           1403070000         1.05           1403070000         1.25           1403070000         1.25           140307000         1.35           140307000         1.35           140307000         1.35           140307000         1.35           140307000         1.35           140307000         1.35           140307000         1.35           140307000         1.35           140307000	74(25) 2.49 74(28) 1.95 74(29) 1.95 74(27) 1.95 74(27) 1.95 74(27) 1.95 74(27) 2.15 74(27) 2.15 74(27) 2.15 74(27) 2.15 74(27) 2.15 74(27) 2.15 74(27) 2.15 74(27) 2.15 74(27) 2.15 74(27) 2.49 <b>LINECAR</b> LM340(7-12) 2.49 <b>LM340(7-12)</b> 2.55 LM340(7-12) 2.55 LM340(7	74C161         2.49           74C173         2.64           74C173         2.49           74C193         2.49           74C193         2.49           74C193         2.49           74C193         2.49           74C193         6.25           74C193         6.25           74C193         6.25           74C193         6.25           74C193         7.14           74C193         7.14           74C193         6.25           7470376         6.25           7470376         1.50           147110         7           147374         1.01           147374         1.01           147374         1.02           147374         1.32           147474         1.32           147474744         1.32           147474744         1.39           147474744         1.39           147474744         1.39           147474744         1.39           147474744         1.39           147474744         1.39           147474744         1.39           147474744         1.39	MMA 6910         Common Anote-eninge market (1)         560         99         5082-7304         Operatinge dual cert (1)         600         15:00           RCA         LINDEAR         CALCULATOR CHIPS/DRIVERS         Calculator 4 x 7 Set 05, Hereadee         MOTOROLA           CAUSIT         2 15         GAUSIN         2 00         12.05         MAX 510         13:00         4 x 7 Set 05, Hereadee         MOTOROLA           CAUSIT         2 15         GAUSIN         2 00         MS313         4 50         MC10010         5 4 95           CAUSIT         2 15         GAUSIN         2 00         MS313         4 50         MC10010         5 4 95           CAUSIN         1 30         GAUSIN         1 30         MAX 510         5 95         MC40167/4167         7 50           CAUSIN         3 50         CAUSIN         9 95         MC40167/4167         7 50         MMS318         9 95         MC40167/4167         7 50           CAUSIN         2 50         CAUSIN         9 97         7 7 80         MMS318         9 95         MC40167/4167         7 50           CAUSIN         2 50         CAUSIN         9 50         MC40167/4167         7 50         MMS318         9 95         MC40167/4167         7 50	11525         15         500m         28         111183         50         703         54,00           11455         25         7m         67,00         11118         50         7m         57,00         1,70           11455         25         7m         67,00         11118         150         7m         57,00         11118         50         7m         57,00         11118         50         7m         57,00         11118         50         7m         50,00         151         11118         50         7m         53,00         151         11118         50         7m         50,00         151         11118         50         7m         53,00         11118         50         7m         7m         7m         50         7m         7m<
P4004         39           74008         49           74008         49           74008         49           74008         49           74011         195           74020         39           74030         195           74030         195           74030         195           74040         195           74030         175           74030         175           74030         175           74030         175           74030         100           14106H         95           14106H         95           1413070H         100           141308H         100           141320H         195           141320H         195           141320H         105      <	74(25) 2.49 74(28) 1.95 74(29) 1.95 74(27) 1.95 74(27) 1.95 74(27) 2.15 74(27) 2.15 74(25) 2.5 74(25) 2.5 75 75 75 75 75 75 75 75 75 75 75 75 75	74C161         2.49           74C173         2.49           74C173         2.49           74C193         6.95           740275         6.95           740376         6.95           740376         9.95           740376         9.95           740376         9.95           740376         9.95           740376         9.95           740376         9.95           740376         1.90           147731704         7.8           147731714         1.9           147731714         1.9           1477417141         1.9           147741714         1.9           147741714         1.9           147741714         1.9           147741714         1.9           1477417144         1.9           1477417144         1.9           1477417144         1.9	MM 6910       Common Anote-eninge marker (1)       560       99       5082-7304       Operatinge dual cert (1)       600       1500         RCA       LINEEAR       CALCULATOR CHIPS/DRIVERS       Currentinge dual cert (1)       600       1500         RCA       LINEEAR       CALCULATOR CHIPS/DRIVERS       Currentinge dual cert (1)       600       1500         CAUSING       2.00       MM3725       82.99       MM3713       2.46       MOTOBOLA         CAUSING       1.30       CAUSING       2.00       MM3725       82.99       MM3311       4.56       MOTOBOLA         CAUSING       1.30       CAUSING       1.30       KM3319       2.90       MM3316       6.56       MOTOBOLA         CAUSING       1.32       CAUSING       1.30       CAUSING       9.90       Metallity       9.90       9.90       9.90       9.90       9.90       9.90       9.90       9.90       9.90       9.90       9.90       9.90       9.90       9.90       9.90       9.90	15:25:25         15         500m         28         111133         50 PV 35 AuP         1.00           11:45:56         25         40m         67.00         11:18         150 PV 35 AuP         1.70           11:45:56         150         7m         67.00         11:18         150 PV 35 AuP         1.70           11:45:56         150         7m         67.00         11:18         150 PV 35 AuP         1.70           11:46:56         150         PV 35 AuP         127.00         11:18         400 PV 35 AuP         3.00           C36D         154:07         127.00         11:18         400 PV 35 AuP         3.1.95           C28D         154:07         00V         5CR         1.95         3.1.95           C28D         154:07         00V         5CR         1.95         3.1.95           C08D         12A:07         PV BIDDE REC         1.95         3.1.95           C08D         12A:07         PV BIDDE REC         1.95         4.11.00           MPSA05         71:00         PV SA05         1.00         2.94395         4.11.00           MPSA05         71:00         PV SA05         1.00         2.94490         4.10.00           MPSA05
P4004         39           74008         49           74008         49           74008         49           74008         49           74011         195           74020         39           74021         195           74031         295           74042         295           74043         295           74044         295           74046         195           1403010         195           1403010         100           1403010         100           1403010         100           1403010         100           1403010         100           1403010         100           1403010         100           1403010         100           1403010         100           1403010         100           1403010         100           1403010         100           1403010         100           1403010         100           1403010         100           1403010         100           1403110         100           1403110         100 </td <td>74(25)         2.49           74(26)         1.95           74(27)         1.95           74(26)         1.95           74(27)         1.95           74(25)         2.50           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.15           141(10)         1.25           143(10)         1.25           143(10)         1.25           143(10)         1.25           143(10)         1.25           143(10)         1.25           143(10)         1.25           143(10)         1.25           143(10)         1.25           143(10)         1.25           143(10)         1.25           143(10)         1.25           143(10)         1.25           143(10)         1.25           143(10)         1.25</td> <td>740161         2.49           740173         2.649           740173         2.649           740193         2.49           740193         2.49           740193         2.49           740193         2.49           740193         6.25           74022         5.95           74033         6.25           74033         1.9           00097         1.50           1.40356         6.25           1.40356         1.50           0.47110         78           1.47327         1.50           1.47337         1.9           1.474274         3.5           1.474744         3.5           1.474744         3.6           1.474744         3.9           1.474744         3.9           1.474744         3.9           1.474744         3.9           1.474744         3.9           1.474744         3.9           1.474744         3.9           1.474744         3.9           1.474744         3.9           1.474744         3.9           1.4747444         3.9</td> <td>MMA 6910       Common Another energy of the second se</td> <td>1152/5         15         500n         28         111113         50         703         54,00           11455         25         7m         67,00         11118         150         7m         67,00         11118         150         7m         67,00         11118         150         7m         67,00         11118         50         7m         67,00         11118         50         7m         50         7m         7m         67,00         11118         50         7m         50         7m         7m</td>	74(25)         2.49           74(26)         1.95           74(27)         1.95           74(26)         1.95           74(27)         1.95           74(25)         2.50           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.15           141(10)         1.25           143(10)         1.25           143(10)         1.25           143(10)         1.25           143(10)         1.25           143(10)         1.25           143(10)         1.25           143(10)         1.25           143(10)         1.25           143(10)         1.25           143(10)         1.25           143(10)         1.25           143(10)         1.25           143(10)         1.25           143(10)         1.25	740161         2.49           740173         2.649           740173         2.649           740193         2.49           740193         2.49           740193         2.49           740193         2.49           740193         6.25           74022         5.95           74033         6.25           74033         1.9           00097         1.50           1.40356         6.25           1.40356         1.50           0.47110         78           1.47327         1.50           1.47337         1.9           1.474274         3.5           1.474744         3.5           1.474744         3.6           1.474744         3.9           1.474744         3.9           1.474744         3.9           1.474744         3.9           1.474744         3.9           1.474744         3.9           1.474744         3.9           1.474744         3.9           1.474744         3.9           1.474744         3.9           1.4747444         3.9	MMA 6910       Common Another energy of the second se	1152/5         15         500n         28         111113         50         703         54,00           11455         25         7m         67,00         11118         150         7m         67,00         11118         150         7m         67,00         11118         150         7m         67,00         11118         50         7m         67,00         11118         50         7m         50         7m         7m         67,00         11118         50         7m         50         7m
P4004         39           74008         49           74008         49           74008         49           74008         49           74011         195           74020         39           74021         195           74023         39           74024         245           74024         245           74024         245           7403         175           14106H         99           141300H         80           141300H         60           141300H         60           141300H         10           141311H/H         10	74(25) 2.49 74(28) 1.95 74(29) 1.95 74(27) 1.95 74(27) 1.95 74(27) 2.15 74(27) 2.5 74(27) 2.5 75 74(27) 2.5 75 75 75 75 75 75 75 75 75 75 75 75 75	740161         2.49           740173         2.649           740173         2.49           740173         2.49           740173         2.49           740173         2.49           740173         2.49           740173         2.49           740376         5.55           740376         5.55           740376         5.55           740376         5.55           740376         5.55           740376         5.55           740376         1.50           1.4771704         73           1.4773747         1.0           1.4773747         1.0           1.47747047         1.39           1.47747047         1.39           1.47747047         1.39           1.47747047         1.39           1.47747047         1.39           1.47747047         1.39           1.47747047         1.39           1.47747047         1.39           1.47747047         1.39           1.47747047         1.39           1.47747047         1.39           1.41456047         1.39           1.41456047	MM 6910       Common Anote-eninge marker (1)       560       99       5082-7304       Operatinge dual cert (1)       600       1500         RCA       LINEEAR       CALCULATOR CHIPS/DRIVERS       Currentinge dual cert (1)       600       1500         RCA       LINEEAR       CALCULATOR CHIPS/DRIVERS       Currentinge dual cert (1)       600       1500         CAUSING       2.00       MM3725       82.99       MM3713       2.46       MOTOBOLA         CAUSING       1.30       CAUSING       2.00       MM3725       82.99       MM3311       4.56       MOTOBOLA         CAUSING       1.30       CAUSING       1.30       KM3319       2.90       MM3316       6.56       MOTOBOLA         CAUSING       1.32       CAUSING       1.30       CAUSING       9.90       Metallity       9.90       9.90       9.90       9.90       9.90       9.90       9.90       9.90       9.90       9.90       9.90       9.90       9.90       9.90       9.90       9.90	1152/5         15         500n         28         111113         50         703         54,00           11455         25         70n         67,00         11118         150         713         54,00         1,70           11455         25         70n         67,00         11118         150         713         54,00         1,70           11455         150         70n         67,00         11118         400         713         34,00         1,70           11456         150         174         400         713         34,00         713         34,00         71,150         711         71,150         711         71,150         711         71,150         711         71,150         711         71,150         711         71,150         711,00         711,150         71,150         71,150         71,150         71,150         71,150         71,150         71,150         71,150         71,150         71,150         71,150         71,150         71,150         71,150         71,150         71,100         71,173         71,150         71,100         71,173         71,100         71,173         71,100         71,173         71,100         71,1745         71,100         71,100
P4004         39           74008         49           74008         49           74008         49           74008         49           74008         49           74001         195           74020         39           74001         195           74001         195           74001         195           74001         175           74001         175           14106H         95           14106H         100           14106H         100           14106H         100           1410070H         100           141070H         100	74(25)         2.49           74(26)         1.95           74(27)         1.95           74(27)         1.95           74(27)         1.95           74(27)         2.15           74(15)         2.00           74(15)         2.01           74(15)         2.15           74(15)         2.49 <b>LINEEAR</b> 1.35           LM300-18         1.35           LM300-17         1.25           LM300-18         1.00           M65000         .00	740161         2.49           740173         2.649           740173         2.49           740173         2.49           740173         2.49           740173         2.49           740173         2.49           740173         2.49           740173         2.49           740173         2.69           740275         6.55           80056         1.50           00037         1.50           UM7100         7           UM7101         10           UM7304         10           UM7304         10           UM7404         13	MM 8900       Common Another energy       560       99       5982-734       Overange Puracer (L1)       600       1500         RCA       LINDEAR       CALCULATOR       CLOCK CHPS       MOTOROLA         CA30317       215       GA30581       200       200       2582-734       Overange Puracer (L1)       600       2500         CA30317       215       GA30581       200       CALCULATOR       CLOCK CHPS       MOTOROLA         CA30317       215       GA30581       200       MM 5736       229       MM 5316       650       MOTOROLA         CA30397       235       CA31607       129       MM 5316       650       MOTOROLA       900       710         CA30598       325       CA31607       129       MM 5316       650       MC30076       320         CA30601       325       CA31607       129       MM 5377       729       MM 5316       650       MC30076       730         MM 5316       CA3107       129       MM 5377       729       MM 5316       650       MC3016744161       730         CA3060       325       CA3107       129       MC3016744167       730       MM 5316       650       730       730       730<	IN-256         25         00m         28         IN-118         50         PV3.54.44         1.70           IN-256         25         00m         67.00         IN-118         150         PV3.54.44         1.70           IN-256         25         7m         67.00         IN-118         150         PV3.54.44         1.70           IN-256         25         7m         67.00         IN-118         400         PV3.54.44         1.70           IN-256         27.00         IN-118         400         PV3.54.44         1.70         IN-118         400         PV3.54.44         1.90           C280         354.18         600V         SCR         1.95         1.
P4004         39           74008         49           74008         49           74008         49           74001         195           74020         39           74021         195           74023         39           74024         195           74024         245           74024         245           74024         245           74036         1.75           141064         99           14130024         80           14130044         60           14130044         60           14130044         10           14130044         10           14130044         10           14130044         10           14130044         10           14130044         10           14130044         10           14130044         10           14130044         10           14130044         10           14130044         10           14130044         10           14130044         10           14130044         10           14131144         10 <td>74(25)         2.49           74(26)         1.95           74(26)         1.95           74(26)         1.95           74(26)         1.95           74(26)         2.15           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.49           74(15)         1.35           1.4140(-6-2)         1.25           1.4140(-6)         1.25           1.4140(-6)         1.25           1.4140(-6)         1.25           1.4140(-7)         1.25           1.4140(-7)         1.25           1.4140(-7)         1.25           1.4140(-7)         1.25           1.4140(-7)         1.25           1.4150(-7)         1.95           1.4150(-7)         1.95           1.4150(-7)         1.95           1.4150(-7)         1.95           1.4150(-7)         1.95           1.4150(-7)         1.95           1.4150(-7)         1.95           1.4150(-7)         1.95           1.4</td> <td>74C161         2.49           74C173         2.649           74C173         2.49           74C193         2.49           74C193         2.49           74C193         2.49           74C193         6.25           74C193         6.25           74C193         6.25           74C193         6.25           74C193         7.14           60059         1.50           1470376         1.59           1471170         7           1473374         1.51           1473374         1.51           1473374         1.51           1473374         1.51           147474744         3.24           147474744         3.24           147474744         3.24           147474744         1.39           147474744         1.39           147474744         1.39           147474744         1.39           147474744         1.39           147474744         1.39           147474744         1.39           147474744         1.39           147474744         1.39           1474747444         1.39<!--</td--><td>MMA 6970       Common Another energy 500       560       99       5002-7304       Operating enurgy (1,1)       600       1500         RCA LINEAR       CALCULATOR       CALCULATOR       CUCCCHPS       MS309       94       MC1401.7       54.95         CAUSITI       2.10       CAUSITI       2.00       CAUSITI       2.00       MUSTIN       2.00<td>1152/5         15         500m         28         111113         50         703         54,00           11455         25         70m         67,00         11118         150         713         54,00         1,70           11465         150         70m         67,00         11118         150         713         54,00         1,70           11465         150         70m         67,00         11118         400         713         34,00         713         34,00         713         34,00         713         34,00         713         34,00         713         34,00         713         34,00         713         34,00         713         71,00         71118         71,00         71118         71,00         71118         71,00         71118         71,00         71118         71,00         71118         71,00         71118         71,00         711,00</td></td></td>	74(25)         2.49           74(26)         1.95           74(26)         1.95           74(26)         1.95           74(26)         1.95           74(26)         2.15           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.00           74(15)         2.49           74(15)         1.35           1.4140(-6-2)         1.25           1.4140(-6)         1.25           1.4140(-6)         1.25           1.4140(-6)         1.25           1.4140(-7)         1.25           1.4140(-7)         1.25           1.4140(-7)         1.25           1.4140(-7)         1.25           1.4140(-7)         1.25           1.4150(-7)         1.95           1.4150(-7)         1.95           1.4150(-7)         1.95           1.4150(-7)         1.95           1.4150(-7)         1.95           1.4150(-7)         1.95           1.4150(-7)         1.95           1.4150(-7)         1.95           1.4	74C161         2.49           74C173         2.649           74C173         2.49           74C193         2.49           74C193         2.49           74C193         2.49           74C193         6.25           74C193         6.25           74C193         6.25           74C193         6.25           74C193         7.14           60059         1.50           1470376         1.59           1471170         7           1473374         1.51           1473374         1.51           1473374         1.51           1473374         1.51           147474744         3.24           147474744         3.24           147474744         3.24           147474744         1.39           147474744         1.39           147474744         1.39           147474744         1.39           147474744         1.39           147474744         1.39           147474744         1.39           147474744         1.39           147474744         1.39           1474747444         1.39 </td <td>MMA 6970       Common Another energy 500       560       99       5002-7304       Operating enurgy (1,1)       600       1500         RCA LINEAR       CALCULATOR       CALCULATOR       CUCCCHPS       MS309       94       MC1401.7       54.95         CAUSITI       2.10       CAUSITI       2.00       CAUSITI       2.00       MUSTIN       2.00<td>1152/5         15         500m         28         111113         50         703         54,00           11455         25         70m         67,00         11118         150         713         54,00         1,70           11465         150         70m         67,00         11118         150         713         54,00         1,70           11465         150         70m         67,00         11118         400         713         34,00         713         34,00         713         34,00         713         34,00         713         34,00         713         34,00         713         34,00         713         34,00         713         71,00         71118         71,00         71118         71,00         71118         71,00         71118         71,00         71118         71,00         71118         71,00         71118         71,00         711,00</td></td>	MMA 6970       Common Another energy 500       560       99       5002-7304       Operating enurgy (1,1)       600       1500         RCA LINEAR       CALCULATOR       CALCULATOR       CUCCCHPS       MS309       94       MC1401.7       54.95         CAUSITI       2.10       CAUSITI       2.00       CAUSITI       2.00       MUSTIN       2.00 <td>1152/5         15         500m         28         111113         50         703         54,00           11455         25         70m         67,00         11118         150         713         54,00         1,70           11465         150         70m         67,00         11118         150         713         54,00         1,70           11465         150         70m         67,00         11118         400         713         34,00         713         34,00         713         34,00         713         34,00         713         34,00         713         34,00         713         34,00         713         34,00         713         71,00         71118         71,00         71118         71,00         71118         71,00         71118         71,00         71118         71,00         71118         71,00         71118         71,00         711,00</td>	1152/5         15         500m         28         111113         50         703         54,00           11455         25         70m         67,00         11118         150         713         54,00         1,70           11465         150         70m         67,00         11118         150         713         54,00         1,70           11465         150         70m         67,00         11118         400         713         34,00         713         34,00         713         34,00         713         34,00         713         34,00         713         34,00         713         34,00         713         34,00         713         71,00         71118         71,00         71118         71,00         71118         71,00         71118         71,00         71118         71,00         71118         71,00         71118         71,00         711,00



CIRCLE 16 ON FREE INFORMATION CARD

SEPTEMBER 1979



-20-

POCKET CRICKET

SENCORE

Reg S125 00 \$99.95

Auto Stereo 40 Watt

Auto Storer Power Booster Power Stores \$24.95

\$40.00

0

1

TF 40

Magnifier

LAMP

Model MG 10A

\$49.50

**VOM Multimeters** 

20K ohm/v \$19.95

1K ohm/v \$9.95

CIRCLE 3 ON FREE INFORMATION CARD

A. 19 0

ł

1

30MHz

Portable

\$59.95

Frequency

1827

\$654.50

-

> 700 Series

AM/FM 8 Track

\$52.50

Cassette

\$57.50 Stereo

**Advertised Price**"

AM/FM

Stereo 🚅

Counter "We Will Beat Any

Sub-

stitution

Box Model 2910

Model WTCP N

FREE

1979

Catalog

V/SA

Soldering

Station

Call TOLL FREE

MasterCharge 

Bank-Americang

COD

Check

Money

Order

(800) 645-9518

# Radio Shack - Your No. 1 Parts Place

Why Wait for Mail Order Delivery? You'll Find Friendly Salespeople, Low Prices and New Items Every Day at Our Store or Dealer Near You!

#### Low-Power Schottky ICs




Improved 5-volt logic devices use Schottky diode technology for minimum propagation delay and high speed at minimum power.

Туре	Cat. No.	ONLY		
74LS00	276-1900	.49		
74LS02	276-1902	.59		
74LS04	276-1904	.59		
74LS08	276-1908	.49		
74LS10	276-1910	.59		
74LS13	276-1911	.99		
74LS20	276-1912	.59		
74LS27	276-1913	.69		
74LS30	276-1914	.59		
74LS32	276-1915	.69		
74LS47	276-1916	1.29		
74LS51	276-1917	.59		
74LS73	276-1918	.69		
74LS74	276-1919	.69		
74LS75	276-1920	.99		
74LS76	276-1921	.79		
74LS85	276-1922	1.29		
74LS90	276-1923	.99		
74LS92	276-1924	.99		
74LS93	276-1925	.99		
74LS123	276-1926	1.19		
74LS132	276-1927	.99		
74LS151	276-1929	.99		
74LS157	276-1930	1.19		
74LS161	276-1931	1.49		
74LS164	276-1932	1.49		
74LS175	276-1934	1.19		
74LS192	276-1935	1.49		
74LS193	276-1936	1.49		
74LS194	276-1937	1.49		
74LS196	276-1938	1.59		
74LS367	276-1835	1.19		
74LS368	276-1836 276-1943	2.39		
74LS373 74LS374	276-1943	2.39		
14L53/4	270-1944	2.39		
4000-Series CMOS ICs				

4000 001103 011100 105					
Туре	Cat. No.	EACH			
4001	276-2401	.69			
4011	276-2411	.69			
4012	276-2412	.79			
4013	276-2413	.99			
4017	276-2417	1.69			
4020	276-2420	1.69			
4021	276-2421	1.69			
4023	276-2423	.69			
4027	276-2427	.99			
4028	276-2428	1.29			
4046	276-2446	1.69			
4511	276-2447	1.69			
4049	276-2449	.79			
4050	276-2450	.79			
4051	276-2451	1.49			
4066	276-2466	1.39			
4070	276-2470	.79			
4518	276-2490	1.49			
4543	276-2491	1.99			

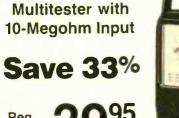All from Major Semiconductor Mfrs., and Prime. Specs and Pin Out Diagram Included with Each Device.





28-Range

Dual FET Input

• 5" Mirrored Scale Overload Protected

U.L. listed. 22-125

- Polarity Reverse Switch

High-accuracy 25 μA meter with single-knob range selector measures DC Volts: 0-3-1-3-10-30-100-300-1000 at 10 Megohms. AC Volts: 0-3-30-100-300-1000 at 10 kΩ per volt. DC Current: 0-100 μA, 3-30-300 mA, 10A. Resis-+62 in 5 ranges. Accuracy:  $\pm 3\%$  DC,  $\pm 4\%$  AC.  $7x5^{1/2}x3^{1/6}$  overall. With leads, test probes, batteries. 22-208



6-Digit Frequency

Counter

Save

50%

Reg.

99.95

**Q**95

30 mV up to 30 MHz, Accuracy is 3 ppm at 25° or less than 30 Hz at 10 MHz, With antenna, leads, case, instructions. 22-351 Sale 49.95

Pocket Multitester

- 8 Ranges - Fits in Shirt Pocket

**Save 20%** 

Reg. 9.95 88


Sale 49.95





(None Sent by Mail) Prices may vary at individual stores and dealers

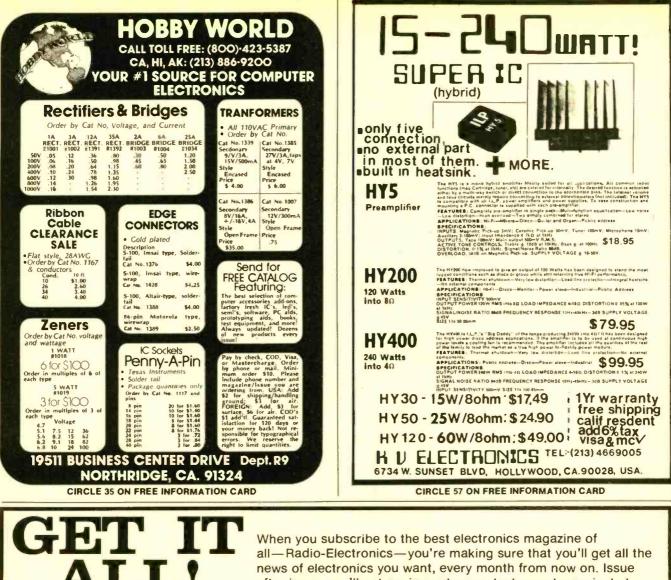Come in for Your FREE Copy of Our New 176-Page 1980 Catalog!



all—Radio-Electronics—you're making sure that you'll get all the news of electronics you want, every month from now on. Issue after issue, you'll get equipment news, test reports, projects to build, computer technology, servicing tips and more, including regular columns on computers, solid state, hi-fi, hobbies and servicing. And every one is written by the experts, the outstanding authorities in the most exciting, fastest-growing field in the world today—electronics.

And . . . you save money, too, as much as \$11 off the newsstand price of Radio-Electronics when you select one of the subscription offers listed on the handy coupon. More important—you'll be assured of having your copy reserved, even if it runs out on the newsstands. You save money and time. Make sure you get all the excitement in every issue of Radio-Electronics, every month, by filling in and mailing the coupon, today.

ED	GET THE BEST!Rad 1 Year-12 issues ONLY \$9.98 (You save \$5.02 off newsstand price.) 2 Years24 issues ONLY \$19.00 (Save Morel \$11.00 off newsstand price.)	o-Electroni	CS (please print)	4099
	Payment enclosed     Bill me	Address		
S	Extra Shipping: Canada \$3.00 per year.	City		
	all other countries \$5.00 per year.	State	Zip Code	
		dio Electronic	s BOX 2520, BOULDER, COLO	80222

RADIO-ELECTRONICS

**Radio-Electronics** 

TV ADD-ON GADGETS

- New FM Ja - 2 R.E.A.L Lab T

UBSCRIB

ODAY, AN

A SINGLE

ISSUE.


DON'T MIS


WIRING SYSTEMS

ADAPTIVE NOISE FILTER

SATELLITE TV RECEPTION

AC POLARITY CHECKES

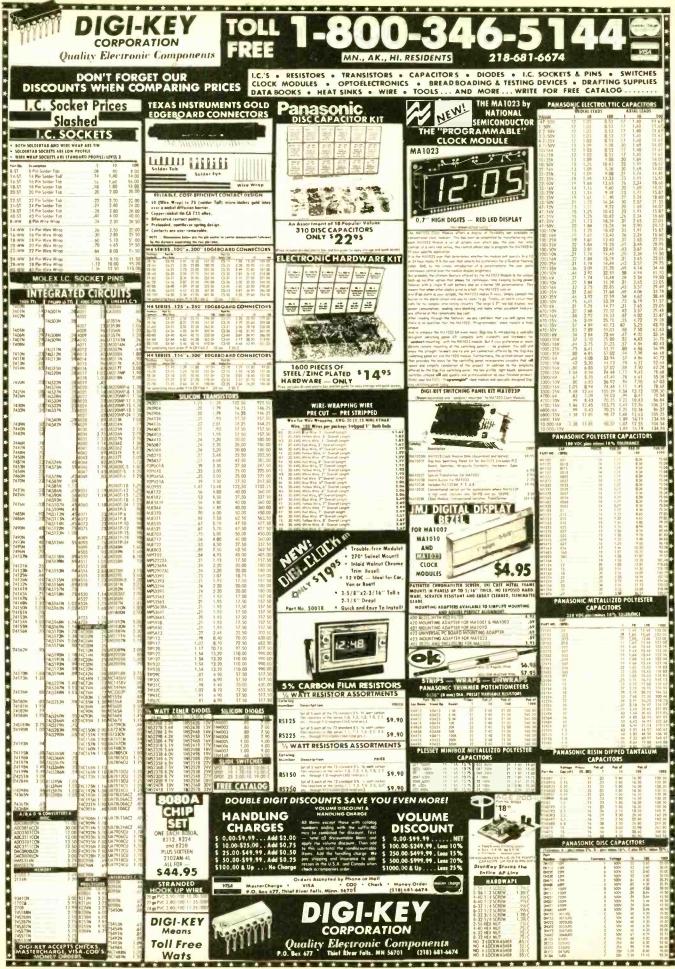

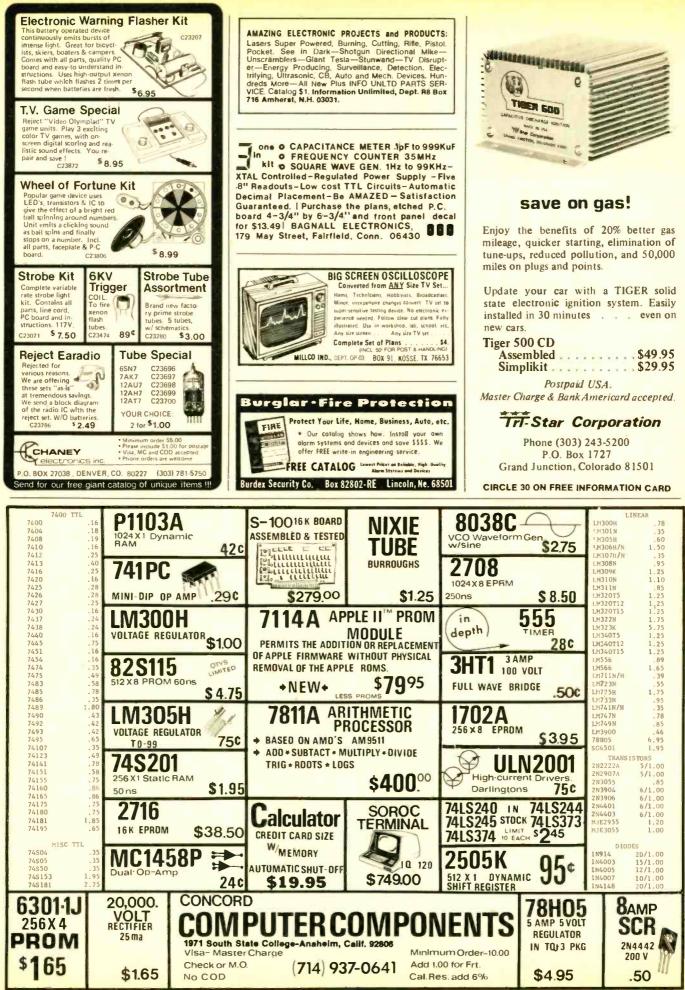

**CIRCLE 46 ON FREE INFORMATION CARD** 

RADIO-ELECTRONICS



#### ATTENTION ELF OWNERS ANNOUNCING QUEST SUPER BASIC

At last a Full Size Basic for 1802 systems. A Tiny Basic Source now available At last a full Size Basic for 1802 systems. A complete function Basic for 1802 systems. A solution of the second minimum for Basic and user programs. Cassette version in stock now for immediate delivery. ROM versions coming soon with exchange privilege allowing credit for cassette version. Super Basic on Cassette \$40.00

\$19.00 S-100 Slot Expansion, Add 3 more S-100 slots to your Super Expansion Board or use as a 4 slot S-100 Mother Board. Board without connectors \$9.95 Coming Soon: High resolution alpha/numerics

with color graphics expandable up to 256 x 192 resolution for less than \$100. Economical ver-sions for other popular 1802 systems also.

16K Dynamic RAM board expandable to 32K for less than \$150.

#### RCA Cosmac Super Elf Computer \$106.95

Compare features before you decide to buy any other computer. There is no other computer on the market today that has all the desirable benefits of the Super Elf for so little money. The Super Eff is a small single board computer that does many big things. It is an excellent computer for training and for learning programming with its machine language and yet it is easily **expanded** with additional memory, Full Basic, ASCII Keyboards, video character generation, etc.

Before you buy another small computer, see if it includes the following features: ROM monitor; State and Mode displays; Single step; Optional address displays; Power Supply; Audio Amplifier and Speaker; Fully socketed for all IC's; Real cost of in warranty repairs; Full documentation.

The Super Elf includes a ROM monitor for pro gram loading, editing and execution with SINGLE STEP for program debugging which is not in-cluded in others at the same price. With SINGLE STEP you can see the microprocessor chip opera-ting with the unique Quest address and data bus displays before, during and after executing in-structions. Also, CPU mode and instruction cycle are decoded and displayed on 8 LED indicators

An RCA 1861 video graphics chip allows you to connect to your own TV with an inexpensive video modulator to do graphics and games. There is a speaker system included for writing your own music or using many music programs already written. The speaker amplifier may also be used to drive relays for control purposes

A 24 key HEX keyboard includes 16 HEX keys plus load, reset, run, walt, input, memory protect, monitor select and single step. Large, on board displays provide output and optional high and low address. There is a 44 pin standard connector slot for PC cards and a 50 pin connector slot for the Quest Super Expansion Board. Power supply and sockets for all IC's are included in the price plus a detailed 127 pg. instruc-tion manual which now includes over 40 pgs. of software info. Including a series of lessons to help get you started and a music program and graphics target game.

Many schools and universitiles are using the Super Eff as a course of study. OEM's use it for training and research and development.

Remember, other computers only offer Super Elf leatures at additional costs or not at all. Compare before you buy. Super Elf Kit \$106.95, High address option \$8.95, Low address option \$9.95, Custom Cabinet with drilled and labelled plexiglass front panel \$24.95, Expansion Cabinet with room for 4 S-100 boards \$41.00. NiCad Battery Memory Saver Kit \$6.95. All kits and options also come completely assembled and tested

Questdata, a 12 page monthly software publication for 1802 computer users is available by sub-scription for \$12.00 per year.

Tiny Basic Cassette \$10.00, on ROM \$38.00. original Elf kit board \$14.95

#### Super Expansion Board with Cassette Interface \$89,95

This is truly an astounding value! This board has been designed to allow you to decide how you want it optioned. The Super Expansion Board comes with 4K of low power RAM fully address-able anywhere in 64K with built-in memory protect and a cassette interface. Provisions have been made for all other options on the same board and it fits neatly into the hardwood cabinet alongside the Suger Elf. The board includes slots up to 6K of EPROM (2708, 2758, 2716 or TI 2716) and is fully socketed. EPROM can be used for the monitor and Tiny Basic or other purposes.

A IK Super ROM Monitor \$19.95 is available as an on board option in 2708 EPROM which has been preprogrammed with a program loader/ editor and error checking multi file cassette read/write software, (relocatible cassette file) another exclusive from Quest. It includes register save and readout. block move capability and video graphics driver with blinking cursor. Break points can be used with the register save feature to isolate program bugs guickly, then follow with single step. The Super Monitor is written with subroutines allowing users to take advantage of

monitor functions simply by calling them up. Improvements and revisions are easily done with the monitor. If you have the Super Expansion Board and Super Monitor the monitor is up and running at the push of a button.

Other on board options include Parallel Input and Output Ports with full handshake. They allow easy connection of an ASCII keyboard to the input port. RS 232 and 20 ma Current Loop for teletype or other device are on board and if you need more memory there are two S-100 slots for static RAM or video boards. A Godbout 8K RAM board is available for \$135.00. Also a 1K Super Monitor version 2 with video driver for full capa-bility display with Tiny Basic and a video interface board. Parallel I/O Ports \$9.85, RS 232 \$4.50, TTY 20 ma I/F \$1.95, S-100 \$4.50. A 50 pin connector set with ribbon cable is available at \$12.50 for easy connection between the Super Elf and the Super Expansion Board.

The Power Supply Kit for the Super Expansion Board is a 5 amp supply with multiple positive and negative voltages \$29.95. Add \$4.00 for shipping. Prepunched frame \$7.50. Case \$10.00. Add \$1.50 for shipping

Multi-volt Computer Power Supply 8v 5 amp, ±18v .5 amp, 5v 1.5 amp, -5v .5 amp, 12v .5 amp, -12 option. ±5v, ±12v are regulated. Klt \$29.95. Klt with punched frame \$37.45. Woodgrain case \$10.00

60 Hz Crystal Time Base Kit \$4,40 Converts digital clocks from AC line frequency to crystal time base. Outstanding accuracy. Kit Includes: PC board, IC, crystal, resistors, capacitors and trimmer

TERMS: \$5.00 min. order U.S. Funds. Calif residents add 6% lax. BankAmericard and Master Charge accepted. Shipping charges will be added on charge cards.

Same day shipment. First line parts only Factory tested. Guaranteed money back Quality IC's and other components at factory prices

INTEGRATED CIRCUITS

7400171E LM31777K 2 92 CD4015 86		ELECTRONICS		
7400N .17 LM318 1.35 CD4016 36	2102-11 2102-14 2102-14 2102-14 2102-14 2102-14 2102-14 2102-14 2102-14 2102-14 2102-14 2102-14 2102-14 2114-2 2114-2 2114-2 2114-3 2	And Based Bas		
Auto Clock Xit     \$17.95       6502 based single board with full ASCII keyboard and 20 column thermal printer. 20 char. ai- phanumeric display. ROM monitor, fully expand- able. \$375.00. 4K version \$450.00. 4K Assem- bler \$85.00. 8K Basic Interpreter \$100.00.     Auto Clock Xit     \$17.95       DC clock with 4-50° displays. Uses National MA-1012 module with alarm option. Includes light dimmer, crystal timebase PC boards. Fully regulated, comp. instructs. Add \$3.95 for beau- tiful dark gray case. Best value anywhere.       Not a Cheap Clock Kit \$14.95 Includes everything except case. 2-PC boards.     Stopwatch Kit 3.2768 MHz crystal accuracy. Times to 59 min., 59 sec., 99 1/100 sec. Times std., split				
650" LED Displays. 5314 clock chip, former, all components and full in struu Orange displays also avail. Same kit displays. Red only. \$21.95 Case \$11.	ctions. w/.80°	and Taylor. 7205 chip, all components minus case. Full instructions. NiCad Battery Fixer/Charger Kit		
and the second se	8.95	Opens shorted cells that won't hold a charge and then charges them up, all in one kit w/tull parts and instructions. \$7.25		
without affecting normal usage. Comp with full instructions.		PROM Eraser Will erase 25 PROMs in 15 minutes. Ultra-		
	<b>35.00</b>	violet, assembled \$34.50 Hickok 31/2 Digit LCD Multimeter		
24K Static RAM Kit 32K Dynamic RAM Kit 64K Oynamic RAM Kit 8K/16K Eprom Kit (less PROMS)	23.00 310.00 70.00 89.00 39.00	Batt/AC oper. 0.1mv-1000v. 5 ranges. 0.5% accur. Resistance 6 low power ranges 0.1 ohm-20M ohm. DC curr01 to 100ma. Hand held, $\frac{1}{2}$ LCO displays, auto zero, polarity, overrange. <b>\$69.95</b> .		
<b>79 IC Update Master Manual S</b> Complete IC data selector, 2500 pg. mas ence guide. Over 50,000 cross referenc update service through 1979. Domestic 33.50, 1978 IC Master closeout \$19.50, No orders.	Digital Temp. Meter Kit \$39,95 Indoor and outdoor. Switches back and forth. Beautiful. 50° LED readouts. Nothing like it available. Needs no additional parts for com- plete, full operation. Will measure – 100° to – 200°F, tenths of a degree, air or liquid. Beautiful woodgrain case w/bezel \$11.75			
FREE: Send for your copy of our NEW 1979 QUEST CATALOG. Include 28c stamp.				

P.O. Box 4430E Santa Clara, CA 95054 For will call only: (408) 988-1640

2322 Walsh Ave



#### **RADIO-ELECTRONICS** does not assume any responsibility for errors that may Free Information Number Page AMC Sales Active Electronics. 97 Bullet Electronics 102 Chaney Electronics 112 C I E-Cleveland Institute of Data Precision 24 EMC-Electronic Measurements Corp..... 34 11,12 Fuji-Svea 103 Godbout Electronics 100 Gould, Inc .- Instruments Div. 16 International Correspondence Schools.. 72-75 Meshna 102 \_ National Radio Institute (NRI) Div. of

52	Netronics			
_	New England Business Service, Inc 25			
2	O.K. Machine & ToolCov. 3			
19	Ohio Scientific 1			
20	Optoelectronics			
23	PAIA			
21	PTS Electronics			
47	Panavise			
22	Poly Paks			
62,63	Professional Aids			
25	Quest			
24	Quimtronix			
26	Radio Shack			
59	Ramsey Electronics			
27	Rye Industries			
_	Sabtronics			
33	Soar 22			
28	Solid State Sales 100			
56	Southwest Technical Products 88			
_	Speakerlab, Inc			
38	Sprague Products, Inc			
	Surplus Center			
	Technology Trends			
50	Tek-El Corp. 104			
30	Tri-Star			
41	Trionvx Industries 87			
37	Vaco			
58	Vector 90			
	V.I.Z. Mfg			
31	Wersi Electronics 78			
32	Zemco 78			
36	221110			
[				
	FITABLE UNE-IVIAIN			
ELECTRONIC FACTORY				
Investment unnecessary, knowledge not re-				
quired, sales handled by professionals. Ideal home business. Write today for facts!				
Postcard will do. Barta-RE-U, Box 248,				
	Walnut Creek, CA 94597.			

MOVING?	
Don't miss a single copy of Radio-Elec- tronics. Give us: Six weeks' no- tice	ATTACH LABEL HERE
Your old ad- dress and zip code	
Your new ad- dress and zip code	
name (pleas	e print)
address	
SUBSCRIPTION DE	zip code lio-Electronics EPT., P.O. BOX 2520, COLO. 80322

## ADVERTISING INDEX

appear in the index below.

WHY CUT? WHY STRIP? WHY SLIT? WHY NOT...

AWG 30 Wire

• .025" Square Posts

• Daisy Chain or Point To Point

• Built In Cut Off

• No Stripping or Slitting Required

Easy Loading of Wire
 Available Wire Colors:

Blue, White, Red & Yellow

		Î	Í	

# JUST WRAP Wire-Wrapping

JUST WRAP TOOL WITH ONE 50 FT. ROLL OF WIRE					
COLOR	PART NO.	U.S. LIST PRICE			
BLUE	IW-1-B	\$14.95			
WHITE	ĴŴ·1∙W	14.95			
YELLOW	JW-1-Y	14.95			
RED	JW-1-R	14.95			
REPLACEMENT ROLL OF WIRE 50 FT.					
BLUE	R·JW·B	\$ 2.98			
WHITE	R·JW·W	2.98			
YELLOW	RJWY	2.98			
RED	R JW R	2.98			
JUST WRAP-UNWRAPPING TOOL					
	JUW-1	\$ 3.49			



WIRE

TOOL

U.S.A., FOREIGN PATENTS PENDING

WRAPPING

OK MACHINE & TOOL CORPORATION 3455 CONNER ST., BRONX, N.Y. 10475 (212) 994-6600/TELEX 125091

\* MINIMUM BILLING \$ 25.00/ADD SHIPPING CHARGE \$ 2.00/NEW YORK CITY/STATE RESIDENTS ADD APPLICABLE TAX.

The **Speech Processor.** So unique it's patented. So good its guaranteed to out-perform any microphone on any radio.

#### CLIPS ANYWHERE WITHOUT A CLIP!

Molded four-pole internal magnet clamps instantly to any steel surface. Steering column, metal dash, roof top, or the side of your CB radio. No groping for your mounting clip

#### PROCESSES **SPEECH WITH A COMPUTER CIRCUIT!**

It's its own computer-it automatically monitors your speech and adjusts it in micro-second increments pumping so much db gain into your speech that you get 400% more power than a standard mike.

## **Double Guarantee**

GUARANTEE I: The K40 Speech Processor is guaranteed to outperform any microphone it replaces or return it for a complete and full retund within 7 days from the K40 Dealer that installed and tuned it.

#### **GUARANTEE II:**

Unconditionally guaranteed for 12 months. Guaranteed against cracking, chipping, or rusting. Guaranteed against mechanical failure. Guaranteed against electrical failure. No exclusions. No gimmicks. For a full 12 months

#### **SOUND SENSITIVE 2 INCHES OR 2** FEET!

A microphone so sensitive it will select your voice and process your speech no matter how close or far you are from the microphone.

#### **TWO MICS** WITH ONE SWITCH!

Switch up for a highpitched transmission for cutting congested city traffic. Switch down for a mellow base in open, uncluttered rural areas.



**Pull the Processor directly** to your mouth and speak directly into the mic. The Processor adjusts to your voice-and blanks out all the cab noise while you're speaking. Automatically.

#### **FRESH CHARGE** WITH NO **BATTERIES!**

Patented electronic storage system recharges while you listen to the radio. It provides a fresh electrical charge every time you squeeze the trigger. You never replace batteries.



American Antenna Elgin, Il 60120 suggested retail.

**CIRCLE 5 ON FREE INFORMATION CARD**