

Radio- Electronics

**INFORMATION EXPLOSION
ON YOUR TV—VIDEOTEX!**

\$1.25 FEB. 1982

**How speech synthesis works
New car telephone technology
Build a digital thermometer**

**Build a hi-fi sub-woofer
Using IC voltage references
Dolby HX for hi-fi**

**BUILD THIS PROM PROGRAMMER
AND ZAP YOUR OWN PROM'S**



390736 DHM 09976093 6V A NOV82
MR ROBERT DAHM
997 GRAND AV
AURORA
IL 60505



Weller®



The line of professional soldering stations that gives accurate temperature control all the time!

The EC 1000, 2000, 3000, 4000 soldering stations respond automatically to soldering load variations and maintain the temperature you select to within $\pm 10^\circ\text{F}$.

LED read-out on the EC 2000 and 4000 displays actual tip temperature with a $\pm 1^\circ\text{F}$ resolution. Unbelievable? See your distributor. Get an on-the-job demonstration. Now!

from Cooper The Toolmaker.™



The Cooper Group

BOKER® CRESCENT® LUFKIN® NICHOLSON®
PLUMB® WELLER® WISS® XCELITE®

The Cooper Group
P.O. Box 728
Apex, NC 27502, U.S.A.
Tel: (919) 362-7510 Telex: 579497

CIRCLE 2 ON FREE INFORMATION CARD

We gave solderless breadboarding a new name.

Proto-Board® breadboards, by Global Specialties. The leading name in solderless breadboarding.

You find them wherever electronics is important. From labs to production lines to classrooms to home workshop benches. Their name, synonymous with solderless breadboarding. And for good reason.



Proto-Board breadboards introduced engineers, technicians and hobbyists to a new way

of designing and building electronic circuits, as fast as they can think. Testing, modifying and expanding as quickly as new thoughts occur. Saving precious time and money by freeing creativity from manual labor.

Global Proto-Board products are arrays of solderless sockets and bus strips that emulate PC board layouts

while permitting instant insertion and removal of components from the largest DIP to the smallest discretes. With a rugged construction built to provide positive connections and withstand day-in, day-out professional use—even as test fixtures. And mounted on sturdy metal backplanes, for extended high-frequency use and extra durability.

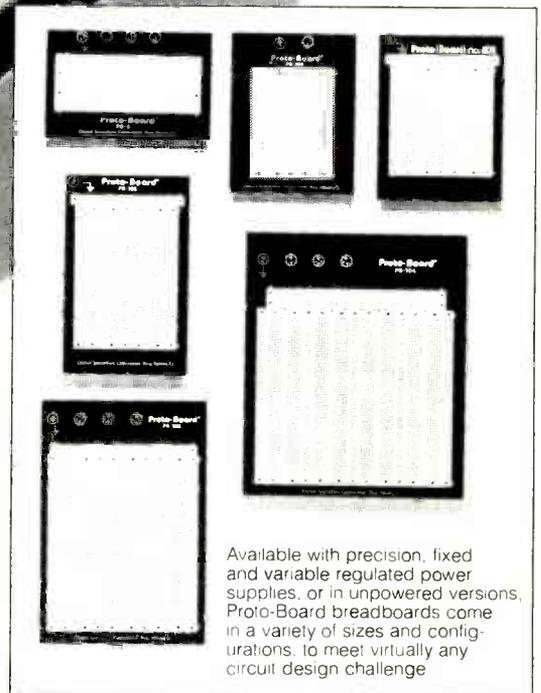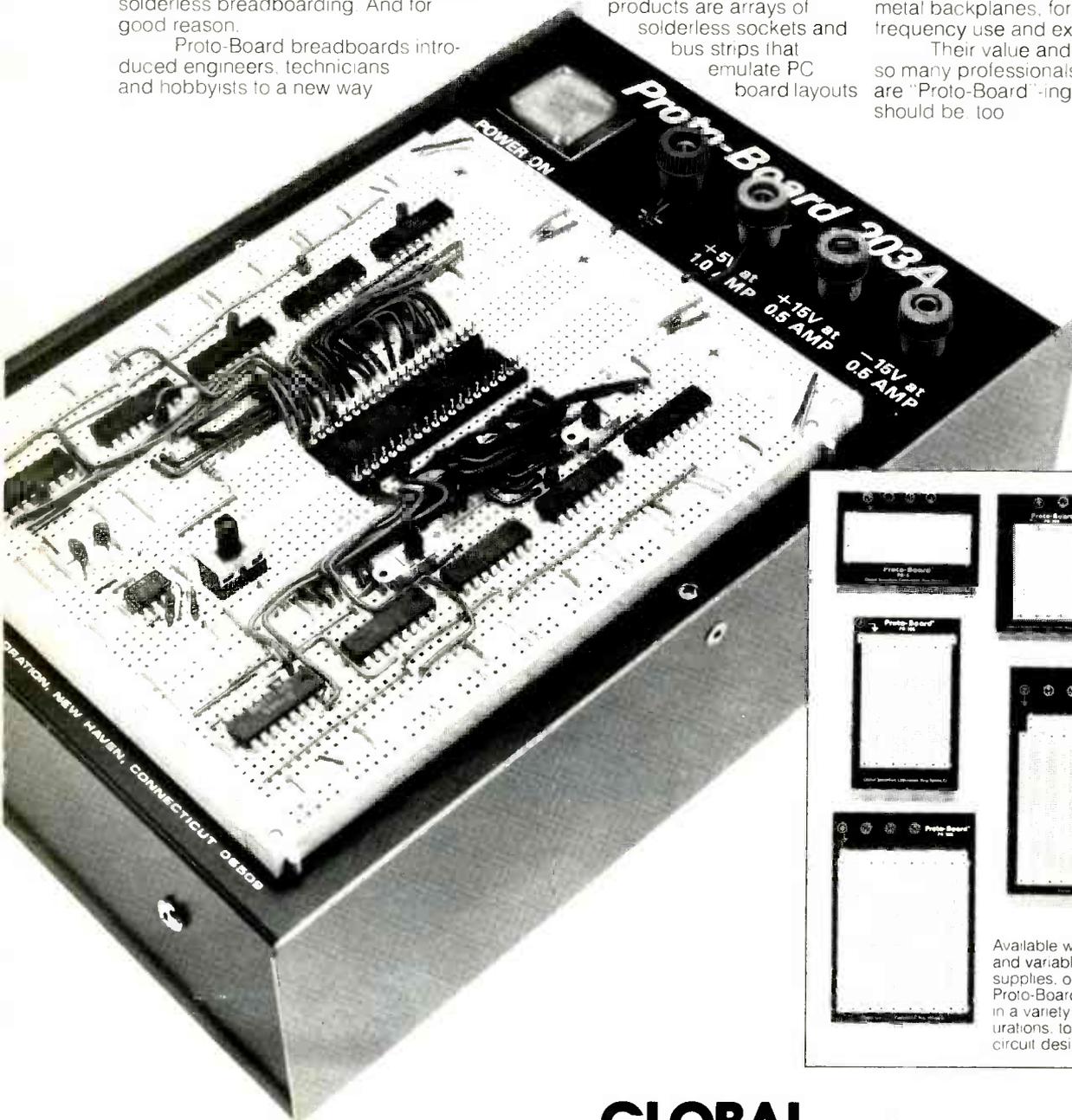Their value and versatility are why so many professionals and hobbyists are "Proto-Board"ing. And why you should be, too.



Available with precision, fixed and variable regulated power supplies, or in unpowered versions, Proto-Board breadboards come in a variety of sizes and configurations, to meet virtually any circuit design challenge.

70 Fulton Terr. New Haven, CT 06509 (203) 624-3103, TWX 710-465-1227
 OTHER OFFICES: San Francisco (415) 648-0611, TWX 910-372-7992
 Europe: Phone Salford-Walden 0799-21682, TLX 817477
 Canada: Len Finkler Ltd., Downsview, Ontario

GLOBAL SPECIALTIES CORPORATION

© Copyright 1981 Global Specialties Corporation.

Call toll-free for details
1-800-243-6077
 During business hours

CIRCLE 8 ON FREE INFORMATION CARD

Listen to your planet on a short-wave receiver!

Communications Electronics, the world's largest distributor of radio scanners, is pleased to introduce Panasonic Command Series shortwave receivers. Panasonic lets you listen to what the world has to say. Unlike a scanner, a Command Series radio lets you listen to shortwave broadcasts from countries around the world, as well as the U.S.A. It's the space age shortwave performance you've been waiting for...at a down to earth price you can afford.

All Panasonic shortwave receivers sold by Communications Electronics bring the real live excitement of international radio to your home or office. With your Command Series receiver, you can monitor exciting radio transmissions such as the BBC, Radio Moscow, Ham Radio and our own Armed Forces Radio Network. Thousands of broadcasts in hundreds of different languages are beamed into North America every day. You can actually hear the news *before* it's news. If you do not own a shortwave receiver for yourself, now's the time to buy your new receiver from CE. Choose the receiver that's right for you, then call our toll-free number to place your order with your credit card.

We give you excellent service because CE distributes more scanners and shortwave receivers worldwide than anyone else. Our warehouse facilities are equipped to process thousands of orders every week. We also export receivers to over 300 countries and military installations. Almost all items are in stock for quick shipment, so if you're a person who needs to know what's *really* happening around you, order today from CE.

Panasonic® RF-6300

Allow 30-120 days for delivery after receipt of order due to the high demand for this product.
List price \$749.95/CE price \$499.00
Bands: LW 150-410 KHz. MW 520-1610 KHz. SW1-5 1.6-30 MHz. FM 87.5-108 MHz.

The new Panasonic RF-6300 Command Series PLL synthesized 8-band portable communications receiver, lets you hear the world. The RF-6300 has features such as microcomputer pre-set tuning and PLL quartz synthesized digital tuner. Microcomputer stores up to 12 different frequencies for push-button recall. FM/MW/LW/SW1-5 reception. Manual tuning knob. Wide/Narrow bandwidth selector. Double superheterodyne system. Fast/Slow manual tuning. Built-in quartz digital alarm clock. 5 inch dynamic PM speaker. 3 antennas. Multi-voltage. Detachable AC cord. Operates on 6 "D" batteries (not included). Made in Japan.



Panasonic RF-6300



RF-4900

Panasonic® RF-4900

List price \$549.95/CE price \$389.00
Bands: MW 525-1610 KHz. SW1-8 1.6-30 MHz. FM 88-108 MHz.
The Panasonic RF-4900 shortwave receiver features a 5-digit fluorescent display for all 8 SW bands, as well as for AM/FM. AC or battery operation. Full coverage from 1.6 to 30 MHz on SW. Covers SSB and CW. Premix Double Superheterodyne. Fast/slow 2 speed tuning. AFC Switch on FM, narrow/wide selectivity switch for AM and SW. Antenna trimmer. Calibration control. FET RF circuit. Mode switch for AM-CW/SSB. BFO Pitch control. ANL switch for AM. RF gain control. Tuning-Battery meter with meter function switch. Separate bass and treble tone control. Dial light switch. Digital display on/off switch. Separate power switch. Rack type handle. Made in Japan.

Panasonic® RF-3100

Allow 30-120 days for delivery after receipt of order due to the high demand for this product.
List price \$369.95/CE price \$269.00
Bands: MW 525-1610 KHz. SW1-29 1.6-30 MHz. FM 88-108 MHz.
The Panasonic RF-3100 portable 31-Band portable radio has PLL Quartz-Synthesizer tuning that "locks" onto SW stations. Operates on AC or battery. SW frequencies from 1.6 to 30 MHz. are in 29 bands. All-band 5-digit frequency readout. Horizontal design with front mounted controls for shoulder strap operation. Double superheterodyne for clean SW reception. BFO pitch and RF gain controls. Separate bass and treble controls. Wide/Narrow bandwidth selector. Meter for tuning and battery strength. LED operation indicator. Meter light switch. 3 1/2" PM dynamic speaker. Comes with detachable shoulder belt. Battery power (8 "D" batteries not included). Made in Japan.


Panasonic® RF-2900

List price \$349.95/CE price \$249.00
Bands: MW 525-1610 KHz. SW1-3 3.2-30 MHz. FM 88-108 MHz.
The Panasonic RF-2900 is a portable five-band shortwave radio with digital five digit fluorescent frequency display. Full coverage from 3.2 to 30 MHz. on SW. Covers SSB and CW. Double superheterodyne receiver. Fast/slow 2 speed tuning. AFC switch on FM, narrow/wide selectivity switch for AM and SW. FET RF circuit. BFO switch and pitch control. RF gain control. Tuning battery meter. Separate bass/treble tone control. SW calibration control. Dial light switch. Digital display on/off switch. Separate power switch. Detachable dial hood included. Rack type handle. Includes whip antenna and ferrite core antenna, speaker, earphone, recording output jacks, AC line and detachable adjustable shoulder belt. Made in Japan.



Command Series RF-2900

Panasonic Command Series

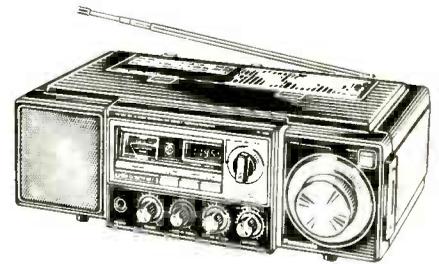

Panasonic RF-3100

TEST ANY RECEIVER

Test any receiver purchased from Communications Electronics for 31 days before you decide to keep it. If for any reason you are not completely satisfied, return it in original condition with all parts in 31 days, for a prompt refund (less shipping and handling charges).

NATIONAL WARRANTY SERVICE

All Panasonic receivers listed in this ad are backed by a two-year limited warranty on parts and labor. In addition, this warranty is backed by a broad network of Panasonic service centers. For two years after original purchase, Panasonic will repair or replace your receiver if purchased and retained in the U.S.A. Customer must take it to an authorized service center. Warranty does not cover damage from abuse, misuse, or commercial use. Proof of purchase is needed for in-warranty service.

BUY WITH CONFIDENCE

To get the fastest delivery from CE of any receiver send or phone your order directly to our Consumer Products Division. Be sure to calculate your price using the CE prices in this ad. Michigan residents please add 4% sales tax. Written purchase orders are accepted from approved government agencies and most well rated firms at a 10% surcharge for net 10 billing. All sales are subject to availability, acceptance and verification. Prices, terms and specifications are subject to change without notice. Out of stock items will be placed on backorder automatically unless CE is instructed differently. International orders are invited with a \$20.00 surcharge for special handling in addition to shipping charges. All shipments are F.O.B. Ann Arbor, Michigan. No COD's please. Non-certified and foreign checks require bank clearance.

Mail orders to: Communications Electronics, Box 1002, Ann Arbor, Michigan 48106 U.S.A. Add \$12.00 per receiver for U.P.S. ground shipping and handling. If you have a Master Card or Visa, you may call anytime and place a credit card order. Order toll free in the U.S.A. Dial 800-521-4414. Outside the U.S. or in Michigan, dial 313-994-4444. Dealer inquiries invited. Order your Panasonic Command Series receiver today at no obligation.

CE logos are trademarks of Communications Electronics. † Panasonic is a registered trademark of Panasonic Company, a Division of Matsushita Electric Corporation of America.

Copyright © 1981 Communications Electronics™



COMMUNICATIONS ELECTRONICS™

Consumer Products Division

854 Phoenix □ Box 1002 □ Ann Arbor, Michigan 48106 U.S.A.
Call TOLL-FREE (800) 521-4414 or outside U.S.A. (313) 994-4444

We're first with the best.™

CIRCLE 5 ON FREE INFORMATION CARD

SPECIAL FEATURE

- 41 **CELLULAR CAR TELEPHONES**
Cellular technology promises to make mobile telephones more accessible to more users. Here is an inside look at this proposal that is before the FCC. **Danny Goodman**
- 59 **VIDEOTEK FOR TV**
Part 3—The alphanumeric and graphic capabilities of the competing systems that promise to turn your TV set into an information center. **Richard Larratt**
- 62 **SPEECH SYNTHESIS**
A look at the various techniques and methods used to make circuits talk. **Karl Savon**

BUILD THIS

- 45 **PROM PROGRAMMER**
Self-contained 2716 programmer stores your programs in reusable EPROM's quickly and efficiently. **Robert N. Beaber**
- 57 **DIGITAL THERMOMETER**
Easy-to-build thermometer for your home has a unique clear plastic enclosure. **Michael Rigsby**
- 66 **SAFE SUBWOOFER**
Based on the patented SAFE principle, this add-on speaker system provides extended bass response. **George Pappanikolaou**

TECHNOLOGY

- 4 **VIDEO ELECTRONICS**
Tomorrow's news and technology in this quickly changing industry. **David Lachenbruch**
- 24 **SATELLITE/TELETEXT NEWS**
The latest happenings in communications technology. **Gary H. Arlen**
- 84 **STATE-OF-SOLID-STATE**
What's new in solid-state technology. **Robert F. Scott**

**CIRCUITS
AND COMPONENTS**

- 50 **REMOTE VOLUME ATTENUATOR**
A single IC lets you remotely control the volume of a radio, hi-fi or TV. **Martin Bradley Weinstein**
- 53 **PRECISION VOLTAGE REFERENCES**
How these solid-state components work and how to use them. **Joseph Carr**
- 80 **HOBBY CORNER**
A one-IC programmable sound generator. **Earl "Doc" Savage, K4SDS**
- 94 **NEW IDEAS**
Automobile ignition substitute.

VIDEO

- 74 **STEREO AUDIO FOR TV**
Dual audio channels for broadcast TV is right around the corner. Here is a look at the competing systems and how they work. **Len Feldman**
- 96 **SERVICE CLINIC**
Solid-state vertical sweep circuits. **Jack Darr**
- 97 **SERVICE QUESTIONS**
R-E's Service Editor solves technicians' problems. **Jack Darr**

AUDIO

- 77 **INSIDE DOLBY HX**
New version of the Dolby HX headroom-expansion system for cassette decks. **Len Feldman**

COMPUTERS

- 88 **COMPUTER CORNER**
Dial-up software networks. **Les Spindle**

RADIO

- 82 **COMMUNICATIONS CORNER**
A window-mounted CB antenna that really works. **Herb Friedman**

**EQUIPMENT
REPORTS**

- 29 **MXR Model 156 CX Decoder**
- 30 **Sabtronic 8610A Frequency Counter**
- 34 **Grove Enterprises DSC-2 Code Breaker**

DEPARTMENTS

- | | |
|----------------------------------|---------------------------|
| 22 Advertising and Sales Offices | 139 Free Information Card |
| 138 Advertising Index | 13 Letters |
| 104 Books | 108 Market Center |
| 110 Computer Market Center | 99 New Products |
| 16 Editorial | 6 What's News |

ON THE COVER

A completely self-contained PROM programmer for storing your programs in reusable 2716 EPROM's. This project is a must for experimenting with microprocessors and designing microprocessor based projects. Construction details start on page 45.

**ANNUAL INDEX
JANUARY—DECEMBER**

1981

To present the maximum number of articles to our readers, we have not published the Annual Index as part of this issue. A 4-page brochure containing this index is available for those who need one. To get your free copy, send a *stamped self-addressed envelope (legal size)* to:

Radio-Electronics
Annual Index
45 East 17th Street
New York, NY 10003

Any requests postmarked on or before April 30 are free. After that date there is a 50¢ fee. Questions and comments about anything other than the Index that are included with your request cannot be handled. Send them separately to our Editorial Offices.

Radio-Electronics, (ISSN 0033-7862) Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Second-Class Postage Paid at New York, N.Y. and additional mailing offices. One-year subscription rate: U.S.A. and U.S. possessions, \$13.00; Canada, \$16.00. Other countries, \$20.50 (cash orders only, payable in U.S.A. currency.) Single copies \$1.25. © 1981 by Gernsback Publications, Inc. All Rights reserved. Printed in U.S.A.

Subscription Service: Mail all subscription orders, changes, correspondence and Postmaster Notices of undelivered copies (Form 3579) to Radio-Electronics Subscription Service, Box 2520, Boulder, CO 80322.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

As a service to readers, Radio-Electronics publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, Radio-Electronics disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

VIDEO ELECTRONICS

DAVID LACHENBRUCH
CONTRIBUTING EDITOR

TUBELESS CAMERA



Video cameras have entered the all-solid-state age in the United States with the start of marketing of Hitachi's MOS camera, which uses a single $\frac{2}{3}$ -inch metal oxide silicon IC as an image sensor. The MOS sensor has 180,000 picture elements, providing a claimed 260-line horizontal resolution. The camera weighs 3.96 pounds.

The most noticeable aspect of the camera is its small size and light weight—indeed, the lens and viewfinder combined are larger than the camera itself. The picture differs from any made with a Vidicon pickup tube in that there is no lag, smear, or burn-in even when the camera is aimed directly at a light. Hitachi claims that the MOS is good for 100,000 hours, as compared with 5,000 hours' average life of a Vidicon. Among its advantages are low power consumption (5.3 watts), rapid start (picture appears in a half second), reliability, and ruggedness. The suggested list price is \$1,995.

MINI-VHS

While Japanese manufacturers were meeting to standardize on the portable VCR of the future using quarter-inch tape, it was revealed that JVC has developed a miniature cassette compatible with the VHS system that can be in production as early as next spring.

It will record for up to an hour at the slowest VHS speed in a new ultra-compact portable VCR developed by JVC that weighs about 5.5 pounds and is about 20% smaller than the Technicolor VCR, which uses non-standard quarter-inch cassettes.

The mini-cassettes can be played back through the portable recorder, or, with an adaptor, through any VHS recorder. JVC is understood to be talking with other companies in the VHS group to adopt its new system as a standard for portables. The new mini-VHS development isn't expected to deter Japanese companies from working on a new quarter-inch standard, but it could take some of the urgency out of their efforts.


NEW MINI-VCR

The smallest and lightest VCR to date made its debut in Germany this past September, and will be headed this way soon. Ironically, it's made in Japan, not Germany, but will bear the Grundig label in this country. The new recorder is made by Funai Electric and is compatible with the small recorder Funai makes for Technicolor, but it has been completely redesigned. Weight and battery has been trimmed to five pounds (four pounds without battery) as compared with Technicolor's seven pounds, and the entire recorder is about the size of a cigar box. It provides slow and fast speeds, freeze-frame, and records for up to an hour on a quarter-inch cassette only slightly larger than an audio cassette. The price will be about \$1,000 in the U.S., including power supply.

HIGH- DEFINITION TV

There have been plenty of proposals for high-definition television, most of them centering on 1,000-plus-line standards requiring about 30 MHz of bandwidth per channel. Now, along comes Imagevision, developed by Compact Video, which requires 10 MHz, is claimed to be "ready for delivery," and uses modified conventional equipment. Imagevision was demonstrated before the Society of Motion Picture and Television Engineers, where it received favorable comment.

Imagevision uses a new television standard called "PALAF" (for Phase Alternate Line Alternate Frame) and has 665 lines, claimed to provide the definition of 1,250 lines in other systems, with 24 non-interlaced frames per second. All the equipment used (such as cameras and videotape recorders) was commercially available gear modified for the system. The most successful demonstration of Imagevision was the projection of part of a movie being made using the system. The movie had been transferred to 35-mm film and was projected on a theater screen. Most observers agreed it looked every bit as good as a movie made directly on 35-mm film. Somewhat less successful were satellite-relayed video pictures projected by light-valve projection-TV systems—but that may be because the projectors became the limiting factors. R-E

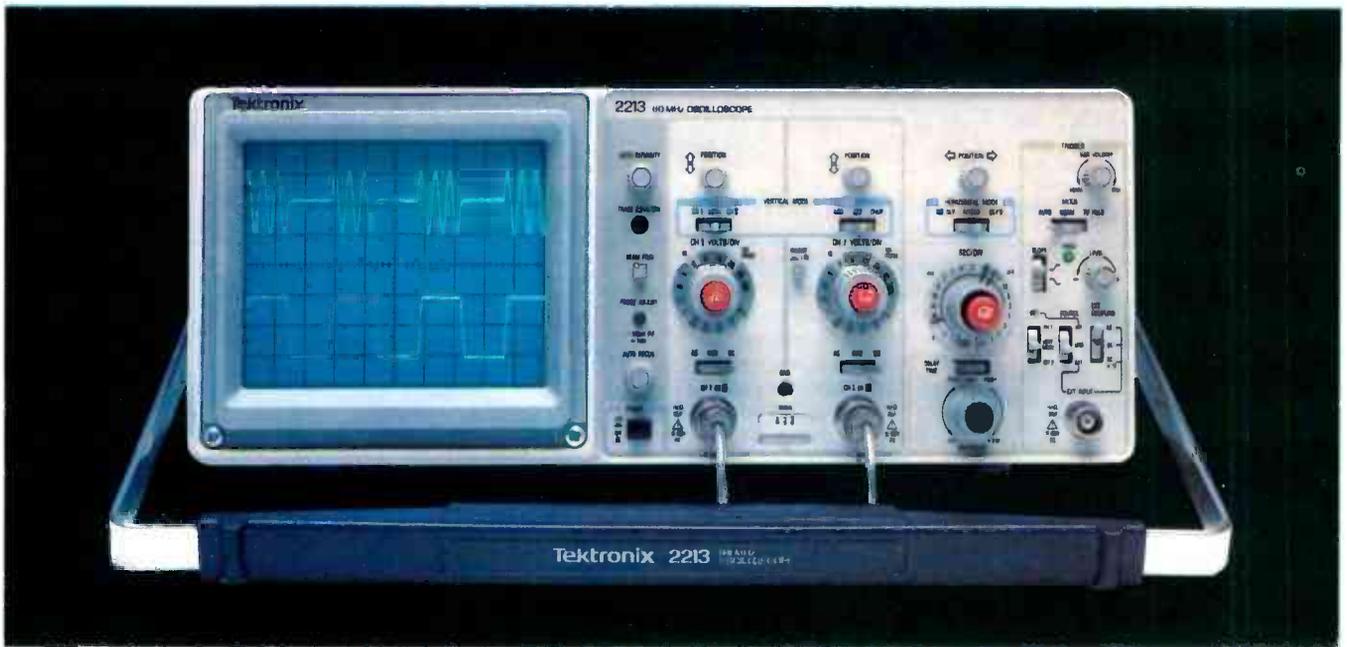

Introducing a direct line to a 60 MHz Tektronix scope built for your bench!

From the world's most respected name in oscilloscopes: a new scope, plus a new direct order number, that finally makes it practical to put Tektronix quality on your bench... at work or home.

Among professional engineers and technicians there is no substitute for the performance and reliability of Tektronix oscilloscopes.

Now, for the first time, Tektronix is offering an advanced scope at an unprecedented low price—and has a direct order line that lets you get your order processed today!

The scope: the 2213. Its radical new design brings you Tektronix quality for well below what you would pay for

lesser-name scopes.

The 2213's practical design includes 65% fewer mechanical parts, fewer circuit boards, electrical connectors and cabling. Result: a lower price for you plus far greater reliability.

Yet performance is pure Tektronix: there's 60 MHz bandwidth for digital and high-speed analog circuits. The sensitivity for low signal measurements. The sweep speeds for fast logic families. A complete trigger system for digital, analog or video waveforms. And new high-performance Tektronix probes are included!

2213 PERFORMANCE DATA

Bandwidth: Two channels, dc—60 MHz from 10 V/div to 20 mV/div. (50 MHz from

2 mV/div to 10 mV/div)

Sweep speeds: Sweeps from 0.5 s to 50 ns (to 5 ns/div with X10 mag).

Sensitivity: Scale factors from 100 V/div (10X probe) to 2 mV/div (1X probe). Accurate to $\pm 3\%$. Ac or dc coupling.

Delayed sweep measurements: Standard sweep, intensified after delay, and delayed.

(Need dual time-base performance and timing accuracy to $\pm 1.5\%$? Ask about our 2215 priced at \$1400.)

Complete trigger system: Modes include TV field, normal, vertical mode, and automatic; internal, external, and line sources; variable holdoff.

Probes: High perform-

ance, positive attachment, 10-14 pF and 60 MHz at the probe tip.

The price: Just \$1100 complete*. Order direct from Tektronix National Marketing Center. Phones are staffed by technical people to answer your questions about the 2213. Your direct order includes a 15-day return policy and full Tektronix warranty.

Now it's easier than ever to get your hands on a Tek scope!

ORDER TOLL-FREE

800-547-1845

Ask for Department 100

(In Oregon, Alaska and Hawaii: 1-503-627-5402 collect.) Lines are open from 8 am EST to 5 pm PST.

*Price FO B. Beaverton, OR.

WHAT'S NEWS

Educators confer on microcomputers

Microcomputer Week '82, the third annual conference co-sponsored by the Center for Advancement of Teaching and Learning (CATALYST) of Jersey City State College, will be held at the college from the 3rd to the 7th of March 1982.

The conference centers on microcomputers in education. Some 66 all-day seminars or short courses will be offered for professional development and improved performance. Each will include eight hours of instructions. Some seminars will extend over two or three days. There will also be 24 informal evening sessions—during dinner and continuing after dinner—for groups with special interests and problems.

Cost of the seminars range from \$95 for one day to \$73 per day for the whole week. A brochure with complete details, registration forms, etc., has been prepared. Further information is obtainable by phone from 201-434-2154 or 201-547-3094, or by mail from CATALYST Conference, H 112, Jersey City State College, 2039 Kennedy Boulevard, Jersey City, NJ 07305.

TV standards converter for video recorders

Early international television broadcasts were hampered by differing television standards. Systems using the 525-line frames of the United States, Japan, and other countries were incompatible with the 625-line standard of most of Europe. (At one time, France had an 815-line system.)

Those difficulties were overcome in a number of ingenious ways for the first few broadcasts, and very soon "system converters" were designed to input the signals of one system and change the number of lines, modulation method, sync signals, etc., to those of the system to which the signal was being relayed.

Color, with its NTSC, PAL, and SECAM systems, brought new difficulties, which were also quickly ironed out with new converters. Video recording

raised the problem anew, an unfortunate circumstance, since videotapes can be shipped more easily than international broadcasts can be set up.

But now a company called Instant Replay (2980 McFarlane Rd., Coconut Grove, FL 33133), has put on the market an Image Translator, in two models. The SMP-1 permits a viewer with a PAL recorder and receiver to play NTSC tapes, without modifying the receiver. The SMP-2 permits a viewer to play back tapes recorded in the PAL format in full color on an NTSC VCR, using an American TV receiver, without modification. It can be used with either direct-view or large-screen projection TV. Thus international video broadcasting's objective of cultural exchange is being extended to video recording.

The Image Translator is an extension of the publishing efforts of the manufacturer, *Instant Replay Video Magazine*, "the world's first video magazine," a two-hour tape published bi-monthly at a price of \$59.95 per issue. Believing the television image to be the most nearly perfect medium of international cultural exchange, and the videotape the most nearly universal unit for such exchange, owner and editor Chuck Azar developed the Translator to internationalize the videotape. To promote the internationalization further, a printed list of all Image Translator owners will be sent to all subscribers, to enable them to swap tapes between countries.

Improved approach in auto-focus camera

A new Pentax 35-mm SLR camera, the ME-F, expected on the market in early 1982, introduces a new computerized through-the-lens electronic focusing system. Measuring the actual focal contrast at the center of the field of vision, in a manner similar to that of the human eye, the system is claimed to be far more accurate than those that cover the whole field, or range-finder electronic systems that measure the image-field distance.



PENTAX ME-F single lens reflex camera with new 35-mm-70-mm Zoom lens.

The new camera focuses correctly on complex patterns, subjects behind glass, and over the whole depth-of-field range.

The ME-F lets the photographer know when the subject is in focus by means of a dual-signal indication: An LED lights in the viewfinder at the point of optimum focus and a beep signal sounds.

The list price of the ME-F—with zoom lens—is expected to be about \$1,000.

New VideoDisc features demonstrated in France

Dr. Jon K. Clemens, co-recipient of the Rhein Prize 1979, and Director of VideoDisc Systems at RCA's research laboratories, demonstrated the advanced capabilities of the new RCA 'CED' (Capacitance Electronic Disc) system at the recent Vidcom convention in Cannes, France. Dr. Clemens showed such features as programmable random access, high-speed visual search, repeat picture, and automatic repetition of selected program segments.

In demonstrating the visual-search feature, Dr. Clemens used the prototype system's two

search speeds, 16× and 120×. He also programmed the player to repeat sections of the disc, demonstrated its repeat-picture capability, and proved its wear-free feature by playing a still picture from a single groove for 20 minutes—amounting to 9,000 replays of the same groove.

No date was set for the introduction of those advanced VideoDisc player features to the market.


FAA renovating nation's air traffic control

The Federal Aviation Administration is undertaking a program to upgrade air-traffic control computers throughout the country. The program is aimed at meeting projected air-traffic demands of the 1990's and beyond. It will call for replacement of the 23 Air Route Traffic Control Center computers with an advanced system.

RCA has been awarded a \$4 million contract to provide system engineering and technical analysis in the program. RCA's work will cover five areas: requirements specification and allocation; cost, schedule, and

continued on page 12

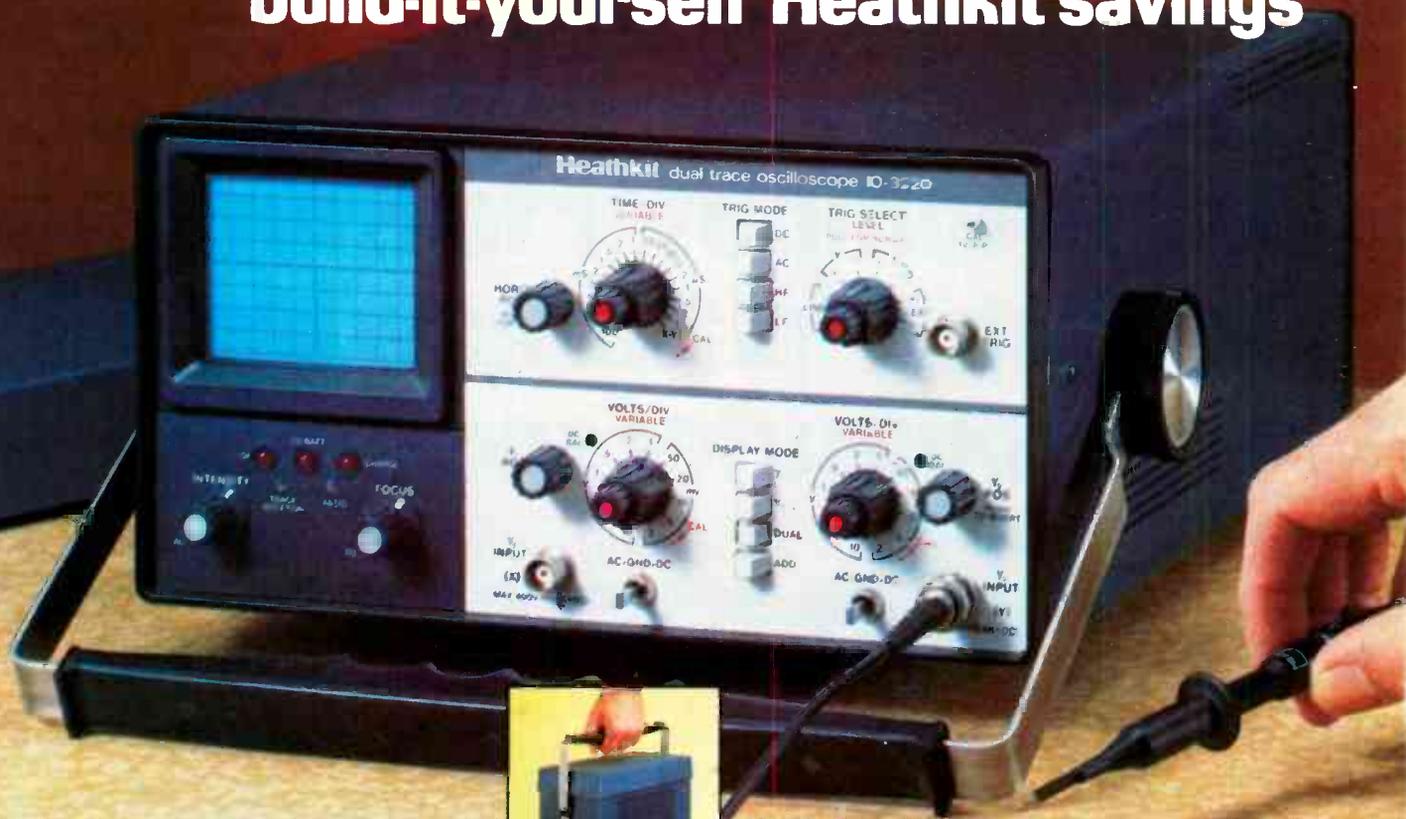NEW! Here's a professional, portable DC-20 MHz Oscilloscope with build-it-yourself Heathkit savings



Compact enough to fit under an airplane seat, the Heathkit IO-3220 represents outstanding value in its class. Weighing only 16 pounds, the IO-3220 is designed for field service troubleshooters who need a light, portable battery-operated scope for use where AC power is not available.

Dual-trace versatility: The IO-3220 allows you to compare two different signals simultaneously – to make input/output comparisons, check phase relationships and accomplish other complex measurements. Algebraic functions add versatility.

Special invert display function: Enables you to compare two waveforms that are nearly 180 degrees out of phase – by inverting one of the waveforms.

FREE CATALOG

Complete details on Heathkit oscilloscopes – and nearly 400 other electronic kits for your home, work or pleasure – are in the new Heathkit catalog. Send the coupon at right for yours today, or pick one up at any of the 65 convenient Heathkit Electronic Centers** located throughout the U.S. and Canada.

If coupon is missing, write Heath Co., Dept. 020-866, Benton Harbor, MI 49022.



Heathkit®

*Mail Order, F.O.B. Benton Harbor, MI. Also available assembled, mail order priced at \$995.00. F.O.B. Prices, specifications and product availability subject to change without notice. **See the white pages of your telephone book for the Heathkit Electronic Center nearest you. Heathkit Electronic Centers in the U.S. are operated by Veritechnology Electronics Corporation, a wholly-owned subsidiary of Zenith Radio Corporation. GX-387

X-Y inputs for Lissajous measurements: Feed two separate input signals to the IO-3220.

Wide DC-20 MHz bandwidth: The IO-3220 can measure a very wide range of input signals.

Outstanding sensitivity: Vertical signals as low as 2 millivolts can be accurately measured by the very sensitive IO-3220. Accuracy is as high as 3 percent (from 20-30 deg. C), on both vertical and horizontal measurements.

Save more than 30% when you build it yourself: The IO-3220 Portable 20 MHz Oscilloscope Kit is value-priced at just \$689.95*.

Easy to build: Thorough Heathkit assembly manuals take you step-by-step, from unpacking to final plug-in. Anyone can do it. And experienced service techs are just a phone call away, to help you during building or servicing.

MAIL TO: Heath Company, Dept. 020-866
Benton Harbor, MI 49022

YES, Please send me your free Heathkit Catalog.
I'm not currently receiving your catalog.

Name _____

Address _____

City _____ State _____

GX-387 _____ Zip _____

Now NRI takes you inside the new TRS-80 Model III microcomputer to train you at home as the new breed of computer specialist!

NRI teams up with Radio Shack advanced technology to teach you how to use, program, and service state-of-the-art microcomputers.



It's no longer enough to be just a programmer or a technician. With microcomputers moving into the fabric of our lives (over 250,000 of the TRS-80™ alone have been sold), interdisciplinary skills are demanded. And NRI can prepare you with the first course of its kind, covering the complete world of the microcomputer.

Learn At Home in Your Spare Time

With NRI training, the programmer gains practical knowledge of hardware, enabling him to design simpler, more effective programs. And, with advanced programming skills, the technician can test and debug systems quickly and easily.

Only NRI gives you both kinds of training with the convenience of home study. No classroom pressures, no night school, no gasoline wasted. You learn at your convenience, at your own pace. Yet you're always backed by the NRI staff and your instructor, answering questions, giving you guidance, and available for special help if you need it.

You Explore the New TRS-80 Model III Inside and Out

NRI training is hands-on training, with practical experiments and demonstrations as the very foundation of

your knowledge. You don't just program your computer, you go inside it...watch how circuits interact...interface with other systems...gain a real insight into its nature.



Training includes the new TRS-80 Model III microcomputer, 6-function LCD Beckman multimeter, and the NRI Discovery Lab with hundreds of tests and experiments.

You also work with a precision 26-scale, 6-function LCD Beckman multimeter featuring full portability and a 3½ digit display. Using it along with the exclusive NRI Discovery Lab and your TRS-80, you perform over 60 separate experiments in all. You learn how to troubleshoot and gain greater understanding of the information

your tests give you.

Advanced Technology Microcomputer Is Yours to Keep

As part of your training, NRI sends you the new, state-of-the-art TRS-80 Model III microcomputer. This functional unit is complete with 65-key keyboard and 12" display in one desk-top unit. It features

high-speed cassette loading, built-in interface for parallel printer, and provisions for optional disk drive. Its 4K RAM is internally expandable to 16K or 48K and its BASIC language is compatible with most Model I software.

Along with your multimeter and the NRI Discovery Lab, this latest concept in advanced microcomputers is yours to learn with, yours to keep and use for your own personal programs, business use, and other applications.

Send for Free Catalog...No Salesman Will Call

Get all the details on this exciting course in NRI's free, 100-page catalog. It shows all equipment, lesson outlines, and facts on other electronics courses such as Complete Communications with CB, TV and Audio Servicing, Digital Electronics, eleven different interest areas in all.

Send today, no salesman will ever bother you. Keep up with the latest technology as you learn on the world's most popular computer. If postcard has



been used, write to NRI Schools, 3939 Wisconsin Ave., Washington, D.C. 20016.

NRI Schools
 McGraw-Hill Continuing
 Education Center
 3939 Wisconsin Ave.
 Washington, D.C. 20016
We'll train you for the good jobs.



(TRS-80 is a trademark of the Radio Shack division of Tandy Corp.)

WHAT'S NEWS

continued from page 6

risk analysis; performance analysis; simulation; and modeling; feasibility and trade studies; and technical management standards and practices.

Super circuit chips speed data tenfold

"Super chips," that Hughes Aircraft call "electronic circuits that resemble an array of 100 Los Angeles street maps on a thumb tack," are now being developed at Hughes' laboratories. Called Very High Speed Integrated Circuits (VHSIC), they will be more reliable and require less power than integrated circuits now in use.


The chip technology used in the program includes CMOS (Complementary Metal Oxide Semiconductor) and SOS (Sili-

con On Sapphire). The SOS technology is especially significant for military systems, because it is inherently hardened against radiation.

Hughes has also received an Army contract to develop a high-speed electron-beam lithography system that will focus beams of electrons to write circuit patterns in submicron dimensions. Those circuit patterns will be converted into transistors and interconnects smaller than any now in production.

Yankee chess computer is new world champion

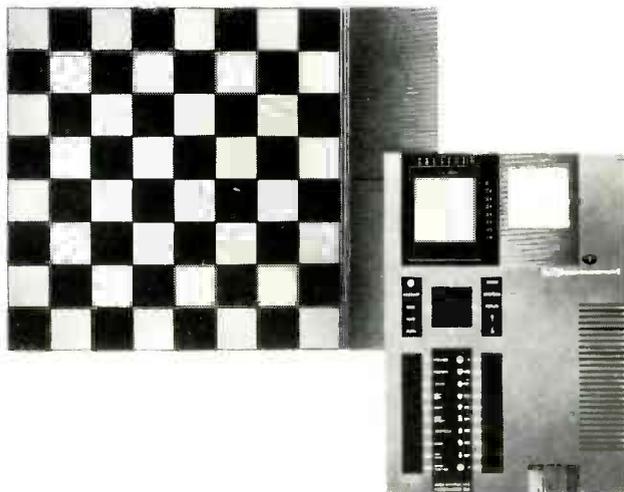Chess Champion Mark V, made by SciSys Computer Inc. of New York City, emerged as the winner in the Commercial Division, World Micro Computer Chess



THE CHESS CHAMPION MARK V.

Championships, held last Fall in Travemunde, Germany. The tournament was held under the auspices of the International Chess Association and the World Chess Federation. It was open to all chess programs executed by readily available one-chip microprocessors.

The *Chess Champion Mark V* is an AC-powered chess computer with an integral LCD chessboard. Its 32K memory is many times more powerful than the average home computer, and its variable time control enables it to play any form of chess, from Speed to Tournament. It can play 12 games simultaneously against humans, other computers, or even against itself. On request, it can analyze, comment, or advise on the game in progress, and can provide a complete game history or predict the outcome.

Sony Corp sets up a U.S. laboratory

Sony Consumer Electronics Laboratories (SOCEL) a division of Sony Corp of America, will be located in the Century Plaza in Paramus, NJ, reports Sony Corp. executive vice president Kenji Tamiya. The laboratories will conduct research, development, and design work, particularly the areas of CATV systems and terminals, receivers

for direct satellite broadcasts, and videotext/teletext systems and terminals. "The laboratories will offer a unique opportunity for interaction between American and Japanese engineers," said Mr. Tamiya.

The new laboratory is the latest in a number of Sony "firsts" in America. In 1972 Sony opened the first U.S. color TV plant owned by a Japanese-based company, in San Diego, CA. In 1977, it established what is now one of the largest magnetic tape plants in the world, in Dothan, AL. The Sony Technology Center in Palo Alto, CA, carries out broadcast equipment research, development, and manufacturing, and was the first Sony facility to be located outside Japan.

Electronic newspaper debuts in Chicago

NITE-OWL, a full-channel teletext publication, is now being broadcast on WFLD-TV, Channel 32, Chicago. Designed for late-night information, it supplies up-to-the-minute news, sports, weather, and other information, and advertising.

Information is presented in text form (teletext) on the screen. Teletext was first developed in Great Britain and is now being offered commercially in the United States by Field Electronic Publishing. **R-E**



PHOTO-LITHOGRAPHY MACHINE that will be used to etch VHSIC circuits on chips the size of a thumbtack. Hughes and five other firms are in the program conducted by the Defense Department to develop the high-speed superchips. The machine is being operated by Hughes technician Margaret Sanchez.

LETTERS

SENDING GOOD CW

Fie on Herb Friedman, and a fig in his ear! He seems to be showing an infirmity of old age—intolerance—and maybe even a lack of good sense in "Communications Corner," **Radio-Electronics**, October 1981.

As a ham, from my earliest days, I tried diligently to send good CW, first on a straight key, then on a swiper (homebrew) and then on the ultimate (for those days): a bug (also homebrew). And, I, too, share his view that handwrought CW is a pure performing art.

First ticketed in 1933, I am now (after a long layoff) a reconstituted ham. Once I got back on the air, I was thunderstruck by the bad straight key fists, the miserably misadjusted and misrun bugs, and that ultimate abomination: the key running its operator instead of the other way around. Do you ever hear a "6" sent with four dots any more?

Then, I, too became aware of the beautiful CW coming from microprocessor keyboards, whether at 20 or 60 wpm. What a joy! As with good writing, I believe that CW should be sent with clarity and intelligibility, and to hell with dialects or accents. If it takes a machine to do it, so be it! It's all right with me.

So come on, Herb. Don't display the length and condition of your teeth. Get a good keyboard and join the fun. I have one (homebrew) and it's better than crackerjack.

C.H. FRERES, KJ6G,
San Diego, CA

NIKOLA TESLA

I would like to associate myself with the thoughts expressed in the letters by Marc Seifer and Vince Marasco in the June 1981 **Radio-Electronics** about Nikola Tesla.

Tesla is one of my favorites. I can turn on my Edison light bulb and visualize, in some vague manner, Tesla's rotating magnetic field at some remote point miles away. Yes, it is truly Tesla's rotating magnetic field—the one he discovered before he invented a device wherein the field could reside and produce rotating power: the induction motor. And subsequently, he was forced to invent a device to generate that magnificent field—the polyphase alternator.

Had Edison's proposal for electric power distribution prevailed, we would now have direct-current generating power plants spaced about every mile where electricity is in use today. And we would know no such thing as the sealed motor-compressor system used in modern refrigeration and air-conditioning sys-

tems. Edison's DC voltage could not be stepped up or down with transformers, and the losses in his system would be great.

What about electric-power transmission without wires? Some large company—I would suggest Westinghouse—should embark upon a research project to rediscover that lost art.

I could go on and on. I am interested in Tesla and his discoveries. A machinist friend of mine is also fascinated, as are others in the electronics field. Had Nikola Tesla never existed, nevertheless, civilization would have required one like him just the same.

Knowledgeable people have been made aware of most of the other great men of the past—so why not the unique Nikola Tesla?

ALFRED C. POWELL,
Pensacola, FL

Why not, indeed? Well, you're doing your part.

LED VU METER ENCLOSURE

Reading through the May 1981 **Radio-Electronics**, I was struck by the appearance—in the article, "Build This LED VU Meter"—of an enclosure produced by our client, PacTec Corp., subsidiary of LaFrance Corp. I checked carefully for a reference to the PacTec Enclosure, to no avail. In fact, I noted that the kit for the VU-1 available from BFA Electronics actually includes no case at all.

Your readers might like to know that the case seen in the article is available from PacTec, Enterprise and Executive Avenues, Philadelphia, PA 19153. It is one of the series CM enclosures, and appears specifically to be a CM 5-200.

We have many prototyping kits in our line. The kits are particularly useful to designers and hobbyists, and are available in a wide range of sizes. I hope that you and your readers will find this material useful.

JON H. CLINCH,
Larwin/Livers Associated, Inc.

RADAR DETECTORS

In reading the "Letters" department in **Radio-Electronics**, and being the owner of one of the best "Super Het" radar detectors on the market, I can only feel sorry for those people who must constantly challenge the right to own and operate such devices. It is a shame that, for once, the foxes were "outfoxed themselves" by allowing a hole in the law big enough to

continued on page 22

WHY K40 BECAME THE LARGEST SELLING CB ANTENNA IN JUST ONE YEAR!

Because

K40™

OFFERS A MONEY BACK

DOUBLE GUARANTEE

- TRANSMITS FARTHER
- RECEIVES CLEARER

...THAN ANY ANTENNA IT REPLACES!



**AN AMERICAN MADE PRODUCT
FROM AN AMERICAN COMPANY.
Call your local CB Dealer**



For a **FREE** demo!

AMERICAN ANTENNA
© Copyright 1979 American Antenna Elgin, Illinois

The \$149⁹⁵ personal computer.



Introducing the Sinclair ZX81

If you're ever going to buy a personal computer, now is the time to do it.

The new Sinclair ZX81 is the most powerful, yet easy-to-use computer ever offered for anywhere near the price: only \$149.95* completely assembled.

Don't let the price fool you. The ZX81 has just about everything you could ask for in a personal computer.

A breakthrough in personal computers

The ZX81 is a major advance over the original Sinclair ZX80—the world's largest selling personal computer and the first for under \$200.

In fact, the ZX81's new 8K Extended BASIC offers features found only on computers costing two or three times as much.

Just look at what you get:

- Continuous display, including moving graphics
- Multi-dimensional string and numerical arrays

*Plus shipping and handling. Price includes connectors for TV and cassette, AC adaptor, and FREE manual.

- Mathematical and scientific functions accurate to 8 decimal places
- Unique one-touch entry of key words like PRINT, RUN and LIST
- Automatic syntax error detection and easy editing
- Randomize function useful for both games and serious applications
- Built-in interface for ZX Printer
- 1K of memory expandable to 16K

The ZX81 is also very convenient to use. It hooks up to any television set to produce a clear 32-column by 24-line display. And you can use a regular cassette recorder to store and recall programs by name.

If you already own a ZX80

The 8K Extended BASIC chip used in the ZX81 is available as a plug-in replacement for your ZX80 for only \$39.95, plus shipping and handling—complete with new keyboard overlay and the ZX81 manual.

So in just a few minutes, with no special skills or tools required, you can upgrade your ZX80 to have all the powerful features of the ZX81. (You'll have everything except continuous display, but you can still use the PAUSE and SCROLL commands to get moving graphics.)


With the 8K BASIC chip, your ZX80 will also be equipped to use the ZX Printer and Sinclair software.

Order at no risk**


We'll give you 10 days to try out the ZX81. If you're not completely satisfied, just return it to Sinclair Research and we'll give you a full refund.

And if you have a problem with your ZX81, send it to Sinclair Research within 90 days and we'll repair or replace it at no charge.

**Does not apply to ZX81 kits.

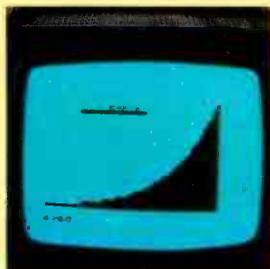

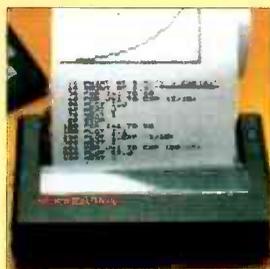NEW SOFTWARE: Sinclair has published pre-recorded programs on cassettes for your ZX81, or ZX80 with 8K BASIC. We're constantly coming out with new programs, so we'll send you our latest software catalog with your computer.



ZX PRINTER: The Sinclair ZX Printer will work with your ZX81, or ZX80 with 8K BASIC. It will be available in the near future and will cost less than \$100.



16K MEMORY MODULE: Like any powerful, full fledged computer, the ZX81 is expandable. Sinclair's 16K memory module plugs right onto the back of your ZX81 (or ZX80, with or without 8K BASIC). Cost is \$99.95, plus shipping and handling.



ZX81 MANUAL: The ZX81 comes with a comprehensive 164-page programming guide and operating manual designed for both beginners and experienced computer users. A \$10.95 value, it's yours free with the ZX81.

The \$99⁹⁵ personal computer.

Introducing the ZX81 kit

If you really want to save money, and you enjoy building electronic kits, you can order the ZX81 in kit form for the incredible price of just \$99.95* It's the same, full-featured computer, only you put it together yourself. We'll send complete, easy-to-follow instructions on how you can assemble your ZX81 in just a few hours. All you have to supply is the soldering iron.

How to order

Sinclair Research is the world's largest manufacturer of personal computers.

The ZX81 represents the latest technology in microelectronics, and it picks up right where the ZX80 left off. Thousands are selling every week.

We urge you to place your order for the new ZX81 today. The sooner you order, the sooner you can start enjoying your own computer.

To order, simply call our toll free number, and use your MasterCard or VISA.

To order by mail, please use the coupon. And send your check or money order. We regret that we cannot accept purchase orders or C.O.D.'s.

CALL 800-543-3000. Ask for operator #509. In Ohio call 800-582-1364. In Canada call 513-729-4300. Ask for operator #509. Phones open 24 hours a day, 7 days a week. Have your MasterCard or VISA ready.

These numbers are for orders only. For information, you must write to Sinclair Research Ltd., 2 Sinclair Plaza, Nashua, NH 03061.

sinclair



AD CODE 02RE	PRICE†	QTY.	AMOUNT
ZX81	\$149.95		
ZX81 Kit	99.95		
8K BASIC chip (for ZX80)	39.95		
16K Memory Module (for ZX81 or ZX80)	99.95		
Shipping and Handling	4.95		\$4.95
TOTAL			

MAIL TO: Sinclair Research Ltd., One Sinclair Plaza, Nashua, NH 03061.

NAME _____

ADDRESS _____

CITY/STATE/ZIP _____


† U.S. Dollars

At CIE, you get electronics career training from specialists.

If you're interested in learning how to fix air conditioning, service cars or install heating systems – talk to some other school. But if you're serious about electronics...even earning an Associate Degree... come to CIE – The Electronics Specialists.

John E. Cunningham

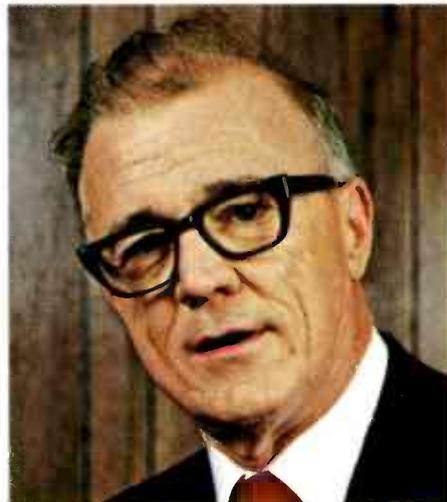**Special Projects Director
Cleveland Institute of Electronics**



My father always told me that there were certain advantages to putting all your eggs in one basket. "John," he said, "learn to do one important thing better than anyone else, and you'll always be in demand."

I believe he was right. Today is the age of specialization. And I think that's a very good thing.

Consider doctors. You wouldn't expect your family doctor to perform open heart surgery or your dentist to set a broken bone, either. Would you?

For these things, you'd want a specialist. And you'd trust him. Because you'd know if he weren't any good, he'd be out of business.

Why trust your education and career future to anything less than a specialist?

You shouldn't. And you certainly don't have to.

FACT: CIE is the largest independent home study school in the world that specializes exclusively in electronics.

We have to be good at it because we put all our eggs in one basket: electronics. If we hadn't done a good job, we'd have closed our doors long ago.

Specialists aren't for everyone.

I'll tell it to you straight. If you think electronics would make a nice hobby, check with other schools.

But if you think you have the cool – and want the training it takes – to make sure that a sound blackout during a prime time TV show will be corrected in seconds – then answer this ad. You'll probably find CIE has a course that's just right for you!

At CIE, we combine theory and practice. You learn the best of both.

Learning electronics is a lot more than memorizing a laundry list of facts about circuits and transistors. Electronics is interesting because it's based on some fairly recent scientific discoveries. It's built on ideas. So, look for a program that starts with ideas – and builds on them.

That's what happens with CIE's Auto-Programmed® Lessons. Each lesson uses world-famous "programmed learning" methods to teach you important principles. You explore them, master them completely. . . before you start to apply them!

But beyond theory, some of our courses come fully equipped with the electronics gear to actually let you perform hundreds of checking, testing and analyzing projects.

In fact, depending on the course you take, you'll do most of the basic things professionals do every day – even use a Digital Learning Laboratory to apply the digital theory essential today to keep pace with electronics in the eighties.

Plus there's a professional quality oscilloscope you build and use to "see" and "read" the characteristic waveform patterns of electronic equipment.

You work with experienced specialists.

When you send us a completed lesson, you can be sure it will be reviewed and graded by a trained electronics instructor, backed by a team of technical specialists. If you need specialized help, you get it fast . . . in writing from the faculty specialists best qualified to handle your question.

People who have known us a long time, think of us as the "FCC License School."

We don't mind. We have a fine record of preparing people to take . . . and pass . . . the government-administered FCC License exams. In fact, in continuing surveys nearly 4 out of 5 of our graduates who take

the exams get their Licenses. You may already know that an FCC License is needed for some careers in electronics – and it can be a valuable credential anytime.

Associate Degree

Now, CIE offers an Associate in Applied Science Degree in Electronics Engineering Technology. In fact, all or most of every CIE Career Course is directly creditable towards the Associate Degree.


Find out more! Mail this card for your FREE CATALOG today!

If the card is gone, cut out and mail the coupon.

I'll send you a copy of CIE's FREE school catalog, along with a complete package of independent home study information.

For your convenience, I'll try to arrange for a CIE representative to contact you to answer any questions you may have.

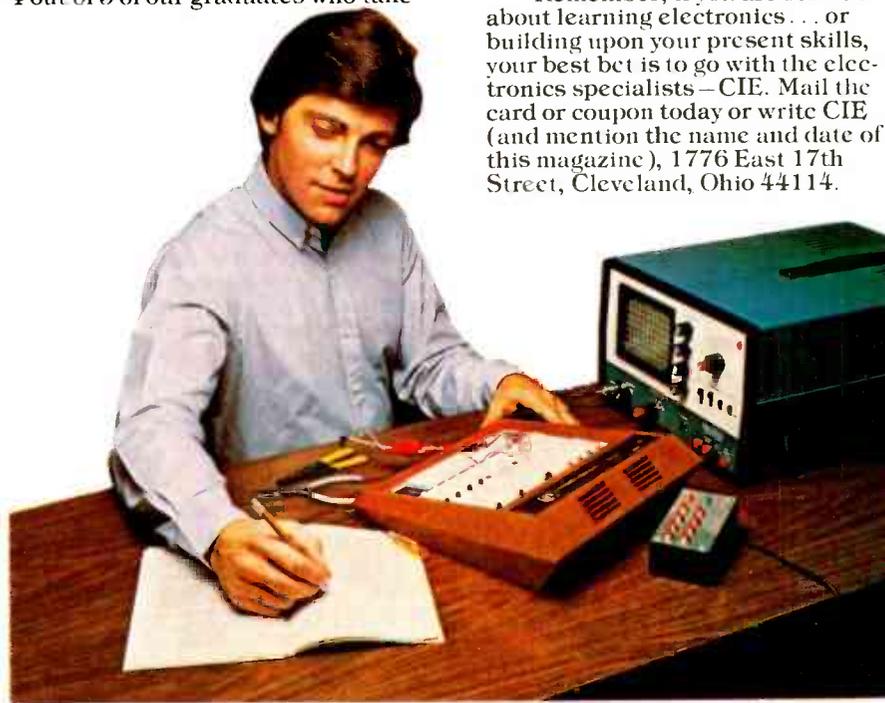Remember, if you are serious about learning electronics . . . or building upon your present skills, your best bet is to go with the electronics specialists – CIE. Mail the card or coupon today or write CIE (and mention the name and date of this magazine), 1776 East 17th Street, Cleveland, Ohio 44114.



Pattern shown on oscilloscope screen is simulated.

CIE Cleveland Institute of Electronics, Inc.
1776 East 17th Street, Cleveland, Ohio 44114

YES . . . John, I want to learn from the specialists in electronics – CIE. Send me my FREE CIE school catalog – including details about the Associate Degree program – plus my FREE package of home study information.

Print Name _____

Address _____ Apt. _____

City _____

State _____ Zip _____

Age _____ Phone (area code) _____

Check box for G. I. Bill information: Veteran Active Duty

Mail today!

RE-30

FEBRUARY 1982

21

50MHz DUAL TRACE



MODEL MS-6050

THE FEATURES YOU WANT

- 6" flat faced PDA/CRT with 15kV acceleration, internal graticle and external trace rotator.
- 50MHz dual trace (-3db), 70MHz (-6db); triggers beyond 80MHz, rise time ~7ns.
- Built-in signal delay of 50ns in display, plus trigger delay of 100ms to 1μs in 5 steps plus vernier.
- 1 mV sensitivity thru 10MHz, 5mV thru 50MHz; with CH2 invert.
- Time base has 20 ranges from 0.2μs to 0.5s/Div plus x5 magnifier.
- Fully shielded switching regulator power supply and shielded transformer.
- Has TV sync, X-Y or X-Y-Z.
- Clean lay-out with glass PCB's etc. for easy service and calibration.
- Complete with two hook-on probes, spare fuse and detachable UL listed AC cord. One year parts and labor warranty.

AT PRICES YOU CAN AFFORD!

	1-9 Ea.	10 Up Each
MODEL MS-6050	\$1079	\$1025
MODEL MS-6040	899	825

(Same as shown above but 40MHz dual trace with sweep delay only)

**NORTH
AMERICAN**



1126 Cornell Avenue, Cherry Hill, NJ 08002
Tel. (609) 488-1060

CIRCLE 26 ON FREE INFORMATION CARD

LETTERS

continued from page 13

squeeze my Q-1000 detector through.

I don't believe for one moment that the policeman operating the radar unit is primarily interested in saving my life on the roadways, or is instructed and knowledgeable enough to use the device without error. When I see a policeman just sitting behind a bush, operating those objectionable devices, I see my state and local tax money being wasted.

With crime the way it is today, I think that speeding is the lowest rung on the ladder when it comes to breaking the law. If as much time went into combatting other areas of crime as is spent in playing "cat and mouse" with the motorist, I think we would see a sharp decline in crime in those really important areas. Besides, if it were not for the high revenue collected by ticketing motorists for their deeds, I doubt whether we would see policemen just sitting around, relaxing in their cars with their radar units.

To say that every radar-detector owner has it solely for the purpose of speeding without getting caught is like saying that anyone who owns a gun is planning a bank job or an assassination. What the complainers need is to be tagged by radar; then their attitudes would change. I have seen so many radar traps that were cleverly set up, that I hate to think about how much money was collected that way.

Let us face the facts: As long as radar is used the way it is, and radar detectors are legal—as they should be—then the game will continue on the highways. I, for one, will continue to plug in my detector for protection.

M.J. RYBICKI,
Berwyn, IL

THE PIANOCORDER

We read Warren Baker's article about the Pianocorder in your November 1981 issue with much interest. It is certainly a fascinating development, and we are pleased to have licensed Superscope to reproduce many of our piano rolls on their cassettes.

I do object to a few minor points, however. The so-called "old-fashioned" pneumatic players are still being manufactured by the thousands; and so are the rolls, which are not nearly as "fragile" as you might be led to believe. Some of our products are 80 years old, and still performing well.

In addition, rolls bear not only the music but the printed lyrics as well, positioned to appear simultaneously with their corresponding notes. Grouping around an "old-fashioned" player, and singing along with the rolls, is a pleasure that no electronic update has yet surpassed.

QRS MUSIC ROLLS, INC.,
Robert J. Berkman, Adm. Assistant

BACKSCATTER

I'd like to comment on the article by Mr. Stanley Leinwoll, "Why Radio Moscow is
continued on page 103

Radio- Electronics

Hugo Gernsback (1884-1967) founder

M. Harvey Gernsback, editor-in-chief

Larry Steckler, CET, publisher

Arthur Kleiman, managing editor

Josef Bernard, K2HUF, technical editor

Carl Laron, WB2SLR, assistant editor

Jack Darr, CET, service editor

Leonard Feldman

contributing hi-fi/video editor

Robert F. Scott, semiconductor editor

Herb Friedman, communications editor

Gary H. Arlen, contributing editor

David Lachenbruch, contributing editor

Earl "Doc" Savage, K4SDS, hobby editor

Ruby Yee, production manager

Robert A. W. Lowndes, production
associate

Joan Burwick, production assistant

Joan Roman, circulation director

Arline R. Fishman,

advertising coordinator

Cover photo by Robert Lewis

Radio-Electronics is indexed in *Applied Science & Technology Index and Readers Guide to Periodical Literature.*

Gernsback Publications, Inc.
200 Park Ave. S., New York, NY 10003
President: M. Harvey Gernsback
Vice President: Larry Steckler

ADVERTISING SALES 212-777-6400

Larry Steckler
Publisher

EAST

Stanley Levitan
Radio-Electronics
200 Park Ave. South
New York, NY 10003
212-777-6400

MIDWEST/Texas/Arkansas/Okla.


Ralph Bergen
The Ralph Bergen Co., Inc.
540 Frontage Road—Suite 325
Northfield, Illinois 60093
312-446-1444

PACIFIC COAST Mountain States

Marvin Green
Radio-Electronics
413 So. La Brea Ave.
Los Angeles, Ca 90036
213-938-0166-7


SOUTHEAST

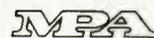Paul McGinnis
Paul McGinnis Company
60 East 42nd Street
New York, N.Y. 10017
212-490-1021



NEW!

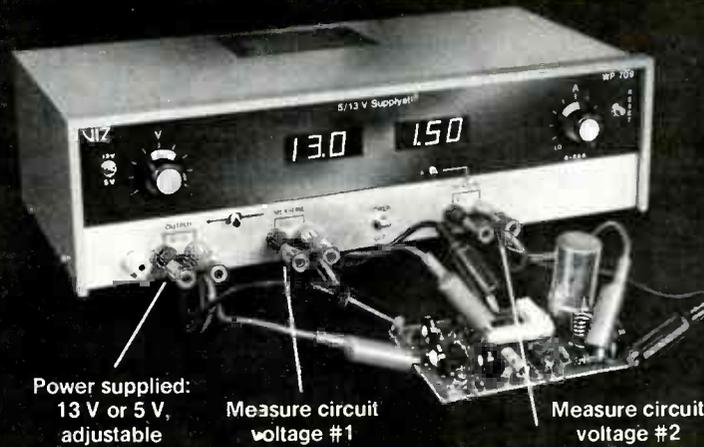**WP-709.
Double-slot
Supplyst™
power supply.**



Power supplied:
13 V or 5 V,
adjustable

Measure circuit
voltage #1

Measure circuit
voltage #2

Outputs: 5V or 13V DC,
adjustable $\pm 1\frac{1}{2}$ V
Zero to 7.5 amp, each voltage.

Two LED displays,
monitor V or A—
or two DC voltmeters

Adjustable current limiting

Only
\$299.75.

DC power to test logic or mobile equipment. Another VIZ Value

HERE'S REAL PRECISION

Select the precise voltage you want: 5V or 13V, adjustable $\pm 1\frac{1}{2}$ V at each range. Output is laboratory quality. Ripple less than 10mV, peak to peak. Regulation better than 0.1%.

HERE'S REAL POWER

Up to 7.5 amp. at each voltage—

plenty for computer circuits, PA systems, mobile transmitters, autos, boats, planes.

HERE'S REAL CONVENIENCE

Front panel controls for instant voltage adjustment and precise fine adjustment to within 0.1V. Two 3-digit LED displays permit continuous

monitoring of both voltage and current during use. Current limiting control with instant pushbutton reset.

The WP-709 is like two precision power supplies for a price less than you might pay for one— PLUS two digital DC voltmeters.

VIZ Supplyst™

power supplies with digital displays of voltage and current



WP-705 \$289.95

Single output
0-50VDC, 0-2A.



WP-707 \$374.75

Dual output
Two 0-25VDC, 0-2A.

WP-706 \$295.95

Single output
0-25VDC, 0-4A.



WP-708 \$424.95

Triple output Two 0-20VDC, 0-2A.
One 5VDC, 0-4A.



VIZ DC power supplies

Fully regulated, continuously adjustable voltage outputs with short circuit protection. Analog meters and overload indicators.



Dual WP-702A Two 0-20VDC, 0-200mA **\$150.75**



Single WP-703A
0-20VDC, 0-500mA **\$107.00**



Single WP-704A
0-40VDC, 0-250mA **\$117.55**

VIZ RELIABILITY

VIZ is a 50 year-old company. Our instruments are fully warranted, parts and labor, for a year. All items tested to NBS standards. We offer service and parts availability for a minimum of ten years. Over 15 repair depots in U.S.A.

Want full technical details and a demonstration? Call toll-free. 1-800-523-3696, for the VIZ distributor nearest you

VIZ

**Look to VIZ for value, quality, availability.
Over 70 instruments in the line— PLUS full accessories.**

VIZ Mfg. Co., 335 E. Price St., Philadelphia, PA 19144

CIRCLE 7 ON FREE INFORMATION CARD

SATELLITE/TELETEXT NEWS

GARY ARLEN
CONTRIBUTING EDITOR

TELETEXT LOOK-ALIKE SERVICES

Although line 21 of the vertical blanking interval is used primarily for closed captions for people with impaired hearing, a number of new activities are making that channel look more like teletext. Dozens of programs on ABC, NBC, and PBS are transmitted with those closed captions each week; a special *TeleCaption* decoder is required.

But in the past few months, several projects have gotten underway to add more text services. For example, early in the year the networks began transmitting "InfoData," which is a text sequence, used initially to announce which programs will be captioned during the coming week. More recently, KCET-TV Channel 28 in Los Angeles began carrying "Newsline," a version of the Associated Press news "ticker" used by cable TV systems. In that service, electronic versions of the news wire scroll across the screen of TV sets keyed into the captioning system. WHA-TV in Madison Wisconsin, KWCM-TV in Appleton, Minnesota and WNET in Newark, NJ are planning similar news and information systems on line 21. All are public-TV stations.

TEXT VIA SATELLITE

Several teletext packages, intended primarily for cable-TV usage, are going aloft via satellite during the coming months. The most ambitious is one that will supplement "The Weather Channel," a new all-day weather-information service due to get under way in 1982. The teletext portion will include local weather reports transmitted from the Weather Channel's Atlanta headquarters to "Weather STAR" addressable teletext receivers in various cities. Meanwhile, another 24-hour text-only weather-information service, "View Weather," is being transmitted as part of the CableText package on Satcom I Transponder 6.

Perhaps the most substantial teletext-via-satellite project is the one now under way at Time Inc. About 4,000 pages of information are being sent over a full transponder from Time Inc. headquarters in New York to Southwestern Cable TV in San Diego (owned by a Time subsidiary) as part of a major teletext test.

AROUND THE SATELLITE CIRCUIT

Blonder-Tongue Laboratories, a long-time respected supplier of cable-TV hardware, is getting into the earth-station business with a new dish and earth-station modulator.

Forget any ideas about using satellites to collect solar power and beam it down to earth as the next big wave of satellite activity after communications satellites. The U.S. Department of Energy gave a tentative approval to such a concept, which would probably take 50 years to put into place. But a few months ago the National Research Council recommended against such a plan, saying it would be far too costly—as much as 3 trillion dollars. Furthermore, such a solar-power satellite would probably create interference with communications satellites and there would be other technical and political problems in developing such a system. But, just in case, NASA is going to continue keeping an eye on the idea. ...

Metromedia is now sending the Merv Griffin Show to TV stations; Merv's show is transmitted on Westar III every morning, to be taped by stations which run it later in the day.

CANADIAN JUDGE APPROVES PRIVATE TERMINALS

A British Columbia judge has found an apartment-house manager "not guilty" of accusations that he operated a private satellite dish to provide video programming to tenants. The decision is seen as a victory for backyard satellite-receiver users in Canada, where the federal government has been trying to crack down on use of such private terminals. The ruling, however did not resolve the question of reception of video transmissions via satellite from across the border.

Meanwhile, prosecutors in other Canadian provinces are continuing their cases against other private-terminal owners—both commercial operators (such as the apartment-house manager) and personal users. The Canadian Radio-Television Commission requires earth-station operators to have a technical certificate and a broadcast license.

R-E

PERFORMANCE BEYOND PRICE



Just what you expect from Data Precision.

A Better Way to Get A Better Meter.

If you've been holding off getting a digital meter until the right deal came along, it's here!

Data Precision is offering better-than-ever prices on its most popular high-performance hand-held 3½ digit meters. It's the ideal time to get rid of finicky, hard-to-read analog meters—or even digital meters that have seen better days.

No matter what you measure, now's the time to upgrade your bench. With Data Precision.

3½ DMMs

Model 936: ~~\$165~~ \$145 with coupon

Model 935: ~~\$155~~ \$135 with coupon

Get 29 ranges with all the functions, with 0.1% basic accuracy, protection up to 6kV spikes and hi/lo ohms excitation. All in a one-hand case toughened for the field, yet accurate enough for most bench needs.

Both models read 100µV-1000VDC, 100µV-700VAC; 1µA-2A AC or DC; and 100mΩ-20MΩ.

The 936 also features audible continuity beep and overvoltage alarm, for faster "eyes-off" testing.

CAPACITANCE METER

Model 938: ~~\$219~~ \$199 with coupon

Measure from 0.1pF to 2000µF with 3½ digit 0.1% accuracy. This surprisingly economical meter offers immediate direct reading, and simple pushbutton operation, outperforming capacitance meters, DC time constant meters, and even bridges costing 2 to 5 times as much.

TEMPERATURE METER

Model 940: ~~\$195~~ \$175 with coupon

You can read -65°C (-85°F) to 150°C (302°F), with 0.1° resolution below 200°. You also get a detachable 6" semiconductor probe with 4' cable. The 940 offers an extremely short settling time, and main-

tains 0.4°C (0.7°F) accuracy.

Every one of these high-performing LCD meters operates up to 200 hours on a standard 9V transistor battery, and is warranteed for 2 full years.

We want you to discover Data Precision quality, so from now through March 31 we are offering a \$20.00 saving when you present this coupon to one of our distributors.

Visit your local Data Precision distributor. Or call toll free

(800) 343-8150 or (800) 892-0528

in Massachusetts for the name of the distributor nearest you.

Save \$20.00 on a Data Precision 935-6 DMM, Capacitance Meter or Temperature Meter (any quantity)

\$20

Name _____

Address _____

\$20

Offer expires March 31, 1982.

Data Precision Division of Analogic Corporation.

Prices USA

DATA PRECISION
DIVISION OF ANALOGIC CORPORATION

Data Precision, Division of Analogic Corporation, Electronics Avenue, Danvers, MA 01923, (617) 246-1600, TELEX (0650) 921819
CIRCLE 17 FOR DEMONSTRATION CIRCLE 83 FOR ADDITIONAL INFORMATION



Two ways to find replace

When you think about the number of new electronic gizmos that come off the boat every year, it's staggering.

If you happen to be a repairman, it's enough to drive you crazy. It seems there's absolutely no way for you to keep on top of all those new electronic components required.

But don't worry. There's a very easy way to keep up. Get a Sylvania ECG®

CIRCLE 16 ON FREE INFORMATION CARD



Parts for foreign parts.

Replacement Guide from your ECG distributor. It contains references more than 170,000 part numbers to over 2,500 devices including most of the domestic and foreign parts. It features concise descriptions on each part, clear illustrations of packaging and wiring diagrams. And, you have the full technical resources of Philips at your

disposal for any tricky replacements you might have questions about.

What's more, the ECG parts you receive are of the highest quality. Specifications on these devices are equal to, and usually exceed, those of the original part. To maintain quality and performance levels, all of the ECG's are checked in accord with military standard testing procedures.

But the best part is that you don't have to go every which way to get them. You just go to your nearest ECG distributor.

Philips ECG

A North American Philips Company

CIRCLE 16 ON FREE INFORMATION CARD

ALBIA Electronics COMPLETE ELECTRONIC WORKSHOP CATALOG

SEND
TODAY!

LP-3 LOGIC
PROBE

PROBE

64 PAGES
OF ELECTRONIC
BARGAINS!

FREE 1982 SUPPLY CATALOG

YOUR FREE

DLBI²

Electronics

Complete Electronics Supply Catalog

FOR ADDITIONAL COPIES, CIRCLE READER SERVICE NUMBER 13

...A BOOK FULL OF EXCITING PRODUCTS!

THE COMPLETE ELECTRONIC WORKSHOP REFERENCE

- Capacitor Kit
- C-Kit
- Space-Saving Storage Cabinets
- Pressure Hunter Metal Detector
- New Beckman HD100 Multi-Meter
- Beckman Hand-Held Meters
- Tool Kits
- M-3 Logic Monitor
- Resistor Kit
- Triple Regulated P.C. Board
- DM-13 Resistor Substitution Box Kit
- Mitschi 50 MHz Scope
- Mitschi 100 MHz Scope
- DM-11 Frequency Meter Module
- Low Ohm Meter Module
- Channel Scope Multiplexer
- Capacitance Meter Module
- 10 MHz Frequency Counter
- DM-5A Circuit Designers
- Power Supply Adapter
- Simple Power Supply Bargain
- Inclination Generator
- Phase Generator
- Hard Solderless Breadboards
- M-2 Logic Monitors
- Box & Accessories
- Oscilloscopes
- Universal Counter Timer
- Monitor & G.T. Sockets & Bus Strips
- 10 MHz Frequency Counter
- Inclination Generator
- Phase Generator
- Frequency Standard
- Digital Capacitance Meter
- Hand-Held Frequency Counter
- Strip IC Test Clips
- Wire Jumper Kit
- Print Cases & Hardware
- PB-203AK & PB-203A Powered Protobreadboards
- P-2 Logic Probes
- DM-9 Probes
- Logic Pulser
- LTC-2 Logic Analysis Test Kits
- Accessories
- 10 MHz Scope
- 10 Hz 3 Scope
- Variable Transistor Tester
- Impedance Meter
- Inclination Generator
- Generators
- Dot Matrix Computer Printers
- IC-211 Pocket Computer
- Printer/Cassette Interface
- Digital Thermometer
- Technical Library Selections
- Frequency Counter Kit
- DM-1, DM-1A-1, Hardware Posts & Quick Hooks



SEND FOR YOUR COPY TODAY!!

EQUIPMENT REPORTS

MXR Model 156 CX Decoder



CIRCLE 101 ON FREE INFORMATION CARD

MXR	156									
OVERALL PRICE	[Bar chart showing 10/10]									
EASE OF USE	[Bar chart showing 8/10]									
INSTRUCTION MANUAL	[Bar chart showing 10/10]									
PRICE/VALUE	[Bar chart showing 10/10]									
	1	2	3	4	5	6	7	8	9	10
	Poor			Fair			Good			Excellent

MXR INNOVATIONS, INC. (740 DRIVING Park Avenue, Rochester, NY 14613) offers an interesting line of audio accessories. Their latest one is a CX decoder, the *model 156*.

As you must be aware by now, CX is a compatible companding system for CX-encoded records. Without a decoder, the records sound normal. With a decoder, they attain a dynamic range of about 85 dB, with the extension being at the "quiet" end. That means that the noise floor drops by 20 dB, resulting in virtually noise-free playback and a much more natural-sounding reproduction of the recorded material.

My first experience with the *model 156* decoder was uncanny. I cued the turntable arm, stepped back, and waited for the music to begin. Nothing happened. Thinking that maybe I had switched my speakers off, I went up to check them. As I was looking, the music began. There'd been no noise when the stylus contacted the record, and no noise from the lead-in groove. Nothing!

And the quality of the sound! Loud passages were, of course, loud—CX doesn't concern itself with headroom. What was amazing was that during quiet passages, I could hear things that I would otherwise have missed because of record surface-noise. And, between cuts, there was nothing to indicate that

a record was on the turntable—just dead silence. It was like being present at a performance in a hushed room. The only thing you heard was what you were *supposed* to hear, and then, you heard it all. It's something that has to be experienced to be believed.

About the time you read this, CBS is expected to have about 50 CX-encoded records on the market, and a number of other recording companies have signed agreements with CBS to also use the CX companding system.

The MXR decoder

The *model 156* is extremely simple to connect and use. Two sets of audio cables connect it to the tape-recorder loop of your preamp or receiver; it obtains its power from a 117-volt power line. (My early-model decoder did not have provisions for restoring the use of the jacks that it occupied; MXR tells me that this will be remedied in later models. In any event, the fact is that the decoder can be placed just about anywhere in the loop with other equipment, thus still allowing your sound system full flexibility.)

All the controls are located on the small unit's front panel (the jacks are on the rear apron). A 7-inch calibration record is included with the decoder, and calibration is simply a matter of playing the record and adjusting the REFERENCE LEVEL control until neither one of the two LED's mounted in the front panel is on. That's all there is to it. The adjustment isn't even critical—an error of as much as 6 dB will not be noticeable.

After the unit has been calibrated, nothing has to be adjusted until a different phono cartridge or amplifier is brought into the system.

Aside from the REFERENCE LEVEL control, there are only two others—one for DISPLAY that brings the LED's into the circuit, and one to switch the decoder into or out of the system. There's no power switch—the device draws only 2.4 watts when in use and the assumption is made that it will probably be connected to a switched outlet on your equipment, anyway.

The frequency response of the decoder is given as 20 Hz-20 kHz, +0, -0.5 dB. THD is less than 0.09% over that range, with 0.05% typical at 1 kHz.

Total dynamic range available is specified as 100 dB.

The manual, while short, explains everything you'll need to set up and use the decoder.

One word of caution: The decoder works *only* for CX-encoded records. If a CX-encoded record is recorded on tape and played back through the decoder, only the characteristics of the material on *that record* will be modified; any tape hiss that was present before will still be there.

Finally, while CX records are on the shelves, they may be hard to locate—the fact that a recording is CX-encoded is shown on the *back* of the jacket, not

the front. (That may be due to the fact that, since the records can also be played on ordinary equipment without a decoder, the record companies don't want to scare away record buyers who don't know about the system and don't have special equipment.) Once CX gets a foot in the door, though, the CX logo will probably move to the front, where it can easily be seen.

The MXR *model 156* decoder is a good example of how simple it is to improve the pleasure you can get from a good recording. It has a suggested list price of \$99.95...and don't forget to watch for the CX logos on the back of the record jackets.

R-E

Get **MORE** in capacitor types and ratings at a Sprague Q-LINE™ Distributor

No matter what type of capacitor you're looking for, look for it on a Q-MART® capacitor display. You'll find exactly what you want. That's because the Sprague Q-LINE features a computer-selected inventory of most-frequently-used capacitors. And blister-pak packaging keeps the capacitors clearly visible and fully protected.

Q-MART

ALUMINUM LYTIC TANTALUM LYTIC Q-LINE CAPACITORS FILM CERAMIC

6 MAJOR TYPES OF CAPACITORS STOCKED IN HUNDREDS OF RATINGS.

A complete self-service capacitor center . . . axial-lead and vertical-mounting electrolytics, solid tantalums, general-application ceramics, single-ended films, and epoxy-dipped micas.

For detailed information on all Q-LINE products (capacitors, switches, chassis boxes, optoelectronic devices, DIP/SIP components, resistors, wiring components, etc.) write for 40-page Catalog C-652 to Sprague Products Co., Distributors' Division of the Sprague Electric Co., 509 Marshall St., North Adams, Mass. 01247.

Where **MORE** is more than a promise.



CIRCLE 20 ON FREE INFORMATION CARD

Sabtronics Model 8610A 600-MHz Frequency Counter



CIRCLE 102 ON FREE INFORMATION CARD

Sabtronics	8610A									
OVERALL PRICE	[Progressive bar chart]									
EASE OF USE	[Progressive bar chart]									
INSTRUCTION MANUAL	[Progressive bar chart]									
PRICE/VALUE	[Progressive bar chart]									
	1	2	3	4	5	6	7	8	9	10
	Poor			Fair			Good			Excellent

FOR ANYONE—WHETHER HE'S A TECHNICIAN, ham, or designer—who has to measure signal-frequencies, a frequency counter is a necessity. For a long time I tried getting along without one. I'd borrow one from friends or, more usually, take the equipment to be checked out—usually an amateur radio handie-talkie or a piece of digital equipment I'd put together—to someone who had a counter.

Eventually that became too much. The stuff I was building was getting too awkward to carry, and frequently required more than a simple yes-or-no frequency check. So, I finally broke down and purchased a counter of my own.

My choice was the Sabtronics *model 8610A* 600-MHz counter. Although it has a smaller brother (the *model 8110A*, good to 100 MHz) and a bigger one (the *model 8000B*, that goes up to 1 gigahertz), the 600-MHz version offered just what I needed, with a little bit to spare.

It covers all the radio bands I use and has a low-frequency limit of 20 Hz: some of my projects involve audio frequencies and the *model 8610A* is ideal for that end of the spectrum, too.

Putting it together

The counter is available either as a kit or assembled. Naturally, I chose the kit form. I was very pleasantly surprised with the quality of the components—and of the manual—that came with the kit. The main PC board is silk-screened and solder masked. The 600-MHz pre-scaler board is not, but very clear diagrams make it difficult to go wrong.

The construction manual is excellent. There are plenty of diagrams and (literally) step-by-step instructions with

continued on page 32

“You fix TV’s... what brand should I get?”

You’re on the spot. Any set you tell your customer about has a chance of failing sometime.

But though we’re not saying we’re perfect, we’d like you to recommend RCA. Because we’re sure your customer will love its picture performance.

You can find the problem and repair it quickly if anything does go wrong. Because with RCA’s unitized chassis, failures are easy to handle.

RCA gives frequent hands-on workshops, as well as lectures. So when failures do occur, you’ll be ready.

RCA has more than 500 parts distributors nationwide. We have this large network because we don’t want you to have to wait too long for parts.

We also keep your inventory expenses lower by using components instead of modules, in most circuits.

We know your customers think you’re responsible for everything about their sets.

Good and bad.

And that’s why we here at RCA are doing everything possible to make sure that when you finish a service call, everybody’s smiling. Your customer’s happy with your recommendation. And you’re still the expert.

RCA

**RCA IS MAKING
TELEVISION
BETTER AND BETTER.**



For your free subscription to RCA COMMUNICATOR, our magazine of news and advice for service technicians, write RCA, Dept. 1-455, 600 North Sherman Drive, Indianapolis, IN 46201.

EQUIPMENT REPORTS

continued from page 30

a space for you to make a mark indicating that you've successfully completed that step.

There are also a number of construction hints along the way, at places where a novice builder might find himself wondering exactly what he was supposed to do. There's even an introductory section on how to make good solder connections. The manual includes a table showing what readings should be obtained with different switch settings and, finally, provides troubleshooting hints. Sabtronics leaves nothing to chance!

Calibration of the unit is easy. An internal SENSITIVITY control is adjusted using a voltmeter, and a small variable capacitor trimmed to bring the counter right on frequency. That calibration can be performed in two ways. The first is conventional—input a 10-MHz signal from a known-to-be accurate source. The second method requires a short-wave receiver, but is just about as accurate. A receiver tuned to WWV at 10 MHz is used as a standard, and the counter, placed close to the receiver, adjusted to read the same frequency. The accuracy of the receiver isn't criti-

cal—when the National Bureau of Standards says it's transmitting on 10 MHz, who's to doubt it?

Construction went quickly, and the unit worked the first time it was turned on.

Features

The *model 8610A* has an 8-digit LED display. The decimal point, which adjusts its position automatically, also serves to indicate the gate time: 0.1, 1, or 10 seconds, by flashing at that rate. There is also an overflow indicator on the display to indicate an out-of-range condition.

Three switches on the front panel select frequency range, gate time, and turn the counter on and off. A single BNC connector is used for input. Power is supplied either by four "C"-type nickel-cadmium rechargeable cells (optional) or from a power supply/charger, also available as an option. The counter can be used while the batteries are being charged.

Earlier, I mentioned a low-frequency limit of 20 Hz. I should clarify that by stating that the *guaranteed* operating range is 20 Hz-600 MHz. Typical operating range, though, is specified as being from 10 Hz to 750 MHz. Resolution is claimed to be 0.1 Hz up to 10 MHz, 1.0 Hz to 100 MHz, and 10 Hz to 600 MHz.

The counter features input protection—from 150-volts RMS up to 10 MHz to 4-volts RMS above 100 MHz. Its sensitivity is 10-mV RMS up to 100 MHz, 70-mV RMS up to 450 MHz, and 150-mV RMS to 600 MHz.


The unit uses a temperature-controlled crystal oscillator and, while there is some drift—under 200 Hz during the first few minutes of operation—the counter is essentially rock-stable after less than half an hour. Temperature stability is given as 0.1 ppm (Parts Per Million) per °C, with an aging rate of less than 5 ppm per year. According to the specifications, setability is claimed to be ± 2 ppm: I found it even better.

The counter measures $8 \times 6.5 \times 3$ inches and weighs 1.2 pounds without batteries. A bail is provided to tilt the unit up for better visibility. There's quite a lot of empty space in the enclosure, which leads me to wonder what other items Sabtronics has in mind to put in there.

I feel that the *model 8610A* frequency counter is one of the best equipment choices I could have made for my bench. It's available from Sabtronics International, Inc., 3709 N. 50th Street, Tampa, FL 33610 for \$119.00 in kit form and \$149.00 assembled, plus \$5.00 for shipping and handling.

R-E

continued on page 34

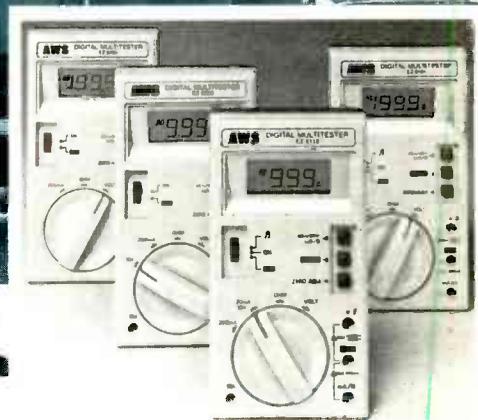

"Fast and accurate readings. That's why we use the AWS EZ-Meter™ DMMs."

Bob Murray, ITS Equipment & Leasing Corp

"At ITS, we maintain and service hundreds of pieces of computer equipment used by over 200 airline companies throughout the world. If even one piece of equipment goes down, serious back-up problems can occur. So our job is not only to make the proper repairs, but to make them fast. That's why we use the AWS EZ-Meter series of Digital Multi-Meters. With their Autoranging feature (volts & ohms) we can count on quick, accurate readings hundreds of times a day—both on the bench and in the field. And with their Five-Year warranty, we think they're the best hand-held DMMs you can buy."

Other outstanding features include:

- Autoranging and full manual mode (Models EZ-6100 & 6110)
- Audible continuity tone with 5 settings (Models EZ-6100 & 6110)
- Nominal DC volt accuracy 0.5% of reading (Models EZ-6100 & 6110)
- Zero adjust feather-touch button
- Low and normal power Ohm ranges
- 300 hours minimum continuous operation with two 1.5V "AA" batteries
- 3½ digit LCD indicates the function, reading and feature simultaneously
- Exclusive FIVE-YEAR Warranty!

CIRCLE 21 ON FREE INFORMATION CARD

For more information on the EZ-Meter series or any of the other fine AWS instruments call your local distributor or contact A.W. Sperry Instruments Inc., 245 Marcus Blvd., Hauppauge, N.Y. 11788 • 800-645-5398 Toll-Free (N.Y., Hawaii Alaska call collect 516-231-7050).

A.W. SPERRY INSTRUMENTS INC.

The Measurable Advantage.

If you can beat these prices, you must have a brother-in-law in the business.

16 K RAM KITS

13.95

Set of 8 NEC 4116 200 ns
GUARANTEED ONE FULL YEAR.

DISKETTES

ALPHA DISKS® 21.95

SINGLE SIDED, CERT DOUBLE DENSITY
40 TRACKS, WITH HUB-RING, BOX OF 10,
GUARANTEED ONE FULL YEAR.

VERBATIM DATALIFE

MD 525-01, 10, 16	26.50
MD 550-01, 10, 16	44.50
MD 577-01, 10, 16	34.80
MD 577-01, 10, 16	45.60
FD 32 OR 34-9000	36.00
FD 32 OR 34-8000	45.60
FD 34-4001	48.60

PRINTERS

ANADEX DP 9500	1295.00
ANADEX DP 9501	1295.00
CENTRONICS 739	765.00
C-I TOH 25 CPS PARALLEL	1440.00
C-I TOH 25 CPS SERIAL	1495.00
C-I TOH 45 CPS PARALLEL	1770.00
C-I TOH 40 CPS SERIAL	1870.00
C-I TOH TRACTOR OPTION	195.00
EPSON MX-80	\$CALL
EPSON MX-80 F/T	\$CALL
EPSON MX-100 GRAPHIC	\$CALL
EPSON GRAPHICS ROM	90.00
IDS-445G PAPER TIGER	779.00
IDS-460G PAPER TIGER	945.00
IDS-560G PAPER TIGER	1195.00
NEC SPINWRITER 3510 Ser.RO	2195.00
NEC SPINWRITER 3530 Par.RO	2195.00
NEC SPINWRITER 7710 Ser.RO	2645.00
NEC SPINWRITER 7730 Par.RO	2645.00
NEC SPINWRITER 7700 D Sellum	2795.00
NEC SPINWRITER 3500 Sellum	2295.00
OKIDATA MICROLINE 80	389.00
OKIDATA MICROLINE 82A	549.00
OKIDATA MICROLINE 83A	849.00
OKIDATA MICROLINE 84	1199.00
QUME 9/45	2149.00
MALIBU 200 DUAL MODE	2695.00

APPLE GAME SOFTWARE

POOL 1.5	29.95
ALIEN RAIN (AKA GALAXIAN)	20.95
SNOGGLE (REQ. JOYSTICK)	27.95
RASTER BLASTER	24.95
APPLE PANIC	24.95

APPLE SOFTWARE

MAGIC WINDOW Word Processor	89.00
MAGIC WAND	275.00
WORDSTAR	259.00
MAIL MERGE(Req. WORDSTAR)	90.00
SPELLSTAR(Req. WORDSTAR)	169.00
DATASTAR	199.00
EXPEDITER II Applesoft Compiler	89.00
PFS: PERSONAL FILING SYSTEM	79.00
PFS: REPORT GENERATOR	79.00
ASCII EXPRESS Terminal Program	59.95
Z-TERM CP/M* Comm. Software	89.95
MICROSOFT FORTRAN	165.00
MICROSOFT COBOL	550.00
DB MASTER 3.0	179.00
VISICALC 3.3	169.00
VISILOT	149.00
VISIDEX	159.00
CCA DATA BASE MANAGER	99.00
A-STAT COMP. STATISTICS PKG.	119.00

MODEMS

NOVATION CAT ACOUSTIC MODEM	145.00
NOVATION D-CAT Direct Connect	165.00
NOVATION AUTO-CAT AUTO ANS.	219.00
NOVATION APPLE-CAT	349.00
UDS 103 LP DIRECT CONNECT	175.00
UDS 103 JLP AUTO ANSWER	209.00
D.C. HAYES MICROMODEM II(Apple)	299.00
D.C. HAYES 100 MODEM(S-100)	325.00
D.C. HAYES Smart Modem(RS 232)	249.00
LEXICON LX-11 MODEM	109.00

APPLE HARDWARE

VERSA WRITER DIGITIZER	249.00
ABT APPLE KEYPAD	119.00
MICROSOFT Z-80 SOFTCARD	299.00
MICROSOFT RAMCARD	159.00
VIDEX 80 x 24 VIDEO CARD	299.00
VIDEX KEYBOARD ENHANCER	99.00
M&R SUPERTERM 80 x 24 Video Bd.	315.00
NEC 12" GREEN MONITOR	199.00
SANYO 12" MONITOR(B&W)	249.00
SANYO 12" MONITOR(Green)	269.00
SANYO 13" COLOR MONITOR	469.00
SSM AIO BOARD (INTERFACE)A&T	165.00
SSM AIO BOARD (INTERFACE)KIT	135.00
ZENITH 13" HI-RES. Green MON.	139.00

CP/M SOFTWARE

MICROSOFT BASIC-80	299.00
MICROSOFT BASIC COMPILER	319.00
MICROSOFT FORTRAN-80	369.00
PEACHTREE SYSTEMS	CALL
MAGIC WAND(Requires CP/M®)	275.00
WORDSTAR(Requires CP/M®)	325.00
MAILMERGE(Requires WORDSTAR)	110.00
SPELLSTAR(Requires WORDSTAR)	199.00
CALCSTAR	239.00
DATASTAR	249.00
SPELLGUARD	239.00

CP/M is a registered trademark of Digital Research.

We built a reputation on our prices and your satisfaction.

Alpha Byte STORES (213) 706-0333

We guarantee everything we sell for 30 days. If anything is wrong, just return the item and we'll make it right. And, of course, we'll pay the shipping charges.

We accept Visa and Master Card on all orders. COD orders accepted up to \$300.00.

Please add \$2.00 for standard UPS shipping and handling on orders under 50 pounds, delivered in the continental U.S. Call us for shipping charges on items that weigh more than 50 pounds. Foreign, FPO and APO orders please add 15% for shipping. California residents add 6% sales tax.

The prices quoted are only valid for stock on hand and all prices are subject to change without notice.

31245 LA BAYA DRIVE, WESTLAKE VILLAGE, CALIFORNIA 91362

CIRCLE 10 ON FREE INFORMATION CARD

NEW 23 K PERSONAL COMPUTER

\$239

SPECIAL FACTORY SALE PRICE!!

You get this new APF IM-1 full size, extra featured Computer: Includes a powerful 6800 Motorola Microprocessor, 14,000 Bytes ROM with a simplified LEVEL 11 BASIC built in, 9,000 Bytes user RAM, Color, Sound, Full 53 professional keyboard. Two 10 key numeric pads, two controllers, high speed built in cassette that operates at 1200 baud, loads and reads 4 times faster than other computers. Has built in speaker with volume control, microphone jack, and 3-digit counter, high resolution graphics 256x192 (LIKE APPLE). Test display is 16 lines, 32 characters. It has 8 colors, will accept TAPE-DISK or PLUG IN CARTRIDGES. Includes owners manual and BASIC language book, 90 days parts and labor warranty, UL listed, FCC approved. All this in a beautiful black and white CONSOLE CASE. Weighs 20 pounds, list price \$599.95.

15 DAY FREE TRIAL Return within 15 days complete and undamaged for refund of purchase price.

DON'T MISS THIS FANTASTIC SALE!! Phone 312/382-5244 to order and get delivery in 7 days, or send a certified check, money order or personal check to **PROTECTO ENTERPRISES, BOX 550, BARRINGTON, ILLINOIS 60010**. We honor Visa and Master Charge, Ship C.O.D. Add \$15.00 for shipping, handling and insurance. Illinois residents add 6% tax.

CIRCLE 27 ON FREE INFORMATION CARD



You know the problem. Station fading...picket fencing...generally poor and frustrating FM car radio reception in the country and suburbs. We've ended all that with our great little space-age Stereo Expander devices. Hooked up between the radio and the broadcast antenna, they create a tremendous boost in sensitivity—over 15 dB—bringing in far-away FM stations sharp and clear. Simple, effective. Model ASC-100 hides completely out of sight; Model ASC-100DX mounts neatly anywhere underdash, has an off switch when the boost isn't needed.

the antenna specialists co.  a member of The Allen Group Inc.


© "Stripes of Quality"
12435 Euclid Avenue, Cleveland, OH 44106
International Div., 2200 Shames Dr.
Westbury, L.I., New York 11590
Canada: A. C. Simmonds & Sons, Ltd.

CIRCLE 28 ON FREE INFORMATION CARD

EQUIPMENT REPORTS

continued from page 32

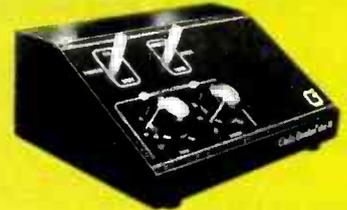Grove Enterprises Model DSC-2 Code Breaker



CIRCLE 103 ON FREE INFORMATION CARD

Grove	DSC-2									
OVERALL PRICE	[Bar chart showing 8 bars]									
EASE OF USE	[Bar chart showing 8 bars]									
INSTRUCTION MANUAL	[Bar chart showing 8 bars]									
PRICE/VALUE	[Bar chart showing 8 bars]									
	1	2	3	4	5	6	7	8	9	10
	Poor			Fair			Good			Excellent

WITH THE CASUAL MONITORING OF VHF/UHF frequencies at an all-time high, it is not surprising that many law-enforcement agencies, among others, are concerned with the privacy of their communications. While many of those agencies prefer to use a simple "10" code, or a variation of it, still others prefer the additional protection of a voice privacy system.

There are many ways to garble a voice transmission including speech inversion, rolling code, spread spectrum, frequency hopping, and voice digitizing. The new model DSC-2 from Grove Enterprises restores intelligibility to speech-inverted communications.

In speech inversion, high voice-frequencies and low voice-frequencies are transposed by the mixing action of a local audio-oscillator. A descrambler simply takes the inverted speech and restores it by passing it through a circuit that is identical to the one that originally scrambled it. That is what this unit does.

Since an agency that wishes to scramble its transmissions can choose any oscillator frequency it wants, the unit has a control to "fine tune" the restored speech. Often, a speech-inverted signal will also have an audio tone superimposed over it for increased security. That technique, called tone masking, reduces the intelligibility of even restored speech. The Code Breaker has a tunable audio notch-filter to re-

move such an audio tone, leaving the restored speech out in the clear. The unit can also be used with shortwave receivers to remove heterodyne interference that is often heard on broadcast transmissions as well as when monitoring single-sideband and CW signals.

The unit requires 12-volts DC for operation. There is an optional power supply available from the manufacturer, or you can use any mobile power supply. The power jack is of the recessed coaxial variety, eliminating the possibility of a short circuit while plugging in the power supply. There is also an internal diode that is used to prevent damage if the power-supply connections are accidentally reversed. Although designed for 12-volt operation, in our tests (more on that later) we noticed that the unit operated at power inputs ranging from 8 to 16 volts without any noticeable degradation of the audio signal. Incidentally, all of the required interconnection cables are included with the unit.

The unit has an internal speaker. If you wish, an external speaker, ear-phones, or a recording device can be connected using the rear-panel-mounted external speaker jack. Other rear-panel jacks allow you to connect up to two receivers to the descrambler.

Our test

The notch-filter control allowed for considerable rejection (up to 60 dB at midrange) over the 800-3000-Hz frequency range. Tuning was sharp, permitting the removal of distracting tones without destroying the audio character of the speech. Incidentally, the audio quality of the speaker seemed quite good; that may be because the rugged metal cabinet provides a favorable acoustical housing. The local oscillator for the speech descrambler was tunable from 2600 to 4000 Hz, defeating all types of single-inversion speech-scrambling systems.

Quiescent current during idle (no input driving the unit) was measured at 55 mA. The current increased to approximately 200 mA during high-level audio transients. Since the audio circuitry is designed around a 2.5-watt LM380N, no appreciable heating or distortion was evident.

At normal volume levels, a 2N3904 twin-T oscillator injects a sine-wave tone into a Motorola MC1496P balanced-mixer IC. The output is passed through the notch filter to the audio stage. Signals can be processed by the audio filter even when the unit is not in the descramble mode, allowing for greater flexibility.

The decoder sells for \$97.95, plus \$2.25 shipping, with the AC adaptor: \$89.95, plus \$2.25 shipping, without. It is available from Grove Enterprises, Brasstown, NC 28902. R-E

RCA's New See-and-Do VCR Video Tape Training Program . . .

"Familiarization and Servicing the VFT190 Video Cassette Recorder"




- Video Tape . . .
60-Minutes
Full Color
- Workshop Manual . . .
Fully Illustrated
Servicing Procedures
- Training Workbook . . .
Reinforces Your Learning
With "Hands-On" Exercises

The 60-minute full-color Technical Training Video Tape (VHS Format) will prove to be invaluable for technician training or for use at the bench when the VFT190 is being serviced. Includes specific visual instruction with audio narration on Microprocessor System Control Operation and Servicing, Servos, and Signal Processing.

The most vital circuit areas are referenced to the VCR counter number so the technician can proceed directly to the related subject matter on the tape.

Complete Package Only \$125.00

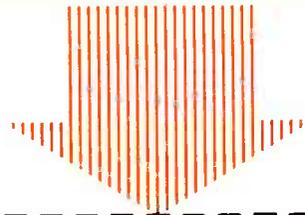

Yes!

RCA



Send the number of tapes I have indicated to address below:

Enclosed is my check or money order payable to RCA Corp.

Quantity _____ @ \$125.00 Each

\$ _____ Total Enclosed

Allow 4-6 Weeks Delivery

THIS IS YOUR SHIPPING LABEL — PLEASE PRINT

NAME _____

STREET ADDRESS _____

CITY _____ STATE _____ ZIP _____

**MAIL TO: RCA Technical Training 1-450
600 N. Sherman Drive, Indianapolis, IN 46201**

8205RE

EQUIPMENT AND TRAINING NO OTHER SCHOOL CAN MATCH.

**NTS HOME TRAINING INVITES YOU TO EXPLORE MICROCOMPUTERS,
DIGITAL SYSTEMS AND MORE, WITH STATE-OF-THE-ART EQUIPMENT
YOU ASSEMBLE AND KEEP.**

Without question, microcomputers are the state of the art in electronics. And NTS is the only home study school that enables you to train for this booming field by working with your own production-model microcomputer.

We'll explain the principles of troubleshooting and testing your microcomputer and, best of all, we'll show you how to program it to do what you want.

You'll use a digital multimeter, a digital logic probe and other sophisticated testing gear to learn how to localize problems and solve them.

Send for the full color catalog in the electronics area of your choice—discover *all* the advantages of home study with NTS!

NTS also offers courses in Auto Mechanics, Air Conditioning and Home Appliances. Check card for more information.




We believe that training on production-model equipment, rather than home-made learning devices, makes home study more exciting and relevant. That's why you'll find such gear in most of NTS's electronics programs.

For instance, to learn Color TV Servicing you'll build and keep the 25-inch (diagonal) NTS/HEATH digital color TV.

In Communications Electronics you'll be able to assemble and keep your own NTS/HEATH 2-meter FM transceiver, plus test equipment.

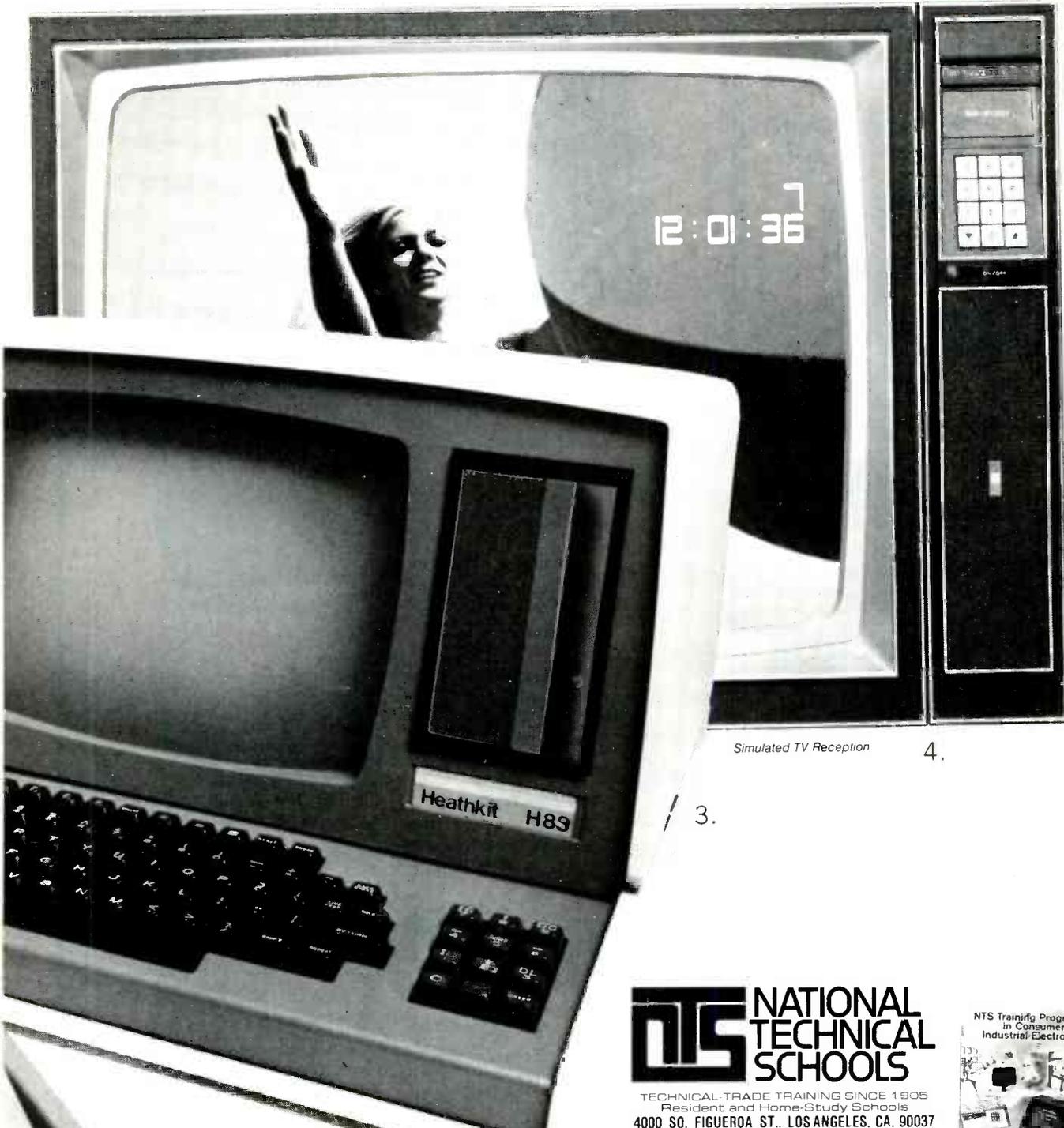But no matter which program you choose, NTS's Project Method of instruction helps you quickly to acquire practical know-how.



Simulated TV Reception

4.

3.

1. **The NTS/Rockwell AIM 65 Microcomputer** A single board unit with on-board 20 column alphanumeric printer and 20 character display. A 6502-based unit 4K RAM, expandable.
2. **The NTS/KIM-1 Microcomputer** A single board unit with 6 digit LED display and on-board 24 key hexadecimal calculator-type keyboard. A 6502 based microcomputer with 1K RAM, expandable.
3. **The NTS/HEATH H-89 Microcomputer** features floppy disk storage, "smart" video terminal, two Z80 micro-processors, 16K RAM memory, expandable to 48K.
4. **The NTS/HEATH GR-2001 Digital Color TV** (25" diagonal) features specialized AGC-SYNC muting, filtered color and new solid-state high voltage tripler rectifier.

NTS NATIONAL TECHNICAL SCHOOLS

TECHNICAL TRADE TRAINING SINCE 1905
Resident and Home-Study Schools
4000 SO. FIGUEROA ST., LOS ANGELES, CA. 90037

NTS Training Programs
in Consumer and
Industrial Electronics



NATIONAL TECHNICAL SCHOOLS

4000 South Figueroa Street,
Los Angeles, California 90037 Dept. 205-022

Please rush FREE: color catalog on course checked below

- | | |
|---|---|
| <input type="checkbox"/> MicroComputers/MicroProcessors | <input type="checkbox"/> Auto Mechanics |
| <input type="checkbox"/> Communications Electronics | <input type="checkbox"/> Air Conditioning |
| <input type="checkbox"/> Digital Electronics | <input type="checkbox"/> Home Appliances |
| <input type="checkbox"/> Industrial Technology | <input type="checkbox"/> Color TV Servicing |

Name _____ Age _____

Address _____

Apt. _____ City _____

State _____ Zip _____

- Check if interested in G.I. information.
 Check if interested ONLY in classroom training in Los Angeles.

» FEBRUARY SPECIAL «

BK PRECISION

New Portable Digital Capacitance Meter



MODEL 820
Call For Our Price



KEITHLEY MODEL 130 DIGITAL MULTIMETER

	RANGE	ACCURACY
DC VOLTAGE	200mV, 2V, 20V, 200V, 1000V	.5%
AC VOLTAGE	200mV, 2V, 20V, 200V, 750V	1%
DC CURRENT	2mA, 20mA, 200mA, 2000mA, 10A	2%
AC CURRENT	2mA, 20mA, 200mA, 2000mA, 10A	3%
RESISTANCE	200Ω, 2kΩ, 20kΩ, 200kΩ, 20MΩ	.5%

CALL FOR OUR PRICE

HITACHI

KEITHLEY



Non-Linear Systems

FLUKE

HICKOK

VIZ formerly RCA

TRIPLETT



PHILIPS

WESTON

Simpson

BK PRECISION

LEADER

DORIC



DATA PRECISION

ADVANCE ELECTRONICS

THE TEST EQUIPMENT SPECIALISTS



TOLL FREE HOT LINE
800-223-0474



54 WEST 45th STREET, NEW YORK, N.Y. 10036
IN NEW YORK STATE 212-687-2224

PORTABLE OSCILLOSCOPES

BATTERY OPERATED



Non-Linear Systems

Call For Our Prices

MS-15



Single Trace 15MHz

MS-215



Dual Trace 15 MHz

MS-230



Dual Trace 30MHz

New Sweep/Function Generator

BK PRECISION

MODEL 3020

- Four instruments in one package—sweep generator, function generator, pulse generator, tone-burst generator.
- Covers 0.02Hz-2MHz
- 1000:1 tuning range
- Low-distortion high-accuracy outputs
- Three-step attenuator plus vernier control
- Internal linear and log sweeps
- Tone-burst output is front-panel or externally programmable



Call For Our Price

- V-151B 15 MHz Single Trace
- V-152B 15 MHz Dual Trace
- V-202 20 MHz Dual Trace
- V-301B 30 MHz Single Trace
- V-302B 30 MHz Dual Trace
- V-352 35 MHz Dual Trace
- V-550B 50 MHz Dual Trace, Dual Time Base
- V-1050 100 MHz Dual Trace, Dual Time Base

Call For Special Intro Price Offer



HITACHI



We carry a full line of multimeters, oscilloscopes, frequency counters, audio and RF generators, power supplies and accessories.

Just call our Toll-Free number and one of our experts will answer all your questions about test equipment.



CAR TELEPHONES Cellular Technology Promises More Channels

DANNY GOODMAN

Long waiting lists for phones and a lack of channels have limited the usefulness of the mobile-telephone system. A sophisticated new system is about to change all of that.

AN EXECUTIVE HEADS FOR HIS CAR parked in a downtown Chicago office-building garage, hoping to make it home to suburban Lake Forest in time to entertain dinner guests. Weighing heavily on his mind are sensitive negotiations taking place in California with which he must be in constant touch during his drive up the expressway.

Still in the garage, he dials the number of his Los Angeles contact on the pushbutton mobile phone, just as he would from his office upstairs. In a couple of seconds the phone in L.A. is ringing, and our busy executive starts his drive. During his hour-long mobile conversation, neither he nor his associate will notice that their full-duplex communications channel will have shifted frequency three times, with the

mobile call going through three separate base-station sites.

The entire process is channelled through one of the most sophisticated land-based communications systems available to the general public, cellular mobile telephone. A cellular mobile-telephone system divides a metropolitan area into a mosaic of small cells, each with its own low-power transmitter, so that the same channel can be used for different conversations in non-adjacent cells. The result is more available channels for mobile-phone customers. To accomplish that, cellular telephone uses a remarkable system of computer-controlled radios that "hand off" a mobile call from one cell to the next as a vehicle travels across town. The hand-off is done so smoothly that

the caller will probably not even notice it.

In a conventional mobile-telephone setup, with a high-power base transmitter covering an entire metropolitan area, our executive would have just a 50% chance of getting an open channel at some time during his hour drive. If he did manage to get on the air, he would be occupying one of the 23 valuable channels in the Chicago area. (There are only 12 such channels in New York City!) But with the cellular system, there is a 99% chance that his call would go through on the first try. And, as he moves from one cell to another, our friend's telephone call shifts to a different channel on that other cell's transmitter/receiver, and the original channel opens up for another caller.

FEBRUARY 1982

Additionally, the cellular system makes portable telephones feasible.

This is not a science fiction dream, but a real system proven in two trials in congested areas: Chicago, sponsored by an AT&T subsidiary called AMPS (Advanced Mobile Phone Service), and Washington, D.C./Baltimore, sponsored by Motorola and operated by American Radio-Telephone Service Incorporated. Because of the success of those tests last year, the FCC, in a preliminary action, allocated two 20-MHz segments of the 800-MHz band for cellular-telephone communications. If final approval is granted (a decision was



FIG. 1—CELL-SITE BUILDING is dwarfed by the 150-foot antenna tower. The two antennas below the platform are used for reception; the antenna above the platform is used for transmission.

expected just after this issue went to press early last December), within two years the first fully operational systems could be in place; the system should be available in 70 cities within 5 or 6 years. When that happens, a cellular network will allow so many more people to have mobile phones in their automobiles and trucks, that the usual waiting list for those phones will all but disappear.

Basic cell systems

A cellular mobile phone system consists of a deceptively simple network of remote duplex transceivers. Cells are connected by landlines (telephone lines) to a central MTSO (Mobile Telecommunications Switching Office). It is at the MTSO that mobile calls are automatically patched into the regular telephone network, without the need for mobile operators.

A typical cell site, like AMPS' Lyons, Illinois site, is little more than a small building (about 20 feet by 20 feet at Lyons) to house the equipment racks, and a 150-foot tower for the antenna system (see Fig. 1). In more urban areas, cell sites can be located on building roofs.

The base station's receiving antennas are two vertical monopoles set up in a diversity reception mode. Two antennas are used in diversity reception so that a moving vehicle can maintain contact with the base station at all times. In that mode, the base-station's receiver is able to choose between the stronger of the two signals coming from the antennas; if a car is temporarily shielded from one antenna, the receiver simply

switches over to the other.

The base station's transmit antenna, which is also a vertical monopole, is capable of handling up to eight transmissions on different frequencies at once. Since line losses at 800 MHz can be incredibly high with conventional cables, all antennas are fed with Heliax gas-filled coaxial cables that are maintained at a constant pressure.

Equipment in the small building is completely automated. One typical site that we visited recently with an AMPS official had two racks of transceivers, each rack with eight channels in operation (see Fig. 2). Small fans on the 45-watt air-cooled amplifiers hummed quietly. Each cell site performs repeated self-testing of its equipment and reports irregularities to a central AMPS office. Only then is a service technician dispatched to a site. In addition, an outside transmitter tests the voice quality of each channel throughout the system by sending a 1-kHz tone and comparing the signal coming through the radios and phone lines to the original. That, too, is automatic, with a central printer logging the results of each test at approximately one-minute intervals.

In the event of power failures at the site, a wet-battery back-up power supply can operate the communications gear for about eight hours. Part of that back-up is also a power inverter to keep the automatic test gear in operation.

Mobile installations

Vehicle installations are quite simple affairs. A one-piece trunk-mounted unit is a combination 800-MHz duplex FM-transceiver and sophisticated logic unit. Installation in most vehicles takes about 4½ to 5 hours, including complete testing. The vehicle's phone number is entered into the radio by way of a PROM chip that is programmed at the installation site. Because of the 45-MHz separation between the transmit and receive frequencies, cellular mobile phones use two 2.5-dB gain antennas at the car: one each for transmit and receive. The antennas are precisely tuned for the proper segment and can be either roof or trunk-lid mounted; roof-mounted antennas are $\frac{5}{8}$ wavelength, while the longer trunk-lid antennas are $\frac{1}{2}$ wavelength center-fed verticals.

Control heads vary somewhat with manufacturer. In the Chicago test, for example, mobile equipment was supplied by Motorola, Oki, and E.F. Johnson. Some heads have a *Touch-Tone* pad and resemble a standard desk phone (see Fig. 3). The deluxe model has a pushbutton pad and digital display built into the modern-looking angular handset.

Costs for cellular phone privileges have not been set, but the rates used in the Chicago test will give you an idea of how much is involved. Mobile equip-

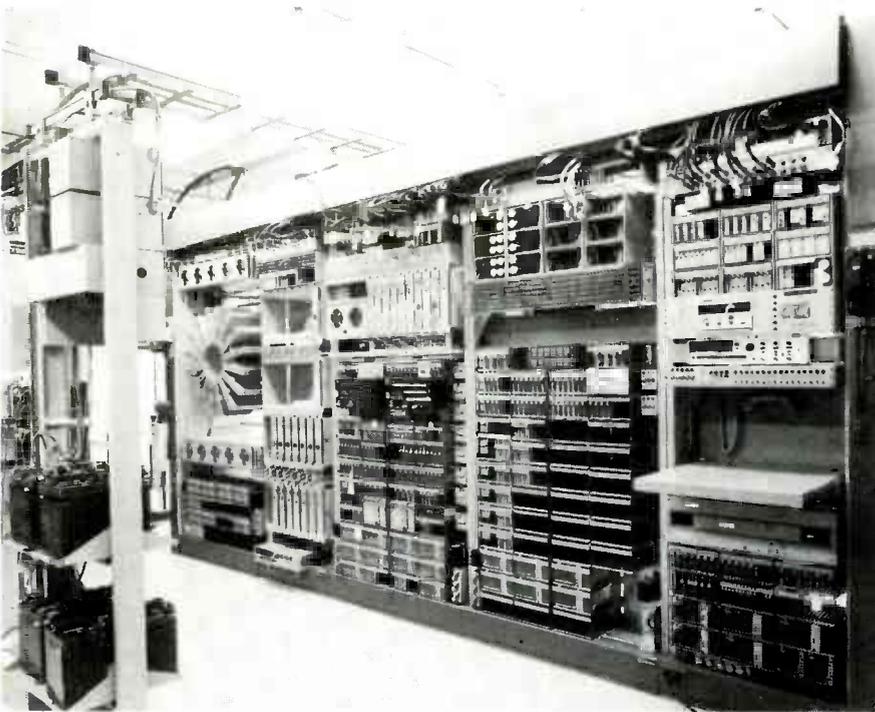


FIG. 2—RACK-MOUNTED TRANSCEIVERS and logic components are totally automated. Self-testing is done by the equipment on the right and the battery back-up system in the foreground is provided in case of a power failure.

ment is leased for \$45-60 per month, depending on control-head style and options. For air time, there is a basic charge of \$25 per month, which includes 120 minutes of air time. Additional minutes are 25 cents each.

The Chicago test divided the 2100-square-mile metropolitan area into ten cells as shown in Fig. 4. While the downtown cell had the smallest geographical area, it also had the highest number of voice channels (26). Mobile units used 10-watt transmitters, but when the operational system is permanently set up, there will be more and smaller cells, allowing the mobile units to communicate comfortably using 3 watts. In the test, cells at opposite ends of the city used the same nine channels.

Growing cells

Cell sites are assigned a number of channels, based on the projected number of calls within that cell. More congested sites, such as the central business district of a major city, will have perhaps three or more times as many channels as an outlying cell. Because the base transmitters run at a low power-level of about 40 watts, the signal does not cover the entire metropolitan area—channels can be used by several cells as long as those cells are far enough apart. Motorola uses a four-cell cluster, while AT&T prefers a seven-cell cluster before reusing a channel.

Moreover, as the number of users increases within a cell, or throughout the system, cells can be subdivided into smaller cells with lower-power transmitters and directional antennas allowing channels to be used even more times within the system. Theoretically, a cell can be as small as one mile in diameter. With the number of channels currently allocated to cellular telephones, a large city with 500 one-mile cells could serve a quarter of a million users!

Typically, a cell will go through three stages to accommodate greater traffic. In the first stage, a transceiver and omnidirectional antenna are centrally located within a cell. The second, or transitional stage, establishes additional cell sites, with directional antennas for some of the channels. The new cell sites will service a more localized area with a lower-power transmitter. More channels are switched over to the new cells until the original cell becomes a final-stage cellular system, consisting of a complete network of directional, low-power cell sites. In practice, the growing system will always be in a transition stage because service needs in any area will always be changing. And since the mobile units are capable of switching to any channel, as instructed by the MTSO, the user will be unaware of any of the changes in cell locations and frequencies.



FIG. 3—HUMP-MOUNTED CONTROL HEAD with handset and Touch-Tone keypad. A deluxe model (not shown here) also has a readout of the last number dialed.

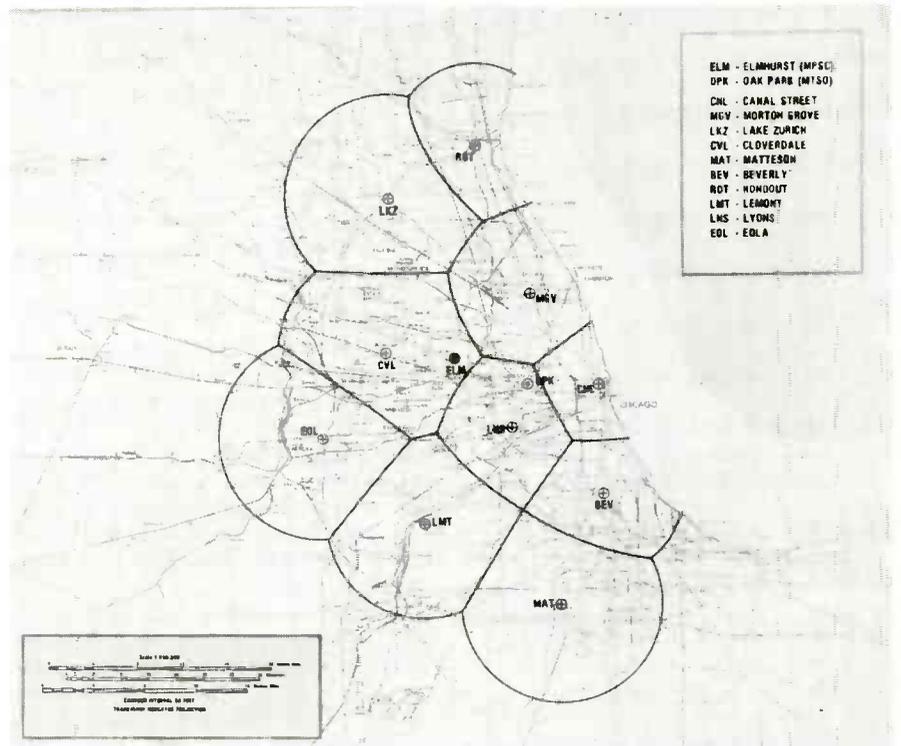


FIG. 4—THE CHICAGO TEST of the cellular mobile phone system divided the metropolitan area into 10 cells. Future networks will have smaller cells and use lower-power equipment.

How cellular phones work

The secret to the cellular system lies in two-way digital-data communications between car-and-cell, and cell-and-MTSO, plus one central computer at the MTSO keeping everything under control.

Perhaps the best way to describe all the intricacies of the system is to follow

a couple of telephone conversations from start to finish, with a cell hand-off added for good measure. This example is based on calls through the Chicago developmental system, operated since 1978 by Bell Laboratories and Illinois Bell Telephone, and used by about 2000 willing customers from a cross-section of professions and businesses.

You get in your car and turn on the engine as you always do. Then you switch on your deluxe telephone-control head mounted on the transmission hump. Using the *Touch-Tone* buttons, you key in your own three-digit security code that makes sure you're the only one making calls from your mobile phone. Nothing is coming through the speaker, but the logic unit of the trunk-mounted transceiver scans through the control channels of all cell sites in your metro area and determines by Cell A's set-up channel's signal strength that you are in Cell A. The set-up channel is a data-only frequency pair, and is a critical link in cellular telephone. Your radio is then kept on Cell A's set-up channel as long as the data signal there stays strong enough. At the cell site, there is a back-up setup channel transceiver if one should fail. The setup process takes less than a second.

As you drive along, you want to call your friend to see if he needs your help with a personal-computer problem he's been having. Without picking up the headset, you enter his telephone number on the *Touch-Tone* pad. An audible "beep" comes from the head's built-in speaker when each button is pushed, and the number appears in a display by the buttons. A quick glance at the display confirms you have properly entered the number, so you press the SEND button.

The following sequence takes place about as quickly as if you were calling your next door neighbor from your kitchen: The mobile logic unit sends out a data burst on the setup channel that identifies your radio, sends the number you're calling, and alerts Cell A that you have an outgoing call. Cell A's receiver passes the information over a landline to the central MTSO, where the Western Electric computer assigns an unused voice channel for the call. That frequency is passed back through Cell A to the mobile radio. The mobile transceiver obeys, and shifts frequency to the specified channel. When the MTSO senses the mobile unit's signal on that channel (the information is again relayed via Cell A's receivers), it places the call over the landline phone system.

The next sound you hear over the console speaker will be the ringing of your friend's phone. If the called number is busy, no problem. You will hear a busy signal, as you would expect. Simply press END, which alerts the MTSO to "hang up." Your channel opens immediately for other callers, as your radio shifts back to silently monitor the setup channel. Since that last number you dialed is still shown by the display, pressing SEND will automatically re-dial the call. The same instantaneous data exchange and frequency shift, though perhaps on a dif-

ferent channel, will take place.

Well, this time your friend answers the phone, and you become engaged in a long conversation. Unknown to you or him, your car is about to go from Cell A to Cell B. Here's what happens at a hand-off: The MTSO computer is busy monitoring the signal strength of every mobile signal coming through every cell site. It "sees" that your signal is starting to fall off from Cell A (though you don't realize it on your end) and it must find an open channel for you in Cell B. Since channels are not shared by adjacent cell sites, your hand-off involved a shift in both transmit and receive frequencies in addition to a change in cell sites.

The computer spots an open channel for you in Cell B. When your signal drops to a specified level, the MTSO sends a data burst (at a data rate of 10 megabytes-per-second) to your radio's logic unit via Cell A. In that one-quarter second, the audio is interrupted as the radio gets its instructions to shift channels—which it does without your even suspecting that brief "blank and burst" sequence.

When you hang up the handset, your radio goes back to the setup channel—but a different set-up channel, because you are now in Cell B. As you continue your drive, you decide that a quick call home may save you from having to go out later for milk. So you press a two-digit memory code to speed dial your home phone number, one of several frequently called numbers you previously stored. You find out that you are to pick up your children at a softball game on the way home.

At the field you find that the game is just about over, so you decide to park the car nearby and watch the last inning. Meanwhile, your wife finds that she does need milk, and wants to let you know before you get home. She dials your mobile phone number—a regular seven-digit number assigned to your telephone through an exchange located at a conventional (landline) telephone switching office.

The call is automatically sent to the central MTSO, whose job is to find you. It sends your identity code through every cell site in the service area on every set-up channel. Your radio, which you purposely left on, is constantly listening to the setup channel. When it hears your number, it tells Cell B via the setup channel that you are in Cell B. The MTSO then assigns a voice channel in Cell B for your wife's call. Your radio shifts to that channel, and your phone rings. Fortunately, you select the option that honks your horn when the phone rings.

As in that example, business users in the AMPS Chicago test found that the system saved them time and gas. A survey found that 84% of them were "very

satisfied" with the service provided by the cellular telephone system.

Our test

To test for ourselves the voice quality of the AMPS system, we took a ride in a car with a specially equipped mobile telephone. In addition to the telephone control head, that unit had a little box under the dash called a System Access Monitor, which gives a readout of the channel currently being used and has a signal-strength meter.

Local and long distance calls were as easy to make as if from a desk. Audio quality of the mobile phone was equal to any land-line, except when going through very low-elevation tunnels and extended viaducts. Even then, a couple of static crackles at the mobile end were at a very low level—perhaps inaudible to someone who did not know what he was listening for. None of those we called suspected we were talking on a mobile phone until we let them in on the secret. Communication was consistently flutter-free, even when the System Access Monitor meter showed that there were extreme changes in signal level.

The next test was to force a hand-off to an adjacent cell to detect the blank-and-burst used to shift frequencies. As the channel readout changed on the System Access Monitor, we heard a slight electronic "click," and that was all. Again, we were listening for it with a tuned ear; otherwise we would have missed it. And since normal installations don't have the Monitor readout or meter, you would never know when to expect a hand-off—or when one had occurred.

As the demand for mobile communications increases, especially with the growth of microwave digital telecommunications, a system is needed that will make every megahertz count. Cellular mobile telephone is such a system, and it will soon provide many of us with high-technology, reliable, two-way voice communications that will be just as convenient as dialing your home or office telephone. **R-E**



BUILD THIS



ROBERT N. BEABER

THE 2716 EPROM (ERASABLE PROGRAMMABLE Read Only Memory)—currently available for ten dollars or less—is ideal for microprocessor-based projects. It permits storage of 2K (2048 bytes) of user program and operates from a single 5-volt supply. Because it can be erased by strong ultraviolet light, its contents can be changed if a modification must be made to the program it contains, or it can simply be erased for reuse in another project.

The programmer described here allows the project designer to program the 2716, using hexadecimal code, at each memory location by entering the required data with two thumbwheel switches and pressing a single PROGRAM switch. After programming a given memory location, the device automatically selects the next highest one. It also has a SINGLE STEP or CONTINUOUS RUN option to provide access to address locations at a rate determined by the user. Those options provide the control needed to verify the data contained by the EPROM. Both the memory location addressed and its contents are indicated by 7-segment LED's.

Circuit operation

Figure 1 is a schematic of the EPROM programmer. Refer to it as we discuss how the circuit works.

The programming sequence begins when the PROGRAM switch, S3, is pressed. That switch is debounced by IC11-c, and the resulting pulse is used to clock one-shot IC7-b. The output of the one-shot enables NAND gate IC8-c and allows the 40-Hz oscillator—IC9-b—to clock counter IC14.

Initially, the counter's output is set at 0. As it is clocked by IC9-b its outputs go to a logic-high (+5 volts) state one at a time, in sequence. *Note that only five of the ten possible outputs are used—pins 1, 4, 5, 7 and 11; they correspond to counts of 5, 2, 6, 3 and 9, respectively.* As the outputs of IC14 change state,

they control the actions of latches IC13-a and IC13-b.

When pin 4 of IC14 goes high, pin 1 of IC13-a is latched high. That, through buffer IC2-c, brings pin 20, CS (Chip Select—sometimes referred to as "data enable") of SO1, which contains the EPROM, high, and readies the EPROM for programming.

The output of IC14's pin 4 also turns on Q1 and Q2, which provide the programming voltage (25.5 volts) to pin 21 of SO1, and enables the three-state drivers, IC1 and IC2. The inputs of those two IC's are connected to S1 and S2, the BCD-output thumbwheel switches used to provide the programming data. The outputs of the two IC's are connected to pins 9-11 and 13-17 of SO1, which correspond to the eight data lines of the 2716 EPROM.

After 25 milliseconds— $1/40$ -second, equal to one period of the 40-Hz clock—pin 7 of IC14 goes high and IC13-b is also latched high. That, in turn, takes pin 18 (CE/PGM—CHIP ENABLE/PROGRAM) of SO1 high and the data from the thumbwheel switches is programmed into the EPROM. The address programmed usually starts with 0, but can

be selected by S4, (SINGLE STEP), and S5 (RUN).

When 50 milliseconds have passed, pin 1 of IC14 goes high. That resets IC13-b, removing the logic-high from pin 18 of the EPROM. After another 25 milliseconds, pin 5 of IC14 goes high, resetting IC13-a. That removes the CS voltage, removes the 25.5 volts from pin 21 by turning Q1 and Q2 off, and disables IC1 and IC2, thus removing the thumbwheel-switch data from the EPROM's data lines.

When pin 11 of IC14 goes high, it resets one-shot IC7-b, disabling NAND gate IC8-c and cutting IC14 off from the 40-Hz clock. Pin 11's going high also resets IC14 to 0 and advances counter IC3 to the next address to be programmed.

The remainder of the logic circuitry provides RESET, SINGLE STEP, and RUN functions.

Switch S6 (RESET) is used to reset the cascaded address counters IC3, IC4, and IC5, to zero. Switch S4 provides SINGLE STEP capability—every time the switch is pressed, IC7-a, a one-shot, supplies a pulse to counter IC3, causing the memory location being addressed

PROM PROGRAMMER

It is frequently convenient for the computer or microprocessor user to store his programs in reusable EPROM's (Erasable Programmable Read Only Memories). This programmer for 2K 2716 EPROMS allows the job to be done quickly and efficiently.

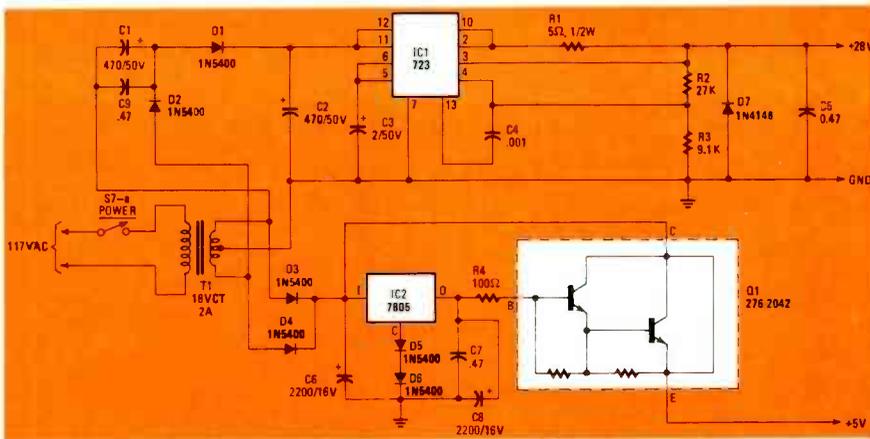


FIG. 2—POWER SUPPLY provides both the 5-volts needed for the logic circuitry and the 25.5-volts used to program the EPROM.

to be incremented by one. Finally, S5 (RUN) allows the variable-frequency oscillator formed by IC9-a and controlled by R10 to clock counter IC3 at a rate determined by the user.

The three switches provide the user with several means for accessing EPROM memory addresses to enter or verify data. The LED displays on the address and data lines provide a continuous indication of the memory address being accessed and of its contents.

Power supply

The power supply shown in Fig. 2 provides all the voltages required by the programmer. Power switch S7 has two sections—one for 117-volts AC (Fig. 2) and one for 28-volts DC (Fig. 1). That is necessary because when the AC voltage is cut off by S7-a, an induced current in the secondary of the transformer will cause a pulse to appear on the 28-volt DC line. Since that pulse can be transmitted to pin 21 (V_{pp}) of the EPROM—a pin used in the program-

PARTS LIST—POWER SUPPLY

All resistors 5%, 1/4-watt unless otherwise specified

R1—5 ohms, 1/2-watt

R2—27,000 ohms

R3—9100 ohms

R4—100 ohms

Capacitors

C1, C2—470 μ F, 50 volts, electrolytic

C3—2 μ F, 50 volts, electrolytic

C4—.001 μ F, ceramic disc

C5—0.47 μ F, ceramic disc

C6, C8—2200 μ F, 16 volts, electrolytic

C7—0.1 μ F, ceramic disc

Semiconductors

IC1—LM723N adjustable voltage regulator

IC2—7805 5-volt regulator

Q1—high-power Darlington, NPN-type

(Radio Shack 276-2042 or similar)

D1—D6—1N5400, 3 amps, 50 PIV

T1—18 volts, center-tapped, 2 amps

Miscellaneous: TO-3 heat sink, PC board or perforated construction board, 14-pin IC socket, hardware, etc.

ming process—erroneous data may be entered into the IC. Therefore, S7-b is used to cut off the 28-volt supply at the same time the main 117-volt supply is turned off.

Construction

The 2716 EPROM programmer can be constructed on perforated construction

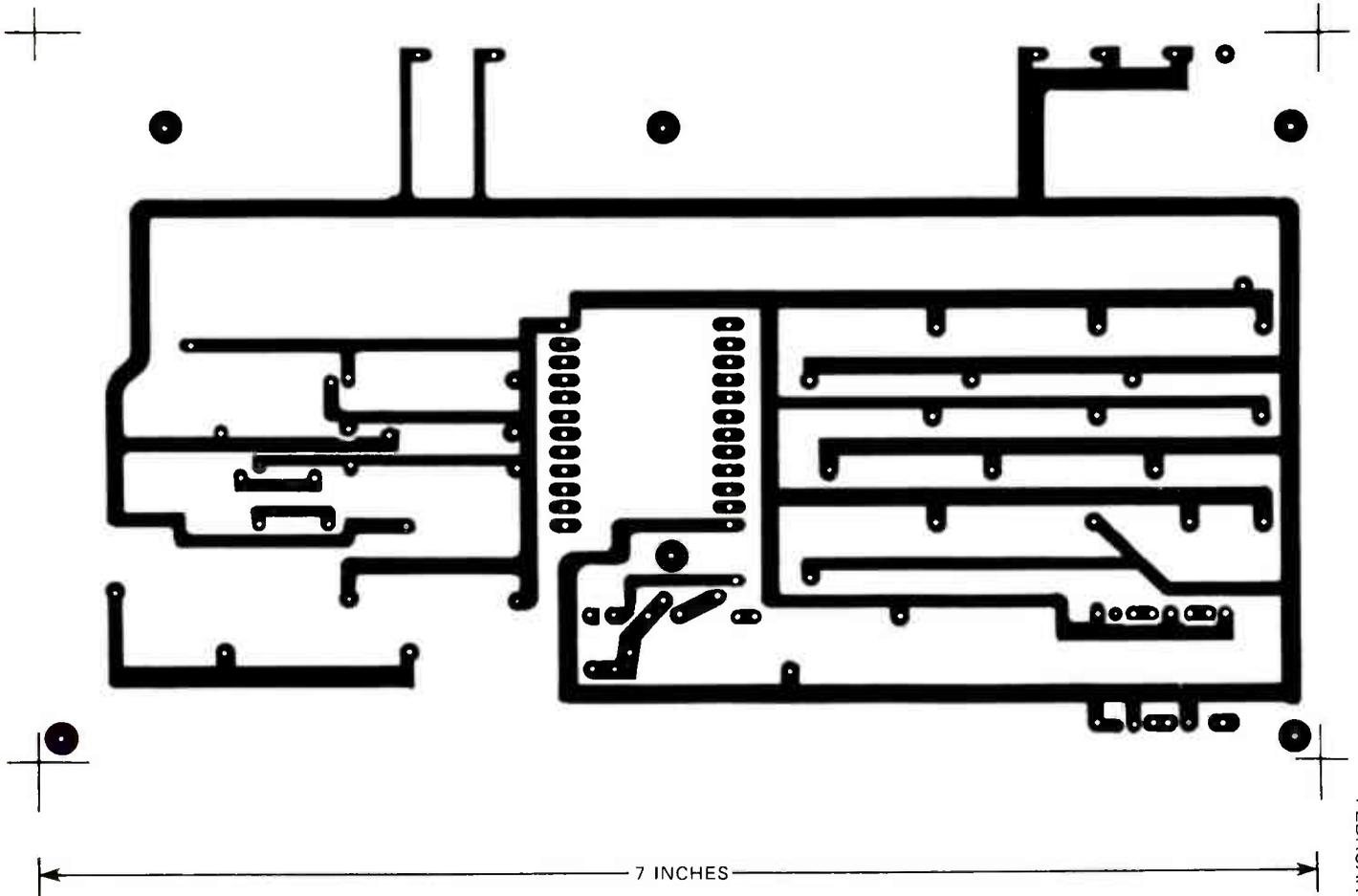


FIG. 3—PERFORATED CONSTRUCTION BOARD is used to mount components. Stick-on copper traces can be applied to serve as power and ground buses.

REMOTE VOLUME ATTENUATOR

This IC can be used to make a great remote volume-control. But what's even better is that the device can be operated by either analog or digital means.

MARTIN BRADLEY WEINSTEIN


THERE'S AN INTEGRATED CIRCUIT AVAILABLE from Motorola, the MC3340P, capable of effectively attenuating an audio signal by 90 dB or introducing up to 13 dB of gain (or anything in between) while exhibiting a total harmonic distortion of about 0.6%. Attenuation can be controlled by either a DC voltage (between 3.5 and 6.0 volts) or a resistance (0-33 kilohms) applied to its control pin and referenced to ground. Suggested for use with approximately 100-millivolt RMS input-signals, it can be used with signals up to 0.5-volt RMS. The supply-voltage range is wide—9-18 volts DC. And it's priced in the \$1.00-\$1.50 range.


This little wonder can accomplish a number of remarkable wired-remote-control functions. For example, a radio receiver in the trunk of your car feeding a rear-deck speaker can be easily modified by using the circuit shown in Fig. 1 in place of its volume control; a single wire to a dash-mounted pot then provides complete control of its volume. But there's an even better way to use this device.

Digital control

The circuit shown in Fig. 2 gives you complete control over attenuation using a set of resistors arranged in a network. Grounding any combination of four (or fewer) lines (labelled A, B, C, and D) provides a specific degree of attenuation.

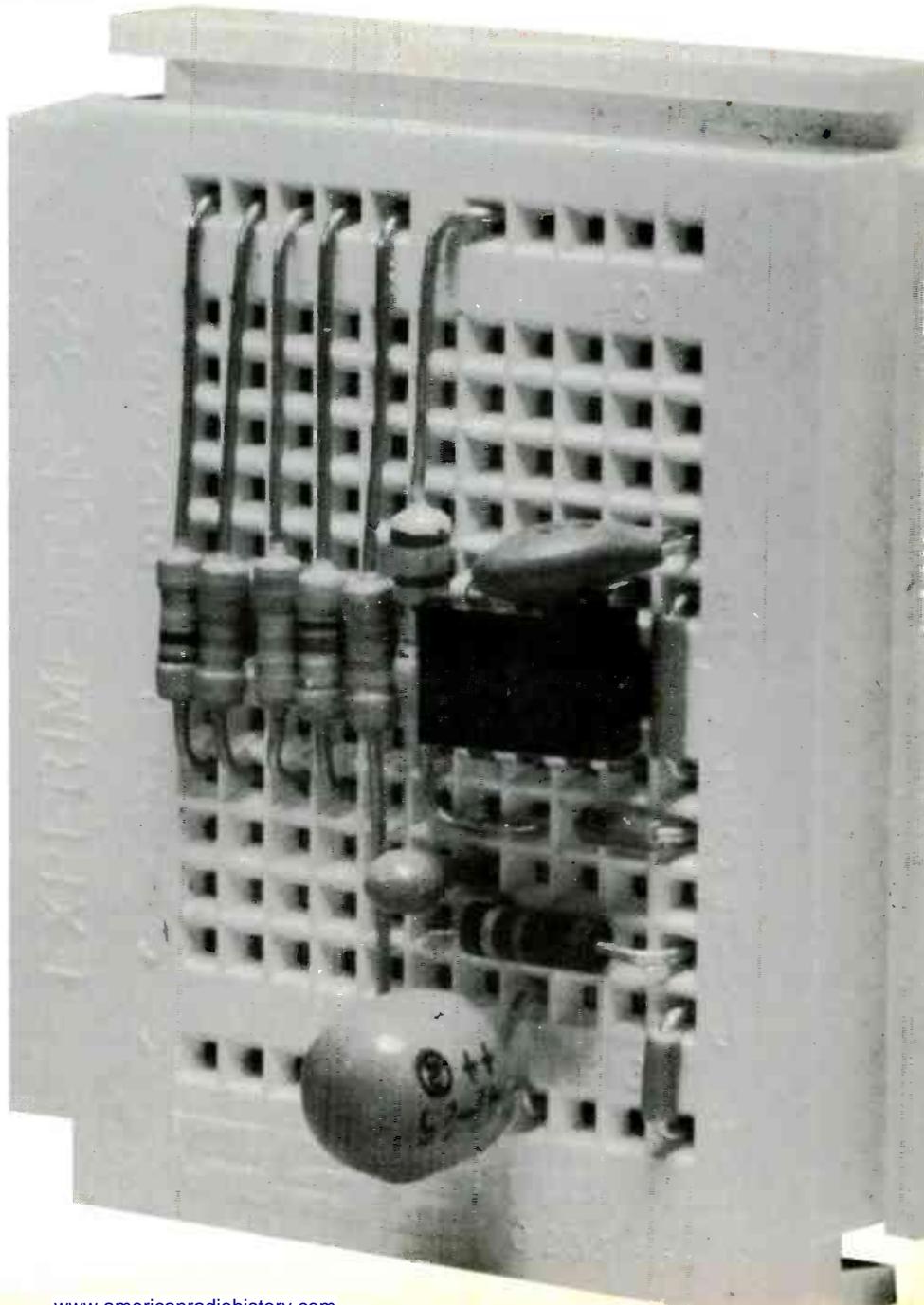
Getting the circuit to perform properly is harder than it appears. The control characteristics of the MC3340P are far from linear. Another complication is getting a reasonably linear analog control characteristic starting with binary values and off-the-shelf resistors.



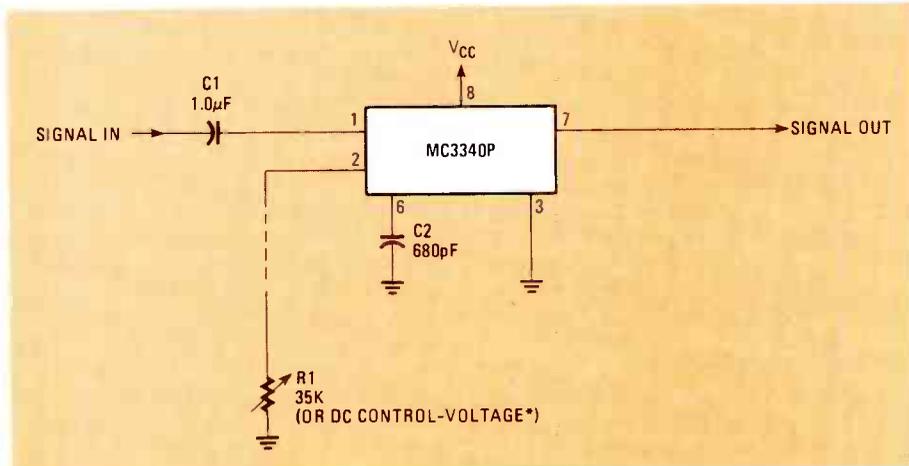

*ATTENUATION PROPORTIONAL TO VOLTAGE AT PIN 2 WHEN 3.5VDC V_C 6.0 VDC, OR PROPORTIONAL TO RESISTANCE FROM 0 TO 33K OHMS

FIG. 1—THIS SIMPLE ATTENUATOR CIRCUIT allows you to control the volume of a receiver hidden in the trunk of your car with a dash-mounted potentiometer.

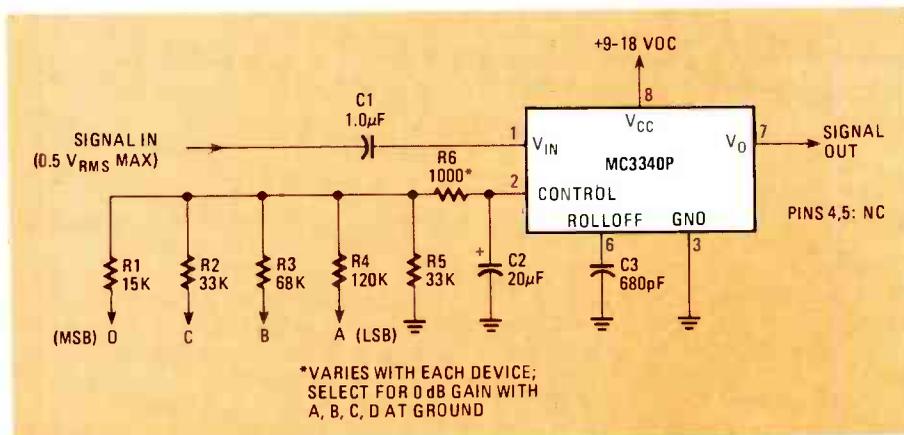

*VARIES WITH EACH DEVICE; SELECT FOR 0 dB GAIN WITH A, B, C, D AT GROUND

FIG. 2—SCHEMATIC DIAGRAM of a digitally-controlled attenuator circuit. Lines A, B, C, and D, can be driven by the simple circuit shown in Fig. 4.

The technique required is common to a number of digital-to-analog conversion schemes. You can get a fairly linear response by using resistors with a 1-2-4-8 (powers-of-two) relationship. But there are no combinations of standard resistors with that relationship, although the 15K-33K-68K-120K-ohm combination used here (for R1, R2, R3, and R4) comes very close.

Trial-and-error had a great deal to do with establishing the final component values, but there were also a few educated guesses involved. The parallel combination of R1, R2, R3, and R4, for example, is itself in parallel with a 33K resistor (R5) because that value is the maximum control resistance and corresponds to the maximum attenuation of the IC. It took a very long night with

PARTS LIST

Resistors ¼ watt, 5% or better

- R1—15,000 ohms
- R2, R5—33,000 ohms
- R3—68,000 ohms
- R4—120,000 ohms
- R6—5100 ohms (see text)

Capacitors

- C1—1.0 µF
- C2—20 µF, electrolytic
- C3—680 pF

Semiconductors

- IC1—MC3340P (Motorola)

TABLE 1

D	C	B	A	Net resistance
0	0	0	0	7650Ω
0	0	0	1	8040Ω
0	0	1	0	8370Ω
0	0	1	1	8860Ω
0	1	0	0	9330Ω
0	1	0	1	9950Ω
0	1	1	0	10500Ω
0	1	1	1	11310Ω
1	0	0	0	12960Ω
1	0	0	1	14280Ω
1	0	1	0	15510Ω
1	0	1	1	17500Ω
1	1	0	0	19750Ω
1	1	0	1	23220Ω
1	1	1	0	26880Ω
1	1	1	1	34000Ω

a scientific calculator to double-check the calculated performance of the circuit, and that's why R6 is there—to adjust the performance so that it is slightly more linear. Table 1 gives the calculated net resistance for each control code and Fig. 3 plots both net control-resistance and calculated attenuation values against the binary control codes.

Unfortunately, errors can occur almost anywhere in this design. For one thing, the manufacturer's curves, while accurate enough when you're controlling the IC with a potentiometer, aren't very precise as far as determining actual attenuation vs. resistance performance when you're using fixed values. Another problem is that even 5%-tolerance resistors can vary enough to cause jarring nonlinearities in their combined performance in this network. For example, one combination can easily yield a lower net resistance than another combination representing a higher binary value. The solution is either expensive precision resistors

INPUT
LOGIC-LEVELS

D	C	B	A
1	1	1	1
1	1	1	0
1	1	0	1
1	1	0	0
1	0	1	1
1	0	1	0
1	0	0	1
1	0	0	0
0	1	1	1
0	1	1	0
0	1	0	1
0	1	0	0
0	0	1	1
0	0	1	0
0	0	0	1
0	0	0	0

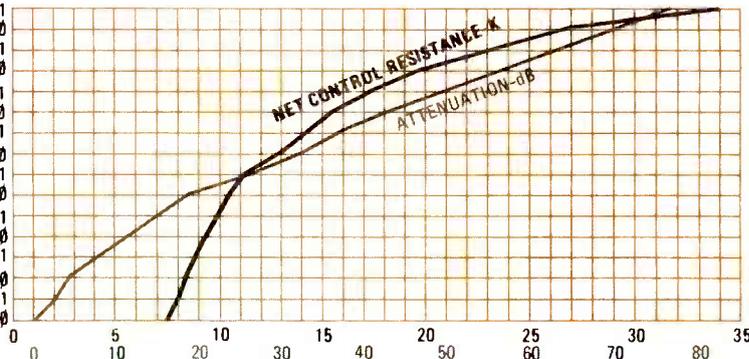


FIG. 3—NET CONTROL RESISTANCE and calculated attenuation plotted against four-bit control signals. Note that the calculated attenuation curve is nearly, but not quite, linear.

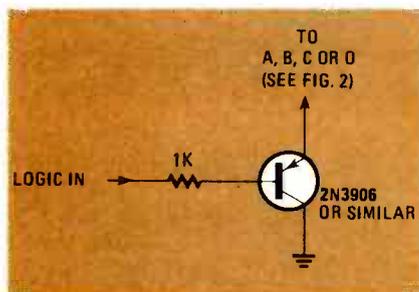


FIG. 4—THIS CIRCUIT can be used to drive a digital volume attenuator's control lines. Almost any PNP transistor can be used.

or—as you'll probably choose—hand-selection of 5% resistors.

Even with selected resistors, the performance of the breadboarded circuit was not as predicted by the graph in Fig. 3 when input and output signals were measured and actual attenuation calculated. The problem turned out to be R_6 : the value I had chosen was too small and the circuit had some gain

when it should have had 0-dB attenuation. That made the whole system's performance nonlinear. Increasing R_6 to 5100 ohms helped performance significantly, but note that the value of R_6 will vary from device to device. You wouldn't think a circuit this simple could have caused so many problems. But the end result was worthwhile.

Driving the control lines

There are several ways to provide the digital control-signals the circuit requires. Most computers and digital control-systems can easily drive a PNP transistor (Fig. 4), possibly using a latch. A hexadecimal thumbwheel switch (or any 4-bit binary-encoded switch) can be used without drivers. A four-channel optical system could be used where isolation was required.

A SIPO (Serial In, Parallel Out) shift register could also be used. A serial Baudot or ASCII code, for example, following a specific control-character

on a teletypewriter circuit could raise the volume of an alert tone-generator or monitor receiver in a network or a remote-control application.

Perhaps more exciting is the prospect of full keyboard control of a communications system, including volume levels, with or without the assistance of a computer. A single dashboard-mounted keypad could select synthesizer frequencies or channels, set volume and squelch levels, adjust mike gain, and more—even for several transceivers. All the valuable hardware could then be secured in the trunk.

Most exciting of all is the fact that this simple circuit makes computer coordination of our living and working environments possible. With the attenuators installed and the proper control bussing routed, the "turn-it-up" and "turn-it-down" nuisances in life might be eliminated. If the phone should ring, for example, the computer might use the circuit to turn down the volume automatically on the TV or stereo. If your clock radio wasn't quite rousing you, the computer could make it louder; or at night, it could fade the music down as you fell asleep. You could also program maximum volume levels for any number of devices and vary them with the time of day—to let the kids blast the stereo from, say, 4 to 5:30, but to keep it under control at other times. (The prospects for fading in romantic mood-music are also promising.)

Basically, this circuit is just an elaborate volume control (although the MC3340P responds very well to signals up to 600 kHz, and fairly well through 2 or 3 MHz)—a potentiometer with "bells" and "whistles." I'm sure you can think of quite a few places to use something like this. **R-E**

SERVICE QUESTIONS

TUBE BURNOUT

In a GE M704 (a Canadian model) the horizontal-output tube went out too often. I wrote to you and you said that the problem could be caused by the failure of the horizontal oscillator to start, resulting in overload of the output stage. You suggested that I change the capacitors across the oscillator coil. I did, and that did the trick. Thanks.—*D.H., London, Ontario*

SNOW, NO AGC

I've got a CTC-43A with far too much snow on all channels. The RF AGC control has no effect at all. The plate of the 2DS4 RF-amp tube reads +250 volts and

the grid reads -30 volts. The 16K resistor isn't shorted, and a new tube didn't help.—*P.B., Ewa Beach, HI*

I think you've got your finger on it. Note that the plate voltage on the RF tube is the same as the supply voltage—+250 volts. You're not drawing any current. That must be due to the excessive grid voltage. The normal RF-AGC voltage with no signal should be only +0.79 volts. Check the AGC keyer collector; also the 10-megohm resistor that feeds it from the +270-volt supply. Also check the 2.2-megohm resistor between that point and the tuner.


I'd be inclined to suspect a leaky AGC transistor. Check to see whether the IF-AGC voltage works. If so, something is wrong in the resistors in the RF-AGC circuit and I am inclined to suspect the 10-megohm one (we've had problems with that resistor changing value before).

DAMPER DIODES

This RCA EP454W portable works fine for a while, then the horizontal-output tube gets red hot and blows the damper diode. I suspected the oscillator stopping, but every time I check, it's running. I am totally confused, do you have any ideas?—*J.G., Mentone, IN*

I think you've got one thing reversed. Probably, the damper diode shorts and that blows the tube. Check the solid-state damper. If it's a single unit, Part No. 125932, it's the original. That part has been known to cause problems. RCA recommends replacing it with a dual "piggy-back" type, Part No. 120818.

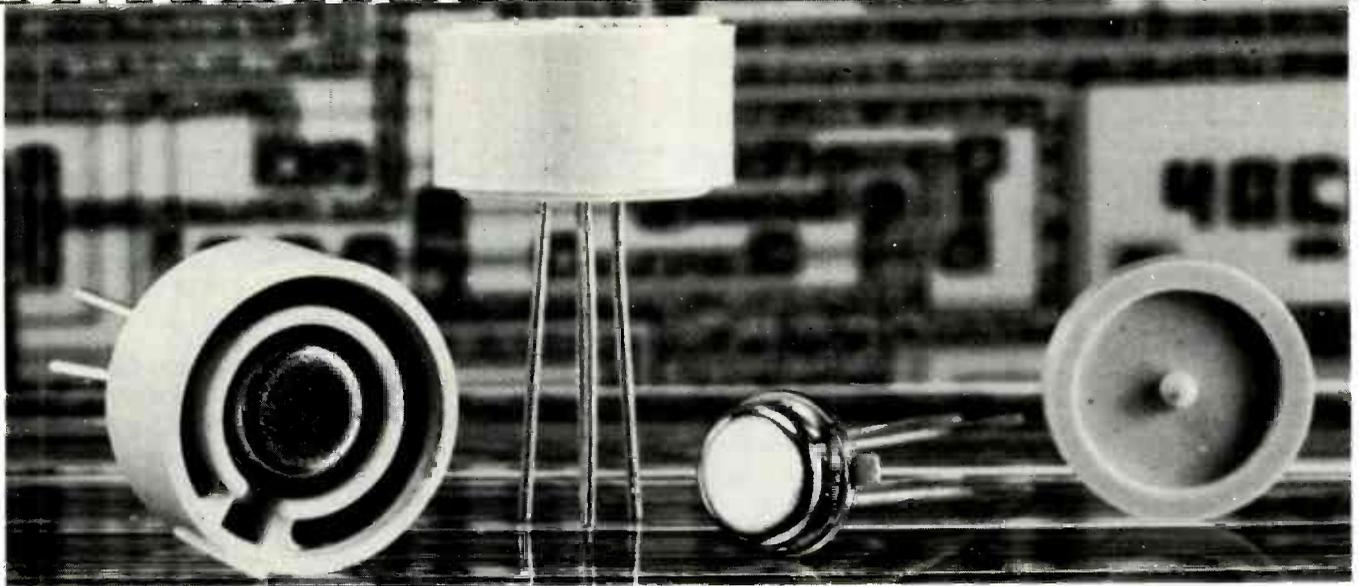By the way, the parts list you're using is incorrect. It recommends using a GE-504 as a replacement. That's a plain sine-wave type, but you must use a fast-recovery type here and in all horizontal-frequency circuits. **R-E**



Precision Voltage References

An electronic instrument or circuit can only be as accurate as the reference used to calibrate it. Build your own low-cost, high-precision voltage references using the information presented here.

JOSEPH CARR

PRECISION VOLTAGE-REFERENCE CIRCUITS are constantly needed by anyone who works with electronics. They are needed in an electronics workshop, for example, to calibrate voltmeters and oscilloscopes. In the laboratory, they can be used to troubleshoot, test, and calibrate instruments such as pH-meters. Computer applications include A/D and D/A converters; most of the popular circuits that are used for those applications require an external voltage reference to make them reasonably accurate. In addition, projects such as electronic thermometers, and anything based on the Wheatstone bridge (and that includes quite a few electronics instruments) will require a precision voltage-reference.

Commercially available voltage references can be very expensive, but we can make references that are precise enough for all but the most demanding applications for a small cost. The technology that is available today allows us to do things that a hobbyist could only dream about a decade ago. In this article, we will discuss some of the more common precision voltage-references, and offer both finished projects and design notes for those who would

like to "roll their own."

Why does a hobbyist need a precision voltage-reference? Let's say, for example, that you want to build an A/D or D/A converter. We all know that the greater the bit-length of those converters, the better the accuracy and resolution of the measurements made, or voltage produced. But no data converter is better than the analog voltage-reference used to make the conversion. All data converters produce an output that is the product of a binary word and an analog reference voltage (or current, in some cases). In practical terms, that means that an error in the voltage reference will foul up the accuracy of the conversion.

Let's consider two data converters that a hobbyist might use: 8-bit and 10-bit D/A converters. The resolution of the 8-bit converter is 0.391%; the resolution of the 10-bit converter is 0.098%. Those figures are the maximum possible resolution based only on bit-length. If the reference voltage for both is 10.00 volts, then the actual reference voltage must fall within the range of 10.00 volts ± 391 mV in the 8-bit case and 10.00 volts ± 98 mV in the 10-bit case. A 12-bit D/A converter, which is now avail-

able at relatively low cost, requires an analog reference of 10.00 volts ± 24 mV.

Clearly, as the bit length of the converter increases, the voltage reference must become more precise. Reference voltage sources for 8-, 10-, and 12-bit D/A converters are easily constructed at a low cost using components available today.

Zener diodes

One of the most important voltage references used in electronics is the Zener diode. Figure 1 shows the basic circuit for a Zener-diode regulator; a graph of the voltage-versus-current characteristic for a typical Zener diode is shown in Fig. 2.

The Zener diode acts much like an ordinary PN-junction diode as long as the applied voltage is less than a specified value of reverse bias (V_Z), or when the diode is forward biased. In the range between V_Z and a forward bias of approximately 700 mV (the actual figure is usually 600 to 700 mV), the current through the diode is a small reverse current called leakage. The diode is essentially turned off in that region. When the voltage exceeds a forward bias potential of 700 mV, the

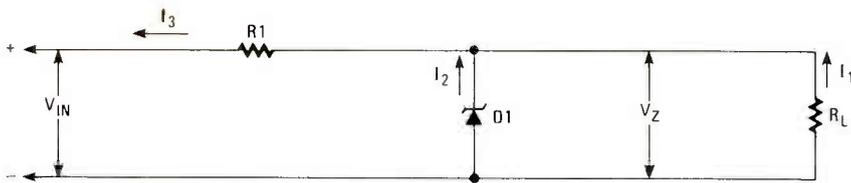


FIG. 1—THE ZENER DIODE is often used as a voltage reference or as a simple voltage regulator. A basic circuit for a Zener diode regulator is shown here.

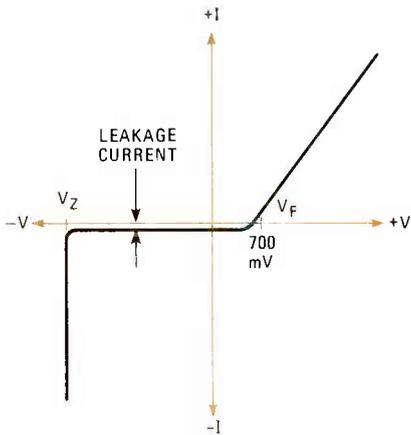


FIG. 2—WHEN THE REVERSE BIAS exceeds V_Z the negative current through the Zener increases rapidly.

positive current increases in the same manner as in an ordinary PN junction. The Zener acts quite differently, however, when the reverse bias exceeds V_Z . When that voltage is reached, the negative current rapidly increases. No matter how much more negative the applied voltage becomes, the voltage across the diode remains relatively constant.

But the Zener diode is not the best voltage reference for many applications. The Zener's voltage rating is nominal, not absolute. When the package says "6.2 volts," it may mean some potential in the neighborhood of 6.2 volts. It is also true that the Zener's voltage tends to change a little bit with changes in temperature—hardly something that you would want a voltage reference to do!

Figure 3 shows a circuit that overcomes the temperature-drift problem of Zener diodes. Two Zeners are used in that circuit; the output is the difference between their two V_Z potentials. The

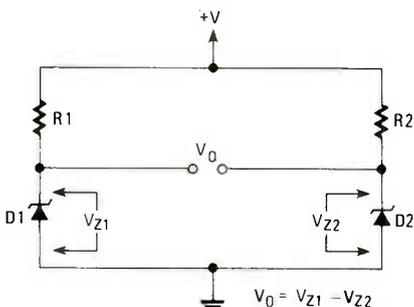


FIG. 3—THIS CIRCUIT shows one way to overcome the problem of temperature drift in Zener diodes.

circuit works reasonably well as long as both Zener diodes are kept in the same thermal environment. It is common practice to bond the two diodes together and coat them with silicone grease in order to keep them at the same temperature.

Several manufacturers once offered four-terminal "Zener diode" packages that used four to eight Zeners, in two series circuits, to form the output potential. Those devices were arranged like the circuit in Fig. 3, except for the number of diodes and the fact that all were on a common substrate, thus tracking each other in temperature.

Op-amp voltage-reference sources

One problem with Zener references, even precision Zener's that have been trimmed to a specific, accurate voltage, is that they are limited to values selected by the diode manufacturer—often not the voltage required in some particular application. We can, however, use an op-amp circuit to scale the voltage to a needed value. Such a circuit will also keep the load across the Zener at a constant, low level.

Almost any op-amp will do for that type of circuit, but it is generally best to use a premium-grade type. Some of the best are BiMOS and BiFET op-amps, such as the RCA CA3140 device.

The basic properties of an operational amplifier tell us that applying a voltage to one input will cause a voltage to appear at the output. In the circuit of Fig. 4 we apply the voltage from a Zener diode to the non-inverting input of the op-amp. That means that the output voltage will have a value equal to that voltage times the gain of the operational amplifier, or:

$$V_O = V_Z[(R_2 + R_3)/R_1 + 1]$$

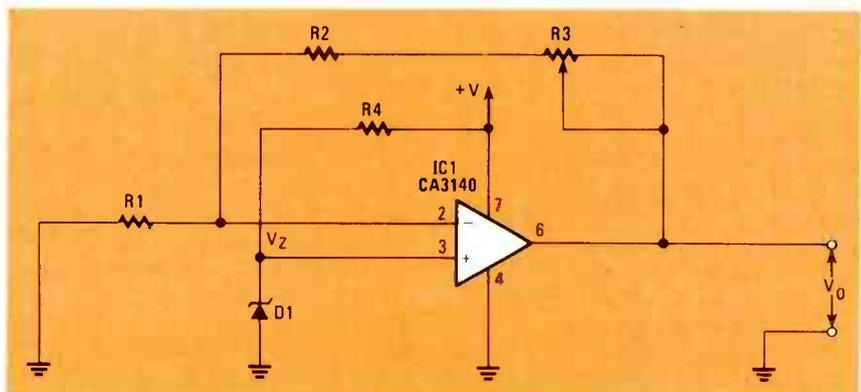


FIG. 4—AN OPERATIONAL AMPLIFIER can be used to scale the voltage from the Zener diode to whatever value is needed.

If we make the gain larger than one, then the output voltage will be greater than the Zener voltage. Similarly, if we make the gain one (i.e. if we short out R2 and R3, causing the output to be connected directly to the inverting input), then the output voltage is the same as the Zener voltage.

We can trim the value of the output voltage by making the feedback resistance variable. To keep tight control over the feedback resistance, a series combination of a fixed resistor and a potentiometer (R2 and R3) is used. It is generally good practice to make the resistance of potentiometer R3 approximately 10 percent of the total resistance (R2 + R3), and to make it a 10-, or 15-turn trimmer pot.

Special devices

In the past couple of years, semiconductor manufacturers have brought out several different types of voltage references. Some of those are two-terminal devices that act like diodes in the circuit, even though they are complete integrated circuits in themselves.

An example of such a device is the LM199 from National Semiconductor (2900 Semiconductor Dr., Santa Clara, CA 95051); the functional block diagram of that IC is shown in Fig. 5. That reference is a four-terminal device that combines a 6.95-volt Zener diode with an on-chip heater element. The Zener diode is maintained at the same temperature as the heater because it is buried on the same I.C. die (silicon chip) as the heater element.

The heater is not an actual resistance element, but is a Class-A amplifier with the input shorted. One property of such an amplifier is that it will dissipate a constant power, so that the amplifier will maintain a constant heat level after the die comes to equilibrium.

Burying the Zener in the same die as the heater element has many benefits including lower noise operation and thermal stability. Ordinary discrete Zener diodes have a drift specification on the order of 5 mV/°C, while for the LM199 devices the drift is specified in terms of microvolts per degree.

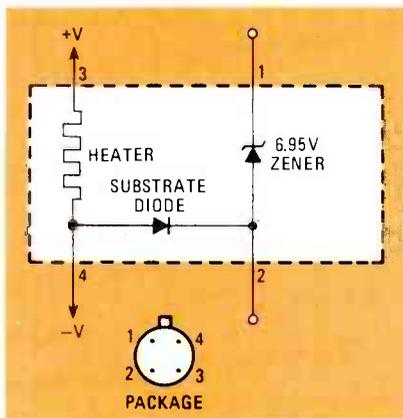


FIG. 5—A ZENER DIODE and an on-chip heater element are combined in the LM-199. The resulting IC is a highly stable voltage-reference device.

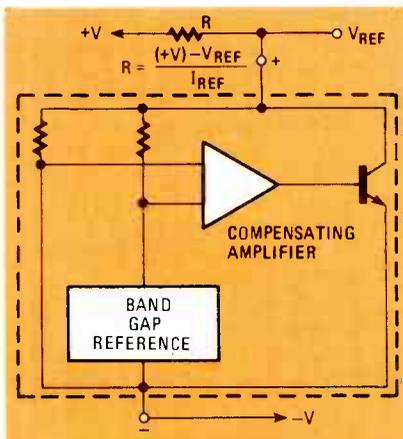


FIG. 6—THIS TWO-TERMINAL REGULATOR from Ferranti Electric can be used just like a Zener diode. It has a stability as great as 10 ppm per 1000 hours of operation.

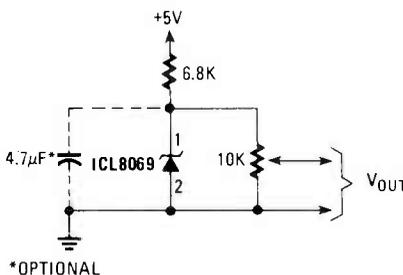


FIG. 7—A 1.2-VOLT temperature-compensated voltage reference, the Intersil ICL8079 used in this circuit is well suited to high-speed A/D and D/A converter projects.

The LM199 is rated to have an initial operating voltage of ± 2 percent of the rated nominal voltage, and the device is very stable over periods of time. The long-term stability is rated at 20 ppm, while the short-term stability is 1 ppm.

In most cases, the LM199 device is operated with a potential of 9- to 40-volts DC across the heater terminals (pins 3 and 4), while the Zener is hooked up in a circuit in the normal manner.

Ferranti Electric (87 Modular Ave., Commack, NY 11725) offers a two-terminal regulator. Those devices can be used in the same manner as ordinary

Zener diodes, but they use band-gap technology to produce a stable output voltage. Ferranti offers versions with output voltages of either 2.45 or 1.26 volts. The internal circuitry for the different types is essentially the same, and is shown in Fig. 6.

The Ferranti band-gap devices are available in five versions: ZN404, ZN458, ZN458A, ZN458B, and ZN423. The first four of those are 2.45-volt reference devices, while the last is a 1.26-volt reference device. All of the devices except the ZN423 are capable of sinking anywhere from 2- to 120-mA DC; the ZN423 can sink 1.5- to 12-mA DC.

The long-term stability of the Ferranti devices is 10 ppm per 1000 hours. Temperature coefficients range from 30 ppm to 200 ppm, depending on the device.

As in ordinary Zener-diode operation, a single series current-limiting resistor is used with the Ferranti regulators (see Fig. 6 for the formula to calculate the value of that resistor). For example, using a 2.45-volt regulator ($V_{REF}=2.45$), a +5-volt DC power supply ($+V=5$), and a current of 3.75 mA ($I_{REF}=.00375$), the resistance required would be 680 ohms.

The Intersil (10710 N. Tantau Ave., Cupertino, CA 95014) ICL8069 diode shown in Fig. 7 is another of a band-gap reference source. That device is a 1.2-volt temperature-compensated voltage reference that features very low-noise operation. As a result, it is suited well to applications in high-speed data conversion projects, at Zener currents up to 50 microamperes.

Various versions of that device are made with differing temperature coefficients and temperature ranges. Of course, the selection of a particular device depends upon the nature of the application it is to be used for. A device that would be suitable for an 8-bit A/D converter would not be suitable for a 12-bit converter.

Two applications for the ICL8069 are shown in Figs. 8 and 9. The application shown in Fig. 8 is similar to the operational amplifier circuit shown earlier. That circuit uses the ICL8069 in the feedback loop of a premium-grade LM108 op-amp. A potentiometer is used to trim the output to exactly 10.00 volts. That circuit can be used in a wide variety of applications. The circuit in Fig. 9 uses the ICL8069 device in a data-converter application. While an Intersil ICL7107 is used in that specific circuit, the ICL8069 can be used with any similar device whose output voltage is within the operating range of the diode.

Precision Monolithics, Inc. (1500 Space Park Dr., Santa Clara, CA 95050) offers two different IC voltage references, the REF-01 and REF-02. The REF-01 is a 10.00-volt device. It is housed in an eight-pin TO-99 case

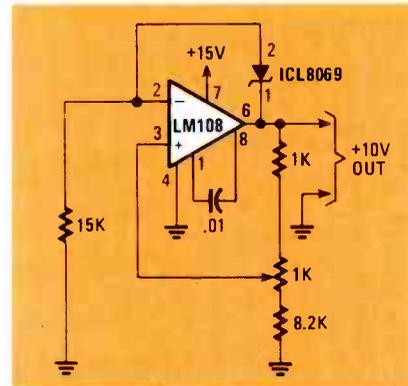


FIG. 8—A ICL8069 IS PLACED in the feedback loop of an LM108 op-amp in this voltage reference circuit. The potentiometer is used to trim the output to exactly 10.00 volts.

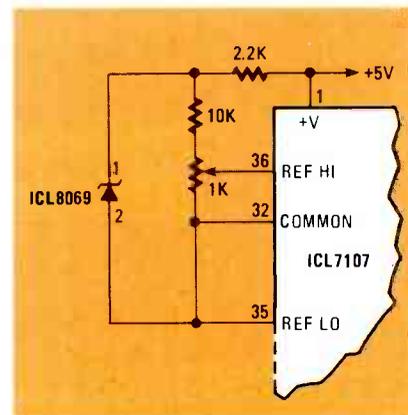


FIG. 9—USED HERE in an A/D converter circuit, the ICL8069 is well suited for such an application.

although just four of the pins are used. The REF-02 is a 5.00-volt device. It is also housed in a TO-99 case, but in this instance five of the pins are used. The fifth pin is a temperature-dependent terminal so that the REF-02 can be used as a temperature sensor.

The simple circuit shown in Fig. 10 contains a potentiometer that lets you set the output of either the REF-01 or REF-02 to exactly 10.00 volts. Either device can be used in a number of A/D or D/A converter circuits.

Selectable output supplies

All of the circuits presented thus far supply just a single output voltage. Even in the devices and circuits that use a potentiometer, it is used to adjust the output to a single value and then left alone. Sometimes however, a multiple-output voltage reference is needed. An example of that might be a voltage calibrator used with oscilloscopes and voltmeters.

The simplest way to make a multiple-output voltage reference is to place a resistance network between the output of one of the circuits presented in this article and the load. A typical network is shown in Fig. 11. In that network, each tap is a decade higher in voltage than the next lower tap. The lowest value shown is 10 ohms, but that might

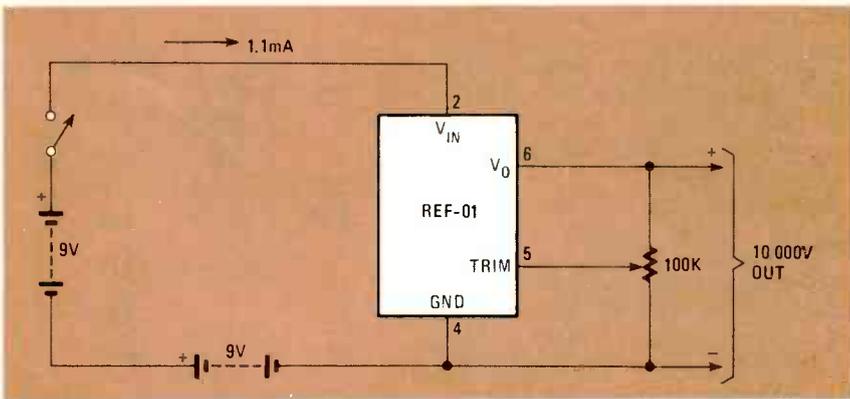


FIG. 10—A SIMPLE POTENTIOMETER is used to trim the output of the PMI REF-01 voltage reference to exactly 10.00 volts.

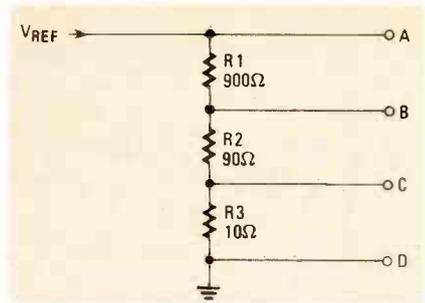


FIG. 11—A RESISTOR NETWORK can be used to get a multiple-output voltage reference. The voltage at each tap is 10 times higher than the voltage at the tap below it.

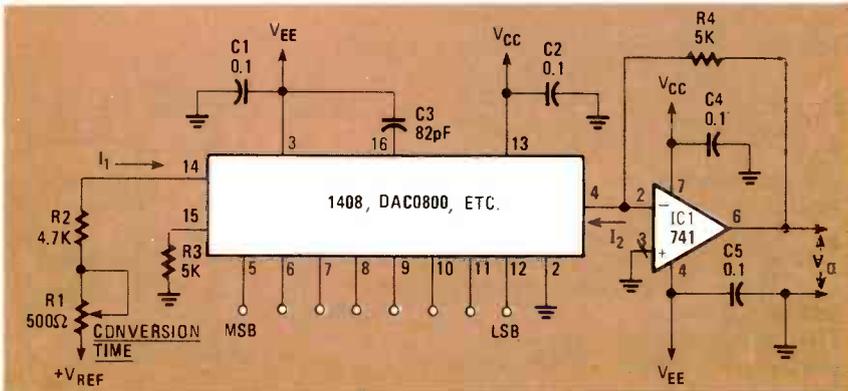


FIG. 12—A DIGITALLY SELECTABLE voltage reference. Once the input current (I_1) to the D/A converter is set, the output from the circuit (V_O) is determined by digital input (pins 5-12) to the D/A converter.

be too low for some applications. In that case, make the lowest value 100 ohms, and increase each of the other resistances by a factor of ten (i.e. make the sequence 100-900-9000-90,000-900,000 etc.). With the resistances used in Fig. 11, the voltages found at the taps would be as follows:

- A—10.00 volts
- B—1.00 volts
- C—100 millivolts
- D—0 volts

We can also make a digitally selectable reference source by using a D/A converter. Figure 12 shows how such a converter can be used to control the output voltage (V_O) of a reference supply.

The output current of any D/A converter is the product of the input current (I_1) and the binary word input, divided by the maximum possible value of the binary word:

$$I_2 = I_1 \times (N/2^n)$$

Where: I_1 is the reference current.

I_2 is the output current, N is the decimal value of the binary word input, and n is the bit-length of the D/A converter.

Try this problem out as an example: Find the output current (I_2) when V_{ref} is +10.00 volts, and R_1 is adjusted so that I_1 is exactly 2 mA. Assume that the binary word applied to the output is 10010110 (i.e. decimal 150), and that the D/A converter is 8-bits (as in Fig. 12).

The solution would be found as follows:

$$I_2 = (2\text{mA}) (150/2^8)$$

$$I_2 = (2\text{mA}) (150/256)$$

$$I_2 = (2\text{mA}) (0.586)$$

$$I_2 = 1.17 \text{ mA}$$

The output voltage from the circuit (V_O) in Fig. 12 is the product of the D/A converter current and the feedback resistors, so:

$$V_O = (I_2) (R_4)$$

$$V_O = (1.17 \text{ mA}) (5.00 \text{ kilohms})$$

$$V_O = 5.895\text{-volts DC}$$

Once the reference current I_1 is set, the output from the D/A converter is determined by the digital input to the converter. It is a simple matter to vary that input to give us precisely the reference voltage that is needed. There are many ways to do that, including connecting the D/A converter's digital input to the output port of the microcomputer or to binary-output thumbwheel switches. R-E

Solid State News

Power FET's data sheets

Power MOS Field-Effect Transistors is the title of a 30-page booklet from Motorola. It includes data sheets, cross-references, and operating theory for the company's enhancement-mode N-channel silicon-gate TMOS FET.—**Motorola Semiconductor Products**, Box 20912, Phoenix, AZ 85036.

RCA COS/MOS product guide

COS/MOS Digital Integrated Circuits (COS-278H) is a 30-page product guide written to aid the user in selecting the optimum types of devices for specific applications. It provides maximum ratings, recommended operating conditions, static electrical-char-

acteristics, selection charts, and functional diagrams for the complete line of RCA A-Series (15-volts maximum rating) and B-Series (20-volts maximum rating) COS/MOS devices. Devices covered include gates, buffers, inverters, encoders, decoders, multivibrators, flip-flops, and triggers. Also included are IC's intended for use in microprocessor, memory, and timekeeping circuits.—**RCA, Solid State Division**, PO Box 3200, Somerville, NJ 08876.

RF diodes catalog

RF Signal-Processing Diodes Selector Guide is a 6-page listing of all Motorola tuning diodes for frequency control, hot-carrier diodes for mixing and detec-

tion, and PIN diodes for switching. Included are design curves and package outlines.—**Motorola Semiconductor Products**, PO Box 20912, Phoenix, AZ 85036.


RF transistor catalog

Transistor Designers 1981 Catalog is a 159-page VHF/UHF/microwave transistor selection-guide. Included are detailed data on low-noise, general-purpose, and linear power silicon-transistors, and low-noise and linear power GaAs FET's for use between 60 MHz and 18 GHz. Charts show performance curves and typical contours for the constant-gain and noise-figure functions. Some devices are available both packaged and as unmounted chips.—**Avantek**, 3175 Bowers Ave., Santa Clara, CA 95051. R-E

BUILD THIS

AN EYE-CATCHING AND USEFUL PROJECT need not cost a great deal of money. The device described here is a combination digital clock/outdoor thermometer; the total cost of project as shown is less than fifty dollars.

To make things more interesting visually, the project was housed in a clear case—an acrylic butter dish—so that the entire circuit can be seen. Three reed switches are used to set the time or turn on the thermometer; that is done by bringing a magnet near the case, close to where the appropriate switch is located. Although standard subminiature panel mounted switches can be used, we choose the reed switches because it simplifies the construction and gives the completed

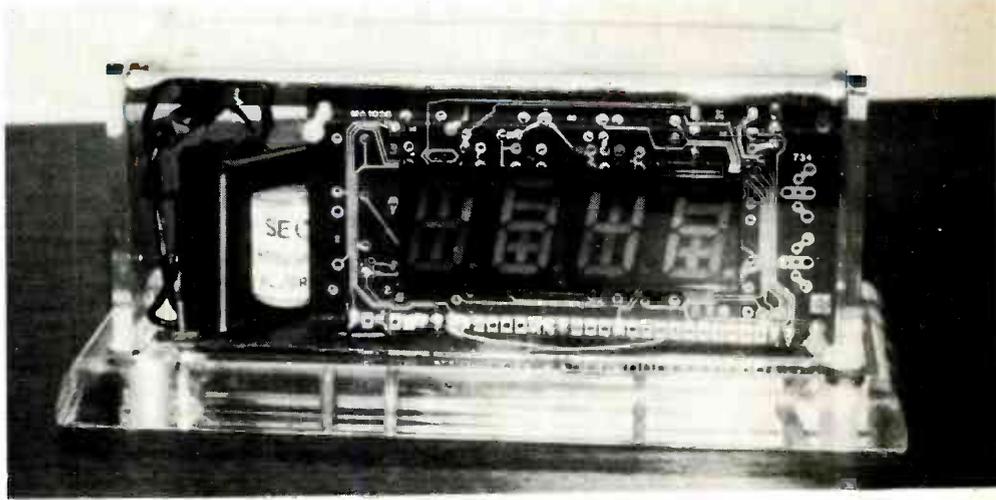

DIGITAL THERMOMETER

project a modern appearance. As a thermometer, the project displays temperature in either °C or °F over a range of -40°C to +90°C or -40°F to +193°F. The temperature sensor does not require a separate power supply and is not affected by lead length.

About the circuit

The heart of the circuit is a National Semiconductor MA1026 digital LED alarm clock/thermometer module as is shown in Fig. 1. That module features a 0.7-inch LED display, snooze alarm, 24-hour alarm, 12/24 hour mode, 50/60-Hz select, fixed/flashing colon, and sleep cycle. The sleep cycle can be used, with external circuitry, to turn off a radio or appliance after a time period of 59 minutes or less.

For this project, the module can be treated as a "black box," requiring just a transformer for input power, switches for display selection, and sensors for temperature measurement. The transformer has three windings—a 120-volt primary, a 6-volt center-tapped secondary (125-milliampere current-handling capability on either side of the tap), and a 10.5-volt secondary capable of supplying 25 milliamperes. Power consumed by the module is minimal, therefore the power-handling capacity of the switches is not important. An LM334 adjustable current source is used as the temperature sensor; that three-legged device looks like a small plastic transistor. A 220-ohm resistor, R1, is used to scale the output of the LM334 so that the IC will supply a current of one microampere-per-°C. Because the output from the sensor is a current, lead length is not critical. Note that a low temperature-coefficient resistor should

Know the time and temperature instantly with this easy-to-build project. The clear, acrylic case makes it an interesting conversation piece.

MICHAEL RIGSBY

be used for R1 (either a metal-film or, if you can find it, wire-wound unit), and that it should be part of the sensor package so that it will change temperature with the IC. To make the sensor package, mount the LM334 and the resistor on a small piece of perforated construction board.

In the basic clock/thermometer shown in Fig. 2, pin 8 is tied to pin 16, letting you set the time using the FAST SET and

SLOW SET switches. Closing the TEMP switch puts the device in the "thermometer mode." In that mode, if pin 10 on the clock module is left unconnected, the temperature readings will be in °F; if pin 10 were tied to pin 8, the temperature readings would be in °C.

The basic clock/thermometer can also be adapted for battery operation. If you want to do that, the schematic shown in Fig. 3 should be used. In that circuit, a

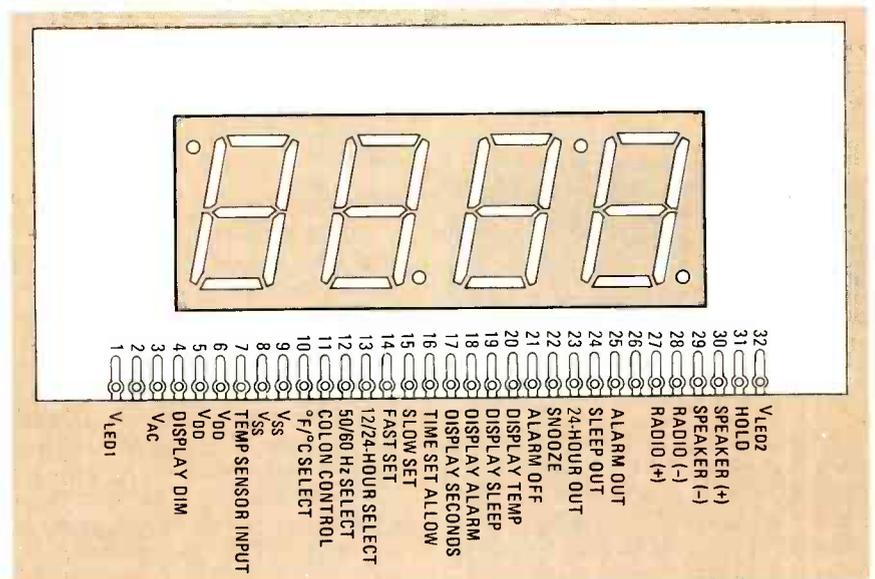


FIG. 1—THE COMPLETE PIN-OUT for the National MA1026 clock module is shown here.

PARTS LIST

Resistors ¼ watt, 5%

R1—220 ohms, metal film or wire wound

R2—10 megohms

Capacitors

C1, C2—47 pF, ceramic disc

Semiconductors

IC1—MA 1026 clock module (National)

IC2—LM334 adjustable current source/temperature sensor

IC3—MM5369 oscillator/divider

J1—miniature phone jack, panel mount

PL1—miniature phone plug

RY1-RY3—reed switches

T1—dual secondary; 10.5 volts at 25 mA, 6 VCT at 25 mA

XTAL1—3.58 MHz crystal

Miscellaneous: acrylic case, small piece of perfboard, wire, solder, hardware, epoxy glue, etc.

NOTE: If you are unable to obtain IC1, T1, or XTAL1 from your usual dealer, they can be ordered from Digi-Key Corporation, Hiway 32 South, PO Box 677, Thief River Falls, MN 56701

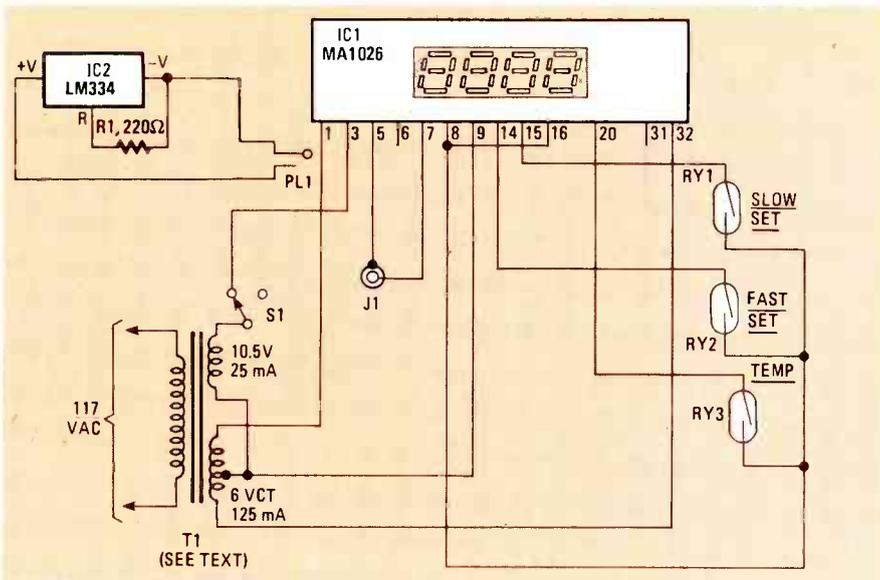


FIG. 2—SCHEMATIC DIAGRAM of the digital clock/thermometer and the temperature sensor. To make the temperature sensor, mount IC2 and R1 on a small piece of perforated construction board.

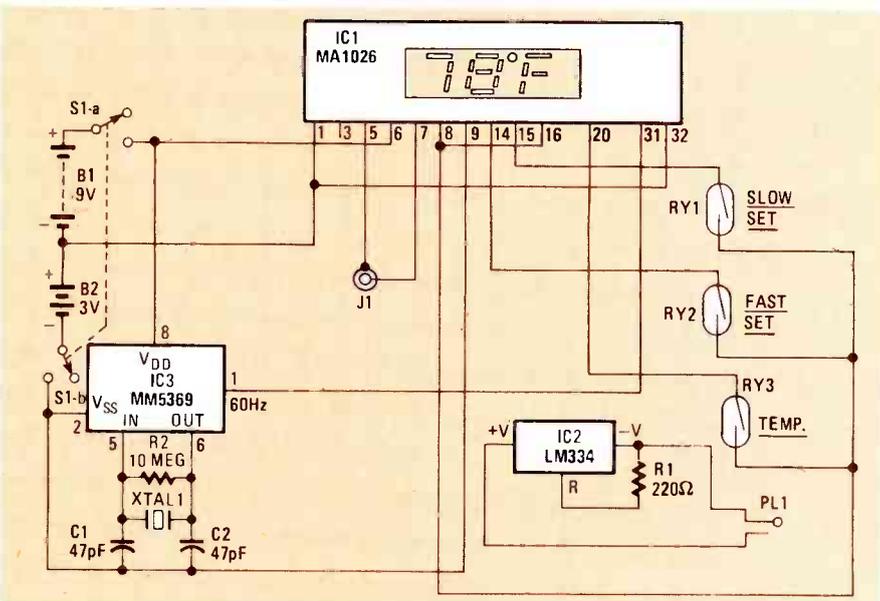


FIG. 3—FOR PORTABLE OPERATION, build this version of the clock/thermometer project. The oscillator circuit draws just 1.5 milliamperes.

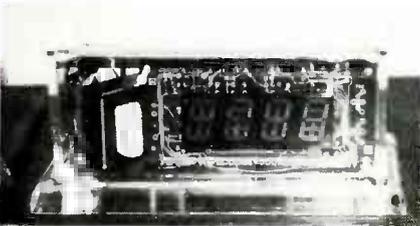


FIG. 4—THIS IS HOW the project will look when it is finished. The clear case—an acrylic butter dish—makes the clock more interesting visually.

crystal-controlled oscillator is used to drive the clock. In the oscillator, the MM5369 CMOS oscillator/divider takes the output from a 3.58-MHz crystal (that crystal is used in color television sets) and divides it using an internal 17-stage binary counter to produce an accurate 60-Hz output. Typically, the

oscillator draws less than 1.5 milliamperes.

Construction

While such things as wire size and lead length are not critical, certain precautions should be taken with component placement. Traces on the module must not be shorted by the transformer case, temperature-sensor input jack, fastening bolts, or uninsulated wires. Since the reed switches are operated magnetically, they should be placed as close to the edge of the acrylic case as possible. Also keep in mind that the transformer generates a magnetic field, and could affect the operation of the reed switches if they are placed too near it.

When drilling the case, it is very easy

to scratch or shatter the acrylic material unless you are careful. To make holes, place the case on a cloth and drill a "pilot" hole using a 1/16-inch bit. When you enlarge the hole, it is best to reverse the direction of the drill just before breaking through; use the friction of the moving bit to melt the remaining plastic. That technique avoids the danger of a snag and the resulting damage.

Fast-drying epoxy is clear and forms an excellent bond for mounting the module and other components to the acrylic—do not use glue on the face of the module as it will appear as a trapped drop of water. Avoid "super" glues; their fumes will create a permanent cloudiness in the clear plastic.

Before closing up the case, you will need to calibrate the module so that it reads the correct temperature. The temperature-sensor assembly should be stabilized in a known environment. To do that, prepare an ice-point bath of water and ice. Place a mercury thermometer in the bath, and watch the temperature until it drops to 32°F (or 0°C). Once that happens, the temperature of the bath should remain constant until all of the ice melts. Before then, however, place the sensor in the bath, and adjust the module potentiometer (the blue knob on back of the module) until the temperature reading is precisely 32°F (or 0°C). Once that is done, remove the sensor from the bath and close up the case. If you use epoxy, use only small drops—you might want to open up the case again someday. The completed project is shown in Fig. 4.

Options

As we mentioned earlier, the MA1026 module is loaded with features and

continued on page 107

Part 3 EAR-
lier in this series we discussed the data that's transmitted on the vertical-blanking interval lines, preparing the videotex decoder for the video data that is to follow it, but did not talk about that information itself.

The actual display data—the alphanumeric and graphics—is placed on a video line on a "space-available" basis, in accord with the North American Broadcast Teletext Standard proposal. That's the reason for the bytes in the headers that indicate where the next information is to be found. The data contained in the headers also allows the control information to be multiplexed with the display information.

The videotex decoder separates the two and stores them in RAM. At the appropriate time, the alpha-graphic (display) information is called up by the decoder and acted upon by the control information to determine character-size, color, etc. That system is known as the parallel-attribute format.


Prestel—which has also filed with the FCC for acceptance—does it differently. As mentioned earlier, Prestel data is transmitted sequentially—the first character is sent first, and the last one last, and that's how they appear on the screen. The character-attribute data is sent along with the alpha-graphic data. That means that when an attribute (such as color), is changed, a pixel (picture element) is sacrificed and nothing is seen in the space that would otherwise be occupied by a character. Because one character or control element follows the other, the system is known as serial-attribute transmission.

(Editor's note—*This is known as Level-1 Prestel. There are a total of five levels of Prestel, each more advanced than the previous one. Level 1, while the most "primitive," is also the most common at this stage. The proposal before the FCC includes all five levels.*)

Alpha-graphics are sent using the ASCII (American Standard Code for

*President, Richard Larratt and Associates Inc.

Videotex for TV—

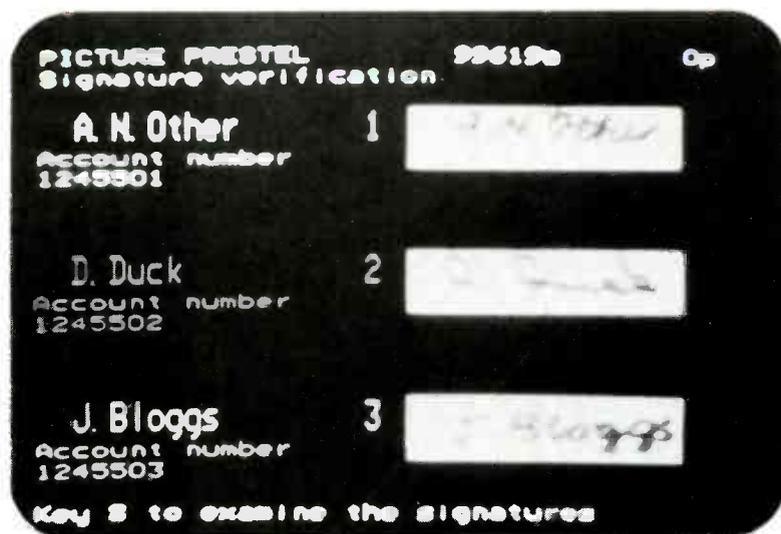

How it works

Videotex has several levels of alphanumeric and graphics capabilities. Here's a discussion of how they work, as well as a look at videotex's future.

RICHARD LARRATT, M.A., P. Eng.*

Information Interchange) code—the one that is used by most computers. In it, each character is represented by a 7-bit word. For example, the letter "A" is represented by the decimal value 65, and a space by the decimal value 32. Since the information is transmitted in digital form, the "A" becomes "1000001," and the space "0100000." Table 1 shows videotex alphanumeric characters and their ASCII values. A switchable control byte allows the same numbers to be used to obtain other characters.

In the simplest forms of videotex (see Fig. 5 in Part 1 of this series in the November 1981 issue of *Radio-Electronics*) the ASCII data is sent to a character-generator ROM. That IC contains the information needed to display all the letters and graphic symbols

required by the system. When it is fed an ASCII value, it responds by outputting the dot pattern needed to form the character on the video display.

DRCS

The next step up in videotex technology calls for the use of a DRCS (Dynamically Redefinable Character Set). The DRCS allows the use of more graphics elements than are contained in the character-generator ROM. A videotex decoder equipped for DRCS's must contain some RAM. That memory stores the DRCS downloaded from the videotex computer over the air (or cable) and in effect acts as a secondary character-generator ROM. An example of videotex graphics using a

DRCS is shown in Fig. 15.

In addition to providing enhanced graphics, DRCS's allow the use of special alphabets, such as Greek or Hebrew, to transfer mathematical data or for foreign-language captioning.

PDI's

PDI's (Picture Description Instructions) allow the supplier of videotex information even more flexibility. Table 2 shows the PDI's described in the North American Broadcast Teletext Standard proposal. Once they are downloaded into the decoder's memory, they make possible very complex graphics with very little effort. For instance, the LINE PDI could be used to instruct the decoder to draw a "...LINE from here to there..."

Once the PDI's are loaded into memory, they make possible a wide variety of high-quality graphics, such as the illustration shown in Fig. 16.

PDI's also require RAM (typically 16K) but can make a PDI-equipped decoder worth its expense when graphics are of the essence.

Alpha-photographic

An example of alpha-photographic videotex is shown in Fig. 17. Alpha-photographic videotex allows the transmission not only of text, but also of still

TABLE 1

Decimal	Binary	Character	Decimal	Binary	Character	Decimal	Binary	Character
32	0100000	SPACE	96	1100000		64	1000000	@
33	0100001	!	97	1100001	a	65	1000001	A
34	0100010	"	98	1100010	b	66	1000010	B
35	0100011	#	99	1100011	c	67	1000011	C
36	0100100	\$	100	1100100	d	68	1000100	D
37	0100101	%	101	1100101	e	69	1000101	E
38	0100110	&	102	1100110	f	70	1000110	F
39	0100111	'	103	1100111	g	71	1000111	G
40	0101000	(104	1101000	h	72	1001000	H
41	0101001)	105	1101001	i	73	1001001	I
42	0101010	*	106	1101010	j	74	1001010	J
43	0101011	+	107	1101011	k	75	1001011	K
44	0101100	,	108	1101100	l	75	1001100	L
45	0101101	-	109	1101101	m	77	1001101	M
46	0101110	.	110	1101110	n	78	1001110	N
47	0101111	/	111	1101111	o	79	1001111	O
48	0110000	0	112	1110000	p	80	1010000	P
49	0110001	1	113	1110001	q	81	1010001	Q
50	0110010	2	114	1110010	r	82	1010010	R
51	0110011	3	115	1110011	s	83	1010011	S
52	0110100	4	116	1110100	t	84	1010100	T
53	0110101	5	117	1110101	u	85	1010101	U
54	0110110	6	118	1110110	v	86	1010110	V
55	0110111	7	119	1110111	w	87	1010111	W
56	0111000	8	120	1111000	x	88	1011000	X
57	0111001	9	121	1111001	y	89	1011001	Y
58	0111010	:	122	1111010	z	90	1011010	Z
59	0111011	;	123	1111011	}	91	1011011	[
60	0111100	<	124	1111100		92	1011100	\
61	0111101	=	125	1111101	~	93	1011101]
62	0111110	>	126	1111110	~	94	1011110	^
63	0111111	?	127	1111111	DELETE	95	1011111	_

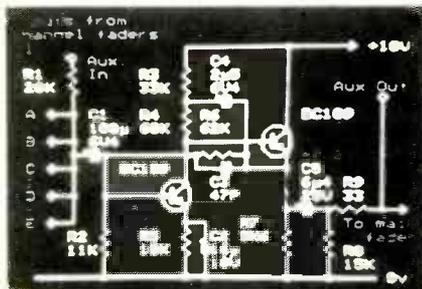


FIG. 15—A DYNAMICALLY REDEFINABLE character set (DRCS) makes the presentation of pictures such as this schematic relatively easy.

video frames—something that will be very important when shopping-by-videotex becomes widespread and the buyer wants to see not a drawing, but a real picture of the item he is interested in.

Figure 10 in the December 1981 issue of *Radio-Electronics* shows an alpha-photographic system. Several layers of RAM are overlaid, and their contents taken as a whole to provide varying brightness levels, which are not available in less sophisticated forms of videotex. As an example, let's look at bit-1 of each of the four planes of RAM shown in that figure. If we consider the four planes together, we can build values ranging from 0 to 15, depending on whether the bits are "1" or "0". That means that each pixel can be assigned one of sixteen brightness levels, if the values are converted into

TABLE 2

TEXT:	Present a string (group) of characters.
POINT:	Set the position for a point and, if requested, draw it.
LINE:	Draw a line using its end-points as starting and stopping coordinates.
ARC:	Draw a circular arc using three sets of coordinates (any circle or part of a circle can be defined by three points).
RECTANGLE:	Draw a rectangle of a specific height and width.
POLYGON:	Draw a polygon based on the coordinates of its vertex points.
BIT:	Produce an image using bit-mapped graphics.
CONTROL:	Provide control over the modes of the drawing commands.

voltages that will control the electron beam of the video display.

Scanned sequentially, the contents of the bit-plane memory will appear as a series of brighter or darker pixels—a photograph! Even color is possible.

Of course, there is a tradeoff involved. Depending on the baud rate at which the data is sent, it can take several seconds for the picture to be

completed. (Actually, that process would not be apparent to the user because the data would be loaded into RAM and not displayed until everything was present.) That's one reason why the "photograph" in Fig. 17 fills only part of the screen—a small picture requires less memory and can be transmitted and displayed more quickly (about two seconds for the one shown). Despite its apparent disadvantages, though, alpha-photographic videotex can be quite useful.

Which is best?

We've presented several levels of videotex—alpha-mosaic, alpha-geometric, and alpha-photographic. Which one is going to win out?

That's difficult to say. Eventually, of course, we'll be using the alpha-photographic mode, and every level below it. For the immediate future, however, we are faced with a conflict between a rather simple (although technically sophisticated) alpha-mosaic system, typified by Level-1 Prestel, and a more expressive but more complex—and, initially, more expensive—alpha-geometric system of the Antiope/Telidon-type.

Proponents of both systems have petitioned the FCC for acceptance of their method as the North American standard. Those backing the Prestel system claim that it is simple, inexpensive, and has a proven history.

Those in favor of the Antiope/Telidon

system say that its flexibility outweighs its apparent complexity, and that component prices will decrease rapidly once it is accepted and decoders are produced in volume.

At the moment, the decision lies with the FCC. Recent developments in FCC policy, however, indicate that the ultimate decision may be up to the user: both systems may be allowed, and the winner will be the one with the most subscribers. It's even possible that the two systems will coexist, one in some areas, and one in others.

That, however, invokes memories of "quad" sound, and the controversy and confusion that surrounded it before it more or less disappeared. Whatever the outcome, videotex—in one form or another—will be with us, and will make life a bit simpler and more rewarding.

Using videotex

Let's take a look at a not-so-hypothetical videotex system. We'll assume that the system used is that proposed to be the North American Broadcast Standard and that the videotex data is being sent over the air on two lines of the vertical-blanking interval. The equipment involved is an ordinary television receiver equipped with a videotex decoder and a small numeric keypad like a *Touch-Tone* pad. Also attached to the decoder is a modem, through which information can be sent back by telephone to the videotex computer.

A good videotex information-system will be constructed like an onion—the outside layer of information will be general. More detailed information can be obtained by requesting pages indicated by the first level. Still *more* detailed information will be available by selecting pages indicated by the second level. Also available will be an alphabetical directory—it might tell you that the page numbers for categories beginning with the letters "VAA" through "ZZZ" can be found on page number such-and-such.

Let's assume that you want to make an airline reservation from New York to San Francisco. The first thing you will do will be to find out what page carries airline information. Upon entering the page number, a directory to various airlines will appear on the screen within about 10 seconds.

When the airline you select appears on the screen, it may present a menu showing the cities served, with each city identified by a number. By keying in that number, you will find another page showing the line's flights to that city, and possibly the status of each flight ("BOOKED FULL," "STANDBY ONLY," or even "SEATS AVAILABLE").

By keying in the number associated with the flight you want, a menu will be presented for you to "fill out" to make



FIG. 16—PDI's (Picture Description Instructions) allow very complex graphics to be generated.



FIG. 17—THE ALPHA-PHOTOGRAPHIC mode allows photographs to be included as part of the videotex material. The picture shown took about two seconds to transmit.

your reservation and, at that time, you will be instructed to set up your telephone link to transit that information to the videotex or airline computer.

You'll be asked for your videotex account number, which may be reconfirmed on the screen. That not only automatically tells the airline just who is buying the ticket, but can also be used for direct-billing purposes. You'll then fill in the blanks on the screen to indicate how many people will be traveling, what class of service is desired, departure date, etc.

Finally, you will be given the option of committing yourself to that reservation, or—and sometimes more important—simply telling the computer to forget the whole matter.

Getting detailed news would also be done through a series of ever-more-detailed menus. The first page would be an index by subject ("WORLD," "NATIONAL," "SPORTS," "COMICS," etc.) and would also contain the latest headlines. By unpeeling layers of the information "onion," you could scan the items of interest to you, or read about them at length.

Who pays for it?

There's no such thing as a free lunch. Videotex equipment is not cheap, and the time that goes into programming the system also costs money. Where does the money come from?

In some instances, the company selling a service or product (such as an airline) pays out of its own pocket—it's probably less expensive than running a

sales office. In other cases, such as financial reports like the Dow Jones index, a charge of 10 or 25 cents would be made to your account each time you accessed the service, or you would be billed for the time that you used.

Finally, to encourage the use of the system, some services, like news headlines or weather, might be provided without charge. After all, if you're going to use your videotex terminal for that, you'll also eventually find yourself using it for services that you (or someone else) pays for.

How we'll use it

Technically, videotex is quite an achievement. What, though, will it do for you? Some ideas were presented above; here are a few more.

Initially, interactive videotex—where the user can communicate with the service—will be limited. Broadcast videotex, using a full video-frame occupying all of a TV channel will predominate, presenting a continuously scrolling display of information. But the viewer will have no opportunity to take advantage of it, except as a non-selective information source.

At the beginning, interactive videotex will probably be available at selected public terminals (in airports, offices, and other places where its capabilities can justify the initial expense).

Our world, though, is changing. We are, more and more, becoming a "wired society." Right now that pertains primarily to telephone service—you can speak to anyone in the world for what would have been considered, a few years ago, a ridiculously low price.

Now, cable-TV is becoming a part of our lives and, if one channel were used to receive videotex information, and another to transmit multiplexed viewer response (at a relatively low-data-rate), interactive videotex over cable could easily become a reality.


In the near future we'll see two more developments that will further the interactive aspect of videotex.

The first is fiber optics. By using light, rather than RF, as a transmission medium, it will be possible to have an almost unlimited number of channels for information interchange. Fiber optics, using hair-thin transparent light-guides instead of cables, is their logical replacement. We'll be seeing a lot more of that technology soon.

The second could very well be DBS (Direct Broadcast Satellites). They could replace *any* wired—or light-piped—information service and, although it may take a while, they may become two-way. Not only would you be able to receive the programs or data they sent, but a relatively-low-power transmitter might transmit *your* information into the system.

continued on page 103

HOW IT WORKS

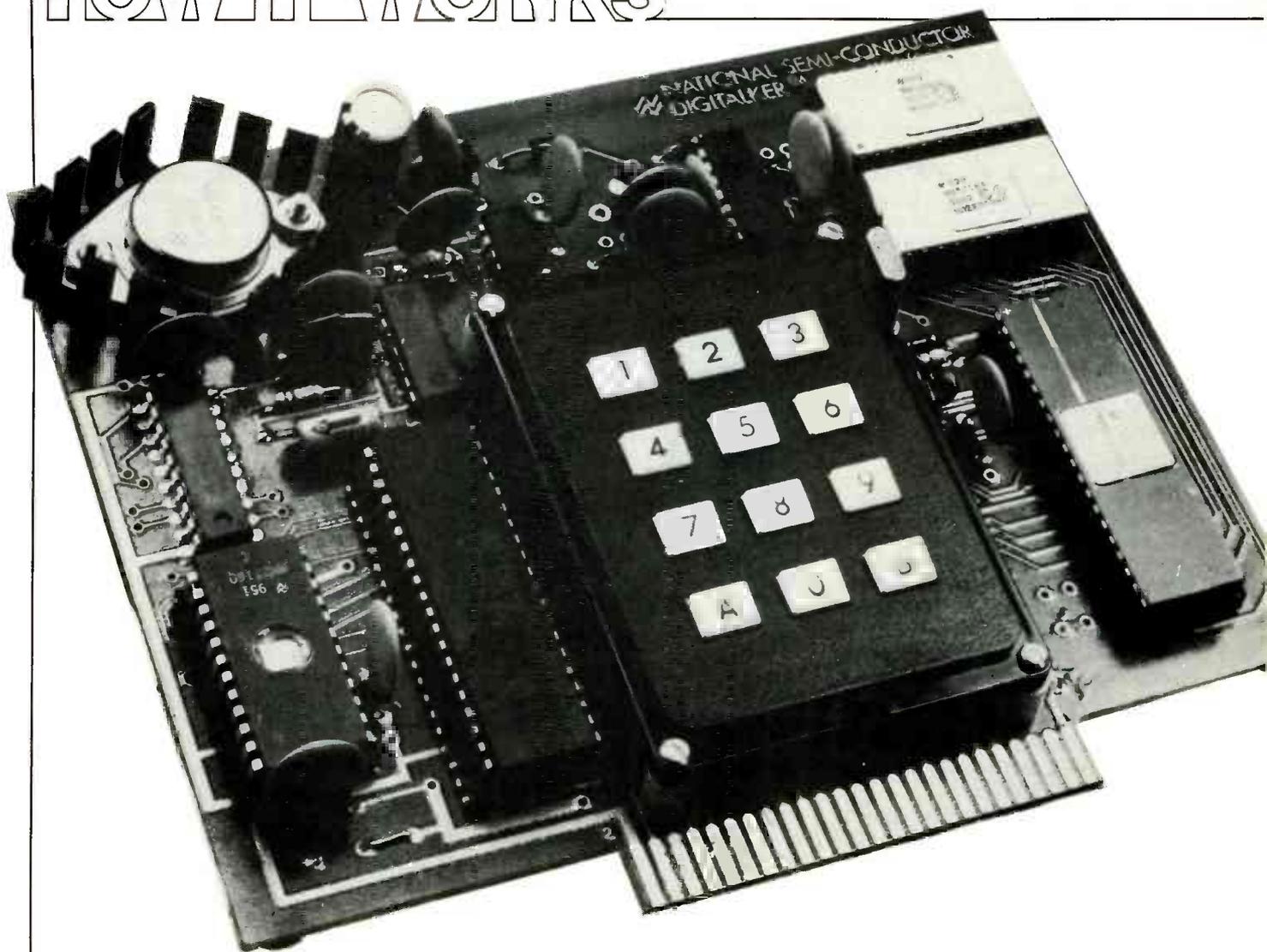

SPEECH SYNTHESIS Techniques

KARL SAVON

Electronic speech-synthesis has come a long way from the Voder, which took seven people to operate when it was demonstrated at the 1939 N. Y. World's Fair. Now all you need are a couple of IC's.

SPEECH SYNTHESIS—THE ARTIFICIAL generation of that series of sounds known as "speech"—has advanced beyond the novelty stage to become a real alternative to the simple audible and visible indicators and displays common to so much of our society. There is very little you can do with a light or buzzer that can't be done better with a "spoken" word.

"Toys" such as Texas Instruments' *Speak & Spell* have been recognized as effective learning tools. Through the electronics mouths of those machines, children are exposed to new words in an exciting interactive way. Talking calculators and timepieces have expanded the horizons for the blind; pilots and drivers are relieved of the need to watch their meters and gauges continu-

ously; alarms can be given with instructions as to what actions should be taken. Speech-synthesis devices are finding a myriad uses in communications, appliances, automotive applications, clocks, instrumentation, language translators, and annunciators. It is estimated that the speech-synthesis market will grow to hundreds of millions of dollars in the next five years.

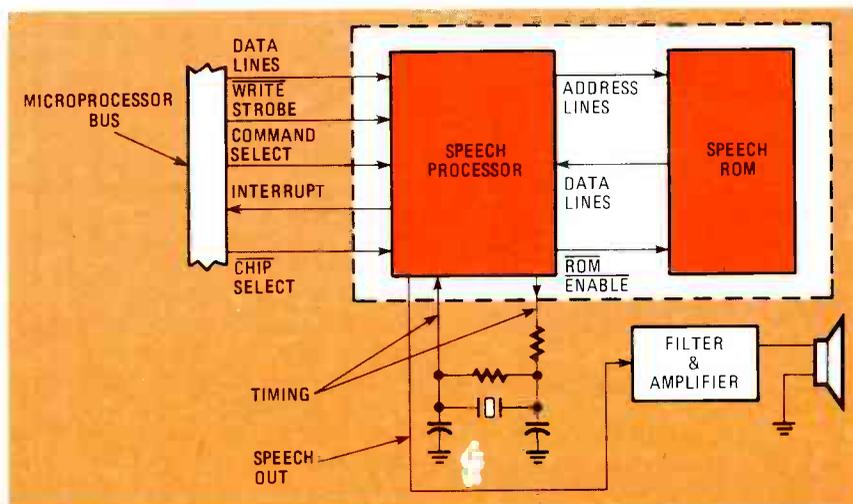


FIG. 1—A TYPICAL IC SPEECH-SYNTHESIZER uses a ROM containing speech data, circuitry to process the data and turn it into analog form, and an amplifier and speaker.

Fundamentals

Human speech begins in the cortex of the brain but, so far, that *creative* process has been imitated only crudely. The *mechanics* of speech, though, have been simulated with uncanny precision.

The human speech process begins in the lungs and proceeds through the larynx to create the noises and tones that correspond respectively to *unvoiced* and *voiced* human speech output. The wideband hissing "s", "f," and "sh" are unvoiced sounds, created by the random flow of air particles through the voice tract, but the voiced consonants like "b" and "l" are constructed of discrete narrowband frequencies; the vibrating vocal cords generate the voiced sounds. *Fricatives* like "v" and "z" combine the two types of sources and the *plosives*, such as "p," "t" and "k" are produced by the controlled release of air from the mouth.

The speech process is completed by articulation—changing the shape of the throat, and the shape and positioning of the teeth, tongue, palate and lips. Together, those parts of the mouth and respiratory system form an adaptive filter that alters the resonances of the vocal tract.

While there are more similarities than differences among the approaches to speech synthesis, they can be separated into three general groups: direct waveform-digitization, phoneme synthesis, and linear-predictive coding.

Direct waveform-digitization

Direct waveform-digitization is the process of taking a live or recorded speech-waveform and passing it through an analog-to-digital converter. The final quality of the reconstructed speech (obtained by passing the digitized data through a digital-to-analog converter) depends on several factors, including the rate at which the speech waveform is sampled (how many times each second the waveform is "looked at" and its value digitized) and the number of amplitude levels into which it is segmented. As the number of levels increases, more information must be processed and stored in memory; as the number of levels decreases the memory and processing requirements decrease—at the expense of intelligibility.

It is necessary to sample the waveform at a frequency that is at least twice as high as the highest frequency in the original waveform. If the sampling frequency is too low, *aliasing*, which causes the higher frequencies to appear falsely as lower frequencies, takes place.

Playback of the digitized signal is (in theory) a simple matter of recalling the sequences of data stored in memory and processing them with a digital-to-analog converter.

Direct waveform-digitization of human speech is highly redundant; it wastes a lot of memory storing, for example, drawn-out sounds like "oooooh."

Methods used to reduce the memory requirements and rate of processing of redundant information may actually cause this synthesis technique to be classified in one of the other simulation groups.

National Semiconductor (2900 Semiconductor Dr., Santa Clara, CA 95051) uses a direct-digitization method that reconstructs the speech using pulse-coded modulation. It calls its system the *Digitaltalker*. Compressed speech data is stored along with frequency and amplitude information in a read-only-memory (ROM). Figure 1 shows a typical configuration connected to a microprocessor bus complete with an output filter, amplifier, and speaker. Figure 2 shows a block diagram of the speech processor chip, referred to as the SPC.

It cannot be overemphasized that the key to the practicality of this, as well as the other systems, is *speech-compression*—coding of the signals that minimizes the redundant information. National points out that its system produces speech quality far better than the crude sound you may associate with early demonstrations of speech digitization. In terms of memory space, the result is that male voices require about 100 bits per word and female voices somewhat more. The system is more like a digital recorder that digitizes actual voices, stores, and then plays back, than the other methods which model the vocal tract.

The compression method combines three techniques. First, redundant pitch periods are removed. Then, adaptive delta-modulation, which uses the difference between two successive sampling points rather than the values at those points, is used to conserve memory space by storing only the difference information. Phase adjustments and half-period zeroing, remove the "direction" component of the waveform; that information is not needed for intelligibility, so can be safely done away with. Computer processing is used to accomplish the compression. National claims that its compression scheme, combined with waveform digitization, is very competitive with other systems, including linear-predictive coding.

The *Digitaltalker* is programmed with control information that instructs it how many times to repeat a specific waveform. A programmable frequency-generator is used to add inflection. The system is easy to use because it requires only a start pulse and an 8-bit address to trigger any message. Simple switches can be used if a microproces-

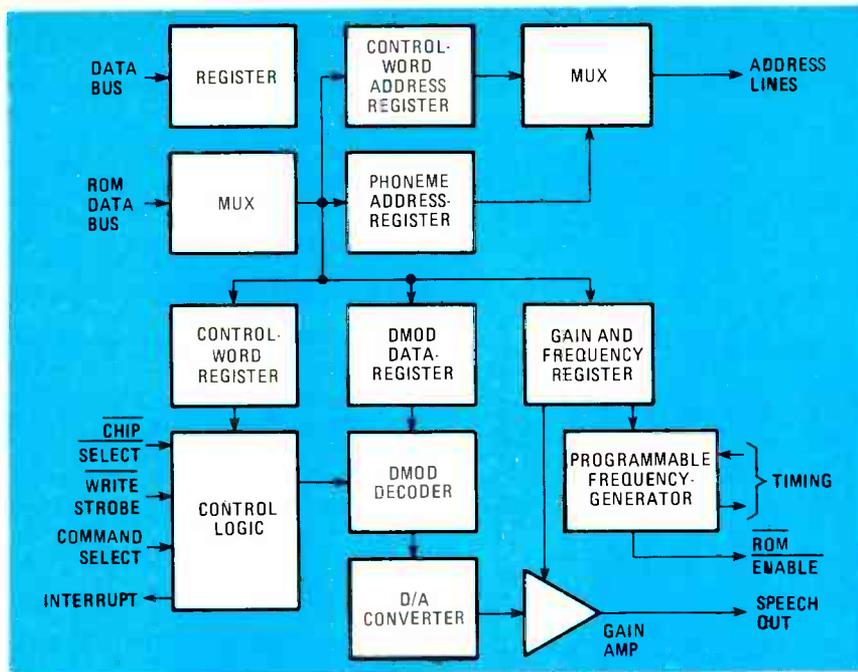


FIG. 2—NATIONAL SEMICONDUCTOR'S DIGITALKER has a fixed vocabulary in ROM; several different ROM's are available. Programmable frequency-generator (lower right) is used to add inflection to speech.

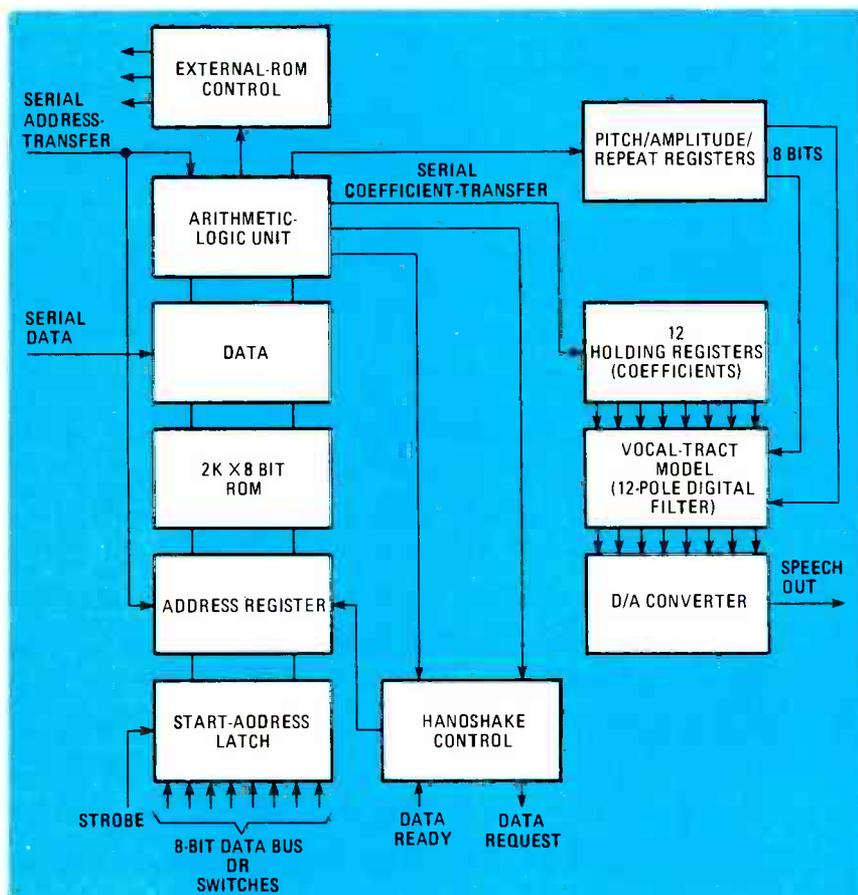


FIG. 3—A PHONEME-BASED synthesizer, such as General Instruments' SP0256, uses the sound elements that make up words to provide an almost unlimited vocabulary.

pin edge connector. A demonstration package is available with a vocabulary aimed at several industrial markets. The 5×6 -inch DT1000 evaluation board is priced at \$495. The DT1050 three-piece IC set is \$85. Write directly to National Semiconductor for more information.

Phoneme synthesis

Phoneme synthesis works by combining basic sound elements (phonemes) that are made up into complete words and sentences. In theory, any spoken word can be synthesized by stringing phonemes together. The quality of the resulting speech depends on the extent of the phoneme library. To cover a wide range of inflection requires a correspondingly large number of phonemes. Again, compromise is necessary to put together a practical system; redundancy-elimination coding techniques are used.

The phoneme method is particularly suitable when the extent or type of vocabulary required is not fixed: When there is no definite vocabulary list, speech cannot be constructed from stored words and phrases but must be generated from the more elemental phoneme sounds.

General Instruments (600 W. John St., Hicksville, NY 11802) has taken the approach just described, combining phoneme synthesis with a digital filter. The design is versatile enough to operate in a linear-predictive filter mode (more about that shortly). GI has released a product specification that describes the SP0256 speech-processor IC; it is an LSI n-channel metal-gate device that can synthesize up to 256 sound sequences.

Figure 3 shows a block diagram of the processor. The speech process is started by addressing the ROM location that contains the phoneme desired. Up to 256 phonemes can be stored in the 16K bits of the on-board ROM, but that can be extended to as many as 3825 phonemes (or, more usually, complete words or phrases) through the addition of up to 491K bits of ROM.

The device includes a controller and a vocal-tract model (VTM). The VTM is a digital filter similar to that used in linear-predictive coding. The system generates complex sound-sequences under the control of 15 slowly varying parameters including: repeat count, pitch period, source amplitude, and 13 digital filter-coefficients. The controller is a sequential processor that gets its instructions and data from the ROM and alters the contents of the 15 parameter-registers controlling the VTM.

One-byte inputs specify 256 entry points. The entry points in the internal ROM are spaced by 8-byte increments, meaning that each phoneme can be defined by 8 bytes (64 bits). Expanding

processor controller is not justified. One *Digital* device can produce up to 256 different messages.

An evaluation board is available which includes the NMOS speech-pro-

cessor IC, two speech ROM's containing 138 words, and an erasable programmable ROM (EPROM). The DT1000 board can be connected to an external control-system through a 22-

the input format to 2 bytes increases the number of entry points to 3825, assuming that the full complement of ROM has been added. The controller has 16 executable instructions and supports one level of subroutine nesting. JMP (*JuMP*) and JSR (*Jump to Sub-Routine*) instructions are included to allow chaining of program segments and the reuse of code sequences.

External ROM interfaces to the speech-processor device through serial input and output lines. Sixteen-bit serial addresses are used for addressing. Serial-to-parallel conversion is handled internally by the SP0256. The analog output is developed by a 7-bit pulse-width modulation, digital-to-analog converter. The output is passed through a 5-kHz-cutoff low-pass filter and is then amplified externally. The single-unit price for the SP0256 is \$26.70. The price will probably be even lower from a General Instruments distributor.

Votrax's phoneme system

Votrax, Div. of Federal Screw Works (500 Stephenson Highway, Troy, MI 48084) offers another phoneme-based system. Votrax uses a switched capacitor filter in its CMOS-technology SC-01 LSI integrated circuit. Phonemes require an average of 6 bits and each phoneme is 40 to 200 milliseconds long. The device has a 64-phoneme library accessed by a 6-bit code. Typical speech-data uses 70 bits per second. Votrax plans to provide a text-to-phoneme translator algorithm that will let the user do his own programming. Figure 4 shows a block diagram of the system. The price of the SC-01 is \$55.00 each in quantities of five (single units may be available from distributors).

Linear-predictive coding

Linear-predictive coding—used extensively by Texas Instruments (P.O. Box 225012, Dallas, TX 75265)—is a combination of techniques that model the vocal tract electronically. Noise and tonal sources generate signals that are processed by the LPC filter. The method derives its name from the fact that it predicts the parameters of the next speech sample using a linear combination of the preceding speech samples. That results in a major reduction in the amount of memory required for the storage of speech data.

Speech-synthesis techniques using that method require as few as three integrated circuits: a digital lattice-filter, a ROM, and a controller. Present systems are based on the 10-stage filter shown in Fig. 5; its output is set by pitch, amplitude, and filter coefficients.

The lattice-filter structure includes multiplication, summation, and delay blocks. Digital filters are constructed of memory-register delay components, and of summers and multipliers con-

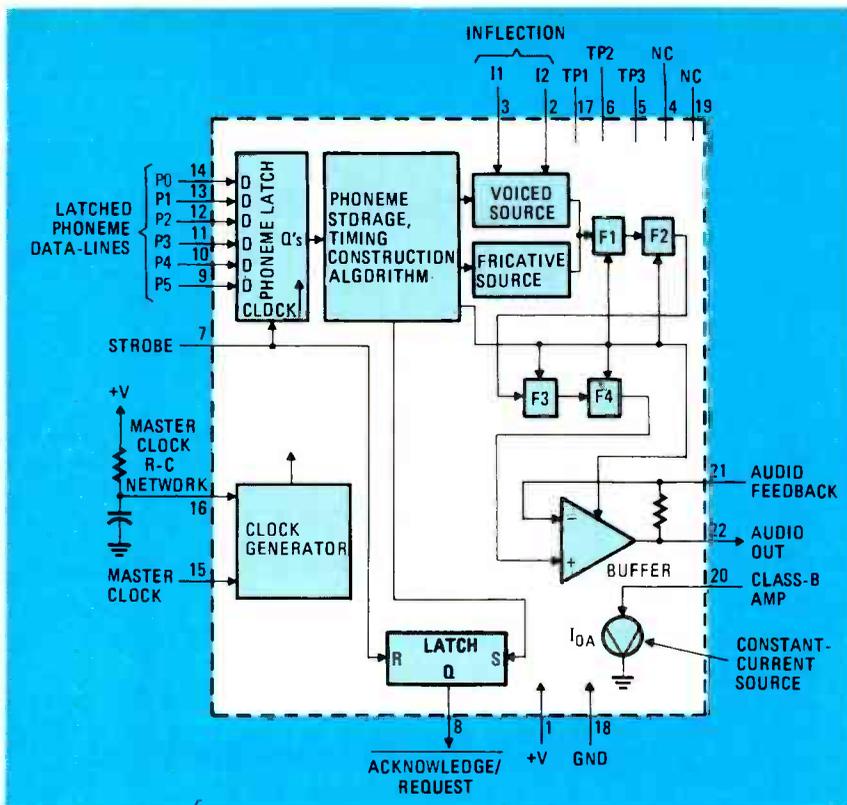


FIG. 4—VOTRAX'S SC-01 is a single-IC, phoneme-type, speech synthesizer intended for computer control.

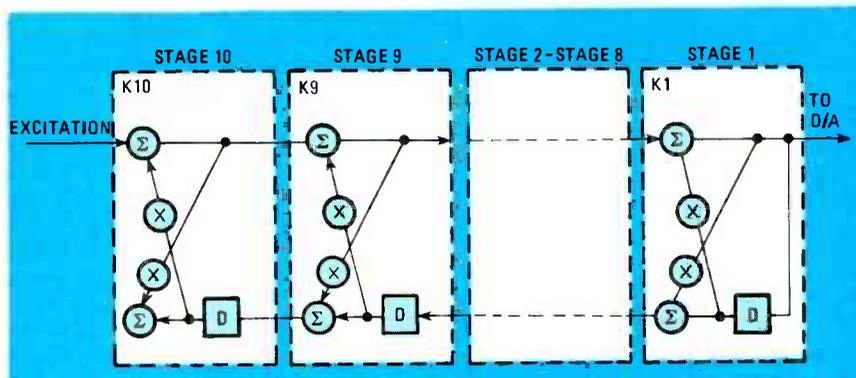


FIG. 5—TEN-STAGE LATTICE FILTER used in Texas Instruments' linear-predictive-coding synthesizer simulates the resonant effects of the mouth and nasal cavities.

nected in either feedback or nonrecursive, direct path configurations. Multiplication takes longer than addition, so pipeline techniques are used to synchronize the filter's operation to the sampling rate of the system. The all-pole filter is described by the equation:

$$H_z = \frac{G}{1 - \sum_{k=1}^{10} a_k z^{-k}}$$

The a_k terms are the ten filter-coefficients, G is a gain factor, and the z^{-k} terms represent time delays.

The voice-synthesis processor performs about 400,000 multiplications and additions each second. A frame (complete set of speech data) is supplied to it about every 25 milliseconds. Data from

adjacent frames is interpolated about every 3 milliseconds to generate a smooth output. Once again a tradeoff is made among flexibility, fixed or variable vocabulary, speech quality, and cost-per-second of speech output.

A computer program is used to produce an optimal set of coefficients for the vocal tract filter, the 8-bit energy and pitch information, and to generate the one-bit repeat codes. A technician corrects any audible deficiencies.


Texas Instruments' TMS5100 speech-processing computer, which includes a 50-milliwatt power amplifier, is a key component in its speech-synthesis line. The TMS5220 is designed for easy 8-bit data bus interface. It is used in the TI-99/4 home computer speech-synthesizer peripheral. Single-unit prices for the TMS5100 and TMS5220 are \$32.00 and \$48.00 respectively.

R-E

SAFE SUB-WOOFER

A subwoofer allows your sound system to reproduce very-low bass, such as that found in organ recordings. This SAFE subwoofer may be small, but it's mighty where it counts.

GEORGE PAPPANIKOLAOU

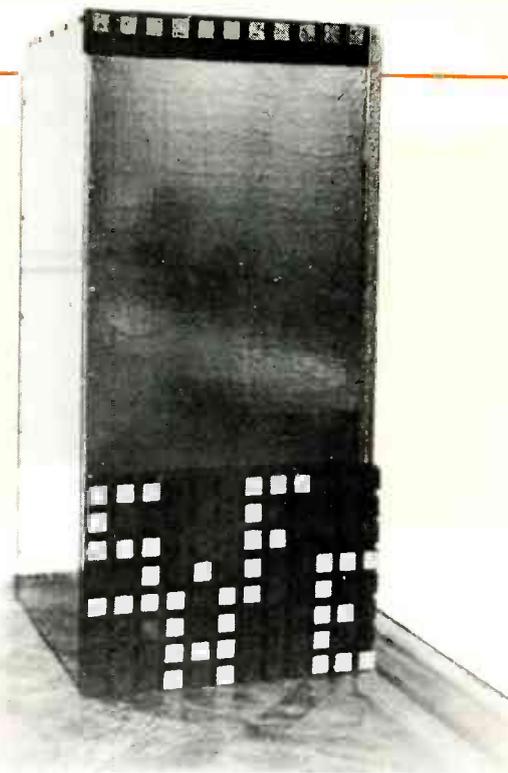

IN THE DECEMBER 1981 ISSUE, **RADIO-ELECTRONICS** PUBLISHED plans for constructing a speaker that used the SAFE (Symmetrical Air Friction Enclosure) principle (U.S. patent no. 4,168,761, other patents pending) to obtain good sound from a small enclosure. This article deal with a companion subwoofer using the SAFE principle that provides extended bass response from a relatively small enclosure.

The heart of the system is an 8- or 10-inch speaker in a cabinet with a volume of under six cubic feet. It uses no special devices, such as passive radiators, to increase the effective size of the speaker, and the SAFE design provides an extremely rigid enclosure.

The SAFE principle

The SAFE principle is an outgrowth of the labyrinth-type enclosure invented by Benjamin Olney in the 1930's. A labyrinth-type enclosure is simply a long tube placed behind a speaker and into which the low-frequency back wave from the speaker is propagated. The length of the tube is used to

provide "reflex action," causing the back wave to emerge from the tube in phase with the front wave. This boosts the low-frequency output of the system over a specific range of frequencies. The longer the effective length of the tube, the lower the frequencies that will be boosted.

The reason for using the term "effective length" is that friction between the air set in motion by the speaker and the internal surface of the labyrinth causes the velocity of the back wave to be decreased and making it take longer to pass through the tube than would be the case if there were no friction. The fact that it takes the sound wave longer to transverse the labyrinth than it normally would, makes it appear that the wave has traveled a longer path than it actually did.

Two methods commonly used to increase effective length of the labyrinth are to line its interior with acoustic padding such as fiberglass, or to completely fill it with the same material.

Many designs usually fold the tube (run it back and forth instead of in straight line) to keep the size of the enclosure

R-E TESTS IT

LEN FELDMAN
CONTRIBUTING HI-FI EDITOR

WE PUT AN EIGHT-INCH SAFE SUBWOOFER through extensive listening tests in our laboratory and also subjected it to several measurements. We drove it using an amplifier rated at about 40-watts-per-channel and a passive crossover network.

Based on our sensitivity measurements, we would classify this speaker as being low-to-medium in efficiency (an electronic crossover would have helped). Nonetheless, we noted a fundamental output from the subwoofer down to 25 Hz. We measured relatively uniform response from the system from 30 Hz up to

the 100-Hz cutoff frequency and were able to produce sound-pressure levels in excess of 100-dB SPL before any significant doubling or distortion was observed.

The unit was tested using both single-tone signals and musical material. In reproducing the music, the improvement in bass reproduction was apparent only when the program source contained a fair amount of low-bass energy. Not too many program sources do, but when you find one that *does*, the added impact of the low, low bass contributed by the subwoofer made the project decidedly worthwhile.

One word of caution. Trying to reproduce ultra-low bass in a small

room can prove to be a frustrating experience. Standing waves set up in the room are responsible for that, and it is possible to move about the room and hear thunderous bass in one location while hearing virtually none in another spot, where virtually complete cancellation of bass frequencies takes place.

We used close-miking techniques in our sound-pressure measurements, placing the microphone both at the upper back-wave ports of the enclosure and at close proximity to the driver itself. Below 40 to 50 Hz, most of the energy, as might have been expected, came from the back-wave ports rather than from the front of the woofer. **R-E**

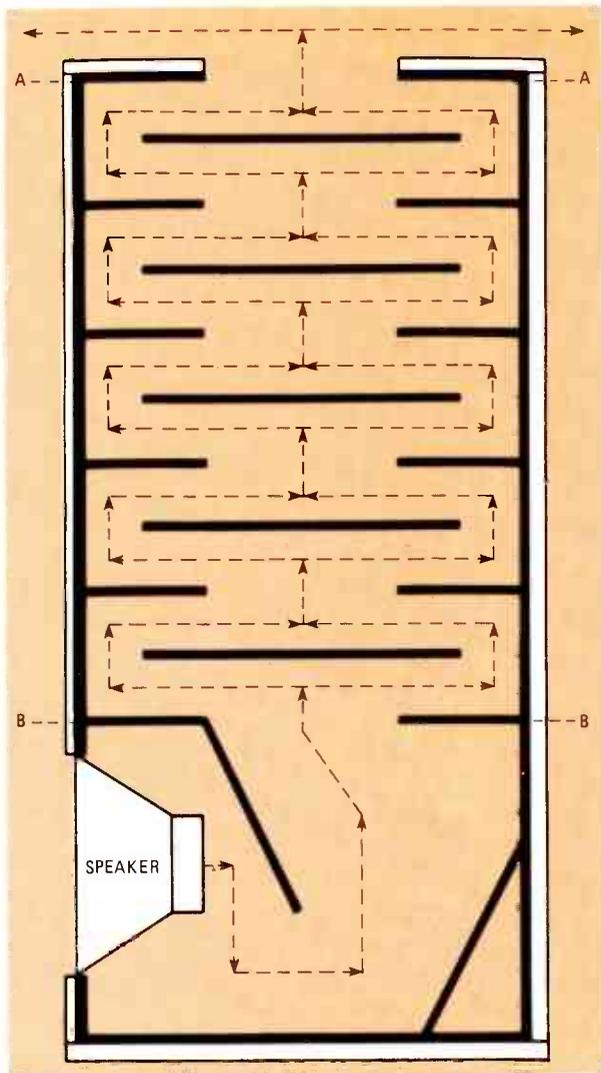


FIG. 1—SIDE VIEW OF SAFE ENCLOSURE showing speaker back-wave path. Path is symmetrical between points A and B.

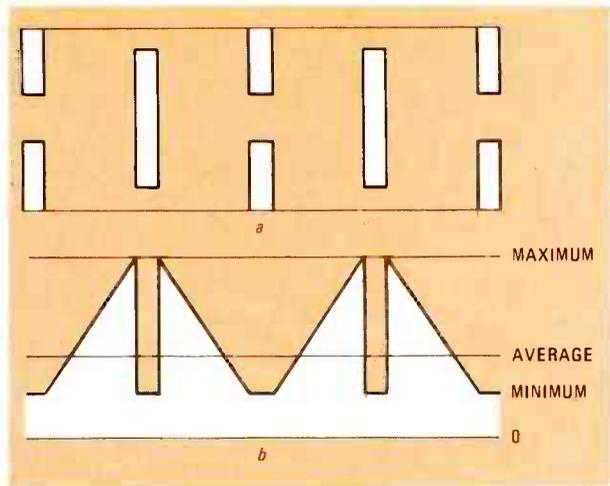


FIG. 3—PARTITIONS USED IN SAFE ENCLOSURE (a) affect its effective cross-sectional area (b).

down. Also, the effective length of the tube and the free-air resonance of the speaker are chosen so that the speaker is damped at its free-air-resonance frequency, avoiding objectionable excess output at that frequency.

There are, however, two other factors that can be used to increase air friction, and thereby the effective length of the labyrinth. These factors are what's involved in the SAFE principle. First, the internal surface-area—not the length—of the tube can be increased; second, the back-wave path can be made longer by increasing the number of bends in it.

A SAFE enclosure uses a number of small chambers in series (see Fig. 1) to both increase the internal surface-area and to insert more bends in the path of the speaker back-wave. The small chambers are constructed by alternating two types of partitions within the tube as shown in Fig. 2. The first type completely blocks the tube, except for a square hole in its center. The second is smaller and is centered so that the area between it and the inside perimeter of the tube is equal to that of the hole in the first type. This forces the back-wave from the speaker to be alternately spread out and combined as it passes through and around the tube. (It is obvious that this design increases the internal surface-area of the tube and

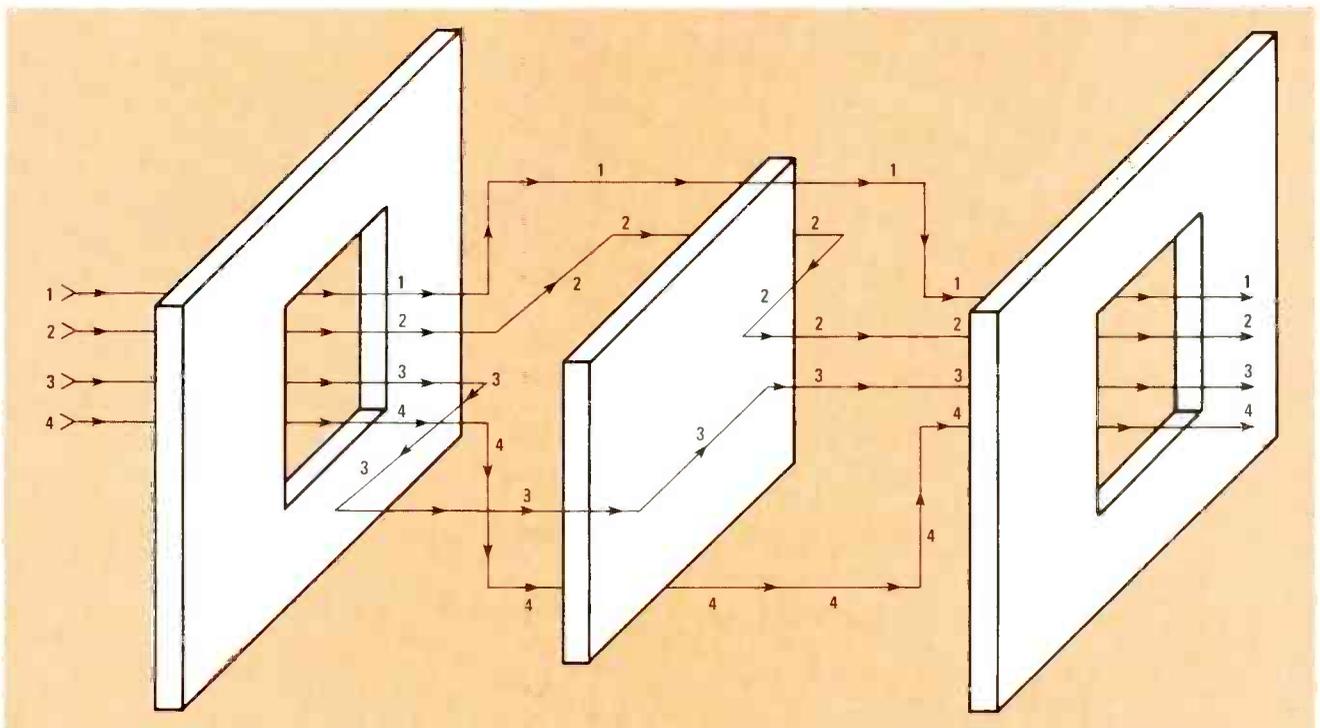


FIG. 2—SPEAKER BACK-WAVE is alternately combined and separated as it passes through and around SAFE enclosure's baffles.

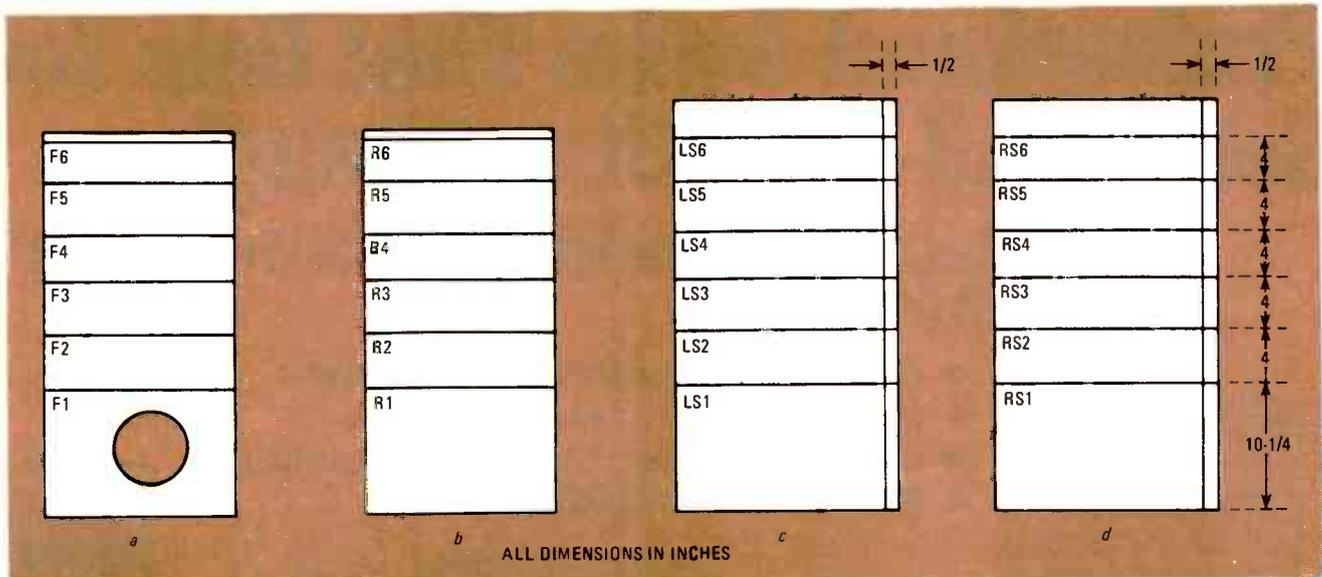


FIG. 8—PARTITION MOUNTING STRIPS for the front are shown in (a), rear are shown in (b), left side are shown in (c) and right side are shown in (d).

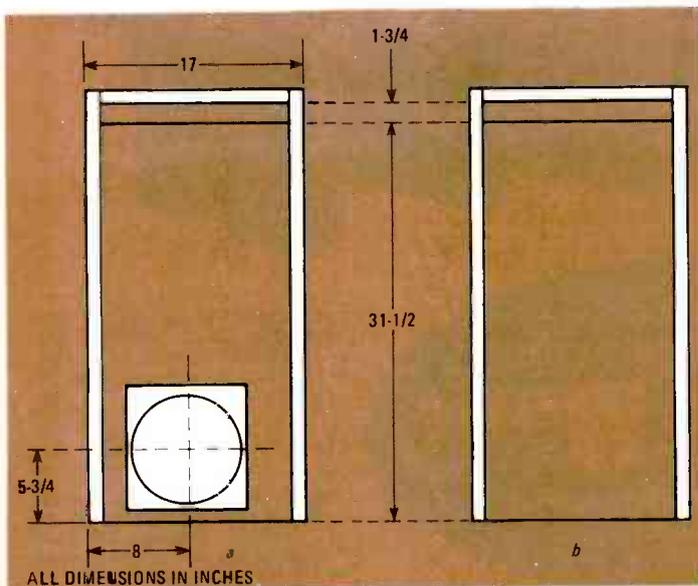


FIG. 9—SPEAKER SHOULD BE MOUNTED slightly off-center to prevent standing waves. Center figure shows distance between partition 1 and top of enclosure.

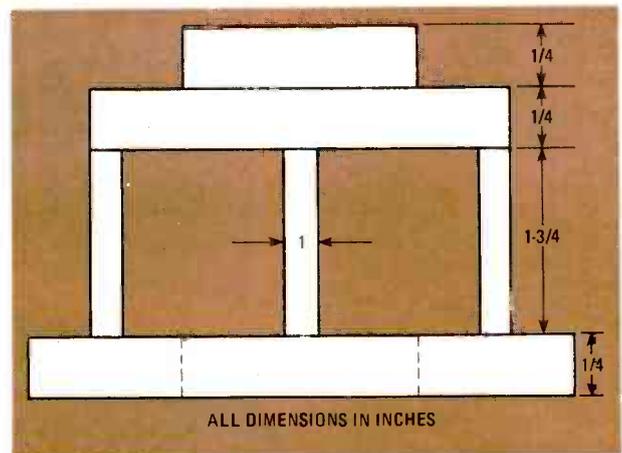


FIG. 11—SIDE VIEW of even-numbered partition mounted atop odd-numbered partition using partition mounting strips. Each strip is located as shown in Fig. 10 and measures 1 x 1 x 1/4 inches.

sirable), is not as effective as one that provides reflex action and does not increase the speaker's free-air resonance.

The SAFE subwoofer enclosure is designed so that it does not significantly restrict the action of an 8-inch speaker (which would increase its free-air resonant frequency) while providing good reflex action. A 10-inch speaker can also be used. A 10-inch speaker would offer the advantage of increased power-handling capacity and, perhaps, better efficiency.

Construction

The choice of a speaker is not critical. Almost any 8- or 10-inch open-frame woofer will do; an 8-inch unit should have a ceramic magnet weighing about 20 ounces. JBL's LE8T is a good choice for an 8-inch system; the same firm's LE10A should do nicely in a 10-inch one.

While detailed step-by-step instructions will not be provided, the figures and the captions accompanying them should be studied closely; they will allow you to construct the enclosure with little difficulty. (The only tricky part—the area behind the speaker—will be explained below.)

Like all subwoofers, the SAFE enclosure should be constructed from solid, heavy material, such as 3/4-inch particle board, to prevent cabinet vibrations that will decrease the output of the system. The partitions can be made from 1/4-inch plywood, with the exception of partition 11, which should be 1/2-inch thick.

Use plenty of screws and glue! The former will add mechanical integrity and the latter will make the enclosure

continued on page 106

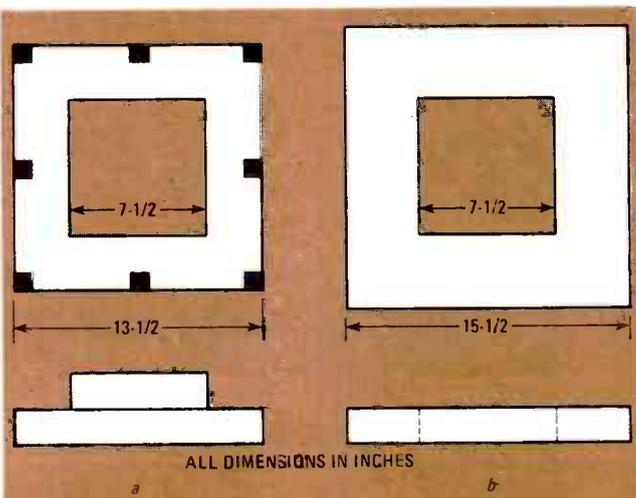


FIG. 10—EVEN-NUMBERED PARTITIONS (a) have "top hat" structure caused by using center piece cut out of odd-numbered partitions.

Professional Books That Help You Get Ahead—And Stay Ahead!

Join the **Electronics and Control Engineers' Book Club** and...

- Keep up with current technology
- Sharpen your professional skills
- Be ready for new career opportunities
- Boost your earning power

INTUITIVE IC ELECTRONICS: A Sophisticated Primer for Engineers and Technicians. By T. M. Frederiksen. 208 pp., illus. Covering both the simplest and the most complicated IC designs, this lively, easy-to-read volume provides a sophisticated, nonmathematical explanation of the basic internal mechanisms common to all semiconductor devices. Gives you a solid understanding of devices like MOS transistors, the new I²L designs, the bipolar digital logic families, JFETs, and much more. 219/230 Pub. Pr., \$18.50 Club Pr., \$14.50

HANDBOOK OF SEMICONDUCTOR AND BUBBLE MEMORIES. By W. A. Triebel and A. D. Chu. 416 pp., illus., over 50 worked-out problems. This detailed, comprehensive guide brings you right up to the minute on such newly developed devices as the PLA, FIFO, CAM, CCD, and magnetic bubble memory—as well as all the standard storage devices from ROMs and RAMs to shift registers. Analyzes, categorizes, and explains in full working detail more than 75 different semiconductor ICs and MBM devices. 582376-4 Pub. Pr., \$24.95 Club Pr., \$18.50

MICROPROCESSOR APPLICATIONS HANDBOOK. Editor-in-Chief, D. F. Stout. 472 pp., 284 illus. At last—a reference guide to microprocessor applications to help you make your systems timely, versatile, and cost-effective. Emphasizing applications that are immediately useful, the 16 experts provide in-depth treatments of each topic so you can completely analyze, design, construct, and program. Both hardware and software are thoroughly discussed. 617/988 Pub. Pr., \$35.00 Club Pr., \$26.50



New members!
Any one of these great professional books for only **\$1.89** as a premium with your 1st selection!

Spectacular values up to **\$75.00**

INTRODUCTION TO RADAR SYSTEMS, 2/e. By M. I. Skolnik. 698 pp., 244 illus. This new edition of a widely used text on radar from the systems engineer's point of view brings you full discussions of the many major changes that have occurred in the field recently. 579/091 Pub. Pr., \$38.50 Club Pr., \$30.50

USER'S GUIDEBOOK OF DIGITAL CMOS INTEGRATED CIRCUITS. By E. R. Hnatek. 339 pp., 245 illus. Providing the first comprehensive overview, this practical guide covers CMOS logic performance characteristics and selected circuit applications, data conversion and telecommunication circuits, CMOS memories, and commercially available CMOS microprocessors. 290/679 Pub. Pr., \$24.50 Club Pr., \$18.50

RADAR TRANSMITTERS. By G. W. Ewell. 252 pp., 211 illus. This all-around reference provides complete, up-to-date details on device capabilities and design procedures—with plenty of specific design examples. Helps you know your radar transmitter capabilities inside out—brings you abreast of latest design techniques to improve your designs—cuts your design time in half! 198/438 Pub. Pr., \$24.50 Club Pr., \$18.50

MODERN ELECTRONIC CIRCUITS REFERENCE MANUAL. By J. Markus. 1,264 pp., 3,666 circuit diagrams. This 103-chapter guide means you can speed up the production of new electronic devices with ease and thereby lower your production costs. Complete with values of components and suggestions for revisions, plus the original source of each circuit in case you want additional performance or construction details. 404/461 Pub. Pr., \$61.50 Club Pr., \$48.50

ELECTRONIC FILTER DESIGN HANDBOOK. By A. B. Williams. 576 pp., 408 illus. The book is organized so that you can start from practically any set of requirements and follow a sequence of clearly outlined steps and design filters ranging from simple networks to very complex configurations. Each design technique is illustrated with step-by-step examples and is accompanied by a wealth of applicable schematics, graphs, and tables of normalized numerical values. 704/309 Pub. Pr., \$37.50 Club Pr., \$28.50

ELECTRONICS CIRCUITS NOTE BOOK: Proven Designs for Systems Applications. By S. Weber, Editor in Chief. 344 pp., illus. Containing 268 ready-to-use or adapt circuits—each a proven solution—this book brings you the best of the best articles published in *Electronics'* popular Designer's Casebook section. Covers display circuits, encoders and decoders, filters, function generators, logic and memory circuits, microprocessors, and more. 192/448 Pub. Pr., \$32.50 Club Pr., \$25.50

Just Published

ELECTRONICS ENGINEERS' HANDBOOK, 2/e

Edited by D. G. Fink; D. Christiansen, Assoc. Editor
2,272 pp., 2,189 illus., 43 photos

80% New or Revised From First Edition!

Hot off the press, this updated and enlarged Second Edition, prepared by 173 expert contributors, covers the entire body of knowledge in the field, including new advances in integrated circuits (particularly those related to microprocessors), pulsed and logic circuits, laser technology, digital recording of music and voice, computer systems, telecommunications (especially switching and data transmission) and much, much more.

209/812 Pub. Pr., \$75.00 Club Pr., \$57.50

McGraw-Hill's NATIONAL ELECTRICAL CODE® HANDBOOK, 17/e. By J. F. McPartland. 1,162 pp., 1,096 illus. Bigger and better than ever! This mammoth reference explains and clarifies the many complex provisions of the current (1981) Code® to help you meet rules exactly and pass inspections the very first time.

456/933 Pub. Pr., \$24.50 Club Pr., \$18.95

DIGITAL HARDWARE DESIGN By J. B. Peatman. 428 pp., over 400 illus. Taking you beyond the microcomputer, this guide re-examines traditional techniques and focuses maintainability as a key goal, on the design of circuitry too fast for the microcomputer alone, and on designing for usefulness. It covers everything from algorithmic state machines to separately clocked circuits—with scores of examples.

491/321 Pub. Pr., \$31.95 Club Pr., \$24.95

INTRODUCTION TO THE THEORY AND DESIGN OF ACTIVE FILTERS. By L. P. Huelsman and P. E. Allen. 430 pp., illus. Once you add active filter design to your repertory of specialties, you'll possess a skill that's in great demand today. Here's one of the best texts we know on the theory, design, application, and evaluation of modern active filters and the various techniques used today.

308/543 Pub. Pr., \$28.50 Club Pr., \$21.50

ELECTRONICS ENGINEERING FOR PROFESSIONAL ENGINEERS' EXAMINATIONS. By C. R. Hafer. 336 pp., more than 200 illus. Actually two books in one—a quick preparation manual to help you pass your P.E. exams on the first try and a rich source of practical electronics engineering information and know-how.

254/303 Pub. Pr., \$22.50 Club Pr., \$17.50

ELECTRONIC COMMUNICATION, 4/e. By R. L. Shrader. 801 pp., 870 illus. This thoroughly updated edition offers all the theory and fundamentals you need to prepare yourself for the FCC commercial and amateur grade license examinations—and pass them the first time!

571/503 Pub. Pr., \$21.95 Club Pr., \$16.95

STANDARD HANDBOOK FOR ELECTRICAL ENGINEERS, 11/e. By D. G. Fink and H. Beaty. 2,448 pp., 1,414 illus. Today's most widely used source of electrical engineering information and data serves you as no other single work when you need detailed, timely, and reliable facts and how-to on the generation, transmission, distribution, control, conversion, and application of electric power.

209/74X Pub. Pr., \$59.95 Club Pr., \$44.95

DIGITAL CIRCUITS AND MICROPROCESSORS. By H. Taub. 608 pp., heavily illus. This fast-paced, carefully written guide gives you thorough explanations of all the basic principles of digital systems and logic design—plus a solid introduction to microprocessors and microprocessor-based designs. Anticipates every conceivable question you could have to make sure you understand every detail.

629/455 Pub. Pr., \$28.95 Club Pr., \$22.50

Be sure to consider these important titles as well!

PRINTED CIRCUITS HANDBOOK, 2/e. By C. F. Coombs. 126/089 Pub. Pr., \$38.50 Club Pr., \$28.95

DESIGNING WITH FIELD-EFFECT TRANSISTORS. By Siliconix, Inc. 574/499 Pub. Pr., \$24.50 Club Pr., \$18.50

BIT-SLICE MICROPROCESSOR DESIGN. By J. Mick & J. Brick. 417/814 Pub. Pr., \$24.00 Club Pr., \$18.50

MICROPROCESSORS/MICROCOMPUTERS/SYSTEM DESIGN. By Texas Instruments Learning Center & Engineering Staff. 637/58X Pub. Pr., \$24.50 Club Pr., \$19.50

ENGINEERING MATHEMATICS HANDBOOK, 2/e. By J. J. Tuma. 654/298 Pub. Pr., \$28.50 Club Pr., \$22.95

HANDBOOK OF OPERATIONAL AMPLIFIER CIRCUIT DESIGN. By D. E. Stout & M. Kaufman. 617/97X Pub. Pr., \$34.50 Club Pr., \$25.50

OPTICAL FIBRE COMMUNICATION. By Technical Staff of CSELT. 148/821 Pub. Pr., \$39.50 Club Pr., \$29.50

THE ARCHITECTURE OF PIPELINED COMPUTERS. By P. M. Kogge. 352/372 Pub. Pr., \$27.95 Club Pr., \$21.95

MICROCOMPUTER-BASED DESIGN. By J. Peatman. 491/380 Pub. Pr., \$32.50 Club Pr., \$25.50

MICROELECTRONICS. By J. Millman. 423/27X Pub. Pr., \$31.95 Club Pr., \$24.50



MAIL THIS COUPON TODAY

McGraw-Hill Book Clubs
Electronics and Control Engineers' Book Club
 P.O. Box 582, Hightstown, New Jersey 08520

Please enroll me as a member and send me the two books indicated, billing me for the \$1.89 premium and my first selection at the discounted member's price, plus local tax, shipping, and handling charges. I agree to purchase a minimum of two additional books during my first year of membership as outlined under the Club plan described in this ad. A shipping and handling charge is added to all shipments.

Write Code No. of \$1.89 selection here

Write Code No. of first selection here

Signature _____

Name _____

Address/Apt. # _____

City _____

State _____ Zip _____

This order subject to acceptance by McGraw-Hill. All prices subject to change without notice. Offer good only to new members. Orders from outside the U.S. cannot be accepted.

E33547

Why YOU should join now!

■ **BEST AND NEWEST BOOKS IN YOUR FIELD**—Books are selected from a wide range of publishers by expert editors and consultants to give you continuing access to the best and latest books in your field.

■ **BIG SAVINGS**—Build your library and save money too! Savings ranging up to 30% or more off publishers' list prices—usually 20% to 25%.

BONUS BOOKS—You will immediately begin to participate in our Bonus Book Plan that allows you savings of between 70%–80% off the publishers' prices of many professional and general interest books!

■ **CONVENIENCE**—12-14 times a year (about once every 3-4 weeks) you receive the Club Bulletin FREE. It fully describes the Main Selection and Alternate Selections. A dated Reply Card is included. If you want the Main Selection, you simply do nothing—it will be shipped automatically. If you want an Alternate Selection—or no book at all—you simply indicate it on the Reply Card and return it by the date specified. You will have at least 10 days to decide. If, because of late delivery of the Bulletin you receive a Main Selection you do not want, you may return it for credit at the Club's expense.

As a Club member you agree only to the purchase of three books (including your first selection) during your first year of membership. Membership may be discontinued by either you or the Club at any time after you have purchased the first selection plus two additional books. Orders from outside the U.S. cannot be accepted.

Other McGraw-Hill Book Clubs: Accountants' and Controllers' Book Club • Architects' Book Club • Chemical Engineers' Book Club • Civil Engineers' Book Club • Computer Professionals' Book Club • Mechanical Engineers' Book Club

For more information, write to:

McGraw-Hill Book Clubs, 26th fl., 1221 Avenue of the Americas, New York, NY 10020

STEREO AUDIO FOR TV

Stereo and multichannel TV programming is already a reality in several countries. Here's the latest on what's happening here.

LEN FELDMAN
CONTRIBUTING EDITOR

BY THE TIME YOU READ THIS, ALL THE tests should have been completed. Even the report prepared by the Electronic Industries Association's Broadcast Transmission Standards (BTS) Committee may already be in the hands of the FCC, and we will be a step closer to having stereo audio for television broadcasts in the U.S. And, with two (or more) audio channels available, not only will stereo be able to be broadcast, but the second channel can also be used for the transmission of a second monophonic program—perhaps a sound-track or commentary in a second language, for viewers whose native tongue is not English.

No matter how soon a multichannel audio system is adopted for U.S. TV, and no matter which system is chosen, the U.S. will still be a late starter in adopting stereo for TV. In Japan, that type of service has been available since 1978. In fact, of the three basic systems being proposed for use in the United States, one is the Japanese system that was developed and tested over a period of four years by the Technical Research Laboratories of NHK, the Japanese Broadcasting Corporation.

The two other systems currently being considered for use in this country are by Telesonics Systems, Inc. and by the Zenith Radio Corporation. The Japanese system under consideration is officially known in this country as the EIAJ system, since it is being sponsored in the U.S. by the Electronic Industries

Association of Japan. Finally, a fourth system, developed—and just being introduced—in Germany, may have some influence on what method is finally adopted. (That system will be discussed in detail soon in a future issue of **Radio-Electronics**).

Further complicating the decision-making process is the fact that, in addition to the three basic transmission-systems just referred to, there are also three noise-reduction systems being proposed for use with them, making a total of nine possible combinations. The incorporation of more audio channels in the bandwidth now assigned to a single TV audio channel will degrade the audio signal-to-noise ratio, regardless of which of the three stereo systems is selected. That is what has prompted Dolby, dbx, and most recently, CBS, to propose noise-reduction encoding/decoding systems. Those,

coupled with any of the proposed multichannel TV-audio systems, would reduce background noise to acceptable levels and allow broadcasters to maintain the quality of fringe-area signals.

Since multichannel TV-audio will eventually be with us, it would be a good idea to understand how the three basic transmission-systems that have been proposed work. The principles involved in audio companding are familiar to most readers of **Radio-Electronics** so we will not include a description of the three noise-reduction schemes in this discussion.

The EIAJ system

The components of the signal used by the Japanese system are shown in Fig. 1. Note that the "x" axis (horizontal) serves two purposes—it shows both the audio-frequency response of each channel and the frequency of the



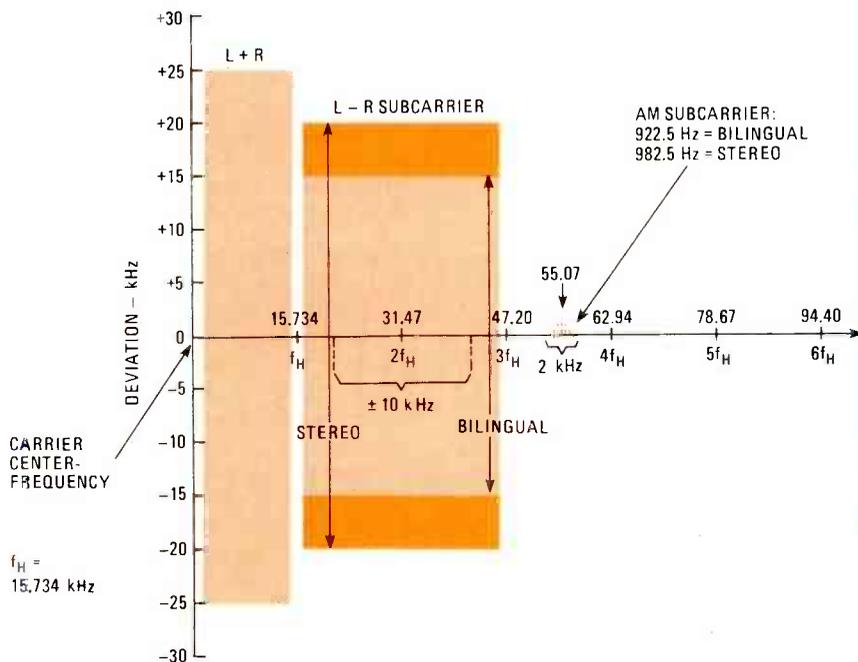


FIG. 1—ORIGINAL EIAJ SYSTEM uses a subcarrier with a deviation of ± 10 kHz to transmit the L-R or second-channel audio information. Maximum frequency-response is 12 kHz.

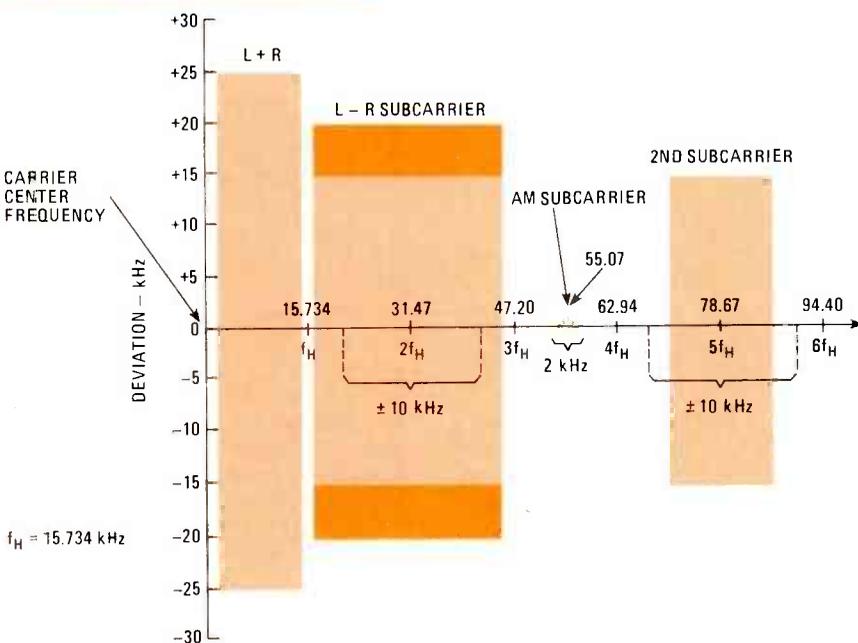


FIG. 2—U.S. VERSION of the EIAJ system extends frequency-response of the subcarrier to 15 kHz. In addition, a second subcarrier, with an 8-kHz bandwidth, is provided for.

subcarrier and pilot tone relative to that of the main audio carrier. The "y" axis (vertical) shows the frequency deviations of the main and sub-carriers.

The main audio carrier—used for monophonic transmissions, for one

channel of multichannel transmissions, or for the L+R component of a stereo transmission—has a maximum deviation of ± 25 kHz (just like the NTSC system used in the U.S.) and a frequency response from 50 Hz to 15 kHz.

The subcarrier, located at a frequency of 31.47 kHz (twice the TV horizontal line-frequency) above the main carrier, is used for the second channel of a multichannel transmission, or for the L-R component of a stereo transmission. That frequency was chosen because it minimizes interference between the video signal and the subcarrier in intercarrier-type receivers. When frequency-modulated, the subcarrier has a maximum deviation of 10 kHz on either side of the center frequency. In Japan, the frequency response of that channel is from 50 to about 12 kHz, but the system has been modified for use in the U.S. to extend the response to 15 kHz.

The subcarrier is used to modulate the main carrier—a technique known as *injection*. When stereo is being transmitted, the amount of injection is ± 20 kHz, giving the main carrier a total deviation of ± 45 kHz; in the multichannel mode, the amount of injection is ± 15 kHz, producing a total deviation of ± 40 kHz.

An amplitude-modulated control signal having a bandwidth of 2 kHz is transmitted at a frequency 55.07 kHz ($3\frac{1}{2}$ times the horizontal line-frequency) above the main carrier. Its purpose is to inform the decoding equipment at the receiver which mode is being used. A 982.5-Hz tone indicates that a stereo program is being transmitted; a 922.5-Hz tone indicates that a multichannel program is being broadcast. The absence of a tone means that the program material is monophonic. The control signal can also be used to activate a visual indicator to inform viewers/listeners which audio mode was being used with the video they were watching.

Tests made by the developers of the Japanese TV multiplex-system have shown that a *second* subcarrier can be added without making it necessary to change the parameters of the first subcarrier. In tests conducted by the EIA last summer in Chicago, such a system—as shown in Fig. 2—was used. The characteristics of the second subcarrier were the same as those of the first, with the exception that the audio-frequency response was restricted to an upper limit of 8 kHz. It is expected that that subcarrier would be used for services where limited frequency-response would not pose a problem.

The Telesonics system

The Telesonics system, whose arrangement is shown in Fig. 3, uses a double-sideband, suppressed-carrier. AM subcarrier similar to that used in stereo-FM broadcasting in the United

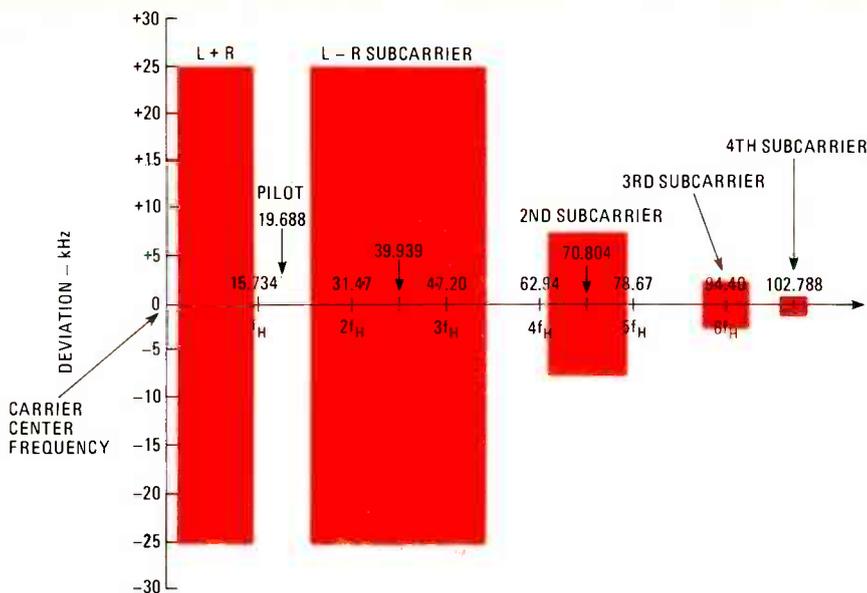


FIG. 3—TELESONICS SYSTEM uses amplitude modulation for its subcarriers. The scheme allows as many as four subcarriers.

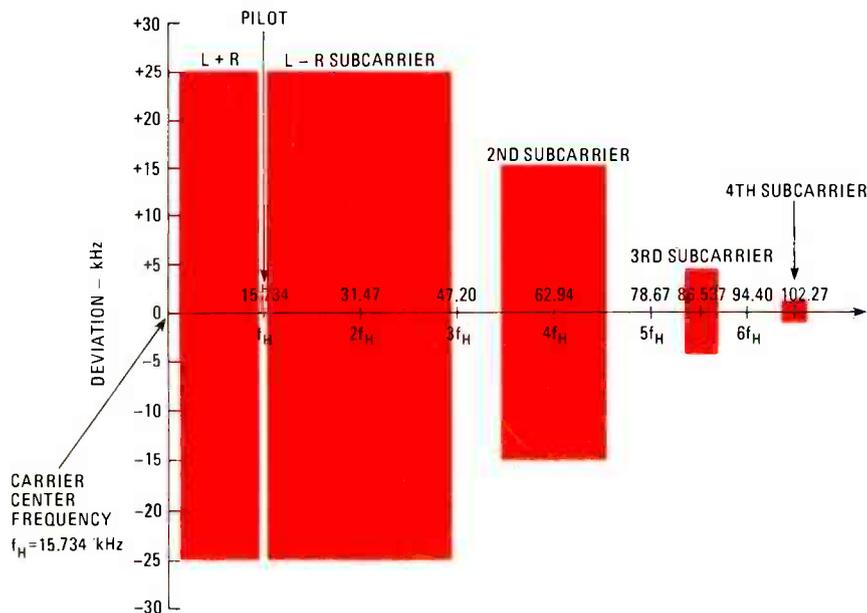


FIG. 4—ZENITH RADIO CORPORATION'S system uses the horizontal line-frequency, 15.734 kHz, for the pilot tone.

States and many other countries. (The EIAJ system, with the exception of the control signal, is all-FM.) Such an arrangement requires a pilot signal, which is used at the receiving end to restore the suppressed carrier. In the Telesonics system, the pilot signal has a frequency of 19.668 kHz, or 1.25 times the TV horizontal line-frequency. The double-sideband suppressed-carrier used for transmission of L-R information is 39.939 kHz, or 2.5 times the horizontal line-frequency, away from the audio carrier center-frequency. Tests of the system have been proposed using three different levels of deviation of the main carrier by the subcarrier: 11.25 kHz, 25 kHz, and 33.75 kHz. Tests using additional FM subcarriers at other frequencies, in order to provide a second

subchannel for sound transmission; a third carrier for ENG (*Electronic News Gathering*), telemetry, or another service, and a fourth subcarrier for telemetry alone have also been suggested. The additional FM subcarriers are impressed upon the main carrier at very low levels and with highly restricted audio-frequency ranges, as shown in Fig. 3.

The Zenith Radio system

Frequency allocations and subcarrier arrangements used in the Zenith Radio Corporation system are shown in Fig. 4. Like the Telesonics system, the Zenith system also uses a double-sideband, suppressed-carrier AM subcarrier. Instead of using a separate pilot sig-

nal, the Zenith system uses the horizontal line-frequency itself for that purpose, with the center frequency of the suppressed subcarrier falling at twice the horizontal line-frequency, or 31.47 kHz. Provision for a separate audio program (such as a second-language summary of the news) is made using an FM subcarrier having its center frequency at four times the video horizontal-line rate, or 62.94 kHz, while other FM subcarriers at 5.5 and 6.5 times the horizontal frequency can also be included for telemetry or other telecommunications purposes.

Signal-to-noise ratios

As we noted earlier, all the stereo/multichannel TV-audio systems involve some degradation of the signal-to-noise ratio. In Japan, where the system employed uses a frequency-modulated subcarrier for transmission of the L-R information (or the second-channel information), results at station JOAX (the anchor station of the national network, based in Tokyo), using an 85 kW audio carrier, show that the signal-to-noise ratio is about 60 dB on both the main and sub-channels at receiving points within the city, fairly close to the transmitter site. In fringe areas, of course, that figure would be worse.

Experiments have already shown that the systems using AM subcarriers (Telesonics and Zenith, so far) for their difference (L-R) information or second-channel transmissions suffer a greater reduction in signal-to-noise ratio than do all-FM subcarrier systems. That's especially true in fringe areas, where the main audio-carrier is of insufficient strength to send the receiving circuitry into full FM-limiting. It is for that reason that the EIA Broadcast Television Standards Committee deemed it advisable to incorporate the companding system proposals mentioned earlier in the test recently completed.

Several critical listeners, none of whom knew which companding systems were being used (or, for that matter, that they were being asked to judge the merits of three companding systems), were asked to listen to a variety of recorded material and to judge which "sounded best." Having monitored some of the tests myself on behalf of the EIA, I can report that, while each companding system was judged effective for certain kinds of music, the difference in background noise between *all* the uncompanded transmissions and those using noise reduction was obvious, regardless of which system was used for the test. That was particularly true when "fringe area" reception conditions were simulated.

Audio enthusiasts have complained for many years about the poor quality

continued on page 102

Inside Dolby HX

Designed to provide the ideal cassette tape bias level for signals at any frequency, this new version of the Dolby HX system overcomes the problems of the original and adds some interesting refinements.

JUST ABOUT TWO AND A HALF YEARS ago, Dr. Ray Dolby, of Dolby Laboratories, introduced a new signal-processing scheme that he called *Dolby HX*; the HX stood for "headroom expansion." That circuit was Dolby Laboratories' first attempt at signal processing that had nothing to do (at least directly) with noise reduction. While Dolby noise reduction has been very widely accepted by tape-deck manufacturers, the *Dolby HX* system was not greeted with the same sort of enthusiasm.

At least one manufacturer, however, must have been fascinated by the ideas behind *Dolby HX*—enough so to have developed a version of the headroom-expansion idea that overcomes earlier objections to the HX approach, and provides benefits that were not part of Dolby's original system. That manufacturer is the Danish firm of Bang & Olufsen, and, with the unqualified blessing of Dolby, their version is called *Dolby HX Professional*.

In order to appreciate the improvements in this new version of *Dolby HX*, it will be helpful to review the concepts behind Dolby's original version of the headroom-expansion system. The underlying concept is based on the fact that there is an ideal level of tape bias for every audio frequency. As can be seen in Fig. 1, the bias level that provides the highest output level and acceptably low distortion for a mid-frequency tone of 333 Hz is quite different from the optimum bias level needed when recording a 10-kHz signal. Figure 1 also shows that as we attempt to record higher and higher frequencies, lower and lower levels of bias are required. Generally, most makers

of cassette decks choose a bias level that, of necessity, is a compromise—one that covers reasonably well as much of the audio range as possible. Usually, that bias level is set so that it is a bit lower than optimum for best low-frequency/mid-frequency maximum output level (MOL), and for a reasonable output level at high frequencies. Since such compromise settings of bias tend to favor low and mid frequencies, the phenomenon known as high-frequency tape saturation is common in cassette decks.

The earliest version of *Dolby HX* worked on the assumption that, if the bias level of a recorder is made variable and allowed to change dynamically with changing input-signal content, it should become practical to record high-frequency signals at higher levels by reducing the bias levels when high-level,

high-frequency signals dominate the program content being recorded. Furthermore, since the headroom expansion takes place entirely during the recording process, no "decoding" or correction circuitry is needed during playback to get the benefits of such a variable bias system.

A block diagram of the original system is shown in Fig. 2. For the system to work, there must be a control signal that is sensitive to amplitude and frequency content. But such a control signal already exists in any *Dolby B*-equipped deck. All *Dolby B* noise-reduction circuits generate a voltage signal that depends on the strength and frequency content of the stronger of the two input channels. That voltage is used to control the amplifiers in the *Dolby B* noise-reduction circuits.

But, while the *Dolby B* control signal may be ideal for noise-reduction compressing, it is less than ideal for bias level control. In *Dolby B*, the control signal is derived without regard to the recording pre-emphasis curve. That curve shapes the frequency response of the signal that, after processing for noise reduction, reaches the recording head. As the bias level changes, the frequency response of the system also changes. The problem of varying frequency response during recording was dealt with in the original *Dolby HX* system by allowing the control signal to alter pre-emphasis at the same time that it alters bias. If everything was adjusted perfectly, the bias and pre-emphasis changes were supposed to balance each other out to provide the flat response and expanded headroom for which the system was designed.

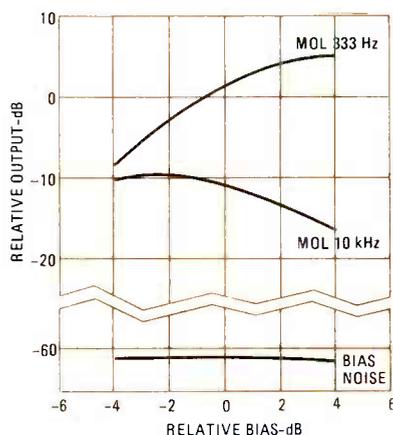


FIG. 1—THE BIAS LEVEL that provides the highest output with acceptably low distortion for a 333-Hz tone is quite different than the bias level required by a 10-kHz tone.

LEN FELDMAN
CONTRIBUTING HI-FI EDITOR

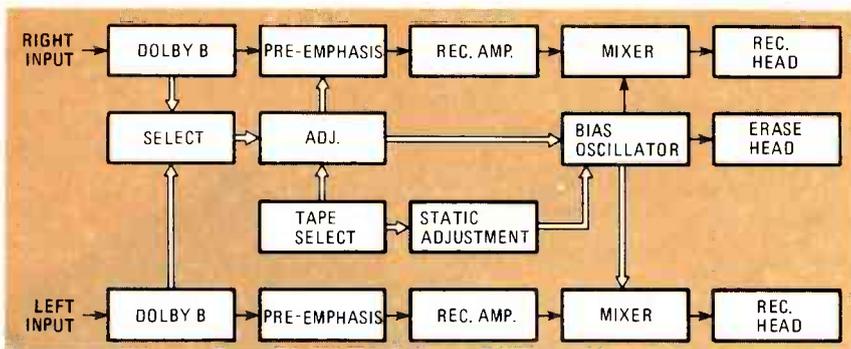


FIG. 2—THE ORIGINAL DOLBY HX system is shown in this block diagram. For the system to work, a control signal that is sensitive to amplitude and frequency content is required.

Self biasing and mutual biasing

While studying how *Dolby HX* works, and the dynamics of magnetic recording in general, the engineers at Bang & Olufsen noted two phenomena. They noted that any signal fed to a recording head acts as bias for the signal to be recorded, with high-frequency signals being more effective as a bias than low-frequency signals. A signal even acts as a bias for itself (self-biasing), though that effect is quite small for audio signals. Nevertheless, self bias may be a small part of the reason why high-frequency signals require a much lower bias setting than low-frequency signals.

Much more important, however, is the biasing effect of the high-frequency content of an audio signal on the low-frequency part of the same signal. While that effect is only a small part of the total bias applied to the recording head, it is enough to alter the bias conditions for low frequencies. That is shown dramatically in Figs. 3 and 4.

Figure 3 is a spectrum analysis of a single 300-Hz tone, recorded at a level of 250 nanowebers-per-meter (nWb/m). That is about 2 dB above the Dolby

calibration level—not an exceptionally high level. The bias on the recorder used was adjusted to a conventional level: slightly below optimum for the best low-frequency MOL. The tall spike at the left is the 300-Hz signal. The spike at around 900 Hz is the third-order distortion component and its level is about 46 dB below that of the 300-Hz signal, which corresponds to a third-order harmonic distortion level of 1.58%. Those are not unusual values for a good-quality cassette recorder. (In Figs. 3 and 4, each vertical division is 10 dB, while the horizontal scale is logarithmic and runs from 20 Hz at the left to 20 kHz at the right; key frequency points are shown at the top of the scope display).

In Fig. 4, the 300-Hz signal has been kept at the same input level, but a pair of tones with frequencies of 9 and 10 kHz have been mixed into the signal at a level some 50 dB below that of the lower-frequency signal. You'll note that there is a dramatic reduction in third-order distortion of around 6 dB, while the recorded level of the 300-Hz signal actually rises about 2 dB. The net third-order distortion is now 8 dB lower

than before (relative to the 300-Hz fundamental), or 0.63%. Both the reduced third-order distortion and the increased level of the recorded signal are caused by the additional biasing effect of the high-frequency signals; that additional biasing has raised the total effective bias level for the low-frequency signal to near its optimum value. The biasing of one part of an audio signal that is being recorded by another part of the same signal can be called mutual biasing.

It follows that the flat frequency-response obtained under static test conditions (using a single-tone test signal) may not be so flat when complex musical signals are recorded on tape. When such musical signals are recorded on a machine with fixed bias, the frequency response changes continuously due to mutual biasing, depending upon the instantaneous high-frequency content of the overall signal. Such dynamic changes in frequency response are present not only in cassette recorders, but in any tape recorder using high-frequency bias, such as studio tape decks and high-speed duplicating machines used to produce prerecorded tapes.

Dolby HX Professional

Dolby HX Professional was developed jointly by Bang & Olufsen and Dolby Laboratories. Although the principles of *Dolby HX* and *Dolby HX Professional* are similar, the aims of the two systems are different. In *Dolby HX*, the chief aim was to allow high-frequency signals to be recorded at higher levels on cassette tape. *Dolby HX Professional* has the more fundamental aim of keeping the active or effective bias constant, regardless of signal content. Active bias is defined here as the effective bias seen by each frequency in the audio spectrum. In keeping the active

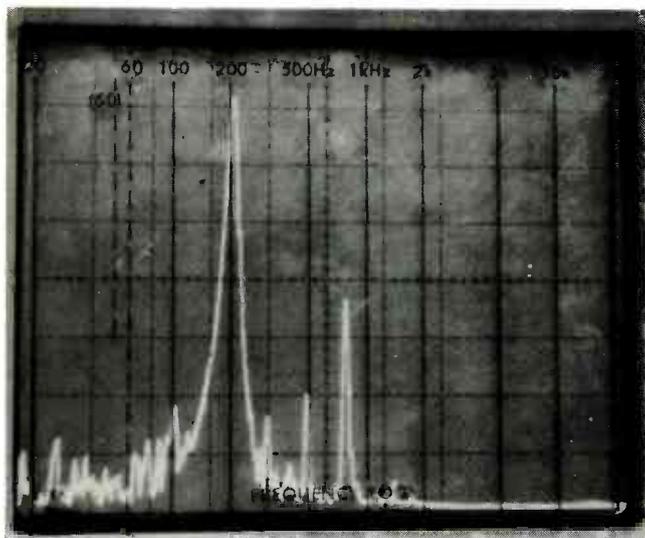


FIG. 3—SPECTRUM ANALYSIS of a single 300-Hz tone recorded at a level of 250 nanowebers-per-meter.

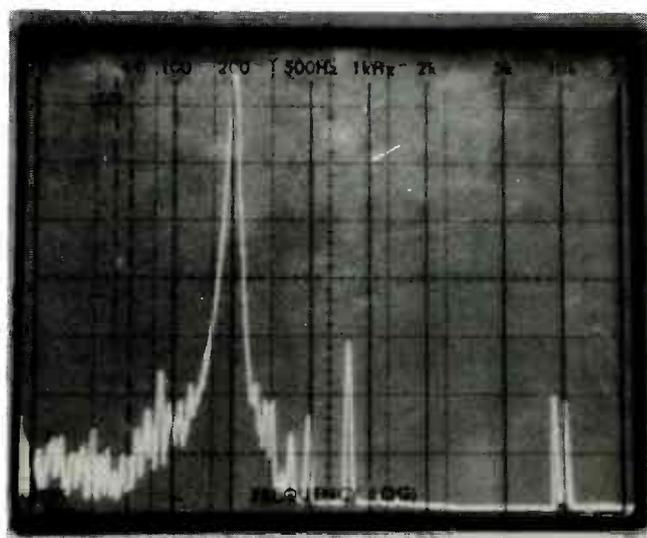


FIG. 4—MUTUAL BIASING is demonstrated here. Two low-level, higher-frequency (9 and 10 kHz) tones were mixed with the 300-Hz tone.

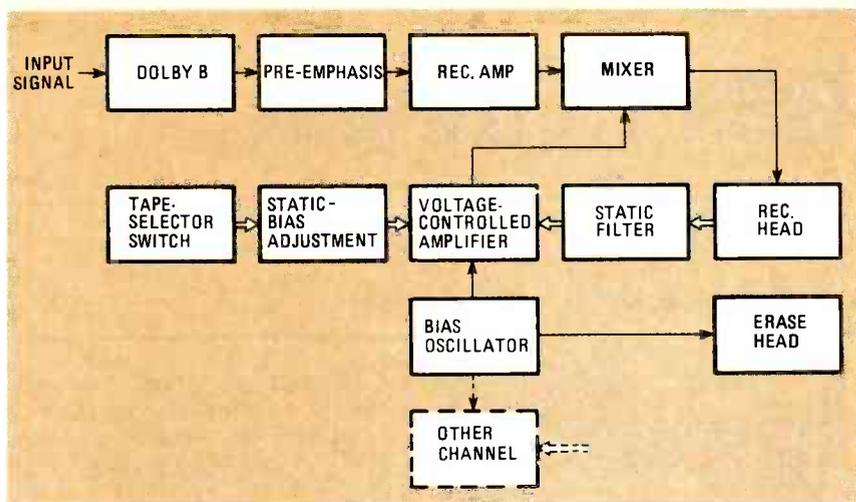


FIG. 5—BLOCK DIAGRAM of the *Dolby HX Professional* system. Unlike *Dolby HX*, this system measures the sum of the audio signal, including any preprocessing, and the bias at the record head.

bias constant, all of the recording parameters that would normally be affected by a change in bias under static conditions, will remain stable under the dynamic conditions that prevail during the recording of more complex music signals. For example, the frequency-response changes shown in Fig. 4, which were caused by mutual biasing, would not occur if active bias were kept constant for all audio frequencies.

Dolby HX Professional and *Dolby HX* are similar to the extent that both systems change the level of the bias signal dynamically, but the reason for doing it and the method used are different. As things worked out, all of the original aims of *Dolby HX* are fulfilled by *Dolby HX Professional*, but that is a secondary benefit of the latter system. *Dolby HX Professional* has other advantages over *Dolby HX*. It is a dedicated system: one that is completely independent of Dolby noise-reduction modules or other electronic circuits within the recorder. (Remember, the original *Dolby HX* system uses the same control voltage that was developed by the *Dolby B* noise-reduction circuits.) That makes the system suitable for professional applications, such as in studio recorders, as well as for use in high-quality cassette decks.

Figure 5 is a block diagram which shows how *Dolby HX Professional* works. Unlike *Dolby HX*, which only measures the audio signal to determine the bias compensation required, *Dolby HX Professional* measures the sum of the audio signal, including any preprocessing, and the bias at the tape head. The signal from the recording head is fed to a processing circuit consisting of an accurately designed static filter. Once that filter has modified the signal, the signal is rectified to form a control voltage that is an accurate replica of the total biasing effect of the processed audio signal, plus the bias at the record-

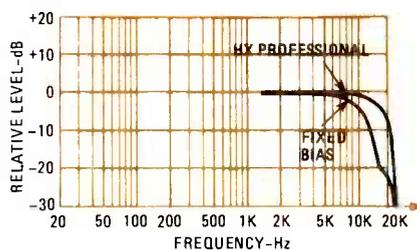


FIG. 6—HIGH-FREQUENCY CAPABILITIES of a cassette recorder equipped with *Dolby HX Professional* versus a conventional machine of the same quality.

ing head, or the "active bias." By measuring those signal components at the recording head, the system insures that the control voltage is always an accurate representation of the flux across the air gap in the recording head, regardless of signal strength or of any signal processing that may have taken place in previous stages. All processes and signals are carefully accounted for when the control voltage for bias compensation is derived from *Dolby HX Professional*. The control voltage is compared with a reference voltage that is adjusted for the static bias needed for the particular type and brand of tape being used, and a correction signal is generated. That signal is used to adjust a voltage-controlled amplifier that in turn alters the amplitude of the bias voltage supplied to the recording head. That maintains a constant active bias for the signal recorded. Once the circuit is correctly designed and installed, there is no need for any further adjustments for any tape or any signal-processing circuitry. Furthermore, since effective bias remains constant, no changes in pre-emphasis with changing bias are required; with *Dolby HX*, such changes in pre-emphasis were needed. *Dolby HX Professional* can be used with any noise-reduction circuitry currently available, or, for that matter, no noise-reduction circuitry at all.

If an audio signal having only low frequencies is fed to a recorder equipped with *Dolby HX Professional*, the circuit will "recognize" that fact and the bias level will remain fixed; since there are no high frequencies present in the signal, no bias-level change is required. If high frequencies are added, the *Dolby HX Professional* circuitry reduces the bias signal from the bias oscillator. The amount of reduction is determined by the passive filter, which monitors the entire signal applied to the tape head. That reduction in bias level will be almost exactly equal to the mutual biasing caused by the high frequencies. Thus, low frequencies see a constant bias level, but bias is reduced for high frequencies since they receive no added bias from the audio signal; low frequencies and high frequencies both see their optimum bias levels.

Should the signal consist of high frequencies only, the *Dolby HX Professional* circuit will reduce the bias from the oscillator even more; to a level that is very close to ideal for that type of signal. In that way, the original purpose of *Dolby HX*—namely, substantially increased headroom for high-frequencies—is also a characteristic of *Dolby HX Professional*. With *Dolby HX Professional*, the bias setting is adjusted to give the lowest possible distortion at low- and mid-frequencies, and the best MOL—compromises are no longer required.

Figure 6 shows the difference in high-frequency capability between a fixed-bias machine and one with *Dolby HX Professional*. The machine equipped with *Dolby HX Professional* delivered an output that was attenuated only 1.4 dB with respect to our 0-dB reference (250 nWb/m) at 13.5 kHz. A conventional machine of equal quality, on the other hand, delivered an output that was attenuated 8.6 dB at the same 13.5 kHz frequency, or fully 7.2 dB poorer response at that relatively high frequency. The same type of tape was used in both machines.

Dolby HX Professional includes another refinement. It functions totally independently on each of the two stereo channels of a tape deck. That means that bias for each channel is always optimally adjusted for the signal being applied to that channel, even though the signal applied to the other channel may have a completely different content, requiring a totally different bias level.

At the moment, Bang & Olufsen is the only company making use of that refinement of the *Dolby HX* circuit. The new circuitry appears in their *Beocord Model 8002* cassette recorder. If the circuit proves to be as effective as claimed, you are likely to see it used by quite a few manufacturers before too long.

R-E

HOBBY CORNER

This little IC can produce a great deal of sound.

EARL "DOC" SAVAGE, K4SDS, HOBBY EDITOR

IT IS ALMOST UNBELIEVABLE THAT SUCH a variety of sounds can be created by one small 28-pin IC. The Texas Instruments 76477 can generate everything from simple tones to very complex sounds. Best of all is the fact that you can create any sounds you desire by just adding a few resistors and capacitors.

Before we get into how to make some of those sounds, perhaps we should mention some of the ways you can use the 76477. There are, of course, sound effects. While I can't guarantee it, I believe that this IC can produce any sound you have ever heard. Further, I know that it will produce many that you have never heard before!

The more mundane uses for the 76477 are obvious. They include such things as chimes, musical "instruments," door bells, noise generators—in fact, just about anything that requires sound. Now, let's see how to make the IC perform.

For now, we'll treat the 76477 as a "black box." To explain what actually goes on inside the IC would require a book, so we'll largely ignore the "how" and discuss the "what" of the IC.

First, there is a matter of the power supply. Texas Instruments' has made this easy by providing two ways to power the IC. A voltage regulator has been built into the 76477 so you can apply anything from 7.5- to 9-volts DC to pin 14. If you do that, you can also take 5-volts DC at up to 10 mA from pin 15 for use with external circuits! The other way to power the IC is to apply a regulated 5-volts DC to pin 15. In either method, pin 2 is the ground connection.

The next thing is the audio output. A small audio amplifier is built into the IC, but further amplification is needed to bring the signal level up to a useful level. The manufacturer suggests the simple two-transistor amp shown in Fig. 1. For a permanent installation, that will do nicely. However, I prefer a different approach for experimentation (and you will be doing a lot of experimenting to find new sounds). What I did was to use a small all-purpose amplifier such as the Radio Shack 277-1008, and connect it to the IC as shown in Fig. 2.

There is also a master switch for the IC: pin 9. If pin 9 is connected to

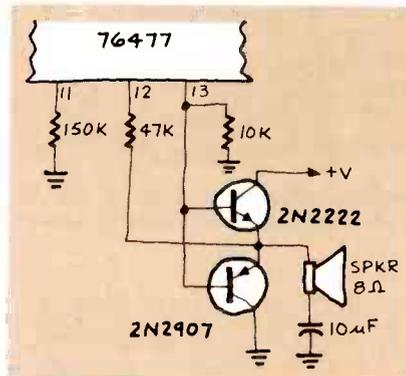


FIG. 1

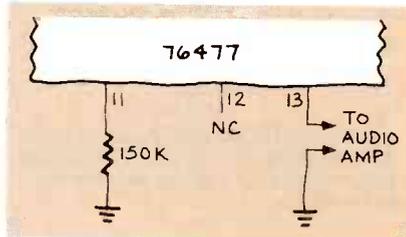


FIG. 2

ground, the IC is on; if it is connected to 5-volts DC, the IC is off.

Now that we've discussed the power, audio, and master switch pins, that leaves us with just 21 more pins. Those 21 are the ones that are used to program the sounds you want. Seldom, if ever, will you use all of them at once but you do need to know what all of them do.

To make things a little easier, we'll group those 21 pins into functions.

Table 1 contains those functions and the pin numbers associated with each function. Note that most pins have an

TABLE 1

Super Low Frequency Oscillator (SLF)

- 20R 7500 ohms to 1 megohm
- 21C 500 pF to 100μF

Voltage Controlled Oscillator (VCO)

- 18R 7500 ohms to 1 megohm
- 17C 100pF to 1μF
- 19 Duty-cycle (normally +5-volts DC)
- 22 Switch (+5-volts DC = SLF; 0 = pin 16)
- 16 External (High voltage = Low frequency)

Noise

- 5R 7500 ohms to 1 megohm
- 6C 150pF to .01μF
- 4R Switch (43,000 ohms)

Mixer

- 25, 26, and 27 See text

One Shot

- 24R 7500 ohms to 1 megohm
- 23C 0.1 to 50μF

Envelope

- 1 and 28 See text

Attack/Decay

- 10R Attack (7500 ohms to 1 megohm)
- 7R Decay (7500 ohms to 1 megohm)
- 8C Timing (.01 to 10μF)

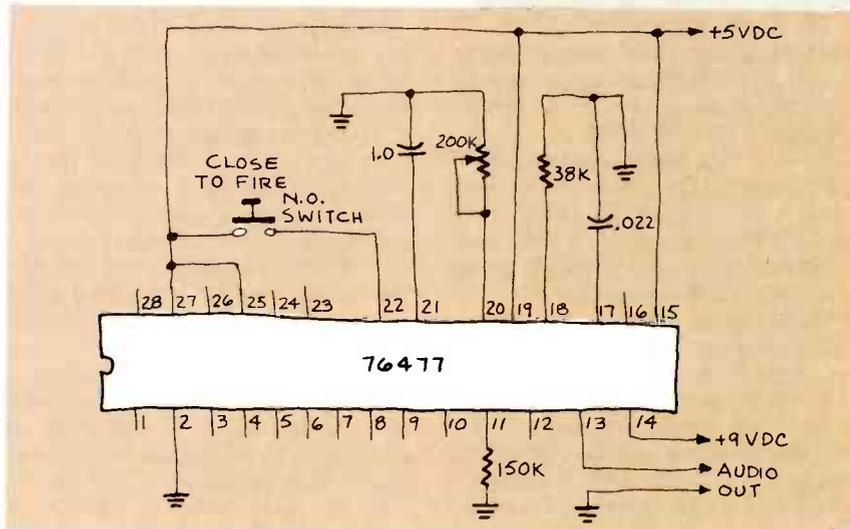


FIG. 3

Put Professional Knowledge and a
COLLEGE DEGREE
in your Electronics Career through
HOME STUDY

Earn Your DEGREE

No commuting to class. Study at your own pace, while continuing your present job. Learn from easy-to-understand lessons, with help from your home-study instructors whenever you need it.

In the Grantham electronics program, you first earn your A.S.E.T. degree, and then your B.S.E.T. These degrees are accredited by the Accrediting Commission of the National Home Study Council.

Our free bulletin gives full details of the home-study program, the degrees awarded, and the requirements for each degree. Write for *Bulletin R-82*.

Grantham College of Engineering
2500 So. LaCienega Blvd.
Los Angeles, California 90034

COMPUTERS

Complete Microprocessors line, peripherals & Terminals.

Green Monitor	199.00	SOROC IO 135	795.00
Leader 100 Mon.	139.00	TI-99/4	399.00
Viscalc	160.00	Epson MX-80	call us
Microsoft 2/80	320.00	Color Monitor	call us
IDS 445G	call us	TI-810	1395.00
TI-745	1440.00	80 Column Board	299.00

Texas Instruments

Invest. Anal	\$ 42.00	TI-59	\$175.00
Accessories	Call us	TI-55 II	39.95
TI-58C	80.00	Speak & Spell	49.95
PC100C	155.00	TI Programmer	47.95
TI BAII	39.00	MBA	49.95

HEWLETT-PACKARD

HP/125 Computer	call us	HP-11C NEW	call us
HP/37E	\$60.00	HP-12C NEW	call us
HP-33C	70.00	HP-41C Mem Module	26.00
HP-34C	115.00	HP-41CV	call us
HP-38C	114.99	HP-67	295.00
HP-41C Prog	189.00	HP-97	570.00
HP-41C Printer	285.00	Quad Ram	call us
HP-41C CRD RDR	169.00	Application Pac	call us

HP-83 HP-85 and accessory - call us for prices

SCM TYPEWRITER SPECIALS

SCM 2200	\$279.00	INTREPID	\$274.00
SCM 2500	289.00	CLASSIC 12	159.00

All units shipped in original cartons with accessories according to manufacturer's specification. Send money orders, personal check 2 weeks to clear. In Illinois add 6% sales tax. Add \$6.95 minimum shipping & handling charges per unit. We ship UPS. Subject to availability. Written warranty for specific products can be obtained free upon request. Above prices are for mail order and prepaid only. Prices and specifications subject to change without notice. Send mail orders.

Nabik's, Inc.

519 DAVIS, EVANSTON ILL 60201 TEL 312-869-6144

appended letter (R or C) that indicates whether a resistor or capacitor is to be connected to it. In all cases, the component is connected from the indicated pin to ground. In addition, some of the pin numbers are followed by the normal range of values for the components that are to be connected to it.

The Super Low Frequency oscillator (SLF) has a normal range of 0.1 to 30 Hz, but it will operate at a much higher frequency if needed. The value of the resistor and capacitor attached to the appropriate pins determines the frequency. The SLF can also be used to "modulate" other IC functions such as the VCO and/or mixer.

The Voltage Controlled Oscillator (VCO) produces a tone. The basic pitch of the tone is determined by a resistor connected to pin 18 and a capacitor connected to pin 17. Remember, each of these components are connected between the pin and ground. In addition to the two components, the pitch of the tone is also determined by either the output voltage from the SLF or by a voltage applied to pin 16. Pin 22 is the switch: connecting it to +5-volts DC causes the SLF to be the controlling voltage; grounding that pin lets you control the frequency by applying a voltage to pin 16. In addition, the duty cycle of the output waveform can be controlled by a voltage applied to pin 19. Normally, pin 19 is connected to +5 volts.

The noise source is switched by pin 4. Leaving that pin unconnected keeps the noise source off; shunting pin 4 to ground through a 43,000-ohm resistor turns it on. The resistor connected to pin 5 and the capacitor connected to pin 6 determines the sound quality of the noise. An external noise source can also be input at pin 3.


The mixer does just what you would expect—it allows you to mix the generated sounds in any combination. It is programmed by a binary control signal on pins 25, 26, and 27. The three pins gives you up to eight possible combinations, ranging from binary 0 (000) to binary 7 (111). A logic high (1) is +5-volts DC and a logic low (0) is ground. The mixer code is as follows: 000 = VCO; 001 = SLF; 010 = Noise; 011 = VCO/Noise; 100 = SLF/Noise; 101 = SLF/VCO/Noise; 110 = SLF/VCO; and 111 = inhibit all. For example, 011 (a binary 3) will cause the VCO and noise source to be mixed and passed on while inhibiting the SLF.

Let's pause for a minute and take stock. The SLF can generate a frequency—even a sound—that can be fed into the VCO or the mixer. The VCO can generate a sound that can be modulated by the SLF or an external voltage and fed into the mixer. The noise generator can also be fed into the mixer.

continued on page 83

WE TAKE YOU BY THE HAND!

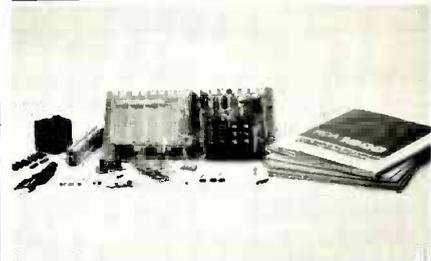You'll learn all about computers: how to build, program, service, even play TV games—without knowing the first thing about it!



The New ELF II "Beginners" Package

Your own expandable micro-computer kit, 5 diagnostic analyzers plus circuit, programming, diagnostic manuals, even games you can play on TV. All only \$139.95.

Even if you don't know bits from bytes, now it's easy and inexpensive to build your own micro-computer. Learn how it works, program it, service it, even play games with it on your TV! It's here in the New ELF II "Beginners" Package, only from Netronics. Only \$139.95. Here's the package: 1. your own micro-computer, the famous ELF II (featuring the RCA 1802 CMOS microprocessor) in kit form with step-by-step instructions on how to build it. Diagnostic Analyzers including 2. your own Logic Probe, 3. Pulse Catcher, 4. 8 bit Test Register, 5. Logic Analyzer, 6. Gate Arrays, 7. Non-Technical Manuals on how to use analyzers, how to get into the guts of the computer, what makes it tick, how to service it. 8. Sample Programs that teach you machine language programming plus how to correct or "debug" any programming mistakes. 9. TV games you can play. If your TV set has no video input, an optional converter (RF Modulator), is available. Then, once you've got this "Beginners" Package under your belt, keep on expanding your ELF II with additions like the Typewriter Key Board, added RAM, Full Basic Interpreter, Electric Mouth Talking Board, Color/Music, A/D-D/A Boards for Robot Controls and much, much more. We'll take you by the hand with the New ELF II "Beginners" Package. Only \$139.95. Mail or phone in your order today and begin.

Specifications: ELF II "Beginners" Package
The computer features an RCA CMOS 1802 8 bit microprocessor addressable to 64K bytes with DMA, interrupt, 18 Registers, ALU, 256 byte RAM expandable to 64K bytes. Professional-Hex keyboard, fully decoded so there's no need to waste memory with keyboard scanning circuits, built-in power regulator, 5 slot plug-in expansion BUS (less connectors), stable crystal clock for timing purposes and a double-sided, plated through PC Board plus RCA 1861 video IC to display any segment of memory on a video monitor or TV screen along with the logic and support circuitry you need to learn every one of the RCA 1802's capabilities. The diagnostic analyzers aid in understanding and trouble shooting your ELF II, as well as other computer and microprocessor products.

Continental U.S.A. Credit Card Buyers Outside Connecticut

CALL TOLL FREE 800-243-7428

To Order From Connecticut or For Technical Assistance, Etc.,

Call (203) 354-9375

NETRONICS R&D LTD. Dept. NE 22
333 Litchfield Road, New Milford, CT 06776

Please send the items checked below:

- ELF II "Beginners" Kit \$139.95
- RF Modulator \$ 8.95

Plus \$3.00 for postage, handling and insurance
(\$6.00 Canada)

Connecticut Residents add sales tax

Total Enclosed \$

- Personal Check
- Cashier's Check/Money Order
- Visa
- Master Charge (Bank No. _____)

Acct. No. _____
Signature _____ Exp. Date _____
Print Name _____
Address _____
City _____
State _____ Zip _____

COMMUNICATIONS CORNER

Here's a window-mounted CB antenna that really performs.

HERB FRIEDMAN, COMMUNICATIONS EDITOR

BECAUSE OF THE MORE FREQUENT RE-strictions on the use of rooftop anten-nas, many hams, SWL's, and CB'ers have had to resort to the use of so-called "portable antennas;" usually an inductively loaded short antenna that is intended to clip on to a window sill or ledge. Unfortunately, if it isn't some eagle-eyed busybody who can spot No. 50 wire 100 feet in the air and run to the building's manager screaming they have found the source of all TV inter-ference (even when there isn't any), it's the lack of ready access to a window ledge that prevents many "cliff dwellers" from using some form of "window antenna."

The past summer, however, I dis-covered an effective "window anten-na" for CB, one that really works. While it's designed specifically for CB, any hobbyist that's reasonably handy with a soldering iron can fabricate a model for a VHF ham band.

The little gem that's the subject of this month's column is the Gold Line *Intenna*. Before I get into the details, let me tell you how I discovered it, since this will give you a better picture of what it can do.

I was standing in a CB/auto shop in a 4-block tourist town just chatting, and commented that when I pulled into a motel I can't keep in contact with the rest of the family when they take the car down the road to some stores and shops to pick up supplies. One of the customers breaks in to say that he had the same problem until he purchased a CB antenna that sticks to the window, even those that don't open, and he usually can get coverage up to one mile or so depending on what floor his room is on and which direction the window faces. You can just bet I had to try this gadget, but unfortunately, it wasn't the easiest to locate because CB is not the market it once was. But I finally did get hold of one, and it really works.

The Gold Line *Intenna* is essentially a half-wave loaded (dipole) antenna combined with a reflected power indicator of a standard VSWR meter. The main section is a lightweight metal cabinet that measures approximately 5 × 1.5 × 2 inches. On the back are two rubber suction cups that permit the box to be attached to the window.

Coming from each end of the box is a

32-inch long antenna element, which is actually a flexible wire with a suction cup on the end. On the bottom end of the box is a UHF (coaxial) connector to which the output of a CB transceiver is connected. The box is first attached to the window and then the antenna elements are stretched out and also attached to the window.

On the control box are two knobs labelled TUNE and the meter, which is arbitrarily calibrated from one to five. The knobs are actually mounted on the tuning slugs of variable inductors that are used as "loading" coils for the antenna elements.

The complete circuit is shown in Fig. 1. The dashed lines represent the metal cabinet. The two tuning coils are L1 and L2. The reflected power indicator is made up of L3, D1, R1, C1, and M1. Inductor L3 is really an RF pickup coil that takes a sample of the reflected power from the transmission line. Notice that loading coil L2 is actually between the antenna element and the metal cabinet. There might be some inclination to eliminate L2 and convert the design into a loaded ¼-wave vertical. It could be done, but the tuning would be even more critical and the antenna would not be as efficient for keeping the signal low to the ground.

Using the Intenna

To use the *Intenna*, the CB rig is first connected to the control box with a

length of coax cable long enough to let you keep the rig at least 10-feet from the antenna. (If you build a similar device for some other frequency, try to keep the transmitter at least ¼-wave-length from the antenna. I realize this is impossible at the lower VHF frequencies, so all you can do is try and hope. Sometimes it will work, but other times the RF feedback will do strange things to the signal—particularly to the modulation.)

Then the top antenna element is secured to the highest point on the window using the suction cup. The wire is stretched out and the control box is secured to the window. Finally, the lower element is allowed to hang down and is then secured to the window. If the element is longer than the window, the wire is simply left hanging free or it can be taped to the wall.

The transmission line must be oriented at right angles to the antenna, or as close as possible to a right angle for at least ¼-wavelength, or whatever you can squeeze in. A few strips of masking tape will easily support the RG-58 cable on a wall.

When the antenna is in place have someone key the rig. (You could do it yourself but it might prove somewhat difficult to adjust the antenna if you're also keying the transmitter.) Adjust each of the two tuning controls for the lowest meter reading. Step away from the antenna when you check the meter

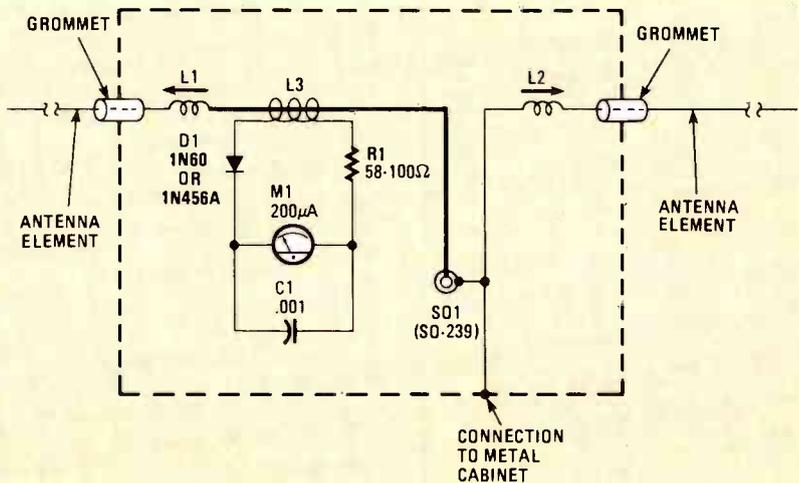


FIG. 1

Power Line Filters



These filters protect any sensitive electronic equipment from power line transient damage and radio frequency interference. Both models offer common mode and differential mode surge suppression for power line "spikes". Rf interference is suppressed using both inductive and capacitive components. Ideal for computers, test equipment or TV.

LF2 a duplex outlet, 120V, 8 amps max. \$39.95

LF6 three separately filtered duplex outlets, 120 V, total fused capacity 15 amps, power switch and indicator lamp \$59.95

Add \$2.50 shipping and handling per order.

Send check with order and provide street address for UPS shipment. Ohio residents add Sales Tax. Charge card buyers may call toll free:

1-800-543-5613



In Ohio, or for information call: 1-513-866-2421

R. L. DRAKE COMPANY

540 Richard Street, Miamisburg, Ohio 45342

INSTITUTIONAL AND DEALER INQUIRIES INVITED
CIRCLE 34 ON FREE INFORMATION CARD

reading (your body could affect the tuning). It will take a few tries to get it right, but eventually the meter will indicate near zero, or somewhere below 1/3 scale. That's it, the *Intenna* is ready for use.

As I said, CB gear isn't that easy to locate, so if you want information on pricing and availability of the *Intenna* write to Gold Line, P.O. Box 115, West Redding, CT 06896. R-E

HOBBY CORNER

continued from page 81

Since the output of the mixer can be any combination of those, you can see that it can produce very complex sounds. Even so, we can still process the sound further before it gets out of the 76477.


The signal from the mixer is fed to an envelope generator where it is shaped. Control of the envelope is determined by the binary signal on pins 1 and 28. Since there are only two pins, we are limited to just four control signals: 00 = VCO; 01 = mixer; 10 = one shot; and 11 = VCO alternating. For example, 10 (binary 2) would cause the one shot to shape the output from the mixer. Incidentally, the pulse duration of the one shot is determined by the resistor/capacitor combination on pins 23 and 24: its maximum duration is about 10 seconds.

Before the signal gets to the audio amp, there is one more opportunity to process it! You can set the speed of the leading edge (attack) and the trailing edge (decay) of the envelope by connecting resistors to pins 10 and 7 and a timing capacitor to pin 8.

Finally, the signal is fed to the built-in audio amplifier and out of the 76477. With all of those possible combinations, is it any wonder that this little IC can produce very complex sounds?

Of course, there is much more that could be said but you have enough to go on to create your own sounds using the 76477. To give you a start, the circuit in Fig. 3 can be used to generate a "laser gun" sound. R-E

The world of electronics gee-wizardry

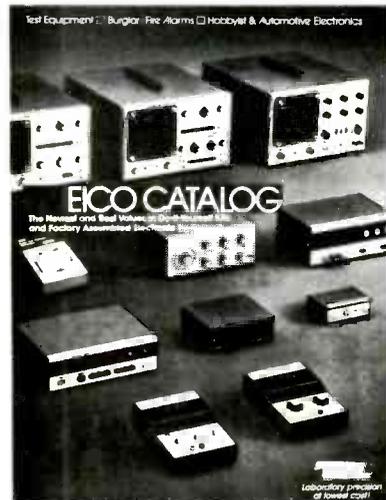

-YOURS FREE.

32-pages of test instruments — from the latest digital multimeters to the famous EICO scopes. Security systems. Automotive and hobbyist products. Kits and assembled. EICO quality. EICO value. For FREE catalog, check reader service card or send 50¢ for first class mail.

EICO® 108 New South Road
Hicksville, N.Y. 11801

CIRCLE 33 ON FREE INFORMATION CARD

IRS TAX TIP

On Tax Credits

Home Energy-Savings Credit—If you paid for insulation or other energy-saving devices, you may be able to claim a credit for these expenses.

Check your tax instructions for details.

RECEIVE A GREAT TRANSMISSION FROM SAM'S!

From its first printing in 1934 to today's newly revised 22nd edition, Sams highly popular RADIO HANDBOOK has remained the undisputed leader among textbooks in the field of short-wave radio communications.

This big, new 22nd edition explores the basic principles of radio communications, including signal propagation, equipment design and operation, and transistor and IC technology. You'll also find comprehensive comparisons of vacuum tubes and transistors, a complete discussion of amplifiers, power supplies, electronic test equipment, antenna designs, and construction techniques!

Order now and start taking the static out of your radio communication system today!



SAMS BOOKS™

Mail to: Howard W. Sams & Co., Inc., 4300 West 62nd St., P.O. Box 7092, Indianapolis, IN 46206

	Quantity
RADIO HANDBOOK—	
22nd Edition	No. 21874 \$34.95 _____
	Amount of order \$ _____
	Add handling costs \$ 2.00 _____
	Add local sales tax where applicable \$ _____
	Total amount of order \$ _____

Full payment must accompany your order.
 Payment enclosed: Check Money Order
 VISA MasterCard Interbank No. _____
 Account No. _____ Expiration Date _____
 Name (print) _____
 Signature _____
 Address _____
 City _____ State _____ Zip _____

Call toll-free 800-428-3696 for the name of your local Sams Book outlet or to order by phone. Offer good in U.S.A. only. Offer expires 4/30/82. Prices subject to change without notice. When phone ordering, give Sams Operator the code number in this box.

AD140

CIRCLE 23 ON FREE INFORMATION CARD

STATE OF SOLID STATE

SCR arrays and bar-graph displays

ROBERT F. SCOTT, SEMICONDUCTOR EDITOR

LET'S BEGIN THIS MONTH WITH A LOOK at two new SCR arrays from Sprague. They are the UTN-2886B and UTN-2888A monolithic multiple-SCR arrays designed for coupling microprocessors, demultiplexers, and similar devices to high-current loads such as relays, solenoids, and lamps. The devices feature low input-current; TTL, LS-TTL, and CMOS compatibility; 35-volts minimum forward-blocking-voltage, and a 2-amp in-rush-current capability. They can be used with either full-wave or half-wave power sources.

The UTN-2886B consists of six individual SCR's and two pairs of paralleled SCR's (pins 1-16 and 8-9). Each separate SCR can handle 250 mA—the paralleled units at pins 9 and 16 handle 500 mA—at +50°C ambient temperature. Power dissipation can be increased by attaching an external heat sink. The UTN-2888A array contains eight isolated SCR's (see Fig. 1), each capable of continuous and simultaneous operation at +50°C.

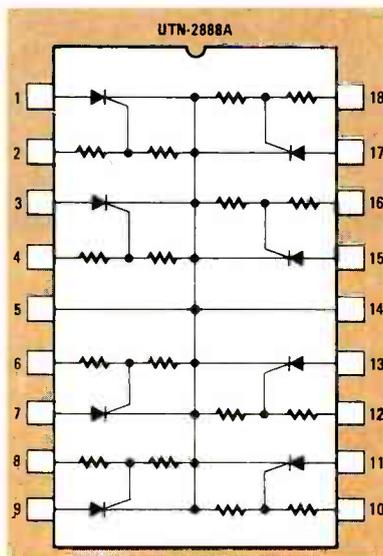


FIG. 1

Characteristics of any individual SCR (maximum limits are given unless otherwise specified) are: Forward blocking-current, 50 μ A; gate-to-anode leakage, 250 μ A; forward ON-voltage, 1.2 volts at +25°C and 1.15 volts at +55°C; gate trigger-voltage, 2.5 volts; gate trigger-current, 300 μ A; gate OFF-current, 10 μ A; holding current, 10 mA at 0°C and 5.0 mA at +55°C, and anode

OFF-voltage, 400 mV minimum.

The devices operate from unfiltered DC from half-wave or full-wave-rectified sources. They cannot be used with raw AC. In operation, the SCR is triggered ON by applying a positive voltage to its gate. It continues to conduct, even though the gate voltage is removed or made slightly negative, until the anode-cathode voltage is reduced to below 400 mV.

The diagram in Fig. 2 shows a typical application, using the SCR's as lamp

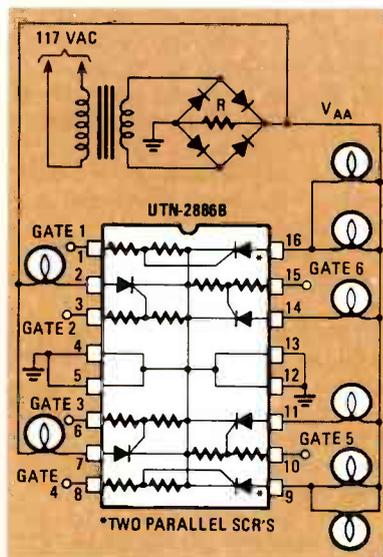


FIG. 2

drivers. When using multiple SCR's and a common V_{AA} supply, gate-to-anode leakage currents (I_{GA}) can hold the supply voltage above the anode OFF voltage, $V_{AK(OFF)}$, and prevent proper turn-off. Resistor R is connected across the power supply to insure proper SCR operation.

The maximum value of the resistor can be calculated from the following formula:

$$\frac{400 \text{ mV}}{(n-1) 250 \mu\text{A}}$$

where n is the number of SCR's being used in the system. Be sure to add 2 to the SCR count if you use the paralleled devices connected to pins 9 and 16 of the UTN-2886B.

For further information, contact Sprague Electric Co., Semiconductor

Division, 155 Northeast Cutoff, Worcester, MA 01606.

Circuit of the Month

Bar-graph displays are popular as replacements for analog meters in radios, audio equipment, etc. The bar-graph circuits are simple and easily adapted for use with existing equipment. The analog signal needs little processing before being fed to the bar-graph display.

The display may consist of a number of discrete LED's, arranged in a linear array, or you can use a 10-element device such as the HDSP-4820, HDSP-4830 or HDSP-4840 series from Hewlett-Packard. In those devices, the LED's have been matched for color and brightness. A cut-away drawing of a 10-element bar-graph is shown in Fig. 3. The light from each LED element is "stretched" by diffusion and reflection to form individual elements. The array series is available in standard red (HDSP-4820), high-efficiency red

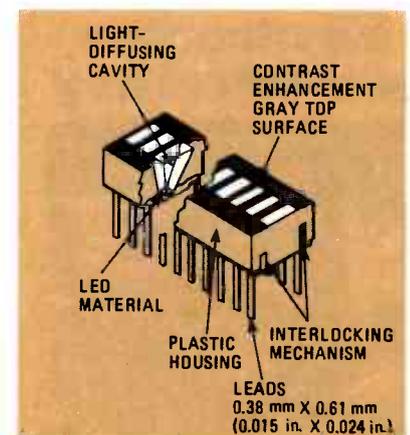


FIG. 3

(HDSP-4830), and high-efficiency yellow (HDSP-4840); the pin-outs for all three are the same.

There are a number of rather simple display-drivers for use between an analog or digital source and the LED arrays. Some display drivers or decoder/drivers provide a logarithmic display with 2- or 3-dB increments. Other drivers provide a linear display with either fixed or variable voltage increments. The drivers are made by, among others, National, Texas Instruments, Exar, Siemens, and AEG-Telefunken.

continued on page 86



Find exciting projects, troubleshooting and repair tips, and hands-on, do-it-yourself info, plus hundreds of time- and money-saving ideas in the

ELECTRONICS BOOK CLUB

Select 6 outstanding volumes for only **\$2.95** (total value up to \$114.70)

GET TWO EXCITING PROJECT BOOKS FREE!

1306 List \$15.95

1347 List \$9.95

1108 List \$11.95

1218 List \$16.95

1225 List \$15.95

1370 List \$22.95

1249 List \$15.95

672 List \$8.95

1066 List \$14.95 (paper)

1241 List \$12.95

1076 List \$12.95

1305 List \$15.95

1250 List \$16.95

1333 List \$18.95

1338 List \$19.95

800 List \$15.95

1323 List \$10.95

1233 List \$14.95

1070 List \$14.95

1062 List \$12.95

1283 List \$18.95

1330 List \$15.95

Join now . . . get two extra books absolutely free!
Modern Transistor Radios
and Modern Crystal Radios

7 very good reasons to try Electronics Book Club

Blue Ridge Summit, PA 17214

- **Reduced Member Prices.** Save up to 75% on books sure to increase your know-how
- **Satisfaction Guaranteed.** All books returnable within 10 days without obligation
- **Club News Bulletins.** All about current selections—mains, alternates, extras—plus bonus offers. Comes 14 times a year with dozens of up-to-the-minute titles you can pick from
- **"Automatic Order".** Do nothing, and the Main selection will be shipped automatically! But . . . if you want an Alternate selection—or no books at all—we'll follow the instructions you give on the reply form provided with every News Bulletin
- **Continuing Benefits.** Get a Dividend Certificate with every book purchased after fulfilling membership obligation, and qualify for discounts on many other volumes
- **Bonus Specials.** Take advantage of sales, events, and added-value promotions
- **Exceptional Quality.** All books are first-rate publisher's editions, filled with useful, up-to-the-minute info

ELECTRONICS BOOK CLUB

Blue Ridge Summit, PA 17214

Please accept my membership in Electronics Book Club and send the 6 volumes circled below, plus a free copy of Modern Crystal Radios and Modern Transistor Radios. I understand the cost of the books selected is \$2.95 (plus shipping/handling). If not satisfied, I may return the books within ten days without obligation and have my membership cancelled. I agree to purchase 4 or more books at reduced Club prices during the next 12 months, and may resign any time thereafter.

672 800 1062 1066 1070 1076 1108 1218 1225
 1230 1233 1241 1249 1250 1283 1305 1306
 1323 1330 1333 1338 1347 1349 1370

Name _____ Phone _____
 Address _____
 City _____
 State _____ Zip _____

(Valid for new members only. Foreign and Canada add 20%) RE-282

CIRCLE 14 ON FREE INFORMATION CARD

STATE OF SOLID STATE

continued from page 84

A typical bar-graph decoder consists of a set of voltage comparators and a precision voltage-driver that supplies reference voltages to the individual comparators. Figure 4 shows a representative analog-input 5-stage bar-graph-display decoder. The decoder drives the display in a logarithmic or linear manner, depending on the scaling of the reference-voltage network.

Some decoders provide displays in either bar or dot-position modes. In the bar mode, the decoder lights all the LED's whose comparator voltage-thresholds are below the level of the applied input signal. In the dot-position mode, the display shows a moving dot

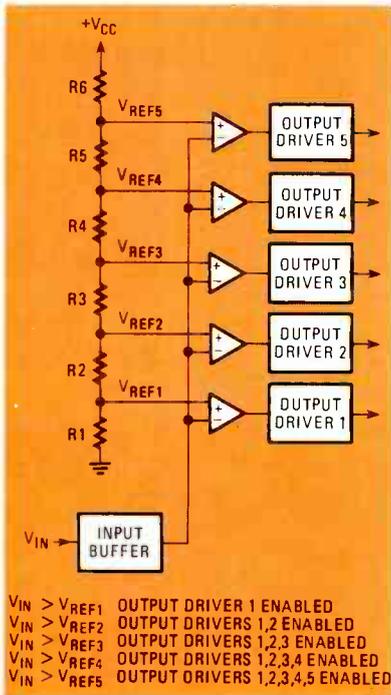


FIG. 4

whose positive is determined by the highest-threshold-voltage comparator triggered by the applied signal voltage.

Figure 5 shows a circuit that displays signal levels from zero to five volts in either a dot or bar pattern. It is based on the Hewlett-Packard 10-element bar-graph display and National Semiconductor's LM3914 dot/bar display driver. In this circuit, the display is a moving dot when the driver's MODE pin (pin 9) is tied to pin 11 and a bar graph when pin 9 is tied directly to +VCC at pin 3. (The National Data Book recommends leaving pin 9 floating for a dot display. Try it both ways.)

The incremental voltage-steps and thus the full-scale voltage, are determined by the voltage developed by the

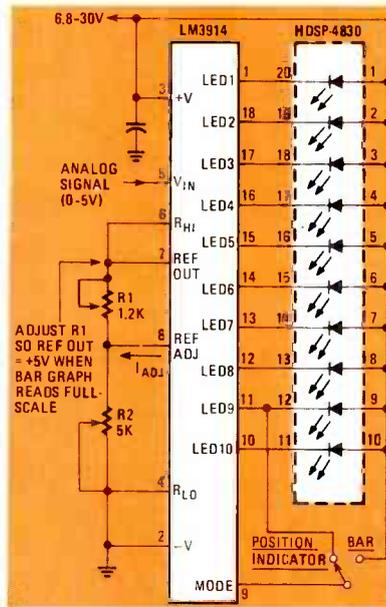


FIG. 5

internal reference source between pins 7 (REF OUT) and 8 (REF ADJ). That constant voltage forces a constant current through R1 and through an adjustable resistor, R2. Therefore the total voltage between the REF OUT pin and ground can be easily determined by using the following formula:

$$V_{OUT} = V_{REF} (1 + R2/R1) + I_{ADJ}(R2)$$

where $V_{REF} = 1.25$ volts and I_{ADJ} is $75\mu A$ typical, $150\mu A$ maximum.

The current drawn from the voltage-reference pin determines the LED current. Approximately 10 times this current passes through each lighted LED. The LED current, and thus the brightness, can be adjusted by resistor R2. With a 7-volt supply, the LM3914 dissipates approximately 110 mW in the DOT

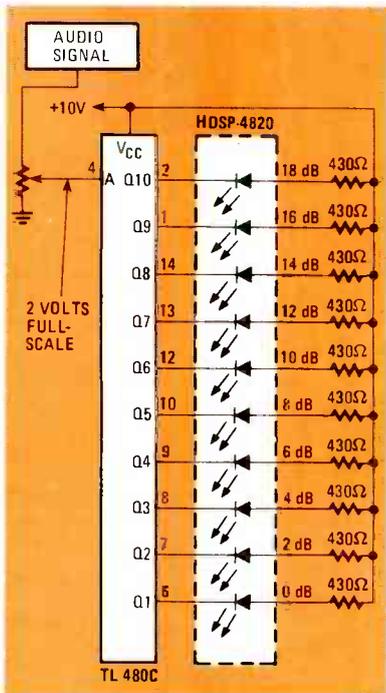


FIG. 6

mode, and around 720 mW in the BAR mode.

A low-cost VU meter is shown in Fig. 6. The bar-graph display is driven logarithmically by a Texas Instruments TL480C 10-step logarithmic analog level-detector. The device uses ten comparators to detect the level of the analog signal applied to the analog input (pin 4). Output Q1 is switched to a logic-low, turning on the 0-dB indicator LED when the input signal reaches approximately 218 mV. The comparators switch

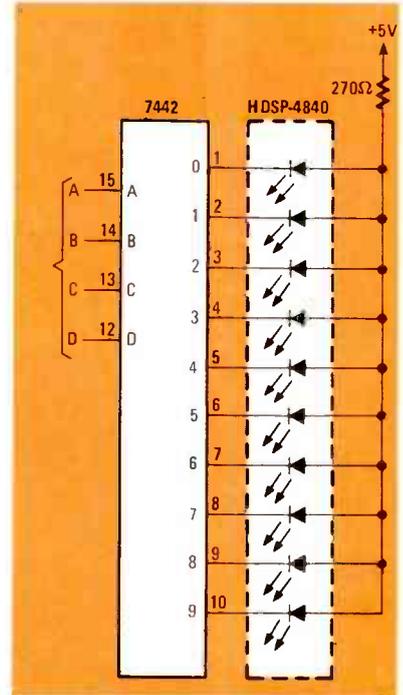


FIG. 7


in 2-dB increments until they are all low at an input value of approximately 1.732 volts.

In some systems, a BCD (Binary Coded Decimal) signal is the most convenient way to drive a bar graph. Figure 7 shows a 7442 BDC-to-decimal (1 to 10) decoder connected to drive a 10-element bar-graph display in the DOT mode. In the case of that circuit, the LED's light singly to indicate the level of the BCD signal.


The material for these circuits came from National Semiconductor's *Linear Databook* and Hewlett-Packard's *Bar Graph Array Applications*. If you want to see other applications such as "chaining" for dot or bar displays of 20 or more LED elements, or interfacing to a 6800 or 8080A microprocessor, we recommend those two publications. *The Linear Databook* is available for \$9.00 from National Semiconductor Corp., Literature Distribution, 2900 Semiconductor Drive, Santa Clara, CA 95051. The Hewlett-Packard literature is available from Hewlett-Packard Components, 640 Page Mill Road, Palo Alto, CA 94304; ask for *Application Note No. 1007* and the *10-Element Bar Graph* data sheet.

R-E

I WISH I HAD...

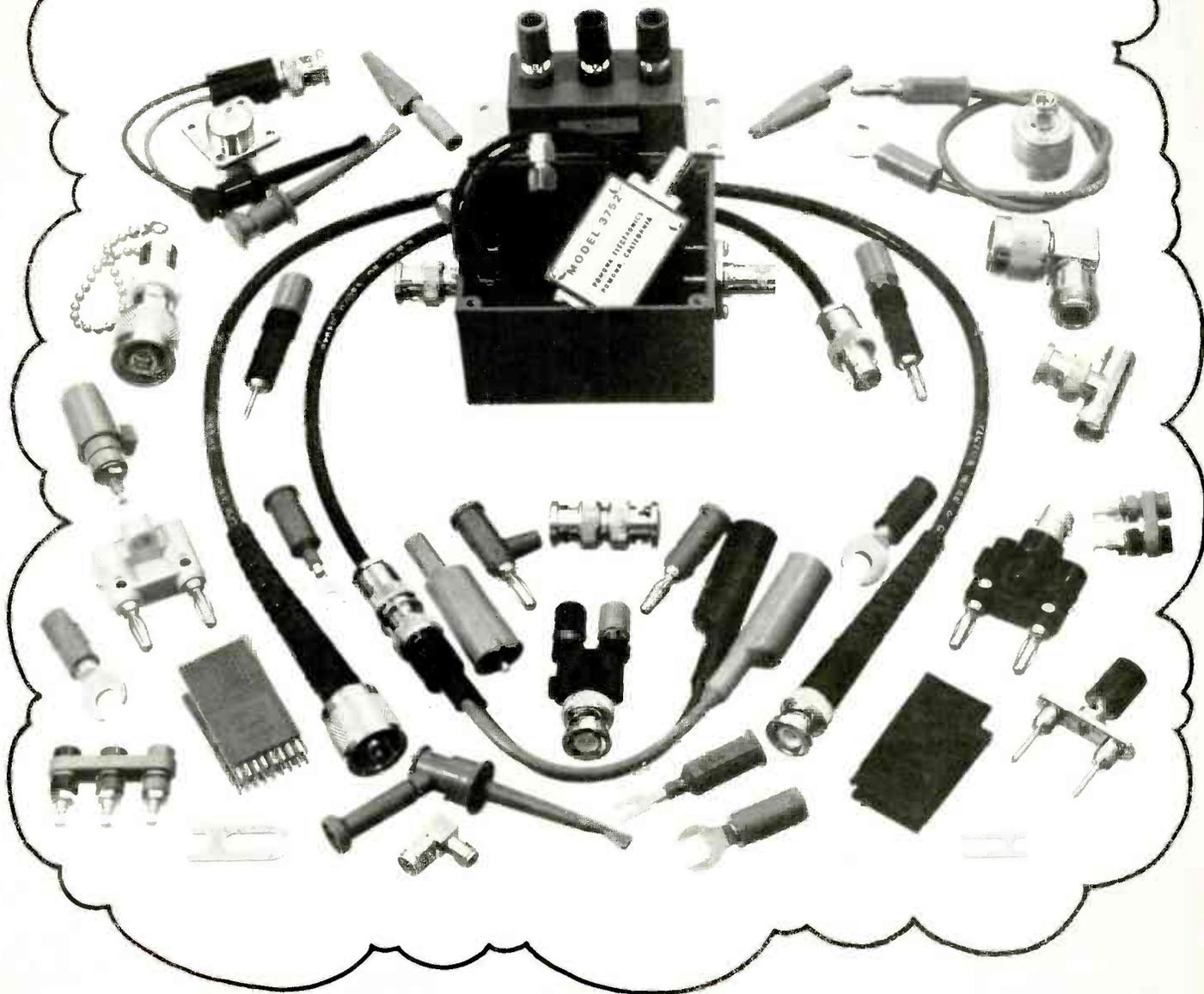

OUR WISH BOOK CATALOG HAS IT.

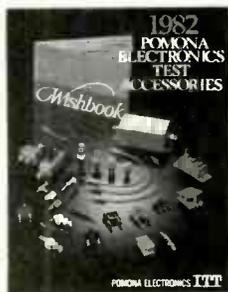

Why settle for 3 wishes. Pomona Electronics can grant you more than 650 — virtually every whim you could have for electronic test accessories. With new products like an anti-static DIP remover and a spring-loaded binding post. And favorites such as DIP CLIP™ test clips, GRABBERS™ test clips, black boxes, and shielded cables, breakouts and connectors. Plus all those many unglamorous but indispensable items you're always needing. You couldn't hope to find better quality anywhere.

So, let your first wish of the year be for an

electronic test accessory wish book—the new, 1982 Pomona catalog. Just ask for one. Your wish is our command. Full catalog also contained in EEM.

ITT Pomona Electronics, 1500 E. Ninth St., Pomona, CA 91766. Phone (714) 623-3463.

In Europe, ITT Industries Belgium S.A., Pomona Division, 250 Avenue Louise, Box 121, Brussels, Belgium. Phone 02/640. 34. 00.

PRODUCTS AVAILABLE FROM YOUR FAVORITE PARTS DISTRIBUTOR

Pomona Electronics **ITT**

CIRCLE 9 ON FREE INFORMATION CARD

COMPUTER CORNER

A world of information

LES SPINDLE*

WHEN A DISCUSSION ABOUT COMPUTERS of the future occurs, the conversation often discloses bizarre fears about a dehumanized society. In these cynical scenarios, students acquire their education awkwardly because they interact with a machine rather than a human teacher; patients have difficulty recovering from illnesses because their diagnosis is done by an unfeeling computer rather than a sensitive doctor, and social interaction suffers because people seldom have to leave their home for any purpose. Such predictions of doomsday are, of course, ridiculous. If anything, a computerized society is a more efficient society—with more leisure time for people to spend on social and recreational pursuits. A world linked via computer terminals has to do with more communication among more people—not social repression.

Computer data bases will provide much of the impetus for these improved communications by enabling a world of information to be instantaneously ac-

cessible to just about anyone. Whether practical or frivolous, vocational or recreational, social or clinical, information is immediately available from a data base. A computerized data base is essentially an electronic information file that is accessible to consumers that have a computer terminal and the necessary data communications peripherals.

They are currently over 600 commercial data bases in the U.S. alone, providing students, lawyers, farmers, computer hobbyists, stockbrokers, home consumers, and all types of business people with a wealth of vital information. The essential benefit of accessing data this way is obvious: it eliminates the time and hassle involved in searching for information sources, scanning through the sources to find specific information, and copying or transcribing that information. With a terminal and a data base, the desired information is retrieved and printed out within minutes after the appropriate information has been keyed in.

To illustrate how a data base can aid the average computer user, let's con-

sider two popular data-base networks geared towards the home user or small businessman: The Source, provided by Source Telecomputing Corp. (a subsidiary of Telecomputing Corporation of America, 1616 Anderson Rd., McLean, VA 22102) and CompuServe, Inc. (formerly MicroNet), 5000 Arlington Center Blvd., Columbus, OH 43220.

Both services were introduced in 1979 and both essentially thrive on the same premise: providing sophisticated networking capabilities to the average consumer at an affordable cost. The technology is scarcely new. Computer networking and timesharing have been used as methods of doing business for large corporations and government agencies for several years. What is revolutionary about the home-computer network concept, however, is that it demonstrates the potential for a world linked up electronically in the most widespread mass-communication network conceivable. Like television, radio, the telephone, and every other mass-communication technology that has come along, the home computer will not become a true social phenomenon or booming economic industry until it is affordable by the average consumer. The computer is now affordable to a large number of consumers, but the telecommunications technology must catch up.

What makes CompuServe and the Source work is the fact that it is offered at a discount rate during hours that are not marketable for "nine-to-five" business transactions. During peak hours, the mainframe computers are heavily in demand by corporate clients. By tapping the heretofore little used evening and weekend hours, which coincide with the ideal time for consumer usage, the networks can offer the mainframe computer capabilities—and the special consumer data bases—at a much lower price.

The CompuServe network is available between 6 PM and 5 AM weekdays, all day weekends and holidays. Cost is \$5 per hour. At all other times, the rate is \$22.50 per hour. For The Source, a one-time registration fee of \$100 is required. From 7 AM to 6 PM on Monday through Friday, the fee is \$15 per hour. From 6

continued on page 92

*Associate Editor, Interface Age Magazine

>DATA LIBALL

*** THE SOURCE ***

ADVANCED APPLICATIONS & PROGRAMS.....	DATA ADAPPR
AIRSCHEDULES.....	DATA AIRSCHED
ANNOUNCEMENTS (UPDATED FREQUENTLY).....	DATA ANNOUN
ASTROLOGY LIBRARY.....	DATA ASTRO-LIB
AWARE FINANCIAL SERVICE.....	DATA AFS
BUSINESS & FINANCE.....	DATA BIZDEX
CLASSIFIED ADS & BULLETIN BOARD.....	DATA CLASSI
CONSUMER INFORMATION.....	DATA CONSUM
CROSS X-ASSEMBLERS.....	INFO X-ASSEMBLERS
DINING OUT..(WASHINGTON, D.C.).....	RESTGD
DISCOUNT SHOPPING SERVICE (MONEY SAVERS).....	DATA BUCKS
EDUCATION.....	DATA EDUCAT
ENERGY SAVING NEWS & TIPS.....	ENERGY
FINANCIAL NEWS.....	DATA BIZDEX
GAMES.....	DATA GAMES
HOME ENTERTAINMENT.....	DATA HOMET
INFORMATION ON DEMAND.....	DATA IOD
MAILCALL.....	DATA MAILCALL
MAIL DELIVERY.....	INFO DATAPOST
NEW YORK TIMES NEWS SUMMARY.....	DATA NYTNS
NEW YORK TIMES CONSUMER DATA BASE.....	NYTCDB
POLITICAL ACTION REPORT.....	DATA PAR
PERSONAL CALENDAR & NOTEBOOK.....	DATA PERSON
PERSONAL FINANCE.....	DATA PERSFI
SCIENCE & ENGINEERING.....	DATA SCIENG
SELF-PERCEPTION.....	DATA ESP, DATA LORE
SPORTS.....	DATA SPORTS
SUGGESTION BOX.....	DATA SUGBOX
TRAVEL CLUB.....	DATA TRAVEL
UNITED PRESS INTERNATIONAL (UPI).....	DATA DANEWS
USER DIRECTORY.....	DATA USEDIR
VOICEGRAM.....	DATA VOICEGRAM
WEATHER.....	DATA WEATHR
WISDOM OF THE AGES.....	WISDOM

FIG. 1

Innovations

Complete Satellite Receiver System brings you movies, concerts, sports events.*

The Heathkit Earth Station includes a heavy-duty, 3-meter antenna, an integrated low-noise amplifier/down-converter, and a receiver with electronically-synthesized tuning for stable, drift-free reception. 24 channels let you receive just about everything the satellites have to offer. Special *Earth Foundation Kit* anchors your antenna firmly to withstand winds of up to 100 mph. And it's all yours at a very affordable price.

Complete computer system in one compact unit.

The Heathkit All-In-One Computer takes the guesswork out of selecting a balanced computer system. It includes built-in floppy disk drive, smart video terminal, heavy-duty keyboard, 12-key numeric pad, two Z80 CPU's, and 48K RAM—all in one compact unit. Save 30% over comparable assembled units. Heath makes it easy to build with detailed, step-by-step assembly manuals that anyone can follow. A complete line of software for home, work and play is also available.



The first fully programmable keyer stores commands as well as text.

You HAM's will love the Heathkit μ Matic Memory Keyer with custom microprocessor to store up to 240 characters of text or commands. *Variable-length buffers* eliminate wasted memory space. *Command strings* take several text buffers and string them together in any sequence for most efficient use of memory. Command strings can also select speed, weight, spacing and auto-repeat count. *Integral capacitive touch paddles* unplug and store in their own compartment. Put the fun back in CW.

Solar Water Heater saves you up to 80% on hot water costs.

As fuel costs rise, the Heathkit Solar Water Heater keeps paying you back. Because you build it yourself, you build it better, for less. And with Federal and State tax credits, solar pays for itself in no time. Based on computerized data, we help you select the correct system size to produce 50 to 80 percent of the annual BTU requirement for water heating, based on available sunlight in your area. So you know it's practical before you buy. The system includes solar panels, pumps, heat exchanger, storage tank, and complete assembly and installation instructions.



Free Catalog

See all the newest innovations in build-it-yourself kits in the new, free Heathkit Catalog.



Heathkit®

If coupon is missing, write Heath Co.
Dept. 020-862, Benton Harbor, MI 49022
In Canada, write Heath Co.
1480 Dundas Highway East,
Mississauga, Ontario L4X 2R7.

Heathkit Products are displayed, sold and serviced at Heathkit Electronic Centers† in major cities in the U.S. and Canada. See your telephone white pages for locations.

†Units of Veritechnology Electronics Corporation in the U.S.

*Viewing of some satellite TV channels may require the customer to obtain permission from, or make payment(s) to, the programming company. The customer is responsible for compliance with all local, state and federal governmental laws and regulations, including but not limited to construction, placement and use. For use only in Continental U.S.

Send to: Heath Co., Dept. 020-862,
Benton Harbor, MI 49022.

Yes. Send me a Heathkit Catalog.
I am not currently receiving one.

Name _____

Address _____

City _____ State _____

CL-753 Zip _____

CIRCLE 92 ON FREE INFORMATION CARD

COMPUTER CORNER

continued from page 88

PM to 12 AM on weekdays and all day on weekends, the cost is \$4.25 per hour. From midnight to 7 AM daily, the cost is \$2.75 per hour.

For hookup, the basic requirements for both networks include a terminal, a 300-baud modem (communications interface) and a telephone. Upon registration, the user receives an information packet including a user's manual, an index of data bases and services, an account number, and a private pass-

word. The system is accessed by dialing an assigned phone number, waiting for the tone to commence, placing the receiver in the modem, then entering the I.D. number and password. The modem translates electrical signals into sounds, and vice versa, to communicate with the host computer, or other computers plugged into the network. When a set of instructions appears, the user is told how to proceed in order to access the services or data bases he desires. Now he is ready to begin his interaction with the network.

By providing the possibility of terminal-to-terminal communication among the various subscribers, the network

has the potential to achieve a communication method with mass appeal. Beyond providing a fun communication source among users in true CB-radio tradition, the network can function as a virtual electronic library and shopping center. The subscriber can browse through merchandise catalogued into specific programs, and even order the products directly through the terminal. If computer art is of interest to him, for example, he can browse through CompuServe's art-gallery listing and order a computer-generated picture for future delivery. Also available are programs on stock market data, filing capabilities for information storage, financial advice, games, educational aids, theater and movie reviews, news, weather, and sports.

The advantages of such a time-sharing network for the home user or small business are numerous and varied. As the programs and subscriber services become more diverse and useful, it is not hard to imagine that having a personal computer in every home, hooked up to major mainframe data bases, will eventually be as commonplace as a television or a telephone.


Electronic mail, for instance, is no longer a service strictly for major corporations. Exciting new directions for inexpensive mass communication at all levels of business and consumer usage are now evident. Even personal correspondence can be less expensive through a computer network than by a long distance phone call, although the personal interaction, in some cases, is obviously preferable.

The process of ordering merchandise can be streamlined. The home consumer can do tedious shopping for groceries or household goods without ever leaving the home. Such services, of course, are still somewhat limited, but expansion in this area is certainly inevitable as more homes become equipped with computer terminals.

Both CompuServe and The Source emphasize their extensive stock market services. CompuServe's *MicroQuote* includes information on over 32,000 stocks. A recent survey by The Source indicated that a large percentage of its subscribers sign up for the stock market facilities alone.

Because new data bases are constantly being added, both networks distribute a monthly news magazine to subscribers, detailing the latest services. The master index for CompuServe lists over 350 separate data bases with a wide range of subjects: adventure games, child care, want ads, tax advice, gold prices, text from various newspapers including the *Washington Post*, and photography. Among services described in the latest issue are a guide to admissions information and entrance

continued on page 102

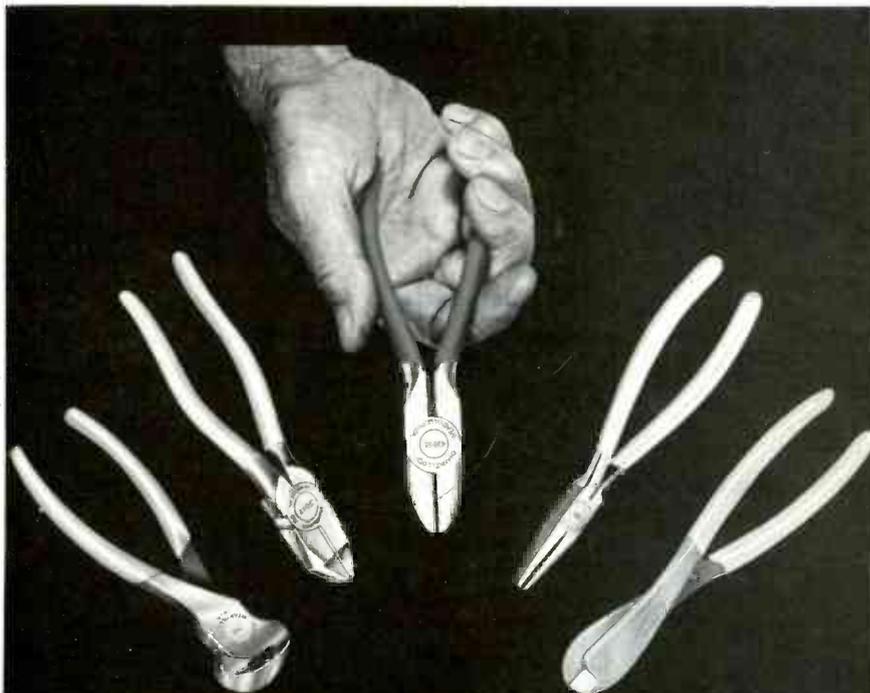

There's Never A Dull Moment With One Of These On The Job

Keen enough to cut a human hair, tough enough to cut piano wire - cleanly, quickly, time after time, year after year. Cutting pliers by CHANNELLOCK. Hand honed, perfectly mated cutters scientifically heat treated to hold their edge. Precision made of highest grade forged steel. Beautiful high polished finish. Blue dipped plastic comfort grips. Quality in every detail (at no premium in price). CHANNELLOCK. Be sure that name is on the pliers you buy.

CHAN NEL LOCK

CHANNELLOCK, INC. • Meadville, Pennsylvania 16335

Meet The Rest Of The Family. Send For Free Catalog.

CIRCLE 19 ON FREE INFORMATION CARD



Solve your perplexing paging problems...

No one microphone is correct for every paging situation—different circumstances require different and sometimes unique solutions. That's why Shure has drawn on its unparalleled knowledge of microphone design to create a series of paging microphones specifically designed to reduce or eliminate the most common paging problems.

- If you're facing high ambient noise levels, use the Model 562;
- moderate background noise levels require Model 515SBG or 515EB-G1E
- for permanent mounts, Model 561;
- mobility for paging or dispatching calls for Model 450;
- if you have limited space,

use Model 414B; • an excellent limited space model that can stand up to extreme abuse is Model 507B; • and if these won't solve your problem, read on.

...by the book

For all the facts on Shure's full line of paging microphones fill out and return the coupon below for your FREE copy of our new 72 page catalog describing over 150 microphones. No matter what your needs, there's a Shure microphone right for you.



The Sound of the Professionals®

Shure Brothers Inc., Dept. 63, 222 Hartrey Ave., Evanston, IL 60204
 In Canada: A. C. Simmons & Sons Limited
 Manufacturer of high fidelity components, microphones, loudspeakers, sound systems and related circuitry.

Yes, send me your new Full Line Microphone/Circuitry Catalog, AL700. (Outside the U.S., enclose \$2.00 for postage handling.) PLEASE PRINT

Name _____

Address _____

City _____ State _____ Zip _____

N/2/82

CIRCLE 11 ON FREE INFORMATION CARD

NEW IDEAS

Automobile ignition substitute

HERE'S A DEVICE THAT CAN HELP YOU find out what's wrong when suddenly one morning your car refuses to start. The ignition substitute described here can even be used to verify that repair work done to your engine by someone else has been done correctly.

Basically, the ignition substitute provides a constant power-source for the ignition coil. Its frequency (0.5-1.0 kHz) is that used by an 8-cylinder engine with an idling speed of 650 RPM, and the unit provides a rapid spark at a 17% duty cycle, while nonetheless staying within the power-dissipation limits of the components.

Construction is straightforward, and any method can be used. The circuit, shown in Fig. 1, consists of a 555 timer IC configured as an astable free-running multivibrator that is used to drive a high-current NPN transistor, such as a 2N6384. (That transistor should be heavily heat-sinked because it may be drawing several amps over quite a long period of time.)

The coil ballast can be from 0.68 to 6.5 ohms, depending on what's available. The 2.5-ohm, 20-watt ballast shown in Fig. 1 works well. All the other resistors can be either 1/4- or 1/2-watt devices, and the capacitor between pins 1 and 5 of the 555 can range from 0.01 to 0.05 μ F. Do not omit the 100-volt, 0.05 μ F capacitor across the transistor; it prevents voltage spikes from damaging the device. Use 4-foot-long clip leads to obtain power directly from the automobile's battery; that length is suggested for convenience.

You can use either your car's own

ignition coil, or a separate one. If you choose the latter, be sure to disconnect the one in the vehicle. A good coil will produce a spark between the high-tension lead and ground about 1/4- to 1/2-inch long, and a strong bright spark across a plug with a gap smaller than 0.040-inch. That, by the way, is the first test for ignition problems.

To determine whether there's a problem with the car's distributor, supply a spark derived from the ignition substitute to the center distributor lead leading to the rotor and slowly rotate the distributor cap. Crank the engine and, at some point, the engine should catch and run. If the engine cannot be started, but seems to be trying to, the problem is probably in the timing chain, valves, camshaft, or elsewhere. If the engine doesn't even try to start, inspect the rotor, cap, wires, and plugs for damage. Once the ignition problem has been found and corrected, the normal procedure for setting the timing and dwell should be followed.

Do not attempt to adjust the distributor using the ignition substitute. That can not be done because the spark the substitute produces is slightly different from that produced under normal conditions.

Although designed for an 8-cylinder engine, this device can be used with other types. In addition, a neon bulb can be added to the circuit to verify the presence of a spark, and, in fact, can be used as a timing light if placed close to timing marks that have been painted white with fingernail polish.

—Stan K. Stephenson II


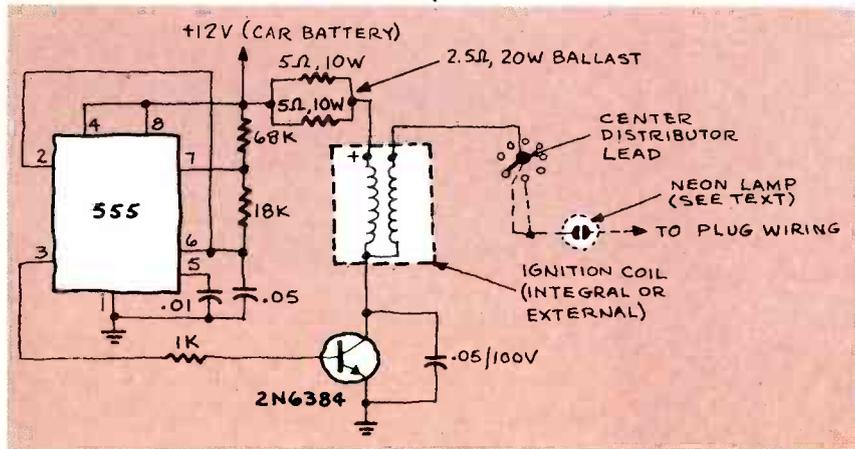


FIG. 1

NEW IDEAS

This column is devoted to new ideas, circuits, device applications, construction techniques, helpful hints, etc.

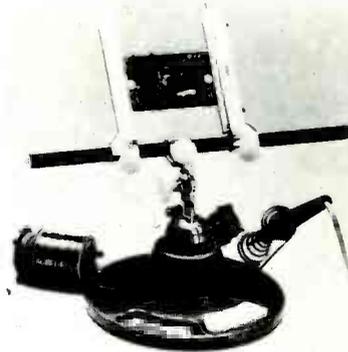All published entries, upon publication, will earn \$25. In addition, Panavise will donate their model 324 Electronic Work Center, having a value of \$49.95. It combines their circuit-board holder, tray base mount, and solder station (see photo below). Selections will be made at the sole discretion of the editorial staff of **Radio-Electronics**.



I agree to the above terms, and grant **Radio-Electronics** Magazine the right to publish my idea and to subsequently republish my idea in collections or compilations of reprints of similar articles. I declare that the attached idea is my own original material and that its publication does not violate any other copyright. I also declare that this material had not been previously published.

Title of Idea

Signature

Print Name

Date

Street

City

State


ZIP

Mail your idea along with this coupon to: **New Ideas Radio-Electronics**,
200 Park Ave. South,
New York, NY 10003

FEBRUARY SPECIALS

WE CARRY THE COMPLETE LINE OF ATARI SOFTWARE, PERIPHERALS AND ACCESSORIES.

EPSON MX-80

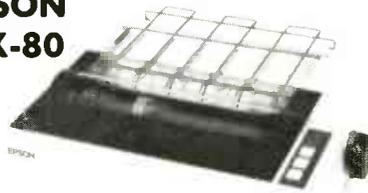

INTERFACES & CABLES

APPLE INTERFACE & CABLE \$90.
IEEE \$55 RS-232 \$70.
TRS-80 CABLE \$35.

\$449.00

NEC GREEN 12" MONITOR JB 1201M



\$159.00

PERSONAL COMPUTERS

CBM 8032 Computer	1149.00	NEC PC-8023 Printer	\$629.00
CBM 8050 Disk Drive	1349.00	NEC 5510 Spinwriter (7710)	\$2345.00
CBM 4032 Computer	1029.00	NEC 5520 Spinwriter (7720)	2695.00
CBM 4040 Disk Drive	1029.00	NEC 5530 Spinwriter (7730)	2345.00
CBM 4022	649.00	NEC JC 1201 M(A) — Color 12" Monitor	359.00
CBM VIC-20	269.00	NEC 12" JB1201M Monitor	159.00
Amdek 100G	169.00	Okidata Microline-80	379.00
Amdek Color — 1 13" Color Monitor	329.00	Okidata Microline-82A	499.00
Microtek 16K Ramboard for Atari 800	79.00	Okidata Microline-83A	729.00
Microtek 32K Ramboard for Atari 400 and 800	149.00	Diablo 630	1995.00
Qume Sprint 9/45 (Full Panel)	2295.00	Apple II Plus 48K	1199.00
Atari 400 16K	349.00	Apple Disk w/3.3 DOS Controller	569.00
Atari 825 Printer	599.00	Apple Disk w/o Controller	469.00
Atari 850 Interface	139.00	Hazeltine 1420	799.00
Atari 810 Disk Drive	449.00	Northstar Horizon II 32K QD	2925.00
Atari 800 16K	749.00	Anadex DP-9500/9501	1249.00
Epson MX-70	349.00	Telvideo 910	559.00
Epson MX-80	449.00	Televideo 912C	669.00
Epson MX-80 FT	549.00	Televideo 920C	729.00
Epson MX-100 FT	729.00	Televideo 950	929.00



OKIDATA MICROLINE 80 MATRIX PRINTER \$379.00



ATARI 810 DISK DRIVE \$449.00



AMDEK COLOR-1 MONITOR \$329.00



EPSON MX-100 FT PRINTER \$729.00

PRICES ARE SUBJECT TO CHANGE WITHOUT NOTICE

CALL OMEGA TOLL FREE!

WEST COAST

1-800-235-3581

OMEGA SALES CO.
3533 Old Conejo Rd. #102
Newbury Park, CA 91320
1-805-499-3678

CA. TOLL FREE 1-800-322-1873

EAST COAST

1-800-556-7586

OMEGA SALES CO.
12 Meeting Street
Cumberland, RI 02864
1-401-722-1027

OMEGA SALES COMPANY



We Accept C.O.D.'s • Stock Shipments Same Day or Next • No Surcharge for Credit Cards
• All Equipment Factory Fresh w/MFT Warranty • We Carry the Complete Line of Personal Software
• Prices do not Reflect Shipping Charges
Rhode Island and California Residents please add 6% Sales Tax

SERVICE CLINIC

Solid-state vertical-sweep circuits

JACK DARR, SERVICE EDITOR

TUBE-TYPE VERTICAL-SWEEP STAGES ARE familiar to all the old-timers, and to most of the younger gang. They generally consisted of a high- μ triode and power pentode (often in the same "bottle"), a matching transformer, and a fairly-high-impedance yoke. The tubes were coupled by a feedback loop, so they served both as oscillators and as output stages.

Solid-state sweep stages perform the same functions, of course, but their designs may vary from manufacturer to manufacturer. Furthermore, the symptoms that they show when something goes wrong are not usually what you used to see in tube-type circuits—about the only familiar one is the thin white horizontal line indicating a total lack of vertical sweep.

A solid-state sweep circuit uses several small-signal transistors as oscillators, wave-shapers, drivers, etc. The output stage is a type familiar to anyone who has worked on audio equipment—a two-transistor "stacked totem-pole," or complementary-symmetry type. The yoke is fed from the junction of the two power transistors; it's usually a fairly-

low-impedance type, driven directly through a very large electrolytic coupling capacitor.

A variation on that is used in some sets—they use a complementary-symmetry pair, with a dual-polarity power supply. Figure 1 shows a circuit of that type, used in a General Electric QB chassis. The output pair there is Q267 and Q268. Note that there is no large coupling capacitor. The reason for that is that the junction of the two transistors is at ground potential, or very close to it.

Both circuit-types do the same thing—they deliver voltage, in the form of a square wave, to the yoke. When you feed such a square wave into an inductance (like the yoke) you get a sawtooth wave, which is what's required.

Two-transistor circuits seem to be almost universal these days. In some early sets, though, a single transistor was used, with a "loading choke" for matching and for the DC supply, and a blocking capacitor. That circuit operated in the class-A mode, like the tube types; the two-transistor circuits operate in class-B fashion, with each device

amplifying one half-cycle of the driving signal.

An oscilloscope is invaluable for working with transistor sweep-circuits. Begin with the oscillator, make sure it's running—and on frequency. There may be several amplifier (and other) stages between the oscillator and the output stage, so just follow the signal through them to the yoke.

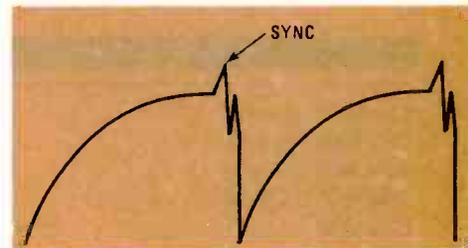


FIG. 2

You'll find one waveform at some points that you'll never see in tube-type circuits—a perfect sawtooth. With tubes, the signal on the oscillator grid (Fig. 2) shows the familiar rising curve with a spike at the top. Solid-state oscillators, on the other hand, show a

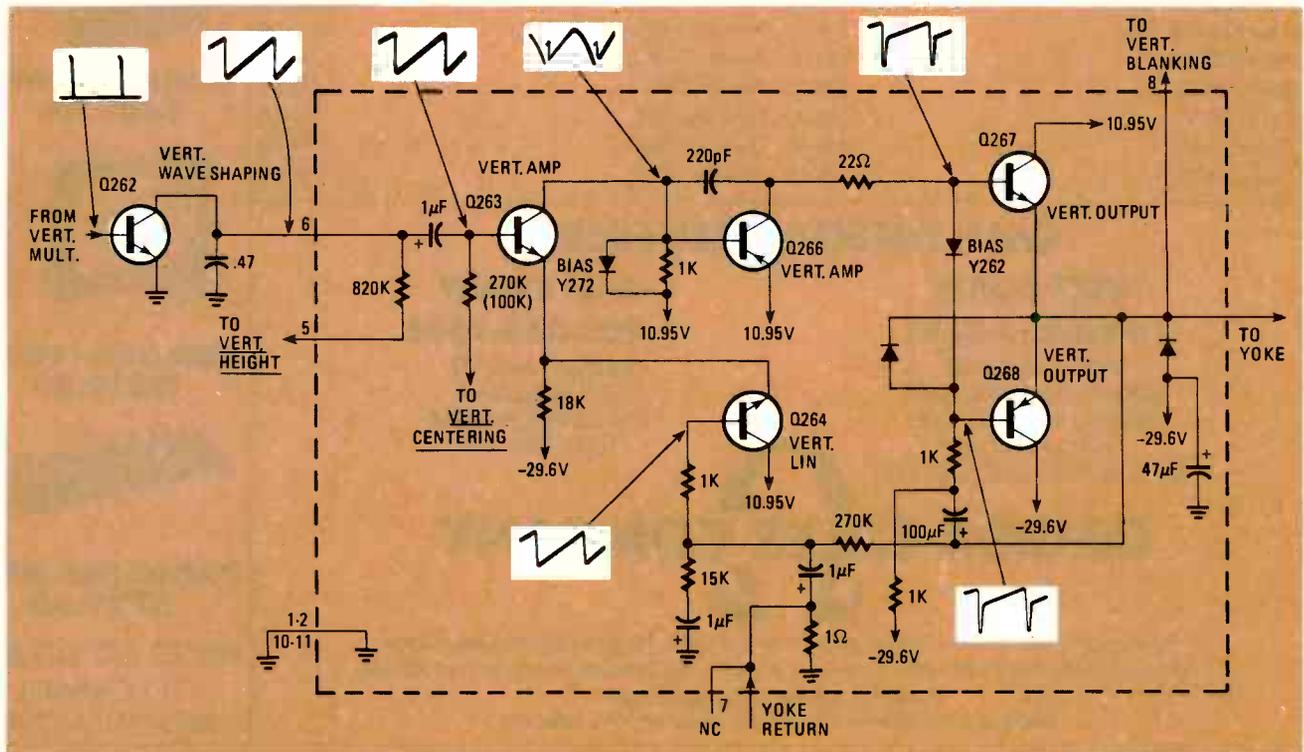


FIG. 1

series of pips, as can be seen in Fig. 1. A sawtooth wave is developed from them by a stage called a "wave shaper." The normal drive waveform on the bases of the output transistors is almost the same as in tube sets—a trapezoidal wave. In late-model sets you may find all of the stages, except for the output transistors, on a single IC. When checking this type of circuit, be sure that all the waveforms are correct, that all of the external components are OK, and that the proper DC supply-voltages are present before changing the IC.

Yoke returns

The vertical-yoke winding must return to ground, or to a level defined as a common ground. In quite a few circuits, a large blocking-capacitor is used between the bottom end of the yoke and ground. If it opens, there's no sweep, so always suspect it in such cases.

In many sets using circuits like the one in Fig. 1, you'll find the yoke return coming back to the module and running to ground through a 1-ohm resistor (R288). You must see a sawtooth waveform at the top end of that resistor; it's developed by the sawtooth current flowing through it. That current is fed to the base of a separate transistor, Q261, labelled "Vert. Lin." The reason for that is that all solid-state stages of that type are slightly non-linear! They develop a slight bend in each half of the waveform, causing what is known as "S-bending." The extra transistor and the feedback network are used to correct for that, and the end result is a perfectly linear sawtooth wave. If you run into a linearity problem, always remember to check that feedback resistor. Leakage and other defects there can cause some weird problems.

The feedback from that stage is applied to the emitter of the first vertical amp. The troubleshooting logic is clear: If the problem is linearity, go to the stage that's supposed to correct it.

Dual-polarity DC power-supplies can cause a symptom that would not be believed by a strictly tube-type technician. I know that the first time I saw it I said, "That *can't* happen!" The symptom is a perfectly good raster, but with only the top half of the picture present. That's all—there's no severe compression or other effect, as there would be in a tube set with a similar problem. The bottom half just *isn't there*.

The problem is either a loss of the DC supply to the "bottom" transistor (Q268 in Fig. 1) or the loss of the -29-volt supply to it. One other possibility exists: In the set where I first saw the problem, the vertical-sweep circuit was on a small module. The output transistors were clamped to one end of it and their leads went into individual socket-pins on the chassis. That was fine, ex-

cept for the fact that the emitter lead of the "bottom" transistor was not in its socket. It was leaning on the outside of the pin, and making contact intermittently. Plugging the module (and the transistor) in properly restored things to normal. You may find that type of situation in sets with bad solder joints at one of the pins of the output transistors, so check for it.

In quite a few popular circuits, you'll find the signal passing through little low-voltage electrolytic coupling capacitors. If you're getting no signal to the output stage, check to make sure that one of them isn't open. You can do that instantly with a scope: If a signal's going in but not coming out, you've found at least part of your problem.

Here's another problem that's also common in audio circuits: If your symptoms include distortion at the center of the screen—compression or stretching of the picture—check to make sure that the bias diodes in the output stages are good. Failure of one or more of them can cause crossover distortion in audio, and also in TV sweep circuits. **R-E**

SERVICE QUESTIONS

VCR PLAYBACK PROBLEM

I have a Toshiba V-8000 VCR and an RCA CTC-25. If I record a program off the air, it will play back nicely. However, if I try to play back a pre-recorded tape, I can't get a stable picture. I had the set checked, and it's OK. Tried out the VCR with some newer sets, and it played fine. What's going on?—D.B., Memphis, TN

I've heard of that problem before. Apparently in older sets the horizontal AFC time-constant was considerably longer than the one used today, to make the set a little less susceptible to such things as airplane flutter, etc. However, the sync on pre-recorded tapes requires the shorter time constant. As a fix, try varying the size of C82/R124, or C23/R126 on the grid of the AFC tubes.

(Feedback: We tried both capacitors, and wound up taking them out completely. When we did that, the tapes played back perfectly, but we lost the sync on a broadcast signal after about five minutes. We took care of that by connecting the capacitors to a DPST switch so that they can be switched in and out of the circuit. Everything works fine now—thanks!)

COLOR BARS

This Magnavox T-982-12 makes its own color bars! The bars—blue, green, and red from left to right—divide the screen into thirds and are present all the time. When I

NOW, a mini-scope with the features most wanted by field engineers!



B&K-PRECISION MODEL 1420 \$825

This new 15MHz dual-trace mini-scope was designed by B&K-PRECISION engineers to respond to the special needs of field engineers... a mini-scope with lab-scope features.

It easily fits into a standard attache case with plenty of storage room for a DMM, tools and accessories. The 1420 can be powered from the AC line, 10-16VDC or an optional internal battery pack.

The rugged 1420 features dual-trace operation and an honest 15MHz response, with useful response beyond 20MHz. An efficient rectangular CRT displays waveforms with good readability under all field service conditions.

There is no sacrifice of features or performance for compact size. The 1420 has 18 sweep ranges from 1 μ S/div. to 0.5S/div. in a 1-2-5 sequence; variable between ranges. Sweep magnification is X10, extending the maximum sweep rate to 100nS/div. For use with computer terminals or video circuits, a video sync separator is built in. Automatic selection of chop and alternate sweep modes is provided, as is front-panel X-Y operation.

The Model 1420 measures only 4.5 X 8.5 X 12", weighs 7.75 lbs., with batteries and comes with two 10:1 probes.

FOR IMMEDIATE DELIVERY contact your local distributor or call TOLL-FREE, 800/621-4627 for a 16-page catalog brochure on the complete B&K-PRECISION oscilloscope line.

BK PRECISION
DYNASCAN
CORPORATION

6460 West Cortland Street
Chicago, Illinois 60635 • 312/889-9087
Int'l. Sls.: 6460 W. Cortland St., Chicago, IL 60635
Canadian Sales: Atlas Electronics, Ontario.

use a color-bar generator, all of the colors are wrong. Nothing I've tried, including purity, will get rid of the bars. Incidentally, the waveforms out of the demodulator module are normal. Can you shed some light on what's going on?—M.D., Aberdeen Proving Ground, MD

I ran into something like this in a Philco. In that case half the screen was blue and the other half gold. Eventually found the source to be an open bypass-capacitor on the screen grid of the second color-bandpass amplifier. Since you've checked the DC-power supply with a scope, try checking all of the bypassed points in and around the color-amplifier stages, bandpass, etc. There

should be no signal on any bypassed point, so look for a signal where it does not belong.

Since the three color-amplifier stages are separate, the cause of this should be something that is common to all. For example, check to see if there's anything odd in the video feed to those stages.

MORE ON "REDUNDANT" CAPACITORS

Here's a test that was shown to me by a technician for Hollander and Co. of St. Louis, Mo. This is for those Zenith chassis that use several parallel

shunt-capacitors in the collector circuit of the horizontal-output stage. If the high voltage measures too high, one or more of those capacitors may be bad. To test, connect new capacitors in parallel with the ones already in the set. The high voltage should drop to normal, or lower. Now, disconnect the original capacitors one-by-one until you find one that has no effect on the high voltage—that's one of the bad ones. That procedure is almost as fast as using a capacitor tester, and it can be done under "normal" operating conditions.

Most of those capacitors are Zenith 22-5001's. Those are .0018 μ F, 1600-volt units, but they use a special dielectric; ordinary 1600-volt units won't work. For an inexpensive replacement, use a Sprague PP16-D18. The Sprague catalog lists a lot of those; they are *Metfilm* and *Filmite* types.

DEAD SHORT

This CB is driving me crazy. It's got a dead short somewhere but I can't find it. My tests show no short to ground anywhere. Any ideas that you might have would be appreciated—W.G., Kingston, NY

We've run into something like this before. Check the "protective diode" used in the crowbar circuit; it's a Zener. It will test out OK on an ohmmeter, but when voltage is applied it becomes a "0-volt Zener!" A crowbar circuit is exactly what the name implies: If anything goes wrong, it is supposed to break down and short the DC supply to ground. That one may be getting a little bit too eager and breaking down too quickly.

FLYBACK SUBSTITUTE

I asked you about a replacement transformer for a Broadmoor 6911-C, and you said you didn't have any information on it. I wrote to Thordarson-Meissner, and they had one! (It's a FLY-677, if anyone else needs one.)—James E. Higley, Hanover Park, IL.

LEAN ON IT

I wrote you a while ago about a Sharp TV-96P with weak audio, and thought you'd like to know that I fixed it. I tried everything I could think of, and everything you suggested, without any luck. Then, while checking around the second IF tube, the sound suddenly came in loud and clear.

It seems that this happened when I inadvertently leaned on the chassis, which suggested a bad solder-joint. Even though the joints looked good. I reworked about 15 of them and turned the set back on. It worked perfectly. A simple—but not immediately obvious—solution.—L.P., Potomac, MD R-E

Electronics Paperback Books

Quality Paperbacks at Affordable Prices

CHECK OFF THE BOOKS YOU WANT

Electronic Timer Projects
ELECTRONIC TIMERS & BOATS \$5.00. Packed with 15 fairly simple projects. Includes stripboard layouts. All circuits are 12V designs.

Digital IC Projects
ELECTRONIC TIMER PROJECTS \$5.00. 96 pages of projects. All kinds of timing circuits for all kinds of needs.

IC LM3900 Projects
DIGITAL IC PROJECTS \$4.95. Simple and advanced projects based on digital IC's. We count 28 different circuits.

IC LM3900 Projects
IC LM3900 PROJECTS \$3.50. A very versatile op-amp with audio, linear, digital and signal generator applications you'll want to try.

Second Book of CMOS IC Projects
SECOND BOOK OF CMOS IC PROJECTS \$3.75. Multivibrators, amplifiers and oscillators. Trigger devices and special devices are described.

Power Supply Projects
POWER SUPPLY PROJECTS \$4.95. Complete instructions for building all kinds of power supplies for a variety of applications.

Model Railway Projects
A MICROPROCESSOR PRIMER \$4.50. A painless approach to computing, starting with a design for a simple computer.

Model Railway Projects
MODEL RAILWAY PROJECTS \$4.95. Controllers, signals and sound effects that bring your railroad to life.

Electronic Synthesizer Projects
ELECTRONIC SYNTHESIZER PROJECTS \$4.50. All the individual sections of a music synthesizer are described along with construction details.

50 Simple LED Circuits
50 SIMPLE LED CIRCUITS \$3.50. It would be difficult to come up with a circuit not described in this book.

Build Your Own Electronic Experimenters Lab
BUILD YOUR OWN ELECTRONIC EXPERIMENTERS LAB USING IC'S \$3.25. Basic lab gives plans for 14 instruments you need to own. All built with IC's.

Counter Driver and Numerical Display Projects
COUNTER DRIVER & NUMERICAL DISPLAY PROJECTS \$4.50. Practical counter and display projects that can be used in almost any device you care to design and build.

International Transistor Equivalents Guide
INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE \$7.50. 320 pages filled with user-oriented selection of modern transistors. Also shown are the material type, polarity, manufacturer and use.

Essential Theory for the Electronics Hobbyist
ESSENTIAL THEORY FOR THE ELECTRONICS HOBBYIST \$3.50. All the theory you need to know before you build that first electronic project.

Introduction to Radio DXing
INTRODUCTION TO RADIO DXING \$5.00. Everything you need to know to get started in this exciting hobby.

Radio Control for Beginners
RADIO CONTROL FOR BEGINNERS \$4.50. Tells how devices work—including transmitters, receivers and actuators.

Simple LED Circuits, Book 2
SIMPLE LED CIRCUITS, Book 2 \$3.75. More uses for LED's. Excellent complement to the book listed above.

Electronics Using Solar Cells
ELECTRONICS USING SOLAR CELLS \$5.00. Simple circuits with applications around the home. All are powered by the free energy from the sun.

PRICES GOOD UNTIL MAR. 30, 1982

ELECTRONIC TECHNOLOGY TODAY INC.
P.O. Box 83, Massapequa Park, NY 11762

2-82

Number of books ordered

Total Price of Books

Sales Tax (NY State Residents only)

Shipping and Handling (75c 1 or 2 books 25c each add. book)

TOTAL ENCLOSED

Name


Address

City State Zip

NEW PRODUCTS

For more details use free information card inside back cover.

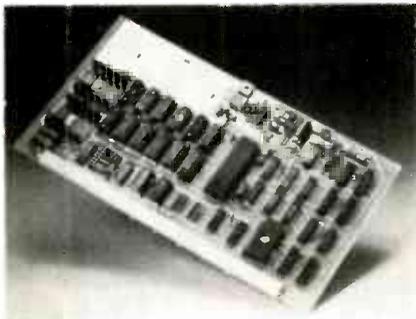COLOR VDG CARD, the *ColoRAMa*, is a color video display generator/controller for SYSTEM-50 (SS-50, SS-50C) 680x computers. It permits software selection of any of 11 different display formats, including eight-color semigraphics, two- and four-color graphics, and two-color alphanumeric.



CIRCLE 111 ON FREE INFORMATION CARD

Two- and four-color displays may also be switched between primary and complementary color sets, either under software control or from the keyboard. Resolution of full-graphic displays ranges from 64 x 64 picture elements (pixels) to 256 x 192 pixels.

All of the 64 characters of the standard ASCII character subset are generated by the on-card character generator. The *ColoRAMa* is configured with one kilobyte of display RAM. One-kilobyte of RAM accommodates alphanumeric displays, eight-color semigraphic displays and two full-graphic displays modes. The *ColoRAMa* is priced at \$219.95. — **Percom Data Company, Inc.**, 211 N. Kirby, Garland, TX 75042.

INTEGRATED HARDWARE/SOFTWARE SYSTEM, *TerminalI* (Model T1 and Model T3), converts the TRS-80 microcomputer (Model I or Model III) into a state-of-the-art communications terminal. It includes all the necessary computer-interfacing, audio-demodulating, AFSK tone-generating, and transmitter-keying hardware integrated in one cabinet. That reduces equipment interconnection to a minimum and allows the operator to be on the air



CIRCLE 112 ON FREE INFORMATION CARD


receiving and transmitting Morse code or RTTY in minutes.

The user can plug it into the receiver headphone jack and copy Morse code, Baudot, or ASCII; plug it into the CW key jack and send Morse code, or attach a microphone connector and send Baudot or ASCII using audio tones (AFSK). In addition, the *TerminalI* is expandable: disk-based (mailbox) RTTY software may be added at any time.

TerminalI model T1 requires Model I TRS-80, 16K RAM and Level II BASIC. *TerminalI* model T3 requires Model III TRS-80, 16K RAM, and model III BASIC.

TerminalI model T1 or model T3 are priced at \$499. — **Macrotronics**, 1125 N. Golden State Blvd., Suite G, Turlock CA 95380.

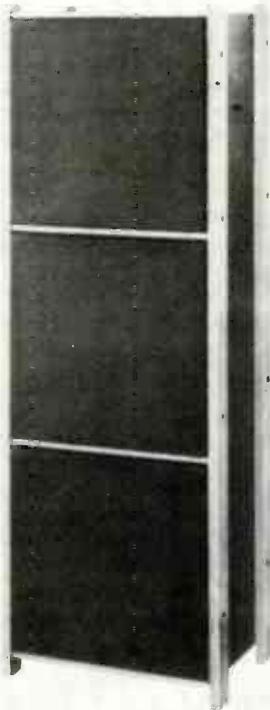SUBWOOFER, model AS-1320, is designed to add bass to an existing small system, but will enhance the bass response of even 10-inch and 12-inch systems. By extending the low-frequency range of the audiophile's present system, the model



CIRCLE 113 ON FREE INFORMATION CARD

AS-1320 will reduce the bass distortion that occurs when the wing speakers try to reproduce the low-bass notes. A ported cabinet alignment uses computer-aided



In general, spring reverbs don't have the best reputation in the world. Their bassy "twang" is only a rough approximation of natural room acoustics. That's a pity because it means that many people will dismiss this exceptional product as "just another spring reverb". And it's not. In this extraordinary design Craig Anderton uses double springs, but much more importantly "hot rod's" the transducers so that the muddy sound typical of most springs is replaced with the bright clarity associated with expensive studio plate systems.

Kit consists of circuit board, instructions, all electronic parts and two reverb spring units. User must provide power (± 9 to 15 v) and mounting (reverb units are typically mounted away from the console).

PA Electronics, Inc.

Dept. 2AR 1020 W. Wilshire Bv. Oklahoma City, OK 73116 (405) 843-9626

Send the 6740 REVERB KIT \$59.95 plus shipping (\$3) enclosed or charged.

Send Free Catalog

name _____

address _____

city _____ state _____ zip _____

visa _____ mc _____ card no _____

CIRCLE 37 ON FREE INFORMATION CARD

A Classroom In Your Mailbox!

STUDY
Two-Way Radio

THROUGH THE
REVISED

MTI

Home Study Course

Send coupon below for free course outline
No obligation - No salesman will call

Professional Training in a Unique Career Field

Providing Training to the Industry Since 1960

study FM two-way
radio at home!

I am interested in learning more about professional FM two-way radio. Please send me full details on the MTI training program.

Name _____

Address _____

City/State/Zip _____

MTI

D3B

Mobile Training Institute

Box 735, Camp Hill, PA 17011 · U.S.A.

CIRCLE 32 ON FREE INFORMATION CARD

Vital protection for PC Boards



Be safe. Desolder PC components with Endeco irons. Get *proper* HEAT TO MELT and *strong* VACUUM ACTION TO LIFT solder and *cool* both PC board and component without damage.

These PC components replaced fast with Endeco desoldering or soldering tools.



Endeco professional features include safety light that denotes *high*, *low* and *off* on switch models, SS construction for long life, light weight and balance for easy use.

Contact your distributor for Endeco desoldering and soldering irons, kits and equipment—or write us today.

Enterprise Development Corp.

5127 East 65th Street
Indianapolis, IN 46220
Phone: (317) 251-1231

CIRCLE 38 ON FREE INFORMATION CARD

design techniques to maintain an extended low-frequency response with as flat a response as possible. A six-inch tuned vent is loaded into the floor for even better response. The driver is mounted near the floor so that the first boundary cancellation is above the frequency limits of the subwoofer.

The *model AS-1320* requires either the Heathkit *model ASA-1320-1* Passive Crossover (mail-order priced at \$44.95) or the Heathkit Electronic Crossover, *model AD-1702*, (mail-order priced at \$194.95). A complete step-by-step instruction manual makes the subwoofer kit a one-evening project. The *model AS-1320* is mail-order priced at \$299.95. — **Heath Company**, Benton Harbor, MI 49022.

DESOLDER PUMP, *model DP-1*, features all-metal construction with precision components for maximum reliability and ease of operation. Compact size facilitates comfortable, one-hand operation. Suction is precisely regulated for efficient solder removal without damage to



CIRCLE 114 ON FREE INFORMATION CARD

delicate circuitry. Self-cleaning at each stroke, the *model DP-1* is quickly disassembled without special tools for maintenance or repairs. The rugged Teflon tip is easily replaced. The *model DP-1* is priced at \$10.95. — **OK Machine and Tool Corporation**, 3455 Conner Street, Bronx, NY 10475.

STEREO MIXER/PREAMPLIFIER, *model DM500*, has two stereo phono/line inputs; one microphone input; pro-style slide controls for fading and cueing; a talk switch that attenuates the phono/line



CIRCLE 115 ON FREE INFORMATION CARD

volume 14 dB for making smooth, professional voiceovers without touching any volume settings, and an easy-access headphone output for monitoring. The built-in, low-noise preamp handles virtually any signal source, including magnetic phono cartridges and low-impedance microphones, and is powerful enough to drive almost any power amplifier. It can also be plugged into the

auxiliary input of any receiver or integrated amplifier. The *model DM500* is priced at \$149.00. — **Numark Electronics Corp.**, 503 Raritan Center, PO Box 493, Edison, NJ 08817.

ANTENNA, *model PD-1610*, is a fiberglass collinear antenna of the "Super-Station-master" design. The frequency range is 806-896 MHz and gain is 3.0 dBd. Maximum input power is 500 watts; bandwidth, for 1.5:1 VSWR, is 60 MHz, and vertical beamwidth, 1/2-power points, is 36 degrees.




CIRCLE 116 ON FREE INFORMATION CARD

The overall length of the *model PD-1610* is 44 inches. The fiberglass housing is 1.5 inches in diameter, and the aluminum support pipe is 12 inches long and 1.66 inches in diameter. Copper alloy is used as the radiating element material. The *model PD-1610* attains a resistance to rated wind velocity of 200 miles per hour, with a lateral thrust at rated wind of 48 pounds. Bending moment 1 inch below the top of the support pipe is 47 foot pounds, and lightning protection is direct ground. Termination is direct with an 18-inch, flexible extension of RG-393/U; mounting hardware is supplied.

The *model PD-1610* is priced at \$175.00. — **Phelps Dodge Communications Company**, Route 79, Marlboro, NJ 07746.

ELECTRONIC CROSSOVER, *model 6000*, is housed in a compact aluminum chassis with its own power supply, and is fully compatible with both tube- and transistor equipment. A choice of 16 different crossover frequencies is standard, with custom frequencies available at additional charges. The *model 6000* crosses-over from 200 through 10,000 Hz, contains two tweeter-level controls, and features very low distortion (.002%) and noise (-90 dB). The 12 dB/octave slope is suitable for

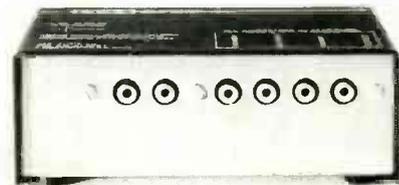

CIRCLE 117 ON FREE INFORMATION CARD

Digital Multimeter

The Drake DM2350 Digital Multimeter is a convenient, small handheld liquid crystal display meter ideal for the serviceman or hobbyist. This 3 1/2 digit meter is auto-ranging, auto-zeroing, has polarity indication, and an over-range warning signal. Battery life is greater than 300 hours with a "low battery" indicator. A continuity test sounds a signal when circuit resistance is less than 20 ohms. Dc accuracy is a basic 0.8%.

Batteries, probes, 20 amp current shunt, spare fuse and soft carrying case all included at \$95.95

Add \$2.50 shipping and handling per order.

Send check with order and provide street address for UPS shipment. Ohio residents add Sales Tax. Charge card buyers may call toll free:

1-800-543-5613



In Ohio, or for information call:
1-513-866-2421

R. L. DRAKE COMPANY

540 Richard Street, Miamisburg, Ohio 45342


INSTITUTIONAL AND DEALER INQUIRIES INVITED.

CIRCLE 35 ON FREE INFORMATION CARD

both horn and dynamic drivers.

The *model 6000* can be used either for bi-amping or tri-amping, and features a plug-in frequency module that allows changing frequencies readily. For tri-amping, a second *model 6000* is needed to provide the bandpass filter for the mid-range speakers. The *model 6000* is priced at \$156.00. — **Ace Audio Co.**, 532 5th Street, East Northport, NY 11731.

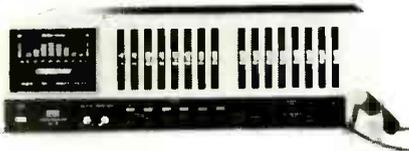GRAPHIC EQUALIZER, *model SE-9*, is a microprocessor-controlled, octave-band stereo graphic equalizer designed for either room equalization or recording. It features 4-curve memory storage, spectrum-analyzer display, and a built-in pink-noise generator; in addition, it comes supplied with an external electret condenser microphone.



CIRCLE 118 ON FREE INFORMATION CARD

A motorized fader-setting system, operating under CPU direction simplifies the digital-processing requirements; all 16 of the frequency controls are dual-slide potentiometers, one section of which can vary the boost or cut within its audio band by ± 12 dB. The other section produces a varying DC voltage that is fed to comparator circuits that determine when the motors have positioned the sliders correctly. When the vertical motor has placed one slider properly, the horizontal motor shifts the adjustment mechanism to the next potentiometer, in turn. Using the automatic adjustment procedure minimizes fader-to-fader interaction, and requires only 30 seconds overall. Manually-derived settings, or factory-preselected equalizations, may also be stored in the 4-curve memory and recalled at any time.

The *model SE-9* is available in brushed aluminum and is priced at \$700.00 (Also available as *model SE-9B* in matte black with rack mounting, at the same price.) — **Sansui Electronics Corp.**, 1250 Valley Brook Ave., Lyndhurst, NJ 07071.

SPEAKERS, *model 5300*, are 5-inch wedges, shaped for mounting in car doors and other surfaces. They feature a



CIRCLE 119 ON FREE INFORMATION CARD

5-inch woofer, separate 1 $\frac{3}{4}$ -inch tweeter, 3-ounce ceramic magnet, and cloth-roll air-suspension. They have a 15-watt RMS rating, 100–15,000 Hz frequency response, and an impedance of 8 ohms.

The *model 5300* speakers are made of

molded ABS plastic and are sold in kits containing two speakers and cables. The suggested retail price for the kits is \$19.95 — **BP Electronics**, 855 Conklin Street, Farmingdale, NY 11735.

SOUND-ENHANCER, the *Imager 801-A*, can fit almost any size car or truck dashboard, and uses very little current. By connecting it to an auto, truck, or van's



CIRCLE 120 ON FREE INFORMATION CARD

speaker system, the speakers' performance is improved dramatically. The sound appears to be coming from many speakers, surrounding the listener with an extra dimension of depth, clarity, and realism. It comes complete and with full instructions, so that it should not be difficult for the average do-it-yourselfer to install. The *Imager 801-A* is priced at \$149.95. — **OmniSonix, Ltd.**, P.O. Box 430, Rt. 17, c/o Carrano Bldg., Northford, CT 06492. R-E

Get A GNOME

the original micro-synthesizer

Every day more people discover that PAIA's GNOME is the most versatile, cost effective special effects device on the market today.

John Simonton's time-proven design provides two envelope generators, VCA, VCO and VCF in a low cost, easy to use package. Use alone with it's built in ribbon controller or modify to use with guitar, electronic piano, polytonic keyboards, etc.

The perfect introduction to electronic music and best of all, the Gnome is only \$69.95 in easy to assemble kit form. Is it any wonder why we've sold thousands?



PAIA 1020 W. Wilshire Blvd. Oklahoma City, OK 73116

1) Send GNOME MICRO-SYNTHESIZER Kit (\$69.95 plus \$2.00 postage)

2) Send FREE CATALOG



name _____

address _____

city _____ state _____ zip _____

visa _____ mar. _____ card no. _____

PAIA Dept. 2R (405) 843-9626
1020 W. Wilshire Blvd. Oklahoma City, OK 73116

CIRCLE 36 ON FREE INFORMATION CARD

Radio-Electronics REPRINT BOOKSTORE

- | | |
|---|--|
| <input type="checkbox"/> Build Your Own Satellite TV Receiver \$7.00 | <input type="checkbox"/> Radio-Electronics back issues (1980) (each) \$3.50 |
| <input type="checkbox"/> 8-Ball Satellite TV Antenna \$5.00 | (March, May 1980 not available) |
| <input type="checkbox"/> Build Your Own Robot \$12.00 | Write in issues desired _____ |
| <input type="checkbox"/> TV Descrambler (January, February 1981) \$3.00 | |
| <input type="checkbox"/> Video Entertainment (January 1982) \$2.00 | <input type="checkbox"/> Radio-Electronics back issues (1977-79) (each) \$4.00 |
| <input type="checkbox"/> Your Own Computer (October 1981) \$3.00 | Write in issues desired _____ |
| <input type="checkbox"/> Radio-Electronics Back issues (1981) (each) \$3.00 | <input type="checkbox"/> Special Projects (Spring 1981) \$4.00 |
| (February, March 1981 not available) | <input type="checkbox"/> How To Make PC Boards \$2.00 |
| Write in issues desired _____ | <input type="checkbox"/> All About Kits \$2.00 |

To order any of the items indicated above, check off the ones you want. Complete the order form below, include your payment—check or money order (DO NOT SEND CASH), and mail to Radio-Electronics, Reprint Department, 200 Park Ave. South, New York, NY 10003. Please allow 4 - 6 weeks for delivery.

If you need a copy of an article that is in an issue we indicate is unavailable you can order it directly from us. We charge 50¢ per page. Indicate the issue (month & year) pages and article desired. Include payment in full, plus shipping and handling charge.

ARTICLE _____

MONTH _____ YEAR _____

PAGES _____

TOTAL PAGES _____ @ 50¢ ea TOTAL PRICE _____

MAIL TO:

Radio-Electronics
Reprint Department, 200 Park Ave. South, New York, NY 10003

All payments must be in U.S. funds

Total price of order \$ _____

Sales Tax (New York State Residents only) \$ _____

Shipping & Handling (U.S. & Canada only)
(includes FIRST CLASS POSTAGE)

\$1.00 per item \$ _____

All Others (\$2.00 per item, sea mail) \$ _____

(\$4.00 per item, air mail) \$ _____

Total Enclosed \$ _____

Name _____

Address _____

City _____ State _____ Zip _____

STEREO AUDIO FOR TV

continued from page 76

of TV sound. In fact, the NTSC system has always been capable of providing "high fidelity" FM sound, with response up to 15 kHz. Small-speaker TV sets, together with TV-station-owner apathy, has resulted in a vicious circle that has kept us from enjoying the kind of sound we get from FM radio and other high-fidelity program sources.

The coming of stereo-TV sound may change all that, if only for the reason that the TV tuners and adaptors needed

to supply the two channels of audio will permit us to connect our stereo component-systems directly to the line outputs of those new products. In that way, we will finally be able to bypass the sound systems contained in our TV sets. When will that happen? Best estimates suggest that the FCC's decision will not come before mid-1982, and most likely, it will arrive later than that.

I am indebted to my friend William S. Halstead, who provided me with much of the background material used for this description of the stereo-multiplex TV systems being considered by the EIA and the FCC.

R-E

COMPUTER CORNER

continued from page 92

procedures for various colleges, and the first magazine to distribute its monthly articles via electronic transmission: *Better Homes and Gardens*. A banking-by-home project is described in an experimental program being tried through CompuServe by the United American Bank, Knoxville, TN.

The program provides checking and savings information, financial advisory services, paying of bills, sending of messages, and bank loan applications. (The only thing it can't do, presumably, is eject dollar bills upon request, as the computerized teller stations do, because they can't be transmitted via electronic signal.)

The Source offers over 1,200 services, including the American stock exchange, etiquette, Black studies, New Mexico news and sports, ham radio, French wines, and unidentified flying objects. (A sample partial listing from the Source is shown in Fig. 1.) A recent news magazine details such added services as Legi-Slate, a listing of Congressional records and a career-placement center that matches job seekers with prospective employers.

Both networks offer computerized flea market and want-ad type services, linking consumers across the nation with the most sophisticated and comprehensive resources imaginable for trading services, selling or buying merchandise, or doing the sundry things that want ads traditionally do.

The list of consumer services goes even further: restaurant guides; travel agent transactions; receiving the latest UPI news breaks as soon as they occur. Of special interest to computer hobbyists is the ability to load and unload complete programs.

Which service is the best? The Source is, at least, the biggest, with a much larger index of services offered and access in over 300 U.S. cities. Purchased last year by the Reader's Digest Corporation and having been introduced several months earlier than CompuServe, the Source would seem to have the edge in versatility and growth potential. CompuServe, on the other hand, is not far behind, currently available in over 250 cities, with highly visible market exposure—it's sold through Radio Shack stores. Both companies have passed the 10,000 subscriber mark. Both services have their admirers and detractors. It is probably wise to request literature from each network and peruse the list of data bases offered and to study the specific hookup requirements. That way, you can decide which would be least expensive and easier for you to access.

R-E

Radio-Electronics

SPECIAL REPRINT
BUILD THIS ROBOT FOR UNDER \$400



**AVAILABLE—COMPLETE
for the FIRST TIME!**

BUILD YOUR OWN ROBOT!

Send today for your 52-page (8½ × 11") booklet containing complete reprints of all eleven articles in the Build Your Own Robot series by Jim Gupton.

This all-inclusive reprint gives you all the data you need to build your own Robot.

■ TELLS EVERYTHING YOU NEED TO KNOW to build the Unicorn-1 Robot without the need for an engineering degree or special equipment. The robot is fully mobile with manipulator arms to grasp, lift and carry.

■ MANIPULATOR ARMS and end-effectors (hands) are what enable the robot to perform useful tasks. Details of construction techniques and considerations are fully explored.

■ MOBILITY BASE is not a lunar space station. It is the drive system that permits the robot to move from here to there. Full construction details along with a discussion of power sources is included.

■ THE BODY—FRAME AND ROTATION MECHANISM. This is the part that makes Unicorn-1 look like a robot. Wood and Formica are the materials for the body. Motors and gears are what make it function.

■ COMMUNICATIONS. How you can tell your robot what to do. Preprogramming techniques...radio control...computer control are all detailed.

■ SENSORS. How to add sensors so your robot doesn't bump into things.

Radio-Electronics

Robot Reprints
200 Park Ave. South
New York, N.Y. 10003

I want to order _____ reprints @\$12.00 plus \$1.00 postage and handling for U.S., Canada and Mexico.
Add 99¢ sales tax for New York State residents only.
U.S. Funds only.
I want to order _____ reprints @\$12.00 plus \$3.00 Air Postage and handling for all other countries.
U.S. Funds only.

Allow 6-8 weeks for delivery.

Please print

282

(Name)

(Street address)

(City)

(State)

(Zip)

We do not bill, check must be enclosed.

LETTERS

continued from page 22

Winning the DB War," in your December 1981 issue of **Radio-Electronics**.

If we are to assume that that is, indeed, the technique used by the Russians, then Mr. Leinwoll is giving them more credit than they deserve. The concept of backscatter, and its relationship to propagation, is common knowledge. It would appear that the Russians merely expanded the concept.

The sensing or sampling of the backscatter wave would be somewhat akin to over-the-horizon radar, with computer evaluation as the key to that technique.
CHARLES DERAPELIAN,
Port Neches, TX

SINGLE BOARD COMPUTER

I found Jorma Hyypia's article on "Learning About Microprocessors" (May 1981) very interesting, even though it left out the assembly-language computer that I'm using and that I think your readers might be interested in learning about, the Pacom 8085AKT.

It uses the 8085 CPU and comes either as a kit or assembled. Memory includes 1K of RAM, 1K or PROM, and 1K of EPROM that contains the system monitor. (Two EPROM sockets are provided, and either 1K- or 2K-IC's can be used.)

This computer can be used either as a trainer or as a controller and is supported by several very good books (that come

VIDEOTEX FOR TV

continued from page 61

However it works out, eventually you will be tied into the videotex network. You'll be able to do your shopping and banking, and plan your day using videotex. Even your work may be affected.

Much of the time that many people spend in the office concerns work that could just as well be done at home. That includes: phone calls, correspondence (assuming the user can type), and preparing reports. Imagine being able to do that without having to commute three hours each day to and from work!

Along other lines, farmers could request the latest weather information, or—perhaps more important—the selling price of their produce in a particular market, or find the market offering the best price. Sales could even be made using videotex.

The ability to communicate with the rest of the world—not only by voice, but by visual information—is something that we not only desire, but will need.

Whatever form of videotex we use, it can only stand to benefit us. **R-E**

with it). It is especially good for control purposes because, of 44 lines brought out to the card edge, 36 can be wired to meet the user's specific needs.

Programming is done using a 24-key keypad and 9-digit LED display. The computer can be programmed in either octal or hexadecimal (some of us *still* prefer octal, you know).

The price of the 8085AKT kit is \$249.95 and more information on it can be obtained from: Pacom, 14905 N.E. 40th, Redmond, WA 98052.
ALLAN EGAN
New York, NY

TEMPERATURE SCALES

I wish to point out two errors in Joseph J. Carr's discussion of temperature scales

in the November 1981 **Radio-Electronics**. Firstly, the absolute zero temperature is -273.15°C , relative to the freezing point of water, which is 0°C . The triple point of water, the point where gas, liquid, and solid exist in equilibrium at 1-atmosphere pressure, is defined as 273.16°K and the freezing point of water is found to be 0.01°C lower.


Second, all molecular motion does not cease at 0°K . All molecules in a potential field, such as exists in a crystal of the solid, retain a zero-point vibrational motion due to the uncertainty principle, which prevents both the particle momentum and position from being known exactly at the same time.

DAVID G. HENNINGS, Ph.D.,
Omaha, NE

R-E

Radio-Electronics

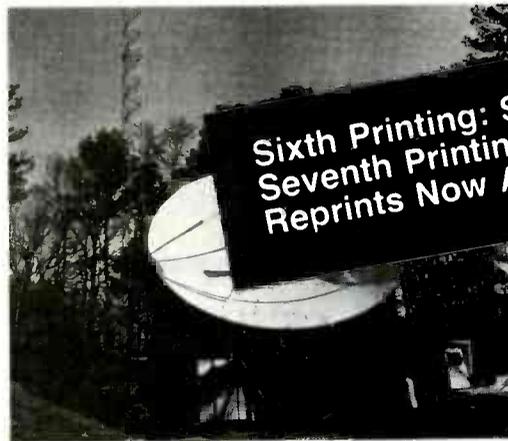SPECIAL REPRINT
BUILD A BACKYARD SATELLITE TV RECEIVER



Don't miss out again!

Send away today for your 36-page booklet containing a complete reprint of all seven articles in the series on Backyard Satellite TV Receivers by Robert B. Cooper Jr.

This all-inclusive report gives you all the data you need to build your own Backyard Satellite TV Receiver.

- TELLS ALL ABOUT domestic satellite communications, with full details on how you can pull those elusive TV signals from space.
- LEGAL REQUIREMENTS, technical specifications, and how you, the

home constructor, can meet them. Find out what mechanical and electronics skills you need.

■ RECEIVER CHARACTERISTICS, technical details and specifications, along with examples of actual receivers built at comparatively low cost.

■ ANTENNA DESIGN... and exactly how you can build a spherical antenna, while keeping total earth-station cost for the complete system under \$1,000.

■ THE FRONT END is critical when you build your own system. We help you explore several different ap-

proaches to making one that will work for you.

■ RECEIVER-SYSTEM hardware, and how it goes together to bring you direct-from-satellite TV reception in your own home.

To order your copy: Complete coupon and enclose it with your check or money order for \$7.00, plus \$1.00 for postage and handling. We will ship your reprint within 6 weeks of receipt of your order. All others add \$4.00 for postage. New York State residents must add 58¢ sales tax.

Radio-Electronics

Satellite TV Reprints
45 East 17th Street
New York, N.Y. 10003

282

Please print

(Name)

(Street address)

(City)

(State)

(Zip)

I want _____ reprints @ \$7.00 each, plus \$1. Handling & Postage.
I have enclosed \$ _____ . N.Y. State residents must add sales tax.

NEW BOOKS

For more details use free information card inside back cover.

HOW TO BUILD YOUR OWN WORKING MICROCOMPUTER, by Charles K. Adams. Tab Books, Inc., Blue Ridge Summit, PA 17214. 308 pp including glossary, appendices, and index; 5½ × 8¼ inches; softcover; \$9.95. (A hardcover edition is also available at \$16.95.)

Compared to the monstrous computers of a decade or more back, the microcomputer is simple, inexpensive, and easy to use—facts well proven by its popularity and ubiquity. Microcomputers now control almost everything from toys to automobile combustion-efficiency; from games to microwave ovens, and from stop lights to numerically-controlled machines. And the microcomputer boom is just beginning.

This book is for the electronics hobbyist who would like to build and program a simple microcomputer, but doesn't know just how or where to begin. It is an easy-to-read manual, showing the way to get started...the *right* way. Whether one is a beginner or a seasoned electronics buff, building a microcomputer from scratch will give one a taste of the electronics world that can't be experienced any other way. The book shows how a computer works, and provides simple (and more advanced) programming exercises for use with a self-built computer after presenting a step-by-step outline of every aspect of construction, assembly, and testing. Diagrams and tables are presented clearly, as well as parts lists, layout, power-supply sources, keyboard and display

circuits, and even plans for an EPROM programmer.

The book may be used in any one of three ways: as a general reference book; as a guide to building a computer, or as a guide to building and programming the specific computer described.

CIRCLE 151 ON FREE INFORMATION CARD

ELECTRICAL INTERFERENCE IN ELECTRONIC SYSTEMS: Its Avoidance within High-Voltage Substations and Elsewhere, by R. E. Martin, C. Eng., D.F.H., F.I.E.E., F.I.E.R.E. Consultant. Research Studies Press, PO Box 92, Forest Grove, Oregon 97116. 198 pp including references, bibliography, and appendices—no index; 5½ × 8½ inches; hardcover; \$31.00.

Semiconductors used in modern electronic equipment and in computers are very sensitive to electrical interference, and due to their low thermal inertia, they are easily destroyed by overloads lasting even one millisecond. Many such devices normally operate at microwatt or milliwatt power-levels, so that even if destruction is avoided, false operations can easily be caused by interference. Computers are one of the most difficult devices to protect against interference, because the spectrum of signals they use is extremely wide.

The pulses used by the computer may have durations of a few tens of nanoseconds and rise times of a few nanoseconds; they will thus represent frequencies extending to 100 MHz or more.

HAMEG PRESENTS THE NEW HM 203



High performance
at
low cost.

\$580
(PROBES INCLUDED)

A quality scope,
made in the U.S.A.,
by a company with
over 23 years
experience.

Hameg introduces high performance at low cost in the HM 203, a full featured, highly reliable, dual trace 20 MHz oscilloscope. For only \$580, the HM 203 has specifications normally associated with higher priced scopes. Bandwidth - DC → 20 MHz • Risetime 17.5 ns • Overshoot 1% max. • Y amp range 5 mv/cm to 20 v/cm • Max. input voltage 500V • Timebase .5 μs/cm to .2s /cm • Sweep mag. x5 • Trigger 5 Hz to 30 MHz • X:Y plot • Built-in probe calibrator and more. Its sturdy construction and light weight (13.2 lbs.) make the HM 203 equally at home in the field and on the test bench.

HAMEG

88-90 Harbor Rd.

Port Washington, N.Y., 11050

Tel (516) 883-3837



CIRCLE 18 ON FREE INFORMATION CARD

Very short interference-pulses can easily be interpreted by the computer as instructions, and that may corrupt a program in storage, or inhibit the running of a program.

This book is intended to be used in conjunction with other documents referenced, to aid immunity from interference by isolation, screening, filtering, and earthing—a scheme designed for use with electronic systems in electrically noisy environments. It is particularly concerned with the use of electronic equipment in high-voltage electricity substations and outlines the ways in which harmful interference may enter electronic systems within an electricity station, as well as indicating appropriate measures for controlling the effect of such interference.

Although there is no index, the table of contents, which lists nearly every page, should suffice to enable the reader to find any particular material easily. There are many clearly printed diagrams, a section on the scope of the book and on how to use it, and a glossary of terms.

CIRCLE 152 ON FREE INFORMATION CARD


MUSICAL APPLICATIONS OF MICROPROCESSORS, by Hal Chamberlin. Hayden Book Company, Inc., 50 Essex Street, Rochelle Park, NJ 07662. 661 pp including appendix, bibliography, and index; 6¼ × 9¼ inches; hardcover; \$24.95.

This book covers digital-microprocessor sound and music synthesis comprehensively, featuring previously unpublished techniques that are practical only with microprocessors. Standard linear techniques for microprocessor applications are discussed and musical applications for the newer and more powerful 16-bit microprocessors are explained in non-mathematical language. All phases of waveform shaping and filtering, as applied by digital devices to music generation, are also covered.

In the first section, "Background," chapters 1 to 5 cover the fundamental material necessary for full appreciation of the sections to follow. The second section, chapters 6 through 11, deals with computer-controlled analog synthesis, and in section three, chapters 12 to 18 cover the principals of digital synthesis and sound modification.


Throughout the discussions, mathematics is kept to a minimum, and even then is limited to elementary algebra and trigo-

An enclosure as good as your idea.

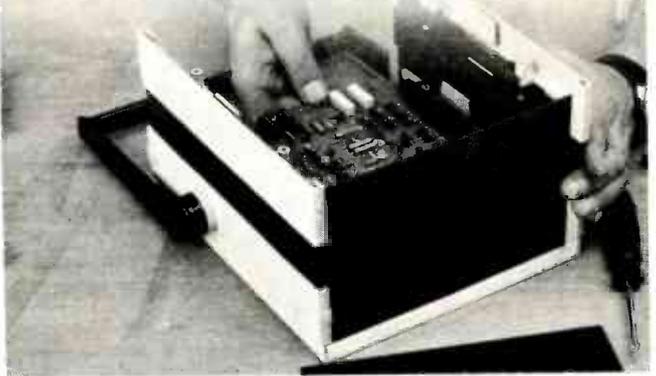

You've turned a good idea into a piece of equipment—now you need a good enclosure. Here's how PacTec can help you with our versatile enclosures:

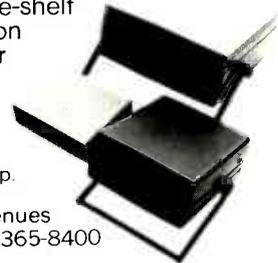- Attractive yet inexpensive.
 - Durable ABS construction.
 - Many sizes, colors, accessories.
 - Built in bosses and slots speed component mounting.
 - Available off-the-shelf from single unit to production quantities.
- See them at your PacTec Distributor.** And ask him for your free catalog.



PACITEC™ Corp.
 subsidiary of La France Corp.
 Enterprise and Executive Avenues
 Philadelphia, PA 19153 (215) 365-8400

CIRCLE 29 ON FREE INFORMATION CARD


Radio-Electronics

mini-ADS

CALL NOW AND RESERVE YOUR SPACE

- \$550 for a 6X frequency insertion.
- Reaches 211,387 readers.
- Fast reader service cycle.
- Short lead time for the placement of ads.
- We typeset and layout the ad at no additional charge.

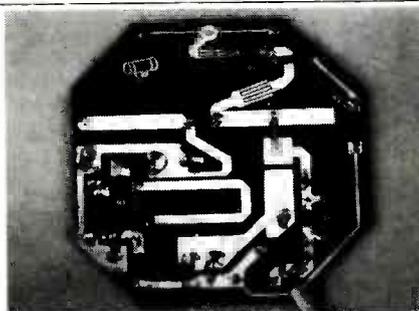
Call **212-777-6400** to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: mini-ADS, RADIO-ELECTRONICS, 200 Park Ave. South, New York, NY 10003.



2300 MHz DOWNCONVERTER kit for Amateur microwave reception. \$35.00 postpaid. Highest quality components. Send SASE for information filled catalog of other converter kits, preamps, accessories and parts. VISA and MASTERCARD accepted.

SMP - Superior Microwave Products, Inc.
 PO Box 1241 Vienna, VA 22180
 1-800-368-3028 1-703-255-2918

CIRCLE 39 ON FREE INFORMATION CARD

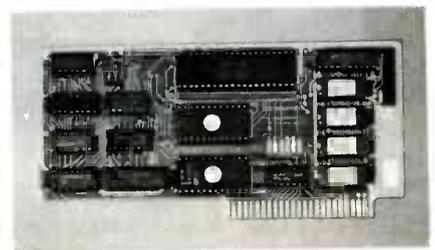

The Microbuffer II is an intelligent buffered parallel printer interface for the Apple II computer. Includes 16K of on-board RAM. Buffer memory size is user expandable to 32K. Compatible with Applesoft, CP/M, and Pascal. Includes advanced high resolution graphics print routines for the Epson MX-80 with Graphtrax, Anadex, IDS Paper Tiger, NEC Prowriter. Price: \$259. Contact Practical Peripherals, Inc., 31245 La Baya Dr., Westlake Village, Calif. 91362 (213) 706-0339.

CIRCLE 41 ON FREE INFORMATION CARD

For truly superb FM-stereo reception...

The **G-A-M Stereo One** vertical antenna

- Transforms fuzzy stations into 'tape quality'
- Reduces multipath problems
- Up to twice the power of the conventional dipole antenna
- Receives from all directions
- Pulls in stations you never knew existed
- Sturdy, stainless steel and PVC construction
- Silver plated brass joints for ultra-sensitive signal passage
- Built to withstand weather stands just 76" tall
- May be mounted on a mast, windowsill, balcony, or just stand it in the corner

Test it yourself! We offer an honest-to-goodness 30 day MONEY-BACK guarantee. If it doesn't measure up to your standards, send it back for a refund of the purchase price.

The suggested list price for Stereo One is \$69.95.

BUY DIRECT AND SAVE \$10.00
Send your check or money order for \$59.95 + 3.50 (shipping and handling) to: (N.Y. residents, please add 7% sales tax)

VISA & MASTER CARD buyers may call toll free 1-800-448-8490 9-5 EST Mon-Fri
N.Y. Residents please call 1-315-482-2589



Castle Marketing

Dept. RE
Holland Street
P.O. Box 219
Alexandria Bay,
New York 13607

CIRCLE 30 ON FREE INFORMATION CARD

PRINTED CIRCUIT KITS MAKE CARDS QUICKLY



ONLY Vector kits contain:

- Positive photo-resist coated AND uncoated copper laminate—no messy photo-reversal—no spraying, dipping, or baking.
 - 4 types of art aids: rub transfers, ink, tape, cut and peel—use 1 or all.
 - 1:1 circuit art rub transfers—IC sets, pads, lines, connectors, symbols, letters, and numbers.
 - Everything included—just add water and sunlamp or bright sunshine.
 - Liquid etchant and developer—no dry chemical mixing problems.
- AND
- Process choices—make circuit on copper and etch for 1 card. Make circuit on film, expose, develop and etch for 1 or many cards.



+ mylar film + sunlamp + developer & etchant = 1 or many PC's
+ card + etchant = 1PC

32XA-1 kit makes 7 PC cards, \$46.41, 32X-1 starter kit makes 2 cards, \$18.24
(If not available locally factory order include \$3.00 shipping, U.S. only
Prices subject to change without notice)

510177

Vector Electronic Co., 12460 Gladstone Av., Sylmar, CA 91342

CIRCLE 31 ON FREE INFORMATION CARD

nometry. Important concepts are illustrated through charts, graphs, and, at times, computer programs in BASIC.

CIRCLE 153 ON FREE INFORMATION CARD

ELECTRICAL AND ELECTRONICS DRAWING, Fourth Edition, by Charles J. Baer and John Ottaway. Gregg Division, McGraw-Hill Book Company, 1221 Avenue of the Americas, New York, NY 10020. 473 pp including appendices, glossary, and index; 6½ x 9½ inches; hardcover; \$16.25.

This new Fourth Edition provides a complete course in electrical and electronics drawing that reflects the latest drafting techniques, technology, and the National Electrical Code.

Presented in a logical, easy-to-master sequence, the text is designed to expand students' knowledge of electronics functions and systems. An up-to-date picture of electrical drafting is provided with basic "how-to" information, plus coverage of electronics, automation, micro-electronics, electric power, and architectural wiring. Included are new chapters on computer-aided design (CAD), microprocessors and industrial controls, and new material on flow and logic diagrams, laying out circuits, using templates and drawing printed circuits.

The book is illustrated extensively and presents questions and problems at the end of each chapter.

CIRCLE 154 ON FREE INFORMATION CARD

SAFE SUB-WOOFER

continued from page 69

airtight. A hot-melt glue gun will make construction easier.

The rather elaborate construction of the initial chamber, behind the speaker, serves two purposes. First, it directs the back-wave from the speaker into the labyrinth. Second, it prevents standing waves from building up.

Three views of that first chamber are provided in Figs. 4, 5, and 6. It contains two angled partitions. The first behind-the-speaker partition, whose outline is shown in Fig. 7, is attached to mounting strips on the side panels; the second one is attached to the enclosure at all four of its edges.

The only acoustic insulating-material used in the system is in the first chamber, where indicated by asterisks in Figs. 5 and 6. It should be loosely-fluffed ¼- to ½-inch fiberglass.

Two binding posts will be needed to connect the sub-woofer to your amplifier. Locate them at the side or rear of the enclosure, and make sure that there is an airtight seal where they pass through the panel.

Prepare the front, rear, and side panels by attaching partition-to-cabinet mounting strips at the positions shown in Fig. 8, on what will become their insides. Cut out the hole for the speaker, bearing in mind that it is offset slightly from the middle of the front panel. Refer to Fig. 9 as you do this.

Prepare partitions 1-11 as shown in Fig. 10 and attach the even-numbered partitions to the odd-numbered ones as shown in Fig. 11. Now, join the sides at rear of the enclosure, leaving the front panel off for the time being. Install the first and second behind-the-speaker partitions, doing the second one first. Don't forget the acoustic installation where indicated. Attach the speaker to the front panel and connect it to the binding posts on the rear panel. Then attach the front panel to the rest of the enclosure and install partitions 1-10 on their mounting strips. Finally, add partition 11, and the top of the enclosure.

Use

The SAFE subwoofer is connected directly to your amplifier's output through a crossover network with a cutoff frequency of about 100 Hz. While an L-C-L "pi" network can be used, an electronic crossover would be better.

With much program material, the benefits of the subwoofer will not be noticeable—music just doesn't contain that much low-frequency information. When the low frequencies are present, however, you'll hear your music as you've never heard it before.

R-E

DIGITAL THERMOMETER

continued from page 58

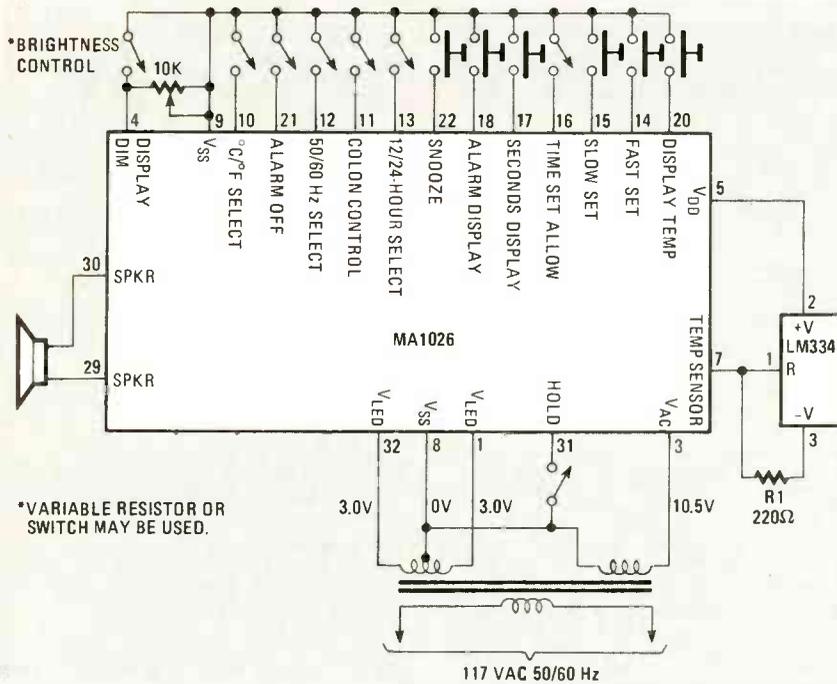


FIG. 5—EXPAND THE BASIC CLOCK/THERMOMETER project and make a full-function alarm clock with snooze alarm, using this circuit.

functions. While the clock/thermometer described in this article does not make use of some of them, there is no reason you can't expand the project to include them. For instance, with the appropriate additional circuitry you can turn the project into a full-feature alarm clock with a snooze alarm such as the one shown in Fig. 5. If you have a low-wattage soldering iron and a good eye, you might want to try accessing the traces going to individual segments of each digit. With a little ingenuity, doing that would let you build a time-of-day clock and temperature monitor for a computer. If you are interested in exploring the potential of the MA1026 further, be sure to order the data sheet and applications notes when you order the module (note that there is sometimes a small additional charge for those items). The module is simple and economical, but it has many features available to those who want to use it fully.

R-E


This Publication is available in Microform.

University Microfilms International

300 North Zeeb Road, Dept. P.R., Ann Arbor, Mi. 48106

HITACHI DUAL TRACE PORTABLE OSCILLOSCOPES

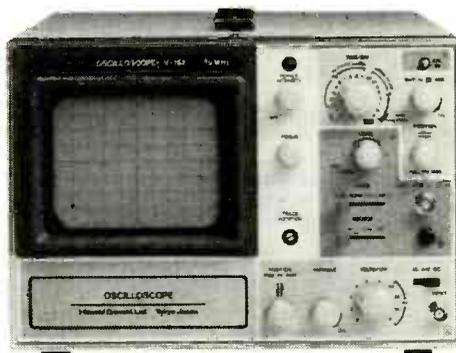- TV Sync-Separator Circuit
- High Sensitivity 1 mV/div (5 MHz)
- X-Y Operation
- Sweep-Time Magnifier (10X)
- Trace Rotation
- Z-Axis Input (Intensity Modulation)



	15 MHz	20 MHz	30 MHz	35 MHz
MODEL	V-152B	V-202	V-302B	V-352
DISPLAY AREA	8 X 10 div (1 div = 9.5 mm)			
INTENSITY MODULATION	Over 5V p-p			
VERTICAL DEFLECTION				
Rise Time	24 ns	17.5 ns	12 ns	10 ns
Non Distorted Max Amp	More than 4 div	More than 8 div	More than 4 div	More than 8 div
Display Mode	CH 1, CH 2, DUAL, ADD, DIFF			
HORIZONTAL DEFLECTION				
Sweep Mode	AUTO, NORM, TV (+), TV (-)			
Sweep Time	0.2 μs/div ~ 0.2s/div ± 5% 19 calib. steps			

Buy any of these instruments and get a FREE Bonus Gift!

Call for our prices **TOLL FREE (800) 645-9518**
in N.Y. State call (516) 752-0050

FORDHAM
855 Conklin St. Farmingdale, N.Y. 11735

- Master Charge
- BankAmericard
- VISA
- COD
- Money Order
- Check
- COD's extra

FEBRUARY 1982

MARKET CENTER

BUSINESS OPPORTUNITIES

MECHANICALLY inclined individuals desiring ownership of Small Electronics Manufacturing Business - without investment. Write: **BUSINESS**, 92-R, Brighton 11th, Brooklyn, NY 11235

PROJECTION TV... Make \$200.00+ per evening assembling projectors... Easy... Results equal to \$2,500 projectors... Your total cost less than \$15.00... Plans, lens & dealer's information \$14.00... Illustrated information free... **MACRO-COMGFFX**, Washington Crossing, PA18977. Credit card orders 24 hours. (215) 736-2880.

WINNERS! Build on your technical skills to create a successful computer business. Free report tells how. **SEABIRD PRESS**, Box 461T, Lexington, MA 02173

HIGHLY PROFITABLE

ONE-MAN ELECTRONIC FACTORY

Investment unnecessary, knowledge not required, sales handled by professionals. Ideal home business. Write today for facts! **Postcard will do, Barta-RE-V, Box 248, Walnut Creek, CA 94597.**

EDUCATION & INSTRUCTION

UNIVERSITY degrees by mail! Bachelors, Masters, Ph D's... Free revealing details. **COUNSELING**, Box 317-RE2 Tustin, CA 92680

ATTENTION ELECTRONIC TECHNICIANS



Highly Effective Home Study BSEE Degree Program for Experienced Electronic Technicians Our New Advanced Placement Program grants Credit for previous Schooling & Professional Experience. Advance Rapidly! Our 36th Year! **FREE DESCRIPTIVE LITERATURE!**
Cook's Institute of Electronics Engineering
DESK 15, P.O. BOX 20345, JACKSON, MS 39209

To run your own classified ad, put one word on each of the lines below and send this form along with your check for \$1.65 per word (minimum 15 words) to:
Radio-Electronics, 200 Park Avenue South, N.Y., N.Y. 10003

ORDER FORM
PLEASE INDICATE in which category of classified advertising you wish your ad to appear. For special headings, there is a surcharge of \$10.

() Plans/Kits () Business Opportunities () For Sale
() Education/Instruction () Wanted ()

Special Category: \$10

(PLEASE PRINT EACH WORD SEPARATELY, IN BLOCK LETTERS.)

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35

PLEASE INCLUDE FOR OUR FILES YOUR PERMANENT ADDRESS AND PHONE NUMBER.

Be an FCC LICENSED Electronic Technician

Earn up to \$600 a Week & More!
No costly school - The Original FCC Tests
Answers exam manual that prepares you at home for FCC General Radiotelephone License
Newly revised multiple choice exams cover all areas tested on the actual FCC Govt exam!
No previous experience required. \$12.95 post-paid. Moneyback Guarantee.
Dept. E P.O. Box 26348, San Francisco, CA 94126



WANTED

ADDRESSERS—mailers—homeworkers needed! 50 firms listed, rush 50 cents, addressed envelope. **BONNIE NIEUWENDAAL**, P.O. Box 23432, Tampa, FL 33623

A "Antenna Specialists" Monitor Preamplifier
Mon 26. **ALFORD N. LALUM**, Minnewauken, ND 58351

FOR SALE

HAMS, 6 meter, RT-70 portable 115-channel military FM receiver/transmitter, 47-58.4 MHz. \$17.50 each, \$30.00 pair. Schematic, hookup and battery information included. Add \$7.50 shipping. **V. THIERS**, Box 6, Richboro, PA 18954

COMPLETE line of microwave television converters and accessories to suit your needs. Converters have a one year warranty backed by a 3 year reputation. Call or write for complete specifications and pricing. **Dealer inquiries invited.** **TRITON MARKETING**, 1933 Rockaway Parkway, Brooklyn, NY 11236 (212) 531-9004

MICROWAVE receiver system. Write: "Dealers Wanted," Dept. RE, POB 4181, Scottsdale, AZ 85258 (602)941-9345

VARIETY electronic surplus parts and equipment in our monthly picture flyer. Send \$2.00 for 6 issues. **STAR-TRONICS**, POB 683, McMinnville, OR 97128

SCANNER/monitor accessories—kits and factory assembled. Free catalog. **CAPRI ELECTRONICS**, Route 1R, Canon, GA 30520

YOUR SOURCE FOR SAVINGS

- B&K Test Equipment
- MATV CATV Access
- Tubes, Electrolytics
- Soldering Irons
- Chemical Products
- Wire & Cable
- Power Access
- Audio Accessories
- Speakers
- Etc Etc Etc.

NEW 1982 CATALOG
TREMENDOUS SAVINGS
ON 1000's OF ITEMS
Call or Write for **FREE** Gift & Catalog
Toll Free 800 645-5833
In NYS call 516 226-2700
RNJ ELECTRONICS INC.
P.O. Box 528
Lindenhurst, N.Y. 11757

POLICE/fire scanners, scanner crystals, antennas, radar detectors. **HPR**, Box 19224, Denver, CO 80219

TEST equipment, new and used. Catalog \$1.00. **PTI**, Box 8756, White Bear Lake, MN 55110. (612) 429-2975

RESISTORS 1/4W, 1/2W 5% carbon films 3c ea. **No minimums**. 1% metal films. Send for details. Bulk pricing available. **JR INDUSTRIES**, 5834-C Swancreek, Toledo, OH 43614

FREE speaker catalog! Woofers, mids, tweeters, hardware, crossovers, grille cloth, plans, kits, information, much more. Discount prices. **UNIVERSAL SOUND**, Dept. RE, 2253 Ringling Blvd., Sarasota, FL 33577, (813) 953-5363

SAVE up to 50% on name brand test equipment. Free catalog and price list. **SALEN ELECTRONICS**, Box 82-F, Skokie, IL 60077

TELEPHONE or office bugged? Latest detection equipment finds out fast. Literature \$1.00. **CLIFTON**, Box 220-M, Miami, FL 33168

THE Intelligence Library. Restricted technical secrets—books on **electronic surveillance, lock-picking, demolitions, investigation**, etc. Free brochures: **MENTOR**, Dept. Z, 135-53 No. Blvd., Flushing, NY 11354

TV antennas. New designs solve problems. Free list. **TELE-COMM**, Box 2910, Station A, Champaign, IL 61820

WHOLESALE lowcost MATV/CATV, antennas, needles, batteries, free catalog. 212-897-0509. **D d W**, 66-19 Booth, Flushing, NY 11374

SPEAKERS by Electro-Voice and others. Build your own speaker system and save. Also microphones, mixers, amps, etc. Free list. **SONIX CO.**, Box 58-RE, Indian Head, MD 20640. Phone (301) 753-6432.

TRS-80C color computer morse code and Rtty programs. FSK and hardware. Free info. **FRANK LYMAN**, 12 Reservoir St., Cambridge, MA 02138

CABLE TV block converter. A must for videotaping from cable TV. Standard 2-13, mid and super bands on UHF. Converter only \$29.95; with installation kit \$34.50. \$2.50 S&H. CA add 6% sales tax. M/C, Visa, money order. **Video accessories**: Copyguard stabilizers/detailers/video fader/switchers/etc. Send \$1.00 for catalog. **ACCESSORY SPECIALISTS**, P.O. Box 71089, Los Angeles, CA 90071

PICTURE tube rebuilding equipment—we sell and buy new and used equipment. Free training. **ATOLL TELEVISION**, 6425 Irving Park, Chicago, IL 60634, Phone 312-545-6667

ANALOG delay, audio, and music synthesizer (IC's plus more)! Free flyer. **PGS Electronics**, P.O. Box 735B, Terre Haute, IN 47808

MICROWAVE 2 GHz. Best in the West! Down-converter kits \$39.00. Complete with antenna and control box \$99.00. Factory assembled—90-day warranty \$159.00. **GALAXY ELECTRONICS**, 6007 N. 61st Ave., Glendale AZ 85301 (602) 247-1151

RADIO-ELECTRONICS





NEW 1982 IC MASTER

Two full volumes of product data.

- Deluxe 2-Volume Set (Hard Cover)
- New Section on PROM Programmers
- 62 Manufacturers Data Sheets
- 2400 Data Sheets

REGULAR PRICE \$82.50
Active's Special Introductory Offer \$69.95

FREE ACTIVE'S NEW Comprehensive Catalog
 Write for a free copy

Name _____

Address _____

City _____

State _____ Zip _____

TTL STANDARD AND LOW POWER SCHOTTKY

7400N	23	74165N	64	74LS125N	44
7401N	25	74166N	68	74LS126N	44
7402N	24	74170N	96	74LS132N	44
7403N	24	74172N	4.95	74LS133N	1.68
7404N	26	74173N	7.9	74LS136N	4.2
7405N	26	74174N	6.6	74LS138N	5.6
7406N	36	74175N	5.8	74LS139N	5.6
7407N	36	74176N	7.7	74LS145N	1.09
7408N	26	74178N	1.17	74LS147N	1.96
7409N	28	74179N	1.32	74LS148N	1.96
7410N	25	74180N	7.5	74LS151N	4.2
7412N	47	74182N	5.2	74LS153N	4.2
7413N	42	74184N	2.35	74LS155N	4.2
7414N	42	74185N	2.36	74LS156N	4.2
7416N	45	74190N	6.8	74LS157N	5.6
7417N	45	74191N	6.8	74LS158N	5.6
7420N	29	74192N	6.8	74LS160N	5.6
7421N	37	74193N	7.2	74LS161N	5.6
7423N	37	74194N	7.2	74LS162N	1.10
7425N	32	74195N	5.5	74LS163N	5.8
7426N	39	74196N	7.9	74LS164N	5.8
7427N	32	74197N	7.2	74LS165N	8.9
7428N	48	74198N	1.50	74LS166N	2.20
7430N	22	74199N	5.8	74LS167N	1.58
7432N	42	74221N	6.8	74LS173N	5.9
7433N	42	74246N	1.44	74LS174N	4.4
7437N	38	74247N	1.29	74LS175N	4.4
7438N	38	74251N	1.19	74LS178N	1.99
7440N	25	74259N	1.89	74LS189N	4.45
7442N	44	74273N	2.39	74LS190N	7.2
7445N	95	74276N	1.19	74LS191N	7.2
7446N	84	74278N	2.38	74LS192N	6.4
7447N	65	74279N	5.9	74LS193N	6.4
7450N	25	74283N	1.10	74LS194N	6.4
7451N	29	74284N	1.10	74LS197N	6.4
7453N	29	74296N	8.4	74LS221N	8.9
7454N	29	74315N	2.20	74LS240N	1.50
7472N	36	74365N	6.9	74LS241N	1.50
7473N	36	74366N	6.9	74LS242N	1.50
7474N	36	74367AN	5.8	74LS243N	1.36
7475N	42	74368AN	5.8	74LS244N	1.84
7476N	42	74369AN	5.8	74LS245N	1.84
7483AN	48	74373N	1.29	74LS247N	8.4
7484AN	1.36	74LS248N	1.09	74LS248N	1.09
7485N	68	74LS249N	1.10	74LS249N	1.10
7486N	39	74LS251N	7.8	74LS251N	7.8
7490AN	42	74LS252N	7.8	74LS252N	7.8
7491AN	44	74LS253N	7.8	74LS253N	7.8
7492AN	38	74LS254N	7.8	74LS254N	7.8
7493AN	38	74LS255N	1.29	74LS255N	1.29
7494AN	68	74LS256N	1.25	74LS256N	1.25
7495AN	54	74LS257N	1.64	74LS257N	1.64
7496N	59	74LS258N	1.64	74LS258N	1.64
7497N	1.89	74LS259N	1.64	74LS259N	1.64
74100N	1.56	74LS260N	1.64	74LS260N	1.64
74101N	64	74LS261N	1.64	74LS261N	1.64
74107AN	44	74LS262N	1.19	74LS262N	1.19
74109N	44	74LS263N	1.19	74LS263N	1.19
74110N	52	74LS264N	1.19	74LS264N	1.19
74111N	72	74LS265N	1.19	74LS265N	1.19
74116N	1.38	74LS266N	1.19	74LS266N	1.19
74120N	1.38	74LS267N	1.19	74LS267N	1.19
74121N	48	74LS268N	1.19	74LS268N	1.19
74122N	54	74LS269N	1.19	74LS269N	1.19
74123N	48	74LS270N	1.19	74LS270N	1.19
74124N	68	74LS271N	1.19	74LS271N	1.19
74126AN	68	74LS272N	1.19	74LS272N	1.19
74128AN	64	74LS273N	1.19	74LS273N	1.19
74132N	45	74LS274N	1.19	74LS274N	1.19
74134N	52	74LS275N	1.19	74LS275N	1.19
74141AN	84	74LS276N	1.19	74LS276N	1.19
74142N	3.27	74LS277N	1.19	74LS277N	1.19
74143N	3.79	74LS278N	1.19	74LS278N	1.19
74144AN	3.79	74LS279N	1.19	74LS279N	1.19
74145AN	67	74LS280N	1.19	74LS280N	1.19
74147N	1.32	74LS281N	1.19	74LS281N	1.19
74148N	69	74LS282N	1.19	74LS282N	1.19
74150N	1.44	74LS283N	1.19	74LS283N	1.19
74151AN	44	74LS284N	1.19	74LS284N	1.19
74152N	38	74LS285N	1.19	74LS285N	1.19
74154AN	1.44	74LS286N	1.19	74LS286N	1.19
74155AN	48	74LS287N	1.19	74LS287N	1.19
74156N	52	74LS288N	1.19	74LS288N	1.19
74159N	1.52	74LS289N	1.19	74LS289N	1.19
74160AN	48	74LS290N	1.19	74LS290N	1.19
74161AN	64	74LS291N	1.19	74LS291N	1.19
74162AN	64	74LS292N	1.19	74LS292N	1.19
74163AN	64	74LS293N	1.19	74LS293N	1.19
74164AN	64	74LS294N	1.19	74LS294N	1.19

CMOS

CD4001BE	22	CD4073BE	28
CD4002BE	18	CD4075BE	28
CD4006BE	59	CD4076BE	59
CD4007BE	24	CD4078BE	28
CD4008BE	67	CD4510BE	58
CD4009BE	39	CD4511BE	67
CD4010BE	39	CD4512BE	72
CD4011BE	22	CD4514BE	1.68
CD4012BE	39	CD4515BE	1.68
CD4013BE	36	CD4516BE	7.75
CD4014BE	56	CD4519BE	52
CD4015BE	32	CD4520BE	68
CD4016BE	56	CD4522BE	7.9
CD4017BE	54	CD4526BE	1.25
CD4018BE	52	CD4527BE	1.59
CD4019BE	48	CD4528BE	72
CD4020BE	68	CD4531BE	84
CD4021BE	57	CD4532BE	84
CD4022BE	79	CD4539BE	1.44
CD4023BE	19	CD4543BE	1.90
CD4024BE	44	CD4553BE	2.99
CD4025BE	20	CD4555BE	58
CD4026BE	1.45	CD4556BE	5.8
CD4027BE	42	CD4581BE	1.89
CD4028BE	54	CD4582BE	6.9
CD4029BE	75	CD4584BE	4.2
CD4030BE	38	CD4585BE	7.9
CD4033BE	1.67	CD4702BE	16.25
CD4034BE	2.44	CD4081BE	25
CD4035BE	75	CD4082BE	25
CD4040BE	64	CD4085BE	47
CD4042BE	54	CD4093BE	5.9
CD4043BE	59	CD4094BE	1.75
CD4044BE	52	CD4104BE	2.36
CD4045BE	79	40097PC	83
CD4047BE	72	40089PC	97
CD4050BE	32	74C14N	73
CD4051BE	55	74C20N	28
CD4052BE	65	74C76N	41
CD4053BE	79	74C85N	1.25
CD4060BE	89	74C107N	35
CD4066BE	54	74C161N	1.39
CD4068BE	24	74C163N	1.39
CD4069BE	25	74C173N	53
CD4070BE	29	74C175N	1.04
CD4071BE	29	74C192N	1.40
CD4072BE	19	74C193N	1.32

LINEAR IC'S

LM309K	1.56	LM741CH	5.8
LM323K	5.60	LM747CN	56
LM324CN	5.2	LM1488CN	64
LM339CN	5.2	LM1489CN	64
LM348CN	96	LM2240CN	1.60
LM555N-8	2.9	LM3403CN	1.19
LM556CN	5.2	LM4136CN	96
LM567N-8	9.8	LM4558CN	44
LM623CN	4.4	ULN2003AN	8.4

STATIC RAM'S

2101-35	1K (256 x 4)	350NS	22 PIN	2.95
2102-25	1K (1K x 1)	250NS	16 PIN	1.25
P2111-45	1K (256 x 4)	450NS	18 PIN	2.65
P2112-35	1K (256 x 4)	350NS	16 PIN	2.25
2114L-30	4K (1024 x 4)	300NS	18 PIN	8.65
2147	4K (4K x 1)	55NS	18 PIN	7.45
2147	4K (4K x 1)	70NS	18 PIN	19.95
P2016-15	16K (2K x 8)	150NS	24 PIN	14.88
P2016-20	16K (2K x 8)	200NS	24 PIN	14.88

DYNAMIC RAM'S

P4060-30	4K (4K x 1)	300NS	22 PIN	2.65
P4116-20	16K (16K x 1)	200NS	16 PIN	2.40
C4164-15	64K (64K x 1)	150NS	16 PIN	24.00
C4164-20	64K (64K x 1)	200NS	16 PIN	22.00

EPROM'S

C2708-45	8K (1K x 8)	450NS	24 PIN	3.75
C2716	16K (2K x 8)	450NS	24 PIN	5.95
Single 5V Supply, Intel Pin Out				5.95
C2716/TMS251616K (2K x 8)	450NS	24 PIN		5.95
Single 5V Supply, T1 Pin Out				12.95
C2532	32K (2K x 8)	450NS	24 PIN	12.95
T1 Pin Out				12.95
C2732	32K (4K x 8)	450NS	24 PIN	12.95
Intel Pin Out				44.00
C2564	64K (8K x 8)	450NS	24 PIN	44.00
T1 Pin Out				44.00
C2764	64K (8K x 8)	450NS	24 PIN	44.00
Intel Pin Out				2.98

SHIFT REGISTERS

1404A	TO-5 Single 1024 bit	2.98
3341APC	FIFO 1MHz	4.45
3342PC	64 bit	3.95
3347PC	80 bit	3.95

★ ★ ★ MEMORY SPECIALS ★ ★ ★

ONE TIME PRICES ONLY - Any order over \$50 receive free - MOS Memory Data Book

DYNAMIC RAM'S

P4060-30	4K (4K x 1)	300NS	22 PIN	2.65
P4116-20	16K (16K x 1)	200NS	16 PIN	2.40
C4164-15	64K (64K x 1)	150NS	16 PIN	24.00
C4164-20	64K (64K x 1)	200NS	16 PIN	22.00

PROM'S

74S1088	32 x 8	16 PIN	1.75
74S288N	32 x 8	16 PIN	1.75
93417/82S126	256 x 4	16 PIN	2.45
93427/82S129	256 x 4	16 PIN	2.45
93436/7620	512 x 4	16 PIN	4.60
93436/7621	512 x 4	16 PIN	4.60
93448/7641	512 x 8	24 PIN	7.45
93453/7643	1024 x 4	18 PIN	6.70
93451/82S181	1024 x 8	24 PIN	7.45
82S185/7128	2048 x 4	18 PIN	17.95
82S191/7138	2048 x 8	24 PIN	68.00

Z80 FAMILY

Z80-CPU	2.5 MHz	7.55
Z80A-CPU	4.0 MHz	9.45
Z80-PIO	2.5 MHz	6.65
Z80-PIO	4.0 MHz	7.65
Z80-CTC	2.5 MHz	5.95
Z80A-CTC	4.0 MHz	7.65
Z80-OMA	2.5 MHz	17.95
Z80-OMA	4.0 MHz	22.95
Z80-SIO/0	2.5 MHz	22.45
Z80-SIO/1	2.5 MHz	22.45
Z80A-SIO/1	4.0 MHz	27.85
Z80-SIO/2	2.5 MHz	22.45
Z80A-SIO/2	4.0 MHz	27.85
Z80-SIO/9	2.5 MHz	16.85
Z80A-SIO/9	4.0 MHz	21.54
Z80-DART	2.5 MHz	11.95
Z80A-DART	4.0 MHz	14.85

AP PRODUCTS TERMINAL AND DISTRIBUTION STRIPS

923285	12 Four Tie Point Terminals	2.40
	Distribution Strip 3.5" x .35"	
923281	18 Four Tie Point Terminals	2.80
	Distribution Strip 4.9" x .35"	
923277	24 Four Tie Point Terminals	3.50
	Distribution Strip 6.5" x .35"	
923293	36 Four Tie Point Terminals	3.95
	Distribution Strip 6.5" x .43"	
923273	34 Five Tie Point Terminals	5.35
	Terminal Strip 1.8" x 1.36"	
923291	54 Five Tie Point Terminals	6.75
	Terminal Strip 6.5" x .63"	
923269	68 Five Tie Point Terminals	9.55
	Terminal Strip 3.5" x 1.36"	
923265	86 Five Tie Point Terminals	11.20
	Terminal Strip 4.9" x 1.36"	
923261	128 Five Tie Point Terminals	14.00
	Terminal Strip 1.8" x 1.36"	

SCR'S and TRIAC'S

SATELLITE TELEVISION

SATELLITE TV antenna. 10 ft. fiberglass, complete, polar mount, \$1950.00, electronics at cost also. **TRI-STAR COMMUNICATIONS**, Box 843, Erie, MI 48133 (419) 726-1095

SATELLITE TV

- SYSTEMS • COMPONENTS • LNA's •
- ANTENNAS • RECEIVERS •

WE CAN HELP YOU!

HIGH FRONTIER

2230 E. Indian School Rd., Phoenix, AZ 85016
(602) 954-6008

Enjoy Satellite TV Now



Better than Cable TV—Over 200 TV and radio services. Why waste money? Learn the whole story and build a video system the family can enjoy. No commercials, **FREE** movies, sports and Vegas shows—worldwide, crystal clear reception connects to any TV set. Big (8 x 11 in.) book loaded with details, photos, plans, kits—**TELLS EVERYTHING! Satisfaction Guaranteed.**

Send \$7.95 TODAY! Add \$2.00 for 1st class (air mail) or call our 24 hour C.O.D. rush order line (305) 862-5068.

GLOBAL ELECTRONICS,
P.O. Box 219-E, Maitland, Florida 32751

SATELLITE Receiver kit. Antenna Kit. IF Strips. Mixers. IC'S. LNA'S. Hardware. Alignment service. **LANEY SCIENTIFIC INSTRUMENTS**, Box 20131, Jackson, MS 39209

GEOSTATIONARY satellite TV antenna aiming angles. Azimuth and elevation (true and magnetic) coordinates calculated by digital computer for your location. 23 satellites. Send name, address, your location's latitude and longitude (deg. min. sec.); or distance and direction from nearby town; or explicit geographical location in your city; plus \$6.50 to: **HUTSON INDUSTRIES, INC.**, P.O. Box 155, Scooba, MS 39358

Satellite TV

FOR THE HOME

Sick of Network TV?

Our receiver lets you get over 75 channels of television directly from earth-orbiting cable TV satellites: HBO, Showtime, super stations, sports and movies worldwide



From offshore oil rigs, data links to hotels and backyard installations, we wrote the book. Constantly updated, our 94 Page technical information book and catalog gives you all the facts. Inexpensive dishes, feeds, telemetry software, kits and more. Recommended reading by NASA, The Office of Consumer Affairs and quality companies like Rockwell/Collins. Send \$7.95 today!

We don't just sell information! We Manufacture Hardware!

CALL
24-hr. C.O.D. Hotline
(305) 339-7600

© **SPACECOAST**
RESEARCH CORPORATION
P.O. Box 442-E, Altamonte Spgs, FL 32701

SATELLITE antenna: build your own low cost, light weight, low wind resistance 12 ft. dish. For engineered drawings, instructions, and bill of materials, send \$15.00 to **KULICK ANTENNA**, 88 Standiford Ave., Sayreville, NJ 08872

Satellite Earth Station

complete systems from \$2,200.00

Send \$4.00 for our complete 50 page color catalog

TEI ELECTRONICS
P.O. Box 181108, Dept. 286A, Memphis, TN. 38118
901-795-4504

SATELLITE equipment catalog. Over 25 of the best manufacturers and suppliers. LNA's, receivers, antennas and complete systems covered in detail. Four different sections. \$12.00. **TMS CO.**, P.O. Box 8369, Roseville, MN 55113

SATELLITE TV

Make your first investment in Satellite TV the intelligent one!

* **Complete Handbook & Buyers Guide** - detailed, yet simple to understand. Includes equipment costs, kits, turnkey manufacturers - \$7.95.

* **Comp-Sat Location Analysis** - 6-page computer print out locates all 11 satellites. A must for any station. Send zip code, longitude & latitude or nearest intersection. - \$9.95.

* Both of the above for only \$16.95

INTERNATIONAL COMMUNICATIONS CO.

P.O. BOX 25036 - CHARLOTTE, N.C. 28212



McKAY SETS THE STANDARD FOR COMPACT AM RECEIVING ANTENNAS

DA100D OUTDOOR ANTENNA and DA9-DL4 LOOP ANTENNA


For specs & details contact these dealers

HARVEY RADIO & BARRY ELECTRONICS New York City
HENRY RADIO Los Angeles, CA
GILFERT ASSOCIATES Park Ridge, NJ
EDMOND SCIENTIFIC CO. Barrington, NJ
ELECTRONIC EQUIPMENT BANK Vienna, VA (D.C. Area)
PROMAR Tampa, FL
FRANK L. BEIER RADIO INC. Jefferson, LA
THE BASE STATION Concord, CA

J-MAR ELECTRONICS Toronto, Canada
INTERNATIONAL RADIO WORLD INC Vancouver, Canada

800/854-7769 Local • 714/621-6711
except Telex • 910-581-4990
Calif., Alaska, Hawaii

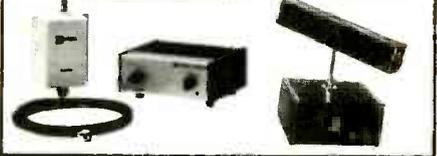McKay **G. E. McKAY & CO.**
SINCE 1932 111 S. College Ave.
PO Box 5000
Claremont, CA 91711



SATELLITE wall chart. 32"x24". color. Communications satellite programming and look angles. \$4.50 unframed. **GILLASPIE**, 950 Benicia Ave., Sunnyvale, CA 94086. Visa, Mastercard (408) 730-2500

SATELLITE TELEVISION EARTH STATION KIT LOW COST COMPLETE SYSTEM

Special Offer \$2,995.00

Kit includes all electronic and mechanical parts needed to assemble a complete operating Earth Station. You provide the labor and hand tools.

Included in the kit are a 12-foot fully steerable parabolic dish, low noise amplifier, antenna, rotator, receiver, modulator, necessary cables/connectors and complete assembly/operating instructions. **EVERYTHING** — down to the last nut, bolt and screw is provided.

Illustrated Brochure with Complete Details — \$2.00

MICRO TENNA ASSOCIATES
2335 South, 2300 West
Salt Lake City, Utah 84119



FREE \$200 value TVRO P.C. board set. when you join our development group. Complete systems low as \$700. Newest low cost designs, antennas, group purchasing, more. Info \$1.00, membership \$50. 509-534-8088 6-9 PM PST. **COMPUTER SATELLITE SERVICES**, 1604 N. Smith St., Spokane WA 99207

COMPUTER MARKET CENTER

COMPUTER MARKET CENTER ADVERTISING RATES 1" by 1 column (1 5/8") \$55.00. 1 1/2" by 1 column (1 5/8") \$82.50. 2" by 1 column (1 5/8") \$110.00. All ads must be prepaid. Send order and remittances to Computer Market Center, **Radio-Electronics Magazine**, 200 Park Avenue South, New York, New York, 10003. Address telephone inquiries to 212-777-6400. Frequency rates are available.

TEXAS

USED COMPUTER TERMINALS, PRINTERS, MODEMS, SURPLUS ELECTRONIC PARTS. CATALOG \$1.00

RONDURE COMPANY
THE COMPUTER ROOM
2522 BUTLER STREET
DALLAS, TEXAS 75235
(214) 630-4621



Thanks to you... it works...
for ALL OF US

United Way

A Public Service of This Magazine & The Advertising Council


RETAILERS

An ad for your computer store in this space in **Radio-Electronics COMPUTER MARKET CENTER** puts you in touch with our computer audience. They use micro-computer equipment for both business and hobby interests. For further details call 212-777-6400.

MICRO USERS

Colorful 8 1/2"x11" 100% plastic reference cards save you time and effort. Surpasses books, booklets, & fold-up paper summaries 2 sided & very complete. Clear info on instruction set, disassembly, ASCII, diagrams & much more. 1000's of delighted users. Just \$9.95 each. (Add \$1 p&h any quan.) Buy 4 get 5th free. 280, 6502, 8080 & 8085, 8088, ALGORITHMS. Full prompt money back guarantee. **Micro Logic Corp.** P.O. Box 174-A, Hackensack, New Jersey 07602.

SUPPORT
MARCH
OF DIMES

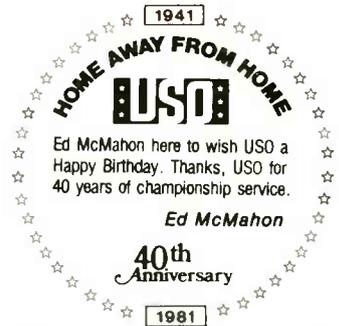

Ed McMahon here to wish USO a Happy Birthday. Thanks, USO for 40 years of championship service.

Ed McMahon

40th
Anniversary

1981

Take stock in America.
Buy U.S. Savings Bonds.

ramsey**the first name in Counters!****9 DIGITS 600 MHz \$129⁹⁵ WIRED**

PRICES
 CT-90 wired, 1 year warranty \$129.95
 CT-90 Kit, 90 day parts warranty 109.95
 AC-1 AC adapter 3.95
 BP-1 Nicad pack + AC Adapter/Charger 12.95
 OV-1, Micro-power Oven time base 49.95
 External time base input 14.95

The CT-90 is the most versatile, feature packed counter available for less than \$300.00! Advanced design features include; three selectable gate times, nine digits, gate indicator and a unique display hold function which holds the displayed count after the input signal is removed! Also, a 10mHz TCXO time base is used which enables easy zero beat calibration checks against WWV. Optionally, an internal nicad battery pack, external time base input and Micro-power high stability crystal oven time base are available. The CT-90, performance you can count on!

SPECIFICATIONS:

Range: 20 Hz to 600 MHz
 Sensitivity: Less than 10 MV to 150 MHz
 Less than 50 MV to 500 MHz
 Resolution: 0.1 Hz (10 MHz range)
 1.0 Hz (60 MHz range)
 10.0 Hz (600 MHz range)
 9 digits 0.4" LED
 Display: Standard-10,000 mHz, 1.0 ppm 20-40°C.
 Time base: Optional Micro-power oven-0.1 ppm 20-40°C
 Power: 8-15 VAC @ 250 ma

7 DIGITS 525 MHz \$99⁹⁵ WIRED**SPECIFICATIONS:**

Range: 20 Hz to 525 MHz
 Sensitivity: Less than 50 MV to 150 MHz
 Less than 150 MV to 500 MHz
 Resolution: 1.0 Hz (5 MHz range)
 10.0 Hz (50 MHz range)
 100.0 Hz (500 MHz range)
 Display: 7 digits 0.4" LED
 Time base: 1.0 ppm TCXO 20-40°C
 Power: 12 VAC @ 250 ma

The CT-70 breaks the price barrier on lab quality frequency counters. Deluxe features such as, three frequency ranges - each with pre-amplification, dual selectable gate times, and gate activity indication make measurements a snap. The wide frequency range enables you to accurately measure signals from audio thru UHF with 1.0 ppm accuracy - that's .0001%! The CT-70 is the answer to all your measurement needs, in the field, lab or ham shack.

PRICES:

CT-70 wired, 1 year warranty \$99.95
 CT-70 Kit, 90 day parts warranty 84.95
 AC-1 AC adapter 3.95
 BP-1 Nicad pack + AC adapter/charger 12.95

**7 DIGITS 500 MHz \$79⁹⁵ WIRED****PRICES:**

MINI-100 wired, 1 year warranty \$79.95
 AC-Z Ac adapter for MINI-100 3.95
 BP-Z Nicad pack and AC adapter/charger 12.95

Here's a handy, general purpose counter that provides most counter functions at an unbelievable price. The MINI-100 doesn't have the full frequency range or input impedance qualities found in higher price units, but for basic RF signal measurements, it can't be beat! Accurate measurements can be made from 1 MHz all the way up to 500 MHz with excellent sensitivity throughout the range, and the two gate times let you select the resolution desired. Add the nicad pack option and the MINI-100 makes an ideal addition to your tool box for "in-the-field" frequency checks and repairs.

SPECIFICATIONS:

Range: 1 MHz to 500 MHz
 Sensitivity: Less than 25 MV
 Resolution: 100 Hz (slow gate)
 1.0 KHz (fast gate)
 Display: 7 digits, 0.4" LED
 Time base: 2.0 ppm 20-40°C
 Power: 5 VDC @ 200 ma

8 DIGITS 600 MHz \$159⁹⁵ WIRED**NEW
READ
RECEIVER
FREQUENCY****SPECIFICATIONS:**

Range: 20 Hz to 600 MHz
 Sensitivity: Less than 25 mv to 150 MHz
 Less than 150 mv to 600 MHz
 Resolution: 1.0 Hz (60 MHz range)
 10.0 Hz (600 MHz range)
 Display: 8 digits 0.4" LED
 Time base: 2.0 ppm 20-40°C
 Power: 110 VAC or 12 VDC

The CT-50 is a versatile lab bench counter that will measure up to 600 MHz with 8 digit precision. And, one of its best features is the Receive Frequency Adapter, which turns the CT-50 into a digital readout for any receiver. The adapter is easily programmed for any receiver and a simple connection to the receiver's VFO is all that is required for use. Adding the receiver adapter in no way limits the operation of the CT-50, the adapter can be conveniently switched on or off. The CT-50, a counter that can work double-duty!

PRICES:

CT-50 wired, 1 year warranty \$159.95
 CT-50 Kit, 90 day parts warranty 119.95
 RA-1, receiver adapter kit 14.95
 RA-1 wired and pre-programmed (send copy of receiver schematic) 29.95

**DIGITAL MULTIMETER \$99⁹⁵ WIRED****PRICES:**

DM-700 wired, 1 year warranty \$99.95
 DM-700 Kit, 90 day parts warranty 79.95
 AC-1, AC adaptor 3.95
 BP-3, Nicad pack + AC adapter/charger 19.95
 MP-1, Probe kit 2.95

The DM-700 offers professional quality performance at a hobbyist price. Features include; 26 different ranges and 5 functions, all arranged in a convenient, easy to use format. Measurements are displayed on a large 3 1/2 digit, 1/2 inch LED readout with automatic decimal placement, automatic polarity, overrange indication and overload protection up to 1250 volts on all ranges, making it virtually goof-proof! The DM-700 looks great, a handsome, jet black, rugged ABS case with convenient retractable tilt bail makes it an ideal addition to any shop.

SPECIFICATIONS:

DC/AC volts: 100uV to 1 KV, 5 ranges
 DC/AC current: 0.1uA to 2.0 Amps, 5 ranges
 Resistance: 0.1 ohms to 20 Megohms, 6 ranges
 Input impedance: 10 Megohms, DC/AC volts
 Accuracy: 0.1% basic DC volts
 Power: 4°C cells

AUDIO SCALER

For high resolution audio measurements, multiplies UP in frequency.

- Great for PL tones
- Multiplies by 10 or 100
- 0.01 Hz resolution!

\$29.95 Kit \$39.95 Wired

ACCESSORIES

Telescopic whip antenna - BNC plug \$ 7.95
 High impedance probe, light loading 15.95
 Low pass probe, for audio measurements 15.95
 Direct probe, general purpose usage 12.95
 Tilt bail, for CT 70, 90, MINI-100 3.95
 Color burst calibration unit, calibrates counter against color TV signal 14.95

COUNTER PREAMP

For measuring extremely weak signals from 10 to 1,000 MHz. Small size, powered by plug transformer-included.

- Flat 25 db gain
- BNC Connectors
- Great for sniffing RF with pick-up loop

\$34.95 Kit \$44.95 Wired

ramsey electronics, inc.
 2575 BAIRD RD. • PENFIELD, NY 14526

PHONE ORDERS
 CALL 716-586-3950

TERMS

Satisfaction guaranteed - examine for 10 days, if not pleased return in original form for refund. Add 5% for shipping insurance to a maximum of \$10. Overseas add 15% COD, add \$2. Orders under \$10, add \$1.50. NY residents add 7% tax.

CIRCLE 49 ON FREE INFORMATION CARD

Someday you'll need a computer; that's when you should remember the best way to buy a stereo.

When buying a stereo, you pick and choose the best components available.

Computers are like stereos. You can buy all-in-one models that are great for the kids; but for business, scientific, and industrial computer applications, the only way to protect your investment and optimize performance is with a component system.

CompuPro makes the fastest most reliable, highest quality S-100 components in the industry; the same components chosen by companies like IBM can solve your computing problems too.

IBM is a registered trademark of International Business Machines Inc.

CompuPro™

division

GODBOUNT ELECTRONICS

OAKLAND AIRPORT, CA 94614-O355 (415)562-0636

Our nationwide network of authorized sales centers will be glad to introduce you to CompuPro quality computing. Call 415-562-0636 today for the center nearest you.

CIRCLE 66 ON FREE INFORMATION CARD

SATELLITE TV. Books, parts, low-noise micro-wave transistors. Specs and catalog \$2.00. ELITE ELECTRONICS, RR1, St. George, Ontario, Canada N0E 1N0

Satellite Television: THE ILLUSTRATED Jamescomm Report

\$12.95 mailed 1st class
\$18.95 outside N. America (air)

24 Hour COD Line:
312-672-6996

JAMESCOMM Publications
P.O. Box 31
Crete, Illinois 60417



SYSTEM 20

- Precision 25" Parabolic Antenna
- Prebuilt Converter and Preamp
- Assembled Power Supply
- Low-loss Coaxial Cables
- One Year Warranty
- Completely Built and Tested

\$289.95
+ \$5.00 shipping

DATA SERVICE CO.
3110 Evelyn Street
Roseville, MN 55113
612-636-9469

PLANS & KITS

OSCILLOSCOPE performance from your unmodified television for less than \$25. Super simple, accurate, practical. Order Tele-Scope circuit board and plans \$8.50. Get two for dual trace \$15. MICROGRID, Box 613, Ithaca NY 14850

SATELLITE TVRO parabolic aluminum dish, local materials \$500. Plans, formulas \$10.00. **WARD MICROWAVE**, Box 100, Conway, NC 27820

DECODE Morse, RTTY, and ASCII signals from airwaves with new **Code*Star**. LED readout or connect with your computer/printer. Keyboard, other items also available. Kits or assembled. **MICROCRAFT**, Box 513R, Thiensville, WI 53092 (414) 241-8144

FREE KIT Catalog

FUNCTION GENERATOR KIT \$59.95
Auto-Ranging Cap-meter kit \$79.95

Phone 415-447-3433

Write or Phone for FREE CATALOG.
Average 1 minute Saturday call is 21¢.

contains TEST & EXPERIMENTER'S EQUIP.

DAGE SCIENTIFIC INSTRUMENTS
BOX 1054R LIVERMORE CA 94550

KIRLIAN photography as a hobby. Complete plans for do-it-yourself machine. Includes easy instructions and ways to improve quality of prints. \$5.00. **C.E.L.C. ELECTRONICS**, P.O. Box 805, Missouri City, TX 77459

NEGATIVE ion generators. Send for free information to **THE SEAWARD COMPANY**, P.O. Box 2039, Burbank, CA 91507



WERSI KEYBOARD KITS

WERSI Organs are demonstrably superior in overall performance, to ALL commercially built instruments, regardless of price. Best of all, you save 1/2 to 2/3 the cost with our easy to build kits. (Also factory assembled).

And now — after 3 years in research, the totally unprecedented "Pianostar" electronic piano (and much more!) has been unveiled to international raves! You have to hear it to believe it!

Explore the exciting world of WERSI, Free information package.
Call free, 24 hrs.: 1-800-233-3865
(in PA call: 717/299-4327, 9-5)
Ask for "WERSI DATA PAK #M33"
Please specify Piano or Organ

ATV Research ...specialists in CCTV and computer monitors!

Video monitors - color & B/W * TV Cameras, kits, parts & plans * Video-to-RF modulators * Free catalog, Phone or write. (402) 987-3771

13-RE Broadway Dakota City, NE. 68731

MICROWAVE downconverter kit \$169.00. Includes everything. Informative catalog on subscription TV products \$2.00. **J & W ELECTRONICS**, P.O. Box 61, Cumberland, RI 02864


MICROWAVE HORN ANTENNA KIT

1.7-26 GHz Frequency Range 17-19 db Gain Kit w/Assembly Instructions \$39.95*
Down Converter Board \$19.95* (w/Antenna Kit \$14.95)
Parts Kit for Board \$29.95* (w/Antenna or Board \$24.95)
Complete Package (Antenna, Board & Parts Kit) \$79.95

MICROTENNA ASSOCIATES

2335 South 2300 West, Salt Lake City, Utah 84119
Check or M.O. only — Allow 2-4 Weeks Delivery (Cost includes shipping)
*Utah Residents Please Add 5% Sales Tax

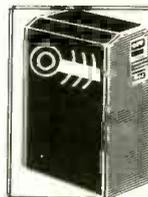MICROPROCESSOR trainer, learn by constructing and programming a microcomputer for under \$70.00. Instructions/plans \$6.00. **MICRO-DEVELOPMENT CORPORATION**, Box 419, Edwardsburg, MI 49112



MINI FM MIC

Compact size, only 2" x 1" x 3/4". Transmit to FM radio 88-108 MHz. Exceptional audio quality. Transmits stable signal up to 900 ft. Complete kit incl. case, battery & instructions Only \$13.95. Assembled \$18.95. Add \$1.55 S&H ea. Send 18c stamp for brochure

S.E. Corp., Box 19699-R
Temple Terrace, FL 33687

MUSICAL car horn 64 tunes. No chips to buy. Kit with case less horn. \$31.95. Factory assembled with horn. \$41.95. Add \$2.50 shipping. **ELECTRONIC SOUND**, P.O. Box 401951, Garland, TX 75040

MICROWAVE television "downconverters" under \$50.00. High quality, easily assembled. Catalogue: \$2.00 (refundable). **NDS**, Box 12652-R, Dallas, TX 75225

PROJECTION TV...Convert your TV to project 7 foot picture. Results equal to \$2,500 projector. Total cost less than \$20.00. Plans & lens \$16.00. Illustrated information free. Credit card orders... 24 hours. (215) 736-3979. **MACROCOMGFF** Washington Crossing, PA 18977

COAXIAL CABLE SALE

POLYETHYLENE DIELECTRIC
RG213 noncontaminating 95% shield mil spec... 36c/ft.
RG58AU stranded MIL-SPEC... 12c/ft.
RG8U 95% shield MIL SPEC... 31c/ft.

LOW LOSS FOAM DIELECTRIC
RG8X (mini 8) 95% shield... 17c/ft.
RG8U 97% shield... 30c/ft.
RG58U 95% shield... 10c/ft.
RG58AU stranded center 80% shield... 11c/ft.
RG59/U 100% foil shield TV type... 10c/ft.
Rotor Cable 2-18 ga 6-22 ga... 19c/ft.
Cable-shipping \$3.00 1st 100 ft., \$2.00 each add'l 100 ft.

CONNECTORS

PL-259 & SO-239... 10/\$5.89
Reducer UG-175 or 176... 10/\$1.99
UG-255 (PL-259 to BNC)... \$3.50

Connectors—shipping 10% add'l. \$1.50 minimum

FREE CATALOG

COD add \$1.50 — FLA. Res. add 4% Sales Tax

NEMAL ELECTRONICS

5685 SW 80th Street, Miami, FL 33143
Call (305) 661-5534

PCB. 15c sq-in. Free drilling. Satisfaction guaranteed. **INTERNATIONAL ENTERPRISE**, 6452 Hazel Circle, Simi Valley, CA 93063

PRINTED circuit boards from sketch or artwork. Kit projects. Free details. **DANOCINTHS INC.**, Box 261, Westland, MI 48185

There's no place like Radio Shack's Parts Place™

No waiting! Huge selection! Top quality and value!

A SPDT DIP relay

5 VDC, 56-ohm coil. Ideal for transistor projects and low-power switching. Contacts rated 1 amp at 125 VAC. For socket or PC board mounting. Just $\frac{3}{16} \times \frac{1}{8} \times \frac{7}{16}$ ".
275-216 2.99

B Mercury switch

Subminiature size, rated 100 milliamps at 24 VDC. Great for anti-tamper alarms and position sensing. 275-025 ... 89¢

C Lighted switch

SPST. Looks great in projects or vehicles. Red LED in handle glows when "on." Rated 5 amps. 12 VDC only.
275-680 2.99

D DPDT knife switch

For model railroads, reversing polarity, antenna switching, and many other low-voltage uses. 275-1537 99¢

E Six mini red lamps

Cute incandescents for model railroads, dials, winken-blinken boxes and more. 60 milliamps at 6 volts. 5" leads.
272-1144 Pkg. of 6/99¢

F "Helping Hands"

This sturdy, fully adjustable holder frees your hands for easier building and repair. Cast iron base, nickel-plated clamps. 64-2093 7.95

G 25-range VOM

Ready-to-use Micronta® multi-tester features a mirrored scale and 20,000 ohms per volt DC sensitivity. Measures 0 to 1200 volts DC in seven ranges, 0 to 1200 volts AC in five ranges. DC current, 0 to 250 milliamps in four ranges. Resistance in four ranges. Decibels, -20 to +63 in five ranges. $5\frac{1}{2} \times 3\frac{7}{8} \times \frac{1}{2}$ ". Requires "AA" battery. 22-202 27.95

H IF amplifier

MC1350. Operates from DC to beyond 60 MHz. 8-pin DIP with specs. 276-1758 2.19

J Video detector

MC1330. Excellent linearity. Used in many late-model TV receivers. Separate video and AFT outputs. 8-pin with specs. 276-1757 2.49

K FM detector

MC1358/CA3065. IF amp, FM detector, audio driver in a 14-pin. 276-1759 1.79

L Ohm's law guide

Pocket slide rule solves Ohm's law and parallel resistance problems—a real timesaver for your workbench!
271-1211 49¢

M Three mini motors

Ideal for solar displays, models and more. $1\frac{1}{2}$ to 6 VDC. 273-208 Pkg. of 3/1.49

N Test clips

Spring action—a "must" for testing on crowded boards. $3\frac{1}{2}$ " long. One red, one black. 270-352 Pkg. of 2/1.69

O IF filter

SFE10.7MA5-A. Full-spec, 3-lead ceramic device for 10.7 MHz FM IFs. 272-1301 Pkg. of 2/1.99

P Schottky IC sale!

All are first-quality devices, include pin-out and specs.

Type	Cat. No.	Reg.	SALE
74LS00	276-1900	.79	.59
44LS02	276-1902	.79	.59
74LS04	276-1904	.79	.59
74LS08	276-1908	.79	.59
74LS32	276-1915	.89	.69
74LS74	276-1919	.79	.59
74LS75	276-1920	.99	.79
74LS90	276-1923	1.09	.89
74LS123	276-1926	1.49	1.19
74LS138	276-1939	1.19	.99
74LS161	276-1931	1.39	1.09
74LS164	276-1932	1.39	1.09
74LS175	276-1934	1.19	.99
74LS193	276-1936	1.49	1.19
74LS240	276-1940	1.99	1.49
74LS244	276-1941	1.99	1.49
74LS245	276-1942	2.99	1.99
74LS367	276-1835	1.29	.99
74LS373	276-1943	2.39	1.59
74LS374	276-1944	2.39	1.59

Q Logic probe

Indicates high, low or pulsed logic states with easy-to-read LEDs. Overload and reverse polarity protected.
22-301 19.95

R Portable mini vise

Handy for soldering, glueing, drilling. Instant vacuum mount on any smooth non-porous surface. 64-2094 2.99

S Tech books

Understanding Satellite Communications Systems. 256 pages. 62-2018 ... 2.95
Understanding Optronics. 62-1384 2.95
Understanding Computer Science. 62-1383 2.95

T Transformer

Primary: 120 VAC. Secondary: 24 VAC at 300 milliamps. Top quality. 273-1386 3.49

U Binding posts

Pushbutton release and secure contact. One red, one black. 274-660 Pkg. of 2/1.39

V PC transfers

Simply rub strips, circles, pads on your board and etch! 276-1577 Set of 4/2.49

W Project cabinet

Distinctive 2-tone styling with easy-to-work end panels. $2\frac{1}{4} \times 5 \times 5\frac{1}{4}$ ". 270-218 .. 7.95

Radio Shack®

A DIVISION OF TANDY CORPORATION • OVER 8200 LOCATIONS IN 73 COUNTRIES

Retail prices may vary at individual stores and dealers.

CIRCLE 46 ON FREE INFORMATION CARD

LOW TIM DC STEREO PRE-AMP KIT TA-10 20

Incorporates brand-new D.C. design that gives a frequency response from 0Hz-100KHz $\pm 0.5dB$! Added features like tone defeat and loudness control let you tailor your own frequency supplies to eliminate power fluctuation! Specifications: • T.H.D. less than .005% • T.I.M. less than .005% • Frequency response: DC to 100KHz $\pm 0.5dB$ • RIAA deviation: $\pm 0.2dB$ • S/N ratio: better than 70dB • Sensitivity: Phono 2MV 47K/Aux. 100MV 100K • Output level: 1.3V • Max output: 15V • Tone control: bass $\pm 10dB$ @ 50Hz/treble $\pm 10dB$ @ 15Hz • Power supply: ± 24 D.C. @ 0.5A
Kit comes with regulated power supply, all you need is a 48V C.T. transformer @ 0.5A

ONLY \$44.50
X'former
\$4.50 ea.



100W CLASS A POWER AMP KIT

Dynamic Bias Class "A" circuit design makes this unit unique in its class. Crystal clear, 100 watts power output will satisfy the most picky fans. A perfect combination with the TA-1020 low T.I.M. stereo pre-amp. Specifications:

- Output power: 100W RMS into 8-ohm 125W RMS into 4-ohm
- Frequency response: 10Hz-100KHz
- T.H.D.: less than 0.008%
- S/N ratio: better than 80dB
- Input sensitivity: 1V max.
- Power supply: $\pm 40V$ @ 5 amp
- One channel, needs two for stereo



TA-1000KIT
\$51.95
Power transformer
\$24.00 each

50 WATTS AUTO STEREO BOOSTER BY VERTRONIX

- Specifications:
- 50 watts RMS total (25W + 25W)
 - Frequency Response: $\pm 0.5dB$, 20Hz~20KHz
 - T.H.D.: 0.2% at full rated output
 - Input Impedance: 20K ohms
 - Crosstalk: Better than 90dB
 - Sensitivity: 1.5V for full rated output
 - S/N Ratio: Greater than 95dB
 - Speaker Load: 2~8 ohms
 - Voltage Supply: 9~18V D.C.

Model V-Amp 500

REG. PRICE \$119.00 EACH
OUR SPECIAL PRICE \$55.00 EACH

"FISHER" 30 WATT STEREO AMP

Kit includes 2 pcs. Fisher PA 301 Hybrid IC all electronic parts with PC Board. Power supply $\pm 16V$ DC (not included). Power band with (KF 1% $\pm 3dB$). Voltage gain 33dB. 20Hz-20KHz.

Super Buy Only \$18.50

5W AUDIO AMP KIT

2 LM 380 with Volume Control Power Supply 6 18V DC
ONLY \$6.00 EACH

2 WATT AUDIO AMP

Pre assembled units. All you need is to hook up the speaker and the volume control. Supply voltage from 9~15V D.C. measures only 2" x 3 1/2", making it good for portable or discrete applications. Comes with hook up data.

BUY 2 FOR \$4.99

1 WATT AUDIO AMP

All parts are pre-assembled on a mini PC Board. Supply Voltage 6~9V D.C.
SPECIAL PRICE \$1.95 ea.



NEW MARK III 9 Steps 4 Colors LED VU

Stereo level indicator kit with arc-shape display panel!!! This Mark III LED level indicator is a new design PC board with an arc-shape 4 colors LED display (change color from red, yellow, green and the peak output indicated by rose). The power range is very large from -30dB to +5dB. The Mark III indicator is applicable to 1 watt - 200 watts amplifier operating voltage is 3V-9V DC at max 400 MA. The circuit uses 10 LEDs per channel. It is very easy to connect to the amplifier. Just hook up with the speaker output!

IN KIT FORM \$18.50

MARK IV 15 STEPS LED POWER LEVEL INDICATOR KIT

This new stereo level indicator kit consists of 36 4-color LED (15 per channel) to indicate the sound level output of your amplifier from -36dB +3dB. Comes with a well-designed silk screen printed plastic panel and has a selector switch to allow floating or gradual output indicating. Power supply is 6 12V D.C. with THG on board input sensitivity controls. This unit can work with any amplifier from 1W to 200W!
Kit includes 70 pcs. driver transistors, 38 pcs. matched 4-color LED, all other electronic components, PC board and front panel.



MARK IV KIT \$31.50

MARK V 15 STEPS LED POWER OUTPUT INDICATOR KIT

All functions same as Mark IV but this is with heavy duty aluminum front plate and case. Can be easily slot into the front panel of your auto, truck or boat. Operates on 12V DC.



\$41.50 EACH KIT

SOLID STATE STEREO GRAPHIC EQUALIZER PRE AMP KIT TA-2500

Specifications:

- Total Harmonic Distortion: Less than 0.05%
- Intermodulation Distortion: (70Hz:7KHz = 4:1 SMPTE Method) Less than 0.03%
- Frequency Response: Overall 10Hz ~ 100KHz +0.5dB, -1dB
- RIAA Curve Deviation: (Phono) +0.2dB, -0.2dB (30Hz ~ 15KHz)
- Channel separation (at rated output 1KHz)
- Phono, Tuner, Aux and Tape Monitor better than 70dB.
- Input sensitivity and impedance (1KHz for rated output) Phono: 2MV 47K ohms Aux: 130MV 50K ohms Tuner: 130MV 50K ohms Tape: 130MV 50K ohms
- Graphic Equalizer control: 10 Band Slide Control
- Frequency Bands: 31.5Hz; G3Hz; 125Hz; 250Hz; 500Hz; 1KHz; 2KHz; 4KHz; 8KHz; 16KHz also with on panel selector for Phono, Tuner, Aux 1 and Aux 2.
- Power Supply: 117 VAC

Kit comes with all electronic components, transformer, instructions and a 19" rack mount type metal cabinet.



MODEL TA-2500 \$119.00 PER KIT

ELECTRONIC DUAL SPEAKER PROTECTOR




Cut off when circuit is shorted or over load to protect your amplifier as well as your speakers. A must for OCL circuits.

KIT FORM \$8.75 EA.

PROFESSIONAL REGULATED VARIABLE D.C. POWER SUPPLY KIT

All solid state circuitry with high efficiency power transistor 2SD388 and I.C. voltage regulator MC1733. Output voltage can be adjusted from 0-30V at 1 amp current limited or 0-15V at 2 amp current limited. Internal resistance is less than 0.005 ohm; ripple and noise less than 1 MV. dual on panel meter for voltage and amp reading, also with on board LED and audible over load indicator. Kit comes with predrilled P.C. board, instructions, all necessary electronic components, transformer and a professional look metal cabinet. The best project for school and the most useful instrument for repairman. Build one today!

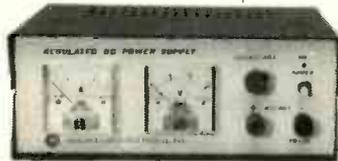MODEL TR 88A 0 ~ 15V D.C. 2 amp
MODEL TR 88B 0 ~ 30V D.C. 1 amp



\$59.50 PER KIT

REGULATED DUAL VOLTAGE SUPPLY KIT

± 4 ~ 30V DC 800 MA adjustable, fully regulated by Fairchild 78MG and 79MG voltage regulator I.C. Kit includes all electronic parts, filter capacitors, I.C., heat sinks and P.C. board.



\$12.50 PER KIT


POWER SUPPLY KIT

0-30V D.C. REGULATED
Uses UA723 and ZN3055 Power TR output can be adjusted from 0-30V, 2 AMP. Complete with PC board and all electronic parts. Transformer for Power Supply, 2 AMP 24V x 2



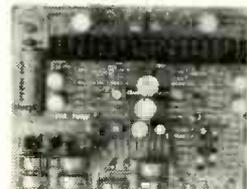0-30 Power Supply
\$10.50 each

TA-323 6 WATTS TOTAL 30W + 30W STEREO AMP KIT



★ SPECIAL ★
EXCELLENT PRICE!

MODEL 001-0034
Transformer (Optional)

This is a solid state all transistor circuitry with on board stereo pre-amp for most microphone or phone input. Power output employs 2 pairs matching Darlington Transistors. Driven by the popular 2N3053 Driver Transistors. Four built on board controls for; volume, balance, treble and bass. Power supplies requires 48 VET 2.5 amp transformer. T.H.D. of less than 0.1% between 100 Hz and 10KHz at full power. (30 Watts + 30 Watts loaded by 8~).

\$29.50 PER KIT
\$10.50 EACH

POCKET STEREO CASSETTE PLAYER WITH STEREO HEAD PHONE



This unit is a high fidelity stereo player which will give you years of listening pleasure and follow you wherever you go. Made by the same company in Japan who use the "Big Name."

Complete set comes with 1 Stereo head-phone, 3 AA size alkaline batteries, 1 leather like carrying case for player and 1 carrying case for storage of 4 cassette tapes and 1 demo tape.

MODEL SWM-33
OUR DIRECT IMPORT PRICE

\$67.50



FORMULA INTERNATIONAL INC.

2/82

	SHIPPING AND HANDLING CHARGES	
	Under \$50.00 purchase	Over \$50.00 purchase
Inside California	10%	5%
Outside Calif. (includes Mexico & Canada)	15%	10%
Overseas	25%	20%

Send \$1.00 For Detailed Catalogue

Minimum Order: \$10.00/Call! Residents Add 6% Sales Tax
Phone Orders Accepted on Visa or MC ONLY, NO C.O.D./Store Hours 10-7 Mon. thru Sat.

12603 CRENSHAW BLVD., HAWTHORNE, CA 90250
PHONE: (213) 973-1921 • (213) 679-5162



FOR COMMERCIAL FREE TV BOX BUILDERS

MC 1358	\$2.50	LM 7815	\$1.20
MC 1350	\$2.00	NE 565	\$2.00
MC 1330	\$3.00	Connectors Set	\$1.00
LM 1458	\$1.00	I.C. Socket Set	\$2.00
LM 380	\$2.00	Marching Transformer	\$1.40
Sanyo UHF Tuner	\$35.00	Tolrid Coils	
Capacitors Set	\$12.50	(Set of 4)	\$3.00
Resistors Set	\$2.00	Speaker Cabinet	\$12.95
Trim Pots:		Transformer	
Trim Caps Set	\$13.50	18V 800MA	\$3.00
Pots and Knobs	\$2.00		

We sell you all the above components in a package for **\$125.00** and you will receive a free predrilled P.C. board and instructions at no charge!

SANYO UHF VARIATOR TUNER

For UHF CH 14 83

Tuning voltage +1V~+28V D.C. Input impedance 75 OHM. I.F. band width 7~16 MHz. Noise figure 11.5dB MAX. Size 2 3/4" x 1 1/4" x 3/4". Supply voltage 15V D.C. Sound I.F. = 58.0 MHz. Video I.F. = 62.5 MHz.



All units are brand new from Sanyo. MODEL 115-B-405A **\$35.00 EACH**

Tuner is the most important part for the circuit. Don't let those \$19.00 tuners fool you!


TV GAME BOARD

PLAYS 4 GAMES: TENNIS; HOCKEY; HANDBALL AND JAI-ALAI.

All boards complete with all parts ready to play. Requires 6C size batteries and a small speaker for sound effects. The boards were surplus from a famous game manufacturer. They will play on all US standard black and white or color TV sets. (Regular price for these games were \$39.50 each) **OUR PRICE ONLY \$6.50 EACH**



PART #57456

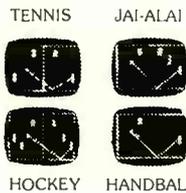

ELECTRONIC PIN BALL MACHINE



That sounds and plays like the real thing. All units are brand new but without the case. Functions of the game include double flipper control, kicker control, 1-4 players, 3 speed ball control, tilt switch, automatic score, extra bonus cave and many more. All solid state with LED panel, no moving parts. Requires 9V battery to operate, speaker not included.

A perfect gift for yourself or friends.

SPECIAL **\$8.99 EACH** SPEAKER **\$1.25 EACH**

ELECTRONIC MUSICAL TELEPHONE REST KIT

This telephone rest can be used as a door charm, an audible indicator and for many other sound projects. The special custom made I.C. is pre programmed with 4 musical tunes. Kit comes with a nice looking plastic case, pre-drilled P.C. board, volume control, special sound I.C. speakers and all electronic components and instructions. Ideal for home or school projects.



MODEL FIH-3000

BUY NOW!

SPECIAL PRICE! ONLY

\$15.50 PER KIT

DIGITAL TIMER/CLOCK

- 24 Hour preset time to turn on or off
- 12 Hour green 0.5" display for time
- operated on 12~16V A.C.

The whole timer is self contained in a compact plastic case (as seen in photo). Designed for VTR with push button switch for easy setting. Limited quantity available



NOW ONLY \$12.94 MODEL VEQ 0143

SANYO ANTENNA SIGNAL BOOSTER

This Booster is specially designed for UHF Channels (14-83). After installed this unit (between the antenna input cable and the UHF tuner) will have a minimum of 10dB gain, that is approximately 2 times better than what you are seeing now. Ideal for those who live in apartments that cannot put up an outdoor antenna. Size is so small, only 2" x 1 1/2" x 1". Supply voltage is 15 VDC.



★ NEW ITEM ★

MODEL 001-0076

\$12.50 EACH

13 FUNCTIONS LCD TIME MODULE



MODEL 001-0062

\$7.94 EACH

- Displays month, date and day of the week
- Displays hour, minute and second
- AM, PM Indicator
- Alarm 1 and Alarm 2 (Independent)
- 10 Hours Stop Watch
- 12 Hours presettable count down time
- Hour Charm Indicator
- Back light by touch of the switch

These modules are brand new and made by LITRONIX. Designed for a man's watch. Can be used for many applications. Comes with 2 silver batteries and the ceramic round transducer.

MATCHED PAIR POWER TRANSISTORS BY MOTOROLA

MJ2955 PNP	150 Watts	BV=60 V	\$3.50
2N3055 NPN		I.C.=15 A	per pair
MJE2955 PNP	90 Watts	BV=60 V	\$3.00
MJE3055 NPN		I.C.=10 A	per pair
MJ15003 NPN	250 Watts	BV=140 V	\$12.00
MJ15004 PNP		I.C.=20 A	per pair

All above parts guaranteed to be prime and come with data sheets.

MUFFIN FANS FOR EQUIPMENT COOLING



These fans are pulled out from used computers. But carefully cleaned by ultrasonic cleaner. All in "like-new" condition. Size 4 11/16" x 1-1/2" x 4 11/16".

MODEL MF505 **\$9.50 EACH**

FLUORESCENT LIGHT DRIVER KIT



12V DC POWERED Lights up 8~15 Watt Fluorescent Light Tubes. Ideal for camper, outdoor, auto or boat. Kit includes high voltage coil, power transistor, heat sink, all other electronic parts and PC Board, light tube not included!

\$6.50 Per Kit

PRESS-A-LIGHT SELF GENERATED FLASHLIGHT

Never worry about battery, because it has none! Easy to carry in pocket and handy to use. Ideal for emergency light. It generates its own electricity by squeezing grip lever. Put one in your car, boat, camper or home. You may need it some time!



Model F-179

EXCLUSIVE! **\$3.95 ea.**

No FCC license required. **OUR PRICE \$49.50** ADDITIONAL MICROPHONE (TRANSMITTER) AVAILABLE AT **\$28.00 EACH**



MURA WMS-49


monitors the signal strength from the microphone. Standard phone jack outlet connection to a P.A. or other phone input. 9V battery included. This professional set is ideal for on stage, in field, church, in house or outdoor use.

CRYSTAL CONTROLLED WIRELESS MICROPHONE SYSTEM

Transmitter: FET mic for flat 30 ~18 KHz response extra controlled 49MHz AM Band for drift-free performance. 100 MW output (range approx. 1/4 mile) for reliable long range transmission. Powered by a 9V radio battery (included).

Receiver: Extra controlled locks on 49MHz transmitter signal. With on panel VU meter

SUPER FM WIRELESS MIC KIT— MARK III

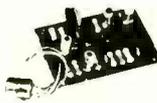

This new designed circuit uses high FEQ. FET transistors with 2 stages pre amp. Transmits FM Range (88-120 MHz) up to 2 blocks away and with the ultra sensitive condenser microphone that comes with the kit, allows you to pick up any sound within 15 ft. away! Kit includes all electronic parts, OSC coils, and P.C. Board. Power supply 9V D.C.

FMC-105

\$11.50 PER KIT

WEM-36 FM WIRELESS MICROPHONE

TEET MODEL WEM-36 is a factory assembled FM wireless microphone powered by two AA size batteries. Transmits in the range of 88-108 MHz with 3 transistor circuits to meet with F.C.C. part 15 regulations. Element is built in a plastic tube type case with an omni-directional electret condenser microphone unit. By using a standard FM radio, signal can be heard anywhere on a one-acre lot. Sound quality was judged "very good."



MODEL WEM-36

\$16.50 EACH

WHISTLE ACTIVATED SWITCH BOARD

All boards are pre-assembled and tested. Your whistle to its FET condenser microphone from a distance, as far as 30 feet away (sensitivity can be easily adjusted) will turn the switch on, then match your whistle to it again, then it turns off. Ideal for remote control toys, electrical appliance such as lights, coffee pots, TV, Hi-Fi, radio or other projects. Unit works on 9V D.C.



MODEL 968 **\$4.50 EACH**

ULTRASONIC SWITCH KIT




Kit includes the Ultra Sonic Transducers, 2 PC Boards for transmitter and receiver. All electronic parts and instructions. Easy to build and a lot of uses such as remote control for TV, garage door, alarm system or counter. Unit operates by 9-12 DC. **\$15.50**

ELECTRONIC SWITCH KIT

CONDENSER TYPE Touch On Touch Off uses 7473 I.C. and 12V relay

\$5.50 each

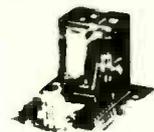

FORMULA INTERNATIONAL INC.

2/82

	SHIPPING AND HANDLING CHARGES	
	Under \$50.00 purchase	Over \$50.00 purchase
Inside California	10%	5%
Outside Calif. (includes Mexico & Canada)	15%	10%
Overseas	25%	20%

Minimum Order \$10.00/Calif. Residents Add 6% Sales Tax. Phone Orders Accepted on Visa or MC ONLY. NO C.O.D./Store Hours 10-7 Mon. thru Sat

12603 CRENSHAW BLVD., HAWTHORNE, CA 90250
PHONE: (213) 973-1921 • (213) 679-5162

Send \$1.00 For Detailed Catalogue






Components Express, Inc.

"Have you kissed your computer lately?"

1380 E. Edinger, Unit CC Santa Ana, CA 92705 (714) 558-3972

BROAD BAND MICROWAVE RECEIVER SYSTEM 1.8GHZ to 2.4 GHZ

only
\$295.

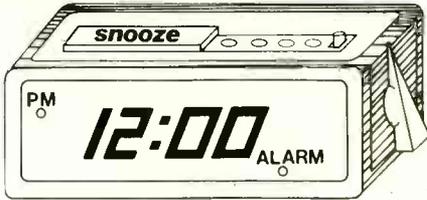

With built-in-converter to channel 2, 3, or 4 of any standard TV set.

- 24" Dish
- Feed-Horn Receiver
- Mounting Bracket
- Mounting Clamp
- Instructions
- 300 Ohm to 75 Ohm Adapter
- 750 Ohm to 300 Ohm Adapter
- 60 Feet Coax Cable with Connectors
- 3 Feet Coax Cable with Connectors

RANGE: Line of sight to 250 miles.
SCOPE: Will receive within the frequency band from satellites, primary microwave stations, and repeater microwave booster stations.


CONTENTS: Completely packaged in 19"x19"x4 1/2" corrugated carton complete with list.

WARRANTY: 180 days for all factory defects and electronic failures for normal useage and handling. Defective sub assemblies will be replaced with new or re-manufactured sub assembly on a 48 hour exchange guarantee.

This system is not a kit and requires no additional devices or equipment other than a TV set to place in operation.

Dealer inquiries invited

DON'T FORGET

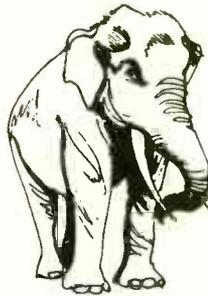

USE
YOUR
READER
SERVICE
CARD

ADD CURVE-PLOTTING to your ohmmeter (VOM, TVM, VTVM). Simple mod. Details \$3.50
HOCO LAB., PO Box 176, Waltham, MA 02254

30 tune melody microprocessor \$6.95 ea. 2 for \$6.50 ea. 6 for \$5.50 ea. Add \$1.50 shipping. Specs only. 50c. **SRJ INTERNATIONAL CORP.,** 1936 Hillman Ave., Belmont CA 94002




ELECTRONIC ORGAN KITS 3-4 Manuals

THEATER and CLASSICAL
Refundable Parts

Wurlitzer reproductions Brochure \$2.00 Catalog \$1.50
DEVTRONIX ORGANS, INC., Dept 60
6101 WAREHOUSE WAY, SACRAMENTO, CA 95826

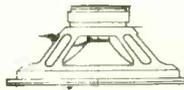BURGLAR alarm, home or auto. Optically sensed, no switches. Electronic police type siren. Schematic \$4.50. **THEIS ENTERPRISES,** 29 Ivy Ct., Maple Shade, NJ 08052



WRITE FOR McGEE'S

SPEAKER & ELECTRONICS CATALOG

1001 BARGAINS IN SPEAKERS

Tel.: 1 (816) 842 5092

1901 MCGEE STREET KANSAS CITY, MO. 64108

SUPER class-A: preamp, 120W power amp and many other high-power audio kits. Free flyer. Florida agent wanted. **AUDIOVISION,** 578 Marlee Ave., Toronto, Canada M6B 3J5

CABLE TV converters and equipment. Plans and parts. Build or buy. For information send \$2.00. **C & D ELECTRONICS,** PO Box 21, Jenison, MI 49428

39⁹⁵ ADD \$2.50 FOR POSTAGE

30 CHANNEL CABLE TV CONVERTER

FREE! UNUSUAL 96 PAGE ELECTRONIC PARTS & IDEAS CATALOG!

ORDER No. 171AE047
ROUTE 9N, PLATTSBURGH, N.Y. 12901
Tel.: (518) 561-8700.

CASSETTES/REEL-TO-REEL TAPES

OPEN reel tape—mostly Ampex, used once, unspliced, unboxed, 1800' 50 reels; \$65.00. Sample: \$2.00. 3600' 10 reels; \$25.00. Sample: \$2.50. New, premium C-60 cassettes; sample: \$1.00. **AUDIO TAPES,** BOX 9584-G, Alexandria, VA 22304

PROFESSIONAL MUSIC SYNTHESIZER PLANS

This manual contains complete plans and schematics for 5 professional synthesizers. Included are a polyphonic, monophonic, 2 voice duophonic, 4 voice duophonic and a bass synthesizer. Additional circuitry like glide, noise, LFD's, etc., is also included. Send \$15 to **SYN-TEX,** 702 117th Pl. SW, Everest, WA 98204

COMPUTER SOFTWARE

HP-41C software. Electronics, engineering, business applications. Free information. **SOFTWARE SPECIALISTS, INC.,** Dept. RE/1, Box 329, Springboro, OH 45066

SAMS SCHEMATICS

PHOTOFACTS for televisions. Complete set through number 1941 with 6 heavy-duty cabinets all in excellent condition. Only \$2,300.00 but hurry, they won't last long at this price. Call collect 503/389-4157



American Heart Association

WE'RE FIGHTING FOR YOUR LIFE

SAVE TIME AND MONEY!

6100

UNIVERSAL DESIGNER

- Easy transition from proto-type to wiring diagrams
- Aids digital circuit design
- Save on digital bread boarding

6100 Universal Designer \$59.95
1 0159S Breadboard 12.50
2 0159B @2.99 5.98
1 Jumper Wire Assl. 9.95
Kit \$49.95
Assembled \$59.95

SAVE \$10.43 ON COMPLETE DIGITAL DESIGN LAB NOW ONLY \$77.95

SELF-TEACHING AID:

6101 DIGITAL LOGIC COURSE \$29.95

Learn digital logic with 26 self teaching experiments.

0101 SOLID STATE CLOCK/CALENDAR UNIT

BIG 2 1/2" DISPLAY!

- 12/24 hour selectable
- Alarm output Kit \$49.95
Assembled \$79.95
Oak Case \$29.95



NEW! JUMPER WIRE DESIGN ASST.

Contains 350 wires cut to 14 different lengths, to fit breadboard modules. Pre-cut, pre-formed and individually color-coded. All wire solid tinned, 22 gauge with PVC insulation. Packed in convenient, sectioned box. \$9.95

Satisfaction Guaranteed on All Assembled Units



14803 N.E. 40th, RE022
Redmond, WA 98052

NAME _____
ADDRESS _____
CITY, ST., ZIP _____
CARD NO. _____ EXP. _____
SIGNATURE _____


FOR FAST DELIVERY CALL TOLL-FREE **1-800-426-1044** VISA MSTRCD

CIRCLE 80 ON FREE INFORMATION CARD

CB RADIO

GET more CB channels and range! Frequency expanders, boosters, speech processors, how-to books, plans, modifications. Catalog \$2. CB CITY, Box 31500RE, Phoenix, AZ 85046

MICRO-VIDEO II

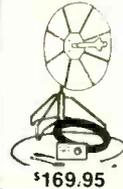

\$169.95

Cable T.V. Equipment In Stock

Complete Satellite Systems

- Micro-Wave T.V. System
- Precision Parabolic Antenna
- Advanced Down Converter
- Power Supply
- Low-Loss Coaxial Cables
- Complete - Ready To Install

Call Toll-Free 1 - 800 - 626-5533

SOUND & VIDEO RESEARCH

P.O. Box 19462
Louisville, KY 40219

LIVE VIA SATELLITE

- **DISH ANTENNA**
 - **PREAMPLIFIER** \$399
 - **RECEIVER**
- MDS COMPLETE RECEIVING SYSTEM

JUST PUBLISHED: 8 1/2 X 11 BOOK gives a wealth of updated information on
• Antennas • Low Noise Amplifiers • Sources • Receivers • Services • Equipment • Manufacturers • Much More.

Our book takes the mystery out of the sophisticated technology of satellite transmission and reception. This volume represents all the essential knowledge made easy to understand, and will show you how easy it is to have a 90 channel reception system so that you can enjoy: first run movies, foreign films, Las Vegas entertainment, live sports, and much more. Everything being telecast in the world could be yours at a twist of a knob!

LIVE VIA SATELLITE, INC.

P.O. Box 2561, Dept. RE-2 Delray Beach, FL 33444

Send \$9.95 plus \$2.50 shipping & handling or call our 24 hr. C.O.D. order line (305) 845-4447

Name _____
Address _____

7400

SN7400N	.20	SN7472N	.29	SN74156N	.75
SN7401N	.20	SN7473N	.35	SN74157N	.69
SN7402N	.25	SN7474N	.35	SN74160N	.69
SN7403N	.25	SN7475N	.40	SN74161N	.89
SN7404N	.25	SN7476N	.50	SN74283N	.89
SN7405N	.29	SN7477N	5.00	SN74163N	.89
SN7406N	.35	SN7478N	.50	SN74164N	.89
SN7407N	.35	SN7482N	.99	SN74165N	.89
SN7408N	.35	SN7483N	.69	SN74166N	.69
SN7409N	.29	SN7485N	.69	SN74167N	1.25
SN7410N	.25	SN7486N	.35	SN74170N	.15
SN7411N	.29	SN7489N	1.75	SN74172N	1.35
SN7412N	.29	SN7490N	4.99	SN74173N	4.99
SN7413N	.40	SN7491N	.99	SN74281N	.99
SN7414N	.29	SN7492N	.45	SN74175N	.89
SN7415N	.69	SN7493N	.45	SN74176N	.79
SN7417N	.29	SN7494N	.69	SN74177N	.79
SN7420N	.29	SN7495N	.69	SN74179N	1.49
SN7421N	.29	SN7496N	.69	SN74180N	.79
SN7422N	.45	SN7497N	1.00	SN74181N	2.26
SN7423N	.29	SN74100N	3.49	SN74182N	.79
SN7425N	.29	SN74104N	.89	SN74184N	2.49
SN7426N	.29	SN74105N	.89	SN74185N	2.49
SN7427N	.26	SN74107N	.26	SN74186N	.26
SN7428N	.49	SN74109N	.39	SN74191N	1.26
SN7430N	.25	SN74116N	.95	SN74192N	.89
SN7432N	.29	SN74121N	.39	SN74193N	.89
SN7433N	.25	SN74122N	.35	SN74194N	.89
SN7434N	.40	SN74123N	.59	SN74195N	.69
SN7439N	.25	SN74125N	.49	SN74196N	.89
SN7440N	.25	SN74126N	.49	SN74197N	.89
SN7441N	.29	SN74132N	.75	SN74198N	1.49
SN7442N	.59	SN74135N	.75	SN74199N	1.49
SN7443N	.10	SN74141N	.99	SN74221N	.99
SN7444N	.10	SN74142N	3.25	SN74251N	.99
SN7445N	.89	SN74143N	.49	SN74276N	1.95
SN7446N	.89	SN74144N	3.49	SN74279N	.99
SN7447N	.69	SN74145N	1.49	SN74280N	3.35
SN7448N	.79	SN74147N	1.95	SN74284N	.79
SN7449N	.20	SN74148N	1.29	SN74285N	.95
SN7450N	.20	SN74150N	1.26	SN74365N	.69
SN7451N	.20	SN74151N	.69	SN74366N	.69
SN7452N	.20	SN74152N	.69	SN74367N	.69
SN7453N	.20	SN74153N	.79	SN74368N	.69
SN7454N	.20	SN74154N	1.25	SN74390N	1.49
SN7455N	.20	SN74155N	.75	SN74393N	1.49

74LS

74LS00	.29	74LS192	1.15
74LS01	.29	74LS193	1.15
74LS02	.29	74LS194	1.15
74LS03	.29	74LS195	1.15
74LS04	.29	74LS196	1.15
74LS05	.29	74LS197	1.15
74LS06	.29	74LS198	1.15
74LS07	.29	74LS199	1.15
74LS08	.29	74LS200	1.15
74LS09	.29	74LS201	1.15
74LS10	.29	74LS202	1.15
74LS11	.29	74LS203	1.15
74LS12	.29	74LS204	1.15
74LS90	.29	74LS282	1.15

74S

74S00	.45	74S243	3.25
74S01	.45	74S244	3.25
74S02	.45	74S245	3.25
74S03	.45	74S246	3.25
74S04	.45	74S247	3.25
74S05	.45	74S248	3.25
74S06	.45	74S249	3.25
74S07	.45	74S250	3.25
74S08	.45	74S251	3.25
74S09	.45	74S252	3.25
74S10	.45	74S253	3.25
74S11	.45	74S254	3.25
74S12	.45	74S255	3.25
74S90	.45	74S333	3.25


CA-LINEAR

CA3010H	2.15	CA3089N	3.75
CA3011H	2.15	CA3090N	3.95
CA3023H	3.25	CA3130H	1.25
CA3035H	2.45	CA3140H	1.25
CA3039H	1.35	CA3160H	1.25
CA3066N	1.30	CA3011N	5.00
CA3099N	1.30	CA3082N	1.60
		CA3086N	.85
		CA3090N	3.50

CD-CMOS

CD4000	.39	CD4098	2.49
CD4001	.39	CD4099	.75
CD4002	.39	CD4506	.95
CD4003	.39	CD4507	.95
CD4004	1.19	CD4508	.95
CD4005	.39	CD4509	.95
CD4006	.39	CD4510	1.39
CD4007	.39	CD4511	1.39
CD4008	.39	CD4512	1.39
CD4009	.39	CD4513	1.39
CD4010	.39	CD4514	1.39
CD4011	.39	CD4515	1.39
CD4012	.39	CD4516	1.39
CD4013	.39	CD4517	1.39
CD4014	.39	CD4518	1.39
CD4015	.39	CD4519	1.39
CD4016	.39	CD4520	1.39
CD4017	.39	CD4521	1.39
CD4018	.39	CD4522	1.39
CD4019	.39	CD4523	1.39
CD4020	.39	CD4524	1.39
CD4021	.39	CD4525	1.39
CD4022	.39	CD4526	1.39
CD4023	.39	CD4527	1.39
CD4024	.39	CD4528	1.39
CD4025	.39	CD4529	1.39
CD4026	.39	CD4530	1.39
CD4027	.39	CD4531	1.39
CD4028	.39	CD4532	1.39
CD4029	.39	CD4533	1.39
CD4030	.39	CD4534	1.39</

National Semiconductor Clock Modules

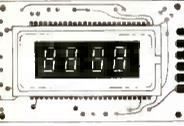

12VDC AUTOMOTIVE/ INSTRUMENT CLOCK

APPLICATIONS:

- In-dash autolocks
- After-market auto/ RV clocks
- Aircraft/marine clocks
- 12VDC Oper. Instru.
- Portable/battery powered instruments.

Features: Bright 0.3" green display. Internal crystal time base. ±0.5 sec./day accur. Auto. display brightness control logic. Display color filterable to blue, green, red & yellow. Complete—just add switches and lens.

MA1003 Module (3.05" L x 1.75" H x .98" D) \$16.95

CLOCK MODULES

MA1023	7" Red Digital LED Clock Module	8.95
MA1026	7" Dig. LED Alarm Clock/Thermometer	18.95
MA5035	3" Red Digital LED Clock/Timer	6.95
MA1002	5" Red Digital LED Clock & Xformer	9.95
MA1010	8" Red Digital LED Clock	7.95
MA1032	CBA 5" Digital LCD Clock	17.95
MA1043	7" Green Digital LED Clock	8.95

TRANSFORMERS

102-P20	Xformer for MA1023, 1043 & 5035 Mods.	3.49
102-P22	Xformer for MA1026 Clock Modules	3.49
102-P24	Xformer for MA1010 Clock Modules	3.49

Sun Power Your Electronics! SOLAR CELL PANEL KIT



Features:

- Output: 10VDC, to 100mA in Parallel 5VDC, to 200mA in Parallel Series or Parallel out
- Panel may be easily connected to Series or Parallel out
- Over 11 square inches of active cell surface
- Voltage line tap @ 0.5V increments
- Provision for charging batteries
- Overall panel size: 4 1/4" L x 4 1/4" H x 1/4" D

The JE305 Solar Cell Panel Kit contains 20 each solar cells. On the panel board are power line taps which allow the user to select voltages (one voltage at a time) from 0.5VDC to 10VDC. The applications of each panel can be further expanded by coupling additional panels in series for more voltage or in parallel for more current. The premium grade solar cells provide the current necessary for the operation of a portable transistor radios, small battery powered cassette tape players and unlimited experimental solar projects.

JE305 \$39.95

EPROM Erasing Lamp



Features:

- Erases 2708, 2716, 1702A, 52030, 52040, etc.
- Erases up to 4 chips within 20 minutes.
- Maintains constant exposure distance of one inch.
- Special conductive foam liner eliminates static build-up.
- Built-in safety lock to prevent UV exposure.
- Compact—only 7-5/8" x 2-7/8" x 2"
- Complete with holding tray for 4 chips.

UVS-11EL Replacement Bulb \$16.95

UVS-11E \$79.95

JOYSTICKS



JS-5K

JVC-40

JS-5K	5K Linear Taper Pots	\$5.25
JS-100K	100K Linear Taper Pots	\$4.95
JVC-40	40K (12) Video Controller in case	\$4.95


ALLIGATOR CLIP TEST LEADS



Heavy-duty leads, color coded. Insulated alligator clip on each end. 15" long. Two each black, red, blue, white and yellow.

#ALCP (10 per pack) \$2.95/pkg.

JE215 Adjustable Dual Power Supply

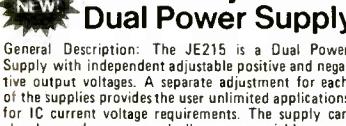

General Description: The JE215 is a Dual Power Supply with independent adjustable positive and negative output voltages. A separate adjustment for each of the supplies provides the user unlimited applications for IC current voltage requirements. The supply can also be used as a general all-purpose variable power supply.

FEATURES:

- Adjustable regulated power supplies, pos. and neg. 1.2VDC to 15VDC.
- Power Output (each supply): 5VDC @ 500mA, 10VDC @ 750mA, 12VDC @ 500mA, and 15VDC @ 175mA.
- Two, 3-terminal adj. IC regulators with thermal overload protection.
- Heat sink regulator cooling.
- LED "on" indicator.
- Printed Board Construction.
- 120VAC input.
- Size: 3-1/2" w x 5-1/16" L x 2" H

JE215 Adj. Dual Power Supply Kit (as shown) \$24.95
(Picture not shown but similar in construction to above)

JE200 Reg. Power Supply Kit (5VDC, 1 amp) \$14.95
JE205 Adapter Pwr. Kit (JE200) 5, 9 & 12V. \$12.95
JE210 Var. Pwr. Sply. Kit, 5-15VDC, to 1.5amp. \$19.95

MICROPROCESSOR COMPONENTS

8080A/8080A SUPPORT DEVICES

INS5808A	CPU	4.95
DR921A	8-Bit Input/Output	2.95
DR921A	Priority Interrupt Control	1.95
DR921B	BI-Directional Bus Driver	1.49
DR922A	Clock Generator/Driver	1.95
DR922B	Bus Driver	1.49
DR922C	System Controller/Bus Driver	4.95
OP923A	System Controller	1.95
INS5813A	Quad 8-Bit Serial 48 Series	9.95
INS5820	Asynchronous Count. Element	16.95
OP9251	Prog. Count. I/O (USART)	6.95
OP9253	Prog. Interval Timer	1.95
OP9255	Prog. Peripheral I/O (PPI)	5.95
DR9257	Prog. DMA Control	9.95
DR9259	Prog. Interrupt Control	1.95
DR9275	Prog. CRT Control	36.95
DR9279	Prog. Keyboard/Display Interface	9.95
OP9830	System Timing Element	4.95
DR9834	8-Bit BI-Directional Receiver	3.95
DR9837	8-Bit BI-Directional Receiver	3.95
DR9838	8-Bit BI-Directional Receiver	3.95
DR9839	8-Bit BI-Directional Receiver	3.95
DR9840	Octal Latched Peripheral Driver	5.95
DR9841	Octal Latched Peripheral Driver	5.95

6800/6800 SUPPORT DEVICES

MC6800	MPU	14.95
MC6802CP	MPU with Clock and RAM	14.95
MC6810AP	128K Static RAM	14.95
MC6821	Peripheral Inter. Adapt. (MC6820)	17.95
MC6822	Priority Interrupt Controller	17.95
MC6830L3	1024x8 Bit ROM (MC6830A)	14.95
MC6860	Asynchronous Count. Adapter	6.95
MC6862	Synchronous Serial Data Adapter	6.95
MC6860	4000bps Digital MODEM	10.55
MC6862	2400bps Modem	12.95
MC6860A	Quad 8-Bit Serial Trans. (MC6862)	11.95

MICROPROCESSOR CHIPS

Z80 (780C)	CPU (1MHz)	11.95
Z80A (780-1)	CPU (1MHz)	11.95
CP1802	CPU	18.95
MPU8	MPU	14.95
DM2001AD	CPU—4-Bit Slice (Com. Temp. Grade)	18.95
MC5600	MPU w/Clock (8K Bytes Memory)	11.95
INS5828A-4	MPU—8-Bit Dynamic	7.95
INS5828A-4	CPU—5.5K, Ch18 (128 Bytes RAM)	5.95
INS5828A-4	CPU (256 Bytes RAM)	24.95
INS5828N	CPU—4 Bytes RAM	2.95
INS5828N	CPU w/Basic Micro Interpreter	29.95
MPU85	MPU	14.95
TM5900-UL	MPU—16-Bit	39.95

SHIFT REGISTERS

MV580H	Dual 25-Bit Dynamic	50
MV580H	Dual 50-Bit Dynamic	50
MV580H	Dual 100-Bit Static	50
MV580H	Dual 64-Bit Accumulator	50
MV442N	25-Bit Dynamic	2.95
MV580JN	1024-Bit Dynamic/Accumulator	1.95
MV580JN	500/512-Bit Dynamic	1.95
MV580JN	Quad 8-Bit	9.95
MV580JN	Quad 16-Bit	9.95
250V (100A)	1024-Bit Dynamic	1.95
251R	Hex 32-Bit Static	2.95
252V	Dual 132-Bit Dynamic	3.95
253V	512-Bit Dynamic	3.95
254V	1024-Bit Dynamic	2.95
255V	Dual 256-Bit Static	4.00
256V	Dual 256-Bit Static	4.00
257V	Quad 260-Bit Static	4.00
258V	Quad 80-Bit Static	6.95
33APC	File (Dual 8)	6.95

DATA ACQUISITION

AF100-1CN	Universal Active Load Filter 2.5%	5.95
AF121-1CJ	Touch Tone Low Band Filter	19.95
AF121-1CJ	Touch Tone High Band Filter	19.95
LVX8CH	Super Gain Op Amp	1.15
LM33Z	Constant Current Source	1.30
LVX35Z	Temperature Transducer	1.40
JF150	JFET Op Amp	1.10
LF398N	Remote & Hold Amplifiers	3.50
LVX99H	Temp. Comp. Prec. Ref. (300mV)	5.00
ADAC001CN	8-Bit A/D Converter (1LSB)	4.95
ADAC001CN	8-Bit D/A Converter (0.78% Lin.)	2.25

JE608 Kit JE608A Assembled and Tested. \$399.95 \$499.95

JE608-16K ADAPTER BOARD FOR 2716/2758 EPROMS

GENERAL DESCRIPTION: The JE608-16K Adapter Board allows the JE608 Programmer to be modified for the additional programming of the 2716 and 2758 EPROMs. The adapter provides for adding an address switch for the 2716 and 2758 for selecting the proper power and timing pulses to be applied to the EPROM. Programming and erasing the 2716 (16K) EPROM is done separately to each half (1024x8) of the EPROM because of the existing 8K RAM capacity in the JE608 Programmer.

JE608-16K Adapter Board Kit \$29.95
JE608-Upgrade (Send assembled JE608 to factory for adapter installation) \$89.95
JE608A-16K Mod. Assembled JE608 w/Adapter (JE608-16K) Installed \$599.95

\$10.00 Min. Order—U.S. Funds Only
Calif. Residents Add 6% Sales Tax
Postage—Add \$5 plus \$1.50 Insurance

Spec Sheets—25¢
Send \$5 Postage for your FREE 1982 JAMECO CATALOG

aneco ELECTRONICS (415) 592-8097

MAIL ORDER ELECTRONICS—WORLDWIDE
1355 SHOREWAY ROAD, BELMONT, CA 94002
PRICES SUBJECT TO CHANGE

BOOKS

National Semiconductor—Interall—Intel

30001	National CMOS Data Book (540 pages) 74C, CD4000, and A/D Converters	\$6.95
30002	National Interface Data Book (742 pages) DP, DS8000, DS9000, DS75000, etc.	\$6.95
30003	National Linear Data Book (1376 pages) LM, LF, ADC, DAC, LH Series	\$6.95
30004	National Series 80—Board Level Computer (224 pages)	\$4.95
30005	National TTL Logic Data Book (624 pages) 7400 L, S, L, S, and DM8000 Series	\$8.95
30006	Buy above (3) 30001, 3, 5 as a set	\$19.95/lot
30009	Internal Data Book (1074 pages)	\$6.95
31040	Intel Component Data Catalog. Full data sheets for intel's products incl. memory devices, microproc., peripherals & input/ml. products (1328 pages)	\$7.50
205610	Intel Peripheral Design Handbook. Full data sheets, app. notes for Intel peripheral devices components (644 pages)	\$3.25

AC and DC Wall Transformers

With Universal Plug and 9V Battery Snap

Selective voltages: 6.9, 12VDC. polarity selection (+ & -) six-foot line from adapter to plugs—six inch line from adapter to battery snap, 120V/60Hz, 30mA.

Part No.	Input	Output	Price
AC 250	117V/60Hz	12VAC 250mA	\$3.95
AC 500	117V/60Hz	12VAC 500mA	\$4.95
AC 1000	117V/60Hz	12VAC 1 amp	\$5.95
AC 1700	117V/60Hz	9VAC 1.7 amp	\$3.95
DC6812	120V/60Hz	6.9, 12VDC 300mA	\$9.95
DV5200	117V/60Hz	5VDC 500mA	\$3.95
DC300	120V/60Hz	9VDC 500mA	\$3.95

CONNECTORS

DB25P	D-Subminiature Plug	\$2.95
DB25S	D-Subminiature Socket	\$3.50
D20418-2	Screen Lock Hdw. (2) DB25S/P	\$2.99
DB25122E	Cover for DB25P/S	\$1.75
22/44-26	P.C. Edge (22/44 Pin)	\$2.95
UG8/U	BNC Plug	\$1.79
UG8/U	BNC Jack	\$3.79
UG175/U	UHF Adapter	\$.49
SO239	UHF Panel Recp.	\$1.29
PL258	UHF Adapter	\$1.60
PL259	UHF Plug	\$1.60
UG260/U	BNC Plug	\$1.79
UG1094/U	BNC Bulkhead Recp.	\$1.29

TRS-80 16K Conversion Kit

Expand your 4K TRS-80 System to 16K.

Kit comes complete with:

- * 8 ea. MM5290 (UPD416/4116) 16K Dyn. Rams (*NS)
- * Documentation for Conversion

TRS-16K2	*150NS	\$29.95
TRS-16K3	*200NS	\$24.95
TRS-16K4	*250NS	\$19.95

JE610 ASCII Encoded Keyboard Kit



The JE610 ASCII Keyboard Kit can be interfaced into most any computer system. The kit comes complete with an industrial grade keyboard switch assembly (62-keys), IC's, sockets, connector, electronic components and a double-sided printed wiring board. The keyboard assembly requires: 45V @ 150mA and -12V @ 10 mA for operation. Features: 60 keys generate the 126 characters, upper and lower case ASCII set. Fully buffered. Two user-definable keys provided for custom applications. Caps lock for upper-case only alpha characters. Utilities a 2376 (40-pin) encoder read-only memory chip. Outputs directly compatible with TTL/DTL or MOS logic arrays. Easy interfacing with a 16-pin dip or 18-pin edge connector. Size: 3 1/2" H x 14 1/4" W x 8 3/4" D.

JE610/DTE-AK (After assembled) \$124.95

JE610 Kit	62-Key Keyboard, PC Board, & Components (no case)	\$ 79.95
K62	62-Key Keyboard (Keyboard only)	\$ 34.95
DTE-AK	(case only—3 1/2" H x 14 1/4" W x 8 3/4" D)	\$ 49.95

JE212—Negative 12VDC Adapter Board Kit for JE610 ASCII KEYBOARD KIT \$9.95
Provides -12VDC from incoming 5VDC

JE600 Hexadecimal Encoder Kit



The JE600 Encoder Keyboard Kit provides two separate hexadecimal digits produced from sequential key entries to allow direct programming for 8-bit microprocessor or 8-bit microcontroller. Three additional keys are provided for user operations with one having a bistable output available. The outputs are latched and monitored with 3 LED readouts. Also included is a key entry strobe. Features: Full 8-bit latched output for microprocessor use. Three user-definable keys with one being bistable operation. Debounce circuit provided for all 19 keys. 9 LED readouts to verify entries. Easy interfacing with standard 16-pin edge connector. Size: 3 1/2" H x 16 1/2" W x 1 1/2" D.


JE600/DTE-HK (After assembled as pictured above) \$99.95

JE600 Kit—19-Key Hexadec. Keyboard, PC Board & Cmpnts. (no case) \$59.95
K19—19-Key Keyboard (Keyboard only) \$14.95
DTE-HK (case only—3 1/2" H x 16 1/2" W x 1 1/2" D) \$44.95

BULLET ELECTRONICS

P.O. BOX 401244R
GARLAND, TX. 75040
(214) 278-3553

Sound Effects Kit \$18.50

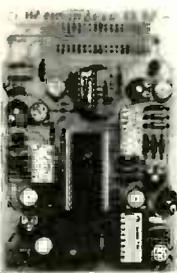

The SE-01 is a complete kit that contains all the parts to build a programmable sound effects generator. Designed around the new Texas Instruments SN76477 Sound Chip, the board provides banks of MINI DIP switches and pots to program the various combinations of the SLF Oscillator, VCO, Noise, One Shot, and Envelope Controls. A Quad Op Amp IC is used to implement an Adjustable Pulse Generator, Level Comparator and Multiplex Oscillator for even more versatility. The 3 1/2" x 5" PC Board features a prototype area to allow for user added circuitry. Easily programmed to duplicate Explosions, Phasor Guns, Steam Trains, or almost an infinite number of other sounds. The unit has a multiple of applications. The low price includes all parts, assembly manual, programming charts, and detailed 76477 chip specifications. It runs on a 9V battery (not included). On board 100mW amp will drive a small speaker directly, or the unit can be connected to your stereo with microphone quality. (Speaker not included). 76477 is included. Available separately for \$3.15 each.

7 Watt Audio Amp Kit \$6.95

SMALL, SINGLE HYBRID IC AND COMPONENTS FIT ON A 2" x 3" PC BOARD (INCLUDED). RUNS ON 12VDC. GREAT FOR ANY PROJECT THAT NEEDS AN INEXPENSIVE AMP. LESS THAN 3% THD @ 5 WATTS. COMPATIBLE WITH SE-01 SOUND KIT.

Doomsday Alarm Kit \$9.95

If you have trouble sleeping and you would like the rest of the neighborhood to share your misery then this little kit will be for you! There is no way to accurately describe the unearthly howls, screams and tones that come out of this kit. Four separate tone oscillators are mixed, cancelled and stepped at a varying rate. 10 Watts of crazy sounds. A great fun kit or a practical burglar alarm. Complete with PC board and all necessary components less speaker. For 6-12 VDC. ORDER DA-02.

New! 3TZ Time Zone Clock Kit

Microprocessor/ROM clock kit keeps local time (12 hour format), and 2 world time zones (24 hour format). Large 6" ORANGE readouts 10 min. ID timer for HAMS. Comes complete with attractive plastic case and wallplug XFMR.

- 6 Digit (hrs., min., sec.)
- Quartz XTAL Timebase
- Battery backup
- 3 Time Zones (Selectable)
- Feathertouch front panel switches
- Quality solder masked and plated PC boards
- Seconds Reset/Hold feature

\$54.40

SEE SPECIAL WINTER PRICES BELOW

The Super Music Maker REVISION 2 \$24.95 (Basic Kit)

Does not include speaker switches or 2708 ROM.

Now you can play hundreds of songs using the Bullet Super Music Maker. The unit features a single factory programmed microprocessor IC that comes with 20 pre-programmed short tunes. By adding the additional PROMS (2708s) the system can be expanded to play up to 1000 notes per PROM. Just think... a compact electronic instrument that will play dozens, hundreds or even thousands of selections of music. The kit comes with all electronic components (less the PROM), and a drilled, plated and screened PC Board which measures 4" x 4 1/2". The 7 watt amplifier section is on the same PC board and drives an 8 ohm speaker (not included), from a whisper to ear splitting volume. Since the unit works on 12 VDC or 12 VAC, vehicle or portable operation is possible. What do you get for \$24.95? Everything but a speaker, transformer, case, switches, and PROM. Additional 2708 albums containing popular tunes are available for \$9.95 each or you can program your own PROMS using information provided with the kit instructions. Lists of available PROM albums are available on request. (Note: Unit plays electronic music one note at a time, it is not possible to play chords or a melody with harmony simultaneously.)

* Envelope control gives decay to notes.
* On board inverter allows single voltage (+12) operation.

OPTIONAL ACCESSORIES
DIP Switches (One 8 pos., One 5 pos.) 2.00/set
(Can be directly soldered to PC Bd. to access tunes)
Rotary Switches Two 5 position 2.50/set
(For remote wiring to PC Bd. to access tunes)
Attractive Tan Plastic Case 6.50
Wallplug Transformer 3.00
(For operation on 117VAC house voltage)

SPECIAL WINTER PRICES
1. Super Music Maker with case and two 5-position rotary switches \$32.00
2. Super Music with one 2716 2K X 8 PROM filled with over 50 selections of additional music (1500 notes) \$32.00
3. The Whole Ball of Wax! #2 + case and switches \$39.95

ORDERING INFORMATION: Call or Write For Free Catalog

• COD MINIMUM \$20.00 • ADD \$2.50 FOR COD'S
• UPS DELIVERY ADDRESS MUST ACCOMPANY ALL COD ORDERS
• \$1.00 HANDLING ON ORDERS UNDER \$10.00
• VISA, MC CARDS OK CHECK
• ADD 9% FOR SHIPPING CHARGES
• TEXAS RESIDENTS ADD 5% STATE SALES TAX
• ALL FOREIGN ORDERS ADD 25% FOR SHIPPING (CANADA 15%) NO FOREIGN COD'S
• CALL (214) 278-3553 TO PLACE CREDIT CARD OR COD ORDER

ELECTRONIC KITS FROM HAL-TRONIX

2304 MHZ DOWN CONVERTERS. TUNES IN ON CHANNELS 2 TO 7 ON YOUR OWN HOME T.V. HAS FREQUENCY RANGE FROM 2000 MHZ TO 2600 MHZ. EASY TO CONSTRUCT AND COMES COMPLETE WITH ALL PARTS INCLUDING A DIE-CAST ALUM CASE AND COAX FITTINGS, REQUIRE A VARIABLE POWER SUPPLY AND ANTENNA (Antenna can be a dish type or coffee can type depending on the signal strength in your area.)

- 2304 MOD 1 (Basic Kit) \$49.95
(Less case & fittings)
 - 2304 MOD 2 (Basic / Pre-amp) \$59.95
(Includes case & fittings)
 - 2304 MOD 3 (Hi-Gain Pre-amp) \$69.95
(Includes case & fittings)
- POWER SUPPLY FOR EITHER MODEL ABOVE IS AVAILABLE. COMES COMPLETE WITH ALL PARTS, CASE, TRANSFORMER, ANTENNA SWITCH AND CONNECTORS (Kit) \$24.95
Assembled \$34.95
Slotted Microwave Antenna For Above Downverters \$39.95

PREAMPLIFIERS

HAL PA-19—1.5 mhz to 150 mhz. 19db gain operates on 8 to 18 volts at 10ma. Complete unit \$8.95.
HAL PA-1.4—3 mhz to 1.4 ghz. 10 to 12 db gain operates on 8 to 18 volts at 10ma. Complete unit \$12.95.
(The above units are ideal for receivers, counters, etc.)

- 16 LINE TOUCH TONE DECODER KIT WITH P.C. BOARD AND PARTS\$69.95
- 12 LINE TOUCH TONE DECODER KIT WITH P.C. BOARD AND PARTS\$39.95
- 16 LINE ENCODER KIT, COMPLETE WITH CASE, PAD AND COMPONENTS\$39.95
- 12 LINE ENCODER KIT, COMPLETE WITH CASE, PAD AND COMPONENTS\$29.95

MANY, MANY OTHER KITS AVAILABLE

Send 20 cents stamp or S.A.S.E. for information and flyer on other HAL-TRONIX products. To order by phone: 1-313-286-1782.



HAL-TRONIX
P.O. Box 1101
Southgate, MI 48195

SHIPPING INFORMATION: ORDERS OVER \$25.00 WILL BE SHIPPED POSTPAID EXCEPT ON TEXAS ORDERS. ADDITIONAL CHARGES ARE REQUIRED ON ORDERS LESS THAN \$25.00 PLEASE INCLUDE ADDITIONAL \$2.00 FOR HANDLING AND MAILING CHARGES.


FUJITECH AUDIO KITS

LATEST AUDIO TECHNOLOGY FROM JAPAN

Model A501 Power Amp

- Pure Class A 25W + 25W
- Switchable to Class AB 100W + 100W
- Switchable to Bridge Class A 100W mono
- Switchable to Bridge Class AB 300W mono
- Frequency Response 5-200KHz (-1dB)
- Signal-to-Noise Ratio 120dB
- Non-magnetic Chassis
- "Out-board" comprehensive protection circuitry
- DC circuitry with limited use of NFB
- High Efficiency Fluid Convection Cooling
- THD under 0.007%

**KIT ONLY
\$299.00**

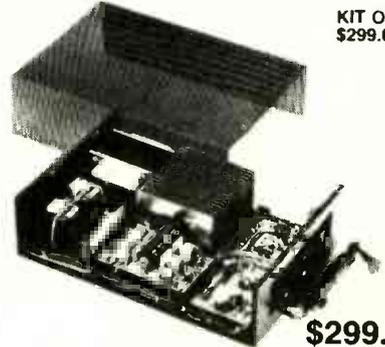

\$299.00

Model A502 DC Stereo Control Center

- Direct DC coupling from Input to Output
- DC servo circuitry
- Cascade FET Input in all stages
- Separate Moving Coil RIAA amplifier
- Distortion below 0.005% (3V)
- Max Output 15V
- Frequency Response 20Hz-20KHz ±0.2 dB
- Maximum Phono Input
MC = 16mv RMS (1KHz)
MM = 270mv RMS (1KHz)
- Built-in Headphone amplifier
- Relay Output Muting

**KIT ONLY
\$349.00**



\$349.00

Model A1033 Integrated Tube Amplifier

- Latest Japanese Design
- Distortionless Output Transformer using special winding techniques
- Most circuitry on PCB for easy assembly and humfree performance
- Output 30W x 2 Ultra Linear (Switchable to Triode)
15W x 2 Triode Output (near class A performance)
- THD under 0.4%
- Frequency Response 30~30,000 Hz (-1dB)
- Separate Pre-Out and Main-In

**KIT ONLY
\$499.00**



\$499.00

Send \$5.00 for each assembly manual, refundable with order.

Monarchy Engineering, Inc.
380 Swift Avenue, Unit 21
South San Francisco, CA 94080

Visa or Mastercharge acceptable.

Special

2SC1308K 2SC1308K 2SC1308K

POPULAR HORIZONTAL OUTPUT TRANSISTOR

\$260
(10-99)



\$229
(100-up)

1500V 7A 50W—This original Sanyo transistor replaces most horizontal outputs in the market today.

ERS

Exact Replacement Semiconductors. Now for a limited time you can take advantage of quality replacement semiconductors at a special introductory price. Sale ends April 1, 1982. Minimum order 10 pieces.

ERS 123A **28¢**

ERS 154 **\$1²⁹**

ERS 238 **\$3⁴⁰**

ERS 128 **95¢**

ERS 162 **\$3⁹⁰**

ERS 283 **\$3⁹⁰**

ERS 129 **90¢**

ERS 163A **\$3⁹⁰**

ERS 712 **\$1⁵⁰**

ERS 165 **\$2⁴⁰**

ERS

The Professionals Choice. Why pay more for others when you can get **QUALITY** replacement semiconductors **DIRECTLY** from MCM? Each ERS semiconductor is backed by a **TWO** year warranty.

mcm distributes ERS semiconductors as well as thousands of electronic parts you use everyday—at

- prices that are too low to pass up. Japanese and American semiconductor listings by the hundreds!
- CATV Supplies
- Chemicals and solvents for the technician
- Replacement and original speakers for hi-fi and musical instrument reproduction
- Ceramic and magnetic replacement cartridges
- Connectors
- High Voltage Triplers
- Test Equipment
- Video and Audio Replacement Heads.



Call MCM toll-free to place your order and ask for our latest catalog.

CALL OUR TOLL-FREE LINES TODAY FOR IMMEDIATE DELIVERY!

1-800-762-4315
Ohio Watts Line

mcm
ELECTRONIC PARTS

1-800-543-4330
National Watts Line

858 Congress Park Drive, Centerville, Ohio 45459
Business Office 1-513-434-0031

CIRCLE 52 ON FREE INFORMATION CARD

FEBRUARY 1982

121

VIDEO

36 Channel Up Converter for TV & VTR

1-3 pieces
\$29.95 ea.

4 pieces & up
\$24.95 ea.

Model V5736



- Allows complete programming of VTR
- Watch or record any combination of standard or Pay-TV programs
- Receives Midband and Superband channels on UHF
- For Beta/VHS type recorders

BRUCE 37-Channel Wireless Remote Control TV Tuner

1-5 pcs.
\$109.95 ea.

6 pcs. & up
\$99.95 ea.

Reg. \$199.95



- For all channels; for all TVs
- Red LED channel readout 1-99
- Master power switch and fine tune controls on remote
- Easy to install
- Scan channels up and down

TEKNIKA Wireless Remote Control TV Tuner

\$109.95 ea.

Reg. \$169.95

Model 6301




- Easy to install; just 4 wires
- Electronic channel selection and indication. VHF: 2-12, UHF: 14-83,
- Ultra-Infrared Beam Control
- Master power switch

Video Control Center

Model VTS-157

\$59.95

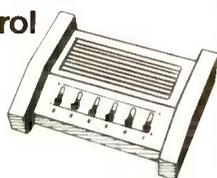

- No need to change cable to access input to TV set.
- One output; 4 inputs
- No AC power required to operate.
- Auxillary input and output.

CATV 30-Channel Remote Control

Model RSC-8C

\$79.95

Consists of 2 units: remote control channel selector with fine tuning, ON/OFF switch, and converter body.

TV Accessories

7002 2 Set VHF/FM Amplifier \$ 9.95 ea.
7004 4 Set VHF/FM Amplifier \$ 12.95 ea.

Coax Accessories

DCS-A/B CATV/MATV Switch \$9.00 ea.

FORDHAM

855 Conklin St. Farmingdale, N.Y. 11735

- Master Charge
- BankAmericard
- VISA = COD
- Money Order
- Check

N.Y. State residents add appropriate sales tax. Minimum order \$25 plus \$4.50 shipping and handling.

TOLL FREE (800)645-9518

in N.Y. State call (516) 752-0050

AMAZING DEVICES

PHASORS/SHOCK WAVE

PPF-1. PHASOR PAIN FIELD — Is being tested by Gov't for riot control. Soon to come under weapons restrictions as an internal machine. Easily hand-held. Hazardous — Use with discretion. SOLD ONLY FOR ANIMAL CONTROL.

PPF-1 PLANS \$15.00

IPG-3. INVISIBLE PAIN FIELD GENERATOR — Produces directional field of moderately intense pain to lower back of head up to 50 ft. Cigarette pack sized enclosure is easily hidden.

IPG-3 PLANS \$7.00 IPG-3K KIT \$39.50

IPG-30 ASSEMBLED FOR ANIMAL CONTROL \$49.50

HUG-1. HIGH POWERED ULTRASONIC GUN — Produces directional 130 db's of sound pressure energy at 20-24 kHz. Hand-held, intended for lab use.

HUG-1 PLANS \$10.00

LASERS

PARTICLE BEAM WEAPON PLANS \$15.00

LHP-2. BEGINNER VISIBLE RED NON-HAZARDOUS OPTICAL DEVICE. Adjustable pulse

LHP-2 PLANS \$7.00 LHP-2K KIT \$39.50

LP-3/LRG-3. LASER PISTOL AND RIFLE COMBINATION — 7-24 watts of infrared energy

LP-3/LRG-3 PLANS \$10.00

LGU-1. VISIBLE RED LASER GUN for holography, special effects, cloud writing, etc.

LGU-1 PLANS \$10.00

LC-1. BURNING/CUTTING CO2 LASER — 10-40 watts continuous.

LC-1 PLANS \$15.00

RUB-1. WELDING/DRILLING RUBYIYAG LASER, intense red.

RUB-1 PLANS \$15.00

HPS-1. HIGH POWERED PORTABLE ENERGY SOURCE FOR LASERS & MAGNETIC WEAPONS exploding wires, shock waves, etc.

HPS-1 PLANS \$8.00 HPS-1K KIT \$49.50

SECURITY/PERSONAL PROTECTION

INF-1. INFINITY TRANSMITTER — Uses telephone lines for selective home or office listening while away on business or vacation.

INF-1 PLANS \$15.00

SD-4. SEE IN THE DARK — Device, long range.

SD-4 PLANS \$10.00

VWPM-5. WIRELESS TELEPHONE TRANSMITTER — Long range.

VWPM-5 PLANS \$10.00 VWPM-5K KIT \$34.50

FBT-7. WIRELESS MICROPHONE — Extended range.

FBT-7 PLANS \$7.00 FBT-7K KIT \$34.50

HOD-1/TT-6. ELECTRONIC TRACKING AND HOMING DEVICE —

HOD-1/TT-6 PLANS \$6.00 HOD-1K/TT-6K KIT \$39.50

TAT-2. TALK AND TELL — Device records telephone when in use.

TAT-2 PLANS \$5.00 TAT-2K KIT \$14.50

PSW-3. PHASOR STUN WAND — Produces energy capable of burning flesh. Intended as a last resort personal defense weapon.

PSW-3 PLANS \$8.00 PSW-3K KIT \$59.50

Send for free catalog descriptions of above items, kits and parts, plus hundreds more. We accept, Master Charge and VISA or when ordering send check or money order for.

SCIENTIFIC SYSTEMS

DEPT. R8 BOX 716, AMHERST N.H. 03031

CIRCLE 77 ON FREE INFORMATION CARD

ELECTRONIC COMPONENTS



128 PAGE
FREE CATALOG

MANUFACTURERS OF QUALITY ELECTRONIC COMPONENTS

- Battery Clips & Holders
- Cable Sets Connectors Capacitors
- Displays, LED Fuses Jacks & Plugs
- Knobs Lamps Potentiometers
- RF Coils Relays Resistors
- Switches Semiconductors Speakers
- Test Equipment Transformers Tools
- Wire & Cable

WE STOCK What We Catalog!

- Sales and Order Desk
- Phone and Mail Orders Welcome
- Open from 6:00a.m.(PST)
- Over 10,000 Different Items in Stock
- TERMS: C.O.D., Visa, MasterCard
- (Open Accounts Available)

MOUSER ELECTRONICS

11433 WOODSIDE AVE., SANTEE, CA 92071
PHONE: (714)449-2222 T*X: 910-331-1175

CIRCLE 78 ON FREE INFORMATION CARD

SIMPLE SIMON ELECTRONIC KITS, Inc.


7 + 11 SWD PARTS KITS

MITSUMI VARACTOR UHF TUNER

Model UES-A56F

\$34.95

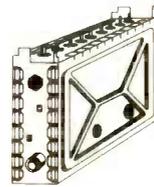Freq Range UHF470 - 889MHz
Antenna Input 75 ohms
Channels 14-83 Output Channel 3



KIT NO	PART NO	DESCRIPTION	PRICE
1	V71-SW	Varactor UHF Tuner, Model UES-A56F	\$34.95
2	CB1-SW	Printed Circuit Board, Pre-Drilled	18.95
3	TP7-SW	P.C.B. Potentiometers, 1-20K, 1-1K, and 5-10K ohms, 7-pieces	5.95
4	FR35-SW	Resistor Kit, 1/4 Watt, 5% Carbon Film, 32-pieces	5.95
5	PT1-SW	Power Transformer, PRI-117VAC, SEC-24VAC, 250ma	6.95
6	PP2-SW	Panel Mount Potentiometers and Knobs, 1-1KBT and 1-5KAT w/Switch	5.95
7	SS14-SW	IC's 7-pcs, Diodes 4-pcs, Regulators 2-pcs Heat Sink 1-piece	29.95
8	CE9-SW	Electrolytic Capacitor Kit, 9-pieces	5.95
9	CC33-SW	Ceramic Disk Capacitor Kit, 50 W.V., 33-pieces	7.95
10	CT-SW	Variable Ceramic Trimmer Capacitor Kit, 5-85pfd, 6-pieces	5.95
11	L4-SW	Coil Kit, 18mhs 2-pieces, 22µhs 1-piece (prewound inductors) and 1 T37-12 Ferrite Torroid Core with 3 ft. of #26 wire	5.00
12	ICS-SW	I.C. Sockets, Tin Inlay, 8-pin 5-pieces and 14-pin 2-pieces	1.95
13	SR-SW	Speaker, 4x6" Oval and Prepunched Wood Enclosure	14.95
14	MISC-SW	Misc. Parts Kit Includes Hardware, (6/32, 8/32 Nuts, & Bolts), Hookup Wire, Ant. Terms, DPDT Ant. Switch, Fuse, Fuseholder, etc.	9.95
When Ordering All Items, (1 thru 14), Total Price			139.95

UHF ANTENNAS and ACCESSORIES

ZYZZX


VHF-UHF WIDEBAND

ANTENNA AMPLIFIER

MODEL ALL-1

50 MHz — 900 MHz
12 dB GAIN ± 0.5db

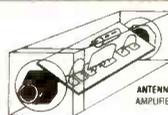A Revolutionary New One Stage HYBRID IC Broadband Amplifier



This unit is not available anywhere else in the world. One unit serves many purposes and is available in Kit or Assembled form. Ideal for outdoor or indoor use. Input-output impedance is 75 ohms. Amplifier includes separate co-ax feed power supply. Easily assembled in 25 minutes. No coils, capacitors etc. to tune or adjust.

ALL-1 Complete Kit plus Power Supply \$24.95

ALL-1 Assembled / Tested plus Power Supply \$34.95

INTRODUCING OUR NEW 14 ELEMENT — 14.5 dB GAIN YAGI ANTENNA



STVA-3 Yagi Antenna, 14.5 db, 75 ohm, Chan. 60-68 . . . \$19.95

STVA-4 Yagi Antenna, 14.5 db, 75 ohm, Chan. 44-52 . . . \$19.95



STVA-1 Yagi Antenna, 11.5 db, 75 ohm, Chan. 42-54 . . . \$9.95

STVA-2 Yagi Antenna, 11.5 db, 75 ohm, Chan. 20-28 . . . \$9.95

- RG-59/U 75 ohm Low Loss Coax Cable . . . \$.12 p/ft
- F-59 Coaxial Connectors, ea.39
- MT-1 Special UHF 75-300 ohm Matching Transformer, ea. 1.45
- ALL-1 HYBRID IC Wideband VHF-UHF-FM Antenna Amplifier Kit . . . 24.95
- ALL-1 HYBRID IC Wideband VHF-UHF-FM Ant. Amp. Assembled . . . 34.95

Mail Order Only — Send Check or Money Order To:

SIMPLE SIMON ELECTRONIC KITS

Calif. Orders:

3871 S. Valley View, Suite 12, Las Vegas, Nevada 89103

Tel: (702) 322-5273

All Other Orders:

11850 S. Hawthorne Blvd., Hawthorne, Calif. 90250

Tel: (213) 675-3347

Minimum Order: \$19.95. Add 10% Shipping and Handling.

For Orders over \$40.00, Add 5% Catalog \$1.00.

— VISA and Mastercard Acceptable —

TTL

7400	2/.85	7490	.85
7402	2/.85	7493	.85
7404	2/.85	74100	2.25
7406	2/1.19	74109	2/1.19
7407	2/1.19	74121	.69
7408	2/.89	74123	.99
7410	2/.85	74150	1.95
7414	.99	74154	1.95
7417	2/1.10	74157	.99
7420	2/.85	74161	1.19
7447	1.19	74164	1.59
7474	.69	74174	1.59
7475	.79	74175	1.49
7476	.69	74192	1.19
7485	1.19	74193	1.19
7486	2/1.19	74367	.99
7489	2.99	74393	1.95

POTENTIOMETERS



2 Watt @ 70°C
7/8" Slotted Shaft
Linear Taper
1K, 5K, 10K, 25K, 50K,
100K, 1 Meg
CMU\$2.95



3/4 Watt @ 70°C
15 Turn Pot.
Linear Taper
100 Ohm, 500 Ohm,
1K, 5K, 10K, 50K,
100K, 500K, 1Meg
830P\$1.79

5-WAY DC VOLTAGE ADAPTER

With Universal Plug & 9V Battery Snap
Selective voltage: 6.9, 12VDC.
Pol. selection (+/-). 6' line — adapter to plugs. 6' line — adapter to batt. snap.
120V/60Hz, 300mA.
DC6912\$9.95



CMOS

4000	.55	4030	.75
4001	.55	4040	1.79
4002	.59	4044	1.39
4006	1.49	4046	1.95
4009	.79	4047	2.75
4010	.79	4049	.79
4011	.55	4050	.89
4013	.79	4051	1.59
4016	.79	4066	.95
4017	1.39	4069	.69
4018	1.39	4070	.75
4020	1.39	4071	.69
4023	.49	4081	.59
4024	1.19	4093	1.19
4027	.79	4511	1.95

CONNECTORS



DB25P	D-Subminiature Plug	3.95
DB25S	D-Subminiature Socket	4.95
DB51226	Cover for DB25P/S	2.25
22/45E	P.C. Edge	2.95
UG88/U	BNC Plug	2.19
UG89/U	BNC Jack	3.95
UG175/U	UHF Adapter	.59
SO239	UHF Panel Recp.	1.49
PL258	UHF Adapter	1.95
PL259	UHF Plug	1.95
UG260/U	BNC Plug	2.39
UG1094/U	BNC Bulkhead Recp.	1.49

LINEAR

LM301N	.59	LM7805T	1.75
LM305H	1.39	LM7812T	1.75
LM307N	.75	LM7815T	1.75
LM308N	1.19	LM380N	1.49
LM309K	2.25	LM384N	2.49
LM310N	2.69	LM555N	.69
LM311N	1.49	LM556N	1.49
LM317T	2.29	LM565N	1.95
LM318N	2.95	LM566N	1.95
LM319N	2.95	LM567N	1.79
LM320K-5	2.25	LM723N	.79
LM7905T	1.75	LM741N	.65
LM7912T	1.75	LM1310N	2.95
LM7915T	1.75	LM1458N	.99
LM323K	5.95	LM1488N	1.59
LM324N	1.29	LM1489N	1.59
LM337T	2.29	LM1800N	4.49
LM339N	1.29	76477N	3.95

Phone Tunes

REPLACES THE TELEPHONE RINGER BELL WITH A SELECTION OF 30 FAMILIAR TUNES




PT030 Phone Tunes\$49.95
AD30 AC Adapter\$8.95

FEATURES
Replaces monotonous telephone ringer bell. Easily connects to any standard phone. Use alongside regular phone or replace remote ringer elsewhere in building or outside. FCC approved. Use on any phone system — worldwide. Use different tune to identify extension phones. Microprocessor controlled. Adjust. vol. control and variable tune speed control. Operates on 2-9V batteries or AC Adapter (not incl.).

JE215 Adjustable Dual Power Supply

General Description: The JE215 is a Dual Power Supply with independent adjustable positive and negative output voltages. A separate adjustment for each of the supplies provides the user unlimited applications for IC current voltage requirements. The supply can also be used as a general all-purpose variable power supply.

FEATURES:

- Adjustable regulated power supplies, pos. and neg. 1.2VDC to 15VDC.
- Power Output (each supply): 5VDC @ 500mA, 10VDC @ 750mA, 12VDC @ 500mA, and 15VDC @ 175mA.
- Two, 3-terminal adj. IC regulators with thermal overload protection.
- Heat sink regulator cooling
- LED "on" indicator
- Printed Board Construction
- 120VAC input
- Size: 3-1/2" w x 5-1/16" L x 2" H



JE215 Adj. Dual Power Supply Kit (as shown) . . . \$24.95
(Picture not shown but similar in construction to above)
JE200 Reg. Power Supply Kit (5VDC, 1 amp) . . . \$14.95
JE205 Adapter Brd. (to JE200) ±5, ±9 & ±12V. . . . \$12.95
JE210 Var. Pwr. Sply. Kit, 5-15VDC, to 1.5amp. . . . \$19.95

DESK TOP ENCLOSURES



DTE-8 (Pictured)\$31.95
DTE-11 (Pictured)34.95
DTE-14 (Pictured)36.95
DTE-HK (Case for JE600)47.95
DTE-AK (Case for JE610)52.95

Sun Power Your Electronics!

SOLAR CELL PANEL KIT

Output: 10VDC, to 100mA in Series 5VDC, to 200mA in Parallel

- Panel may be easily connected for Series or Parallel out
- Over 11 square inches of active cell surface
- Voltage line tap @ 0.5V increments
- Provision for charging batteries
- Overall panel size: 4 3/4" L x 4 1/2" H x 1/2" D

The JE305 Solar Cell Panel Kit contains 20 ea. solar cells. On the panel board are power line taps which allow the user to select voltages (1 voltage at a time) from 0.5VDC to 10VDC. The applications of each panel can be further expanded by coupling additional panels in series for more voltage or in parallel for more current. The premium grade solar cells provide the current necessary for the operation of most portable transistor radios, small battery powered cassette tape players & unlimited experimental solar projects.

JE305\$39.95

LS Schottky

74LS00	.55	74LS109	.75
74LS02	.55	74LS123	1.49
74LS04	.69	74LS138	1.29
74LS08	.55	74LS139	1.29
74LS10	.55	74LS154	1.95
74LS14	1.09	74LS157	1.19
74LS30	.55	74LS161	1.29
74LS32	.69	74LS174	1.19
74LS38	.69	74LS175	1.19
74LS42	1.29	74LS192	1.49
74LS47	1.29	74LS193	1.49
74LS48	1.79	74LS221	1.49
74LS73	.75	74LS244	1.89
74LS74	.69	74LS245	3.49
74LS75	.75	74LS367	.89
74LS85	1.49	74LS374	1.95
74LS90	.89	81LS97A	2.29

SOCKETS

Low Profile		Wire Wrap	
8 pin LP	2/.59	14 pin WW tin	.75
14 pin LP	2/.69	14 pin WW gold	1.09
16 pin LP	2/.79	16 pin WW tin	.79
18 pin LP	2/.89	16 pin WW gold	1.19
20 pin LP	2/.99	24 pin WW gold	1.69
22 pin LP	2/1.09	40 pin WW gold	2.75
24 pin LP	.79	14 p. plug/cover	1.29
28 pin LP	.82	16 p. plug/cover	1.39
36 pin LP	.99	24 p. plug/cover	1.95
40 pin LP	1.19	Also, The Molex Line	

DIODES & TRANSISTORS

IN751	2/.59	2N2219A	2/1.19
IN757	2/.59	2N2222A	2/.89
IN1188	2.69	2N2907A	2/.89
IN3600	5/.99	2N3055	.99
IN4001	4/.59	2N3772	2.25
IN4004	4/.69	2N3904	2/.69
IN4007	4/.79	2N3906	2/.69
IN4148	10/.99	2N4401	2/.79
IN4733	2/.69	2N4403	2/.79
IN4734	2/.69	2N5129	2/.69
IN4735	2/.69	2N5139	2/.69
IN4742	2/.69	2N5210	2/.79
IN4744	2/.69	2N5951	2/1.29

CAPACITORS

Dipped Tantalum		ELECTROLYTIC	
.1mf @ 35V	2/.89	1mf @ 50V	3/.69
.47mf @ 35V	2/.89	4.7mf @ 50V	2/.59
1mf @ 35V	2/.89	10mf @ 50V	2/.69
2.2mf @ 25V	2/1.09	22mf @ 50V	2/.79
3.3mf @ 25V	2/1.19	47mf @ 50V	2/.89
4.7mf @ 25V	2/1.39	100mf @ 50V	.59
10mf @ 25V	1.19	220mf @ 50V	.69
33mf @ 25V	3.95	1000mf @ 25V	1.19
		2200mf @ 16V	1.39
100V MYLAR		50V CERAMIC	
.001-.01mf	4/.79	10pf-.022mf	4/.59
.022mf	4/.89	.047mf	4/.69
.047mf	4/.99	.1mf	4/.79
.1mf	4/1.19		
.22mf	4/1.29		

MICROPROCESSORS

Z80A	CPU (4MHz)	13.95
MC6800	8 Bit MPU	8.95
8080A	CPU	6.95
8212	8 Bit I/O Port	3.95
8216	Bi-Directional Bus Driver	4.49
2513/2140	Character Generator	12.95
8T97	Tri-State Hex Buffer	2.25
AV-5-1013	30K Baud UART	6.95
AV-5-2376	88-Key Keyboard Encoder	11.95
2114-2	4K Static RAM (200ns)	3.95
MK4116	16K Dynamic RAM (250ns)	3.95
2708	8K EPROM	5.95
2716	16K EPROM (+5V)	9.95

Function Generator Kit

Provides 3 basic waveforms: sine, triangle and square wave. Freq. range from 1 Hz to 100K Hz. Output amplitude from 0 volts to over 6 volts (peak to peak). Uses a 12V supply or a ±6V split supply. Includes chip, P.C. Board, components & instructions.



JE2206B\$19.95

PRECISION AUDIO FILTERS

LINEAR PHASE LOW PASS FILTERS CAN BE USED IN EQUALIZERS, ANALYZERS, MULTI-AMPING ETC. USING OP-AMPS, HIGH PASS AND BAND PASS FUNCTIONS ARE EASILY DONE ORIGINAL COST WAS OVER \$100 EACH! 1-3/4" SQUARE X 1/2" HIGH. 18 DB/OCTAVE, LINEAR PHASE

\$3 EACH YOUR CHOICE

STOCK # FREQUENCY STOCK # FREQUENCY

F-0312 .312 KHZ F-0110 10 KHZ
 F-0125 1.25 KHZ F-0200 20 KHZ
 F-0205 2.5 KHZ F-0400 40 KHZ
 F-0500 5.0 KHZ F-0800 80 KHZ

BUY FROM DIAMONDBACK & SAVE!!

PRECISION 10-TURN PANEL MOUNT 5K CLAROSTAT 1/4" shaft 3/8" Bushing \$3

B-2155 3.0Z

A/D BOARD

4/D BOARD CONTAINS ONE ANALOGIC MP-270 VERY HI SPEED SAMPLE & HOLD MODULE, ONE ANALOGIC MP272C VERY HI SPEED 12 BIT A/D CONVERTER MODULE, PLUS ASSORTED IC'S, POT'S, ETC.

A/D and D/A Converter Boards \$35

FANTASTIC GIVEAWAY PRICES!! THESE ASSEMBLED & TESTED BOARDS WERE DESIGNED FOR USE IN DIGITAL INSTRUMENTATION RECORDERS BY A TOP MFR.—USE AS IS OR REMOVE THE A/D OR D/A MODULES FOR YOUR OWN USE—THE MODULES ON EITHER BOARD ARE WORTH IN EXCESS OF \$1,000.

—INTERFACE YOUR COMPUTER TO THE REAL WORLD—

D/A BOARD CONTAINS (4) ANALOGIC MP412 HI-SPEED 12-BIT DAC MODULES; PLUS NUMEROUS POT'S, IC'S, ETC.

YOUR CHOICE

A/D BOARD WT. 9 OZ D-5020

D/A BOARD WT. 9 OZ D-5010

16 TRACK TAPE HEAD ASSEMBLIES \$35 PER HEAD

M-1600 19 OZ

QUANTITIES LIMITED

WE'VE GOT OUR HEADS TOGETHER! THESE ARE BRAND NEW, ULTRA-HIGH QUALITY HEADS CURRENTLY LISTING OVER \$1,000 EACH! THEY ARE NESTED 1/2 OR 3/4 TO AN ASSEMBLY MOST ARE 8 TRACKS PER HEAD, 2 STAGGERED THIS YIELD 16 TRACKS PER ASSEMBLY. BOTH RECORD & PLAY HEADS ARE AVAILABLE. CALL FOR FURTHER INFORMATION

Auto/Marine Goodies \$99c

DPDT 10A CENTER OFF TOGGLE SWITCH 99c

PANEL MOUNT PUSH BUTTON CIRCUIT BREAKER 10 OR 11 AMP 99c

PUSH-PULL 3 POSITION LITE SWITCH WITH HARDWARE 99c

PANEL MOUNT 50 AMP CIRCUIT BREAKER CHROME TOGGLE 99c

MAP LITE STAINLESS STEEL WITH 12V BULB & ALL HARDWARE 99c

HEAVY CHROME PLATE 12" LEADS 99c

PANEL MOUNT 30 AMP CIRCUIT BREAKER CHROME TOGGLE 99c

PILOT LIGHT WITH RUBY LENS 99c

MAP LITE STAINLESS STEEL WITH 12V BULB & ALL HARDWARE 99c

HEAVY CHROME PLATE 12" LEADS 99c

MAP LITE STAINLESS STEEL WITH 12V BULB & ALL HARDWARE 99c

PANEL MOUNT 30 AMP CIRCUIT BREAKER CHROME TOGGLE 99c

DPDT 10A CENTER OFF TOGGLE SWITCH 99c

PANEL MOUNT PUSH BUTTON CIRCUIT BREAKER 10 OR 11 AMP 99c

PUSH-PULL 3 POSITION LITE SWITCH WITH HARDWARE 99c

PANEL MOUNT 50 AMP CIRCUIT BREAKER CHROME TOGGLE 99c

MAP LITE STAINLESS STEEL WITH 12V BULB & ALL HARDWARE 99c

HEAVY CHROME PLATE 12" LEADS 99c

PANEL MOUNT 30 AMP CIRCUIT BREAKER CHROME TOGGLE 99c

100 PIN BARE WIREWRAP PROTOBOARDS \$15

CUT HERE FOR TWO PROTO-BOARDS

P-1010 1 LB

COMMERCIAL QUALITY 6-10 CONSTRUCTION WITH GOLD EDGE FINGERS FIT S-100 CONNECTORS. EACH BOARD HAS ROOM FOR 306, 14, 16 OR 18 PIN SOCKETS, DOUBLE SIDED, HEAVY TIN PLATE WITH POWER BUSES AND ROOM FOR LOADS OF BY-PASS CAPACITORS. BOARD CAN BE CUT IN HALF YIELDING TWO COMPLETE 153 SOCKET BOARDS. 10-1/2" X 7-1/2" SIZE WITH 100 PIN EDGE CONTACTS—WOW! YOU CAN'T LOSE!

TRANSISTOR DEALS

2N706 TO-18 NPN 25V HI-SPD SWITCH 20¢

2N2955 TO-18 PNP COMP TO 2N3055 89¢

2N3055 TO-3 NPN 15W 60V 15A 16¢

2N3904 TO-92 NPN 40V 100-300HF 16¢

2N3906 TO-92 PNP 40V 100-300HF 16¢

2N4036 TO-5 PNP 7W 65V 50MHZ 85¢

2N5160 TO-5 PNP 5W 40V 500MHZ 95¢

2N5088 TO-92 NPN 30V 300-900HF 20¢

S-100 connectors \$3.50

FIT ABOVE BOARD'S TWO ROWS OF 50 PINS, .100" CENTERS, GOLD BIFURCATED CONSTRUCTION

B-1910 (2 OZ)

4K STATIC RAMS \$16

SET OF EIGHT

2114L 300 ns

22K TRIMPOT PC MOUNT 8¢

B-1922 1/2 OZ

4 FT. LINE CORDS \$1.50 each

C-1000 2 OZ

SOLID CARBIDE DRILL BITS \$1.50 each

049" D-0490
 073" D-0730
 096" D-0960
 101" D-1010

DIAMONDBACK ELECTRONICS COMPANY

PO BOX 12053 SARASOTA, FL 33578

PHONE ORDERS 813-953-2829

CONTINENTAL US ADD \$2.25 FOR THE FIRST LB. B 25¢ FOR EACH EXTRA POUND WEST COAST ADD \$3 FOR THE FIRST LB. & 25¢ FOR EACH ADDITIONAL POUND — \$7 MINIMUM ORDER —

CIRCLE 64 ON FREE INFORMATION CARD

SOUND EFFECTS GENERATOR KIT

Exciting sound effects kit uses the popular T176477 chip to develop phasor, locomotive, siren, tweeting bird, organ, model T, etc. sounds. Uses dip switch for simple programming of the generator. A programming chart is included for many different sounds! The kit produces good volume and tone from 2" speaker. Operates from 9V battery. Size of board: 3.25" x 2".

C4422 \$12.95

FASCINATING STAR KIT

Produces an "Exploding Star" visual effect using 25 LEDs. The center LED lights first then the next and so on. The outer LEDs light and then another set lights until the outer edge of the star lights up. The process then reverses itself. Great attention getter for game rooms, discos, etc. Operates from 9V battery.

C4432 \$10.95

ELECTRONIC WHEEL OF FORTUNE KIT

Very popular game device! Push the start button and a bright red ball (LED) appears to spin around ten numbers gaining speed as you hold the button down. When you release the button the electronic ball appears to slow down and finally comes to a stop on one number. As the ball spins a small speaker emits a ticking sound in synchronization. Unit operates from 9V battery. Size of board: 2.9" x 2.6".

C3806 \$9.99

PHOTO SLAVE TRIGGER KIT

Probably the most sensitive slave trigger kit on the market. Not affected by ambient light. Much superior than LASCR types. This kit can operate from bounce or indirect flash. Simply connect shutter cord (included) to the strobe that will be used as the slave. When the master strobe is fired the slave strobe will also flash. Size of board: 1.5" x 1".

C4450 \$6.00

120 VAC Xenon Strobe Kit

Complete variable rate strobe light kit. Contains all parts, PC board, line cord and instructions.

C3071 \$7.50

DUAL STROBE LIGHT KIT

DUAL XENON STROBE TUBES FLASH ALTERNATELY ON THIS UNIQUE KIT. BRILLIANT FLASHES OF WHITE FLASH WITH THE ADDED DIMENSION OF 2" XENON BULBS. KIT FEATURES FIXED FLASH RATE AND OPERATION FROM 120VAC. COMPLETE WITH ALL PARTS, PC BOARD AND STROBE TUBES. SIZE OF BOARD: 3" x 3".

C4564 \$12.00

CHANEY electronics Inc.

P.O. BOX 27038 DENVER, COLORADO 80227

Phone Orders: 303-781-5750 • Minimum AD Order \$6.00
 303-781-5750 • Please include \$1.50 for postage
 • VISA MC accepted
 • Phone orders are welcome

Send for our free catalog of unique items

CIRCLE 73 ON FREE INFORMATION CARD

CALIFORNIA COMPUTER SYSTEMS

S100

2032 32K STATIC RAM A & T. 200 NSEC. \$629.00

2116 16K STATIC RAM A & T. 200 NSEC. \$329.00

2065 64K DYNAMIC RAM A & T. \$548.95

2200 S-100 MAIN FRAM A & T. \$379.95

2422 FLOPPY DISC WITH CP/M 2.2" \$329.95

2802 6502 PROCESSOR A & T. \$282.95

2810A Z80 CPU A & T. \$249.95

2710A 4 SERIAL 1/0 A & T. \$291.95

2718A 2 SERIAL, 2 PARALLEL A & T. \$305.95

2720A 4 PARALLEL A & T. \$214.95

PROTO BOARDS WW \$39.95

APPLE PRODUCTS

7114A 12K ROM/PROM. \$68.50

7424A CALENDAR/CLOCK. \$106.95

7440A PROGRAMMABLE TIMER. \$98.50

7470A A TO O CONVERTER \$105.95

7490A GPIB (IE 488) INTERFACE. \$265.95

7710A ASYNC SERIAL. \$125.95

7712A SYNC SERIAL. \$153.95

7720A PARALLEL STANDARD. \$98.95

7720B PARALLEL CENTRONICS. \$98.95

7811B ARITHMETIC PROCESSOR W/DISC. \$342.95

7811C ARITHMETIC PROCESSOR W/ROM. \$342.95

7500A WW BOARD. \$22.95

7510A SOLDERTAIL BOARD. \$23.95

SOFTWARE

2610 CP/M™ MACRO ASSEMBLER ON DISK. \$76.95

2620 CP/M™ SYMBOLIC INSTRUCTION DEBUGGER. \$64.25

2630 CP/M™ TEXT FORMATER. \$64.25

2640 CP/M™ BACKGROUND PRINT UTILITY. \$42.95

OTHER CCS PRODUCTS ARE AVAILABLE. CALL FOR PRICE.

SSM MICROCOMPUTER PRODUCTS

S100 PRODUCTS

CBIA 8080 PROCESSOR PCBD. \$32.95

KIT. \$155.95. A & T. \$215.95

CB-2 280 PROCESSOR BOARD. \$198.95. A & T. \$269.95

VBIC 64 x 16 VIDEO, PCBD. \$32.95

KIT. \$153.95. A & T. \$199.95

VB2 64 x 16 VIDEO, PCBD. \$32.95

KIT. \$175.95. A & T. \$234.95

VB3 80 CHARACTER VIDEO 4MHZ. \$345.95. A & T. \$425.95

UPGRADE RAMS FOR VB-3. \$42.00

I04 2 PARALLEL, 2 SERIAL, PCBD. \$32.95

KIT. \$155.95. A & T. \$194.93

PB-1 2708, 2716 PROGRAMMER BOARD. \$135.95. A & T. \$185.95

MB-10 16K STATIC RAM. \$299.95. A & T. \$339.95

APPLE PRODUCTS

A488 IEEE 488 INTERFACE. \$399.95

A10 SERIAL/PARALLEL INTERFACE. \$125.95. A & T. \$155.95

AS10 SERIAL I/O. \$87.95. A & T. \$97.95

AP10 PARALLEL I/O W/O CABLES. \$67.95. A & T. \$87.95

OTHER SSM PRODUCTS ARE AVAILABLE. CALL FOR PRICES.

MIKOS

MONDAY-FRIDAY, 8:00 TO 12:00, 1:00 TO 5:30
 THURSDAYS, 8:00 TO 9:00 P.M.

(415) 728-9121

P.O. BOX 955 • EL GRANADA, CA 94018

PLEASE SEND FOR IC, XISTOR AND COMPUTER PARTS LIST

CIRCLE 59 ON FREE INFORMATION CARD

FEB SPECIAL SALE ON PREPAID ORDERS

(CHARGE CARDS, C.D.D. OR P.O.'S NOT AVAILABLE)

WAMECO PCBD'S: EPM-1, PTB-1, ATC-1, IOB-1... \$19.95 EA.

SSM PCBD'S: IO-2, DB-1... \$22.95 EA.

MB-1 (MK8, 4K x 8)... \$14.95 EA.

MISC: 8K x 8 RAM, A & T 450 NSEC... \$59.95 EA.

250 NSEC... \$79.95 EA.

IO-2 KIT... \$45.95 EA.

74 LS SERIES PRIME PARTS

EA 5 FOR	EA 5 FOR	EA 5 FOR
LS00 25 1.23	LS132 75 3.56	LS197 85 4.04
LS02 25 1.23	LS136 50 2.38	LS221 1.15 5.46
LS04 25 1.23	LS138 75 3.56	LS240 1.80 8.55
LS05 25 1.23	LS139 75 3.56	LS243 1.75 8.31
LS08 35 1.66	LS145 1.20 5.70	LS244 1.75 8.31
LS10 25 1.23	LS147 2.49	LS245 2.15
LS13 45 2.14	LS148 1.35	LS251 1.00 4.75
LS14 99 4.50	LS151 75 3.56	LS257 85 4.04
LS20 25 1.23	LS153 75 3.56	LS258 85 4.04
LS26 35 1.66	LS155 90 4.28	LS260 65
LS27 35 1.66	LS156 90 4.28	LS266 46 2.19
LS30 25 1.23	LS157 75 3.56	LS279 50 2.38
LS32 35 1.66	LS158 75 3.56	LS290 80 3.80
LS37 55 2.50	LS160 90 4.28	LS293 80 3.80
LS38 35 1.66	LS161 95 4.51	LS295 1.05 4.99
LS42 55 2.50	LS162 95 4.51	LS367 70 3.33
LS74 45 2.14	LS163 95 4.51	LS368 70 3.33
LS75 50 2.38	LS164 95 4.51	LS373 1.85 8.55
LS85 1.15 5.46	LS166 1.75 8.31	LS374 1.85 8.55
LS86 40 1.90	LS173 80 3.80	LS377 1.45 6.89
LS90 60 2.85	LS174 95 4.51	LS378 1.18 5.61
LS92 60 2.85	LS175 95 4.51	LS620 2.25
LS93 60 2.85	LS190 1.00 4.75	LS626 2.25
LS122 45 2.14	LS191 1.00 4.75	LS629 1.44
LS123 95 4.50	LS192 85 4.04	LS682 3.20
LS125 90 4.28	LS193 95 4.51	LS683 2.30
LS126 75 3.56	LS196 85 4.04	LS688 2.40

QUANTITY OF 5 FOR MUST BE OF THE SAME DEVICE. THEY MAY NOT BE MIXED. AN ADDITIONAL 5% OFF PURCHASES OVER \$50 ON LS PARTS ON PREPAID ORDERS BY CHECK OR MONEY ORDER ONLY.


VISA or MASTERCHARGE. Send account number, interbank number, expiration date and sign your order. Approx. postage will be added. Orders with check or money order will be sent post paid in US. If you are not a regular customer, please use charge, cashier's check or postal money order. Otherwise, there will be a two-week delay for checks to clear. Calif. residents add 6% tax. Money back 30-day guarantee. We cannot accept returned IC's that have been soldered to. Prices subject to change without notice. \$20 minimum order. \$2.00 service charge on orders less than \$10.00.

www.americanradiohistory.com

Aaron-Gavin Kits

Equalizers Mixers LED Meters

COMPARE! 31 BANDS

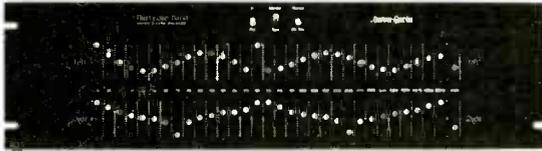

Audiophile & Professional 2 CH., 1/3 Octave Equalizer. unique LINEAR Mirror Image Circuitry. Totally eliminates snap-on. Generates a TRUE ±15db Boost and Cut on EVERY BAND without band to band phase cancellation or rainbow effect.

- Super Low Noise J-Fets ON ALL BANDS
- Regulated Power Supply
- Slew Rate: "13 Volts" per microsecond
- Built-in Record Switching - no need to re-patch

And as always with Aaron-Gavin Instruments. Lowest Noise. Lowest distortion and Great Over-All PROFESSIONAL Quality.

GRAPHIC EQUALIZERS

Description	Kit	Mfg.
31 Band Stereo EQ	\$279.56	\$544.54
31 Band Mono EQ	\$157.05	\$322.53
21 Band Stereo EQ	\$205.02	\$421.02
21 Band Mono EQ	\$125.05	\$258.64
11 Band Stereo EQ	\$114.94	\$230.00
11 Band Mono EQ	\$75.84	\$151.57
11 Band Stereo EQ	\$129.50	\$249.80
5 Band Stereo EQ	\$74.50	\$148.99
5 Band Mono EQ	\$49.14	\$98.27

LED METERS (All Integratec circuits)

Description	Kit	Mfg.
DOT or BAR Pattern, 3 position range switch		
Front panel mount only:		
10 LED (Mono)	\$44.40	\$55.80
20 LED (Stereo)	\$52.20	\$68.00
Cabinet or Rock Mount:		
20 LED (Mono)	\$50.40	\$68.00
40 LED (Stereo)	\$67.00	\$88.60
Down to -71db!		

Order with this Coupon or send for product specifications.

Check box for the item of your choice send check, money order, COD or Visa, Master

Charge. Your card number _____ Exp. date _____
 Add \$7.00 for shipping and handling. Check Freq. Range: 16Hz-16KHz 20Hz-20KHz
 Check style: Rock Mount Flat Cabinet Upright Cabinet

NAME _____ PHONE _____
 ADDRESS _____
 CITY _____ STATE _____ ZIP _____
 Aaron-Gavin, 1901 E. Deere St., Dept. 18, Santa Ana, CA 92705. Phone: (714) 957-8770

CIRCLE 68 ON FREE INFORMATION CARD

Fall & Winter '81 - TEST EQUIPMENT Electronic Component Catalog

FREE 160 Page Book

We carry the Following:

TEST EQUIPMENT

- B & K
- LEADER
- VIZ
- BECKMAN
- HITACHI
- GLOBAL SPECIALTIES
- DATA PRECISION
- HICKOK

ELECTRONIC COMPONENTS

- JAPANESE & MOTOROLA Transistors
- IC's, FET, Diodes
- Capacitors
- Resistors
- Connectors, Cables

TOOLS

- Weller, Ungar, Xcellite, Vaco, etc.

SEEKING ELECTRONIC COMPONENTS AT WHOLESALE COST

半導体

FALL CATALOG 1981

SELECT FROM OUR LARGE INVENTORY READY TO SHIP

O.E.M. INQUIRIES WELCOME

FUJI-SVEA INC.

- Over 10 million components in stock to serve you
- Over 20,000 sq. ft. of warehouse in the East & West
- NO MINIMUM ORDER!



FUJI-SVEA®

CALL TOLL FREE
800-421-2841

P.O. Box 40325 Cincinnati OH 45240
Dept. Radio-Electronics

Local: 513-874-0220
Telex: 182 392

Name _____ Phone _____
 Company _____
 Address _____
 City _____ State _____ Zip _____

CIRCLE 69 ON FREE INFORMATION CARD

<p>\$395</p> <p>SONALERT</p> <p>MALLORY SNP-428 4-28 VDC 3-16 ma. Fits 1 1/8" hole</p>	<p>\$795</p> <p>SOLDER</p> <p>KESTER 60/40 Rosin core. .020 dia. 1 Pound Roll</p>	<p>\$1200</p> <p>FAN</p> <p>Whisper by Rotron WR2H1 4-3/4" Sq. 115 VAC 7 Watt</p>	<p>5 VOLT STEPPING MOTOR \$2000</p> <p>SLO-SYN MP70-1A-Z9-1A-005 5.2 V @ 1.44 A 48 Steps/Rev. 1/4" Shaft 1/8" L. Mtg. Holes 2-3/16" C-C</p>	<p>SHUGART HEAD</p> <p>Fits SHUGART 800/801</p> <p>\$6500</p>	<p>DYNAMIC RAMS</p> <p>4K x 1 300 ns D2104A 16 Pin TMS 4030 22 Pin</p> <p>95c</p> <p>PROM Harris 7640 512 x 8 VOL OC 24 Pin \$795</p> <p>UART COM 2502 25KHz 40 Pin + 5 -12 \$495</p>
<p>JOYSTICK</p> <p>4 - 10K Linear pots 1 - 1/2" metal handle 2 - 1/8" square</p> <p>\$595</p>	<p>POWER SUPPLY</p> <p>\$4750</p> <p>IN PUT 110 - 220 VAC 5 - 3/4 x 7 - 1/2 x 4" h</p> <p>OUTPUT + 5 VDC - 5 Amp. + 12 VDC - 1 Amp. - 12 VDC - 1 Amp.</p>	<p>DIABLO PRINT HEAD</p> <p>Matrix Head #24800 Fits DIABLO 1660</p> <p>\$9500</p>	<p>BRIDGE 10 AMP 600 VOLT 200 ns Tr</p> <p>VARD VJ648X 1/4" Leads</p> <p>\$200 10 for \$1500</p>	<p>1000 VOLT 12 AMP DIODE</p> <p>MR 1130 R</p> <p>\$125 10 for \$1000</p>	
	<p>SHIELDED POWER CORD</p> <p>6' - 7" Lg. \$250 10 for \$2000</p>	<p>RS-232 CONNECTOR</p> <p>DBC-25P male Crimp Pin \$225 DB-25 cover \$125</p>	<p>LM 323 5 VOLT 3 AMP</p> <p>\$395</p> <p>Heat Sink 75c</p>	<p>COMPUTER GRADE CAPS</p> <p>5,200 MFD 25VDC 1-7/16 x 2-3/8H \$125</p> <p>11,000 MFD 35VDC 1-3/4 x 4-1/2 h \$350</p> <p>12,000 MFD 25VDC 1-7/16 x 3-7/16 h \$250</p> <p>22,000 MFD 25VDC 1-7/16 x 41/4 h \$350</p>	
<p>EDGE METER</p> <p>0 - 15 VDC 25/32 x 1-13/16</p> <p>\$350</p>	<p>PN2222A</p> <p>10 for \$100 100 for \$700</p> <p>Same as 2N2222A</p>	<p>TRIAC</p> <p>MAC 10-4 10 AMP \$125 200 V 10 for \$1000</p>	<p>PHONE JACK</p> <p>25c</p> <p>Switchcraft #12A 1/4" 2 conductor with Switch</p>	<p>7812 12 VOLT 1 AMP</p> <p>90c 10 for \$750 Heat Sink 25c</p>	<p>DATA CASSETTES</p> <p>\$175</p> <p>10 for \$1500</p> <p>Made for Datapoint by Maxell 90 min. with case 5 screw high strength shell</p>
<p>ROTARY DIP SWITCH</p> <p>10 Position BCD</p> <p>\$150 10 for \$1250</p>	<p>REFLECTIVE SENSOR</p> <p>MONSANTO MCA 7 Infrared emitter and Photo Darlington output</p> <p>\$150 10 for \$1250</p>	<p>TERMS</p> <p>Quantities Limited COD, check, money order VISA, Mastercharge</p> <p>Texas residents add 5% state sales tax. Add \$3.00 shipping charges for orders under \$50.00.</p>	<p>ALTEX ELECTRONICS</p> <p>618 W. Sunset San Antonio, Texas 78216</p> <p>In Texas Call (512) 828-0503</p> <p>1-800-531-5369</p>		

CIRCLE 56 ON FREE INFORMATION CARD

7400

SN7400N	.19	SN74123N	.39
SN7401N	.22	SN74125N	.59
SN7402N	.22	SN74126N	.44
SN7403N	.22	SN74128N	.59
SN7404N	.22	SN74132N	.59
SN7405N	.23	SN74135N	.75
SN7406N	.23	SN74139N	.95
SN7407N	.23	SN74141N	.79
SN7408N	.26	SN74142N	2.95
SN7409N	.23	SN74143N	2.95
SN7410N	.22	SN74145N	.62
SN7411N	.29	SN74145N	.62
SN7412N	.29	SN74147N	1.95
SN7413N	.39	SN74148N	1.20
SN7414N	.59	SN74150N	1.09
SN7415N	.29	SN74151N	.67
SN7416N	.29	SN74152N	.87
SN7420N	.22	SN74153N	.67
SN7421N	.35	SN74154N	1.19
SN7422N	.29	SN74155N	.78
SN7423N	.29	SN74156N	.78
SN7425N	.29	SN74157N	.89
SN7426N	.29	SN74158N	1.65
SN7427N	.25	SN74160N	.88
SN7429N	.45	SN74161N	.88
SN7430N	.23	SN74162N	.89
SN7432N	.29	SN74163N	.87
SN7433N	.29	SN74164N	.87
SN7438N	.29	SN74165N	.87
SN7439N	.29	SN74166N	1.20
SN7440N	.19	SN74167N	1.95
SN7441N	.79	SN74170N	1.69
SN7442N	.59	SN74172N	4.75
SN7443N	.55	SN74173N	2.95
SN7444N	.55	SN74174N	.89
SN7445N	.79	SN74175N	.85
SN7446N	.79	SN74176N	.85
SN7447N	.55	SN74177N	.75
SN7448N	.79	SN74178N	1.34
SN7450N	.19	SN74180N	.75
SN7451N	.19	SN74181N	1.75
SN7453N	.19	SN74182N	.75
SN7454N	.19	SN74184N	2.25
SN7459N	.29	SN74185N	2.25
SN7460N	.23	SN74186N	.85
SN7470N	.29	SN74188N	3.00
SN7472N	.29	SN74190N	1.15
SN7473N	.34	SN74191N	1.15
SN7474N	.34	SN74192N	.85
SN7475N	.34	SN74193N	.85
SN7476N	.34	SN74194N	.85
SN7479N	4.60	SN74195N	.68
SN7480N	.49	SN74196N	.85
SN7482N	.95	SN74197N	.85
SN7483N	.95	SN74198N	1.39
SN7485N	.85	SN74199N	1.39
SN7486N	.35	SN74221N	.95
SN7489N	1.75	SN74225N	1.19
SN7490N	.39	SN74227N	1.05
SN7491N	.57	SN74229N	.75
SN7492N	.45	SN74231N	1.40
SN7493N	.45	SN74284N	3.00
SN7494N	.69	SN74285N	3.90
SN7495N	.65	SN74290N	1.25
SN7496N	.69	SN74298N	.95
SN7497N	.29	SN74301N	.88
SN74100N	1.20	SN74366N	.68
SN74101N	.32	SN74367N	.68
SN74109N	.37	SN74368N	.68
SN74116N	1.95	SN74390N	1.45
SN74121N	.39	SN74393N	1.90
SN74122N	.39	SN74490N	1.90

74LS00

74LS00N	.28	74LS164N	1.19
74LS01N	.28	74LS165N	.89
74LS02N	.28	74LS166N	2.48
74LS03N	.28	74LS168N	1.15
74LS04N	.35	74LS169N	1.15
74LS05N	.35	74LS170N	1.39
74LS08N	.28	74LS173N	.89
74LS09N	.35	74LS174N	.89
74LS10N	.28	74LS175N	.89
74LS11N	.39	74LS181N	2.20
74LS12N	.33	74LS190N	1.15
74LS13N	.47	74LS191N	1.15
74LS14N	.95	74LS192N	.98
74LS15N	.35	74LS193N	.98
74LS20N	.26	74LS194N	1.15
74LS21N	.33	74LS195N	.95
74LS22N	.33	74LS197N	.89
74LS27N	.33	74LS221N	1.15
74LS28N	.33	74LS240N	1.69
74LS30N	.26	74LS241N	1.69
74LS32N	.33	74LS242N	1.69
74LS33N	.55	74LS244N	1.89
74LS34N	.49	74LS244N	1.89
74LS38N	.29	74LS245N	2.20
74LS40N	.26	74LS247N	1.10
74LS42N	.79	74LS248N	1.10
74LS47N	.79	74LS249N	1.19
74LS48N	.95	74LS251N	1.89
74LS51N	.26	74LS253N	.98
74LS54N	.29	74LS257N	.85
74LS55N	.29	74LS258N	.98
74LS57N	.45	74LS259N	2.95
74LS74N	.42	74LS260N	.59
74LS75N	.49	74LS261N	2.49
74LS76N	.45	74LS266N	5.29
74LS78N	.45	74LS273N	1.75
74LS83AN	.79	74LS275N	4.40
74LS85N	1.19	74LS279N	.99
74LS86N	.45	74LS283N	.99
74LS90N	.59	74LS290N	.99
74LS92N	.75	74LS293N	.99
74LS93N	.75	74LS295N	1.10
74LS95N	.88	74LS298N	1.19
74LS96N	.98	74LS324N	1.75
74LS107N	.45	74LS323N	1.95
74LS109N	.45	74LS348N	1.95
74LS112N	.43	74LS352N	1.19
74LS113N	.43	74LS353N	1.19
74LS114N	.43	74LS363N	1.49
74LS122N	.43	74LS365N	.69
74LS123N	1.19	74LS366N	.69
74LS124N	1.35	74LS367N	.69
74LS125N	.89	74LS368N	.69
74LS126N	.52	74LS373N	1.89
74LS132N	.79	74LS374N	1.89
74LS136N	.49	74LS375N	.89
74LS138N	.75	74LS377N	.95
74LS139N	.85	74LS385N	.95
74LS145N	1.25	74LS386N	1.65
74LS148N	1.49	74LS390N	1.95
74LS151N	.79	74LS391N	.95
74LS152N	.79	74LS395N	1.70
74LS154N	1.79	74LS399N	2.35
74LS155N	1.10	74LS424N	2.95
74LS156N	.99	74LS668N	1.75
74LS157N	.85	74LS70N	2.29
74LS158N	.75	81LS95N	1.69
74LS160N	1.05	81LS96N	1.69
74LS161N	1.15	81LS97N	1.69
74LS162N	1.05	81LS98N	1.69
74LS163N	1.05		

16K UPGRADE ONLY
\$24.95
 SPECIFY COMPUTER

hp HEWLETT PACKARD
 HP-85 \$2695.00
 HP 7225 Graphics Plotter 1795.00
 HP 16K Memory Module 285.00
 HP 5 1/4" Dual Master Flex. Disk Drive, 2100.00
 HP 5 1/4" Single Master Flex. Disk Drive 1295.00
 HP Personality Module 700.00
 HP ROM Drawer 40.00
 HP Plotter/Printer ROM 130.00
 HP Input/Output ROM 260.00
 HP Matrix ROM 130.00
 HP Serial Interface (RS-232C) 350.00
HP-83 \$1895.00

HP-41: Powerful, Yet Easy to Use
HP 41-CV
 • The HP-41 communicates with you in words as well as numbers
 • You can customize the HP-41 to your own design
 • Programming is fast and easy.
 • Continuous Memory saves everything
 • Optional Peripherals allow you to expand capabilities.

HP-41 System I 398.00
 HP-41 System II 675.00
 HP-41 Card Reader 178.00
 HP-41 Optical Wand 105.00
 HP-41C HP-Plotter/Printer 315.00
 HP-41Q HP-Quad RAM 85.00

MINIMOVER-5 ROBOTIC ARM
 Completely Assembled W/Applications Manual
 • Automation or Robotic Assembly
 • Education in Robotic Principles
 • Artificial Intelligence Experiments
 • Computer Art and Games

\$1695.00

Armbasic Software for TRS-80 W/Applications Manual \$39.95
 Applications/Reference Manual \$16.95

California Computer Systems 2200
SUPER S-100 BUY!

- 12 Slot Mainframe
- 64 Dynamic RAM
- CP/M 2.2
- Z-80 CPU 4 Mhz w/Serial IO
- Double Density Disk Controller
- Interface to Vista V-1000 Chassis

SPECIAL PACKAGE PRICE 1899.00
 FOR COMPLETE SYSTEM
 with (2) Shugart Double Density Floppys mounted. add 1495.00

Proto Clips

14-Pin Clip	PC-14	\$ 4.25
16-Pin Clip	PC-16	\$ 4.50
24-Pin Clip	PC-24	\$ 9.50
40-Pin Clip	PC-40	\$14.95

Proto Boards

PB-6	16.95	PB-104	54.00
PB-8	21.95	PB-105	37.00
PB-101	21.00	PB-203A	149.00
PB-102	21.00	PB-203A-KIT	129.00
PB-103	43.00		

Novation AUTO-CAT™
 Automatic Answer Direct Connect 0-300 Band
 List 279.95
ACP 249.95

CAT™
 Answer Originate
ACP 169.00

D-CAT™
 direct Connect 0-300 Band.
 List 249.00
ACP 189.00

Rockwell Single Board Computers

AIM 65 w/1K	435.00
AIM 65 w/4K	475.00
8K BASIC ROM	99.00
ASSEMBLER ROM	84.00
SD Z-80 STARTER KIT A&T	450.00
SD SBC 10 Z-80 AIT	367.00
SD SBC 20 Z-80 AIT	399.00
RCA COSMAC VIP	139.00
CHROMEMCQ Z-80 SBC	449.00

ADVANCED COMPUTER PRODUCTS

apple computer Sales and Service
Apple II® 64K
 • Z-80 Softcard
 • 16K Ram Card
 • Disk II w/controller
 • Apple II w/48K

Call for more pricing!
Total Value \$2719.00 your price \$2229.00 save!
For Pascal System add \$425.00

"Apple Products Sold In-Store ONLY"

VISTA COMPUTER Database/Interruptible P.S.	395.00	New	CCS Parallel Card 7720A	155.00
Vocalizer™/Voice Card	225.00	New	Apple Computer	
Video 80/80x24 Card	325.00	New	Apple II Speedster II	174.95
Video 40/40x24 Enhancement	175.00	New	Centronics Printer I/O	179.95
A800 Quad Density 8" Controller	595.00	New	Apple II Firmware	139.95
Microsoft Z-80 Softcard	259.00	New	Apple II	244.95
Microsoft 19K Ramcard	169.00	New	Apple Graphics Tablet	99.95
SSM A10 Same/Parallel IO	185.00	New	Apple Prototype Card	21.95
CCS Asynchronous T10 & Serial	139.00	New	Apple Disk II w/cont. 3.3	509.95
Apple JoyStick™ "GSE"	54.95	New	Apple Disk II	439.95
Mouse/Computer	279.00	New	MS II Apple II	49.95
RomPacs	169.00	New	Pascal Language Card	159.95
Rom Writer	158.00	New	Apple II Printer Card	159.95
IntrosX-10 Remote Cont. Sys.	180.00	New	Communications Card	189.00
IntrosX-10 Remote Cont. Sys.	249.00	New	Integar ROM Card	159.95
SuperTalker	229.00	New	Call. Prod Viscalc Keyboard	169.00
Music System	499.00	New	MS II Apple II	29.95
CPS Multifunction	229.00	New	Corvus 5MB Hard Disk	3699.00
Expansion Chassis	599.00	New	Corvus 10MB Hard Disk	Call
DC Hayes Smart Modem II	299.00	New	Corvus 20MB Hard Disk	Call
DC Hayes Smart Modem	349.95	New	Conv. Controller Card	Call
Thunderbolt	125.00	New	Corvus Mirror	Call
X-10 IO Option™	49.00	New	Apple 16K Upgrade Kit	24.95
Pascal For Above™	29.00	New	Scan Viscalc Recognition VET-2	995.00

apple Triple Play!

- Apple III 128K RAM Information Analysis Pkg. 12" Green Phosphor Monitor 4200.99
- Apple III 128K RAM Information Analysis Pkg. 12" Green Phosphor Monitor Disk II for Apple III 5100.00
- Apple III Information Analysis Pkg. 12" Green Phosphor Monitor Disk II for Apple III Silentwriter Printer 5500.00

Buy a System and Save

New apple software

Visicalc—Now Better Than Ever 169.00
 Visiplot—Graph your Visicalc Worksheets 149.00
 Visitrend/Visiplot—Visiplot w/Trend Analysis 239.00
 Visidex—The Ultimate DBMS Viscalc Compatible Visitem—Communicate w/other Systems 209.00
 BPI General Ledger 299.00
 BPI Accounts Receivable 299.00
 BPI Inventory 349.00
 Stockpile Inventory System 289.00
 Factory Inventory System 289.00
 Microcom Microcographer 229.00
 Microcom Microtelegraph 229.00
 Accounting Plus II Biz Pkg. 1250.00
 Stoneware DB Master 189.00
 Stoneware Utility Pkg. (For above) 89.00

WORDSTAR The Benchmark of Wordprocessing software requires Z-80 & 80K 349.00
 VTS-80 CP/M-Wordprocessor has no screen menus uses new keycaps (suggested) to display key functions 319.00
 MAIL-MERGE A Wordstar Enhancement Pkg. allows form letter generation & chained printing 169.00
 SPELLGUARD-Will proofread Wordstar & VTS-80 Text files against an expandable 20,000 word dictionary 169.00
 SUPER SORT-Will sort, merge, & perform record selection on your CP/M Data Files 169.00
 FORTRA 80 By Microsoft! 195.00
 COBOL 80 By Microsoft! 749.00

ACS BASIC ACCOUNTING SYSTEM, Total accounting system includes G/L, A/R, A/P, PAYROLL 699.00

Breakthru in Apple II® Mass Storage!
Vista A800 Quad Density DMA 8" Disk Controller
 Model A800... only \$595.00

Special Complete Subsystem Offer

- V1000 w/Two Qume Datatrack 8" • Cable, ready to run
- A800 Apple II 8" Disk Controller • BASIC Game Programs

Total Value \$2939.00 your price \$2495.00

ATARI® 800 & 400 Personal Computer System
ATARI 800 \$799.00
ATARI 400 \$375.00

ATARI 800 Includes: Computer Console, BASIC Lang. Cartridge, BASIC Language Programming Manual, 800 Operator's Manual w/Notebook, 16K RAM Module, Power Supply, TV Switch Box

Computer Press	35.00	Spelling	35.00
810 Disc Drive	499.00	Basic Electricity	35.00
820 Printer +10 Disk	295.00	Basic Algebra	35.00
825 Printer +10 Disk	795.00	Basic Geometry	35.00
850 RAM	19.95	Basic Trigonometry	35.00
16K RAM	84.95	U.S. Government	35.00
850 RAM	189.95	Business Communications	35.00
Printer/Recorder	69.00	World History	35.00
Software - IBM Cartridges	28.00	Basic Microscopy	35.00
Atari BASIC	55.00	Coursing Procedures	35.00
Assembler/Debugger	55.00	Principles of Accounting	35.00
Life	42.00	Basic Calculus	35.00
Super Brainout™	42.00	U.S. History	35.00
Music Composer	55.00	U.S. Government	35.00
Basic Business	42.00	Business Communications	35.00
		World History	35.00
		Basic Microscopy	35.00
		Coursing Procedures	35.00
		Principles of Accounting	35.00
		Basic Calculus	35.00
		U.S. History	35.00
		U.S. Government	35.00
		Business Communications	35.00
		World History	35.00
		Basic Microscopy	35.00
		Coursing Procedures	35.00
		Principles of Accounting	35.00
		Basic Calculus	35.00
		U.S. History	35.00
		U.S. Government	35.00
		Business Communications	35.00
		World History	35.00
		Basic Microscopy	35.00
		Coursing Procedures	35.00
		Principles of Accounting	35.00
		Basic Calculus	35.00
		U.S. History	35.00
		U.S. Government	35.00
		Business Communications	35.00

DIRECT FROM TOMAR: THE RIGHT DMM AT THE RIGHT PRICE.



\$49.95 kit
\$54.95 assembled & tested

Four function: DCV, ACV, Ohm & DCmA. Battery powered for field or laboratory. All functions protected against overload. Excellent resolution in all modes.

Factory direct. By eliminating the middle man, Tomar is able to offer the DMM813 digital multimeter at these remarkably low prices. Satisfaction is guaranteed by a 30-day money back offer.

Ordering. Send your check or money order (\$49.95 for a complete kit, \$54.95 for the DMM813 assembled and tested) to Tomar, Ltd. Allow 30 days for delivery. Add 6% tax for delivery in California.

TOMAR, LTD.

6322 Mojave Drive
San Jose, CA 95126

CIRCLE 62 ON FREE INFORMATION CARD

A 10 HOUR TAPE RECORDER


WAS \$125.00
NOW only \$95.00*

LONG PLAY

Modified Panasonic Slimline high quality AC-DC Recorder provides 5 continuous hrs. of recording & play back of top quality sound on each side of cassette for a total of 10 hrs. Built-in features include:

- Voice level control
- Auto. tape stop
- Digital counter, etc.

TDK DC-180 Cassette included.

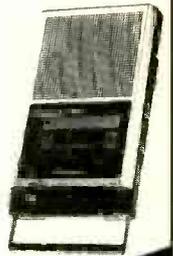

PHONE RECORDING ADAPTER

Records calls automatically. All Solid state connects to your telephone jack and tape recorder. Starts recording when phone is lifted. Stops when you hang up.

\$24.50*

FCC APPROVED

VOX VOICE ACTIVATED CONTROL SWITCH

Solid state. Self contained. Adjustable sensitivity. Voices or other sounds automatically activate and control recorder. Uses either recorder or remote mike.

\$24.95*

*Add for ship. & hdlg. Phone Call Adapter & VOX Recorder \$4.00. Cal. Res. add tax. Mail order. VISA, M/C, cod's ok. Qty. disc. avail. Money back guar. Free data. Dir. inq. inv. AMC SALES, Dept. 19, 9335 Lubec St., Box 928, Downey, CA (213) 90421 Phone 869-8519

CIRCLE 72 ON FREE INFORMATION CARD

COMPUTERS ATARI 800™ COMPUTER SYSTEM

16k → \$750.00
48k → \$898.00

"APPLE II Plus"
48k → \$1199.00
64k → \$1399.00

ATARI ☆
Software
Missile Command
Asteroids
Star Raiders
Chess
All, \$3600/ea

REAL-TIME CLOCK CALENDAR (MSM 5832)

Features: Mono Metal Gate CMOS I.C.
Time, Month, Date, Year, Day of Week
Bus Oriented
4 Bit Data Bus
14 Bit Address
14 Day Hold Select.
Inter Signal
32.768KHz xtal Control
5v Pow Sup
Low Power Dissipation

\$7.45
XTAL \$2.85

CARDS

MICROSOFT:
Z80 \$295.00
16K RAM \$160.00
VIDEO TERM 80 column \$295.00
KEYBOARD ENHANCER \$120.00

CALIF COMP SYS

APPLE CLOCK \$12400
PROTO BOARD \$2500
PRINTERS EPSON MX-80 \$535.00
FT- \$645.00
Interface & cable \$78.90

POWER SUPPLY MODEL #CP198
input - 110/125v output - 5vdc
at 6amps
THE MPD 117
Turns an ordinary outlet into a controlled power source
\$29.95
Qty. price avail.
\$79.50

DISKETTE «SALE»

Wabash:
5 1/4 → 10/ \$24.95
8inch → 10/ \$27.95
Dysan & Spectrum also available!!
call for price

WE CARRY COMPUTER BOOKS!!!

CONCORD COMPUTER PRODUCTS

1971 SO. STATE COLLEGE
ANAHEIM, CALIF. 92806

(714) 937-0637
CHECK - M/O
NO COD

\$10. MIN ORDER / CA. RES. ADD 6% FRT

\$10-49 \$2.00 \$50-99 \$4.00 \$100-240 \$8.00 \$250-499 \$9.00 \$500-999 \$11.00 \$1000-UP CALL

★SPECIALS★

ZENITH ZVM-121 Video Monitor: Green Phosphor 12 inch. 15+Mhz. → \$134.00
3inch MUFFIN FAN w/card → \$9.95
UPD 765: Floppy Disk Cont. → \$19.95
8155- RAM → \$11.50
8255- PPI → \$7.95
2111- Static RAM → \$1.75
8085A CPU → \$8.50
MC 6800- CPU → \$7.75
ER 2501- EAROM → 4.95

AY3-8603 → \$4.95
LM300H → 45c
6802 → \$9.50
6502 → \$6.50
6821 → \$4.95

MONITORS

AMDEK Corp.
12in. B/W → \$129.00
12in. Green → \$155.00
13in. Color → \$365.00

T-bar inc.

RS-232 COMPATIBLE DIGITAL TRANSFER SWITCH WILL SWITCH MODEMS BETWEEN PROCESSORS / PRINTERS. 24 PINS ARE SWITCHED. PIN 1 WIRED TO GROUND.
#5712
DESK TOP #5722
\$149.00

COMPONENTS

SN7400N	16	SN7482N	30
SN7402N	27	SN7489N	48
SN7404N	31	SN7493N	45
SN7408N	22	SN7498N	50
SN7410N	18	SN7499N	68
SN7412N	30	SN74129N	39
SN7413N	22	SN74138N	66
SN7414N	28	SN74141N	69
SN7416N	27	SN74151N	65
SN7417N	29	SN74153N	65
SN7420N	17	SN74154N	125
SN7425N	20	SN74155N	75
SN7430N	17	SN74157N	58
SN7437N	27	SN74160N	69
SN7438N	24	SN74161N	65
SN7440N	18	SN74163N	65
SN7442N	45	SN74164N	67
SN7443N	42	SN74165N	65
SN7445N	64	SN74174N	68
SN7451N	19	SN74175N	79
SN7454N	18	SN74180N	75
SN7474N	27	SN74181N	115
SN7475N	35	SN74383N	165

74LS00

74LS00	28	74LS158	69
74LS02	28	74LS161	63
74LS03	28	74LS162	69
74LS04	28	74LS163	69
74LS05	22	74LS164	65
74LS08	29	74LS165	65
74LS10	26	74LS166	65
74LS14	89	74LS167	65
74LS16	22	74LS168	65
74LS17	28	74LS169	65
74LS18	28	74LS170	175
74LS19	28	74LS171	175
74LS20	22	74LS172	175
74LS21	26	74LS173	175
74LS22	26	74LS174	175
74LS23	27	74LS175	175
74LS24	37	74LS176	175
74LS25	29	74LS221	125
74LS26	29	74LS222	125
74LS27	31	74LS240	165
74LS28	31	74LS241	165
74LS29	31	74LS242	165
74LS30	31	74LS243	165
74LS32	31	74LS244	150
74LS33	31	74LS245	150
74LS34	31	74LS246	150
74LS35	31	74LS247	150
74LS36	31	74LS248	150
74LS37	31	74LS249	150
74LS38	31	74LS250	150
74LS39	31	74LS251	150
74LS40	31	74LS252	150
74LS41	31	74LS253	150
74LS42	31	74LS254	150
74LS43	31	74LS255	150
74LS44	31	74LS256	150
74LS45	31	74LS257	150
74LS46	31	74LS258	150
74LS47	31	74LS259	150
74LS48	31	74LS260	150
74LS49	31	74LS261	150
74LS50	31	74LS262	150
74LS51	31	74LS263	150
74LS52	31	74LS264	150
74LS53	31	74LS265	150
74LS54	31	74LS266	150
74LS55	31	74LS267	150
74LS56	31	74LS268	150
74LS57	31	74LS269	150
74LS58	31	74LS270	150
74LS59	31	74LS271	150
74LS60	31	74LS272	150
74LS61	31	74LS273	150
74LS62	31	74LS274	150
74LS63	31	74LS275	150
74LS64	31	74LS276	150
74LS65	31	74LS277	150
74LS66	31	74LS278	150
74LS67	31	74LS279	150
74LS68	31	74LS280	150
74LS69	31	74LS281	150
74LS70	31	74LS282	150
74LS71	31	74LS283	150
74LS72	31	74LS284	150
74LS73	31	74LS285	150
74LS74	31	74LS286	150
74LS75	31	74LS287	150
74LS76	31	74LS288	150
74LS77	31	74LS289	150
74LS78	31	74LS290	150
74LS79	31	74LS291	150
74LS80	31	74LS292	150
74LS81	31	74LS293	150
74LS82	31	74LS294	150
74LS83	31	74LS295	150
74LS84	31	74LS296	150
74LS85	31	74LS297	150
74LS86	31	74LS298	150
74LS87	31	74LS299	150
74LS88	31	74LS300	150

Bare Bones APPLE II

W/O Keyboard \$450.
W/O Pwr. Supply

74800	38	74S138	75
74822	48	74S140	100
74803	38	74S164	75
74804	38	74S174	135
74805	38	74S175	135
74810	38	74S182	75
74815	45	74S186	4.25
74820	55	74S201	6.75
74822	55	74S240	2.75
74830	75	74S244	2.85
74837	55	74S251	2.75
74850	65	74S287	2.95
74851	65	74S288	2.95
74854	55	74S290	5.75
74876	65	74S470	9.25
74886	65	74S471	9.50
74891	1.95	74S473	9.50
748132	1.45	74S474	9.50

2708	3.25ea	8 for 2.05ea
2716	5.50 ea	8 for 5.00ea
2732	12.95 ea	4 for 11.00 ea
4116	300NS 2.00ea	8 for 14.00
200NS	2.45ea	4 for 2.00ea
2114	300NS 2.25 ea	4 for 1.90ea
200NS	2.45ea	4 for 2.00ea
2111	450NS 2.90ea	10 for 2.00ea

.95	1103A	.75
2.95	UPD765	18.85
.27	Floppy disk controller	w/ram
4.25	AYS-1013A	
.95	ULN2001	1.95
.95	TMS4400	1.40
1.30	MC4008P	1.50
1.30	MN1026	1.65
1.95	0382A	1.95
1.95	03001	1.95
1.95	03002	1.95

.85	I.C. SOCKETS	
.85	ww	p
.85	10/15.30	10/1.20
.85	10/5.70	10/1.40
1.80	10/8.70	10/1.80
1.15	10/9.70	20/1.20
1.80	10/12.70	22/1.20
1.10	10/13.70	24/1.20
.95	10/14.70	28/1.30/3.00
.25	10/17.70	40/1.30/3.00
.85	3085A	13.50
1.30	w/overwrap	solder

Z-80	CPU's	7.95
Z-80A	CTC	10.50
Z-80A	CPU	10.50
Z-80 002	16-84K	128.00
3085A		13.50
Z901A		7.50
MC6800		9.50


CIRCLE 57 ON FREE INFORMATION CARD

SURPLUS ELECTRONICS CORP.

7294 N.W. 54th Street
Miami, Florida 33166

WHOLESALE/RETAIL
EQUIPMENT/COMPONENTS/WIRE & CABLE/ACCESSORIES

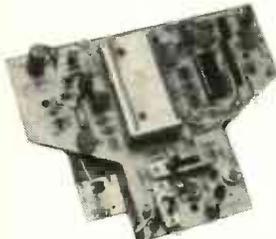Phone: (305) 887-8228
TWX: 810-848-6085
We accept MasterCard and Visa.



"TANK BATTLE" TV GAME

In just a short time and with a few minor parts, the most novice hobbyist can complete this exciting Tank Battle game. Create a fun-filled evening for the whole family. Two independent tanks rumble thru land mine fields, shoot shells and fragment when hit. Four distinct engine sounds are produced for the different speeds. Sounds of gunfire, shell bursts and tank explosions are realistic. Automatic on-screen scoring. Supplied with schematic drawing.

SOLD AS IS
\$9.95 ea.



C.B. SPECIAL

CONVERT THESE TO 10 METER FM


New HY-GAIN printed circuit board assembly with PLL02A chip and 3 crystals. (Squelch pot, volume control and channel switch not included.) Boards sold as is, the way we bought them from the manufacturer. Board dimensions 6" x 6 1/2"

1-9 **\$7.50** 50-99 **\$6.00**
10-49 **\$6.50** 100-UP **\$5.50**

COPPER CLAD BOARD (Double Side)


Size 9.25 x 10.75
Thickness .062
\$2.00 ea.

DIP SWITCH

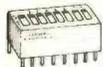

5 POSITION **\$1.00 ea.**
8 POSITION **\$1.50 ea.**
10 POSITION **\$2.00 ea.**
12 POSITION **\$2.50 ea.**

AMP METERS

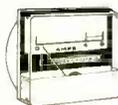

2 1/4" square, no shunt required.
Easy-to-read dial.
Movements: 0-6, 0-10, 0-17
\$2.50 ea.

SPEAKER



3" Diam.,
8 OHM,
5 Watts.

\$2.00 ea.

COAX CONNECTORS

UG-273/U BNC-F/UHF-M **\$2.50**
UG-255/U BNC-M/UHF-F **\$3.00**
UG-146 A/U N-M/UHF-F **\$4.50**
UG-838/U N-F/UHF-M **\$4.50**
UG-175 RG-58 Adapt **\$.20**
UG-176 RG-59 Adapt **\$.20**
UG-1094 BNC-F/Panel **\$1.00**
S0239 **50c**
PL259 **60c**

COAXIAL CABLE

50 OHM-RG 174

\$4.95/100' \$3.00/50'

SCREW DRIVER KIT




Handle stores four blades
2 single slot 5/32" & 3/32"
1 phillips 1 scratch awl
6" long with one blade inserted
\$1.00 ea.

TRIMMER CAP




1.5-20pF
(ARCO PC-4J2)
50c ea.

SUB-MINI 10K POT

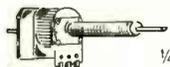

with On-Off
1/4" hole mount,
1/8" D sl aft,
3/4" thread section.
5/\$1.00

POWER TRANSFORMER

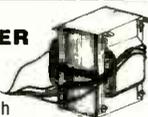

Primary - 115 vac
Secondary - 32 v with
24 v tap at 15 amps
Dim. 4 1/2" h X 3 3/4" w X 4" deep

SOLID GEL BATTERY

6 volt @ 8 a.h. with Charger



\$14.95


Elpower EP 680 may be charged constant voltage or constant current. Battery is self-contained and requires no maintenance. Connections made with quick connect lugs. All plastic case size 5 1/2 h x 2 3/4 w x 4 1/2 l, weight 4 lbs.

TEXAS INSTRUMENT KEYBOARD



Has 3 slide switches, 26 different keys, key pad removable by 4 screws
\$1.95 ea. 5/\$8.00

C & K SWITCHES

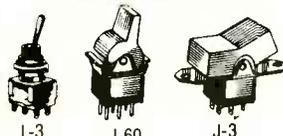

Part # Movement


J-60 7101 SPDT

L-3 7108 SPDT (momentary)

J-3 7201 DPOT (special large rocker)

\$1.00 ea. 6/\$5.00

E. F. JOHNSON "S" METER

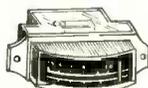

Edge Meter 250 UA, fits in 5/8" x 1 1/8" hole. Black background. Scale 1-20 Top, 0-5 Bottom.

\$1.25 ea. 5/\$5.00

COMPUTER GRADE ELECTROLYTICS

VALUE/MFD	VOLTS	DIAM./LGTH.	PRICE
63,000	@ 15V	3" x 5 1/2"	\$4.00 ea.
10,000	@ 20V	1 1/2" x 5 3/4"	\$3.00 ea.
2,700	@ 25V	1 1/4" x 2 1/4"	\$2.00 ea.
2,900	@ 25V	1 1/4" x 2"	\$2.00 ea.
100,000	@ 30V	3" x 5 1/2"	\$6.00 ea.
39,000	@ 30V	1" x 5 3/4"	\$4.00 ea.
34,800	@ 50V	3" x 5 1/2"	\$3.00 ea.
450	@ 75V	1 1/4" x 2 1/4"	\$2.00 ea.
500	@ 100V	1 1/2" x 3 1/4"	\$2.00 ea.
50	@ 450V	1 1/4" x 2"	\$2.00 ea.

TELEPHONE & TTY INTERFACE MODEM

MFG by Anderson Jacobson
DAA Modem Model DC 230 with A-36 Telephone Coupler



\$69.95

Rated 300 Baud, half or full duplex. DAA level adjustable 0 to 3, 4 to 5, 7 to 10. TTY and DAA outputs brought out to 15 pin Molex connectors. FSK oscillator sends 1070 Hz space and 1270 Hz mark. Receives 2025 Hz space and 2225 Hz mark. Telephone coupler has 4-ft. cord and plug. Size 4 1/4" W x 15 L x 3" Dp. designed to be recessed in desk or panel. Electronics in case, 6 1/2" W x 12 x 2 3/4" Dp. with 8-ft. 3-wire U-ground cord and plug. Operates on 115 vac, 50/60 Hz, 1/2 Amp. Supplied with connection sheet. Removed from equipment, excellent condition, guaranteed.

AXIAL LEAD ELECTROLYTIC CAPACITORS

2 uF @ 15V 12/**\$1.00**
10 uF @ 15V 12/**\$1.00**
20 uF @ 15V 12/**\$1.00**
50 uF @ 15V 12/**\$1.00**
2.2 uF @ 25V 12/**\$1.00**
3.3 uF @ 25V 12/**\$1.00**
1 uF @ 35V 12/**\$1.00**
2 uF @ 150V 12/**\$1.00**
25 uF @ 25V 15/**\$2.00**
3 uF @ 50V 15/**\$2.00**
5 uF @ 50V 15/**\$2.00**
10 uF @ 50V 15/**\$2.00**
250 uF @ 25V 10/**\$2.00**
50 uF @ 75V 10/**\$2.00**

MODEM CABLE ASSEMBLIES


\$5.50 ea.



Conn & Hood	22 AWG # Cond	Length
25 P	14	15'
25 S	10	17'

9 VOLT NiCd RECHARGEABLE BATTERY

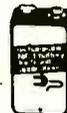NEW. Replaces the popular 9V Transistor Battery.



\$4.75 ea.

MAHOGANY PROJECT BOX


\$1.50 ea.



4 3/8" w x 7 3/8" l x 3/4" to 1 1/2" h

Has a lip for recessed face plate and a felt bottom

POWER SUPPLY

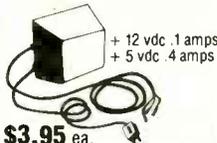

\$3.95 ea.

IC SOCKETS GOLD-PLATED WIRE WRAP

14 pin **40c ea.**

16 pin **45c ea.**



MUFFIN FANS



MFG By Rotron Inc.
3 Blades 4 3/4" Square
USED

110 VAC **\$5.95 ea.**
NEW
230 VAC Model MU3A1
\$12.00 ea.

NEW SPRITE FAN

Mfg. by Rotron Inc.,
Model SU2A5.
115v AC. 19 amps.
(Impedance protected.)
3 1/4" x 3 1/4" x 1 1/4"

\$12.00 ea.

7' POWER CORD HEWLETT PACKARD TYPE



Molded 3 Prong Plug with molded receptacle
Belden 16 AWG

\$3.00 ea.

24-Volt POWER SUPPLY 5.4 AMPS

MFG by ACDC Electronics Inc.
Model OEM 24N5.4-1



Input 105-125 vac 50/60 Hz. Has volt adj and O.L. adj. Output terminals contain + out, + sen, - sen, - out, ac neut, ac line and GND. 13 LBS.

\$45.00

TERMS: All material guaranteed unless otherwise stated. If you are not satisfied with our product, it may be returned within 10 days for a refund (less shipping). Please add \$4.00 for shipping and handling on all orders. COD's accepted for orders totaling \$50 or more. All orders shipped UPS unless otherwise specified. Florida residents please add 4% sales tax. Minimum order, \$15.00. Foreign orders - US funds only, add 20% for shipping and handling.

16K Memory

4116-200ns

8/15.95

ALL MERCHANDISE 100% GUARANTEED!

CALL US FOR VOLUME QUOTES

EPROMS

			Each	8 pcs
1702	256 x 8	(1ns)	4.95	4.50
2708	1024 x 8	(450ns)	2.99	2.75
2758	1024 x 8	(5V) (450ns)	9.95	8.95
TMS2516	2048 x 8	(5V) (450ns)	6.95	5.95
2716	2048 x 8	(5V) (450ns)	5.50	4.95
2716-1	2048 x 8	(5V) (350ns)	9.00	8.50
TMS2716	2048 x 8	(450ns)	9.95	8.95
TMS2532	4096 x 8	(5V) (450ns)	12.95	11.95
2732	4096 x 8	(5V) (450ns) (200ns)		CALL
2764	8192 x 8	(5V) (450ns)		CALL

DYNAMIC RAMS

				100 pcs
4027	4096 x 1	(250ns)	2.50	2.00
4116-120	16,384 x 1	(120ns)	8/29.95	CALL
4116-150	16,384 x 1	(150ns)	8/18.95	1.95
4116-200	16,384 x 1	(200ns)	8/15.95	1.80
4116-300	16,384 x 1	(300ns)	8/14.95	1.75
4164	64,536 x 1	(200ns)		CALL

STATIC RAMS

				100 pcs
2101	256 x 4	(450ns)	1.95	1.85
2102-1	1024 x 1	(450ns)	.89	.85
21L02-4	1024 x 1	(LP) (450ns)	1.29	1.15
21L02-2	1024 x 1	(LP) (250ns)	1.69	1.55
2111	256 x 4	(450ns)	2.99	2.49
2112	256 x 4	(450ns)	2.99	2.79
2114	1024 x 4	(450ns)	8/16.95	1.95
2114L-2	1024 x 4	(LP) (200ns)	8/19.95	2.35
2114L-3	1024 x 4	(LP) (300ns)	8/18.95	2.25
2114L-4	1024 x 4	(LP) (450ns)	8/17.95	2.10
2147	4096 x 1	(55ns)	9.95	CALL
TMS4044-4	4096 x 1	(450ns)	3.49	3.25
TMS4044-3	4096 x 1	(300ns)	3.99	3.75
TMS40L44-2	4096 x 1	(LP) (200ns)	4.49	4.25
TMM2016	2048 x 8	(200ns) (150ns)		CALL
HM6116	2048 x 8	(200ns) (150ns) (120ns)		CALL

LP = LOW POWER

CRYSTALS

32.768 KHZ	3.95
1.0 MHZ	4.95
1.8432	4.95
2.0	3.95
2.097152	3.95
2.4576	3.95
3.2768	3.95
3.579545	3.95
4.0	3.95
5.0	3.95
5.0688	3.95
5.185	3.95
5.7143	3.95
6.5536	3.95
8.0	3.95
10.0	3.95
14.31818	3.95
18.0	3.95
18.432	3.95
20.0	3.95
22.1184	3.95
32.0	3.95

MISC.

AY5-2376	12.50
11C90	13.95
XR2206	4.95
3242	7.95
3480	9.00
MC4024	3.95
MC4044	4.50
7103	9.50
7106	9.95
7107	12.95
76477	3.95
8038	3.95
95H90	7.99
9602	1.50

DISC CONTROLLERS

1771	24.95
1791	36.95
1793	44.95
1797	54.95

UARTS

AY3-1014	6.95
AY5-1013	3.95
TR1602	4.95
IM6402	7.95

INTERFACE

8T26	1.69
8T28	2.49
8T95	.99
8T96	.99
8T97	.99
8T98	.99
DM8131	2.95
DS8836	1.29

CLOCK CIRCUITS

MM5369	3.95
MM5375	3.95
MMS5832	7.45
7207	7.50
7208	15.95

CONVERTERS

MC1408 L8	4.95
DAC-0800	4.95
ADC-0804	4.95

February Specials

Z-80A-CPU	6.00
Z-80A-PIO	6.00
8214	2.95
8216	1.50
6800	4.95
6810	3.95

TMS 40L44-20

4096 x 1 low power 200ns RAMS

By Texas Instruments - not equivalent part number made by another manufacturer as sold by others:

4.49 each 125.00/32 pcs.
Specials end February 28, 1982
Please state "February Specials" when ordering

800-538-5000

800-662-6279

(CALIFORNIA RESIDENTS)

CALL JDR BEFORE YOU BUY!
WE WILL BEAT ANY COMPETITORS' PRICES

6502

6502	6.95
6502-A	12.95
6504	6.95
6505	8.95
6507	9.95
6520	4.35
6522	9.95
6532	14.95
6551	11.85

Z80

Z80-CPU	8.95
Z80A-CPU	6.00
Z80-PIO	6.50
Z80A-PIO	6.00
Z80-CTC	5.95
Z80A-CTC	8.65
Z80-DART	15.25
Z80A-DART	18.75
Z80-DMA	17.50
Z80A-DMA	27.50
Z80-S10/0	23.95
Z80A-S10/0	28.95
Z80-S10/1	23.95
Z80A-S10/1	28.95
Z80-S10/2	23.95
Z80A-S10/2	28.95
Z80-S10/09	17.95
Z80A-S10/9	22.95

Z80B-CPU	18.95
Z80B-CTC	17.95
Z80B-PIO	17.95

Z8671	39.95
Z6132	34.95

CMOS

74C00	.35	74C374	2.75	4019	.45	4098	2.49
74C02	.35	74C901	.80	4020	.95	4099	1.95
74C04	.35	74C902	.85	4021	.95	14409	12.95
74C08	.35	74C903	.85	4022	1.15	14410	12.95
74C10	.35	74C905	10.95	4023	.35	14411	11.95
74C14	1.50	74C906	.95	4024	.75	14412	12.95
74C20	.35	74C907	1.00	4025	.35	14419	4.95
74C30	.35	74C908	2.00	4026	1.65	4502	.95
74C32	.50	74C909	2.75	4027	.65	4503	.65
74C42	1.75	74C910	9.95	4028	.80	4508	1.95
74C48	2.10	74C911	10.00	4029	.95	4510	.95
74C73	.65	74C912	10.00	4030	.45	4511	.95
74C74	.85	74C914	1.95	4034	2.95	4512	.95
74C76	.80	74C915	2.00	4035	.85	4514	1.25
74C83	1.95	74C918	2.75	4040	.95	4515	2.25
74C85	1.95	74C920	17.95	4041	1.25	4516	1.55
74C86	.95	74C921	15.95	4042	.75	4518	1.25
74C89	4.50	74C922	5.95	4043	.85	4519	1.25
74C90	1.75	74C923	5.95	4044	.85	4520	1.25
74C93	1.75	74C925	6.75	4046	.95	4522	1.25
74C95	1.75	74C926	7.95	4047	.95	4526	1.25
74C107	1.00	74C927	7.95	4049	.55	4527	1.95
74C150	5.75	74C928	7.95	4050	.55	4528	1.25
74C151	2.25	74C929	19.95	4051	.95	4531	.95
74C154	3.25	74C930	19.95	4053	.95	4532	1.95
74C157	1.75	4000	.35	4060	1.45	4538	1.95
74C160	2.00	4001	.35	4066	.75	4539	1.95
74C161	2.00	4002	.25	4068	.40	4543	2.70
74C162	2.00	4006	.95	4069	.35	4555	.95
76C163	2.00	4007	.29	4070	.35	4556	.95
74C164	2.00	4008	.95	4071	.30	4581	1.95
74C165	2.00	4009	.45	4072	.30	4582	1.95
74C173	2.00	4010	.45	4073	.30	4584	.95
74C174	2.25	4011	.35	4075	.30	4585	.95
74C175	2.25	4012	.25	4076	.95	4702	12.95
74C192	2.25	4013	.45	4078	.30	4724	1.50
74C193	2.25	4014	.95	4081	.30	80C07	.95
74C195	2.25	4015	.95	4082	.30	80C95	.85
74C200	5.75	4016	.45	4085	.95	80C96	.95
74C221	2.25	4017	1.15	4086	.95	80C97	.95
74C373	2.75	4018	.95	4093	.95	80C98	1.20

HOURS: Mon.-Fri., 9 to 5; Sat., 11 to 3



JDR MICRODEVICES, INC.

1224 So. Bascom Ave.

San Jose, CA 95128

800-538-5000 • 800-662-6279 (CA)

(408) 995-5430 • Telex 171-110

TERMS: For shipping include \$2.00 for UPS ground, \$3.00 for UPS Blue Label air. \$10.00 minimum order. Bay Area residents add 6 1/2 % sales tax. California residents add 6 % sales tax. We reserve the right to limit quantities and substitute manufacturer. Prices subject to change without notice. Send SASE for complete list.

CIRCLE 53 ON FREE INFORMATION CARD

2716 EPROMS 450NS (5V)

8/4.95 ea.

ALL MERCHANDISE 100% GUARANTEED!

CALL US FOR VOLUME QUOTES

8000

8035	16.95
8039	19.95
8080A	3.95
8085	12.95
8085A-2	16.95
8086	99.95
8088	39.95
8155	11.95
8156	11.95
8185	29.95
8185-2	39.95
8741	39.95
8748	29.95
8755	44.95

8200

8202	45.00
8205	3.50
8212	1.85
8214	3.85
8216	1.80
8224	2.50
8226	1.80
8228	4.90
8237	19.95
8238	4.95
8239	4.85
8243	4.45
8250	14.95
8251	4.75
8253	9.25
8253.5	9.85
8255	4.75
8255.5	5.25
8257	8.75
8259	6.90
8272	39.95
8275	29.95
8279	9.50
8279.5	10.50
8282	6.65
8283	6.65
8284	5.70
8286	6.65
8287	6.50
8288	25.00
8289	49.95

TV CIRCUITS

MC1330	1.89
MC1350	1.29
MC1358	1.79
LM380	1.29
LM386	1.50
LM565	.99
LM741	.29
LM1310	2.90
LM1800	2.99
LM1889	1.49



APPLE FAN \$69.00

- EXTRA PLUG-IN CARDS CAN CAUSE YOUR APPLE TO OVERHEAT
- ULTRA-QUIET APPLE FAN DRAWS COOL AIR THROUGH YOUR COMPUTER
- ELIMINATES DOWN TIME
- SAVES REPAIR CHARGES
- INCREASES RELIABILITY
- CLIPS ON — NO HOLES OR SCREWS
- COLOF MATCHES APPLE
- LONG LIFE LOW NOISE MOTOR



*APPLE IS A TRADEMARK OF APPLE COMPUTER INC.

IC SOCKETS

	1-99	100
8 pin ST	.13	.11
14 pin ST	.15	.12
16 pin ST	.17	.13
18 pin ST	.20	.18
20 pin ST	.29	.27
22 pin ST	.30	.27
24 pin ST	.30	.27
28 pin ST	.40	.32
40 pin ST	.49	.39
ST = SOLDERTAIL		
8 pin WW	.59	.49
14 pin WW	.69	.52
16 pin WW	.69	.58
18 pin WW	.99	.90
20 pin WW	1.09	.98
22 pin WW	1.39	1.28
24 pin WW	1.49	1.35
28 pin WW	1.69	1.49
40 pin WW	1.99	1.80
WW = WIREWRAP		

CONNECTORS

RS232 MALE	3.25
RS232 FEMALE	3.75
RS232 HOOD	1.25
S-100 ST	3.95
S-100 WW	4.95

DIP SWITCHES

4 POSITION	.85
5 POSITION	.90
6 POSITION	.90
7 POSITION	.95
8 POSITION	.95

6800

6800	5.70
6802	10.95
6808	9.95
6809	24.95
6809E	29.95
6810	4.60
6820	4.95
6821	4.95
6828	9.95
6834	16.95
6840	14.95
6843	42.95
6844	44.95
6845	16.95
6847	15.95
6850	4.75
6852	5.75
6860	10.95
6862	11.95
6875	6.95
6880	2.95
68800	10.95
68821	12.95
68850	12.95

EPROM ERASERS

PE-14	78.50
PE-14T (with timer)	108.50
PE-24T (with timer)	154.50

ALL ARE HIGH QUALITY UNITS ENCLOSED IN A BLACK ANODIZED ALUMINUM ENCLOSURE.

OUR AD MAY BE IMITATED BUT OUR SERVICE CAN NEVER BE DUPLICATED.

VOLTAGE REG's

7805T	.79	7905T	.89
7808T	.99	7912T	.89
7812T	.79	7915T	1.19
7815T	.99	7924T	1.19
7824T	.99		
7805K	1.39	7905K	1.49
7812K	1.39	7912K	1.49
7815K	1.39	7915K	.79
7815K	.69	7912K	.79
7812K	.69	7915K	.79
7815K	.69		
LM309K	1.49	LM317K	3.95
LM317T	1.95	LM323K	4.95
		LM337K	3.95

T = TO-220 K = TO-3 L = TO-92

LINEAR

LM301V	.34
LM308V	.98
LM309K	1.49
LM311	.64
LM317T	1.95
LM317K	3.95
LM318	1.49
LM323K	4.95
LM324	.59
LM337K	3.95
LM339	.99
LM377	2.29
LM380	1.29
LM386V	1.50
LM555V	.39
LM556	.69
LM565	.99
LM566V	1.49
LM567V	1.29
LM723	.49
LM733	.98
LM741V	.29
LM747	.79
LM748V	.59
LM1310	2.90
MC1330V	1.89
MC1350V	1.29
MC1358V	1.79
LM1414	1.59
LM1458V	.69
LM1488	.99
LM1489	.99
LM1800	2.99
LM1889	2.49
LM3900	.59
LM3909V	.98
LM3914	3.95
LM3915	3.95
LM3916	3.95
75451V	.39
75452V	.39
75453V	.39

7400 SERIES

7400	.19	7451	.23	74136	.50	74186	18.50
7401	.19	7453	.23	74141	.65	74190	1.15
7402	.19	7454	.23	74142	2.95	74191	1.15
7403	.19	7460	.23	74143	2.95	74192	.79
7404	.19	7470	.35	74144	2.95	74193	.79
7405	.22	7472	.29	74145	.60	74194	.85
7406	.22	7473	.34	74147	1.75	74195	.85
7407	.22	7474	.35	74148	1.20	74196	.79
7408	.24	7475	.49	74150	1.35	74197	.75
7409	.19	7476	.35	74151	.65	74198	1.35
7410	.19	7480	.59	74152	.65	74199	1.35
7411	.25	7481	1.10	74153	.55	74221	1.35
7412	.30	7482	.95	74154	1.40	74246	1.35
7413	.35	7483	.50	74155	.75	74247	1.25
7414	.55	7485	.65	74156	.65	74248	1.85
7416	.25	7486	.35	74157	.55	74249	1.95
7417	.25	7489	4.95	74159	1.65	74251	.75
7420	.19	7490	.35	74160	.85	74259	2.25
7421	.35	7491	.40	74161	.70	74265	1.35
7422	.29	7492	.50	74162	.85	74273	1.95
7423	.29	7493	.49	74163	.85	74276	1.25
7425	.29	7494	.65	74164	.85	74279	.75
7426	.29	7495	.55	74165	.85	74283	2.00
7427	.29	7496	.70	74166	1.00	74284	3.75
7428	.45	7497	2.75	74167	2.95	74285	3.75
7430	.19	74100	1.00	74170	1.65	74290	.95
7432	.29	74107	.30	74172	5.95	74293	.75
7433	.45	74109	.45	74173	.75	74298	.85
7437	.29	74110	.45	74174	.89	74351	2.25
7438	.29	74111	.55	74175	.89	74365	.65
7440	.19	74116	1.55	74176	.89	74368	.65
7442	.49	74120	1.20	74177	.75	74367	.65
7443	.35	74121	.29	74178	1.15	74368	.65
7444	.39	74122	.45	74179	1.75	74376	2.20
7445	.39	74123	.55	74180	.75	74390	1.75
7446	.59	74125	.45	74181	2.25	74393	1.35
7447	.39	74126	.45	74182	.75	74425	3.15
7448	.39	74128	.55	74184	2.00	74426	.85
7450	.19	74132	.45	74185	2.00	74490	2.55

74S00 SERIES

74S00	.44	74S74	.69	74S163	3.75	74S257	1.39
74S02	.48	74S85	2.39	74S168	4.65	74S258	1.49
74S03	.48	74S86	1.44	74S169	5.44	74S260	1.83
74S04	.79	74S112	1.59	74S174	1.09	74S274	19.95
74S05	.79	74S113	1.98	74S175	1.09	74S275	19.95
74S08	.48	74S114	1.50	74S181	4.47	74S280	2.90
74S09	.98	74S124	2.77	74S182	2.95	74S287	4.75
74S10	.69	74S132	1.24	74S188	3.95	74S288	4.45
74S11	.88	74S133	.98	74S189	14.95	74S289	6.98
74S15	.70	74S134	.69	74S194	2.95	74S301	6.95
74S20	.68	74S135	1.48	74S195	1.89	74S373	3.45
74S22	.98	74S138	1.08	74S196	4.90	74S374	3.45
74S30	.48	74S139	1.25	74S197	4.25	74S381	7.95
74S32	.98	74S140	1.45	74S201	14.95	74S387	5.75
74S37	1.87	74S151	1.19	74S225	8.95	74S412	2.98
74S38	1.68	74S153	1.19	74S240	3.98	74S471	9.95
74S40	.44	74S157	1.19	74S241	3.75	74S472	16.85
74S51	.78	74S158	1.45	74S244	3.98	74S474	17.85
74S64	.79	74S161	2.85	74S251	1.90	74S482	15.60
74S65	1.25	74S162	3.70	74S253	7.45	74S570	7.80
						74S571	7.80

HOURS: Mon. - Fri. 9 to 5; Sat. 11 to 3

VISIT OUR RETAIL STORE!



JDR MICRODEVICES, INC.
1224 S. Bascom Ave.
San Jose, CA 95128
800-538-5000 • 800-662-6279 (CA)
(408) 995-5430 • Telex 171-110

TERMS: For shipping include \$2.00 for UPS Ground, \$3.00 for UPS Blue Label Air. \$10.00 minimum order. Bay Area residents add 6 1/2% sales tax. California residents add 6% sales tax. We reserve the right to limit quantities and substitute manufacturer. Prices subject to change without notice. Send SASE for complete list.

SCR SUPER-BUYS

① **FREE SCRAMBLER PLANS** plus a brochure describing our new UHF-VHF Conversion Kit are yours just by sending us your name, address and a 20c stamp. **FREE**

② **9-INCH BLACK AND WHITE CRT MONITOR.** Ideal for microcomputer or security use. 22 transistors. Designed for excellent resolution. Frequency response — 12 MHz. Continuous DC restoration for superior contrast. **\$165.00 ea.**

③ **UHF-VHF CONVERSION KIT.** Complete with PC board; all required components; cabinet with speaker; and comprehensive brochure incl. schematic, board layout, mounting and hook-up diagrams, parts list and assembly and set-up instructions. All parts are industrial prime quality. **\$119.95 ea.**

④ **NEW ZENITH ZVM-121 HIGH-LEGIBILITY CRT MONITOR.** Features 12" green phosphor CRT, with 15 MHz Bandwidth. 40 or 80 character widths are operator switch-selectable. Fully compatible with 80-column Apple cards, etc. **\$117.95 ea.**

⑤ **MITSUMI VARACTOR-TUNER.** Channels 15-82. Modified for kit use. **\$300 ea.**

Standard versions. **\$280 ea.**

SCR ELECTRONICS INC. (714) 527-2554 • (213) 596-7553
9533 Valley View Street, Cypress, CA 90630

\$10.00 MIN. ORDER HANDLING/SHIPPING \$5.00
Pay by CHECK, M.O., VISA, M/C, C.O.D.
UPS ANYWHERE IN CONTINENTAL U.S.
For Free Buyers Guide Catalog Circle No. 79

CIRCLE 79 ON FREE INFORMATION CARD

ELECTRONIC COMPONENTS

Wholesale - Retail - O.E.M.
1 Amp TO-220 Voltage Regulators

PART #	1-24	25-99	100-499	500 +
7805 (LM340T-5)	89	.75	.65	Call
7812 (LM340T-12)	89	.75	.65	for
7815 (LM340T-15)	89	.75	.65	Quote
7818 (LM340T-18)	89	.75	.65	

5% Carbon Film Resistors
We stock all 5% standard values between 1 ohm and 1 Meg ohm.

1/4 watt	
Package of 5	.20
Package of 100 (one value)	1.65
Package of 1000 (one value)	12.00
1/2 watt	
Package of 5	.25
Package of 100 (one value)	1.75
Package of 1000 (one value)	15.00

Sampler box consisting of 5 each of all 145 standard 5% values between 1 ohm and 1 Meg Ohm

1/4 watt sampler box 22.00
1/2 watt sampler box 27.00
- \$10.00 minimum order -

Send for our full line catalog of IC's, sockets, capacitors, trim pots, diodes, bridges, LEDs, Enclosures, switches, crystals, etc.

WESTLAND ELECTRONICS, INC.
37387 Ford Rd., Westland, MI 48185
- Toll Free Order Line -
1-800-521-0664

CIRCLE 81 ON FREE INFORMATION CARD

CPU'S & SUPPORT CHIPS

3080A	3.75	8226	2.75
3080B	7.50	8229	2.75
AM92201	35.00	8235	6.95
8212	2.25	8236 (RAM517)	7.50
8211	3.80	280A S10	12.95
8218	2.90	8237	7.10
8224	3.25	280A P10	9.95
MM537	9.95	TMS 9817 N1	16.95

RAM's

Part #	Price	Part #	Price
82K (20K NS1)	14.00	2708	3.25
2116-3	2.75	2710 + 5V	6.25
4116-3	1.75	2732	16.95
4162	2.50	1702A	4.95
2112-3	.80	2802	16.95
2102-4	2.80	82323	2.50
TMS 3420	1.75	825112	2.50
MK4027.3	3.50	825115	2.50
MK4026.11	2.85	825120	1.50
TMS4045	4.50	825129	1.90
MS4050N	3.95	825130	1.50
2101.1	2.45	825131	1.50
MM5270	1.45	825181	3.00
MK5008	1.95	8256174 (181)	1.25
IM7001	4.95	AM9218C	2.95
5101E	2.95	8256174 (181)	1.25
2111AL	2.45		

UART's

AYS-1013	3.75	M8868A	8.95
TR1802B	8.95	CDM3017	3.75
PT1482B	3.25	AY38700	2.25

INTERFACE & DRIVERS

FD1771	19.95		
1466	1.10	MM1402	1.75
8130	2.50	MM1403	1.75
8830	2.50	MM1404	1.75
8831	2.50	MM5013	2.50
8834	2.00	MM5016	2.50
8837	2.00	MM5056	2.50
8838	2.00	MM5056	2.50
87380	2.00	MM5057	2.50
MM5271	4.50	MM5058	2.50
MM5369	2.50	MM5060	2.50

14 PIN HEADERS	3/51.00
16 PIN HEADERS	.40
24 PIN HEADERS	.75
40 PIN HEADERS	1.10
50 PIN EDGEBOARD CONN.	3.95
25 PIN EDGEBOARD CONN.	2.50
50 PIN RIGHT ANGLE CONN.	3.95
20 PIN RIGHT ANGLE CONN.	2.25

50 PIN RUBBER CONNECTORS	43.25
40 PIN RUBBER CABLE CONN.	8.25
20 PIN RUBBER CABLE CONN.	8.25
20 PIN RUBBER CABLE CONN.	11.50

PRINTED CIRCUIT BOARD
4" x 6" DOUBLE SIDED EPOXY BOARD 1/16" THICK
850 ea. \$9.50

EPOXY GLASS VECTOR BOARD

1/16" thick with 1/10" spacing
4 1/2" x 6 1/2" \$1.95

DAT'L'S DAC-08C

8 bit DAC — \$ 4.95

14 PIN 4" LONG	\$2.00
16 PIN 12" LONG	\$2.50

REDICON SAD 1024 ANALOG DELAY LINE \$10.95

74500	30	74574	70	745158	1.25
74502	30	74586	60	745159	1.25
74503	30	74588	1.90	745169	1.75
74504	40	74512	1.40	745174	1.40
74505	45	74533	1.40	745175	1.40
74508	40	74535	1.50	745194	1.10
74510	30	74536	1.50	745291	1.50
74511	35	74538	1.10	745298	1.60
74515	40	74540	1.60	745299	1.50
74520	40	745153	1.10	745299	1.50
74530	40	745151	1.25	745301	2.25
74532	40	745157	1.25	745302	2.50

7 WATT LD 65 LASER DIODE (IR) \$8.95

25 watt Infra Red Pulse (SG 2006 equiv.)
Laser Diode (Spec sheet included) \$24.95

2N3820 P FET	\$.45
2N5457 N FET	\$.45
2N2646 UJT	\$.45
ER 500 TRIGGER DIODES	4/51.00
2N 6028 PROG. UJT	\$.65

DISC CAPACITORS

.1UF 16V	10/51.00	100/98.00
01UF 35V	16/31.00	100/35.00

IN4148 (IN914) 15/1.00

TANTALUM CAPACITORS

47UF 35V	5/91.00	22UF 10V	— \$.40
68UF 35V	5/91.00	15UF 16V	3/81.00
1UF 35V	5/91.00	30UF 6V	5/81.00
2.2UF 20V	5/91.00	33UF 20V	\$.60
3.3UF 20V	4/81.00	47UF 20V	\$.85
4.7UF 35V	4/81.00	68UF 10V	\$1.00
6.8UF 35V	3/81.00	120UF 6V	\$.75
		200UF 20V	\$1.75

SANKEN AUDIO POWER AMPS

Si 1020 G 20 WATTS \$12.50
Si 1050 G 50 WATTS \$27.50
200 PRV 1A LASCR .95

RS232 CONNECTORS

DB 25P male	\$2.75
DB 25S female	3.75
HOODS	1.50

POSTAGE ADD 10% FOR ORDERS UNDER \$20.00
RATES ADD 5% FOR ORDERS BETWEEN \$20.00 AND \$50.00
ADD 3% FOR ORDERS ABOVE \$50.00

C/MOS

4001	20	4037	—	4081	20	74C74	—	50
4002	20	4038	—	4082	20	74C75	—	50
4006	—	4029	—	4083	—	74C76	—	50
4007	27	4032	—	4084	—	74C77	—	50
4008	—	4034	2.25	4501	—	74C78	—	50
4009	—	4036	—	4510	—	74C79	—	50
4010	—	4040	—	4511	—	74C80	—	50
4011	20	4042	—	4514	1.40	74C151	—	75
4012	20	4043	—	4515	1.50	74C152	—	75
4013	20	4044	—	4516	—	74C150	—	120
4014	—	4046	—	4518	1.25	74C151	—	115
4015	—	4047	—	4520	—	74C153	—	120
4016	—	4048	—	4521	—	74C154	—	120
4017	80	4050	—	4740	2.75	74C173	—	120
4018	—	4052	—	74C08	27	74C174	—	130
4019	—	4054	—	74C09	27	74C175	—	130
4020	—	4056	—	74C10	27	74C176	—	130
4021	—	4058	—	74C11	27	74C177	—	130
4022	80	4060	—	74C12	27	74C178	—	130
4023	20	4072	—	74C13	27	74C179	—	130
4024	25	4076	—	74C14	27	74C180	—	130
4025	—	4077	—					

TRANSISTOR SPECIALS

2N3007 PNP GE TO 5	1.40
2N3004 PNP GE TO 5	3/81.00
HEP 6801A — PNP GE TO 3	1.85
2N2907 NPN SWITCHEING TO 9	1.15
2N2908 NPN SWITCHEING TO 9	1.15
2N2909 NPN SWITCHEING TO 9	1.15
2N3000 NPN SWITCHEING TO 9	1.15

TTLIC SERIES

7400	—	17	7474	—	60
------	---	----	------	---	----



COMPONENT TESTER
 • Easy-to-use
 • Safety Class II
 • Check Semiconductors in circuit
 • Check Electronic Components
 HZ65 for use with all HAMEG scopes . . . \$58.00



4-CHANNEL AMPLIFIER
 • DC-50 MHz Bandwidth
 • AC/DC Operation
 • Algebraic Addition
 • Compact Shape and Easy-to-use
 HZ64 \$451.00



10 MHz SINGLE TRACE
 • DC-10 MHz
 • LPS-Triggering
 • Component Tester Built-in
 • Timebase


The HM307 is a compact light weight single trace oscilloscope which has been specially designed to meet the requirements of both the service technician and advanced amateur. A principal feature of the HM307 is the built-in component tester. It allows both passive and active components to be tested while still in-circuit for more cost effective servicing.
 HM307 \$405.00

HAMEG Oscilloscopes to meet every need



20 MHz DUAL TRACE
 • Overscanning • LPS Trig to 40 MHz
 • Delayed Sweep • DC-20 MHz

Internal stabilized power supplies. Both vertical channels incorporate a variable gain control which increases the gain to 2 mV/cm. Channels can be Added or Subtracted. A special feature of the HM412 is the vertical Overscanning facility, location of a "lost" trace is indicated on two LEDs. Both the trigger and delayed conditions are indicated by LEDs. These facilities coupled with graticule illumination, Z Modulation, and a square-wave calibrator make the HM412 a very versatile instrument.
 HM412 with sweep delay \$880.00
 HM412N with delay and long persis. \$985.00

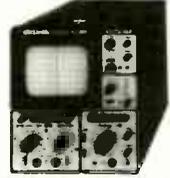

70 MHz DUAL TRACE
 • DC-70MHz • Sweep Delay 0.1µs-1s
 • Sens. 2mV/cm • Graticule 8x10cm

General-purpose scope designed for both laboratory and field service. The HM705 triggers even complex signals beyond 100MHz. Two non-synchronous signals, or a composite signal with a non-synchronous component, and also aperiodic events can likewise be triggered. Single-shot operation is also possible. The wide sweep range from 5ns/cm (including x10 magnification) to 2.5s/cm gives an excellent resolution. These features and others make the HM705 an instrument of great flexibility in all fields.
 HM705 with delay \$885.00
 HM705N with delay and long persis. \$1000.00



20 MHz DUAL TRACE
 • DC-20 MHz • 8 x 10cm Display
 • Triggering up to 30 MHz

The high performance of the HM203 has been achieved by the optimum use of both discrete semiconductor and integrated circuit technology. Quality and long term reliability are assured through the use of high quality components throughout this instrument. Each unit is supplied with a comprehensive manual which includes operating and servicing instructions, circuit diagrams, and PCB layouts.
 HM203 \$580.00
 HM203N \$600.00

ANCRONA P.O. Box 2208R, Culver City, CA 90230

★ **SPECIAL COUPON** ★

Bring this COUPON into one of our stores or mail to our Mail Order address shown below to receive the SPECIAL PRICES listed on these two pages.
 Offer EXPIRES on March 31, 1982

NAME _____
 ADDRESS _____
 CITY _____ STATE _____
 ZIP _____ PHONE _____
 Coupons accepted only with full name and address filled in.

MINIATURE DOT MATRIX IMPACT PRINTER




The Unique New Printer That Gives You All These Exciting Features.

- Low Cost
- Disposable printing head
- Simple interface
- Handles any type font
- Needs only one 12-volt DC power supply
- Uses standard 2 1/4" adding machine tape or carbonless paper
- 21-column printing at 25 lines per second
- Easy to install and maintain

Model DP-822 **\$80.00**

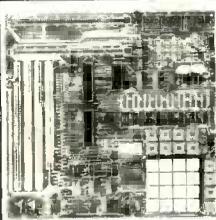Dot Matrix Printer Control/Drive Card
 Model DP-822-08B **\$125.00**



SO SYSTEMS Z-80 STARTER KIT
 A COMPLETE MICRO-COMPUTER ON A BOARD
 Regular \$401.00
 ★ SPECIAL WITH COUPON ★
\$368.00

- FEATURES**
- Z-80 CPU with 158 instructions
 - On-Board Keyboard and Display
 - On-Board PROM Programmer for PROMS (2716, 2758, TI2516)
 - Kansas City Standard Cassette Int.
 - Simple Key Controlled Audio Cassette Load and Dump
 - Expansion Provision for Mounting Two S-100 Connectors
 - Wire Wrap Area for Custom Circuitry
 - Single Step through RAM or PROM
 - Memory Examine and Change
 - Port Examine and Change
 - Z-80 CPU Register and Change
 - 2K Byte ZBUG Monitor in ROM
 - 1K Bytes of RAM (expandable to 2K)
 - 4 Channel Hardware Counter/Timer
 - Two Bi-Directional 8-Bit I/O Ports
 - Up to 5 Programmable Breakpoints
 - Switch Selectable PROM or Monitor Restart
 - Vectored Interrupts provided by Z-80-CTC and Z-80-P10

Full ASCII Encoded Keyboards



RCA 128-Character, 58-Key Typewriter Format for Alphabetic Entry
 VP-601 8-bit parallel output . . . \$69.00
 VP-606 Async serial output . . . \$99.00
58-Key Typewriter Format Plus Calculator-Type Keypad for Fast Numeric Entry
 VP-611 8-bit parallel output . . . \$89.00
 VP-616 Asynchronous serial output . . . \$119.00
 Operation From Single +5 Volt Supply


HITACHI SCOPES

15MHz SINGLE TRACE 1 mV SENS 5" CRT with PROBE V-151B \$570.00	15MHz DUAL TRACE 1 mV SENS 5" CRT with 2 PROBES V-152B \$735.00	30MHz SINGLE TRACE 1 mV SENS 5" PDA CRT SIGNAL DELAY with X-10 PROBE V-301 \$745.00
---	--	---

30MHz DUAL TRACE 1 mV SENS 5" PDA CRT SIGNAL DELAY with 2 X-10 PROBES V-302B \$995.00	
---	--

SPECIAL 20% DISCOUNT WITH COUPON	50MHz 3rd TRACE TRIGGER VIEW 6" SQ CRT 5 ns/div — 1 mV/div V-550B CALL FOR PRICE	100MHz 3rd & 4th TRACE TRIGGER VIEW 6" SQ CRT 5 ns/div — 5mV/div V-1050 CALL FOR PRICE
---	---	---

Universal Oscilloscope

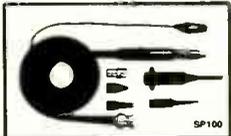


Probe \$36.00
 ★ SPECIAL WITH COUPON ★
 ★ \$29.50 ★

SWITCHABLE X1 and X10 Attenuation Factor
KEY ADDITIONAL FEATURES: • 100MHz bandwidth • Heavy duty tip • Break resistant center conductor • Slender, flexible cable • 6ft. cable length • Wide compensation range • Fits all scopes
 • Ground reference can be activated at tip • Includes SPRUNG HOOK, I.C. TIP, BNC ADAPTOR, INSULATING TIP and TRIMMER TOOL ACCESSORIES.

ANCRONA
 P.O. BOX 2208R, CULVER CITY, CA 90230
 STORES DO NOT ACCEPT MAIL ORDERS
MAIL ORDER
PHONE ORDERS: (213) 641-4064

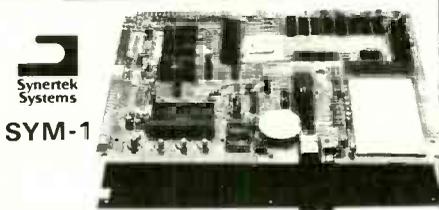Minimum Order \$10.00. Add \$2.00 to cover postage and handling. Master Charge and VISA welcomed. Please include your-charge card number, interbank number and expiration date. Some items are subject to prior sale. Not responsible for typos. Store pricing may vary from Mail Order pricing. We reserve the right to substitute manufacturer.



SYM AND KTM PRODUCTS

SYM-1 Single Board Computer with 6502 Processor and Firmware	\$239.00
SM100 OEM Version of SYM-1 without Keyboard/Display/Drivers/Tone Generator/Manuals	229.00
SYM-1/68 Single Board Computer with 6800 Processor and Firmware	329.00
SYM-1/69 Single Board Computer with 6809 Processor and Firmware	359.00
KTM-2 40 Column Keyboard Terminal Module for CRT/TV	329.00
KTM-2/80 80 Column Version of KTM-2	399.00
KTM-3 40 Column Expanded KTM with Power Supply and Case. Requires only CRT Monitor	389.00
KTM-3/80 80 Column Version of KTM-3	449.00
SRM-1 1K Bytes Static RAM Kit	42.00
SRM-3 3K Bytes Static RAM Kit	90.00
PEX-1 SYM Port Expansion and Connector Kit	60.00
CAS-1 Audio Cassette Recorder with Tape Counter and Tone Control	79.00
MOD-68 Adapter Board for SYM-1 with 6809 Processor and Firmware	119.00
MOD-69 Adapter Board for SYM-1 with 6809 Processor and Firmware	149.00
MON-1-1 Revised 4K Bytes SUPERMON SYM Monitor	15.00
BAS-1 8K Basic Plug-in ROMs for SYM-1	95.00
EPS-1 SYM Diagnostic Test Program in 2716 EPROM	75.00
RAE-1 Resident Assembler/Editor ROM-8K (1 Chip Version)	159.00
RAE-1/2 Resident Assembler/Editor ROM-8K (2 Chip Version)	95.00

MBC SINGLE BOARD COMPUTERS

MBC01A2 Second Source SBC Micromodule for Motorola MM01A2	400.00
MBC01A2-1 MBC01A2 with Four Connectors	440.00
MBC010-65 Single Board Computer with 6500 Series Microprocessor	369.00
MBC010-68 Single Board Computer with 6800 Series Microprocessor	369.00
MBC020-65 SBC 6500 Series CPU with Complete Video Capability	495.00
MBC020-68 SBC 8000 Series CPU with Complete Video Capability	495.00

Z-80 SERIES MICROPROCESSOR IC's

2.5 MHz Z-80-DART \$14.30	4.0 MHz Z-80A-DART \$15.50
Z-80-CPU \$7.10	Z-80-S10/0 20.10
Z-80-CTC 5.90	Z-80-S10/9 15.70
Z-80-P10 5.90	Z80-DMA 21.50
	Z-80A-CTC 6.35
	Z-80A-S10/9 15.70
	Z-80A-P10 6.35
	Z-80A-DMA 22.70

★ SPECIAL 20% DISCOUNT WITH COUPON ★

6500 SERIES MICROPROCESSOR IC's

A = (2 MHz)	B = (3 MHz)	C = (4 MHz)
P6502 \$ 8.82	P6506A \$8.82	P6520A \$3.74
P6502A 9.66	P6507 8.09	P6820 3.40
P6502B 15.02	P6507A 8.82	P68820 3.74
P6502C 21.00	P6512 8.82	P6521 4.90
P6503 8.09	P6512A 9.66	P6521A 5.34
P6503A 8.82	P6513 8.09	P6821 4.90
P6504 8.09	P6513A 8.82	P68821 5.34
P6504A 8.82	P6514 8.09	P6522 8.40
P6505 8.09	P6514A 8.82	P6522A 11.24
P6505A 8.82	P6515 8.09	P6530-004 15.84
P6506 8.09	P6520 3.40	P1793-02 40.00

★ SPECIAL 20% DISCOUNT WITH COUPON ★

ATLANTA 3330 Piedmont Rd. N.E. Atlanta, GA 30305 (404) 261-7100	CULVER CITY 11080 Jefferson Blvd. Culver City, CA 90230 (213) 390-3595	HOUSTON 2649 Richmond Houston, TX 77098 (713) 529-3489	PORTLAND 1125 N.E. 82nd Ave. Portland, OR 97220 (503) 257-9464	SANTA ANA 1300 E. Edinger Ave. Santa Ana, CA 92705 (714) 547-8424	SUNNYVALE 1054 E. El Camino Real Sunnyvale, CA 94087 (408) 243-4121	TUCSON 4518 E. Broadway Tucson, AZ 85711 (602) 881-2348
---	--	--	--	---	---	---

CIRCLE 54 ON FREE INFORMATION CARD

MICROPROCESSORS			MEMORY			INTERFACE		
Z-80	\$9.20	6809 \$23.50	2101 (256x4)	\$2.70	4116 (160Ns)	\$4.25		
Z-80A	9.50	8080A 4.50	2102 (1024x1)	3.20	4116 (200Ns)	4.50		
6502	7.84	8085A 5.70	2112 (256x4)	2.80	4116 (300Ns)	4.10		
6800	7.50	8035 5.50	2114	3.20	4164 (200Ns)	25.40		
6802	11.48	8086 9.50	2114L-2	4.50	8155	7.40		
8080A SUPPORT DEVICES 2147 (4Kx1) 6.64								
6520	\$6.65	8251 \$4.90	MISC					
6522	9.95	8253 7.50	8282	\$6.72	8288	\$24.51		
8212	2.25	8257 10.00	8286	6.72	INSI 771	24.13		
8216	2.00	8259 11.50						
8224	2.50	8275 32.00						
8228	4.50	8279 7.20						
8238	4.50							
EPROMS/PROMS								
2708	\$6.20	2758 \$12.50						
2716	7.30	8355 6.80						
2732	16.92	8743 \$37.70						
MICROPROCESSOR INTERFACE IC's								
8720	\$3.25	8796 \$1.49	74LS242	\$1.79	74LS245	\$2.85		
8726	2.15	8797 1.49	74LS243	1.79	74LS273	1.69		
8728	2.30	74LS241 1.10	74LS244	1.10	74LS373	2.50		
8795	1.49							
AMP SWITCHES								
925	SPST 8 pos w/cover	\$4.99	958	SPST 8 pos Low Profile	\$4.28			
930	DPST 4 pos w/cover	8.45	920	SP 10 pos P.C. Rotary	7.81			
932	SPST 4 pos w/cover	4.08	921	10 pos P.C. Rotary NCD	6.81			
933	SPDT 4 pos w/cover	8.82	927	16 pos Hex Dip Switch	4.28			
WE STOCK THE FULL AMP LINE OF ELECTRONIC ACCESSORIES								
A.W. SPERRY INSTRUMENTS								
EZ6100	3 1/2 Digit DMM with LCD Display	\$140.95						
EZ6110	3 1/2 Digit DMM with LCD Display	159.95						
EZ6220	3 1/2 Digit DMM with LCD Display	172.95						
SP1000F	F.E.T. Input Volt-Ohm Milliammeter	105.95						
SP15	Pocket Size Volt-Ohm Milliammeter	19.95						
SP80	Extra Sensitive Volt-Ohm Milliammeter	40.95						
C30	Carrying Case for EZ6100, 6110, or 6220	19.95						
C11	Carrying Case for SP1000F	19.95						
C18	Mini Probe	1.75						
F7	Fuse for SP15	1.05						
F8	Fuse for EZ6100, 6110, or 6220	2.65						
LINEAR DEVICES								
LM301N	\$.32	LM380N	\$.50	NE565N	\$.85	LM1458N	\$.40	
LM309N	2.00	LM384N	1.75	NE566N	1.65	LM1488N	.80	
LM310N	1.75	LM386N	1.10	NE567N	.85	LM1489N	.80	
LM317N	1.15	NE555N	.36	LM723N	.45	7805CK	1.60	
LM318N	1.95	NE556N	.70	LM741N	1.35	7812CK	1.60	
LM319N	1.65	NE561N	3.69	LM747N	.55	7815CK	1.60	
GLOBAL SPECIALTIES, CORP.								
LOGIC PROBES			EXPERIMENTER SOCKETS			QUICK TEST SOLDERLESS BREADBOARD ELEMENTS		
LP-1	\$50.00	EXP-300	\$10.50	QT-595	\$12.00	QT-698	\$2.75	
LP-2	28.00	EXP-300P	2.40	QT-475	9.50	QT-478	2.50	
LP-3	76.00	EXP-350	6.10	QT-585	7.25	QT-358	2.10	
IC TEST CLIPS			POWERED PROTO-BOARD			4001 Pulse Generator		
PC-14	\$4.50	PB-104	\$70.00	5001	Universal Counter	\$360.00		
PC-16	4.75	PB-102	32.90	Logic Monitor	JUMPER			
PC-24	10.00	PB-101	25.00	100K Impedance	WIRE KIT			
PC-40	16.00	PB-100	20.10	LM-1	\$75.00	WK-1	\$9.00	
VECTOR								
P164-1DF	SLIT-N-WRAP TOOL w/50' spool of 28 gage wire	\$39.00						
P160-1B	DUAL-WAY UNWRAP TOOL Unwraps 26-30AWG	\$12.50						
P160-2A	DUAL-WAY WRAP-N-STRAP TOOL Wraps 26-30awg	\$13.25						
8804	UNIVERSAL Microcomputer/Processor Plugboard	\$27.65						
8800V	UNIVERSAL Microcomputer/Processor Plugboard for Altair 8800 & IMSAI 8080	\$24.95						
4607	UNIVERSAL Computer Plugboard, fits DEC SLI-11, PDP-8, PDP-11 and Heathkit H-11	\$21.40						
4609	MICROPROCESSOR PLUGBOARD, for Apple II	\$26.80						
WE STOCK THE FULL VECTOR LINE Catalog Available On Request								
TECHNICAL DATA ON COMPUTERS								
An Intro to MP's (The Beginner's Book...\$7.95, An Intro to MP's (Basic Concepts)...\$12.99, 4 and 8 Bit MP Handbook \$19.95, 16 Bit MP Handbook \$19.95, The CRT Controller Handbook...\$6.99, The 68000 MP Handbook...\$6.99, Z80 Assy Language Prog...\$16.99, 6502 Assy Language Prog...\$16.99, 6809 Assy Language Prog...\$16.99, Business System Buyer's Guide...\$7.95, CP/M User's Guide...\$12.99, Apple II User's Guide...\$15.00, MP's for Measurement & Control...\$15.99, CBASIC User's Guide...\$15.00, Interfacing to S-100/IEEE 696 MP's...\$15.00, Some Common BASIC Prog...\$14.99, Practical Basic Prog...\$15.99, Some Common BASIC Prog — Atari Edition...\$14.99, Some Common BASIC Programs — TRS-80 Level II Edition...\$14.99, Science and Engineering Basic Prog — Apple II Edition...\$15.99, TTL Cook Book...\$11.95, TV Typewriter Cook Book...\$11.95, CMOS Cook Book...\$12.95, Z-80 MP Handbook...\$11.95, Using the 6800 MP...\$8.95, The Cheap Video Cook Book...\$7.95, I.C. Converter Cook Book...\$13.95, The 555 Timer Appl's Source Book/with Exp's...\$7.50, TRS-80 Interfacing Book 1...\$10.95, TRS-80 Interfacing Book 2...\$11.95, Prog. and Interfacing the 6502...\$15.95, 8085A Cook Book...\$13.95, MP Primer (2nd Edition)...\$14.50, Z-80 MP Design Projects...\$13.95, IC Op-Amp Cook Book (2nd Edition)...\$15.95, Guidebook to Small Computers...\$6.95, Mostly BASIC Appls for Your TRS-80...\$12.95, Circuit Design Prog. for the TRS-80...\$14.50, Mostly BASIC Appls for Your Apple II...\$12.95, Mostly BASIC Appls for Your PET...\$12.95, CP/M Primer...\$14.95, The S-100 and Other Micro Busses (2nd Edition)...\$9.95, Your Own Computer...\$7.95, Applesoft Language...\$10.95.								

5% Carbon Film Resistors			
1/4W 10 for 40c			
1/2W 10 for 50c			
LED DISPLAYS			
FND357	\$1.50	FND800	\$1.95
FND500	1.50	MAN3620	2.00
FND507	1.50	MAN3630	2.00
LOW POWER SCHOTTKY TTL			
74LS00	\$.22	74LS42	\$.50
74LS01	.22	74LS47	.80
74LS02	.22	74LS54	.30
74LS04	.25	74LS74	.35
74LS08	.25	74LS76	.35
74LS10	.25	74LS83	.60
74LS11	.30	74LS86	.35
74LS12	.30	74LS89	.50
74LS13	.25	74LS92	.50
74LS14	.30	74LS96	.70
74LS16	.30	74LS112	.35
74LS16	.30	74LS122	.40
74LS18	.45	74LS123	.70
74LS20	.30	74LS125	.45
74LS22	.45	74LS126	.45
74LS23	.40	74LS128	.45
74LS24	.40	74LS132	.65
74LS28	.40	74LS137	.65
WE ALSO STOCK			
TTL • CMOS • LINEAR • DIP SOCKETS • EDGE CONNECTORS • SPRAGUE CAPACITORS & SWITCHES • E-Z HOOK TEST ACCESSORIES			
OUR NEW CATALOG			
AVAILABLE ON REQUEST		VOLUME QUOTES	

SUNTRONICS CO., INC.
 12621 CRENSHAW BOULEVARD
 HAWTHORNE, CALIFORNIA 90250
 (LOCATED NEXT TO FORMULA INTERNATIONAL)
 STORE HOURS: Mon-Fri 10am to 6:30pm — Sat 10am to 5pm
 IN CALIFORNIA OUTSIDE CALIFORNIA TOLL FREE
(213) 644-1149 1-800-421-5775
 Mail Order—Minimum Order: \$10. Send Money Order or Check to:
 P.O. BOX 1957—Dept. R, HAWTHORNE, CA 90250. Use your VISA or Mastercard (please include expiration date). Add \$2.00 postage and handling to order. California residents add 6% sales tax.

WARNING!
 Electric Power Pollution, Spikes, Interference & Lightning HAZARDOUS to HIGH TECH EQUIPMENT!!

MicroComputers, VTR, Hi-Fi, Lasers, Spectrometers are often damaged or disrupted due to Power Pollution. High Tech components may interact! Our patented ISOLATORS eliminate equipment interaction, curb damaging Power Line Spikes, Tame Lightning bursts & clean up interference. Isolated 3-prong sockets; integral Spike/Lightning Suppressor. 125 V, 15 A, 1875 W Total, 1 KW per socket.

ISO-1 ISOLATOR. 3 Isolated Sockets; Quality Spike Suppression; Basic Protection \$69.95
 ISO-3 SUPER-ISOLATOR. 3 DUAL Isolated Sockets; Suppressor; Commercial Protection \$104.95
 ISO-17 MAGNUM ISOLATOR. 4 QUAD Isolated Skts; Suppressor; Laboratory Grade Protection \$181.95

Master-Charge, Visa, American Express
TOLL FREE ORDER DESK 1-800-225-4876
 (except AK, HI, MA, PR & Canada)
SATISFACTION GUARANTEED!

Electronic Specialists, Inc.
 171 South Main Street, Natick, MA 01760
 Technical & Non-800: 1-617-655-1532

CIRCLE 71 ON FREE INFORMATION CARD

FREE CATALOG OF Burglar/Fire Alarms

Controls • Power Sources • Remote Stations • Holdup Alarms • Wireless Components • Magnetic Contacts • Ultrasonic • Microwave • Infrared • Sirens • Bells • Glass Protection • Shock Sensors • Phone Dialers • CCTV • Locks • Safes

mountain west
 4215 N. 16th St. Dept. RE-2
 Phoenix, Arizona 86016
 1-800-528-6169

CIRCLE 74 ON FREE INFORMATION CARD

TRI-TEK

LO PROFILE DUAL BEAM FACE WIRE (TIN) SOCKETS

	1-24	25-99	100-499	500 up
6 PIN LP	.08	.075	.070	.060
8 PIN LP	.09	.085	.079	.065
14 PIN LP	.15	.135	.120	.112
16 PIN LP	.17	.150	.135	.128
18 PIN LP	.19	.170	.150	.144
20 PIN LP	.22	.195	.170	.160
22 PIN LP	.26	.230	.210	.178
24 PIN LP	.26	.240	.220	.195
28 PIN LP	.31	.290	.270	.228
40 PIN LP	.44	.415	.370	.325

3 LEVEL WIRE WRAP DIP SOCKETS (TIN)

	1-24	25-99	100-499	500 up
8 PIN WWT	.33	.31	.290	.270
14 PIN WWT	.38	.36	.330	.320
16 PIN WWT	.42	.39	.370	.360
18 PIN WWT	.58	.55	.515	.471
20 PIN WWT	.68	.64	.704	.620
24 PIN WWT	.81	.77	.726	.662
28 PIN WWT	.93	.87	.862	.798
40 PIN WWT	1.27	1.20	1.136	1.092

D Subminiature Connectors — Compare These Prices!!

PLUGS	1-9	10-24	25-99	1-9	10-24	25-99
(DE) 9P	\$1.95	1.75	1.60	(DE) 9S	\$3.10	2.75
(DA)15P	2.35	2.10	1.90	(DA)15S	4.20	3.75
(DB)25P	2.60	2.35	2.15	(DB)25S	3.35	3.05
(DC)37P	4.55	4.15	3.80	(DC)37S	8.85	8.00
(DD)50P	5.65	5.15	4.65	(DD)50S	11.65	10.60

DB 51226 Cover. For DB 25P and S (RS 232 Type) \$1.39

CYBERTONE like a super loud SONALERT this "warning" alarm works from 9-12VDC and has variable rate and pitch. Ideal for smoke or burglar alarms or far-out games. Only 1 1/4" diameter, 6" long leads. Model CT-1100. \$7.95

25Amp STUD DIODES 200V 59¢ 600V 79¢
 200 ohm Carbon mica element 1/4" diameter 98¢
 Miniature 600A—600mA moderm transformer \$1.49
 6 foot 3wire Gray line cord. Rt angle plug \$1.69

JOHNSON 1/4" BUSHING Air Variable Capacitors 49¢
 #189-567 2-19.3pf, #189-563 1.4-9.2pf, #100-107-1 2.3-14.2pf

Calendar/Clock Chip and Vacuum-Fluorescent Display.
 Mostek MK50362-N, 20 pin clock/calendar I.C. with a FUTABA 5-1T-02-8G V.F. display and spec sheets, 1/2" high characters, AM/PM indicators, color. Blue-green color ideal for daylight operation. \$5.98/set

6 digit L.E.D. display 65¢ common cathode 13.98
 FND 503 85¢ FND507 \$1.49 MAN6710 (DUAL) \$1.98
 Switch Craft 142A miniature "TINI-D" phone jack 49¢
 Line master chrome foot switch SPDT, 6' cord GEM-36 \$4.98
 Line master black foot switch SPDT 7 Amp AND-T-51-S \$2.98
 Cherry E-03 Super Sensitive snap switch SPDT 27¢ 00
 C&K DPDT 1/4" toggle switch w/flat designer handle #1 98¢

MOOSE™ National Semi LM 396 Regulator adjustable from 1.25-15V at 10 Amp. w/specs \$19.95

Super Cap. 1 FARAD at 5V. Use as memory supply back-up. Only 1 1/4" dia. x 1/4" tall w/P.C. leads \$10.50

R/C Transmitter/Receiver chip set. National LM1871/72 has RF & Encode/Decode up to 6 channels of digital or analog link. With specs \$15.95/set

100V 25 Amp Bridge Rectifier (Rem. from Eq.) \$1.79
 400V 4 Amp TRIAC w/Heat Sink RCA 405036 69¢
 400V 35 Amp Q mode TRIAC. (isolated) \$1.99
 80V 5A Darlington TIP121 in TO-220 package 99¢
 200V 4A TO 202 TRIAC Q 2004F3 59¢

NYLON CABLE TIES
 4" 135JC, 11.001K 5" 1195C, 11575/K 7" 7250C, 211K

TRI-TEK

**7808 N. 27th Avenue
 Phoenix, Arizona 85021**

ORDER TOLL FREE: 1-800-528-0183
 (Order desk only)

TERMS: \$10.00 minimum order.
 Visa, MC, BAC, Check, M.O. or UPS C.O.D.
 U.S. Funds only. AZ residents add 5% sales tax.
 Prepaid orders over \$50 shipping prepaid.

OTHERS: Add \$3.00 shipping & handling.
 Add \$1.50 for C.O.D. orders.
 Outside U.S. add 20%.

CIRCLE 61 ON FREE INFORMATION CARD

ETCO™ ...HEADQUARTERS FOR CABLE TV CONVERTERS AND VIDEO ACCESSORIES

DEALERS WANTED
WHOLESALE
HOTLINE
1-514-342-1555
CALL FOR
QUOTATIONS

THE ETCO MICRO 1000 36 CHANNEL VCR PROGRAMMER & CABLE TV CONVERTER



Equivalent to or better than:
VIDCOR 2000 - PHILIPS CTC-2
MAGNAVOX MX-40CC - LINDSAY V2U - RHOADES CO-500-
PHILIPS CTC-30 - WINEGARD
VC-7600 and others...

TRY ONE ON
OUR 30 DAY
MONEY BACK
GUARANTEE

ONLY
69⁹⁵
AT ETCO

The ETCO Micro 1000 takes the midband and super-band channels your TV, VCR or projector can't receive and converts them to standard UHF channels any set can tune in. Easy installation no moving parts - FCC & UL approved. Channel conversion chart and detailed instructions included. 448VB114.

As above - with Vernier Tuning: adjustable tuning insures total tracking compatibility with all TV sets. 448VC477 \$79.95

THE ETCO COMMANDER 5000 37-CHANNEL WIRELESS REMOTE CONTROL CABLE TV CONVERTER!

24 MONTH WARRANTY!




ONLY
169⁹⁵
\$149.95 EA./5

Makes cable viewing an absolute joy! Connects between the TV cable and antenna input terminals of your TV set. Allows you to turn your TV on and off, change channels, recall the last channel, fine tune, all by remote control! Handsome woodgrain cabinet, pushbutton remote control. Your TV stays tuned to channel 3. The Commander 5000 does all the tuning! Covers low, mid, high and super band channels. Order today! 448ZA008.

NEW - As above, 58 channel version. 448ZA017 \$189.95

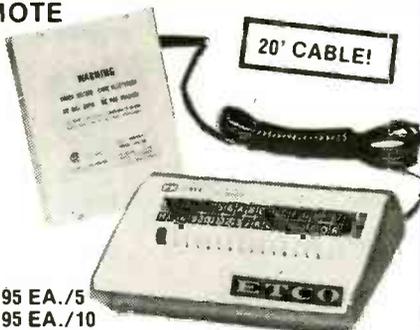CHAIRSIDE REMOTE CONTROL 30 CHANNEL CABLE CONVERTER




ONLY
89⁹⁵
AT ETCO

\$79.95 EA./5
\$74.95 EA./10

YOUR SET STAYS TUNED TO CHANNEL 3 - No need to jump up to change channels! Converter and control unit are connected by a long flexible cable to permit chair or bedside tuning. Remote channel selection, ON/OFF and fine tuning Complete with all instructions. 448VA275.

30 CHANNEL CABLE TV CONVERTER

ONLY
39⁹⁵
\$34.50 EA./5

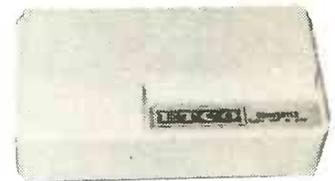

GET THE MOST out of your cable TV system! Easy hookup - completely safe - and you get up to 30 channels! Converted channels appear on the UHF portion of your set; channels 2 to 13 can also be seen on the VHF portion of the tuner. Easy to install - with instructions. 448AE047.

INCREDIBLE ETCO COPYGUARD STABILIZER AND VIDEO IMAGE ENHANCER SELLS AT A PRICE BELOW WHAT YOU WOULD PAY FOR EITHER UNIT IF PURCHASED SEPARATELY!

ONLY
99⁹⁵
AT ETCO



An ETCO exclusive! Combines both instruments in one. It works like a charm! Try one on our 30 day money back guarantee! DEALERS WANTED 448ZA021.

MORE CABLE TV BARGAINS

448ZA018	LINDSAY 40 channel programmable wireless converter	\$189.00
448VA850	VIDCOR 2000 converter & VCR programmer	\$89.95
448VA277	Midband to lowband 3 channel block converter	\$39.95
448VA276	Midband to highband 7 channel block converter	\$39.95
448VA963	Used (as-is) OAK V-26, 26 channel cable TV converters	\$39.95
448VA995	Used (as-is) TOCOM DC1000 remote control 20 channel converters	\$29.95
448VA996	Used (as-is) MAGNAVOX FV-25 remote control 20 channel converters	\$24.95
448VA335	75 ohm A/B switch with "F" connectors	\$9.95
448VA904	VHF/UHF/FM high gain broadband cable distribution amplifier	\$59.95
448VA992	Defective (as-is) wireless remote control converters - "u-Fix"	\$99.95
448VA503	75 ohm 3 position pushbutton co-ax switch with "F" connectors	\$19.95
448VC231	MDS microwave TV antenna with downconverter	\$239.00

NOTE: Converters on this page work only if you have cable TV. Number of extra channels available differ from cable system to cable system. Use of cable converters may be subject to rules by your local cable company.

DELIVERY HANDLING & INSURANCE CHARGES
Find the total amount of your order and your zip code below.

If Your Order Totals	01000		29000		58000	
	to	28999	to	57999	to	99999
Up to \$20.00	2.47	2.99	3.78	3.78	4.41	4.41
\$20.01 to \$30.00	2.89	3.32	4.11	4.11	4.74	4.74
\$30.01 to \$40.00	3.30	3.73	4.52	4.52	5.15	5.15
\$40.01 to \$50.00	3.71	4.14	4.93	4.93	5.56	5.56
\$50.01 to \$90.00	4.12	4.55	5.34	5.34	5.97	5.97
Over \$90.00	4.53	4.96	5.75	5.75	6.38	6.38

Check with order, please.
Visa & Mastercard O.K.
(Sorry, no C.O.D.'s) N.Y. state residents add 7% sales tax.
Dealer & Export inquiries invited. Our telephone order desk never closes.

ETCO Electronics
Dept 458
Plattsburgh, N.Y. 12901-1095

Send my free ETCO Catalog now.
I am not currently receiving your catalog.


Name _____
Address _____
City _____
State _____ Zip _____

ETCO™ ELECTRONICS
PLATTSBURGH, N.Y. 12901-1095. Tel. (518) 561-8700.

FREE CATALOG

Get it all! Subscribe today to RADIO-ELECTRONICS. Don't miss a single issue and ... you save as much as \$7.50 off the newsstand price.

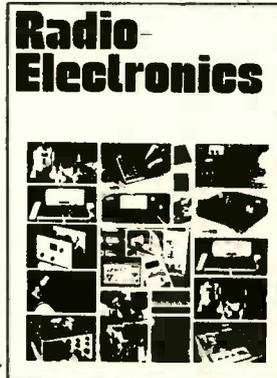When you select one of the subscription offers listed on the handy coupon—you'll be assured of having your copy reserved, even if it sells out on the newsstand. Make sure you get all the excitement in every issue of RADIO-ELECTRONICS, every month, by filling in and mailing the coupon, today.



This will be coming to you when you subscribe to **RADIO-ELECTRONICS:**

• **HELPFUL CONSTRUCTION ARTICLES ...**

- Test Equipment
- Hi-Fi Accessories
- Telephone Accessories
- Music Synthesizers
- Computer Equipment
- Automotive Equipment
- Intruder Alarms—Home & Car

• **NEWS ON NEW TECHNOLOGY ...**

- Android Design (Robots That Think and Do)
- Automotive Electronics
- Speech Synthesizers
- IC Applications
- Video Disc Players
- Video Tape Recorders

• **HOW YOU AND THE COMPUTER CAN BE FRIENDS ...**

- Getting Started Programs, Circuit Design, Games
- A/D-D/A Interfacing
- Peripheral Equipment

• **TV WONDERS FOR YOUR FUTURE ...**

- Latest Receivers and Circuits
- Projection TV Today
- Satellite TV Receivers
- Jack Darr's Monthly Service Clinic
- Service Problems and Solutions

• **FASCINATING "HOW TO DO IT" ARTICLES ...**

- Build Your Own Projects
- Make Your Own PC Boards
- Wiring Techniques
- Soldering and Desoldering
- Design and Prototyping

• **NEW AUDIO DIMENSIONS FOR YOUR PLEASURE ...**

- Noise-Reduction Devices
- Correct Bias for Your Tape Deck
- How to Connect that Extra Add-On
- Monthly Features by Len Feldman

AND you also get these regular MONTHLY FEATURES:

- **LOOKING AHEAD** by Dave Lachenbruch
- **HOBBY CORNER** by "Doc" Savage
- **WHAT'S NEWS**, new products, stereo news
- **and NEW IDEAS, STEREO PRODUCTS, NEW COMPUTER PRODUCTS FOR HOME/JOB and MUCH MORE!**

Radio-Electronics

SAVE MONEY, enclose your payment and you get ONE EXTRA ISSUE per year.

YES! please send me

7HB2

Payment enclosed, **13 issues for \$13.00**
(You save \$3.25 off newsstand price.)

Every Month! Get the Best-Clip Coupon-Mail Today!

Payment enclosed, **26 issues for \$25.00**
(Save More! \$7.50 off newsstand price.)

Bill me, 1 year—**12 issues only \$13.00**
(You save \$2.00 off newsstand price.)

Bill me, 2 years—**24 issues only \$25.00**
(Save more! \$5.00 off newsstand price.)

Extra postage: Canada \$3.00 per year.
All other countries \$7.50 per year.

U.S. Funds Only

Name _____ (please print)

Address _____

City _____ State _____ Zip Code _____


Mail to: RADIO-ELECTRONICS
P.O. Box 2520,
Boulder, Colorado 80322

Allow 6-8 weeks for delivery of first issue.

BUY of the YEAR!!!

Parallel, TTL Input WORD PROCESSOR I/O "Selectric"® TYPEWRITER/PRINTER

The manufacturer put 'em into storage to depreciate 'em... Now they're FINALLY AVAILABLE!! Removed from working systems, these fantastic machines have built-in driver and decoder circuitry and take TTL level, 6-bit character, plus 4-bit function input signals... Easily driven by most any micro. Use as a typewriter (with minor "repeat" circuitry) or as a KSR I/O printer or both. Requires 115, 60Hz for typewriter motor, 5 VDC for TTL and 24 VDC for solenoids. "Table top" style case. Each "Selectric" I/O machine is complete and in operational condition! Includes schematics, data, case, platen and ribbon. (Type element not included).

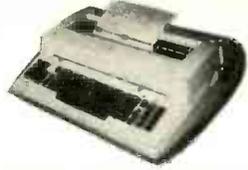

New Type Element \$21.00ea. I/O Selectric **\$399.00ea.**
Add \$20 for Packaging and Handling - Pay Shipping on Delivery

WORD PROCESSOR CPU ASSEMBLY



Linked to and used with the above machine, this unit completes a system which originally sold for over \$3000.00 each! Features include: standard cassette deck, auto centering, auto repeat, auto underline, suppressed notations, record/playback, auto merge, editing, margin adjusting and much, much more. Parts include tape or "mag" card deck, cabinet, fans, power supply, mother board, connectors, cables, LEDs and more. Worth much more than our price for the parts alone. Includes schematics and data. Tested and functional.

..... **Only \$199.00ea.**
Add \$20 for Pkg. and Handling - Pay Shipping on Delivery
Additional Cassette or 'Mag' Card Ass'ly
Add-on package includes everything you need to add on the second deck. Easy to retrofit.

..... **Only \$199.00ea.**
New, Unused Cassettes or 'Mag' Cards
For above Word Processor.
Tape Cassette **\$7.99ea., 10/\$69.00**
'Mag' Card **\$2.49ea., 10/\$19.00**

We Offer New and Used FLOPPY DRIVES, DISK DRIVES, PRINTERS, & MORE at BARGAIN PRICES!!! Ask for our Latest Flyer Listing NOW!

COMPUTERS, PERIPHERALS, UNLIMITED!

WAREHOUSE: 18 Granite St., Haverhill, Mass. 01830

MAIL ORDER Box 204, Newlon, N.H. 03858

TELEPHONE ORDERS: 617/372-8637

Sorry, No Collect Calls
MasterCharge & VISA Accepted

CIRCLE 67 ON FREE INFORMATION CARD

JAVANCO

Your Parts Super Market

50 ELECTROLYTICS, ASSORTED AXIAL AND RADIAL TYPES.

ECK-50 \$3.60

10 ASSORTED JACKS & PLUGS
JAK-10 \$2.25

REV-1 REVERB COILS. TYPICAL DIAGRAM INCLUDED.



20 ASSORTED KNOBS.
KNK-20 \$2.20

(1) \$12.00 (2) \$18.00

21 POLYSTYRENE CAP S.
100 HV CERAMIC DISC CAP'S.
10 UNIVERSAL SIGNAL DIODES.

DCK-21 \$0.90
DCK-100 \$2.40
DIK-10 \$0.55

25 SMALL CASE TRANSISTORS.

TRAK-25 \$2.25

7 FILTER CAPACITORS.
1 6800mfd 50V.
1 20-20-20-20 450v.
+ 5 Assorted Usables.

FPK-7 \$3.60

20 SQUARE OHM TYPE WIRE WOUND RESISTORS, PRK-20 \$1.40

25 AXIAL LEAD ELECTROLYTICS.
ALL ARE 50 VOLT OR MORE.

ECK-25A50 \$2.90

20 ASSORTED TERMINAL STRIPS. 2-8 TERMINALS, SOME SOLDER, SOME WIRE WRAP.

TK-20 \$0.90

3 2N6099 75 WATT 10 AMP (House marked 393-1) TRA-33 \$1.25

5 NE555 TIMER IC

5 FOR \$1.00

4 2.5 AMP 1KV RECTIFIERS

4 FOR \$.35

QUANTITIES LIMITED ON SOME ITEMS.

*Note: ADD \$2.50 TOTAL FOR SHIPPING ON ALL ORDERS

Javanco 150 Second Ave South, Nashville, TN
(VISA & MASTERCARD ACCEPTED) 37201
TENN. RESIDENTS ADD 6.75% SALES TAX.

TO ORDER TOLL FREE 1-800-251-8130
INFORMATION & CONVERSATION 615-244-4444

CIRCLE 70 ON FREE INFORMATION CARD

UNBELIEVABLE!

HITACHI 30 MHZ DUAL TRACE OSCILLOSCOPE

AT THE LOWEST PRICES YOU CAN FIND!



Model V302B

List 995.00

Sale 815.00

See below for freight allowance

- Signal delay line
- 5" CRT
- 12 ns rise time
- TV sync separator
- 1 mV/division sensitivity (max.)
- Vertical magnifier (x5)
- Sweep magnifier (x10)
- X-Y operation
- Front panel trace rotation
- CH1, CH2, Add, Diff. display modes
- "Z" axis (intensity) modulation
- Two years parts and labor warranty
- Two -X10 probes included!

15 MHz dual trace AN EVEN GREATER VALUE!



Model V152B

List 735.00

Sale 599.95

- 5" CRT
- 24 ns rise time
- TV Sync separator
- 1 mV/div sensitivity to 5 MHz
- Vertical and sweep magnifiers
- Front panel trace rotation
- Five modes of vertical deflection
- Two years parts and labor warranty
- Two -X10 probes included

ALL OTHER HITACHI SCOPES ON SALE

50 MHz, 100 MHz, 35 MHz, 20 MHz. Call for details

Also available:

Leader Instruments, Beckman, Univolt, Fluke, and other quality test equipment.

To order call toll free: (800) 423-5336

In Calif. (800) 423-5336

Local, Alaska, Hawaii (213) 701-5848

A DIV. OF ALLIANCE RESEARCH CORP

ORA Electronics

18215 Parthenia St. Northridge, CA 91325

TERMS: All items are subject to prior sale. Limited quantity on hand. Payment: Visa, Mastercard accepted. Exact freight and insurance will be added. C.O.D. orders accepted from recognized businesses. Prepaid orders: Payment must be made with U.S. currency. Orders paid with personal or company check will be held for check to clear. Free freight policy: Prepaid orders paid by cashiers check will be shipped UPS freight free to any point in the continental U.S. (Alaska, Hawaii, Canada excluded.)

CIRCLE 58 ON FREE INFORMATION CARD

★ **QUALITY parts at DISCOUNT PRICES!** ★

BSR FULLY AUTOMATIC RECORD CHANGER



- FULL SIZE CHANGER
- B.S.R. MODEL C198
- CERAMIC CARTRIDGE
- PLAYS 33, 45 & 78 RPM RECORDS...
- CUE/PAUSE LEVER
- ADJ. TRACKING FORCE

RECORD CHANGER DOES NOT INCLUDE BASE OR A.C. CORD...
\$25.00 EACH 4 for \$90.00

4PDT RELAY

- 14 pin style
- 3 amp contacts
- 24 volt d.c. or 120 volt a.c. coil
- Used but fully tested

\$1.70 EACH
 SPECIALLY COIL VOLTAGE
 LARGE QUANTITIES AVAILABLE
 SOCKETS FOR RELAY 50¢ each

COMPUTER GRADE CAPACITOR

- 3,600 mfd. 40VDC **\$1.00**
- 1 3/8" DIA. X 4 1/4" HI
- 6,400 mfd. 60VDC **\$2.50**
- 1 3/8" DIA X 4 1/4"
- 20,000 mfd. 25VDC **\$2.00**
- 2" DIA. X 2 1/2" HIGH
- 22,000 mfd. 25VDC **\$2.50**
- 2" DIA. X 2 1/2" HIGH
- 22,000 mfd. 40VDC **\$3.00**
- 2" DIA. X 4" HIGH
- 45,000 mfd. 25VDC **\$3.50**
- 2" DIA. X 4" HIGH
- 52,000 mfd. 15VDC **\$3.00**
- 2" DIA X 4 1/2" HIGH
- 72,000 mfd. 15VDC **\$3.50**
- 2" DIA. X 4" HIGH

CLAMPS TO FIT CAPACITORS 50¢ ea.

MINI SIZE BUZZERS

- 1 1/2 to 3 volts 75¢ ea WITH WIRE LEADS
- 1 1/2 to 3 volts 75¢ ea WITH PIN TERMINALS
- 3 to 7 volts WITH PIN TERMINALS 75¢ each

MITSUBI MODEL UES-A55F VARACTOR UHF TUNER

- FREQ. RANGE 470 - 889 MHz
- ANTENNA INPUT 300 OHMS

\$25.00 each 10 for \$220.00

SEND FOR NEW 1982 Free! 40 PAGE CATALOG Free!

TYPE N CONNECTOR

KINGS UG 536 8/U
 FLT5 RG55, RG58, RG141, RG142, RG223

SOLDER TYPE
\$1.75 EACH 10 for \$16.00

L.E.D.'s STANDARD JUMBO DIFFUSED

- RED 10 FOR \$1.50
- GREEN 10 FOR \$2.00
- YELLOW 10 FOR \$2.00

FLASHER LED 5 VOLT OPERATION JUMBO SIZE

- 2 FOR \$1.70

BI POLAR LED 2 FOR \$1.70

SUB MINI LED

- .079" x .098" 20 mA at 1.75v 10 FOR \$1.00
- 200 FOR \$18.00

QUANTITY PRICES AVAILABLE

TRANSFORMERS

120 volt primaries

- 6 VOLTS at 150 mA \$1.25
- 12 V.C.T. at 500 mA \$2.50
- 16.5 V. at 3 AMPS \$6.50
- 18 VOLTS at 1 AMP \$4.50
- 25.2 V.C.T. at 2.8 AMP \$5.50

CANNON XLRA-3-13 CONNECTOR

3 PRONG CHASSIS MOUNT CONNECTOR

- \$2.00 EACH
- 10 for \$19.00

SUPER SMALL PHOTO-FLASH

170 MFD 330 VOLT

- 1 1/4 x 7/8" 2 for \$1.50
- 10 for \$7.00

RECHARGEABLE SEALED LEAD-ACID BATTERIES

- 6 VOLTS 6 AMP/HR 3 1/2 x 2 x 4 1/2 IN. \$10.00
- 6 VOLTS 7 1/2 AMP/HR 4 1/2 x 2 x 4 1/2 IN. \$12.50

750 MFD 330 V PHOTO FLASH

2" HIGH X 1 1/4" DIA.

- \$1.25 EACH
- 10 FOR \$11.00

FLAT LEVER MINI-TOGGLE S.R.D.T. (ON-OFF) 5 AMP @ 120 VAC

CEK # 7105

- \$1.00 EACH
- 10 for \$8.50
- 100 for \$75.00

2" ALLIGATOR CLIPS

- 7 clips for \$1.00
- 100 clips for \$12.00
- 500 clips for \$50.00

★ SPECIAL ★ MRF 901 MICROWAVE TRANSISTOR

\$2.50 EA

ALL ELECTRONICS CORP.

905 S. Vermont Ave.
 P.O. BOX 20406
 Los Angeles, Calif. 90006
 (213) 380-8000

Mon. - Fri. Saturday
 9 AM - 5 PM 10 AM - 3 PM

TERMS

- Quantities Limited
- Min. Order \$10.00
- Add \$ 2.50 Shipping USA
- Calif. Res. Add 6%
- Prompt Shipping

ADVERTISING INDEX

RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.

Free Information Number Page

72	AMC Sales	128
-	ATV Research	112
51	Active Electronics	109
-	Advance Electronics	40
43	Advanced Computers	126-127
13	Albia Electronics	28,29
65	All Electronics	138
10,41	Alpha Byte Stores	33,105
56	Altex	125
24	American Antenna	13
54	Ancrona	133
28	Antenna Specialists	34
22	B&K Precision Dynascan Corp.	97
-	Karel Barta	108
4	Beckman Instruments, Inc.	
-	Electro-Products Group	Cover 3
-	Bullet Electronics	120
-	CIE, Cleveland Institute of Electronics, Inc.	18-21
30	Castle Marketing	106
73	Chaney Electronics	124
19	Channellock	92
-	Command Productions	108
5	Communications Electronics	2
67	Computer Peripherals Unlimited	137
-	Components Express	116
57	Concord Electronics	128
-	Cook's Institute of Electronics	108
2	Cooper Group	Cover 2
-	Dage Scientific	112
17	Data Precision	25
-	Data Services	112
-	Devtronics	116
64	Diamondback	124
47	Digi-Key Corp.	117
34,35	Drake Company	83,100
33	Eico	83
14	Electronic Book Club	85
71	Electronic Specialists, Inc.	134
-	Electronic Technology Today	98
38	Enterprise Development	100
-,50	Etoe Electronics	116,135
80	Etronics	116
-	Fair Radio Sales	138
-	Fordham Radio	107,122
42	Formula International	114-115
69	Fuji Svea	125
66	Godbout Electronics	112
8	Global Specialties	1
-	Global TV	110
-	Grantham College of Engineering	81
76	Hal-tronix	120
18	Hameg	104
-,82	Heath	7,16,17,89-91
77	Information Unlimited	122
-	International Communications	110
53	JDR, Microdevices	130-131
44	Jameco Electronics	118-119
-	Jamescomm	112
70	Javano	137
45	Jim-Pak	123
68	Komac	125
-	Live Via Satellite	116
52	MCM Audio, Inc.	121
32	MTI	99
-	McGee's Radio	116
-	McKay Dymek	110
-	McGraw-Hill Book Co.	70-73
-	Microtenna	112,110
59	Mikos	124
-	Monarchy Engineering, Inc.	120
74	Mountain West	134
78	Mouser Electronics	122
-	NRI, Schools	8-11
-	NTS, Schools	36-39
-	Nabih's, Inc.	81
-	Nemal Electronics	112
-	Netronics	81
12	Omega Sales	95
58	Ora Electronics	137
-	PGI	110
29	Pac - Tec Corp.	105
36,37	Paia Electronics	101,99
16	N.A. Philips	26-27
75	Poly Paks	120
9	Pomona Electronics	87

27	Protecto Enterprises	34
-,6	RCA	35,31
-	RNJ Electronics, Inc.	108
46	Radio Shack	113
49	Ramsey Electronics	111
-	Rondure	110
79	SCR Electronics, Inc.	132
39	SMP, Inc.	105
-	Sabadia Exports	112
23	HW Sams	83
11	Shure Brothers	93
-	Simple Simon Electronics	122
-	Sinclair Research	14-15
26	N.A. Soar	22
55	Solid State Sales	132
-	Sound Video Research	116
20	Sprague Products Co.	30
21	A.W. Sperry Instruments, Inc.	32
60	Suntronics	134
48	Surplus Electronics	129
-	Tektronix	5
-	Tennessee Electronics	110
62	Tomar Ltd.	128
61	Tri - Tek	134
31	Vector Electronics	106
7	VIZ Mfg. Co.	23
-	Wersi	112
81	Westland Electronics	132
3	Zenith Radio Corp.	Cover 4

Govt. SURPLUS ELECTRONIC EQUIPMENT CATALOG

New ITEMS . . . New BARGAINS!
FREE UPON REQUEST!
 Send today for FREE copy of CATALOG WS-81 and Supplement. Dept. RE

FAIR RADIO SALES
 1016 E. EUREKA - Box 1105 - LIMA, OHIO - 45802

MOVING?

Don't miss a single copy of **Radio-Electronics**. Give us:

Six weeks' notice

Your old address and zip code

Your new address and zip code

ATTACH LABEL HERE


name (please print) _____

address _____

city state zip code _____

Mail to: Radio-Electronics
 SUBSCRIPTION DEPT., P.O. BOX 2520,
 BOULDER, COLO. 80322

RADIO-ELECTRONICS

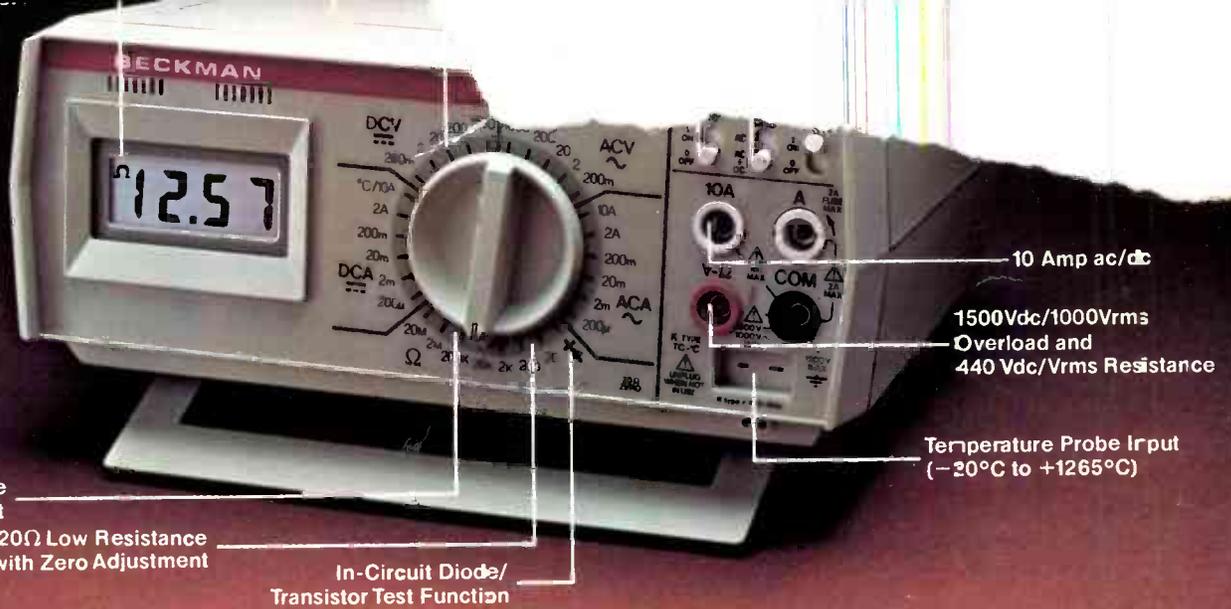

Introducing the TECH 360™ DMM. Never has it been so easy to do so much so little.

Beckman's TECH 360 bench/portable DMM puts unmatched capability and convenience at your fingertips.

You can select from 8 functions and 31 ranges with one turn of the single selector switch.

On or off the bench, you can accurately measure all complex waveforms with True RMS AC functions. Extend resistance measurement to 1/100 ohm resolution. Read temperatures from -20°C to 1265°C . Perform continuity checks

quickly, with audible and visible indications. Measure up to 10 amps without adding special adaptors. All with 0.1% basic Vdc accuracy.

12,000 hour battery life

Designed for ultimate ease of operation, the TECH 360 delivers 12,000 hours continuous service (up to 4 years of normal use) from standard heavy-duty batteries. You'll never have to search for power outlets or contend with ground loop errors. The expense of rechargeable battery packs is eliminated.

The TECH 360 is available for just \$289 (U.S. only), including batteries. The companion TECH 350 (without RMS and temperature measuring capability) is priced at \$229.

For information on the complete line of Beckman DMMs and accessories, call your local distributor today. For the one nearest you call: (714) 993-8803 or write Beckman Instruments, Inc., Electro-Products Group, 210 South Ranger Street, Brea, California 92621.



Convenient storage and multiple viewing angles are featured in the new line of Beckman bench/portable DMMs.

CIRCLE 4 ON

INFORMATION CARD

BECKMAN

VIDEO ORGANIZER permits

switching from one program source to another without changing cable connectors. Lets you select up to six different program sources for viewing. Up to three different sources for recording. Even lets you view one program source while simultaneously recording another. All this without changing cable connections!



Model S10W

At last the nuisance of manually changing cable connections is a thing of the past!

With Zenith's new Video Organizer, separate input and output jacks enable you to make a complete connection of TV and VHF antenna or cable TV antenna, subscription video disc player, video cassette recorder, video game and home theater equipment, and other auxiliary equipment.

So you switch from one program

source to another with pushbutton ease - without changing connections.

Equally important, the Video Organizer's advanced engineering design by Zenith results in low insertion loss and high isolation. Eliminates electromagnetic interference for maximum picture quality. And permits greater flexibility in use and ease of operation for more hours of uninterrupted home video enjoyment.

Write now for more information!



The quality goes in before the name goes on.®

Zenith Radio Corporation/Service, Parts & Accessories Division/11000 Seymour Avenue/Franklin Park, Illinois 60131

CIRCLE 3 ON FREE INFORMATION CARD