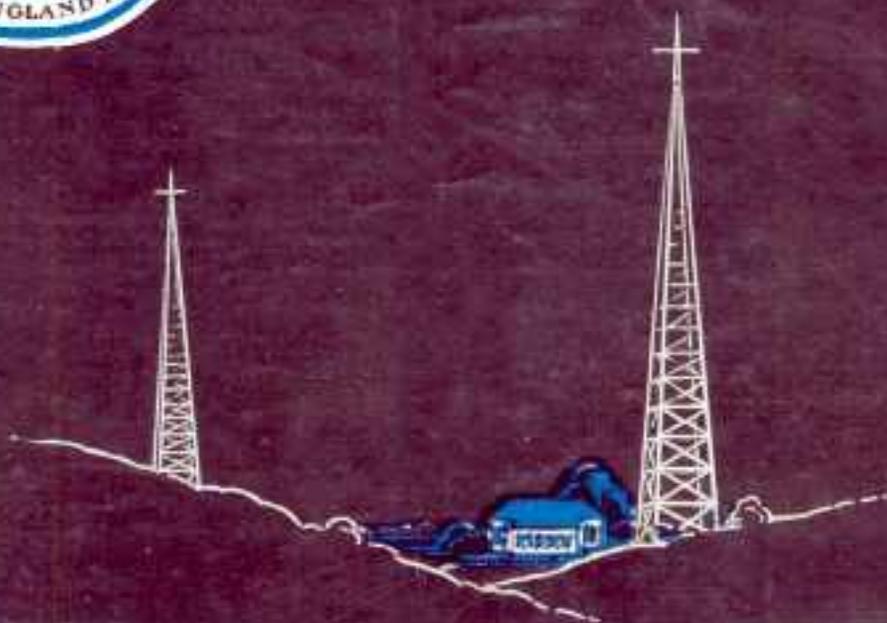


# RADIO Engineering

A Magazine of Technical Accuracy for the  
Radio Set Builder, Engineer and Manufacturer



*Edited by*  
**M.B.SLEEPER**



FEBRUARY, 1925

VOL. V NO. 2



*Dry "B" Batteries  
are an economical,  
dependable and  
convenient source  
of plate  
current!*



No. 110C, 45-volt extra large version. For heavy duty only. The ideal "B" Battery for use on multi-tube sets. Price \$4.75.

## *Scientists constantly improve battery quality*

EVEREADY "B" Batteries today contain more electricity, more service, more satisfaction than ever before.

Processes evolved by the scientists of the Union Carbide and Carbon Research Laboratories, Inc., when put in effect in the Eveready factories, are responsible for this great accomplishment.

At the same time the factories have effected a still higher standard of workmanship. A system of inspection that is a marvel of efficiency was inaugurated. The results, gratifying beyond measure, were accomplished with a speed and completeness that have few

parallels in industry. The final tests showed more electricity, more battery service, greater Eveready satisfaction without increasing battery size and with a substantial reduction in price. "B" Battery operating costs, using the new Evereadys, in most cases show a reduction of at least one-half.

There is an Eveready Radio Battery for every radio use.

Insist on Eveready "B" Batteries.

Manufactured and guaranteed by  
NATIONAL CARBON COMPANY, INC.  
Headquarters for Radio Battery Information  
New York San Francisco  
Canadian National Carbon Co., Limited, Toronto, Ontario

EVEREADY HOUR  
EVERY THURSDAY at 7 P. M.  
(Eastern Standard Time)


For real radio enjoyment, tune in the "Eveready Hour," broadcast through

WEAF New York WJAB Providence  
WEEB Boston WFS Philadelphia  
WGR Buffalo WCAE Pittsburgh

# EVEREADY

## Radio Batteries

*- they last longer*

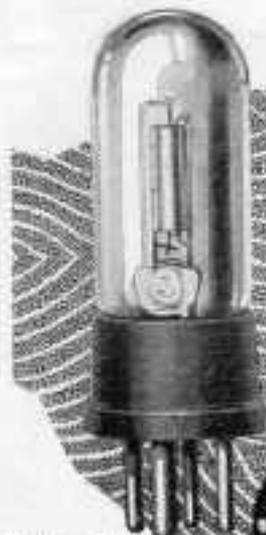

Radiotron WD-11.  
The ideal dry-cell  
tube.



Radiotron WD-12.  
The standard base  
dry-cell tube.



## For *Distance* ~ the *tube* is important

Radiotrons WD-11 and WD-12 are the same except for the base.

Radiotron WD-12 has a standard Navy type base. Use it to change your set to dry battery operation. Ask your dealer today.



This symbol of  
quality is your  
protection

Radio reception is not only a question of power, but of sensitivity to weak signals—and clear amplification. Radiotrons WD-11 and WD-12 are sensitive to the extremely feeble signals from distant stations—are silent in operation—and economical. They are famous for radio frequency amplification as for audio frequency—and detection. Get genuine WD-11's or WD-12's. Look for the name Radiotron and the RCA mark.

Radio Corporation of America

Sales Offices:

233 Broadway, New York

10 So. La Salle St., Chicago, Ill.

28 Geary St., San Francisco, Cal.

# Radiotron

REG. U. S. PAT. OFF.

# RADIO ENGINEERING

Edited by M. B. SLEEPER

Associate Editor, Alfred A. Chirardi

Fifth Year

Vol. V, No. 2

## Contents—February, 1925

	Page
Balkite Chemical Charger and B Battery Substitute . . .	69
The Browning-Drake UV-199 Receiver . . . . .	72
Construction of a Vacuum Tube Voltmeter . . . . .	80
Editorial Page . . . . .	83
Construction of the Improved Rasla-2 . . . . .	84
Samson Units for Super-Heterodyne Circuits . . . . .	90
Are Design Standards Changing? . . . . .	92
The Cabot Circuit Receiver . . . . .	94
How to Build the Splitdorf R. F. Receiver, Part 2 . . .	98
Standardized Parts List . . . . .	102

---

Radio Engineering, February, 1925, Vol. 5, No. 2. Published monthly by M. B. Sleeper, Inc., Publication office, Lyon Block, Albany, New York. Editorial and General offices, 52 Vanderbilt Ave., New York, N. Y. Printed in U. S. A. Yearly subscription \$2.00 in U. S. and Canada; ten shillings in foreign countries. Entered as second class matter at the postoffice at Albany, New York, January 9, 1923, under the act of March 3, 1879.

---



## Tune by Sight

Tune your favorite stations once, mark them on the Ultra-Vernier, then forget wave lengths. Tedious tuning, blind fumbling and guessing are over for all time.



Designed by R. E. Lamont, E. E. A. M. I. R. E., inventor of the famous Ultra-tetrode circuit. This monogram and (R. E. L.) is your assurance of Lamont design.

Now it's possible to pick your entertainment from the radio program and turn the dial instantly, accurately, to your station and know your receiver is tuned with infinite precision.

The silvered Ultra-Vernier dial mounts fast to panel. Single control 20-1 ratio, operates vernier for hair-splitting adjustment and governs station indicator. Replace your old dials with Ultra-Verniers. You've never known such tuning ease.


\$2.50

Made by The Hammarlund Mfg. Co., your assurance of quality and dependability — produced solely for the Direct Radio Corporation. All your dealers, electrical and hardware stores and you will be supplied promptly.

Write for Description Circular
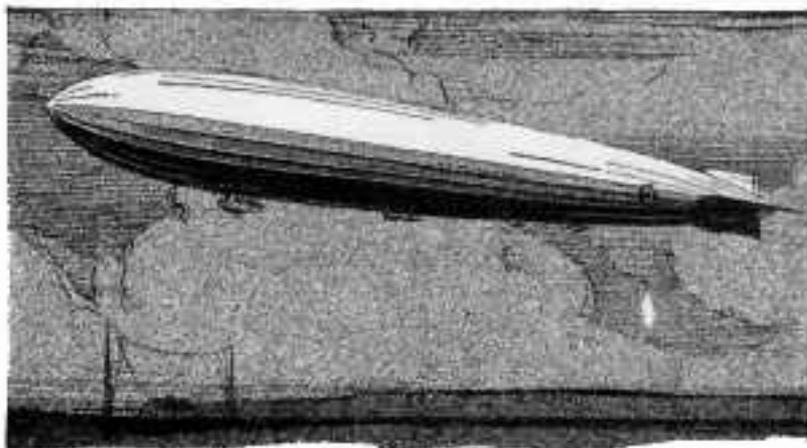
## ULTRA-VERNIER TUNING CONTROL

PHENIX RADIO CORPORATION  
7 Beckman Street  
NEW YORK CITY



## DUBILIER CONDENSERS

*Important Links between  
the Shenandoah and Land!*

Communication with land—under all conditions—at all times—this was the imperative need of the Shenandoah on its experimental flight across the continent. Impressed with this need, army and navy engineers equipped both transmitting and receiving sets with Dubilier mica condensers—not specially designed condensers but the regular standard product. Only complete confidence in the supreme reliability and efficiency of Dubilier condensers can explain their use in this important and daring adventure.

# Dubilier

CONDENSER AND RADIO CORPORATION



Fig. 1. The chemical cells used in the Balkite unit.

## The Chemist Contributes in the Radio Field

Unlike other storage battery chargers and B battery substitutes, the Balkite devices use chemical rectification instead of vacuum tubes. This makes the charger noiseless, gives the battery substitute better voltage regulation, and eliminates replacements

**T**HE radio market has been literally swamped with battery chargers, and of late a number of B battery eliminators have made their appearance. Some are efficient, others are not; some are noisy in operation, others do their work in silence; some employ rectifying tubes others use mechanical vibrators and still others depend upon chemical reactions for their operation; some are handsome enough in external appearance to

warrant their being placed right alongside of the radio set, others look so bad that they are put under tables, in cupboards, down in cellars, anywhere out of sight. We can truly say we have our full measure of the 57 varieties.

The tendency in the higher class of radio installations at the present time seems to be toward the use of the storage battery, in conjunction with a battery charger, for the filament current supply.

and a plate voltage supply working directly from the 60 cycle lighting mains. The Balkite units shown in the accompanying photographs represent one of the highest developments in the solution of the problem. They are enclosed in handsome metal cases, the two units being nearly the same size and matching each other in appearance. The operation of the B battery substitute unit is absolutely noiseless. The storage battery

negative side. A rubber covered duplex wire with a universal plug goes to the lighting socket. To stop the charging it is only necessary to turn the current off at the lamp socket. The clips can be left connected permanently to the battery if so desired without running it down or affecting the radio set. While in operation the charger consumes about 0.5 ampere or as much as an ordinary 60 watt lamp. A 4-ampere safety fuse is

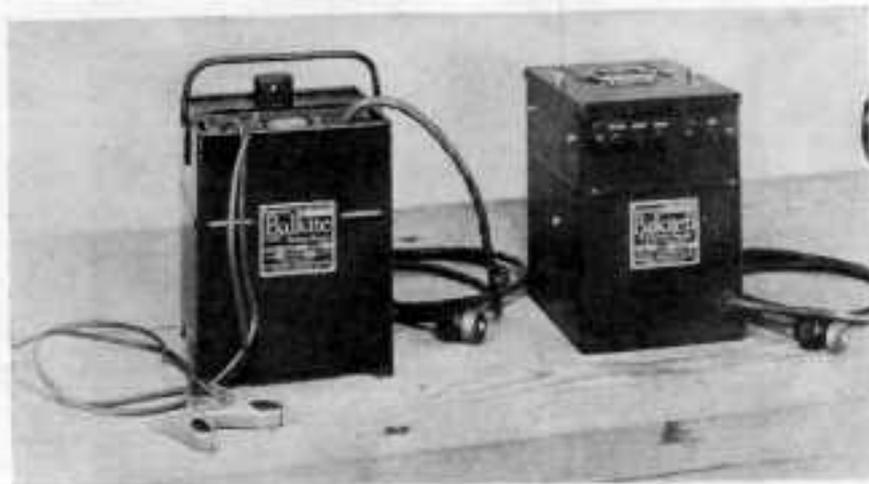


Fig. 2. At the left is the storage battery charger. The only attention it requires is the occasional addition of a little distilled water. This is also true of the B battery substitute shown at the right.

charger makes a slight bubbling sound but it cannot be heard at a distance of over four or five feet. Both units employ electro-chemical reactions as a means of rectification.

The battery charger shown on the left in Fig. 2 is used for charging 6 volt storage batteries and can be used while the set is in operation. The standard type is designed to work from 110-120 A.C. 60 cycle current, a special type being made for 50 cycles. The outfit comes packed in a box with a bottle containing electrolyte. To put the device into operation it is only necessary to remove the rubber filler cap from the top of the cell and pour the entire contents of the bottle into the opening. The two rubber covered leads which connect to the battery are fitted with heavy clips. The red one goes to the plus terminal of the battery and the gray one goes to the

provided on the lighting side to protect the charger from any overload currents. An extra fuse is also furnished. The only care necessary is the addition of a few drops of distilled water every once in a while to keep the plate in the cell covered, as is done with a storage battery.

The Balkite B unit shown on the right of Fig. 2, supplies the plate current directly. Five binding posts are arranged on the front connection board. There are three voltage taps, +100, +50, and +20 volts, the -B post, and the GR post which should be connected to ground. The +100 post is for the A. F. amplifier tubes and should be connected to the post marked +90V on most sets. The +50 post is for the A. F. amplifiers and also for the detector, when a hard tube is used. If soft tubes are employed, the +20 post is connected to the

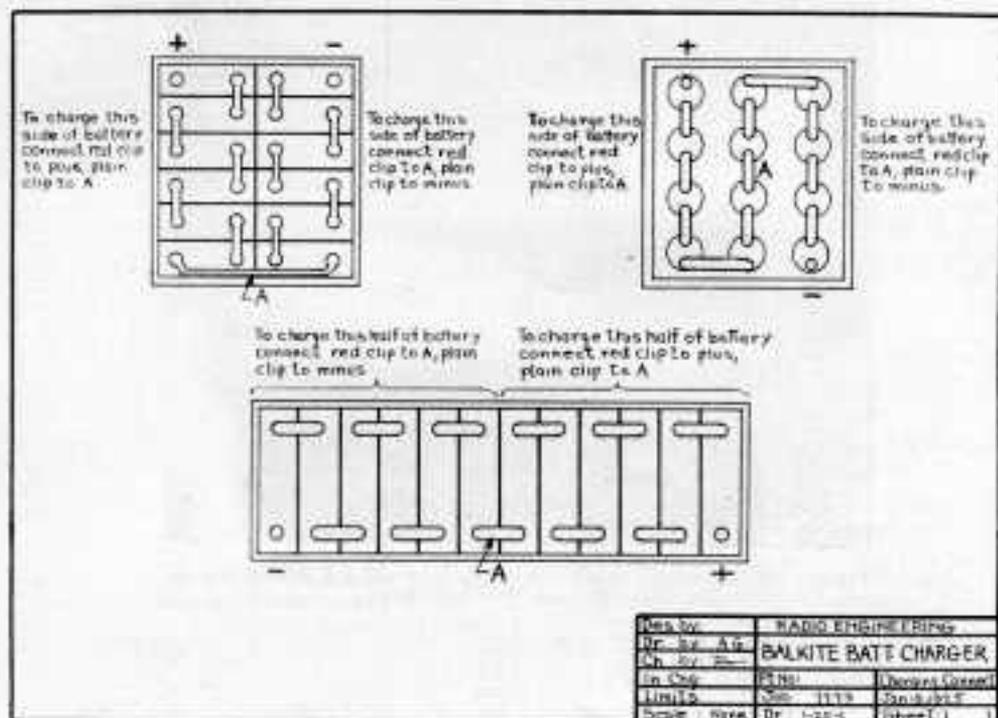


Fig. 3. Showing the connections for charging storage B batteries.

DET binding post of the set. The —B post goes to the B— post of the set.

This unit is packed in two compartments; one containing the electrical circuits and the other containing the glass cell assembly shown in Fig. 1. After unpacking the cell assembly, the six small rubber stoppers must be removed from the vent holes in the cell covers. These are put in to prevent leakage of the electrolyte during shipment. Then unscrew the two knurled nuts on top of the metal case and lift off the cover. Now unscrew the two composition binding posts A and B from the threaded studs, and place the cell assembly in the compartment case so that the two lead lugs extending beyond the cover of the cell assembly drop over the screws from which the binding posts have been removed. Replace the binding posts on the studs and secure them firmly so that good electrical connection is made between the cell assembly and the studs.

If it is desired to get higher voltage or more current for operation of sets with more than six tubes, remove the

cover from the case and loosen the binding post to which the slotted switch arm is attached. Swing the arm over to the post marked H and fasten it in place by screwing down the fibre posts at each end. This is a very important feature as it permits an additional control of the voltage over the inherently good voltage regulation characteristics.

When the set is not in operation it is only necessary to disconnect the Balkite B at the lamp socket. A few drops of distilled water added to the cells once or twice a year is all the attention required. To do this the power should be turned off and the cell assembly removed from the case. The water in the glass jars should always be up to the level mark.

The storage battery charger can be used also to charge the 22½ volt rechargeable B batteries now on the market. This must be done by charging half the B battery at a time. The connections necessary for charging the various types of B batteries are shown in Fig. 3.

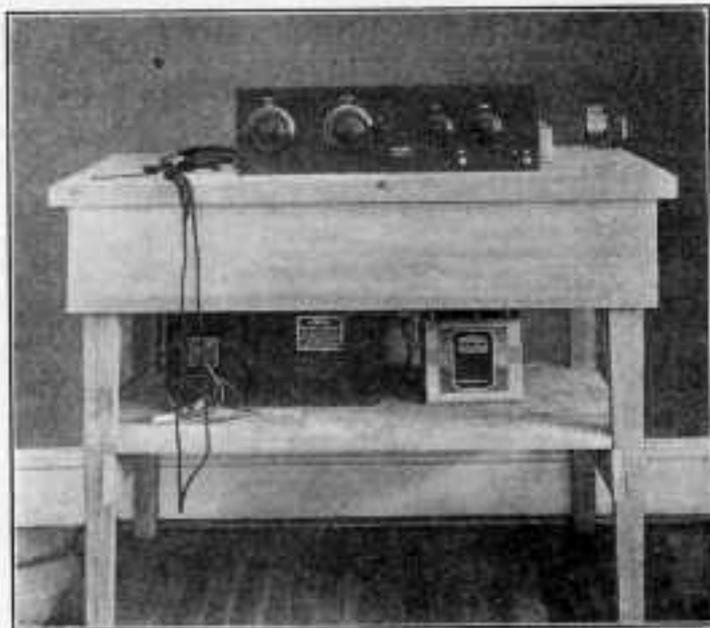


Fig. 1. The Browning-Drake 199 as it was set up at the Darlen laboratory for the final tests.

## The Browning-Drake 199

The data presented here is authorized by Mr. Browning, and the design has been personally approved by him. This set, using all UV-199 or C-299 tubes, can be operated from dry cells, and is practically equal to the type 6600 Browning-Drake receiver

**W**HEN the type 5300 DX receiver was described in the August 1923 issue of the magazine, the reports were so consistently enthusiastic that we thought it would be impossible to design a set which would be an improvement on it. The Browning-Drake, however, has left the type 5300 far behind for, altho it employs no more tubes, and is even simpler to build and operate, it is far superior to the other set in distance as well as volume.

Strangely enough, the original design for the DX receiver came from Boston, and again Boston scores as the home of the Browning-Drake, for both Mr. Browning and Mr. Drake are Boston men and graduates of Harvard University.

The Browning-Drake 199 Receiver  
Altho the type number of this set is 7000, we call it the "Browning-Drake 199" because it operates on UV-199 or

C-299 tubes, while the original type 6600 uses a 199 for the R. F. tube and UV-201-A's or C-301-A's for the detector and audio amplifiers. In the matter of volume and distance, there is not as much difference between the 6600 and 7000 as might be expected, altho the quality with the type 6600 is slightly better. On the other hand, there is a tremendous advantage in being able to run a Browning-Drake receiver from dry cells. Moreover, the total B battery current consumption on the type 7000 set is only 5 milliamperes. Therefore, the No. 764 Ever-ready B batteries can be used. Four are required, as these batteries give 22½ volts each, or two No. 772 45-volt batteries. These units will last for several months. You will note that 4½ volts C battery, obtained from a No. 771 Ever-ready unit, is also needed. This is essential or the B battery current will be considerably increased.

For A batteries, the type 7111 is recommended. If eight of these are used, connected with two sets of four in parallel, they will have a life of approximately two months if the set is used on an average of four hours a day. The total filament current is 0.20 to 0.25 ampere.

This outfit is not only more economical to operate but it is less expensive to build because the design has been simplified in a number of ways. No set could be neater in appearance for, on this four-tube receiver, there are only eight or nine wires that can be seen when the cover of the cabinet is opened.

lengths, but with this set very nearly maximum results can be obtained over the entire wavelength range without adjusting the tickler at all. It is not necessary to neutralize this set.

The filament current of the R. F. amplifier tube is automatically adjusted by means of an Amperite. A 30-ohm General Instrument rheostat regulates the detector and another, of the same resistance, controls the two A. F. amplifier tubes. Right between the rheostat dials, and below them, is a Walbert filament lock switch by means of which the tubes can be turned on or off without changing the

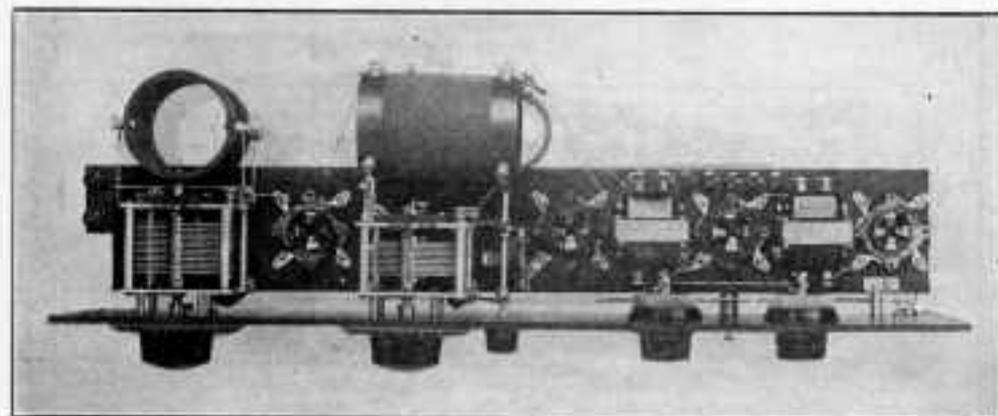


Fig. 2. You will see that few sets can match this outfit in appearance, nor can they surpass it in receiving range and volume.

**Operating And Results Obtained** Several views of the Browning-Drake 199 are given in the accompanying illustrations. You will see in Fig. 1 the outfit as it was installed for testing at the Darien laboratory. It is identical to the type 6600 from the front.

The Browning-Drake circuit is made up of one stage of tuned radio frequency amplification, a regenerative detector, and two stages of audio. The large dial on the left tunes the R. F. amplifier while the right hand dial tunes the detector circuit. There is a small knob just beside the latter dial which controls the regenerative effect. Unlike ordinary regenerative receivers, however, it is not critical, nor is it necessary to readjust it each time a station is turned in. Most regenerative circuits use much more feedback coupling at the longer wave

rheostats. A Carter jack in the lower right hand corner provides connections for the telephones.

Antenna, ground, and battery posts are located at the rear of the set, as you will see in Fig. 2. For testing purposes, it is very convenient to use the Belden battery cord. This has five wires, each of a different color, formed into a cable. The insulation is very heavy, so there is no danger of short circuiting the batteries. The C battery is mounted right behind the set, as the leads should be kept as short as possible.

To tune the set, the large dials are rotated together. They run evenly at the center of the scale altho at the low and high waves the reading on the right hand dial is higher than on the left hand dial. The dials furnished with the National Regenaformer tuning units are of



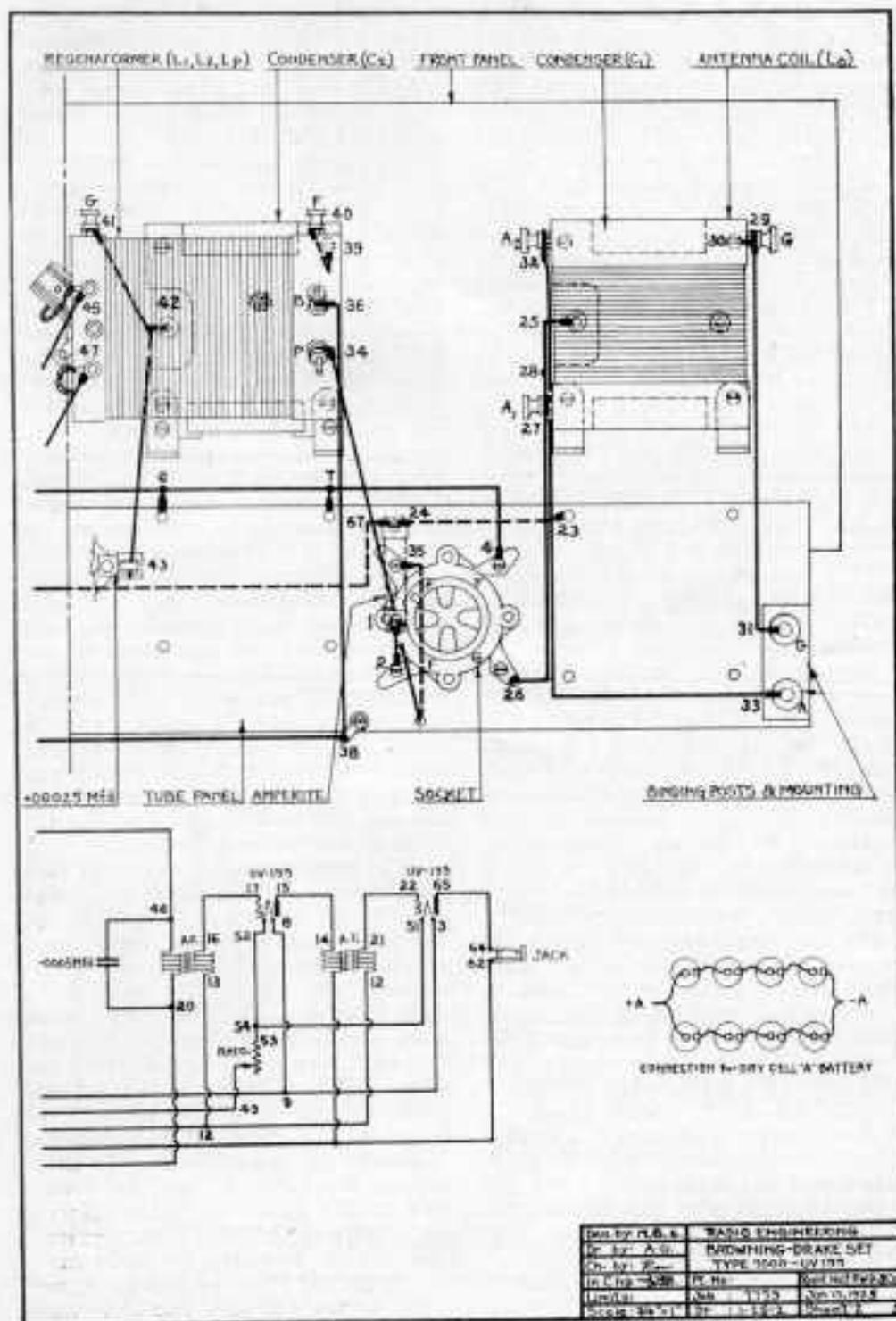


Fig. 6. Right hand half. Note that the tube panel is tipped down to show the parts

the vernier type. As the knob is rotated, the dial itself moves separately, approximately six revolutions of the knob being required for one revolution of the dial. This is about right for a vernier, and the adjustment is so smooth and positive that it is a pleasure to tune these dials. When a station is brought in, the small knob on the tickler is rotated in an anti-clockwise direction to bring up the signals to maximum. Then the condensers are re-adjusted for the exact settings.

There is no danger that this set will interfere with reception at other stations because the first tube does not oscillate at all and the detector tube cannot be used in an oscillating condition because the signals become distorted. This action serves as an automatic check against the operation of the set in a manner which would cause annoyance at other stations.

**Standard Parts Required** The front panel for this set is of polished black Formica, measuring 7 by 24 by 3/16-in., while the base panel is of the same material, 3 1/2 by 23 by 3/16-in. The little terminal panel for the antenna and ground binding posts can be cut from a piece of scrap Formica. It measures 1 3/4 by 3/4 by 3/16-in. Formica can be obtained with a mahogany or walnut finish if you want to make the panels match the woodwork on the cabinet. Celoron, Dilecto, or Duresto, are also satisfactory for this set. The mechanical strength is very important, as well as the electrical characteristics, for the panels must support considerable weight.

The key instruments for the set are the two National Regenaformer units. These are of the design developed by Browning and Drake and are licensed by them for use in the Browning-Drake Receiver. The first unit consists of a 0.0005 mfd. National condenser with the antenna and R. F. tuning inductance, while the second is made up of a 0.00035 mfd. National condenser with the R. F. transformer and tickler coil.

On the front panel are mounted the two 30-ohm General Instrument rheostats, Walbert lock switch, and open circuit Carter jack. The base panel carries four Benjamin 199 sockets, a 0.00025 mfd. New York Coil fixed condenser

with mounting clips for a 2-megohm Daven gridleak two 1 to 4 Modern transformers, a 0.0005 mfd. Dubilier Micadon, and seven Eby or Marshall-Gerken binding posts, two of which are on the antenna and ground terminal strip. Beneath the tube panel there is the 6V-199 Amperite. This can be seen in Fig. 4.

For hardware, two terminal support pillars, 3 3/8-ins. long by 3/8-in. in diameter, threaded at each end for 6-32 screws are required, as well as one angle bracket and three coil support pillars. One of the pillars holds the tube panel to the front panel at the right hand end, while the other two are fastened to the underside of the tube panel as supports, for they rest on the inside of the cabinet.

**Suggestions For Wiring** The best mechanical design is unavailing if the connections are not properly made. With the picture wiring diagram and the illustrations it is an easy matter to copy the original set. A little care in shaping the wire will not only prevent trouble when the set is in operation but will greatly improve the appearance of the outfit as well. There is a tendency to encourage set builders to make connections without soldering but this practice should be discouraged, for screws and thumb nuts have the most mysterious way of letting wires slip out from under them and they give no warning except that the set stops functioning as it should.

Altho many set builders feel that they must have an electric soldering iron, this is really not necessary. If you do not feel that you can get a good electric iron, such as the American Beauty, a Nokorode soldering kit, which costs only half a dollar, will do astonishingly good work when used in accordance with the very thorough instructions supplied with the soldering kit. The secret of successful joints does not lie in the design of the iron but in its correct manipulation. Moreover, you must use non-acid paste, such as Nokorode, or rosin core solder, such as the Kester or Belden brands, which are made with the correct proportion of rosin necessary for radio work. If you use the paste, be sure to get soft solder or you will have trouble in making it melt properly.

**Assembly And Wiring** Figs. 5 and 6 show the picture wiring diagram for the set as well as the schematic circuit. The former illustrates connections as they were actually made. The base panel is dropped down in order that the parts can be seen more clearly. Wires shown in dotted lines are run beneath the tube panel. The terminals are numbered in both diagrams, but if the indications are not clear in the schematic, you can see just how they should be from the

diagram. Otherwise you are liable to blow out a tube. When you fasten the third socket from the left, looking at the set from the rear, instead of putting a thumb nut between the spring and the upper side of the tube panel, put the screw through one of the corner holes of the New York Coil fixed condenser, first removing the Fahnestock clip. The arrangement is shown in the picture wiring diagram. This does away with any grid lead. Remove the mounting springs

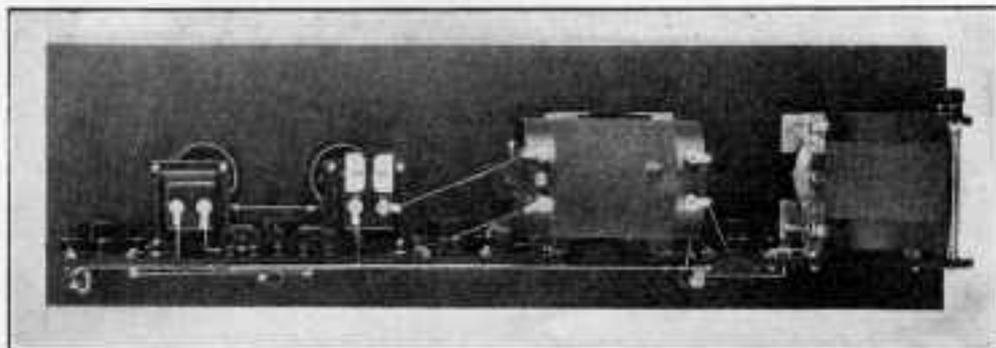


Fig. 3. The rear view. Note the arrangement of the transformers and the Micadon mounting.

picture wiring diagram. Wire is recommended for the connections instead of the familiar, heavy buss bar.

1. On the original set the bases of the Benjamin sockets were removed from the upper parts and the upper part mounted directly on the tube panel. It may be more satisfactory, however, to leave them on. If you want to leave the bases on the sockets, remove the screws which serve as terminals, then throw away the thumb nuts. Put the machine screws in the opposite direction with the round head resting directly on top of the contact spring. Put the screws right through the tube panel and fasten them with nuts on the under side. Do not forget the soldering lugs. The arrangement can be seen in Fig. 2. If, however, you do not use the bases, put the machine screws in with the heads on the contact springs but put the thumb nuts between the springs and the upper surface of the tube panel. Then put on the nuts and lugs underneath as before. Make sure that the markings on the sockets come in the exact positions shown in the picture wiring

from the Aniperite base strip, and fasten the springs to the under side of the base panel. The holes for the mounting screws are in line with the plate and filament terminal holes for the right hand socket. Use a flat head screw for holding the rear mounting spring so that it will not come in contact with the plate contact spring on the socket.

2. Solder lug 1 directly to lug 2. They are so close together that no connecting wire is necessary. Terminal 1 is the rear lug on the Amperite mounting spring and 2 is the lug on the socket filament terminal.

3. Fasten an angle bracket to the left end of the tube panel, using a  $\frac{1}{2}$ -in. 6-32 R. H. screw and nut. Put a lug on the screw under the panel. Fasten lugs to the under side of the tube panel, using  $\frac{1}{2}$ -in. 6-32 R. H. screws and nuts, at points 6 and 7.

4. Connect 3 to 4, and solder this wire to lugs 5, 6, and 7, past which the wire should run. Put No. 7 M-R varnished tubing over the wire between points 3, and 5, 5 and 9, and 9 and 11. Leave

spaces for connections 9 and 11 as they are to be made afterward. Connect 8 to 9, and 10 to 11.

5. Mount the two audio frequency transformers on the tube panel, using  $\frac{1}{2}$ -in. 6-32 R. H. screws and nuts. Make sure that the primary terminals are at the rear. Connect 12 to 13. These are the F posts on the transformers. Connect 14 to 15. 14 is the P terminal on the transformer and 15 the P terminal on the socket. Connect 16 to 17. 16 is the G

terminal on the transformer and 17 the G terminal on the socket.

6. Mount the five binding posts on the tube panel, making sure that the connection holes run from front to rear. Connect 18 to 12. 18 is the -C binding post and 12 the F post on the transformer. This wire runs from the transformer straight down through a hole in the tube panel and around to a lug on the binding post screw beneath the panel. Connect 19 to 20. 19 is the +45V binding post and 20 the F post on the transformer. This wire runs up through a hole in the tube panel. Connect 21 to 22. 21 is the G post on the transformer, and 22 the G post on the socket.

7. Solder soldering lugs to the lugs furnished on the Dubilier condenser and have them pointing down so as to slip over the primary terminals on the right hand audio transformer. The arrangement can be seen in Fig. 3. This condenser is of 0.0005 mfd. Eight mounting legs are supplied with the Browning-Drake kit. The vertical part of each leg has two holes. Fasten the long parts of

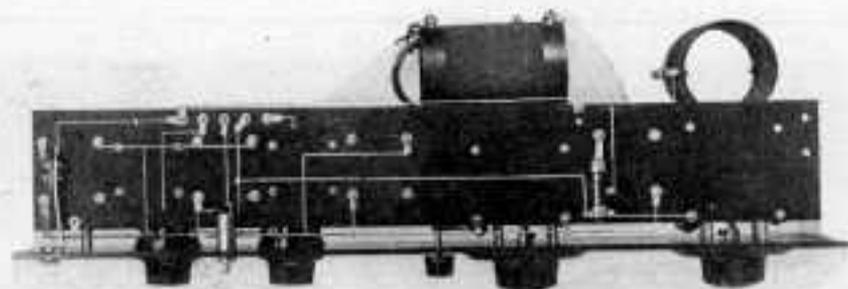


Fig. 4. Here you can see the wires concealed under the tube panel.

legs and the tube panel and holding them in place with nuts on the under side.

Put a lug under the front left hand nut on the under side of the panel to provide connection 23.

8. Connect 23 to 24. 23 is a lug under the nut of the screw holding the condenser mounting leg to the tube panel and 24 the front contact spring screw on the Amperite. Connect 25 to 26. 25 is a lug under the binding post nut which serves as a terminal for the fixed plates and 26 the grid contact on the socket. Connect 27 to 28. 27 is the A1 terminal on the coil and 28 a connection made to the wire running from 25 to 26. Connect 29 to 30. 29 is the G terminal on the coil and 30 a lug put on the screw which holds the rear end plate to the spacing pillar of the condenser in the upper right hand corner.

9. Fasten the two long panel support pillars to the tube panel with  $\frac{1}{2}$ -in. 6-32 R. H. screws and, after removing the nuts from two Eby binding posts, put the binding posts screws through the short terminal panel and thread them into

the mounting legs to the four screws which hold the front and rear end plates to the lower spacing pillars. Remove the screws passing through the end plates into the spacing pillars one at a time. Put the screw through the lower hole in the mounting leg and then turn the screw back into the pillar again. Have the short ends of the legs pointing toward the rear of the set. Fasten the right hand unit to the tube panel, putting  $\frac{1}{2}$ -in. 6-32 R. H. screws through the mounting

legs and the tube panel and holding them in place with nuts on the under side. Put a lug under the front left hand nut on the under side of the panel to provide connection 23.

8. Connect 23 to 24. 23 is a lug under the nut of the screw holding the condenser mounting leg to the tube panel and 24 the front contact spring screw on the Amperite. Connect 25 to 26. 25 is a lug under the binding post nut which serves as a terminal for the fixed plates and 26 the grid contact on the socket. Connect 27 to 28. 27 is the A1 terminal on the coil and 28 a connection made to the wire running from 25 to 26. Connect 29 to 30. 29 is the G terminal on the coil and 30 a lug put on the screw which holds the rear end plate to the spacing pillar of the condenser in the upper right hand corner.

9. Fasten the two long panel support pillars to the tube panel with  $\frac{1}{2}$ -in. 6-32 R. H. screws and, after removing the nuts from two Eby binding posts, put the binding posts screws through the short terminal panel and thread them into

the mounting legs to the four screws which hold the front and rear end plates to the lower spacing pillars. Remove the screws passing through the end plates into the spacing pillars one at a time. Put the screw through the lower hole in the mounting leg and then turn the screw back into the pillar again. Have the short ends of the legs pointing toward the rear of the set. Fasten the right hand unit to the tube panel, putting  $\frac{1}{2}$ -in. 6-32 R. H. screws through the mounting

legs and the tube panel and holding them in place with nuts on the under side. Put a lug under the front left hand nut on the under side of the panel to provide connection 23.

8. Connect 23 to 24. 23 is a lug under the nut of the screw holding the condenser mounting leg to the tube panel and 24 the front contact spring screw on the Amperite. Connect 25 to 26. 25 is a lug under the binding post nut which serves as a terminal for the fixed plates and 26 the grid contact on the socket. Connect 27 to 28. 27 is the A1 terminal on the coil and 28 a connection made to the wire running from 25 to 26. Connect 29 to 30. 29 is the G terminal on the coil and 30 a lug put on the screw which holds the rear end plate to the spacing pillar of the condenser in the upper right hand corner.

9. Fasten the two long panel support pillars to the tube panel with  $\frac{1}{2}$ -in. 6-32 R. H. screws and, after removing the nuts from two Eby binding posts, put the binding posts screws through the short terminal panel and thread them into

the upper ends of the terminal panel supports. A lug must be put between each pillar and the terminal panel.

10. Connect 30 to 31 and 32 to 33. 32 is the A2 terminal on the coil and 33 the rear binding post.

11. Remove the two screws holding lugs 6 and 7 and mount the second unit on the tube panel with the mounting feet as previously explained. Put a  $\frac{1}{2}$ -in. 6-32 R. H. screw through the tube panel at terminal 38, with soldering lugs above and below the panel. Fasten this screw with a nut and then put a coil mounting pillar on the screw.

12. Connect 34 to 35. 34 is the P terminal on the Regenaformer and 35 the P terminal of the socket. This wire runs through a hole in the panel and forward to the socket terminal. Connect 36 to 37, fastening the wire at 38. 36 is the B+ terminal on the Regenaformer and 37 a lug on the +90V binding post. Put a  $\frac{3}{8}$ -in. length of M-R varnished tubing on this wire at the binding post end to prevent possible short circuits, and hold the tube in place by a drop of solder on the wire at the right hand end. Connect 39 to 40. 40 is the F terminal on the Regenaformer and 39 a lug put under the screw which holds the rear condenser end plate to the spacing pillar at the upper right hand corner. Connect 41 to 42. 41 is the G terminal on the Regenaformer and 42 a lug under the thumb screw which provides connections to the fixed plates. Connect 42 to 43. 43 is a connection made to the Fahnestock clip on the grid condenser. 44 indicates the connection between the other side of the grid condenser and the grid contact on the socket, altho no wire is employed. Connect 45 to 46. 45 is the upper terminal of the tickler coil and 46 the P terminal on the transformer. Connect 47 to 48. 47 is the lower terminal of the tickler coil and 48 the P contact on the socket.

13. Mount the two rheostats on the front panel using the screws provided. Adjust the thumb nuts at the rear so that the knobs turn smoothly. Mount the telephone jack with the frame up and down, as shown in Fig. 4, put the lock switch in place, and fasten a coil mount-

ing pillar to the front panel with a  $\frac{1}{4}$  in. 6-32 R. H. screw put through the panel in the hole just above and to the right of the jack.

14. Connect 49 to 50. These are the adjacent terminals on the rheostats.

15. Fasten the front panel to the two variable condensers. It is necessary to remove the dials from the condensers. First loosen the set screw which holds the knob to the shaft. Then take out the three R. H. screws which fasten the dial to the gear box, remove the four screws which hold the gear box to the condenser mounting posts, and undo the set screw on the collar which fits over the condenser shaft. You will find three washers on each condenser mounting post. Take off all but one from each post. Put the condenser behind the panel and put in the screws which go through the gear box and thread into the mounting pillars, put back the three screws holding the dial to the gear box, and finally, fasten the knob in place by tightening the set screw in it. Turn the condenser plates so that they are totally interleaved, loosen the set screw on the collar over the condenser shaft, set the dial so that the 100 division line coincides with the line on the panel and tighten the set screw again. Fasten the angle bracket at the left hand end of the tube panel to the coil mounting pillar on the front panel by means of a  $\frac{1}{2}$ -in. 6-32 R. H. screw.

16. Connect 51 to 52. These are the F terminals on the two left hand sockets. This wire must be covered with M-R tubing, leaving a space for connection 54. Connect 53 to 54. 53 is the left hand rheostat terminal and 54 a connection made to the wire running from 51 to 52. This wire drops down and then runs back under the tube panel. Connect 55 to 56. Connect 57 to 8. 57 is the left hand contact on the lock switch. Connect 58 to 59. 58 is the right hand terminal of the lock switch and 59 the +A -B binding post. Connect 60 to 61. 60 is the -A +C binding post and 61 a connection made to the wire running from 49 to 50. Connect 62 to 63. 62 is the frame contact

(Concluded on page 116)

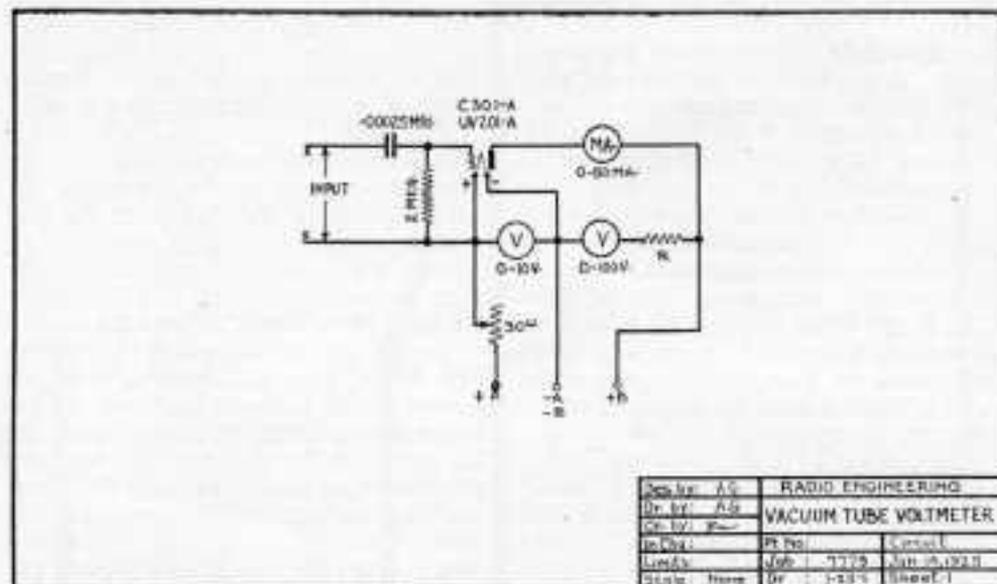


Fig. 1. The input leads are connected to the device across which the voltage is to be measured, and voltage determined by the calibration of the plate milliammeter.

## Our Laboratory Type Vacuum Tube Voltmeter

Complete description of an extremely accurate 201-A type voltmeter for measuring small voltages

THE vacuum tube voltmeter shown in the accompanying illustrations is one of the most useful measuring instruments we have in our laboratory at Darien. It provides a quick, accurate means of measuring potentials up to 2 to 5 volts, and possesses a feature which is invaluable in radio work, it does not draw any current from the circuit whose voltage is being measured.

The circuit is shown in the diagram, Fig. 1. The data on it was furnished to us by Mr. Samuel Cohen, Chief Engineer of the General Instrument Company. You will see that it is simply a UV 201 - A or C 301 - A tube connected up as a detector with measuring instruments in the various circuits. It operates on the principle of rectification and slight amplification produced by a vacuum tube when used as a detector. The voltage to be measured is applied at XX, across the

grid and plus filament side of the tube. The filament return lead goes directly to the plus side of the filament so that the grid is not biased. When a difference of potential exists between the grid and filament of the tube, the current flowing in the plate circuit is a function of this difference of potential. If, then, we apply various known voltages to XX and measure the corresponding plate currents we can plot a calibration curve with voltages as ordinates and plate currents as abscissae. After this has been done, any unknown voltage to be measured can be applied and corresponding plate current observed, and by referring back to the calibration curve the value of the unknown voltage found. Some may find it preferable to make up a scale for the plate milliammeter so that the voltage may be read directly.

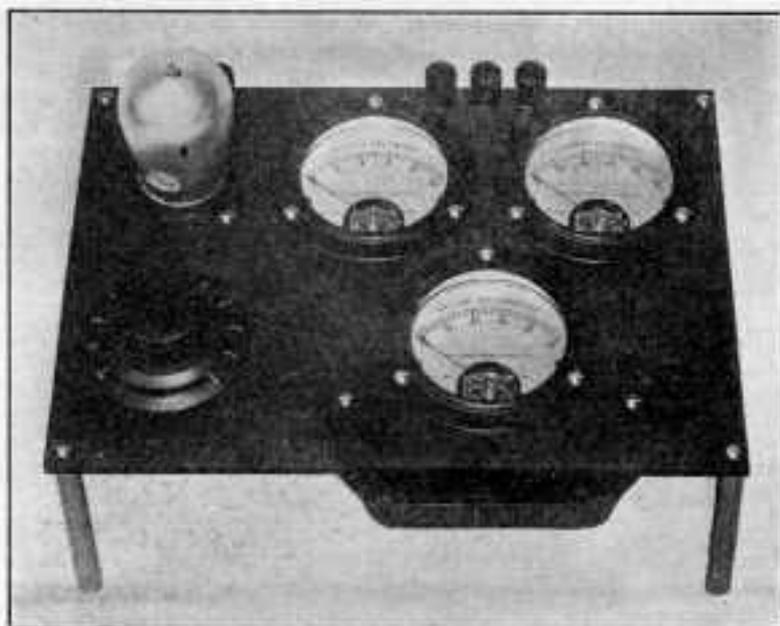


Fig. 2. When the filament and plate voltages have been adjusted, the voltage to be determined is read from the milliammeter.

The photographs of the top and bottom views together with the wiring diagram should give ample information for construction of one of these instruments. You will see that the parts are all fastened to a horizontal Formica panel measuring 7 by 10 in.  $3/16$  ins. thick, supported on four panel support pillars.

The arrangement of the instruments has been worked out very carefully. Notice that the rheostat is in front of the tube and in line with it. This puts the tube back out of the way so that it does not cause any interference when adjusting the rheostat or reading the instrument. The two voltmeters have been placed side by side in the rear as it is not necessary to refer to them after the filament and plate voltages have been checked up at the beginning of the test. This leaves the milliammeter in front by itself so that it is read instinctively without any mental interference caused by the presence of the two voltmeters. In addition this layout balances very well and makes the instrument attractive. The horizontal panel construction matches up with the receiver unit previously described, and with other instruments which will be taken up later.

The two Eby binding posts at the left are the XX posts. In the group of three, the left one is  $-A-B$ , the middle one is  $+A$  and the one on the right is  $+B$ . Since it is important that both the voltage applied to the filament and the B battery voltage be always of the same value as when the instrument was calibrated, two voltmeters have been included in the instrument. The filament voltmeter is a Weston model 301, 0 to 10 volts D. C. The plate voltmeter is a model 301, 0 to 100 volts D. C. with multiplier R. The plate current meter is a model 301, 0 to 50 milliamperes, D. C. An advantage of these instruments is that they can be placed either horizontally or vertically without affecting the calibration. The Kellogg No. 2 socket is supported to the panel by screws and two coil mounting pillars. The clips from a Daven grid leak mounting were removed from the base and fastened directly to the F and G terminals of the socket. A 2-megohm Daven grid leak, and .00025 mfd. and .005 mfd. Micadon were used. The 30-ohm General instrument rheostat is for fine filament control. The multiplier for the 0 to 100V. voltmeter is fastened to the panel with four coil mounting pillars.

Two pillars at each side are held together by a screw. Either a Pawood or Stevens adjustable circle cutter can be used to cut the holes in the panel for the various instruments.

Possibly the simplest way to calibrate the instrument is to pass an alternating current through a potentiometer arranged for obtaining a variable voltage. The voltage for each setting of the slide

voltage can vary by two or three volts from this value, and the ordinary Eveready B battery can be employed. Moreover, with 80 volts on the plate, the filament voltage can be varied between about 3.6 volts and 4.2 volts with a change in calibration of only about 2%. So the ordinary storage battery is all right for a filament current supply for, by means of the rheostat, the filament

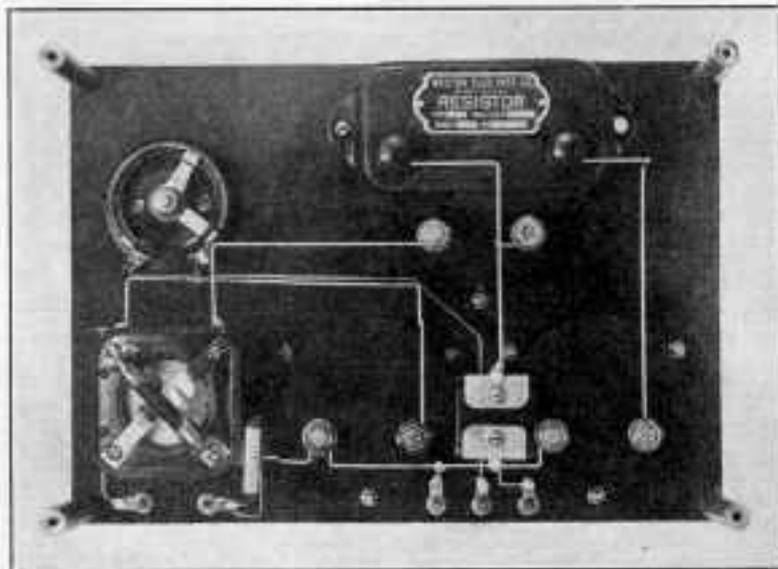


Fig. 3. Here is a view of the underside of the vacuum tube voltmeter

arm can be read with an AC voltmeter. The source of alternating current can be an ordinary 60-cycle lighting supply. There is no need to doubt a calibration at low frequency, for with the .005 mfd. condenser connected as shown, the calibration will hold good for all frequencies as long as the same tube is used.

The calibration is made by observing and plotting the various readings of the milliammeter as the applied emf. is varied and measured. If the voltage to be measured does not exceed 2.5, the calibration curve is a straight line which cuts one of the axes.

Small changes in plate voltage affect the calibration less and less as it is increased, in fact if it is about 80 volts, a change of 4% in its value has no effect whatsoever. This is fortunate since, by using say 80 volts on the plate, the plate

voltage can be held at about 3.7 volts, making the life of the tube almost indefinite. Changing the grid leak from 2 to 4 megohms changes the calibration about 4% so that any slight changes in its resistance caused by atmosphere conditions will have no detrimental effect on the instrument.

It is almost impossible to sit down and think of all the uses to which the voltmeter can be put. A few of its uses in radio work, as applied to everyday laboratory testing will be mentioned. It may be used to measure the amplification produced by either audio or radio frequency amplification at any frequency by measuring the potential difference between the grid and filament of each tube. This makes it possible to ascertain the performance of an amplifier exactly since no load is put on the coil.

# RADIO ENGINEERING

M. B. SLEEPER, Editor  
F. A. SKELTON, Managing Editor

Published monthly by  
M. B. SLEEPER, Inc.  
Publication Office, Lyon Block, Albany, N. Y.  
Editorial and General Offices  
A-52 Vanderbilt Ave., New York, N. Y.  
Chicago Advertising Office  
Morley Company, 157 E. Ontario Street.

Twenty cents per copy in the United States and Canada; in foreign countries one shilling. Two dollars per year, twelve numbers in the United States and Canada; ten shillings in foreign countries.

Copyright 1924 by M. B. Sleeper, Inc.

Vol. V      FEBRUARY, 1925      No. 2

## EDITORIAL

**J**UDGING from the way rumors spread throughout the radio industry, from dealer to jobber to manufacturer and publishing house, with a speed that suggests simultaneous broadcasting, a lot of us must think we're back in the Army. The only difference is that rumors didn't really amount to much then, but now they make the difference between dollars and sense.

Right now we are being told that radio parts are not selling. Dealers, all of a sudden, have assumed the elbow-on-the-counter pose, and are sighing over the recent and very serious falling-off in parts sales. As usual, the dealer asks plaintively, "Why don't they buy?" instead of taking stock of himself by asking, "Why don't I sell?"

If parts manufacturers find their sales falling off, and their dealers complaining that parts won't move, it may be that sales have dropped, or that they are moving in disguise.

To expand — Parts must be sold. It isn't enough to put them out on the shelves, just as the manufacturer who simply offers a high quality instrument does only half the work that must be done to start repeat orders on their way. Nor is the manufacturer doing his part by displaying his wares in the advertising sections of newspapers and magazines.

In 1920, approximately one million dollars' worth of radio equipment was sold, bought by real experimenters who were doing more or less original and independent work. But the people who bought two hundred million dollars' worth of parts in 1924 are of a different class. They are novices, men and boys who, in most cases, made their initial attempt to assemble the wonderful this-circuit or that-circuit they read about. And, sad to relate, a very high percentage of the home-built sets, assembled from assorted parts, didn't work, nor did the dealer who sold the parts help much to straighten out the troubles. With certain exceptions, parts sales have dropped off, and for the very good reason that the sets built from them haven't been satisfactory. Why? Because the manufacturers haven't shown the set builders how to use the parts, because most magazine and newspaper articles don't give sufficient instructions, or purposely omit the names of the particular instruments which should be used, and because the dealer can't do the work that the manufacturers, the magazines, and the newspapers should do for him.

On the other hand, some parts are selling very well indeed because, through carefully planned advertising, publicity, and instruction booklets, set-builders have been shown how to use them successfully. An excellent example of this is the campaign of the Rauland Manufacturing Company.

Then there are the parts "moving in disguise." Dealers don't think of construction kits when they say "Parts are dead." If you think that radio sales are all on complete outfits, ask Acme Apparatus, Erla, Phenix, Freshman, and the other kit manufacturers, or try to get deliveries on the National units.

Companies making parts and materials must get them out in the form of kits, or sell the parts to other companies that do put out kits. Parts will be sold in greater quantities in 1925 than in 1924, parts will always be sold and in huge quantities, but an increasing proportion of them will be disguised as construction kits.

M. B. SLEEPER,  
*Editor.*

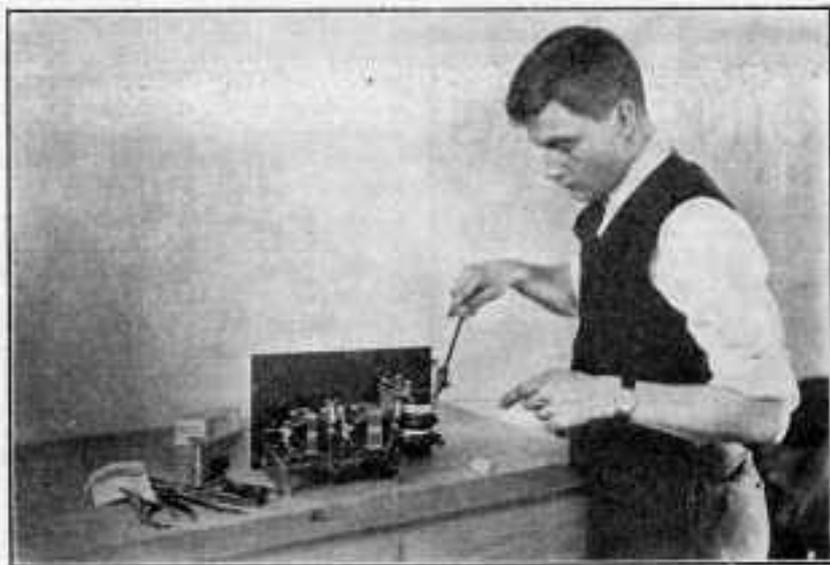


Fig. 1. Putting the finishing touches on the Rasla set at the Darien laboratory

## Rasla Reflex-2

The popular two-tube Rasla Reflex makes a powerful, compact, and attractive set capable of operating a loud speaker.

**W**E HAD read and heard so much about the new Rasla type two-tube receiver that we had to make up one for ourselves. After testing out the circuit thoroughly and making little changes here and there the problem resolved itself into the construction of a compact unit which could be easily built and used as a portable set if desired. The hardest job was to arrange the parts so that the wiring would be short and simple and yet preserve the high efficiency of the receiver. In presenting the type 7100 receiver we feel that all of the obstacles have been surmounted. The set is small, measuring 7 by 12 ins., by 7 ins. deep. At the Darien laboratory we brought in all of the broadcasting stations around New York City as well as many DX stations on the loud speaker. The set is extremely selective when used with an aerial about 60 feet long.

**The Rasla Reflex Circuit** The circuit employed in this set is not of the trick variety, but rather depends for its high efficiency on the correct design of the various parts. Referring to the schematic wiring diagram you will notice that

the Rasla tuning unit consists of an un-tuned primary with a tap for use with long aerials, and a secondary coil tuned by a 0.0003 mfd. Cardwell variable condenser. The condenser tunes the entire secondary winding, but only part of the coil is included in the grid circuit. This increases the selectivity. Oscillations are controlled by a small two plate Rasla balancing condenser used in conjunction with the remainder of the secondary winding. This condenser also serves as a volume control. The first tube is reflexed to provide both radio and audio frequency amplification. The interstage Rasla radio frequency transformer is designed so that its impedance matches that of the fixed Rasla crystal detector, giving efficient coupling. The high ratio Modern A. F. transformer used in the first stage has a low primary impedance to match that of the crystal detector and provides the unusual kick peculiar to this circuit. A .00025 mfd. Micadon bypasses the radio frequency current around the secondary. The second stage of straight A. F. amplification uses a low ratio Modern transformer to prevent dis-



riable condenser is fastened in the position shown so as to make the connections as simple as possible.

**Standard Parts** The panels may be either of Formica or Celoron. The Required front panel measures 7 by 12 ins., 3-16 ins. thick, the tube panel is 7 by 6 $\frac{3}{8}$  ins., 3-16 ins. thick, and the binding post strip is 2 by  $\frac{5}{8}$  ins., 3-16 ins.

coil mounting pillars, thirty-five soldering lugs, twentytwo  $\frac{1}{2}$  in. 6-32 R. H. machine screws, and twenty nuts.

**Drilling** If you desire, you can scale off the location of the holes in the Panels tube panel from the picture wiring diagram, as it is shown at exactly one-half size here. However it is easier to work from the full size blueprints.

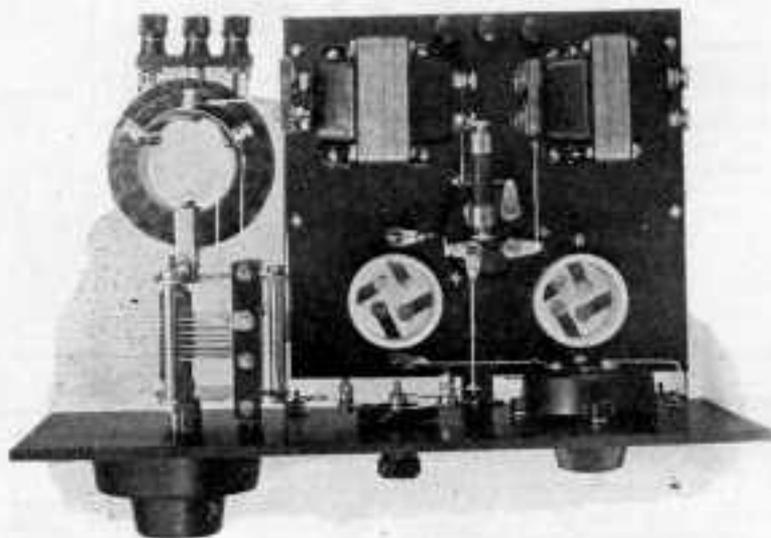


Fig. 3. The Benjamin mounting brackets helped us in working out an attractive mechanical design.

thick. The instruments required are a Rasla tuner, fixed crystal detector, compensating condenser and knob, and type CR radio frequency transformer, a Modern 1 to 10 and 1 to 4 ratio A. F. transformer, two General Instrument Isolantite sockets, one Cico 30-ohm rheostat and knob, a pair of Benjamin panel support brackets, 1-A Amperite, Carter 3-spring filament control jack, six Eby or Marshall-Gerken binding posts, Cardwell 0.0003 mfd. variable condenser, two 0.00025 mfd. type 601G Micadons with grid leak clips, and one 4-in. Accuratune vernier dial. In addition there are the following standard small fittings: Five

All of the screw holes in the tube panel are made with a No. 18 drill, and the holes through which the wires pass are made with a No. 27 drill. The holes for the sockets are 1 $\frac{3}{8}$  ins. diameter and the hole for the R. F. transformer 1 $\frac{5}{8}$  ins. diameter. These can be easily cut with a Pawood adjustable circle cutter. This tool is inexpensive and is very useful around the laboratory.

**Assembly and Wiring** Fig 5 shows a picture wiring diagram of the set, in which the connections have been drawn exactly as they were arranged in the original receiver. The diagram is drawn looking up at the bottom of the set.



Place the lugs on the instruments as they are mounted, having them pointing in the directions shown by the short heavy lines in the picture wiring diagram and have nuts tightened securely. Spintite wrenches are very good for this work.

1. Put the R. F. transformer through the middle large hole in the tube panel and fasten its base to the panel with three  $\frac{1}{2}$ -in. 6-32 R. H. machine screws and nuts. Be sure that the terminals are located correctly. Remove the two nuts from the P and -F terminals of each socket and put a coil mounting pillar on each screw instead. Now

thick core, goes on the left, looking at the panel from the top-front. Flatten out the grid-leak clips on the two Micadons and mount one on the secondary of the 1 to 10 transformer and one on the primary of the 1 to 4 A. F. transformer. Fasten a soldering lug to the Micadon on the 1 to 10 transformer with a  $\frac{1}{2}$ -in. 6-32 R. H. screw put through the front eyelet hole.

2. On top of the panel, connect 1, the P. terminal of the R. F. transformer, to 2, the lug which is fastened to the P. terminal of the left hand socket, looking at the panel from the front. Con-

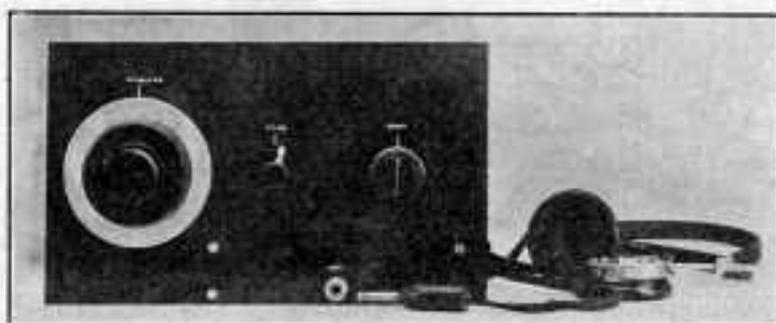


Fig. 4. All the tuning is done with the Accuratune dial, the center knob being for the control of regeneration only

fasten the sockets to the underside of the tube panel by means of a  $\frac{1}{2}$ -in. 6-32 R. H. screw threading into the coil mounting pillars from the top of the panel. Before fastening the left hand socket, remove the mounting clips from the base of the Amperite, and cut off the clips where they bend over the ends of the base. Mount one of these clips under the coil mounting pillar on the -F terminal of this socket so that when the screw is put in from the top of the panel the whole unit is clamped tightly together. Mount the other Amperite clip on the panel with one of the F. H. screws from the Amperite base. Snap the Amperite in place between the clips. Mount the three binding posts on the panel with the holes pointing to the back edge. Fasten the two Benjamin panel support brackets to the panel with the R. H. screws and nuts provided. Now mount the two A. F. transformers on top of the panel with  $\frac{1}{2}$ -in. 6-32 R. H. machine screws and nuts. The 1 to 10 transformer, the one with the

connect 3, the B terminal of this transformer to 4, the P terminal of the 1 to 4 A. F. transformer. Connect 5, the F. terminal of the R. F. transformer to 6, the P terminal of the 1 to 10 transformer.

3. Put a lug on each terminal of the Rasla crystal detector.

4. Solder one lug 7, to the lug on the G terminal of the R. F. transformer. Solder the other lug 8, to that on the primary F terminal of the 1 to 10 transformer. These lugs may have to be twisted slightly in order to get the crystal detector straight. Now turn the tube panel upside down and connect the two +F lugs on the tube sockets together. This is connection 9. Connect 10, the secondary F terminal of the 1 to 4 transformer, to 11, a point on the panel support bracket. This wire runs through the small hole in the panel. Connect this same point, 11, to 12 and through the small hole in the panel to 13. Connection 12 is made to the lug on the Amperite terminal and 13 is the secondary

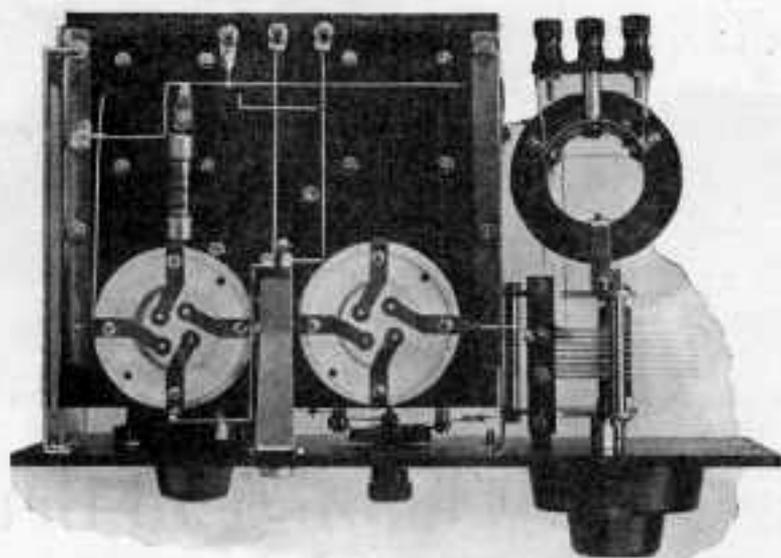


Fig. 6. The under side of the Rasla-2 is quite as neat as the top

F terminal of the 1 to 10 transformer. Connect 14 a point on this wire to 15, the —A binding post. Connect 16, the G terminal of the 1 to 4 transformer, to 17. Keep this wire clear of connection 11.

5. Mount the jack on the front panel, keeping the frame toward the bottom. Loosen the set screw in the knob of the compensating condenser, and take off the knob, pointer, lock nut, and washer. Fasten the condenser to the panel with the lock nut and washer, keeping the rotor plate terminal facing the side of the panel where the Cardwell condenser is to be mounted. Put on the knob and dial so that the dial is vertical when the rotor plates are halfway interleaved with the stator. Mount the rheostat on the panel, and fasten the knob so that the arrow points to the line on the panel when it is turned all the way to the left. Mount the two outside binding posts on the small terminal strip, putting a lug under each nut. Remove the outer nut from the SA terminal of the Rasla tuner and screw a coil mounting pillar on it. Now put the middle binding post through the terminal strip and screw this into the free end of the coil mounting pillar, keeping the strip parallel to the tuner coils. Mount the two legs of the tuner

unit to the end plate of the Cardwell condenser, fastening them with  $\frac{1}{2}$ -in. 6-32 R. H. machine screws threaded into the two holes which you will find in the end plate. It so happens that these holes in the end plate are spaced correctly for the mounting.

6. Connect the LA terminal, 18, of the tuner to the LA binding post, 19. Connect the GND terminal, 20, to the GND binding post, 21.

7. Mount the condenser and tuner unit on the front panel with the three flat head screws. Put the Accuratune dial on the shaft so that the 100 division line coincides with the line engraved on the panel when the condenser plates are totally interleaved. If you use the old style Accuratune you will find it necessary to cut off the shaft of the condenser just a little bit, so that the dial will fit flush up against the panel. Make sure that you press the dial on firmly before tightening the set screw for, otherwise, the cork friction disc will not hold. Remove the two binding posts from the rheostat and put on lugs and ordinary nuts instead. Fasten the front panel to the brackets on the tube panel with the four flat head machine screws provided. Make sure that the nut on the top screw

(Concluded on page 91)



## Spark-Coil Windings for Better Radio Transformers

The helical windings used for Samson transformers were developed for spark coil, but this method has special advantage for radio use not found in the layer-wound coils

SEVERAL years ago the Samson Electric Company undertook the development of a combination ignition coil and spark plug for use on motor boats. The purpose of the devices was to eliminate high tension wiring which would break down when, in heavy weather, the engine and ignition system got wet. The necessity for making the ignition unit very small complicated the problem of winding coils which would stand up under the high voltage. Layer wound coils were unsatisfactory because of the high potential difference between the layers and the paper between layers increased the mechanical dimensions considerably.

To overcome these two difficulties, experiments were carried out on winding coils in vertical pies, one turn thick, instead of making them in horizontal layers. This work extended over a period of several years and, by the time the winding machine was perfected, there was no demand for the ignition units be-

cause motor boat engines had begun to use regular automobile ignition systems.

Then the Samson Company discovered that, in working on spark coil design they had produced an ideal type of radio transformer winding.

The helical winding machine is an exceedingly clever mechanism for it does a most unusual job in a very simple way. However, the action of it cannot be described intelligently without photographs and the details of the machine are not yet available. The effect of the winding method, however, is to produce a coil in the form of a continuous winding in which the turns form flat spirals, alternately wound from the inside out and the outside in. Some people have been under the impression that the coils were wound in the form of separate pies subsequently joined together. Actually, the winding is continuous, the spindles revolving at the same speed throughout the entire winding process.

As to the advantages of the system:

The difference in potential between pies is much lower than between layers in a layer-wound coil. Consequently, no paper insulation is required. In the Samson transformers, the coils are of average size but larger wire is employed than would be possible with paper insulation. Reducing the potential difference also decreases the capacity effect in the coils. A perfect transformer would have no capacity effect for, then, there would be no tendency to by-pass the audio frequency currents through the transformer instead of doing their work by following through one turn after another in the coil. This effect becomes very marked as the frequency increases. In reflex sets radio and audio frequency transformers are put in series and the radio frequency currents by-pass around the transformer without going through the windings at all.

The accompanying illustrations shows the Samson audio and long wave transformer, in which the helical windings are employed. The audio frequency transformers are at the right and the long wave and filter transformers at the left and center. The audio transformers, however, are not furnished with the super kit.

Altho these transformers go through a number of very elaborate tests as a part of the inspection and the main-

tenance of electrical and mechanical standards, the final tests are particularly interesting.

Samson audio transformers are not tested for short circuits, open circuits, or short circuited turns. Instead, each transformer is measured for the actual amplification it produces at audio frequencies. In this way an additional check is obtained upon the quality of the core iron, the insulation, and the winding of the coils. As a matter of fact, this is the only way to get a final and complete check upon an audio transformer.

The long wave and filter transformers are similarly tested. At the same time, while the amplification is being measured, an adjustable oscillator is employed by means of which the transformers are matched. On the bottom of each long wave transformer you will find a number written in pencil. This number indicates the setting of the oscillator condenser at which maximum amplification was obtained. On the condenser scale, 12 divisions represent a change of one kilo-cycle. Each transformer is marked with the condenser scale reading and, in this way, the transformers are matched and put into kits. Therefore, the matching is accurate to one-twelfth kilo-cycle.

### Rasla Reflex-2

(continued from page 89)

on the right hand bracket has a tinned lug under it.

8. Turn the set so you are facing the bottom of the tube panel and connect 9, the junction of the F+ terminals of the sockets, to 22, the lower right hand tab of the jack. Connect 23, the +B binding post, to 24, the right hand tab next to the frame. Connect 25, a point on this wire, to 26, the primary F terminal of the 1 to 4 transformer. Connect 27, the +A — B binding post, to 28, the lower left hand tab of the jack. Connect 29, the remaining tab on the jack, to 30, the P terminal of the left hand socket. Connect 31, the G terminal of the right hand socket, to 32, the stator terminal of the Cardwell condenser. Keep this lead clear of the bracket. Turn the set right side up again

and connect 33, the lug under the nut on the bracket, to 34, the outer terminal of the rheostat. Connect 35, the other rheostat terminal, to 36. Connect 37, the P terminal of the R. F. transformer, to 38 on the compensating condenser. Connect 39 to 40. 40 is a lug under the spacer rod of the Cardwell condenser. Connect 41, the —A terminal of the tuner, to 42 on the .00025 Micadon. 41 is shown as a free dotted line in the picture wiring diagram. Connect 43, the C1 terminal of the tuner, to 44 on the rear end plate of the condenser. Connect 45, the C2 terminal, to 46 the top stator terminal of the condenser.

This completes the assembly and wiring of the set. It will be well to check over every connection against the picture wiring and schematic diagrams as well as the illustrations.

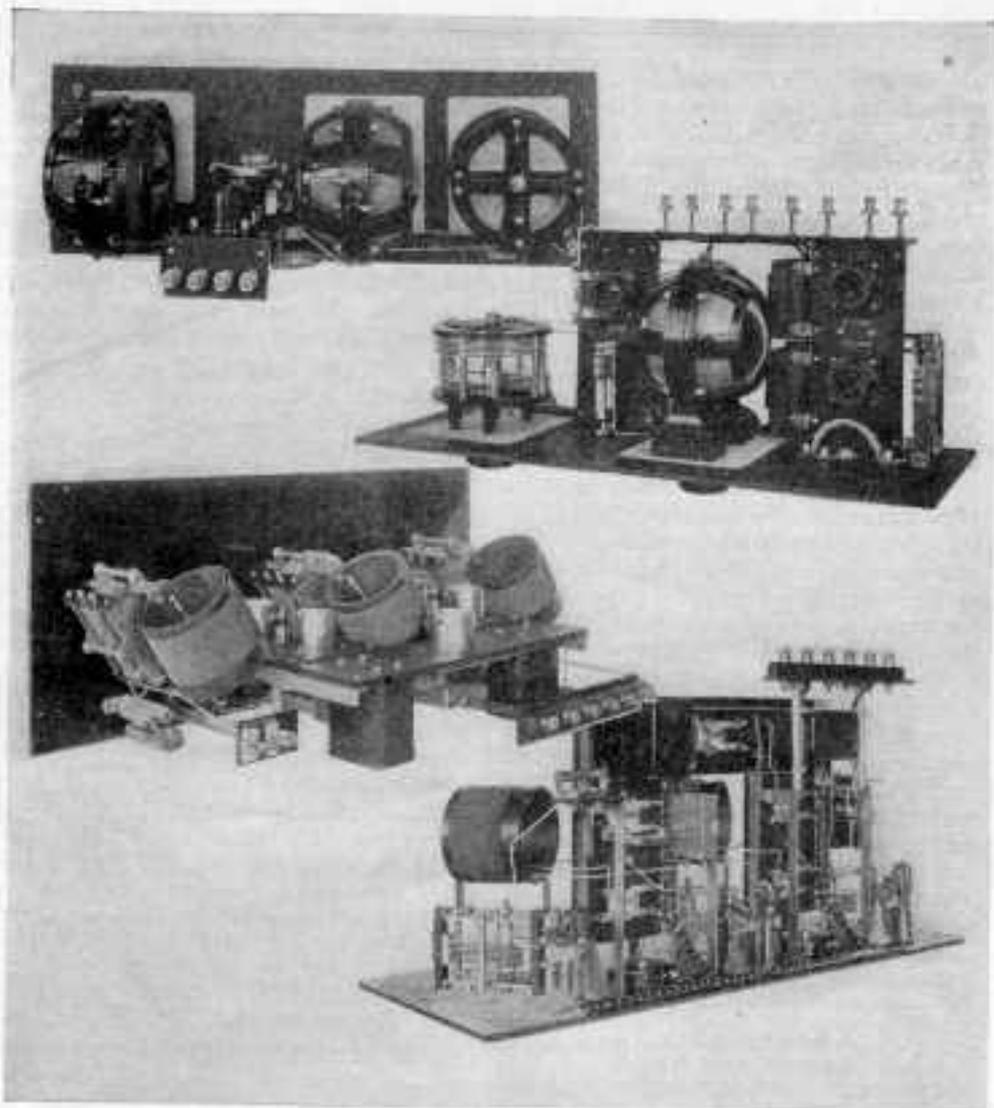


Fig. 2. Examples of sturdy designs as developed by Cardwell and Grebe

## Are Standards Changing?

There seems to be a tendency toward flimsy, awkward designs, indicating a lowering of the standards set during the 1923 season

**R**ADIO instruments are, by their nature, really precision devices. That is, they should be substantially designed so as to maintain themselves against long and hard use. It is necessary for them to be substantial mechanically, the insulation must be strong and permanent,

they must not develop faults, the coils must be carefully wound, and the condensers must maintain their alignment. It is upon these factors that continued satisfactory operation depends.

Experienced designers of radio apparatus realize the importance of these

points and, unless they are prevented from doing so by the policy of the companies employing them, make a conscientious effort to work out the details as well as the assembly in a creditable manner. Unfortunately, however, they are sometimes prevented from doing their best because of the unwillingness of the concern to make the necessary investments to produce good equipment on an economical basis. Moreover, there are many men designing radio equipment

out of the business but, fortunately, this is true only in specific instances.

It is rather alarming, for example, to see wooden panels and parts employed in radio sets. Wood is not satisfactory because it lacks permanence and the necessary insulating qualities, and is liable to cause trouble from splitting in transit or warping in use.

The accompanying illustrations show a few examples of really good design. In Fig. 1, at the top, are two Grebe sets.

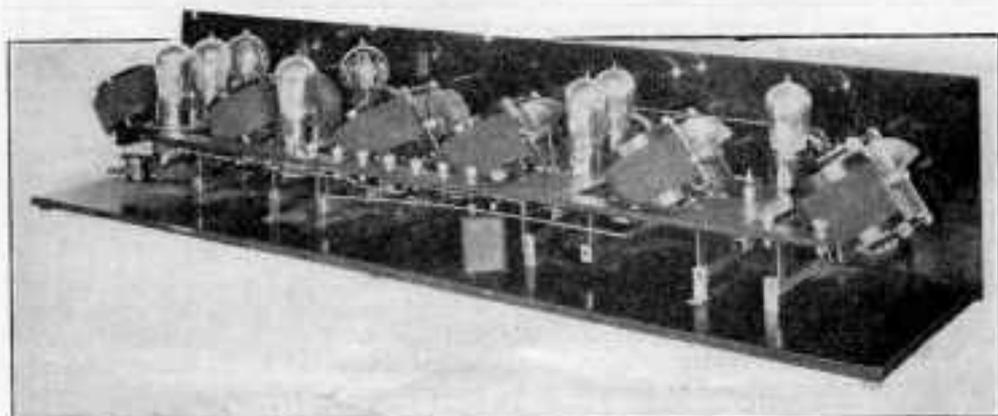


Fig. 2. This tuned intermediate frequency super-heterodyne from Cardwell's gives the impression of construction made to last

who are not familiar with the fundamentals of correct design.

Judging from the apparatus produced in 1924 and some of the 1925 models, the standards of design are being lowered or else there is an increasing amount of apparatus developed by inexperienced men.

Price competition may be responsible for this change. With the greater production and the increased resources of radio concerns it is hard to understand why they are not making better equipment today. Instead, so many of our receiving sets are flimsy mechanically, provisions for insulating are unsatisfactory, and a general impression of cheapness is most apparent. There are concerns, of course, who are simply capitalizing their present opportunities with the idea of getting out large stock issues, after which the present management will step

Comparing these with almost any of the outfits now found in radio stores the reasons for the foregoing remarks are quite obvious. The lower illustrations show some of the first Adler neutrodyne outfits built for that concern by Allan Cardwell. Of course, a great deal is to be expected from the Cardwell Company because one of their specialties is the manufacture of the Kolster decimeter and the Bureau of Standard's wavemeters, as well as precision instruments for the Western Electric Company. In Fig. 2 a special receiver, also from the Cardwell Company, is illustrated.

There is no reason why the standards of design should not be raised from year to year. In fact, manufacturers are bound to come to the realization that a great part of their service expense is a result of their failure or unwillingness to build quality and substance into their receiving sets.

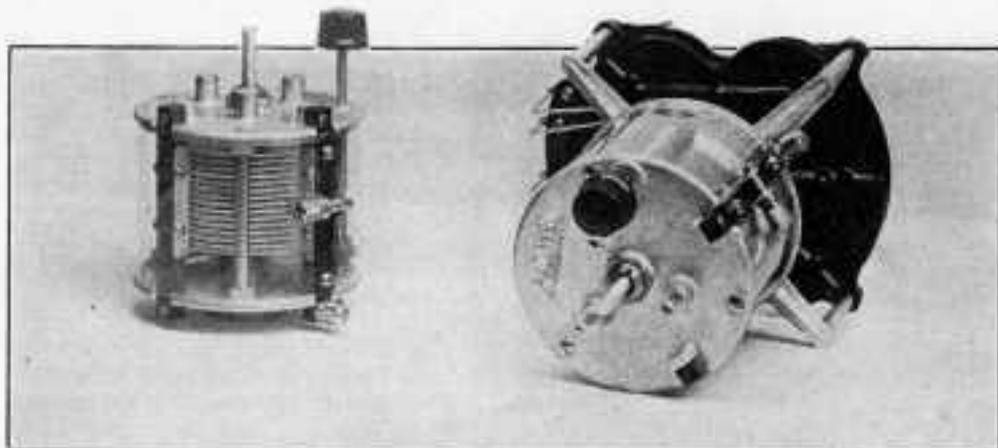


Fig. 1 The key instruments in the tuning circuits of the Cabot set

## Cabot Circuit Receiver

While New York may be the radio center, Boston is producing a large share of the new things. Sewell Cabot, of the Acme Apparatus Company, is responsible for this remarkable inductance-tuned reflex receiver

Have you a long distance receiver? Easy, now before you answer, for you may have to alter your reply. Mr. Zwicker, of the Acme Apparatus Company makes a standing offer that he will pay ten dollars each night he does not hear the Pacific coast from Boston, receiving on a small loop, to anyone who will pay him ten dollars every night he gets across. Is your set that kind of a long range outfit?

The set Mr. Zwicker uses is the new Cabot reflex, developed by Sewell Cabot for the Acme Company. Mr. Cabot, by the way, is one of those rare engineers who can conceive that a certain thing is possible, and can then make the possibility an actuality. And, while he is very much of a theorist, he has surprised many of us who were inclined to criticize the design of the instrument upon which the success of the circuit is most dependent.

In Figs. 1 and 2 you will see the D-coil unit, a tuned R. F. transformer, mounted on the shaft of the variable condenser which tunes the loop. The unit comprises a rotor and stator, each carrying two D coils. One rotor and one stator coil are in series, serving as the primary, and the other rotor and stator coils form the secondary of the R. F.

transformer. In Fig. 3 you will see that a fixed condenser of 0.0004 mfd., a special type of Dubilier Micadon, is connected across the R. F. transformer secondary.

Thus there is, in the tuning unit, a variable condenser working with the fixed inductance of the loop and a variable inductance working with the fixed capacity of the Micadon. A second variable condenser is put across the Micadon, but it is only for close tuning, to compensate for any inaccuracy in the tuning from the R. F. transformer secondary. The condenser is varied only a few degrees over the entire wavelength range. Therefore, this set is practically a mono-control outfit, since the second condenser is only used to bring the signals to the peak of intensity.

While the tuning unit is sold separately, for those who want to experiment with it, the complete construction kit is more interesting and much safer to use since the design for the set has been worked out with such great care. Every item necessary is included in the kit—front panel, base-board, tools, and all the other parts and devices. With no other kit are such full instructions given. There is a drawing which shows the exact dimensions and shape of each wire,

so that the connections can be formed first and fitted to the terminals afterward. By careful planning, all butt joints have been eliminated. Consequently no soldering is required, although lugs are furnished for those who prefer soldered connections. The assembly instructions are arranged in steps following each other in

similar to the familiar four-tube Acme reflex, except that only one tube is reflexed. You will note that one side of the reflex A. F. transformer is not connected. This is done purposely, because of the characteristics of the Sodian. The complete circuit provides one stage of tuned R. F., two stages of transformer

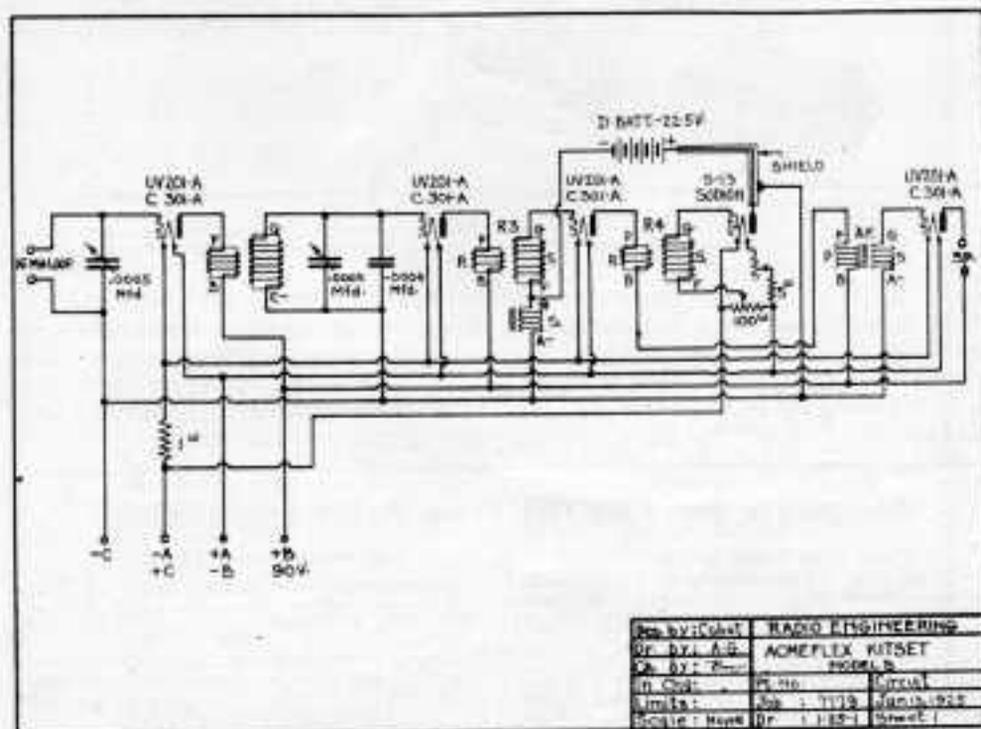


Fig. 3. Another innovation in this set is the use of an S-13 Sodian for the detector. This accounts in part for the sensitiveness of the set and the quality of reception.

the proper sequence to make the work as easy as possible.

Another unique feature of this set is the use of an S-13 Sodian tube for the detector. In fact, the extreme sensitiveness of this set, as well as the excellent tone quality, is due to the Sodian. A standard socket with an adapter are provided in order that a UV201-A or DV-3 tube can be used as a detector. This is the first multi-tube set designed for an S-13 detector, although other concerns will probably arrange for its use as soon as the manufacturers can make further increases in their production schedule.

The amplifying part of the circuit is

coupled R. F. detector, a stage of reflexed A. F., and a stage of straight A. F. amplification, UV201-A or DV-2 tubes can be used for the amplifiers.

No rheostats are provided for the amplifiers, the 1-ohm resistance in the -A lead being relied upon to regulate the current. While this is contrary to customary practice, it seems to work out in a satisfactory manner, although a rheostat would give a better control. Both a rheostat and potentiometer are used with the Sodian, because it is more critical than the amplifiers. The pot-rheo, or combination rheostat and potentiometer, is shown between the A. F. transformers

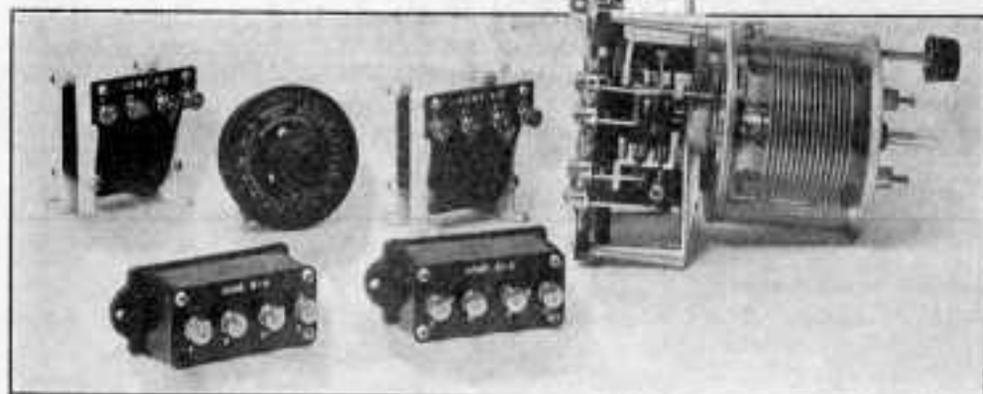


Fig. 2. The complete construction kit includes the A. F. and R. F. transformers, pot-rheo, tuning instruments, and every single item that is needed to complete the set.

in Fig. 2. It is fitted with two concentric resistance elements and concentric shafts which move the two contact arms. By turning the smaller knob at the front the potentiometer can be regulated, or the rheostat adjusted with the larger one.

A construction article describing the assembly and operation of this set is now in process at the Darien laboratory. You will find it in the March or April issue of *RADIO ENGINEERING*, illustrated with photographs and diagrams.

## Blueprints You Can Get From Radio Engineering

### ONE-TUBE SETS

**3 CIRCUIT REGENERATIVE RECEIVER**, the famous X-1900 type, sharply tuned and very sensitive. 150 to 600 meters. Type X-1900, 3 sheets..... 75c.

**REINARTZ RECEIVER**, one of the most popular models ever described in *Radio Engineering*. A splendid set for all-around broadcast work. Type 3300, 4 sheets..... \$1.00

**ONE-TUBE REFLEX RECEIVER**, using an Acme R-2 transformer and a crystal detector. Type 4200, 3 sheets..... 75c.

**TC CIRCUIT SET**, a 2-control regenerative receiver exceptionally sharp and sensitive. Particularly adapted for indoor antennas. Type X-4000, 3 sheets..... 75c.

**IMPROVED RASLA REFLEX**, unusually attractive in design as well as in the results produced. This set is also intended for a small antenna. Type 3900, 3 sheets..... 75c.

**HAYNES TUNER**, known as the "One Thousand Miled for Fifteen Dollars" set. 2 sheets..... 50c.

**R-D-X REFLEX**, brings in local stations on a loud speaker and distant stations with surprising volume. Type 6400, 3 sheets, 75c.

### TWO-TUBE SETS

**TUNED RADIO REFLEX**, using fixed couplers tuned by variable condensers for maximum amplification. Type 5100, 3 sheets..... 75c.

**NO-LOSS REGENERATIVE RECEIVER**, with condenser control for feed back. Equipped with 1-step AF amplifier. Type 6300, 3 sheets..... 75c.

### FOUR-TUBE SETS

**BROWNING-DRAKE 201-A**, using one UV199 and three UV201-A tubes, the 100% receiver. Type 6600, 6 sheets..... \$1.50

**BROWNING-DRAKE 199**, using UV199 tubes thruout, designed for dry cell operation. Type 7000, 5 sheets..... \$1.25

**DX RECEIVER**, because of its high efficiency, owing to the use of tuned RF, this is one of the most popular sets ever described in *Radio Engineering*. Type 5300, 6 sheets.... \$1.50

**PORTABLE TUNED RF RECEIVER**, similar in design to the Type 5300 set, but very compact and built for UV-199 tubes. Type 5800, 3 sheets..... 75c.

**4-TUBE REFLEX**, with the standard Acme circuit in an improved design. Can be used with the Run-A-Radio battery substitute. Type 6500, 5 sheets..... \$1.25

### AMPLIFIERS

**2-STEP AF AMPLIFIER**, designed for use with any type of receiving set where additional amplification is required. Type 3100, 3 sheets..... 75c.

**4-TUBE AMPLIFIER**, with one stage of transformer coupling and three stages of resistance coupling. Gives tremendous undistorted amplification. Type 6200, 3 sheets..... 75c.

**HAYNES AMPLIFIER**, two stages AF. Can be used with any set, although it is designed particularly for the Haynes tuner, 2 sheets..... 50c.

### DV-3

For dry battery. Filament potential 2 volts; Filament consumption 2/100 of an ampere. Price \$4.00.



### DV-2

For average battery. A general purpose tube for use with 6 volt battery. Filament potential 4 volts; consumption 27/100 of an ampere. Price \$4.00.

## One radio trouble you can stop

**Y**OU can't prevent static. You can't hold up your hand and stop interference from surrounding sets. These things affect the reproduction of the finest set made.

But you can see to it that your reception is not handicapped by imperfect tubes. You can make sure your tubes detect and amplify without distorting the sound that comes to them or adding to that sound the common tube noises.

De Forest Audion Tubes are the remedy for such radio and tube trouble. They transmit incoming sound waves clearly, accurately, with freedom from microphonic noises—rings, sings, and howls. De Forest Tubes reproduce exactly the richly soft beauty of the most

delicate tones as well as the full volume of the strongest.

You have a right to expect De Forest Tubes to be all that good tubes should be. Lee De Forest, one of radio's greatest geniuses, invented and perfected them. His first three-electrode vacuum tube was the forerunner of all present-day tubes. With his tube he made modern broadcasting possible.

De Forest Tubes are economical of battery current, are constructed to withstand sudden current overloads, have standard bases, and can be used on all standard circuits. Try De Forest Tubes in your set and use them for experimental purposes.

DE FOREST RADIO COMPANY  
Jersey City, N. J.

# DE FOREST TUBES

Mfg. U. S. Pat. Off.

The "Magic Lamp" of Radio

# The Splitdorf Self-Neutralized R. F. Receiver

In this five-tube set, the problem of neutralization has been attacked in a unique manner incorporating many interesting mechanical features. Part 2

7. Fasten the binding post panel to the baseboard with the three 1-in. F. H. wood screws provided. Bend the soldering tabs on the jack so that they fan out giving room for a connection.

8. Bend a piece of bus wire in the form of a U and connect 13 and 14, the two outside springs of the jack together. The horizontal part of this wire should just clear the baseboard. Connect 15, the B Amp + binding post, to the middle point of this wire. Run the wire close to the baseboard and 1-in. from the edge. Connect 16, the Speaker + binding post to the second jack spring from the left, running this wire  $\frac{3}{4}$ -in. from the top of the baseboard and  $\frac{3}{4}$ -in. from the edge.


9. Mount the 1 mfd. by-pass condenser at the back edge of the baseboard flush against the binding post panel, using the two short R. H. wood screws provided. Mount the deck assembly in place using the four long wood screws, and brass spacers. The three tube sockets face toward the front panel.

10. Turn the set on end so you are looking at its left hand side. Connect 17, the front terminal of the A. F. transformer under the deck, to the fourth spring of the jack from the left. Connect 18, the other terminal of the transformer, to the second jack spring from the right. Connect 19, the lug on the end socket under the deck, to the third jack spring from the left. This completes the jack wiring. Connect the free end of the copper braided wire from 2, the left hand terminal of rheostat No. 2, to 20, a lug under the deck. Connect 1, the right hand terminal of rheostat No. 1, to 21 in the same manner. Con-

nect 22, the left hand stator terminal of condenser No. 2, to 23, a lug under the deck. Use a piece of the flexible braided copper wire for this connection. Solder the 2-in. piece of bus wire sticking up from the Speaker—binding post to terminal 24, directly over it, under the deck. Do the same with the wire from the C Bat— post to 25, and from B Det + to 26. Connect the 4-in. wire from the B Bat— post to 27 on the deck, and 28, the left hand terminal of the 1 mfd. condenser. Make sure that this wire clears connection 26. Connect 29, the right hand terminal of this condenser, to the B Bat + binding post.

11. Mount the two radio frequency transformers, the shorter tubes, behind the I plate condensers, making sure that the two heavy-wire primary terminals face the binding post panel. Use the short R. H. wood screws put into the holes drilled in the baseboard.

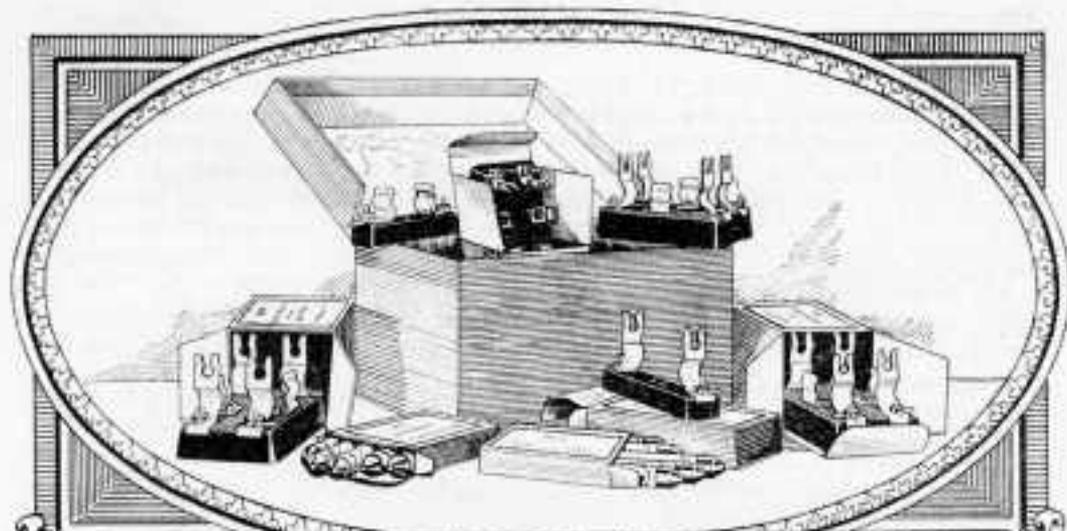12. Connect 30, the rotor terminal of 17 plate condenser No. 2, to 31 on R. F. transformer No. 2. Connect 32 on this same terminal to 33, a lug on the A. F. amplifier units. Use a piece of the copper braided wire for this connection. Connect 34, the right hand stator terminal of the same condenser, to 35, the front right hand terminal of R. F. transformer No. 2. Connect 36, the P terminal of the left hand socket, to 37, the rear right hand terminal of the R. F. transformer. Connect 38, a point on the wire connecting 29 and the B Bat + binding post, to 39 and 40. 40 is the rear left hand terminal of R. F. transformer No. 1. Connect 41, the G terminal of the left hand socket, to 42, the adjacent stator terminal of 17 plate condenser No. 1. Connect 43,



## RADIO PRODUCTS of DISTINCTION

### The DAVEN Resistance Coupled Amplifier Kits



THE DAVEN SUPER-AMPLIFIER UNIT

For those who prefer to buy a complete Resistance Coupled Amplifier Unit rather than build. This unit comes ready to install—it is the most compact amplifier now offered to the public.

It is laboratory tested and represents the ultimate in amplifier design. The base is of molded bakelite and is small enough to fit within any cabinet. All connections are hidden beneath the base.

Sold everywhere.

Ask your Dealer for a copy of our 25c handbook—“RESISTOR MANUAL”—telling about the many possibilities of Resistance Coupled Amplification and how to use it with any of the standard forms of receivers.

These highly perfected Resistance Coupled Amplifiers have convinced the most skeptical that Resistance Coupling is matchless. Add the DAVEN Resistance Coupled Amplifier to your favorite tuner and you will have a worthy combination hard to beat and amplification that is perfect.

The assembly is very simple, while the satisfaction of having built such a perfect device yourself is beyond mere words to describe. Its volume is adequate for all purposes—its perfect tone quality and absolute lack of distortion place it beyond comparison.

These Kits can be purchased at all good Radio Stores—they come with complete instructions for assembly so that the novice will have the same success as would be expected of Radio Engineers. Sockets and mica fixed condensers are not included, but instructions are furnished giving complete information and diagrams. Supplied for either three or four stages.

TRADE MARK  
**DAVEN RADIO**  
*"The Sine of Note"*  
**CORPORATION**  
*Resistor Specialists*

Newark

New Jersey

**"The Aristocrat of Amplifiers"**

a point on wire 10 to 12, to 44 and 45. 44 is the rotor terminal of the condenser and 45 is the front left hand terminal of R. F. transformer No. 1. Connect 46, the other stator terminal of the condenser, to 47. Connect 48, the P terminal of the right hand socket, to 49.

13. Fasten one terminal of the .00025 mfd. fixed condenser directly to the G terminal of this socket, placing a soldering lug under the same nut for a latter connection.

14. Connect 50, the other terminal of the fixed condenser, to 51, the Ant binding post. Connect 52, the A Bat + binding post, to 53, the right hand terminal of the filament switch. Keep this wire at the edge of the baseboard. Connect a piece of wire 5 ins. long at 54, the grid binding post, letting it stick up vertically.

15. Now mount the antenna coupling coil in the position shown.

16. Connect the other end of the wire from 54 to 55, the rear terminal of this coil. Connect the wire sticking up from connection 4, the rotor terminal of the 43-plate condenser, to 56, the right hand terminal at the front of the coil. Finally connect 57, the lug on the G terminal of the right hand socket, to 58, the stator terminal of the 43 plate condenser, to 59, the remaining terminal of the antenna coupling coil. Now put the three large dials on the condenser shafts making sure that the 100 mark coincides with the vertical line engraved on the panel, when the condenser plates are totally interleaved. Put the two rheostat dials on so that the zero mark coincides with the line engraved on the panel when the shaft is turned all the way to the left. This completes the assembly and wiring of the set.

**Testing** After the set has been wired, and go over each connection, checking it against the picture wiring diagram. See that the filament switch knob is pushed in. Connect a 6-Volt A battery across the A Bat + and A Bat - binding posts. The A+ terminal on a storage battery is usually painted red. Insert the five tubes in the sockets, pull out the knob of the filament switch, and turn the left hand rheostat


dial, looking at the set from the front, up to about 8. This should light the first and second tubes. Turn up the other rheostat knob. This should light the remaining three tubes. Leaving everything else in the same position, disconnect the A Bat + lead and connect it successively to the B Amp +, B Det +, and Bat + binding posts. The tubes should not light up for either of these connections if the set is wired correctly.

To put the set into operation, connect the + terminal of the battery to the A Bat + binding post. Connect the aerial and ground to their respective binding posts. Connect five 22½-volt, or two 45-volt and one 22½-volt Eveready B batteries in series. Connect the - terminal of the first B Bat - binding post. Connect the 22½-volt tap of the same battery from which the B- lead was taken off, to the B Det + binding post. Connect the + 67½-volt tap to the B Bat + binding post. Connect the + terminal of the last battery in the series, 112½-volt tap, to the B Amp + binding post. Connect the C Bat + and C Bat - binding posts together with a short piece of wire. Now connect the two cord tips from the loud speaker to the two speaker binding posts, the cord with the colored thread woven in it going to the Speaker + post.

Pull out the knob of the filament switch to turn on the tubes. Turn up the rheostat dials to about 8 and insert the phone plug in the jack. This should give a loud click in the phones. Set the three large dials at zero. Move the second and third dials in step one degree at a time, and for each of these settings rotate the first dial back and forth very slowly. Continue this process until a station is heard. Now readjust all three dials to get the best possible reception. Write down the name of the station and the dial settings. This station will always come in on the same setting provided the aerial and ground are not changed. By

Now try varying the B battery voltage on the detector, A. F. and R. F. amplifier tubes by using different voltage taps on the B battery. In each case use the lowest voltage consistent with good reception, as this increases the life of the B battery.

BETTER APPEARANCE and BETTER RESULTS

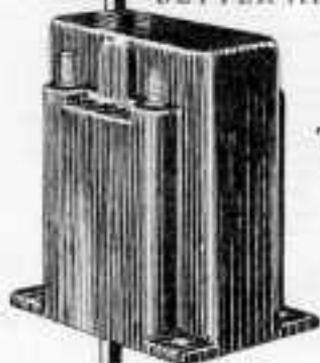


BAKELITE  
**Noiseless  
Transformer**

AMPLIFICATION  
WITHOUT  
DISTORTION

PERFECT SIDE WIPE  
BAKELITE  
**Socket**

MAXIMUM  
EFFICIENCY

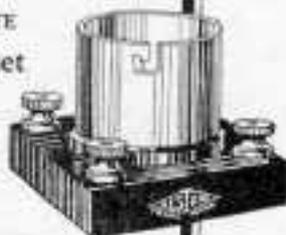

NEW  
**Bestone**  
PARTS

*On sale at all good dealers*

HENRY HYMAN & CO., Inc., Makers, 476 Broadway, NEW YORK



BAKELITE  
**One-hole Rheostat**  
IMPROVED TYPE



**Phosphor Bronze Jack**  
STURDILY CONSTRUCTED  
POSITIVE GRIP

The materials used to make up the set described in this issue were supplied by the following companies. The manufacturers whose names appear below will be glad to send you bulletins describing other products which they make. Please mention RADIO ENGINEERING when you write them.

#### COMPLETE PARTS FOR THE TYPE 7000 BROWNING-DRAKE 199

Type No.	Name	Price
199	4-UV-199 Sockets..... Benjamin Elec. Co., Chicago, Ill.	\$4.00
1-4	2-Modern transformers 1-4 ratio..... B. L. Sales Co., A-218 Fulton St., New York, N. Y.	10.00
101	1-Open circuit jack..... Carter Radio Co., G-209 So. State St., Chicago, Ill.	.70
D	1-2-megohm gridleak..... Daven Radio Corp., 9-15 Campbell St., Newark, N. J.	.50
	1-Mahogany Celoron panel 7 by 24 by 3/16 in..... Diamond State Fibre Co., A-423 Broome St., New York, N. Y.	3.94
	1-Mahogany Celoron panel 3 1/2 by 23 by 3/16 in.....	1.90
601	1-0.0005 mfd. Micadon..... Dubilier Condenser & Radio Corp., A-48 W. 4th St., New York, N. Y.	.55
Ensign 7	Ensign binding posts..... H. H. Eby Mfg. Co., X-40 S 7th St., Philadelphia, Pa.	1.40
	423-Q Broome St., New York, N. Y.	

40	2-30-ohm rheostats with dials... James Goldmark Co., E-83 Warren St., New York, N. Y.	3.00
W	1-100-ft. spool of Wirit..... Mitchell-Rand Mfg. Co., 18-F Vesey St., New York, N. Y.	.90
7	1-Length special No. 7 varnished tubing..... National Co. Inc., Brookline St., Cambridge, Mass.	.15
B-D	1-Complete Regenerator kit, including two condensers, 2 coil units, hardware, and Vel- vet vernier dials..... New York Coil Co., 138 Pearl St., New York, N. Y.	22.00
	1-0.00025 mfd. mica condenser with gridleak clips.....	.45
	1-1-Ampereite and mounting for UV199..... Radial Company, RE-320 W. 42nd St., New York, N. Y.	1.10
F	1-Filament lock switch..... Walbert Mfg. Co., A-931 Wrightwood Ave., Chicago, Ill.	.50
<b>MISCELLANEOUS PARTS</b>		
58	3-Pkgs. of 25 soldering tugs....	.60
185	1-Left hand nickeled angle bracket.....	.10
14	3-Nickeled coil mounting pillars....	.24
151	2-Terminal panel supports.....	.60
62	1-Pkgs. of 10 1/2-in. 6-32 F. H. nickeled screws.....	.12
63	3-Pkgs. of 10 1/2-in. 6-32 R. H. nickeled screws.....	.36
49	3-Pkgs. of 10 6-32 nickeled nuts Complete set of parts.....	\$53.15
<b>BROWNING-DRAKE 199 BLUE PRINTS</b>		
7000	Set of full-size panel patterns and diagrams, 5 sheets.....	\$1.25

## Back Issues of Radio Engineering

If you have missed any issues of RADIO and MODEL ENGINEERING for this year, check over the following list and order those that you did not get so as to make your file complete.

January—Tuska Superdyne, 4-tube Monotrol, oscillating wavemeter, . . . 10c.

February—7-tube super-heterodyne set, Cockaday Receiver.

March-April—Portable tuned R. F. set using UV-199 tubes, Harkness circuit for Diode or crystal detector.

May—Improved Raala reflex, the most successful 1-tube receiver ever built, 100-meter Sodian receiver.

June—Sodian reflex set using UV-201—A amplifier, the Bestone V-60, tuning filter for cutting out interference.

July—Resistance coupled amplifier, Tools for the radio model shop, Crystals that oscillate.

August—Construction of 4-tube No-Loss regenerative receiver, Description of the Boonton light four receiver, The R-A-R receiving circuit.

September—Out of print.

October—Improved design for Acme 4-tube reflex, Effective losses in inductances, Construction of Haynes audio amplifier, B. M. S. type super-heterodyne, Use of crystallizing lacquer.



November—Browning-Drake set for 201-A tubes, Die-castings in radio manufacturing, Assembly of the Melco R. F. receiver, Tools for the radio shop, Crosley Trirdyn 3R3, Inspecting telephone jacks.

December—Construction of the Ballantine receiver, Capacity measurements, Laying out instrument panels, Assembling the Silver-Marshall super-heterodyne, Standard receiver for testing, Super-heterodyne with Acme units.

January, 1925—Manufacture of variable condensers, Haynes transformer resistance amplifier unit, Condensers for laboratory tests, Coto symphonic receiver, Assembling the Splittorf R. F. receiver, Part I, Making A. F. transformer amplification curves, Assembly of the Receptrad multiflex.

The price of these issues is 20 cents each. They will be sent promptly upon receipt of a check, money order, or stamps to cover the cost. Postage is prepaid.

**8** improvements  
at ONE stroke

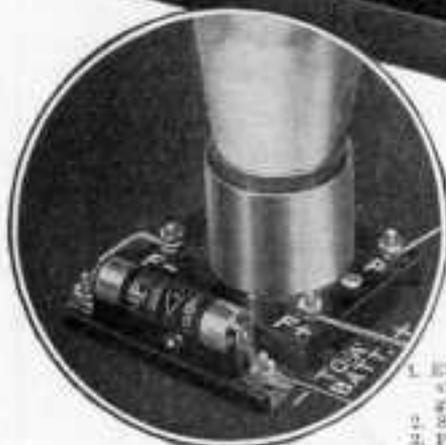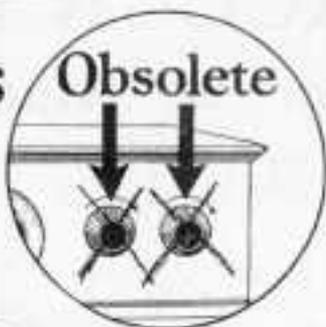

*The  
Self-Adjusting Rheostat*

*Price \$1.10 Everywhere*

Write for  
**FREE**  
Hook-Ups

1. Eliminates hand rheostats—simplifying control and giving compactness.
2. Simplifies wiring.
3. Prolongs life of tubes from 2 to 3 times.
4. No moving parts—therefore no grinding noises.
5. Permits use of any type of tubes or combination of tubes.
6. No filament meters necessary.
7. Brings the most out of each individual tube—automatically—in guessing.
8. Makes perfect tube operation absolutely fool proof.

AMPERITE takes the place of a good hand rheostat, a delicate meter and an expert operator. Operates on the thermo-electric principle. Automatically changes in resistance as the "A" battery voltage changes. Mounts conveniently inside the set. No knobs to turn. Nothing to get out of order. Approved by every prominent laboratory. Standard equipment in such sets as Somerset, Ultradyne, Marshall, Fluorsteel, Kilbourne & Clark, Heteroplex, Cockaday and numerous others. Fully guaranteed.

**RADIALL COMPANY**

Dept. R.E.-6

50 Franklin St., New York

**AMPERITE**  
REG. U.S. PAT. OFF.

*"means right amperes"*

# ACCURATE Screw Machine PRODUCTS

1-2 " / 1000  
*guaranteed!*

## MANUFACTURERS:

**R**EJECTED screw machine products mean increased production cost. Save time, trouble and money with *guaranteed accurate* screw machine products. Where required, our Brown and Sharpe equipped plant can turn out a part for a condenser, jack, switch, etc., with a *guaranteed accuracy* of 1/1000" to 2/1000".

*Estimates gladly quoted—*

Kindly submit sample, blue prints or other specifications. We have done precision work for radio manufacturers everywhere in the United States.

*Accurate Screw Machine Products*

## COLUMBIA

Metal Products Co.

*Accurate Screw Machine Products*

357-365 East Ohio Street

CHICAGO, U. S. A.

**All**

**Brown and Sharpe**

**EQUIPMENT**

## New and Improved

18  
Styles  
Engraved  
Ready for  
Immediate  
Delivery in  
Any  
Quantity.



The Utmost  
in Quality  
and Appearance at  
the  
Lowest  
Price  
15c.

FULLY PROTECTED BY  
PATENTS

**Read'em<sup>®</sup>**  
**Binding Posts**

*Made by the Originators of High  
Grade Engraved Terminals*

THE MARSHALL-GERKEN CO.  
Toledo, Ohio.

## MANUFACTURERS SPECIFY STASCO RHEOSTATS



*The Spring does it!*

### Permanent Contact Guaranteed

Gives better results with all types of tubes. Cannot work loose on panel. A scientifically correct laboratory instrument used by manufacturers and engineers—a real improvement.

*May we send you booklets and further information?*

**SHEFFIELD TRIMMING  
& STAMPING CORP.**

211 Centre St. NEW YORK CITY



The greatest factory of its kind in the world has worked day and night since September

## *This was the Greatest Formica Year!*

**F**OR years Formica has supplied more radio manufacturers with panels, strips, winding tubes, and washers than any other maker of radio insulation.

This year the list of companies supplied by Formica was extended by the addition of many other leaders in the industry.

These makers consistently test every new offering in the way of insulation—and always decide that Formica finish, Formica uniformity, Formica insulating quality, Formica service, and deliveries are the best that are available.

Formica panels provide an absolutely permanent front for a radio set—one that will not discolor, warp, craze, check or in any way change. They are a mark of genuine quality in any instrument.

Four beautiful finishes: Walnut, Mahogany, Gloss and Dull Black.

*Write for booklet*

### THE FORMICA INSULATION COMPANY

4653 Spring Grove Avenue, Cincinnati, Ohio

#### *Sales Offices*

40 Church St., New York, N. Y.  
9 South Canton St., Chicago, Ill.  
515 Canton Bldg., Cleveland, Ohio  
1142 Granite Bldg., Rochester  
N. Y.  
422 First Ave., Pittsburg, Pa.  
5 Beaman St., Boston, Mass.

35 Calle Obispo, Habana, Cuba  
289 Victoria St., Toronto,  
Ontario, Canada  
1026 Second Ave., Minneapolis,  
Minn.  
1210 Arch St., Philadelphia, Pa.  
708 Title Bldg., Baltimore, Md.

345 Mission St., San Francisco,  
Cal.  
419 Ohio Bldg., Toledo, Ohio  
309 Plymouth Bldg., New Haven,  
Conn.  
Whitney Central Bldg., New  
Orleans, La.


---

# FORMICA

Made from Anhydrous Bakelite Resins

## SHEETS TUBES RODS

---

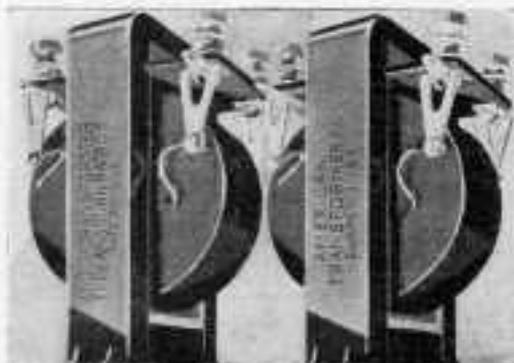

## Sell AmerTrans For Replacement!

All sets need the most from audio amplification to give the best of loud speaker performance. AmerTrans assure the buyer that the audio side of his receiver is right.

When you sell AmerTrans you are selling appreciation of the highest transformer quality. In new sets or as a replacement, AmerTrans deliver the most volume and clarity from audio amplification.

*Sell AmerTrans by the pair.*

AmerTrans is made in two types—one quality—Type AF 6 (ratio 5), Type AF 7 (ratio 3 1/2). List either Model \$7.00 — discount regular.

**American Transformer Co.**  
Newark, N. J.

"Transformer builders for over twenty-four years."

# AMERTRAN



## DeJUR JR COMMERCIAL RHEOSTATS

*(Genuine Bakelite)*

The DeJur Jr. is the only rheostat that does not have to be taken apart in order to mount. There is nothing to get loose in back of the panel. Positive connections throughout assure permanent contact. The DeJur Jr. is made especially for manufacturers requiring efficient parts at the right price. Write for Prices and Samples.

**DeJUR PRODUCTS CO.**

Lafayette and Greene Sts., New York

Patents

Applied for



## KURZ-KASCH ARISTOCRAT



**DIALS  
AND  
KNOBS**

### LEADERS IN THEIR LINE

Manufacturers use them for their beauty and efficiency. Moulded of Bakelite—the quality is guaranteed. No set screws to tighten—the Patented Split Bushing eliminates the need.

Set builders use them for easy handling and recognized superiority. Assembly is simple. The bushing is placed on the shaft, the dial goes over the bushing, and the knob is screwed on. All dials are finished in a smooth black, without set-screw holes to mar the surface. They must be good.

Genuine Kurz-Kasch products bear the trademark on the back of each part, except as substitutes.




The cost — 1" — \$1.00.  
1 1/2" — 1.50. 2" — 2.00

**THE KURZ-KASCH CO.**  
DAYTON, OHIO

**RASLA**

## *Improved!*

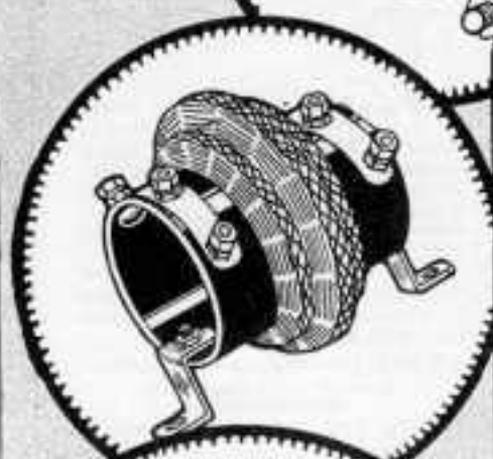

**T**HE Improved Rasla Reflex for Two Tubes will startle you. You won't believe that such great volume can be gotten from two tubes. You'll marvel at the selectivity and at the distant stations that come roaring in.




The Improved Rasla Reflex is the most powerful circuit so far devised! Never before has it been possible to do with two tubes what the Improved Rasla Reflex can do. You will convince yourself of that quickly.

The Improved Rasla Reflex is easy to build, very easy. The complete wiring diagrams eliminate all chance of going wrong. The four RASLA units pictured make results certain.

*Go to your dealer today and ask for the Improved Rasla Reflex Construction Bulletins for one and two tubes FREE. If he cannot supply you write us.*

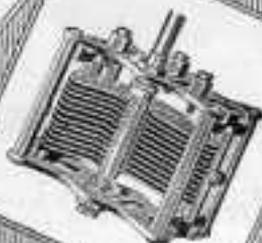**DAVIDSON RADIO CORP.**  
222 Fulton St. N.Y.C.





## Amsco Quality Parts

The standard of excellence by which all others are judged. Used by many of the leading set manufacturers as well as by foremost radio engineers. They are laboratory instruments.

*At dealers everywhere.  
Free literature on request.*

**AMSCO PRODUCTS, Inc.,**  
416 Broome Street New York

# WIRIT

JAMES GOLDMARK COMPANY

**1921** The first concern to manufacture the familiar square tinned copper bus bar was James Goldmark Company. This bus bar was drawn to the specifications furnished by M. B. Sleeper.

**1925** Again James Goldmark leads the wire manufacturers as the first to produce WIRIT, the newer, hotter conductor for wiring radio sets, also drawn to M. B. Sleeper's specifications.

*WIRIT is No. 18 tinned wire of electrolytic copper, specially tempered to be flexible and at the same time hold its shape.*

Both manufacturers and set builders will find that, with WIRIT, sets can be wired more neatly and in less time than with any other conductor.

WIRIT, per 100 ft. spool.....90c

*Special Prices in Quantity to  
Manufacturers*

**JAMES GOLDMARK COMPANY**  
83-A Warren St., New York City

CERTIFIED  
GRID  
LEAKS

Always fully  
accurate

calibrated, permanent fixed resistance units from 1k to 10 megohms. Price 50c.



USE THE AUDIOHM for clarity and volume control. Put one across the secondary of your transformer. Price \$1.50 with adjustable transformer.



L. A. M. P. SOCKET ANTENNA. Just plug it on any electric light line, no need of outdoor or indoor aerials. Simplest, easiest, most efficient on market. Price 50c.



INDOORIAL—Hang or lay anywhere. Roll up when not in use. Wonderful directional effects, sets out local stations. Use as ground. Price \$1.50.



**GET** Clear, Distortionless Reception. Distortion, weak signals, lost signals are almost always caused by inferior small parts. Protect yourself from disappointment, insure getting

**Distance, Clarity and Volume**

By using Electrad radio parts. Money back guarantee. They will improve your set. Electrad Parts are on sale at most all reliable radio stores. Sold direct if dealer cannot supply you. Money back guarantee.



VARIABLE, a variable grid leak will give you exactly the correct grid resistance. Any resistance \$1.50, from 1k to 10 megohms. Price set in permanent. Price \$1.50.

# ELECTRAD


428 Broadway, New York

# The Fun of Radio is Building Your Own Equipment

You know how the B. C. L.'s love to show off their factory-made sets, and the perfect line of excuses they've developed to explain their failures on the special nights when they promised to get everything. They think it's wonderful the way they can tune their sets.

But anyone can tune a set. It's nothing to be so proud about. The only man who has a right to swell out his chest is the one who built his outfit himself. That's something to talk about, and there is the real fun of radio. If you like to operate a set, you might as well have all the enjoyment there is in radio—build a set yourself. You will find that you can handle a receiver far more skillfully if you know about it from the inside out—and when the B. C. L.'s start gossiping about their store-sets you'll have something real to tell them about the outfit you made yourself.

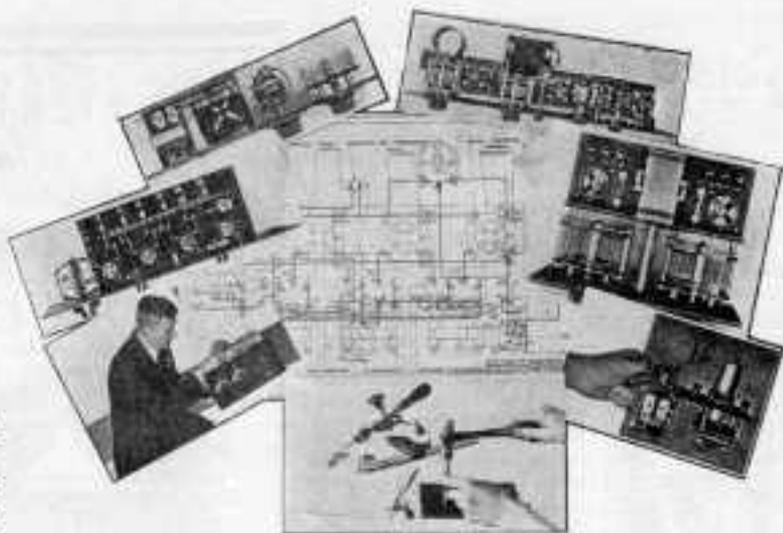As for your ability to make your own outfit, don't worry about that. The M. B. Sleeper books are your success insurance, for they take you thru each individual step of assembly with picture wiring diagrams, drawings, photographs, and detailed instructions.



## Some Illustrations from the **RADIO SET-BUILDERS' BOOK**

By M. B. SLEEPER

**What to Build** The sets described in this book were chosen from the various types which have been shown in Radio Engineering Magazine, and are the ones on which we have had the most favorable comments. They are the R-D-X, a one-tube reflex, the NoLoss two-tube regenerative, the new design Acme Reflex with four tubes, and the super-sensitive Browning-Drake four-tube set.

**How to Build It:** Each set is described in detail, with clear photographs, picture wiring diagrams, scale drawings, and step-by-step assembly instructions. It is also possible to get full-size panel patterns for these outfits if you want them. A special chapter gives in pictures all information about the panels and their preparation.

**Parts Required:** All the sets described are made of standard parts which you can obtain from your local radio store. You don't need special apparatus to make up the sets, or a machine shop to assemble them—just the simple tools which you probably have in your home right now.—Certainly, you can build your own set.

SEND 25c IN STAMPS for THIS NEW BOOK

# M. B. SLEEPER, Incorporated

Technical Publisher

A-52 Vanderbilt Avenue

New York City

# Gets DX— SLOW MOTION Tuning



REMEMBER how the "slow-motion" picture helped you see details that were unnoticed in the usual running?

In a similar way the "slow-motion" (12-to-1 ratio) of the new UNIVERNIER helps you find dozens of stations that are missed if "something" is done with the usual coarse adjustment (as you are compelled to do with many so-called vernier dials which merely duplicate the action of the obsolete vernier condenser.)

With its continuous "slow motion," the UNIVERNIER first finds the station you want — then dials it up. That's why it's such a record-breaker for locating those hard-to-get distant stations and bringing them in so easily, quickly, clean and loud. Promise yourself a real surprise—replace your dial with UNIVERNIER's tonight! At your dealer's or sent postpaid on receipt of purchase price. (Please mention dealer's name.)

Mahogany Knob and  
Cold-plated dial . . . \$1.50

Black Knob and Silver  
plated dial . . . . . \$1.25

Jobs and Dealers: Write for Discounts

WALBERT MFG. CO.


931 Wrigwood Ave., Chicago, Ill.

FREE!  
Send 25 stamps for  
FREE copy of  
UNIVERNIER  
LOG BOOK.



**WALBERT**  
**UNIVERNIER**  
Micro-Selective Tuning Control
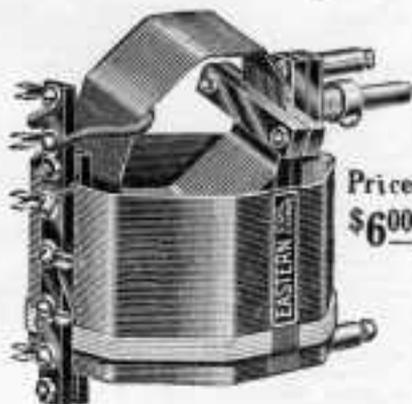
## FANS EVERYWHERE Are Replacing Their Coils With EASTERN Low-Loss Couplers



Price  
\$6.00

### THE IDEAL TUNER!

This coil, for the standard 3 circuit tuner, has replaced numerous other coils, and in every case has improved the results of the set in distance range, selectivity and increased volume reception.

One fan writes—"Several of my friends have purchased your coil after seeing mine (EASTERN LOW-LOSS COUPLER) and have replaced the tuners which they had in their sets. They are very enthusiastic over the improved quality and selectivity.

Very truly yours,  
(Signed) "B. J. AUGHE, Detroit, Mich."

Do not take a chance using ordinary coils when an EASTERN LOW-LOSS COUPLER, acclaimed by radio editors as "the best LOW-LOSS COIL yet designed," can be had at no greater cost.

Broadcast Type, 200 to 600 Meters, \$6.  
Short Wave Type, 40-200 Meters, \$6.

Eastern Low-Loss Couplers are extremely efficient in the following circuits:

Superdyne .....	\$8.00
Harkness .....	\$4.00
Tuned R. F. .... (Set of 3)	\$6.00
Roberts Knockout .....	\$8.50

At your dealers or sent postpaid.

**EASTERN COIL CORP.**  
22 Warren Street, New York

# New National Regenaformer Wins Enthusiastic Approval of Boston's Radio Editors Unanimous Agreement



## Only Sheer Merit

Could have evoked such unanimous applause from radio experts.

THE NATIONAL REGENAFORMER is a tuned radio frequency transformer kit of highest efficiency. It makes a wonderful set. Results are truly amazing.


Order one for the set you now have—or plan to build.

Price \$22.00

Send for Bulletin 105 N. E.

**NATIONAL COMPANY, Inc.**  
110 Brookline St.  
Cambridge  
Mass.

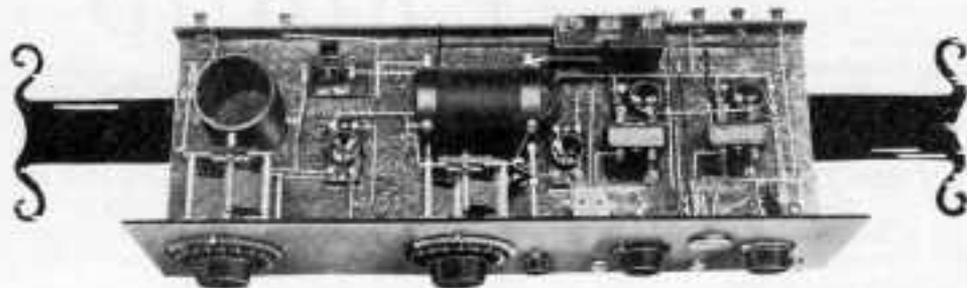*Sole Licensees under  
Deering-Orville  
patents*





# ZIP!



**"Every Tube Blown  
Out Again"**

**—Ever Happen to You?**

**Y**OU can't foresee when it will occur—loose connection, bit of solder, slipping screwdriver—and there's all five tubes gone in a flash! Not only money loss but the evening spoiled.

**These Costly Accidents  
Can be Prevented**

A KANT-BLO on your set gives absolute, permanent protection for any number of tubes. Just install it and forget it.

**Not Additional Apparatus**

KANT-BLO simply takes the place of a binding post or battery switch. Only one needed for any set and then you are protected indefinitely. Not only prevents blow outs but warns you that there is something wrong. If your dealer is out of stock, send us \$2 for a KANT-BLO Binding Post Style, or \$3 for the Switch Style and we will ship direct to you charges prepaid.

## Kant-Blo



**Lights on any Short Circuit**

Manufactured by  
GANDY-KRAMER Co., Inc., NEW YORK

Sole Distributors  
APEX RADIO Co., Inc., 503 Fifth Ave.,  
NEW YORK

## The Standard of the World



The base-type  
**Freshman Variable Grid Leak**

is the standard for those who build their own sets. It is the most compact and being entirely sealed it always remains unaffected by any climatic conditions.

Complete with either .00025 or .0015 Freshman Condenser—without condenser..... **\$1.00**

At your dealer's, otherwise send purchase price and you will be supplied postpaid  
Chas. Freshman Company, Inc.  
240-W. 40th St., New York

# MORE MONEY?

*A Dollar and a Half an Hour  
for You*

**C**AN you do radio installation and maintenance work? If so, have yourself officially registered in the I and M Registry in Radio Engineering, so that set owners in your town will know that you are doing this work.

It costs only two dollars to have your name, address, and telephone number listed in the Registry for a whole year—less than what you are paid for a single job. Send in this data at once, so you will be all set for the big winter business.

Send your registration to  
I and M Registry

**M. B. SLEEPER, Inc.**  
A-52 Vanderbilt Ave., New York City

## ALL-AMERICAN Guaranteed Radio Products

Standard Audio Transformers  
3 to 1 Ratio, type R-12... \$4.50  
5 to 1 Ratio, type R-21... 4.75  
10 to 1 Ratio, type R-13... 4.75

Power Amplifying Transformers  
(Push-Pull)  
Input type R-20... \$6.00  
Output type R-31... 6.00

Random-Lytic  
A laboratory grade audio  
transformer for music  
lovers. R-500... \$9.00

Universal Coupler  
Antenna coupler or tuned r. f.  
transformer. R-350... \$4.00

Self-Tuned  
R. F. Transformer  
Wound to suit the  
tube. R-199 \$5.00. R-201A \$5.00

Long Wave Transformer  
(Intermediate Frequency)  
(15-75 kc.) R-110... \$6.00

10,000 Meter (30 kc.)  
Transformer  
Tuned type (filter or  
input). R-120... \$5.00

Radio Frequency Coupler  
(Oscillator Coupler). R-130 \$5.00

Super-Fine Parts  
Consisting of  
three R-110's,  
one R-120 and  
one R-130 \$26.00

All-American  
Reflex  
Receivers  
Complete receiving sets with  
extraordinary  
range, volume  
and selectivity.  
All parts  
mounted on  
panel and baseboard, with full  
instructions for wiring. All-Amax  
Junior (one-tube)... \$22.00  
All-Amax Senior (three-tube)  
\$42.00

## KESTER Radio SOLDER



Oh boy it sure is  
Safe & Simple

Here's the solder that contains the flux recommended by radio engineers! The pure rosin core inside of Kester Radio Solder is a natural flux and does not leave its harmful chemical or electrical action on delicate parts or joints. It requires only heat.

In developing radio frequency, it was found that all fluxes, except rosin, spatter, fume and run over delicate parts and joints. This causes leakage and makes the test irrefragable as poor as a grid leak.

In developing radio frequency, it was found that all fluxes, except rosin, spatter, fume and run over delicate parts and joints. This causes leakage and makes the test irrefragable as poor as a grid leak.

holder with Kester Radio Solder. You will have no need to go over and wipe away surplus flux. Leave what rosin still remains — it is a good insulator!

There you have it: Kester Radio Solder is a safe and simple solder with which your set can be quickly, neatly, safely and satisfactorily soldered. Get a handy can of Kester from your dealer.

CHICAGO SOLDER COMPANY  
4224 Wrightwood Ave.  
Chicago—U. S. A.

# 100 to 1 AMERICAN BRAND CONDENSER

with the Worm Drive  
VERNIER

23 PLATE \$5.00  
only

For Sale  
Everywhere

AMERICAN BRAND CORPORATION  
8 WEST PARK ST. NEWARK, N. J.



## ALL-AMERICAN

AMPLIFYING TRANSFORMERS

Largest Selling Transformers in the World

## Special Construction Kits

### Browning-Drake 199

The outstanding success of this season is the Browning-Drake receiver. With the sharpness of tuned R.F. and the sensitiveness of regeneration, it surpasses in results most seven and eight-tube sets. The Browning-Drake 199 operates about two months on a set of dry cells, because it uses four UV-199 or C-299 tubes. B batteries last indefinitely, making this outfit extremely economical. The receiving range on a loud speaker is almost unlimited. The B-D199 construction kit contains every item required to build the set, including panels drilled and engraved. Type 7000 B-D199 kit, complete .....\$54.90

### Browning-Drake 201-A

The Browning-Drake 201-A set is the outfit for the man who wants to hear everything that's in the air. It is designed for one UV199 and three UV201-A tubes, working from a 6-volt storage battery. For sensitiveness, freedom from oscillations, ease of tuning, and attractiveness of appearance, the Browning-Drake is unsurpassed. Since the panels are drilled and engraved, the outfit can be assembled with the simplest tools. Build the Browning-Drake and you'll discover new things about radio sets. Type 6600 B-D 201-A kit, complete.....\$59.50

## Parts for Set Builders

In spite of the extreme shortage, DURRANT is one of the few companies that can ship the genuine licensed Browning-Drake regenerative units made by the National Company. This is an example of the unusual mail order service that DURRANT can give you.

Postage is paid by DURRANT, but no responsibility for safe delivery is assumed unless ten cents extra is remitted to cover the cost of registry.

## DURRANT RADIO, Ltd.

T-52 Vanderbilt Avenue

New York City

## Browning-Drake 199

(continued from page 79)



Made of rigid metal, heavily nicked. Fits standard phonographs. Retail list \$7.50. In correct of twelve, each unit in gold embossed leatherette box.

## THAT SAME N & K CLEARNESS

**M**ANY radio set owners do not want to pay the price of a good speaker. And they don't consider cheap speakers worth having.

Many of these owners are among your customers. You can please them, and at the same time make excellent profit for yourself, by selling them N & K Imported Phonograph Units. Attached to Victrola or other good phonograph this unit reproduces with a clear, mellow tone such as few speakers—except the N & K Imported Loudspeaker—have. It gives the equivalent of a speaker of very highest quality.

If not already carrying the N & K Imported Phonograph Unit, write for address of nearest N & K distributor.

THE GOLDSCHMIDT CORPORATION,  
Dept. R2, 15 William St., New York



## Imported PHONOGRAPH UNIT



### N & K IMPORTED LOUDSPEAKER

New in appearance, in principle and in the wonderfully mellow clearness of its tone. 14 1/2 in. High. Retail list \$27.50. Each speaker in handsome display carton.



### N & K IMPORTED PHONES

Famous for clear, mellow tone. Unusually comfortable. Generous length of cord. Big popular seller. Retail list \$8.50. In display cartons of ten.

on the jack and 63 the second lug on the +90V binding post. Connect 64 to 65. 64 is the spring contact on the jack and 65 the P contact on the socket. Connect 66 to 67. 66 is a connection on wire 60 to 61, and 67 the second lug on the forward Amperite spring. Connect F post of the left hand transformer to the wire from 62 to 63 by a short lead put thru a hole in the tube panel.

This completes the wiring of the Browning-Drake 199 receiver.

**Testing and Installation** When the set is ready to install, put on the A battery first.

The picture wiring diagram shows how the connections should be made. Either 4 volts or 6 volts can be used for the A battery, as the rheostats are of sufficiently high resistance to take care of it and the Amperite controls the R. F. amplifier current automatically. Insert the tubes and see that they light properly. Then put on the 4 1/2 volt C battery. If everything seems to be O. K., put 90 volts of B battery across the -B and + 90V binding posts and bring off a tap at 45 volts to the +45 V binding post. Light the filaments and plug in the telephones or loud speaker. This should give a strong click. If the click is not clear, the plate circuit is open. You may find that the brilliancy of the filaments will change slightly when the B battery is connected but this does not affect the operation of the set.

At the Darien laboratory we find it very convenient to use the new Bolden battery cable for the A and B batteries with the C battery mounted in the cabinet.


The antenna should be a single wire 50 to 100 ft. long from the set to the far end. An indoor antenna is quite satisfactory, made with annunciator wire or Talking Tape run around the wall. The ground connection must be made to a water pipe which has water in it at all times.

Set the tickler coil at right angles to the main winding and revolve the left hand condenser slowly while the other is turned back and forth. As soon as a station comes in, get accurate settings with the dials and increase the volume by turning the tickler coil.
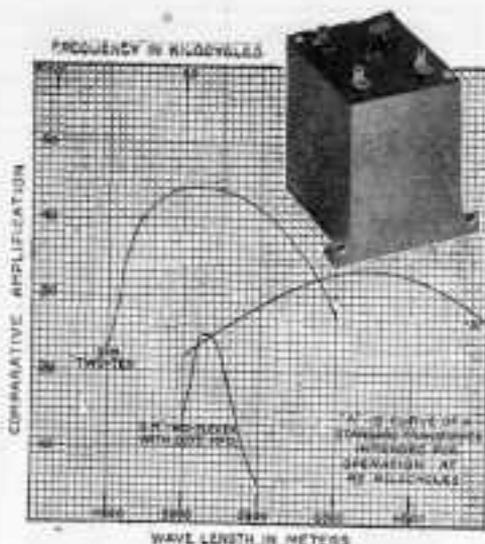
# A CURVE

*That Means Something*

An amplification curve has no definite significance unless it applies to a particular transformer. That's why the curve of each TWO-TEN (long wave) and each TWO-ELEVEN (filter) is plotted in the S-M laboratory. That's why the curve goes on the tag attached to each instrument—to show the peak—the side-bands passed—amplification expected—to eliminate guesswork—to supply you with definite data. Insist upon the individual curve-sheet. It applies to only one transformer—the one you buy.



S-M Long Wave Transformers have been proven by many laboratory tests to be the most efficient ever produced for super-heterodyne circuits. Housed in sturdy aluminum cases. Peaked at 6,000 meters.

S-M TWO-TEN and TWO-ELEVEN Long Wave Transformers and Filter are supplied in matched sets of one TWO-ELEVEN, and two, or three, TWO-TENS, with individual amplification curves for each. Price, (each) .....\$6.00

Circulars on all S-M products will be sent upon receipt of stamp.


## Silver-Marshall, inc.

110 So. Wabash Ave.

CHICAGO

## MULTIPLE CONDENSERS

LICENSED UNDER HOGAN PATENT 1014062

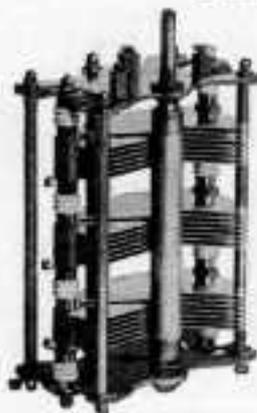

INSULATED WITH PYREX

OR CORANTUM

OF EXTREME PRECISION FOR  
SINGLE CONTROL CIRCUITS

ALL CAPACITIES

### General Instrument Corp.

*Manufacturers of Laboratory Equipment*

423 Broome Street

New York City



# WILL THIS HAPPEN TO YOU?

**G**USTAV A. SOHRE, 35 Manhattan Avenue, Jersey City, N. J., wrote us: "Enclosed are two dollars for which please send me a Kant-blo tube protector and extend my subscription to Radio Engineering for one year.

"If I had sent this in a week sooner, I would have saved myself \$16.00, for last Sunday I blew out four tubes which was a nice blow to me and my pocketbook.

"So after the horse is stolen I lock the stable as the saying goes. Send this tube protector at your earliest convenience so I can put it in my set before more tubes give up their ghosts."

The Kant-blo tube protector and signal absolutely protects the tubes from burning out when the B battery is accidentally connected to the filaments. It does not affect the operation of the set, as its normal resistance is only a few ohms, jumping instantly to 900 ohms when the B battery is put on the filaments. No changes in the wiring are needed. Protects one to ten tubes of any type.

A Kant-blo is given free with every year's subscription or extension to RADIO ENGINEERING. Send \$2.00 with your name and address.

**IMPORTANT:** In order to get a free Kant-blo, your letter must be addressed to the Tube Insurance Department.

## M. B. SLEEPER, Inc.

*Technical Publisher*

A-52 Vanderbilt Avenue

New York City

# CICO

 <p>CICO BATTERY SWITCH</p>	 <p>NESTOR BEND-RITE \$1</p>	 <p>CICO AUTO- MATIC PLUG 75c</p>
 <p>CICO BAKELITE JACKS</p>	<p>CICO BAKELITE RHEOSTATS Plain, \$1.00 Vernier, \$1.25 2 Ohm, \$1.25</p>	 <p>CICO BAKELITE POTENTIO- METERS \$1.15</p>
 <p>CICO BAKELITE JACKS</p>	<p>Definite angles, per- fect eyes, and straight wire from coil to point does make a difference in radio reception. The NESTOR BEND-RITE gives satisfactory results.</p>	 <p>CICO 2-WAY PLUG 40c.</p>

**JACK PRICES**  
Single coin No. 10-13  
Single coin No. 21-25  
Double coin No. 25-30

**SWITCH PRICES**  
"A" Battery No. 25-30  
Combination "A" & "B"  
Battery No. 34-31.00

Write now for descriptive literature.

CONSOLIDATED INSTRUMENT COMPANY OF AMERICA, INC.  
41 East 42nd Street, New York

## The Latest Achievement in Audio Amplification



Type 285

Price \$7.00

Discriminating radio listeners—this instrument has been designed for you. It is an achievement of which the designing engineers are justly proud; it is an instrument which merits the admiration of trained radio ears.

High and low notes are amplified evenly over the whole audio range so that instrumental or vocal tunes are reproduced individually or in combination with a naturalness which delights the most critical radio listener.


Seldom is more than one transformer necessary to operate a loud speaker with good volume.

If you want the best there is in transformer design, the type 285 should be your choice.

Ask for them by Name  
At all Reliable Radio Dealers.


# GENERAL RADIO Co

CAMBRIDGE, MASS.

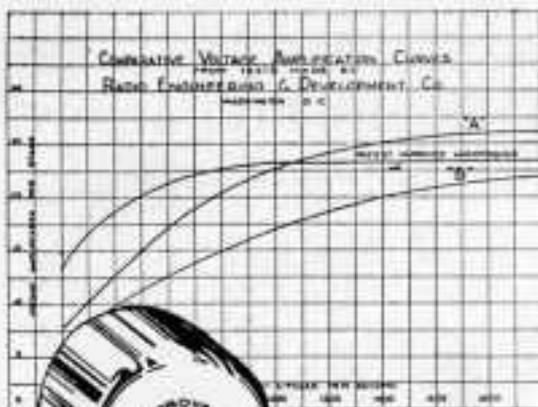

Comparative voltage amplification curves from tests made by the Radio Engineers and Development Company of Washington D.C.

## The Chart tells the story

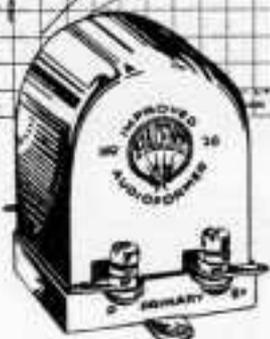

High amplification over entire band of sound frequencies. Undistorted reproduction at all frequencies, with no one high peak of amplification at any point of the band. Brass grounded case, with satin nickel finish. Ratio 1½ to 1. Location of binding posts permit short leads.

The better class dealers carry Pacent Radio Essentials. Send for complete catalog.

PACENT ELECTRIC COMPANY, Inc.  
91 Seventh Avenue, New York City

Washington Minneapolis Boston San Francisco  
Chicago Birmingham Philadelphia St. Louis  
Buffalo Jacksonville Detroit


**Pacent**  
RADIO ESSENTIALS

⚡ DON'T IMPROVISE - PACENTIZE ⚡
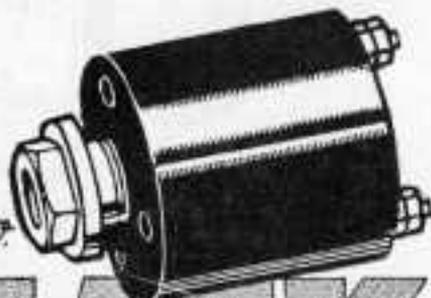
## three jacks in one

WHATEVER the circuit, TRI-JACK does the trick! Single open, single closed, double closed—TRI-JACK is the best bet for any of these jack duties. TRI-JACK is three jacks in one. Other TRI-JACK features are super-compactness, practically zero capacity, bakelite body, and solderless connections. Fits any standard plug.

90c at all good dealers, who also sell and recommend B. M. S. Fan-tail Jacks (6 types), TRI-COIL (\$2) and TRI-PLUG (75c)



BROOKLYN METAL STAMPING Corp.  
718 Atlantic Avenue Brooklyn, N.Y.

# TRI-JACK

# At Last! Toroidal Radio Frequency Transformer

THE "Donut" or toroid coil is already in itself and represents a new step in radio frequency application. To the discriminating Radio Fan who demands the utmost of his receiver from the standpoint of distance, selectivity, sensitivity, and volume, the SUMMIT TOROIDAL TRANSFORMERS will prove a revelation. They are designed in accordance with modern transformer engineering principles, adding greatly to the distance of any receiver.

THE SUMMIT TOROIDAL TRANSFORMERS are used in exactly the same manner as the open radio frequency coils—they have the correct ratio and are self balanced and self neutralized. There are no near fields, leakage, or any other bad luck, thus assuring the experimenter and radio set builder of correct operation without heating or buzzing. Their low distributed capacity and low loss give the greatest distance and power possible.



Diagrams and complete instructions for the assembly of the Five-Tube Summit Receiver attached with each set of transformers. The beginner in radio set building (if he follows these instructions) will experience no difficulty in producing a finished set that will do all and more than any other set of like size.

List Price (Set of Three Mated Units) \$10.00

*Territory Open to Distributors and Jobbers*

**SUMMIT RADIO MANUFACTURING CO., Inc.**

481 Broad Street

Dept. 20

Newark, New Jersey

## PUDLIN SCIENTIFIC RESISTANCE



### WILL STAND THESE TESTS

Put a Pudlin Resistance in a glass of water for any length of time, or subject to a heat test of 300° Fahrenheit. Then compare with any grid leak on the market.

Our Resistance elements are super-impregnated—our own laboratory development. Endorsed officially by leading Universities and Experts throughout the world.


Beautiful Metal and Glass Cabinet furnished to Dealers and Jobbers FREE with every purchase of 100 Grid Leaks.

*Send for Our Resistance Booklet*

**PUDLIN ENGINEERING CO., Inc.**

91 Seventh Ave.

New York City

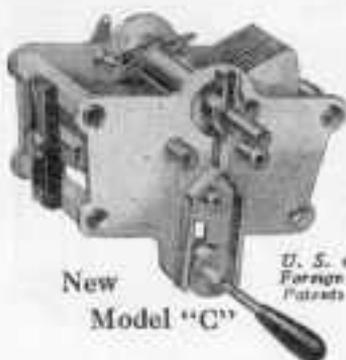

New

Model "C"

U. S. and  
Foreign  
Patents

## "What a Difference The Hammarlund Makes!"

Stations you never heard before—wonderful volume—pleasing clarity—freedom from interference—are the advantages the new model "C" Hammarlund Condenser brings to you. No watch was ever built with more precision—no design more carefully thought out. All capacities; plain and vernier. Sold by the better radio dealers.

Write for Descriptive Folder.

HAMMARLUND MANUFACTURING CO.  
424-438 West 33rd Street New York

For Better Radio  
**Hammarlund**  
PRECISION  
CONDENSER

### 9 Points of Superiority

- |   |  |  |  |  |   |  |                        |   |
|---|--|--|--|--|---|--|------------------------|---|
| 1—Sintered brass plates, spherically coated against corrosion; perfect alignment. | 2—Dialer plates specially shaped by sand casting or low wax. | 3—Adjustable bell-downing rotor + dial, grounded through metal end-plates. | 4—External shock spring six-tail, with automatic stop. | 5—Minimum dielectric losses—no wax to be melted. | 6—Rugged, compact, construction; cannot warp. | 7—Microscopic surface spaces on plates; no backlash. | 8—Takes any size dial. | 9—The product of 14 years experience, making precision instruments. |
|---|--|--|--|--|---|--|------------------------|---|

# ROYALTY



**VARIABLE  
GRID LEAKS**  
*Patents Pending*

\$150

**VARIABLE  
HIGH RESISTANCES**  
*Patents Pending*

\$150

**R** OYALTY Variable Grid Leaks will clear up those distant stations for you. You will never realize what your set can really do in the way of distance and clarity until you use the ROYALTY!

ROYALTY Variable Grid Leaks are non-microphonic. The resistance is variable by minute progressive steps; the same dial setting always gives the

same resistance. The lever cannot scrape away the resistance because the contact is metal on metal.

ROYALTY Variable High Resistances are identical in appearance and construction with ROYALTY Variable Grid Leaks. They embody the same exclusive features. (Type B, 1,500 to 100,000 ohms; Type C, 500 to 50,000 ohms.) Ask your dealer!

*(We also make the Gem Guaranteed Fixed Grid Leaks, the Royalty Fixed Grid Leaks, and the Gem Broad and Narrow Lead-ins.)*

WIRELESS PRODUCTS CORPORATION  
136 Prince Street, New York City

## METRO RADIO PRODUCTS




### METRO KEELOK SWITCH

You lock your automobile when you leave it. Why don't you get ownership of the same kind?

The KEELOK SWITCH system puts out four bolts (sufficiently threaded) who are not familiar with radio and who can cause irreparable damage to your tubes and instrument. The KEELOK combines the advantages of the popular push-button switch with absolute safety. Two keys are provided "on-off" sign with such satisfaction.

.....List, 75c

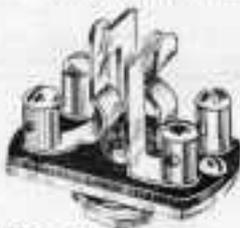

### METRO NON-SOLDER JACK (Double)

Eliminate that messy soldering job! Use the METRO DOUBLE JACK—solder-free to insert—no solder.

.....List, 50c




### METRO NON-SOLDER JACK (Single)

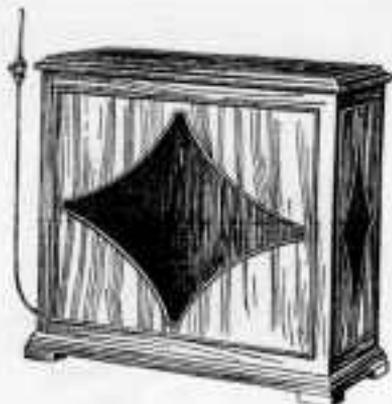1. Eliminate soldering.
  2. Compact—occupies very little panel space and is very neat.
  3. Dismounts from springs.
  4. Steeling silver contacts.
  5. Genuine Bakelite insulation.
  6. Other parts brass, with laser nickel plating.
  7. Attractive appearance.
- .....List, 50c

Metro Products are carried by the better dealers. If not in stock write us direct.

METRO ELECTRIC MFG. CO.  
121 Prince St. New York City



## At last--

### A practical solution to the "B" Battery Problem

Now you can get "B" Battery current direct from your electric light socket—without interference—and at the trifling cost of less than one-fifth of a cent per hour.

Throw away your "B" Batteries—install a Kellogg Trans-B-former and your set will operate at maximum efficiency all of the time. You will also get these definite results:

1. Improved reception.
2. Reduced operating expenses.
3. Increased DX possibilities.
4. Improved appearance.

Developed, perfected and guaranteed by the Kellogg Switchboard and Supply Company, 1066 West Adams Street, Chicago, Ill.

Dealers—write for unusual trade proposition.

# KELLOGG

## Trans-B-former

# Perfect Control With FAMOUS Dials and Rheostats



## GENUINE BAKELITE

FAMOUS Dials and Rheostats make it easy to obtain that perfect control so necessary for distant reception.

## FAMOUS RHEOSTATS

Scientifically designed and made by skilled radio workmen, FAMOUS Rheostats enable you to control perfectly the current flow to the filament and maintain perfect contact

under all conditions. Assure best results with any type tube.

## FAMOUS SUPER GRIP DIALS

The super grip allows the FAMOUS dial to be rotated slowly and easily, assuring sharp tuning and perfect control. Just the dial for finding distant stations. Made in two, three and four inch sizes.

## DISTRIBUTORS WANTED

Good Territory Open—Write for Proposition.



Famous Radio Products, 33 Grand St., New York

# NEW CARTER "IMP" BATTERY SWITCH

Pat. 1-30-32

Most compact Switch on the market. "OFF and ON" Name Plate and Pointer clearly indicate position at all times.



One hole mounting. Operates by turning. — just like your dial. Knob matches your other Knobs and Dials. CARTER quality.

65c

Write for Catalogue of Other CARTER products

**Carter Radio Co.**  
7 209 S. STATE STREET 7  
CHICAGO

Any dealer can supply

# NOKORODE

## FOR EASY SOLDERING

Clean with file or sharp cloth all four (2000) sq. mils of iron.

Heat soldering iron, apply melted and of lead coating in stream of flux.

Apply a thin NOKORODE soldering paste.

While iron is still hot, rub with flux quickly on all four sides until iron is bright.

Apply a thick NOKORODE to both parts to be soldered.

Whenever possible heat the soldering iron underneath parts to be soldered. When the solder is running freely take away soldering iron and let soldered parts cool.


NOKORODE is so thoroughly effective that only a little is required for perfect results.

M. W. DUNTON CO.  
PROVIDENCE, R. I.  
U. S. A.

Perfectly soldered joints in the building of radio sets are a thing essential for best results. Perfect soldering the easy way has been achieved by amateur builders every where who have used NOKORODE, the Soldering Flux which is recommended by leading electricians and radioicians through-out the world.



## PAWOOD CIRCLE CUTTING TOOLS

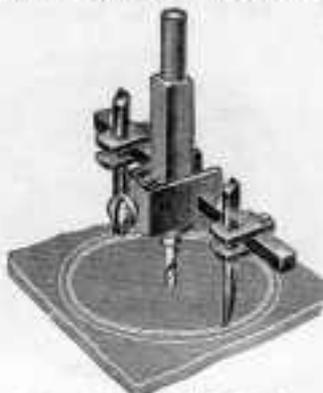

Made in 2 sizes—Retail—\$65-7.50. I. 50

Especially designed for the Radio Constructor. Made of the finest material and equipped with the highest grade high speed steel cutting bits. It does three things at once. It drills its own pilot, cuts out plug, and puts bead or scroll around the hole in one operation. Hole size—1 to 4 inches diam.

At leading hardware and radio stores or write direct to us.

Manufactured by  
GENERAL HARDWARE MFG. CO.  
34 Warren St. New York City

## HERCULES Aerial Mast

### All Steel Construction



Today, anyone may have an aerial mast of sufficient height to get mast to coast reception. A mast that is ideal for both receiving or transmitting. This mast is painted black and is furnished complete with galvanized steel guy wires and galvanized masthead pulley. You have no extras to buy. We pay the freight. 30' mast \$19. 40' mast \$25. 60' mast \$43. Mail the coupon for literature and large technical blueprint (supply limited).

S. W. HULL & CO.

Largest Manufacturers of Aerial Mast in the World  
2048 E. 79th St. Dept. M3. Cleveland, O.

# FREE BLUEPRINT COUPON

S. W. Hull & Co. Mail me without cost or obligation literature and large FREE Aerial Mast blueprint.

Name .....

Address .....

City .....

## POSTER'S PERFECT PANELS

### THE RECOGNIZED STANDARD

### ENGRAVING-MACHINING

## FORMICA

### RADIO PANELS

"POSTER'S Perfect Panels" is more than a slogan. It is a recognized fact. POSTER today supplies panels to manufacturers of national reputation. The POSTER plant is the largest organization in the country devoted exclusively to the machining and engraving of radio panels. What the POSTER plant has learned from years of panel specialization it is ready to put at your disposal. Write us!

**POSTER & CO. INC.**  
26-28 BARCLAY ST. N.Y. TEL. CORT. 4-965-6  
(WHOLESALE ONLY)

# I<sup>a</sup><sub>d</sub>M REGISTRY

The men whose names are listed below are prepared to handle all emergency work, take care of batteries, and replace tubes. Their charge is \$1.50 per hour, not including travelling time except to unusual distances.

The charge for listing in this section is 50c. for one month, \$2.00 for six months, \$3.00 for twelve months, payable in advance. The \* indicates that we have received letters from six set owners stating that the man after whose name the \* appears has handled their I and M work satisfactorily.

## A REGISTRY OF RADIO INSTALLATION and MAINTENANCE SERVICE MEN WHO INSTALL, MAINTAIN, and REPAIR RADIO EQUIPMENT

Conn., South Norwalk—A. GHIRARDI\*  
White Bridge. Tel. Nor. 2724

D. C., Washington—A. C. BURG  
U. S. Soldiers' Home. Tel. Col. 750 Br. 41

Ill., Oak Park—F. H. LESTER  
1155 Wisconsin Ave. Park 975

Me., Bangor—JOHN FOX  
120 Essex St. Tel. Ban. 7591

Md., Baltimore—OTTO U. JAHNELKA  
3710 No. Rd., Walbrook. Tel. Liberty 1202

Mass., Boston—H. A. NICKERSON  
201 Devonshire St. Tel. Cong. 5156

Mich., Detroit—R. J. McLEOD  
7725 Kolfog Ave. Tel. Bal. 9525

Mich., Detroit—WM. MILLIGAN  
6545 Woodward Ave. Tel. Northway 5691W

Minn., Minneapolis—GEO. A. BECKER  
4709 Wentworth Ave. Tel. Locust 6291

Mo., Kansas City—J. K. O'BRIEN  
2116 Penn. St. Tel. Oak. 9533

Neb., Omaha—W. J. F. SACKRIEDE  
2622 Jaynes St. Tel. Kenwood 5628

N. J., Trenton—F. C. SCOBAY  
478 Stuyvesant Ave. Tel. Web. 7254

N. Y., New York—APEX RADIO CO.  
123 Liberty St. Tel. Rector 3176

N. Y., New York—HERBERT MULLER  
954 Lexington Ave. Tel. Rhldr. 3905  
154 Nassau St. Book. 8040

N. Y., New York—RONALD MAAR  
470 W. 157 St. Tel. Wads. 9799

N. Y., New York—PAUL FRANCK  
317 West 119th St. Tel. Morningside 9140

N. Y., Brooklyn—J. McPARTLAND  
932 Flushing Ave. Tel. Fla. 1758R

N. Y., Buffalo—L. A. JEWELL  
69 Leslie St. Tel. Lan. 9234

N. Y., New York—RADIO CONST. LABS.  
71 W. B'way. Tel. Walker 2143

N. Y., New York—J. ROEMISCH  
841 Lexington Ave. Tel. Lex. 4420

O., Kent—KLADAG RADIO LABS.\*  
Kline Bldg. Tel. 127

Pa., Scranton—J. J. MAHON  
730 Capouse Ave. Tel. Bry. 2944

Pa., Lewistown—S. T. ROBINSON  
123 S. Main St. Tel. Lew. 723

Pa., Pittsburgh—L. E. SIEGFRIED  
1513 Tyndall St. Tel. Can. 6913

Tex., Fort Worth—C. L. FARRIS  
500 Taylor St. Tel. Wor. 3927

**SCREW MACHINE  
PRODUCTS  
& SPRINGS**

**Wm. STEINEN & CO.**  
297 Washington St.  
NEWARK - - - N. J.  
TEL. MARKET 9077


**fits Grid Leak  
any mounting**

**FRESHMAN PLUNGER  
TYPE VARIABLE GRID LEAK**  
was designed especially for the non-technical set owner who can replace in an instant the fixed grid leak with this new, efficient cartridge type Variable Grid Leak without requiring the change of a single wire.

At your dealer  
or by mail post-  
paid. Write for  
free catalogue.

**65c**

240 W 40 St.  
New York

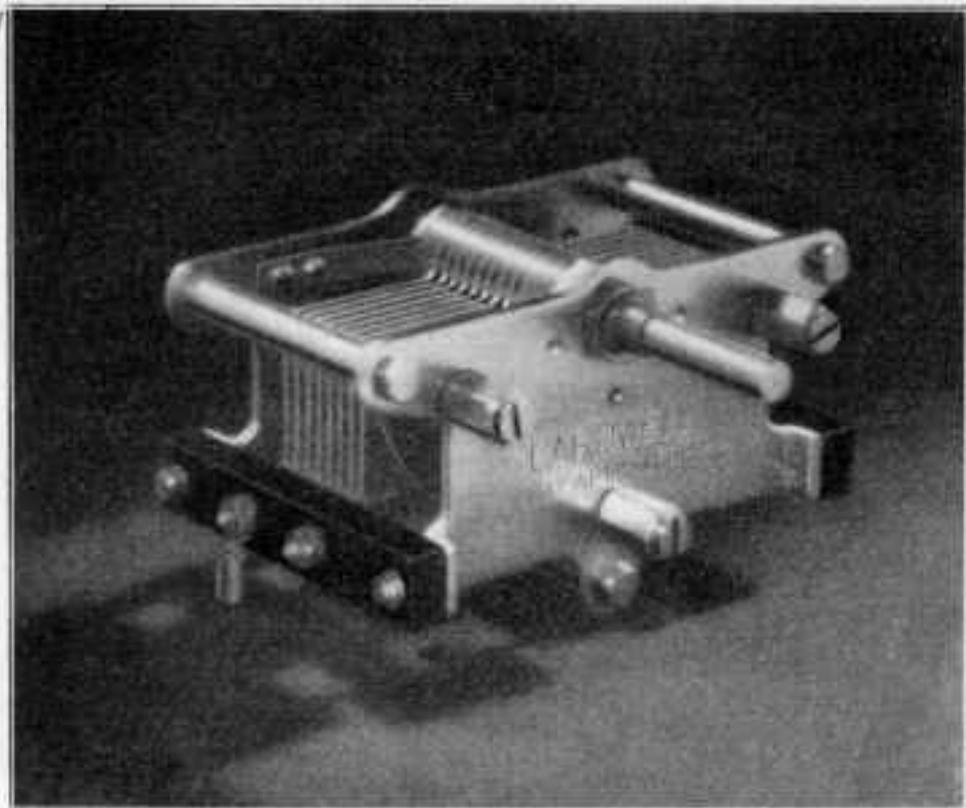

## Insist on **CARDWELLS**

### The *first* "low-loss" condensers

**C**ARDWELL invented the original *low-loss* condenser, using metal end plates and a grounded rotor. The phrase "low-loss" was in fact first applied to Cardwell Condensers by engineers to distinguish these highly efficient condensers from the ordinary varieties.

Cardwell Condensers have been universally adopted by radio editors, experts, and professionals. Cardwells have become the standard of comparison.

Performance is the only real test of a condenser. And Cardwell Condensers have proved their superiority because of their scientifically correct

design—small area of contact between insulation and stator supports, rigid three-point frame, permanent alignment, accurate adjustment, etc.

Such details permit exceptional distance records, smooth tuning free from noise, and prevent changes in capacity at given settings.

Use Cardwell Condensers in all receivers. There's a Cardwell Condenser for every requirement—seventy-six different types. A post-card brings you an education on condensers.

**Allen D. Cardwell**

*Manufacturing Corporation*

81 Prospect St., Brooklyn, N. Y.

---

# Improve your set with an **ACME** low loss condenser

**I**F YOU'VE got a good set, make it **better** with an Acme "lowest loss" Condenser.


To keep interference of all kinds out of your headphones or loud-speaker, you must have a sharp tuning system.

The Acme "lowest loss" Condenser will sharpen your tuning

circuit so much that not only will your range be increased but your fun won't be spoiled by interference.

Write us for 36-page book "Amplification without Distortion," containing many diagrams and useful hints on making a set and getting the most out of it. Enclose 10 cents in stamps.

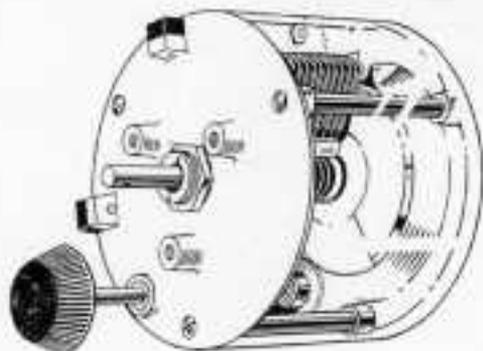ACME APPARATUS COMPANY  
Dept. HI Cambridge, Mass.



Acme low loss condenser  
Price \$6.50

# ACME

*~for amplification*

---

# RADIO TOOLS

*of Technical Accuracy for the  
Radio Set Builder, Engineer and Manufacturer*



The Radio Tool Department of Hammacher, Schlemmer & Co. places at your disposal a complete stock of the highest grade radio and testing instruments. Whether you need sets or a screw driver or a complete set of guaranteed tools—whether you are a radio or a radio repair man, your order will be delivered to you the day it is received.

The most accurate tools, the name of Hammacher, Schlemmer & Co. has been known wherever good tools are used. It is a name which is known to stand for reliability. It is a name which stands as a permanent guarantee of satisfaction to its customers.

## RADIO MANUFACTURERS

Since at Hammacher, Schlemmer & Co. when producing their work shops, instruments and testing machines and sets for radio assembly work and testing instruments, but for serious, reliable hardware of all kinds, good work, good wiring and necessary tools—in fact for all lines of radio hardware, work and repairs.

A free to Dept. 200 will bring an immediate answer concerning any problem relating to tools or radio hardware.



### "Genuine Brand" Test Kit No. 200

Radio Kit No. 2-25 Radio Set (Standard)..... \$25.00 each for  
Radio Kit No. 200A Tools..... 10.00 each for

#### (In Kits or Separable)

Handmade Solder  
Fluxes and Sippers  
Nutrun  
Screw  
Soldering Irons  
Hesseltman's Plaster  
Pocket Wrenches (Standard)  
Auto-Clutch Pliers  
Circuit  
Solder

#### Also

Voltsmeter  
Ammeter  
Galvanometer  
Detector Instruments  
Precision Instruments  
Files  
Screw Drivers  
(Screw and Hand)  
Screw Drills

Machinist Screws  
Steel Screws  
All Sizes  
Machinist Screw Nuts  
Pocket Squares  
High Bits  
Chisel and  
Machinist Tapping  
Screw and Drill Bits  
Sheet Copper  
Sheet Aluminum  
Copper Wire  
(Hard and Soft)



**HAMMACHER, SCHLEMMER & CO., INC.**  
NEW YORK, SINCE 1848 4TH AVE. & 13TH STREET