RADIO'S GREATEST MAGAZINE



EXPERIMENTER PUBLISHING COMPANY, 230 FIFTH AVENUES NEW YORK

The Vacuum Tube of Today

remains the most sensitive device in the radio world. During the past year it has reached new heights of performance in making A C reception possible. Cunningham Radio Tubes have pioneered and blazed the way for each progressive step and maintained their high standard of quality from the earliest days of the industry.

> E. T. CUNNINGHAM, INC. NEW YORK CHICAGO SAN FRANCISCO



J OINING the Radio Association enables you to cash in on Radio *now!* Follow its success-proven plans and you can earn \$3 an hour, in your spare time, from the very first. Over \$600,000,000 is being spent yearly for sets, supplies, service. You can get your share of this business

can get your share of this business and, at the same time, fit yourself for the big-pay opportunities in Radio.

Founded on a New Idea

Members of the Association do not wait for months before they make money out of Radio. Without quitting their jobs. our members are earning \$25 to \$75 a week spare time by building "tailored" radio sets, serving as "radio doctors," selling ready built sets and accessories, or following one of the many profitmaking plans of the Association.

Earned \$500 in Spare Hours

Hundreds earn \$3 an hour as "radio doctors." Lyle Follick, Lansing, Mich., has already made \$500 in spare time. Werner Eichler, Rochester,

time. Werner Eichler, Rochester, N. Y., is earning \$50 a week for spare time. F. J. Buckley, Sedalia, Mo., is earning as much in spare time as he receives from his employer.

We will start you in business. Our cooperative plan gives the ambitious man his opportunity to establish himself. Many have followed this plan and established radio stores. Membership in the Association has increased the salaries of many. Scores are now connected with big radio organizations. Others have prosperous stores.

A year ago Claude De Grave knew nothing about Radio. Today he is on the staff of a famous radio manufacturer and an associate member of the Institute of Radio Engineers. He attributes his success to joining the Association. His income now is 350% more than when he joined.

Doubled Income in Six Months

"I attribute my success entirely to the Radio Association," writes W. E. Thon, Chicago, who was clerk in a hardware store before joining. We helped him secure

the managership of a large store at a 220% increased salary.

What a Membership Can Do for You

- 1—Enable you to earn \$3 an hour upwards in your spare time.
- 2—Train you to install, repair and build all kinds of sets.
- 3—Start you in business without capital, or finance an invention.
- 4—Train you for the \$3,000 to \$10,000 big-pay radio positions.
- 5—Help secure a better position at bigger pay for you.
- 6—Give you the backing of the Radio Association.

A MEMBERSHIP NEED NOT COST YOU A SINGLE CENT "In 1922 I was a clerk," writes K. O. Benzing, McGregor, Ia., "when I enrolled. Since then I have built hundreds of sets from 1-tube Regenerative to Superheterodynes. I am now operating my own store and my income is 200% greater than when I joined the Association. My entire success is due to the splendid help it gave."

Easiest Way Into Radio

If ambitious to become a Radio Engineer, to fit yourself for the \$3,000 io \$10,000 opportunities in Radio, join the Association. It gives you a comprehensive, practical and theoretical training and the benefit of our Employment Service. You early while you learn. You have the privileg of buying radio supplies at wholesale. You have the Association behind you in carrying out your ambitions.

ACT NOW—if you wish Special Membership Plan

To a limited number of ambitious men, we will give Special Memberships that may not-need not-cost you a cent. To secure one, write today. We will send you details and also our book, "Your Opportunity in the Radio Industry." It will open your eyes to the money-making possibilities of Radio. Write today.

RADIO ASSOCIATION OF AMERICA, 4513 Ravenswood Ave., Chicago, 111.	Dept. RN-4
Gentlemen: Please settd me by return mail full Membership Plan and also copy of you tunity in the Radio Industry."	details of your Special ur book, "Your Oppor-
Name	
Address	
CityState	

1090

Radio News for April, 1928



General Advertising Dept., 230 Fifth Avenue, New York City

General Advertising Dept., 250 Finth Astronov, ADVERTISING REPRESENTATIVES L. F. MCLURE, 720 Cass Street, Chicago, 111, DAVIES, DILLON & KELLY, 15 West 10th St., Kansas City, Mo. A. J. NORRIS HILL CO., 5 Third St., San Francisco, Calif. 112 West 4th St., Los Angeles, Calif. Leary Building, Scattle, Wash.

G



Check it with any set you choose! -then hook it up and learn first hand its

her up	n hook it up and led erior tonal and red	arn first have ception qua	nd lit <mark>ie</mark>	its es!	UNIT
S	PECIFICATIONS	AC BANDBOX 704	?	?	SINAC
1.	Genuine Neutrodyne circuit.	Yes			ATTEO
2.	All elements totally shielded.	Yes			DAND
3.	Full 180 volts on plate of output tube.	Yes			PA
4.	Supplemental tuning devices for hair line alignment of con- densers to secure sharpest possible tuning (Acumina- tors).	Yes			or in two units for console installatio
5.	Single station selector.	Yes			at \$90
6.	Illuminated dial.	Yes			
7.	Volume control that will reduce heavy local reception to a whisper without detuning and without distortion.	Yes			
8.	Power plant with a condenser of 30 mf capacity.	Yes			and the second second
9.	Self-healing condenser.	Yes			The NEW dry cell 4
10.	Modern, neat, compact, richly finished cabinet.	Yes			Bandbox Juni
11.	Adaptability to any type of con- sole cabinet by being available in single or double units.	Yes			A new dry cell receiver with all the Crosley Ba features—selectivity, sensitivity, volume and a ance. Ideal for homes having no alternating li
12.	Quantity production price of less than \$100.	Yes			current or where storage battery service is not able or desired. Especially desired because economical installation cost and opera- tion. Batteries last months! Use Crosley

or in two units console installation



NEW dry cell 401 ndbox Junior

A new dry cell receiver with all the Crosley Bandbox features—selectivity, sensitivity, volume and appear-ance. Ideal for homes having no alternating lighting current or where storage battery service is not avail-able or desired. Especially desired because of its economical installation cost and opera-tion. Batterieslast months! Use Crosley Musicone for perfect reproduction!

Battery type Bandbox operating with storage batteries or power supply \$55.

"You're there with a Crosley

Crosley is licensed only for Radio Amateur, Experimental and Broadcast Reception. Montana, Wyoming; Colorado, New Mexico and West prices slightly higher. Write Dept. 23 for descriptive literature. THE CROSLEY RADIO CORPORATION CINCINNATI, OHIO POWEL CROSLEY, Jr., Pres.

INDEX TO ADVERTISERS

A Page P	2			
Abox Co., The 1096 Deutschmann Co., Tobe 1171 Karas Electric Co. 1180 Radio Equipment Co. 1166 Acue Wire Co. 1166 E L Radio Equipment Co. 1166 Acue Vire Co. 1187 E L Radio Equipment Co. 1166 Acue Vire Co. 1187 E Lacauft Radio Electric Corp. 1171 Radio Equipment Co. 1166 Acue Vire Co. 1187 E Electric Specialty Co. 1187 Radio Equipment Co. 1160 American Mechanical Labs. 1189 Electric Specialty Co. 1171 Karas Electric Corp. 1187 American Mechanical Labs. 1189 Firsthure Supply Co. 1157 Sangamo Electric Co. 1187 Marce Corp., The 1191 Firsthure Supply Co. 1157 Lacauft Radio Co. 1167 Barawik Co., The	A Page	D Page	R Page	Page
All Radio Co. 1187 S American Bosch Magnete Orp. 1188 Electric Specialty Co. 1171 R. E. 1160 Lacey 1160 American Mechanical Labs., marican Mechanical Labs., marinando Mecheris, marican Mechanical Labs., mariatan Me	Abox Co., The 1096 Acme Wire Co. 1163 Aero Products, Inc. 1176 Aerovox Wireless Corp. 1185	Deutschmann Co., Tobe 1171 E Ellia Products Mfg. Co	Karas Electric Co 1180 Knapp Electric Corp 1177 L	Radio Equipment Co
B Fanspeaker Radio C_0	All Radio Co	Electric Specialty Co	Lacault Radio Electric Labs., R. E	S Sangamo Electric Co
$ \begin{array}{c} \begin{array}{c} \begin{array}{c} \begin{array}{c} 1180\\ Burt, Dr. Rob't C. \dots 1187\\ Burt, Dr. Rob't C. \dots 1187\\ Burt, Dr. Rob't C. \dots 1157\\ Burt, Dr. Rob't C. \dots 1157\\ Burt, Dr. Rob't C. \dots 1157\\ \\ \end{array} \end{array} \\ \begin{array}{c} \begin{array}{c} \begin{array}{c} \begin{array}{c} \begin{array}{c} \begin{array}{c} \begin{array}{c} \begin{array}{c}$	B Barawik Co., The1159, 1188, 1191 Boudette Mfg. Co	Fanspeaker Radio Co	M M. & II. Sporting Goods Co 1189 Midwest Radio Corp	Shure Radio Co
G North Shore Radio Labs., 1180, 1188 Tower Mig. Corp	Burt, Dr. Rob't C 1159	Formica Insulation Co	N National Company, Inc	T Telephoue Maintenance Co 1184 Teleplex Co 1166 Thordarson Electric Mfg. Co 118;
Central Radio Labs. 1189 H Omnigraph Mfg. Co. 1167 Chemical Institute of N. Y., 1095 H Uteration of the state of the stat	C. F. Mfg. Co., Inc 1178 Carborundum Co., The 1157 Carter Radio Co 1169	G General Electric Co 1159 General Radio Co 1171	North Shore Radio Labs., 1180, 1188 O	Tower Mfg. Corp 1167 Townsend Laboratories1165, 1187 Tyrman Electric Corp 1188
LineHamilton-CarrRadioCorp.1173 \mathbf{p} ChicagoNatioApparatusCo.1181Hamilton-CarrRadioCorp.1173ChicagoStockGearWorks1157Hamilton-CarrRadioCorp.1169CloverleafMfg. Co.1168HammarlundMgc. Co.1162Parker, C. L.1188ConsoradCo., Inc.,1173IIamilton-CarrRadioMarren Electric Co.1167ConsumersRadioCo.1173IIamilton-CarrNatioNationConsumersRadioCorp.1173IIamilton-CarrNationConsumersRadioCorp.1173NationNationConsumersRadioCorp.1173NationNationConsumersNationNationNationNationNationConsumersRadioCorp.1173NationNationConsumersNationNationNationNationNationConsumersRadioCorp.1164NationNationConsumersNationCorp.1164NationNationConsumersMationNationNationNationNationConsumersNationNationNationNationNationConsumersNationNationNationNationNationCuruningham,Inc.J.NationNationNationCuruningham,Inc.Infe </td <td>Central Radio Labs,</td> <td>н</td> <td>Omnigraph Mfg. Co 1167 Outdoor Enterprise Co 1176</td> <td>Ultradyne Sales Co 108</td>	Central Radio Labs,	н	Omnigraph Mfg. Co 1167 Outdoor Enterprise Co 1176	Ultradyne Sales Co 108
Cuntain gram, Inc., P., L., J.M.P. Mfg. Co. 1164 Radio Association of America 1089 N-L Radio Labs. 117. Curtan Mfg. Co. Jewell Electrical Inst. Co. 1182 Radio Engineering, Inc. 1154 Yaxley Mfg. Co. 119.	Chicago Radio Apparatus Co 1093 Chicago Stock Gear Works 1157 Cloverleaf Mfg. Co	Hamilton-Carr Radio Corp 1173 Hammarlund Mfg. Co 1169 Hammarlund-Roberts, Inc 1182 Harco Co., The 1161 I Illinois Transformer Co., Back Cover Independent Electric Works 1165 J	P Parker, C. L	₩ Walker Co., The, Geo. W 1166 Warren Electric Co
	Cunningnam, Inc. F. 1. Inside Front Cover Curtan Mfg. Co	J-M-P Mfg. Co 1164 Jewell Electrical Inst. Co 1182	Radio Association of America., 1089 Radio Engineering, Inc	N-L Radio Labs 117. Yaxley Mfg. Co 119

Now in limp, syede leather binding S. Gernsback's Radio Encyclopedia

THE most valuable of Radio Books—S. Gernsback's Encyclopedia—now the most beautiful. This foremost Radio Encyclopedia is now offered in this luxurious new binding to meet the demand for a more handsomely bound volume. The limp suede leather edition sells for \$5.00. The Keratol-leather stiff binding still can be had for \$2.00.

Remember—this is an encyclopedia—not a dictionary! It took over two years of intensive labor to compile it. It is the first Radio Encyclo-

S. GERNSBACK 230 FilmSBACK Radio Exerciclopedia. I will pay bost D Linnp State of the state of the state Check while have based of the state Name. Address. Town. State. State. State. State. State State. State State. State S

pedia ever published. S. Gernsback's Radio Encyclopedia contains the

KERATOL BINDING

/ Simply pay the postman on delivery. Over 25,000 copies in the stiff binding already sold. The book is nearly 1 inch thick and measures 9x11 inches.

S. GERNSBACK, 230 FIFTH AVENUE, NEW YORK CITY

Will TrainYou at Home to Fill a Big-Pay



You can build

100 circuits with

the six big outfits of Radio parts

1181111111

RICH REWARDS

RADIO

3 of the 100 you

can build

I give you

IF you are earning a penny less than 50 a week, send for my book of information on the opportunities in Radio. It's FREE. Clip the coupon NOW. A in Radio. In Radio. It's FREE. Clip the coupon NOW. A flood of gold is pouring into this new business, creating hundreds of big pay jobs. Why go along at \$25, \$30 or \$45 a week when the good jobs in Radio pay \$50, \$75, and up to \$250 a week. My book, "Rich Rewards in Radio," gives full information on these big jobs and explains how you can quickly become a Radio Expert through my easy, practical, home-study training.

SALARIES OF \$50 TO \$250 A WEEK NOT UNUSUAL

Get into this live-wire profession of quick success. Radio needs trained men. The amazing growth of the Radio business has astounded the world. In a few short years three hundred thousand jobs have been created. And the biggest growth of Radio is still to come. That's why salaries of \$50 to \$250 a week are not un-usual. Radio simply hasn't got nearly the number of thoroughly trained men it needs. Study Radio and after only a short time land yourself a REAL job with a REAL future.

YOU CAN LEARN QUICKLY AND EASILY IN SPARE TIME

Hundreds of N. R. I. trained men are today making big money-holding down big jobs—in the Radio field. Men just like you-their only advantage is training. You, too, can become a Radio Expert just as they did by our new practical methods. Our tested, clear training, makes it easy for you to learn. You can stay home, hold your job, and learn quickly in your spare time. Lack of education or experience are no drawbacks. You can read and write. That's enough.

MANY EARN \$15, \$20, \$30 WEEKLY ON THE SIDE WHILE LEARNING

My Radio course is the famous course "that pays for itself." I teach you to begin making money almost the day you erroll. My new practical method makes this possible. I give you SIX BIG OUTFUTS of Radio parts with my course. You are taught to build practically every type of receiving set known. M. E. Sullivan, 412 73rd Street, Brooklyn, N. Y., writes, "I made S720 while studying." Earle Cummings, IS Webster Street, Haverhill, Mass.: "I made S375 in one month," G. W. Fage, 1807 21st Ave., Nashville, Tenn.: "I picked up \$935 in my spare time while studying."

YOUR MONEY BACK IF NOT SATISFIED

"Til give you just the training you need to get into the Radio business. My course his you for all lines-manufacturing, selling, servicing sets, in business for yourself, operating on board ship or in a broad-casting station-and many others. I back up my training with a signed arreement to retund every penny of your money if, after completion, you are not satisfied with the course I give you.

ACT NOW-64-Page Book Is FREE

Send for this blg book of Radio in-formation. It won't cost you a penny. It has put hundreds of fellows on the road to bigger pay and success. Get it. Investigate. See what Radio has to offer you, and how my Employment Department helps you get into Radio after you graduate. Cilp or tear out the coupon and mail it RIGHT NOW.

J. R. SMITH, President Dept. 4S National Radio Institute Washington, D. C.

Originators of Radio Home Study Training



to big pay Mail This FREECOUPON Today J. E. SMITH, President Dept. 4S, National Radio Institute Washington, D. C. Dear Mr. Smith: Kindly send me your big book, "Rich Rewards in Redio," giving information on the big model Employment Service to all Graduates

Find out quick

about this

practical way

opport ing with and the	th six	s in big s pl;	Rai	lio itflt mo	ano s.	l y I Ide	Un un T	r p sde	rat rst ob	an	cal d ati	ni th	eth s h	od	of	10
Namc.													A	je.		
Address	8															
Ctty													Sta	ile.		
Occupa	tion															



Earns Price of Course in One Week's Spare Time Inverbeen so busy with Radio vock that I have hoe thad time spare ilmed. I earned enough to pay for may course. I have more work than I can do. Recently I made enough mourse in one month's spare time to pay for a \$35 beautiful console all-elec-tric fuello. When I enrolled I did not know the difference be-tween a rheostat and a coil. Now I am making all kinds of money. —Earlo Cummings, 18 Webster Street, Haverhill, Mass,



Here's the

PROOF







1093





Know your Radio Repair your Radio Set yourself--it's easy!

No matter how much or how little you know of your radio receiver, this new "Radio Trouble Finder" book is going to be a big help.

It explains the common and special faults of all the standard receivers of today; tells how to recognize instantly, by various methods, where the trouble lies and also gives special simple tests by which you can determine what is wrong with your receiver. Then for each particular fault there is explained the proper procedure for correcting it.

> Book Contains 64 Pages Size, 6 x 9, Illustrated Handsome 2 Color Cover



THE CONSRAD CO., Inc. 230 Fifth Avenue New York, N. Y.

he bought the





Rockville, Conn.

Chemical Institute of New York, Inc., 66 West Broadway, New York, N. Y. Gentlemen:

You will probably be pleased to learn one of the lessons gave me an idea to turn my chemical knowledge to profitable account. I am now making a varnish and paint which undersells the other type products by \$2.60 a gallon, in some cases more. Have been receiving gallon orders from painters during past week which has netted me a profit of \$13.50 for my "spare-time chemical industry. Wany thanks for your training thus far. Youre very truly.

James J. Xelly

Chemistry Student turns Knowledge into big Sparetime Profits!

Because he knew how to prepare his product from a knowledge of chemistry, J. J. Kelly produced a highly profitable article far below the price of organized competition. Sales came easy—because competition was overcome. Chemistry solved his problem.

Boundless Sparetime profit opportunities from Chemical Formulas—for those who grasp them

Chemical Formulas are the basis of, not one, but *thousands* of big profit sparetime businesses, such as selling soaps, cleaning and polishing compounds, paints, acids, inks, cements, extracts, glues, gold, silver, and bronze hacquerings, oils, perfumery, rust removers, etc.

With a knowledge of chemistry you can beat J. J. Kelly's record by many dollars a week. You need not be dependent on wholesale or retail companies to supply your finished products for sale.

You can make up your own products at home and sell cheaper than any competitor. That means quick, easy sales in large quantities.

YOU CAN LEARN AT HOME

To qualify for this remarkable calling requires elaborate specialized training. For-

merly it was necessary to attend a university for several years to acquire that training, but thanks to our highly perfected and thorough system of instruction, you can now stay at home, and let us educate you in Chemistry during your spare time. Even with only common schooling you can take our course and equip yourself for immediate practical work. Dr. Sloane gives every one of his students the same careful, personal supervision that made him celebrated throughout his long career as a college professor. Your instruction from the very beginning is made interesting and practical, and we supply you with apparatus and chemicals for performing the fascinating analyses and experimental work that plays such a large part in our method of teaching, and you are awarded the Institute's diploma after you have satisfactorily completed the course.



T. O'CONOR SLOANE A.B., A.M., LL.D., Ph.D.

Noted Instructor, Lecturer, aud Author. Formerly Treasurer American Chemical Society and a practical chemist with many well-known achievements to his credit. Not only has Dr. Sloane taught chemistry for years, but he was for many years engaged in commercial chemistry work.

EASY MONTHLY PAYMENTS

You don't have to have even the small price of the course to start. You can pay for it in small monthly amounts—so small that you won't feel them. The cost of the course is very low, and includes everything, even the chemistry outfit—there are no extras to buy with our course. Our plan of monthly payments places a chemical education within the reach of everyone.

EXPERIMENTAL EQ	UIPMENT	FURNISHED	то
EVER	Y STUDEN	T	

We give to every student without additional charge this chemical equipment, including fifty-two pieces of laboratory apparatus and supplies, and fifty-two different chemicals and reagents. These comprise the apparatus and chemicals used for the experimental work of the course. The fitted heavy wooden box serves not only as a case for the outfit but also as a useful laboratory accessory for performing countless experiments.

Don't Wait—Mail Coupon Now! CHEMICAL INSTITUTE OF NEW YORK 16-18-R—East 30th Street NEW YORK, N. Y.

MAIL THE COUPON FOR FREE BOOK

Clip the coupon below and mail it at once. Your name and address on the coupon will bring you by return mail our interesting free book, "OPPORTUNITIES FOR CHEMISTS," and full parabout the course and what it will do for you.

CHEMICAL INSTITUTE OF NEW YORK, Home Extension, Division 4, 16-18-R-E. 30th St. New York, N. Y.	R-4-28
Please send me at once, without any obligation on m free Book. Opportunities for Chemists, and full parti- the Experimental Equipment given to every student. tell me about your plan of payment.	y part, your culars about Also please
Name	
Address.	
CityState.	

595,728 Hours of Actual Operation on 1182 Different Sets Proves Beyond All Doubt the ABOX Claim to Superiority



 1182 users of ABOX ELIMINATORS wrote The Abox Company between January 17th and February 10th, 1928, giving a detailed account of their own experiences with the ABOX. All kinds of sets were used in this test under all conditions. Remember, this is not a report of a laboratory test, but is a test made in the hands of users like yourself.

The following comments are typical:

"Better reception"—"Would never go back to battery operation"—"Superior to battery service"—"No comparison with battery service"—"Much better"—"Entirely satisfactory"—"Improved volume and quality of reception"—"Has batteries skinned a mile"—"50% better than my old battery."

Practically without exception, the 1182 users who wrote us say:

"I most heartily recommend the Abox to my friends."

It is no longer necessary to be without electric operation. More than likely you are now using a "B" power unit. Don't even consider discarding your set or your "B" power unit—simply attach ABOX to your present set and you have true electric operation.

ABOX distribution is nation-wide. Any dealer can supply you. In case your local dealer does not carry ABOX, send us your order and we will see that you receive your ABOX immediately.

Remember the ABOX is guaranteed for one year. If it doesn't do what we claim for it, your dealer is authorized to exchange it for a new one.

Use coupon for further information

The **Abox** Company

215 North Michigan Avenue

Chicago, Illinois



Editorial and General Offices, 230 Fifth Avenue, New York

APRIL, 1928

No. 10

Radio News' New Policy

By Hugo Gernsback

THE articles in RADIO NEWS are in my opinion "inspired" by your ad-vertisers and of little value to your subscribers. Most radio magazines are similarly unreliable. Why don't you occasionally publish something worth while? Your readers are not all mo-

schile? Your readers are not all mo-rons. When and if you publish a radio magazine for the benefit of your sub-scribers rather than your advertisers. I will again subscribe. Who wants a

Yours very truly,

FRANK II, CHASE, M.D., 2362 W, 21st Street, Los Angeles, Calif.

catalog?

W HEN the first number of RADIO NEWS was launched in July, 1919, 1 said as follows: "And here is the platform upon which RADIO NEWS stands. 1 pledge myself to a strict adherence to every plank :

Vol. 9

Third: Absolute 100% of it—nothing else.
 "First: Only Radio—100% of it—nothing else.
 "Second: An organ for and by the amateur. The anateur's likes and wants will always come first in this nagazine.
 "Third: Absolute Independence. RADIO NEWS has only one Boss—its readers. This magazine is not, nor will it ever he, affiliated with any stiffing. commercial radio interests whatsoever.
 "Fourth: Truth—first, last and always. When you see it in RADIO NEWS you may be sure that it is so. Not being affiliated with commercial radio interests, this magazine will have no reason to suppress important articles, discoveries, etc.
 "Fifth: RADIO NEWS is and will be the sworp enemy of all adverse and unfair radio legislation.
 "Sixth: Instructive first and last. Up-to-date scientific articles for your instruction will always have first place in RADIO NEWS. We shall publish purely scientific articles every month, articles that on account of their length are often crowded out of other my opinion "in vertisers and of all important radio news in this magazine from one to three months ahead of all other publications— That was before the days of broadcasting and

always." That was before the days of broadcasting and when radio fans still were "bugs" and transmit-ting amateurs; but, as a whole, the situation has not changed, nor has the platform of RADIO NEWS changed at all. On the other hand, in an art that grows as rapidly as radio, changes occur overnight and it is necessary for any organization, whether a pub-lisher or a factory, to conform itself to those changes. For instance, in 1919 there were some 10,000 amateurs, and not one of the so-called "broadcast fans," because there was yet no broadcasting.

changes. For instance, in 1919 there were some 10,000 anateurs, and not one of the so-called "broadcast fans," because there was yet no broadcasting.
When broadcasting came along, it meant an important change, not only to the amateurs and fans, but to the radio industry as a whole function of the source of the so

Since the radio parts dealers declined from 30,000 to 2,500 in a few years, if this decline were allowed to go on, it would soon be impossible to print RADIO NEWS; because the manufacturers of the radio material would have no longer an outlet, and the radio constructors and home builders would find it impossible to buy materials. It is true that a builder can wind his own coils, and drill his own panels; but certain articles, such as switches, condensers, tubes, sockets and others, he can never hope to make, and must buy. Against its better judgment, RADIO NEWS, during 1927, endeavored to better trade conditions by publishing manufacturers' names and giving manufacturers' specifications in its text pages; because it scemed that it would thus be made easier for the reader to buy suitable material than if no names were given and he had to guess them. In doing so, RADIO NEWS honestly believed that not only would it serve its readers, as it had always done, but the radio trade as well. It is, however, admitted now that this policy was wrong and, beginning with this issue, we revert to our former custom of not mentioning any manufacturers' names or trademarks of parts and circuits of any kind in the text pages of RADIO NEWS in that respect, we go back to our former practice of the years previous to 1927. It was soon found that readers of RADIO NEWS were controlling the text pages; and it must be calmitted find that that is the way it often looked to the outsider. We the scants a

includ of your sub-your advertisers, I Who wants a Who wants a Who wants a Who wants a At no time, however, did RADO News reap any material benefit from specifying manufac-turers' names and materials. If any proof is wanted, the constant advertising shrinkage of RADIO News during 1927 is glowing testimony of this fact. At no time did the trade (par-ticularly the parts manufacturers) really support RADIO News, in spite of its publishing their names and specification was reached, since it was im-tolerable situation was reached, since it was im-tolerable situation was reached, since it was im-one issue the products of all manufacturers, many enemies were made.

wherever one friend was usade among the parts manufacturers and, memies were made. But the worst part was that many readers became dissatisfied with seeing so many circuits, which to them seemed sponsored by kit manu-facturers; and some refused to read RADIO NEWS any longer. Letters like that printed here became numerous as time went on. Yet it must be evident to every fair-minded reader that the publishers did not reap a harvest from the manufacturers. Quite to the contrary, the publishers lost heavily during the experiment. So, beginning with this issue, we revert to our former rule, as follows: RADIO NEWS will no longer mention any radio material by a trade-marked name; no manufacturers' names will be printed in an article on construction. Circuits originated by parts and kit manufacturers will not be given the manufacturers' names; if a worth-while circuit comes along, RADIO NEWS will bestow on it its own proper name. An important new policy will be initiated, under which RADIO NEWS will give away free the blueprints that, for over two years, have been sold for from \$1.00 to \$2.00. These blueprints with full specifications will, however, contain the names of the parts which were used by the constructor who designed the actual assembly. On the blueprint will be mentioned the trade name and the manufacturers' names, so that the constructor who wishes to build the eircuit can do so with the least amount of difficulty. But this information, as we have said, will *not* be published in the text pages of RADIO NEWS. In all other respects RADIO NEWS in all other respects RADIO NEWS. In all other respects mare NEWS policy will be the same, except that hereafter only one featured constructional articles will be published each month. This does not exclude the publication of constructional articles for beginners, describing circuits in which not more than three tubes are used. There will, therefore, be not more than three tubes are used. There will, therefore, be not more than three tubes are used. There will, theref

Mr. Hugo Gernsback speaks every Tuesday at 9.30 P. M. from Stations WRNY (326 meters) and 2XAL (30.90 meters) on various radio and scientific subjects.

www.americanradiohistory.com



B ACK a few years—and not so very many at that—it was said that but one human faculty could jump in a fraction of a second from one end of the earth to the other—the imagination. Up to a comparatively short time ago this was true; but, with the advent of radio broadcasting as it is known today, it became possible practically to annihilate the

limitations of space, with respect to sound. Is it now considered marvelous when a singer is heard, three thousand miles distant? Indeed, no; the listeners take it as a matter of course, as they do the other wonderful inventions in daily use.

But until very recently it was still up to the overworked imagination to picture the appearance of the performer who was broadcasting. In some

broadcasting. In some cases this may have been for the best; as the imagination is a wonderful artist, and produces often beauty where beauty is not. But, for better or for worse, thanks to the further developments made by Dr. E. F. W. Alexanderson in the art of television, what actually occurs in the broadcast studio can now be seen by the radio audience.

At the top of the page, tuning the television receiver: the image is seen through the small square opening on a level with the openator's eyes. Notice the broadcast receiver and lond speaker. At the left, Fig. D, shows the rear of the receiver: one man is pointing out the universal motor, which drives the scanaing disc. Above the motor is the Moore neon lamp. On the lower shelves are batteries and the amplifier and receifier tubes, Dr. E. F. W. Alexanderson is seen at the left in each illustration. Although the picture as seen in the television receiver appears no more than three inches square, and there are instants when it is obliterated by static or some other interference, the remarkable part of the story is that the device worked at all. Every so often, during the last few years, enthusiastic articles have appeared, telling how television is rapidly becoming a reality instead of an engineer's dream. But these fulfillments of dreams were in laboratories; now television has been carried to the home.

TELEVISION DEMONSTRATION

In one corner of a vast room in the General Electric Company's research laboratory at Scheneetady, N. Y., a few days ago, were set up an are light, a rapidly-revolving metal disc, four photoelectric cells in a frame, and several boxes. Just around a corner a group of men were gathered in a room totally dark, save for two squares of pinkish light about three inches square. These two squares of light were the cynosure of all eyes; these pinkish squares were what many of the men in that room had travelled hundreds of miles to see; for they were the proof that television in the home is no longer a dream, but an actual fact. A young woman was seated before the bank of photoelectric cells, with narrow bands of light and shadow playing across her features. She smiled, frowned, rolled her eyes, and smoked a cigarette-and all these actions were instantly and faithfully pictured in the little squares of pinkish light in the adjoining dark room. At the same time, the conversation which she kept up with one of the operators came into the dark room through a loud speaker. Then



her place was taken by a young man with a ukelele and, although the instrument was invisible (being below the line of vision of the transmitting apparatus), his voice and the music came from the loud speaker as his fave appeared in the magic squares.

The question will present itself naturally to the reader's mind: "How well did these faces come over the air?" It was possible to see every detail in the features, the individual teeth, for example; when the eyes were rolled, one could follow with ease the movement of the pupils." In short, the transmission of faces by radio can be compared in quality to moving pictures in their earliest days.

In three homes in different sections of Schenectady, similar television receivers had been installed to show that reception in the home is possible and practicable. A short antenna was employed to pick up the 37.8meter wave on which the television impulses were broadcast. The results obtained in the homes were of the same excellence as those demonstrated in the laboratory.

THE ELECTRIC EYE

The transmitting apparatus for broadcasting television is not very complicated, as can be seen from Figs. A and B, which show the pick-up. In the left foreground of Fig. A is a powerful are light, the rays of which are broken up by the spirally-arranged holes in the disc, which is rotating at the rate of eighteen revolutions per second, being driven by a small motor. The light rays are concentrated and focused on the face of the girl by means of the lens held in the square wooden support. See Fig. B.

After the rays of light from the arc have been broken up by the revolving disc and focused on the face of the subject (where they appear to the camera as a series of light and dark lines; see Fig. C), they are reflected from the surface of the face to the four photoelectric cells in the thick, square frame of galvanized iron. These possess the property of changing light energy into electric energy. (These cells were described on page 640 of the December, 1927, issue of RADIO NEWS; previous television experiments will be found described in the June, 1927, issue.) The output of these cells, after being amplified, modulates the carrier wave of the 37.8-meter transmitter, the antenna of which is located on the roof of the research laboratory. In Fig. B may also be seen at the right of the table the condenser microphone for picking up the voice, which was simultaneously broadcast on WGY's regular wave of 379.5 meters. A very short wavelength was chosen for broadcasting these "pictures" because a channel 40 kiloeycles wide is needed; this is because of the depth of modulation necessitated by the great range of differences in shading, which must be reproduced in the transmission of vision.

THE ELECTRIC PAINTBRUSH

The average radio enthusiast is most likely much more interested in the apparatus for reception than in that just described. Compared with the television receivers that have been described in this magazine previously, the latest one is simplicity itself. In place of the loud speaker, a Moore neon tube is connected in the output of a short-wave

t of a short-wave receiver of the regenerative type. The most interesting property of the neon lamp, which was invented by D. Mc-Farlan Moore (as related in Mr. Moore's biography, "Thirty years in the Dark Room," which appeared in RADIO NEWS, from December, 1925, to May, 1926), is that it responds to the changes in intensities of the current and causes fluctuations in the intensity of the emitted light; just as the diaphragm of a loud speaker produces pulsations in the air in response to alternating-current impulses. It is said that this lamp will go on and off in a millionth of a second; so that in its



D. McFarlan Moore (left) and E. F. W. Alexanderson discussing the neon lamp used in the television receiver

use there is none of the "time lag," which is the greatest problem those working in television have had to meet.

The plate of the Moore tube, on which the image is built up, is about 11/2 inches long and 1 inch wide. The scanning disc, which can be seen in front of the lamp in the rear view of the apparatus (Fig. D), is of the same size as that used in the transmitter, 24 inches in diameter. The 48 holes (which have a diameter of 35 mils each-or about 1/30-inch) trace successive lines on the picture, literally "painting" it in one revolution. The disc is turned by a standard "universal" motor; which is to say that it can be operated from either direct or alternating current. The speed of this motor and, therefore, of the disc, is controlled by a push-button. In order to enlarge the image as much as possible, a magnifying lens is placed between the scanning disc and the observer's eye; thus bringing the image up to 3 inches square.

Fig. A at the left and Fig. B below show the relative positions of the apparatus used in transmitting by radio the image of the girl. In Fig. A the are lamp is at the left and, between the revolving disc and the square frame holding the photoelectric cells, is the small square wooden holder carrying the lens. The amplifier is in the two bases at the right. The groupping of the photoelectric cells is shown in Fig. B below, three being visible and a fourth behind the amplifier bases. Note the microphone at the right and the lines of light and shadow on the girl's face in Fig. B; and the enlargement in Fig. C, at the lower left.







A diagram of the Alexanderson method of operation in the transmission and reception of television. At the upper left are the transmitter for the image and the microphone for the voice, which is broadcast on a different wavelength. At the right are the receivers for television and speech.

SYNCHRONIZATION BY HAND

In most of the television receivers built heretofore, there has been employed some automatic means of synchronizing the receiver with the transmitter; such as the broadcasting of a certain frequency that would make two motors run at exactly the same speed. In Dr. Alexanderson's system no such complicated method of synchronization is employed; the simple and only speed control is a push-button that varies the speed of the universal motor turning the disc.

When the receiver is first started the speed of its motor is far below that of the one at the transmitter, and the resultant image is a straight line of light. As the motor is brought nearer and nearer to synchronous speed, this line of light breaks up into a series of parallel lines, slanting first one way and then the other. Then there appears a distorted image of a face, again breaking up into splotches of light and dark. Finally, when the two motors are running in synchronism, a true image may be seen on the lens. This image constantly shifts from one side to the other, as the speeds of the two motors vary; but this shifting from side to side does not interfere with the reception, as the movement can be made to be very slow.

Here it is that the operator must exercise his skill, in keeping the received image as near the centre of the lens as possible. This is done by "whipping" the motor; *i.e.*, sending an electric impulse to the motor by means of the push-button, and thereby increasing the speed. This is far from being a difficult feat, as it requires no more skill than steering an automobile along a road. Sometimes, when the two motors get slightly out of synchronism, the lower half of the image may be above the upper; so that a man's collar and tie may be seen above his head. This condition can be easily adjusted, however; just as a like condition is remedied by the motion-picture operator when the picture gets out of its "frame."

In the lower part of the cabinet, which (as may be seen) is about the same size as that which houses an ordinary talking machine, is an amplifier with two rectifier tubes. A storage battery and dry-cell "B" batteries for the short-wave unit are on a shelf over this amplifier, which utilizes A.C. house current. By the use of a universal motor and the rest of the equipment as mentioned above, it may be easily seen that the television receiver is one that can be used in almost any home; the only provision being that 110 volts of either A.C. or D.C. be available.

NEW DISCOVERIES IN RADIO

When introducing his apparatus in preparation for the demonstration, Dr. Alexanderson mentioned the fact that he expects television to have within five years the

Fig. E. The new type of short-wave transmitting antenna, called the "checkerboard." The sides of each square are equal to one-half a wavelength. These half-wave antennas are so connected that they oscillate in phase and need not be tuned. s for general use; but, considering the rate at which television engineers are progressing in their work, the time is approaching rapidly when it will be possible to see as well as hear the artists as they appear in the studio. (Continued on page 1156)

same status that voice transmission has

today. Of course, there are still a number

of "bugs" that have to be eliminated before

the apparatus can be put on the market





Fig. A. The apparatus for receiving photographs by radio, installed in the home of Dr. Alfred N. Goldsmith in New York City.

N OT quite two weeks after "television in the home" had been successfully demonstrated in Scheneetady, N. Y., the transmission of photographs by radio and their reception in the home was exhibited by the National Broadcasting Company in New York City. Dr. E. F. W. Alexanderson, consulting engineer of the General Electric Company, is credited also with the development of this simplified system for receiving pictures with apparatus that can be connected in the output of an ordinary receiving set. The pictures were broadcast on WEAF's regular wavelength of 492 meters.

The apparatus demonstrated by Dr. Alexanderson is far from complicated, yet it does not seem quite as simple as the receiver for picking up television broadcasts. The transmitting apparatus was installed in a studio of the National Broadcasting Company, at 55th Street and Fifth Avenne, New York City. A photograph of the mayor of the city, the Hon. James J. Walker, was clamped around the cylinder of the transmitter, as shown in Fig. B.

As the cylinder is turned by a synchronous motor at a constant speed, a photoelectric cell, contained in the box next to the wall, transforms the light energy into electrical energy. The light is reflected to the cell from the surface of the photograph and is broken up by the revolving disc, which has a slotted edge. The output of the photoelectric cell is amplified and is connected to the regular broadcast transmitter, in this case at Bellmore, L. L., by means of land lines. At the WEAF transmitter the picture was put on the air, and received in the home of Dr. Alfred Goldsmith at 82nd St. and West End Ave., New York, (See Fig. A), a distance of approximately twenty-five miles. The results of this transmission, which took about 90 seconds, are shown in Fig. D. The photograph at the left is the original and the other the picture after it was developed in Dr. Goldsmith's home.

THE PHOTOGRAPHIC PICK-UP

In Figs. B and C are shown two views of the pick-up apparatus in the studio. Fig. B shows E. C. Ballentine placing a photograph of D. McFarlan Moore, the inventor of the neon tube used in the receiver, on the cylinder. In Fig. C the synchronous motor in the foreground turns the cylinder at a constant speed, properly reduced by the gears. A source of light is concentrated on a small portion of the photograph, this small area reflecting the light through a lens and the scanning disc to the photoelectric cell. (See Fig. 1.)

The rapidly-revolving dise, at the front end of the case containing the photoelectric cell, has around its circumference a series of indentations or notches. These notches interrupt the light rays at a certain frequency and the photoelectric cell is energized, every so often, by a reflected ray of an intensity which depends upon the depth of shade in the minute area of the photograph them being reflected. These variations of light are translated into electrical impulses by the photoelectric cell and after being amplified are put on the air as a modulation of the carrier wave.



At the left is an unretouched reproduction of an original photograph of Jessica Dragonette, WEAF artist, and at the right the unretouched picture, as it was received in Dr. Goldsmith's home.

1102



Fig. E. Dr. E. F. W. Alexanderson is here shown beside his receiving apparatus. At the rear of the table is the special amplifier and, in the foreground, the receiver with the revolving cylinder exposed.

The ordinary transmitting equipment of the station is used, the only substitution being that of the photographic pick-up for the microphone. Ordinary land-line, or "remote control," is employed as usual. One of the most important things that Dr. Alexanderson has done, besides simplifying the apparatus, is the speeding up of the entire process. The picture shown in Fig. D was transmitted in about one minute and a half, a rate about twenty times as fast as that of other processes.

THE RECEIVING EQUIPMENT

One of the first requirements for receiving pictures from the air is an ordinary

Radio News for April, 1928

broadcast receiver. This is tuned to a station which is transmitting the pictures, in the same manner as though music were to be heard. Instead of the loud speaker the apparatus shown in Figs. E and F is connected to the output terminals of the set.

In Fig. E Dr. Alexanderson is shown beside the receiving apparatus, from which the cover has been removed. The sheet of bromide photographic paper is wrapped around the cylinder, preparatory to receiving a picture. This paper must, of course, be protected from the light of the room, until after its exposure to the light controlled by the incoming radio signal; this protection is afforded by a light-proof cover, which is shown in position in Figs. A and F. Standing open against the wall is the shielded box containing the amplifier, which strengthens the impulses before they are sent to the neon lamp.

This lamp, which operates on the same principle as the one used in the television apparatus, was also developed by D. Mc-Farlan Moore. Instead of the tube's having a plate on which the images are built up, its central electrode is a rod, in which there is a small crater. By the variations in light intensity produced by the neon lamp the light and dark portions of the photograph are faithfully printed on the sheet of photographic paper, on which they are focused by a lens. (See Fig. G.)

The cylinder is driven by a synchronous motor and gears, similar to those at the transmitter. As the cylinder revolves, it also moves along a threaded rod, thus exposing the entire sheet of sensitive paper





The diagram illustrates the process through which a photograph goes when being transmitted through the ether. When "developed" and "fixed" as with an ordinary print.

to the light rays. Before the actual transmission of the photograph takes place, instructions from the transmitting station are broadcast and received through the regular

Fig. F, below. Dr. Alteranderson in his laboratory adjusting the receiver. Fig. G, on the right, shows the Moore neon lamp being placed in its brass container on the rear of the cylinder cabinet. Note the simplicity

of apparatus.

loud speaker at the receiving end. A milliammeter on the box containing the amplifier indicates to the receiving operator when his receiver is properly "framed" and set to the correct intensity strength for tone shades. These adjustments are easily and quickly made. After the entire surface of the paper has been exposed to the rays of

the Moore lamp, the picture is developed and fixed, just as in the case of an ordinary photographic contact print.

STATE OF THE ART

What this phase of broadcasting will do, for the art as a whole, is still a matter for conjecture. Officials of the National Broadcasting Company, when questioned at the time of the demonstration, refused even to guess when regular transmissions of this nature would be inaugurated. They stated, however, that a possibility of its use is the broadcasting of a printed program each day, so that listeners may be able to know when certain features will be on the air. This (Continued on page 1163)

www.americanradiohistorv.com



"Chains and Slavery"

Editor, RADIO NEWS:

When the hat is passed for that big col-lection that Geo. W. Pangborn advocates, don't stop there. Who would want to pay for some of the jumbled-up mess that sometimes comes via independent and network stations? Where would there be any justice in letting listeners decide what stations should be allowed freedom of the air? The big network that he advocates would be a rank injustice unless all were forced to go on one wavelength-which is very plausible. Patents have been issued for that purpose, but where have they gone? I am opposed to any desire to permit a furtherance of the chain; there are too many chain stations now occupying a number of channels with the same program. Nightly there are 25 stations in one chain. Formerly we had a diversity of 25 different programs from those stations-who cares whether it is the highly-paid artists from New York that entertain us? Many times I have thought that undiscovered nincompoops provided better entertainment than those headliners played by the chains. Let freedom of the air go unchallenged. Fin sorry I am not a business man, but I am down among those wage earners where money counts. W. M. BROWN,

Germantown, Ohio.

(Few subjects seem to arouse deeper feelings among radio listeners than the question of chain broadcasting. Many of our readers, especially in the Middle West, condemn them bitterly, and advocate "one program, one channel." Yet, as stated by the Radio Commission, the larger stations show more and more tendency to affiliate themselves with these costly programs, and the head-liner talent they furnish. Many appeals have been made for a poll of listener, pref-erences; and, while it would be impossible to publish all the individual expressions of opinion, RADIO NEWS will be glad to tabulate those for and against the present situation. On the side of the network entertainment, we give the following letter from a reader who is thankful for the excellent entertainment with which he is favored .--Eniron.)

"They Satisfy"

Editor, RADIO NEWS:

I like to read the different opinions as to the operation and control of broadcasting. Some, in my opinion, are good; while I think others have about as good ideas as I would have should I undertake to straighten out the air waves, so to speak.

Your editorials and such articles as I find on pages 869 and 871 of the February issue are very interesting. It is very amusing to listen in on Norman Baker of KTNT when he is giving the N. B. C. and chain programs "Hail Columbia." Personally, I prefer a chain program any time to his and others in his class, such as W. K. Henderson, continually finding something to gripe about. I suppose they want to monopolize the air with "Canned food for sale," "Horse collars," and canned music.

I can truthfully say that 90% of the programs I get are chain programs-that is,

A New Addition to **RADIO NEWS**

SINCE this magazine was estab-lished in 1919, it has become the most important in the radio field in this country, if not in the world. RADIO NEWS has been read, not only by the radio amateur, the set builder and the set owner, but by practically everyone who is interested in radio. More than 30,000 of these readers are radio manufacturers, distributors, jobbers and retailers. So great has been the growth of this circulation, that it has been found necessary to issue a trade section of this magazine, to be known as

Radio News **Dealers** Personal Edition

This section is for the radio trade ONLY, as its entire contents will be of interest to those who are in the radio business, but not to anyone who is deriving his livelihood from other activities. For this reason, it will not be put on sale at the newsstands, but distributed solely through the mail to the radio trade.

The publishers will be only too glad to send you, without charge, a copy of the new DEALERS PERSONAL EDITION, if you are a radio manufacturer, distributor, wholesaler or retailer. You can obtain it only by asking for it-ON YOUR BUSINESS LETTERHEAD-and you are cordially invited to do so. See page 1176 of this issue, and

WRITE FOR YOUR COPY NOW!

A COLORADA DE LA COLORADA DE LA

at night. The reason, of course, is that they are better than others, and I can't see any special benefit that it would be to the small stations that are fighting the chain programs to have all the latter on one wave.

I am quite a DX hound; at least I think I am until someone writes you what they are doing, and then I find I haven't gone so far. However, you will think that, from

what I have to work with, I'm not so bad at that.

Since the first of December, and I only try one or two nights every two weeks, I have logged 142 stations, and WRNY was the 142nd. Have been fishing for you some time, and last night (January 17), at 9:45 Central Time, your station came in good and clear and with good volume. I am using a four-tube regenerative set (R. C. A. with model 10 speaker.) I have also a Radiola 25, but can get better results with the regenerative.

E. T. BATES, Plevna, Alabama.

Not a Man's Job

Editor, RADIO NEWS:

I wonder if the women wouldn't all like (I know I would) to hear more lullabies sung over the radio by women singers instead of men.

Of course, it's fine to hear men sing lullabics, but in real home life it's the women who sing most of them, and the men really seem to be intruding on babies' and women's rights in singing them so much on the air. I'm afraid the lullabies they sing to "Mike" would only arouse the wrath of the baby, and it would probably join lustily in the chorus.

Although it is nice to see a man take an interest in his infant, the chances are that his singing of a lullaby in the home would be a forced transaction, and not very soothing.

So lets hear more lullables sung by women, so that our minds may picture a baby with sweet drooping evelids.

> MRS. H. GERSTEN, 900 Oakdale Avenue, Chicago, Illinois.

Radio for Every Flight

Editor, RADIO NEWS:

With reference to the recent catastrophe, the loss of Mrs. Frances Grayson and companions in her transatlantic plane "Dawn," I would appreciate it if you would publish, in your excellent magazine, a suggestion to future transatlantic fliers, and the general public, regarding the danger of inadequate radio equipment, heretofore used on transatlantic flights, and lack of trained radiomen, which is partly responsible for the complete disappearance of several planes and their occupants.

To give an instance of the value of radio on these flights, I will quote the case of Commander Byrd's successful flight from New York to Paris in "Miss America." Of all the planes, that have flown, or have at-tempted to fly the North Atlantic, I believe his plane was the best equipped in the case of a forced landing.

(Continued on page 1187)

Kathleen Stewart

Staff pianist of W&AF and a favorite of that station's large audience. She was featured in one of the recent-Eveready Hours.



Chuse unique abilile as a soliistler has made her an especialle pepular member of Revy's "Gaug"--Her first name is really Margaret.

J.Andrew White

Dean of vadio sport announcers, who was recently appointed, president of the Columbia Broadcasting System, second largest chain in the country.



Above is the doomed ship "Antinoe" as seen from the rescuing American liner "President Roosevelt," which was summoned by an SOS to stand-by in a raging gale for four days, until the crew of the British wessel could be saved. © Herbert Photos.

D ID you ever tune-in on the radio and find it "dead" for no apparent reason? The tubes burn in all their glory, but all is silent. You rush to the roof to see if the aerial is still there. Then you test the batteries; the voltmeter needle jumps to a high mark. Well, you do about everything imaginable in an effort to bring back the music, but every diagnosis fails. Why is the set "dead"? A radio service man will have to perform an autopsy. It is Sunday, of course; the radio store is closed, so the "doctor" cannot be summoned until morning. The home seems "lost" without its radio!

So you decide to go out to the movies, but you don't enjoy the show because, all the time, there is that tingle in your brain that such a fine radio set as yours cannot have anything wrong with it. It never failed before. No one was tinkering with it. And what makes it more aggravating is the fact that there is absolutely no symptom of anything out of order. You reason it all out in the movie theatre. At 10:30 you return home determined to perform the autopsy on the receiving set yourself. The switch is snapped and—lo and behold—the loud speaker pours forth its music! What a grand and glorious feeling!

But what could have been the trouble? The next morning you read in the paper that "An SOS silenced broadcasting for an half hour last night." The moral is—when the radio set goes "dead," have more confidence in it. Call up a neighbor and see if his loud speaker is silent too, before you become "expert" and begin the hunt for trouble. When a radio set owner begins to look for trouble he will find it, or, more precisely, create it, nine times out of ten. An SOS applies the most exacting test of the confidence you have in your receiver.

THE PROGRAMS GO ON

But what happens in a broadcast studio when the three dots, three dashes and three dots of distress flash in from the sea? It matters not who is facing the microphone, whether it be a staff bedtime-story teller or \$67,000 worth of talent-the SOS has the right of way!

An SOS does not necessarily suspend the activities of all broadcast transmitters. The "key" stations of the radio "chains," as they are on the Atlantic seahoard, may go off the air; but the program is sent out over the wire lines to the inland network, unaffected by the call from the sea. In fact the artists continue to entertain blissfully unaware that an SOS has greatly reduced their audience.

When an SOS silences broadcasters along the Atlantic seaboard at night, it opens up for the DX fan an excellent opportunity to tune for the clusive waves of distant stations. An SOS clears the New York air for broadcast reception, like the arrival of midnight when many of the eastern announcers bid their audience good-night.

It is seldom that such broadcasters as KDKA, Pittsburgh, and others west of the smoky city sign off because of an SOS. But the fifty-two transmitters nestled in the metropolitan area of New York go off the air immediately; because the big transmitter known as WNY at Bush Terminal, in Brooklyn, N. Y., or that of NAH at the Brooklyn Navy Yard instantly endeavors to calm the ether and establish communication with the ship in distress, or with other vessels in the immediate vicinity. A 2-kilowatt "spark" transmitter is used at such times. because it radiates a much broader wave than a vacuum-tube outfit and, therefore, is more likely to be intercepted by a greater number of stations when it broadcasts "QRT (stop transmitting), ship in distress."

THE RIGHT OF WAY

The Federal Radio Commission is authorized to designate radio stations the communications of which are liable to interfere with the transmission or reception of distress signals from ships. Such stations are required to keep a licensed radio operator listening in on the wavelengths designated for distress calls, during the entire period while the broadcast transmitter is in operation.

Every radio station on shipboard must be equipped to transmit distress calls on the frequency or wavelength specified by the licensing authority, with apparatus capable of transmitting and receiving messages over a distance of at least 100 miles by day or night. When sending signals of distress, the transmitting set may be adjusted in such a manner as to produce "a maximum of radiation irrespective of the amount of interference which may be caused."

The radio law stipulates that, "All radio stations, including government stations and stations on hoard foreign vessels when within the territorial waters of the United States, shall give absolute priority to radio communications or signals relating to ships in distress; shall cease all sending on frequencies or wavelengths which will interfere with hearing a radio communication or signal of distress, and, except when engaged in answering or aiding the ship in distress, shall refrain from sending any radio communications or signals until there is assurance that no interference will be caused with the radio communications or signals relating thereto, and shall assist the vessel in distress, so far as possible, by complying with its instructions.'

So while you are sitting comfortably at home enjoying the Goldman band, the Edison String Ensemble or the New York Philharmonic Orchestra, just picture the licensed radio operator on his tiresome watch, wearing the headphones connected to a set tuned to the 600-meter wave, not so far above the broadcast hand. What does this man do if he hears the three dots, three dashes and three more dots?

When a radio watchman in the New York area hears a plea for assistance, he first verifies it by telephone with the District Communications Superintendent of the Navy Department in the Whitehall Building, which is in constant touch with the Brooklyn Navy Yard station, NAH.

THE CODE SIGNALS

Many times, before the watchman at the broadcast transmitter has had time to verify the call with the District Communications office, NAH flashes "QST DE NAH QRT 808"-meaning, in the parlance of dots and dashes, "General Call from NAH, clear the air because of an SOS!" This is an order to all stations in the district to sign-off, whether they be broadcasters, ship or shore transmitters. When this call is heard-or before that time, in the case of an SOS which has been intercepted by the watchman and verified by the District Communications office-the operator at the broadcast transmitter immediately tlps a little switch which cuts the station's program from the air. Then speaking into a microphone, he announces that the station is signing off because of an SOS. The transmitter is silent, Init the tubes are kept burning because, generally within a short time, the air will be clear again.

In the meantime, code transmitters from Cape Race to Key West are endeavoring to communicate with the disabled vessel, using for this purpose every fraction of the power they possess. The Navy Yard station continues to send out its warning, in case a ship unaware of the SOS begins to transmit.

Broadcast listeners who are able to read the Continental Morse code and the quick flashes of radio abbreviations can often follow the rescue arrangements; for the

broadly-tuned signals will penetrate into the upper reaches of the broadcast band. Usually, one shore station will direct the rescue, and within a short time this station will have communicated with vessels close to the ship in need of assistance. In comnunicating with the coast station, ships first ascertain the position of the disabled vessel and then report their distance from the ship in hours. One or two vessels will be assigned to speed to the rescue and, once they have changed their courses, the "All clear" signal, which is two dots-space-dot, is sent out by the land station and broadcasting is resured.

EARLY DAYS OF "WIRELESS"

Do you know the evolution of the cryptic "SOS" that silences your radio? It really begins with the first marine accident to be reported by "wireless," on April 28, 1899 (long before the days of broadcasting), when the steamer R, F. Mathews collided with the East Goodwin Sands Lightship, off the coast of England. The call for help was picked up by a shore station twelve miles away and a rescue party was dispatched to the scene of the wreck, reaching it in time to save all lives. This proved the value of radio at sea, and revealed the necessity of an international distress signal which could be understood easily by the operators of all nations, despite differences in language.

The call "SOS" passed through a process of evolution. The first suggestion for an international distress call for ships was made by the Italian delegates at a preliminary meeting to consider radio telegraphy, held at Berlin in 1903. The Italians suggested the adoption of "SSSDDD." All agreed that such a call was needed but the choice was left to a special conference, Shortly after the Marconi Company instituted "CQD."

Erroneously, "CQD" was translated by the public to mean "Come Quick, Danger." It was one of the signals radio adopted from the land telegraph which, because of its higher state of development, was governed by rules formulated and established by an international convention. Among the telegraph rules was the authorization of a group of double-letter symbols used by operators to abbreviate and speed-up traffic.

"Q," being one of the least-used letters in the English alphabet, is distinctive and can be recognized easily. The call "Ct?" on a railroad or commercial telegraph line means that the operator sending it desires all other operators along the wire to listen to his message. When radio adopted "CQ," it took the meaning "Stop sending and listen." Alone, it is important but no cause for immediate alarm. But, in the early days of radio, if the operator followed the "CQ" with the letter "D"—the signal of danger and distress—it became a message of general alarm.

So harmless is the "CQ," without the "D, that even today it is a custom among amateurs and commercial operators to send "CQ" in dots and dashes, as a signal that the station is on the air and free to handle traffic.

"SOS" FROM THE "TITANIC"

Several minor emergencies at sea revealed that "CQ" did not sufficiently express the urgency required for distress purposes. This prompted the Marconi Company to issue a General Order "Circular No. 57" on (Continued on page 1160)

Below (lower left), the switch which is turned at station W EAF when a SOS is received by the operator who keeps constant watch. This disconnects the remotecontrol line from the trensmitter and broadcenting stors, so far as this station is concerned; though inland stations may continue. ^(C) Herbert Photos.

Ū.



In the center, above, is the latest Marconi Automatic alarm upparatus which takes the place of an operator in seatching for SOS signals. It selects the distress signal from any other messages and sounds a bell. Wide World.

Below (at the lower right), a view of the operator's room on the SS. "Southern Crass," showing receiver and telegraphic transmitting key. © Herbert Photos.



"-I've got you logged, and my dials are set. Your program's nice and loud on my super-het; and Long-Wave Papa, you ain't a-gonna fade on me!"

1110

T'S one of those August afternoons just made for white duck pants, a stiff breeze and a sunburned neck, and I'm out on the Sound in our new speedboat, Bow Stealer, practicing the lyrics and learning the libretto of My Radio Girl-the oncoming season's musical smash, if you believe the producers. Suddenly the telephone rings!

No, it's not the heat. Besides studying my part I've been helping The Master in some minor experiments, and we've a flock of apparatus aboard, including a small twenty-meter radiophone, with an auxiliary transmitter to ring a bell, so's I won't have to keep the cans on in the sun. I grabs the instrument and answers Jerry.

"Go out beyond Buoy 3," he directs, "and turn knob B-44 on Panel 2 until the red indicator on Dial 6 registers 18.5."

I haven't the least idea what it's all about, but being wedded I can obey orders; I does as asked and shortly receives The Master's thanks, and the request to come ashore and help somewhere.

Formally, I'm Joe Hammerstein, dancing comedian, and reside with my exit-light, Doris, and four radio sets, at Brightmere-on-the-Deep, Long Island. We're due to begin rehearsals with a musical comedy next week; and, as a novelty, they've given the opera a plot, so we've lines to remember.

Jerry Lawson, alias The Master, is our local gift to science; he's twenty-five, tall, slim, dark-haired, a power in Wall Street and an authority on radio. Once, in the fall of '09, he was known to make an original wise-crack, wholly by accident; since then he's basked in its memory and turned his mind to higher things like aerials.

I runs the boat up to the dock and Jerry helps me take the stuff back up to his joint. We putters around up there for a coupla spasms, until the evening papers arrive. The Master always allots a certain daily period for getting the low inside on how the other half lives, and he flops into his old morris chair with a lapful of sheets. I'd not have given any thought of it, only I happens to get a slant at one of the papers. It's a publication devoted exclu-sively to the art of losing currency on the ponies:

Jerry plays a scientific hand of bridgehe would-and can, when in the mood, he astute at poker; also, on certain memorable occasions, the dice have displayed remarkable gathering proclivities while under his guidance. But he's not essentially a gambler, unless it be for a principle; that he's taken up horse racing is a new one on me, and I've known him four years.

"Since when?" I demands, seizing the sheet. "And at your age, too! I thought you knew better!"

The Master smiles faintly. "Only morbid curiosity, Joe," he answers. "Curiosity plus a mild determination."

"To what—beat the game?" I inquires. "Don't tell me you've worked out a system !"

Jerry almost laughs out loud. "I fear you've misconstrued my meaning," he replies. "No, Joe, I'm not gambling. But the career of one horse is interesting me strangely."

"Other people have been affected the same way," I grins. "Only they had to walk home. What's the racket this time?"

I hands him the paper, and he hunts through it until he finds the results on a certain race, away back in the sticks. His face sorta tightens, and then relaxes, with an expression of puzzled annoyance crossing his handsome map.



"The box in the burn contained a radio receiver tuned to one wavelength and operating the main switch to the primary, which gave Fuse Plug the radio whip."

"Again !" he mutters.

"No !" I exclaims. "Impossible !"

"But she did-oh, you're fooling!" declares Jerry, coming out of his daze. ".loe, did you ever play the horses, as they say?"

I grins. "Prior to annexing Doris I blew my split-week savings on the Saratega Ships, but none of them ever made port. In recent years I've been kept in sight too much."

"What I mean is, do you know the cus-tomary methods of betting, and have you any acquaintances in the game?"

"More than I know what to do with," I grins, making a wry face. "I wouldn't wish any of those touts on you, though. Why?"

The Master sits up, and it's plain the old dome is working without static. "I never would have learned about this, except for a casual friend who wrote me from upstate."

"Yes?"

"The particular horse involved runs under the cryptic name of Fuse Plug; it is an outlaw, of course, playing only the minor events at small county fairs." "Fuse Plug!" I snorts. "What's his ca-

pacity?"

"From Harry's description, the animal seems to be an old mare and, while originally of racing stock, has been in commercial service on a transfer line until this spring."

I nods. "So far so good."

"But, no," declares The Master. "This horse, Fuse Plug, while only entered in free-for-all meets, invariably wins first prize by the simple trick of lagging until the final stretch, and then rushing ahead in a final blaze of glory."

"Common enough," I disparages. "The nag can't stand up under a continuous grind. They save the steam for the end."

"I realize that," mumbles Jerry, again perusing the paper. "Yes, here it is-the horse is nine years old, but has never been beaten since the opening of the season." "Framed," I states, laconic. "Those gyp

horses run under cheap syndicates, and it's all pre-arranged."

The Master shakes his head. "No, Joe, this case is different. Harry saw her race five times, and in each instance Fuse Plug performed as I just told you."

"Doped, perhaps."

"A drug could hardly be regulated to take effect at a given moment," argues Jerry, "and even so, it would be noticed. While the supervision at these small races is not thorough, it would nevertheless he difficult to use a stimulant of that nature without eventually being apprehended."

I scratches my dome. "They used to use a battery and a spark coil, to shock the horse," I offers.

Jerry arises and paces the floor. "That seems to be eliminated, too. There have heen other inquiries concerning Fuse Plug. Indeed, it is only through her peculiar

method of running that the racing sheets even list her exploits. Harry tells me that authorities, including the S. P. C. A., have gone over the animal, but have been unable to find any traces of either drugs or other artificial means. There is something inordinately clever about it all. I should like to investigate."

"Hop to it," I says. "Need any help?"

"When do your rehearsals start?" This was a Monday. "A week from to-morrow," I replies. "Can we catch Fuse Plug somewheres near here by then?"

Together we goes over the paper and finally locates a dinky county-fair outfit that's billing Fuse Plug to run for three days.

"Tuesday, Wednesday and Thursday," reads Jerry. "Why, that's tomorrow. I've been through the town-it's only seventy miles upstate. Will you come?" "Delighted," I answers. "Have you any

idea what it's all about?"

The Master nods vaguely. "I've several theories, but I'll have to do some experimenting first. We'll drive up in my lab truck."

This latter is a small, inconspicuous car with an enclosed body, like a delivery wagon. The Master uses it on tour, and at times when he don't want to be bothered by spectators. The bus is built low, and has a straight-eight motor-there have been times when speed was very, very necessary.

Early the next morning we drives up to

the fair. Our plans have been made; in order not to create suspicion, I leaves The Master just outside the town limits, and walks in as a hick visitor. Unless he needs me, in which case he'll signal, I'm to meet him after the races at this spot.

According to our arrangements, I'm to watch Fuse Plug run and, if she wins, go to the management and claim the horse is crooked. This is to give me a chance to inspect the animal at close range, also the jockey and saddle.

The Master gets an infield permit-he's supposed to be a news-reel photographer, and fusses with a camera for atmosphereand drives up to the turn just above the home stretch. Should we pass each other, we're to be strangers. All's lovely.

Our horse is entered in the third, with a field of nine; one look at her is the cue for a big howl.

Fuse Plug was a racing filly once, but she's sorta forgot herself and grown heavy. At that, though, the heast has pep, and is in good trim for her age.

I mixes with the gang until the track events come up. Then I privately places a wager on Fuse Plug-just a hunch, and Doris'll never be the wiser-and edges through to the rail.

At the start Fuse Plug brings up the rear, but she holds her own, and in spite of her apparent clumsiness it's plain she once knew how to run. Until they rounds the curve where our truck is parked Fuse Plug remains last; then the mare suddenly whoops into it, passes the others like a Parisian taxicab, and crosses the line a winner by two lengths!

Something spurred that horse on, and it wasn't ambition!

Then I quietly collects, so as not to run too much risk of being identified later. Somebody might recognize me as having won; but only the payoff guy was there, and he was still busy when I put in my kick.

I finally gets a chance to examine the nag, with a couple other bozos that says they lost. Nothing wrong with the horse, nor with the jockey. The saddle is regulation.

"I guess she's square," I mumbles to the owner. "Sorry."

I walks to our meeting place and pretty soon The Master rolls along. He hasn't much to say, but I can see he's learned something, so I stays shut and lets his brain function.

The next day, Wednesday, Fuse Plug is due for a double-header, morning and afternoon. We're there again, early, and apparently separately.

Just before we reaches my stop, Jerry confides a few facts.

"Across the track from where I parked, on the outside, is an old barn, abandoned as a part of the fair grounds except for storage. I shall have to explore that immediately. In the meantime, you keep your eyes open, and be ready for anything."

"O.K.," I replies, saluting.

The morning race goes off just like the one the afternoon before. Fuse Plug does (Continued on page 1164)



He shows the fat Mayor the saddle. The official grunts. "Battery?" he demands. The Master shakes his head. "No, strange as it may seem, Fuse Plug was controlled by radio." But strange to say nobody slipe Jerry the bird.



PAPA WAS NO JACK BARRYMORE!

Mother (wife of famous radio announcer): "N o w run along to bed, kiddies; and, when you say your prayers, don't forget to do as daddy said, and pray that television may neven come." — Wm. G

Mortimer.

THE CONTROL THAT FAILED

FIRST HOUSEMAID: "Is Professor Wise absent-minded?"

SECOND DITTO: "Is he? Last night, when the baby cried, he twisted its nose to eliminate the static."



THE BOOKSHELF UP-TO-DATE LYDIA: "I've often thought how romantic it would be to be cast away on a desert island." NYDIA: "What ten-tube set would you take with you?"

FOSITIVELY THE LATEST

VAN: "He's the last word in radio announcers." PHAN: "Yes, he's the guy who signs off

the station every night!" -Wm. G. Mortimer.

SPEECHES GO ON FOREVER

FIRST WEA



FIRST WEARIED VOTER: "What did you think of Senator McBuncombe's speech over WAAK last night?"

SECOND W. V.: "I think they ought to have given him a shorter ravelength." TOO TECHNICAL!

AST C

MABEL: "I just love to sit with Jim in a darkened room with the radio playing soft music." MARJORIE: "Oh,

I might with some boys—but Freddy will keep both hands busy on the dials."

NOT A BARK IN A BARRELFUL

Hogues: "Say old man, how do you man-

age to get such perfect radio reception?" Joques: "I blow New Silver cigarette smoke into my loud speaker, to ease its throat."

THIS page is devoted to humor of purely radio interest; and our readers are invited to contribute pointed and snappy jokes-no long-winded compositions-of an original nature. For each one of this nature accepted and printed, \$1.00 will be paid. Each must deal with radio in some of its phases. Actual humorous occurrences, preferably in broadcasting, will be preferred. Address Broadcastatics, care RADIO NEWS, 230 Fifth Avenue, New York City.

HOW HE REMEMBERED

CHANCE ACQUAINTANCE: "So you live in Wolfville, eh? Didn't you have a terrible storm down there last summer?"

RADIO FAN: "We sure did. That was the night my aerial blew down.""

NOR THE AUDIENCE (LUCKILY)

FIRST MICRO-PHONE: "A good mike is a broadcaster's best friend."

SECOND MICRO-PHONE: "Y es, it will never tell him when he has halitosis."



NO DOUBT ABOUT IT!

LOUD SPEAKER (in its best static manner): "Bang! Crash! Help! Police! Murder!! BANG!!!"

RADIO FAN (whose location is more pacific): "Hooray! I've got Chicago!!"



-Mrs. Bill Howard.

NOT THAT KIND

JOHNNIE: "I got Greece on the radio last night!"

MOTHER: "Well, you wipe it off before your father sees it ?"

-Leslie Carpenter.

ALWAYS FOLLOW INSTRUCTIONS

SHARPE (radio expert: "What on earth are you grinding up 'that copper wire for?"

DULLE (radio novice): "Well, I'm putting in my radio set and RADIO NEWS SAYS a good ground wire



is the most important thing about the installation." —Paul Harvey.

SOLVING THE MYSTERY

Doctor: "You're color - blind, m y good man!" Jones: "Ah! I het that's why I

het that's why I always get the Blue Chain program when I try to tune in the Red!" — Wm. G.Mortimer.



RADIO RHYMES





I CRAVE TO HEAR ONE SINGLE SONG AND NOT A MOTLEY SCRAMBLED THRONG!"



HERE TO SHOW A REAL SELECTIVE RADIO!



YOU TUNE ONE VOICE FROM A DUET --AND HEAR A SOLO ON THIS SET! "

Dr. de Forest Talks on Radio



Forecasts of the Near and the Distant Futures of Broadcasting, Television, Radio Apparatus and Radio Entertainment



N the "Home Science University" series of Station WRNY, broadcast on January 11, 1928, Dr. Lee de Forest was interrogated by the Editor of RADIO NEWS on a number of radio subjects. The entire interview is published, verbatim.

MR. GERNBRACK:—The questions which I am going to ask you tonight. Doctor de Forest, are put to you in such a way as perhaps the man in the street would put them to you, if he had the opportunity or, may I say, the good fortune to speak to you. I shall try and make the questions as simple as possible; because you appreciate that, perhaps, not all of our listeners are technicalities. The first question is:

"What do you consider the greatest step in radio progress for the year 1927?"

Da. ng Forest:---Mr. Gernsback, before I answer that and the following questions, I want to say to the radio audience, that my remarks tonight will not be too technical. From the tenor of the questions which are being proposed to me, 1 am talking on strictly radio technical matters; but I trust that I will use language that those really interested in radio will understand. Now in answer to your first question, I consider that the most important radio developments in 1927 come under the heads of the rapid elimination of "A" and "B" batterics for radio receiving sets, and the progress in the development of short-wavelength broadcasting. Great progress has also been made during the past year in the simplification and standardization of funing devices; so much so that, for all local work. the single-dial control, even though this may operate three or four condensers, gives tine selectivity and adequate volume. The DX fan still wants individual-stage control with vernier condensers; but the great mass of radio listeners, who now overwhelmingly preponderate in and around our larger cities, are rapidly becoming educated to the fact that the very hest they can obtain of radio anywhere comes from ocarby stations. Therefore the extreme accuracy in tuning each individual R.F. amplification stage, in order to pick up with maximum volume long-distance stations, no longer appeals as it did.

MR. GERNSBACK:— Thank you, Doctor. Another question:

What are your views on the present broadcast art?

DR. DE FORESTE--It is a source of immeasurable gratification to me to observe the very marked increase in the quality of musical programs now being broadcast, as compared with that of two years, or even one year ago. This is particularly noticeable on Sundays; a lover of good music may then listen to his radio for hours at a time and hear nothing but music of the highest order. Today's radio is abundantly making good my prediction of many years ago, that radio would be instrumental, as no other institution of man's creation possibly could be instrumental, in a rapid develop-



Dr. Lee de Forest

ment of the public's taste for good music. Countless thousands are now educated to hunt for and genuinely appreciate a type of music of which five years ago they were entirely ignorant, or under no conceivable condition would trouble themselves to hear. This cultural influence of radio is cumulative, accelerative. I have no doubt that, five years from now, most of the cheap jazz and mediocre music which the public now enjoys will be as distasteful in the United States as it has always been among the more cultured and music-loving peoples of Europe.

MR. GERNSBACK:—That probably answers the next question, which 1 shall put to you anyhow.

In what directions do you think present broadcasting should or can go? What are your views?

 $D_{R, DE}$ FOREST:—That calls for a somewhat more technical answer. As to the technical developments awaiting us in 1928,

The accompanying lecture was recently given over Station WRNY, New York, during its regular Wednesday evening feature, "The Home Science University."

During this hour, well-known personages in the arts and sciences lecture at WRNY and Mr. Hugo Gernsback, Editor of this publication, conducts an open forum.

1 am suce that great strides will be made in the matter of improved quality of reproduction. The better type of console radio with built-in loud speakers, particularly the higher-priced ones with phonograph combined, will be more and more in demand. And as prosperity becomes more widely distributed, and particularly as the educative influence of radio, above men-tioned, works its indirect benefits, more and more will discard their cheap "noiseboxes" in favor of more expensive and properly-designed amplifiers and loudspeakers. Much progress will be made in 1928 in the field of broadcasting with short wavelengths below 50 meters; but it will take more than one year to iron out successfully the intricate difficulties involved in building reliable receivers for operating on such short waves. It will be a long and slow process of infiltration that short-wave broadcasting must undergo before it can invade, to any large degree, the popularity which the present range of broadcasting channels now enjoys.

MR. GERNSBACK:—Dr. de Forest, you probably read a few days ago, that Harry Lander said he would never broadcast. He said the present reception is not at all what it should be. I don't know whether you read that in the newspapers. That brings the question:

"Wherein does the present-day radio set fail, if it does fail?"

DR. DE FORST:--I had not read that article; but it exactly fits with a statement made to me at luncheon today with a friend who recently met ten of the Players at the Players Chib. He said he talked with them about radio, and he found that only one of the ten owned a radio set; five of the ten had owned radio sets but, with their ears so well trained to fine enunciation and fine music, they discarded the sets; and the other four were not interested in radio.

Many present-day radio-sets are deficient in the quality of their audio amplifiers and particularly in the loud speakers employed. The radio-frequency and detector systems have attained a high state of refinement, but too little attention has been paid up to date to the audio-frequency-amplifier end of the receiver. Too little iron is used in most of the transformers; too few amplifiers employ push-pull circuits; and there is too little inclination to employ expensive power tubes in the last stages; with the result that we frequently have distortion due to saturation in the transformers, or overloaded tubes somewhere along the line.

MR. GERNSHACK:--That partly answers my next question, which I will put to you if you have something more to say about it, and that is:

What is lacking to make present day sets more perfect?

DR. DI: FOREST:--I think the greatest need in that direction is better audio-frequency (Continued on page 1177)

CTURINUM STATES OF S





A problem which recently has been solved is that of com-municating from any point with an airplane by means of the portable transmitter shown in the above illustration. It has a power rating of 50 watts and can be used for either telegraphy or telephony. © Underwood & Underwood.



One of the main troubles ex-perienced when communicating between an airplane and the ground, or between two airplanes in flight, is that an operator in the airplane has trouble in hear-ing the radio signals in the phones, because of the motor noises. In the illustration above is shown a new helmet, designed for aviators, in which the phones are an integral part of the head covering. The microphone is especially constructed and is strapped to the operator's chest. O Underwood & Underwood.



R. dittas

1 A State State

In the illustration above is one of the two 210-meter masts sup-porting the transmitting aerial at the Zeesen broadcast station; it is designed for a 100-ton strain. The wavelength of the station, which supplants that at Koenig-which supplants that at Koenig-which supplants that at the station, the style of architecture is the station building. © P. & A. Photo.

In the illustration at the left is the novel horizontal control board of the Zeesen station; all the operations are controlled from this central point. © Underwood & Underwood.



How the headphones are hung over the outlet panel which contains the three jacks supplying the three optional radio programs.



Above, the radio instellation in the Hotel Georg-Washington, Jacksonville, Florida. In every guest room and throughout the lobbies, a ning rooms, etc., are loud speakers which bring to the mests the best radio programs of the day. In case special announcements or emergency requests have to re made, the management can get in touch with every guest within a very fees seconds. The radio equipment shown above can be used for either reception of programs or general announcing, by the throwing of two or three switches At the right, cue of the booms, showing the loudspeaker equipment which is provided for the quests whe wish entertainment rought to them.



Three antenas are available for these receivers in the Robert Morriz Hotel; the fourth set is for emergency use. Special amplitures are used, so that every guest has clear reception available at good headphone volume.



SE REPORTED IL REPORTED REPORTED FOR THE REPORTED AND A CONTRACT AND A



The Radio School Teacher is Here



Further Opportunities for the Custom Radio Builder, in the Equipping of Schools With Receivers, are Explained

By Armstrong Perry

A NATIONAL system is being developed for broadcasting short, superlative radio programs intended especially for schools. Already, in Connecticut, a course in music appreciation has been conducted for a year and courses in trees, geography, children's books, birds, animals, insects and flowers are now being broadcast. They are received in schools throughout this and other states.

A group of philanthropists is at work on a plan to offer free of charge to every school in the United States, the services of preeminent teachers to assist in the work of the faithful resident teachers. For good measure, it plans to add music and talks by outstanding national leaders, men and women who are making history. Leading educators are cooperating in the movement.

With such prospects in view, and with radio receivers available everywhere, it is no wonder that schools are hurrying to install equipment. One located in Brooklyn is considering estimates for installing a master receiver with eighty loud speakers in the classrooms.

CREATING A MARKET

The experience in Connecticut shows how radio programs help the schools. The ConW E have often pointed out that a good deal of money can be made by custom radio builders, through equipping of schools with special radio sets for educational purposes. As Mr. Perry shows in this article, there is a big market for radio sets which up to this time, has not been exploited; and great possibilities are in it.

Though it is, of course, possible (and in many cases desirable) for schools to purchase factory-built sets, it is true also that, even when such sets are used, power amplification becomes necessary and, for best results, a number of loud speakers should be stationed at different points in the school. Here is where the custom radio builder can do a worthwhile job.

In larger schools, it will be desirable to build a special set for local requirements; particularly where one such set supplies different classrooms, each of which has a loud speaker. It would seem that here is one of the best markets for the custom radio builder at the present time.—EDITOR. necticut State Board of Education conducts the courses; Station WTIC gives its services. The Connecticut State College of Agriculture was hooked up with WTIC in broadcasting the lessons, as long as money was available to pay for the telephone line that connected it with the studio.

Announcements of the course are broadcast at the beginning of the year, and are sent in printed form to the officials and teachers of the schools throughout the state. There were only half a dozen radio receivers in the schools when the first announcement was made; but, before many lessons were broadcast, it was found that 60 schools had purchased receivers, 35 were renting them and 162 were sending pupils to private homes, where they were invited to listen in.

One enterprising radio dealer installed a receiver in the school in his town, each day when there was a radio lesson, and connected it with lond speakers in seven class rooms. He says that it has proved good advertising. Forty-five superintendents of schools report that pupils in 75 out of the 169 towns under their supervision have received the instruction. The officials at WTIC report that 275,000 pupils in five states heard one lesson in which the Travelers Symphonic Ensemble provided the music. Has any



other new school method ever made such a gain in its first year?

PUPILS ARE ENTIFUSIASTIC

Educators are inclined to conservatism and many of them prefer to follow wellbeaten paths, but pupils are cager for new experiences and adventures. Wherever a progressive teacher grasped the possibilities of the course and placed it before a class with reasonable preparation and enthusiasm, it was appreciated. In Poinfret, Connecticut, for example, they could hardly wait for the next program; Pomfret has always been progressive and adventurous, ever since the day when Israel Putnam pulled the wolf out of the cave in that historic town.

The pupils of one school asked if they might make booklets about the radio music course; permission was given and it became an absorbing game. They yied with each other to produce the most attractive designs for the covers; they wrote accounts of the music that they heard and told about the lives of the composers; they illustrated the pages with original drawings or with pictures clipped from newspapers and magazines. They prepared and bound the pages with the greatest care. One little girl re-wrote one of her pages four times before it came up to her ideal.

MUSIC COURSE INCREASED INTEREST

The teachers were surprised by unexpected developments; they themselves began to appreciate music as they never had done before. Pupils renewed their interest in class-room work, because the music and the facts concerning it were closely related to other studies. They learned to tell the stories of MacDowell's "Of a Tailor and a Bear," Nevin's "The Rosary," and other songs. That led to development in oral composition. The note books made written composition more interesting. Penmanship improved as each pupil tried to make his book the best. They learned to spell the common words used in music; those which they misspelled were likely to appear in the next day's spelling lesson!

The social studies, history, geography and civies, took on new meaning; because the homes of many of the composers were in places found on the maps and their lives were associated with the history of the United States and many other countries, "The Ballet of the Flowers," "The Pussy Willow Song," "Raindrops," "The Trout," and "The Mouse Trap" connected up with nature study. The course led the pupils to more serious reading, for they wanted to know more about the men who had expressed their thoughts and feelings so beautifully in music. Drawing improved when the note book covers and illustrations were under way. Even arithmetic became more interesting, because the nusic was written in three-four, four-four and other times and the why of it had to be figured out.

The course increased the use of the phonograph: for, after hearing a musical composition rendered and explained by the radio teacher, it was a delight to hear it again and again on the phonograph in order to catch every phrase and expression,

The most popular lessons were those in which pupils took part. Glee clubs, bands and orchestras from city high schools were heard sometimes in the course. More of them were heard after that through the radio sets at home. It was a great incentive for pupils to learn to play and sing and try to improve, so that they might some day become radio artists instead of mere listeners.

Classical music, which often bores the children of this age of jazz, came to be understood, appreciated, longed for. The course developed a demand for lectures, but that came from teachers-the pupils were almost unanimous in requesting "more pupile, less talk!" Some, however, said: "We like programs that are like regular lessons."

The effect of the course was not confined to the school room. Pupils went home to tell their parents about the new teacher who talked to them from way over in Hartford, and found that mother had been listening

in also. A new bond was created between the school and the home.

USE OF RADIO BY EDUCATORS INCREASING

The selection of the course in music appreciation, as the first to be offered to the Connecticut schools, was made after careful study. England has a broad curriculum of formal courses of instruction broadcast on a national basis. Atlanta, Oakland and Denver have provided regular courses by radio for several years. Music has been found the best subject to start with.

The Connecticut State Board of Education provided its schools with printed syllabi in advance, which gave the educators an opportunity to plan their work. Printed programs were distributed, one for each room in each school, on requisition of the superintendents. That gave each lesson the enjoyable aspect of a concert.

Dr. N. Searle Light, director of the division of rural education, has been placed in charge of the courses, because the need for them seems even greater in the country than in the city. He reports that the first year's experience justifies the continuance and development of instruction by radio. Martin B. Robertson, state supervising agent, says that the course developed appreciation of the best in music, gave an oppor-tunity for the growth of an attitude of careful listening, and enriched material for

(Continued on page 1165)



Custom radio builders should carefully con-sider the boards of education as a poten-tial radio market.



Simple Device Provides "A" Power For Farmers

WHEN designing accessories for radio receivers, a large percentage of the manufacturers in this country have considered only the demands of the broadcast listeners who reside in the cities and towns, and have ignored almost entirely the needs of the farmers, who wish also to enjoy radio programs. In more than nine cases out of ten the socket-power units, chargers, automatic relays, etc., designed for the benefit of the city user are of no value to the farmer whose house is not supplied with electricity from the city power stations.

In a large number of modern farm and rural houses electric power is obtained from a 32-volt farm-lighting plant; this consists of a bank of storage batteries, which are



Complete schematic diagram of "A" power unit which operates from a 32-will D.C. source. R, resistance bank; FR, wiltage-regulator; CB, circuit-breaker; FM, wiltmeter.

charged each day with current from a small electric generator driven by a gasoline motor. Such an outfit provides an ideal source of filament power for a radio receiver, and recently a manufacturer has placed on the market an "A" current-supply unit which, when connected to a 32-volt D.C. supply, reduces the voltage to the 6 required for operating the average set. The unit will be found pictured on this page.

The schematic wiring diagram which accompanies this article shows that the "A" current-supply unit is of very simple design. Essentially it consists of a bank of resistance units, a multi-point switch, a voltmeter and a circuit-breaker. The resistors (R) are connected in series and reduce to a suitable amount the voltage ap-



General view of farm "A" power unit housed in a compact metal case. The knob, VR, adjusts the filament voltage; the voltmeter,, VM, shows the potential at the output binding posts (A); and the knob B may be used to prevent the shunt circuit-breaker from operating.

plied to the filament. The switch (VR) connects various portions of the resistance bank into the circuit and in this way adjusts the output voltage to the required value. The voltmeter (VM) registers accurately the exact voltage at all times; and the circuit-breaker (CB) prevents the possibility of applying accidentally an excessively high voltage to the tubes, as it is so adjusted that it opens the circuit when the potential difference is over $6\frac{1}{2}$ volts between the output terminals.

The entire device is housed in a compact metal case which measures $5 \times 73_4 \times 91_4$ inches. The voltage-control knob (VR) and the voltmeter (VM) are mounted on the top. The plug (P) is connected into the 32-volt supply circuit, and the binding posts (A) provide the 6-volt supply to the receiver. B is an adjustment knob which may be used to prevent the circuit-breaker from operating. The view with the cover removed shows the location of parts inside the unit; the series resistors are located under the sub-base.



THE "A" power unit illustrated on this page was designed especially for use in the battery compartment of a popular superheterodyne receiver, which uses tubes of the 199 type; but it may be employed to advantage for electrifying any receiver using 4-volt dry-cell-type tubes.

A large majority of the receivers using 199-type tubes obtain their filament power from three No. 6 dry-cell batteries connected in series; and these batteries are usually located in the receiver cabinet. Therefore, an "A" power unit for sets of this type should be small in size, in order that it may fit in the space formerly occupied by the batteries. The "A" power unit under discussion answers this requirement. It is housed in a metal case 4 by 9 inches by 6 inches high and weighs only $11t_2$ pounds. It will provide pure direct current of 0.6 amperes at 4 volts, which is ample for the operation of any receiver using 10 tubes or fewer.

There are on the power unit no knobs or dials which require adjustment. Two



This compact unit may be used to provide filament power for sets using up to ten 199-type receiving tubes. It supplies 0.6 amperes at 4 volts D.C.

binding posts are provided, for connecting wires to the battery posts of the set, and there is a filler hole where distilled water

CB VR B

The arrangement of apparatus inside the "A" supply unit is clearly shown at the left. The resistance bank is located under the sub-base and the heavy wires run from the contact points of the voltage-regulator to various points in the resistance unit.

is added at rare intervals; in addition, there is the wire and plug which connects with the lamp socket. To install the unit it is necessary only to connect two wires to the posts and insert the plug in the socket. After it has been installed it is necessary to add water to the filler hole on an average of only once every six months. It should also be remembered that the unit is turned on and off at the lamp socket and not by the filament switch on the panel of the receiving set.

Electrically, the unit consists of a stepdown transformer, a rectifier of the electrolytic type, and a filter system consisting of a heavy-duty choke coil and a highcapacity electrolytic condenser bank. Power units of this type, which were designed to supply filament current to receivers using 6-volt tubes, have been described previously in this department. Those who are interested in a more technical explanation of the action of the electrolytic rectifier and condenser bank should refer to articles which were published in the December 1927 and February 1928 issues of RADIO NEWS. Although the devices described in these articles are different in external appearance and larger in size, they operate on identical electrical principles and are of similar construction.

It should be explained that this unit does not supersede *all* batteries. It provides filament power for 4-volt tubes and replaces the " Λ " battery; but "B" batteries or a "B" power unit are still required. It should also be pointed out that the unit may be operated only with 110-volt, 60cycle house current.

New Trickle Charger For Use In D. C. Circuits

Many different types of trickle chargers have been developed for operation from 110volt, alternating-current house-lighting circuits, and these units have become very popular among set owners who wish to electrify their receivers at a low cost. However, few trickle chargers have been designed for use in direct-current circuits. As the public utilities, in a number of the large eities in this country, including New York City, furnish homes with direct current,



A compact trickle-charace unit for operation in 110-volt D.C. circuits.

there is a demand for such a device.

The accompanying illustration shows a simple, efficient direct-current trickle charger. It may be used to charge storage "A" or "B" batteries direct from a 110-125-volt direct-current line. It will charge from one to forty lead-battery cells at one time and the rate of charge is between 0.1 and 0.3 amperes, depending upon the number of cells in the series connection. A standard 6-volt



Diagram shows method of connecting trickle charger (M) to a radio set when batteries are used for the "W" supply.

storage battery, of the type used for radio purposes, is charged at a rate of approximately 0.3 amperes.

The construction of the unit is very simple. It consists of a fixed resistor and an annueter, connected in series with the battery and 110-volt D.C. line. The ammeter is of the "charge—off—discharge" type and is used to indicate whether the charger is correctly connected. The resistor is wire-wound, vitreous-enameled and will not burn out when operated under the conditions described above. The unit is enclosed in a cylindrical metal case, 6 inches long and 2¼ inches in diameter, which stands on legs one inches line.

There are several precautions, which must be taken in connection with operating directcurrent trickle chargers. As one of the mains carrying direct current is connected to the ground, it is necessary to place in series with the ground lead of the radio set a condenser between .002- and 0.5-mf. capacity, to prevent a short circuit of the 110-volt line. It is wise, also, to connect a similar condenser in the antenna circuit. If "B" batteries are used for the operation of the receiver, the trickle charger may be connected as illustrated in the diagram, However, if the receiver is operated with a "B" socket-power unit, it is necessary to disconnect the trickle charger from the house-current supply, by means of a doublepole switch, when the set is being used.

When connecting the charger with the house current for the first time, it is important to make sure that the plug is inserted in the light socket in such a way that

(Continued on page 1184)

\$100.00 Monthly Prize for Set Builders

In conjunction with the change of policy editorially announced in this issue, RAMO NEWS, during 1928, will offer a monthly prize of \$100,00 to radio constructors, set builders and custom radio builders for the best practicable radio circuit or constructional development of the month.

The idea of this prize is to encourage constructors in building. The prize is not given for all radio sets or hook-nps, or all power packs and other constructional articles, that are accepted for publication. Prizes will only be given on those published in our so-called "Blueprint Articles," where full constructional details are given.

If you have experimented with a new circuit—if you have made an important improvement on a known circuit—if you have designed a new power pack—and providing the material is acceptable, RADIO NEWS will publish the article and pay \$100.00 for the best one submitted.

It should be understood, that we are not interested in mere circuits or mere ideas. If you wish to enter into the monthly contest, it is necessary that you must give some evidence that you have actually built and tested the new feature. It is necessary that, with your first letter, photographs should be submitted, showing what work has been performed. If the editors are sufficiently impressed with the novelty of the idea, they will do in their discretion one of two things: RADIO NEWS will either build the circuit or power pack, whichever it may be, in its own laboratories, or will call upon you to sen $^\circ$ the model to New York for test.

In any event, RADIO NEWS reserves for itself the right, when accepting the article, to substitute and specify other apparatus, leaving the selection to the editors, if such should be advisable; but the main features of the design as recommended by the constructor will always remain intact.

All radio manufacturers are excluded trout the contest, as it is designed only for the encouragement of constructors and radio lmilders.

In the past, RADIO NEWS has been responsible for the publication of many important circuits; just to mention a few, the Ultradyne, the Tropadyne, the Interflex Series, the Strobodyne, the Peridyne and many others. RADIO NEWS desires the best and latest, and is willing to pay for it.

Furthermore, in many instances, the builder has made capital from his circuit. In a recent circuit published in RADIO NEWS (the Super-Hilodyne) the inventor, Mr. Jewell, was paid a very large sum for his novel circuit. It was first published exclusively in RADIO NEWS.

Furthermore, as an added incentive to the constructor, providing also the circuit is patentable, RADIO NEWS hereby agrees to take out a patent in the inventor's name, paying the entire patent fecs; and when a patent is issued, it will, of course, belong to the inventor in whose name it is taken ont. Do not, under any circumstances, send sets to RADIO NEWS without having first obtained the consent of RADIO NEWS. Kindly read the following conditions carefully and you will see what is wanted:

CONDITIONS AND RULES OF THE MONTHLY RADIO NEWS BUILDERS' COMPETITION

1. RADIO NEWS desires all new or novel circuits, power packs, amplifier combinations, television sets, etc.

2. No one shall be eligible for a prize unless some experimental work, showing the practicability of the device, has been demonstrated by the builder.

3. Photographs evidencing proof of the above nunst be sent with the article first to RADIO NEWS. If the article is accepted, RADIO NEWS will either send for the device, paying transportation therefor, or build the device in its own laboratory, in its discretion.

4. Parts used may either be standard parts obtainable on the market, or they may be homemade. The designer must submit a complete wiring diagram, drawn in ink on white paper, also sketches showing the outstanding features of the device in general. Articles giving complete constructional and detailed information to be sent at the same time.

5. Bundle all papers firmly together so they cannot be separated, and note that on each sheet and photograph, cutrant's name and address must be clearly printed. No penciled matter considered, Use typewriter or pen and ink. Rolled manuscripts are excluded from the contest. Use wherever possible, photo-mailers which are obtainable at all stationery stores.

6. The monthly competition closes on the fifteenth of every month. From the contest are excluded all radio manufacturers, as well as the employees of the Experimenter Publishing Company and their families.

Address all entries to Editor. Monthly Construction Feature, c/o RADIO NEWS, 230 Fifth Avenue, New York City.

When Radio Turns Street Lamplighter

By S. R. Winters

XPERIMENTALLY, a scientist in Washington, D. C., has opened the door of his automobile garage by means of radio. On a railway train in France the stations are announced by the use of electromagnetic waves. Various cities are employing broadcasting and receiving equipment in issuing orders to their police forces. Hundreds of radio fans are using their receiving sets in conjunction with clocks as alarm systems to wake their families in the mornings. An automobile traffic count has been made by virtue of radio apparatus. And, now, the street lights of an entire town are turned on and off through the magic of the wonderful radio waves.

A vacuum-tube transmitting set, using a small amount of power and operating on a wavelength of 7,500 meters, and five receiving sets responding to only one wavelength, control the street-lighting system of Glens Falls, New York. Street lamplighters in that town, like a buggy-whip soeket on an automobile, are now out of date. A lowpowered tube transmitter, not very dissimilar to the transmitting sets that bring ating the transmitter only 15 seconds each day. With five seconds' operation of the radio transmitter, the street lamps are lighted; when the operator twists the "off" button in the power house the radio transmitting set operates automatically for ten seconds and the lights are simultaneously cut off. The feeder or electric-power lines extend to five different sections of Glens Falls and, although each section or unit is independent of the other, the entire town's thousand street lamps are controlled by virtue of the carrier-current system.

This wired radio system involves the use in the powerhouse of a small panel board holding all of the radio transmitting equipment; the latter consists of two 50-watt vacuum tubes and a simple oscillator circuit. This panel hoard contains the electric switches or buttons which are designated as "off" and "on," respectively. Turning the "on" button places the radio transmitter in the circuit for five seconds. The result: radio-frequency impulses are generated, these heing fed to five wires leading to as many receiving stations, where radio apparatus is installed.



One of the automatic receivers which governs a lighting district is contained in the box on the pole.

tential in the feeder wires to the desired lighting voltage—110—and the street lamps are then lighted. At daybreak the operator at the powerhouse turns the "off" button on the radio-transmitter panel and the radio waves—in this case "wired wireless" again pass over the feeder wires; they are picked up by the radio receiving sets and the relays, and, at the proper instant, the street lights are turned off.

Each of the receiving sets employed in



music and speech to our homes, feeds a carrier-current or radio-frequency wave along wires leading to the receiving stations. There radio receivers tuned to that single wavelength, or frequency, respond to the radio wave and, in turn, electric switches are tripped, relays operated, and street lamps lighted.

QUICK WORK

This radio system does not disperse waves in all directions, but concentrates its force along the electric-power wires and thereby a whole town can be illuminated by operAbove, the line-tuning units and coupling condensers which feed the carrier current into the power lines. Right, the panel of the automatic transmitter which controls the lighting system of Glens Fells, N. Y.

NIGHT AND MORNING WORK

The five receiving sets, one in each of the five sections of the town's street-lighting system, control the relay circuits to complete the lighting-current supply. Transformers in each of the five independent units of the lighting system step down the pothis radio-operated street-lighting system contains one vacuum tube, relays, transformers, and other necessary units for the reception of radio impulses and for actuating the control circuit. The tube used in each receiver is operated below its rating and has an anticipated life of twelve (Continued on page 1161)

(Communed on page

List of Broadcast Stations in the United States

Radio Call Letter	BROADCAST STA. Location	Wave (Meters)	Power (Watts)	Radio Call Letter	BROADCAST STA, Location	Wave (Meters)	Power (Watts)	Radio Cali Letter	BROADCAST STA, Location	Wave (Meters)	Power (Watts)	Radio Call Letter	BROADCAST STA. Location	Wave (Meters)	Power (Watts)
KDKA (Abo 62:) pow KDLR KEXW KDYLW KEXW KFAB KFFBB KFFBB KFFBB KFFBB KFFBB KFFBB KFFBB KFFBB KFFBB KFFB KFFI KFFI	East Pittsburgh, Pa., 4 5, 42.95, and 27 meter t-wave transmissions er.) Devils Lake, N. D., Salt Lake Chry Utah Burbank, Calif. Portland, Ore Lincoln, Neb. Phoenix, Ariz. Boise, Idaho, Atz. Boise, Idaho, Atz. Boise, Idaho, Atz. Saeramento, Calif. Everett, Wash, Calif. Everett, Wash, Ariz. Banta Barbara, Calif. Broupont, Ariz. Brookings, S. D. Minneapolis, Minn. Portland, Ore. Bone, Idwa, Woo, Kellogy, Idaho Bone, Idwa, Wichita, Kan, Gunnison, Colo, Oskaloosa, Iowa, Junean, Ataka, Fond du Lae, Wis, Marshaltown, Iowa, Oskaloosa, Iowa, Junean, Ataka, Fond du Lae, Wis, Marshaltown, Iowa, Oskaloosa, Iowa, Los Angeles, Calif. Fort Worth, Texas Status, Colo, Oskaloosa, Iowa, Los Angeles, Calif. Fort Borth, Colo, Oskaloosa, Iowa, Los Angeles, Calif. Fort Morth, Texas Status, Ore Spokane, Wash, Juncan, Ataka, Fond du Lae, Vis, Marshaltown, Iowa, Okalabona City, Oka, Astoria, Ore Fort Dodge, Iowa, Fort Worth, Texas, Lawrence, Kansus, Lawrence,	$\begin{array}{r} **316 \\ **3 \\ 100$	0000 001kcr (ry1ng 15 500 500 500 500 500 500 500	WYZZBFGHIJKLNOWXFHM® GGGGGGGGGFFFFFFFGGGG HHHHO GGGGGGGGGGGGGGG HHHHO GGGGGGGGGG	 Fort Morgan, Colo.,, TDenver, Colo. TDenver, Colo. Kallspell, Montana, Jowa City, Iowa. Alva, Oklahoma. Oklahoma. Calif. La Crescenta. Calif. San Angeles, Calif. Itallock, Minn. Raton, N.M., Aneta, No. Dak. Los Angeles, Calif. Itallock, Minn. Raton, N.M., Aneta, No. Dak. Aneta, No. Dak. Los Angeles, Calif. Itallock, Minn. Raton, N.M., Aneta, No. Dak. Los Angeles, Calif. Italock, Minn. Pienér, Okla. Cedar Grove, La. Inglewood, Calif. (port. Natoria, Minn. Pueble, Colo. Hardin, Mont. Dakland, Catif. Parelio, Colo. Hardin, Mont. Oakland, Catif. Parelio, Colo. Hardin, Mont. Oakland, Catif. Parelio, Colo. Hardin, Mont. Dakand, Catif. Pueble, Colo. Hardin, Mont. Dakand, Catif. Parelio, Colo. Hardin, Mont. Parelio, Calif. Parelio, Calif. Parelio, Calif. Parelio, Calif. Cola. Cordano Parelso. Martinee, Tex. Spokane, Wash. Martinee, Tex. Spokane, Wash. Martelsoc. Calif. Martinee, Calif. Martin	$\begin{array}{c} 219\\ 219\\ 294\\ 205\\ 224\\ 205\\ 224\\ 222\\ 220\\ 213\\ 222\\ 220\\ 207\\ 213\\ 222\\ 207\\ 207\\ 213\\ 207\\ 207\\ 213\\ 207\\ 210\\ 207\\ 210\\ 207\\ 210\\ 207\\ 210\\ 207\\ 210\\ 207\\ 210\\ 207\\ 210\\ 207\\ 210\\ 207\\ 210\\ 207\\ 210\\ 207\\ 210\\ 207\\ 210\\ 207\\ 207\\ 210\\ 207\\ 207\\ 207\\ 207\\ 207\\ 207\\ 207\\ 20$	* 100 100 100 100 250 250 250 250 100 100 100 100 100 100 100 1	KWKC KWKC KWSC KWUC KWSC KWUC KWC KWC KWC KWC KWC KWC KWC KWC KWC KW	St. Louis, Mo Kansus City Mo Shreveport, La. Decorati, Iowa Pullman, Wash Banta Ana, Calif LeMars, Iowa (day), " Brownsville, Texas. Scattle, Wush San Francisco, Calif. Ohleago, III. Oaklaud, Calif Arlington, Virginia" Chileago, III. Oaklaud, Calif Arlington, Calif Arlington, Calif Arlington, Calif Arlington, Calif Arlington, Nash Hersey, City, N. J. Jangor, Mc, (Sandays) See WHEC Wooster, Ohlo Detrolt, Mich Taunton, Mass. Tcolumbus, Ohlo Detrolt, Mich Appleton, Wis Willow Groye, Pa Auburn, Ala. Grand Rapids, Mina Auburn, Ala. Grand Rapids, Mina Auburn, Ala. Grand Rapids, Mina Auburn, Ala. Grand Rapids, Mich Tenses issued lay hority, will rema	2242 3905 3905 3905 3905 2918 3905 2918 3905 2918 3905 2918 3905 2918 3905 2918 3905 2918 3905 2918 3905 2918 3905 2918 2918 2918 2918 2918 2918 2918 2918	1000 1000 500 500 1000 1500 500 500 *2500 *2500 *2500 *500 *500	WDDGORCF- WDDACKF- WDDACKF- WWEAAAN WWWWWWWWWWWWWWWWWWWWWWWWWWWWWWW	Orianido, Fia (SKE, variable, 250 wai Wilmington, Del Minncapolis, Minn. Chattanooga, Tenn. New Haven, Conn. Muss. Tuiseola, Ili, (daytime) Heelinore, N Y. Bellonere, N Y. Cherotanere, R I. Columbus, Ohio. Liso 54.02 meters, 250 w. Cleveland, Ohio. Maostanov, Wis Cambridge, Ohio. Liso 54.02 meters, 250 w. Cleveland, Ohio. Superior. Wis Cambridge, Ohio. Chicago, Ili. Superior. Wis Cambridge, Ohio. Chicago, Ili. Berlott, Wis. Chicago, Ili. Beston, Mass. Harstsburg, Ili. Berten Spas., Mich. Chicago, Ili. Beston, Mass. Hasshort-wave transmit Evanston, Ili. Berten Spas., Mich. Chicago, Ili. Boston, Mass. St. Cloud, Minn. Philadeiphia, Pa. Knoxyellie, Tenn. Coligereville, Minn. Syraeuse, N. Y. Indlanapolis, Ind. Balthuore, Md. Coligereville, Minn. Syraeuse, N. Y. Indlanapolis, Ind. Balthuore, M. J. Philadeiphia, Pa. Hopkingylle, Pa. Philadeiphia, Pa. Hopkingylle, Nen.	$\begin{array}{l} 238\\ 82975\\ 2243\\ 22752\\ 2243\\ 22752\\ 2243\\ 22752\\ 2233\\ 14400\\ 22242\\ 223550\\ 12243\\ 22242\\ 224550\\ 12243\\ 22245\\ 12243\\ 1248\\ 22245\\ 122222\\ 222222\\ 222222\\ 222222\\ 222222\\ 222222$	*500 100 500 500 256 1000 256 256 256 256 256 256 256 256 250 1000 1000 1000 1000 1000 1000 1000
KERVERSE KARKER KERVERSE KERVE	itockford, Ill. Galveston, Texas. Slouv City, Iowa. Slouv City, Iowa. Slouv City, Iowa. Slouv City, Iowa. Slouv City, Iowa. Long Leach, Calif. Lincoln, Neb. Omnha, Neb. Omnha, Neb. Omnha, Neb. Common. Greenville, Texas. Greenville, Texas. Greenville, Texas. Calif. Carterville, Mo. Spokane, Wash. Anetoraue, Alaska. Holy City, Calif. J. 53, 03, 106 meters, 50 w. San Poince, Calif. Commiss, Mo. Fort Worth, Texas. Holy City, Calif. J. 53, 03, 106 meters, 50 w. San Pinelsco, Calif. Coloratio, Spiss. Coloratio, Calif. Asia Dio meters, 50 w. Houston, Texas. Si Dometers, 50 w. Independence, Kat. Houston, Texas. Si Dometers, 50 w. St. Louis, Mo. San Pranelseo, Calif. Avalon, Calif. San Diegener, Colo. San Autonio, Texas. Son Autonio,	$\begin{array}{c} 268\\ -268\\ $	$\begin{array}{c} 100\\ 100\\ 100\\ 100\\ 500\\ 2000\\ 500\\ 500\\ 500\\ 500\\ 500\\ $	KJR KJR KLDS KLLS KLLS KLLS KLLS KLLS KLZ KMBCC KMMC KMMC KMMC KMMC KMMC KMMC KMM	ree until April 1, Scattle, Wash	$\begin{array}{c} 349 (1) \\ 349 (1) \\ 349 (1) \\ 349 (1) \\ 349 (1) \\ 357 (1) \\$	2300 s) 15 500 1500 2500 500 500 500 500 500 500	WATT WBAAA WBAAL WBAAL WBAAA WBAAA WBBAP WBBAA WBBAP WBAA WBAA	Boston, Mass (portable West Lafayette, Ind., J. Harrisburg, Pa. (day) Halilimore, Md) 2011 *273 300 *285 500 2250 2250 2250 2250 2250 2250 22	100 5000 5000 100 5000 10000 1000 1000 1000 1000 1000 1000 1000 1	WFLAL WGGBBC WGGBSS WGGBSS WGGBSS WGGBSS WGGBSS WGGBSS WGGBSS WGGBSS WGGBSS WGGBSS WGGBSS WGGBSS WGGBSS WGGSS WHAS	Clearwater, Fla. Lancaster, Pa. Freeport, N. Y. Memiphis, Tenn. Evansville, Ind Scranton, Pa. tNew York, N. Y. Newark, N. J. tChleago, Ill. tStranton, Pa. tNew York, N. Y. Newark, N. J. tChleago, Ill. tStranton, Pa. tStanton, N. Y. Stanton, N. J. Human, N. Y. Stanton, N. Y. Stanton, N. Y. Stanton, N. Y. Stanton, N. Y. Stanton, N. Y. Scheneetady, N. Scheneetady, Scheneetady, N. Scheneetady, N. Scheneetady, Scheneetady, N. Scheneetady, N. Scheneetady, N. Scheneetady, Scheneetady, Scheneetady, Scheneetady, N. Scheneetady, Scheneetady, Scheneetady, Scheneetady, Scheneetady, N. Scheneetady, Scheneetady, Scheneetady, Scheneetady, Scheneetady, Scheneetady, Scheneetady, Scheneetady, Scheneetady, Scheneetady, N. Scheneetady, Scheneetady, Scheneetady, Scheneetady, Scheneetady, Scheneetady, Scheneetady, N. Scheneetady, Scheneetady, Sche	517 2166 2252 2269 2236 2231 3499 2248 2242 2268 2242 2268 2242 2268 2242 2268 2242 2268 2244 200 3033 2270 220 2200 200	7500 15 4000 15 2500 250 2500 2500 2500 2500 2500
KGCDA KGDDA KGDDP KGDDP KGDDW KGDDW KGDDW KGDDW KGCP KGCP KGCP KGCP KGCP KGCP	Mandari, No. Dak. Vida, Montana. Dell Rabids, So. Dak (daytime). Barreit, Minn Stockton, Calif. Pueblo, Colo. San Antonio, Texas Humboldt, Neb Oklitam, So. Dak Los Angeles, Calif. Eugene, Ore. Yuma, Colo. El Centro, Calif. Grand Island, Neb Minneapolis, Minn Long Beach, Calif Central City, Neb	240 244 254 255 205 217 224 207 207 263 207 263 201 263 201 263 205 205 205 204 204	100 15 50 10 10 15 500 50 15 100 50 100 50 100 50 100	KTHS KTNT KTSA KUU KUU KUU KUU KUU KVU KVU KVU KVU KVU	Hot Springs, Ark. Muscatthe, Iowa. San Antonio, Texas. Uouston, Texas. Seattle, Wash. Seattle, Wash. Fayettevelile, Ark. Missonih, Mont. Vermillion, So. Dak. Austin, Texas. Taeoma, Wash. Seattle, Wash. Tateva, Okla. Bellingham, Wash. Portland, Oregon. Cedar Rapids, Iowa. Shreveport. La. Stockton, Calif. Portland, Ore Stockton, Calif.	**384 2566 2613 3955 2000 2971 4844 2322 2345 210 2400 2400 2400 240 240 240 240 240 240	*1000 2000 2000 500 500 500 500 500 500 1000 500 1000 500 250 250 250 250 500	WCMA WCOC WCOT WCRW WCSH WCSO WCSO WCSO WCSO WCSO WDAD WDAD WDAD WDAA WDAAF WDAA WDAA WDA	Culver, Ind. Perssacola, Fia Columburs, Milss. tolneyville, R. L. Chlengo, Ill. Portland, Maine Iso 63.79 meters, 250 w Springdeld, Ohio. Fort Wayne, Ind Danbury, Conn See WJR See WLAC Tanupa, Fia Kansas City, Mo Amerillo, Texas. Fi Paso, Texas. Fi Paso, Texas.	261 230 231 225 224 366 256 214 265 268 370 263 263 263 234 545 231	500 500 500 500 500 500 100 500 100 250 1000 250 1000 *750 *750	WISN WIVA WJAG WJAG WJAK WJAK WJAK WJAS WJAS WJAS WJAS WJAS WJAS WJAS WJBB WJBB WJBL WJBL WJBS	Milwaukkee, Wis. Norfolk, Va. Norfolk, Neb. Kokomo. Ind. Cedar Rapids, Iowa. Providence, R. I. Pittsburgh, Pa. Jacksonville, Pla. Cleveland, Ohlo Mt Prospect, Ill. Jollet, Ill Sarasota, Fla. LaSalle, Ill. Red Bank, N. J. Ypsilanti, Mich. Decatur, Ill. New Orleans, La. Chicago, Ill.	2210 3233 22333 22340 4840 224484 2244 2247 2263 2223 2263 2213 2263 2213 2263 2213 2263 2213 2263 2213 2263 2213 2263 2213 2263 2213 2263 2213 2263 2213 2263 2213 2263 2213 2263 226	250 10(500 250 250 500 500 500 500 500

www.americanradiohistory.com

daylight power, **Standard or constant-frequency transmission. †Remote Con

(Continued on page 1147)

"Weighing In" Radio Stations

A Description of Easily-Constructed Apparatus That Will Tune in Different Radio Stations by the Addition of Weights on a Balance



By A. Binneweg, Jr.

ATTE Marconi of our college was Philip Randall; he was a young man, not over twenty-five years of age, who had recently received his E.E. degree. He had been promised the first vacant assistant-professorship in the electrical department and, while waiting for this opening, he had accepted the position of laboratory assistant. He was kept very busy with his official duties during the day but, frequently after dinner, he would retire to a corner of the laboratory and experiment with new radio apparatus of his own invention. Often a light would be noticed in the laboratory during the early hours of the morning and everyone knew that Randall was occupied in perfecting some new radio device.

From our brief description of Philip Randall, we do not wish you to gain the impression that he was eccentric; for he was not. Randall was well-liked among the students of the college and was popular also with the fair sex. On the nights when special dances were held he was always to be found in the crowd, and he was present at all athletic events of importance. Participation in the rehearsals of the glee club was another college activity which he enjoyed greatly. However, he had always saved at least three or four evenings each week for experimenting in the laboratory, and during the course of a year he would develop many very interesting receivers.

THE PLOT THICKENS

It so happened that, for over a month prior to the Easter vacation, Randall appeared to be very busy with his radio experiments, and most of his associates aecused him of being unduly secretive. It was noticed that he had not been present at three consecutive meetings of the glee club and that he had left the Saturday evening dance before 11 o'clock. In addition to these suspicious circumstances, a light was seen burning in the laboratory every evening.

Usually, when busy with his experiments

in the laboratory, Randall would welcome the company of students, who were interested in his work, as often they would be able to assist him and check his results. During the period we are describing, he acted peculiarly, in this respect also; when anyone would enter the laboratory he would quickly cover up his work and plainly show that he did not desire company. When questioned about his work he would avoid giving any details, but promised to give a demonstration of his invention when it was complete.

A few days before the Easter vacation a complete change came over Randall. He seemed anxious to join everyone in having



"Randall scleeted a weight, placed it on the scale . . . and the signals were heard coming from the speaker."

a good time and was glad to be included in all social activities. He accepted several invitations to parties and surprised all by



The schematic diagram of a receiver which employs for a loop antenna a spiral spring which is tuned by its stretching under the strain of different weights.



inviting a number of students to a party at his home during the coming week.

Everyone was in the best of spirits on the evening of Randall's party. Six men who were particularly interested in radio had been invited and they were accompanied



This sketch illustrates the manner in which the balance is attached to the spring coil.

by an equal number of girls from the Giy itself. In the early part of the evening they played bridge; later the tables were removed and they danced to the times of an electric phonograph; and, around 10:30 P. M., refreshments were served. After all had finished eating it was suggested that radio music would finish up the evening in great style. This, it seemed, was exactly what Randall had been waiting for; as he stood up in preparation for making a speech.

A REMARKABLE DISCOVERY

"Ladics and gentlemen," he began, "for the past several weeks I have been spending all my spare time on a new invention which may revolutionize the entire radio industry, and tonight I will demonstrate to you a remarkable receiver which exemplifies my new deas. In my experimenting I have found that there is a distinct relationship between wavelength and weight, and, with the data which have been discovered after hundreds of tests, I have been able to develop an entirely new system of tuning. With this receiver, a different weight is used for tuning in each station. When this method is used the owner does not have to learn the technique of tuning, but has merely to select a weight which is marked with the call letters of the station he wishes to hear. This weight will automatically tune in the program. Now, gentlemen, if you will assist me, I will remove the set from the closet."

When the closet door was opened all persons in the room could see the apparatus which was to be used in the demonstration. There was a large table and over it a cover which extended almost to the floor. On one end of the table there was a small radio (Continued on page 1159)

. www.americanradiohistory.com


Whispering Across the Hudson River

A Loud Speaker with 30-Watt Distortionless Output, which Can be Heard Over a Distance of a Mile

By Joseph Riley

At the left the top plates of the unit have been removed, slowing its interior. Below, right, the diaphragm and coil of the speaker: the detached coil shows the method of veinding the fine aluminum strip. Insulation is provided by a layer of varnish, 0002-inch thick. The proximity of the coil to the pole pieces has a beneficial cooling action. NE of the most rigorons tests to which a loud speaker has ever been subjected was recently performed in New York City by engineers of the Bell Telephone Laboratories, when they installed a giant speaker on the roof of a thirteen-story building on the New York side of the Hudson River for direct communication with the Jersey shore, which is over a mile distant. Engineers on the opposite side of the water heard both music and voice reproduced with enormous volume, but without distortion.

(Continued on page 1167)



Above, the completely-assembled lond-speaker unit: two of the binding posts are connected to the moving coil and the other pair to the onds of the electromognet's windings.



Above is diagramed the assembly of the new loud-speaker unit; the diaphragm with its attached coil works like the plunger of a pump, at high (andio) frequencies.

At the right, the two horns used in the tests across the Hudson River; nine units were used on the smaller one. Both are of the exponential type, giving maximum range and quality to the transmission of sounds.





www.americanradiohistory.com



What a Radio Tube Is, and What It Does

THOROUGH understanding of the functions of the vacuum tube, the heart of broadcast transmitting and receiving apparatus, is of fundamental importance to the radio beginner if he wishes to understand even the most elementary principles under which his equipment operates. Articles explaining the action of these tubes have been published many times in this and other magazines; but they have been usually so technical that the ordinary listeners, the rank and file of the vast audience which now enjoys the pleasure of radio entertainment, find considerable difficulty in apprehending the meaning. Too often a valuable article is made puzzling for them by the presence of electrical terms which, though elementary, are not frequently used in ordinary conversation.

In this article the writer will attempt to explain the operation of a vacuum tube, in language which the average reader is able to understand; and he will avoid, as far as possible, the special terms used by scientists. Of course, it will be impossible to explain here some of the more complicated applications of radio tubes, as these require a fundamental knowledge of radio circuits in order to learn what takes place; but the way in which a tube functions as an *amplifier* will be described. This is the use of the majority of tubes in radio receivers and, therefore, this explanation should clear up many problems which perplex the mind of the beginner.

USE OF THE FILAMENT

A tube consists of a filament, a grid and a plate, all "hermetically" scaled in an "evacuated" bulb, which is provided with convenient external terminals for making contact with these three "elements" inside.

The filament is simply a thin wire of

By Clyde A. Randon

special composition which usually becomes "incandescent" when in operation, but not Some filaments must be necessarily so. heated to incandescence (glowing whiteness) for best results, while others perform more satisfactorily when operating at a cherry-red heat; different filaments require different temperatures for highest efficiency, but all operate in a similar manuer. A filament may be looked upon as composed of a "volatile" substance, which evaporates when heated and thus gradually disappears. Water at ordinary room temperatures, for example, evaporates slowly but, as it is heated, more and more evaporates; and finally there is violent "ebullition" (boiling) and the water becomes steam and passes into the atmosphere. The action of evaporating water and the escape of particles of matter from a heated filament are very similar. (See Fig. 1.)



At .1, the "B" battery switch is open, and the electrons gathered in an aimless erowd around the filament. At B the plate is POSITIVELY charged by connection to the "+" of the "B" battery, and electrons are attracted in a steady stream from filament to plate.

All substances are composed of almost inconceivably small particles called "molecules." At ordinary temperatures, these small bodies are continually colliding with



At A, the disconnected grid has little effect on the electron flow from filament to plate; but at B the "+" charge on the grid adds attraction and greatly increases the flow. On the contrary, the "-" charge on the grid, shown at C, will drive back the electrons and let few or none reach the plate.



At A we have no current in the filament, no electrons coaporating. At B, with the battery switch closed, the filament is lighted and from it electrons in countless billions are escaping.

cach other, and in a liquid or gas they are traveling in random directions. If a body is heated, these molecules speed up and thus bombard their neighbors with greater velocities. At high temperatures, ("high" for one substance may be "low" for others; this is only relative) the molecules reach such velocities that some are capable of breaking away from the influence of the others, and thus pass away from the substance, in the form of *vapor*; that is, "evaporation" takes place.

Due to the influence of neighboring molecules, there is a tendency on the part of a solid or liquid substance to "cohere," or hold on to its constituent parts. In the case of water, for instance, there is what is called "surface tension"; that is, the surface of the liquid acts like a *stretched membrane* and it is thus made more difficult for molecules to escape (or the liquid to evaporate) at ordinary temperatures. (One can easily perform a simple experiment in this connection. A small needle can be made to float by laying it carefully and perfectly flat on the surface of a glass of water; thus showing that there is "surface tension." The needle must be perfectly dry or even oily; otherwise the water will "creep" around the needle and it will sink.)

"EVAPORATING" THE FILAMENT

If water is heated, the molecules reach such velocities that the surface tension is no longer strong enough, and they simply break through in large numbers and leave the liquid—as we have explained, *evaporate*. This is almost exactly what takes place in a heated filament. At high temperatures (very much greater than the boiling-point of water, of course) the velocity of the "clectrons" or particles of *negative* clee-



tricity in the filament becomes so great that they simply shoot out into the surrounding space, with relatively large velocities.

If another element (such as the "plate," found in all radio vacuum tubes) were placed around the filament, but *insulated* from it, some of these electrons would strike the plate; the rest would tend to form a "cloud" around the filament, some electrons leaving the filament and others again entering it. (This "space-charge" effect is illustrated, and explained, on page 846 of RADIO NEWS for February, if any readers desire to follow it further.) A condition approaching *equilibrium* would be reached; that is, there would be the same number of electrons leaving the filament as returning, and no useful result would occur. (See Fig. 2.)

If, however, a *positive* charge (compared with that on the filament) or voltage is placed on the plate, electrons will flow to the plate and continue to do so as long as the filament is heated and the positive charge maintained; since electrons constitute *negative* electricity, they are attracted by a positive voltage (for *unlike* electrical charges attract each other.)

THE ELECTRON STREAM

In the vacuum tube, when connected in this way, there would thus be a *continuous flow of electrons*, and this constitutes an electric "current." It is to be noted that such a stream can proceed in only one direction, from filament to plate—negative to positive. It is often said that the current travels from positive to negative, and this is because in the early days the scientists This diagram shows the simplest way to "hook up" a tube to make a radio receiver. The "A" battery lights the filament; the "B" battery "puts volts on" the plate and causes a flow of current, the changes in which are heard in the plates as sounds. The "C" battery puts on the grid the voltage, commonly called a "bass," which is needed because this tube must be a "detector" (see page 1151) as well as an "amplifier." A pictorial diagram of this one-tube set will be found on page 1168.

IN THE REPORT OF T

Blueprints

Interpretation of FREE

BEGINNING with this notice, RADIO NEWS will give away, free, complete blueprints for sets described in the constructional articles that will be printed in its pages, beginning with the April issue. Blueprints of sets published previous to the April issue are not offered free.

Under the new policy of RADIO News, no manufacturers' names nor trade marks are given in the text pages of RADIO NEWS. For the information of those who wish to construct sets and power packs, however, and to facilitate their work, the blueprints will contain complete specifications of all the material which is used in making the complete apparatus described in the constructional article. These blueprints will be given free to readers who apply in person at the office of RADIO News, between the hours of 9:00 a. m. and 5:30 p. m., daily. Those who apply by mail should enclose ten cents, for postage and mailing only. Address Blueprint Department, Ranio NEWS, 230 Fifth Avenue, New York City.

A RA A MARANA MANANA MANANA

had their choice of two guesses and they guessed wrong. To this day, this erroneous assumption is still prevalent, in common speech, just as we say "the sun rises;" but if the reader will remember that the electrons proceed from filament to plate, there need be no confusion in his mind.

THE ELECTRON-CONTROL GRID

By introducing a third element, called for short a "grid," the stream of electrons between plate and filament can be controlled. The grid consists only of very line wires, spaced at definite distances apart so that a large proportion of the electrons can pass between them. Just as the positive charge on the plate tends to cause a flow of electrons from the filament, so a positive charge on the grid will also tend to increase this flow. (See Fig. 3.)

The grid, however, is much nearer to the filament than the plate is; and any charge or "voltage" on the grid will thus have a much greater effect on the electron flow than an equal charge on the plate. A negative charge on the grid will decrease the electron flow to the plate (the "plate current") and the amount of decrease will depend upon the strength of the charge on the grid.

It is readily seen, therefore, that the grid acts as a delicate control of the plate current. Since a very small charge on the grid has a relatively large effect on the plate current, the tube "amplifies" the small electrical impulses which are "impressed" on the grid. Very small effects thus give large response.

USE IN A RECEIVER

In the simple circuit shown in the diagrams, the tube is used to amplify the weak "signal" impulses which arrive from a broadcast station. A passing wave *induces* a small current in the antenna and this flows through the coil between the aerial and ground. (Note that the current *oscillates* [reverses its direction, back and forth] between the aerial and ground and, therefore, for best results the ground connection must be well-designed also). The current in the primary coil gives rise to a *magnetic field*, which induces another current in the secondary. This gives rise to a difference (Continued on page 1168)



Above we have several of the steps in the assembly of a vacuum tube. At the left: above, the filament; below, the.

plate and the grid. The four following views show successive stages of manufacture.

An R.F. Short-Wave Broadcast Receiver*

(Awarded \$100.00 Monthly Prize-See page 1119)

Incorporating an Optional R. F. Stage, Interchangeable Coils for the 10-725-meter Bands, and Push-Pull Amplification

Bv W. Francis Goodreau



Not only in the United States, but in a number of other countries (including England, France, Germany, Holland, etc.) many stations are broadcasting on waves between 30 and 200 meters. A majority of these programs, even those originating on the

 $B_{\ ers}^{\ ECAUSE}$ of the demands of read-ers for the constructional article on a short-wave receiver which it contained, the issue of RADIO NEWS for October, 1927 has been completely exhausted. To satisfy the many people who want to get into the short-wave "game," we are presenting herewith a second article describing another shortwave receiver of excellent design. We earnestly recommend it to our readers who wish something new .--- Enrror.

other side of the Atlantic, are available to the owner of an efficient short-wave receiver. A number of these stations are broadcasting on regular schedules, while a great number are "on the air" quite frequently, especially when unusual programs are being offered. Practically all of the short-wave stations in this country broadcast the same program simultaneously on their broadcast and short-wave transmitters.

Because of their musical excellence, these programs are interesting to every listener, and especially to the DX fan who, having received practically all of the American and Canadian stations, is looking for new worlds to conquer. Unfortunately, until recently it was not possible to hear the short-wave broadcasts with any degree of satisfaction, because of the lack of suitable receivers. The sets that were used were mostly designed for code reception and, although they were very efficient, they were not designed to give the quality of reception demanded of broadcast receivers to-day.

Recently, however, articles have appeared in a number of radio magazines describing the construction of sets designed for quality of tone reception on short waves. Most strictly-short-wave receivers use condensers of very small maximum capacity in order to tune to the short wavelengths. When receivers of this type are used for the reception of waves above 200 meters, it is



This picture shows the location of practically all parts used in the construction of this short-wave receiver; the symbols correspond to those used in the wiring diagrams and the list of parts. L1 and L2, R.F. coils; T1, T2 and T3, audio trans-

formers; V1, V2, V3, V4 and V5, tube sockets; C1, C2, tuning condensers; C3, regeneration condenser: R2, R3, R4 and R5, filament ballasts: R6, volume control; PH, oscillation control, Sw, switch controlling R.F. amplifier stage.

* RADIO NEWS Blueprint Article No. 52.



appreciated.

the regular waves.

AVELENGTHS below 200 meters

are rapidly becoming established

as channels for the broadcasting

of radio entertainment. The re-

cent announcements of the decision of a

number of popular broadcast stations to

operate special transmitters on these waves

proves that the industry's growing faith

in transmission on high frequencies is be-

ginning to be manifest in a concrete form.

On the other hand, the interest of the gen-

cral public in the construction of short-

wave receivers shows that the special pro-

grams which are being transmitted on waves

ontside the broadcast band are being

Short waves have many advantages, from

the viewpoints of both the broadcaster and

the listener. In the first place, they seem

to be more efficient, as the programs of

low-power stations are frequently heard

half-way around the world. Secondly, there

is less congestion, as more individual chan-

nels are available; and, as a result, a listener

may often receive the program from the

short-wave transmitter of a station with less interference than would be experienced

in receiving the same program broadcast on



Diagram gives complete details for building the six sets of coils required in order to give this set a wavelength range from 10 to 725 meters. The primary coil consists of 10 turns of No. 24 8.8.C. wire wound on a form $2\frac{1}{2}$ inches in diameter, with whichever set of coils it is used.

necessary to use coils having a large number of turns of wire, in order to get an inductance value high enough to cover the waveband between 200 and 500 meters. While it is true that a tuned circuit having a large inductance and a small capacity will usually give londer signals from any given station than a smaller inductance and large capacity tuned to the same station, it is also true that the *selectivity* of the circuit using the small condenser and large inductance will not be as great as that of the other combination.

FAULTS OF EARLY DESIGN

It seems to have been the idea of the designers, of most short-wave receivers, that these were to be used entirely for reception of short waves; and that a separate reeeiver would be used for the regular broadcast band. While the use of plug-in coils will enable the operator of a short-wave receiver to cover the different bands, it will result in a receiver that is not very selective above 200 meters. The design of most of these short-wave receivers is rather a step backward, when compared with the usual set used for broadcast reception; since practically all of the sets designed for shortwave work are of the plain regenerative type.

It must be admitted that the use of two receivers has some advantages; but it must also be pointed out that the cost of two receivers is beyond the means of many. Besides this, there is the requirement of additional space, not only for the receivers but for the separate sets of batteries that would probably be used.

The special short-wave receiver described in this article was designed to be a flexible

receiver, suitable for use on any wavelength band merely by plugging in the proper coils. By referring to the schematic diagram of this set, you will see that a stage of tuned radio frequency has been placed before the usual regenerative circuit. Because of this additional tuned circuit, the receiver is very selective on wavelengths above 200 meters, even though small tuning condensers are utilized. The audio-frequency amplitier has been designed for quality reception; it includes one stage of straight transformercoupled and one of push-pull amplification. Thus, it will be seen that this set combines the advantages of both the broadcast and short-wave receivers in one flexible all-wave circuit.

CONSTRUCTION

The set is so designed that the experi-

menter will find it easy to construct according to his personal desires, since a wide number of types of tubes can be used in the set. If it is not so desired, the audiofrequency end of the circuit need not be of the push-pull type; although the quality of reception will probably be somewhat better if this type of amplifier is used. Another point in favor of this receiver is that, although a complete equipment of coils to cover all the wavebands over which the set is capable of operating would be rather expensive, the constructor may purchase the coil mountings and two coils for the short-wave band at which the receiver is to be operated most frequently, and add the other coils later when finances permit. This feature alone is a good indication of the flexibility of this receiver.

With the panel and sub-panel drilling layouts shown here, it will be a simple matter to place the various parts in their proper positions. It will be noted that, although the front panel measures only 24 inches long, the spacing from center to center of the variable condensers is 8 inches; more than the usual spacing of such instruments. Because of the short wavelengths to which this set can be tuned, this spacing was deemed desirable to prevent interaction between units and climinate any need for shielding. The coils are placed at right angles to each other and sufficient space is left between them to assure correct operation.

In assembling the set, the sub-panel should be drilled first and the apparatus mounted on it. After this, the front panel should be drilled and the condensers (C1, C2 and C3) volume control (R6) and oscillation control (PH) mounted. Care should be taken in laying out the panel and sub-panel, in order to get the holes at the right points; as otherwise considerable difficulty will be encountered when mounting the apparatus. After all of the parts have been mounted on the panel and sub-panel, the brackets should be screwed into place and the set is ready for wiring. The oscillation control bas been mounted on the front panel because of the need of readjusting it with the different coils and tubes that will possibly be used.

It will be noticed that a double-pole, double-throw, jack switch (Sw) has been incorporated in the set between the radiofrequency and detector tubes. This switch is for the purpose of comparing results obtained with the set when the radio-frequency stage is used and when the set is operated as a simple regenerative receiver. It is also helpful in adjusting the receiver when it is first tried out.



This shows the arrangement of controls on the front panel of the set. C1 and C2, wavelength tuning dials; C3, regeneration control; PH, oscillation control: R6-Fil. SW, volume control and filament switch. The plug-in coils are partly visible.





Care should be taken in placing the grid leak R1 and grid condenser C4, to keep them away from the plate wires leading to the radio-frequency tube (V1) and also from the radio-frequency choke (RFC) in the detector plate circuit. The sub-panel mounting brackets are placed as indicated; one slightly off center to provide additional support for the weight of the audio-frequency transformers (T1 and T2).

TESTING AND OPERATING

After the wiring is completed the set may be tested. It is best to throw the double-pole switch so that the acrial and ground are connected to the primary of the second tuning unit, in order to get accustomed to tuning the regenerative part of the receiver. It will be noticed that the set is very selective on the short waves; but, the nearer you come to the band be-tween 200 and 500 meters, the more interference will be experienced. However, when the radio-frequency stage is connected in the circuit, the selectivity is very good, on both broadcast and short waves.

Having spent some time testing the receiver in this manner, the acrial and ground should be connected to the primary of the first tuning unit by throwing the switch (Sw) in the opposite direction. The ad-justment of the oscillation control (PH) is not difficult. Tune in a station near the lower end of the condenser scale, turn back the dial of C3 and then slowly turn the dial on the oscillation control (PH) to the left. On retuning the dials C1 and C2 no squeals should be heard; if they are heard, turn the oscillation control still farther to the left. If it is found impossible to control the oscillation in this manner, move the primary

are used to identify them correspond with those in the other illustrations, as well as the text.

> of the second tuner further away from the secondary. The relation of the primaries on the tuning coils L1 and L2, to their respective secondaries, governs the selectivity of the set.

> It was found in testing the receiver that different adjustments of the oscillation control (PII) were needed for some of the coils, although most of the coils could be operated without the adjustment. When experimenting with the set, a 199 tube was tried in the radio-frequency stage and was found to be easier to control than a 201A but, since it was not difficult to adjust the 201A and since the signals were louder with this tube, it was finally chosen. In changing the tubes, the automatic filament controls (R2, R3, R4 and R5) were found very convenient, since they are easily changed, permitting the use of any type of tube without clumging the batteries.



ment of all wiring under the sub-base panel. Letters and numbers in this drawing refer to corresponding wires and

wiring above the sub-base panel and the leads to panel apparatus, which appears on the opposite page.

Radio News for April, 1928





This drilling layout shows the exact location of all holes required for mounting parts on the front panel of the receiver.

In the audio-frequency stages, care should be taken to secure the proper "C" and "B" battery voltages recommended by the manufacturer. This information will be found in the cartons in which the tubes are sold. When using two 171-type tubes in push-pull,

it is possible to secure dance-hall volume. Using the 210-type tubes with 425 volts on the plate, terrific volume can be obtained.

The grid condenser (C4) has a capacity of .00025-mf., and the grid leak (R1) has a resistance of 5 megohus. Grid leaks of different values should be tried, in order to determine which produces the best results. If the set has a tendency to howl, try a grid condenser of .0001-mf. capacity.

In testing the receiver in the RADIO $N \in w$ s Laboratories, coils covering all the wave-lengths from 10

to 550 meters were used. Amateur shortwave stations from great distances were tuned in, and some very interesting phone conversation between amateurs on the Pacific coast was heard on the Atlantic seaboard with sufficient volume to operate a loud speaker. On the regular broadcast band, it was not unusual to find a station at almost every degree on the tuning dials.

COIL DATA

The illustrations of the receiver, which ac-



Above is shown the arrangement of parts and wiring under the sub-base panel. R1-C4, grid condenser and leak; RFC., R.F. choke coil; SW, D.P. D.T. switch. company this article, clearly show how various coils may be plugged in the coil sockets in order to receive stations on different wave bands. For receiving stations on any particular wave band two coils of identical construction are required. One coil (L1) is

used as an antenna coupler, and the other (L2) as a radio-frequency transformer, Each coil consists of two windings, a secondary (S) and a tickler (T). The primary winding (P) has the same number of turns for all wavelengths and is attached to the coil socket with a hinge, which makes it possible to adjust the coupling between the primary and secondary coils. The tickler windings of the coils for position L1 are not used. If manufactured inductors are purchased, the tickler connections may be disregarded. If the

coils are made at home the tickler may be omitted altogether.

In one of the drawings complete details will be found for making the various coils which are required for receiving stations

(Continued on page 1174)



The panel layout showing location of holes required for mounting parts on sub-base panel.

A Novel Automatic Volume Control

The Amplification of the Radio-Frequency Tubes is Controlled by the Output of a Two-Element Rectifier, Which Replaces the Usual Detector



N the present radio receiving sets employing high amplification, it is necessary to adjust carefully a "volume control" in order to reproduce signals of different intensities with the same audible intensity from the lond speaker. There are various devices which could be employed to regulate automatically the amplification of the signal, some of which employ moving mechanical parts. It is the purpose of this paper to describe a simple electric circuit, without moving parts, in which the amplification is regulated automatically by the signal, and the loud-speaker intensity reaches approximately the desired level for each signal, independent of the signal intensity and therefore irrespective of a reasonable amount of fading.

Any device to accomplish this object without introducing distortion of music or speech must be operated by the signal-carrier wave. Any variations in this wave's intensity must be compensated by reciprocal variations in its amplification. The method to be described provides for controlling the radio-frequency amplifier, thereby main-taining the desired signal level in the detector or rectifier, audio-frequency amplifier and loud speaker.

ESSENTIALS OF THE CIRCUIT

A set which has been constructed for broadcast reception, embodying this automatic volume control, comprises the following component sections: (1) A four-stage radio-frequency amplifier of the well-known



neutrodyne type, with UX-201A tubes, the antenna circuit tuned by one dial and the four coupling transformers tuned simultaneously by a second dial. The total amplification is controlled by varying the negative grid potential of the first three tubes. (2) A two-element rectifier with simple filter circuits to reject the radio-frequency currents and to segregate the direct and audioin the form of a voltage-attenuator connected to the grid of the first audio-frequency amplifier tube. (4) A four-stage audio-frequency amplifier and loud speaker. The entire set, except the last two audiofrequency stages, is enclosed in a grounded metal box divided into compartments, one for each tube with its preceding coupling circuit.

Fig. 2: These curves show the performance of the R.F. amplifier with and without the automatic vol-ume control. It will be seen that with three tubes (curve III) the regulation is much more uniform than with two tubes (curve II) or with one tube (curve I).

frequency components of the pulsating rectified voltage. (3) A manual volume control

THIS article explains the principle of a most ingenious device by which it is possible to make a radio set adjust itself to the fluctuations in the strength of the received signal, thus partially overcoming fading, etc. This is brought about through the use of a rectifier circuit, rather than the common amplifying detector; and employing the variations in the rectifier output to vary the voltage on the grids of the R.F. tubes, and thereby their amplification. While the system, owing to the many problems yet to be solved in its operation under present-day broadcast conditions, is yet only in the experimental stage and further data are not available for publication, it is very interesting and will afford the more inquiring constructor an opportunity to study a very novel circuit action. -EDITOR.



Fig. 1 shows the essential circuit details pertaining to the control system. The direct component of the rectified voltage, free of audio-frequency variations, is applied to the grids of the first three tubes. If the radiofrequency-rectifier voltage could exceed a value of about ten volts, this automatic grid bias would thereby cut off the signal through the radio-frequency amplifier; so the rectifier voltage cannot exceed this value.

RESULTS OBTAINED

Fig. 2 shows graphically the performance of the radio-frequency amplifier with and without the automatic control. With the system described, the rectifier voltage and audio-frequency voltages are nearly independent of the antenna voltage, when the latter exceeds the threshold value. The curves 1, 2 and 3 show the performance of the system when the automatic grid bias is applied to one, two, or three tubes, respectively, of the radio-frequency amplifier.

The degree to which the signal can be cut off in one tube is limited by two factors. First, any error in neutralizing the gridplate capacity permits signal current to pass



through the tube, even when its mutual conductance is zero. Secondly, the sharp bend in the plate-current-grid-voltage curve causes distortion of a strong signal on the grid, when the mutual conductance is reduced too far by the grid bias. In view of such limitations, it is undesirable to reduce the amplification ratio per stage below about 1/10 of its normal value. When controlling several tubes, these limitations become unimportant. The last radio-frequency stage is not controlled because it must supply as high as ten volts to the rectifier.

DISTORTION AVOIDED

The properties of the two-element rectifier contribute largely to the simplicity of the control system. Fig. 3 shows the nearly linear proportionality between alternating and rectified voltages in this form of rectifier, as contrasted with the irregular performance of the three-element detector. The signal modulation is rectified without distortion. Also the average rectified voltage is equal to the carrier voltage rectified; (Continued on page 1156)

A Really Portable Radio Set

An Efficient Little One-Tube Receiver, Which Weighs Less Than Four Pounds and Can Be Slipped Into an Automobile Side Pocket, Is Easily Made of Old Parts

By J. B. Armstrong

OST of the so-called "portable" radio receivers which the writer has seen are portable in about the same sense that a steamer trunk is; that is, you can put a handle on the latter and drag it around with you. It is easy enough to compress the parts of a four- or five-tube set, or even those of a superheterodyne, into a box about the size of a lady's overnight bag; but, after you've installed half a dozen dry cells and at least two "B" battery blocks and attempted to carry the outfit a few blocks, you will lose your enthusiasm for portable radio and drop into the nearest drug store for a bottle of muscle liniment.

The writer has designed a portable radio receiver which is really portable in that it can be carried in one hand and will not cause drooping of the shoulders. It weighs less than four pounds, *complete with batteries;* so a description of it will undoubtedly be of interest at this time of the year, with Spring not so far away, and the call of the open faintly audible in the distance. The metal case for this receiver measures 7 x $4\frac{1}{4}$ x 3 5/16 inches and is made of aluminum 1/16-inch thick. The long sides are flanged over and screwed to the ends, and the bottom is attached with angles.

DISPOSAL OF BATTERIES

Referring to the sketches of the set, A and B are the "A" and "B" batteries, which are used to operate a UX-199 tube fitted into the UX socket shown at D. The "A" battery consists of two of the larger unit cells used for flashlights; these are connected in series and held in a special compartment composed of two bakelite end pieces separated by two sides of aluminum. This compartment is fastened to the case by machine screws going into one bakelite endpiece, as shown in the sketch at point X, top view. The lower cell goes into the compartment with the "+" terminal towards the side of the box to which the compartment is fastened. The upper cell goes in with the "+" terminal facing the other way. This arrangement is used in order to allow



The two clips marked R (side view) make contact with the binding posts on the "B" battery block. The 199 tube fits in the socket D, occupying the corner formed by the tuning coil O and the "B" battery B. The other symbols in these drawings correspond with those in the illustration and diagram on the opposite page.

It is evident from this illustration that the portable radio set described in the accompanying article is really portable. The whole instrument weighs less than four pounds and can be easily carried with one hand.

the cells to be connected in series with a strip of bronze screwed to the bakelite end piece on the side of the box. These bakelite end pieces should have a groove running from top to bottom, to leave room for the brass ferrule of the terminal to slide into the compartment. The series bronze strip is screwed into the groove in the bakelite on the box side; this is done in order to allow the "+" and "--" terminals of the battery compartment to come out conveniently for wiring. The bronze connector is bent outwards from the bakelite to make contact with the lower cell's "+" terminal and the upper cell's "--" case. Two separate clips are screwed to the other bakelite strip of the compartment to form the "+" and "--" terminals of the battery compartment.

The "B" battery consists of a single 221/2volt block of the smallest size. It goes into the box upside down and connects with bronze clips screwed to a block of wood M, fastened to the bottom of the box with wood If these clips R, are bent, Uscrews. shaped, the lower side of the U can be used as a lug to which is soldered a connection as shown in the sketch, side view. The wooden block is made to fit close between the "B" battery terminals so that, because of the difference in spacing of the terminals from the edge of the battery, it can be connected in only one way; insuring correct polarity.

PLACEMENT OF PARTS

The grid condenser, of .00025-mf. capacity, is shown at G; it is screwed to the side of the box before the bottom of the box is attached.

A .001-mf. fixed condenser F is screwed to the bottom of the box and used as a radio-frequency by-pass condenser.

The variable condenser, C, is of .00035nif. capacity; any condenser of this size may be used providing its spread will not exceed the depth of the box when it is rotated. The condenser is secured by small brass angles, four in number, which are fastened to it by using longer assembly screws. The frame and rotary plates are thus connected to the box and so to ground and "A+" and "B-". The condenser is controlled by the knurled disc H of 1/16-inch aluminum, which projects through a slot in the lid of the box. To allow it to project only through the lid, the center line of the shaft of the condenser must be above the half-way line of the box by an amount equal to the distance the disc projects. No clearance need be allowed, between the frame of the con-denser and the "A" battery compartment, if the condenser is fitted with countersunk assembly screws and the bearing parts are sawed off flush with the frame as shown. A paper dial can be borrowed from some old vernier dial and cemented to the aluminum disc with household cement or collodion. The figures on the dial are read through a window in the side of the box, under the handle.

A filament switch L, which is mounted on a brass plate, consists of a brass sliding member with a cross bar which slips beneath two small spring-bronze strips, one of which is grounded to the supporting plate. The other strip is screwed to a piece of bakelite and so insulated from the base. The sliding member slides through two brass bridges milled to fit and is bent over at right angles on the top to provide a grip. The switch is "on" when pulled out, and can be made flush when "off;" although this necessitates opening the box to turn the tube on. This filament switch is the only control used on the tube filament; as the two unit cells give the proper voltage without the use of a rheostat, and should be discarded when the tube will no longer function. This will be usually after approximately one hundred hours of service.

THE CIRCUIT

Now we come to the tuner; this consists of three coils, used in the conventional regenerative circuits as primary P, secondary O, and tickler J. The secondary, O, was wound first, using as a form, a cardboard tube such as comes around the large unit flashlight cells; it consists of a two-layer banked winding of No. 28 enameled cottoncovered wire, 1¼ inches long, and held in place by celluloid cement. No taps were brought out, as the tuner was found to cover the broadcast band nicely, with the .00035-mf. condenser.

(Editor's Note: Ordinarily it is against the policy of RADIO NEWS to publish hookups or descriptions of plain regenerative receivers, because of their obnoxious property of causing interference in neighboring sets. This portable receiver is excepted from the ban, as it is unlikely to be used in crowded districts.)

The primary, which is wound directly over the secondary on the filament end, which is nearest the tickler coil, consists of three turns of No. 22 D.C.C. and is untuned.

The tickler coil consists of a winding 7/16-inch long, of No. 28 S.C.C. wire in two layers (not hanked, simply one over and then back on the first layer) on a bakelite tube 7/8-inch in diameter. Two pig-tails covered with soft sleeving are brought out from the coil of stranded wire. To rotate the tickler, the disc N, of 1/16-inch aluminum, is used with a tight-jointed brass angle support Q, which is clamped at K to the disc shaft and screwed to a bakelite end piece cemented into the coil form. The control disc has bearings in a U-shaped brass strip fastened to the bottom of the box. The shaft has a shoulder turned on each end, to keep it from sliding out of the hearings; and the bearing strip itself is split and sprung to take up all play.

Four binding posts are mounted on the

condenser end of the box and insulated with fiber bushings and washers, with the exception of the ground post, which is mounted right on the aluminum case without insulation. Two of these posts are connected to aerial and ground respectively, the other two being phone connections in the plate circuit of the tube. This brings one pest at 221/₂ volts above ground with the tube filament also grounded; so that the tube



The complete wiring diagram of the portable receiver. The extra phone coil prevents damage to the tube filament, in case of an accidental short-circuit.

would be burned out in case the post should be accidentally connected to the box, as when inserting the phone tips, etc. To get around this difficulty, there should be mounted within the set (under the variable condenser) an old headphone coil, of approximately 500 ohms resistance, which should be connected in series with the "B+" battery circuit. This will limit the shortcircuited current to a harmless value, yet not impair the operation of the set.

ACCESSORIES

A handle, such as that supplied for a hand bag or small suit-case, was procured from a leather-goods store and fastened to the box with small metal clips, as shown; the set complete with batteries weighs 3 pounds 91/2 ounces. It is completely shielded and may be handled while tuning in stations without the slightest body-capacity effect. It has brought in broadcasting over distances of 1500 miles on a good antenna during the summer months. A single-turn loop 24 inches in diameter works excellently with this little receiver; it is connected across the primary coil as with a regular antenna. Station WGY has been heard very clearly with this type of antenna and receiver over a distance of twenty-five miles; at a distance of six miles, it comes in loudly enough on an outdoor aerial to be heard across the room on a loud speaker without amplifiers. Carrying the set with one hand and using a loop consisting of three feet of wire laid across the shoulders and hanging vertically, one may hear broadcasting from WGY while walking about-if insane enough about radio to try it. (Yes, the writer has tried it.)



A view of the portable set with the cover opened. H and N are the dials which control the tuning condenser C and tickler coil J, respectively. F, by-pass condenser; A, filament batteries; L, filament switch; O, secondary coil; D, tube socket.





What Constitutes Tone Quality?



Part II of an Article in Which is Considered Sound Reproduction and its Relation to the Reception of Radio Broadcast Signals

By Robert Neil Auble

I T was pointed out in the first part of this article, which appeared in March RADIO NEWS, that a radio set may be regarded as perfect only when the sound reproduced at the loud speaker is faithfully like that originally produced before the microphone. This involves the problem of insuring that every fundamental tone and every overtone sounded before the microphone may be reproduced at the loud speaker, with emphasis unchanged and without the intrusion of any other sound whatever.

While it is no doubt true that the relative emphasis of the various partial tones must be preserved in the ideal transmitting system, it is also possible, however, that a transmitting system may fall somewhat short of this ideal without objectionable results. Certain types of extraneous sounds must apparently be always present in any soundreproducing system-as needle noises in the phonograph, line noises on the telephone, static and other background noises on the radio. Still, it is obvious that, in amplifying radio speech and music above the general noise level, the idea will be to amplify all the partial tones to the same degree. Certainly no radio set designed up to this time may be regarded as perfect in this respect.

So many factors are involved, and so many difficulties are encountered, that it is nothing short of miraculous that radio speech and music are so deceptively like the originals. Very fortunate it is that so few of us have cars so delicately attuned to sounds that we are able to find any fault at all.

"CHARACTERISTICS"

It has been shown by various investigators that no reproducing instrument yet devised is capable of amplifying with equal efficiency all the possible frequencies within the range of hearing. The amplification curves of even the best horns, for example, show very great



A series of resonance pipes of the above general dimensions would reproduce tones for which they were especially designed, but no others, with full efficiency.

irregularities. Horns usually amplify the upper ranges of frequencies more or less satisfactorily, but give only selective amplification to the lower frequencies. Cones amplify the lower frequencies more efficiently, but fail usually to handle the upper tones so well.

To simplify the discussion of quality, it is desirable to remember that the transmitting unit is essentially a device to convert the energy of sounds produced before the microphone into electrical energy; and that it is with *electrical* energy with which we are concerned until the coil windings of the loud



Two types of modern loud speakers. The exponential horn at the left has a chamber approximately nine feet long, with an opening 18 x 24 inches. The cone-type speaker at the right is 24 inches in diameter and has five points of suspension.

speaker are reached. Obviously, there is possibility of change of quality—"distortion"—at every point: any imperfection in the microphone, any fault in the amplifying and modulating systems at the broadcast station, any atmospheric disturbances between the transmitting aerial and the receiving aerial, any faults in the tuning circuit, the detector circuit, or in the audiofrequency amplifier of the receiver—all of these will modify the wave form of the electrical energy delivered to the loud speaker and introduce changes in the sound waves into which the electrical energy is converted by the loud-speaker unit.

We do not intend to go into any extended discussion of the electrical factors enumerated above, since the whole science of radio design is involved. It will be sufficient here to state that almost any welldesigned radio set now on the market, if properly handled, will deliver to the loud speaker electrical energy whose wave form is practically identical with that which left the antenna of the broadcasting station.

DISTORTION IN THE SPEAKER

Loud-speaker design has not, however, kept pace with the design of other radio units. As was mentioned above, most of the horn-type speakers amplify the higher partials well enough, but do not handle the low notes efficiently. And without the support of the strong bass notes, the principal charm of music is lost. The writer has frcquently heard through radio receivers orchestral arrangements which seemed pitched a full octave higher than the musical score indicates. The horn was failing to deliver any of the fundamental notes, leaving the listener to depend entirely upon the overtones. Such loud speakers are especially cruel to the voices of male speakers, whose voices are robbed of the sonorous tones of the lower register which give them their character and identity.

On the other hand, the cone and drum types of loud speakers so emphasize the lower tones that speech and music acquire a disagreeable rumbling character, resembling the sound of thumping on an cupty barrel.

A horn is essentially a resonance chamber which amplifies the sound of the loudspeaker diaphragm, by virtue of the fact that the air column confined within the horn is forced into vibration in unison with the diaphragm. If the horn were cylindrical in shape, it would respond only to sounds whose wavelengths are twice the length of the tube, or to sounds whose wavelengths are such that the tube is exactly one-third, one-fourth, one-fifth of them, and so on. For example, if the tube is approximately 27 inches long it will respond to middle C (256 vibrations per second), to C' (=512), to G' (=768), etc. The intermediate tones are not amplified. Since a cylindrical resonance tube responds only to selected sounds, to reproduce the whole range of audible sounds with cylindrical resonators would require a series of resonance pipes like a concert pipe organ. Such a "loud speaker" would, of course, be out of the question in the average residence. A sketch diagram of a possible loud speaker of this type is given in Fig. 8.

Such a loud-speaking unit as represented would efficiently amplify only the tones



A cross-sectional view of a sound-amplifying horn designed by Dr. A. L. Foley, of Indiana University.

which are harmonics (even multiples) of the major scale (without the "semitones") beginning with C = 32 vibrations per second. This would include most of the notes ordinarily used in music, but even so, would not be completely satisfactory, unless the instruments at the broadcast studio were tuned to physical pitch and unless the temperature in the studio were the same as in the room containing the speaker. Under such conditions the device would be highly efficient.

THE "EXPONENTIAL" HORN

Fortunately, however, the effect of a multiple series of resonance pipes may be secured by gradually increasing the diameter of the tube from its mouth outward toward the bell. If such a horn is used the sound waves are internally reflected so that the tube becomes less and less selective; *i.e.*, it becomes resonant for an increasingly large number of tones, the fundamental tone, however, remaining the same as that of an open cylindrical tube of the same length. A simple straight "conoidal" horn having a *logarithmic* rate of increase in its diameter from vertex to bell, will respond to practically all the audible frequencies; provided its length is of the order of twenty-five to thirty feet.

A horn of such length would be unwieldy, and despite its superiority over every other type of amplifying horn, must give way to less cumbersome, though less perfect horns in the average home.

If a horn, such as described above, be curved more or less abruptly the number of internal reflections is increased, making it possible to reduce the length without diminishing the number of frequencies to which it will respond. There is, however, a considerable loss of energy at such points of curvature, unless the amount of curvature at each point be exact. The superiority of certain horns now on the market is principally due to a better calculation of the curvatures.

But no matter how perfectly the curvatures are calculated, there is a lower limit to which the length of a horn, measured along its axis, may be reduced. So many horns, answering the demand for reduction of size to the dimensions of the cabinets in which they are to be placed, cannot respond to the lower notes adequately. Music heard through such horns lacks depth and character. The melody and harmony may be ever so brilliant but, without the background of the bass notes, the final product seems shallow and uninteresting. The basses are like the background of mountain and forest, over which the strings and woodwinds play with all the gorgeousness of a beautiful sunset.

ACTION OF THE CONE

The cone type of loud speaker depends upon another principle of sound amplification. The loudness of a sound, at a given distance from its source, may be increased by increasing the amplitude of the vibration (increasing the actuating forces), or by increasing the area of the vibrating object. The cone accomplishes its purpose by substituting its larger surface for the small diaphragm, which is the source of sounds in the horn type of speaker.

Such a large vibrating surface disturbs a much larger volume of air than is possible with the diaphragm, so that the amount of energy reaching the ear is increased without the use of amplifying horns. The material of the cone must vibrate in munerous irregular segments if it is to amplify all the elements of the complex tones. The cone is a modified Chladni plate, such as was described in Part I. As pointed out there, the higher the frequency of the note sounded, the smaller must be the vibrating segment. Since the factors of texture and elasticity establish a limit to which the segments may be reduced, such a vibrating cone cannot amplify sounds whose frequencies pass a fixed upper limit, if it is at the same time to amplify the bass notes, for which it is especially suitable. The absence of the upper partials in sound reproduced by a cone gives it the peculiar "empty-barrel" effect.

It is now evident that it would be desirable to combine the advantages of the cone with those of the horn. The writer described one possible scheme for accomplishing this result (RAMO NEWS, October, 1927), by means of an ordinary loud-speaker unit, so arranged that the diaphragm actuates the drive-rod of a cone on its lower surface, while the upper surface is open to the conventional horn.

A much better arrangement has been designed by Dr. A. L. Foley, of Indiana University (*Proceedings of The Indiana Academy of Science*, 1926, p. 131). Dr. Foley constructs a horn of massive elastic material, so curved and with such a rate of increase in its diameter that the best advantages of the horn are retained. Within the horn, and forming one wall of the air passage, is placed a sounding board of thin elastic material (see Fig. 9). The sounding board preserves the amplification ratio for the lower notes, while the horn amplifies the upper notes, as explained above. Dr. Foley describes the action of his horn, as follows:

"The cross-sectional area of the passage P being relatively small, the sound waves (compressions and rarefactions of the enclosed air) tend strongly to produce vibrations of the walls of the passage. The two side walls W and the lower wall L arc massive and stiff. The upper wall, called the vibrator, V, is of thin clastic material and is of such a shape that it can readily vibrate in unison with the sound waves passing underneath. The vibration of V sets up waves which pass across the horn (transverse to the horn's axis), where they are again transversely reflected by the top T to the vibrator board. Several such reflections may take place before the waves finally emerge at B. This multiple reflection again greatly increases the effective length of the horn and increases the frequency range of resonance.

"Note that the wider end of the vibrator is at the rear end of U and that it naturally vibrates at a lower rate than the narrow

(Continued on page 1179)



A gigantic exponential horn made in 1922 for the purpose of studying sound waves in this type of horn. It is capable of amplifying the lowest audible tones.

Controlling Volume in Your Receiver



An Explanation of the Respective Merits of the Methods of Controlling Receiver Volume by Means of Variable Resistors



HE method by which volume is to be controlled in a radio receiver deserves a considerable amount of attention. When listening to a local station it will be usually found necessary to utilize this control on the receiver to reduce the signal somewhat, so that the reproduced program will not be too loud. Therefore, the method used should be one which will regulate the volume without affecting the performance of the receiver in any way.

We may define the ideal volume control as one which will control the volume output of a receiver without affecting in any manner the receiver's selectivity or fidelity of reproduction. Few of the methods usually adopted measure up to this standard; but there are several which are quite satisfactory. In the following paragraphs we will indicate the characteristics of the various types; so that the reader will be able to determine, by examining his receiver, whether that employed is really the most satisfactory one.

To make our discussion systematic, we will begin by dividing volume controls into two broad classes, according to their positions in the circuit. The first group will include all the methods whereby the volume is controlled by some device in the radiofrequency circuit. The second group includes all controls that function in the audio-frequency circuits.

METHODS IN THE R.F.

In Fig. 1 is shown a conventional circuit consisting of two stages of tuned-radiofrequency amplification, followed by a nonregenerative detector. In this single circuit we have indicated five volume controls, as follows:

(A) A variable resistor across the primary coil (P) of the antenna coupler.

(B) A variable resistor in series with a tuned circuit.



Three methods of volume control in a transformer-coupled audio-frequency amplifier are shown at F, G and H.

By John B. Brennan Jr.

(C) The filament rheostat.

(D) A variable resistor in series with the "B+" lead to the R.F. tubes.

(È) A variable resistor across a tuned circuit.

Method A, utilizing a variable resistor of about 200,000 ohms connected across the antenna coil, is generally quite satisfactory. no coil pick-up, or unless the receiver is being operated at a point sufficiently distant from the nearest broadcast transmitter so that there is negligible pick-up by the coils.

You can determine whether this effect will be bothersome by disconnecting aerial and ground and tuning the set to receive the station whose signals are normally the loudest.



Five different methods of controlling the volume are indicated by letters in this diagram of an R.F. amplifier and non-regenerative detector.

However, if the receiver is unshielded and is being operated close to one or more broadcast stations, it is possible that the coils themselves will pick up quite some energy; and therefore the output of the receiver will not be zero even when the volume control is set for zero resistance. This is a distinct disadvantage, for the control is not effective on those stations (powerful nearby locals) where it is most essential. This type of volume control is not recommended unless the receiver is shielded so that there is Under these conditions a good healthy signal indicates that there is coil pick-up, and volume-control method A should not be used.

A resistor in series with one of the tuned circuits, as indicated at B in Fig. 1, is frequently an effective means of controlling volume where the selectivity problem is not severe. When resistance is introduced into a tuned circuit the selectivity of the circuit is seriously reduced, and it is possible that interference will be experienced between stations operating on adjacent channels.

REGULATING "A" AND "B" VOLTAGES

A rheostat controlling the R.F. tube filaments (C, Fig. 1) is frequently used as a volume control and really proves very satisfactory, except, of course, with A.C.-filament tubes. As the filament current is reduced, the emission from the filament is decreased and the resultant increase in the plate impedance of the tube causes the amplification to decrease; the signal finally reaching the detector is thereby reduced. It is a good idea, when such a control is used, to place a fixed filament resistor R (Fig. 1) in series with the volume-control rheostat. This resistor protects the tubes from an overload of filament voltage for then, even with the rhcostat resistance all out, the filament voltage is limited to the correct value for the tube.

Since this control functions by limiting

TABLE OF RECOMMENDED RESISTANCE VALUES FOR VOLUME CONTROLS

		Avera	ige Value in	
See Fig.	Position of Resistor	Ohms	(Maximum)	Characteristics
(1 A)	Across antenna coll	• • • • •	200,000	Very good, except for an unshielded receiver in a congested broadcast area.
(1 B)	In tuned R. F. circuit		400	Decreases selectivity.
άčί	Filament rheostat		†	Very good.
(1 D)	In series with R, F, "B+" lead		200,000	Satisfactory with most types of receiver.
(1 E)	Across tuned R. F. circuit		200,000	Decreases selectivity.
(2 F)	Across A. F. T. primary		100,000]	
ίζĠ	Across A. F. T. secondary		500,000	These methods are generally less satisfactory, as
$(\bar{3},\bar{A})$	*Potentiometer-grid leak		500,000 }	they permit the detector and A. F. amplifier to
(3 B)	*Variable grid leak	1	000,000	be overloaded by strong signals, with consequent
ά ií	Across loud speaker		25,000)	distortion.
*1n	resistance-canacity-coupled A. F. all	nplifier.	. †1	Depends on number and types of tubes.

the emission current, thereby increasing the plate impedance of the tube, it follows that it must produce some distortion. By experience, however, we know that the distortion created is not generally noticeable and the method can therefore be considered a good one

At D in Fig. 1 we have indicated another volume control arrangement which functions by lowering the amplification in the R.F. amplifier through a reduction of the plate voltage. When this type of control is used, a by-pass condenser (BP) should always be connected from the " Λ —" to that side of the variable resistor or leading to the primary of the R.F. transformer. The condenser should have a value of .005-mf. or more.

Method E, utilizing a variable resistor across a tuned circuit, falls into the same class as method B. A resistance of given value across a tuned circuit is equivalent to a smaller resistance connected in series with the tuned circuit. Methods B and E therefore fall heir to the same objections and neither of them can be considered a really satisfactory method of volume control. This completes our story on volume controls functioning in the R.F. portion of a re-The various controls listed are eciver. grouped in the table; you will find listed there the major facts concerning each method.

	congested broadcast area.
 400	Decreases selectivity.
 †	Very good.
 200,000	Satisfactory with most types of receiver.
 200,000	Decreases selectivity.
 100,000	
 500,000	These methods are generally less satisfactory, as
 500,000	they permit the detector and A. F. amplifier to
 1,000,000	be overloaded by strong signals, with consequent

) distortion. †Depends on number and types of tubes.

IN A.F. CIRCUITS

We now come to the method of controlling the volume by means of some adjustment in the audio amplifier of a receiver. First, let sistance across the secondary of a tra former being equivalent to a lower resis. ance across the primary. The method used is optional, the major difference being that a variable resistor across the primary for volume control should have a maximum value of about 100,000 ohms, and a resistor across the *secondary* should have a value of about 500,000 ohus. Method II is not satisfactory, except in special cases; as, for example, when the receiver is located some distance from the loud speaker.

Volume control in a resistance- or impedance-coupled amplifier can easily be accomplished by using a high-resistance potentiometer (Fig. 3, A) or by simply using a variable high resistor for the grid leak



Two ways of controlling the output volume of a resistance-coupled amplifier. A-potentiometer-type grid leak; B-straight variable grid leaks.

us consider a two-stage, transformer-coupled amplifier (see Fig. 2). Here we have indi-cated three controls, F, G and II. Methods F and G are really similar; a very high re(Fig. 3, B). The method indicated at A is somewhat preferable if a high-resistance potentiometer with a resistance value from (Continued on page 1158)

How Powerful a Tube Does Your Set Need?

'S exceedingly high plate voltage necessary for high quality in radio reproduction? Many set owners, noticing the numerous constructional articles dealing with "B" power devices having an output of 500 or more volts, and designed for use with power tubes of the 210 type, are perhaps inclined to believe that real quality can only be obtained through the use of these voltages and tubes.

This, however, is not always the case. A moderately powered amplifier, using tubes of the 112 or 171 type with plates supplied from a 150- or 180-volt source, can, in most circumstances, give results that will satisfy the most critical. The main advantage to be expected through the use of higher power is a gain in volume and the increased realism that comes in having, let us say, the volume of an orchestra, as it comes from the speaker, equal or exceeds that of the orchestra itself. However, it is obvious that the average set owner is not desirous of having a twenty- or sixty-piece orchestra going full tilt in his or her living room. In a small room-and many rooms are small nowadays-this would be unpleasant, even painful. Therefore, an amplifier capable of giving this volume could seldom be used.

USE OF SMALLER TUBES

Now in a case like this, where quality, rather than quality plus tremendous volume, is the primary consideration, there is nothing to be gained by the use of very high power, To be enjoyable, the device of very high voltage would of necessity have to be operated at a point considerably under maximum output. If a proper means of controlling this volume were used, the quality would not suffer; but it would not be better than the maximum output of an amplifier more in accordance with the tastes of the average set owner and the acoustical capacity of his home.

Of course, there is no denying the fact that power and fidelity in reproduction are, up to certain points, closely associated. The set owner should remember, however, that a moderately-powered amplifier puts every bit as much energy into the loud speaker as a very-high-voltage device operated at a fraction of its volume. In the latter case, the energy, as expressed in the A.C. variations of the plate current, remains in reserve, or is dissipated by means of the volume control. When control is attempted by means of reducing the filament voltage, or through slightly detuning the set, the re-

sults, particularly in the case of the highvoltage amplifier, are far from satisfactory. In the case of sharply-tuned receivers, scrious distortion results from the suppression of the side bands when the set is defined; while extraneous noises, static, line disturbances, etc., are amplified out of all proportion to the signal.

VOLUME OF QUALITY

In the last analysis, quality in the reproduced signal is not so much a matter of volume as of freedom from overloading. Were it purely a matter of amplification, tubes of the 201A type, or the "high mu" tubes, would be far superior to those of the 171 and 210 types. The superiority of the power tube lies, not in its ability to amplify, but in its ability to handle great volume without overloading.

When, for example, a tube of the 201A type is used in the last stage of an amplifier with, let us say, 90 volts on the plate, the sounds issuing from the loud speaker are apt to be thin and with the tones in the lower end of the musical scale missing. Now, as we increase the plate voltage, the quality of reproduction improves until a

(Continued on page 1161)





By Herndon Green

F an investigation were made, of the various steps which have been taken in the progress and development of radio receiving sets, an interesting story would unfold itself. Even our now-commonplace "B" battery has behind it some interesting history which, to the majority of broadcast listeners, is unknown.

Toward the end of the crystal-detector era, when attention was turning to the de Forest bulb and the audiotron, there was no such unit as a $22\frac{1}{2}$ - or a 45-volt "B" battery. A set-builder who was so bold as to employ one of these new-fangled tubes relied chiefly on a bank of $4\frac{1}{2}$ -volt flashlight cells for his plate supply. Today we have quite efficient heavy-duty "B" batterics; but still the quest goes on for something in the line of "B" power-supply devices with which to obtain "B" potential for the tubes in a radio receiver, via the light socket.

The last few years have seen great strides of progress in the "B" socket-power field. In fact, the advance has been so rapid as to leave the majority of listeners-in without an understanding of the principles embodied in these devices; with the result that unscrupulous manufacturers and dealers have unloaded on an unsuspecting public a great deal of worthless and useless junk labeled as "B" power-supply apparatus. It is the aim of this article to acquaint the readers of RAMO NEWS with a simple, non-technical explanation of the function of the component parts of a representative "B" power-supply device.

THE HOUSE CURRENT

If our houses were powered with direct current, of say, 180 or 220 volts, there would probably be no need for any more complicated device than a smoothing or filter device and a voltage divider; so that various lower values of voltage might be obtained in addition to the voltage value of the house supply. (An assembly of similar nature was described in RADIO NEWS for January, 1927). However, in only a few sections of the country is direct current available, and then it is usually not of sufficient voltage to be useful as a "B"-battery substitute. Alternating current is decidedly cheaper to distribute than direct; but with alternating current we encounter a number of conditions which make its ultimate use for powering a receiver somewhat complicated.

The voltage that is supplied to the plates of radio vacuum tubes must be of a directcurrent nature, be steady in value, and free of pulsations that produce hum. Alternat-



The action of a filter unit may be likened to that of a system comprising a pump, a tank and a discharge tap. The tank stores up the periodic charges and discharges them in a steady stream.

ing current is usually considered as steady in value, not fluctuating appreciably; but it is not of direct-current nature and it does produce considerable hum. Therefore, in utilizing alternating current for a "B" substitute, a number of electrical changes must take place before it is satisfactory for use.

In the first place, the line-voltage of a house supply is usually too low for immediate use. When a receiver employs a power tube of the 171 variety, at least 180-volt "B" potential is desirable and a 40.5-volt



"B" and "C" voltages from a "B" powersupply device is not difficult; yet immediately we see that at the output of the device at least 220 volts are required. Since this is just double the value of the line or house voltage, a transformer unit is employed to "step up" this line voltage. Engincers can, by calculation, determine the electrical and physical dimensions of a transformer that will step up the line voltage to a predetermined value. Now, one step of progress has been made toward the ultimate goal, that of changing the lowvalue alternating-current to a higher value, suitable for use as "B" supply. Yet, even in its stepped-up state, the alternating current is not immediately suitable for use. It is necessary to change the A.C. to D.C., this operation being accomplished by a "rectifier" unit (see Fig. 1).

"C" battery is employed. To obtain both the

SMOOTHING OUT THE CURRENT

Rectifiers may roughly be divided into three classes: chemical, gaseous and thermionic. While they operate somewhat differently, they produce the same general results, and have the same purpose; that is, they pass current in one direction only, thereby changing an applied A.C. to a pulsating D.C. While rectifiers generally take the form of one of the three types mentioned, it is possible that any of these three may be of the "full-wave" or the "halfwave" type of rectifier. In the half-wave rectifier only half of the alternating-current impulses is used, as illustrated in Fig. 2A. In the full-wave type of rectifier tube, the elements are so arranged within the tube as to utilize that half of the wave unemployed in the half-wave type of tube; with the result that the number of pulsations in the resulting direct current is doubled; thus making the job of "filtering" not so difficult.

Still, this pulsating direct current is not ready for use. The pulsations would produce a disagreeable hum in the loud speaker; so it is necessary to smooth them out. The unit used for this purpose is called a "filter" and consists of large choke coils and large fixed condensers. The choke coils have the property of retarding the flow of alternating or pulsating current, but quite readily pass direct current; while the condensers act as a storage tank or reservoir, so that the current may build up to a usable value and not immediately dissipate itself, as would be the case if these condensers were not included in the circuit. The action of the filter unit might very well be likened to a tank, which receives at its top a series of charges of water from a pump. The tank stores up these periodic charges and then, through an outlet at its bottom, discharges the water in a strong, steady stream (see Fig. 3).

Three of the four necessary steps have

1138

half-wave rectification.



In this schematic diagram we have indicated the use of a thermionic rectifier tube for converting the A.C. to pulsating D.C. Appropriate circuit constants are given.

now been described. That is, the original 110-volt alternating current has been stepped-up, it has been rectified or changed to a pulsating direct current, and finally it has had these pulsations eliminated or ironed out by means of a filter system; leaving only pure, non-pulsating direct current of the correct voltage value.

DIVIDING THE VOLTAGES

Now if only one value of "B" voltage were required by a receiver, the job would end here; but the various tubes in a receiver require different values. For instance, the radio-frequency amplifier tubes may require 67 or 90 volts; the detector may operate most satisfactorily at 45 or 67 volts; the first audio amplifier may take 90 volts and the final or power stage may require 135 or 180 volts-depending on whether a 112 or a 171 type of tube is em-ployed here. Therefore, it becomes necessary to utilize the maximum output of the "B" power-supply device in order to make possible the use of these intermediate values of voltage. This is best accomplished by means of a series of fixed or variable resistors located in the circuit, directly across the output terminals of the filter section.

It is one of the laws of electricity that, if a resistance R be placed across a source of voltage, E, as in Fig. 4, any intermediate value of voltage (Es) can be obtained. This will vary from zero to maximum volts, depending upon the position of the movable contact arm C; it will be least when this arm is brought nearest to the negative side of the output. This "potentionicter" principle is applied in the "voltage-divider" units employed in "B" power-supply devices; with the addition that, not alone one conlact arm, but as many as there are intermediate voltages required are used. Usually the resistance does not consist of one unit but of several individual units, as shown in Fig. 5.

THINGS TO SEE TO

To recapitulate: there are a number of requirements which the several units comprising a "B" power-supply device must possess. In the matter of the transformer, one should be selected that is well made, mechanically, and has sufficient windings, not only for the "B" supply, but also for the rectifier tube (should the latter be of the filament type). and for the filament of the power amplifier tube.

The rectifier tube should have a guaranteed life of 1,000 hours or more; it should have the proper current rating in milliamperes to insure its suitability for use with the other apparatus employed. Nowadays it is



These two diagrams illustrate how different voltages are obtained from the maximum output of the rectifier.

possible to purchase rectifier tubes which are entirely satisfactory for use in "B" power-supply devices and have current ratings ranging from 85 milliamperes to 300 and 400 milliamperes; the latter type is suitable for " Λ " or filament-current supply.

In the filter unit, caution must be exereised in choosing the condensers and chokes which go to make up this very important part of the complete device. The chokes should have a sufficient current-carrying rating, in excess of what will ultimately be drawn from the "B" device, so that at no time is its carrying peak reached. When the current rating of a choke is exceeded it rapidly decreases in inductance value, and does not then measure up to the requirements of a satisfactory choke.

High operating-voltage rating of the filter condensers is essential to the successful opcration of a "B" power-supply device. Here again, as with every part of the device, reliable apparatus should be employed. A rating of 600 volts, D.C., for the condenser nearest the rectifier part of the circuit is not too great, and lower operating-voltage values for this particular condenser should be avoided. The condensers in the remainder of the filter circuit may be of the 400-volt rating.

In the voltage divider, we are presented with the problem of selecting resistance units that are constructed in such a manner that they will not only carry the maximum current under full load but also dissipate the heat generated by the passage of the current through them. There are a munber of types of resistor now obtainable, which fall generally into two classes: (1) the wire-wound type; and (2) the earboncompression type.

In summarizing, we find that all A.C. "B" power-supply devices can be analyzed as follows: first, there is a transformer which steps up the line voltage to a value in excess of what will ultimately be employed at the output (this high starting voltage is necessary hecause of voltage "drops" in the rectifier and filter systems): secondly, there must be a rectifier, of either the half- or full-wave type, which converts or changes the stepped-up alternating current into pulsating direct current; thizdly, there is a filter system which smooths out the pulsations and acts as a storage tank or reservoir; and fourth, there is a voltagedivider system wherein the use of variable or tapped resistors makes available intermediate values of output voltage, satisfactory for application to the plate of the different tubes in a radio receiver.

In Figs. 6 and 7 are shown representative "B" power-supply circuits, employing the thermionic and gaseous types of rectifiers.



A gaseous tube, RT, is the rectifier used in this "B" socket-power unit. Appropriate values for all parts are given.

How to Pick An Audio Amplifier

An Elementary and Unbiased Discussion of the Resistance-Capacity, Impedance-Capacity and Transformer-Coupled Types



UDIO-FREQUENCY amplifiers fall into three principal classes, viz.: transformer-coupled, resistance-capacity-coupled and impedance-capacity-coupled, or combinations or modifications of these three types. During the past few years newspaper radio sections and other radio periodicals have published much propaganda in favor of and against each of the three systems; with the result that the general public is greatly confused on all matters concerning the subject. In this article no attempt will be made to give a

definite solution to the riddle, "What is the best type of audio amplifier?"; but the writer will endeavor to point out the desirable and undesirable characteristics of e a c h arrangement. This information should aid the reader in deciding the particular combination of instruments which will best satisfy his requirements.

In the first place, it should be explained that it is impossible to say that one basic

audio-amplifier circuit is better than another, as every amplifier has limitations or features which may be considered objectionable. On the other hand, with any one of the three types described in this article, it is possible to obtain reproduction which is practically perfect, provided the amplifying units have been correctly designed by an experienced engineer. It is, therefore, necessary for the set builder to sum up all the facts he can learn about each amplifier and then decide which is the most desirable for his purpose.

At first thought it may be difficult for the beginner to understand exactly where the problem lies, if each type of amplifier, when

By Fred H. Canfield

properly designed, is capable of providing the same high quality of reproduction. It should be explained that there are such questions as first cost, efficiency, case of construction, etc., which should be considered. For an example, compare the resistance-capacity-coupled amplifier with the standard transformer-coupled amplifier. In most cases the first cost of the former is much less, but the efficiency per tube of the latter is much greater. Therefore, it may be seen that in this particular instance it is necessary for the owner to decide which is the more desirable feature. But these



Three different types of audio transformers are shown in the above illustration. The two large units are of modern design and are highly efficient, while the one in the center is typical of the old-type instruments, which were small and inferior.

are not the only questions which must be taken into account.

DISTORTION NEVER ABSENT

Before continuing further with this discussion, the writer wishes to correct one impression which seems to exist in the minds of a large number of radio amateurs. The statement has been published frequently, that resistance-capacity-coupled amplifiers do not introduce distortion into speech or music. This is contrary to the fact. No amplifier has yet been developed which is *entirely free from distortion*, even though the actual amount has been reduced to a very low minimum in some instruments. In the case of the resistance-capacity-coupled amplifier the fact, that the resistor units are impartial to the frequency of the currents they amplify, is probably responsible for the "distortionless" claim, but two other possible causes of distortion remain. First, the impedance of the coupling condensers varies inversely with the frequency of the current and as a result the low notes are

not amplified at full yolume; and second, the tube will introduce distortion if it is not operated with the correct bias applied to the grid. Also, overloading any stage of this amplifier will cause distortion, just as in any amplifiers of other types.

Another false impression which the advocates of resistance capacity-coupled amplifiers have tried to establish is that a

transformer-coupled amplifier *must* cause distortion. This is true in the strict meaning of the word, but the authors of the statement tried to create the understanding that the distortion in such units is always excessive. The fact is that, under ideal conditions, the reproduction would be so natural that any further improvement could not be detected by the human ear.

Now that a few facts about amplifiers in general have been made clear the different types of amplifiers may be considered separately. In Fig. 1 there is shown the schematic wiring diagram of a standard resistance-capacity-coupled amplifier. The circuit shown employs three stages, which is



The amplifier illustrated at the left is a standard, factory-built, three-stage, resistance-capacity-coupled unit. At the right is shown



a typical, home-made, impedance-capacity-coupled amplificr. Both units are small in size and furnish very satisfactory reproduction.



Schematic wiring diagram of a typical resistance-capacity-coupled audio-frequency amplifier. RP, plate resistors; RG, grid resistors; C, conpling condensers; V1 and V2, "hi-mu" tubes; V3, power tube; L1-C1, output lilter.

the number usually required for loudspeaker volume,

In circuit arrangement the resistancecapacity-coupled amplifier is very simple. The plate voltages for the first two amplifier tubes (VI and V2) and the detector tube are applied through three resistors (RP). The plate of one tube is coupled to the grid of the tube in the next stage by means of a condenser (C), which prevents the plate potential from being applied to the grid. The resistors RG in the grid circuit of each tube complete the circuit between the grid and filament and make it possible for the grid charges to leak to the filament.

Although the circuit of the resistancecapacity-coupled amplifier is not in the least complicated, the selection of the proper sizes of resistors and coupling condensers, and the use of the proper kind of tubes, is highly important. If the various pieces of apparatus used in the amplifier are not suited to the respective purposes for which they are used, the amplification will be very low or the reproduction will be very unsatisfactory.

RESISTANCE VALUES

In the first place it should be explained that the amplification obtainable from this type of amplifier depends entirely upon the amplification factor ("mm") of the tubes employed. For this reason the 201A-type tube with an amplification factor of 7 is not entirely satisfactory, and a tube of the 240 type, with an amplification factor of 30, should be selected. Secondly, the plate resistors should have as high a resistance as possible and in no case should the value of these resistors be less than the plate resistance of the tube. In the case of the 240 tube the plate resistance is 150,000 ohms and, in order to obtain satisfactory amplification, the plate resistor must have a resistance of at least 250,000 ohms. A third important factor is the selection of the proper plate voltage. Because the resistance of the plate resistor is always greater than the plate resistance of the tube, more than 50% of the plate voltage is wasted in the plate resistor. Therefore, it is imperative that a high voltage be applied to the resistor, in order that the plate shall receive sufficient potential for the efficient operation of the tube. In the case of the

240 tube, with a 250,000-ohm plate resistor, the plate potential should be 180 volts. Under these conditions a grid bias of 3 volts is required.

Probably the most important problem in the design of a resistance-capacity-coupled amplifier is that of the proper values for the coupling condenser and the grid re-sistor. In this connection there are three things which must be remembered: first, distortion is reduced as the capacity of the coupling condenser is increased : second, the amplification is increased as the resistance of the grid resistor is increased; and third, as the values of the coupling condenser and grid resistor are increased, a time log tends to destroy the utility of the amplifier. The time lag is caused by the fact that the grid resistor is unable to discharge the coupling condenser rapidly enough when loud signals are being received and, as a result, the grid becomes blocked.

From the above it may be seen that two conflicting conditions exist which prevent the amplifier from delivering perfectly distortionless reproduction. Of course, the ideal solution would be to eliminate the coupling condenser and grid resistor from the circuit entirely and substitute a "C" battery of the proper voltage at the point marked X; but, as the voltage of the "C" battery would have to be equal to the voltage applied to the plate of the preceding tube, plus the potential required for biasing the grid, this is an impractical arrangement. Therefore, it is usually necessary to select for the coupling condenser a value which does not cause too much distortion, and then to use a grid leak which gives most satisfactory results. The value of the condenser may be as high as 0.1 mf. if great volume is not required from the receiver; but when it is desired to operate a loud speaker with good volume it may be necessary to reduce the capacity of the condenser to .01 mf. The size of the grid resistors must be determined by experiment and the highest value which gives satisfactory results on loud signals should be selected. In many cases it will be found that best reproduction is obtained when a comparatively high resistance is used in the first stage, a lower resistance in the grid circuit of the second stage and a nuch lower resistance in the grid circuit of the power tube. The value of the resistors may vary from 2 megohius to 500,000 olmis.

ELIMINATING R.F. EFFECTS

In operating resistance-capacity coupled amplifiers there are several things which should be remembered. In the first place, amplifiers of this type amplify radio-frequency currents just as well as audio-frequency currents and, to prevent the tubes from being overloaded with R.F. potentials, it is essential that a radio-frequency choke coil shall be connected in the plate circuit of the detector tube. Also, a small by-pass condenser (approximately .002 mf.) should be connected between the detector plate and the filament. Secondly, if a power tube of the 210 or the 171 type is used in the last stage, an output filter or output transformer of some type should be connected in the plate circuit to protect the windings of the loud speaker from the large value of plate current used by the power tube. Thirdly, an efficient source of "B" supply must be employed and, if a "B" power unit with a high output resistance is used, special precautions must be taken to prevent "motorboating." These are discussed later.



The circuit arrangements of a typical impedance-capacity-coupled audio-frequency amplifier. LP, plate impedance units; RG, grid resistors; C, coupling condensers; V1, V2 and V3, vacuum tubes; L1-C1, output filter.

Lastly, best results will usually be obtained when a 240-type tube is used in the detector circuit with a plate potential of 180 volts and a grid bias of $4\frac{1}{2}$ volts.

To conclude the discussion of resistancecapacity-coupled amplifiers it may be said that they are capable of providing excellent reproduction when properly designed, and the total cost is considerably less than that of other types of amplifiers. However, they are not foolproof in operation, as there are many factors which may cause severe distortion. Usually they require more stages than does a transformer-coupled amplifier, to produce a given amount of volume. In operation these amplifiers are most satisfactory where large volumes are not required. Also, the tubes in the resistance-capacitycoupled amplifiers require a higher plate potential for their operation.

CHOKE-COIL COUPLING

In Fig. 2 will be found the wiring diagram of a standard impedance-capacitycoupled amplifier. From the circuit it may be seen that it is very similar to the resistance-capacity coupled type, the only difference being that audio-frequency choke coils (Lp) are connected in the plate circuits of the stages in place of the resistors used in the resistance-capacity-coupled amplifier. In operation this amplifier is very similar to the resistance-coupled type, but it is more economical as to plate voltage; as the large voltage drop across the plate resistors is obviated by the substitution of choke coils. It is also easier to obtain a degree of amplification which closely approaches the amplification factor of the tube than with resistance-capacity coupling. This is because, in a resistance amplifier, the value of the plate resistors must be several times the output impedance of the tube before the amplification of the stage approximates that of the tube.

In the impedance-coupled amplifier the audio-frequency choke coils vary in impedance with the frequency of the current which they amplify, and as a result the amplifier gives slightly better results on high notes than on low frequencies. However, if the impedance of the audio choke coil at the lowest frequency which it is to



The wiring of a standard two-stage, transformer-coupled amplifier is shown in this schematic wiring diagram. T1 and T2, audio-frequency transformers; T3, output transformer; V1, first amplifier tube; V2, second amplifier (power) tube.

amplify is three or four times as great as the output resistance of the vacuum tube, the distortion from this cause is not serious. Choke coils which have an inductance of 100 henries or more are satisfactory when using the 201A-type tubes. With the impedance-capacity-coupled amplifier the difficulty in obtaining a satisfactory value for the coupling condensers and the grid resistor is identical with the problem in the resistance-capacity-coupled amplifier.

From the above it may he seen that the impedance-capacity-coupled amplifier is almost identical with the resistance-capacitycoupled amplifier in operation, circuit design and construction, and produces very similar results. It will give equal results with lower values of plate voltage, but the parts used in its construction are slightly more expensive. When operating the impedance-capacity-coupled amplifier in connection with a plate-power-supply unit one is apt to experience a "motorhoating" effect unless provision has been made to guard against it in the design of the amplifier or the power unit.



The amplifier shown in the above schematic diagram employs a combination of resistance-capacity and impedance-capacity coupling which proves very satisfactory. "Motorboating" is usually absent in this circuit.

"MOTORBOATING"

"Motorboating," probably more than any other single factor, has prevented amplifiers of the resistance-capacity- and impedance-capacity-coupled types from achieving greater popularity than they have done. It may be described as a form of interference, heard in the reproduction, which sounds like the exhaust of a motorboat's engine. It is most annoying and sometimes ruins reception. It is seldom heard if the amplifier is supplied with a plate potential obtained from batteries, but is very frequently the cause of unsatisfactory results when an inefficient socket-power unit is used. The elimination of the "motorboating" effect puzzled radio experimenters for a long time, but several methods have been found for overcoming the disturbance.

Motorboating can frequently be eliminated by correcting the design of either the amplifier or the socket-power unit; but the most satisfactory method is to attack the trouble at the source, the socket-power unit. It has been found that socket-power units which have a low output resistance and an adequate filter, and which provide a con-stant voltage, do not cause "motorboating." Also, it has been found that by the use of an 874-type (voltage-regulator) tube in the output circuit of a socket-power unit, the current may be made constant and the output resistance may be reduced at the same time. The problem of improving the filter need not be discussed, as this is merely a matter of selecting efficient apparatus. If it is desired to make changes in the amplifier, a 3-henry choke coil, connected in the plate-supply lead of each stage, often pro-duces the desired effect. If the choke coils do not entirely eliminate the trouble, the use of an impedance leak in place of the grid resistor in the last stage often improves results. Sometimes it will be found that, by alternating between stages of resistancecapacity- and impedance-capacity-coupled amplification, one can obtain even better performance. A typical combination of this kind is shown in Fig. 5.

While on the subject of impedance-capacity-coupled audio amplifiers, it should be pointed out that there is a variation of the circuit which makes it possible to obtain an amplification greater than the amplification factor of the tube, and still retain the advantages of this type of amplifier. The

Transmitting on a Wavelength of Three-Quarters of a Meter

Remarkable Work of German Fxperimenters With Radiophone on Ultra-High Frequencies Develops Interesting Circuits



OW wavelengths? and "high frequencies" are radio terms which may be considered as entirely relative, as they have no particular significance of their own. Several years ago all channels below 600 meters were classed as "short waves"; and, when the American radio law of 1912 was passed, the legislators thought that the amateur transmitter could be climinated by assigning stations of this class to wavelengths below 200 meters, as this field was considered valueless. When broadcast stations started operating on waves near the amateur band, the amateur was forced to use still shorter wavelengths; and at that time it was discovered that satisfactory results could be obtained on less than 100 meters. Later amateurs found that waves as low as 40 meters provide valuable channels for communication.



* Physical Institute of Technology, Darmstadt. Germany.



Today there are many high-power commercial stations operating on wavelengths which were considered entirely impractical less than six years ago. It has been found that the very short waves possess many unusual characteristics which make them ideal for certain types of communication, particularly over long distances. In addition to the stations which are actually operating on short waves, there are hundreds of experimenters endeavoring to obtain data on the *ultra-short* wavelengths which have not yet shown their commercial value.

While engineers are busy trying to find some connucrcial use for the wavelengths below 13 meters or so, scientists are still seeking shorter wavelengths to conquer. In this field the latest development is a new transmitter which operates on a wavelength of 75 centimeters (three-quarters of a meter, or 291/2 inches). Of course, no practical use has yet been found for such a transmitter, but the inventors of the system are very much pleased with the fact that they have been able to produce oscillations at such high frequencies, and are equally clated over the development of a receiver which will detect the oscillations. Not only have they been able to transmit and detect continuous-wave signals on a wavelength of 75 centimeters, but they have been able to send and receive LC.W. (interrupted continuous wave) and even telephone signals on these high frequencies. These signals have been received over distances of approximately a quarter of a mile.

PRINCIPLES UTILIZED

In this article no attempt will be made to give constructional details of a receiver or transmitter for operation on 75 centimeters, but the experiments with this apparatus which have been conducted in Germany will be described for the benefit of the qualified experimenter who may wish to do some original research work with ultra-short wavelengths. However, it must be remem-

> The telescoping horicontal rods A form the only aerial of the 75 - centimeter radiophone transmitter at the left; they ar e s 1 i d up and down the vertical mast to decrease or increase the length of the parallel wires included in the oscillatory circuit of the tube V1, and connecting the latter with its batteries.

bered that the results described were obtained with foreign equipment and, therefore, entirely different results may be obtained from American tubes and apparatus. Two German radio engineers, Bark-



The 75-cm, resonant circuit comprises only the parallel wires of length (1) varied by the sliding bridge B, and the tube's internal capacity.

hausen and Knrz, are responsible for the first research work attempted in this direction. The discovery which pointed to the possibility of operating radio apparatus on wavelengths of less than one meter came as a result of a study of the characteristic curves of vacuum tubes. It was found that in these graphs certain irregularities appear, which are similar to the resonance curves obtained in high-frequency phe-nomena. In the experiments which followed this discovery it was proved that high-frequency oscillations can be produced by applying a high positive potential to the grid of a vacuum tube and a negative potential to the plate. Measurements were made which showed that the oscillations which were produced in this way had a frequency greater than one hundred million cycles per second, corresponding to a wavelength less than three meters.

Barkhausen and Kurz explain the results described above as follows: the electrons emitted from the incandescent filament are so strongly attracted by the positive grid that they move at high speed across the space between the filament and the grid, and into the space between the grid and the plate. As the electrons approach the plate, they are strongly repelled by the negative potential and, as a result, are driven back toward the grid. In this way a pendulumlike movement is established around the grid; or in other words, electrical oscilla-tions are produced. The frequency of the oscillations has been found to be governed by the characteristics of the vacuum tube and the value of the plate and grid poten-



Maximum plate current in the 75-cm, transmitter practically coincides with maximum oscillatory current; thus making tuning possible,

tials. The oscillations are accelerated by an increase in the potential producing them, and vice versa.

SPECIAL TUNING CIRCUIT

The research of Barkhausen and Kurz has been confirmed by Scheibe, another well-known German scientist, who has in addition developed an exact formula by which the frequency of the oscillations may be determined in every case. With the method described above, Scheibe found the oscillations very feeble, and only with the most sensitive indicator was he able to detect their existence. However, he found



The circuit which he used for this purpose is shown in Fig. 1. Two parallel wires (P and P1) are connected to the grid and plate terminals of the tube, and these wires are connected by a sliding bridge, B. The grid-plate capacity of the vacuum tube, plus the inductance of the two parallel wires, composes the closed oscillatory circuit, which may be adjusted to the desired frequency by the sliding bridge. The grid and plate potentials are brought to the tube through the parallel wires and the by-pass condenser (C) is used to prevent a shortcircuit of these power-supply wires. Because of its relatively large capacity, the presence of the condenser in the bridge has little or no effect upon the high-frequency circuit.



A graph of the sensitivity of the 75-cm. antenua as it is revolved through 360 degrees. It is very directional.

A TWO-WAY CURRENT

The operation of such a circuit as shown in Fig. 1 may be explained as follows: with a negative potential applied to the plate, under ordinary circumstances, it would seem that there should be no current between the plate and the filament. On the contrary, in a poor vacuum tube it is possible to detect an "ionic" current flowing in the opposite direction from that of the normal stream of electrons. If oscillations are now produced in the tube, in the manner previously described, a positive stream of "ions" will be found to exist; and this stream will reach its maximum when resonance is produced between the outer oscillatory circuit and the oscillations inside the tube. The ion represents a particle of gas which has lost an electron (unit negative charge) and therefore has a unit positive charge; it tends to move toward a negative potential, thereforc.

With a millianometer (Ip) connected in the plate circuit, it is possible, by observing the current registered on the scale, to determine with certainty the best position for the sliding bridge. It is possible also to measure the frequency of the oscillations. Fig. 2 shows that the plate current of the tube (the solid line of the graph) varies with the length of the wire in the bridge circuit. The dotted line of the graph indicates how the R.F. current of the closed oscillatory circuit varies with the length of wire in the bridge.

This measurement was obtained by connecting a thermo-coupled milliammeter in series with the condenser (C) and in this way the high-frequency current in the bridge circuit was directly measured. By comparing the two curves of the graph, it may be seen that the maximum intensity of oscillations is approximately at the point of maximum plate current. Therefore, by adjusting the bridge until maximum plate current is obtained, it is possible to determine the frequency of the oscillations by measuring the length of wire in the bridge; and, at the same time, be assure of maximum intensity of oscillations. The curves shown were obtained with a Schott transmitting tube (type N) under a plate potential of 240 volts.

USE FOR TRANSMITTING

In order to convert the oscillator described above into a short-wave transmitter, it is necessary only to connect a bi-polar antenna to the bridge in the proper manner (see Fig. A). Such a transmitter will send out a considerable amount of energy, and, with proper modulation, will serve for radio telephony. The bi-polar antenna consists of two straight wires (each half as long as the wave produced), which are fastened directly to the bridge in a horizontal position, in the manner shown in the pictures accompanying this article. In Fig. 3 the complete schematic wiring diagram of a transmitter of this type is given. The bipolar antenna is shown at A and is con-nected directly to the bridge C. The two inductors in the filament circuit are choke coils which prevent undesired self-oscillations.

DIFFICULTY OF ADJUSTMENT

Development of apparatus for receiving signals from transmitters operating on a wavelength of less than one meter presented another problem which scientists did not find easy to solve. With signals having a frequency of approximately 400,000,-000 cycles per second, it may be seen that the usual method used for receiving continuous-wave signals (i.e., the audio beatnote system) would be entirely impractical; as it is almost impossible to adjust the frequency of the receiver so exactly that the oseillations received from the transmitter, when "beating" with the locally-generated oscillations, would produce a steady audio note. Therefore, another system was found necessary and I. C. W. and phone were tried; both of these proved satisfactory.

In their original experiments Barkhausen and Kurz endeavored to modulate the output of the set with a buzzer connected in the plate circuit of the tube. However, this proved entirely unsatisfactory because, when the plate circuit was opened, the grid



The circuit of the 75.cm. vacuum-tube receiver pictured in Fig. C.



received the entire emission current and, as a result, quickly overheated. In Fig. 3 the buzzer (B) is shown connected directly in the grid circuit and this has been found to be very efficient.

Barkhausen and Kurz also attempted to modulate their transmitter for telephone, but the results have been more or less unsatisfactory. A modulation transformer was used to replace the buzzer in the platesupply wire, and a microphone was connected in series with the primary winding. This method, however, modulates only a small percentage of the output.

TELEPHONE WORK

The only experiment which has given satisfactory results employed a circuit such as is shown in Fig. 3, in which an extra tube is used as a modulator. In this circuit the fluctuating current of the microphone (M) is carried through the microphone transformer (T) to the grid of the modulating tube (V) and this changes the internal resistance of the tube so that low-frequency potential variations exist in the choke coil (L). As a result, the grid potential of the transmitting tube (V1) is increased and diminished in accordance with the voice frequency.

Figure A gives a complete view of the radio-telephone transmitter which has been designed to operate on a wavelength of 75 centimeters. The two parallel wires (P and P1 in the diagram) are supported by the wooden pole and the oscillator tube V1 is mounted on the top. The sliding bridge and the bipolar antenna, (A-C) which are adjusted to tune the closed oscillatory circuit to resonance with the transmitted frequency, are provided with a telescoping brass rod. B is the buzzer which is used to modulate the system for telegraphy, and the telephone modulation equipment is located to the right. The designating letters of all parts correspond with those in the diagram (Fig. 3.)

The 120 storage cells located under the table are used for providing the grid potential to the oscillator tube.

THE RECEIVER

The apparatus used for receiving signals on wavelengths of 75 centimeters is shown in Fig. B. The construction of the receiver is very similar to the transmitter, although the circuit is somewhat different. The long wooden rod supports a crystal detector in an insulated tube (D) at the top, and the two parallel wires are carried up the sides of the rod. The bi-polar antenna (A and A¹) and the sliding bridge are also mounted in much the same manner. The wires to the headphones go up the inside of the rod and the escape of R.F. currents is prevented by small choke coils (L.)

If, in place of the headphones, an extremely sensitive measuring instrument is connected to the detector circuit of the receiver, the transmission of short waves through space can be observed and investigated. Here we must refer to an observed



phenomenon; if the waves from the transmitter or the receiver are thrown back or reflected by a metal plate, they will then interfere with the direct transmission and, in this way, there are produced "standing waves" which can be recognized by the rising or falling of a galvanometer needle. The apparatus is so sensitive that waves reflected at a distance of several meters can be observed.

The intensity of reception is at maximum when the transmitting and the receiving antennas are parallel. If one of them is turned through 90 degrees, the reception disappears completely, and then by further turning is brought again to maximum. Plotting the galvanometer changes with polar coordinates produces a graph for a bi-polar antenna similar to that shown in Fig. 4.

LATEST DESIGN

For reception over greater distances, we have to design an efficient vacuum-tube receiver. After various experiments the circuit shown in Fig. 5 was chosen, and this has given very good results. V is a vacuum tube, with a grid condenser (C) and a grid leak (R) of one megohm. The oscillatory circuit is formed just as it is in the transmitting circuit, with two parallel wires on which slides the bridge extending to the antenna. Now, as only the plate potential is carried over the parallel-wire system, the condenser portion of the bridge is superfluous. The tuning in of the signal from the transmitter must be accomplished by sliding the bridge and by lengthening or shortening the antenna. The tuning of the oscillatory circuit with these methods is extremely difficult and the highest sensitivity is finally obtained by variation of the plate potential.

Fig. C shows the receiver as it appears completed. As in the detector circuit previously described, the high-frequency section must be withdrawn as far as possible from the disturbing influence of the ground, and supported on the vertical insulating tube. The circuit constants with ultra-short waves are very small; so that the entire length of the system of parallel wires is only about 50 millimeters (two inches). The connections to the battery lead are brought down through the rear of the tube. 'To increase the amplification of the receiver, a Loewe triple tube (three sets of elements in one glass bulb, as described in RADIO NEWS for July, 1926) is connected in an audio amplifier circuit. With this apparatus, it is possible to demonstrate to a large number of listeners the phenomena of fixed waves, interference, reflection, etc., by means of a lond speaker. The experimenters have covered a distance of about 300 meters; but the intensity of the sound was still so great that the limit has been by no means reached.



Letters from Home Radio Set Constructors

EARLY WORK IN RADIO

Editor, RADIO NEWS:

I read the Somersalo frequency-filter article with I read the Somersalo frequency-filter article with interest, because the first receiver I ever built had three stages of untuned R.F. amplification. After months of experiment, I was able to secure razor-edged scleetivity with this receiver. It was used to give concerts in small towns in Louisiana and Arkansas, and was the first radio set seen and heard but thereafter of needle

Arkansas, and was the first radio set seen and heard by thousands of people. The signal was first selected by a single-tube regenerator, having a lamp-cord aerial about 20 feet long. This regenerator was in a separate cabi-net and placed a few feet away from the other receiver and its loop. The regenerator had the regeneration control for all stations, hence opera-tion was easy. The signal radiated by the regener-ator was picked up by the loop. It was found ad-vantageous to place a R.F. choke and "C" battery between the loop and the potentiometer lever, be-cause the latter then had the same setting for all stations, and the selectivity was improved. The combination of receivers was operated as a two-dial tuned set, and it was not necessary to readjust either the regeneration control or potentiometer either the regeneration control or potentiometer lever. It was necessary that the coupling between the regenerator and the loop should be very loose. An outdoor aerial was never needed. C. J. ROGERS, Mc.Allen, Texas.

RADIO IN THE FIREPLACE

Editor, RADIO NEWS:

Liantor, RADIO NEWS: In your editorial, "What's What in Radio, you mentioned that two speakers will give the best music. Well, "you said it;" and if anyone wants to go to the trouble to do what 1 did, he will be well repaid. I have been using for over a year now the combination shown in the diagram; and many of my friends who have heard this outfit have asked me to write to you and let other fans know what can be done.

know what can be done, First of all, when you enter my living-room, you cannot detect a wire, speaker or set. The receiver, 'B'' power unit and switches are in my bookcase, and the speakers are in the fireplace, hidden be-hind a Chinese screen. All wires, including the aerial lead-in and ground, are in the walls. The ".A" battery and trickle charger are in the base-ment. When the switch C is thrown up, it con-nects the battery with the set, ready to operate; when the switch is down, the charger is connected and switch E starts it charging. The double socket

when the switch is down, the charger is connected and switch E starts it charging. The double socket D gives a place to plug in a lamp. To get really good reproduction, the fireplace should be hung with heavy vclvet; but in order to get a good soundbox, I first had it limed with limbleum. The horn is a Rola and the cone a West-ern Electric. Lust at this time there is corrent music crn Electric. Just at this time there is organ music on the radio, and I tell you it is a pleasure to listen to it. I am using Thordarson autoformers listen to it.

and two power tubes, with 200 volts "B"; this hook-up will bring a symphony concert to your home in proper style.

am an old radio bug-since 1919--and distance does not mean anything to me; but on quality I'm a crank. I always enjoy reading your magazine, and I can boast of having all your copies. Should anyone wish any more information, I will gladly write to anyone.

Write to anyone. J. LARDEMER, 355 Douglas Street, San Francisco, Calif. (Our caution should be repeated; readers should not write for clementary radio information, or for instructions on points which should be apparent to anyone who has the mechanical or electrical skill preserve to build another install the write south anyone who has the mechanical or electrical skill necessary to build such an installation. The equip-ment pictured here is an excellent combination for those who have a suitable nook in which to install it. The speakers might well be tested in series and in parallel. In previous issues of this magazine full directions have been given for a connection which permits, with the aid of a suitable switch, all possible combinations of one or both.— FUTOR.) EDITOR.)

MISSIONARY WORK

Editor, RADIO NEWS:

You are a friend to me for publishing the

You are a friend to me for publishing the Peridyne Five. I have built three or four sets up to now, and when I read that article, I thought "This fellow is making a broad statement, but it reads good to me." I am using a four-tube re-generative set, and four other fellows at the same plant had the same kind, and they thought they had the last word in radic; all were bugs of five or six years' standing. Well, my set has two .0005 geared condensers, so I bought one more and made all the coils, and caus of copper about .02-inch thick; and for about \$10.00 completed the set out of the four-tuber I was using, with only two alterations from the pub-lished circuit (three condensers instead of a gang and a resistor of 10,000 to 700,000 ohms). I used 201A tubes throughout, and 22½ volts on the first audio tube, 90 on the second, with a 4½-volt "C" battery. battery.

I want to tell you, honestly, the owner of an S-tube superhet and a batteryless 6-tube set with 180 volts on the last stage, admitted I had him beaten with my five-tube Peridyne. I brought one of the fellows from the plant down to the house: he had had a four-tuber for a couple of years, and thought it was "it." Well, he stayed four and a half hours, and went home; and the next night he tore his set down and started making the Peridyne shields. The other three fellows who have the same old set are coming down this week to see it, and, of course, I know what will happen. The fellow that heard mine told one of them, confi-dentially, that mine was 100 per cent. better than theirs. theirs.

Auyhow, I am perfectly satisfied with this out-fit, and then some. There is only one thing I



Mr. Lardemer's reception room makes use of a tastefully-screened fire place. The arrangement is shown above, and its convenience is apparent at & glance.

want, and that is another aerial in the other direc-tion; the one I have is east and west, and all sets should have aerials north, south, east and west. I have proved this by trying previous sets for months at a time, first on a street east and west, and then on a house whose street lay north and south. An aerial in one direction only is directional, like a loop or a superhet. You don't notice it, because you can't move it around; but put another aerial in the crosswise direction, and you will get sta-tions you never had before on the same set. I am going to write you again in the near future -don't forget I am 500 miles north of you, up in Canada. I have had the set working one week, and here are the stations I have logged. (List of 51 stations in the United States and Canada, ranging to St. Petersburg, Fla., and Fort H'orth, Tex.) and a bunch more that I haven't had time to log. I will send you a full list later on. I might also state that I think those who buy RADIO NEWS buy all there is in radio literature. I have tried them all. Again allow me to thank you. Yours in ap preciation, JOSEPH ADAMSON, 14 Balsam Avenue, North, Hamilton, Outario.

A SATISFIED SET BUILDER

Editor, RADIO NEWS:

I have noted, carefully, practically every circuit that you have published in your magazine for the past five years; but I am still using a five-tube

LETTERS for this page should be as short as possible, for so many are re-ceived that all cannot be printed. Unless a set is made from a published descrip-tion, a schematic sketch should be sent; photos can be used only to illustrate a novelty, and then only if large and very clear. Inquiries for information not given here should be sent to the constructor direct; but he should NOT be asked to furnish data already published, here or elsewhere. elsewhere.

This department is for free discussion to the extent that space permits; but RADIO NEWS accepts no responsibility for the opinions of readers as to the rela-tive merits of apparatus and circuits.

THE REAL PROCESSION AND A DESCRIPTION OF THE REAL PROCESSION AND A DESCRIPTION OF THE REAL PROCESSION AND A DES

neutrodyne which I constructed from Fada parts

neutrodyne which I constructed from Fada parts over three years ago, and I have found no other circuit any more satisfactory for my use here in the country, where I am located, sixteen miles west of Richmond on the James River. Speaking of DX reception, I can uearly always get KFI on the loud speaker, and with good vol-ame, at any time at night during their broadcast-ing hours, except when WRC at Washington is on the air. When Lindbergh was in Mexico City, I was prompted to tune in for the G.E. station there (CYJ) and experienced no difficulty in hearing the station clearly before 9 o'clock in the evening. My success with my receiver is due principally to the fact that I am using regeneration in addi-tion to the already excellent amplification of the neutrodyne circuit, which results in a real DX-getting set. The method of doing this success-fully was first brought to my attention by a most interesting article by Mr. A. L. Graves, "The Re-generative Neutrodyne," published in RADIO NEWS in April, 1925. Instead of getting regeneration from a variometer in the detector circuit, I am using a winding which was inserted in the tube of the second R.F. transformer; regeneration being controlled by a variable condenser in series with this special winding. I can get all the regeneration the second R.F. transformer; regeneration being controlled by a variable condenser in series with this special winding. I can get all the regenera-tion desired with fine control throughout all the wavelengths from 200 to 575 meters. I am using five UV-201A R.C.A. tuhes, and three of them have given over 3,200 hours' service and are still doing good work! W. D. Moss, M.E.. "Huguenot," R.F.D., Mossley, Va.

ECCENTRIC CONE WORKS WELL

Editor, RADIO NEWS:

The second prize wrinkle in your January issue interested me, as the possessor of one of the origi-nal Crosley Musicones. I tried out the eccentric cone idea and really believe Mr. Crosby should have been awarded first prize.

In making the new cone I used Fonotex paper and found that in the small cone for the apex I had to cut out seven-eighths, instead of five-eighths. to get a sung fit. I made a light wooden frame mounting for the Crosley unit and, as the weight of the new cone hauging on the states call activities aim of the

hanging on the rather small actuating pin of the



Mr. Hurley's aerial, showing how areat length is obtained in small space. His letter is on page 1191.

unit caused it to assume a position with the long diameter toward the bottom, I had to remount the unit and cone on a longer upright shaft. The weight of the cone caused the short, or top

part, to lean over against the top edge of the cover of the unit, and bent the actuating pin upward into a considerable curve. Believing from what I had -ead that the pin must always be perfectly straight, and perpendicular to the unit, I could see no

reason why the contrivance I had built should be worth a cent as a loud speaker, or even speak at

all. However I hitched it up and turned on the set; result, the finest-toned speaker 1 have ever lis-tened to, and 1 have heard the Radiola, Western Electric, Peerless and all the rest of them. The tone was unbelievably pure, true and natural, low tone was unbelievably pure, true and hatural, low notes just right in volume and absolutely no sounds that should not be there. I have more respect for the little Crosley unit than before. Should have said that I built the 20-inch cone

which, I believe, is plenty large enough for home use where quality alone is desired. Would like to try it again, but am afraid I would never again have such hick.

C. E. CURRIER, 1476 Belmont St., N. W., Washington, D. C.

AN OLD FAVORITE

Editor, RANO NEWS: Recently I constructed the Interflex Four, de-scribed in the September, 1925, issue of RADIO NEWS, and I find that it is the best four-tube set that I have ever seen or heard. The volume is good, it has remarkable tone quality, and it's fine for DX. The furthest station I have received is KFON at Long Beach, Calif., on the loud speaker. I advise anyone who wants a good set to build the Interflex Four.

It works very well with the simple "B" power It works very well with the simple "B" power unit described in the April, 1927, issue of SCIENCE AND INVENTION. This unit works very well with a 201A tube, but I am using a 216B. All fans who want a good power unit that works as well as bat-teries should build it. Anyone wanting information on either can get it from me by seuding a letter or card. ILENDERT L. TRAYLOR, JR.

or card. HERBERT L. TRAVLOR, JR. (II'e will do Mr. Traylor a favor by leaving out his address, because we know what will happen as a result of his generous offer, if we do not. To make his DX record clear, however, we may say that he is a resident of Virginia. The Interflex Four is an early design using the same principle which is exemplified, with improved components, in the Peridyne Five. Some constructors, however, cling to the earlier and simpler model, with which some remarkable results have been obtained.— EDITOR.) EDITOR.)

AN "SOS" COMES IN

Editor, RADIO NEWS: HELP! Since the publication of my letter in the January issue of RADIO NEWS—which letter, by the way. I did not intend you to publish—re-ferring to my success with the RADIO NEWS Short-Ways Researce. I have been received ways short-Wave Receiver, I have been receiving communica-tions in flocks requesting all sorts of information (Continued on page 1191)

List of Broadcast Stations in the United States

(Continued from page 1121)

Radio Cali Letter	BROADCAST STA. Location	Wave (M eters) Power	Radio Call Lette	BROADCAST STA.	Power (Watts)	Radio Call Letter	BROADCAST STA.	Power (Watts)	Radio Call Letters	BROADCAST STA Location	Wave (Mieters)	Power (Watts)
Letter UUWJBWY WJBBZ QQR QQR QQR QQR QQR QQR QQR QQ	Lewisburg, Pa. New Orleans, La Gadsden, Ala. Chicago Heights, Ill. Mtooseheart, Ill. Astitabula, Ohio. (Z Y Pontlac, Mich. (Also 32 meters, 75 watts tNew York, N. Y** Sart, 50-96 meters, 30 kx San Juan, Porto Rico. San Juan, N. H. Lacoona, N. H. Hermingham, Ala. Webster, Mass. Indianapolis, Ind. Alexandrow, Mich. Joliet, Ill. Webster, Mass. Chicago, Ill. Gorosee, Wiss. Chicago, Ill. Montroc, Mich. Youngstown, Ohio. Jersey City, N. J. Hattle Orcek, Mich. New York, N. Y. Gatesbuiltz, Ill. New York, N. Y. Gatesbuiltz, Ill. New York, N. Y. Landington, Mich. Hikenosha, Wiss. Amherst, N. Y. Lanenster, Pa. Chichana City, Okla WOAO Nasilville, You. Muncie, Ind. Kanass City, No. Petersburg, Va. Farmingdale, N. Y. East Wenona, Ill. Rockford, Ill. (portable, Alexandrow, Ne. Chicago, Ill. (portable) Galesburg, Ill. Conwn Point, Ind. Mansel, Ohio. Oil City, Jra. Long Siand City, V. Y. Fron Mountain, Mich. Dover-Foxeroff, Me. Hunca, N. Y. Landingto, Miss. Chicago, Ill. Mansield, Ohio. Oil City, Jra. Long Siand City, V. Y. Fron Mountain, Mich. Dover-Foxeroff, Me. Hunca, N. Y. Heatwide, Jand. Dovershor, Mass. See WGN Philadelphia, Pa.	$\begin{array}{c c c c c c c c c c c c c c c c c c c $	Letter	Location *24 tChicago, III*345 See WOWF H Brooklyn, N. Y	▲ > 5000 250 100 5000 2000 2000 5000 500 500 500 500 500 500 500 500 500 500 500 500 500 500 5000	Letter WOAI WOAN WOAX WOBR WOBU WOBU WOBU WOCL WOCL WOCL WOCL WOCL WOCL WOCL WOCL	Location 75 San Antonio, Tex	▲ € 5000 5000 500 500 50	WRM WRMU (2XA WRMU (2XA WRMU WRMU WRM WRM WRM WRM WSAI WSAI WSAI WSAI WSAI WSAI WSAI WSAI	Urbana, III. New York, N. Y. (po 0. ship. 105.9 meters, fNew York, N. Y. (po 0. ship. 105.9 meters, fNew York, N. Y. (Jalas, 20.91 meters, 500 Terre Haute, Ind., Dalkas, Tex. Racine, Wis. Bay Shore, N. Y Gainesville, Fia. Richmond, Ya. Clineinnail, Ohio. Grove City, Pa. Allentown, Pa. Allentown, Pa. Millentown, Pa. Allentown, Pa. Chileago, II. (port) Hundington, W. Ya. Chileago, II. (port) Hundington, W. Ya. South Faend, Ind. South Faend, Ind. New Orleans, La. Mikiland Park, N. J. Chicago, III. New Orleans, La. New Orleans, I.a. Asheville, N. C. Wwookidde, N. Y.	Level 2 2 2 3 2 3 2 6 1 2 1 2 7 3 2 6 1 2 1 2 0 2 1 2 1 2 0 2 1 2 1 2 1 2 1 2	■.≥ *500 100 200 200 200 200 200 200 2
# A 110 WOV	bither dealight horner	Ligt on de	rd or cond	und from on the graning of the	amute f	Control						

LIST OF CANADIAN BROADCAST CALLS

Calgary, Alta 435	500	CHGS	Summerside, P. E. L., 268	25	0010	Lethbridge, Alta 268	50	скос	Hamilton, Ont 342	I 104
'i'oronto, Ont	500	CHIC	Toronto, Ont	500	CJOR	Sea Island, B. C 291	50	CKOW	Scarboro, Out	I 500
Montreal, Que 411	1650	CHMA	Edmonton, Alta.,	250	CJRM	Moose Jaw, Sask 297	500	CKPC	 Preston. Ont 248 	8 C
Iroquois Fails, Ont 500	250	CHML	Mt. Hamilton, Out 311	50	CJSC	Toronto, Ont 357	500	CKPR	Midland, Ont	<u>s 5</u> 8
Calgary, Alta	1800	CHNC	Toronto, Ont	500	CJWC	Saskatoon, Sask 330	250	CKSH	St. Hyacinthe, Que 31	2 50
Vancouver, B. C., 411	10	CHNS	Halifax, N. S	100	CJYC	Scarboro, Ont.,, 291	500	CKSM	Toronto. Ont 29	1 1000
Victoria B. C 476	250	CHPC	Vancouver, B. C., 411	1000	CKAC	Montreal, Que 411	1200	CKUA	Edmonton, Alta 51	7 50
Charlottetown, P.E.L. 312	100	CHRC	Ouchec, Que	5	CKCD	Vancouver, B. C 411	1000	СК₩Х	 Vancouver, B. C 41 	1 50
Brantford, Ont 297	50	CHSC	Unity, Sask	50	CKCI	Ouebcc, Oue	23	CKY	Winnipeg, Man 38-	1 500
Kamloops, B. C 268	15	CHUC	Saskatoon, Sask 330	500	CKCK	Regina, Sask	500	CNRA	Mencion, N. B 323	2 500
Prescott, Ont 297	50	CHWC	Regina, Sask	15	CKCL	Toronto, Ont	500	CNRC	Calgary, Alta 43/	5 500
Kingston, Ont 268	20	CHWK	Chilliwack, B. C 218	5	CKCO	Ottawa Ont	100	CNRE	Edmonton, Alta 517	7 500
Fredericton, N. B 248	25	CHYC	Montreal, Que 411	750	CKCR	St. George Ont 258	25	CNRM	Montreal, Ouc 41	1 165
Saskatoon Sask 330	500	CJBC	Toronto, Ont	500	CKCV	Onebee One	50	CNRO	Ottawa, Ont 43	5 50
Toronto, Ont	1000	CJBR	Regina, Sask 312	500	CKCX	Toronto Ont 291	500	CNRQ	Quebec, Que	1 50
Kingston, Ont 268	500	CICA	Edmonton, Alta	500	CKEC	Vancouver B C 411	50	CNRR	Regina, Sask 315	2 - 500
Burnaby, B. C 411	500	CICI	Colcory Alto 435	250	CKCW	Rowmanyillo Ont 319	5000	CNRS	Saskatoon, Sask	0 500
Calgary, Alta 435	250	0.00	Ded Deem Alter 057	1000	OKUM	Ded Deep Alte 257	1000	CNDT	Toronto Ont 35	7 500
Hamilton, Ont	10	CJCK	Red Deer. Alta 357	1000	CKLC	Red Deer, Alta 30/	1000	CNET	Manual D (2)	500
Red Deer, Alta 357	1000	CJGC	London, Ont 330	500	CKMC	Cobsit, Ont 248	5	GNRV	vancouver, B. C 291	1 000
Edmonton, Alta 517	250	CJGX	Yorkton, Sask 476	500	CKNC	Toronto, Ont 357	500	CNRW	Winnipeg, Man 384	50
	Calgary, Alta	Calgary, Alta. 435 500 'toronto, Ont. 357 500 Montreal, Que. 411 1650 Calgary, Alta. 435 1800 Vancouver, B. C. 476 250 Charlotteitown, P.E.I. 312 100 Brautiori, Ont. 207 50 Kamioobs, B. C. 208 15 Prescott, Ont. 207 50 Kingston, Ont. 207 50 Kingston, Ont. 208 20 Fredericton, N. B. 248 25 Saskatoon Sask. 330 500 Kingston, Ont. 208 100 Kingston, Ont. 208 100 Kingston, Ont. 218 500 Calgary, Alta. 435 250 Calgary, Alta. 435 250 Calgary, Alta. 435 210 Calgary, Alta. 435 250 Calgary, Alta. 517 1000	Calgary, Alta 435 500 CHGS Toronto, Ont 357 500 CHIC Montreal, Que. 411 1650 CHMA Iroquois Falls, Ont. 500 CHMC Calgary, Alta 435 1800 CHNC Vancouver, B. C. 411 10 CHNS Vetorin B. C. 476 250 CHPC Garauttori, Ont. 297 50 CHSC Kamioos, B. C. 297 50 CHWK Frederictown, P.EL. 312 00 CHWC Fredericton, N. B. 248 25 CHWC Fredericton, N. B. 248 25 CHYC Saskatoon Sask. 330 500 CJBC Kinsston, Ont. 268 200 CJCJ Calgary, Altn. 435 250 CJCJ Kinsston, Ont. 268 500 CJCJ Calgary, Altn. 435 250 CJCJ Calgary, Altn. 435 250 CJCJ Calgary, Altn. 435 250 CJCJ <	$ \begin{array}{c} \text{Calzary, Alta.} & 435 & 500 \\ \text{Choroto, Ont.} & 357 & 500 \\ \text{CHORD, Ont.} & 357 & 500 \\ \text{CHORD, Ont.} & 357 & 500 \\ \text{CHML} & \text{Michanic Characteria} \\ \text{Charlotterial, Que.} & 411 & 1650 \\ \text{CHML} & \text{Michan Characteria} \\ \text{Charlotteria, R.} & 435 & 1800 \\ \text{CHNC} & \text{Toronto, Ont.} & 357 \\ \text{Vancouver, B.} & 435 & 1800 \\ \text{CHNC} & \text{Toronto, Ont.} & 357 \\ \text{Vancouver, B.} & 435 & 1800 \\ \text{Charlotteria} & \text{B.} & \text{C.} & 476 \\ \text{Charlotteria} & \text{B.} & \text{C.} & 476 \\ \text{Charlotteria} & \text{B.} & \text{C.} & 476 \\ \text{Charlotteriown, P.E.L.} & 312 & 100 \\ \text{Charlotteriown, P.E.L.} & 313 & 500 \\ \text{CHWC} & \text{Saskatonn, Sask.} & 312 \\ \text{Kinsston, Ont.} & 293 & 50 \\ \text{CHWC} & \text{Contreal, Que.} & 411 \\ \text{Saskatoon Sask.} & 330 & 500 \\ \text{CJER} & \text{Regina, Sask.} & 312 \\ \text{Kinsston, Ont.} & 293 & 500 \\ \text{CJCA} & \text{Edmonton, Alta.} & 517 \\ \text{Calzary, Altn.} & 435 & 250 \\ \text{CHARC} & \text{Red Deer, Alta.} & 357 \\ \text{Iamilton, Ont.} & 341 & 10 \\ \text{Red Deer, Alta.} & 357 & 1000 \\ \text{CJGC} & \text{London, Ont.} & 330 \\ \text{Sonder, Alta.} & 517 \\ \text{CJGC} & \text{London, Ont.} & 340 \\ \text{CHonotno, Alta.} & 517 \\ \text{CJGC} & \text{London, Ont.} & 340 \\ \text{CHardton, Alta.} & 517 \\ \text{CJGC} & \text{London, Ont.} & 340 \\ \text{CHardton, Alta.} & 517 \\ \text{CJGC} & \text{London, Ont.} & 340 \\ \text{CHardton, Alta.} & 517 \\ \text{CJGC} & \text{London, Ont.} & 340 \\ \text{CHardton, Alta.} & 517 \\ \text{CJGC} & \text{London, Ont.} & 340 \\ \text{CHardton, Alta.} & 517 \\ \text{CHARDTON, Alta.} & 5$	$ \begin{array}{c} \text{Calzary, Alta.} & 435 & 500 \\ \text{Charlow Dut.} & 357 & 500 \\ \text{Montreal, Que.} & 411 & 1650 \\ \text{Toroutos, Palks, Out.} & 500 \\ \text{CHMA} & Edmonton, Alta. & 357 & 550 \\ \text{CHMA} & Edmonton, Alta. & 317 & 250 \\ \text{Charlow Palks, Out.} & 500 \\ \text{CHMA} & \text{Edmonton, Alta.} & 317 & 250 \\ \text{Charlow Palks, Out.} & 435 & 1800 \\ \text{Charlow Palks, Out.} & 435 & 1800 \\ \text{Charlow Palks, Out.} & 4311 & 100 \\ \text{Charlow Palks, Out.} & 4311 & 100 \\ \text{Charlow Palks, Out.} & 237 & 500 \\ \text{Charlow Palks, Out.} & 297 & 50 \\ Kambons, B. C$	Calzary, Alta	Calary, Alta	$ \begin{array}{c} \text{Calgary, Alta,, 435} & 500 \\ \text{Cherry, Numerside, P. E. I., 268} & 250 \\ \text{CJOC} & \text{Lethbridge, Alta,, 268} & 500 \\ \text{Cherry, Numerside, P. E. I., 268} & 250 \\ \text{Montreal, Que,, 411} & 1650 \\ \text{CHMA} & Edmonton, Alta,, 517 & 250 \\ \text{CJRM} & Moose Jaw, Sask,, 297 & 500 \\ \text{Calgary, Alta,, 435} & 1800 \\ \text{CHMC} & \text{Toronto, Ont,, 357 } 500 \\ \text{CJRM} & Moose Jaw, Sask,, 297 & 500 \\ \text{Calgary, Alta,, 435 } 1800 \\ \text{CHMC} & \text{Toronto, Ont,, 357 } 5700 \\ \text{CJRM} & Moose Jaw, Sask,, 297 & 500 \\ \text{Calgary, Alta,, 435 } 1800 \\ \text{CHMC} & \text{Toronto, Ont,, 357 } 5700 \\ \text{CJRC} & \text{CJRM} & Moose Jaw, Sask,, 297 \\ \text{Substation, Sask,, 330 } 250 \\ \text{Charlotterbwn, P.E.I., 312 } 100 \\ \text{CHRC} & \text{CHPC} & Vaneouver, B. C, 411 \\ 1000 \\ \text{Charlotterbwn, P.E.I., 312 } 100 \\ \text{CHRC} & \text{CHPC} & Vaneouver, B. C, 411 \\ 1000 \\ \text{Wanutord, Ont,, 297 } 50 \\ \text{CHPC} & \text{Vaneouver, B. C, 411 } 1000 \\ \text{CHAC Montreal, Que,, 411 } 1000 \\ \text{Kantloons, B, C, 298 } 15 \\ \text{CHUC} & \text{Saskatoon, Sask,, 312 } 500 \\ \text{CHCC} & Quebec, Que,, 411 \\ 1000 \\ \text{Crastation, N. B. 248 } 20 \\ \text{CHWC} & Restano, Sask,, 312 \\ 500 \\ \text{Kingston, Ont,, 298 } 50 \\ \text{CHWC} & Restano, Sask,, 312 \\ 500 \\ \text{Kingston, Ont,, 298 } 50 \\ \text{CHCC} & \text{Vaneouver, B. C, 411 } 757 \\ \text{CKCR} & \text{Refina, Sask,, 312 } 500 \\ \text{Kingston, Ont,, 298 } 500 \\ \text{CJER} & \text{Refina, Sask,, 312 } 510 \\ \text{CHCC} & Vaneouver, B. C & 411 \\ 500 \\ \text{CJER} & \text{Refina, Sask,, 312 } 510 \\ \text{CKCC} & Vaneouver, B. C & 411 \\ 500 \\ \text{CLBC} & \text{Coronto, Ont,, 291 } 500 \\ \text{CHCC} & \text{Refina, Sask,, 312 } 510 \\ \text{CKCC} & \text{ChCC} & Nece Ont,, 258 \\ 250 \\ \text{CKCC} & Reed Deer, Alta,, 357 \\ 1000 \\ \text{Clagary Alta,, 435 } 500 \\ \text{CHCC} & \text{Calgary Alta,, 435 } 500 \\ \text{CKCC} & Red Deer, Alta,, 357 \\ 1000 \\ \text{Clagary Alta,, 357 } 1000 \\ \text{CLBC} & \text{Refina, Sask,, 317 } 500 \\ \text{CKCC} & \text{Coronto, Ont,, 291 50 \\ \text{CHORTON, N. R, 411 }$	Calary, Alta	Calgary, Alta



R-1DIO manufacturers are invited to scud to RADIO NEWS LABORATORIES samples of their products for test. It does not matter whether or not they advertise in RADIO NEWS, the RADIO NEWS LABORATORIES being an inde-pendent organization, with the improvement of radio apparatus as its aim. If, after being tested, the instruments submitted prove to be built according to modern radio engineering practice, they will each be awarded a certificate of merit; and that apparatus which embodies novel, as well as meritorious features in design and operation, will be described in this department, or in the "II hat New in Radio" department, as its news value and general interest for our readers shall deserve. If the apparatus does not pass the Laboratory tests, it will be returned to the manufacturer with suggestions for improve-

BINDING POSTS

Of the five shown here, No. 2 con-Of the five shown here, No. 2 con-sists of two separate part: a round base and a knurled knob. Inside this knob slides a threaded cylindrical nut, into which fits the screw which attaches to the base of the panel. The nut is held in position by a short, but strong spring. To attach a lead to this binding post, the knob may be either completely unscrewed or simply pulled ont with the fingers.



3 is similar in construction to 2, from which it differs slightly No. 3 No. No. 2, from which it differs singledy in that the sliching threaded nut is somewhat longer and passes through the top of the knurled knob. To op-erate this binding post, the knob is held between the index and middle fingers while the thinh is pressed on the ten of the cliching way No. 4 the top of the sliding unt. No. 4 has a spring-operated hexagonal sleeve and is provided with two holes; one approximately 5/32-inch



a smaller one used exclusively for telephone tips. No. 5 is designed to be used only with telephone tips. These four types of binding posts are made of nickel-plated brass with a fine finish, and are very satisfactory in operation.

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 2263.

No. 1 resembles in construction No. 2, but has its knob molded in



Its threaded base is likebakelite. wise molded in a bakelite nameplate. This binding post is very neat in appearance and satisfactory in operation.

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 2264.

PHONE TIP The phone tips shown are of the spring-operated type. Each consists of a sliding knurled sleeve and the



tip proper. The part of the tip passing through the sleeve is flat, and is provided at its end with a hole for the phone cord. This cord is tightened by the pressure of the sleeve, which is operated by a small spring device.

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO, 2265,

JACK SWITCH The jack switch shown is of the single-pole double-throw type, and



cspecially suitable for usc as a se-lector switch for long and short aerials. It is compact and of ex-cellent construction. The nickelcellent construction. The nickel-plated brass frame is insulated from the contact springs, which are made of phosphor bronze. These springs VERNIER DIAL

The tuning dial shown is of very The number of the second seco its entire circumference. The in-dicator is of the hair-line type and has a vernier calibration which per-mits reading up to 1/10 of a divi-sion. This dial has two knobs; one sion. This dial has two knobs; one in the center for rough adjustment, and a smaller one at the lower end of the dial for controlling the re-duction gear, which has a very high ratio, namely 260:1. By pulling the little knob upwards, this may be disconnected, and the larger knob in the center can be used. A four-inch handle permits the operation of the reduction gear at a distance which prevents body-capacity, as far as possible. It is of German manuas possible. It is of German manufacture



AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 2270.

POWER TRANSFORMER

This power-unit transformer is de-signed to be used in "B" power-supply units, operating from the 110-volt 60-cycle house-lighting line, and using a half-wave rectifier tube of the UN-281 or UX-216B type. It has three secondary windings; one, which supplies 110 milliamperes

accordance with the new editorial policy which RADIO I News has elsewhere announced, the names of the manufacturers or distributors of the apparatus and components described in this page will no longer be printed here. Readers who desire to know the names and addresses of the manufacturers of any articles described here, or whether any given turers of any articles described here, or whether any given type of radio material made by a certain manufacturer has been tested and certified as meritorious by the RADIO NEWS LABORATORIES, may obtain this information by sending a spe-cific inquiry with a stamped and self-addressed envelope to the "I Want to Know" department of RADIO NEWS, 230 Fifth Avenue, New York City. Inquiries as to the comparative merit of two or more articles, which are both of approved quality, cannot be answered, even confidentially.

insure a perfect contact and are operated by a quarter-turn of a small metal knob of attractive de-

sign. AWARDED THE RADIO NEWS LABORATORIES (ERTIFICATE OF MERIT NO. 2269,

at a maximum voltage of 750, is tapped at 550 volts for use with a rectifier of the 216B type. An-other winding supplies 1.25 am-peres at 712 volts for heating the filament of the rectifier. A third, which is center-tapped, takes care

of two power tubes of the UX-210 type with filament current of $2\frac{1}{2}$ amperes at 7½ volts and makes possible the addition of a power ani



plifier to the "B" supply unit. This transformer is rugged and compact and is sealed in a heavy japanned iron shell,

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 2271.

CONDENSER

The variable condenser shown is of the one-hole-mounting low-loss type. The plates of the stator and rotor are of such shape that the straight-line characteristic of this condenser is of neither the fre-quency, capacity, nor wavelength type; but it is a combination of all three, being nevertheless very close to the S.L.F. variation rate. It is of good electrical and mechanical design; the make is German.



AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 2272. OF

EXPONENTIAL HORNS The loud-speaker larger horn



shown here has a coiled air chamshown here has a coiled air cham-ber of the exponential type, is made of compressed wood-pulp and ap-proximately 90 inches long; its rect-angular bell is 18×24 inches. This horn has a low cut-off frequency, and affords brilliant reproduction when used with a good speaker unit. The depth of this assembly is approximatcly 14 inches and its compact-ness adapts it for inclusion in any of a great number of radio cabinets.

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO, 2273.

This speaker horn, of the same make as that shown above, but much smaller, is also of the coiled type and made of compressed wood-pulp. Its air column is approximately but 30 inches long; nevertheless during



the tests, satisfactory reproduction of music and speech was obtained from it, in connection with a good loud-speaker unit, and it may be in-corporated in radio receivers where relatively little space is available.

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 2274.

FILAMENT BALLAST

The resistor shown is intended for use in series with the filament of a screen-grid (type 222) vacuum tube when operated on a 6-volt storage resistance battery. Its



changes automatically with and takes care of variations in the voltage of the storage battery, and insures an approximately constant value of the current flow through the filament. It may be used with any vacuum tube of a type requiring 132 milli-amperes at 3.3 volts and operating from a 6-volt storage battery.

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO, 2275.

"B" POWER UNIT

"B" POWER UNIT The "B" power unit shown oper-ates from the 110-125-volt, 50-60-cycle house-lighting line, and uses an 85-milliampere full-wave tube as rectifier; five binding posts supply taps for the necessary voltages re-quired to operate the average com-tenerate realing reading. The unit harcial radio receiver. The unit has a maximum output of approxi-mately 50 milliamperes at 180 volts.



A selector switch, located on the output panel and operated by a plug, is provided to take care of the cur-rent demands of different radio re-ceivers; it can be used also to com-pensate the different line voltages. Two extra binding posts on the panel are connected to an automatic double-pole relay switch built into the unit; this switch is operated by the filament current and controlled from the filament switch of the re-ceiver. It requires approximately 600 milliamperes to operate and has ceiver. It requires approximately 600 milliamperes to operate and has a resistance of approximately 0.21 ohms. The entire unit is enclosed in a molded hard rubber case of attractive mahogany finish.

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NOS. 2276-2277.

CONE SPEAKER

The loud speaker shown is of the The loud speaker shown is of the double-cone type, and uses a 24-inch diaphragm of parchment-paper, having a beautiful leather finish. The unit is of the balanced-armature type, and of interesting construc-tion. Its laminated "U"-shaped pole pieces, made of silicon steel, are cast into the aluminum frame. are cast into the aluminum frame. A heavy horseshoe permanent mag-net, which has one side 5½-inch longer than the other, is held in position with regard to the pole pieces by set screws in the aluminum frame; so that drilling the magnet is not re-quired. The two coils, which are of elliptical section, are relatively large and are clamped into the pole pieces; two special holes in the frame allow easy mounting of this unit on the loud-speaker frame. The tone quali-



ties of this speaker are excellent; the reproduction has naturalness and great volume. AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 2278.

CONE SPEAKER

The speaker shown is a reproducer The speaker shown is a reproducer of the free-edge cone type, with a paper diaphragm 11 inches in diam-eter. It has a unit of floating-armature type, which is equipped with an adjusting screw. An iron housing of pleasing design, in brown crystalline finish, encases the unit



The reproducing with the cone.

LABORATORIES CERTIFICATE OF MERIT NO. 2279.

EXPONENTIAL HORN

The loud-speaker horn shown is of the couckspeaker norm shown is of the exponential type and made of impregnated fabric: the effective length of its air column is approxi-mately 100 inches, and its bell sec-tion is 18 x 24 inches. This coiled horn has a denth of approximately



inches and may be very conveniently installed in many radio cabinets. The results, obtained when this horn was tested in connection

with a powerful unit, were excep-tionally good; particularly remark-able was the response to the lower musical notes.

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO, 2281.

POWER TRANSFORMER

The power transformer shown is intended for use in units supply-ing the required "A.B.C." power to radio receivers having in series up



to eight tubes of the 201A type, and to eight tubes of the 201A type, and using in the fast stage power tubes of the UN-171 or UN-112 type. It operates from the 110-volt, 50-60 cycle house line, and uses a 350-milliampere full-wave rectifier. Two center-tapped secondary windings supply 400 milliamperes at 300 volts on either side for the rectifier, and one ampere at 5 volts for the fila-ments of the power tubes. This transformer is of sturdy construction and is housed in a strong metal case and is housed in a strong metal case having a black crystalline funish. AWARDED THE RADIO NEWS

LABORATORIES CERTIFICATE OF MERIT NO. 2282.

HEAVY DOUBLE CHOKE

The double choke shown may be used in the filter systems of powersupply units operating on 50-60-



cycle A.C., when the current does not exceed 400 milliamperes. The windings of the choke are connected to three outgoing leads. The ohmic to three outgoing leads. The ohmic resistance of each coil is, approxi-mately, 106 ohms and its inductance, approximately, 10 henries. This double choke is sealed in a heavy sheet-iron container.

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 2283.

CONE SPEAKER

The double-come loud speaker shown has a driving unit of the balanced-armature type. The repro-ducing come is 20 inches in diam-eter and very handsomely decorated; the base of the speaker is of cast brass and has a very pleasing de-



The performance of this insign. strument in reproduction of both music and speech has been found to be satisfactory.

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 2284.

HIGH-RESISTANCE POTENTIOMETER

This instrument is a high-resistance potentiometer, using as a re-



sistance element a paper strip coated with graphite. The contact between the movable arm and the resistance the movable arm and the resistance strip is effected by means of a rol-ler, which insures a smooth and a good contact and does not wear out the resistance element. This poten-tiometer is of the one-hole mounting type and has a very neat housing, made of nickel-plated brass, which contributes to perfect cooling.

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 2286.

ANTENNA COUPLER

The basket-weave coil shown is an antenna coupler of the auto-trans-former type, with an inductance



value of approximately 170 micro-henries. It is enclosed in a casing of compressed cardboard with tips, connected to the corresponding ends of the coil. This device is of German manufacture.

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 2287.

LOUD SPEAKER

The cone speaker shown is of the free-edge type, and uses a unit of the balanced-armature type. The the balanced-armature type. The paper cone is 14 inches in diameter and is housed, together with the unit, in a beautiful metal casing, having a golden-brown crystalline finish. This instrument has been found a very good reproducer of found a very good reproducer of nusic and speech.



AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 2288.

INTERFERENCE ELIMINATOR The filter device shown climinates completely, or reduces to a great ex-tent, the radio interference due to motors up to five horse power, when inserted between the motor and the inserted between the motor and the power line; it consists of two choke coils and two condensers of .05-mf. each. The two coils are inductively coupled and have a common core unide of iron strips; the D.C. re-sistance of each coil is very low, approximately .037 ohms. Coils and condensers are housed in a heavy iron case, with several holes on its sides to permit good air circulation and insure effective cooling. and insure effective cooling.

(Continued on page 1191)



THE INTERPLANETARY RECEIVER



1150

NETARY RECEIVER Astronomical note from the New Haven Sunday Register of Dec. 18: "Panel template for drill-ing METEOR holes, bind-ing posts and variable re-sistances." If you have to wait until some night when meteors are falling thick and fast before you can get holes in your panel, we would advise, "Build some other set." Contributed by , Contributed by H. Naftal.

IT'S WORTH A LEG OR TWO!

1YA

THAT BLASTING STUDIO

THAT BLASTIN Station 1YA. Auckland, unist put some strong stuff on the air, according to the N. Z. Radio Record of Dec. 23: "Mr. Fletcher insists on carrying on his radio work. 'I love it.' he says. So do his nephews and PIECES.'' If you see a man with an arm or leg missing you'll know he's been tuned in on 1YA. But they like it. Contributed by W. Satterly (New Zealand)

LADY LUCK, THEIR PATRONESS



THEIR PATRONESS Interesting item from the Cincinnati Enquirer of Jan. 8: "For some time KWKH has been styling itself as 'the SUPERSTITION of the South?" We were well aware that the South is the land of the rabbit's foot, horseshoe, conjures and other things smacking of the supernatural; but this is a new one on us. Where's it worn! Contributed by Roy J. Satyper.

PRODIGIOUS PORTABILITY

PRODIGIOUS PC Exacting r c q u i r e-ments for the set con-structor in a prize compe-tition sponsored by the S out h African II ircless Wcckly, of Dec. 14: "The C O M P A C T N E S S and weight must be reduced to a MINIMUM." Much in-genuity was required by these terms: but the prob-lem has at last been solved by a gas-filled cabinet. Contributed by Edwin Potter, (So. Mrica)

HELP FOR THE FARMERS



THE FARMERS Advertisement found in the Toronto Daily Star of Ian, 16th: "R AD IO STABLE and tubes, prac-tically new, real snap." No, Mirandy, I ain't agoin' to get' outa bed this cold mornin'. Let that gol-durned radio feed the stock. Waddya thiuk I paid that agent all that money for, if I have to get up and do the chores? No. sirec. Contributed by H. Garlick.

HAIL, HAIL, THE GANG'S ALL HERE!

SHTAT

HAIL, HAIL, THE GA Volsteadiau motif in re-ceiver design, mentioned in the Radio World of Dee. 3: "A friction drive RUM is employed. . ." this in connection with a gang con-denser. We wish the manu-dacturers of sets to under-stand that this bootleg stuff can NOT be trusted. We want the varnish left on our set, so well stick to the old dials. *Contributed by Wim. Wiche.*





YOU TELL 'EM!



SEXTRACION RY

A .07

PAGE MR. WEBSTER In Crosley's advertisc-ment in Radio News, Feb-ruary, 1928, a new adject-ive is discovered that smacks strongly of Elinor Glynn: "The new type D Musiconc is a SEX-TRAORDINARY as its companions and promises Al usicon c is a SEX-TRAORDINANY as its companions and promises great satisfaction. . . "At last a loud speaker with sex appeal! Boys, remem-ber the female of the spe-cies is more deadly. . . *Contributed by* L. 11'. Battin,

For the property of the printed printe

Editor, RADIOTIC DEPARTMENT, c/o Radio News.

Is THIS FADING? Why you lost that sta-tion the other night is re-vealed in the Chelsea, Mass. Record of Dec. 30: "It is alleged hy the police that the boys stole 643 pounds of R.DIATION, valued at \$20 from Philip Lewis' junk shop." Our guess is that the junk man collects worn out radio waves and peddles them to stations dissatisfied with their wave-length allocations. Contributed by Don Emery.



DUCK, MEN, HERE THEY COME In the Chicago American of Dec. 24 we see this in-teresting piete of informa-tion: "These statious will try out 200-meter broad-casting next week: WORI using 5000 watts and WB-BR 1000 MATTS." There is no doubt in our mind that WIBBR would cover quite a stretch if these matts were rubber. We'll quit. quit.

Contributed by Owen McArdle.

FOR THE RURAL RECEIVER

FOR THE RURA Pastoral gesture from the Chicago Evening Post of Jan. 5: "A quarter-inch GRANS shaft is provided so that the condenser may be used as any ordinary variable condenser." When your set doesn't tune in a station so very well, you might look inside and see if someone thoughtlessly used grain or alfalfa, there-by elogging up the works. Contributed by Ronald A. McNeill.





WASHINGT

OUR BATTERY A new method of remov-ing battery oxide is men-tioned in the *I*¹*CFL*. *Radio Maguazine*. (Vol. 1, No. 2): "The green oxide may be removed.... by pouring warm WEATHIER slowly over the surface of the bat-tery." Mike of the Inves-tigation Dept. is now on his way to Washington to get some warm weather from the Weather Bureau. He's having a hot time (?). *Contributed by R. J. Haase.*

WHAT PRICE EUGENICS?

WHAT PRICE I Commenting on a new type of antenna, the Radio World of Dec. 31 says it is "so simple a \$4 child this cugenics and compan-ionate-marriage stuff stir-ring up the country, you can't be sure of anything these days. \$4 is a low price for a healthy child; but the trouble isn't the initial cost—it's the upkeep. Contributed by R. Calvacchi.



AFTER YOU, MY DEAR GASTON



MY DEAR GASTON Influence of the Book of Etiquette upon electric phe-nomena related in the Ra-dio II orld of January 21: "The alternating current does not flow through the condenser. It BOWS in and out of the condenser." We should, indeed, be able to extract the height of harmony from radio sets operated by so considerate a medium. Contributed by W. S. Roscuik.

FOOD FOR THOUGHT

FOOD FOR T Television is with us. and also other things reported in the News Sentinel, of Fort Wayne, Ind., on Jan. 14: "Light BEANS Take Pace of Sound Wave in Ordinary Radio." Soon in old New England, in the heart of the Bean Belt, the good housewives will dis-card their ovens on Satur-day and use radio to get the Sunday breakfast. Contributed by D. R. Baker.



EXPENSIVE FUEL



A burning question is found in an advertisement in the Portland Oregon Daily Journal of Jan. 20: "\$950 brand new 8-tube R a d i o l a and Brunswick Panatrope COMBUSTION ..." Mike of the I. D. informs us that coal is still rather expensive but, hon-cstly, we would rather hurn coal than stuff that costs anything like that men-tioned in the advertisement. Contributed by J. L. S. Sucad.

TWENTY-FOUR VOTES FOR-

TWENTY-FOUR V Forerunner of the coming political campaign men-tioned in the Radio II orld of Dec. 31: "IRE Conveu-tion Here Soot." We have finally persuaded Mike of the Investigation Dept. to run for Generalissino of Broadcasting. Among his other jobs will be to find out why tenors live. They're the outes that are stirring up all the ire. *Contributed by L. Geiser.*

L. Geiser.



www.americanradiohistorv.com





Conducted by C. W. Palmer

THIS Department is conducted for the benefit of our Radio Experimenters. We shall be glad to answer here questions for the benefit of all, but we can publish only such matter as is of sufficient interest to all.

1. This Department cannot answer more than three questions for each correspondent. Please make these questions brief; if the inquiry is concerning a circuit other than a standard, published one, delay will be prevented by enclosing a diagram and other necessary information.

2. Only one side of the sheet should be written upon; all matter should be typewritten or else written in ink. No attention paid to penciled matter.

3. Sketches, diagrams, etc., must be on separate sheets. This Department does not answer questions by mail free of charge.

4. Our Editors will be glad to answer any letter, at the rate of 25c. for each question. If, however, questions entail considerable research work, intricate calculations, patent research, etc., a special charge will be made. Before we answer such questions, correspondents will be informed as to the price charge.

WHAT IS DETECTION?

(2272) Mr. R. J. Wentworth, of St. Louis, Mo., writes:

(Ω.) "Will you explain how crystals and vacu-um tubes operate, when used for 'detecting' radio

signals?" A. The crystal detector, which was very popu-lar several years ago, and is still used in a very large number, if not a majority, of the radio



Three radio circuits using common detection methods: 1, crystal: 2, plate-current or "bot-tom-bend" rectification, with negative grid bias; 3, grid rectification with positive bias regulated by grid leak and condenser.

receivers outside of the United States, has the peculiar property of offering a higher resistance to electric currents passing through it one way than it does to those passing in the opposite direc-tion. The radio-frequency alternating current, which we call the *sigual*, comes from the aerial (or possibly through an R.F. amplifier) and tries to pass through the crystal, first in one direction, and then in the other; but its flow is practically confined to one way, because of the increased resistance offered to the current whenever it is reversed. Thus, only one-half of the incoming current passes through the headphones in the simple crystal-detector circuit shown by the dia-pram in Fig. 2272A at (1). When we use the well-known three-element vacuum tube as a detecting or "rectifying" radio signals; they are called "plate rectification" and "grid rectification." While the first is more casy to explain diagrammatically, the second is more

"grid rectification." While the first is more casy to explain diagrammatically, the second is more commonly used. In addition to its detecting effect, the tube introduces also the action of "amplifica-tion." A rather simple analogy may serve to convey the idea, though not with complete details, in a form easier to comprehend. We may compare the radio signal to waves caused by agitating water; these will travel a

considerable distance, and by this means we might, considerable distance, and by this means we might, for instance, send a message. Disregarding the complexities which are presented by the very in-tricate sounds of music and speech, let us con-centrate on the idea of sending a succession of impulses, in the form of waves, which are com-parable to the dots-and-dashes which puzzle, and accasionally aunoy, the ordinary radio fan occasionally annoy, the ordinary radio fan.

A Hydraulic Comparison

A Hydraulic Comparison If we dip out and pour back a bucketful or so at more or less regular intervals from aud into the body of water which is to be our medium of succession, for a considerable distance from our of the water, for the bucketful we pour in stars near us for a considerable length of time; it is a backward-and-forward, up-and-down motion, cor-voltage" changes that we picture when we talk of a "radio wave." We can put a small float of the surface of the water, at the point where wish to receive the message carried on these at the surface of the water will spill over; but when of all our excision water will spill over; but when the "crest" arrives, it will break over the top of our little dam. This action we may compare to that of our crystal detector, which respond to four little dam. This action we have one that of our of the value, buck, " that is, the impulse in the radio wave by passing only the half of it when is "alove the line;" that is, the impulse on the radio wave by massing only the half of it when the surface on the so-But we desire to get something more than the

very feeble little wave which we thus receive;

very feeble little wave which we thus receive; we want to put in motion in one channel a much larger amount of water. Here is where the "am-plifying" action comes in. A radio tube is truly a "valve," as they call it in Europe; a small volt-age applied to its grid, under certain conditions, *turns on and off the current from the "B" battery*, which is much greater in its electrical effect. To illustrate the action of a tube, we have what is known as its "characteristic curve." Without explaining too technically the action it represents (see the department, "The Radio Beginuer," in this issue) this curve indicates the amount of "plate current" which the tube passes, for any given amount of voltage difference between its filament and the grid and with a fixed value of plate voltage. The plate current is proportioned to the *height* of any given point on the curve just above the point on the scale indicating the corre-sponding grid voltage. At the bottom we have shown the effect of a typical "train" of radio waves on the grid voltage, and in the horizontal curve the corresponding "wave" in the plate cir-cuit of current which can be used to actuate the diaphragm of a telephone (See Fig O 2272 C) cuit of current which can be used to actuate the diaphragm of a telephone (See Fig. Ω , 2272 C.)

Returning to our water analogy, the simple rectifier, such as the crystal, cannot put into the rectiner, such as the crystal, cannot put into the telepthones any more energy than it receives—less in fact, as current is used up in overcoming its resistance. Just so our little dam in Fig. Ω . 227211 (2) must surround a depression kept lower than the water level, so that the incoming wave can spill into it.

The Hydraulic Amplifier

But we can use the rise and fall of a float on the waves to operate a gate and control the



Above is a comparison of radio detection with that of water waves. In 1 and 2 we have simple "half-wave" rectification; only the top half of the wave spills over the dam. In 3, 4 and 5, the float repre-sents the tube grid, and the water in the aqueduct the plate current. In 6 the tank represents the grid condenser; it discharges through the "siphon" (the grid "leak") when the pressure becomes high enough.

flow of water from a higher level to a lower, as flow of water from a higher level to a lower, as in Fig (0.2272B (3). Above our float we have an aqueduct containing a "weir," or water outlet, and a "shuice gate" regulating the flow of water. This gate, when it is perfectly level, permits a very slight amount of water to escape. It is pivoted far over to one side, so that tilting it one way permits a great deal of water to escape; while tilting it the other way practically cuts off the flow. We connect one end of this sluice to our little float. the flow. We onr little float.

our little float. When the float rises, as pictured at (4), a great deal of water escapes; when it falls (5), the flow is practically cut off. The result is that, as the waves come in aud lift our float, they increase and decrease the flow of water, at a much higher level and to a much greater amount; but that flow is steady and in one direction, not the back-ward-aud-forward motion of waves. This is also the difference between the radio wave and the direct-current impulse which operates our tele-phone diaphragm.

Plate-Current Rectification

Returning to the electrical action, Fig. Q.2272C shows the *flate-rectification* effect which corresponds to the apparatus we have just described. It depends on the "bend" which we see at the bottom of the "characteristic curve" of our tube, and which corresponds to a limiting range of negative grid voltages, varying with the type of tube. In order to keep the grid at this negative voltage, compared with the filament, it is necessary to use a "C" battery or voltage-supply source with its positive terminal connected to the " $\Lambda \rightarrow$ " for the " $\Lambda \rightarrow$ " voltage alone is not far enough below that of all points on the filament. Such a "C" battery is usually composed of several dry cells in series; or the "voltage drop" between the ends of a resistor in a power unit may be used for the purpose. (Fig. Q2272A at 2.) Returning to the electrical action, Fig. Q.2272C

(22272A at 2.) At the bottom of the diagram, below the bend in the characteristic curve, we have pointed out the "voltage wave form" of the incoming radio wave. If we draw a line directly upward from any point on this curve, representing the voltage on the grid at that instant (the grid negative volt-age or bias," plus or minus the voltage of the received signal, according as the incoming wave is at a positive or a negative stage) until it meets the characteristic curve, and then extend another line horizontally to the upright scale marked "plate current." we will get the value of the current flow-ing between filument and plate at that instant. If, for each value of the plate current, we find the corresponding value of the plate current, we can draw the resulting wave form of the plate current— which is all divect current. It will be seen that there is present some "distortion" of the wave form; that is, the variations in current are greater in one direction than in the other, when compared with the resulting is present. with the variations in voltage. In the diagram this result has been exaggerated to make it evident.

It is plain that we have in this case, not a true rectifying action, as with the crystal—but a relay or *amplifying* action. It will also be noticed that, with this method, no current flows in the grid circuit—unless the grid is allowed to become positive—and there is no drain on the "C" battery.



"characteristic curve" of a vacuum tube is The "characteristic curve" of a vacuum tube is a diagram of the amplification it gives, and every student of radio should be familiar with the idea sepresented. The "signal" in every tube comes in as voltage on the grid; it goes out as current through the plate circuit. A "characteristic currer" drawn for a given tube, at a given plate voltage, shows what response may be expected from it for any given grid bias. The

Grid Rectification

When we refer again to Fig. Q.2272A, at (3), we find that the grid return has been changed from the " Λ ---" to the " Λ +" filament lead, and that, in place of the "C" battery, we have a "grid leak" and a "grid condenser" in the grid-filament circuit. This places on the grid a positive bias of half the value of the voltage across the filament (when the grid is compared with the middle point of the filament); this is usually sufficient, without requiring an external application of positive voltage. tive voltage.

The action when this method is used is as fol-lows: the incoming signal voltage tends to send a current through the circuit, from the grid to the filament, and back again. But this current can flow in only one way, from the grid to the filament; because of that property of the vacuum tube which permits electrons to travel only from a hot element (the filament) to a cold one (the grid or the plate). This current flow builds up an electric charge on the grid condenser, and causes the voltage on the plate of the condenser, which is nearest the grid to become negative, as well as the grid itself. Whenever the radio wave reverses, it merely The action when this method is used is as fol-

well as the grid itself. Whenever the radio wave reverses, it merely stops the flow of electrons; for the space between the filament and the grid will pass a current in only one way. Thus the flow from the filament keeps increasing the negative charges on the grid until they oppose the incoming signal voltage and overcome it. The grid leak then allows the charge to leak off through the grid return to the filament. This cycle is repeated with each train of waves, the grid being in the same condition at the end as at the beginning. The resistance of the grid leak

the grid being in the same condition at the end as at the beginning. The resistance of the grid leak must be of a suitable value, to secure smooth operation, however. This variation of the voltage on the grid, caused hy the incoming signal, will also produce a varia-tion in the plate current; as the grid becomes more negative, it decreases the flow of current from the "B" battery or power unit; and, as it becomes positive again, the flow of plate current becomes normal. normal.

It will be, perhaps, more difficult to explain the difference between these two methods of tube detection by our hydraulic-gate analogy, to the satisfaction of our readers. They would correspond detection by our hydraulic-gate analogy, to the satisfaction of our renders. They would correspond most closely to a readjustment of our wave-operated float, and of the point of pivoting in the shuice-gate which it opens and closes. In oue method, we may say, the *rise* of the float closes the open-ing; in the other, the *fall* of the float closes the gate. Also, let us suppose that, to correspond with the grid-rectification process, the float is in a compartment into which successive waves spill, cach raising the float a little more, until the water rises above an overflow level and discharges through a *siphon* (6). In comparing this system to radio waves, we must suppose that these waves are created in series or "trains" by the millions, in regular succession with varying intervals and heights; and it is our desire to gauge, not the height of single waves, but the respective rapidity of the changes which are made in the rate of their production and the height of their crests. This corresponds to "modu-lation" in radio; and the reverse process is "detection."

lation" in radio; and the reverse process is "detection."

There are several differences between these two There are several differences between these two types of tube rectification. Plate rectification does not consume any grid current, normally; but with grid rectification there is a flow of eurrent (drawn from the " Λ " battery) in the grid circuit. An-other difference is that the plate-current method produces the sounds in the plate share an *increase* in the plate current; the grid-current method by a *decrease* in the plate current. The latter actu-ally rectifies the incoming signal in the *grid* ciri-cuit, because the changing bias on the *grid* allows the grid current to flow in only one direction; the former rectifies the current in the *plate* circuit, because it is possible for it to flow there in one way only.

because it is possible for it to now there in one way only. The sum of the current changes, with either method of detection, over a period of thousands of cycles of the radio wave, will be found to correspond very closely to the electrical modifi-cation caused at the microphone of the broadcast tation is the sounds of scaech or music which ware station by the sounds of speech or music which were being hroadcast. For this reason, the phones or loud speaker in the output of a detector circuit will reproduce these sounds very closely.

Modulation and Rectification

The grid-rectification method is more sensitive, because the effect of the small individual waves of the signal impulses is "cumulative" in its influence on the plate current, thereby producing much greater voltage changes on the plate than does the plate-rectification method. See Fig. 2272D. Each audible note reproduced in radio is con-

verted into electrical alternations (1) at rates varying from about 30 to 5,000 per second; and then allowed to *modulate* more powerful alterna-tions (2), made at a rate of from 550,000 to 1,500,000 per second, in the case of ordinary broad-cast stations. In the case of short-wave stations, the carrier-frequency alternations may be at the rate of 20.000,000 a second. It is evident that each vibration of a 256-per-second (256 cycles equals "Middle C" on the piano) audio-frequency



In the illustration above, 1 and 2 represent the broadcast A.F. modulating wave and the station carrier wave, which are combined by "modulation?" to form the alternating signal wave shown at 3. At 4 we have the result of detection, a somewhat distorted, pulsating direct current; this is separated by suitable means into an A.F. direct-current signal impulse, 5, and an R.F. component, 6, which is by-passed back to the filament, used for regeneration, or otherwise disposed of.

note covers the period of 5,000 alternations of the carrier wave of a 1280-kilocycle (234.2-meter) hroadcast station; and its influence is therefore spread over 5,000 successive alternations on the grid of the detector tube of a radio set receiving a broadcast from this station. It is therefore desirable that, so far as possible, the effects of the carrier-wave be eliminated entirely from the audio stages of a radio receiver; as their presence (6) causes a "radio-frequency conponent," which is a source of trouble, and is combated by the use of radio-frequency chokes (the action of which was described in this department for February).

ELECTROLYTIC RECTIFIERS

 $(\Omega, 2.)$ "I would like to obtain some information, about electrolytic rectifiers and the solutions used in them. What is the best electrolyte, and what are the comparative advantages of ammonium phosphate and ammonium borate over the usual borax used in aluminum-lead-type rectifiers?"

used in aluminum-lead-type rectifiers?" (A. 2.) In the usual home-constructed rectifier, a saturated solution of commercial borax ("sodium biborate") is employed. This electrolyte is suit-able in most cases; but if the borax is not entirely pure considerable trouble may be encountered. Am-monium phosphate or ammonium borate dissolved in distilled water, is much more suitable. The former is prepared by dissolving as much "pri-mary" or acid ammonium phosphate as the water will take up, thus making a saturated solution. Crystals should be added until they fall to the bottom, and then the liquid should be filtered off and used. A similar procedure may be followed with the borate; care should be taken to procure a chemically-pure "salt."

The ammonium-phosphate electrolyte may be al-The ammonium-phosphate electrolyte may be al-lowed to stand idle for a long period of time with-out injury. The ammonium-borate electrolyte, dur-ing an idle period, will increase its internal re-sistance, which causes the voltage to drop off cou-siderably. In some cases, it is necessary even to scrape the electrodes to make the rectifier function. The annonium-borate solution reacts upon the lead plate: thus forming "lead peroxide." which gradu-ally falls to the bottom of the container. No such trouble is encountered with anunonium phosphate. The aluminum clectrode should be of the puresu metal obtainable; since any slight impurity will cause a "local action" which will ruin the recti-fer. It is advisable to place a rubber tube over the aluminum plate at the point where it leaves the solution, so that exidization cannot take place at this point.

(Continued on page 1191)



1153



Radio News for April, 1928

A Novel Radio Dial

TUNING devices have assumed many odd shapes; but there is a great deal of ingenuity in the indicator now used on a French make of receiver. The pointer of one tuning condenser moves horizontally, and the other vertically, across a scale; and their intersection shows the position of the station tuned in. \mathfrak{Z}^* will be noticed that



Tuning scale of a new French receiver, for two wavelength bands.

there are two curves across the chart of wavelengths. One represents the lower range of European broadcast stations, practically equivalent to our broadcast band; and the other the long-wave stations, between a thousand and three thousand meters.

The Voice of Wales

WELSH members of the English Parliament have united in a demand on the British postmaster-general for the establishment of a broadcast station in Wales devoted exclusively to programs in the Welsh language. It is represented that this would be a great stimulus to the sale of radio sets in Wales, as well as of cultural value.

Airplane SOS Saves Ships

THE "SOS" has more than once of late called shipping to the assistance of aviators; the compliment was returned in the English Channel not long ago, when the pilot of a London-Paris aerial express observed that a small steamer below him was on fire. He at once used his transmitter to notify Croydon, England, which broadcast the alarm. It was picked up at Boulogne, France, from which port a tug at once put out, rendered timely aid, and towed the distressed vessel with her crew of fifteen safely into port.

A New Radio Gadget

FROM the columns of our British contemporary, *The Wireless Trader*, we reproduce the illustration of a new accessory, which, as its editor remarks, is long overdue. The vessel is composed of baked red clay, like the ordinary flowerpot, but is equipped with a handle, and filled with the highest quality of ground, in which is embedded a small copper terminal for quick connection to the "ground" terminal of the receiver. This convenience is, of course, especially designed for

especially designed for use with portable receivers; but may, suggest the makers, be used as well for growing rhubarb or hollyhocks. (We would suggest currants, but care must be taken that the fruit does not fall from the shrub and go astray.) As April brings pleasant outdoor and garden



A new portable ground, designed by a British inventor.

weather, as a rule, there should be a considerable demand for this portable ground —especially around the first of the month. Our enterprising American manufacturers will undoubtedly be prepared to meet it.

A Proposed Television Set--"The Motorist's Friend"



The Bystander.



If you do not have a piano, use it on the table or a panel, or door. It works!

You Ever Spent!

Sold under money-back guarantee. You must be satisfied or your money will be refunded. Price only \$10.00. Complete with 20-foot cord. Ask your dealer or send order to our nearest office. Shipped prepaid on receipt of check or money order or C. O. D. with postage added. Price in Canada-\$11.50

25 CHURCH STREET NEW YORK 28 E. JACKSON BLVD. CHICAGO, ILL. 331 BAY STREE TORONTO, ONTO	
--	--



Television Comes to the Home

(Continued from page 1100)

But there is another side to the story. In studying radio reception, as we know it today, static, interference and fading are factors about which very little is known. These are also present in television, but instead of being andible they are *visible*. Not only that, but the eye is more sensitive to differences in shading and minute changes of position than is the ear to differences in sounds. For that reason, the study of the problems of transmission will be made much more effective by the use of television apparatus.

In television "static" appears on the screen as black splotches, which momentarily blot out the image. "Fading," such as that experienced in voice transmission, results in, literally, the gradual fading out of the image on the lens. When the receiver is oscillating or "squealing" the image has more contrast; *i.e.*, the shadings and shadows become a dead black with a corresponding lightening of the "high lights."

Another interesting part of radio transmission, which is brought out by television, is the "echo image." This condition is evidenced on the lens by a double image, i.e., the appearance of a perfect secondary image beside the fundamental image, and almost as strong. This occurs only under certain weather conditions and is believed to be a visible "echo" of the wave due to vertical reflection from the electronic layer of the upper atmosphere. The echo image is usually displaced on the lens to a distance corresponding to a delay of one fifteen-hundredth of a second; showing that the echo wave had travelled about 124 miles and yet was nearly as strong as the other, which had only travelled a few miles. Obviously such phenomena as this could never be detected by the ear.

A NEW TYPE OF ANTENNA

Experiments in the fields of television have brought about a new type of antenna, which is illustrated in Fig. E. From the arrangement of the wires it has been named a *checkerboard* antenna; the sides of each square being equal to half a wavelength. All these half-wave antennas are connected in such a way that they oscillate *in phase* and require no tuning.

The checkerboard antenna is *not* a beam antenna, although all the energy is projected in the general direction toward which it is desired to transmit. The angle at which the antenna is arranged is of great importance; for example, the one shown in Fig. E is intended for work with San Franeisco and the left side of the illustration is toward the west.

As mentioned previously in this article, there are still many mechanical and electrical obstacles that must be overcome before television apparatus, such as that illustrated here, can be available for ordinary home use. But the important thing is that it is at present a reality, and no longer merely an engincer's dream. In three homes in Schenectady today television receivers stand beside the regular broadcast receiver and, although members of the families at present have to crowd a bit to see what is coming over the air, yet the time surely is not far distant when they will be able to sit comfortably before the television receiver and see with the same ease as they hear today.

There certainly can be no doubt that we are on the threshold of a new era. Television has been demonstrated several times before in this country and abroad; but now it has been brought into the home in a manner that can be readily comprehended and by apparatus simple enough for the average man, who is not mechanically inclined, to operate. And that is a real step forward. Although it is the technical man and the experimenter who have made radio what it is today, the layman—who is typical of the great majority of radio enthusiasts—is the one to be pleased and catered to in the perfection of radio utilities.

A Novel Automatic Volume Control

(Continued from page 1131)

while with a "voltage-squared" detector, the average rectified voltage is proportional to the average total power of carrier and sidebands. This last feature is worthy of mention in connection with the control system; since the automatic grid bias should depend on only the carrier amplitude, independent of the modulation.

With the circuit constants shown in Fig. 1, the time constant of the circuit which connects the rectifier to the grids of the control tubes is 1/40 second; so that the control system comes nearly to equilibrium in 1/20 second. This time can be reduced further if necessary, but is ultimately limited by the allowable reduction of the signal modulation at the lowest audio frequencies. In consequence of the automatic control action, it becomes difficult to tune the receiving set accurately by car to a desired signal. The amplification is decreased as the response to the signal is increased by tuning, and *vice versa*: so that the point of resonance is indicated by minimum plate current in the radio-frequency amplifier. Taking advantage of this fact, a millianmeter (MA, Fig. 1) is connected in the plate circuit of the first tube, to be used as a resonance indicator, and also to give an indication of relative signal intensities.

USE OF "B" UNIT

There is an incidental problem in supplying the plate current to all tubes of the set described, from a common rectifier-and-filter

Radio News for April, 1928

system. In the controlled radio-frequency amplifier tubes, when operating at low plate current, the signal carrier is modulated appreciably by small fluctuations in the plate voltage. Such fluctuations are caused by plate-current pulsations in the audio-frequency amplifier. In the presence of a strong carrier wave, these two effects may cooperate to generate a low-frequency oscillation. This disturbance may be avoided by reducing the internal output impedance of the rectifier filter, by decreasing the amplification at low frequencies in the audiofrequency amplifier, or by using separate rectificr-filter systems to supply the plate currents of the radio-and audio-frequency amplifiers, respectively.



The above graph shows the nearly-vectilinear proportionality between the alternating and the simply-vectified voltages as against the output of a three-element detector.

The performance of the automatic volume control as described can be summarized briefly as follows. A maximum variation of signal voltage in the ratio of 1:1000, corresponding to differences in distance, fading, or tuning, results in a maximum variation of the rectified earrier voltage in the ratio of only about 1:3. This small variation, together with possible differences in the degree of modulation of different stations, can readily be compensated if necessary by adjusting the manual volume control for the audio-frequency amplifier, which also determines the "volume level" for the automatic volume control.

The name "Audiostat" has been selected for this device, by reason of its tendency to

40 Non-Technical Radio Articles

every month for the beginner, the layman and those who like radio from the nontechnical side.

SCIENCE AND INVENTION, which can be bought at any newsstand, contains the largest and most interesting section of radio articles of any non-radio magazine in existence.

in existence. Plenty of "How to Make It" radio articles and plenty of simplified hook-ups for the layman and experimenter. The radio section of SCIENCE AND INVENTION is so good that many RADIO NEWS readers buy it solely for this feature.

Radio Articles Appearing in April Science and Invention Magazine

Photographs in the Home by Radio New Broadcast Station in Milan, Italy An All-Electric Six Exponential Horns—How to Make Them New Radio Devices Radio Oracle—Questions and Answers Latest Radio Patents Radio Wrinkles



1157

BRIDGE

45 stations broadcast every week

Take your daily lesson now--

get any one of these Bridge Books to help

By Wilbur C. Whitehead:

Complete Auction Bridge	\$2.00
Auction Bridge Standards	1.50
Auction Bridge Summary	1.00

By Milton C. Work:

Bridge Pointers and Tests	\$1.00
Contract Bridge	1.50
Auction Bridge Complete	2.00

Foster's Contract Bridge	1 00
100 Bridge Lessons	.50 50
Practical Auction Bridge Shortcut to Standard Auction Bridge.	2 00 1.50
Auction Bridge (Annual Magazine)	.75

Prepared by Famous Broadcasters

"Listeners in ' need no introduction to Work and Whitehead. They are the most famous of Bridge Broadcasters, and masters of the game.

This is a selection of their best books.

Many of the plays that did not clear up in your mind over the radio can now be studied at leisure.

Whatever is to be known about Bridge will be found in these books.

These are books to fit every need and every purse.

Pick your books now—and be assured that your knowledge will be coming from masters

Each book is well bound, printed in legible type, and contains anywhere from 160 to 500 pages.

Order Direct

CONSRAD CO., INC. 230 Fifth Ave., New York City maintain the audible intensity at a constant value.

Attention might be called to British Patent 259,664 (Western Electric Co., July 14, 1925), in which a somewhat similar system is presented. This other system is applied to a superheterodyne receiving set, and is more involved in several respects than the system described in this paper. It is desired to acknowledge the co-operation of the Howard Radio Company of Chicago, in whose laboratory the set described was assembled.

(From an address delivered before the Institute of Radio Engineers, at a meeting in New York, Nov. 2, 1927, and published by permission of the I. R. E.)

Controlling Volume in Your Receiver

(Continued from page 1137)

500,000 ohms to one megohm can be obtained. The resistor used in method B should have a maximum value of about one megohm.

In the preceding paragraphs we have discussed in a general way various common methods of volume control and have pointed out, to some extent, the relative advantages and disadvantages of the various methods. The reader should now have a good conception of their operation and characteristics. One phase of the subject remains to be covered, which is whether, broadly speaking, it is better for the volume control to be before the detector (in the R.F. amplifier) or after the detector (in the audio amplifier).

R.F. METHOD RECOMMENDED

In general, it can be said that the volume control should be placed ahead of the detector. The signals received from local stations are comparatively strong and, after amplification in the R.F. amplifier, the voltage is considerable. A detector tube can handle voltages only up to a certain value, beyond which overloading takes place and distortion results. If the distortion is to be prevented, the input to the detector must always be kept below the overloading point. If the volume control is located ahead of the detector tube, this is possible; but if the control is located in the audio amplifier a reduction of the signal strength before detection is not possible and overloading of the detector may occur.

The control of the output from a superheterodyne type of receiver is best accomplished in the intermediate-frequency amplifier. A high resistance in series with the "B+" load to the intermediate-frequency amplifier will serve very well. In many superheterodynes the oscillation control, regulating the amplification in the I.F. amplifier, is used also as a volume control.

Owners of receiving sets equipped with poor volume controls must frequently rcsort to detuning one or more of the R.F. stages to adjust the volume properly. Such practice is not to be recommended, and a better volume control should be installed in the set.

Why Batteries are Still in Fashion For Short-Wave Receivers

ANY of us have probably wondered why, in the numerous diagrams appearing in the various radio publications, of short-wave receivers, whether designed for short-wave-broadcast or code reception, "B" batteries, rather than socket-power devices, are always designated as a source of plate supply. That there is a good reason for this, however, is indicated by some interesting tests recently made.

In the first place, a short-wave receiver is almost invariably of the regenerative type, consisting of a detector and one or two stages of audio amplification. It is de-signed on the low-loss principle (which in short-wave reception really means something) and consequently is extremely sensitive and must be capable of maintaining the most critical adjustments. When it is used in connection with a power unit, the remaining unsuppressed A.C. hum, which may be entirely unnoticed in the ordinary broadcast receiver, becomes pronounced and grows in intensity as the regenerative coupling is tightened. In addition to this residual A.C. hum, the alternating-current variations may also be picked up through the antenna system. Many radio fans, who possessed in the old days broadcast receivers of the regenerative type, will probably recall how easily the 60-cycle hum was

picked up when the aerial lead-in paralleled the house wiring, even though it might be separated by many feet, and how the proximity of an electric light was sufficient to also cause this effect.

Furthermore, a stable plate current is vital to success in short-wave reception. The tickler is almost always in a state of micrometrically-critical adjustment; consequently, if the plate current is not stabilized and varies ever so slightly, it will cause the tube to spill over, thus necessitating readjustment. As the A.C. input to the power unit is varying constantly and this variation on a smaller scale, is reflected in the output of the device, the impossibility of maintaining a state of critical adjustment is obvious.

This varying voltage is a factor also in broadcast reception on the higher waves, and has caused a few manufacturers of "B" power units to incorporate a regulator or glow tube in their outfits. This glow tube has as its function the preservation of a uniform current flow, but, unfortunatoly, its current consumption is so heavy that it can be used only in climinators especially designed for it; as otherwise it drags down the over-all voltage, causes choke-coil core saturation, and intensifies the A.C. hum.

Because of the sensitivity of the short-
Radio News for April, 1928

wave receivers to all forms of electrical disturbance, background noise must be eliminated whenever it rests within the power of the set operator to accomplish this. Power units, when used on short-wave receivers and highly-sensitive broadcast sets, are inherently noisy, owing to line fluctuations. If some kind of vibrating household device, which operates on the make-andbreak principle from the house current, is in use, it will generate strong waves, which will probably be picked up by the receiver through its antenna even when "B" batteries are used. However, when the receiver's plate supply is obtained from the same power source as that operating the interfering device, the interference will be greatly magnified. In neighborhoods supplied with direct current for lighting, because of the fact that connections are direct rather than through transformers, interference of this character may attain astonishing volume.

For this reason, additional importance is to be attached to the increasing vogue of constructing the power unit and amplifier as a separate instrument from the receiver proper-R.F. and detector. Not only is there greater flexibility in the use of a phonograph combination with the amplifier; but a small, highly-sensitive short-wave receiver may be used with the amplifier for the purpose of receiving the programs now available from great distances. Even with a stage of R.F. ahead of the regenerative detector, as in the short-wave broadcast receiver described in this issue of RADIO NEWS, the amount of current consumed by the two tubes required would be but a small drain on batteries and entail little trouble.

Weighing in Radio Stations

(Continued from page 1122)

receiver and a conc-type loud speaker. On the other end of the table were a pair of scales and a number of weights, which were labeled with the call letters of the popular nearby broadcast stations.

"Now, gentlemen," continued Randall after the lable had been moved to the center of the room, "if you will suggest the call letters of a station you would like to hear, I will endeavor to show how my set operates." Someone called out "WJZ" and Randall selected a weight, placed it on the scales and turned on the filament switch. Much to the surprise of everyone, the signals from WJZ were heard coming from the speaker.

Jack Dallas was the most skeptical mem-



By adding shot to a hollow weight and plugging it with a cork, the tension can be determined at which stations are tuned in.





Write for our list of "Specials" -lowest prices in country.

DIO LECTRIC NEW YORK CITY 116 WEST 65th STREET

ber of the party, and he immediately said that he considered the demonstration a fake. To prove his point he placed the WEAF weight on the scale and to his surprise WJZ's signal disappeared, but WEAF was not heard. Randall immediately explained that he should remove the WJZ weight, and then WEAF could be heard. This was tried and found to be true. All persons in the room then became interested and, for the next hour, we tried placing the various weights on the scales; and, in each case, the loud speaker brought in the signal of the station which was called for.

THE SECRET EXPOSED!

When Randall was asked for an explanation of his new receiver, he lifted the table cover and disclosed a large coil spring which had been concealed beneath the table.

"It is very simple," he explained. "The coil spring which you see under this table acts as a loop aerial for the set on the table and, at the same time, it serves as the grid coil for the first R.F. amplifier tube of the set. You will notice that one end of the coil is attached to one side of the scales in such a way that, when weights are placed on the other side of the seales, they will cause the coil to expand in length. Probably you know that the inductance of a coil decreases as the separation between the turns is increased; and this principle is used in tuning the set. A heavy weight placed in the scales will greatly increase the length of the coil and, as a result, tune the set to a low wavelength; whereas a much lighter weight is used for the high-wave station."

"Well, Randall," exclaimed Jack Dallas, "Your set provides a fine after-dinner trick, even if it isn't of much value to the radio industry. Give me the full details sometime so I can fix up a set to fool the folks back home."

"Sure, I'll be glad to," Randall replied: "This arrangement is the easiest thing in the world to fix up, but it takes considerable time to make weights of the correct size. The first thing you need is a loop-operated radio receiver, which may be tuned with a single variable condenser. In most cases the set must have three stages of untuned radio-frequency amplification, as other systems usually require a more complicated tuning arrangement. The size of the spring coil isn't very important; as the set can be adjusted to the desired waveband with the variable condenser and then the weights may be used to select the various stations. Twenty-five turns of aerial wire wound on a hat box are used, and they make a very satisfactory loop antenna."

"There are any number of systems which may be followed in making the weights, and none is very difficult. I used some weights which I found in the laboratory and filled them with a sufficient quantity of shot to tune in the desired station. However, pill boxes, which you can buy at any drug store, would be just as satisfactory and might make the trick even more mysterious; as they are all of the same size. It is also possible to add to the trick by placing a weight in both pans of the scales. Of course, the weight in one of the pans would be the same for all stations, and the weight in the other pan must be changed each time."

"Now that we know what it is, and how it works, tell us how you thought of the

idea, and why," someone asked. "Well, I'll tell you," Randall answered: "Last week, while experimenting with my new invention, I dropped my fountain pen and its weight on some wires changed the inductance of the circuit enough to tune in a new station. That gave me the idea and I could not resist the temptation to have some pleasure at the expense of a few curious persons who have tried to find out what I am doing in the Lab."

When the SOS Flashes

(Continued from page 1109)

January 7, 1904, establishing "CQD" as the official distress signal on and after February 1. 1904.

At the Radio Telegraphic Conference in Berlin, in 1906, the German government suggested "SOS" to replace "CQD." German ships had previously used a call "SOE" when they doring? when they desired to communicate with all other vessels within range. Since the letter "E" consists of only one dot it is easily susceptible to loss by interference; so the delegates suggested that "S" be used as the last letter. "CQD" was superseded in July, 1908, by "SOS," selected as the international distress call by the Radio Telegraphic Convention held at Berlin. (To be exact, this call differs from "SOS" by the fact that the groups of dots and dashes are not separated like separate letters. This gives it a striking and attention-compelling note.)

The acts of the convention were not ratified by all nations until about a year later, so "CQD" remained in force long enough to call rescue ships to the wreck of the Republic in 1909.

"SOS" came into prominence when the Titanic sank in the North Atlantic, April 14, 1912. As soon as the plight of the big ship was realized, Captain E. J. Smith ordered Operator Jack Philips to broadcast the distress call. Immediately the aerial of the sinking vessel radiated "Come at once! We've struck a berg! It's a CQD, OM!" (The "OM" is the radio sign meaning "Old Man," which adds a friendly personal touch to the dots and dashes.)

Then Junior Operator Harold Bride suggested, "Send 'SOS.' It's a new signal and it may be your last chance to send it." So Philips flashed "CQD" and then "SOS." "CQD, 'SOS' from MGY. We have struck

iceberg. Sinking fast. Come to our assistance. Position Lat. 41.45 N., Long. 50.14 W. MGY." (MGY was the radio call of the Titanic.)

Philips went down with the ship, but Bride was among those rescued by the Carpathia. That tragic scene enacted in midccean proved without a doubt the true value of "SOS," the call that still vibrates the ether as a signal for help and silence.

And so loud speakers become quiet when it sounds, as if to pay tribute to those who have "gone down to the sea in ships."

How Powerful a Tube Does Your Set Need?

(Continued from page 1137)

point is reached where, on loud signals, scrious distortion occurs, owing to the fact that tubes of this type have a comparatively high amplification factor, so that signals of even moderate intensity drive the grid positive. This overloading, in the case of the 201A type, occurs long before the volume has reached a point commensurate with the requirements of the listener, and before sufficient current is flowing in the plate circuit to reproduce accurately the bass notes. In a broadcast station, for example, only signals of little more than telephone intensity are expected from tubes of the 201A type; whereas, in the set of the average radio enthusiast, they are expected to furnish unlimited volume.

When Radio Turns Street Lamplighter

(Continued from page 1120)

months. The receiving circuit is extremely simple and requires no tuning or adjustment. In other words, it is an automatic receiver and the DX fan would scoff at the service of such an outfit, operating at only one frequency or wavelength-40 kilocycles or 7,500 meters-which is outside the broadcast band.

This marks the first commercial application of radio as street lamplighter, but a somewhat similar radio service is operating in Washington, D. C., where the electricpower distributing company has installed two small broadcast stations and equipped its repair trucks with radio receivers, for the purpose of maintaining communication between headquarters and the repair forces afield. These, and developments of a like vein, suggest the daily unfoldings of radio in strange fields and likewise explain the rush by various industries for government licenses to use short waves.

> NE STORIES IN OUR APRIL ISSUE:

The Story of the Days to Come, by II. G. Wells. We are always interested when we read a story of the far future, and of the wonders that might be in store for our descendants. But when such a story is written by Wells, it be-comes all the more realistic and the more absorbing.

The Miracle of the Lily, by Clare Winger Harris. Insects are and were man's greatest enemy. What if they should gain ascendancy over human beings ence more? The author, who was the third prize winner of our \$500,00 contest, weaves a fascinating story around this idea.

The Return of the Martians, by Cecil B. White. Being an astronomer, our author is well informed on the subject and in this sequel to "The Retreat of Mars," he gives us a most unusual, as well as powerfully written, story, which is not too technical.

Baron Münchhausen's Scientific Adven-tures, by Hugo Gernsback. Our resourceful Baron, in his quest for further first-hand information about the universe, lands on Mars.

The Ancient Horror, by Ilal Grant, Pre-historic mansters are no novelty in litera-ture, but here is one so totally different you will not be at all sure that it is not entirely truth.

And Others.



Brings in Far Away Stations Loud and Clear Regardless of Static Conditions

static conditions share everywhere are replacing their troublesome and static gathering up-in-the-air aerials with the marveious new GROUND ANTENNA-Aero-Liminator. Radio engineers and hundreds of users testify that Aero-Liminator sets better long dis-tance reception, almost unbelievable freedom from outside noises, far greater selectivity and marvel-ously true, clear sweet tone quality. John E. Christenson, Radio Engineer, Chicago, writes: I have tested and thorougily approve the Aero-Liminator. I find it increases selectivity and volume without distortion, practically elimin-ates static, gives good clear tones, both on local and distant stations. I would recommend the use of the Aero-Liminator to every radio owner to get the best reception from his set."

FREE TRIAL

Make this thrilling test at our risk!

Install an Acr-O-Liminator (Ground Antenna). Leave your old overhead aerial up. Try out on a night when static is bad. If you do not get a wonderful improvement in freedom from static, greater selectivity and clear sweet tone without interfering noises, if you can't get good recepiton on stations tha' are drowned out by static on your old aerial, you need not pay us a red cent for this test. Send coupon at once for scientifie explana-tion of Aer-O-Liminator (Ground Antenna) proof of performance and our conclusive iron-bound guarantee and remarkable Free Trial Offer-Mail Coupon TODAY!





Daval an

Endorsed by Foremost Engineers and Dealers

CURTANMFG.CO.

Please send me at once complete description of Acr-O-Liminator, with details of guarantee, celentific Proof, and FREE TRIAL OFFER. Name	CURTAN N 154 E. Erie Chicago, III	St., Dept	827-E.		
duress ity	Please send Aer-O-Liming Scientific Prod	I me at one tor, with of, and FR	ce completa details EE TRIAI	description of guarant OFFER.	of tee,
ity	ddress	· · · · · · · · · · · · · · · · · · ·	••••••	• • • • • • • • • • • •	• •
	ate.		· · · · · · · · · · · ·	**********	



Amicurs Hanvibook by the most eminent RADIO EXPERIMENT

Radio Fans! get together

with



Amateurs' Handibook and get the big things done!

HERE is a brand-new edition of the selected articles that have appeared in Radio News, Radio's Greatest Magazine.

These are the big things-the high lights in Radio achievement!

Plenty of the latest circuits, with diagrams, construction details, and all necessary data for the set builder.

All the latest—most far advanced methods known to the Radio World amplification, shielding, parts—everything!

This is the greatest Radio Handibook ever published. Size 9 x 12 inches—116 pages—fully illustrated—elaborate circuit diagrams—everything convenient for the fan.



How to Pick An Audio Amplifier

(Continued from page 1142)

circuit shown in Fig. 3 illustrates the way in which it is accomplished.

USE OF AN AUTOFORMER

Fig. 3 shows one stage of an impedancecapacity-coupled amplifier in which an *autoformer* is used in place of the usual audio choke coil in the plate circuit. The autoformer is identical with the usual audio choke coil, except that it is wound with more turns of wire and a separate tap has been provided for connection to the plate of the tube. As the circuit is arranged, the entire winding of the autoformer is connected in the grid circuit of the tube; but only a part of the winding is in the plate circuit. This arrangement produces a voltage step-up in much the same way as does a transformer, the increase in voltage being



ll'hen autotransformers are used in place of impedance units in an impedance-capacitycoupled amplifier, the above circuit arrangement is employed.

determined by the ratio of the number of turns in the entire winding to the number of turns in the plate section of the winding. In a circuit of this type the amplification per stage is often as high as one and one half times the amplification factor of the tube.

TRANSFORMER COUPLING

Fig. 4 presents the schematic wiring diagram of a standard two-stage transformercoupled, audio-frequency amplifier. This is probably the most popular type of audio amplifier in use today, and the reasons for its popularity are not difficult to understand. It provides a very simple method for securing maximum amplification from a given number of stages. It is more foolproof than either of the other two systems described, and provides ample volume with two tubes. However, it will introduce distortion if equipment of the highest quality is not selected.

From the wiring diagram it may be seen that the tubes of the amplifier are inductively coupled together by means of a transformer, the primary of which is connected in the plate circuit of one stage and the secondary in the grid circuit of the following one. In the drawing T1 and T2 are the two interstage coupling transformers; and T3 is a 1:1-radio output transformer which prevents the plate current of the last tube from passing through the windings of the loud speaker.

It is not within the scope of this article to discuss the problems of transformer design, but it may be said that the quality of reproduction obtained from a transformer-coupled audio-frequency amplifier is largely dependent upon the electrical characteristics of the audio transformers which are used. Of course, the selection of the proper tubes and the use of the correct grid and plate voltages is just as important in this amplifier as in any other amplifying apparatus, but it is equally necessary to have correctly-designed transformers.

PROPER TURN RATIOS

In the transformer-coupled amplifier the amplification per stage is equal to the amplification constant of the tube multiplied by the ratio between the turns of the secondary and those of the primary windings of the transformer. Thus, if a 201A tube is used in the first stage and the coupling transformer has a turn radio of 3:1, the amplification of the stage will be equal to 3 multiplied by 8 or 24.

Several years ago, when the public learned the fact stated above, it gained the impression that, in order to increase the volume of a set, it would be only necessary to employ a transformer with a higher turn ratio; and the poor results which were obtained with high-ratio transformers were largely responsible for the "black eye" which transformer-coupled amplifiers received at the time resistance-capacity coupled amplifiers were first introduced to the radio setbuilding fraternity.

It has already been explained that transformer design is too large a subject to cover in this article; but it must be pointed out that the turn ratio of a transformer does not determine its quality. The fact is that, the higher the turn ratio of a transformer, the more difficult it is to build a unit which will give good reproduction. Usually it will be found that transformers with a high turn ratio have insufficient turns on the primary winding and have a large capacity effect between the primary and secondary windings, with the result that the instrument gives very poor efficiency on both the high and the low tones and in the middle range the amplification is full of resonance peaks which distort the music. Voice and nusic from such an instrument is often distorted to a point where it bears but slight resemblance to the original.

On the other hand, the reader should not gain the opinion that all low-ratio transformers give good quality, for such is not the case. There are many good transform-ers of the low-ratio type, and there are many which do not give ideal reproduction. For an example, we will say that one manufacturer makes two different types of 3:1 ratio transformers. Both transformers are the same size, shape and approximate weight; but one delivers only average quality and sells for about \$3, while the other delivers practically perfect quality and sells for \$10. In the case of these two transformers the color of the case is the only way in which they may be distinguished by external examination; so it may be seen that the person who desires best results must buy quality equipment and cannot judge the efficiency of a transformer himself.

It must also be explained that the range of frequencies over which uniform amplification is obtained in a transformer-coupled amplifier is never as great as in a resistancecapacity-coupled-amplifier. However, this is not always an undesirable characteristic. A modern broadcast station transmits frequencies only within the band of 30 to 5,000 cycles; and there is no reason why the audio amplifier of a radio receiver should reproduce over a wider band. In fact, when an amplifier reproduces sounds having a frequency of 8,000 cycles, many circuit noises and hissing sounds are amplified; and these cause interference with the music. Therefore, if a transformer which amplifies efficiently over the range mentioned is selected, it is possible to have reproduction which closely approaches the original.

Home Radio Photography

(Continued from page 1103)

would be of benefit to people who live in places where newspapers arrive too late in the day to inform them of the current programs.

At the present stage of affairs, radio experimenters cannot hope to build photoradio receiving apparatus of the kind described in this article. The Moore neon lamp, which is the heart of the equipment and which is absolutely necessary for its successful operation, is not available at all; and, according to such high officials of the Radio Corporation of America as David Sarnoff and Dr. Alfred N. Goldsmith, it will not be available for private use for several years. Besides, special mechanical, optical and photographic apparatus, such as only a very fully-equipped physics laboratory would possess, is essential for the construction of the picture receiver.

RADIO NEWS, therefore, requests its read-ers not to write in for further details of the system described in this article. No constructional information of any kind can be obtained from the designers of the apparatus, and even if it were available, it would be of little practical value. When television and radio photography develop out of the laboratory and single-demonstration stage, and when regular experimental transmissions are inaugurated, then RADIO News will supply its readers with practical data which will enable them to construct working machines. Until such a time, the editors will discourage the publication of half-baked information dealing with socalled television and photo-radio equipment which never existed outside of the designer's imagination, and the materials for which can be procured only by someone possessing a skeleton key to the General Electric laboratories.

A VOLUME CONTROL

Loud speakers, gramophones and dogs are forbidden in some West Surrey flats. We understand, however, that the tenants are allowed to play eards, on the condition that the game is whist .-- London "Humorist."

MODERN MOTHER GOOSE RED RIDING Hoop: "What big cars you have, grandmother!"

GRANDMOTHER: "All the better to listenin with, my dear."-Popular Wireless, London.



ACME PARVOLT Condensers 101 many years and never had have one break down."

S.W. Cikeda

Showing the well-known L. C. 28 wired for A. C. power supply. Only the finest parts are specified in this high class set, including PARVOLT By-Pass Condensers. ACME PARVOLT Filter Condensers are also recommended for use in the power end.

OU hether You Buy or Build

a Power Supply Unit for Your Radio PLAY SAFE WITH PARVOLTS!

WHEN you buy an electrified radio or power supply unit for your receiver, look for ACME PARVOLT Condensers; they are your guide to quality They cost the in all other parts. manufacturer a trifle more, but they are both his and your guarantee against costly condenser break-down.

Should you build your own power supply, be sure to use ACME PARVOLT Condensers and be safeguarded against

the possibility of break down. Remember that poor filter condensers causeduntoldthousands of dollars worth of loss in the past year or two, for blown out condensers mean blown tubes, burned out transformers and frequently the ruination of speaker units.

Just as PARVOLT By-Pass Condensers have been used for years in high-grade receivers, so PARVOLT Filter are



ACME PARVOLT FILTER CONDENSERS In all required mfd. capacities for 200, 400, 600, 800, 1000, and 1500 Volt D C requirements. Supplied singly or in com-plete wired blacks for the important power supply units.

ACME PARVOLT BV-PASS CONDENSERS Supplied in all required mfd. capacities and for all standard working voltages.

Condensers rapidly replacing ordinary condensers in electrified radio. These condensers are wound with the very finest insulating papers, combined with highest grade foils. Every detail produced in one of America's most modern plants and under the supervision of experts in condenser design and manufacture.

Uniformity of capacity and uniformity of sizes are two big features. Accuracy of all ratings, based upon the R.M.A. standards, is another guarantee of uninterrupted service. Play safe with PARVOLTS!

Made by THE ACME WIRE COMPANY, New Haven, Conn., manufacturers of magnet and enameled wire, varnished insulations, coil windings, insulated tub_ ing and radio cables.



Enameled copper twire in both stranded and solid types. Also Acme Lead-ins. Battery Cables, Indoor and Loop Aerial Wire.

For all types of radio wiring. High insulation value; non-inflammable, 10 colors.

A superior cambric tubing for all practical radio and other electrical requirements. Supplied in 10 colors.





Matched in a few minutes An amazing value that can't be beat! Lat-stremely selective, marrelous sensitive. There stages of radio frequency, detector, and two stages of low ratio audio frequency. An amazing value that can't be beat! Lat-tremely selective, marrelous sensitive. An amazing value that can't be beat! Lat-tremely selective, marrelous sensitive. An amazing value that can't be beat! Lat-tremely to the the sense of the sense of the sense and two stages of low ratio audio frequency. An amazing value that the sense of the sense and two stages of low ratio audio frequency. An amazing value sense of the sense of the sense and realistic reception guaranteed. Beautiful black front panel (7 in, x 18 in.); ornamental design, de-front panel (7 in, x 18 in.); ornamental design, de-trea and kilocycle markings in sold. Metal banel and here and kilocycle markings in sold. Metal banel and sub-name! (7 in, x 18 in.); ornamental design, de-trea the sense of the sets. Owners and colored batters of but included. Simply connect a few wires. No special banel (7 in the set sure is a dandy." B. J. (1) The sense to wire this set with the instructions we fur-set in short order. Getting stations all orer the coun-tre. Plenty of volume. The set sure is a dandy." B. J. (1) The sense to wire this set with the instructions we fur-sist. Just connect a few minutes by anyone. No ratio knowledge needed. Make money wiring these sets in your spare time and scilling them to rour friends.

SEND NO MONEY Just write your name and address on a post card and ask us to send you this great outfit with six tubes. We ship right nuax. Upon arrival pay only 516.95. Plus a small delivery charge, (Foreign countries send \$19.50 with order. We pay shipping charge, 1549 S.Wells St., Chicago Radio Equipment Co., Dep. 12-D 549 S.Wells St., Chicago

Changes Your Set Into a Short-Wave Receiver

Sent postpaid anywhere in U. S. upon receipt of 515.00 M. O., or C. O. D. plus postage, upon receipt of 51.00 to guarantee carrying charges. charges. When ordering state kind of set so that detailed di-rections for use may be given if necessary. Also state type of tubes, such as UX199, UV199, WD11, or 201A.

The SUBMARINER

Regardless of the kind of set you have, this device will permit you to listen to short-wave stations between 26 and 68 meters. Operates with sets such as T. R. Neutrodyne, Super-Herero-dyne, regenerative sets, and many other types. No additional tubes or batteries required. No short types, No additional tubes or batteries required. No short the wring of the set. A short aerial and ground is connected to the "Sub-mariuer" and a cable and plug attaches it to be set. Requires less than a minute to attach or detach. Operates as a wave changer with Super-Hererodynes, and as a detector unit with others.

SHORT-WAVE RECEPTION

Is practical because they penetrate better, and there is less static. There are several powerful stations using the wave band covered by the "Submariner" for broadcasting programs. You may also learn code by listening to amateurs from all parts of the world. You will have a bighly efficient short-wave receiver when the "Submariner" is attached to your set. Nothing else like it on the market. Take a trip in the low waves on board the "Submariner."

ORDER TODAY We guarantee to refund if the "Submariner" fails to operate

J-M-P MANUFACTURING CO. Dept. 120 Milwaukee. Wis.



The Old Dray Mare

(Continued from page 1111)

the rush act. They tries to pocket her, but don't succeed; again I wins, this time \$250. Little Joe is very happy.

I don't even see The Master all morning, though I mingles with the gang at the fair exhibits, and eats hot dogs until I'm barking.

At noon it starts to cloud up, and for about half an hour it rains. Not hard, but enough to muddy things up considerable. I tries to locate Jerry, but he's disappeared.

The rain stops before race time, and the sun comes out, but the track's slow, and I ain't got any dope on how Fuse Plug acts in mud. Finally, I decides to slip my morning's winnings on the mare, and take a chance, although she's the favorite and the best I can get is even money. I'm figuring strong on the external impulse.

There's only seven in this race, and none of them seems to be a mudhen. They starts, with Fuse Plug bringing up the tail end, no better nor any worse. They're slowed, but as a whole; up and around the bend they splashes, the marc trailing, until they comes abreast of the lab truck.

Then the nag gives the expected lungeand how! Fuse Plug takes half a dozen frantic leaps, forges to the front, her mouth frothing. Twenty feet from the tape, four lengths ahead of the rest, Fuse Plug stops, flops, and slops-in requiem, so to speak.

The grandstand rises on masse as the field thunders past, but Fuse Plug has been blown out.

They carts her remains to the stables, but before they can do anything The Master exhibits his detective badge-he's an employee, and valued, of a well-known international agency-and makes for the corpse. The owner and trainers make futile efforts to hold him back, but with the aid of the local sheriff he gets there.

Quickly he removes the saddle and examines it.

"As I thought!" he exclaims, triumphant. We're shown two small copper contacts, about three inches apart, on that portion of the saddle that is directly over the horse's backbone,

There's a noise in the crowd, and a big, portly guy breaks through. He eyes us sternly. "What's this?" he demands.

Jerry shows his badge. "I have been endeavoring to ascertain the secret of this horse's former spurts of speed," he ex-plains. "I have found out."

He shows the fat man-who happens to be the mayor-the saddle. The official grunts. "Battery, ch?"

The Master shakes his head. "To the contrary, no. Strange as it may seem, Fuse Plug was controlled by radio!"

This statement gets a stir outa the crowd, but nobody gives him the bird. The mayor squints at Jerry, and spits out a wad of tobacco.

"Radio?" he queries. "Whadda ya mean, radio?"

"Just that," replics 'The Master. He rips open the saddle, displaying a network of fine insulated wire, the two ends of which terminate each at one of the copper contacts.

"This," explains Jerry-and, give him

credit, he holds his audience-"is a secondary coil, part of an alternating-current inductance. It is half of an ingeniouslycontrived step-up transformer.

"Shortly after the first race, when I had by test established the method that was being employed, I searched the old stable across from the turn. Concealed therein, and plugged into the lighting circuit, I discovered the primary that actuates the secondary here in the saddle. There was other apparatus deftly connected with it, in such a manner and so wired that when the current was on, and the horse passed the barn, she received directly through her spine a very strong shock-I have not yet determined the exact potential. But it was sufficient to spur the mare on and, as the pressure lessened with distance, common sense nmst have kept Fuse Plug running until the distance eliminated the induction.

There's a round of applause, but the mayor's still there with a question.

"You said radio," he reminds.

Jerry smiles faintly. "Indeed I did. You see, when I first heard of Fuse Plug I surmised to an extent the method that was being used. On her first race Tuesday I verified my hunch. This morning, before the first race, I discovered the apparatus in the barn. I didn't have time to open a box that contained some part of the device, because I had to get back to my truck to get set for the first race.

"I saw nobody enter the barn, and all entrances were visible from where I was parked; when the primary functioned, and with no one to operate it, I was puzzled, but only for a moment.

"Immediately after the first race this morning I returned to the barn. No one was there. But this time I took apart the box that I previously had not had time to look into. This box contained a radio receiver, tuned to one wavelength, and operating the main switch to the primary!

"The actual control was indeed remote. It took me an hour to find the wavelength the receiver was set for; I returned to my truck, arranged my own receiver as near likewise as possible, set up a loop for direction-finding, and waited.

"On the last race I had but a few seconds to tune and get my directions in, and it had to be done against the interference of the operating primary. But I located the transmitting station—in the Belvedere Hotel across the street!"

No sooner said than a deputy comes up with a small, scraggly guy handcuffed and surly. It develops, after questioning, that he is the genius behind the fracas.

Until then it hasn't dawned on me that I've lost all that I made. I turns to The Master, forgetting our agreement.

"Say, Jerry, how come the nag passed out?"

There's others that want to know, too. The Master smiles, and then gazes sadly at the remains of the horse. Jerry loves animals.

"In planning their radio control, the conspirators were very clever in making plans for their personal safety," he states. "But for their personal safety," he states. evidently they thought their scheme so sccure from detection that they didn't even

Radio News for April, 1928

bother to visit the barn to look at the apparatus before each race."

"Didn't dare," mutters the radio operator. "Looked suspicious."

The Master nods. "As I surmised. But the rain leaked in on the wiring, and caused a 'short' when the switch was thrown in. Since water increases the natural conductivity of earth, and the ground at that end of the track was almost a small pond, poor Fuse Plug got it coming and going. It was a bit too much for her old carcass. She tried to get away from it by crossing the tape, as experience had taught her she could. But this time the mare couldn't quite make it."

The mayor shakes hands, and asks us to stay for the big dance in the evening, but The Master hates being stared at, so we breezes back to Long Island, me minus my long green.

"Why didn't you tip me off?" I demands.

"After all your good advice on the subject, I never thought you'd bet on a horse," declares Jerry. "How much did you lose?"

I grunts. "Oh, I'm even—just lost what I made. But like a fool I got generous last night and promised Doris a new set of furniture for the parlor."

"What kind does she want?" asks Jerry, "Mohair?"

"No," I growls, "horschair !" (Copyright, 1928, by Robert Francis Smith)

The Radio School Teacher Is Here

(Continued from page 1117)

the expression of all school activities. These attitudes were reflected in the conduct of the children on the way home from school, in their homes and in their communities. Dana S. Merriman, musical director of WT1C, and other members of the station staff are enthusiastic over the success of the course.

Anyone who followed a group of pupils from their school to a home, where they were invited to listen to the radio music lesson, would have noticed that the well-bred ones showed their good nanners and that the underprivileged quickly initiated them. They all removed their rubbers outside the door. The boys courteously waited for the girls to enter first. Each thanked the hostess for her hospitality as they left.

CONNECTICUT SHARES HER BLESSINGS

Other states benefit from Connecticut's radio course. The commissioners of education in Massachusetts, New Hampshire and Vermont appointed music supervisors to act with the advisory committee appointed by the Connectient commissioner; schools in Maine received the lessons also. Private and parochial schools and many homes heard and appreciated them.

Radio undoubtedly will play a larger part in our schools in the future. A large number of schools have heard President Coolidge's addresses, by means of radio veceivers loaned for the occasion. One state school official is using radio as a means of "visiting" his schools; he can reach more than a hundred at a time. The broadcasting companies are ready to cooperate with the schools, especially because the schools can be reached in the morning and carly





CITY......STATE....

afternoon when the air is uncrowded and many stations lack an audience.

IF YOU WERE IN SCHOOL TODAY

Think back to your own school days. Education has progressed, but still it fails unless it can secure attention and excite interest. There are 5,000,000 within our borders who seem to be in the same fix as the Florida cracker, who said that there was only one thing that stood in the way of his getting an education. That was "them durned ABC's—there was so many of 'em he couldn't learn 'em."

The burden of education rests ultimately on a teacher with a roomful of restless, squirming boys and girls. They have to be coaxed or forced through text books from which the breath of life has been crushed by excessive condensation. The out-of-doors is calling.

A vaudeville artist has to entertain his audience for about twelve minutes, and he faces a new audience every time he does his act. Λ school teacher—and many are very young and inexperienced—must interest her group five or six hours a day, five days a week, forty weeks a year, and there must be no deviation from the straight and narrow path that men higher up have laid out for her.

Whether you were a teacher or a pupil, would you welcome a lesson by radio, with nusic?

Would you like to hear Coolidge, McAdoo, Al. Smith, Will Rogers, Byrd, Anundsen, Lindbergh? Would you?

The State of Connecticut has shown us what to do about radio education.

A Nation-Wide Experiment in Radio Music for Schools

O NE of the most ambitious experiments with radio as an adjunct to its regular teaching facilities was made by the New York public school system on February 10 last when Walter Damrosch led the New York Symphony Orchestra in a concert for school children. The program, lasting one hour, was radiated over a network of twenty-three stations, including WJZ, and heard throughout the entire Eastern half of the United States.

Mr. Damrosch's audience numbered at least 500,000 pupils in the seventh and cighth grades. New York City alone was represented by 110 schools, whose combined audiences totaled more than 100,000. Telegranus reporting reception of the concert were received from as far West as Fairbury, Neb.

A message from the Listeners League in Des Moines, Iowa, said: "All the city schools listened to your program. Children and teachers are enthusiastic."

This telegram was typical of scores of others that flooded in from the West, South and East and from the New England States. In Worcester, Mass., the pupils of several schools which were not equipped with receiving sets marched in a body to the City Hall, where the program was reproduced for their benefit. From Council Bluffs, Iowa, four separate messages from the pupils of different schools requested Mr. Damrosch to continue the programs in the future.

PLANS FOR NEXT SEASON

Immediately after the concert Mr. Damrosch expressed himself as pleased with the response which was pouring in by messenger, telegram and telephone. He spoke optimistically of his plans for the coming year.

"My plan for next Fall, if consummated," he said, "is to conduct twelve concerts for grammar school children, to be offered during school hours and to be broadcast as widely throughout the country as possible at that time. I hope we shall be able to go as far West as the Rocky Mountains perhaps even to the Coast.

"Over a like period I hope to conduct twelve concerts for students of high school and college age. The idea is not to present music in these programs which will differ widely from that which was just broadcast for the children, but to make explanations more suited to listeners of more matured minds. The lecture concerts will be accompanied by sets of questions and answers in order that instructors may, if they choose, give examinations on the course.

"I should like to bring out most clearly that what I plan is not designed to supplant whatever musical training may already be in the course of instruction but rather to supplement the teachers' work. It is 'the little red school house' in the rural districts that interests me most of all, for these are districts where good music by a great orchestra is so seldom heard."

SPECIAL INSTALLATIONS

Many cities throughout the country installed radio apparatus in the schools especially for this event. Among these were Des Moines and Davenport, Iowa; Nashville, Tenn.; Baltimore, Md.; Worcester, Fitchburg and eighteen other cities ar towns in Massachusetts. Other telegrams reporting enthusiastic reception of the concert came from Georgia, where radio has been used in the city schools of Atlanta for more than two years.

The enthusiasm outside of New York, however, was no greater than that displayed in the 110 schools of that city which heard the concert. George II. Gartlan, director of music for the board of education, said:

"The children who heard the concert were delighted, and we are already making plans for the broadcast next Friday. There is no question of its educational value. We are recommending to the board of estimate that all new school buildings be equipped with radio. Equipping the old schools with adequate receiving sets is a matter that will require some time because of the great expense.

⁴From time to time I have suggested to local neighborhood organizations, chambers of commerce and other civic organizations that it might be advisable for them to interest themselves in the movement to equip schools in their districts with first-class receiving sets. Up to the present time these appeals have met with but little response. The enthusiasm with which the children received today's program should do much to stimulate interest among these hodies." (Continued from page 1123)

The units operating the loud speaker are of the electro-dynamic type and of a new construction. In its present form the loud speaker uses a huge horn, as may be seen in the accompanying illustration. The moving diaphragm or armature of the receiver is not made of magnetic material, but consists of a sheet of very light aluminum alloy, about two thousandths of an inch thick and so constructed that it moves back and forth, somewhat as a piston. Attached to the diaphragm is a small coil of strip aluminum wound edgewise and insulated with varnish. This coil lies in the field produced by a very powerful electromagnet. (See Fig. 1 for the disposition of the various parts.)

During the operation of the speaker the voice current passes through the small aluminum coil, eausing the diaphragm to vibrate to and fro. Because of the phingerlike motion of the diaphragm and the special shaping of the air chamber between the diaphragm and the mouth of the horn, the resulting efficiency is many times greater than that obtained in other types of loud speakers. The large load-earrying capacity of the speaker arises from the fact that the aluminum coil lies very close to the heavy iron pole-pieces of the electromagnet.

This loud speaker is designed expressly for public-address systems and for the reproduction of speech and music in connection with "talking moving pictures." Τf is interesting also because its reproducing qualities are as fine as its capacity is enormous. It reproduces frequencies from 60 to 6000 cycles without distortion, and reproduces down to 40 cycles and up to 8000 eveles with distortion so slight that it is almost impossible to detect it.

A LESSON IN QUALITY

During the recent exhibition the musical qualities of the speaker were displayed by using it to reproduce the pure notes of an electrical oscillator, the frequency of which was varied from the lowest to the highest pitches. The importance of using such a reproducing device for obtaining good musical quality was demonstrated by cutting out from musical selections certain frequencies by means of electric filters. With these filters any frequency or band of frequencies can be taken from the music or voice. For example, in the case of voice reproduction, it is possible to take out all the sibilant ("s") sounds or, in musical selections, to climinate either all the high or all the low notes, etc. This is a striking object lessor. in the nature of "quality,"

An interesting side-light on the demonstration was obtained when an engineer in New Jersey spoke into a telephone connected directly with the laboratory on the other side of the river. This phone was connected to the input of the giant speaker and the engincer across the river heard the Gargantuan echo of his own voice, five or six seconds after he had pronounced the words. It took this length of time for the sound waves to travel back from New York to the New Jersey shore from the mouth of the horn, though the electrical reproduction had been practically instantaneous.



PRODUCTS

ON SALE EVERYWHERE

SCHOOL OF ENGINEERING RN328 M. Waukee, W's.



The Radio Beginner

(Continued from page 1125)

of voltage between the filament and grid which may be compared to placing a charge on the grid.

As explained before, the plate current is continually changing in accordance with whatever variations are present in the original signal from the broadcast station; and, therefore, these electrical variations are transformed into *sound variations* which may be heard in the telephones, and reproduce the sounds originally converted into electrical variations by the "microphone" in the broadcast studio. A vacuum tube used in this manner is called a "detector."

No matter how rapid are the fluctuations that are impressed on the grid, the plate current faithfully follows these. Even such extremely rapid variations as "radio fre-quencies," thousands of times more rapid than the musical or speech ("audio") frequencies, may be successfully amplified also. For further amplification, it would be necessary only to connect the grid and filament of another tube in the position occupied by the head telephones in the case described in the previous paragraph, and the incoming audio-frequency pulsations could be still further amplified by the second tube. There is no limit to the amplification that can be obtained, but various "extraneous" or outside noises are also amplified; so that enormous amplification may give too much importance to useless noises.

VARIOUS USES

Although the action of all common radio tubes is the same in principle, there are other factors which determine which *type* of tube should be used for a given purpose. Certain features of construction or the spacing of elements may adapt a tube to some particular use. Different materials and designs in filament wires may be used; so that different tubes require different battery voltages to operate them. Certain filaments require more current than others for proper heating and "evaporation;" some tubes successfully operate from alternating current merely "stepped down" from the house-lighting circuits, while others require batteries or power units which contain rectifiers.

For detection, a small quantity of certain gases, introduced into the glass bulb, often gives a tube greater sensitivity to small grid charges, "weaker signals." A tube to handle large amounts of power, and such are necessary for good lond-speaker operation, must be of special construction so that the plate voltages necessary and the power handled will not overload the tube; overloading may give rise to tube failures, or distortion in the speech or music.

One of the governing factors in the use of a tube as a radio-frequency amplifier is the *capacity* between the elements of the tube. A special construction may, therefore, give better results for such purposes. It is evident, therefore, that the design of a tube is greatly influenced by the use which is to be made of it; it may justly be said that there is a particular tube for each and every use in a radio receiver if best results are to be obtained.

CARE OF TUBES

The filament of a tube is designed to give best results at a definite voltage or current, and at this value, a certain length of life for the filament is obtained. If the tube is operated at a filament voltage higher than the rated value, the electron evaporation is greatly increased, with little useful gain; but the life of the filament is very greatly reduced. Some filaments do not actually burn out when the voltages are exceeded, but they become "deactivated;" that is, the useful material has disappeared from the surface of the filament. This may often be restored by turning on the tube with somewhat above normal voltages on the filament, and with the plate ("B")battery temporarily disconnected; but prevention is much easier than a cure.

The new "screen-grid" tube makes use of



This type of circuit drawing explains more clearly the meaning of the different parts diagramed in Fig. 4, the connections being exactly the same.

Radio News for April, 1928

a second grid, which surrounds the plate completely, and shields the first or controlgrid from the plate. It thus makes negli-gible the "capacitive" effect between grid and plate, which causes complications in the use of ordinary tubes for radio-frequency amplification. The screen-grid tube, when used as a radio-frequency aniplifier, has this second grid connected to a source of positive voltage, about onethird as high as that applied to the plate. The capacitive effect within the tube is thus reduced to a negligible amount. The action of this tube is otherwise the same as that of the ordinary tube, which has been deseribed. (The screen-grid has been explained in more detail, in the article in February RADIO NEWS, mentioned before.)

THE ACCESSORIES

The tube socket is designed so that the tube may be easily removed from it, in case replacement is necessary, and is equipped with convenient screws for attaching the "lead" wires from the external circuits to the socket; the *springs* of the sockets in turn complete the connection to the tube's *prongs*, which lead by wires inside the tube to its elements, respectively.

Two prongs in the ordinary tube connect to like ends of the filament, sometimes designated as "plus" and "minus" when in use, and one each to the grid and to the plate.

The most common type of socket is the "UX." It is often necessary to have a socket which is "spring-supported" or "cushioned;" so that ringing or "microphonic" noises from tubes are eliminated. Proper internal construction, resulting in greater rigidity of the tube's elements, has done much toward eliminating this effect.

All common types of tubes fit into the ordinary "UX" socket; but different tubes require different resistances in series with the filaments to reduce the voltage applied to the ends of the filament when using a given "A" voltage, such as that furnished by a storage battery. Resistors of various types are available for this purpose and may be changed about for the different tubes, by merely plugging units of the proper resistance value into the convenient holders.

POWER SUPPLIES

As explained before, the filament of a tube must be heated; this is done by passing through it a current of the proper value. Various means are used for furnishing such filament-heating currents; the storage battery has been widely used and the direct current thus furnished is usually very steady and noiseless. Tubes have







PRICE \$5.00 700 Pages

500 Illustrations

Contents of each chapter— I. Aircraft Types. II. Lighter-than - Air Craft. III. Early Airplane De-Bigns. General Design Considerations. IV. De-sign and Construction of Aerofoils. V. Arrange-of Airmiene Win-

Airplane Fuselage and Landing Gear Construction, VIII. Airplane Fuselage and Landing Gear Construction, VIII. Airplane Power Plant Types and Installation, VIII. Airplane Power Plant Types and Installation, Air-Cooled Engines. IX. Aviation Engine Design and Construction. Water-Cooled Engines. X, Avia-tion Engine Auxiliaries. XI. Aircraft Propeller Construction and Action. XII. Airplane Equilib-rium and Control Principles. XIII. Uncraft Propeller Construction Principles. XII. Uncraft Schull Maintenance of Airplanes and Engines. XV. De-tails of Modern Airships and Airplanes. XVI. Sea-planes, Flying Boats, Amphibians and Other Air-craft. XVIII. Some Aspects of Commercial Aviation, XIX. Standard Nomenlature for Aeronautics Report No. 240, Part I. This book is written in simple, understandable language

This book is written in simple, understandable language.

> AVIATION ENGINES

EXAMPLE This treatise, written by a recognized authority on all of the practical aspects of internal combustion engine construction, maintenance, and repair, fills the need us no other book does. The matter is logically arranged all descriptive mat-ter is simply expressed and copously liu strated, so that anyone can understand air-iane eneite operation and repair even if without pre-vious mechanical training. This work is invaluable for anyonc desiring to become anyotator or aviator mechan-icat. 274 PACES

274 PAGES



VIATION ENGINES AGÉ

A. B. C. OF AVIATION

PRICE \$1.25

This book describes the basic principles of aviation, tells how a balloon, or dirigible is made, and why it floats in the air. Describes how an airplane files. It shows in detail the different parts of an airplane, what they are, and what they do. Describes all types of air-planes and how they differ in construction, as well as de-tailing the advantages and disadvantages of different types of aircraft. It includes a complete dictionary of avia-tion terms and clear drawings of leading airplanes.

PRICE \$1.25

Remit by cash; stamps, check, or money order No C.O.D.'s

We Pay Postage On All Books

CONSRAD COMPANY, Inc. 230 FIFTH AVENUE NEW YORK

been developed which employ small dry batteries; and others which operate from the electric-light socket by means of a small transformer, which changes the available house-lighting voltage to a low value for this purpose. The tubes which operate from the light socket, in this manner are very convenient to use, and proper circuit design has practically eliminated the troublesome "hum" occasioned from the rapid changes in the direction ("cycles") of the alternating current.

A still higher voltage must be available to furnish the potentials necessary on the plates of the tubes; and this may be derived from "B" batteries, which are simply many small "cells" (usually giving 11/2 volts each) all connected in series and enclosed in a suitable container. A "B" socket-power unit consists simply of a transformer-andfilter arrangement which gives the proper direct voltages when merely plugged into the house supply. It is possible, therefore, to have a set which is entirely operated from the light socket. Such sets, although somewhat more expensive in first cost, are very convenient and economical in the long run; the only replacement needed on such sets is the tubes and these should last, with care, as long as electric-light bulbs, or considerably more than a year, under conditions of ordinary use.

(An elementary explanation of the more intricate action of a vacuum tube as a detector will be found in the "I Want to Know" department of this issue of RADIO News, on page 1151.)

Some Suggestions About Resistance Coupling

ITH the advent of better "highmu" tubes, reliable resistors and high-voltage socket-power operation, the resistance-coupled method of amplification once more comes into its own as a means of obtaining excellent tone quality together with ample volume.

In the first place, the all-important thing with resistance coupling is to employ highmu or high amplification tubes. Today, for this very purpose, several tubes are available, such as the 240 type, with a mu or "amplification constant" of 30 as compared with about 7 for the usual 201A type, and 20 for the high-mu tubes previously available. Therefore, the present high-mu tubes give a step-up effect 50 per cent. greater; which is essential in a system in which the amplification is solely a function of the tube, without the step-up transformer to help out, as in transformer-coupled amplification.

SELECTION OF RESISTORS

The second consideration is the use of proper resistors; not only in the matter of correct values, but particularly in assuring stability of operation. Resistance coupling is particularly susceptible to changes in resistance, which alter the results and sometimes introduce serious noises. For this reason it is desirable to employ heavy-duty resistors which are capable of providing accurate and lasting resistance values, even when handling considerable currents, without danger of resistance changes to cause noises.

The third consideration, and one of great importance, is to have available sufficient plate voltage. It is often overlooked that, in resistance coupling, the voltage impressed on the plate of the tube must pass through the plate-coupling resistor, the value of which is usually 100,000 ohms and over; in the case of the 30-mu tube, the platecoupling resistor is of 250,000 ohms. Obviously, to overcome this high resistance in the circuit and still have sufficient voltage to operate the tube efficiently, it is necessary to start out with high voltage (preferably 180 volts) on the plate-coupling resistor, or at the maximum-voltage tap of the usual radio power unit. If "B" batteries are employed, there should be four blocks, of 45 volts each and of the heavy-duty type, to provide the necessary current over a long period of service,

An excellent resistance-coupled amplifier, using present-day components, is shown in Fig. 1. It will be noted that, thanks to the 30-mu tubes now available, three stages of A.F. are no longer required, provided a high-mu detector is employed. Also, it will be noted that a speaker filter is employed (preferably in the form of a choke coil and series-condenser arrangement) to avoid introducing distortion and also to keep the direct-current component out of the loudspeaker. The speaker filter promotes the use of maximum voltage on the plate of the power tube, since the plate current does not have to flow through the high-resistance winding of the loud speaker, as it must when the latter is connected directly to the amplifier output.

RESISTANCE VALUES

The resistance values indicated in the figure do not run as high, in the case of the grid leaks, as those usually specified for the present high-mu tubes. While there is a slight loss in volume, which is certainly not noticeable, there is better assurance of a grid leakage ample to avoid any possibility of "blocking" or the piling up of successive signals.

The layout shown in Fig. 1, comprising a 30-mu tube for the dctector, a 30-mu tube for the first stage, and a 171 or 210-type of power tube for the second stage, will provide ample volume, with a tone quality noticeably better than the average transformer and at comparatively low cost.



A two-stage resistance-coupled amplifier, using "high-mu" tubes.

The use of a high-mu detector tube serves to obtain considerable amplification as well as signal rectification. A 3-megohm metalized resistor should be employed for the detector grid leak, in combination with a .00025-mf. grid condenser.

PUSH-PULL CIRCUIT

For those seeking enormous volume, together with a remarkable depth and detail of tone, resistance coupling presents many interesting possibilities in conjunction with present-day high-voltage, socket-power operation. In Fig. 2 we present an interesting development in the way of a powerful pushpull amplifier, with excellent tone quality in conjunction with a good speaker capable of handling the full volume. Indeed, this amplifier provides the volume of a small orchestra, with a realism that is quite startling, even to blasé radio enthusiasts. The cost of this amplifier is surprisingly low. With resistance coupling employed in this manner, we remove the possibility of overloaded tubes and therefore the last vestige of distortion in power amplification.



Complete details of a circuit applying the advantages of push-pull action to a resistancecoupled amplifier. The constants given may be modified by experiment.

The diagram is virtually self-explanatory. It is best to use 2½-watt power resistors for the 8,000-ohm units employed in coupling the output to the loud speaker, in order to handle the considerable current without material change of resistance value. Because of the power handled with this amplifier, none but reliable resistors can be employed.

POWER UNIT

It will be noted that the power must be supplied by a radio power unit capable of delivering 425 volts for the plate circuits and $7\frac{1}{2}$ volts A.C. for the filaments of the large tubes. One 216-B-type rectifier tube will be rather heavily taxed if made to supply two 210-type power tubes, and the plate voltage is apt to drop below the value necessary to operate these tubes at proper efficiency. A 281-type rectifier, substituted for the usual 216-B, will help out in this connection. However, for best results the radio power unit should have two 216-B or 281type rectifiers arranged for full-wave rectification, which will supply ample plate voltage and current for the operation of two 210-type power tubes.

If we change the "C" battery to 45 volts and the plate voltage to 200, with the output plate resistors 5,000 ohms each, good results will be obtained with two 171 tubes in place of the 210 tubes, for those who must operate on "B" batteries or on moderate voltage radio power units.

While the values given in these diagrams have been found highly satisfactory, there is considerable room for variation.

lucidentally, in Fig. 2 we have not indicated the filament-supply current, but it goes without saying that the first-stage tubes are of the 240 type, operating on 5 volts of battery current, while the two power tubes are operated on either $7\frac{1}{2}$ volts raw A.C. or battery, if of the 171 type.







Seattle and Australia Talk:

World's Radio Phone Record

Special to The New York Times.

SEATTLE, Wash., July 2 .- Ra-

dio telephone communication has

been established between Seattle

THE Type 440-A Transformer illustrated is designed for use on 105-125 V. (50-60 cycle) A. C., and is rated at 65 watts. The following voltages and currents are available:

2	Volts									•	•		10	Amperes
3.5	"												5	" "
5	66			•								2	.5	
7.5	4.6												2	66

Type 440-A Transformer Price—\$10.00

The use of this transformer, together with the new A. C. tubes, and a dependable plate supply unit such as the General Radio type 445 Plate Supply and Grid Bias Unit, makes the conversion of a batteryoperated receiver into one operated from the light socket very simple. If you do not care to undertake this change yourself, go to your community set builder. He is well qualified to serve you.

GENERAL RADIO CO.

30 STATE STREET





The distance, about 8,000 miles,

is the longest over which a two-

way conversation ever has been

conducted. It is all the more re-

markable because the power was

only 100 watts. Most broadcasters,

with ranges of a few hundred

miles, use from 1,000 to 5,000

watts. The wave length of both



Entire factory stock of Conner Convenient Cabinets now being closed out at



25% REDUCTION Prices NOW \$26.25 to \$74.75 hepbeap. Benaissance

Jacobean, Renaissance and Sheraton designs, done in beautifully highlighted walnut and mahogany. Fronts open down into convenient desks. Write today for illustrations.

A Conner Cabinet assembles every detail of your receiving set, batteries and accessories, in a scientifically convenient arrangement and encloses everything in an exceptionally beautiful piece of period furniture. You can secure one at this emergency bargain price if you act quickly. Write today for illustrations and details.

CONNER RADIO CABINET CO. New Albany, Indiana



Radio "Bugs"

WHAT is, probably, the best "bug" which the intrepid explorers of Radio Land have discovered for the edification of our readers is given below; and the sceptic who cares to trace the lines will find it a real circuit. The contributing entomologist,



Francis D. Johnston of Pittsburgh, chooses the somewhat intriguing title: "A Dry-Battery Manufacturer's Impression of a 'B' 'Eliminator.'"

"A Lightning Kick on the Grid-Iron" is the title selected by P. Beck of Herrick, Ill., for this scene of action. It seems to us,



however, that this terrific kick is being bestowed on the filament, which may not survive the indignity.

At the right is a grim hunter; we might have been at a loss to name him, but Jackson Edwards of Tucson, Ariz., supplies the data: "This is a Lou Pantenna, found only in the wilds of Laboratoria. His eyes can detect anything, and he is holding a Peridyne, a weapon against the tribe of Poo Receptionia."

Whether or not the political events of the year will confute the prophets, time alone



can tell. This sketch of "A Broad-Tuning Receiver," however, will appeal to Demicans

and Republocrats alike. It comes from the hasty, though oracular, state of Oklahoma. Audie Robertson of Alex, Okla., is the discoverer.



"The Younger Generation-Whereto on Roller Skates?"

Madison, Wis., is a co-educationally-collegiate city, and affords opportunity for the observance of coruscating youth at the most plastic period. We may suppose, therefore, that this couple have been drawn from life by James W. McGrath of that city.

The DX Hound is famous in radio lore, but his habits are distinctly nocturnal, so that he has hitherto escaped observation.



The animal, however, has been drawn during a brief moment of hesitation while stalking his prey. "A true specimen," comments Joseph W. Sine of Salt Lake City. "Observe the distance-getting nose, the crystalline ears and, last but not least, his *tales*, which pass all understanding."

Carl Sipe of Anderson, Ind., pictures a parade of the Thoriated Soldiers, which



hardly needs the brief explanation: "The Nine-in-Line." Long leads are evidently conspicuous by their absence.

A. J. Manson of Nelson, B. C., pictures a pair whom we took at first glimpse for The Heavenly Twins. The legend informs us



of their full names: "Clarifier and Eliminator get good reception."

Some of our bugs are far from home; this spirited scene. with Tilden on the left and Suzanne on the right, comes from A. Hacrtel of Offenbach, Germany. But while Herr



Haertel is fair DX, he is not to be compared with the two which close our symposium.

E. G. Castro of Manila (Philippine Islands), sends in "The Ham's Covered Wagon." Whether it is drawn by a broncho



or a carabao, we cannot say; but it is evidently on its westward way.

A companion piece shows the effect of progress. The radio automobile is the work of a fellow-Filipino, Enrique G. Hinlo of Manapla, Occ. Negro. Pending returns from



Kerguelen, Macquarie Island, and the South Shetlands, we award to these contributors the prizes for greatest distance covered by transmission.

Entomologists, for your labors in the cause of radio science, and on behalf of the radio public—your public—we thank you!

A FILAMENT ELIMINATOR

There was a young radio student Who was told to be careful, but wouldn't;

On "A+" he placed "B 90" in haste—

Then he tried to tune in, and he couldn't! -J. Hope.

> TUNING OUT His voice was full of static— "Oh, can't you learn to care?" Her answer was emphatic: Said she, "Get off the air!" —Dorothy Pownall.

RADIO TERM ILLUSTRATED



"A Control Switch."

Watch the Last Stage

LARGE percentage of the distortion, A in most radio receivers, is caused by overloading the tube in the last stage of audio amplification. When tubes of the 201A or 112 type are used, the only ways to reduce the distortion may be to substitute a larger tube or to decrease the volmne; but with tubes of the 171 and 210 types, the distortion can usually be remedied by correctly adjusting the grid-bias voltage ("C" battery) on the last stage. The instruction sheets, which are packed with the tube, give approximately values of gridbias voltage suitable for use with various plate potentials; but, in order to make sure that the tube is not being overloaded, it is necessary to connect a millianumeter in the plate circuit of the last tube.

If there is no appreciable movement of the needle of the milliammeter when loud signals are being received, the grid is correctly biased. On the other hand, when the needle of the meter oscillates as the intensity of the signal is increased, the tube is being overloaded and the bias must be increased or decreased, as the case may be. If it is impossible to prevent the needle from oscillating by any adjustment of the grid bias, this fact indicates that too much volume is being obtained from the amplifier.

The meter used for this purpose should have a range from 0 to 25 milliamperes, and the maximum fluctuation of the plate current should not be greater than 10% of the total current. In the case of the 171-type tube, the plate current should be 20 milliamperes with a plate potential of 180 volts, and the correct grid bias is approximately 40 volts. With the 210 tube, operating with a plate potential of 425 volts, the proper plate current is 18 milliamperes, and the grid-bias potential approximately 35 volts.

Use of Separate Amplifier

THERE is no unanswerable reason why the audio-frequency amplifier of a receiving installation should be built as part of the radio set; while, on the other hand, it is often more satisfactory to construct it as a separate unit. The practice of combining the audio amplifier with the "B" socket-power unit is now becoming very common, and has received the endorsement of a large number of radio engineers.

With the amplifier and "B" supply device in one unit, the installation is much more flexible; as it may be connected quickly and easily with any type of either radio set, phonograph pick-up unit, or microphone. In addition, this prevents the necessity of rebuilding the audio amplifier every time one builds a new set, and climinates the danger involved in having exposed high-tension wires between the "B"-supply unit and the power tube.

The reproduction obtained will be no less satisfactory when an external amplifier is used, provided one simple precaution is taken in the design of the receiver; *i.e.*, an R.F. choke coil and a by-pass condenser must be connected in the plate circuit of the detector tube. The by-pass condenser should have a capacity of approximately .001-mf. and be connected between the detector plate and the "A—" lead. The R.F. choke coil should be mounted near the detector tube and connected directly in series with the lead to the A.F. amplifier.



The

N

THE

How to Make

STROBODYN

RECEIVER

monten An R. F. Short-Wave Broadcast now/ Receiver

(Continued from page 1130)

operating on wavelengths between 10 and 550 meters. Six different types of coils and two coils of each type (12 coils in all) are needed to cover this wide band. However, all the coils are not required if the builder wishes to limit the wavelength range of the set to a narrower band. The waveband which each of the six coils covers approximately is as follows: coil No. 1, 10 to 25 meters; coil No. 2, 15 to 33.5 meters; coil No. 3, 31.5 to 68 meters; coil No. 4, 57 to 133 meters; coil No. 5, 125 to 250 meters and coil No. 6, 235 to 550 meters. If it is desired to increase the wavelength range of the set to 725 meters it is possible to do so by connecting a .0001-mf. mica fixed condenser in shunt with each of the tuning condensers (C1 and C2) when coil No. 6 is being used.

In constructing the coils the secondary windings must be spaced. The chart in the drawing gives the number of turns, the size of wire and the length of each secondary winding; and with this data the builder can determine the proper spacing between turns by experiment. The tickler and primary coils are wound with insulated wire and are not spaced. The primary coil consists of 10 turns of No. 24 S.S.C. wire wound on a form 21/2 inches in diameter. The tickler coils are merely glued inside the secondaries, or held in place with a few drops of sealing wax or paraffin from a candle.

The following is a complete list of the parts required for the construction of this short-wave receiving set:

LIST OF PARTS

L1, 1.2-Two sets of coils (see drawing for

details); C1, C2—Two S.L.F. variable condensers, .00014-mf.:

- C3-One S.L.F. variable condenser, .00025mf.;
- C4-One mica fixed condenser, .00025-mf.;
- T1-One A.F. transformer, 3:1 ratio;
- T2-One A.F. transformer, push-pull input
- type; T3-One A.F. choke coil, push-pull output
- type; R1-One grid leak, 5-megohm;

R2, R3, R4-Three filament-ballast units, 5volt, 1/4-amp. type;

R5-One filament-ballast unit, 5-volt, 1/2amp. type;

R6-One 500,000-ohm volume-control rheostat and filament switch;

RFC-One R.F. choke coil, 60-millihenry;

- PH-One oscillation control, variable resistor-condenser type;
- V1, V2, V3-Three vacuum tubes, 201Atype;

V4, V5-Two power tubes, 171A-type;

SW-One jack switch, D.P.D.T. type;

Three tuning dials, vernier type;

Five vacuum-tube sockets, UX-type;

- One panel, 7 x 24 x 3/16 inches;
- One sub-panel, 7 x 23 x 3/16 inches;

Three brackets, 3 inches high;

Twelve binding posts;

Two coil mountings (see drawing for details).

FREE BLUEPRINTS

A set of full-size blueprints, covering all the constructional details of the flexible short-wave receiver described in the foregoing article, may be obtained free of charge at the office of RADIO NEWS, 230 Fifth Avenue, New York City. Readers desiring to have these prints delivered by mail should send ten cents in stamps or coin to cover the cost of mailing.

Short-Wave Broadcast Information

By E. T. Somerset (England)

IN view of the difficulty experienced by most people in obtaining a comprehensive list of short-wave radio-telephone stations, and the fact that a large number of the readers of RADIO NEWS have constructed the short-wave broadcast receiver featured by this magazine, the writer has compiled the list of stations given below, grouped into three divisions, corresponding to the tuning coil which must be used with that waveband.

Of course it must be realized that the bands overlap; for instance, 2XAF may be found to come in at the extreme upper end of the scale with No. 1 coil, as well as at the lower end of No. 2. This is explained also by the fact that different tubes and detector voltages will cause an alteration in readings.

Should the reader be unfortunate enough to experience trouble with what is known as "Threshold Oscillation" (that is to say, the set bursts into oscillation after a station has been tuned in and the hands removed from the dials) this may almost certainly be cured by inserting an extra R.F. choke in series with that used already; and by-passing the second choke to "A---" with a .0005-mf. fixed condenser on each side.

If there is trouble with body-capacity effects, however slight, an improvement can always be obtained by taking a sepa-rate ground lead direct from the "A--" hattery terminal to the ground binding post on the set, and also by grounding the filament end of the grid inductor.

The following list is, of course, subject to changes, as these transmissions are largely experimental; by the time it appears, WJZ will probably be operating on 22.207 and 18.715 meters. Likewise, Norway's and Denmark's short-wave transmitters will be on the air, and as well PCJJ, which has been removed from Eindhoven;

The new improved **Consrad** Pattern Book

HOOK-UP

The Strobodyne, the most sensational development of the age, is the greatest Super-Heterodyne ever designed. The best known features of Radio construction have been incorporated in this amazing circuit.

And Consrad, the famous Pattern publishers of Radio, have printed the entire constructional details for this entire constructional details for this ultimate development in up-to-date Radio efficiency in a new and most convenient form. The new Consrad creation, a handsomely-bound booklet, contains all the details in complete simplified form.

In this Pattern Book are four complete, full-size blueprints and all necessary constructional data required for as-sembling the Strobodyne—step-bystep instruction.

Write now-get your Pattern Bookyou will enjoy building this marvelous circuit—you will enjoy the results which are sure to be yours with this epoch of radio development—the STROBODYNE.

THE CONSRAD CO., INC. 230 Fifth Ave. New York City



but the wavelengths are not at present definitely known.

-	Meters
Ocean Township, N. J. (WNJ*)	13.88
Rocky Point, N. Y. (2NU)	16.02
Bandoeng, Java (ANII)	17.00
Berlin, Germany (AGC)	17,20
Malabar, Java	17.40
Kootwijk, Holland (PCLL) (beam)	18.70
Scheneetady, N. Y. (2NAD)	21 .9 6
Richmond Hill, N. Y. (2NE)	22.10
Fort Wayne, Indiana	22.80
Houlton, Maine (2XAA)	23.00
Chebusford, England (5SW)	24.00
Pittsburgh, Pa. (KDKA)	27.00
Sydney, Australia (2ME)	28.50
Hilversum, Holland (PCJJ)	30.20
(Temporarily silent)	
New York, N. Y. (2X.M.)	30,00
Berne, Switzerland (EII-9 OC)	32.00
Sydney, Australia (2FC)	32.00
Drummondville, Canada (CF)	-32.00
Zurich, Switzerland (EII 9ND)	32.00
Johannesburg, So. Africa (JB)	32.00
Caterham, England (2NM)	32.50
Coil No. 2 (31.5-68 meters)	
Schenectady, N. Y. (2XAF)	32.77
San Francisco, Calif. (6NAR)	33,00
Malabar, Java	33,00
Melbourne, Australia (3LO)	36.00
Tomsk, Siberia (RA19)	37.00
Paris, France (Radio-Vitus)	37.00
Taipeh, Formosa, Japan (JFAB)	39.50
Lyons, France (Radio Lyons)	40.00
Los Angeles, Calif. (6XBR) (portable)	40.00
Stuttgart, Germany	42.00
Pittsburgh, Pa. (KDKA)	42.95
New Brunswick, N. J. (W1Z)	43.35
Langenberg, Germany (LA)	43.90
Rome, Italy, (LAX)	45.00
Ocean Tp., N. J. (WND)	46.48

Konigswusterhausen, Germany	52.00
Cincinnati, Ohio (WLW)	52.02
Brooklyn, N. Y.	54.00
Columbus, Ohio	54.02
Melbourne, Australia (3AR)	55.00
Nanen, Germany (AGJ)	56.70
Bound Brook, N. J. (3NQ)	60.00
Council Bluffs, Iowa (9NU)	61.06
East Pittsburgh, Pa. (KDKA),	62.50
Richmond Hill, N. Y. (WABC)	64.00
Newark, N. J. (2XBA)	65,18
Inglewood, Calif. (6NAI)	66.04
Coil No. 3 (57-133 meters)	
Perth, Australia (6WF)	100.00
Spokane, Wash, (7XAB)	105.90
Richmond Hill, N. Y. (2NE)	106.00
Los Angeles, Calif. (6NBR) (portable)	106.00
Tilton, New Hampshire (1NY)	109.00
Transatlantic phone.	

WEATHER BROADCASTS FROM NAA

On February 1 the U. S. Weather Bureau began a series of daily transmissions, in Morse code, from the high-power radio station at Arlington, Va., by means of remote control. These schedules are as

the high-power radio station at Arlington, Va., by means of remote control. These schedules are as follows, in Eastern Standard Time: 8:15 a, m, on 74.7, 37.4 and 24.9 meters, 10:00 a, m, on 2.677 and 18.6 meters, 11:00 a, m, on 24.9 meters, 8:15 p, m, on 74.7 meters, 10:00 p, m, on 8,238 and 2,677 meters, 11:00 p, m, on 8,238 and 2,677 meters, 11:00 p, m, on 7.4.7 meters, The 8:15 broadcasts, morning and evening, are in the regular Weather Bureau code; those at 11:00 in the International code, especially for the tise of European weather bureaus, and are re-peated from the Elifel Tower in Paris. Further details may be obtained directly from the Weather Bureau. Bureau.

Short-Wave Data Wanted

 $R^{\rm ADIO}$ stations in many parts of the world are now broadcasting on short wavelengths (i.e., below 200 meters); but because most of their transmissions are still only of experimental nature, RADIO NEWS has found it difficult to obtain, even from the stations themselves, accurate information about their operating frequencies, hours of broadcasting, etc. Readers owning short-wave receivers are therefore requested to report to RADIO NEWS any strange short-wave broadcast (not code)

Convenient Phonograph Socket

FAN who attempts to use the audio A FAN who attempts to use an a circuit of his radio receiver as an amplifier for phonograph music often finds it inconvenient to remove the detector tube each time he desires to insert the plug from the pick-up unit in the detector socket. This may be avoided by mounting an additional vacuum-tube socket on the baseboard of the set, and connecting it in *parallel* with the detector socket. With the receiver arranged in this manner it is necessary only to turn out the filaments of the detector and R.F. tubes, by means of a rheostat on the front panel, and insert the plug from the phonograph in the extra socket.

Special Sets for Navy

 $^{\diamond}O$ prevent its seaplanes when forced To prevent us scapions. To down in flight from being without means of communication, the United States Navy will equip them with short-wave transmitters having hand-driven generators for an emergency. The standard frequency will be 8,770 kilocycles, corresponding to 34.19 meters.

stations they may hear; giving the wavelengths as closely as they can guess the figures from the dial settings, by comparing the latter with the settings for such consistent transmitters as KDKA, WGY and WLW. These reports can be written conveniently on the backs of posteards.

RADIO NEWS will publish the data it receives, for the benefit of the many people who have built short-wave receivers and wish to be informed about everything they can expect to hear with them.

Wholesale Radio Lawsuit

 \mathbf{A}^{N} unusual scene was staged recently in a London courtroom, when a large installment house dealing in radio and other equipment brought suit against 541 of its customers who had entered into "hire-purchase" agreements, for balances due, varying from five shillings (\$1.25) up to five pounds (\$25). Judgments were given by the presiding magistrate for payments in monthly amounts, varying from two shillings (50 cents) up, according to the circumistances of the defendants.

An Obliging Radio Artist

 ${f T}^{
m IIE}$ Sandman," who carries sleep to millions of tired little eyes, is a very real individual to the wee folks in and around Brisbane, Australia, where he broadcasts at times over the local station. More than that, "he can sometimes be seen perched on the top of 4QG with a small searchlight, signalling to his little radio friends. In return, the youngsters acknowledge 'Sandy's' greeting by waving lights, indicating that they have spotted the signals."



The facts prove that YOU can achieve Success in Radio!

Radio News writes us: "In looking over the deater mail received in the last three months we find that the average income of all dealers who gave us their income figures, 38 in number, averages more than \$6,000 a year."

> (Signed) C. W. EMERSON RADIO NEWS

Why don't you think this over and say to yourself, "These dealers are no smarter than I am. If I knew radio thoroughly, I could make that much and more. I know that the Radio Institute of America is America's oldest radio school-that it gives the finest radio instruction obtainable anywhere, and the finest and fullest radio equipment.

"I know that RIA is conducted by the Radio Corporation of America and is backed by General Electric and Westinghouse-that their course in radio is complete and entirely covers every phase of radio, including operating, broadcasting, in fact everything in radio. I know that I can make progress because everything is told so clearly. I can get this instruction at home, and prepare for success in radio without giving up my present job. I can study when I please and as long as I please. With the tremendous opportunities opening up in radio today, I certainly can't

pass up this opportunity to learn more about the RIA course. Here's one coupon I will clip. I want the full facts.' Tear out the coupon and mail it now.



RADIO INSTITUTE OF AMERICA Dept. A-4 326 Broadway, New York City - ---- ---- -RADIO INSTITUTE OF AMERICA, Dept. A-4 326 Broadway, New York City Dear Mr. Duncan:

know	mor	se se e abe	out y	ne j 70ui	your r r new	radio co	og. 1 want to urse.	>
Name	• • • • • •			• • • •			· · · · · · · · · · · · · · ·	-
Addre	\$\$	••••						

Radio News for April, 1928



Proper constants for A. C. operation of the improved Aero-Dyne 6 and the Aero Seven have been studied out, and these excellent circuits are now adaptable to either A. C. or battery opera-tion. A. C. blueprints are packed in foundation units. They may also be obtained by sending 25c for each direct to the factory.



AERO Universal Tuned Radio Frequency Kit

Especially designed for the Improved Aero-Dyne 6. Kit consists of 4 twice-matched units. Adaptable to 201-A, 199, 112, and the new 240 and A. C. tubes. Tuning range be-low 200 to above 550 meters.

This kit will make any circuit better in selec-tivity. tone and range. Will eliminate losses and give the greatest receiving efficiency. Code No. U- 16 (for .0005 Cond.)...... \$15.00 Code No. U-163 (for .00035 Cond.)...... 15.00



AERO Seven Tuned Radio Frequency Kit

Especially designed for the Aero 7. Kit consists of 3 twice-matched units. Coils are wound on Bakelite skeleton forms, assuring a 95 per cent air di-electric. Tuning range from below 200 to above 500 meters. Adaptable to 201-A, 199, 112, and the new 240 and A. C. tubes. Code No. U- 12 (for .0005 Cond.)..... \$12.00 Code No. U-123 (for .00035 Cond.)..... 12.00

NOTE-All AERO Universal Kits for use in tuned radio frequency circuits hats packed in each coil with a fixed primary a twice matched calibration sitp showing reading of each fixed primary AERO Universal Coll at 250 and 500 meters; all having an accurate and similar calibration. He sure to keep these sitps. They're valuable if you decide to add another R. F. Slage to your sci.

A NEW SERVICE

We have arranged to furnish the home set builder with complete Foundation Units for the above named Circuits, drilled and engraved on Westing-house Micarta. Detailed blueprints for both battery and A. C. operation and wiring diagram for each circuit included with every foundation unit free. Write for information and prices.



Metering The Popularity of Programs

T has often been asserted that the multiplicity of aerials in a modern city weakens the field strength of a broadcast station by their absorption effect, when all are tuned in to its wave; and some time ago test experiments were carried on in the suburbs of London by British investigators, who reported confirmation of these theories. It is true that in the United States the studies of station field strength have shown a much greater influence upon broadcast waves by the huge masses of steel and networks of clectric wires in urban centers. The English engineers are now debating more or less seriously the question whether, if a "load indicator" could be devised, showing the output load on a broadcast station's aerial, it would not be possible to determine the popularity of a program, locally at least, by the number of nearby antennas tuned to its frequency and absorbing power.

This would indeed be a welcome gadget for the station owner, and solve by elimination the problem of luring the elusive "applause card" from the coy listener; but, unfortunately, it must be added, no such indicator has yet been invented. There is an opportunity for our ingenious readers, who are always discovering new hook-ups; but we will have to stipulate that plans and specifications for such a device must be accompanied by a working model before they are considered seriously at the office of RADIO NEWS.

HAUNTED!

"You haven't forgotten Freddy, then?" "No, no, even though we've parted forever I still can hear his voice in the still watches of the night."

"Ah, that is the curse of memory."

"Not at all, silly; it's the curse of having loved a radio announcer !"-Gleason Pease.

ALL BUT ONE THING



"Now, my dear, do you understand how the set works?" "Yes, Henry, but how often does the man call to read the wave-meter?" -Wircless Magazine, London

ealers **SOMETHING NEW** MAIL YOUR ORDER

A Radio Trade Paper Edited by You and For You

ALL the latest trends of the industry - modern merchandising methodsproven sales building practices that have been actually tested by brother dealersa complete merchandising service, having for its background years of experience with both dealers and fans.

This is what RADIO NEWS **DEALERS PERSONAL EDI-**TION gives you. Be sure and mail your order now. It means bigger businessbigger profits. Regular price \$2.50 (yearly subscription). Special offer brings this remarkable service to you for \$1.50.

ATTACH YOUR LETTERHEAD!

EXPERIMENTER PUBLISHING CO. 230 Fifth Ave., New York City
Gentlemen: Kindly send me the Radio News—Dealers Persona' Edition, for one year, beginning with the next issue. I am enclosing check for one dollar and fifty cents to cover. This I understand is a special reduced price, two dollars and fifty cents being the regular subscription rate.
Name
Address
City

Contraction of the local division of the loc

www.americanradiohistory.com

2

Dr. de Forest Talks on Radio

(Continued from page 1113)

amplification and, particularly, better loud speakers. I do not consider any of the cones now on the market come anywhere near the perfect loud speaker. Cones invariably favor some frequencies at the expense of others and most of the cones, while over-emphasizing the bass, put a mask of "paper mstle" over the higher frequencies. Although more expensive, more clumsy, and demanding more space, and altogether less artistic, there are certain types of nonmetallic horns now on the market which, with proper loud-speaker units, give far better reproduction than any 18-inch cone. I strongly advocate a radio set built into a large console cabinet with sufficient room to take in one of the larger exponential horns. I know of one or two such combinations of radio and phonograph in one cabinet now being developed, though not yet on the market, which give incomparably better sound reproduction than anything with which the radio public is familiar.

MIL GERNSBACK :---

Dr. de Forest, are you convinced that the present-day alternating-current set is a step in the right direction?

DR. DE FORIST:---As to the technical developments awaiting us in 1928, very rapid progress has been made by a number of leading manufacturers in the solving of the problem of applying raw A.C. to the filaments of the tubes and several first-class sets are now on the market using these tubes, thereby being made enfirely independent of "A," "B," and "C" batteries. There is no question that the trend of the industry is entirely in this direction and that, during the ensuing twelve mouths, we will see the storage battery eliminated, except for the cheaper class of sets. This will be a development which every user of radio must heartily appreciate. The storage battery has from the start been a very serious muisance in the home and will shortly be quite superfluous wherever electric current, A.C. or D.C., is available. The better type of console radio with huilt-in speakers, particularly the higher-priced ones with phonograph combined, will be more and more in demand. And as prosperity becomes more widely distributed, and particularly as the educative influence of radio works its insinuative benefits, more and more will the radio public favor the more expensive and properly-designed amplifiers and loud speakers.

MR. GERNSBACK:-

For the next question, Dr. de Forest, the new so-called "screen-grid" tubes make it possible to use much less current than the old-type tubes. Do you think multi-tube sets with little battery consumption a possibility, and that battery-operated sets might yet prevail in the future?

DR. DR. FOREST: -- Notwithstanding the greater current economy which the doublegrid tubes permit, I do not think that multitube sets for battery consumption will ever again be popular. I think the day of general use of the storage battery and the dry battery is rapidly drawing to an end. The great convenience and sense of satisfaction in knowing that you are not dependent upon a battery which may give out in the midst of a particularly-desired program, will outweigh any other considerations just as soon

as the socket-power units and the A.C. tubes are a little further perfected,

MR. GERNSBACK :--

What are your views on television, in view of the past experiments by Baird of London, and by the research engineers of the American Telegraph & Telephone Corporation? Do you believe television attachments to radio sets a matter of the near future? If so, how soon?

DR. DE FOREST:-I am quite naturally interested, and have inspected the work in television which has been carried on in this country, particularly that by the American Telegraph & Telephone Corporation. Ĩ must pay the highest possible tribute to the ingenuity and patient research which has made possible the system employed by the American Telegraph & Telephone Corporation. It is little less than a scientific mir-Nevertheless, I know my views on acle. television have been somewhat disappointing to those who wish to believe that in the next few years every one can have a moving-picture show at home, broadcast direct from his favorite theatre. Frankly, I cannot foresee such a millennium for the radio fan. Until some radically new discovery has been made in physics, some new principle or operation of which we today have no clear conception, television apparatus must continue to be extremely intricate, delicate, requiring the constant and most careful attention of highly-skilled experts, and be built and operated at very great cost. Until such a new discovery, therefore, I think we must limit our television expectations to an occasional demonstration under the auspices of one of the few great electrical engineering and manufacturing corporations. Television in the popular mind means radio broadcasts of distant scenes as they transpire.

I have little patience with some of those whose names are associated with the history of this new development, who seem willing to impose on the gullibility which the public evinces whenever the word "Television" is used. A few years ago it was impossible to get anyone to believe in wireless telegraphy, and later in the possibilities of the wireless telephone. Of recent years, however, the progress in popular science has been so phenomenal that general gullibility, or willingness to accept any prediction along the lines of invention, takes the place of the skepticism which formerly made the work of pioneers so difficult.

MR. GERNSBACK - According to your thoughts, Dactor, I presume what you mean by a new development in physics would be a television apparatus without revolving parts, such as that we have at the present time?

Dr. DE FOREST:-Yes, I think that such a development will eventually be made, but it will be the result of some discovery as radical and as unexpected as was the invention of the X-ray by Roentgen; and not until we have another Roentgen or Michelson who produces or makes a new discovery as radical as the X-ray was at the time he made it, may we bring into existence the television which we all would so gladly welcome.

MR. GERNSBACK :--- I think you are a little too modest, Doctor, when you mention as an example the X-ray. Why didn't you say the vacuum tube? You are the one who invented that unexpected wonder. Let me ask you the next question.

What, to your mind, while we are talking

electrify your set the easy practical Knapp way



The Kit completely assembled with a metal cover in place. Operates on a metal cover in place. Operator 105-120 volts AC, 50 to 60 cycles.

Knapp & power kit

No expensive short lived AC Tubes, no troublesome re-wiring, no annoying hum. Increase instead of decrease the efficiency of your set, no waiting ... the Knapp "A" Power gives you music *instantly* at the snap of a switch.

shap of a switch. This absolutely dry "A" Power is not in any way a battery combination ••• not something to add to your battery ••• it is the most efficient "A" Battery Elimina-tor ever designed. It supplies unfailing "A" current to any set using 201-A or 6 volt tubes, regardless of number.

Magic Silence

So silent is Knapp "A" Power, that you can place a pair of head phones directly across the output and not be able to detect This is made possible by the a hum. efficient Knapp filter system, consisting of 2 over sized chokes and 2 condensers of 1500 microfarads each. A new discovery makes these amazing capacities possible in the small space of 2x2x8 inches !

Absolutely Dry

ADSOLUTELY Dry There is not a drop of moisture in this absolutely dry unit. The condensers are backed so that not a drop of moisture remains. The mique, fully patented, solid, full-wave rectifier is absolutely dry. No water...no acid ... no alkali ... no these... no electrolytic action. Nothing to get out of order. Nothing that needs attenton.

Assemble in Half an Hour

Assemble in Hall an Hour The Knapp "A" Power Kit is so easily assembled, that within half an hour after you receive it, you can have it in operation. "The parts seem to fall in place, No drilling and very little soldering. Everything supplied, even to the screws, wire, drilled base-board and metal cover. It is so complete, that even a plug is supplied so that a "B" Eliminator may be operated from the same switch. We have never seen such simple instructions.

Big Profits for Set Builders

Our president, Mr. David W. Knapp, is offering the set builders of America, for a limited time only, a money-saving, profit-making plan which is unique in the annals of radio. Send the coupon today, before it is too late.



Knapp Electric Corporation Port Chester, N. Y. MR. DAVID W. KNAPP, Pres.

Knapp Electric Corporation 312 Fox Island Road, Port Chester, N. Y. Send me complete information regarding the Knapp "A" Power Kit and your special discount to Set Builders.

			•••	•••	• • •			•••	•••		•••		••	••	••	••	• •	 • •	•••	•••
Addr	css.	•	•••	•••		• • •		•••	•••	•••	•••	•••	•••	••	••	••	• •			•
Nanu	e	• • •	•••	• • •	• • •	•••	•••	• •	•••	••	•••	••	•••	•••	••	• •	• •	-	•	• •





Operating your A. C. Radio Set with a worn or defective tube is like running your car with a missing cylinder!

Replace the defectives with CeCo A. C. Tubes. They will work in harness with any other unworn tubes you have.

But you'll get better results, clearer tone, greater volume, longer life if you CeCo-ize your receiver by putting a CeCo Tube in every socket.

Your dealer will help you select the correct types for your set. Ask him.



Write for descriptive circular

C. E. MFG. CO., Inc., Providence, R. I. Largest Exclusive Radio Tube Mfrs. in World. OVER 3 MILLION TUBES IN USE



of vacuum tubes, is the ideal vacuum tube of the future? What should be its outstanding point?

DR. DE FOREST:—I think the ideal vacuum tube of the future should operate without batteries, it should be small, ruggedly-built, absolutely free of all tube noises and nonmicrophonic. It goes without saying, that it should be operated without overloading and with absolute freedom of alternatingcurrent or direct-current noises. I think that such a vacuum tube will be produced within the next two or three years.

MR. GERNSBACK:-That is very interesting, Dr. de Forest.

May I ask you, what are the latest developments on your "Phonofilm?" Has it been completely commercialized, and where, at the present, is it most used?

DR. DE FOREST :- Answering that question, it has not been commercialized completely, but everything is being done to prove, to most of the motion-picture magnates and authorities in this country, that it is going to occupy a very important part in almost all motion-picture programs in the future. In this respect, the attitude of the men that control the industry has completely changed within the last two years. I might say that great technical progress has been made during 1927 in perfecting talking motion pietures, including the method using phonograph records, and the Phonofilm method of photographing sound-waves on the margin of the film. Both systems have been amply demonstrated before the public in motion-picture theaters, so that it is now fair to draw certain conclusions relative to the practical and commercial possibilities of the two-the one exploited by Warner Brothers as "Vitaphone," and the other by the Phonofilm Company and by Fox under the name of "Movietone." It is only fair to state at the outset that Movietone is a complete copy of Phonofilm, differing in no essential manner from the earlier method, but having been exploited commercially to a much greater degree. The practical advantages of the Phonofilm method over that of the synchronized phonograph in producing, and also in reproduction, have been so elearly demonstrated to those who are familiar now with the actual manipulation of the two methods in studio and theater, as to confirm beyond any question the correctness of my prediction (made in 1919), that the success of the talking picture would lie eventually entirely with the method which photographs sounds on the film margin. With the Phonofilm method an entirely new art and technique had to be developed from the very beginning; whereas, with the synchronized phonograph we had a highlydeveloped industry of the past thirty years to fall back on. The first six years of Phonofilm pioneering resulted in solving the basic problems and demonstrating to any unbiased technician that the method was practical and could without question be eventually worked out to a point of perfection equal to, or excelling, the phonograph art. Both the modern method of recording and reproducing from the phonograph and that of recording and reproducing from the Phonofilm owe an immeasurable debt to the radio art, or more particularly to the art of vacuum-tube amplification. Without the vacuum-tube amplification. highly-advanced technique along this line which the demands of radio broadcasting have produced, Vitaphone or the Phonofilm in their present states of perfection would be quite impossible. But taking full advantage of what the radio broadcasting art has





There'll be no Radio Trouble Wrinkles now!

Here are the solutions to Radio Questions of every conceivable nature.

Have you a question to ask about Radio?—about this circuit, that circuit — this method or that method of Amplification, Balancing, Regeneration, Transmission, Set Construction, Operation, Speaker Design, Control, Electrification, Accessory Installation, Antenna Possibilities—?

Then keep this book of 1001 Radio Questions and Answers always near at hand.

1001 RADIO QUESTIONS AND ANSWERS—wherever there is a question or a doubt you are certain to find a solution here.

These are the questions that the readers of Radio News have asked, are asking, and will ask—and now, with this book in your home, you can have them answered whenever you ask them.

1001 RADIO QUESTIONS AND ANSWERS

50c.
ON ALL NEWSSTANDS
If your dealer has none on hand USE COUPON
EXPERIMENTER PUB. CO., Inc. 230 Fifth Ave., N. Y. C. Gentlemen: Kindly send immediately your 1001 RADIO QUESTIONS AND ANSWERS book. Enclosed is 50c.
Name
Street address
CityState

produced along these lines, there still remain very difficult and intricate problems in Phonofilm; particularly as regards the lightrecording, sound-photographing means; and the successful taking off of sound from the photographic record on the film. And in between lie many problems in photography, exposure, development, printing, and proteeting the sound record.

Great progress has been made in the perfecting of the "photion," or gas-filled lamp, which is placed in the camera and which, when connected to the output of the vacuum-tube amplifier, reproduces perfectly in light variations the electrical values impressed upon its terminals. The photion tube, which I first conecived in 1918 and patented in 1923, has thus far proved its distinct superiority over other methods of telephonic light control, such as the vibrating mirror and the "light-valve." (The latter is a type of bi-filar Einthoven string galvanometer, acting as a shutter to "valve" the light from a fixed source). While the photion is not yet fully perfected, its reproduction, in light fluctuations, of telephonie currents impressed upon it is so nearly perfect, throughout the useful range of audio frequencies, as to justify our faith in its continued supremacy in the field of sound photography. Its simplicity, compactness, lightness of weight, and ruggedness, as compared with that of the vibrating mirror and light-valve, argue powerfully for its continued use in preference to the other types.

Particularly do the above advantages hold for portable Phonofilm or Movietone equipment, where a light, casily-portable camera, to be quickly carried from a truck and set up at a moment's notice for recording swiftly-passing topical events, is absolutely essential. And the success of the audible topical weekly is already so abundantly demonstrated as to prove that, in the future, this feature will become more and more essential in every motion-picture program. Much progress has been made also in the design of compact portable amplifiers for such recording of outdoor news events.

The difficulties in scenring perfect motion of the film past the light source in the camera have been eliminated during the past year; so that now it is possible to secure as perfect film motion with a cheap portable projection machine as can be obtained with the finest phonograph turntable,

For use in the projection room of the motion-picture theater highly improved amplifiers with sound "fade-in" and "fadeout" devices have been largely perfected. The Phonofilm amplifier for the theater has been made very compact and fool-proof, requiring practically no skill on the part of the motion-picture operator for its proper manipulation. Back of the screen has seen possibly the most striking advances of any in this art during the past year. New loud speakers of entirely novel design, permitting a naturalness of reproduction which is almost uncanny, have been worked out. A new form of screen, transparent to sound and possessing the necessary optical property to throw a brilliant picture, has been found; so that the sound no longer seems to emanate from one side or the other of the screen, but directly from the mouth of the speaker, wherever he may be in the picture. 1928 will see these various improvements, which I have described, exploited and demonstrated to the public in many hundreds of theaters scattered throughout the country.

The chief remaining problems in the talking-picture art lie, not in the theater or engineering laboratory, but in the motionpicture studio. There scenario writers, producers, artists and comeramen must gradually acquire working knowledge of the new art and how to take full artistic advantages of the countless and immeasurably rich possibilities which this new art has now brought forth, for the entertainment and cultural uplift of the motion-picture public.

Mr. GERNSBACK :- My final question:

On what particular new thing are you working now, and can you tell us something about it?

DR. DE FOREST :- I am working exclusively on Phonofilm and allied problems at the present time. Among these are improved audio-frequency amplifiers and loud-speaker devices which can be used in connection with either Phonofilm or with radio, or the electric phonograph.

What Constitutes Tone Quality?

(Continued from page 1135)

portion of the vibrator near B. The lowerpitched waves produced at the rear must travel farther before emergence than the higher-pitched waves generated near B; in both cases the necessary conditions for amplification. It should be noticed that the vibrator board, as a sound amplifier, functions much as does the disc of a fixed-edge cone.

"It may be seen that the horn described is not a simple air-volume resonator, but that it is a combination in a single instrument of a series of air resonators, a reflex horn, a straight horn, a curved horn, a reentrant horn, and a resonating diaphragm or sounding board; and that it makes use of both multiple and cross resonance, all in the effort to secure as nearly as possible uniform tone amplification."

BREAKING INTO GOOD COMPANY

It is evident that Walter Damrosch, conductor emeritus of the New York Symphony Orchestra, derives great enjoyment from his fan mail. He told with particular zest of a South Dakota listener-a plainsmanwriting to say that when Mr. Damrosch was broadcasting the "Pilgrim's Chorns" from Tannhaüser that he grabbed up "his old celio" and joined in,

"I did that," the plainsman confided, "so that I could say I once played with Walter Damrosch and the New York Symphony Orchestra."

LET THE BUYER BEWARE

ALTHOUGH European listeners are held strictly to payment of a fee for the privilege of owning receiving sets, in Bavaria they are allowed a week's free trial of a set purchased on approval, without taking out a license. In England, however, the radio magazines complain, a number of public functionaries seem to be of the opinion that it is an offense against the law to purchase a radio set without having a license in advance. This places radio apparatus somewhat in the category of revolvers and narcotics.

- PAST NO "TUBES" - NO "B" BAT-TERIES - NO COSTLY "ELIMINATORS" WITH THE SKINDERVIKEN TRANSMITTER

OPERATION

from a

SPEAKE

UNIT



Simple microphone unit provides a most effec-tive and inexpensive way to satisfactory speaker operation. Easy to build and operate circuit. Everybody can do this now with a Skinderviken Transmitter Unit. The unit is fastened to the dia-phragm of the speaker unit. It will act as a "microphonie relay." Every time an incoming signal actuates the diaphragm, the electrical resist-ance of the microphone unit will be varied correspondingly and the cur-rent from the battery, in series with it and the loud-speaker, will fluctuate accordingly solved.

solved.

The results from this very novel and simple unit

The results from this very novel and sumple only will astound you. The expense of this hookup is trifling compared to elaborate tube circuits that give no greater actuation of the speaker. Besides this there are many other valuable uses in Radio Circuits for this marvelous little unit. Every builder of Radio sets should have a few on hand.

LISTENING THROUGH WALLS

This Unit makes a highly sensitive detectaphone, the real thing—you listen through walls with ease. Plenty of fun and real detective work too.

CONDUCTING SOUNL WATER SOUND THROUGH

Make yourself a miniature submarine signaling apparatus like those used during the war. Simple circuit with this microphone unit gives splendid results.

12-PAGE INSTRUCTION BOOKLET containing suggestions and diagrams for innumerable uses malled with each unit.



Order as many as you want—use the coupon below When the postman delivers your order you merely pay him 95c plus a few cents postage. If you order two units you pay him only \$1.75, plus postage.

PRESS GUILD, INC. 16-18-R-East 30th St., New York, N. Y.
Please mail me at once
Name
Address
CityState



4614 Srping Grove Avenue.

Broadcasting in Foreign Tongues

IN the September, 1927, issue of Ramo NEWS, one of our contributors, Charles Magee Adams, discussed the effect of radio broadcasting on American speech, and commented that foreign-language broadcasts in this country, save for a few elementary lessons, seemed unknown.

He was corrected by the sponsors of German broadcasting over station WIBO, Chicago, who had put on regular cultural programs on Sundays for those of German speech; but since that time "Mike" seems to have acquired the gift of tongues. Station WCDA, New York, devotes a considerable portion of its time to the exploitation of the melodious Italian language; and now WMBI, owned by the Moody Bible Institute of Chicago, has undertaken Scandinavian services on Saturday evenings and Tuesday afternoons, German services on Thursday afternoons, and Yiddish services on Friday evenings.

The European listener may acquire a radio familiarity with practically every language of the Continent, as he sweeps his dials from Moscow, Motala and Angora to Madrid, Paris, and Cork; perhaps the American will have an opportunity to cultivate the linguistic faculty hitherto so neglected in the United States.

Possibility of Receiving Europe

H AVING the advantage of the time difference, European fans hear American stations in the small hours, as Yankees hear the Pacific Coast. Recent reports indicate that on January 16 unusually good reception of American stations, even as far west as Oakland, was reported throughout England.

While the distance from the castern United States to Europe is not so great as that from California to Japan, the American is handicapped by the fact that midnight in England, or 1:00 a. m. in Germany, is only seven o'clock in the evening in New York. For that reason transatlantic reception, though highly interesting, has never been practicable for many American listeners; especially as hitherto the highest powered stations of Europe have been out of the 200-600-meter hand, requiring special coils in receivers tuned to them.

However, during the past year there has been a great increase in the number of super-power medium-wave stations in Europe; and it is quite possible that in good locations, free of other interference, some of these might be received early in the evening in parts of the United States.

Poland has opened a 10-kilowatt station at Katowice, operating on 422 meters. The short-wave transmitter of Daventry, England, 5GB, has been increased to 30 kilowatts, it is said; though unfortunately its wave is that of WEAF, 491 meters. Milan, Italy, has now much higher-powered equipment on 545 meters. Hungary has a "60kilowatt" (25-kw. input) at Czepel in the Danube, near Budapest. And headlines announce that Zeesen, in Germany, is to be of higher power than the 100-kilowatt transmitter at Schenectady (something to be regarded with a grain of salt), and that "Radio-Paris" contemplates going this better, with a 150-kilowatt input.



THE PERIDYNE, due to the new principle on which its construction is based, assures positive true Interstage Resonance, and thus the perfect onedial receiver has become a reality.

Distance, tone, remarkable performance under all circumstances—these are but a few of the remarkable accomplishments which can be had with the Peridyne.

Note the schematic symbol that had to be specially designed to designate the Peridyne character. No other symbol of this arrangement is provided in radio practice.

5 Full-sized blueprints and a 16-page instruction book.

Send today for the complete blueprints and constructional data for the Peridyne—only 50c. Build this set and prove to yourself its remarkable features and high efficiency.

CONSRAD CO., INC. 230 Fifth Avenue New York City

CONSRAD COMPANY, INC. 230 Fifth Ave., New York City Gentlemen: Enclosed find 50c., for which kindly send me a complete set of blueprints and full constructional data for the Peridyne. Name. Address. City.

Cincinnati, Ohio

What the Federal Radio Commission Needs

1275 Nelson Avenue The Bronx, New York City.

Editor, RADIO NEWS:

This letter should interest you, because it has to do with a great invention which should revolutionize the radio industry, both commercially and scientifically.

Ever since radio became popular, I began to tinker and experiment with different kinds of hook-ups and devices for the improvement of radio. It got me like a crossword puzzle. Once I began, I just had to finish. I spent almost as much money on triple bromides as I did for radio material. Edison paid large dividends last year because of me; because I stayed up every night, every night until carly morn, until my eyes shut involuntarily.

But my efforts have not been in vain.

I have finally succeeded in inventing a device that will undoubtedly prove the biggest and most amazing radio feature since Marconi sent the first message through the other

My invention has been tried out in a practical way, and those few who witnessed the first exhibition marvelled at its wonders.

You will marvel too when I describe what this new invention can do. Remember, I have tried it out, and it worked.

Here's what this new device will do:

It will automatically stop any broadcast station from broadcasting, at the same time causing that same station to broadcast a program sent through my invention, but on the carrier wave of that station.

It will be impossible for any one to deteet who has stopped the programs of the station, and unless that station shuts off its power, I will be able to send my own program on the station's carrier wave. 1 have done it, and it has proved entirely satisfactory.

It took me almost four years to perfect this device. Hard work and money bor-rowed from friends and relatives are responsible for its success.

Two weeks ago I gave it a practical test at a radio broadcast station, located in New Jersey.

My device had to be delivered on a truck and had to remain on the truck as the machine, or Vicograph as I call it, weighs about one thousand pounds. The Vicograph is portable, especially so made on account of its necessity of being moved from place to place.

The machine consists of numerous coils, water jackets, water coolers, heavy cables, dry- and wet-cell batteries, tubes, dials, switches, and other accessories especially



"The shrill, whistling sound ceased, and all that was heard was the carrier wave; a sound similar to the one caused when steam escapes from a radiator."



Mozart-Radioceive Speakers and Speaker Units FOR SEASON 1928-9

FANS who know that the Loud Speaker Unit is the very heart of any Radio, are demanding better and better performance, hence the reason for the Radio-ceive Twin Balanced Armature, far outselling all others in this market.

Here indeed is true Push-Pull Tone Reproduction at a fraction of the cost it can be obtained in any other way, and with the very minimum of current consumption, and voltages ranging all the way from 90 to 400.

ú

And for those who want a good cone unit at a lower figure, we offer our single balanced armature, which will outperform most others selling at twice its price.

Or in a complete speaker, our Mozart 26-in. Wall-Cone (not a kit) and Drum Type with these units, are guaranteed on a moneyback basis to excell in appearance and performance all others in their class.

Single Unit, 5 (t. cord (1150 ohms)......\$4.00 Twin Unit, 10 (t. cord (2000 ohms)...... 6.00 26-in. Wall Cone Speaker, Single Unit......8.00 Zo-in. Wall Cone Speaker, Twin Unit......10.00 Drum Type Speaker, Twin Unit......15.00

THE FERGUS CO.

TRANS MITTING

APPARATUS

A Complete Stock at "Chi-Rad"

In addition to our regular broadcast apparatus we carry a very good stock of transformers, chokes, grid leaks. high test condensers, etc., for trans-mitting purposes.

NEW SHORT-WAVE COILS Specially built by "Chi-Rad." Write for descriptive bulletin and catalog. Dealers and set-builders please use business letterhead when writing for discounters.

Chicago Radio Apparatus Co.

415 S. Dearborn St., Dept. RN, Chicago

NEWARK, N. J.

239 ELIZABETH

AVENUE

discounts.





(Rosbloom)



Fourth Enlarged Edition

A remarkable book of greatest value to all engineers, mechanics, and others interested in Diesel engines for land, marine, locomotive, automobile, and aircraft use. Over 300 tables, hundreds of formulae, profusely illustrated with color and plain views. Courses of instruction on all leading types.

830 pages. Size 5×7 inches. Bound in flexible, semi-flexible and stiff covers of very attractive imitation leather with reinforced back.

Price \$5.00 Prepaid

Order Direct from Book Department

EXPERIMENTER PUB. CO. 230 Fifth Avenue, New York



designed for this particular device. They are too numerous to mention here.

I will now give you a description of what occurred at the New Jersey broadcast station when I made my first practical test.

The truck was placed about a hundred yards from the transmitter. The station began to broadcast a program of dance music played by a fourteen-piece orchestra. The station used a frequency of about 1010 kilocycles. (I do not wish to mention the name or exact frequency of the station at the present time.)

The band got well on its way into the middle of its first selection, when I began to move a lever, slowly, to the point on a dial on the *Vicograph* where appeared the figures 1010. Through my receiver, which was part of the outfit, I could hear a whistling, shrill noise, becoming fainter and fainter, until the pointer on the dial was directly over 1010, the corresponding number of the transmitter's frequency. The shrill, whistling sound ceased, and all that was heard was the carrier wave; a sound similar to the one caused when steam escapes from a radiator.

That was wonder number one.

Of course, the staff of the station were aware of what was going on. I was doing all this with their permission, and they were truly amazed, bewildered, astonished, and puzzled. The six men, all radio engineers, stood there, open mouthed, open eyed. They were stunned.

 \ensuremath{I} did not stop the experiment right there. \ensuremath{I} went on.

Included in the outfit was a small portable talking machine. This machine was mounted next to a microphone of my own design. I turned on the phonograph, and a record was played.

I began to move another pointer on another dial. As soon as the pointer was over the figures 1010 of the second dial, the receiver brought forth music being played by the phonograph.

That was wonder number two.

One of the men present skeptically asked me if it weren't possible that the *Vicograph* also consisted of a transmitter which broadcast the phonograph music on its own wavelength, and picked up by the receiver.

I suggested that we ride over about a mile from where the truck and device stood, and listen to some other radio receiver.

We got into a car and drove off to a Chinese restaurant. There we were permitted to tune in on 1010 kilocycles, and sure enough, we heard the song being played on the phonograph. My assistant remained, of course, to continue to play the record as soon as it ended.

One of the men even called up the engineer at the broadcast station to learn if the band was playing. He replied in the affirmative, and also gave out the information that an entirely different program was being entited from the transmitter's radio than the one being played by the band. He too was puzzled.

Assured that my invention was perfect, we all went back to the truck. Then I readjusted the dials, and once more the station's program was heard. However, I went a step further.

We tuned into a powerful New York broadcast station. An opera was going on. I moved the pointer to that station's corresponding wavelength. The music ceased.

Not only did it cease coming through my receiver, but when we inquired whether the program was coming over the New Jersey



LOUDSPEAKER TillS book, a complete history of radio acoustics, has been compiled by Clyde J. Fitch and many other eminent authorities on loud-speaker construction. The data thus assembled is now ready to be presented to you in the most comprehensive

Way back in the days of "canned music," those hectic days when distance was all-engrossing to the radio enthusiast, and up to the present time when true tone reproduction is the objective of every radio fan through every phase of this development—to each milestone of this progress, this little book will take you.

manner yet achieved.

Every type of loud speaker—the Exponential Horn — the Cone — the Piczo Electric Loudspeaker—Power Speakers, and Roll Type Speakers, and many more, fully explained. Complete constructional data, diagrams, etc., assure positive results for the experimenting fan.

52 pages, 6 x 9 in., illustrated

25 Cts.

On all newsstands---if dealer has none write direct

CONSRA	D CO., INC.
230 Fifth	Ave., New York City
Gentlemen Kindly new book, for which	a: send me a copy of your interesting "How to Build Modern Loudspeakers," I am enclosing 25c.
Name	
Address	••••••••••••••••••••••
Clty	State

Radio Netes for April, 1928

transmitter's radio receiver, the operator told us no. We even tried out the receivers of some nearby dwellers, but there was no program heard. Only a carrier wave.

Some of the radio listeners thought their sets had gone wrong, or that an SOS was being relayed, or that the station had some technical trouble. But we let them know that we were doing this and that everything would be all right in a few minutes.

And everything was all right in a few minutes.

I tried the experiment on at least thirty stations, both nearby and distant, with the same results. We even phoned several of the local ones asking if they had any difficulty a few minutes ago, and they all informed us yes. Two told us that they had many phone calls advising them that their programs were discontinued, but that they could not understand the reason. They were puzzled,

1 wasn't.

The other men and I went back to the transmitter, then to Newark, to the studio. There I was introduced to the real owners of the station.

Soon, several other prosperous looking men joined us.

The engineers explained the invention to the newconcers and for their benefit, I went through the experiments again. They were amazed like the first ones.

Before long, we began to talk about the commercial value of my amazing invention, and soon an offer was made me. I refused any offer. I told them so. But they insisted that I sell the invention. Of course, it was patented, and I had fifteen claims on various patents.

They took the initiative and offered me \$250,000. I merely sat back and took another puff on my Lucky. "Well, gentlemen," I said, "if I am going

"Well, gentlemen," I said, "if I am going to sell, I wouldn't consider anything less than a million for the *Vicograph*."

At that remark, several of the gentlemen got up and went into a conference in one of the corners of the spacious room. In a few minutes they returned to the table. One of the men slood up and said, "Sir, we have talked the matter over carefully, and upon careful consideration, we have decided to pay you the amount asked for a million dollars."

Of course, I did not act surprised because I expected that amount. I knew that someone would pay it, and I considered this party of men fortunate in having obtained such a wonderful device, a device that will revolutionize radio.

One of the party took a small check book from his pocket, and with a quick stroke of his fountain pen, wrote out a check for one million dollars.

I took the check, shook hands with all the men around me—and then I woke up! Victor W. COITEN.

THE DEPTH OF DEBILITY

 M_{RS} , WILL DOOLTTLE: "My husband's so lazy he won't do nothin' but set to home and listen to the radio."

Mrs. U. S. Less: "Huh! My old man's so durned lazy he won't listen in unless I'm home to turn the dials for him."

ENOUGH TO RILE 'EM

It is said that both Dempsey and Tunney want to fight in England. We're not surprised, considering the dreadful radio pictures of the pugilists published in this country.—London Opinion.



36.



What's New in Radio

(Continued from page 1119)

the current flows through the battery in the correct direction. To do this, serew the connecting plug into the socket and turn on the switch; if the connections are correct the animeter should read "charge." If the meter reads "discharge," remove the cap of the connecting plug (leaving the body in the lamp socket) turn the cap one-half turn (180°) and replace the cap in the body. The meter should now read "charge," indicating that the circuit connections are correct.

Center-Tapped Resistor For A. C. Tubes

Experimenters who are rewiring their old receivers for use with the new A.C. tubes and those who are building alternating-current-operated receivers will find great convenience in the use of a new type of centertapped fixed resistor. The units are available in several resistance values, and so designed that they may be fastened directly to the filament terminals of any tube socket. One connected in this way provides an ac-



Drawing shows details of new "V" type centertapped resistor unit. It consists of two units of fine resistance wire wound on an asbestos core.

curate electrical center for grid-return leads. The illustration on this page shows the mechanical construction of the resistor unit. It consists of two wires fastened together at one end and forming a "V" shape, with soldering lugs attached to their other ends for making connections. Each wire is of identical construction and resistance, and consists of a core of asbestos cord on which has been wound a single layer of very fine resistance wire. The resistance wire is spacewound on the asbestos core, in order to give the unit a total resistance equal to that of the wire used; and each resistor unit is covered with spaghetti tubing for insulating purposes.

The resistance units described may be used in many different parts of A.C. receivers. They are available in eight sizes, ranging in resistance from 10 to 200 ohms, for connection directly across circuits having maximum working voltages of from 3.5 volts to 17 volts. For use in the filament circuit of 226- or 227-type tubes a 10-ohm unit should be used, in that of a 171-type tube a 20- or 30-ohm unit; and with a 210or 280-type tube a 50-ohm unit is required. For circuits having higher voltages, the re-

sistance of the units employed should be increased in proportion.

Two New Resisters Answer Power-Unit Needs

Two new resistance units, which answer the requirements of the builders of "B" socket-power units, have recently been put on the market; both will be found illustrated in these columns. One is an $\operatorname{adjustable}$ (tapped) resistor, designed especially for providing a voltage drop to be used in biasing the grids of amplifier tubes; and the second is a rheostat potentiometer in different values, for which there are many applications in the voltage-dividing circuits of power units.



Rear view high - vesist Rear trice of high - resistance theostat shores method of mak-ing adjustment ceith contact arm. The units are variable in the steps and are 16 netted as either potentiometers or rheestats.

RE 1 MILLI AS INCLUSION OF A PARTY

Both the tapped resistor and the rheostat are made by winding a special wire whose resistance changes little with the heat, on a tube or base which is very heat-resistant, and coating the entire surface of the unit with a glass-like enamel. The enamel is applied by a method which is largely responsible for the long life and permanent accuracy of units of this type; it covers the

The high-resistance rhe-ostat - potentiometer is designed for one-hole mounting, and is ad-justed by a small knob located on the front of the panel. NUMPERSONAL AND ADDRESS AND ADDRESS ADDRE

IN MURILINES IN MEAN AND DURING MINING



entire surface of the resistor and, in a firing process, is intimately bonded with the surface of the resistance wire. The heat developed under the load, when the resistor is used, is instantly transmitted to the enamel and from the enamel to the air. Heating and cooling do not affect either the wire, the enamel, the refractory tube or base; as they all expand and contract alike. Also, the total resistance of the unit remains practically constant, regardless of the temperature. Therefore, these units are excellently suited to the requirements of the radio power units.

The tapped fixed resistor has a total resistance of 375 ohms and is capable of dissipating 12 watts. It is equipped with three taps and the arrangement is such that it is possible to obtain 15 different resistance



This tapped resistor may be used to obtain grid bias for power tubes, when a sacket-power unit is used





These are the circuits to build / FULL CONSTRUCTIONAL DATA.

dio - read the RADIO their homes at all times. LISTENERS' GUIDE and Besides CALL BOOK. Full con- tional data there is a structional data for the complete and up-to-date above circuits, also for list of all radio stations many others. The RA-**DIO LISTENERS' GUIDE** and CALL BOOK is the accepted chronicle of the latest developments of the RADIO WORLD.

Learn how to improve your set by simple little adjustments and changes. Every radio fan or layman should have one of

Follow the trend of ra- these valuable books in the construc----their owners; call letters, wave length and power (watts), also their locations.

> No home is complete without this accurate guide.

> The RADIO LISTENERS' GUIDE and CALL BOOK is revised and brought up to date quarterly.



Gentlemen: Enclosed find 50c., for which send me a copy of the latest issue of RADIO LISTENERS' GUIDE AND CALL BOOK.

Address

Name.....

values between 25 and 375 ohms. The unit is four inches long, approximately 5%-inch in diameter, and provided with five soldering lugs for terminals. It will pass a current of 300 milliamperes and may be used in any "B" socket-power unit without danger of burning out. It is especially intended for use in circuits where the entire plate and shunt-resistor load of the socket-power unit passes through the grid-bias-voltage resistor.

The rheostat illustrated is made in thirteen different values, ranging in resistance from 1 to 50,000 ohms. Each type is of identical construction, and is capable of dissipating 20 watts when mounted inside a cabinet or 25 watts when exposed to the air. The unit is provided with 16 steps, and its slider is adjusted with a bakelite knob; three terminals are provided, so that it may be connected as a potentiometer if desired.

Radio in Italy

WIIILE in America, we are told, it is up to the radio manufacturers to help out the broadcasters, in Italy the broadcasters are anxious to promote the sale of radio apparatus. This is because every new owner of a radio sct, no matter how small, pays a license fee for the support of broadcasting. Accordingly, the Italian Broadcasting Co. (Unione Radiofonica Italiana) has announced a prize of 40,000 lire (about \$2,100) for the best new set design, presented by an Italian manufacturer, of a set capable of bringing in all the Italian stations on the loud speaker, as well as adapted to mass production. A quarter of this sum will be awarded as a prize for the best home-built set, and an exposition of the entries will be held. The company has been reorganized as the "E.I.A.R.," with a capital increase to \$420,000.

The possession of radio receiving sets, even for broadcast listening, has been prohibited in several districts, such as the cities of Finnic and Zara, near the Jugoslavian frontier. This is an extension of the former forbidden district, and is made for military and political reasons. A military as well as civil permit must be obtained for an exception from this rule. In addition, a group of patents obtained by Manrico Compare for radio inventions have been "expropriated" by the Italian government for purposes of national defense. They include combination telegraphic instruments for radio or land-line use, which may be used with a form of typewriter.—E, Z.

Care of Electrolytes

I N order to obtain long life and satis-factory service from rectifiers and condensers of the electrolytic type it is essential that nothing but pure distilled water be added to the electrolyte. This rule is just as essential in the operation of electrolytic cells as in the case of storage batteries; for, if city water from the pipes in the house is used, the mineral contents may cause a chemical action which will destroy the efficiency of the unit. If the electrolyte of a cell is evaporating too rapidly, it is possible to correct this by adding a small quantity of thin mineral oil; this will form a film which retards evaporation.

The Listener Speaks

(Continued from page 1104)

During the period of this flight, the writer was at Belle Isle Station, which is situated on a rock 9½ miles long, and 3 miles wide, lying between Newfoundland and Labrader, at the entrance of Belle Isle Straits, where the Canadian Government has established a fully-equipped high-power commercial and radio direction-finding station.

When Commander Byrd flew in the plane "Miss America" from New York to Paris, the writer was on duty up to midnight, and took several radio bearings on the signals cmitted by his radio apparatus (call WTW) so that if, by chance, he had fallen into the sea we could have plotted his position fairly accurately. The signals of his auto-matic transmitter came in very loud and clear until he was more than half-way across, and could even be heard until daylight intervened. I mention this as an example of the value of adequate radio apparatus on these transatlantic flights.

Now the point is, why is radio not used more extensively in planes on transatlantic flights, and also why don't these ships of the air carry experienced and competent radiomen, who are well versed in the handling of radio traffic, instead of men who can barely receive 5 words per minute, and whose knowledge of radio traffic regulations is practically nil?

I have heard repeated efforts of experienced men on passenger vessels endeavouring to work these planes, and either due to the inefficiency of the receiving apparatus, or the inefficiency of the operator on the plane, extraordinary difficulty was encountered in the exchange of radio traffic. It is a well-known fact among commercial operators that one or both should be improved.

I would advocate the passage of a law, if necessary, to make these planes conform to the radio laws of the United States, and carry adequate radio apparatus, and competent radio operators, similar to the oceangoing steamships.

This would not only ensure the safety of life, but would be the means of saving the U. S. Government, and other governments thousands of dollars which have been spent, and which will continue to be expended in fruitless search for lost planes, which can only be likened to "hunting a needle in a haystack,"

> M. C. Wusox, (Radio Operator) 17 Warren Avenue, Boston, Mass,

(While radio might not ensure the safety of flight in planes incapable of sustaining themselves even temporarily in case of a forced landing, it would lessen the uncertainty which at present exists as to the fate of many aerial expeditions. In France, where commercial flight is more common. radio equipment on passenger planes is required by law.-Ebrron.)

Editor, RADIO NEWS:

I live 150 miles north and a little west of Minneapolis and WCCO is our "local" station. While listening to a national-interest speech, such as the president's address, I have many times turned to WOC,



INVERTORS who derive largest motifies know and heed errialn simple but vital facts before applying for Patents. Our book Patent-Sense gives those facts: sent free. Write LACEY & LACEY, 631 F St. Washington, D. C.

The Last Word in Radio Reception.

ULTRADYNE A.C. COMMANDER

Ultradyne A.C. Commander, an all-electric improved superheterodyne, which has set the whole radio industry agog from coast to coast. If only for its circuit, which employs the original Ultradyne modulation system, this set would hold its own in competition, but it does more than that! It is a thoroughbred in every sense of the word.

Here at last is a circuit that operates on A.C.without hum. It is receptive to the weakest distant signals and brings them in with a volume that is almost uncanny. Coupled with the Ultradyne Power Unit it equals the tone quality of any

Complete construction article appears in March issue of

74 STATIONS IN ONE EVENING

The Ultradyne has an established record for distance which cannot be surpassed. An Ultradyne owner in La Grange, Texas, records reception from 74 stations in one evening— Stations from coast to coast and as far distant as Australia. Nine thousand six hundred miles away!

You can have the utmost in radio enjoyment and a real thrill in the reception of distance if you assemble the Ultra-dyne A.C. Commander or have your local set builder assemble it for you. DEALERS AND SET BUILDERS! Write for our proposition. We are exclusive distributors. Parts not

ULTRADYNE SALES COMPANY 509 South Federal Street, Chicago, Ill.

City..... ...State

NEW BOOKLET

On Audio Amplification, A.C. and D.C. Power Amplifiers, and Specially Developed Receivers—How to Get Better Tone, Volume and Power.

Newest circuits. 30 pages with diagrams and photographs Send 10c. to cover mailing cost

FERRANTI, Inc. 130 West 42nd St. New York, N.Y.

EVERYTHING IN RADIO AT ATTRACTIVE PRICES. SETS OR PARTS. Orders shipped exactly as ordered. Prompt Service. Write for Prices, Mail Order Only. Send Your Address. ALL RADIO COMPANY. 417 North Clark St., Chicson

AMAZING STORIES



Exciting-Original-Scientific Stories. Each one a literary treat. The plausible scientific background adds greatly to the remarkable interest these stories arouse.





Each edition of AMAZING STORIES is full of remarkable tales by some of the world's best-known writers. Stories, not of this world, but of worlds to come. Huge Get your copy now. Read fantasies of the mind. Interesting, exciting, entirely plausible from the scientific arouse surge up in you.

viewpoint. These stories make one of the most amazing collection of literary works of the age.

STORIES by such

M.J.BREUER,M.D.

can be found in the

AMAZING

STORIES.

ଭୁତ

of

Famous Writers as

H. G. WELLS

IULES VERNE

G. P. SERVISS

EARL L. BELL

monthly isues

these stories and feel the excitement which thev



AMERICAN BOSCH MAGNETO CORP. Springfield Massachusetts

Davenport, or WHO, Des Moines, Iowa, 275 miles away, or WOW, Omaha, 335 miles, receiving the speech with equal clearness and volume. The larger Chicago stations, 400 miles, are received consistently with good clarity and volume. WWJ, Detroit, 542 miles, is usually available, and WTAM, Cincinnati, 700 miles, comes in good but not regular; some days it cannot be heard. WJZ and WEAF, 1019 miles, and KDKA, 850 miles, come in consistently, with good clearness and volume, any afternoon when there isn't an electric storm. For some reason we cannot get KOA, Denver, 800 miles, with sufficient volume in the daytime; though at night it roars like a 50,000 watter.

The above is loud-speaker work; I haven't used the headphones on this set since testing after building. It contains only seven tubes with two stages of intermediate ficquency. My advice to Mr. Woodruff would be to either get a *real* superhet or move out of the dead area. Or is Mayor Thompson causing too much disturbance with his campaign against the missing "haiches?"

Seriously speaking, there must be a large absorption of radio waves in a large city like Chicago. I know that interference is terrible compared to out here in the large open spaces. I had my superhet in Minneapolis where it seemed to have equal reach, but a whale of a difference in noise pickup. When the static season comes around, and this seems to be one of its favorite spots, for pleasurable radio entertainment we are confined almost entirely to daylight reception and would certainly be highly disappointed if we could not reach ont.

> M. P. MASSEURE, Aitkin, Minn.

(The number of letters that Mr. Woodruff's inquiry has elicited is enormous, and it is evident that there is much interest in duylight broadcasting. Many stations have been authorized to use much higher power in the hours before 7 p. m., and do so; this compensates to some extent for the greater dissipation of radio waves in sunlit atmosphere. Incidentally, it must be remembered in all comparison of DX records that, while a good receiver has much to do with them, a favorable location is also a most important factor.-EDITOR.)

Use of Long Aerial

Editor, RADIO NEWS:

With reference to Mr. Woodruff's letter, the writer recently installed a "Silver Ghost" receiver at the home of D. G. Haley, Terra Ceia, Florida, and perfect daylight reception was obtained from Fort Worth, Texas, and Shreveport, Louisiana, at noon. During the broadcasting of President Coolidge's speech from Havana, WJZ and WEAF were clearly heard at 10 and 11 in the morning. From 4 p. m. on, programs can be received from all over the United States with great loud-speaker intensity. It must be remembered that the temperature at Terra Ceia runs around 80 in the daytime.

Daylight reception is greatly assisted by the use of an efficient antenna. At Terra Ceia we used a 600-foot single wire, 50 feet high and running east and west. A separate aerial is used for north-and-south rcception.

C. R. LEUTZ, President, C. R. Leutz, Inc., 195 Park Place, Astoria, L. I., N. Y.

A Simple Test Device

WHEN a radio set "goes dead" it is often very difficult to determine the exact location of the trouble; though frequently, however, it will be found that one of the tubes of the set is not receiving plate current. When such trouble is experienced a small magnetic compass may sometimes be used to locate the defective circuit. Turn the set on, place the compass in or near the coil or the transformer which is connected in the *plate* circuit of one of the tubes of the set, and then remove the lube from the socket. If the needle of the compass moves when the tube is removed from the socket, it indicates that a current was flowing in the circuit. The experiment should be repeated with each tube until the faulty circuit is discovered. If should be remembered, however, that in the case of audio by transformers which are shielded grounded cases the compass will be unable to detect the flow of current. It is not suitable, however, for current measurements; a reliable millianmeter should be used for this purpose.

The Community Aerial

 $\mathbf{I}^{\mathrm{N}}_{\mathrm{for}}$ Gothenburg, Sweden, a new solution for the apartment-house aerial problem has been found, by the suspension of a metal ving in the courtyard of a multiple dwelling. It is held tightly by steel wires; and the radio aerials, to the number of fifty, are attached to it-by insulators of course-and to the tops of the neighboring roofs. Each is of the T-type, with a lead-in from the center; and the assembly is said to resemble a gigantic spiderweb. A charge of about \$4.00 is made for connection to this system. Incidentally, it may be said that the European custom of depending upon one station for entertainment, as only the local can be received consistently with crystal sets, prohably makes for less interference than would be thus caused in an American apartment neighborhood.

Radio Term Illustrated



"INTERFERENCE" —The Listener-In, Melbourne,

Indian Program Numbers

FEW American listeners have as yet even imagined that they have received the new high-power stations at Bombay and Calcutta, India. However, the noveltyseekers who are dissatisfied with the monotony of our own programs have a mark to shoot at. We take a few items from a recent schedule of 7BY, Bombay, which appears in a late issue of the *Indian Radio Times*, with which a correspondent kindly supplies us:

"Ustad Hamman Parshad of Jaipur. Vocal music in Purvi, Nat, Behag and Kamod Ragas.

"Walwalkar of Balgandhary Natak Mandali. Dramatic songs,

"Gopaldas Purshottanıdas. Vocal music in Bageshree and Yamankalyan Ragas and a Tumri.

"Balakrishna Buwa, Vocał musie in Rageshree, Latat, and Tilak Kamod Ragas and a Tumri,

"Jayaram Achrekar, Vocal music, "God save the King-Emperor, Close down."

Now Broadcasting Checks

CHESS is said to be the oldest of games —as its partisans conveniently overlook the claims of dice; it is also popularly reputed, among those less familiar with it, to be the slowest-moving. This may account for the fact that it has not been broadcast by radio until lately. The chess fams of St. Louis have shown some more of the spirit which made that city famous; and chess talks are now featured weekly on Tuesday afternoons, by KMOX of that city. We do not understand that there is a popular demand sufficient, as yet, to put them on the chain programs beside bridge.

MODERN MARY Our Mary's bought a Superhet— My WORD, it is a WOW! Most any station it WIL get: 'Twill WALK them in, and how!

Poor Mary sold her lamb and KOW To KICK in with the KOIN, But said, "It's worth it, don't you see, The BCLs to join."

Her erstwhile peaceful cottage Is now the svene of WARS; The family for the locals WAIT, While Mary will WOO Mars.

Father says, "Now KUT it out!" He's a perfect WREC, you know: For WATT little sleep her poor Dad gets Is WHN the batteries are 2LO. —Joseph W. Sine.

> RIGHTEOUS RETRIBUTION The Queen of Hearts, She made some tarts From a radio recipe; The Knave of Hearts, He stole those tarts And suffered perceptibly. --Popular Radio Weekly, Australia. (Original source not given.)

THE SPRATTS Jack Spratt liked Mike and Pat, His wife liked String Quartets; And so betwixt them both, you see, They had two radio sets. -F. P. A., in New York World.

A New and Improved Volume Control for

"AC" Circuits



Centralab Radiohms RN-100 and RX - 025 have been built with exact taper of resistance to give effectual control of v o l u m e smoothly, with-

out jumps and sudden blasts. When the RX-100 is placed across the secondary of one of the R. F. stages it surely and positively controls the volume from a whisper to maximum on all signals —powerful locals notwithstanding. This Radiohm will also control oscillation very effectively. The RX-025 has the exact taper of re-

The RX-025 has the exact taper of resistance for a volume control when placed in the antenna circuit, or across the primary of an R, F, transformer.

In the antenna Cheff, of across the primary of an R. F. transformer. One of these two Radiohms and the Centralab Power Rheostat are essential resistances for all "AC" circuits. They help to maintain the delicate balance of voltages throughout the circuit and in no way affect the balance between plate and filament current, so necessary to maximum efficiency.





Our Superior Proposition will net you \$100 a week, every week in the year. Equipment and car furnished. No capital or experience necessary, homediate profits, Write today for hartheulars, AMERICAN PRODUCTS COM-PANY, 1503 Monunoath, Cincinnati, Ohlo.

Business Opportunities

Inventions Commercialized. Patented or Unpatented. Write Adam Pisher Mfg. Co., 278 Enright St. St. Louis, Mo.

67 Ways to Increase Income. 96-hage book "Spare-time Maney Handbook" contains 67 practical and complete blans to observe spatterline langluess. For everyone who wan's more money. Price only 50e. Constad Combany, Inc., 230 Fifth Avenue, New York.

Amateur Cartoonists: Make money in spare thme with new cartoon selling plan. Write Smith's Service, Wen-atchee, Wash.

Free Book. Starl little Mail Order business. Hadwil, 5A-71 Cortlandt Street, N. Y.

\$5.00—Astounding Chemical Offer—\$5.00. We will shih prejuid autwhere in United States our chemical outfit consisting of 100 expensive pure laboratory chemicals, each or C.O.D., \$5.00. Swimmer ('hemical Company, 1500 St. Marks Ave., Brooklyn, N. Y.

Chemistry

Learn Chemistry at Home. Dr. T. O'Conor Sloanć, noted educator and scientific authority, will teach you. Our home sindy correspondence course fits you to take a position as chemist. Nee our full-page ad on page 1095 of this issue. Chemical Institute of New York, 16 E. 30th Street, New York City.

Correspondence Courses

Used correspondence school courses sold on repurchase hasis. Also rented and exchanged. Money-hack guarantee. Calalog free. (Courses bought), Lee Mountain, Pisgah. Alabama.

Detectives

Detectives Needed Everywhere. Travel. Experience un-necessary. Particulars free. Write, American Detective System, 2190 Droadway, N. Y.

Electricity

Electrie Fun! Seventy stunts, 110 volts, \$1. Cooperco. Campbell. Callf.

For Inventors

Inventions Commercialized. Patented or Unpatented. Write Adam Fisher Mfg. Co., 278 Enright, St. Louis, Mo.

Help Wanted

National Publisher, needs agents, boys and shops to help sell great national magazines. No investment re-mired, Big profits, sparetime work very successful. Write Agency Division, Experimenter Pub. Co., 230 Fifth Avenue, New York.

Miscellaneous

Inventions Commercialized. Patented or Unpatented. Write Adam Fisher Mfg. Co., 278 Enright, St. Louis, Mo.

UNIT CONTRACTOR OF A CONTRACTO

Save Money at Home. You can build many home neces-sities yourself, such as furniture, kitchen utensils, decora-tive material, etc., thus saving many dollars. All construc-tional information on hundreds of things given in 116-page book "How to Make It." Price 50c. Experimenter Pub-lishing Co., Inc., 230 Fifth Avenue, New York.

Send us your portrait and we will enlarge it for \$5.00. Ben Griep, Carthage, Mo.

Transformer forms turned from word. 25c each Send sketch. Mabry Radio Shop, Beaumont, Texas, 1912 Hazel.

Forms to Cast Lead Soldiers, Indians, Marines, Trap-pers, Animals, 151 kinds, Send 10c for illustrated Cata-logue, H. C. Schiereke, 1034 72nd St., Brooklyn, N. Y.

Musical

Play Piano by Ear. A Sound System. Booklet free, Bourber's Harmony Studio, Ottawa 12, Canada.

Old Coins

Statul e statulis a lista da la seconda seconda e s

Old Coins, Large Spring selling catalogue of coins for sale, free. Catologue quoting prices paid for coins. 10e. William Hesslein. 101 K, Tremont St., Boston, Mass. 0.007.010101.00101.00101 1211220001010²0702²0702

Old Money Wanted

\$2 to \$500 each paid for hundreds of Old or Odd Coins. Keep all old money, it may be very valuable. Send 10^o for New Hlustrated Coin Value Book, 4x6. Guaranteed prices. Get posted. We pay Cash. Clarke Coin Company, 14 Street, Leitoy, N. Y.

Old Meney Wanted. Will pay \$100,00 for 1894 Dime, S. Mint; \$50,00 for 1913 Liberty Head Nickel (not Buf-falo). Big premiums paid for all rare coins. Send 4e for Large Coin Folder. May mean much profit to you. Numismatic Co., Dept. 112, Ft. Worth, Tex.

Patent Attorneys

Patents-Send for form "Evidence of Conception" to be signed and witnessed. Form, fee schedule. Information free. Lancaster and Allwine. Registered Patent Attnrneys in Vinited States and Canada. 269 Ouray Bildg., Washington, D. C.

Patents-Send drawing or model of your inteniion for examination and instructions. Advice and booklet free. Highest references. Best results. Promptness assured. Watson E. Coleman, Patent Lawyer, 724 9th Street, N.W., Washington, D. C.

Inventors-Should write for our Guide Book, "How to Obtain a Patent" and Record of Invention Blank, sent free. Send model or sketch of inventions for our Inspec-tion and Instructions Free. Radio, Electrical, Chemical, Mechanical and Trademark Experts. Terms Reasonable. Victor J. Erans & Co., 922 Ninth, Washington, D. C.

Patent Sense-V. tuable book free. See Lacey's ad. page 1181. Lacey & Lacey, 631 F. St., Washington, D. C. Established 1869.

Wanted, ideas. Domand for novel devices, however small. If patentialle, may be the means of your independence. Patents obtained. Sales negotiated. Advice free. IN-YENTOBS SERVICE BUREAU, Bay 1648. Washington.

Radio

Press and public concede it to be the best ever produced, "Radio Theory and Operating," by Mary Texanna Loomis, member Inatiture of Itadio Engineers, Lecturer on radio Loomis Radio College, Throughl text and reference look; 886 pages, 700 illustrations, Price 83.50, postace pair Vised by Radio Schools, Technical Colleges, Universities, bent, of Commerce, Gov't Schools and Engineers. At Doublestres, or sent on receilt check or money order. Laomis Publishing Company, Debt. 15, 405-9th St., Wash-Inston, D. C.

100-volt Edison element rechargeable "B" battery kit \$8,00. 110-volt, \$11,00 IS9-volt, \$14,00, "B" Charger \$2,00. Edison elements with weided connectors 5c pair. Send for Hat. Zieil, \$31 North Randolbh, Piladelphila, Pa.

Transformers 650-742, \$5.50, 550-5, \$4.00, Knock-down primary only \$3.00 Write for lists. Radio Parts Sales Co., Orange, N. J.

Write about our efficient power devices, KIMLEY ELEC-TRU' CO., 411 E. Ferry, huffalo, N. V.

Edison Element "It" Interles, Prices (voluced, 100) volts complete, \$9,50. Trickle Battery Chargers, \$1,57. 6-will 100-annere Batterles, \$5,80. Mators, 1-dur-selower, \$7,00. Hoffman, \$21 North Fifth, Philadelphia, Penn.

To highest bidders-Radlola Superheterodyne and West-ern Electric Power Amplifier. Write, Leslie Frazer, Ivor, Virghia,

Wanted: Men to work with National Radio Service Or-ganization. No selling scheme. Co-operative Radio Doc-tors, Dept. N. 131 Essex St., Salem, Mass.

Salesmen Wanted

A paying position open to representative of character. Take orders shoes, hostery, direct to wearer. Good income. Perunanent. Write now for free book. "Getting Ahead." Tannets shoe Mfg. Co., S74 So. C. St., Boston, Mass.

Scenery to Rent

World's Most Beautiful settings for operas, plays, min-rels. Amelia Grain, Philadelphia.

Song Writers

Sone Writers-Substantial Advance Royaltles are paid on publishalde work. Anyone having original ideas for songs may submit poems for examination and free advice. Waiter Newcomer, 1674 Broadway, New York.

Telegraphy

Telegraphy—Both Morse and Wireless taught thoroughly. Big satarles. Wonderful opportunities. Expenses low. chance to earn part, School established fifty years. Cata-log free. Dodge's Institute, Cour St., Valparaiso, Ind.

Wanted to Buy

Full Value Paid for Old Gold. Jewetry, Watches, Dia-monds, crowns, bridges, dental gold, silver, platinum, gold or silver ore: magneto polnts, old false teeth. Packages re-turned if our offer is not snisfarfory. United States Smelling Works (The Old Relianie). 39 So. State St., Dept. 16, Chicaso. Ill.

Set Constructors' Letters

(Continued from page 1147)

Please be so good as to publish this, and help.

and help. Please he so good as to publish this, as I an almost inundated. Of all these letters which I have received, only a comparatively small number enclosed a stamp for reply. Those who did not I have not an-swered; as I had to draw the line somewhere. I am not a Member of Parliament or a Congress-man, consequently I can not send my correspondence "franked."

Let me say to those asked for information and Let me say to those asked for information and plaus that they will find complete information in RADIO NEWS for October, 1927, or RADIO NEWS Elineprint No. 31. I have **done** considerable ex-perimenting with the hook-up and made certain changes which, in my opinion, are improvements. If any of your readers **desire** this information it may be obtained if they will send a dime for same: no attention will be paid to letters otherwise.

no attention will be paid to letters otherwise. Alany correspondents report great difficulty with distortion. Let me say that I have the same trouble here: while a friend using a Short-Wave receiver about a mile from me gets the Short-Wave broadcasts with perfect clarity. The answer is, evidently, location. There is no remedy known except to move!

except to move! I might mention that 5SW at Chelmsford, Eng-land is now on a regular schedule from 7 to 8 a.m., and 2 to 5 p.m., E. S. T., daily except Saturday and Sunday. The broadcast is by remote control from 2LO at London; announcements are very infrequent. The wavelength is 24 meters, CARL W. BEESE. 146 Market Street, Hamilton, Ontario, Canada.

(Mr. Beese's offer is so plainly not intended for profit, that it is given here: though this de-portment is obviously not a medium for the sole of information and diagrams. The good nature of an experimenter who is willing to impart in-formation as to his results should not be imposed repon by the merely-curious, and correspondents should bear in mind that they may number hun-dreds. Incidentally we may say that the October, 1927, issue of RADIO NEWS has been exhausted, proving the interest of our readers in short-wave reception. For that reason an excellent model, which should prove equally serviceable, is described at length in this issue of RADIO NEWS. If e shall be glad to hear of the results obtained.—EDITOR.)

AN UMBRELLA AERIAL

Editor, RADIO NEWS: 1 am enclosing a picture of my residence, show-ing a type of aerial which can be installed con-veniently where there is no room to string a long wire. I have copied very good distance; received KFI on this aerial. It contains over two hundred feet of wire. (See page 1147 for picture.) IL NOULD II. HURLEY, Box 355, Lake Como, New Jersey. (Under conditions such as those described, it is possible to put up a system of this kind, with considerable signal-collecting capacity, in a small area. The length given, however, is rather too much for selectivity with an ordinary receiver. — Ентов.) Editor, RADIO NEWS:

THAT SIBERIAN TRANSMITTER

THAT SIBERIAN TRANSMITTER Editor, RADIO NEWS: I have heard the announcer of the Siberian short-wave station at Khabarovsk giving call of RSN and his wavelength in English last night. He gave it as 56 meters. This comes in on my set, which is fully shielded, at about 44 on the dials with a 12-turn coil; and KDKA at 54. I have heard G2NB and PCJJ and one Japanese; others too weak.

C. A. BLACKINGTON, Wrangell, Alaska. (A Japanese friend, Mr. N. Miyake, favors us with a news dispatch indicating that "'RFM.' operating on 60.12 meters, has been heard quite distinctly in Japan every night from about 7 to 9 p. m." This is from 5 to 7 a. m., U. S. Eastern Standard Time. It is quite possible that this 20-kilowatt phone station has been rowing the short-wave band.—Entros.)

MORE WORK ON THE PERIDYNE Editor, RADIO NEWS:

In answer to your request for letters from builders of the Peridyne, here is mine, with very many thanks for the guidance in setting it up, as well as the good results. I had great faith in its possibilities of reception and performance, the first time I saw the hook-up, but it has really passed my expectations.

The first night, KFI and other distant stations galore. I was listening to KFI this morning from

12:30 to 1:30, very clear and distinct, no fading— just a little "steaming" one gets occasionally when tuned to a distant station. There is great interest being taken in it locally; but it gave me a thrill when it performed so faithfully at first. I use two aerials: one in the basement of 35 feet, and an outside one of 120 feet (too long). The inside one gives me as far as Kausas City or Lincoln₁ Neb., etc. But the reproduction! It is simply wonderful. LEONARD F. Scorr, 670 Jane Street, Toronto, Canada. simply wonderful. LEONARD F. SCOTT, 670 Jane Street. Toronto, Canada.

I Want To Know

(Continued from page 1152)

There is still another type of electrolytic recti-fier which is very efficient. This consists of a tantalum plate and a lead plate in a solution of sulphuric acid and distilled water; this solution should have approximately the same specific gravity as that used in storage batteries. The advantage of this type of rectifier is that the tantalum does not corrode as quickly as the aluminum, and natu-rally the electrodes last longer. Another advantage is that this type of electrolytic rectifier does not heat up as quickly as the other. heat up as quickly as the other.

AN ACKNOWLEDGMENT

The data which form the answer to ques-tion number 2265, printed in the "I Want to Know" department of RADIO NEWS for February, 1928, seere taken from the Radio Broadcast Laboratory Information Sheets (Nos, 27, 28 and 65), and should have been credited to that source. Acknowledgment is made herewith to Radio Broadcast Maga-vine for the reduchle information zine for the valuable information

Radio News Laboratories

(Continued from page 1149)



AWARDED THE RADIO NEWS LABORA-TORIES CERTIFICATE OF MERIT NO. 2290.

MULTIPLE SPEAKER SWITCH

The demonstrating unit shown is a very practical The demonstrating unit shown is a very practical switching device which allows comparison of various loud speakers and phones. It consists of a small neat wooden box, $4\frac{1}{2} \ge 3\frac{5}{4} \ge 5\frac{4}{6}$ inches, carrying a small bakelite panel $4\frac{1}{2} \ge 3\frac{1}{2}$ inches. On this panel are mounted a switch and five contact points, and in it are drilled six pairs of holes to fit standard phone tips. Five pairs of tips are for the instru-ments to be tested, and one for the output leads



from the receiver. Inside the box, ten springs which make contact with the phone tips are ar-ranged in two rows; those in the first are elec-trically connected together and to the correspond-ing contact springs of the incoming lead. The other five springs are connected, each to a contact point, and the second input lead through its contact spring is connected to the switch. The operation of this is connected to the switch. The operation of this switch is very satisfactory,

AWARDED THE RADIO NEWS LABORA-TORIES CERTIFICATE OF MERIT NO. 2291.



NOW!—Lowest-Priced Quality Tube "B" \$ 18.50 Eliminator - -

Since 1921 Ferbend Products have been famous for outstanding quality and long-life efficiency at lowest prices—prices "Within Reach of All."

The new IIEAVY DUTY "B" Power Unit is no exception. In workmanship, performance, ma-terials and appearance it is the equal of any. We INVITE comparison.

SEE YOUR DEALER, OR SEND DIRECT

Shipment will be made upon re-ceipt of price or C. O. D. Use for thirty days to convince yourself. In that time and purchase price will be refunded. Order today. 10 Days' Trial

Complete, Including Long Life Perfected

85 MIL. TUBE

Delivers up to 180 volts on any set

NO LIQUIDS **OR ACIDS**

FERBEND ELECTRIC COMPANY 425 WEST SUPERIOR STREET CHICAGO, ILL.



For automatically switching on and off your B Eliminator and Charger, or either, and in addition, automatically switching off your Charger when the battery is fully charged.

With the Full Automatic Voltage Relay it is now practical to utilize the advantages of a high rate charger and at the same time control the switching of the charger as well as the B Eliminator with the switch or filament control on the set.

No. 440.....\$7.50

Yaxley Mfg. Co. Dept. N, 9 So. Clinton Street Chicago, Ill.



MERSHON CONDENSERS For full information address Department RN, THE AMMRAD CORPORATION Medford Hillside



The MOST Sensational "B" Eliminator Announcement ever Made!

Now-you can buy as good a "B" Eliminator as is possible to build-at a price that won't cramp your purse. Now-you can enjoy the thrill of Louder, clearer, better reception that a good "B" Eliminator aflords. And you buy the PEERLESS without risk of any kind, for it is backed with a

Year Guarantee 2

Mail Coupon

Direct from factory This astounding offer is without a precedent. Never before has such a value been offered. A "180" volt "B"—a 'B" that will ran your set and a power tube too —and guaranteed for two long years—at the ridiculously low price of only \$12.45.

The PEER-LESS is small, thin and compact. Slides into small spaces, table type cabl-nets, etc. Case is heavy eel, marcon crackle inish, nets complete with cord sparable plug. Uses **85 MIL.TUBE** Delivers

Because of its very low price, don't confuse the PEERLESS with Eliminators which deliver only 90 or 100 volts. Also, don't confuse it with chemical type Eliminators. The PEERLESS uses the standard 85 milliampere gas-hiled Raytheon or Q. R. S. rectifying tube. It is dry. No water, no acids to add. Requires no attention whatever. Delivers pure, hum-free "B" current of $22\frac{1}{2}$ —45—90—135 and 180 volts. Out-put Voltage taps are fixed. No adjustments. Will run any set. Will operate any power tube requiring no more than 180 volts. Will not "motor-boat" on superheterodyne receivers. Operates resistance-coupled audio amplifiers, when other "B" Eliminators fail. In every sense of the word, the PEERLESS provides the finest kind of "B" Eliminator performance - at only \$12.45. Why pay more?

OFFER SPECIAL INTRODUCTORY

This is the first announcement of this new, super-powered, better quality guaranteed "B" Eliminator. Its regular price is \$12.45 without the rectifying tube. But, as a special introductory offer to get thousands of these units out on sets, we will include, for a limited time only, a genuine \$4.50 Q. R. S. 85 Mil. Tube free with your or-der. Think of it! A 180 Volt "B"—a 2 year guarantee—the privilege of trying it 30 days at our risk—and a \$4.50 tube free—all for \$12.45. Mail coupon now.

Read all about this great new, better, tube type "B" Eliminator in the left column of this page. Then order it at once. Hook the PEERLESS up to your set. Compare the reception you get to that which you got before, or to that which you can get from any other "B" Eliminator. Put the PEERLESS to every test you can. Make it drive a "171" power tube, if that's the tube you use in your set. Enjoy this "B" for 30 days. Then—send it back, if you think that any other "B"—at any price is as good. We'll refund your money instantly.



tube foi YEA ch

(Name)

(Street)

(Town)

(State)

3977 Cottage Gro Avenue Chicago, Ill.

Se enclose

Peerles?

Avene no M

DNL

LOOP for SWITCH

The loop of wire shown in back of the transformer are is an extension of one side of the 110 volties. It is provided for the other wire of the construction of of the construction of the construction of the income of the construction of the construction of the income of the construction of the construction of the income of the construction of the construction of the income of the construction of the construction of the income of the construction of the construction of the income of the construction of the construction of the construction of the income of the construction of the construction of the construction of the income of the construction of the construction of the construction of the income of the construction of the income of the construction of the cons

The

Famous ILLINOIS "All-Frequency"

AUDIO TRANSFORMERS

97c Each

LIMITED

OFFER

Supplies Proper Voltages for All 226, 227 and 171 Tubes

ALLINOIS

With this A-C Filament Supply Transformer you can operate a set combining 6 type 226 A-C tubes, 2 type 227 tubes and type 226 A-C tubes, 2 type 227 tubes and elaborate super-heterodyne receiver may be operated with this unit. Each of the three secondaries are center tapped, thereby doing away with the peed for center-tap resistances required by other specific filament transformers. Don't confuse the Thmois A-C Filament Trans-

Only

former with others which supply only five and six tube sets.

Works Perfectly With the New A-C Harnesses

Use The Illinois A-C Filament Fransformer with the new A-C conversion harnesse. Convert any battery operated set into an A-C set in a few minutes time. Enjoy the freedom from "A" battery nuisance which these new harnesses and the Illinois A-C Filament Transformer master possible. Order

makes possible. Order one of these guaranteed units today. Take advantage of the low \$4.87 price.

This is the most amazing radio value ever offered. Think of it! A 4.00 audio transformer—a real "all frequency" unit of the finest musical capability, offered direct from the factory for only 97c. Never before such a bargain opportunity. Thousands have bought them. Sold with a positive guarantee of satisfaction or money back. Supplied in ratios of 1% to 1, 3 to 1 and 5 to 1. Order now. Use coupon.

ALLINOIS TRANSFORMER CO. 223 W. Elm St. Dept. 101 Chicago, Ill.

Filament Supply TRANSFORMER

FOR THIS

Now—at a reasonable cost—you can build a set using A-C tubes, or convert your present set into an A-C set. This new, advanced type, better quality, heavy duty and the very low price of only \$4.87—instead of the \$12.00 price at which it has always sold. You can't buy the equal of this transformer any place for how than \$12.00 or \$14.00. Why pay more than \$12.00 or \$14.00. Why pay



Guaranteed to deliver the correct voltages at the taps as marked—Guaranteed against def ct in material and workmanship—Guaranteed the best performing A-C filament supply transformer built.

Test This Unit at Our Risk

Order it. Connect up to your set. Check the voltages with an accurate voltmeter, if you like. Put it to any test you wish. If you think, for any reason at all, that this unit is not the best A-C filament transformer you can buy, send it back and your money will be refunded to you *instantly*. You are the sole judge. Order NOW. Attach dollar bill to the coupon and mail right now. Pay postman \$3.87 plus few cents postage when the transformer arrives. Then, make your tests. Remember—you take no risk. Guarantee protects you. Clip coupon. Order today.

MAIL THIS COUPON
ILLINOIS TRANSFORMER CO., Dept. 101 223 W. Elm St., Chicago, Ill.
☐ I enclose \$1.00. Pleaseship me one Illinois A-C Filament Trans- former for 226, 227 and 171 standard tubes. I agree to pay postman \$3.87 balance and small postage. It is understood that I can have my money back if not satisfied.
I enclose \$ Ship me the following Illinois Audio Fre-
quency Transformers:
not satisfied.
Name
Street.
TownState

¥.

DOWN