

MAY
1948
35¢

RADIO NEWS

Portable Radios- FOR RENT

(A Profitable Business)

Page 42



RN-125-J27125-118
SIDNEY M BERG
1011 PLEASANT AVE
YAKIMA WASH



ATTEND THE RADIO PARTS SHOW in Chicago May 11-14

AUDIO TRANSFORMERS for [UNIFORM RESPONSE LOW DISTORTION IN 3 FREQUENCY RANGES

*Write for Catalog
showing complete
new stock line*

Full Frequency Range

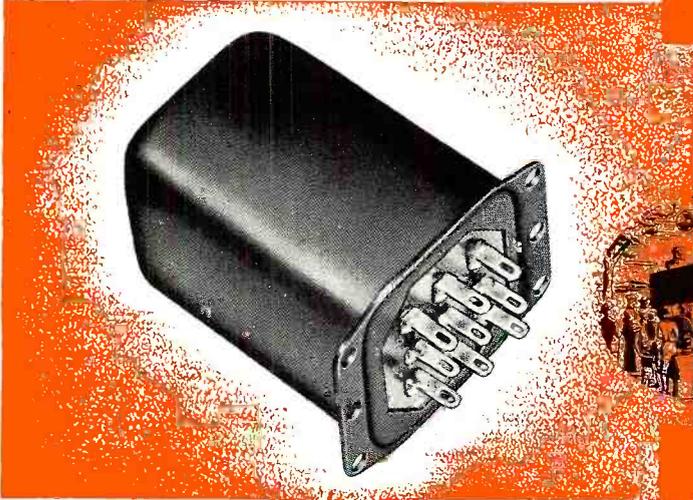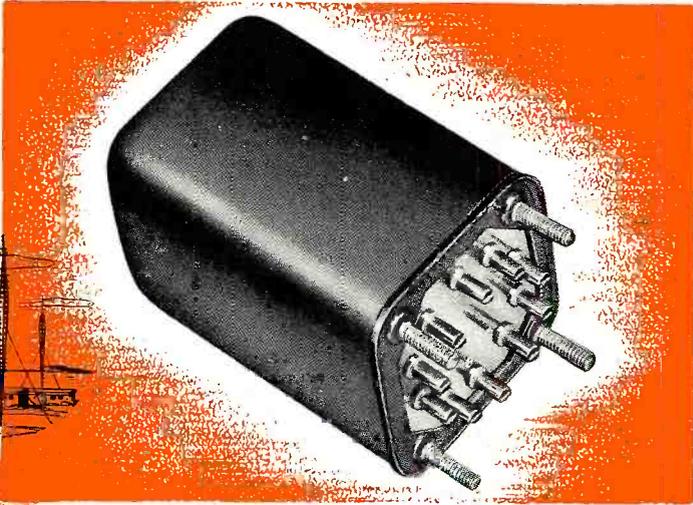30 to 15,000 Cycles, provides uniform response over this entire band with $\pm 1/2$ db up to 10 watts of audio power, within ± 1 db over 10 watts. Standard RMA impedances. Hum balancing coil structures and nickel alloy shielding. Included are Input, Output, Driver, and Modulation Transformers; Modulation Reactors. *Sealed in Steel* construction, stud mounting, with pin-type terminals.




Public Address Range

50 to 10,000 Cycles, frequency response within $\pm 1/2$ db up to 10 watts of power, within ± 1 db over 10 watts, throughout this range. Secondary impedances match 600 and 150-ohm lines, 16, 8 and 4-ohm reproducing systems. Listed are Driver and Output Transformers. *Sealed in Steel* construction, flange mounting, with solder lugs or wire leads.

Communications Range

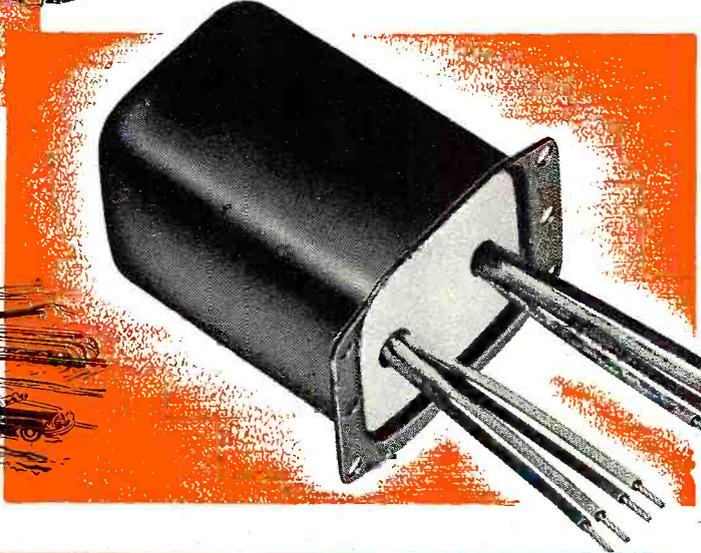200 to 3,500 Cycles, affords response with variations not exceeding ± 1 db over the range of voice frequencies. For use with 600 or 150-ohm lines. Input, Output, Driver and Modulation Transformers offered. *Sealed in Steel* construction, flange mounting, with wire leads or solder lugs.




CHICAGO TRANSFORMER

DIVISION OF ESSEX WIRE CORPORATION

3501 ADDISON STREET • CHICAGO 18, ILLINOIS



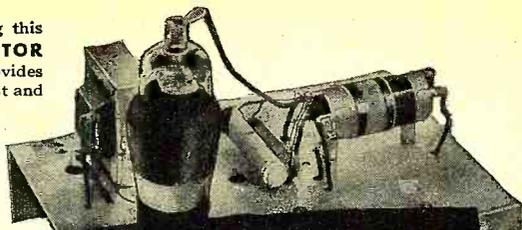Building this
A. M. SIGNAL GENERATOR
gives you valuable experience. Provides
amplitude-modulated signals for test and
experiment purposes. (right)



RADIO SERVICING

pays good money for full-time work. Many others
make \$5, \$10 a week EXTRA fixing Radios in
spare time. (left)

VETERANS

You can get this training right
in your own home under G. I.
Bill. Mail coupon for full details.

Learn RADIO by PRACTICING in Spare Time

with Big Kits of Radio Parts I Send You

Do you want a good-pay job in Radio—or your own
money-making Radio Shop? Mail Coupon for a
FREE Sample Lesson and my FREE 64-page book,
"How to Be a Success in RADIO-Television, Elec-
tronics." See how N.R.I. gives you practical Radio
experience at home—building, testing, repairing
Radios with BIG KITS OF PARTS I send.

**Many Beginners Soon Make Good Extra Money
in Spare Time While Learning**

The day you enroll I start sending EXTRA
MONEY manuals. You LEARN Radio principles
from my easy-to-grasp illustrated lessons—PRAC-
TICE what you learn with parts I send—USE your
knowledge to make EXTRA money fixing neighbors'
Radios in spare time while still learning! From here
it's a short step to your own full-time Radio Shop
or a good Radio Job!

**Future for Trained Men is Bright in Radio,
Television, Electronics**

It's probably easier to get started in Radio now
than ever before because the Radio Repair Business
is booming. Trained Radio Technicians also find
profitable opportunities in Police, Aviation, Marine
Radio, Broadcasting, Radio Manufacturing, Public
Address work. Think of even greater opportunities
as public demand for Television, FM and Electronic
Devices continues to grow. Send for free books now!

Find Out What N.R.I. Can Do For You

Mail Coupon for Sample Lesson and my 64-page book.
Read the details about my Course. Read letters from men
I trained, telling what they are doing, earning. See how
quickly, easily you can get started. No obligation! Just MAIL
COUPON NOW in an envelope or paste it on a penny postal.
J. E. Smith, President, Dept. 8ER, National Radio Institute,
Pioneer Home Study Radio School, Washington 9, D. C.

My Course Includes Training in
TELEVISION * ELECTRONICS
Frequency Modulation



You build this SUPERHETERO-
DYNE CIRCUIT that brings in local
and distant stations. You get practical
experience putting this set
through fascinating tests.

You build this
MEASURING INSTRUMENT
yourself early in the course—use it for practical
Radio work on neighborhood Radios to pick
up EXTRA spare time
money!

**BE A SUCCESS in RADIO
I Will Train You at Home**

Sample Lesson FREE

Gives hints on Receiver Servicing,
Locating Defects, Repair of Loud-
speaker, I.F. Transformer, Gang
Tuner, Condenser, etc. 31 illustrations.
Study it—keep it—use it—without
obligation! Mail Coupon NOW for
your copy!




GETTING ACQUAINTED WITH
RECEIVER SERVICING

**GET BOTH 64 PAGE BOOK
SAMPLE LESSON FREE**

Mr. J. E. SMITH, President, Dept. 8ER
National Radio Institute, Washington 9, D. C.
Mail me FREE, without obligation, Sample Lesson and
64-page book about how to win success in Radio and
Television—Electronics. (No salesman will call.)

Age.....
Name.....
Address.....
City.....Zone.....State.....

Check if Veteran

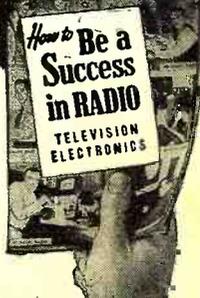

APPROVED FOR TRAINING UNDER GI BILL

Editor
OLIVER READ, W9ET1
 Managing Editor
WM. A. STOCKLIN
 Technical Editor
H. S. RENNE, EX-W8PTS
 Associate Editors
RAY FRANK, W9JU
P. B. HOEFER
E. HITZEL
S. KRUMBACH
 Staff Photographer
ARTHUR E. HAUG
 Staff Artist
R. S. KUPIACK
 —
 Advertising Manager
L. L. OSTEN
 Midwestern Advertising Manager
JOHN A. RONAN, JR.
 —
 Art Director
HERMAN R. BOLLIN

RADIO NEWS

Trade Mark Registered U.S. Patent Office No. 378427

First in radio-electronics

Average Paid Circulation over 148,000

MAY, 1948

CONTENTS

Two-Way Mobile Radio—A New Field for Servicemen.....	Leo G. Sands	39
Portable Radios—For Rent!.....	Max Alth	42
A Crystal Diode Wave Shaper.....	Rufus P. Turner, W1AY	44
A 2-Tube Phono Amplifier.....	Herbert Keroes	45
An Inexpensive FM Tuner.....	Wilbert T. Peterson	46
The Pigeon Catcher.....	Wes Bell, W7QB	48
A Crystal Controlled Signal Generator.....	J. Bann	51
A Television Oscilloscope (Part 2).....	L. H. Van Arsdale, Jr.	52
The Ideal Grid Dip Oscillator.....	James N. Whitaker, W2BFB	56
More Pep for Your FM Pilotuner.....	Malcolm H. Brown	58
The Recording and Reproduction of Sound (Part 15).....	Oliver Read	60
The Inductuner.....		62
Mac's Radio Service Shop.....	John T. Frye	63
Trough Line Tuner for V.H.F.....	Wardell H. Smith	64
A Universal A.F.-R.F. Wattmeter.....	Guy Dexter	66
A Regulated Power Supply.....	D. H. Rogers	68
360 Watt Transmitter for Phone or NBFM.....		
.....R. N. Palmer, W2GSN and H. C. N. Longacre		69
Additional Notes on Recording Amplifier.....		73
Modern Television Receivers (Part 2).....	Milton S. Kiver	74
Voltage, Current, Capacitance, and Resistance Measuring Devices.....		112

DEPARTMENTS

For the Record.....	The Editor	8	What's New in Radio.....	86
Spot Radio News.....	Fred Hamlin	18	Letters from Our Readers.....	104
Within the Industry.....		28	Manufacturers' Literature.....	124
Short-Wave.....	K. R. Boord	72	Technical Books.....	182
New Receivers.....		188		



COPYRIGHT 1948
 ZIFF-DAVIS PUBLISHING COMPANY
 185 North Wabash Ave., Chicago 1, Ill.
 VOLUME 39 • NUMBER 5



Member
 Audit Bureau of
 Circulations

RADIO NEWS is published monthly by the Ziff-Davis Publishing Company, 185 N. Wabash Ave., Chicago 1, Ill. Subscription Rates: in U. S. and Canada \$4.00 (12 issues), single copies 35 cents; in Mexico, South and Central America, and U.S. Possessions, \$4.00 (12 issues); in British Empire, \$5.00 (12 issues)—all other foreign countries \$5.00 (12 issues). Subscribers should allow at least 2 weeks for change of address. All communications about subscriptions should be addressed to: Director of Circulation, 185 N. Wabash Ave., Chicago 1, Ill. Entered as second class matter March 9, 1938, at the Post Office, Chicago, Illinois, under the Act of March 3, 1879. Entered as second class matter at the Post Office Dept., Ottawa, Canada. Contributors should retain a copy of contributions and include return postage. Contributions will be handled with reasonable care but this magazine assumes no responsibility for their safety. Accepted material is subject to whatever revisions and by-line changes that are necessary. Payment made at our current rates, covers all authors', contributors', or contestants' rights, title, and interest in and to accepted material, including photographs and drawings.



COVER PHOTO: The girl on the cover is Diane VanDusen, one of the famous Aqua-maids of Florida Cypress Gardens. Her father is R. H. VanDusen, President of Southern Corporation, Morris F. Taylor Company's manufacturers' representatives in the southeastern states. (Photo by Gordon Lord)

Chairman of the Board and Publisher
WILLIAM B. ZIFF

President
B. G. DAVIS

Secretary-Treasurer
ARTHUR T. PULLEN

Vice-Presidents
GEORGE BERNER
 Advertising and Sales Director

MICHAEL H. FROELICH
 Dir. Eastern Div.

H. J. MORGANROTH
 Production Director

H. G. STRONG
 Circulation Director

BRANCH OFFICES
 NEW YORK (1)

Empire State Bldg., WI 7-0400

LOS ANGELES (14)
 815 S. Hill St., TUcker 9213
 Manager, **WILLIAM L. PINNEY**

TORONTO

21 King Street, East

ASSOCIATED WITH
 Ziff Davis, Ltd., Grampians Bldg.
 Western Gate, London, England




What hallicrafters **MODEL HT-18** variable master oscillator does for improved amateur transmission

The HT-18 is called by hams who have used it the most efficient, flexible piece of gear to be developed in recent years. Easily added to your present transmitter, it brings it right up to date. Narrow band FM and calibrated 5 band V.F.O. complete in one compact cabinet with all coils and power supply concentrates and simplifies your entire operation. Put your transmitter anywhere, place the neat, highly functional HT-18 on the operating table and you're in action. Narrow band FM quality like you've never heard before. The HT-18 places your signal *anywhere in the band* with excellent stability. Go to your nearest Hallicrafters distributor today for a demonstration and complete technical data on this splendid instrument **\$110⁰⁰**

Amateur Net

Copyright 1948, The Hallicrafters Co.

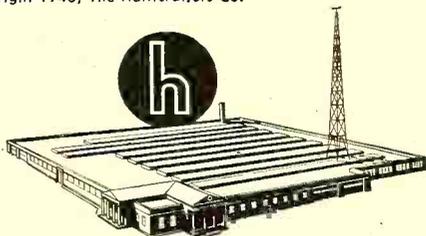

EASY, PRECISE, FLEXIBLE OPERATION FOR THESE REASONS:

- Converts any good CW transmitter to a high quality phone transmitter.
- Eliminates 90% of broadcast interference.
- Puts your signal *anywhere in the band* with stability comparable to crystal controlled transmitter.
- Gives you direct calibration, direct output on all bands 80, 40, 20, 15, 11, 10.
- Simplifies operation of entire station. Puts both frequency selection and power control at your finger tips. 72 ohm output. Remote power control terminals.

hallicrafters RADIO

THE HALLICRAFTERS CO.

4401 W. Fifth Ave., Chicago 24, Illinois

MANUFACTURERS OF RADIO AND ELECTRONIC EQUIPMENT

LISTEN FOR THE *Gatti* - hallicrafters expedition

Hallicrafters mobile, radio-equipped expedition now operating via short wave from the Mountains of the Moon, Africa. Listen for these call letters:

VQ5-GHE

VQ3-HEG

VQ4-EHG

VQ5-HEG


Visit your distributor for maps, itinerary, schedules, other details.

SNC

transformers are

"TOPS" in Quality

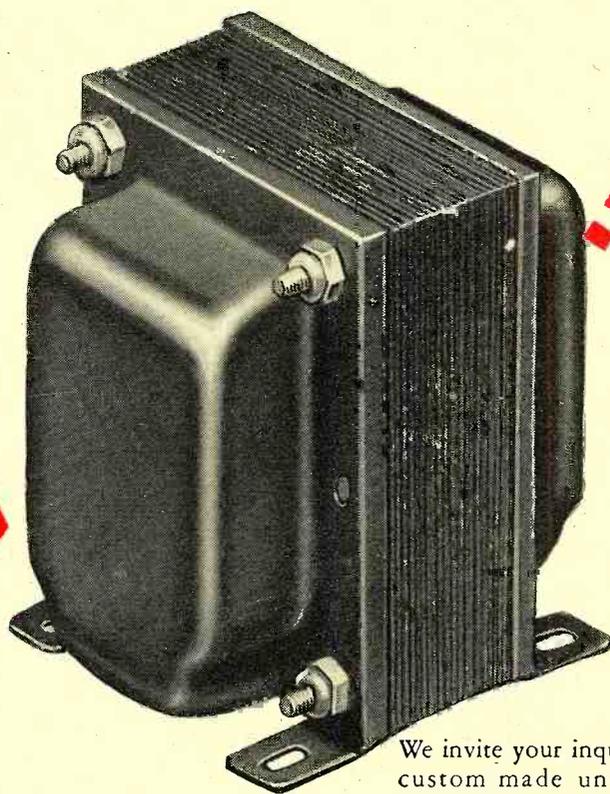Skillful engineering, highest quality materials, latest production techniques, and careful workmanship are combined in SNC transformers to give you perfect installations . . . a minimum of rejects . . . *outstanding* performance!



We invite your inquiry on custom made units for industrial application.



Get this easy-to-read catalog from your distributor — or write to factory direct.

SNC MANUFACTURING CO., INC.

Quality Transformers

WEST LAKE AVE. NEAR LEHIGH

GLENVIEW, ILLINOIS

RADIO NEWS

I'll Send You 8 Big Kits of Training Equipment including


TWO-BAND 6 TUBE SUPER RECEIVER AND 16 RANGE METER SET-UP
for Testing

Learn Fast... Earn Fast
HOME TRAINING
Planned For Your Needs
You Build All These
TESTERS... and MORE!

I give you a fine, moving-coil type Meter Instrument on Jewel Bearings—with parts for a complete Analyzer Circuit Continuity Tester. You learn how to check and correct Receiver defects with professional speed and accuracy.

Practice Does It!
Soldering, wiring, connecting Radio Parts...

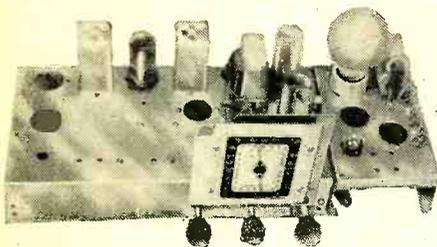
... building circuits with your own hands — you can't beat this method of learning. When you construct this Rectifier and Filter Resistor and Condenser Tester, etc., you get a really practical slant on Radio that leads to a money-making future.




Building this Signal Generator and multi-purpose Tester will give you the kind of valuable experience and practice that is so important as a foundation for making good money in Radio. It makes a breeze out of fixing Radios, and you don't have to spend money on ready-made Equipment.

VETERANS

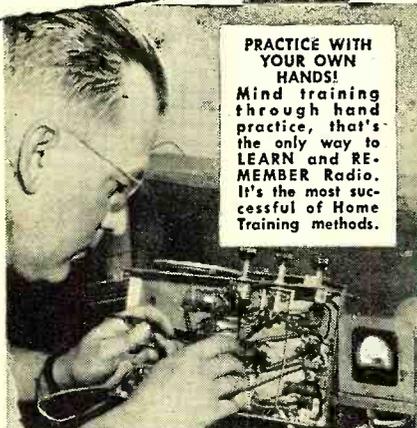APPROVED FOR G.I. TRAINING UNDER PUBLIC LAWS 16 AND 346.



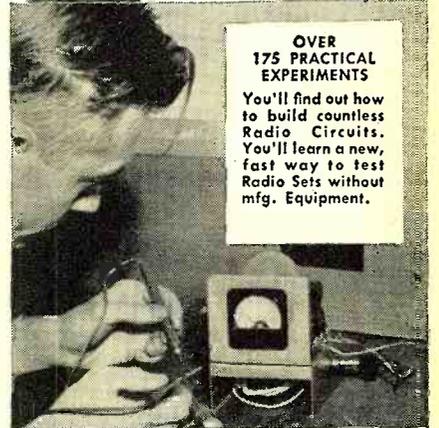PRACTICE WITH YOUR OWN HANDS!
Mind training through hand practice, that's the only way to LEARN and REMEMBER Radio. It's the most successful of Home Training methods.



OVER 175 PRACTICAL EXPERIMENTS
You'll find out how to build countless Radio Circuits. You'll learn a new, fast way to test Radio Sets without mfg. Equipment.

LOW COST HOME RADIO TRAINING! Easy Monthly Payments!

The answer to the PRACTICAL results, I show my Students lies in the way I train you. Not books and lessons alone. But "sight demonstrations" with real Radio Parts worked out with your own hands. You LEARN! You UNDERSTAND! You REMEMBER! Pay special attention to the quality and completeness of the Equipment which comes with the Sprayberry Course. You get a big 6 Tube Super Receiver and a 16 Range Meter Set-up for testing. When I put you to work with the 8 big Kits of Radio Parts I send you, you'll really LEARN Radio and learn it RIGHT! You'll get the practical experience

and pre-conditioning you need to be useful in Radio, and that's what it takes to make money. You don't need any previous experience. The Sprayberry Course starts right at the beginning of Radio — you can't get lost!

Soon after you begin your Sprayberry Course, I'll send you my sensational BUSINESS BUILDERS. You'll learn how to get and do neighborhood Radio repair jobs for nice profits and rich experience. With the kind of Training I give you, you will be able to set up your own Business, or step into a good-pay job in Radio, Television, FM, Radar, Industrial Electronics. Don't waste time! Make your start NOW!

MAIL COUPON FOR THESE 2 BOOKS!



"How to Read Radio Diagrams and Symbols" and "How to Make Money in Radio, Electronics and Television." Immense, practical value to you — and they're yours FREE!

SPRAYBERRY ACADEMY OF RADIO
F. L. Sprayberry, President
2558 Sprayberry Building, Pueblo, Colorado
Please rush my FREE copies of "How to MAKE MONEY in RADIO, ELECTRONICS and TELEVISION" and "How to READ RADIO DIAGRAMS and SYMBOLS."


Name _____ Age _____

Address _____


City _____ State _____

(Mail in envelope or paste on penny postcard)

VEE-D-X means VIDEO DISTANCE

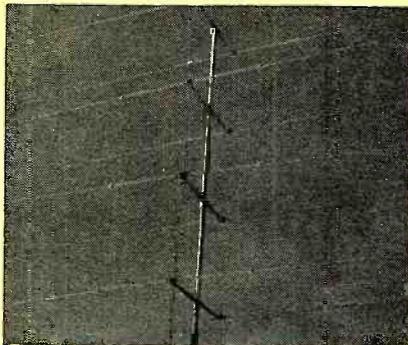


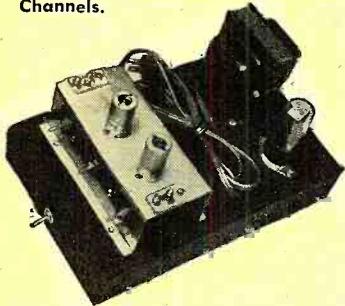- Highest Gain of any Antenna on Market.
- Sharply Directional assuring maximum desired signal.
- Weighs less than 25 pounds—sturdily built of Duraluminum.
- Completely equipped with Matching Stubs.
- Broad Band—Model R.D.-6; for Channels 1 to 6; Model R.D. 13, for All 13 Channels.



2-Stage Pre-Selector Model R. C.-2

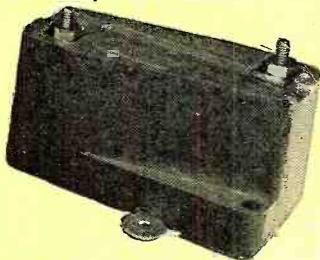- Guaranteed 5 megacycle band width. (assures quality pictures)
- Gain 40 d. b.
- Matches Impedence. of Transmission line to input of Receiver.



Lightening Arrester High Frequency—Low Loss

- Designed Especially for Video, and F. M.
- Unnecessary to cut Transmission line for installation.
- Unnecessary to change spacing of Transmission line.
- Does not vary impedance.
- High dielectric, low loss Plastic material.

"THERE'S MORE VISION IN TELEVISION"

See your nearest Jobber or write direct
La Pointe-Plascomold Corp.
UNIONVILLE, CONNECTICUT

For the RECORD.

BY THE EDITOR

THE AM-FM DILEMMA

THE insistent demand by the public for FM receivers and tuners at low cost has resulted in a flood of low-priced units that leave much to be desired in the way of fidelity and performance. As a matter of fact, we find 5 and 6 tube, so-called FM receivers and 2 tube tuners being sold as representing the ultimate in FM broadcast reception. For the most part these little sets include speakers averaging six inches in diameter. Many models currently being offered will certainly do little to increase the popularity of FM. In fact, from many that we have heard, they certainly should discourage many a prospective purchaser from buying one when they hear the mediocre tone quality and when they compare the audio response to inexpensive AM sets in their possession. For several years the public has been sold on the merits of FM as a cure-all for the problem of securing high fidelity and static free reception.

In order to satisfy the requirements of true high fidelity and to take full advantage of the benefits of true FM, it is essential that a receiver have an excellent audio system (including a good speaker). How the manufacturers expect to justify the use of 69 cent five and six inch speakers in FM receivers (200-2500 c.p.s.) is not clear. The use of single beam power output stages, employing such tubes as 6V6, 50B5, etc. with as much as 10% distortion, will certainly not contribute to the listening pleasure promised for FM.

A few manufacturers have produced FM tuners without audio. They recommend that these units be fed into quality amplifier and speaker systems. That's a step in the right direction.

The noise suppression qualities of FM are lost in many receivers due to the use of trick methods of demodulation. For best results it is essential that the receiver have a high gain, sufficient to give adequate suppression action. This gain is needed regardless of the method of detection used. Now let's take a look at the frequency response capabilities of various types of receivers. The small table sets selling between \$15.00 and \$30.00 normally have a range from 200 to 2500 cycles-per-second. Larger table sets have a range of from 150 to 3500 c.p.s., consoles from 100 to 5000 c.p.s., and high fidelity consoles from 50 to 10,000 c.p.s. Does it not stand to reason then, if we are to enjoy the full benefits

from FM transmissions we must have adequate consoles to house the equipment? Furthermore, for decent audio range we cannot get by with small diameter loud speakers with their many limitations *even if these speakers are installed in consoles.*

FM stations are looming on the horizon every day and production of FM sets continues at a high rate. The public is fully aware by now that satisfactory daytime AM reception is limited to the city dweller. Interference at night becomes more and more of a serious problem as new AM stations go on the air. At the present time there are about 2000 AM stations in operation. That's more than two times the number on the air on V-E Day. In addition there are more than 350 applications before the FCC for new AM stations. As new stations are placed in operation the increased interference problem becomes more and more acute. Reception, to all except the city dwellers, becomes progressively worse. As a result AM coverage in service areas, in most cases, has been reduced in alarming proportions. As a further complication, Cuba and Mexico are asking for more and more clear channel frequencies at the expense of those now used by U. S. A. stations. Cuba has asked for 12 frequencies for clear channel operation. This all adds to our present dilemma.

The behavior of FM signals do not recognize the difference between day and night time operations. On a watt-for-watt basis, FM will far outperform the coverage of AM stations as far as static-free, fade-free and interference-free primary service is concerned.


About 30 FM stations will operate with powers in excess of 100,000 watts, and a few of these will probably use close to 500,000 watts. Many millions of dollars are being spent for the proper installation of FM stations capable of high-fidelity transmission — but what about the receiving end? It is high time that we recognize and take full advantage of the superior capabilities of FM by selling *quality*—not just a "static eliminator."

If the trend towards 5 tube sets and 5 inch speakers continues the full benefits of FM will be of little value. It won't make much difference whether or not the signal wiggles back and forth or up and down. After all—it's what comes out of the speaker that counts!...O.R.

RADIO NEWS

Get Your ALLIED Catalog Now

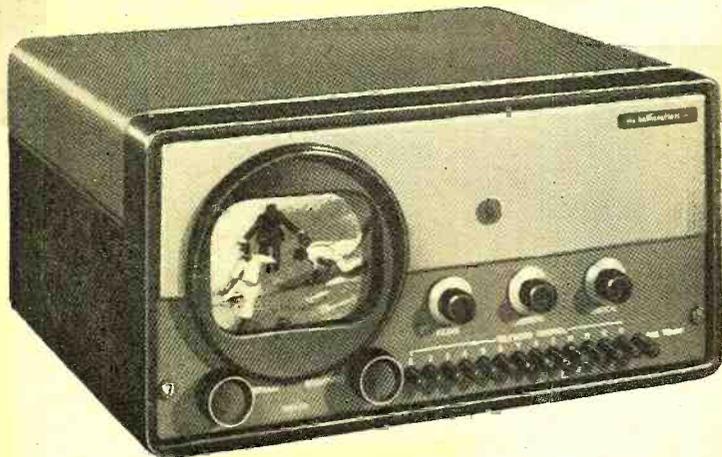
172 Value-Packed Pages Including Everything New in Radio . . .



FIRST WITH TELEVISION by hallicrafters Amazing Performance at Low, Low Cost!

Fully described in ALLIED'S latest Catalog—the new Hallicrafters Model T-54 Television Receiver for use in all television areas! Here's perfected, clear, sharp, bright Television at low, low cost. The 7" diameter viewing tube provides a brilliant picture 5¾" long by 4" high—a full 23 square-inch picture area. Push-button tuning is factory pre-set to the 13 television channels. Receive the station in your area just by pressing the proper button. Easy to operate! Combined power switch and contrast control turns set on and regulates picture for best definition; brightness control adjusts for best viewing brilliancy; horizontal and vertical controls frame picture properly; fine tuning with 1 mc range provides exact tuning of sound channel. FM audio channel circuit eliminates man-made static. Has built-in 4" x 6" oval PM speaker; plenty of audio output and exceptional tonal fidelity. Distinctively styled, completely self-contained in furniture steel cabinet finished in rich silver-gray with airodized top; handsome control panel in two-tone gray. Overall size, 20½" long, 9½" high, 16" deep. For 105-125 volts, 50-60 cycles AC. Complete with tubes and operating instructions. Underwriters' approved. Shpg. wt., 45 lbs.

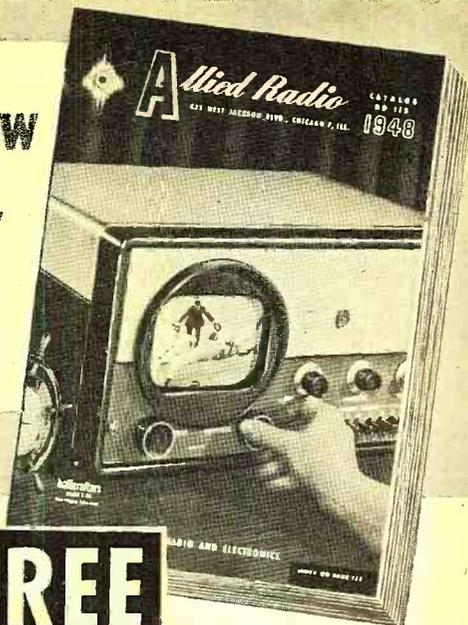NET, f. o. b. Chicago, Only **\$169⁵⁰**
Easy Payment Terms: \$33.90 down, \$11.98 monthly for 12 months.



FREE

172-Page Buying Guide


MORE THAN 10,000 ITEMS

Everything in radio for everyone in radio! Complete lines of all leading makes of parts and equipment—all from one great, centralized source. For newest developments and best values, see your ALLIED Catalog.



TELEVISION & HOME RADIOS

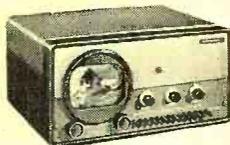A special selection of outstanding models—table radios, consoles, combinations, FM-AM—plus new Television, offered first by ALLIED at real savings. Hand-picked models—the choice of experts!



AMATEUR STATION GEAR

Here's heaven for the Ham! You'll find everything you need for your shack in the new ALLIED Catalog. See all the latest releases in receivers, transmitters, parts, station equipment—biggest Ham listings in radio!



NEW P. A. EQUIPMENT

Packaged, ready-to-use Sound Systems; amplifiers guaranteed for one full year; everything in speakers, microphones, P. A. accessories, intercom and recording equipment—leading headquarters for Soundmen!



Send for Radio's
Leading Buying Guide

FREE



THE WORLD'S
LARGEST
RADIO
SUPPLY
HOUSE . . .

★ **ALLIED RADIO**
*Everything in Radio
and Electronics*

ALLIED RADIO CORP.
833 W. Jackson Blvd., Dept. 1-E-8
Chicago 7, Illinois

- Send FREE New ALLIED Catalog.
- Ship Hallicrafters' T-54 Television Receiver.
 - Enclosed \$..... Full Payment
 - Part Payment (Balance C.O.D.)
- Send ALLIED Easy Payment Plan details and order blank.

Name.....
Address.....
City..... Zone..... State.....

THORDARSON



**CONTINUOUS
DEVELOPMENT
ASSURES**

Lasting Leadership

Progress is dependent upon advancement and development. Here at Thordarson, we are never satisfied with a "status quo" position. That is why we have a staff of highly qualified engineers who are pioneering improvements in power circuits involving transformers . . . for the amateur . . . as well as highly specialized industry. As a result, our "in stock" list of transformers are transformers that incorporate every new development. This creative thinking by Thordarson engineers eliminates costly, suppositional thoughts in the resolution of new products. Let Thordarson engineers translate your needs into practical, workable shop specifications that make development jobs easier for all industry.

Shown on this page is a typical variable power supply . . . Write for our latest catalog showing a variety of matched components.

POWER SUPPLY EMPLOYING THYRISTORS FOR VARIABLE DC OUTPUT AND RECTIFIER GRID KEYING. SEE TABLE BELOW FOR CIRCUIT VALUES FOR DC RANGES. OMIT T₃, R₁ AND 250K TO ELIMINATE KEYING FEATURE.

T-22R50 SPECIAL PHASE SHIFT TRANSFORMER -- PRI. 117V.

D. C. Voltage and Current	T ₁	T ₂	T ₃	CH ₁	V ₁	C ₁	R ₁
50- 400V 200MA	T-21P89	T-21F10		T-20C54	2050	8 Mfd.	20K
500-1500V 500MA	T-21P79	T-21F02	T-21F10	T-20C57	TT17 or FG17	4 Mfd.	50K
1500-2500V 500MA	T-21P75	T-21F20	T-21F10	T-20C57	873	4 Mfd.	75K

The variable power supplies shown in the circuit are ideal for amateur phone and CW transmitters as well as in laboratory applications where a variable source of D. C. voltage is desired without resorting to expensive methods of primary voltage control. There are a variety of applications of this circuit. For further details write directly to Thordarson.



**The New Thordarson
Catalog Is Now Available,
Send For Your
Copy Today.**

THORDARSON

Manufacturing Quality Electrical Equipment Since 1895
500 WEST HURON CHICAGO 10, ILLINOIS
A Division of Maguire Industries
Export - Scheel International Inc.

**FOR THE
NEWEST IN
TV AERIALS**

**Watch
WARD**

**GREATER TV
EFFICIENCY WITH
NEW "HIGH-LOW"
ARRAY BY WARD**

All major parts pre-assembled.
Saves costly installation time.

Here's another "first" by Ward in the rapidly expanding field of television reception. Advanced Ward design and engineering makes receivers work to their highest degree of efficiency.

That's the opinion of satisfied set owners, service installers, and major set manufacturers, who are all directly interested in the improved performance of television.

As a result of months of exhaustive scientific research and field testing, Ward now makes available a high band TV array which can be stacked above the standard television elements, and independently oriented! Also new is a kit for stacking two of Wards finest television assemblies into a two-bay array for a greater gain than ever before.

Sure, there have been other multiple antennas, but none with the scientifically measured spacing and complete adaptability of the new Ward models. You can see the difference yourself on the television screen when a "Magic Wand" aerial is connected to the set.

Send in coupon today for free copy of new Ward catalog.

ORIENTING AND GAIN. Each bay tilts in any plane, can be oriented in any direction to give sharpest focus possible. Eliminates awkward or tricky installations. Permits hairline adjustments for utmost gain on both the high and low band stations.

ADAPTABILITY. Ease of combination of assemblies in basic kits makes "Magic Wand" Aerials more adaptable than ever to the varying requirements of each installation. This superior flexibility means a highly specialized Ward TV aerial for each purpose, with fewer models in stock, no obsolescence, and greater profits! Write today for free catalog!

Please send me free copy of your new catalog showing latest developments in television aerials.
NAME _____
ADDRESS _____
STATE _____ CITY _____
IF JOBBER OR DEALER
COMPANY NAME _____


**THE WARD PRODUCTS CORPORATION
DIVISION OF THE GABRIEL COMPANY**

1524 E. 45th STREET, CLEVELAND 3, OHIO
IN CANADA: ATLAS RADIO CORP. LTD., TORONTO, CANADA

WORLD'S LARGEST PRODUCER OF AERIALS FOR CAR AND HOME

WARD
Magic Wand
AERIALS

Announcing New Addition

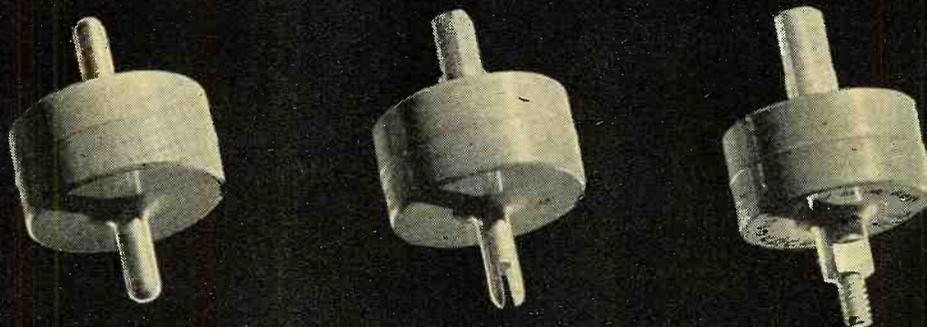

THREE TYPES OF TERMINALS FOR FLEXIBILITY, CONVENIENCE

TV1-501 AND TV1-502 ROD TYPES: .160" diameter rod type terminals. For use with fuse or clip-type connections. Terminals are solid brass, silverplated and soldered directly to electrodes.

TV2-501 SLOT-AND-THREAD TYPE: .160" diameter with $\frac{1}{16}$ " x $\frac{3}{16}$ " slot in one terminal. Other terminal tapped 6-32, $\frac{3}{16}$ " deep for "twinning" or convenient chassis mounting.

TV3-501 DUO-THREAD TYPE: One terminal tapped 6-32, $\frac{3}{16}$ " deep full threads. Other terminal, 6-32, male thread $\frac{1}{4}$ " length. Designed for convenient series or tapped series connections.

Centralab Unit	User	Mfg. Part Number
TV1-501 List Price \$1.75	Andrea Radio Corp.	HCH2701
	Allen B. DuMont	3-14-41
	Philco	30-1299
	RCA-Victor	M-940173-1
TV2-501 List Price \$1.75	Stromberg-Carlson	110504
	Crosley	W137477-1
	Admiral	65A11-1
	Fada	17.41
TV3-501 List Price \$1.75	Garod	N6917
	Sonora	21A90013
	Telequip Radio	BB106
TV1-502 List Price \$2.25	Motorola	
	Cleervue Telev. Consolidated Telev. Lectrovision Inc.	3-1488
	Allen B. DuMont	

LOOK FOR "HI-VO-KAPS" ON CURRENT TV SETS!

Already in use on television equipment of leading manufacturers (see table), *Hi-Vo-Kaps* were designed and developed by Centralab to meet the stated requirements of television project engineers. Save this handy table to check users, prices and parts numbers.



Cutaway view shows integral ceramic construction

Solid brass terminals, soldered directly to electrodes.

Metallic silver electrodes fired directly to high dielectric constant Ceramic-X.

Low loss, mineral filled phenolic resin.

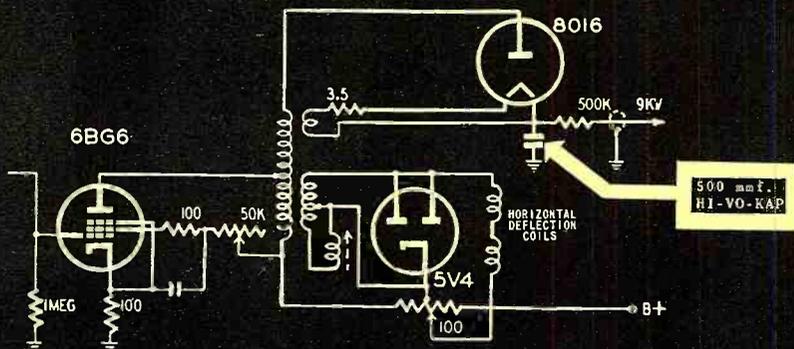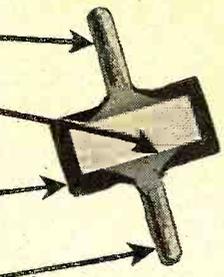Three terminal types for strong, fast connections.



New Centralab *Hi-Vo-Kaps* made with Ceramic-X, combine high voltage and small size for television and high voltage applications. Diameter 1.000", Length .510".

Circuit diagram of simplified typical television power supply shows where and how *Hi-Vo-Kaps* fit into this high voltage by-pass application. Ceramic construction of *Hi-Vo-Kaps* assures long life, dependable performance under all types of operating conditions. The word *Hi-Vo-Kaps* is a registered trade mark.

MODEL VH-24
List Price, \$74.50

MODEL VH-20
List Price, \$63.00

MODEL VH-15
List Price, \$47.00

MODEL VH-91
List Price, \$32.50

Listen 4 New
Jensen
*Hypex**
PROJECTORS

AFTER months in the laboratory and a long and costly tooling program, this dominant new line of HYPEx Projectors is now ready. In their design, JENSEN engineers started with complete recognition of the shortcomings of all equipment of this kind and then added their own high concepts of performance and convenience requirements. The result is a striking new high in every detail of design and performance, and a new low in price.

Generous use of such materials as stainless steel and other corrosion-resistant materials, plus elaborate treatment of necessary steel parts, insures against weather exposure. Mounting brackets using clutch-type, heavy trunnion mountings (on all except VH-91), solve finally the problem of adjustment and positive locking into position.

Weatherproof terminal boxes provide a long needed feature in equipment of this kind. The completely new driver unit with molded plastic diaphragm is entirely enclosed within the one-piece rigid horn. And, of course, the recognized superiority of the Hypex formula is employed in the reflexed horn design.


The sound industry has long deserved equipment of this kind. Now it is here and at prices right back to prewar levels.

Write or wire for complete information, we haven't space here to give more than an outline of the features and performance ability of these outstandingly new products.

JENSEN MANUFACTURING COMPANY
6617 S. LARAMIE AVE., CHICAGO 38

In Canada: Copper Wire Products, Ltd., 11 King St., W., Toronto

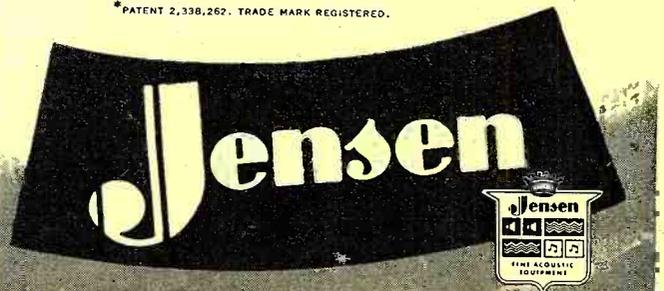*PATENT 2,338,262. TRADE MARK REGISTERED.




RADIO NEWS

TELEVISION ASSEMBLY CO.

INTRODUCES THE

Champion Models
with

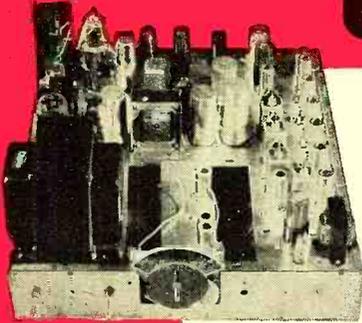


DUMONT INPUTUNER

The Dumont Inputuner tunes continuously from 44 to 216 megacycles without a break, covers all 13 channels as well as FM, amateur, and aviation channels. For ease and convenience of operation no band switching of any kind is required when tuning from channel to channel with the inputuner system. Just one simple operation to reach any desired station.

Assemble the Champion model of your choice, 10" flat surface screen picture, 51 sq. in. picture, 12" screen picture with 75 sq. in. picture or the 15" screen picture with 120 sq. in. picture.

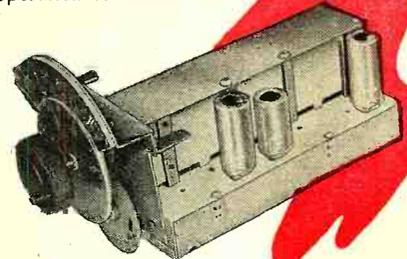All Champion Models are complete with all tubes and components including the CR Tube.



10" FLAT SURFACE

\$ 273.10

DEALERS NET

12" SCREEN PICTURE

\$ 303.10

DEALERS NET


15" SCREEN PICTURE,

\$ 393.10

DEALERS NET


Standard Models

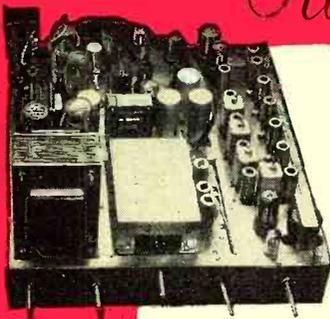NOW AVAILABLE WITH
THE STANDARD MODELS—
FM RADIO AT A SLIGHT
ADDITIONAL COST OF
\$7.95.



All Television Assemblies are complete and include: 29 RCA Tubes plus CR Tube—Heavy duty RCA 6.8 oz. slug PM speaker—Specially designed dipole antenna, with 60 ft. lead in—complete pictorial charts for placement of components and schematic diagrams for wiring supplied with assembly.

Superior performance is obtained with a new IF Video & Sound IF Strip (Pat. Pend.) aligned, wired, pretuned, tubed and tested. All circuits are contained on one chassis ready to use with the front end unit supplied. This front end will handle 13 channels and is aligned and tested, mounted on a separate chassis. Merely connect B plus filament and output IF leads to the television chassis. It is not necessary to make any RF alignments. These units utilize a clipper circuit which filters out ignition noises.

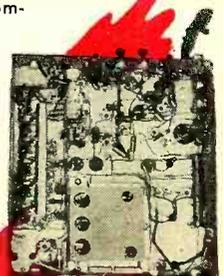

10" FLAT SURFACE

\$ 229.50

DEALERS NET

12" SCREEN PICTURE

\$ 259.50

DEALERS NET

15" SCREEN PICTURE

\$ 349.50

DEALERS NET

Guaranteed

All Television Assemblies are guaranteed to operate to your satisfaction when simple directions are followed.

IN CHICAGO MAY 11TH-14TH
SEE OUR EXHIBIT AT THE CONGRESS HOTEL

TERMS: 10%
DEPOSIT WITH
ORDER. BALANCE
EXPRESS COLLECT.

TELEVISION ASSEMBLY CO.

540 BUSHWICK AVE.
BROOKLYN 6, N. Y.


OHMITE plate chokes

"FREQUENCY-RATED"


for easy selection and top performance

● Now, for the first time, you can select a plate choke for a particular frequency and know that it will give excellent performance at this frequency. The Ohmite line of plate chokes are "frequency-rated"—their frequency characteristics have been accurately predetermined. The chart below gives the operating frequency range for each of the seven sizes.

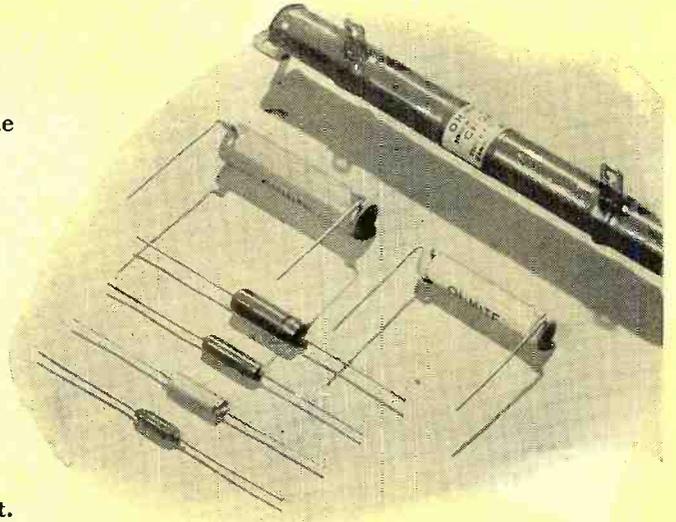Ohmite single-layer wound, r.f. plate chokes cover the entire frequency range of 3 to 520 megacycles. These chokes are wound on low power factor plastic or steatite cores, and are insulated and protected by a moistureproof coating. All chokes are rated 1000 ma except the Z-14 and Z-28, which are rated at 600 ma. Further information will be supplied upon request.



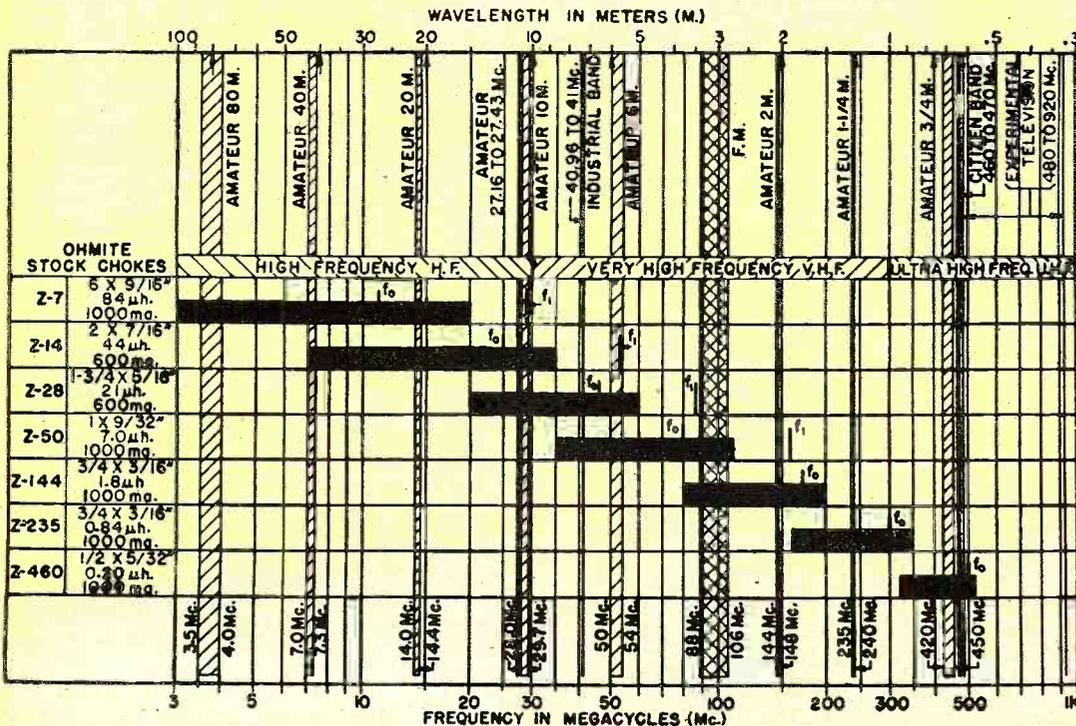RECOMMENDED OPERATING FREQUENCY RANGES OF OHMITE R. F. PLATE CHOKES



WRITE FOR
PLATE CHOKES
BULLETIN
No. 133.

OHMITE
MANUFACTURING
COMPANY

4884 Flournoy St.,
Chicago 44, Ill.

See the
Ohmite Display
Booth No. 43
Radio Parts Show
Stevens Hotel
Chicago
May 11-14





Be Right with...

OHMITE



RHEOSTATS • RESISTORS • TAP SWITCHES • CHOKES

RADIO NEWS

only **STANCOR**
gives you all this...

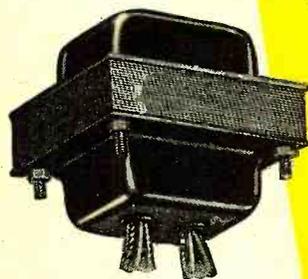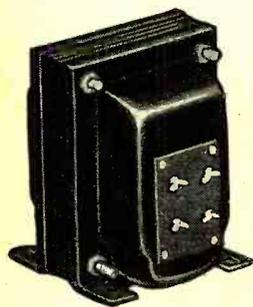

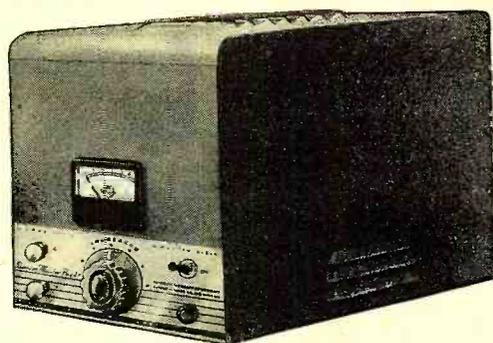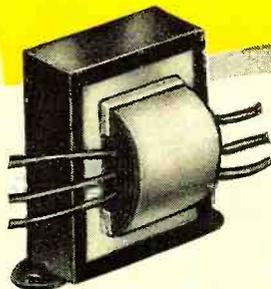- IMMEDIATE DELIVERY!
- DEPENDABLE PERFORMANCE!
- MORE FOR YOUR DOLLAR!
- MOST COMPLETE LINE IN THE INDUSTRY!



NO Transformer can match Stancor for all-round dependable performance and universal adaptability. And no Transformer can fulfill the complete needs of the Radio Service Engineer as Stancor... the Transformers that meet your radio replacement requirements. Immediate delivery!... Any quantity!... Priced right!... Guaranteed satisfaction!

SEE YOUR STANCOR DISTRIBUTOR TODAY!

GET YOUR FREE CATALOG TODAY!

This book contains important technical data and approximately 410 catalog items. See your STANCOR DISTRIBUTOR or write direct.



See Us May 11th - 14th at the
Radio Parts & Electronic Equipment Show
Booth 88, Hotel Stevens, Chicago


standardize on

STANCOR




TRANSFORMERS

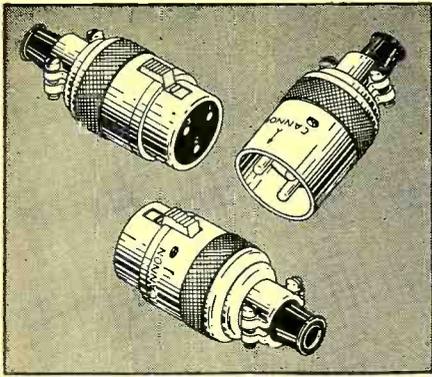STANDARD TRANSFORMER CORPORATION • ELSTON, KEDZIE AND ADDISON • CHICAGO 18, ILLINOIS
May, 1948



NEW AND IMPROVED TYPE "P" PLUG

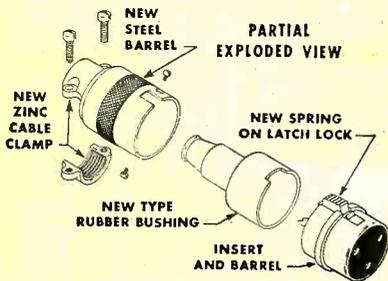On December 1st, 1947, Cannon Electric announced the completion of a new Type "P" to replace the P-CG-11 and P-CG-12 straight cord plugs. At the same time, list prices on all "P" fittings were revised, mostly up, a few down.



The new -11S and -12S plugs replace both the old -11, -12 and former -11S, and -12S. Features of the new fittings are shown by arrows on the view above. The shell is lightweight steel with an integral clamp of zinc. The zinc clamp is superior to the removable clamp and prevents twisting of leads. The rubber bushing adds insulating factors within the solderpot cavity and acts as a cable relief on the P2, and P3. The latch is stronger and better than on the old design.

For complete information, write for Special Bulletin No. PCG-1, and any other catalog material which you may require. Please use your company stationery when writing. Address Dept. E-228.

SINCE 1915

CANNON ELECTRIC

Development Company

3209 HUMBOLDT ST., LOS ANGELES 31, CALIF.
 IN CANADA & BRITISH EMPIRE:
 CANNON ELECTRIC CO., LTD., TORONTO 13, ONT.
 WORLD EXPORT (Excepting British Empire):
 FRAZER & HANSEN, 301 CLAY ST., SAN FRANCISCO

Spot Radio News

★ Presenting latest information on the Radio Industry.

By FRED HAMLIN

Washington Editor, RADIO NEWS

THE WAY THINGS ARE GOING, don't be surprised if television turns out to be the runaway best-seller in electronic circles this year. Production, sales, and public acceptance of the new medium is progressing great guns and there is every indication that the spring boom in video is only a sample of the sensational progress to come during the summer, fall, and winter.

STRAWS-IN-THE-WIND were pre-spring production figures which, while of course not in the same bracket with FM sets, nevertheless rivalled percentage-wise that division's equally sensational rise last year. Latest tabulations of the Radio Manufacturers Association indicate that television production during February totaled 35,889 or 5888 ahead of the January figure and 141 per-cent ahead of the 1947 monthly output. The February rate indicates an annual production during the year of nearly half a million sets. That's almost twice the total television output since the end of the war.

THERE'S A LOT more news on television this month, but before going into details it should be noted that other branches of the industry are doing much better than all right as far as production goes. RMA figures, representing 90 per-cent of the industry, showed for February an AM-FM output of 140,629 units, up 4614 from January. The total was less than the average during the last quarter of '47, but that was something that the industry had long since anticipated, seasonal buying being what it is. Over-all set production in February reached 1,379,605 units, comparing favorably with a year ago and ahead of the January score of 1,339,256. Portables and auto sets were coming off the lines in increasing numbers. In the AM-FM-television field, smaller sets were also playing leading roles. A total of 36 per-cent of the AM-FM production was table models and converters, while table models in television accounted for a startling two-thirds of the production.

ANOTHER THING, reports from all over indicate that television is by way of


attaining its long-dreamed-of goal—mass acceptance. The bar trade started the ball rolling, as was noted here last year, but now it's almost understatement to say that everybody's reaching for sets. Recent surveys indicate that a sizeable percentage of buyers are from the less prosperous side of the tracks. Another potent factor that figures in the spring audience news is the coke-and-sundae trade—everything on two legs from the ages of six to sixteen. Maybe you've already heard the story of the younger-younger generation character, aged five, who, on being taken to his first movie, said: "Look, mummy, television!" More and more frequently, kids are seeing television before they see movies, and the medium is already being hailed as having excellent juvenile educational possibilities. Indicative of the trend is a recent story in the New York Sun about one Charles Feldman, who runs a candy store on New York's East Side. Feldman reports that he fills his store with junior-juniors all the way from grade school kids (afternoons and early evenings) through high schoolers (late evening). Reason; a video receiver. Incidentally, the Feldman story gives you an idea how television has reached the small-income groups: the candy store is in the lower East Side, heart of a community where Manhattan's lowest income groups reside.

ON THE TELECASTING front, big things have been doing and bigger are promised in the months to come. By now, if you haven't heard tell of the U. S. Treasury's Security Loan Drive—well, you've just been out of circulation. But maybe something that you didn't hear was that television played a leading role in getting the drive started. To high treasury officials as well as TV leaders, the effort was history-making. It marked the first attempt by a government agency to recruit volunteers and to let the public sit in, visually as well as with sound, with a national planning conference. The conference, held in Washington March 18-20, was attended by some of the nation's leading financial and business leaders, who told their Security story to television screens. Also to at-

Now IN YOUR OWN HOME Learn

RADIO ELECTRONICS

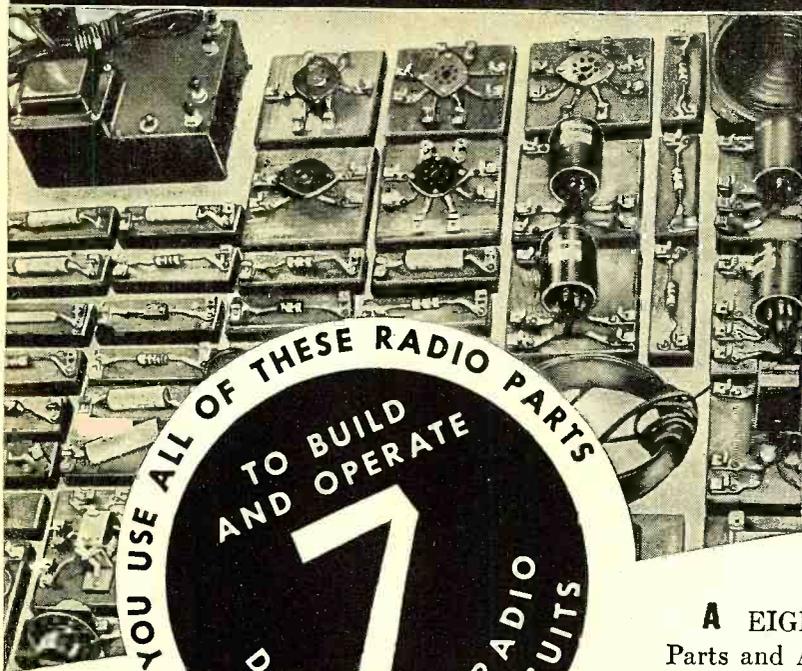The Practical
"HOME-TESTED"
Modern "A-B-C" Way



YOU USE ALL OF THESE RADIO PARTS
TO BUILD AND OPERATE
7
DIFFERENT RADIO RECEIVING CIRCUITS

NO PREVIOUS RADIO OR ELECTRICAL EXPERIENCE NECESSARY

DeForest's Training, Inc. provides every major home study aid to help you learn Radio-Electronics rapidly and thoroughly . . . to give you the experience and confidence needed for a responsible, Good-Pay Job, or to Start a Business of Your Own! Here is a REAL opportunity field for YOU . . . when you are a trained Radio-Electronics man! Just think of the tremendously exciting future ahead of FM Radio, Aviation and Broadcast Radio, Sound Motion Picture Equipment, Servicing and Sales of Radio Equipment, etc. Put yourself in this picture . . . See how you can benefit from a PRACTICAL training in this fascinating work! Think, too, of the coming possibilities ahead of Radar, Facsimile and Television. Send TODAY for the interesting, opportunity-revealing book, "Victory for You!" See how others probably no more talented or ambitious than you, have advanced in earning power after this training . . . how YOU can do it too! Mail the coupon NOW!

INCLUDING:

1. Simple Receiver
2. Two Tube Receiver
3. Tuned Radio-Frequency Receiver
4. Short Wave Receiver
5. Aviation Band Receiver
6. 4-Tube Superheterodyne
7. 5-Tube Superheterodyne with Magic Tuning Eye

... PLUS SCORES OF OTHER FASCINATING, INSTRUCTIVE RADIO-ELECTRONIC EXPERIMENTS

WITH THE HELP OF


A EIGHT Big Kits of Actual "Learn-by-Doing" Radio Parts and Assemblies with which you make 133 fascinating SHOP METHOD EXPERIMENTS in your own home! Imagine building 7 different Radio Receivers that operate!

B A 16 mm Home Movie Projector and Twelve Reels of "Learn-by-Seeing" Home Movie Films . . . for picture-clear, fast understanding of Radio Fundamentals!

C Modern, well-illustrated, Loose-leaf Lessons, prepared in clear, simple, understandable language . . . to guide you throughout your training!

THEN GET THE HELP OF OUR EFFECTIVE EMPLOYMENT SERVICE

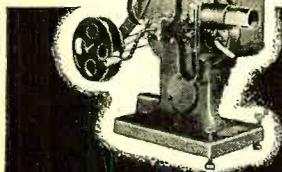
16 MM MOVIE PROJECTOR YOU USE "LEARN-BY-SEEING" MOVIES



DEFOREST'S TRAINING, INC. INCLUDES INSTRUCTION IN MOTION PICTURE SOUND EQUIPMENT, FM RADIO AND TELEVISION . . . RESIDENTIAL TRAINING IN OUR MODERN CHICAGO LABORATORIES ALSO AVAILABLE—ASK US FOR INFORMATION!

VETERANS!

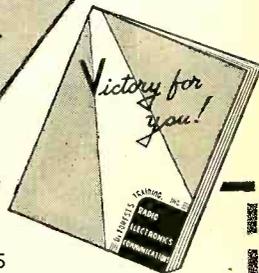Big things are happening at DeForest's Training, Inc. for veterans! See how you can prepare yourself WITHOUT COST for a GOOD JOB or a BUSINESS OF YOUR OWN in the vast Radio-Electronic opportunity field.



E. B. DEVRY, President
DeFOREST'S TRAINING, INC.
2535-41 North Ashland Ave., Dept. RN-E5
Chicago 14, Illinois, U.S.A.

Send FREE "VICTORY FOR YOU!" BOOK, showing how I may make my start in Radio Electronics.

Name _____ Age _____
Address _____ Apt. _____


City _____ Zone _____ State _____

If under 16, check here for special information.

If a discharged Veteran of World War II, check here.

DeFOREST'S TRAINING, INC.
CHICAGO 14, ILLINOIS

May, 1948

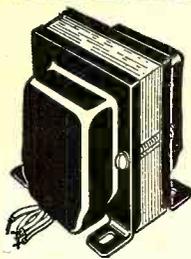

MERIT Model "D"

POINT OF GREATEST SAVING


SPECIFIC APPLICATIONS are constantly calling for new advance in types of transformers — a challenge for which MERIT, with its long specialization and plant facilities, is well equipped to meet. With MERIT only one thing remains unchanged in this changing science — MERIT QUALITY.

MERIT MODULATION TRANSFORMERS For Specific Applications

Type No.	List Price	Output Tubes	Ohms Impedance Pri.	Sec.
A-3110		PP801, 6L6, 10, 46 HK-24, HY-25	10000-6600CT	4000-5000 7500-10000 12000
A-3113	\$15.75	PP800, 809, TZ-40, T-55, HK-54, RK-31, HY-40, 811, 807	15000-6900CT	3000-4000 5000-6000

Dimensions

	Max. Pri.	MA Sec.	Watts	H	W	D	Mtg.
A-3110	175	150	60	4 1/4	3 1/2	3 3/4	D
A-3113	250	300	175	4 5/8	3 13/16	5 5/8	D

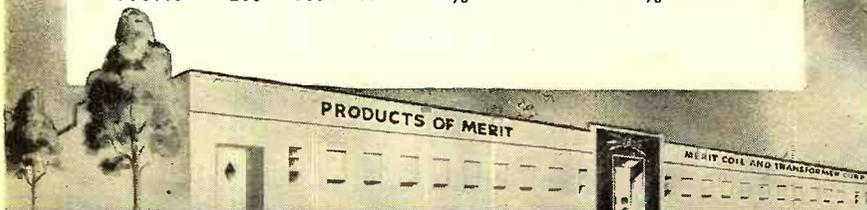

MERIT COIL & TRANSFORMER CORP.

TELEPHONE
4427 North Clark St. Long Beach 6311 CHICAGO 40 ILL.

tract attention of volunteers were chalk-talks by a battery of famous cartoonists led by Rube Goldberg. Recruitment of bond salesmen in areas reached by television was rapid and spontaneous as a result, Treasury leaders report.


AS FOR THE FUTURE—among other things, you will be able to attend both national political conventions via video. What's more—we checked this around town the other day—both national headquarters are planning special TV programs during the sessions. Everybody is happy about the whole thing from what we can gather, and happiest, perhaps, are the television engineers. In case you don't know, it's one whale of a job getting video equipment set up for anything as colossal as a political convention, and to make separate installations for both Republicans and Democrats would multiply the work by two. But the politicians have obligingly eliminated the problem by scheduling their meetings in the same place—Convention Hall, Philadelphia, where the Republicans will face up to the mikes beginning June 21, the Democrats beginning July 12.

INCIDENTALLY, looks as if broadcast advertising, though now including both FM and television, isn't falling off so far as AM is concerned. Indeed, if 1947 figures recently completed by the Federal Communications Commission are an indication, AM is still doing fine. Net time sales, according to the FCC report, showed a 5.6 per-cent increase over '46. The report covers the four national networks, their ten key stations, three regional networks, and 821 stations. Sales for the four national networks and their ten key stations totalled \$72,352,636, up 3 per-cent over 1946. Three regional networks were up 1 per-cent. FCC adds that preliminary reports from 343 new stations licensed during 1947 showed an average monthly income of about \$5900. Total broadcast revenues of these stations came to an estimated \$15,261,819 . . . How much of this money went to radio workers hadn't been figured as we go to press, but FCC did report on the payroll score in '46. It shows the tab on 1015 stations, excluding networks keys, and shows a jump from \$7,483,715 paid to 29,571 employees in January, '46, to \$11,300,760 paid to 32,548 employees in December of the same year. Total 1946 payroll was more than a hundred million dollars, FCC reports. Not bad, not bad.

WE'VE BEEN EXPECTING this one for a long time, but not until recently was anybody willing to stick out his neck and ask for it. Now FCC reports that it's happened—there's now a station

(Continued on page 191)

Another Good Deal—From Mallory To You

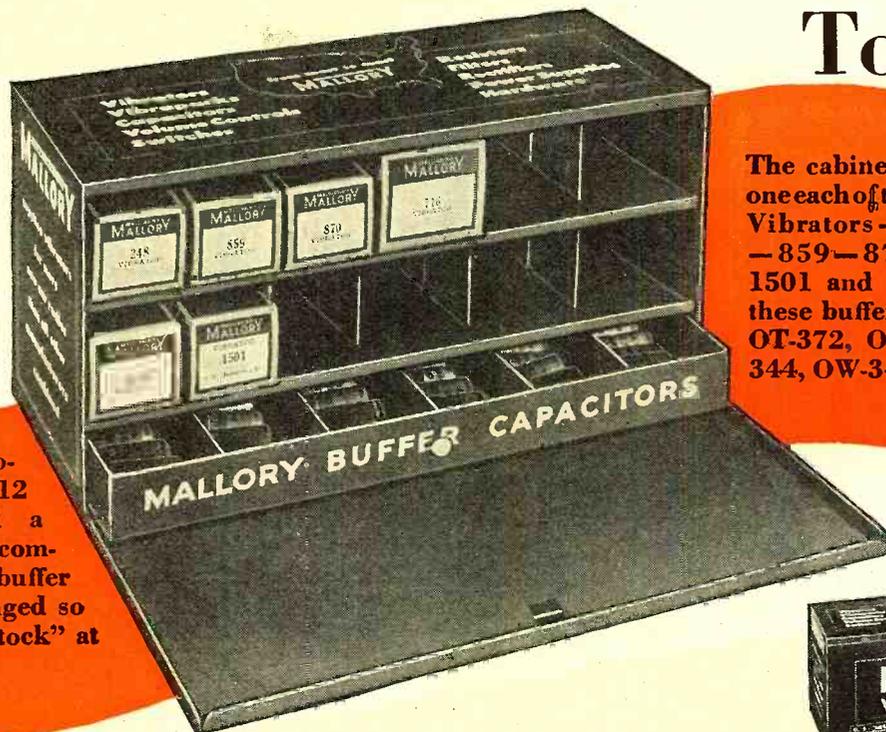

The cabinet provides space for 12 vibrators and a drawer with 6 compartments for buffer capacitors, arranged so you can "take stock" at a glance.

The cabinet contains—
one each of these Mallory
Vibrators—248—716
—859—870—1100—
1501 and two each of
these buffers—OT-371,
OT-372, OT-373, OW-
344, OW-345, OW-346.

The Fastest Selling Vibrators in the Finest Line Made— The Mallory "2448 Vibrator Deal"

Mallory, first producer of the vibrator, builder of the sturdiest, most reliable vibrators made, offers you an attractive deal on this important replacement part. A fast moving selection of 6 vibrators, that will cover 75% of your requirements, together with an assortment of 12 buffer capacitors (2 each of 6 ratings), in an attractive metal cabinet at a net price of \$24.48 to the serviceman.

This is the serviceman's regular price for these parts; no charge is made for the cabinet. You sell the parts for \$40.80—make your full \$16.32 profit.

Your Mallory Distributor has them in stock for immediate delivery. Place your order now, and get this handsome, convenient cabinet for *your* shop.

More Mallory Vibrators are in Use Than All Other Makes Combined

WHAT WILL
MALLORY
DO NEXT?

See Us at
the Radio
Parts Show


P. R. MALLORY & CO., Inc.
MALLORY

CAPACITORS . . . CONTROLS . . . VIBRATORS . . .
SWITCHES . . . RESISTORS . . . RECTIFIERS . . .
VIBRAPACK* POWER SUPPLIES . . . FILTERS

*Reg. U. S. Pat. Off.

APPROVED PRECISION PRODUCTS


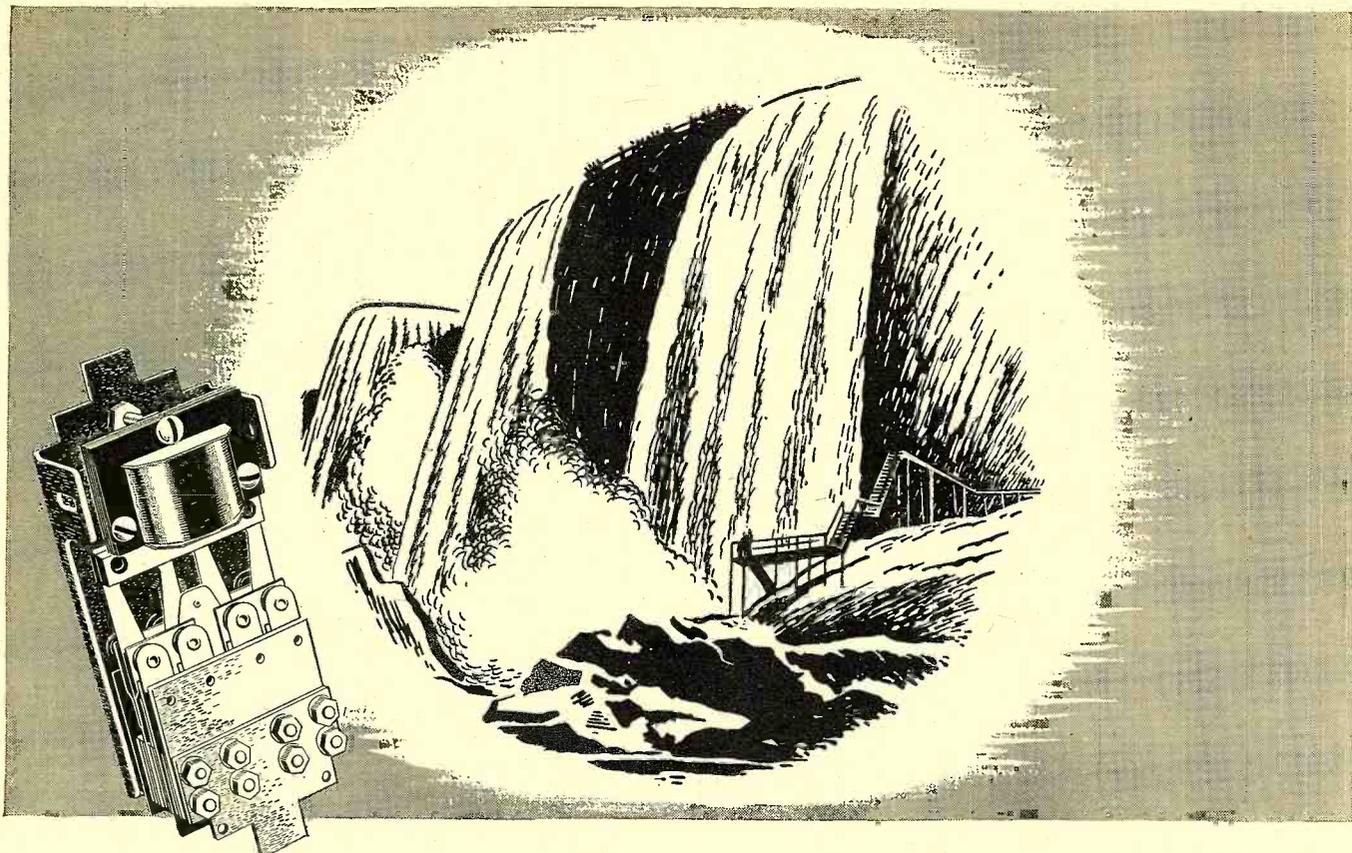
P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA



Power Unveiled

Here it is! The answer to a thousand problems . . . possible because of the skillful design and engineering that has made Radiart the leader. We are proud to unveil this POWERFUL VIBRATOR in conjunction with the annual Chicago showing, an event of great moment. The old rotary inverter is replaced with this rugged vibrator where high voltage changes from D. C. to A. C. are required. This advanced design incorporates vast improvements on anything the field has previously known, and has a wide variety of industrial and domestic applications.

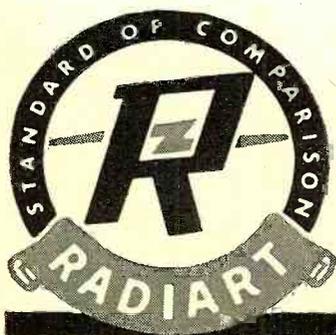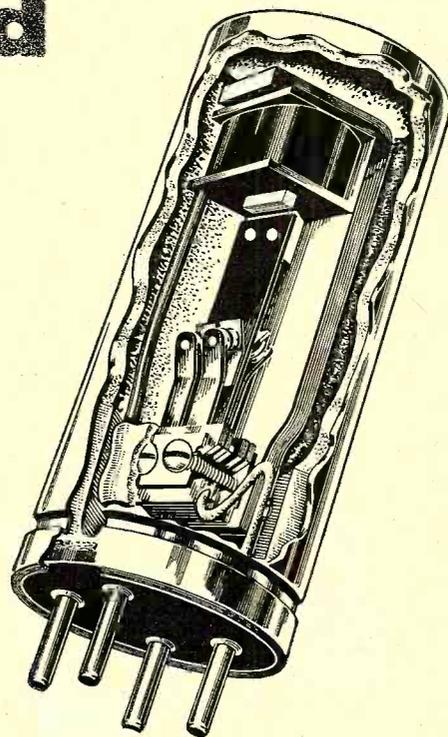See this, and other Radiart products at our display booth.



The Radiart Corp.
CLEVELAND 2, OHIO

Make More Money in

Radio TELEVISION & ELECTRONICS

NOW!

Get these 2 BIG BOOKS
FREE!



**LEARN
BY DOING**

Work with Real Experimental Equipment
Furnished without
Extra Cost as Part of
your National Schools
Training

Experience is the best teacher. You learn by experience with the exclusive National Shop-Method of Home Training. With the apparatus sent you, you actually build various types of standard equipment—a powerful super-heterodyne receiver, a signal generator, an audio oscillator, low power Radio transmitter and other units. You make tests and conduct experiments that show you the why and how of Radio. You understand what makes the various elements of Electronics operate because you actually see them work for you. Not only do you gain splendid experience by this method of learning, but you receive valuable equipment you will use on the job in the practice of your profession as a Radio Technician. Mail the coupon and learn what this means to you.

Send Coupon
and prove to
yourself what
**YOU can do
in RADIO and
TELEVISION!**

FREE LESSON INCLUDED

Examine the exclusive National Shop Method of Home Training. See for yourself how sound and practical it is. Be convinced that you can learn Radio, Electronics, Television—quickly and easily in your spare time. This trial is ABSOLUTELY FREE.
Mail the coupon here for the books that tell you the complete story of National Schools Master Shop Method of Home Training in Radio, Electronics and Television.
This is the MODERN SYSTEM OF TRAINING, it matches the rapid progress constantly being made in Radio, Television and Electronics. It is TIME TESTED, too. National Schools has been training men for more than a third of a century. It is the very same training that has helped thousands to more pay and greater opportunity. You owe it to yourself—your future—to read the book "Your Future in Radio, Electronics and Television"—FREE to you when you send in the coupon.
May, 1948

If you are already employed in the great Radio industry, you know how great the demand is for trained, experienced servicemen, operators and technicians. You know how fast the field is growing and how important it is to keep up with new developments in R.M., Television and Electronics. The Radio Industry is alive with opportunity for the qualified technician whose knowledge is up-to-the-minute. You can be an R.M., and Television specialist . . . get into the lucrative Radio Service Field . . . own a business of your own, if you prefer. National Schools of Los Angeles, for over 40 years a practical resident and home study trade school, has put into effect its New 1948 Training Program. This program, adapted to National's Master Shop Method Home Study Course, can qualify you in your spare time as a Radio and Television technician. For details of this Program fill out and mail the coupon below.



You build this fine modern Superheterodyne Receiver and 10 other units, with the complete standard parts we send you. This valuable equipment becomes yours to use and keep.

You learn by building equipment with standard radio parts we send you



**NOW! New Professional
Multitester Included!**

This versatile testing instrument is portable and complete with test leads and batteries. Simple to operate, accurate and dependable. You will be able to quickly locate trouble and adjust the most delicate circuits. You can use the Multitester at home or on service calls. It is designed to measure AC and DC volts, current, resistance and decibels. You will be proud to own and use this valuable professional instrument.

**SHOP METHOD HOME TRAINING
FROM A TECHNICAL TRADE RESIDENT SCHOOL**

National Schools brings its exclusive Shop Method of training right into your own home. You can learn the most up-to-date approved practical training projects, systems and modern circuits from the very beginning in your spare time. Here is sound and practical home training—the development of experienced instructors working with students right in the shops, NEW Television and Broadcast Studios and Experimental Laboratories of NATIONAL SCHOOLS—one of the most advanced technical trade education centers in the world.

Take Advantage Now of these Outstanding Features of National Schools 1948 Training Program

1. National Schools' 1948 Course is planned to prepare you for real success in Radio, Television and Electronics.
2. Experimental equipment supplied with the Course has been completely revised to give you the most up-to-date practical experience with new circuits, new units, etc., right in your own home.
3. New Television Lessons have been expanded to give you training in the latest developments in this important field.
4. The 1948 Course includes a Professional Multitester (shown above) for your use in spare or full-time Radio work.
5. National Schools gives you advanced training—the key to the better positions in Radio, Television, Electronics.
6. You are sent standard Experimental Equipment, including tubes and accessories, for building a modern Short Wave and Standard Broadcast Superheterodyne Receiver. All equipment becomes your personal property.
7. National Schools' 43 years of experience in Technical Trade Training . . . our modern shops and laboratories . . . highly trained instructors are back of your time-tested Training Plans for a brighter future.

**Approved
for
Veterans**

Check Coupon

G. I. APPROVED

NATIONAL SCHOOLS

LOS ANGELES 37, CALIFORNIA EST. 1905



MAIL OPPORTUNITY COUPON FOR QUICK ACTION

MEMBER: NATIONAL COUNCIL OF TECHNICAL SCHOOLS MEMBER: NATIONAL HOME STUDY COUNCIL

NATIONAL SCHOOLS, Dept. RN-5
4000 South Figueroa Street, Los Angeles 37, California (Mail in envelope or paste on penny post card)

Mail me FREE the two books mentioned in your ad, including a sample lesson of your course. I understand no salesman will call on me.

NAME AGE

ADDRESS

CITY ZONE STATE

..... Check here if Veteran of World War II

Modern HAS ALL 17 VOLUMES

"We would never try to operate . . . without a complete set of RIDER MANUALS . . ."

"We would never try to operate a radio servicing business without a complete set of Rider Manuals, for we service sets of all makes and ages, must have all the data at hand to locate quickly troubles in all receivers. That's why we always order the latest volume as soon as it's published"

Says **JACK E. KENNEY**

of Modern Radio and Television Sales and Service, Spokane, Washington


Operators of successful servicing shops know that the shortest path to profit lies through speedy diagnosis. That's why complete sets of Rider Manuals, well-worn from much use, are found over their benches.

Nowhere . . . nowhere else but through Rider Manuals can you build a library of circuit data containing so many models of so many single-band receivers, so many multi-band receivers (beginning with Vol. XV all broken down into "clarified-schematics"), so many manufacturers, wire recorders and record players . . .

so much vital information. From no other single source can you get such complete coverage of U. S. receivers and allied equipment.

Give Your shop The Sign of Successful Servicing . . . a complete set of Rider Manuals.

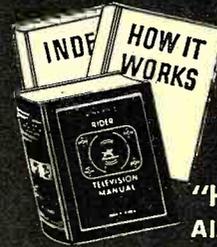COMING IN JUNE!
Vol. 1 . . . RIDER TELEVISION MANUAL



Approximately
1000 PAGES
PLUS—Separate

"HOW IT WORKS" Book.
Also index . . \$15.00.

Provides the servicing information you need on the products of major manufacturers; complete sets and kit sets. "How it Works" book explains theory of operation on TV sets.

RESERVE YOURS AT YOUR JOBBERS

Complete **ORIGINAL MANUFACTURERS DATA**

You **NEED ALL 17**

Volume XVII	\$15.00
Volume XVI	8.40
Volume XV	18.00
Volumes XIV to VII (ea. vol.)	15.00
Volume VI	11.00
Abridged Manuals I to V (one vol.)	17.50
Record Changers and Recorders	9.00
Master Index, covering Manuals, Vols. I to XV	1.50


VOL. XVII NOW AT YOUR JOBBER'S

RIDER MANUALS

Mean Successful Servicing

JOHN F. RIDER, PUBLISHER, Inc., 404 Fourth Avenue, N. Y. 16

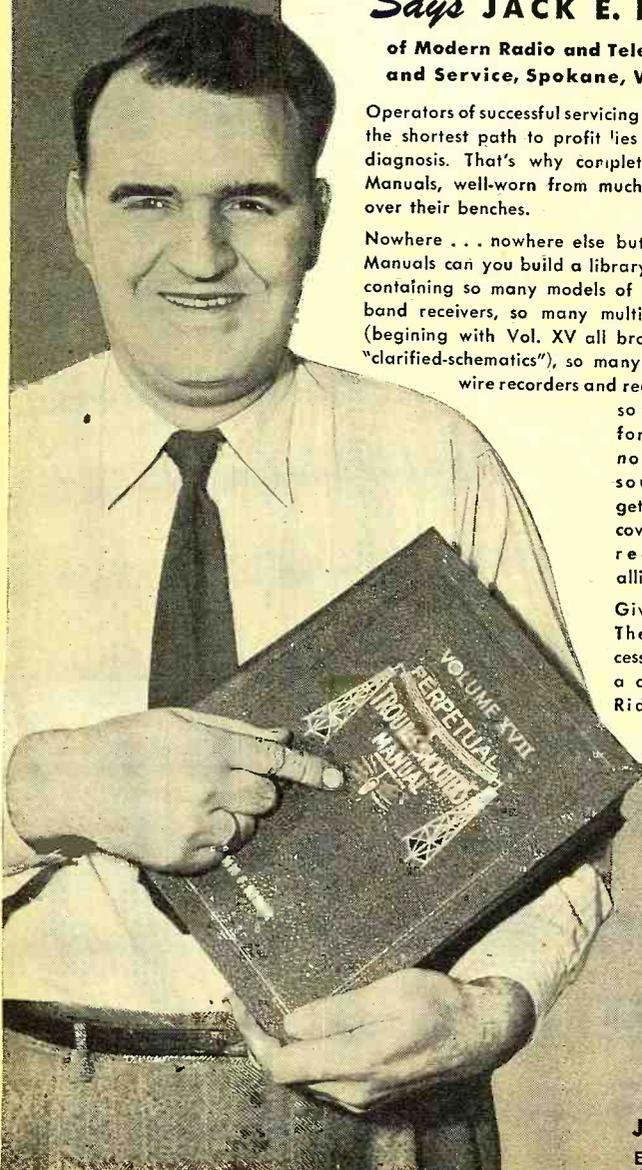Export Agent: **Rocke International Corp., 13 E. 40th St., N.Y.C. Cable ARLAB**



NOTE: The Mallory Radio Service Encyclopedia, 6th Edition, makes reference to only one source of Radio Receiver Schematics.—Rider Manuals.

Welcome IN EVERY HOME IN AMERICA



GENERAL  **ELECTRIC**

FIRST AND GREATEST NAME IN ELECTRONICS

170-GA4-0850



May, 1948

25


Why play "PENNY-ANTE" . . . when your business is at stake?

A good reputation, like good-will, is built by many deeds, but may be destroyed by a single dissatisfied customer. Your reputation is too valuable to risk for the few pennies "saved"

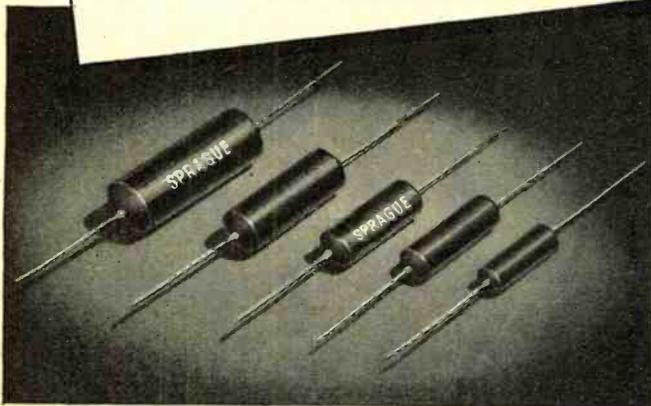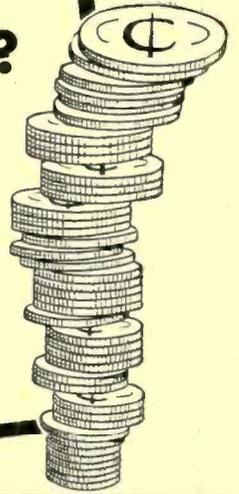
by buying inferior or unknown "bargains." That's why we keep repeating "Your Reputation and your customers deserve the best!" And the best means Sprague.



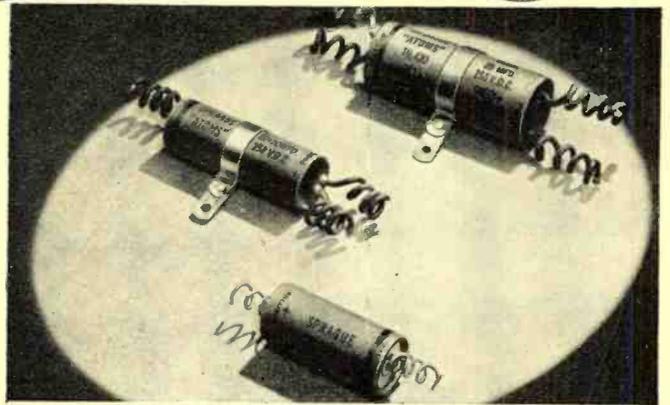SPRAGUE TM TUBULARS—The first truly practical MOLDED Paper Tubular Capacitors!



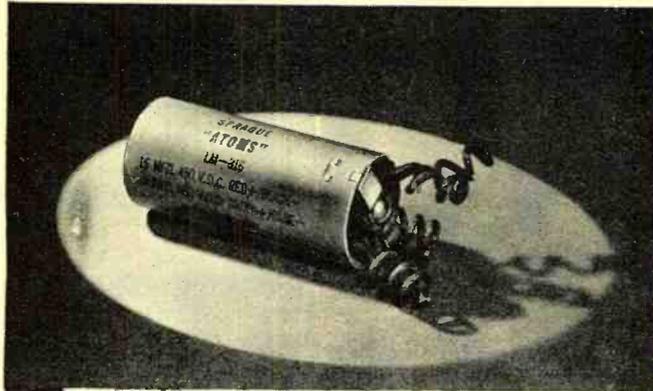SPRAGUE ATOMS—Universal Midget Dry Electrolytic!



SPRAGUE LM—Universal Mounting Replacements!



SPRAGUE EL—Self-Mounting Midget Can Type!



Reach for a **SPRAGUE**
and Know You're Right!

THESE SPRAGUE PRODUCTS ARE UNCONDITIONALLY GUARANTEED!

When used at their capacitance and voltage ratings, these Sprague Products are unconditionally guaranteed to render satisfactory performance.

CAPACITORS

*KOOLOHM
RESISTORS

SPRAGUE

*T.M. Reg.
U.S. Pat. Off.

SPRAGUE PRODUCTS COMPANY, North Adams, Mass.

(JOBGING AND DISTRIBUTING ORGANIZATION FOR THE PRODUCTS OF THE SPRAGUE ELECTRIC COMPANY)

RADIO NEWS

RADIO SERVICEMEN!

19 PRIZES FOR 18 IDEAS


HERE'S HOW EASY IT IS TO WIN

Right now, you may have a winning idea at work in your shop. An idea for a simple service tool which makes your work easier, faster, more profitable. Hytron wants to help make such needed tools available to all servicemen — at cost. You can cash in on your idea easily — and also help the other fellow.

Simply obtain an official entry blank from your Hytron jobber — or write us. Answer a few simple questions on the blank. Then include a sketch with constructional details — or a photograph — or a model of your proposed tool. Mail

to Hytron Contest Editor. The tool should be simple, practicable, durable, compact, easy and economical to manufacture. Examples: Hytron Tube Tapper and Miniature Pin Straightener.

That's all there is to it. Nothing to buy. Nothing difficult. No fancy writing. And could you use one of those beautiful deluxe test equipments — or one of those crisp new Savings Bonds! Check the easy rules. Get an official entry blank today for full details on how to win. Send in as many entries as you wish — in any or all six contests. Everyone wins a Tube Tapper. Your idea may hit the jackpot. Let's go!

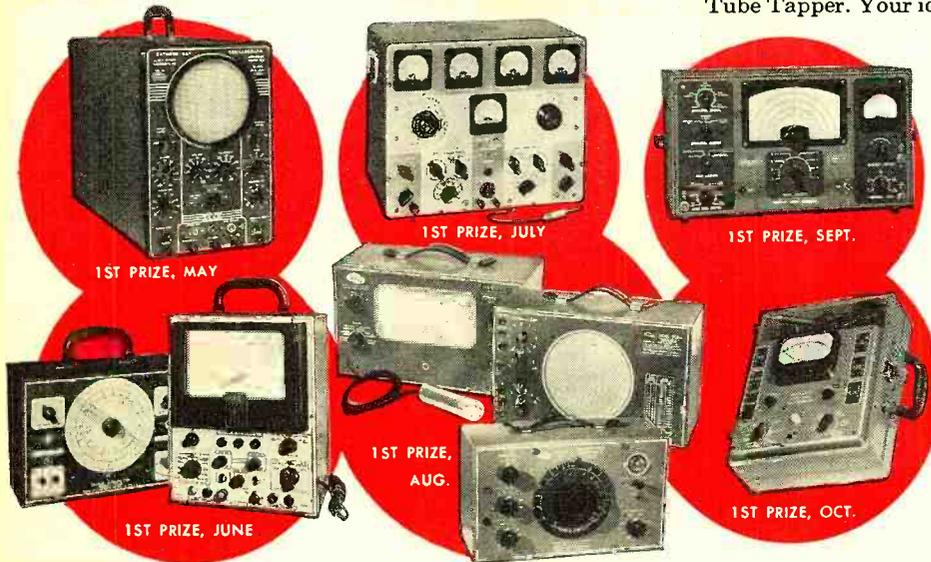

HERE ARE SOME EXAMPLES



Hytron's Tube Tapper and Miniature Pin Straighteners show you the kind of tool wanted. Check off the qualities. Simple? Yes. Practicable? Usable time-savers. Durable? Built to last. Compact? Carry them in your pocket. Easy and economical to manufacture? Adapted to mass production. Tube Tapper a nickel; Pin Straightener 49¢ — both under 50¢. Tools associated with tubes preferred, but other original service tools also acceptable.

HERE ARE THE PRIZES

First Prizes

- MAY DuMont Type 274 Five-Inch Oscillograph.
- JUNE Radio City Products Model 665-A, the "Billionaire", V-T Volt-Ohm-Capacity Meter, Insulation Tester; and Model 705-A Signal Generator.
- JULY Hickok Model 156A Indicating Traceometer.
- AUG. McMurdo Silver Model 900A "Vomax" Electronic Volt-Ohm-Milliammeter; Model 904 Condenser/Resistor Tester; and Model 905A "Sparx" Dynamic Signal Tracer/Test Speaker.
- SEPT. Jackson Model 641 Universal Signal Generator.
- OCT. Weston Model 769 High Frequency Electronic Analyzer.

- Second Prize — Each Month \$50 U. S. Savings Bond
- Third Prize — Each Month \$25 U. S. Savings Bond

Grand Prizes

- \$200 U. S. Savings Bond — to contestant whose idea is judged to be best of the 6 winning monthly first prizes.
- \$200 U. S. Savings Bond — to Hytron jobber indicated on entry blank as serving grand prize winner.

HERE ARE THE EASY RULES

WHO . . . Any bona fide radio serviceman who repairs radios for the general public and who lives in continental United States is eligible for these contests, except employees of Hytron, their advertising agencies, and their families.

HOW . . . Get official entry blank from your Hytron jobber, or write us. Describe on blank your idea for a shop tool for radio servicemen. Include sketch and constructional details — a photo — or model. Make your proposed tool simple, practicable, durable, compact, easy and economical to manufacture (preferably to sell without profit at 50¢ or less) — like the Tube Tapper or Miniature Pin Straightener.

WHERE . . . Mail to CONTEST EDITOR, HYTRON RADIO & ELECTRONICS CORP., SALEM, MASS.

WHEN . . . There are six monthly contests. Opening and closing dates for each contest are the first and last days of each of the months from May through October, 1948, inclusive. The postmark date determines month of entry. Entries for final month's contest must be postmarked before midnight, October 31, 1948, and received by November 15th. At judges' discretion, unsuccessful entries in any month's contest may be re-considered among following months' entries. You may submit as many different ideas as you wish in any or all six monthly contests. Use separate blank for each entry.

PRIZES . . . See special listing of prizes.

JUDGES . . . Entries will be judged on originality, simplicity, practicability, durability, compactness, and ease and economy of manufacture. Judges will be: Sanford Cowan, Editor & Publisher of *Radio Service Dealer*; W. W. MacDonald, Managing Editor of *Electronics*; Oliver Read, Chief Editor of *Radio News*; Joseph Roche, Editor of *Radio Maintenance*; J. L. Stoutenburgh, Executive Editor of *Radio & Television Retailing*; Lewis Winner, Chief Editor of *Service*.

Judges' decisions final. Duplicate prizes in case of ties. No entries returned. Entries become property of Hytron, who may, at its option and by special arrangement with the entrant, pay the cost of a patent application (if the tool is patentable) with the understanding that Hytron is to have a non-exclusive license to manufacture, distribute, and sell the tool without royalties. Contests subject to all Federal and State regulations. Winners will be notified by mail. Grand prize winner will be announced in radio service trade papers shortly after close of final contest. Prize winner list available approximately one month after close of last contest.

SPECIALISTS IN RADIO RECEIVING TUBES SINCE 1921

HYTRON

RADIO AND ELECTRONICS CORP.

MAIN OFFICE: SALEM, MASSACHUSETTS




free radio book

RADIOS HAM P.A.

Mail coupon for buying guide to the best values in Radio, Ham and P.A. Equipment. Send too for the newest flyer jam-packed with bargains.

Spot-lite Values

performs 25 Ceramicon Condensers

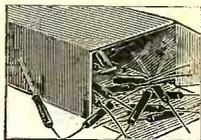

Provide ultimate stability. Temperature coefficient is determined by the ingredients of the ceramic di-electric; controllable to within very fine limiting values. Color coded. Flexible pig-tail leads. Shpg. wt. 1 lb.

AP5511—Your Cost **69c**

Crystal FM Converter

Change old FM (40-50 Mc) to new FM in a few moments and at lowest cost. Efficient operation; this is a superior device. No loss of signal. Easy to install.

AP5700—Your Cost.

Only **\$6.00**



from **Safayette**

MAIL NOW

New York
100 SIXTH AVE.
110 Federal St., Boston 10
24 Central Ave., Newark 2



RADIO WIRE TELEVISION, INC.
Dept. RE-8, 100 Sixth Avenue, N. Y. 13

Send #AP5511 @ 69¢ ea. quantity

Send #AP5700 @ \$6.00 ea. quantity

Enclosed: check money order

Send catalog New Flyer C42

Name

Address

City Zone State

28

Within the INDUSTRY

CAPTAIN DAVID R. HULL, U. S. Navy, (retired) has been appointed Assistant Technical Director of the *International Telephone and Telegraph Corporation*. Mr. Hull has been associated with the electronic research and radar development for the Navy during the past 23 years, the last two as Assistant Chief of the Bureau of Ships for Electronics.



Mr. Hull, who has been awarded the Legion of Merit and other military honors for his services during the war, has been engaged in radio and electronic research work since his graduation from the U. S. Naval Academy in 1925. As assistant Director of the Naval Research Laboratory at Washington, D. C., and later as head of the Design Branch and Deputy Director of Electronics of the Bureau of Ships he aided in perfecting the latest radar and electronic techniques for use by the U. S. Navy during the war.

* * *

SOLAR MANUFACTURING CORPORATION recently announced the appointment of Alfred S. Gartner as Assistant Sales Manager.

Mr. Gartner, who has been connected with the *Solar* organization for nearly five years, will devote his time to sales of capacitors and radio noise filters to equipment manufacturers in the radio and electrical industries.

* * *

JOHN W. CRAIG has been appointed General Manager of *Crosley Division, Avco Manufacturing Corp.* His new duties will include direction of all manufacturing and purchasing operations of *Crosley* and the *Carrollton Furniture Co.*, of Carrollton, Ky., an *Avco* subsidiary.



Mr. Craig is a graduate of the University of Dayton and holds a B.S. in mechanical engineering. He joined the *Crosley* organization in 1937 as assistant chief refrigeration engineer, later being promoted to chief engineer. Since 1945 he has been Works Manager of the *Crosley Shelvador* refrigeration plant in Richmond, Indiana.

During the war, Mr. Craig devoted his efforts to the development and improve-

ment of the Mark 14 anti-aircraft gun-sight.

* * *

THE EMPIRIA CORPORATION recently announced the visit of the Messrs. Shah of the *Terra Trading Company* of Bombay. The gentlemen are interested in the purchase of quantities of machinery for the production of plastic and other electrical accessories, radio, electronic and cinema equipment, and engineering materials.

They would like to contact manufacturers of such products and may be reached at the *Empiria Corporation*, 149 Broadway, New York 6, New York.

* * *

ALBERT J. ROSEBRAUGH has been appointed manager of small radio set sales for *Philco Corporation*.

In his new capacity Mr. Rosebraugh will be responsible for nationwide sales of the *Philco* line of small radio sets through the company's distributor and dealer organization.



Mr. Rosebraugh has held various positions in the company since he first joined *Philco* in 1928 and was employed in the service department of the company's Chicago wholesale organization.

* * *

PACKARD-BELL COMPANY of Los Angeles has announced three new appointments. William H. Cies has been named Sales Manager; Kenneth Johnson, Assistant Sales Manager; and Frank E. Ware, Field Sales Manager.

Before joining the *Packard-Bell* organization over a year ago, Mr. Cies was associated with *Booz, Allen and Hamilton*, Management Engineers, and *U. S. Steel Corporation*. Mr. Ware has been with *Packard-Bell* for the past nine years and has acted as Sales Manager since 1945. In his new capacity, Mr. Ware will spend the majority of his time in the field working with company distributors and dealers, and aiding dealers with their promotional work.


* * *

JOHN CLUNE, Sales Manager of *Air King Products Co., Inc.* and formerly sales manager of *National Union Radio Corporation's* Replacement Tube Division, passed away recently as the result of injuries sustained in an auto accident.

With Mr. Clune at the time of the accident was Russell Aiken, midwest

RADIO NEWS

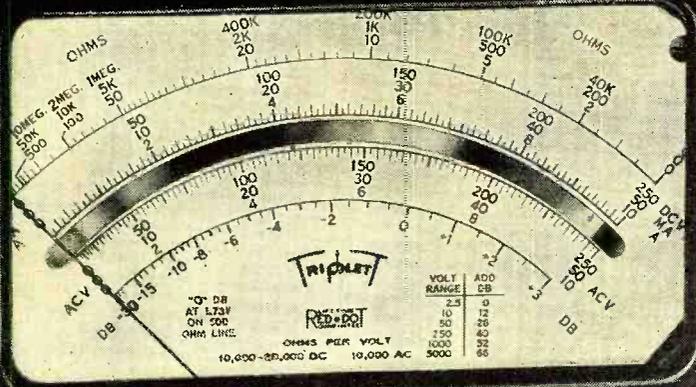READ MORE RANGES • MORE ACCURATELY • MORE EASILY



CAUTION ON HIGH VOLTS

5000V

MODEL 625 NA

V-Ω-MA-A

5000V
1000V
250V
50V
10V
2.5V
2K

10AMP
1000MA
100MA
10MA
1MA
50μA
40MEG

OHMS
ADJ

Ω-MA-A
DCV
10KΩ/V
DCV+2
20KΩ/V


ACV
OUT
PUT
COM

- 12 D. C. Voltage Ranges on 4.4" scale. Mirrored for Accuracy. Special multipliers for permanent accuracy.
- 6 A. C. Voltage Ranges on 4" Scale. Mirrored for Accuracy. Special multipliers for permanent accuracy.
- 6 D. C. Current Ranges on 4.4" Scale. Mirrored for Accuracy. Wire wound shunts for permanent accuracy.
- 3 Resistance Ranges on 5" scale. Mirrored for Accuracy. Special multipliers for permanent accuracy.
- 6 Decibel Ranges on 3.33" scale. Mirrored for Accuracy. Special multipliers for permanent accuracy.


**MODEL
625-NA**

Dealer Net Price \$45⁰⁰


Solve your Service Problems Better—with TRIPLETT

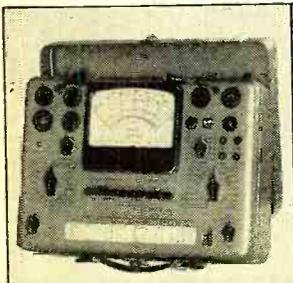


Model 3480—Combination Tube Tester and Volt-Ohm-Mil-Ammeter U.S.A. Dealer Net, \$89.75

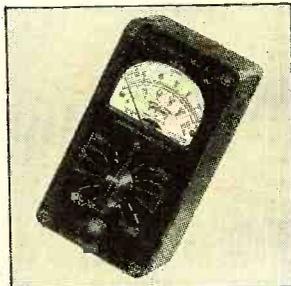

Model 666-HH—Pocket-size Volt-Ohm-Milliammeter, U.S.A. Dealer Net \$22.00

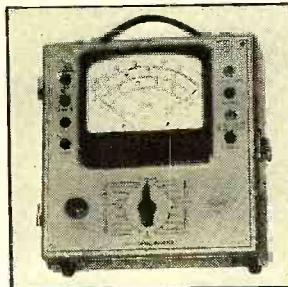

Model 2405-A — Sensitive Volt-Ohm-Mil-Ammeter U.S.A. Dealer Net \$54.75

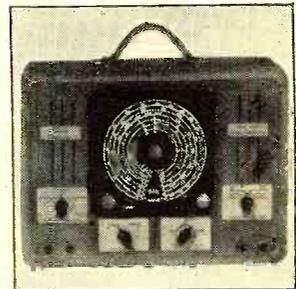

Model 3432—Test Oscillator with illuminated dial. U.S.A. Dealer Net \$63.25

For Descriptive Material Write Dept. N-58

TRIPLETT ELECTRICAL INSTRUMENT CO. • BLUFFTON, OHIO

In Canada: Triplett Instruments of Canada, Georgetown, Ontario

NEW TRIPLETT TELEVISION TESTERS COMING
WATCH

Precision first...to Last



Free



NEW Complete
Concord
RADIO CATALOG
160 VALUE-PACKED PAGES

MAIL the coupon below now for your copy of this great, new comprehensive Concord Catalog—a vast, complete selection of everything in Radio, Radar, Television, Test and Electronic Equipment. Featuring thousands of items . . . new, latest 1948 prices. See the new LOWER prices on finest-quality RADIO SETS, PHONO-RADIOS, RECORD CHANGERS, RECORD PLAYERS, RECORDERS—wire and disc, PORTABLES, AMPLIFIERS, COMPLETE SOUND SYSTEMS, TESTERS. See complete latest listings of all the well-known, standard, dependable lines of radio parts and equipment—all available for IMMEDIATE SHIPMENT from huge stocks in CHICAGO and ATLANTA. Whatever your needs in Radio and Electronic Parts, Supplies and Equipment—before you buy—SEE THIS GREAT NEW CONCORD CATALOG. Mail coupon for your FREE copy.

WE HAVE WHAT YOU WANT!

The new Concord Catalog displays the most comprehensive stock in years! All well-known, standard lines are fully represented. Equipment—accessories—parts for all radio and electronic use . . . for building, repair, maintenance . . . for engineer, amateur, serviceman, soundman, retailer . . . complete lines of tubes, instruments, tools, speakers, condensers, resistors, relays, etc. . . PLUS a complete radio set department . . . PLUS the exciting line of MULTIAMP Add-A-Unit Amplifiers offering many innovations in public address units obtainable only from Concord.

- RADIO PARTS**
- RADIO SETS**
- AMPLIFIERS**
- TESTERS**
- ELECTRONIC EQUIPMENT**
- HAM GEAR**

Mail **COUPON**

CONCORD RADIO CORPORATION, Dept. 136
 901 W. Jackson Blvd., Chicago 7, Ill.
 Yes, rush FREE COPY of the comprehensive new Concord Radio Catalog.

Name _____
 Address _____
 City _____ State _____

CONCORD
RADIO CORPORATION
 CHICAGO 7 ATLANTA 3
 901 W. Jackson Blvd. 265 Peachtree St.
 Downtown Chicago Branch: 229 W. Madison
 Lafayette Radio Corp.,

representative for *Air King* who is recovering from a broken neck received in the accident.

H. D. JOHNSON, formerly Assistant Sales Manager for *The Hickok Electrical Instrument Co.*, has been appointed Sales Manager, succeeding the late Robert Williams.



Connected with the radio and test instrument industry since 1928, Mr. Johnson received his initial experience as a "test man" in the radio receiver department of the *General Electric Company*. During the past war, he was in charge of Test Instruments for the War Production Board. Mr. Johnson also previously represented *Hickok* in the Philadelphia territory.

O. B. WILSON has been named industrial manager for the eastern sales region of the *Brown Instrument* division of the *Minneapolis-Honeywell Regulator Company*. Mr. Wilson's territory will include the New England States and northern Virginia.

He has been with the *Honeywell-Brown* organization for the past 25 years and has served as a sales engineer in various parts of the country. Mr. Wilson was formerly industrial manager in Houston, Chicago, and New York. His headquarters will continue to be in New York City, where he has been the *Brown* manager for the past two years.

LEOPOLD M. KAY, formerly Chief Engineer, has been promoted to the post of Vice-President in Charge of Engineering for *Air King Products Co., Inc.* Mr. Kay, who has been with the Brooklyn manufacturer of radios, combinations, and wire recorders for the past two years, held the position of research engineer for the *Raytheon Manufacturing Co.* before joining *Air King*. Prior to that he was in charge of wire recorder research for *Lear, Inc.*



Mr. Kay is a graduate of Lehigh and New York Universities and holds a B.A. degree in mathematics.

ALTEC SERVICE CORPORATION has announced the organization of a group of 250 special engineers to handle the emergency servicing of complex electronic devices now being used in every type of industry. These engineers are trained to handle electrical and mechanical engineering problems with preference given to mechanisms involving the principles and techniques of the vacuum tube which is usually outside

(Continued on page 184)

Put This Formula To Work For You

$$I = \frac{E}{IRC}$$

The formula $I = \frac{E}{IRC}$ is a favorite and easily-remembered solution to resistance problems. Radio and electronic Engineers know that IRC offers the most complete line of resistance products in the industry . . . a fixed or variable resistor for most every requirement . . . with uniform dependability proved by years of rigorous laboratory and field tests. Purchasing Agents and material control executives like IRC's service . . . "on-time" deliveries . . . factory stock-piles of the most popular types and ranges from which they can draw in emergency . . . IRC's distributor network, providing speedy, 'round-the-corner service for small order requirements.

Put this formula to work for you . . . check below the catalog bulletins in which you are interested, and write for them today on your letterhead, giving your name and title. International Resistance Company, 401 N. Broad Street, Philadelphia 8, Pennsylvania. In Canada: International Resistance Company, Ltd., Toronto, licensee.



INSULATED COMPOSITION INSULATED WIRE WOUND RESISTORS
IRC types BT & BW



FINGER-TIP CONTROLS AND SWITCHES
IRC types H & SH



WIRE WOUND RESISTORS
IRC type MW



MATCHED PAIR RESISTORS



POWER RESISTORS



FLAT POWER RESISTORS
IRC type FRW



VOLUME CONTROLS
IRC type DS



WIRE WOUND POTENTIOMETERS
IRC type W




VOLTMETER MULTIPLIERS
IRC types MFA & MFB



POWER RHEOSTATS
IRC types PR & PRT



WATER-COOLED RESISTORS
IRC type LP

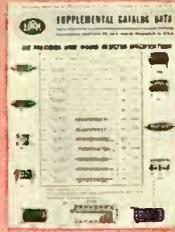

PRECISION RESISTORS



HIGH VOLTAGE RESISTORS
IRC type MV



HIGH POWER RESISTORS
IRC type MP

INTERNATIONAL RESISTANCE COMPANY

Wherever the circuit says 

Power Resistors • Precisions • Insulated Composition Resistors • Low Wattage Wire Wounds • Rheostats • Controls • Voltmeter Multipliers • Voltage Dividers • HF and High Voltage Resistors

McMurdo
SILVER

Announces the NEW 900A VOMAX



Net Price
\$68.50

CONTINUOUS RESEARCH, study of thousands of cases of actual field experience now enable us to offer you the new 900A "VOMAX". Revolutionary as was the original, the new 900A forges far ahead in simplicity, dependability all-around *usability*.

Just 34 months ago McMurdo Silver Co. announced "VOMAX"—the first truly stable, ultra-high input resistance v.t.v.m. Lifting the v.t.v.m. out of the limited laboratory-application class, Silver engineering and use-experience made "VOMAX" the first *universal* v.t.v.m. Its acceptance was instant and overwhelming — for "VOMAX" will measure, at input resistance so astronomically high as not to "load down" any circuit to which it may be connected — d.c. volts, a.c., a.f., i.f. and r.f. volts, d.c. milliamperes and amperes, resistance and db. — all over tremendous range and with laboratory accuracy. Used in scores and hundreds by such competent organizations as the National Bureau of Standards, the Navy, Army, F.C.C., C.A.A., Veterans Administration, G. E., Western Electric Co. Recommended by Bendix, "VOMAX" is consistently copied, never equalled — stands today as "standard of comparison" for the entire industry.

In announcing the new "VOMAX" we think you'll agree that we can feel just a bit proud of having again done the impossible to give you the world's finest *universal* Laboratory Caliber Electronic Test meter at only Net \$68.50.

FEATURES

- Non-breakable glass 7" meter completely protected behind panel.
- Single hand-convenient probe gets into tight places, banishes usual snarl of easily lost and broken test leads.
- Newer — and fewer — miniature u.h.f. tubes.
- 51 ranges at highest available a.c. and d.c. input resistance.
- Absolutely stable—one adjustment sets meter zero for all ranges.
- No grid current error. Exclusive to "VOMAX", this vital feature is carried to new heights in new 900A.
- 24 d.c. ranges at 51 and 126 megohms, constant input resistance. 0 thru 3, 7.5, 12, 30, 75, 120, 300, 750, 1200 and 3000 volts. Polarity reversing switch.
- 6 a.c./r.f. ranges, 20 Ω thru 300 mc., 20 megohms input resistance shunted by 7 mmfd. 0 thru 3, 12, 30, 120, 300 and 1200 volts.
- 3 db. ranges.—10/+10, +10/+20 and +20/+50 db.
- 6 resistance ranges. 0 thru 2000, 20,000 and 200,000 ohms. 0 thru 2, 20 and 2000 megohms.
- 6 direct current ranges. 0 thru 1.2, 30, 120, 300, 1200 ma. and 12 amperes.
- True vacuum tube meter in all but current functions. No low-resistance, frequency-erroneous copper oxide rectifiers.

Every good jobber features the new "VOMAX", new *super-sensitive* 905A "SPARX" Signal Tracer, 910 Universal Test Speaker & 18 Watt Universal Output Transformer, 906 FM/AM Signal Generator, new 909 and 911 TV and FM Sweep Signal Generators, 904 Resistance/Capacitance Tester. All, Laboratory Caliber Electronic Test Instruments at a price you can afford.

OVER 37 YEARS OF RADIO ENGINEERING ACHIEVEMENT

McMurdo Silver Co., Inc.

EXECUTIVE OFFICES: 1240 MAIN ST., HARTFORD 3, CONN.
FACTORY OFFICE: 1249 MAIN ST., HARTFORD 3, CONN.

So small! So light! So powerful!

... IT'S YOUR WESTINGHOUSE TONIC FOR TIRED SUMMER SALES

Here's the portable your customers have always wanted! The new Westinghouse 185 is packed with all the features your salesmen need to make sales easier—exclusive Westinghouse Plenti-power for clear-as-a-bell tone, razor-sharp sensitivity . . . smart

modern cabinet design, molded from beautiful *but tough* Burgundy-and-white plastic . . . plus a modest price customers can afford to pay. Pep up summer sales with this pint-size portable powerhouse, and let it pile up profits for you!

HOME RADIO DIVISION WESTINGHOUSE ELECTRIC CORP. SUNBURY, PA.




Radio's first name is

Westinghouse

PLANTS IN 25 CITIES OFFICES EVERYWHERE

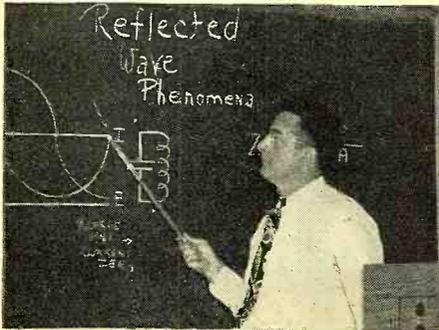NOW! FAMOUS \$500 TELEVISION COURSE YOURS WITH PHOTOFAC FOLDERS!



Mr. Albert C. W. Saunders' background includes association with the Marconi Company, teaching experience at Harvard and M.I.T.; founder Radio Technician's Guild; full member I.R.E.; Graduate, Portsmouth College, England. Mr. Saunders gave the first actual television demonstration in New England in 1935.

Famous Saunders' Course **EXCLUSIVE** in Howard W. Sams' PHOTOFAC

We have been able to prevail upon Mr. Saunders to transcribe his famous course on Television for PHOTOFAC *exclusively*. The only other way you can get this course is by paying \$500 and attending the Saunders School. *Now*—with PHOTOFAC at no extra cost to you—you can have this wonderful instruction that fits you for Television servicing!

Get Ready to Make Big Money in Television Servicing with This Practical, Successfully Proved Instruction!

NOW! AT NO EXTRA COST TO YOU—you can have the nationally-famous \$500 Saunders' Television Course! It's the world's finest training—*practical* down-to-earth training that actually prepares you for Television and keeps you 'way out ahead of the game. Here's the *first real help* in Television for Servicemen—brought to you *exclusively* by PHOTOFAC and PHOTOFAC alone! If you want to stay in Radio Servicing, you can't afford to miss a single installment of this amazing Television Course! Read every word of this announcement and then ACT!

Not Just a Book—A Complete Training Course in Television!

You get the actual \$500 Television Course, exactly as taught in the nationally-famous Saunders Radio & Electronics School at Newton, Mass. We literally bring this course to you in print—transcribed word for word from the original lectures, supplemented by graphic training aids, exclusive PHOTOFAC "exploded" views and hundreds of visual illustrations, prepared under Mr. Saunders' personal supervision. This is the *same* course attended by hundreds of established service technicians and by service personnel of leading set manufacturers—the *same* \$500 course!

First Installment Appears in PHOTOFAC Set No. 38!

The Television Course will appear in regular installments in each PHOTOFAC Folder Set, beginning with Set No. 38. Each installment will include the *right* amount of material so that you will be able to digest it easily and completely between issues. Instruction will be kept up-to-date and will include the latest information promptly as it is available on the subject. There's no need to wait now for books that will never cover the ground adequately, or to buy books that are obsolete already. Be sure to order PHOTOFAC Set No. 38 *now*—and begin to qualify yourself for Television!

PRACTICAL, CLEAR, EASY-TO-FOLLOW TELEVISION TRAINING

Experts in the field of Television and Radio training acclaim the famous Saunders Course. It is remarkable in its ability to simplify and explain the most complicated theory and practice. It describes the action of an electronic circuit so originally and simply that it can be visualized in an unforgettable manner. The Saunders Course avoids higher mathematics and engineering terminology beyond the experience of the practical man. You know where you are every step of the

way, and you bridge the gap between Radio and Television with quick, simple understanding that makes unfamiliar subjects easy to master. As you progress in the course, Television circuits will unfold and become as clear and understandable to you as the Super-heterodyne circuit. You will be able to follow and use effectively the practical servicing data on specific Television receivers prepared for you by PHOTOFAC. Get started in the Course today with PHOTOFAC Set No. 38.

Get Television Training Worth \$500—Plus Incomparable Photofact Service Data at the Cost of PHOTOFAC Alone!

Here's the chance of a lifetime that really fits you for a profitable, successful career in Television servicing. Just think of it—you get the world's finest radio service data in PHOTOFAC—at only \$1.50 per set—and at the same time you train practically and successfully for Television with the finest course available in the country—a course worth \$500.00 that *costs you nothing extra!*

DON'T MISS A SINGLE INSTALLMENT OF THIS TELEVISION COURSE! MAKE SURE YOU OWN IT ALL! GET STARTED WITH PHOTOFAC SET No. 38 TODAY . . .!

Yours! AT NO EXTRA COST

\$500 TELEVISION COURSE BEGINS IN SET No. 38. ORDER TODAY!

HOWARD W. SAMS & CO., INC.
INDIANAPOLIS 6, INDIANA

Export—Ad. Auriema—89 Broad St., New York 4, N. Y.—U. S. of America
Canada—A. C. Simmonds & Sons, 301 King St., East—Toronto, Ontario

PHOTOFAC SERVICE

"The Service that pays for itself over and over again"

Mail This Order Form to your local Parts Distributor, or to HOWARD W. SAMS & Co., Inc. 2924 E. Washington St., Indianapolis 7, Ind. My (check) (money order) for \$1.50 enclosed.

Send PHOTOFAC Folder Set No. 38, including the first installment of the famous \$500 Saunders Television Course.

Name.....

Address.....

City..... State.....



Traffic is heavy under the street, too

Surely the busiest thoroughfare in the world is a telephone cable. But it is more than "telephone"; for these thousand or more wires, carrying sound and pictures at lightning speed, are highways for many different services.

Each one of these presents its own problems to Bell Laboratories scientists and engineers: for the telephone differs from television, and television differs from a radio program. And yet they have an essential unity: they

involve transmission of alternating currents, with frequencies from zero up to several million cycles. Each calls for new thinking, new ideas, new goals of accomplishment.

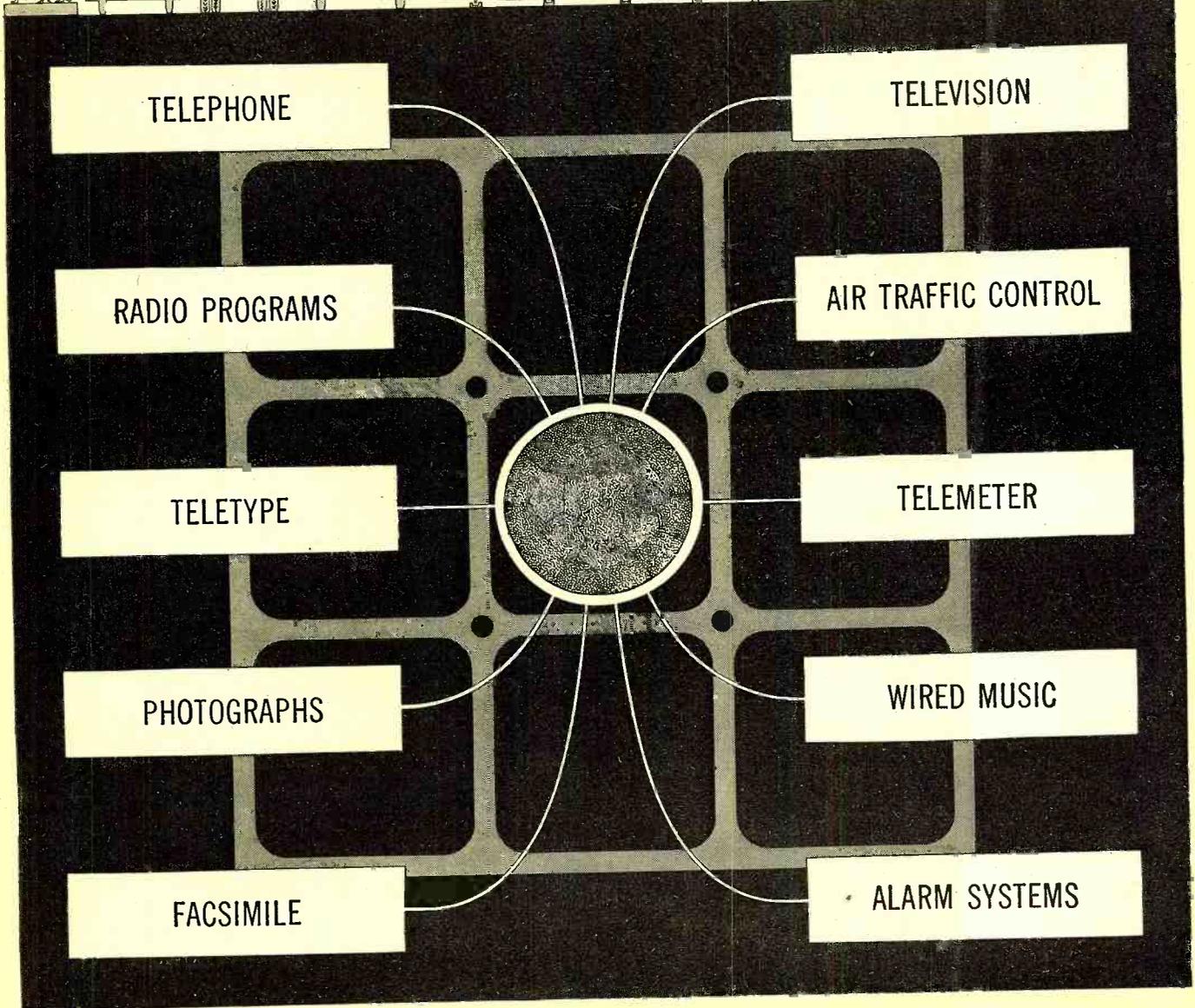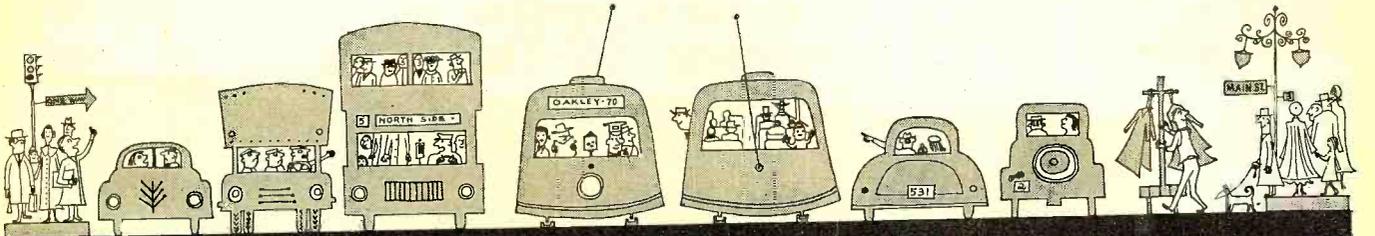The diversity of the cable's many services speaks for the unity of Bell Laboratories' purpose. That is, to know the theory of communication so thoroughly, to practice the art so skilfully, that any transmission of sight or sound can reach its destination clearly, quickly, economically.



BELL TELEPHONE LABORATORIES

Exploring and inventing, devising and perfecting for continued improvements and economies in telephone service



two *Brilliant* new stars
in the microphone world



Turner
Cardioid
MODEL 77

Impressively styled... brilliantly engineered with a combination two-element interior structure of improved design. Sound is effectively controlled to produce the true Super-Cardioid pickup pattern which reduces feedback to the minimum. The Model 77 features a wide-range pickup at the front and a sharply attenuated output at the rear... with approximately 15 db discrimination between front and rear at all frequencies. Response: ± 5 db from 70 to 10,000 c.p.s. Level: 62 db below 1 volt/dyne/sq.cm. at high impedance. Built-in switch giving 50, 200, 500 ohms, or high impedance output permits use with any standard equipment. Smooth, tilting action and quick-disconnect plug. Standard $\frac{5}{8}$ "—27 mounting. Finished in gun-metal gray and chrome. Recommended for recording studios, commercial broadcasting, and high quality public address systems.

Send for literature

Visit the Turner Exhibit at the Parts Show,
Booth 146, Stevens Hotel, Chicago
May 11-14

THE TURNER COMPANY
900 17th Street N. E., Cedar Rapids, Iowa


LICENSED UNDER U. S. PATENTS OF THE AMERICAN TELEPHONE AND TELEGRAPH COMPANY, AND WESTERN ELECTRIC COMPANY, INCORPORATED



Turner
Velocity
MODEL 87

An outstanding new microphone, developed to bring world famous Turner *dependability* to the velocity microphone field. Exceptional quality and trouble-free operation. Engineered with single element ribbon supported in high quality Alnico V magnet for maximum sensitivity. Well shielded output transformers exclude hum pickup. Bi-directional pickup pattern with smooth response within ± 5 db from 80 to 10,000 c.p.s. for most exacting studio work. Level: 62 db below 1 volt/dyne/sq.cm. at high impedance. 4-position output switch permits use with any 50, 200, 500 ohm, or high impedance input. Equipped with Universal swivel mounting, $\frac{5}{8}$ "—27 thread. Richly finished in gun-metal gray with polished chromium screen. Attached 20 ft. balanced line shielded cable. Recommended for broadcast and recording studios where highest quality performance is required.


Write for Complete Details

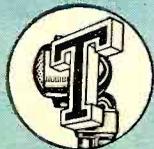

Microphones
BY TURNER

*Come and See One of the
World's Largest Displays of
Radio-Electric Components*

**PARTS SHOW
VISITORS
WELCOME!**

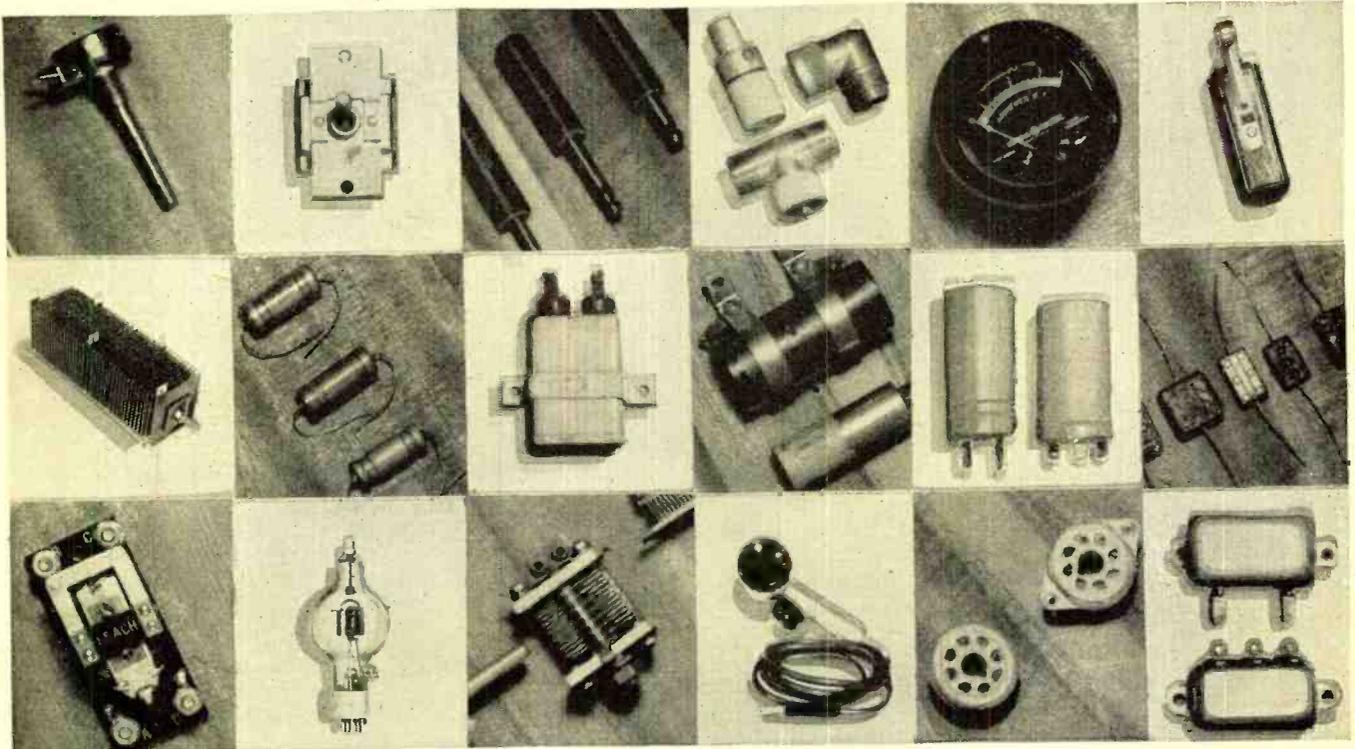

A National Service

For those who are unable to visit Chicago, Wells maintains a complete catalog service covering every item in our huge inventory. Catalogs or descriptive lists are now available in the following categories: Relays, Volume Controls, Micro Switches, Phone Jacks and Plugs, Transmitting Tubes, Condensers, Transformers, Resistors, Jones Strips, Wafer Switches, Radio Amateur Equipment, Dry Disc Rectifiers, Wire, and Coax Connectors. Send for your copies today.

Visit Wells in Chicago

Thousands of types of radio-electric parts and equipment have been assembled in one tremendous display area located within easy walking distance of Chicago's Loop. Manufacturers, distributors and radio amateurs are cordially invited to see this extraordinary selection of the best nationally known electronic components. Everything is priced at a fraction of the original cost and is backed by the substantial Wells guarantee.

Distributors: Write for the Wells 1948 Catalog


Amateurs & Mfgs.: Write for Wells Catalog H400

**WELLS
SALES, INC.**

320 N. LA SALLE ST. DEPT. R-5, CHICAGO 10, ILL.

*Six Months
from Today*

Which will YOU hold?

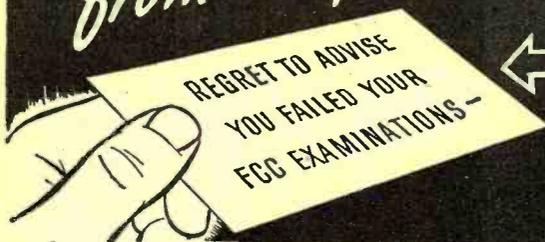

← THIS
OR THIS →



WANT YOUR FCC COMMERCIAL LICENSE IN A HURRY?

Use CIRE Training and Coaching Service—and Get Your "Ticket" in a Few Short Weeks!

Thousands of new jobs are opening up—FM, Television, Mobile Communication Systems. These are only a few of the radio fields which require licensed radio technicians and operators.

Get your license without delay. Let Cleveland Institute prepare you to pass FCC license examinations, and hold the jobs which a license entitles you to, with CIRE streamlined, post-war methods of coaching and training.

Your FCC Ticket Is Recognized in All Radio Fields as Proof of Your Technical Ability

More than ever before an FCC Commercial Operator License is a sure passport to many of the better paying jobs in this New World of Electronics.

Employers frequently give preference to the license holder, even though a license is not required for the job. Hold an FCC "ticket" and the job is yours!

Hundreds of Satisfied, Successful Students

"I have taken the first class phone license examination and received my first class ticket last Saturday, May 31. In closing I must say yours is an excellent radio course, and I really appreciate your help and the fine service you have rendered me."

Student #2876N12

"I passed the FCC examination in radiotelephone 2nd class, at Detroit on June 3rd, and I want to thank you for your ready assistance as my instructor on Section I of Nilson's Master Course."

Student #2799N12

"I have had my 1st class radiotelephone license since March of this year, and plan to continue with your course since I find it a great help in studying transmitters."

Student #2779N12

"After sending in Lesson E-9 I took the commercial operator's license examination for 2nd class radiotelephone, and passed O.K. I received the license last week."

Student #2772N1

FREE BOOKLET—Tells you the Government requirements for all classes of FCC commercial licenses. (Does not cover Amateur License examinations.) Use coupon below for Booklet B.

OTHER

Cleveland Institute Home Study Courses Offer Complete Technical Radio Training from Low-Level to College-Level, for the Radioman with Practical Experience!

COURSE A—Master Course in Radio Communication

A complete course covering the technical fundamentals of radio-electronics, for the radioman who wants a general review. Includes preparation for Broadcast station employment.

COURSE B—Advanced Course in Radio Communication Engineering

A genuine college-level radio engineering course, completely mathematical in treatment. For the advanced radioman with considerable practical experience and training.

COURSE C—Specialized Television Engineering

An advanced college-level course for the radioman who has had formal training equivalent to A and B.

These three courses in radio-electronics offer a complete, thorough technical training for radioman who wants to cover the field. Available separately or combined.

FREE CATALOG—Describes all Cleveland Institute home study courses—tells of CIRE unique, post-war methods of training. Use coupon below for Catalog A.

How To Pass
FCC
LICENSE
EXAMINATIONS

CLEVELAND INSTITUTE
OF
RADIO ELECTRONICS
Terminal Tower - Cleveland, Ohio

Don't Delay—
Write Today!

Approved for
Training
Under "G-I
Bill of Rights"

HOW TO PASS Commercial FCC LICENSE EXAMINATIONS...

CLEVELAND INSTITUTE OF RADIO ELECTRONICS
Contractors to the Canadian Broadcasting Corporation

RN-5 TERMINAL TOWER

CLEVELAND 13, OHIO

Cleveland Institute of Radio Electronics
RN-5 Terminal Tower, Cleveland 13, Ohio

Gentlemen: Please send me your Booklet B, "HOW TO PASS THE FCC COMMERCIAL LICENSE EXAMINATIONS," and information about your home study course for preparation for FCC License Examinations. (Does not cover Amateur License Examinations.)

Please send me your Catalog A, describing all of your home study radio-electronics courses.

I desire training in course A B C

Veterans check for enrollment information under G-I BILL NO OBLIGATION—NO SALESMEN.

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

Two-Way MOBILE RADIO— a new field for Servicemen



By LEO G. SANDS

Bendix Radio Division, Bendix Aviation Corp.

A review of the techniques and equipment needed to service all types of v.h.f. radio equipment.

UE to the rapid expansion of the use of two-way radio in the mobile services, a new field has been opened to the enterprising and progressive radio technician, particularly so since equipment for the 152 to 162 megacycle band has become available in large quantities.

The taxicab industry has shown a tremendous interest in two-way radio. Thousands of taxicabs throughout the country are already equipped with radio and thousands more will be so equipped in the next few months. So great has been the interest of the taxicab industry that more than a thousand taxicab companies have applied for construction permits from the Federal Communications Commission. The use of radio by taxicab operators has resulted in the elimination of countless dead miles and increased business brought about through better service to the public.

The nation's railroads are adopting

radio to provide better communication in yard and terminal operations, from cabooses-to-engine, wayside-to-train, train-to-train, and even point-to-point, to supplement existing landline communications. Many of the railroads have hired radio technicians to maintain their radio equipment while

EDITOR'S NOTE: Most manufacturers of vehicular radio equipment are advising their customers that it is up to them to make arrangements for the servicing of that equipment with local servicemen. Technicians who have the proper equipment and "know-how" are in a position to augment their incomes impressively with this new type of maintenance work.

others plan to farm out their radio work to private radio service organizations.

Very high frequency radio is being used for ship-to-shore communications in harbor operations by tugboat operators and shipyards. Municipal

police and fire department radio services are gradually shifting from the 30 to 44 megacycle band to the 152-162 megacycle v. h. f. band. Power companies and other utility services are employing v. h. f. radio to dispatch service vehicles. Ambulance operators are being licensed to use v. h. f. radio. The field is so great that the surface has barely been scratched.

Radio dispatching service is being offered in many cities under limited common carrier licenses. These operators either sell or lease mobile radio units to their subscribers or in some cases, the subscriber buys his own mobile equipment. This type of service differs from the telephone company's urban mobile telephone service in that the subscriber can talk only to the dispatch land station and does not tie in with the regular telephone system.

In the future, a very large field will be open to the radio technician, the Citizen's Radio Service. Equipment for this service is not yet available, but when it is, the response by the public should be tremendous.

There is a crying need for skilled radio technicians to install and maintain two-way radio equipment for the many users of radio. In spite of the large number of well equipped radio service organizations manned by skilled technicians, too few of these organizations have the facilities to handle the maintenance of two-way radio equipment. An opportunity exists for the progressive radio service organization to get into the two-way radio field where a continuous and worth-while income is to be had.

To get into the two-way radio field, it will be necessary for all technicians to hold either first or second class radio telephone operator's licenses, if they are to make adjustments to radio



This dispatcher at High Point, North Carolina routes Bluebird cabs quickly and efficiently with radio. The company estimates savings up to 20 per-cent have been effected by eliminating dead-mileage and savings in gas, oil, etc.

transmitters. Furthermore, these technicians will have to familiarize themselves thoroughly with the characteristics of radio at the very high frequencies.


Test equipment for two-way radio maintenance must be of higher quality and more accurately calibrated than the equipment normally used for servicing broadcast receivers. The equipment needed will include:

1. Signal generator covering v. h. f. bands.
2. Signal generator for i. f. alignment.

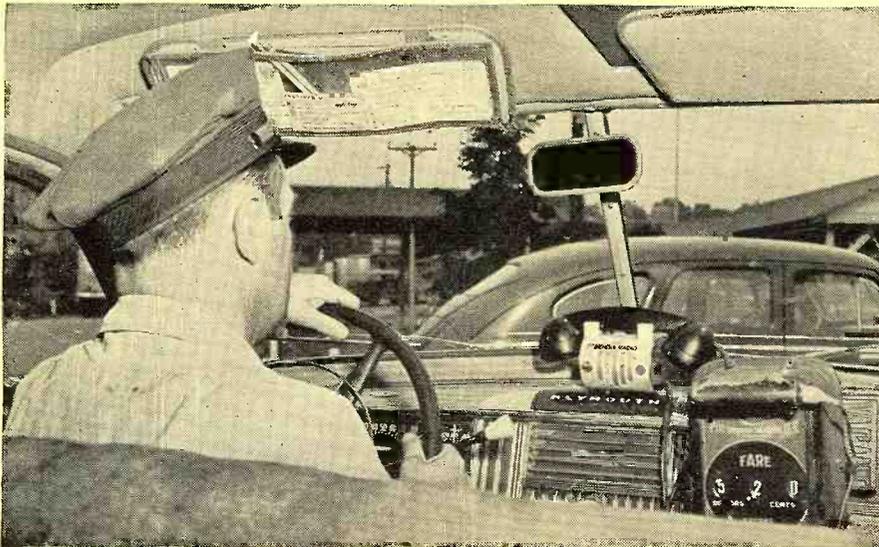3. Field strength meter.
4. Vacuum tube voltmeter.
5. Tube tester.
6. Test jigs.
7. Frequency measuring equipment to cover necessary bands.

The 152 to 162 megacycle band is the most widely used of the v. h. f. bands. A signal generator covering this frequency range, with or without frequency modulation, is an essential piece of equipment. In selecting a signal generator, one of the requirements is low signal leakage. If the attenuator or shielded case leak excessively, the

The two-way radio telephone handset is within easy reach of the driver. The "Instant Call" feature keeps unwanted noise from the loudspeaker. Only a short tone preceding the conversation is audible throughout the cab. After the driver answers the call, conversation between him and the dispatcher is localized to the receiver of the handset. Cab customers are not annoyed by the loudspeaker noises.



signal generator will be useless for sensitivity measurements.

For i. f. alignment, a signal generator covering from about 1 to 30 megacycles is required. A high degree of frequency calibration accuracy is essential unless some sort of accurate measuring device is available for checking the signal generator's output frequency. A crystal controlled signal generator is ideal or a war-surplus BC-221 frequency meter may be used as a signal generator for this purpose.

For tuning and checking performance of mobile and land station transmitters, some sort of field strength measuring device is useful. A crystal detector and microammeter attached to a dipole is quite adequate. A v. h. f. receiver may be used as a field strength meter by measuring limiter or a. v. c. voltage.

A vacuum tube voltmeter is an indispensable instrument for servicing v. h. f. equipment, particularly for i. f. and discriminator alignment. Battery operation of the meter is desirable so mobile units, when necessary, can be serviced in a vehicle. Normally, adjustments requiring a vacuum tube voltmeter should be performed on the bench.

Testing of tubes to be used in v. h. f. equipments cannot always be done with an average or even better-than-average tube tester. Substitution methods are often required unless the technician possesses a truly adequate laboratory-type tube analyzer. However, a tube tester is a time saver in rejecting really poor tubes and the tester should provide means for checking all of the new miniature types as well as many low power transmitting tubes.

To handle servicing of many mobile units of the same type, the technician should equip his shop with test jigs that will permit operation of the unit on the bench even if partially disassembled. Usually, the manufacturer of the equipment will be happy to provide information on the fabrication of test jigs for his own equipment.

Under existing FCC regulations, every radio station must have its frequency checked at regular intervals. Usually, in the urban mobile services, a frequency check is made at least once every six months. Some users of two-way radio have purchased frequency monitoring devices which will give a continuous check on carrier frequency and frequency deviation. However, the monitoring device must itself be checked against an accepted standard.

A secondary frequency standard is an expensive piece of equipment, and very few shops can afford to own one. In its stead, a frequency monitor with switch selection of desired frequencies, or a continuously tunable heterodyne type frequency meter is often used. These devices should be checked with a secondary standard which in turn is usually checked against the Bureau of Standards station WWV. Absorption type wavemeters or lecher wires

are totally unsuitable for frequency measurement in this type of service.

Experimental taxicab radio stations are required to maintain a transmitter frequency stability of 0.01%, whereas regularly licensed services above 100 megacycles are required to stay within 0.005% of their assigned frequency. This means that equipment used to measure frequencies should be accurate to at least 0.0025%. Lecher wires can usually be used to measure frequencies to within 1%, which is not anywhere near close enough.

Radio services in the 152 to 162 megacycle band employ land station transmitters with power outputs ranging from 2 to 250 watts. Power is not a measuring stick for range at v. h. f. Quite often a 10 watt station can be heard as far as a 250 watt station. The higher powered station does provide greater field strength within its service area, but at the risk of causing interference to other services. For example, a spurious emission from a 250 watt station can be considerably more annoying than a spurious emission from a 10 watt transmitter.

When coverage of the metropolitan area of a large city is required, and one 10 to 50 watt transmitter will not provide adequate coverage, one 250 watt transmitter is sometimes employed. An alternate method is to employ two or more strategically located 10 watt transmitters on the same frequency. Generally this method provides greater coverage than is obtainable with one high powered transmitter.

In two-way radio, you must be able to receive as far as you can transmit. Generally, the land station transmitter and receiver are at the same location, and employ the same antenna. Under these circumstances, a high power transmitter has very little to offer, as the associated receiver must be able to pick up signals from mobile units of relatively low power.

For large area coverage, a high power transmitter may be used with reception from the mobile units through one or more strategically located receivers connected to the control office through landlines. On the other hand, two or more lower powered transmitters may be used with a receiver at each transmitter location and all controlled from one point.

The average land station installation consists of a transmitter, receiver, and power supply, located on the roof of a tall building, or hill top, remotely controlled from a central office by means of a leased telephone line. Where the control office is situated at a good radio location, the equipment is located in the same building and the antenna is mounted on a tall pole or tower. Generally, a 65 to 85 foot unguyed telephone pole will serve as an excellent antenna mast. Steel towers, guyed or unguyed, are readily available and are widely used.

As the range of v. h. f. radio is considered to be roughly line-of-sight, the height of the land station is the most important factor in governing com-

May, 1948



Taxi driver demonstrates the small size of two-way radio telephone units. The entire unit occupies little space in trunk compartment. Note antenna stub atop cab.

munications range. Excellent communication between buildings, under bridges, and even through short tunnels, is often provided in the service area of a v. h. f. system due to the reflection characteristics of v. h. f. radio signals.

A good antenna at the land station is desirable. Many types of antenna are available, some that will afford a power gain of as much as 3.5 db. over a dipole and yet are non-directional in a horizontal plane. Vertical polarization is most commonly used in the mobile services, although experiments have proved horizontal polarization to be quite effective. Circular polariza-


tion has merit too, and is a combination of horizontal and vertical polarization.

Land station receivers are, in nearly all cases, of the crystal controlled superheterodyne type. They differ among manufacturers in circuit details. Both double and single superheterodyne circuits are widely used. One manufacturer employs a unique single superheterodyne circuit wherein the intermediate frequency is doubled in one of the limiter stages without using a second converter stage. This arrangement permits greater amplification and selectivity

(Continued on page 177)

Radio serviceman uses crystal frequency indicator to check transmitter frequencies. The most used items of test equipment for v.h.f. two-way radio installations include an r.f. signal generator, variable audio oscillator, set of absorption-type wavemeters, sensitive volt-ohm-milliammeter, secondary frequency standard, tube tester (preferably of the dynamic mutual conductance type), and a crystal frequency indicator. The latter item is a "must" since the FCC insists on "on the beam" accuracy. Also required are test harnesses designed to incorporate a voltmeter and milliammeter to give continuous indications of input voltages and current during servicing.



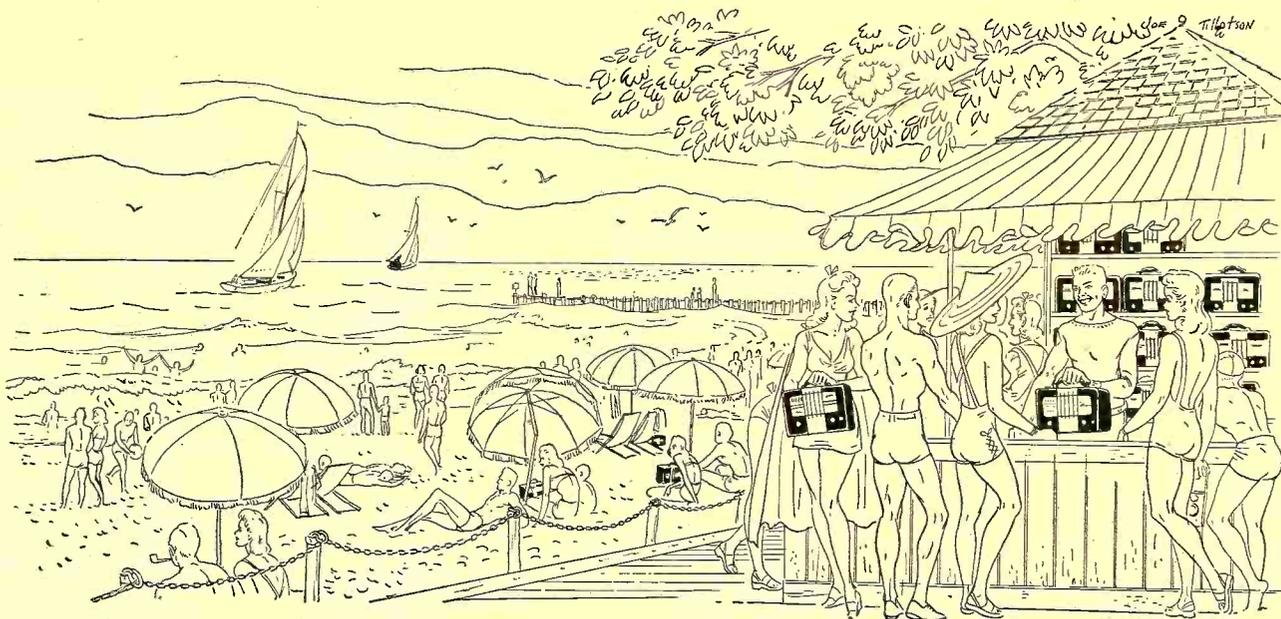

Portable Radios FOR RENT

By MAX ALTH

A good time for the vacationer can mean a big time financially for your radio shop. Why not try this money-making scheme this summer in your home town.

IF SPRING comes, can Summer be far behind? This paraphrasing of the well-known line from the poet means that soon it will be time for thinking of vacations and all forms of outdoor sports. Radio is closely linked to all forms of recreation—canoeing, sunbathing, picnicking, beach partying, etc.

For every person with a portable radio for such occasions there must be hundreds who say, "Gee, I wish I had a portable!" plus many hundreds more who exclaim, "Gee, I wish I had the money for a portable!"

Last summer Mr. Wolf of Brighton Beach, New York decided to do something about the natural affinity between radio and recreation. He hung a small sign over a card table placed in front of his store on Coney Island Avenue—the sign read "Portable Radios for Rent." All during the summer months there wasn't a sunny day during which he failed to rent every one of his portable radios at least once.

He charged thirty-five cents an hour rental with a \$1.00 fee for the minimum of three hours.

Coney Island Avenue is only one of the many streets leading to the four mile beach that often draws more than a million bathers a day. All over the country there are hundreds of other streets and highways leading to local recreation spots. Your street might be one of these.

In addition to renting portables, Mr. Wolf has derived a steady profit from the sale of these units. Many of his customers rent

portables out of curiosity—they have never heard one out-of-doors before. Since it provides them with so much pleasure—especially the ball fans who love to bury their heads in the sand and listen to the game—they make excellent prospects for the purchase of portable receivers.

Last year Mr. Wolf had to go easy on the set sales as new stock was hard to get. This year, with plenty of portables on the market, sales should provide an impressive part of the income derived from his beach business.

The sets being used for rental are the usual three-way receivers, covered in bright red or green imitation alligator and equipped with a shoulder strap. They list at \$39.50. The words "Brighton Rental" appear in large black letters across the gold speaker grille to make the sets easy to identify.

Mr. Wolf operates his business from the sidewalk because he believes that summer beach business is carnival business and the right way to operate is out in the middle of the crowd.

He keeps four or five sets on the table beside him and the rest of his stock in the store behind him. He uses no advertising other than the sign over the table and the identification on the portables he rents out. When he first started the radio rental business he had some 8 x 10 two-color throw-aways printed—and he threw them away—literally and figuratively because he received no returns that were directly traceable to the handbills. That finished that.

Mr. Wolf has an unparalleled trust in his

fellow man. He hands a radio to anyone who gives him a dollar and identifies himself by means of a driver's license, card, phone bill, etc.

Heaven is going to be filled with Brooklynites, because after six weeks of operation last summer, Mr. Wolf has yet to lose his first radio! Judging by the first six weeks, it is conceivable that the loss of radios by theft is going to be a negligible factor in the cost of running the radio rental business—in Brooklyn anyway.

True, most of us would feel a bit self-conscious walking the boards at, say, Atlantic City with a radio marked "Brighton Rental." It would be rather like punting a rowboat around Lake Onondaga marked "Property of Central Park, New York City."

Considering the other side of the coin called "faith," few people come to the beach with \$39.50 in their swimming trunks. To ask for a deposit that would cover theft—or even a five spot—would be a healthy deterrent for at least 90 per-cent of the customers.

Likewise, if time were spent in securing more positive identification, it would slow business down to a crawl. It would take an estimated 15 minutes to sign up each customer or twenty-five hours to hand out 100 sets. Fifteen minutes per customer means that a potential renter standing fourth in line would have to wait forty-five minutes before he or she received the set. People in a hurry to get on the beach just won't spend the time in line. The "Honor System" that Mr. Wolf uses takes only a minute or two and it keeps things moving.

The cost of operating this business is quite low. Mr. Wolf figures on two flashlight batteries for every eight hours' operation and one "B" battery for every two-hundred hours. At eight cents per "A" and \$1.50 for each "B," battery running time cost is approximately three cents an hour. This cost could, of course, be further reduced by using larger batteries.






Since the sets used in the rental business are new they seldom break down but when they do it is usually just a tube gone west so Mr. Wolf doesn't find it necessary to maintain a servicing department. He sends the sets out for service when more than a tube is involved. He estimates that each set will cost him less than one dollar per year, on an average, for repairs, including lost knobs, torn straps, etc.

All in all, renting radios seems like a very good "pitch" for the serviceman. You don't even need a fast line of patter!

—30—



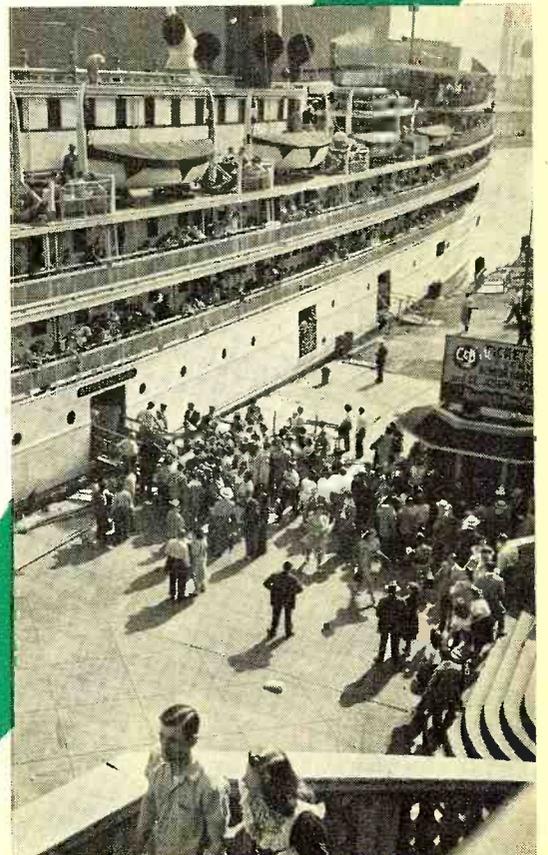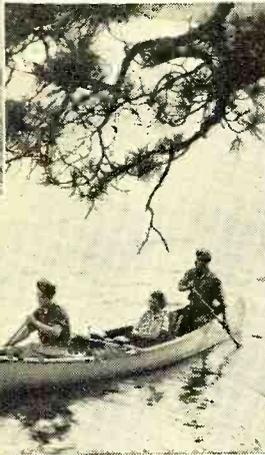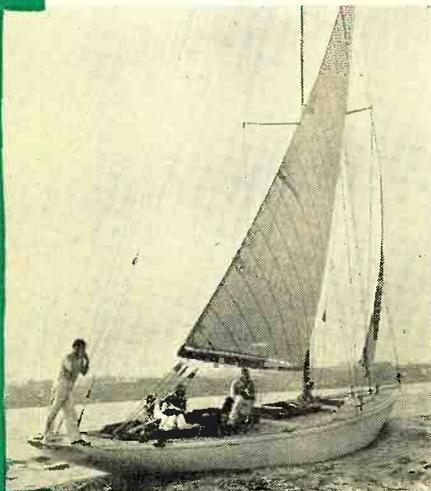Location ideas—all recreational spots are potential sites for that profitable radio rental service.



A Crystal Diode Wave Shaper

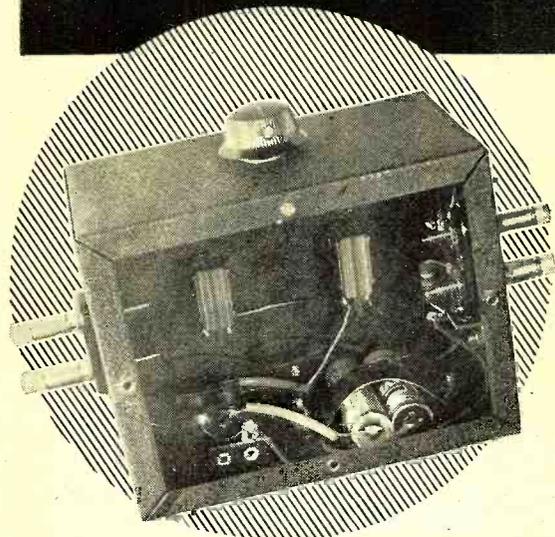


Fig. 2.

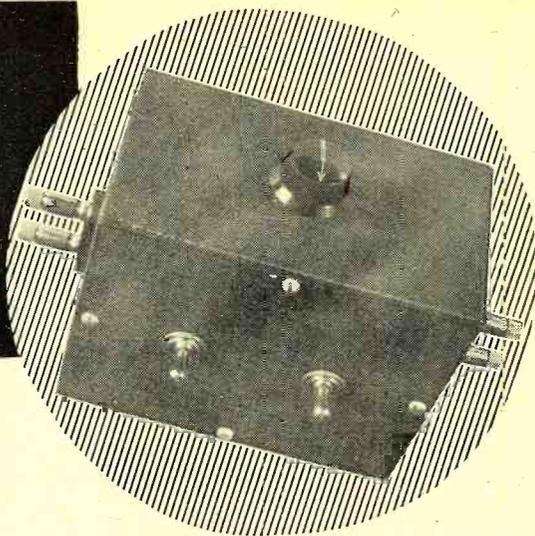


Fig. 1.

By
RUFUS P. TURNER, W1AY

This compact, tubeless test instrument will give square waves, positive pulses, or negative pulses from your audio oscillator.

A PAIR of germanium crystal diodes, a single 1 watt resistor, one wire-wound volume control-type potentiometer, two pen-size flashlight cells, two s.p.s.t. toggle switches, and two pairs of binding posts are the only parts required to build a simple, compact wave shaper. The results obtained with this little unit are good enough for most experimental purposes.

Operated from a sine wave input

signal, this shaper may be employed in experimental work, testing, and classroom demonstration as a limiter or clipper and as a source of essentially positive pulses, negative pulses, or square waves. When it is connected to the output of an audio test oscillator, the shaper will deliver square waves of controllable amplitude at the oscillator frequency. Thus, square waves for amplifier testing may be obtained with a small-sized

device employing no tubes. In the amateur radio station, the shaper will find use as a speech clipper, noise limiter for c. w. reception, and in a host of other applications requiring clipping of either positive or negative peaks, or both.

Circuit

The complete circuit diagram of the shaper is given in Fig. 3. This will be recognized as the familiar diode "slicer" circuit, so arranged that both rectifier legs may be switched-in for true slicing (peak limiting of both positive and negative half-cycles of the sinewave input signal) or one leg at a time may be switched-in for either positive or negative peak limiting.


Operation of the device is simple. A sine wave signal (See Fig. 3A) is applied to the "INPUT TERMINALS." If both switches, S_1 and S_2 , are opened, the sine wave is delivered at the "OUTPUT TERMINALS" (See Fig. 3B) and its amplitude may be adjusted by means of potentiometer R_2 .

When switch S_1 only is closed, the positive half-cycles of the sine wave input voltage cannot rise to a value higher than the voltage of cell B_1 . The positive peaks therefore level off at that voltage, but the negative half-cycles are free to increase to their maximum value. This results in the essentially negative output pulses shown in Fig. 3C.


When switch S_2 only is closed, the

(Continued on page 92)

Fig. 3. Complete wiring diagram of crystal diode wave shaper. (A) A sine wave input; (B) sine wave output, S_1 and S_2 open; (C) pulses essentially negative, S_1 closed, S_2 open; (D) pulses essentially positive, S_1 open, S_2 closed; and (E) output essentially square wave, S_1 and S_2 closed.

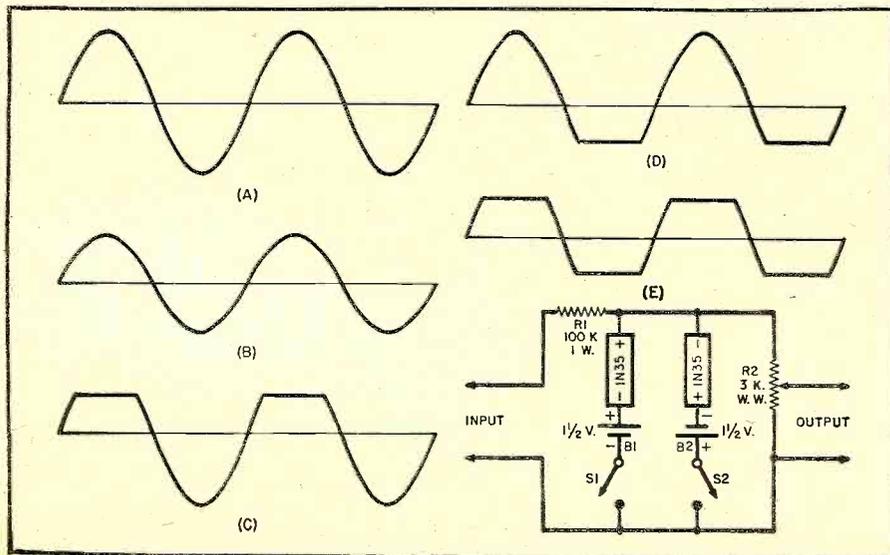

A 2-TUBE PHONO AMPLIFIER

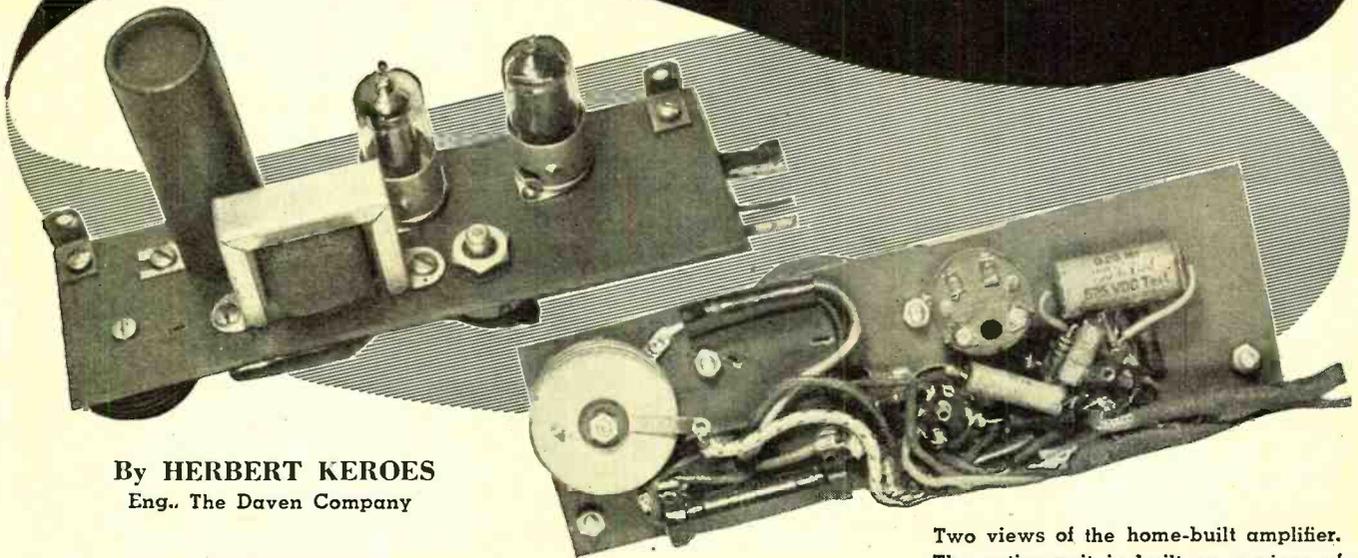

By HERBERT KEROES
Eng., The Daven Company

'A low output, easy-to-build phono amplifier that can be used with any standard type crystal pickup.


Two views of the home-built amplifier. The entire unit is built on a piece of bakelite measuring 2¼ by 6 inches.

THE amplifier to be described was built primarily to convert a record player into a self-contained phonograph for a child's use. While the maximum output is not as great as that of the usual single beam power tube

phono-amplifier, it is nevertheless entirely adequate to provide a good volume level in the average room. Several features have been included in the design that particularly suit the requirements of operation by a child.


The usual warm up period that takes place in conventional amplifiers using heater type tubes has been eliminated through the use of filament tubes and a selenium rectifier. The maximum volume level can be regulated in accordance with the wishes of the parent by means of an internally adjustable volume control. The usual external control has also been provided.

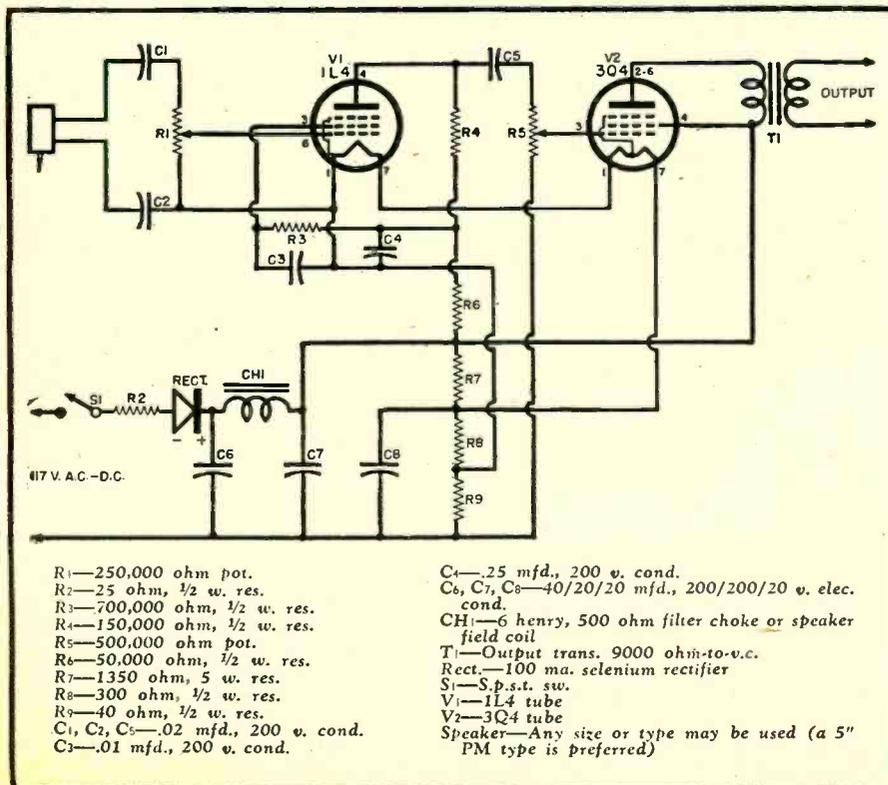Schematic diagram. Maximum power output is approximately 240 milliwatts.



A stage of voltage amplification (see diagram) using a type 1L4 tube was included, since the average crystal cartridge does not develop sufficient voltage alone to drive the 3Q4 to full output. The d.c. filtering circuit is of the inductance-capacity type and provides an extremely low hum level. A speaker field winding may be substituted for the filter choke. It will be noticed that .02 μ fd. condensers have been placed in series with each crystal pickup lead. This serves to prevent line voltage from being developed between the pickup arm and grounded objects in the room. In the diagram, the internally adjustable volume control is R_5 and the external control R_1 .

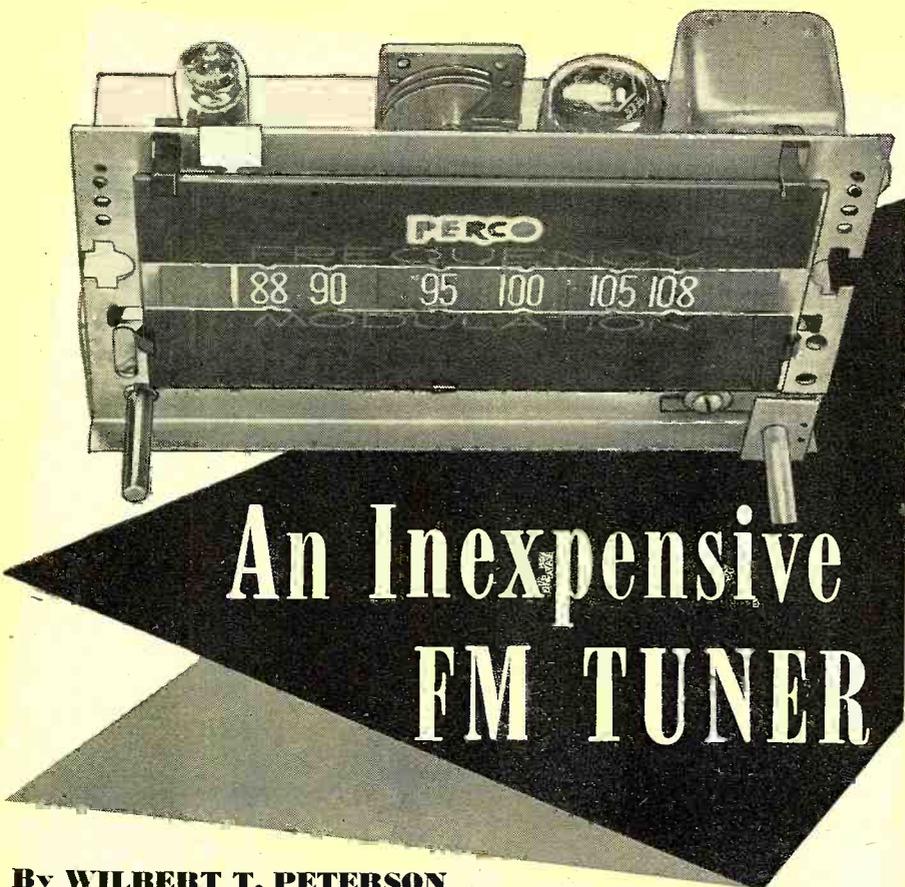The amplifier was constructed on a piece of bakelite 2¼" wide, 6" long, and 1/16" thick. The approximate location of the parts can be obtained by referring to the photographs. To further preclude the possibility of accidental shock, the amplifier was mounted within the cabinet with the back of the amplifier located closely adjacent to a side of the cabinet. Two angle clips,
(Continued on page 154)



An Inexpensive FM TUNER

By **WILBERT T. PETERSON**

Pioneer Electric & Research Corp.

**Construction details for a low-cost FM tuner
based on a relatively new circuit design.**

SINCE the advent of frequency modulation, experimenters interested in the new art have been faced with the problem of constructing, at considerable cost, a high frequency superheterodyne incorporating r.f. and i.f. stages followed by either a limiter or two and a discriminator or a ratio detector to perform the function of noise elimination and detection. As a result, the experimenter has been reluctant to spend time and money building an FM tuner or receiver when, in many cases, he lacked the facilities for properly aligning the unit when it was completed.

In addition to the increasing popularity of FM broadcasting, a new circuit¹ has made its appearance, thus stimulating new interest in the medium. This circuit makes possible the construction of an inexpensive FM tuner in a single evening by even the most inexperienced constructor. Results compare favorably with tuners costing from five to ten times as much as the components used in this unit.

The circuit utilizes a dual high frequency triode with one section performing the function of a high frequency local oscillator, while the other section serves as a converter, i.f. amplifier, and superregenerative detector. In the design of this circuit the superregeneration takes place at the i.f. frequency of 21.75 mc., thus allowing the quenching action to be adjusted for optimum performance at a single frequency and eliminating the necessity for a separate quench ampli-

tude control. This makes the operation of the detector circuit independent of antenna characteristics and reactance changes in tuning over the signal frequency band. The quench frequency is in the vicinity of 20 kc. with the waveform and amplitude determined by the resistor-condenser combination R_2C_{11} . The inherent noise rejecting features of the superregenerative detector have been retained in this circuit.

Fig. 1 shows the completed tuner, while Fig. 3 shows the bottom view with all parts and wiring in place.

The secret of the clean, professional-looking layout lies in the design of the 21.75 mc. i.f. coil assembly. All of the parts shown within the dotted lines (Fig. 2) are assembled within the shield can. The coil itself is close-wound with 12 turns of No. 30 enameled wire on a form having an o.d. of .400". This coil, L_6 in the circuit diagram, is tuned to a frequency of 21.75 mc. by means of its associated 20 $\mu\text{fd.}$ ceramic condensers (C_{12} , C_{13}) and a powdered iron core $\frac{3}{8}$ " in diameter and $\frac{1}{2}$ " long. The 2000 and 5000 $\mu\text{fd.}$ condensers (C_{11} and C_{15} respectively) associated with this coil are of the recently-announced "Hi-K" ceramic construction. Coil L_5 , the cathode injection choke, is wound on a bakelite form $\frac{7}{32}$ " in diameter. The coil consists of 100 turns of No. 36 enameled wire. There is no inductive relationship between L_5 and L_6

1. "The FreModyne FM Detector", RADIO NEWS, February, 1948.

Fig. 1. Over-all view of FM tuner. The unit is simple to build and does not require any special component parts.

despite the fact that they are mounted within the same $1\frac{3}{8}$ " x $1\frac{3}{8}$ " x 2" shield can.

The antenna primary winding, L_1 , is made of plastic insulated hookup wire and is comprised of one turn pushed between the turns of the secondary winding, L_2 . The leads from this winding are twisted together and soldered directly to the antenna connection terminals on the rear of the chassis.

Windings L_2 and L_3 consist of three and four turns of No. 16 tinned copper wire respectively. The coils are self-supporting and spacewound to an i.d. of $\frac{1}{2}$ ". The oscillator coil should be tapped 1 turn from ground end. The coils are adjusted for tracking by squeezing or spreading the turns as required. The grid choke coil, L_4 , consists of 120 turns of No. 36 enameled wire on a $\frac{7}{32}$ inch diameter form. The placement of coils L_1, L_2, L_3 , and L_4 , is clearly shown in the photograph of Fig. 3. Coils L_5 and L_6 are mounted within the i.f. can.

Coils L_2 and L_3 are soldered directly to the terminals of the two-gang 15 $\mu\text{fd.}$ variable condenser and the grounded end in each case is soldered to a terminal placed under the screw which holds the condenser in place.

Condenser C_5 can be a small 2 $\mu\text{fd.}$ ceramic unit or can, as shown in Fig. 3, be made up of two pieces of plastic insulated hookup wire twisted together for a distance of one inch and soldered into the circuit at the variable condenser terminals.

The balance of the wiring is straightforward in every respect. The location of all parts, especially those associated with the 14F8 dual triode, should follow the layout shown. The use of dummy tie lugs to mount C_7 , C_{10} , R_3 , and R_4 as well as one end of R_7 and the leads from C_{16} and C_{17} , adds to the neatness and rigidity of the wiring.

After construction has been completed and all wiring has been checked the unit is ready for test and adjustment. Before proceeding, it should be noted that the chassis is "hot" with respect to the line. Care must be exercised in connecting the unit to test equipment, amplifiers, and other equipment. It is recommended that .1 $\mu\text{fd.}$ isolating condensers be placed between the audio output terminals and the amplifier or radio to which the tuner is connected. It will also be noted that the hum level can be lowered by polarizing the line plug for minimum hum. Isolating condensers should be placed in each of the output leads.

If the i.f. transformer assembly is factory-built it is already aligned for the operating frequency and little adjustment will be required. On the other hand, a homemade coil will require alignment. Feed a 21.75 mc. amplitude modulated signal into the 14F8 grid (terminal 8) and adjust the iron core for maximum output as indicated on an output meter connected across the output of the amplifier used with the tuner.

If a signal generator having a range extending to the high frequency end of the FM band is available, it should be connected to the antenna circuit through a 300 ohm resistor and the oscillator trimmer adjusted for maximum output. The low frequency end of the band is now checked and the coil turns may be squeezed or spread, as required, to make the range agree with the dial calibration. Squeezing the coil increases the range while spreading it decreases the range. After

each coil adjustment it will be necessary to return to 108 mc. and readjust the trimmer, repeating this step as often as required. After the oscillator agrees with the dial calibrations, the r.f. coil should be adjusted in a similar manner, all the while observing maximum output indications. It will be found that a slight interlocking occurs in adjusting the r.f. coil and, as a result, the condenser should be rocked slightly during the adjusting process.

If a signal generator covering the FM band of 88-108 mc. is not available it is still possible to align the set properly by employing actual FM stations. In this case a good dipole antenna is an absolute necessity to assure reception from at least two stations—one near the high frequency end of the band, the other near the low frequency end.

The exact procedure is as follows; set the dial pointer so that its travel is an equal amount above and below the 88 and 108 mc. calibration points on the dial scale when the condenser is at its extreme maximum and minimum capacity. After setting the dial and carefully checking the wiring to make sure the converter is in operating condition a careful search of the band should be made to determine whether an FM station can be received. It may be necessary to also adjust the trimmer condenser mounted on the bottom of the gang condenser since this capacity is an appreciable part of the total circuit capacity and thus could prevent reception over the complete band. As soon as a station of known frequency is heard, the r.f. trimmer can be set for maximum signal intensity and a check made to determine if other stations can be received, adjusting the oscillator trimmer to bring the station in at approximately the correct dial reading. As soon as this is done other FM stations should be heard and we are now ready for the actual coil and trimmer adjustment.

The first circuit to be adjusted is the oscillator and this is accomplished by attempting to make the dial agree with the station frequency by means of the trimmer condenser, adjusting the trimmer while tuning to the highest frequency station received. If it is found that the dial indicates lower in frequency on a station tuned in near the low frequency end of the band, the oscillator coil is too low in inductance resulting in too small a range and the coil should be "squeezed" to increase the inductance. After each "squeeze" repeat the adjustment of the trimmer to the station on the high frequency end of the band. If, on the other hand, the station received near the low frequency end of the band comes in at high indicated frequency on the dial it is necessary to lower the coil inductance by "spreading" the turns until proper frequency coverage is obtained.

After the oscillator is made to agree with the range, the r.f. can be adjusted in the same manner for tracking with the oscillator. In this case the r.f. trimmer is adjusted to the high frequency station and a check is made to see whether the setting of the r.f. trimmer needs to be changed for the station received on the low frequency end of the band.

An outside dipole antenna should be rigged up for best reception especially in outlying districts where the receiving point may be at a relatively great distance from the FM transmitter. Although a superregenerative receiver has an inherent high sensitivity, the signal-to-noise ratio increases considerably on a weak carrier. Since slope detection is used, the signal will be found at two places

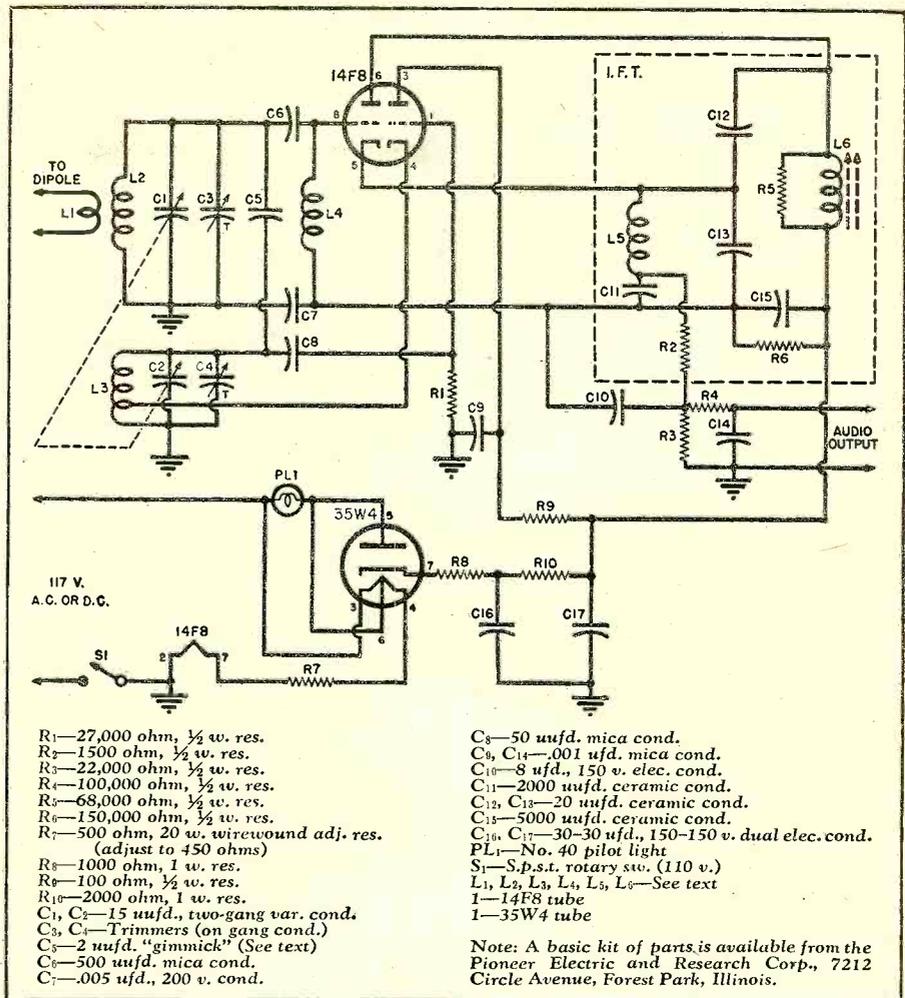


Fig. 2. Complete schematic diagram of low-cost tuner. A dual high frequency triode is used in a superregenerative superheterodyne arrangement.


on the dial. Correct tuning is accomplished not at the point of maximum quieting but on either side, preferably toward the side removed from a possible interfering carrier.

The audio output obtained from this tuner is sufficient for its use in conjunction with a conventional table or console model receiver. A pair of high impedance headphones may be connected to the audio output and the

tuner used as a complete receiver if desired. The audio fidelity, of course, cannot be expected to compare with that of the more complex FM receivers, but this tuner does bring FM reception within the range of the most meager budget in addition to providing even the novice experimenter with a simple and useful project.

—30—

Fig. 3. Bottom view shows identity of all under chassis components.

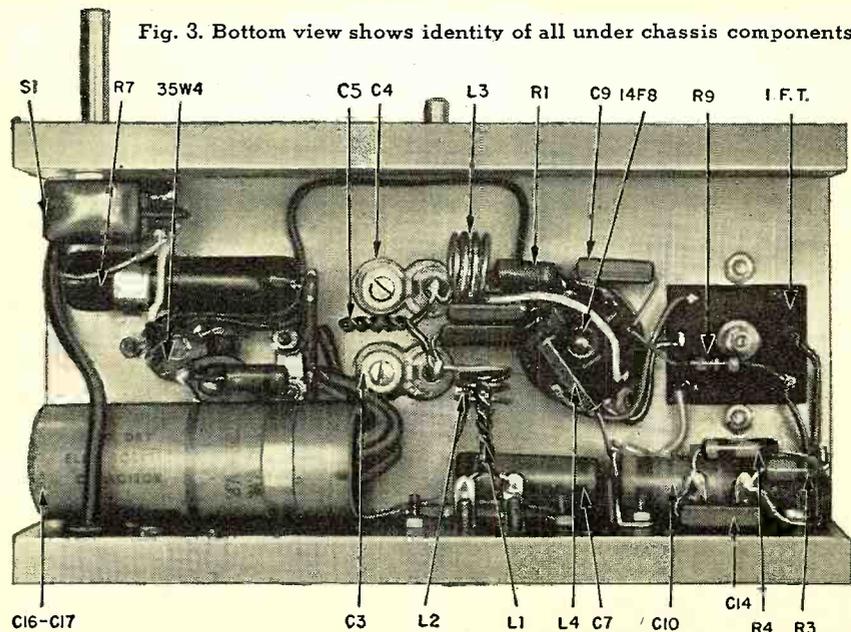

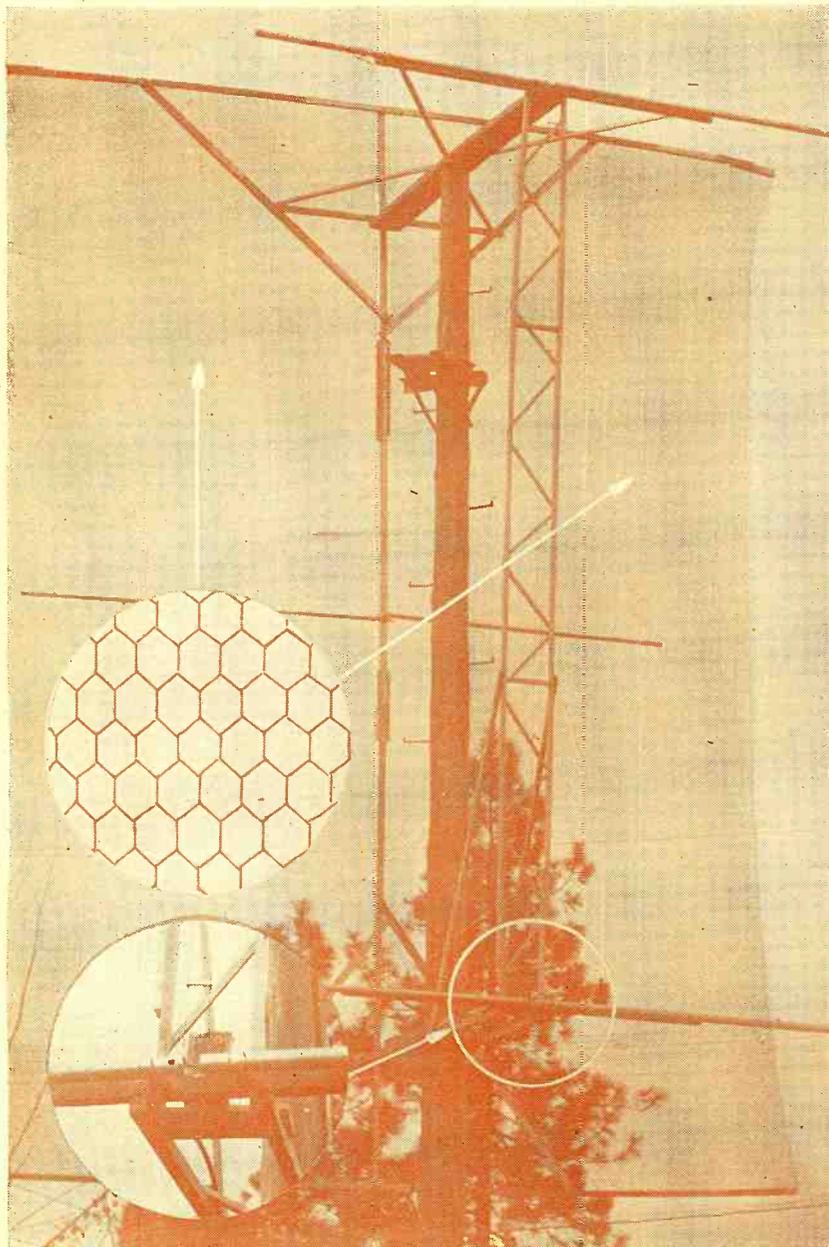


Fig. 1. Over-all view of antenna array. Ordinary chicken wire, as shown in the inset, is used for the reflector.

This is clearly shown in the picture, Fig. 1.

Such an arrangement has the following features:

1. A very low angle of radiation, necessary for DX.
2. A very excellent front-to-back ratio. This helps reception.
3. Good gain.
4. Ease of feed. Will exactly match a popular ribbon.
5. Resonant over a broad band, permitting QSY without loss of transmitter loading or excessive standing wave ratio on the feeder.
6. Low cost.

Before going into mechanical details, it is best that we devote a few lines to some basic theory which will explain the "whys" and "wherefores" of construction. In Fig. 2 (left) is shown an end view of two half-wave dipoles, A and B, excited in phase. To an observer at point p or p^1 , signals from the dipoles arriving at the same time add in phase so that addition results. At any other point, the signals will not arrive at the same instant, and will not be in phase. At any point on a line passing through both A and B, complete cancellation will result.

The vertical pattern of such a configuration is shown in Fig. 2 (center). If one radiating element is placed directly above the other and remote from ground, maximum radiation will take place along a line parallel with the earth. In other words, we will have a very low angle of radiation. This same principle is employed by those excellent performers, the Sterba Curtain and the Lazy H.

A wire screen reflector placed one quarter-wave behind the radiating elements makes the system unidirectional with a pattern somewhat like that shown in Fig. 2 (right). Due to the lack of a sky hook, the vertical pattern of the "Pigeon Catcher" has not been plotted. The actual size of the screen used is arbitrary. Sufficient size is necessary so that side lobes will not be present. A glance at Fig. 3 will show that the size actually used, 18 feet wide by 22½ feet high, is sufficient. This horizontal pattern was obtained by placing a thermogalvanometer in the center of a dipole placed about three wavelengths directly south of the beam. With enough power to cause the meter to read full scale (115 ma.) with the beam pointing towards it, radiation from the back and sides was so low that the pointer fell within the first division on the meter. Thermometers have cramped scales at the bottom and our meter had a wide pointer. It was therefore impossible to make accurate readings of the back and side lobes. It may be safely assumed that this beam has a front-to-back power ratio of 100 to 1 or 20 db.

Conventional dipoles, when used in

THE PIGEON CATCHER

By WES BELL, W7QB

A novel 29 mc. rotary beam—although massive it has a number of very desirable features.

THE "Pigeon Catcher" was so named by a local ham during an evening roundtable. His remarks were made after he had viewed the large wire screen reflector. This beam is patterned after the Signal Corps radar radiating system used to "shoot" the moon. The feed system however, is radically different. The Signal Corps SCR-270

radar antenna used 32 horizontal elements, 4 wide by 8 high, on frequencies near 100 mc. Such an array was out of the question on 28 mc. so we used only two elements. Basically the system described is nothing more than two half-waves in phase, stacked, backed up with a wire mesh reflector placed one quarter-wave behind the radiating elements.

beam antennas, exhibit a very low impedance from the parasitic elements. This low impedance is not a desirable feature for several reasons. In the first place, a very low impedance is hard to match. Secondly, the losses are higher. Power in a dipole is equal to the current squared multiplied by the resistance. This resistance comprises two parts; radiation resistance and loss resistance. These act as if in series. This may be stated as $Watts = I^2 (R_{rad} + R_{loss})$. Assuming a power of 300 watts, it can be seen that I^2 equals 75 in the case of a 4 ohm antenna and equals 1 in a 300 ohm antenna. If R_{loss} is .1 ohm in each case, it follows that 7.5 watts will be wasted in a 4 ohm dipole against 1 watt in a 300 ohm system. This is an improvement of 75 to 1 or 18.75 db. more r.f. will be wasted in a low impedance dipole than in a high impedance one if we assume that the dielectric losses do not go up. If the feed point impedance is not made too high, there is no need to worry about this. Folded dipoles provide a means of raising the feed point impedance and may well be used with the arrangement described here. However, we did something else to arrive at the same result.

Each dipole consists of two radiating sleeves of 2 inch o.d. dural. Each sleeve is shorter than a quarter-wave and the two are placed end-to-end with a two inch space between. This is the same as placing the radiation resistance in series with a condenser. See Fig 4A

A section of 1/4 inch copper tubing is inserted in each sleeve and shorted to the wall at a distance of 40 inches each side of center. See Fig. 4B This 40 inch section of rigid coaxial line acts like an inductance, and the two in series (each side of center) make up an inductance that parallel resonates with the series combination of C and R_r . By this means, the feed point impedance of the dipole is raised considerably. The impedance of one of these dipoles placed at sawhorse height above ground, was measured and found to be 1160 ohms. Paralleling a second dipole and adding a reflector brought the impedance down to 300 ohms. A perfect match for a popular cable!

A crossover is necessary in the line connecting the upper and lower dipoles, because a half-wave line reverses the phase, and we want the radiator to operate in phase. This line may be of any characteristic impedance because a half-wave line repeats the load. In other words, a resistance at one end is not changed in magnitude when viewed at the other end. We used #14 wire spaced two inches. This line is a full half-wave long ($Lft = 492/Fmc.$) and is not shortened to compensate for end effect as is done with antennas. The lengths shown are for 29 mc. The length of the inductive section for other frequencies can be computed from the following formula: $Linches = 1131/Fmc.$ This is the length of inner conductor for each side. The gap between halves is not included. The length of the radiating sleeves is found

May, 1948

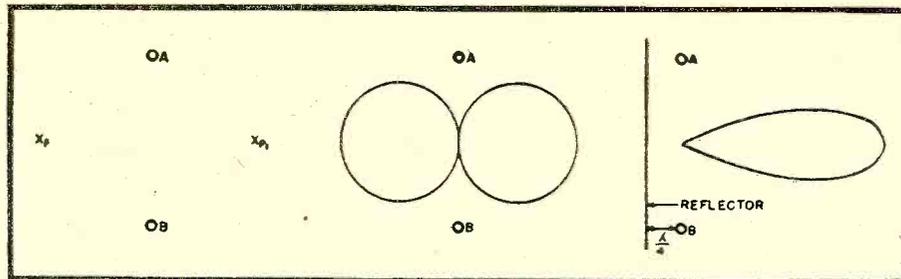


Fig. 2. (Left) Assuming that two half-wave dipoles, A and B, are excited in-phase, the signals emitted would arrive in-phase at points X_p and X_{p1} . (Center) Shows vertical pattern of antenna array (Right) Shows uni-directional pattern of antenna obtained with wire screen reflector placed one-quarter wave behind the radiating elements.

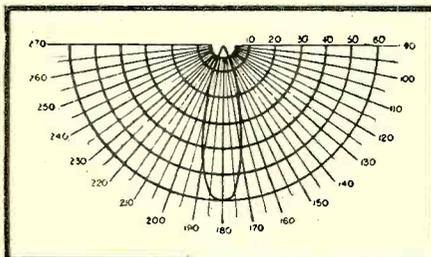


Fig. 3. Antenna field pattern at 29 mc. The dipoles were center-spaced with a current squared galvanometer indicator. Readings shown are proportional to the power

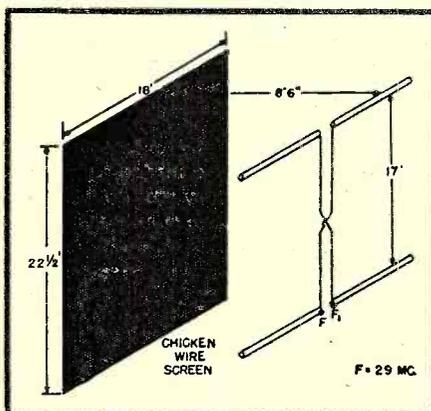


Fig. 5. Mechanical details of antenna.

from $Linches = 2015.5/Fmc$ This is the length for each sleeve. Two are required per dipole. These formulas hold for 1 1/8 inch i.d. tubing only.

The copper tubing is spaced inside the 2 inch dural tubing by means of lucite discs held in place by bushings obtained from worn out volume controls. The nut that originally held the control to the


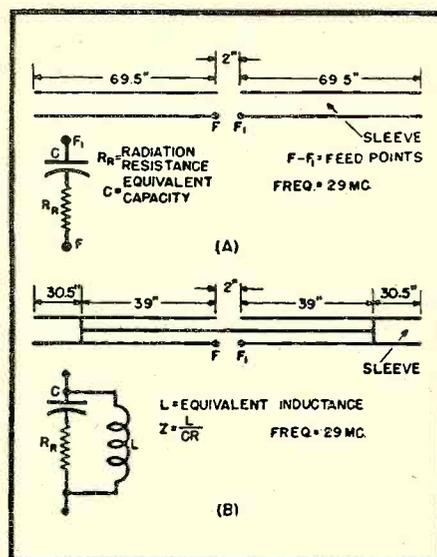
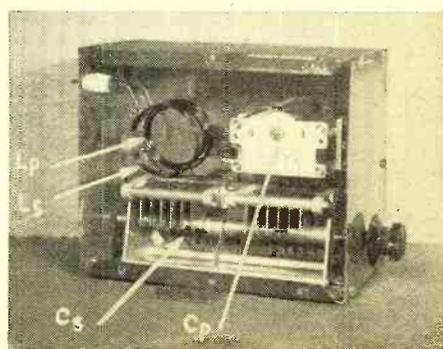


Fig. 4. Each dipole consists of two radiating sleeves which are placed end-to-end with a two inch space between. The effect, as shown by the equivalent circuit, is the same as placing the radiation resistance in series with a condenser. (B) A section of one-quarter inch copper tubing is inserted in each sleeve and shorted to the wall at a distance of 40 inches each side of center. As shown by the equivalent circuit, the entire assembly appears as an inductance in parallel with a series combination of resistance and capacity

panel is used to hold the disc, and the bushings themselves are soldered to the tubing at about 12 inch intervals. Some volume control cases are made of bakelite and a blow with a hammer will break the bushing loose. Warning: Do not attempt to solder the bushing with the disc in place as lucite softens under heat. The shorting bar at each end of

Fig. 6. Front and rear views of coupling unit used in conjunction with antenna array.

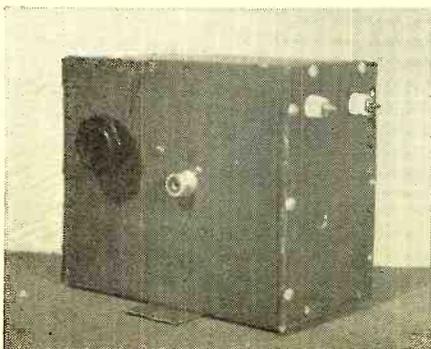

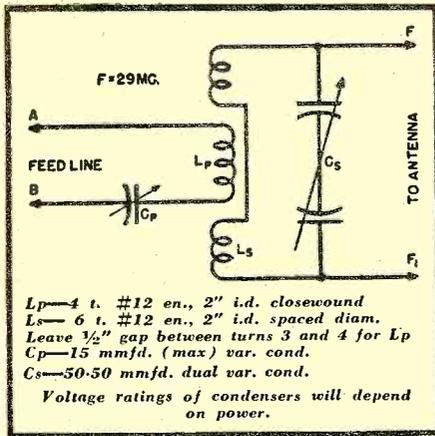


Fig. 7. Circuit diagram of coupler unit suitable for 1 kilowatt operation at 29 mc.


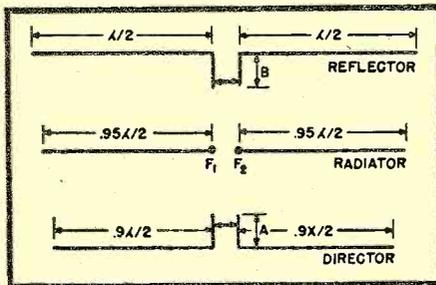


Fig. 8. Twin three-beam antenna array. Adjust sliding bars for maximum gain or best front-to-back ratio as you desire. Distance (A) from shorting bar to director will probably be somewhat less than a quarter wave. Distance (B) from shorting bar to reflector will be a little more than a quarter wave. A wide spacing between elements is generally preferred. Antenna coupler should be connected to the feed points, indicated as F_1 and F_2 .

the inner conductor is made of phosphor bronze with bent lips that firmly bear against the inner surface of the radiating sleeve. These, too, are held in place with old volume control bushings. The dipoles themselves are supported from a 6 foot piece of 2 x 2 using two insulators each side of center. Full dimensions of all parts of the complete 29 mc. antenna are shown in Figs. 4B and 5. The reader is left to figure out his own frame

Fig. 9. Preferred method of connecting coupler to various types of antenna arrays.

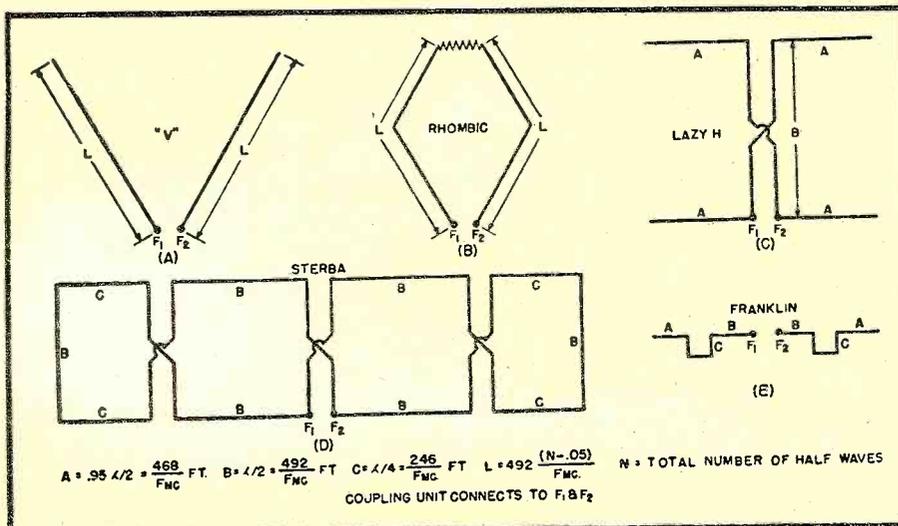

work and means of rotation. The screen support pictured used only 2 x 2 material and withstood some very heavy winds. However, every ham has his own ideas on the subject.

The Coupling Unit

The coupling unit used with the "Pigeon Catcher" has the following points in its favor:

1. Extreme ease of adjustment.
2. Low cost.
3. Simple to construct.
4. Will tune out reactance due to improper length of radiating elements.
5. Provides a means of connecting a balanced load to an unbalanced line.
6. Small in size and low in weight.
7. Will provide an exact impedance match between any line and any load of 300 or more ohms. (Can be modified to match a lower load impedance but design becomes difficult as will be seen.)
8. Provides a means for using the popular RG cables to feed rhombic, V, Lazy H, Sterba, Franklin, and similar beams.

A coupler unit suitable for a full kilowatt is shown in Fig. 6. The physical size and electrical ratings of components can be considerably reduced for use with low power. Circuit values are shown in Fig. 7.

This article is of the practical type, however those who are interested in the mathematics and theory will find the following data of value. In coupled circuits, the condition for maximum energy (impedance match) is expressed as $K_0 = 1/\sqrt{Q_p Q_s}$ where K_0 is the coefficient of coupling, Q_p is the "Q" or figure of merit of the primary circuit, and Q_s the same for the secondary circuit. In our case the primary is a series resonant circuit with a "Q" equal to $1/wCR$. The larger the inductance and smaller the capacity, the higher the Q. The secondary of this coupler is a parallel resonant circuit with a Q numerically equal to

wCR . The larger the capacity, the higher the "Q". Setting C_p to 5 mmfd. and C_s to 50 mmfd. with resistances of 72 and 300 ohms respectively, gives a required coefficient of coupling of .16. This value is easily obtained in practice.

From the foregoing, it can be seen that adjustment of the coupling between primary and secondary will provide a means of matching impedance. It is much simpler to slide a link in and out of a coil than to adjust a T-match or to cut and prune a quarter-wave matching section. Condensers are capable of more precise adjustment too, so that residual reactance will not cause trouble. It is not necessary to make any calculations to construct such a coupler or to put it into operation. The auxiliary equipment needed consists of a standing wave indicator and a low power source of r.f. energy. Your transmitter may provide the latter if you can reduce the coupling to the final sufficiently.

In most cases, a split stator condenser has been found necessary for C_s . A single ended condenser causes a slight unbalance and one terminal becomes "hotter" than the other. The effective C_s then is, of course, one half of the capacity-per-section. With power of up to 75 watts or so, ordinary receiver spacing is sufficient for both C_p and C_s .

To adjust this coupling unit, connect the antenna across C_s and the feed line in series with the primary. Insert the standing wave meter in the feed line, then adjust C_p and C_s for minimum standing wave ratio (SWR). If the SWR does not go down to almost 1, adjust the coupling between L_p and L_s . High antenna impedances will require less coupling than those of low impedance. If tighter coupling is indicated with the link (L_p) all the way in, it will be necessary to use smaller C_p and larger L_p , larger C_s and smaller L_s , or to tap down equal amounts from each end of L_s .

It is best to insert the SWR meter at the transmitter end of the feed line, because slight discontinuities introduced at the antenna end may give erroneous readings. In this case it will be necessary to keep one man at the transmitter end to read and relay the SWR readings while you adjust the coupler. Make certain that both primary and secondary circuits will tune to resonance before connecting the antenna. If the antenna is too long, less C_s will be needed; whereas if it is too short more C_s will be required. If minimum SWR is obtained with C_s fully in or out, adjust the length of the antenna elements accordingly.

With a flat line, your transmitter may not load as well as you feel it should. Flat lines require rather tight coupling at the transmitter end. It may even be necessary to resort to series or parallel tuning to the transmitter link. This is permissible and will not affect the SWR.

To feed rhombic, V, Sterba, Franklin, Lazy H, and similar systems, connect the coupler at a voltage loop near the center of the array. Suggested spots (Continued on page 132)



Fig. 1. All adjustments are on front panel. The desired frequency is obtained by plugging proper crystal into the socket on the front panel.

By J. BANN

Eng., Premier Crystal Laboratories, Inc.

Although commercially built, this generator can be easily duplicated at home or in the shop.

SEVERAL interesting features have been embodied in one newly developed quartz crystal controlled miniature signal generator. In addition to possessing the well-known precision characteristics and stability of quartz crystals the instrument is compact, portable, light weight, flexible in its applications, and extremely simple to operate.

The "Crystal Controlled Mini-Signal Generator" was developed by Premier Crystal Laboratories, Inc. of New York City. It may be used with crystals that can be plugged into a front panel socket for frequencies from 100 kc. up to well over 12 mc. Harmonics of these frequencies are useful into the v.h.f. region. No tuning is required to set the oscillator up at any frequency for which a crystal is available. A panel adjustment is provided to make small frequency corrections when the generator is used as a standard of frequency. The standard 100 kc. crystal supplied with the unit can be adjusted in this way to zero beat at the crystal fundamental or any harmonic with standard frequency transmissions of WWV or a secondary standard of frequency. This enables the operator to use the crystal harmonics as standard frequency markers throughout the radio spectrum (up to 30 mc.), with sensitive detecting equipment. If the same results are desired at higher frequencies (up to the upper limits of the television bands) this can be achieved by the use of crystals at a higher fundamental fre-

(Continued on page 180)

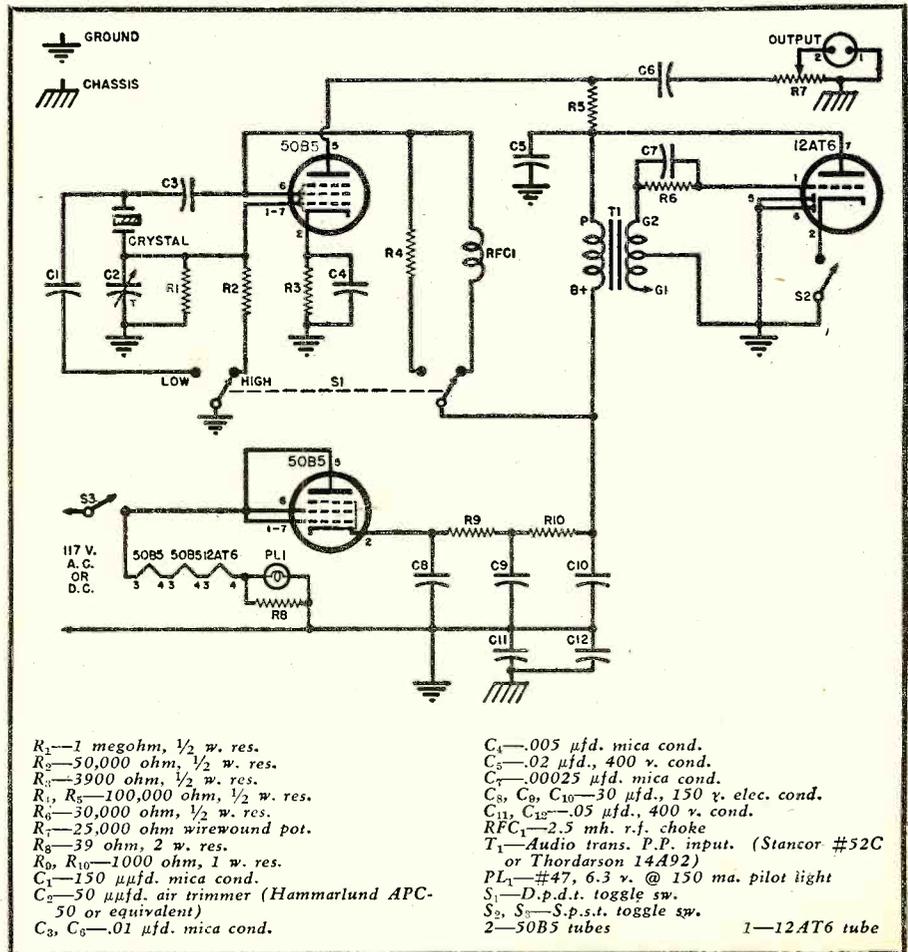


Fig. 2 Schematic diagram of signal generator. The standard 100 kc. crystal can be adjusted to zero beat with WWV. The harmonics can then serve as accurate frequency markers throughout the radio spectrum.

A Television Oscilloscope

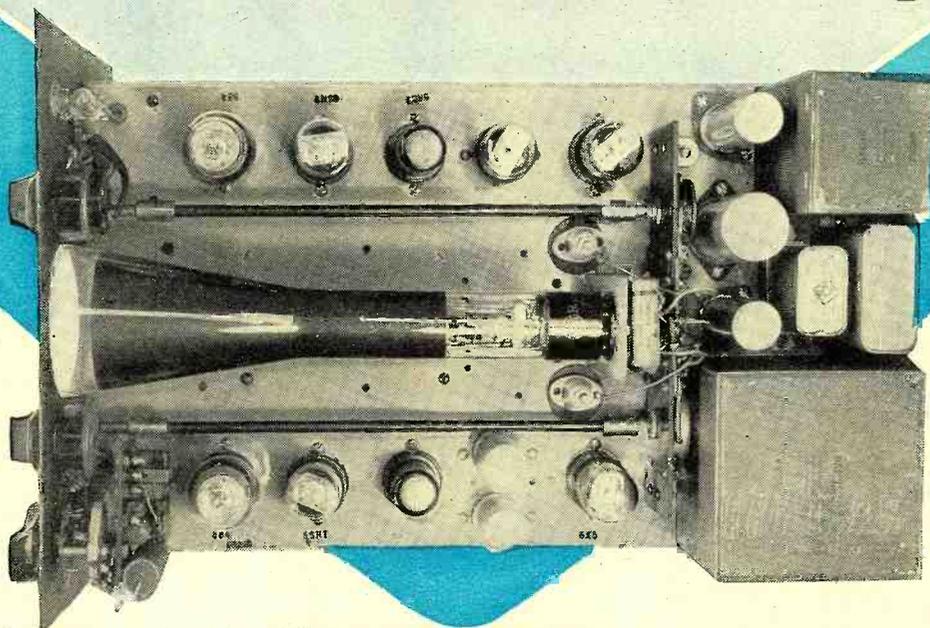


Fig. 1. Top view of completed scope. To actually view television pictures the instrument must be preceded by the necessary r.f., i.f., and video stages.

By
L. H. VanARSDALE, JR.

Part 2. Concluding article on the construction of a TV oscilloscope. This test instrument can also be used as part of a television receiver.

IN the first installment of this series presented in last month's issue, the various requirements for an oscilloscope suitable for general television use were discussed, and some circuits were given illustrating these various points. The reader may have found such a technical essay a bit dry, but understanding the engineering basis for a piece of electronic equipment makes its construction and use considerably more enjoyable and satisfactory.

This second installment describes an instrument designed around the previously outlined principles. This instrument is suitable for observing, with excellent fidelity, the various waveforms found in television receiving equipment. It will also serve all the more common test functions for audio equipment; and—most appealing to the television newcomer—the instrument may be used to actually view television pictures when preceded by the necessary r.f., i.f., and video stages!

Figs. 1, 3, and 7 show the top, panel, and bottom views of the complete Television Oscilloscope. The instrument utilizes ten tubes including the 3-inch cathode-ray tube. Three tubes are required for the various power supplies; two tubes are used in each of the two de-

flection amplifiers; one gas triode tube is used in each of the two saw-tooth scanning oscillators.

Circuit Details

Fig. 2 shows a block diagram of the complete circuit, and Fig. 4 is the circuit diagram. It will be found helpful in studying the circuit to refer occasionally to the block diagram in order to keep the relationship between the various parts of the circuit in mind. The heart of the instrument is the 3-inch cathode-ray tube. This size was chosen as it gives a comfortable viewing area, yet permits the instrument to be conveniently portable.

A brief study of the circuit will reveal that the instrument is entirely straightforward. The only unfamiliar circuit is that of the power supply, which makes use of a voltage tripling arrangement to supply the high voltage to the cathode-ray tube; and a voltage doubler, which is a part of the voltage tripler, to supply all other d.c. voltages for the set. By such an arrangement, standard receiving type rectifier tubes may be used. All voltages aside from the 2.5 volts for the cathode-ray tube filament, including the 1200 volts for the cathode-ray tube anode, may be supplied from a

standard 70 ma. power transformer having approximately 375 volts each side of center tap.

While discussing this power supply, one possible change should be noted. The transformer shown in this instrument is one of the "war surplus" variety and happened to have two 6.3 volt filament windings instead of the usual one 6.3 volt and one 5 volt windings. As a result, V_{10} , which is the only tube supplied by the second filament winding, was chosen as a 6X5. However, if this second filament winding is for 5 volt tubes, V_{10} should be changed to a 5W4, 5Z4, etc.

V_{10} and V_{11} are connected as voltage doublers and supply plus 775 volts to the amplifier and oscillator stages. This supply must be very well filtered since the slightest ripple will show up as an annoying "wobble" of any pattern or picture being observed. The 40 μ fd. electrolytic condensers used in this supply must have 450 volt ratings so that the two series groups will withstand the 775 volts without difficulty. The resistors shunting these condensers are important as they equalize the voltage drop across each of the two condensers in series.

V_{12} is the third tube making up the voltage tripler supplying the cathode-ray tube. The 425 volt output of this part of the circuit is poled with the plus grounded and the minus hot. This minus lead is connected to the grid-cathode end of the high voltage divider, placing the cathode-ray tube grid and cathode approximately 425 volts below ground, and the second anode about 775

volts above ground, thus making a total of 1200 volts supplying this tube.

The usual four controls for the cathode-ray tube; Intensity (R_{34}), Focus (R_{32}), Horizontal Centering (R_{24}), and Vertical Centering (R_{25})—are to be found in the voltage divider associated with the cathode-ray tube which connects across the 1200 volt supply. Sufficient centering adjustment has been provided to permit moving the pattern the full screen width both horizontally and vertically.

The "Input Selector" switches, S_1 and S_3 , for both amplifiers have three positions and determine what is fed to the respective channels. The first position, which occurs when the knob points to the gain mark, connects the "H. Amp-In" jack directly to the grid of the cathode follower, which is the first tube in each deflection amplifier. In this position, inputs up to 20 volts peak-to-peak may be viewed. In the "Low" gain position of the "Input Selector", the input terminal is connected to the cathode follower grid through a 10 to 1 attenuator permitting observation of voltages up to 200 volts peak-to-peak. Voltages larger than this latter value may be observed either by connecting directly to the deflection plates as provided for at the rear of the chassis, or by adding an external attenuator at the input jack. Most waveforms to be observed in television and audio work, however, fall within the input limits provided.

In the "Scan" position of the "Horiz. Input Selector" and "Vert. Input Selector" switches, the 775 volts d.c. is applied to the scanning oscillators, and the outputs of the oscillators are, in turn, connected to the inputs of the deflection amplifiers through attenuators. The saw-tooth-shaped output voltage from a gas triode scanning oscillator, such as used in this instrument, is considerably in excess of what is required by the amplifier, hence the output attenuator is included to reduce this voltage to a more usable value. Details of the attenuators for both the "Low" and "Scan" positions were given in Part 1. It will be recalled that the purpose in the arrangement of condensers and resistors is to keep the amount of attenuation constant at all frequencies and thus prevent any frequency discrimination in this part of the circuit.

The circuits for the scanning oscillators also follow the description given previously. It will be noted that minor differences do, however, exist between the horizontal oscillator, V_1 , and the vertical oscillator, V_6 . These differences are in the "Horizontal Scan Frequency" selector switch, S_4 , and the variable cathode bias adjustment, R_7 , provided in the horizontal oscillator, neither of which are required for the vertical oscil-

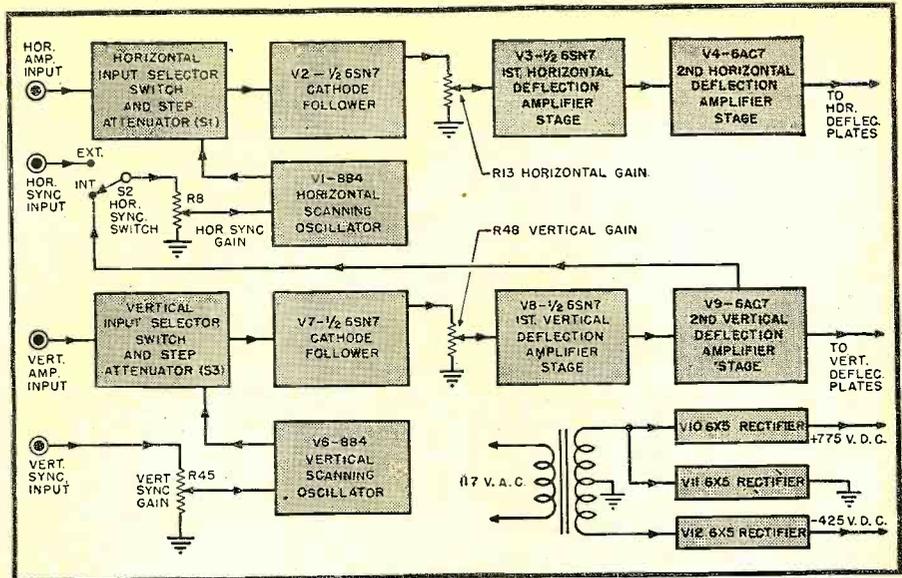


Fig. 2. Simplified block diagram shows functional operation of TV oscilloscope.

lator. This arises from the fact that the vertical scanning oscillator is intended to operate over only one range of 25 to 60 cycles, while the horizontal oscillator must operate from 20 to 20,000 cycles.


The vertical oscillator is required only when the oscilloscope is used to observe actual television pictures. It will operate at 30 cycles per second, the frame frequency for 120 line amateur-standard television pictures, and at 60 cycles per second, the field frequency for 525 line commercial standard television pictures. It will be noticed that the vertical scanning oscillator may be synchronized from an external source only, while a switch, S_2 , is provided so the horizontal oscillator may be synchronized either internally or externally. Selecting the

exact value of R_{44} requires special care, and is discussed under the heading of "Testing and Adjustments."

The cathode resistor, R_7 , for V_1 has been made variable so that the tube's oscillations may be made to coincide with the panel markings adjacent to the "Horizontal Scan Frequency" switch, S_4 . R_7 is located on the chassis, inside the instrument, directly under the group of condensers mounted on S_4 . The 25 μ fd. cathode condensers, C_7 and C_{35} , are required to maintain the bias on the scanning oscillator tubes constant during their ionized periods, i.e., during the return traces.

Both the horizontal and vertical deflection amplifiers have been made identical for the purpose of simplifying the

Fig. 3. Front panel view showing proper placement of all operating controls.

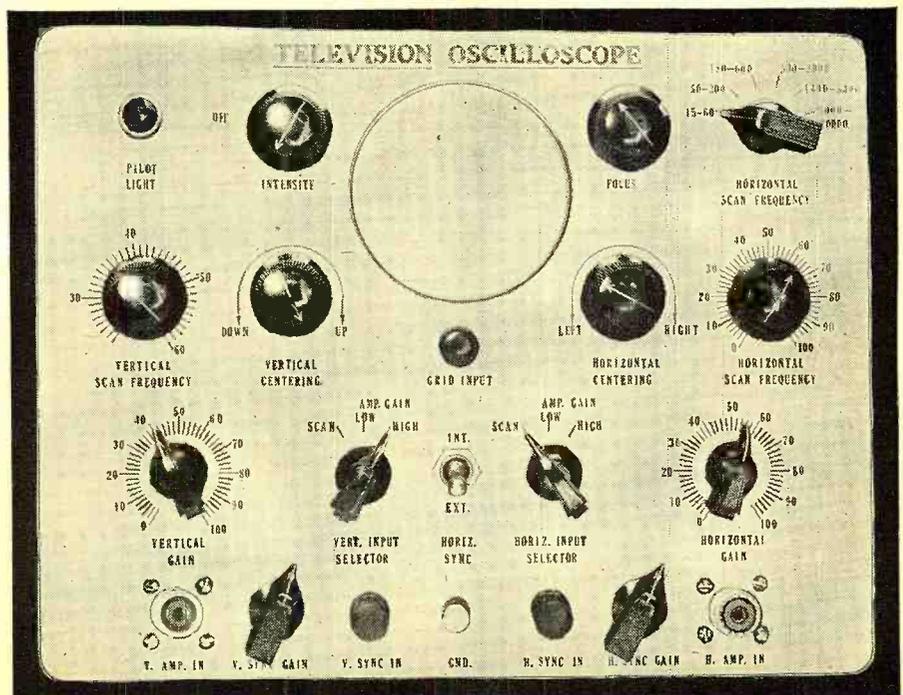

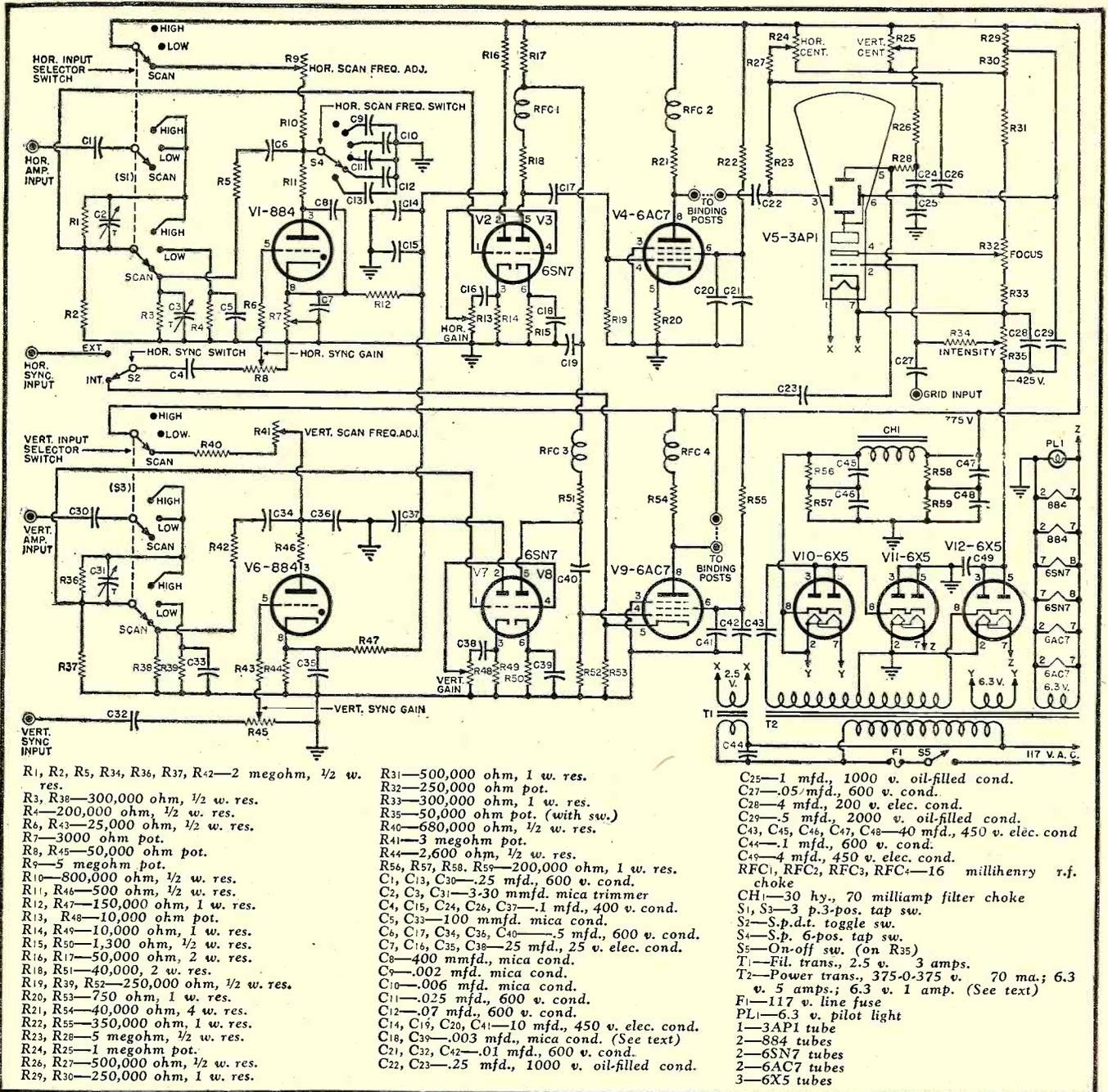


Fig. 4. Complete schematic diagram of the television oscilloscope.

construction and design, and because of the added fact that the circuit requirements are nearly the same. The complete horizontal amplifier, for example, consists of the "Horiz. Input Selector" switch, S_1 , the $\frac{1}{2}$ 6SN7 cathode follower triode, V_2 , and two stages of amplification made up of the $\frac{1}{2}$ 6SN7 triode, V_3 , and the 6AC7 pentode, V_4 . Voltages to be observed on the cathode-ray tube screen are fed from the "Horiz. Input Selector" switch to the cathode follower, V_2 . This tube is provided with a variable output control permitting fine adjustment of the pattern size. From this control the signal is then fed through the two-stage wideband deflection amplifier and applied to the deflection plate.

The two stages of amplification have

been designed in accordance with the procedure described in the previous installment to have a substantially flat frequency response from 20 to 200,000 cycles with an available gain in excess of 150. This wide frequency range is achieved by utilizing smaller-than-usual plate load resistors (40,000 ohms) and placing in series with these resistors an inductance which will further assist in keeping the gain constant at higher frequencies. The small cathode bypass condensers, C_{18} and C_{39} , also aid the high frequency response. Incidentally, it was through coincidence that the values for the plate load resistors and peaking chokes for the first and second amplifier stages calculated to approximately the same value.

One other important feature of the deflection amplifiers should be noted at this point. Inspection of the circuit in Fig. 4 will reveal that the cathode resistors of both output deflection amplifier tubes, V_4 and V_9 , have been left unbypassed. This connection introduces a considerable loss in gain per stage when compared to a circuit having a large cathode bypass condenser, but it has advantages which far outweigh these losses.

Two principal effects are achieved. First, any tendency toward non-linear distortion in the stage is corrected, and second, peak-to-peak output voltages in excess of 60% of the available d.c. high voltage may be obtained without appreciable distortion. This latter feature is

of particular importance, since it permits deflections in excess of $1\frac{1}{2}$ times the cathode-ray tube screen width to be utilized, when required. Two other minor benefits are also achieved, namely, the flatness of the frequency response is assisted, and no care is required in selecting amplifier tubes, since the degeneration permits any good tube to operate equally well.

While small condensers, C_{18} and C_{39} , have been connected across the cathode resistors, R_{15} and R_{50} , of the two triode amplifiers, these stages, too, may be considered degenerative for all but the higher frequencies around 200 kc., since these cathode condensers are only effective at these frequencies. Their primary function is to assist in maintaining the high-frequency response of the amplifier, and their use is discussed more fully under "Testing and Adjustment."

Construction

This complete oscilloscope is built on a steel chassis measuring 10" wide x 17" deep x 4" high. The etched front panel measures $11\frac{1}{2}$ " x 9". All power supply components have been grouped at the rear of the chassis to isolate them as much as possible from the cathode-ray tube and associated circuits which occupy the front. The etched metal nameplate making up the front panel, shown in Fig. 3, was used since the multiplicity of controls makes memorizing difficult. It will be noted, however, that the controls have been laid out in accordance with a definite system, since all horizontal controls fall to the left of center while all vertical controls are to the right. In addition, the position of the various horizontal and vertical controls which perform similar functions have been arranged in complementary panel positions.

For those not having had previous experience in the construction of equipment utilizing cathode-ray tubes, it is suggested that the construction procedure be followed in the order given. By so doing, an instrument of this type becomes "self-checking", i.e., the proper performance of the circuits may be checked as the construction progresses directly on the cathode-ray tube itself.

To begin with, both the chassis and panel should be laid out, the holes for all tube sockets and controls drilled, and the various sockets and controls mounted. The only components requiring special attention in mounting are the power transformer and electrolytic filter condensers. The transformer utilized in the instrument shown in Figs. 1 & 7 is a fully-shielded unit, and very little external leakage flux is present to cause magnetic interference to the cathode-ray tube. Such a shielded unit should be used if possible, but if not procurable, a standard half-shell replacement transformer may be used. If this latter

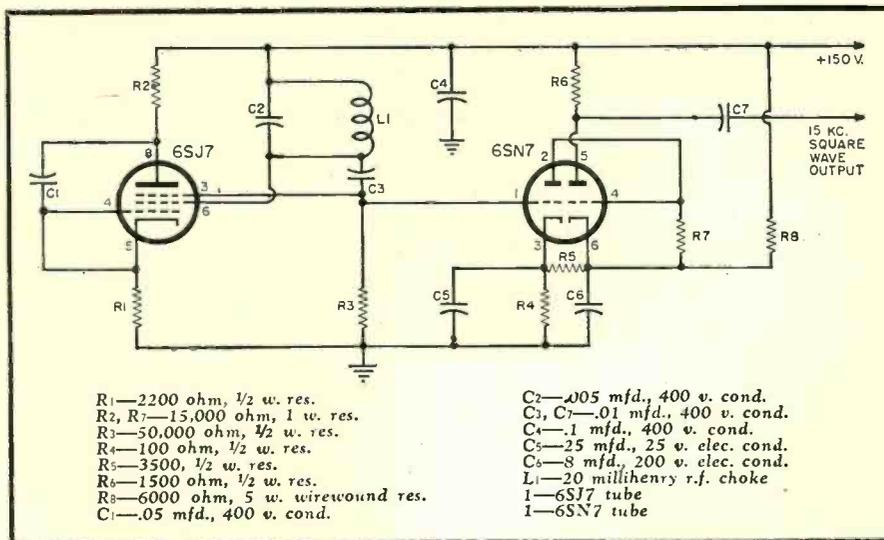


Fig. 5. Circuit for simple square-wave generator suitable for checking high frequency response and attenuator adjustments for TV scope deflection amplifiers.

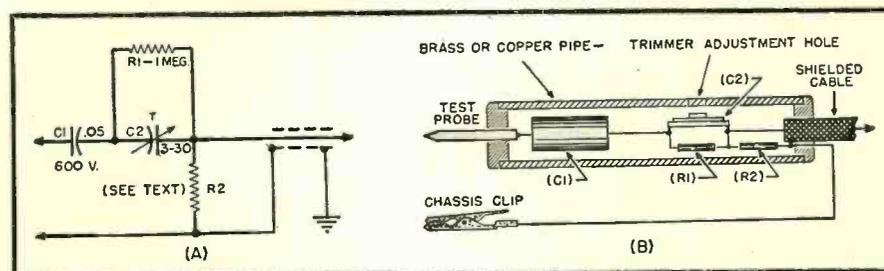


Fig. 6. (A) Schematic diagram of wide bandpass test prod and cable for use with television oscilloscope. (B) Physical layout for the test prod and the cable.


type transformer is used, it is important that it be mounted as far to the rear as possible and *directly* behind the cathode ray tube, preferably *under* the chassis, if the parts can be so arranged. Such placement will tend to minimize the magnetic interference that may be present.

It will undoubtedly be found most satisfactory to utilize electrolytic condensers in cans for the various high-

capacity filters, since these afford convenient connection terminals and are mounted easily. It should not be overlooked that the two filter condensers, C_{45} and C_{47} , adjacent to the filter choke must be in separate cans, and these cans must be insulated from the chassis as must C_{49} . This is readily accomplished with the condensers shown in the instrument, since both non-insulated and

(Continued on page 155)

Fig. 7. Under chassis view of the television oscilloscope.

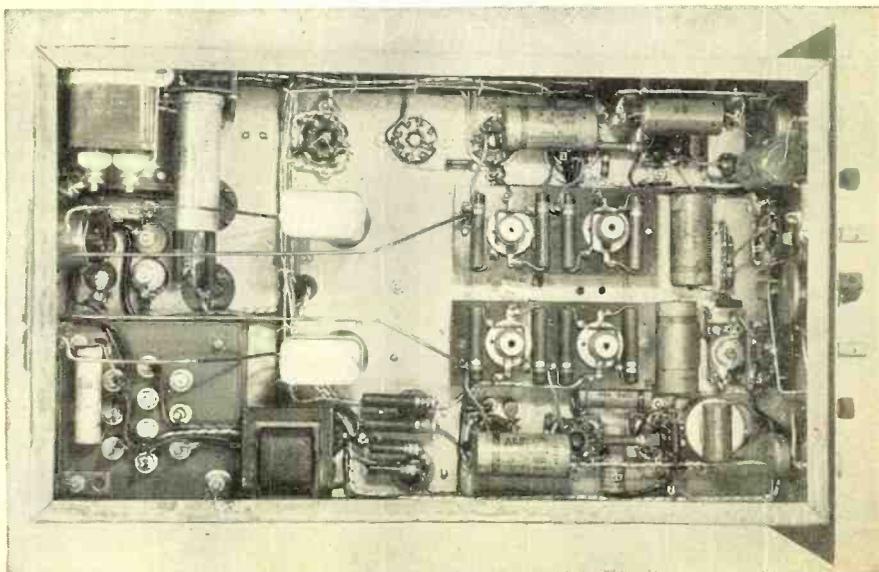

The Ideal Grid Dip OSCILLATOR

By JAMES N. WHITAKER, W2BFB

Details for constructing a versatile, self powered unit which has many uses. The ham or serviceman can use it often in his work.

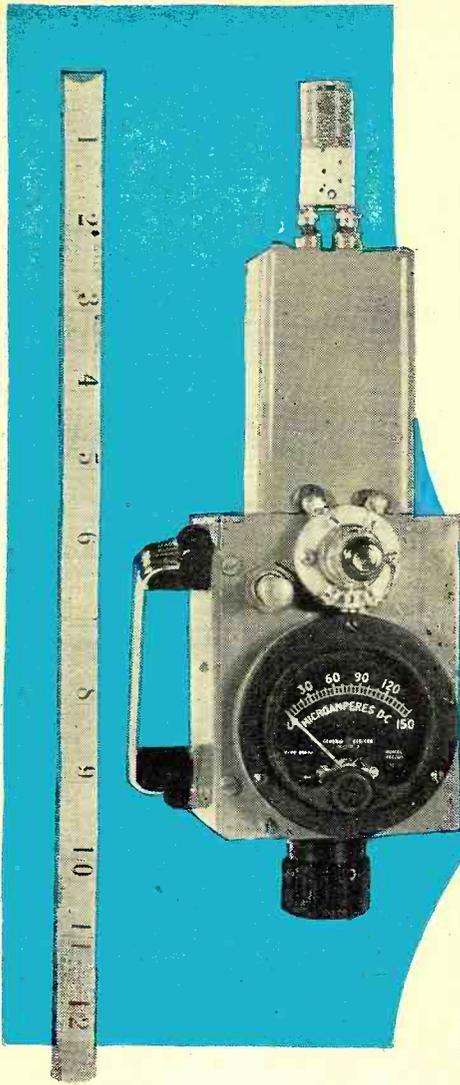


Fig. 1 — Complete unit as built by the author. Batteries are self-contained and are housed in case directly under the microammeter.

A GOOD grid dip oscillator has become a most necessary instrument for all laboratories and experimental workshops. It can be used for such a wide variety of purposes that it is almost as essential as a voltmeter. It serves as a wavemeter to measure the frequency of tuned circuits before the circuits are energized by the equipment in which they are used. It is a heterodyne frequency meter, an absorption wavemeter having greater than usual sensitivity, and many other things. This versatile instrument is old to the art of radio, but seems to have been forgotten for a period of time only to be rediscovered recently. At the present time there are a number of different versions of this instrument available commercially, and several others have been described in various recent publications. The circuits used are similar in many respects. None are entirely satisfactory for all uses, either because of the physical size, or need for power supply cables, etc. The ideal grid dip oscillator must be as easy and simple to use as a flashlight, and yet be sufficiently accurate for all but very precise measurements. It was the need for such an instrument that prompted the investigations leading up

to the design of the instrument described in the following paragraphs.

The specific application that required this type of a meter was a series of antenna investigations. The measurements were to be made at the antenna, which was mounted on the top of a fifty foot high tower. Even the most compact of grid dip oscillators described in the past required a long length of wire to provide the necessary power. The connecting cable was continually in the way of the user, and also presented somewhat of a hazard when used in such precarious positions as out on the end of the boom supporting an antenna array far above the ground.

The radiated power from a grid dip oscillator does not need to be of any appreciable magnitude. The smallest vacuum tube readily available will perform quite satisfactorily. The 957 tube was selected because of its low filament power requirements (1.5 v. at .050 amperes), and for its ability to oscillate freely with a relatively low plate potential. These factors permit the use of a "penlite" dry cell for the filament power, and a 67½ volt miniature "B" battery of the hearing aid type for the plate power. The tube is also physically small and therefore ideally suited to a compact design. The 957 being a filament type tube, it is of the instantly usable type, eliminating the need for filament power when not actually in use. This greatly prolongs the battery life.

Almost any self-excited oscillator circuit is suitable for use in a grid dip oscillator. If the instrument is to cover a wide frequency range where coil changing is required, the most practical circuit is the well-known Colpitts oscillator, since this system uses a two terminal inductance, with the electrical center tap provided by the split stator type tuning condenser.

The over-all mechanical arrangement may be that which best suits the builder, bearing in mind the following requirements. The inductance should extend well out beyond all other metal parts in such a manner as to permit coupling to the circuit under investigation without bringing too much of the metal case into the field of the coil or other inductance being measured. The complete instrument, including batteries, should be as light in weight as possible. It should be equipped with a handle located at a position convenient for both carrying and operating the instrument. The distribution of weight with respect to the handle must be carefully considered, if the instrument is to be used without undue fatigue. The push-button filament switch should be located in a natural position for operation by the thumb of the holding hand, leaving the other hand free for the manipulation of the tuning control of the instrument or the device under investigation.

The usual precautions should be followed in the electrical design of the r.f. portions of the circuit. The circuit as a whole is not at all critical, but the shorter and more symmetrical the leads, the better the performance will be, particularly in the higher frequency ranges.

The instrument designed and built by the author is shown in Fig. 1. The batteries are located in the body of the instrument, under the microammeter. The weight of the batteries counterbalances the tuning system and induc-

tance extending out from the case, placing the center of gravity at the hand grip which is mounted on the left side cover. The filament push-button switch is located on the top adjacent to the tube, in a position normally under the thumb of the left hand when holding the instrument. The tuning dial and knob are located on the end of the assembly. The inductance is plugged in at the far end of the shield housing the tuning condenser.

Fig. 4 is the end view, showing the tuning control. Four of the plug-in coils are pictured beside the instrument. This view also shows that the hand grip is on an angle. This increases the ease and comfort in holding and using the instrument.

The electrical schematic diagram is shown in Fig. 2. The resistor R_1 across the tuning inductance L_1 will vary with frequency and is not used on the highest frequency coil. The purpose of this resistor is to maintain stability and amplitude of oscillations when the L/C ratio becomes unfavorable as it does on the lower frequencies. The value of R_1 is best determined by experimentation, as it will depend upon many factors. If this resistor is omitted, the meter reading for different values of inductance will vary greatly. If adjustments are made to obtain a satisfactory meter reading on the highest frequency, it will be found that the meter will read completely off scale when a larger coil is plugged in for the lower bands. In practice, the instrument is adjusted to give approximately $\frac{3}{4}$ full scale reading with the coil for the 28 mc. band in place. Resistors are added across the lower frequency band coils to produce the same approximate reading.

The grid current will not be constant over the entire range of tuning, but the change should be gradual and constantly in one direction with a given direction of rotation of the tuning control. With a larger value of tuning condenser C_1 , the tuning range will be greater, but the errors in dial readings will be greater. The changes in the grid current will also increase. For the sake of accuracy, it is better to have more coils and use a lower capacity condenser, than to use a large condenser and try to cover a greater range with one coil. A satisfactory compromise will permit the range of each coil to overlap the amateur bands by a comfortable margin, with a separate coil used for each band.

The tuning condenser used in the instrument shown is a Hammarlund HFAD 50, with all except three rotor and three stator plates removed from each section. This condenser was chosen because it has ceramic end plates on both front and rear containing identical holes. This permits the condenser to be mounted to the main chassis, and also permits the bakelite jack panel to be mounted to the rear. The stator support rods run the full length of the condenser, permitting electrical connections to be made directly with a minimum of wiring. A "butterfly" type

of variable condenser would be better for operation in the higher frequency bands, but would require some sort of a geared dial to provide ease of tuning and fineness of dial readings. The set-up as shown performs admirably up to and including 30 mc. and probably could be operated at higher frequencies if desired.


Bakelite end plates are mounted on both ends of the tuning condenser by means of 6/32 screws and spacers. These bakelite plates are 2" square with rounded corners to fit into a standard 2" square shield can, such as is commonly used on i.f. coils. Holes are tapped in the corners of the rear end bakelite plate to permit the shield can to be held in place with screws. This plate contains two countersunk holes for the flat head screws used for mounting on the condenser end plate. Two "banana" jacks are mounted in the center of the bakelite end plate to receive the coil plugs. This general arrangement is shown in Fig. 3.

Fig. 3 indicates the manner in which the various parts of the tuned circuit are mounted and connected. The shield can that houses the tuning condenser has sufficient clearance to permit the plate and grid blocking condensers, as well as the grid resistor, to be mounted as indicated in the drawing. The grid and plate leads are brought out through rubber grommets to the tube socket terminals. Grooves are cut in the shield can to accommodate the grommets. The blocking condenser leads are soldered directly to the approximate centers of the stator support bars as indicated, to maintain symmetry in the circuit. The stator connecting lugs are bent down to meet the lugs under the coil jack nuts, and soldered in place.

Dimensions of the various spacers are not given, as they are not critical, and can be made any convenient length to suit the builder. As long as the general trend is followed, keeping in mind the major requirements, satisfactory operation will be assured.

The main body of the instrument contains the r.f. choke RFC and the batteries, switch, meter, and the meter

(Continued on Page 131)

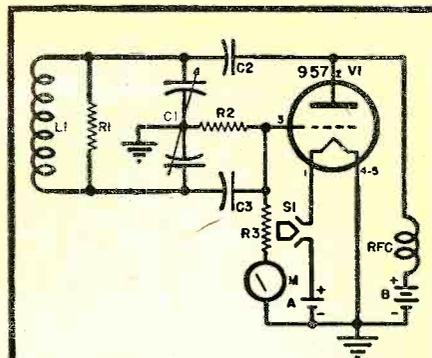

- R_1 —See note below
- R_2 —47,000 ohm, $\frac{1}{4}$ w. metalized res.
- R_3 —100,000 ohm, $\frac{1}{4}$ w. metalized res.
- C_1 —Air cond. (Hammarlund HFAD50 modified, see text)
- C_2 C_3 —100 mmfd. mica cond.
- S_1 —S.p.s.t. push-button sw. (normally open)
- RFC—2.5 millihenry r.f. choke.
- M—150 microamperes, $\frac{1}{2}$ " d.c. meter
- V1—957 tube
- L_1 —26.4-31 mc.— $8\frac{1}{2}$ t. #24 en. wire on $\frac{3}{4}$ " form, spaced 32 t. per inch. R_1 not used
- 13.5-18 mc.—21 $\frac{1}{2}$ t. #24 en. wire on $\frac{3}{4}$ " form, spaced 32 t. per inch. R_1 —220,000 ohms, soldered across coil
- 6.8-8.1 mc.—43 t. #28 en. wire close-wound on $\frac{3}{4}$ " form. R_1 —100,000 ohms soldered across coil.
- 3.45-4.6 mc.—100 t. #28 en. wire close-wound on $\frac{3}{4}$ " form. R_1 —47,000 ohms soldered across coil.

Note: Where R_1 is required use resistor such as Allen Bradley $\frac{1}{4}$ watt type, inside coil form, soldered across lugs under plug where ends of winding terminate.

Fig. 2—Circuit diagram of the complete grid dip oscillator. Note resistor R_1 is not used with the 26.4-31 mc. coil.


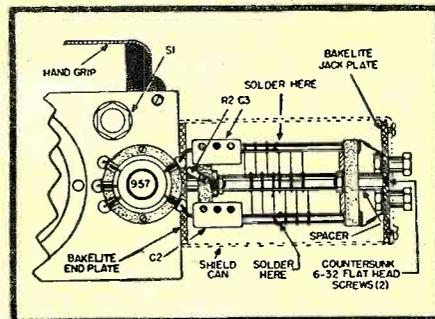


Fig. 3—Cutaway view shows details of mechanical construction of the unit.

Fig. 4—Completed unit shown with its set of four plug-in coils. These coils cover 3.45-4.6, 6.8-8.1, 13.5-18, and 26.4-31 mc. Coils covering other frequencies may be used.

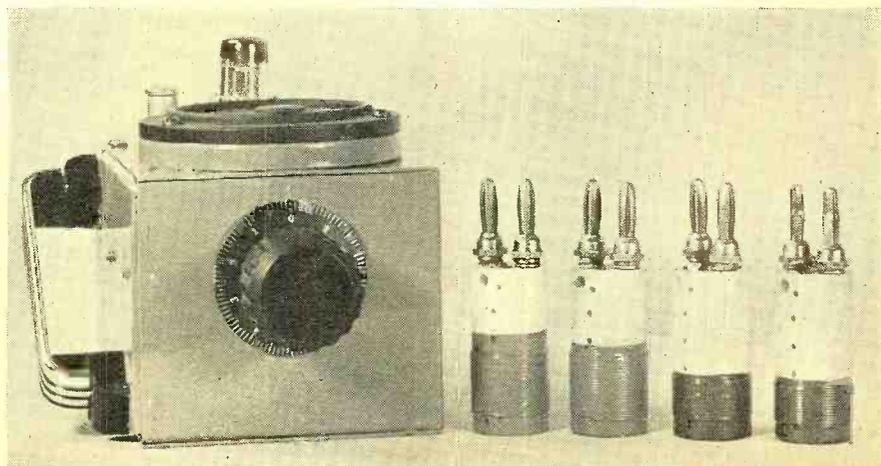

More PEP for your FM PILOTUNER


Underchassis view of Pilotuner with C_1 removed and R_1 wired into new position.

The addition of a 6AK5 i.f. stage increased the performance and range of this popular FM tuner without elaborate alterations.

By
MALCOLM H. BROWN

LIVING in a rather poor location for FM reception on the new frequencies, the nearest transmitter being hidden by hills so that reception is unreliable, it was a definite problem to get good reception on my newly acquired *Pilotuner* without using excessive audio gain.

After experimenting unsuccessfully with the built-in antenna, I installed an indoor dipole made up of two No. 16 enameled wires, each 27½ inches long with a two-inch insulator between and a lead-in consisting of a twisted pair as used with a prewar short-wave receiving antenna. This brought the signal strength up so that, with the dipole oriented in a north-south direction, fairly good reception was possible from both transmitters to the east. The weaker transmitter, however, was difficult to tune as the

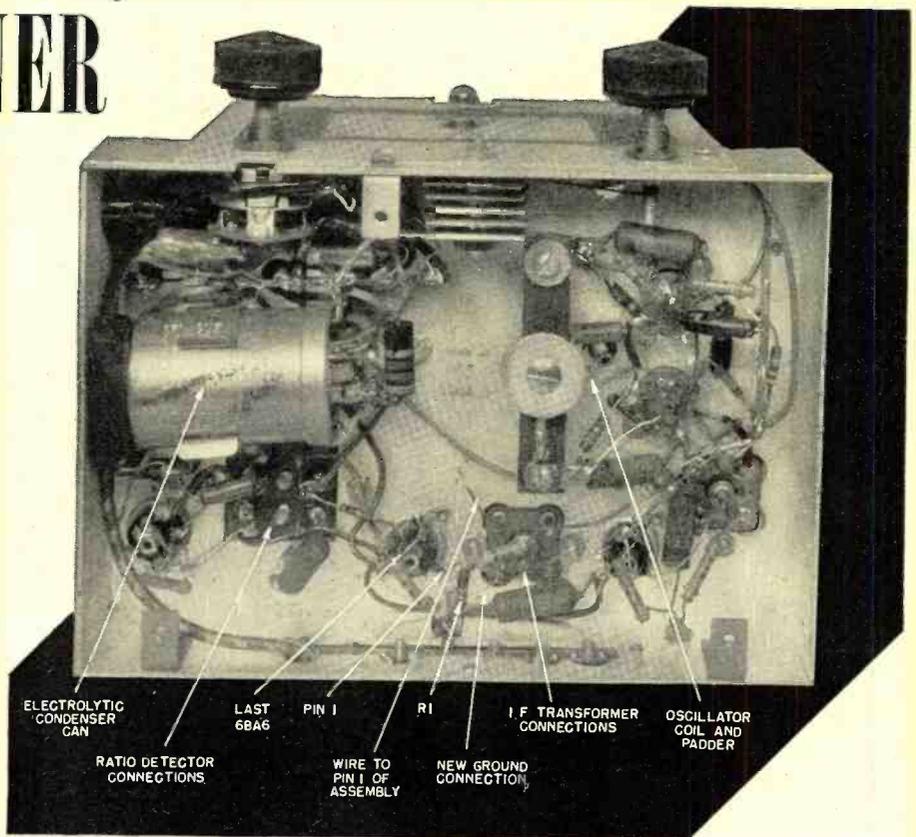


silent spot centered between the noise sidebands was very narrow, and the drift of the *Pilotuner*, even though very low, was still sufficient to require fairly frequent retuning. An effect similar to that of an AM receiver slightly off tune was also present, accentuating the higher audio frequencies and causing ignition

noises to linger to a greater extent on the weaker stations.

I assumed that these effects were caused by low signal strength but I did not want to install a dipole on the roof for two reasons. First, the mounting and lead-in problems were unusually difficult, and second, the tree branches and power lines at my location would screen the signal to an extent at least as great as the screening caused by using an indoor antenna. Besides the local police and fire radio service had run into a pronounced dead spot at a slightly higher elevation than my indoor antenna and their transmitter was also located to the east.

Another i.f. stage with a gain of from 8 to 12 would bring the signal presented to the ratio detector high enough to make tuning easier and the quality better, as the center frequency presented to the detector would appear broader. In making this assumption I was guided by the fact that a fourth FM station to the west, with higher radiated power, could be received with much greater signal strength than the other stations as its signals for the metropolitan area to the east are beamed directly over my house. The advantages of greater signal strength were readily apparent when listening to this station and suggested the incorporation of additional gain.

Diagram shows changes made in the original circuit of the *Pilotuner*.

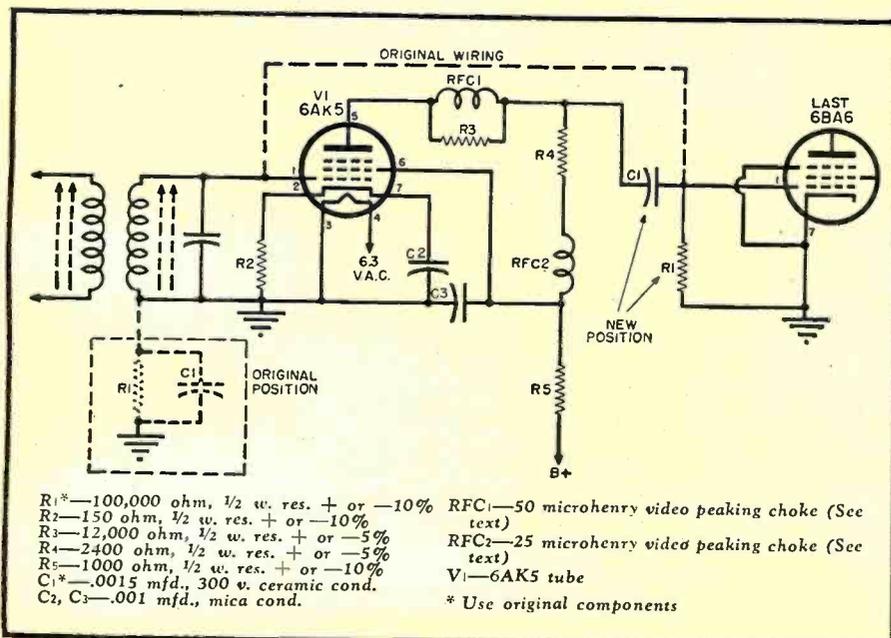


There is insufficient space in the *Pilotuner* for a coil can containing a 10.7 mc. i.f. assembly plus a tube and its associated wiring. However, under the chassis between the oscillator coil and the electrolytic filter condenser there is room to add a 6AK5 tube and socket plus the necessary parts for a series-shunt peaking i.f. circuit. In addition to occupying a very small space, this stage requires no tuning, which means that additional i.f. gain can be had without upsetting the factory tuning.

Circuits of this type have become quite common with the advent of television and very wide bands can be amplified with reasonable gains. As the frequencies we are interested in here are 10.7 mc. plus and minus 75 kc. the large components necessary to make the low frequency response good are not needed and all the parts required are relatively small. A further advantage is that the space chosen for this added tube permits connection to its grid with no increase in lead length.

In the design of the series-shunt peaking circuit the values chosen were adapted to standard values of resistors and condensers. The coils used in the circuit are ordinary video peaking coils wound on bakelite forms and are of the low-*Q* type. These are available from *The National Company* as No. R33. This unit is a dual section r.f. choke and can be secured in the 50 microhenry size. By removing one section the remainder will do for the 25 microhenry coil.

There probably are some video peaking chokes available in the assorted components that sell for a few cents or so in the war surplus items. The easiest way to get the values shown would be to measure the inductance on a *Q*-meter and, if necessary, strip off enough turns to reach the required values. With universal wound coils care should be taken in this stripping operation as the inductance will go down by a factor of greater than two with respect to the linear length of wire.

An alternative method of measuring the small inductances would be to use an r.f. oscillator. By shunting a small condenser of known value across the coil and connecting the assembly directly across the output terminals of the oscillator the output voltage will be a maximum at the resonant frequency of the combination. This can be read directly on the oscillator output meter or if care is taken to isolate the input capacity of the device with a resistor of 100,000 ohms or so, with a separate v.t.v.m. or a cathode-ray oscilloscope. Shunting the 50 microhenry coil with a 50 micromicrofarad condenser the resonant point will come at about 3.18 mc. Using the same condenser with the 25 microhenry coil, the frequency will be about 4.5 mc. With care this reading can be made to better than 5% which will

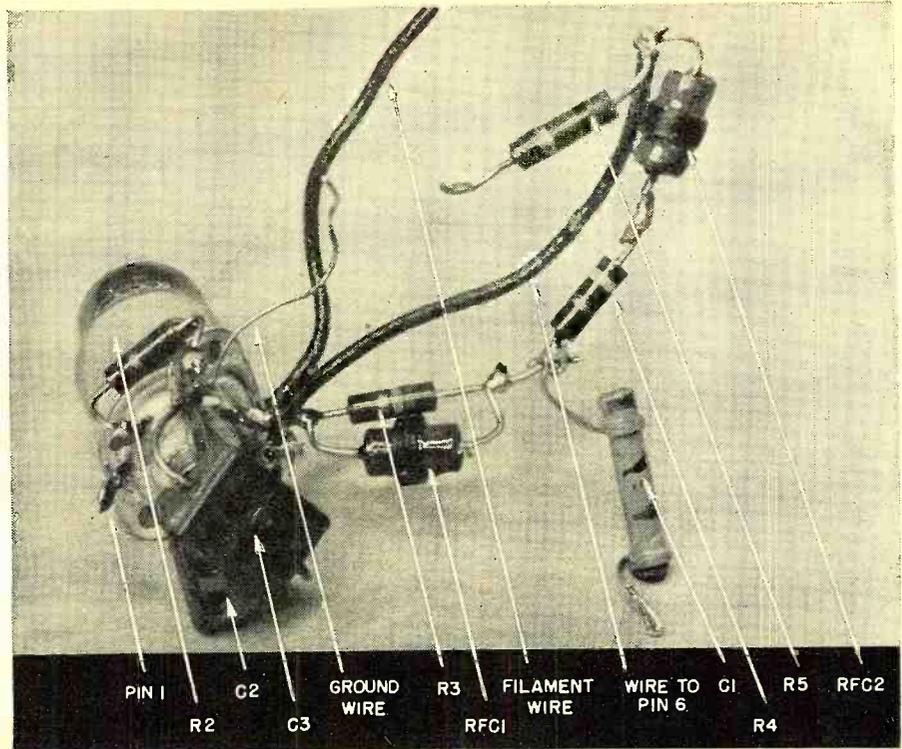


New tube and components shown ready to insert in the *Pilotuner* chassis.

be accurate enough for this circuit.

As in all video circuits the high frequency response of any stage is dependent on the output capacity of the tube, the input capacity of the following stage, the wiring capacity of the

circuit plus the load resistance used with the tube. The inductances are used to increase the load resistance of the tube as the frequency increases to compensate for the losses caused by the
(Continued on page.150)

Assembly wired into place. Note that it is installed as far as possible from the oscillator coil. Assembly is supported by its connecting wires.

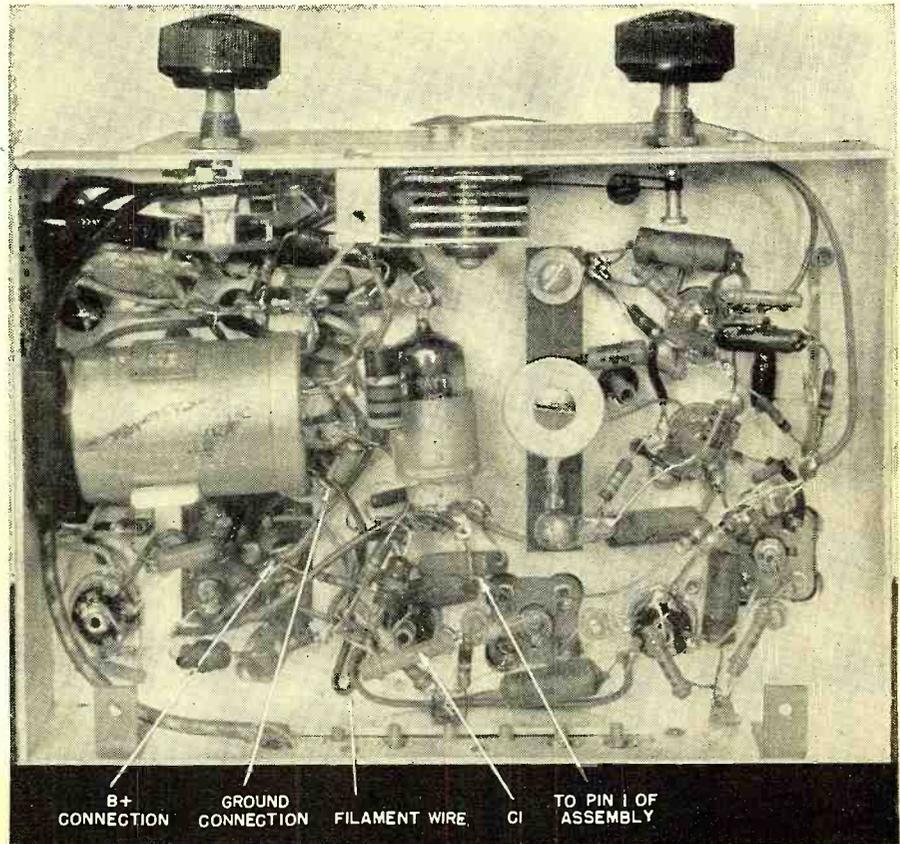

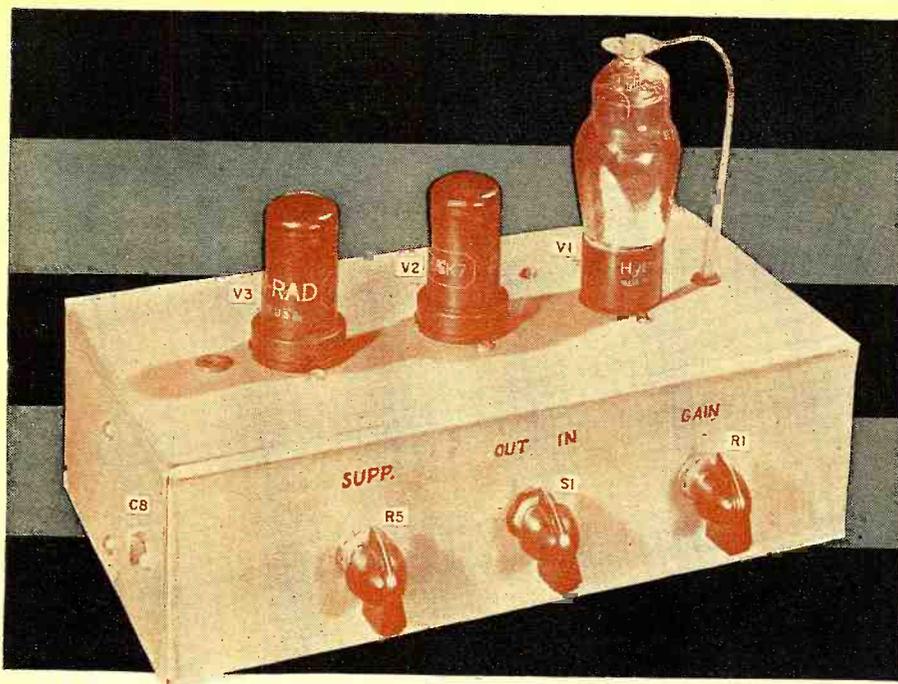


Fig. 1. Over-all view of the home-built Dynamic Noise Suppressor which uses readily available components.

The RECORDING and REPRODUCTION of SOUND

By OLIVER READ
Editor, RADIO NEWS

Part 15. Theory, design, and construction of a Dynamic Noise Suppressor that uses standard parts.

A PROPERLY designed Dynamic Noise Suppressor is an extremely worthwhile adjunct to any high quality playback system. On the other hand, an improperly adjusted suppressor is worthless and will cause many a headache to the soundman. Therefore, one should not attempt to build a unit unless he has access to an accurate audio oscillator and an oscilloscope. In addition the builder will need to borrow a second audio oscillator, for initial adjustments.

The suppressor to be described has been stripped to a minimum of components and tubes. It is capable of doing an excellent job and may be built successfully by any well-informed radio technician. Construction should not, however, be attempted by the tyro.

Various types of amplifiers require special changes in component parts val-

ues for best results. Therefore, this suppressor should be inserted into audio channels having similar characteristics to that of the record-reproduce amplifier shown on page 56 of the January 1948 issue of RADIO NEWS.

Originally this amplifier was to contain the integral Dynamic Noise Suppressor circuit. Extended research, however, indicated the desirability of building it on a separate chassis so that if any further changes were needed, these could be made without "messing up" the amplifier. In addition, it was discovered that there was a tendency for the two chokes, CH^1 and CH^2 (Fig. 2) to pick up hum from within the amplifier. This hum has now been eliminated by employing a separate chassis.

All of the components fit nicely into a standard chassis measuring $9\frac{1}{2}'' \times 5'' \times 3''$. Two automobile radio type connec-

tors are provided on the chassis for the two shielded leads connecting the suppressor into the amplifier. The output voltage from C^6 (Fig. 4, page 56, January 1948 RADIO NEWS) connects to the input of the Dynamic Noise Suppressor. The output of the D.N.S. connects to the input of R^{11} . In other words, the D.N.S. is inserted at the junction between C^6 and R^{11} of the record-reproduce amplifier.

Necessary filament and plate voltage for the D.N.S. may be taken from the power supply of the amplifier. It is recommended that the +250 volts d.c. be taken from the screen of the 6V6 through an additional dropping resistor of 10,000 ohms and an added filter condenser of 16 μ fd. Likewise, the filament voltage may be taken from the filament winding supplying the 6V6.

This simplified circuit of the Dynamic Noise Suppressor uses a 6B8G to provide the necessary voltage amplification so that sufficient drive will be available to the d.c. control circuits for 6SK7 reactance tubes. The desirability of the 6SK7 as opposed to a sharp cut-off pentode such as a 6SJ7 is associated with smooth and continuously variable action of the "gate" circuits. A sharp cut-off tube tends to produce an undesirable "on-off" effect while the transconductance of the 6SK7 may be varied over a wide range. The diodes in the 6B8G envelope are used to rectify the control voltage.

Since it is desirable to provide a control voltage for the high frequency reactance tube derived from the upper fundamentals, and a derivative of the harmonics of low frequencies to drive the low frequency reactance tube, suitable RC filter networks are inserted ahead of the diodes. The reason for making the control voltages selective with regard to frequency is to avoid the possibility of the noise (either low frequency rumbles or high frequency needle scratch) from developing sufficient voltage to open the gates.

The rectified control voltage is further filtered by the networks following the diodes and the resultant d.c. applied to the grids of the reactance tubes. The speed with which the gates will open is largely a matter of time constants of these networks. The closing speed is also controlled by this factor but is further affected by the maximum voltage to which the condensers have been charged. In other words, if x volts are required to open the gates fully and the signal is sufficiently large to develop $2x$ volts across the filter condensers, they must discharge down to x volts before the gates will begin to close. Thus the closing time is longer for large signals than for medium signals. In general this is desirable because large signals usually require a longer reverberation time for realistic reproduction. In the

more elaborate versions of the Dynamic Noise Suppressor these effects may be controlled more accurately by the use of a separate amplification stage for the d.c. control voltage and arrangements to limit the maximum control voltage that may be developed. However, this is not so important in the more limited range devices as it is in those designed to handle very wide frequency response ranges.

The use of the diodes in the 6B8G for rectifying the control voltage requires that the cathode of this tube be used as the effective ground return for all other tubes.

The resistors R^6 and R^7 are selected to divide the voltage properly so that an adequate drive will be available for the control circuits and also to produce a proper input impedance for the gate circuits. The "roll-off" ahead of the sharp dip in the high frequency gate circuit is a function of the value of these resistors. The series filter consisting of CH^1 and C^2 in parallel is tuned to resonate at 10 kc. It serves the dual purpose of holding down the very high frequencies when the gates are closed and the rise above resonance in the reactance tube circuit is appreciable in a region of considerable noise, and also provides the proper impedance for the shunt reactance tube tuned circuit to "work on." Since the condenser is capable of tuning this inductance over a broad range its inductance value is not extremely critical, but it is important that it be of high "Q" design.

The inductance CH^2 is also in a tuned circuit controlled by the condenser C^8 and its value is not critical although the "Q" is obviously important. C^7 is simply a blocking condenser to keep the plate voltage off the tuning condenser.

Analysis of these circuits will involve viewing the tube as a condenser in a tuned circuit. A simple method of understanding the results obtained is to think of it as a feedback device. A portion of the feedback voltage is applied to the grid of V^2 through condenser C^8 . The voltage appearing on this grid is in phase with the signal on the plate. The grid voltage causes a corresponding change in plate current which produces a change in plate voltage that is 180 degrees out of phase with the input signal to the plate and is therefore degenerative.

The signal appearing in the grid circuit will vary with frequency in accordance with the characteristics of the network consisting of C^8 and R^{28} . The magnitude of the degenerative signal produced depends upon the transconductance of V^2 . Under static conditions this will vary with the cathode bias developed across R^{10} and R^5 as well as the screen voltage. The screen voltage is held relatively constant by the divider

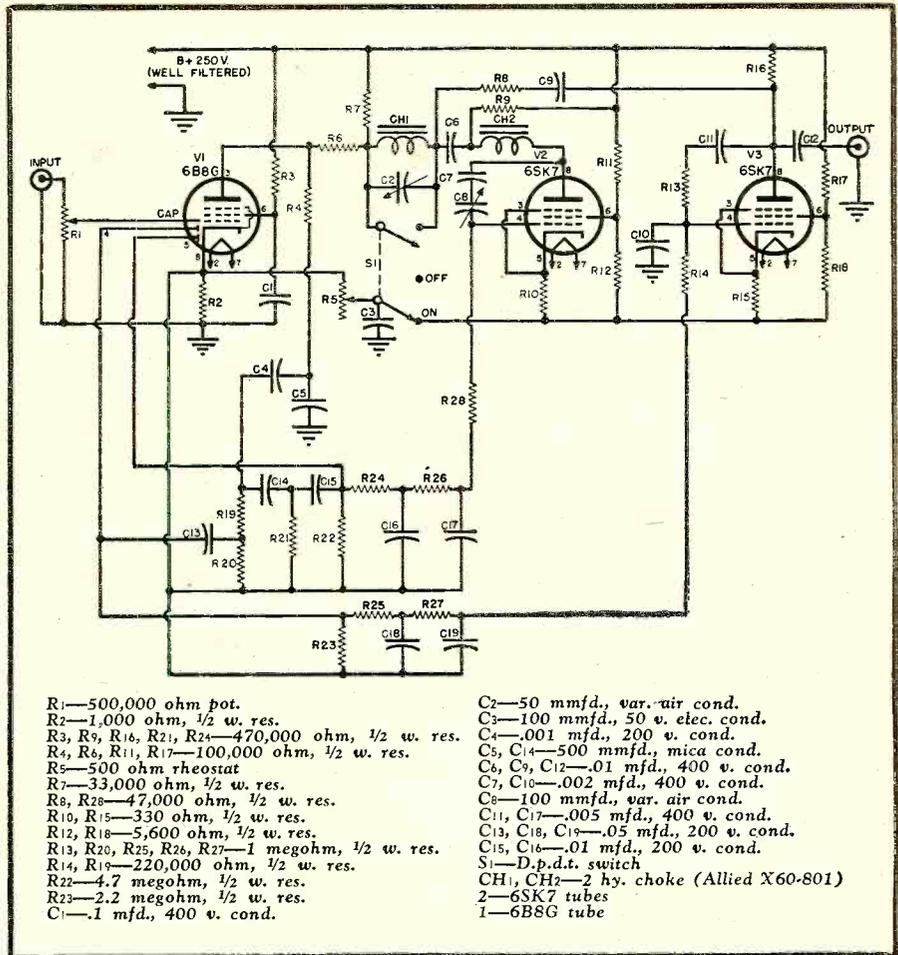


Fig. 2. Circuit diagram of the home-built Dynamic Noise Suppressor.

R^{11} - R^{12} . For any given frequency the attenuation produced by the degenerative signal on the plate of V^2 will vary with the adjustment of C^8 and the setting of R^5 . The results obtained may be superior with lower values of R^{10} , or

even eliminating it entirely, but the circuit will then be more critical with regard to tube replacement.

When a signal of sufficient magnitude to develop an appreciable voltage across (Continued on page 184)

Fig. 3. Under chassis view showing location of important components.


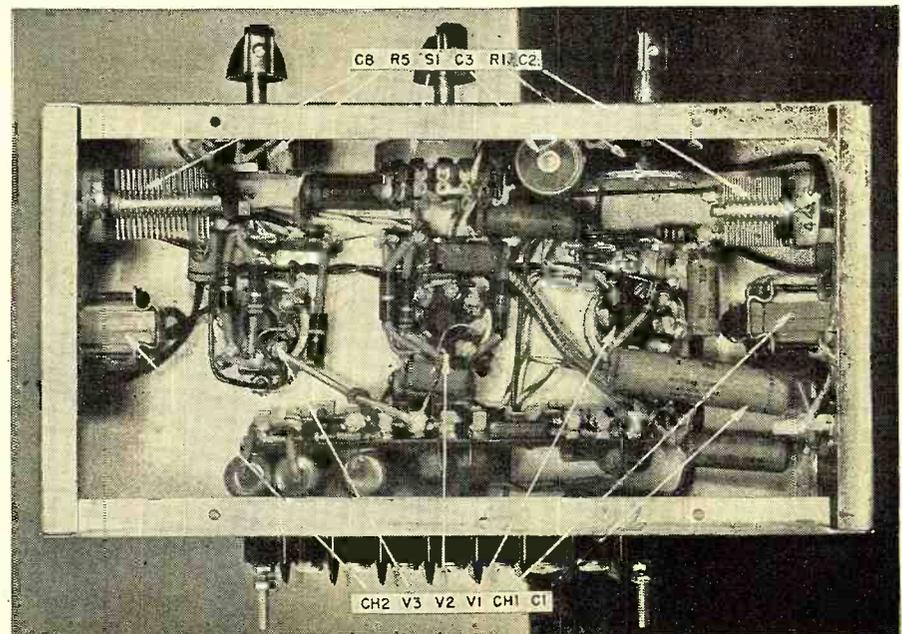


Fig. 1. Cutaway view of "Inductuner" and the over-all view of the front end assembly incorporated in DuMont video receivers.

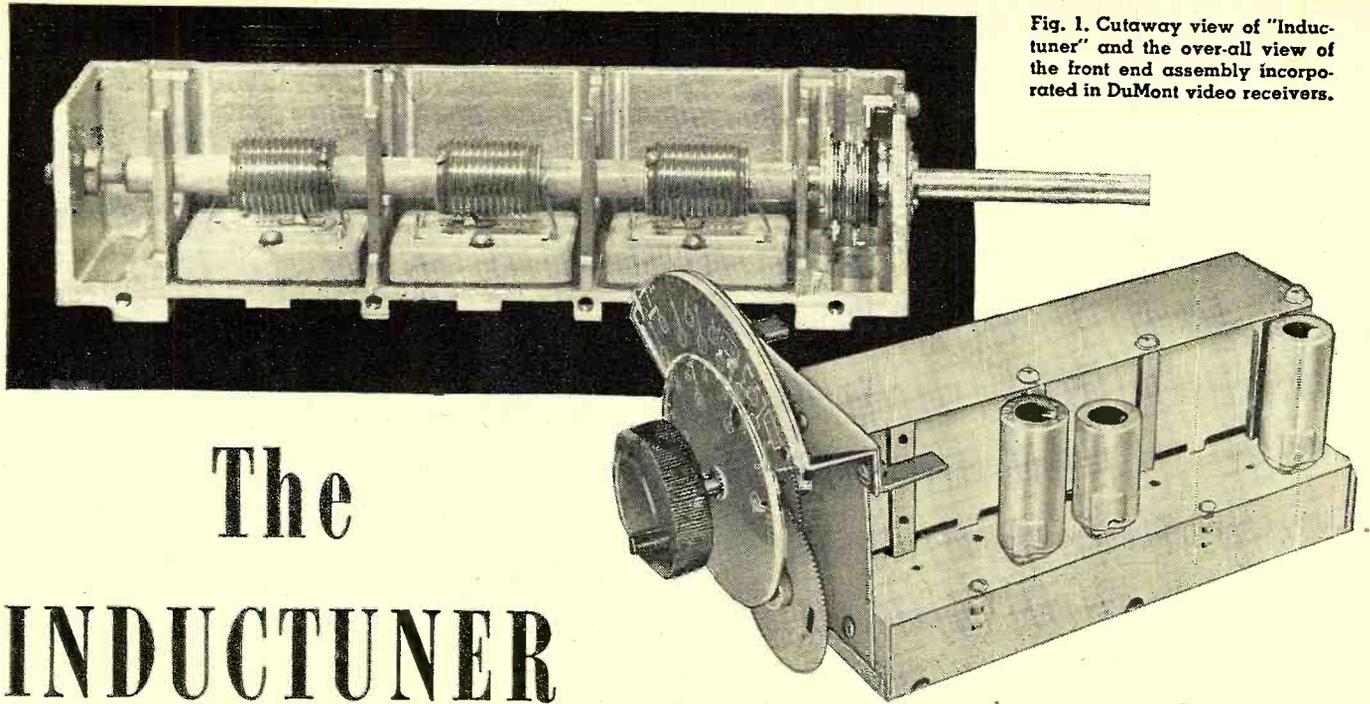

The INDUCTUNER

Variable inductances providing wide tuning range (44-216 mc.) at high Q are used as tuning elements in front end assembly of DuMont video receivers.

THE proximity of the television channels to the FM bands makes it desirable to employ a tuner in television receivers which will enable users to receive the FM stations as well. One such tuner is the "Inductuner," designed by Paul Ware, manufactured by the P. R. Mallory & Co., Inc., and used in DuMont television receivers.

As shown in Fig. 1, the "Inductuner"

consists of three separate variable inductances mounted on a common shaft. The coils are wound on ceramic forms and movable trolley sliders make contact at each point on the coil. Rotation of the shaft causes the inductance to vary from approximately .02 to 1.0 microhenry providing an inductance ratio of 1 to 50 and permitting a tuning range from 44 to 216 mc. It is generally


true that the use of a variable inductance permits a wider tuning ratio than a variable condenser. This is because a length of wire and its inductance can be reduced to a smaller degree than the minimum capacitance of a variable condenser. Furthermore, as the inductance decreases, the losses reduce proportionately and it is even possible to have the losses decrease faster than the inductance, producing a rising Q with frequency. The important advantage of this is the rise in gain at the higher frequencies, something which is usually lacking in most receivers.

The movable trolley contact divides each coil into a used and an unused portion. As the trolley moves along, the low frequency end of the coil is shorted to the contact. This raises the natural frequency of the unused part and maximum occurs when the trolley is nearest the high frequency end of its travel. The upper frequency limit of the band over which this is to be used should be slightly lower than the highest frequency of the unused part. In this 10 turn unit, the natural frequency of the unused part is somewhat lower than 300 mc.

The equivalent diagram of one section of the "Inductuner" is shown in Fig. 3A. *Ch* and *Cl* are the stray capacitances from the variable inductance coil to the case, the latter generally being at ground potential. In shunt with the coil is a third capacitance *C* which consists of a fixed portion representing the interelement stray capacitance and a variable portion which is the distributed capacitance of the winding itself. As the trolley moves along, the active distributed capacity changes and eventually becomes a minimum when the trolley has reached the end of its run. Note that it is not necessary to use the full ten turns of the coil. The internal stop mechanism can be set so as to restrict

(Continued on page 130)

Fig. 2. Circuit diagram of the r.f. stages of DuMont television receivers.

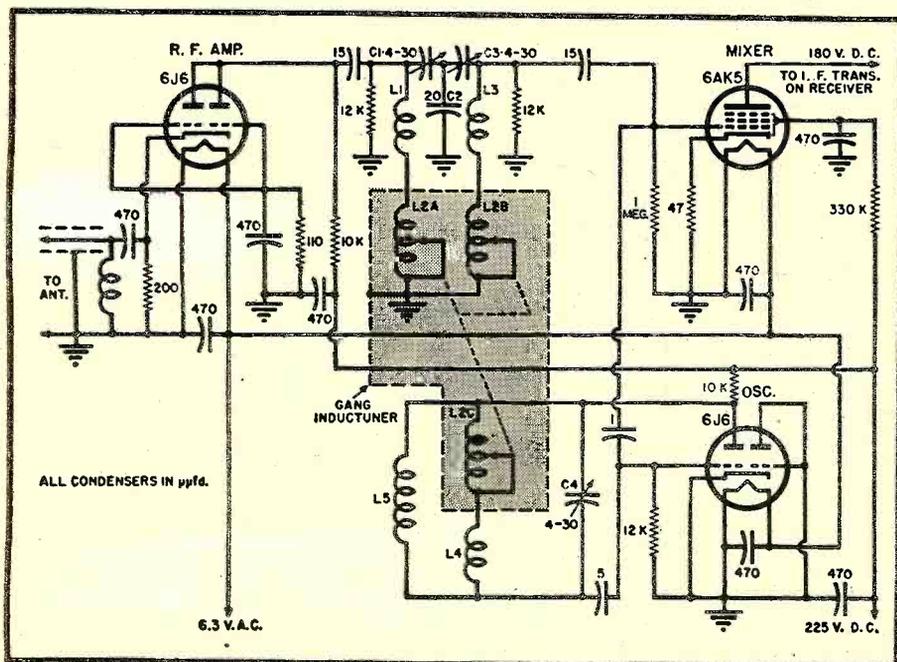

"How is that one, Mac?" Barney asked as he set a gleaming radio chassis on the end of the bench.

Mac dropped his soldering iron in the holder and looked the freshly-cleaned chassis over critically.

"Not bad, Barney; not bad at all! In fact, you have been doing such a good job in the cleaning department this past month that we are going to have to give you a little promotion. It is time you learned how to replace parts. Now is a good time to start, too, for this set I've been looking at is an example-and-a-half of how not to do it."

He turned the set on which he had been working upside down and pointed an accusing finger at a tubular electrolytic that had been bridged across an inverted-can condenser.

"There, my red-headed friend, is something I never want to see you do," he warned.

"You mean to replace a tin can condenser with a paper one?"

"The words are 'inverted can' and 'tubular electrolytic,'" Mac said reprovingly. "In learning a trade, the first thing to do is to learn the language so that fellow-mechanics will know what you are talking about when you ask questions or try to explain something to them. That business of calling a particular radio part a thing-amajig or a doo-hickey is all right for a school girl, but it does not go around the shop."

"What is more," Mac went on, trying not to grin at Barney's crest-fallen appearance, "I was not objecting to the use of the tubular condenser. They are okay. In many instances, they make good and inexpensive replacements. The mistake was in not cutting out the bad condenser from the circuit. The lazy guy who did this simply soldered the new unit right across the old one."

"That's ungood, huh?"

"Very 'ungood!' An old condenser often has a low resistance. This low resistance shunted across the new condenser increases its power factor, and a condenser is one place where a high power factor is bad. What is worse, sooner or later the old condenser is likely to short out—as it did in this case—and then the customer has to pay two service bills for what should have been one job."

"But where do you tie all those wires that used to be soldered to the old condenser after you take it out?" Barney wanted to know.

Mac opened a drawer and picked up a handful of little one- and two-lug mounting strips. "You use these," he said. "Often you can place the mounting-angle beneath a nut, or you can solder it directly to the chassis. Then you can use the insulated lugs for holding the connections removed from the condenser."


"Is there anything else wrong in that set?" Barney asked.

"What do you think?" Mac quizzed with a sidelong glance.

Barney's red head bent over the set
May, 1948

Mac's RADIO SERVICE SHOP

By JOHN T. FRYE

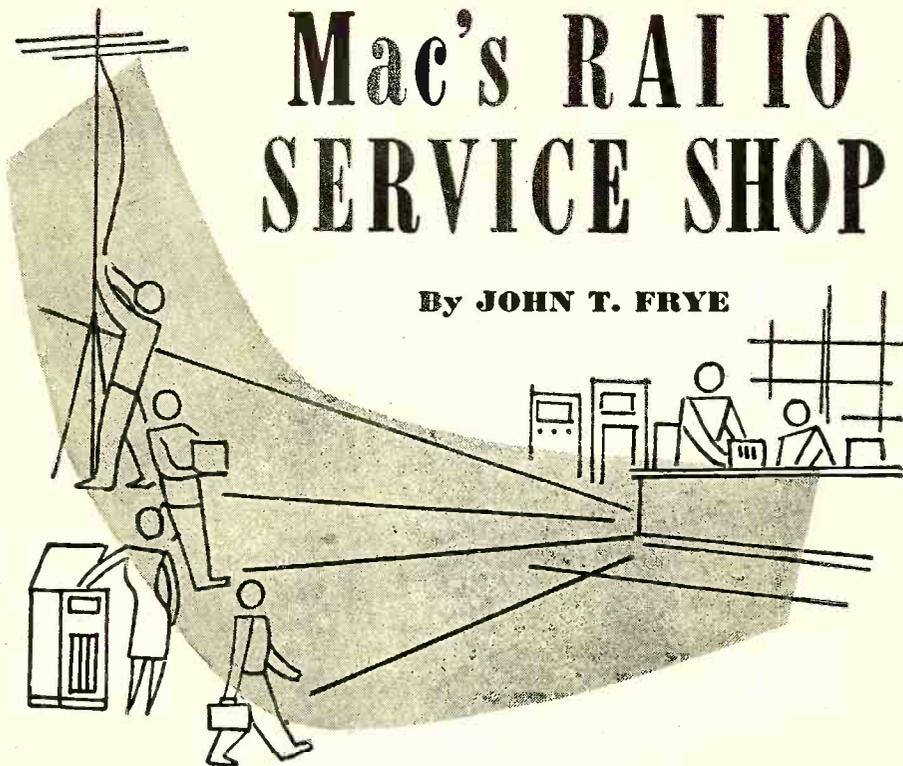

BARNEY IS PROMOTED

as he inspected it gravely. "Well-I-I," he offered cautiously, "the terminals on that gadg—I mean that volume control seem to have an awful lot of solder on them."

"Good!" Mac said. "I hoped you would notice that. And let me show you something else."

Picking up his soldering iron, he touched it to the lumps of solder on the volume control terminals. As he touched each one, the wires attached to it dropped off.

"The fellow who put in that control must have been the world's laz-

est," Mac said disgustedly. "He did not take the trouble to attach the wires firmly to the terminals before soldering them. He just tacked them in place and then piled the solder on to cover up. That is breaking the first commandment of radio servicing: *Always make your joints mechanically secure before you apply the solder.*"

"I catch; that saves solder."

"It saves more than solder, Barney; it saves you from getting sets back. In radio work, solder is not used to hold things together. That is up the tinner's alley, and he uses a different kind of solder. Radio solder is intended for the sole purpose of making a good electrical connection."

As he talked, Mac was skillfully removing the caked solder from the terminals. He held the point of his iron below each terminal so that when the lump of solder melted it flowed down on the iron, and then he wiped it off on the wad of steel wool he kept in a holder on the bench for that purpose. When the terminals were clean, he inserted the proper wires in each, wrapped the ends tightly around with his sharp-nose pliers, and then clamped the wires tightly in place. As Barney watched him closely, he applied the bright tip of the iron to each for a few seconds before he touched the rosin-core solder to the connection. The instant the solder touched the heated wires it flowed smoothly over them in a thin, seamless coat.

"It takes just two things to make a good soldered connection," Mac explained. "One is clean, bright surfaces; the other is plenty of heat. Most

(Continued on page 196)



JOHN T. FRYE

Born 1910, near Weiner, Arkansas, moved to Logansport, Indiana in 1924, attended Logansport High School, continued his studies at Indiana, Chicago, and Columbia Universities.

Has been in radio servicing since 1928. Started with a battery tester, a soldering iron, and a confident look. Secured amateur license W9EGV in 1932 and radio has since remained an avocation as well as a vocation.

TROUGH LINE TUNER for V. H. F.

By WARDELL H. SMITH,

The design and construction of a highly efficient r.f., mixer, and oscillator tuning system. Covering the frequency range from 78 to 153 mc., it includes the FM broadcast and 2-meter amateur bands.

UNMPED constants employed as tuned circuits in the form of coils and condensers become increasingly inefficient and difficult to handle as the resonant frequency of the combination increases. The limit of efficient operation for coils and condensers is in the neighborhood of 50 or 60 megacycles. When dealing with higher frequencies than these the size of the circuit elements—that is, capacity and inductance—becomes very small in proportion to the length of the connecting leads, making it difficult to confine the r.f. energy to the desired paths.

The problems of shielding the various components in such a manner that there will be no ground loops or feedback paths become more complex.

The use of coaxial lines as tuning elements solves all of these difficulties, but results in a system which is mechanically difficult to construct.

A very efficient, but relatively little known method of v.h.f. tuning is the trough line. The trough line, briefly, as can be seen by the drawings, consists of a central conductor, surrounded on three sides by a metal plate, one side remaining open. The

Q , or factor of efficiency, of this type of line, when used as an inductance in a resonant circuit, is several hundred times as great as an equivalent coil and condenser, although not quite as good as a full coaxial line.

The front end for v.h.f., whose construction is described herein, gives a performance several times better than any similar piece of apparatus that the writer has yet seen. Its tuning range is from 78 to 153 megacycles, covering the standard FM broadcast band and the 144 megacycle amateur band. It is built of parts obtained at surplus together with components constructed by sheet metal bending.

The first 6AK5 tube is employed as an r.f. amplifier. This stage of amplification has a voltage gain of a little better than 25 at the low frequency end of the tuning range and 32 at the high frequency end of the range.


This apparent inconsistency with the usual state of affairs is explained by the fact that although the efficiency of the tube falls off slightly at the higher frequencies, the Q of the tuned circuit increases more rapidly, thus offsetting the decrease in tube efficiency.

The next tube in the lineup is the mixer, another 6AK5. This tube gives a gain of 8 at the lower frequency and approximately 10 at the higher frequency. No signs of instability or regeneration are present in the r.f. and mixer stages and they can be adjusted to track exactly throughout the entire tuning range.

Another very interesting feature of this tuning unit is the oscillator section. As can be seen by an examination of the diagram, it is a tuned plate, tuned grid oscillator; a circuit which has a great deal of merit but which has not been widely used of late. This circuit adapts itself beautifully to the trough line construction. For the oscillator with a trough line for grid inductance and a trough line for the plate inductance, a very high degree of stability is obtained, due to the high Q of the trough lines. In this tuning unit, Q is about 1500 as against 300 to 325 for the very best coil and condenser combination.

With the dimensions shown, the oscillator will track for an i.f. frequency of 10.7 megacycles. If it is desired to employ an i.f. frequency of between 4 and 5 megacycles, a 10

Fig. 1. Side view of trough line tuner showing construction details.

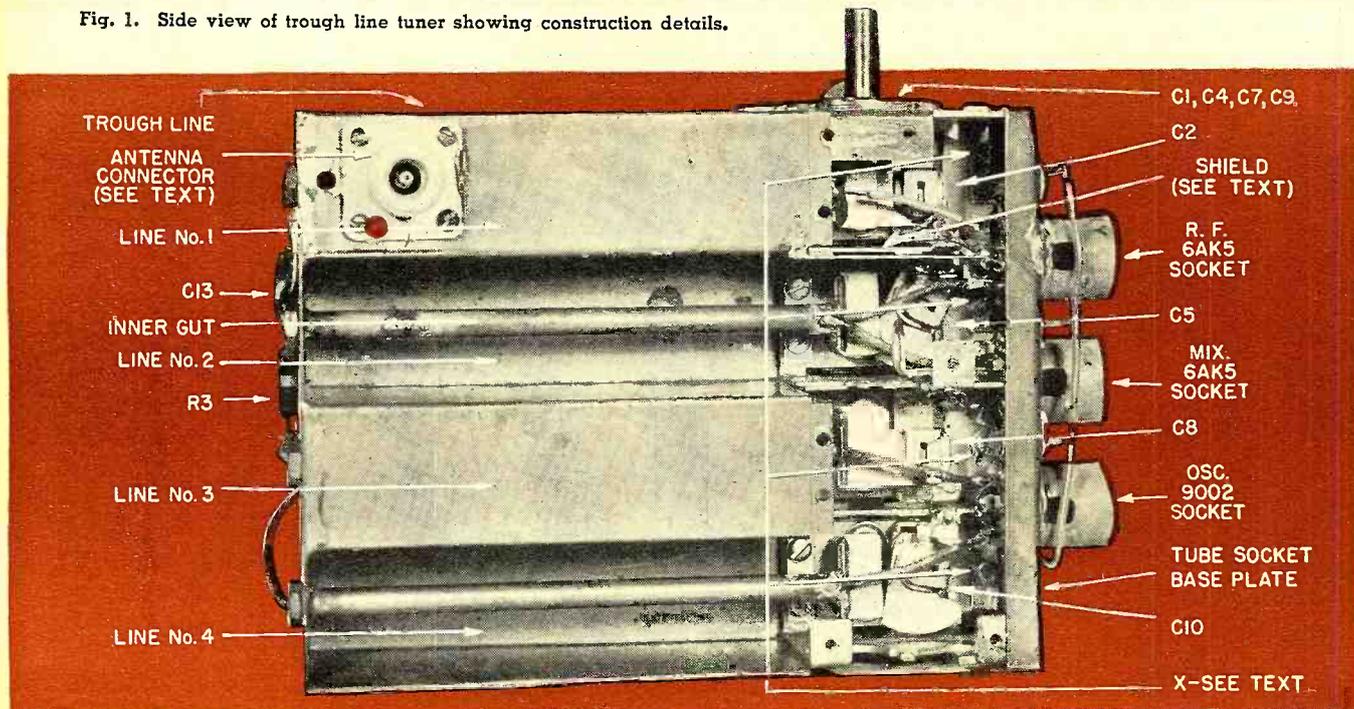

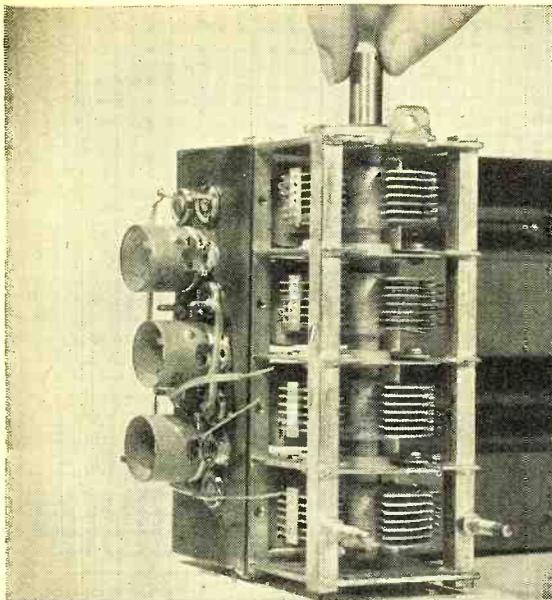


Fig. 2. Top view of trough line tuner. Note position of tube sockets and button mica condensers.

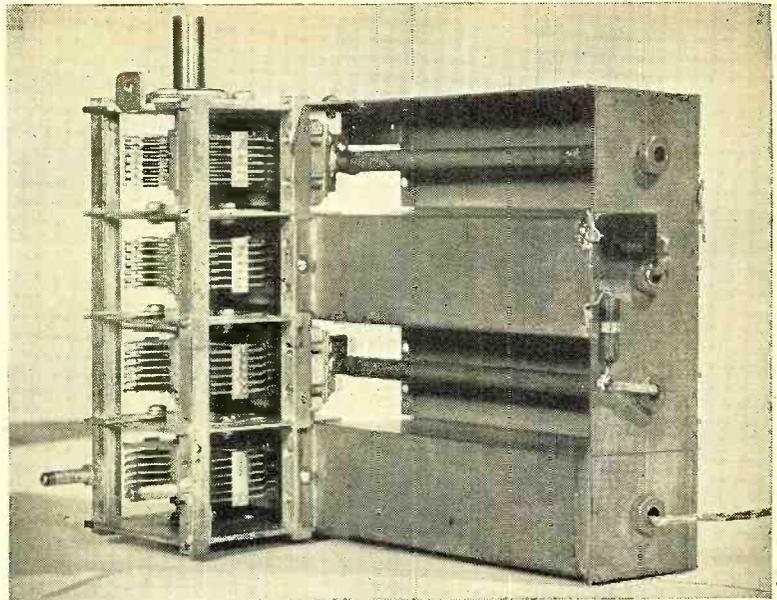


Fig. 3. Under chassis view. The resistor is R_3 and condenser is C_{13} . Wire emerging from "inner cut" line #4 (bottom) is connection "B+."

$\mu\text{fd.}$ fixed condenser should be connected between the grid and plate of the oscillator tube.

The entire unit is constructed around a 4-gang tuning condenser which was obtained in the surplus market. This condenser is of the split-stator, floating-rotor construction, and has a ceramic shaft and ball bearings. It has 90 degree rotation and a minimum capacity per section of $8 \mu\text{fd.}$ and a maximum capacity of $38 \mu\text{fd.}$ per section. The two outside rotor plates of each section have a number of small slots running almost all the way to the hub, which greatly facilitates alignment. These condensers may be obtained from several surplus sources, among them *Sherwood Associates*, Box 327, Jackson Heights, N. Y.

In order to start construction of the unit, obtain a piece of half hard brass or copper $1\frac{1}{2}$ " long, $7\frac{1}{8}$ " wide and $\frac{1}{32}$ " thick. Cut the bend as shown in Fig. 6. Obtain another piece of the same material $4\frac{1}{16}$ " long and $1\frac{1}{8}$ " wide


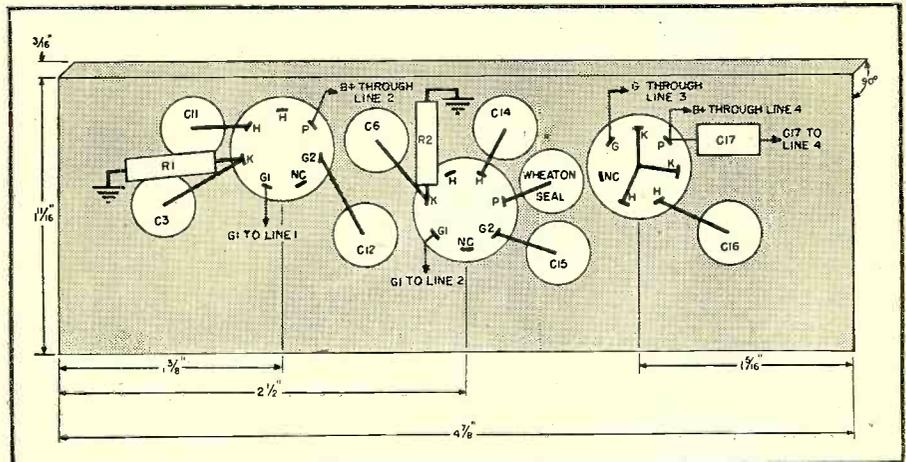


Fig. 4. Tube socket base plate shows relative position of component parts.

and drill as shown in Fig. 6. Assemble these two plates to the tuning condenser, as shown in Fig. 1, soft soldering all points of contact.

The tubes and button mica condensers are assembled on a plate which is drilled in accordance with
(Continued and page 174)


Fig. 5. Complete schematic diagram of the trough line tuner.

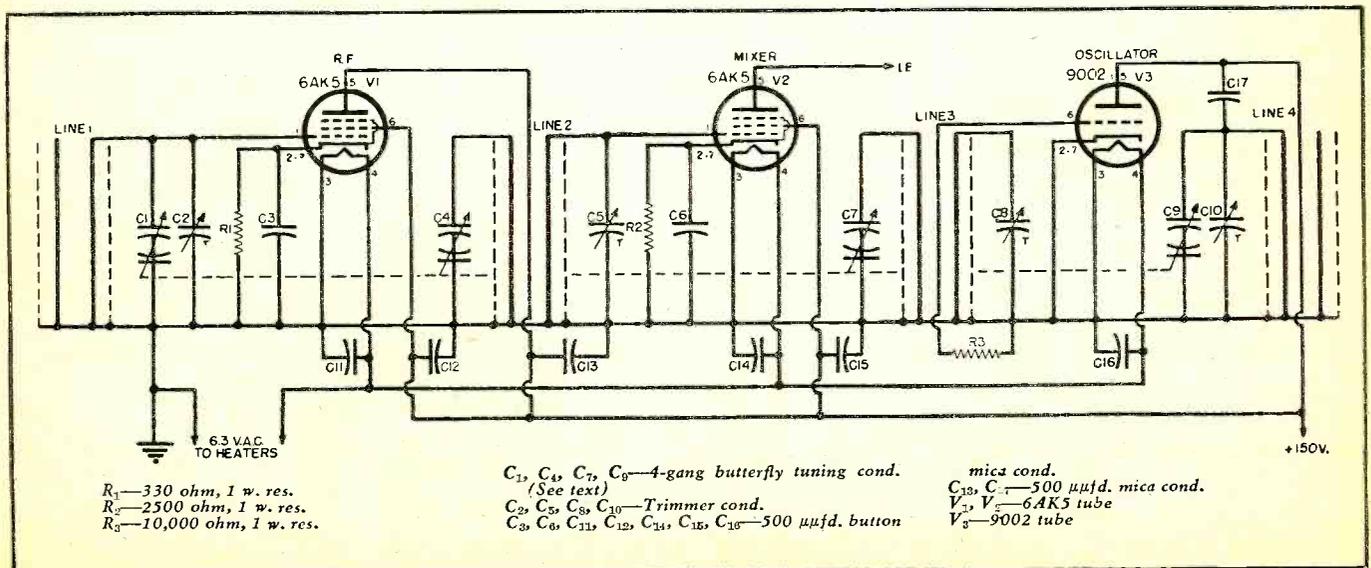

A Universal A.F.-R.F. WATTMETER

Fig. 1. External view of wattmeter. Instrument is small enough to be held in one hand.

By
GUY DEXTER

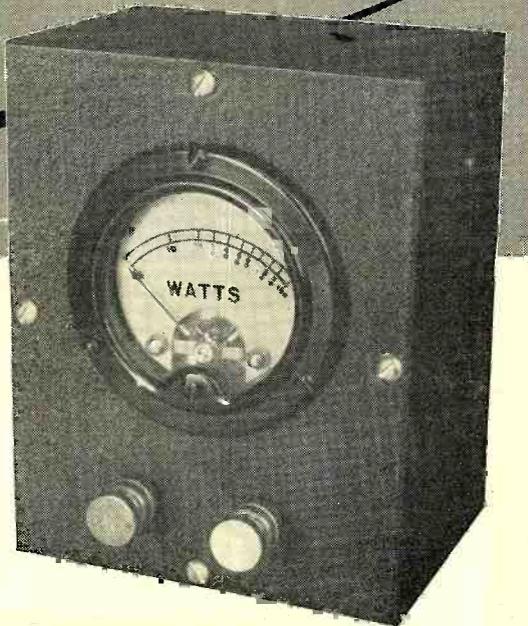

Construction details for a simple crystal type wattmeter for audio and radio frequencies. Instrument is a direct-reading unit.

THE busy radio technician should be able to measure watts as easily as volts, milliamperes, and ohms. There is no doubt that a direct-reading output wattmeter is a useful addition to any test bench. If the instrument will measure radio-frequency as well as audio-frequency power, it will be equally useful in the transmitting station and radio shop. Wattmeters are not owned by more radio men chiefly because the manufactured instruments are costly. Furthermore, most available wattmeters are suitable only for a. f. measurements.

A few everyday applications of a direct-reading output wattmeter for a. f. and r. f. are measurements of (1) receiver power output; (2) p. a. amplifier output; (3) transmitter r. f. oscillator output; (4) exciter output; (5) complete transmitter output; (6) power output of such test instruments as a power-type r. f. signal generator or audio test oscillator; and (7) power output of industrial and scientific instruments and devices, such as r. f. heaters, supersonic generators, and diathermy machines. Obviously, there are many other applications too numerous to mention here.

The compact wattmeter described in this article may be made direct reading from $\frac{1}{4}$ to 100 watts a. f. or r. f. It is small enough in size to be held in one hand, and uses no tubes, batteries, or power supply. It does not have to be connected to the electric power line. All parts used in this instrument are standard components which are obtained easily at any radio store. The design is extremely simple, so that any radio man can duplicate the instrument without difficulty. If the builder takes the time to make a special meter scale, or to inscribe wattage figures on the regular scale of the milliammeter used in this instrument, reading the wattmeter will be a simple operation.

Operating Principle

The wattmeter shown on these pages operates on the simple principle of determining power in watts from a voltage drop across a known resistance. The resistance is connected to the output terminals of the power-delivering device, such as an amplifier or oscillator, under test. The power (in watts) in such a test circuit is equal to the square

of the voltage (E^2) divided by the resistance (R). Basically therefore the instrument is an a.f.-r.f. voltmeter operated in parallel with a standard resistor of constant ohmage. An a.c.-type vacuum tube voltmeter usually is employed for this purpose.

Here is an example of the voltage method of determining power output: A certain amplifier has an output impedance of 500 ohms. We connect a 500-ohm, non-inductive load resistor temporarily to the amplifier output terminals in place of the loudspeaker or line, and connect an a.c. voltmeter (one which has good frequency response) in parallel with the resistor. We then apply a sine-wave audio signal to the amplifier input terminals and adjust the amplifier gain controls for maximum undistorted output. We read the output voltage (E) which is set up across the 500-ohm resistor (R). Let us say this voltage is 5. The power output in watts (P) then is determined from the formula $P = E^2/R$. In this case, $P = 5^2/500 = 25/500 = 0.05$. The power output therefore is 0.05 watt or 50 milliwatts.

From the preceding discussion, it is easily seen that if R is made 1 ohm, the denominator of the E^2/R fraction becomes 1, and one calculation (division) is eliminated. Moreover, if the voltmeter scale is graduated in *volts squared* instead of volts (that is, marked off to read say 1, 4, 9, 16, 25 instead of 1, 2, 3, 4, 5), *all* calculations are eliminated and the voltmeter reads directly in watts.

These last operations simplify considerably the job of reading watts output by the voltmeter method. A direct-reading wattmeter is produced, but in this form the instrument is accurate only when the output impedance of the amplifier or other device under test is 1 ohm. Many various output impedance values from 1 ohm to several thousand ohms are encountered in practice and a universal wattmeter must be able to match any of these values, not just 1 ohm alone.

One simple scheme for impedance matching over a wide range of values results in the instrument circuit shown in Fig. 2. Here the voltmeter (reading in watts) is connected permanently across the 1-ohm resistor, R^2 . Enough extra resistance, represented by R^1 , is added in series to bring the total resistance $R^1 + R^2$ up to equal the output impedance of the device under test. Thus, when we must match a 100-ohm output, we make R^1 99 ohms. $R^1 + R^2$ then equals $99 + 1 = 100$ ohms. Addition of the external resistance will not disturb the watts calibration of the meter scale. Whenever power measurements are to be made in conjunction with a 1-ohm impedance, R^1 is made zero—that is, terminals A and B (Fig.

2) are short-circuited temporarily for the test.

If R^2 is made 1 ohm, we see (from the basic E^2/R formula) that a 0-10-volt meter range will indicate 0-100 watts when R^1 equals zero. For all other values of R^1 (corresponding to similar values of output impedance), the wattage indications must be multiplied by $R^1 + R^2$. Thus; a $\frac{1}{2}$ -volt deflection of the voltmeter indicates $\frac{1}{4}$ watt when R^1 is zero. But when matching a 500-ohm output, $R^1 = 499$ and $R^1 + R^2 = 500$. The same $\frac{1}{2}$ -watt deflection of the meter must then be multiplied by 500 and would indicate 125 watts instead of $\frac{1}{4}$ watt.

Complete Instrument

The complete a.f.-r.f. wattmeter circuit is given in Fig. 3. The simplicity of the instrument will be evident from this schematic and from the photograph, Fig. 1.

The indicating meter, M , is a regular 0-1 d.c. milliammeter. This meter, the 1N34 crystal diode, bypass condenser C , and calibration rheostat R^1 comprise a simple a.f.-r.f. voltmeter. Response of the voltmeter circuit is linear for full-scale voltages of 10 and higher, which makes calibration easy. The 0-10-volt range is used here. The voltmeter has excellent frequency response (negligible frequency error) throughout the audio spectrum and is useful up to several hundred megacycles.

The crystal voltmeter is connected in parallel with the 1-ohm, 100-watt standard resistor, R^2 . Input terminals 1 and 2 are connected, in use, to the output terminals of the power-delivering device under test. Terminals 3 and 4 are connected to an external 100-watt load resistor, such as R^3 shown in dotted lines. The total resistance of R^2 plus R^3 must equal the output impedance of the device under test.

Provision is made for connection of an external load resistor, since it would be physically impractical to mount inside the instrument case enough fixed resistors, to be selected by a rotary switch, to take care of the multitude of output impedance values run across in practice.

Construction

The complete wattmeter (See Fig. 1) is built in a 4" x 5" x 3" metal box. This box is a standard item obtained at radio stores. A 2-inch milliammeter is employed in the author's instrument.

Input terminals 1 and 2 are seen directly below the milliammeter in Fig. 1. These terminals are heavy duty binding posts insulated from the metal box by means of polystyrene washers. Load resistor terminals 3 and 4 are on the left-hand side of the box and are not visible in Fig. 1.

The calibration rheostat, R^1 , is a min-

ature 10,000-ohm wirewound unit with its shaft sawed off short and slotted for screwdriver adjustment. This rheostat is mounted on a metal bracket inside the instrument box. When the rheostat has been set, in the calibration process, it usually does not have to be touched again unless the crystal diode is replaced or the rheostat adjustment disturbed.

All wiring is done with rigid bus bar and connections are kept as short as possible. Since the wattmeter is intended for r.f. measurements, sharp corners and coiling in wiring must be avoided. Adequate clearance must be provided between the input terminals and the metal panel by making large clearance holes for the terminal screws to pass through. This will eliminate short-circuit (grounding) hazards and will minimize shunt capacitances.

The crystal diode must be connected, by means of its own pigtail leads, between the rheostat and input terminal No. 3. Correct polarity of both crystal and milliammeter must be observed. Follow the polarity markings shown in Fig. 3.

It is not necessary to stick to the size and shape of meter case employed by the author. An individual builder may satisfy his own tastes concerning arrangement and size of his wattmeter. Some builders, for example, will prefer a sloping-front cabinet and may favor a 3-inch or larger milliammeter.

Adjustment and Calibration

Adjustment and calibration of the instrument are made easy by the linearity of the voltmeter circuit. Single-point calibration is all that is required.

To make the single adjustment: Disconnect temporarily one end of the 1-ohm resistor, R^2 , and short-circuit terminals 3 and 4. Apply an accurately-known 10-volt r.m.s. signal to input terminals 1 and 2 and adjust rheostat R^3 for exact full-scale deflection of

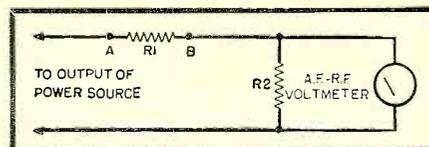


Fig. 2. Simplified circuit of wattmeter. Basic 0-100 watt scale of the meter is read when R^1 equals zero. For all resistance values multiply meter reading by sum R^1 and R^2 . R^2 should be 1 ohm while the sum of R^1 and R^2 should equal the output impedance of the device under test.

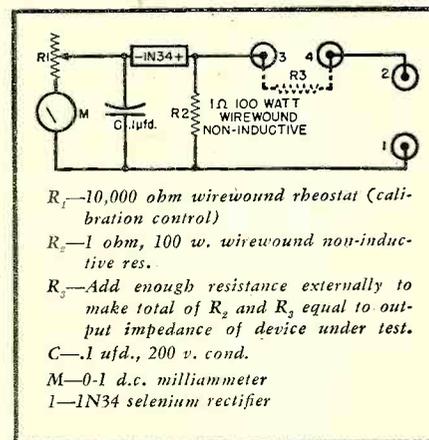


Fig. 3. The a.f.-r.f. wattmeter circuit.


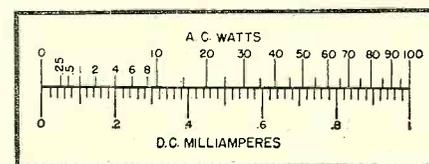


Fig. 4. Comparison of wattage and current scales. 1 milliamper equals 100 watts.

meter M . The rheostat setting will be determined by the conduction characteristic of an individual crystal. After this adjustment is made, remove the signal voltage source from terminals 1 and 2, remove the short-circuiting jumper

(Continued on page 193)

Fig. 5. Calibration curve of universal a.f.-r.f. wattmeter.

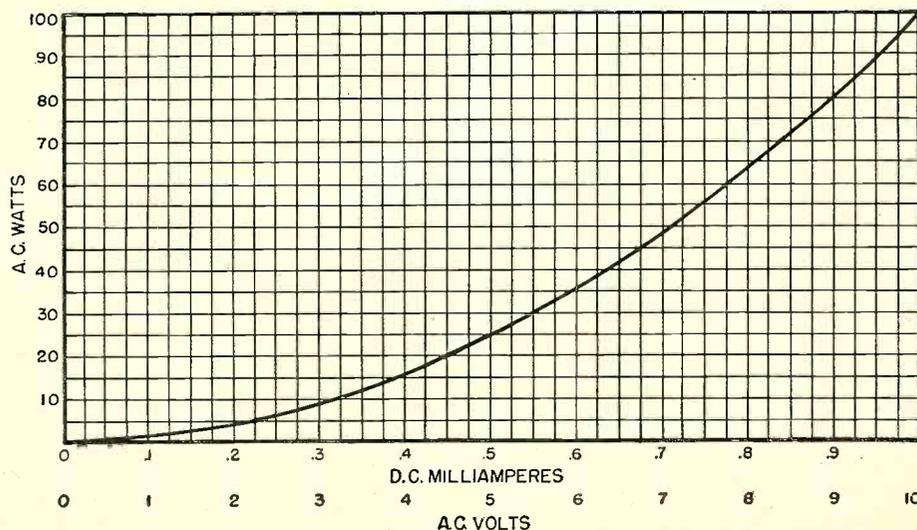

A REGULATED POWER SUPPLY

By D. H. ROGERS
Eng., Western Electric Co., Inc.

Design characteristics of a new, relatively simple shunt-type power supply regulator.

GOOD regulation is essential in power supplies furnishing plate power to high gain amplifiers, Class B amplifiers and stable oscillators, or bias to Class B and C amplifiers. In order to satisfy this requirement, the regulation of straightforward rectifier-and-filter supplies is improved by selecting heavy-duty, conservatively-rated components and arranging them in circuits which experience shows to be preferable. Mercury-vapor rectifiers, choke-input filters, and heavy bleeders are frequently used.

When better regulation is required than can be readily achieved by considering these factors, a series-valve regulator is sometimes selected. The basic circuit is shown in Fig. 1A. Here a tube, V_1 , is connected in the positive lead so as to form a valve which controls the output by means of the voltages applied to its grid. The grid is driven by a d.c. amplifier tube V_2 which picks up and amplifies any variations in the output voltage. V_1 then operates so as to correct these variations.

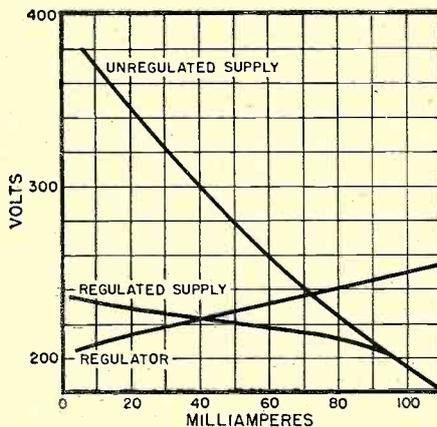


Fig. 2. Graph shows regulation obtained by means of new circuit shown in Fig. 1C.

In detail, the grid of V_2 is normally slightly negative, at a potential equal to the difference between the drop in the negative portion of the bleeder, which applies a large positive voltage, and the slightly larger negative voltage of the bucking battery. A large fraction of any increase in output volt-

age therefore appears on the grid of V_2 , and produces an increase in plate current. The increased drop across the load resistor R_1 causes the grid of V_1 to become more negative, thereby increasing its impedance to the output current and tending to reduce the output voltage.

Tube V_1 must be large enough to pass the full load current with low voltage drop, and to dissipate comparatively large amounts of power when the drop across it is high. A 2A3, 6L6, or 6Y6G is usually chosen for this service, or two of them in parallel. Tube V_2 may be any suitable voltage amplifier such as a 6SJ7.


In some designs the battery is omitted, and bucking obtained from the constant voltage drop across a gas discharge tube inserted in the cathode lead of V_2 . The bucking battery affords slightly superior regulation and permits design for slightly lower output voltages, but it requires periodic replacement on a shelf-life cycle. The condenser shown in the diagram is used to feed back all hum appearing in the output so that it will be degenerated. This action provides improved filtering.

A second common type of regulator works by shunt loss. In it the regulating element acts as a variable shunt, compensating for varying external load by presenting an alternate internal load, and increasing the load with higher line voltage so that the excess is taken up by internal drop. The most widely used shunt regulator is the VR type of gas-discharge tube, which shows a comparatively high voltage drop but very little change in drop with change in current. Or to put it the other way around, it requires a fairly high voltage to sustain a discharge but relatively small increases in voltage over this critical value will cause relatively large currents to flow. With these tubes, lumped resistance must often be added to increase the source impedance to the point where the current will remain within safe limits under the lightest load condition to be encountered. The basic circuit is shown in Fig. 1B.

Another way to obtain shunt regulation is to connect a battery of the proper voltage across the supply, usually a storage battery. Circuits may also be designed in which the shunt element is a vacuum tube controlled by a d.c. amplifier feeding back degeneratively any discrepancy between the output and a reference bucking voltage, in the same fashion as in the series circuits. One important advantage of shunt regulators over the series type is that they will pass a reverse current entering the supply from the load, with the same ease as a normal forward current. This characteristic makes them suitable for furnishing bias to tubes drawing grid current, whereas a series regulated supply will present an impedance equal to its bleeder under these conditions.

A new and comparatively simple shunt regulator circuit is shown in (Continued on page 195)

Fig. 1. Three methods that may be used for power supply regulation: (A) series type, (B) shunt regulator, and (C) new Western Electric circuit covered in this article.

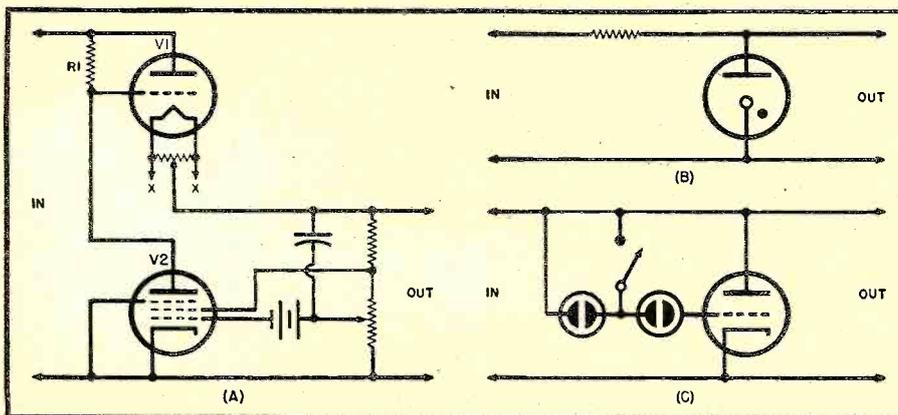

360 Watt TRANSMITTER for PHONE or NBFM

THE NEW 360 watt transmitter at W2GSN was designed to provide a compact unit for 10, 20, and 40 meter c.w., phone, or narrow-band FM transmission. Features of the transmitter include convenient switching; adequate metering for adjustment of all stages; rectified bias supplies to eliminate batteries; and facility for the adjustment of final tubes to normal ratings in all operating conditions. A pair of 3D24 tubes was selected as the final tubes for reasons of low driving power and no neutralization required.

The conventional circuit used, exclusive of exciter unit, is shown in Fig. 2. Front view of transmitter, which is housed in a cabinet 28" high, 14 3/4" deep and 22" wide, is shown in Fig. 1. Power pack including 807 supply at left, 3D24 supply at right and the small metal box housing the two bias supplies is shown at left in background of Fig. 6. Figs. 3 and 4 show side and rear views of the transmitter removed from cabinet.

The transmitter was designed for use with available low cost exciters such as the Meissner "Signal Shifter" and Sonar "FX" narrow-band FM unit. Operation may be switched from c.w. to plate modulation by means of S_2 shown in Fig. 2. This switch energizes No. 1 relay to open the plus lead of the 3D24 supply and add modulation transformer ahead of resistors R_6 , R_7 and R_8 . S_2 also energizes the No. 2 relay to cut out the c.w. self bias resistor, R_{11} , and cut in plate modulation self bias resistor, R_{12} . Since the 3D24 is a tetrode and linear modulation depends on linear variation of space current, both plate and screen must be modulated.

R_6 , R_7 and R_8 serve as a power supply bleeder and also to feed screen voltage to the 3D24 tubes. R_7 is variable to provide close screen voltage adjustment for c.w. and phone. Linear variation of both plate and screen voltage is provided by placing the modulation transformer ahead of the three resistors. The filters L_4C_{12} , L_5C_{13} , placed in the 3D24 plate leads are tuned to 57 mc. to prevent television interference from harmonics of the fundamental frequency. This arrangement also helped on the fourth harmonic during 20 meter operation when television channel No. 2 was on the air.

Power supplies shown in Fig. 6 include bias providing correct voltage values for 807 and 3D24 grids for complete cut-off when excitation is removed. Voltage dividing resistors, which provide correct screen voltage for 3D24 tubes, are mounted beneath the compact chassis in such a way as to facilitate easy replacement of parts.

Figs. 3 and 4 show a side and rear view of the complete transmitter removed from its cabinet. All d.c. leads are electrostatically shielded. The final tank condenser is mounted on insulated blocks. Its rotor is grounded at the center to the common r.f. ground point for final tube filaments and screens. The 3D24 tubes are mounted in shielded wells, recessed to the bottom edge of their anodes. Recessing provides proper shielding for filament and grid leads. Holes provided in the wells allow a free flow of air over the tubes. The copper enclosure at right of the 3D24 tubes is a shielded box housing the 807 buffer amplifier shown in Fig. 7.

May, 1948

By

R. N. PALMER, W2GSN
H. C. N. LONGACRE
Sylvania Electric Products Inc.

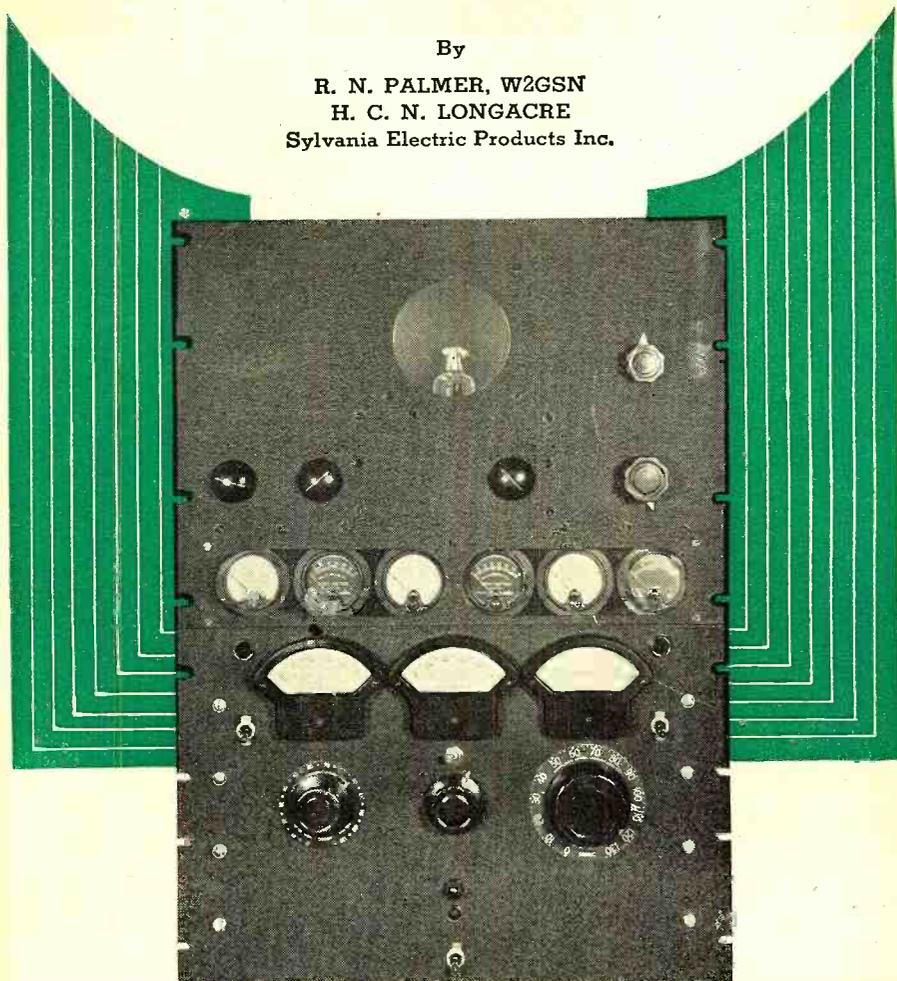


Fig. 1. Front view of W2GSN's 360 watt transmitter. Meters (left to right top row) are; buffer grid current, buffer screen current, buffer plate current, final grid current, final screen current, and final plate current. Meters (bottom row) indicate plate voltage and bias voltages.

**Flexible, compact design for 10, 20, or 40 meter operation
uses 4-watt exciter and eliminates need for neutralization.**

The tuned grid stage is shown in the rear with a copper shield between the input and output stage. Coupling leads between the 807 output and 3D24 grids feed through the side wall to a point equidistant from each tube where the 3D24 grid coil is located, as shown in Fig. 5, a bottom view of the buffer and final amplifier chassis. Filament transformers for the 3D24 and 807 tubes are shown to the right. Shielding of the buffer and final stage is complete and neutralization is entirely unnecessary. Band switching is completely eliminated to keep the unit as small as possible and to eliminate switch contact trouble. All coils are easily accessible for quick band change. The 80 meter band, which has not been included in the design, can be easily accommodated by the

insertion of a 25 mmfd. padding condenser across the grid and plate tank of the final stage.

The exciter unit, connected by 300 ohm line feeding through the upper left side of the cabinet, may be placed anywhere near the transmitter. Antenna connection is also made with 300 ohm transmission line passing through the upper right side of the cabinet. The modulator is connected by the large Jones plug shown at the lower left of the plate supply in Fig. 4.


A Sonar narrow-band FM exciter is used for both c.w. and phone and eliminates the need of a 180 watt modulator for phone operation. Final tubes are operated for narrow-band FM under the same conditions used for c.w., providing higher power output

than would be possible with plate modulation. If plate modulation is used, the secondary of the modulation transformer should be connected to pins 1 and 3 on the 4 prong plug.

Transmitter Adjustments

After a one minute filament warm up, the external driver stage is adjusted to the proper frequency. The 807 grid circuit is then tuned to resonance, indicated by a maximum deflection of its grid current meter. The 807 power supply adjusted to about 400 volts is then applied and the 807 plate tank condenser is adjusted for minimum dip of the 807 plate current meter. A signal voltage is now being supplied to the 3D24 grid coil and by tuning the 3D24 grid stage, resonance is obtained and is indicated by a maximum deflection of the 3D24 grid current meter. With the signal applied to the grids of the 3D24 tubes, the 3D24 power supply is switched on and adjusted to about 1000 volts. With loose coupling to the load circuit, the plate tank circuit should be tuned to resonance, indicated by a minimum deflection of the plate current meter. With resonance obtained, the load circuit is adjusted to draw 90 ma. plate current.

Fig. 2. Schematic diagram of 360 watt transmitter. Note that the new 3D24 tubes are used. These tubes have the advantage of low driving power and they automatically eliminate all neutralization problems.

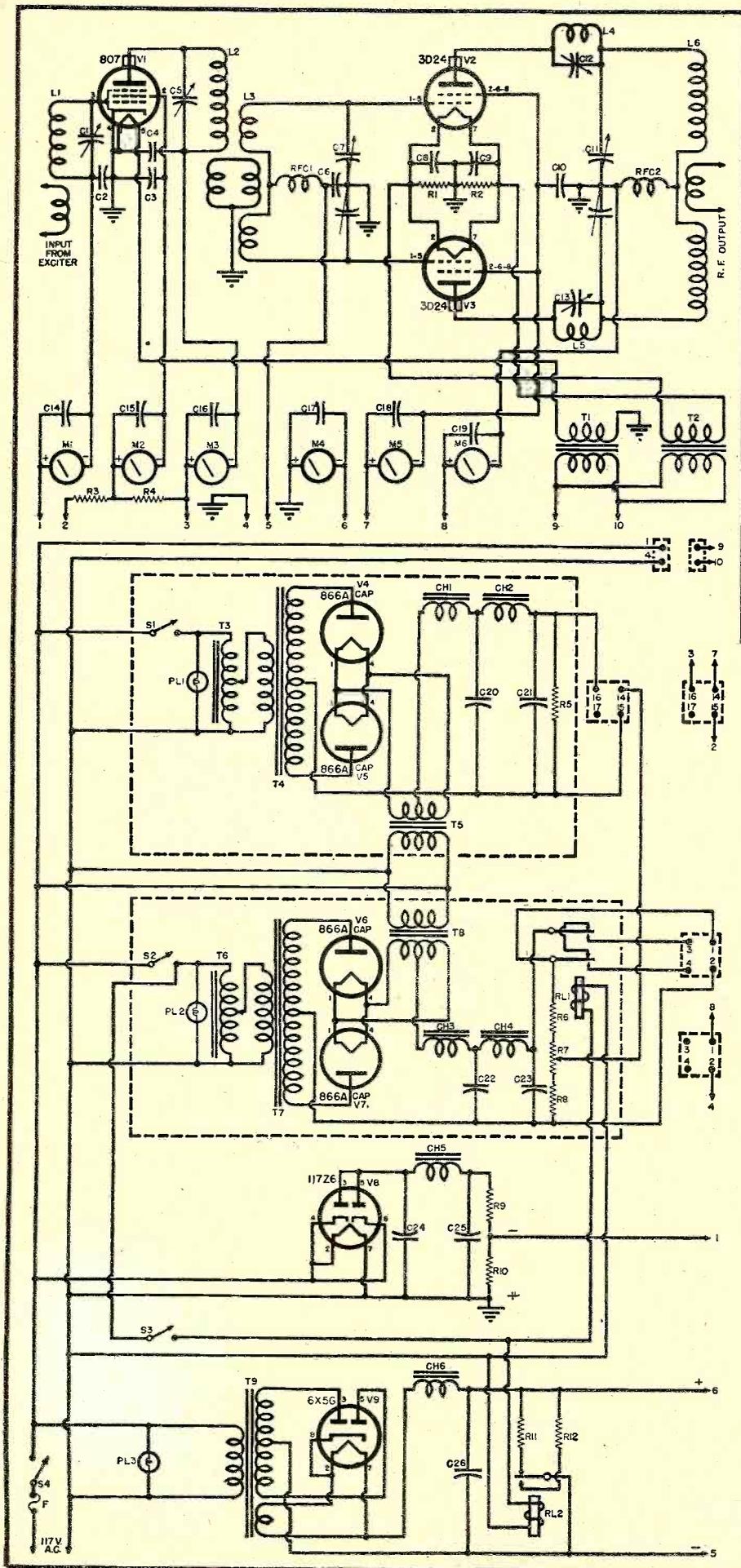

- R₁, R₂—5 ohm, 10 w. wirewound res.
- R₃—25,000 ohm, 20 w. wirewound res.
- R₄, R₅—20,000 ohm, 20 w. wirewound res.
- R₆—27,000 ohm, 50 w. wirewound res.
- R₇—10,000 ohm, 50 w. wirewound pot.
- R₈—8,500 ohm, 50 w. wirewound res.
- R₉, R₁₀—10,000 ohm, 2 w. res.
- R₁₁—15,000 ohm, 10 w. wirewound res.
- R₁₂—10,000 ohm, 10 w. wirewound res.
- C₁—70 μfd. var. air cond. (Johnson No. 70H15)
- C₂, C₃, C₄, C₁₀—0.002 μfd., 600 v. mica cond.
- C₅—0.002 μfd., 1000 v. mica cond.
- C₆—70 μfd. var. air cond. (Johnson No. 70H30)
- C₇—100/100 μfd. dual var. air cond. (Johnson No. 100HD15)
- C₈, C₉—0.2 μfd., 400 v. mica cond.
- C₁₁—100/100 μfd. dual var. air cond. (Johnson No. 100DD70)
- C₁₂, C₁₃—35 μfd. var. air cond.
- C₁₄, C₁₅, C₁₆, C₁₇, C₁₈, C₁₉—0.1 μfd., 400 v. cond.
- C₂₀, C₂₁—10 μfd., 600 v. oil-filled cond.
- C₂₂, C₂₃—4 μfd., 2000 v. oil-filled cond.
- C₂₄—1 μfd., 200 v. elec. cond.
- C₂₅—16 μfd., 200 v. elec. cond.
- C₂₆—16 μfd., 600 v. elec. cond.
- L₁, L₂—10, 20, 40 meter coils, 75 w. (Bud OEL)
- L₃—10, 20, 40 meter coils, 75 w. (Bud OCL)
- L₄, L₅—9 L., No. 12 copper wire, 1/2 diam., 1 long
- L₆—10, 20, 40 meter coils, 500 w. (Bud VLS)
- PL₁, PL₂, PL₃—110 v. pilot light
- M₁—0.15 ma. d.c. grid current meter
- M₂—0.35 ma. d.c. screen current meter
- M₃—0.100 ma. d.c. plate current meter
- M₄—0.35 ma. d.c. grid current meter
- M₅—0.100 ma. d.c. screen current meter
- M₆—0.200 ma. d.c. plate current meter
- RFC₁—2.5 mh., 150 ma. r.f. choke
- RFC₂—2.5 mh., 500 ma. r.f. choke
- RL₁—117 v., a.c., d.p.d.t. relay (Leach type 117C.B.F.)
- RL₂—117 v., a.c., s.p.d.t. relay
- T₁—Fil. trans., 6.3 v. at 3 amps. (Kenyon No. T351)
- T₂—Fil. trans., 6.3 v. at 8 amps. (Kenyon No. T368)
- T₃—110 v., 1 amp. Variac (Kenyon No. T655)
- T₄—Plate trans., 575-0-575 v. at 250 ma. (Kenyon No. T655)
- T₅, T₈—Fil. trans., 2.5 v. at 10 amp. (Kenyon No. T352)
- T₆—110 v., 5 amp. Variac (General Radio V5)
- T₇—Plate trans., 2360-0-2360 v. at 300 ma. (Kenyon No. T670)
- T₉—Power trans., 210-0-210 v. at 40 ma.; 6.3 v. 2 amps. c.t.; 5 v. at 2 amps. (not used) (Stancor P6289)
- CH₁, CH₂—10 hy., 150 ma. filter choke (Kenyon No. T165)
- CH₃—5-20 hy., 400-50 ma. swinging choke (Kenyon No. T516)
- CH₄—10 hy., 250 ma. filter choke (G.E. K34J253)
- CH₅, CH₆—10 hy., 60 ma. filter choke
- S₁, S₂, S₃, S₄—S.p.s.t. toggle sw.
- F—15 amp. fuse (Littelfuse 3AB)
- V₁—807 tube
- V₂, V₃—3D24 tubes
- V₄, V₆, V₇—866A tubes
- V₉—6X5G tube

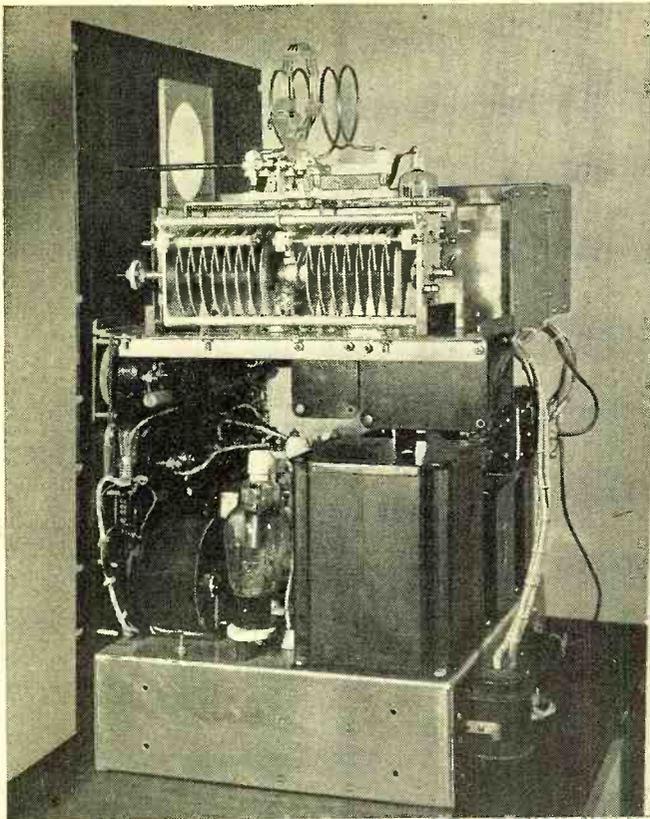


Fig. 3. Side view of transmitter shown removed from cabinet. The entire unit is housed in a cabinet 28 x 14 $\frac{3}{4}$ x 22 inches.

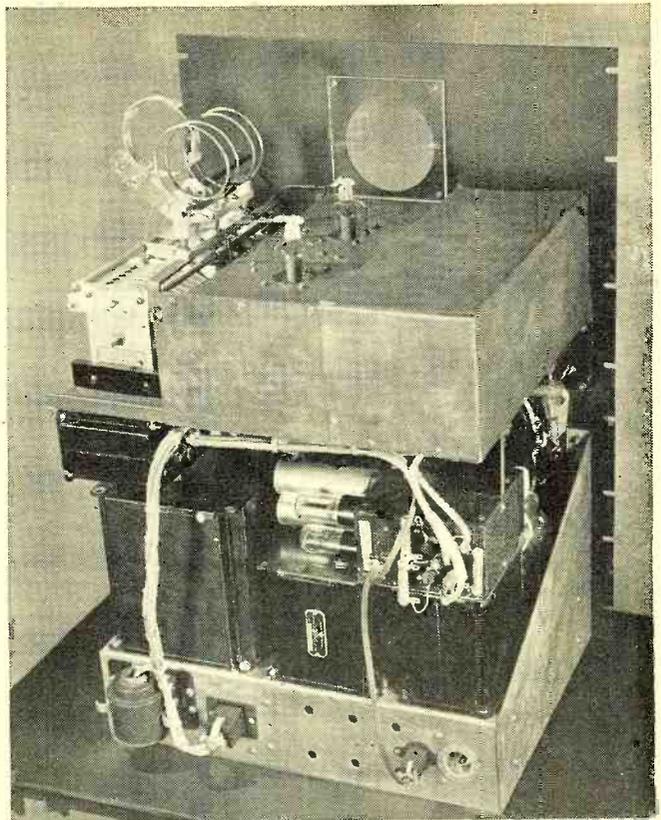


Fig. 4. Rear view of transmitter. The small assembly lying on its side, under top chassis, is the bias supply pack.

The next step is to increase the 3D24 plate voltage gradually to 2000 volts making sure that plate current does not exceed 180 ma. Retuning the plate tank will be necessary as the load is increased. Screen voltage should be adjusted to 375 volts after the loading and plate tank are properly adjusted.

A slight readjustment of both the 807 and 3D24 stage will tune the transmitter to maximum efficiency. The final stage when properly tuned and adjusted for c.w. or narrow-band FM CCS conditions will show plate current at 180 ma. and grid current at 20 ma. when plate voltage is set at 2000 volts, the screen at 375 volts, and the developed grid bias is 300 volts.

For plate modulated phone, the transmitter is adjusted as described above except that plate voltage is adjusted to 1250 volts, screen to 300 volts for 140 ma. plate current

and 20 ma. grid current with developed grid bias of 200 volts.

Chassis and Cabinet Arrangement

In the completed unit shown in Fig. 1 the lower panel and chassis holds all the power supplies, voltage controls, and voltmeters. At bottom center is the main switch for power to all filaments, bias supplies, and plate switches. A pilot light and fuse are mounted above. Switch for the 807 d.c. supply is at the extreme left below an indicating pilot lamp. Next is shown the d.c. voltmeter and Variac control for the 807 supply. The voltmeter for 3D24 screen voltage is located at center. Directly below is the switch for changing from c.w. or narrow-band FM to plate modulation. Below the switch is the 3D24 screen voltage control.

Next is the 3D24 plate voltmeter and below, the plate voltage Variac control. To the extreme right is the 3D24 power supply switch and above it a pilot light indicator.

The upper panel and chassis holds the 807 buffer amplifier stage at left, with final 3D24 push-pull amplifier from the center to the extreme right. Metering is as follows: left to right, 807 grid current, screen current, and plate current meters; and 3D24 grid current, screen current, and plate current meters.

Tuning knobs for the 807 and 3D24 stages are above the current meters. Both 807 and 3D24 stages are tuned plate, tuned grid circuits. Starting with the tuning knob at left are knobs for 807 buffer amplifier tube grid and plate. Next, are the tuning knobs for the grid and plate for the 3D24 final amplifier. (Continued on page 128)

Fig. 5. Bottom view of buffer and final amplifier assembly.


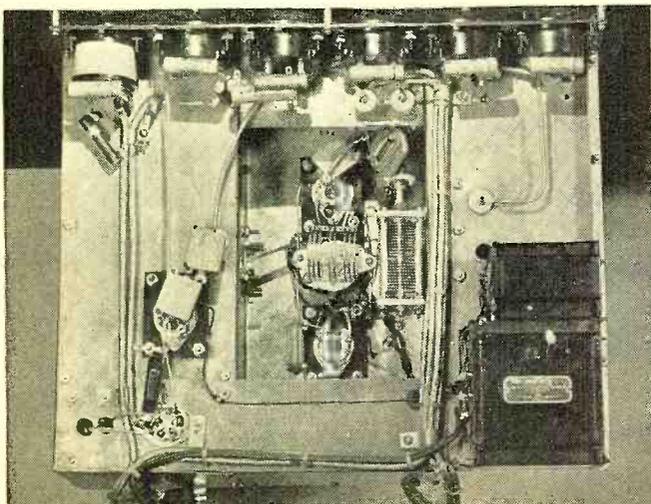



Fig. 6. Top view of power unit shows position of components.

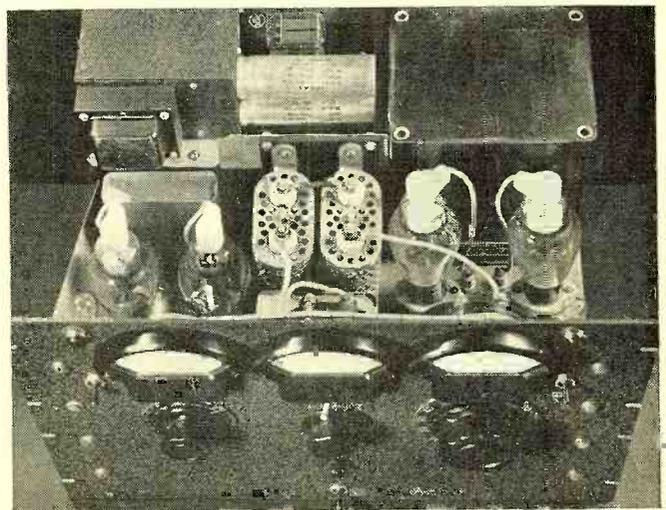



International SHORT-WAVE

Compiled by KENNETH R. BOORD

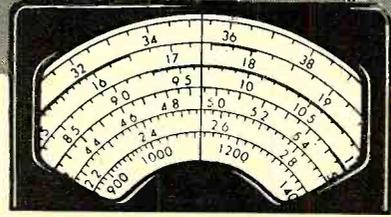

THIS month we are happy to salute HCJB ("Heralding Christ Jesus' Blessings"), "The Voice of the Andes," located in Quito, Ecuador, South America, the pioneer missionary broadcaster of the world.

As the silver wings of *Panagra* flash over the heart of the Andes, one sees the rugged form of old Mount Pichincha looming to the north of Quito. On the lower slopes of this extinct volcano, the plane passenger sees one particular spot of green on which cluster several buildings and a radio tower. *That is HCJB!*

The visitor to Quito who takes the time to stop in at "The Voice of the Andes" sees abundant evidence of the present-day working of God. For HCJB is the outgrowth of a vision of *reaching the regions beyond by radio*—doing missionary work in many fields from one spot.

Here is the story of HCJB as related to me by Clayton Howard, its chief technician:

HCJB was founded in 1931 by two men—Clarence Jones and Reuben Larson. Mr. Larson had been a missionary in Ecuador for a number of years and had felt that *radio* could be of great value in missionary work. Mr. Jones had had a great deal of radio experience in religious broadcasting in Chicago, USA, but had felt a call to use *radio* in the mission field. While Mr. Larson was on furlough, these two men met and soon

found that they had the same idea. They decided to see what could be done about it.

As soon as Mr. Larson returned to Ecuador, he approached the Government there and was able to secure a permit to operate a station for 25 years. Immediately, a 200-watt transmitter was purchased and was sent to Quito.

The city of Quito, capital of Ecuador, was chosen as the location although it is in the heart of the mountains at an elevation of 9500 feet and is about 12 miles south of the equator. Engineers had advised the use of Guayaquil, on the coast, as they said the mountains would affect transmission and that proximity to the equator would also be a distinct disadvantage. Nevertheless, Quito was chosen and both reasons given for "not" locating there have since been proved to be of great advantage.

The 200-watt transmitter was set up on a wavelength of 73 meters (4.107) and the first broadcast went out on Christmas Day, 1931. For the small group of missionaries gathered in the living room which served as studio in the HCJB home, the occasion meant much more than just another radio station "coming on the air." HCJB was the answer to years of faith and prayerful vision. Fervent and sincere were the grateful hearts that offered thanks to God for providing and preserving the

fragile equipment that had been transported thousands of miles to bring to pass another chapter in the romance of modern missions!

At that time, HCJB was the only station in Ecuador carrying regular programs, which makes HCJB actually the oldest station in that country. It is still the only station in the world owned and operated entirely by missionaries for the primary purpose of spreading the Gospel. Incidentally, at the time of the first programs, *there were only five or six radios in the entire country of Ecuador.*

From this humble beginning, HCJB has grown until it is what it is today. A station in the broadcast band (974 kcs.) soon was added to the original transmitter. In the spring of 1940, a new 10-kw. transmitter (12.455) was inaugurated by the President of Ecuador. At this time, the station moved to a new location (Inaquito) on the northern fringe of Quito. In 1942, a 30-meter channel (9.958) was added, and in 1943 wavelengths were added in the 19- and 49-meter bands (15.115 and 6.240). Just recently, 4.107 (73 m.) has been dropped, a *new* frequency of 5.995 (50 m.) has been added, and the use of 6.240 (49 m.) has been discontinued (at least for the time being).

In the meantime, personnel has increased from the two original families until now there are some 26 full-time

(Continued on page 134)


(Left) Enrique Romero, one of the Ecuadorean operators, handling studio controls at Station HCJB. (Right) HCJB's transmitter building and antenna arrays at Quito.



Additional Notes on

RECORDING

AMPLIFIER

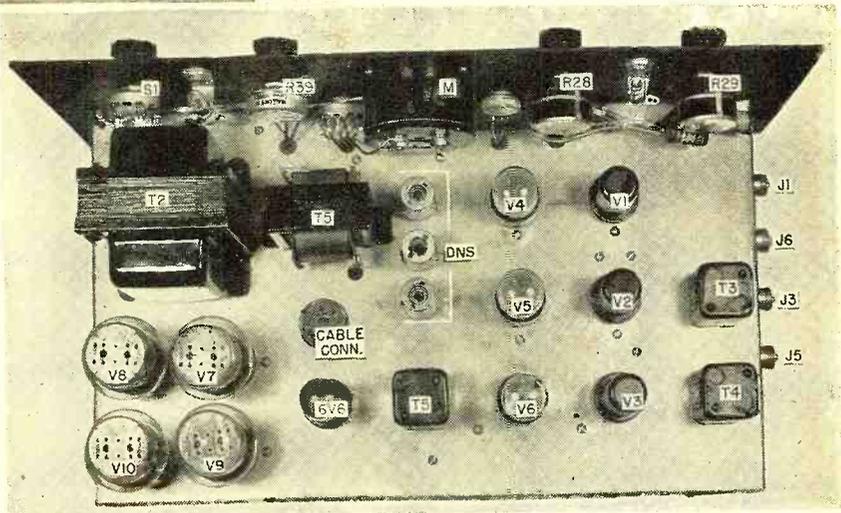

Top view of the improved recording amplifier showing location of important parts.

Improving the performance of the record-reproduce amplifier which appeared in the January 1948 issue.

THREE minor improvements have been incorporated in the original amplifier which have greatly enhanced its over-all performance. An increase in audio output (30 watts) has been made possible by employing fixed bias to the push-pull parallel 2A3's.

In order to supply the necessary bias voltage, an attempt was made to design a flexible circuit to meet this requirement. By employing selenium rectifiers in a full-wave circuit, the required bias is readily available.

Considerable hum reduction in the high gain preamplifier stages has resulted from the improved d.c. supply for the series filament string. A special transformer was designed (Stancor P-6349) which would not only provide 75 volts at 150 millamperes for the filaments, but would also supply the necessary 60 to 75 volts bias as previously explained.

By isolating this d.c. supply from a direct ground connection, which was not done in the original model, we eliminate the hazard of possible reversed polarity of the line supply in addition to reducing all traces of hum to a minimum. A 10,000 ohm, 50 watt adjustable voltage divided resistor makes it possible to adjust the ground point so that the plus 75 volt d.c. and the minus 60 to 75 volt bias may be set accurately to proper values.

A high fidelity output transformer (Stancor A-8060) was substituted for the A-7938 used in the original model. This unit is designed especially for fixed bias operation. By using fixed bias circuits, a power output of 30 watts at only 2.5% distortion is obtained without employing any feedback. This output is more than adequate to drive any high quality coaxial speaker system or magnetic cutter.

Isolating resistors have been inserted in series with each plate coming from the 12AH7 mixer tubes.

Dynamic Noise Suppressor

The original laboratory model was designed to include a three-tube Dynamic Noise Suppressor. Complete technical specifications were not available at the


time of the original design. Later experiments were continued in an attempt to find a trouble-free circuit that would use a minimum of components. It was discovered that the two special chokes required in the Dynamic Noise Suppressor were subject to considerable hum pickup when incorporated within the amplifier proper and in the space provided. We therefore recommend the construction of a separate unit, as de-


scribed in Part 15 of the recording series in this issue.

In answer to many requests for additional information on the name plates, these were made from regular printing cuts and were used simply to dress up the unit. Other suitable plates are, of course, to be found in most radio jobber catalogues.

Reference to the photograph will show
(Continued from page 144)

Diagram shows important changes which were incorporated in the new amplifier.

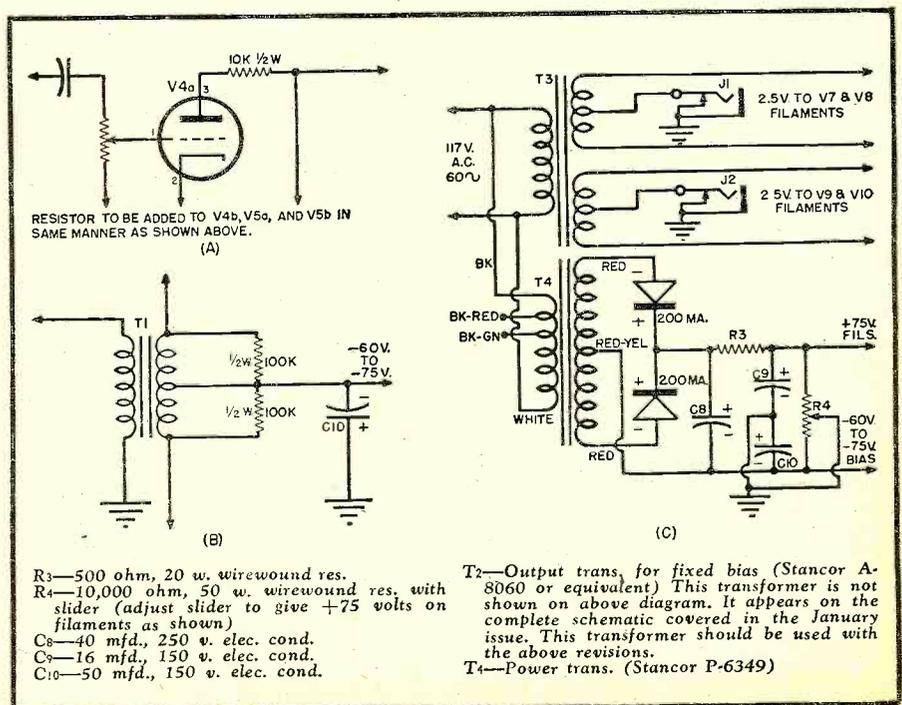

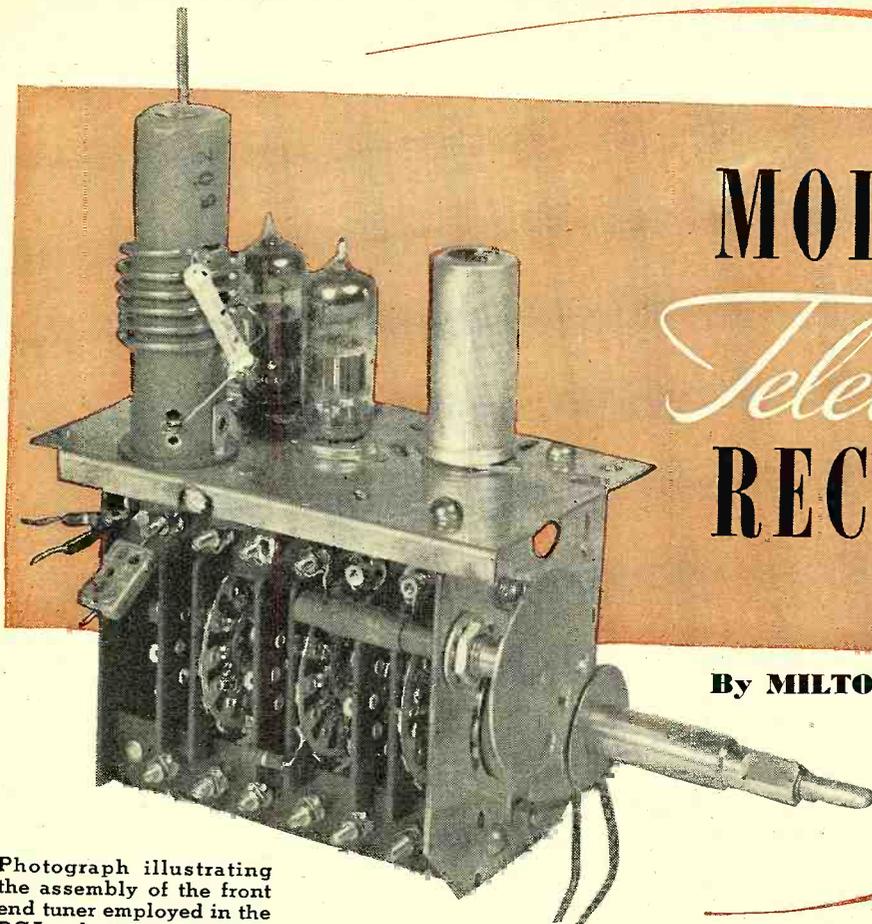


Photograph illustrating the assembly of the front end tuner employed in the RCA television receiver.

MODERN *Television* RECEIVERS

By MILTON S. KIVER

Part 2. A comparison of the design and operation of different oscillator circuits used in TV sets.

Fig. 1. Circuit diagrams show the similarities between the Colpitts (A) and the ultraudion (B) oscillators. The circuit diagram (C) illustrates how the ultraudion oscillator is usually drawn.

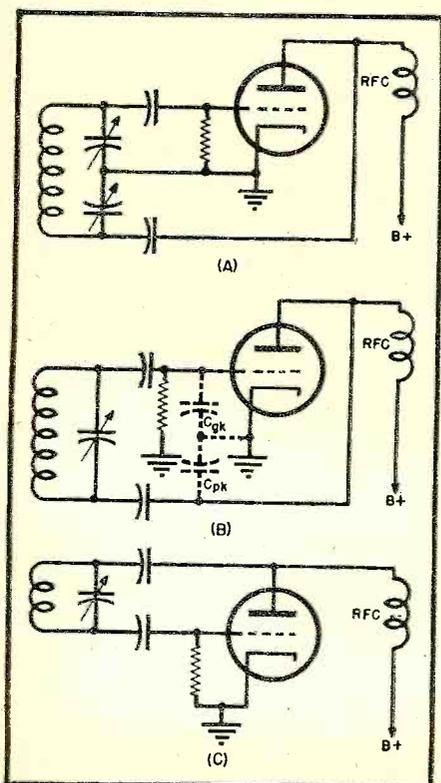

SINCE the television receiver is a superheterodyne, the incoming signal that was previously amplified by the r.f. stage is now ready to be converted to the lower i.f. value. Toward this end, the signal is transferred to a mixer stage where it is brought into electrical contact with the oscillator voltage.

Oscillator stability is one of the most important engineering aspects of television receivers and this is governed almost entirely by the FM audio signal. The signal spread of the FM audio signal is plus and minus 25 kc. and when this is compared to the 4.0 mc. of the video signal, it appears to be almost negligible. For this reason it is highly important that oscillator frequency drift be held to a minimum because even such a relatively small oscillator drift as .03 per-cent will, at 100 mc., shift the i.f. signal by 30 kc. or enough to produce a distorted sound output. To minimize drift, oscillators in television receivers are constructed as separate units, feeding their signal to the mixer by capacitive and/or inductive coupling.

Motorola Perhaps the most frequently employed oscillator circuit in current television receivers is the circuit shown in Fig. 1B. It is known as the ultraudion, and is equivalent in its action to the well-known Colpitts circuit. See Fig. 1A. In the ultraudion, the voltage division across the tank circuit is accomplished through the grid-to-cathode (C_{gk}) and the plate-to-cath-

ode (C_{pk}) capacities within the tube. The feedback voltage which sustains oscillations is developed across C_{gk} . In *Motorola* Model VT 101 receivers, the oscillator stage has the actual form shown in Fig. 2A and the equivalent network indicated in Fig. 2B. The tank capacity consists of the effective capacity of C_{gk} in series with the parallel combination of C_{pk} and C_1 , while C_T consists of the grid-plate capacity, C_2 , and the distributed capacity. C_2 is a temperature compensating condenser and helps reduce oscillator drift. In spite of this, some drift does occur, hence C_1 is provided to permit the set user to adjust the oscillator frequency for the best sound output. Because C_1 is actually a vernier adjustment it is labeled "fine-tuning control" and placed on the front panel. Condensers C_3 and C_4 keep the d.c. plate voltage off the exposed coils. C_4 also makes it possible for the oscillator to develop grid-leak bias across R_1 . A separate coil is brought in for each channel and each coil can be individually adjusted as to frequency. This is necessary because the oscillator frequency must be accurately set for each channel.

Modified Ultraudion In the Colpitts oscillator of Fig. 1A, it is entirely possible to shift the placement of the ground connection from the cathode to the plate end of the tank coil without affecting the operation of the oscillator. Now, however, we must provide a d.c. path from the cathode to ground, otherwise the tube electron flow will be

RCA Television Models The simulated quarter wave section transmission line tuner that RCA employs for their r.f. amplifier is also found in their oscillator circuit. See Fig. 7. The oscillator is actually a push-pull circuit with the r.f. plate voltage of one triode section feeding the grid of the other triode. The channel switch, as it progressively moves down the line, adds more and more

inductance to the line, effectively lowering the tank frequency. For tuning each channel, brass screws are placed close to the high-frequency tuning straps L_{14} , L_{16} , L_{18} , L_{20} , L_{22} , L_{24} , and L_{26} and brass cores are adjusted through coils L_2 , L_4 , L_6 , L_8 , L_{10} , and L_{12} .

C_1 is a fine-tuning control which is connected across the entire tuning line. It pro-

vides a frequency variation of approximately plus or minus 300 kc. on channel 1, and this increases to plus or minus 750 kc. on channel 13. Coupling between the oscillator line and mixer line is accomplished by a single turn of link coupling and physically locating the oscillator line close to the converter grid line.

Philco Receivers Philco television circuits employ an oscillator which at first glance appears to be similar to one of the preceding ultraudion oscillators. This much is true. See Fig. 5. However, further examination reveals that the second triode of the 6J6 is also connected across the oscillator and therefore would affect its operation. This second tube is known as a reactance (or control) tube and through its effect on the oscillator, the circuit is enabled to counteract any reasonable shift of oscillator frequency. Here, then, is an automatic system for keeping the oscillator on frequency, thereby removing the need for a fine-tuning control.

In order to understand and appreciate the operation of this reactance tube let us determine how a tube can simulate the action of a resistance, a capacitance, or an inductance. In Fig. 6A, a tube is connected with normal plate and grid voltages, so that plate current is flowing through the tube. When we increase the plate voltage, the plate current will increase and the two will follow each other directly within fairly wide limits of plate current flow. The same is true of a plate voltage decrease; the current will decrease in step. Since the two follow each other directly, we obtain essentially the same action as the voltage and current in a resistor and consequently the tube is functioning as a resistor, although at some points, as a nonlinear resistor.

Now, let us alter the circuit to the form shown in Fig. 6B. A source of r.f. voltage is connected to the plate of the triode and the "B+" voltage now reaches the tube through an r.f. choke. The choke prevents the r.f. plate current from traveling through the d.c. voltage source. In the same circuit, a small capacitance and resistor transfer a portion of the r.f. voltage to the grid of the tube. Let us investigate this section of the circuit more closely.

Since C_1 and R_1 are placed directly across the r.f. voltage source, an r.f. current will flow through both components, the amount of current being governed by the impedances of C_1 and R_1 . In the diagram it is specified that C_1 is small, resulting in a large impedance. The resistor, on the other hand, is low in value. Thus the circuit impedance will be largely capacitive and the current flowing through C_1 and R_1 will lead the r.f. voltage by approximately 90 degrees. The r.f. current, flowing through R_1 , will develop a voltage e_g which is in phase with the r.f. current and leading the r.f. voltage from the generator by 90 degrees. It is further true that since e_g is also the alternating grid voltage for the tube, the plate current will lead the applied r.f. voltage by the same 90 degrees. Whenever any electrical component exhibits the property of having the current through it lead the voltage applied across it by 90 degrees, it is said to act like a capacitance. Thus, by properly connecting the tube, we have made it appear to the circuit as a condenser. The tube will have this effect on any circuit in which it is placed.

To indicate how a tube can be made to

Table 1. A comparison of present-day television receivers. The chart below includes only those models which are on the market and which have been discussed in the articles thus far. As new models become available, they will be added to chart and adequate explanation of their operation given.

Manufacturer	Model No.	Picture Type		Tube Size (diam.)	Screen Size	Model Type		Tuning Method		R.F. Amp.	R.F. Osc.
		Direct	Proj.			Table	Console	Continu-ous	Selector Switch		
Andrea	T-VJ12	X		12	7 1/2 x 10	X			X ¹	6J6	6J6
	C-VJ12	X		12	7 1/2 x 10		X		X ¹	Same as Model T-VJ12	
	CO-VJ12	X		12	7 1/2 x 10		X		X ¹	Same as Model T-VJ12	
Belmont	21A21	X		7	5 1/2 x 4 1/2	X		X		6AK5	6C4
General Electric	801	X		10	6 x 8		X		X	6AU6	1/2-7F8
	802	X		10	6 x 8		X		X	Same as Model 801	
Motorola	VT71	X		7	4 1/2 x 6	X			X	1/2-7F8	1/2-7F8
	VT101	X		10	6 3/8 x 8 1/2		X		X	6AG5	1/2-6J6
Philco	48-1000	X		10	6 x 8	X			X	6AG5	6J6
	48-1050	X		10	6 x 8		X		X	Same as Model 48-1000	
	48-2500		X	5	15 x 20		X		X	6AG5	6J6
RCA	621TS	X		7	4 1/2 x 5 1/2	X			X	6J6	6J6
	630TS	X		10	6 3/8 x 8 1/2	X			X	6J6	6J6
	721TS	X		10	6 3/8 x 8 1/2	X			X	6J6	6J6
	630TCS	X		10	6 3/8 x 8 1/2		X		X	Same as Model 630TS	
	721TCS	X		10	6 3/8 x 8 1/2		X		X	Same as Model 721TS	
	730TV1	X		10	6 3/8 x 8 1/2		X		X	Same as Model 721TS	
	730TV2	X		10	6 3/8 x 8 1/2		X		X	Same as Model 721TS	
	641TV	X		10	6 3/8 x 8 1/2		X		X	6J6	6J6
	8TS30	X		10	6 3/8 x 8 1/2	X			X	Same as Model 630TS	
	648PTK		X	5	15 x 20		X		X	6J6	6J6
United States Television	T-502	X		10	6 x 8		X		X	6AG5	6AG5
	T-507		X	5	21 x 16		X		X ²	6AG5	6AG5
	T-525		X	5	25 x 19		X		X ²	Same as Model T-507	
	T-530		X	5	30 x 22 1/2		X		X ²	Same as Model T-507	
	T-621		X	5	22 1/4 x 16 1/4		X		X ²	Same as Model T-507	
Admiral	30A14	X		10	6 x 8		X		X	6J6 ⁶	6J6 ⁶
	30A15	X		10	6 x 8		X		X	Same as Model 30A14	
	30A16	X		10	6 x 8		X		X	Same as Model 30A14	
Industrial Television Inc.	1T3R	X		See Note 3					X ⁷	6J6	6J6
Du Mont	RA-101	X		See Note 4					X	6J6	6J6
	RA-102	X		12	7 1/2 x 10		X		X	6J6	6J6
	RA-103	X		12	7 1/2 x 10		Note 5		X	6J6	6J6

¹The Andrea receivers employ a tuner "turret" which is somewhat similar to the Philco tuner except that all 13 channels are wired into position. The r.f., modulator, and oscillator tubes, with their circuit components, are also contained within the copper-plated steel case. This reduces reradiation and protects the circuits from external fields.

²The r.f. tuning circuits of U.S.T. receivers closely resemble those employed in G.E. receivers. See explanation in Part 1 of this series.

³Industrial Television receivers are designed solely for commercial use. The picture tube is housed separately and controlled by a control unit located some distance away. Picture sizes can range from 6 x 8 inches for a 10 inch diameter tube to 12 1/4 x 17 1/4 inches for a 20 inch diameter tube.

⁴The set appears in six different style cabinets: Hampshire, Sherwood, Westminster, Revere, Plymouth, and Devonshire. Differences between models are in the size of the cathode-ray tube. The Hampshire and Westminster use a 20 inch tube, the other four models use a 15 inch diameter tube.


⁵This model receiver is available in three types of cabinets, two of which are table models and one is a console.

⁶Models 30A14, 30A15, and 30A16 employ an r.f. end section which is very similar to the RCA front end system.

⁷Industrial Television employs the "Inductuner" in an arrangement similar to that found in DuMont receivers.

THE OSCILLOSCOPE THAT IS

Sensitive!

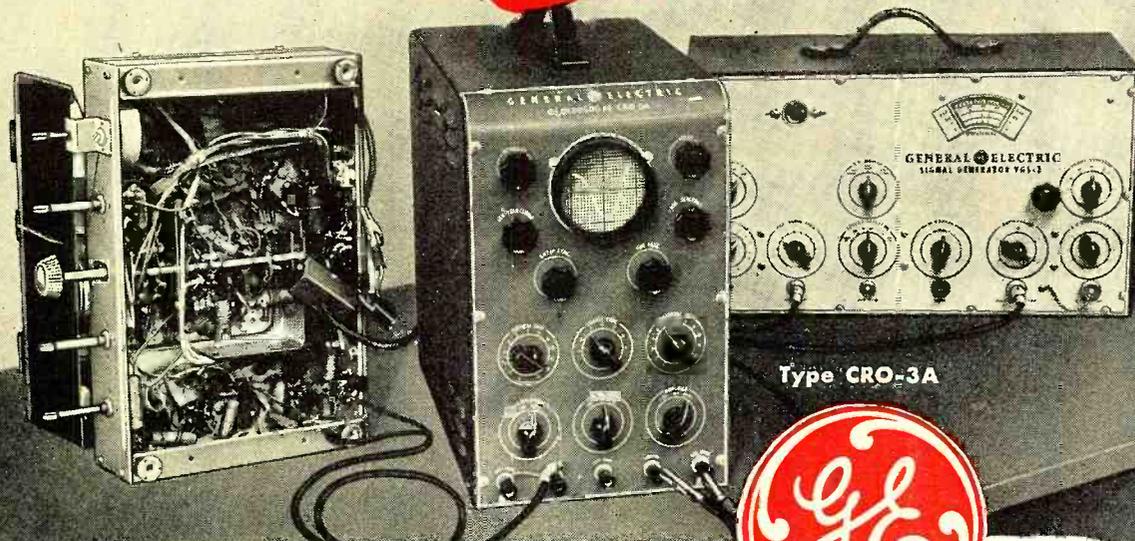

SENSITIVITY is the all-important feature in your oscilloscope if it is to do the service job you require. The CRO-3A can provide a larger image than many bigger oscilloscopes which have less amplification. It has exceptional stability, which means a trace without "jumping" or "jittering."

The CRO-3A is the oscilloscope you will want for AM-FM servicing—because it is most flexible in use—can do more jobs on the bench—gives real performance.

Take a minute to review these additional features which mean oscilloscope satisfaction:

- Exceptionally sharp trace—pinpoint focus.
- Length of trace can be expanded to several times the tube diameter, giving same advantage as larger tubes.

- Heavy case is an inherently good shield from magnetic fields, provides rugged protection of instrument.
- Normal deflection polarity: vertical is positive up and horizontal is positive to the right.
- The CRO-3A is well laid out and cleanly wired with a simple, yet effective circuit.
- Removable calibrated screen for measure of wave amplitude and symmetry of form.
- Removable light shield.
- Binding posts will take ordinary leads or banana plugs.
- The CRO-3A is well-styled—compact—requires minimum space—and is light enough to be portable.
- Due to its sensitivity it can be used with the YGS-3 Signal Generator for single stage alignment.
- Highly recommended for visual alignment of AM-FM receivers.
- And the price—extremely modest.

Check these features again—then order the CRO-3A.

For further information on this oscilloscope write: *General Electric Company, Electronics Park, Syracuse, New York.*

GENERAL ELECTRIC

164-G3

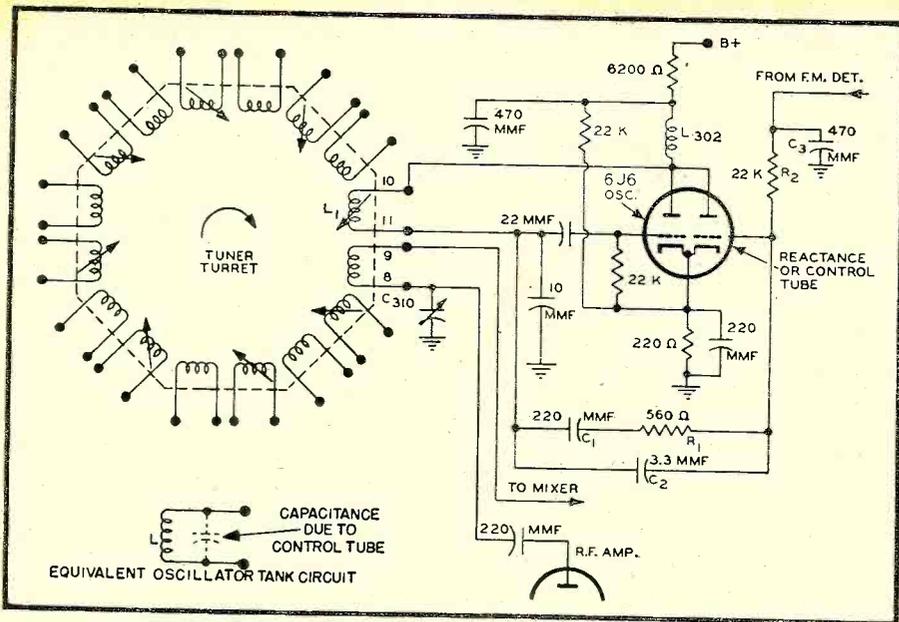


Fig. 5. Circuit diagram of the Philco oscillator and control tube stage.

function as an inductance, we can employ the circuit shown in Fig. 6C. Now, we find that R_1 and C_1 have been interchanged and now the impedance of R_1 greatly exceeds the impedance of C_1 , at the operating frequency of the r.f. voltage generator. The current now through R_1 and C_1 will be in phase with the applied r.f. voltage. However, across any capacitance, the voltage always lags 90 degrees behind the current and, therefore, the r.f. grid voltage, in Fig. 6C, will lag the current through R_1 and C_1 by 90 degrees. By the same token, it will lag the r.f. generator voltage by 90 degrees. Within the tube, the plate current, being in phase with the grid voltage, will also lag the r.f. voltage by 90 degrees. To the circuit, the tube will appear as an inductance in which the current lags 90 degrees behind the applied r.f. voltage. (If desired, a high resistance can be shunted across C_1 to provide a leakage path for any electrons accumulated at the grid. With a high value of resistance, the circuit operation remains unchanged.)


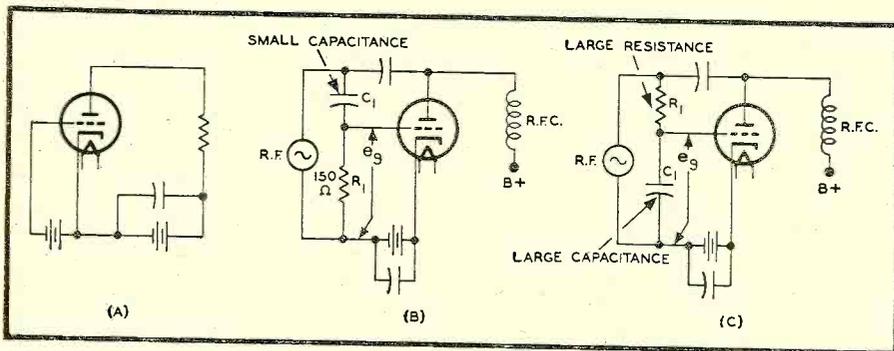


Fig. 6. Circuit diagrams show how a vacuum tube can be made to appear as a resistor (A), a condenser (B), or an inductor (C).

In each of the foregoing instances, the amount of inductance and capacitance that the tube injects into the circuit will depend upon the amount of plate current flowing through the tube. If we increase the d.c. bias for the tube in the positive direction, the plate current will increase and its reactive effect on the circuit will likewise increase. For a greater negative d.c. bias, the opposite action and effect will occur.

We are now in a position to examine the operation of the *Philco* oscillator circuit. Referring to Fig. 5, we note that the left-hand triode of the 6J6 is connected as an ultrasonic oscillator. The plate of the second triode is connected directly to the oscillator plate lead and consequently feeds its plate current into the oscillator tuned circuit. The grid of the control triode receives an r.f. voltage from the oscillator tuned circuit through the capacitive-resistance network of C_1 , R_1 , and C_2 . The same grid also re-

Fig. 7. Circuit diagram of the simulated transmission line tuner employed in RCA television receivers.

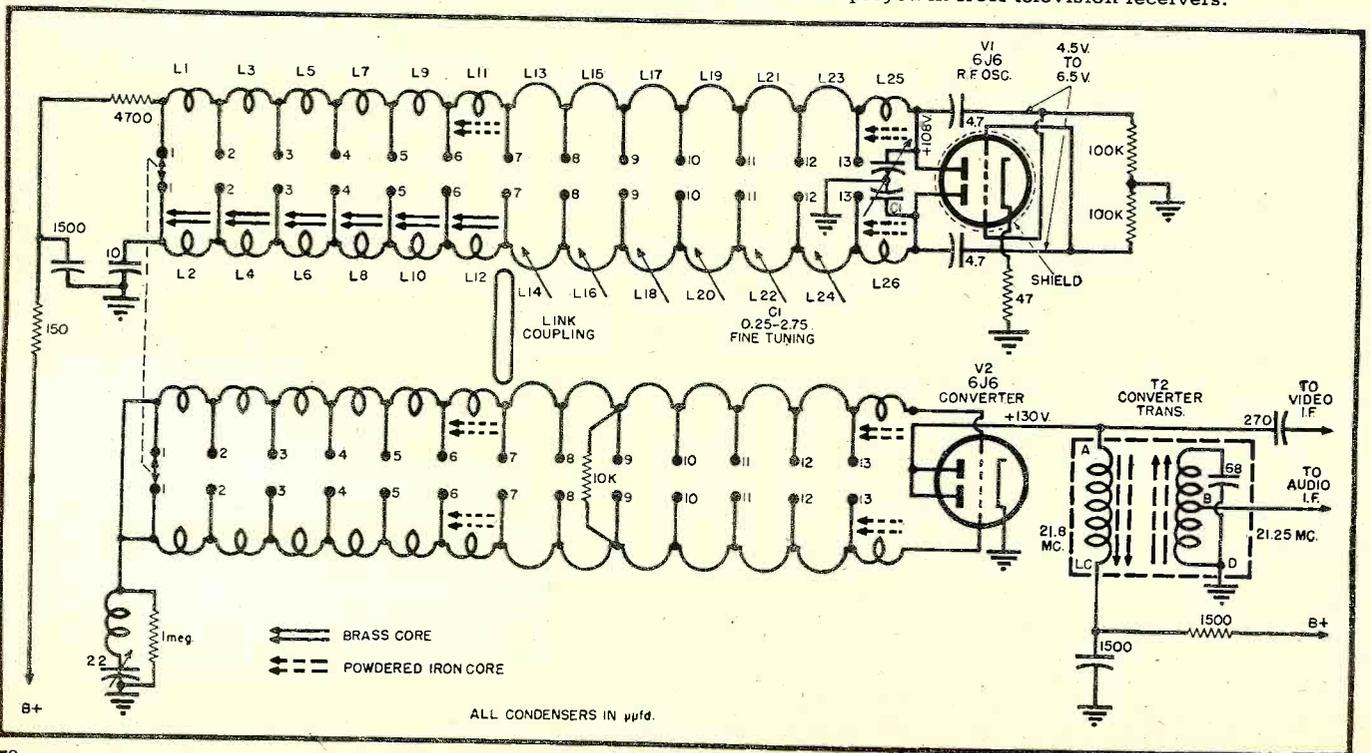

A GREAT **TRANSVISION** FIRST!

**NEW...Sensational TRANSVISION Development now offers
LARGE-IMAGE DIRECT-VIEW TELEVISION at low cost!**

BIGGEST VALUE in TELEVISION!

**Model 10BL TELEVISION KIT with FM Radio
... Features Beautiful CABINET with BUILT-
IN LENS ... Gives LARGE 120 Sq. In. Picture**


Roto-picture effect: Picture "rotates," giving the appearance of being in focus and clearly visible from every angle! Uses 10" Electromagnetic Direct-view Picture Tube.

Features new-type cabinet with built-in lens which magnifies, clarifies and heightens contrast of the picture. The lens also creates the effect of apparent rotation of the picture, so that when the observer moves, the picture still seems to be in focus and clearly visible from any angle.


ECONOMICAL KIT, EASY TO ASSEMBLE. In point of value, this Television Kit provides the opportunity of acquiring a LARGE-IMAGE direct-view television set at a VERY LOW PRICE; also very economical from a tube replacement angle. This model is available in KIT FORM, for easy assembly; no technical knowledge required. Simple step-by-step instructions are included. Saves as much as 50% over the cost of receivers with similar picture magnitude.

TECHNICAL DATA: Model 10BL uses a 10" Electromagnetic Direct-view Picture Tube; has complete F.M. Radio which comes completely factory-wired; receives all channels in any area; supplied complete with antenna and lead-in wire. The LENS is 15" x 11", giving a picture size of approx. 10" x 12" or 120 sq. in.; the highly-styled cabinet measures 26" wide x 17" high x 19" deep, available in Mahogany, Walnut, or Blonde finishes.

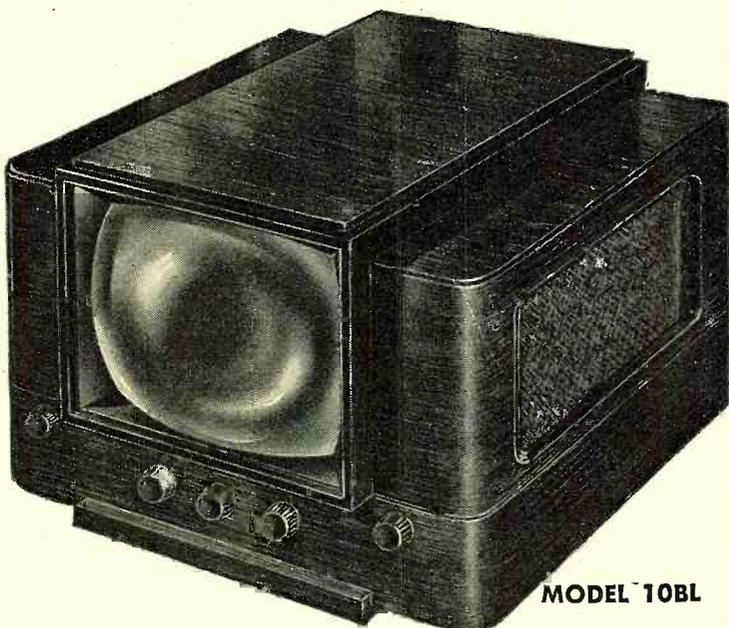PRICES: Transvision MODEL 10BL Television Kit, with FM, 10" tube, cabinet with built-in lens, antenna, 60 ft. lead-in wire.....LIST \$359.00
MODEL 12BL, same as 10BL except that it uses 12" tube, giving picture area of 130 sq. in.....LIST \$389.00



MODEL 10BL

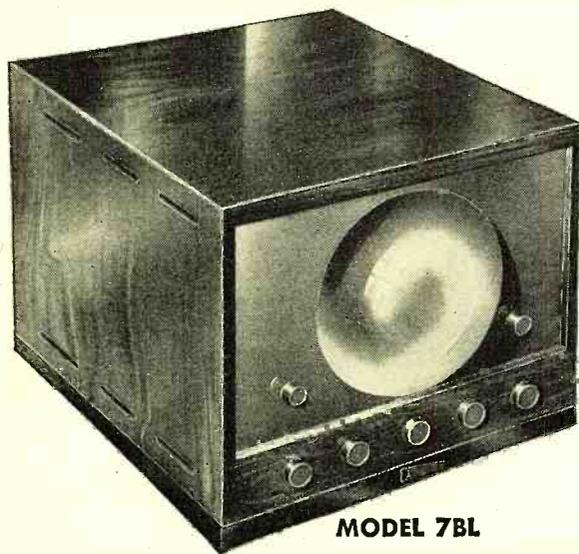

MODEL 7BL

Scoop! New Revolutionary MODEL 7BL Television Kit with Specially Designed CABINET with BUILT-IN LENS

- Uses 7" Electrostatic Picture Tube
- Gives 50 square inch picture of superior quality

FEATURES: Though it has a 7" tube, the effect is equivalent to a 10" set because the built-in lens magnifies the picture. Also picture performance is superior because the lens clarifies and heightens contrast of the image. Picture "rotates" apparently, as the observer moves, giving the effect of always facing the observer. This is effective to a very wide angle. Pre-tuned for 5 channels.

PRICE: Including cabinet with built-in lens, antenna, 60 ft. of lead-in wire. NET \$189.00

TRANSVISION "SERVICE NOTES"

The Key to Successful Television Servicing

Transvision's "Service Notes" is a compilation of confidential Television Notes and Information, the product of experience with over 20,000 television receivers, now made available to the public.

The "Service Notes" is a most valuable compilation of instructions and data on Magnetic and Electrostatic Television Receivers. Though compiled in the course of servicing Transvision Kits, the information is applicable to any type of television receiver.

"Service Notes" is complete with photographs and diagrams. The information is worth a small fortune. The cost is low. LIST \$2.95



All prices 5% higher west of Mississippi; all prices fair traded.

For further information see your distributor, or write to:
TRANSVISION, INC. Dept. RN, NEW ROCHELLE, N. Y.

See TRANSVISION at the PARTS SHOW! There will be a SPECIAL TRANSVISION EXHIBIT from May 10th through the 14th at the SHERMAN HOTEL (Chicago) in the GOVERNOR'S SUITE! Be sure to see the interesting new Transvision Developments in Television and FM.



Better Products for the Radio Industry

NEW G-C STATIC CHASER INJECTOR and POWDER



Tire static powder kits—improve auto radio reception. Eliminates wheel static interference. New powder is blown into all inner tubes—easy to use. For every car owner!

No. 5604—Injector for G-C Static Powder—List . . . \$1.50
 No. 5605—G-C Static Powder Packet for 5 tires—List . . . \$1.00
 No. 5606—Kit—One Powder Packet and Injector—List . . . \$2.50



"Visit our booth at the May Show" Have you seen the new G-C "Speedex" Wire Strippers . . . write for illustrated literature.
 RADIO DIVISION, DEPT. H

NEW G-C TUBE PULLER



Makes it easy to remove or insert miniature tubes . . . simple to operate. Inserts or extracts tubes where fingers will not reach—into hard-to-reach places. Saves time and money. Ends tube breakage. Prevents burnt fingers.
 No. 5093—Miniature Puller . . . List \$ 1.65
 No. 5093-D—Display of 12 . . . List 19.80

NEW G-C FIELD CHASS EZ



Holds almost any radio chassis in position! Has special reversible hooks for flanged type chassis or, to tilt chassis back if necessary. Made with slide adjustment—takes only 5 seconds to install. No parts to lose—will never wear out. A real convenience for the radio serviceman!
 No. 5207—Chass Ez . . . List \$3.65

G-C Products are available at leading distributors. Write for your copy of our new illustrated catalog.

GENERAL CEMENT Mfg. Co., Rockford, Ill., U. S. A.
 Manufacturers of over 3,000 products • Sales offices in principal cities

Channel Number	Freq. (mc.)	Video Carrier (mc.)	Audio Carrier (mc.)	Rec. R.F. Osc. Freq. (mc.)
1	44-50	45.25	49.75	71
2	54-60	55.25	59.75	81
3	60-66	61.25	65.75	87
4	66-72	67.25	71.75	93
5	76-82	77.25	81.75	103
6	82-88	83.25	87.75	109
7	174-180	175.25	179.75	201
8	180-186	181.25	185.75	207
9	186-192	187.25	191.75	213
10	192-198	193.25	197.75	219
11	198-204	199.25	203.75	225
12	205-210	205.25	209.75	231
13	210-216	211.25	215.75	237

Table 2. Oscillator frequencies for a TV receiver in which the video carrier i.f. is 25.75 mc. and the audio i.f. 21.25 mc!

ceives a d.c. voltage from the FM ratio detector (not shown here).

The r.f. voltage that the grid of the control triode receives from the essentially capacitive network of C_1 , C_2 , and R_1 produces a leading current through R_2 and C_3 . At the frequency of operation of this circuit, the opposition of C_3 is low in comparison to R_2 , and the capacitive current from C_1 , C_2 , and R_1 flowing through R_2 and C_3 produces a voltage across R_2 which leads the oscillator tank voltage by 90 degrees. Since this voltage is also the grid driving voltage for the control tube, we find that the plate current of this tube will also lead the oscillator tank voltage by 90 degrees. Consequently, the plate current that the control triode feeds into L_1 will be a capacitive current, causing the tube to appear as a condenser shunted across L_1 .

Now, whenever the oscillator drifts in frequency, a positive or negative resultant voltage will be developed at the ratio detector and this voltage will be fed back to the reactance tube. (How this positive or negative voltage is obtained will be discussed when we reach ratio detectors. For the moment let us just accept these results.) At the tube, a positive increase in d.c. biasing voltage will cause the oscillator tank frequency to decrease, whereas a negative rise will cause the oscillator frequency to increase. In this way, oscillator frequency drift is instantly counteracted and the set is kept on frequency.

The positive rise in d.c. grid voltage on the reactance tube will increase the capacitive current in the oscillator tuned circuit. A greater capacitive current is the same as adding a larger capacitance across L_1 . This is so because $E = IX_c$ and if I increases, with E constant, then X_c must have decreased. Since $X_c = 1/2\pi fC$, a decrease in X_c can be brought about by an increase in C . However, the frequency of a tuned circuit is equal to $f = 1/2\pi \sqrt{LC}$ and an increase in C decreases the resonant frequency of the tuned circuit. Conversely, a more negative d.c. grid voltage will reduce the plate current of the reactance tube, thereby lowering C and raising the frequency of the circuit.


This is the first attempt to use automatic frequency control in a television circuit, although a.f.c. systems were standard equipment in AM sets several years back before the practice was abandoned as unnecessary.

All oscillators in television receiver practice are operated above the incoming signal frequency by an amount equal to the i.f. As an illustration, consider a receiver in which the video carrier i.f. is 25.75 mc. and the audio i.f. is 21.25 mc. The frequencies in



Serving the **RADIO TRADE** since 1929

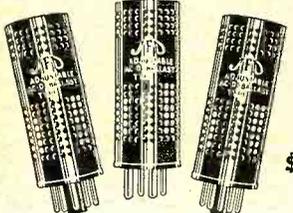Just **3** **JFD**
ADJUSTABLE BALLASTS
 Replace Over **3000** Exact Duplicate AC-DC Resistance Tubes!



List Price
\$1.50 each

New features!


- ✓ 1. Air-Cooled Perforated Shell
- ✓ 2. Larger Insulating Surface
- ✓ 3. Longer Life, Heavier Resistance Wire
- ✓ 4. Exact Adjustments made

Buy these essential JFD parts from your Nearest Parts Jobber



Write for COMPLETE JFD CATALOG today!
JFD MANUFACTURING CO. Inc.
 4111 Fort Hamilton Parkway
 Brooklyn 19, New York, U.S.A.

now ready for *Immediate Delivery...*

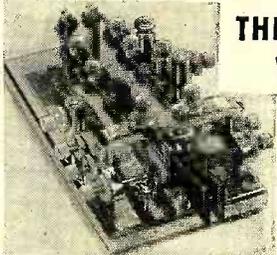

THE MELEHAN VALIANT

DELIVERED PRICE
\$27⁵⁰

25% required on all C. O. D. merchandise. Calif. purchasers please add 2 1/2% sales tax.

"Truly, the World's Finest Telegraph Key"

EXCLUSIVE FEATURES OF THE MELEHAN VALIANT

- Automatic dots plus automatic dashes.
- Adjustable from fifteen to eighty words per minute.
- Massive base 4x1/2x7 inches and cradle unit provide solid foundation.
- Purely mechanical in operation, self-contained and self-sufficient, no superfluous electrical forces being utilized.

Deliveries of this superior instrument have been interrupted because the manufacturer would not substitute inferior materials or in any way change the perfected design.

MELEHAN RADIO PRODUCTS CO.
 7061 E. Monroe St. Rt. No. 1
 Anaheim California

What Does it Take to Wake YOU Up?

● **T**he tremendous growth of radio-electronics is so rapid and spreading in so many directions that the demand for **TECHNICALLY QUALIFIED** radiomen has created a condition wherein there are many **MORE GOOD JOBS** than there are capable men to fill them.

● **B**Y THE END of 1948 the total number of broadcasting stations (AM, FM and Television) will triple those since shortly before the war. Airlines and airports are rapidly installing new radio communications and radar equipment. Major railroads have adopted radio communications, as have large trucking and taxicab companies. Manufacturing is at an all-time high as millions of home receivers, broadcasting equipment, etc., are being produced. Television receivers are in mass production.

All of this means that OPPORTUNITY IS HERE . . . Now!

Every page in this magazine could be filled with similar astounding facts concerning career opportunities available to trained radiomen. The point is, *what are you going to do about it?* Just figure out for yourself how many good jobs are waiting to be filled. You can't say, "I don't need more training." EVERY radioman needs to increase his technical knowledge if he wants to keep ahead of the competition that is bound to come . . . if he wants to go after—and GET—the better jobs that offer good money and personal security.

If you have a commonplace job. If you have the ambition to hold a position of greater responsibility with higher pay . . . then a CREI spare time program for self-improvement will help you accomplish your ambition at this opportune time. It costs you nothing to read the interesting facts. Write today for the outline of CREI courses and the free booklet, "CREI Training for Your Better Job in Radio-Electronics."

If you have had professional or amateur radio experience and want to make more money, let us prove to you we have the training you need to qualify for a better radio job. To help us intelligently answer your inquiry—PLEASE STATE BRIEFLY YOUR BACKGROUND OF EXPERIENCE, EDUCATION AND PRESENT POSITION.

VETERANS: CREI TRAINING AVAILABLE UNDER THE "G. I." BILL.

CAPITOL RADIO ENGINEERING INSTITUTE

An Accredited Technical Institute

Dept. RN-5, 16th and Park Road, N. W., Washington 10, D. C.

Branch Offices: New York (7): 170 Broadway • San Francisco (2): 760 Market St.

May, 1948



MAIL COUPON FOR FREE BOOKLET

CAPITOL RADIO ENGINEERING INSTITUTE
 16th and Park Road, N. W., Dept. RN-5 Washington 10, D. C.
 Gentlemen: Please send me your free booklet, "CREI training for your better job in RADIO-ELECTRONICS", together with full details of your Home Study training. I am attaching a brief resume of my experience, education and present position.

CHECK ONE PRACTICAL RADIO-ELECTRONICS COURSE PRACTICAL TELEVISION

NAME _____
 STREET _____
 CITY _____ ZONE _____ STATE _____

I am entitled to training under the G. I. Bill.
 Check field of greatest interest:
 RADIO-ELECTRONICS BROADCASTING AND TELEVISION
 AERONAUTICAL RADIO ENGINEERING
 RECEIVER SERVICING INDUSTRIAL ELECTRONICS



ON FLOOR STAND



ON E.V. 415 DESK MOUNT



HAND-HELD



MOBILE COMMUNICATIONS

*New FLEXIBILITY
New BEAUTY
New LOW COST*



CENTURY

CRYSTAL, DYNAMIC, CARBON MICROPHONES

FOR RECORDING, COMMUNICATIONS, PUBLIC ADDRESS

Heralds a new era of brilliantly engineered and superbly styled low-cost microphones! Complete adaptability permits widest use. Excellent reproduction and high output. Light weight . . . rugged.

Highest purity diecast case finished in lustrous gray-brown. The perfect answer for all economical installations. List prices from \$8.95 up. Get full details —send for Bulletin No. 137.

Authorized Distributors Everywhere

Crystal Mike licensed under Brush patents

NO FINER CHOICE THAN **Electro-Voice**

ELECTRO-VOICE, INC., BUCHANAN, MICH. Export: 13 E. 40th St., New York 16, U.S.A.—Cables: Arlab



this instance, for each of the thirteen channels are given in Table 2.

It is interesting to note that because the oscillator frequency is above the incoming signal, the relative positions of the video and audio carrier are reversed at the i.f. frequencies. That is, the video r.f. carrier is lower in frequency than the audio r.f. carrier whereas, after mixing, the audio i.f. carrier is below the video i.f. carrier.

Oscillator Servicing Whenever a defect in a television receiver has been traced to the r.f. section, it is best to begin the troubleshooting procedure at the oscillator. The oscillator is the most critical stage in the front end of the set and most likely to be at fault. First, change the oscillator tube and then the mixer and r.f. amplifier tubes, in that order. Next, check the tuning circuit operation according to the procedure outlined in Part I of this series. If the defect still exists, then remove the receiver chassis from the cabinet and measure the voltage between the control grid and cathode of the oscillator. By doing this we can determine whether or not the stage is functioning. Measure this voltage using a high-resistance voltmeter, otherwise the readings obtained can be very misleading. The voltage at the oscillator control grid (with respect to the cathode) may have any value between -2 and -10 volts. Consult the service manual issued by the manufacturer for the proper values. Too low a value may be due to lowered operating potentials or low cathode emission. Low cathode emission reduces the oscillator voltage generated and this, in turn, lowers the conversion transconductance. Too low emission will eventually cause the oscillator tube to stop functioning. Measure the plate and screen voltages to determine whether these values are within the correct range. The oscillator grid voltage should be measured on all bands since it is very possible that the tube will function at some frequencies and not at others. Reasons for this may be a defect in the switching system or lowered emission. Oscillations are not generated as readily when we increase the frequency and subnormal emission can be the cause.

(To be continued)

WE HEAR -- THAT

THE recently released "Photofact" folder No. 38, published by Howard W. Sams & Co., Inc., carries the first section of a presentation covering television principles for radio service technicians.

Prepared by Albert C. W. Saunders and patterned after the course being offered resident students at the Saunders Radio and Electronics School at Newton Corner, Massachusetts, this new series will be included in consecutive sets of the folders. While the series is basic in its concept, it has been assumed that the serviceman has a good grounding in radio fundamentals. Each section of the series will be profusely illustrated with diagrams, sketches, and pictorials to assist the service technician grasp the principles involved.

The first presentation is a discussion of the picture tube while later issues of the folders will cover all of the different phases of television receivers and their servicing.

NAVY SPECIAL

Famous Make

FILAMENT TRANSFORMER

Hypersily Core

Extremely light weight—8 lbs.

5x4 1/2 x 4 1/2

PRI-115V-60 cycle
Sec. #1-6.3V-22.0 amp.
#2-6.3V-2.4 amp.
#3-6.3V-2.25 amp.
#4-6.3V-0.6 amp.

The 22 amp. winding consists of 2-6.3V at 11 amp. windings in parallel. Case is easily removed. Windings can be re-arranged in series, for 12 volt at 11 amps. Also connect for 18 or 24 volts. An extremely versatile transformer at a REAL GIVEAWAY **\$2.95**
PRICE. New—Each

Hermetically Sealed Filament Transformer

T-7—PRI-115V-60 cycle
Sec. #1-6.3V-3 amp. Sec #2-2.5V-6 amp.
(Hi-Volt insulation)
Grey Navy case porc. terminals. **\$2.50**
New—Each

POWER TRANSFORMER

T-20—PRI-115V-60 cycle
Sec. 550 Volt-3.2KVA
11x8x7—open frame-porcelain terminals. New **\$20.00**

CONDENSER SPECIALS

C-1 Rect. Case 1.0 Mfd. 1000VDC dozen \$5.00
C-2 Rect. Case 6.0 Mfd. 600VDC 10 for 6.00
C-3 Rect. Case 4.0 Mfd. 600VDC dozen 5.00
C-14-cyl. can.—.03-7500VDC—Each 1.05

New Bulletin off press—write

GREENWICH SALES CO.

59 Cortland St.
New York 7, N. Y.

RADIO SERVICEMEN & HAMS No Army Surplus—All New

300 ohm twin lead.....	\$2.75 per C; \$21.00 per M
72 ohm Coaxial Cable.....	\$6.50 per C
Microphone Cable, Good.....	\$6.50 per C
Car aerials, Brass Chrome, side cowl.....	\$1.67 ea.
	10 @ \$1.47
Car aerials, Fender or top cowl.....	\$2.90 ea.; 10 @ \$2.70
4 Frong Universal Vibrator.....	\$1.25 ea.
All Mallory and Radiart Vibrators.....	40% off
10 Watt Wire Wound Resistors, all sizes.....	27c ea.
New Tubes, RCA, Philco, Sylvania—No Surplus	
Raytheon National Union.....	50% off, min. 10 tubes
All type Ballast tubes.....	59c ea.
New Condensers, Solar, Aerovox, Sprague, etc.	
16 mfd tubular 450 W.V.....	59c ea.; 10 @ 49c
10 mfd tubulars 450 W.V.....	79c ea.; 10 @ 70c
Dual 8 mfd tubular 450 W.V.....	79c ea.; 10 @ 70c
005-01-02-1700 V. Buffer Cond.....	29c ea.; 10 @ 24c
10 mfd can with nut and leads, 450 W.V.....	79c ea.
	10 @ 72c
16 mfd can with nut and leads, 450 W.V.....	89c ea.
	10 @ 79c
30 mfd can with nut and leads, 450 W.V.....	90c ea.
40 mfd can with nut and leads, 525 W.V.....	\$1.45 ea.
40-20-20-150 W.V. tubulars.....	69c ea.; 10 @ \$1.29
30-20-150 W.V-2025 W.V.....	69c ea.; 10 @ 63c
001-006 mfd-600 W.V.....	9c ea.; 10 @ 59c
01-02-mfd 600 W.V.....	10c ea.
05 mfd 600 W.V.....	11c ea.
1 mfd 600 W.V.....	13c ea.
4" PM Speaker.....	\$1.49
5" PM Speaker.....	\$1.59
6" PM Speaker.....	\$1.99
12" PM Speaker.....	\$3.75
3" Cinanograph PM.....	\$2.25
3" Utah 450 ohm.....	\$2.95
5" Quam 6 volt field Auto Spk.....	\$2.95
7 1/2" Mopar type 6 volt field Auto.....	\$4.65
Phono. motor and turntable.....	\$2.95
Pickup arm and L70 crystal.....	\$2.10
Pickup arm and Webster NS crystal.....	\$2.75
Dipole Antenna FM or Telv.....	\$4.95 ea.; 10 @ \$4.50
Folded Dipole FM or Telv.....	\$5.95 ea.; 10 @ \$5.00
Centralab and IRC volume controls with switches	
long shaft, 500 M and 1 meg.....	59c ea.; 10 @ 49c
100 assorted resistors.....	\$1.50
Aerial wire, No. 14—7 strand copper, 90 ft. rolls	
	65c ea.; 10 @ 55c
4 tube Automatic Portable Radio.....	\$15.95 ea.
6 tube 3 gang Automatic Car Radio.....	\$27.95 ea.

Write for special Price List or any parts you need.
\$2.00 min. order add postage
25% Deposit Balance C.O.D.

BRUCE ELECTRONICS CO.

82 Speedwell Ave. MORRISTOWN, N. J.

250,000 CARTONED RADIO TUBES ¹⁰⁰ ASSORTED FOR \$3500

INDIVIDUALLY CARTONED — FULL REPLACEMENT — BRANDED HYVAC — YOU PICK THE TYPES FROM LIST BELOW

39c EACH — 100 FOR \$35.00

11P7GT	12F5 GT	12S07 GT	6K6 GT	6SN7 GT	12BA6	1U4	12A6	6S5F	6BH6
32L7GT	658 GT	35L6 GT	6Q7 GT	6S07 GT	12BE6	1R5	12SF7	6BA6	6CS
12A8GT	6P5 GT	35Z5 GT	6V6 GT	25L6 GT	35W4	1S5	6F5	6BE6	11P7P
12K7 GT	3V4	50L6 GT	6X5 GT	7017 GT	35B5	3Q4	6J5	6AT6	32L7
25Z6 GT	6C5	6K7 GT	6SA7 GT	117L7 GT	50B5	354	6J7	6X4	12A8
6A7	12SA7 GT	6A8 GT	6SD7 GT	117Z3	1174	1B4	12SJ7	68J6	
47	12SK7 GT	5Y3 GT	6SK7 GT	12AT6	1L4	12K8	6AJ5	6AK5	

Popular P.M. Speakers

AT LESS THAN HALF PRICE EVERY SPEAKER GUARANTEED



4 in. P.M. 1 oz. Alnico V. mag.	\$0.99
5 in. P.M. 1 oz. Alnico V. mag.	\$0.99
5 in. P.M. 1.47 oz. Alnico V. mag.	\$1.19
5 in. P.M. 2.15 oz. Alnico V. mag.	1.49
6 in. P.M. 1.47 oz. Alnico V. mag.	1.49
6 in. P.M. 2.15 oz. Alnico V. mag.	1.98
6 in. P.M. 3.16 oz. Alnico V. mag.	2.95
6 in. P.M. 2.15 oz. Alnico V. mag.	2.95
8 in. P.M. 3.16 oz. Alnico V. Mag.	3.45
10 in. P.M. 20 oz. Alnico 3. mag.	4.45
12 in. P.M. 7 oz. Alnico V. mag.	4.95
12 in. P.M. 46 oz. Alnico 3. mag.	9.95

SAVE ON FIELD SPEAKERS

4 in. Dynamic. 450 ohm field.	\$1.89
5 in. Dynamic. 450 ohm field.	1.89
5 in. Dynamic. 1000 ohm field.	1.89
8 in. Dynamic. 1000 ohm field.	2.95
8 in. Dynamic. 1000 ohm field.	2.95
12 in. Dynamic. 1000 ohm field.	4.95
12 in. RCA 450 Reg. 10.00 net 1 1/4" Voice Coil	4.95
Scoop Price	4.95

BIG SPEAKERS—12" and 15"—SAVE UP TO 60%


12" 3 LB. MAGNET P.M. \$9.95

Nationally known make—12" 3 lb. Alnico 3 magnet P.M. speaker. 1 1/4" 8 ohm voice coil. Factory carton, fully guaranteed. Will take 25 watts. Stock No. 12P3 NET \$9.95. Two for \$17.95.

15" 1000 OHM FIELD \$13.95

Nationally known make—15" 1000 ohm speaker. 1 1/4" 16 ohm voice coil. Will take 25 watts. Factory carton, fully guaranteed. Stock No. 15UZ NET \$13.95. Two for \$26.50

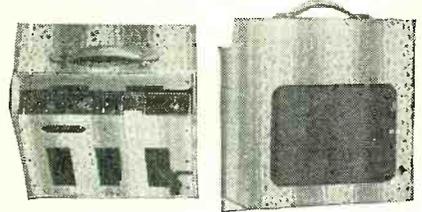\$59.50 VALUE MUSICAL AMPLIFIER WHILE THEY LAST \$19.95



8 watt musical amplifier, 4 tube AC type. Inputs for crystal or dynamic mike and phono or instrument pick-up. 2 gain controls and tone control. Has heavy duty built-in 8" speaker. Attractive leatherette covered case. Made by a large manufacturer to sell at \$59.95. Brand new, fully guaranteed. For 110 volt AC operation. Our scoop price, \$19.95. Stock No. C-LX. Compact instrument pick-up, \$6.95 extra. Deluxe instrument pick-up with volume control, \$8.95 extra. Crystal mike and desk stand \$4.95. Shipping weight, 20 lbs.


14-WATT AMP. \$29.95

THIS AMP. SHOULD SELL FOR \$50.00

Here is a high fidelity amplifier scoop we may never be able to offer again. Licensed under Western Electric patents. Brand new factory carton, 14 watt average output, 25 watt peak output. Matches 4-8-16 or 500 ohm line. Complete with tubes 6SL7, 6SN7, 2-12SL7, 2-6V6GT and 5Y3. Designed for 110 volt AC, 60 cycle operation. Frequency response 50 to 12,000 CPS. Hum level down 69 DB. Gain for two mikes and one phono pick-up. Eastern amplifier. Model E14A. Net \$29.95 Model E25A. Same as model E14A, except it has 2 6L6 output tubes, giving 30 watts output. Net \$44.95

RECREATION ROOM CONSOLE \$19.95

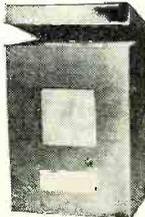Recreation room console size leatherette covered cabinet, made of heavy plywood. Covered with bright blue leatherette. Size 16"x24"x36" high. Has 7" depth under hinged lid. Room for any make of automatic changer. Cabinet is ideal for a recreation room, record player. Out for speaker 12" speaker. Stock No. RL-B12. Weight 50 lbs. Net \$19.95.



SCOOP! ON NEW C.R. TUBES

Brand New Fully Guaranteed

3 BP1	\$1.95	5 FP7	\$1.95
3 BP1	1.95	7 FP7	2.95
5 BP1	1.95	9 LD7	2.95
5 BP4—Has white screen; ideal for television.	\$2.95		

2 Band coil, condenser kit. Consists of a matched 2 gang condenser, band switch and antenna and oscillator coil; for broadcast and foreign short wave. Scoop price \$1.95. Crystal hand mike, with 12 feet of cable. A handy item to have around. Scoop price; while they last, \$3.95, each.

SPEAKERS WITH OUTPUT ATTACHED

5 in. P.M. 1.47 oz. Alnico V. mag. with 50L6 output.	Special \$1.49
5 in. P.M. 1.47 oz. Alnico V. mag. with Push-Pull output trans.	Scoop \$1.69
5 1/2 in. G.E. P.M. Square with 50L6 output trans. mounts in place of regular 6 in. speaker.	\$1.95
6 in. P.M. 1.47 Alnico V. magnet with 7000 ohm primary output trans.	Special \$2.25
Heavy Duty 8" 450 Ohm Speaker with 6V6 output.	\$2.95

POPULAR OVAL SPEAKERS

4x6 in. P.M. 1.47 oz. Alnico V. mag.	\$1.49
5x7 in. P.M. 2.15 oz. Alnico V. mag.	1.95
4x6 Dynamic. 450 ohm field	1.95

15" 7 LB. MAGNET—45 WATTS \$21.95

Nationally known make—15" speaker with 7 lb. Alnico 3 magnet. 1 1/4" Voice coil. 8 ohms. Factory carton, fully guaranteed. Super heavy-duty. This speaker will take up to 40 watts. A \$40.00 value. Stock No. 15PV. NET \$21.95. Two for \$41.95

15" 1 LB. ALNICO V P.M. \$16.95

15" Nationally known make speaker, with 1 1/4" 8 ohm voice coil and 1 lb. of the famous new Alnico V magnet. Will take 20 watts. A \$35.00 value. Stock No. 15-RY. NET \$17.95. Two for \$35.00

PORTABLE RECORD PLAYER KITS



KIT MODEL J-41. Our leader record player kit. Fine tone, low needle scratch; includes two-tone leatherette covered portable case, rim-drive photo motor, high output crystal pick-up and 5" Alnico 5 PM speaker. 70L7 ready wired and tested amplifier. No wiring to do, just mount the parts in the case. Has the tone and volume controls. Kit Model J-41 Net \$14.95
Kit model 61-X. Has a beautifully made leatherette covered portable case; similar in appearance to our model J-41. Has an even speed 78 RPM phono motor, light weight crystal pick-up and a powerful, 4 tube transformer type wired and tested, push-pull 705 phono amplifier. Has separate tone and volume controls. Full 6 1/2" heavy duty PM speaker. All you do is mount the amplifier, motor and pick-up. This is the last word in portable record players. Kit 61-X. Net \$22.95. Above kit model 61-X, with single post automatic record changer \$29.95.

POWERFUL SINGLE RECORD PLAYER KIT Z-26. Housed in an attractive leatherette covered cabinet. Latest 78 RPM rim drive motor and light weight pick-up. Ready wired and tested 70L7 type tube amplifier. Tone and volume control, 5" PM speaker (Alnico V). This kit easily slips together. Priced complete with tubes and hook-up instructions. Kit Z-26. Net \$9.95

PORTABLE P.A. \$39.95



18 watt complete portable public address system. Has inputs for a crystal or dynamic mike and phono pick-up. Has push-pull 7C5 tubes in output. Attractive leatherette covered split type case. Priced complete with two 10" PM speakers. This is a complete public address system wired ready to play. Stock No. RC-18. Net \$39.95. Priced complete with crystal mike and desk stand. We guarantee every condenser to be of fresh stock. Made by nationally known manufacturers. No junk. F. P. ELECTROLYTICS
40x20 MFD 150V. \$3.39 20 MFD 350 V. 20x20
40x20 150V 10-25V. .49 25V
40x20 150V. 200-6V. .59 20x20 300V. 25-25V. .39
TUBULAR ELECTROLYTICS
Exactly as you buy every day. Best National Brand. If these are not brands you prefer, your money back.
8 Mfd 450V Aluminum Tubular. \$0.39
20 Mfd 150V Aluminum Tubular. .39

75% OF ALL THE TUBES YOU USE 49c EACH

Guaranteed Standard Brands Cartoned and Uncartoned

12AH7	6J5	6S07	12AT6	12S07
27	6K7	68H7	12BA6	12SR7
26	9001	6S17	12BE6	50L5
78	9002	68K7	12H6	12SK7
76	9003	68L7	12J5 GT	25L6 GT
354	1625	68N7	12S7	35L6 GT
5U4G	954	68P7	12SH7	35Z5 GT
5Y3G	955	68R7	12SJ7	35W4
6AC7	68A7	6V6 GT	12SA7	50B5
6C5	68C7	6X3 GT	12SL7	
6H6	68F7	6AB7	12SC7	

59c each 1/2 Volt Octal—1N5 GT, 1H5 GT, 1A7 GT, 1A5 GT. 69c each Loctal Tubes—50A5, 35A5, 7A7, 7B7, 7E7, 7F7, 7N7, 7C5, 7Y4, 024, 35Y4, 14A7, 14B6, 14Q7, 7E5. 79c each 1/2 Volt Loctal Tubes—1LN5, 1LC6, 1LH4, 1LD5.

BIG SALE OF GENERAL ELECTRIC AUTO AERIALS

Genuine General Electric Auto Aerials. Individually factory carton. All are made by Ward. This is a real scoop on autoaerials. Order a good supply now, and save from 50 to 75 cents. on these top quality aerials. G.E. Model UZA-006, same as Ward SC-6. Side cowl 3 section 66". 36" shielded lead List \$4.95. \$2.49
G.E. Model UZA-007, same as Ward SC-8. Side cowl 4 section 100". 36" shielded lead List \$6.95 \$3.49
G.E. Model UZA-011, same as Ward TCF-3. Universal top-cowl mounting, 3 section 56". With 36" shielded lead. List \$5.35. \$2.65
G.E. Model UZA-012, same as Ward DCF-3. 3 Section 56" fits all fenders, regardless of contour. With 36" shielded lead. List \$6.25. \$3.10

DETROLA CHANGER \$12.95 2 for \$25.00



Detrola Changer, Base size 11 1/2x12 inches, \$12.95. Two for \$25.00. Aero Changer, Base size 12x13 inches, \$12.95. VM-800 Changer, Base size 13x14 inches, \$14.95. Oak, twin-post changer, base size 14x14 inches, \$17.95. General Instrument changer, base size 10 1/2x12", \$16.95. Seeburg, triple post, World's best, base size 14x14 inches, \$37.95. Made to fit leatherette bases for above changers \$1.95. Specify type of changer for base.


Compact Paper Tubular Electrolytics Condensers, Flexible Leads. Aerovox-CD or 1st Line 8x8x8 MFD 400 Volt, Long leads. \$0.49; 10 for \$4.50
40x20x10 MFD 150 Volt. .39; 10 for 3.50
50x30 MFD 150 Volt. .49; 10 for 4.50
50x30 MFD 150 V. 25 MFD 25V. .59; 10 for 5.25
HOT ITRM DEBUXXE
8x8x8 MFD Inverted Aluminum Can Condenser 450 Volt. Standard Screw Mounting. Made by Aerovox. Special. \$0.69; 10 for \$6.25



G.E. VARIABLE RELUCTANCE PICK-UP. \$4.65

Scoop—Pre-amplifier for General Electric Variable Reluctance pick-up. Easily connected to any AC or AC-DC amplifier. Wired and tested with 68C7 or (128C7) tube. Diagram for connections is furnished. Specify whether you want pre-amplifier for AC or AC-DC use. Net price. Pre-amp. with Tube and G.E. Pick-up—\$6.95. G.E. Variable reluctance pick-up cartridge with permanent needle. Net \$4.69.

COAXIAL 12" PM

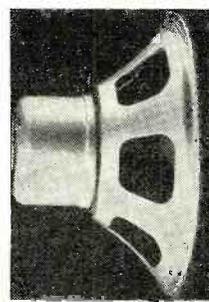

BRAND NEW IN FACTORY CARTON SALE PRICE

\$12.95 TWO \$20.00 FOR

Designed by one of America's finest speaker builders, for FM high fidelity radios; selling in the \$500.00 bracket. Has 12" Alnico V PM with 4" built-in tweeter. The hi-pass filter is built-in. Just hook on to any 8 ohm output transformer. Will take approximately 18 watts. This speaker should sell for \$35.00. Why buy a regular speaker, when we are offering a coaxial speaker at only \$12.95. Stock No. 4-12X. Weight 8 lbs. Only a few hundred available.

PERSONAL

PORTABLE RADIO KIT MAKES A \$32.50 RADIO

\$14.95

Complete with Batteries

Size: 6 1/2" x 3 1/4" x 4 1/8"

Weights Only 3 1/2 Lbs.

- Two-Tone Ivory, Red Plastic Cab.
- Loop Aerial, Built-in Lid
- 4-Tube Superhet
- AVC.
- Looks like and is a Commercial Radio Kit
- Two-Gang Cond., Lucite Dial
- Simple Assembly and Wiring Instructions



This kit is ready for immediate delivery. The same nationally known factory that manufactures tens of thousands of this radio, is line-producing this radio kit for us. Every part, from the cabinet down to the last resistor, is matched. The chassis is ready punched; all you do, is mount the parts and wire. This radio kit will assemble into a beautiful personal radio for you, just the same as it does for the factory. We furnish you a diagram, photograph of the completed chassis and full assembly instructions so that those with a minimum knowledge of radio may wire this kit. The beautiful case is made of metal with plastic hinged lid and snap on back. The lucite face of the receiver has an inlaid gold design. The circuit is the conventional two gang superhet type, with A.V.C. Receives the broadcast band, 540 to 1650 KC. Uses miniature tubes: 1B5 converter, 1B5 detector A.V.C., 1T4 amplifier and 3N4 power amplifier. Alnico V PM speaker. The loop antenna is built in the lid. Radio comes on automatically when lid opens. Operates on self-contained batteries. Priced complete with tubes and 6 7/8 volt "B" battery and flash cell (Not AC-DC). Nothing else to buy. Model X-45, Price \$14.95. Include Postage for 6 lbs.



SCOOP MODEL X-45 PERSONAL PORTABLE KIT WIRED AND TESTED WITH BATTERIES. NET \$17.95

8-TUBE RADIO KIT WITH COAXIAL SPEAKER, \$37.95

A COMBINED BROADCAST SUPERHET RADIO CHASSIS AND 15 WATT P. A. SYSTEM HEAVY DUTY 12" P.M. SPEAKER CROW 8" SLIDE RULE DIAL. 2 GANG COND. REC. BROAD. 550 TO 1700 KC AND 19 TO 49 METERS

PUSH PULL 6V6-TONE CONTROLS INPUTS FOR CRYSTAL OR DYN. MIKES AND PHONO-PICKUP. WE FURNISH EVERYTHING TO BUILD THIS DELUXE CHASSIS

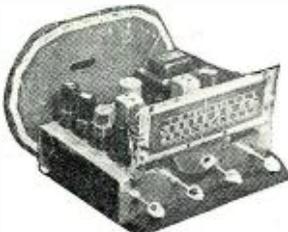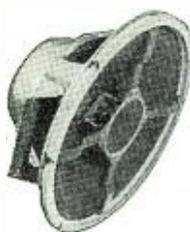- WHY NOT ORDER THE ARMCHAIR CABINET WITH THIS KIT
- HAS INPUT GAIN FOR THE G.E. VARIABLE RELUCTANCE PICKUP
- CHASSIS SIZE 9 1/2 x 11 x 8" HIGH



Here is something new in radio. A real 15 watt power amplifier with bass and treble controls. Has extra gain stage for crystal or dynamic mikes. And on the same chassis, a standard superhet radio receiver. We furnish all parts, knobs, escutcheon plate and tubes: 6SA7, 6SK7, 6SN7, 6S17, two 6V6 and 5Y3. No cabinet. Extra care in designing the power supply section assures low hum level, making this unit ideal for recording as well as P.A. use. We furnish everything as well as schematic diagram and photos of the completed chassis. Weight 35 lbs.


PRK-24 Radio-Amp. Kit with 12" P.M. speaker With tubesNet **\$29.95**

CPR-15. Exactly the same kit as the PRK-24 kit; except it is furnished with a 12" Cinaudagraph wide range speaker. (Has built-in high frequency tweeter.) This is our finest kitNet **\$37.95**

ARMCHAIR CABINET

ONLY **\$29.95**

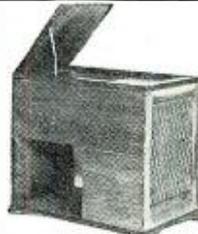Beautifully made walnut armchair cabinet. Outside dimensions 24" high, 16 1/2" deep, and 27" wide. Ample room for radio receiver 14" long, 9" high and 10" deep. Will hold a changer up to 14" square. Will accommodate speaker up to 12". Has record album storage compartment. Hinged lid covers changer compartment. Cabinet Ar-15 Net \$34.95. Detrola automatic changer \$12.95 extra.



NAVY GLIDE PATH SCOOP \$3.95

Navy model ZA Glide path receiver. Has 3-6C6 tubes; several controls, transformer and handy case; size 6x7x12 inches. Ideal for salvage, near new condition \$2.95; 2 for \$5.50



FACTORY RADIO KITS MADE FROM DETROLA, etc. MATCHED COMPONENTS

EVERY PART FITS—CHASSIS ARE PUNCHED—DIALS PROPERLY DESIGNED—COMPLETE DIAGRAMS



1949 MODEL AC-DC KIT \$12.95

This is our latest and finest AC-DC radio kit. Receives Broadcast, 540 to 1650 KC. Has full length illuminated slide rule dial. Choice of Ivory or Walnut plastic cabinet. Full high efficiency 2 gang superhet circuit, with loop antenna. Ready punched chassis, full 5" PM speaker. Every parts fits. Everything furnished, including tubes, 12SA7, 12SK7, 12SQ7, 35Z5 and 50L6. This kit will go together just like it would on the production line. Diagram, photos and instructions are furnished. Shipping weight 9 lbs. Kit model XA-49. Net \$12.95.

20-WATT UTILITY AMP. KIT, \$17.95


Build this 20 watt utility 110 volt AC, 20 Watt power amplifier. Ready punched chassis, size 12 x 6 x 2 1/2 inches. Has two input circuits, one mike and one phono. Mike stage has 135 DB gain, for crystal or dynamic mike. Has bass and treble controls. Designed for use with PM speakers; has 8-16 ohm output transformer. All parts and easy-to-follow diagram furnished, including tubes: 2-6SN7, 6J5, 2-6L6GA, 5Z3. Kit Model 20-LX. Net \$17.95



12 WATT AMPLIFIER KIT, \$10.95

Push Pull 6V6's Gain for Mike

KIT MODEL AC-12. 12 watt amplifier kit. Ideal for high quality record player as well as public address or recording amplifier. Matched component parts, ready punched chassis pan. One control fades from phono to microphone. Gain enough for crystal or dynamic microphone, 100 mill power transformer, for 110 volt AC 60 cycle operation. Priced complete with tubes: 2-6V6, 6SN7, 6S17 and rectifier. Diagrams and photos furnished. Kit AC-12. Net \$10.95. 12" Alnico 5 PM speaker \$6.95 extra; crystal microphone and desk stand \$4.95 extra.

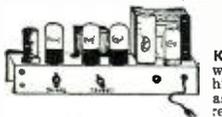

PORTABLE RADIO DISC-RECORDER KIT, \$54.95

\$90.00 value for only \$54.95. We furnish every part to build a powerful radio and dual speed recorder. The attractive leatherette case houses the sensitive superhet broadcast radio and General Industries R90L 3 3/4 and 78 RPM dual speed recorder; play back mechanism. The 6 tube receiver and amplifier is all on one chassis: 12SA7, 12SQ7, 12SK7, 12SL7, mike gain; two 35L6 push-pull output; plus disc rectifier. Has plenty of gain for crystal or dynamic mike. Has 6" heavy duty PM speaker and tone control. Kit G-31, everything complete, with tubes and diagram. \$54.95. Crystal mike and desk stand \$4.95 extra. This is without a doubt one of the best values in kits we have ever offered. Wt. 40 lbs.



AMERICAN AND FOREIGN KIT \$14.95

550 to 1600 KC and 6 to 18 MC

This radio kit is housed in an attractive grey opalescent finished metal cabinet. Incorporates a standard 2 gang superhet circuit. Receives Broadcast (550 to 1600 KC) and foreign short wave (6 to 18 Megacycles). This kit is complete, nothing else to buy; just as all our kits. Ready-punched chassis. It will go together just as it would down a production line. Has full 5" PM speaker. Complete with tubes: 12SA7, 12SK7, 12SQ7, 35Z5, 50L6. Diagram, photos and instructions are furnished. Shipping weight 10 lbs. Kit model DT-5. Net \$14.95



\$50.00 VALUE DAYCO TUBETESTER \$32.50

Latest up to date Darco portable tester, with illuminated roll chart; with wide angle magnifying lens. Never becomes obsolete. Sockets are provided for all bases: 4, 5, 6, 7, 8, 9, 10, octal, Joctal, scorb, tantam, miniature, etc. Has both quality and short tests. Best tube checker value today. Portable Model 2194 Net \$32.50. Model 2193 is the same as the 2194 except it is a counter model in black wrinkle finish, with sloping front panel. Counter Model 2193 Net \$29.50. These tube checkers should sell for at least \$10.00 more.



AMERICAN XTAL CARTRIDGE \$1.49

American crystal replacement phono cartridge. Standard mounting; most one size used. Long shielded leads. Scoop price \$1.49

SCOOP PRICES ON VIBRATORS

Standard 6 volt vibrators for every day replacement use—All guaranteed. Genuine Mallory sync vibrator unit. Ideal to put in old can for Buick, Delco, etc.	
Scoop price	\$0.99
4 prong war surplus; new in bent cans	0.79
4 prong UTAH NY-42 for Philco	1.29
4 prong SMALL for Ford	1.49
4 prong OFF-Set for Delco	1.49
5 prong standard sync	1.49
6 prong standard sync	1.49
6 prong reversible sync	1.99
7 prong reversible sync	1.99
5 prong OFF-Set sync	1.99
Sync. unit; Vibrator unit only; with cond.	1.99
7 prong 2 volt; G. E. sync.	1.99

DETROLA CHASSIS \$16.95

Detrola Factory wired and tested chassis. Size 7 1/2" x 10 1/2" x 4 1/2" tall and 13" long. Receives 550 to 1600 KC. RF stage and 3 gang tuning condenser. Loop ant. Etched glass slide rule dial. With tubes 2 6SK7, 6SA7, 6SQ7, 6K6, 5Y3. 8 in. Heavy duty speaker. This chassis is ideal for the above arm chair cabinet. Input for phono pick up. Tone control and phono switch. Brand new. Should sell for \$40.00 Stock No. DTR-6 Net \$16.95. Weight 20 lbs.



WALNUT CABINET KIT \$11.95

Attractive 13" walnut cabinet AC-DC radio kit, with illuminated slide rule dial. Has made-to-fit metal front grille. Incorporates a standard 2 gang superhet circuit. Loop antenna ready-punched chassis. This is another one of our line production radio kits. Every part is furnished. Includes tubes: 12SA7, 12SK7, 12SQ7, 35Z5 and 50L6. Diagram, photos and instructions are included. Has full 5" Alnico 5 PM speaker. Receives broadcast 550 to 1650 KC. Shipping weight 9 lbs. Model ES-6. Net \$11.95




WIRE RECORDER \$69.95

Portable Wire Recorder Model GN-11 Has ready wired and tested 5 tube AC type amplifier with push-pull 6V6 tubes. Built-in eraser circuit. Input for crystal mike or phono pickup. Diagrams show how you can record from any radio receiver. 3 position switch enables you to quickly change from record to playback or conventional P. A. system. This unit delivers 12 watts of good clean audio. Here is what you get: Webster 79 recording mechanism, with 15 minute spool of wire, attractive leatherette covered case, 6" heavy duty PM speaker and wired and tested 12 watt AC wire recording amplifier. All you do is mount the amp, recording mechanism and speaker. Simple instructions furnished. Portable Recorder Model GN-11 Net \$69.95. Crstl mike \$4.95 extra.




DELUXE WIRE RECORDER \$79.95

This wire recorder incorporates all necessary circuits for recording and playback. Has built-in eraser circuit. The amplifier is of the AC transformer type, with push-pull 6V6 output tubes. Has tone control and eraser control. Input stage for wire recording from either crystal mike, radio receiver or phono pickup. Amplifier is wired, tested and ready to operate. This unit is classified as a kit, only because you have to mount the Webster wire recording mechanism, amplifier and speaker. Everything is furnished, including a 15 minute spool of recording wire. Kit includes wired and tested 12 watt amplifier, expressly made for wire recording and public address use. Leatherette split type case and 10" PM speaker, furnished with regular \$52.92 Webster wire recording mechanism. Kit model GN-12. Net \$79.95. Crstl mike and desk stand \$4.95 extra.

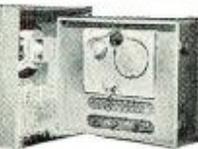

NEW BC-1206 \$5.95

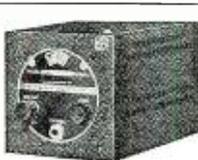Designed to receive A-N beam signals. 24-28 vdc. Tube complement: 14H7, 14A7, RF 14H7, 14T7, 14A7, 14H7, 1F amplifier; 14R7, detector and 1st audio; 28D7, output. 195 to 420 KC 4" high x 4" wide x 6 3/4" long. Weight 4 lbs.






**BRAND NEW
BC-645**
9.95 TWO FOR \$19.00

A small complete Transmitter and superhet receiver, for the 450 megacycle band. Diagrams for building AC power supply and conversion furnished. Ideal for M.W. CW or phone. The tubes (4-7F7, 4-7H7, 2-7E6, 2-6J6, 2-955 and VE-316A) are worth more than our sale price. BC-645 I.F.F. unit \$9.95 each. Two for \$19.00 Extra. WE-316A tube 99c. 12 volt DC dynamotor (furnished all power) \$2.95. BC-645 shipping weight 25 lbs.

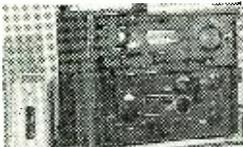**BC-654
TRANS-REC**
\$12.95
TWO FOR \$25.00



BC-654 Portable Transmitter and Receiver. 7 tube superhet receiver and 6 tube transmitter. Covers from 800 to 500 KC. Furnished with all 12 tubes (low drain battery type). Units have been used but are in good condition. BC-654 weight 50 lbs. One of our best surplus values. \$12.95 each, two for \$25.00. Vibrator pack for 6 or 12 volt operation \$4.95, extra.

**PE 206A INVERTER—
BRAND NEW \$4.95**

P.E.-206A Inverter. Brand new factory cartoned. For 25 to 28.5 volts input. Output of 80 volts (plus or minus 3 volts) at 800 cycles, at 500 volt amperes. This is a perfect inverter. Has carbon pile regulator, built-in voltage control. A 20 stack selenium rectifier. Shipping weight 45 lbs.

PE-206A Net \$4.95

PE 101C Dynamotor Brand New \$2.95
Dynamotor PE-101C. Input voltage 13 or 26 volts DC, at 12.6 or 6.3 amps. Output voltage 400 volts DC at 135 Mils and 800 volts at 20 Mils, 9 volts AC at 1.2 amps. Brand new factory cartoned. Shipping weight 13 lbs. PE-101C Net \$2.95

Pulse Forming Networks

Used in small radar modulators, available in three sizes, 67 ohms impedance. 7.5 Kilowatt rating.
H-603, one micro second, 200 pulses per second \$1.95
H-601, three micro seconds, 200 pulses per second \$2.95
H-602, 16 micro seconds, 60 pulses per second 3.95
All three of above, for only 5.95

Crystal Calibrator \$2.95
Crystal Calibrator, gives 50 KC beat note through an Xtal synced, multivibrator. Furnished complete, less 200 KC Crystal. With tubes 12SA7 and 2-12SL7. A handy item to have. Scoop price... \$2.95

PORTA-POWER
Electro Porta Power. Converts any 4, 5, or 6 tube 1 1/2 volt, 90 volt portable or farm radio to 110 volt AC operation. Multiple socket arrangement makes easy, quick connection possible. Every shop should have one of these. Regular \$9.95 value. Scoop price \$5.95

SELSYN INDICATORS \$2.95
Selsyn Indicators. 5" diameter. Will operate on from 15 to 24 volts 60 cycle AC. Model I-82A can be used as either selsyn transmitter or selsyn receiver. Scoop Price, \$2.95. 2 for \$5.49

VIBRATOR SCOOP \$1.99
Heavy Duty Vibrator—Made for 6-110 volt amplifiers. Freq. 60 CPS. Scoop price..... \$1.99
135 ma 6-110 volt conventional power transformer, with all windings; will run phono motor. \$5.95 (Use with above vibrator)

SMALL PHONO MOTOR. This 110 volt AC, 60 cycle phono motor is used on 50% of all automatic changers. Order one just to have around for replacement. Scoop price. \$1.49; Two for \$2.79

\$4.95 EACH
3 FOR \$14.00

Super value. Folded Di-pole antenna, for FM and Television. Complete with 60 feet of twin 300 ohm line and 4 low-loss stand-off insulators. This folded di-pole covers frequencies 42 through 108 megacycles. Trombone action makes exact tuning to any one weak station. Furnished with adjustable mounting bracket. Has 5 foot mast. Made for Stromberg-Carlson. Stock No. Mt-300—Net \$4.95; lots of three, \$4.50 each. Weight 4 lbs. Individually packed.



**ELECTRONIC
MEGAPHONE
SCOOP PRICE**
\$39.95

Only 50 of these to sell. Amplifier straps on shoulder, then just hold megaphone and speak into mike, mounted on rear of projector. These units are brand new. Amplifier is dry battery operated. Just pull trigger switch, amplifier comes on immediately. Net \$39.95

**MARKER BEACON
REC. \$2.95**

BC 1023 A Marker beacon receiver. Designed for reception of modulated signals of the 75 MC band. Variable tuning permits coverage of 62 to 80 MC. Brand new factory cartoned. With tubes 6SQ7, 6U6, 6SC7 and 12SH7. Operates directly from 12 or 14 volts DC. Priced for quick sale only \$2.95.

SCOOP! 110 M.C. REC. \$6.95

BC-733 D Localizer Receiver
Freq. 108-110 Mc; Tube complement; 10 tubes—1-12SQ7, 2-12SR7, 1-12A6, 1-AH7GT, 2-12SG7, 3-117A. Now only \$6.95
BRAND NEW
A RED HOT VALUE.

ARC-4 \$14.95
IDEAL FOR 2 METERS
Priced Complete With 20 Tubes—and 12-28 Volt Dynamotor

FOUR CHANNELS CRYSTAL CONTROLLED. ARC-4 for VHF frequencies 140 to 144 megacycles. There are 7 tubes in the transmitter: 832, two 1614, two 6V6 and two 6L6. The receiver section has 13 tubes: two 6AC7, four 6X7, three 12SR7, two 12SQ7 and two 12A6. The unit is actually two receivers and one transmitter in one piece. One receiver is for stand-by use. Has built on dynamotor for 12 or 24 volt DC operation. Priced complete with tubes and four crystals and dynamotor. Hams convert this for two meter operation. It's a scoop at this price. Used.

RDF RECEIVER \$19.95

MM-26-C Compass Receiver. Brand new factory cartoned. This unit covers from 150 to 1500 KC inclusive; in three bands. Complete with eleven tubes of the 6 volt type; 6SA7, 6SK7, 6F6, etc. Has 25 volt built-in dynamotor. There is no dial built on unit and no remote cables are provided. MM-26-C receiver \$19.95 Remote control \$3.95 extra. Manually operated loop..... \$6.95 extra

**SCR-518
ALTIMETER \$2950**

Brand New

Famous SCR 518 A Altimeter. Brand new factory cartoned. Worth over \$900.00. Made by RCA. Complete as pictured. Has 29 tubes. Works in the 500 MC region. This is the complete unit. Transmitter, receiver, power supply and 3" scope indicator. Reads altitude up to 30,000 ft. Operates on 28 volts. D.C. Complete with tubes. 6SK7, 2 8012, 2 6SJ7, 6C8, 6SN7, 6F8, 23D4, 6V6, 10 6AC7, 3 2X5, 954, 955, 956, 615 and 3 in. CR tube 1808P. A RED HOT scoop at only \$29.95 complete.

ARMY \$695

Field Telephones


EE-8 Army field telephone. These units are used, but in good condition. Priced complete with telephone hand set, hand powered magnets and canvas carrying bag; as pictured. Net \$6.95, each.

15 TUBE SCOOP \$995

BRAND NEW
AM 61A Indicator Amplifier. Brand new factory cartoned. Has 28 volt DC Blower motor and fan. 2 2mfd 1000 volt cond. 2 2X .5 mfd. 1000 volt cond. and many other parts. Complete with 15 tubes, 7 6SN7, 3 VR 105A, 5Y3, 3 6SL7, 8016. As a salvage item this is a RED HOT Buy. The tubes are worth more than our price. Weight 30 lbs. Net \$9.95

**COMMAND REC. with
Diagrams**

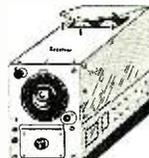Order your Aircraft command receivers from McGee. We furnish you a schematic of the BC-454 (all are the same except for frequency). Also, a diagram showing how to convert receivers for 110 volt operation.



Used BC-453, 200 to 500 KC, with tubes..... \$4.95
Brand new BC-453, 200 to 500 KC, with tubes... 7.95
Used BC-451, 3 to 6 MC, with tubes..... 3.95
Brand new BC-454, 3 to 6 MC, with tubes..... 5.95
Used BC-455, 6 to 9 MC, with tubes..... 3.95
Triple remote control head for 3 receivers..... 1.95
Triple mounting rack for 3 receivers..... .99
28 volt receiver dynamotor 99

**NEW
COMMAND
XMITTERS \$5.95**

With each command transmitter, we furnish a schematic of the BC-458 (All command Transmitters are essentially the same; except for frequency.)



Used BC-457, 4 to 5.3 MC, with tubes..... \$4.95
Brand new BC-457, 4 to 5.3 MC, with tubes..... 6.95
Used BC-458, 5 to 7 MC, with tubes..... 4.95
Brand new BC-458, 5 to 7 MC, with tubes..... 6.95
Twin rack, for 2 transmitters..... .99
Antenna Current Meter, used \$1.95. New..... 2.95
New Modulator, BC-456..... 2.95
Used Modulator dynamotor, 28v..... 1.95
Extra VT-136 (Tras. output Tubes). Each..... .49

VEEDER ROOT METER

Counts number of feet of trailing wire antennae; number turns when winding on coil; applicable for many uses; beautiful bakelite case, jewelled dial, pilot light enclosed, 3 position switch, counts up to 1000. Each95c

3" SELSYN INDICATOR
Works on 16 to 25v. 60 cycle
\$2.45 EACH
Two for \$4.45

TURBO AMPLIFIER \$1.95

Aircraft Turbo Amplifier, complete with 4 tubes. 7F7, 7Y4 and 2-7C5. Terrific salvage scoop. Ideal to wreck for parts. Priced new with tubes..... \$1.95
Monthly Special. Turbo amplifier less tubes. Weight 4 lbs. Only..... .69

AM-26 \$1.49

AM 26 interphone amplifier. This unit is nice for parts salvage and the aluminum case is usable for receiver building etc. Size 9 1/2 x 4 1/2 x 5 1/2". Has two transformers, four tube sockets, three filter condensers, three position panel switch, toggle switch, and many small parts. All are in perfect condition. \$1.49; 2 for \$2.49

MODULATOR SALVAGE \$2.95

Another red hot value in salvage. All kinds of good usable parts in this unit. Con. Res. Relays, Modulation trans. and tubes VR150, 1255 and 1625. Brand new and in factory carton. Originally designed to modulate the BC-457 W.E. Transmitter. You can find many uses for this BC-456 Modulator scoop. 28V Dynamotor..... \$1.95

**ANT CURRENT
METERS \$1.95**

Antenna Current Meter as used with the popular command transmitters. Has 0 to 10 2 inch. Thermo coupled meter. Built in vacuum condenser. A scoop value. Used \$1.95; two for..... \$3.69
New \$2.95; two for..... \$5.50

PACKARD BELL PRE-AMP \$1.99

Housed in a handy aluminum case 5x4x5, priced complete with tubes 6SL7, 28D7, has many usable parts. Relay and control PL68 plug and patch cord.

McGEE RADIO COMPANY

May, 1948

PRICES
F O B
KANSAS CITY

SEND 25% DEPOSIT—BALANCE C.O.D.
1225 McGEE ST., KANSAS CITY, MISSOURI

85

What's New in Radio

"PORTABLE SERVICE SHOP"

Radio City Products Company, Inc. has developed and is marketing a new test instrument, a "portable service shop," which is a combination of six essential servicing units.

Housed in a single carrying case are a tube tester, multimeter, FM signal



generator, AM signal generator, audio oscillator, and condenser tester. Designated the Model 8073 Servishop, the unit is available in a natural oak carrying case which measures 5"x13"x9 1/2" and weighs 15 1/2 pounds. The unit comes complete with all tubes, test leads, and operating instructions. It will operate on 50 or 60 cycle lines from 105 to 135 volts.

The tube tester will check all the new miniature tubes and carries 800 listings in the tube charts. The meter is fused as an added protection. The condenser tester reads "good" or "bad" for leakage of electrolytics, paper, or mica condensers. Both FM and AM signal generators are set for four needed calibration frequencies. The audio oscillator has a 400 cycle output.

For further details readers are requested to write to the company direct. Address inquiries to Radio City Products Company, Inc., 152 West 25th Street, New York 1, New York.

TV AND FM COIL KITS

Of interest to the experimenter and radio amateur are the complete coil kits now being placed on the market by Special Products Company of Silver Spring, Maryland.

The new "Specocoils" are designed for



the builder who wishes to construct his own FM tuner or television receiver. Two kits are available. One includes a set of six coils for building a high

86

fidelity FM tuner. A circuit diagram showing a typical FM tuner is enclosed with each coil. The second kit is a set of eleven television coils complete with circuit diagrams for building the TV sound and video sections.

The coils are slug-tuned with the tuning adjustment at the top, thus making it unnecessary to get on the under side of the chassis.

The kits are now being merchandised by parts distributors throughout the country. Additional data may be secured from Special Products Company, Silver Spring, Maryland.

NEW VARIAC

General Radio Company of Cambridge, Massachusetts has recently introduced the Type V-20 Variac for the manual control of a.c. voltage.

Latest item in the company's line of Variacs, the new unit is capable of handling 20 amperes in the 115 volt model. The 115 volt model, designated the Type V-20M is rated at 3.45 kva., while the 230 volt model, the Type V-20HM, is rated at 2.3 kva.

Output voltage is continuously ad-



justable from zero to 17 per-cent above input line voltage. Both models are supplied with case and terminal box cover. The terminal box is designed for use with BX or conduit. The overall dimensions are 7 7/8" x 9 5/8" x 5 1/2" and the unit weighs 22 3/4 pounds.

For additional details on this unit write General Radio Company, 275 Massachusetts Avenue, Cambridge 39, Massachusetts.

NOISE FILTER

A new noise filter, the Type X6, is now being distributed by P.R. Mallory & Co., Inc. of Indianapolis.

Designed to eliminate radio interference caused by various electrical appliances, this filter may be installed between the plug of the offending appliance and the wall outlet.

A colorful display card for merchandising these filters has been designed for radio servicemen and appli-

ance dealers. Details are available from the company's distributors or from the Wholesale Division, P. R. Mallory & Co., Inc., Indianapolis, Indiana.

NEW WIRE RECORDER

A new wire recorder, especially designed for easy connection to existing amplifier circuits, has been announced by Webster-Chicago Corporation.



The Model 78 utilizes push-button controls for greater flexibility of operation in any of four "record" and "listen" positions. The unit consists of a wire transporting mechanism, a pre-amplifier, interstage amplifier, oscillator, and built-in power supply. An accurately calibrated recording level meter assures correct recording volume. The recorder is housed in a metal case measuring 11 1/2"x11"x5 1/2".

Webster-Chicago Corporation, 5610 W. Bloomingdale Avenue, Chicago 39, Illinois will supply additional details on request.

MONITOR AND SENDING KEY


Of particular interest to hams is the new "Mon-Key" electronic monitor and sending key being manufactured by Electric Eye Equipment Company.

This electro-timed automatic key makes dashes proportional to dots and keeps spaces uniform for the sending speed. Sending speed can be regulated by a dial setting from approximately 8 w.p.m. to 40 w.p.m. The unit is also a monitor, producing a clear tone that can be regulated as to volume or tone or the monitor tone can be cut out entirely by turning a knob.

The key controls a multivibrator of extremely simple design. No open condenser is switched in and out of the circuit. Resistors of 5 per-cent tolerance are used in the timing network. These, in conjunction with two equal condensers, are the only components in the "critical" category. The multivibrator drives the grid of the keying relay tube. This tube actuates a relay having two 2-amp. contacts, one set of contacts terminating on binding posts under the key. The other contacts key the grid of an electronic audio oscillator. This oscillator drives a 2" PM

RADIO NEWS

New SUPREME 1948 and F.M. Manuals

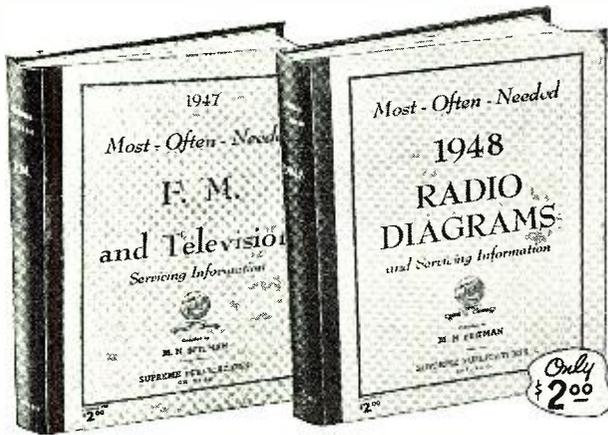

BIGGEST BARGAIN IN RADIO DIAGRAM MANUALS

Make these two new mammoth volumes your money-saving source for data on all recently released receivers. Learn about modern circuit developments, be ready to repair any new radio no matter how complex. You pay only \$2.00 for each of these large manuals. With these two volumes on your workbench there is nothing else to buy, nothing else to pay — a whole year of service data and radio diagrams yours for a couple of dollars total. Again **Supreme Publications** beats all competition and gives radio servicemen greatest bargains in service information. Read about other volumes for previous years described below at left. **No-risk** examination granted to servicemen.

FIND ALL RADIO FAULTS DOUBLE-QUICK

You can speed-up and simplify radio repairs with SUPREME PUBLICATIONS Manuals. Service radios faster, better, easier, save time and money, use these **most-often-needed** diagram manuals to get ahead, earn more per hour. For the remarkable bargain price (only \$2 for most volumes) you are assured of having in your shop and on the job, needed diagrams and other essential repair data on 4 out of 5 sets you will ever service. Every popular radio of all makes from old-timers to new 1948 sets, including F.M. and Television, is covered. Clearly printed circuits, parts lists, alignment data, and helpful service hints are the facts you need to improve your servicing ability. Save hours each day, every day, begin to earn more by making repairs in minutes instead of hours. Let these manuals furnish you with diagrams for 80% of all sets. There is no need to spend large sums for bulky, space-wasting manuals, or to buy additional drawings every few weeks; be wise, use SUPREME Manuals to get the most in diagrams and service data for the smallest cost.


F.M. and Television

Use this new giant manual of factory instructions for troubleshooting, repairing, and alignment of any 1947-1948 **F.M. and Television** set. Covers every popular make, including F.M. tuners, AM-FM combinations, and all types of television receivers. Detailed circuit diagrams, theory of operation, test hints, alignment data, including both **meter** and oscilloscope methods. This is the material you need to fix any modern F.M. or Television set. Don't turn this profitable work away for lack of knowledge and information. Use this newest **Supreme** manual to save time and money on your very next F.M. job. Data presented on 192 large-size pages, 8½ x 11 in. Sturdy, manual-style binding. Special price, postpaid. **\$2.00**

New 1948 Manual

Be prepared to repair quickly all new 1948 receivers. In this big single volume you have clearly-printed, large schematics, needed alignment data, replacement parts lists, voltage values and information on stage gain, location of trimmers and dial stringing, for almost all recently released sets. A worthy companion to the 7 previous volumes used by over 120,000 shrewd radio servicemen. New manual covers models of 42 different manufacturers. Giant size: 8½ x 11 inches, 192 pages + index. Manual-style binding. **\$2.00** Bargain price, only

YOU CAN SERVICE ALL OLDER RADIOS WITH

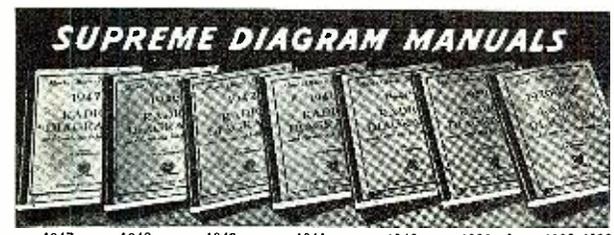

MOST-OFTEN-NEEDED RADIO DIAGRAMS
Each manual has between 192 and 208 pages of diagrams and service hints; large size, 8½ x 11". Price, each **\$2.00**
DIAGRAMS 240 Pages Price \$2.50

SATISFACTION GUARANTEED

Select **Supreme** Diagram Manuals and Record Changer Books you want to examine. These manuals pay for themselves with time saved on a few jobs—after that you use them **FREE**. See listing in left-hand column. Send trial coupon. Use these manuals in your own home or shop for 10 days at our risk. Decide for yourself that **Supreme Publications** are the greatest values in service data. You must be completely satisfied, or return manuals and receive your money back. Write today—24-hour shipping service.

Models Made by:
R.C.A., Zenith, Philco, Sears, Fada, Emerson, Belmont, Detrola, Crosley, United Motors, G.E., Westinghouse, Arvin, Majestic, Midwest, Meck, Olympic, Pilot, Stewart - Warner, Admiral, Delco, Stromberg-Carlson, Western Auto, Sparton, Motorola, Wards, Gamble, and many others.



Compiled by M. N. Beitman, radio engineer, teacher, author, and serviceman.

Record Changer Manuals

Post-War Models

Service expertly all modern (1945-1948) record changers. Just follow simplified factory instructions to make needed adjustments and repairs. Hundreds of photographs and exploded views; thousands of test hints; service instructions for all popular makes. Large size: 8½ x 11". 144 fact-filled pages. Available at your jobber or sent postpaid, special price, only. **\$1.50**

Pre-War Models

Just what you need to repair quickly thousands of pre-war (before 1942) automatic record changers, manual units, pickups, wireless oscillators, recorders, and combinations. Hundreds of mechanical and electrical diagrams. Instructions for adjustments and repairs. Most popular units of all makes. 128 large pages; size: 8½ x 11 inches. Price postpaid, only **\$1.50**

See Your Radio Jobber or Send Coupon →

Supreme Publications
PUBLISHERS OF RADIO BOOKS, MANUALS, AND DIAGRAMS
9 South Kedzie Ave. Chicago 12, Illinois

NO RISK TRIAL ORDER COUPON


SUPREME PUBLICATIONS, 9 S. Kedzie Ave., Chicago 12, ILL.

Ship the following manuals on trial under your guarantee of satisfaction or money-back.

<input type="checkbox"/> New F.M. and Television Manual \$2.00	<input type="checkbox"/> 1948	} \$2 EACH
<input type="checkbox"/> Post-War Record Changers..... 1.50	<input type="checkbox"/> 1947	
<input type="checkbox"/> Pre-War Record Players & Recorders 1.50	<input type="checkbox"/> 1946	
<input type="checkbox"/> I am enclosing \$....., send postpaid.	<input type="checkbox"/> 1942	
<input type="checkbox"/> Send C.O.D. I am enclosing \$..... deposit.	<input type="checkbox"/> 1941	
	<input type="checkbox"/> 1940	
	<input type="checkbox"/> 1939	
	<input type="checkbox"/> 1926-1938..... \$2.50	

Name:.....
Address:.....

HOT SPECIALS!! FM TRANSMITTER

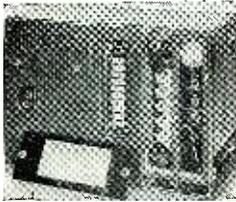

For 10 & 11 meters. BC-604, 30 watt. 20 to 30 MC. 10 channel push-button. x t a l controlled. Complete with 7-1619's, 1-1624 tubes, meter, diagram, case and covers. 12 or 24 volt. Good, used \$12.95

Set of 80 crystals in drawer when purchased with transmitter\$12.95

FM RECEIVER

For 10 and 11 meters. BC-603, 20 to 30 MC superhet. BFO, squelch; 10 push-buttons and manual tuning. Makes fine wide-band IF strip for 88-108 MC FM with converter. Includes 10 tubes, speaker, case and diagram. 12 or 24 volt. Good, used\$12.95



FREE CONVERSION INSTRUCTIONS

Simple, easy change to 115 VAC. Converter diagram furnished. Complete conversion (power supply and converter) costs less than \$7.00 to build.

COMBINATION OFFER, above, Rec. and Xmtr. Used\$24.95

HERE'S YOUR 2-METER RIG AND RECEIVER!!

RT-19/ARC-4, 140 to 144 mc; 4 xtal controlled channels. Super-het receiver has 13 tubes, xmtr has 7 tubes including 4 6L6's, 832A final. With all tubes, xtals, shock mount, dynamotor, control box, diagram, orig. crates, BRAND NEW\$24.95

SPECIAL MAY ONLY!

RF METER, W'house 0-1 amps with couple in 2" bakelite case, NEW\$2.95



MIDGET HEADSET

Hearing aid type HS30. Wt. ea. unit only 3/4 oz., total wt. 6 oz. Imped. 250 ohms, diam. 7/8". Fine for miniature radios, crystal sets, all around use. Can be used as low-imped. mike. Complete with headband, rubber ear plugs and shirt clip. BRAND NEW, orig. boxes. Gov't cost \$5.

YOUR COST.....2 Sets \$1.00

Please add postage for 3 lbs. Discounts in larger quantities.

BARGAINS !!

FINAL TANK COILS for BC-610, 500V plug-in fixed link: 2-3.5 mc 89c, 4.5-5.7, 5.7-8.0, 8-11, 11-14 mc\$1.19
25 mfd or .5 mfd 600v tubular.....12 for \$1.00
7 mfd. 600v oil-filled.....\$.65
Neut. Cond. for 807, 6L6, 1" plates .5-9mmf....\$.79
20 Meter center link 100V plug-in.....\$1.00
Var. Cond. 500 mmf Nat'l EMC500.....\$1.00
WIRE, 1/2 lb. No. 32 enam.....45c
1 lb. No. 20 enam.....60c

TRANSFORMER BARGAINS



B, 4v @ 16a, 2.5v @ 1.75a\$1.88
C, 'Scope 4000 vrms @ 10 ma\$3.65
D, Power, 315 VDC 85 ma; 5v 3a, 6.3v 2.1a No. 1159\$2.15
E, Power, 250 VDC 150 ma., 5v 3a, 6.3 5a, No. 1138 similar to "D".....\$2.65
CHOKE, 5h 225 ma 112 ohms GE, stick.....\$1.95

ARE YOU CONFUSED?

LET US SET YOU STRAIGHT

Cross-reference tube list—Army VT Numbers to commercial types. Price50c
Schematic diagrams for SCR274N, ART-13, BC375; BC191; BC221B, J, O, or R; BC348C; SCR269G; SCR522; BC721 Handi-Talkie; R19A/TRC-1; T14A/TRC-1; RT7/APN-1; ARC-1; RA34; BC611 Handi-Talkie; BC312N or NX; BC324N; BC314G; BC344D; BC659; BC603; BC604, Each.....\$1.00

WRITE FOR FREE LIST

Postage extra. Minimum order \$2.00
TERMS: Net Cash, 25% deposit on C.O.D.'s

ELECTRONIC SUPPLIES


317-R East 2nd St. Tulsa 3, Oklahoma

dynamic speaker. Operation is from 110 volts a.c. or d.c.

Further details may be secured from *Electric Eye Equipment Company*, 8 West Fairchild Street, Danville, Illinois.

NBFM ADAPTER

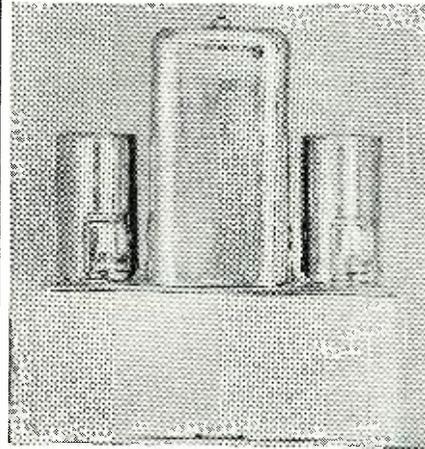By means of their newly-developed NBFM adapter, *Schuh's Radio Parts* of Chicago advises that any AM re-



ceiver can now be adapted to narrow-band FM to provide noise-free reception of amateur communications.

Available in two models 455-465 kc. and also 915 kc. for use with BC-348 receivers, this unit is small and compact. Designed for simple mounting in a variety of positions, the unit is completely chrome plated. A 6AK5 is used as a limiter while a 6AL5 serves as a discriminator. Complete instructions for attaching the unit are provided.


Full details will be supplied on request by *Schuh's Radio Parts*, 1253 Loyola Avenue, Chicago 26, Illinois.

CIRCLE CUTTER

Pittsburgh Coil Company of Carnegie, Pennsylvania, manufacturers of radio equipment, have added a unique circle cutter to their line of products.

This tool has been designed to cut servicing time in the workshop. The cutter is available in two sizes to take care of most circle cutting needs. The unit has a pin which keeps the tool from slipping when used in a hand brace. As this pin is removable, the cutter may also be used with an electric drill or drill press.

Furnished with a small adjustment

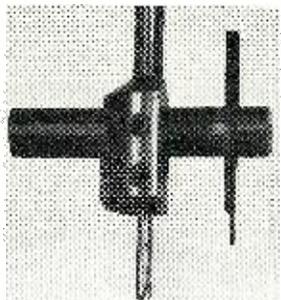

wrench, the *Pitco* circle cutter can be utilized to cut any desired radius from 3/8" to 6 1/2". Adjustment for depth of cut is also possible with this wrench.

The company, *Pittsburgh Coil Com-*

pany, will supply further details to those writing them at Carnegie, Pennsylvania.

THERMISTORS

The *Metallurgy Division* of *General Electric Company's Chemical Department* is currently introducing a line of Thermistors which will be available in the form of rods, discs, and beads.

Especially adaptable as the sensitive element in flow meters, time delay relays, switching devices, and other types of indicators and controls, these units can be used with either a.c. or d.c. current.

These Thermistors may be actuated either by ambient temperatures or by internal heating of the element. The negative coefficient of resistance of these units may be used to offset the positive coefficient of resistance of conventional types of electrical conductors, and they can be used in instruments, meters, or other circuit components to correct errors caused by extreme temperature conditions.

Additional information on these new Thermistors may be secured from the *Metallurgy Division, Chemical Department, General Electric Company*, Pittsfield, Massachusetts.

CRYSTAL MIKE

The *Astatic Corporation* has just introduced a new convertible type crystal microphone which features a de-



tachable "quick-lock" base. This feature permits the microphone to be used as a hand or desk mike or to be mounted on a floor stand.

The "Velvet Voice" is made with bright chrome grille, gold finished housing and handle, and dark brown baked enamel base. The unit is supplied in two models; the No. 200 provides a frequency response characteristic from 30 to 10,000 c.p.s. while the No. 241 has a similar range but with rising characteristics between 1500 and 5500 c.p.s. Either model may be supplied with or without switch.

The *Astatic Corporation*, Conneaut, Ohio has further details available on these two models.

TV CABINETS

In response to the demand for cabinets suitable for housing television receivers constructed from kits, the *Tel-*
(Continued on page 146)

EVERYTHING IN RADIO and ELECTRONICS IN ONE BOOK The Radio Data Book More Than 1000 Pages

All data and basic knowledge in radio and electronics digested into 12 sections . . . in a complete, quick to find, easy to read, handbook form.

HANDSOMELY BOUND IN RED AND GOLD

Plan every operation in radio and electronics with the *Radio Data Book*. This new radio bible will be your life-long tool . . . you will use it every day, on the board, at the bench, in the field! Use it for engineering, construction, troubleshooting and testing. The RADIO DATA BOOK will be your invaluable aid in design, experiment and in layout. It will help make your production better, faster and easier. In any and every operation in radio and electronics, you will use the RADIO DATA BOOK!

The RADIO DATA BOOK is a work of complete authority, prepared by engineers with many years of practical experience. They have been assisted by the Boland & Boyce staff of editors skilled in preparing electronics manuals for the U.S. Signal Corps for many years. These men have worked for several years gathering material for this book . . . all the knowledge of radio principles and operation . . . all the statistics . . . all the newest developments in electronics . . . every possible angle and detail. Eighteen months were spent digesting this material into the most concise, the clearest, and the most readable form. The result is this invaluable manual . . . The RADIO DATA BOOK. Whether you use this book for general reference, for scientific instruction, or for education, one thing is certain—the practical help, the daily usefulness you will derive from it will prove to be worth many, many times its astonishingly low price!

Advance Sale . . . first printing. Only 10,000 available . . . To make sure to get your RADIO DATA BOOK, mail your order

NOW!
12 complete books in one only **\$5.00!** Less than 42c per book!

CONTENTS

Each section is a COMPLETE coverage of its subject . . . 12 sections . . . 12 books in ONE, 1000 pages . . . Schematics . . . Accurate photographs . . . Specially prepared drawings . . . White on black charts . . . Diagrams . . . Isometric projections and exploded views.

Section 1. THE 150 BASIC CIRCUITS IN RADIO.

Every circuit is analyzed and explained in a Johnny-on-the-spot reference for any occasion.

Section 2. COMPLETE TEST EQUIPMENT DATA.

Know more about the test instruments you now have . . . Find the new ones you want to buy . . . They're All in here—impartially described!


Section 3. RECORDING.

Section 4. ALL ABOUT ANTENNAS.

AM-FM-Television . . . design, installation, characteristics, construction and feed.

Section 5. SOUND SYSTEMS.

Planning, installing and servicing a PA System. A complete chapter on every component . . . How to select and combine components . . . estimating costs . . . even acoustic requirements!

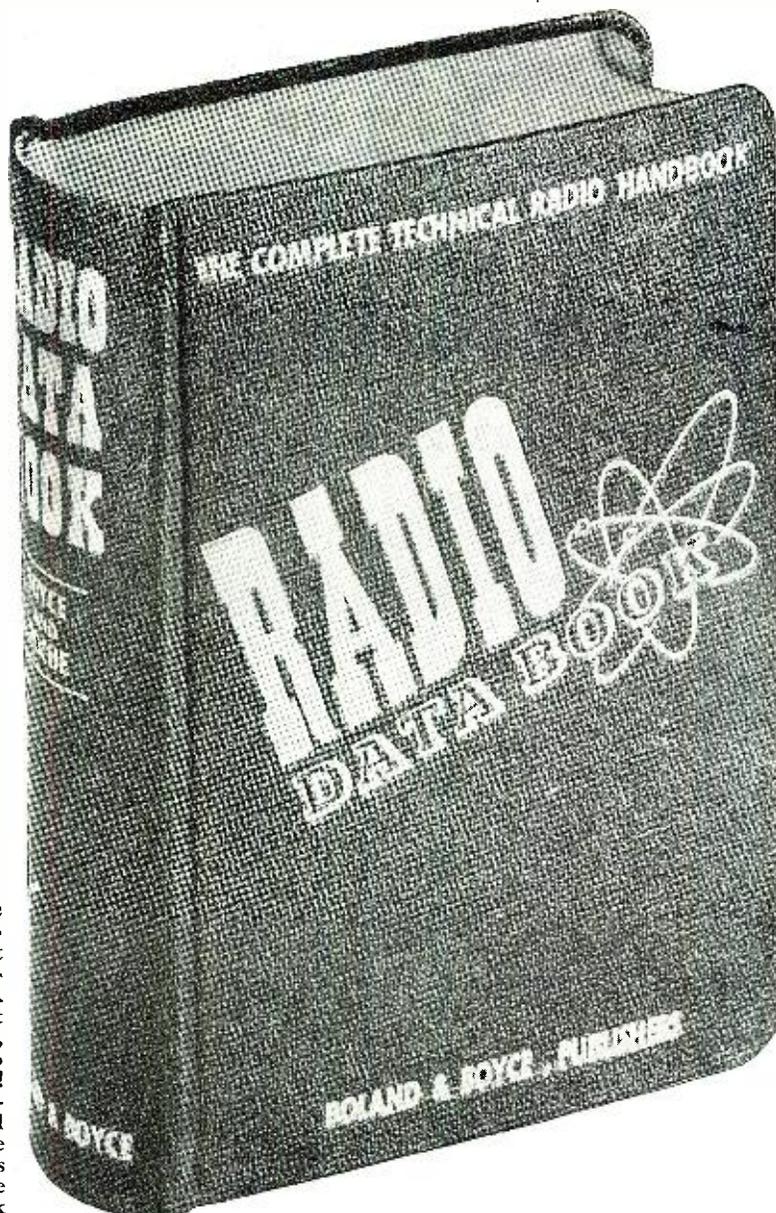

Section 6. ELECTRICAL AND PHYSICAL CHARACTERISTICS OF RADIO COMPONENTS.

Know the size, the power, the shape! A quick reference on the construction and design of any circuit or equipment.

Section 7. COMPLETE TUBE MANUAL: Receiving, transmitting and commercial.

A flick of the pages brings to you all the data and ratings of any tube made.

Section 8. CHARTS, GRAPHS AND CURVES.

Quick calculation devices . . . Plotting curves, nomographs, rules and tables for speedy solutions to radio problems.

Section 9. CODES, SYMBOLS AND STANDARDS.

Handy reference to all radio symbols and abbreviations; code symbols, phrase and characters . . . Where you want them . . . When you want them!

Section 10. 50 TESTED CIRCUITS DESIGNED FOR OPTIMUM PERFORMANCE.

Find any circuit you want with complete parts lists and specifications . . . One tube receivers to complete AM, FM and Television receiver circuits . . . Amplifiers . . . Transmitters . . . Test Equipment and Control Circuits . . . All with the latest engineering refinements.

Section 11. DICTIONARY OF RADIO AND ELECTRONIC TERMS.

Section 12. RADIO BOOK BIBLIOGRAPHY.

Mail this Coupon to Your Jobber or Direct to:

BOLAND & BOYCE INC., Publishers
460 Bloomfield Ave., Montclair, N. J.

Please send me a copy of
THE RADIO DATA BOOK Enclosed is \$5.00. (\$5.50 Foreign)

NAME.....
ADDRESS.....
CITY.....ZONE.....
STATE.....

BOLAND & BOYCE INC., PUBLISHERS

More for Your Money R & M RADIO

Satisfaction
Guaranteed
or your
money back

TRANSMITTERS & RECEIVERS FOR

10 Meter Mobile Rig

WAR SURPLUS SCR-274-N COMPLETE FOR ONLY

Conversion Book
gives details for low-cost,
easy conversion to


- 10 METER MOBILE RIG
- 20—40—80 METER BANDS

\$24.50




**COST GOVT
OVER \$600.00**

This sensation of all surplus is not only an ideal 10 Meter Mobile Rig! It's a complete amateur radio station! Here are a few more ways to use the equipment included in this Command Set. The transmitter VFO driver stage gives your BC-375-E higher RF output—as high as 150 watts. Make swell standby receivers with the BC-348 on round-table "rag chews." You get all this equipment: 3 Receivers—190-550 kc, 3-6 and 6-9.1 mc; two transmitters, 4-5.3 mc, 5.3-7 mc; four dynamotors—28 volts DC input; 1 modulator with carbon mike input; two tuning control boxes; one antenna coupling box with r-f ammeter; antenna relay and 5000 volt 50 mmfd. WE vacuum condenser (antenna relay can be used with most rigs); and a complete set of tubes for each unit—29 POPULAR TUBES in all. Mechanical cables for remote tuning of receivers supplied for \$1.00 extra.

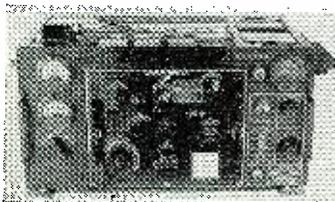

NAVY TRANSMITTER GP-7

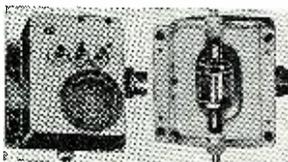125 watt xmtr., self-contained AC, 400 cycle power supply; uses suppressor grid modulation for phone, VFO controlled, 803 in final; built of std. parts. **\$17.50**



ANTENNA RELAY

BC-442-A, SWITCHING RELAY, ANTENNA CURRENT INDICATOR with 19.5 millivolt movement, current transformer and thermocouple, 50 MMFD vacuum condenser, fixed, 5000 volt rating (CAN BE USED WITH ANY RIG). **\$2.45**



Be sure to write for details of our complete AMATEUR RADIO STATION

CONVERSION BOOK

\$2.00

(with a purchase of \$5 or more,
available to you at just \$1.00)

Data on conversion, with schematic diagrams, instructions, and discussion, on the following:
Diag. and Conversions: BC-348, SCR-522, BC-375, SCR-274, SCR-274-10 meter mobile.
Diagrams for: BC-221, ART-13 Collins Xmtr., APN-1, APN-4, SCR-718.

Save \$1 by ordering when you purchase \$5 (or more) worth of equipment.



T-17 CARBON MICROPHONE

Brand new

\$1.85
each


Used \$1.00 each

Proclaimed "BEST BUY" by Hams from coast to coast

BC-453—190-550 kc.
BC-454—75 meters
BC-455—40 meters

Slight conversion for
10 and 20 meters

\$6.95

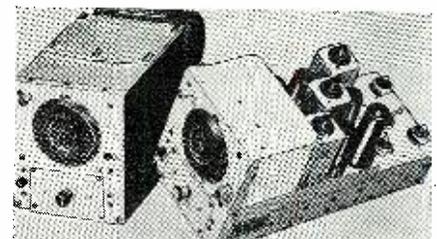

FOR PERFECT SINGLE SIGNAL RECEPTION

Says Jan. *QST* (p. 40, Tech. Topics): "... (BC-453A) will perk up that old broadband superhet of yours and make it cut through the QRM and pull out the desired signal like nothing you ever saw or heard." BC-455 is easily adapted to 10 and 20 meter reception as well as it works on 40 meters. Then all you need is one BC-454 to cover 75 meters and you have covered almost all of the Ham bands. Order yours today!


WAR SURPLUS BC-375-E TRANSMITTER

WITH THOUSANDS OF USABLE STANDARD RADIO PARTS

(Gov't cost, \$1800) **\$24.50** COMPLETE

It's been written about and talked about—just the thing for beginner or old-timer; has five tubes, five tuning units. Xmtr. designed to operate from 200 kc. to 12 mc. (less BC band). Equipped with antenna tuning unit BC-306-A — variometer and tap switch. Dynamotor (PE-73-C) complete with relay, fuses and filter. Diagram and instructions for its use supplied with each set. Weight: approx. 275 lbs.

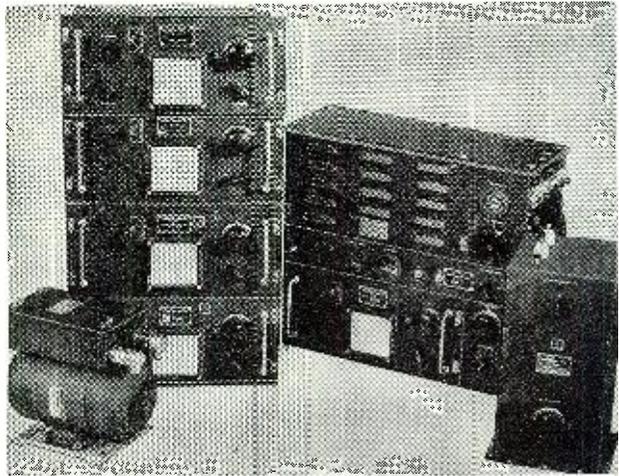Shipment from our nearest warehouse—East, Mid-West, or West Coast



APN-4 RECEIVER-OSCILLOSCOPE POWER SUPPLY



HEADPHONES

69c

HS-33 with cord and plug, 600 ohms — Used, in A-1 condition.




Has four screw-driver tuned R.F. channels selected by switch— I.F. frequency 1050 kc, I.F. band width 45 to 60 kc, R.F. frequencies 1600 kc to 2000 kc. Tube lineup: (2) 2Y2, (1) 5U4, (3) 6B4, (1) 6SU7, (1) 6SA7, (4) 6SK7, (1) 6SN7, (1) 6SL7, (1) 6H6 and (1) VR150.


The components of this receiver are the finest money can buy. Makes excellent fixed tuner for medium frequency police calls or public address system. Has power supply for 5 inch scope—just the set to make a panoramic scope for those high frequency I.F. receivers—power transformer 400 cycle. Low voltage supply is electronically controlled and delivers 260 v.d.c. 150 mills regulated to .01%. The power supply alone is worth more than the price. Only **\$12.50**

APN-4 INDICATOR—PRECISION OSCILLOSCOPE

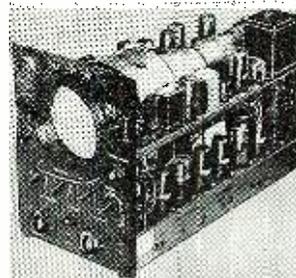Special for amateurs, experimenters and repairmen; can be converted into the following:



5-inch panoramic set with marker pips at 100 kc - 20 kc - 2 kc to enable you to observe crystal and V.F.O. drift and width of frequency deviation of FM; a precision sweep scope that is accurate with electronic switch for observing two signals simultaneously, and 100 kc lab. type crystal with TPTG oscillator circuit feeding six frequency divider stages. Tube lineup: (1) 6CP1, (3) 6SL7, (14) 6SN7, (6) 6H6 and (1) 6SJ7. Only **\$19.50**

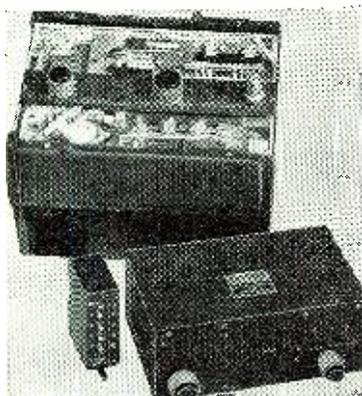


TWO METER MOBILE OR GROUND STATION

SCR-522, designed to operate from 100-156 mc. makes an ideal two-meter rig for two-way mobile radio; has one of the finest two-meter receivers ever designed. Complete trans. and rec., remote control Dynamotor PE-94 and all plugs.

\$24.50

PE-98 Dynamotor, 12 v. input, for use with SCR-522..... **\$12.50**

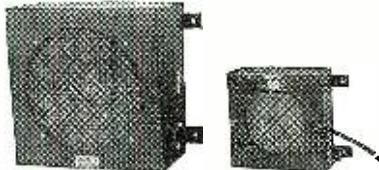PE-94 Dynamotor, 24 v. input..... **\$3.95**



HIGH FIDELITY SPEAKERS

6-inch, 10-watt PM Speaker, ea. **\$7.95**

12-inch, 15-watt PM Speaker, ea. **\$14.50**

Brand new in Heavy Duty Steel Cabinets with beautiful black wrinkle finish.

Also has T-pad volume control and 600 ohm line to speaker transformer. Wall mounting brackets and slope front.

HEADPHONE EXTENSION CORDS....25c

Approx. 72" long, rubber cov., with JK-26 & PL-55 plugs

HEADPHONE ADAPTERS MC-385....30c


(4 for \$1)

From high to low impedance, 4000 to 600 ohms; contains matching transformer.

ANTENNA SWITCHES

- Single pole, double throw..... **39c**
- Double pole, double throw..... **49c**
- Triple pole, double throw..... **\$1.25**

40 WATTS OUTPUT

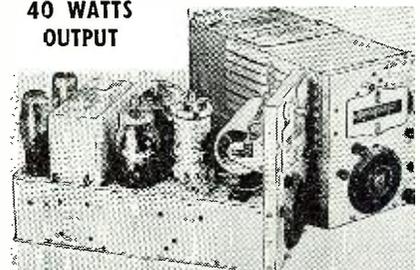

These famous VFO Drivers available:

BC-457 75 meters with slight conversion. **\$6.00**

BC-458 40 meters with slight conversion. **\$6.00**

● SAVE C.O.D. CHARGES by remitting in full, or send 25% deposit with orders. Please don't send money for postage; we ship "transportation charges collect".

All Equipment F.O.B.

R & M RADIO COMPANY, Dept. RN-58, 1426 N. Quincy St., Arlington, Va.

- Send Conversion Book. \$2 inclosed.
- Send C.O.D. Send FREE catalogue on kits:
- Xmtr. Receiver. Television.
- Transformer Listing

Name.....

Address.....

City.....

Zone..... State.....

R & M RADIO COMPANY

1426 N. QUINCY ST. DEPT. RN-58 ARLINGTON, VIRGINIA

INDUSTRIAL & ELECTRONIC POWER SUPPLY EQUIPMENT

TRANSFORMERS



T-103—Voltage regulator Transtat, American Transformer Co. Spec. 29145 Max. KVA output 11.5, 50/60 cyc. 0-15 V., 100 amps or 230 V., 50 amps. \$75.00 Net Wt. 134 lbs. Dim. 25" W x 16" D x 17 1/2" H (Encl. 8" shaft ext.)

T-101—Plate Transformer, Amerfran Spec. 29108. Primary 115 V. 60 cyc. 10.4 KVA. Secondary 17600 V. .520 amps. 35 KVA test. 8800/8800V W/center top grounded (specify)\$65.00 Net Wt. 500 lbs. Dim. 19" W x 15 1/2" D x 41" H. O. A.



T-102 — Filament Transformer. American Transformer Co. Spec. 29106. Type WS .050 KVA. 50/60 cyc. Single phase. 35 KVA test, 12 KV D.C. operating. Primary 115 V., secondary 5 V., 10 amps with integral standoff insulator and socket for 250T, 371, 872, 5563, etc. rectifier tubes. \$12.50 Net Wt. 15 1/2 lbs. Dim. 6 1/2" W x 6" D x 12" H. O. A.

CHOKE COIL

R-106—Amerfran Disc. Type. Specification No. 29107. Line volts 15,000 V. D.C., Ripple frequency 120, 149 ohms resistance, .020 D.C. amps at 900 henrys 48% ripple, .52 amps D.C. at 25 henrys 48% ripple.\$42.00 Net Wt. 280 lbs. Dim. 17" W x 12" D x 31 1/2" H. O. A.

CAPACITORS

C-107—G.E. Capacitor Cat. No. 14F59 or Westinghouse Inerteon, 1.0 mfd. 25,000 V. D.C.\$36.00 Net Wt. 65 lbs. Dim. 14 1/2" W x 8 1/2" D x 15" H. O. A.

RELAY

RC-117—Westinghouse Time Delay Current Relay. Type SC-M .2 to 1 amp A.C. or D.C. 8 amp continuous rating. Rating 20-40% drop out ratio. \$12.95 Net Wt. 3 lbs. Dim. 8" W x 5" D x 5 3/4" H.

METERS

M-140AB—Weston Model 476—3" A.C. Ammeter. 3 amp full scale, calibrated 0-120 amps. flush mounting, with 40/1 current trans.\$8.50 Net Wt. 3 lbs.


M-143AB—Weston Kilovoltmeter—3". Model 301. 20 KV. @ 1000 ohms per volt, flush type, calibrated for steel panel mounting, with 20 meg. 20 KV Weston resistor complete with clips and standoff insulators.\$18.00 Net Wt. 4 lbs.

HEATERS

H-149—Chromolox strip heaters, 300 W., 115 V. (1/2 x 1 1/2 x 12")\$1.00

POWER SUPPLY

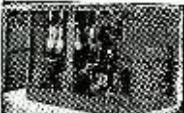(RA-38) 115 V., 60 cyc. input, adjustable output 0-15,000 V. A.C. or D.C. @ 500 Mils. Shipping weigh. 2100 lbs.. \$200.00 Can be furnished to deliver 0-7,500 V. @ 1.0 amp for\$250



All merchandise in "as new" condition. Add approximately 20% to net weights for estimated shipping weights. Terms are 30% with order balance C.O.D. All prices f.o.b. Los Angeles Warehouse. Write for additional detailed information on any of the above items and for special quantity discounts.

1527 E.
Seventh
Street

EPCO

Los Angeles
21,
California

Wave Shaper

(Continued from page 44)

opposite result is obtained. The negative half-cycles of sine wave input voltage cannot increase to a value higher than the voltage of cell B_2 , with the result that the negative peaks level off at that potential. However, the positive half-cycles are free to increase, and the essentially positive output pulses shown in Fig. 3D are obtained.

When both switches, S_1 and S_2 , are closed, both positive and negative half-cycles are clipped simultaneously, as they were limited separately in the preceding examples. The output under these circumstances then is an essentially square wave, such as is shown in Fig. 3E. For best squareness, the sine wave input voltage must have an r.m.s. value of 30, although at lower voltages the output waveform is sufficiently square for a number of test purposes. Only a few audio oscillators available to the serviceman and amateur deliver as high as 30 volts output. However, it is comparatively easy to connect a suitable stepup transformer between the low-voltage oscillator and the "INPUT TERMINALS" of the shaper.

With each type of output (See Fig. 3), the amplitude of the output signal may be adjusted to a desired level by means of the output potentiometer, R_2 .

When the shaper is not in use, both switches may be thrown to their open position, to prevent continuous drain of the dry cells through the crystals in series.

Construction

Small-sized parts were employed in the construction of the author's shaper unit. The photographs, Figs. 1 and 2 show external and internal assembly of the device. The metal case is a 4"x5"x2 3/4" "instrument box." It is not necessary to employ this same size in duplicates, however. A much smaller housing might have been used, but the particular box shown in the photographs simply happened to be in shop stock.

The experimenter who is interested solely in obtaining square waves from his audio oscillator and who has no need for the positive or negative pulses, might build an extremely small version of the shaper (with a single d.p.s.t. toggle switch to close both rectifier legs simultaneously) as an "adapter" to be plugged directly into the oscillator output terminals.

A *Sylvania* type 1N35 dual crystal diode is shown. This unit furnishes the two required crystals in a convenient mounting bracket. If an individual builder desires, two separate 1N34 crystals can be used.

As can be seen in Fig. 2, the pen-size dry cells are held to one inside wall of the case by a curved spring clip made of flat brass stock. The

toggle switches are mounted through the top cover of the case, the output control potentiometer through the front edge, and the insulated binding post blocks through opposite "end edges."

Wiring is simple and straightforward, but it is imperative that proper polarity of both the crystal diodes and the dry cells be observed.

If considerably higher sine wave input voltages must be handled, and higher battery voltages are to be used, selenium rectifiers may be substituted for the crystal diodes shown in Fig. 3.

Adjustment

After the shaper is completed and all wiring verified, the unit may be tested by feeding a sine wave voltage (power or audio frequency) to the shaper "input terminals" and connecting the shaper "OUTPUT TERMINALS" to the vertical amplifier input terminals of an oscilloscope. Throw both switches in the shaper to their "off" (open) position, set potentiometer R_2 for maximum output, and set the oscilloscope controls for internal sweep and internal synchronization.

With both shaper switches open, the sine wave pattern of Fig. 3B should be seen on the oscilloscope screen. Run potentiometer R_2 from one end of its range to the other to check its control of the output signal amplitude from zero to maximum. Then, reset R_2 for maximum output.

Close shaper switch S_1 only, noting that the positive peaks, as viewed on the scope screen, are clipped as in Fig. 3C. Open switch S_1 and close switch S_2 , noting now that the negative peaks are clipped, as shown in Fig. 3D.

Close both shaper switches, S_1 and S_2 , noting that both positive and negative peaks are clipped, as shown in Fig. 3E.

If the foregoing results are not obtained, and the wiring is found to be correct, it is very likely that the polarity of the cells or crystals, or both, have been reversed.

Operation

Connect source of sine wave voltage (audio oscillator or 60-cycle transformer secondary) to "INPUT TERMINALS" of shaper. Connect shaper "OUTPUT TERMINALS" to oscilloscope or to device (such as audio amplifier or network) under test.

Sine Wave Output. Open both shaper switches and adjust potentiometer R_2 for desired output signal strength.

Positive Pulse Output. Close shaper switch S_1 , leaving S_2 open, and adjust potentiometer R_2 for desired output signal strength.

Negative Pulse Output. Close shaper switch S_2 , leaving S_1 open, and adjust potentiometer R_2 for desired output signal strength.

Square-wave Output. Close both shaper switches and adjust potentiometer R_2 for desired output signal strength.



TUNING UNIT

A wealth of expensive parts. Contains: 6-A.P.C. Condensers, 6-coils, 3 or more mica condensers and registers, 1-porcelain two gang wafer switch and dozens of other useful units.....**\$2.98**



SPERRY AMPLIFIER

Brand new Servo amplifier containing two beam power output tubes (1632) similar to 2516, two twin triodes (1633 and 1634) similar to 6SC7, two mica condensers, dozens of color coded half-watt resistors, two dual and four section bathtub condensers, three transformers, two wafer switches, one volume control, four octal sockets. Easily convertible.....**\$3.95**



SCR-522 VHF TRANSCEIVER

The finest all purpose equipment on the surplus market. Tunes 100-156 MC. Don't confuse these with other incomplete and abused 522s. Sun Radio offers electronically perfect and guaranteed 522s AND COMPLETE with tubes (one 10 tube superhet receiver squelch circuit and one 7 tube transmitter), remote control box, 28 volt dynamo (can be converted to 110 V operation), 4 crystals and ALL CABLE CONNECTORS but less cable.....**\$24.95**

Sun Radio

FOR THE HOTTEST VALUES IN

Surplus Parts

CRYSTALS!

In the greatest purchase of radio transmitting crystals ever made by one wholesaler in the history of the Radio Parts Industry, Sun Radio acquired title over a half million dollars (500,000) of Army Surplus, precision built, exactly tooled crystals in moisture proof holders which are shock mounted. Please note that crystal shipments of 6 or less are packed in cloth containers to expedite handling. No worry because all crystals are shock mounted and guaranteed delivered perfect. All crystals have Army IIC harmonic rating but Sun encloses directions for deriving the correct fundamental frequency in kilocycles.

CRYSTALS WITH A MILLION USES

ke													
412	420	429	437	445	470	481	491	498	507	518	518	518	518
413	422	430	438	446	470	483	492	501	508	519	519	519	519
414	423	431	440	447	459	472	484	493	502	509	522	522	522
415	424	433	441	448	463	473	485	494	503	511	523	523	523
416	425	434	442	451	463	474	487	495	504	512	512	512	512
418	426	435	443	453	468	475	488	496	505	515	515	515	515
419	427	436	444	468	477	488	496	505	515	515	515	515	515

49c
each

I.F. Frequency Standards		Crystal Frequency Standards 98.356kc		For Crystal Controlled Signal Generators 525kc	
ke	ke	ke	ke	ke	ke
450	454.166	461.111	461.111	526.388	531.944
451.388	464.815	100 kc Standard	100 kc Standard	532.777	533.333
452.777	459.259	465.277	465.277	534.166	534.722
				536.888	538.888

ASSORTED MISCELLANEOUS CRYSTALS		FOR HAM AND GENERAL USE	
Fractions Omitted		Fractions Omitted	
370kc	376kc	381kc	384kc
372	377	383	386
374	379	388	388
375	380		
		390kc	395kc
		391	396
		403	406
		404	407
		405kc	408kc
		392	398
		394	401

• Payments must accompany order. Enclose 20c for postage and handling. Minimum order—\$2.00 plus postage.
• Crystals are shipped packed in cloth bags inasmuch as they are shock mounted. All shipments guaranteed.


BRAND NEW TUBES

SAVE UP TO 80% AT SUN RADIO

ALL STANDARD BRAND TUBES

No.	Price	No.	Price	No.	Price
024	\$1.32	8B7	\$1.00	12C8	\$1.59
1A5GT	1.00	8BA6	1.50	12F5GT	.81
1A7GT	1.08	8BA6	1.08	12H6	.90
1B4P	1.08	8BE6	1.08	12J5GT	.81
1B5/255	1.08	8BF6	.90	12J7GT	.90
1C5GT	1.08	8C6	.90	12K7GT	.81
1C6	1.08	8C6	.80	12K8	1.32
1E5GP	1.32	8C7	.57	12L7GT	1.08
1E7G	1.08	8E6	.80	12SC7	1.00
1F5G	1.08	8D7	1.08	12SF5	.90
1G4GT	1.08	8E5	1.32	12SF6	1.08
1F6	1.32	8D8G	.90	12SG7	1.00
1J6G	1.08	8F5	.90	12SH7	1.08
1G6GT	1.32	8F6	.90	12SJ7G	.90
1H4G	.90	8F8G	1.00	12SL7GT	1.32
1H5GT	1.08	8G6G	1.00	12SN7GT	1.08
1H6G	1.08	8H6	.75	12SP7GT	.90
1J5G	1.08	8J5	.75	12SR7	.90
1L4	1.08	8K6	1.08	1223	.81
1L44	1.08	8J6	1.59	1223	1.30
1L6	1.08	8K7	1.08	14A7/1287	1.32
1L84	1.08	8K6	.80	14A6	1.32
1LH4	1.08	8K7	.80	14H7	1.32
1LN5	1.08	8L6G	1.50	15L6GT	.90
1N5GT	1.08	8L7	1.32	25L6GT	.81
1Q5GT	1.32	8L7	1.32	25L6GT	.81
1R5	1.25	8N7	1.08	27	.57
1S4	1.25	8P7	1.32	30	.81
1S5	1.25	8P7	.80	31	.81
1T4	1.25	8SA7	.90	32L7GT	1.59
1T5GT	1.32	8SA7Y	1.59	35	.81
1V	.81	8SB7-Y	1.00	35L6GT	.81
2A6	.81	8SC7	.70	35W4	.69
2B7	.81	8SF7	1.08	35Z3	1.08
2E5	1.08	8SF7	1.08	35Z3	.66
3ABCT	1.59	8SG7	1.08	35Z4GT	.66
3Q5GT	1.32	8H7	.80	35Z5GT	.69
3S4	1.08	8J7GT	.75	36	.81
5T4	1.50	8K7	.80	37	.69
5U4G	.81	8L7GT	1.10	38	.90
5V4G	1.08	8M7GT	.90	39/44	.75
5W4	.90	8SQ7	.80	41	.69
5X4G	.90	8T7	.80	45	.66
5Y3GT	1.57	8S57	.80	45Z3	.90
5Y4G	.63	8U5/6G5	1.08	46	.90
5Z3	.90	8V6	1.35	50A5	1.50
5Z4	1.10	8V6	1.10	50B5	1.08
6A4	1.32	8W7G	1.10	50L6GT	.90
6A6	1.25	8V6G	1.10	56	.66
6A8	1.08	8V7	1.08	59	1.32
6A85/8N51	1.32	8V6G	1.08	75	.69
6AB7/1853	1.50	8Z5G	1.00	76	.75
6AC5GT	.90	7A4	1.00	77	.75
6AC7/1852	1.50	7A5	1.00	78	.75
6AD6G	1.32	7A7	1.00	79	.63
6AD7G	1.08	7C7	1.08	80	.44
6AEBGT	1.08	7E6	1.08	85	.75
6AEGG	1.08	7F7	1.32	89	.50
6AF6G	1.32	7H7	1.30	117L7GT/	1.92
6AG5	1.92	7J7	1.59	117M7GT	1.08
6AG7	1.92	7K7	1.32	117Z6GT	1.32
6AK6	1.32	7Q7	1.08	XK6	1.32
6AL5	1.08	7Y4	1.08	XFBT	1.32
6AQ5	1.08	12A5	.90	VR-90/30	1.92
6AQ6	1.08	12A6	1.32	VR-105/30	1.92
6AT6	.90	12AH7GT	1.32	182B	1.92
6AU6	1.08	12AT6	.50	485	1.92
6B4C	1.32	12B6	1.08	489	1.92
6B6G	.90	12B6E	1.08	2051	1.00

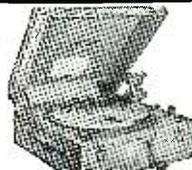10% additional discount in total quantities of 100 or more.



GI PORTABLE WIND-UP PHONOGRAPH

A high quality, sturdily built, full toned windup phone originally built for armed forces as moral phono. Special triple spring motor plays 3 records on 1 winding. Speed adjustable from 33-75 revs. Brand new packed with 100 multiple play needles.....**\$17.95**



GI RECORD CHANGER

This is the same record changer used in West, G.E., Emerson, etc. combinations. Changes up to 12—10" or 12" records at the lowest price ever offered. Brand New. Hurry!
\$15.95

PANEL METERS ALL BRAND NEW AND GUARANTEED

West 2" Round	
0-300 D.C.-M.A.	\$2.97
0-500 D.C.-M.A.	2.97
Simpson 2" Round	
0-15 D.C.-V	2.97
Triplet 2" Square	
0-40 D.C.-V	2.97
Sun 2" Round	
0-300 D.C.-V	2.97
GE 3" Square	
0-150 A.C.-V	3.49


PORTABLE AMPLIFYING MEGAPHONE

U. S. Army Signal Corps Surplus Complete in portable carrying case with electric megaphone and microphone. Pistol Grip and trigger switch. Additional hand microphone and switch. Portable tripod stand. Combination amplifier and battery case. Projects voice up to 1/4 mile. Used but guar. perfect. Complete with batteries.....**\$59.95**




100 WATT BENDIX TRANSMITTER

Four Separate Electronic Coupled Oscillators These can be easily converted to 20-40-80 meters. Crystal required for 10 meters. Each electronic coupled oscillator dial has 3000 divisions enabling quick precision shifting. This transmitter was constructed of the highest quality of precision parts, with laboratory precision. Four separate output tanks; one 4-position selector channel switch having seven sections which changes the ECO, IPA and output tanks simultaneously. All the controls are mounted on the front panel. The housing is cast aluminum; shields and case are sheet aluminum. Dimensions 11 x 12 x 15 inches, weighing 35 1/2 lbs. Complete, simple instructions for conversion furnished. Uses three 807, four 12SK7 tubes; one 2-inch 5 amp. R.F. meter. A complete coverage transmitter, for the new or experienced amateur. A TRUE HAM VALUE—BRAND NEW, complete with tubes.....**\$49.95**

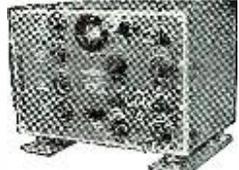

110 Volt AC Superheterodyne Receiver

This crystal fixed frequency receiver comes with full conversion instructions for variable tuning of all ham bands and broadcasts. A highly selective superheterodyne receiver, 110 V.A.C. power supply built in. Uses the following tubes: 6K7 RF Amplifier; 6F7 Detector and A.V.C.; 6C8 Output and Noise Suppressor; 80 Rectifier. Dimensions: 3 1/2 x 19 x 11 1/2 inches. Comes complete brand new, with one set of coils and two sets of tubes Extra Coil Sets With Set Only.....**\$16.95**

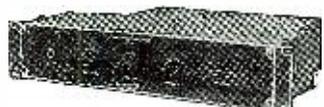

• All items F.O.B. Washington, D.C. All orders \$30.00 or less cash with order. Above \$30.00 25 per cent with order balance C. O. D. Foreign orders cash with all orders, plus exchange rate.


SUN RADIO

OF WASHINGTON, D. C.

938 F STREET, N. W. WASH. 4. D. C.

**Now! Get Your New
HALLICRAFTERS Set
From FEDERATED**

TRANSMITTER HT 17

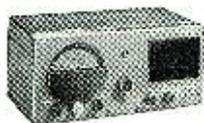


\$4950

Low price high quality transmitter. Covers 3.5 to 30 mc amateur bands with minimum output of 10 watts. Pi section

matching network permits use with any antenna, or easy coupling to a high pwr. final amplifier. Uses 6V6-GT osc.; 807 final amp. and 5Y3-GT rectifier. Self contained pwr. supply for 105-125V, 50/60 cycle operation.

**RECEIVER
S 53**

\$7950

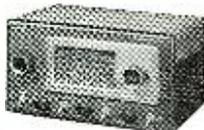

A reliable communications receiver. Covers the frequencies from 540 kc to 54.5 mc. Has a 2mc IF which eliminates images and repeat points. Features: voltage stabilized osc.; full electrical bandwidth; latest series type noise limiter; built in P.M. speaker; phone and phono jacks. Operation: 105-125V. 50/60 cycles. Complete with 7 tubes and rectifier.



**MARINE
REC. S 51**

\$12950

Especially adaptable to marine and air communications. Frequency from 132 kc to 13 mc allows reception on all vital communication channels. 3 fixed frequency channels can be preset. Built especially rugged to withstand all types of usage. Operation: 110V, AC/DC; provisions for pwr. supplies of 6, 12, or 32V batteries. Complete with 9 tubes plus rectifier.

TELEVISION RECEIVER

\$16900



Completely new Hallicrafter set. Pushbutton tuning on 13 channels. Intercarrier modulation type FM sound system insures fine sound reproduction. Designed for simple installation. Features: 7" picture tube (23 sq. in.); 18 tubes plus rect.; 110V, 60 cycle operation. Picture tube shipped in place. Size: 20"x16"x9 3/4". Shpg. Wgt. 40 lbs.



**AM-FM
REC. S 47**

\$25000

15 tube AM-FM receiver. 35 kc to 108 mc in three bands—5 pos. band sw. Push-button tuning for both AM and FM. Specially designed for custom installation. Automatic frequency control on FM band. 12 Watts audio output. Flat AM response from 30 to 7500 cps-FM: from 30 to 15,000 cps. Operation: 105-125V, 50/60 cycles.

**USE FEDERATED'S CONVENIENT TIME
PAYMENT PLAN**

Pay 20% down, balance in twelve monthly payments. Get your Hallicrafters set now . . . pay for it later.

**ALL MODELS AVAILABLE FOR IMMEDIATE
DELIVERY**

Federated Purchaser
INCORPORATED
distributor of RADIO-ELECTRONIC
SOUND EQUIPMENT
80 PARK PLACE, N. Y. 7
Phone: Digby 9-3050

FM SIGNALS Received in Australia

By CHARLES LYNCH

**General details of a home-built receiver that has
logged many FM stations in the United States.**

A HOME-MADE radio receiving set, designed by an Australian radio mechanic, which has been receiving FM signals and messages from stations in the United States, has aroused much interest in trade circles in various countries. This set was constructed by Frank Graham of Lower Plenty Road, Rosanna, a suburb of Melbourne, capital of the State of Victoria.

Mr. Graham discounts some suggestions that his receptions are freakish. He states that since September 1946, when he made the set at home in his spare time, more than 200 stations have been logged on a number of frequencies from 30.7 to 39.9 mc. Of these, approximately 100 would be on FM. They comprised police, special emergency messages, such as forestry and fire department signals.

The v.h.f. has been heard throughout the past 12 months, Mr. Graham says. The best periods for reception were from September to early December, and in March and April. Lower frequency bands (30.33 mc.) were the more consistent, though when the higher frequency bands (35.39) did open up they provided some splendid signals.

Reports were forwarded to many of the stations, and a considerable number of verifications have been received. In almost every case it was acknowledged that the report was the first received from Australia.


Mr. Graham provided the following data on his set which should be of interest to technicians.

The set is a 15-tube combined AM/FM receiver, with tube line-up as follows—6AK5 r.f.; 954 mixer; 955 oscillator; 6J8 second mixer; 6SK7 i.f.; 6SK7, i.f.; 6SJ7 first limiter; 6SJ7 second limiter; 6H6 discriminator; 6SJ7 tone control; 6SJ7 audio; 6V6 output; 5V4 rectifier; VR150 voltage regulator; and 6C5 "R" meter tube.

The 6AK5 is used under maximum voltage conditions, and seems to have good gain up to at least 100 mc. The 954 is used with grid injection from the 955 oscillator; a 2 μ fd. condenser being used to couple both grids. Plug-in coils, wound on 807 micanol tube bases, are used with the oscillator frequency 5 mc. higher than the signal frequency. Two sets of coils are used to cover the police and amateur bands—tuning from 55-40 mc., and from 40-22 mc. respectively.

The 954 is coupled to the 6J8 second

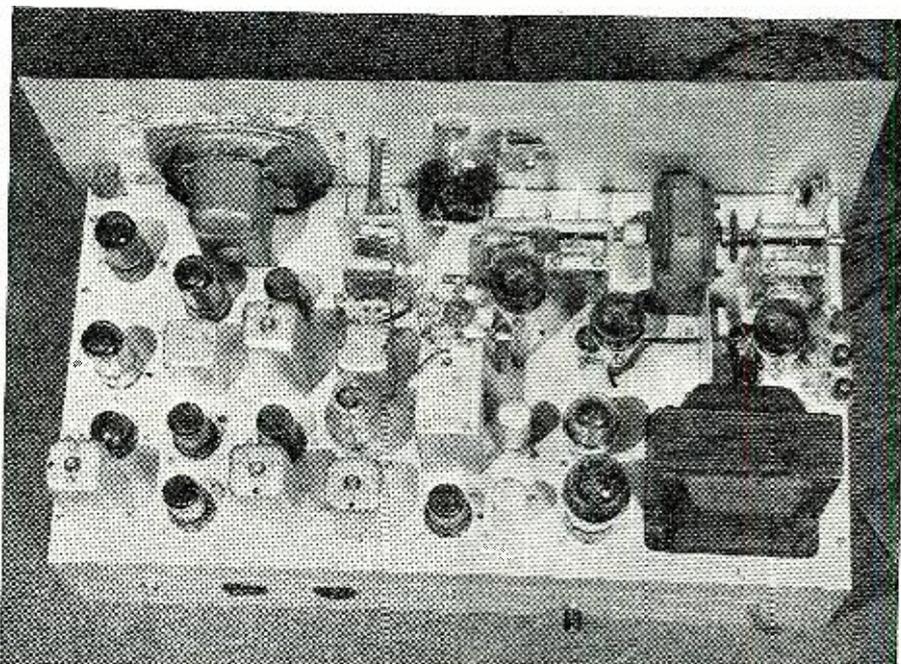Top view of chassis shows construction of Australian-built receiver.



mixer through a 5 mc. i.f. transformer. The oscillator section of the 6J8 is tuned to a fixed frequency of 5 mc. plus 455 kc. with a crystal oscillator. The 6J8 is coupled to the first 6SK7 through a 455 kc. crystal filter i.f., and a 5 mc. i.f. wired in series. The crystal filter is a variable selectivity *Hammarlund* type. The 6SK7 is coupled to the second 6SK7, and the second 6SK7 to the first limiter through 455 kc. and 5 mc. i.f.'s wired in series. The 6SJ7 first limiter has a grid resistor and condenser in the grid return. The a.v.c. for both FM and AM is taken from the voltage developed across this resistor, which also acts as diode load for AM. The first limiter is resistance-coupled to the second limiter. The screen and plate voltage of both limiters is 20 volts to give good limiting on weak signals. A standard Foster-Seeley discriminator is used. The tone control tube is of the voltage divider type with a large amount of high frequency attenuation, .002 μ fd. coupling condensers are used for bass attenuation to get maximum intelligibility on speech. The output of the 6V6 is fed to a 5-inch speaker which is built-in.

The FM/AM switch has three positions—narrow-band AM, with a 455 kc. i.f. channel and crystal filter; wide-band AM, with a 5 mc. i.f. channel; and FM, with 5 mc. i.f. channel and approximate bandwidth of 40 kc.

In the narrow-band AM position the plate voltage to the 6J8 oscillator section is switched on. The plate and screen supply to the first limiter is switched off, and the 6SJ7 acts as a diode detector with the audio output switched to the diode load.

For the wide-band AM the plate voltage to the oscillator section of the 6J8 is switched off, and this tube functions as a straight i.f. amplifier at 5 mc., followed by the two 6SK7's as i.f. amplifiers at 5 mc.

In the FM position the voltage to the limiters is switched on, and the audio output is taken from the discriminator.

The 5 mc. i.f.'s have 50 turns #32 enamel wire primary and secondary on $\frac{1}{2}$ -inch formers, spaced $\frac{1}{2}$ -inch apart and slug tuned. The discriminator i.f. has 40 turns on the primary and 60 turns, center tapped on the secondary—the secondary being at right angles to the primary, and spaced $\frac{3}{8}$ -inch apart.

The VR150 regulates the voltage to the 955 oscillator plate, 6J8 oscillator plate, and 6C5 "R" meter tube plate.

At present no special antenna is used for the v.h.f. bands. An L-type, approximately 60 feet in length, has been found to give quite satisfactory results.

-50-

PUEBLO SERVICEMAN'S ASSOCIATION

BY R. C. TRAVERS

FOR MANY years servicemen's associations have been a subject of controversy. However, the Pueblo Serviceman's Association has adopted a program which could very well serve as a blueprint for other associations in the United States to follow.

There are, at present, twenty-seven members of the Pueblo Serviceman's Association, all of whom are radio technicians. Before being accepted for membership in the association, all candidates must pass a two-part examination. The first part of the test consists of fifty "true and false" questions while the second part is a so-called "practical" examination.

Questions for the written examination are submitted by the membership. Each member formulates three questions covering radio servicing and from this group of questions fifty are chosen to comprise the examination.

Each serviceman, as a condition of membership, has to take a new examination every year. These examinations include questions involving television, FM, wire recording, etc.

Association members are required to adopt certain standards of shop operation. A service fee of \$1.75 per hour has been adopted as standard by the organization and members must agree not to cut this fee nor indulge in unfair competition. Members of the association are further required to present customers with itemized service invoices showing the nature of the services rendered, the cost of parts, and the period of the service guarantee, if such applies.

Members have access to the association's library which houses copies of schematic manuals, latest volumes covering television, FM, etc. In addition, the group has just purchased

a television kit and weekly association meetings feature a discussion of practical video circuit techniques from the service standpoint. Each member of the association is privileged to use the kit in the association laboratories for one three-hour period a week. The laboratories are equipped with a beat oscillator, cathode-ray oscilloscope, tube tester, set analyzer, wire and voice recorder, and three test benches. Association members may use the laboratory facilities for a period not to exceed three hours per week.

The organization cooperates in sponsoring newspaper ads and spot announcements on the radio. Each member has a radio spot dedicated to his shop some time during the week.

An inspection committee, consisting of four members, visits each membership quarterly to determine whether or not association standards with regards to shop cleanliness are being met. Shops which meet the standard are given a clean bill of health, those falling below par are given thirty days in which to correct the condition after which membership in the association is withdrawn. The standards are neither over-elaborate or burdensome. They consist of keeping the shops clean and free from junk.

The association meets once a week on Wednesday evenings from seven to ten-thirty. Dues are \$0.50 a week which sum goes toward the rental of laboratory space, etc. An assessment of \$1.00 a month is paid by every association member to cover the cost of the laboratory equipment.

Although the group is relatively small at the present time, applications for new memberships are being received in heartening numbers. -50-

LEARN RADIO

LEARN FAST
LEARN RIGHT
AT A PRICE YOU
CAN AFFORD

A. A. Ghirardi



Easy-to-understand BASIC TRAINING FOR BEGINNERS

(Used by U.S. Army & Navy!)
The best training costs the least! Actually, Ghirardi's famous 972-page RADIO PHYSICS COURSE" book has given more Radio-Electronic beginners their start than any other book or course ever published. Contains complete basic training to fit you for a career in any phase of Radio - Electronics work. Over 300 pages make Basic Electricity easy to learn. Other subjects include Radio Transmission; Broadcast Stations; Receiving Units; Vacuum Tubes; Detection; Amplification; Photoelectric Cells; Short Waves—a total of 36 basic subjects. If broken into lessons and sold as a "course," you'd regard this big book as a bargain at \$50 or more! Over 500 illustrations. Use coupon. Read it for 5 days at our risk!

Only \$5

RADIO
PHYSICS
COURSE

36 Courses
in one
giant book.

A COMPLETE COURSE IN RADIO-ELECTRONIC SERVICING

Learn professional service
work at home!

Study now for a good job as a Radio-Electronic service repair expert! It's easy to learn from Ghirardi's 1300-page, profusely illustrated MODERN RADIO SERVICING book that costs you only \$5 complete. Covers all phases of the work. Explains service test instruments and when, where and why to use each type. Even tells how to build your own. Tells how to troubleshoot all kinds of radios, analyze their circuits, test components, make all types of repairs, adjustments, installations, etc. Even explains how to start successful radio service business. See Money-Saving Combination offer.

Only \$5

MODERN
RADIO
SERVICING

Learn to be a
Service Expert—
at home—without
an instructor!

CUTS SERVICE TIME IN HALF ON 4 JOBS OUT OF 5

Whether you repair radios professionally or only work with them occasionally, Ghirardi's RADIO TROUBLESHOOTER'S HANDBOOK can save you time and useless testing on almost any job. Just look up the make and model of the radio you want to fix. Book covers common troubles in over 4800 receivers by 202 manufacturers. Tells what to do—exactly how to do it. Over 300 additional pages contain charts, data, tube information, codes, etc. that will help you save time, do better work in repairing any radio ever made. 744 big, manual-size pages. Weighs almost 4 lbs. Use coupon. See Money-Saving Offer!



Only \$5

RADIO
TROUBLE-
SHOOTER'S
HANDBOOK
NOT a "study"
book!

SAVE
MONEY!

Let RADIO TROUBLESHOOTER'S HANDBOOK save you time on common service jobs! Let MODERN RADIO SERVICING train you for truly professional radio-electronic service work. Get both big books for special price of only \$9.50 for the two. Use coupon.

5-DAY MONEY-BACK GUARANTEE

Dept. RN-58, Murray Hill Books, Inc.,
232 Madison Ave., New York 16, N. Y.

Enclosed find \$..... for books checked; or send C.O.D. (in U.S.A. only) and I will pay postman this amount plus a few cents postage. In either event, it is understood I may return books after 5 days if not satisfactory and my remittance will be refunded.

RADIO PHYSICS COURSE \$5 (\$5.50 foreign)

RADIO TROUBLESHOOTER'S HANDBOOK \$5 (\$5.50 foreign)

MODERN RADIO SERVICING \$5 (\$5.50 foreign)

MONEY-SAVING COMBINATION. Both Modern Radio Servicing and Troubleshooter's Handbook for only \$9.50 for the two (16.50 foreign).

Name

Address

City & Zone State

DUE TO POPULAR DEMAND WE REPEAT THESE TERRIFIC BARGAINS

- Three assorted new MICROPHONES, including push-to-talk type..... \$1.49
- Ten assorted R. F. Chokes including high frequency types..... \$.35
- Five assorted AUDIO or FILTER CHOKES..... \$.99
- One hundred assorted RESISTORS..... \$1.95
- Ten assorted JAN CABLE CONNECTORS, including SCR274, 522 and BC 375 types..... \$.99
- Six assorted OIL FILLED CAN TYPE CONDENSERS, all with mounting brackets..... \$1.49
- Ten assorted METAL & BAKELITE KNOBS—(no wooden knobs)..... \$.39
- Six assorted VARIABLE CONDENSERS, including butterfly types..... \$1.49
- Six assorted POWER and AUDIO TRANSFORMERS, all new..... \$1.98
- Six assorted isolantite and bakelite R. F. COILS, shielded and unshielded..... \$.99

The above ten assortments totaling over \$12.00 at the unbelievable bargain prices listed can be purchased together as one lot at a super-special total price of only \$10.00. All merchandise guaranteed to be as advertised.


RT1463 7 tube amplifiers containing 3-7F7, 1-7Y4, 3-7N7, 4 potentiometers, numerous resistors, filter and bypass condensers, filter chokes, power and audio transformers, and six sensitive plate relays. A military development that provided amazing stepless control proportional to correction required for ailerons, rudder and elevator, in the original control amplifier of the ordinary type would defect the would be too great, starting a series of lockings and would greatly increase fuel consumption and elapsed time in reaching the objective. This phenomenal unit, with its 3 amplifiers and six 5000 ohm relays in bridge circuits, will accurately control any 3 operations, related or unrelated, in minutely adjustable uniquely quantitative variations either forward or reverse directions. 9"x7"x8" black crackle aluminum case. Brand new in original carton. \$9.95.

Aluminum gear box 18x8x7 that contains two powerful electric motors and two matched gear trains. 62 gears in all varying in size from 1/2 to 4 inches in diameter. This unit is readily converted to rotate a beam antenna or any other similar usage..... \$3.00


BRAND NEW 110 V AC INPUT POWER SUPPLY, in grey enameled shock-mounted case 9" x 10" x 16". Several heavy duty resistors, 3 chokes, 4-1000 V and 600 V oil-filled condensers, 1 relay, 2-5U1's, 3 voltage regulator tubes safety interlock, and several fuses are included in this regulated power supply at the bargain price of..... \$9.95

SCR-274N COMMAND SET

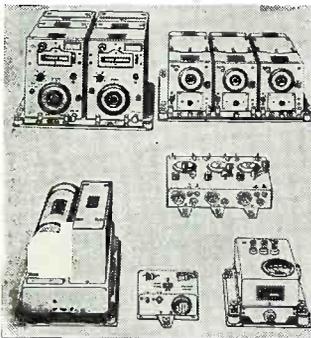The greatest radio equipment value in history



A mountain of valuable equipment that includes 3 receivers covering 190 to 550 KC; 3 to 6 MC; and 6 to 9.1 MC. These receivers use plug-in coils, and consequently can be changed to any frequencies desired without conversion. Also included are two Tuning Control Boxes; 1 Antenna Coupling Box; four 28 V. Dynamotors (easily converted to 110 V. operation); two 40-Watt Transmitters including crystals, and Preamplifier and Modulator. 29 tubes supplied in all. Only a limited quantity available, so get your order in fast. Removed from unused aircraft and in guaranteed electrical condition. A super value at \$29.95, including crank type tuning knobs for receivers. Without these knobs the receivers can't be tuned, and are only useful for parts. Don't buy without knobs! We also include one 60 cycle, 110 to 24 volt filament transformer for receiver—FREE.

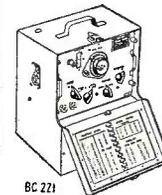

BC-221 FREQUENCY METERS with calibrating Crystal and calibration charts. A precision frequency standard that is useful for innumerable applications for laboratory technician, service man, amateur, and experimenter at the give away price of only \$36.95.

100 KC crystal calibrator kit containing everything that is necessary to construct a 100 KC osc. that will supply 100 KC marker points to your receiver so that it may be used for frequency determination. The 100 KC crystal is worth far more than the price that we are asking for the complete kit.

- Kit 100K Plate and fil voltage supplied by receiver..... \$9.95
- Kit 100KA Same as above, including 110 VAC or DC self-contained power supply... \$12.95


RECORDING AMPLIFIER. 3 stage, 110 V, 25 or 60 cycle high gain amplifier built by recently bankrupt manufacturer specifically for recording use. Transformer for low impedance wire recorder head and magnetic cutter included on chassis. Tone and volume controls and switches on chassis for playback, recording or use as public address amplifier. Complete with tubes..... \$9.95



SCR-284 TRANSMITTER-RECEIVER. This medium power transmitter and the accompanying 7-tube very sensitive receiver are naturals for 80 or 40 meter operation (phone or CW), on either fixed stations or mobile applications. These units are brand new and come complete with 100 KC calibrating crystal and instructions and diagrams for use with up to 100 watts input to the final stage on 40 or 80 meters for either phone or CW, using vehicle or 110 Volt power supply. Your cost..... \$39.95

PE-109 32-VOLT DIRECT CURRENT POWER PLANT

This power plant consists of a gasoline engine that is direct coupled to a 2000 watt 32 volt DC generator. This unit is ideal for use in locations that are not serviced by commercial power or to run many of the surplus items that require 24-32V DC for operation. The price of this power plant is only \$58.95. We can also supply a converter that will supply 110V AC from the above unit or from any 16-32V DC source for \$12.95.

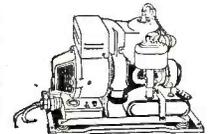


BRAND NEW INVERTERS AND DYNAMOTORS
 PE 6A: A 24 to 32 V DC input, to 80 V AC regulated output converter—\$12.95.
 PE 19A: A 24 to 28 V DC input, to 80 V AC at 80 cps output—\$9.95
 (We include a stepup transformer with each of the above so that 110 VAC is available from either.)
 27 V DC input. Output 300 V @ 75 MA, output—98c.
 12 V DC input. Output 300 V @ 150 MA, 150 V @ 15 MA and 12 V @ 5 Amp—\$5.95.
 13 or 26 V DC input. Output 800 V DC, 400 DC @ 135 MA, and 9 V AC—\$12.00.
 (By running on 8 V AC, 60 cycle input, with a sma amount of DC for field excitation, the above dynamotor will provide a good source of 12, 24, 400 or 800 V DC.)

GENERAL ELECTRIC RT-1248 15-TUBE TRANSMITTER-RECEIVER

TERRIFIC POWER—(20 watts) on any two instantly selected, easily pre-adjusted frequencies from 435 to 500 Mc. Transmitter uses 5 tubes including a Western Electric 316 A as final. Receiver uses 10 tubes including 955's, as first detector and oscillator, and 3-7H7's as IF's, with 4 slug-tuned 40 Mc. IF transformers, plus a 7H7, 7E6's and 7F7's. In addition unit contains 8 relays designed to operate any sort of external equipment when actuated by a received signal from a similar set elsewhere. Originally designed for 12 volt operation, power supply of a received signal from a similar set elsewhere. Originally designed for 110V AC, using any supply capable of 400V DC at 135 MA. The ideal unit for use in mobile or military service in the Citizen's Radio Band where no license is necessary. Instructions and diagrams supplied for running the RT-1248 transmitter on either code or voice in AM or FM transmission or Facsimile transmitter or receiver, as an amateur television transmitter or receiver, for remote control relay for marine or mobile use. The dynamotor which will work on either 12 or 24V DC and supply all power for the set is only \$15.00 additional.


14-Tube UHF Superhet Receiver — \$39.95

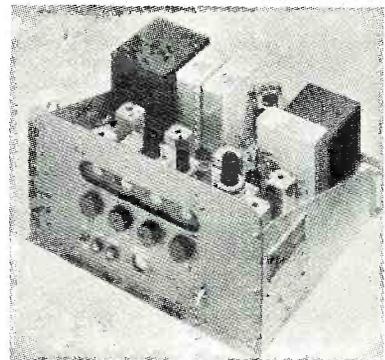

This beautifully constructed receiver was designed especially for Signal Corps communication service, and is one of the finest and most sensitive sets ever manufactured. Operating from 110V 60 cycles, this set has two tuned RF stages, tuned converter and oscillator, five I.F. stages, using iron core I.F.'s a diode detector, tuning eye, and a two stage amplifier that will drive a speaker or phone. The frequency range is 158-210 Mcs. It is a simple matter to operate on other bands by making a slight alteration in the tuning coils. A complete set of tubes is included with each receiver, along with a circuit diagram and parts list. The high-voltage power supply delivers 150 milliamperes, and is well filtered by a heavy-duty choke and three 7 Mfd. oil-filled condensers. This buy of a lifetime cost the government about \$700. Amateurs and experimenters will never again be able to purchase fine equipment at such a tremendous saving! See January Radio-Craft, Page 57, for complete conversion to television receiver.

GENERAL ELECTRIC 150 WATT TRANSMITTER

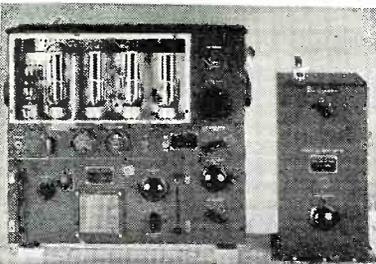Cost the Government \$1800.00
 Cost to you \$44.50!!!!




This is the famous transmitter used in U.S. Army bombers and ground stations, during the war. Its design and construction have been proved in service under all kinds of conditions, all over the world. The entire frequency range is covered by means of plug-in tuning units which are included. Each tuning unit has its own oscillator and power amplifier coils and condensers, and antenna tuning circuit—all designed to operate at top efficiency within its particular frequency range. Transmitter and accessories are finished in black crackle and are in a transmitter, well-protected in a black crackle case. **FREQUENCY RANGE:** 1100 to 500 KC and 1500 to 12,500 KC. (Will operate on 10 and 20 meter band with slight modification.) **OSCILLATOR:** Self-excited, thermo compensated, and hand calibrated. **POWER AMPLIFIER:** Neutralized class "C" stage, using 211 tube, and equipped with antenna coupling circuit which matches practically any length antenna. **MODULATOR:** Class "B" uses two 211 tubes. **POWER SUPPLY:** Supplied complete with dynamotor which furnishes 400V DC at 350 MA. Complete instructions are furnished to operate set from 110V AC. **SIZE:** 21 1/2 x 23 9/16 inches. Total shipping weight 200 lbs. comes with all tubes, dynamotor power supply, five tuning units, antenna tuning unit and the essential plugs. These units have been removed from unused aircraft but are guaranteed to be in perfect condition.

BUFRAD CAR RADIO ANTENNAS

All of our car radio antennas are made of triple plated Admiralty Brass Tubing, complete with low loss shielded antenna leads and high quality fittings.
SIDE COWL—BR-1, 3 sections extend to 66". Your price—single units—\$1.50; in lots of 12—\$1.35 ea.
SKYSCRAPER—BR-2 has 4 heavy duty sections that extend to 98". Your price—single units—\$2.45; in lots of 12—\$2.25 ea.
TILT ANGLE—BR-3, may be adjusted to all body contours. 3 sections extend to 66". Single unit price—\$1.50; 12 lot price—\$1.25 ea.
VERSATILE—BR-4, single hole fender or top cowl mounting may be adjusted to conform with all body contours. 4 sections extend to 56". Single unit price—\$2.90; 12 lot price—\$2.75 ea.
THE MONARCH—BR-5, single hole top cowl mounting, 3 sections extend to 56". Single unit price—\$1.90; 12 lot price—\$1.75 ea.

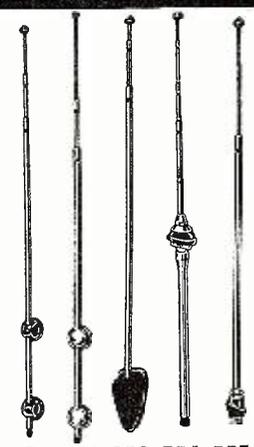After Seeing our Antennas and Comparing, You Will Never Buy Any Other Make!



BR1 BR2 BR3 BR4 BR5

BENDIX SCR 522—Very High Frequency Voice Transmitter-Receiver—100 to 156 MC. This job was good enough for the Joint Command to make it standard equipment in everything that flew, even though each set cost the Gov't \$2500.00. Crystal Controlled and Amplitude Modulated—HIGH TRANSMITTER OUTPUT and 3 Microvolt Receiver Sensitivity gave good communication up to 180 miles at high altitudes. Receiver has ten tubes and transmitter has seven tubes, including two 832's. Furnished complete with 17 tubes, remote control unit, 4 crystals and the special wide band VHF antenna that was designed for this set. These sets have been removed from unused aircraft and are guaranteed to be in perfect condition. We include free parts and diagrams for the conversion to "continuously variable frequency coverage" in the receiver. The SCR 522 complete with 24 volt dynamotor sells for only \$37.95. The SCR 522 is also available with a brand new 12 volt dynamotor for only \$42.95.

\$9.95 TAKES ALL THREE BIG BARGAINS

- 1. AUDIO AMPLIFIER** Undreamed of value. Uses 6V6's. Has 4 microphone inputs brought to jacks at rear panel. Various output impedances available at rear panel connections. Steel case with chrome handles. 9" long x 9" high x 6" deep. Tubes included. New in original cart. Shipping weight 20 lbs. **SUPER SPECIAL—\$4.95** while supply lasts.
- 2. RADIO HEADSETS** Latest supersensitive type with rubber earpieces. Every pair guaranteed perfect. \$5.99 per pair OR 3 PAIRS FOR \$1.00.
- 3. HOME WORKSHOP AT BARGAIN PRICE** Accurate and precise 2 speed guaranteed hobby lathe, the essential machine for the home workshop. Sturdy enough for light production work or factory shop service. Supplied with 66" of belt for connecting to any available electric motor or power take-off, such as on a jeep or tractor. Also included in this unbelievably advertised price are such accessories as a 1/2" drill chuck with specially hardened tool steel jaws, a 4" electric furnace high speed grinding wheel, a cotton buffing wheel with a large supply of buffing compound, and a 4" steel wire scratch brush. Your cost \$6.00. Sole export agent. Distributor inquiries invited.
NO C. O. D.'s—ORDER NOW—DON'T DELAY


FLUORESCENT LIGHT BALLASTS. Single 30 or 40 watts. \$1.68; Dual 40 watt High Power Factor—\$3.75.
HEADPHONES—Highest quality Signal Corps headsets with 12" cord and plug \$1.25. 5" rubber covered patchcords with phone plug and socket—45c.
LINE FILTERS—110V—each unit contains two 2 mfd. oil filled condensers and a 15 amp. iron core choke. This filter has innumerable uses such as oil burner line filter, etc. A ten dollar value for 98c.

RT-1579 consists of a three stage (cascade 6SJ7's and 6F6 output stage high gain, high fidelity amplifier with 60 cycle, 110V power supply on the same 13 1/2 x 1 1/2 chassis, which is protected by a substantial steel cover over tubes and parts. Made by Western Electric with typical quality components such as a husky power transformer and oil condensers. This unit is obviously intended to give years of trouble-free service with no more need for repairs than a telephone. Disconnecting one wire each, from the special input and output filters, will result in as high a fidelity amplifier as can be obtained. Your cost with tubes, diagram and parts list included—\$14.95.

SENSATIONAL SCOOP—Brand new 1948 model 7 1/2 H.P. twin cylinder outboard motor made by the world's second largest manufacturer of outboard motors. Regular price everywhere \$169.95. Our amazing price on this hard-to-get item at the peak of the seasonal demand is \$142.95.

AT LAST YOU CAN AFFORD A LABORATORY STANDARD MICRO VOLTER

The famous Measurements Corp. Model 78B, 5 Tube Laboratory Standard Signal Generator (that sold new, FOB Boonton, N. J., for \$810.00 net) is available in perfect condition for 25 to 60 cycles, 115 V AC operation. Until now this is the sort of topflight lab equipment that discriminating buyers have only vainly hoped would be released at a bargain price. Worth every cent the manufacturer asks, but available FOB Buffalo while our limited supply lasts for only \$79.95. Such companies as Admiral Corp. and John Meck, Inc., have ordered from us and repeated many times on these 78 generators for use in their labs and production line testing.

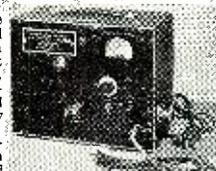

Model 78-B Standard Signal Generator. Two Frequency Bands between 15 and 250 megacycles.

"REMEMBER THAT A STANDARD IS ONLY AS RELIABLE AS ITS MAKER."

FILTER CHOKES: 200, 300, 400, 500 ohm light duty—59c; 200 or 300 ohm heavy duty—99c; 250 ma 35 ohm, made for U.S. Navy; fully shielded—\$1.95; 75 ohm 125 ma—25c or 25 for \$4.25; "Meissner type" tapped filter chokes—25c; 8 amp. iron core A filter—25c; Choke-condenser combination, ideal to replace any size speaker field when installing PM speaker—79c.
110V. CIRCUIT BREAKERS of Magnetic type; Following Current Ratings in Stock: 1.25, 3, 4, 8 Amps. Please specify. \$1.95 each.
SEVEN ASSORTED 1:1 TRANSFORMERS—\$1.98; Five Assrd. Oscillator Coils—69c.
SELENIUM RECTIFIERS—Dry disc type 1 1/2", 1", 1.2 Amp. maximum, suitable for converting DC relays to AC, for supplying filament source in portable radios, converting DC meters to AC applications, and also may be used in low current chargers—90c.
METER RECTIFIER—Full wave, may be used for replacement, or in construction of all types of test equipment—\$1.25. Half wave—90c.
FREE !!! THIS MONTH ONLY
A HIGH GRADE CRYSTAL PICK-UP WITH THE PURCHASE OF EACH PHONO MOTOR AT \$4.95.

MICROPHONES—All nationally known brands. Bullet crystal—\$5.45; Bullet Dynamic—\$7.45; Mike Jr.—60c; Handy Mike—90c; La-pel Mike—93c; SHURE T-17 MIKES, with push to talk switch—90c.
20 ASS'D COIL FORMS, including 11 ceramic, 3 polystyrene, and 6 fiber, all useful sizes—50c.
VARIABLE CONDENSERS: 350 MMFD—5 gang—\$1.95; 5 gang—\$1.49; 3 gang—\$1.00; 7.5 to 20 MMFD—1750V spacing, extra long shaft Hammarlund—69c; miniature variables, 25 MMFD—39c; 50 MMFD—49c; 75 MMFD—59c; 100 MMFD—69c; 140 MMFD—79c.
INTERRUPTION FREQUENCY COILS for super-regenerative receivers or the tremendously popular FM adapters for standard broadcast sets. Iron core with a resonant frequency of 50 KC—39c; Air Core. 100 KC—29c.
30 MC IF TRANSFORMERS, double slug tuned—25c.
30 MC VIDEO AMPLIFIER PLATE COILS—Slug tuned—25c.
REMOTE CONTROL UNIT: Aluminum case 4x3x2" containing 2 potentiometers, triple pole switch, 4 knobs, gear mechanism, counter and phone jacks—59c.
MODULATION TRANSFORMERS—10 watt, metal case 98c; 30 watt, open-type \$1.95; 40 watt, cast aluminum case, \$2.95; Class "B" input transformers, cast aluminum case, \$1.95; Transceiver audio transformers, 65c; Transformer modulation transformers, 65c.

AUTO RADIO DEALERS! ATTENTION!
 Nationally advertised brand of 1948 car radio which will fit practically any car and every pocketbook. Six tube superheterodyne with three gang condenser and 2 1/2" speaker. \$32.00 for sample, or Dealer price \$29.97 each, in lots of two or more.
 Here is an item that no serviceman who repairs auto radios should be without. Nationally advertised **ATR BATTERY ELIMINATOR** that supplies perfectly filtered 12 VDC or 6 VDC at 14 amp from 110 VAC.....\$36.00

RADIO SERVICEMEN! Buffalo Radio Supply's lower prices mean increased profit for you. Order all of your needs from us and receive in return courteous service and first class merchandise at the lowest prices in the country.

TUBES: all types in stock, 60% off on all tubes if ordered in lots of 10 or more.
TRANSFORMERS—All types in stock. **AUTO-TRANSFORMERS**: Steps up 110V, or steps down 220V to 110V—\$1.95. **FIL. TRANS.**: 6.3V, 20 Amps—\$1.98; Universal Output Trans. 8 Watt—89c; 18 Watt—\$1.29; 30 Watt \$1.69. **AUDIO TRANSFORMERS**: S. Plate to S. Grid. 3:1—79c; S. Plate to P.P. Grids—79c; Heavy Duty Class AB or B. P.P. inputs—\$1.49. **Midget Output for AC-DC sets—69c; MIKE TRANSFORMER** for T-17 Shure microphone, similar to UTC oncener type—\$2.00. **Stancoer SR or DB mike** to line or grid—\$1.95.
POWER TRANSFORMERS—14lf-shell type. 110V, 60 cy. Centertapped 11V winding. Specify either 2.5 or 6.3V filament when ordering.
 For 4-5 tube sets—650V, 40MA, 5V & 2.5 or 6.3V.....\$1.49
 For 5-6 tube sets—650V, 45MA, 5V & 2.5 or 6.3V.....1.75
 For 6-7 tube sets—675V, 50MA, 5V & 2.5 or 6.3V.....1.90
 For 7-8 tube sets—700V, 70MA, 5V & 6.3 or 2.5V.....2.35
 For 7-8 tube sets—700V, 70MA, 5V & 6.3 (25 Cycle).....3.60
 For 8-9 tube sets—700V-90MA, 5V-3A, 2.5V-3.5A, 2.5-10.5A.....2.85
 For 9-11 tube sets—700V, 5V & 6.3V-4A.....2.85
 For 9-15 tube sets—800V, 150MA, 5V & 6.3V.....2.95

CONDENSERS—PAPER TUBULAR 600 WV—.001, .002, .005—.8c; .01, .05—9c; .1—10c; .25—23c; .5—35c; **ELECTROLYTICS**: 8ufd 20V—20c; 16mfd 15V—20c; 30mfd 15V—25c; 20/20mfd 150V—35c; 30/20 150V—46c; 50mfd 150V—43c; 8mfd 475V—34c; 16mfd 350V—65c; **OIL CONDENSERS**: 4mfd 600V—49c; 2mfd. 600V—29c; 3X 1mfd. 600V—29c.

SPEAKERS—These PM speakers are the finest that are available. All have heavy oversize Alnico V magnets.
 3 1/2"\$1.15 6 for \$ 6.60
 4"\$1.15 6 for \$ 6.60
 4 1/2"\$1.15 6 for \$ 6.60
 5"\$1.50 6 for \$ 7.70
 6" (Car Radio Size).....\$4.50 6 for \$21.50
 8" 10 oz.\$3.95 6 for \$20.50
 8" 21 oz.\$4.95 6 for \$26.50
 10" 21 oz.\$5.50 6 for \$30.00
 12" 21 oz.\$7.95 6 for \$42.00


CLOSING OUT

THE FOLLOWING DESIRABLE ITEMS AT SACRIFICE PRICES TO MAKE ROOM IN OUR WAREHOUSE FOR INCOMING STOCK

5" "SO" RADAR P.P.I. SCOPE, complete with 9 tubes including 807 tube in final power stage that provides deflecting current for magnetic yokes. Selsyn motor and self-contained 110 V. power supply designed to run on the AC supply on LST and PT boats. Various ranges from 2 to 80 miles. The most satisfactory scope available for navigational radar or panoramic television applications. **Nationally advertised as surplus at \$100.00 by others. Our price, only \$39.95.**
LORAN INDICATOR OSCILLOSCOPE complete with 26 tubes and a 5" cathode ray tube. Greatly superior to other scopes because the multivibrator circuit incorporated can be used to present two traces simultaneously on screen. Thus input and output of an amplifier stage can be viewed at same time on screen. Distortion is indicated conclusively by difference between input and output traces, while fidelity is made evident by identical traces. Government instruction manual included.....\$39.95

TERRIFIC VALUE—PORTABLE ELECTRIC DRILL
 (Sold at less than established factory price so we cannot mention brand name)
 Only \$19.95 equipped with 3/4" Jacobs Geared Chuck and Key. Not an intermittent duty drill, but a full size rugged tool. Most convenient type switch, natural grip handle, and balance like a six shooter.
 Precision cut gears—turbine type cooling blower—extra long brushes: No stalling under heaviest pressure because of powerful 110 Volt AC-DC motor and multiple ball bearing thrust.
 Other bearings self-aligning lifetime-lubricated Oilite type. Made for toughest year-in and year-out service in plant or on construction jobs.
 Amazing perpetual factory guarantee assures you of a lifetime of trouble-free use.
 25% deposit on C.O.D.'s. Full refund (you pay transportation) if not pleased with drill after trial.

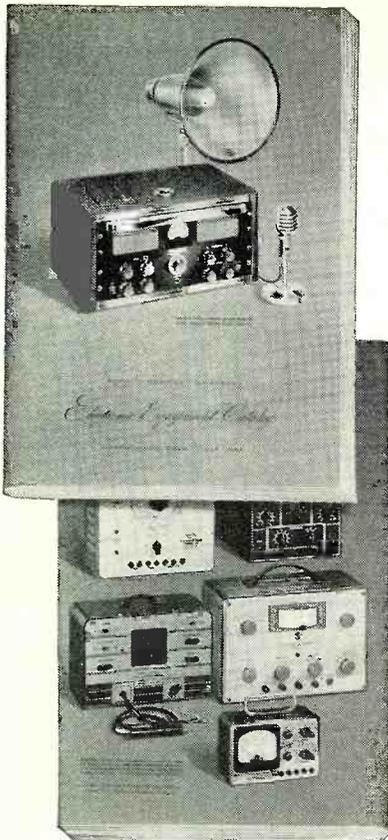BUFFALO RADIO SUPPLY, 219-221 Genesee St., Dept. 5N, BUFFALO 3, N. Y. CABLE ADDRESS BUFRAD



Radio Servicemen

FREE CATALOG

Wards 1948

Electronic Equipment
Catalog

Contains nationally-known set testers, analyzers, tube testers, oscilloscopes, signal generators, volt-ohm milliammeters, etc., all available on Wards Convenient Monthly Payment Plan. This new issue of the Electronic Equipment Catalog also features Amateur transmitting and receiving equipment plus a complete line of Wards Airline Sound Systems. Use Coupon below.

Mail this coupon to May 48
MONTGOMERY WARD, Chicago, Ill.
Please send your free 1948 Edition of Wards
Electronic Equipment Catalog.

Name _____
(Please PRINT Plainly)

Address _____

City _____ State _____

CAMERA CLUB Meets by Radio

By URBAN M. ALLEN

"The meeting will come to order" and a four-station ham net in the territory of Hawaii snaps into action.

DELEGATES from the four largest islands in the Hawaiian group had just wound up the convention at which the Camera Club Council of Hawaii had been organized, officers and directors from the four islands had been elected, when the problem of how to hold directors' meetings was raised.

The minimum air transportation cost to get the directors together for a meeting was more than \$150.00 in addition to hotel accommodations, etc. This sum was more than the infant council's treasury could stand and more than the directors individually felt they could expend on their photographic hobby in addition to their budgets for film, paper, and gadgets.

It was suggested that directors' meetings be held by mail, but this suggestion was quickly voted down as being too time consuming. Secretary Alvin O. de Long then suggested that radio might be used to conduct the meetings. A commercial radiophone conference was found to be feasible but the cost was almost as high as that of getting the directors together in person.

Jack C. Wada, council treasurer and a ham, offered his station if the directors on the other islands could line up stations to complete the network.

Secretary de Long, a radio expert with the CAA in Honolulu thought he would


have no trouble in lining up a station in Honolulu and the senior directors on Maui and Hawaii, A. K. Jim and Millard Mundy, respectively, thought they could do the same on their islands.

It required only a little correspondence in the intervening six weeks to set up the circuit as follows: With Treasurer Wada's KH6LG for the Kauai or northernmost link, the chain was completed with KH6DA, owned by Lt. Comdr. H. E. Warren, 3992 Lurline Drive, Honolulu, a retired navy officer now connected with a Honolulu electrical firm; KH6FF, owned by David Kiyo Enomoto of Kahului, Maui; and KH6EJ, owned by William Seymour of Hilo, Hawaii, a veteran radioman who has set up most of the police radio stations in the territory.

Slightly more than a month after the initial conference the four radio stations were ready for a "dry run" to test equipment and see if the idea could be carried out. This test was a success and eight nights later, the directors and officers assembled in the four radio shacks for what is believed to have been the first over-water directors' meeting ever conducted by amateur radio.

In Jack Wada's shack on Kauai were Wada, and directors Pat Shannon and Kiyoshi Sasaki. In Comdr. Warren's station in Honolulu were Council Pres-

Key station of the four-island network is that of Lt. Comdr. H. E. Warren (ret.), KH6DA, in Honolulu. At left is Alvin O. de Long, council secretary and originator of the idea for the hookup. Standing in the rear is A. H. Tarleton, grand old man of photography in Hawaii and "chief kibitzer" of the council. Seated in the foreground is Urban M. Allen, council president, and behind him is Comdr. Warren.

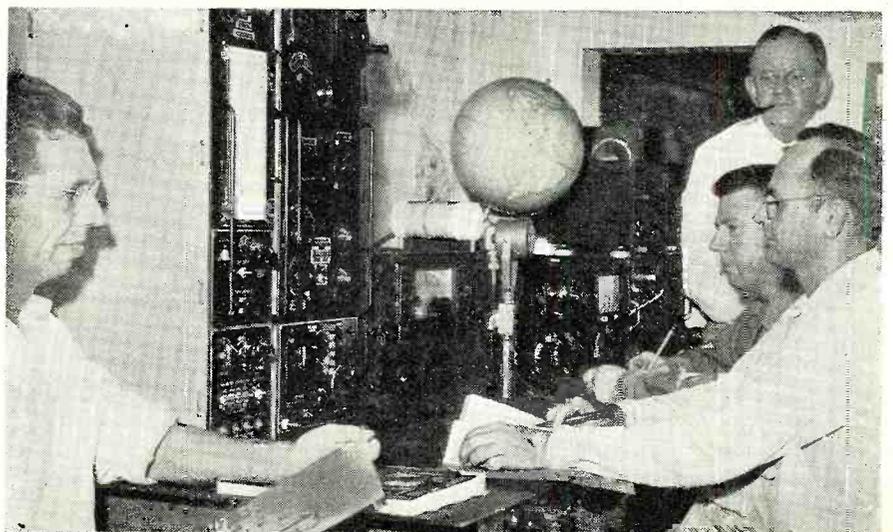


War Surplus Bargains Sold As Used Unless Otherwise Specified!

NAVY CRV-46151 AIRCRAFT RADIO RECEIVER

INCLUDING CASE


\$19.50

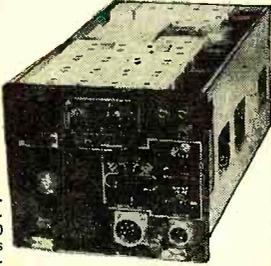

Four bands, including broadcast (195-9,050 KC). Circuit is six-tube super-heterodyne with mechanical band change or remote operated electrical band change. Remote band change and tuning controls included, making this set readily adaptable to mobile ham use. Powered from self-contained 24 V. DC dynamotor.

The sets are complete with tubes, mounting rack and remote controls.

(HRU) DC POWER SUPPLY

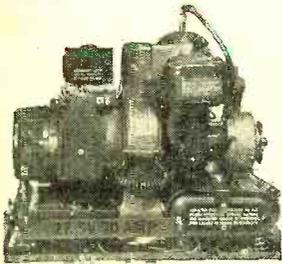

24-28 V. at 70 amp. 2000 watts gasoline engine generator with electric starter. Power supply which can be used to operate 24-28 V. equipment, start airplane engines,

charge batteries, as a welding machine, lighting system, or for amateur radio station. 21 1/2", 17 1/2" x 24 3/4". Wgt., 115 lbs.

Includes 20' plug-in cable.

\$72.50

NEW WILLARD RECHARGEABLE STORAGE BATTERIES



New 6 Volt battery in spill-proof clear plastic case, housed in metal case for easy mounting. Applicable for a wide range of uses where battery power is needed. Shipped dry. Uses standard battery electrolyte available everywhere.

Price, each\$4.00
In lots of ten, each.....\$3.35
Without metal case.....\$3.00
In lots of ten, each.....\$2.95



OXYGEN TANKS

These oxygen tanks, removed from surplus aircraft, have a capacity of 500 lbs. pressure. Type D2, with complete regulator assembly. Size of tank 22"x5".

\$5.95

TERMS: CASH WITH ORDER

AMERICAN SURPLUS PRODUCTS CO.

537 N. CAPITOL AVE.
INDIANAPOLIS, IND.



BRAND NEW SCR-625 MINE DETECTORS

ATTENTION, PROSPECTORS, MINERS, OIL COMPANIES, PLUMBERS, ETC.

Used by the Army to detect buried metallic mines. Its private use suggests the location of underground or underwater pipes, cables and ore-bearing rock, the location of metallic fragments in scrap materials, logs, etc., and the screening of personnel in plants for carrying of metallic objects. New, complete in original overseas packing container. Originally sold by War Assets for \$166.00. The U. S. Forestry Service has recommended procedure for using the SCR-625 Mine Detector to find concealed metal in tree logs and other timber products.

\$79.50

SCR-274N COMMAND SET

SCR-274N Transmitter and Receiver Assembly consists of 13 pieces which are: 4 dynamotors, 1 modulator, 1 remote control box, 2 transmitters, 3 receivers and one antenna relay unit and it has its own individual dynamotor. Each receiver employs 12 V. tubes. Each transmitter contains four 12 V. tubes and has a variable frequency and crystal calibrated master oscillator, driving two 1625 final amplifier tubes. 55-watt output, with built-in silver plated variable inductance antenna matching device. Oscillator and final stage have simultaneous tuning and the dial is directly calibrated in MC. Transmitters have slugged and capacity tuning, built-in high voltage and antenna switches. Modulator furnishes plate supply for transmitters and is equipped with a dynamotor for high voltage. Also supplied is one antenna relay with built-in antenna meter. Transmitters make ideal VFO driver unit. Easily converted to 110 V. 60 cycle operation. Wt., approximately 100 lbs. PRICE.....

\$24.75

ANTENNA RELAY UNITS


Switching Relay—Current indicator BC-442. Consists of 50 MMFD vacuum condenser,—19.5 millivolt movement, current transformer and thermo couple.

\$195

(use with any rig).

★ ★

NOTE: ALL PRICES F.O.B. INDIANAPOLIS

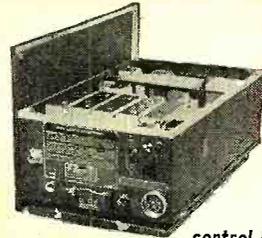


R5/ARN-7 RECEIVER

ONLY

\$19.95

control heads available

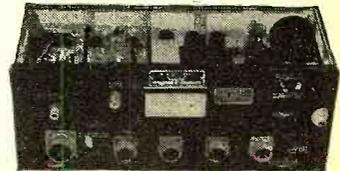Three bands 200 to 1750 KC. Complete with 17 tubes required. This set is ideal for conversion to home broadcast Receiver addition to ham shack, etc. Reported sold for many times the price when brand new. A Receiver that would be hard to pick up at this price.




RADIO ALTIMETER APN/1

A complete 460 mc. radio receiver and transmitter which can be converted for ham or commercial use. Tubes used and included: 4-12SH7, 3-12SJ7, 2-6H6 1-VR150, 2-955, 2-9004. Other components such as relays, 24 V dynamotor, transformers, pots, condensers, etc., make this a buy on which you can not go wrong. Complete as shown in aluminum case 18" x 7" x 7 1/4".

\$895


INTERPHONE AMPLIFIER RL-9

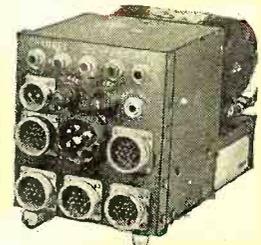Convert to high fidelity phone Amp. or speech Amp. Complete with tubes and dynamotor, for 24 V. DC operation. Used but in good condition.



\$195

SPECIAL PRICE

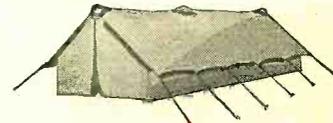

Brand New - Navy Surplus HOSPITAL TENTS


New Navy Hospital Tents—fire resistant heavy canvas, 16' wide, 30' long, 12' at apex, 4' side walls—Complete except poles. Specially priced**\$150.00**

TERMS: CASH WITH ORDER

AMERICAN SURPLUS PRODUCTS CO.


537 N. CAPITOL AVE.
INDIANAPOLIS, IND.

**YOUR GUARANTEE
OF ACOUSTIC QUALITY**

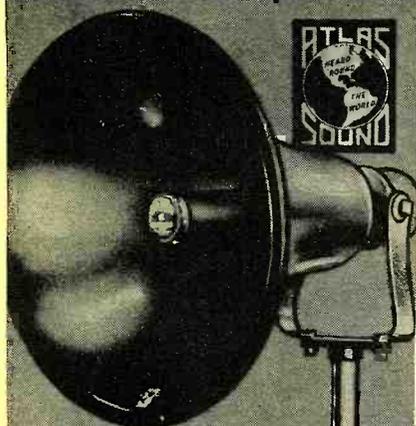

**IF IT'S GOOD
SOUND
EQUIPMENT
YOU WANT**

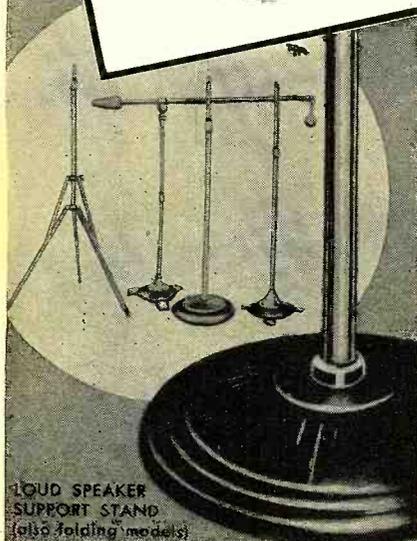... You'll welcome the new
Atlas ALNICO V PLUS super-
efficient Driver Units ... mag-
netically shielded ... hermet-
ically sealed. Specify ATLAS,
the Best!



LOUD SPEAKER
SUPPORT STAND
(also folding models)

Write for illustrated catalog

ATLAS SOUND

CORPORATION

1451—39th Street, Brooklyn 18, N. Y.

100



The Maui unit of the four-station chain is KH6FF, operated by David Enomoto (left). The Maui directors are A. K. Jim (right) and Harold Yamaguchi (center).

ident Urban M. Allen, Council Secretary de Long, and Salon Division Chairman A. H. Tarleton.

On Maui, in Kiyo Enomoto's shack were directors A. K. Jim and Harold Yamaguchi, and in Hilo, in Seymour's shack were directors Millard Mundy and Miss Mikie Kunieda.

Business was completed during the first session in 2½ hours (starting at 8:10 p.m.), requiring about 45 minutes longer than it would have taken if all the directors and officers had been in the same room but days faster than would have been possible by mail.

The plan worked so successfully that monthly directors' meetings were set up. Now, only two of the twelve directors' meetings each year will be held "in the flesh"—the rest will be by radiophone.

Among the decisions reached by the first directors' meeting were plans for holding Hawaii's first international photographic salon in conjunction with the annual meeting to be held on the island of Hawaii in July.

Information on this salon is available

from A. H. Tarleton, Black & White Division Chairman, c/o Honolulu Paper Company, Ala Moana and South Street, Honolulu.

After the first successful meeting the directors agreed that radio was hard to beat as a medium for getting things done in a hurry and recommended it to other similar clubs.

For the benefit of anyone who may want to eavesdrop on a future council meeting, the sessions are held at 7:30 p.m. (Hawaiian time) the fourth Tuesday of each month. This would be 12:30 a.m., the fourth Wednesday, EST; 11:30 p.m., the fourth Tuesday, CST; 10:30 p.m. MST, or 9:30 p.m. PST. All four stations work on the 75-meter band.

According to the council's president after the first meeting "Two of America's greatest hobbies, photography and amateur radio, have joined forces in helping each other. Who knows, perhaps our radio friends will become infected with the shutterbug from their contact with us—and some of us may add radio to our hobbies."

—30—

The southernmost station in the network is that of William Seymour (right). Hilo's KH6EJ on the island of Hawaii. The Hawaii directors, Miss Mikie Kunieda and Millard Mundy meet in his shack each month for the camera-radio confab.



RADIO NEWS

"TAB"

That's A Buy

1N23B X Diode, ea. \$1.75	10 for \$15.00
RD/APN 4 Receiver LN*	39.95
GE RIF MTR 1 or 5 Amp 2 1/2" B' Csd	ea. 1.95
BE GALVO 2.5 & 25ma 0 center/3 3/4" B' CSD	3.95
GE 2000V/1000 ohms V & RESISTOR	5.95
WEST AN 30VDC 3/2" B' Kite Cased	2.49
W.E. 0 200 or 0 500VDC/1000 ohms V/3 3/4" ea.	4.95
HICKOK 1" Illuminated MTR Tube Chkr	7.95
WESTON 4" Twin Galvo 10x10ma/.5%	12.95
DYNMTR 6Vin/out240V/100ma or 12x24Vin/500V/50ma; PM Name Vary	3.49
DYN 28Vin/out540V/250ma USED LN*	2.50
DYN 12x24Vin/275V/100ma/P MAGNET	1.95
DYNMTR 28Vin/out250V/60ma 2 for	1.98
DYN 12x24Vin/220V/100ma & 440V/200ma	5.95
DYN 24Vin/300V/260ma/150V 14.5V/5A	4.95
PE94A Same as above Plus Filters & Start	9.95
GE GLYTRAL -1276 Cement GALLON	4.95
VOLTAGE REGULATOR RAYTHEON New	10.95
55 150V/60cy Out 115V/60V	
VREGULATOR SAME 198 242Vmp/50 60cy	
Output 220V/500Watts/.5% Regtn	29.95
T17 MICROPHONE PUSH BUTTON & PLUG	.89



PRECISION RESISTORS for METERS BRIDGES, AMPLIFIERS ALL STANDARD MAKES

*1/2%	*5/5%	*10%	(Rest 1%)
2000*	4300*	5100*	12000**
245000**	250000	150000**	220000**
245000**	250000	950000	1155

ABOVE SIZES 20c. EA. ASSTD.	10 FOR \$3.95			
.116	89.8	580	2550	8500
.42	100	600	2680	9000
.5	105	612	2635	8415
1.3	101	610	2700	9710
1.75	113.1	733	2860	10,000
2	120	750	2900	10,500
3	121.2	800	3000	12,000
4	125	900	2100	14,460*
4.35	130	910	3290	15,000
5	140	1000	3384	15,000
5.025	165	1030	3730	17,000
6	170	1110	4000	17,000
7	182.1	1150	4300	18,000
7.5	200	1135	4440	19,000
7.8	209.4	1275	4444	20,000
7.9	225	1250	4500	20,520*
8	235	1250	4720	21,500
10	210	1260	4850	22,000
12	245.1	1322	4885	23,000
14.5	250	1350	4900	24,000
20	260	1500	5000	25,000
25	280	1510	5000	29,900
26	286	1600	5100	30,000
30	299	1640	5270	33,000
37	300	1650	5500	37,000
40	320	1800	5730	40,000
45	340	1830	6000	50,000
45.1	400	1865	6200	54,400*
49	418.8	1900	6300	60,000
50	426.9	2000	6500	65,000
55	440	2080	7000	68,000
56.7	452	2142	7500	73,000
60	480	2300	7700	80,000
61.4	487	2400	7500	84,000
70	500	2485	7950	90,000
75	500	2490	8000	91,000
80	520	2490	8250	95,000
81.4	540	2500	8250	95,000

ABOVE SIZES EACH 45c.	TEN FOR \$3.00			
0.1 MEG	1.6675	25 MEG	4 MEG	6 MEG
.1	1.75	.351	.402	.62
.12	1.85	.265	.422	.654
.13	1.91	.240	.458	.7
.135	2.2	.294	.478	.75
.14	2.20	.314	.5	.7613
.14	24	.33	.57	.8
.147	245	.3335	.575	.8
.15	25	.3535		

ABOVE SIZES EACH 60c.	TEN FOR \$5.00		
1 MEG	2	5	11.5
1.2	2.855	4.23	9.05
1.579	3	4.5	10
1.8	3.673		


VICTOREEN VACUUM PRECISION RESISTORS

83MEG, 1MEG, 1.5MEG, 2MEG, 3MEG, 3.75MEG, 1/2 OF 1% ACCY HIVOLTS AT \$1.00. TEN FOR	\$7.50
IRC NAVY PRECISION 1MG. 1/2 OF 1%	1.89
IRC NAVY WW 2MEG. 1/5 OF 1% HV.	4.95

CONDENSER OIL RATED WVDC CD.	
TAPPED 2x.5x.3mrd/200V	15 for \$1.50
CD 2mrd/330VAC/1000VWDC	5 for 1.98
5mrd/600VWDC/220VAC & brackets	2 for 1.95
7mrd/600V 80c. 10mrd/600V	1.49
8.3mrd/225VAC \$1.25. 4mrd/600V	1.39
20mrd/600V/\$2.50. 4mrd/330VAC/1000VDC	4.99
15mrd/330VAC/1000V/\$3. 2mrd/2000V	2.25
3mrd/2000/\$3. 4mrd/3000V	5.00
2mrd/5000V \$10. 4mrd/500V	15.00
1mrd/1000V \$25. 1mrd/2500V	4.95
2mrd/440V 12 for \$1; 3mrd/440V/10.	1.00
1mrd/440V 12 for \$1; 2mrd/440V	5 for 1.00
.5mrd/550V 10 for \$1; 1mrd/500V	8 for 1.00
.05mrd/660V 30 for \$1; 2x.05mrd/600V	25 for 1.00
3x.05mrd/600V 15 for \$1; 3x.25mrd/600V	12 for 1.00
1mrd/600V 10 for \$1; 2x.1mrd/600V	8 for 1.00
3x.1mrd/600V 8 for \$1; 2x.25mrd/600V	6 for 1.00
3x.25mrd/600V 5 for \$1; .5mrd/600V	8 for 1.00
2x.5mrd/600V 6 for \$1; 1.22mrd/600	8 for 1.00
1mrd/1000V 4 for \$1; .25mrd/100V	4 for 1.20
.2mrd/5000V \$2.25; 1mrd/3000V	3.25

BLOWER AIR 100CMF/115V AC	7.95
BC Metal Navy 5 1/2 Hx10 Lx9 3/4 W/WHDS	1.45
Universal Tube to Voice Coil TRANSF	.98
GIBSON GIRL XMITTER ONLY NEW	\$10.95
GIBSON GIRL SCR5875, COMPLETE	19.95
BC1073 WEMTR 150-210 mc's LN*	10.95
BC290 XMITTER 4.5 to 7.7 mc's LN*	5.95
COMPASS RCVR BC433/MN26 LN*	21.95
NEW Compass Revr LESS TUBES LN*	14.95
AP513/RCVR & XMITTER less tubes LN*	6.95
ARN 5/BC733 RCVR less tubes LN*	9.95
APN 1 ALTIMETER less tubes LN*	12.95
BC457/458 Like New	ea. 5.95
BC456 MODULATOR less tubes LN*	1.69
BC212/BANK Intercom & tubes & DYA	3.95
BC191/BC375 one TU & Tubes LN*	ea. 9.95
USN Flashlight perspective projector & ENLARGER 16 C 166 TM	5.95
FM TUNER & TEN TUBES Higain & pwr Supply 115V/60 Cy - Sens 5 microV	69.95
TBY VIBRPACK & S'BATTERY	9.95
BOX KITE NYLON	2.49
BALLOON 4 ft. & Hydrogen gas Generator	4.50
GIBSON GIRL HAVERSACK waterproof	.98
STROBO FLASH AN/ #1503/TWO LAMPS	
Impt 12 V. Complete power supply. Cables & buttons	2 KRYPTON Hi-Intensity lamps
12,000,000 lumens	98.50
STROBO FLASH #1503 CONVERTED TO 115VAC & 3 KRYPTON lamps mtd in Reflector & check bulbs	198.50
STROBOFLASH KRYPTON Lamps & Igntr	
Transit, 12,000,000 LUMENS/15 to 30,000 flashes sealed new	2 for 21.00
CONDNSRS STROBOFLASH GE 8mfd & 660 VAC/2000VWDC/32mfd/4 units pyranol	11.50
MILLEN 150mrd/3000V Variable Cond	1.90
Cond Var Split Stator 90 mmf per Sec.	1.98
BELL 115VAC HIGZGER CALOT	1.49
COIL CW-8 5-10mc's	2.70
WILCOX RCVR CW3 & COILS NEW	16.95
AUTOSYN AXI5/24-28V/60x400cy	3.95
AUTOSYN Type 5/30V/2 for 115V/60cy.	ea. 18.00
AUTOSYN Type 5/115V/60cy NEW	2 for 18.00
BENDIX GYRO SERVO NEW	2.95

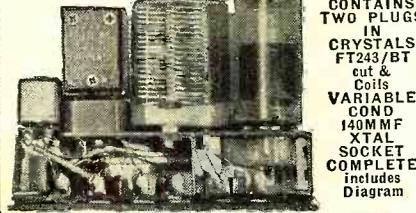Dual Crystal Tuning Unit BC746 & Handy Talkie-Coils & Crystals



CONTAINS TWO PLUGS
CRYSTALS FT243/BT cut & Coils
VARIABLE 1M 140MMF XTAL SOCKET COMPLETE Includes Diagram

DATA DESIGN MINIATURE CRYSTAL CONTROL XMITTER AS PER QST TAB	
SPECIAL 98c	5 for \$3.49
COIL 5 Prong Slugtuned 2 to 2.7mc's	10 for 1.00
GE TELV 0.4MU/SEC PULSE TRANSF	1.49
LACING COIL for 1 Pound	1.49
GE SAFETY SWITCH 69c	2 for 1.00

TRANSFORMERS 115V/60cy INPUT	
7500V or 15000V Doubles/35ma	15.95
10800 VCT or 21600V Dcrd/195ma	19.95
300V/100ma 34.50 4000V/10ma	5.95
1320V/375VCT/110ma. 5V/3A. 2.5V/3.25A & 6.3V/2.75A Cased HV insld	7.95
1350VCT/150ma. 6.3V/5A. 5V/2A Cased	6.95
640VCT & 1250V/250ma \$4.95	2 for 8.95
500VCT/60ma. 6.3V/3A HV Insld Cased	1.29
1100VCT/212ma \$5.95 110V/12KV	6.95
5V/115Amp \$9.95; Input 165V output 2x330 CT	1.25
1000VCT/40ma; 795VCT/80ma; 3x5V/3A & 6.3VCT/TA. 6.3VCT/3A 11V/Hmtchly Csd.	4.95
7.5VCT/6.5A. 6.3VCT/3A	3.75
700VCT/150ma; 10V/3.25A. 2.5V/10A & 6.3VCT/2A 5V/3A HV Insld CASED	5.00
115 or 230V/10Amp/2KW Transformer	19.95
93. 103. 112. 117 or 230 V/1.6KW	14.95
115 or 230V/8Amp/1.8KW Auto Transf.	14.95
110 or 220 or 220 or 440V/190W	4.50
2.5V/1.75A. 4V/6A/20KV Cased	5.50
TRANSFORMER ONLY for Two 866A's	3.95
872A'S COMBINATION TRANS sockets.	12.00
872A TRANSFORMER 115 60cy	6.95
866A COMBINATION TUBES, sockets, Xformer 720/20ma. 5V/3A. 6.3V/3A CASED.	2.95
220Vin/7.5V/24A HV-CASED	5.95
220Vpct. 10VCT/5A or 10Vpct/5VCT/5A	2.95
570VCT/180ma. 5V/3A. 12V/43 CSD	3.95
510VCT/125ma. 5V/2A. 6V/4A CSD	3.25
TRIPLETT TUBE CHECKER TRANSF	4.95
220 to 440V-or-110 to 220V/250 Watt	2.95
AUTO TRANSF 6V/2A. 150V/1.6A. 35V/1.2A	3.95
SEL RECT TR/115/60c. 42.5V/2A	4.25

CHOKES	
15-29HV/150ma SWINGING CASED	2.95
12HV/300ma \$3.95; 3Hy/40ma	3 for 1.00
15Hy/400ma or 20Hy/300ma/15KV Voms	7.95
3Hy/400ma; 15KV \$2.75; 8Hy/200ma	2 for 2.89
0.5Hy/400ma for 98c; 50Hy/150ma	1.95
8Hy/110ma \$1.29; 12Hy/275ma	3.29
TIME DELAY RELAY 115V/10Amp/ACDC.	1.49
DECADE SWITCH 5 POINT	2 for .98

"TAB" MONEY BACK GUARANTEE, \$5 MIN. ORDER F.O.B. N.Y.C. ADD SHIPPING CHARGES & 25% DEPOSIT.

XTAL-DIODES 1N21A, 22, 23A, 25, 26, 27	
NEW boxed lead sealed G' insp @ \$1.	12 for \$10.00
1N34 X-DIODE @ \$1.08; 2 for \$2.10.	10 for 19.85
HUBMAN CKT BKRS 3, 5, 10, 15, 20, 25, 30, 35 @	1.25
Dual 10 Am \$3.95; KLIXON 60 Amp	.69
SQUARE D 25 Amp Bkr & Toggle Switch	.89
VIBROPLEX KEY NEW Orig. Packing	5.75
E665 TELEPHONE TEST SET	19.95
THERMISTOR W/B/D/6001/70c @ 3 for	2.00
THERMISTOR BEAD WE/D/0396/79c @ 3 for	2.00
MICROSWITCH 2 for 39c	10 for 1.49
MICROSWITCH SPDT 35c @	10 for 3.00
MICROSWITCH LEAF OR ROLLER	2 for 1.39
MICROSWITCH Plunger Type	2 for 1.39
CERAMICONS .001 or .001 mrd.	12 for 1.25
CONDNSRS 2x 1/500V	2 for 1.80
15mfd/1500V @ 75c; 1mrd/2000V	2 for 1.00
.03mfd/7500V \$1.10; .05mfd/1500V	2 for 1.00
EES TELEPHONE AND RINGER	2 for 9.95
Pilot Light 1" & S6/115V bulb	2 for .98
EDISON 35 Sec delay Relay 115V/10 Amp.	1.49
GE Volt Control Relay 17V 115/60 cy.	5.95

"TAB" FOR TUBES

0A4G	\$.90/2575	\$.70 8013	\$3.95
OZ4	1.20/28K7	.88 8012	3.95
1B3/8016	2.00 35Z5	.61 8020	4.95
1E7G	.98 35L6	.74 9005	.49
1L4	.98 30L6	.72 9003	.49
1P6G	.79 80	.52 9004	.49
2C40	.73 83V	1.25 9001	.49
2D21	.49 OC3/VR105	.74 9006	.49
2X2	.49 OC3/VR150	.74 902A	2.85
2V3G	.98 211	.85 2A1P	1.95
3A4	.75 250TH	18.00 2A1A	1.95
3BT/1391	.95 250TH	18.00 3AP	3.25
3D6/1299	.95 304TH	3.95 3BP1	1.98
3S4	.90 304TH	2.49 3DP1	2.75
5R4G	1.00 307A	3.75 3FP7	2.98
5T4	1.53 393	5.95 3G1P	3.95
5W4	.69 416A	1.98 3J12	3.95
5Y3G	.69 450TH	25.00 5AP1	2.75
5Y3G	.53 450TH	29.95 5BP1	3.75
5V4G	1.00 WL531	9.95 5BP4	3.75
5Z3	.80 703A	4.95 5CP1	3.75
5Z4	1.00 717A	.89 5PT	3.95
6AB7	.98 723	2.95 5R1	3.95
6AC7	.72 732AB	4.95 1PB7/1813	3.95
6AG5	.97 725	4.95 9J1P	3.95
6AG7	.98 803	7.95 12DP7	5.95
6AJ5	.98 804	8.95 1B24	2.95
6AK5	.81 805	4.95 1B37	2.95
6B4G	1.20 807	1.98 1P24	4.95
6B6G	.98 808	1.95 2E22	


HEATHKIT SERVICE INSTRUMENTS

BUILD . . . LEARN . . . SAVE

Ideal for Schools, Training Courses,
Laboratories—Service Shops, Hobbyists.

HEATHKIT

SIGNAL GENERATOR KIT

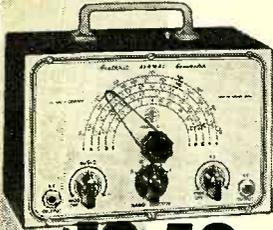


\$19.50

NOTHING ELSE
TO BUY

Every shop needs a good signal generator. The Heathkit fulfils every servicing need, fundamentals from 150 Kc. to 30 megacycles with strong harmonics over 100 megacycles covering the new television and FM bands. 110 V 60 cycle transformer operated power supply.

400 cycle audio available for 30% modulation or audio testing. Uses 6SN7 as RF oscillator and audio amplifier. Complete kit has every part necessary and detailed blueprints and instructions enable the builder to assemble it in a few hours. Large easy to read calibration. Convenient size 9" x 6" x 4 3/4". Weight 4 1/2 pounds.

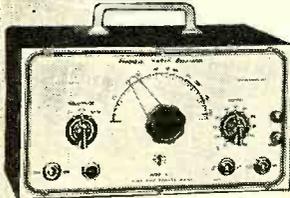HEATHKIT SINE AND SQUARE WAVE AUDIO GENERATOR KIT




\$34.50

NOTHING ELSE
TO BUY

The ideal instrument for checking audio amplifiers, television response, distortion, etc. Supplies excellent sine wave 20 cycles to 20,000 cycles and in addition supplies square wave over same range. Extremely low distortion, less than 1%, large calibrated dial, beautiful 2 color panel, 1% precision calibrating resistors, 110 V 60 cycle power transformer, 5 tubes, detailed blueprints and instructions. R.C. type circuit with excellent stability. Shipping weight 15 pounds.

HEATHKIT SIGNAL TRACER KIT

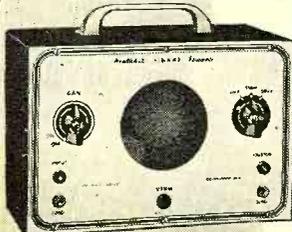


\$19.50

NOTHING ELSE
TO BUY

Reduces service time and greatly increases profits of any service shop. Uses crystal diode to follow signal from antenna to speaker. Locates faults immediately. Internal amplifier available for speaker testing and internal speaker available for amplifier testing. Connection for VTVM on panel allows visual tracing and gain measurements. Also tests phonograph pickups, microphones, PA systems, etc. Frequency range to 200 Mc. Complete ready to assemble. 110 V 60 cycle transformer operated. Supplied with 3 tubes, diode probe, 2 color panel, all other parts. Easy to assemble, detailed blueprints and instructions.

Small portable 9" x 6" x 4 3/4". Wt. 6 pounds. Ideal for taking on service calls. Complete your service shop with this instrument.

HEATHKIT HIGH FIDELITY AMPLIFIER KIT

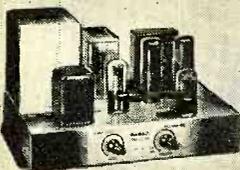


\$14.95

NOTHING ELSE
TO BUY

Build this high fidelity amplifier and save two-thirds of the cost. Push pull output using 1619 tubes (military type 6L6's), two amplifier stages using a dual triode (6SN7), and a phase inverter give this amplifier a linear reproduction equal to amplifiers selling for ten times this price. Every part supplied; punched and formed chassis, transformers (including quality output to 3-8-15 ohm voice coil), tubes, controls, and complete instructions. Add postage for 20 lbs. 12" PM speakers for above.....\$6.95

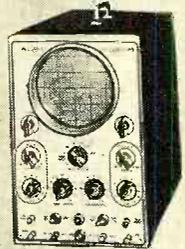NEW 1948 HEATHKIT 5 INCH OSCILLOSCOPE KIT



A necessity for the newer servicing technique in FM and television at a price you can afford. The Heathkit is complete, beautiful two color panel, all metal parts punched, formed, and plated and every part supplied. A pleasant evening's work and you have the most interesting piece of laboratory equipment available.

Check the features—large 5" 5BP1 tube, compensated vertical and horizontal amplifiers using 6SJ7's, 15 volts to 30 M cycle sweep generator using 884 gas triode, 110 V 60 cycle power transformer gives 1100 volts negative and 350 volts positive.

Convenient size 8 1/2" x 13" high 17" deep, weight only 26 pounds.


All controls on front panel with test voltage and ext. syn post. Complete with all tubes and detailed instructions. Shipping weight 35 lbs.

Order today while surplus tubes make the price possible.

\$39.50

NOTHING ELSE
TO BUY

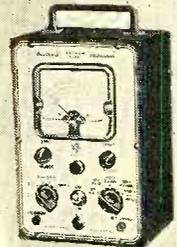The NEW HEATHKIT VACUUM TUBE VOLTMETER KIT



The most essential tool a radio man can have, now within the reach of his pocketbook. The Heathkit VTVM is equal in quality to instruments selling for \$75.00 or more. Features 500 microamp meter, transformer power supply, 1% glass enclosed divider resistors, ceramic selector switches, 11 megohms input resistance, linear AC and DC scale, electronic AC reading RMS. Circuit uses 6SN7 in balanced bridge circuit, a 6H6 as AC rectifier and 6X5 as transformer power supply rectifier. Included is means of calibrating without standards. Average assembly time less than four pleasant hours, and you have the most useful test instrument you will ever own. Ranges 0-3, 30, 100, 300, 1000 volts AC or DC. Ohmmeter has ranges of scale times 1, 100, 1000, 10M and 1 megohm, giving range .1 ohm to 1000 megohms. Complete with detailed instructions. Add postage for 8 lbs.

\$24.50

NOTHING ELSE
TO BUY

HEATHKIT CONDENSER CHECKER KIT

A condenser checker anyone can afford to own. Measures capacity and leakage from .0001 to 100 MFD on calibrated scales with test voltage up to 500 volts. No need for tables or multipliers. Reads resistance 500 ohms to 2 megohms. 110V 60 cycle transformer operated complete with rectifier and magic eye indicator tubes.

Easy quick assembly with clear detailed blueprints and instructions. Small convenient size 9" x 6" x 4 3/4". Weight 4 pounds. This is one of the handiest instruments in any service shop.



\$19.50

NOTHING ELSE
TO BUY

A WORD ABOUT HEATHKIT INSTRUMENTS

All Heathkit service instruments are supplied complete in every way—grey crackle cabinets, 2 color calibrated panels, all tubes, test leads (where required) etc. All are 110 V transformer operated. Calibrations are complete and exact, 1% precision resistors are supplied where needed.

Heath engineers are ready to assist and advise.

Heathkits are sold direct to customer, order from this ad. All are guaranteed.



The **HEATH COMPANY**

BENTON HARBOR, MICHIGAN


COMMAND SET ACCESSORIES

BEST of SURPLUS

TRANSMITTER POWER SUPPLY KIT

For BC645, 223, 522, 274N's, etc. Ideal for powering military transmitters. Supplies 500 to 600 volts at 150 to 200 MA plate, 6.3 at 3.6A, also 9V and 12V A.C. Kit supplied complete with husky cased Acme 110V 60 cycle power transformer, 5U4 rectifier, Sprague oil filled condenser, cased choke, punched chassis, and all other parts, including detailed instructions.

Complete — nothing else to buy

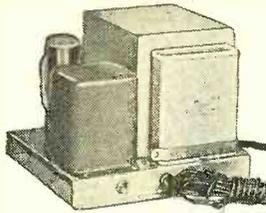

\$11.95

110V RECEIVER POWER SUPPLY KIT

With 24 volt filament, no wiring changes inside set, punched chassis and volume control

\$5.95

5" PM SPEAKER

With output transformer, matching headphone output

\$2.80

Dual receiver rack FT277A with connecting plugs

\$1.00



Single transmitter rack FT234A

\$1.00

MILITARY CONVERSION POWER TRANSFORMERS

Convert your military receivers without rewiring the filament. "A" type supplies 500 VCT at 50 MA, 5V at 2A and 24V at 1/2A. "B" type supplies 500 VCT at 50 MA, 5V at 2A and 12V at 1 amp.

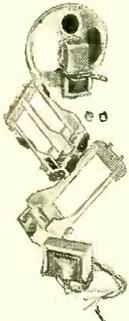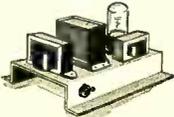
State whether A or B type desired. **\$2.95**



POWER TRANSFORMER Specials

A wonderful buy in a new production heavy duty power transformer. Primary 117V 60 cycle. Secondaries supply 746 V.CT at 220 MA, 6.3V. at 4.5 A., and 5V at 4 A. An ideal transformer for high quality amplifier modulator, small transmitter or quality radio. Will handle 13 tube radio receivers. Supply is limited, order early.

\$3.95 . . . 3 FOR \$9.95

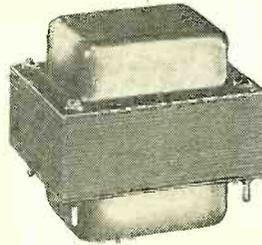

INPUT AND OUTPUT TRANSFORMER

Two units in one case carbon microphone input and output from 155 to 150 ohm load used in Handie Talkie No. 744 special 4 for **\$1.00**



OUTPUT TRANSFORMER Push pull 6V6's to 6-8 ohm voice coil excellent characteristics No. 800. 3 for **\$1.95**

OUTPUT TRANSFORMER Couples, 6C4, 6J5, etc. to 500 or 5,000 ohm line No. 716. 2 for **\$1.00**




MIDGET

AMATEUR TRANSMITTER KIT

Complete kit to assemble a 1 Watt battery operated amateur 80 meter transmitter, including tube and crystal. Range up to 500 miles. Only accessories needed are sending key and batteries. Complete instructions supplied. Add postage for 2 lbs.

ACCESSORIES

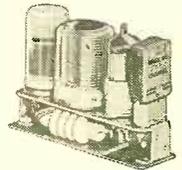Key (add postage for 2 lbs.) **\$1.00**
Kit of batteries (add postage for 4 lbs.) **3.25**



\$3.95

AN/APN1 RADIO ALTIMETERS

Brand new, complete with tubes, dynamotor, antennae, indicator, switch, plugs and instruction manual. Consists of 420 MC transmitter and receiver. Converts into excellent boat radar indicating in feet, or amateur 420 MC rig. In original crate.



\$34.95



T32 TABLE MICROPHONE

One of the Army's best. Built by Kellogg, ideal for factory call system, public address, amateur use. Brand new in original cartons, add postage for 5 lbs. **\$2.95**


DYNAMOTORS

Consists of electric motor operating generator on same shaft. Many applications—operating radios from storage battery—using as motor.

Dynamotor C—Input 28 volts, output 220 volts at 60 MA. Shipping Weight 6 pounds. **\$1.50**

Dynamotor A—Input 12 volts, output 1000 volts at 350 MA. Shipping Weight 72 pounds. **\$5.95**

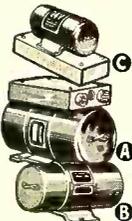Dynamotor B—Input 6 or 12 volts, output 500 volts, 160 MA. Shipping Weight 30 pounds. **\$5.95**



HEARING AID HEADPHONES

The Army's best—eliminate flat ears and outside noise. Complete with transformer for conversion from low to high impedance. With cord and plug complete. Add postage for 1 lb. **\$1.00**




HEATHKIT 3-TUBE ALL-WAVE RADIO

110-volt AC operation

An ideal way to learn radio. This kit is complete ready to assemble, with tubes and all other parts. Operates from AC. Simple, clear detailed instructions make this a good radio training course. Covers regular broadcasts and short wave bands. Plug-in coils. Regenerative circuit. Operates loud speaker. Battery model for use where no AC house current is available. Add postage for 3 lbs.


\$5.95

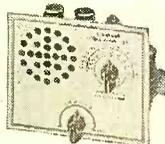

Heathkit Beginners' Radio 110-volt type **\$5.95**
Heathkit Beginners' Radio, battery type (2 tubes, no rectifiers) **\$5.95**
Headphones for either type HS 30 per set **\$1.00**
2 1/2" permanent magnet loudspeaker for either type **\$1.95**
Batteries, complete kit for battery type set **\$3.25**

INTERPHONE 2-WAY CALL SYSTEM KIT

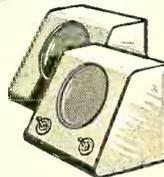Ideal call and communication system for homes, offices, factories, stores, etc. Makes excellent electronic baby watcher, easy to assemble with every part supplied including simple instructions. Distance up to 1/5 mile. Operates from 110 V.A.C. 3 tubes, one master and one remote speaker. Shipping Weight 5 pounds. **\$14.50**




SOCKET SPECIALS

Single hole mounting octal, brown, low loss, bakelite, less locking rings, **25 FOR \$1.00**
2 hole flange mounting octal bakelite 1-5/16" mounting centers. **20 FOR \$1.00**
Ceramic 2 hole flange mounting octals, 1 1/2" mounting **10 FOR \$1.00**
Ceramic acorn sockets **5 FOR \$1.00**

SOCKET KIT
20 beautiful octal, octal and miniature sockets. **20 FOR \$1**



G. E. MODEL BC-375 TUNING UNITS

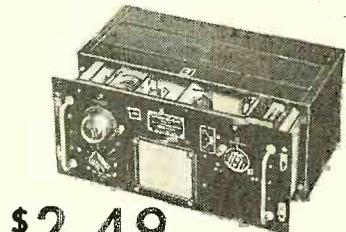


\$2.49

These General Electric 150 Watt transmitter tuning units are the greatest surplus buy. Over \$30.00 worth of new condensers, coils, switches. National Velvet vernier dial, etc. Supplied complete with cabinet and two reprints of conversion articles for transmitter and receiver reprinted from RADIO NEWS. Specify TU5B, TU10B or TU26B. Add postage for 20 lbs.




The HEATH COMPANY

BENTON HARBOR, MICHIGAN

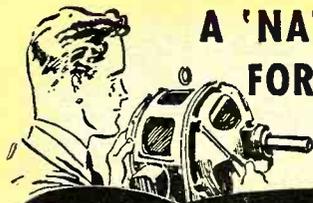

A 'NATURAL'
FOR RADIO
MEN!

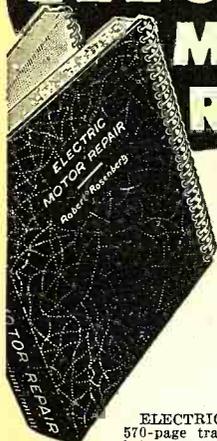Train for Good
pay in
**ELECTRIC
MOTOR
REPAIR**



The busiest,
most profitable
electrical service
of all!

ELECTRIC MOTOR REPAIR is a big, 570-page training book that can quickly help you learn this important work at home—for only \$5 for the complete course. Written especially for beginners. Tells what to do—exactly how to do it. Everything is explained simply, thoroughly and understandably. Based on what can be learned from this big book alone, you can train for prompt, profitable service on practically every electric motor in common use.

AN UNCROWDED, BIG-PAY FIELD!

The electric motor repair expert is a valuable, well-paid man. There are big opportunities for the work almost anywhere. Statistics show there are 11 electric motors in the average small American home. Big homes have many more—in oil burners, air conditioners, record players, cleaners, refrigerators, clocks, mixers, fans, washers, etc. And there are millions more in industry! Good motor repair men are scarce. Even many big appliance shops must send motors back to the factory for repair or to motor specialists! Be the man in your locality who gets this profitable business!

ELECTRIC MOTOR REPAIR book teaches you the work from the beginning. Every important step is demonstrated both in text and visually by more than 900 special illustrations. Quick reference guides show how to handle specific jobs. Widely used for training beginners and for daily reference in busy motor shops. Covers practically every modern motor type and BOTH mechanical and electrical motor control systems. Unique Duo-Spiral Binding divides book into 2 sections so that both text and related illustrations can be studied together.

**BORROW IT FOR
5 DAYS**

Send coupon now. Practice from **ELECTRIC MOTOR REPAIR** for 5 full days. See how interesting the work is—how rapidly it can be learned. Then, if not more than satisfied, return book and your money will be cheerfully refunded and no questions asked!



**ALL THIS ...
for only \$5!**

ELECTRIC MOTOR REPAIR includes complete discussions of motor parts, connections, reversing, trouble analyzing procedure, rewinding, etc. Gives full instructions on split phase motors; capacitor motors; repulsion-type; polyphase; alternating-current and direct-current types; universal, shaded-pole and fan motors; d-c generators; synchronous motors and generators, etc., as well as motor control units.

YOU CAN'T LOSE ON THIS OFFER!

Dept. RN-58, Murray Hill Books, Inc.
232 Madison Ave., New York 16, N. Y.

Rush me a copy of "ELECTRIC MOTOR REPAIR" for which I enclose \$5 (\$5.50 foreign); or send C.O.D. in U.S.A. only, for this amount and I will pay postman \$5 plus postal charge when he delivers book. If book is not what I need, I'll return it within 5 days and you guarantee to refund my \$5.

Name
Address
City & Zone State

LETTERS

from our readers

INTERFERENCE

I AM quite interested in the problem discussed by Jack Watt of Ontonagon, Michigan in the February issue of RADIO NEWS. He points out the chaotic situation at night on the broadcast band in all but the metropolitan areas of the country.

"It seems that the FCC is extremely slow in realizing that the broadcast band should be utilized to the best advantage for entertainment of the people and not primarily for the profit of the owners of the stations. Occasionally the FCC gives signs, by concrete action such as the frequency shift and clear channel assignments, that the policy of the Commission calls for best coverage for the entire country. However, since the war, with the addition of so many new stations and the power increases, the situation has grown rapidly worse. The FCC completed, about November 1, 1947, a hearing on the general broadcast band problem which it began in May, 1945.

"Out of the mass of evidence presented have come two general proposals. Oversimplified they seem to be: (1) That the FCC reduce the number of 1-A stations and allow more local stations and more power to bring reliable groundwave signals and local programs to rural areas. (2) That the U. S. be divided into five parts with four high-power, clear channel stations of at least 750 kw. each (more later). In general, these four stations covering one area should each carry different network programs to make the widest choice of entertainment available. Small stations would receive an increase in daytime power.

"To even the occasional listener, proposal (1) seems a big step in the wrong direction. Regardless of power, reception is disgusting when interfering signals are present. It is generally recognized that increasing power increases areas of interference between stations on the same frequency. As would be expected this plan is pushed by the regional broadcaster, that is, the small station group.

"The second plan seems the best so far proposed. All who remember back to the days when WLW had a half-million watts recall the excellent nighttime reception provided for most of the country. The regional group contend that this proposal will make it impossible for some states to have any fulltime

stations with more than 5 kw. of power and thus the distribution would not be equitable. Wouldn't most listeners prefer good reception from neighboring states to poor reception from their own? The networks, of course, oppose the plan because it would mean a reshuffling of the network affiliations. It seems surprising that such objections should stand in the way of a choice of programs being made available to all.

"It is believed by many qualified engineers that daytime reception can be greatly improved by increasing daytime power of many stations and by limiting many old stations and all new ones to daytime only.

William L. Brown
Instructor, Electrical Eng.
Mississippi State College
State College, Mississippi

* * *

I FEEL exactly as Reader Watt does about the mess that the FCC has allowed to come upon the rural radio listeners of America by permitting an exorbitant increase in the number of broadcast stations without seemingly making any effort to determine the amount of interference it would cause.

"I am a radio serviceman and I hear plenty of indignant remarks from customers about the cluttered up mess of stations that are on the air, especially at night. If you want to hear a prize fight or other program that doesn't happen to be on a strong, clear channel station, well you just can't hear it.

"Unless the FCC changes its course of action and rectifies its mistakes in this unlimited granting of broadcast permits, the radio manufacturing industry as well as the serviceman is going to suffer because there is a time coming soon when the buying public will refuse to spend money on broadcast receivers when they get such a small amount of satisfaction from them.

"I think it is high time that radio listeners, servicemen, and all other interested parties begin flooding the FCC with protests about the present setup and demand remedial action."

Lloyd Butler
Shoals, Indiana

* * *

I WANT to add my word of protest against indiscriminate licensing of radio stations in the United States as told by Mr. Watt in the February issue.

"May I point out one error, typographical, I presume, in his letter? The

Go to WESTERN for Values...

THE LAZIEST Q-5'er

FL-8-A. Used when flying radar range. RANGE-VOICE-BOTH switch selects 1020 pass ONLY, or voice freq. minus 1020 cps, or by-passes filter completely. Put in series with hi-impedance headset when listening to 1 kc MCW. **95c**

SCR-518-A

Radar altimeter 515 mc. Fast screen CR tube, hi-voltage power supply, connectors, cables. 29 tubes: 1-SK7, 2-8012, 2-6S17, 1-6C8C, 1-6SNTGT, 1-6F8G, 1-23D4, 1-6Y60, 1-6V8GT, 10-6AC7, 3-2X2, 1-954, 1-955, 1-956, 1-6J5, 1-1808PI cathode ray tube. **\$24.95**

Brand new

SCR-522 CONTROL UNIT

BC-602-B. Brand new, export packed. 1 "off" push-button switch, 4 channel-selecting push-button switches, 5 pilot lamp assemblies with pilot bulbs and film dimmer and lever switch with locking control. With Schematic. **98c**

80 and 40 METERS

7-tube Superhet RA-10. Bendix DF and communications receiver. 200-1100 kc and 2-10 mc. In excellent condition, inside like brand new. Complete with tubes and dynamos. Easily converted to 110V. Schematic furnished. **\$14.95**

Only

12V RADIO SET SCR-AR-183

New equipment: Transmitter and coil sets to cover 2.5-7.7 mc, transmitter tubes 2 No. 10 special and 2 No. 45 special, receiver (less the receiver coil sets), receiver tubes 1-37, 1-38, 4-39/44, shock mounts, dynamo, antenna switching relay, receiver control box, transmitter control box, charts, dials, and instruction book. **\$14.95**

What a sweet buy!

R-5/ARN-7 COMPASS RECEIVER

Very late model ADF receiver. Includes broadcast band. Frequency 100 to 1750 kc. in 4 bands. 5-stang tuning capacitor. With 15 tubes: 4-8K7, 1-6L7, 1-6J5, 2-6I8, 2-6F6, 1-6N7, 1-6SC7, 2-2051, 1-5Z4. SCHEMATIC FURNISHED. With shock-mount base. Like new. **\$19.95**

SPECIAL

BC-433-G COMPASS RECEIVER

SCR-269-G ADF receiver, similar to the R-5/ARN-7 described above and uses same tubes. Frequency 200-1750 kc in 3 bands. SCHEMATIC FURNISHED. **\$14.95**

Like new. SPECIAL

ANTENNA EQUIPMENT BUYS

AN-109-A. 62" long solid whip antenna, very flexible, made of cad. plated silicon vanadium steel. 1/4" dia. at threaded end, tapering to 0.1" at tip end. A dandy antenna, a dandy fishing rod, a dandy pipe. **\$2.69**

4 to carton, per carton

Doublet Antenna Kit, used with the famous Hallcrafters BC-610, consisting of 7 steel-alloy mast sections in a handy canvas bag. Each section is 5'6" long, 1 1/2" OD with the last 6" rolled to a smaller OD to telescope into the end of the preceding section. No taper. Assemble into mast up to 35' high or shorter by any multiple of 5'. Finished in weatherproof olive drab. Ideal for erection of FM and Television Beams! Drop your coaxial cable right through the center! Brand New, export packed. **\$14.95**

Kit of 7 and bag

COAXIAL CABLE BUYS

RG-8/U: 52 ohm coax. cable, brand new, cut to length, min. quant. 100 ft. **\$2.95**

per foot

RG-7/U: Low capacity 95 ohm coax. cable, only 12.5 mmfd./ft. Similar to RG-8/U. Brand new. Ideal for high-quality PA installations. Air and polyethylene dielectric, vinyl overall. O.D. 0.370". Loss at 1 mc is 0.15 db/C', at 30 mc is 1 db/C'. Cut to length. Minimum quantity 100 ft. **6 1/2c**

per foot

VIBRATOR EQUIPMENT

Generate 60 CPS with 3116694. Western Electric 4-pin vibrator. 12VDC input. **\$1.98**

3 for

3H6691-17 Vibrator, 6V in, for 150 V. **\$2.49**

100 MA. 7-pin, 3 for

3H6785-3. Vibrator pack. Mallory. 12V in. 225 VAC out at 50 MA. With transformer and input and output hash filters. Rotate vibrator in socket for either negative or positive grounded. **\$1.89**

negative or positive grounded

systems. 229625-33. Vibrator transformer. Pri 1.5V DC either side of CT, tapped for 122 VCT. 22 ma. Potted. 4"x2-13/16"x2-11/16". **\$1.49**

3 for

RELAYS

Starting Relay: Leach. 3-contract. 20 amp cont. duty. 2 NO. 1 double-throw at 20 amp in the energized position, about 10 amp in the deenergized position. Coil 22-30 vdc. resistance 180 ohms. Brand new. **98c**

Brand new

Telegraph and Local Relay: 2 make, 1 break. Micrometer adjustment, 2 coils, each 150 ohm. For use with 115V DC. Special: 2 for. **\$1.29**

BARGAIN OF THE MONTH 2-METER TRANSMITTER SCOOP!

The famous AN/ARC-5 VHF Transmitter (T-23/ARC-5), brand new 100-156 mc but less tubes, crystals, and the holders for the 832A tubes. Furnished with complete schematic. 4 Xtal-controlled channels selected by 3 motor-driven turrets. Motor can be spun by hand for manual band switching or driven by low-power rectifier power pack. Tubes required are 2-1625 and 2-832A. Don't pass this up at ONLY. **\$4.95**

Same as above except with crystals, tubes, and the 832A tube holders. Also brand new and with schematic. **\$12.95**

AN/ARC-4

Receiver-transmitter component. Range 140-144 mc. Xtal-controlled, 4-channel, complete with 20 tubes, 4 Xtals, and 24v dynamo. Good used. With schematic. **\$17.86**

A real buy at only

T-26/APT-2

Radar jamming transmitter, 450-710 mc. Heising amp.-mod. by noise from 931A photo-tube. Output 3 to 7 watts. All controls on front panel. 2-6AC7 and 1-6AG7 video circuit supply random noise, with pass band of 20 kc. to 4 mc. to the 807 mod. 2-368AS tubes in a push-pull 1/4-wave transmission-line osc. circuit supply the RF. Power furnished by 2-5H4GY and 1-2X2 tubes. Consumes 27vdc blower. Input 27vdc and 75-85v or 105-125v. 400 to 2600 cy. Brand new in original export case, with all tubes and handbook. Don't let this get away from you—Order today! **\$9.95**

At only

T-27/APT-3

Another noise-modulated radar jamming transmitter, companion to the APT-2, 85-135 mc. Power output 9 to 12 watts. M.O.P.A. type transmitter. Built with 4 demountable sub-chassis: R.F. Osc.; R.F. Amp.; photoelectric noise source, video amplifier and modulator; power supply. Tubes are: 1-899B RF Amp., 1-832 RF Osc., 1-931A photo-tube, 2-6AC7 video amp., 1-6AG7 mod., 1-5R4GY rectifier. Brand new, in original export case, with all tubes and handbook. **\$10.95**

and handbook

TRANSFORMER AND CHOKE SPECIALS

Output: Hammarlund Super-Pro 6F6 push-pull class AB self biasing, 10,000 ohm CT primary, two secondaries: Monitoring headset output 8000 ohms and power output 600 ohms. **\$1.89**

Output: Push-Pull 6L6's, 20 watts to 50 ohm load. Impedance ratio 15,000 to 50. Fully potted. **98c**

Output: 10 assorted uncouplers for. **1.89**

Driver: For push-pull output. Used in Bendix radio-compass receiver. Pri. 6000 ohms. Sec. 3000 ohms CT. Tertiary 15 ohms. **79c**

Filter Choke: Westinghouse, potted. 15H at 150 MA, insulated for 300 volts. **\$1.49**

183 ohms DC

PANEL METER BARGAINS

0-1 MA. DC. No. 3F8003-1. 2" round. Bakelite case. Calibrated 0-3v. At 1/3 usual net price. **\$2.03**

0-1 MA. DC. No. 3F13400. 3" round. Bakelite case. Calibrated 0-4 kv. At 1/3 usual net price. **\$2.45**

0-500 uA. DC. No. 3F8600-2. Simpson Model 125. 2" round. Bakelite case. Calibrated 0-15v and 0-600v. At 1/3 usual net price. **\$2.55**

0-500 uA. DC. No. 3F4069A/M1. Supremo foundation meter for Model 504A tube and set tester. 4 1/2"x4 1/2" wide vision, rectangular bakelite case. Multi-color calibrations for tube and capacitor checks. Ohms, volts DC and AC, and MA. At 1/2 usual net price for same size 500 uA meter. **\$5.39**

0-40 uA. DC. No. 3F4067/M1. 25,000 ohms per volt! Supremo foundation meter for Model 592 multimeter described in detail, with circuit diagrams, in the March issue of Vision. Craft. 1% accuracy. 4 1/2"x4 1/2" wide vision, rectangular bakelite case. Multi-color calibrations for ohms, AC, DC, and DB. At 1/2 usual net price for same size in 50 uA. **\$11.37**

Sensitive Output Meter, RX-1140 Control Box for SCR-625 Mine Detector contains six-tuned coils, switches, etc., in addition to a panel meter with built-in rectifier, movement sensitivity 200 uA. 2" face. **\$2.29**

0-100 uA. DC. No. 3F4067/M1. 25,000 ohms per volt! Supremo foundation meter for Model 592 multimeter described in detail, with circuit diagrams, in the March issue of Vision. Craft. 1% accuracy. 4 1/2"x4 1/2" wide vision, rectangular bakelite case. Multi-color calibrations for ohms, AC, DC, and DB. At 1/2 usual net price for same size in 50 uA. **\$11.37**

Sensitive Output Meter, RX-1140 Control Box for SCR-625 Mine Detector contains six-tuned coils, switches, etc., in addition to a panel meter with built-in rectifier, movement sensitivity 200 uA. 2" face. **\$2.29**

COMMAND SET COMPONENTS

T-20/ARC-5. Transmitter, 4-5.3 mc. **\$5.95**

Brand new, with tubes, crystal, schematic. BC-456. Modulator for SCR-274-N. Brand new, with tubes, less dynamo. **\$2.95**

With schematic

ATTENTION AMPLIFIER BUILDERS:

Range Calibrator 1-108. 115v, 60 cy. equipment, with self-contained power supply. Has power transformer and choke, three Solar 3-8-3x450 v upright can lytics, many other condensers, resistors, pots, jacks, etc. No batteries. Tubes: 6S17 pulse generator, 6F6 pulse amplifier, 6S17 overdriven amplifier, 6C5 and 6S17 frequency multipliers, 2 more 6S17 amplifiers, 5V4 rectifier. Pull-out type chassis and panel 12"x8 1/2" ideal for amplifier builders. Compartment in top of case contains test leads and cables. Outer case slightly marred in shipping, inside like new. With schematic. **\$9.95**

pasted in case

MOTOR AND WORM DRIVE

Reel RL-42-B. 1/2 HP 24VDC motor mounted to gear box, approx. 30:1 reduction, with hardened and ground steel worm, bronze worm gear, niter gears, two micro-switches, and removable reel drum. Brand new. **\$2.95**

All for only

TUBE SPECIALS OF THE MONTH All New, in Cartons

2051 Gas Tetrode Relay Tube. Use as saw-tooth generator with absolute griffon control, in synch, or as relay, or to energize relay, in triggering. Plate supply may be 115V, 60 cy. and tube will not be fired by line-voltage surges at plate. Cathode current may be as high as 375 ma peak for trigger circuits. Heater takes 6.3 V at 0.6A. A Dream Tube For Experimenters! **\$1.47**

3 for

304TL **\$1.95**

5BP1 **\$1.29** 5BP4 **1.95**

5FP7 **.95** 7BP7 **1.19**

12A6 **.5** for **1.49**

R-89/ARN-5A

Glide path receiver. Crystal control of local oscillator. 332-335 mc, complete with relays, 7-6AJ5, 1-12SR7, 2-12SN7, 1-23D7, and 3 crystals; 6497 kc, 6522 kc, 6547 kc, 90-cycle band-pass and 150-cycle band-pass filters, excellent for making an intermodulation checker. Beautiful cabinet and chassis as foundation for many interesting experimental and construction projects. Broad pass band on 29.7 mc IF's ideal for television. Schematic furnished. Used, excellent. Only. **\$6.35**

HEADSET BUY

HS-33 (Red plus), low impedance. Used. **95c**

almost like new. With rubber cushions. **65c**

4' Extension Cord for above. **65c**

DESK STAND MICROPHONE T-32

The perfect mike for hams and for PA work, factory call systems, etc. Single-button carbon transmitter with long, easy-acting press-to-talk switch, felt-padded base, and 8' cord terminating in PL-8. Transmitter is Western Electric 635A. 30 ohms at 1 MA, 2 MA maximum. Designed for clear, crisp speech. ±1db from 300 to 3000 cps with cut-off at 265 cps. HAMS: Buy at least three while you have the chance. PA MEN: Stock up on these mikes for your speech amplifier installations. ONLY. **\$2.79**

LINESMAN'S HANDSET

An ultra-sturdy handset, receiver and mike, with press-to-talk switch and 5 1/2' cord terminating in two wire-tapping clips. Clips have wire-piercing point and alligator jaws with powerful spring on one end, and 3/16" diameter plug on other end. Handset is designed to be banged around in a tool chest. Construction is almost entirely steel. Here is a lifetime telephone unit at a once-in-a-lifetime price. New. **\$4.95**

EE-8 TELEPHONES

Portable field telephone in case with hand-crank rining generator. With schematic. Highest quality at less than toy price. All you need to put it in operation is 2 flashlight batteries for each unit and 2-conductor wire to the other unit or units. Fair used, each. **\$4.95**

Good used, each. **5.95**

ATTENTION BROADCAST ENGINEERS

Aerovac capacitor type 15020, .25 MFD, 15,000 VDC. A last-chance steal at. **\$4.95**

DYNAMOTOR AND INVERTER

DYNAMOTOR UNIT PE-101-G: Made for the BC-645, useful for any other mobile job. Choose 12 or 24 vdc in. get outputs of 800 v at 20 ma plus 400 v at 135 ma plus 9v at 1.1 amp. **\$2.75**

Brand new, Special at only. **\$3.95**

PE-206 Inverter Unit: Rotary converter. **\$3.95**

28v in. Sov at 500 VA. 800 cy. out. **\$3.95**

MINIMUM ORDER \$2.00 . . . SEND FOR FREE CATALOG


WESTERN RADIO CO., Inc. • 3633 South Racine Avenue
Chicago 9, Illinois

ONE OF A SERIES

GAUGED ALIGNMENT



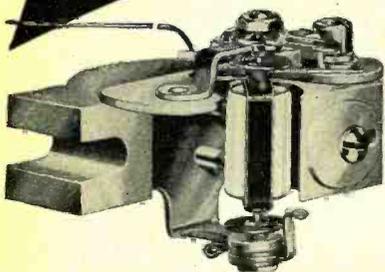
WHY BURLINGTON PANEL INSTRUMENTS PROVIDE UTMOST RELIABILITY . . .



JEWEL SUPPORTS are machined and assembled with aid of precision gauging fixtures to assure perfect alignment. All ranges AC and DC available in 2½", 3½", 4½" rectangular or round case styles and are fully guaranteed for one year against defects in workmanship or material. Refer inquiries to Dept. K58.

Burlington INSTRUMENT COMPANY
BURLINGTON, IOWA

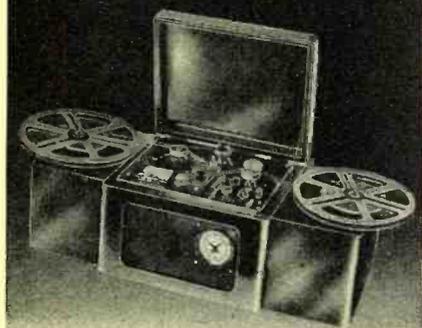Now Available! **8 HOURS OF CONTINUOUS PLAY WITH THE MAGNETAPE* RECORDER!**



Now — record and play back on this amazing instrument any sound that can be heard, and many that cannot — from a concert hall symphony to the beat of your heart. Simple interchangeable capstans provide a choice of three tape speeds for high fidelity, medium fidelity, or up to 8 hour voice recording. The ideal recorder and playback unit for home, office, industry, and broadcast station.

Other standard and portable models of shorter playing duration also available. Write today for our free illustrated catalog featuring our complete series of Magnetape Recorders and accessory equipment.

Send 25c. in stamps or coin for A.C. Shaney's new booklet, "Elements of Magnetic Tape Recording — and 999 Applications." Trademark

AMPLIFIER CORP. of AMERICA

398-2 Broadway, New York 13, N. Y.

HELP MAN THE KILOCYCLES

The Armed Forces recognizes the tremendous contribution of radio amateurs and communication personnel of all classes in war and peace. Those of you who have served actively, in the Army, Navy or Air Force or who intend to in an emergency or are otherwise interested, should retain contact with military communications, which will continue to pioneer in radio and electronics. Keep abreast of developments and read about past accomplishments in this field through the columns of the illustrated magazine "SIGNALS" which is free to all Association members. Join our association, supported by both industry and the military, the chief purpose of which in to ensure, through preparedness, that America will remain strong. Fill in this form and mail with \$4.00 or write for full details to:

ARMED FORCES COMMUNICATIONS ASSOCIATION
(Formerly Army Signal Assn.)

President, David Sarnoff

1624 I St. N.W. Washington 6, D.C.

NAME: _____
Last First Middle Initial Grade
Army — Navy — Air Force

ADDRESS: _____
Street City State

count of US radio stations has now reached the staggering total of 1824 stations between 500 and 1600 kc., not 800 as the printed letter states. Couple this total with the superpowered Mexican illegal border stations (being run by people who can't get licensed in the United States) and the many Cuban transmitters and you really have an astonishing figure.

"Within the past few years, even great stations like WBBM, WCBS, and W2XR have lost their clear channel daytime status due to the friendly feeling the FCC seems to have for any local merchant with enough money to erect a transmitter and purchase a few hundred cheap records. The remaining clear channel stations, like WLW in Mr. Watt's letter, must surely have a powerful lobby somewhere.

This situation is becoming intolerable. Instead of more radio (AM) service, the FCC is defeating its own ends. Let there be a stop to this feverish licensing and the transfer of all these local potboilers with their Sinatra records to one section of the dial where they can annoy no one except themselves."

John D. Sadler
Springfield, Ohio

* * *

JACK Watt expressed my sentiments in the February issue of RADIO NEWS exactly.

"May I add this. Today, a cold overcast Sunday afternoon, no static, and low noise level I checked on a 19 tube Silver receiver each channel of the broadcast band, starting about 4:30 p.m. and found the following:

"Channels hopelessly garbled—41.

"Channels with strong signal clear enough for voice reception, that is, the farmer could get the weather report, but no good for continued listening to any type of program because of background speech or music on carrier beats—43.

"Clear, noise free channels held that way by strong local stations (except late at night)—3.

"Clear, noise free channels held by distant stations where reception was good except for fading—2.

"Channels with signal below noise level or no signal—3.

"One channel featured a 1000 cycle test note and one or two had weak signals, etc."

Byron E. Dickensheets
Milton, West Virginia

* * *

That the problem of interference is not a local matter has been clearly indicated by the letters which have been received from all parts of the country. Thanks to all of the readers who took the time to write their experiences and suggested solutions. Space doesn't permit us to print all of the comments we received.

To keep Ahead of the Game-

FM! TELEVISION!

Keep up with PHOTOFACT Folders— The Key to Profitable, Progressive Servicing!

Build the service data library that keeps you out ahead, abreast of all the newest radio developments. Have at your finger-tips the most accurate, uniform and practical servicing data—everything you need for easier, more profitable work. From the moment you get them, PHOTOFACT Folder Sets increase in value. They pile up increasing profits for you month after month, year after year. You can't afford to miss a single PHOTOFACT Set! Buy every issue regularly—it's the easy pay-as-you-use way to build the world's most practical service data library. Published 20 times **\$1.50** per year. Price per Set, Only.


FREE

Cumulative Index to All Post-War Receivers

New Cumulative Index to all PHOTOFACT Folders now available! Send for this invaluable guide to the most practical and useful data available on all post-war radio receivers. Locates in a jiffy the Folder Sets you need for quicker, more profitable work. Ask your parts jobber today for a FREE copy, or use coupon below.




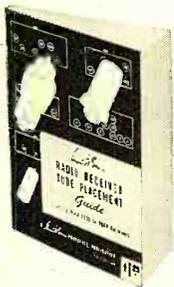THESE HOWARD W. SAMS BOOKS EARN MONEY FOR YOU EVERY SINGLE DAY



RADIO RECEIVER TUBE PLACEMENT GUIDE

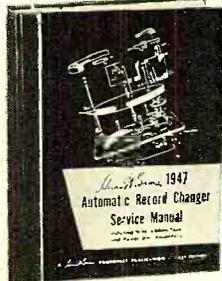The book that shows you exactly where to replace each tube in 5500 radio models. Covers receivers from 1938 to 1947. Each tube layout is illustrated by a clear, accurate diagram. Saves time—eliminates risky hit-and-miss methods. A handy pocket-sized 192-page book, indexed for quick reference. You'll use it profitably every single day! Order **TODAY! ONLY \$1.25**



1947 AUTOMATIC RECORD CHANGER MANUAL

Nothing like it! Complete, accurate data on over 40 post-war models. Exclusive exploded views, photos from every angle. Gives full change cycle data, information on adjustments, service hints and kinks, complete parts lists. PLUS complete, accurate data on leading Wire, Ribbon, Tape and Paper Disc Recorders! 400 pages; hard cover; opens flat. Don't be without this manual. **ONLY \$4.95**



DIAL CORD STRINGING GUIDE

The book that shows you the one right way to string a dial cord. Here for the first time, in one handy pocket-sized book, are all available dial cord diagrams covering over 2300 receivers, 1938 through 1946. Makes dial cord restringing quick and simple. Pays for itself in time saved on a single dial cord repair job. A "must" for every service bench and tool kit. Order your copies now. **ONLY \$1.00**

SEND FOR the FREE Cumulative Index to PHOTOFACT Folders covering all post-war receivers up to the present. You'll want this valuable reference guide.



FREE

PHOTOFACT VOLUMES PHOTOFACT Folders are available in handy DeLuxe volumes. Volume 1 covers all post-war models up to Jan. 1, 1947. Volume 2 covers models from Jan. 1, 1947 to July 1, 1947. Volume 3 covers models from July 1, 1947 to Jan. 1, 1948. Order from your parts jobber today. Your price, each Volume in DeLuxe Binder. **\$18.39**



HOWARD W. SAMS & CO., INC.
INDIANAPOLIS 7, INDIANA

Export—Ad. Auriema—89 Broad St., New York 4, N. Y.—U. S. of America
Canada—A. C. Simmonds & Sons, 301 King St., East—Toronto, Ontario

PHOTOFACT SERVICE

"The Service that pays for itself over and over again"

Mail This Order Form to HOWARD W. SAMS & CO., INC. 2924 E. Washington St., Indianapolis 7, Indiana.

My (check) (money order) for \$.....enclosed.

Send FREE PHOTOFACT Cumulative Index.

Send PHOTOFACT Sets Nos..... (\$1.50 per set)

Send PHOTOFACT Volume 3 (including Sets Nos. 21 through 30) in DeLuxe Binder.

Send Volume 2 (Sets Nos. 11 through 20).

Send Volume 1 (Sets Nos. 1 through 10), \$18.39 each.

Send.....SAMS' TUBE PLACEMENT GUIDE(S) AT \$1.25 per copy.

Send.....SAM'S 1947 AUTOMATIC RECORD CHANGER MANUAL(S) at \$4.95 each.

Send.....SAMS' DIAL CORD STRINGING GUIDE(S) at \$1.00 per copy.

Name.....

Address.....


City.....State.....

In New Jersey...
...it's **VARIETY-**

TELEVISION KITS

**TRANSVISION
STANDARD
MODEL 12" KIT**

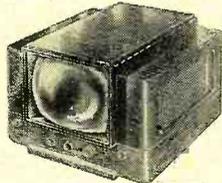Picture size 7 1/2 square inches. 22 tubes and 12 inch picture tube. High fidelity FM sound reproduction. Advanced television circuit provides exceptionally clear pictures. The Aristocrat Special (illustrated above), Model 10BL, 130 sq. in. picture.



List \$389.00*

The Magnifier Model 7BL 52 sq. in. picture-Cabinet and Lens inclusive. List \$249.00--dealers price **\$18900** net

Magnifier Cabinet, For 7" Kit with Lens...list \$ 44.95*
The Aristocrat Model 10BL, 110 sq. in. picture Cabinet and Lens, inc. list \$359.00*
The Aristocrat Cabinet with Lens suitable for 10" or 12" receiver...list \$ 99.00*
12" Standard Television Kit.....\$289.00*
12" Deluxe Television--FM Radio Kit..... 359.50*
15" Standard..... 365.00*
15" With FM Radio..... 372.95*
7" Television Kit..... 169.00*
(Complete with tubes, less cabinet)
Cabinet for 12" Television, Receiver..... 44.95*
Cabinet for 15" Television Receiver..... 59.00*
Espey Basic Television Kit, less tubes..... 69.50
Complete Line of Television Components.
*Dealers' Price on Request.


REPUBLIC TELEVISION KITS

7" kit.....\$165.00 10" kit..... 199.50
7" kit conversion to 10", includes all parts, tube, instructions..... 75.00

SPECIAL

VARELCO 300 ohm television.....\$2.70 per 100 ft. twin lead wire
NATIONAL NC-33 RECEIVER..... 20.00 per 1000 ft.
AC-DC 4 band superhet..... \$65.95
We carry a full line of National receivers and parts.
National NC183 Receiver complete with 10" speaker.....\$269.00

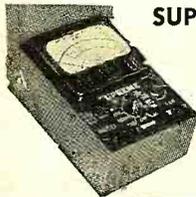**SUPREME MODEL 584
SUPER SENSITIVE
MULTI-METER**




D.C. VOLTS 25-5000,
20,000 Ohms per V. A.C.
VOLTS 100-5,000, 1000
ohms per V. Resistance
Ranges 0-20 megs. D B &
Output ranges. **\$33.77**
Net

VARIETY RADIO KITS


Pictured: 2-tube, electric kit, complete with tubes and all parts but solder and hookup wire.

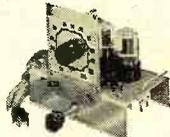RT2.....\$7.95 net
One-tube kit,
RT-1.....\$5.95 net
Three tubes and selenium rectifier kit, RT4 including speaker and tubes, complete with cabinet, less hookup wire and solder.....\$12.95
RT5--Five tube super-hot, less cabinet.....\$15.95
VA3--Five tube special super-hot kit, complete with tubes, cabinet, etc.....\$14.75
Phono Oscillator, 2 tube kit.....\$4.20
3-Tube amplifier kit.....\$6.25



NEW!

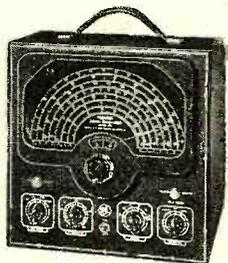**PREMIER
Model 570
MICROMASTER
Band Spread
Dial SIGNAL
GENERATOR**



For testing and aligning BROADCAST SHORTWAVE, FM and TELEVISION RECEIVERS. Exclusive Band Spread Dial geared to the tuning condenser and main dial, giving a total scale length of approximately 60 inches. Three-color dial directly calibrated in Kilocycles and Megacycles. Range: 75 KC--50MC. Up to 150MC on 3rd harmonic. Size 12 1/2"x12"x5 1/2".

COMPLETE WITH TUBES AND CO-AXIAL CABLE. **\$5475** Net

Write Dept. RNS. 20% Deposit with order required. Please add sufficient postage. Excess will be refunded.

Variety ELECTRIC CO., Inc.
601 Broad St., Newark 2, N. J.

Novel Servicing Idea Proves Profitable

By R. C. TRAVERS

There is good profit to be made from radios that travel aloft. Here's how one alert group does it.

THE Aurora Sales and Service of Aurora, Colorado (a suburb of Denver) believes that alert and enterprising radiomen can subsist nicely on the business derived from airport radio servicing.

The company has concluded agreements with a number of regional air lines (Monarch and Challenger) which operate in Utah, Colorado, and Wyoming. Under terms of the agreement hostesses or ticket clerks hand out cards to all arriving or departing travelers, suggesting that the passenger have his or her portable checked at the radio service station while shopping or doing business in Denver. Radios may be left at the airport ticket office, the patron is given a receipt, and then the set may be picked up at the close of the day--completely checked. Radios are picked up from the local airport ticket office every few hours and taken to the service shop.

Pilots, ticket sellers, and officials of all regional air lines are issued certificates entitling them to have their radio service work done at a ten per-cent discount. In addition, the company furnishes all airliners with three or four reconditioned portable radios which may be rented to passengers for their use during the flight. Rental fees on this item are split between the air line and the radio service organization.

Each airplane operated by these regional groups are provided with a conventional recorder which passengers may rent for a nominal fee. When passengers depart they can take the waxings with them. These records may range from important business communications to a record for the family. Fees for this service are split on a 50-50 basis by the air line and the service shop.

Aurora Sales and Service has inaugurated several other interesting promotions. Patrons of the radio shop living in small communities served by the air line can have their aching radios picked up at their homes and transported to the airport. From there they are flown to the Denver airport where the company picks them up, services them, and returns them via air. This service has proven popular with restaurant or nightclub operators who have a "sick" p.a. system which needs a quick repair job. The regional air lines give such radios a special air freight rate and on all repairs over \$15.00 Aurora Sales pays one-third the air freight rate. Newspaper advertisements offering this service are run in weeklies and dailies in more than sixteen communities with air line transportation facilities to Denver.

Aurora Sales is especially interested in the several aviation parks where students are taught to fly. It has an arrangement with four flying schools to check over all

radio installations daily at a special weekly rate. This check up takes only fifteen minutes per radio and a \$10.00 weekly charge covers this service on a seven day basis. (Sunday is a busy day for aviation schools.)

The company also places coin-operated radios in the waiting rooms of the regional air lines where passengers may enjoy fifteen minutes of selected radio entertainment for a dime. The patrons are offered a choice of four local stations.

This alert organization goes even farther afield to garner business. As a sideline it makes sound motion pictures of the local aviation training programs. These films are used by the aviation schools as an aid to selling their courses to likely prospects. These aviation "soundies" last fifteen minutes and show students being put through the lesson paces.

They have also entered into an agreement with airplane sales agencies whereby each purchaser of an aircraft receives a voucher good for six yearly inspections of the plane's radio installation at a fee of \$25.00 per year. Letters are sent periodically to all owners of aircraft pointing out that in order to keep their insurance in force they must have their radio equipment in A-1 working condition at all times.

Aurora's service charge for private aircraft radios is \$2.50 per service hour for the first hour and \$2.25 per hour thereafter. A 30-day guarantee is given owners of the private aircraft radio equipment.

The company has also arranged a tieup with national air lines, such as United, Continental and Braniff, to check radio equipment on the short hauls operated by those companies. This checkup takes only ten minutes daily and covers every plane landing at the Denver airport. Aurora technicians meet all main line planes flying the coast-to-coast runs, check with the radio operator who reports any specific difficulties --otherwise a routine check is made. These checkups lessen the chances of radio failures aloft. According to Aurora, air line radio servicing is both profitable and pleasurable.

Finally, the company has contracts with a number of municipalities within a 75 to 200 mile radius whereby, for a yearly stipend of \$200.00, airport beacon and tower radio systems are inspected weekly during the year. Many smaller communities are happy to include this small amount in their yearly airport maintenance budget as it minimizes chances of crashes within the vicinity of the airport.


All in all, Aurora Sales and Service is making a big thing of airborne radio, whether it flies as a part of the plane equipment or as a portable clutched in the hand of a passenger.

STAHL'S ★ Star ★ Studded ★ Specials!!

BC-645A 450MC X-Mitter-Receiver

BRAND NEW

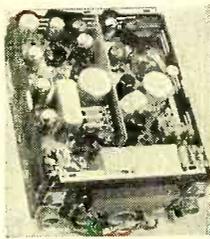Complete with Tubes includes 4-7F7, 4-7H7, 2-7E6, 2-6F6, 2-955 and 1-WE 316A door knob. Can be easily converted for Phone or CW on 420-450Mc Bands. **\$7.95 each**



6 TUBE BRAND NEW Receiver with tubes

Receivers of the SCR-274-N / (AN / ARC-5) Series. All-aluminum aircraft receivers 5" wide, 8" high, 12 1/2" long; weight 6 1/2 lbs. Typical tubeline-up is: 12SK7 RF, 12K8 Converter, two 12SK7IP's, 12SR7 Detector and BFO, 12A6 Output, gas-filled antenna-signal voltage limiter, and gas-filled output signal voltage limiter. Each set comes complete with all tubes in sockets.




Item 1: 3 to 6 Meg. less dynamotor \$5.95
Item 2: 1.5 to 3 Meg. less dynamotor \$6.95
Item 3: Dynamotor for above \$1.95

WILCOX CW 3 Complete 7 Tube Receiver with Coils \$12.95



Complete with 1 set of coils—5.1 mc. to 10 mc. & Additional set of tubes. Brand new in original cases. Export packed. Highly selective Superhet. 5,100 to 10,000 KC range. The h-f oscillator is xtal controlled. 110V. AC. 60 cycles 2-6K7; 1-6K8; 2-6C8G, 1-7SN7; 1-80. Single stage r-f amplifier single stage i-f, second detector, b.f.o., audio output and output limiter stage and a rectifier, less crystal. While they last at this low price of \$12.95

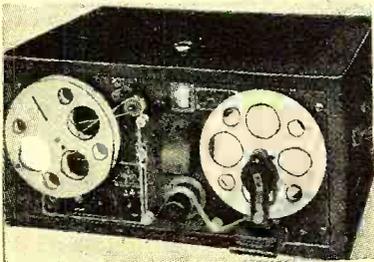

CODE KEYSER TG-10

An automatic unit for code practice signals, from an inked type recording. It's a self contained unit, complete with 7 tubes and electric eye tube; operates on 110-120 volts AC, 60 cycles. Size 11x24x18 1/2 inches. Weight approximately 63 lbs. Audio frequency output of 800 cycles per second. Power unit can be converted to P.A. system. Also a 78 RPM, 110 volt AC motor, can be used for turntable. Complete, only... **\$19.50**

METERS

2" Round Westinghouse Bakelite Case 0-30 Milliamps. D.C.	\$2.25
2" Round Triplitt Bakelite Case 0-35 Mill D.C. in Black Wrinkle Finish. Round Metal Box ..	2.25
2" Round Westinghouse Bakelite Case 0-100 Mill D.C.	2.50
2" Westinghouse 0-150V A.C. Bakelite Case ..	3.00
3" Square General Electric Bakelite Case 0-15 Mill D.C.	3.45
3" Round General Electric Bakelite Case 0-500 Mill D.C.	3.45
3" Round Beede 0-1000 Mill D.C. Bakelite Case	1.95
3" Round Western Electric 0-1000 Mill D.C. Bakelite Case	2.25
3" Round Westinghouse 0-15 Mill. D.C. Bakelite Case	3.45
3" Square G.E. Type. D. O. 500 Microamperes with odd scale, Bakelite Case	3.45
3" Round Westinghouse Bakelite Case 0-1 Mill. D.C. with bad & good colored scale can be used in tube checker	3.45
3" Square Bakelite Case Westinghouse 7.5 Volt A.C.	3.45
3" Round Western Electric Bakelite Case 100-0-100 Milliamps. D.C.	3.45
3" Round Burlington Bakelite Case 0-75 Amperes A.C.	3.45
3" Round Triplitt Bakelite Case 0-150 Volts A.C.	3.45
3" Round General Electric Bakelite Case 0-30 Mill.	3.45
3" Square Triplitt Model 327A Bakelite Case 0-200 Milliamps. D.C.	3.45
3" Triplitt Model 321 Bakelite Case 0-300 Milliamps	3.45
4 1/2" Weston Panel Board flush metal case 0-5 amp. A.C. with a 0-200 amp. scale	3.95
Weston Model 506; 1.5 Mill. D.C. Metal Case ..	2.25
Weston Model 508; 15 Mill. D.C. Metal Case ..	2.25
Weston Model 507 Metal Case 1.2 Mill. 0-100 Scale	1.95
Roller Smith portable lab 0 to 150 Mill. D.C. Bakelite Case with handle; 5 1/2 x 6 x 3 1/2	19.50
Roller Smith portable lab 0 to 15V D.C. Bakelite Case with handle; 5 1/2 x 6 x 3 1/2	19.50

CONDENSERS

G. E.	.35 Mfd.	5000V	\$1.50
Aerovox	10 "	600V	.95
G. E.	4 "	1500V	1.50
G. E.	1 "	2000V	.95
G. E.	4 "	600V	.50
C. D.	2 "	2000V	1.95
C. D.	2 "	1000V	.95
Sprague	1 "	3800V	.95


IN21 & IN23 Western Electric Crystals .35c each 3 for \$1.00

Hi-power quartz. Crystal units, type CF5, 5000 KC, complete with holder \$1.95
Jefferson step down (or step up) power circuit transformer double wound 230V input 50-60 cycle, to 115V output, 250KVA. Weight 17 lbs. \$7.95
Standard rack cabinets heavy gauge steel, gray crackle finish; panel opening 19" wide. 27" high \$12.95
Parallel No. 18 Zip wires; 10 feet lengths, with lugs on each end. Each \$1.10
Hammerlund variable APC210 micro microfarad .50

RCA-CRV-51019 Hand Sets self contained battery operated. Uses 4 pen light batteries excellent for Television Antenna installation. Sold in pairs only Pair \$15.00

Blank Calibration Books for BC 221-Frequency from 125KC to 20000KC printed in 10 divisions —68 pages, aluminum cover, spiral bound... \$1.50

Interphone Amplifier Brand New

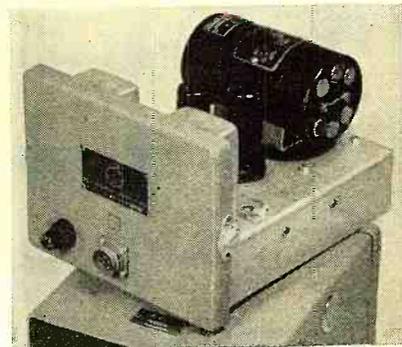


Beautifully constructed, in grey finish sturdy metal cabinet. Operates on 24 volt input, complete with dynamotor. Has 1-6V6 and 1-6S17 tube, volume control, carbon or magnetic microphone input. Fastened to sturdy resilient mounting on rubber. The case is worth the price. Only **\$3.45**

Navy Standard Battery (Brand New)



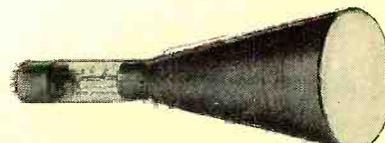Made by Gould Storage Battery Corp. 6 volt 15 amp hour. Excellent for amateurs, experimenters, radio servicemen, &c. Shipped dry, with complete instructions for charging. 4 1/4 x 6 1/4 x 6 1/4 high. Shipping weight 12 lbs. While they last **\$4.95**




5 Inch Cathode Ray Type 5 B1P tubes. In their original cartons; Brand New. At this price every scope owner should buy a few, and keep in reserve. How can you go wrong for only **\$1.95**

SCOPE Tubes—2"—2AP1 \$1.95

RAYTHEON RECTIFIER W-3155

\$49.50

Supply Current at a constant voltage and supplies current to a storage battery, providing an automatic AC-DC power system. Has no moving or expendable parts — therefore no frequent adjustment or maintenance is necessary. The life of the battery increases as much as 40%. Eliminates voltage variations. Range of unit 11/12 cells, 22 to 24 volts @ 3 amp. output. Input supply source 95 to 130 volts, 60 cycles, weight 180 lbs.

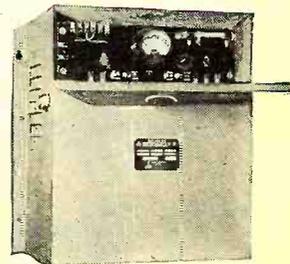

Prompt Delivery—Write Dept. RN5. 25% deposit required on C. O. D. order. Shipped F. O. B. New York.

MICHAEL STAHL, INC

39 VESEY ST. NEW YORK 7, N. Y.

TELEPHONE WORTH 4-2882

"ARROW" leads with Better Buys!

BRAND NEW!

TUBES

BRAND NEW!

304TL
Transmitting Tube \$1.95 ea.

CATHODE RAY TUBES
5CP1 5FP7 } \$1.19 each
5BP1 7BP7 }
3FP7

5BP4
Cathode Ray Tube \$1.95 ea.

39c each
 lots of 50—10% discount

RECEIVING TUBES

954	2051	12BE6	12J5	6G6
957	12AT6	864	6AT6	Amperite
9003	12SR7	RK34	6F7	10T1
9006	12C8	12A6	5R4	110AC
35W4	12K8	6SJ7	36	Neon Light

39c each
 lots of 50—10% discount

SPECIAL TUBE OFFERS

841—79c ea.	837—\$1.95 ea.	8693—\$25.00
839—\$2.95 ea.	832A—\$2.95 ea.	2C26A—49c ea.
	2132—\$20.00 ea.	

DYNAMOTORS AND INVERTERS
 BD-77, Dyn. Unit 14v in, 100v, 350 ma out, with relay fuse box and filters.....\$5.35
 DM-21 Dynamotor; Part of BC-312 and BC-314, 14v in, 235v, 100 ma out.....\$2.47
 DM-34 Dyn; 12v in, 220v, 80 ma out.....\$2.29
 DM-35 Dyn; 12v in, 625v, 225 ma out.....\$3.25
 PE-101-C Dyn. Unit; 12 or 24v in, outputs 800v, 20 ma, 400v, 135 ma, 9v, 1.1A.....\$2.75
 PE-55 Dyn. Unit; 12v or 24v in, either 16 or 25 amp, 500v out, either 200 or 400 ma.....\$3.75
 PE-206 Inverter Unit; rotary converter, 28v in, 80r at 500 VA, 800 cy. out.....3.95
 PE-103 Dynamotor, used.....\$6.95
 DM32A—each.....95c 3 for.....\$2.00



BIAS METER
 Brand New
 Originally used for measuring voltages and tele-type and telephone equipment. Can be used for measuring DC voltages and bias voltages also checking polarity of DC voltages. Complete with adaptor plug and schematic. Enclosed in metal carrying case. Requires no batteries for operation.....\$3.95 ea.

ELECTRONIC MEGAPHONE
 Brand New
 Only 40 of these to sell. Amplifier straps on shoulder, then just hold megaphone and speak in mike mounted on rear of projector. Amplifier is conventional type, shipped with tubes. Amplifier-dry battery operated less battery **ONLY.....\$29.95**



SCR-522 VHF COMMAND UNIT
 2-Way Radio; freq. range 100-156 MC.; complete with crystals, tubes, plugs, dynamotor..... used, in excellent condition..... **\$24.95**

ARC 4 TRANSMITTER and RECEIVER
 For operation VHF frequencies in range of 140-144 mc. Four channel crystal controlled, manufactured by Western Electric—24V operation. Complete with crystal and dynamotor. Used..... **\$19.95**
 Good condition.....

PE-117 UNIVERSAL POWER SUPPLY
 6 or 12 volt input; output 145 volts and 90 volts; less vibrator, voltage regulator and rectifier tube; ideal mobile power supply unit; excellent condition, each..... **\$2.95**

POWER SUPPLY FOR BC-223 PE-125 VIBRATOR TYPE
 12 or 24 volt input DC; output 475 volts-200 ma. 8 volts DC at 4.5 amps. BRAND NEW **\$8.95**
 with schematic diagram.....


RA-10 BENDIX RECEIVER
 3 band, good cond., 7 tube super heterodyne circuit, direction finder and communication receiver, freq. range 200 to 110 KC and 2 MC to 10 MC, complete with dynamotor and tubes, easily converted to operate from 110 volt **\$14.95**
 AC-DC.....

SELSYN INDICATORS
 For use with beam rotators for indication of direction of beam. Operate from 15-24V, 60 cycle AC supply. Small model, 3 inch diameter, only..... **\$2.45**
 Large model, 5 inch diameter, only..... **2.95**

GE METER
 0-10 amps., DC.....each **\$2.29**
OUTPUT TRANSFORMER
 Hi-Fi; used in Scott-made Navy receiver. Fully potted, Pri. 5000 ohms, output secondary 600 ohms CT, inverse-feedback secondary..... **\$1.49**
 60 ohms CT. ONLY.....

RADIO SET SCR-AR-283
 BRAND NEW... transmitter and coil sets to cover 2.5-7 MC., transmitter tubes 2 No. 10 special and 2 No. 45 special, receiver (less the 2 receiver coil sets), receiver tubes 1—37, 1—38, 1—39/44, shock mounts, dynamotor (24 V.), antenna switching relay, receiver control box, transmitter control box, charts, dials, a n d instruction **\$14.95**
 manual..... ONLY.....

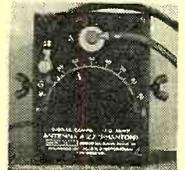PHANTOM ANTENNA
 Brand New
 Used with any 80 meter transmitter as a dummy load for adjusting transmitter for maximum output before going on air. Freq. range: 2MC to 4.5MC, with instruction manual, enclosed in metal case with cover..... **\$1.95 ea.**



SPRAGUE PULSE FORMING NETWORKS
 Used in small radar modulators, available in 3 sizes, 67 ohms impedance, 7.5 kilowatt rating.
 H-603, one micro second, 200 pulses per second..... **\$1.95**
 H-601, 3 micro seconds, 200 pulses per second..... **2.95**
 H-602, 16 micro seconds, 60 pulses per second..... **3.95**
ALL THREE ABOVE FOR ONLY... 4.95

OIL-FILLED CONDENSERS
 .25 MFD at 1500 VDC.....59c
 .25 MFD at 15,000 VDC.....\$4.95
 2 MFD 220 VAC.....29c
 .25 MFD at 6000V DC.....\$1.49
 2 MFD at 600V DC......29
 4 MFD at 220V AC......29
 5 MFD at 750V AC......29
 2 X .25 at 2000V DC......29
 3000 MFD at 3V DC......19

ARROW SALES, INC.

SOUTH SIDE BRANCH
 8310 SOUTH HALSTED ST.

MAIN OFFICE
 59 WEST HUBBARD ST., CHICAGO 10, ILL.
 Telephone SUPERior 5575

NORTH SIDE BRANCH
 1802 NORTH HUMBOLDT BLVD.

"ARROW" leads with Better Buys!

SCR-274 MEDIUM FREQUENCY COMMAND SET

Complete installation with 2 transmitters, 3 receivers, racks, tubes, crystals control box and plugs.
Excellent condition **\$24.95**

BLOWER MOTOR

24V, small portable with fan, ideal for defroster or ventilator unit, 17,000 RPM, BRAND NEW **\$1.95**

TEST CABLE

Coaxial cable used for connecting signal generator to receiver, complete with PL-55 on one end, 2 spare terminals on other end; shielded, 6 ft. long, NEW **19c**

CD-307 Phone Extension Cord PL-55 on one end and JK-26 on other end, 8 ft. long, used for extension of headsets or speaker **29c**

AUTOMATIC FREQUENCY CONTROL UNIT

Western Electric type used for controlling frequency for teletype and telephone work, complete with 3-6SJ7 and 2-6H6 tubes. Complete unit, brand new in original box **\$4.95**

BC-604 FM 35 WATT TRANSMITTER

A-1 condition, complete with tubes, 10 channel push buttons, less crystals and power supply, each **\$10.95**
Set of 80 crystals for above **\$14.95**
BC-603 Receiver for above **10.95**

BC-788 FOR 420 MC

Complete with tubes, excellent cond. Complete transmitter-receiver, 14 tubes including 3-6L6; 9-6AG5; 1-6L6; 1-5Y3. Six wide band IF stages. Has 98.356 KC crystal. Details on page 53 of "QST", Nov. 1947. ONLY. **\$10.95**

PE-151 INVERTER

12V DC input; 115V AC output; 150 watts; ideal power supply for mobile work and sound systems. BRAND NEW **\$12.95**

Wave Meters

Freq. range: 22 to 30 meg. } Each
Freq. range: 37 to 53 meg. } **\$795**
Freq. range: 155 to 230 meg. }

AC operated, complete with carrying case and magic eye for tuning indicator, vernier tuning dial.

FILTER CHOKES—All Fully Enclosed

3.7 H. @ 145 MA. DC., 125 ohms DC. Res. **59c**
4 MTG. Studs, each **59c**
100 ml 10H. **59c**

APN-1 RADIO ALTIMETER

Complete 420 MC transmitter-receiver unit, complete with all plugs, indicators.
BRAND NEW **\$34.50**

AN/PRS-1 MINE DETECTOR—BRAND NEW **\$9.50**

PE-103 DYNAMOTOR . . . used **9.95**

BC-929-A

Contains power supply 110 V. 400 cycles, has 7 tubes such as 3CP1, brand new, complete with tubes. Each \$17.95; Used, ea. **\$14.95**

R-78/APS-15

Has 45 tubes, one 5" scope tube, one 2" scope tube, has 3 meters, 4 power supply units 110V 400 cycles, complete with tubes.
Each **\$39.50**

BENDIX COMPASS RECEIVER MN-26

Remote control commercial type navigational receiver. Indicates direction of any desired transmitting station. 3 bands—frequency range: 150 Kc to 1500 Kc; has 12-6 V. type tubes. Brand new, original cost \$600.
\$24.95

Now

Accessories for Above: **\$6.95**

Loop MN-20 . . . Box **5.95**

MN-28 Control Box **1.95**

MN-52 Loop Control Unit **8.95**

Loop Transmission cable—168" long. **8.95**

T-17B HAND MIKE

BRAND NEW . . . perfect carbon hand mikes, light wt., 200 ohms, single button, press to talk switch, 5 ft. rubber cord, plug, dust cover. **89c**
ONLY

COMMAND RECEIVERS and TRANSMITTERS

(274N Series)—Complete with Tubes NEW

BC-454A; 3 to 6 MC. **\$5.95**

BC-458; 5.3 to 7 MC. **5.95**

BC-457; 4 to 5.3 MC. **5.95**

BC-456 MODULATOR.

Brand New **2.95**

RECEIVER

Low impedance, magnetic type receiver, ideal unit for pillow receiver or small microphone, NEW **39c**

AN18/APT-10

Pre-amplifier Model K-1, designed to raise output level of magnetic type microphone, complete with 2 tubes 6SL7GT and 28D7 and hand switch, brand new in original cartons.

Each **\$1.95** 3 for **\$5.00**

VHF TRANSMITTERS

T-26/APT-2 = 450 — 710 mc = **\$ 9.95**

T-27/APT-3 = 85-135 mc = **10.95**

Above transmitters are amplitude modulated radar transmitters. Complete with all tubes such as 829, 832, 931, 6AC7, 6AG7, 5R4GY. Also 110 volt 400 cps. power supply. Brand new in original cartons. Manuals included.

GO-9

Navy type low and high frequency transmitter with power supply and tubes. Operates from 200 Kc to 18,100 Kc; requires 115V. 800 cycles. **\$29.50**
Used. Complete with tubes.

RCA AVT-112A—AIRCRAFT TRANSMITTER

For radio-telephone communication; for 6, 12 or 24 volt source freq. range from 2,500 to 6,500 Kc. Small in size and wt. (wt. 6 lbs.). Complete with 6 tubes, oscillator circuit, power amplifier modulators, dual tuning indicator and amplifier, with instruction manual, less crystal. BRAND NEW in ORIGINAL CARTONS—
ONLY. Each **\$12.95**

ALTIMETER TRANSCIEVER RT-7/APN-1

Frequency 418-462 Mc FM, with 14 tubes: 3-12SJ7; 4-12SH17; 2-12EH6; 1-V1T150; 2-955; 2-9004; 27 V. Dynamotor, used in working condition **\$7.95**

RECEIVER-POWER SUPPLY UNIT

For the APN-4 indicator; complete with 16 tubes; 110 V. 400 cycles.

BRAND NEW **\$10.95**

MONTHLY SPECIALS

SMALL PORTABLE MOTORS

No. 1—Universal type, 24 volts DC shunt with two leads, 1½" diameter by 2½" long, with ¼" shaft, ¾" long. New, Ea. **\$1.49**

No. 2—Delco motor, 24 volts DC shunt type, 4 leads, 6000 R.P.M., 1½" diameter by 2½" long, ¼" shaft one inch long. NEW, Ea. **\$1.49**

No. 3—Pincor motor, 24 volts DC shunt type, 4 leads, 5000 R.P.M., 1½" diameter by 2½" long, ¼" shaft, ¾" long. NEW, Ea. **\$1.49**

Above motors are ideal for small hand-driven portable applications.
Set of 3 **\$3.95**

All shipments F.O.B. Chicago—20% Deposit Required on all orders. Minimum order accepted \$5.00.

REMOTE CONTROL BOX

BC-450—Triple receiver control box, can be modified to a FT-260 local control for command receivers, NEW **\$1.95**

SETCHELL CARLSON RADIO RECEIVER

Designed to receive A-N beam signals. 24-28 vdc 21.6 watts. Tube complement: 14H7 or 14A7, RF amplifier; 14H7 or 14J7, mixer; 14A7 or 14H7, IF amplifier; 14R7, detector and 1st audio amplifier, 28D7, output amplifier, 195 to 420 kc. 4" high x 4" wide x 6½" long—wt. 3 lbs., 4 oz.
BRAND NEW in original carton **\$5.95**

ANTENNA THERMO-COUPLE METER

BC-442; 0-10 amps, with extra relay and 50 MMFD 5000 Volt condenser . . . used with command transmitters. BRAND NEW **\$1.95**

ARB AIRCRAFT RADIO RECEIVER

The ARB is a six tube, four band, superheterodyne Aircraft Radio Receiver with built-in dynamotor, designed for the reception of MCW (tone or voice) or CW within the frequency range 195 to 420 Kc to 9.05 megacycles. Used **\$15.95**

GLIDE PATH RECEIVER R-89/ARN-5

Glide Path Receiver used in the Instrument Landing System covering the frequency range 352 to 395 mc; complete with the following tubes: 7-6AJ5, 1-12SR7, 2-12SN7, 1-28D7, and including three crystals 6497KC, 6522KC, 6457KC units **\$6.95**
are in A-1 condition for ONLY. Complete with Tubes and Crystals

BC-733 D LOCALIZER RECEIVER

Freq. 108-110 Mc; Tube complement: 10 tubes—1-12SQ7, 2-12SR7, 1-12A6, 1-AH7GT, 2-12SG7, 3-717A; **\$6.95**
NOW ONLY. Complete with Tubes and Crystals

VEEDER-ROOT METER AND CASE

Counts up to 1000. **59c**

Each

BC-732 CONTROL BOX

With 6 position, selective switch, volume control and toggle switch. each **59c**

HAND-TYPE MICROPHONE RS-38

Carbon type, with PL-68 plug, brand new. **\$1.95**
Used **1.00**

BC-645 TRANSMITTER-RECEIVER

BRAND NEW . . . 15 tubes interrogator-transmitter designed for airborne use, 435 to 500MC frequency range. With some modifications the set can be used for 2-way communication, voice or code, on the following bands: ham band: 420-450mc; fixed and mobile: 450-460mc; citizens radio band: 460-470mc; television experimental: 470-500mc; complete with all tubes, including W8 Doorknob tube. Size 10½x13½x4¼". Net **\$9.95**
wt. only 25 lbs. Your cost. Only
DYNAMOTOR FOR ABOVE Model
PE-101-C **\$2.95**

RADIO PARTS

100 Resistors ¼ to 1 watt. **95c**

100 Tubular bypass condensers, assorted. **\$4.69**

.01 to .1, all 600 Volt.

Electrolytic condensers

50-30, 150 Volt. 10 for **\$2.89**

½ Meg. Volume Controls

1" shaft with switch. 10 for. **\$3.00**

½ Meg. Volume Controls

1" shaft without switch. 10 for. **1.95**

Crystal Pick-up, **1.79**

new light wt. each

400 CYCLE AUTOSYN MOTOR

Ideal for indicating direction of antenna systems—BRAND NEW. each **\$2.95**

HEADPHONES

Signal Corps, 8000 ohms or 200 ohms, each used **79c**

ARROW SALES, INC.

MAIN OFFICE

59 WEST HUBBARD ST., CHICAGO 10, ILL.

Telephone SUPERior 5575

NORTH SIDE BRANCH

1802 NORTH HUMBOLDT BLVD.

SOUTH SIDE BRANCH

8310 SOUTH HALSTED ST.

Voltage, Current, Capacitance, and Resistance

MEASURING DEVICES

A complete technical analysis of the many basic types of test circuits used in radio servicing.

THE equipment described in this article is not limited to use in the radio servicing field, but is fundamental to the repair of all types of electronic equipment. Such instruments do, however, form the basis and the framework around which the equipment of a radio service shop is built.

The fact that these instruments are used for the measurement of fundamental quantities such as voltage, current, capacitance, and resistance offers the fortunate assurance that such meters will not become obsoleted by

development of newer types of test equipment of a more specialized nature.

These instruments can be broadly classified into two groups:

1. Single purpose instruments which are used for the measurement of only one electrical characteristic or quantity.
2. Combined instruments in which a single meter movement or electron ray indicator tube is employed for the measurement of a number of different quantities by using selector or function switches. These combined types

are known as multimeters or analyzers.

Another classification can be made from the standpoint of portability:

1. Pocket type or small instruments which can be taken on outside service calls or which may be used to check equipment in its cabinet or on the bench.


2. Panel type instruments which are normally installed in a fixed location on the service bench.

The factors which govern the purchase of test instruments involve the following considerations:

1. The total investment contemplated.
2. The accuracy, sensitivity, ruggedness required for the type of operation intended.
3. The probability of requiring the simultaneous use of more than one piece of equipment.

The relative importance and necessity of these factors will be included as a part of the discussion of the various instruments.

Fig. 1. Typical d.c. voltmeter circuit of multi-range instrument (20,000 ohms per volt). (B) Typical a.c. voltmeter. (C) Conventional d.c. milliammeter circuit of multi-range instrument. (D) Commonly-used ohmmeter circuit.

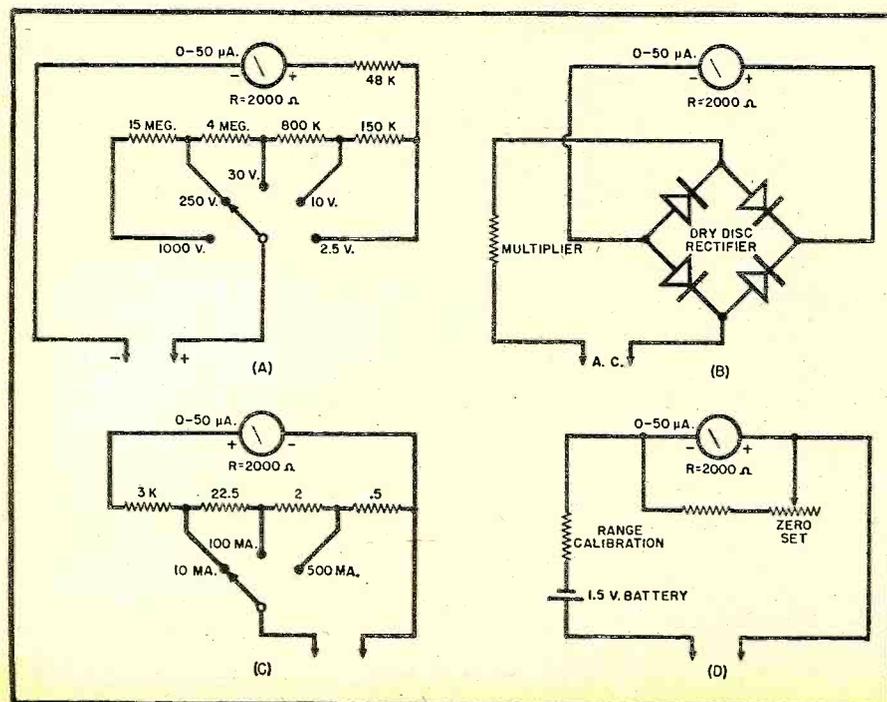

Basic Indicators

The two basic devices used as indicators in present radio service test equipment are the electron ray indicator tube and the indicating meter.

1. *Electron Ray Indicator Tube.* The electron ray indicator tube is basically a voltage sensitive device. In general two types exist; the electron ray indicator tube alone and the indicator with a built-in triode amplifier. This latter type with sharp cut-off characteristics is the one usually employed in test instruments. This type is characterized by the 6E5. It normally takes from 3 to 8 volts applied to the grid of this tube to close the shadow angle to zero. For more sensitive applications amplifiers are often used. Frequently the electron ray indicator tube is employed in bridge devices to indicate a zero or balance point. In this case, the operation of the electron ray

* Our thanks to Howard Browning for permission to reproduce this speech which was originally presented at the "Town Meeting of Radio Technicians" held at the Bellevue-Stratford Hotel in Philadelphia.

indicator is for a minimum signal and the point of measurement is determined by the maximum shadow angle. As the measurement departs from the correct point in either direction, the shadow on the target will tend to close. Electron ray indicator tubes are inexpensive, universally available for replacement, and satisfactory where extreme accuracy of measurement is not required.

2. *Indicating Pointer Type Instruments.* Indicating pointer type of instrument is the heart of any service test equipment which uses it and any equipment employing this type of indicator is only as good as its basic meter movement. There are many types of basic meter movements, the most common of which are:

1. The moving coil permanent magnet or d'Arsonval,
2. Moving coil—fixed coil or Dynamometer,
3. Moving iron vane, and
4. "Hot wire" type.

Of these the d'Arsonval movement is by far the most widely used in radio service test equipment; primarily because of its ruggedness, basic sensitivity, and the fact that its indication is directly proportional to the current through the moving coil. For the purpose of this discussion we will consider only the d'Arsonval type instrument.

Voltmeters

At the start, it should be pointed out that the d'Arsonval movement is essentially a current measuring device and in any application, no matter what the electrical quantity being measured, the meter indication will always be in terms of a direct current through this movement. D'Arsonval type meter movements are classified by their current sensitivity; and the two most popular types for radio servicing equipment require currents of 1.0 milliampere and .05 milliampere for full scale deflection. When these basic meter movements are used for reading voltages, these sensitivities can be stated in terms of "ohms-per-volt"; and meter sensitivities of 1.0 milliampere and .05 milliampere are used in "1000 ohms-per-volt" and "20,000 ohms-per-volt" instruments. A "1000 ohms-per-volt" instrument will have a total resistance of 10,000 ohms on its 10 volt scale; because according to Ohm's law a potential 10 volts across a resistance of 10,000 ohms produces a current of exactly one milliampere. If the meter uses a .05 milliampere movement the total resistance will be 20 times as much (i.e. 200,000 ohms for its 10 volt scale) or "20,000 ohms-per-volt."

It must be remembered that any multipliers only have the effect of limiting the full-scale current of the indicating instrument to its basic sensitivity. In multiple range voltmeters (See Fig. 1A) the various series multipliers are selected by means of a switching arrangement and the full scale voltage for each range is usually noted on the meter scale. For protection of the meter in the measurement

*For the Finest
Phonograph Performance Ever Achieved . . .*

Newcomb ANNOUNCES 2 GREAT NEW PHONOGRAPH AMPLIFIERS with the **MAGIC RED KNOB**

LOGICAL culmination of years of electronic research and engineering development continuously carried on in Newcomb laboratories, these new phonograph amplifiers, used in conjunction with suitable accessories, will produce unbelievable realism from recorded music or from AM-FM radio tuners connected to them. Their improved response at low volume, their beautifully clear, undistorted treble tones and the exclusive new "Magic Red Knob" control, which virtually eliminates surface noise and distortion from records in any condition, make these two amplifiers the best possible choice for those custom phonograph installations.

MODEL KXLP-30: Its ample power permits use of the famous Newcomb KX-Series dual tone control circuit, which provides tonal range and balance unattainable in less costly circuits. This circuit allows controlled emphasis of the desirable but power-consuming fundamental bass tones, avoiding emphasis of harmonic bass, so unacceptable to discriminating listeners.



MODEL HLP-14: Brings to music lovers an entirely new listening pleasure in a somewhat less expensive unit than the superb KXLP-30. Exceptional tonal balance at whisper volumes is a feature of the HLP-14. Its adaptability to use with the new AM-FM tuners, wide range loudspeakers and new phonograph pickups make it an ideal starting point for those increasingly popular custom installations.



Both include inputs for G.E. type pickups.

AUDIO PRODUCTS CO.

Dept. F, 6824 Lexington Avenue • Hollywood 38, California

Send for Specifications

TELEVISION CONDENSERS

That Can Really Take It!

.10 Mf 2500V ..\$0.74	.05 Mf 5000V ..\$0.86
.10 Mf 3500V .. 0.83	.005 Mf 7500V .. 0.62
.005 Mf 5000V .. 0.60	.001 Mf 10000V .. 0.59

Many other sizes available. Write for descriptive folder. If not available at your dealer, order direct from factory.

UNITED CONDENSER CORP.

422-J E. 138th Street New York 54, N. Y.

SHORT CUT **CODE SPEED**

Be an Expert

Learn to be a Telegraph or Radio Operator. Thousands of men need—good pay. Learn at home or wherever you are, quickly, easily, with the famous Candler Code Speed System. Qualify for Amateur or Commercial License. Book of particulars Free.

CANDLER SYSTEM CO.

Dept. 2-E, Box 928, Denver 1, Colo.



**Close-Out
Crescent
Record
Changers
\$16.95**

BUILD YOUR OWN COMBINATION

Genuine Crescent Model C-200. One of the most popular record changers in use today. Plays twelve 10-inch or ten 12-inch records automatically. Has rapid change cycle. Simple, foolproof, compact, noiseless motor. Feather weight crystal pick-up. May be connected to play through any radio. Base measures 15 1/4 x 11 1/2 inches. F.O.B. Chicago. Send 25% deposit on C.O.D. Shipped prepaid when check accompanies order. Each only \$16.95.

PEERLESS, INC.

514 So. Laramie Ave.—Chicago 44, Ill.

NESSCO ELECTRONICS Presents

TU-10B or TU-5
 Tuning unit for BC-375... a terrific parts value with a metal case Brand **New ONLY \$2.10**

REMOTE CONTROL UNIT RM-12
 Has built-in EE-8 with hand set, 3" DB meter and remote control unit. Used, very good **\$9.95**

BC-306
 Antenna loading unit for BC-375. Brand New. Another parts value **\$1.50**

SOLDER

One pound spool, highest grade compound of tin and lead, rosin core, on metal spool, Brand New. **69c**
 A REAL BUY, Ea. **69c**
 6 spools\$3.95

CORD CD-370
 A six foot head set extension cord with a PL-55 Plug on one end and a jack on the other. NEW **59c**
 EACH

BC-733D
 A 10-tube superhet receiver for lateral blind landing guidance (CAA type certificate) (TC-1045) Excellent condition: 108-110MC. Tube complement: 1-12SQ7; 2-12SR7; 1-12A6; 1-AH7GT; 2-12SG7; 3-717A—tubes alone worth more than this low Price of **\$4.95**
 EACH

WILLARD

2 Volt Storage Battery
 Brand new, spill-proof, use standard electrolyte. Suitable for all farm sets and portables. Built-in hydrometer. SPECIAL **98c**
 EACH

SHOCK MOUNTS

4 each of 3 sizes—small, medium and large. New. ALL FOR **99c**
 ONLY

R5ARN/7
 15-tube superhet radio compass receiver 100 to 1750KC; CW-tone-voice. Like New! **\$19.95**
 AT ONLY

ANTENNA RELAY UNIT

BC-442
 0-10 Weston Meter and 50MMF 5000 V. vacuum condensers change over unit, with mounting FT-229. Brand New. Ea. ONLY **\$1.95**

HEADSETS

HS-23 high impedance, Army Air Force Type, cord and plug, used, **99c**
 EACH

1625 TUBE

Army-Navy Standard
 This is a 12 V. filament 807 tube. A tremendous buy at.....Ea. **39c**
 3 for\$1.00

CD-605

A two-foot cord with a PL-55 plug; with low to high impedance xformer for your headset **39c**

PLUGS and Connectors
 Your choice for ONLY **49¢** each

20% deposit required on all C.O.D. orders

For the SCR-522.....PLQ-167
 For the BC-733.....PL-172
 For your 269-F Radio Compass.....PLQ-254
 inverter.....PL-3108-22-4S
 For the SCR-274-N.....PL-147, 148, 151,
 152, 154A, 156, 258
 For the BC-375.....PL-59—PL-61—PL-64
 Coax Fittings
PL-258—PL-259A—UG-21U—UG-22U

division of

NATIONAL EQUIPMENT & SUPPLY CO., INC.
 1500 S. Western Avenue Chicago 8, Ill. MOncroe 9504

LEARN RADIO!

IN ONLY 10 MONTHS
PREPARE FOR A GOOD JOB!
 COMMERCIAL OPERATOR (CODE)
 BROADCAST ENGINEER
 RADIO SERVICEMAN

Television Servicing—15 Months

Veterans get \$130.00 Equipment
 SEND FOR FREE LITERATURE
BALTIMORE TECHNICAL INSTITUTE
 1425 EUTAW PL., DEPT. R, BALTO. 17, MD.

TELEVISION COIL KIT

\$2350

Complete
LOOK AT THESE FEATURES!

- Video IF Bandwidth of 4.25 MC that can operate ANY size Picture tube with maximum resolution.
 - Five stages Video IF Permeability tuned with sound and adjacent channel rejection traps in shielded cans.
 - 6 Channel RF Tuner, permeability tuned mounted on switch assembly plate.
 - FM Sound Discriminator for TRUE FM.
 - Detailed Construction Manual & Parts List with every kit, for 20 Tube, 7 In. Television Set.
- Order Direct or Thru Local Dealer—Terms**
 Shipped Parcel Post prepaid with order, or P.R. Collect on receipt of 25% deposit, balance C.O.D.

RAY-LECTRON CO.

706 Tenth Avenue Belmar, N. J.

RADIO TUBES • STANDARD BRANDS • BULK

	Each		Each
80, 5Y3GT, 5Y4GT, 6C4, 9002.....	\$.42	43, 6A7, 6A8, 7B7, 25L6.....	\$.59
35W4, 25Z5, 25Z6GT, 35Z5.....	.45	OZ4, 6X5GT, 7F7, 7N7, 7Y4.....	.65
6F5GT, 6J5, 6SA7, 6SK7, 6SQ7.....	.47	1A5GT, 1A7GT, 1H5GT, 1N5GT.....	.74
36, 37, 77, 78, 6H6, 6D6.....	.49	1S4, 1R5, 1S5, 1T4, 3Q4, 3Q5, 3S4.....	.79
12AT6, 12BA6, 12BE6, 12SQ7.....	.49	14A7, 14B6, 14Q7, 35Y4, 50A5.....	.95
12SA7, 12SK7, 6F6GT, 75.....	.49	1LN5, 6AC7, 6L6G, 70L7.....	.95
6J7, 6K7, 6Q7, 6SP5, 6SN7.....	.55	1LC6, 1LH4, 1LA6, 117Z3, 117Z6.....	.95
35A5, 35L6, 50B5, 50L6, 50Y6.....	.55	25A6G, 117LGT, 117N7GT, 117P7GT.....	1.35

TELEVISION

Dipole Antenna, list price \$14.50.....\$ 7.25
 Lead-in-Wire, 300 ohms, 1000 feet on reels.....17.50
 100 Feet, 300 ohms, on reels.....1.95
 Coaxial Cable, RG59U, 72 ohms, 500 feet on reels.....32.10

ELECTROLYTICS

	Each		Each
16—150V.....	\$.24	8—450V.....	\$.27
20—150V.....	.25	10—450V.....	.32
20—20—150V.....	.26	16—450V.....	.36
30—150V.....	.28	16/16—450V.....	.59
50—150V.....	.35	20—450V.....	.39
40/40/20—150V, 25V.....	.44	30—450V.....	.47
50/30—150V.....	.44	40—450V.....	.54

CONDENSERS

	Each		Each
100—ast'd, .001 to .02.....	\$3.95		
.001—600V per Hundred.....	3.95		
.002—600V per.....	3.95		
.006—600V per.....	4.40		
.01—600V per.....	4.40		
.05—600V per.....	4.95		
.1—600V per.....	7.20		

A.C.-D.C. CHOKE.....\$.39
 SPEAKERS—4" PM, Alnico Magnet.....1.19
 OUTPUT TRANS (50L6).....\$.39
 5" PM, Alnico Magnet.....1.39
 VOLUME CONTROLS—½, 1, and 2 Meg or 50M ohm, all with switch......39
 SELENIUM RECTIFIERS.....75 ma......49
 100 ma......59
 FM CONDENSER & COIL KIT with instructions and schematic.....4.95

-BROOKS RADIO DIST. CORP. • 80 Vesey Street • Dept. B • New York 7-

of voltage, the highest available range should be used and the range selector switch progressively moved to lower voltage ranges until a satisfactory indication is obtained. For maximum accuracy, measurements should always be made as close to full-scale deflection as possible since the error of the instrument is normally least at or near full-scale deflection. Most commercial radio service multimeters now have an upper range, full-scale, of 1000 volts. The necessity for the measurement of high voltages will arise in the servicing of certain types of television receivers. External multipliers are available for most commercial instruments of the 20,000 ohms-per-volt type and although these external multipliers are provided with well insulated test leads, extreme care should be exercised in their use since these voltages may be lethal. In fact, many instrument manufacturers make the recommendation that the operator keep one hand in his pocket while making these high voltage measurements and this seems to be very worthwhile advice.

The a.c. voltages can be measured on the same d.c. meter movement (See Fig. 1B) by means of a dry disc rectifier bridge whose function is to provide a direct current for the indicating movement. The ranges of a.c. voltmeters are also extended by means of multipliers with their corresponding range switches. Usually the combination of the meter movement and the rectifier bridge results in current sensitivity which approximates 1000 ohms-per-volt when used for a.c. measurements.

Ammeters and Milliammeters

Since any pointer type indicating instrument is essentially dependent upon current for its operation, these instruments may be used as current measuring devices with the selection of proper shunts, (See Fig. 1C) which will limit the flow of current through the meter movement to that required for full-scale deflection. Current measurements are infrequently resorted to in the servicing of radio receivers and only then are direct currents measured. This is occasioned by the fact that the successful operation of a service shop usually does not allow the time required for the breaking or unsoldering of leads to permit the insertion of current measuring devices. In addition there is the hazard of meter burnout, since an unsuspected short in a receiver circuit can cause a flow of current that is many times normal.

Multiple range instruments, which include a dry disc rectifier bridge, often provide alternating current ranges as well as a.c. voltage ranges. Frequently, the alternating current ranges are of value in determining defects in power transformers by the measurement of current drawn from the power line or currents provided by the various secondary windings.

Multimeters

Since multimeters or analyzers for the measurement of d.c. and a.c. volt-

ages and currents are the most frequently used instruments in the service shop, it is wise to choose them with care and to acquire instruments having long scales which are easily read. The highest sensitivity instrument which is within the budget of the technician should be purchased, since high sensitivity with its consequent high effective resistance produces the least disturbance of voltages being measured.

In this regard, it should always be kept in mind that the pointer type or moving coil instrument requires power for its operation, and since this power must be provided by the circuit under measurement, the readings will be in error in proportion to the voltage regulation of the circuit. Electronic or vacuum tube voltmeters, which will be discussed in some detail later, draw extremely low amounts of power from the circuits under measurement and their use is indicated for certain specialized measurements in high impedance circuits, and for the measurement of radio frequency voltages.

Ohmmeters

Precise measurement of resistance is an operation which can best be performed by the bridge type laboratory instruments. However, it is possible to use the d.c. milliammeter as a basis for a reasonably accurate direct reading ohmmeter. The most popular circuit is one in which the leads of the ohmmeter are shorted together and an adjusting resistor used to set full-scale deflection of the meter. This indicates zero ohms on the meter scale, and is concurrent with the full-scale current of the indicating movement. (See Fig. 1D.) After this adjustment is made, any resistance inserted in the meter circuit by the use of the test leads causes less current to flow through the indicating meter and the scale of the meter is directly calibrated in terms of this inserted resistance. Different ranges are obtainable through the use of multiplying resistors and additional battery voltage. The above type of ohmmeter is usually used in commercial instruments with ranges of 1000 ohms to several megohms. A shunt type ohmmeter has been developed for more accurate readings of resistance in the range of zero to 1500 ohms and in this type ohmmeter the zero setting is made with the leads unshorted and the meter adjusted to full-scale deflection. Unknown resistances then applied across the test leads cause the meter current to be lessened by the parallel effect of their resistance. Incidentally, in this type of device the midscale reading in ohms will approximate the resistance of the meter and its associated shunt adjusting circuit. In most multimeters, operation of the ohmmeter circuits are provided by an internal battery. As this battery becomes exhausted its internal resistance increases and the adjusting resistance moves towards the end of its range. Under these conditions, the accuracy of reading is impaired and it is therefore wise to check the condi-


May, 1948

A New Model!

At a New Low Price!

GOODELL

Dynamic Noise Suppressor Amplifier

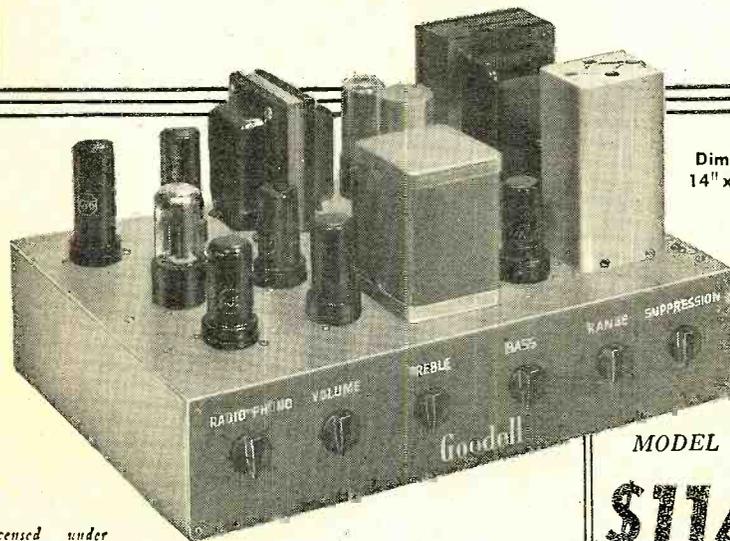

Dimensions
14" x 3" x 10"

MODEL NSA-2

\$114.50

Licensed under
Hermon Homer Scott
Pat. Pend. for use only in
phonograph and phonograph
distribution systems.

The six-tube Dynamic Noise Suppressor with separate range and suppression controls—two complete high-frequency reactance tube filter sections with one low-frequency reactance tube. Response is maintained under dynamic operating conditions to beyond 12,000 cycles per second with effective reduction of objectionable noise amounting to more than 25 decibels! Continuously variable treble and bass controls, center setting flat. Both controls boost clockwise, attenuate counter-clockwise. Power output conservatively rated at 10 watts.

This amplifier has all the facilities of the larger model and is designed with ample reserve power for most home installations. Separate inputs for radio and phono with front panel switch. Tube socket connection provides power and input facilities for magnetic pickup pre-amplifier. Tubes—1-5U4G; 3-6SG7's; 2-6SJ7's; 1-6J5; 1-6H6; 1-6SN7; 2-6L6's. Model No. NSA-2 \$114.50 net, tax and tubes included, f.o.b.

The same two-tube pre-amplifier in double shielded plug-in construction used in the larger models is available for an additional \$12.50 net, tax and tubes included. This pre-amplifier has built-in equalizer to provide proper characteristics for Pickering, General Electric and similar magnetic pickups.

MODEL NSA-1

2-Chassis construction—18 watts

Model NSA-1 includes the pre-amplifier using 2-6AT6 tubes as standard equipment. This model includes dual G.E. indicator eye tube for visual observation of gate action. Dynamic Noise Suppressor, tone control sections and pre-amplifier are built on one 15"x3"x7" 14-gauge aluminum chassis. Power supply and power amplifier on separate chassis 17"x3"x7". Two-chassis construction minimizes hum and simplifies cabinet installation. All power supply filter capacitors oil-filled, 600 volt paper types. Push pull 807 output tubes conservatively rated at 18 watts. Tubes—1-5U4G; 2-6AT6; 3-6J5; 2-6SJ7; 3-6SG7; 1-6H6; 2-807; 1-6AL7. Model No. NSA-1 \$248.00 net, tax and tubes included.

A demand for the Dynamic Noise Suppressor in an amplifier using triode output tubes has led to the development of a special two-chassis model similar to the above in every respect except for the use of a push-pull driver stage consisting of 1-6SM7 driving 4-6B4 output tubes in push-pull parallel, conservatively rated at 18 watts. Model No. NSAT-1 \$297.00 net, tax and tubes included.

Models NSA-1 and Model NSAT-1 available with 19"x8 3/4" 11-gauge aluminum panels or optional 5" panels. When the 5" panel is used, a separate mounting hole must be provided in the installation for the indicator eye tube.

These are laboratory amplifiers of the highest quality, designed and constructed to provide music reproduction fidelity limited only by the available signal and loud speaker equipment used. The amount of objectionable noise reduction will depend on the hearing characteristics of the individual, as well as the ability of associated pickup and loud speaker equipment to provide full range response. In general, objectionable noise is lowered to the extent of 25 decibels or more under dynamic operating conditions with response maintained to 12,000 cycles per second when music signal provides adequate masking. Output impedances of 500 ohms and 250 ohms for feeding long speaker lines or high powered amplifiers, as well as multiple standard voice coil impedances are provided on all models. All inputs are high impedances. Plug-in low impedance input transformer available on special order with large model. Cathode follower output stage on control chassis of dual chassis models permits separation of the two chassis up to more than 25 feet without line losses.

ALL PRICES F. O. B. ST. PAUL, MINN.


The Minnesota Electronics Corporation • St. Paul 1, Minn.

PROJECTION TELEVISION!

Convert your RCA 630 or Crosley 307 to this

OUTSTANDING TELEVISION CONVERSION OF 1948!

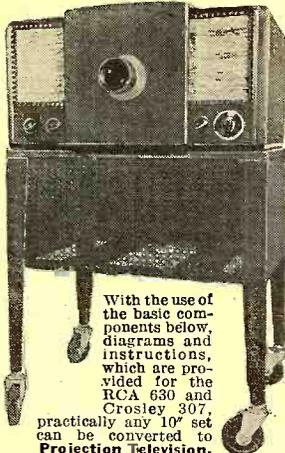The gigantic picture this set is capable of projecting must be seen to be believed! One set converted by a Los Angeles company, was demonstrated at the Shriner's Temple in Los Angeles, during the Rose Bowl game. It was viewed by 4800 people at one sitting! A 12x16-foot rear projection plastic screen of our type was used.




With the use of the basic components below, diagrams and instructions, which are provided for the RCA 630 and Crosley 307, practically any 10" set can be converted to Projection Television.

F 1.9 TELEVISION PROJECTION LENS

Dimension—
Length 7", Diameter 4 1/4".

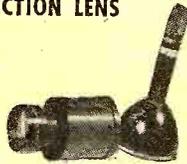
F 1.9 EF. 5 in. (127.0 mm). This lens incorporates in barrel a corrective lens for use with a 5TP4 projection tube. It is easily removable for use with flat type tubes. Lens can be utilized to project picture sizes from several inches to 7x9 feet. Made by Bausch & Lomb Optical Co. Price..... **\$125.00**
Mounting ring available for above lens... Price **\$2.50**



30 KV RF POWER SUPPLY

Dimensions—
Length 14", Width 11", Height 1 1/4".

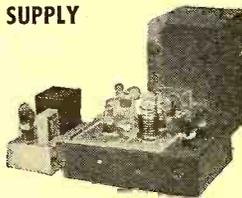This unit has a low voltage supply separate from high voltage pack. Low voltage DC supply has control which enables you to vary voltage from approximately 12 KV to 40 KV. Unit has focus control built in for use with 5TP4 projection tube. Price, complete..... **\$99.50**



STAND FOR PROJECTION TELEVISION SETS

Dimensions—23" High, 25" Wide, 18 1/2" Depth. For use with RCA 630 chassis or Crosley table model sets. Unit mounted on ball bearing soft tired wheels. Depth is designed to accommodate RF Power Supply. Open grill allows free circulation of air. This stand a natural for mounting scopes and other lab. equipment for easy mobility. Specify whether for Television use or shop. Stand as shown in top photo. Price..... **\$31.50**

REAR PROJECTION TELEVISION SCREENS

The screen surface consists of a conglomerate arrangement of microscopic plastic crystals that "Pin Point" the projected image providing unexcelled angular viewing with a minimum loss of projected light. It is estimated that there is a loss of approximately 10% of light viewing the image at 45 degrees off center.

Light transmission percentages are controlled to obtain the maximum efficiency of the television optical projection system.

The percentage of 80% of transmission has been determined as that providing maximum efficiency.

Stock sheets are available from 3x4 feet down. Specify inside dimensions of screen desired. If larger sizes are required, they can be made to order.

Frames can be had on request, small sizes \$5.00—large sizes \$10.00. Price of screen, per sq. foot..... **\$4.50**

Include 25% Deposit With Order, Balance C.O.D.

Pioneers in Projection Television
SPELLMAN TELEVISION COMPANY
2398 JEROME AVENUE, NEW YORK 58, N. Y.

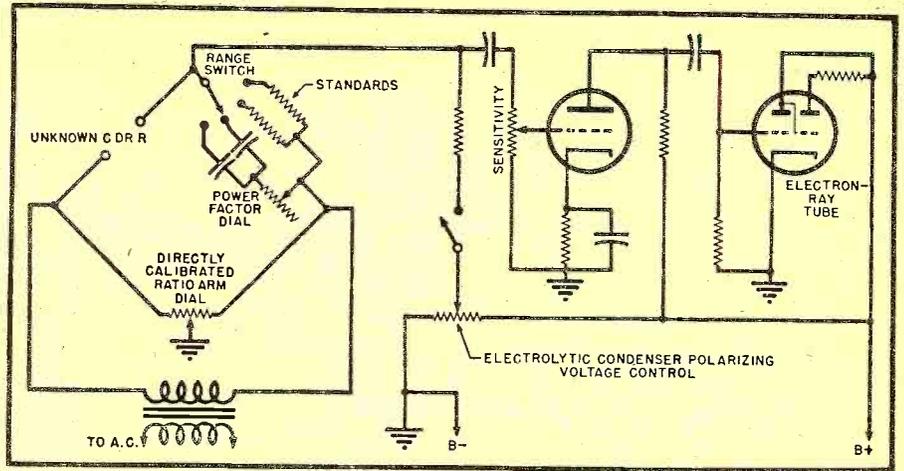


Fig. 2. Simplified circuit of a typical capacitance-resistance bridge.

tion of the batteries and replace them at regular intervals.

The application of the ohmmeter principle in multimeters and set analyzers is limited by the type and sensitivity of the basic indicating instrument, and commercial practices require that multimeters be the best compromise available to adequately serve as voltmeters, milliammeters, and ohmmeters. The electronic or vacuum tube type of instruments can provide more facilities for the measurement of extremely high resistances since most of these instruments employ a voltage comparison method of the drop across the known resistance compared to the drop across the unknown resistance.

Output or Db. Meters

The use of a signal generator in stage-by-stage servicing of radio receivers requires some type of meter connected across either the voice coil or a resistor substituted for the voice coil to indicate standard output. The provision for such an instrument is made in many multimeters by using the a.c. voltage ranges of the instrument with the scale calibrated in terms of decibels, and the coupling to these a.c. ranges is furnished by a rather large paper condenser. Meters not specifically equipped with db. ranges

can be used as output meters taking zero db. level as 1.73 volts across a 500 ohm load, and by proceeding from this point to the calculation of power ratio in the particular load used.

Summary

Voltmeters, ohmmeters, and milliammeters commercially available as multi-purpose instruments and on which measuring functions are selected by means of function and range switches, commonly provide ranges with the following full scale values:


a. On d.c. volts 3 to 5, 10 to 15, 30 to 50, 75 to 100, 250 to 300, 500 to 600, and 1000 to 1500 volts at sensitivities of 1000 ohms-per-volt and/or 20,000 ohms-per-volt or 25,000 ohms-per-volt.

b. The a.c. voltage ranges are usually the same with a sensitivity of 1000 ohms-per-volt.

c. The usual direct current maximum scale ranges are 50 microamperes, 100 microamperes, 1 milliamperes, 10 milliamperes, 50 milliamperes, 250 milliamperes, 500 milliamperes, and 1 ampere. In some cases, the lowest (50 microamperes) and the highest (10 ampere) current ranges are provided by separate jacks or binding posts and are not a part of the multiple switch deck.

d. For measuring a.c. amperes. Some instruments provide for the

Fig. 3. Diagram of cathode-bias or reflex type vacuum tube voltmeter. (A) The bypassed circuit and (B) a degenerative circuit.

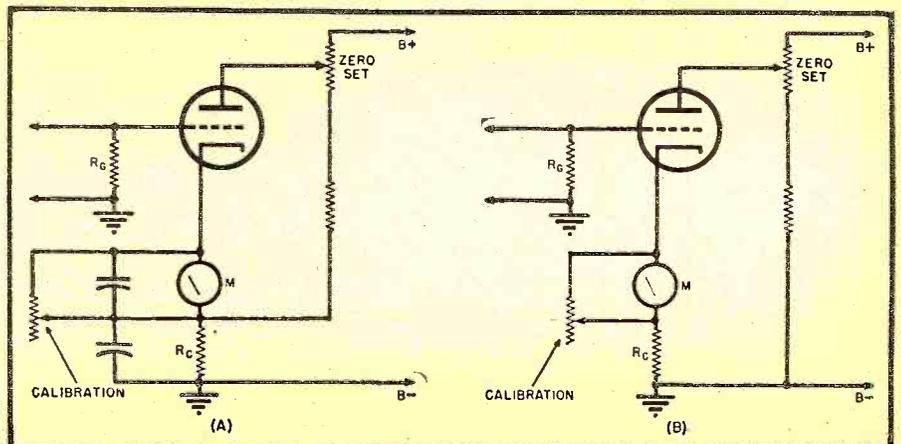

MASTER OSCILLATOR MI-19427-B
EASILY CONVERTED TO BECOME COMPLETE
TRANSMITTER WITH SIGNAL SHIFTER


IDEAL FOR TELEVISION WORK

This unit was built for R.C.A. Add a final—becomes a complete transmitter with signal shifter. 2:20 mg—also FM—only a few cycles drift from cold start. Complete with regulated power supply and heavy duty deluxe rack. Power supply is electronically regulated 330 v. output—maximum current 400 mills—1/2 v. variation between no load and full load output—uses 10 tubes: 5—6Y6G: 2—5U4G: 2—VR150/30: 1—1852—Perfect for Television sweep circuits for field or station use or wherever 300 v. must be maintained under varying load conditions. Write for free illustrated folder giving complete details.
COMPLETE (less tubes).....

\$225.00



TRANSMITTER BUY OF 1948

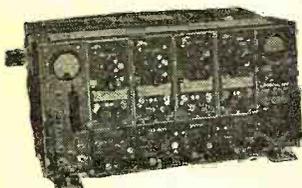

MODEL ATD AIRCRAFT TRANSMITTER
BUILT TO RIGID NAVY SPECIFICATIONS

This unit covers 540 Kc. to 9050 Kc. C.W. or tone, designed for Dynamotor Operation. Power supply requirements are 380 volts and 1000 volts DC.

Separate Ant. Tuning units covering the following frequencies:

- 540-1500 Kc.
- 1500-3000 Kc.
- 3000-9050 Kc.

Tube line-up as follows: RF Osc. 6L6-RF Amp. 814—Audio—5L7 Pre Amp. into 6L6 driver and side tone amplifier with pair of 6L6 modulators, screen oscillator tube, regulated with VR 150 Tube. All circuits are metered.

10 1/2" high, 12 1/4" deep, 21 1/2" long. Shipping weight 100 lbs. Price, F.O.B., New York City.

FOR QUICK SALE—
COMPLETE.....\$49.50

K T S

KITS!

KITS!

TUBE KITS
Complete set of tubes for SCR-522
\$17.95

Complete set of tubes for BC-348
\$7.95

Complete set of tubes for BC-312
\$7.95

Specify Model Numbers

POWER!! POWER!!

Niagara can supply a power supply kit which will completely power the ARC 5 Transmitter used as a VFO or any one of the ARC 5 receivers. All basic components included for delivering 300 v. @ 150 mills & 24 v. or 12 v. for the filaments—no rewiring of equipment necessary. This kit will also power the BC-348, BC-312 and the BC-1206. A good buy at.....**\$7.50**

DO YOU OWN AN SCR-522?

We have a complete power supply containing all the necessary parts down to the line cord, pilot light switch & terminal blocks & delivers the following voltage—300 v. DC @ 250 mills, 150 v. of regulated bias and sufficient 12 v. to operate the tubes of both receiver and transmitter. Complete at the amazingly low price of.....**\$14.95**

Model 200-EA. 5-ELEMENT 2 METER BEAM KIT. Folded di-pole driven element. All-aluminum construction. Feeds with low impedance coaxial cable. A amateur net price.....**\$8.40**

BC-348 Owners

CONVERTER for Broadcast Band

Convert that BC-348 without any alteration in your circuit. Our special converter takes power from receiver. Just tune your set to 450 kc. and forget it. All tuning is done on a converter panel covering 530 to 1600 kc.—double conversion means High Sensitivity, Excellent Fidelity and High Selectivity—complete basic kit with schematic and full instructions—less chassis dial and tuning knobs. Terrific Buy at.....**\$6.50**

INDUSTRIAL TRANSFORMERS

- 110-220 v. Primary—General Electric Cat. #7469125 1.0 KVA 50/60 cycles Secondary volts 2050 C.T. @ .487 amps..... **\$17.95**
- Prim 220 v. N. Y. Trans. Co. 50/60 cys. Sec. #1—10.2 volts @ 6.5 amps
- Sec. #2—10.2 volts @ 3.25 amps
- Sec. #3—6.4 volts @ 1.8 amps..... **6.50**
- Primary 220 v. N. Y. Trans. Co. 50/60 cys. Sec. 5.07 v. C.T. @ 13.5 amps..... **4.25**
- Primary 220 v. N. Y. Trans. Co. 50/60 cys. Sec. #1—6.4 v. C.T. @ 2.7 amps..... **4.75**
- Sec. #2—10.1 v. C.T. @ 6.5 amps..... **2.50**
- Primary 205 volts 50/60 cys. Sec. 6.4 C.T. @ .9 amps..... **12.95**
- Primary 220 v. N. Y. Trans. Co. 50/60 cys. 1220 volts C.T. @ .57 amps..... **12.95**
- Scope Transformer Potted Trans. Primary 110 volts Leads out the bottom
- Sec. #1—2500 v. @ 15 ma.
- Sec. #2—2 1/2 volts @ 3 amps insulated for 5000 v..... **8.95**


TRANSFORMERS

- All 110 v. 60 cy., unless otherwise specified
- FILAMENT TRANSFORMER 2 windings each 2.5 v. @ 10 A. Ceramic Terminals—High-voltage insulation—ideal for 866A's. Wt. 6 lbs. Secondaries can be serised for 5 v. @ 10 amps..... **\$ 4.25**
- FILAMENT TRANSFORMER Dual 6.3 v. C.T. 115 v. AC 60 cycles @ 4 amps. each. Federal Telephone & Radio Co. Wt. 7 lbs. Special at..... **3.95**
- FRAME TYPE G.E. 115 v. 60 cycles. Dual 5 volt windings .005 KV-A 12.5 kv. Insulation. For industrial application. Wt. 16 lbs..... **8.75**
- JEFFERSON ELECTRICS Hermetically sealed grey, ceramic insulators 6.3 v. @ 12 amps. Wt.

- 8 lbs. Western Electric D Spec. D161937. Feeds left @..... **4.25**
- PLATE TRANSFORMER General Electric frame type 110 or 220 v. primary 2050 volts @ 487 milliamperes. Wt. 52 lbs. Can be used in bridge to deliver 200 v. DC at 4880 ma..... **17.95**
- PLATE TRANSFORMER 870 v. Ct. @ 250 ma. Hermetically sealed Desirable for all PA or medium power requirements. Wt. 12 lbs..... **4.25**
- FRAME TYPE TRANSFORMER General Electric 1224 v. Ct. @ 213 ma., 118 v. Ct. @ 204 ma., 110 or 200 v. 50/60 cycle primary. Perfect for medium power..... **9.95**
- POWER TRANSFORMER hermetically sealed, electro-static shield and case, 330 v. D.C. @ 95 ma., 5 v. @ 2 A., 6.3 v. @ 7.5 A. Wt. 10 lbs. Special at..... **8.95**
- SHELL TYPE TRANSFORMER 600 v. Ct. @ 80 ma., 5 v. @ 2 amp. Wt. 4 lbs. Special at..... **3.95**
- POWER TRANSFORMER, Western Electric KS 8931—Pri. 115 v. 50-65 cycles. Sec. #1—815 volts @ .058 amps. Rated good for 100 mills. Sec. #2—506 v. @ 3 amps. Sec. #3—6.41 v. @ 6 amps. Special at..... **3.49**
- "TELEVISION" TRANSFORMER—Kenyon type, 2500 v. @ 3 ma. 6.3 v. @ 6 amp. 2.5 v. @ 1.75 amp. For 5" scope or 5 or 7" television receiver. Wt. 9 lbs..... **9.95**
- Scope or Television Transformer—Western Electric D spec D-161913 25500 v.—primary 115 v. 60 cycles..... **6.93**
- FILAMENT TRANSFORMER—Hermetically sealed, Ceramic insulators, Jefferson Electric. 6.3 v. @ 3 A., 2.5 v. @ 2 A. Western Electric D spec. D161917 Insulated for Television or scope use. Wt. 6 lbs..... **3.99**
- Combination of the last two Transformers—Special WRITE FOR OUR COMPLETE HALLIDORSON CATALOG OF BRAND NEW TRANSFORMERS FOR EVERY APPLICATION..... **9.95**

SELSYN MOTORS

CLOSE OUT

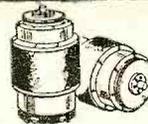

SPECIAL

Synchronous Type

- Pair in Series for 110 v. AC. Type 1—5 1/4" long, 3" dia.—50 v. AC. 50 cy.—4 lbs. **\$ 9.95 pr.**
- Type 11—6" long, 4 1/4" dia.—115 v. AC. 50 cy.—1 oz. **12.95 pr.**

SYNCHRO—DIFFERENTIAL

- Model #1943 — C78249-CAL-11280 Bendix Aviation 115 v.—60 cy. 6" length to end of shaft x 1/4" diameter..... **\$ 9.95**

DYNAMOTOR SPECIAL



Summer is here—Now is the time to be thinking of your portable rigs. These 12 v. dynamotors are ideal to power your portable 2 meter rig—low battery drain—235 v. output at 90 mills. Can be run at 50% overload—gives up to 110 mills at 215 v. without damage for continuous duty—complete with filter 6 1/4" x 5 1/4" x 3 1/2".

2 for \$3.95

CONDENSERS

- Cornell Dubilier dual .05 @ 9000 volts DC working #PC-2151-1..... **\$14.50**
- General Electric Pyranol #23F49-G2 1 Mfd 5000 v. DC working..... **6.75**
- Aerovox 1509—6 Mfd 1500 volts Working DC..... **2.89**
- Aerovox .1 Mfd 7500 Volts Working DC C-59644..... **3.95**
- Cornell Dubilier TJH 25010-G 1 Mfd 2500 v. Working DC..... **2.25**
- General Electric Pyranol 2 Mfd 4000 volts —DC working #23F47..... **5.50**
- General Electric Pyranol .005-.005-.01 Mfd 10,000 working volts DC..... **5.95**
- Micamold 2.5-2.5-5.0 Mfd 600 volts Working DC #C-8B..... **1.60**
- Micamold 4 Mfd. 600 volts DC working CP70E1DF405V..... **.95**
- General Electric Pyranol 4 Mfd 400 V. working #25F785..... **.95**
- General Electric Pyranol 2 Mfd. 1000 V. DC working #23F11..... **1.25**
- General Electric Pyranol .5 Mfd 2000 v. DC Working #26F698..... **2.40**
- Cornell Dubilier 2 Mfd 5000 v. DC Working #C-8B-2784..... **3.00**
- Cornell Dubilier 8 Mfd 2000 v. DC Working TJU 2080G..... **4.95**
- General Electric Pyranol .1 Mfd 12000 v. DC Working #26F628..... **12.50**
- Sprague 4 Mfd 1000 DC Working CSF 481903-10..... **1.95**
- General Electric Pyranol .04-.04 Mfd 7500 v. DC Working #26F415G2..... **6.50**
- Tobe Filtermite 8-8 Mfd 600 v. DC Working PT-SC-2 plug in capacitor..... **1.25**
- General Electric Model 2, Mark 3 type 9C Synchro-Capacitor 30-30 Mfd Delta connected 90 volts 60 cycles..... **10.50**
- Aerovox 4 Mfd — 1500 working V DC #1509..... **2.10**

WRITE FOR BULLETIN 5RN

NIAGARA RADIO SUPPLY CORP.

160 GREENWICH STREET


NEW YORK 6, N. Y.

ALL PRICES
F.O.B., N.Y.C.

Now

FM-AM RECEIVER COMBINATION

DESIGNED for CUSTOM INSTALLATION

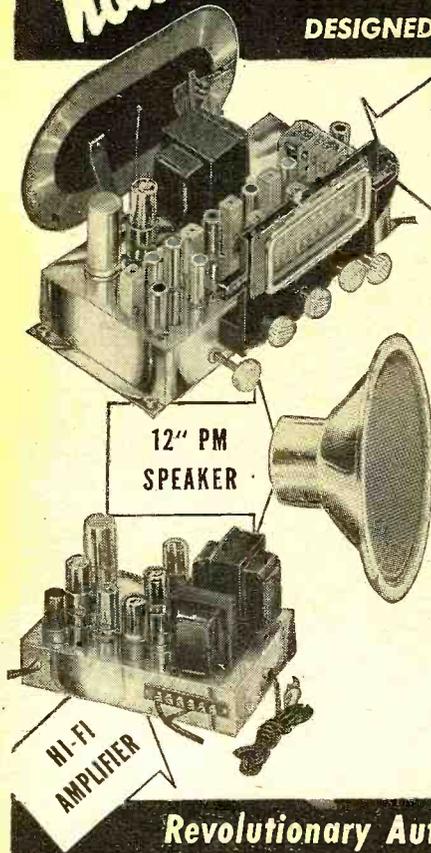

FM-AM TUNER

12" PM SPEAKER

HI-FI AMPLIFIER

A Receiver Combination you'll be proud to own or sell:

- No-drift FM-AM Receiver
- Hi-Fidelity Amplifier
- 12" PM Alnico V Speaker

FM-AM TUNER—RC-1 Features automatic frequency control, most revolutionary development in FM design—entirely eliminates drift and multiple tuning responses. Nine shielded miniature tubes plus rectifier include double limiter. Polished chrome chassis. Complete with cable, escutcheon, decals and antennae.

HI-FIDELITY AMPLIFIER—RC-2 High impedance input. 12 watts output at 1% distortion. Taps: 4, 6, 8, 15, 500 ohms: 65 db gain, including inverse feedback. Uniform frequency response from 20 to 20,000 cycles up to 8 watts output. Hum 65 db below rated output. Tubes: 6J5, 6SN7, (2) 6V6, 5Y3. Durable polished chrome chassis.

12" PM SPEAKER—RC-3 Outstanding performance. Handles up to 16 watts audio power. Alnico V 6.8-oz. permanent magnet. Voice coil 6 ohms. Completely dustproofed. Beautifully chrome plated.

Write for Descriptive Circular

The **RADIO CRAFTSMEN, Inc.**
1341 S. Michigan Ave. • Chicago 5, Ill.

Revolutionary Automatic Frequency Control

"America's Best Buy"

TUBULAR ELECTROLYTICS

Fresh Stock. Fully Guaranteed

Capacity	W.V.	Each	per 10	100
25 mfd.	25V	\$0.17	\$1.59	\$14.95
50 mfd.	50V	.21	1.79	16.95
100 mfd.	50V	.24	2.29	19.98
20 mfd.	150V	.21	1.89	17.95
30 mfd.	150V	.22	1.95	18.95
40 mfd.	150V	.23	2.04	19.74
50 mfd.	150V	.24	2.14	20.45
20-20 mfd.	150V	.29	2.49	22.98
30-20 mfd.	150V	.32	2.95	25.98
40-20 mfd.	150V	.36	3.25	29.95
50-30 mfd.	150V	.39	3.49	32.98
8 mfd.	450V	.21	1.99	19.50
8-8 mfd.	450V	.42	3.98	35.76
16 mfd.	450V	.39	3.74	33.78


BY-PASS CONDENSERS

.01	600V	\$0.06	\$0.55	\$ 4.60
.02	600V	.06	.55	4.75
.05	600V	.06	.55	4.95
.1	600V	.07	.65	4.49
.25	600V	.11	.98	8.95
.005	1700V	.14	1.25	9.95
.007	1700V	.14	1.25	9.95
.01	1700V	.15	1.30	10.20
.02	1700V	.16	1.40	10.95

An assortment of 50 of the above By-pass condensers. Fine value for the small shop or experimenter, only \$2.98

RESISTOR ASSORTMENT

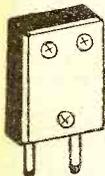100 assorted 1/4-1/2 watt carbon resistors. All RMA color coded. Special \$1.29.



CRYSTALS 98c each

Your frequency plus or minus 10 KC


- 80 Meter, 3500-4000KC
- 40 Meter, 7000-7300KC
- for multiplying into
- 20 Meter, 7300-7425KC
- 10 Meter, 7300-7425KC
- 6 Meter, 6250-6750KC
- 2 1/2 Meter, 8000-8225KC

Postage extra 20% deposit on COD. Write for latest bargain list featuring "America's Best Buys."

POTTER RADIO CO.

1314 McGee St., Kansas City 6, Mo.

CU-24 / ART 13 LOADING CONDENSERS

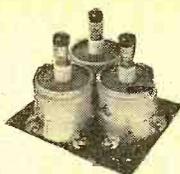

- *Part of the famous ART-13 TRANSMITTER
- *Three 25 mmf.-10,000V condensers in each set!
- *Worth more than 10 times this low price
- *BRAND NEW—ORIGINAL CARTONS

\$395

Shipped anywhere in U.S.A. for 50¢

BC-348 SHOCKMOUNT BASE

Dress up your "348" with a new base—fits all models—brand new in original cartons. Shipped anywhere in U.S. for 35¢. Enclose \$2.00 for each base wanted. Money Back Guarantee.

\$165

EACH

SCR-274-N RECEIVER RACKS

Three section racks for your SCR-274-N receivers. Will hold three of the following: BC-453, 454, 455, and 946-B.

BRAND NEW—ORIGINAL CARTONS
Shipped anywhere in U.S.A. for 50¢

87c

Get On Our Mailing List

Discounts on Larger Quantities On Request
Mail Orders Promptly Filled—Your Satisfaction or Your Money Back

ELECTRONIC SALES CO.

5559 W. ADAMS BOULEVARD
LOS ANGELES 16, CALIF.

DEPT. RN-548

PHONE WEBSTER 3-7173

measurement of a.c. amperes in the range of 1/2 to 10 amperes.

e. Ohmmeters usually cover a span of from zero to 100 megohms in 5 ranges.

Capacitance and Resistance Measurement Devices

The normal method of measuring capacitance is by means of an alternating current bridge in which the unknown condenser becomes one arm of the bridge. An internal standard condenser comprises another arm, and measurement is accomplished by varying resistance ratio arms. (See Fig. 2.) In most cases, the point of balance of the bridge is indicated by the use of an electron ray indicator tube. Several instruments on the market employ pointer type meters for indication of bridge balance. Capacitance bridges provide a number of ranges to enable the measurement of mica, ceramic, paper, and electrolytic types.

The degree of balance of any arc bridge is affected by both the reactance of the condenser and its resistance. For this reason, additional controls are provided on these bridges to balance the out-of-phase or resistive component, and the final setting of this control can be taken as an indication of the losses of the condensers. This control is usually calibrated in terms of power factor. Electrolytic type condensers which in most radio applications are of the polarized type, operate in the receiver with d.c. voltage of the proper polarity impressed across the condenser. Accordingly provision for an adjustable polarizing voltage of the correct value is usually made in a condenser checker. Since alternating current bridges of the various types designed for capacitance measurement can readily be converted by switching to pure resistance bridges, this class of instruments usually has resistance as well as capacitance scales, and many such types are commercially available. In a few capacitance-resistance bridges, other features are provided which enable the suspected condensers to be spot checked quickly on a "good or bad" basis without their removal from the circuit. Other features sometimes included in this type of instrument are the provision for measurement of direct current and voltage although the instrument is not primarily intended for this purpose.

Some multimeters are provided with capacitance scales which employ the 60-cycle power line as a source of standard voltage and measure the alternating current through the condensers, the scale or scales being calibrated directly in microfarads.

Electronic Multimeters and V.T.V.M.'s

As previously noted in this article, an undesirable feature of the indicating instruments which are directly connected with circuit components for voltage measurements is that these instruments must draw power, which though small may upset accurately

RADIO NEWS

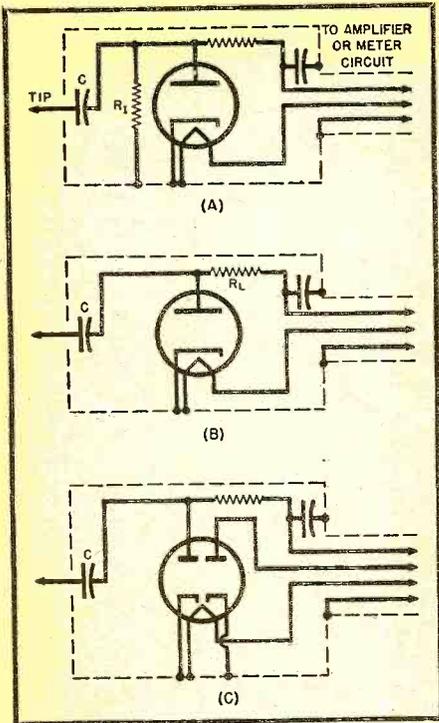


Fig. 4. Diode probe circuits. (A) Parallel input load and filter, (B) series load and filter combined, and (C) dual diode for use with balanced circuits.

tuned circuits or cause incorrect voltage readings. For this reason primarily, the electronic or vacuum tube voltmeter was developed. This instrument is essentially a device which isolates the indicating instrument from the circuit under measurement; and many different circuits have been developed which will perform this function.

Classification of V.T.V.M.'s

Vacuum tube voltmeter circuits may be classified with regard to use. These are three principal functions:

1. Measurement of d.c. voltages.
2. Measurement of audio and low frequency r.f. voltages.
3. Measurement of radio and u.h.f. voltages.

1. *Measurement of d.c. Voltages.* The instruments for this purpose may provide for reversal of polarity by means of switching and, in this case, the test leads need not be color-coded or marked. In many instruments, the d.c. measurement probe contains an isolation resistance of from 1 to 3 megohms located immediately behind the contact point. This assures a very low input capacitance which combined with the rest of the voltmeter input circuit provides negligible loading in the average radio circuit. It should be noted that the use of such an isolation resistor makes it possible to measure d.c. voltages in circuits which are operating with r.f. or a.f. voltages superimposed. The d.c. voltage measurement is not affected by the presence of the other voltages and the circuit operation is not disturbed by the measurement.

2. *Measurement of Audio and Low Frequency r.f. Voltages.* In instru-

May, 1948



THAT IN 2 MINUTES
AN AVERAGE RADIO
SPEAKER EXERTS
ENOUGH ENERGY TO
HIT A BASEBALL
OVER 850 FEET?

That's a homerun in any ball game but of course you can't put a loudspeaker in as a pinch-hitter. However, it is true that the amount of energy exerted by an average radio speaker in just 2 minutes could hit a baseball 850 feet! This means that although OPERADIO builds speakers with the skill and care of a watchmaker... these speakers are sturdily constructed to stand up under heavy, continuous use. OPERADIO speakers are delicately balanced to authentically reproduce the sweetest high notes of a piccolo, yet, carry the tremendous power of a full orchestra crescendo.




ASK FOR OPERADIO SPEAKERS —
A FULL LINE OF OUTSTANDING
SPEAKERS FOR EVERY PURPOSE!

OPERADIO

RADIO REPLACEMENT and
PUBLIC ADDRESS SPEAKERS

OPERADIO MFG. COMPANY • St. Charles, Illinois

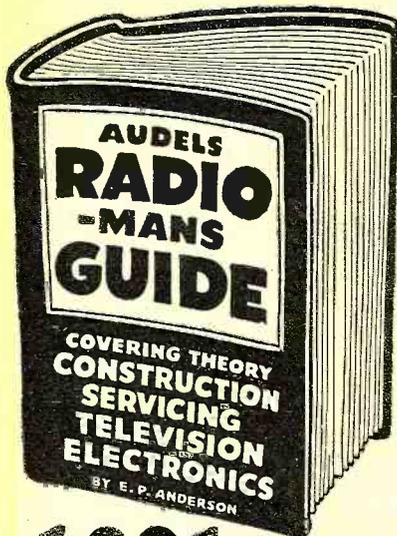**PLEASE TEAR OUT THIS
ADV. AS REMINDER**



1001 RADIO FACTS AND FIGURES

AUDELS RADIOMANS GUIDE—914 Pages, 633 Illustrations, Photos, Wiring Diagrams, 88 Big Chapters, covering Radio Theory, Construction, Servicing, including Important Data on Developments in Television, Electronics and Frequency Modulation, Review, Questions and Answers, Calculations & Testing. Highly Endorsed—Indispensable for Ready Reference and Home Study.

\$4 COMPLETE • PAY ONLY \$1 A MONTH
Step up your own skill with the facts and figures of your trade. Audels Mechanics Guides contain Practical Inside Trade Information in a handy form. Fully illustrated and Easy to Understand. Highly Endorsed. Check the book you want for 7 days' Free Examination.

Send No Money. Nothing to pay postman.

CUT HERE
MAIL ORDER

AUDELS, Publishers, 49 W. 23 St., NEW YORK 10, N. Y.

Please send me postpaid for **FREE EXAMINATION** books marked (x) below. If I decide to keep them I agree to mail \$1 in 7 Days on each book ordered and further mail \$1 monthly on each book until I have paid price—otherwise, I will return them.

- RADIOMANS GUIDE, 914 Pages . . . \$4
- ELECTRICIANS EXAMINATIONS, 250 Pages . . . 1
- WIRING DIAGRAMS, 210 Pages . . . 1
- ELECTRIC MOTOR GUIDE, 1000 Pages . . . 4
- ELECTRICAL DICTIONARY, 9000 Terms . . . 2
- ELECTRICAL POWER CALCULATIONS, 425 Pgs. . . 2
- HANDY BOOK OF ELECTRICITY, 1440 Pages . . . 4
- ELECTRONIC DEVICES, 216 Pages . . . 2
- ELECTRIC LIBRARY, 12 vol., 7000 Pgs., \$1.50 vol. . . 1
- OIL BURNER GUIDE, 384 Pages . . . 1
- REFRIGERATION & Air Conditioning, 1280 Pgs. . . 4
- POWER PLANT ENGINEERS Guide, 1500 Pages. . . 4
- PUMPS, Hydraulics & Air Compressors, 1658 Pgs. . . 4
- WELDERS GUIDE, 400 Pages . . . 1
- BLUE PRINT READING, 416 Pages . . . 2
- SHEET METAL WORKERS Handy Book, 388 Pgs. . . 1
- SHEET METAL PATTERN LAYOUTS, 1100 Pgs. . . 4
- AIRCRAFT WORKER, 240 Pages . . . 1
- MATHEMATICS & CALCULATIONS, 700 Pgs. . . 2
- MACHINISTS Handy Book, 1600 Pages . . . 4
- MECHANICAL Dictionary, 968 Pages . . . 4
- AUTOMOBILE GUIDE, 1700 Pages . . . 4
- DIESEL ENGINE MANUAL, 400 Pages . . . 4
- MARINE ENGINEERS Handy Book, 1280 Pages . . . 4
- MECHANICAL DRAWING GUIDE, 160 Pages . . . 1
- MECHANICAL DRAWING & DESIGN, 480 Pgs. . . 2
- MILLWRIGHTS & Mechanics Guide, 1200 Pgs. . . 4
- CARPENTERS & Builders Guides (4 vols.) . . . 6
- PLUMBERS & Steamfitters Guides (4 vols.) . . . 6
- MASONS & Builders Guides (4 vols.) . . . 6
- MASTER PAINTER & DECORATOR, 320 Pgs. . . 2
- GARDENERS & GROWERS GUIDES (4 vols.) . . . 6
- ENGINEERS and Mechanics Guides . . . 1
- Nos. 1, 2, 3, 4, 5, 6, 7 and 8 complete . . . 12
- Answers on Practical ENGINEERING . . . 1
- ENGINEERS & FIREMANS EXAMINATIONS . . . 1

Name _____

Address _____

Occupation _____

Employed by (x) _____ RN

120

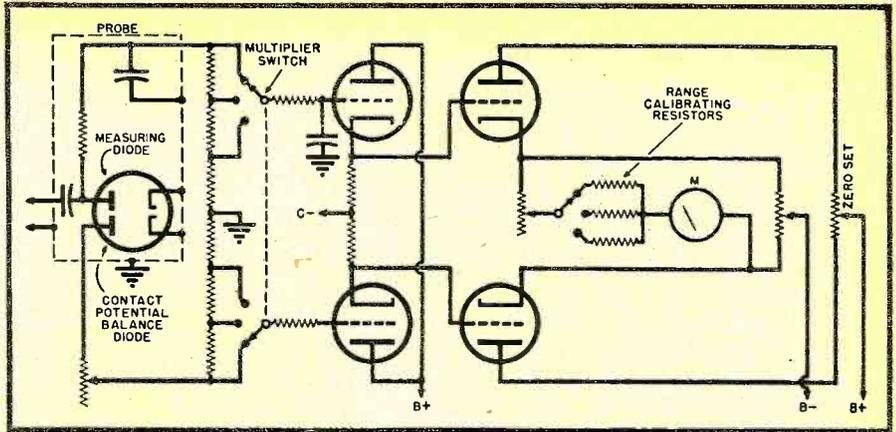


Fig. 5. Multi-range electronic voltmeter with balanced cathode follower circuit.

ments for this purpose the vacuum tube and its associated circuit are normally mounted within the instrument and connections to them are made by pin-jacks and ordinary test leads. The input circuit has a coupling condenser that is large enough to assure response to the low audio frequencies in the neighborhood of 60 cycles. This type of voltmeter is superior in its capabilities to the dry disc rectifier type instrument previously described since such rectifier instruments rarely have sensitivities higher than 1000 ohm-per-volt; whereas the a.f. vacuum tube voltmeter may have input resistance in the order of 10 megohms or more.

In addition, the vacuum tube voltmeter will have good accuracy over the entire audio range; whereas the dry disc rectifier type meter falls off in response at the higher audio frequencies.

3. *Measurement of Radio and u.h.f. Voltages.* The r.f. probe type instruments employ a vacuum tube, usually of the miniature or subminiature type, mounted directly in the measurement probe and in which the input circuit design features low capacitance and a very high natural resonant frequency. Some of these instruments permit measurement to as high as 300 megacycles. The probe type instrument cannot replace the other two mentioned above since the low coupling capacity required causes the measurement to be in error in the audio frequency range.

Classification as to Type of Circuit

Since the vacuum tube voltmeter is essentially an application of the detection or demodulation principle, all of the methods of operation of a vacuum tube as a detector may be employed in designing a vacuum tube voltmeter. These include grid rectifier types commonly known as grid leak detectors, plate rectification types, cathode bias or reflex types, diode rectifiers, and "slide back" bias types: The choice of circuit type depends on several factors such as the functions of the instrument as discussed above, the necessity for combining several functions in one instrument, cost of design, and susceptibility to variations due to line voltage fluctuation, tube aging, tube replace-

ment, and contact potential effects. Many instruments employ direct current amplifiers, bridge circuit amplifiers, and cathode follower circuits. Since the foregoing circuit types have been used in many combinations, it is felt that an individual description of circuits with a few examples of their combined use may be of value.

Slide-Back Voltmeters: The slide-back voltmeter was a very early application of vacuum tubes to voltage measurement. It is essentially a plate circuit detector in which the input signal causes an increase of plate current as indicated on a pointer type meter. The bias voltage, which is also indicated on a meter, is changed by means of a control to restore the plate meter reading to the value which it read prior to the measurement. The change of bias voltage is equal to the peak voltage under measurement. This type has been abandoned since it is not direct reading and does not accommodate itself to multi-function instruments.

Grid Rectifier Meters: The grid rectifier or grid leak detection meter, also an early type, actually combines diode action in the grid circuit with amplification in the plate circuit of the same tube. Its use has been superseded by separating these functions so that wider range multi-purpose instruments may be commercially available.

Cathode Bias or Reflex Type: This type employs a meter in the cathode circuit in series with a resistor which develops bias potential from the plate current. (See Fig. 3) There is no load in the plate circuit which either returns directly to "B-plus" or to an adjustable plate voltage for the purpose of zero setting the instrument. The grid circuit is normally returned to "B-minus" through an extremely high resistor in the order of 10 megohms. The cathode bias resistor is of such a value as to reduce the plate current to a point near cut-off; and, for this reason the circuit is another form of plate rectifier. An alternating voltage or a positive potential on the grid will cause an increase in plate current and an upward reading of the meter in the cathode circuit. The circuit is of value in measuring instruments since it can be used for both a.c. and d.c. measure-

A CHALLENGE—Order a model 247. Disregard the unbelievably low price and compare it on the basis of appearance, quality and performance to any other Tube Tester (*Any make, any price*). If you are not completely satisfied with the model 247 after a 15 day trial, return it to us for full refund—no explanation necessary. The model 247 is not surplus nor is it a hashed-over pre-war model. It is newly designed and incorporates new advances in Tube Tester design. Read the description below and order one today!



THE NEW MODEL 247

TUBE TESTER

Incorporates a newly designed element selector switch which reduces the possibility of obsolescence to an absolute minimum. Any pin may be used as a filament pin and the voltage applied between that pin and any other pin, or even the "top-cap."

The new free-point system described above permits the Model 247 to overcome the difficulties encountered with other emission type tube testers when checking Diode, Triode and Pentode sections of multi-purpose tubes, because sections can be tested individually when using the new Model 247. The special isolating circuit allows each section to be tested as if it were in a separate envelope.

The Model 247 provides a super sensitive method of checking for shorts and leakages up to 5 Megohms between any and all of the terminals. Continuity between various sections is individually indicated. One of the most important improvements, we believe, is the fact that the 4 position fast-action snap switches are all numbered in exact accordance with the standard R. M. A. numbering system. Thus, if the element terminating in pin No. 7 of a tube is under test, button No. 7 is used for that test.

Model 247 comes complete with new speed-read chart. Comes housed in handsome, hand-rubbed oak cabinet sloped for bench use. A slip-on portable hinged cover is included for outside use. Size: 10 3/4" x 8 3/4" x 5 3/4"


ONLY
\$ 29⁹⁰
NET

THE MODEL 650—AN A.C. OPERATED

SIGNAL GENERATOR

RANGE: 100 KILOCYCLES TO 105 MEGACYCLES

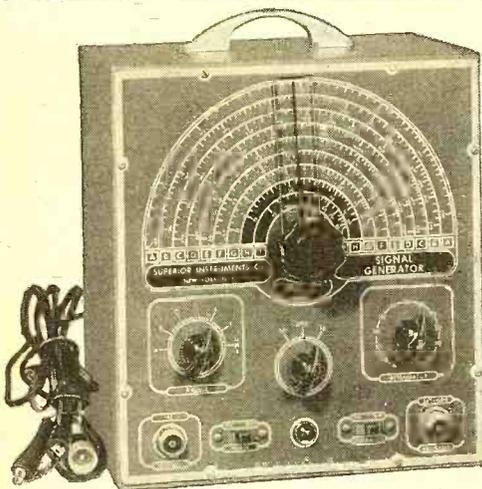- ★ RF obtainable separately or modulated by the Audio Frequency.
- ★ Audio Modulating Frequency — 400 cycles pure sine wave — less than 2% distortion.
- ★ Attenuation—3-step ladder type of attenuator (T pad).
- ★ Uses a Hartley Excited Oscillator with a Buffer Amplifier.
- ★ Tubes: 6J5 as R.F. Oscillator; 6SA7 as modulated buffer and Mixer; 6SL7 as audio oscillator and rectifier.



Model 650 comes complete with coaxial cable, test leads and instructions. Housed in heavy gauge grey crystalline cabinet with beautiful two tone etched front panel. Size 9 1/2" x 10" x 6".....NET PRICE:

\$ 39⁹⁵


The New Model 670 SUPER METER

A Combination VOLT-OHM-MILLIAMMETER plus CAPACITY REACTANCE, INDUCTANCE and DECIBEL MEASUREMENTS.

D.C. VOLTS: 0 to 7.5/15/75/150/750/1500/7500.—A.C. VOLTS 0 to 15/30/150/300/1500/3000 Volts.—OUTPUT VOLTS: 0 to 15/30/150/300/1500/3000.—D.C. CURRENT: 0 to 1.5/15/150 Ma.; 0 to 1.5 Amps.—RESISTANCE: 0 to 500/100,000 ohms, 0 to 10 Megohms.—CAPACITY: .001 to 2 Mfd., 1 to 4 Mfd. (Quality test for electrolytics).—REACTANCE: 700 to 27,000 Ohms; 13,000 Ohms to 3 Megohms.—INDUCTANCE: 1.75 to 70 Henries; 35 to 8,000 Henries. DECIBELS: -10 to +18, +10 to +38, +30 to +58.

The Model 670 comes housed in a rugged, crackle-finished steel cabinet complete with test leads and operating instructions. Size 5 1/2" x 7 1/2" x 3".

\$ 28⁴⁰
NET

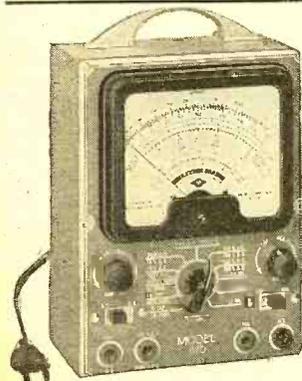


AVAILABLE FOR IMMEDIATE SHIPMENT FROM STOCK—20% DEPOSIT REQUIRED ON ALL C.O.D. ORDERS

MOSS ELECTRONIC DISTRIBUTING CO.

DEPT. RN-5, 229 FULTON STREET
NEW YORK 7, N.Y.

for **QUALITY of Reproduction . . .**

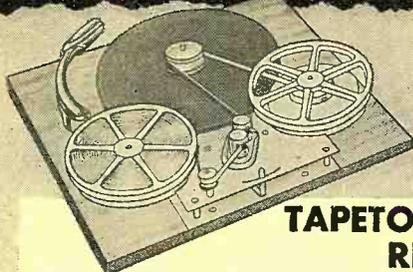

tapetone
is TOPS!

TAPETONE MAGNETIC TAPE RECORDING KIT

For Homes, Schools, Studios . . . Set Builders, Hams, Radio Engineers are all enthusiastic about the newly developed TAPETONE Magnetic Tape Recorder. ● Records voice and music on tape. ● Plays up to 12" platter records and reproduces from the records on to the tape. ● Records radio reception on tape. Tape can be played back and re-recorded hundreds of times.


THE RECORDING-PLAYBACK MECHANISM

(Illustrated above) comprises heavy duty General Industries motor mounted on rubber, and 10" 3 lb. turntable. Complete tape drive mechanism of exclusive TAPETONE design. Precision tooled with bronze bearings throughout for marvelously smooth quiet operation. Lever has Record-Play, Neutral, and rewind positions. Crystal pickup with permanent stylus. Separate Record-Play and Erase Heads, plug-in type TAPETONE exclusive design. Recording magnetic paper tape is simple to thread and can be edited more easily than home movie film. TAPETONE MAGNETIC TAPE RECORDING MECHANISM, NOW AVAILABLE SEPARATELY, includes; Recording-Playback mechanism illustrated and described above, for 115 Volt 60 cycle AC only; completely assembled plus mounting board; Amplifier wiring diagram; one 1/2 hour roll (1225 ft.) of new SCOTCH HIGH FIDELITY MAGNETIC RECORDING TAPE. Shpg. Wt. 22 lbs.

Your net cost **\$62.50**

THE EQUALIZED AMPLIFIER

This specially-designed 6-tube recording and playback amplifier is equipped with exciter circuit for operation with mechanism above. Has high impedance microphone and phono-radio inputs with separate gain controls, permits mixing. Output connects to 4 or 8 ohm speaker voice coil. Supplied in kit form, with all components, tubes, drilled chassis, wire connectors, plugs, cables, nothing else needed — no special knowledge required to construct it. For 115 Volt 60 cycle AC only.

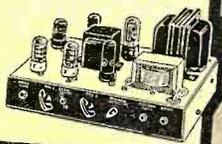

COMPLETE TAPETONE MAGNETIC TAPE RECORDING KIT

Includes Recording-Playback Mechanism and Amplifier Kit described above, plus one 1/2 hour roll (1225 ft.) of new SCOTCH HIGH FIDELITY MAGNETIC RECORDING TAPE. Shpg. wt. 30 lbs. Express collect.

Your net cost, Complete **\$98.50**

Please include 20% deposit with C.O.D. Orders

OPTIONAL ACCESSORIES: Crystal Desk Mike with removable base and 7-ft. cable . . . List \$12.20. 8-inch Heavy Duty PM Speaker . . . List \$8.85. Additional 1/2 hour rolls Scotch Recording Tape, per roll. . . \$3.00 (Plus 15¢ postage when ordered separately)

TAPETONE MFG. CORP.

37-06 36th St. Long Island City 1 N.Y.

Phone: STillwell 4-8380

Columbia



KIT OF ASSORTED WIRE

Ten 100 foot coils of wire, assorted colors and sizes No. 18 to No. 24. Lead-in, push-back and hook-up wire.

\$4.50
A REAL BUY

We carry in stock for immediate delivery many types of wire and cable in gauges of from 23 to 2, in addition to various types of multi-conductor cable for many uses. We also manufacture cord sets and cables to specifications. Send us your inquiries for prompt attention.

OUR NEW CATALOG IS NOW AVAILABLE FOR DISTRIBUTION

Write for your copy today!

COLUMBIA WIRE & SUPPLY CO.

5734 ELSTON AVE.
CHICAGO 30, ILLINOIS



**More Money
for You
in Radio**

*Qualify here for your
Radio Operating
Engineer's Licenses*

Complete instruction for passing F.C.C. Commercial and Amateur Radio Operator's License Examinations.

*Small classes and
individual attention*

NEW CLASSES FORMING REGULARLY

G. I. Approved Training

Write for complete information

**RADIO INSTITUTE
OF CHICAGO**

165 North Michigan Ave.
Chicago, Ill.

ments. The bias resistor and the meter circuit may be bypassed for high sensitivity or may be left unbypassed to obtain a longer range due to the degenerative action of the unbypassed bias resistor. This circuit has sometimes been referred to as a d.c. amplifier since it can be directly connected to a diode probe. This allows a multiple instrument in which a.c. voltages are measured by the probe and d.c. voltages by switching directly to the cathode loaded tube.

Diode Rectification Type: In practically all the u.h.f. probe type instruments, of which a number have appeared recently on the market, a diode or a double diode is positioned with its input circuit elements in the end of a probe. (See Fig. 4) The development during the war of subminiature or proximity type tubes of extremely small dimensions with very low inter-electrode capacitances and high resonant frequencies have provided the instrument design engineer with a new and extremely useful tool. The probe input circuit consists of a small coupling condenser between the contact point and the diode plate. Parallel leak resistance of a high value usually 10 megohms or more connects the diode plate with the cathode which in turn is connected to the metal shell or ground lead of the probe. A filter circuit consisting of a resistor of from 1 to 5 megohms followed by a parallel condenser of approximately .002 μ fd. is used to isolate the diode from the grid of the meter tube in the instrument case. This combination will present input characteristics of from 2 to 10 μ fd. with parallel resistances of from 5 to 10 megohms depending upon the design of the particular probe circuit. One problem presented by the diode in calibration of the instrument and in interchange of tubes on replacement is that of contact potential.

In any vacuum tube an element having a potential nearly equal to the cathode will assume a negative charge due to electrons received from the cathode. This is the so-called "space charge," and the presence of this space charge effect prevents the rectified output from being linear with respect to the input at low input levels. Certain designs of vacuum tube voltmeters overcome this space charge or contact potential effect by feeding a small positive bias to the diode plate through an extremely high parallel resistance. In more recent circuits, advantage has been taken of the fact that dual diodes are available in miniature size tubes and the contact potential of the other diode is employed to balance that of the measurement section. This has been accomplished by the use of a balance type circuit in which each tube is of a dual type with an identical section to perform the balance function. Such an arrangement has the advantage that line voltage fluctuations and the drift characteristics of the tubes with age are balanced. An additional feature is the fact that the replacement of any tube will auto-

RADIO NEWS

matically rebalance the circuits since each section and its twin are likely to have identical characteristics.

Balanced Cathode Follower Metering Circuits: A recent and popular type of circuit which combines a number of the features covered consists of a dual-diode r.f. probe followed by a dual-triode cathode follower coupling tube, which in turn feeds another dual-triode cathode loaded meter tube. (See Fig. 5) Such a combination isolates the metering circuit from the range switches, allows the measurement of direct currents of either polarity and in conjunction with the diode probe permits measurements of a.c. voltage to be taken over the entire range including the highest contemplated FM and television frequency assignments.

The most recent multiple instruments combine the electronic voltmeter principle with the measurement of resistance, alternating current, and capacitance.

In conclusion it is suggested that the following factors be considered when contemplating the purchase of this class of service instruments: 1. range of measurement; 2. basic sensitivity; 3. accuracy required; 4. clarity of scale presentation; 5. stability; 6. ruggedness; 7. quality of components employed.

Since these devices will be in daily use in the radio technician's shop over many years, careful choice should be made from the lines offered by established manufacturers of known reputation and integrity. —30—

Freak TV Reception

THE San Diego area has one hundred television receivers in operation in spite of the fact that the nearest TV transmitter is 115 miles away!

Harry R. Lubeke, Director of Television for the Don Lee Broadcasting System, reports that television fans in San Diego agree that when the weather is "right" they see television in San Diego as clearly as persons viewing the programs in Los Angeles.

According to Mr. Lubeke, although San Diego is considerably below line-of-sight the television waves are gradually bent around the surface of the earth by a convenient coastal "temperature inversion". That is, warm desert air normally overlays the cool ocean air at elevations above 2000 feet. This is in the "tropospheric region" of the atmosphere, the region which affects almost all weather; hence the correlation between weather and this long distance television transmission. A "frontal disturbance", namely a rainstorm, destroys the above stratification and the signals from Hollywood drop to an undesirably low value. San Diego viewers claim that they can predict a storm because television reception drops out a few hours before.

In San Diego television receiving antennas are characterized by their considerable height and complexity. It is usual to see a half-dozen horizontal elements atop a forty-foot pole located on the highest portion of the building being served. It has been reported that the most successful installations are near the ocean. —30—

May, 1948

TEST CRAFT Instrument Co. Proudly presents
THE NEW MODEL TC-48

COMBINATION TEST SPEAKER



A COMBINATION TEST SPEAKER

plus resistor tester
plus condenser tester
plus resistor substituter
plus condenser substituter
plus output meter

No need to carry the speaker to your shop in servicing any radio from the small midget to the most elaborate console. Any output tube or tubes can be matched simply by rotating input switch to tube listed and rotate field switch for proper impedance. External voice coil connection permits testing of set speaker to determine if output transformer is open or shorted.

SPECIFICATIONS

RESISTOR CONDENSER TESTER: 110 Volt A.C. power source for basic indications of either shorts and opens in both resistors and condensers. Leakage indication for condensers only. CAPACITY SUBSTITUTION: 7 capacity values available. .001, .01, .02, .05, .10 at 500 volts and 30 mfd. and 50 mfd. at 150 V. Provides substitution of by-pass coupling and electrolytic condensers. RESISTOR SUBSTITUTION: 6 resistance values available. 400, 50K, 100K, 500K, 2 meg. and 5 meg. at 1/2 watt. Provides substitution of grid bias and other types of resistors. OUTPUT METER: Neon type of output indicator for receiver alignment. UNIVERSAL AND SUBSTITUTION SPEAKER: Field—500-1000-1500 and 2500 ohms at 175 ma. Speaker:—Permanent magnet type. Voice Coil:—2.8 ohms. Input:—Single or push pull.

Available at your regular radio parts jobber. If your jobber cannot supply you, send your order directly to us.

A MUST FOR EVERY RADIO
SERVICEMAN AND ENGINEER

\$27⁵⁰
NET PRICE

THIS UNIT COMES HOUSED IN A RUGGED, BATTLESHIP GRAY, CRACKLE-FINISHED, STEEL CABINET, COMPLETE WITH FULL OPERATING INSTRUCTIONS, READY TO OPERATE ON 110-125 Volts A.C., 50-60 Cycles. SIZE: 7"x11"x5".

Now Available for IMMEDIATE SHIPMENT

TEST CRAFT INSTRUMENT CO.

42 WARREN STREET Dept. RN NEW YORK 7, N. Y.

Watch for additional TEST CRAFT quality instruments.

30,000 SUCCESSFUL RADIO SERVICE- TECHNICIANS READ



EVERY MONTH

RADIO MAINTENANCE today fills a breach that has existed in the radio field for a long time. Already 30,000 technicians read RADIO MAINTENANCE every month because it is devoted entirely to the radio servicemen.

The RADIO MAINTENANCE staff specializes in the preparation of articles on every phase of Radio Maintenance in series form which may be filed and used for reference. The leading articles cover everything for the radio servicemen on Television, FM and AM; Test Equipment; Electronic Appliances; Tools; Antennas; Alignment; Troubleshooting; Repair; Construction; Pick-Ups and Sound Amplification and Reproduction Equipment. Also, in RADIO MAINTENANCE each month there are departments on hints and kinks, the latest news of the trade, review of trade literature, radiomen's opinions, new products and news from the organizations. All articles are presented in a step-by-step precision style, clearly illustrated with schematics, accurate photographs, specially prepared drawings, white on black charts, color diagrams, isometric projection and exploded views.

Binders in beautiful green simulated leather are now available for your RADIO MAINTENANCE magazine. See the current issue for details. RADIO MAINTENANCE is not sold on newsstands.

RADIO MAINTENANCE
MAGAZINE

RN-5

460 Bloomfield Avenue,
Montclair, N. J.

Please send me RADIO MAINTENANCE for
() 2 years, \$5 () 1 year, \$3
() Payment enclosed () Bill me later

Name
Address
City—State
Occupation
Title
Employed by

* Independent Serviceman—Dealer Serviceman—Service Manager—Dealer—Distributor—Jobber.

BOLAND & BOYCE INC., PUBLISHERS

Manufacturers' Literature

CARRIER TELEPHONE

The *Lenkurt Electric Co.*, of San Carlos, California have recently published a 68 page bulletin covering their Type 32 Carrier Telephone Systems.

This bulletin covers frequency allocations for carrier telephone, and continues with descriptions of the terminals, repeaters, pilot regulators, and auxiliary units which make up the system.

Auxiliary units discussed include; voice-frequency terminating equipment, ringdown signaling gear, carrier-frequency dialing facilities, carrier-transfer equipment, voice-frequency repeater-balancing devices, bridged-station filters, autotransformers, repeating coils, relay racks, test units, and power supplies.

Performance details are included, and a useful appendix provides engineering data on line attenuation and cable losses, together with information required in planning a carrier system.

Further information may be obtained by writing to the *Lenkurt Electric Co.*, 1115 County Road, San Carlos, California.

"ENGINEERING NEWS"

The second issue of "Engineering News" has been issued by the *American Phenolic Corporation*. This is a resumption of the prewar "Engineering News" which was suspended during the war.

In this second issue is an article by Charles Adams called "Industrial Electron Tube Sockets" in which Mr. Adams discusses materials and design of the new *Amphenol* sockets.

A copy of the booklet may be obtained from the *American Phenolic Corporation*, 1830 S. 54th Avenue, Chicago 50, Illinois.

RADOLEK CATALOGUE

Of interest to radio servicemen, amateurs, experimenters, and engineers is the announcement of the new enlarged 64 page catalogue just published by *The Radolek Company*.

This catalogue contains many new items that have only recently become available. These include merchandise that was discontinued during the war plus a complete showing of all the standard parts and supplies essential to those engaged in the electronic and radio service fields.

A free copy of this buying guide may be obtained by sending your name and address to *The Radolek Company*, 601 W. Randolph Street, Chicago 6, Illinois.

EQUIPMENT HOUSINGS

Par-Metal Products Corp. have announced the release of a new catalogue listing various housings for electronic equipment.

This catalogue presents a complete description of cabinets, chassis, panels, racks, and accessories as applied to electronic apparatus.

A copy of this catalogue may be obtained by writing to *Par-Metal Products Corp.*, 35-62 49th St., Long Island City 3, New York.

REPLACEMENT GUIDE

A new guide to phonograph crystal replacement entitled "RCA Crystal-Pickup Data Folder" has been released by the *RCA Tube Department*.

This folder shows the exact crystal replacement to use in the different models of *RCA Victor* phonographs. Outline diagrams of the crystal cartridges used in the pickup arms of all models of the company's phonographs are also shown. The diagrams show the shape, mounting holes, and other necessary information for easy installation of each cartridge. In addition, the folder contains two indexes. The first lists *RCA* phonographs by model number and shows the proper crystal replacement for each. The second lists the crystals by stock number and shows phonographs in which they may be used.

The "Magic Tone Cell" and the newly announced "Silent Sapphire Crystal Pickup" are also described in the folder, together with indexes showing how they may be used as "universal" replacements in many pickup arms. The "Magic Tone Cell" may be used for modernization of 69 different *RCA* radio-phonograph models. The "Silent Sapphire Crystal Pickup" is smaller in size and may be used to replace 70 different crystals used in a large variety of makes and models of phonographs produced by other manufacturers.

This guide is available to all radio servicemen and dealers through *RCA Parts Distributors*.

TRACERLOG

"Tracerlog," a booklet issued by *Tracerlab, Inc.*, contains articles of general interest to those working in the field of radio-activity for research or industrial control problems.

Featured in this booklet is the *Tracerlab* SU-3 Laboratory Monitor developed for use as a routine contamination monitor in radio-activity laboratories. The instrument comes completely equipped, including a thin end-windowed sensitive Geiger tube, enclosed in a detachable probe assembly and connected to the instrument by a flexible cable.

The SU-3 may be used for many applications including checking laboratory bench tops for contamination from very low energy Beta emitters such as the C-14 and S-35. It may also be used for checking laboratory glassware, fingertips, and lab coats for contamination, and monitoring of laboratory "background" counting rate to detect large scale fluctuations from various causes that might interfere with precise radioassays in progress.

The booklet is available, free of charge, from *Tracerlab, Inc.*, 55 Oliver Street, Boston 10, Massachusetts.

"MAGNETAPE" RECORDER DATA

A new circular covering the "Magnetape" Recorder manufactured by *Amplifier Corp. of America* has recently been released.

Uses, applications, and complete operation of this tape recorder are described in this circular. This recorder may be equipped with voice-activated, start-stop mechanism and an automatic repeat-reverse control for transcribing as optional built-in features. The reverse control allows the typist to reverse the machine without unthreading the tape.

A new feature of the "Magnetape" Recorder is the constant-speed drive whereby a synchronous motor is employed to drive the capstan pulley to keep the tape feeding

RADIO NEWS

MORT SAYS
"YOU DON'T HAVE TO BE CRAZY TO BE IN THE RADIO BUSINESS BUT IT SURE HELPS A LOT"


MEISSNER FM RECEPTOR



Covers complete FM band from 88-108 MC. Easily installed for quick conversion of any AM receiver. PA system, or phono-amplifier. Has 8 tubes—latest miniature design. 2 Volt output. Combination Volume Control and Line Switch. Comes in a handsome walnut cabinet. Swhg. wt. 8 lbs.


List Ea.\$57.50
 Net Ea. 38.33

RECORD PLAYER CASE

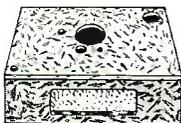

Simulated Leather Cover. 11"x13"x5". All holes punched. A real buy* Each **59c**

MINI VOLT METERS

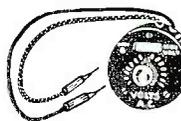


A rugged, simple meter of moderate accuracy — virtually burn-out proof. Calibrated for use on AC or DC 65 to 660 Volts. Impedance approximately 1/2 Megohm. List \$2.50 Each **\$1.50**

STEVENS CO-SPIRAL SPEAKER




15" high fidelity speaker with a reproducing range of 40 to 16,000 cps. Power handling capacity 15 watts. Input impedance 16 ohms. Alnico V magnet weight 2 1/2 lbs. Brings new listening pleasure to all types of high fidelity equipment. List \$80.00 Net, Each **47.04**

2 TUBE WIRELESS PHONO OSCILLATOR

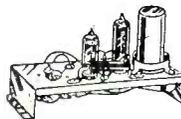

This fine piece of equipment is being sold at almost the price of the tubes alone. A real bargain while quantity lasts. Each **\$3.25**

VACO KITS

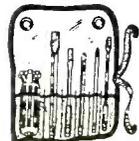

No tool rack is complete without these handy kits. Vaco K-5 Bench Set. Available in Screw Drive or Wrench Socket Set. Vaco S-6 Nut Driver Kit Each **\$2.21**

YEP! WE'RE SO CRAZY WE'RE GIVING STUFF AWAY FREE!!!



brings you this dandy box absolutely free.

Free with every order of \$10.00 or more—this handy, sturdy steel parts box ideal for storing those small easily lost parts. Box measures 7 1/4" L. x 6 1/4" W. x 4 1/4" D. Remember your order for \$10.00 or more absolutely free.


ALL NEW FULLY GUARANTEED STANDARD BRAND TUBES

35Z5	50c	3Z6	59c
12A6	29c	50L6	59c
50B5	59c	1L0C	97c
25L6	59c	1LN5	97c
6K7	60c	1H5	59c
117Z6	75c	1A7	59c
117L7	98c	50A5	75c
1N5	59c	12SQ7	59c
12K7	59c	35L6	59c
70L7	98c	35W4	45c
VT52	49c	024	79c
7N7	50c	6N7	85c
		12BE6	59c

INSULATED WIRE

1000 feet of live rubber insulated lead-in wire. Per 1000 ft. **\$1.95**

CHASSIS RACK

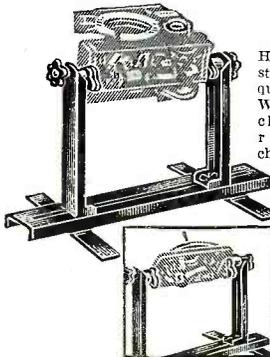

Heavily constructed of quality steel. Will fit any chassis or record changer.

Easily adjustable to any size Grey Crackle Finish. Each **\$3.95**

6 TUBE DETROLA PHONO COMBINATION AC CHASSIS

Complete with tubes, speaker, and aerial. Completely wired. \$60 value. Each **\$14.95**



6 TUBE DETROLA AC-DC CHASSIS

Complete with tubes, speaker, and built-in antenna. Completely wired. Each **\$9.95**

"ULTRA MIKE" WIRELESS MICROPHONE

Light — Economical operation. Completely self contained. No connections to power lines. Complete with batteries, tubes, etc. Retails at \$18.00 Your price Each **\$6.63**



G. E. VARIABLE RELUCTANCE CARTRIDGE


A wonderful new magnetic cartridge that provides excellent high fidelity reproduction. Practically eliminates needle noise. Fits almost any pickup. Requires preamplifier.



List Each\$7.95
 Each **4.67**


PREAMPLIFIER FOR G. E. VARIABLE RELUCTANCE CARTRIDGE

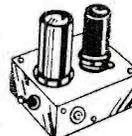3 1/2"x3 3/4"x1 1/4". Increases output, and equalizes cartridge for flat response. Attaches easily. Complete with tube and diagram. List, each\$9.00
 Net, each 4.82



METAL CAN AEROVAX REPLACEMENT FILTER CONDENSERS

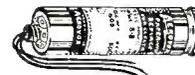Replaces 8x8 at 600 working volts. DC test volt 800. Each\$ 1.29
 10 for 11.75



IRON CLAMP VISE

1 1/2" Grip. Precision made. Holds with firm rigid grip. No wobbling or loosening of jaws. A regular \$3.00 value at the amazingly low price of only **99c**



25 POUNDS OF RADIO PARTS INCLUDING PHONO PICKUP ARM, Transformers, Condensers, Hardware, Etc. 25 pound assortment of highly useful radio parts. Only **\$2.95**

Write for our new, FREE 1948 Catalog . . . Terms: 25% Deposit with order . . . Balance C.O.D. F.O.B. Chicago.

Mort's Radio Shack
 630 W. RANDOLPH STREET
 CHICAGO 6, ILL.


PREMAX FM-130 "Highly Satisfactory"

Says FM Broadcast Station . . .

Eliminates Noise In Reception. Low Cost
V Dipole Type Proving Popular In Installations

A Chief Engineer reports: "... set up several unfavorable locations where man-made electrical noises abounded, and we found that the 3d dimensional adjustment in the dipole arms helped considerably to reduce noises..."

Premax V Dipole Antennas are designed to permit adjustment of the angle for strongest reception and, when the proper vertical or horizontal adjustments are made the "direct" and "reflected" signals combine in phase, thereby increasing the received signal. This type of Antenna will insure proper reception of FM Signals and is being adopted by dealers and service men who have been seeking some way to counteract man-made electrical noise in receiving sets.

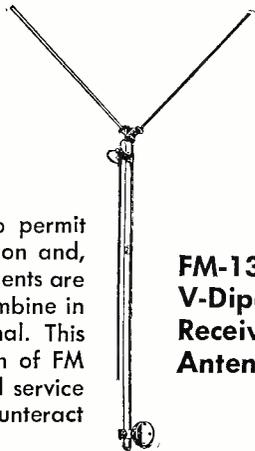

**FM-130
V-Dipole
Receiving
Antenna**

Write for special Bulletin FMT-148, telling why an Adjustable V Antenna is best for FM and TV.

Premax Products

Div. Chisholm-Ryder Co., Inc.
 4813 Highland Ave. Niagara Falls, N. Y.

RADIO TUBES

For immediate shipment
 R.M.A. Guaranteed
 Below Distributor Costs
 Individually Sealed Cartons

Type	Price
6K6GT	.40
6K5GT	.46
6V6GT	.46
6SA7GT	.46
6SJ7GT	.46
6SK7GT	.46
6SQ7GT	.46
6X5GT	.40
12SA7GT	.46
12SQ7GT	.46
12SK7GT	.46
12SJ7GT	.46
35L6GT	.40
35Z5GT	.32
50L6GT	.46

25% DEPOSIT REQUIRED ON C.O.D.
 10% DISCOUNT ON LOTS OF 50 OR MORE
 2% C.O.D.

RAVAC ELECTRONICS CORP.

432-4th Avenue
 New York 16, N. Y.

SAVE at R. P. D.

Close Out Materials

SPECIALS IN TUBES — BULK PACK

5U4G	ea. 45c	Lots of 10	\$3.50
6SN7GT	ea. 60c	Lots of 10	5.50
6L6G	ea. 79c	Lots of 10	6.90
Thordarson Choke T74	(29 15 Hy 150 Ma		
200 Ohm DC upright intg.		Each	\$1.97
Jefferson Elect. Sealed Filter Choke 40			
Ma 20 Hy Size 2x2 1/2x2 3/4		Each	.79

FRACTIONAL MOTORS

Compound Wound 115 V DC 3/16 H.P. Input
 115 V DC—3/16 H.P. 2 amp. (18 Pds)
 3450 R.P.M. Oil Impregnated Ball Bearings. Each \$3.69; 4 to case \$14.00

3" Triplet 0-500 DC Micro ampere meters. Special each	\$4.69
3" Triplet 0-1 DC Ma Meters, Each	3.39

Centralab 500,000 K Control No. 1 taper. 1/2" Shaft, ea. 19c; 10 for	\$1.50
Little fuse 3AG—2 amp 250 Volt fuses. 50 for \$1.00; 100 for	1.50
3AG—10 amp 250 Volt fuses. 50 for \$3.00; 100 for	5.00
Buss Fuse Holders for 3AG Fuses, Each 15c; 10 for	1.25
Bathub Cond. 1.0 mfd 100 Volt. Each 9c; Lots of 25	1.25
5000 Ohm Controls with Switch. Each 35c; Lots of 10	3.00

HARDWARE

Asst. Screws, nuts, washers, rivets, solder lugs, springs and 1000 other useful parts. 5 pounds for	\$1.49
G.E. Pyronol Capacitors 23F47-2 mfd 4000 V D.C. Each	\$4.79
Amphenal 2 Pole Receptacle MIP61F. Each 10c; Lots of 25	2.00
Amphenal 2 Pole Plug 61M4. Each 12c; Lots of 25	2.50
Pickup Arms Astatic D9 with L26 Cartridge. Each \$2.29; 5 for	9.85
Tobe Filterite 4 Prong Plug in Type 8-8 mfd 600 Volt. Each	89c
Slide Switches DPDT. Each 18c; Lots of 100	\$15.00

FREE! Write for R.P.D.'s latest bulletin for more sensational values.

Terms: Remittance with order PLUS POSTAGE or 25% deposit, balance C.O.D.

RADIO PARTS DISTRIBUTORS
 925 E. 55th St., Chicago 15, Ill.

at an unvarying speed. Three-separate motors are used in these machines.

Additional information on these recorders may be obtained by writing to *Amplifier Corp. of America*, 396-398 Broadway, New York 13, New York.

NEW VARIAC LINE

General Radio Company has just released a new folder covering the company's line of "Variacs."

This bulletin describes several new models and introduces the V-10 series. This is a new intermediate size with a load rating of 1.725 kva. on 115 volt lines and 1.15 kva. on 230 volt lines. The 115 volt models of the V-10 are rated at 10 amperes with a 15 ampere maximum. This maximum rating coincides with the capacity of outlets, plugs, cords and No. 14 wire circuits ordinarily found in the laboratory and in the home.

Further information on these "Variacs" may be obtained by writing to *General Radio Company*, 275 Massachusetts Avenue, Cambridge 39, Mass. for a copy of the new folder.

1948 FEDERALOG

Federal Electric Products Company, has just released the latest edition of the "Federalog." This catalogue contains information on the complete *Federal* line.

Featured in the catalogue are the company's newest motor controls, safety switches, service equipment, circuit breakers, panelboards, switchboards, and bus duct.

Copies of this catalogue may be obtained by writing to *Federal Electric Products Company*, 50 Paris Street, Newark 5, New Jersey.

NEW AM-FM LINE

Radio Wire Television Inc., has just issued a flyer featuring FM and AM radio sets in the low-price field. Also featured is a low-cost FM-AM tuner with an automatic frequency control circuit (a radar development) to keep FM at optimum tuning without manual readjustment.

For the serviceman, ham, and hobbyist, there are hundreds of replacement parts, sets, and kits ranging from standard resistors and capacitors to NBFM and television components. Space is also devoted to a complete line of amplifiers and accessories with power capacities ranging from 1 to 75 watts.

Television kits incorporating large size picture tubes are available as well as a new adjustable magnifier lens that triples the area of 7" pictures. For the devotee of high quality, combination-type 15" speakers, magnetic pickups, and console FM-AM installation are given substantial coverage.

This flyer, C-41, is free upon request by writing to *Radio Wire Television Inc.*, 100 Sixth Avenue, New York, New York.

PRECISION INSTRUMENTS

A new catalogue compiled by *Associated Research, Incorporated* has recently been released containing a wide range of precision instruments for industry and utility.

In this catalogue is information and engineering data on insulation and ground resistance testing, and insulation breakdown testing.

Other instruments shown include ohmmeters, ammeters, soil resistivity meters, limits bridges, transformers, and tachometers. The Keeler Polygraph (known as the "Lie Detector") is also described and engineering service representatives are listed.

Associated Research, Incorporated, 231 S. Green Street, Chicago 7, Ill. will furnish a copy of the catalogue upon request.

INSTRUMENTS CATALOGUE






Electro-Tech Equipment Company has

RADIO NEWS

NOW

is your OPPORTUNITY TO BUY TUBES

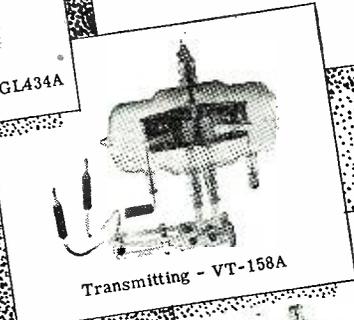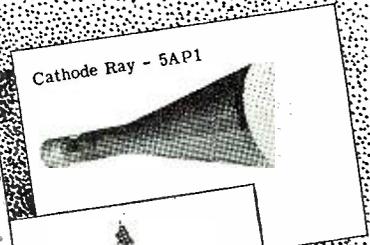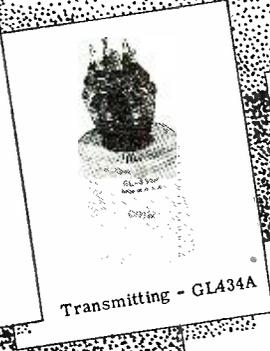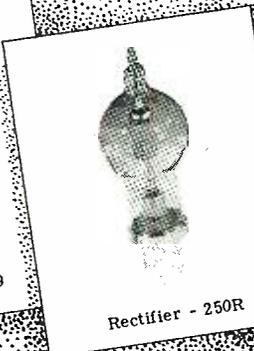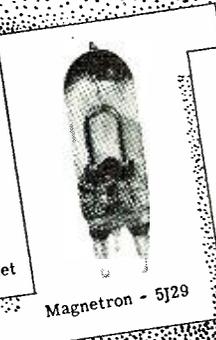at *Ridiculously Low Prices*
Transmitting - Special Purpose
 Every tube is *Brand New* in original unbroken factory package



Magnetrons		Klystrons	
2J22	\$ 15.00	417A	\$9.80
2J38 w/magnet	15.95	723A/B	3.95
2J48	15.95	726A	4.75
4J26	15.95		
5J23	15.95		
5J29	15.95		
714AY	9.80		
725A	12.50		
Cathode Ray		Rectifiers	
3CP1/S1	\$.95	CRP-72	\$2.95
5AP1	2.49	250R	4.95
5JP2	3.95	WL531	29.95
12GP7	12.50	866A/86698
		WL869B	29.95
		1641/RK6069
Receiving			
VT-25A	(Special 10)		.69
VT-52	(Special 45)		.69
6J6	Twin Triode69
717A	(6AK5 w/octal base)		.98
9002	Miniature UHF Triode		.95
Special Purpose			
1B24	T-R Tube		2.95
724B	Spark Gap Tube		1.95
2051	Thyratron49
"	" (in lots of 100) ea		.35
VR-150	Voltage Regulator69
6AMP	Tungar Rectifier		3.00

Transmitting	
5D21	Tetrode 9.95
15E	UHF Triode 2.95
24G	UHF Triode . Plate Diss. 25W . 2000V at 75 ma good up to 300 Mc.69
VT-158A	UHF Triode with Tuned Circuits Built-in 4.90
388A	Door Knob Triode 4.95
GL434A	Lighthouse 7.95
GL446A	Lighthouse(2C40)74
WL530	Water Cooled Triode 39.50
715B	Tetrode 9.95
804	Pentode 3.75
807	Beam Power Tetrode 1.19
813	Beam Power Tetrode 6.95
829	Beam Power Tetrode 2.95
841	Triode69
1625	Beam Power Tetrode49
1626	Low Drift Osc. Triode49
7193	UHF Triode39
8011	(VT-90) Micro-Pup98

TERMS - Orders under \$3.00, cash with order; orders over \$3.00 require 20% deposit, balance C.O.D.
 ALL PRICES ARE NET,
 F.O.B. DAYTON, O.

Everything in Electronics


STANDARD RADIO & ELECTRONIC PRODUCTS CO.
 136 E. SECOND ST. DAYTON 2, OHIO.

Don't Delay - Order Today!

New! New!

CHIMNEY MOUNT ANTENNA BASE

- for TELEVISION
- FM • AMATEURS

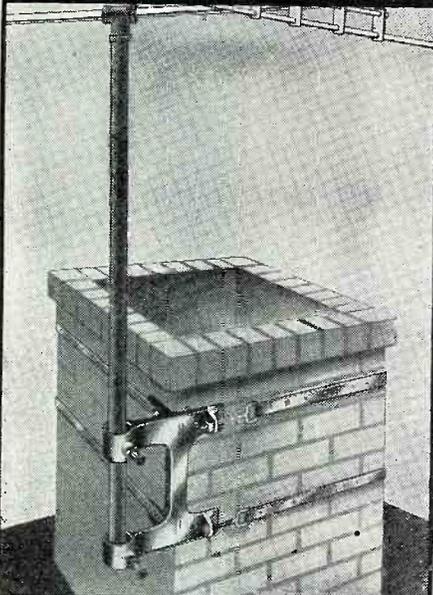

**INSTALLED IN 10 MINUTES
PERMITS USE OF SEVERAL
MOUNTS ON ONE CHIMNEY**

"Chimney Mount" is a brilliantly engineered new antenna base that can be installed in 10 minutes without the use of special tools or drilling of holes. Several can be strapped to one chimney—also mounts on pole, 2 x 4, side of house or to any rectangular roof extension. Fastens aerial to highest point with galvanized steel bands having a combined tensile strength of more than 3,000 pounds. Made of corrosion-resistant aircraft-type aluminum alloy. Weight: 3 lbs.

"Chimney Mount"

List Price, \$7.50

Cost to Trade, \$4.50

Pat.

Pending

Available Through All Leading
Jobbers or Write to:

South River Metal Products Co.

South River, New Jersey

made available a 66 page catalogue containing a comprehensive coverage of all standard makes of instruments and controls.

In addition to its illustrations, this catalogue also gives data, specifications, and prices on a vast number of items needed by manufacturers and industry in general for control purposes. One page is given over to suggestions on the purchase and use of instruments together with charts illustrating conventional instrument connections.

Included in this book are tables and connection diagrams on rectifiers, variable voltage transformers, etc. There are also sections on portable and laboratory standard instruments, panel and switchboard meters, electrical and electronic service instruments, oscilloscopes, variable and constant voltage transformers, rectifiers, pyrometer and temperature controllers, rheostats, relays and miscellaneous measuring and control equipment. This catalogue can be obtained by writing to the *Electro-Tech Equipment Company*, 117 Lafayette Street, New York 13, New York.

ELECTRIC MICROMETER

Stevens-Arnold Inc. has released information on the Type 156 Electric Micrometer in their new catalogue sheet.

This electric micrometer is a dual purpose instrument. It can perform the usual measuring and gauging operations and it is also suitable for telemetering where remote indications of small movements are wanted.

The micrometer is arranged for battery operation and consists of a transmitter unit and a control unit together with connecting cable.

The transmitter is a sealed unit having a projection plunger which will accept motions of .010" from the center position, or .020" total in one direction. This mechanical motion is translated, inside the housing, into changes in electrical energy which are sent to the control unit.

Further information on this micrometer may be obtained from *Stevens-Arnold Inc.*, 22 Elkins Street, South Boston 27, Mass. Ask for catalogue sheet 227.

CARBON-GRAPHITE SPECIALTIES

The *Stackpole Carbon Company* has compiled a booklet on the numerous carbon and graphite specialties which they produce. Interesting engineering and production data are given in this 44 page booklet.

Of particular interest is a section devoted to analyzing the physical and electrical properties of carbon and graphite in relation to their applications over a broad industrial front.

Included among the many items discussed are tube anodes, battery carbons, ground rods, electrical contacts, carbon piles (voltage regulator discs), chemical carbons, trolley and pantograph shoes, water heater and pasteurization electrodes, seal rings, friction segments, clutch rings, bearing materials, brazing and welding carbon supplies, resistance welding tips, carbon molds and dies, spectrographite, and many others.

This booklet may be obtained free upon request by writing to the *Stackpole Carbon Company*, St. Marys, Pa., and asking for the "Stackpole Carbon Specialties Booklet" on your company letterhead.

—30—

360 Watt Transmitter


(Continued from page 71)

fier. Above at right is a variable coupling adjustment. In the center at the top is a circular lucite window for visual inspection of the tubes during operation. When properly loaded the 3D24's operate with dull red plates. The inspection window allows the operator to determine, by the color of the plates, when the tubes are properly balanced.


The transmitter is used with a 10 meter three-element beam of the "Plumbers' Delight" variety and on 20 meters with a half-wave horizontal dipole running in a north-south direction. During the first week of operation, WAC was worked on 10 and 20 meters c.w. Using NBFM on 10 and 20 meters, Europe, South America, Australia, and South Africa have been contacted. In all cases reports were as good as those received when operating the old standby transmitter which normally operates at 450 watts input both c.w. and phone.

—30—

Fig. 7. Looking down on the final amplifier. The two tubes peeking through are the 3D24's. The 807 buffer is in section shown with the cover off.

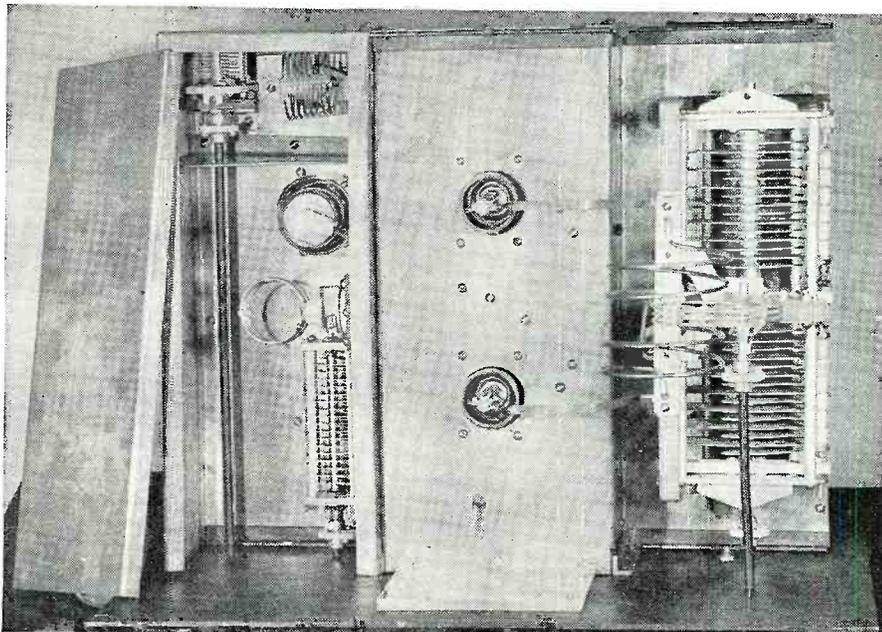

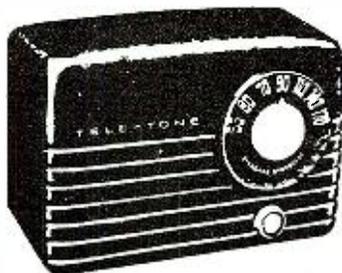IRVING JOSEPH—WHERE PRICE IS AN OBJECT AND QUALITY IS UNDERSTOOD—EVERY ITEM WE SHIP IS BACKED BY AN UNCONDITIONAL GUARANTEE



**NEW FOR 1948
NOT SINCE 1939**

A Full Powered
Superheterodyne Radio
TELE-TONE

Model No. 165—Styled for tomorrow . . . powered for sharp, clear, reception. A wondrously toned superhet circuit. In practically unbreakable plastic cabinet.

\$9.95

For Only

\$12.95

Amazing!

Here's the EXTRA Radio You Need For—Kitchen, Bedside Use, Playroom

MODEL 175

Same as 165 in ivory




**MODEL 159
5 TUBE AC-DC
TABLE MODEL**

Walnut **\$19.95**
Ivory **22.95**



**MODEL 166
5 TUBE SUPERHETERODYNE
WITH HANDLE**

Ivory only **\$16.95**

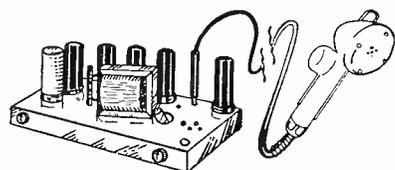

Each kit contains all necessary components, including 5 tubes, diagrams and pictorials, selenium rectifiers, resistors, condensers, etc., etc.

HI-FI UTILITY AMPLIFIER KIT PUT YOUR T-17-B (CARBON MIKE) TO WORK!!

Utility amplifier will take a lot of kicking around while giving you these important "big amplifier" features.

1. Voltage doubling circuit. Uses two 100 MA Selenium Rectifiers.
2. Full 6 Watt Power Output.
3. Hi-Fi response. 50-20,000 C.P.S.
4. Inverse feed back for finer quality.
5. Push pull balanced output. Heavy duty universal output transformer.
6. Uses most efficient beam power output tube available. (12A6) 12.6V—150 MA filament. Power output rated at 250V, 6W.
7. Bass Boost.
8. Excellent for use with phono, F. M. Tuner or Crystal mike.

Rugged simplicity, inexpensiveness and extreme versatility make this unit a must for every radio man, beginner or professional.

Complete Kit, less Mike and Speaker **\$9.50**

Same As Above, 3W output less voltage doubling circuit **\$6.50**

25 POUNDS OF RADIO PARTS AND ASSEMBLIES

We are swamped with tons of samples and odds and ends which cannot be placed in our regular stock. We must dispose of this useful merchandise immediately to give us elbow room. Buy 25 pounds of parts and assemblies at the ridiculously low price of

\$3.00

600V PAPER TUBULAR BY-PASS CONDENSERS

Wax impregnated. Mfg. by John E. East.

.001	12c
.002	12c
.005	12c
.01	12c
.02	12c
.05	15c
.1	18c

Freshness Guaranteed
BUFFER CONDENSERS

.005—2000V	20c ea.
.0075—2000V	20c ea.
.01—2000V	20c ea.



TRIMMER CONDENSER
275-550 mmfd. For broadcast band application.
10 for 80c

MICROAMMETER, 0-200

2" round. New. Ideal for field strength meter. Each **\$2.75**



Midget 1 Meg. Control
3/8" Dia. Shaft long enough for knob. 10 for **\$1.29**



PHONO MOTOR & TURNTABLE

Name brand—sells for much more. 75 R.P.M. Rim-driven. Self-starting induction motor. 115V—60 cycle. 9-inch turntable.
\$2.95

TUBES!!

No "off" brands, seconds or Used Tubes. Some in cartons. Return for refund if not satisfied.

1A550	6SA750	12SR760
1A760	6SG760	2750
1LC6	1.10	6SH760	35L660
1LH4	1.10	6SJ750	35W450
1LN5	1.10	6SK750	35Z560
1N560	6SL775	39/4450
1R575	6SN760	50B560
1S575	6SQ750	50L660
1T475	6SR750	7550
3Q575	6V660	7650
5U450	6X575	7750
5Y350	12AT650	7850
6AC7	1.10	12BA660	8050
6AG5	1.10	12BE660	84/62450
6C450	12J550	117L7	1.10
6C550	12SF750	95475
6H650	12SG760	95575
6J550	12S1750	95675
6J650	12SK760	900150
6K650	12SN750			
6S850	12SQ760			

Deduct 10% from all orders \$20.00 or over. Write for other receiving tube requirements.

TERMS

Minimum order \$2.00. All orders shipped f.o.b. Chicago. 25% deposit on all c.o.d. shipments.

GENERAL PURPOSE HOOK-UP WIRE

For all uses where a low loss dielectric is required. Every foot guaranteed to give you the best buy in wire. Buy it in hundred or hundred thousand foot lengths.

	Per C	Per M		Per C	Per M
No. 12 Stranded	\$1.15	No. 20 Choice of Sol. or Str.	\$0.65
No. 16 Stranded	7.50	No. 22 Choice of Sol. or Str.55
No. 18 Choice of Sol. or Str.75	No. 24 Solid45

Please Specify First and Second Choice of Colors

IRVING JOSEPH

220 S. Halsted St., Chicago 6, Ill.

For that better fist... **SPEED X**



Transmitting & Semi-Automatic Keys, Buzzers, Code Practice Sets

Because of their precision construction, Speed-X keys give you the most in smooth operation and ease of adjustment. It's the reason they are used throughout of the world as standard equipment in amateur and commercial service.

Speed-X semi-automatic keys possess a feature skilled operators value highly: full adjustment from lowest to highest speeds.


In addition to the units illustrated, the Speed-X line comprises 27 additional manual keys, practice sets and repair parts for all semi-automatic keys.



JOHNSON *a famous name in Radio!*
E. F. JOHNSON CO. WASECA, MINNESOTA

See Sped-X at your jobber or write Johnson for catalog and additional information.

ILLINOIS CONDENSER CO. NOW HAS UMP!

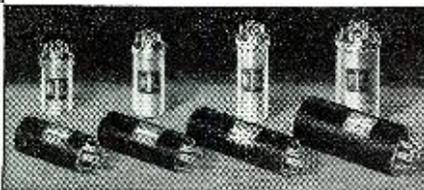

Type Ump

A popular replacement twist prong line of Compact, Hermetically Sealed, efficient, dry electrolytic condenser, is now a member of the ILLINI line of highest quality capacitors.

The "Illini" UMP capacitors are now available at your local jobber. Our latest catalog, listing complete Illinois line, will be mailed to you upon request.



ILLINOIS CONDENSER CO.
1610 NORTH THIRD STREET • CHICAGO 22, ILL.

BC 221 complete with xtal and calibration book	\$41.00
Co-ax RG8U (52 ohm) per ft. 6c.—per 100 ft.	5.50
RG30U (58 ohm) per ft. 6c.—per 100 ft.	5.50
RG30U 385 ft. in one roll, standard co-ax connectors on each end, new	17.50
BC 464 receiver and audio band pass selection for five channel control-Rcvr. 68 to 73 m.c.	11.80
BC 454 Command rcvr. 3-4 m.c., 3-6 megs or m.c.	6.50
BC 455 Command rcvr. 7-9.1 m.c.	6.75
24 volt Xfmr for above rcvrs or 459 series xmtr-1-amps	2.85
BC 696—Only a dozen left at	15.00
BC 375 Xmtr. with ant. tuner and one tuning unit	21.50
PE 73cm dynamotor for above—1000 v. at 300 mils	5.00
BC 929 Indicator—400 cy but works fb at 75 v. 60 cy.	12.00
APS 15 indicator—45 tubes, 7 6L6's 2" & 5" CRT	35.00
BC 456 Modulator (for 459 series)—buy a few at	1.55
BC 306 Antenna tuner for BC 375	1.75
APN 4-4 channel (abt 2 m.c.) rcvr.	14.50
BC 639-BC 636 VHF Rcvr. 100 to 156 megs, 110 v. 60 cy, standard rack mtg, directly calibrated dial, knob ratio 30 to 1-w/pwr sup on separate panel with tapped Xfmr for voltage regulation "S" meter, no modification required—beautiful, 10 tubes	75.00
Headphone, less headband, Utah, ANB H-1	.45
Power supply, 800 volts, 375 mils DC output, tapped at 485 volts, standard rack mtg, 220 volt 60 cycle input, single phase, 3 filament windings, complete with tubes—uses 4 5Z3's, filtered	22.50
Switches, toggle, dpst, dpdt. 30 amp capacity, each	.35
1/40 hp motor, reversible, 28 vde, w/gear for beam	2.75
Throat mikes, carbon, makes swell carbon mike	.20
BC 433G Compass, as advertised in April RN	30.00
Sealed beams, 28 volt, 5.3 a. or 6.6 a. either (new)	.50
28 volt light bulbs, 420 watts, new	.20
BC 357 Beacon receiver	4.80

Please refer to this ad as we are reserving sufficient quantities of these items to supply reasonable demand. All items are in good and usable condition and complete with tubes. Please enclose at least 20% deposit for C.O.D. orders. Minimum Order \$5.00.
S & S RADIO Rochelle, Georgia
Phones 403 and 5101 (nite)

The Inductuner (Continued from page 62)


the movement of the trolley to only a certain portion of the unit.

Now, it is entirely possible to attach a small condenser across each inductance and use the trolley to tune the coil over whatever range is desired. However, better results can be obtained if an end inductance having a high Q is connected to the "Inductuner" coil and this is employed to determine the highest frequency of the unit. See Fig. 3B. By the addition of this fixed coil, we can obtain a better Q characteristic than if the variable coil were run out to the limit in order to reach the highest frequency. By adding the coil, the trolley is run as far as it is desired to go, and whatever remains on the "Inductuner" unit plus the added end inductance gives the highest frequency of the tuning range. With proper design, it is possible to produce a rising Q with frequency, which is highly desirable in view of the poorer over-all performance of receivers at the high frequency end of the band.

The use of the "Inductuner" in Dumont television receivers is illustrated in Fig. 2. The input circuit leading to the antenna transmission line is an unbalanced arrangement with an impedance of 72 ohms. The signal is received in the cathode leg of the r.f. amplifier, because the tube is being operated as a grounded-grid amplifier with both triode sections connected in parallel. The signal output of the 6J6 r.f. amplifier is transferred to the mixer via the complex coupling network of L_1 , L_2a , C_1 , C_2 , C_3 , L_3 and L_2b . L_2a and L_2b are two sections of the three-section "Inductuner." L_1 and L_3 are end coils, inserted in series with the "Inductuner" windings for the reasons previously given. The third winding of the "Inductuner" is employed in the oscillator, together with an end coil, L_4 , a shunt coil, L_5 , and a shunt condenser, C_4 . The shunt coil is required because the oscillator frequency is higher than the incoming signal frequency by an amount equal to the i.f. The oscillator, incidentally, is one of the ultradion variety.

The variable trimmer condensers C_1 , C_2 , and C_3 permit adjustments to be made in order to adjust the coupling

Fig. 3. (A) Equivalent electrical circuit of the "Inductuner". (B) Adding an end coil to the "Inductuner" often provides better high frequency characteristics.

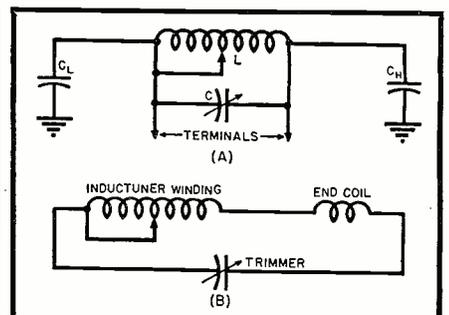

network for a 6.0 mc. bandpass. In the oscillator, C_4 is adjusted to permit the oscillator to track over the band. A photograph of the complete r.f. section of the receiver, assembled with the "Inductuner," is shown in Fig. 1.

-50-

Grid Dip Oscillator

(Continued from page 57)

series resistor. The tube is mounted on the outside for convenience, but could just as well be mounted inside the case, if the case is made correspondingly larger. The "penlite" cell is mounted on the inside of the side cover by means of two standard cartridge fuse clips. The paper covering is removed from the battery so that the clips form the ground connection. A wire is soldered to the positive terminal of the battery and connects to the push-button switch. Wires are also soldered to the terminals of the plate supply battery. These wires are left long enough to permit easy replacement of the battery when necessary. The life of the "penlite" filament battery and the "minimax" plate battery apparently will be very good, as the original batteries are still in good condition after over six months of use.

The coils used with this instrument are wound on forms obtained from war surplus supplies. These forms are $\frac{3}{4}$ " in diameter and $1\frac{5}{8}$ " long, with tapped holes in each end spaced $\frac{1}{2}$ " apart. They are ideal for this purpose. Any similar form may be used, and the plug-in mountings arranged accordingly. It is advisable to use a coil of similar proportions for this purpose, preferably not over 1" in diameter. The winding data for the coils used is included in the parts list.

When the instrument is finished, the coils may be easily calibrated with a receiver, using the grid dip oscillator as a heterodyne frequency meter. Care should be exercised when using a receiver having only one stage of r.f. amplification, lest the image be confused with the true frequency. Some receivers have very little image rejection to strong signals and errors may result. It is best to reduce the gain of the receiver until the "S" meter reading is approximately one-half of full scale reading, and be sure to record only the signal having the highest response when two or more responses are noted, close together in frequency.

Once having built a satisfactory grid dip oscillator, it will be found almost indispensable. It will enable you to properly adjust tuned circuits in a transmitter or receiver during construction instead of later. It will enable you to find spurious resonances in r.f. chokes and wiring that may otherwise be very difficult to locate. It is handy to carry up to the antenna for preliminary tuning of the elements without power from the transmitter. It is a handy heterodyne frequency meter for rough checking. If a snap switch is installed to disconnect the "B" battery,

May, 1948

LOOK! 3¢

**THAT'S ALL!
A POSTAGE STAMP
IS O. K.**

"Powerful Pete"

**POCKET SCREW DRIVER WITH
LUCKY 4-LEAF CLOVER DESIGN . . .**

**LIMIT
ONLY ONE
TO A
CUSTOMER**

OLSON practically gives away the slickest pocket piece you ever saw! A hardened steel tool, big as a half dollar, that fits four sizes of screws and drives them with amazing power! Engraved with four-leaf clover design! Sturdy key chain attached! Send OLSON a 3c stamp and get "Powerful Pete" pronto. Use the coupon below.

(THIS OFFER GOOD ONLY IN U.S.A.)

**Order your RADIO PARTS
from OLSON**

and get lightning Service!

Brother, you really get SERVICE from Olson! Our whirlwind electric Letter Opener opens 12,000 letters per hour. Our mailing system is geared for ACTION, so that every order we receive is shipped out the SAME DAY. And every order is handled ACCURATELY, too, so you get exactly what you want when you want it. Send the coupon below for our FREE Bargain Bulletin, and try OLSON next time you order Radio Parts and Equipment.

MAIL THIS COUPON TODAY!

OLSON RADIO WAREHOUSE, Inc.

73 E. MILL ST., DEPT. 120, AKRON, OHIO

I enclose 3¢. Send me one "Powerful Pete" Screw Driver with Key Chain, and the FREE Olson Bargain Bulletin.


NAME _____

ADDRESS _____

CITY _____


STATE _____

HARVEY for GOOD REPRODUCTION

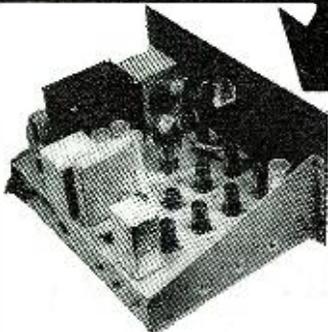

GOODELL DYNAMIC NOISE SUPPRESSOR AMPLIFIER

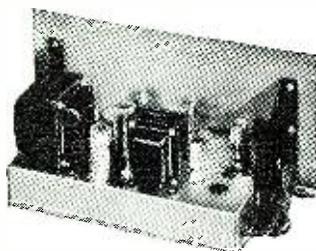18 watts with less than 2% harmonic distortion. Incorporates Scott noise suppression circuit; frequency range 20-20,000 cycles; 15 tubes; rack or cabinet mounting \$248.00



FISHER DYNAMIC NOISE SUPPRESSOR WIDE RANGE AMPLIFIER

20 watts with only 1% distortion. Uses Scott noise suppression circuit; frequency range 20-20,000 cycles; 8 & 16 ohms output, line matching transformer extra \$254.50

- GRAY Transcription Arm—for your favorite cartridge; has adjustment and scale for ideal operating conditions... \$35.00
- Vibromaster Type K Arm—for GE and Pickering Cartridges; flat resonance characteristic..... 34.50
- Livingston Arm—A good arm at an economical price 10.00
- GE Reluctance Cartridge—with sapphire needle 4.77
- GE Reluctance Cartridge with diamond needle 29.70
- GE Pre-amplifier to match GE Reluctance Cartridge to amplifiers not equipped with built-in pre-amplifier 5.95
- Pickering Cartridge gives professional quality, with sapphire needle (S120M) 15.00
- Pickering Cartridge with diamond needle (D120M) 39.75
- Pickering Equalizer-Amplifier 19.50
- Gray Equalizer Model 601, 42.50

All prices Net, F.O.B., N.Y.C.
Subject to Change Without Notice

Telephone: **TRC** LO. 3-1800

HARVEY RADIO COMPANY INC.

103 West 43rd St., New York 18, N. Y.

it will be a very sensitive absorption wavemeter. It will be useful in dozens of applications, with new ones coming to mind as the user becomes familiar with its operation and capabilities. In short, it will soon become one of those "I don't know how I got along without it" items, so build it carefully and you will be well rewarded for your trouble.

-50-

Pigeon Catcher

(Continued from page 50)

(F_1 and F_2) are shown in Fig. 9.

A phased array that has shown exceptional results is shown in schematic form in Fig. 8. This may well be called a twin-three or two colinear, three-element beam. A ten-meter version is the

same size as a twenty-meter, three-element beam of conventional design. The radiator is two half-waves in phase and each half-wave has its own reflector and director. The adjusting stubs may be arranged so that they come near the center of the support pole, and the shorting bars adjusted without recourse to a sky hook. Such a beam was once tried on the same pole that later held the "Pigeon Catcher." With only 18 watts input some rare DX was worked on 10-meter phone. We did not get a chance to try high power on the twin-three or lower power on the "Pigeon Catcher." Both are now torn down and we may never know which is the better.

Our sincere thanks go to Charles McLaughlin, W7FLY, for his help on our various antenna brainstorm.

-50-

A NOVEL TWO-TUBE "PICNIC PORTABLE"

By GLENN A. MARSH

MOST experimenters will have many of the parts needed to build this simple little set. By virtue of a loop antenna it is completely portable and in spite of the fact that it uses only two tubes gives plenty of loudspeaker volume on local stations. Even though a regenerative detector is used there is no hissing or howling, and the selectivity is as good as that of a superhet.

The circuit is shown in Fig. 1. The original model was built on a 6 x 4 inch chassis but almost any layout should work well. Hence the chassis should be chosen to fit into an available case or box. The only critical dimension was found to be the distance from the antenna loop to the chassis. Standoff insulators should support the antenna at least 1 1/4 inches away from the chassis.

The regeneration was found to depend upon the value of R_3 , and the value given (50,000 ohms) yielded the best results.

Two flashlight batteries in parallel


serve as the "A" supply, and a small 45 volt hearing aid battery may be used for the "B" battery. The "B" drain is only 6.5 ma.; with normal use the battery will last 60 to 80 hours. Ninety volts may be used as the "B" supply for stronger volume on weak and distant stations, if desired. It is also possible to increase the sensitivity by connecting a 20 foot wire to the grid terminal of the loop antenna, although this sacrifices the portability.

Notice that there are no coils to wind and nothing to align. In this sense this is probably the most easily constructed loudspeaker portable to be reported.

We are perhaps cheating a little by calling this a two tube set when actually one of the tubes, the 1D8GT, is used as a triode a.f. amplifier and as a power output pentode. Be that as it may, for sensitivity, selectivity and simple construction, this "picnic portable" will be hard to beat.

-30-

Fig. 1. Schematic diagram of two-tube portable receiver. Resistor, R_3 , is shown as a fixed unit. Since this is the regeneration control, it may be advisable to use a potentiometer instead. If a 90 volt "B" supply is used, it will be necessary to make some changes in component values. Condensers C_3 , C_4 , and C_5 should be 400 v. units. Condenser C_6 should be of 150 w.v. rating. The output transformer should then be matched at 12,000 ohms to voice coil.

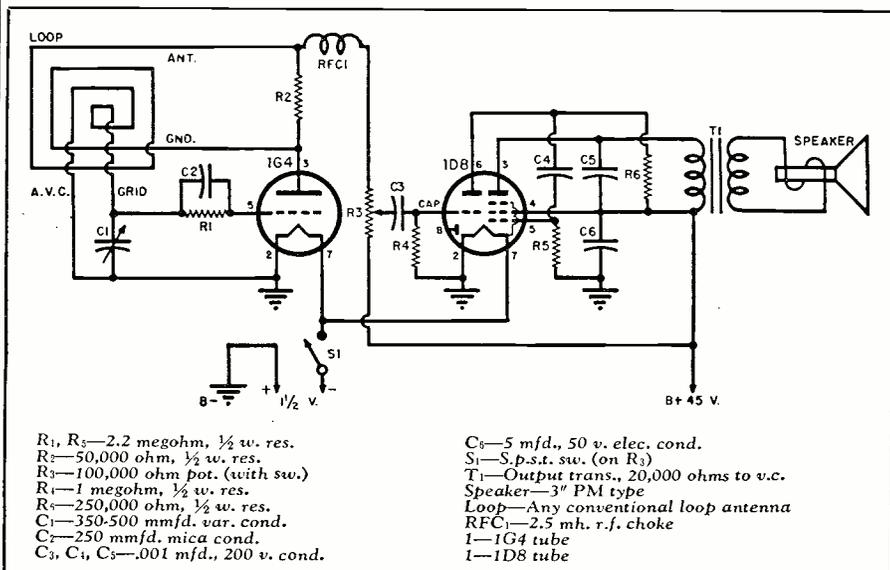

METERS WESTON #467
Whiteface
0.150 V.A.C.

\$3.25



TUBE TYPE
7193/2C22
29c each

5 for \$1

ATR INVERTER
Model RSA

Input 12 v DC—output 110 v 60 c. 125 w Int. 100 w Cont.
 Special **\$18.95**

SELENIUM RECTIFIERS

Full Wave Bridge Type

INPUT	OUTPUT		
up to 18v A.C.	up to 12v D.C.	1 Amp.	\$1.95
up to 18v A.C.	up to 12v D.C.	5 Amp.	4.45
up to 18v A.C.	up to 12v D.C.	10 Amp.	7.45
up to 18v A.C.	up to 12v D.C.	15 Amp.	9.95
up to 18v A.C.	up to 12v D.C.	30 Amp.	14.95
up to 36v A.C.	up to 28v D.C.	1 Amp.	3.45
up to 36v A.C.	up to 28v D.C.	5 Amp.	7.45
up to 36v A.C.	up to 28v D.C.	10 Amp.	12.45
up to 36v A.C.	up to 28v D.C.	15 Amp.	18.95
up to 54v A.C.	up to 36v D.C.	.25 Amp.	.98
up to 115v A.C.	up to 100v D.C.	.25 Amp.	2.95
up to 115v A.C.	up to 100v D.C.	.6 Amp.	6.95
up to 115v A.C.	up to 100v D.C.	5 Amp.	19.95

OIL CONDENSERS

NATIONALLY ADVERTISED BRANDS

All Ratings, D.C.

2X.1mf. 600v	.35	1mf. 2000v	.95
.25mf. 600v	.35	3mf. 2000v	2.75
.5mf. 600v	.35	4mf. 2000v	3.75
1mf. 600v	.35	15mf. 2000v	4.95
2mf. 600v	.35	2mf. 2500v	2.49
4mf. 600v	.60	1mf. 2500v	1.25
8mf. 600v	1.10	.25mf. 2500v	1.45
10mf. 600v	1.15	.5mf. 2500v	1.75
3X.1mf. 1000v	.45	.05mf. 3000v	1.95
.25mf. 1000v	.45	1mf. 3000v	2.25
1mf. 1000v	.60	.25mf. 3000v	2.65
2mf. 1000v	.70	.5mf. 3000v	2.85
4mf. 1000v	.90	1mf. 3000v	3.50
8mf. 1000v	1.95	12mf. 3000v	6.95
10mf. 1000v	2.10	2mf. 4000v	5.95
15mf. 1000v	2.25	1mf. 5000v	4.95
20mf. 1000v	2.95	1mf. 7000v	2.95
24mf. 1500v	6.95	2X.1mf. 7000v	3.25
.25mf. 2000v	1.05	3mf. 4000v	6.95
.5mf. 2000v	1.15	2mf. 3000v	3.45

HIGH CAPACITY CONDENSERS

2x3500 mfd.—25WVDC	\$3.45
1000 mfd.—15WVDC	.99
100 mfd.—50WVDC	.49
4x10 mfd.—400VDC	.89

CODE KEYSER TG-10

This practice Code Keyer contains a 7 tube 110 volt 60 cycle Amplifier plus an electric eye tube. It also contains a 110 volt 60 cycle motor which runs your code tape through at the rate of 5 to 25 words per minute. The amplifier would make an excellent P.A. system and the motor would turn a timetable very nicely.

NEW — \$24.95
 (Less Tubes)

R5/ARN-7 RADIO COMPASS RECEIVER

Three bands 200 to 1750 K.C. Complete with 17 tubes required. This set is ideal for conversion to home broadcast Receiver, addition to ham shack, etc. Reported sold for many times the price when brand new. A Receiver that would be hard to pick up at this price. Only **\$31.95 NEW** USED—**\$17.95**

BC 733

RECEIVER

A Western Electric 10 tube Receiver cover 100-120 Mc. Complete with 10 tubes, crystals, etc.

New **\$12.95**
 Used **\$ 7.95**

PERMALLOY SHIELDS

for CATHODE RAY TUBES

3" Shield	\$1.49
5" Shield	1.98

TUBES (Brand New)

Standard Brands

1N21	\$0.39	F-127A	22.50
2AF1	2.25	371B	\$5.95
2C40	1.19	450TH	39.95
2D21	.89	703A	7.95
2V8G	1.25	715B	7.95
2X2	.84	721A	4.35
3AP1	3.00	723A/B	23.50
3BP1	2.95	726A	23.50
3E29	2.95	801	1.49
3GP1	3.95	802	1.98
5BP4	4.95	803	8.95
5CP1	3.95	804	9.95
5JP1	11.95	805	4.95
5LP1	8.95	806	14.95
5R4GY	.98	807	1.15
5Y3	.41	808	2.95
6AB7	.99	809	1.50
6AC7	.99	810	5.95
6AG5	.99	811	1.95
6AG7	.99	812	3.15
6AJ5	.99	813	8.95
6AK5	.90	814	4.45
6AL5	.99	815	3.95
6AQ6	1.09	829-A-B	3.00
6AR6	1.29	832	2.25
6B4G	1.29	833A	39.50
6C4	.69	836	1.75
6C5	.49	837	2.50
6D4	.99	838	3.95
6F6	.89	861	69.50
6F6G	.59	866	.75
6J4	1.50	872A	2.50
6J5	.55	884	.98
6J6	.89	885	.98
6L6	1.23	902P1	8.45
6L7	.98	954	.75
6N7	1.02	955	.75
6SH7	.59	956	.75
6SL7	.89	957	.75
6SN7	.69	958	.75
6SR7	.89	959	.75
7A4/XXL	.81	1005	.69
7F7	1.25	1616	2.95
7L7	1.59	1619	.75
10Y	.98	1622	1.98
15E	1.50	1624	.90
HK24G	1.75	1625	.75
28D7	.98	1626	.75
30	.75	8001	6.49
35T/IG	3.50	8005	4.95
VR75	.99	8011	3.75
VR90	.75	8016	1.65
VR105	.75	8025A	4.95
VR150	.75	1654	1.98
100TH	12.95	9001	1.15
100TS	3.00	9002	.98
211	1.25	9003	.98
75T	2.95	9004	.98
250TH	17.50	9005	.98
257B	6.49	9006	.98
304TH	9.95	F-128A	75.00

GLIDE PATH RECEIVER R-89/ARN-5

Glide Path Receiver used in the Instrument Landing System covering the frequency range 332 to 335 mc; complete with the following tubes: 7-6A15, 1-12SR7, 2-12SN7, 1-28D7, and including three crystals 6497KC, 6522K.

Brand New **\$14.95**
 Used **\$ 9.95**

TRANSFORMERS—115 V 60 CYC.

HI-VOLTAGE INSULATION

3710v @ 10 ma.; 2x2½v @ 3A	\$9.95
2500v @ 15 ma.	6.50
2500v @ 4 ma.; 2½v @ 2A; 6.3v @ 1 amp.	9.95
2150v @ 15 ma.	7.50
1750v @ 4 ma.; 6.3v @ 3A	6.50
1700v @ 4 ma.; 6.3v @ 6A; 2½v @ 1.75A	8.50
1600v @ 4 ma.; 700v CT @ 150 ma.; 6.3v @ 9A	8.50
1600v @ 2 ma.; 6.3v @ 6A; 2½v @ 1.75A	8.50
1200v CT @ 400 ma.; 10v CT @ 10A	9.95
550-0-550 @ 150 ma.; 5v @ 3A; 2x6.3v @ 5A CT	7.95
525-0-525v @ 60 ma.; 925v @ 10 ma.; 2x5v @ 3A; 6.3v @ 3.6A; 6.3v @ 2A; 6.3v @ 1A	8.95
525v @ 35 ma.; 5v @ 35 ma.; 2½v @ 1.75A	1.98
520-0-520v @ 120 ma.; 5v @ 2A; 6.3v CT @ 5A	5.95
500-0-500v @ 25 ma.; 262-0-262v @ 55 ma.; 6.3v @ 1A; 2x5v @ 2A	4.49
500-0-500v @ 100 ma.; 5v CT @ 3A	4.95
400-315-0-100-315 @ 200 ma.; 2.5v @ 2A, 5v @ 3A; 6.3v @ 9A; 6.3v @ 9A	7.50
400-230-0-230-400v @ 250 ma.; 3x5v @ 3A; 6.3v @ 5A; 6.3v @ 3A; 6.3v @ 1A	7.95
400-0-400v @ 200 ma.; 5v @ 3A	4.95
375-0-375v @ 400 ma.	4.95
350-0-350v @ 150 ma.; 5v @ 3A; 6.3v @ 6A; 78v @ 1A	4.95
350-0-350v @ 45 ma.; 675v @ 5 ma.; 2½v @ 2A; 2x6.3v @ 1A; 6.3v @ 2½A	4.95
350-0-350v @ 80 ma.; 6.3v @ .6A; 6.3v @ 3.75A; 2x5v @ 3A	3.98
385-0-385-550 @ 200 ma.; 2½v @ 2A; 5v @ 3A; 3x6.3v @ 6A—PRI. 110/220	9.95
350-0-350v @ 150 ma.; 5v @ 3A; 6.3v @ 7.5A; 6.3v @ 3A	5.95
350-0-350v @ 35 ma.	1.49
340-0-340v @ 300 ma.; 1540v @ 5 ma.	7.50
335-0-335 @ 60 ma.; 5v @ 3A; 6.3v @ 2A; 0-13-17-21-23v @ 70 ma.—PRI. 110/220	5.49
325-0-325v @ 120 ma.; 10v @ 5A; 5v @ 7A	3.49
300-0-300v @ 65 ma.; 2x5v @ 2A; 6.3v @ 2½A; 6.3v @ 1A	3.49
250-0-250v @ 100 ma.; 2x6.3v @ 4A; 6.3v @ 5A; 6.3v @ 1A	4.95
200-0-200v @ 140 ma.; 6.3v @ 4A; 5v @ 2A	3.98
120-0-120v @ 50 ma.	1.50
24v @ 6A	9.95
3x10.3 @ 7A; CT	3.50
6.3v @ 10A; 6.3v @ 1A	3.95
6.3v @ 1A; 2½v @ 2A	3.95
6.3v @ 2½A; 6.3v @ 2A; 2½v @ 2A	6.95
6.3v @ .25A; 6.3v @ 3A; 5v @ 12A; 6.3v CT @ 9A	4.95
5v CT @ 16A	\$3.49
5v-190A	17.50
5v-115A	14.95
220v to 110v @ .75 kv.	2.98
6.3v CT @ 3A; 5v CT @ 4A	4.25

FILTER CHOKES

HI-VOLTAGE INSULATION

10 hy @ 400ma.	\$4.95	10 hy @ 250ma.	\$2.49
8 hy @ 300ma.	3.95	10 hy @ 200ma.	1.98
25 hy @ 160ma.	3.49	10/20 @ 85ma.	1.59
12 hy @ 150ma.	2.25	15 hy @ 125ma.	1.49
12 hy @ 100ma.	1.39	15 hy @ 100ma.	1.39
30 hy @ 70ma.	1.39	3 hy @ 50ma.	.29
120 hy Dual @ 17ma.	1.39	30 hy Dual @ 20ma.	1.49
.1 hy @ 5 amps.	6.95	10/20 hy @ 85ma.	1.49
.4 hy @ 600ma.	5.95	10 hy @ 100ma.	1.29

ATTENTION!

INDUSTRIALS — LABS — SCHOOLS — AMATEURS

Let us quote on components and equipment that you require. We have too many items to be listed on this page. Place your name on our mailing list now for new catalog.

ALL PRICES SUBJECT TO CHANGE WITHOUT NOTICE


All merchandise guaranteed. Mail orders promptly filled.
 All prices F.O.B. New York City. Send money order or check.
 Shipping charges sent C.O.D. Minimum order \$5.00.

20% DEPOSIT REQUIRED WITH ALL ORDERS

RADIO HAM SHACK Inc.
63 DEY STREET • NEW YORK 7, N. Y.

WE ER SOLDERING GUN

Time Saving-Money Making Features

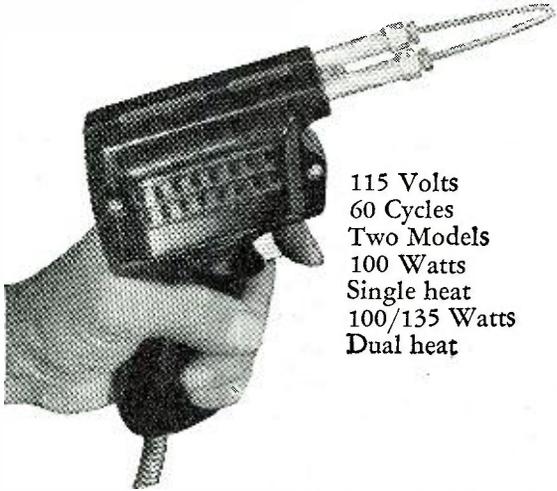

115 Volts
60 Cycles
Two Models
100 Watts
Single heat
100/135 Watts
Dual heat

See your radio parts distributor or electrical wholesaler. Or write direct for bulletin.

WELLER Mfg. Co.
810 Packer St. • Easton, Pa.

5 SECOND HEATING

ADJUSTABLE TIP

BUILT-IN SPOTLIGHT

LONG REACH

DUAL HEAT

International Short-Wave (Continued from page 72)

missionaries on the staff in Quito as well as many Ecuadorian workers. In the United States there are some 15 additional workers—either on furlough or soon to come to Ecuador for the first time.

Languages have increased from the original Spanish and Quechua (the most cultured of all the linguistic stocks of South America, which at one time was spoken by an unbroken chain of tribes for nearly two thousand miles from north to south), to the 18 languages now employed (with others to be added soon).

"We are at present looking for new property since we are badly crowded in our present location," Mr. Howard explains. "It is our hope to be able to increase our power so as to get out even better. Rotary beam antennas are used on all short-wave frequencies although only the 15.115 and 12.455 antennas are regularly turned. We also operate a surplus Army SCR-299 radio bus with public address equipment, transmitter, receivers, and a 10-kw. portable power unit. This makes possible many types of remote broadcasts and special events, as well as publicity work.

Since HCJB is missionary-operated and owned, programs given the greatest emphasis are naturally religious ones. Many of the best known Gospel programs from the United States are carried—such as "The Old Fashioned Revival Hour", "Haven of Rest", "Young People's Church of the Air", "Lutheran Hour", "Back to the Bible", "Radio Bible Class", "Miracles and Melodies", "Word of Life Hour", and many others. More than 700 Gospel programs are aired monthly.

HCJB is also the Quito outlet of the *Cadena Panamericana* of the National Broadcasting Company (USA), and as such has carried hundreds of rebroadcasts of Spanish programs from New York. Particularly during World War II, many "Goodwill" programs are rebroadcast.

Although religious programs take pre-eminence, many cultural and educational programs are presented as well.

The fact that HCJB broadcasts are heard well around the world is proved by the thousands of letters which reach the station from listeners in practically every corner of the universe.

"Quito is a city of some 220,000 people," Mr. Howard points out, "and is located at an elevation of some 9500 feet in the heart of the Andes mountains, about 12 miles south of the equator. On a clear day one can see some seven snow-capped peaks from the city, really a wonderful sight to behold. The

RADIO NEWS

MORE FEATURES for your money in this miniature

AM SUPERHET TUNER

with self-contained Power Supply
by "Adaptol"

Adaptol offers the outstanding buy in compact efficient AM Superhet Tuners (540 to 1700 KC) Here are just a few of the useful applications:— Highly suitable for use in conjunction with wire and tape recorders . . . Installed in record player makes phono-radio combination . . . Has many experimental uses . . . Tuner for custom-built radios . . . For modernizing obsolete radios and PA systems . . . For conversion of military, foreign, and short wave receivers to broadcast band at flick of a switch

CIRCUIT FEATURES:—Self-contained power supply for 110V. AC-DC 50-60 cycles . . . Three tube circuit of conventional design, using the latest miniature and dual purpose tubes. . . Permeability tuned drift-free I.F.'s. **COMPACT:** Approximately 4 1/2" x 3 1/2" x 3 3/4"

List price \$20.00 complete with tubes. Add 5% west of Rockies. FOB Brooklyn, N. Y. See your local distributor, or write for further information to:

ADAPTOL CO., 120 New Lots Ave., Brooklyn, N. Y.

SCOOP SCHUH DOES IT AGAIN!

NARROW BAND F. M. Noise Free Reception!

Only adapter for BC-348 receiver using 915 KC IF. Also made in 495-465 KC Model 3 1/2" x 4 1/2" x 1 1/2". Completely Chromium Plated. Easily mounted. Uses 6AK5 limiter and 6AL5 discriminator. Instructions supplied. Price

(less tubes) **\$10.95**
6AL5 tubes.....90c each
6AK5 tubes.....90c each

Trade in your AM modulator on Sonar NBFM equipment. Liberal Allowance.
BC 610 Components . . . Modulator Decks Less modulation transformer. Completely wired. **\$14.95**

RA20 Powerpack converts BC312 receiver to AC operation. Fits in dynamotor compartment. Also for external use with BC348, 314, 224, and used with BC696 and 459 as ECO. Input 110-120 VAC, 60 cycles. Output 250 VDC @ .95 MA, 12V @ .6 A, 12V CT @ .3A.
Shipping weight, 12 lbs. **\$7.95**
5W4 rectifier tube.....**.75**
5PB4 White screen 5" Cathode Ray tube suitable for Television sets..... **4.50**
250TL tubes. Limited Quantity..... **12.95**
2X2 Tube..... **.70**
2500 Volt Scope transformer—Pri. 117V Sec. 2500V @ .01 amp. **2.50**
11 Hy. 1600 amp. Chokes..... **7.95**

800 Volt Power Supply Kit
All electrical components for 800VDC @ 200 amp with 117VAC 60 cycle input. 150 amp when used on 25 cycles. 2 Power transformers 800 volts each to be used in series — 2 — 6U4 tubes and sockets. 2 — 10 mid condensors and 1 — 8 Hy choke. 10x17x3" chassis **\$14.25**

Swap your old receiver for a NEW NATIONAL
Let us know which model you want. Send us your old equipment prepaid and we will thoroughly inspect it and let you know how little it will cost you to own the National Receiver of your choice. Open 5 Evenings and Saturday Afternoons!
TERMS: 30% with order. Balance C.O.D. Shipt. F.O.B. Chicago

SCHUH'S RADIO PARTS

1253 Loyola Avenue • Chicago 26, Illinois

weather is just about ideal, with the temperature averaging 60 to 65 degrees F. every day of the year. Corresponding to winter in the United States, we have our rainy season when it usually rains in the afternoon but is sunny and nice in the morning. Corresponding to summer in the States, we have a dry season when it seldom rains at all. Quito has often been called 'the land of Eternal Spring,' and Ecuador is often termed 'the Switzerland of South America'.

"Our relationship with the Ecuador Government has been very cordial through the years," Mr. Howard continues, "and they have often gone out of their way to help us. During the past Christmas season when HCJB observed its 16th anniversary, a decoration was received from the Ecuador Government in recognition of the service the station has rendered to the country. This was a decoration of Merit of the *Order of Caballeros*, the highest honor that can be given to an organization of this kind."

Languages used by HCJB include Arabic, Bohemian, Czech, Dutch, *English*, French, German, Greek, Italian, Latvian, Lithuanian, Portuguese, Quechua, Russian, Spanish, Swedish, Urdu, Yiddish, with more languages to be added soon.

Frequencies now in use include 974 kcs. (308 m.), 1 kw.; 5.995 (50 m.), 1 kw.; 9.958 (30 m.), 1 kw.; 12.455 (24 m.), 10 kw., and 15.115 (19 m.), 1 kw. The 15.115 and 12.455 antennas are beamed on (1) London, (2) Omaha, Nebraska, (3) California, and (4) Brazil. The 9.958 and 5.995 outlets are fixed on Omaha, Nebraska. Usually, two or more frequencies are used in parallel.

Normal daily (*Tuesday through Saturday*) schedule is 0530-0900*, 1130-1330, 1600-0000; Sundays, the same and also 1430-1600; on Mondays the station is on *only* 0000-0100, which period is also carried on Wednesdays, Thursdays, Fridays (extends to 0115), Saturdays, and Sundays.

English periods are 0630-0800 (daily), 1630-1700 (Saturdays), 1700-1800 (daily), 2100-2200 (daily), 2200-2230 (daily), 2230-2300 (daily), and 2300-0030 (daily); "daily" means *except* Mondays.

HCJB verifies and is glad to receive reports from listeners anywhere in the world. Quito address is P.O. Box 691; offices are maintained at 156 Fifth Avenue, New York 10, New York, USA. It is operated by the World Radio Missionary Fellowship, incorporated in the state of Ohio, USA, in 1931.

As we take our leave of HCJB, *pioneer missionary voice*, we quote this paragraph from "Radio — The New Missionary" (Moody Press, Chicago), by Clarence W.

* (Note: Unless otherwise stated, time herein is expressed in American EST on a 24-hour clock basis; add 5 hours for GCT. "News" means in the *English* language.)


May, 1948



Your dollar buys more at MID-AMERICA!

VALUES! VALUES! VALUES!

PERMEABILITY TUNER

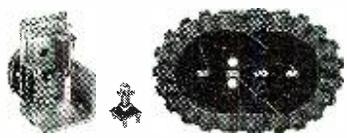

Build a really HOT 5 or 6 tube AC-DC superhet receiver! Takes place of old-style gang condenser, rf and antenna coils; regular 455 KC intermediate frequency. Complete with permeability tuned oscillator coil. 4" x 2 1/2" x 2 1/2" diameter dial drum. Order MA-2169 Loop Antenna 15c; and MA-2914 drilled, punched Chassis 39c. MA-2167 \$1.24

FM and HAM ANTENNA




AN-104-B. 1/2-wave at 100-150 MC; formerly used with SCR-522, 274-N, ARC-5. A pair make an excellent broad-band dipole for FM reception. Coaxial connector in base. Very sturdy; use anywhere. MA-2153. 39c

Stromberg-Carlson DYNATENNA EXCLUSIVE FEATURES! Brilliant Performance!

This famous-make FM antenna has been advertised and sold for many times the low price MID-AMERICA asks. Dynatenna covers both FM bands . . . delivers FM reception at its best. Complete with 60 feet of 300-ohm twin lead-in. Line is standard approved flat-type, solid dielectric with weather-resisting insulation. Dynatenna mounts anywhere easily . . . vertically or horizontally to match polarization of transmitting station. Installation is simple! Easy-to-follow illustrated instructions and all necessary hardware included.


Screw-driver is the only tool needed for assembly. Dynatenna is seamless, all aluminum, heat-treated . . . will withstand severest weather conditions. MA-2186. ONLY \$4.95 EACH \$4.45 each IN LOTS OF 3

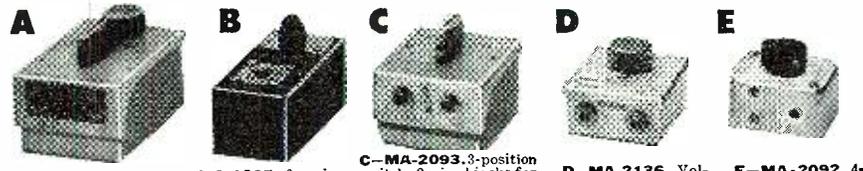19c Each—YOUR CHOICE of CONTROL BOXES—19c Each



A—MA-2135. 5-position switch, vol. control & jacks for PL-55 and PL-68. 3" x 4 1/2" x 2 1/4". Aluminum fin. sh. B—MA-2095. 6-position 5-prong female receptacle. 2 1/4" x 4 1/2" x 1 1/2". Black crackle finish. C—MA-2093. 3-position switch, 2 wired jacks for PL-55 plugs, internal jack strip, circuit diagram. 3" x 3 1/4" x 1 1/4". Aluminum finish. D—MA-2136. Volume control, jacks for PL-55 and PL-68. 2 3/4" x 3 1/4" x 1 1/4". Aluminum finish. E—MA-2092. 4-position switch. 2 1/2" x 2 1/4" x 1 1/4". Aluminum finish.

USE A PRE-PUNCHED MID-AMERICA CHASSIS

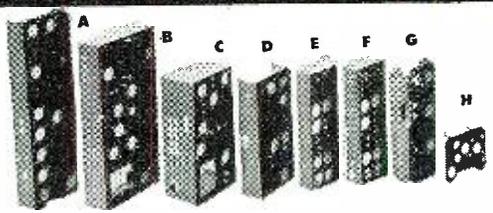

Save time and effort with a punched chassis. Takes the hard work out of building receivers, amplifiers, etc. (A) MA-2913 16" x 5" x 2" 10 tube 59¢ (E) MA-2907 10 1/4" x 3 3/8" x 1 1/2" 6 tube 29¢ (B) MA-2910 14" x 6 3/4" x 2 1/2" 8 tube 49¢ (F) MA-2911 10 1/4" x 3 1/2" x 1 1/8" 7 tube 29¢ (C) MA-2903 10 1/2" x 5 1/2" x 3 1/2" 7 tube 29¢ (G) MA-2912 10" x 3 3/4" x 2" 5 tube 29¢ (for chassis lock sockets) (D) MA-2914 10" x 5" x 2" 6 tube 39¢ (H) MA-2915 5 1/2" x 1 1/2" x 3 tube 15¢

Save on RG-8/U Coaxial Cable

Get your share of this fine-quality coaxial cable. Solid, moisture-proof polyethylene dielectric; fully shielded. 52 ohms nominal impedance. Not sold in less than 100 foot lengths. MA-5018 per 100 feet . . . \$2.89

COAXIAL CABLE CONNECTOR

PL-259. Low-loss connector for RG-8/U and RG-11/U, or use adapter for other coaxial cables. Silver-plated . . . machined brass. Inserts are low-loss mica. Exceptional quality at a rock-bottom price. MA-2828 29¢

Order from this Ad!

Rush your order now! Minimum order we ship is \$2.50. Send 25% with order. Balance C.O.D. And ask for *Mid-America's Big Bargain Bulletins* that list latest, greatest buys in RADIO PARTS, TUBES, ELECTRONIC EQUIPMENT. Send orders to Desk E-58

MID-AMERICA CO. Inc. 2412 S. Michigan Avenue Chicago 16, Ill.

SPECIAL! BRAND NEW TRANSMITTING TUBES!



1625 TRANSMITTING BEAM POWER AMPLIFIER. Same as 807 except 12.6 volt filament medium, 7 pin base**14c** ea.

829 PUSH PULL TWIN-UNIT. Beam Power Amplifier tube..**\$1.49** ea

836A/3B27 Half Wave High Rectifier. **49c** ea.

2050 Negative-control, heater-cathode type. Can be operated directly from a high-vacuum phototube. Octal 8-pin base. **69c** ea.

955 ACORN TUBE. Detector Amplifier Oscillator Tube**19c** ea.

2C26 U.H.F. TRIODE 6.3 Filament 8 Pin Base. Specially adapted to high altitude applications by reason of special mechanical construction. **19c** ea.

2C34 DOUBLE TRIODE 6.3 Filament . . . Max Plate V.300 . . . 7 pin base . . . Class C Amplifier — Oscillator . . . Class B. Amplifier**39c** ea.

350B BEAM TYPE TETRODE — Class A — Audio Amplification. 30 Watt.....**99c** ea.

7193/2C22 TRIODE Class A Amplifier. **19c** ea.

306A**19c** ea.

304TH Medium-mu class B modulator and rf amplifier. Will handle high current at relatively low voltages. Beaded small cap. **\$3.95** ea.

E1148 TRIODE 6.3 Filament, 5 Pin Base. Max. Plate V.300**69c** ea.

1626 RF oscillator. Heater-cathode type. Octal 8-pin, micanol, base.....**14c** ea.

LAST MINUTE SPECIALS!

VT52/45 Special**39c** ea.

801A**89c** ea.

830B**\$3.95** ea.

803**\$5.95** ea.

872A**\$1.39** ea.

MINIMUM ORDER—\$4.00

25% deposit on all orders, balance C.O.D., F.O.B. New York

SENGO RADIO, Inc.

71 West Broadway, N. Y. 7, N. Y. TELEPHONE BEEKMAN 3-649B.

Jones, one of the founders and co-directors of the station:

"God's bringing to pass that dream and hope which He had implanted makes up the remarkable story of spiritual romance that constitutes the day-by-day progress of Radio Station HCJB since its inception. Here is a promise and a method transformed into a missionary radio station, flashing the good news to the 'uttermost parts of the earth'."

* * *

Radio War in Orient

We quote some interesting excerpts from an article called "Radio War For Asia's Ear," as reprinted in *Radio Times of India*, and which originally appeared in *The Sunday News of India*. The author, Arthur Fay, wrote:

"A radio war is going on in the Far East and will be intensified as Britain, America, France, Holland, Soviet Russia, China, and other nations build more powerful transmitters to help them to 'win friends and influence people' in the Orient. By the end of next year there

will be about 20 transmitters of 100 kilowatts and over putting out entertainment and propaganda designed for Asiatic ears . . . You can get a long-wave radio set for next to nothing in Shanghai these days. But—and this, of course, is why you can get them for next to nothing—nobody wants long-wave sets. The radio dealers who have a lot of them cluttering up their shelves are victims of the wireless war now in full swing in East Asia where many nations are striving for the ear of the Oriental listener. Britain, America, France, Holland, Soviet Russia, and China, too, are in the field with powerful transmitters either operating or planned. India and Pakistan are expected to enter the lists, and Siam and Indonesia have projects of their own.

"Early casualties in the war have been Shanghai's numerous privately-operated stations, closed down because the Chinese Government wants no rivals in its own territories to its State-owned broadcasting service. The drive against


NEW PRESSURE ROLL FOR BRUSH TAPE RECORDER

THE Engineering Department of Minnesota Mining & Manufacturing Company has announced a new pressure roll to be used in conjunction with the Brush "Soundmirror" taperecorder.

According to R. Marchant of the Engineering Department this small pressure roll rides against the surface of the tape on the capstan during operation. A small ball bearing assembly having a 1/4 inch face and a 3/4 inch o.d. can be mounted on a pivoted arm so as to be held against the capstan by light spring pressure. This arrangement is designed to provide more uniform movement of the tape throughout the entire reel.

In the course of developing a new plastic recording tape for use with the machine, Minnesota Mining & Manufacturing Company found that some machines vary considerably in the amount of spring pressure applied to the felt pads that hold the tape against the recording and erase heads. Since this pressure is quite important it has been suggested that the value be checked by means of a small spring scale. The pad pressure should be about 1 1/4 ounces on each head. If the machine does not have the proper pressure, the adjustment may be varied by lifting the motor board out of the cabinet.

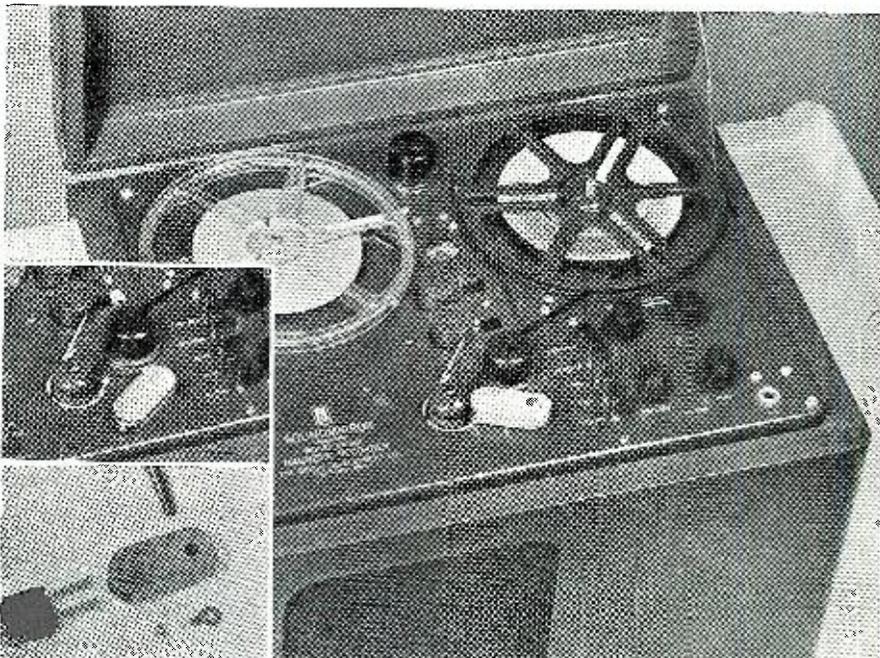Top view of Brush "Soundmirror" shows position of new pressure roll.





NOW! BUILD 15 RADIOS \$14⁷⁵

COMPLETE KIT ONLY...

**ABSOLUTELY NO KNOWLEDGE OF RADIO NECESSARY
YOU NEED NO ADDITIONAL PARTS**

THE PROGRESSIVE RADIO KIT is the ONLY COMPLETE KIT. Operates on 110-120 volts AC/DC. Contains everything you need. Instruction Book, Metal Chassis, Tubes, Condensers, Resistors and all other necessary radio parts. The 36-page Instruction Book written by expert radio instructors and engineers teaches you to build radios in a professional manner. The first circuit built is a simple one-tube detector receiver. Each succeeding circuit incorporates new arrangements of detectors, RF and AF amplifiers. This kit is excellent for learning the principles of receiver, transmitter and amplifier design. It is used in many radio schools and colleges. All of the commonly used detectors are used, including diode, grid leak, plate and infinite-impedance. The transmitters are designed with Hartley and Armstrong oscillators, using screen-

grid and control-grid modulation. Both vacuum tube and selenium rectification are employed in these circuits. The circuits are designed to provide excellent performance. Altogether, fifteen circuits are constructed, including 11 receivers, 1 audio amplifier, and 3 transmitters. The sets start with simple circuits of 1 tube plus rectifier, gradually grow more complex, and finish with several examples of radio sets using three tubes plus rectifier.

Progressive Radio Kit, only...\$14.75

SPECIAL FREE OFFER!

Electrical and Radio Tester sent absolutely FREE with each Progressive Radio Kit. PLUS FREE membership in Progressive Radio Club. Entitles you to free expert advice and consultation service with licensed radio technicians. Write for further information or ORDER your KIT NOW!

PROGRESSIVE SCOOPS!

FM COIL & CONDENSER KIT

Designed for operation on 88-108 MC (new band) contain 2 1F transformers, 1 Limiter Transformer, 1 Discriminator Transformer, 1 RF coil, 1 Variable condenser, Schematic and wiring instructions. Excellent for Schools, Experimenters and Radio Hobbyists.

Price, only.....\$4.95

CONDENSER KIT 50 PAPER TUBULAR CONDENSERS

Values from .002 mfd. to .1 mfd. 400 V. DC to 600 V. DC.

Only.....\$1.95

RESISTOR KIT

100 CARBON RESISTORS
Values from 120 ohms to 2.2 1/2 Watt, RMA color-coded. megohms.....\$1.50

PROGRESSIVE RADIO TOOL KIT

Contains 75 Watt 110/120 Volt Soldering Iron, long nose pliers and cutters, screw-driver, insulated alignment tool.....\$3.25

10-10 MFD. 450 W.V. DC

Electrolytic Condensers.....65c

20-20 MFD. 150 W.V. DC

Electrolytic Condensers.....30c

40-40 MFD. 150 W.V. DC

Electrolytic Condensers.....45c

75 Watt Soldering Iron.....\$2.40

(UL approved)

55 Watt Soldering Iron.....\$1.90

(UL approved)

MIDGET SOLDERING IRON

35 WATTS
110/120 Volts, UL approved.....69c

6" Alnico Slug Speaker.....\$1.69

Selenium Rectifiers.....79c

ANTENNA and RF COIL SET.....59c

(Broadcast Band)

Long Nose Pliers and Cutters \$1.45

PROGRESSIVE AMPLIFIER KIT \$15⁷⁵

HIGH FIDELITY, HUMLESS AMPLIFIER SEVEN TUBE PERFORMANCE

This newest Progressive Kit will enable you to build a newly designed, high fidelity, humless amplifier.

Beautiful aluminum custom-punched chassis, etched tone and volume control plates.

Designed by former Western Electric engineer. Ideal amplifier for television kit or set, FM tuner, AM tuner, microphone, phonograph, wire and instantaneous recorders.

Electrify your musical instruments by connecting them to the Progressive Amplifier by means of a contact mike.

Amplifier can be readily modified to match the GE reluctance pick-up.

Separate mike and phono input. Regulated power supply maintains constant voltage supply. DC heater supply, whether amplifier is used on AC or DC, provides humless operation by eliminating cathode-heater leakage hum.

Contains degenerative feedback for improved frequency response, balanced phase inversion and push-pull beam power output. Every stage thoroughly decoupled to improve low-frequency response and to prevent motor boating. Tone and volume controls completely variable.

Seven-tube performance. Uses 2 selenium rectifiers, 2-beam power amplifiers, 1 high-mu pentode mike amplifier, 1 twin-triode phase inverter, and 1 voltage regulator tube.

Seven-tube performance. Uses 2 selenium rectifiers, 2-beam power amplifiers, 1 high-mu pentode mike amplifier, 1 twin-triode phase inverter, and 1 voltage regulator tube.


**PROGRESSIVE AMPLIFIER KIT
(less Tubes and Speaker) Only..... \$15.75**

**TUBES for Progressive Amplifier Kit
1-12SL7, 1-12SJ7, 1-VR75, 2-12A6's
Complete Set, Only.....\$3.00**

BUILD A 5 TUBE AMPLIFIER Only . . . \$9.75

Ideal for phonograph, FM tuner or microphone. Has 5 tubes including rectifier. Kit is complete with tubes, chassis, volume control, tone control, radio parts, hook-up wire, solder and instructions. We can provide a 4-inch PM Speaker with

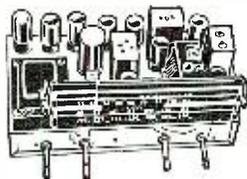mounted output transformer to fit on chassis, priced at \$1.95. Or use this kit with your own Speaker. It has 5 watts output, more than enough to drive a 12-inch Speaker.
ONLY.....\$9.75



1. AC Superheterodyne AM-FM receiver.
2. Improved Frequency Modulation Circuit.
3. 11 finest quality tubes, including rectifier.
4. 4 dual purpose tubes give 15 tube performance.
5. Automatic volume control.
6. Full-range volume control.
7. High-Fidelity AM-FM reception.

ESPEY CUSTOM-BUILT AM-FM HIGH FIDELITY RECEIVERS MODEL No. 7-BC

8. Full-range combination bass-treble tone control.
9. 13 watt (maximum) Push-Pull Audio Output.
10. 10 inch FM speaker with Alnico V magnet.
11. Indirectly illuminated "slide-rule" dial.
12. Loop antenna for AM and Folded Dipole antenna for FM reception supplied.
13. Provisions for external antennas.
14. Wired for phonograph operation.
15. Licensed under RCA and Hazeltine patents.
16. RMA listed.

YOUR PRICE . . . \$84.00

\$25.00 deposit required with C.O.D. orders

WRITE FOR
PROGRESSIVE
QUANTITY PRICES

PROGRESSIVE ELECTRONICS CO.
DEPT. RN-9 997 UNION AVE. BROOKLYN 11, NEW YORK

We Pay Postage on
pre-paid orders. All C.O.D.
orders shipped collect.

AMPERITE MICROPHONES

The ultimate in microphone quality, the new *Amperite Velocity* has proven in actual practice to give the highest type of reproduction in Broadcasting, Recording, and Public Address.

The major disadvantage of pre-war velocities has been eliminated — namely "boominess" on close talking.

- Shout right into the new *Amperite Velocity*—or stand 2 feet away—the quality of reproduction is always excellent.
- Harmonic distortion is less than 1%. (Note: best studio diaphragm mike is 500% higher.)



P.G. Dynamic Models PGH, PGL List \$32.00

- Practically no angle discrimination . . . 120° front and back. (Best studio diaphragm microphones . . . discrimination 800% higher.)
- One *Amperite Velocity* Microphone will pick up an entire symphony orchestra.

STUDIO VELOCITY, finest in quality; ideal for Broadcasting and Recording.

Models R80H-R80L — List \$80.00

There is an *Amperite Microphone* for every requirement.

WRITE FOR ILLUSTRATED 4-PAGE FOLDER giving full information and prices.



Amperite Velocity Microphones for Public Address Models RBHG, RBLG List \$42.00



"Kontak" Mikes Model SKH, list \$12.00 Model KKH, list \$18.00

Address inquiry attention Dept. RN

AMPERITE Company
561 BROADWAY NEW YORK

In Canada:
Atlas Radio Corp.
560 King St. W.
Toronto, Ont.

Just off the Press! 1948 Radolek RADIO PROFIT GUIDE



NEW COMPLETE RADIO PROFIT GUIDE FREE

Radio Repair Parts • Tools
Sound Systems • Tubes
Phono Equipment & Supplies
Test Instruments • Etc.

Big, new ENLARGED complete catalog showing thousands of Radio Bargains sent to you immediately. Helpful, money-saving buying information. Send coupon today!

BIG VALUES, LARGE STOCKS,
FAST, DEPENDABLE SERVICE



FREE...SEND TODAY

RADOLEK CO., Dept. B-058
601 W. Randolph St., Chicago 6, Ill.
Please send your Free Profit Guide Catalog and regular Supplements.

Name
Address
City.....Zone.....State.....

SAVE AT RADOLEK

TECHNICAL KO's

OIL FILLED CONDENSERS

.05 MFD	1000 V	\$0.28
.05	500 V	.14
.1	2500 V	.60
.1	7500 V	1.85
2x.1	7000 V	4.75
.12	15000 V	6.95
.25	1000 V	.35
.25	4000 V	2.75
.25	6000 V	4.00
10x.25	600 V	1.00
.5	600 V	.28
.5	1000 V	.35
.5	2000 V	.40
.75	2000 V	.55
.77	330 VAC	.35
1.0	1000 V	.45
2.0	1000 V	.60
4.0	600 V	.60
4.0	1000 V	1.00
5.0	220 VAC	.65
6.0	600 V	.70
8.0	600 V	.80
8.0	1000 V	1.75
10.0	600 V	1.00
30.0	90 VAC	1.40
30.0	330 VAC	3.75

TRANSMITTING MICAS

.000025	2500 V	\$0.11
.00005	2500 V	.14
.00005	3000 V	.30
.00005	5000 V	.85
.00007	2500 V	.20
.00007	2500 V	.20
.00025	2500 V	.25
.00025	5000 V	.85
.0004	2500 V	.22
.0005	2500 V	.22
.00072	5000 V	.89
.0008	5000 V	.89
.001	2500 V	.25
.0011	5000 V	.89
.002	1200 V	.17
.002	3000 V	.66
.0025	1200 V	.15
.00275	2000 V	.28
.003	2500 V	.30
.003	3000 V	.66
.004	2500 V	.36
.005	600 V	.13
.005	3000 V	.66
.006	2000 V	.35
.008	1200 V	.15
.01	600 V	.13

CHOKE; 30MA-12H; 100MA-10H, 250 OHM.....	\$1.59
POTS; 20K-50K, 100K.....	.16
POTS; DUAL 1 MEG, DUAL 250K-50K.....	.20
SHIELDED WIRE #22.....	.50' for .65
RESISTOR KIT ASSORTED 1/4&1W.....	100 for 1.49
BATHTUB KIT 3x1.5. .05. ETC.....	10 for .59
CONDENSER KIT .01-.00001.....	100 for 3.00
MICAS .002, .005, ETC. ALL VALUES.....	.08
.01 150V PAPER (MIDGET).....	60 for 1.00
0.1 600V PAPER.....	8 for 1.00
6V6 METAL.....	\$0.89
12K8 METAL.....	.25

\$2.00 min. order F.O.B. N.Y.C. Add postage
50% deposit, balance C.O.D. with all orders.
Manufacturers' Inquiries invited. Send for Flyer.
Prices are subject to change without notice.

TECHNICAL RADIO PARTS CO.

265 Greenwich St. Dept. RN-5 N. Y. 7, N. Y.

these 'foreign stations' started in January (1947) when a Soviet-subsidized station was raided and 'sealed.' Then the other stations, including a French one, were abolished, to be replaced by the Government-managed XORA. XORA is attacked in the local press for its poor announcing and lack of good musical programs. Both foreigners and educated Chinese prefer to tune in on the short-waves for programs from other lands. And so nobody buys long-wave sets. Shanghai's listeners and Asiatics in general are to have a much wider range of programs to choose from as time goes on.

"Already there is considerable competition among the powers to win friends and influence people among the public-opinion-forming classes who own radio sets and the poorer people who in one way or another get in some group-listening. The United States, with one eye on future trade expansion and another on the threat of Communism, is going for the Eastern listener in a big way and will do so in a bigger way before long. From Los Angeles, New York, Honolulu, Tokyo, and Manila, 'the Voice of America' is heard. Special programs designed for Asiatic ears go out daily putting the U. S. point of view. Now six 250-kilowatt transmitters in Manila are planned to make America's voice still louder in the East.

"Britain has four transmitters operating from Singapore. Five or six more, each of 100 kilowatts and costing between 15,000,000 and 20,000,000 Straits dollars, are to be added. Between 50 and 100 technicians and other staff will look after the new apparatus, which is to go up in South Johore, though the studios will remain in Singapore. The BBC will operate the new station. The use of radio for the education of the young is to be developed in the Malayan Union, schools being provided with standard sets. Asia also hears BBC programs relayed from Australia as well as Australia's own programs.

"Some former Dutch stations are now operated by the Indonesian Republic, but the Netherlands is far from having given up the struggle to put her case in the Far East. She will soon have a 100-kilowatt American-installed transmitter broadcasting from Batavia. France is to modernize her Saigon station, which has many fans outside Indo-China.

"The Chinese Government stations, Chungking, Logan, and Shanghai, and the Communist North Shensi station broadcast daily their own brands of xenophobia along with European and Chinese music and contradictory communiques on the civil war. The Communist station, following the Party line, concentrates these days on attacking United States "imperialism." Kuomintang radio propaganda also increasingly

displays a continuously anti-foreign outlook.

"Chiang Kai-shek's Government intends within the next two-and-a-half years to have four powerful short-wave stations, at Shanghai, Chungking, Canton, and Changchun (Manchuria). Besides catering to Chinese nationals, they are to have programs for listeners in Europe, America, and Australia. There is also to be a new high-power station at Nanking.

"Siam is increasing the power of Bangkok Radio with a view to keeping herself before the foreign listener, and India and Pakistan are both in the market for short-wave broadcasting equipment to spread the sound of the rival voices further.

"Soviet broadcasts in every imaginable language are heard throughout the East. But where these broadcasts actually come from even the experts are not sure. There must be a number of stations in the Far Eastern Republic, but exactly where they are is one of the many secrets of this 'forbidden land.' Much of the material is relayed from Moscow, which broadcasts a good deal of material intended for the Asiatic listener. It would seem highly probable, in view of Russian ideas about Asia, that some of the 28 powerful stations which are to be completed by 1950 under the current Five-Year Plan will be located round about Vladivostok, Khabarovsk, and Krasnoyarsk.

"Altogether, by the end of 1949, something like 20 transmitters of 100 kilowatts and over will be directing diverse streams of propaganda, mingled with entertainment and education, at the ears of Eastern Asia."

* * *

Gatti-Hallicrafters Expedition

The Gatti-Hallicrafters Expedition to Africa's Mountains of the Moon has been allotted call letters and wavelengths by the Conference of East African Governors in Nairobi, Kenya Colony, as follows: Uganda, VQ5GHE; Kenya, VQ4EHG (28.3), Uganda (mobile), VQ5HEG, and Tanganyika, VQ3HGE; frequencies assigned are 1.8-2.0 mcs., 7.0-7.2 mcs., 28-30 mcs., and 58.5-60 mcs. At the time this was written, schedule was 0100-1530 EST, using 28.375 (phone) and 28.050 c.w.). The Expedition has been reported widely in the East, contacting U. S. "hams."



The Expedition is combining scientific research and adventure—to test equipment and study radio phenomena at the same time it broadcasts the sounds of the jungle and descriptions of fantastic tribal rituals to thousands of short-wave listeners in the United States and elsewhere. Constant touch is being kept with the outside world by radio as the Expedition makes its way through parts of Tanganyika, Kenya, and Uganda, visiting

May, 1948

TELEVISION INDUSTRIES Co.

PICTURE IF & SOUND IF STRIP and FRONT END. This sensational picture If & Sound If Strip developed by our engineering staff enables you to build a 10"-12"-15"-20" direct view or projection type receiver with FM sound. Supplied with a

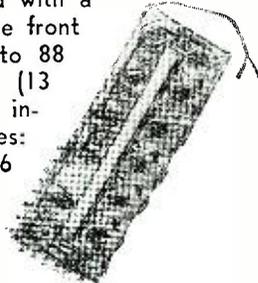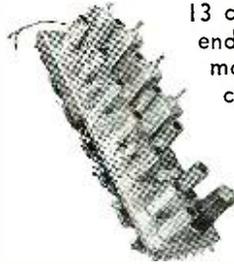
13 channel RF front end unit. The front end covers channels from 44 to 88 mc/s and 174 to 216 mc/s (13 channels). Matched antenna input for 300 ohm line. Tubes: 1-6J6 RF amplifier 1-6J6 converter 1-6J6 oscillator.



\$119.50

DEALERS NET

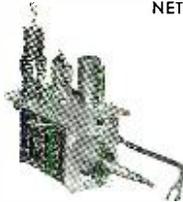● PICTURE IF — 5 picture IF stages of amplification and second detector. SOUND IF STAGES 2 IF stages with limiter and discriminator. VIDEO amplifiers — 2 stages video with a frequency response of 4.5 mc/s ONE DC RESTORER. IF FREQUENCY audio 21.25 — picture 25.75.



Picture IF band width 4.5 mc/s. All the above circuits and tubes are contained on one chassis. Front end unit on separate chassis. Both picture IF and sound IF delivered completely wired, tested, tubed, and matched ready for use.


DUMONT INPUTUNER

The Dumont Inputuner tunes continuously from 44 to 216 megacycles without a break—covers all 13 television channels as well as FM, amateur, and aviation channels. For ease and convenience of operation no band switching of any kind is required when tuning from channel to channel with the inputuner system. Just one simple operation to reach any desired station.



\$97.90

LIST

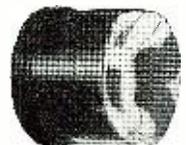

Deflection Yoke similar to RCA part # 20 ID1

\$13.75

LIST

BAUSCH & LOMB TELEVISION PROJECTION LENS



Television Industries Co. is proud to announce that they have been appointed national wholesale distributors for the Bausch & Lomb f: 1.9 Television Projection Lens. Sample orders filled immediately.

\$125.00

DEALERS NET



R. F. POWER SUPPLY

27 — 30 K.V.
for

Projection Television

\$125.00

DEALERS NET

Contact Us for your Local Distributor

TELEVISION INDUSTRIES Co.

540 BUSHWICK AVE.
BROOKLYN 6, N. Y.

University LOUDSPEAKERS

-can whisper, too!

And that's important because the primary purpose of any loudspeaker is to convey intelligence and not just make a loud noise. UNIVERSITY loudspeakers — with the highest conversion efficiency of any speaker of comparable size — not only give maximum sound output with minimum power input, but reproduce every detail and inflection of the voice at all levels from a whisper to a shout.

**A JOB-RATED SPEAKER
FOR EVERY APPLICATION!**

REFLEX TRUMPETS




A wide variety available for every requirement — voice, music, paging and talk-back. Weather-proof, sturdy construction for years of dependable use.

DRIVER UNITS

Several high efficiency models with continuous power capacities up to 25 watts and response to 15,000 cycles. All unconditionally guaranteed for one year.



PAGING, CALL-BACK SPEAKERS

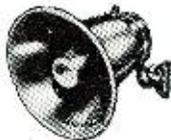

Available in many types and power ranges. Compact design, high conversion efficiency and high sensitivity. Standard voice coil impedances permit easy installation.

SUPER POWER SOUND PROJECTORS

Many sizes — 100, 150 and 300 watts with conservative ranges to a few miles. Excellent quality even at full power. Ideal for installation in aeroplanes and church steeples.



EXPLOSION PROOF SPEAKERS



Radial and directional types for use in mines, refineries, railroads and shops. Immune to live steam, salt-spray or complete immersion. Power handling capacity 15 watts.
24 PAGE TECHNICAL CATALOG ON REQUEST.



UNIVERSITY LOUDSPEAKERS · INC.

80 SO. KENSICO AVE., WHITE PLAINS, N. Y.

obscure tribes of pygmies and giant Wattusi enroute. At Africa's fabulous Mountains of the Moon, the Expedition is to explore the mysterious Lost Lakes of the Ruwenzori. The legendary Mountains of the Moon lie surrounded by almost impenetrable jungle forest — the "Fons Nilus" of the ancients, with snow-clad mountain peaks towering nearly 17,000 feet into the equatorial sky, whose snowfields and glaciers spread over an area of 100 square miles. Present plans call for terminating the Expedition at Nairobi, Kenya Colony.

Sample verification cards, signed by Commander Attilio Gatti, leader of the Expedition, are quite attractive, giving locations as Base Camp, Tanganyika; Base Camp, Uganda, and Base Camp, Kenya.

* * *

Club Notes

New Zealand—All correspondence regarding the New Zealand DX Club should be addressed to 10, Koraha St., Remuera, Auckland, S. E. 2, New Zealand, according to Harold J. Barr, Hon. National Secretary of this group.

Sweden—The Jonkoping - Huskvarna DX-Club has a new name—*Scandinavian DX-Club*, but is still issuing its monthly house organ under the same name, *Nattugglan* (The Night Owl). Officers for 1948 include Karl Ake Bergstrom, president; Aka Hallman, vice-president; Sune Engdahl, secretary; Karl Gustav Frick and Stig Wahrling, cashiers (co-treasurers); Harald Svahn and Rolf Johanson, editorial staff. The club now has over 350 members and is the largest active group in Scandinavia. (Bergstrom, Sweden.)

United States—A unique organization is the "Silent QRM-ers," a group of short-wave listeners banded together for the purpose of exchanging ideas, information, complaints, SWL cards, reports, and so on. Any active short-wave listener is in-

vited to become a member—whether his main interest is amateur fone, c.w. or regular broadcasting station listening. Only requirement is that he is active as a SWL and sends out cards. There is no fee of any kind, "simply because we are not promising anything in return," the organizers point out. "But we think it is a swell way to get acquainted with other SWL's, and to exchange ideas with an objective of improving SWL-ing activities. Anyone interested should write SWL-W2, Walter (Rocky) Hastrich, 19 Holland Ave., Lancaster, New York, for an application blank. Currently, the 'Silent QRM-ers' are engaged in a 'new member campaign,' trying to build up membership to a respectable figure." (Cooley, Pa.)

* * *

Verification Data

Radio Douala verified for Kary, Pa., in 32 days (airmail both ways). QRA is Radio Douala, Service Radio-electrique, Douala, Cameroun Francais.

QRA of the PZR outlets is Avros Studio, The "Prince Bernhard Transmitter," Paramaribo, Netherlands Guiana. (Southall, Pa.)


The Guatemala stations (TGW series) verify by return mail, cards have been received in less than a week on occasion. (Eyles, Ga.)

YSUA, 6.250, verified promptly by Spanish letter (airmail); announces long-wave call YSU, *Radio Mil Cincuenta* (1050 kcs. which is frequency of medium-wave outlet); power was given as 1 kw.; QRA is Radio Mil Cincuenta, la Avenida Sur No. 50, San Salvador, Republica de Salvador, Central America. (Eyles, Ga.)

Calcutta, 4.840, verifies with prewar type of large QSL card; Bombay, 4.880, verifies with small-type QSL card and letter. (Pearce, England.)

QRA of the Norwegian s.w. outlets is Norsk Rikskringkasting, Oslo, or Norwe-

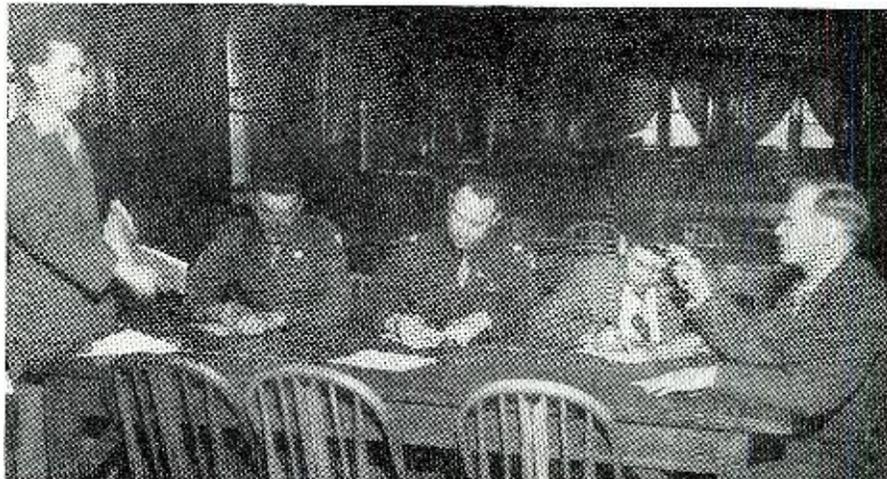Potential hams take exam conducted by the XXIV Corps' radio officer, Willard B. Anker (standing at left) at Seoul, Korea. Would-be hams include T/5 Frederick A. Liebold, Memphis, Tenn.; Lt. Col. Elmer F. Estrumse, San Antonio, Texas; Henry Ramirez, Bronx, New York; and Lt. Robert S. Monk, Boise, Idaho, in the usual order.



WITH A "SURPRISE"
TRADE-IN ALLOWANCE
ON YOUR USED
TEST INSTRUMENTS

\$SAVE 2 WAYS

ON THESE
SUPER BARGAINS
IN SURPLUS EQUIPMENT




**ARMY
SURPLUS
HEADPHONES
HS23A**

HS23A—Used but in A-1 Electrical condition, 8000 ohms impedance. Complete with leather headband. Shpg. Wt. 3 lbs.

ONLY..... **98c**

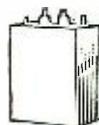Type HS-16A—Canvas web headband and long standard type cord. Brand New in original boxes. Shpg. Wt. 3 lbs.
ONLY..... **\$1.47**



CHOKES

No. 5269—4.5 HY x 150 MA. 79 ohms DC Res. Shpg. Wt. 6 lbs.

**TWO FOR..... 79c Each
ONE ONLY..... 99c**

No. 2785—Dual 12 HY x 250 MA. 150 ohms. DC Res. per section. Shpg. Wt. 17 lbs.

ONLY **\$4.95**



No. 6317—4 HY x 300 MA. 40 ohms DC RES. Shpg. Wt. 13 lbs.

ONLY **\$4.95**

TRANSFORMER

No. 4891—1200/1400 VCT x 200 MA. PRI. 115 VAC 60 cy. Shpg. Wt. 18 lbs.

ONLY..... **\$7.45**



**EXTRA
SPECIAL!**

ONLY
\$1.96

**SURPLUS
CATHODE RAY
TUBES**

5", 5BPI (Green Screen) and 5 BP4 (White Screen) Surplus C. R. tubes Brand new in original boxes. Get yours while the supply lasts. Shpg. Wt. 5 lbs.

Shipped by Express Only

"BEST DEAL I EVER MADE!"

That's what every bargain conscious Radio Serviceman, Dealer and Amateur says after experiencing the satisfaction that results from a Walter Ashe "Surprise" Trade-In Allowance. For sensational savings, trade-in your used, factory-built equipment today! Let us know what you have to trade. Indicate your preference in new equipment. Back will come our big, money-saving offer. Phone, wire, write or use the handy coupon below.



SURPLUS KEY

Type J-37—Ruggedly built. 1/4" silver contacts. Bakelite base. Shpg. Wt. 2 lbs.

ONLY **98c**



BRAND NEW PE-103A DYNAMOTOR

Here's the answer to your mobile station power supply requirements. Original Boxes with overseas packing, 6 or 12 VDC input and 500 VDC @ 160 MA output. The ideal power source for the Sonar MB-611 Transmitter.

ONLY **\$9.95**

**SURPLUS
OCTAL SOCKETS**

Similar or equal to the MIP-8. Molded in plate 8 prong socket.

Shpg. Wt. 1 lb. **12 for 50c**



EACH **5c**



**SURPLUS
SENSITIVE RELAY**

6500 ohm, 2 MA coil. SPST contacts. Shpg. Wt. 1/2 lb.

ONLY **98c**

**SURPLUS
T-17 HANDMIKES**

S. B. Carbon Mike with push-to-talk switch on handle. Complete with cord and plug. Brand New—in Original Cartons. Shpg. Wt. 3 lbs.



ONLY **69c**


**Limited Quantity SURPLUS TUBES
While They Last — Brand New...
Original Cartons**

3C24/24 G. \$1.10	872 A. 3.00
811. 1.95	VT-127 A. 2.95
813. 5.95	807. 1.13

WRITE FOR COMPLETE SURPLUS LIST

**SURPLUS
SPARE TUBE KIT**

ONLY
98c

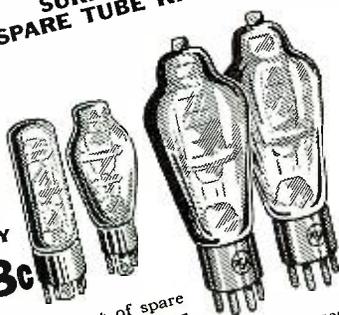

Complete set of spare tubes for BC-459-A or similar unit. Consists of 1—1626, 2—1625, and 1—1629. Shpg. Wt. 2 lbs.



SEND FOR YOUR
FREE COPY
OF OUR LATEST CATALOG

COMPLETE SELECTION OF
TOP CONDITION, SLIGHTLY
USED TEST AND COMMUNICATION
EQUIPMENT

ALL THE BIG NAME BRANDS of
New Test Instruments and Communication
Equipment in Stock... ready for
immediate delivery.

ALL
PRICES
F. O. B.
ST. LOUIS

TIME PAYMENTS
AVAILABLE

PHONE: Chestnut 1125

**Walter Ashe
RADIO CO.
1125 PINE ST. • ST. LOUIS 1, MO.**



WOJWD W9NRF W0W7M W0QDF W0PGI W0IYD

Use this coupon to get Walter Ashe's "Surprise" Trade-in Allowance on your used factory-built test equipment. RN5

WALTER ASHE RADIO CO.
1125 Pine St., St. Louis 1, Missouri

Am interested in the following top condition, slightly used Test Equipment. _____ (list preference)

I want to trade. _____ (describe used equipment)

for _____ (show make, model of new Receiver desired or other equipment)

Rush my FREE COPY of the big, New 1948 Walter Ashe Catalog.

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

TUBES! NATIONALLY ADVERTISED BRANDS TUBES!

RCA — Kenrad — Sylvania — Tung-Sol — National Union — Raytheon — Philco — Hytron
All new tubes. 100% guaranteed. Individually boxed.

TYPE	PRICE	TYPE	PRICE	TYPE	PRICE
024	.80	6SL7GT	.80	7C5	.60
1A5GT	.54	6SN7GT	.80	7C7	.60
1A7GT	.65	6S07	.50	7E3	.60
1L5GT	.54	6SQ7GT	.54	7F7	.60
1LX3	.16	6SR7	.60	7N7	.60
1N3GT	.60	6U5/665	.65	7Z6	.60
1R5	.60	6V6GT	.65	7V7	.60
1S4	.60	6X5GT	.45	7V9	.60
1S3	.60	7A4	.60	7Z4	.60
1T4	.60	7A6	.60	12A76	.54
3Q5GT	.60	7A7	.60	12BA6	.54
3S4	.60	7B5	.60	12BE6	.54
6U4B	.45	7B6	.60	12A6	.54
6V4B	.72	7B7	.60	12A8GT	.50
6Y3GT	.40			12C8	.50
6Y4G	.45			12H6	.54
6A8	.72			12I5GT	.45
6A7	.55			12SA7GT	.65
6A8	.60			12SC7	.65
6AC7	.75			12SF5	.65
6AK5	.75			12SH7GT	.65
6BBG	.72			12SJ7	.54
6C4	.60			12SJ7GT	.54
6C6	.65			12SK7GT	.54
6C8G	.72			12SL7GT	.80
6E5	.65			12SN7GT	.54
6F5	.65			12SQ7GT	.54
6F6	.96			12SR7	.54
6F8G	.54			14A7/12B7	.60
6H6	.50			14Q7	.60
6H6GT	.50			25L6GT	.54
6J5	.50			25Z6GT	.54
6J5GT	.50			26	.50
6J6	.50			27	.45
6J7	.60			35A5	.65
6K6GT	.45			35L6GT	.51
6K7	.54			35M4	.65
6L6	.96			35Y4	.65
6L6GA	.96			35Z5GT	.55
6N7	.80			39/44	.45
6R7G	.54			50A5	.65
6SA7GT	.54			50B5	.54
6SC7	.65			50L6GT	.54
6SF5	.65			53	.72
6SF7	.65			70L7GT	.66
6SH7GT	.50			71A	.65
6SJ7	.50			77	.54
6SJ7GT	.50			84/624	.54
6SK7	.50			89	.54
6SK7GT	.50			14Z6GT	.86
				VR150-30	.70



ELECTRIC PORTABLE PHONOGRAPH
Leatherette Covered. 2 Watt Amp-lifier. Plays 12 inch records with cover closed. 5 inch Alnico 5 Speaker. Rim drive constant speed. Self starting motor. High fidelity pickup. Size 17"x13"x7 1/2". List Price \$29.95.
NET PRICE\$15.95
LOTS OF THREE\$14.95

TERMS: 25% with Order—
Balance C.O.D.—F.O.B. Chicago

ORDER TODAY FROM

FRANKLIN ELLIS CO. 1313 West Randolph St. Dept. R-5 Chicago 7, Ill.

SENSATIONAL SELLER!



LAKE DELUXE CHANGER

Revolutionizes the Industry!
A Sensational Seller!

11 Outstanding Features:

- Positive Intermix
- Service Adjustments Eliminated
- Minimizes Record Wear
- Single Knob Control
- Plays ALL Records
- Pick-up arm may be grasped at any time
- Completely Jam-proof
- Records Gently Lowered on Spindle —not dropped
- Automatic Shut-off on last record

Dimensions: 13 1/2" W x 12 1/4" D x 7 3/8" H. No. 116A. YOUR NET **\$28.73**

WEBSTER CHANGER, Model 56.....\$26.66 Net
WEBSTER CHANGER, Model 50..... 21.17 Net

FREE

DEALERS and SERVICEMEN: Write for our NEW 16-page 1948 illustrated catalog on radio parts, tubes, accessories, cabinets, sets, electrical appliances, etc. Get on our mailing list today!

Lake Radio Sales Co.
615 W. Randolph Street
DEPT. A
Chicago 6, Ill.

CONVERSIONS and SCHEMATICS

SCR-274-N Receivers

BC-453, BC-454, BC-455: Explanation of control and power circuits and plug terminals. Conversion of the front plug to a local control adapter with volume control, on-off and CW-MCW switch. Schematic for AC power pack. Alignment instructions. Top and bottom views showing parts location. Voltage and resistance readings. Schematic of 3-unit rack, control box, adapters and interconnection.
12 8 1/2"x11" pages. Price **\$2.00**

Conversion of BC-946-B Broadcast-Band Receiver
Practical wiring diagram. Control circuit explanation. Complete conversion schematic, 106 step-by-step instructions, alignment instructions. Top and bottom views with parts location arrows.
12 8 1/2"x11" pages. Price **\$2.00**

BC-645, original and conversion, fixed or mobile \$1.00
BC-375, conversion to AC, with power supply.. \$1.00

SCHEMATICS for Other Equipment:

\$1.00 each AN/ARC-5, Receivers, (less the VHF)
SCR-274-N Transmitters, Modulator, etc.
AN/ARC-5 Transmitters (less the VHF), Push-Pull Modulator, Relay, Switching, etc.
T-23/ARC-5, the VHF transmitter.
ARB (CRV 46151). Alignment, etc.
AN/ART-13A Transmitter, Control Box, etc.
SCR-522 Receiver, Transmitter, etc.
BC-348-J, N, or Q, plus AC Power Pack
BC-348-H, K, L, or R, plus AC Power Pack.
R-89/ARN-5 Glide Path Receiver.
RC-103-A, (includes RC-733-D).
AN/APN-1, (includes RT-7/APN-1).
MN-26-C Bendix Radio Compass Receiver.
R-65/APN-9 Loran Receiver-Indicator.
EE-8 Field Telephones.

R-5/ARN-7 AN/APT-2 RA-10
AN/ARC-4 AN/APT-5
DZ-1, DZ-2 BC-1206-C

SCR-269-G (Includes BC-433-G)
PLEASE SPECIFY which you want. Remit with order. Print your name and complete address in the upper-left corner of the envelope.

R. E. GOODHEART
2616 N. Spaulding Ave. Chicago 47, Ill.

gian State Broadcasting, Oslo Studios, Oslo, Norway. (Anderson, California.)

Radio Algerie is sending out a QSL card now instead of a letter; QRA given as Radio Algerie, 10 Rue Hoche, Alger, Algerie, Afrique du Nord. (Pearce, England.)

QRA for Radio Bissau is CQM, Emissora de Guine, Bissau, Portugues Guine, Africa. (Persson, Sweden.)

EA9AA, 7.080, Tangiers, verified by Spanish letter from Radio Africa, 39 Calle Shakespeare, Tangier, International Zone, Morocco. Report sent in Spanish.

QRA for HLKA is Korean Broadcasting System, 1 Chung Dong Jung, Seoul, Korea, or Commanding General, USAMGIK A. G. Personnel, A. P. O. No. 235-2, c/o Postmaster, San Francisco, California, USA. (Kary, Pa.)

Jerusalem QRA of the Near East Arab Broadcasting Station (Jaffa) is Bab Ez Zahira, P. O. Box 1170, Jerusalem, Palestine. (Kary, Pa.)

Address of CS9MB, Azores, is Emissor Regional dos Acores, Avenida Gaspar Frutuoso, Ponta Delgada, S. Miquel, Acores. (Kary, Pa.)

For those who do not already have it, QRA of Radio Damascus is Posts, Telegraphs, and Telephones Dept., Syrian Republic, Damascus, Syria (Syrie).

Radio Club de Tenerife can be addressed as Estaciones EAJ-43 y EA8AB, Apartado de Correos 225, Santa Cruz de Tenerife, Islas Canarias. (Kary, Pa.)

* * *

This Month's Schedules

(NOTE: Between the time this was compiled and now, some stations will have gone on Summer Time — making their transmissions one hour earlier than listed herein.—K.R.B.)

Anglo-Egyptian Sudan—Radio Omdurman operates on 13.320, 9.650, and 572 kcs., with powers of 250 w., 350 w., and 750 w., respectively; is scheduled in Arabic daily 2315-2345, and except Friday at 1130-1300, 1400-1930; on Fridays in Arabic at 1130-120, 1400-1430, and also has transmissions at 0300-0430, 0900-1000; on Fridays between 1230-1300 has English period. (Persson, Sweden.)

Argentina — LRY is back on 9.545. (Beck, N.Y.) Operates 0500-2200. (Balbi, California, via URDXC)

Australia—Perth appears to have replaced VLW7, 9.52, with VLW5, 9.610. (Stark, Texas.) Move to 9.610 confirmed by Dilg, California, and by Eyles, Georgia. Has powerful signal here in West Virginia until around 0845 when begins to fade badly.

Austria—Radio Wien, Vienna, has been heard in England on 7.240 and 9.664 to 1805 sign-off following a news summary in German; some days has "English by Radio" at 0415-0430; (on Fridays at least, this program is also carried by the Rot-Weiss-Rot station, 9.575); German programs are resumed at 0430; the 11.78

RADIO NEWS

channel is heard well in Britain mornings and afternoons (EST). (Pearce)

Belgian Congo—Leopoldville has moved from approximately 9.745 to (announced 9.767 (may vary); in the North American beam, now following the 2100-2115 news, there is a program called "Amongst Friends" when listeners' letters and reports are answered over the air (not Sundays). (Wellnitz, Illinois.) Moved due to QRM from a telephone transmitter; operates here only 1700-2300. (Beck, N.Y.)

Belgium — Radio Nationale Belge, 17.840, Brussels, has been heard in Philadelphia at 1100 with musical program and talks. (Southall, Pa.) Evidently, this is beamed to Leopoldville, Belgian Congo.

British Honduras—ZIK-2, 10.598, Belize, is scheduled daily 1330-1358; is partly readable in Georgia; program is world and Honduras (local) news. (Eyles.) Some days may come on as early as 1300.

Burma—Radio Rangoon, 6.035, still has news daily 1000. (Radio Week, South Africa). Confirmed by Dilg, California.

Cameroun—In verifying for Kary, Pa., Radio Douala listed transmitter as a *Temco* with 600 watts output, frequency of 7.950, scheduled daily 1300-1500, but runs to 1600 Sundays; has concert music 1300-1330; local and world news (French) 1330-1350; French songs 1350-1400; "Varietes Douala" 1400-1415; concert music 1415-1500; the Sunday period 1500-1600 is devoted to uninterrupted dance music. A new period is to be heard on Sundays at 0615-0745 with a variety program. On the 1st, 2nd, 15th, and 16th of each month at 1325 they answer letters and reports from listeners (presumably in French), it was stated. Kary heard this station around 1430-1500. Is also heard in Newfoundland. (Peddle)

Canada — Summer schedules effected April 18 by CBC's International Service are: To Europe—0800-1700, CKNC, 17.82; 0800-1045, CKCX, 15.19, and 1045-1700, CKCS, 15.32. To the Caribbean (*English*)—1820-1930, CKNC, 17.82, and CKCX, 15.19. To Latin America—1930-2000 (Portuguese, Tuesdays only), 2000-2100 (Spanish), CKNC, 17.82, CKCX, 15.19. To the Canadian Arctic (*English*)—2310-0005 (Sat.-Sun. only), CKLO, 9.63, and CKOB, 6.09. To Australia and New Zealand (*English*) — 0345-0530 (Sundays only), CHOL, 11.72, and CHLS, 9.61. All these programs are beamed from 50-kw. transmitters at Sackville, New Brunswick, with programs originating from studios in Montreal, Quebec.

CJXC, 6.010, Sydney, Nova Scotia, is heard in Philadelphia, signing on 0645.

Celebes—Major, Western Australia, reports YFA4, 9.380, Macassar, good to 0930 sign-off (is in parallel with YFA10, 5.030, which is good at 0830). However, Pearce, England, reports hearing the 9.350 outlet to 1500 (closedown).

May, 1948

Look at these EXCLUSIVE "G & G" BUYS!

BC-645 XMTR RECEIVER 15 TUBES 435 TO 500 MC

The electronic equipment that saved many lives in the war. Set can be modified to use for 2-way communication, voice or code, on following bands: ham band 420-450 mc, citizens radio 460-470 mc, fixed and mobile 450-460 mc, television experimental 470-500 mc. 15 tubes (tubes alone worth more than sale price!): 4-7F7, 4-7H7, 2-7E6, 2-6F6, 2-955 and 1-WE316A. Now covers 460 to 490 mc. Brand new BC-645 with tubes, less power supply in factory carton. Shipping weight 25 lbs.

BRAND
NEW!

\$975

2 for \$1895



PE-101C DYNAMOTOR for above BC645.....

\$2.95

UHF ANTENNA ASSEMBLY

A rare bargain for UHF experimenters! Consists of 7 aluminum rods, in calibrated lengths as follows:

- 3 rods 12" long for 200-247 Mc
- 1 rod 9 1/4" long for 248-313 Mc
- 1 rod 7 1/2" long for 312-400 Mc
- 1 rod 5-13/16" long for 402-517 Mc*
- 1 rod 4-13/32" long for 512-667 Mc

All rods in handy fabric pouch. Two UHF coaxial coupling insulators included. All BRAND NEW, in original carton, yours for only.....

\$2.45

*2 of these rods suitable for BC-645 Transceiver

TU-75-B XMTR TUNING UNIT

Hams! You'll want this! Tuning unit uses 3-815 tubes. Has 5 tuning condensers, coils, all components easily converted to 2-meter rig! BRAND NEW, in original carton, with tubes, all yours for.....

\$14.95



TERRIFIC VALUE! 24-VOLT STORAGE BATTERY, BRAND NEW! 11-AMP. HRS.

Made by Delco. 12 cells, heavy duty, very rugged. Shipped dry, uses standard

sulphuric acid electrolyte.

VERY SPECIAL... \$14.95

SPECIAL! 24 VOLT


Delco 12-cell Storage Battery
17 ampere-hours. Only a few left at. \$16.95

6-VOLT

STORAGE BATTERY

Navy Standard BRAND NEW. 15 ampere-hour rating.....

\$4.95

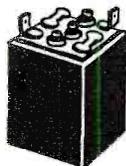


WILLARD 6-VOLT STORAGE BATTERY

27 amp. hrs.

3-cell battery, transparent plastic case, very specially priced.....

\$4.50

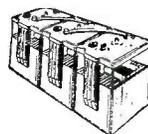


WILLARD 2-VOLT STORAGE BATTERY

20 Ampere-Hours

Exact replacement for GE portables—brand new. Each.....

\$1.49

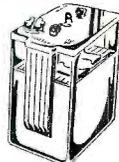

ONE-QUART BOTTLE BATTERY ELECTROLYTE

Made by Willard, for above storage batteries. 1 quart sufficient for two 2-volt cells. Hermetically sealed. SPECIAL. per qt. bottle 95¢

7-PRONG 2-VOLT RADIO VIBRATOR for Portable and Farm Sets Replacement for GE LB 530.....


\$1.65

Down Come Prices! CATHODE RAY TUBES

All Brand New, in Original Cartons



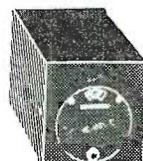5BP1 Lots of 4, each.....\$1.79
5BP4 Lots of 4, each.....1.95
3FP7 Lots of 4, each.....1.49
304TL Eimac, each.....\$2.95
GE-211 Each.....1.22



RCA AVT-112A AIRCRAFT XMTR

2500 to 6500 Kc., 6 tubes, compact, powerful, operates on 12 volt source.

Less crystal, BRAND NEW \$12.95

RADIO RECEIVERS


All Brand New in Original Cartons
BC-454A 3-1 to 6 Mc complete with tubes \$6.95
40-WATT VFO DRIVER
BC-457A 4 to 5.5 Mc.....\$6.95
BC-458A 5.3 to 7 Mc.....6.95

SENSATIONAL Smash Value!

COMPLETE I.F.F. Equipment RC-188-A

Bargain opportunity of a lifetime! This I.F.F. equipment originally cost about \$20,000, you can now buy it for a tiny fraction of cost! Easily converted for Television. Complete assembly consists of Control unit with 5" C.R. Tube, transmitter and receiver assembly (157 to 185 Mc) Indicator unit, and Power Supply (450 watts) operating on 110 volts, 60 cycles AC. All assembled, ready to operate. 62 Tubes included: 8-6V6GT, 9-6SL7GT, 14-6SN7GT, 1-5CP1, 2-9006, 1-6Y6G, 2-6E5, 1-100TH, 2-6J5, 2-2C26, 1-3E29, 1-6H6, 7-6AG5, 3-6AK5, 1-6C4, 3-2X2, 1-6X5GT, 3-5U4GT. Overall size 55" high, 28" wide, 20 1/2" deep. Shpg. weight 85 lbs. Your cost, complete, BRAND NEW, in original packing.....

\$195.00

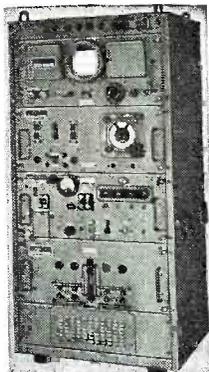

BC367 Interphone AMPLIFIER

Here's a terrific value for you! Unit comprises a 2-watt audio amplifier with input and output transformers; 600 cycle audio oscillator for signalling. Housed in compact metal case. Originally built for Signal Corps. Complete with two 6V6 tubes. Slightly used, your cost.....

\$4.95

BRAND NEW, in original carton.....\$6.95

HANDMIKE T-17

Shure model T-17 mike 200-ohm carbon single button, with press-to-talk switch, 5-ft. rubber cord and plug. BRAND NEW, individually packed, lots of 3 ea. 99c



Please include 25% Deposit with order—Balance C. O. D. Minimum order \$3.00. All Shipments F.O.B. Our Warehouse N.Y.C.


GENUINE MAJESTIC
G & G RADIO PARTS SERVICE
53 VESEY STREET · NEW YORK 7, N.Y.

Sun Radio Presents:

A New Idea In HI-FIDELITY Reproduction

At Low Cost!

BOGEN "PK" SYSTEM

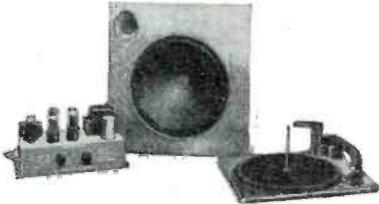

A carefully matched combination of high-quality, custom-engineered components, especially designed for high fidelity reproduction of music.

INCLUDES:

BOGEN PH-10 AMPLIFIER

A virtually humless, high-fidelity, 10 Watt Amplifier, with Multi-Range Tone Control. Frequency response (full range): ± 1 DB, 40-15,000 cps.

WEBSTER RECORD CHANGER

Latest Model Webster No. 148 automatic record changer, equipped with superb new Astatic Nylon IJ crystal cartridge and permanent sapphire needle. This changer features automatic disconnection of pickup during change cycle, eliminating transfer of changing-noise to speakers.

DUAL HI-FIDELITY SPEAKERS

Consists of Alnico V 12" woofer speaker and single University tweeter with cross-over network, all mounted and wired on flat baffle, 16" x 16". Frequency response: 60-15,000 cps. Crossover freq: 2500 cps. The entire unit is fully wired and complete with tubes. Instructions for assembly and mounting included.

LIST \$141.60

COMPLETE PACKAGE

Full trade discounts to all servicemen, dealers, amateurs, students, experimenters, engineers, sound men, etc.

WRITE FOR YOUR COST!

FREE BARGAIN BULLETIN!

Write for Sun Radio's bulletin of big, money-saving specials in sound equipment, as well as bargains for amateurs, hobbyists, etc.

SUN RADIO

& ELECTRONICS CO., Inc.

ESTABLISHED 1922

122-124 DUANE ST. - NEW YORK 7, N. Y. - BARday 7-1840

USE COUPON — PLEASE PRINT

Irv Greene, Mgr. Sound Division
Sun Radio & Electronics Co., Inc.
122-124 Duane Street
New York City 7, N. Y.

Send me further data on the Bogen "PK" System, and full information on MY cost.

Send me descriptive literature on Bogen R602 high-fidelity, low priced, FM-AM tuner

Send me your Big Bargain Bulletin.

Name.....

Address.....

City.....Zone.....State.....

Ceylon—Major, Western Australia, reports ZQO16, 21.630, Colombo, heard at 0700-0800 contacting ZLT7, Wellington, New Zealand, and later with ZLM5, linking this station with ZQO16 in contact with GL12, London, for radiophotos. He says ZOH, 4.900, Colombo, has good signal 0730.

Cushen, New Zealand, recently informed *Radio Australia* that *Radio SEAC*, Colombo, had been heard on 9.915 instead of listed 9.520; may have moved?

China—(NOTE: It is quite likely that by this time most Chinese outlets will have gone on Summer Time, making their schedules 1 hour earlier than listed below.—K. R. B.)

Major, Western Australia, reports these Chinese stations—XPTA, 11.650, Canton, good 0700, relays XGOY news 0900; XLRA, 11.500, Hankow, good 0600, but with heavy QRM; XGAS, 11.680, *Changsha*, good 0700-1000 sign-off, relays AFRS news 0800, carries same program as 7.105; XGOE, 9.868, Kweilin, good 0630; XPSA, 7.010, Kweiyang, poor with QRM, a close watch reveals no *English* used; XGHT, 6.070, Hantan (Communist-controlled), fair 0820; signals from ZBW-

3, 9.525, Hong Kong, improve around 0900. Dilg, California, says Hong Kong's signal remains poor there, signs off 1000; he also reports XGAS often takes AFRS news at 0800, the same as XMAG, 4.275 (Nanking), and JKD, 6.015, and JKE2, 4.860 (both Tokyo). Location of XGAS remains in doubt; New Zealand sources give it as Kungchun. Clark, New Zealand.)

XGIO seems to be on approximately 8.400, has very good signal on West Coast some days around 0830, may run later on occasion. (Dilg) Sanderson, Australia, reports this one as 8.450 at 0530 with AFRS programs; lists it also on 9.99, "very close to WWV," at 0645 with Chinese news and music.

XGOY, Chungking, has left 6.140. Current schedules appear to be: To Australia. New Zealand, East Asia, 15.17, 0455-0630; no *English* except Saturday at 0600 has "Back to the Bible" and Sunday at 0530-0630 has "The Baltimore Gospel Hour." To East Asia, South Seas, 15.17 and 7.153, 0635-0835; news 0700; on Wednesdays at 0735-0750 has "Sermons in Song." To North America, Europe,

(Continued on page 163)

Recording Amplifier

(Continued from page 73)

the proper position of the cable connector. Note also the elimination of one extra tube which was found to be unnecessary but which was shown in the original photographs.

Shunt resistors are inserted across each half of the secondary of T_1 to provide suitable transformer loading for fixed-bias operation.


While all of the improvements mentioned above are recommended, many readers may prefer to use self-bias, and if so, we recommend only the alteration

of the filament supply. In such cases the tap on the full-wave selenium rectifier supply should be adjusted to the value of +75 volts, and the "C"-tap eliminated.

Many readers have requested the design of an amplifier to be used specifically for phono-reproduction and employing 6V6's or 6L6's in the output. We are, therefore, engaged in the design of two amplifiers that provide high fidelity and which incorporate full equalization for almost any type of response required for various types of applications. Complete data will appear in an early issue.

—30—

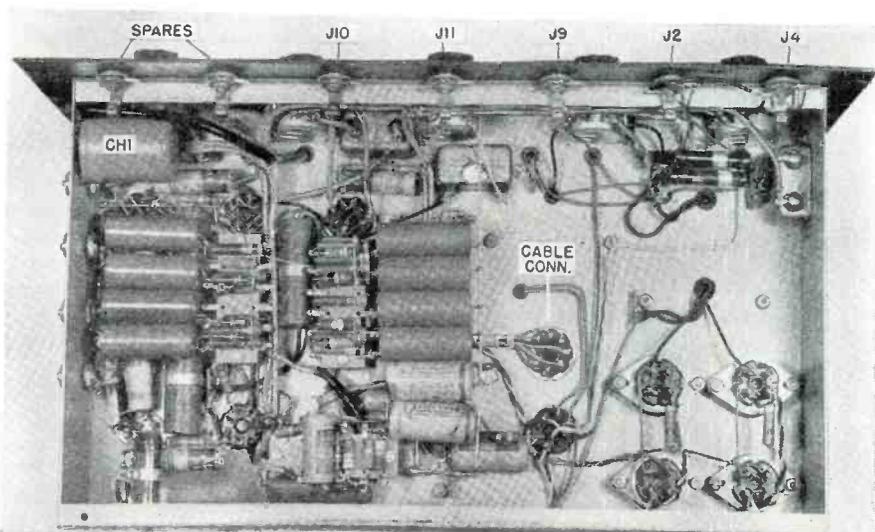Under chassis view showing wiring detail and location of various components.



RADAR AIRCRAFT



DYNAMOTORS


PE 73 CM (G.E.) Power supply for BC 375 Input: 28 VDC Output: 1000 VDC @ 350 Ma. New \$4.95
 BD 77KM Power supply for BC 191 with spare fuse links, etc. Input 11 v.d.c. Output 1000 v. @ 350 ma. Army re-issue, ex. cond. \$3.95
ALFRS: Write for quantity prices and discounts on above items.
 PE 101-C Input 13/26 VDC @ 12.6/6.3 A. Output: 400 VDC @ 135 Ma. 800 VDC @ 20 Ma. 9 VAC 1.12 A. New \$3.49
 PE 86 N. Input: 28 VDC. Output: 250 V19 @ 60 ma. without filter \$3.95
 PG 77. Input 12 VDC. Output 275 VDC @ 110 Ma. 500 VDC @ 50 Ma. \$3.25
 DAG 33A Input: 18 VDC @ 3.2 A. Output: 450 VDC @ 60 Ma. \$2.45
 DM 33: Input 28 VDC @ 7 a. Output: 540 VDC @ 250 Ma. Power supply for SCR 274 modulator \$3.95
 DM 23550: Input: 27VDC @ 1.75 A. Output: 285 VDC @ 75 Ma. \$1.75
 DM 21: Input: 14 VDC Output 235 VDC @ 90 Ma. Power supply for BC 312 \$2.49
 PE 55. Input: 12 vdc @ 25 amp. Output 500 vdc @ 400 ma. (slightly used) ex. cond. \$4.95
 MP 10 G Power supply, using 2 dynamotors. Input: 24-28 vdc. Output: 1000 vdc @ 400 ma. 250 vdc @ 100 ma. New, complete with relays, filters, etc. BENDIX \$40.00
 B-19 power pack (dynamotor). Input: 12 vdc @ 9.4 amp. Output: 275 vdc @ 110 ma. 500 vdc @ 50 ma. New, complete in metal case with 2 plugs, filters, etc. \$4.75
 DM 28-R. Input: 28 v.d.c. @ 1.25 amp. Output: 270 v.d.c. @ 70 ma. New, with enclosed terminal box \$3.25
 ZA/USA .0515. Input: 12/24 vdc @ 4/2 amp. Output: 500 vdc @ 50 ma. Compact square shape, size 7 1/4" x 4 1/2" x 3" \$3.95
 ZA/USA .0516. Input: 12/24 vdc @ 3/4 amp. Output: 275 vdc @ 110 ma. 12 vdc @ 3 amp. Compact square, size: 7 1/2" x 4 1/2" x 3" \$4.25
 35X055. Input: 19 vdc @ 3.8 amp. Output: 300 vdc @ 95 ma. \$2.20
 DM-25: In 12VDC 2.8A Out 250VDC 50 ma. \$2.49
 DM-34: In 14VDC 2.8A Out 220VDC 80 ma. \$2.49
 DM-42: In 14VDC Out 515/1030 VDC 215/260 ma. and 2/8VDC \$3.95

INVERTERS

PE 206-A. Input: 28 vdc @ 28 amp. Output: 80 volts @ 500 volt-amp. 800 cy. Leland Electric. New, complete with instruction book, relays, filters, etc. \$12.50
 PE 218—Input: 25-28 vdc @ 92 amp. Output: 115 volts. 1500 volt-amps. 380/500 cy. Leland Electric. New \$15.00

HI-FI OUTPUT TRANSFORMER

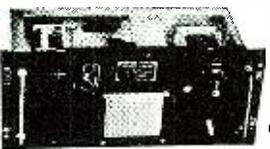W.E. #KS 9496. 9000 ohms p-p plates to 9 ohm voice coil. Handles 250 watts. Freq. response:— 1.25 db @ 100 cy. 0 db @ 1000 cy.—3 db @ 10 kc.—3 db @ 50,000 cy. Weight: 14 1/2 lbs. New \$3.95



TU-6B TUNING UNIT
 From BC 375 xmt. freq. range: 3—1.5 mc. Makes an excellent VFO on 80 meters. Complete—only \$2.25

"Communications"

ARC-5 ACCESSORIES

CONVERSION COILS FOR ARC-5 TRANSMITTERS

M.O. Coils	P.A. Coils	Antenna Loading Coils	Freq. Range
\$1.00 each	\$1.00 each	\$3.85 each	
#6029	#7247	#6033	3-4 Mc.
#6030	#9293	#6034	4-5.3 Mc.
#6032	#9295	#6035	7-9.1 Mc.

CONVERSION KIT, consisting of 1-M-O coil, 1-P.A. coil, 1-ANTENNA COIL, in any one particular frequency range \$2.00
 ARC No. 6558 variable receiving capacitor, 62 mmf/section, 3 sections, .03" spacing, 8 rotors. Worm drive ratio 33:1 \$1.75
 ARC No. 4990 variable xmtg. capacitor, 22.4—115 mmf, .05" spacing, 11 rotors. Each \$1.00
 ARC 5032 Var. Xmtg. capacitor, 29.2—117 mmf, .06" spacing, 16 rotors, worm drive: 96:1 \$1.00
 Single revr. mtg. racks \$1.00
 Dual mtg. racks (revr.) \$1.50
 Single shock mounts for rack \$1.50
 DUAL CONTROL BOXES FOR RCVRs \$1.00

CATHODE RAY TUBES

5BP1 . . . \$1.20



3BP1—\$1.25
 3FP7—\$1.20
 5FP7—\$1.75
 5J12—\$4.00

24-Volt Filament Transformers

Input: 117 V, 60 cy. Output: 24 volts @ 3 A. (As shown) Size: 8" x 3 1/2" x 3" each \$1.50



HEADSETS

Dynamic mike and headset combination. A high quality efficient unit, used in B-19 tank Xmters. Mike & phones comp., new \$2.75

R-15 headsets: 8000 ohms impedance, rubber cushions. Comes with 8" cord & plug PL 55, New \$1.95. Used, in good cond. \$1.60

IIS 30 headset. Insert type headset cuts out background noise, and low impedance (500 ohms) assures efficiency and high fidelity. A MUST for every ham at this price...\$3.85

Xfmr to match 800 ohms output \$3.35

H.V. MICA CONDENSERS

.08 mf @ 1500 VDC. Sprague MX60 \$11.50
 .03 mf @ 2000 VDC. CD 551A-50 . . . 12.75
 .045 mf @ 2000 VDC. Sangamo G1 12.75
 .00115 mf @ 20 KV. Aerovox 1970-404. 25.00
 .001 mf @ 20 KV. Sangamo G3 . . . 25.00
 .0051 mf @ 15 KV. Sangamo G4 25.00
 .006 mf @ 15 KV. Sangamo G3 17.50
 .002 mf @ 15 KV. Sangamo 20.00
 Isolating Capacitor, Cornell-Dubilier PL 1417, 100-110 mmf @ 10 KV AC (peak) Each 3.50

MPRS.: Send your requirements for hardware, Micas, Hardware, resistors, and connectors.

AMATEUR INDUSTRIAL

TEST SET 159TPX



Measures frequency between 150-200 Mc. by heterodyne method. Pwr. Output of XMTTR can be measured directly. Measures DC voltages up to 500 V. Operates on 110 V, 400 cy. Complete with tubes, crystal, calibration chart. Conversion kit for 60 cy \$29.95

SONAR SOUND DETECTION UNIT

Ideal for detecting under water sounds, such as fish swimming in schools, within a 15 mile area. Using a Rochelle salt crystal, which is about 1000 times more sensitive than quartz. It is completely enclosed in a solid rubber sheath. This sound detector was originally used in harbor defense. Coupled to an audio amplifier, this can be found to have many valuable applications. It's the Model JR which contains 7 microphone units \$12.50

TRANSFORMERS

(ALL PRIMARIES 117 V, 60 CYCLES)
 #5084. POWER TRANSFORMER. 550-0-550 volts @ 250 ma. 1/2 sec. tapped @ 400 v, 65 ma. Sec. #2: 6.3 v. @ .3 amp. net. \$5.95
 Power Pair: Xfmr 470 v.c.t. @ 60 ma. 6.3 v. @ 2 amp. PLUS a 6hy 50 ma. choke. Both for only \$1.75

FILAMENT TRANSFORMERS

#5123: 6.3 vct @ 5 amp, 6.3 vct @ 1 amp \$2.15
 #5109: 27 volts @ 8.8 amp, 6.3 v. @ 2.5 amp \$2.75
 #18163: 2.5 v. @ 1.75 amp, 5 v. @ 3 amp, 6.5 v. @ 6 amp, 6.5 v. @ 8 amp \$5.35
 Doughnut Fil. Xfmr. Two 5.1 v. windings @ 5 amp each, 15,000 volt test. \$7.50
 No. 5058: 6.3 VCT @ 2A, 6.3 VCT @ 2A, 6.3 VCT @ 2A \$2.25
 No. 5109, 6.3 VCT @ 1.2 A, 5000 V test \$1.35
 No. 5083: 6.3 V NCT @ 6A, 6.3 V NCT @ 1.5 A \$1.40
 No. 5056: 6.3 VCT @ 9 A, 6.3 VCT @ 2.2 A, 6.3 VCT @ 2.2 A \$2.50
 No. 5057: 6.3 VCT @ 1 A, 5 VCT @ 3 A, 5 VCT @ 3 A \$2.50
 UX 6899: 5 V @ 5.5 A, 5 V @ 5.5 A, 29,000 Volts Test \$24.50
 #5083: 6.3 vct @ 1 amp, 5 v. @ 2 amp. \$1.55

POWER CHOKES

6 Hy @ 150 ma. \$1.50
 6 Hy @ 300 ma. \$3.25
 1 Hy @ 800 Ma. 7.5 Ohms \$8.95
 Dual-Choke: 2-2 Hy @ 100 Ma. \$1.90
 Dual Choke: 7 Hy @ 75 Ma. 11 Hy @ 60 Ma. \$1.50
 8.5 h @ 135 ma. \$1.50
 25 h @ 65 ma. \$1.10

MICROWAVE TUBES

TUBE	FREQ. RANGE	PK. PWR.	OUT PRICE
2131	2820-2880 mc.	295 Kw.	\$15.00
2121-A (725-A)	9345-9405 mc.	50 Kw.	\$25.00
2122	3267-3333 mc.	265 Kw.	\$15.00
2126	2992-3019 mc.	275 Kw.	\$15.00
2127	2965-2992 mc.	275 Kw.	\$15.00
2132	2780-2820 mc.	285 Kw.	\$15.00
2138	PKG. 3249-3263 mc.	5 Kw.	\$25.00
2135	PKG. 9345-9405 mc.	50 Kw.	\$25.00
3131	24,000 mc.	35 Kw.	\$17.50
W.E. 700-A	680-710 mc.	100 Kw.	\$35.00
W.E. 720BY	2800 mc.	1000 Kw.	\$25.00

MAGNETS for 2121-A (725-A), 2122, 2136, 3137, 2126, 2127, 2131, 2132 and 3131, each \$8.00

Field Strength Gauss	Distance pole faces	Bet. pole faces	Pole Face Diameter	Price
4850	1/2"	3/4"	3/8"	\$8.00
1500	1 1/2"	1 1/2"	1 3/8"	\$8.00
1000	Adjustable	Adjustable	Adjustable	\$12.00
(Electromagnet)	2 3/4" to 3"	2 3/4"	3/8"	\$4.00

ANTENNA, AN/122-A. Used in 4-element adcock arrays for high gain and directivity (as shown), each dipole element is 12' long, made of 3/4" tubing. Excellent for that new 6 or 2-meter beam. Don't miss this great value. \$5.65 each or 4 for \$20.00

ANTENNA AN/104-A. The famous Ax-handle antenna, used with the SCR 520. Ideal for mobile quarter wave, because of its streamline construction; or 2 units can be used to form a dipole for 2 meters or for TV and FM reception. Consists of copper sheath 21" long moulded about a wooden support, with 83-1R coax connector. \$7.95 each or 2 for \$13.95

AN/128-A. For high gain and directivity on 2 meters. Consists of 2 vertical elements working against a square reflector, approx. 3' x 4'. Impedance is 50 ohms. \$40.00

WIRE RECORDING MAGAZINES

Magazine for KS 12009 recorder, made by W. E. Comes with wire for 1/2-hour recording. Has elapsed time indicator, recording and erase features. Size: 14 1/4" L x 7" W x 5 3/4" H. Less Drive Motor \$30.00

THOUSANDS OF ITEMS IN STOCK. WRITE FOR YOUR NEEDS.

All merchandise guaranteed. Mail orders promptly filled. All prices, F.O.B. New York City. Send Money Order or Check. Shipping charges sent C.O.D.

COMMUNICATIONS EQUIPMENT CO.
 131 N. Liberty Street, New York City 7, N. Y. Digby 9-4124

A COMPLETE LINE OF MICROWAVE EQUIPMENT IN STOCK. WRITE FOR MICROWAVE FLYER



HARD TO GET LEOTONE SPECIALS

WIRE AND TAPE RECORDING COMPONENTS

Essential "hard-to-get" basic parts for units described in Radio News, Feb., '48.

WIRE RECORDING-PLAYBACK HEAD. Precision built Three-Coil (Record, Playback & Erase), 4 Pin plug-in type. Moulded bakelite case (1 1/4" x 1" x 3/8"). "y" grooved to provide maximum wire contact & sensitivity. \$6.95

WIRE SPOOL SPINDLE. Polished aluminum. Takes spool with 1 1/8" hole. 3/4" shaft hole. 3/8" deep. \$3.99

RM-4 RECORDING MOTOR. Recommended heavy duty type. 110V., 60 cycles. Adaptable to WIRE, TAPE or DISC RECORDING & PLAYBACK. 5/16" O.D. shaft. 3 3/8" sq., 2 1/2" deep. Less turntable, mtg. plate & reduction drive wheel. \$14.95

PERMALLOY RECORDING TAPES. Hydrogen annealed. Specifically for use in constructing TAPE RECORDING-PLAYBACK HEADS Per ounce (containing laminations). \$4.00

ALNICO ERASE MAGNET. For TAPE or WIRE. "U" shape; polished poles. 3/4" x 3/8" x 3/16". \$1.39

Send for latest Illustrated ALNICO MAGNET supplement.

RADIO HARDWARE TREASURE. An indispensable assortment of approx. 1000 nuts, screws, washers, lugs, etc. \$4.99

CASED POWER RHEOSTAT. 25 watt-350 ohm, ceramic. Moisture-proof metal case (3 1/2" x 3 1/2" x 3") with bronze pointer knob. Shpg. wt. 4 lbs. \$9.98

HEARING AID PARTS



Famous make miniature audio units having many applications where space is limited.

BONE CONDUCTION RECEIVER. Sensitive moving armature type. Makes excellent CONTACT (musical pick-up) MIKE; MINIATURE or PILLOW SPEAKER. 1 1/2" x 3/4" x 1/2". 1 ohm impedance. \$2.95

MIDGET OUTPUT TRANSFORMERS (1 1/2" x 1/2" x 1/2"). One of the smallest made. High imped. to Voice Coil. For personal & portable set, intercoms, etc. \$4.99



MIDGET AUDIO CHOKES (3/4" x 3/4" x 1/2"). 4500 ohms DC. Use in filter circuits, impedance coupling, etc. \$4.99



ALNICO V MAGNETIC PHONE UNITS (HS-30 headset replacements). Wide freq. response & sufficient volume for use as PM or PILLOW SPEAKER; DYNAMIC or CONTACT MIKE. 250 ohms imped. 3/4" O.D., 1/2" deep. \$3.99

TUBES! TUBES! TUBES!

STOCK UP NOW AT THESE LOW PRICES— All in perfect condition, but in unsealed cartons. Most types available at up to 80% off list. Every tube guaranteed 90 days.

#20, 27 or 31 \$2.99
 #12, 75, 76, 77, 78, 6H6 or 6K7 \$3.99
 #36, 37, 39, 5Y4, 5W4, 5Z4, 6C5, 6P5, 6J7, 6X8, 6SA7, 6SD7, 6SF7, 6SH7, 6S7, 6U7 or 12SK7 \$4.99
 #1A7, 1H5, 6U5, 6X5, 7A7, 50, 50B5 or 50L6 \$5.99

TUBE CARTONS, PLAIN

Miniature (1" sq. x 2 1/4") per 100 \$98
 GT size (1 1/4" sq. x 3 1/4") Per 100 \$1.25
 Medium (1 1/2" sq. x 3 1/4") Per 100 \$1.49
 Large (2" x 5") Per 100 \$1.79

4 TUBE AMPLIFIER (2-7C5, 7F7, 7Y4). See Radio Craft, July, '47, for conversion to Phono Amplifier. Orig. supercharger control, 110v., 400 cycle. Contains: power trans., 7 mica & oil cond., 7 resistors, 4 loctal sockets. PLUS other components worth several times the price. Black wrinkle finish case & slide-in chassis. 3 3/4" x 4 1/2" x 3 3/4". Shpg. wt. 4 lbs. Less tubes \$1.49

SPEAKER CONE KIT

12 asstd. 4" to 12" molded and free-edge (magnetic incl.) Less voice coils \$2.00

Get on our mailing list • Always something new • Factory Repair Service on all speakers and phono pick-ups • Minimum Order \$2.00 • 20% deposit required on all orders • Please add sufficient postage



MAKERS OF CONES AND FIELD COILS
 65-67 DEY STREET, NEW YORK 7, N.Y.
 WORTH 2.0284-5
 12,000 SQ FT OF RADIO PARTS

What's New in Radio

(Continued from page 88)


Craft Company of Brooklyn, New York has begun production of a series of hardwood cabinets.

The cabinets feature 8" speakers, lucite masks, safety glass, recessed base design, and felt cushioning. In addition, the company is manufacturing a "liquor service cabinet" which may serve as a base for table model television sets.

MULTI-RANGE V.O.M.

A wide range tester with several new features has been introduced by The Triplett Electrical Instrument Co.

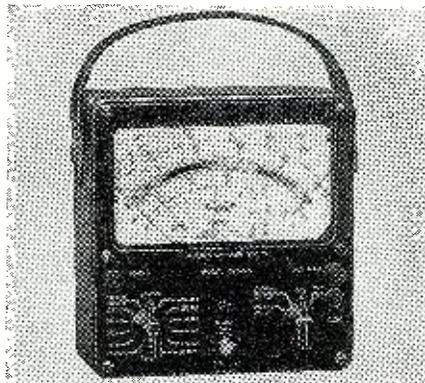The new unit has a 5.6" mirror scale for improved reading accuracy and features 39 ranges. Resistance measurements can be made on ranges covering from 0-2000 at the low end to a high of 40 megohms. Dual d.c. voltage ranges 2500 and 5000 at 20,000/10,000 ohms/volt respectively provide double the number of full scale readings usually



available. The a.c. volt ranges to 5000 at 10,000 ohms/volt permit checking audio and high impedance a.c. circuits where a vacuum tube voltmeter is usually required. Low voltage ranges permit direct measurement of many bias and output voltages. The d.c. current ranges are covered from 0-50 microamperes to 0-10 amperes while decibels may be read from minus 30 to plus 69 db.

The Triplett Electrical Instrument Co., Bluffton, Ohio will provide added details on the Model 625-NA to those requesting such information.

SOLDERING GUN

A new type soldering gun designed especially for the radio, television, and appliance serviceman has been announced by Weller Manufacturing Co.

A small spotlight, placed between the terminals of the loop tip, keeps the work in plain sight. The tip can be flexed to suit the job and can be shaped to get into difficult and tight places. The spotlight goes on automatically when the trigger switch is closed for heating the gun. It spots the joint to be

MAY SPECIAL

RESISTOR KITS \$1.45 100 assorted carbon and wire wound resistors . . . 1/2 to 10 watt. Wide range of value. All standard items.

CONDENSER KITS \$1.75 50 assorted paper and mica condensers . . . all new . . . good value.

Wireless Phono Oscillator \$4.52

Operates as far as 100 ft. from radio and can be used with automatic record changer and players . . . complete with 2 tubes all wired and tested. Diagram.



Phono Pre-Amplifier \$4.95 This unit is for G. E. Reluctance type cartridge. Completely wired, tested. Supplied with diagram, and tube 6SC7.



Mike and Phono Amplifiers \$4.95 This unit sold complete with power transformers, 3 tubes and 3 controls . . . all wired and tested. Diagrams supplied.

RADIO PARTS

Astatic Crystal Pickups \$1.89
 Astatic Crystal Cartridges, L-70A, L-26A, L-40 1.60
 Selenium Rectifiers 100 MA69
 1/2 Meg. Volume Controls & Sw. Long Shaft.35
 Osc. Coil 12SA713

STANDARD MAKE CONDENSERS

50x50—150V.	\$.45	.01, .02, .05	\$.06
2x8—450V.50	1" or 5" PM Spk.	1.02
2"—25V.30	6" PM Speaker	1.53
2"—50V.30	5" 450 ohm Dynamic
2"—450V.40	with output	2.39

All Prices F.O.B. N.Y.C.—On C.O.D. 25% Dep.

THE ROSE COMPANY

88 West Broadway Dept (N) N.Y. 7, N.Y.

"MUST" for TELEVISION SERVICING

for trouble shooting on the kinescope high voltage power supplies.

HIGH VOLTAGE KILOVOLT METERS

0—15 KV
 0—30 KV
 0—50 KV
 20



MICROAMPERES FULL-SCALE!

50,000 ohms per volt

Will not overload the cathode ray tube power supply or change picture size.

SAFE • ACCURATE • PORTABLE

A 10" long lucite safety handle permits voltages to be measured without turning the H.V. power supply on and off to connect in the voltmeter. Housed in oak case with black bakelite panel and leather carrying handle.

Don't take chances of burning out valuable test equipment! Use a meter designed especially for measuring ultra high voltages.


USED BY ALL LEADING TELEVISION MANUFACTURERS AND THEIR SERVICEMEN THROUGHOUT THE COUNTRY: R.C.A.; Dumont; Sylvania; Philco; U.S. Television; Tele-tone; R. H. Scott and others.

15, 30 KV ranges 11" x 8" x 5" \$69.50
 50 KV range 13" x 9" x 6" \$110.00
 F.O.B. New York

BETA ELECTRONICS CO.
 1762 Third Ave., New York 29, N. Y.

soldered in the maze of wiring, thus facilitating the work and saving time.

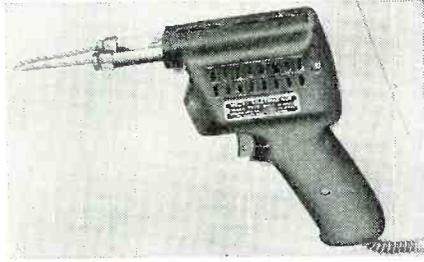The gun features 5-second heating which makes the tool suitable for intermittent duty. The unit operates on a.c. only. Two models are available, one with a single heat of 100 watts, the



other with a dual heat control which provides 100 watts normal heat and a 35% instantaneous reserve heat.


Weller Manufacturing Company of Easton, Pennsylvania will supply additional details on request.

DISTORTION-NOISE METER

The Specialty Division of General Electric Company has announced production on a new distortion and noise analyzer, the Type YDA-1.

Designed for broadcast, television, research, and developmental applications the new unit combines four basic functions. It will measure percentage of distortion down to .1 per-cent, measure hum or noise present on an audio signal, act as a high sensitivity vacuum tube voltmeter, and perform as a frequency meter over the range 50 to 15,000 cycles.

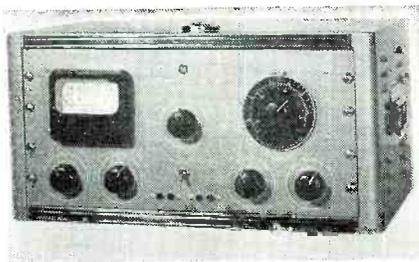Distortion ranges of 1, 3, 10, 30, and 100 per-cent full scale are provided.



Accuracy is 5 per-cent of full scale, plus .1 per-cent.

Further information on the Type YDA-1 distortion and noise meter is available from the Specialty Division, General Electric Company, Electronics Park, Syracuse, New York.

SMALL TRANSMITTER

Harvey-Wells Electronics, Inc. has introduced a new small transmitter, the TBS-50. This 50 watt unit has been designed for phone or c.w. operation with eight bands from 80 to 2 meters with bandswitch and no plug-in coils.

The transmitter is crystal controlled
May, 1948

SAVE \$ ON RADIO SURPLUS

ATTENTION: Prospectors, Explorers for Hidden Treasures!

Do you seek hidden treasures or rare metallic ores? If so, construct a U.S. Army Type of Metallic Mine Detector from these U.S. Army Mine Detector Amplifiers that we are offering at a ridiculously low price. Complete Amplifier (as illustrated) (less tubes and batteries) with Battery case and cables. Cables, headphones and Jack (no phones). Complete Army wiring diagram, U.S. Army DETECTOR SET Amplifier Type AN/PBS-1, as described... Only

No C.O.D.'s. Eveready 45 volt batteries #482, \$1.65 ea., 6 volt A. 73c. 2-1N5 tubes, 95c ea.

U.S. SIGNAL CORPS 5 METER SHORT WAVE XMITRS.

(72.2Mc) XMITRS and TUBE only. Less mike, batteries and antenna. One 1 1/2 volt dry cell and 67 1/2 volts of B operates it. Just attach di-pole, key or mike, connect the batteries and it's ready to use. Signal Corps spec. wired with silvered wire, mica condensers, and precision resistors. Highly stable circuit with Lo-Loss silvered inductance. (Adjustable padder) Schematic supplied. Converts easily to walkie-talkie and Ham bands

SELENIUM RECTIFIERS
Lost of 12.....65c Single Lots.....75c

GENUINE SIGNAL CORPS FEATHER-WIGHT HEADPHONES WITH CORD AND PLUG 2000 OHMS—8000 OHMS IMPEDANCE\$1.00

SPRAGUE—NATIONALLY KNOWN OIL FILLED FILTER CONDENSERS
1.—MMFD—1000 working volts. 4 for\$1.00

FAMOUS BRAND RECORD CUTTING HEAD
These units are all Brand new and were made for a nationally advertised manufacturer to be in their quality Home Recording Radios. Size 1 1/2"x2 1/2" ready to fit your cutting arm or bracket. SPECIAL\$2.95

3 BAND ALL-WAVE DIAL 6" DIAMETER.....75c

AMPLIFIER CHASSIS, SIZE 18"x8"x2 1/2" BLUE CRACKLE FINISH DRILLED FOR CONDENSERS TRANSFORMER AND SOCKETS65c

STROMBERG-CARLSON, 3 BAND ALL-WAVE TUNING UNIT, COMPLETE WITH TRIMMERS, BY-PASSES AND BAND SWITCH, READY TO INSTALL—DIAGRAM, etc.\$3.75

8 OR 9 GANG PUSH BUTTON TUNING UNIT (PLEASE SPECIFY). COMPLETE WITH BUTTONS25c

24 VOLT D.C. AIRCRAFT MOTOR, APPROX. 1/2 H.P. ALMOST NEW\$1.50

U.S. AIR FORCE RESISTOR ASST. 1/4-1/2 WATT —100 PIECES95c

U.S. AIR FORCE MICA COND. ASST. 100 PCS.\$1.25

Low-Loss-Short Wave Variable Condensers 1/2" Shaft Type	3 GANG T.R.F. VARIABLE CONDENSERS .000365 Cap
3 Plate—12-17 MMFD.15c	D.P.D.T. SLIDE
5 Plate—20 MMFD.20c	T O G G L E
9 Plate—36-40 MMFD.25c	SWITCH23c
14 Plate—55-60 MMFD.27c	
27 Plate—100-110 MMFD.45c	
37 Plate—150 MMFD.50c	
38 Plate—150-155 MMFD.55c	H. & H. SP.ST. T O G G L E SWITCHES—
53 Plate—210-21 MMFD.60c	8 for\$1.00

Lock Type Air Trimmer Variable Condensers

3 Plate—12-15 MMFD.10c	AMPHENOL
5 Plate—20 MMFD.13c	2 piece 4-pole . . .
8 Plate—30-35 MMFD.14c	Male and Female
10 Plate—40 MMFD.14c	Separable plug
13 Plate—50 MMFD.14c	Male is for panel
14 Plate—56 MMFD.20c	mount. Female for
20 Plate—80-100 MMFD.25c	Flex. cord. A steel
27 Plate—100-110 MMFD.35c	at only. .35c per pr.

SIGNAL CORP TRANS. KEYS—\$1.49 per C; 3c each

4 PRONG WAFER SOCKETS—\$1.49 per C; 3c each

ISOLANTITE OCTAL WAFER SOCKETS—\$4.25 per C.....6c each

ISOLANTITE UNDER PANEL CLAMP SOCKETS—\$4.50 per C.....5c each

PHILCO 4 MF—300 V—1 1/2" CAN CONDENSER—\$8.00 per C.....10c each

W-L—10 W. 1,000 ohm POWER RHEOSTAT—29c ea.

5-6 PRONG WAFER BAKELITE SOCKETS—\$2.50 per C

100 ASST. SOCKETS—4-5-6-7—OCTAL \$3.50 per C

1 R.C.—1,000 OHM WIRE WOUND POTENTIAL—15c

30 HY-FILTER CHOKE SHIELDED.....49c UNSHIELDED.....39c

100 ALLEN BRADLEY—1 WATT—1/2 MEG RESIS.\$1.25

100 ERIE—1 WATT—2,000 OHM RESIS.\$1.15

10 WIRE WOUND RES. KIT—5-50 W. ASST.49c

2 METER RF CHOSES.....7c

PHONE PICK-UP REST. RUBBER—1 HOLE MTG. 6c

YAXLEY 2,000 OHM WIRE WOUND RHEOSTATS.....\$1.00 per doz.

RCA-VICTOR NEEDLE CAPS—2 PIECE TOP & BOTTOM.....10c ea.

CARTER WIRE WOUND C.T. VARIABLE 20 OHM RECTIFIERS.....\$1.00 per doz.

C.T. TAPPED VOLTAGE DIVIDER—200 WATT—230 OHM—MOUNTED ON ASBESTOS BASE—TAPPED AT 180-205 ohms.....25c

RCA 6 OHM POWER RHEOSTATS.....39c

RCA RUNNING BOARD AUTO AERIAL.....49c

PHILCO AUTO SUPPRESSORS—\$5.00 per C; 7c ea.

3 BAND RADIO SET CHASSIS short wave continuous to broadcast. These chassis are incomplete. Manufacturer started them, went bankrupt. Chassis has variable condenser, filters, 6 tube super-het., all filament wiring complete. 13y-pass condenser, resistor, padders, band-changing switch, tone control, volume control, all wired ready, less transformers less IF (IF 50c each, extra). This is for straight AC; may be converted for AC-DC. Limited quantities only.....\$2.50 each

6 TUBE 3 BAND AC-DC CHASSIS complete with filter condensers, volume control, dial drive, tone control, band switch, by-pass condensers, resistors, sockets, all wired ready for use with phone attachment (IF 50c each, extra)\$2.00

Signal Corps Flex. hook-up wire asst. contains approx. 150 ft. asst. colors, glass insulation. 1 lb.....25c

GENERAL ELECTRIC 60 CYCLE WATT HOUR METERS, slightly used, perfect condition, same as used in your home. 110-125 volts. 5 Amperes.....\$3.50
10 Apm.\$4.50; Glass enclosed \$1.00 extra

PHILCO MAGNETIC RELAY TAP SWITCH. Operates on 6 V DC—15 V AC. When contact is made relay operates rotary contacts switch to 20 different contacts. Brand new89c

Philco rotary tap tone control, 3 position, including condenser. Only 1 wire to connect to grid of audio tube. 1/4" shaft 25c

Oil-filled by-pass condenser asst. removed from govt. apparatus—electrically perfect. dual 1-600 volt—5-600 volt. 25 piece asst.\$1.00
I. C. A. 30 MH RF choke.....25c

Television or Oscilloscope power transformer for use up to 5" tubes. 117 V. pri.-60 cy. 1-2 1/2 V-25 amp. 2-5 V 2 amp., 1-470 V-10 MI. 1-750 V-CT-60 Mil.\$2.95

Grind your own crystals—Pure Brazilian Quartz, all sizes and thicknesses—1/2 lb. package.....\$1.00

National Velvet Vernier Dial Attachment—1/4" shaft—converts any dial to slow motion vernier.....75c

340 degree dial with 10 push button attachment—1/4" shaft—ideal for Xmitters—Sig Gen. or Osc.49c

Yaxley Band Switches—3 gang 3 posit. 3 band.....30c
5 gang 5 posit. 4-5 band.....40c

Trimmer-Padder Asst.—all isolantite—singles, dual, triples—100 asst. pieces.....\$2.25

Signal Corps V. T. I receiving tubes—\$1.00 per doz.

Walkie-Talkie Telescoping Aerials—extends 36".....75c

MAGNAVOX—12"—1000 ohm Dynamic speakers.....\$3.95
8"—10,000 ohm1.35

P. A. System wall speaker box. 8" diameter covering screen grille for hospital, factory or school installation. Will take up to 6" speakers. Each.....35c
Lots of 25, each.....25c

Radio Hardware, nuts, bolts #62-832 solid brass cadmium plated—\$7.00 value. 4 lbs. for.....\$1.00

Spaghetti Assortment75c

30-WATT—6L6 BEAM POWER AMPLIFIER KIT. COMPLETE KIT OF PARTS WITH ALL NECESSARY PARTS—TUBES—READY TO ASSEMBLE AND WIRE—NOTHING ELSE TO BUY—BUT SPEAKER AND MIKE. CHASSIS 20" LONG x 8 1/2" WID x 4" HIGH CADMIUM PLATED STEEL EXTRA HEAVY PLATE SUPPLY—IS PROVIDED BY AN OVERSIZED EXTRA HEAVY TRANSFORMER 6" x 4 1/2" x 4"—(1) FILAMENT SUPPLIED BY AN EXTRA HEAVY TRANSFORMER FILTER. BY PASS AND FILTER CONDENSERS, SOCKETS ALL READY MOUNTED ON CHASSIS. VOLUME AND TONE CONTROLS WITH SEPARATE AC SWITCH ARE PROVIDED. CIRCUIT IS THE LATEST TYPE OF PHASE INVERTER SYSTEM USING 1-5U4, 2-6L6, 1-6C5, 1-6S7, 1-6N7. CHASSIS HAS AMPLE ROOM TO WORK ON OR ADD MORE TUBES—TERMINAL STRIPS FOR MOUNTING RESISTORS, ETC. ARE ALSO PROVIDED. BRAND ALL PARTS ARE SIGNAL CORPS SPEC. BRAND NEW NEVER USED BEFORE. A LARGE PICTORIAL DIAGRAM IS PROVIDED SO THAT A NOVICE MAY BE ABLE TO ASSEMBLE THIS KIT WITH EASE, MERELY BY FOLLOWING THE POINT TO POINT CONNECTIONS THAT ARE OULINED ON THE PRINT. COMPLETE 6L6 KIT, LESS SPEAKER\$18.95

TUBES—6SN7—45c. 51—39c. 2A7—39c. 55—39c. 1171—52c. 2-25c. 2-15, same as #24—20c. DRY ELI. FILTER COND. ASST. CONTAINS 10 PIECES ALL BRAND NEW 150-450V. \$1.10
6 ASST. WET ELECTROLYTIC CONDENSERS 59c

RADIO EXPERIMENTER'S SURPRISE PACKAGE—CONTAINS BY PASS & FILTER CONDENSERS, SHORT WAVE TUNING UNITS, POWER AND AUDIO TRANSFORMERS, SOCKETS, RESISTORS, CHASSIS HARDWARE, OVER 15 LBS. OF VALUABLE PARTS\$4.95

MINIMUM ORDER \$2.00—NO C.O.D. SHIPMENTS—PLEASE INCLUDE POSTAGE
NEWARK SURPLUS MATERIALS CO. 324 Plane Street Dept. N Newark 1, N. J.

www.americanradiohistory.com

LARGEST WAR SURPLUS STORE IN AMERICA



METER BARGAIN BUYS!

Dejur model 210 0-2MADC 2 1/2" round
Westing RX-35 0-1 MADC 3/4" sq. 4.95
Weston 478 0-150 VAC 3 1/2" 4.95
Roller-Smith MR34W 0-150 VAC 3 1/2" round
Weston 506 (blk. face) 0-200 MADC 2 1/2" 4.95
Dejur 210 0-50-0 MADC 2 1/2" 2.95



INVERTER PE218-C 19.95

Input 28 volts. Exciting voltage 28 v. Output 115 VAC at 1500 watts. 1 phase, 400 cycles. Complete with starting relays, filter and mounting bracket. New.

Dynamotor DM 32

For 274 N Receiver. Input 28 VDC. Output 250 VDC at 60 mls. Now95c



DYNAMOTOR DM33A

28 volts output 575 V, 160 mls. For 274 N modulator1.95



DYNAMOTOR BD-AR

Input 28 VDC, output 375 volts. 150 mls with hash filter & mounting bracket. New1.95

DM 28—For BC 348 Receiver.....95c




1147 B U.H.F. SUPERHET RECEIVER
Frequency 100 to 160 megacycles contains 7 tubes — some lokal type, some ocal, 2 gang butterfly condensers, single dial control, less power supply..... 4.95

5 assorted DYNAMOTORS 3.00
(less filters)

DYNAMOTOR

BD 77C

6.95

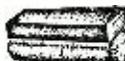

Input 14 volts, output 1000 V at 350 mls. Comp. with mounting bracket, hash filter and solenoid starting relay.

PE 73 C—Input 28 volts, output 1000 V at 350 mls. Comp. with mounting bracket, hash filter, and solenoid starting relay. New..... 4.95



BC 375 TUNING UNITS
TU-6B, TU-5B, TU-7B, TU-8B, TU-9B, TU-10B, TU-26B. Will ship no. indicated 'til sold out, then nearest no. sent.

(without cases) **1.75** 5 for 8.25


(with cases) **2.25** 5 for 10.95

BK 22 RELAY BLOCK, 95c

BEACON RECEIVER 1206B

Six tube superhet, 200 to 400 kilocycles.

3.95

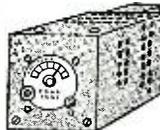

JOHNSON'S FAIR

No orders filled for less than \$2.00 • 8th & Allegheny, Philadelphia 40, Pa. • F.O.B. Phila.



TALK ANYWHERE

TO ANYONE ANYTIME instantly with "Inter-Talkie" the new Lowest Cost talking system. No Tubes—No Electric Plugs Needed! Simple to install Yourself — Takes Only A Few Minutes! Most Beautiful Design! Real loudspeaker volume—No Phones—radio, buzzers, lights—bells—howls—hum or trouble! Always ready to use. Sets On Desk or Hangs on Wall! Average Yearly Cost 30c.

GUARANTEED 3 YEARS!

2 Way System \$19.95—"Up To 7 Way" \$12.95 Each For Homes—kitchen to upstairs, bedroom, front door. For Business, Offices, Stores, Cafes, etc.—Works Up To 1/2 Mile! Write For Free Details! Dealers Write!

PAKETTE RADIO CO.

Dept. RN-5

Kearney, Nebr.

A CAREER WITH A FUTURE! TELEVISION

SHOP WORK • SHOP TECHNIQUES • THEORY • FULLY EQUIPPED LABORATORIES
• **RADIO SERVICE & REPAIR**
• **F. M. & TELEVISION**
• **TRANSMITTER COURSES**
Preparing for F. C. C. LICENSES
• **RADIO TECHNOLOGY**
MORNING • AFTERNOON • EVENING CLASSES • MODERATE RATES • INSTALLMENTS
AVAILABLE UNDER G. I. BILL

DELEHANTY SCHOOL OF RADIO • ELECTRONICS • TELEVISION
105 EAST 13th STREET, NEW YORK 3, N. Y. • DEPT. S
LICENSED BY STATE OF NEW YORK

SELENIUM RECTIFIERS

FULL WAVE BRIDGE TYPES

Input	Output	Current	Price
From 0-18 V.A.C.	From 0-14 V.D.C.	1 AMP.	\$2.49
0-18 V.A.C.	0-14 V.D.C.	3 AMP.	3.49
0-18 V.A.C.	0-14 V.D.C.	5 AMP.	4.95
0-18 V.A.C.	0-14 V.D.C.	10 AMP.	7.95
0-18 V.A.C.	0-14 V.D.C.	15 AMP.	10.95
0-18 V.A.C.	0-14 V.D.C.	20 AMP.	13.95
0-18 V.A.C.	0-14 V.D.C.	30 AMP.	19.95

Input	Output	Current	Price
From 0-36 V.A.C.	From 0-28 V.D.C.	150 MA	\$1.25
0-36 V.A.C.	0-28 V.D.C.	2 AMP.	4.95
0-36 V.A.C.	0-28 V.D.C.	5 AMP.	7.95
0-36 V.A.C.	0-28 V.D.C.	10 AMP.	13.95
0-36 V.A.C.	0-28 V.D.C.	15 AMP.	19.95
0-36 V.A.C.	0-28 V.D.C.	20 AMP.	25.95
From 0-120 V.A.C.	From 0-100 V.D.C.	2 AMP.	14.95
0-120 V.A.C.	0-100 V.D.C.	2 AMP.	19.95

RAYTHEON RECTIFIER CHOKES

.03 Henry at two amperes.....\$2.25
.02 Henry at five amperes..... 3.25

HALF WAVE TYPES*

Input	Output	Current	Price
From 0-18 V.A.C.	From 0-7 V.D.C.	3 AMP.	\$2.25
0-18 V.A.C.	0-7 V.D.C.	5 AMP.	2.95
0-18 V.A.C.	0-7 V.D.C.	10 AMP.	4.95
0-18 V.A.C.	0-7 V.D.C.	15 AMP.	6.95
0-18 V.A.C.	0-7 V.D.C.	20 AMP.	8.95
0-18 V.A.C.	0-7 V.D.C.	25 AMP.	10.95

Input	Output	Current	Price
From 0-36 V.A.C.	From 0-14 V.D.C.	3 AMP.	\$2.95
0-36 V.A.C.	0-14 V.D.C.	5 AMP.	4.95
0-36 V.A.C.	0-14 V.D.C.	10 AMP.	7.95
0-36 V.A.C.	0-14 V.D.C.	15 AMP.	10.95
0-36 V.A.C.	0-14 V.D.C.	20 AMP.	13.95
0-36 V.A.C.	0-14 V.D.C.	25 AMP.	16.95

*Use with capacitor to obtain any voltage up to twice rated output.

CAPACITORS

1000 MFD., 15 V.D.C. 98c
3000 MFD., 25 V.D.C. \$2.45
100 MFD., 350 V.D.C. 1.69

FULL WAVE BRIDGE RECTIFIER TRANSFORMERS

PRIMARY	SECONDARY	TO DELIVER	CURRENT	PRICE
115 V.A.C. 60 cy.	10 V.A.C.	7 V.D.C.	18 AMP.	\$3.75
115 V.A.C. 60 cy.	15 V.A.C.	12 V.D.C.	12 AMP.	3.75

It would be impossible to give a complete listing of all our rectifier types. Our engineering staff is at your service to help you work out the application of selenium rectifiers to your specific problems. Write us for quotations or further information on capacitors and transformers to be used in conjunction with selenium rectifiers.
25% Required on all C.O.D.'s—Add 10% for Parcel Post.

OPAD GREEN COMPANY • 191 GREENWICH ST. Dept. 2
NEW YORK 7, N. Y. • Phone: BEEKMAN 3-7385

on all bands yet requires no oscillator or multiplier tuning. Because of its compact size the TBS-50 may be used for either fixed station or mobile operation.

As an exciter unit, the r.f. output is capable of driving a 1000 watt Class C amplifier, the separate winding on the modulation transformer permits the audio system to be used to drive a 500 watt modulator. The TBS-50 employs a pi antenna, matching the network. There is a separate coaxial output terminal for 144-148 mc. antenna.

The power input to the final is 50 watts with 450 volt power supply on bands 1 through 7 and 30 watts on band 8. The unit has a 6AQ5 crystal oscillator, a 6AQ5 buffer-multiplier, an 807 final amplifier and two 616 Class B modulators. The entire transmitter is housed in a steel cabinet measuring 8"x12"x8".


For complete information and literature on the TBS-50 write directly to *Harvey-Wells Electronics, Inc.*, Southbridge, Massachusetts.

DYNAMIC NOISE SUPPRESSOR

Herman Hosmer Scott, Inc. has developed a new and improved model of the *Scott Dynamic Noise Suppressor*, the Type 910-C.

Designed to allow broadcast stations to transmit recorded music with a wide frequency range and greatly reduced background noise, this new unit functions on the exclusive dynamic band-pass principle which is inherently distortion free.

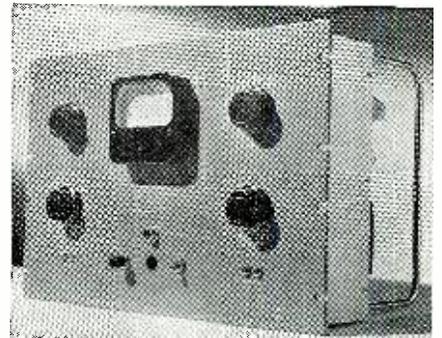Compared with previous models, the new type features improved control circuits, extended frequency range, a con-



tinuous suppression control, and more flexible remote control facilities.

Complete specifications on the Type 910-C are available from Dept. RN, *Herman Hosmer Scott, Inc.*, 385 Putnam Avenue, Cambridge, Massachusetts.

"VIDEAMP"

Crystal Devices Co. has announced the "Videamp", a new 13-channel, two-stage preamplifier for television receivers. The unit is self-powered and provides a gain of 10 or better on all 13 channels, according to the company.

With this new unit sets can be operated in the primary service area with

RADIO NEWS



Esse Specials!

Do not fail to closely examine this list of bargains. We believe that every item listed below is a sensational value. All equipment advertised herein is unconditionally guaranteed to the customer's satisfaction to this extent: Return any item advertised within five days after delivery for full refund except transportation charges (both ways).

Filter condenser, G.E. Pyranol, oil filled 8 MFD @ 1000 volts DC working voltage about 1 1/2"x4"x5" high, shipping weight about 3 lbs. Brown porcelain stand off insulator terminals. New \$2.00.

Filter condenser, Sprague, oil filled, 8 MFD @ 1000 volts DC working voltage size about 1"x4"x5" high, shipping weight about 2 lbs. New \$2.00.

Filter condenser, 8 MFD @ 700 volts DC working voltage, oil filled, well insulated terminals. Size about 2"x4 1/2"x5" high, with mounting flanges, kray metal case shipping weight about 4 lbs. New \$1.25.

Filter condenser Cornell Dubilier, 1 MFD @ 4000 volts DC working voltage, oil filled. Size about 2 1/4"x4"x7" high over all. Shipping weight about 4 lbs. Heavy stand-off insulator type terminals. New \$3.75.

Transformer, 110 volts 60 cycle input; output being two secondaries—each giving 14 volts @ 11 amperes, which can be used alone, in parallel, or in series for various voltage and current combinations. Size about 3 1/2"x3 1/2"x4" high. Ideal for operation of propeller pitch motors used for beam antenna rotation. Shipping weight 7 lbs. Manufactured for "Esse Radio Company" brand new \$5.95.

Transformer, for use on 110 volt 60 cycle primary line; secondary giving 28 volts, center tapped, @ 11 amperes, auto-transformer type of winding, size 3 1/2"x3 1/2"x4" high, shipping weight 7 lbs. made for "Esse" new \$4.95.

Condenser, electrolytic, 100 MFD. @ 300 volts. 2 1/2" diameter, 4 1/2" high, metal can, shipping weight 2 lbs., brand new \$2.00

Filter condenser, Tobe, oil filled, 1 MFD @ 600 volts DC working voltage, size about 1"x1"x2 1/2" high, new 20c.

Condenser, bath tub type .1 MFD @ 1000 volts DC, new 20c.

Condenser, Tobe, oil filled, 3 x .1 MFD @ 600 volts DC at 25c.

Filter condenser, Aerovox, oil filled, 2 MFD @ 900 DC working volts size about 1 1/2"x1 1/2"x5" high, shipping weight about 1 lb., new 35c.

Condenser, Cornell-Dubilier, oil filled, 4 MFD @ 1000 volts DC working voltage, size about 1"x2 1/2"x5" high, shipping weight 2 lbs., new \$1.75.

Condenser, mica, .25 MFD @ 250 volts, new 15c.

Jack Box BC-631-B, size about 2"x2"x4", aluminum case, contains 10,000 ohm volume control knob, Jones Barrier strip, brand new 40c.

Switch, push-button type DPST on/off type, to fit standard switch box, 10 amperes @ 250 volts, new 25c.

Micro-switch completely standard, metal grate well cast rated 15 amperes @ 115 volts normally open type, plunger has override feature. New 35c.

Vibrator, Radiart VS-3, for 6 volt battery operation, used in vibrator supply PE104—which is used with BC654A transmitter-receiver. Type J-4, new \$1.95.

Vibrator, Radiart VS-3 for 6 volt battery operation, used in vibrator supply PE104—which is used with BC654A transmitter-receiver. Type J6 (probably exactly the same as (A), new \$1.95.

Relay, 110 volt 60 cycle AC plunger type for interlock, new 85c.

Lord Shock Mount, heavy duty type, base size 3" square x 1 1/2" high—3/8" diameter bolt may be used. New 35c.

HAND SET T-S-10-G—Sound powered telephone. No batteries required for operation; connect to any two wire fence, wire fence in ground, etc., by convenient clips included. \$9.50
 Price each \$17.50
 Per Set


RADIO MODULATOR

BC-424, made by Westinghouse, 110 volt, 60 cycle AC operated. Size 9" x 14" x 9" high, weight about 30 lbs. packed. Has National Velvet Vernier Dial, Thordarson power transformer and chokes, tubes used and included are: 6F6, 6J7, 6J7, 5W4 and 955. Frequency about 190 megacycles. Comes with heavy steel case..... **\$22.50**

RELAYS

ALL BRAND NEW

RBM DPDT 110v 60 cycle, make before break.....	.75
Relay, 6 MA 5000 ohm DC resistance, SPDT.....	.85
Leach type 1127-FR 110v 60 cycle DPST.....	1.50
Automatic Electric Co. DPDT 24v DC 6 amp silver tungsten contacts40
Automatic Electric Co. Delay relay, 20 ohm, silver tungsten contacts.....	.40
Starter relay, 28 volt operated, heavy duty construction50
Switch, pushbutton type DPST on/off type, to fit standard switchbox, 10 amps at 250 volts....	.25
Switch, toggle type, bat handle, DPDT heavy duty contacts35
Leaf type switch, 4 poles, single throw, single hole mounting25

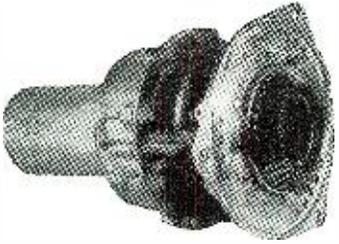

BEAM ROTATING MOTOR
 as shown
\$12⁹⁵

METERS

BRAND NEW AND ALL CHECKED FOR ACCURACY

0-500 MA DC 3 1/2" round NX35 Westinghouse.....	\$3.00
0-5 Amps RF 3 1/2" round NT35 Westinghouse, Internal TC	4.50
0-3 Amps RF 2 1/2" round NT33 Westinghouse, less TC	3.50
0-10 & 0-250 MA DC combination round NX33 Westinghouse	2.50
0-10 & 0-250 MA DC combination round DW41 G.E.	2.50
0-2 volts full scale 2000 ohms/volt Volume Level meter, Westinghouse, round 2 1/2".....	3.00
0-100 MA DC 2 1/2" round MD20601 McClintock.....	2.50
0-3 MA DC 3 1/2" square 327A Tripplett.....	4.50
0-500 Volts AC 3 1/2" square 337A Tripplett.....	6.00
C-2 Volts AC rectifier type 10,000 ohms/volt 327A Tripplett 3 1/2" square	15.00
0-50 MA AC 337A Tripplett 3 1/2" square.....	7.50
0-30 amps AC 3 1/2" round case, 331JP Tripplett....	6.00

Dual volume control wire wound, each section 2500 ohms, new 35c.

Toggle switch, bat handle, DPDT, new 30c.

I. F. Transformer, 19.2 megacycles, slug-tuned, New 15c ea.

Microphone transformer, Ouncer type, for carbon mike to tube grid, circuit printed on case. New 50c.

Transformer, two sets of windings each 1 to 1 ratio, good for frequencies of 1000 CPS and higher. New 25c.

Filter Choke, 19 henry 105 MA DC, resistance 170 ohms, metal cased, size about 3"x3"x4" high. New \$1.50.

Neon tube clear glass about 1/2" O.D. overall length about 11" excellent for transmitter RF tuning indicator. New 40c.

Microswitch, completely weather-proofed, metal-clad or cased, rated 15 amps at 115 volts, normally open type, plunger has override feature. New 35c.

Battery type BA-3S, 103.5 volts, used in Handie-Talkie, Mine detectors, or for any purpose where low current drain is required. Size 1"x1"x1 1/2" long. Out-dated, but tests O.K. New \$3.00.

Tube socket, RCA, for 866 or similar type tube bases. New 35c.

Tube socket, wafer octal type, excellent mica insulation, new 10c.

Tube socket for 813 type tube, Johnson type 237. New 60c.

Tube socket, for Acorn type tubes, made by Millen Co. New 20c.

Tube socket, porcelain octal type, less mounting ring. New 10c.

Cord CD-132, has PL-55 type plug and 9" cord, with spade type lug tips 35c.

Sylvania type 1N26 crystal 35c.

Resistor 20 watt, one-half ohm, 10c.

Fuse holder for type 3AG fuses, 10c.

Amphenol co-axial chassis connector, new, type 83-1R, 40c.

Amphenol co-axial junction connector, new, type 83-1AP, 40c.

Connector, bakelite insulation, male and female section, 6 pin polarized, 00c.

Canvas bag, moisture & fungus proofed, with carrying strap, leather re-enforced corners, weight 3 lbs., size 9"x14"x12" high. Ideal for tool case, for sportsmen, etc., \$1.00.

First IF transformer for BC348 type receiver, 915 kilocycles. New \$1.00.

Ohmite tap switch, model 111, 9 taps, non-shorting, will handle 10 amps at 115 volts. New 35c.

Kit of potentiometers, twenty-five assorted sizes carbon and wire-wound, New \$2.25.

Resistor, voltmeter multiplier type, rated at 2 megohms 2 kilovolts insulation, 1 MA maximum current, about 1" diameter x 5 1/2" long, mounts in clips. New 75c.

Resistor, 100 watt type, 5 sections having 7500, 3000, 23, 23 and 750 ohms (total of 11,269 ohms) resistance. 1 1/2" diameter by 8 1/2" long. New 35c.

Radio Co

Unless Otherwise Stated, All of This Equipment Is Sold As Used

CASH REQUIRED

WITH ALL ORDERS

Orders Shipped F.O.B. Collect

140 W. NEW YORK ST. INDIANAPOLIS 4, IND.




DOWN — DOWN —
GOES THE COST OF

TELEVISION

GENUINE — BRAND NEW

R.C.A. TELEVISION KIT

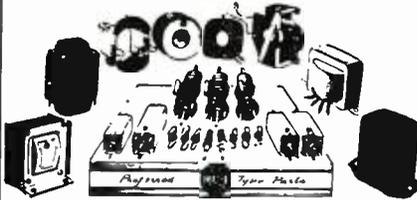

Now, for the first time you are offered a basic kit consisting of the finest essential components enabling you to build anything from a 7" to a 20" Television Receiver. These parts are the best the industry has to offer—All genuine R.C.A. Also included is a schematic diagram and a complete parts list of the minor components necessary to make up a complete TV receiver. Described and pictured below are the various components included in this sensational kit.

KIT CONSISTS OF:

- Deflection Yoke Type 201D1
- Width Control Type 201R1
- Horizontal Linearity Control Type 201R3
- Power Transformer Type 201T6
- Yoke Mounting Hood Type 201X1
- Focus Coil Type 202D1
- Vertical Output Transformer Type 204T2
- Filament Choke Type 204L1
- Television I.F. and Video Coil Kit Type 204X2
- Vert. Blocking-Oscillator Transformer Type 208T2
- Horiz. Blocking-Oscillator Transformer Type 208T3
- Horiz. Output Transformer Type 211T1

\$6950

The parts in this kit, if purchased separately, would list at over \$150.00. Niagara saves you over 50%, or a big \$61.20. GET YOURS TODAY.

RADIO MAN'S SPECIAL 5" or 7" TELEVISION FOUNDATION KIT

Here is one of the biggest bargains ever offered in Television Foundation Kits.

This TELEVISION FOUNDATION KIT consists of the most essential (and expensive) parts needed in constructing a television receiver. Starting with the hi. volt. power supply, for the scope, right through to the antenna. This kit contains: high voltage scope transformer (for 5" or 7" tube), 2x2 filament transformer, lo. volt. transformer for receiver, cathode ray filament transformer, filter choke, 6.3 filament transformer for 16 six volt tubes along with five volt transformer for the 5U4, the two hi. volt filter condensers, blocking osc., transformer for all RF's sound and video IF's, peaking coils and discriminator transformer. The rectifier tubes 2x2 and 5U4, the picture tube 5BP4, and an all aluminum dipole antenna are also included.

A 26 page instruction book, including a large 12 by 18 schematic diagram, theory of television, circuit functions, explanation of scanning, preliminary volt. measurements, parts lay-out and final adjustment of the television receiver which facilitates easy alignment without the use of elaborate test equipment comes with each unit.

If you are a radio man you will probably have all of the minor parts not included in this foundation kit. By following the simple schematic diagram and instructions you can thus build a television receiver at many dollars savings.

The above kit with parts as mentioned.....\$34.75
The above kit with 7EP4 for an additional..... 12.95
Remaining set of necessary tubes..... 14.95
Completely punched chassis for above kit..... 5.50

BRAND NEW 7EP4'S
INDIVIDUALLY BOXED—STANDARD
BRAND—A STEAL AT..... **\$17.95**

Write today for our new television folder on special kits, components, tubes, and other TV. supplies. Be sure you are on our special television mailing list.

Please put my name on your television mailing list for special TV. bulletins.

NAME

ADDRESSZONE

CITYSTATE.....

NIAGARA RADIO SUPPLY CORP.

160 Greenwich St. New York 6, N. Y.

simple indoor antenna equipment. For receivers located in excess of 100 miles from the transmitter, this accessory is said to provide adequate video reception.

The equipment is shipped from the factory to match 300 ohm input and outputs but provision is made for any other input or set impedance values by adding resistive components at installation terminals.


Additional information on the "Vide-amp" may be secured from Dept. RN, Crystal Devices Co., 1819 Broadway, New York 23, New York.

"HI-TEMP" TUBULARS

Two new types of all-purpose capacitors are now being mass-produced by Solar Manufacturing Corporation at the company's North Bergen, New Jersey plant.

Known as the ST and STM, the new units are plastic-encased and of molded paper construction. The "Hi-Temp" plastic molding compound which encases these units is heat-resistant to 100 degrees C and is exceptionally resistant to penetration by atmospheric moisture, requiring no wax or varnish outer impregnation for surface sealing.

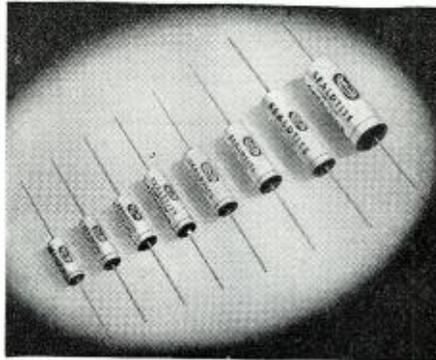These "Sealdtite" units are available with either mineral oil or Halowax impregnated sections to fit application re-



quirements for all types of personal, home, and automobile radios.

A descriptive bulletin is available from Solar Manufacturing Corporation, 1445 Hudson Boulevard, North Bergen, New Jersey.

D.C. CONVERTER

Special converters which have been designed to permit persons in direct current metropolitan areas to have television receivers in their homes or offices have been announced by Electronic Laboratories, Inc. of Indianapolis.

Two models of converters are available, the Model No. 11OR15 for operating table model television receivers, and the Model No. 11OR30 for operating console units.

No special wiring is required for the converters which operate with a new-type automatic remote starting system. The unit for table models weighs 15 pounds while the converter for the con-

sole weighs 55 pounds. Either converter may also be used for wire recorders, juke boxes, radio-phonograph combinations, and office dictating machines.

Further data on these two converters may be obtained from Electronic Laboratories, Inc., Indianapolis, Indiana.

—30—

Pilotuner

(Continued from page 59)

capacities mentioned. With the values shown in the diagram and keeping the wiring capacities at a minimum by following the arrangement as shown in the illustrations, it will be found that the high frequency response will be down 3 db., to the half-power point, at about 13.26 mc. and will still be flat at 85% of this, or 11.27 mc.


The low frequency response will depend partly on the reactance of the cathode and screen bypass condensers giving, in effect, degeneration and less gain in the stage as the reactance increases. At 10 mc. the values used will have a reactance of approximately 16 ohms and at 1 mc. this will be about 160 ohms. The low frequency response is also dependent on the coupling condenser and the grid resistor of the following stage. Roughly, the low frequency response will not fall off to an appreciable degree for sine waves if the time constant, or RC product, of this combination is equal to the period of the lowest frequency desired. This can also be thought of as a voltage divider, with the reactance of the condenser increasing as the frequency decreases.

The gain of the stage will be essentially GmR_1 at 10.7 mc. The GmR_1 of the 6AK5 tube used with the voltages available in the Pilotuner measured about 5000 micromhos. This will give a gain for the stage of approximately 12 which is entirely sufficient to give satisfactory output, even in such a poor location as mine.

In wiring the circuit most of the parts are wired directly to the tube socket and then set in place as an assembly. The socket used is an Eby or Amphenol 7-pin miniature ceramic socket with a shield base extending about 11/16 of an inch. The shield itself is not used. Use pin 3 as ground and run the 150 ohm cathode resistor from pin 2 to pin 3 and the .001 mfd. cathode condenser from pin 7 to pin 3. The .01 mfd. screen bypass condenser will go from pin 6 to pin 3 and a piece of No. 18 bus wire will also be soldered to pin 3 for the ground connection and to help hold the assembly in place.

The 12,000 ohm resistor and the 50 microhenry choke are paralleled and soldered to pin 5. At the opposite end of this, a junction is made with the .0015 mfd. coupling condenser and the 2400

FAMOUS for Finer Performance

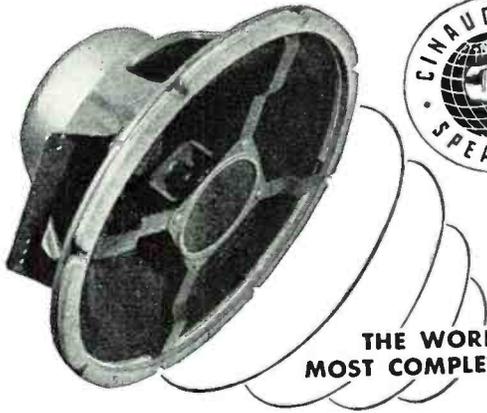

THE WORLD'S MOST COMPLETE LINE

When quality of tone counts, insist on the finest speaker you can buy . . . because tone fidelity is only as good as your speaker makes it.

Don't handicap your F.M. and television receivers by using an ordinary speaker — rather, take full advantage of the tone potentialities of F.M. and television sound-channels by using a speaker especially designed for the purpose . . . Pictured above, Model CIN 12A, list price \$27.50 for immediate delivery.

When speaking of speakers, specify **CINAUDAGRAPH**.

Write today for the new **CINAUDAGRAPH** catalog Dept. 2424

"See Cinaudagraph Display in Booth 27"

Cinaudagraph Speakers

DIVISION OF AIREON MFG. CORP.

SALES OFFICE and FACTORY 1401 FAIRFAX TRAFFICWAY KANSAS CITY, KANSAS

Fixing Radios the Old Hard Way?



The Feiler Stethoscope does everything but make the actual repair. And the Stethoscope does it faster, better and much easier. Thousands of radio men, many with little experience, are already fixing radios and other electronic equipment this new way.

You will find that just this one low priced unit and a few basic hand tools are all you need to fix practically any radio.



The "Inside Story" of the **STETHOSCOPE**—how it works—how it instantly locates trouble in any circuit—is yours for the asking. The "Inside Story," a 24 page illustrated booklet, is full of practical tips and hints on radio servicing. To get your free copy, send your name and address on a penny post card today.

"MAKES RADIO REPAIRS AUTOMATIC"

Available for Export—Choice Territories Still Open



FEILER ENGINEERING COMPANY

945 George St. Dept. 5H8 Chicago 14, Illinois

May, 1948

Why
DO

AMPHENOL

**FM ANTENNAS
GIVE YOU
BETTER
RECEPTION**



BECAUSE:

- 1 Amphenol antennas are precisely cut—to the exact center of the FM band to give you the most antenna efficiency, precision to the fraction of an inch. You will find that Amphenol antennas are longer than other makes—no skimping to cut costs at the expense of performance.
- 2 Engineered to give smooth, even, crystal-clear FM reception all across the band, at every point (not just the center).
- 3 20% more transmission line of genuine Amphenol Twin-Lead—finest of its kind and specified by other antenna engineers.
- 4 Rigid low-loss, stand-off insulators at precise intervals absolutely prevent any loss of signal between antenna element and your receiver.
- 5 Not just another antenna: specifically engineered for finest FM performance—to produce the best reception and optimum gain.
- 6 Made to withstand severest wind, sleet and snow.

BEHIND THE NAME AMPHENOL:
Years of research and precision engineering, resulting in products of proven quality.




GET AN AMPHENOL FM ANTENNA . . . folded dipole, folded dipole and reflector, or all-direction double folded dipole . . . and get the best out of your receiver. See your dealer—today!

AMERICAN PHENOLIC CORPORATION

1830 South 54th Street, Chicago 50, Illinois
COAXIAL CABLE AND CONNECTORS • INDUSTRIAL CONNECTORS, FITTINGS AND CONDUIT • ANTENNAS • RADIO COMPONENTS • PLASTICS FOR ELECTRONICS

151

QUAM *Adjust-a-Cone* SPEAKERS

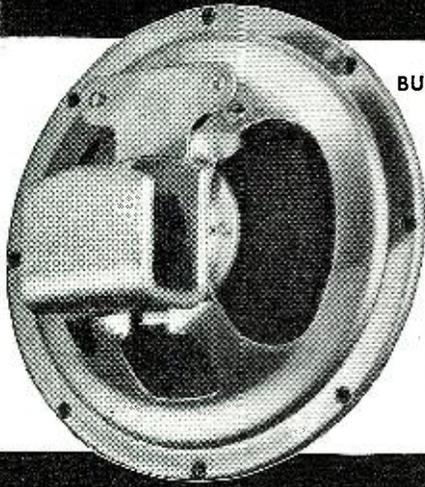

BUILDERS OF FINE SPEAKERS SINCE 1923

LOOK FOR THE
U-SHAPED
COIL POT

Electro Dynamic and P. M. Speakers in the following sizes: 3 1/2", 4", 4"x6", 5", 5 1/4", 6 1/2", 6"x9", 7", 8", 10" and 12".

Write for Catalog...

QUAM-NICHOLS COMPANY, 522 East 33rd Place, Chicago 16, Ill.

INSIDE INFO!

Get your copy today

ELEMENTS OF
MAGNETIC TAPE
RECORDING
and 999
APPLICATIONS



Available
For Only
25c

by **A. C. SHANEY**

Contains schematic diagrams

AMPLIFIER CORP. of AMERICA

398-2 Broadway • New York 13, N. Y.

EASY TO LEARN CODE

It is easy to learn or increase speed with an Instructograph Code Teacher. Affords the quickest and most practical method yet developed. For beginners or advanced students. Available tapes from beginner's alphabet to typical messages on all subjects. Speed range 5 to 40 WPM. Always ready—no QRM.

ENDORSED BY THOUSANDS!

The Instructograph Code Teacher literally takes the place of an operator-instructor and enables anyone to learn and master code without further assistance. Thousands of successful operators have "acquired the code" with the Instructograph System. Write today for convenient rental and purchase plans.



INSTRUCTOGRAPH COMPANY

4711 SHERIDAN ROAD, CHICAGO 40, ILLINOIS

ohm load resistor. The 25 microhenry choke follows this and joins the 1000 ohm decoupling resistor and a lead from pin 6 for the screen voltage. With an insulated wire soldered to pin 4 for the filament supply and another to the free end of the 1000 ohm resistor, unless the resistor lead itself is long enough, for the "B plus" connection, the assembly is ready to place in the chassis.

From the i.f. transformer feeding the last 6BA6 tube in the *Pilotuner* remove the .0015 mfd. condenser and the 100,000 ohm resistor. The other end of the condenser should be removed from the ground stud as well and may be used as the coupling condenser for the added stage. Ground the terminal just vacated on the i.f. transformer to the stud above. Remove the wire between the i.f. transformer and the 6BA6 grid, pin 1, at the grid end only and solder the end of the 100,000 ohm resistor which was detached from the i.f. transformer to the 6BA6 No. 1 pin.

Now take the end of the wire from the i.f. transformer which formerly went to pin 1 of the 6BA6 and solder this to pin 1 of the 6AK5 assembly. Set the tube in the chassis as shown in the photograph and solder the wire from pin 4 of the assembly to pin 4 of the 6BA6, keeping this wire close to the chassis and away from other parts of the circuit. The wire from pin 3 of the assembly can be conveniently soldered to one of the ears of the filter condenser can.

Next the coupling condenser which was removed from the *Pilotuner* is soldered to pin 1 of the 6BA6 and the junction previously mentioned on the 6AK5 assembly. Now solder the "B plus" wire from the 1000 ohm resistor to the "B plus" point on the ratio detector transformer and arrange the added tube in the empty chassis space between the oscillator coil and the filter condenser, keeping it as far away from the coil as possible.

The changes described enabled me to use one less stage in my audio amplifier to which the tuner is connected and provided tuning ease comparable to narrow-band AM. The warm-up time of the *Pilotuner* was slightly greater but the minor drifting was no longer objectionable, suggesting that it may have been due in part to inaccurate tuning. The FM station that was mentioned as being behind some hills could now be received and the tonal balance of the whole combination seemed richer than before.

The striped wire shown in the illustrations in the corner of the chassis behind the ratio detector connections is not in the original *Pilotuner*. It goes from the switch to the audio output, and was added for the following reason.

In wiring the *Pilotuner* to my audio amplifier I originally ran the audio out-

RADIO NEWS



RADIO INSTITUTE

Outstanding PRE-WAR Technical

Training Center for

TELEVISION & RADIO

Under the personal direction of Frank Melville, former Airlines, Merchant Marine, and Broadcast technician, you may soon qualify as:

- RADIO TECHNICIAN
- AIRLINES RADIO OFFICER
- PT. TO PT. TELEGRAPHER
- RADIO AMATEUR
- MERCHANT-MARINE RADIO OFFICER
- TELEVISION TECHNICIAN
- HOME RECEIVER REPAIRMAN
- VISUAL TELEGRAPH OPR. (SLIP TAPE)

MELVILLE RADIO INSTITUTE believes vocational training means vocational training. Thus we, like many radio schools, teach ample theory. But, unlike most schools, two-thirds of our technical students' time is spent in laboratories and shops, where, with superior equipment, they learn by doing — not memorizing.

FREE employment service is available to all MELVILLE graduates.

Visit the 10-story MELVILLE Building today as our guest and observe the school in operation.

Day and evening classes approved for veterans. Licensed by the State of New York.

MELVILLE RADIO INSTITUTE
Melville Building
15 West 46th St., N. Y. 19 • LOngacre 4-0340


MAIL THIS COUPON NOW!

MELVILLE RADIO INSTITUTE R N
Melville Building
15 West 46th St., New York 19, N. Y.

Gentlemen Send me Free information about your school.

Name _____


Address _____

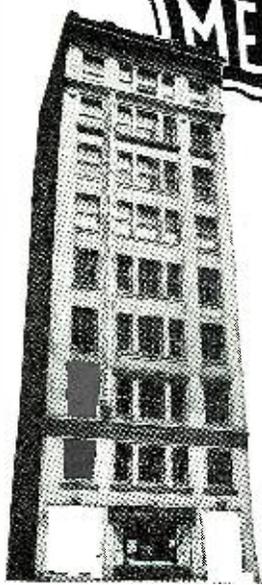

MONEY BACK GUARANTEE We believe units offered for sale by mail order should be sold only on a "Money-Back-If-Not-Satisfied" basis. We carefully check the design calibration and value of all items advertised by us and unhesitatingly offer all merchandise subject to a return for credit or refund. You, the customer, are the sole judge as to value of the item or items you have purchased.

The Model 88-A COMBINATION

SIGNAL GENERATOR AND SIGNAL TRACER

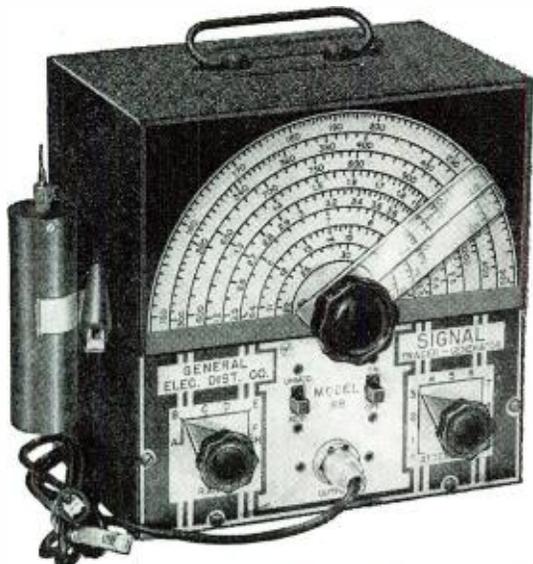

The Model 88 comes complete with all test leads and operating instructions. Only.....

\$28⁸⁵
NET

The ultimate in signal tracing procedure is achieved by the Model 88, for the use of this model, enables you to use either the broadcast signal itself or the signal injected by the Signal Generator. This is especially useful of course when servicing "dead" or "intermittent" receivers. The Model 88 you will find is the greatest time-saver ever provided for by combining a full range Signal Generator and Signal Tracer into one unit; the set up time for interconnecting, etc., is entirely eliminated.

Signal Generator Specifications:

- Frequency Range: 150 Kilocycles to 50 Megacycles.
- The R.F. Signal Frequency is kept completely constant at all output levels. This is accomplished by use of a special grid loaded circuit which provides a constant load on the oscillatory circuit. A grounded plate oscillator is used for additional frequency stability.
- Modulation is accomplished by Grid-blocking action which has proven to be equally effective for alignment of amplitude and frequency modulation as well as for television receivers.
- Positive action attenuator provides effective output control at all times.
- R.F. is obtainable separately or modulated by the Audio Frequency.

Signal Tracer Specifications:

- Uses the new Sylvania IN34 Germanium crystal Diode which combined with a resistance-capacity network provides a frequency range of 300 cycles to 50 Megacycles.
- Simple to operate—Clips directly on to receiver chassis, no tuning controls.
- Provision is made for insertion of phones of any impedance, a standard Volt-Ohm Milliammeter or Oscilloscope.

THE MODEL S-35

REFLEX PROJECTOR



COMPLETE WITH BUILT-IN DRIVER UNIT CONSERVATIVELY RATED AT 35 WATTS — WILL HANDLE UP TO 55 WATTS WITHOUT BLASTING

For the sound technician who demands the best in reflex speakers. Heavy gauge non-corrosive aluminum in the main trumpet section completely eliminates blasting and blaring. The Driver is conservatively rated at 35 watts and can safely handle 55 watts without blasting. It incorporates a number of new improvements. The standard metal diaphragm heretofore used has been replaced with a new plastic diaphragm. This overcomes the resonant peaks of the old type; also, because the new plastic diaphragm is absolutely impervious to atmospheric changes whereas the old type was subject to atmospheric corrosion we are enabled to guarantee the unit for one year. Model S-35 provides a maximum of coverage with a minimum of power thus reducing installation costs.

Specifications:

POWER (CONSERVATIVE)—35 WATTS; AIR COLUMN—3½ FT.; DISPERSION—80°; POWER (PEAK)—55 WATTS; BELL DIAMETER—15"; IMPEDANCE—8 ohms; FREQUENCY RANGE—130 TO 5000 C.P.S. PROJECTION—½ mile; FINISH—Attractive two-tone crystalline.

The Model S-35 Comes Complete with Built-in Driver Unit, ONLY **\$28⁵⁰**

20% DEPOSIT REQUIRED ON ALL C.O.D. ORDERS

GENERAL ELECTRONIC DISTRIBUTING CO. Dept. RN-5, 98 Park Place
New York 7, N. Y.

Look!

Send for FREE BULLETIN

Sent you every month. It's crammed full of real buys. A post card with your name and address brings it to you. You can't afford to miss its bargains. Mail your card today.



QUALITY ITEMS AT LOWER PRICES

OZA's at 73% OFF!
 Until sold out—RSE offers 15000 new guaranteed OZA tubes. You know who made them—You can't go wrong at **59c**

GENERATOR CONDENSERS
 Made by nationally prominent eastern manufacturer. Standard merchandise—.5 mfd— $\frac{1}{8}$ " x 1- $\frac{1}{8}$ "— $\frac{3}{8}$ "— $\frac{1}{2}$ " lead - slotted mounting strap. Present list \$1.00. Discount 87%. While **13c**
 8000 last they're yours

UNIVERSAL PHONO CRYSTALS
 One model will replace all the following types: L22, L25, L26, L27, L32, L40, L70, L75, L76, W41A, W42A, W57A. Size: $\frac{3}{8}$ " x $\frac{3}{4}$ " x $2\frac{1}{8}$ ". List price \$4.45. **THEY COST YOU \$1.39**
 10 for \$12.90

.5 mfd—300 VOLT CONDENSERS
 Made by one of the big four. $\frac{3}{4}$ " x $2\frac{1}{2}$ ", with tinned leads. New fresh stock—all guaranteed. Only 10,000 available at **6c each**
 10 for 49c
 100 for \$3.95

ORDER INSTRUCTIONS
 Minimum order—\$2.00. 25% deposit with order required for all C.O.D. shipments. Be sure to include sufficient postage—excess will be refunded. Orders received without postage will be shipped express collect. All prices F.O.B. Detroit.

DEMAND THIS SEAL OF QUALITY

RADIO SUPPLY & ENGINEERING CO., Inc.
 129 SELDON AVE. DETROIT 1, MICH.

put direct to a grid which was left connected when the amplifier was used as a phonograph. This connection was not made as *Pilot* shows in their book as I am using a coil type pick-up and not a crystal. With the audio amplifier connected for phono and the audio output from the *Pilotuner* unchanged, the *Pilotuner* output condenser was close enough to the transformer and the 60 cycle wiring to pick up a noticeable hum.

This hum disappeared when using the *Pilotuner* due to their method of balancing out the supply voltage pickup. However, I changed the condenser connection to the switch and made the audio output wire shielded from the switch so the hum could not be picked up when the *Pilotuner* was turned off and the amplifier was used for phono.

Since then I have changed the input and switching in my amplifier so this hum pickup would no longer be a problem even with the original *Pilotuner* wiring.

Phono Amplifier (Continued from page 45)

secured by screws to the bakelite, were used to mount the amplifier, and the use of the screws as tiepoints in the circuit wiring was carefully avoided.

The record player to which this amplifier was applied is an *RCA* model PRP-1 which was in popular use before the war. A two-inch speaker was mounted in the cabinet in the open location immediately in front of the bushing that mounts the pickup arm.

E. J. Biesekerski was one of two Eastern Air Lines' employees to be awarded membership in the DX Century Club. A foreman in the carburetor shop at the Eastern Air Lines Base in Miami, he has received confirmation cards from 110 countries since becoming a ham in 1930. He has talked with amateurs in 139 foreign countries but 29 failed to send confirmation cards. His call is W4KA. R. J. Miller, the assistant chief of the operating section of the company's Communication Dept., has contacted 129 countries and received confirmation from 107.



SURPLUS

TRANSMITTERS

- B.C. 457-4—5.3 mc.....\$5.95
- B.C. 458-5.3—7 mc.....\$5.95
- B.C. 459-7—9.1 mc (new).....\$9.95

- | | |
|--------------------------|----------------|
| ARC/5-7-9.1 mc 40 m..... | \$6.95 |
| ARC/5-4-5.3 mc 80 m..... | \$5.95 |
| Special both for..... | \$10.95 |

RECEIVERS

- B.C. 454-3—6 mc (new).....\$6.95

MODULATOR UNITS

- B.C. 456.....\$3.95

OIL FITTED CONDENSERS

- 2 mfd-4000V.....\$4.95
- 3 mfd-4000V.....\$5.95
- 2 mfd-5000V.....\$6.95

- Beacon receiver tunes to 75 meg., has current relay. Operates on 2 mils.....\$1.79

- 10 meter conversion diagram furnished for B.C. 454 Rec.

- Also thousands of additional special items. Inquiries invited. Cash with order—express C.O.D.

Prices subject to change without notice.

ESEGE SALES CO. LTD.

Distributors of
Surplus Radio and Electronic Parts

1306 Bond St. Los Angeles 15, Calif.

Sick of BACK ORDERS

????????????

MARCO GIVES IMMEDIATE DELIVERY

TUBES

5R4GY.....	\$0.90	725A.....	\$9.95
6AK5.....	.59	804.....	6.50
6CA.....	.35	807.....	1.25
6Y6.....	.80	829B.....	2.95
VR105/30.....	.75	9003.....	.50

OIL FILLED CONDENSERS

4 Mfd. 400 V.....	\$ 0.45
4 Mfd. 600 V.....	.60
10 Mfd. 600 V.....	.90
10 Mfd. 1000 V.....	1.95
15 Mfd. 1000 V.....	2.25
8 Mfd. 2000 V.....	3.95
2 Mfd. 4000 V.....	5.75
4 Mfd. 4000 V.....	10.95

MISCELLANEOUS

Choke 9-38 H. @ .075/.75A.....	\$14.95
Relay D.P.D.T. 115 V. AC.....	1.25
Volt-Ohm-Ma. Meter (Portable w/ Test Leads) (Orig. Pack).....	12.50

A/N CONNECTORS

Large Selection In Stock At All Times.
Catalog For Industrials.

Write your needs. We can supply them from our own large stock of thousands of electronic specialties, too numerous to list... AMAZING VALUES... Prices will rise!... BUY NOW AND SAVE AT

BALTIMORE'S BARGAIN CENTER

Minimum Mail Order \$2.00
25% Deposit With Order Balance COD

MARCO ELECTRONICS, INC.

513A W. Franklin St.

Baltimore 1, Md.

Lex. 0198

RADIO NEWS

Television Scope

(Continued from page 55)

insulated mounting wafers are provided with each condenser. These condensers should be covered by a suitable cardboard tubing or by tape in order to protect the user from a substantial "jolt" which would result from touching the metal cans and the chassis at the same time.

Next to the various power supply components and directly behind the cathode-ray tube will be noted, in the photograph in Fig. 1, a bakelite terminal strip. On this terminal strip are mounted the two centering controls, R_{25} and R_{24} , plus several other components associated with the cathode-ray tube itself, principally R_{20} , R_{30} , R_{26} , R_{28} , R_{27} , R_{23} , C_{24} , and C_{26} . By arranging these parts in this fashion the components associated with the cathode-ray tube are convenient for wiring to its socket, the centering controls which carry high voltage are insulated from the panel and chassis, and much wiring from top to bottom of the chassis is saved. It is suggested that this terminal board be laid out and wired before being mounted in place.

Actual wiring of the oscilloscope should start with the power supply, following the wiring and mounting of the above-mentioned terminal board. When this is completed, the three rectifier tubes V_{10} , V_{11} , and V_{12} , should be put in place, the power supply turned on and the output voltages measured. If operating correctly the voltage at the junction of C_{47} and CH_1 should be about 800 volts plus with respect to the chassis, and the voltage at the plates of V_{12} should be about 425 volts minus.

When it has been determined that the power supply is operating correctly, the "Focus" control, R_{32} , and the "Intensity" control, R_{34} , should be wired into the circuit together with the terminal board previously described and the socket of the cathode-ray tube itself. A good grade of high voltage hookup wire should be used for the high voltage circuits associated with the power supply and cathode-ray tube to prevent any possibility of arc-over. One of the smaller types of automobile ignition wire is preferred by the author.

Probably the most important test to be made during the entire construction of this oscilloscope occurs at this point. This consists of testing the actual operation of the cathode-ray tube in conjunction with its power supply. The object of the test is to secure a very small round spot of light on the cathode-ray tube screen which can be properly focused and brightened with the appropriate controls, and also moved nearly the full distance across the screen both

Proved in Millions of Applications!



RELAYS RESISTORS RHEOSTATS

Vast Variety of Stock Units

ANSWERS EVERYDAY NEEDS ECONOMICALLY

Relays are available from stock in general-purpose, industrial, and radio amateur types for continuous or intermittent duty.







Vitrohm wire-wound Fixed Resistors are available in 8 stock sizes from 5 to 200 watts. Adjustohms in 7 stock sizes from 10 to 200 watts. Plaque Resistors in 3 sizes from 20 to 125 watts. Discohms in 18 watts. Stripohm in 5 stock sizes from 30 watts to 75 watts. Ring-type close control Rheostats in 4 stock sizes from 25 to 150 watts. (Plate Type Rheostats recommended for larger sizes.) Wide variety of Resistance Values.

**AUTHORIZED DISTRIBUTORS EVERYWHERE
WARD LEONARD ELECTRIC COMPANY**

Radio & Electronic Distributor Division
53-N West Jackson Blvd., Chicago 4, U. S. A.

SEND FOR HELPFUL CATALOGS

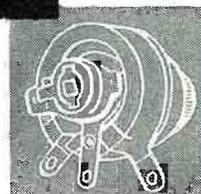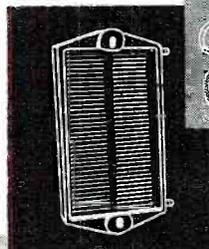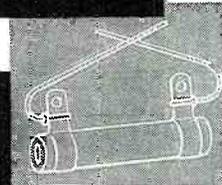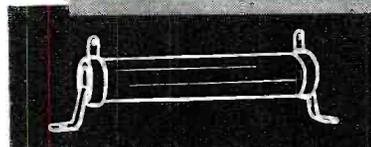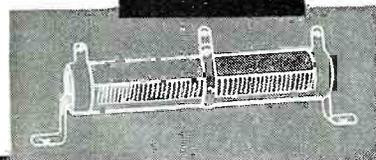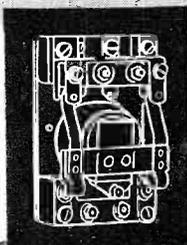Catalog D-30 gives complete data and listings on stock units available in Resistors, Rheostats and Radio Amateur Relays. Catalog D-20 lists Industrial and General-Purpose Relays. Write for them today!



WARD LEONARD

Basic 3R's in Current Control

BARGAINS UNLIMITED

Hundreds of money-saving values at today's lowest prices—for your every need.

FREE CATALOG of Refrigeration, Radio, and electrical Supplies. Send for yours at once!

G. & E. Equipment Supply Co.
Ogden at Fulton Chicago 7, Ill.

ATTENTION RADIO DEALERS AND SERVICEMEN!

• Are you fed up with those so-called war surplus bargains? Then call on us for standard radio parts at regular dealers discounts.

EL MONTE ELECTRONICS SUPPLY CO.
992 East Valley Blvd., El Monte, California
BUlong 8-4228

HARDIN COLLEGE SCHOOL OF RADIO ANNOUNCES!!

18 MONTH RADIO REPAIR COURSE

Train in the Southwest's most modern equipped Radio School.

Approved by the V.A. for Veterans. This school is located on the Hardin College Campus.

Dormitory facilities available.

For Further Information Write:
James F. Marshall, Director

**HARDIN COLLEGE SCHOOL
OF RADIO**

WICHITA FALLS, TEXAS

PEAK SUPER SPECIALS

SPECIALS OF THE MONTH

Western Electric Filter Choke 4.3 henry
620 mills 42 ohms DC resistance. 47x5%
-x5%. Ceramic Insulators \$4.95 ea.
NYT Choke—8 Hy 160 ma. 140 ohms
DC \$1.39
2" Meter Basic 0-1 ma (volt scale) Bakelite
Case. Ideal for use as "S" meter etc. \$2.75



**SPEERT RF
VACUUM SWITCH**
9200 volts peak 8 amps. Used
as antenna switch in Collins
RT 13. Brand new **\$1.75**

FEDERAL SELENIUM RECTIFIER
Full wave. 36 volts input. 28 volts output at 6.1
amps. Brand new **\$7.95**

DAVEN AUDIO FREQUENCY METER—Model 837E




Direct reading from 0-30 KC in 4 separate ranges
on 8" Weston Model 271 Fan Meter. Built-in
voltage regulated power supply operates from 115
volts 60 cycles, has high input impedance. With
pick-up can be used to determine frequency in
vibration tester. With suitable mixer can check
deviation of R.F. carrier from standard. Mounts
on 8 3/4"x19" rack panel. Complete with tubes.
Slightly used but perfect. Only **\$59.50**

A SWELL BC 348

"S" METER

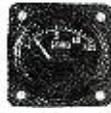This G.E. tiny but accurate meter
is only 1 1/2" sq. Basic 0-1 ma.
Swell for "S" or field
strength meter, etc. Only **\$3.95**



SCOPE TRANSFORMER

Hermetically Sealed. 1800 v. 4 ma, 6.3 v. @ .9
amps 2.5 v. @ 1.75 amps **\$5.95 ea.**

Genuine Vibroplex "Lightning Bug" model \$6.95
Copy of above by Lionel **\$4.95**

AMERTRAN TRANSTAT

and Variable
Stepdown Transformer

110/220 volts 60 cycle input.
Output variable plus or minus
10% of 115 volts at 8.5 amps.
Also can be connected to give
different voltage combinations.
Brand new **only \$12.95**



METERS (Standard Brand)

2" 0-5 ma. (amp scale)	\$1.95
2" 0-1.2 (0-100 scale)	2.49
2" 0-1 amp. R.F. (internal thermo)	3.49
2" 150-0-150 microamps. Model 506 (Sperry scale)	3.49
2" 0-50 microamps. (square)	7.50
2" 0-120 Ma RF	4.95
2" 0-1 Ma Basic (0-3 V scale)	2.95
3" 0-50 microamps	9.95
3" 0-2 ma D.C.	3.95
3" 0-20 ma D.C.	3.95
3" 0-15 ma D.C. (square)	3.95
3" 0-150 volts A.C.	7.95
3" Running Time Meter	3.95
4" 1-0-1 ma D.C. (Blank scale)	3.95

OIL CONDENSERS Nationally Known

2 mfd 600 vdc	\$.39	3 mfd 3000 vdc	\$3.95
4 mfd 600 vdc	.59	1 mfd 5000 vdc	4.50
3/3 mfd 600 vdc	.79	1 mfd 7500 vdc	1.95
14 mfd 600 vdc	1.35	1/2 mfd 7500 vdc	2.45
2 mfd 1000 vdc	.79	.01/.01 12 KV dc	5.75
4 mfd 1000 vdc	.95	.65 mfd 12500 vdc	12.95
2 mfd 1500 vdc	1.25	.75/.35 mfd (dual)	7.95
1 mfd 2000 vdc	1.11	8/16 KV dc	14.95

MISCELLANEOUS SPECIALS

BC 454B-3506 Mc Superhet. with 6 tubes **\$4.95**
2-11 mmf. Butterfly (Ball Bearings) **.59**
CD 16 mfd 450 v in can with leads **.59**
Heineman Circuit Breaker 6 amp. 110 v. AC **.95**
Telephone Handset (TS13) Hi-Imp. **2.95**
Hammarlund Variable 150 mmf. .07 spacing **1.95**
SC Test Set with Weston 150 v AC Meter **3.95**

If not rated, 25% with order, balance C.O.D.—
Minimum order \$3.00.

PEAK ELECTRONICS CO.

188 WASHINGTON ST., DEPT. MR
NEW YORK 7, N. Y.

horizontally and vertically by means of the centering controls. Emphasis is placed on the words *small round spot* since the principal source of trouble at this point may be magnetic interference from the power transformer. If such a disturbance is present, it will show up as an elongation of the cathode-ray tube spot, or even may appear as a small circle instead of the desired *small round spot*.

Two means of remedying these magnetic disturbances are available, namely, shielding the cathode-ray tube, magnetically, and shielding and/or altering the position of the power transformer. If the disturbance is small, causing the spot to be deflected only a small amount—say 1/8 inch or less—the difficulty can usually be remedied by placing a commercial cathode-ray tube shield or piece of iron pipe—the thicker the metal wall the better—around the neck of the tube. In general, this tubing should fit as close to the outside diameter of the tube's neck as possible. More stubborn cases may require more than one piece of tubing located coaxially around the neck of the tube. A combination that frequently does the trick is one piece of close fitting iron pipe around the tube's neck and a second much larger piece to shield the entire tube. Extremely troublesome cases may require that the power transformer be shielded and/or rotated or altered in its position, but this is unlikely if the transformer is mounted as previously described. The end result of the work at this point is the very small round fluorescent spot, and patience in eliminating the last small amount of magnetic interference will pay off in clean, sharp patterns and pictures later on. One further caution—the fluorescent screens of cathode-ray tubes "burn" quite easily if the spot is made too bright. Therefore, during the process of eliminating magnetic interference, caution should be used in keeping the intensity of the spot as dim as possible at all times. This same test should be repeated when the scope is completed, since the additional load of the various tubes may aggravate any magnetic trouble.

Once this point has been passed, the construction proceeds easily and rapidly. Both output deflection amplifier tubes, V_4 and V_9 , should be wired next. It will be noted in the photograph of Fig. 7 that the amplifier output coupling condensers, C_{22} and C_{23} , have been mounted with their metal cases *insulated* from the chassis to minimize the stray capacity to ground. These condensers are mounted by one of their connection terminals on a ceramic feedthrough insulator, thus making a convenient means of connecting to the cathode-ray tube on top of the chassis. It should be further noted that the plate load re-

sistors and peaking chokes for both the input and output stages of each amplifier have been mounted on bakelite terminal boards which, in turn, are mounted a substantial distance away from the chassis. This mounting system affords convenient terminals for the components themselves, and what is more important, minimizes the capacities between these components and ground. Connections between the plates of V_4 and V_9 and the coupling condensers, C_{22} and C_{23} , are made with heavy copper wire, as can be seen in Fig. 7, and go via the terminal strip on the rear of the chassis, thus permitting direct connection to the two deflection plates if desired.

Once the wiring of V_4 and V_9 has been completed, these stages may be readily tested by connecting a potentiometer between ground and the hot side of the 6.3 volt a.c. filament winding, then connecting the arm to the grid of V_4 or V_9 through the input coupling condensers, C_{17} or C_{40} . If the amplifier is functioning properly, a line will appear on the tube screen as the voltage from the potentiometer is increased. This line should expand an equal amount in both directions as the voltage is increased and should continue to do so until both ends are deflected off of the screen.

The horizontal amplifier cathode follower and triode amplifier tube, V_2 and V_3 , and its vertical counterpart, V_7 , and V_8 , may be wired and tested next. The preliminary test procedure for either complete amplifier chain is the same as for the output deflection amplifier previously described, except that in this case, the 6.3 volts a.c. may be direct-connected to the grid of the cathode follower, and the gain controls, R_{13} and R_{48} , (See Fig. 4) used to vary the amplitude.

Following the completion of the amplifiers, the "Horizontal" and "Vertical Input Selector" switches, S_1 and S_3 , should be wired next. The various components associated with these switches should be mounted directly on the switches themselves insofar as is possible. These switches may be seen in Fig. 7. As the full 775 volts is applied to the sweep oscillator through these selector switches, it is desirable to mount them with their shafts insulated from the panel to assist in preventing any voltage breakdown between the high voltage contacts and ground. The attenuator trimmers, C_2 and C_{31} , are mounted on these switches in a position convenient for adjustment. Setting of the attenuator trimmers is discussed under "Testing and Adjustments."

The final stages to construct in this instrument are the Horizontal and Vertical Scanning Oscillators, V_1 and V_6 .

MAY SPECIALS

ANTENNA PARTS from a BC610
50 ft. R G 34 U. with connector N-1.....\$3.95
250 FT. PHOSPHOR BRONZE Stranded transmitting antenna wire NEW.....\$3.95
100 FT. STEEL MEASURING TAPE in metal rewind case NEW.....\$5.95
65 FT. WATERPROOF guy rope with pulley ring and snap NEW.....65c
2 - 65 FT. guy ropes with four pulley rings and snaps NEW.....\$1.25
Brush displacement pickup DP-1. NEW.....\$20.00
FT-167 FEDERAL TRANSMITTER, 200 watts output, 2 to 18 MC with tubes less power supply. NEW.....\$195.00
RA-20 POWER SUPPLY, 115 volts A.C. for BC-312, etc.....\$8.50
GSAP 16 MM CAMERA, f3.5 lens, converted with viewfinder, battery case, etc.....\$45.00
ELECTRONIC MEGAPHONE with amplifier. NEW.....\$44.50
WESTON MODEL 45 AMMETER, 0-15-150 D.C. omfs. NEW.....\$59.00
MOBILE AMPLIFIER - 14 watts output - 12 volts input with mike. NEW.....\$44.50
Dynamic headset and mike. NEW.....\$1.95

SCR522 SPECIALS

Two meter transmitter-receiver with tubes, N-1, \$24.95; U-1, \$17.95; U-2, \$14.95.
Dynamotor - SCR522, N-1, \$3.95; Plugs for SCR522 N-1, \$4.00 per set.
BC602 Control Box, N-1.....\$1.00

BC1206-C SETCHELL CARLSON BEACON RECEIVER 28 volts D.C. 195-420 KC, 5 tubes, N-1.....\$4.95

BC464 TARGET RECEIVER and selector for 5 channel remote control with battery container and ant. 68-73 MC. N-1.....\$14.95

PE104A 6-12 volt vibrapack, N-1 \$5.95; U-1 \$4.95
Vibrator for PE104A. NEW.....\$1.50
BC357J Beacon Receiver, 75 MC, tubes N-1.....\$3.45
GENERAL ELECTRIC BATTERY CHARGER: Tungor 6RB6B17, 12 battery, 12 amp.; 24 battery, 6 amp. N-1.....\$67.50

SCOOP: MN26 RADIO COMPASS RECEIVER with tubes 150-1500 KC U-1.....\$18.95
U-2.....\$14.95

SIGNAL BOX KITE, N-1.....\$2.00
TRIMM commercial 17,000 ohm headset, N-1.....\$4.25
HS-23 8,000 ohm headset, U-2......89c

EE-8 TELEPHONE field sets with handset and ringer N-1, \$15.00 ea., \$28.00 pr.; U-2 \$10.00 ea., \$18.00 pr.; U-3 \$7.00 ea., \$13.00 pr.

TUBE SPECIALS

5PB1.....\$1.15	5BP4.....\$2.50
3AP1.....2.25	4E27.....6.00
872A.....1.75	304TL.....1.75
2X2......75	EF50......90
316......90	9002......75
726.....4.95	211.....1.00
75TL.....2.50	717-A......69

GIBSON GIRL SCR578B transmitter for sending distress signals from boats. Trans., complete with balloon, hydrogen gen., kite and inst. manuals. N-1. Export packed.....\$25.00

EXTENSION CORDS, PL55 plug incl. N-1.....\$.40
HS-30 Ear plug headset N-1, \$.95; U-1.....\$.50
MATCHING TRANSFORMER, HS-30.....\$.50
200FD Johnson var. cond. dual N-1.....\$1.19

APN-1 ALTIMETER INDICATOR - basic movement O-1 m.a. 5 m.a. shunt 270° scale. An excellent basic G.E. movement for constructing your own meters. N-1.....\$1.95
METER RECTIFIER, full wave midget Selenium, 10 volts, 30 MA, N-1.....\$.29

A.C.-D.C. BUZZER, N-1.....\$.89
PL-55 PLUG, N-1 \$.29; 4 for.....\$1.00
AN-160 ANTENNA, N-1, 2,000-6,000 KC; 9 insulators and jumpers 100 ft. long.....\$1.00
.01mFD, 300 V. mica Cap. - Ideal by-pass cond. N-1 \$.25; 7 for \$1.00; per 100.....\$6.00

PHOTOCON SALES

1062 N. Allen Avenue

Pasadena 7, Calif.

BC733D GLIDEPATH RECEIVER NEW.....\$14.95
T-17 MIKE NEW \$1.50, USED.....\$.75
SCR-274 Remote tuning head, 3 crank.....\$1.50
AS-89/ART Ant. System, N-1.....\$2.95

PE-103A DYNAMOTOR N-1.....\$9.95
CD-501A CABLE for PE-103A-BC654A
N-1.....\$1.95
Frame for mobile mounting BC654A-PE-103A.....\$4.95
ANTENNA, 8 sec. 24 ft. for BC654A. Base N-1.....\$7.95

TRANSTAT 10 amp. 0-135 V. N-1.....\$29.50
INTERPHONE AMPLIFIER 9C709. Ideal for aircraft, booster for telephones, etc. 1 tube, batt. operated. N-1.....\$5.00
THROAT MIKE \$.50; **HAND KEY,** N-1, \$.50

BC-348 MNTG. BASE Postpaid.....\$2.50
BC-348 OUTLET PLUG Postpaid......80
BC-348 MNTG. BASE & OUTLET PLUG..... 3.00

LIONEL SPEED KEY, N-1.....\$5.95

Crank for 274-N Receivers..... \$.60

SOUND POWERED chest set, N-1.....\$3.95
SOUND POWERED HANDSET, TS-10, N-1, \$15.00 ea.; per pair.....\$25.00
PHOTOFLASH CAPACITOR, 25 mfd., 2000 V; N-1.....\$10.00
6 CONDUCTOR Plastex Cable for Photoflash, N-1.....\$.35 ft.
PL-8 Range Filter, \$1.95; With cord and plugs.....\$2.50
ANTENNA knife switch, S.P.D.T.\$1.00
SOLA CONSTANT voltage Transformer, 80 V.A., 60 cycle, 115 V.A.C.....\$13.50


APN-4 Receiver, tubes N-1.....\$17.50

PEERLESS A-4233Q Line matching transformer 50/125/200/250/500 ohms, N-1.....\$1.50
CODE: N-1-NEW, U-1-USED EXCELLENT, U-2-USED GOOD.

TERMS: F.O.B. Pasadena unless postpaid. No C.O.D.'s under \$5.00. 25% deposit on ALL orders. All C.O.D.'s shipped by Rail Express. Send full price with order and we will ship by fast truck, transportation collect. Minimum order \$2.00. Californians include 2 1/2% sales tax.

OUTSTANDING VALUES NOW AVAILABLE

AUTOMATIC CAR RADIO

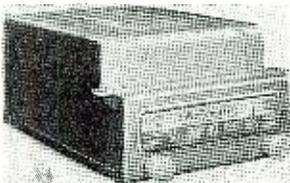

The Best Buy on the Market

Six tube superheterodyne. Two dual purpose tubes, giving 8 tube performance. Simple Universal Mounting. Equipped with G.E. 5" Speaker.

FITS ANY CAR

FEATURES:

- 3 gang tuning condenser
- Beautifully finished case
- Hearing this fine radio is a thrill

Only \$39⁹⁵ includes

One 66" 2 POINT SIDE MOUNT, RUST PROOF ANTENNAS, a \$5.95 SELLER.

SPECIAL ON RECORD CHANGERS DETROLA



FEATURES:

- Plays 12-10 in. or 10-12 in. records
- Extremely smooth action
- 9" turntable
- Size 12" x 12" - 6 1/2" deep

This changer is compact enough to fit in most installations.

PRICED AT ONLY.....\$14⁹⁵

REGAL PORTABLE RADIO

A fine performing set, AC-DC and Battery operation. Attractive case, small and sturdy built. Slide rule dial, 4" heavy magnet speaker.

You and your customers will be pleasantly satisfied with this fine bargain.

Your Cost—\$20.95.
Price of Batteries \$2.01.



CROWE HEADS for AUTOMOBILE RADIOS

A dial to fit any radio and car 1940 thru 1948
Custom Dash Mounting Dials

Under 1940—Universal Underdash Mounting Dials. Dealers Price.....\$3.82

Tuning Units 706-T1 up thru 720-T1. Dealers Price.....\$1.71

Tuning Units with switch 706-T2 up thru 720-T2. Dealers Price.....\$2.40

Volume control units 700-VI. Dealers Price.....\$0.73

Volume controls units with switch. 700-V2. Dealers Price.....\$1.80


Cable kits to fit Delco-Arvin-Philco. Dealers Price.....\$1.74

When ordering, specify Make, and Model of car and make and model of radio.

Complete dial kit consists of "Head, Tuning Unit, and Volume Control Unit.

We carry a complete line of all auto radio equipment and accessories.

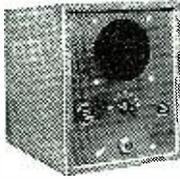Radio Parts Company, 614 RANDOLPH ST., CHICAGO 6, ILL.



FOR THE FIRST TIME! MASTER SELECTIVE SIGNAL CORPS TALKING SYSTEM DRESSED IN A PIANO FINISH WOODEN CABINET.

Talk to any one station, privately or all 5 at once. Any sub-station can originate a call to the master. Ready to plug into 110 volt. AC or DC. Tube line-up 12J5, 12J5, 50L6 and 35Z5. The 45 Ohm voice coil permits tremendously long transmission lines, amazing fidelity on voice. All equipment guaranteed perfect.

Master station with one sub-station and 100 ft. of wire..... \$59.95
 Sub-stations, ea. 6.95
 Wire per 100 ft. 4.00

KITS

Broadcast Band Converter for BC-348, BC-342, BC-312, NC-100, etc. uses 6SA7 fixed oscillator. Nothing extra to buy \$5.00
 10 Meter Converter Kit for BC-342, BC-348, BC-312, etc. Read article in Oct. '47 Radio Craft. Complete kit. Nothing else to buy 7.95
 Home Broadcast Microphone consists of aviator's throat mike, matching transformer, batteries and a sketch to hook to your radio..... 1.98

FM-IF COIL KIT

4-1F Transformers, 20.7 megs, slug tuned including one diode trans. 1.49

SURPLUS SPECIALS

Empty Jack Box Case, dimensions 3-3/16"x4-7/16"x2 1/8"14
 PL68 and PL55 Jack11
 11 Prong Male and Female Plug, banana type, combination24
 Hook-up Wire In Lace Cable Form, per lb.25
 28 Volt Dynamotor, 250 V. Output, Brand New Western Electric79
 800 Ohm, 15 Mil Choke, encased15
 1F Crystal Transformer for BC-312, 342 complete with crystal 7.95

All Merchandise Guaranteed No Orders Less Than \$3.00 Cash—Check— or Money Order

12 Volt Relay19
 Terminal Strip 2-.01, 3.05 Cond. 2-390,000, 2-47,000, 1-27,000 Resistor24
 HS-30 Headset with High Z trans.89

TUBES—NEW—BULK

12A624
 161918
 OZ468
 6SA749
 35Z554
 50L660

SERVICE SPECIALS

45 Ohm Voice Coil 4 in. PM Speaker for intercoms 2.99
 Metal Speaker Baffle for 4 in. PM 1.29
 Extractor Fuse Panel Mount18
 3 Wire Cable per ft.04
 100 Assorted Knobs 1.65
 Condensers—005 Mica04
 Condensers—2 400 Volt, Paper electrolytic06
 50—30 Mfd, 150 Volt, oil filled in can29
 2 Mfd, 600 Volt, oil filled in can16
 8 Mfd, 600 Volt, bathtub39
 PWR Trans. 350-0-350, 60 Mils, 6.3 @ 3 Amps, 5 V, 2A 2.15

THOR ELECTRONICS
 5051 N. Clark St., Chicago 40, Ill.

20 LB. SURPRISE PACKAGE 2.00

Learn and Earn! TELEVISION

RADIO F. M. COMMUNICATION

offer profitable occupation for both men and women. You learn by actual work, how to build and operate, and fit yourself for a higher pay job. Write for catalog.

Approved for Veterans

HOLLYWOOD SOUND INSTITUTE

1040-A N. Kenmore

Los Angeles 27

AVAILABLE NOW

May 1948 Issue of

TELEVISION NEWS

8 pages 10c

Send 10c in coin to

ZIFF-DAVIS PUBLISHING COMPANY

Circulation Dept.

185 North Wabash Avenue

Chicago 1, Ill.

BOOST YOUR TV SIGNAL



on all
13 CHANNELS

VIDEAMP VIDEO BOOSTER

A 13 channel, self-powered, 2 stage TV signal preamplifier.

Pretuned selector system.

Non oscillating original circuit combination with easy matching for any antenna impedance to any tele-set input impedance.

WRITE FOR INFORMATION

List Price \$30

See Your Local Jobber

CRYSTAL DEVICES CO. Dept. B
 1819 BROADWAY NEW YORK 23, NEW YORK

In completing this wiring several precautions may prove helpful. It is wise to insulate the frequency adjustment controls, R_9 and R_{41} , from the panel as the full 750 volts are applied to these potentiometers. In the horizontal oscillator circuit the condenser, C_8 , should be soldered directly between plate and cathode with short leads. It is also desirable to mount the output coupling condenser, C_6 , at least 1/4" from the chassis to keep its capacity to ground low. If metal cased condensers are used for this or any of the other coupling condensers between the amplifier stages, their metal cans *must* be insulated from the chassis to keep these capacities to ground small.

Testing and Adjustments

The adjustments necessary to complete this Television Oscilloscope are not unduly difficult. The frequency range of the two scanning oscillators must be properly set by adjusting the resistors, R_7 and R_{44} ; the high frequency response of the deflection amplifiers should be checked; the two input attenuator trimmers, C_2 and C_{31} , must be properly adjusted; the horizontal scanning oscillator attenuator trimmer, C_3 , must be set.

To adjust the vertical scanning oscillator frequency, the hot side of the 6.3 volt heater winding should be connected to the "H. Amp. In." jack and the "Horiz. Input Selector" set to the "Low" gain position. The "Vert. Input Selector" is then set in the "Scan" position and the "Vertical Scan Frequency" control set at the position of *minimum* resistance, which should be fully clockwise. A potentiometer having about 10,000 ohms resistance should now be connected temporarily in place of R_{44} and adjusted until one cycle a.c. waveform stands approximately stationary on the screen. The resistance required to bring about this condition is then measured with an ohmmeter, and a fixed resistance of this value is then permanently soldered in the circuit.

In adjusting R_7 to the proper value, the same general procedure is followed. However, it is preferable to use a frequency of 1400 cycles, which coincides to the lowest frequency limit of the second highest frequency range of S_4 . This requires an accurate audio oscillator, but if one is not available, fairly satisfactory results may be had in setting R_7 by utilizing the 60 cycle point of the lowest frequency range in conjunction with the 60 cycle a.c. filament voltage.

In either case, the a.c. frequency comparison voltage is connected to the "V. Amp. In." jack, the "Vert. Input Selector" is set at "Low" and the "Horiz. Input Selector" is set at "Scan". Care should be taken to see that the "Horiz. Sync" switch is in the "Ext." position.

It should be remembered that the lowest frequency on any range is secured when all the resistance of R_0 is in the circuit, and the highest when none of it is in. Once all controls have been properly set, R_7 is rotated until *one* sine wave cycle of oscillation appears approximately stationary on the screen.

While not absolutely necessary, it is desirable, if an audio oscillator is available, to check the frequency coverage of all six ranges of the "Horizontal Scan Frequency" selector switch, S_4 , to make sure that the frequency ranges coincide approximately to those shown on the panel in Fig. 3, thus making certain that there is continuous frequency coverage between 20 and 20,000 cycles.

The commercial tolerances of components together with their placement within the oscilloscope may make the *actual* frequency response of a deflection amplifier a little different than its *expected* frequency response. This deviation, if any, will be most noticeable at the high frequency limit. Therefore, if peak performance is expected from the instrument, it is highly desirable to actually check the high-frequency response. Fortunately, this may be accomplished very easily with the aid of a square-wave generator operating at approximately 15 kc. This frequency was chosen since an amplifier's high frequency response must be substantially flat up to approximately the 15th harmonic of the square-wave fundamental frequency in order to actually pass the square-wave without noticeable distortion.

Since a square-wave generator is seldom found in the experimenter's laboratory, a simple circuit for such a device is shown in Fig. 5. As can be readily seen, it consists of a 6SJ7 transitor sine wave oscillator driving a 6SN7 wave-squaring amplifier. No adjustments have been included, since only one frequency and one output voltage are needed. The circuit is nearly fool-proof in operation. Upon completion, it is desirable to check the actual output wave shape to secure a basis for comparison when checking the amplifiers. This is accomplished by running the output of the square-wave generator through two, short, unshielded leads directly to the vertical deflection plate connection on the rear of the oscilloscope and to the "H. Sync. In" jack on the panel. An additional ground lead should connect the two chassis. With the "Horiz. Sync." switch in the "Ext". position, the "H. Sync. Gain" and "Horizontal Scan Frequency" controls are adjusted until two or three stationary square waves are observed on the cathode-ray tube screen. This pattern should be carefully noted, as it is the "standard" by which the amplifier's performance is judged.



HAS THE VALUES!



HERE ARE A FEW TYPICAL OF WHAT IS TO BE FOUND IN THE BIG NEW B-A CATALOG #481

116 BIG PAGES PACKED WITH THE LATEST DEVELOPMENTS IN RADIO AND ELECTRONICS, Sets, Supplies and Apparatus . . . For Trade—Industry—Communications—Public Utility—Experimental and Hobby Applications.

A Bargain Section Packed With OUTSTANDING VALUES in desirable WAR Surplus and other SPECIAL VALUES.

Write For Your Copy of Catalog #481 If You Did Not Receive It.

Only \$13.88 for this Quality RECORD CHANGER



A fortunate purchase from an overstocked manufacturer enables us to offer these popular UTAH Model 650 Record Changers AT A BIG SAVING.


Features: Single post, gearless construction. Quiet and fast during change cycle. Plays 10 twelve-inch or 12 ten-inch records. Rejects any record desired. Light weight balanced tone arm with quality crystal cartridge for any standard needle.

Has heavy, die cast base plate 10 $\frac{3}{4}$ " x 12 $\frac{1}{8}$ ". Mounting size approx. 12 $\frac{1}{4}$ " x 13 $\frac{3}{8}$ ", extends 5 $\frac{3}{4}$ " above and 2" below mounting. Operates from 110 volts, 60 cycle.

No. 40A1000 Bargain Priced, Each.....\$13.88 Two in Factory carton, for only.....\$25.00

BIG VALUE—AC-DC Superhet

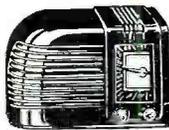Graceful design, dependable performance anywhere. An outstanding value! Proven Superhet circuit, 5 dependable tubes (including rectifier). Full size 5" Alnico "V" PM speaker for wonderful tone. Airplane dial. Modern Plastic cabinet Ivory finish size 10 $\frac{1}{2}$ x 5 $\frac{1}{2}$ x 6 $\frac{3}{8}$ ". No. 31A224, SPECIAL EACH.....\$15.94




3 WAY "PERSONAL" AC-DC and BATTERY OPERATED PORTABLE

Superhet circuit, 4 tubes plus Selenium rectifier. 5" Alnico PM speaker. Iron core I.F. Safety switch for operation from 110 volt AC or DC electric current or from self contained batteries (1-746 "A" and 1-467 "B") available anywhere. Beautiful dual colored Polystyrene Shatter-proof molded cabinet with plastic easy grip handle. Large slide rule dial. Vernier Hi-ratio tuning. Small, only 4" wide, 8 $\frac{3}{8}$ " long, 7 $\frac{1}{4}$ " high. Weight only 5 $\frac{1}{4}$ lbs. with batteries. A "Honey" for in the home or "on the go." No. 36A66 Less Batteries, ONLY.....\$21.95 Set of batteries (1-746 and 1-467).....\$2.40



ALUMINUM UTILITY CASE LIGHTWEIGHT DURABLE EYE APPEALING IDEAL FOR

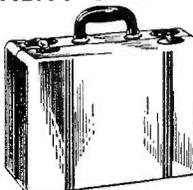- Radio Serviceman's parts and tool kit
- Tube carrying case
- P.A. accessory case
- Camping, Fishing, Picnics, all family use



Life time aluminum case with bakelite handle, lock and key. Size 15" long, 11" wide, 5" deep. Weight only 3 lbs. Shipping weight approx. 5 lbs. No. 36A75—Very Handy For Everyone, NET EACH.....\$3.65

1000 V.—200 Ma. Power Supply FILTER KIT

Consist of Two 4 mfd. 1000 volt DC oil filled condensers size 2 $\frac{1}{2}$ x 1 $\frac{1}{8}$ x 5 $\frac{1}{2}$ " high overall and One Thordarson 10 Hy.-200 Ma. filter choke fully enclosed metal case size 3 $\frac{3}{8}$ " sq x 4 $\frac{3}{8}$ " H. No. 21T3983 ONLY.....\$3.65




2 MFD. 2500 VOLT OIL FILLED CONDENSER

Well known brand. Ceramic pillar terminals, in hermetically sealed metal case, size overall 1 $\frac{3}{4}$ x 3 $\frac{3}{8}$ x 5 $\frac{1}{2}$ " high. Comes with handy removable mtg. bracket and solder lug terminals. No. 21T3990, Special, Each.....\$2.95



"Re-Mote" REAR SEAT

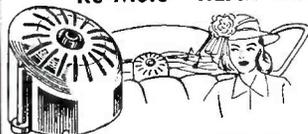

Car Radio Speaker

Easy to install in a few minutes—no cutting of holes required. Furnished complete with 17 ft. wire, fittings, resistor to match speaker to any standard Auto Radio and complete instructions. Consist of 5" quality PM speaker in beautiful marbled french gray plastic case, volume control built in. No. 14A650 Your Cost Each.....\$6.37

80, 75 and 40 Meter CRYSTALS, 10 for \$3.95

In FT 243 holders, cut from highest quality quartz, accurately ground and acid etched. Frequency marked on each with in 2 KC. Sorry we must sell them in ass't. our pick of frequencies—but you can't go wrong! There are plenty of choice frequencies for 80, 75 and 40 meters or for doubling to 20 and 10 meters in each ass't. Every one guaranteed to be an active oscillator. Stock No. 21T 3991 Assortment of TEN — ONLY.....\$3.95

WEATHERPROOF WIRE at GIVE AWAY PRICES

Stranded tinned conductors (3 copper, 4 steel) flexible, yet unusually strong to stand long runs. Conductor is rubber covered with overall weather-proof saturated braid; OD 5/32". Perfect for lead-ins, telephone, intercoms, etc. BRAND NEW in original factory wound coils. No. 4A503, Three Conductor Per 550 Foot Coil, ONLY.....\$4.95

No. 4A502, As above except Single Cond. Per 900 Foot Coil, ONLY.....\$2.95

Order direct from this ad. Our Terms: Cash With Order or C. O. D. with 20% deposit please. Radio Sets Shipped Via. Express Only.

WRITE FOR YOUR COPY OF CATALOG No. 481 IF YOU DID NOT RECEIVE IT.



BURSTEIN-APPLEBEE Company

1012 McGEE, KANSAS CITY 6, MO.

IF IT'S IN RADIO
Resco Has It!

Preferred by the Experts!

**XCELITE
NUT DRIVERS**



DE LUX SET NO. 27
Colored handles for easy identification. Comes in handy, lockable metal tool holder. Fire- and shock-resistant plastic handles. Precision formed sockets deep enough to handle two nuts.

Set of 7 Drivers and Handy Holder **3.90** Net

XCELITE SET NO. 17

Set of 7 nut drivers similar to above with handles all same color. In metal stand. **3.36** Net

**SPECIAL! PYREX
ENTERING INSULATORS**

- NUMBER—67076
- BOWL—67037
- GLASS — OPAQUE
- LENGTH, CENTER PIN — 11 1/2"
- OUTSIDE BASE DIAMETER — 8 3/4"



Furnished with a template ring 1/16" thick for locating mounting holes for the 2-9/16" studs. Template can also be used as backing ring or washer. Equipped with two 3/8" jamb nuts for lower end of center pin and two 1/2" jamb nuts for each stud. Same as illustration, but opaque.

REGULAR PRICE \$29 **\$5**

A Resco Special!

**2-VOLT SINGLE CELL
STORAGE BATTERY**



As used in models of General Electric Portable receivers, 3" wide, 4" deep, 5 1/2" high. In clear plastic case, with 3 colored balls to show state of charge. Complete with charging and maintenance instructions. Shipped dry.

Qt. Bot. of Acid **95¢** **1.49** Net

**Special! 4-Prong 6-Volt
VIBRATOR**



Similar to Mallory 294 or Radiant 5300.

95¢ **90¢** Ea. **85¢** Ea.
Each Lots of 12 Lots of 25

Write for Big, Value-Packed Bulletin. Include Postage with Cash Orders

Radio Electric
SERVICE CO. OF PENNA., INC.

7TH AND ARCH STREETS, PHILA. 6, PENNA.
Branches: 5930 Market St. & 3145 N. Broad St., Phila.
Also in Wilmington, Del., Easton, Pa., Allentown, Pa., Camden, N.J.

To check the vertical amplifier's high frequency response, the output of the square-wave generator is fed to the "V. Amp. In." jack and the "Vert. Input Selector" is set in the "High" gain position. With the "Horiz. Sync." switch now in the "Int." position, the various frequency and gain controls are adjusted until several stationary square-waves appear.

If the amplifier is performing properly, these square waves should have exactly the same waveshape as when the generator was connected directly to the vertical deflection plate. The important points to notice are the sharpness of the corners and the flatness of the tops. If any of the corners are rounded, or the tops not perfectly straight, the value of cathode condenser, C₃₀, should be altered to achieve the squarest possible waveshape.

By simply rotating the "Vert. Input Selector" switch to the "Low" gain position and advancing the "Vertical Gain" control somewhat, the input attenuator condenser, C₃₁, may now be set. This adjustment should be made with an insulated screwdriver and will be correct when the same, undistorted square wave is obtained.

In testing the horizontal amplifier, altering the value of C₁₈, and setting the attenuator trimmer, C₂, the same procedure is followed except that the horizontal and vertical control functions and connections are interchanged. One additional lead must be run from the output of the square-wave generator to the "V. Sync. In." jack, and the vertical sweep frequency condenser, C₃₆, must be temporarily changed to .001 μfd. to secure a sufficiently high sweep speed. In this case the square waves will appear vertically instead of horizontally.

The final adjustment on the Television Oscilloscope is the setting of C₃, part of the output attenuator for the Horizontal Scanning Oscillator. To do this most easily, a source of 150 kc. oscillations should be available. If not handy, such as oscillator may be easily made by changing the values of the tuned circuit for the 6SJ7 transitor oscillator in Fig. 5 to 2.5 millihenrys for the inductance and .0005 μfd. for the condenser. With the 150 kc. output (taken directly from the 6SJ7's suppressor grid, pin No. 3), connected to the "V. Amp. In." jack, the "Horiz. Sync." switch is placed in the "Int." position, the "Horizontal Scan Frequency" selector switch is placed in the highest frequency position, and the instrument is then adjusted until 10 cycles of oscillation, including those which can be seen on the return trace, are stationary on the screen.

It will be found that the setting of C₃ influences both the linearity of the scanning trace (the equidistant spacing of

the a.c. cycles) and the return trace time (the dimmer of the two traces). The proper setting of this condenser will be the point where the fewest number of cycles appears on the return trace, while maintaining good linearity on the scanning trace. If the circuit is functioning correctly, it should be possible to get less than one and one-half cycles appearing on the return trace while keeping good linearity. This indicates that less than 15% of the time for each scanning cycle is occupied by the return trace.


Test Leads

The simplest method of connecting voltages to be observed on the cathode-ray tube screen to the instrument is through a short length of unshielded wire, with an additional short wire run between the ground connection of the oscilloscope and the chassis under observation. Such a connection, however, requires that the oscilloscope and the item under test be close together, and in addition, if the voltage being observed is small the stray pickup of the unshielded lead may seriously distort the pattern. Although a shielded lead does overcome stray pickup, it is generally unsatisfactory, as any usable length may have sufficient capacity to upset both the circuit under test and the high frequency response characteristics of the oscilloscope.

To overcome these difficulties, it is most desirable to construct one or more of the attenuator-type test leads similar to those furnished with some commercial oscilloscopes. This type of test lead may be made any reasonable length from shielded cable without any frequency discrimination taking place, and in addition, it affords a very light load to the circuit under test. The circuit for this test lead is shown in Fig. 6A and a sketch of one possible layout for the test prod and cable is shown in Fig. 6B. This will be recognized as the familiar resistance-capacity attenuator used several times previously in this instrument, but in this case, one of the condensers making up the attenuator is the actual capacity of the shielded cable itself. No value is given for the resistance connected across this cable capacity, since the value will depend on the type and length of cable used. It will probably fall, however, in the vicinity of 150,000 ohms. The small trimmer in the test prod is adjusted just like the similar trimmer was adjusted for the "Low" position attenuators in the oscilloscope itself with the aid of the 15 kc. square-wave generator output applied to the input of the prod itself. The resistor across the cable capacity should be cut and tried until the familiar square wave can be obtained. Once properly set, the prod capacity adjustment should be covered as it will not require changing unless the cable itself is changed.

NEW GUARANTEED SURPLUS!!

SYNCHROS

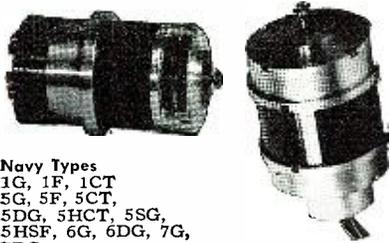

Navy Types
1G, 1F, 1CT
5G, 5F, 5CT,
5DG, 5HCT, 5SG,
5HSF, 6G, 6DG, 7G,
7DG, etc.

Pioneer Autosyns—AY-1, AY-14, AY-20, AY-30,
AY-54, AY-101D, 851, etc.

Elinco M1-1, M1-2. Kollsman 775-01. G.E.
2J5HA1, 2J5FB1, 2J6F3, 2JD5HB1, etc.

DC MOTORS

John Oster. Series wound. 27 V. 7000 rpm.
1/100 H.P. Stock #SD-30. Price \$2.75 ea.

Westinghouse—1171391. 27 V. 6.5 amps. series.
Fan cooled. 3" diam. 4 1/2" lg., 1/8 H.P. Cont.
duty stock #SD-156. Price \$6.75 ea.

Delco 5069370. 27.5 V. Alnico field. 10,000 rpm.
Similar to S-65 but has straight shaft extension.
Stock #SD-16. Price \$4.75 ea.


DC Timing Motor—Haydon 1/2 rpm. 29 volts,
100 mills. Stock #SD-157. Price \$3.75 ea.

Constant Speed D.C. Motor—G.E. 5BA25MJ24.
24 V. D.C. 7100 rpm. RC noise filter. Stock
#SD-100. Price \$8.50 ea.

Radio Compass Loop LP-21-LM. Stock #SD-99.
Price \$9.50 ea. net.

Phase Shift Capacitor — 4 stator single rotor.
0-360° phase shift. Stock #SD-114. Price
\$4.75 ea.

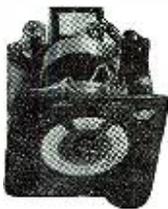Magnesyn—Pioneer CL-3, 6 power. Transmitter
or receiver. Stock #SD-6. Price \$3.75 ea.



Null Type
Synchro Indicator


Consists of Bendix size 5 synchro, rectifier,
transformer, magic eye tube and illuminated
360° dial. Manually tuned to null. Ideal for
experimenters and labs. Stock #SD-119. Ship-
ping wt. 10 lbs. Price \$6.95 ea.



Size 5
Synchro
Generator

Similar to Navy Ordnance type 5G with shaft
detail per Army Ordnance Dwg. C-78414. 115
V. 60 cy. Stock #SD-43. Price \$9.50 ea.

SERVO MOTORS

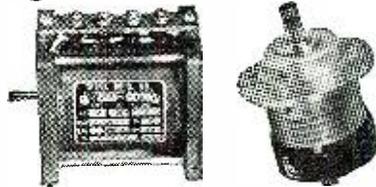

Pioneer CK-2, CK-5, 10047-2-A and
Kollsman 776-01 for 400 cycles.
Diehl FP-25-3, FPE-25-11 (CDA-211052) and
ZP-106-8 (CDA-211377) for 60 cycles.
Quantity Prices on Request.

400 CYCLE MOTORS

E.A.D. J-33. 115 V. 3 phase. Synchronous. 8000
rpm. 2" x 3". Stock #SD-59. Price \$6.75 ea.

E.A.D. J-72B. 115 V. 2 phase induction motor.
4700 rpm. Stock #SD-140. Price \$9.75 ea.

Westinghouse Blower. Type FL. 6700 rpm.
Capacitor type motor. 17 C.F.M. blower. Out-
let 3/4" x 1 1/8". Includes capacitor. Stock
#SD-144. Price \$6.75 ea.

Quantity prices on request.

D.C. Motor-Delco 5069466

Alnico field. 27.5 V. 10,000 rpm. 1" x 1" x 2".
Use as motor or as tachometer generator. Stock
#SD-65.



Price \$1.95
each
Add 15c for
P.P. & handling

Microwave Antenna—

AS-217A/APG 15B. 12
Cm dipole and 13 inch
parabola housed in
weatherproof Radome
16" diam. 24 V. DC
spinner motor for conic
scan. Stock #SD-95.
Shipping wt. 70 lbs.
Price \$9.50 ea.



Remote Position
Indicating System—



6-12 V. 60 cycles. 5 inch indicator with 0 to
360° dial. Heavy duty transmitter. Stock
#SD-115. Price \$9.95 per system

PIONEER SERVO AMPLIFIERS
PIONEER TORQUE UNITS
KOLLSMAN COMPASS SYSTEMS
SINE COSINE GENERATORS

INVERTERS



Pioneer
12116, 12117,
12121, 12123, etc.
Holtzer Cabot MG-149F, MG-149H, MG-153F,
etc.

General Electric 5D21NJ3A, etc.
Leland 10563, etc.

60 CYCLE AC MOTORS

G. E. Reversible. 1/150 H.P. Shunt wound. 40
volts 5000 rpm. Split field. Stock #SD-18.
Price \$4.75 ea.

Stock #SD-19. Similar to above but not split
field. Price \$2.75 ea.

Barber-Colman. 0.001 H.P. wound shaded pole
type. Reversible by relay or s.p.d.t. switch.
Stock #SD-27. Price \$3.75 ea.

Timing Motor — Haydon 1 rpm. 115 V. A.C.
Stock #SD-133. Price \$2.85 ea.

G. E. Amplidyne—5AM45DB15. MG-16-A. In-
put 115 V. 60 cy. Output 250 V. D.C. at 0.6
amps. Cont. Duty. Stock #SD-147. Price
\$59.50 ea.

DC Selsyn System—24 V. D.C. transmitter and
indicator. Indicator calibrated for flap position.
360° dial easily added. Stock #SD-129. Price
\$9.50 per system.

Pioneer Magnetic Amplifier Assembly. Saturable
core type output transformer. 400 cycle. Oper-
ates from plates of 6SN7 to supply 1 phase of
servo motor. Stock #SD-44. Price \$8.75 ea.

Sinusoidal Potentiometer — Navy Type CFW-
631539. 32000 ohms. 2 output voltages. Sine
and Cosine function of shaft position. D.C.
input. Stock #SD-124. Price \$12.50 ea.

TACHOMETER GENERATORS



Elinco PM-2

1.75 V. D.C. 100 rpm.
Use to 2000 rpm. Stock
#SD-53. Price \$6.25 ea.

Elinco FB-55. 4.7 V. per 100 rpm. Use to 10,000
rpm. Stock #SD-3. Price \$12.50 ea.

ALL PRICES F.O.B., CLIFTON, N. J.

SERVO-TEK PRODUCTS Co.

INCORPORATED
Surplus Division

ARmory 4-2677

Write or call for
complete listing.

Open account shipments
to rated concerns,
others may order C.O.D.

247 CROOKS AVE.

CLIFTON, N. J.

GREEN

"The House of Bargains"

ALNICO V 5" PM SPEAKERS

1 oz. magnet

For added power and performance order these Alnico Speakers. Truly a fine buy!
Less output transformer **\$1.19**



"Utah" 2,000 Ohm DUAL HEADSET

A favorite, high quality, dependable headset. Highly sensitive. Practical phones for every headset use. Has adjustable, flexible metal-split headband; 4 1/2 Ft. covered cotton cord **\$1.79**

BY-PASS CONDENSERS

600 VOLT

STANDARD BRAND

mfd	price ea.	price per 100
.01	.07	\$ 6.00
.02	.07	6.00
.05	.13	12.00
.001	.07	6.00
.002	.07	6.00
.005	.07	6.00
.25	.16	15.00



TUBE SPECIALS!

BRAND NEW STANDARD BRAND

	list	Our Special!
1LN5	\$2.55	96c
024	2.20	88c
35Z5GT	1.15	46c
50L6GT	1.50	60c
12SA7GT	1.80	72c
12SK7GT	1.50	60c
12SQ7GT	1.50	60c
35W4	1.15	45c
616	2.65	79c
50B5	2.80	70c
6SN7GT	2.20	88c
117L7GT	3.90	1.56
12A8GT	1.80	72c
75	1.50	60c
3S4	1.80	72c
7C5	1.80	72c
6AB7/1853	2.65	1.26

OTHER SPECIALS

8x16 Mfd., 450 V. Tub. Electrolytic Condenser.....	69c
20 Mfd./450 V. Tubular Condenser.....	49c
50 Mfd./50 V. Condenser.....	39c
40 Mfd., 450 Can Condenser; inverted neck mtg.....	99c
40 Mfd., 150 Condenser.....	39c
50-L-6 Output Transformers.....	44c
1 meg.-2 meg. 500,000 Ohm Vol. Cont. with switch & Tap.....	54c
100 mfd 25 volts Tub. Cond.....	29c

Tubular Type

Television Condensers
up to 10 Watts 83c
.002 2500 Working Volts 73c
.03
.03

SPECIAL 63c each

.05-3000 Working Volts	83c
.005-3000 Working Volts	73c

Antenna Loops—Medium Size	\$.24
Selenium Rectifiers—100 mill74
8" 4 ohm auto speaker.....	3.19
12 inch PM Speaker, Alnico 5 Magnet handle up to 10 Watts.....	4.79
No. 22 Solid Pushback wire, 100 Ft. rolls; Var. Color49
No. 40, No. 42, No. 44, No. 46, No. 47 PILOT LAMPS. Box of 1044

ALL MERCHANDISE BRAND NEW AND 100% GUARANTEED
NO SECONDS! NO REJECTS! NO OFF-BRANDS!
STANDARD BRAND MERCHANDISE ONLY

20% Deposit Required with C.O.D. Orders.
All orders FOB New York. Minimum orders \$2.00.

GREEN RADIO DISTRIBUTORS

Electronic Supplies and Equipment

482 SUTTER AVENUE
BROOKLYN, NEW YORK
DI. 2-4444

The uses to which this instrument may be put are almost limitless and no attempt will be made here to list all the possibilities. However, a few generalities concerning its use may assist those not having had previous experience with such a device.

This instrument will serve two basic purposes, namely, permit observation of various voltage waveforms, and function as the picture and scanning portions of a complete television receiver. When viewing waveforms, the generally followed procedure is to apply the voltage under test to the "V. Amp. In." jack. The "Horiz. Sync." switch is usually used in the "Int." position and the various sync and amplifier gain and frequency controls are then adjusted until the desired number of cycles of the waveform under observation appear stationary on the screen.

The following generalities should always be observed for most satisfactory use of the oscilloscope. (1) Always view the various waveforms as large as possible consistent with the information desired. (2) Always turn the intensity of the pattern to the lowest point which still gives an image of comfortable intensity. (3) Always use the lowest value of sync. voltage which will permit the pattern to stand still as too much sync. will lengthen the return trace time in some cases and cause pattern distortion in others. (4) Always keep the spot moving either with the sweep oscillator or some other voltage so that the cathode-ray tube beam will not burn the screen.

Using this instrument to observe television pictures is relatively simple. Horizontal and vertical sync. signals having positive polarity are required to syn-

chronize the two scanning oscillators, and a negative video voltage is required to operate the grid of the cathode-ray tube. Both "Input Selector" switches are turned to the "Scan" position. The frequency of the horizontal oscillator is then set to approximately 15,000 cycles per second (in the case of standard 525 line television pictures) and the vertical oscillator is set at approximately 60 cycles. The "Horiz. Sync." switch is set in the "Ext." position, and the two synchronizing voltages are connected to the "H. Sync. In." and "V. Sync. In." jacks respectively. The video voltage is connected through the shortest possible lead to the "Grid" terminal. The two "Sync. Gain" controls are then simultaneously adjusted with the two "Scan Frequency" controls until the television picture is synchronized both horizontally and vertically, then the "Horizontal Gain" and "Vertical Gain" controls are adjusted to give the desired picture size. The reader may be interested to know that the instrument described herein was used for some months to watch the experimental transmissions from the DuMont television station in Washington, D.C., with considerable success.

This instrument cannot rightly be called "simple", yet it is completely straightforward in most respects. In completing the construction and adjustment of this oscilloscope the work should not be rushed, as it will be found that the satisfaction of building and using an instrument of such versatility and performance will make the effort expended well worthwhile. A modest amount of skill and a considerable amount of care will pay off handsomely in this project.

-30-

1948 PARTS SHOW HELD MAY 11-14

THE 1948 Radio Parts and Electronic Equipment Conference and Show being held at the Hotel Stevens in Chicago from May 11-14th promises to be the biggest the industry has ever sponsored.

Arrangements have been made with American Television, Inc. to televise the Show. From vantage points in several parts of the Exhibition Hall, latest model orthicon cameras and links will scan the 168 booths and also telecast interviews with Show officials, exhibitors, and prominent visitors.

This year's "Keynote Dinner" will feature a novel program which will include some of show business' brightest stars. No formal speeches have been scheduled for the banquet as the emphasis is being placed on theatrical entertainment.

According to this year's program, Sunday, May 9th and prior days will be devoted to sales meetings with the erec-

tion of displays in the Exhibition Hall on Sunday. Monday will be "Associations' Meeting Day" with meetings scheduled for NEDA; "The Representatives" of Radio Parts Manufacturers, Inc.; "Canadian Luncheon", Radio Parts Sales Manager Assn. of Canada; Sales Managers Club, Eastern Division, and the Association of Electronics Parts and Equipment Manufacturers in joint session; Radio Parts and Electronic Equipment Shows, Inc.; and the Industry Dinner.

Tuesday will be "NEDA Day" with attendance at the Exhibition Hall confined to exhibitors, their booth attendants and sales representatives, and to members of NEDA. Wednesday will be "Invitation Day (Courtesy NEDA)" and Thursday will be "All Distributor Day"—both days being open to all distributors. Friday will be "All Industry Day" with attendance open to all persons connected with the radio parts and electronic equipment industry.

-30-

International Short-Wave

(Continued from page 144)

11.913 and 7.153, 0845-1100; news 0900, and Ministry of Foreign Affairs news 0915; on Sundays at 0930-1000 has "Bringing Christ to the Nations." To Europe, America, China, South Seas, 11.913 and 7.153, 1100-1145; news 1100; off 1145 with Chinese National Anthem.

Kary, Pa., has received these late schedules of XGOA, Nanking — (1) to North America, 1930-2300, news 2110, 2330, commentary 2140, talks 2200, Chinese opera (*English* introduction) 2240, 11.835, 9.730; (2) musical hour (Mon., Peiping Opera; Tue., symphony; Wed., Cantonese Opera; Thurs., Chinese Concert; Fri., symphony; Sat., Peiping Opera; Sun., Sunday Music), 0300-0400, 11.835, 9.730, 660 kcs.; (3) to Philippines, Australia, New Zealand, South Pacific Islands, 0400-0600, 11.835; news 0500, commentary 0530, talks 0440; (4) to Mongolia, Tibet, South Sea (Chinese), 0600-0700, 11.835, *no English*; (5) to Japan, Siberia, 0700-0830, 11.835, *no English*; (6) to India, South Africa, Eastern Europe, 0830-1015, 11.835, news 0900, Fr. news 0840. (*It is quite likely that XGOA will replace 11.835 with 15.350 for the summer months.* The 11.835 outlet has been heard with improved signals since the Manila relay of "Voice of America" moved to 11.89 from 11.84.—K.R.B.)

Sanderson, Australia, reports XPSA, 7.010, Kweiyang, is heard with Western music at 0630 and with short *English* news at 0700; reports XMAG, 4.27, Nanking, with AFPS program at 0600, good level, and XMNG, 7.34 (location not indicated) at 0615 with news in Chinese, some QRM.

Curacao—PJC2, 7.250, "Radio Princess Juliana," Willemstad, has *English* program on Wednesdays at 2000-2030; power is given as 3 kw. (Boice via Southall, Pa.)

Czechoslovakia—Prague appears to be using 11.840 to North America daily, 2000-2100, with news around 2000 or 2035; signal has been improving lately. (Bishop, Ohio)

Dominican Republic—H12T, "La Voz del Yuna," located at Ciudad Trujillo, has been reported using various frequencies in the 31-meter band, but more recently seems to have settled on about 9.735, signing on around 0700 with powerful signal.

Egypt—SUX, 7.867, Cairo, is heard in Ireland around 1445-1630. (MacAnaspe)

Ethiopia—ETA, Addis Ababa, 15.057 (varies) has not been heard in Newfoundland recently. (Peddle) Brownless, England, reports that one on about 15.075 on Saturdays at 1230. Also heard Saturday at 1320 (some weeks ago) in Philadelphia. (Southall, Pa.)

May, 1948



ESPEY Television Training Kit

Learn television through this unique "assembly line" procedure. Modern circuits and postwar design make up-to-the-minute training an absolute necessity. This ESPEY television training kit will help you understand and gain a working knowledge of TELEVISION—the latest development in electronics. FREE with every kit—a new type of pictorial instruction book, giving easy-to-follow, step by step method. No previous knowledge of television necessary to build—and LEARN from—this ESPEY kit.

FEATURES

- 18 tubes, including 15 miniatures.
- 3 stage, stagger tuned pix i.f.
- 21.25 Mc sound i.f. Trap tuned.
- Balanced FM discriminator.
- Portable—weighs only 17 lbs.
- Uses 3" low-cost cathode ray tube. Magnifier makes 20 sq. in. picture.
- Can be aligned with ordinary test oscillator and V.T. Voltmeter.

KIT INCLUDES: All i.f., power blocking oscillator transformers, chokes, capacitors, resistors, controls, speaker, and sockets riveted into place on punched and welded chassis. All tubes are easily-obtainable types available through distributors everywhere.

*Prices 5% higher West of Rockies.

FOR FURTHER DETAILS WRITE TO:
Dept. A

ESPEY MANUFACTURING COMPANY, INC.

528 EAST 72ND STREET-NEW YORK 21, N.Y.

RADIO ENGINEERING DEGREE IN 27 MONTHS

Intensive, specialized course, including strong basis in mathematics and electrical engineering, advanced Radio Theory and Design, Modern laboratory, Low tuition. Self-help opportunities. Also 27-month courses in Aeronautical, Chemical, Civil, Electrical and Mechanical Engineering. Gov't approved for G.I.'s. Enter June, Sept., Dec., March. Catalogue.

INDIANA TECHNICAL COLLEGE

958 E. Washington Blvd., Fort Wayne 2, Indiana

PEN-OSCIL-LITE

Extremely convenient test oscillator for all radio servicing; alignment • Small as a pen • Self powered • Range from 700 cycles audio to over 600 megacycles u.h.f. • Output from zero to 125 v. • Low in cost • Used by Signal Corps • Write for information.

GENERAL TEST EQUIPMENT
38 Argyle Buffalo 9, N. Y.

GREYLOCK

A Dependable Name in
RADIO TUBES

GT, Glass, and Miniature Types

ALL TUBES IN INDIVIDUAL CARTONS
12SA7, 12SK7, 12SQ7, 50L6, 12AT6,
12BA6, 12BE6, 35W4, 50B5 ...each 39c
1R5, 1S5, 1T4, 3S4, 3Q4, 6AK5, 6AC5,
6AC7, 6AQ5, 6BE6, 6BA6, 6AU6,
6BJ6, 6X4each 49c
32L7, 70L7, 117L7each 59c
All Tubes Carry RMA 90-Day Guarantee

PM SPEAKERS

4" Alnico No. 5each \$1.19
5" Alnico No. 5each 1.29
TERMS: Net C.O.D. No order accepted for
less than \$5.00

Write for Bargain Catalog N-5
GREYLOCK ELECTRONIC SUPPLY CO.
30 Church Street New York 7, N. Y.

Studio Quality AMPLIFIERS

WITH CUSTOM-BUILT FEATURES

Design of Bardwell & McAlister's New Commercial Amplifiers embodies the principles which have been proven in custom-built units developed in the Motion Picture Industry, where quality is requisite. Fully licensed.

12w. models operate up to 8 indoor speakers, effectively cover outdoor audience of 2500.

25w. models operate up to 16 indoor speakers, effectively cover outdoor audience of 8000.

Designed & fabricated by manufacturers of high quality Sound & Recording Equipment for the Motion Picture Industry. Union made.

2 to 4 high gain input channels and 2 to 4 high or low gain radio or phonograph input channels.

With or without professional "T" type bass and treble equalizers.

High fidelity reproduction at any setting of volume controls up to full rated output with less than 4% distortion.

Frequency response flat within 1/2 db from 50 to 10,000 cycles

Output impedances 500, 250, 16 & 8 ohms. Overall gain 105 db. Hum level 85 db below full output.

Write today for informative catalog & Technical data.
Dealer inquiries invited.

12



ELECTRONIC DIVISION
BARDWELL & McALISTER, INC.
BOX 1310, HOLLYWOOD 28, CALIFORNIA

TRADIO-ETTE



Here's the **KEY** to more profits every day!

Here's one of the finest business opportunities in years. You can cash in on the fact that people like radio with their meals. That's why Tradio-ette—a small, compact coin-operated radio designed for restaurant and tavern booths—has become so nationally popular. Plays 15 minutes for 10c.

Small Investment

Thousands of high-yield locations are available if you get in on the ground floor. Only a small investment needed to operate this lucrative full or part-time business. Tradio is the nation's leading manufacturer of coin-operated radios.

For Complete Details . . .
Contact Us Today!

Write Dept. P-5

TRADIO, Inc. ASBURY PARK
NEW JERSEY



1 WATT NEON

NE-30 105-125 volts, Medium screw base. Fits standard light socket. Excellent night light or R F indicator. Original factory cartons.
14¢ ea. 10 for \$1.29



MICA TRIMMER

10-140 mmfd. Micomold. Isolantite mounting. OD 1 1/4" x 1" x 3/8"

BRAND NEW . . . 5¢ ea.



3 CONDUCTOR TELEPHONE CORD

5 1/2 feet long. Brown cotton braid. Color coded. Spade lugs on all leads.

BRAND NEW . . . 9¢ ea.




VHF TANK CIRCUIT

BRAND NEW 29¢ ea.



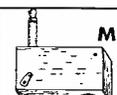Split-stator midjet variable condenser. 4 plates per section. Isolantite insulation. OD 2 1/4" x 2 1/4" x 2"



MC-385-B HEADSET IMPEDANCE ADAPTER

High to low impedance. Has PL-55 plug & socket for PL-55. For use with HS-33 or HS-38.

BRAND NEW . . . 19¢ ea.



TUBES

7C4 (1203A) . . . 39¢ ea.
VR92 49¢ ea.
CEQ-722A 69¢ ea.

(7C4 100 to carton)
ALL BRAND NEW ORIGINAL CARTONS



SHAKE PROOF WING TERMINALS

Solder lugs. Size #4
100 for 25¢
1000 for \$1.98



PL-64 PLUG for BC-375

BRAND NEW, 49¢



45' COIL ANTENNA WIRE

7 strand #22 weatherproof. BRAND NEW. 19¢ per coil.

• SATISFACTION GUARANTEED OR YOUR MONEY BACK
• HUNDREDS OF SURPLUS BARGAINS IN OUR FREE ILLUSTRATED LIST

DICK ROSE
2912 HEWITT AVE.

ERECO
EVERETT 20, WASH.

Finland—OIX2, 9.500, and OIX4, 15.19, have improved signals in 0715 news, latter still has QRM from Delhi. (Peddle, Newfoundland)

Formosa—XURA, 7.222, Taiwan, recently has not been carrying the XGOY (Chungking) news relay 0900. (Dilg, California)

France—"Ici Paris," 6.200, is heard in England with powerful signals around 0700, may be 100 kw. (Pearce)

French Equatorial Africa—Radio Brazzaville, 9.44, 11.972, has a short Mailbag session after the 1900 news period on Mondays. (Boice via Southall, Pa.) The 9.984, 17.84, and 6.024 outlets have not been heard lately. (Peddle, Newfoundland)

French Indo-China — Major, Western Australia, reports Radio France, 6.048, Hanoi, still using this frequency with news 0700, with musical theme of "Beer Barrel Polka." The Broadcaster, Western Australia, lists Radio France, 6.048, Hanoi, as operating 1900-2030, 2330-0115, and 0500-0930; Radio Cambodge, 6.035, Pnom-Penh, at 1900-2015, 0000-0115, 0600-0800.

French Morocco—CNR3, 16.666, Rabat, is heard in East around 0700-0845 sign-off. (Kary, Pa.)

Germany—Frankfurt, 6.190, is heard in England at 1715; no English; Radio Stuttgart, 6.180, is heard closing down at 1730 in German and English, sometimes giving weekly program schedule resume. (Pearce, England)

Baden-Baden, 6.320, is heard fairly well in New Zealand around 0200. (Clark)

AFN, 6.080, Frankfurt, is scheduled 0000-1800; sends nice QSL card. (Miers, Berlin)

Relays from the United States are carried by Munich III, 6.170, 1300-1400; Munich IV, 7.250, 1115-1215, 1415-1700; Munich II, 9.540, 1115-1700; Munich I, 11.870, 1115-1700, and Munich IV, 15.150, 1230-1400; all are beamed on East Europe.

Greece—"Edo Ethnikos Stathmos Tis Eleftheria Elathos" ("This is the National Station of Liberated Greece"), in Gen. Markos' territory, Communist, now runs 0100-0130 on 7.646. (Bouras, Michigan, via URDXC)

SVM, 9.935, often contacts New York at 1415, and around 1700-1930. (Beck, N.Y.)

Greenland—OZI, 5.942, Godthaab, is heard in Newfoundland with weak signal, bad CWQRM, at 1700-1745. (Peddle) Is heard in Sweden QSA-2-3, at 1645-1745. (Bergstrom)


Guatemala—TGWA, 9.76, and TGWB, 6.435, run to 0005 (in dual).

Haiti—According to a "temporary" verie received by Kary, Pa., from HHYM, operating at present on a "reduced" 6.000, Port-au-Prince, the transmitter is power of 500 watts; very soon they will be permanently installed and will have

RADIO NEWS

Now... at a sensationally
LOW PRICE!
 ECA QUALITY
FM & TELEVISION

Sweep Signal
GENERATOR
\$34⁹⁵
 COMPLETE

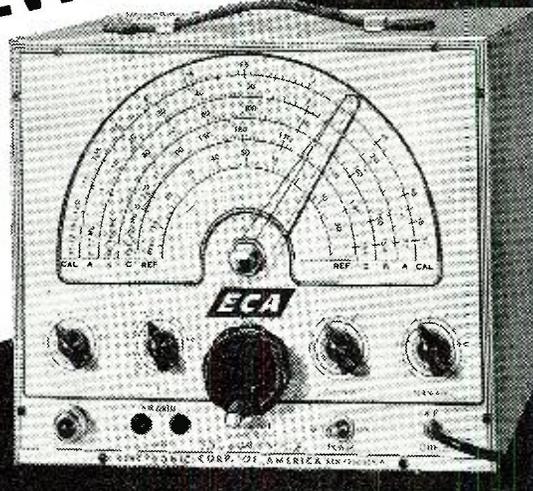

**A MUST
 FOR FM
 & TELEVISION
 SERVICE
 SHOPS!**

Here's great news for FM and TV Service Shops! A new, top quality sweep signal generator—product of a manufacturer with vast resources, advanced engineering "know-how", and war-time experience in producing test equipment. **DIRECT FROM THE FACTORY**—at a phenomenally low price!

FRONT PANEL CONTROLS

- Sweep width 500 KC to approx. 10 MC
- Phasing control
- Tuning vernier control 10 to 1 ratio
- Selecto switch FM—RF—CAL
- RF Output control
- 60 cycle horizontal sweep output
- Amphenol RF output shielded connector

FREQUENCY RANGE


- 3 BANDS**
 (No band switching necessary)
 (2 to 227 Megacycles)
- 2—77 MC
 - 40—154 MC
 - 151—227 MC
 - Calibration and reference scales
 - Dial scale length

TUBE LINEUP

- 6C4—Fixed frequency modulated oscillator
- 6C4—Continuously variable beat frequency oscillator
- 6C4—Mixer—Cathode follower output tube
- 5Y3—Rectifier tube

GENERAL INFORMATION

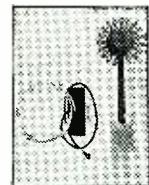- High frequency insulation throughout
- Maximum output 500,000 U/V
- Power required 105-125 Volt 50-60 AC 35 Watts
- Power line filter built in
- Special Midline capacity tuning condenser
- Pilot light line indicator
- Generator output can be used either frequency modulated or pure RF



RADIATION LOOP AND ALIGNMENT WAND

Provides loose coupling. Checks loop-oscillator tracking. Increases efficiency of receiver's alignment or mistracking. Enables the service engineer to make gain measurements. Professional appearance and appearance on any signal generator. Complete with operating instructions.

\$5⁹⁵


FM FRONTEND

Complete with 3 tubes, including Magic Eye. 88-108 MC.

For use with 10.7 MC I.F.S., high Q resonant tuned lines. Heavy silver overlay on lines and contacts. High frequency insulation throughout 1-RF stage, detector, and oscillator. Large 7" slide dial. Chassis floated, non-microphonic.



\$15⁹⁵

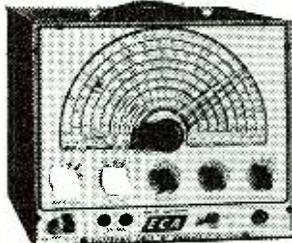

AM SIGNAL GENERATOR

8 RF bands. Frequency coverage 100KC-75 MC. External modulation from 40 to 30,000 cycles. Internal modulation at 440 cycles. Phase shift audio oscillator and internal modulator. A.C. 105 to 120 volts, 50 to 60 cycles. Special Hammarlund variable condenser, 3 step RF attenuator. Continuously variable RF-AT attenuator control. Ultra stable two terminal RF oscillator. Pilot light line indicator. Cathode follower output tube. Modulator percentage continuously variable from front panel, internal or external, 0 to 100%. Heavy 16-gauge steel cabinet. Complete with 4 (standard brand) tubes. Amphenol co-axial connecting cable, ground cable, operating instructions and guarantee.


\$32⁵⁰

Backed by ECA with R.M.A. Guarantee. For prompt delivery, rush your order today to Dept. RN-5. 20% deposit with order required. F. O. B. New York City.

Write for ECA circular on parts and additional equipment.

ELECTRONIC CORPORATION OF AMERICA
 353 WEST 48TH STREET • NEW YORK 19, N. Y. • PHONE: CIRCLE 6-1985

May, 1948

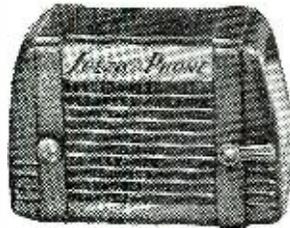

**SALE
 PRICE
 \$17⁵⁰**

**INTERCOMMUNICATION
 SYSTEM**




In the office, factory, store, farm or baby's nursery, immediate personal contact between any two points can be established with this system. It is efficient, dependable and economical. Small and compact. It requires little space, and is easy to install. This handsome black plastic 2-way system includes a Master and sub-station (calls may originate from either one), a 3-tube amplifier, 4" FM speaker, and 50 feet of cable. Operates on 105-125 volts AC-DC. Made to list for \$37.50, dealer special \$17.50 price, complete.....

\$17⁵⁰

5" P.M. SPEAKER

**WITH OUTPUT
 TRANSFORMER**

SPECIAL BUY!

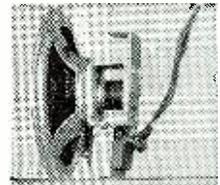

High quality 1.47 oz. permanent magnet speaker with output transformer that is ideal for replacement use.


Transformer primary matches a 50L6 and is tapped for filter. Mounting bracket on magnet frame is tapped for 8/32 screw for mounting to chassis. Stock up on these while they are available at these prices:

Stock No. E138

Price each \$1.59

Lots of 3 each . . 1.49

Lots of 100 ea. . . 1.35

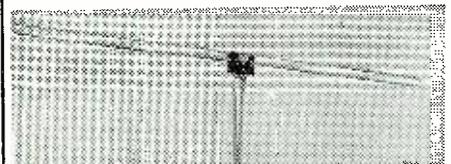

**VALUE PLUS! STROMBERG CARLSON
 FM FOLDED DIPOLE ANTENNA**

All FM receivers require an outside antenna for maximum efficiency and performance. Here, without a doubt is the best antenna buy on the market today. The folded dipole is adjustable as a half wave antenna by means of the movable "U" tube sections, and covers a frequency range from 88 MC to 106 MC. Each antenna is supplied with 60 feet of 300 ohm low loss transmission line. Mast is made of aluminum and is 5 feet in length. Universal mounting bracket permits attaching to any roof or wall angle.

#2036—Complete kit with Hardware and Installation Instructions

LIST PRICE \$15.00

SPECIAL! \$4.75

ELECTRONIC CORP. OF AMERICA, Dept. RN-5
 353 West 48th Street, New York 19, N. Y.

Gentlemen: Please send the following items. Enclosed find check (or money order) in full 20% deposit, balance COD.

- Send at once, your free catalogs, supplements and bargain lists as published.
- FM Sig. Generator.....\$34.95
- AM Sig. Generator..... 32.50
- Radiation Loop 5.95
- FM Front End 15.95
- 5" PM speaker \$1.59
- FM Dipole 4.75
- Intercom 17.50

Name.....
 Address.....
 City..... Zone..... State.....

Radio - Television - Electronic Parts & Equipment Specials

TELEVISION-CATHODE RAY HIGH VOLTAGE

2000 volt D.C. Power Supply

Why bother with bulky and dangerous 60 cycle supplies or expensive R.F. power supplies when you can purchase a complete 2000 volt D.C. unit (not a kit), ready to plug into the 110 volt A.C. power line. The ridiculously low price has been made possible by a fortunate purchase of high quality components. These units are brand new, completely tested and guaranteed. Price.....\$7.95

4000-6000 VOLT TELEVISION SUPPLY

Similar to the unit above, but has a much higher D.C. output voltage suitable for use with the new 7" and 10" television tubes. Price.....\$12.50

TELEVISION PICTURE TUBE

We have an exceptional buy in a 9-inch electromagnetic cathode-ray tube. The MW22-2 is an exact replacement for the nine inch tubes used in GE Television Receivers. This tube may be placed in practically any receiver designed for electromagnetic deflection. Price—Only.....\$13.95

A SCIENTIFICALLY DESIGNED PHONO SCRATCH FILTER

Resonated at approximately 4500 cycles effectively reducing objectionable needle scratch without altering the brilliancy of reproduction. Contains a HI-Q SERIES resonated circuit. Tested by means of an audio oscillator and an oscilloscope to give 22 db. attenuation with very low signal loss. Attenuation may be regulated by means of a SPECIAL MINIATURE gain control.

EASY TO ATTACH.

Just two wires to clip on. Compact.

Price.....\$1.65

TRANSTAT VOLTAGE REGULATORS

Manufactured by Amertran, three Models are available.

Model No. TH 21½ B

Fixed Winding 230/130, 60 cycles
Commutator range 0-260 Volts, .65 KVA.

Max. amp. 2½

Price \$19.95

Model No. 1244

Fixed Winding 115 Volts—60 cycles
Commutators range 103-126 Volts

Maximum output .25 KVA

Housed in shielded case 5" x 6" x 6"

Price 6.95

Type RH

Fixed Winding 115 Volts—400 cycles
Commutator range 75-120 Volts

Load — .72 KVA

Housed in Shielded case 5½" x 6" x 6½"

Price \$1.95

RELAYS

TIME DELAY RELAY

Thermal vacuum type

S. P. S. T. 100 ohm coil

24 Volts AC/DC

90 second delay.....Price \$ 9.95

RCA Vacuum Relay, Relay contacts will break 3000

volts and carry 10 amperes Solenoid resistance 2000

ohms. 25 volts DC—Excellent as R.F. antenna relay

.....Price \$ 9.95

Western Electric No. KS 10149 60 second Time Delay

Relay Cramer Motor 115 volts 60 cycles Switch

S.P.S.T. 15 amps.....Price \$4.95

Cramer 3 second Time Delay Relay No. 44844 Motor

120 volts 60 cycles Contacts S.P.D.T. 10 amps at

120 Volts A.C.....Price \$4.95

Weston Sensitrol Relay SR 2 No. 21120 Operates on

7 microamps.....Price \$3.95

Cramer Time Delay Relay No. 44SP3 N.L. Motor 115

Volts 60 cycles Two Poles Switch 115 Volts at

10 amps.....Price \$4.95

Relay S.P.S.T. WE Co. No. D163781 Coil with special

glass sealed switch. Whole unit encased in vacuum

tube shell which is filled with wax & attached to a

4 pin octal base. 2 pins term for coil; two for

switch, 2500 ohm 10 V.D.C. Operating current 4.3

ma, release current 2.5 ma. cont. rating 1 amp.

Price \$1.95

Relay Switchboard WE Co. No. D164816 3 windings.

Price \$2.95

PHOTOTUBE

GE PJ23 Gas type—very sensitive especially in infrared region.....Priced for quick sale \$2.95

WRITE FOR LATEST CATALOGUE

EDLIE ELECTRONICS, INC.
131 LIBERTY STREET
NEW YORK 6, NEW YORK

a definite schedule of operations, and will send out QSL cards.

Hawaii—KRHO, Honolulu, relaying U. S. programs, is scheduled on 15.250, 0400-1005, and on 17.800 (UN programs), 0230-0345, beamed to Philippines and China.

Iceland—Although TFJ, 12.235, Reykjavik, is scheduled Sundays (only) at 1115-1145 with news in Icelandic and music for Icelanders abroad, it has not been reported to me as having been heard in America.

Italy—Radio Italiana appears to be using 9.63 and 11.81 for the North American beam around 1915-2010, news 1950. (Dunham, North Carolina) An English period is also scheduled 1445-1500 on 9.63, 6.085. (Pearce, England)

Java—Major, Western Australia, lists YDH2, 11.030, Semarang, good at 0600, heard signing off 0630, but heard later back on the air; "have seen this listed as Borneo, but Semarang is in Java."

Radio Batavia's daily 0930-1000 transmission to the U. S. and Canada is now radiated on a new (announced) frequency of 8.916, replacing 11.440, but appears to be much lower, around 8.900 to 8.910. (Stark, Texas, and Dilg, California) The 15.145 outlet, used in parallel to Australia, Malaya, is heard well here in West Virginia but I have not yet found the new (8.916) channel audible. Call-sign of the new outlet is PLA8. (Stark, Texas)

Dilg, California, reports improvement in signals from Java—Bandoeng, 10.062 Sunday (which is not regular schedule); and 7.997, recently were heard on a some days 10.062 appears to be used all morning for phone traffic; Batavia's 10.365 at times is good to 1030 sign-off; 25.-m. outlets have been weak usually on West Coast.

Dorothy Sanderson, Australia, lists Sourabaya on 8.12, heard at 0630 with musical program and announcements in Dutch.

"The Voice of Indonesia," 11.000, is heard in Texas with new 0630. (Stark)

Korea—The Seoul outlets of HLKA, 2.510 and 7.933 (used in parallel), although scheduled to sign-off around 0835, recently have been heard in California as late as 0905. (Dilg) In verifying for Kary, Pa., Howell S. Teeple, Advisor, Radio Bureau, Dept. of Public Information, Seoul, said transmitter is a 5-kw. Japanese Electric; antenna is a half-wave doublet; schedules are listed 2100-0000, 0330-0830, 1630-1830; Kary's was first report received from the U. S.; it was stated that this station is a key network station for a series of 10 stations located throughout south Korea, necessary for relaying programs due to a lack of telephone lines in that country. Station is operated by Koreans under the supervision of Americans; frequency on verie was listed 7.935, but has been measured in East as 7.933.

Lebanon—News of Syria (in English) is read by a woman at 1100 from Radio Beirut, approximately 8.017 (listed 8.020V). (Radio Week, South Africa) Is heard in Newfoundland 0000-0100, 1345-1600. (Peddle) Some days runs to 1630.

Luxembourg—Radio Luxembourg's 15.35 channel, formerly heard in East around 0700-0830, has not been reported as heard lately.

The 6.090 outlet is heard in Newfoundland at 1415-1445. (Peddle)

Madagascar—Radio Tananarive, 10.615 and 6.065, is heard in Newfoundland at 1330-1400 sign-off (closes with "La Marseillaise"); has symphonic music at 1330-1345, followed by world news in French; the 9.695 channel (scheduled in parallel) is not audible. (Peddle)

Malaya—Major, Western Australia, says "Radio Malaya," 4.825, Singapore, is good level at 0930, signs off 1030.

According to a letter received by Kary, Pa., from the British Far Eastern Broadcasting Service, Singapore, hours of broadcasting have been greatly curtailed for the present and most programs are now relayed from the BBC's Far Eastern, Eastern, or General Overseas Service; schedule was given as 6.77, 0400-1135; 9.69, 0530-1135; 11.73, 0400-1135; 15.30, 0400-1135; 21.720, 0400-0530; all were listed 7½ kw. except 21.72 which uses only 5½ kw.; news headlines 0400, news 0450, news 0645 (news, talk, English lesson), news 0915, news 1100. Both Purple and Orange Networks have been discontinued, and about 60 per-cent of the personnel has been dismissed, the letter stated.

The 9.690 outlet is heard in California signing off daily 1130. (Dilg) Is audible but weak here in East to around 1030 or later. The 21.720 outlet has been heard in England from 0400 sign-on, news 0403 and 0450, then Eastern session from 0500-0530 sign-off. (Pearce)

Mexico—XEEP, 6.155, "Radio Education," Mexico City, is heard in New York evenings with fair signal, much classical music. (Legge)

Monaco—Prendergast, New York, reports Radio Monte Carlo, listed 6.132, has been heard at 1645-1715 sign-off, announcing return at 0100; uses French.

Mozambique—CR7BJ, 9.645, Lourenco Marques, is heard in Newfoundland as late as 1525; "always has excellent signal." (Peddle)

Norway—Norsk Rikskringkasting (Norwegian State Broadcasting), Oslo, informs Stanley Worris, Florida, that due to rationing of electricity (caused by an exceptionally dry summer last year), they have not had an opportunity to expand transmission times as they would have liked. They add, "Our transmitter is located in southern Norway at Fredrikstad at the east side of the Oslo Fiord, and the antenna is directed East-West from that city. This particular short-wave service for Norwegians

RADIO NEWS

abroad takes place each night between 0100-0200 GMT (2000-2100 EST). That is the only time of the day when our 100 kw. transmitter operates on 9.610, and 11.850 and 6.185 (8 kw. each) are in parallel for the 2000-2100 EST transmission; the latter two are beamed South and West and North and West, respectively.) The letter mentioned a broadcast in Norwegian at 0130-0230 on 11.735.

Is heard on 11.735 and 9.610 occasionally in New York around 0200. (Beck) The 9.610 channel is heard irregularly on West Coast around 0145-0230 (off Sundays), news in Norwegian 0200. (Balbi, California)

The 6.185 outlet has been heard in England signing off around 1724, after news in Norwegian. (Pearce)

Pakistan—According to Radio Times of India, headquarters of the Pakistan Broadcasting Service are reported to have decided to move to Karachi from Lahore. Future plans include a 100-kw. short-wave station and a 5-kw. medium-wave station for Karachi; a 20-kw. short-wave station for Dacca; and a 5-kw. medium-wave station for Hyderabad. Karachi should be on the air on s.w. by this time. (*Your ISW Editor would appreciate details on operations of Pakistan Radio as they are available.*—K.R.B.)


Palesine—According to overseas publications, JCKW, Jerusalem, has left the air. (Southall, Pa.) Not reported as heard lately.

Paul Kary, Pa., recently received a letter from the Chief Engineer, Near East Arab Broadcasting Station (Jaffa) stating that "the old British Mediterranean Station was a wartime station set up by the Military Authorities for propaganda and was disbanded with the termination of hostilities. I was Chief Engineer of this station at that time and eventually secured employment with the Near East Arab Broadcasting Station. There is, of course, no connection between the two stations, but with the disbandment of the old S.M.S., I was able to 'snaffle' some of its frequencies and equipment for use with my new employers . . . Present station is Arab-operated, using two RCA-4750 transmitters and two station-made 7½-kw. transmitters. I am also using a 2-kw. Airaco transmitter for test purposes on 3.320 and your reception report on the frequency is particularly interesting because I am using with it a vertical aerial of experimental design. Your reports on other Middle East stations are also very interesting and I would appreciate further information you can give on such transmissions."


Panama—HP5A, 11.695, Panama City, has English session at 1615-1715 Sundays; verie still gives frequency as 11.700. (Segal, via URDXC)

May, 1948

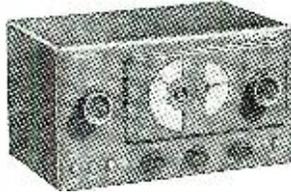make henry your hallicrafters headquarters



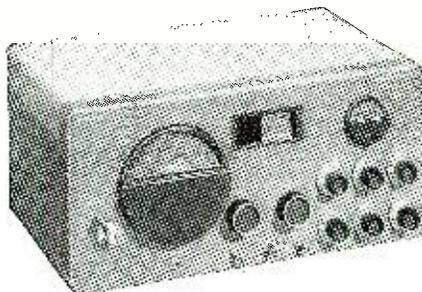S-38 Biggest little buy on the market. Frequency range: 540 kc to 32 Mc in 4 bands. Self-contained PM dynamic speaker. **\$47.50**



SX-43 All essential ham frequencies from 540 kc to 108 Mc. In the band of 44 to 55 Mc, wide band FM or narrow band AM, just right for narrow band FM reception is provided. **\$169.50**

COMPLETE STOCKS . . . Henry has everything in the ham field.

QUICK DELIVERY . . . Shipments 4 hours after receipt of order.

EASY TERMS . . . I have the World's Best Terms because I finance the terms myself and cooperate with you. I save you time and money. Write for details.

TEN DAY FREE TRIAL . . . Try any receiver ten days. Return it for full refund if not satisfied.

FREE NINETY DAY SERVICE . . . I service everything I sell free for 90 days. At a reasonable price after 90 days.

TRADE-INS . . . Trade-ins solicited. Big allowances made. Other jobbers say we allow too much. Write, wire, or phone. Tell me what you want and what you have to trade.

BUTLER MISSOURI **HENRY RADIO STORES** 11240 Olympic Blvd. LOS ANGELES 25 CALIF.
"World's Largest Distributor of Short Wave Receivers"

Permoflux SPEAKERS

YOUR JOBBER CAN SUPPLY YOU!

Permoflux quality and dependability—the same as supplied to the major set manufacturers—is your assurance of complete customer satisfaction. You'll find Permoflux Speakers easy to install and readily available in both PM and Electrodynamic types. You'll find too, that it pays to give your customers "tops n tone" with a Permoflux Replacement Speaker.

TWO COMPLETE FACTORIES TO SERVE YOU **PERMOFLUX** WRITE FOR FREE BULLETIN
PIONEER MANUFACTURERS OF PERMANENT MAGNET DYNAMIC TRANSDUCERS

PERMOFLUX CORPORATION
4900 WEST GRAND AVE., CHICAGO 39, ILLINOIS
236 SOUTH VERDUGO ROAD, GLENDALE 5, CALIFORNIA

TUBES! TUBES! TUBES! THOUSANDS OF TUBES LOWEST PRICES!

(NEW, STANDARD BRANDS—DEALERS PRICES ON REQUEST—MINIMUM ORDER \$5.00)

TYPE	PRICE	TYPE	PRICE	TYPE	PRICE	TYPE	PRICE	TYPE	PRICE	TYPE	PRICE		
1A3	.96	5Z4	.89	6SF5	.79	14A7	1.10	100TH	12.95	832A	2.25	8020	5.05
1A5	.49	6A6	.75	6SG7	.75	14B7	1.10	100TS	3.00	833A	39.50	841	.69
1A7GT	1.10	6AB7	1.25	6SH7	.39	14H7	1.25	117L7	1.89	836	1.15	843	1.50
1R24	2.49	6AC7	.99	6SJ7GT	.69	14F7	1.25	117Z7	.89	837	3.75	8025	2.45
1R38	4.50	6AG5	.99	6SK7	.79	15E	1.50	117Z6GT	1.10	838	3.75	9001	.89
1R4	.99	6AG7	.99	6SL7	.89	25D4	.49	121A	2.65	845	3.75	9002	.49
1G5	.44	6AK5	.99	6SN7GT	.69	25D6	.49	205B	4.50	860	3.00	9003	.49
1G6	.98	6AL5	.99	6S07	.99	25E6	.49	215A	3.00	866A	.75	9005	.49
1H4G	.98	6AQ5	.99	6SR7	.80	25L6GT	.75	217G	17.50	872A	1.85	9006	.49
1L4	.89	6AT6	.75	6S7	.75	25Z5	.75	304TH	2.49	874	1.85	9007	.79
1R4/1294	1.29	6AU6	.89	6S87	.75	25Z6	.99	307A	6.25	884	.49	HV75	3.95
1T4	.59	6B4	1.29	6S87	.75	25Z7	.99	316	.89	923	.75	HV615	1.25
1H5	.99	6B6G	.89	6S87	.75	25Z8	.99	371A	1.39	954	.49	OZ4	1.25
1N3GT	1.10	6B8	3.49	6V8GT	.75	35L6GT	.75	371B	3.00	955	.49	RK60	.79
1L5	1.82	6C4	.64	6V6G	.89	30	.78	381A	4.50	956	.75	RK72	5.50
1R5	1.10	6C4	.64	6X4	.98	32L7	1.50	384A	4.50	957	.49	T40	1.95
1S5	1.85	6C5	.81	6X5	.89	34	.58	417A	1.95	957	.49	V700	6.95
2A3	1.39	6C6	.79	7AE7	.75	35L6GT	.75	446A	4.25	958A	.49	VR75	.45
2C22	.89	6C21	12.95	7B7	.69	35Y4	.69	450TH	17.50	959	.49	VR78	.75
2C26A	.75	6D4	.99	7C4	1.50	35W4	.69	705A	1.85	1005	.39	VR90	.75
2D34	2.60	6D6	.75	7C4	.75	35Z3	.89	705A	1.85	1006	.39	V8105	.75
2D44	1.75	6F6	.79	7F7	1.25	35Z5	.89	715A	4.95	1006	.39	V8150	1.69
2D71	.75	6F6G	.80	7F7	.89	36	.69	715B	4.95	1013	.95	Z35	1.95
2E22	1.50	6F7	.96	7L7GT	1.39	37	.89	723A/B	5.50	1016	1.59	Z40	2.25
2E25	3.95	6F8	1.10	10Y	.69	37	.69	725A	12.50	1019	.98	ZAP1	2.25
2F30	2.25	6G6	1.10	12A6	.89	38	.89	800	2.25	1022	1.75	ZAP1	1.95
2B32	20.00	6H6	.49	12AH7	1.10	39/44	1.10	801	1.10	1024	.98	ZBP1	1.89
2B33	20.00	6H6	.49	12A7	1.10	41	.89	804	1.10	1024	.98	ZBP1	2.49
2JB51	4.95	6J4	1.50	12A7	1.10	41	.89	804	1.10	1024	.98	ZBP1	1.49
2K2	.89	6J5	.49	12BA6	.89	45	.89	804	1.10	1024	.98	ZBP1	1.49
3A1	.49	6J6	.49	12BE6	.89	47	.90	803	8.95	1025	.49	ZBP1	1.49
3B7	.99	6J7	.89	12C8	.89	50B5	.89	804	6.75	1026	.49	ZBP1	1.49
3B22	4.95	6J7	.89	12H6	.44	50L6GT	.75	805	3.75	1029	.99	ZBP4	4.95
3B24	.98	6K6	.59	12J5	.69	70L7	.89	807	1.25	1031	1.49	ZCP1	3.95
3D6/1299	.99	6K7	1.25	12K8	1.25	71A	.69	808	2.95	1041/RK60	.79	ZP7	4.50
3E29	2.99	6K8	1.25	12SA7GT	.99	75	.69	809	1.95	1051	1.23	ZP4	11.95
3G4	1.10	6L6	1.20	12SH7	.89	75T	2.39	811	1.95	2050	.99	ZP4	17.95
3G5GT	.59	6L6G	.98	12SH7	.89	77	.75	812	3.00	2051	.49	ZP4	19.40
3S4	.45	6L7	.89	12S7	.79	78	.75	812H	6.90	5514	3.95	10CP4A	42.20
4E27/257B	4.95	6L7	.89	12SK7	.69	79	1.10	813	5.95	7193	.39	10BP4	37.50
4R4GY	1.15	6N7	.89	12SL7	1.10	80	.53	814	4.39	8001	4.95	10FP4	42.20
6T4	1.25	6Q5	.98	12SN7GT	.79	82	.96	815	2.25	8005	3.25	10HP4	electro-
6AB7	1.25	6Q5G	.98	12S07GT	.99	83V	.89	828	1.75	8011	2.95	static	
5U4	.44	6Q7	.89	12SR7	.79	84	.75	829A/B	2.95	8012	4.95	Tube	49.50
5V4G	.98	6R7	.98	12X3	.98	85	.89	830B	5.25	8016	1.95	12P4	60.00
5W4	.98	6SA7	.90									15AP4	110.00
5Y3	.60	6SC7	.85									20AP4	270.00
5Y4G	.49												
5Z3	.89												

20% DEPOSIT WITH ALL ORDERS UNLESS RATED

NIAGARA RADIO SUPPLY CORP.

160 GREENWICH STREET
NEW YORK 6, N. Y.

Front row center!
With the new
**UNIVERSITY
TWEETER**




FOR FULL RANGE
REPRODUCTION UP TO
15,000 CYCLES

Tambores and triangles—cymbals and snare drums—castanets and clarinets—these are a few of the elusive instruments the tweeter brings you with concert hall quality and brilliance. Connect it to any good cone speaker and hear every frequency—all the over-tones—right to the top of the audible spectrum. Listen to one at your nearest distributor. Three inexpensive models available—a cabinet type and single or dual mounted units. List prices from \$20.00. Write UNIVERSITY LOUDSPEAKERS, INC., 80 South Kensico Ave., White Plains, New York.

University Loudspeakers

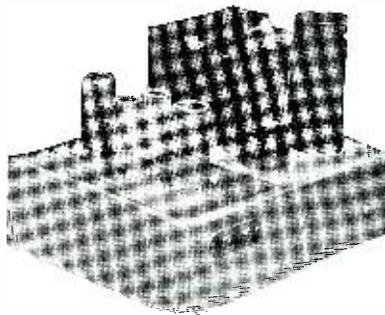Move That Television Station
30 Miles Closer! With a
Magic View Preampfier



Here's the preampfier you need to put "fringe" installations into the service area of your favorite TV station. Designed to obtain the last ounce of signal-to-noise ratio out of any single channel, this amplifier uses the newest 9 pin miniatures for maximum gain in a push-pull grounded grid circuit.

By concentration on one channel per preamp, all losses due to tuning or switching are avoided, a high LC ratio is maintained and remarkable gains (20 times on the high band, 30 times on the low band) are achieved.

Besides gain, the preselection gives freedom from local interference, such as FM, amateur, and short-wave, which cannot be approached by the best commercial receivers alone.

Installation requires a screwdriver and 117 volts a.c. to operate the self-contained power supply.

Write, wire, or phone your order, stating what channels you need (2 to 13 inclusive) and watch that television signal move in!

PRICE \$49.50 complete with tubes.

Catalog on television kits and components mailed free upon request.

TELEVISION SPECIALTIES CORP.

315 Madison Street Oak Park, Illinois
Phone: Village 5830

Philippines—KZFM has been heard in Texas on 11.840, announcing as "The People's Station" in Manila, poor signal and erratic, heard as late as 1000. (Star, Texas) Also reported by Dilg, California. Radio Australia has announced 6.170 is in parallel, but this has not been confirmed.

The Manila relay of "Voice of America" is scheduled on 11.890, 0400-1005, to Far East, and on 15.330, 0230-0345, to India and Pakistan (UN programs).

Poland—Warsaw schedules on 48.25 (approx. 6.215) are currently listed 1030-1900, with news at 1530-1550. (May be an hour earlier during summer.)

Portuguese Guinea—CQM-4, Radio Bissau, 7.947, has a fine signal in East 1630-1800, signing off with Portuguese National Anthem. (Southall, Pa.) Radio Bissau was scheduled to test on 16.667 at 0700-0800 on February 26, but was not reported to me as heard in America.

South Africa—SABC identifies in English and Afrikaans at beginning and end of all transmissions, says Mervyn P. Laubscher, our ISW monitor in South Africa, who sends these late schedules for SABC:

Johannesburg No. 4, 1 kw., 4.800, weekdays 2345-0130, 0900-1605, Sundays 0050-0110, 0945-1605, news 0000 (except Sun.), 0100 (BBC); runs to 1645 Sat. Johannesburg No. 4, 1 kw., 9.870, weekdays 0315-0710, Sundays 0313-0930, news 0615; on Tue., Thur., Sat. comes on 0245 with programs for Africans. Johannesburg No. 5, 200 w., 4.373, weekdays 2345-0130, 0315-0710, 0900-1605, Sundays 0055-0110, 0315-1605, news 0000 (except Sun.), 0100 (BBC), 0615, 1100 (BBC), 1200 (except Sun.), 1500; runs to 1645 Sat.; Tue., Thur., Sat. comes on 0245 with program for Africans. (This group normally carries programs in English.)

Johannesburg No. 3, 5 kw., 4.895, daily 1200-1605; news 1200 (except Sun.); runs to 1645 Sat. Johannesburg No. 3, 5 kw., 6.007, weekdays 2345-0130, Sundays 0055-0110, news 0100 (BBC). Johannesburg No. 3, 5 kw., 9.523, weekdays 0315-0710, 0900-1145, Sundays 0315-1145; news 0615; Tue., Thur., Sat. comes on 0245 with program for Africans. (This group normally carries programs in Afrikaans.)

Cape Town No. 3, 5.880, weekdays 2345-0130, 1200-1605, Sundays 0055-0110, 1200-1605, news 0100 (BBC); Sat. runs to 1645. Cape Town No. 3, 9.610, weekdays 0315-0710, 0900-1145, Sundays 0315-1145, news 0615. (These stations normally carry programs in Afrikaans—but the 9.610 outlet has English programs Wed. at 1320-1500.) Power is 5 kw. each.

Pietermaritzburg No. 2, 200 watts, 4.878, weekdays 2345-0130, 0315-0710, 0900-1605, Sun. 0055-0110, 0315-1605; news 0100 (BBC), 0615, 1200 (except Sun. when has news 1500); (normally

new! KITS - PARTS & ACCESSORIES

LOWEST prices in U.S.A.



RADAR ANTENNA
 Makes Excellent Mechanism For Rotary-Beam Antennas
 • Has 2 husky motors for azimuth & tilt variations—easily converted for 110v AC operation. Pair of precision potentiometers included for direction indicators. BRAND NEW—in original cases. An amazing bargain! . . . ONLY \$34.50 ea. (Conversion instructions included).



S-C-O-O-P — S-C-O-O-P!
 New EIMAC VT-127-A.

Hard-Pumped. Will handle up to 15,000 Plate Volts.
 1,000 Watts Input on 6-Meters with a pair of these BRAND NEW Eimac triodes. (Similar to 100-TH, but heavier filament). Fil: 5v at 10a. Platinum grid. Surplus price, \$2.45 ea., or 4 for \$8.40. Filament Connector Blocks (brass) 25c pr.



25-WATT P-A SPEAKER


Get Ready for the Election Conventions

• Heavy-duty Jensen driver unit and UTC line-matching xfmr. 250, 500, 1000 and 2500 ohms, 20" lonx. 13" diam. Re-rant type. Greatest P-A speaker value ever offered. BRAND NEW. \$21.60 net. Standard Crate of 2 Speakers \$40.85 (Only a few left).



MAGIC-EYE KIT

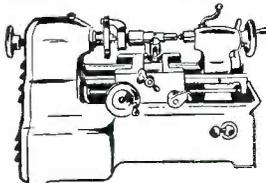
• This Zenith kit contains one 6D5 tube, socket, cord, 4-prong plug, (fits standard 6-prong socket) and tube shield-cone. Brand New. SACRIFICE PRICE. .98c ea. net.



OVER 30% REDUCTION ON SMALL LATHE

• Regular price \$60.75. Our special price, \$31.50, to liquidate overstock due to cancellation of export order. A precision machine, 110v AC operation, with MOTOR and cooling fan. Automatic feed. Work capacity 3" between centers. Swing over bed 3". Price includes face plate, 2 lathe centers, tool post and rocker, and one do. BRAND NEW. IN ORIGINAL FACTORY CARTONS \$41.50 net!
 • Complete ACCESSORY KIT, including 4-jaw chuck, drill chuck, center countersink drill, 2 tool-bits, 2 lathe dogs, 1 face plate with 8 drilled and tapped holes, 4 collets, 1 collet chuck, 1 Allen wrench. FORMER PRICE \$36.25. NEW LOW PRICE ONLY \$24.50.

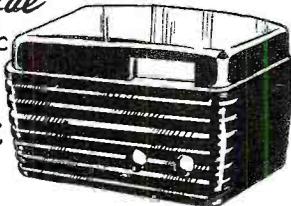Beautiful MODERNISTIC BAKELITE CABINET 98¢



• With each order for \$10.00 worth of merchandise advertised on this page, you can buy one of these beautiful bakelite cabinets for only 98¢ additional. Ideal for receivers, intercomms, test equipment, control units, etc. (List price of cabinet \$7.50).

BUILD your own Save \$



5 tube SUPER-HET kit

\$14.95 WITH TUBES & CABINET


• De-Luxe Superhet KIT, including everything—tubes, speaker, \$7.50 value cabinet, loop antenna, dial, and ALL brand new, finest best-known parts. Standard circuit. A-V-C. 5-Tubes. Complete wiring diagrams with each kit. Nothing else to buy, \$14.95. SPECIAL—4-Tube TRF Kit, fits same cabinet. . . . \$11.85 (with \$7.50 cabinet!)



POWER SUPPLY FOR ANY 274-N RECEIVER


Here it is—at last! Just plug it into the rear of your 274-N RECEIVER, in any model! Complete kit, and black metal case, with ALL parts and diagrams. Simple and easy to build in a jiffy. Designed especially for the 274-N receiver! (Resistance-filter KIT \$6.95) Standard model has choke filter. . . . \$7.95

CONDENSER TESTER

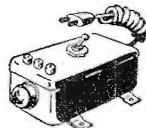

• One of our best sellers! Useful, versatile laboratory item in kit form. Simple and easy to build in less than an hour. Checks condenser leakage and continuity up to 8-megs. Will test any paper, electrolytic, mica or oil condenser from 50-mfd. to 50-mfd. Self-contained power supply and neon bulb indicator with socket and bezel. Drilled Metal Cabinet. Complete instructions and diagrams included with each kit. ONLY \$4.85

400-V. 200-MA. POWER SUPPLY

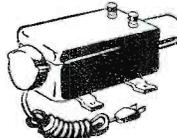

• Fits in palm of your hand. Complete power-supply KIT, with 3 selenium rectifiers, and ALL parts, finest best-known brands, and 160-mfd. in condensers. Voltage-tripler circuit. Delivers 300-v under full load. Drilled metal shield can. All diagrams and instructions included. BRAND NEW . . . \$8.85

TREMENDOUS SAVINGS ON BRAND NEW JENNINGS VACUUM CAPACITORS



• NOT war surplus, but STANDARD, new items of which an overstock is on hand. Must be sold quickly at lowest prices ever offered!

Type	Regular Price	Your Price
VC-6	\$ 9.65	\$ 2.80
VC-12	11.80	3.50
VC-50	16.09	4.50
VC-100	25.74	7.65
VC-150	36.83	11.60
VC-200	48.46	14.60
VC-250	57.92	17.30


All In Original Factory Cartons. ALL GUARANTEED UNCONDITIONALLY!!

COMPONENT KITS

• Standard Cartons of Finest, nationally-known brands. Stock-up now at these all-time low prices. Limited quantities. First come, first served!



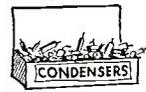Resistors
 • 100 most practical sizes and values, 1/2, 1 & 2-watts, 50 ohms to 8 megs. Allen-Bradley, ITC. Continental, etc. Every one BRAND NEW, perfect in every respect. This is truly a GREAT BUY. Kit of 100 for ONLY \$1.95



Condensers
 100 of the finest C-D Aerotox and Solar capacitors, all 600 working-volt sizes. ALL BRAND NEW. Assortment includes .01, .02, .05 and .1-mfd. sizes. Imagine it—the entire lot for only \$6.90.



Tie-Pins
 Another mighty useful kit of assorted tie-pin connectors, various sizes and types. Excellent assortment of dozens of 1, 2, 4 and multi-lug types. NOT SURPLUS, but brand-new products . . . at new low price of only \$1.00.



Relays
 • A box-full of perfect, guaranteed 12-volt and 24-volt relays of various types and sizes. (sixteen assorted types) offered to you for the worth of the silver contacts alone. Every relay is a standard product. NO OFF-BRANDS. A \$50.00 assortment for ONLY \$4.95 net. Only a few on hand.


KITS - KITS - KITS - KITS

Just Released—New Kits of Many Kinds

40-Meter Beginners' C-W Transmitter Kit. 150-WATTS
 • Beautiful, brand-new kit, consisting of TU-10B unit in black metal case, 1 type-211 tube, 1 type-807, 1 50-watt socket, 3 variable condensers, 3 resistors, and ALL essential components. Everything complete, less power supply. Wiring diagrams and instructions in detail for adapting TU-10B Tuning Unit as 40-Meter Xmr. ONLY \$9.85, WITH TUBES! What a Buy!

INSTANT-ACTION INTERCOM KIT!!
 • New, instant-acting tubes (operate only when talking) enable you to build a PAIR of the BEST intercom stations, EASILY and QUICKLY. Complete kit of EVERYTHING, all finest, NEW parts, wiring diagrams, instructions. 1L1S two beautiful \$7.50 value ea. bakelite cabinets, as shown at 100 center of this page. ALL FOR ONLY \$27.54 PER PAIR, including RECTIFIER POWER UNITS, tubes, etc., etc. ELECTRIC SHAVER KIT

• Speed-up your shaver. Use D-C! Use our new, inexpensive Rectifier Kit, especially designed for this purpose. Complete kit with selenium rectifier, filters, cords, switch, socket, condensers and shielded case. EVERYTHING FOR ONLY \$3.26 net. Diagrams included. New D-C Filament Supply KIT. ELIMINATES 60-Cycle Hum & Hum-Modulation! Operate amplifier tubes, etc. from DC. Eliminate Hum! Improve quality of high-gain amplifiers, etc. DC Fil. Supply kit with selenium rectifier, condensers, resistors, switch, cord, etc. and WIRING DIAGRAMS. 150-ma Kit for 12-v. Fil. Tubes. . . . \$2.67 net 300-ma. Kit for 6.3v. Fil. Tubes. . . . \$3.80 net

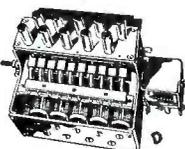

PUSH-BUTTON TUNING UNIT

• Has 10 push-button keys, 10 variable condensers, (100µf), padders, etc. BRAND NEW. Sold for one-third the value of condensers alone . . . \$1.95 net.



B-C 211 Pwr. Unit

Selenium rect., fil. xfmr. and all other parts, including case, wiring diagrams, etc. COMPLETE \$5.85 net.

FREE CATALOG No. 86
 READY NOW
 write FOR YOUR COPY

SEND 25% DEPOSIT WITH ALL ORDERS. BALANCE C.O.D.

OFFENBACH & REIMUS CO.

372 Ellis Street

San Francisco 2, California

Tel. — ORdway 3-8551

The **ONLY** POWER SUPPLY

That gives these ratings* without overheating

Electro
BATTERY AND RADIO EQUIPMENT

MODEL "A"

- *6V at 15 amps. in parallel
- *12V at 7½ amps. in series
- *6V at 7½ amps. separately

Operates auto radios with solenoid tuning and tone controls—also 12 volt marine and aircraft radios from 115v., 60 cycle supply.


Oversize transformers, chokes and rectifiers insure against overheating. Large capacity condensers for wide-range voltage regulation. Instantaneous power for solenoid operation. Two separately filtered DC output sources.

Compact. Sturdy. 18-gauge steel construction. Handsome blue Hammerloid finish. Comes completely equipped including 6' rubber cord and plug. Vastly superior and costs no more than batteries for equal service.

Send for complete description of this up-to-the-minute power supply.

ELECTRO PRODUCTS LABORATORIES

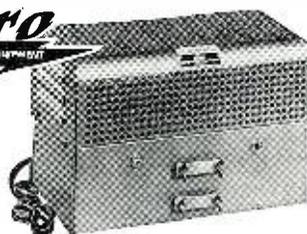Pioneer Manufacturers of Battery Eliminators
549 WEST RANDOLPH STREET CHICAGO 6, ILLINOIS



Height: 7¼". Length: 11¼".
Width: 7¼". Ship. wt.: 31 lbs.

DC OUTPUT

ATTENTION!

Manufacturers Reps

and

Distributors

If you are interested in the finest line of centralized, portable and base type amplifier systems, recording and intercommunication equipment, see our display and meet the sales engineers at

The Congress Hotel,
May 11, 12 and 13.

Some territories still
available

WESTERN SOUND AND ELECTRIC LABS., INC.

805 S. 5th Street

MILWAUKEE 4, WISCONSIN

WANTED!

Articles by Radio Amateurs

2000 to 2500 words

Covering any material of genuine interest to radio amateurs, such as:

- Transmitters
- Receivers
- Antennas
- Test Equipment

Articles should be typewritten (double spaced) and accompanied by suitable diagrams, photos, and parts lists. Liberal payment will be made upon acceptance.

Address all communications to
Box 419

RADIO NEWS

185 North Wabash Avenue
Chicago 1, Illinois

carries programs in Afrikaans, but carries *English* programs weekdays from 1500, Sundays from 1300); runs to 1645 Sat.; Zulu session daily 0245; Indian session on Sun. at 0215 prior to Zulu period. Transmitter is located at Pietermaritzburg, but all programs originate in the Durban studios.

Mr. Laubscher adds that call-signs have not as yet been allocated to SABC.

ZRB, 9.110, Pretoria, is reported heard irregularly in East around 0000; appears to open at 2345, relaying SABC. (Kary, Pa.) Heard in Ohio at 0100-0130. (Sutton) Also heard on West Coast. (Dilg, Baxter) And in Texas. (Stark)

Spanish Morocco—Radio Tetuan, 6.067, is scheduled 0230-0330 (except Sunday); Spanish first half hour, Arabic second half. (Beck, N.Y.) Heard in Newfoundland signing on 1600. (Peddle)

Sumatra—Major, Western Australia, lists a Sumatran station on 7.220, heard with good level at 0730. Radio World, Australia, says location of the Indonesian heard around 0630 (presumably on about 7.220) is Fort de Kock, East Coast of Sumatra.

Surinam—Arthur, W. Va., notes that recently PZH5, Paramaribo, has been using 5.757, replacing 5.843, and paralleling 15.402. Latter is listed 15.405 by the station but is actually lower.

Station lists schedule Mon.-Sat. 0930-1100, 1700-2200, Sundays 0930-1300, 1700-2200. (Southall, Pa.) (It is possible these listings are *not* EST, in which case *subtract* a half-hour.—K.R.B.)

Sweden—Arthur, W. Va., reports SDT2, 15.665, Motala, has been heard lately with news pickups, probably around 1800-1930.

Switzerland—The "mystery" station on 6.345 is the International Red Cross, Geneva; scheduled Wednesdays 0145-0230 in German to Austria; 0230-0300 tests in French, *English*, German; also daily 1245-1445, presumably on same frequency. (Beck, N.Y.) Has been heard well in New Zealand, asking for reports. (Clark) Has been heard in Northwest. (Park, British Columbia, Canada)

Syria—Damascus is building three new powerful s.w. transmitters. (Pearce, England) Schedules are listed as 0000-0100, 0700-0800, 1100-1500. The 12.000 (approx.) outlet is heard in Newfoundland at 1215-1445. (Peddle) Reported heard in Eastern U. S. around 0000-0100.

Tangier Zone—Radio Internationale, 6.200, has *English* at 1500-1530. (Peddle, Newfoundland)

U. S. A.—The World Wide Broadcasting Foundation (WRUL), Boston, Mass., recently announced power would be increased to 250 kw. (Southall, Pa.)

U. S. S. R.—Moscow's North American morning transmission, 0745-0815, is being radiated on 6.11, 7.26, 9.54, 9.57, 11.72, 15.17, 17.77. (Southall, Pa.)

Vatican—HVJ has not been heard lately on West Coast at 1000 when formerly carried news. (Dilg) The 15.095 outlet has news at that time, has been signing off at 1015. (By now this transmission is likely heard one hour earlier for the summer.—K.R.B.)

Yugoslavia—Radio Belgrade, 6.107, is heard in Newfoundland with news 1530-1545. (Peddle) Also has news at 1230; French news 0745, 1430; German news 1445; Spanish news 1615. (Hansson, Sweden)

* * *

Last Minute Tips

Radio Espana Independiente, believed located somewhere in the Soviet Union, is heard in Newfoundland, with poor modulation, in Spanish at 1230-1245 on 13.65 at 1330-1345 on 8.76, and at 1530-1545 on 9.255. (Peddle)

In a second letter to Kary, Pa., Director Fu Hwa Hau, of XMPA, Nanking, reaffirmed that he is quite anxious to receive reception reports. It is possible this station can still be heard early mornings. Frequency is 12.220 and schedule is 1800-1900, 2300-0100, 0430-0930. QRA is Radio Station XMPA, Chinese Army Radio Service, 10 Snake Mountain, Nanking, China. Clark, New Zealand, says this station is heard well there at 0545 with news in English.

LQX, Gamma Islands, Melchior Archipelago (South Shetlands), has been heard contacting Buenos Aires, Argentina, at 1700 on 12.330 (varies), announces as "Antartida Argentina." LQX2, Deception Island, has been heard contacting LSD9, Buenos Aires, 18.115, at 1800 on 14.820 (varies), dictating commentaries which are recorded by LSD9. (Villela, Brazil)

ZSS, (approximately 15.8) Cape Town, South Africa, has been heard in England around 0835 contacting GBC, London, on open circuit, then going into inverted speech to 0845. (Brownless, England)

Cushen, New Zealand, reports Radio SEAC moved to 17.730 from 17.820 due to having interfered with a BBC outlet on latter channel. (Radio Australia)

The unidentified Chinese station (call may be XUPB?) on about 6.11 relays the XGOY news 0900. (Balbi, California) Sometimes call sounds XGFP. (Dilg, California)

YV1RC, 6.150, "Radio Cabimas," Cabimas, Venezuela, is a new station heard evenings. YSCP, 5.200, San Salvador, El Salvador, is a new station heard 2000-2100. HCQRX, 4.985, "Radio Quito," Quito, Ecuador, has moved here from 6.000. YV9RA, 4.820, "La Voz de Apure," San Fernando de Apure, Venezuela, is a new station, heard evenings to 2130 sign-off. HC4FS, 4.560, "La Voz de Esmeraldas," Ciudad Esmeraldas, Ecuador, is a new station, heard to 2300 sign-off. YV6RK, 3.330, "La Voz del Tigre," El Tigre, Venezuela, is a new station heard evenings to 2130 sign-off. (Legge, N.Y.)

The Communist-controlled Chinese outlet, XNCR, 7.945 (varies), North Shensi, has been poor lately, audible on West Coast around 0630, carries news 0640, followed by Western music, signs off 0700; XGHT, another Communist outlet, 6.065 (varies), signs off 0830. (Dilg)

Canada's International Service now "speaks to the world by short-wave regularly in ten languages, and this service will be expanded to reach an even larger audience during the coming year," officials of CBC state.

QRA for KZBU, Cebu, Philippines, is Philippine Broadcasting Co., Gotiaoca Building, Comercio St., Cebu City, Philippines; the station wrote Gillett, Australia, verifying his report and stating it was the first one received from outside the Philippine Republic; slogan is "Cebu Calling," and by now the station should be operating 18½ hours per day (probably from around 1630 to around 1105). Gillett says KZRC, also Cebu, is heard opening on 6.135 with fair to good signals 1600, and KZRH, 9.64, Manila, is an excellent signal when testing prior to opening at 1600.

CR6AA, 7.177, Lobito, Angola, is scheduled weekdays 1130-1530, but Sunday schedule is not definitely established.

May, 1948

GOVERNMENT Surplus Savings

POWER SUPPLY

Designed for nationally known transmitter:

2-807, 1-6F6, 1-6N7—Class B
Modulated Maximum Signal
Carrier Output 75 Watts.
Value determination — 200
Watts off generator — Fed
into 10,000 or 12,000 Ohm
load.

INDIVIDUALLY BOXED
COMPLETE WITH TUBES

NEW \$5⁹⁵ EACH




SIGNAL GENERATOR

1-198 A

Frequency Range 7 to 15 mc.,
which multiplies into 20 and 10
meter band. Modulated 110 AC.
Can be used as frequency meter.

NEW \$19⁹⁵ EACH

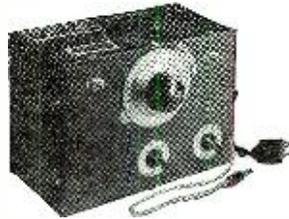

RHEOSTATS

25 Ohms, 50 Watts
15 Ohms, 25 Watts
20 Ohms, 1½ Amps.

Your choice

49^c
EACH

R. F. AMMETERS

Nationally Adver-
tised Make.

NEW
\$1²⁹
0 to 2 Amps.
2½ Inch
EACH
INDIVIDUALLY BOXED

954 TUBES

Well-known
standard brand
Individually
boxed.

NEW
\$2⁰⁰
DOZEN

HIGH VOLTAGE TRANSFORMERS

90 V. Primary, 6400
V. Secondary, Ap-
prox. 100 Mills.

NEW
\$1⁹⁵
EACH

VOLUME CONTROLS

Assortment of 12

\$1⁵⁰

RELAYS


110 Volt A.C.

NEW \$1²⁵ EACH

I. F. F. RECEIVER AND TRANSMITTER

Complete with 14 tubes

EACH \$5⁹⁵

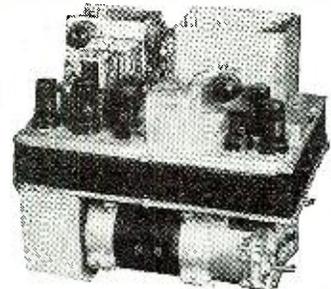

All Orders F.O.B. DETROIT, Shipped RAILWAY EXPRESS

No order under \$5.00—Please send check or money order.
Orders shipped C.O.D. subject to 25% advance deposit.


RADIO CENTER
2530 E. DAVISON AVE. DETROIT 12, MICH.

CUT ACCURATE HOLES IN RADIO CHASSIS




WITH A GREENLEE
RADIO CHASSIS PUNCH

• Make smooth, true holes quickly this easy way. Just turn GREENLEE punch with an ordinary wrench and have an accurately-sized opening for plugs, sockets, and other receptacles. No reaming or filing. A GREENLEE Punch for each of these sizes: $\frac{1}{2}$ " ; $\frac{5}{8}$ " ; $\frac{3}{4}$ " ; $\frac{7}{8}$ " ; 1" ; $1\frac{1}{16}$ " ; $1\frac{1}{8}$ " ; $1\frac{1}{4}$ " ; $1\frac{3}{8}$ " ; $1\frac{1}{2}$ " ; $1\frac{5}{8}$ " ; $1\frac{3}{4}$ " ; $1\frac{7}{8}$ " ; $2\frac{1}{4}$ ". Also GREENLEE Knockout Punches and Cutters for conduit and meter holes up to $3\frac{1}{2}$ ". Get facts now. Write Greenlee Tool Co., 1885 Columbia Avenue, Rockford, Illinois.

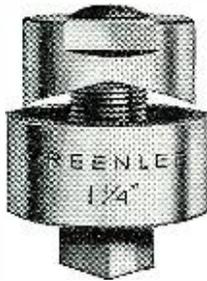

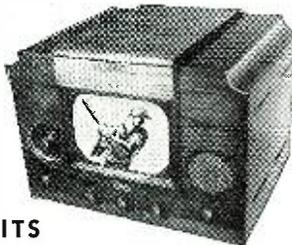TRANSVISION!!! WEST COAST HEADQUARTERS COMPLETE STOCK



KITS
ACCESSORIES
PARTS

12-INCH KIT 75 Sq. In. Picture List* \$28900	15-INCH KIT 125 Sq. In. Picture List* \$36500
---	--

Save \$200 - \$300

No technical knowledge needed... simple step by step instructions... nothing else to buy - Kit complete with folded Dipole Antenna - 60' Lead-in wire.

ORDER NOW - IMMEDIATE DELIVERY

5% Higher west of Mississippi

*WRITE FOR DEALER NET PRICES



8572 Santa Monica Blvd. Hollywood, Calif.

The *Radio Clube de Huilla*, 9.230, a new Angola outlet, is heard in South Africa around 1300-1330, but with weak signal. Lourenco Marques, Mozambique, has been heard testing on Saturdays on 9.71 at 0700-0900, preparatory to extension of schedules which may by this time be 0700-1700 weekdays and 0200-1700 on Sundays; 9.710 will probably be used to around 1100. It is noted that SABC (South Africa) has eliminated its 1545 relay of BBC news. (Laubscher, South Africa)

XLRA, 11.500, Hankow, signs off at 1000, signals are fair to good. Manila's KZFM, 11.84, has news 0500 and signs off 1000. PLY, 10.060, Java, is being heard again to 1030 (irregularly, not heard daily). *Radio Tabriz*, 6.105, is heard to 1000, weak to fair. (Balbi, California)

The "mystery" surrounding location of XGAS, 11.680 and 7.105, deepens. A report just in from Major, Western Australia, now gives it as Chung Chin. Earlier, Major listed it to me as Changsha, and New Zealand sources say location is Kungchun (may be same as Chung Chin). (If anyone can clear up this matter, please advise your ISW Editor.) Incidentally, Major says the station signs off at 1000 with an orchestra playing "Anchors Aweigh," followed by a chorus, with no announcements in English.

Kary, Pa., has received word from a Danish correspondent (Friis) that by this time Denmark's new short-wave transmitter should be on the air "with regular transmissions to the East on wavelengths from 13-20 meters and to North and South America on 30-40 meters." No other details. Other late tips from Kary are:

Reports from Jerusalem for American networks are now coming direct from that city instead of being relayed via land-line to Cairo transmitters. A frequency of about 19.203 (drifts) is used with a call of ZNT-18 (may be a Cable & Wireless station), generally heard around 0800 weekdays and 0900 Sundays. TGZA, Zacapa, Guatemala, appears to have a nightly schedule of roughly 2103-2310; signs on with marimba music, usually announces in Spanish but sometimes identifies in English as "TGZA, the *Oriental Radio* of the city of Zacapa in Guatemala, Central America, transmitting on 6655 kilocycles." Measures 6.660. A "mystery" station previously reported on 7.788 but more recently heard on 7.790 around 1900-2150 sign-off, rather strong signals, may be Stalinbad, Soviet Union. Is heard well here in West Virginia. Has usual deep hollowness of Soviet stations, often a clock is heard ticking, and there are frequent periods of long silence (with carrier on).

-[30]-

HOW TO TAKE TELEVISION PHOTOGRAPHS

By LESLIE ORTON
Editor, *Radio Entertainment World*
England

TO PHOTOGRAPH people miles away is quite simple if you have a television receiver and a camera. You merely have to photograph people appearing upon the television screen!

However, to make a decent job of it, it is advisable that the operator have some knowledge of the construction of the picture on the screen. Most of us know that when we see a movie at the theater we are actually observing a number of still pictures, with slight differences, which are cast upon the screen at such speed that, through the persistence of our vision, appear not as individual still pictures but as a moving picture. In some ways this description applies to television pictures.

Looking at the screen we observe a moving picture. Take a camera and photograph that picture at a high speed and we see recorded, not a picture, but a spot of light for television pictures are made up of a spot of light which travels the screen at high speed, varying in intensity in response to impulses radiated from the transmitting station and picked up by the receiver. (In actual fact that "spot of light" may appear as a part of a picture through the retention of light,

after the spot has passed, by the sensitized material used to coat the screen or blunt end of the cathode-ray tube.)

Thus it is clear that in order to obtain a photograph of the whole picture an exposure sufficiently long to enable the spot to traverse the complete screen must be made.

British television pictures are scanned at a rate of 25 pictures a second while American pictures are scanned at the rate of 30 per second. Therefore, in order to obtain the correct exposure on a single picture we must photograph at one twenty-fifth of a second for British pictures and one-thirtieth of a second for American pictures.

The aperture of the lens will naturally vary in accordance with the brilliance of the picture recorded and the speed of the plate or film employed.


Finally, it cannot be too strongly emphasized that the speed of taking is all important. It should be borne in mind that if too great a speed is employed in taking television photographs, very peculiar effects may be obtained, while if too slow a speed is chosen a blurred picture will result.

-[30]-

BIG MONEY IN RADIO

SEE THESE BRAND NEW RADIO BOOKS FREE

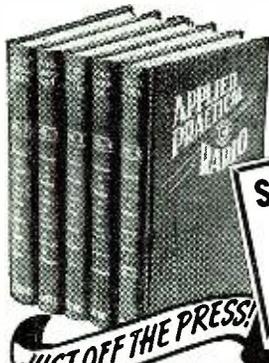COYNE'S New 5 Volume Set "APPLIED PRACTICAL RADIO"



You men who want to go places in Radio, and who know how much a solid working knowledge of the field helps to get the big money—this is IT! Over 1500 pages of down-to-earth Radio, from simplest principles to newest Television! It's all there easy to understand—how and why it works... how to construct, install, service. P.A. short-wave, auto-radio, aviation, radio-phonographs, FM, testing instruments and trouble-shooting short-cuts, phototubes — you name it, COYNE'S got it, in "Applied Practical Radio"!

SEE SET FREE FOR 7 DAYS

JUST OFF THE PRESS!

VALUABLE BOOK FREE for Looking at 5-Volume Set

Send This Coupon NOW

GET THIS BOOK FREE for LOOKING AT SET



Brand New! Explains circuits of latest sets.

PRACTICAL! CLEAR! COMPLETE!

5 big volumes—1000 illustrations and diagrams, with step-by-step photographs which "break down" the equipment for you to show what makes it "tick". Up-to-the-minute, complete, easy to follow... written as only COYNE books are written!

You must SEE these books to know how easy it is to prepare for the big jobs in radio. Here's our special offer—we'll send the complete 5-volume set for your 7-Day FREE Examination. And with it, we'll include our valuable, new guide for all radiomen, "150 New Radio Diagrams Explained," absolutely FREE! If you keep the 5-volume Set all you pay is \$3.00 within 7 days after the books arrive and \$3.00 per month until \$16.75 is paid—or you can pay \$15.00 cash price. If you don't want the set, return it and you OWE NOTHING. But either way you keep the "150 Radio Diagrams Book" as a gift. That book is ABSOLUTELY FREE.

SEND NO MONEY

REMEMBER—COUPON IS NOT AN ORDER. Just a request to see set free and get the FREE BOOK. But offer is limited, so act at once!

EDUCATIONAL BOOK PUBLISHING DIVISION
COYNE ELECTRICAL & RADIO SCHOOL
DEPT. 58-T3, 500 S. Paulina St., Chicago 12, Ill.

O.K., send me, postpaid, your new 5-volume set, "Applied Practical Radio" on 7 Days' Free Trial per your offer in Radio News. Be sure to include as a gift the book of 150 New Radio Diagrams Explained, absolutely FREE.

NAME AGE.....

ADDRESS

TOWN ZONE..... STATE.....

COYNE ELECTRICAL & RADIO SCHOOL (Founded 1899)
500 S. Paulina St. Dept. 58-T3 Chicago 12, Ill.

Our 26th Year



Quality-Price-Dependability

ATTENTION!!!

All SCR-522 Owners:

Remote Control Boxes for SCR 522's. Brand New in Original Packing; Consists of 5 push button switches, 5 Western Electric Pilot Assemblies, with Pilot Bulbs and Dimmer, and lever Switch all finished in Black Crackle. Order yours today for only **\$1.25** each

Antenna Plug 46-PS-1 for 522A.....Each 15c

STEEL CHASSIS

11 x 17 x 3.....\$1.85	10 x 17 x 3.....\$1.38
13 x 17 x 3.....2.22	5 x 10 x 3......87
7 x 7 x 2......63	7 x 13 x 2......96
4 x 17 x 3......99	10 x 14 x 3.....1.35

STEEL CANS AND BOXES

12 x 7 x 6.....\$1.68	4 x 4 x 2.....\$0.68
15 x 9 x 7.....2.35	4 x 5 x 3......76
11 x 12 x 8.....2.25	6 x 6 x 6......99

1/8 INCH STEEL PANELS

10 1/2 x 19.....\$1.22	5 1/4 x 19.....\$0.87
12 1/4 x 19.....1.46	7 x 19......96
14 x 19.....1.62	8 1/4 x 19.....1.10

1/8 INCH ALUMINUM PANELS

8 3/4 x 19.....\$2.25	5 1/2 x 19.....\$1.74
10 1/4 x 19.....2.87	7 x 19.....1.84

All above Black Crackle finish. Grey panels to order.

RELAYS

CS--DIFFERENTIAL RELAY

Dual coil with armature pivoted between coils. All contacts normally open. Operates 220-250 Volts. 8000 Ohms each coil, contacts S.P.D.T. Controls rated 2 amps. at 110 VAC. Ideally suited for balanced or bridge type circuits where limited current or power is available. Will withstand 12 G Vibration up to 60 cycles at 35000 feet altitude. Special low price..... **95c**



G.E. 2500 ohm 4 Ma SPDT 5 prong plug in type Hermetically sealed. Brand New..... **95c**

CLARE TYPE RY-2

Sensitive Relay 6500 ohm SPDT Coil Wound with 35700 Turns of No. 39 Ec..... **95c**

TUBES

5BP1 CR tubes 5" Green screen brand new... \$1.45

5BP4 CR Tubes 5" White screen brand new... 1.45

3BP1 CR Tubes 5" Green screen brand new... 2.15

832A Dual Beam Power Tetrode... .50

616 H.P. Twin Triode... .39

3C24 Triode 100W Power output 6.3V Fil. @ 3 amp. Max. Plate 2000V @ 75 Ma... 10 for 3.50

OIL FILLED CONDENSERS

1 Mfd. 600 VDC.....\$0.35	3 Mfd. 1000 VDC......98
2 Mfd. 600 VDC......98	5 Mfd. 1000 VDC......69
10 Mfd. 600 VDC......98	7 Mfd. 330 VAC.....1.50
0.1 Mfd. 7500 VDC.....2.00	2s.1 Mfd. 7000 VDC......98
.02 Mfd. 8000 VDC......98	SPECIAL—16 Mfd. 400 VDC W.E.....2.95
	1 Mfd. 5000 VDC Solar.....

SELINIUM RECTIFIERS

FEDERAL TYPE Half wave 100 Ma. size.....\$.50
FEDERAL TYPE Half wave 200 Ma. size......60

WHILE THEY LAST

OUNCER TRANSFORMER

As per Schematic.	
1-2 1 ohm D.C. Res. 25 ohm. Imp.	
3-4 220 ohm D.C.	
4-5 235 ohm D.C. Res.	
6-7 350 ohm D.C.	
Res. 6-8 2000 ohm. Imp.	
7-8 400 ohm D.C. Res.	35c ea.
Special At.....	\$2.95


If not rated 25% with order, balance C.O.D. All prices F.O.B. our warehouse New York. No order under \$2.00. We ship to any part of the globe.

LEEDS RADIO CO.

Dept. RN5
75 VESEY STREET
Cortlandt 7-2612 New York City 7

BC-645A 450MC X-MITTER-RECEIVER

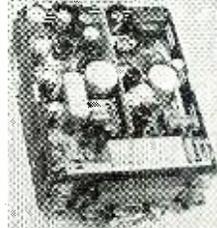BRAND NEW, Complete with Tubes, includes 2-7E6, 2-6F6, 4-7F7, 4-7H7, 2-955 and 1-WE316A door knob. Can be easily converted for Phone or CW on 420-450Mc Bands.



\$7.95
Each

DYNAMOTOR 5047

D.C. input 27.0 volts at 1.75 amps. D.C. output 285 volts at .075 amps. Continuous Duty Rating. Brand New. **95c** Each

DM-43A DYNAMOTOR

Manufactured by G.E. New. Input 24v @ 23 amps. 7500 RPM; output 515/1030/238 v. @ 215/260 milliamps; altered. SPECIAL..... **\$2.95**

ITEMS YOU MAY BE LOOKING FOR

IN 23A Xtal Diodes.....35c ea. 3 for.....\$1.00
ARC-5 Silver Plated Banana Plugs.....Per Doz. .10
De Jur Wire Wound Pot 20,000 ohms. 12 watt... .49
RS-8 Octal Sockets. Low Loss......08
110V Pilot Assemblies 1" Bulls Eye—Red......39
3/4 watt Bayonet Base Neons......20
1/25 watt Bayonet Base Neons......08

MICA CONDENSERS

.01—600V Postage Stamp.....	Each 5c
.003—2000V Postage Stamp.....	100 for \$4.75
.006—600V Postage Stamp.....	

WIRE WOUND POTENTIOMETER


100,000 ohm. precision made G.R. type. 23 watt 6" diameter. Brand new. **\$1.95**



METERS

5-0-5 AMPS. D.C. charge and discharge scale, 2" RD..... 69c
0-1 AMP. R.F. G.E. 2" RD..... 2.45
100 AMP-6 volt. D.C. 3" Scale 4 1/2" square Gray finish with shunt......295

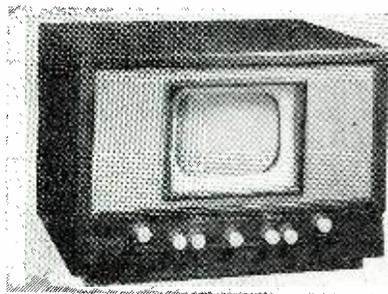A Beautiful Cabinet To Double The Value Of Your Chassis!



Specially Designed For Your "Transvision" Kit (12" and 15" Standard Models)

A hand-crafted cabinet made of the best $\frac{3}{4}$ inch walnut, finished by expert piano polishers, for the custom-builder who seeks to give his set the advantage of commercial styling combined with exclusive construction. Dimensions: 29 $\frac{1}{2}$ inches wide, 21 inches high, 20 inches deep.

INCLUDES THESE BETTER FEATURES:

- 8 inch Rola P.M. speaker for natural tone
- Specially built milk-white Lucite mask, curved to fit 12" picture tube—protected with safety glass.
- Conveniently located slide switch operates concealed illumination for Lucite printed dial and jewel-covered light in base.
- English design recessed base—felt cushioned.
- Thoroughly ventilated for heat dissipation.


IT'S THE "NEW LOOK" FOR THE COMMERCIAL BUILDER!

This highly polished cabinet comes to you completely assembled, drilled for shafts, wired and ready for your chassis. Nothing else to buy. Furnished complete with step-by-step instructions and following kit of parts to complete installation of chassis: pin jacks, plugs, pilot brackets, 6-8 volt pilot bulbs, onyx catalin knobs (6 plain, 1 with pointer), special low-loss antenna block, assembly to raise CR tube, masonite back-board drilled for ventilation, heavy stack output transformer, fuse holder, strap for CR tube, caution labels, nuts, washers, bolts, screws.

12" MODEL	WALNUT OR MAHOGANY (BLOND MAH. \$10 ADD.)	15" MODEL
\$79	Available for both 5 and 7 shaft chassis	\$89
NET		

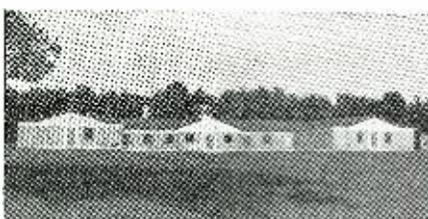F. O. B. B'klyn, N. Y. Terms: 10% with order, balance C.O.D.
Order direct or thru distributor

TEL-CRAFT COMPANY
108 HAVEMEYER STREET
BROOKLYN 11, N. Y.



RADIO ENGINEERING TELEVISION ELECTRONICS

Thorough training in all phases of radio and electronics, open to high school and junior college graduates. Old established school specializing in Radio training exclusively. Modern laboratories and courses. Enrollments limited. Approved veteran training.

VALPARAISO TECHNICAL INSTITUTE
Dept. RD Valparaiso, Ind.

Trough Line Tuner

(Continued from page 65)

the information given in Fig. 4.

The location of the tube sockets is extremely important if the shortest leads are to be obtained. It will be observed that when this plate is placed over the tuning condenser, the small tubular shield in the center of the tube sockets comes exactly in contact with portions of the condenser frame. These should be soldered to the frame at these points. A small additional brass shield should be soldered to the condenser frame at the point indicated in the photograph Fig. 1.

In Fig. 1, four points marked X will be observed. These are ground lugs which must be carefully soldered to the plate on which the tube sockets are mounted. This tube mounting plate is also soldered to the frame of the condenser at all four corners.

These ground lugs form part of the trimmers in the tuning condenser, and care must be used in soldering. If too much heat is used, the trimmers will fall apart. It is advisable to hold the lugs with a pair of long nose pliers while soldering.

The center conductors shown, which are marked "inner gut" in Fig. 1, are made of $\frac{1}{4}$ " brass tubing and are threaded at their lower end with a


$\frac{1}{4}$ "/28 thread and clamped to the base plate with a pair of nuts.


These lines are soldered to the opposite set of lugs on the trimmer condensers. After soldering, $\frac{3}{16}$ " holes should be drilled through the lugs supporting lines 2 and 3 to permit the wire inside the lines to be passed through the lugs.

Fig. 4 shows a *Wheaton* seal going through the mounting plate for the plate connection to the first i.f. transformer.

No connections for an antenna or transmission line are shown in the drawing. If a coaxial line is employed, a fitting may be mounted as shown in Fig. 1, and the center conductor of the coaxial fitting should be soldered directly to the inner gut at a point $1\frac{1}{4}$ " for a 50 ohm line and $1\frac{3}{8}$ " for a 72 ohm line. If a two-wire line is employed a hole may be drilled at a point indicated by the large dot directly to the left of the antenna connector at a distance from the connector equal to the width of the two wire line. One side of the transmission line may be cut one inch shorter than the other. Solder the short end of the line to a point on the outer shield designated by the dot, after passing the short end of line through the hole. Pass the long end of the line through a rubber grommet inserted at the point indicated by the dot and solder to inner gut at a point

Fig. 6.

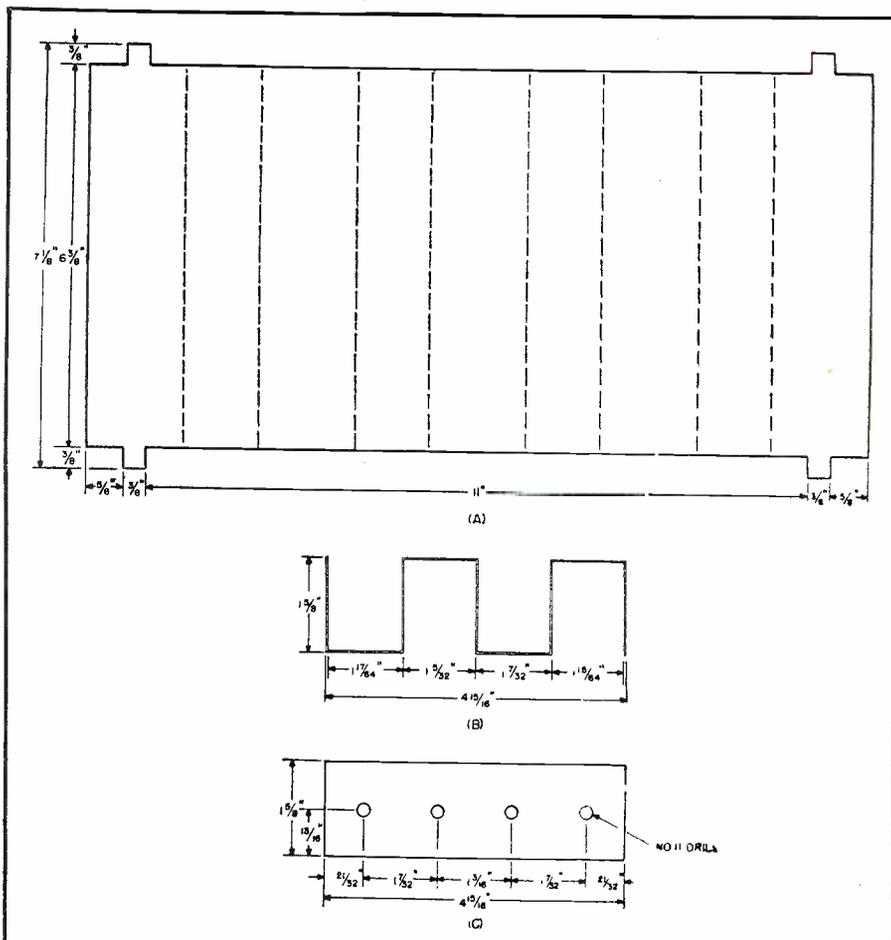

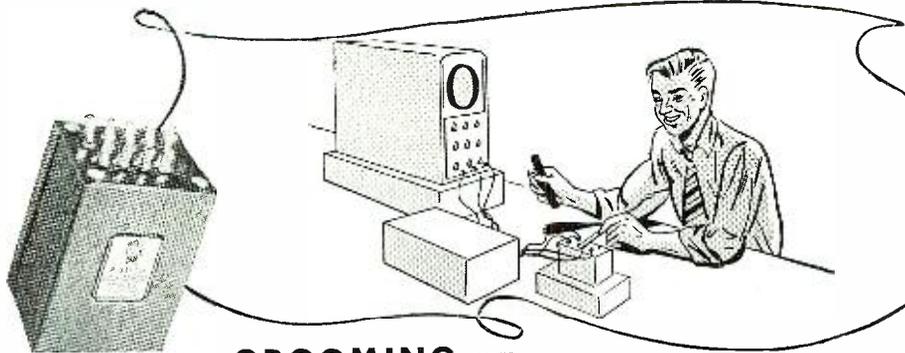

GROOMING an

Features

- $\pm 1/2$ db 30-15,000 cps for—Quality Plus Series.
- $\pm 1 1/2$ db 50-10,000 cps for—Industrial Series.
- Low transmission loss.
- Excellent balance on all "balanced" windings.
- Power ratings taken at 30 cps for Quality Plus Series, at 30 cps for Industrial Series.
- Either top or bottom mounting.
- Extremely low hum pickup.

ADC AUDIO TRANSFORMER for FAULTLESS PERFORMANCE

3 Complete Tests to Meet Rigid ADC Specifications.

Strict electrical tests are given each and every ADC Audio Transformer at three different stages of production. In order to give you faultless performance on the job, every transformer must come within catalog specifications on all tests. (Custom specifications on special transformers.)

1st TEST. After assembly of coil and laminations, each component must perform within ADC specifications on frequency response, impedance ratio, phasing, breakdown and balance tests. Any unit failing to meet all requirements is rejected.

2nd TEST. After impregnation, baking and casing, each transformer is re-checked for continuity breakdown and other requirements of the particular unit. This guarantees correct wiring, perfect insulation—no "shorts" or "opens."

3rd TEST. After cleaning, labeling, etc., a final continuity, breakdown and thorough visual check is made. This quality control test—plus the finest materials and workmanship available—assures you of faultless ADC performance on the job.

Consult your jobber about ADC Audio Transformers and other Components. Ask for Catalog 46-T.

Other ADC Components: JACKS • JACK PANELS • PLUGS • PATCH CORDS




Audio Development Co.

2833-13th Avenue So., Minneapolis, Minn.

Audio Develops the Finest

MORE FOR YOUR MONEY

COMPLETE
\$995
35-FT. MAST

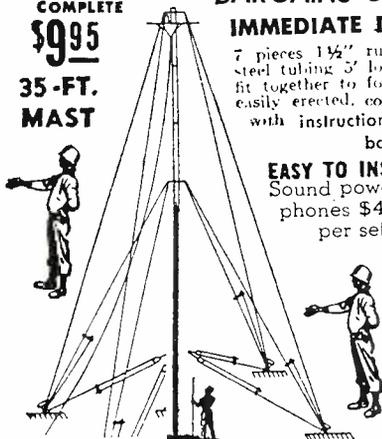

BARGAINS GALORE
IMMEDIATE DELIVERY

7 pieces 1 1/2" rustproofed steel tubing 3' long which fit together to form mast, easily erected, complete with instruction booklet.


EASY TO INSTALL
Sound powered: phones \$4.95 per set

BRAND NEW mast KITS SEPARATELY OR COMPLETE UNITS

7 SECTIONS - 5 FEET LONG

Handy for Camping Trips, also Useful for Transmitting, FM and Television sets.

FOR HAM AND GENERAL USE

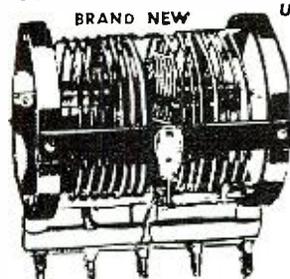

Use The Best!

SURPLUS TRANSMITTING COILS

B & W 3400 SERIES INDUCTORS

Frequency Range (mc)	Coil 500 watts	No. of turns on Link Coil	
2.0 - 3.5	C-387-D	14	6.5
3.5 - 4.5	C-388-C		4.5
4.5 - 5.7	C-389-C		4.5
5.7 - 8.0	C-390-C		4.5
8.0 - 11.0	C-447-B	Per Set	4.5
11.0 - 14.0	C-448-B		2.5
14.0 - 18.0	C-449-B		1.5

\$5.00 matching up to 600 ohms.

DOW RADIO

1759 E. COLORADO PASADENA 4, CALIF.

Pasadena Phone—SYcamore 3-1196
Los Angeles Phone—RYon 16683

Send for Our Special Bulletin of Government Surplus Items

ATTENTION !!!

ALL SCR-522 OWNERS:

Remote Control Boxes for SCR 522's, Brand New in Original Packing, Consists of 5 push button switches, 3 Western Electric Pilot Assemblies, with Pilot Bulbs and D11 meter, and lever Switch, all finished in Black Crackle. Order yours Today for only...each **79c**



SCOOP! 110 M.C. REC. BARGAIN
BC-733 D Localizer Receiver

Freq. 108-110 Mc; Tube complement; 10 tubes—1—72S47, 2—12SR7, 1—12A6, 1—AH7GT, 2—12SG7, 3—717A.

NEAR NEW CONDITION. A RED HOT VALUE!

Companion to the glide path receiver. Also contains 90 and 150 cycle band-pass filters. Has the best AVC system yet developed; can use parts or use as a model for construction. 10 tubes, crystals, relays, etc. Schematic included. Don't pass this up! At only..... **\$3.95**



BIGGEST SAVINGS IN HISTORY!


Gov't Surplus

**MODULATOR
OSCILLATOR
AMPLIFIER**

SUPER SPECIAL BRAND NEW!
Eimac 304 TH
JAN inspected
\$3.95 ea.

ORDER NOW

EIMAC 304 TL

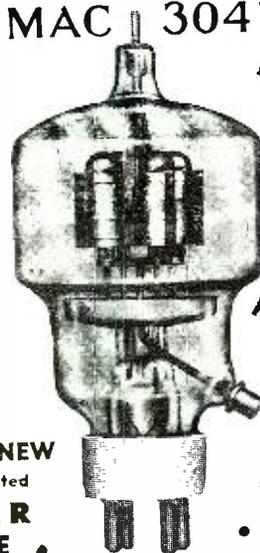

POWER!!

POWER!!

BRAND NEW
JAN inspected

SUPER VALUE!

BETTER! ORDER 4 or more TODAY!

MISCELLANEOUS ACCESSORIES Express Collect
Mail Orders Promptly Filled While they last—Any Quantity

Distributors of amateur radio equipment and parts.

Only **.90c** ea.

SEND FOR THESE SPECIALS

ALL NEW MERCHANDISE

CONDENSERS

.05 mfd. (2) 600 V. Bathtub.....	\$.09
.1 mfd. (3) 600V. Bathtub.....	.09
.1 mfd., 1,500 V. Bathtub.....	.15
2.0 mfd., 600 V. tubular oil filled.....	.45
5.0/5.0 mfd., 600 V. Rectangle oil filled....	1.05
10.0 mfd., 600 V. Rectangle oil filled w/stand off insulators.....	.95
3.5/5 mfd., 1,000 V. Rectangle oil filled w/ stand off insulators.....	.90
10.0 mfd., 1000 V. Rectangle oil filled w/ stand off insulators.....	1.40
2.0 mfd., 2,500 V. Rectangle oil filled w/stand off insulators.....	2.20
.25/.25 mfd., 6000 V. Rectangle oil filled w/ stand off insulators.....	3.75
1.25/1.25 mfd., 7,500 V. Rectangle oil filled w/stand off insulators.....	16.95
.001 mfd., 25,000 V Rectangle Mica w/stand off insulators.....	20.00
50 mmf., 32,000 V. Tubular Vacuum.....	5.95
250 mmf./250 mmf 3,000 V. Variable .070"	
Spacing #BC-1623.....	7.95

SPECIALS

Telescoping antennae - AN75B, 1'-3" to 7'-0" solid brass clamp on.....	\$1.25
Antennae mast - 1 1/2" tubular steel 35' high in nesting 5'0 sections, complete w/guys and base.....	9.95
Thermo switch - Fenwall - 50 + 400°F. 110/ 220 V., 2500 watt contacts.....	1.60
Sockets moulded mica, 7 prong miniature....	.12
C-H Toggle sw and circuit breaker, 6A.....	.45
Potentiometer-dual, 1-meg.....	.60
Sound Power Phones—Navy Type complete w/ Microphone, Headset, 50' of cord.....	4.95

RECTIFIERS

Dry disc type—Continuous duty ratings

3.5 V.A.C.—1.8 V.D.C. @ 1.0 amp. full wave bridge.....	\$.75
6.5 V.A.C.—2.2 V.D.C. @ 3.0 amp. full wave center tap.....	1.20
36 V.A.C.—24 V.D.C. @ 2 amp. half wave.....	.75
54 V.A.C.—42 V.D.C. @ 1.6 amp. full wave bridge.....	4.40
154 V.A.C.—120 V.D.C. @ .6 amp. full wave bridge.....	6.85
180 V.A.C.—154 V.D.C. @ .4 amp. full wave bridge.....	6.90

TRANSFORMERS

Microphone input, double carbon, 18 to 8000 ohms.....	\$.70
Power, 80-110-220V., 50-1600 Cy. primary 422 V., 15m.1 C.T. and 6.3 V. @ 3.0 amp. secondary.....	.95
Power, 110 V. to 24 V. @ 1.0 A. 60 Cy. uncased.....	1.60
Transtat 115/230 V., 50/60 Cy. input, 0-260 V. @ 2 1/2 A.....	21.50
Transtat 115 V., 50/60 Cy. input, 0-130 V. @ 10 A.....	21.50

TUBES

All new boxed and of standard mfg.	
2D21 Miniature thyratron.....	\$.70
931A Photo multiplier.....	1.45
3C24/24G Transmitting triode.....	.89
872A Mercury rectifier.....	1.15
VT127A Transmitting triode.....	2.40

No Orders Under \$3.00 Please,
30% with Order - Balance C.O.D.

All shipments made Express Collect.
Write for additional information on above items
or for Special Quantity Discounts.

1527 E.
Seventh
Street

EPCO

Los Angeles
21,
California

'MERIT' BRINGS VALUES!

IT'S SENSATIONAL!

HOTTEST ITEM OUT! Make your SCR-522
Receiver operate on 144 to 148 Mc with
ONE DIAL control, in less than 1 hour!
Method is completely mechanical. Track-
ing is adjustable for the individual receiver.
Band-spread is adjustable up to 300
about 160 degrees. Parts and
instructions.....

3

(Please include 8c postage)

ARC/5 2-3 Mc Xmtr..... \$9.00

TRANSMITTING TUBE BARGAINS!

807.....	\$1.15	8025A 500 Mc Triode.....	\$3.95
805.....	3.50	866A.....	.75
810.....	5.95		

(Minimum Tube Order \$5. All Tubes
shipped Express)

MERIT RADIO SUPPLY CO.

471 Merrick Road Lynbrook, N.Y.

1 3/4" from base plate. These dimen-
sions have been found by experiment
to give best results.

It will be noted that no form of
coupling has been provided between

the oscillator and mixer sections as
sufficient oscillator energy is present
without it, and there is no pulling of
the oscillator.

-30-

POLARITY RESPONSE FROM RADIO TUNING EYE TUBES

By NATIONAL BUREAU OF STANDARDS

THE use of electron-tube tuning
indicators for balance or null detec-
tors is well-known. The necessity for
polarity-sensitive tuning indication in
frequency modulation reception has
given impetus to the development of
the new 6AL7-GT indicator tube fea-
turing a dual column type of
presentation. For instrument work,
however, a balance indicator capable of
greater precision is frequently desired.
By means of the circuit shown in Fig. 1,
M. L. Greenough of the Electronic
Instrumentation Laboratory, National
Bureau of Standards, has adapted a
conventional "magic eye" tube of the
variable shadow angle type, such as the
6E5, 6U5, 6N5, etc., to furnish a polar-
ity-sensitive indication. Although this
circuit was developed for instrument
application, it may be of value for
adapting a conventional tuning eye to
balance indication in FM discrimi-
nators.

The obvious method of making the
"magic eye" tube polarity-responsive
is to bias the deflection grid to produce
some arbitrarily chosen reference angle,
which is marked on the scale over the
tube. Positive or negative signals then
cause an increase or a decrease of this
shadow angle. The disadvantages of
such a system are the instability of the
reference angle, which is greatly depen-
dent upon the supply voltages, and
parallax of observation. These disad-
vantages may be avoided by repeatedly
switching the signal on and off at a rate
fast enough to prevent visible flicker,
for example, at power line frequency.
By this means two shadow angles are
maintained on the tube screen itself.
One shadow angle, corresponding to
zero input, appears half the time,
while during the remaining time the
angle is that due to the amplitude of
the applied signal. Zero signal input is
indicated when the edges of these
angles coincide.

Typical patterns obtained for posi-
tive, zero and negative signals are

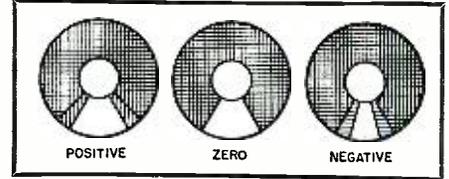


Fig. 2. Typical patterns on 6E5 indi-
cator tube when rendered polarity-
responsive by circuit shown in Fig. 1.


shown in Fig. 2. There appears to be a
half-illuminated angular sector whose
width is proportional to the deflection
signal, and which lies on one or the
other side of a reference line as deter-
mined by signal polarity. Alternatively,
the pattern may be considered as two
superimposed areas of half-illumina-
tion, one fixed and one variable. The
edges of these areas are similar and
sharp in the 6E5. Their superposition
at balance can be precisely observed.
Accurate null indication is maintained
in spite of supply voltage variations,
since such changes merely affect both
illuminated areas identically. Using
reasonable care it has been found
possible to repeat observations of bal-
ance to less than 0.05 volt with the
unaided eye. A simple lens permits
resolution approaching an electrically
imposed limit, which in this case was
measured to be approximately 7 milli-
volts. Although no extended study of
ultimate balance limitations has been
made, higher magnification and im-
proved switching circuits could un-
doubtedly provide higher resolution.

In the circuit shown in Fig. 1 the
diode network acts effectively as a
switch which is opened and closed
during alternate half cycles of the 60-
cycle "switching voltage." The d.c.
input signal is applied across the 1-
megohm resistor in series with the
resistance of the diode switching cir-
cuit between point A and ground. The
voltage across the diode switching
circuit is applied to the grid of the
tuning eye. During the half cycle of
switching voltage which renders the
diodes conducting, the resistance be-
tween point A and ground is low rela-
tive to 1 megohm. This permits a
negligible fraction of the input voltage
to appear between point A and ground.
During the half cycle of diode non-
conduction, the resistance of each
diode is increased to its reverse vol-
tage value, and nearly the entire input
voltage appears between point A and
ground. Due to the symmetry of the
diode network, none of the switching
voltage appears between point A and
ground.

In this circuit diodes of high quality,
particularly with regard to back
resistance, provide maximum sensitivity
of indication. Miniature dry disc recti-
fiers for example, 7 ma. selenium or
copper oxide units having more than
10 megohm back resistance, have
proved satisfactory.

-30-

Fig. 1. Circuit diagram for obtaining polar-
ity-sensitive indications with 6E5 tun-
ing indicator tube. Cathode resistor, R,
is determined by plate supply voltages.

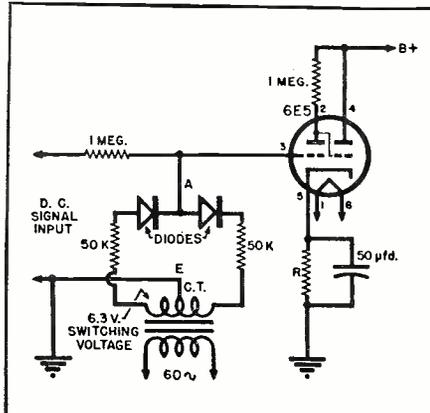

Two-Way Radio
(Continued from page 41)

without feedback than in the conventional single superheterodyne, yet reducing the hazard of spurious responses so common to double superheterodyne receivers unless carefully designed.

A two-way mobile unit consists of a separate transmitter and receiver with associated power supplies or a transmitter, receiver, and power supply all in one housing. A hand microphone or handset and a control unit are usually mounted on or near the dashboard of the vehicle. Transmitter-receiver units vary in size from almost the entire capacity of an automobile trunk to the size of an ordinary brief case. Mobile antennas usually consist of an 18" rod or wire mounted on the auto roof in a vertical position and connected to the transmitter-receiver unit through flexible coaxial cable.


The power output of commonly available two-way mobile units varies from 2.5 to 30 watts. The amount of power required has been widely argued, but today in the same cities various makes of equipment are used on the same channel with equal results. The higher powered units, of course, put out stronger signals but to the FM receiver at the land station, a 1 watt or 50 watt mobile unit will sound just as loud, provided the frequency swing is the same. Although in many cases, users of low powered equipment report ranges as great as that obtained with higher powered units, there is no doubt that the higher powered unit should be able to provide slightly greater range, particularly, in case of adverse locations.

Mobile receivers are often duplicates of land station receivers, whereas some manufacturers have designed more compact receivers for mobile installations. The general electrical design is the same as in land station receivers. Vibrator type power supplies are most commonly used in mobile receivers.

To reduce the nuisance of having all operators as well as passengers in vehicles equipped with mobile units hear all of the transmissions emanating from the land station as well as all other land stations on the same channel in the same service area, means for selective calling or lock out of unwanted transmissions are being provided by some manufacturers. Dial systems can be employed to select desired mobile units only. Transmission of various tones and combinations of tones is being used to select the desired mobile unit.

One of the simplest, yet most effective, selective calling systems provides for the transmission of a tone from the land station to turn on the loudspeakers of all cars in a group or fleet. When the land station operator wishes to call a specific mobile unit, he operates his control unit so it will auto-

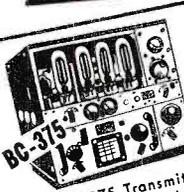You Can Depend On ABELL For . . .
REAL SURPLUS VALUES



100 WATT TRANSMITTER
BC-375 Transmitter. Self-contained oscillator, modulator, and P. A. Uses 4-211's and 1-10. 3-2 1/2" Meters. Requires 1000V Plate at 350 MA and 24V A power. Or can be torn down to provide a bonanza of top quality xmitter parts.
Less tubes and tuning unit. **\$13.95**

With Tubes and Tuning Unit, as illustrated.....\$18.95

BC-191. Same as above, except that filaments are hooked up for 12V. Supplied with all connectors, tuning unit, and 12V Dynamotor.....\$27.95
Set of 6 connecting plugs, only.....\$ 2.95



FLASHLIGHT
79c Less Batteries
Sturdy shock-proof flashlights with handy belt clamp.



CLIP BOARD
Made of sturdy masonite **\$1.49**


CLIMBING EQUIPMENT



Safety Belt \$5.75
(State Belt Size).....

POLE CLIMBERS \$4.50
And Straps....

INSULATED TRIPOD **\$1.49**

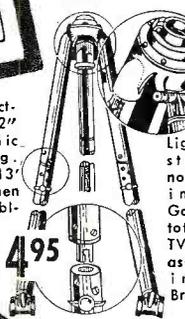

Constructed of 2" phenolic tubing. Stands 13' high when assembled.

Rotating ball-bearing head. Will clamp 2" tube or shaft. Light weight, strong, does not need RF insulation. Good for rotating beams, TV, etc. Easy to assemble and install. Brand new.

SCR-625 Mine Detector.....\$49.95
TS-13 Handset. 2000 ohm earphone, 200 ohm carbon button. 6 ft. cord.....\$2.95
Sound Powered Handset.....\$12.95
Microphone T-32. Desk Stand with press to talk switch and cord. New.....\$2.95

Cable, 7 Conductor, #14 Stranded. 600 V insulation. Heavy duty R C. 65' long. Russell-Stoll #3880. Plug each end. 7/8" OD.....\$4.95
Typewriter. Reconditioned. Guaranteed. Standard Models, Makes.....\$59.50

WRITE OUR HAM DEPARTMENT
Lou Bremer W3LE in charge. Nationally known DX'er and Winner-1939 DX Marathon (Phone Section.)
Almost every type of Cable used by Signal Corps in stock. 1 to 100 Conductors. Send for flyers.
Prices subject to change without notice.

GIBSON GIRL EMERGENCY XMTR **\$34.95**



Transmits automatic SOS signal on 500 KC emergency wave. Can be manually keyed to transmit additional information. Hand cranked. Supplied with parachute, signal light, box kite, balloons with hydrogen generators. Complete, original pack.

No batteries required

SEND FOR OUR FLYERS! TELL US YOUR WANTS

ABELL
Distributing Company
15 E. BIDDLE ST.-BALTIMORE 2, MD.

ELECTRONIC VOLT-OHMMETER
\$11.85

110 VOLTS AC 20 RANGES
0.5/10/50/100/500/1000/5000 volts
DC and AC 0-1,000,000,000 ohms in
six overlapping ranges. Sensitivity:
over MILLION OHMS per VOLT on 5
volt ranges.

Complete kit, panel, chassis, nine inch long dial scale, tubes, components. Cost is low because special slideback circuit eliminates need of expensive meter.

STERLING ELECTRONIC COMPANY
BOWLING GREEN, DEPT. 4, KENTUCKY

FOR PARENTS WITH IMAGINATION

Designed for **RADIO MEN**

60¢  **DOZ.**

ALSO RADIO TUBE SHAPED PLACE CARDS

BIRTH-O-GRAM
Announcements

In Motifs of WORK, SPORT, HOBBY, This and many other designs at leading Baby, Department, Gift, and Stationery Stores. Or write direct for FREE sample.

BIRTH-O-GRAM CO., Dept. R, MADISON 3, WIS.

RADIO COURSES

Preparatory, Broadcast, Marine Operating, Servicing, Aeronautical, Television, Frequency Modulation, Radar.

Classes now forming for June 1st. Entrance Exam. May 17th.

Veteran Training. Literature.

COMMERCIAL RADIO INSTITUTE
(Founded 1920)
38 W. Biddle St. Baltimore 1, Md.



Chicago

INSTRUMENTS

Quality at Low Cost!



POCKET VOLT-OHM-MILLIAMMETERS FOR ONLY \$5.25

Anyone can now own a good volt-ohm-milliammeter. There is a Chicago V.O.M.A. priced at only \$5.25. Chicago "Featherweights" that slip easily into the pocket are the original miniature radio test instruments. They are popular throughout the world.

For years, Chicago Instruments have given radio men accurate, dependable service. And because of simplicity of design and freedom from "gadgets" we have been able to hold down prices to a fraction of what you would normally pay for instruments of similar quality.

Chicago Instruments are available in a variety of ranges and sensitivities. You may see them at your Suppliers or get the complete details by writing for Bulletin No. 10.

CHICAGO INDUSTRIAL INSTRUMENT CO., 536 W. ELM ST., CHICAGO 10, ILL.

SPECIAL •
 5 CP1—Oscilloscope and Picture Tube. New Surplus.....\$1.00
 1/2 Deposit—Balance C.O.D.
THE WALDREF CO.
 1615 N. Genesee, Hollywood 46, Calif.

WELCOME!
RADIO PARTS
SHOW VISITORS
SOUNDMIRROR and MAIL-A-VOICE
DISTRIBUTORS
BUSINESS SPECIALTIES ENGINEERING CO.
 Exclusive Distributor
 542 S. Dearborn Street Chicago, Illinois
 Telephone Harrison 6835


BUILD-A-KIT BIT-BY-BIT And Pay as You Go!

TELECRAFT for "TRANSVISION" KITS

With "King Size" 12-Inch Screen

Only \$49.50 For the Starting Unit

20,000 Kits Now in Operation
 Total cost of Complete Kit, \$289.00 (Cabinet extra)

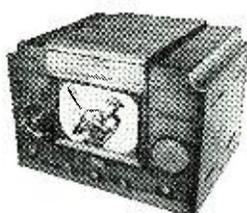TELECRAFT offers you a new idea in building your own Television radio. You get a basic unit at \$49.50. When you have completed the basic assembly, you order Unit 2. There are only 4 units in all!

TELECRAFT Television Kits are easy to assemble, average time about 27 hours. And you get a "King Size" razor-sharp, 12" picture, high fidelity FM sound reproduction, 9000 volts second anode potential for brightness and sensitivity, and other "expensive" features. **TELECRAFT** Television Kits are COMPLETE with ALL tubes, wired and pre-tuned RF units and IF's, di-pole antenna, lead-in, wire and solder.

Order your first unit today... get started on that Television set of your dreams now. Enclose check or money-order. Written guarantee! Write for Details.

TELECRAFT CORPORATION
 2 WEST 15th STREET
 NEW YORK 11, N. Y.

matically transmit a tone for a fraction of a second at the start of the transmission. This tone unlocks the squelch circuit of all the mobile units equipped with filters for that particular tone. The land station operator's voice is then heard over the loudspeakers of these mobile units.

The driver of the desired mobile unit then picks up his handset, and acknowledges the call. For the rest of this communication, the land station operator puts his transmitter on the air without the tone. The loudspeakers in all of the mobile units are then silent and the land station can be heard only through the handset.

The aggressive radio technician with the required technical qualifications and equipment is in demand right now. Taxicab operators in particular are in need of the assistance of capable technicians to install and maintain their radio equipment. Manufacturers of two-way radio equipment are anxious to locate qualified technicians who can be referred to their customers. As the urban mobile radio field expands, the demand for technicians will increase beyond its present critical stage. There are service contracts available to radio technicians who are ready to handle the two-way radio service business.

At the time of writing, the taxicab companies using radio are all operating on the same frequency. In reality, they are using two frequencies, 152.27 megacycles at land stations and 157.53 megacycles at mobile units. By using two separate frequencies for cross channel operation, mobile units cannot communicate with one another because their receivers are tuned to the land station frequency. Neither can two land stations communicate with each other unless a monitor receiver is employed. Although most land stations are not equipped with monitor receivers, under a strict interpretation of FCC rules, each station should have a monitor receiver so it could determine that the air is clear before transmitting. At present, two or more stations do go on the air at once with the result that serious interference is caused. In one of the country's largest cities, a power war exists. Taxicab operators have increased the power of their land stations so they can get through the interference, but they in turn are creating more interference. One of these stations can be heard 60 miles away, which is many times farther than is required. Rather than respect the rights of their competitors, these stations come on the air at will even if the other fellow is already on the air. If monitor receivers were employed, and the owners of the stations would cooperate, the use of radio in taxicab dispatching would be more effective for all concerned. No doubt, when more channels are assigned for taxicab service, and when the service is established on a regular basis, the FCC will police the service to prevent such abuses of the privilege of using radio.

Fixed-tuned v. h.f. receivers are already available and more will be

RADIO NEWS

available soon for monitoring purposes. A superregenerative receiver may be used for monitoring purposes as this type of receiver will demodulate FM. Another method of cooperative use of a channel is to use a leased telephone line between land stations operating on the same channel. When one station is on the air, a lamp will light at the other station, indicating that the channel is busy, or the line may be used to operate interlocking relays that will prevent one transmitter from going on the air while the other is in use.

FCC Applications

A radio technician entering the field of mobile radio maintenance should be familiar with FCC rules and regulations as well as the procedure to be followed in applying for construction permits and licenses. Complete information on this subject may be obtained by writing direct to the Federal Communications Commission in Washington, D. C.

Operators of land stations must hold a third class radiotelephone license, often referred to as a restricted radiotelephone permit. The need for an examination for this grade of license has been waived. It is now only necessary to apply for the license by mail on the new type forms issued by the Commission. Knowledge of the laws governing radio is required but no technical knowledge is necessary. However, anyone actually making adjustments to a transmitter must possess either a first or second class radiotelephone operator's license which requires a written examination.

The need for qualified service stations to maintain two-way mobile radio equipment is growing every day. Qualified men with the proper equipment have a golden opportunity. Now is the time to enter this field to get in on the ground floor. One way of starting would be to write to the various manufacturers of two-way radio equipment stating your qualifications. These manufacturers in turn can contact you when one of their customers in your vicinity is in need of installation or maintenance service.

The rates being charged for installation service vary with companies and localities. A fair price for the installation of a mobile unit in an automobile is about \$15.00. Some firms are charging \$25.00, and others less than \$10.00. However, a lot depends on the make of equipment and the make and condition of the automobile. When installing equipment in a large fleet of cars, production line methods can be used with the result that the installation cost per car will drop. Land station installation charges will vary with the equipment. \$50.00 to \$100.00 seems to be a fair price. However, installation of the antenna or erection of an antenna mast is not included in these figures.

Many fleet operators using two-way radio are contracting for maintenance service on a monthly-per-car basis. In one instance, the radio service agency

LOW PRICES AND BEST SERVICE AT Senco's ENLARGED HEADQUARTERS!


EVERY TUBE A BEST BUY!

Every Tube in Carton		R.M.A. Guaranteed	
Type	Each	Type	Each
024	69c	7A4	53c
1A3	45	7A7	58
1A5GT	59	7B6	44
1A7	59	7F7	49
1U5	36	7N7	49
1V	45	7Y4	44
1L4	55	7X7	44
1T4	69	55 7A7	44
1S5	69	55 12A6	35
2A7	49	39 12A8GT	45
2A5	65	55 12A7	50
2A6	49	39 12BA6	50
2X2	35	29 12BE6	50
3A4	69	59 12SEGT	35
3S4	69	59 12J7GT	45
SU4G	50	40 12K7GT	45
5W4GT	40	36 12K8	65
5Y3GT	40	33 12Q7GT	45
5Y3G	42	37 12SA7GT	40
5Y4G	40	37 12SF7	39
5X4G	40	37 12SQ7GT	40
5Z4	59	49 12SK7GT	45
6A7	50	45 12SR7	39
6A8GT	49	39 12SJ7GT	55
6AC5	98	92 14A7	65
6AC7	66	60 14B6	59
6AK5	74	69 24A	49
6AC7/6AK7	89	79 47	49
6B7G	55	49 57	45
6C4	29	25 58	45
6CSGT	40	35 71A	39
6C6	45	32 75	50
6C8G	37	29 76	45
6F6GT	45	39 77	35
6H6	45	39 80	40
6J6	55	50 83V	99
6H6GT	45	39 85	49
6J5GT	45	39 99V	35
6J7GT	42	38 99X	35
6K6GT	45	39 25L6GT	49
6K7GT	49	39 25Z5	49
6K7G	50	41 25Z6GT	45
6L6G	79	69 35W4	43
6Q7GT	47	39 35Y4	43
6S7	59	48 35Z3	44
6U7G	35	25 35Z5GT	43
6V6GT	45	39 35L6GT	45
6X5GT	49	39 35/51	49
6SA7GT	44	37 50L6GT	50
6SH7GT	40	32 117Z6GT	89
6SJ7GT	44	37 50B5	42
6SK7GT	49	39 32L7GT	59
6SL7GT	49	47 65Q7GT	44
6SN7GT	49	47 65G7	44

STANDARD BRAND MOTOR AND AC CRYSTAL PICK-UP

60 cycles, 115 volts, with Turntable.

\$4.35 Complete

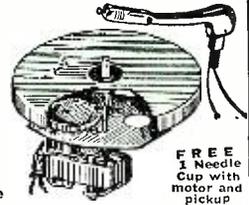

FREE 1 Needle Cup with motor and pickup

VIBRATORS

2V Vibrator for G.E. Portable Set—Model 330ea. 99c
6V Auto Vibrator—4 Prong.....ea. \$1.09

Popular Brand 12" P.M. SPEAKER With 21 oz. Magnet

6V6 push pull output transformer mounted on speaker With cord and plug attached.

\$8.95 Complete



MORE SPEAKER VALUES

3 1/4" Conr 4" Sq. Frameea. \$1.19
4" P.M. Speaker.....ea. 1.19
5" P.M. Speaker.....ea. 1.15
5 1/4" Cone 6" Sq. Frameea. 1.55
6" P.M. Speaker.....ea. 1.55
8" P.M. Speaker.....ea. 2.75
12" P.M. Speaker.....ea. 4.95

SALE! OAK RECORD CHANGER



One of the most popular record changers in use today. Plays 12 — 10" or 10 — 12" records automatically — fast change cycle. Simple — fool-proof — compact. 2-post — noiseless motor — feather weight crystal pick up.

\$15.95

TUBULAR CONDENSERS

30 mfd. @ 150V.....ea. 27c
40 mfd. @ 150V.....ea. 29c
50 mfd. @ 150V.....ea. 38c
10x10 mfd. @ 50V.....ea. 25c
16x16 mfd. @ 150V.....ea. 33c
20x20 mfd. @ 150V 4 leads.....ea. 38c
30x30 mfd. @ 150V.....ea. 40c
20 @ 25V.....ea. 40c
30x50 mfd. @ 150V.....ea. 47c
40x40 mfd. @ 150V.....ea. 47c
30x25 mfd. @ 300V.....ea. 41c
20 @ 25V.....ea. 41c
20x20x20 mfd. @ 150V.....ea. 40c
10 @ 25V.....ea. 40c

VOLUME CONTROLS

Popular Brand 3" shaft tapped with switch.

250,000 ohms
500,000 ohms
1 meg. ohms
2 meg. ohms

39c Each

OUTPUT TRANSFORMERS

50L6ea. 39c
3Q5ea. 39c
6V6ea. 44c
All Sturdily Constructed.

IF TRANSFORMERS

Midget Type 456 KC Input-Output.
Medium Size 456 KC
I F Coils—Input and Output.
49c Each

25% deposit on all orders, balance C.O.D., F.O.B. New York

SENCO RADIO, Inc.

71 WEST BROADWAY, N.Y. 7, N.Y.
TELEPHONE BEEKMAN 3-6498

LEARN TELEVISION ELECTRONICS RADIO

Modern Completely Equipped Laboratories

DAY AND EVENING CLASSES

G.I. Approved—Veterans Receive Subsistence

ENROLL NOW!

ELECTRONICS INSTITUTE, INC.
21 Henry, Detroit 1, Mich.

Guaranteed Radio Tubes

All types for Immediate Delivery
Send For List

Territories Still Open for DISTRIBUTORS

Attention Manufacturers—Large Quantities of 117L7-32L7-6F6-6K6-6SK7-70L7-1-Volt Miniature and 12-Volt Miniatures

LE-HI ELECTRICAL COMPANY


660 Broadway
Humboldt 5-3530

Newark 4, N. J.
Humboldt 5-3531

How to repair RADIOS . .

This manual shows you how to handle 95% of all service problems

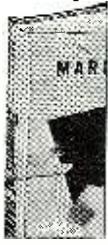Here's a highly practical radio repair manual which leads you in easy steps to a complete understanding of 95% of all radio servicing jobs. It covers the modern superheterodyne A.M. receiver, as well as phonograph-combination service problems and auto radio problems. Detailed "how-to-do-it" explanations enable you to put your finger on exactly what needs to be done.



ELEMENTS OF RADIO SERVICING

By William Marcus, co-author of "Elements of Radio" and Alex Levy, Instructor of Radio Mechanics, Manhattan Trade Center for Veterans and Chelsea Vocational High School.

471 pages, 6x9, illustrated, \$4.50.

This radio servicing handbook is easy-to-read and easy-to-understand. It breaks the superheterodyne into natural stages, and analyzes it thoroughly from a service standpoint, covering everything from setting up the signal generator to the push-pull output stage. Attention is given to the most commonly used testing equipment — the multimeter and signal generator. Schematic diagrams help make this book a practical on-the-job manual.

10 DAYS' FREE EXAMINATION

McGraw-Hill Book Co., 330 W. 42 St., NYC 18
Send me Marcus and Levy's Elements of Radio Servicing for 10 days' examination on approval. In 10 days I will send \$4.50, plus a few cents postage, or return book postpaid. (Postage paid on cash orders)

Name.....
Address.....
City and State.....
Company.....
Position.....RN-5-48

SUPER-SPECIALS

FROM OUR FREE CATALOG

SCARCE TUBES: 6AC5, 25A6, 25A7, 70L7, 2A7, 79c ea.; 25AC589c
5 TUBE KIT: 50L6, 35Z5, 12SA7-K7-Q7...\$2.75
5 TUBE KIT: 50B5, 35W4, 12AT6-BA6-BE6... 2.75
ACORN TUBES: 954, 955, 956, 957, 958A.....49c
Proximity Fuse Diodes, 6.3 fil.....49c
OZ4: 89c; 1LA6: \$1.09; 2V3G.....98c

TUBE SPECIALS: 69c each, 10 for.....\$6.00
1R5, 1R4, 1R5, 1T4, 3R4, 1V, 6AH6, 6AK5, 6AL5, 6AN5, 6AT6, 6BA6, 6BE6, 6C4, 6H6, 6J6, 6N4, 6N7, 6N1, 12BA6, 12BE6, 12BD6, 12SA7, 25Y5, 50B5, 717A, 9001, 9002, 9003, 9006.

ELECTROLYTICS: Fresh, pop. brand, guar. 1 yr.:
20 @ 150 V.; 25c; 20/20 @ 150 V.....39c
8 @ 450 V.; 28c; 8/8 @ 450 V.....59c
16 @ 450 V.; 49c; 50/30 @ 150 V.....49c

VOL. CONTROLS: 10M, 25M, 100M. ¼, ½, 1 & 2 meq. with sw., 2" Shaft.....ea. 47c

ALNICO No. 5 PM SPEAKERS, heavy magnets:
4 in. \$1.35; 5 in. \$1.39; 6 in. \$2.49; 8 in. \$3.45;
12 in.\$4.95
L-70 Pickup & Crystal Cartridge..... 2.25

LOWEST PRICES ANYWHERE

All Items Unconditionally Guaranteed

WRITE FOR FREE CATALOG

20% Dep., Bal. C.O.D. — Min. Order \$3.00

COMMERCIAL RADIO

Dept. N2 36 Brattle St., Boston 8, Mass.

is charging the fleet owner \$10.00 per month per car covering one monthly preventative maintenance check-up and an unlimited number of emergency calls. Tubes and parts are extra. In another case, the radio firm is charging \$12.00 per month per car, including tubes and parts. A compromise might be considered at \$5.00 per month per car for preventative maintenance, plus an hourly charge for additional service call, plus tubes and parts.

In order to make any money in two-way radio maintenance, it will pay to have the fleet owner purchase at least one spare mobile unit for every ten cars. When a unit needs maintenance, a new unit may be slipped into the car and the radio technician can pick up the defective unit at his leisure. In his shop, he should have test jigs and equipment so he can repair the defective unit quickly so it will be ready as a stand by. Working on the equipment in the car is not only difficult, but also ties up the car.

Most manufacturers will be glad to supply technical information on their equipment to interested radio service organizations. These same manufacturers will also be able to suggest makes and types of test equipment most suited for mobile radio maintenance. If you have personnel, the technical qualifications, and proper licenses, now is the time to investigate this new source of business—two-way mobile radio maintenance.

-30-

Signal Generator

(Continued from page 51)

quency possessing the same stability and accuracy as the 100 kc. standard. At any frequency in the entire range of the instrument the signal may be modulated with an internally generated 400 cycle audio tone. The signal output level is adjustable from a panel control. An output cable brings the signal to where it is needed. The tubes employed in this unit include a 50B5 crystal oscillator, 12AT6 a.f. oscillator, and a 50B5 as a rectifier. The crystal controlled generator operates from a 110 to 120 volt a.c. or d.c. power line.

This unit has many applications. As a source of accurate frequencies for the alignment of radio receivers, the generator can be used for r.f. and i.f. frequencies in the broadcast, short-wave and v.h.f. ranges. Receiver manufacturers can use this crystal controlled source of frequencies as a production alignment tool for fixed frequency stations on the production line. It may also be used as a check frequency source for v.f.o.'s in operation on production or maintenance benches.

As an aid to FM receiver alignment the unit will provide i.f. and r.f. frequencies when crystals of the proper frequencies are employed. For example, with a crystal at 10.7 mc., dis-

THE FOLDED DIPOLE ANTENNA

By EDWARD M. NOLL



THE folded dipole, with equal diameter elements, is a 300-ohm antenna which conveniently matches the standard 300-ohm receiver input and the 300-ohm twin-line transmission line. In addition, it is a broad-band unit which has a uniform sensitivity over a wide band of frequencies. Thus, the folded dipole presents an efficient match and does not detract from the picture resolution. The folded dipole is a half-wave antenna comprising a full wavelength of line bent around to form two parallel lines. Spacing between the elements of the antenna is $\lambda/64$ or less. Dimensions are given in the chart.

Antenna resistance can be varied by changing the diameter of one element with respect to the other. When the

diameter of the fed element is decreased with respect to the other element, antenna resistance increases. If the diameter of the fed element is increased, antenna resistance decreases. Antenna resistance can also be increased by increasing the number of elements.

A folded dipole for temporary or test use can be constructed of 300-ohm twin-wire line by cutting a half-wave section and opening one element at midpoint for feeding as shown in the diagram. Although the antenna is a half-wave long, it must be shorted at the 86 per cent point, as indicated, because of the lower velocity constant of the dielectric. The extremities can be either open or shorted.

CHANNELS	1	2	3	4	5	6	7	8	9	10	11	12	13	L	H
Full-wave A to B	240	197	173	163	144	134	63	61½	59½	57½	55½	54¼	53	168	57½
$\lambda/2$ element	120	98	86	81	72	67	31	30½	29¼	28¾	27¾	27	26½	84	29¾
$\lambda/64$ spacing	4	3¼	3	2¾	2½	2¼	1	1	1	1	1	1	1	2¾	1

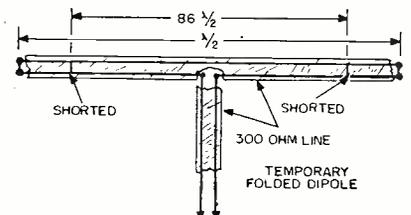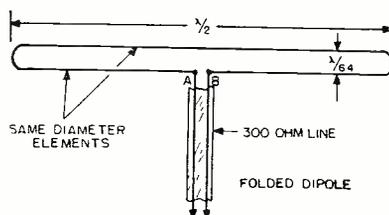

criminator and ratio detectors can be aligned to their respective center frequencies. A 10.8 mc. crystal and one at 10.6 mc. can then be used successively to check the balance in the negative and positive directions, in addition to the band limit amplitudes. The 10th harmonic of the i.f. crystal frequency provides the frequency for the alignment at the h.f. end of the r.f. section of the FM receiver. A 10.8 or 10.6 mc. crystal would be best to use in this case since the 10.7 mc. crystal will ride through the i.f.

For television receiver alignment a group of five crystals can be employed at the five frequencies equal to one-half the frequencies required for stagger-tuned i.f. peaking. RCA receivers are aligned at 21.8 mc., 22.3 mc., 23.4 mc., 25.2 mc., and 25.3 mc. Ordinary peaking methods are employed with an amplitude modulated single frequency at the above points. To use the signal generator in this way five crystals are required; at 10.9, 11.15, 11.7, 12.6, and 12.65 mc. These will double to the desired frequencies. In addition to the above, a crystal for tuning each of the trap frequencies to minimum would be useful. In RCA receivers these frequencies would be 19.75 mc., 21.25 mc., for which the crystal frequencies for doubling would be 9.875 mc. and 10.625 mc. Each crystal is inserted in the front panel receptacle as it is needed, and no further adjustment of the generator is necessary, except, where required, to lower or raise the output level with the control (*R_c*) provided. Where peaking adjustments are being made, the set is trimmed for maximum detector output (or a.v.c. voltage) at each of the peak frequencies and when trap adjustments are made the traps are tuned for minimum output at the trapped frequencies. The 10.625 mc. frequency can be used for sound i.f. alignment at 21.25 mc.

With a crystal at 100 kc. this unit can be used as a secondary standard. Aligned by zero beating against WWV at 2.5 mc. or at 5.0 mc., the 100 kc. frequency can be used as a direct source of harmonics at 100 kc., or, as a sync generator for a multivibrator. A similar application for higher frequency use would employ a 1000 kc. crystal or one at 5.0 mc. or 10 mc. In each instance, after alignment by the zero beat method against WWV's standard frequency transmissions, harmonics of the fundamental crystal frequencies can be used up into the v.h.f. region.

Television receiver local oscillators can be adjusted to their proper fixed frequencies for each channel by use of crystals at a lower frequency with a harmonic at the desired frequency. For example the channel 4 local oscillator in recent RCA receivers is set at 93 mc. by zero beating it against the 10th harmonic of a 9.3 mc. crystal. A prewar television receiver would have a channel 4 local oscillator setting of 80 mc. This can be adjusted against the 10th harmonic of 8.0 mc. or 8th harmonic of 10 mc.

-50-

May, 1948

Modern Hams Junk Old-Style "Cans"!



First basic improvement in headset design in 50 years

TELEX MONOSET

- Gives clear, crisp "near as here" reception
- Blocks outside noise
- Eliminates that "top-heavy" feeling
- Ends headachy ear pressure

Man, what relief to get rid of those pressure headaches from old-style earphones!

The TELEX MONOSET swings lightly under the chin like a stethoscope—never gets in your hair! The TELEX MONOSET delivers the signal into the ears, excludes all room noise automatically. The TELEX MONOSET gives undistorted output at maximum volume... plenty of "sock" easily adjusted with the built-in volume control.

Modernize your rig with a MONOSET
—successor to the earphone! Write
Department BT for information.



Canadian Distributors
Sono Film, Ltd., Winnipeg

QUANTITY SURPLUS BUYERS

We Offer Quick Delivery On Your Largest Orders.

Our large inventory of electronic equipment and parts includes many of those hard-to-get items. Much of our stock is stored in Eastern warehouses, affording quick, low-cost delivery of large orders. Send for latest inventory lists (use your business letterhead, please). Phone and telegraph inquiries invited. Liberal quantity discounts allowed.

WE HAVE A LARGE STOCK OF RUBBER COVERED MULTI-CONDUCTOR CABLES - ALL WIRE GAUGES - ANY NUMBER OF CONDUCTORS - SHIELDED, UNSHIELDED



G. & M. EQUIPMENT CO., Inc.

4505 VAN NUYS BOULEVARD • VAN NUYS, CALIFORNIA • STATE 4-3233

POCKET FAST EASY

EXTRA PROFITS

Selling and Installing


Autone AUXILIARY SPEAKER



Sales will soar to new highs when you display the NEW AUTONE AUXILIARY SPEAKER.

More than 25 million auto-ists in the United States are ready prospects! They want the full, rich "Living Room" reception that an auxiliary AUTONE will give their car radios; they want the inexpensive luxury of a rear seat, separately controlled radio speaker, the pleasant, safe convenience of complete reception at low level volume. The New AUTONE is a high quality speaker. Show it in your store with our dealer aids, and it will sell itself. Your service department, too, will reap extra profits through installations of these popular units. Easily, quickly installed. Retail at \$9.95 complete with switch, cable, etc., plus installation. Long discount, big markup for you. Contact your jobber TODAY or write us direct.

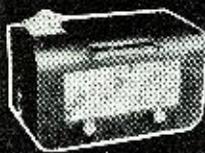NORTHERN PRODUCTS CO.
6349 N. Clark St., Chicago 26, Ill.



STEADY PROFITS

YOUR OWN BUSINESS

with **CORADIO**

THE COIN OPERATED RADIO

Place these specially built radios that play 1 or 2 hours for 25c in the thousands of available hotel rooms, tourists courts, etc. They yield immediate profits and steady income. Install Coradio, the finest made.

Limited capital required. Send for further information. Write today.

CORADIO Coin Operated Radio
Dept. R. N. 108 W. 31 Street, New York 1, N. Y.

Technical BOOKS

"PREPARING FOR FEDERAL RADIO OPERATOR EXAMINATIONS" by Arnold Shostak. Published by *Prentice-Hall, Inc.*, New York. 384 pages. Price \$3.75.

This handbook is both concise and authoritative. Written by a former radio inspector for the Federal Communications Commission, this text is prepared in the familiar "question and answer" form. The book is divided into six elements corresponding to the elements encountered in the FCC examinations.

Representative questions, along with the correct answers, are included under each element. In some instances where the answer is long and relatively complicated, shortened versions of the replies are also given.

Three appendices have been included covering rules governing commercial radio operators, extracts from the Communications Acts, and a table of abbreviations.

Replies to the technical questions are fairly complete and include the necessary mathematics.

This book is admirably suited for home study by prospective licensees and applicants for a renewal of FCC licenses.

* * *

"TELEVISION PRIMER ON PRODUCTION AND DIRECTION" by Louis A. Sposa. Published by *McGraw-Hill Book Company*, New York. 226 pages. Price \$3.50.

This is a practical "how-to-do-it" handbook for video program technicians; directors, makeup and wardrobe personnel, lighting men, etc.

Mr. Sposa, who is Director of Commercial Operations for station WABD, has drawn on his long and varied experience in the field in preparing this handbook. Detailed discussions cover all phases of television entertainment including programming, scenic designing, lighting methods, art work, titles, video effects, microphones and their use, televising motion pictures, etc.

The book is clearly written in non-technical language and is lavishly illustrated with studio shots and line drawings. This text should prove valuable to personnel of both new and established video stations as well as students in training for careers in television.

* * *

"FM TRANSMISSION AND RECEPTION" by John F. Rider and Seymour D. Uslan. Published by *John F. Rider Publisher, Inc.*, New York. 404 pages. Price \$1.80 paper.

This book has been divided into two main sections dealing with FM transmission and FM reception. The authors have provided a detailed explanation of the equipment and techniques used in

transmitting FM program material including transmitting antennas.

While this material provides an excellent background for the all-around technician, servicemen will undoubtedly find the section dealing with FM receiving equipment of more immediate value. Receiving antennas are covered in some detail in a separate chapter with consideration being given to half-wave dipoles, folded dipoles, dipoles with reflectors, and other types of FM receiving antennas.

The chapter dealing with FM receivers discusses the similarities and differences between AM and FM receivers, the r.f. stage, mixer-oscillator and converter systems, sensitivity and selectivity, the i.f. system, demodulation-detection, the limiter stage, the discriminator detector, the double-tuned discriminator, the phase discriminator, the ratio detector, a.v.c. from ratio detectors, oscillator detectors, comparison between detector systems, the audio system, and FM tuners.

Servicemen will welcome the chapters dealing with the alignment and servicing of FM receivers. Procedures are carefully outlined and complete details for performing the various operations are given. An appendix covering vectors, powers of ten, the FreModyne circuit, FM ground wave signal range, i.f. response curves and a reactance tube chart provide a handy reference for the serviceman.

Since the inclusion of mathematics has been limited to the barest essentials, this book may be used by the student and for self-instruction.

* * *

"BROADCAST OPERATORS HANDBOOK" by Harold E. Ennes. Published by *John F. Rider Publisher, Inc.*, New York. 262 pages. Price \$3.30.

This book meets a long-felt need for a practical working guide for broadcast station engineers. The material is designed and written to be used either by the student engineer or by the "old hand" who would like to learn better ways of doing his job.

The text is divided into six parts, a bibliography, and an appendix. The first four parts of the book deal with operating practice in control rooms, the master control, remote controls, and the transmitter. The fifth and sixth parts are technical in nature and provide technical data for operators and technicians. A particularly valuable chapter is devoted to preventive maintenance.

Since this book is written by an operator, for operators, the style is informal and couched in operating language. Those of our readers who have read Mr. Ennes' articles in the RADIO-ELECTRONIC ENGINEERING edition of RADIO NEWS already know and appreciate his lucidity and grasp of his subject.



TRIPLE BONUS

the **GREATEST**

Yes! the **GREATEST**

TEST EQUIPMENT

Story Ever Told

1000 pieces of LATEST MODEL, Standard Brand Test Equipment to be sold this month. TUBE CHECKERS, SIGNAL GENERATORS, OSCILLOSCOPES, VTVM's, MULTI-TESTERS, etc.

LABORATORIES, SCHOOLS, RADIO DEALERS, SERVICE MEN, HAMS, EXPERIMENTERS, STUDENTS:

Get a TRIPLE BONUS on EACH piece of equipment valued at \$40.00 or more. Just fill out the coupon below. Act now!



Store
149 Riverdale Ave.
Yonkers
New York

Store & Warehouse
143 West End Ave.
New York 23
New York

RADIOMART Dept. RN-5
149 Riverdale Ave., Yonkers, New York

I am interested in learning more about the greatest test equipment story ever told. Please send details of your great triple-bonus plan. I am particularly interested in buying the following equipment:

Name

Address

- Laboratory
- School
- Radio Dealer
- Service Man
- Ham
- Experimenter

Now You Can Sell SEEBURG RECORD CHANGERS

This is *really good news!* These are the same Seeburg mechanisms that are standard equipment on many of the finest combination instruments.

When you sell a Seeburg Home Record Changer—as a replacement or for playing through an existing radio—customer satisfaction is complete. Because when the changer is a Seeburg, you can count on simple, dependable operation . . . constant, sustained speed . . . quiet performance . . . the last word in listening pleasure.

Take advantage now of this profitable, good will building business. *Mail the coupon today!*

For Replacement



Model DR-1. Two-post construction. High or low output cartridge. Size: 13 1/4 x 13 1/4 inches



Model DS-1. Single-post construction. High or low output cartridge. Size: 12 x 13 3/8 inches

For Playing Through Existing Radios



Model DR-101. Same chassis as DR-1 with walnut finish wood base. Size: 13 3/4 x 13 3/4 inches



Model DS-101. Same chassis as DS-1 with walnut finish wood base. Size: 12 1/2 x 14 1/8 inches.



Seeburg Home Record Changers are available through our nation-wide distributing organization located in all principal cities.

J. P. Seeburg Corporation
1500 N. Dayton St., Chicago 22, Ill.
Gentlemen: Please send complete information on Seeburg Home Record Changers.

Name.....
Company.....
Address.....
City.....State.....

HIGH FIDELITY AMPLIFIER KIT MODEL "CONCERTO"

This kit is a unit of highly advanced design which will meet the exacting requirements of the most discriminating music lover.

This famous reproducer uses eight tubes in a new circuit design, and the first kit available to the public using the *Cathode Follower* output circuit. This circuit provides remarkable transient response and improves the performance of the loudspeaker itself by heavily damping its resonances.

A very carefully designed tone control system permits separate control of treble and extreme bass registers and while bass boost is substantially greater than with conventional circuits, it does not affect the middle register.

This amplifier accommodates both high and low gain pickups. Incorporates special circuits for G.E. reluctance pickups. Can be used with any microphone or tuner. Complete with tubes, sensibly priced at **\$32.95**



Kit Model 210 A Three Way Portable Receiver

Operating on either AC or DC or self-contained batteries . . . power switch conveniently located on front of set so that "battery" or "AC-DC" may be selected without opening case. Five-

inch Alnico 5 permanent magnet dynamic speaker, and case covered with beautifully grained leatherette. Price of model 210 complete with tubes **\$18.95**



Multimeter Kit Model M-3C

A versatile, compact multimeter 4" x 7" x 3" using a 3 1/2" rd. meter of 1000 ohms per volt sensitivity. Employs the following ranges: Volts AC or DC 0/5/50/150/500/1500. Milliampers DC 0/5/50/150. Ohms

0/2000/20,000/200,000. Price complete **\$10.95**

All kits accompanied by a detailed, illustrated instruction sheet. Many other kit models available. Write for catalog K.

RADIO KITS COMPANY
120 Cedar Street New York 6, N. Y.

Within the Industry

(Continued from page 30)

the aptitude and experience of the usual plant maintenance personnel.

An Engineering Department is also maintained to conduct electronic research and development and to perfect new test equipment and techniques as they are developed.

This organization operates nationally and has 10 district offices located throughout the United States.

* * *

A. M. SKELLETT, Director of Research for *National Union Radio Corporation*, Orange, New Jersey, has been appointed Vice President in charge of the Research Division.



Dr. Skellett joined the Research Division of *National Union* as Chief Engineer in 1944 after spending 15 years as a member of the technical staff of the *Bell Telephone Laboratories*. He is a consultant to the Research Development Board in the Department of National Defense of the Federal Government.

* * *

ROBERT J. HARRINGTON has been appointed Assistant Director of Sales for *Industrial Television Inc.* of Clifton, New Jersey.

Prior to joining *Industrial*, Mr. Harrington was Secretary-Treasurer of *American Time Corp.* of Springfield, Massachusetts. He was formerly associated with *Allen B. DuMont Laboratories, Inc.*

In his new post Mr. Harrington will act as assistant to Edwin C. Hinck, the company's Sales Director.

* * *

ROY BROWN UNGER of the *Ward Products Corporation*, manufacturers of radio, television, and auto antennas, has been promoted to the post of sales manager.



Mr. Unger, who served as a first lieutenant of artillery in the Pacific area, was formerly assistant sales manager of the jobber division of *Ward Products*.

Among Mr. Unger's new duties will be an advertising promotion campaign for the company's new FM and television aerial line.

* * *

DR. W. R. G. BAKER, of the *General Electric Company*, representing the Radio Manufacturers Association, was elected vice-chairman of the Electrical Standards Committee of the American Standards Association. Charles R. Harte, of the *Connecticut Company*, New Haven, Con-

necticut, representing the American Transit Association, was re-elected chairman of the committee.

The Communications and Electronics Section will be under the chairmanship of Dr. Baker while the Power Section will work under the chairmanship of Sidney Withington, chief electrical engineer, *New York, New Haven & Hartford Railroad Company*.

The Electrical Standards Committee of the American Standards Association is the central body for standardization in the United States in the electrical, communications, and electronics field.

New members of the Executive Committee and their organizational affiliations are: L. F. Adams, *General Electric Company*, (NEMA); P. H. Chase, chief engineer, *Philadelphia Electric Company*; L. J. Cumming, technical secretary, IRE; J. J. Pilliod, assistant chief engineer, *American Telephone and Telegraph Company*, (A.I.E.E.); Colonel L. J. Tatom, Commanding Officer, Army Electronic Standards Agency; and C. R. Welborn, executive vice-president, *Underwriters' Laboratories*.

-50-

Recording of Sound

(Continued from page 61)

R^{22} appears, a negative voltage is applied to the grid of V^2 , tending to reduce the transconductance of the tube and reduce the magnitude of the degenerative voltage in its plate circuit. This means that a large input signal to the noise suppressor will produce sufficient negative voltage on the grid circuit of the reactance tube to lower the effective gain and the magnitude of the degenerative voltage in its plate circuit. For this reason the circuit is effectively tuned to a higher frequency when the tube is shifted toward cut-off. These same principles apply to the low frequency reactance tube V^3 except that the signal applied to its grid is produced by a network consisting of a shunt capacitance C^{10} and the resistor R^{14} . This produces a predominance of low frequencies in the grid circuit and a corresponding low frequency degenerative signal in the plate circuit.

The inductance CH^2 is selected to make this circuit resonate sharply to produce a sharp cut-off instead of the roll-off that would be obtained with only an effective shunt capacitance, represented by the reactance tube V^2 .

S^1 is used to eliminate the 10 kc. filter under conditions of no suppression and opens the cathode circuit of both reactance tubes, cutting them off completely and eliminating any effect from them. Thus the circuits are virtually eliminated under conditions of "no suppression". In tuning these circuits the procedure is to switch S^1 to the "on" position and unsolder the lead from the

WAR SURPLUS



TERRIFIC BARGAINS DYNAMOTORS

BRAND NEW G.E. 485 KVA. Input 27V D.C. output 115V. A.C. in original packing. Ea. **\$4.50**
New Dyn. Type S-3416. Input 9 V. output 400 V. 7 Amps and .08 Amps. Ea. **\$1.50**
Dyn. new, Type D. Model No. 5D48b9A. Input 20 amps. Output 350 Ma at 1000 V.D.C. Mfg. by G.E. Ea. **\$4.95**

Dyn. new, Model 23350, R/A. Input 27V D.C. 1.75 Amps. Output 235V D.C. .075 Amps. Ea. **\$1.75**
Dyn. new, Type DY-22/Arc .3V. Input 28V D.C. Output 210V D.C. Duty Cont. **\$1.95**

NEW G.E. SELSYN CONTROL TRANSFORMERS Model No. 2J1G1, 57.5V. 400 cy. Ea. **\$1.00**

NHW RADIO RECEIVER, BC-AC-229, aircraft type size 13"x6"x6 1/4", Ea. **\$3.95**

NEW RADIO RECEIVER U.S. Army, BC-341-A size 6 1/4"x3 3/4"x5" Ea. **\$3.50**

RADIO CONTROL BOX, U.S. Army with 3 positions selective switch, volume control. Ea. **.50c**

JACK BOX new, BC-366, USA signal corp. with 5 positions selective switch, volume control. Ea. **.50c**

RADIO FILTER new FL-S-A. ea. **.75c**

Adel Clips No. 8, 5 doz. for **\$1.00**

ATTENTION, Experimenters, Inventors, Lab. workers

NEW ELECTRIC GENERATORS, While they last

15V., 50 Amps RPM 4200, Mfg. by Bendix, Wt. Approx. 40 lb. Ea. **\$10.00**

GENERATOR NEW, navy type, output 430V D.C. 8g Watts, RPM 3450, Ea. **\$10.00**

Send Check or Money Order no COD's

GENERAL SALVAGE COMPANY

Dept. 5, 2920 E. 27th St.

KANSAS CITY, MISSOURI

bottom part of S^1 that goes to R^{10} . This leaves the series filter in the circuit but eliminates the reactance tubes. Now, feeding an oscillator (set to 10 kc.) into the input of V^1 , tune C^2 for a maximum dip at 10 kc. Next disconnect R^4 from the plate of V^1 , switch S^1 to the "on" position, reconnect the lead from R^{10} to the bottom part of S^1 , and connect a temporary short across the upper terminals of S^1 (across C^2) thus eliminating the 10 kc. filter but making the reactance tubes effective.

With R^5 set for minimum resistance in the circuit and the oscillator set for approximately 4500 c.p.s., tune C^8 for a maximum dip at this frequency. An output meter may be used for this purpose but it is better to observe the output on an oscilloscope. Now it will be found that adjustment of R^5 to introduce an increasing amount of resistance in the circuit will effectively tune the maximum attenuation dip toward higher frequencies. This adjustment is used in operating the Dynamic Noise Suppressor to determine the frequency where the gates cut-off when they are closed completely. With very good records this control may be operated with almost a maximum of resistance introduced so that the cut-off even when the gates are closed will be above 4500 c.p.s. while with very poor records it will be desirable to operate the control for minimum resistance so as to cut off at lower frequencies. This control may be ganged with S^1 although this is complicated by the availability of suitable components. Under conditions of no suppression, S^1 of course should be used in the "off" position.

In order to observe the operation under effective dynamic conditions, it is necessary to employ two oscillators. One oscillator is fed into the input of the 6B8G and the other oscillator is connected between R^4 (at the point where it was previously disconnected from the plate of V^1) and the cathode of V^1 . Now with the output of the oscillator which is connected to R^4 , set at zero, the oscillator fed to the input of V^1 is adjusted to provide a signal at, say, 4500 c.p.s. with S^1 in "off" position. With R^5 set for minimum resistance in the circuit, switch S^1 to the "on" position. If the output is observed on an oscilloscope during this procedure the signal will be observed to be greatly attenuated when the switch is operated as indicated.

The output of the oscillator connected to R^4 should now be adjusted to approximately 2000 c.p.s. and the output level slowly increased. It will be seen that this will effectively drive open the gates and bring the 4500 c.p.s. signal back in the direction of no attenuation.

The point at which the noise suppressor circuits are connected in any given

Take 'em Away!!!

DYNAMOTORS

Model 515 Transmitting: Output 500 V. @ 50 Ma., \$2.69; 2 for.....\$5.00
 Model 516 Receiving: Output 275 V. @ 110 Ma., \$1.69; 2 for.....3.00
 One of each type.....4.00
 Input: 12 to 24 VDC (Navy Type). These are high efficiency units using PM Fields. May be used on 6 V. input with half of the above output voltages.
 DM-416 Input: 28 V. @ 3.1 Amps. Output: 330 V. @ 170 Ma. (Navy Type). Filter assembly in base. Mounting included. New.....\$1.49

VIBROPACK

PE-125 BX for SCR-223. Input: 12 or 24 V. Output: 475 V. @ 200 Ma. A heavy duty unit built for continuous service. Complete with 2 RK-69 Rectifier tubes, Spare Ignitor, Shock Mount and Plug. Ideal for Mobile installations on cabs, trucks, buses, etc. New. Ready for operation.....\$8.95

METERS (Name Brands—New and Like-new)
 0-500 Ma DC 3" Round.....\$1.49
 0-500 VDC @ 1000 ohms per V. 3" Round.....2.49
 0-10 output units (1.25 Ma. F.S.) in wood case.
 2 1/2" Bakelite case (Less thermal unit).....2.19
 0-15 VDC @ 100/opr 2 1/2" Bakelite case......98
 0-50 Amps. DC (less shunt) 2 1/2" metal case (P.S.—50 MV).....1.49
 20-0-20 Amps. Charging Meter 2 1/2" metal case.
 With mounting bracket......69

TELETYPE METERS

Bias Meter I-97A-Zero center, 3" Bakelite case. Reads 115 VDC and 100 Ma + or —. Mounted in sturdy steel case. 5" H., 7" L., 4 1/2" D. Contains cond., trans., plugs, cords and many useful parts. Diagram included. A giveaway.....\$4.95
 Line Unit BE-77-B Same meter as above. Mounted in slotted brass steel case. 5 1/2" H., 8" L., 6" W. Diagram etched on side. Operating instructions on opposite side. Contains switches, relays, precision resistors and many useful precision parts. Just.....\$6.95

POTENTIOMETERS (Name Brands)

Dual Unit. Wirewound, with dial plate and knob. Front section: 1200 ohms @ .35 Amps. Rear section: 3 ohms @ 4.7 Amps. Air-cooled. Includes mounting bracket. New.....\$1.29
 Dual Unit. Carbon. 4 meg each section. Shaft extends 3/4". Standard 3/8" mounting......49c
 DUAL. Carbon. 100,000 ohms each. Shaft protrudes 1/4" slotted for screwdriver adjustment......39c
 Four Gang. Carbon. 1" shaft. Front to back: 6000; 2500; 30,000; 30,000 ohms. Well-made. Sturdy construction. Aircraft type. 1000 ohms wirewound. Enclosed in heavy cast aluminum case. 1/4" shaft. Amphenol connector terminals. Only......49c
 Rheostat. 90 ohms baked enamel wirewound. Air-cooled in metal case. 3/8" Mtg. 1/4" shaft. 1" long. 0.35 Amps. NEW only......59c
 Stage Dimming Rheostat. Heavy duty. L. Asbestos baked element. Tap-switch type. Rated 8 to 25 V. @ 11 Amps. Overall dia. 9. Depth 5". Complete with knob and panel plate. Slightly used.....\$2.69

TG-10 PHOTO ELECTRIC CODE KEYS

A heavy duty unit which may be easily converted to a beautiful high fidelity 25 Watt amplifier for Mic. and Phono. Has complete 110 VAC power supply. Uses 2-6S7, 2-6N7, 2-6L6 and 1-5174G tubes. (less tubes, tapes or reels.) Like New.....\$19.95

TURNTABLES

10" for G.I. phono motor. Brand New.....39c

PL-68 MICROPHONE PLUGS

3 contacts. Specially priced.....3 for 29c

ALUMINUM RIVETS

Assorted.....Lb. 75c

★ Write for FREE copy of UNITED SURPLUS 1948 CATALOG

- Quantities are limited—Order Now! Prices subject to change without notice.
- Minimum order—\$2.00; 25% Deposit Required. Balance C.O.D. All orders shipped f.o.b. Chicago.

UNITED SURPLUS MATERIALS

3313-19 W. OGDEN AVE.

CHICAGO 23, ILL.

Radio Technician and Announcers

A practical 15-month course in First Class Radiotelephone Operation and Announcing is offered by Don Martin School of Radio Arts. Most stations these days require combination men. We specialize in this type of training and maintain a placement bureau for our graduates. Serving the industry for 10 years, the School of Radio Arts can train you. Write for our catalogue outlining the courses offered. Classes can be arranged so you can do part time work on the side.

APPROVED FOR VETERANS

DON MARTIN SCHOOL OF RADIO ARTS
 1655 North Cherokee St. Hollywood 28, Calif.

Serving Radio & Appliances

SERVICE DEALERS

FROM COAST TO COAST

4 JOB CARDS

ASK FOR SAMPLES RADIO PRESS MORGANTOWN WEST VIRGINIA

LOOM

Weather-proof. Heavy fabric. Ideal for sleeving on TV. or FM. lead-ins, thru skylights or around corners. Inside dia. 1/4", 1/2", 3/4", 1" (specify size). Minimum order 50 Feet. Any size.....50 Feet \$1.45

COMPASS REMOTE CABLES

Used with MN-26, BC433G, RA-10, etc., 20 Feet long. Has spline couplings on both ends. New.....\$2.39

HOOK-UP WIRE

Assorted colors, lengths and gauges. Lb......75c

RELAY RACK PANELS

.051 thick, hard aluminum, standard notched. 19"x 10 1/2" (unfinished).....Each 69c

COAX CONNECTORS

10 assorted. Standard types.....\$1.49

HEADSETS

HS-30 Ear plug type. Complete. Pair......98c
 HS-16 Standard makes (slightly used) Pair......98c

PULSE TRANSMITTER—RADAR

ASB-5. 800 cye. power supply. Uses 1-15R and 4-15T tubes. A great parts buy! Includes Tubes! Like New.....\$9.50

BC-729C ANTENNA TUNING UNIT

For BC-610 Transmitter. (less condenser and case) A few left. Just.....\$7.95

B.C. 454-B RECEIVERS

3-6 Mc. aircraft receiver. Like New.....\$4.95

WAVE GUIDES

Fine milled. Silver plated. Slate gray finish. 5 foot lengths with connector at each end. Approx. 3 cm. Per foot......75c

TUNING ASSEMBLY

Contains 2-Pt-243 crystals; 3245 KC and 3700 KC (can be used on 10 M. phone) 2-coils, 1-140 mmf. Variable air trimmer, dual xtal socket and case. A Super Value......95c

MT 5/ARR-2 SHOCK MOUNTS

To fit single receiver rack of 274-N series. New. Each 59c; 2 for.....\$1.00

SCR-522-VHF TRANS. & RECVR.

The Hams' dream on 2 meters! Ask the man who owns one. Our units are in wonderful condition. Like new, with tubes and two power plugs. Just.....\$19.95

HEAD AND CHEST SET

New. Boxed. Well-known brand. Each.....\$1.79

AS/ARN-5 ANTENNA

New. Each.....\$2.95

TRANSMITTING CONDENSERS—Fresh Stocks

Leading Brands!

4 Mfd. 500 VDC Size: 1 1/2"x1 1/2"x1 1/2" Can. Each......69

1 Mfd. 2000 WVDC Size: 1 1/2"x2 1/2"x5" Can. Each......179

3 Mfd. 2000 WVDC Size: 1 1/2"x3 3/4"x5 3/4" Can. Each......235

5 Mfd. 2000 WVDC Size: 2 1/2"x3 3/4"x5 3/4" Can. Each......439

1 Mfd. 6000 WVDC Size: 2 1/2"x1"x9" Can. Each......595

★ ★ THIS MONTH ONLY ★ ★

UNITED SURPLUS Surprise "Package".....\$1.29

More than 10 Lbs. of assorted electronic units and parts.

More than 10 Lbs. of assorted electronic units and parts.

More than 10 Lbs. of assorted electronic units and parts.

More than 10 Lbs. of assorted electronic units and parts.


WAR SURPLUS

BRAND NEW
A New Supply of Sperry A-5
Automatic Pilot Components

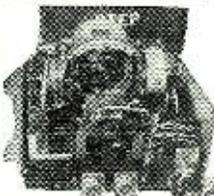VERTICAL
GYRO UNIT
 Originally
 Cost \$2855.00
NOW ONLY
\$14.95



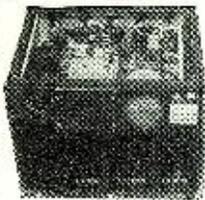Aluminum housing • One 400-cycle, 115-v., 3-ph. Motor Propelled Gyro • Two 24-v. DC shunt-wound motors • 2 Electronic Relays • Auto Transformer • Hundreds of precision parts • 35 lbs.



AMPLIFIER
RACK
 With Relays
 and Meters
Only \$6.95

- Mag. Cabinet • 7 DPDT Allied Relays
- 1 SPST Relay • 1 Weston 0-125 AC Volt Meter
- 1 350 to 450-cycle Frequency Meter
- 1 115-volt, 400-cyc. Transformer
- And many other parts • 25 lbs.

Special! Combination Offer!
VERTICAL GYRO and Together at
AMPLIFIER RACK \$19.95

You pay shipping costs. Send check or money order to

SURPLEX RETAIL SALES INC.
 2409 S. LaSalle St., Chicago 16, Ill.
 Dept. RN-5 Phone CALumet 9130

Prepare For A Good Job Now in

RADIO

SOUND and TELEVISION

LEARN QUICKLY IN
 THE GREAT SHOPS OF
COYNE

NOT A "HOME STUDY" COURSE

Get ready for a better job, bigger pay NOW in Radio. Cash in with "All-around" knowledge of Radio—Sound—Television. Train on actual equipment not by "Home-study". You learn quickest at COYNE because it's a real SHOP course!

G. I. APPROVED... also Finance Plan for NON-VETERANS. Don't let lack of cash hold you back. Many earn while learning. FREE Employment Service to graduates. Get facts today!

SEND COUPON FOR FREE BOOK

Send at once for Big Free Book on Radio, Sound and Television, and facts about our Finance Plan.

MAIL THIS COUPON TODAY

B. W. COOKE, Pres.,
Coyne Electrical and Radio School
 500 S. Paulina St., Dept. 58-1K, Chicago 12, Ill.

Please send Big FREE Book and complete details.

NAME
 STREET.....
 CITY..... STATE.....

amplifying system is, of course, extremely important. If they are connected too near the input and with excessive gain following them, the hum pickup from the inductances may be amplified to an irritating level. If they are connected too far back in the amplifier, the drive to the grids of the reactance tubes may introduce distortion. If the drive to the reactance tube grids is too high, a certain amount of grid rectification will take place with serious distortion. This may be readily observed on the oscilloscope by observing the output in the attenuated regions blown up sufficiently on the screen to see the waveform.

If the circuits are properly adjusted, there will be no observable distortion at any frequency. If the gates are being overdriven, the waveform in some sections of the attenuated region will be seriously distorted. This distortion will be evident under conditions where the gates are driven partially open by a control voltage, but will not appear when the gates are driven fully open. Such an indication clearly shows the introduction of the distortion by the gate tube circuits. If the input signal is of the correct magnitude, this will not be observed and the signal will be entirely clean in all sections of the spectrum under all conditions of gate circuit operation.

It will be clear that this distortion is not a problem of the same kind that is introduced in various volume expander circuits where a variable mu tube is used as an amplifier. The function of the reactance tube circuits is concerned with the proper *percentage* of the signal being fed to the grids and the principles will hold for any given amount of signal supplied, provided it is not so high as to cause grid circuit rectification. Consequently, the operating point with regard to signal amplitude may be chosen to preclude the possibility of distortion on peaks and yet be sufficient so that excessive amplification is not needed in following circuits. This condition is also less troublesome because on peaks where distortion might be otherwise introduced (if the choice of signal amplitude is not optimum) the gates are driven open and the reactance tubes effectively made inoperative. Then any distortion that might be present is observable only under conditions of attenuation. This is not intended to indicate that the distortion introduced by an excessive signal level to the gates is unimportant, but that it is not always easy to observe and should be watched for and investigated with care.

This version of the Dynamic Noise Suppressor will provide, with optimum adjustments, satisfactory operation out to approximately 6000 cycles. If it is desirable to increase the roll-off, where the majority of records played have un-

usually poor signal-to-noise ratios, a small condenser may be inserted from the junction of R^6 and R^7 to ground. This may approximate 250 $\mu\mu\text{fd}$. and will also aid in holding down any tendency of the resonant circuit to permit a rise above cut-off. If it is desirable to broaden the response range, an additional reactance tube may be used instead of this condenser and the values may be approximately the same as those for V^2 .

The inductance CH^2 is not necessary in such a circuit. If very wide range response is desired, additional complete filter sections may be added, tuned to increasingly higher cut-off frequencies. In either case the control voltage to these additional circuits may require an additional section of filtering in order to eliminate possibilities of in-phase signals to the grids of the reactance tubes, producing oscillation or distortion. Abrupt surges in the plate circuit of the low frequency reactance tube may appear in the output of the amplifier, if the low frequency response is extremely good and this may be minimized by the choice of value for C^{12} or other coupling condensers. If it is introduced by the filtering characteristics of the control circuits, it may be controlled by an additional filter section. Resistors R^{23} and R^{22} determine the closing speed of the gate circuits and may be changed in value by the individual designer in order to produce faster or slower closing of the gates. These may be reduced to as low as one megohm or even a half megohm. Optimum values will depend to some degree on the taste of the listener, the importance of reverberation in the type of recordings most played and the signal-to-noise ratios of the average records to be reproduced.

Volume Expansion

If the reactance tube circuits are adjusted so that the effective "Q" of the circuit is poor, there will be a large resistive component. This means that the shunting effect of the circuits under conditions of closed gates will be apparent to some degree at all frequencies. Consequently, when the gates are driven open the response at all frequencies will be increased to some degree. This effect may be deliberately introduced to produce volume expansion. One way to accomplish this is to change the resistor from screen to ground in the low frequency reactance tube circuit. Adjustment of the screen voltage for maximum "Q" is fairly critical. In general, it is desirable to minimize the effect of volume expansion to 2 db. or less. The effect may be deliberately introduced by inserting a potentiometer in place of the screen-to-cathode resistor. The value should be around 10,000 ohms and varying this resistor will produce varying

degrees of volume expansion. As much as 15 db. may be obtained. The expansion will take place simultaneously with the opening of the gate circuits. In these circuits it must be remembered that a really complex effect is obtained if the frequency response and over-all amplitude is being expanded simultaneously. The desirability of this effect, except in very limited amounts, is questionable.

Although this version of the Dynamic Noise Suppressor does not permit sufficiently broad-band response to provide maximum frequency response from transcriptions and commercial pressings of exceptional quality, it does permit superior results on average records over what may be obtained with conventional tone controls. Most commercial records do not have appreciable response in the very high ranges. If it is borne in mind that many very high quality theater sound systems are not required by the signal available to reproduce frequencies beyond approximately 7500 c.p.s., and that music reproduction in high quality theater installations from sound on film is considerably closer to reality than the very great majority of phonograph record reproducers, it will be evident that a system capable of actually reproducing a flat response to 6000 c.p.s. with contribution beyond this frequency, and a minimum of noise, will do a very satisfactory job of reproducing most records, and will be very much superior to the average commercial machine that cuts off abruptly at 4500 c.p.s. in order to minimize noise.

Most of the component parts values are critical, particularly the chokes, CH^1 and CH^2 . Therefore, no attempt should be made to substitute either tubes or parts.

Some practice in using the Dynamic Noise Suppressor will be necessary in order to take full advantage of the results it is capable of giving.

(To be continued)

TV OUTPUT UP

OUTPUT of television receivers for February reached a new high of 35,889, according to data released by Radio Manufacturers Association on production by member-companies.

This tops the previous high of 30,001 reached in January of this year. Total production of television receivers since the war now numbers 250,937 units.

More than two-thirds, or 25,594 of the February TV set production were table models, the remainder being consoles and radio-phonograph combinations.

FM-AM receivers reported by member-companies for February totaled 140,629 or an increase of 4614 over January, but still below the monthly average of the last quarter of 1947. About 36 per-cent of the FM-AM units were table models and converters.

Over-all set production by member-companies reached 1,379,605 units of all types in February.

May, 1948



A Sensational New Invention That Will Revolutionize Television: A Liquid Magnifying Lens Using New Patent Principle Allowing Vision From Any Angle Up To 180°

"ALL-VUE" LENS


Front view of the remarkable, new "All-Vue" liquid lens. Actually makes a picture size equivalent to a 15" tube on a 10" set **without conversion**. Gives results never obtained before. Now you can watch television for hours without eyestrain. Picture can be seen from all sides.

"ALL-VUE" available on order only.

Prices on request.

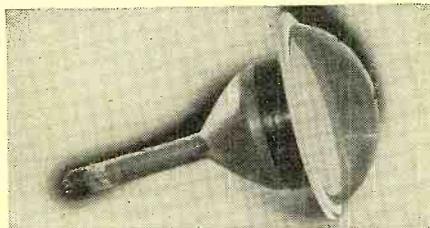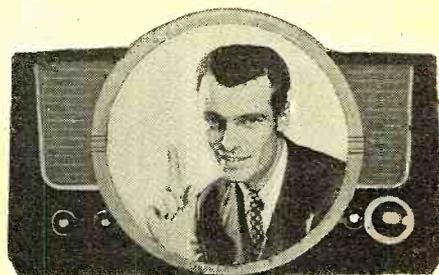

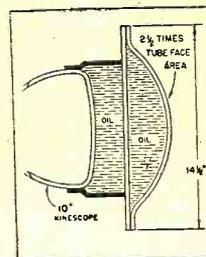The Liquid Lens Corporation magnifier. The black collar connects the kinescope with the lens. Space between the fluorescent screen and magnifier screen is filled with oil.



Cross section sketch of the coupling arrangement and oil chambers of the liquid lens.

For additional information and descriptive literature, write to LIQUID LENS CORP.

Our Stock Line of 80° Hang-on Lenses Available Now For Immediate Delivery!

RCA 630	Crosley 10" Table Model	Motorola VT71 (7") 10" Console
8TS30	Philca 1000	Belmont 7" Table Model
721	1001	Admiral 10" Console
621 (7")	700 (7")	Fado 10" Table Model
721 TCS	10" Console	deWald 10" Table Model

Lenses for most other popular sets on order

All 10" lenses...\$19.95 • All 14½" lenses...\$29.95

"Leading the Lens Field in Television"

LIQUID LENS CORP.

77-17 Parson Blvd., Flushing, N. Y. • JA 3-2004

WRITE... WIRE... PHONE FOR DETAILS

FM Coil & Condenser Kit for RCA Tuner

As diagrammed in Receiving Tube Manual
Radio Detector, 3-Gang Condenser,
3 Front End Coils, 2 IF's, 5 Chokes
CHASSIS LAYOUT & INSTRUCTIONS \$5.75 Postpaid
in U.S.
C-B MFG. CO. 412 W. 37th St.,
N. Y. 18, N. Y.

ELECTRICAL TRAINING

Intensive 32 weeks' residence course in fundamentals of industrial electrical engineering, including radio, electronics. Prepares for technician, engineering aides. Approved for veteran training. 64th year. Enter July 26, Nov. 22. Catalog.

BLISS ELECTRICAL SCHOOL
7698 Takoma Avenue,
Washington 12, D. C.

Mr. Radio Service Dealer "Speed is our Motto"

One day service on all orders. None too small. Only Nationally Advertised Merchandise (No Surplus Handled). TUBES—Any quantity 50% off list.

Mail us your orders.
Illustrated list on request.

Bill Sutton's Wholesale Electronics
Fifth at Commerce Fort Worth, Texas

NEW RECEIVERS

on the Market

TV CONSOLE

Stromberg-Carlson has recently introduced its combination radio-phonograph-television unit, the Model TV 12 M5M.

Known as the "Chinese Classic", this receiver provides a large screen with 12



inch picture tube in addition to FM, AM, and short-wave reception. The receiver is continuously tunable through the complete range of video and FM frequencies. A tuning eye has been included for accurate station selection and optimum reception.


A twelve-inch electromagnetic speaker is mounted in live rubber. Push-button tuning is provided on the standard broadcast band. The record changer plays 10 or 12 inch records in sequence and stops automatically after the last record has been played.

For further information on the Model TV 12 M5M address requests for data to *Stromberg-Carlson*, Rochester, New York.

TABLE RADIO

Housed in a two-piece plastic case, *Garod* is presenting the new "Elite" Model 5A3 table model receiver in the moderate price class.

The five-tube a.c.-d.c. superhetero-

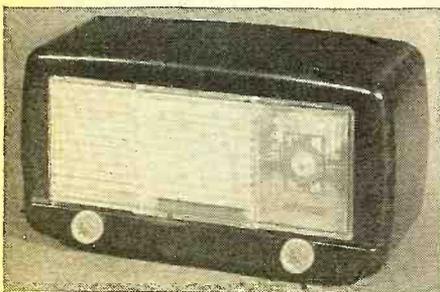

dyne features the "Air-Tenna" loop which insures reception over the entire broadcast band. The illuminated full-vision dial has highly visible markings

for ease in tuning. Controls include a tuning knob, and a volume control and "on-off" switch.

The cabinet measures 12½ inches by 6¾ inches by 5¾ inches.

Garod Electronics Corporation, 70 Washington Street, Brooklyn 1, New York is the manufacturer.

MODERN CONSOLE

Freed Radio Corporation has recently introduced the *Freed-Eisemann* "Modern", a conservatively styled console combination which is available in bleached or brown stripe mahogany finishes.

The "Modern" incorporates a 21 tube radio with Armstrong FM, a separate power supply and audio amplifier with an undistorted output of 20 watts, and coaxially mounted dual speakers with a tonal range of 30 to 15,000 cycles.

An automatic record changer that plays 10 and 12 inch records in any sequence and that employs a new type wide range pickup and a matched semi-



permanent needle is located in a pull-out compartment.

Additional details on the "Modern" may be secured by writing *Freed Radio Corporation*, 200 Hudson Street, New York, New York.

15" TABLE TV

A new addition to the *United States Television* line of home receivers is a 15 inch direct view table model designed especially for long-distance reception.

Housed in a mahogany cabinet, the 15 inch direct view set provides a picture measuring 9½ by 12¾ inches. The cabinet measures 22 inches by 22 inches by 23¾ inches.

Daylight operation of the set is made possible by several advanced features. New automatic circuits lock the picture in synchronism with the transmitter. Only four controls are required to operate this set. An r.f. amplifier, four stages of picture i.f. amplification, and two stages of video amplification are provided for better interference immunity, greater sensitivity, and noise free reception.

FM sound reproduction is achieved by use of three stages of i.f. amplification. An Alnico V permanent magnet speaker gives good sound reproduction.

Further details of this new 15 inch

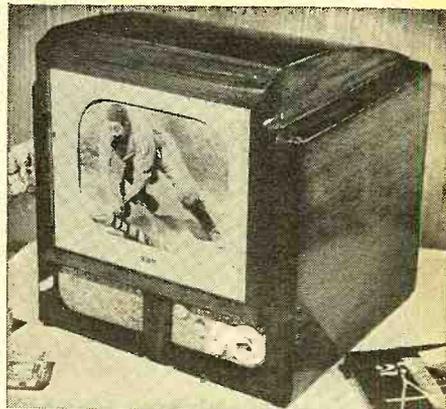


table model receiver may be secured by writing *United States Television Mfg. Corp.*, 3 West 61 Street, New York 23, N. Y.

PHONO CONSOLE

J. P. Seeburg Corporation of Chicago recently introduced the "Select-O-Matic Library" to the trade.

This instrument, which is available in models for the home and industry, plays records vertically and supplies more than fourteen hours of continuous music without repeating a selection or requiring any attention from the listener.

The new unit permits instant choice of any one of 200 selections without touching a record or searching for the desired selection in an album. Either or both sides of a record may be played without the recording being touched or without the record being turned over.

The instrument removes the record from the library, places it in a vertical position and then returns it to the library. Programs may be played automatically in any predetermined time cycle by means of a program timer set by the listener.

The model for the home has been designated the Model SLBA-1 and is housed in a modern cabinet of light wood.


Further information on the Model SLBA-1 may be secured by writing to *J. P. Seeburg Corporation*, Chicago, Illinois.

ARVIN PORTABLE

One of the new portables being introduced in the new *Arvin* line is the Model 240P.

STILL UNQUESTIONABLY THE FINEST

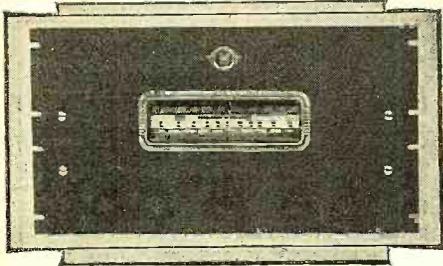The COLLINS
Custom Built FM/AM Tuner
THE ONLY TUNER WITH WIDE RANGE AM



THIS tuner has received wide acclaim throughout the country as the best medium for reception of FM and AM broadcasts. Many extra, personal accessories may be ordered with the tuner to make it exactly what you want. Its 17-tube circuits employ Armstrong FM, fu complement of vacuum tubes, self-contained power supply and latest circuit developments. Write for full information about this marvelous product.


COLLINS AUDIO PRODUCTS CO., INC.
P. O. BOX 368 Westfield, N. J.
* WE 2-4390 *
PLANT AT ROUTE 29, MOUNTAINSIDE, N. J.

Now Available
TRANSFORMERS
TO OPERATE
WAR SURPLUS EQUIPMENT

New small units now available at your favorite distributor. Model F 5069 delivers 24 volts at 3 amperes — \$3.90 net. Model F 5075 delivers 24 volts at 1 ampere — \$2.40 net. Other models for 12 and 24 volt operation.

Write for your free copy of the new
STACO Relay and Transformer Catalog.

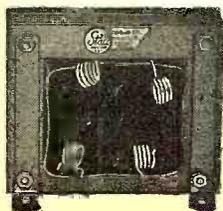STANDARD ELECTRICAL PRODUCTS CO.
407 Linden Ave. Dayton 3, Ohio




Everybody agrees
ATR AUTO RADIO VIBRATORS
are TOPS

ATR AUTO RADIO VIBRATORS
have Ceramic Stack Spacers

VISIT
ATR Booth 137
AT RADIO PARTS
AND EQUIPMENT
SHOW
May 11th-14th



New 34 page
VIBRATOR
GUIDE
FREE

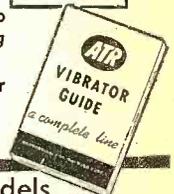

A Complete Line of Vibrators . . .
Designed for Use in Standard Vibrator-Operated Auto Radio Receivers. Built with Precision Construction, featuring Ceramic Stack Spacers for Longer Lasting Life. Backed by more than 17 years of experience in Vibrator Design, Development, and Manufacturing--
ATR PIONEERED IN THE VIBRATOR FIELD.

New Models



"A" BATTERY ELIMINATORS
For DEMONSTRATING AND TESTING
AUTO RADIOS

New Models . . . Designed for Testing D. C. Electrical Apparatus on Regular A. C. Lines. Equipped with Full-Wave Dry Disc Type Rectifier, Assuring Noiseless, Interference-Free Operation and Extreme Long Life and Reliability.

New Models



STANDARD AND HEAVY DUTY INVERTERS

For Inverting D. C. to A. C. . .
Specially Designed for operating A. C. Radios, Television Sets, Amplifiers, Address Systems, and Radio Test Equipment from D. C. Voltages in Vehicles, Ships, Trains, Planes and in D. C. Districts.

NEW MODELS
NEW DESIGNS
NEW LITERATURE
See your folder
or write factory

AMERICAN TELEVISION & RADIO CO.
Quality Products Since 1931
SAINT PAUL 1, MINNESOTA-U. S. A.

LET ME SEND YOU THIS AMAZING...



ELECTRONIC KIT!

S. T. Christensen, Pres.

Get in on the Big Money NOW! It is not unusual for mechanically inclined men to make \$5.00 to \$6.00 an hour repairing electrical household appliances and factory machinery. Lifetime Security can be yours in the fascinating, revolutionary, Electronic Repair Business. My Christy Electronic Kit checks and tests electrical equipment, current consumption, heat controls, shorts, motor winding, etc. and reveals where repairs are needed. My Christy Course tells in simple, easy-to-understand language how to make each repair, how to build power tools, how to secure business, what to charge, where to get repair parts... in fact, everything is told.

Get full facts by writing NOW.


RUSH COUPON TODAY!

Mr. S. T. Christensen, President
Christy Supply Co.
2835 N. Central Ave., Dept. D-140
Chicago 34, Ill.

Mail me FREE without obligation complete illustrated information on how to get the Christy Electronic Kit and Christy Appliance Course.

Name..... Age.....
Address.....
City..... State.....

ORDER BY MAIL! POSTPAID!*

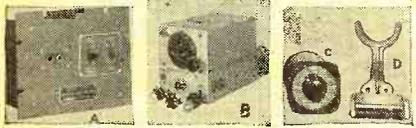

(A) **STATION CONTROL BOX . . . \$2.00**
Contains 2 4P2T anti-cap switches, 3 jacks, 1 ST Jones strip, 2 HD Jones Plugs, 1 full wave meter rectifier, 6 cond., 3 resistors, F.B. for VFO & Trans. control, key jack & fone jack. Brand new.

(B) **TUNING CONTROL KNOBS 69¢ ea., 3 for \$2**
For command set receivers. BC 454, etc. series with locking sleeve. Brand new, not surplus. Makes tuning simple for fixed or mobile use.

(C) **ALTITUDE LIMIT SWITCH . . . \$1.00**
Contains 14 2500 ohm, 2w resistors, 2 gang, 1 pole, 11 pos. switch. Removable glass dial face and dial, attenuator type case. Fine for making decade boxes and attenuators. Brand new.

(D) **TELEPHONE HANDSET HANGER . \$1.00**
Fits most types on market. Made of Navy inspected casting. Fine for desk, mobile or marine use. Brand new.

*All items shipped postpaid upon receipt of cash with order

ALL ABOVE ITEMS BRAND NEW!
Send for Latest Bulletin

ALVARADO SUPPLY CO.
Dept. RN3, 903 S. Alvarado, Los Angeles 6, Calif.


SENSATIONAL VALUES
ALL BRAND NEW
TUBES—STANDARD BRANDS—GUARANTEED

12B6—49¢ ea.	10 for \$4.50
55W4—39¢ ea.	10 for 3.50
Auto Vibrator Replacement Transformer 6V input	
180V output 50MIL. Lists for \$2.50, ea.	\$.98
Standard IF Transformers Shielded 455Kc.	29¢
IF Transformers Unshielded 455Kc.	12¢
Paper Tubular Bi-Pass Condensers .05 MFD, 400V	
30 for	\$1.00
Wire No. 22 Pushback Solid Tinned, 100 ft.	50¢
Wire No. 22 Stranded Tinned, 100 ft.	50¢
Oil Condenser 28 MFD 220V. AC.	49¢
RF Line Filter	10¢

NO C.O.D. \$1.00 MINIMUM ORDER ENCLOSE 10¢
ADDITIONAL FOR POSTAGE AND HANDLING

POLIN SALES
3806 Wilson Ave. Chicago 25, Ill.

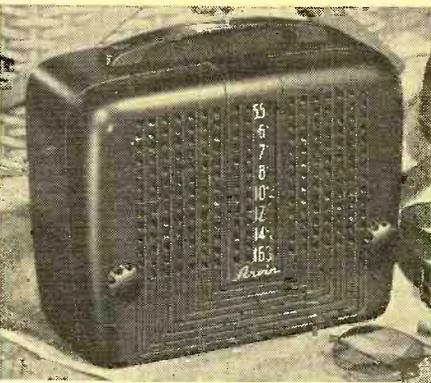This little 4-tube battery portable is housed in a ruby red thermo-plastic case and leads the line of personal port-




ables being offered by the company. Full details on the Model 240P and other receivers in the new line may be secured from *Noblitt-Sparks Industries*, Columbus, Indiana.

SIGHTMASTER VIDEO
Sightmaster Corp. of New York is now offering a 15" television receiver with FM radio.

Housed in either a mahogany, blonde, or walnut cabinet, the Model 15-C-11 features twin speakers. The circuit uses 24 tubes plus a 15" direct view tube which provides a picture area of 120 square inches.

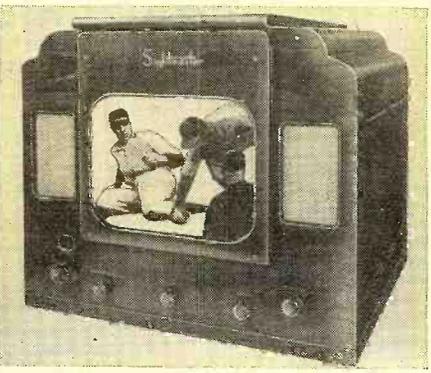The television receiver covers all channels in any television area while the FM tuning range covers from 87 to 109 mc. *Sightmaster Corp.*, 220 Fifth Ave., New



York 1, New York will supply additional details on the Model 15-C-11 upon request.

RCA VIDEO CONSOLE
The *Home Instrument Department of Radio Corporation of America* is now merchandising a new, low-priced console model television receiver which provides a 52 square inch picture on the face of a 10 inch direct-view tube.

Available in both walnut and mahogany finishes, the new console is of contemporary design, featuring clean lines, a permanent flat top, and fine horizontal louvers protecting the grille. Dimensions of the unit are 40½ inches high, 20 inches wide, and 20 inches deep. Per-

formance features include the company's "Golden Throat Tone System" with a 12 inch electro-dynamic speaker, the "Eye Witness Picture Synchronizer", the "Automatic All-Channel Station Selector Switch", a three-stage i.f. video amplifier, and a two-stage i.f. audio amplifier.

The *Home Instrument Department, Radio Corporation of America*, Camden, New Jersey will supply additional details on the Model 721TCS upon request.

PORTABLE WIRE RECORDER
A unique portable wire recorder and phono-combination has been announced by *Air King Products Co., Inc.* of Brooklyn.

This unit uses 5 tubes (including rectifier) in the amplifier and has a radio attachment cord. The recorder will play either 10 or 12 inch records and comes equipped with a permanent needle.

Recordings from a phonograph or



radio can be made directly through the amplifier without using the microphone thus guaranteeing highest fidelity. Voice can be dubbed through the mike while recording from the radio, if desired.

Housed in a luggage-type carrying case, the wooden box offers excellent baffle qualities yet is compact and practical. An automatic shut-off whereby the motor turns off after the wire rewinds has been incorporated in this unit. A safety lock prevents accidental erasures and a visual tone indicator guarantees proper recording level.

Further details on the Model A-750 may be secured from *Air King Products Co., Inc.*, 170 53rd Street, Brooklyn 32, New York.


AM-FM CONSOLE
Templetone Radio Mfg. Corp. is currently introducing its Model G-1430, a 14-tube radio phonograph console which incorporates FM, AM, and short-wave reception.

The automatic record changer plays mixed 10 and 12 inch records in any order and shuts off after the last record has been played. A 4 second change cycle is a feature of this changer.

A 12 inch Alnico V permanent magnet dynamic speaker is capable of handling the peak power output of 40 watts. A four-position switch tone control, bass, music, voice, and treble, changes the tone by boosting bass and/or treble, not

merely attenuating the high frequencies.

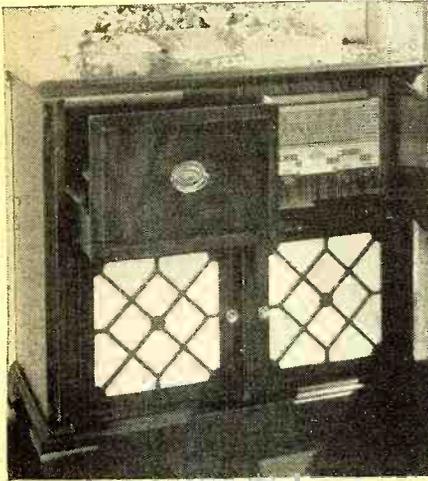A data sheet covering the features of the Model G-1430 is available on re-



quest from Templeton Radio Mfg. Corp., 220 E. 42nd Street, New York, New York.

-30-

Spot Radio News


(Continued from page 20)

named WORM. Belongs to the Easton Broadcasting Company, Inc., Easton, Md., FCC says. The station, authorized for 1-kw. operating on 1480 kc., is now abuilding. WORM will broadcast seven-teen hours daily under the guidance of J. N. Critchlow, its president, with the help of his two sons, John N. and Roger E. Critchlow.

IT'S DIFFICULT to predict too accurately at the moment, but you can bet on this—the Federal government will be a big radio customer before the snowflakes. Maybe not as big a customer as, say, during the closing years of the war, but plenty big, nevertheless. Preparedness is the answer—plus the fact that military thinking is becoming more and more electronics-conscious. This has, of course, been standard for years with the Signal Corps (now busy on new communications devices, the lighter and more mobile, the better), but top brass in other services now have the bug. Significant is the off-the-record statement to this correspondent by a high-ranking Air Force General recently: "Maybe some of us fliers don't know it yet, but I can assure you it's true: the outfit with the best electronic devices, not the best planes, is going to win the next war." He's backing this up with all the influence of his office, which is a key one, to streamline the Air Force along electronic lines as quickly as possible. As this goes to press, there was every indication that a sizable portion of the huge Air Force budget would be given to him to implement his idea with full-

May, 1948

"TOPS ALL DX RECORDS"

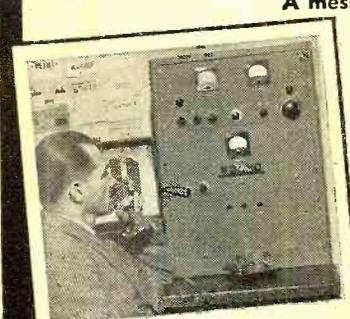

A message from LEO WØGFQ . . .
Hams the world over are praising the WRL-275 watt Globe King XMTR Kit. The WRL-275 watt Globe King is a versatile advanced design transmitter kit which will give you efficient performance on 6, 10, 20, 40, and 80 meter band on phone and CW. COMPARE THESE FEATURES AND TAKE ANOTHER LOOK AT THE PRICE. Front panel control of link to final input—automatic fixed bias for good regulation—voltage controlled buffer and oscillator stages—provisions for ECO—new speech modulator circuit—modulates up to 350 watts—dual power supply for oscillator buffer and RF stage—most compact transmitter on the market—stands 28 1/4" high. For only \$20.00 we wire this kit complete ready to go and all you have to do, in most cases, is hook on your antenna, plug in your mike and you're on the air. Write for complete descriptive literature—plus names of users in your area.



WRL Globe Trotter XMTR Kit

Amateurs the world over are praising the performance of this high quality, low cost rig. It's a 40 watt input kit including all parts, power supply, chassis panel and streamlined cabinet. Write for export prices.
Less tubes\$69.95
Wired\$79.50
1 set of coils, meters, tubes, extra...\$17.49

10 Day Free Trial Standard 90 Day Guarantee
WRL 275 WATT XMTR
This new WRL 275 Watt Globe King Transmitter Kit is available as a complete unit, or individual sections may be purchased separately—Write for prices. Complete with tubes, meters, cabinet, one set of coils.
Wired \$386.45
Kit Form \$366.45
*Liberal Trade In Allowance on your present HAM GEAR.

WRL Exciter Kit

From our own labs Uses 6L6 regenerative Osc. into an 207 driver or final. Similar to unit described in A. R. R. L. Handbook. Output 35 to 40 watts. Mounted on standard relay rack panel 3 1/2" x 19".
Less accessories...\$19.95
Wired\$25.95



Set of coils, meter tubes, extra\$10.78
Power Supply wired with tubes\$22.75



Get Acquainted Offer New up to date Giant Radio Reference Map Just right for your control room wall. Approximately 28"x42". Contains time zones, amateur zones, leading shortwave stations, monitoring stations, Mail coupon today & 25c.

TRY LEO'S PERSONALIZED PAYMENT PLAN—IT'S EASY 20% DOWN—PAYMENTS TO FIT YOUR BUDGET

- | | |
|--|--|
| 757L XMTR Tube, new\$2.49 | Aerovox 1509—MFD—1500 V Oil Filled Condenser 5.49 |
| 6 ft. cable and 2 plugs to fit 654 and PE 103 \$1.95 | 1 Mid. @ 5000 V Oil Filled..... 3.49 |
| 274 N Series VFO and XMTR. Complete with tubes and crystal. Used BC-457A—4 to 5.3 MC.....\$3.95 | 2 Mid. @ 1000 V Oil Filled..... 1.19 |
| Kit of 4 new Original Type Tubes for 274 XMTR's\$1.95 | 1 Mid. @ 2000 V Oil Filled..... 1.55 |
| New completely Shielded Transformers to operate with all 274 series XMTR's. 1200 V.C.T., 200 MA. 5V @ 3a—Two 6.3 V.C.T. fil @ 3 A ea. Series these for 12 Volts to operate XMTR.....\$5.95 | 4 Mid. @ 1500 V Oil Filled..... 1.50 |
| | 50 Ft. RG8U Cable and COAX Connector 83-15P\$1.95 |
| | BC-654 Factory reconditioned with spare set of tubes export crated.....\$22.50 |
| | Brand New H23U—Telephone Handset with switch\$3.95 |
| | Brand New T-17B Mike.....\$ 98 |

- WRL Guarantees Fast, Personal Service
 ● Liberal Trade Ins ● Complete Parts Stock
 ● Orders Filled Same Day ● Ham Gear Our Specialty

Get this 68 Page Bargain Catalogue FREE!

WRITE—WIRE PHONE 7795

WORLD RADIO LABORATORIES
744 West Broadway
Council Bluffs, Iowa

Please send me:

- Radio Map Globe King Data
 Parts Catalogue Globe Trotter Data

Name.....Call Letters.....

Address.....

City.....Zone..... State.....



NOW ON SALE RADIO-ELECTRONIC ENGINEERING

Dec. 1947 Edition

An 8-page magazine with articles of interest for all radiomen

10c in coin

ZIFF-DAVIS PUBLISHING COMPANY

Circulation Dept.

185 N. Wabash Ave. Chicago 1, Ill.

COUPON-OF-THE-MONTH

- | | |
|---|---------------|
| TUBES—Std. Brand 35Z5GT or 35W4..... | 10 for \$3.00 |
| TUBES—Std. Brand 12SQ7 or 12AT6..... | 10 for 4.90 |
| TUBES—Std. Brand 50L6GT or 50B5..... | 10 for 5.90 |
| SAPPHIRE Phono Needles (List 2.50)..... | 10 for 8.80 |
| CTS. Vol. Controls—5 Meg. W.S.V..... | 10 for 4.40 |
| SPRAGUE Cond.—10-40 MFD 150V..... | 10 for 5.40 |
| By Pass Cond.—.005 or .01 MFD 600V..... | 100 for 6.90 |
| ● Combination Kit—All Above Items—Only..... | 37.50 |


WITH THIS COUPON—ORDER AT ONCE

- Radios—4 tube Superhet. (Nat. Known)..... 8.95
 ● Radios—5 tube Superhet. (Nat. Known)..... 13.95

Write for Monthly Coupons and Bulletin
 RADIO DISTRIBUTING CO., PASADENA 18, CAL.

RCA Institutes, Inc.
 Offer thorough training courses in all technical phases of Radio and Television
WEEKLY RATES **DAYS—EVENINGS**
VETERANS! RCA Institutes is approved under G. I. Bill of Rights
 For Free Catalog write Dept. RN-48
RCA INSTITUTES, Inc.
 A Service of Radio Corporation of America
 75 Varick St., New York 13, N. Y.

For added sales
(and profits!)

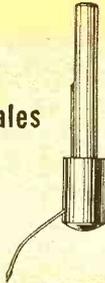

demonstrate

the amazing Shockproof

nylon needle

by

DUOTONE

Actually b-o-u-n-c-e the whole
tone arm on a record without
effect. A spring steel shaft and
nylon elbow—that is the secret! **\$2.50**
LIST

*pat. pending



"STOP CROWDING"


CONTROL DISTRIBUTION OF SOUND WITH
"T M C SUPPLEMENTARY SPEAKERS" CONN-
ECTED TO RADIO AND TELEVISION RECEIVERS
IDEAL FOR BARS, GRILLS, RESTAURANTS,
HOMES, HOSPITALS, P.A. SYSTEMS,
AND MANY OTHER PLACES

To SERVICE MEN
— DEALERS

Direct From Factory

Only, **\$6.95** Net

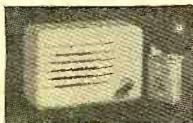F. O. B. Tarrytown, N. Y.
Ship. Wt. 3½ lbs., net



Size: 5" x 7" x 3" Deep

CHECK THESE FEATURES:

- Fully enclosed unbreakable cast aluminum case.
- Built in volume control.
- Best 4" P.M. speaker.
- 7 beautiful glossy colors — Ivory, Red, Mahogany, Light Blue, Nile Green, Gray and White. Unless otherwise specified, speakers will be shipped in Ivory.
- Very simple to install. Installation directions with each shipment. As many as 8 speakers have been connected to standard radio or television sets without altering set in any way.
- Hang on the wall on the key slots provided, or set on a table or shelf.
- Fully guaranteed. If you are not satisfied, return within 30 days and your money will be refunded.

WRITE FOR FURTHER DETAILS
DON'T DELAY • ORDER NOW
25% Deposit with order, Balance, C.O.D.

TARRYTOWN METALCRAFT CORP.

82 CHESTNUT STREET, TARRYTOWN, N. Y.

Vertical waterproof model for outdoor theatre use,
with L-Pad volume control, and waterproof speaker.
Full details on request.

throttle research and development work, followed closely by large-lot orders of the resulting equipment.

PERHAPS TYPICAL of current defense thinking—and indicating how far they intend to go into electronic fields—was the recent development of a weather facsimile service for transmitting weather maps. Signal Corps played a leading role in this work, done for the Air Force Air Weather Service, by developing a service that would be invaluable to combat units of all types as well as to non-combat groups interested in advancing a war effort. The facsimile service—among the most ambitious military projects since war's end—involves some 15,000 miles of circuits, with four separate networks of facsimile transmission channels. The networks are so arranged that they can be interconnected and one station can send to all receiving stations. Domestic as well as international weather maps are prepared at the weather headquarters in Arlington, Virginia, across the Potomac from Washington and in the shadow of the Pentagon. They are broadcast on an almost half-hourly basis throughout the United States. Regional maps are distributed from secondary transmission points in New York, California, Texas, Oklahoma and Georgia. Facsimile makes transmission of a map possible in about twenty minutes. According to Air Force authorities, facsimile will have money as well as time by substantially reducing the personnel engaged in servicing weather data. Engineering problems of the facsimile service were worked out through the Long Lines Department of the American Telephone and Telegraph Company in cooperation with the associated Bell System companies who provide the communication channels needed for the network. The system, as pointed out recently by Capt. G. D. Furlong of the Signal Corps, is making weather-reporting history. "It ultimately will make the conventional weather reporting for pilots obsolete," he says. "It eliminates the hazard of surprise changes in the weather which might, if known, alter the flight plan. Thus safety as well as the convenience of the pilot is served." The complete facsimile plan, Capt. Furlong reports, calls for a network of 166 stations throughout the country. A total of 77 are now in operation.

FACSIMILE CONTINUED to figure elsewhere in the Washington news during the spring, activities in the field highlighted by FCC meetings beginning March 15 to try to find out how far things had gone in the field, and what kind of futures there are. Like everybody else in electronics, the facsimile experts will tell you—as they told the Commission—that developments are un-

limited and all they need is plenty of room on the radio spectrum to prove it. The Commission's problem is to find out how true the claims are—being radio claims, if the past is any indication, they are conservative—and then try to make way for the future in the overcrowded spectrum. That the FCC considers the facsimile problem one of its most serious was indicated at the March 15 meeting, when all FCC commissioners turned out. Facsimile representatives from a score of firms, including Alden Products Company, Finch Telecommunications, Inc., Radio Inventions, Inc. and Faximile (why didn't you think of that one?), were also present. Discussion hinged on how important it is for facsimile to get more room, how much of a public demand awaits it, and how efficient the service is today. The Commission is going to take some time, from all indications, to answer these questions, but the burden of the testimony seemed to indicate a couple or three interesting things that would bear remembering. As was the case with FM and television, facsimile is having a hard time getting started, but its public is steadily increasing. Now it's mostly professional—as used by the Air Force weather boys and for sending pictures to newspapers, to name a couple of services—but it has also reached at least some of the general public via faccasting of newspapers. We reported some of these activities in the last column. Testimony before FCC indicated that this type of work would increase beginning tomorrow. How fast is a question, but if the word of facsimile experts is an index, facsimile, far from still being in a semi-developmental stage, is ready to do business in as big a way as its cousins, FM and television. Full-blown activities in the field will not be as immediate as some hope, however, if former developments may be used as guide posts. Rules must be drawn—suitable to both the industry and FCC—concerning facsimile broadcasting. How much room is really needed must be determined. And then FCC and the facsimile boys are faced with a jackpot question—who's going to move over to make room? It's a tough one, and can't be answered overnight.

LONG AS WE'RE trying to peek into the future, might as well end on a Dick Tracy note. One of these days, we hear, broadcasting equipment, will, possibly, get its power from tiny capsules—buckshots of power—containing nuclear energy. This, in turn, may make possible wristwatch radios and pocket television sets. And we haven't been reading the comic strips, either. Just listening to no less an authority than David Sarnoff, president of the Radio Corporation of America and chairman of the board, NBC...

Universal Wattmeter

(Continued from page 67)

from terminals 3 and 4, and reconnect resistor R^2 . This completes the simple calibration-adjustment procedure.

If it is desired to verify the voltmeter linearity; before R^2 is reconnected and the short removed from terminals 3 and 4, apply 5 volts to terminals 1 and 2, noting that the meter reads 0.5 ma. (exactly half-scale). Also, apply $2\frac{1}{2}$ volts and note that the meter reading is 0.25 ma., or quarter-scale. Check as many voltages between 1 and 10 as desired.

The meter scale may be marked-off in watts according to the scheme given in Fig. 4. This requires no point-by-point calibration—the operator needs only to make his inscriptions according to Fig. 4. Very close graduation of the meter scale may be made by following the curve given in Fig. 5. It is best to make a special watts scale to replace the regular milliammeter card. Such a scale is seen on the author's meter in Fig. 1. A scale of this sort requires a certain amount of patience to draw, but it eliminates the confusion which is caused when the milliamperes and watts appear on the same card, and is well worth the additional time and effort demanded.

Using the Meter

The wattmeter described in this article is as simple to use as a voltmeter. The following procedure is recommended: (1) Determine the output impedance of the amplifier, oscillator, or other device to be tested. (2) Connect to terminals 3 and 4 a 100-watt resistor (preferably non-inductive) which has a resistance value equal to 1 ohm less than the impedance of the power-delivering device. It may not always be possible to obtain a resistor having the exact resistance value required. In this case, it will be necessary to use a wirewound unit with a slider set to the desired ohmic value. When the output impedance is 100 ohms or more, the external resistor connected to terminals 3 and 4 may be chosen equal to the impedance without introducing too much of a practical error in the wattage indications. When the impedance of the power-delivering device is 1 ohm, do not use an external resistor at all. Instead, short-circuit terminals 3 and 4. (3) Connect terminals 1 and 2 to the output terminals of the power-delivering device. (4) Read output watts on the meter scale. (5) Multiply this meter reading by the output impedance (ohms) when this impedance is higher than 1.

When checking the power output of an audio amplifier, disconnect the loud-speaker voice coil, connect terminals 1 and 2 of the wattmeter in place of the

• It's RADIONIC for PRICE • It's RADIONIC for VALUE • It's RADIONIC for DELIVERY •

FREE RADIONIC CATALOG



It's a must for all

- Service Dealers
- Amateurs
- Experimenters
- Industrials
- Institutions
- Government Agencies

TRANSVISION'S

12" GIANT TUBE KIT
(72 sq. in.)

296.95

(includes 88-108 mc. FM)



WRITE FOR DEALER'S PRICES
SPECIAL OFFER: To see for yourself, you may order the instructions separately. Includes parts list, schematic diagrams, stage by stage drawings, etc. Send \$1.75, credit applied to your kit when ordered.

CHANCELLOR RADIO • TELEVISION KITS AND COMPONENTS • RADIOS • TEST INSTRUMENTS • PARTS AND ACCESSORIES • INTER-COMMUNICATORS • DISC AND WIRE RECORDERS • PUBLIC ADDRESS • AMATEUR EQUIPMENT • TUBES • RECORD CHANGERS • TECHNICAL BOOKS • HARDWARE

RADIONIC EQUIPMENT COMPANY


170 NASSAU STREET, N. Y. 7

Tribune Theatre Entrance
Telephone: WOrth 2-0421
Cable "CHANSLOR"

TELEVISION



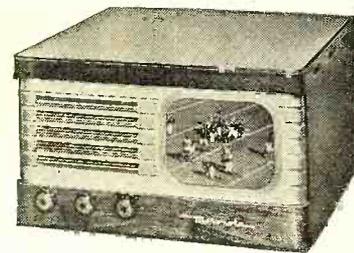HALLICRAFTER Table model Television receiver, Model T54. Fine performance, smart appearance. Rich, silver gray metal cabinet. 13 channels. 26 sq. in. screen. Marvelous entertainment at low cost **\$169.50**



MOTOROLA—Handsome, compact table model. Sharp, stable image. Beautiful tone. Extremely attractive styling. Mahogany or blonde veneer cabinet. Everything you want in television at a price you can afford. Mahogany or Walnut..... **\$179.95**

Model VK101, 54 sq. in. screen, Mahogany Console **\$495.00**

Sales floor open daily 9 to 6, Sat., 9 to 5
RADIONIC distributes parts and equipment of Television's leading manufacturers. Order by manufacturer's part number or write us your requirements.

FREE CATALOG MAIL TODAY!

RADIONIC EQUIPMENT CO., DEPT. 55
170 NASSAU STREET, NEW YORK 7, N.Y.

Send at once your free catalogs, supplements and Bargain lists as published—listing products of leading manufacturers of radio-electronic parts and equipment.
 Please send me Transvision instructions described above. I enclose \$1.75 which is returned to me if kit is ordered.

NAME.....

P.O. BOX or STREET.....

TOWN.....STATE.....



Armature Exchanges

For Vacuum Cleaners, Mixers, Drills and similar size appliances. No flat rates on exchanges. Charges made only for parts you need. Vacuum types \$2.10 to \$3.00... Others \$3.25 and up. Exchanges serviced in large modern, MACHINE-EQUIPPED Winding Dept.

Also available is our large supply of Commutators and most shafts.

ELECTRIC SWEEPER SERVICE CO.

2034 EUCLID AVE. (DEPT. 1) CLEVELAND 15, OHIO

**ANNOUNCING A
NEW SERVICE . . .**

the MCN Company

We stock, or can immediately locate, clean and dependable electronic or communications equipment of whatever type you might need.

Our personnel has been associated with the disposal of war surplus since the inception of the program—has an intimate knowledge of the fields involved and has extensive and nationwide contacts. Ample resources permit the handling of any assignment, regardless of size.


We invite Manufacturers, Jobbers and Dealers to list their surplus stocks with us.

We solicit inquiries from companies interested in receiving quotations on their electronic requirements.

The MCN Company

4408 N. Ravenswood Ave., Chicago 40, Ill.
Telephone ARDmore 1520

RAD-O-RECORDER

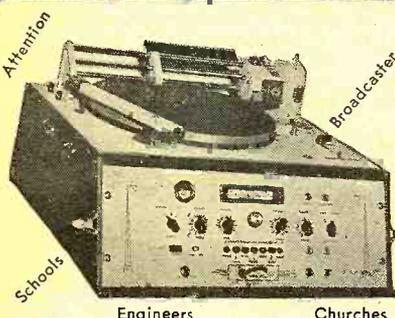

PROFESSIONAL

16" Dual Speed Recorder

The nations finest recording equipment. A complete self contained portable recorder containing all the fine qualities and features of stationary professional Studio equipment. Heavy duty 27 lb. dual speed turntable with silent precision overhead cutting lathe. Instantaneous recordings made with ease, either inside out or outside in. Variable lines per inch while recording is in progress. Ideal for Broadcasting Stations, Schools, Voice culture, Churches, Studios, etc. Write for catalog.

List Price \$585.00

MAKAN INC.


79 Thurman Ave.
COLUMBUS, OHIO

voice coil, and connect a resistor to terminals 3 and 4 equal in ohmage to the voice coil impedance minus one ohm. This resistor must be rated to handle safely at least 2 times the power output of the amplifier. When checking audio amplifier power output, always apply a good sine-wave signal to the amplifier input terminals. 400 and 1000 cycles are standard test frequencies. Before disconnecting the loudspeaker for the wattage test, set the amplifier controls for maximum undistorted output.

When checking r.f. power, such as across a coaxial line, the wattmeter is used in the same manner just described for audio-frequency measurements, except that terminals 1 and 2 are connected to the r.f. output terminals of the device under test. When tests are made across a transmission line, the "far end" of the line must be disconnected. The non-inductive resistor connected to instrument terminals 3 and 4 must be equal in ohmage to the characteristic impedance of the line. When checking r.f. power, use the shortest possible-leads between the r.f. source and the instrument terminals, and between the load resistor and instrument terminals.

The wattmeter must not be used in connection with circuits carrying d.c. Any d.c. component will produce an erroneous deflection of the meter and, if of sufficient voltage, will damage the crystal diode. Usually, some means of magnetic output coupling is available in each a.f. or r.f. power-delivering device. In every other case, use a large-capacitance coupling condenser in series with input terminal 1. No single value can be recommended for this isolating condenser, since the best microfarads value will depend upon the load resistance value and the operating frequency. Follow the rule of choosing a condenser of sufficient size (μ fds.) that it will introduce little signal reduction at a particular operating frequency. What would be a satisfactory capacitance for one combination of frequency and load resistance might be unsuitable for another combination.

-[30]-

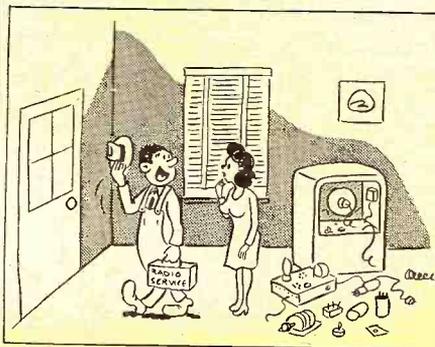

"That's as far as I know. I'll be back when I get my next lesson through the mail!"

**PRACTICAL
TECHNICAL
TRAINING FOR YOU**

SPECIALIZE In 6 Months to 3 Years

**COURSES
SERVICE**

6 to 12 Months

- Electricity
- Welding
- Refrigeration
- Heating

TECHNICIAN

1 to 2 Years

- Electricity
- Radio
- Electronics
- Refrigeration, Heating and Air Conditioning

PROFESSIONAL

3 Years

- Electrical Engineering
- Bachelor of Science Degree
- Major in Machinery or Electronics


Train for a substantial career in industry—or a business of your own. Each 6-month course is complete in itself, yet prepares you for advanced courses. More than 35,000 former students in industries the world over. 1,538 students now enrolled from 48 states and 13 overseas countries. Faculty of 72 specialists.

Write for booklet "Career Building" and mention course interested in.

**MILWAUKEE
SCHOOL of ENGINEERING**

"A Technical Institute" Founded 1903
RN-548, N. Broadway and E. State, Milwaukee, Wis.

1" OSCILLOSCOPE

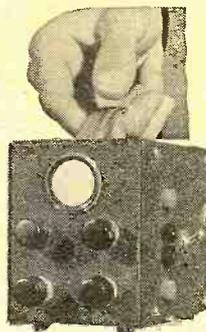

PORTABLE!
MEASURES 3"x4"x5"
SPECIFICATIONS

- Focus and Intensity Controls
- X and Y Input Controls
- Internal Sweep
- Built-In 500 V. Power Supply
- Wrinkle Finish, Red Lettering, Chrome Handle
- 110 V. AC 60 Cycle

MADE FROM NAT'L.
ADVERTISED PARTS.
DEALERS WRITE

Oscilloscope complete, less RCA 913 C. R. tube, \$19.95 net. If you prefer to build your own 1" oscilloscope, send \$1.00 for set of plans and instructions.

PLASTICS & ELECTRONICS COMPANY
272 Northland Ave., Buffalo 8, New York

NOW ON SALE

VIDEO NEWS

An eight-page magazine featuring

**MERCHANDISING TELEVISION
FOR PUBLIC VIEWING**

Send 10c in coin to

ZIFF-DAVIS PUBLISHING COMPANY

Circulation Dept.
185 North Wabash Avenue
Chicago 1, Ill.

MOTOR GENERATORS

Brand New War Surplus Machines built by Allis Chalmers Co. to U. S. Navy Specifications.
Input: 115 V. D.C. at 14 amps., 3600 rpm. Output: 120 V. A.C., 60 Cy. 1 ph. at 10.4 amps., 1000 Watts continuous duty. Ball bearings. Splashproof. Fully enclosed. Centrifugal starter. Frequency adjustable to load. Price \$97.50.
Same machine but for 230 V. D.C. input, Price \$125.00. Spare parts kit with extra brushes, brush-holders, field coils, bearings, etc., for either machine, \$29.50.

All prices FOB Tuckahoe, New York
ELECTRONICRAFT, INC.
5 Waverly Place, Tuckahoe 7, New York

RADIO ENGINEERING I

COMPLETE Radio Engineering Course. Bachelor of Science Degree. Courses also in Civil, Electrical, Mechanical, Chemical, Aeronautical Engineering, Business Administration, Accounting, Secretarial, Science. Graduates successful. 64th year. Enter March, June, Sept., Jan. Write for catalog.



DEGREE IN
27 MONTHS

TRI-STATE COLLEGE 1658 College Ave., ANGOLA, INDIANA

RADIO NEWS

MIRACLE KIT VALUES!

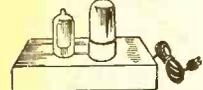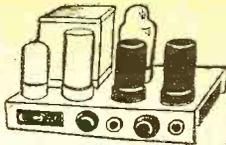10 WATT 4 TUBE HI-GAIN 6L6 AMPLIFIER KIT
Separately controlled Miko & Phone inputs. All parts including drilled chassis, hardware, solder, circuit diagram, info., etc. Less Tubes...\$6.95 ea.



PHONO OSCILLATOR 2 TUBE KIT
Hi-gain with microphone jack and all parts including Tubes...\$2.75

UNIVERSAL TROUBLE SHOOTER
Locates every service trouble. All parts including case, test leads, plug, 2 1/2 "x 6 1/2 " \$3.95

PHONO AMPLIFIER KITS


3 Tubes—all parts including Tubes...\$4.25
2 Tubes—all parts including Tubes...\$2.95
5 TUBE AC/DC SUPERHET RADIO KIT
All parts including 5" Heavy Duty Speaker, Dial, 5 full size Tubes...\$10.25

Write for lists of bargains in Radio & Electronic parts. Also free data, circuits designed by ROBT. G. HERZOG.

Universal general corp.

Dept. N
365 Canal St., New York 13, N. Y. — WALKER 5-9642

PITCO LINE FILTERS

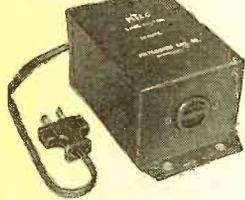

• 5 Amp. 110-220 Volts, A.C. or D.C.
• 10 Amp. 110-220 Volts, A.C. or D.C.

Highest Quality . . . Dependable Performance

Exhaustive tests and actual operating performance have definitely proven the superiority of the Pitco Line Filter over other designs. The dependable unit presents a solution to the problem of serious radio interference from power lines, motors, and appliances provides inductance as well as capacitance, thereby assuring thorough filtering action.

The Pitco Line Filter plugs into the electrical outlet and can be connected at the receptacle of the filter with either the radio set or interfering device. Wherever installed, you'll find this sturdy, compact filter is unsurpassed for high quality and outstanding performance.

For Complete Details, See Your Distributor or Write Direct.

Pittsburgh Coil Co., Carnegie, Pa.

Coils • Test Leads • Line Filters • Indoor Aerials
Phono-Switches • Circle Cutters

BRIDGE and V. O. M. PARTS

Decade Unit 0-10 ohms \$4.50
Decade Unit 10-100 ohms 4.50
Multiplier Unit, multiplies decade unit value by .001, .01, 1, 100, and 1000 5.50
V.O.M. Shunts and Multiplier unit 5.00
Decade switch, 3-deck, 10-point 1.00

These units are mounted on low-loss wafer-type, wiping contact, ten-point switches and with one-half hour's work and your meter can be assembled into highest grade Wheatstone Bridge and V.O.M. All of these units were made by Hickok Electrical Instrument Co. for U. S. Army Air Forces and Navy instruments to most exacting specifications and are accurate within 1/10 of 1%. The V.O.M. unit is a part of the famous Hickok 955 unit and can be used with any good high-resistance meter. Diagram furnished with units.

McCOY SALES COMPANY P.O. Box 335, Berea, Ohio

CORRESPONDENCE COURSES IN RADIO and ELECTRICAL ENGINEERING

ELECTRICAL ENGINEERING Get good grasp of wide electrical field. Prepare yourself at Low Cost, for secure future. Modern course. So simplified anyone can understand quickly.

RADIO ENGINEERING Extra fine course in radio, public address, photo-electric work. Trains you to be super-service man, real vacuum-tube technician. Servicemen needed badly. Diploma on completion. Many graduates earning big pay.

WRITE Send postcard for Free Copies of \$25 Either school catalog. Full details, all Course about deferred payment plan, experimental kits, etc. LINCOLN ENGINEERING SCHOOL, BOX 931-R113 LINCOLN 2, NEBR.

May, 1948

Power Supply (Continued from page 68)


Fig. 1C. In it a triode tube acts as the loss element. A tube is chosen which has considerable power-handling capacity and which can be run with the grid positive, such as one intended for Class B service. The output voltage is fed back to the grid through a bucking battery or gas-discharge tube, so that minor variations in output voltage appear directly on the grid and produce corrective changes in shunt current.

For example, a regulator was arranged using a 6V6G tube with the screen tied to the control grid in the high- μ connection, with four one-watt neon bulbs in series as a reference potential. The impedance of this combination as a shunt arm was found to be 400 ohms in the 250 volt region. When the regulator was applied to a light-duty power supply of 2000 ohms internal impedance, the regulated supply showed an internal impedance of approximately 330 ohms. This is the anticipated value, found by calculating the combined value of 400 ohms in parallel with 2000 ohms. The actual characteristics are shown in graph form in Fig. 2, where the ideal condition would be, of course, for curve C to be absolutely horizontal, representing zero impedance.

This circuit may be arranged to use tubes in parallel or to use one of the transmitting triodes. Its most promising application is to furnish bias to Class B or C amplifiers. For such services the supply may be a cheap, high-impedance device capable of furnishing only the few milliamperes necessary to maintain the gas-discharge, with all the advantages which would come from using a heavy-duty unit with a bleeder of several hundred ohms resistance. For example, a small transformer, half-wave rectifier, resistance-capacity filter, and 6V6 tube with one or two half-watt neon bulbs will be adequate for biasing a Class C r.f. amplifier of about one hundred watts input.

U. S. Patent 2,409,151, on this new circuit, is assigned to the *Western Electric Company, Incorporated.*

-[30]-

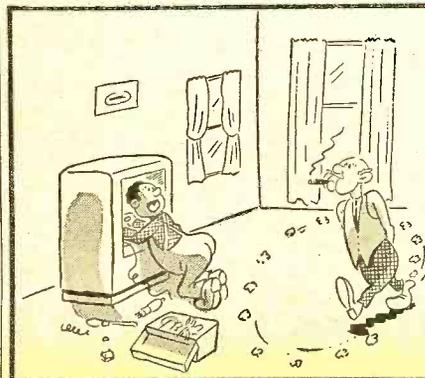

"Stop worrying, I'll have it fixed before the 'Lone Ranger' comes on the air!"

HERE IT IS! JUST PUBLISHED!

The Practical Aspect
of the Future of Radio

Television AND F-M RECEIVER SERVICING

By Milton S. Kiver
Registered Professional Engineer

—As every radio man knows, the limitless possibilities of radio in the fields of F-M and television broadcasting are no longer "just talk"—the future of radio has arrived! With more and more F-M and television sets on the market and in operation, no student or service man can afford to be without the wealth of up-to-the-minute, practical information in *Television and F-M Receiver Servicing*. Written by the author of *U.H.F. Simplified*, *F-M Simplified* and *Television Simplified*, this simple, well-organized text contains enough theory to make crystal-clear all types of servicing problems, and gives specific directions for diagnosing, locating and repairing the common troubles which may occur in an F-M or television receiver. The book is profusely illustrated with valuable schematic diagrams and photographs.

CONTENTS

The Antenna System, Operation and Installation; Television Receiver Installation; Television Test Equipment; The Television Receiver, Operation and Servicing (4 chapters); Television Receiver Alignment; Trouble Shooting Television Receivers; F-M Fundamentals; Commercial F-M Receiver Circuits; F-M Receiver Alignment; F-M Receiver Servicing.

EXAMINE THIS BRAND NEW BOOK FREE!

MAIL THIS COUPON

D. Van Nostrand Company, Inc.
250 Fourth Ave., New York 3, N. Y.

Please send me a copy of *TELEVISION and F-M RECEIVER SERVICING* for examination. Within 10 days I will return the book to you or send you \$3.25 plus a few cents postage.

Name _____
Address _____
City _____ State _____

RN-May '48

JUST OUT! Hard-to-get
New Solid Brass Portable
7 FT. RADIO
ANTENNAS
 9 Exceptionally Rugged
 Sections With Handy
 Mounting Bracket

\$10 Value Only \$2.49 post paid

Sent Postpaid Upon Receipt of
 Price or Mailed C.O.D. Plus
 Postage

FOR HOMES
BOATS or AUTOS

Same as used on Army tanks, Jeeps,
 etc. These telescopic, rustproof an-
 tennas have tremendous pickup,
 eliminate dangerous wiring. Solid
 Brass throughout, practically in-
 suring

NOISE FREE RECEPTION
 Compresses into 1 ft. 3 in.
 Handy for Camping Trips, also
 Useful for Transmitting, FM and
 Television sets.

EASY TO INSTALL ANYWHERE

Each antenna comes securely pack-
 ed with handy mounting bracket
 ready to put up.

QUANTITY LIMITED
MAIL ORDER TODAY

Send check or money order today for
 only \$2.49 for this \$10 Value. Your
 antenna will be sent postpaid or
 mailed C.O.D. plus postage.

Money back in 10 days if not satisfied.

RADIO HOSPITAL
 442 East 86th St., Dept. R12
 New York 28, N. Y.

HOBCO
MAY
SPECIALS

New AIR KING Portable
WIRE RECORDER & RECORD PLAYER

complete with
 microphone

\$139.50 list

AIR KING Portable
RADIO CAMERA
 America's
 first
 Radio-
 Camera
 list
\$29.95
 AIR KING Portable
 Radio Model A-510—
 AC — DC or Battery
 \$37.95 list

—SPECIAL SPRING SALE—
SIDE COWL AUTO RADIO AERIALS
 HOBCO—4 555 63" . . . L.P. \$5.50 Net \$1.98
 HOBCO—4 553 70" . . . L.P. \$5.95 Net 2.19

Write for our Monthly Bulletins
 on Standard Radio Parts featuring
 Nationally Advertised Brands

HENRY O. BERMAN CO., Inc.
 10-12 E. LOMBARD STREET
 Dept. R-8 BALTIMORE 2, MD.
 Electronic Equipment and Replacement Parts

Mac's Service Shop
 (Continued from page 63)

wires and terminals you find in radio work are already tinned or can be easily made that way; so that takes care of number one. A good soldering iron, properly tinned and clean, takes care of number two. I have already told you how to tin the soldering iron, and don't ever let me catch you with it any other way. That thin coating of bright solder on the iron acts as a transfer agent to let the heat flow quickly from it to the connection being soldered.

"If possible, always hold the iron below the connection being heated," he went on. "Since heat rises, that speeds things up; but what is more important, excess solder will flow down onto the iron and stay there instead of falling inside the set where it could cause a short."

"I always thought you were supposed to pick up the solder on the iron and carry it to the joint," Barney said.

"That is okay if you are working in a tight place, but if you have room for both the iron and the solder—and you usually do—it is better to heat the connection for a few seconds before touching the solder to it. When the wires are already hot, the solder flows around them better. Don't take the iron away too soon, though, for you want to be sure to boil out the rosin that sometimes collects around a wire and makes a poor connection."

"Well," Barney said, poking around in the set, "here is one thing the character did a good job on. This coupling condenser certainly doesn't have any long leads. It is stretched tight as a fiddle string."

Without answering, Mac plugged the set in and turned it on. Then he tapped very gently with his pencil the condenser Barney was admiring. Every time he touched the condenser, the volume of the set would change abruptly, jumping first up and then down.

"What's the matter there?" Barney asked resignedly.

"The leads on that condenser were pulled so tight that the continuous strain has broken the connection between one of them and the foil. If he had left a little bit of slack in the leads, this would not have happened."

"Did the joker do anything right?" Barney asked.

Mac looked at the set meditatively. "Well," he finally said, "he didn't burn the insulation on any of the wires or melt the wax out of any of the condensers by not watching where he was putting his iron. That is to his credit. A good serviceman always clears things away and is careful so that his iron puts the heat just where he wants it and only where he wants it."

"He was really a dope," Barney mused. "Say, whose set is this that took such a beating?"

Mac picked up the tag and glanced

PRICES SLASHED
IN QUANTITY LOTS
 All New, Nationally Known Brands

CONDENSERS—Metal encased, oil impregnated tubular, 600 VDC, .1 mfd
\$8.49 per 100 \$69.00 per 1000

Filter Condensers—1500 VDC 1. mfd
\$39.00 per 100 \$295.00 per 1000

DOUBLE CUP TYPE #850—Silver Ceramic Condensers, 3000 Volts, 50 mmfd
\$12.95 per 100 \$98.00 per 1000

PILOT LIGHT ASSEMBLY—high grade movable lens and shutter
\$11.95 per 100 \$89.00 per 1000

RESISTORS—WL 10 watt, 75 ohm, adjustable
\$7.49 per 100 \$49.00 per 1000

RESISTORS—Wire wound cement coated 10-Watt, 10,000 Ohm
\$8.49 per 100 \$69.00 per 1000

JACKS—Famous make, JK34A short mid-gate phone type
\$8.95 per 100 \$79.00 per 1000

Shipping extra—Write for circular

ERIE SUPPLY CO.
 P. O. Box 907 Rochester 3, N. Y.

MAY SPECIALS

G.E. Plate Circuit Relay—10M Ohms—Operates on 8Ma or 110V D.C.—S.P.D.T. 95c; 10 for \$7.50.
 "Penwal" Thermo Switch; 0-400 degrees F-N.C. 25 amps @ 115V. List \$6.75. YOUR COST \$2.50; 10 for \$20.00.

OPERATES FROM A BEAM OF LIGHT
 Photo-electric relay kit complete with all parts including tubes, relay, sensitivity control and simple assembly instructions. Build your own magic eye alarm system—use light beam control. Only \$5.95.

LABS — SCHOOLS — INDUSTRIALS — GET ON OUR MAILING LIST—SEND US YOUR REQUIREMENTS.
 Allied relay-24v. d.o., d.p.d.t. 10 amp, contacts 75c; 10 for \$5.00

G. E. Solenoid operated contactor No. CR2820—controls 6 circuits—operates on 115V, 60 CY., 4 1/2 x 9 3/4, 15 amps contacts double break each circuit, G.E. Catalog price \$25.00. YOUR PRICE...\$5.95

4 mfd. @ 600V oil filled with mts. clamp 59c; 10 for \$5.00
 Leach 6V dc relay, 3 pole n.o., \$1.25; 10 for \$10.00
 UTC "S-6" input Xmtr.—line or mike to grid; dealer's price, \$3.10. Your cost, \$1.25; 10 for \$10.00
 Weston No. 476-3 1/2" Bakelite; 0-8V AC...\$3.95

Filter Chokes, 10HY, @ 160MA, 150 ohms res. \$1.25; 10 for \$10.00
 Westinghouse Filter chokes—4 hy @ 90 mhs, 300 ohms res. hermetically sealed 2 1/2" can 69c; 6 for \$3.00

25% deposit with order; balance C.O.D.; save C.O.D. charges—send full amount. Minimum Order, \$2.00.

RADIO DEVELOPMENT & SALES CO.
 323 Atlantic Ave. Brooklyn 2, N. Y.

AUDIO ENGINEERING SCHOOL

A practical 9 months' course in Sound Fundamentals, Recording, and Sound Transmission measurements; in a laboratory containing transmission sets, oscillators, square wave generator and intermodulation analyzer, and other equipment.

Complete recording studios assimilating broadcast, motion picture and commercial sound recording.

For information write
H. M. Tremaine, Director
SCHOOL OF SOUND RECORDING AND TRANSMISSION ENGINEERING
 1655-A Cherokee Hollywood 28, Calif.

RADIO BOOKS by mail

DOMESTIC Retail only. Same-Day Service on 95% of all orders. Order from us any radio book advertised in this magazine or elsewhere. Send stamp for catalog.

OVERSEAS We specialize in mail exports to all the world. Wholesale and retail. Send (local) stamp for details.

EDITORS AND ENGINEERS, Ltd.
 1302 Kenwood Road, Santa Barbara, Calif., U.S.A.

Wire, Tape, & Disc
RECORDERS
 Write for Our Free Catalog
 of Recorders and Accessories

ACME ELECTRONICS CO.
 6523 Euclid Ave. Cleveland 3, Ohio

YOUR COST

\$9.95



TRANSMITTER-RECEIVER BC 645

BC-645 ultra-high frequency transmitter receiver can be converted to operate on the 420 Mc band with few changes. It's surplus, brand new, packed in original carton—complete transmitter, modulator system and receiver. Comes complete with fifteen tubes. Well worth the price for parts and tubes.

10% Cash with Orders



Phone LO 3.9255

509 ARCH ST., PHILA., PENN.

ELECTRONIC DESIGN ENGINEER WANTED

Production Facilities... Capital... National Distribution Available for New Products in Television Field.

Write full details in first letter.

Box 459, RADIO NEWS
Empire State Bldg.
New York 1, N.Y.

HIGH PRECISION 100 Kc. CRYSTALS

Price \$3.95 each



(No C. O. D.'s. Please include 25c for postage and handling.)

Brand New Surplus at about 1/10 Gov't. cost. An ideal Frequency Standard for Amateurs, Servicemen, Laboratories, etc.

Exceptional Frequency Stability ± 15 cycles from -50° to + 80° c. (.0015) 10G Vibration Test. Calibrated at 30° c. Brand-New, Mounted in Sealed Cases as Shown.

ELECTRONICRAFT, Inc.
5 Waverly Place • Tuckahoe, N. Y.

In Indiana IT'S Stanton Radio Supply
521 State St.
HAMMOND, INDIANA

at it. "It belongs to a Mr. Johnson at 2320 East Linden."

"Mr. Johnson! 2320 East Linden—Why that's—I was the one who—" Barney sputtered and then stopped while brick-red flush crept up his neck and slowly spread over his face until he looked like a summer sunrise.

"Yeah, I know; but don't let it throw you, son," Mac said kindly. "He told me that he had let the young man next door work on it a couple of months ago, and I remembered that you lived at 2318 East Linden."

"I should have had more sense than to work on it—or better say butcher it up," Barney said bitterly; "but he kept insisting that if I knew enough to build a transmitter I ought to know enough to fix a five-tube receiver. That's what he thinks—or thought!"

"That's one of the worst things about being eighteen," Mac mused. "You simply can't say, 'I don't know'; you have to go ahead and prove that you don't know. Of course, there is some faint hope for you. If you live long enough, you may just possibly out-grow it."

At his teasing words, Barney's customary grin crept back across his face. "You say the nicest things, Mr. McGregor," he murmured.

-30-

ELECTRICAL EXPOSITION

PLANS are now underway for the First Annual All Electrical Exposition to be held in the Pan Pacific Auditorium, Los Angeles, August 20th through 29th.

Sponsored by the Southern California Radio and Appliance Association, Inc., the show will feature radio, television, and electrical appliances. Representatives of these various branches of the industry are serving on the Exposition Committee which is headed by Fred J. Tabery.

Famous radio and television shows will emanate from the Auditorium stage. Pageants, parades, contests, and special events will highlight the activities of the ten-day exposition.

-30-

UAL HAM NET

EIGHTY United Air Lines' employees, who are amateur radio operators in their spare time, are forming their own ham net.

One of the company's pilots, Captain John Pincomb of New York, is contacting all United hams and putting them in touch with each other. Captain Pincomb says the membership in this unique net extends across the airline's routes from New York to Honolulu and from Seattle to San Diego.

Tentative time for going on the air has been set for 8 p.m. daily, local time in each zone. Each ham will send out the call "CQUAL" to let his fellow company hams know that he is on the net and wants to chat.

The net will operate on 3510,7020 or 14,040 kc. in the 3.5, 7, and 14 mc. bands respectively. Call letters of Pincomb's station in New York are W2SIM.

-30-

Aviation RADIO and ELECTRONICS



Pay EMBRY-RIDDLE GRADUATES \$\$\$... with a real future

Embry-Riddle-trained aviation radio and electronics technicians and mechanics make top pay in important radio jobs everywhere.

The radio industry needs skilled men. Embry-Riddle has fully staffed, fully equipped laboratories and classrooms for radio and all standard aviation courses as well.

Excellent dormitories are available at Embry-Riddle. Use your opportunity for expert radio and electronics training in busy, beautiful Miami—gateway to radio opportunities and aviation hub of the Americas. Mail coupon for full information TODAY!

Authorized G. I. Training



Dean of Enrollments - Dept. 65 Embry-Riddle School of Aviation
PLEASE PRINT Miami 30, Florida


Name _____ Age _____
Address _____
City _____ State _____
I am interested in Flight Training Technical Training Check One: Veteran Non-Veteran

STUDY IN MIAMI... AIR CAPITAL OF THE WORLD

Order from ARCO

Exclusive Distributors in United States and Canada for Famous

El-Menco CAPACITORS

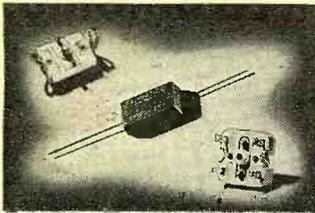

ARCO GIVES YOU THREE STAR SERVICE

- ★ **SPOT DELIVERY** — Orders shipped same day they're received.
- ★ **LOW COST** — Maximum discounts to jobbers and low net costs to manufacturers, other large users.
- ★ **QUALITY** — Wherever product performance is paramount, El-Menco is preferred.

Send Your Condenser Television Requirements to us for Recommendations

New Products: — CM 10 Miniature type capacitor size 9/32" x 1/2" x 3/16", from 2.5 mmfd to 200 mmfd. 500 working volts. New line of capacitors for television, industrial and transmitting uses from 5 mmfd. to 5100 mmfd. in 1,000 and 1,500 working volts, in RCM 20, RCM 35 and RCM 40 cases.

Attention Sales Representatives: Several good territories available. Write for complete information

ARCO Send for Latest Brochure ELECTRONICS, Inc.

135 Liberty Street, New York 6, N. Y.
Contact Al Rothenstein or Ben Stanley at the Stevens.

WAR SURPLUS BARGAIN SPECIAL!

Brand New BEAM ANTENNA ROTATOR MOTOR

\$595

Postpaid in U.S.A.



- OPERATES DIRECTLY ON 110V AC (Requires only 12 MFD Condenser)
- NO STEP-DOWN TRANS. NEEDED
- NO LINE RESISTOR NEEDED
- HIGH TORQUE — NO FREE SWING
- APPROX. 3/4 R.P.M.
- REVERSIBLE — ONLY THREE WIRES NEEDED
- FINE FOR TELEVISION & HAM USE
- LIGHTWEIGHT, RUGGED, QUIET
- MOTOR & GEARS OIL SEALED
- NO EXPENSIVE CONVERSIONS
- FLAT MOUNTING SURFACE — FOUR TAPPED HOLES

ALVARADIO SUPPLY CO.

Dept. RN2, 903 So. Alvarado
Los Angeles 6, California

NOW... 120 PAGE SURPLUS CONVERSION MANUAL

SCR 522 BC 342 1068A/1161A
BC 412 (Tel. Rec.) BC 312 TBY
BC 348 BC 645 SCR 274N
PE 103A BC 946B (Rec. & Trans.)
BC 221

The above items are just a few of the many surplus conversions, along with complete instructions and original Schematic of every unit, plus approx. 35 photos and explanatory diagrams. Plus — 11 page listing & description of available electronic surplus — Cross index of A/N tubes vs commercial types — Amateur frequency chart — Commercial television & FM chart, etc.

\$250

Postpaid

TECHNO-GRAPHIC PUBLICATIONS

Post Office Box 877
Los Angeles 35, California

Classified

Rate 20c per word. Minimum 10 words.

RADIO ENGINEERING

RADIO Engineering Broadcasting, Aviation and Police Radio, Servicing, Marine Operating and Electronics taught thoroughly. Expenses low. Write for catalog. Valparaiso Technical Institute, Dept. N, Valparaiso, Ind.

FOR SALE

IDEAL Chargers for 2-volt batteries, list, \$4.95; in quantities, 98¢; sample, \$1.75. Motelectric Products, Asbury Park, N. J.

NEW and used Collins, Hallicrafters, National, Hammarlund, RME, Millen, Meissner, other receivers, transmitters, test equipment, amplifiers, etc. Lowest prices. World's best terms. Shipped on approval. Write Henry Radio, Butler, Mo.

AMATEUR Radio Station. Only \$24.50. Receiver & Transmitter 10-40-75 meter. For details write. Stanley MacMichael, c/o R & M Radio Co., 1426 N. Quincy Street, Dept. RN-1, Arlington, Va.

WIRE Recorder Magazine new made by W.E. Completely assembled time indicator, steel wire etc. Price, \$25.00. John Kish, 6226 Kendal, Dearborn, Michigan.

NC-57, BRAND new with Bug Key, Transmitter, parts, \$87.50. Gene Taylor, Johnstown, Nebraska

RADIO Tubes, Bargains. National advertised radios, test equipment, etc. Address Radio Tubes, Box 108, Elizabeth City, N. C.

PANELS, magnesium; machines, painted, engraved. Gilpin, Box 638R4, Mt. Clemens, Michigan

YOU can accurately align Superheterodyne receivers without signal generator. Complete instructions, \$1. Moneyback Guarantee. Chas. Gates, Pecos 1, Texas

ERECO Beam Rotator. 110 VAC, Heavy duty, variable speed, selsyn indicator, weather-proofed. Complete indicator and rotator ready to plug in, \$69.95. Satisfied users all over the country. Buy from your dealer or direct. Free literature. Dick Rose, Eresco, 2912 Hewitt, Everett, Washington

WRITE dept. RN18 for our free wholesale list of Radio parts & accessories. R.C. Radio Parts & Distributing Co., 731 Central Ave., Kansas City 6, Kansas

LOWEST Prices. Radio Tubes, parts. Bargain lists 3¢. Potter, 1314 McGee, Kansas City 6, Mo.

WIRE, for Webster, Sears, Air King and other Recorders, 1/2 hour spool, \$2.90, 1 hour, \$4.95. Air King Wire Recorder, \$129.50 complete. McCoy Sales Company, P. O. Box 335, Berea, Ohio

V.O.M. ASSEMBLY. Consists of 18 wire-wound, non-inductive, precision resistors mounted and fully wired on low-loss, wafer-type, rotary switch, ready to connect to your meter to make highest grade instrument. While they last price, \$2.50. Radioco, 1110 Marshall Bldg., Cleveland, Ohio

GOING Out of Business Bargains. G.E. Tube Tester (model TC-3) \$40. Webster Wire Recorder, \$125. Many other bargains. Write: Willis, 61 Hayes Ln., Wilkes Barre, Pa.

JENSEN JAP60, \$40. JHP-52, 35. A121 Bass reflex, \$15. R.C.A. Vertical lateral pick-up M14875, \$75. Lyle Babbitt, RFD 2, Watertown, N.J.

INDISPENSABLE to the practical radio man who wants to keep ahead, Practical Wireless, Britain's leading radio monthly, provides many new ideas for radio workers and experimenters. This journal contains details of latest British radio and television developments, fully explained by experts. Constructional data on all types of radio receiver are a feature. Important circuits are described and analysed, with explanatory diagrams and drawings. Other features include advise bureau, Trade news, and valuable help on every kind of radio problem. Annual subscription (12 issues) only \$2.00 from Practical Wireless, U.S. Subscription Office (Dept. 5), 126 Lexington Avenue, New York, N.Y.

POWER supply, 950 volts 250 mils, choke input, \$40; BC375 transmitter, two tuning units, amateur bands, variometer, \$30. F.O.B. Frank Assenmacher, Mary-Knoll, N. Y.

AMPLIFIER ACA-100DC manufactured by Amplified Corp. of America. Excellent condition. Good price. A. V. Donnelly, 13 E. Burlington St., Iowa City, Iowa.

HEARING Aids. Zeniths, others. All used but working. Make miniature transmitters or receivers. Complete with cords, ear piece. \$20.00 ea. Shelby Instrument, 321 W. 7th, Long Beach, Calif.

RADIOS, record players, tubes, parts. Send for free bargain list. Hallmark, 592A Communipaw, Jersey City 4, N. J.

NEW Hallicrafters S-36H V.H.F. 27.8 to 143 M.C., F.M., A.M., C.W., \$150.00. F.D. Less, 111 E. John, Seattle, Washington.

SELENIUM Rectifiers, full wave, 1/2 ampere, \$1.85; 1 ampere, \$2.50. Half wave 5 amperes, \$4.50; 2.2 Amperes, \$2.25; 1.5 ampere, \$1.85. Bulletin, Bursma Radio, Route 5, Grand Rapids, Mich.

TELEVISION components for assembly of a modern 52 square inch screen receiver using the newest circuits and tubes. The only kit on the market featuring an aluminumized cathode ray tube, A.F.C. on horizontal sync and a wired, pre-aligned r.f. tuner covering any combination from 1 to 13 television channels. Sound and Picture IF's are on one sub-chassis using new 6AH6 miniature tubes having a gm of 9000. The IF Strip and the 9000 volt RF Power Supply are sold in kit form. The main chassis is sold with all holes punched, with suggested chassis layout print. All components individually priced. Our catalog lists television components exclusively and shows parts and circuits of the "hard to find items". You have been looking for. Send for it today. It's free. Television Specialties Co., 315 Madison St., Oak Park, Ill.

BRAND new W E C O Surplus wire recording magazine extra spool of wire, \$30.00. "Record". Featon, Mich.

NEW cartoned tubes 39¢ each. 100 assorted for \$35.00. 1R5, 1S5, 1T4, 1U4, 1U5, 3Q4, 3S4, 5Y3gt, 6A8gt, 6C5gt, 6F9gt, 6C5gt, 6J5gt, 6J7gt, 6SQ7gt, 6SK7gt, 6SA7gt, 6AK5, 6AQ5, 6AT6, 6BA6, 6BE6, 6BH6, 6BJ6, 6K7gt, 6Q7gt, 6V6gt, 12AT6gt, 12BA6, 12BE6, 12J5gt, 12SA7gt, 12SK7gt, 12SQ7gt, 12SJ7gt, 25L6gt, 32L7gt, 35B5, 35W4, 35Z5, 47, 50B5, 50L6, 70L7gt, 117Z3, 117L7gt. Write for bargain flyer. Henshaw Radio Supply, 3313 Delavan, Kansas City 2, Kansas.

NEW GE Pyranol Capacitors; 1000 WVDC, 25 mfd, \$1.25; 2000 WVDC 2 mfd, \$1.75, 10 mfd, \$2.00 15 mfd, \$2.60; Aerovox 3000 WVDC, 2 mfd \$2.95; Sprague 7500 WVDC, 2 mfd, \$5.50; 30 WVDC, 1500 mfd 2 for \$1.00; Sigma sensitive relays, 3 ma dc 3500 Ohm coil, \$.50 (list, \$7.00), 1.6 ma dc 10,000 ohm coil \$.75; Tubes new cartoned, 829B, \$3.00; 826, \$1.95; 838W, \$3.50; 2x2, \$.75; 6Y6G, 6AC7, 6SN7, \$.25; 1624, 1625, 1641, 955, 956, 9002, 9005, \$.50; TS-15C Handsets new, \$2.95. SKL Laboratory, Box 188, Lexington 73, Mass.

WANTED

WANTED for cash 100 to 500, 5 or 6 tube 2 or 3 band table models Battery (A.B. Pack) operated Radios. Radio Supply Co., P. O. Box E-5191, St. John's, Newfoundland

WANTED. Radiola 66 and RCAM 96-T-2 receivers in working condition. Will pay any reasonable price. Box 460, c/o Radio News, 185 N. Wabash, Chicago 1, Ill.

HELP WANTED

INSTRUCTORS in Radio-Electronics and Television. Prefer former Navy Radio Technician Instructors with Teacher Training. Must be willing to locate in Detroit, Michigan. Write to Box 452, c/o Radio News, 185 N. Wabash, Chicago 1, Ill.

PATENT ATTORNEYS

LANCASTER, Allwine & Rommel, Registered Patent Attorneys, Patent Practice before U.S. Patent Office. Validity and Infringement Investigations and Opinions. Booklet and form "Evidence of Conception" forwarded upon request. Suite 414, 815 15th St., N.W., Washington, D.C.

PATENT Attorney, registered U.S. Patent Office. I. Jordan Kunik, 75-F Pearl, Hartford, Connecticut.

CORRESPONDENCE COURSES

USED Correspondence Courses and Books bought, sold, rented and exchanged. Catalog free. Lee Mountain, Pisgah, Alabama.

AMATEUR radio licenses. Complete code and theory preparation for passing amateur radio examinations. Home study courses. American Radio Institute, 101 West 63rd Street, New York 23, N.Y.

LEARN Elements of radio at home. Ideal course for beginners. \$15.00. Write Waca Radio School, 1421 Sixth Street S.E., Minneapolis, 14, Minn.

MISCELLANEOUS

PERMANENT-Magnet Motor. Be wise; think hard; learn how the impossible is made easy solving by the Elliptical Solution. In all History the only solution brought forward which shows a 26% & 37% gain or loss of weight by "Newton's Universal Known Law." Complete 26% data-Conquering Gravitation-plus 15"x21" drawing, \$1.25. Complete 37% data-Gravitation Conquered-by extended elliptical orbits-plus 15x21" drawing, \$1.25. Both sets, \$2.25. Specification & prints of First Permanent Magnet Motor in all History, \$10.00. All Three sets, \$12.00. New ideas wanted, \$1,000.00 offered for ideas accepted. George J. Altman, Elliptical Orbit, Eng., 150 Broadway, New York 7, N.Y.

QSL'S? SWL'S? "America's Finest." Samples, 10¢. Sakera, W8DEP-Press, Holland, Mich.

PHONOGRAPH Records 20¢. Catalogue free. Paramount, NK-313 East Market, Wilkes-Barre, Pa.

RADIOMEN, Servicemen, beginners, make more money easily, quickly. \$250. Weekly possible. We show you how. Information free. Merit Products, 216-32R 132nd Avenue, Springfield Gardens 13, N. Y.
26 YEARS experience radio reaping at your fingertips. I've repaired 45000 radios. Have perfected simple system you can follow step by step. No calculations or formulas. Total price, \$2.00 postpaid or C.O.D. Money back guarantee. Ross Radio, 14615-C Grand River, Detroit 27, Mich.
RUBBING cones on "non-adjustable" speakers quickly and easily repaired. Complete instructions 25¢ coin. Blake Radio, 2215 19th, Lubbock, Texas
BC-348-J, K, Q. OWNERS only. Special Service Manual now available. Contains Schematic, Wiring Diagrams, Alignment, etc. \$1.00. John W. Martin, 3516 Sacramento, El Paso, Texas


Photo Credits

Pages	Credit
40,41	Bendix Radio
42	Joe Tillotson
43	Acme
45	The Daven Company
46,47	Pioneer Electric & Research Corp.
51	Premier Crystal Laboratories, Inc.
60,61,144	Arthur Haug, Staff Photographer
69,71,128	Sylvania Electric Products, Inc.
72	Station HCJB, Quito
74	Radio Corporation of America
94	Australian News & Information Bureau
136	Minnesota Mining & Manufacturing Co.
140	U.S. Army Signal Corps
154	Eastern Air Lines

LOOK AT THESE BARGAINS!

BC-223 TRANSMITTER

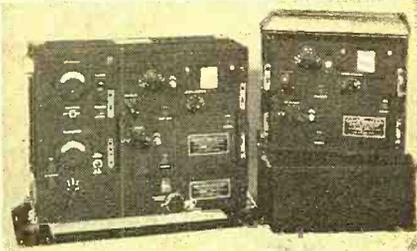Frequency coverage 2000 KC to 5250 KC. Four pre-selected Crystal Frequencies or M.O. Control. Uses 801 OSC. 801 PA - 2-16 Modulator, and 1-46 speech amplifier. Output 10 to 25 Watt on C. W. phone or tone. Complete with Tubes, Freq. Charts, Schematics, Tuning Units in Cases, Cables, Shock-mounted base. Less crystals and power supply. Operation 12 or 24 volts. **\$29.50**
 Brand New



GASOLINE ENGINES

12 D.C. Volt—750 Watt Output. Delco Engine, Self Starter, Voltage Regulator. Reconditioned and tested before shipping. \$59.50
 24 to 30 Volts—1500 Watt Output Homelite Engine—Voltage Indicator. Reconditioned, Tested before shipping

WHIP ANTENNA With MOUNTING

Mast Base Metal Mounting with heavy vertical coil spring made to receive mast sections MS-52, 53, 54. **\$2.95**
 Whip Antenna, mast sections 3 ft. lengths, screw in type used with above Mast Base. Bottom section MS-51— $\frac{3}{8}$ " diameter. Other sections MS-53 to 49 taper down. Antenna can be used any length. Minimum order, four sections. New \$0.50 per section.
 Guy Set: Used for lashing antennas & poles. Includes 125 ft. weatherproof rope, 4 pulleys, 3 clasps, & mounting rings with adjusters. \$1.95



MISCELLANEOUS MAY SPECIALS

2 Volt Willard Storage Battery, BB 54-30 A.H. Ea. \$1.50
 Aluminum Case for carrying 3 above cells, with connectors. Ea. \$1.00
 24 Volt Transformer: Sec. 110 Volt, 60 cycle PRI. 1 Amp. \$2.00 ea. .5 Amp. \$1.39 ea.
 Relays—3 Assorted

SELSYN

Model 2J1G1 can be used on 110 Volt, 60 cycle. Suggested wiring included. Used, but in excellent condition, only \$3.50 per set.
 Write for prices on larger sizes of Selsyns.



TUBES—New, Boxed

\$14 \$3.95 807 \$1.10
 VR-90 \$0.69 21-G \$0.69
 All Tubes Guaranteed.

Mounting Bases: FT-154 for BC 348-224. \$1.50
 FT-151 for BC 375-191


CONDENSERS:

100 Asst. 40- $\frac{1}{2}$ W 40- $\frac{1}{2}$ W 20-1W \$1.69
 25 Asst. 10 to 25 Watt \$2.00
 50 Asst. Micacs. \$1.00
 Condenser Bank 1-2-1-4-600 Volt, housed in Metal Box with slide fastener cover, Size 6 $\frac{1}{2}$ x4 $\frac{1}{2}$ x5" \$1.95
 1 Mfd. 5000 Volt in Test Set with High Voltage Leads and Asst. Parts. \$5.95
 25 Mfd. 1000 Volt DC-2000 Volt Int. G.E. Pyranol Capacitor. (Used in photo flash outfits)

ALL EQUIPMENT IS NEW UNLESS OTHERWISE STATED

FAIR RADIO SALES
 223 S. MAIN ST. LIMA, OHIO

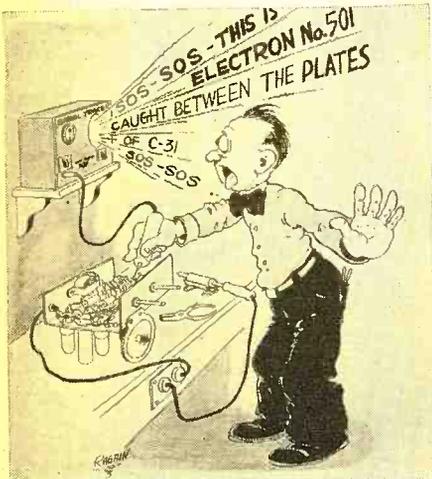
MINIMUM ORDER—\$2.00
 Prices are F.O.B. Lima, Ohio
 25% DEPOSIT ON C.O.D. ORDERS



WHY PAY MORE?

SIGNAL GENERATOR

ONLY **\$1295**

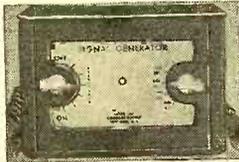

456 KC-465 KC-600 KC-1400 KC

A new, compact, accurate, inexpensive, well-built Signal Generator, Model 522, is now ready for immediate delivery. The 522 is calibrated against crystal controlled standards within 1% accuracy, for the above frequencies. Two open switch positions are provided for the addition of special frequencies for individual needs of the user. This excellent unit is ideal for on-the-spot checking and aligning. The 522 is isolated for safe use on AC-DC sets. Alignment of short wave band possible due to strong even harmonics of 1400 KC-2800 KC-5.6 MC-11.2 MC.

- COMPLETE WITH TUBES READY TO OPERATE
- COMPLETE CRACKLE-FINISH CABINET
- TWO OPEN CHANNELS FOR ADDITIONAL FREQS.
- INDIVIDUAL TRIMMERS FOR RE-CALIBRATION
- SHIELDED OUTPUT LEAD
- FULLY GUARANTEED—FULL INSTRUCTIONS

WRITE FOR DESCRIPTIVE LITERATURE

CONSTANT ELECTRIC
 112 CORNELIA ST B Klyn 21, N. Y.

RISCO HAS IT

All Changers Brand New

V. M. MIXER CHANGER
 PLAYS 10" and 12" Records at the same time.
 DETROLA ... \$13.75
 GI RECORDERS
 Single Speed 22.00
 Dual Speed 26.00
 40% OFF ON RECORDISC. RECORDING BLANKS




\$15.50

Above Easily Attached to Any Radio or CAN BE USED WITH AMPLIFIER BELOW
 ALLIANCE PHONO MOTORS \$2.50
 ASTATIC or SHURE PICKUPS 1.79

PHONO AMPLIFIER 3 TUBE AC-DC

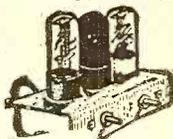Wired Vol. & Tone Control \$2.75
 Uses 12SQ7, 50L6, 35Z5.
 Wired & Tested
 Set of 3 Tubes \$1.95
 Output Trans.39
 5" Alnico Spk. 1.19



PHONO OSC-2-TUBE
 Wired & Tested 2-Tubes—\$1.50 \$2.75

VISIT OUR NEW SHOWROOM
 25% on C.O.D. orders. Orders Filled as Received.
 Free Catalog "R" Just Out.
 We Specialize in Mail Orders.

25 W. BROADWAY NEW YORK 7, N. Y.

RISCO ELECTRONICS
 WHOLESALE DISTRIBUTORS

Musical Distinction WITH ABSOLUTE FIDELITY AMPLIFICATION



A new amplifier development now enables you to clearly identify all the instruments in a full orchestral! If you are one of those discriminating persons for whom anything less than the best is a disappointment, you are one for whom the ACA—100 Amplifier was designed. Send for literature.


AMPLIFIER CORP. of AMERICA

398-2 Broadway, New York 13, N. Y.

WAR SURPLUS AND OTHER BARGAINS

POWER DRIVEN ANTENNA REEL

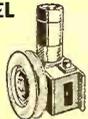1/4 HP. G. E. Motor—12-24V. Removable 6" Reel. Com. worm gears, bevel gear. Solenoid clutch. In gear only when current on. Operates clockwise or counter clockwise. Ideal for power fish line, opening or closing doors, auxiliary power take-off. Can be used as buffing machine or for dozen of other uses. New. Weight 6 Lbs. \$4.50 each




CLIPS: Rubber lined, aluminum, hundreds of uses in any shop. Assorted sizes, all new. 5 Doz. \$1. - 500 \$5.

SEND CHECK, MONEY ORDER, OR CASH

VOLTAGE REGULATOR

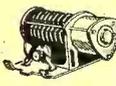Like new 24 V Corban Pyle Type Eclipse Westing house or Leece Neville Mfr. Weight 2 1/2 Lbs \$5.50 each



HIGH SPEED DRILL BITS

Like new! Original value over \$16.00 25 assorted sizes & lengths \$2.50.



ROUTER BIT ground for BORING BAR: High speed steel, right hand, single flute, 1/2" bit, straight shank for 3/4" chucks. Ideal for every machine shop. Like new, original cost about \$10. 3 for \$2



SEE LISTINGS IN CATALOG OR C. D. ORDER

TRANSFORMER: Jefferson Electric step up or step down transformer. Input, primary 110-117 Volts A.C. Output, from 5 Volts to 650 Volts. Suitable for use with war surplus gadgets, heater relays, radio test filaments, electric trains, house chimes, etc. Weight 10 Lbs. New \$7.95 Each



ALL PRICES FOB CULVER CITY, CALIF.

MICROMETER


Chrome plated, precision engineered and carefully tooled to give long life. All new 0-1" capacity, \$2.25. 1-2" capacity, \$3.50 Each.



AIRBORNE SALES CO., INC. DEPT. RN-5-B CULVER CITY, CALIF.

PORTABLE A. C. AMPLIFIER

(Lic. by W. E.)

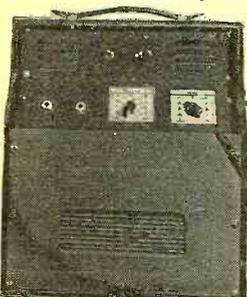

Here is a professional type HIGH FIDELITY unit at an amazingly low price. Wide freq. response for use with Musical Instruments, Speech or Phono input, FM Tuners, etc. 110V, 60 Cycle. Features: 8" Alnico PM speaker; 2 inputs (magnetic or crystal); vol. & tone controls, Beam Power output. Beautiful, sturdy 2 tone brown leatherette case (15" x 15" x 7 1/2"). Shpg. wt.

12 lbs. List price—\$64.50. LEOTONE'S PRICE—While They Last \$24.95 In lot of 3—ea. 21.50 20% DEPOSIT REQUIRED ON C.O.D.'s LEOTONE RADIO CO. 65 DEY ST., NEW YORK 7, N. Y.

RADIO

Technician and Radio Service Courses FM and TELEVISION

American Radio Institute 701 West 63rd St., New York 23, N. Y. Approved Under GI Bill of Rights Licensed by New York State

DG1B CONSTANT VELOCITY FREQUENCY RECORD

Here's an indispensable guide for fast, accurate, direct checking of phono pick-ups and indirect checking of recording heads, loud speakers, p. a. equipment, etc. 12" double-faced Vinylite record. 78 RPM—recorded in 3 sections, 50-10,000 cps, 400 cps, 1,000 cps. Lists \$3.50 ea.—see your distributor or write—

UNIVERSAL MICROPHONE CO. INGLEWOOD, CALIFORNIA

INDEX OF

Advertisers

MAY 1948

ADVERTISER	PAGE	ADVERTISER	PAGE
Abell Distributing Co.	177	G & E Equipment Supply Co.	155
Acme Electronics Co.	196	G & G Radio Parts Service.	143
Adaptol Co.	134	G & M Equipment Co., Inc.	181
Airborne Sales, Inc.	200	General Cement Mfg. Co.	80
Allied Radio Corp.	9	General Electric Company.	25, 77, 202
Almo Radio.	197	General Electronics Distributing Co.	153
Alvarado Supply Co.	190, 198	General Test Equipment.	163
American Phenolic Corporation.	151	General Salvage Co.	184
American Radio Institute.	200	Goodheart, R. E.	142
American Surplus Products Co.	99	Greenlee Tool Co.	172
American Television and Radio Co.	189	Greene Radio Distributing.	162
Amperite Company.	138	Greenwich Sales Co.	196
Amplifier Corp. of America.	106, 193, 199	Greylock Electronic Supply Co.	163
Arco Electronics.	198		
Armed Forces Communications Association.	106	Halicrafters Radio.	5
Arrow Sales, Inc.	110, 111	Hardin College School of Radio Electronics.	155
Ashe Radio Co., Walter.	141	Harvey Radio Company, Inc.	132
Atlas Sound Corp.	100	Heath Company.	102, 103
Audel Publishers.	120	Henry Radio Stores.	167
Audio Development Co.	175	Hollywood Sound Institute.	158
		Hytron Radio and Electronic Corp.	27
Baltimore Technical Institute.	114		
Bardwell & McAlister, Inc.	164	Illinois Condenser Corp.	130
Bell Telephone Laboratories.	35	Indiana Technical College.	163
Berman Co., Inc., Henry O.	80	International Resistance Co.	31
Beta Electronics Corp.	146	Instructograph Company.	152
Birth-O-Gram Company.	177		
Bliss Electrical School.	187	JFD Mfg.	146
Boland & Boyce Inc. Publishers.	89	Jensen Industries.	201
Brooks Radio Distributing Corp.	144	Jensen Mfg. Co.	14
Bruce Electronics Co.	82	Johnson Company, E. F.	130
Buffalo Radio Supply.	96, 97	Johnson's Fair.	148
Burlington Instrument Co.	106	Joseph, Irving.	129
Burstein-Applebee Co.	159		
Business Specialties Engineering.	178	La Pointe Plascomold.	8
		Lake Radio Sales Co.	142
C-B Mfg.	187	Leads Radio Co.	173
Candler System Co.	113	Le-Hi Electrical Company.	179
Canon Electric Development Co.	18	Leotone Radio Co.	108, 200
Capitol Radio Engineering Institute.	81	Lincoln Engineering School.	195
Centralab, Division of Globe Union, Inc.	12, 13	Liquid Lens Corp.	187
Chicago Industrial Instrument Co.	178		
Chicago Transformer, Division of Essex Wire Corporation.	Second Cover	MCN Corp.	194
Christy Supply Company.	190	Mallory & Co., Inc., P. R.	21, 3rd Cover
Cinaudagraph Speakers, Division of Aireon Mfg. Corp.	151	Makan Inc. Electronics.	194
Cleveland Institute of Radio Electronics.	38	Marco Electronics, Inc.	154
Collins Audio Products Co.	189	Martin School of Radio Arts, Don.	185
Columbia Wire & Supply Co.	122	Melehan Radio Products Co.	196
Commercial Radio.	177	Melville Radio Institute.	152
Commercial Radio Institute.	180	Merit Coil & Transformer Corp.	20
Communications Equipment Co.	145	Merit Radio Supply Co.	176
Concord Radio Corp.	30	Mid-America, Inc.	135
Constant Electric Company.	199	Milwaukee School of Engineering.	194
Coradio.	182	Minnesota Electronics Corp.	115
Coyne Electrical & Radio School.	173, 186	Montgomery Ward.	98
Crystal Devices Co.	158	Morts Radio Shack.	125
		Moss Electronic Distributing Co.	121
DeForest's Training, Inc.	19	Murray Hill Books, Inc.	95, 104
Delehanty School of Television.	148	McCoy Sales Co.	195
Dow Radio.	175	McGee Radio Company.	83, 84, 85
Duotone Company.	192	McGraw-Hill Book Company.	180
		McMurdo Silver Company.	32
Editors & Engineers, Ltd.	196	National Equipment & Supply Co.	114
Edlle Electronics.	166	National Polytronics.	201
El-Monte Electronic Supply Co.	155	National Radio Institute.	3
Electric Sweeper Service Co.	193	National Schools.	23
Electro Products Laboratory.	170	Newark Surplus Materials Co.	147
Electro-Voice, Inc.	82	Newcomb Audio Products Co.	113
Electronic Corp. of America.	165	Niagara Radio Supply Co.	117, 150, 168
Electronics Institute, Inc.	179	Northern Products Co.	182
Electronic Sales Co.	118		
Electronic Supplies.	88	Offenbach & Reimus Co.	169
Electronicraft Inc.	194, 197	Ohmite Manufacturing Company.	16
Ellis Co., Franklin.	142	Olson Radio Warehouse.	131
Embry Riddle School of Aviation.	197	Opad & Green Company.	148
EPCO.	92, 176	Operadio Mfg. Co.	119
Ereco (Dick Rose).	164		
Erie Supply Co.	196	Pa-Kette Radio Co.	148
Esege Sales Co., Ltd.	154	Peak Electronics Co.	156
Espey Mfg. Company, Inc.	163	Peerless, Inc.	113
Esse Radio Company.	149	Permoflux Corp.	167
		Photocon Sales.	157
Fair Radio Sales.	199	Pittsburgh Coil Company.	195
Federated Purchaser, Inc.	94	Plastics & Electronics Company.	194
Feller Engineering Company.	151		

ADVERTISER	PAGE
Polin Sales, A. O.	190
Potter Radio Company.	118
Premax Products.	128
Progressive Electronics Co.	137
Quam Nichols Company.	152
RCA Institutes, Inc.	191
R & M Radio Company.	90, 91
Radiart Mfg.	22
Radio Center.	171
Radio Craftsmen, Inc.	118
Radio Development & Sales Co.	198
Radio Distributing Co.	191
Radio Electric Service Co.	180
Radio Ham Shack.	133
Radio Hospital.	82
Radio Institute of Chicago.	122
Radio Kits Company.	184
Radio Maintenance.	124
Radio Parts Company.	157
Radio Parts Distributors.	126
Radio Press.	185
Radio Supply & Engineering Co.	154
Radio Wire Television, Inc.	28
Radiomart, Inc.	183
Radionic Equipment Co.	193
Radolek Company.	138
Ravac Electronics Corp.	126
Ray-lectron Company.	114
Rider Publisher, Inc., John.	24
Risco Electronics Wholesale Distributors.	199
Rose Company.	80
SNC Manufacturing Co., Inc.	6
Sams Company, Howard W.	37, 107
School of Sound Recording & Transmission.	196
Schuh's Radio Parts.	134
Seeburg Corp., J. P.	183
Senco Radio, Inc.	136, 179
Servo-Tek Products Co.	161
South River Metal Products Co.	128
Spellman Television.	118
Sprague Products Company.	28
Sprayberry Academy of Radio.	7
Stahl, Inc., Michael.	109
Standard Electrical Products.	189
Standard Radio & Electronic Products Co.	127
Standard Transformer Corporation.	17
Stanton Radio Supply.	197
Sterling Electronic Company.	177
S & S Radio.	130
Sun Radio & Electronics Co., Inc.	144
Sun Radio of Washington D.C.	93
Supreme Publications.	87
Surplex Retail Sales, Inc.	186
Sutton's Wholesale Electronics, Bill.	187
Sylvania Electric Products, Inc.	Fourth Cover
TAB.	101
Tape Tone Mfg. Co.	122
Tarrytown Metal Craft Corp.	192
Technical Radio Parts Co.	138
Techno-Graphic Publications.	198
Tel-Craft Co.	174
Telecraft Corporation.	178
Television Assembly Co.	15
Television Industries.	139
Television Specialties Corp.	168
Telex, Inc.	181
Test-Craft Instrument Co.	123
Thor Electronics.	158
Thordarson.	10
Tradio, Inc.	164
Transvision, Inc.	79
Transvision of Calif.	172
Triplett Electrical Instrument.	29
Tri-State College.	194
Turner Company, The.	34
United Condenser Corp.	113
United Surplus Materials.	185
Universal General Corp.	195
Universal Microphone Company.	200
University Loudspeakers, Inc.	140, 168
Valparaiso Technical Institute.	174
Van Nostrand Company, Inc., D.	195
Variety Electric Co.	146
Waldref Co., The.	178
Ward Leonard.	155
Ward Products Corporation.	11
Weller Manufacturing Co.	134
Wells Sales, Inc.	36
Western Radio Co.	105
Western Radio Communications Institute.	185
Western Sound & Electric Labs., Inc.	170
Westinghouse.	33
World Radio Laboratories Inc.	191

NEW JENSEN SALES-KIT
Introductory Offer

This handy, pocket-size SALES-KIT holding six Jensen phonograph needles is just the thing for Radio Servicemen to take on service calls. Contains 3 of the famous Jensen Royal Jewel Genuine Sapphire needles retailing at \$2.50, and 3 of the Jensen Classic needles at \$1.50. It helps demonstrate fine needles, sells on sight, adds \$\$\$ to your income. Needles are individually packaged in gold, red and black containers. What's more Jensen needles assure full, clear tone of the instruments you repair, make all records sound better.

Mail us your order for one SALES-KIT at \$6.00 with the name of your distributor and a \$1.50 Jensen Classic Needle will be sent to you FREE.

JENSEN INDUSTRIES, Inc., 327 SOUTH WOOD ST. • CHICAGO 12, ILL.

"Sensational" . . . IS THE WORD FOR
THE NEW SYMPHONIC WIRE RECORDER

So much **QUALITY** at so low a price has never been heard of before.

Offers Ten-Minute Continuous 3-WAY AUTOMATIC RECORDING at low operating cost.

At the flick of a switch the SYMPHONIC Wire Recorder automatically RECORDS, ERASES, and RE-RECORDS. Everybody can use it with best results to record Music, Speech, Business Conferences, Off-the-Air, and a thousand other uses. Each spool gives TEN MINUTES of continuous recording.

REELS MAY BE CHANGED IN 15 SECONDS
This EXCLUSIVE FEATURE allows continuous recording for many hours and easy selection of the desired recordings.

Here at last is a WIRE RECORDER that completely fills the bill for a high-quality popular-priced recorder. Complete with self-contained amplifier and microphone, the SYMPHONIC Wire Recorder is compact, sturdy, and smart looking. It has been designed to be fool-proof and simple in operation, yet it maintains specifications found only in the highest price recorders.




Model 5-A
only \$89.50 list
Complete with 10-minute spool of wire and microphone.

EDITING IS EASY. No technical "recording knowledge" is required to operate the SYMPHONIC Wire Recorder. Editing is done by erasing, or cutting the wire and tying with a square knot.

TECHNICAL FEATURES:


- Records for ten minutes at 2' per second.
- Rewinds at 4' per second.
- 2 Watt AC-DC amplifier with 5 inch Alnico speaker.
- Frequency response 100 to 6000 C.P.S.
- High-quality, hand type crystal microphone.
- Carrying weight 20 pounds.

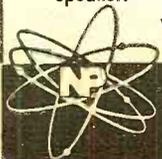Write Dept. RN for name of your nearest supplier



NATIONAL POLYTRONICS, Inc.
2430 Atlantic Avenue Brooklyn, N. Y.

The true test of performance— **DEMAND**

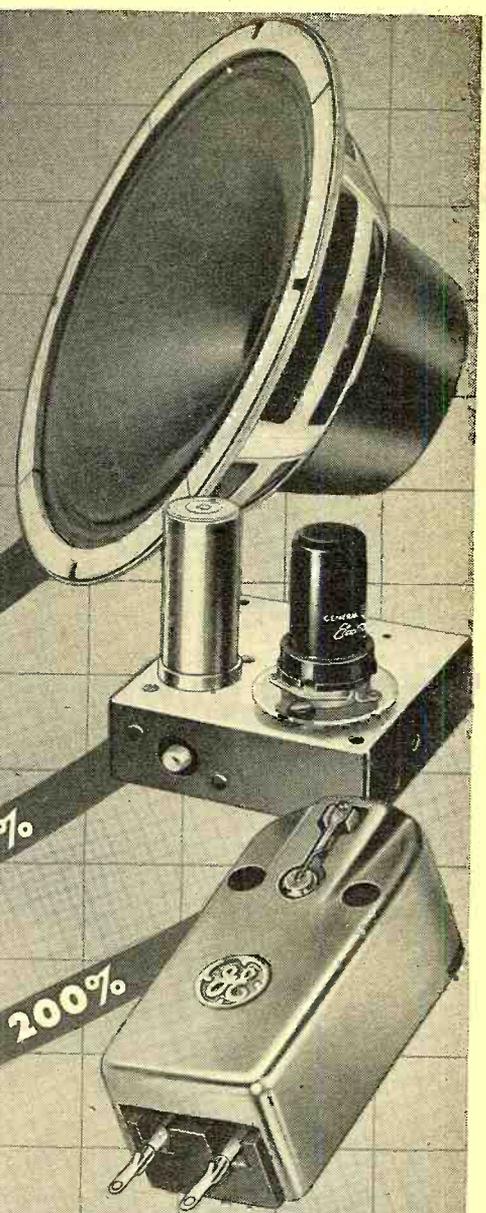

G-E Speaker Sales **UP—NEARLY 100%**
 "The Speaker with the Aluminum Foil Base Voice Coil"

G-E Pre-Amplifier Sales **UP—OVER 100%**
 "The Important Link for Adapting the Pickup"

G-E Variable Reluctance Pickup Sales **UP—OVER 200%**
 "The Pickup They're All Talking About"


Up—Up—Up—go sales on these fast-moving G-E products that every service man needs—day in and day out.

The figures shown here represent the past three months as compared with the previous three months. The reason for these spectacular increases is no secret

—it's simply G-E quality. That, plus proper design and the right price means consumer acceptance—consumer demand—consumer action.

Make that action mean dollars for you. Order your stock of these fast sellers now—start your sales curve rising.

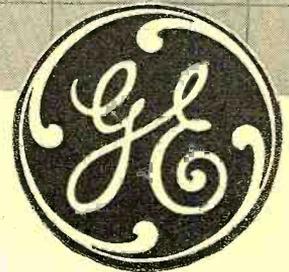For additional information on these three units write:
 General Electric Company, Electronics Park, Syracuse, N. Y.



GENERAL ELECTRIC