BUILD YOUR OWN TV COLOR CONVERTER

RADIO & TELEVISION NEWS

DECEMBER 1954

35 CENTS lin U. S. and Canadá 🥷



World's Leading Electronics Magazine

IN THIS ISSUE-

MIDGET FM TUNER

CHOOSING YOUR HI-FI LOUDSPEAKER ENCLOSURE

100-WATT BANDSWITCHING HAM TRANSMITTER

SINGLE-SIDEBAND **AUDIO TEST OSCILLATOR**

A TRANSISTOR VIORATION AMPLIFIER

SERVICING PRINTED WIRING IN TV RECEIVERS


> **HOW GOOD ARE YOUR** TV. INSTALLATIONS?

SERVICING **GATED-BEAM DETECTORS**

ALL-PURPOSE ENCLOSURE FOR 12" SYSTEMS

> HI-FI ON A TEACART (See page J-2-1)



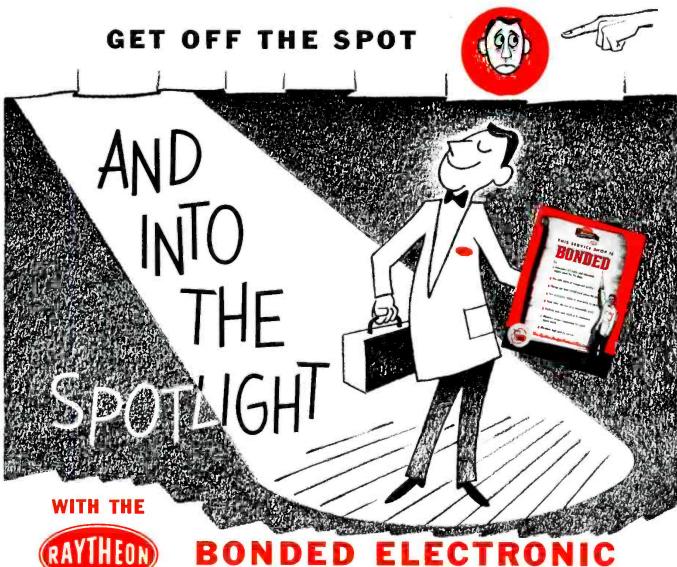

BONDED ELECTRONIC TECHNICIAN PROGRAM

Once you gain the confidence of customers, you're on your way to increased volume and profits. The Raytheon Bonded Electronic Technician program is designed to help you do just that. The Raytheon Registered Bond Certificate, the Raytheon Creed Display Decal and Identification Cards, featuring your bonded status and the fine Raytheon "Code of Ethics", inspire customer confidence. And a recent survey proved that wherever Raytheon Bonded

Technicians took full advantage of their Bonded status — used it to inspire customer confidence — business improved by at least ten per cent.

Ask your Raytheon Tube Distributor if you can qualify for this important sales advantage. If you can, the bond is yours at no cost to you—it is Raytheon's investment in your future.



RAYTHEON MANUFACTURING COMPANY


Receiving Tube Division Newton, Mass., Chicago, III., Atlanta, Ga., Las Angeles, Cal.

Excellence in Electronics

RAYTHEON

RECEIVING AND PICTURE TUBES . RELIABLE SUBMINIATURE AND MINIATURE TUBES . SEMICONDUCTOR DIODES AND TRANSISTORS . NUCLEONIC TUBES . MICROWAVE TUBES

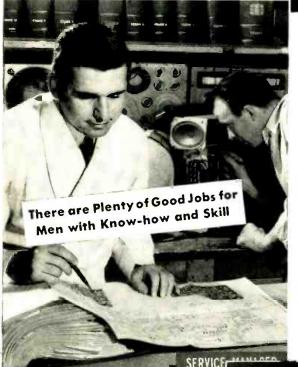Learn to Service TV Setsany make or model-Quickly



New ALL PRACTICE Method trains you at home to become a Professional TV Serviceman


You learn the time saving techniques, methods used by top TV Servicemen

This is 100% learn-by-doing, practical training. NRI supplies all necessary equipment, all tubes, including a 17-inch picture tube; and comprehensive manuals covering a thoroughly planned program of practice. You learn how experts diagnose TV receiver defects quickly. You easily learn the causes of defects—audio and video—and how to fix them accurately.

You get actual experience aligning TV receivers, isolating complaints from scope patterns, eliminating interference, using germanium crystals to rectify the TV picture signal, adjusting the ion trap and hundreds of other valuable Professional techniques.

17" Picture Tube, Components for a TV Receiver, Scope, Signal Generator, HF Probe all included in introductory price under \$200-Easy Terms

If you want to go places in TV servicing, you will act quickly to find out what you get, what you practice, what you learn and how NRI's new course in Professional Television Servicing will help you advance through better technical knowledge and training. See pictures of equipment supplied, read what you practice in book offered FREE to ambitious men with some knowledge of Radio or TV fundamentals. Find out about this ALL PRACTICE Professional TV Servicing Course now.

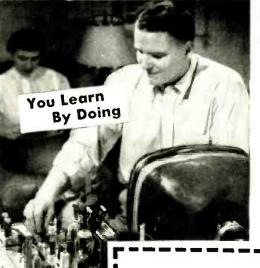

UHF and COLOR Create Growing Opportunities

To eash in on the present UHF and the coming COLOR TV boom you'll need the kind of knowledge and experience NRTs Course gives. You'll get practice installing front-end channel selector strips in modern UHF-VHF receivers. You learn UHF servicing problems and their solution. Mail the coupon now, Discover how NRTs new course in PROFESSIONAL TELE-VISION SERVICING meets the needs of the man who wants to get alread in TV Servicing.

Not for Beginners

If you have some knowledge of Radio-TV fundamentals, or have had some Radio Shop experience or some Radio school training, this course IS FDR YOU. Mail coupon today.





COUPON BRINGS IMPORTANT BOOK FREE

Get this book and judge for yourself how this course will further your ambition to reach the top in TV Servicing or help to build a more secure business of your own in TV. Many of tomorrow's top TV Servicemen... men who can service any make, any model, UHF, VHF or Color TV... will be graduates of this training. Mail the coupon now. There is no obligation.

National	Rad	io In	stitut	e		
Dept. 4	NET,	16th	and	U	Sts.,	N.W.
Washing	ton S	9, D.	С.			

Please send my	FREE copy of	"How to	Reach the	Top in T	V Servicing,"
I understand no	salesman will	call.			

Name	 <mark>Age</mark>

City	Zone	Stat	e	

RADIO & TELEVISION NEWS is published monthly by Ziff-Davis Publishing Company. William B. Ziff. Chairman of the Board (1946-1953), at 64 E. Lake St., Chicago I. III. Entered as second-class matter July 21, 1948, at the Post Office, Chicago, III., under the act of March 3, 1879. Authorized by Post Office Chicago, III., under the act of March 3, 1879. Authorized by Post Office Chicago, III., under the act of March 3, 1879. Authorized by Post Office Chicago, III., under the act of March 3, 1879. Authorized by Post Office Chicago, III. under the act of March 3, 1879. Authorized by Post Office Chicago, III. under the act of March 3, 1879. Authorized by Post Office Chicago, III. under the act of March 3, 1879. Authorized by Post Office Chicago, III. and I

Editor and Asst. Publisher OLIVER READ, D.Sc., WIETI

Managing Editor WM. A. STOCKLIN, B. S.

Technical Editor
H. S. RENNE, M. S.

Service Editor

Assistant Editors P. B. HOEFER M. C. MAGNA

Television Consultant
WALTER H. BUCHSBAUM

Short-Wave Editor KENNETH R. BOORD

Art Editor

Draftsmen

A. A. GANS, W2TSP J. A. GOLANEK

Advertising Manager
L. L. OSTEN

Midwest Adv. Manager JOHN A. RONAN, JR.

Western Adv. Manager
JOHN E. PAYNE



COVER PHOTO: A novel idea for the audiophile who likes his music wherever he is. A household teacart can be used as a mobile carrier for any combination of audio gear, as suggested here by Regency. (Ektachrome by Ken Schmid Studio, Inc.)

ZIFF-DAVIS PUBLISHING COMPANY

President B. G. DAVIS

Vice-Presidents
H. J. MORGANROTH
M. H. FROELICH

Secretary-Treasurer G. E. CARNEY

Circulation Manager
M. MICHAELSON

BRANCH OFFICES

CHICAGO (1) 64 E, Loke St., AN 3-5200

LOS ANGELES [14] Statler Center, 900 Wilshire 8lvd., Mich. 9856 Jirst in radiotelevision-audio-electronics Average Paid Circulation over 246,000



Reg. U. S. Pat. Office @ Television News Trademark Reg. U. S. Pat. Office.

CONTENTS

DECEMBER, 1954

Build Your Own TV Color Convert	er (Part I)	Jay Stanley	37
Midget FM Tuner		Robert J. Larson	40
The Broadcast Recorder		E. E. Berlant	43
How Good Are Your TV Installati	ons?	John B. Ledbetter	45
Choosing Your Hi-Fi Loudspeaker	Enclosure	Abraham B. Cohen	46
All-Purpose Enclosure for 12" Syst	ems (Part 2)	Oliver Read	48
A Semi-Automatic Tube Checker		Phil Weiss	50
Single-Sideband Audio Test Osci	llator	Edmund H. Marriner	51
Servicing Gated-Beam Detector C	ircuits	Matthew Mandl	52
The "Globe Scout"		Leo I. Meyerson, WØGFQ	54
1954 TV Receiver Specifications.		***************************************	56
Servicing Printed Wiring in TV Re	eceivers	Walter H. Buchsbaum	57
Certified Record Revue		Bert Whyte	60
The "Bass Ultraflex" Enclosure	Daniel J	. Plach & Philip B. Williams	61
A Transistor Vibration Amplifier		Louis E. Garner, Jr.	64
A Compact 100-Watt Bandswitch			,,
New FM-Only Tuner		Maurice P. Johnson, W3TRR	66
D. R. Von Recki	inghausen, J.	W. Casey & V. H. Pomper	71
Transistor Amplifier for Meters		,	74
Electronic Memory			76
Mac's Radio Service Shop		John T. Frye	78
Highly-Sensitive Link-Coupled Lo			96
Hi-Fi on a Teacart		***************************************	121
New TV Grants Since Freeze Lift.		***************************************	138
New TV Stations on the Air			138
Radio-TV Service Industry News			146
Radio & Television News Index (V	ols. 51-52)		161
DE	PARTMENTS		
For the RecordThe Editor		nnical Books	84
		at's New in Radio	
• • • • • • • • • • • • • • • • • • • •			
7. (1.)		nufacturers' Literature	
Short-WaveK. R. Boord	70 Nev	Audio Equipment	140



COPYRIGHT 1954
(All Rights Reserved)

ZIFF-DAVIS PUBLISHING COMPANY
WILLIAM B. ZIFF (1898-1953) FOUNDER
Editorial and Executive Offices
366 Madison Ave., New York 17, N. Y.
VOLUME 52 • NUMBER 6




SUBSCRIPTION SERVICE: All communications concerning subscriptions should be addressed to Circulation Dept., 64 E. Lake St., Chicago 1, Ill. Subscribers should silow at least four weeks for change of address.

CONTRIBUTIONS: Contributors are advised to retain a copy of their manuscripts and illustrations. Contributions should be mailed to the New York Editorial Office and must be accompanied by return Postage. Contributions will be handled with reasonable to the New York Editorial Office and must be accompanied by return Postage. Contributions will be handled with reasonable to the New York Editorial Office and must be accompanied by return Postage. Contributions will be handled with reasonable to the requirements of this publication. Payment covers all suthor's, contributor's, and contestant's rights, title, and interest in and to the material accepted will be made at our current rates upon acceptance. All photos and drawings will be considered as part of the material Purchased.



December, 1954

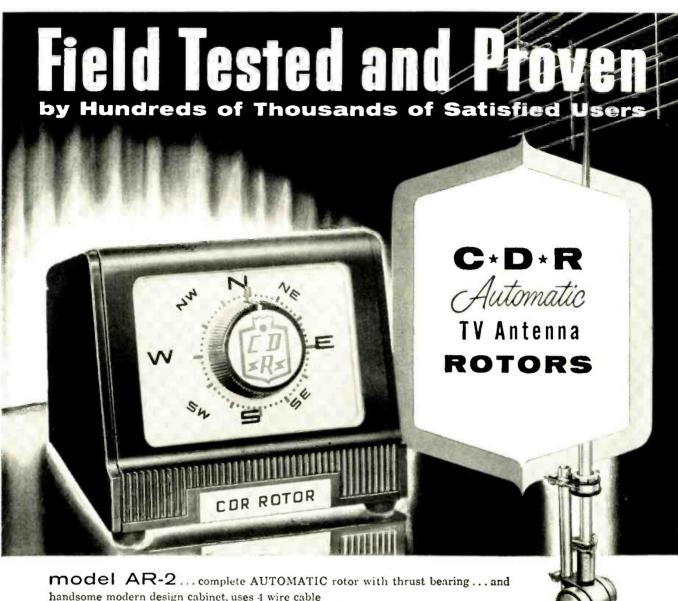

handsome modern design cabinet, uses 4 wire cable


model AR-1... same as AR-2 without thrust bearing

model TR-12

A special combination value consisting of complete rotor including thrust bearing. Handsome modern cabinet with meter control dial, uses 4 wire cable .

model TR-11

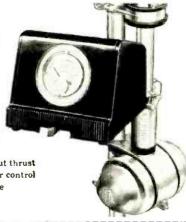The same as the TR-12 without thrust bearing, complete with meter control dial cabinet, uses 4 wire cable



model TR-2

The heavy-duty rotor with plastic cahinet featuring "Compass Control", illuminated "perfect pattern" dial, uses 8 wire cable

model TR-4

The heavy-duty rotor complete with handsome, modern design cabinet with meter control dial, uses 4 wire cable .







THE RADIART CORP. CLEVELAND 13, OHIO

The One Big Reason Big-Screen Color TV Sets are on the Market Now

It took more than engineering promises before leading set manufacturers invested in production of color TV sets. It took a practical bigscreen color picture tube . . . the CBS-Colortron "205."

It took *creative* engineering to conceive this advanced design in color picture tubes. And it took *advanced-engineering* knowledge to produce it.

Today, these set manufacturers are demonstrating their recognition of the leadership of CBS-Hytron. For they are shipping color TV sets and these sets are equipped with the CBS-Colortron "205."

There can be no better evidence of the advanced-engineering knowledge of CBS-Hytron... Advanced-engineering knowledge you can depend upon to produce the finest in television tubes... for color or for black and white.

A Division of Columbia Broadcasting System, Inc.



A member of the CBS family: CBS Radio • CBS Television • Columbia Records CBS Laboratories • CBS-Columbia • CBS International • and CBS-Hytron December, 1954

7



Enjoy the Range and the Realism

New concepts by E-V create new values for you in the enjoyment of sound reproduction. Unique Radax principle and built-in mechanical crossover permit design of the low-frequency cone and high-frequency axial radiator for extended optimum bass and treble response. Heavier "pound-rated" magnets provide more driving power and generous distortion damping factors. These and other E-V quality features assure more listening pleasure.

Hear them at your E-V Distributor or Write for FREE Hi-Fi Bulletins





RADIO-TV SERVICE DEALERS THREATENED

THE almost perennial headache to the TV service profession again threatens the dealer and the technician—especially in large areas like New York City and its environs. Because of persistent complaints against prices charged for repairs and unethical practices by several service dealers, Mayor Wagner (NYC) acted to discuss the problem with Brooklyn's District Attorney who had been conducting a grand jury investigation of radio and television repair "rackets." The Mayor's aides were told to prepare new legislation designed to curb unethical practice in the TV service-repair profession.

The previous "licensing bill" introduced last January was killed by the city council committee. At that time it was charged that the servicing profession was a subject "of great abuse, with the result that the public has been and is being victimized by irresponsible sales methods, unethical and financially unstable service organizations, and inferior installation, maintenance and repairs."

The January bill proposed that all television service technicians be licensed and that they maintain standards set by an eight-man supervisory committee. This group was to be appointed by the Mayor. It was proposed that violators of the license bill be fined amounts of from \$100 to \$500 with license revocation, or six months in prison, or both.

The new legislation, we are told, is designed (in part) against the practice of removing a TV set from a home, taking it to a shop for repair, returning the set to the owner, and charging him for tubes and parts that are not replaced, etc.

Such legislation, in our opinion, would arouse the public to the point that *ALL* TV technicians would be branded as a bunch of bandits, crooks, and sharpies. It would become impossible for legitimate operators to economically handle major repair jobs at their service shops where essential (and bulky) test equipment is required for proper analysis and alignment.


This bill, if passed, would have serious repercussions on the entire service profession and would spread its ugly seeds to every city in the country. Legitimate service dealers would be forced to purchase a full set of shop test equipment for *each technician*, to be hauled out in expensive trucks to the customer's home and to his living room for major TV repair work.

Can you visualize this "shop" set up in a consumer's home with the attendant mess that will result? Even worse, it would only serve to further encourage the unethical service technician (and the bill won't stop him) to put on an "extravaganza" performance for the customer to witness as he tears a complicated TV receiver apart on the living room rug while performing his sleight-of-hand. It would be just as simple to replace a bad tube with a second-hand duplicate right before the customer as it would in his shop if this was his practice. And what could possibly prevent him from replacing components (at will) in the set right before the eyes of the customer? Some characters would really take advantage of the alleged "protection" of their license.

We know, from several years of radio servicing experience, that the average housewife resents repair work on anything in her home that causes mess, noise, or commotion. Little Junior takes care of those details without any trouble.

This new bill—if passed—would result in severe inventory problems for the small service dealer. Field technicians would have to chase back and forth for transformers, picture tubes, et al like a plumber, or would require a truckload of replacement components. Either would result in higher charges to the consumer. Who wins?

As we see it—nobody gains but the cash register of the city fathers. Do these same people license the car dealer and make him send a mechanic to our homes to rebuild the transmissions in our cars? Do they force the jeweler to send a watchsmith to our homes to fix crystals on our *Ingersolls?* The answer, of course, is obvious. But these same industries have escaped legislation for policing—even though they have had their share of shady characters. So why electronics?

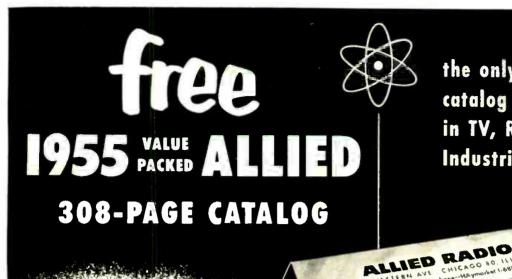

the only COMPLETE catalog for Everything in TV, Radio and Industrial Electronics

1955

Everything in Radio, Television & Industrial Electronics

SEND FOR IT TODAY

Get ALLIED'S 1955 Catalog-308 pages packed with the world's largest selection of quality electronic equipment at lowest, money-saving prices. Select from the latest in High Fidelity systems and components; custom TV chassis, TV antennas and accessories; AM and FM receiving equipment; P.A. Systems and accessories; recorders and supplies; Amateur receivers, transmitters and station gear; specialized industrial electronic equipment; test instruments; builders' kits; huge listings of parts, tubes, tools, books-the world's most complete stocks of quality equipment. ALLIED gives you every buying advantage: fastest shipment, expert personal help, lowest prices, assured satisfaction. Get the big 1955 ALLIED Catalog. Keep it handy save time and money on everything in Electronics. Send for your FREE copy today.

World's largest Stocks

- All TV and Radio Parts
- All Electron Tube Types
- Test and Lab Instruments
- High Fidelity Equipment
- Custom TV Chassis
- AM, FM Receiving Equipment
- Recorders and Supplies
- P. A. Systems, Accessories
- Amateur Station Gear
- Builders' Kits & Supplies
- Equipment for Industry



ALLIED RADI

World's Largest Electronic Supply House

EASY-PAY TERMS

Use ALLIED'S liberal Easy Pay-Ose Allieb's liberal Easy Payment Plan—only 10% down, 12 months to pay—no carrying charges if you pay in 60 days. Available on Hi-Fi and P. A. units, recorders, TV chassis, test instruments, Amateur gear, etc.

HI-FI SPECIALISTS

To keep up with the latest and best in High Fidelity, look to ALLIED. Count on us for all the latest releases and largest stocks of Hi-Fi equipment. We specialize, too, in TV supply -and are foremost in the field of Builders' Kits.

ultra-modern facilities for the FASTEST SERVICE IN ELECTRONIC SUPPLY

ALLIED RADIO CORP., Dept. 1-M-4 100 N. Western Ave., Chicago 80, Illinois

Send FREE 308-Page 1955 ALLIED Catalog

City Zone ... State




UNIVERSAL

Replacement Selenium Rectifiers

1. Use the through bolt or machine screw that previously held the replaced rectifier.

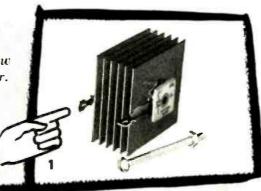
2. Use the special locating lug and mounting stud supplied with every Sarkes Tarzian rectifier.



3. Sarkes Tarzian rectifiers are equipped with "plug-in" type lugs to accommodate even the most modern sets.

A Sarkes Tarzian exclusive on the replacement market.

plus small, small size

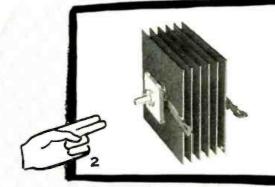


COMPARE

THESE DIMENSIONS* WITH THOSE OF ANY OTHER RECTIFIER ON THE MARKET:

5.T. MODEL	RATING MA DC	LENGTH (MAX.)	PLATE SIZE (MAX.)
300X	300	1 1/8"	1 5/8" SQ.
350×	350	1 11/32"	1 5/8" SQ.
400 X	400	1 1/8"	2" SQ.
500 X	500	1 11/32"	2" SQ.

*SMALLEST OVERALL SIZE FOR FULL RATING

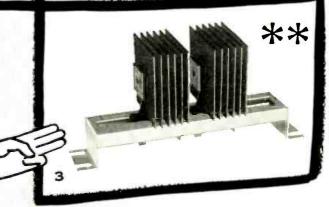SEE YOUR DISTRIBUTOR FOR TRULY UNIVERSAL REPLACEMENT RECTIFIERS



**MODERNIZE OLD TV SETS WITH THE NEW "PLUG-IN" CONVERSION CHASSIS NOW AVAILABLE AT YOUR DISTRIBUTORS.



Rectifier Division

DEPT. R6, 415 NORTH COLLEGE AVE. BLOOMINGTON, IND.

In Canada: 700 Weston Rd., Toronto 9, Tel. Murray 7535 . Export-Ad. Auriema, Inc., N. Y. C.



FINCO 400-SA

FEATURING FOR BAC FULL DIMENSIONAL SCREEN

The engineering masterpiece of the antenna industry! The sensational, new Finco 400-SA eliminates rear signal interference (adjacent and co-channel), ghosts and electronic noise — delivers famous Finco high gain for clear, sharp pictures in the SUPER fringe area on all channels, UHF and VHF. The special electronic FRO-BAC screen has 80 sq. ft. of highest efficiency, FULL LENGTH reflector surface. Preassembled for quick installation.

FINCO 200-A

The ideal antenna for "in-between areas" . . . (too far out to use "Local" type antenna, too close to warrant use of a super-fringe antenna). The new Finco 200-A combines basic, double CO-LATERAL* design with exclusive Finco electronic patents to deliver unbeatable gain and performance in the Semi-Fringe area on all channels, UHF and VHF. Completely pre-assembled.

FINCO 200-SA

The Finco 200-SA was engineered specifically for the "in-between", semi-fringe areas where a FRONT-TO-BACK problem exists. The special FRO-BAC full dimensional screen eliminates rear signal interference, ghosts and electronic noise. This antenna delivers reception power that cannot be matched by ordinary antennas. Completely pre-assembled.

WRITE FOR FREE LITERATURE

Copyright 1954, The Finney Co.


The FINNEY Company

Dept. TN-124
4612 ST. CLAIR AVENUE • CLEVELAND 3, OHIO

MODEL 14-S CONVERSION KIT

FRONT-TO-BACK PROBLEM IN YOUR AREA??? MANY FINCO 400-A INSTALLATIONS???

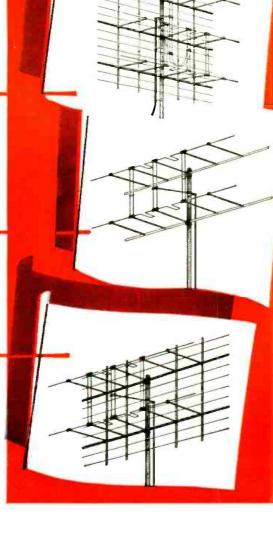This kit contains special electronic FRO-BAC screen and stainless steel hardware far quick conversion of models 400-A and 400 to model 400-SA.





NEW PATENTED RADAR ANTENNA

OPENS NEW HORIZONS TO TV VIEWERS

These are the reasons why the "Riviera" is by far the most powerful VH7 antenna on the market today!

- 1. Utilizes 16 elements 60" long, 12" diameter.
- Utilizes a specially designed, extra low loss four conductor air-dielectric POLYMICALENE transmission line which has up to 50% less loss when wet than the finest conventional transmission lines.
- The "Riviera" encompasses an electro-magnetic capture volume of well over 650 cubic feet, many times more than conventional antennas.
- 4. The antenna works on the revolutionary principle that the approaching wave front is elliptically rather than horizontally polarized.
- The new specially designed 9 position electronic orientation switch, aside from changing directivity, maintains a consistently better impedance match over the entire UHF-VHF spectrum.
- 6. The above features combine to give the "Riviera" antenna greater usable gain at the TV set antenna terminals than the best of any competitive antennas using rotor motors.

This new wonder antenna, called the "Riviera", is already making history. Beyond any question of a doubt, and on an unconditional money back guarantee, it will positively outperform in the field under actual installation conditions, any and all competitive antennas on the VHF channels, with or without rotor motors.

ALL CHANNEL ANTENNA CORP.

47-39 49th STREET, WOODSIDE 77, N. Y.

EXETER 2-1336



The polar directivity response patterns show the major lobes of the "Riviera" antenna an VHF. It shows the fuliness of coverage in all directions of this remarkable, patented antenna as it is surned through each of the nine switch positions. Each degree of shading constitutes a different switch position. This excellent directivity responses, which can be switched at will, plus the extremely high gains, clearly indicate why the Riviera is such a superior performer.

IN UHF-VHF DISTRICTS . . . USE

The NEW Super 60

100 MILES VHF . 60 MILES UHF

Mew UHF&VHF LEAD-IN

PAT. PEND.

Thousands of separately sealed tiny cells, filled with inert gas, make this waterproof cable stable and efficient electrically.

ADVANTAGES:

- 1 Lowest losses at UHF and VHF frequencies.
- 2 Great abrasion resistance and mechanical strength.
- 3 No time-consuming end seal required; easy to install.
- 4 No. internal moisture to cause signal loss.
- 5 No kinking when used with antenna rotors.
- 6 Resistant to snow, ice, rain, and wind.
- 7 Resistant to ultraviolet rays from the sun.
- 8 Uses Belden Weldohm conductor for long conductor life.
- 9 Can be clamped tightly in stand-off insulators without crushing. No special fittings required.
- 10 Conductor spacing is constant even when the lead-in is transposed.
- 11 No stripping problem for attaching the conductor.

This heavy wall of brown virgin polyethylene protects the cable against mechanical abuse and damage from ultraviolet sun rays.

This completely new 300-ohm line results from the development of a new cellular plastic core where each separate cell is filled with an inert gas to make an efficient cable with the lowest possible losses at both UHF and VHF frequencies. With this absolutely waterproof cable, no sealing of the ends is necessary. Celluline cable can be fixed in stand-off insulators without crushing. The thick outer wall of polyethylene serves to protect the cable from abrasion and sun damage.

By fusing only virgin polyethylene, the wall can be made smooth—absolutely free from rough spots—to prevent the adherence of dust and other impurities which would increase the losses.

The copper-covered steel strands, which make up the conductors, assure 49% greater resistance to breaking from flexing or stretching than any all-copper conductor.

8275 CELLULINE

by BELLET CONTRACTOR OF THE STRY

December, 1954



with ATR INVERTERS for changing your storage battery current to A. C. Household ELECTRICITY Anywhere Plugs into Cigarette Lighter Receptacle on Dash in your own car!

AND UP LIST PRICE ATR INVERTERS . . .

especially designed for operating standard 110 volt A. C. . . .

. DICTATING MACHINES . TAPE RECORDER • ELECTRIC RAZORS WIRE RECORDERS

TYPE	IMPUT 9.C. Volts	A.C. OUTPUT 60 CYCLES	OUTPUT WATTAGE	LIST PRICE			
6-DME	6	115 voits	30-40	19.95			
6H-DME	6	115 volts	60.75	29.95			
Above Inverters also available for 12-volt operation.							

See your jobber or write factory today for complete information AMERICAN TELEVISION & RADIO CO. 2nality Products Since 1931 SAINT FAUL 1, MINNESOTA - U.S. A.



 \star Presenting latest information on the Radio Industry.

By RADIO & TELEVISION NEWS' WASHINGTON EDITOR

THE FCC, officially without a chairman since early summer, in view of Commissioner George Sterling's retirement; now has one, George C. McConnaughey, former chairman of the Renegotiation Board. Named by the President, he will serve as a recess appointee until January, when Congress convenes. At that time, his nomination will be submitted to the Senate for confirmation; if approved he will remain on the Commission until June 30, 1957, for the unexpired portion of Sterling's term.

The new headman, a 58-year old attorney, has had extensive experience as an administrator on a number of government Commissions, For six years he was with the Public Utilities Commission, serving as a member and then as chairman. For several years, he was also chairman of the War Transportation Commission of Ohio.

Notification of the appointment was made by Presidential Assistant Sherman Adams, who phoned McConnaughey from the summer White House in Denver, Colorado. The oath of office was taken in the executive offices of Adams in the White House; it was administered by Supreme Court Justice Harold H. Burton, a fellow Ohioan.

Technically, the new FCC chief succeeds Rosel H. Hyde, who had been named chairman by the President on April 18, '53, for a one-year term. Hyde remains on the Commission and will complete his term.

ALTHOUGH THE RESIGNATION of Sterling had been expected for months, because of ill health, it was hoped that he would remain on the Commission. However, upon recommendation of his physician and at the request of his family, he decided to retire.

Everyone in Washington and throughout industry will miss the keen intellect of this brilliant engineer and able administrator. His career in Washington was an outstanding one. Before his appointment to the Commission, he served as chief engineer of that body. and during World War II, he organized the Radio Intelligence Division, and guided its operation. In addition, he served as the official security officer of the Commission. It was his familiarity with the broadcast industry and its engineering capabilities that made it possible to set up the efficient radiosilence system, known as Conelrad, in collaboration with the Office of Civilian Defense.

The genuine admiration of his colleagues was expressed in a glowing resolution and accompanying scroll, tendered during a special ceremony. Said the scroll, in part:

"This scroll commemorates the retirement of a beloved associate, who has proved unfailing in his loyalty to the public trust, and in his sympathy and understanding of his fellow man. ... He brought to that office (the Commission and other Federal posts) an unprecedented experience in radio, which had its beginning in 1908, and as operator, engineer, author, and policy maker has played a prominent role in the development of the radio art. . . . His warmth. sincerity, and fundamental sense of fairness have earned him the respect and affection of all, and his distinguished career long will be an inspiration and example in the organization he served.'

AN INGENIOUS ULTRASONIC photographing device, that may eventually accomplish what x-ray and fluoroscope cannot do, produce well-defined pictures of cancer and other diseases of the body's internal soft organs and tissues, has been invented by Dr. Douglass H. Howry, former Veterans Administration resident in radiology and now an instructor in radiology at the University of Colorado Medical School.

Known as the "Somascope," the instrument, in its present stage of development, can detect masses such as goiters, cysts, and tumors in the body's internal organs. In some cases, it has been found, the device helps distinguish between tumors which are dangerous or of no consequence to the patient's health.

The principles of sonar, radar, and TV have been combined in this outstanding development. From sonar, the unit borrows the principle of sending sound waves through the water and receiving echoes, or the up-anddown principle of ultrasonic sound transmission. From radar, the basis of back-and-forth scanning has been taken, and from television, the medical



NEVER THOUGHT WE COULD GET PICTURES WITH SO MUCH PUNCH 'TIL WE HAD THOSE SPRAGUE CAPACITORS PUT IN.

Don't Be Vague...Insist on SPRAGUE



☆ Trademark



Insist on Sprague CERAMICS

Tiny, tough, dependable . . . in every application . . . whether discs, plates, buttons, or door knobs. And there's a Sprague ceramic capacitor to meet every service need. You give your customers dependable service, guard yourself against costly call-backs, when you use only Sprague Ceramic capacitors.



Insist on Sprague TWIST-LOK* 'LYTICS

Sprague TVL's fill the top performance bill in the toughest TV circuits. High temperatures, surge voltages, ripple currents won't faze them. Like all Sprague capacitors, Twist-Lok 'Lytics are your first line of defense against expensive call-backs.



Insist on Sprague BLACK BEAUTY® TELECAPS®

The most imitated capacitor Sprague ever introduced. But you get Sprague performance only when you insist on Sprague Telecaps. Hundreds of millions are in use today as first choice of quality conscious manufacturers and servicemen. It's the premium molded tubular at no extra cost.

SPRAGUE

Get your copy of Sprague's latest radio and TV service catalog C-610. Write Sprague Products Company*, 51 Marshall St., North Adams, Mass.

*Distributors' Division of Sprague Electric Company

WORLD'S LARGEST
CAPACITOR MANUFACTURER

From NEWCOMB'S Big, NEW HI-FI LINE

The two new Compacts, with amplifier, preamplifier and control unit all in one...the new Classic 200 FM-AM Tuner, the answer to years of demand...just three of the twelve all new components in the Newcomb line - a line which offers an amplifier for every hi-fi need. All twelve reflect the engineering leadership for which Newcomb has been famous since 1937. Visit your dealer... see and hear the full Newcomb line – priced from \$59.50 to \$297.50. You'll understand why Newcomb is your best buy in hi-fi!





HI-FI COMPLICATED? EXPENSIVE? NOT WITH NEWCOMB'S COMPACT 12!

Newcomb offers every music lover authentic high fidelity with a minimum of expense and trouble in the new Compact 12. Provides unequalled flexibility and range of sound control. Needs no cabinet. Just plug it in, connect it to a record changer and speaker. But if you prefer to use cabinetry, it includes Newcomb's exclusive "Adjusta-Panel" feature for easy installation. Simple to move - ideal for apartments! U/L approved.

Compact 10 - A simplified 10-walt version of exceptional performance at only \$7950



Compact 12 Specifications

12-watt high fidelity amplifier—preamplifier—control unit • less than 1% distortion at 12 watts • response ±1 db 20 to 20,000 cycles • separate crossover and rolloff controls give 36 different recording curves • input selector and rumble filter • 7 inputs • mike input • tape input • output to tape • wide range separate bass and treble tone controls, bass range—15 db to +18 db, treble range—18 db to +16 db • hum balance control • new level control • advanced design loudness control • size only 41/6" high x 121/2" x 9".

FOR SUPERIOR RADIO RECEPTION NEW Classic 200-2 knob FM-AM Tuner

For years now, satisfied Newcomb amplifier owners have asked for a tuner by Newcomb. Here it is – the Classic 200 high fidelity tuner to deliver the utmost to a fine amplifier! It, too, is compact in size.

Designed for use with any amplifier having its own controls. Fully enclosed, beautifully finished to use as is, or the exclusive "Adjusta-Panel" makes cabinet installation simple. U/1 approved. Output is 10 volts at less than ¼ %. 1 volt at less than 4/100%. Effective to 200 feet from amplifier. Many new circuit advances in both FM and AM sections. Results: 30 db of quieting with only 1½ microvolts input on FM. 1 microvolt AM sensitivity for 1 volt output. Only 6¾" high x 11½" x 11½". 111/2" x 111/2".





HI-FI GUIDEBOOK

"Hi-Fi Is For Everybody" Explains the how and why of authentic high fidelity . How to buy and install economically . Informative and thoroughly illustrated . Not a catalog



NEWCOMB® SINCE 1937 High Fidelity Amplifiers and Tuners

Here's 25c for new book, "Hi-Fi Is For Everybody."
Please send free catalog of Newcomb's complete
line of 12 new hi-fi prod-
ucts, plus name of my

NEWCOMB, Do	•	38, California
Name		
Address		
City	Zone	State

aid has borrowed the principle of defining these up-and-down and backand-forth impulses on a TV screen.

Since sonar requires water to function properly, the human subject is placed in a tub of water where ultrahigh sound waves are produced. With the instrument aimed at the internal organ to be photographed, the flip of a switch produces a short impulse of electrical energy, almost as powerful as that coming from a 50,000-watt transmitter, but lasting only a quarter of a millionth of a second.

This high-voltage energy passes into a sound head of the instrument, which contains a barium-titanate ultrasonic crystal. Here the electrical energy is converted into sound waves which travel 5000 feet a second.

By the use of ultrasonic sound lenses. these waves are concentrated into a narrow beam of inaudible sound, onesixteenth of an inch wide to improve definition, and are directed through the water into the object to be examined.

As these water-borne sound waves strike the surface of the object, the VA medical-electronics expert pointed out, an echo is reflected back to the sound head. The remainder of the sound pulse penetrates the object, and further echoes are reflected back by different tissues or other objects, with an intensity in proportion to the density of these structures. These echo waves are then picked up by the sound head, converted back into a train of electrical signals which are amplified and passed into the picture tube, producing a line of bright spots on the screen face. As soon as all of the echoes have returned, another electrical blast sends another series of sound waves out, and the process is repeated with another line on the TV screen. Thousands of pulses are gen-

erated in this manner every second.

The "Somascope's" under - water sound head, mounted on a revolving screw and sweeping back and forth across the object to be photographed. causes the sound beam to scan the object from rapidly-changing positions. This radar-scanning motion causes each pulse of waves to take a slightly different path through the object or tissue to produce a series of lines, one next to the other. In that manner, a two-dimensional picture is drawn in the exact shape and dimensions of the object being studied.

It was also disclosed that tissues with different consistencies have a marked difference in reflecting sound waves as, for example, fat; whereas x-ray best differentiates bone or airfilled organs, like the lungs.

Another advantage of this new instrument, it was revealed, is that it can rotate the picture on the TV screen from zero to ninety degrees. This makes it possible to see the tissue being studied as if it were a transparent block-like segment, viewed from any desired angle from above or from the front.

(Continued on page 135)

Get this FREE Booklet Today!

LOADED WITH CAREER-BUILDING FACTS --- IT CAN LEAD YOU TO A BIGGER JOB, BETTER PAY, SECURITY AND SUCCESS IN RADIO — TV — ELECTRONICS

"YOUR FUTURE IN THE NEW WORLD OF ELECTRONICS"contains a proved plan for your successful career in:

- * COMMUNICATIONS
- * AERONAUTICAL ELECTRONICS
- * ARMY, NAVY, AIR FORCE, COAST GUARD ELECTRONICS



* TELEVISION

- ★ MANUFACTURING * SERVICING

A PROVED CAREER-PREPARATION **PLAN THAT WORKS!**

This free book has brought home to thousands of men just like you! They are now enjoying responsible jobs, good pay and the good things of life. So can you! In less time than you think! We tell you how you can carve out a bigger better-paying job. Our proved careerpreparation plan works because it was written by authorities who know exactly what the varied electronic industries want, need and expect from you!

ELECTRONICS' FUTURE CAN BE YOUR FUTURE


You can't keep up with the tremendous changes in the electronic industries. What's predicted for next year becomes outdated in a few months! All phases of the electronic industries are experiencing phenomenal growth. There are thousands of career openings, big ones, Industry can't find enough trained manpower to fill them—in manufacturing, testing, servicing, broadcasting and telecasting.

TAKE TV FOR EXAMPLE!

Four hundred and six stations are on the air! Many more are building or in the plans stage; 32,859,915 sets are in use. Color TV is just starting to really come alive! This same phenomenal growth picture is repeated in every phase of business employing electronics - crime prevention, aeronautics, fire-fighting, communications, to name but a few. CREI has the plan to keep you moving upward, to help you assume your rightful place!

CREI GRADS ARE IN DEMAND!

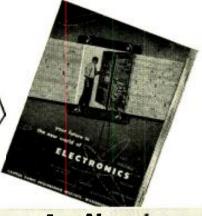The big companies know CREI men have what it takes! CREI grads are at work in America's biggest corporations, in positions ranging from technicians to engineers to top management, Companies such as United Air Lines, Canadian Broadcasting Corporation, Trans-Canada Airlines, Sears-Roe-



Act Now!

TAKE THAT FIRST BIG STEP! NO OBLIGATION

buck and Co., Bendix Products Division. All-American Cables and Radio, Inc., and Radio Corporation of America, are now paying for CRE1 training for their own technical staffs. Our placement bureau has more requests for CREI-trained men than we can presently supply.

CREI GRADS EASILY PASS FCC EXAMS!

You start feeling the benefits of CRE1 training right away, either with your present connection, or with a future employer. You'll have all the training you need to secure your FCC commercial license.

ACT NOW! TAKE THAT FIRST BIG STEP!

Fill out and mail the coupon. When you do. you'll be on the way to higher pay, a better job and complete career security. Act right away. Send for your free book today.

THOUSANDS LIKE YOU HAVE SUCCEEDED WITH CREI'S PLAN! "CREI TRAINING IS BEST"



"—I chose CREI training upon recommendation of two top engineers. Before I had campleted the course I became transmitter chief of a 5 KW station. I am now employed as a technician at a 100 KW TV station, and in spare time have a good TV sales and service business. Anyone interested in his electronic future should have (REI training."...—Arlie D. Patton, San Antonio, Texas

"—I know of no case in which a man who applied himself and completed the CREI course failed to letter himself through promotion and increase in salary," . . .—Il endell L. Friver, Sen Diego, Calil.

"—CREI has raised me to professional status as a radioman. Thanks to your instructors who always gave me needed help."—Victor Mentzer, Wilmington, Del.

"—I have been in radio and electronics for 24 years. I fully recommend CREI as the best school I have seen." —L. McManus, Montreal, Canada

CAPITOL RADIO ENGINEERING INSTITUTE

Accredited technical curricula. Founded in 1927 3324-16th Steet, N.W. Washington 10, D. C.

CREI also offers resident instruction: at the same high technical level, day or night, in Washington, D.C. New classes start frequently during the year. If this type of instruction meets your requirements, check the coupon for Residence School catalog. Qualified residence graduates may earn the degree of Associate in Applied Science.

INFORMATION FOR VETERANS

If you were discharged after June 27, 1950—let the new G.I. Bill of Rights help you obtain resident instruction. Check the coupon

					_	100000
MA	VIII.	THIS	COU	PON	TOC	$-\infty$



CAI	PITOL	RAD	10	ENC	ЭIN	IEEI	RING	INS	TIT	UT	Ε
ept.	1112-A,	3224	16th	St.,	N.	W.,	Washin	gton	10,	D.	Ç.

Please send me your course outline and FREE Illustrated Booklet "Your Future in the New World of Electronics" describing opportunities and CREI home study courses in Practical Electronics Engineering.] Practical Radio Engineering

CHECK)	
FIELD OF	Ş	L
GREATEST		
INTEREST	1	_

Broadcast Radio Engineering (AM, FM, TV) Practical Television Engineering

Aeronautical Electronics Engineering J TV, FM & Advanced AM Servicing

Name
Street

City	 Zone	Sta	e	
CHECK:	Residence	School		Veteran

for full information.

To help us answer your request intelligently, please give

the following information:
EMPLOYED BY
TYPE OF PRESENT WORK
SCHOOL BACKGROUND.
ELECTRONICS EXPERIENCE
IN WHAT BRANCH OF ELECTRONICS ARE YOU MOST INTERESTED?

Pickering Audio

In every field of endeavor... manufacturing, the theatre, concert or contest... there is always one standout.

In HI-FI equipment the standout is Pickering...

pioneer in this field, responsible
for the development and introduction of outstanding
components for highest quality performance;
every product bearing the Pickering name

is engineered to conquer the challenge of optimum performance... in their manufacture

the most stringent quality controls are
exercised to assure and maintain the "Ne Plus Ultra"
reputation for products featured by the emblem.

COMPONENTS... SYNONYMOUS WITH HIGHEST QUALITY

Design...Illanufacture...Performance

Pickering Audio Components . . . they know the values built into Pickering equipment.

INVESTIGATE and you too will use Pickering components for your HI-FI system. . . .

as leading FM/AM good music stations, network
and recording studios... REMEMBER, leading
record companies use Pickering Components
for quality control.











PICKERING and company incorporated •

PICKERING PROFESSIONAL AUDIO EQUIPMENT

Oceanside, L. I., New York

"For those who can hear the difference"

, . Demonstrated and sold by Leading Radio Parts Distributors everywhere.

For the one nearest you and for detailed literature; write Dept. C-6

J. E. SMITH President National Rodio Institute Washington, D. C. 40 years of success training men of home in spare time.

I Will Train You at Home for Good Pay Jobs, Success in RADIO-TELEVISION



Practice Broadcasting with Equipment I Send

As part of my Communications Course I send you kits of parts to build the low-power Broadcasting Transmitter shown at the left. You use it to get practical experience putting a station "on the air," performing procedures demanded of Broadcasting Station Operators. An FCC Commercial Operator's License can be your ticket to a better job and a bright future; my Communications Course gives you the training you need to get your license. Mail card below and see in my book other valuable equipment you build.



Practice Servicing with Equipment I Send

Nothing takes the place of PRACTICAL EXPERIENCE. That's why NRI training is based on LEARNING BY DOING. You use parts I furnish to build many circuits common to Radio and Television. With my Servicing Course you build a modern Radio (shown at right). You build a Multitester which you use to help fix sets while training. Many students make \$10, \$15 a week extra fixing sets in spare time starting a few months after enrolling. All equipment is yours to keep. Card below will bring book showing other equipment you build.





Television is Growing Fast Making New Jobs, Prosperity

More than 25 million homes now have Television sets and thousands more are being sold every week. Well trained men are needed to make, install, service TV sets. About 200 television stations on the air with hundreds more being built. Think of the good job opportunities here for qualified technicians, operators, etc. If you're looking for opportunity get started now learning Radio-Television at home in spare time. Cut out and mail postage free card. J. E. Smith, President, National Radio Institute. Washington, D. C. OUR 40TH YEAR.

VETERANS
UNDER G.I. BILL

Good Jobs, Good Pay, Success in Radio-TV! SEE OTHER SIDE

CUT OUT AND MAIL THIS CARD NOW

Sample Lesson & 64-Page Book

This card entitles you to Actual Lesson on Servicing, shows how you learn Radio-Television at home. You'll also receive my 64-Page Book, "How to Be a Success in Radio-Television." Mail card now!

NO STAMP NEEDED! WE PAY POSTAGE

Mr. J. E. SMITH, President,


National Radio Institute, Washington 9, D.C.

Mail me Lesson and Book, "How to Be a Success in Radio-Television." (No Salesman will call. Please write plainly.)

NAME AGE ADDRESS

CITY. ZONE STATE.

VETS write in date of discharge.

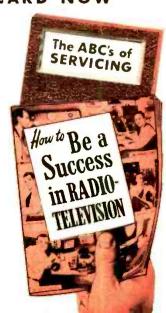

Train at Home to Jump

Get a Better Job — Be Ready for a Brighter Future in America's Fast Growing Industry

Training PLUS opportunity is the PER-FECT COMBINATION for job security, good pay, advancement. When times are good, the trained man makes the BETTER PAY, GETS PROMOTED. When jobs are scarce, the trained man enjoys GREATER scarce, the trained man enjoys GREATER SECURITY. NRI training can help assure you and your family more of the better things of life.

Radio-Television is today's opportunity field. Even without Television, Radio is bigger than ever before. Over 3,000 Radio Broadcasting Stations on the air; more than 115 million home and Automobile Radios are in use. Then add Television. Television Broadcast Stations extend from coast to coast now with over 25 million Television. sets already in use. There are channels for 1,800 more Television Stations. Use of

Extra Fixina Sets

Start Soon to

Aviation and Police Radio, Micro-Wave Relay, Two-way Radio communication for buses, taxis, trucks, etc. is expanding. New uses for Radio-Television principles coming in Industry, Government, Communications and Homes.

My Training is Up-to-Date You Learn by Practicing

Get the benefit of my 40 years experience training men. My well-illustrated lessons give you the basic principles you must have to assure continued success. Skillfully developed kits of parts I furnish "bring to the principles you learn from my lessons. Read more about equipment you get on other side of this page.

Naturally, my training includes Television. I have, over the years, added more and more Television information to my courses. The equipment I furnish students gives experience on circuits common to BOTH Radio and Television.

Find Out About the Tested Way to Better Pay

Read at the right how just a few of my students made out who acted to get the better things of life. Read how NRI students earn \$10. \$15 a week extra fixing Radios in spare time starting soon after enrolling. Read how my graduates start their own businesses. Then take the next step—mail card below: -mail card below.

You take absolutely no risk. I even pay you take absolutely no risk. I even pay postage. I want to put an Actual Lesson in your hands to prove NRI home training is practical, thorough. I want you to see my 64-page book, "How to Be a Success in Radio-Television" because it tells you about my 40 years of training men and important facts about present and future Radio-Television, inh. properturities. You Radio-Television job opportunities. You can take NRI training for as little as \$5 a month. Many graduates make more than the total cost of my training in two weeks. Mailing postage free card can be an important step in making your future successful. J. E. Smith, President, National Radio Institute, Washington 9, D. C. OUR 40TH YEAR.

J. E. Smith, President National Radio Institute

The men whose messages are published below were not born successful. Not so long ago they were doing exactly as you are now . . . reading my ad! They decided they should KNOW MORE . . so they could EARN MORE . . . so they acted! Mail card below now.



Consultant on Antenna Systems I resigned as Chief En neer. Now I am on my wn as consultant or rivate and commercia itenna systems." R. J ailey, Weston, W. Va



In Spare Time Before finishing. I carned as much as 510 a week in Radio servic-ng, in my spare time. I recommend NRI". S. J. Petrug, Miami, Fla.

S10 a Week



Control Operator, Station WEAN

m chief Radio and T



Radia-Televisian Shap Doing Radio and elevision servicing full ne. Have my own op, I owe my success NRI." Curtis Stath. ort Madison, Iowa.



Gat First Job Thru NRI

My tirst job was with Di.R. Now Chier or Radio Equiport for Police and re Dept." T. Norton, amilton, Ohio.

My Training Leads to Jobs Like These

BROADCASTING Chief Technician Chief Operator Power Monitor Recording Operator Remote Control Operator

SERVICING Home and Auto Radias P.A. Systems **Television Receivers** Electronic Controls FM Rodios

IN RADIO PLANTS Design Assistant Technicion

in RADIO.

Service Manager Serviceman Research Assistant

SHIP AND HARBOR RADIO Chief Operator Assistant Operator Radiatelephone Operator

GOVERNMENT RADIO Operator in Army, Navy, Marine Carps, Coast Guard Forestry Service Airways Radio Operator

AVIATION RADIO Plane Rodio Operator Transmitter Technician Receiver Technician Airport Transmitter

TELEVISION Pick-Up Operator Voice Transmitter Operator

Operator

Television Technician Remote Control Operator

Service and Maintenance Technician

POLICE RADIO Transmitter Operator Receiver Serviceman

Keep your job while training. Many NRI students make \$10, \$15 and more a week extra fixing neighbors' Radios

in spare time, starting a few months after

enrolling. I start sending you special booklets that show you how to fix sets, the day you enroll. The multitester you build with parts I furnish helps discover

FIRST CLASS Permit No. 20-R (Sec. 34.9, P.L.& R.) Washington, D.C.

BUSINESS REPLY

No Postage Stamp Necessary If Mailed In The United States

POSTAGE WILL BE PAID BY NATIONAL RADIO INSTITUTE 16th and U Sts., N.W.


Washington 9, D. C.



TELEVISION AS Have Your Own Business

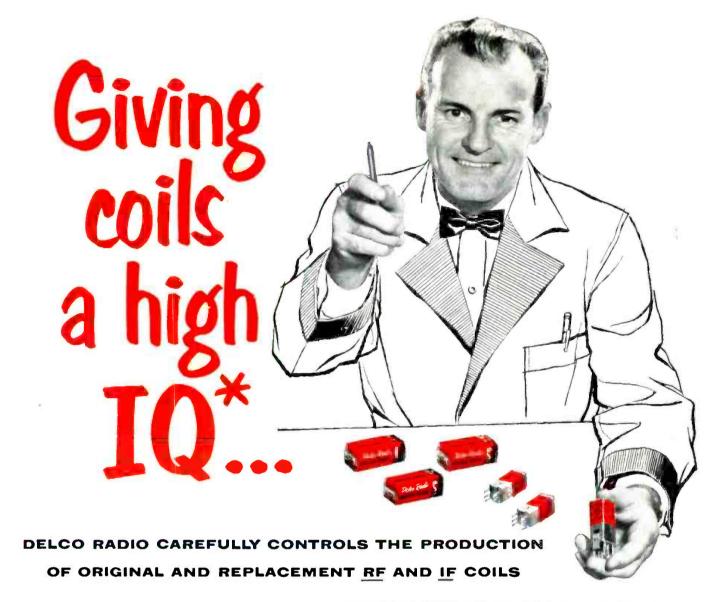Many NRI trained men start their own successful Radio-Television sales and service business with capital earned in spare time. Joe Travers, a graduate of mine, in Asbury Park, N. J., writes: 'I've come a long way in Radio and Television since graduating. Have my own business on Main Street.







Each RF and IF coil is wound under the supervision of a skilled operator, and each is tested at several points along the production line. This painstaking care is what gives a high I Q to Delco Radio Coils.

A GENERAL MOTORS PRODUCT


*1NBUILT QUALITY. The "Q" of a coil affects its performance in the circuit, and is of vital importance to the radio engineer. The "IQ" of all RF and IF coils used for servicing is of equal importance to you, and can mean real customer satisfaction. To assure high IQ, Deleo Radio earefully controls the production of all RF and IF coils—both original equipment and replacement coils.


If you could visit the Delco Radio plant, you would see skilled operators sitting at expensive specially designed machines winding high-quality coils. On the production line, these coils are assembled with their powdered iron cores and shield cans. By controlling all steps of the production, Delco Radio gives its coils not only the required Q, but also the highest possible $IQ-Inbuilt\ Quality$. Delco Radio parts are available through your UMS Delco Electronics Distributor.

DISTRIBUTED BY ELECTRONIC PARTS DISTRIBUTORS EVERYWHERE


DELCO RADIO

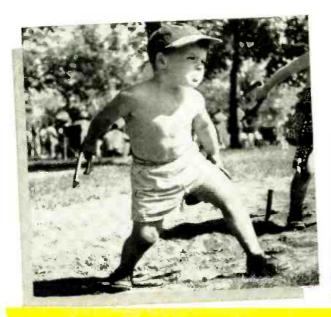
DIVISION OF GENERAL MOTORS CORPORATION, KOKOMO, INDIANA



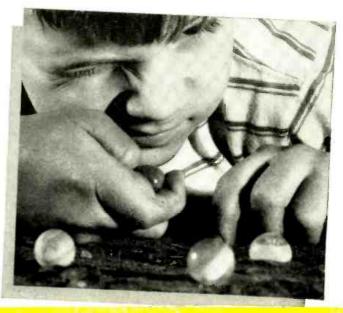

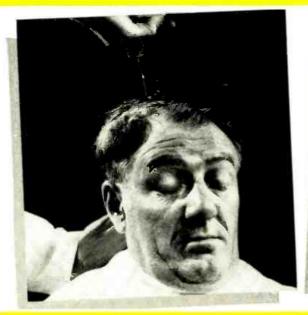=SERIOUS SERVICEMEN = DRAW A BEAD ON QUALITY, =



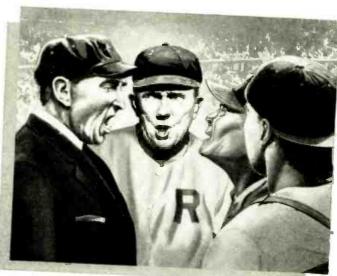

=OFFER PROFESSIONAL TREATMENT AND AVOID RHUBARBS.=

They combine dependable products with skilled workmanship.

They know they can depend on Du Mont Teletrons to do more for their service.

Replacement Sales, Cathode-ray Tube Division,
Allen B. Du Mont Laboratories, Inc., Clifton, N. J. *T.M.



ADVANCE! Raise your earning power-learn EVISION-ELECTRONICS MASTER ALL PHASES! Get Master Shop-Method Home Training from

GOOD JOBS AWAIT THE TRAINED RADIO-TV TECHNICIAN

There is a place for you in the great Radio-Television-Electronics industry when you are trained as National Schools will train you at home!

Trained technicians are in growing demand at good pay —in manufacturing, broadcasting, television, communica-tions, radar, research laboratories, home Radio-TV service, and other branches of the field. National Schools Master Shop-Method Home Training, with newly added lessons and equipment, trains you in your spare time, right in your own home, for these fascinating opportunities. OUR METHOD IS PROVED BY THE SUCCESS OF NATIONAL SCHOOLS TRAINED MEN, ALL OVER THE WORLD, SINCE 1905.

EARN WHILE YOU LEARN

Many National students pay for all or part of their training with spare time earnings. We'll show you how you can do the same! Early in your training, you receive "Sparetime Work" Lessons which will enable you to earn extra money servicing neighbors' and friends' Radio and Television receivers, appliances, etc.



National Schools Training is All-Embracing

National Schools prepares you for your choice of many job opportunities. Thousands of home, portable, and auto radios are being sold daily-more than ever before. Television is sweeping the country, too. Co-axial cables are now bringing Television to more cities, towns, and farms every day! National Schools' complete training program qualifies you in all fields. Read this partial list of opportunities for trained technicians:

Business of Your Own . Broadcasting Radio Manufacturing, Sales, Service • Telecasting Television Manufacturing, Sales, Service Laboratories: Installation, Maintenance of Electronic Equipment Electrolysis, Call Systems Garages: Auto Radio Sales, Service Sound Systems and Telephone Companies, Engineering Firms Theatre Sound Systems, Police Radio And scores of other good jobs in many related fields.

TELEVISION TRAINING

You get a complete series of up-to-the-minute lessons covering all phases of repairing, servicing and construction. The same lesson texts used by resident students in our



modern and complete Television broadcast studios, lab-

oratories and classrooms!

FREE! RADIO-TV BOOK AND SAMPLE LESSON! Send today for

National Schools' new. illustrated Book of Oppor-

tunity in Radio-Television-Electronics, and an actual Sample Lesson. No cost no obligation. Use the coupon now-we'll answer by return

APPROVED FOR VETERANS AND **NON-VETERANS**

NATIONAL SCHOOLS

IN CANADA: 811 W.HASTINGS STREET, VANCOUVER, 8.C

VETERANS: Give Date of Discharge_

airmail. Both Resident and Home Study Check coupon below Courses Offered! LOS ANGELES 37. CALIFORNIA . ESTABLISHED 1905 GET FACTS FASTEST! MAIL TO OFFICE NEAREST

charges.

an Established Practical Resident School

Superheterodyne Receiver

You receive and keep all the modern equipment shown

above, including tubes and

valuable, professional qual-

ity Multitester. No extra

LEARN BY DOING

RADIO IFLEVISION

SAMPLE LESSON

fical Resident Training with its own Training

Shops, Laboratories, Studios — almost 50 Years of Successful Experience in Training Ambitious Men.

You also

receive this

Multitester

We Bring National Schools To You!

NATIONAL SCI	100LS,	Dept. RH-124	
4000 S. Figueroa Street Los Angeles 37, Calif.	or	323 West Poll Chicago 7	
Send FREE Radio-TV Fesson. No obligation, no sa			REE Sample
AME		_BIRTHDAY	19
DDRESS		_BIRTHDAY	19

Check here if interested in Resident School Training at Las Angeles.

(mail in envelope or paste on postal card)

December, 1954

SYLVANIA

Announces

A NEW LOW COST

POLYMETER

The TYPE 303

"the ultimate in precision test equipment"

for only \$54⁵⁰

Engineered by Sylvania - styled by Sundberg-Feran



An outstanding POLYMETER of comportness and quality that was engineered for your every day use. This new low cost instrument is "a must" for all who are skilled in the field of electronics.

FEATURES THAT YOU NEED!

Designed to aid the serviceman in "on-location" servicing

Six DC Ranges.

✓ Six AC Ranges.

Six Resistance Ranges.

Permanently Attached Leads,

10 Megohm Input Resistance.

High Tolerance Components.

Utility Size.

Clear Plastic Meter Case.

Sylvonio again leads the nation with a complete line of Polymeters to meet your every need. The Type 303, the "mighty-mite" of the line is a compact, partable unit in every sense. It was designed when the need of a highly accurate, low cost and extremely readable meter was called for by those who are daily engaged in making measurements on electronic equipment. This modestly priced instrument with permanently attached leads and clear plastic meter case assures speedy, accurate workmanship. The Type 303 is professionally styled to inspire customer confidence in your equipment and service.

Available through your SYLVANIA RADIO TUBE DISTRIBUTOR

SYLVANIA

TEST EQUIPMENT

Sylvania Electric Products Inc., 1221 W. Third St., Williamsport, Pa.
In Canada: Sylvania Electric (Conada) Ltd., University Tower Bldg.,
St. Catharine St., Montreal, P. Q.

RADIO . TELEVISION . LIGHTING . ELECTRONICS



L. C. Lane. 8.5., M.A. President, Radio-Television Training Association. Executive Director, Pierce

THREE COURSES TO TRAIN YOU FOR THE JOB YOU WANT

RITA

RADIO-FM-TELEVISION TECHNICIAN

COURSE — No previous experience necessary. You learn by practicing with the professional equipment I send you. Many of my graduates now have good paying technician jobs with such firms as RCA, NBC-TV, Dumont TV and numerous other TV Studios and plants.

FM-TV TECHNICIAN COURSE — Previous training or experience in radio required. You can save months of time if you have previous Armed Forces or civilian radio experience! Train at home with kits of parts, plus equipment to build BIG SCREEN TV RECEIVER. ALL FURNISHED AT NO EXTRA COST!



EXTRA TRAINING IN NEW YORK CITY AT NO ADDITIONAL COST — After you finish your home study training in either of these two courses, you get two weeks, 50 hours, of intensive Laboratory work on modern

electronic equipment at our associate school in New York City, Pierce School of Radio & Television. THIS EXTRA TRAINING IS YOURS AT NO EXTRA COST WHATSOEVER. My courses are complete without this extra training, but it gives you added opportunity for review and practice.

TV CAMERAMAN AND STUDIO TECHNICIAN COURSE — Advanced training for men with radio or IV training or experience. I train you at home for an exciting high pay job as the man behind the IV camera.

VETERANS

My school fully approved to train Veterans under New Korean G. I. Bill. Available only to Veterans discharged after August 20, 1951. If eligible, CHECK COUPON!

EARN WHILE YOU LEARN — Almost from the very start you can earn extra money while learning by repairing Radio-TV sets for friends and neighbors. Many of my students earn up to \$25 a week . . . pay for their entire training from spare time earnings . . . start their own profitable service business.

FREE FCC COACHING COURSE — Important for BETTER PAY JOBS requiring FCC License. You get this training AT NO EXTRA COST. Top TV jobs go to FCC-licensed technicians.

ENOUGH EQUIPMENT
TO SET UP YOUR
OWN HOME
LABORATORY

With the equipment I send you as part of your course you BUILD and KEEP a professional GIANT SCREEN TV RECEIVER complete with big picture tube (takes ony size up to 21-inch)... also a Super-Het Radio Receiver, AF-RF Signal Generator, Combination Voltmeter-Ammeter-Ohmmeter, C-W Telephone Transmitter, Public Address System, AC-DC Power Supply. Everything supplied, including all tubes. My practical, easy-to-understand lessons have brought success to hundreds of men. You, too, can train for a better-paying job or set up a business



Radio Television Training Association

52 EAST 19th STREET • NEW YORK 3, N. Y. Licensed by the State of New York • Approved for Veteran Training

Just by clipping the coupon below and sending it to me today, you can open up a whole new future for yourself in America's fastest-growing field—Radio-Television-Electronics.

The very day I receive your coupon I will send to you. Free a Sample Lesson and my New 36-page Book showing you "How to Make Money in Television, Radio, Electronics" by STUDYING AT HOME IN YOUR SPARE TIME.

At absolutely no cost or obligation you can see for yourself how you can begin how to prepare yourself for a better-paying career as a TV repairman, studio technician, cameraman or any one of the many promising, jobs in the field that is bringing success and security to handreds of men — many of them with no more than grammar school education and no experience whatsoever.

If you think I was exaggerating when I said, "My Free Lesson May Change Your Entire Life," just see what some of my graduates say about my training —

"RTTA training gave me the skill and know-how to do the work I love best and enjoy better things in life."
Harold Gimlen Flint, Michigan

Public Addre

"If it had not been for you, your instructors and the school, I never would have had this opportunity.
J. A. Irwin Radio.TV Repairman Coburg, Ont., Canada

"I know I would not have achieved this progress if it weren't for the help and guidance from RITA."

Edward Breault Chief Radar Operator National Guard Central Falls, R. L.

These letters and many more like them are in my files. The TV Boom that brought good opportunities to these RTTA graduates is still on with no sign of letting up. Don't let opportunity pass you by. Write hoday for your Sample Lesson, new 36-page book, TV Job Opportunities List, and 48-state list of future TV stations — ALL FREE!

MAIL THIS COUPON TODAY!

Mr. leonard C. Lane, President	Dept. T-12
RADIO-TELEVISION TRAINING ASSOCIATION SEEDS 19th Street, New York 3, N. Y.	N
JA COST 19TH SITEET, NEW TOTE S. N. T.	
Dear Mr. Lane: Mail me your NEW FREE BO	
FREE aids that will show me how I can make	
understand I am under no obligation and no sa	lesman will catt.
(PLEASE PRINT PL	AINLY)
Name	Age
Address	
Address	
Address	ZoneState
City	
City	
City	ED IN:
City	ED IN: VETERANS

NO SALESMAN WILL CALL!

He's using the telephone that lends an extra hand



"Sure . . . I'm looking up the figures right now!" From busy executives to clerks, people in business can work more easily and officiently with Bell's new Distant Talking Telephone. Small white rectangle is the loudspeaker.

For people who want to keep both hands free when they telephone, Bell Telephone Laboratories engineers have devised a new telephone with a sensitive microphone in its base.

To use it, simply press a button. The microphone picks up your voice and sends it on its way. Your party's voice comes to you through a small loud-speaker. Both hands are left free.

The volume can be adjusted to suit yourself. If privacy is needed, you simply lift the handset; this shuts off the microphone and loudspeaker and you talk just as you would on a regular telephone.


This new development of Bell Laboratories increases the number of ways your local Bell telephone company can serve in businesses and homes.

Bell Telephone Laboratories



Improving telephone service for America provides careers

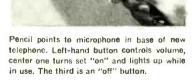for creative men in scientific and technical fields.





YOUR FCC

If you have had any practical ex-perience—Amateur, Army, Navy, radio, repair, or experimenting.



OUR AMAZINGLY EFFECTIVE JOB-FINDING SERVICE HELPS CIRE STUDENTS GET BET-TER JOBS. HERE ARE JUST A FEW RECENT EXAMPLES OF JOB-FINDING RESULTS:

GETS CIVIL SERVICE JOB

"Thanks to your course I obtained my 2nd phone license and am now employed by Civil Service at Great Lakes Naval Training Station as an Equipment Specialist." Kenneth R. Leiser, Fair Oaks, Mtd. Del., McHenry, Illa

GETS STATE POLICE JOB

"I have obtained my 1st class ticket (thanks to your school) and since receiving same I have held good jobs at all times. I am now Chief Radio Operator with the Kentucky State Police." Edwin Healy 264 E. 3rd St., London, Ky.

GETS BROADCAST JOB

"I wish to thank your Job-Finding Service for the help in securing for me the position of transmitter operator here at WCAE, in Pittsburgh." Walter Koschik, 1442 Ridge Ave., N. Braddock, Pa.

GETS AIRLINES JOB

"Due to your Job-Finding Service, I have been getting many offers from all over the country, and I have taken a job with Capital Airlines in Chicago, as a Radio Mechanic."

Harry Clare, 4537 S. Drexel Blvd., Chicago, III.

HERE'S PROOF FCC LICENSES ARE OFTEN SECURED IN A FEW HOURS OF STUDY WITH OUR COACHING AT HOME IN SPARE TIME:

Name and Address	License	Lessons
Lee Worthy, 22101/2 Wilshire St., Bakersfield, Cal	2nd Phone	16
Clifford E. Vogt. Box 1016, Dania, Fla		20
Francis X. Foerch, 38 Beucler Pl., Bergenfield, N. J	1st Phone	38
\$/\$gt. Ben H. Davis, 317 North Roosevelt, Lebanon, III		28
Albert Schoell, 110 West 11th St., Escondido, Cal		23
CARL E. SMITH, E. E. Consulting Eng		

CLEVELAND INSTITUTE OF RADIO ELECTRONICS Desk RN-71, 4900 Euclid Bldg., Cleveland 3, Ohio

December, 1954

If you fail to pass your Commercial License exam after completing our course, we guarantee to continue your training without additional cost of any kind, until you successfully obtain your Commercial license, provided you first sit for this examination within 90 days after completing your course. TELLS HOW

Here is your guarantee

EMPLOYERS MAKE JOB OFFERS LIKE THESE TO OUR GRADUATES EVERY MONTH!

Letter from nationally-known Alclines, "We would also appreciate if you would place the following additional advertisement in your infletin-Wanted—Suncintendent of Communications . . . Salary \$66.66 per month."

Letter from nationally known alrelane manufacturer, "We need men with electronic training or experience in radar maintenance to tectum oberational cheek-out of radar and other electronics systems . , start-ing salary . . . atmenting to \$220.03 per month."

Letter from nationally-known Airlines, "We are templating placing", an Airline Ground I Engineer," Starting salary \$385 per month.

MOREY MAKING

INFORMATION

These are just a few of the examples of the job offers that come to our office periodically. Some ifcensed radioman filled each of these jobs: it might have been you!

Ours is the only home study course which supplies FCC-type examinations with all lessons and final tests.

SAMPLE

FEE THE HAT

TRAINING AND

COACHING

Your FCC Ticket Is recognized by most employers in the electronic field as proof of your technical ability.

27

MAIL COUPON NOW! FCC LICENSE

Cleveland Institute of Radio Electronics

Desk RN-71—4900 Euclid Bldg., Cleveland 3, Ohio
(Address to Desk No. to avoid delay)

I want to know liow I can get my FCC Ticket In a minimum of time. Send me your FREE hooklet. "How to Pass FCC License Examinations" (does not cover exams far Amateur License), as well as a sample FCC type exam and the amazing new booklet. "Money-Making FCC License Information."

Be sure to tell me about your Television Engineering Course.

City	Zone	State	
Address			
Nanie			

FOR PROMPT RESULTS, SEND AIR MAIL
Special tultion rates to member of the U.S. Armed Forces

Picture Tube and Receiver Testing



FOR ALL BLACK AND WHITE SETS.

ADAPTABLE TO COLOR.



30 or 60 KV by

HV Probe.

work out of C-R tube testing and BOLAND TV trouble. shooting! New Boland & Boyce & BOYCE C-R Tube Tester tests all magnetic picture DYNAMIC tubes dynami. cally-under the C.R.T. TESTER receiver's own power. Tells in-Model 701 stantly whether tube or set is at fault. 600 V. d-c range extends to

Separate plugin power supply available for in-carton tube testing. Prices include 2 cabled leads and instruction manual. KIT—\$29.95. FACTORY WIRED & TESTED—\$39.95. Sold by leading distributors.

B&B BIAS BOX Speeds Alignment and AGC Troubleshooting



Supplies steady, accurately adjustable bias valtages from 0 to 17 volts d-c to substitute for receivers' normal automatic-gain- or automatic-volume-control circuits. A "must" for radio and TV alignment. Clips and grounds to chassis apron; powered by receiver's 6.3 v. heater supply. KIT—only \$9.95. FACTORY WIRED & TESTED—\$12.95.

UNIVERSAL HV PROBE for all meters, all ranges



Extends range of any VTVM, or any multimeter or voltmeter having sensitivity of 10,000 ohms-pervolt or more. Supplied with complete set of plug-in precision resistors and in-

structions to accurately match any meter . . any range— 10KV, 30KV, 60KV, and others. Clear, high-dielectric probe body shows resistors in use. Includes shielded coble with Amphenol connectors and phone tips. \$12.95 net.

Write for Brochure Describing B&B Products

BOLAND & BOYCE, INC.

Dept. RN-124, 236 Washington Avenue Belleville 9, N. J.

Within the INDUSTRY

NATHANIEL B. NICHOLS, manager of Ruythcon's research division, has been

appointed assistant vice-president of the firm.

Mr. Nichols, an authority in the fields of servomechanisms and electronics automation, joined the Waltham firm in 1951. He



helped to develop several of the company's unusual products, leading his scientific group through the investigative phases of work that eventually made possible the mass production of transistors.

He is a member of the IRE, Instrument Society of America, American Physical Society, American Chemical Society, AIEE, and other professional groups.

DOUGLAS Y. SMITH has been elected vice-president and general manager of RCA's Tube Division. He was formerly general marketing manager of the division . . . RONALD E. VEDDER is the new supervisor of sales training for the radio and television division of Sylvania Electric Products Inc. . . . The appointment of J. J. LANGLOIS as general sales manager has been announced by General Dry Batteries, Inc. of Cleveland. He was formerly associated with Remington Rand, Inc. for 28 years . . . GENE MILLER has been named to the post of advertising and sales promotion manager for V-M Corporation, phonograph, record changer, and tape recorder manufacturer . . . B. V. K. FRENCH has been appointed to the post of service manager for the Regency Division of I.D.E.A., Inc. He will be in charge of all technical writing and correspondence on service problems
... DR. V. K. ZWORYKIN, television pioneer and inventor, has retired as vice-president and technical consultant for RCA Luboratories and has been elected as the first honorary vicepresident in the Corporation's history in recognition of his epoch-making achievements in the fields of television and electronics. He was associated with Westinghouse before joining RCA in 1930 . . . CARROLL W. HOSHOUR has been named products manager for Magnecord, Inc. He will be in charge of sales engineering, quality control, product service, and technical sales promotion for all divisions of the company. He was formerly associated with Ruytheon . . . ARNOLD E. LINTON has been appointed manager of the RCA tube manufacturing plant in Woodbridge, N.J. He joined the company in 1934 . . . JACK MOORE has been named sales manager of Skyline Mfg. Co., Cleveland antenna manufacturer . . . RALPH L. PALMER is the new director of engineering for International Business Machines Corporation. He was formerly manager of the company's engineering laboratory at Poughkeepsie Krylon, Inc. has named DONALD K. BAXTER to the post of sales manager. He was formerly a manufacturer's representative for the firm in the middle Atlantic states . . . P. R. Mallory & Co. Inc. has appointed DOUGLAS M. CONSIDINE to the post of sales promotion and merchandising manager. He was formerly associated with Minneapolis-Honeywell Regulator Company for fourteen years . . DOUGLAS H. CARPENTER, chief antenna engineer for JFD Manufacturing Company, has been named chairman of the RETMA Antenna Committee . . . WILLIAM A. GOTHARD has been named president and general manager of Gothard Manufacturing Company, succeeding his father, R. W. GOTHARD, as active manager. The founder of the firm will supervise the firm's West Coast activities . . . JULIAN K. SPRAGUE, president of Sprague Electric Co., has been named chairman of the Advisory Group on Electronic Parts of the Department of Defense . . . FRANK ADAMS has been named sales manager of the Mid-Atlantic division of ORRadio Industries with headquarters at 547 Hermitage treet in Philadelphia 🖣 . . HAROLD J. ADLER has been named chief engineer in charge of the color TV development program at Lion Manufacturing Corp. of Chicago. He was formerly associated with Edwin I. Guthman & Co., Inc. . . . JOHN J. TRAVIESAS has been upped to the post of general service manager of United Motors Service, succeeding C. E. REINHARDT who has retired.

ELMER O. WILSCHKE has resigned his post as operating manager of *Altee*

Service Corporation to become vice-president in charge of operations for Fine Sound, Inc.

Mr. Wilschke joined Electrical Research Products. Inc. in 1928 following an association



with Western Electric Company. During the early days of sound motion pictures he served in various capacities in this country and abroad. Upon formation of Altec in 1937 he became manager of the company's division office in Philadelphia.

From 1941 to 1946, he was plants

Home Study Courses in TELEVISION SERVICING offered by RCA INSTITUTES



Study Television Servicing—from the very source of the latest, up-to-the-minute TV and Color TV developments. Train under the direction of men who are experts in this field. Take advantage of this opportunity to place yourself on the road to success in television. RCA Institutes, Inc. (A Service of Radio Corporation of America), thoroughly trains you in the "why" as well as the "how" of servicing television receivers.

FIRST HOME STUDY COURSE

IN COLOR TV SERVICING

Now you can train yourself to take advantage of the big future in Color TV. RCA Institutes Home Study Course covers all phases of Color TV Servicing. It is a practical down-to-earth course in basic color theory as well as how-todo-it servicing techniques.

This color television course was planned and developed through the combined efforts of instructors of RCA Institutes, engineers of RCA Laboratories, and training specialists of RCA Service Company. You get the benefit of years of RCA research and development in color television.

Because of its highly specialized nature, this course is offered only to those already experienced in radio-television servicing. Color TV Servicing will open the door to the big opportunity you've always hoped for. Find out how easy it is to cash in on color TV. *Mail coupon today*.

SEND FOR FREE BOOKLET

Mail coupon in envelope or paste on postal card. Check course you are interested in. We will send you a booklet that gives you complete information. No salesman will call.



you are intera booklet that ation. No sales-

RCA INSTITUTES, INC.

A SERVICE OF RADIO CORPORATION of AMERICA 350 WEST FOURTH STREET, NEW YORK 14, N.Y.

HOME STUDY COURSE IN BLACK-AND-WHITE TV SERVICING

Thousands of men in the radio-electronics industry have successfully trained themselves as qualified specialists for a good job or a business of their own—servicing television receivers. You can do this too.

This RCA Institutes TV Servicing course gives you up-tothe-minute training and information on the very latest developments in black-and-white television.

As you study at home, in your spare time, you progress rapidly. Hundreds of pictures and diagrams, easy-to-understand lessons help you to quickly become a qualified TV serviceman.

There are ample opportunities in TV, for radio servicemen who have expert training. Mail coupon today. Start on the road to success in TV Servicing.

MAIL COUPON NOW

RCA INSTITUTES, INC. Home Study Dept. RN-1254 350 West Fourth Street, New York 14, N. Y. Without obligation on my part, please send me copy of booklet on:

☐ Home Study Course in Television Servicing.
☐ Home Study Course in Color TV Servicing.

Name	(please print)
Address	
City.	Zama State



manager for Altec Lansing Corporation in Los Angeles, returning to the Service Corporation in 1946 as assistant to the vice-president.

EUGENE E. BROKER has been named manager of the *Sylvania* radio tube

plant at Shawnee, Oklahoma, succeeding Charles W. Hosterman who recently was named to the newly - created post of assistant general manager of the company's electronies division.



Mr. Broker joined the company in 1929 and served in various supervisory capacities in the filament department at the company's division headquarters in Emporium, Pa. until 1942 when he became supervisor of a feeder plant at Galeton, Pa.


He is a member of the American Management Association and a 25-year club member of the company. He will make his headquarters in Shawnee.

BLONDER-TONGUE LABORATORIES, INC. of Westfield, N.J. has expanded its production capacity with the opening of a second plant nearby. The company now has a total of over 50,000 square feet of space for the production of its master TV antenna systems and u.h.f. converters... CONRAC, INC. is building a new addition to its main manufacturing plant at Glendora, California. The new facility will provide 20 per-cent more production space for the company's line of custom TV receivers . . . THE RADIO APPARATUS CORP. has moved to new quarters at 7900 Pendleton Pike in Indianapolis. The company, which makes communications equipment, is an affiliate of I.D.E.A., INC. . . SIMPSON ELECTRIC CO. of Chicago has purchased a 4-story building at 4307 W. Lake Street in Chicago. The new plant provides over 100,000 square feet and will be used for the manufacture of the company's new color TV test equipment and suspension type meter . . . BOGUE ELECTRIC COMPANY has opened a west coast office at 13415 Ventura Blvd., Sherman Oaks, California. Wm. J. Hopkins will head the new office . . . RAY R. HUT-MACHER ASSOCIATES, INC. has moved into new and larger quarters at the Chicago International Building located at 6647 N. Oliphant. The firm was formerly at 644 N. Michigan . . . GENERAL CEMENT MFG. CO. and TELEVISION HARDWARE MFG. CO. of Rockford, Ill. are completing two new plant additions which will add 10,000 and 25,000 square feet to their plants #1 and #2 respectively . . . SERVOMECHANISMS, INC. has broken ground for the construction of its seventh plant at 12500 S. Aviation Blvd. at the Los Angeles International Airport. The plant will be ready for operation in the Spring . . . Two new buildings totaling 6000 square feet have been added to the Metuchen, N.J. plant of GULTON INDUSTRIES, INC.

(Continued on page 158)

RADIO & TELEVISION NEWS

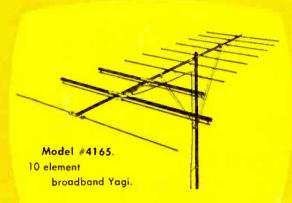A new standard in electrical and mechanical perfection in all 32 new YAGI antennas



Walsco's exclusive
"umbrella" snap-out
design provides perfect
element alignment
instantly.





WALSCO
"futurized"
YAGIS
reach
everywhere



NOW...a complete line of 32 "futurized" Yagi antennas with superlative performance... for fringe and ultra-fringe areas; for black and white and color on all present and future channels. No loose hardware... completely pre-assembled using Walsco's exclusive "umbrella" snap-out design. Nothing compares at any price!

Write for complete information on all 32 "futurized" Yagi models



The state of the s

3602 Crenshaw Blvd. • Las Angeles 16, California

Overseas Distributor: Ad Auriema, Inc. • 89 Broad St., New York 4, N.Y.



ENGINEERING EXCLUSIVES... REASONS WHY...



STOP WATCH TUNING ACCURACY

Pinpoint control system is uncurpassed in consistent accuracy of indication. Stops antenna instantly within ½ degree of desired position. No drift or ambiguity.

SMARTLY STYLED CONSOL WITH PIANO TUNIN

The striking control console is designed for beauty of ase of operation. Actuates the rotator with the slightest touch. Available in mahogany or ivosy cabinet.





REPLACEABLE FACTORY SEALED CARTRIDGE UNIT

Sealed power drive unit eliminates the former need of dismantling the antenna when servicing. Simply loosen 3 screws to remove the sealed un

POWERFUL INLINE DESIGN

Supports direct dead weight load of largest stacked array. Resists downthrust and bending moment. Built-in thrust bearings. No extra parts to buy. No breakable offset bearings.





5 COLORFUL "CARRY ALL" CARTON

Safely protects Roto-Kine in route . . . eases on-the-job carrying of units . . comes in handy in the shop or around the home. A JFD merchandising extra at no extra cost.

AUTOMATIC VOLTAGE COMPENSATION

Advanced circuitry achieves automatic voltage compensation for stability and exactness of indication despite line voltage fluctuations.

BALANCED POWER

Close tolerance 3200:1 reverted gear drive (within .002 in. tolerance) efficiently transmits 100% of developed power. No inherently weak worm gears

8 390 DEGREE ROTATION

390 degrees - the broadest traverse range now in use – speeds and simplifies station selection beyond standard 360 degree revolution.



Roto W King

is rocking the rotator market!

Model

Style

List

RT100-M Mahogany

RT100-IV

lvory

\$44.95

Write for 8-page Roto-King engineering brochure No. 288.





Look to JFD for Engineering Leadership! MANUFACTURING CO., INC.

6101 16th AVENUE, BROOKLYN 4, N. Y.

INTERNATIONAL DIVISION: 15 Moore Street, New York 4, U.S.A.

X-RAYS SHOW THE DIFFERENCE....

3 more new G-E SERVICE-DESIGNED

- Cost no more
- Have longer life
- Improve TV performance
- Cut servicing call-backs
- Interchangeable with prototypes

See your G-E tube distributor today! Tube Dept., General Electric Company, Schenectady 5, New York.

PROVED

PACE SETTERS—
G.E.'s FIRST 6

SERVICE-DESIGNED
TUBES!

NEW IB3-GT

MADE IN TUBE

Does a superior job far longer. Special lead glass wards off electrolysis and air-leakage. New ring around filament stops "bowing" and the filament burnouts that result.

NEW 5U4-GA

Huskier. New mica supports, at both tap and bottom. New straight-side gloss bulb. New double-fin plate, new button-stem base with the many odvantages of this construction.

NEW 5Y3-GT

New sturdiness, new long life. Mica supports now brace tube structure at both top and bottom. Double-fin heat-dissipating plote construction. New button-stem base.

NEW 6BQ6-GA

Runs far cooler, because of larger bulb. Handles higher pulse plate valtages. Highmelting-point solder keeps cap-terminal in place when removing tube for testing.

NEW 25BQ6-GA

Runs cooler. Handles higher pulse plate voltages. Same extensive improvements as new 6BQ6-GA, including larger bulb, high-melting-point solder for cop-terminal. etc.

NEW SERVICE-DESIGNED 125N7-GTA

Side-by-side X-ray pictures at right show that G.E.'s new SERVICE-DESIGNED 12SN7-GTA is smaller (28% less bulb height) than ordinary 12SN7-GT's ... sturdier ... with the many advantages which buttonstem base construction offers.

Comparison with the prototype's pressed-stem base, shows that the tube leads now pass through individual seals at bottom of envelope. Prevents loose bases... gives shorter leads and better lead separation... and brings about better heat conduction, reducing electrolysis and tube leakage. You get a longer-lived tube than ever before.

Tube ratings have been substantially increased. Compare below:

Old New 125N7-GT 125N7-GTA

Max plate voltage 300 v 450 v

Max plate dissip.

3½ w 5 w

And the new 12SN7-GTA is specially tested for dependable operation in all synchro-guide and other circuits! Every tube gets a "chopper" pulse test, made at the lowest TV line voltages that will be encountered.



INSIDE STORY of more compact design, new button-stem base!





OLD 12SN7-GT

NEW 12SN7-GTA


NEW SERVICE-DESIGNED 6AX4-GT

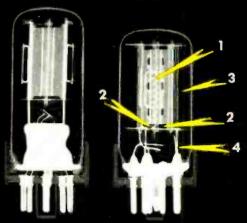- 1. A new "pigtail" winding guards against heater-cathode shorts by interposing a separate insulated barrier between heater wire and cathode. This is much more efficient than other insulating methods used before. Tube failures are greatly reduced.
- 2. Two design features cut down on plate-cathode arc-overs. The plate is notched to avoid any contact with mica spacers in the critical plate-cathode areas. Also, micas are slotted to set up barriers to electrical conduction. Result: fewer fuse blow-outs in horizontal-deflection circuits—a common cause of call-backs.
- 3. Edge of the plate now is flattened out to dissipate electrostatic charge under high-voltage conditions. Stabilizes performance—prevents erratic operation of the tube.
- 4. New button-stem hase adds strength, shortens tube leads, and improves heat conduction ... increasing tube life. Helps to make possible a new bulb 18% shorter, more compact.

ANOTHER PLUS: new SERVICE-DESIGNED 6AX4-GT's are specially tested for arc-overs at maximum ratings. Every tube gets this important test!



INSIDE STORY, why shorts and arc-overs are reduced.



OLD 6AX4-GT

NEW 6'AX4-GT


NEW SERVICE-DESIGNED 6BX7-GT

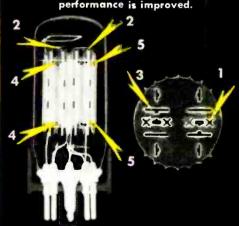- 1. New "flipper" (criss-cross) apertures in the mica spacers apply a firm 4-corner grip to the grid legs—keep grids locked in place top and bottom. This greatly reduces microphonics that result from changes in tube inter-element spacing...helps prevent vertical picture jitter.
- 2. Covered "penthouses" (box enclosures) now shield cathode and heater from getter contamination that causes electrical leakage, disturbing the relationship of tube elements.
- 3, 4. Special slots in mica spacers, and notched plate design, further ward off inter-element arc-overs and leakage.
- 5. Barrels of the plates now are flared out at ends to avoid disturbing delicate grid wires when tube is assembled. Helps assure uniform tube performance.

ALSO: gold-plated grid wires minimize grid emission, a cause of picture shrinkage and foldover . . arc-over test of every tube assures dependability of SERVICE-DESIGNED 6BX7-GT's.



INSIDE STORY, why electrical performance is improved.




NEW 6BX7-GT

NEW 6SN7-GTA

Redesigned to give top performance in all synchro-guide and other IV circuits. Every tube gets "chopper" pulse test at low line voltages. Ratings substantially increased. Progress Is Our Most Important Product

GENERAL



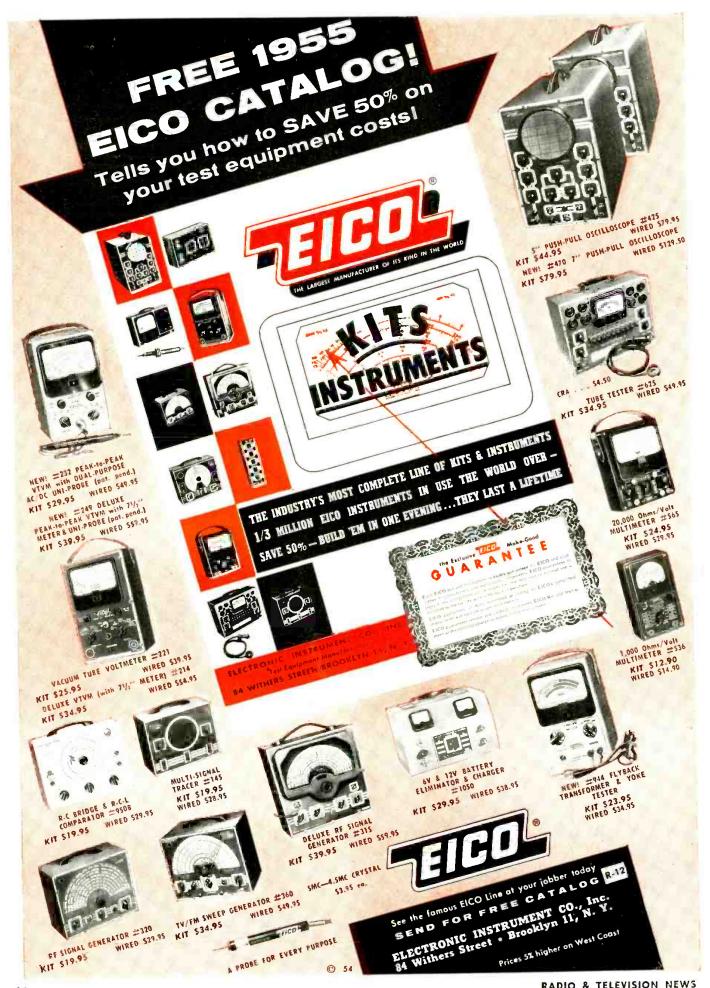

BUILD YOUR OWN TV COLOR CONVERTER

By JAY STANLEY

WHEN black-and-white TV first became a reality, the whole thing was something of a deep, dark mystery to most radio service technicians of the era. But a few brave souls took the plunge, built their own sets, and had the thrill of getting out ahead of most of their competitors and in on the ground floor of a tremendous industry.

Color TV is off to a better start. Many manufacturers are offering courses and a lot of articles have been written about the subject so that the studious can, in a fairly short time, acquire some knowledge of color TV. But, as in all things, there is no substitute for experience with actual equipment on which you have no qualms about experimenting. The cost of present-day color TV sets is high enough to discourage a lot of service technicians (and most consumers) from owning such a receiver.

This article is a practical answer to that problem. Here is step-by-step data for building a color television system. Actually, the original chassis was designed and built by two Denver service engineers; Larry Costa and Paul Dontie.

The unit described in this article is a color converter which can simply be hooked onto a conventional (but carefully selected) black-and-white TV set. It can be used to drive a three-unit projection system, or with a bit more circuitry, a three-gun color picture tube.

A look at the block diagram in Fig. 2 and the circuit diagram of the color converter in Fig. 3 will reveal that it is surprisingly simple when compared to many color TV sets. The secret lies in the fact that the set uses a narrow-band system, with .6 megacycle bandpass limiting. This is possible because demodulation is on the R-Y and B-Y axes instead of the alternative I and Q axes. The I and Q system is a wide-band one.

Thanks to the narrow-band system, eircuitry is much simpler. Likewise,




Part 1: This color TV converter can be used with three projection units or a three-color picture tube and a second-hand black-and-white chassis.

setup, adjustment, and servicing are also much easier. Don't let the "narrow band" worry you. Color quality is impaired so little that it can only be discerned when a narrow-band and a wide-band set are operated side-by-side—and even then it is difficult to see the difference.

Before covering actual construction of the color chassis, let's trace a signal through this circuit to get an overall idea of how it works. As a starting point, we'll begin with the signal which normally drives the grid of the picture tube in the TV set—a signal which is the composite video output, carrying both the black-and-white and

the color information. This signal can be supplied by any really good black-and-white set which has an i.f. bandpass of 4.1 megacycles or more—and maintains this bandpass right through the video amplifier stages. Many of the older TV chassis, built from 1947 to 1949 (split-sound sets), were capable of this bandpass when carefully aligned. The set used here was a *Philco* 1001 chassis, but an *RCA* 630 or an *Admiral* 30A1 (and some others) will work just as well. These are obtainable second hand from many TV dealers.

The composite signal goes to the grid of V_1 , the first video amplifier on

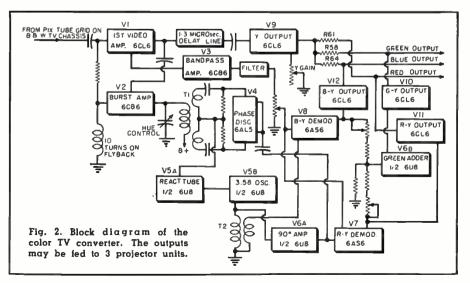

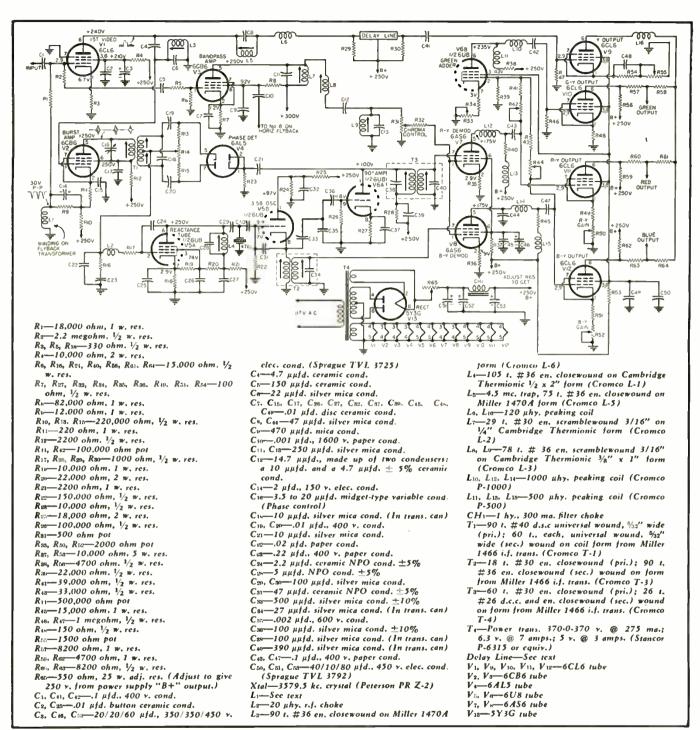


Fig. 3. Complete schematic diagram and parts list for the TV color converter designed to be used with a black-and-white set.

the color chassis. See Fig. 3. The luminance or Y signal is picked up at the plate of the first video amplifier in the color chassis, passes through a 3.58 megacycle trap $(L_{i}-C_{b})$, and is fed to a 1.3 microsecond delay line, which insures that the luminance information and the color signals arrive at the output at the same time. From the delay line, the signal goes to the grid of the Y output tube (V_{\bullet}) . From the plate of this tube, the signal goes through the matrix resistors, $R_{\rm 5s}$, $R_{\rm 6i}$, and R_{64} , where the Y signal and the color-minus-Y signals are mixed to provide green, red, and blue output,

The color-burst signal is also obtained from the plate of V_1 and is fed

to the grid of the burst amplifier, V_2 . This tube is keyed on only during retrace, the keying being accomplished by means of a 10-turn coil wound on the flyback transformer in the black-and-white TV set chassis. (See Fig. 4.) By this means, the color burst, which is on the back porch of the horizontal sync pulse, is amplified—but no other 3.58 megacycle signals get through.

The output of the burst amplifier goes to the phase discriminator transformer T_1 , the secondary of which is also supplied with a comparison signal from the plate of the 90-degree amplifier, $V_{6.4}$. The output of the phase detector is a d.c. correction voltage which is fed to the reactance tube, $V_{6.4}$; this

tube, in turn, controls the frequency and phase of the 3.58-megacycle oscillator, V_{5B} . In this way, the local 3.58 mc. oscillator is locked in exact phase and frequency with the transmitted color burst to supply the synchronous demodulators with the missing color subcarrier, the sidebands of which only are transmitted—the carrier being suppressed at the transmitter.

From the cathode of the 3.58 megacycle oscillator, the signal takes two paths. A signal directly from the cathode goes to the 90-degree amplifier which shifts its phase 90 degrees for proper demodulation in the R-Y demodulator. The secondary winding of transformer T_2 , however, feeds the

B-Y demodulator directly with no phase shift.

The B-Y demodulator and the R-Y demodulator receive their color signals from the bandpass amplifier (V_n) and filter, which has a bandpass of 1.2 megacycles (from 2.9 mc. to 4.1 mc.) and passes only the color subcarrier sidebands. This automatically drops out the low-frequency Y signal.

In the R-Y and B-Y demodulators, the missing carrier is restored and demodulated to produce the R-Y and B-Y signals. The B-Y signal, taken directly from the plate of V_n, goes to the grid of the B-Y output tube, V₁₂. The output of this tube, in combination with some of the Y signal, supplies blue.

The R-Y signal from the plate of the R-Y demodulator goes to the grid of V_{11} , which, in similar fashion to that of the B-Y output stage, supplies the red output signal.

The output of the R-Y and B-Y demodulators is fed to the grid of the green adder, V_{eR}, through a set of resistors. This tube is simply a phase inverter at which the negative signals from the demodulators combine in proper proportion and invert to form the positive green-Y signal. This is fed to the G-Y output for addition with the luminance signal as described previously for the other two colors.

The outputs terminate in jacks along the end of the chassis, making the three color signals and the Y signal readily available for different experimental hookups. Most of the controls are inserted on the rear of the chassis since many of them are setup controls which are left alone once adjusted. Two controls, chroma and phase, are used for minor adjustment during reception, and it is desirable to make them readily available. No "color killer" controls or circuits are needed-simply turning down the chroma control puts the set in shape to receive black-and-white.

In actual construction of the converter, the first step is to round up the needed parts. The careful builder can,

by following the data given in the parts list, "roll his own" coils. A real help in doing this is the setup shown in Fig. 5 which provides approximately the same loading as the converter circuits. This allows the coils to be wound with considerable accuracy without actually inserting them in the circuit. The signal generator should preferably be a 3.58-mc. crystal oscillator. A standard d.c. voltmeter will give a clear-cut indication of resonance. This circuit, however, will indicate when the signal generator is tuned to one-quarter or one-half of the resonant frequency, so if a variable frequency oscillator is used, always switch to the next higher band to make certain that you are actually on the fundamental. The physical layout for the windings of T_1 is shown in Fig. 6.

For those who want to buy coils already wound, the designers of the color converter, Costa and Dontje, will supply coils, and their part numbers are given in the parts list under *Cromco*. Write to *Cromco*, in care of P. Dontje at 7020 W. 38th Ave., Wheatridge, Colo.

The color chassis measures $10 \times 14 \times 3$ inches. The layout is purposely crowded in order to keep leads short and point-to-point. No trouble has been experienced from stray capacity, even though some of the signal carrying leads are longer than were desired.

The chassis illustrated in Figs. 7 and 8 has a cut-out for a *Norelco* video amplifier chassis, to allow use with a single-projection unit and a color wheel. The chassis will eventually be used in this fashion although, at present, three *Norelco* projection units are utilized. There are a couple of other extra holes on the chassis for parts which circuit development later proved unnecessary.

In building, all transformers and tube sockets were mounted first, also terminal strips, filter condensers, and controls. Following usual construction practice, heaters were wired in, and then "B+" voltage leads complet-

(Continued on page 91)

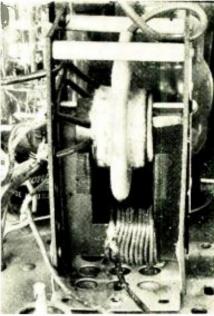


Fig. 4. A ten-turn winding on the flyback transformer keys the burst amplifier on for the proper operation of the 3.58 megacycle color synchronization circuits.

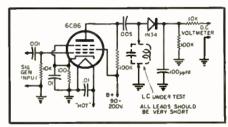


Fig. 5. A test setup which is useful in preparing the coils used in converter.

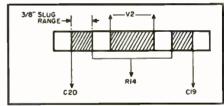


Fig. 6. The physical layout of the phase discriminator transformer windings.

Fig. 7. Top view of the color converter. Note where the crystal is mounted so as to minimize temperature variation effects.



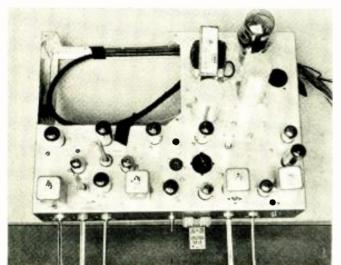


Fig. 8. Bottom view of the converter chassis. The black cable running around the cutout is the delay line in the Y circuit.

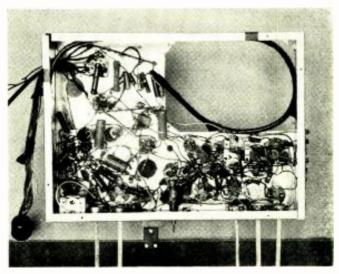

December, 1954 39

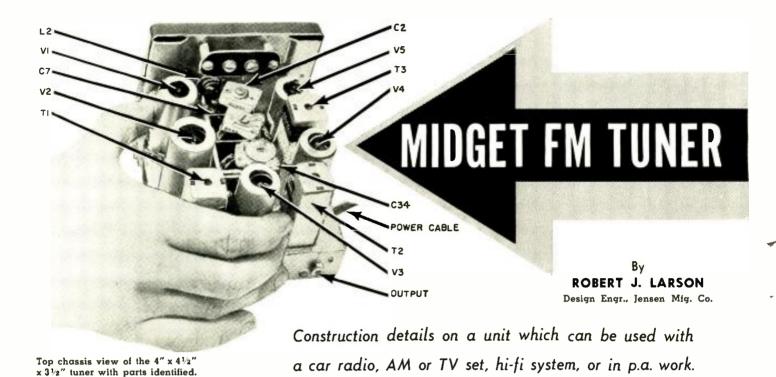

RADIO listeners in most of the larger cities are missing a lot if they have no means of receiving some of the excellent programs to be found exclusively on our FM band. There is little need to mention here the noise-free, wide-range reception possible with this method; one has only to compare the relative fidelity of the AM and FM channels of some of the stereophonic musical programs being broadcast in many cities to hear the difference.

For those who would like to build a tuner for FM, here is a little unit which will be ideal for any of the following applications:

- 1. An FM tuner for use with presently owned high-fidelity amplifier and speaker systems.
 - 2. FM reception in an automobile.
- 3. Use with a tape recorder as a source of wide-range programs and good music.
- 4. Connection to an existing AM-only radio receiver to permit FM reception.
- 5. Connection to a TV set for FM reception.
- 6. Use with a music system in a store or restaurant to provide background music.

Perhaps even more applications will occur to readers after perusing this article.

The entire tuner, shown in the photographs, measures only 4 by 4½ by 3½ inches high, enabling it to be tucked away within the cabinet of existing equipment. Construction is simple and no special mechanical or electrical parts are required. The total cost for parts should be about thirty dollars. The power supply is not included on this chassis, since, in many cases, power may be taken from the associated amplifier or radio. Power requirements are fairly modest as the tuner draws about 30 milliamperes at 150 volts d.c. and 1.65 amperes at 6.3

volts for the heaters. When adding this tuner to an AM receiver it is usually possible to switch off all but the audio tubes and use the additional power supply current thus made available to energize the FM tuner. This has been done successfully with the author's automobile receiver. More about this later in the article. Many hi-fi amplifiers have the extra power available for use with preamplifiers.

For those applications in which the extra power cannot be robbed from accessory equipment a suggested power supply is shown in the inset diagram of the schematic. The components for this supply will easily fit on another chassis the same size as that used for the tuner. The aluminum chassis used for the tuner measures $4 \times 4 \% \times 1$ inch and is made by ICA. Since two sides of the chassis are open the builder may decide to bend his own if materials and tools are available. The tuner uses five high gain tubes: a 6CB6 is used as a pentode r.f. amplifier, feeding a 6X8, which contains a pentode mixer and triode oscillator. Two more 6CB6's are used as 10.7 mc. i.f. stages, followed by a 6AL5 ratio detector. The tuner employs automatic gain control, causing the plate current to vary between 15 and 30 milliamperes, depending upon the signal strength of the station tuned in.

The cathode bias resistor in the 6CB6 r.f. stage is purposely left unbypassed in order to quell a tendency of the stage to oscillate. The r.f. stage is used mainly to isolate the oscillator from the antenna to minimize radiation, and to reduce the presence of images. In the 6X8 mixer, note that the suppressor grid and screen and plate bypass connections are made to the cathode. This causes the oscillator voltage to appear effectively only on

the signal grid, resulting in a highly efficient mixer stage. The use of a single tube here saves valuable space on the small chassis.

Midget 10.7 mc. i.f. transformers made by *Miller* are used in the i.f. stages. These little coils give adequate bandwidth without the use of swamping resistors across the transformer windings, resulting in a high gain per stage. The ratio detector provides, in addition to about one volt of audio, a negative voltage which is used for automatic gain control on all preceding stages of the tuner. About five volts are developed on local stations. R_{12} and C_{31} form a 68-microsecond roll-off network to equalize the pre-emphasis broadcast by all FM stations. Ideally, this time constant should be 75 microseconds, but it was desired to incorporate a slightly rising high-frequency response in the tuner to compensate for the attenuation caused by the shielded cable used to connect the tuner to the amplifier.

The parts layout, as shown in the top chassis photo, provides for short leads and allows the shaft of the tuning capacitor to be centered on the front panel. No volume control is ineluded since in most installations this control is found on the associated equipment. The tuning dial used will depend on the space available. It is suggested that a dial with a large tuning ratio be used, as tuning is more critical than with AM tuners. When installing this little tuner in an AM receiver cabinet it may be possible to arrange the dial cable to turn both the AM and FM tuning capacitors simultaneously.

Shields should be used on all tubes to minimize interference of signals entering at the 10.7 mc, intermediate frequency. A grounding lug is used under one of the screws securing each tube

socket and should be soldered to the central grounding post on the tube socket; all grounds associated with each stage should then be made to this central connection. Mica-filled sockets were used on the first two stages of the tuner to increase gain and minimize drift.

Underneath the chassis a sheet copper partition is used between the r.f. and oscillator/mixer sections of the tuner. One end of the partition is soldered to the grounding lug near the tube socket and the other end is soldered to one of the tuning capacitor ground lugs which projects through the chassis. In addition to shielding, this partition provides a low inductance connection between the capacitor and the coil, which is soldered directly to the copper partition. The r.f. coil, L_{c_i} and the three trimmer capacitors are mounted on top of the variable tuning capacitor. The antenna coil. L_{t_i} is placed adjacent to the grounded end of L_{z} and is supported by a terminal strip fastened to the back of the tuning dial.


Like all equipment used at very high frequencies, this tuner requires some special wiring techniques. All leads should be as short as possible—point to point wiring is used. The new .001 μ fd. disc ceramic capacitors are excellent since the two leads are only about 3/16-inch apart and fit nicely onto the miniature tube sockets. None of these capacitors should have leads over ¼-inch long. Buy a few extra disc ceramics because it is sometimes necessary to bypass both ends of certain long runs of wire on the chassis. This procedure is taken up again later.

The converter filament choke, RFC₂ and RFC₃, is made by winding number 26 enameled wire over an *Ohmite* Z-144 choke. Notice the direction of winding on the choke and wind the number 26 wire over it in a single layer in the same direction. The extra winding is cemented in place with 912-B coil dope or *Duco* cement. Two Z-144 chokes may be used in the filament circuit; this bifilar winding saves space.

Probably the most interesting part of this project is the final alignment and adjustment. You will need a vacuum-tube voltmeter and a signal generator. The author used Heathkit instruments. For the initial tests, connect the tuner to a suitable power supply. A quick check should show about 2 volts at the cathode of each stage except the ratio detector. Then connect the v.t.v.m. to measure the a.g.c. voltage (across R_{18}). Inject a 10.7 mc. unmodulated signal to the grid of the mixer stage and peak the interstage i.f. transformers for a maximum v.t.v.m. reading. If a reading cannot be obtained, try connecting the signal generator to the grid of the first i.f. tube in order to peak up T_2 and T_3 . After these two transformers are aligned it will be possible to obtain a reading by reconnecting the signal generator to the mixer grid. The ratio detector is aligned by using the zero center feature of the v.t.v.m. and connecting to one end of The ground lead of the v.t.v.m. is connected to the tuner chassis. Adjust the top slug of T_3 so that the voltage across C_{30} (or C_{31}) is zero at 10.7 mc. and adjust the bottom slug so that an equal voltage swing is obtained on each side of 10.7 mc. as the signal generator dial is rocked back and forth across the intermediate frequency. These two adjustments interact with each other so this procedure will have to be repeated several times.

If the a.g.c. voltage remains at several volts when the signal generator is disconnected, one of the stages is oscillating. This occurrence is to be expected, and is nothing to become ex-

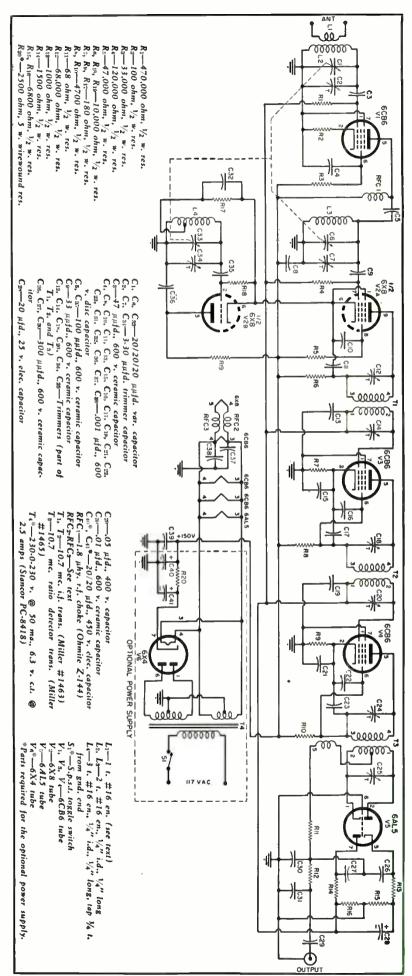Schematic diagram of Midget FM Tuner, An optional power supply is shown within the dotted box.



cited about. Here is where those extra disc ceramic capacitors are useful. Experiment with placement of these bypasses. In the author's tuner, oscillation of the first i.f. amplifier was removed by placing a bypass at both ends of the lead running from the screen to terminal 3 on T_2 . Try bypassing both sides of the filament to ground. Try bypassing both ends of C_{28} to ground. It's safe to bypass anything except a grid or plate lead. If all else fails, try removing the capacitor between cathode and ground. This introduces degeneration and reduces the gain, however.

Alignment of the r.f. stages is easy if there is a station in your area at each end of the FM band. If not, the signal generator can be used. Since signal generator output in the 88 to 108 mc, range is usually a harmonic of some lower frequency signal, the dial calibration should be checked against some accurately calibrated receiver which tunes the 88 to 108 mc. FM band. Connect an amplifier system or earphones to the audio output jack and the antenna to L₁. Connect the v.t.v.m. to read the a.g.c, voltage developed across R_{16} . If the coils have been wound correctly you should be able to tune in some stations. Adjustment of C_{33} should bring the stations to their proper place on the dial. If the FM band is crowded into too few degrees of tuning dial rotation, spread the turns of the oscillator coil, L_1 , apart and realign with C_{ab} . Conversely, to decrease the bandspread squeeze the turns of L_1 together and decrease the capacitance of C_{31} .

When a satisfactory spread of stations is obtained, the mixer and r.f. stages may be adjusted. The author has found the following method of tracking adjustment to be useful in many v.h.f. receivers. Tune in a signal at the high frequency end of the dial and adjust the mixer trimmer, C_{7} , for maximum a.g.c. voltage. Then tune in a signal at the low end of the dial and readjust the trimmer for maximum signal. If it was necessary to increase the capacitance at the low end of the

band, squeeze the turns of the mixer coil, L_{3} , together and try the high and low frequency signals again. A decrease in capacitance indicates that the coil turns should be spread apart. The process is repeated several times until maximum output is obtained at both ends of the dial with one setting of the trimmer. The same procedure is used in adjusting C_{2} and L_{2} in the r.f. stage.


After alignment, the tuner may be connected to the amplifier or radio in its permanent connection. When connecting to an AM radio, connect the output of the tuner across the volume control of the radio in order to be able to control the volume of the tuner as well. An automobile installation is complicated by the extra noise reducing procedures which are usually required. The antenna is somewhat of a problem also, as a horizontal FM dipole exhibits directional characteristics which sometimes cause the station to fade as the automobile turns a corner. After some experimentation the author found the best antenna to be the regular whip used by the car radio in spite of the fact that the transmitting and receiving antennas are cross polarized. Best reception occurred with the whip extended about two feet. Ignition noise, which was troublesome on some of the weaker FM stations, was considerably reduced by the use of resistor type spark plugs. If the tuner is to be used exclusively in an automobile, it is helpful to reduce the capacitance of $C_{\mathbb{P}}$ to 10 microfarads. This decreases the recovery time of the a.g.c. on the rapidly varying signals encountered when the automobile is in motion. The high fidelity FM transmissions may be heard to greater advantage by the use of a better speaker on the car radio, Although the usual oval automobile speaker is adequate for AM listening, better bass and treble response can be quite simply obtained by using one of the new compact loudspeaker cabinets which are now available. The author uses a Jensen "Portable Duette" in the rear seat of his car. The speaker is provided with about forty feet of cable so that it may be used at a distance from the car at the beach or on picnics. This arrangement also provides entertainment while washing the car since it is not necessary to keep the windows open to hear the radio.


An interesting use of this tuner is made when it is used to receive the FM portion of stereophonic radio broadcasts. Several of our leading radio stations are now broadcasting musical programs in this manner. On WMAQ, in Chicago, two microphones are used in the studio, one being connected to their AM transmitter and the other to their FM. In the listener's home, two tuners, two amplifiers, and two speakers are used to recreate the original acoustical atmosphere. For those interested in receiving these broadcasts, it may be advantageous to include an AM tuner circuit on the same chassis with the midget tuner described here.


In spite of its low cost and small size, this little tuner will give many hours of enjoyment. The author's tuner has been in service for over a year, and stations over 50 miles away have been received with the use of a simple indoor folded dipole antenna. Local reception is fully as good as that normally provided by many commercial tuners.

Those builders who live more than 50 miles from an FM station may have better reception if an outdoor antenna is used. Usually, if a television signal is receivable in your area, successful FM reception is also possible. For real DX, one of the commercial yagi type FM antennas should be used. These antennas are installed and oriented in the same manner as TV antennas. If a special FM yagi is not readily available, a channel 6 TV antenna may be modified by cutting down all of the elements to 85 per-cent of their original length. Remove an equal amount of tubing from both ends of each element, of course, and flatten the ends with a hammer. This cut-down TV antenna will resonate at the middle of the FM band, but will be broad enough in its response to be useful over the entire band. -30-

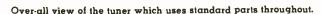Under chassis view. Disc ceramics are used to conserve space.



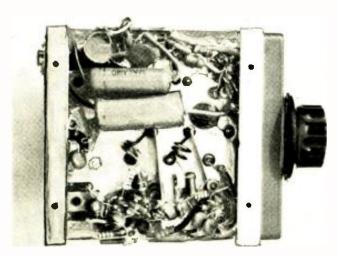

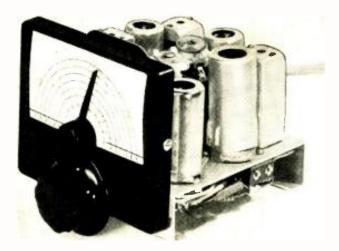

RADIO & TELEVISION NEWS



NEW professional tape recorder, designed to meet the specialized requirements of broadcast and recording studio engineers as well as the advanced audiophile, has recently made its appearance.

Since the keynote of the design was dependability and freedom from maintenance problems, all clutches, belts, pulleys, idlers, and similar components have been eliminated in the construction of this recorder.

To achieve the requisite simplicity, the two reels had to be mounted directly on the capacitor start-and-run induction torque motors which were designed to perform the spooling operations with maximum efficiency. In addition, the tape drive capstan had to be constructed as an integral part of the synchronous drive, with no decoupling to introduce errors of timing or motion.

The main panel, upon which all mechanical components are assembled, was designed for pressure die casting in aeronautical aluminum alloy to combine rigidity, stability, dimensional accuracy, smooth finish, and high impact strength.

The recorder's "Unisync" drive is an innovation in the field of tape metering accuracy. This combination of drive capstan, two-speed (600 and 1200 rpm) hysteresis synchronous motor, flywheel, and cooling blower is engineered as a single integrated unit. The capstan is the exposed end of a precision-ground shaft supported in linebored, self-lubricated bearings mounted in a flanged aluminum mounting sleeve.

On the outside of this bearing mount is fixed the field structure (stator) of the motor. The nickel cobalt hysteresis rotor ring is shrunk-fit into a diecast housing designed for maximum flywheel effect and ribbed to act as a blower. Because the diameter of the rotor is outside the field, efficiency is high and an extremely cool running

Technical details on a recently-introduced professional unit that eliminates clutches, pulleys, idlers, belts, etc.

mechanism results. The entire rotor construction is dynamically balanced as a unit and mounted solidly to the main panel by four bolts.

Each reel-moving assembly is mounted directly on the motor and contains a 3-inch diameter steel brake drum. A brake arm, pressure die-cast of Zamak III alloy, brings a thick white long-staple felt pad against the drum. Both brakes are actuated by a common tension spring, with differential to keep the tape taut in braking established by the self-energizing action of the brakes. Wear of the pads increases clearance and does not require readjustment.

The tape is stripped from the reels over ball-bearing metal rollers with the tension arms concentrically pivoted to bear against the back of the tape. A *Microswitch*, mounted behind the panel, serves as a power cut off switch in the event of tape run-out or failure. The tension arms swing to a lock position for straight-line loading of the tape through the head assembly, then unlock to provide filter action.


The transducers, or heads, are mounted on a precision pressure diecast ribbed mount which has provision for positioning and adjusting five heads with accurate guides for locating the tape's course through the assembly. The mount is fastened to the main panel by three clamp screws. Electrical connection to the heads is by means of individual slip connectors. The added flexibility offered by the provision for two additional heads can be indicated by a few examples. An extra playback before the usual combination of crase, record, and playback heads permits the simultaneous playing of a delayed broadcast while erasing the tape and recording an incoming

signal—thus permitting one recorder to do the work of two. Or, a combination of single- and dual-track erase and record heads gives a choice of dual-track recording for library requirements or single-track master recording with instant switch selection. Other possible combinations provide a choice of single track or stereo-binaural recording and use of multiple playback heads for echo and reverberation effects.

Tape contact with the heads is accomplished by a pressure die-cast Zamak shield mount that wraps the tape into an arc contact with the pole faces of the heads. A hum shield is mounted in close contact on the head shield of the playback heads. The shields are held in place by tapered spiral coil springs and snap lock retainer clips. No pressure pads are used in normal audio work. In fastforward and rewind position the tape clears the heads, close enough for audible location of selections, but without contact to cause excessive wear. Movement of this mount is automatically controlled by the operation of the control levers.

All controls for the drive mechanism are included in one coaxial lever system located in the center of the panel. The tape drive lever moves to the right for "Run." This closes the head pressure mechanism, wrapping the tape into contact with the heads. Moving the lever to the left from "Stop" to "Cue" also wraps the tape around the heads but does not close the pressure roller against the capstan. Since the brakes are released and the spooling motors powered, the reels may be freely rotated to locate any desired point for cueing or editing. Swinging

(Continued on page 132)

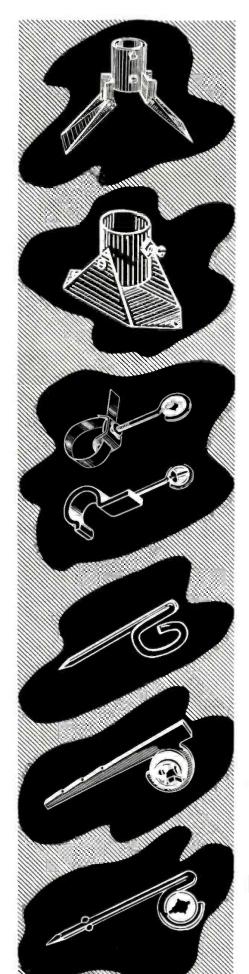

HOW GOOD ARE YOUR

A PROFESSIONAL well-planned antenna installation is important not only for the sake of satisfying your customers and providing the best possible reception—it is also the criterion by which prospective customers and fellow service technicians (possibly future employers) judge your competence.

You should be familiar with the points of good installation practice described in this article if you are furnishing good installations. If not, this review should prove helpful.

1. Anchor the mast properly. Don't use haphazard mounting straps or clamps which rust or stretch. Use pipe clamps or bracket mounts if the antenna mast is to be installed on a wood, stone, or brick wall, or mounted on one side of the house. Use special chimney straps if the chimney is to be used for support.

2. Use guy wires. These are important from the standpoint of safety and rigidity. Storms is New York and other TV areas have shown the importance of proper guying. Use guywires in all cases where the mast extends more than 5 to 8 feet above the chimney or other support. Three guywires are recommended for masts 10 to 15 high; six for masts 15 to 25 feet high, and nine or more guys for greater heights.

Where high winds are encountered, it is best to use a self-supporting or guyed tower instead of the usual hollow mast. The cost is greater but the investment will guarantee your customer far greater protection against collapse and possible damage during storms or high winds.

For the guy wires, use No. 6 or No. 8 stranded steel wires (or solid galvanized clothesline). Break the wires at odd lengths and insert strain insulators to prevent reflections or interaction with the antenna. (If serious ghosts result from some odd combination of guy lengths, try the small plastic-covered clothesline for guying.

This particular type is waterproof, will give in high winds without undue stretching, and is sufficiently strong for most 10- to 15-foot masts.)

3. Use solid anchor points for the guy wires. Ordinary screw-type anchors with a hook or eye in one end are satisfactory if the wood beams, rafters, etc. are solid. For anchoring to brick or concrete walls, use wing-type bolts or special expansion plugs. Space the anchors evenly around the mast if possible (about 120 degrees apart) so the mast will have equal support from all directions. Make sure the anchors are bolted or screwed securely to the supporting surfaces.

The Down Lead

4. Use ring lugs. These lugs clamp on to the lead-in for connecting to the antenna terminals. They insure good electrical contact and take some of the strain off the leads. Wrapping the bared wires around the antenna terminal screws may cause a weak signal later when the terminals become loose or the wires corrode and cause poor contact.

5. Secure the lead-in. Whether the transmission line is twin-lead or coaxial, use a stand-off insulator every 4 feet or so to keep the lead-in taut and to prevent its swaying in the wind. Crimp the outer ring of the insulator just enough to provide firm, positive contact. Excessive pressure does not improve the grip and may result in damage to the wire or insulation. Allow enough slack between the antenna and the first stand-off insulator to allow for wind movement or for the full rotation of the electric rotator if one is used.

Rotator control wires should be run at least 2 or 3 feet away from unshielded twin-lead, all the way to the receiver. Ghosts or a smeared picture will result if these wires are too close together. The same applies if more than one lead-in line is used.

Note: It is not necessary to mount the rotator control wires on insulators. Insulated staples are satisfactory as long as the wires are not damaged nor the insulation punctured.

6. Keep twin-lead away from metal. Drain pipes, down-spouts, roof flashing, gutters, sheeting, vent pipes, metal conduit, electrical or telephone wiring, etc. will greatly attenuate the signal and may introduce serious reflections. Protect the line at roof edges with stand-off insulators, leaving just enough slack to keep the line from rubbing against the roof or other objects. Do not tape unshielded lead-in to the mast or other metal object, and avoid running it near or inside conduit. A wet lead-in touching or taped to a grounded water pipe will amount

RADIO & TELEVISION NEWS

TV INSTALLATIONS?

By JOHN B. LEDBETTER

Are your TV antenna installations getting sloppy? Check the methods you are now using against this brief review of good TV installation procedures.

almost to a short-circuit of the signal, especially at the higher frequencies.

7. Protect twin-lead from the weather. Don't run twin-lead for long lengths horizontally if you can help it. This can spoil reception in rainy or winter weather by allowing rain, snow, or ice to collect on a large part of the lead-in. Run the wire under the caves or straight down as much as possible so that a minimum area will be exposed to the elements.

Note: Where the antenna mast is mounted on an unused chimney, run the lead-in down through the inside. This will provide the shortest possible run and give best weather protection. Use stand-off insulators on the chimney to relieve strain on the line. Run the lead-in into the basement and bring it up through the floor to the receive; or bring the lead-in out through the fireplace if this is more convenient.

If the chimney is active, run the lead-in down the outside as usual and install a metal baffle plate on the chimney to keep soot from collecting on the antenna terminals and insulator. A heavy collection of soot will short-circuit the antenna insulator in damp or rainy weather. See a tinsmith, furnace dealer, or hardware store for the baffle.

8. Use a good ground. For adequate protection against lightning and electrical storms, run a ground wire from the antenna mast to a cold-water pipe or a 3-foot rod driven into the ground. No. 14 copper wire is adequate in most cases, but No. 6 is recommended for tall masts or where exceptionally long lengths of ground lead are used. Be sure the connections at all points are clean and tight. The ground wire can be stapled to one corner of the house and painted.

9. Use a lightning arrestor with twin-lead. Electrical codes in most cities require an approved-type lightning arrestor with twin-lead (none is required with coaxial lead-in if the shield is properly grounded). Connect the arrestor at the point where the lead-in enters the house, and be sure its ground strap or terminal is connected firmly to the regular ground wire. If the lead-in is run inside the chimney, install the arrestor at the closest convenient point to the receiver and run a No. 14 wire to the nearest cold-water pipe, gas pipe, electrical conduit (if properly grounded), or to

an outside ground. If more than one lead-in is used, install a separate arrestor for each line. Always clamp or bolt the ground rod connections, never solder. Avoid using fire escapes, vent pipes, or similar metal objects for grounds. These usually are painted or rusty and make very poor grounds.

10. Check reception before securing lead-in permanently. With the lead-in temporarily connected to the receiver and antenna, check for ghosts, interference, and picture quality. Ghosts may be caused by reflections from a metal roof, large metal pipes, hidden electrical wiring, etc. Passing automobiles, trolley buses, or electrical equipment in the neighborhood may introduce serious interference. If the picture is good, install the lead-in permanently.

11. Check the antenna's safety features. Be sure it is rigidly mounted and that all precautions have been taken to prevent its damaging the roof or falling across electric power lines. If electric lines pass overhead, it is better to reroute the lead-in to avoid possible contact in case one of the power lines should break and fall.

Note: When installing or adjusting the antenna, do not use a metal ladder if power lines of any sort are near. Accidental contact with a metal ladder usually is fatal! Use a dry, wooden ladder to be safe.


Special Considerations

12. Installing on flat roofs, sun porches, etc. If you do not use a regular commercial base mount be sure the mounting base is strong enough to keep the bottom end of the mast from twisting during high winds or rainstorms. Use a block of wood under the mast to prevent damage to the roof. If mounting holes have to be made in the roof, cover these with pitch or caulking compound to keep out rain and snow. Do the same to all mounting-screw heads and around the mounting base edges.

13. Mounting on slate roofs. A chimney mount is the most practical in this case, If you must walk on the slate to reach the chimney, use a wooden ladder as a catwalk to prevent damaging the roof.

Although all the preceding points are essential to every antenna installation, it is surprising how many are neglected—or forgotten. Can your installations pass the test?

—30—

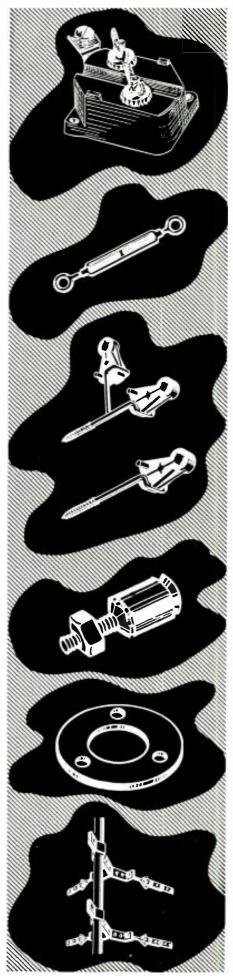



The cabinet to house the speaker or speakers of your choice must be selected carefully if maximum pleasure is to be derived from your high-fidelity equipment.

AST month the author discussed the criteria involved in the selection of speakers for high-fidelity audio systems ("Choosing Your Hi-Fi Loudspeaker"). We will now consider the important factors governing the choice of suitable speaker enclosures.

It is probable that there is just as much uncertainty in the minds of laymen regarding the selection of an enclosure as there is in choosing a loud-speaker. The choice of a speaker often dictates the type of enclosure, and, conversely, the type of enclosure needed will often limit the type of speaker which can be accommodated.

Having examined the various types of speakers in last month's article, we can now consider what types of cabinets can be used with specific speakers. There are two general types of cabinets. Like speakers, they are the direct-radiator type and the horn type. These types are depicted functionally in Fig. 1. The direct-radiator category includes bass-reflex cabinets and all the variations of this basic design. It is, essentially, a resonant device and usually has to be tuned to the particular speaker with which it is to be used. The horn type of cabinet is anti-resonant and, while it does not need to be tuned, it does have to provide the proper loading on the speaker diaphragm by proportioning the expansion of the horn and its throat area and rear chamber to the particular speaker to be used.

A good horn-type cabinet is more difficult to design and build than a


direct-radiator type. This is just one reason for the ready acceptance of the bass-reflex type-its simplicity and economy. The principal reason for its popularity, however, is the compatibility of this type of cabinet with any type of speaker or combination of speakers. As the name "direct radiator" implies, the speaker, mounted in the cabinet, looks directly out at its audience. This is important if one is planning an integrated twoor three-way speaker unit. When such a speaker is mounted in the cabinet. there is no obstruction between the tweeter and the ear, as pointed out last month. Life is almost as simple when using a bass-reflex cabinet for a twoor three-way system composed of separate units. The woofer can be mounted in the cut-out provided for it and the tweeter may be mounted wherever convenient by providing the proper opening for it on top of the cabinet.

A true horn-type cabinet, suitable for the living room, does not lend itself to a coaxial type speaker. In the construction of the horn it is usually necessary to fold it up at least once in order to squeeze it into a reasonable physical volume. The throat of the horn usually gets tucked away within the cabinetry and out of direct line with the ear, as can be seen from Fig. 1B. If the coaxial type of speaker is mounted at the throat of the horn, the tweeter would be forced to radiate into the base of the horn and all of its crispness and clarity is sacrificed. For this reason the tweeter must radiate in an unobstructed path to the ear.

If one wishes to use the horn-type of enclosure, it would be necessary to select separate, independent, and matched loudspeaker units, as shown in Fig. 2. If you want a single integrated unit, then you must stick with the direct-radiator type of cabinet.

Forgetting the matter of being able to select the specific components of a three-way system as against accepting the integrated package deal, is there any other advantage of one system

Fig. 1. Two methods of mounting a speaker within a "box" to give the effect of a direct radiator or a compression-type horn-loaded system. See text for advantages of each.

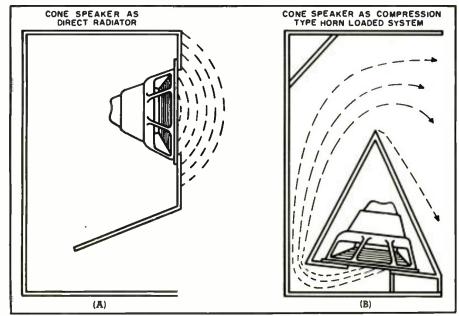

RADIO & TELEVISION NEWS

over the other? The answer is "yes." There is a psycho-acoustical advantage to a three-way system made up of separate units-it is possible to achieve greater spatial effects which tend to give added realism to the music. If a triaxial speaker is used in a directradiator cabinet, as in Fig. 1A, the sound source of all three speakers would then radiate from a single point. In the case of the threeway horn system, the sources of sound are separated by the differences in the lengths of the horns involved so that there is a feeling of physical separation. Moreover, the speakers are separated by the width of the cabinet. adding further to the illusion of acoustic depth.

There are horn variations on the direct-radiator baffle theme and, likewise, there are direct-radiator variations on the horn theme-and there is a large area of overlap between the two. One excellent version of a bassreflex cabinet (Fig. 1A) has its port horn loaded which means that radiation from the port is given an additional boost by coupling to the horn. This enables it to radiate more efficiently.

In addition, there are totally "rearof-speaker" horn-loaded cabinets in which the back of the speaker looks into a folded horn but the front of the speaker looks directly into the listening area. Such a cabinet is compatible with any combination of loudspeaker components.

With the horn family of cabinets there are several subdivisions which must be understood in order to facilitate the intelligent selection of components. The prevalent horn design is one that uses the corner of the room as a part of the horn, as an extension of the horn, if you will. Some of these models use the actual walls of the room to complete the horn while other corner models have their own integral side walls and do not depend upon the room walls. In some instances the corner in which you wish to place the cabinet may have heavy, absorbent drapes or other acoustical treatment which will deteriorate the action of the horn. In this case, the corner enclosure is made independent of the roomcorner acoustics by building into it its own "corner wall." Such a complete horn, independent of the room walls, is shown in Fig. 2, along with the

matched components designed to be used with it.

Another version of the corner-type cabinet has been dubbed the "cornerless corner horn" because it is shaped in such a way that it will fit into a corner or can be placed against a flat wall. These cabinets are made in both the horn-loaded and direct-radiator types.

The size of the enclosure selected will, of course, be governed by the speaker or speakers to be used in it. It will be found that the speaker cabinets now on the market are adaptable to a wide range of component sizes. There are midget enclosures for 8" speakers, medium sized cabinets to house 12" speakers, and extended sizes for larger installations—all of which are available in either direct-radiator or horn varieties. Selection of the cabinet will be rather straightforward if we keep in mind that, generally speaking, the larger the components, the better the low-frequency response and the more speaker components, the cleaner the system. Choose your acceptable cabinet size and choose your system for it-unitized into parts or integrated into one—and your choice will automatically be narrowed to one or two cabinets.

Now that the speakers are in the cabinet of your choice, there is one last detail in the auditory chain that should be covered—the listening room itself. The best spot for a loudspeaker enclosure is the corner of the room. The corner tends to reinforce the action of the cabinet just as an orchestral shell reinforces the sound from an orchestra. Even a rectangular cabi-

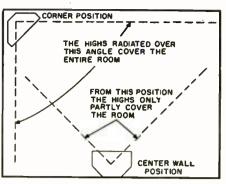


Fig. 3. Corner placement of an enclosure gives better low-frequency reproduction because the corner acts as a horn coupled to the speaker. A corner also provides better high-frequency coverage since the tweeter in this position "sees" all parts of room.

net may have its performance improved when placed in a corner. Not only will the low frequencies be greatly enhanced but the high frequencies will cover more floor area of the room when projected from a corner than when emanating from a cabinet placed against a flat wall. Fig. 3.

The room insulation will greatly affect the quality of the reproduced sound. A room without any absorptive surfaces will make the reproduction too reverberant and destroy the crispness and separation of the various notes. The lower notes will continue to roll around the room long after they have issued from the speaker and will tend to mask the following notes. In a completely untreated room, standing waves may be set up at certain frequencies, giving "hot spots" of energy (Continued on page 120)

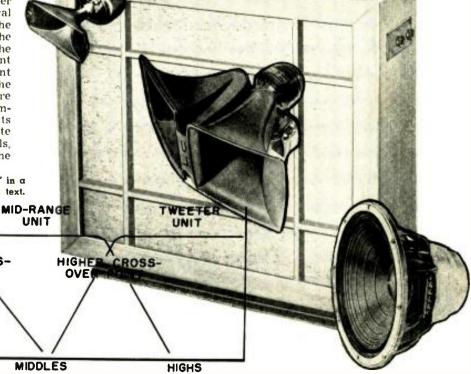


Fig. 2. Matched speakers are a "must" in a horn-type of enclosure, as explained in text.

LOWER CROSS-OVER POINT

WOOFER

UNIT

LOWS December, 1954

47

FOR 12" SYSTEMS Part 2. Performance of some popular high-fidelity loudspeakers in the "Fold-a-flex" enclosure and a By OLIVER READ Editor and Asst. Publisher RADIO & TELEVISION NEWS

• HE enclosure for loudspeakers has a definite effect upon the reproduction that can be obtained from various systems. The damping effect on a moving cone of a loudspeaker has a direct control over the impedance characteristics of the voice coil. The amount of damping required will depend upon the behavior of a given loudspeaker mounted in its enclosure. The loading effect produced by a particular enclosure design can and does act as an acoustical brake to the piston-like excursion of a cone in the low frequency range. Horn type enclosures provide this loading advantage.

These are but two of the factors influencing the behavior of a loud-speaker. The leading manufacturers

of hi-fi speakers have recognized the importance of the enclosure and have designed cabinets to meet the requirements of their own loudspeakers. Such compatibility has resulted in some very fine systems and has greatly simplified the problem of choice for the consumer.

The audio enthusiast, technician, and the serious student, to a great extent, like to build their own enclosures and to study the behavior of several loud-speakers before deciding which is best for their listening pleasure. The all-purpose enclosure, described last month, was a direct result of this search for a "guinea pig" cabinet that could meet the demands for checking the performance of any loudspeaker contained in but one assembly—but

having the essential characteristics of the most popular enclosures: folded horn, infinite baffle, and bass reflex. The "Fold-a-flex" loudspeaker enclosure was the result. A single cabinet instead of three provided the necessary housing for the experiments.

Frequency response measurements were made under "free field" conditions in an outdoor area free from reflective surfaces. The setup included two calibrated microphones; a dynamic (E-V 655) and a crystal (Shure 98-99). The low impedance 655 was coupled through a high-quality broadcast transformer to match the 1 megohm input of the a.c. vacuum-tube voltmeter. Because the 98-99 crystal is designed to feed a load of at least 20 megohms it is necessary to use either a correction factor or to modify the circuitry. We chose the latter so that direct readings would result in plotting the curves. The 98-99 microphone has an internal capacitance of 1000 µµfd. and the cable adds another 200 µµfd. The total then becomes 1200 µµfd. The microphone acts as a Thevenin generator with a constant voltage proportional to the sound pressure and a capacitance of 1200 ##fd. connected in series.


Our trusty Shure "Reactance Slide Rule" shows that a 1 megohm load is equal to the capacitive reactance of 1200 $\mu\mu$ fd. at 130 cycles. The response of the v.t.v.m. will then be down 3 db at 130 cycles and will continue dropping at the rate of 6 db per octave below 130 cycles. Measurements were wanted down to 30 cycles. It was necessary then to connect a capacitor of 3000 $\mu\mu$ fd. across the microphone. This causes a 10 db drop in the output of the microphone but it has the advantage of eliminating a correction factor. The result is an essentially flat output down to 30 cycles.

Spacing between the microphone and the front of the enclosure was maintained at 36 inches. A *Heath* audio generator (calibrated against a *Hewlett Packard* 200 C) was used as the signal source feeding a *Fisher* 70A amplifier to drive the test speakers.

The response curves, Figs. 2 to 4,

Fig. 1. Five distinct speaker combinations are switch-selected for demonstration purposes or for the study of loudspeaker behavior under various conditions.

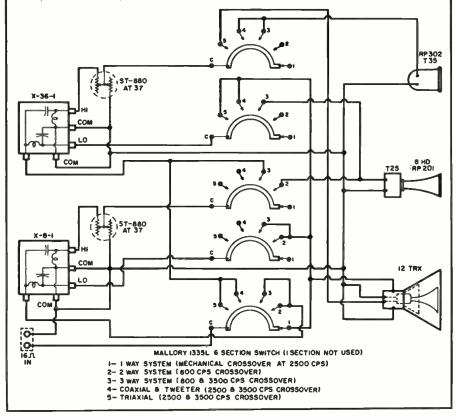description of a new, unique comparator technique.



Pats, Pending.

show the effect of enclosure characteristics. The advantages of a tunable bass reflex port are clearly shown in the curves. The hump (at 150 cycles) results from cabinet resonance produced by an infinite baffle. Tuning the port results in a reduction of the hump and produces two equal humps of lower amplitude which is exactly the effect wanted. The difference can be easily distinguished when heard in the living room. Measurements made in a typical living room all show considerable improvement in bass response. When the enclosure is used as a folded horn, either on a flat wall or in a corner, even greater extension of the bass range is enjoyed.

Another innovation was made to permit demonstration of the "Fold-aflex" at the New York Audio Fair in October. Many of our readers will remember the remote control system devised to show the wide difference in the performance of single and multiple loudspeakers under different conditions of baffling.

The circuit, Fig. 1, is designed for manual switch selection and is self-contained. Relays were substituted in our demo unit so that each function could be selected from across the room. The following components make up the system: A 12" triaxial loudspeaker with electrically independent tweeter, a mid-range horn, a small tweeter, a crossover network (800 cycles) and another at 3500 cycles. The two networks should have a common built-in connection between input and output. The switch is a 6-section (1 not used), 5-position rotary type.

Our demo unit contained an *Electro-Voice* 12TRX triaxial, a T25 driver, and 8HD horn and the *Jensen* RP302. The crossover networks are *E-V* X-8-1 and X-36-1. Level controls permit setting the mid-range horn and the tweeter to best balanced listening. The following are the functions available as selected by the switch:

Position (1): 1-way wide-range system. Here, the audio feeds directly to the voice coil of the 12" duo-cone. Its built-in mechanical crossover at 2500 cycles affords extended single cone coverage.

Position (2): A 2-way system. This shows the effect of adding a high-frequency horn to existing 1-way systems. Audio feeds to the 800-cycle network and utilizes the 12" cone as the woofer (800 cycles and below) and the horn for 800 cycles to the h.f. limits of the horn.

Position (3): A 3-way system comprising low frequency woofer, midrange horn (800-3500 cycles) and u.h.f. tweeter (3500-15,000 cycles).

Position (4): Coaxial (2500-cycle mechanical crossover) and tweeter (3500 cycles). This demonstrates the effect of adding a tweeter to existing coaxial speaker systems.

Position (5): Triaxial. Showing the advantages of single point-source (Continued on page 157)

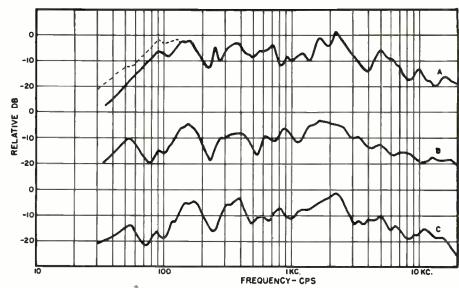


Fig. 2. Response curves of the Stephens 103LX, 216, and 814H two-way system in the original "Fold-a-flex" for 15" speakers described in 1953. (A) Folded horn. Dotted trace is for corner mounted enclosure. (B) Infinite baffle. (C) Bass reflex. Humps at 150 and 300-400 cycles have equal response as a result of tuning reflex port.



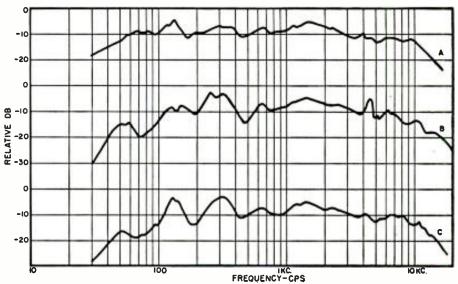


Fig. 3. Improved damping and horn shape of the Model 12 enclosure is reflected in these curves of the Electro-Voice 111 two-way system for 12" low-frequency driver and high-frequency horn. (A) Folded horn. (B) Infinite baffle. (C) Bass reflex.

Fig. 4. Response of the Jensen "Tri-Plex" system in the original enclosure. Dotted trace shows effect of corner mounting in a well-draped living room. (A) Folded horn. (B) Infinite baffle. (C) Bass reflex. See author's discussion in article.

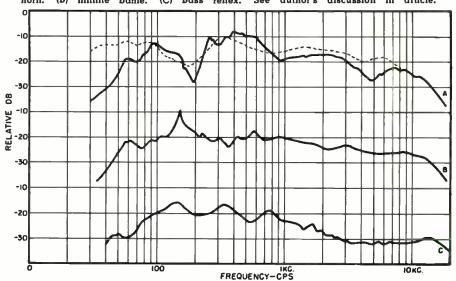

A SEMI-AUTOMATIC TUBE CHECKER

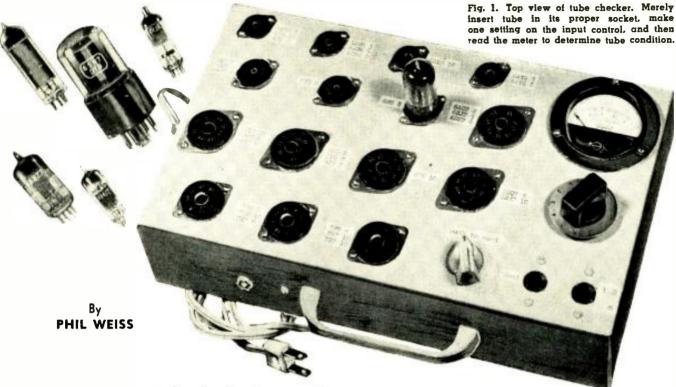

Here's an extra tube checker for your home service calls that is easy to build and easier to operate.

T IS a good idea for a TV service technician to check all the amplifier tubes in every set with a tube checker. From the customer's viewpoint, the set will give better performance if all the weak tubes are replaced, and it is usually cheaper to replace a weak tube than to wait until it goes out and have to pay an additional service charge. From the service technician's viewpoint there are many advantages:

1. It is faster and surer to spot some

- kinds of tube defects with a tube checker, than by substitutionespecially when more than one tube is bad.
- The number of callbacks is greatly reduced when all weak tubes are replaced.
- 3. Many more tubes are sold, espe cially in older sets.
- The tube checker has great prestige value in the eyes of the customer.

Fig. 2, Schematic

diagram of the

tube checker, Labeled points re-


fer to Table 1.

Some important disadvantages to using a tube checker in the home are that many tube defects cannot be found with a tube checker, such as high voltage breakdown; it takes a long time to look up each tube in a chart, and to manipulate all the switches; it is expensive to provide each service technician with a tube checker; and commercial tube checkers are easily damaged when constantly carried about. Also the switches give trouble when used constantly.

The tube checker described in this article and shown in Fig. 1, was built to minimize these disadvantages. It does not attempt to check all tube types, but only about 100 of the most common tubes found in TV sets. This list can be enlarged or reduced, according to the individual preference of the constructor. The list does not include any of the power tubes, such as 6BG6 or 6W4, since the condition of these tubes is usually apparent from observing the performance of the TV set.

Each tube type goes into a socket according to its pin connections. For example: all 7-pin pentodes like the 6AG5 go into one socket, all 9-pin triodes like the 12AU7 into one socket, and so on. There are 15 sockets in all. They are wired in parallel by wires, so that when any tube is plugged into its proper socket it operates under the correct conditions for that type. An a.c. signal, adjustable from 0 to 10 units, is fed into the grid of the tube under test, and the a.c. output of the plate is read on a meter. The instru-

(Continued on page 114)

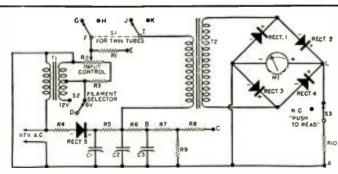

r-25X or equiv.

[.- Interstage trans., 1:3 ratio (Triad A-31X or equiv.)

Rect. 1, Rect. 2, Rect. 3, Rect. 1-Full-wave bridge instrument rectifier (Conant Type M of equiv.)

Rect. s-100 ma. selenium rect. (Federal 1004)

SI-D.p.d.t. slide switch S:-D.p.s.t. slide switch

S.-S.p.d.t. spring-return, normally closed, 10-tary switch (Centralab 1463)

 R_{10} —5 ohm, 1 w. rcs. C₁. C₂. C₅—20/20/20 µfd., 150 v. clec. ca-T1-Fil. trans., 12.6 v. c.t. @ 1.5 amps. (Triad

Ri--> megolim, 1/2 w. re:

Rs, Rs-50 ohm, 1 w. res. R₄-22 ohm, 1 w. res. R₅-200 ohm, 2 w. res.

R=-150 ohm, 2 w. res.

R6-2000 ohm, 5 w. res. R7-4000 ohm, 10 w. wirewound res.

Ri-8 ohm pot

M1-0.1 ma. d.c. milliammeter




SINGLE-SIDEBAND transmission needs a series of new gadgets to test SSB exciters. The following is an oscillator to use in place of the microphone. This makes a convenient way to tune up—just throw the switch and you have a tone with which you can monitor the transmitter on the oscilloscope. This oscillator is especially useful when used with the 10A or 20A SSB exciter and does not tie up any of your regular test equipment. It can also be used with any SSB exciter having a commercial 90 degree phase shift network.

Fig. 2 is the response of the average commercial 90 degree phase shift network used in an SSB exciter for a band of frequencies 200 cycles to 3000 cycles. It is possible to have one point in that range exactly 90 degrees. This point falls about 1225 cycles and can be used for alignment purposes. Some networks may be up or down a bit.

Fig. 1 is a Franklin oscillator with three fixed frequencies of 1200, 1225, and 1250 cycles which would cover any network which might be off slightly. It is necessary that the oscillator have low output, not over .075 volt r.m.s, to properly balance the SSB exciter and avoid distortion. Another reason for this small auxiliary oscillator is that the regular oscillators with a dial are hard to set exactly on 1225 cps because they are not calibrated this close. It is also hard to find the same dial setting each time you want to tune up.

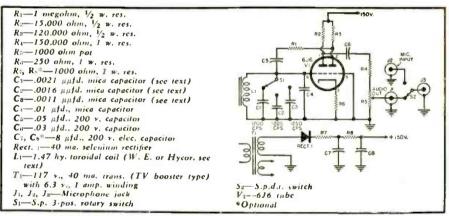
The values given in the schematic were measured on a GR bridge and if followed will give the previously-mentioned frequencies exactly as measured on a Berkeley counter. Paralleling small silver mica capacitors to obtain this value will be close enough to (Continued on page 116)




degree phase-shift networks.

Fig. 1. Complete schematic and parts list covering the SSB audio test oscillator.

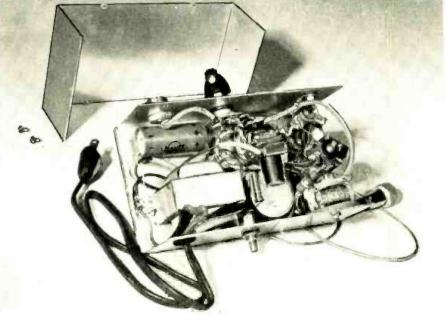Under chassis view. The toroid is visible at far right, mounted on chassis lip.



December, 1954

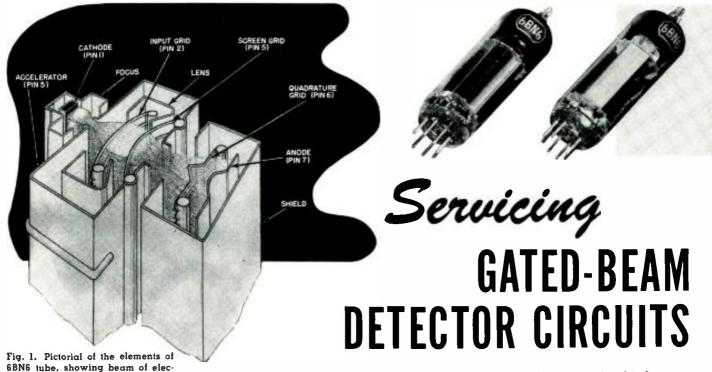

trons going from cathode to anode through the various grids of tube.

By MATTHEW MANDL

Details on the operation of the 6BN6 limiter-detector which is now being used in many present-day TV receivers.

*HE 6BN6 gated-beam FM detector is being used with increasing regularity in modern television receivers as well as FM sets. This unique tube is a combined limiter and frequency modulation detector and at the same time requires much less signal input than the conventional discriminator or ratio detector type of FM demodulator. Thus, only one i.f. stage is required preceding the detector instead of the usual two or three, and the stage of audio voltage amplification can be dispensed with since the output from the gatedbeam detector is sufficient in amplitude to drive the audio output amplifier tube.

The 6BN6 gated-beam tube has an internal construction which concentrates the electron beam into a narrow stream. As shown in Figs. 1 and 2, the major elements which are brought to the tube base consist of the anode, pin number 7; the quadrature electrode, pin number 6; the accelerator grid, pin number 5; the input grid, pin number 2; plus the cathode, pin number 1, as well as the usual heater terminals.

The tube is so constructed that if either the input or quadrature grid has a fixed potential, plate current will not increase beyond a certain value, no matter how positive the other grid is made. If either grid is negative enough, plate current will be cut off, regardless of the potential on the other grid. Plate current cannot flow unless both grids are above cut-off, and a variation in plate current with grid potential is limited in both directions, particularly in the case of the input grid.

The quadrature grid (pin 6) incorporates a resonant circuit tuned to the i.f. frequency. This quadrature grid is coupled to the input grid via the space charge within the tube. When electrons approach the quadrature grid, they repel electrons in the grid wires. Thus, by electrostatic induction, energy is coupled to the resonant quadrature circuit. Such induced energy, however, must reach a maximum value before the interchange of energy can occur between the condenser and inductor of the resonant circuit (flywheel effect). Hence, a 90-degree phase difference exists between the signal voltage at the input grid with respect to the quadrature grid voltage. The potentials which exist at the input grid and the quadrature grid are shown in Fig. 3A.

The 90-degree phase difference between the two signals permits the tube to conduct only during the time when both signals are above the zero reference line as shown. Thus, the average tube conduction is a fixed value when the signal which is applied to the gatedbeam tube is an unmodulated carrier (the i.f. frequency of 4.5 megacycles in intercarrier receivers). With normal operating bias, an input signal of approximately one volt or more causes plate current to reach saturation immediately and the tube conduction interval shown in Fig. 3A occurs. Thus, a square wave of beam current is generated and the input grid of the tube acts as a limiter, since an increase in signal amplitude, as represented by static, does not cause an increase in plate current flow.

When the incoming signal is frequency modulated, the change of input frequency causes a phase displacement between the voltage at the quadrature grid with respect to that at the limiter grid. This comes about because the quadrature resonant circuit is still tuned to the center frequency and for a shift of the applied frequency the inductive reactance of the coil no longer equals the capacitive reactance of the condenser. The voltage at the quadrature grid will, therefore, assume a different phase relationship with respect to the signal at the input grid. This is shown in Figs. 3B and 3C. Thus, if the i.f. carrier shifts to a lower frequency, the inductive reactance of the resonant circuit becomes less than the capacitive reactance. When the inductive reactance is lower than the capacitive reactance, the circuit is predominately inductive since this component has a greater shunting effect on the signal. Voltage leads in an inductive circuit and, thus, the quadrature grid voltage becomes less than 90 degrees out-of-phase with respect to the input grid voltage. This is shown in Fig. 3B, and the result is that tube conduction is increased in duration.

When the carrier frequency shifts higher, the resonant circuit becomes predominately capacitive (lower capacitive reactance). Since voltage lags in a capacitive circuit, the quadrature grid potential is caused to lag more than the 90 degrees, as shown in Fig. 3C. Thus the duration of plate current flow decreases.

Since the i.f. carrier signal deviates in frequency each side of the 4.5 megacycle center frequency during frequency modulation, the audio signal appears in the anode circuit as a variation of average plate current. The plate load resistor (the volume control) of Fig. 2, plus the shunting .001 µfd. con-

denser, form an integrating network which averages out the amplitudes of the square waves of current and thus produces the audio signal voltage variations. The condenser, in effect, holds its charge between successive valleys of the square waves.

The 470-ohm resistor in the anode circuit is for feedback purposes. The voltage drop developed across this is coupled *via* interelectrode capacities to the quadrature circuit to improve the linearity of the detection system.

The variable cathode resistor regulates the amount of bias applied to the limiter grid (about 3 volts). Since this potentiometer is also adjusted to minimize intercarrier buzz as well as set the extent of limiting, it is usually designated as the "buzz control" in television receiver schematics. The "buzz control" is regulated so that the bias permits operation on the best portion of the characteristic curve of the tube. The signal to the limiter grid may reach amplitudes up to 5 or 10 volts which normally would mean a considerable grid current flow. This is held to a minimum, however, by tube design so that the input circuit would not be damped objectionably.

Typical Circuits

Fig. 2 is the type circuit used in some *Crosley* TV receivers. The coupling transformer between the anode of the 6U8 i.f. amplifier and the limiter grid is tuned to the i.f. frequency (4.5 megacycles in intercarrier TV receivers, and 10.7 megacycles for FM receivers). The quadrature coil is tuned to the same frequency as the sound i.f. stage.

Sometimes a separate resonant input circuit is employed, as shown in Fig. 4, which illustrates the system used in many late Westinghouse receivers. The gated-beam circuit is similar to the one previously discussed except for slight changes in component parts. Here, the output of the first sound i.f. amplifier has a separate resonant circuit which is slug-tuned, and the signal is applied to the limiter grid which has an additional inductance to ground. The service notes for this receiver designate a cathode voltage range from zero to 4 volts, in contrast to the 2.6 volts designated for the Crosley receiver in Fig. 2. There is also a difference with respect to the accelerator grid voltage as well as the anode potential. The Westinghouse service notes indicate 100 volts as normal on pin 5 of the tube in this circuit while *Crosley* suggests 110 volts.

The latter receiver indicates 77 volts at the anode pin 7, while *Westinghouse* shows a range from 35 volts to 200 volts.

Except for such slight variations as cited, most other manufacturers employing the gated-beam tube utilize circuits which, basically, are identical. This is indicated in Fig. 5 which illustrates the 6BN6 stage in some Zenith television receivers. Here a single 6AU6 tube precedes the sound detector and this 6AU6 acts as a sound limiter and thus performs some clipping function as well as amplifying the signal derived from the sound take-off coil. The clipping action assures a greater attenuation of amplitude modulation variations.

Alignment Procedures

Since the gated-beam circuit is rather simple as compared to the discriminator types of detectors which may employ two i.f. stages besides a limiter, alignment procedures are much less complex.

Alignment of the gated-beam circuit can be accomplished by using a transmitted television signal. The signal at the antenna terminals of the receiver should be reduced sufficiently so that limiting action in the gated-beam tube is prevented. At such a level, a pronounced hissing accompanies the sound output. A low ohm resistor can be placed across the antenna terminals to reduce the signal input. Several should be tried until one is found which brings the signal level down sufficiently.

When the limiting action of the gated-beam tube no longer prevails and the hiss is heard, adjustments are made to the sound take-off coil, the transformer between the sound i.f. amplifier and the gated-beam detector, as well as the quadrature coil. The buzz control is also adjusted in conjunction with the slug adjustments of the aforementioned coils, until the cleanest sound is produced with a minimum of buzz. Adjustments should be made until the sound output has good quality with minimum buzz, even though the output level may not be at its maximum for minimum buzz. If the hiss disappears during adjustments of the controls, it may be necessary to reduce the input signal by an additional amount so that the hiss may be heard during adjustments.

In the absence of a station with accompanying sound modulation, a sweep generator may be employed. This generator should be capable of producing

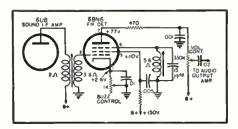


Fig. 2. Schematic diagram of the FM detector circuit used in the Crosley chassis 426. The 6BN6 also serves as limiter.

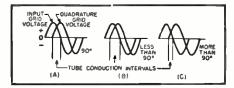


Fig. 3. Current flows through the 6BN6 only when there is a positive bias on both the input and quadrature grids. The length of time that current flows depends on the phase difference between the voltages on the quadrature and input grids.

the necessary 4.5 megacycle signal in frequency modulated form. This can be applied to the input of the video amplifier in lieu of the station signal.

Servicing Factors

If the alignment procedures fail to reduce the intercarrier buzz to a satisfactory level, the 6BN6 tube should be tested or a new one tried. If a new tube does not help, the a.g.c. system of the receiver may require adjustment. If the a.g.c. circuit is functioning properly, the fault may be due to improper tuner tracking or video i.f. alignment. If this has been checked without reducing buzz, the component parts associated with the gated-beam circuit should be checked and compared with the values given in the service notes. Voltages should also be tested and compared with those given.

When parts are replaced, care should be exercised with respect to lead-dress. The leads of new resistors and condensers should be trimmed to the same length as the original components and the units should be placed in approximately the same position as the old parts.

A defective bypass condenser in the cathode circuit of the gated-beam tube will upset the bias on the grid and may increase the intercarrier buzz level. An improper setting will also increase the distortion factor. Distortions will also prevail if the other bypass condensers become defective.

Fig. 4. Sound detector circuit used in Westinghouse TV sets.


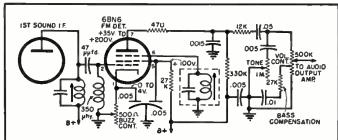


Fig. 5. Sound detector circuit used in Zenith TV receivers.

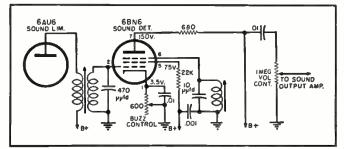

Front panel view of "Globe Scout 65," a bandswitching ham transmitter which is designed for novice ticket holders.





THE "GLOBE SCOUT"

Details on a new transmitter which covers all bands from 10 to 160 meters. Power is 65 watts c.w., 50 watts phone.

HE "Globe Scout 65" transmitter is a general-purpose, 65-watt c.w., 50-watt phone, bandswitching transmitter covering 160 meters through 10 meters and designed for the beginning or experienced amateur or as the "second" transmitter for the higher powered group of hams.

While designed primarily as a fixed transmitter, it has also been used as a mobile unit by amateurs and CAP groups, since it is merely necessary to pull the jumper plug on the back of the chassis and plug in a d.c. power supply. We suggest the use of a 400 volt, 200 ma. d.c. supply.

This transmitter has a 6146 final tube with a 6F6 oscillator using the hot cathode circuit. Complete coverage of 160 through 10 meters is obtained by use of 160-, 80-, and 40-meter crystals. The oscillator stage is easily driven by a small v.f.o. (such as the Lysco model 382). The speech amplifier consists of a 6SJ7 and a 6C5, with a 6L6 as modulator in a combination of Heising and screen-grid modulation which provides ample audio power to fully modulate the final.

A high-impedance microphone input is provided. Metering is done in the final grid and final plate. A pi-network antenna tuner with "L" section is utilized in the output to match most types of antennas. The power supply is self-contained.

All parts are standard with the exception of the coils and bandswitch which may be purchased from the manufacturer.

The oscillator and final coils may also be wound by the builder as follows: Oscillator coil, L_z —72 turns of #28 enameled wire closewound on 1" form with taps at 45 turns and 61 turns. The final coil, L_s , has 82 turns of #22 enameled wire on 1" form with

the first 60 turns closewound, tapped at 30th and 60th turn. Then wind 14 turns on $\frac{3}{4}$ " space with tap at 14th turn, then 4 turns on $\frac{3}{8}$ " space with tap at 4th turn, then another 4 turns on $\frac{3}{8}$ " space.

Circuit Functions

Oscillator: The oscillator circuit was primarily designed for crystal operation, although any v.f.o. with an output of 2 to 5 watts will work equally as well. The stage employs controlled regeneration allowing the

By
LEO I. MEYERSON, WØGFQ
World Radio Laboratories

use of standard 160 to 40 meter crystals and provides more than enough harmonic output to drive the final to full output. Bandswitching is incorporated in this stage and the cathode keying is crisp and clear on all bands. On straight-through operation, the excitation to the final stage may be in excess of requirements; in this instance, the oscillator tuning control must be detuned slightly to reduce the amount of drive to the proper level. The oscillator stage is capacity coupled to the final amplifier.

Rear view of transmitter. This particular unit is commercially available in kit form.



RADIO & TELEVISION NEWS

R.F. Power Amplifier. This stage employs a 6146 tube operated as a class C amplifier. Two types of bias are applied to this stage; one is cathode, or self bias, and the other is excitation bias. The cathode of this stage is keyed as is that of the oscillator. The final operates straight-through on all hands except 10 meters where doubling in this stage does not affect the output to any appreciable extent. Design of the plate circuit in the final stage utilizes bandswitching plus a pi-network. The pi-network allows matching into various antenna impedances.

Speech and Modulator. The speech amplifier circuit is of conventional design, utilizing a 6SJ7 tube. The amplified speech signal is fed into a conventional 6C5 driver stage through the volume control. Latest components such as printed circuit "Couplates" are utilized; these refinements increase efficiency and ease of wiring. Capacity coupling is utilized between the driver stage and a modified Heising-type modulator circuit, Modification of the original Heising circuit consists of heavily modulating the screen of the 6146, as well as the plate. Metering of either the final grid or final plate circuits is provided with a dual scale meter for constant monitoring of circuit operation.

Power Supply. The power supply utilizes a 5U4G tube as the rectifier. The voltage and current supplied are 500 v.d.c. @ 200 ma., which is adequate to power the complete transmitter. An auxiliary socket mounted on the rear of the transmitter provides for external power such as would be required in a mobile installation. Power requirements for mobile operation are 6 v.d.c. @ 4 amps. and 300 to 500 v.d.c. @ 200 ma.

General Information


A two screw terminal strip (labeled "Antenna Relay") on the rear of the chassis, provides a 115 v.a.c. source when the transmit switch is in the "on" position. This provides the necessary voltage for an antenna change-over and receiver disabling relay.

Operation and Loading

A good electrical ground connection to the chassis of the transmitter is essential to efficient operation and proper loading of the final stage. An antenna length of between 60 and 80 feet, at least 15 feet elear of the ground, has been found to be almost ideal for all band operation. A folded dipole type antenna for any band, will match into the pi-section very well, needing no extra matching section.

The extra coax connector labeled "Doublet" is used with doublets on the 80- and 160-meter bands, or with antennas on the higher bands (40-10 meters).

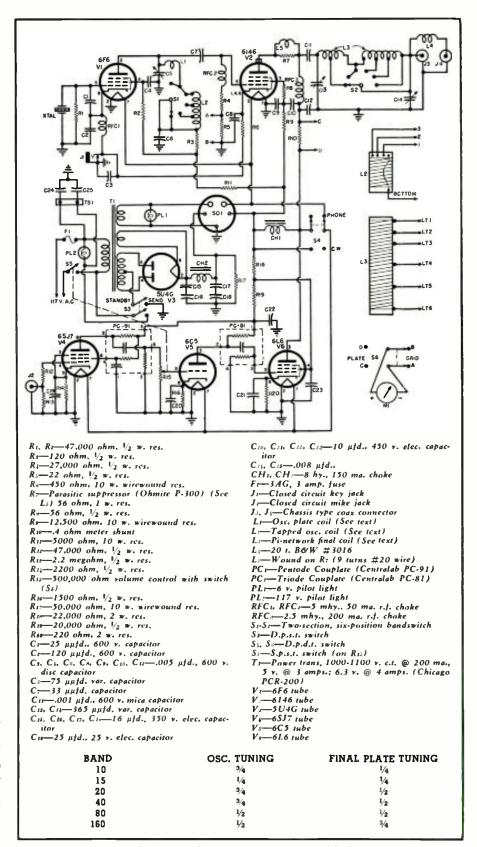Tune up procedure for the pi-section is simple, but care must be exercised so that you do not inadvertently tune to a harmonic of the fundamental signal. The proper tuning point on the final tank is indicated by a sharp,



Complete schematic diagram and parts list covering the "Globe Scout 65". This transmitter is available in kit form or may be built from available components.

clean and low dip in plate current with the plate tuning capacitor approximately half meshed. When attempting to load with the antenna load control, do not operate with the loading capacitor at minimum capacity as this produces excessive reactance and will lead to excessive harmonic radiation. The loading capacitor should load gradually but firmly from maximum capacity, and should show full load at half of its full capacity. Antenna trimming or lengthening is the obvious remedy for any faulty loading conditions.

(Continued on page 113)


1954 TV RECEIVER SPECIFICATIONS

Conclusion of the list of mechanical and electrical specifications on 1954 Television receivers for service technicians.

MFR.	CHASSIS	TUBES							VIDEO 1.F. FREQ. (MC.)	H.V.4 (KV.)	U.H.F. PRO- VISION	POWER (WATTS)	SPECIAL FEA- TURES
		TUNER	I.F.	V1DEO2	AUDIO	SWEEP3	P.S.	CRT	TREO. (MO.)		VISION	(WATTS)	TURES
TRAV-LER (Cont'd)	48A3	6AF4	6CB6	1N64	6AL5	6BQ6, 6C4	1 B 3	17HP4	45.75	14	11	185	10
		6BZ7	6CB6	6AH6	6AU6	6C4, 6S4	5U4	21YP4					
	ļ	6U8	6CB6		6AV6	6SN7, 6SN7							
					6V6	6W 4							
	48C3	6AF4	6CB6	1N64	6ALS	6BL7, 6C4	1 B 3	24CP4A	45.75	16	11	185	10
		6BZ7	6CB6	6AH6	6AU6	6C4, 6CD6	5U4	24TP4					
		6U8	6CB6		6AV6	6SN7, 6SN7							
					6V6	6W4							
WESTINGHOUSE	V2243	6BZ7	6CB6	1N60	6AU6	6ALS, 6AU6	1B3GT	21YP4	45.75	16.5	Strips	225	10, 12,
	V2247	6 X 8	6CB6	or	6BK5	6AX4GT,6BQ6GT	5U4G	21FP4A	45.75	16.5	or	225	Audio
	V2263		6CB6	1N64	6BN6	6SN7GT, 12AT7	5U4G	21YP4	45.75	16.5	11	225	Noise
	V2273			6AU6		12AU7, 12BH7		21YP4	45.75	16.5	11	225	Contr
				12BY7	 								
	V2250	6BQ7A	6CB6	1N60	6AU6	6ALS, 6AS4GT	1 B 3	24CP4A	45.75	18.5	Strips	300	10, 12,
		or	6CB6	or	6BK5	6AU6, 6AX4GT	5U4G	24TP4A			or		Audio
		6BZ7	6CB6	1N64	6BN6	6BL7GT, 6C4	5U4G				11		Noise
Ţ		6 X 8		6AU6		6CD6G, 12AT7							Conti
/ES				12BY7		12AU7, 12AU7							
5	V2260	6BQ7A	6CB6	1N64	6BK5	6ALS, 6AU6	1B3GT	17LP4	45.75	15	Strips	290	
		or	6CB6	6 BK 5	6BN6	6AX4GT, 6BQ6G	5U4G	17VP4			or		
		6BZ7	6CB6			12AU7, 12AU7					11		
		8 X 8		-		12BH7							
	V2270								45.75	15	11	290	
ZENITH	19M20	6BK7A	6CB6	1N64	6AQ5	6AH4GT,6AQ7GT	1B3GT	17LP4	45.75	14	Strips	185	5, 10,
	19M21	8 U 8	6CB6	12AX7*	6AU6	6AX4GT,6BQ6GT	5U4	21YP4			or		12
	19M22		6CB6	12BY7	6BN6	6CS6, 6SN7GT		21YP4			11		
						12AX7*							
	20M20	6ВК7Л	6CB6	1N64	6AU6	6AH4GT,6AQ7GT	1B3GT	21EP4A	45.75	18	Strips	250	5, 10,
		6U8	6CB6	12AX7*	6BK5	6AX4GT, 6CD6	5U4G	21EP4B			or		12, Vide
			6CB6	12BY7	6BN6	6CS6, 6SN7GT	5U4G				11		Amplifi
						12AX7*							Respon
													Contro
	20M21	6BK7A	6CB6	1N64	6AU6	6AQ7GT,6AU5GT		24CP4	45.75	18	Strips	275	5,10,
		6U8	6CB6	12AX7*	6BK5	6AVSGT	5U4G	24CP4A			or		12, Vid
			6CB6	12BY7	6BN6	6CD6, 6CS6	5U4G	27EP4			11		Amplif
						6SN7GT, 6V3A							Respon
				1		12AX7*							1

^{1.} Video i.f. tubes only. 2. Includes detector and a.g.c. 3. Includes sync section and a.f.c. 4. CRT 2nd anode voltage. 5. Removable safety glass. 6. Local-fringe a.g.c. adjustment. 7. High-fidelity sound. 8. Aluminized picture tube. 9. TV-radio-phono combination. 10. Built-in antenna. 11. 82-channel tuner. 12. Adjustable dial light. *Part of tube is used in another section.

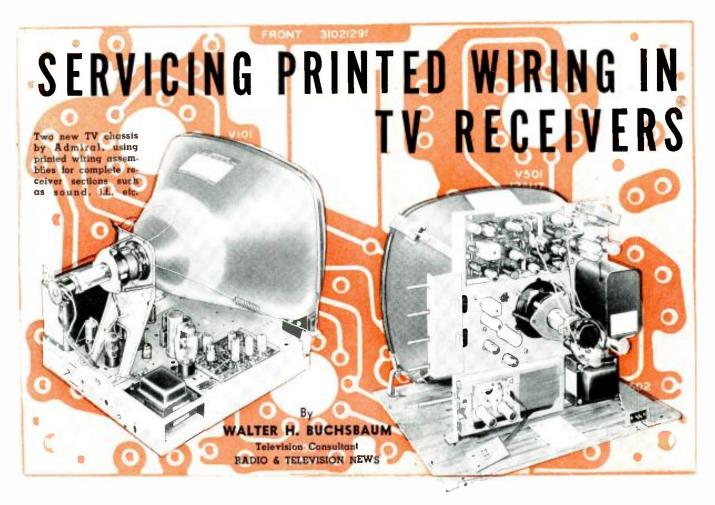If you would like us to publish a similar table listing the specifications on 1955 TV receivers, write to RADIO & TELEVISION NEWS, 366 Madison Avenue, New York 17, N. Y. Tells us also which specifications you would like us to add to this table.



DMIRAL, MOTOROLA, and several other major TV manufacturers have recently begun to use printed wiring in certain subassemblies. Now a complete television receiver made up of printed wiring assemblies has been demonstrated by Walsco. As production techniques are further improved and circuitry becomes more standardized, the use of the printed wiring system in TV receivers will become even more widespread. This will require a different approach from the point of view of the man who has to troubleshoot and repair TV sets. Repairs in printed wiring assemblies are somewhat different than for conventional chassis; this article shows how parts replacement and other chores ean be handled without damaging the assembly.

Before going into technical details, the terminology of this new method should be understood. Printed circuits, as used in hearing aids, vertical integrating networks, etc., involve the printing of eapaeitors, resistors, and eoils on a ceramic base. Printed eircuit assemblies usually cannot be repaired, but must be replaced entirely. Printed wiring, the type of assembly described in this article, uses standard eomponents, but in place of interconnecting wires there is a thin pattern of copper foil, bonded to an insulating material. Either eyelets or holes in the insulating material filled with solder hold the components individually by their pigtails. Larger parts are mounted with straps, sockets, etc.

You will be seeing more and more printed wiring in TV sets; learn how to troubleshoot and repair them.

A typical basic printed wiring plate is shown in Fig. 1. Here the paths of the conducting copper foil are clearly shown,

Manufacture

The most widely used method of making printed wiring sections starts out with a copper-clad laminate consisting of a sheet of Bakelite or similar material bonded onto a thin copper foil. The desired pattern is transferred from a drawing onto a printing matrix by means of photo-engraving methods. This master matrix then prints the pattern, with a special ink, on the copper surface. The ink used is an acid resisting material which covers the copper at those points where a conductor is desired.

Next, the entire assembly is dipped into an acid bath which removes all the copper not covered with the special ink. After a neutralizing and cleaning bath the section is ready for assembly. In some instances the copper foil is plated before assembly which requires reverse printing and an acid which is more active on copper than on the plating material.

Some printed wiring sections have conductors on both sides with holes as connections between the two sides. In many such instances the inside of the hole is plated through or else an eyelet is inserted. The practice of using eyelets at all holes results in a stronger joint and ultimately simplifies parts replacement.

The original copper foil after printing, etching, and cleaning is often only about 0.001 inch thick and naturally very fragile. To connect resistors or capacitors to this very thin foil requires that at the junction point some mechanical anchorage be provided since the copper foil itself is insufficient support. The usual practice is therefore to trim and bend the leads from the components to standard lengths and then insert them into the proper holes, bending them over the copper foil on the other side. The body of the component is then supported by the insulating board and does not rest on the two pigtails.

After all components are in place, the entire assembly is dip soldered. This process requires a special flux and a closely controlled temperature and timing cycle. In many places the dip soldering operation is done completely by machine and this usually makes for a cheaper, more uniform product. During the soldering all holes should fill up with solder and all connections are made at one time. A cleaning bath to remove or neutralize the flux finishes the process. In some instances the residue of the flux is a

December, 1954

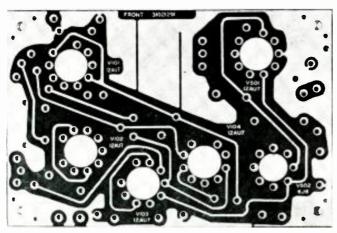


Fig. 1. Phenolic plate showing the copper clad portions which serve as wiring in white. The large holes take tube sockets.

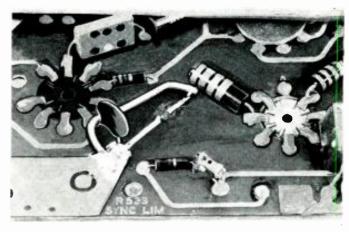


Fig. 2. The method of repairing a break in printed wiring is shown here. A piece of hook-up wire is shunted across the break.

wax coating which is left on to protect the printed wiring against moisture. Other manufacturers finish the assemblies by spraying them with a varnish or similar moisture resisting material.

In order to fully utilize the printed wiring method, many special components were developed. Potentiometers, tube sockets, switches, and electrolytic capacitors are now available with terminals that mount on printed wiring and can be dip soldered. When such components become defective the exact replacement part must be used in most instances. This means that, as printed-wiring type receivers become more popular, the TV service shop must carry additional stocks of special parts.

Troubleshooting

At the time of writing only the Walsco TV chassis employs printed wiring throughout. Most other manufacturers use the printed wiring portion only for certain subassemblies such as the audio section, or the i.f. section. The Walsco model PC-9 chassis has a total of 25 tubes and is made up of 10 separate subassemblies, nine of which are of the printed wiring type. A rear view of the chassis is shown in Fig. 5, illustrating how conventional i.f. shield cans, capacitors, and other components are mounted on the printed wiring subassemblies.

The service technician can use conventional TV troubleshooting methods to trace the defect in a receiver to a particular section and then proceed to find the defective component. If, for example, the entire i.f. section is mounted on one printed wiring assembly, the service technician can remove the individual subassembly from the main chassis for further test. In locating the trouble spot or making various measurements, connections can usually be made to the different resistors and capacitors from the same side on which the components are mounted, simply by clipping directly to their leads.

Although in some printed wiring systems the conductors and components are located on both surfaces, most TV receiver applications use only one side for the actual wiring. Where conductors are found on both sides it is important to remember that the eyelets or solder-filled holes in the insulating material serve as connections from one side to the other and usually hook circuit elements together.

Another important aspect of printed wiring troubleshooting is the relative fragility of the assemblies. Never rest a chassis on a component or any portion of the printed wiring assembly. Even if no break occurs, the flexing of the insulating material may be enough to injure a connection or a lead. Generally, it is good practice to service printed assemblies in the chassis or else lay them on a soft, non-abrasive surface. The use of pin type probes on the printed wiring should be avoided since even a slight slip of the test probe can break a conductor, loosen an eyelet, or otherwise damage the unit. Alligator or crocodile type clips should likewise not be hooked onto joints which could possibly peel off. Another thing to watch for in troubleshooting is to keep the printed wiring assembly away from soldering irons, infrared lamps, or other sources of heat. The solder used in the dipsoldering operation usually has a low melting point and excessive heat can do considerable damage.

In troubleshooting for an intermittent defect in an ordinary TV receiver it is common practice to tap tubes and various parts, pull leads, and probe and scratch connections to find the intermittent. This method must be modified for the printed wiring assembly. Visual inspection is most helpful in this instance. Where a broken wire could not be seen through the insulation or sleeving, the printed wiring assembly clearly shows all conductors, and breaks in them are easily spotted. Intermittent components are not as easily located, but there are certain typical troubles inherent in the assembly method of printed wir-

As mentioned previously, the pigtails of the resistors and capacitors are trimmed and bent to their proper lengths either by machine or else in some kind of jig. Occasionally, some components have a weak spot in the leads or else are dislocated in the crimping jig, with the result that the lead tends to break intermittently at the bending or crimping point. Look at the junction of the individual leads and the body of the component when this type of intermittent is encountered.

Another possible source of intermittents is at the holes through the base board. As can be seen from Fig. 1, the conducting ring around each hole may not be concentric due to slippage, shrinkage, or misregistration of the pattern and this may result in a faulty connecting joint. If the copper does not circle the hole, subsequent plating or dip soldering may also be weaker and with some added strain an intermittent joint may result.

Intermittent tube pins are no more frequent in printed wiring than in an ordinary tube socket, but if one is found it is usually harder to repair.

Repairs

If troubleshooting requires no new technique, the repair of defects found in printed wiring assemblies is certainly different and often more time consuming than for standard wired models. For one thing, the unsoldering of the defective component is considerably more difficult since extreme care must be taken not to damage the assembly. The simplest way to remove a defective small component such as a resistor or pigtail-type capacitor is to cut its leads off near the body. Then, by carefully heating the joint with a small soldering iron, the loose pigtail wire is gently pushed through the hole and extracted at the other side. Never try to apply heat at the joint and pull the crimped end of the pigtail through.

Large components are usually mounted by a strap in addition to the soldered terminals. A good example of this are electrolytic capacitors which have a mounting strap eyeleted directly to the printed assembly. After having elipped the leads of such a capacitor and temporarily substituted a replacement, the mounting eyelet must be drilled out carefully before a new capacitor can be installed. In drilling out eyelets and rivets, the major difficulty is the tendency of the cyelet to spin with the drill. One simple way

to avoid this is to rest the head of the eyelet or rivet on a piece of sand-paper and drill against that. The friction of the head against the sandpaper usually prevents spinning and the drill then makes short work of the eyelet. Another quick method for removing rivets is to use a small grinding wheel attached to an electric hand drill. Grinding off the head and pushing the body of the rivet through with a center punch is often simpler than drilling a rivet out, but care must be taken that the grinding wheel does not slip and damage other parts.

In addition to the use of rivets and eyelets, some large components are staked to the Bakelite board. This is usually done with metal tabs which fit into rectangular slots in the board and are staked or bent after assembly. The best method of removing this type of fastening is to carefully grind off all projecting metal until each tab can be withdrawn smoothly. Bending or attempting to break these tabs off can result in breakage of the insulating board or, at least, damage to the mounting slots which will prevent replacement with the identical part. In replacing a staked lug or tab, the staking operation can be performed with a small chisel or sharpened screwdriver and a light tap hammer. Be sure to work against good support since otherwise the insulating board can be damaged.

In replacing small components such as resistors and paper or ceramic capacitors, be sure to trim and bend the leads properly before actually mounting the part. Fig. 4A shows the correct method of mounting a component by its leads. Note that the body rests flush against the Bakelite board while the leads are bent over at the other side, resting against the copper foil. By leaving one or both of the pigtails loose, as in Fig. 4B, the weight of the component is made to rest effectively on the solder connection. In time, it is possible to peel off the copper foil and, with the aid of vibration, a broken copper conductor may result. In printed wiring assemblies which use an eyelet or a throughplated hole for each connection, the likelihood that the foil will peel off is decreased and the solder joints can support more weight.

Another possible mistake in installing a replacement part is to tighten the bent-over pigtail too much. This creates a stress causing either the Bakelite to bend, the copper foil to tear, or else the pigtail to pull out of the component in time. A word should be said here about bending pigtail leads on resistors and capacitors. Never bend a lead closer than 1/8th inch from the body of a 1/2-watt carbon resistor. Make the minimum bending radius larger as the wire thickness increases. For a 2-watt carbon resistor, the pigtail should be bent at least 1/4 inch from the body.

If the copper foil forming a conductor is broken, the best way to repair this is by shunting a piece of

hook-up wire between the solder joints which the broken lead has connected. Fig. 2 shows how such a break is repaired. In this instance the large metal area at the lower left is a ground strip and the broken conductor was connected from the 2-watt resistor to ground. A short length of hook-up wire has been connected in place of the broken piece.

In many instances the eyelet or terminal hole is not readily accessible for repairs and then it is best to connect directly to the proper leads. Soldering on printed wiring is not the same as for ordinary wiring. Remember, the solder used in printed assemblies is not of the common rosin-core type; its melting temperature usually is much lower than the solder used for general service work. On some printed wiring assemblies, a protective coat of lacquer is sprayed on after dip soldering. Before heat is applied to such an assembly, scrape off the layer of lacquer carefully at the joint with a dull knife or file. Some assemblies have a wax coating which is part of the flux used in the dip soldering operation. This coating can remain, but will smoke and smell slightly when heat is applied.

Fig. 3 shows a preferred method of soldering a new component into place. A small iron tip, rounded and without sharp points, is used. The solderingiron tip is applied to the pigtail wire and never directly to the copper foil. Melt the solder, let it flow, and immediately withdraw the iron. Too much heat from a powerful iron can melt the low temperature solder in nearby holes and loosen some connections. In general, the small soldering irons of the 25- to 50-watt sizes are best for printed wiring repairs. Always use some type of flux to help dissipate the heat from the soldering iron. The rosin flux from the new solder should be cleaned off, either with alcohol or else by wiping with a cloth while the joint is still warm.

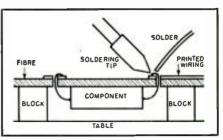


Fig. 3. When making repairs to a printed wiring board, support it as shown.

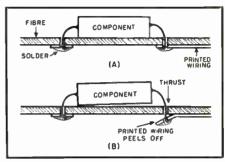


Fig. 4. The correct and incorrect way of mounting components on printed wiring boards. The result of using excessively long component pigtails for a repair is shown in (B).

In the illustration of Fig. 3, the assembly rests on two blocks rather than on the component. Holding the printed assembly properly while working on it is of great importance since otherwise it is very easy to damage parts and connections. One satisfactory and simple way is to put extra long tube shields on some of the tubes and rest the assembly on these shields. Another method utilizes a stiff cardboard box, with the rim of the open box supporting the Bakelite board. More elaborate supports can be made by using long screws and nuts through the regular mounting holes and resting the board on these screws.

The great advantages of using printed wiring in manufacturing make it (Continued on page 155)



Fig. 5. A verticalchassis receiver constructed entirely of printed wiring subassemblies. This set has a separate turret tuner, remotely controlled, shown at the lower left side.





December, 1954 59



By BERT WHYTE

THE Christmas season is here again, a fact which occasions much rejoicing among highfidelity enthusiasts. They can look forward to someone (or perhaps themselves) gifting them with a new amplifier or speaker, or perhaps a nice big batch of new recordings. They might even be the happy recipient of a shiny new tape recorder. Which brings up a point. Ever since I began to review prerecorded tapes, I have had a succession of very sad, and sometimes very irate letters from tape machine owners. Someone had done them dirty, they moaned. Their plight? That old debbil equalization! Seems they had dug deep into their jeans for a copy of one of the new pre-recorded tapes, and instead of sweet music, they heard a discordant dub! Yes, they found out the hard way that there is a great deal of variance in the playback equalization of tape machines. In fact, the problem of differing equalization among the many makes of tape machines, is far more serious than was the recently resolved case of phonograph records. You see, the engineering staffs of the various companies who make tape recorders, have their own particular ideas on how a record and playback head should be constructed and what kind of electrical circuitry is involved. There

is no standardization of equalization in the tape machine business. All that exists is a very tenuous and unenforceable clause in the NARTB "suggested standards" guide, which proposes certain standards of equalization. A few of the large professional manufacturers adhere fairly close to these standards, although they arrive at the results by different methods. The manufacturers who make the small non-professional tape machines ignore these proposals and the result is chaos. However, it must be said that the engineers of these companies are not just being "pig-headed." They have plenty of valid reasons for their non-conformity to a single standard. Cost is a very big factor. Another thing is the desire for increased frequency response at the slower tape speeds. This is done to increase the sales appeal of a unit, and it carries with it the penalty of non-standard equalization. You may be very proud of your unit which gives you "12,000 cycles at 71/2 in. per sec.", but remember this treble equalization with anywhere from 11 to 23 decibels of boost is necessary in some machines to achieve such high frequencies. When you play back a pre-recorded tape which was recorded on a professional machine utilizing far less boost, naturally all that you get is a screechy caricature of the music. There are other variations on this theme with the results always the same tapes recorded on one machine do not necessarily sound good when played back on a different machine. What can you do to correct this situation? Not much, I'm afraid. The prospects for agreement among engineers for a standard equalization are pretty remote at this writing. If you own a professional-type unit which normally doesn't include an integral amplifier, you should have no trouble. They can thus be connected to the preamp of a hi-fi amplifier and judicious use of the bass and treble tone controls will give you a balanced sound. Most of the less expensive "home type" machines have an output jack for connection to an external speaker, While it is less easy of accomplishment, there is no good reason why an output jack could not be provided on these machines which would bypass the integral amplifier and allow connection to a tone control preamp. As with the professional units, this would allow you to balance the music to your particular requirements. It is possible that this modification has been incorporated in some of the newer models which will be shown at the Audio Fairs, I will investigate and report to you what I find. If no help is forthcoming, maybe you can rise up in your collective might and petition the manufacturers to get on the ball!

Christmas is, of course, the season for giving as well as receiving. In addition to the usual reviews, I will list some recordings old and new, which you can use as a "gift guide" in buying for your friends, or for ... yourself. To all my friends everywhere ... a most joyous and Merry Christmas!! Equipment used this month: Electrosonic

cartridge, Fairchild atm; Components Corporation turntable; Fisher 50-C preamp; Mc-Intosh 30-watt amplifier, Jim Lansing D34001 two-way horn speaker; Ampex 600 tape equipment.

equipment.

STRAUSS, RICHARD SALOME

Christel Goltz, Salome; Julius Patzak, Herod; Margareta Kenny, Herodias; Hans Braun, Jokanaan; Anton Dermota, Narraboth. The Vienna Philharmonic Orchestra conducted by Clemens Krauss, London LL1038/39. RIAA eurye. Price \$11.90.

The things that happen in this age of LP! The echoes of Columbia's good but not outstanding "Salome" of a few months ago, have hardly died away, and here we are with a new edition from London. This recording is a bird of a different feather, however. It will take a formidable combination of soloists and orchestra and conductor to supplant this version. In fact, I doubt that few record companies will be foolhardy enough to undertake such a venture. This is not to say that this recording is faultless. Looking at the over-all picture, there is room here and there for improvement. But, hy and large, this is the most exciting "Salome" on records. This is a dramatic work and one that is terribly demanding of the participants. The singers must be superb vocalists; they must also be first rate in their acting. The orchestra must be completely at ease with the complex Strauss orchestration, yet their technical mastery should not make feeling and expression subsidiary. The conductor must maintain a rigid discipline over all his forces, in a score which can destroy itself by its own unchecked momentum. Yet he must not be so inflexible, so unsympathetic that the work loses its poetry and drama. That these impossible conditions are fulfilled, almost to perfection, is as great a tribute to the recording as I can summon. Fate had Christel Goltz as the "Salome" of the first complete (Continued on page 102)

A CHRISTMAS RECORD BUYING GUIDE

Gaite Parisienne Les Patineurs

The Boston "Pops" conducted by Arthur Fiedler, RCA Victor LM1817

Super-fi versions of these old favorites. Fiedler is a master with this sort of thing. Some terrific wood block, snare, and bass drum sounds in the "Gaite"!

Liszt Piano Recital

Orazio Frugoni, pianist. Vox PL8800

If you are looking for some wild and wooly piano in the grand old manner, this is for you. In the "Dante Sonata," and others, Frugoni whips up quite a pianistic storm. Good piano sound.

Violin Concert

Joseph Szigeti in works of Bach, Tartini, and Handel with Columbia Symphony Orchestra conducted by George Szell and Carlo Bussotti, pianist. Columbia ML4891

Szigeti shows off his fabulous skill and versatility in a pair of violin concertos with Szell and in a pair of sonatas with Bussotti. Music making of very high order and recording of more than uncommon merit.

Paganini Recital

Ruggiero Ricci, violinist with Louis Persinger, pianist. London LL-1005

Ruggiero Ricci, violinist with Louis Persinger, pianist. London LL-962

For those of you who like virtuoso violin playing, this is a rare treat. Ricci is one of the brightest young talents today and his technique and tone are amazing, especially when reproduced with the fabulous clarity of this recording.

Christmas Organ Music

Fritz Heitmann, organist. Telefunken LGX66009

One of the most astute masters of the organ plays Christmas hymns of Bach, Buxtehude, and others. Telefunken has always had a great reputation for the quality of their organ recordings and this is no exception. Very clean-lined, Iuminous sound with properly sonorous pedals in the right places.

RADIO & TELEVISION NEWS

THE "BASS ULTRAFLEX" ENCLOSURE

Fig. 1, "Ultraflex" enclosure with back removed to show the three-way system. It can also be used with a single-cone unit or two-way loud speaker systems. See text.

By
DANIEL J. PLACH
and
PHILIP B. WILLIAMS
Jensen Manufacturing Co.

Both 15- and 12-inch versions of this design are included in this article covering Jensen's new speaker housing.

HE major part of design work and experimentation with speaker enclosures has been, and still is being devoted to efforts to get more bass output in a given space—or to retain a certain degree of output in a smaller space. Economic considerations and space limitations dictate that most speaker enclosures must be smaller than the ideal size. Reproduction of low frequencies down to, say, 40 cycles, at approximately constant efficiency over the entire range still requires a very large enclosure, and a rather expensive one if furniture finish is specified.

The battle to achieve more bass in moderately-sized speaker systems still goes on. At *Jensen*, a major program of examination, analysis, and evaluation of all the known principles of enclosure operation has been completed, and several new products have evolved.

The end results of this activity have been most gratifying in the achievement of the greatest total bass output possible at this stage of the art for cabinets of medium size. A new approach retains the desirable features of back-loading corner operation in a simple enclosure structure.

During this development program it was realized that small, compact horns are not capable of reproducing extreme low frequencies at high efficieney with smoothness. Inadequate mouth area produces reflections which create dips in the output, when the horn and driver are properly matched. As it must be assumed that this proper matching is part of the design, it follows that a horn with a too small mouth area does not create peaks which might help offset the dips in total bass output heard, so the net effect is less bass. A small size horn enclosure gives attendant difficulties in development of the path length, as well. So compromises are necessary


which to some degree nullify the theoretical gains of horn-loading. Because of these factors, investigation was restricted to three types—total enclosures, bass reflex, and a new *Jensen* development called "Bass Ultraflex,"

It was determined that medium size total enclosures had these disadvantages:

1. Resonant frequency of the speaker is raised because of the added stiffness behind it. In the case of very large (infinite baffle) total enclosures, this would not happen, but even so, hangover in the speaker is still a problem. The response shape is determined largely by the damping factor of the entire system, including the speaker. Low-frequency performance is definitely limited when amplifiers of high damping factor drive speakers of high efficiency and high magnetic energy. Furthermore, the light low frequency loading may give excessive distortion at moderate or high power inputs.

2. In general, the speaker resonant point is shifted upward even more when the speaker has a cone suspension of high compliance, as with low resonant frequency speakers. This means that these speakers suffer the most, as they will be affected more by

Fig. 2. Comparison of the performance of three different types of speaker enclosures.

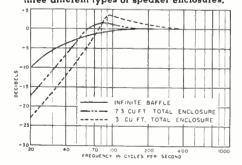

the enclosure-added stiffness than will a speaker with higher resonant frequency. Thus we are limited in how low the resonant point can be placed.


3. Roll-off of the woofer below its resonant frequency is inherently and uncontrollably set at 12 db-per-octave, which severely limits output of the speaker below its resonant frequency. The infinite baffle is far from "pure" and basic as a standard of comparison. In many cases it is out-performed by moderate sized enclosures of other design.

Fig. 2 shows the effect of various sizes of total enclosure. The infinite baffle gives the lowest cut-off. Smaller enclosures produce a rise above cut-off which will increase the "thump" at that frequency. This "thump" effect is sometimes used commercially to give the impression of more bass.

Bass Reflex

The bass reflex principle employs a total enclosure with a vent in the box. The vent uses the back wave by inversion to combine with the front radiation at the enclosure resonant frequency and somewhat above. With proper phasing and damping correlation of the speaker and its bass reflex enclosure, a gain may also be achieved below the speaker resonance frequency, as compared to an infinite baffle. The vent may be considered to add a mass and a parallel resistance shunting the compliance of the enclosure, the compliance being the cushioning effect of the surrounded air. At the anti-resonant frequency of this combination, the impedance is high and can add appreciably to the loudspeaker damping if its system relationships are properly chosen. All these factors are to the good. Furthermore, when large damping in the electrical and speaker systems is used, bass reflex offers definite advantages in over-

Fig. 3. Mechanical details of the 15-inch "Ultraflex" loudspeaker enclosure. For a 12-inch version, use all those dimensions shown circled. The cut-out shown in baffle detail section (bottom right) is incorporated solely to permit the loudspeaker to be inserted or removed easily. Note particularly that the design, as presented, includes all mechanical details for a three-way speaker system. For this condition, the crossover controls are mounted on the side of the cabinet (cut-out detail for these controls is shown in the upper right-hand section). Should other variations be desired, that is, the use of only a single-cone speaker or possibly a two-way system, the front panel cut-outs that would not be required, could be omitted. If the ultra-high-frequency horn is not used, the crossover controls could be moved to the front panel instead of to the side. It is extremely important that all joints be well glued and screwed to obtain an air-tight enclosure.

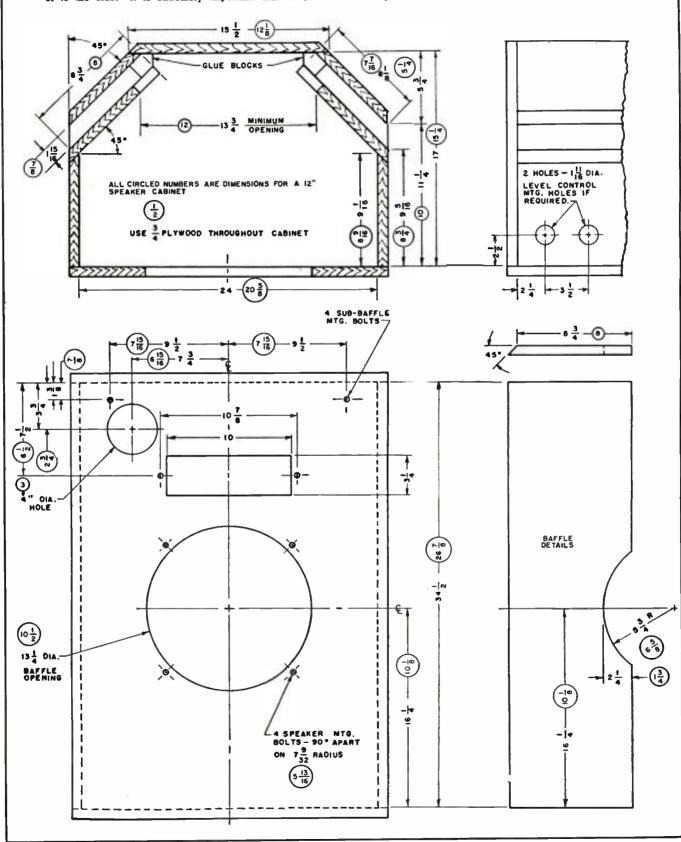

coming the choking effect exerted by the amplifier upon the speaker cone movement at low frequencies. The increased loading makes possible reduced distortion with increased sound pressure output as compared to the total enclosure or infinite baffle.

Some comments have been made from time to time to the effect that bass reflex cabinets are "boom boxes." This may be true where the enclosure and the speaker are not properly matched. Matching does not necessarily mean that resonant frequencies are to be identical, and matching is not as simple a matter as once generally thought. It is possible to get boomy response from bass reflex, especially when the system is not properly tuned and there is insufficient electrical and mechanical damping combined in the over-all system. In this case, an upper resonant mode (above speaker resonant frequency) is likely to appear, and to give a thumpy sound when exc'ted by a fundamental signal at its frequency, or when shock-excited by a different frequency. This condition seems to be the cause of the troubles encountered by experimenters who have not taken into consideration all the factors of operations of this type system.

"Bass Ultraflex" is this company's improved version of the bass reflex. The principle is incorporated in the BL220 and BL250 enclosures shown in Fig. 4. Essentially, it consists of a compliant chamber behind the speaker, this chamber feeding into two rectangular tubes. These tubes add additional mass across the compliance of the chamber in such a manner as to make possible a lower Helmholtz resonance for the system for a given radiating area. This gives the designer an additional tool for controlling performance of the system. This all amounts to furnishing more bass at less distortion than bass reflex can give. The mouths of these tubes are placed, when the cabinet is in a corner, practically flush with the two walls. This placement gives the greatest possible coupling and takes maximum advantage of the "image effect" which increases the usefully applied radiation resistance, and thereby increases the efficiency. The advantages of the back loading feature of folded horns have been obtained with less critical matching and placement factors. When the cabinet is placed against a wall, somewhat less output is produced than with corner operation.

The end result is that matching becomes less critical in regard to variations to be found in different types of speakers, especially when the speakers are fairly efficient. Thus with speakers of moderate (27 ounce) magnet weights or larger, these advantages occur, compared even to bass reflex:

- 1. With speakers of Ligher than recommended resonant frequency, dropoff of the output is smaller below resonant frequency of the speaker,
- 2. Transient response is improved at low frequencies.

Fig. 4. The Jensen BL250 15-



3. Distortion is reduced to negligible levels at moderate powers.


4. Smooth peak and dip-free response occurs down to 40 cycles with recommended 15" speakers. With 12" speakers response is similar, but with somewhat lower efficiency because of the smaller cone area and magnets in the usual 12" speakers.

Fig. 5 shows the comparative sound pressure and distortion characteristics of a 15" woofer driven by a constant voltage source, as measured in an infinite baffle and in the BL250 enclosure.

Fig. 3 shows the dimensioning and construction of the BL250. This cabinet can easily be constructed in the home workshop. Proper performance is assured by following several construction rules:

1. Joints must be well secured and tight.

Fig. 5. Sound pressure and relative distortion of the BL250 loudspeaker enclosure as compared to an infinite baffle. The BL250 is the 15" version described in the article. version described in the article.

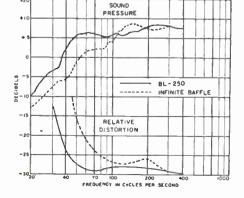

2. The sides of the tubes must be interbraced in at least two spots.

3. Inside dimensions should be held as closely as possible to those specified.

4. There must be no air leaks through any cut-outs or control holes.

5. The back must be tightly sealed, preferably with rubber gaskets,

In the drawing of Fig. 3, a flexible arrangement of holes and blocking covers allows use of various combinations of woofer, mid-channel, and/or tweeter units with only the three front panel holes shown. Unused holes, which can include either or both of the top two front panel cut-outs, can be covered by a sub-panel.

For a coaxial or "Triaxial" speaker, these would be omitted.

The commercial version of this cabinet is supplied with a sub-baffle, or panel, to permit the mounting of various types of mid-range and high-frequency horns. Details of this subbaffle have been omitted since this flexibility would not be required by the home builder. The commercial unit was designed to be used with the company's RP102 2000-cycle unit, or RP302 super-tweeter, and a midchannel unit such as the 600-cycle RP201.

Fig. 1 illustrates the inside of the BL250 with a 3-channel system.

When efficient speakers in these enclosures are driven by amplifiers of even moderately high damping factor, interior padding does not seem to be worthwhile. Under other conditions, padding on sides and top may be called for. When in doubt, apply sufficient 1" glass fiber insulation to cover the bottom and one cabinet side.

A TRANSISTOR VIBRATION AMPLIFIER

Transistorized and simplified version of a circuit first described in Jan. 1953 issue.

THE extremely small power requirements of transistors make it quite advantageous to "transistorize" portable equipment wherever practicable. This is true not only of hearing aids and portable radios, but also of most types of portable test and measuring equipment.

In an earlier article, the author described a small vibration-pickup amplifier built around a used hearing aid ("A Vibration-Pickup Amplifier," January, 1953, Radio & Television News). A "transistorized" version of a vibration pickup and amplifier is shown in Fig. 1, together with the headphones used as an accessory.

No attempt was made, in designing this transistorized version, to exactly duplicate the performance of the earlier unit. Rather, the instrument shown in Fig. 1 was designed for a somewhat different application. Where the earlier unit was used primarily to check for mechanical movements and vibrations in locks, this instrument is designed for checking sounds in heavier mechanical equipment, specifically, to aid an automobile mechanic in diagnosing troubles. Because of this, only one transistor is used (two tubes were used in the earlier version), and less gain is provided.

Circuit Description

The circuit used in the transistor vibration amplifier is quite simple and straightforward, as can be easily seen by reference to the schematic diagram given in Fig. 2. A conventional single-stage grounded-emitter amplifier circuit is employed.

In operation, mechanical vibrations picked up by the probe are converted into electrical signals by a piezoelectric crystal (an ordinary phono crystal cartridge). These signals are, in turn, applied to the primary winding of $T_{\rm c}$.

A piezoelectric crystal has a high output impedance. The transistor amplifier stage has a low input impedance. Hence, in order to match these two impedances to insure maximum signal transfer, a transformer (T₁) having a stepdown turns ratio is employed.

The signal appearing across the secondary winding of T_1 is applied to the base-emitter circuit of the transistor



Fig. 1. Over-all view of transistorized vibration pickup and its amplifier.

through coupling condenser C_1 . A fairly large capacity condenser is used here to prevent loss of signal level at medium and lower frequencies, which might otherwise occur due to introducing a comparatively high impedance in series with the low input impedance of the transistor.

R₁ serves as the "base return" resistor, and, by providing a d.c. path between the power source and the base, establishes the base "bias" current. The value of this resistor determines the "bias" current flow and hence the operating characteristics of the stage.

The collector current also varies with the size of R_0 , as collector current is directly proportional to base current.

The audio signal is amplified by the transistor stage and the amplified signal appearing in the collector circuit is applied to the headphones. Since magnetic headphones are used, they also serve to complete the d.c. path for collector current flow.

A hearing-aid type battery, B_1 , serves as the power supply, and a s.p.s.t. slide switch, S_1 , as the power switch.

No provision has been made for a gain control, as it is not needed with a single stage of amplification.

Construction Hints

Both the pickup probe and the amplifier itself are assembled in a small *Bud* "Minibox." These small aluminum boxes may be obtained with either a gray hammerloid or an etched aluminum finish.

The general parts arrangement used by the author is apparent from the interior photograph given in Fig. 4. Layout is not critical, however, and a somewhat different arrangement may be used by the builder, if desired.

In the author's model, the small transformer and the battery are held

in place by two "Z" brackets, fastened in place by a single machine screw and nut. Connections to the battery are made by soldering leads directly to the terminals. Scotch electrical tape is used over the battery terminals to prevent accidental shorts.

Another builder might prefer to devise a small socket arrangement so that the battery may be installed and removed without soldering.

The transistor has been wired directly into the circuit in the model shown. Where this is done, special care must be taken to avoid overheating the transistor leads. Like most semiconductor devices, the transistor is particularly sensitive to heat, and may be easily damaged by excessively high temperatures.

As an alternative, a socket might well be used for the transistor. An ordinary 5-pin subminiature tube socket is employed (only three of the pin positions are required).

Once the unit is completed, labels may be made up by using standard decals, obtainable through most wholesale parts distributors. In the author's model, black decals were used. After the decals were attached, three coats of clear plastic were applied to protect both the decals and the finish of the case.

Some builders may prefer to omit the labels, however, since they add nothing to the performance of the unit.

Assembling the Probe: A detailed cross-sectional view of the probe assembly is given in Fig. 3 and this sketch is, to some extent, self-explanatory. A few comments are appropriate, however.

The probe itself is made up from an ice pick. The metal point is removed from the handle and the blunt end heated in a gas flame until it changes

RADIO & TELEVISION NEWS

color. This process removes the temper and permits a standard die to be used for threading the end.

Choose a die size that is appropriate for the diameter of the ice pick point used. This will vary somewhat with different ice picks. A 10-32 die was used by the author.

The sharp end of the ice pick should be rounded slightly by using a grinding wheel. This is done to prevent the point from digging into or scratching the surfaces against which it is held. Do not remove the temper from the point by heating, however.

Only that portion of the probe which is to be treated should be re-tempered. For best results, the rest of the probe should be kept in its original state.

When assembling the phono cartridge and probe point as shown in Fig. 3, note that the probe point and its mounting nut bear against the case of the crystal cartridge, not against the needle chuck!

In operation, the case tends to vibrate around and against the crystal with the inertia of the crystal resisting this movement. This provides the necessary bending and twisting motion to operate the crystal so that an electrical signal is produced.

Parts Substitutions: Since so few parts are required for this unit, and these are all standard, the prospective builder should not find it necessary to make substitutions. A number of substitutions are permissible, however.

First, a case different from the one employed by the author might well be used. In choosing another case, keep in mind that it should be fairly rigid—for this reason, a plastic case is not generally recommended.

Another transformer might well be substituted for T_1 . Use any transformer capable of matching a high impedance to the low input impedance of the transistor. A certain amount of mismatch will not cause difficulty. In choosing another transformer, make sure that its physical size is such that it will fit easily into the case chosen.

If preferred, a somewhat smaller condenser may be used in place of C_1 . The author used a 10 μ fd. condenser because of its ready availability. An 8, 4, or even a 2 μ fd. condenser should give equally satisfactory results.

A toggle or rotary switch might be substituted for the slide switch used in the author's model.

Either an open or a closed circuit jack may be used as J_1 , although an open circuit jack will prevent accidental current drain when the headphones are removed (should the switch be in the "on" position). As an alternative, the headphones could be wired permanently in place and no jack provided.

Circuit Modification

Only a moderate amount of gain is provided by the single amplifier stage used in the author's model. This is sufficient, however, where the unit is used on equipment having vibrations of large amplitude.

For some types of work, the builder may prefer an amplifier providing more gain.

One simple technique for increasing the gain of the unit is to substitute a Raytheon type CK721 transistor ("p-n-p" type) for the CK722 shown in the schematic diagram (Fig. 2). The connections are the same, and it should not be necessary to change any parts values.

Where even greater gain is desired, a two-, or even three-, stage amplifier may be used. In such cases, it will be necessary to provide a gain control to prevent overload on strong input signals.

For general information on multistage transistor amplifiers, as well as suggested gain control circuits, refer to Charles W. Martel's article "Transistorize Your Audio Amplifiers" (March, 1953, Radio & Television News).

The builder may find that a tone control will be desirable for some applications. Such a control may be added by connecting a .05 μ fd. condenser in series with a 25,000 ohm rheostat, and connecting the entire assembly between the collector and emitter leads of the transistor. This forms a simple, but effective, "losser" type tone control circuit.

Using the Unit

To use the transistor vibration amplifier, plug a pair of magnetic headphones into the output jack (J_1) and turn the unit "on."

The case is held in the hand and the pointed probe held firmly, but lightly, against the machinery or equipment being checked. Experiment with both the angle at which the probe touches the machinery as well as the exact point at which contact is made.

This technique often enables the user to distinguish between different types of vibration sounds, and to pick out those signals of particular interest.

If the builder has assembled a unit using two or more amplifier stages, and has provided a gain control, this control should be set for minimum gain when the probe is first placed in position. The gain is then gradually

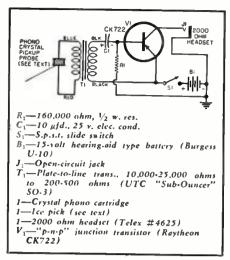


Fig. 2. Diagram of vibration pickup unit.

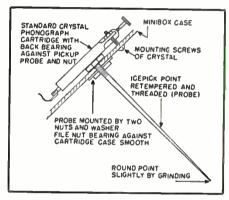


Fig. 3. Mechanical details for assembling the probe. See text for full instructions.


increased, without moving the probe, until the desired signal level is finally reached.

This last technique is used for two reasons. (1) to prevent "blasting" due to high signal levels, and (2) to prevent accidental signal overload, with resulting distortion and changes in signal quality. A distorted signal is difficult to properly interpret.

Applications

Although primarily designed for lis-(Continued on page 160)

Fig. 4. Interior view of unit. Layout may be altered to suit needs of the builder.

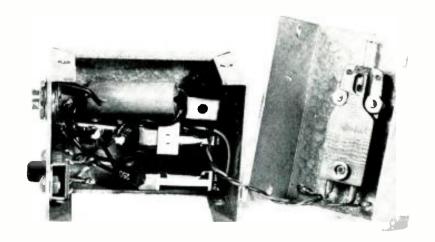

A COMPACT 100-WATT BANDSWITCHING

Front panel view of the home-built 100-watt bandswitching transmitter. Controls are identified and correspond to the schematic. The transmitter covers 80, 40, 20, 15, and 10 meters.

HAM TRANSMITTER



Complete construction details on a TVI-proof transmitter which uses standard components and covers five ham bands.

CONSIDERABLE number of amateurs are interested in a transmitter in the 100-watt class, provided that such a transmitter is compact as well as versatile and includes modern design features. This interest is particularly evident in the terrific sales popularity of the currently available manufactured units and transmitter kits in this power range. This article will discuss a somewhat similar transmitter which meets these specifications, yet is suitable for home construction without the need for complicated sheet metal work or for special components.

This transmitter was designed for maximum flexibility in keeping with its compactness. Four modern tubes are used in the r.f. section, four tubes are devoted to the high-level plate modulator, while three rectifiers and a voltage regulator complete the tube line-up. The transmitter covers five bands in the range from 3.5 to 30 mc., yet is completely bandswitching without plug-in coils. Only three tuning controls require attention when shifting frequency. A continuous tuning pi network is used for the final. All controls as well as the oscillator crystal are accessible from the front panel, eliminating the need for "digging" into the rig when operating. The oscillator also functions as a buffer amplifier for external v.f.o. operation. All power supplies are integral parts of the unit, with a bias pack to supply fixed bias to permit excitation keying. Naturally, AM as well as c.w. output is available, and all stages are completely metered. The cntire transmitter mounts on a 13" x $17" \times 3"$ chassis with an 8%" rack panel.

Modern transmitter design is being influenced by a number of factors,

which, in the light of present day circumstances, arc making construction practices of a few years ago somewhat obsolete and undesirable. Perhaps the most important factor to be considered can be attributed to the rapid expansion of commercial television broadcasting, which has compelled amateurs to consider the reduction of TVI caused by their transmitters. The generally accepted methods of combating TVI involve complete shielding and filtering of the rig. Sometimes these measures are a bit difficult to adapt to existing equipment, but, by considering the problems involved at the onset of design, can be incorporated in a new transmitter without undue trouble.

This attention to TVI reduction and its associated problems led to several of the design features of this rig. Because of its marked superiority in reducing undesired harmonic output, a pi-network was selected for the final output coupling. The E. F. Johnson Company has made available to amateur circles, a line of components for pi-network construction. Their 229-201 rotary inductor allows the network to be tuned from 3.5 through 30 mc. without coil changing, and thus is perfectly suited to a bandswitching transmitter.

It was reasoned that if the r.f. components mounted above the chassis in this transmitter could be assembled in their own small shield box, the problems of complete transmitter shielding would be greatly simplified. To avoid the necessity of fabricating such a shield box at home, some shopping around was done to locate a unit of commercial manufacture which could be used. Fortunately, the *Bud* "Minibox" series met the requirements and

a 10" \times 6" \times 3 $\frac{1}{2}$ " unit, CU-3010, was selected as the correct size to house the pi-network components and the final amplifier tubes.

The proper choice of output tubes for the transmitter was given careful consideration. Beam power and screen grid type tubes are gaining in popularity over triodes for use in ham gear. Undeniably, the higher power sensitivity of such tubes permits the use of low driving power, and the fact that they can operate without neutralization helps to simplify circuitry. On the other hand, many hams recall without relish, the parasitic tendencies and unstable operation sometimes experienced with tubes such as the 807. However, recent tube developments have resulted in a new button-stem construction with short internal leads and multiple base connections for cathode and suppressor to permit better r.f. grounding, as well as internal base shielding. This construction is used in the efficient 2E26, and in the 6146 beam power amplifier tube. This compact 6146 has an ICAS rating of 90 watts input per tube up to 60 mc., so a pair connected in parallel, as used in this transmitter, is easily capable of 100 watts r.f. output.

Separation of the grid and plate circuits of the final amplifier was readily accomplished since the 6146 is provided with a top plate cap. Assembling the plate components in the previously-mentioned "Minibox" shield allows the grid circuitry to be completely isolated simply by mounting these parts under the chassis. This has resulted in an amplifier which is completely stable in operation.

Only two additional stages are used to complete the r.f. section of this

RADIO & TELEVISION NEWS

transmitter. This makes for compact construction, and has the advantage of minimizing the number of stages requiring attention when changing frequency. After some thought, it was decided to avoid the use of broadband circuits; instead, tuned plate loads were selected for their increased efficiency. Several trial constructions were made to investigate various tube combinations and circuits. Finally, the nine-pin miniature 5763 tube was chosen for both the oscillator and multiplier stages, and has proven to be suitable for both applications.

The first stage is connected as a Colpitts harmonic oscillator, which is modified so as to allow operation as a buffer-multiplier as well, with excitation then coming from an external v.f.o. A double-pole, double-throw wafer switch, S_1 , in the grid-cathode circuit of this stage permits this changeover. The screen of this tube is supplied with a well regulated 150 volts, controlled by an 0A2 VR tube.

The second 5763, V_2 , operates as a buffer-multiplier to drive the final to full output on all bands. Approximately 45 volts of negative bias from the bias pack keeps this stage below cutoff without excitation, with additional operating bias developed across the grid leak by the driving signal. A variable screen voltage control functions as an excitation control to adjust the drive supplied to the final grids. The 5763 cathode and suppressor are tied directly to the chassis at the socket, to produce effective r.f. grounding.

The two 5763 stages are made bandswitching, covering five ham bands without plug-in coils, namely 80, 40, 20, 15, and 10 meters. On 80 meters, a 3.5 mc. crystal is used, with the rig operating straight through in all stages. Either 3.5 or 7 mc. crystals may be used for 40 meter operation since the oscillator plate is then tuned to 7 mc., with the buffer and final again running straight through. On the 20 meter band, the oscillator tank is tuned to 7 mc.; however, the buffer stage now acts as a doubler to supply 14 mc, signal to the final grids. To reach 15 meters, the 7 mc. output of the oscillator is tripled to drive the final on 21 mc. Finally, to reach the 10 meter band, the 7 mc, crystal frequency is doubled in the oscillator tank, and again doubled in the multiplier to reach 28 mc. for the final The final stage, it will be noted, functions as a straight amplifier on all bands.

A three-stage audio amplifier is included in the rig, for high level plate modulation of the final amplifier. A 6BA6 is used as the first speech amplifier, intended for use with a crystal microphone of average output. Contact bias is used to develop the slight bias voltage required by this stage, so that the cathode can be returned directly to ground in the interests of minimizing hum pickup at this input stage. An r.f. filter is provided in the grid and heavy decoupling is used in the plate feed. An audio gain control

Docember, 1954

appears at the grid of the following 6AG5 amplifier, which is used as a driver for the modulator tubes. Inverse-feedback is added to the first two stages, and while the gain control is included in the loop, this feedback is desirable in improving the regulation of the driver. A transformer with a 1.5:1 turns ratio is used to couple the driver to the grids of the modulator tubes, which are conventional 807's in push-pull, operating with 30 volts fixed bias and 300 volts on the screens.

While economical in the number of stages, this audio section has been found more than adequate, and fully modulates the final with the gain control less than half open, when used with an Astatic T-3 mike. It is unusually hum free, and the components have been selected to give a restricted frequency response to produce clean crisp quality so necessary for ham work.

To facilitate an accurate check on the operation of the transmitter, a complete metering system is used. A rather tricky metering method, as used in the Johnson "Viking," has been adapted to this rig. For an effective r.f. ground, the 6146 cathodes are grounded directly, and yet with this metering technique, it is possible to measure the final cathode current. This is accomplished by inserting a milliammeter in the high voltage supply negative return lead, a 500 ma. movement being adequate in this case. Notice that the modulator cathodes are returned to the transformer center tap, rather than ground, to prevent their current from flowing through the meter.

An additional 0-50 ma, meter is used to measure the grid and plate currents of the exciter by switching the meter across small resistors provided for this purpose in the desired leads. In addition, this meter is switched


into the 807 cathodes, with a suitable shunt to increase the range to 250 ma., for checking the modulator cathode current. Both meters and leads involved are carefully r.f. bypassed.

A three-deck ceramic wafer switch with 90 degree indexing is used to change the rig from c.w. to phone operation. One deck is used in the oscillator cathode, to switch the cathode return from the key jack to the high voltage panel switch for phone standby. The other decks control the final screen and modulation transformer changeover.

A high voltage power supply furnishes slightly over 600 volts under full load to the final and modulator stages, using a choke input filter to smooth out ripple. A high wattage bleeder is tapped at 300 volts to supply the modulator screens during phone operation, and through a dropping resistor, feeds well regulated voltage to the final amplifier when operating c.w. Under phone conditions, both screen and plate circuits of the class C stage are modulated to secure 100% modulation. An additional resistor with a shorting switch is added to the r.f. screen circuit to reduce power output for tuning.


A low voltage power supply provides slightly in excess of 300 volts for the low level r.f. and audio stages, by using a metal 5T4 rectifier and pisection filter. The input filter capacitor is intentionally kept small to prevent soaring voltages from this supply under conditions of no load. The excitation control also serves as a minimum bleeder across this supply.

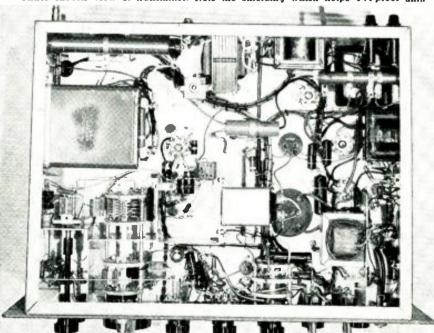The bias pack uses a back-connected filament transformer, into a selenium rectifier and pi filter to produce up to 100 volts bias. The final requires 75 volts, the buffer 45 volts, and modulator 30 volts, available from a low resistance bleeder with three sliders



Under chassis view of transmitter. Note the shielding which helps TVI-proof unit.

67

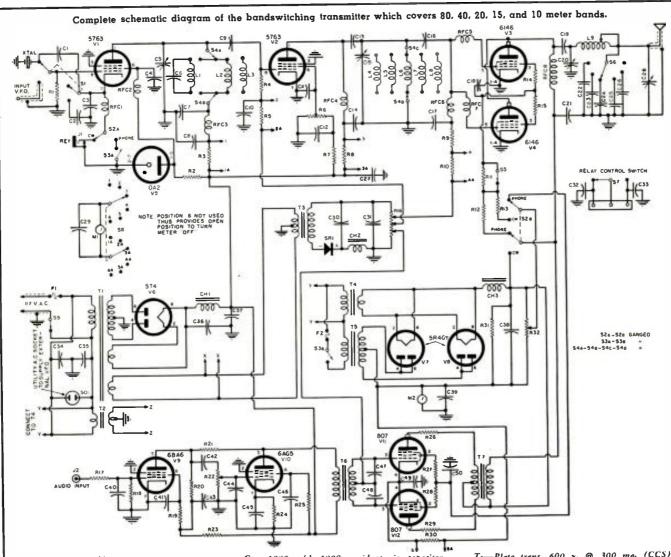

 R_1 —100,000 ohm, $\frac{1}{2}$ w. res. R_2 —25,000 ohm, 10 w. wirewound res. R₂—25,000 ohm, 10 w. reteath 18.8, R₀, R₀, R₁₀, R₁₁, R₂₂—100 ohm, ½ w. res.
R₄—68,000 ohm, ½ w. res.
R₆—25,000 ohm, 5 w. wirewound pot
R₇—2700 ohm, 2 w. res.
R₆—2200 ohm, ½ w. res. R11-20,000 ohm. 10 w. wirewound res. R₁₂-20,000 ohm, 25 w. wirewound res. R₁₈-2500 ohm, 10 w. wirewound res. R14, R15-47 ohm, 2 w. res. -3000 ohm, 50 w. wirewound res. with 3 sliders R17-47,000 ohm. 1/2 w. res. R_{18} —2.2 mcgohm, $\frac{1}{2}$ w. res. R_{19} —1 mcgohm, $\frac{1}{2}$ w. res. R_{20} —250,000 ohm, $\frac{1}{2}$ w. res. R21-1.8 mcgohm, 1 w. res. R==500.000 ohm pot. Rus-27.000 ohm, 2 w. res. R24-270 ohm, 1 w. res. R25-2700 ohm, 1 w. res. R_{30} , R_{29} —120 ohm, V_2 w. res. R_{30} —8 ohm meter multiplier shunt (to increase 50 ma, meter to 250 ma.)

 R_{31} —2.2 megohm, 2 w. res. R_{32} —15.000 ohm, 100 w, wirewound res. with 1 slider

C1-15 μμfd. ceramic capacitor C2, C4, C8, C10, C11, C12, C14, C17, C27, C29, C82, C33, C30, C40, C47, C45, C40-1000 μμfd. ceramic capacitor C8. C9, C13. C16—100 μμ/d. ceramic capacitor

Co. C15-100 uufd. midget var. capacitor C₀—40 μμfd, silver mica capacitor C₇—,02 μfd, mica capacitor

C18-003 µfd., 1500 v. mica capacitor

 C_{21} —.005 μfd .. 2500 ν , mica capacitor C_{22} —1250 $\mu \mu fd$., 1000 ν , midget mica capacitor

-1000 μμfd., 1000 v. midget mica capacitor C₂₆—750 μμfd., 1500 v. midget mica capacitor C₂₅—500 μμfd., 1500 v. midget mica capacitor

 C_{23} —500 $\mu\mu\mu f_{\rm d}$, 1500 v. miaget mica capacitor C_{26} —259 $\mu\mu f_{\rm d}$, 3000 v. midget mica capacitor (1wo 500 $\mu\mu f_{\rm d}$, 1500 v. in series) C_{26} , C_{31} —30/30 $\mu f_{\rm d}$, 150 v. elec, capacitor C_{34} , C_{25} , C_{41} , C_{46} —05 $\mu f_{\rm d}$ by pass capacitor C_{37} —1 $\mu f_{\rm d}$, 1000 v. oil-filled capacitor C_{37} , C_{43} —40/40 $\mu f_{\rm d}$, 450 v. elec, capacitor C₃₅—10 μfd., 1000 v. oil-filled capacitor

C₄₂—,005 μfd. coupling capacitor C₄₄—250 μμfd. ceramic capacitor Ca:—10 µfd., 50 v. elec. capacitor Ca:—11 µfd. bypass capacitor RFC1, RFC2, RFC8, RFC4, RFC6—2.5 mhy., 150

ma, r.f. choke

RFC5, RFC7-,8 µhy., 1000 ma. r.f. choke (Ohmite Z.235)

RFCs-2.5 mhy., 500 ma. r.f. choke (Millen) CH1-6 hy., 150 ma. filter choke

CH₂-30 hy., 60 ma, filter choke CH₃-10 hy., 300 ma, filter choke (Thordarson

T-20C56) L1, L4-80 m.-48 t. B & W "Miniductor" #3012

L2, L5-40 m.-20 t. B & W "Miniductor"

#3012 La, La-20 m.-13 1. B & W "Miniductor"

#3011 L-15 m.-6 t. B & W "Miniductor" #3006 Lb-10 m.-4 1. #14 bus, 3/8" dia., 7/8" long Le-Rotary pi-network inductor (Johnson

#229.201) T₁—Power trans, 350-0-350 v. @ 150 ma.; 5 v. @ 3 amps.; 6,3 v. @ 6.5 amps. (Merit P.3173 or equiv. Author used a now-obsolete

T2. T3-Fil. trans. 6. 3 v. @ 3 amps. Ti-Fil. trans. 5 v.c.t. @ 6 amps. (Stancor P-3062)

-Plate trans, 600 v. @ 300 ma. (CCS) (Stancor P-8042)

(Stancor P-8042)
To-Driver trans, 1.5 to 1 single plate to push-pull grids (Stancor A-4752)
T-Mod. trans, 1.6 to 1, 807's class AB to paralleled 807's r.f. suitable, 75 w. or more audio capacity

M1-0-50 ma. milliammeter (Simpson type 127)

M2-0.500 ma. milliammeter (Simpson type 127)

S1-D.p.d.t. ceramic wafer switch

S2A, S2B-3-pole, 2-pos. switch made from Centralab 90 degree index assembly and 3 ceramic wafers ("C.W.-Phone Switch")

SaA, SaB—D.p.s.t. bat-handle toggle switch
StA, SaB, SaC, Sab—4-pole, 11-pos. exciter band-

A. JAB. JAC. JAD—4-pole, 11-pos. exciter bandswitch made from Centralab 30 degree index assembly and 4 ceramic "Y" sections. (Only 5 pos. required, see text on modifications)

—S.p.s.t. bat-handle toggle switch ("Tune-Up Voltage Control")

—S.p. S.p. Sept. mitch ("

Se_S.p. 6-pos, switch (5-pos, required)
S;_S.p.d.t. bat-handle toggle switch ("Relay Control")

S .- D.p. 6-pos. non-shorting meter switch S.—S.p.s.i. bat-handle toggle switch ("A.C. Line Switch") J.—Closed circuit key jack

J2-Shielded shorting-type audio input connector

SR1-75 ma. sclenium rectifier Xtal.—See text F1, F2—5 amp. fuse

SO3-117 volt utility socket V₁, V₂—5763 tube V₈, V₄—6146 tube V₅—0A2 tube V₆—5T4 tube

V7, V .- 5R4GY tube

Vo-6BA6 tube V11, V12-807 tube Vin-6AG5 tube

which is connected across this pack.

Because of the compactness of this transmitter, the layout is determined, to a great extent, by the sizes and shapes of major components. For this reason, it is suggested that those persons who may be interested in duplicating the rig obtain all parts before commencing work on the chassis. Needless to say, electrical equivalents will be satisfactory providing they are of comparable size.


Construction was inaugurated by fitting the plate components into the "Minibox," and reference to the photographs will aid in this layout. All mounting holes should be drilled in the "Minibox," and then transferred to the main chassis which should be drilled before any assembly is started. Tube sockets for the 6146's are mounted in the main chassis, with larger clearance holes cut in this "Minibox," but all other components are mounted through both chassis and "Minibox."

both chassis and "Minibox."

The "Minibox" should be placed on the main 13" x 17" x 3" aluminum chassis while the high and low voltage power supply and audio amplifier components are arranged as shown in the photographs. It should be noted that the high voltage transformer and filter choke mount near the rear left corner of the chassis with the "Minibox" closely against them, to provide space on the front top of the chassis for the exciter and VR tubes. The counter-dial, Johnson 116-208-4, requires some space behind the panel, which should be considered in spacing out the tubes. Shaft bearings in both "Minibox" and front panel permit brass shaft extensions to protrude to the front panel. The pi-network layout which was best able to utilize the available space, and still result in a neat front panel layout, is evident in the photos. The plate tuning capacitor is to the right of the tubes, with the fixed loading capacitors and switch directly in front of the tubes. The variable coil is immediately to the left, with the variable loading capacitors in the remaining space, with a coaxial cable output lead to the rear.

The two 5R4GY high-voltage rectifiers and the low-voltage power transformer occupy the rest of the back chassis top surface, with the 5T4, filter components, and the audio tubes with modulation transformer taking the space immediately to the right of the "Minibox." The space directly behind the front panel is required for the meters and meter switch, as well as audio and excitation pots.

Viewing the panel from the front the seven controls from left to right stretched across the center section of the panel, are as follows: the audio gain control $(R_{\rm se})$, six position meter switch $(S_{\rm s})$, excitation control $(R_{\rm o})$, plate tuning capacitor $(C_{\rm pe})$, fixed loading switch $(S_{\rm o})$, variable inductor tuning dial $(L_{\rm e})$, and variable loading capacitor $(C_{\rm pe})$. The meters are mounted to the front panel side by side, with the crystal socket located between them and the tuning dial. The

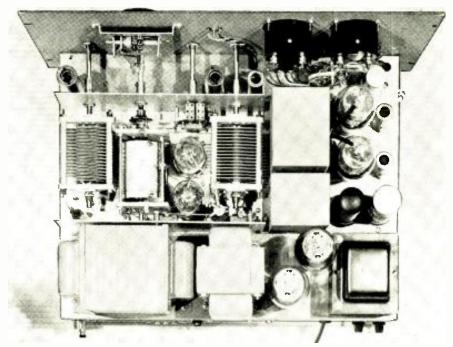

Top chassis view of transmitter with shield cover removed to show parts location.

remaining controls are under the chassis, accessible from the front panel. The key jack and mike input connector (shorting type) are to the extreme left. The four toggle switches are grouped together, and control a.c. input (S_n) , high voltage (S_n) , reduced voltage tune-up (S_n) , and an additional switch for relay control purposes (S_n) , intended for antenna changeover, v.f.o. standby, etc. Next comes the c.w.-phone switch (S_n) , followed by the crystal-v.f.o. switch (S_n) , the oscillator tuning capacitor (C_n) , exciter bandswitch (S_n) , and tuning capacitor (C_n) .


Two fuses, shielded line cord, v.f.o. input jack, v.f.o. a.c. utility outlet, relay switch terminal strip, ground binding post, and the coaxial antenna connector are on the rear chassis edge.

The photograph of the under side of the chassis shows the layout of remaining parts, including bleeders, filament transformers, bias supply, and filter capacitors. A few comments on various phases of construction may be of assistance to builders of the transmitter.

The bandswitch is assembled from four 11-position ceramic switch wafers. Centralab "Y" sections, and a 30 degree indexing unit. The switch is as-sembled on a "Z" shaped aluminum bracket, approximately 3 inches on a side with a 3%" mounting lip along the lower edge. The coils are attached to the switch before mounting to the chassis. Only five of the switch contacts are used per deck, in addition to the wiper, so the r.f. insulation was improved by carefully drilling out the rivet and removing every other contact, with increased spacing and resultant 60 degree coil indexing. The coils are assembled to the wafers so that the 10 meter coil is nearest the wiper, to obtain short r.f. leads on this band.

A small aluminum bracket fastens between the bandswitch shield and the chassis lip to support the multiplier (Continued on page 155)

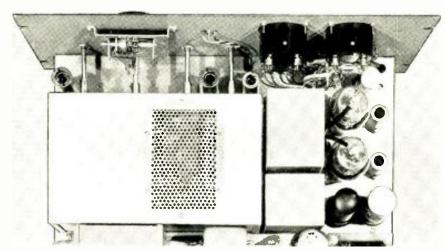Partial view of the top of the chassis with "Minibox" subchassis cover in place.



December, 1954 69



Compiled by KENNETH R. BOORD

N a special DX session, your short-wave editor, Ken Boord, will play a 2710, San Jose, Costa Rica, Central America, at 0000-0030 EST on Friday, December 24th, and repeated at 0000-0030 EST on Saturday, December 25th (0500-0530 GMT on Friday, Dec. 24, with repeat at 0500-0530 GMT on Saturday, Dec. 25). Listed frequencies to be used are 9.645 (actually 9.647), 6.037, and 995 kc. (latter channel on second night only). Reception reports will be appreciated from anyone anywhere in the world. Philip B. Smith, director of TIFC, says all correct reports will be verified with a QSL card and that an IRC will not be necessary.

This Month's Schedules

Albania-Radio Tirana, 7.852, noted 1700 with news; has French session now 1600-1630 (formerly was 1630-1700). (Cox, Dela.) DX-Radio, Sweden, reports Radio Shkodra on 8.215, heard in Sweden 1400.

Algeria-Radio Algerie, 6.160, noted 1710 with Arabic session, strong level. (Catch, England.) Noted closing 1744A with "La Marseillaise." (Pearce, England)

Anglo-Egyptian Sudan — Latest schedule from Radio Omdurman is Arabic daily (except Fri.) 2315-2345, 1130-1430; Fri. 0215-0430, 0900-1000; Sun. 0300-0400; English daily (except Sun.) 0215-0230, 1000-1015, and Sun. 0215-0245 on 6.410, 7.100. (Hardwick,

Angola-CR6RI, 9.340, Radio Diamang, can be heard sometimes in Japan around 1500; all-Portuguese. (JSWC) CR6RA, 4.869, Luanda, noted 1620 in Portguese; closed 1630 with "A Portuguesa," fair strength and readability in England. (Catch) Fairs, England, reports Luanda heard on 6.355 around 1400, (URDXC)

Argentina—Radio Splendid. 9.310A, noted 2040 in Spanish, good level in Mo. (Kirby) LRS, 11.880, Buenos Aires, heard 1720 with tango music in Spanish transmission. (Catch, Eng-

Australia-VLR9, 9.680, noted 0145-0330. (Adam. Brt. Columbia) The Sunday DX session from Radio Australia in the African beam at 0030 is now over 15.200; at 0247 over 9.580, 7.280, 15.320 (and possibly 11.710) to Europe, South and Southeast Asia and South Pacific Islands, and on 9.615 to Eastern North America 0830; is radiated to Western North America Saturday 2300 over 15.200. (Radio Australia) VLX9, 9.660, can be heard in parallel with VLW11, 11.830, at 0300-0330 fadeout. (Kapp, Calif.) VLM4, 4.920, Brisbane, noted 0715-0730 with music. (Peterson, Texas) VLA15, 15.200, is strong level 2155-2315, news 2245, in Western North American beam. (Himber, Calif.)

Austria - Blue Danube Network, 9.617, Salzburg, noted in Sweden 0500-0600 with QSB. (Astrom, Jonsson) Heard on 5.080 at 1245 with music.

(Catch, England)

Azores-CSA93, 4.865. Ponta Delgada, noted at weak level 1540 in Portuguese. (Cox, Dela.) CSA92, 11.925, should now be on winter schedule of 1500-1600. (Ferguson, N. C.)

Bechuanaland - ZNB, 8.252, measured, is weak but in the clear around 1310, says Fairs, England. (URDXC)

Belgium - ORU, 15,335, Brussels, noted 1200-1245 closedown, good level. (Ferguson, N. C.)

Belgian Congo - OTC, 9.655, Leopoldville, is good level in English to North America 2000-2200. (Peterson, Texas, others) Radio Congo Belge, 9.380, Leopoldville, noted 1105 with music, fair level in Calif. (Morgan) Heard on 6.295 with news in French 0000, fair level in N. Z. (Hardwick)

Bolivia—CP5, Radio Illimani, 5.970, is heard well in Denmark from 2100 to 2300 closedown. (ISWC, London) Is weak level in Alberta then. (Duering) CP38, 9.442, La Paz, heard closing 2128 at good level in N. C. (Ferguson)

Brazil-Radio Cultura, 6.165A, still noted in English around 2300. (Niblack, Ind.) PRB23, 15.135, Sao Paulo, is heard in Sweden 1530-1630. (GDXaren, Sweden) ZYB9, 15.155, Sao Paulo, noted 1814-1825, very strong; QSL received. (Machajewski, N. Y.) PSL, 7,936, and PSH, 10.2235, Rio de Janeiro, noted with news in Portuguese 1730. (Catch, England) ZYK3, 9.565, Recife, noted weekdays with "Brazil Calling" (English) 2005-2030. (Peterson, Texas) ZYC8, 9.610, Rio de Janeiro, noted 1830-2015 at strong level. (Duering, Alta.)

British, Guiana - ZFY, measured 3.255, noted closing 2121. (Ferguson, N. C.) Heard on 5.981 at 0500. (Hard-

British Honduras-ZIK2, 3.300, Belize, measured 3.300, noted closing 2231. (Ferguson, N. C.)

Bulgaria-Radio Sofia, 7.256A, good (Continued on page 122)

(Note: Unless otherwise indicated, all time is expressed in American EST; aild 5 hours for GCT. "News" refers to newscasts in the Enrish language. In order to avoid confusion, the 24 hour clock, has been used in designating the times of broadcasts. The hours from midnight intil noon are shown as 10000 to 1200 while from 1 p.m. to indinability as shown as 1300 to 2400 f. The symbol "V" following a 1sted frequency indicates "varying." The station may operate either above or below the frequency given. "A" incans frequency is approximate.

This attractive listening post, owned and operated by Floyd Backus of Richmond. Va., features a National NC-98 receiver. Note Floyd's fine collection of QSL cards.



RADIO & TELEVISION NEWS

NEW FM-ONLY TUNER


Fig. 1. Over-all view of the Model 310-A FM tuner. The tuning indicator is so designed that the entire band can be swept with the flick of a finger. This Lucite tuning indicator also serves as a pilot light and a means of illuminating the etched dial face.

REQUENCY MODULATION broadcasting offers major fundamental advantages over amplitude modulation in the reception of wide-range undistorted sound with minimum interference from atmospheric noise. electrical equipment, etc. To realize the tremendous advantages of FM reception, a good receiver is needed and sensitivity alone is not enough. Good FM reception is determined largely by what is not picked up. In urban areas, strong local stations can cause a multitude of spurious responses resulting from cross-modulation and image interference. Impulse noise from vehicle ignition systems, diathermy machines, and interference from TV and other devices is high. Reflections of the signal from buildings cause multi-path transmissions and consequent fading which often reduces the level of the desired signal. In rural areas, high sensitivity and high selectivity are required to provide noise-free reception and to overcome the fading caused by multi-path transmission,

The performance of a good FM receiver is determined largely by absence of interference and noise. Other desirable factors are reasonable cost, attractive styling, operating convenience, interstation noise suppressor and tuning and signal strength meter.

In the design of the H. H. Scott 310-A FM "Broadcast Monitor Tuner" shown in Fig. 1 every effort was made to avoid undesirable effects in reception while including all desirable performance features. In many cases, appreciable departures from tradition and conventional design were required, including an entirely new tuning drive and a completely enclosed case.

In order to make the most of the desirable features uniquely inherent in FM transmission, wide-band circuitry was used rather than the more common narrow-band circuits. The advantages of wide-band design are significant reduction in adjacent channel, co-channel, and impulse noise interference; improved capture ratio; and significant reduction in distortion caused by overmodulation, by signal detuning or by the inherently greater non-linearity of typical narrow-band circuits. Also, the wide-band design makes possible non-critical tuning and virtually eliminates the effects of minor drift as a result of temperature or power line voltage changes or component aging, thereby making complex and troublesome a.f.c. circuits unnecessary. The wide-band design tunes in a fashion similar to one with a strong a.f.c. circuit but avoids the drift caused by unavoidable aging of a.f.c. circuit characteristics or by

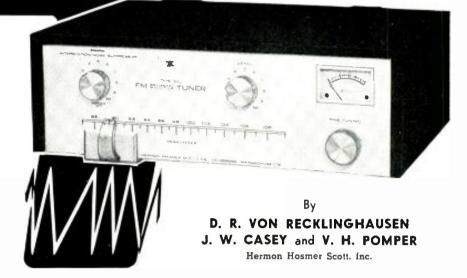

Engineering design details on a new audio component which features an interstation noise suppression circuit, a.g.c., capacitor tuning of the oscillator, and 3 limiting stages.

slight misalignment of critical a.f.c. adjustments. It also avoids the tendency with a.f.c. for strong stations to "pull" the tuning so that adjacent weak stations cannot be received.

The further advantages of wide-band design in reduction of interference and noise were recognized and pointed out in Armstrong's early work. To pass without significant interference a desired signal when an interfering signal has an amplitude almost that of the desired signal, a bandwidth of at least 2 megacycles is required in both limiters and detector. In the design of the 310-A, a 2 megacycle bandwidth in limiters and detector was found practical, thereby providing a capture ratio of less than 2.5 db. Capture ratio is the ratio between desired signal and the maximum interfering signal which still permits good interference rejec-Contrast this with the 300 kc. average detector bandwidth of a good narrow-band receiver, which may have a capture ratio as high as 20 db.

In order that the limiters perform adequately, very high-speed perfect limiting is essential if phase and frequency distortion of the signal are to be avoided. In choosing limiter circuits, the simple diode limiter was rejected as ineffective.


For true FM performance full limiting action must take place on even the weakest input signals. Therefore, three effective stages of limiting are used. The first is an electronic limiter, using a 6BN6 gated-beam tube. The second, a plate limiter using a 6AU6 tube, has high output which is applied directly to the wide-band detector, an

unbalanced ratio detector which also acts as a third stage of limiting.

The unbalanced ratio detector offers several significant advantages over typical discriminator circuits which are not capable of as good co-channel interference rejection. Distortion caused by non-linearity in the discriminator response is responsible for a significant amount of the annoying distortion audible in narrow-band receivers. This cause of distortion is virtually eliminated by use of a wideband ratio detector.

Factors important in the design of the i.f. or intermediate frequency amplifier stages are flatness of the passband characteristics, passband width and selectivity, high overload margin, high gain and low noise. The i.f. passband characteristic must have as flat a frequency response as possible to prevent slight variations in i.f. response from reversing relative strengths of almost equal desired and undesired signals, thereby increasing co-channel interference and degrading capture ratio.

The i.f. passband width was designed to be flat over the full modulation band of 150 kc. With tuners having significantly narrower i.f. passbands, detuning or high modulation causes serious phase distortion in the i.f. signal which cannot be eliminated and may cause as much as 10% audio harmonic distortion. The 150 kc. wide flat passband designed into the i.f.'s virtually eliminates such distortion. High attenuation outside of the flat passband is desirable to minimize interference caused by adjacent-channel stations.

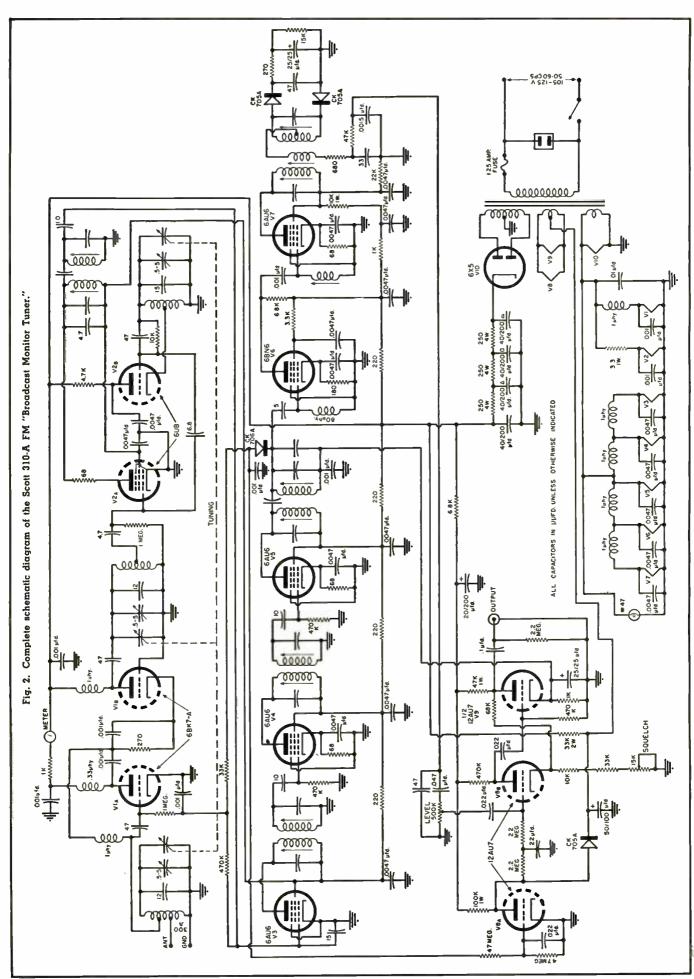

Three i.f. stages with eight tuned circuits were used to obtain maximum attenuation outside of the i.f. passband. This permits listening to weak stations located at only slight frequency separation from strong local stations.

The i.f. stages were designed to have relatively large overload margins so that strong pulses riding in with the incoming signal will not cause stage overloading, with consequent degraded capture ratio. The i.f. stages were also designed with loose coupling to prevent undue detuning on strong signal strengths.

Capacitor tuning of the oscillator was used rather than slug tuning since its basic rotary motion is mechanically easier, smoother, and more reproducible, allowing greater control accuracy and exact tuning over the entire range.

Also, with capacitor tuning it is practical to have the oscillator frequency above the carrier, which is a real advantage in minimizing image interference. With slug tuning it is difficult to get adequate tracking with an oscillator frequency higher than the carrier unless specially shaped slugs are used.

It was considered important that the oscillator frequency be higher than the signal frequency because if the oscillator is tuned above the signal any possible image interference can only be from the aircraft control bands where transmitter powers are only several hundred watts. If the oscillator is tuned below the signal, image interference comes from the TV band where transmitter powers may be 100 kilowatts. A reduction in possible image interference of nearly 30 db is achieved by choice of oscillator frequency.

Another type of interference common in FM receivers is the result of cross-modulation between strong local signals, the oscillator signal, and other signals. This causes spurious responses which show up as reception of the same stations at many different points on the dial. By careful design of selectivity and linearity of the r.f. stage it was possible to obtain a spurious response rejection of 85 db, an outstanding design accomplishment, since sensitivity, which is usually sacrificed, was unaffected.

A neutralized cascode circuit was chosen for the r.f. stage, providing high sensitivity, selectivity, and stability together with lowest noise.

The high selectivity prevents overloading the r.f. stage when the incoming signal is off tune. The input impedance to the r.f. stage and its circuits was designed to be 300 ohms so that a standard 300-ohm folded-dipole antenna may be used with exact matching. The design was carefully chosen to be non-critical so that 75-ohm antennas may be accommodated with entirely negligible mismatch.

Few FM tuners include automatic gain control or a.g.c. The typical FM tuner depends on the limiting action to present uniformly equal voltages on all input signals to the detector. Unfortunately, if no gain adjustment is provided, high signal strengths may cause overloading of individual stages with consequent distortion of i.f. passband shape. This increases distortion, co-channel interference, cross-modulation, and impulse noise interference. Automatic gain control was chosen in order to eliminate need for a manual control to decrease sensitivity on high inputs. The a.g.c. voltage is developed by a diode on the output of the i.f. and is used to reduce the gain of the r.f. and first i.f. stages whenever high signal strengths are encountered. Delayed action a.g.c. is used so that tube noise alone does not institute control action. With undelayed a.g.c, even extremely weak signals will reduce the r.f. gain and increase the equivalent noise, thereby causing weak signals to be received with a substantially degraded signal-to-noise ratio.

The output of the unbalanced ratio detector is applied to a two-stage feedback amplifier which permits very low distortion, less than 0.1% even with 100% signal modulation. This circuit also makes possible a very low output impedance equivalent to that of a cathode follower, so that a long output cable may be used between tuner and power amplifier.

One of the most annoying features of most FM reception is the loud rushing noise heard between stations. A dynamic action interstation noise suppression circuit was provided to eliminate this annoyance. A continuously variable control was provided on the front panel for convenient adjustment from maximum noise suppression to maximum sensitivity.

While tuning is non-critical, a combined signal strength and tuning meter is provided for maximum convenience in tuning very weak signals and in orienting the antenna. The tuning technique is therefore similar to the simple and familiar AM tuning.

Also, with high interstage noise suppression action, weak stations might be passed over completely. However, the combined tuning and signal strength meter provides a visual indication of the existence of a signal with noise suppression on, so suppression may be reduced for receiving weak signals.

To avoid laborious "cranking" of a tuning knob, a basic departure from conventional tuning drives was developed as indicated in the photographs of Figs. 1, 3 and 4. The tuning indicator serves as a sturdy finger grip for sweeping through the entire FM band

(Continued on page 145)

Fig. 3. Top view with cover off, showing unique tuning drive.


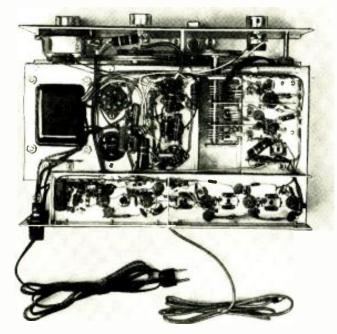


Fig. 4. Under chassis view of unit. Note generous use of shielding.

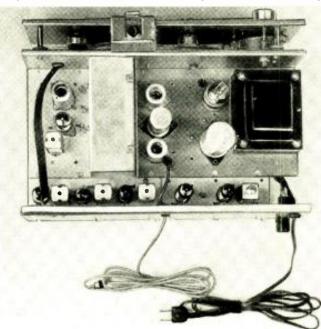

December, 1954 73



A simple amplifier circuit which can be added to standard 0-1 ma. meters to increase sensitivity by a 10:1 ratio.

EW meters are as popular as the standard 0-1 milliampere instrument. In fact, it is hardly likely that there is an experimenter's laboratory, a ham's workshop, or a school or commercial laboratory where at least one of these meters cannot be found.

But the same thing is not necessarily true of the more sensitive instruments—meters requiring 500 microamperes or less current for full scale deflection. Too often, however, the more sensitive instrument will be required, either for conducting a series of experiments, for circuit development work, or for proving in and testing a new piece of electronic equipment.

Unfortunately, the comparatively high cost and greater susceptibility to mechanical damage of the more sensitive meters may make it impractical for many laboratories to keep a quantity of these meters on hand. Certainly the purchase of a 0-50, 0-100, or 0-200 microampere meter represents a

strain on the budget of the average electronics experimenter and ham.

There is one solution, i.e., the use of the common and easily available 0-1 ma, meter together with a low impedance current amplifier to increase its sensitivity. The Raytheon CK722 transistor is ideally suited for this application. A current amplification of 10:1 is comparatively easy to achieve with this component, while at the same time maintaining the low impedance input so necessary in meter circuits.

It thus becomes possible to increase the sensitivity of the average meter by a factor of ten to one. A 0-1 ma. meter can be given a full-scale sensitivity of 100 microamperes. Where a more sensitive basic movement is used, even greater sensitivity is possible. A 0-500 microampere meter can be given a sensitivity of 50 microamperes.

On the other hand, where a less sensitive meter is employed, not as much sensitivity is possible. Thus, if a 0-2 ma. meter is employed, a full-scale

sensitivity of only 200 microamperes is obtained.

Because of the small size of the transistor and the simplicity of the circuit used, the entire amplifier can generally be assembled in the meter cabinet. The meter shown in Fig. 5 calibrated 0-1 ma., has an actual sensitivity of 0-100 microamperes, yet the entire amplifier circuit used to obtain this sensitivity, including batteries, does not even partially fill the cabinet, as can be seen in the rear view of the instrument, given in Fig. 4.

The average technician should have no difficulty in assembling, testing, and calibrating a similar instrument in less than an hour's time, using the schematic diagram given in Fig. 2.

Circuit Description

Referring to Fig. 2A, the CK722 transistor has been connected as a grounded emitter, direct-coupled current amplifier, with the basic meter movement, M_1 acting as the amplifier load. Variable resistor R_1 is used to set the full-scale meter reading, while operating power is supplied by battery B_1 (An alternative connection for the calibrating resistor, R_1 , is given in Fig. 2B, and may give better results in some circumstances.)

In operation, as long as there is no base current flow, the emitter-collector current flow is negligible and may be considered to approach "0" for practical purposes. This condition exists when base (—) and emitter (+) leads are open (as shown in Fig. 2A) or shorted together.

Now, when the base and emitter leads are connected in series in a circuit in

Table 1. The author's calibration table obtained when checking meter shown in photos.

VOLTAGE (B)	RESISTOR	CALCULATED CURRENT	METER READING
1.4 volts	14,000 ohms	100 μα.	1.0 ma.
1.4 volts	18.660 ohms	75 µa.	.749 ma.
1.4 volts	28,000 ohms	50 μα.	.50 ma.
1.4 volts	56,000 ohms	25 μα.	.25 ma.
1.4 volts	100,000 ohms	14 μ a.	.142 ma.
• 0	0	0	0
* Meter leads sho	rted together.		

which direct current is flowing, this current becomes the "base current" for the transistor, permitting a collector current flow that is proportional to its value. As the base current increases, the collector current increases in direct proportion, although of much larger amplitude (approximately ten times greater). Thus, the meter reading indicates a value that is proportional to the base current flow,

Since the maximum battery current drain is equal to the full-scale deflection of the meter (in the model shown, 1 ma.), battery life is quite long, and it is entirely feasible to use small cells.

Construction Hints

Assembly and wiring of the meter amplifier is perfectly straight-forward and no special precautions are necessary. Since d.c. is used throughout, both lead length and layout are non-critical, and the builder may follow his own inclinations as to the arrangement of components. It is suggested, however, that standard good construction practice be followed.

The author used small penlight cells (Burgess #7) for the voltage source (B), Fig. 2), wiring two in series. However, any other suitable batteries may be employed, even regular flashlight batteries. If the larger size batteries are used, the builder may have to experiment somewhat with the arrangement of components within the meter cabinet, taking care that no leads are shorted.

Crowding of parts is permissible, since there are no heat dissipation problems.

If available locally, the builder should consider one of the *Mallory* mercury cells (such as types RM1000, RM1200, etc.), as these have a much longer operating life than standard batteries.

Although practically any meter may be used in the basic circuit, the builder may find it necessary or desirable to change the supply voltage (B_1) , and the size of the calibrating resistor R_1 to obtain the best results with his particular instrument. Both the series (Fig. 2A) and the shunt (Fig. 2B) calibration connections should be tried, with the final connections made using the circuit that gives the best results.

In general, the meter should give a full scale reading for the desired base current flow, and the supply voltage and calibrating resistor should be adjusted accordingly. For example, if an 0-1 ma. meter is to be given a sensitivity of 100 microamperes, full scale, then a reading of 1 ma. should be obtained when there is a base current flow of 100 microamperes.

If the meter reading is less than 1 ma., either the supply voltage should be increased or the calibration resistance decreased (using the series connection). In extreme cases, both steps may be necessary.

On the other hand, should the meter reading be off-scale (above 1 ma.), with a base current of 100 microamperes, then the series resistance should

be increased, or the battery voltage reduced, or both.

Thus, in this way, it is possible to compensate for different types of meters and for minor variations in transistor characteristics

Calibration and Adjustment

Once the wiring is completed and the meter checked for "full-scale" reading, detailed calibration tests may be carried out. The general set-up shown in Fig. 3 may be used. A similar set-up, but without the "Calibration Meter," is shown in Fig. 1,

Battery B is a voltage source capable of supplying the necessary current; an ordinary 1^{1}_{2} volt dry cell is satisfactory for use here. A resistor decade box or resistor substitution box is included in the circuit to limit current flow to the values needed for calibration.


The "Calibration Meter" is a sensitive meter and should have a range approximating the full-scale range of the modified meter. However, this instrument is optional and may be omitted from the circuit if an accurately known voltage source and precision resistors are used. While the resulting calibration will not be as accurate as that obtained with a meter, it is generally satisfactory for practical work.

Next, the current through the circuit is varied from "0" to the full-scale reading of the "Modified Meter" by changing the series resistance of the decade box. Each current value, together with the actual meter reading, is recorded in a table. Table 1 was made up in the course of checking the meter shown in Figs. 1, 4, & 5.

In the model, it was found that the calibration checks followed the scale reading so closely that it was only necessary to take the position of the decimal point into account when reading the meter. In many cases, this will be found to be true, for the operation of the transistor is linear over almost the full range from zero to maximum collector current.

In determining the calculated current

Fig. 4. Rear view of meter case showing how amplifier circuit has been built in.

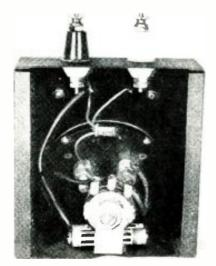

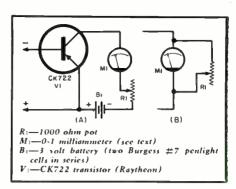


Fig. 2. (A) Schematic diagram of transistor meter amplifier connected as a grounded emitter, direct-coupled current amplifier, with basic meter movement acting as the amplifier load. (B) An alternative connection for the calibrating resistor, R₁, of (A).

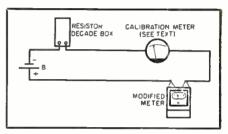



Fig. 3. Calibration set-up using a "Calibration Meter" and resistor decade box.


values given in Table 1, no effort was made to take the internal base-emitter resistance of the transistor into account. This is generally permissible because the impedance of the transistor will usually be low compared to the series resistance used during the calibration procedure.

Where the meter calibration is such as to prevent using the printed meter scale directly, one of several alternative steps may be taken. A "calibration chart" or graph may be prepared for the meter, giving actual current values in terms of meter readings. A multiplying factor other than ten might be employed. Or a new scale can be drawn for the meter.

Once the modified meter has been (Continued on page 118)

Fig. 5. Front view of 0-1 ma. meter whose sensitivity has been increased to 0-100 $\mu\alpha$.

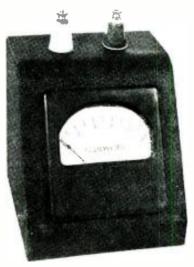

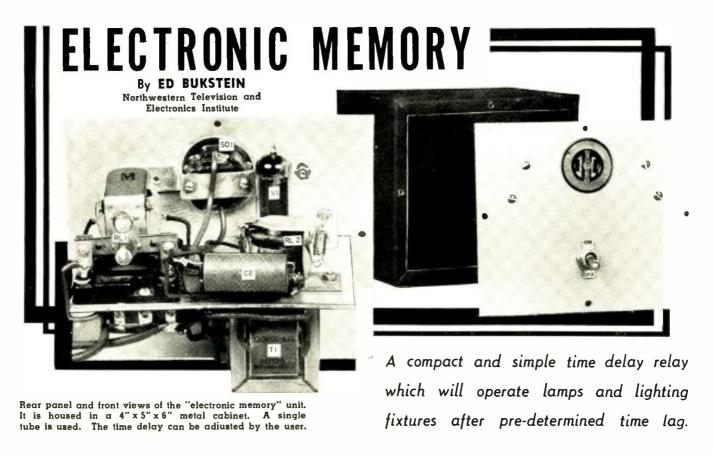

THIS "electronic memory" fits into a 4 by 5 by 6 inch metal cabinet with room to spare, and "remembers" to turn off the lights after you have left. The unit should eliminate the cause of many bruised shins and stubbed toes, and should be appreciated by anyone who has ever (1) been a foreman, guard, or other last-man-out who turns off the lights and feels his way out of the building, (2) parked the family car in the garage and then groped through a dark jungle of clothes lines, forgotten toys, lawn mowers, rakes, etc., (3) turned off the house lights and stumbled through a dark porch or corridor to the walk, (4) switched off the bedroom lights and groped towards the bed.

The front panel of the memory unit contains a toggle switch and outlet.

The lamp or other lighting fixture to be controlled is plugged into this outlet. When the toggle switch is in the "on" position, the line voltage is available at the outlet and the light is on. When the toggle is switched to the "off" position, a sixty-second time delay begins. During this interval, the line voltage is still available at the outlet and the light remains on. At the completion of the time delay interval, the unit turns off the light and also disconnects itself from the power lines so that no standby power will be consumed.

As shown in the diagram, the toggle switch is a double-pole, double-throw type. The two opposite sections of the switch are used so that when one is open the other is closed $(S_{14}$ and S_{18} in the diagram). When the toggle is in


the "on" position, S_{13} is closed and relay RL_1 is energized. The contacts of this relay apply the line voltage to the outlet and also to the time delay eireuit. During the half cycle of line voltage when the grid of the 6AQ5 becomes positive, grid current charges capacitor C_1 .

When the toggle is thrown to the "off" position, S_{1H} closes. Capacitor C_1 is now connected between the grid and cathode of the 6AQ5. The polarity and magnitude of the charge on C_1 are such that the tube is biased beyond cut-off. After an interval of time, however, the charge on C_1 will have leaked off through the resistors connected across it. The 6AQ5 will now draw plate current and energize relay RL2. The normally-closed contacts of this relay now open and interrupt the current flow through RL_1 . When RL_1 de-energizes, the outlet and the time delay eircuit are both disconnected from the power lines.

The length of the time delay is determined by the time constant C_1 - R_1 - R_2 . For the intended application, a sixty-second time delay is a reasonable interval. For special applications however, it may be desirable to either increase or decrease the interval. This can be easily accomplished by changing the value of C_1 or of the resistance in parallel with it. Increasing either the capacitance or resistance will increase the time delay, and *vice versa*.

Almost every home has a few dark areas in the attic, basement, hallway, side entrance, etc. The "electronic memory" can add a new feature of safety and convenience to the home. It is easy to build and relatively inexpensive.

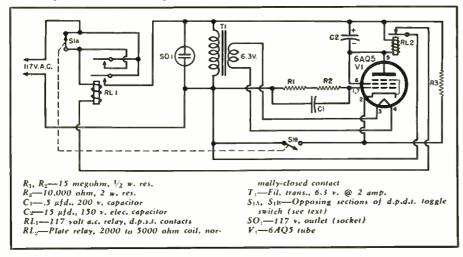Complete schematic of relay. Variations in timing intervals are possible. See text.





NEWEST DEVELOPMENTS

Your training covers U H F, Color Television, FM, Oscilloscope Servicing, High Fidelity Sound and Transistors.

PRACTICE AND TRAIN AT HOME

You get valuable practical experience in construction, lest-You get valuable practical experience in construction. Lest-ing and shop practice. You build a powerful 2 and superbut radio, the all-new 18 range Sprayberry multitester, the new Sprayberry Training Television receiver, signal generator, signal tracer and many other prajects. All equipment is yours to use and keep . . . and you have practically every-thing needed to set up a Radio-Television Service Shop.

All your training is IN YOUR HOME in spare hours. Keep on with your present job and income while learning. I help you earn extra spare time money while you learn. If you expect to be in the armed forces later, there is no better preparation than practical Sprayherry Radio-Television training. Rush coupon below for all the facts—FREEI

SPRAYBERRY ACADEMY OF RADIO

111 NORTH CANAL STREET, DEPT. 25-S. CHICAGO 6, ILLINOIS

NOW 10 MARE MORIT IN CATALOG SAMPLE LI	ing Plan. I understand this does not obligate me and that no salesman will call upon me. Include New Catalog and Sample Lesson FREE.
Rush coupon for my "How to Make Me Radio-Television". P	oney in NameAge
actual sample Spra Lesson without obligatio FREE, Mail coupon NO	ni – ALL Address ———————————————————————————————————
Tille. Mail coupon No	CityZoneState

December, 1954

the training equipment I send my students.



CALLING ALL INVENTORS

A FREEZING RAIN during the night had turned the out-of-doors into a crystal fairyland. Every tree was an immobile fountain of ice; the eaves of every building wore gleaming, sparkling fringes of icicles.

However Amanda Perkins, secretary, office manager, customer buffer, and Chief Worrier of Mac's Radio Service Shop, was oblivious to all this congealed beauty outside. Seated at her desk with her back to the windows, she was playing a staccato tune on the typewriter as she engaged in her daily little game of trying to get through all the correspondence by lunch time.

That was why she did not see the door open stealthily behind her to admit the curly red head of Barney, the shop's service technician, j.g. The boy stepped inside and closed the door behind him with a quietness that was amazing coming from one who was usually about as quiet and gentle as a bulldozer. Holding a small icicle delicately between thumb and forefinger, he tiptoed across the room and gently dropped it down the back of Miss Perkins' dress.

Instantly she gave a loud shriek, exploded out of her chair, and began frantic movements of her body as she tried to dislodge the melting bit of ice.

Mac, who had watched the whole procedure through the open door of the service department came rushing into the office brandishing a length of pipe mast and demanding, "Where's the mouse, Amanda? Just show him to me, and I'll clobber him for you!"

Barney, wearing a look of shocked surprise on his face during all this pandemonium, finally said, "Why, Amanda, I didn't know you could rhumba; or is that a new hula you are showing us?"

At this Miss Perkins suddenly became ominously quiet as she glared at her tormenters. Then she walked deliberately over to her desk and picked up a heavy paper weight. That was all the hint Mac and Barney needed. With one accord they leaped through the door of the service department and slammed it behind them.

Mac grinned at Barney leaning weakly against the door and asked in his best imitation of the "Life With Elizabeth" announcer, "Aren't you ashamed?" Barney was still laughing too hard to do more than shake his head vigorously.

"Well, then I'd better find an outlet for some of this surplus energy of yours," Mac said as he picked up a small pamphlet from the service bench. "As a person who is always eager to think about anything except work, you should find this right up your alley. Ever hear of the National Inventors Council?"

"Don't think so."

"It was created in 1940 by the Secretary of Commerce with the concurrence of the President to establish a means by which the natural inventive talent of the American people could be used to aid the war effort. The chief function of the Council is to receive and evaluate ideas and inventions that may be of use to the military forces. In this capacity it welcomes suggestions from inventors on practically everything from 'toothpicks to tanks.' Since the Council has been in business during the past fourteen years, the public has submitted more than 300 .-000 proposals, some of which have resulted in tremendous savings in men, materiel, time, and money.

"In order to channel inventive thinking somewhat, the Council periodically issues lists of military problems that are current. I have such a list here. Hoping to concentrate your inventive genius still further, I have gone through the list and checked off those items that would seem to lie in the domain of electricity and electronics."

"Fine, fine!" Barney said smugly. "Toss a couple over the plate."

"Often I hear fellows who are studying for a commercial radio license gripe about the questions devoted to batteries on the grounds that batteries are pretty much out of date. Apparently the army does not know about this, for a lot of their inventive needs are connected with batteries. For example they say they need a battery with a very long shelf life and one that will give a constant power output over a widely varying range of temperature; and to the army that means a range of from —100° F to 160° F above zero.

"They are particularly interested in a battery that will perform well at extremely low temperatures. For example, they would like a new electrolyte that could be substituted for the one ordinarily found in an automotive (lead-acid) battery that would have a low viscosity at -65° C and that would work well at this temperature without any damage to the battery. At the same time they would like to have a new miniature battery that would provide more service life per unit of volume and weight."

"How about the RM cells and the low-temperature batteries I've read about?"

"These are mentioned. It is stated the initial production of RM cells was spotty and that while some batteries gave good performance, others did not provide any useful life at all because of defects. My dad, who wears a hearing aid using these batteries, strongly seconds this opinion. He says that when you put in a fresh battery you can never be sure whether it is going to last two hours or two weeks. Low temperature batteries provide some life at -40° F, but not sufficient life to be of practical value. Incidentally, the army is willing to approach this problem from another direction. If you can think up a good way to heat drycells so that the full output can be obtained in extremely cold regions, the army would like to hear about it. They have already tried using heat tablets, activated charcoal blocks, sterno-type and chemical heaters without much success.

"How about the new solar and atomic batteries?"

"They show promise but are not suitable to field applications at their present stage of development. The army would very much like to have a new, efficient, compact, light, and quiet source of power to replace heavy batteries and noisy internal-combustion, engine-driven generators for front line use."

NEW 1955 HOLD HALL Engineering Features


New PRINTED CIRCUITS

One of the many tremendous improvements in the new 1955 Heath-kits is the use of an etched metal process printed circuit board. Printed circuits will be used in Heathkits whenever they will affect construction simplification, performance stabilization, and lend themselves to instrument design. Now for the first time a kit instrument company offers the advantages of modern printed circuit instrument construction technique. For the first time consideration has been given toward reducing kit assembly time. Also this is the first time that printed circuit heards have been hand soldered on a volume lossis. Offered only by Heathkit, the pioneer and leader in kit instrument design.



New PEAK-TO-PEAK VIVM CIRCUIT

New 6AL5 full wave rectifier in AC input circuit, permits full scale peak-to-peak measurements. Seven ranges — upper limits 4000 volts peak-to-peak. Just the thing you TV servicemen lave needed in making TV circuit voltage checks. Precision resistor voltage divider limits AC RMS level to 150 volts. Prevents overloading the rectifier—extends upper limit AC RMS ranges to 1500 volts—further protects meter and circuitry against AC flash-over or arcing. Another definite example of continuing Heathkit design leadership in the kit instrument field.

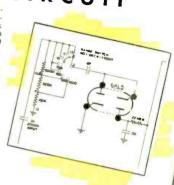

New HIGH READABILITY PANELS

New 1955 Heathkits feature complete panel redesign. Sharp white lettering applied to the beautiful charcoal gray panels, provide a new high in readability. Lettering is easyto-read open style and panel calibrations are vividly clear against the theming soft gray by



pleasing soft gray background. New knobs of exclusive Heathkit design,

New 3" UTILITY SCOPE

The new 3" Scope is a "natural" for the well rounded line of Heathkit instruments, Small in size, 1134" deep, 612 wide, 912 high, yet big in performance. Just think of the value an Oscilloscope for \$29,50. Brilliant intensity, sharp focusing, wide positioning range. An ideal portable Scope for the TV serviceman—a second shop scope — modulation monitor for you hans (deflection plate terminals in rear of cabine

terminals in rear of calbinet).

Performance to spare for all general scope applications. See specifications on fullowing page.




New STYLING New COLOR

New styling and coloring is responsible for tremendons improvement in Heathkit appearance. The new instrument panel color definition white lettering in a soft charcoal gray panel. Cabinet color is a lighter feather gray. The satin gold baked enamel cabinet for the WA-P2 Preamplifier is further indicat



for the WA-P2 Preamplifier is further indicative of the modern pacesetting trend in Heathkit styling.

New SCOPE SWEEP CIRCUIT

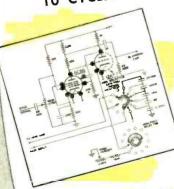

New 1955 Heathkit
Model 0-10 Scope features a new wide frequency range sweep generator covering 10 cycles
to 500.000 cycles. This
coverage is available in
five virtually decading
sweep ranges and is five
times greater than the
sweep frequency range
usually available. Excellent retrace time characteristics, actually less
than 20% at 500 KC.
Use of the free running
Heath circuit provides a
larger margin of stability
and a new high in Heathkit Scope performance.

Continuing PROGRESS FUTURE LINE EXPANSION The outstanding in....

The outstanding improvements featured in the 1955 Heathkit progress characterized by Heathkit progress characterized by Heath Company operation. Jong range planning w.h. pronew kit releases to further examples to further examples to further examples to the which greatest propresents the which greatest propresents the world's kits. The innovations in the additional new models schedyears.

SEE THE INSTRUMENTS ON THE FOLLOWING PAGES

HEATH COMPANY · · Benton Harbor 15, Mich.



Heathkit
VOLTAGE CALIBRATOR



KIT

MODEL VC-2

\$ 1150

Shpg. Wt. 4 lbs.

Another useful oscilloscope accessory particularly in circuit development work and in TV and radio service work. The Voltage Calibrator provides a convenient method for making peak-to-peak voltage measurements with an oscilloscope, by establishing a relationship on a comparison basis between the amplitude of an unknown wave shape and a known output of the voltage calibrator. Peak-to-peak voltage values are read directly from a calibrated panel scale without recourse to involved calculations.

FEATURES:

To off-set line voltage supply irregularities, the instrument features a voltage regulator tube. A convenient "signal" position on the panel switch by-passes the calibrator completely and the signal is applied through the oscilloscope vertical input, thereby eliminating the necessity for constantly transferring test leads.

RANGES:

With the Heathkit Voltage Calibrator it is possible to measure all types of complex waveforms within a voltage range of .01 to 100 volts peak-topeak. Build this instrument in a few hours and enjoy the added benefits offered only through combination use of test equipment.

Heathkit LOW CAPACITY PROBE KIT



No. 342 \$ 350

Shpg. Wt. 1 lb.

An oscilloscope accessory, the 342 Low Capacity Probe permits observation of complex TV waveforms without distortion. An adjustable trimmer provides proper matching to any conventional scope input circuit. Excellent for high frequency, high impedance, or broad bandwidth circuits. The attenuation ratio can be varied to meet individual requirements.

Heathkit
SCOPE DEMODULATOR
PROBE KIT
No. 337-C

0

\$ **3** 5.0

Shpg. Wt. 1 lb.

Extend the usefulness of your oscilloscope by observing modulation envelopes of RF or FF carriers found in TV and radio receivers. The Heathkit Demodulator Probe will be helpful in alignment work, as a gain analyzer and a signal tracer. Easy construction with the new modern printed circuit board. Voltage limits are 30 volts RMS and 500 volts D.C.

HEATH company

BENTON HARBOR 15, MICHIGAN "What else do they need?"

"Well, as an old treasure-locater builder, you may be interested to know the army still wants a device or technique that will positively detect the presence of explosives, as such, buried beneath the earth's surface. I don't think they would be much interested in that gadget you built that goes out after 'pieces-of-eight' and comes up with a roll of rusty fence wire. Along the same line they would like to have a rapid method by which they can determine the density of surface layers of soil to a depth of three feet in six-inch increments without taking actual samples. All attempts to do this electronically so far have failed. On a little different tangent, they would like to have a blasting cap that cannot be initiated by electromagnetic or radar waves."

"Anything else?"

"A lot else. There is need for a recorder that will work over a frequency range of from 5 to 1000 megacycles. A non-heterodyning type of frequency divider is wanted. So is a high voltage power supply that will put out 40,000 volts at up to 50 microamperes of current and yet will be so small and light that it will not add seriously to the burden of the man who must carry the electronic equip-ment this power supply operates. A microwave oscillator capable of 1 kw. of c.w. output is needed. The army would like to have a 12" cathode-ray tube in which the glass envelope is much lighter in weight, shorter, and more rugged. A coaxial r.f. switch of broadband characteristics to handle one to ten kw. of power is on the list. So is a frequency insensitive rotating joint for coaxial and waveguide circuitry.

"I'd like one of those myself for my ten-meter beam," Barney interrupted.

"Yes, and on Field Day you and the army both would like an ultra lightweight field antenna mast or radiator. say one that collapses to only 10 feet in length but that can be extended to any height up to 100 feet and that requires a minimum of guying, preferably none at all at lower extensions. The army would also like to have a coil impregnant that is cheap, easily applied, and unaffected by heat or humidity; and one that will not, on the other hand, affect the "Q" or the physical or electrical performance of the coil on which it is used. The military thinks it would be nice if someone would come up with a semi-conductor material for use in transistors whose color would reveal its conductivity type: n-type being one color and p-type being a different color. Do you get the idea?

"An indicator for carbon-monoxide gas is needed. So is a humidity indicator. So is a rugged, portable, lightweight ammeter that will be 20 to 100 times more sensitive than the conventional D'Arsonval type; yet no external power supply or electron tube amplifiers can be used to accomplish this."

NEW Heathkit 5" PUSH-PULL

OSCILLOSCOPE KIT

FOR COLOR TV

BRAND NEW DESIGN: The new Heathkit Model O-10 Oscilloscope would be something special at any price, but is almost unbelievable at \$69.50. Completely re-designed scope has broadfand amplifiers for color TV work and offers brilliant overall performance. Vertical frequency response within 5 db from 5 cps to 5 me. Even more astounding, the response is down less than 112 db at 3.58 mc, the color TV sync hurst frequency. It is essential that scopes for color work have these broadband characteristics.

PRINTED CIRCUITS: Two printed circuit boards used in this fine instrument to insure

stable, consistent performance. Problems solved by pre-engineering of boards, and their use guarantees completed unit that will have same characteristics as lab development model. Printed circuits simplify construction and save labor.


Simplified, standardized construc-tion technique of vertical and hori-zontal amplifier construction made possible through the use of a single printed circuit

NEW SWEEP CIRCUIT: Sweep circuit operates with exceptionally good linearity from 20 eps to over 500,000 eys, 5 times the usual range for scopes in this price range. An entirely new circuit intro-

duced for the first time in any Heathkit. FEATURES: Other outstanding characteristics of this professional oscilloscope are: Built-in 1V peak-to-peak reference for calibration of plastic CRT face-plate; 5" 5UP1 CRT; push-pull hor, and vert, deflec-

tion amplifiers; hor, trace width expandable to 3 times diameter of CR tube to allow inspection of any small portion of the signal; deflection sensitivity, .025 volts per inch; wiring harness pre-formed and cabled to save construction time and insure professional appearance and operation. Incorporates efficient retrace blanking. Frequency compensated step attenuator at the vertical input. Entire tube face useable. No foldover on vertical over-load. Performance obtainable only in much more expensive laboratory models

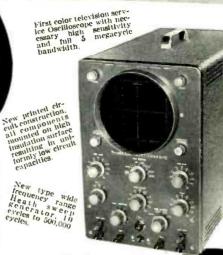Uses 5UPI, 6AB4, 6BO7, 12BH7, 6CB6, 12AT7, 2-12AU7, 6X1, 1V2, and 6C4, Quality components used throughout so that outstanding performance characteristics may be maintained for years to come. Plastic molded condensers are used in all coupling and by-pass applications. The "new-look" in Heathkit styling produces professional appearance in keeping with the professional performance of this instrument.



New electronic position-ing controls for instan-taneous, definite posi-tioning without bounce or overshoot.

MODEL O-10 Shpg. Wt. 27 lbs

New SUPI CR tube



Clean, open. under chassis construction and wiring. Possible only through use of pre-eabled wiring har-ness, and simplified printed circuit boards.

-61/2"

New compact utility Scope-light-weight-portable for service work.

Deflection plate terminals—ideal for ham transmitter modulation monitoring.

NEW Heathkit 3" PRINTED CIRCUIT

OSCILLOSCOPE KIT

MODEL OL-1

Shpg. Wt. 15 lbs.

New easy-to-hulld printed circuit board with high insulation factor.

New Heathkit instrument styling-eharcoal gray panel with high reada-bility white lettering.

New Heath twin triode sweep generator 15-100,000 cycle sweep.

EXCEPTIONAL VALUE: The brand new Model OL-1 Utility Oscilloscope is designed especially for portable applications so that outside servicemen or persons performing field tests can have the advantages of a scope available. Then too, it is ideal for home workshop, the ham-shack, or as an "extra" scope for the service slop. It is compact, light in weight,

91/2"

3GP1 CR TUBE

and surprisingly versatile in operation. An outstanding instrument for the price.

Front panel controls are "bench-tested" for case of operation and convenience. Printed circuit board used for constant circuit performance. Assembly time cut in half!

SPECIFICATIONS: Vertical amplifiers feature frequency response within 1 db from 10 eps to 100 ke, and within 5 Jb from 5 cps to 500 ke. Vertical sensitivity .2 volts per inch at

1 ke, with input impedance of 12 mmfd shunting 10 megohms.

Horizontal response within 1 db from 10 cps to 200 ke, and within 5 db from 5 cps to 500 kc. Hor, sensitivity, 25 volts per inch at 1 ke, input impedance of 15 mind shunting 10 megohins. Sweep generator covers 10 eps to 100.000 eps with stable positive lock-in circuit. Cathode follower input in both vert, and hor, amplifiers; push-pull vertical and borizontal deflection amplifiers; 3° CRT; electronic positioning controls for wide range of vertical and horizontal spot deflection; provision for internal and external syne; 60 cycle line sweep. New modern color styling and unusual performance make this instrument an outstanding value.

NEW Heathkit

5" PRINTED CIRCUIT

OSCILLOSCOPE KIT

MODEL OM-1

2050 Shpg. Wt.

VERSATILE INSTRUMENT: The Model OM-1 general purpose Oscilloscope represents an outstanding dollar value in reliable test equipment. Full 5 inch CRT. Printed circuit boards for ease of assembly, constant circuit characteristics, and

24 lbs.

rugged component mounting, includes all the design features necessary for servicemen, students, experimenters, radio amateurs, etc. Frequency response of amplifiers flat within 1 db from 10 eps to 100 ke, and down only db from 10 cps to 500 kc. Sweep generator range from 20 cps to 100,000 cps. Also features new Heathkit color styling with chargoal gray panel and high definition white lettering for readability even under subdued lighting

DESIGN FEATURES: A full-size, versatile oscilloscope at a price you can afford. Other features are: adjustable spot shape control; RF connections to deflection plates; direct coupled centering controls; external and internal sweep and syne; 60 cycle line syne; built in I volt peak-to-peak panel terminal reference voltage; professional appearance of cabinet, panel, and

SRPI CR TURE

HEATH company

BENTON HARBOR 15, MICHIGAN



The new Heathkit Multimeter is a "must" to complete the instrument lineup of any well equipped service shop. Here is an instrument packed with every desirable service feature, many of which are not found in other Multimeters. All of the measurement ranges you need or want. High sensitivity 20,000 ohms per volt AC.

* ADVANTAGES

Complete portability through freedom from AC line power operation—provides service ranges of direct current measurements from 150 microamps up to 15 amperes—can be safely operated in RF fields without impairing accuracy of measurement.

* RANGES

Full scale AC and DC voltage ranges are 0-1.5, 5, 50, 150, 500, 1500 and 5,000 volts. Direct current ranges are 150 microamps. 15, 150 and 500 milliamperes and 15 amperes. Resistances are measured from 2 ohms to 20 megobms in 3 ranges and db range from —10 to +65 db.

★ CONSTRUCTION

The Heathkit MM-1 features a unique resistor ring switch mounting assembly procedure. With this method of assembly the precision resistors are wired to the rings and range switch before actual mounting of the switch to the instrument panel. This procedure affords the advantage of simpler construction yet complete accessibility of precision resistors in event replacement are ever required. Ohm-meter batteries were selected for convenience of replacement and only standard commercially available types are used. Batteries consist of 1 type C flashlight cell and 4 Penlite cells. All batteries and necessary test leads are furnished with the kit.

Total of 35 meter

ranges on color scale.

Heathkit HANDITESTER KIT



MODEL M-1

Shpg. Wt. 3 lbs.

The Heathkit Model M-1 Handitester readily fulfills major requirements for compact, portable volt-ohm milliameter. The small size of the smooth gleameter which the leaf to one permits the

ing molded bakelite case permits the in-strument to be tucked into your coat pocket, toolbox or glove compartment of your car. Always the "Handitester" for those simple repair jobs.

RANGES:

Despite its compact size, the Handitester is packed with every desirable feature required in an instrument of this type. AC or DC voltage ranges, full scale, 10, 30, 300, 1,000 and 5,000 volts, 2 convenient ohumeter ranges 0-3,000 ohms and 0-300,000 ohms. 2 DC milliammeter ranges 0-10 milliamperes and 0-100 milliamperes.

CONSTRUCTION

CONSTRUCTION

The instrument uses a 400 microampere meter movement which is shunted with resistors to provide a uniform 1 milliampere load in both AC and DC ranges. This design allows the use of but 1 set of 1% precision divider resistors on both AC and DC and provides a simplicity of switching. A small hearing aid type ohms adjust control provides the necessary zero adjust function on the ohmmeter range. The AC rectifier circuit uses a high quality Bradley rectifier and a dual half wave hookup. Necessary test leads and battery are included in the price of this popular kit.

Heathkit RESISTANCE SUBSTITUTION BOX KIT

36 standard RTMA I watt. resistor values between 15 ohms and 10 megohms with an accuracy of 10% are at your fingertips in the Model RS-1 Resistance Substitu-tion Box kit. This sturdy and attractive accessory will easily prove its worth many times over as a time saving device. Order several today.



MODEL MM-1

Shpq. Wt. 6 lbs

Shpg. Wt. 2 lbs.

Heathkit CONDENSER SUBSTITUTION BOX KIT

18 standard RTMA values are available from .0001 mfd to .22 nifd. An 18 position switch set in the panel of an attractive bakelite case allows quick changes without touching the test leads. Invest a few minutes of your time now and save hours of work later on.



Shpg. Wt. 2 lbs.

HEATH company

BENTON HARBOR 15, MICHIGAN

"Looks like a spot to use transistors," Barney commented.

"Possibly. There is also a growing need for something to replace our diminishing supply of natural piezoelectric quartz. One possibility is the development of a high quality synthetic quartz. Another is the application of magnetostriction units to the control of frequency. Whichever is used, it must have an accuracy equal to that of natural quartz oscillators: approximately .02% within the temperature range of -65° to +160° F. We also need a new high resistance material with a resistance of at least 100 .-000.000,000 ohms per centimeter with a low temperature coefficient, good resistance to vibration and shock, capable of being formed into units with a resistance accuracy of 20%. These resistors are needed for use in radiation detection instruments."

"All that stuff is rather small caliber for an inventor of my type," Barney objected. "Don't they need some really big inventions?"

"Oh sure. They would like to have a complete new type of communication that does not depend on electrical impulses, electromagnetic waves, sound waves, or any other method known at present. That should hold you for a while. Then you can work on a new system for converting either light or heat into electrical energy. Of course the Bell Laboratories are kicking this around, too, but I am sure you like a little competition. On your day off you can play around with either a destructive ray that will produce death at 500 yards without excessive power input or with a device that will convert speech directly into writing. I think perhaps IBM has done some work on this, but the army wants a device that is simple to operate and is not bulky-which makes it quite a large order."

"I think I'll help the army out on a few of these things." Barney announced importantly. "Where do I submit my ideas or write for more information?

"Just address the National Inventors Council U. S. Department of Commerce, Washington 25, D. C.." Mac answered; "but before you start inventing, you had better figure out how you can get back into Amanda's good graces.'

"Don't worry about that; it's already taken care of." Barney said airily. "Tomorrow morning I intend to present her with the personally-autographed picture of Liberace I managed to have him sign when he played in Center City a couple of weeks back. Knowing how much she likes to hear him play, I got it especially for her; but I've been waiting to give it to her until the right moment arrived. Now I think it's here! If that doesn't melt

her down, nothing will."
"That's my boy!", grinned Mac. "Old Don Juan had nothing on you when it comes to being a smooth operator. I don't know how you do it-but six or sixty-the gals love it!" -30-

NEW Heathkit VACUUM TUBE .TMETER KIT

PRINTED CIRCUIT DESIGN


New charcoal gray baked charmed panel with high readability. white testering New soft feather gray cabl-net, subdued cable light indicator, pilot

new printed circust board for faster,
easter construction of
exact duplication of
exact duplication of
model.

Another outstanding example of continuing Heath Company pioneering and leadership in the kit instrument field. A new printed circuit VTVM. New peak-to-peak circuit—new styling and new panel design. A prewired, prefabricated printed circuit board eliminates chassis wiring, cuts assembly time in half, assures duplication of Engineering pilot model specifications, and virtually eliminates possibility of com-

CIRCUIT:

A 6AL5 tube operated as a full wave AC input rectifier permits seven peak-to-peak voltage ranges with upper limits of 4000 volts P—P. Just the ticket for you TV servicemen. Voltage divider in the 6AL5 input circuit limits applied AC input to a safe level. This circuitry and the isolation of the meter in the cathode of the 12AU7 bridge circuit affords a high degree of protection to the sensitive 200 microampere meter.

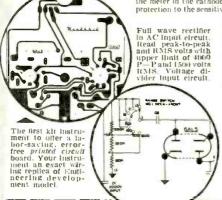

RANGES:


Seven voltage ranges, 1.5, 5, 15, 50, 150, 500 and 1.500 volts DC and AC RMS, Peak-to-peak ranges 4, 14, 40, 140, 400, 1400, 4000, Ohmmeter ranges X, 1X, 10, X100, X1000, X10K, X100K, X1 meg, Additional features are a 4h scale, a center scale zero position, and a polarity reversal switch.

IMPORTANT FEATURES:

IMPORTANT FEATURES:

High impedance 11 megohin input—transformer operated—1°-o precision resistors, 6AL5 and 12AU7 tube—selenium power rectifier—individual AC and DC calibrations—smoother improved zero adjust control action—new panel styling and color—new placement of pilot light—new positive contact battery mounting—new knobs—test leads included.

The new V-7 also sets the pace as a kit instrument style leader. Smart, good-looking charcoal gray panel and soft feather gray cabinet. High readability panel with sharply contrasting white calibrations. The pleasing, eye catching, modern styling is in harmonious balance with the outstanding circuit design improvements. Easily the best buy in kit instruments.

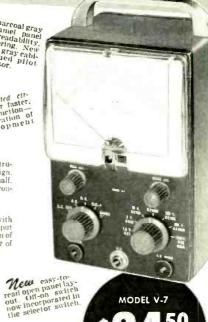

MODEL V-7 Shpg. Wt. 7 lbs.

Heathkit AC VACUUM TUBE

VOLTMETER

MODEL AV-2

Shpa. Wt. 5 1bs.

Extreme sensitivity has been emphasized in the design of the Heathkit AC VTVM. Ten full scale RMS ranges are .01..03.1, 3, 1, 3, 10, 30, 100, and 300 volts. Frequency response is substantially flat from 10 cycles per second to 50 KC with input impedance of 1 megohm at 1 KC. Will accurately measure as low as 1 millivolt at high impedance. Total dh range is -52

db to +52 db. An excellent kit for measuring the output of phono cartridges and the gain of amplifier stages. Use it also to check power supply ripple, as a sensitive null detector, and for compiling frequency response data. Features one knob operation, 200 microampere Simpson meter and precision resistors.

Heathkit 30,000 VOLTS DC

PROBE KIT

Measure up to 30,000 volts DC with the Heathkit VTVM and the 336 high voltage Probe. Precision resistor provides multiplication factor of 100. Can be used with any 11 megohm input VTVM. Housed in a Polystyrene two color sleek plastic probe body for safety of operation.

No. 336 \$450 Shog. Wt.

Heathkit PEAK-TO-PEAK PROBE KIT



\$550

Shpg. Wt. 2 lbs.

Peak-to-peak values not exceeding 80 volts at a DC level of not more than 600 volts. can now be read directly by using 338-C Probe with previous model Heathkit VTVM's or any VTVM with 11 megohm input resistance. Probe construction features a modern printed circuit board for easy assembly. Frequency range 5 KC to 5 MC.

Heathkit RF PROBE KIT

The Heathkit RF Probe will permit the measurement of RF voltages up to 250 MC with an accuracy of ±10%. The limits are 30 volts AC and a DC level of 500 volts. Designed for any 11 megohm input VTVM. Modern styling, Polystyrene aluminum housing, Polystyrene insulation, and printed circuit hoard for easy assembly.



No. 309-C \$350 Shpg. Wt.

Heathkit AUDIO WATTMETER KIT

Read audio power output directly without using external load resistors with the new Heathkit Audio Wattmeter. Built-in non-inductive load resistors provide impedances of 4, 8, 16, and 600 ohms. Flat response from 10 CPS to 250 KC. Full scale power ranges are 0-5 MW, 0-50 MW, 0-500 MW, 0-5 W and 0-50 W. Model AW-1 will operate continuously at 25 watts and has a duty cycle of 3 minutes at 50 watts. Total db range in five positions is -50 db to +48 db, using the standard 1 milliwatt 600 ohms.



MODEL AW-1

Shpg. Wt. 6 lbs.

HEATH company

BENTON HARBOR 15, MICHIGAN



"VADE-MECUM, TELEVISION & SPE-CIAL TUBES", Dr. J. A. Gijsen. ed., P. H. Brans, Ltd.. Antwerp. 244 pages. Price \$5.00. Paper bound. 11th Edition. Available in the U.S. from Editors and Engineers, Ltd., Summerland, California.

With this volume, the trilogy comprising radio tube characteristics (9th Edition), and equivalents (10th Edition) is complete. This book covers tubes for television and special purposes and includes data on cathode-ray tubes, crystal devices, controlled rectifiers, special u.h.f. tubes, gas discharge tubes, phototubes, radiation counters, thermocouples, ballast tubes, and various miscellaneous tubes.

For those not familiar with this work, it would be well to explain that the "Vade-Mecum" covers data on tube types manufactured by companies throughout the world, presented in tabular form, with explanatory material translated into German, French, English, Italian, Spanish, and Dutch.

Companies engaged in the manufacture of export model radio and TV receivers, service technicians who have occasion to service foreign-built equipment, amateurs converting surplus radio gear, etc. will all find this book an invaluable aid in providing equivalent tubes for all types of electronic circuitry.

"ANALYZING AND TRACING TV CIRCUITS" by Milton S. Kiver. Published by Howard W. Sams & Co., Indianapolis. 130 pages plus 14 TV receiver schematics. Price \$3.00. Paper bound.

Technicians who have found the author's previous volumes of help in speeding troubleshooting and servicing will welcome the appearance of this basic and hard-hitting handbook.

The book is especially suitable for the beginning technician since it covers basics before venturing into specific applications. The first chapter covers things that every technician should know about every circuit. In this category is information on resistors, inductances, capacitors, and tubes-what they do in the circuit, why they operate as they do, plus all sorts of valuable and important data on these components.

From this point of departure, the author buckles down to specifics and covers such vital topics as the differences between schematics and the actual sets, how to follow the d.c. power lines in a set, where the boost voltage fits in, the a.g.e. system, deflection systems, troubleshooting procedures in logical order, the unfamiliar circuit, etc.

A valuable appendix which gives the complete schematics on 14 commercial television receivers, completes the book. Readers of this magazine are

RADIO & TELEVISION NEWS

isolating such de-vicesfrom theline.

Many other uses, especially with AC-DC type cir-

cuits. Do not con-fuse the Heathkit Isolation Trans-former with the hazardous auto transformer type line voltage boosters.

MODEL IT-1

\$1650

Shpg. Wt.

urements circuits.

HEATH company

BENTON HARBOR 15,

MICHIGAN

NEW Heathkit **V ALIGNMENT GENERATOR**

Here is the most radically improved Sweep Generator in the history of the TV service industry. The basic design follows latest high frequency techniques which result in a combination of performance features not found in any other sweep generator.

Sweep action is obtained electronically through the use of a newly developed controllable inductor, thereby eliminating all moving parts with their resultant hum, vibration, fatigue, etc. Frequency coverage entirely on fundamentals, is continuous from 4 MC to 220 MC at an output level well over a measurable 1 volt.

Triple marker system, 4.5 MC crystal controlled marker—continuously variable marker—provisions for external marker.



MARKER:

The same instrument incorporates a triple marker The same instrument incorporates a triple marker system with a crystal controlled reference. A variable marker provides accurate coverage from 19 to 60 MC on fundamentals, and 57 to 180 MC on calibrated harmonics. A separate fixed crystal controlled 4.5 MC marker can be used for checking IF, bandpass, calibration, reference, etc. Provisions are also made for external marker use. A 4.5 MC crystal is emplied with the kit. supplied with the kit.

POWER SUPPLY:

The transformer operated Power Supply features voltage regulation for stable oscillator operation. Three sets of shielded cables are furnished with the kit. Sweep range is completely and smoothly controllable from zero up to a maximum of 50 MC, depending upon base frequency.

Here is a TV Sweep Generator that truly no serviceman can afford to be without for rapid, accurate, TV alignment work.

Frequency coverage: 4 MC— 220 MC continuous including FM superrum. HF output well over 1 volt.

Controllable inductor sweep oscillator with out-put entirely on funda-

mentals.

NEW Heathkit SIGNAL GENERATOR KIT



MODEL SG-8

Shoa Wt 8 lbs.

The new Heathkit service type Signal Generator. Model SG-8 incorporates many design features not usually found in this instrument price range. Frequency coverage is from 160 KC to 110 MC in five ranges, all on fundamentals, with useful calibrated harmonics up to 220 MC. The RF output level is well in excess of 100,000 microvolts throughout the frequency range. The oscillator circuit consists of a twin triode tube, one-half used as a Colpitts oscillator, and the other half as a cathode follower output which acts as a buffer between the oscillator and external load, thereby eliminating oscillator frequency shift usually caused by external loading.

All coils are factory wound and adjusted, thereby completely eliminating the need for individual calibration and the use of additional calibrating equipment. The stable, low impedance output, features step and variable attenuation for complete control of RF leyel. A separate 6C4 triode acts as a 400 cycle sine wave oscillator, and a panel mounted switching system permits choice of either external or internal modulation.

NEW Heathkit BAR GENERATOR KIT



MODEL BG-1

Shpq. Wt. 4 lbs.

The Heathkit BG-1 produces a series of horizontal or vertical bars on a TV screen. Since these bars are canally spaced, they will quickly indicate picture linearity of the receiver under test without waiting for transmitted test patterns. Panel switch provides "standby—horizontal and vertical position." The oscillator and video carrier frequencies. A neon relaxation oscillator provides low frequency for vertical linearity tests. The instrument will also provide an indication of horizontal and vertical sync circuit stability as well as overall picture size. Operation is simple and merely requires connection to the TV receiver antenna terminal. Transformer operated for safety.

Heathkit LABORATORY GENERATOR KIT

The new Heathkit Laboratory type Signal Generator definitely establishes a new performance standard for a kit instrument. An outstanding feature involves the use of a panel mounted 200 microampere meter calibrated both in microvolts and percent modulation, thereby providing a definite reference level for using the Signal Generator in design work, gain measurements, selectivity, frequency response checks. he new Heathkit Laboratory type



MODEL TS-3

Shoo, Wt. 18 lbs

50

Triple marker system 4-5 MC crystal controlled—3 sets of low capacity shielded cables included.

MODEL LG-1

7050

Shpg. V/t. 16 lbs.

DESIGN:

Additional design features are copper plated shield enclosure for oscillator and buffer stages resulting in effective double shielding. Fibre panel control shaft extensions in RF carrying circuits, thorough AC line filtering, careful shielding of the attenuator network, voltage regulated B plus supply, selenium rectifier, etc.

RANGES

Frequency coverage from 150 KC to 30 MC all on fundamentals in five separate ranges. Output voltage 1 volt with provisions for metered external or internal modulation. Output impedance termination 50 ohms. Transformer operated

Investigate the many dollar stretching features offered by he LG-1 before investing in any generator for Laboratory

HEATH company BENTON HARBOR 15. MICHIGAN

December, 1954



The new Heathkit Visual-Aural Signal Tracer features a special high gain RF input channel used in conjunca special high gain RY input channel used in conjunc-tion with a newly designed wide frequency range de-modulator probe. High RF sensitivity permits signal tracing from the receiver antenna input. Separate low gain channel and probe available for audio circuit exploration. Both input channels are constantly monitored by an electron ray beam indicator so that visual as well as arral indications may be obtained.

NOISE LOCATOR:

Signal tracing. A decidedly unusual feature is a noise locator circuit used in conjunction with the audio probe. With this system, a DC potential is applied to a suspected cir-cuit component and the action of the voltage in the component can be seen as well as heard. Invaluable for ferreting out noisy or intermittent condensers, noisy resistors, controls, IF and power transformers, etc.

WATTMETER:

Built-in calibrated wattmeter circuit will prove useful for quick preliminary check of total wattage consumption of equipment under test. Separate panel terminals provide external use of the speaker or output transformer for substitution purposes. Saves valuable service time by climinating the necessity for speaker removal on every service job. The same panel terminals also provide case access to a well filtered B plus supply for external use. Don't overlook the many interesting service possibilities provided through the use of this instrument, and let the Signal Tracer work for you by saving time and money.

Heathkit CONDENSER CHECKER KIT



MODEL C-3

\$1950 Shpg. Wt.

Here is a handy test instrument for any Service Shop. Unknown values of capacity and resistance are quickly determined on the direct reading condenser checker dial. Capacity is measured in four ranges from .001 mfd to 1000 mfd. Resistance in the range

Substitution test

MODEL T-3

speaker amplifier.

RF and andio probes supplied along with necessary test leads.

from 100 ohms to 5 megohms.

DC polarizing voltages of 25, 150, 250, 350, and 450 volts are available for leakage tests on all types of condensers. For electro-lytics, a power factor control is provided to balance out inherent leakage and to indicate directly the power factor of a condenser under test. Proper balancing of the AC bridge is reflected in the degree of closure of an electron beam indicator tube.

Model C-3 uses a transformer operated power supply, spring return leakage test switch, and a convenient combination of panel seales for all readings. Test leads are furnished in addition to precision components for calibrating purposes. Quick and easy to operate, the Heathkit Condenser Checker will save valuable time and increase your Shop efficiency.

Heathkit "Q" METER



MODEL QM-1

Shpg. Wt. 14 lbs.

The Heathkit QM-1 represents the first practical popular priced Q meter available within the price range of schools, laboratories. TV service men, and experimenters. This instrument will enable the operator to simulate conditions encountered in practical circuits and to measure the performance of coils or condensers at the operating frequencies actually encountered. All indications of value are read directly on the 412" 50 microampere Simpson calibrated meter scale. Measures Q of condensers. RF resistance, and the distributed capacity of coils. Oscillator section

supplies RF frequencies 150 KC to 18 MC in four ranges. Calibrate capacity with range of 40 MMF to 450 MMF with vernier of ±3 MMF. Investigate the many services this instrument can perform for you.

Heathkit AUDIO OSCILLATOR

MODEL AO-1 \$2450

Shpg. Wt.



The Heathkit Audio Oscillator will produce both sine and square waves within the frequency range from 20 CPS to 20 KC in three ranges. Thermistor controlled linearity results in a variation of no more than ±1 db in a 10 volt (no load) variable output level. There will be less than .6% distortion from 100 CPS throughout the audible range. Low impedance 600 ohm output. Precision 1% resistors, used in the range multiplier circuits to provide accurate calibration.

HEATH company

BENTON HARBOR 15, MICHIGAN

familiar with Mr. Kiver's lucid style and comprehensive approach to the problem. This text conforms to the author's usual high standard of technical excellence and understandability and is, therefore, recommended as a valuable and indispensable servicing

"HIGH FIDELITY" compiled by Trend Staff. Published by Trend Incorporated, Los Angeles. 127 pages. Price \$.75. Paper bound.

This is a non-technical discussion of high-fidelity equipment prepared for the layman-music lover.

It represents a compilation of articles prepared by various authorities in the field. There are fourteen chapters devoted to such subjects as high-fidelity, the cost of a hi-fi system, how hifi works, home music installations, the loudspeaker system, amplifiers, broadcast music, magnetic recording, records, how to install a hi-fi system, modernizing radio-phonographs, available "do-it-yourself" kits, hi-fi for the car, and hi-fi definitions in addition to all sorts of miscellaneous but important audio data.

The book is beautifully illustrated with photographs of actual installations, available commercial equipment, etc. in addition to line drawings of suitable enclosures, system layouts, etc.

Those interested in hi-fi reproduction from a layman's point of view will find this book wonderfully helpful and remarkably complete.

"THE OSCILLOSCOPE" by George Zwick. Published by Gernsback Publications. Inc., New York. 187 pages. Price \$2.25. Paper bound.

The widespread acceptance of television has made the oscilloscope one of the truly essential tools of the technician. To fully understand this instrument and its function requires more of the technician than just a casual perusal of the instruction manual accompanying his scope.

This handbook is intended to supplement and enlarge on the material contained in such manuals as it covers the "how's" and "why's" of scope operation and application.

The book is divided into eight chapters, the first four of which are basic discussions of waveforms, the CR tube, sweep systems, and typical scopes. The balance of the book is devoted to specific application data and covers alignment, scope techniques, tests and measurements which can be made with the scope, and experiments using the scope.

The text is written in simple, easyto-understand form and is lavishly illustrated with line drawings, photographs, and schematic diagrams.

Those attempting to service TV receivers without a thorough-going understanding of their most valuable ally, the scope, would do well to study this manual carefully in order to derive the maximum benefit from this indispensable tool. -30 -

Heathkit TUBE CHECKER

The Heathkit TC-2 Tube Checker was primarily designed for the convenience of radio and TV servicemen and will check the operating quality of tubes commonly encountered in this type of work. Test set-up procedencountered in this type of work. Test set-up procedure is simplified, rapid, and flexible. Panel sockets accommodate 4, 5, 6, and 7 pin tubes, octal and loctal, 7 and 9 pin miniatures, 5 pin Hytron, and a blank socket for new tubes. Built-in neon short indicator, individual 3-position lever switch for each tube element, spring return test switch, 14 filament voltage ranges, and line-set control to compensate for supply voltage variations, all represent features of the TC-2.

Simplified construction—new harness type wiring—closer tolerance resistors.

MODEL TC-2

Improved smooth running roll chart mechanical action.

Heathkit PORTABLE TUBE CHECKER KIT

The portable model is supplied with a strikingly attractive two-tone cabinet finished in rich maroon proxylin impreg-nated fabric covering with a contrasting gray on the inside of the detachable cover.

MODEL TC-2P

Shpg. Wt. 15 lbs.

Results of tube tests are read directly from the large 41/2" Simpson 3-color meter. Checks shorted elements, open elements, open tinuity. Wiring procedure and continuity. Wiring procedure has been simplified through the use of multi-wired color coded cable pro-

ishes detailed information regarding tube set-up procedure for testing of new or unlisted tube types. No delay neces-sary for release of factory data.

Sile that Color Good weler Shpg. Wt. 12 lbs. viding a harness type installation between tube sockets and lever switches. This procedure insures standard assembly and imparts a "factory built" appearance to the instrument. New Construction Manual furnation of the instrument.

Heathkit

REGULATED **POWER** SUPPLY KIT



250

Shpg. Wt 15 lbs.

Here is a source of regulated D.C. voltage for circuit development work. Power supply voltage and current drain to the circuit under test are constantly monitored by the $\frac{1}{2}$ panel mounted meter. Separate 6.3 volt at 4 ampere A.C. filament source available. The regulated and variable output voltage will be constant over wide load variations, and hum ripple will not exceed .012% at 250 volts under a 50 MA load. Completely isolated circuit, standby switch, and other desirable features, make the Model PS-2 extremely useful in a wide variety of applications

Heathkit AUDIO GENERATOR KIT

Here is an Audio Generator with features generally found only in the most expensive instruments. Sine wave coverage from 20 cycles to 1
Megacycle—response flat ±1 db
from 20 cycles to 400 Kc—continuously variable and step attenuated
output. Because the output voltage is relatively constant over wide frequency ranges, the AG-8 is ideal for running frequency response curves in audio circuits. Once set by means



MODEL AG-8

Shpg. Wt. 11 lbs.

of the attenuator, this voltage may be relied upon for accuracy within ± 1 db. Instrument features low impedance 600 ohm output circuit and distortion less than .4 of 1% from 100 CPS through audible range.

Heathkit TV PICTURE TUBE TEST ADAPTER

The Heathkit TV Picture Tube Test Adapter used with the Heathkit Tube Checker Kit, will quickly check picture tubes for emission, shorts, etc. and determine tube quality. Consists of standard 12-pin TV tube socket, four feet of cable, octal socket connector, and data



No. 355

\$450 Shpg. Wt.

Heathkit DECADE RESISTANCE KIT

MODEL DR-1 Shpg. Wt.

Twenty 1% resistors are decaded in 1 ohm steps to provide any value between 1 ohm and 99,999 ohms. Sturdy ceramic switches with silver plated contacts insure reliable service. Use the Decade Resistance in bridge circuits, meter multipliers, calibrations, or any application requiring a wide range of precision resistance values.

Heathkit DECADE CONDENSER KIT

The Heathkit Decade Condenser provides a ready source of capacity values from 100 mmf to .111 mfd inclusive in capacity steps of 100 mmf. Silver plated contacts on husky ceramic switches, assure positive contact for each switch position. Precision silver mica con-

sion silver mica con-densers ± 1% accu-racy for close tolerance accurate

Shpg. Wt. 3 lbs.

HEATH company

BENTON HARBOR 15, MICHIGAN

NEW Heathkit HIGH FIDELITY REAMPLIFIER KIT

Here is the exciting new Heathkit Preamplifier with all of the features Cathode tollower low hard you Audiophiles have asked for and at a down-to-earth price level. pedance output learn gold baked enamel finish, striking controlled to the features of the design.

DESIGN:

Uses three twin triode tubes in a shock mounted chassis, 2-12AX7 and 1-12AU7. Features tube shielding, plastic sealed color coded capacitors, smooth acting controls, good filtering, excellent decoupling, low hum and noise level, and all aluminum cabinet. Special balancing control for absolute minimum hum level. Cathode follower, low impedance output circuit for complete installation flexibility.

SPECIFICATIONS:

Single knob band switching bre-wound colls.

Provides five switch selected inputs, 3 high level, and two low level, each with individual level controls—4 position LP, RIAA, AES, and early 78 equalization switch—4 position roll-off switch, 8, 12, 16 with one flat position. Separate tone controls, bass 18 db boost and 12 db cut at 50 CPS, treble 15 db boost, and 20 db cut at 15,000 CPS. Power re-

Equalization for I.P. RIAA. AES, and early 78. Separate hass and treble control. Five switch selected inputs with unividual tevel controls. Beautiful, modern appearance, blends with any interior color scheme.

quirements from Heathkit Williamson Type Amplifier power supply 6.3 volts AC at 1 am-pere, and 300 volts DC at 10 MA. Over-all dimensions 12% widex 5% deep x 3% high.

APPLICATION:

APPLICATION:

The new Heathkit WA-P2 Preamplifier has been designed to operate with any of the Heathkit Williamson Type Amplifiers and is directly interchangeable with the previous Model WA-P1 Preamplifier unit. Order your kit today and enjoy completely smooth control over the operation of your Hi-Fi system.

Obtain the exact tonal balance of bass and treble with the precise degree of equalization you want. Note that the design of the WA-P2 accommodates the newly established RIAA curve.

Copper plated chassis-ainminum cabinet-casy to build.

MODEL WA-P2

EQUIPMENT

Heathkit AMATEUR TRANSMITTER KIT

The Heathkit AT-1 Transmitter has established a high reputation and has been enthusiastically accepted by hundreds of experienced operators as well as beginners. Power in you up to 35 watts for the novice and suitable as a standby exciter for your higher powered right atron.

MODEL AT-1

\$2950

Shpg. Wt. 16 lbs.

Brand NEW

HEATHKIT

The new Heathkit VFO is the perfect companion to the Heathkit Model AT-1 Trans-

the perfect companion to the Heathkit Model AT-1 Transmitter and it has sufficient output to drive any multi-stage transmitter of modern design. Good mechanical and electrical design insures operating stability. Coils are wound on stable, heavy duty, ceramic forms using Litz or double cellulose wire coated with Polystyrene cement and baked for humidity protection. Variable capacitor of differential type construction, especially designed for maximum bandspread. Kit is furnished with a carefully precalibrated scale which provides well over two feet of scale length. Smooth acting vernier reduction drive and illuminated dial provides easy tuning and zero beating.

Power requirements 6.3 volts AC at .45 amperes, and 250 volts DC at 15 mils. Just plug it into the power recentacle provided on the rear of the AT-1 Transmitter. Seven band coverage 160 through 10 meters with 10 volt average RF output. Uses 6AU6 electron coupled Clapp oscillator and OA2 voltage regulator.

Heathhit ANTENNA



Heathkit

GRID DIP METER KIT

The invaluable instrument for Hams, servicemen and experimenters. Useful in TV service work, for alignment of traps, filters, 1F stakes, peaking compensation networks, etc. Locates spurious oscillation, provides a relative indication of power in transmitter stages. Use if or neutralization, locating parasities, correcting TVI, measuring CI, and Q of components, and determining RF circuit resonant frequencies. The variable meter sensitivity control, healphone jack, 500 microampere Simpson meter, continuous frequency coverage from 2 MC to 250 MC. Prewound coil kit and rack included.

LOW FREQUENCY COILS:

Low frequency range extended to 355 KC by the use of two additional coils. Complete with dial correlation curves. Set 341-A for GD-1B and set 341 for GD-1A. Shipp, wt. 1 lb. Price 53.00



MODEL GD-1B \$**]Q**50 Shpg. Wt. 4 lbs.

IMPEDANCE METER KIT \$1450 Shpg. Wt.

MODEL AM-1 Determine antenna resonance and resistance, Determine antenna resonance and resistance, transmission line surse impedance, and receiver input impedance. Works with one-half and one-quarter wave lines, half wave and folded dipoles, harmonic mobile and beam antennas. Resistance type SWR bridge—100 microampere meter—frequency range 0–150 MC—impedance range 0–600 ohms.



MODEL AC-1

\$1450

Shpg. Wt. 4 lbs.

Heathkit ANTENNA COUPLER

For the Heathkit AT-1 Transmitter or any comparable Amateur Trans-For the Heathkit A1-1 transmitter of any comparative Amatein Transmitter. Will handle power up to 75 watts at its 52 ohm coaxial input. Matches a wide range of antenna impedances with its L type tuning network and neon indicator. A tapped inductance provides coarse adjustment and a transmitting type variable condenser sets it "right on the nose." Will operate on the 10 through 80 meter bands. **HEATH** company

BENTON HARBOR 15, MICHIGAN

New LOW PRICED HEATHKIT SINGLE UNIT Williamson Type High Fidelity

AMPLE R

Rugged, heavy duty, single chassis con-struction. Standard brand com-ronents used. Be sacrifice of quality. Send for free booklet High Fidelity Especially For You," Lowest price high quality Williamson Type Amph-tier ever offered.

Here is the newest Heathkit Hi-Fi Amplifier at the lowest price ever quoted for a complete Williamson Type Amplifier circuit. The W-4 Model has been designed for single chassis construction, and only for the new Chicago Transformer Company Model BO-13 "super range" high fidelity output transformer. This transformer, a new development in the Hi-Fi field, is being offered at substantial saving over transformers of comparable quality. It is outstanding in performance and on the basis of our tests, we find it equal in every respect to transformers used in the W-2 and W-3 Heathkit series.

Through utilization of a single chassis with resultant economy obtained through elimination of duplicate sheet metal fabrication, connecting cables, pluss, sockets, and a new Chicago "super range" output transformer, a 20% price reduction has been made possible without sacrificing kit quality.

COMPONENTS:

The new Heathkit W-4 uses the same heavy duty power transformer and choke. It has all of the features of previous models including individual jacks and a wire wound control to balance the output tubes—plastic high quality capacitors and the exact circuitry previously utilized in Williamson Type Amplifiers, Intermodulation distortion and harmonic distortion are both at the same low level as in the W-2 and W-3 models.

Here is the opportunity for even the economy minded Hi-Fi enthusiast to enjoy all of the advantages offered through Hi-Fi reproduction of fine recorded music. Simplified step-by-step Construction Manual completely eliminates necessity of electronic knowledge or special equipment. Assemble this Amplifier in a few pleasant hours.

COMBINATIONS AVAILABLE

W-4M with Chicago "super-range" transformer only. Single chassis main amplifier and power supply. Shipping \$39.75 weight 28 lbs. Express only

COMBINATION W-1 with Chicago "super-range" transformer only includes single chassis main amptifier and power supply with WA-P2 preampiliter SEO EA kit. Shpg. wt. 35 lbs. Express only \$59.50

NEW Heathkit 20 WATT High Fidelity AMPLIFIER KIT



MODEL A-9B

In keeping with the progressive policy of the Heath Company, further improvement has been made in the already famous Heathkit High Fidelity 20 Watt Amplifier. Additional reserve power has been obtained by using a heavier power transformer. A new output transformer designed and manufactured especially for the Heath Company, now provides output impedances of 4, 8, 16 and 500 ohms. The harmonic distortion level will not exceed 1% at the rated output.

FEATURES.

Outstanding features of the Heathkit Outstanding features of the Heathkit 20 watt Amplifier include frequency response of ±1 db from 20 CPS to 20 KC. Separate (hoost and cut) bass and treble tone controls. Four switch selected input jacks and a special hum balancing control. Flexibility is emphasized in the input circuits and proper equalization for all input devices is incorporated.

12AX7 magnetic preamplifier and first audio amplifier. 12AU7 two stage amplifier with tone controls. 12AU7 voltage amplifier and phase splitter. Two 6L6 push-pull beam power output and 5U4G rectifier. The Heathkit Model A-9B is excellent for custom installation and is designed for outstanding service at a very reasonable cost.

Heathkit SIX WATT

AMPLIFIER KIT



MODEL A-7B

Shpg. Wt. 10 lbs.

An outstanding value, this economically priced 5 watt Amplifier is capable of performance expected only in much more expensive units. Only 2 or 3 watts output will ever be used in normal home applications and Model A-7B will be more than adequate for this purpose.

SPECIFICATIONS:

Two switch selected inputs are available for crystal and ceramic phono pickups, tuner, TV audio, tape recorder, and carbon type microphone. Model A-7B features separate bass and treble tone controls, push-pull balanced output stages, output im-

pedances of 4, 8, and 15 ohms, and extremely wide frequency range ±1½ db from 20 CPS to 20 KC. Not just a souped up ACDC job. Full wave rectification, transformer operated power supply and good filtering, result in exceptionally low hum level.

MODEL A-7C

Provides a preamplifier stage and proper compensation for the variable reluctance cartridge and low level microphone. \$17.50

Heathkit WILLIAMSON TYPE AMPLIFIER KIT

Here is the famous kit form Williamson Type high fidelity Amplifier that has deservedly carned highest praise from every strata of Hi-Fi music lovers. Virtually distortionless, clean musical reproduction, full range frequency response, and more than adequate power reserve.

OUTPUT TRANSFORMERS:

This outstanding Williamson Type Hi-Fidelity Amplifier is supplied with the famous Acrosound TO-300 output transformer. This quality transformer features the popular "ultra-linear" output circuit for clean maximum power level. Separate chassis for amplifier and power supply.

SPECIFICATIONS:

Frequency response within 1 db from 10 cycles to 100,000 cycles. Harmonic distortion at 5 watt output less than .5% between 20 cycles and 20,000 cycles. IM distortion at 5 watts equivalent output .5% using 60 and 3,000 cycles. Output impedances of 4, 8, or 16 ohms. Overall dimensions for each unit 7" high x 5½" wide x $11\frac{1}{2}$ " long.

CONSTRUCTION MANUAL:

This fine kit is supplied with a completely detailed step-by-step Construction Manual and the only effort required is the assembly and wiring of the pre-engineered kit. Even the complete novice can successfully construct this Amplifier and have fun building it.

COMBINATIONS AVAILABLE:

W-3 Amplifier Kit (Includes Main Ampli-

W-3M Amplifier Kit (Includes Main Amplifler with Acrosound Output Transformer and Power Supply.) Shipping \$49.75



HEATH company BENTON HARBOR 15,

MICHIGAN



Heathkit FM TUNER KIT

MODEL FM-2

Shpg. Wt. 8 lbs.

Here is an FM Tuner that can be operated with your Hi-Fi Amplifier or through the "phono" section of the ordinary radio. Completely AC operated to eliminate problems usually encountered in "economy type" AC-DC tuner circuits. Peatures 8 tube circuit with separate mixer and oscillator, 3 double tuned IF stages followed by a limiter discriminator providing maximum sensitivity and selectivity across the full FM frequency band of 88 MC to 108 MC. The tuning unit is factory assembled and adjusted, thus eliminating tedious critical "front end" alignment problems. The attractive slide rule dial and vernier tuning combine to make the Heathkit FM-2 Tuner simple to operate.

Heathkit communications RECEIVER KIT

An excellent example of typical Heath Company ability to produce top quality kit merchandise at ridiculously low prices, is the AR-2 Communications Receiver. Here is a transformer operated all-wave receiver with all of the desired features and none of the disadvantages commonly encountered

wave receiver with all of the desired features and none of the disadvantages commonly encountered in so-called "ceonomy sets."

Receiver employs high gain miniature tubes and 1F transformers, chassis mounted 5½2" PM speaker, headphone jack, slide rule dial with Ham Bands plainly identified, and easy tuning with direct planetary drive. Continuous frequency coverage from 550 KC to 35 MC on 4 Bands, with electrical landspread tuning and logging scales. Other features are RP gain control with AGC on-off switch—phone-standby-CW panel switch—prewound coils in a shielded turret assembly and copper plated chassis and shielding.

Uses 12BE6 mixer-oscillator, 12BA6 1F amplifier, 12AV6 detector-first audio, 12A6 beam power output, 12BA6 BFO oscillator, and 5Y3 rectifier. A lettered control plate is provided for the cabinet of your choice or you can order the optional Heathkit cabinet featuring the full size aluminum panel.

Proxylin Impregnated fabric covered plywood cabinet available for BR-2 and AR-2 receivers. Includes aluminum panel, flocked reinforced speaker grill and protective rubber feet. For BR-2 Receiver, Cabinet 91-9 Shipping weight 5 lbs.

AR-2 Receiver, Cabinet 91-10 Shipping weight 5 lbs.

\$4.50

Heathkit

BROADCAST BAND RECEIVER KIT

The Model BR-2 Broadcast Band Receiver is designed The Model BR-2 Broadcast Band Receiver is designed especially for the beginner without any sacrifice of quality. This receiver features a transformer operated power supply, high gain miniature tubes, sharply tuned IF transformers, new rod type built-in antenna, and a trouble-free planetary tuning system. Exceptional performance with unusually high sensitivity, good selectivity, and excellent tone quality from the 5½° PM chassis mounted speaker. Can be used either as a receiver, tuner, or phone amplifier, Uses 121E6 mixeroscillator, 12BA6 IF amplifier, 12AV6 detector, 12A6 beam power output, and 5Y3 rectifier.



MODEL BR-2

(Less Cabinet) Shpg. Wt. 10 lbs.

EATH COMDANY

II E A I II				V III I	М						
HEAT	YOUR ORDER DAY TO THE H COMPANY ON HARBOR 15, MICHIGAN	From	O R	D	E		B	LA	N	K	SHIP VIA Parcel Post Express Freight Best Way
QUANTITY				ITEM		PLEAS	e PRINI)	,	MOL	DEL NO.	PRICE
Enclosed find () check Please ship C.O.D. () p	() money order for ostage enclosed for	pounds.		On Exp	oress ord press age	ers do not ency at time	include tr of delive	ansportation ry.	charges—	they will t	e collect <mark>ed</mark> by
ON PARCEL POST OF	RDERS insure postage f	or w <mark>eig</mark> ht <mark>sh</mark> own			ORDE	RS FROM	CANAD	A and AP	O's must	include	full remittance.

TV Color Converter

(Continued from page 39)

ed. Finally, the r.f. wiring was put in place.

Important: All resistors earrying fairly heavy loads were grouped on terminal strips below the power supply section, as far from tuned circuits as possible, to avoid the possibility of heat causing detuning of circuits. This is a vital matter in a color set because detuning and accompanying shift will cause color contamination.

The crystal is mounted alongside the chassis where it is out in the open and "runs cool"—again to avoid frequency shift

The heavy black lead which loops around under the chassis is the delay line. Fig. 9 shows how this component is constructed from a 23-inch piece of RG-59 U coaxial cable. As shown, the center wire lead, and its polyethylene sheath, is pulled from the cable, leaving only the metal braid and its plastic cover. These two pieces serve as the foundation of the delay line. First, they are slipped temporarily over a metal rod to provide sufficient stiffness for winding. This winding, which should be put on accurately with a lathe, is made of No. 36 enameled wire. It is wound for a length of 22 inches, 128 turns-per-inch. As shown in the drawing, the leads connect to opposite ends of this coil winding. The winding itself is covered with a layer of very thin dielectric paper (pulled from old condensers) and this, in turn, is covered with a layer of aluminum foil. The latter is grounded to the inside braid as shown in the drawing, being eareful not to short the winding to the grounding foil. Tape completely.

Wiring a set as complicated as this is a job in which even an expert can



Fig. 9. Details on the construction of the time delay line used in the Y channel. The line is made from a piece of coaxial cable from which the center conductor has been removed and an external winding added.

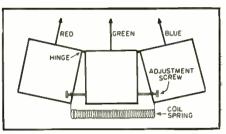


Fig. 10. Three TV projection units can be set up as shown here and used with the converter to give colored TV pictures.

go astray. One bit of insurance is to tape a piece of vellum (a kind of semitransparent drawing paper available at any art store or engineering supply house) over the diagram, and then draw in each lead with a colored pencil as it is done. This process is a little tedious—but not as tedious as trouble-shooting for built-in errors. Once the set is wired, the chassis can be given a rough check by comparing pin voltages with those shown in the diagram of Fig. 3.

When the color chassis is completed, the next step is to tie it to the *Norelco* projection units. These are the standard type, readily available from electronic parts jobbers. The hook-up requires three.

As shown in Figs. 10 and 11, the units are mounted side by side, as elose together as possible, with hinges between them. Then the chassis are

Fig. 11. Front view of the three projection units set up for use with the color converter described in this article. Color filters made of Plexiglas are mounted directly in front of each projector. Touch-ups are provided for registration.



December, 1954

DON'T THROW OLD RADIOS AWAY! Let this big handbook show you EXACTLY HOW TO FIX THEM fast and r-i-g-h-! THE ONLY GUIDE OF ITS KIND!

A, A. GHIRARDI

Covers every model made by 202 mfrs. from 1925 to 1942

> Airline Apex Arvin Atwater Kent **Belmont** Bosch Brunswick Clarion Croslev Emerson Fodo G-E Kolster Majestic Motorola Philco Pilot RCA Silvertone Sparton Stromberg . and over a

hundred more!

There's a "secret" to fixing old radios tast and profitably ... and Ghirardi's big 741-page, manual-size RADIO TROUBLE-SHOOTER'S HANDBOOK is it!

SHOOTER'S HANDBOOK is it?
No other guide like it? Gives common trouble symptoms and remedies for over 1,800 models of old home receivers, autoradios and record changers. Contains tube and component data, charts, circuits, etc., available from no other source.

Even beginners can handle jobs slick as a whistle. Makes to repair old sets for which specifications and how-to-fix-it data are no longer available. Just look up the model you want to fix. Four times out of 5, this giant Handbook leads you right to the trouble shows exactly how to fix it. No useless testing. No guesswork. You repair sets in a jiffy that would otherwise go to the junk pile because no me knows what to do with them.

to do with them.

There are over 400 pages of troubleshooting and service case histories. In audition, you get over 300 pages of helpful 1-F transformer dati; superhet reallgiment data and alignment peaks; handy troubleshooting reminder charts; auto radio gear ratios; complete data and characteristics on old tinle types and components; to es substitution data... and dozens of other invaluable service tips and ideas.

. _ PR /	ACTI	CE	10	DA	rs -	FR	EE!

Dept. RN-124, RINEHART & CO., INC. 232 Madison Ave., New York 16, N. Y.

send Ghirardi's RADIO TROUBLESHOTERS HAND-BOOK for 10-day free samination. If I decide to keep book, I will then send \$6.50 office postage in full payment, Otherwise I will return 50 ok postpiel and owe you nother?

Na							 		٠		,	
3, 1(1)	~ 7											

Or, Zore, 81d
Of PSIDICA STRUCTURE of the Mark of the Structure of a 10 days



Strong steel cup with a soft metal or plastic insert which can be quickly fitted to your present hammer and held firmly in place by taut steel coil-spring as shown.

WALDEN

STEVENS WALDEN Inc.

450 SHREWSBURY STREET - WORCESTER, MASSACHUSETTS MAKERS OF WORLD-FAMOUS HAND TOOLS FOR OVER 30 TEARS



PRECISE DEVELOPMENT CORP.

Oceanside, New York



FREE trial. After 5 days listening—the records you decide to keep are billed you at the low membership price of \$1.50 per disc (average playing time 40 min.). You save 36 the usual retail price? Al-Alt. COTPON NOW before offer expires. Money back guarantee.
The Musical Masterpiece Society, Inc., Dept. 4712 43 West 61st Street, New York 23, N. Y.
Enclosed is \$1 in full payment for recordings of 8 masterpieces listed. Enroll me as trial member. Privileges: No purchase obligation erer! Monthly advance notice of releases. 5 day free trial on any
discs. I may reject records before or after receipt; may cancel membership at any time. For future l.p. discs I decide to keep, I'll pay only \$1.50 each.
Name
Address
CitySlate

spring-loaded, as shown in Fig. 10, and adjustment screws provided so that the outer two projection units can be pointed in slightly—so that the images from all three units fall on top of each other on the screen. The fact that the units are some distance from the screen, and that the middle unit (green) carries 59% of the illumination, makes the very slight "keystoning" of the two outer units a theoretical rather than a practical worry.

Each of the units has a colored filter in front of it. (Colored Plexiglas was found to work the best—even better than photo filters.) The vertical and horizontal adjustments on the projection units, plus the mechanical position of the projection housings themselves, are all utilized to get the best possible registration of the projected images.

Both vertical and horizontal sweep voltages for the three projection units are picked up from the black-andwhite chassis. The vertical sweep is used to drive the vertical yokes on the Norelco units-and the yokes are connected in series. The horizontal yokes are driven in parallel. Doing this will probably require substituting a different output transformer for that originally in the set. In the receiver described here, an RCA 231T1 transformer is used with the proper tap to provide the correct impedance match. The grids of the Norelco units are driven by the color output signals from the color converter chassis.

If everything checks out OK, we're ready for the final step—tuning up the chassis. Complete step-by-step instructions will be given in next month's concluding article.

(To be continued)

SERVICING SWITCHES


THE switching arrangement of a pushbutton tuned radio (with switches on bottom side) is shown removed from receiver.

On this type of switching, with springs and locking devices, one switch rod will stay in when pushed but any other rod will be released.

Some push rods rotate the radio gang condenser directly to pre-set stations, while others, as shown, operate pre-set trimmer condensers across the antenna tuning circuit with the gang condenser cut out for push-button operation.

Switch contacts on the bottom of the mechanism illustrated should be cleaned at intervals, switch rods should be checked for binding in slots and springs must be kept in good condition. 11. L.

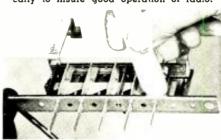Check and clean switch contacts periodically to insure good operation of radio.



RADIO & TELEVISION NEWS



G-C TUNER-KLEEN'R For every Standard Coil tuner. Cleans both stationary and rotary contacts at every twist of the channel selector. Easy to install, means extra profit, better reception.

Na. 9132.....Net \$1.00



G-C SPRA-KLEEN The original power spray electrical contact cleaner and lubricant. Eliminates noises in TV tuners, contacts, controls, relays and switches. Na waste, no need ta remove parts.

No. 8666 6 oz. can.....Net \$1.00



G-C PORTABLE WIRE REEL New, convenient way to handle wire coiled on spools. Just slip spool onto reel and pull aut what you need. No mare twisted ar tangled wire when you go out on a job!

No. 9111......Net \$2.40



G-C SPEEDEX WIRE STRIPPERS New automatic "766" series has delayed return action to prevent crushing of fine stranded wires. Easy to use, with easy-grip handles for easy aperation. Interchangeable blades. Specify wire size.


Series 766 (12 models)....Net \$4.95

Save time... Save money... Speed up your service work!



SERVICE AIDS

AT LEADING PARTS DISTRIBUTORS EVERYWHERE

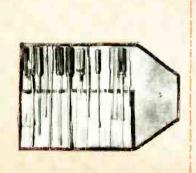


G-C DELUXE ALIGNMENT TOOL KIT Handy roll type case with 16 mostused tools. Tool tips are extra thin, of best grade hardened spring steel for long useful service. Value of tools sold separately \$15.00. No. 8280..... Net \$7.74



hogany, oak—all shades and colors. accidental scratch! No. 909.Net \$0.30

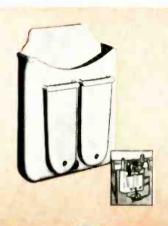
G-C GENERAL SKRATCH STIK Easy to use, in handy carry-with-you case. Removes scratches on walnut, ma-Avoid embarrassment on the job . wipe Skratch Stik on that



G-C "TUX" TOOL KIT Made of remarkable new "Alathon" polyethy-lene. Flexible, tough, will not lose shape. Keep your tools with you, your tape on a chain. Lightweight. No. 8943.....Net \$2.37



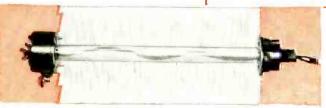G-C ILLUMINATED INSPECTION MIRROR Penlight batteries make this tool independent of cords or connections. Adjustable 1" hinged mirror mounted to 6" transparent lucite rod. No shock. On off switch. Length 121/4". Bulb, less batteries.



G-C COMBINATION LEAD-IN TUBE AND LIGHTNING ARRESTOR Simplest feed-thru idea you ever saw. Drill 34" hole, any wall up to 16" and insert. Arrestor on outside, wall plug inside. A new G-C exclusive!

FREE Your copy of the big, illustrated G-C catalog. Send postcard today!

GENERAL CEMENT MFG. CO.

904 TAYLOR AVENUE

ROCKFORD, ILLINOIS





this great all-channel antenna discovery is smashing sales and performance records in every TV area!

Single bay SUPER RAINBOW model no. 331

the CHAMPION

RAINBOW*

brilliant black-and-white performance — and really ready for COLOR!

these 3 revolutionary, power-packed design features — found in no other antenna today!

- 1. New spacing formula: Radical new spacing arrangements between the directors and reflectors has, for the first time, extended the full efficiency and high gain of the basic narrow band Yagi over the full width of an entire VHF band.
- 2. New "triple power" High Band directors and reflectors: Three-section directors and reflectors, with insulated segments, provide combined power of three High Band Yagis, operating side by side, in phase.
- 3. New "inter-mix" design: Combines—into one single antenna—two separate, independent sets of directors and reflectors, one for High Band, one for Low Band. Each parasitic system operates only on its own band. Fullest efficiency—no compromise design.

PLUS Channel Master's patented, super-gain TRI-POLE... the unique triple-power dipole that made the Champion America's most wanted antenna.

Write for complete technical literature


CHANNEL MASTER creative engineering

Stacked RAINBOW model no. 330-2

Here's how the RAINBOW out-performs the famous Champion:

	CHAMMEL		• 1	4-	5		. 1	. #"		18	- 16	18	1
Gain Over	1 Buy BAINBOW	0	0	DB DB	+1 DB	+ 2 D8	+3	+ 2.5 DB	+1 DB	+.5 DB	+.5 DB	+1.5 DB	+ 2. DI
1-Bay Champion	SUPER BANNOW	+1 00	+1 DB	+1.5 DB	+2.5 DB	+3.5 D8	+3.5 DB	+3 D8	+ 2 DB	+1.5	+2 DB	+3.5 DB	+4.
	C	7	3	4	- 5		7			18	- 11	17	
Gain Over	Stocked BAIMSOW	1.5 00	+2 D8	+1.5	+1.5 DB	+2 DB	+.5 DB	*.5 DB	- DB	+0 D8	- 0 0	+1 DB	+). DE
Champion Champion	Stocked SUPTE RAINEOW	+2 D8	+2.5 DB	+3	+3	+4	+.5 D8	+1 DB	+1 08	+ 2 OB	+ 2 DB	+ 2.5 DB	+3. DI

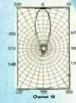horizontal polar pattern (relative voltage)



for fringe and super-fringe areas:

Super Rainbow, model no. 331 \$3750 list stacked Super Rainbow, model no. 331-2 \$7570 list

for suburban and near-fringe areas:

Rainhow, model no. 330
\$2360 list
stacked Rainhow, model no. 330-2
\$4860 list

Copyright 1954, Channel Master Corp.

something new in indoor antennas



- features 3 telescoping sections.
- tilt-proof polystyrene base — cannot tip over.
- handsomely packaged for display.

the ALL-VU*

*all VHF . . . all UHF the only indoor antenna with this "2-Way" feature.

model no. 381 \$695 list

the PRE-VU

for all-channel VHF reception only.

model no. 380

\$595 list

ALUMast

Aluminum Masting.
The new idea in antenna
masting—

can never rust!

- in telescoping sections
- in swaged 5, 10, and 14 foot sections

Lightweight ALUMast is 1/3 the weight of steel, making it so easy to install—it swings right up! Stronger than steel, ALUMast is easier to stock and actually more economical.



brings you today's onewest installation ideas

for . . . more effective installations

- . . . greater customer satisfaction
- ... higher profits for you!

SELECTENNA COUPLING SYSTEM

permits unlimited antenna combinations with only one transmission line!

- for the first time, you can tie together an unlimited combination of antennas, including separate antennas operating on the same band.
- ideal for areas currently using rotators, manually-operated selector switches, and "omnidirectional" antennas.

list price:

\$542 each Including hardware and wire for ipining couplers. This interlocked stack consists of 4 antenna couplers and 1 Hi-Lo coupler; joins 4 antennas.



with features found in no other rotator today:

- flexible worm gear, built-in thrust bearing.
- removable motor, electrical and mechanical stops.
- weatherproof, lightweight, strong.
- straight thru mast mounting, built-in chimney mount.
- · extremely high torque.

model no. 9521, \$4995 list

model no. 9520, without directional indicator, \$4495 list




Beautifully-styled cabinet has great consumer appeal — is smallest on market (2¾" x 4"). Finger-tip control bar.



CHANNEL MASTER CORP. ELLENVILLE, N. Y.

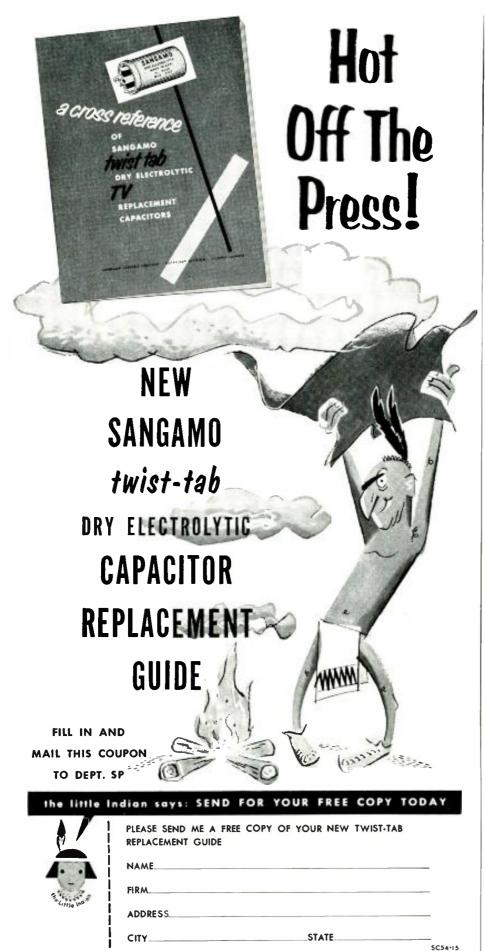WORLD'S LARGEST MANUFACTURER OF TELEVISION ANTENNAS



SANGAMO ELECTRIC COMPANY . MARION.

HIGHLY-SENSITIVE LINK-COUPLED LOOP ANTENNA

By L. S. HANNIBAL


Jry this loop antenna to pull those elusive broadcast signals out of the ether.

FOR several years the writer has wrestled with the problem of picking up an AM hi-fi San Francisco Bay area station which was badly blanketed by a local 50 kw. broadcast station—one of the type that, to all intents, "slobbers" over considerably more of the band than is desired. Wave traps, bandpass couplings, and the like were all tried repeatedly without much effect. None could give the desired 20 kc. separation which was necessary in this instance. Both regenerative r.f. amplifiers and crystal filters were duly considered, but were promptly dropped when a link-coupled loop antenna was given a chance trial.

This loop consisted of 14 turns of No. 20 wire, spaced with an eighth inch clearance between turns, on an X-frame, with each diagonal 16 inches long. A small tuning capacitor from an old 1924 broadcast receiver was used to tune the loop. A single-turn, link-coupling loop was wound inside the 14 turns with 1½ inches of space between each coil. This single turn was fed by a twisted pair to a two-turn coil wound loosely about the first r.f. coil on the broadcast receiver. One leg of the twisted pair was grounded securely where it entered the chassis in order to reduce capacity pickup.

In practice, tuning consists of adjusting the set and loop tuning capacitor for maximum desired signal. Then the set is detuned sufficiently to pick up the undesired signal. The loop is then rotated to a null point for the undesired to a null point for the undesired signal.

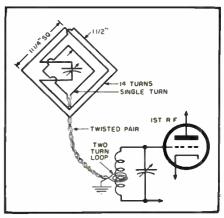Complete details for building loop antenna.



RADIO & TELEVISION NEWS

sired signal. This setting in bearing can be quite sharp and, in this instance, was less than one degree. Once the loop's position was established the desired hi-fi station was tuned in without crosstalk or scratching.

A vernier dial will be found of value in tuning the loop's tuning capacitor. (This capacitor is mounted directly on the loop's X-frame. The 112" coupling between the loop and link permits the loop to tune quite sharply. Placing the link coupling nearer to the tuning loop reduces selectivity, but increases signal input to the set. This also reduces background noise, but aggravates crosstalk or rasping from the local broadcast station.

The effectiveness of this loop system can be appreciated when it is realized that a San Francisco Bay station of 10 kw. power beamed on a north-south axis can be picked up quite satisfactorily 110 miles in an easterly direction under the blast of a 50 kw. station about 4 miles distant from the writer's residence.

440 MEGACYCLE TRANSISTOR

THE time when home TV sets will use tiny transistors instead of a large array of vacuum tubes came closer to realization with the announcement by Bell Tel-ephone Laboratories of a transistor which will operate at 440 me.

Known as an "intrinsic barrier" transistor, the new unit can increase an electrical signal a thousandfold. Frequencies as high as 3000 mc. are theoretically possible.

The new transistor adds a fourth layer to the basic "p-n-p" wafer. This intrinsically pure layer acts as a "shock absorber" for high voltage electrical charges. This chemically pure part of the germanium crystal remains neutral while the three adjoining sections become positively or negatively charged. This "intrinsic" region in the midst of the transistor permits the faster move-ment of positive charges, isolates the input and output areas, and reduces the stored energy to make functioning at higher frequencies possible. The in-ereased separation of input and output areas also permits operation at higher voltages.

A Bell Labs engineer uses a "dry box" to assemble the new u.h.f. transistor. He is shown placing a metal casing over the unit to assure long life. This assembly technique is used to avoid any contamination.



December, 1954



GOODLINE AIRLEAD - 733 GA & 737 GA GOODLINE HOLO - 801 GH GOODLINE SHEATHLEED - 812 GS & 823 GS GOODLINE TELEAD

ALSO THE ECONOMY NON-SILICONE GOODLINE ANGELUS

IT'S EASY TO TELL IF IT'S "GENUINE GOODLINE" All Don Good Television Leadlines are Quickly Identified By The Blue and Yellow Reel.

ALL GOODLINE TELEVISION TRANSMISSION LINES ARE PURE VIRGIN POLYETHYLENE ESPECIALLY COMPOUNDED FOR LONG SERVICE LIFE.

ON SWOOL, INC.

SOLD BY LEADING JOBBERS & DEALERS

Send coupon NOW! Get samples "in your hands" -you'll realize why **Don Good Products make** the finest television reception possible.

DON GOOD, INC.	
1014 Fair Oaks Ave., So. Pasadena,	Calif.
Please rush Samples and Complete mation covering Don Good Products.	Infor-
At	

Street_ City_ State

NEW! FREE CATALOGUE!

For bargains in surplus that can't be bear Get Your FREE Copy Today!

MONTHLY SPECIAL: 0-1 3-INCH MILLI-AMP METER, 270° indication. By-pas shunt and add scale. Only \$1.95.

J. J. GLASS ELECTRONICS CO. 1615 S. Main St. Los Angeles 15, Calif.

RADIO and TELEVISION ELECTRONICS



in all Technical Phases New Classes (Day and Evening) Start 1st of Dec., Mar., June, Sept.

Free Placement Service for Graduates
For Free Catalog write Dept. RN54
RCA INSTITUTES, INC.
Service of Radio Corporation of America
WEST 4TH ST.. NEW YORK 14. N. Y.

110V, AC POWER SUPPLY FOR ANY 274-N RECEIVER

Just plug it into the rear of your 274-N RECEIVER . . . any model. Complete kit and black metal case, with ALL parts and diarrams. Simple and easy to build in a jiffy. Delivers 24 volts plus B voltage. No wiring changes to be made. Designed especially for the 274-N receiver. Only \$8.95.

Filament trans, for 274N receivers. Pri. 110V. 60 cy. AC. Sec. 24V @ .6A. An excellent buy at \$1.95 ea.

SPLINED TUNING KNOB FOR 274N RECEIVERS

An exclusive O-R item manufactured for us. Fits BC-453, BC-454 and other 274N receivers. This is a really hard-to-obtain item. Only. 89c ea.



OFFENBACH-REIMUS

1564 Market Street, San Francisco, Calif.

Now...complete

Protection / Iromethe REALS ...

with a broad-band antenna that rejects unwanted signals from rear and sides ... and It's arother Test May-Townes

Now .. for the First Time!

A full automatic snap-out antenna that is muchanically safe!

Elements are double locked in position and sested in channel to prevent dropping or falling apart.

Manufactured and Distributed in CANADA by DELHI METAL PRODUCTS, LTD. DELHI, ONTARIO the antenna for which all America has been waiting...

this is the PROBLEM

New TV stations by the score plus stepped-up power on existing stations is increasing the difficulty of reception in many areas.

Co-channel interferences and the resulting loss of reception quality cannot be overcome by ordinary antennas now available.

MODEL CHANNEL NUMBER


RG-1-L 2-6

RG-1-H 7-13

RG-1-LH 2-13

(RG-1-L and RG-1-H in combination)

COPYRIGHT 1954

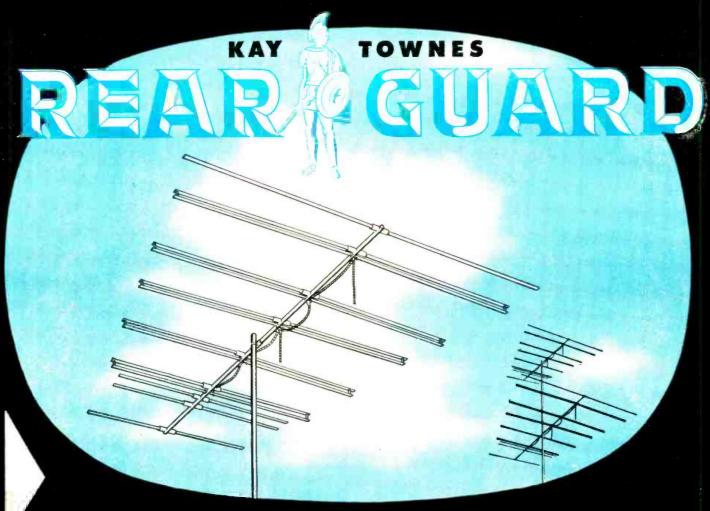

Here is the amazing KAY-TOWNES answer!

Again...KAY-TOWNES is First with the answer!
The new K-T REAR GUARD completely rejects
unwanted signals from the rear and sides to
give televiewers the best possible picture and
sound reception in areas where co-channel

interferences present difficulties. Yes Sir! The new K-T REAR GUARD is ready for you now in arrays to suit your needs . . . It's a Quality Antenna for Quality Reception. It's a Kay-Townes Antenna!

- NO interference from the rear
- High front to back ratio



RADIATION CURVE
REPRESENTING ALL VHF CHANNELS

- Top quality reception
- Sharp definition
- Primary UHF

WRITE TODAY FOR FURTHER INFORMATION AND PRICES

KAY-TOWNES

Use the K-T line
of television
accessories

Antenna Company
Box 593 A, ROME, GEORGIA

IT'S NEW! IT'S COMPLETE! IT'S AVAILABLE!



TRIAD'S*CORRECT REPLACEMENT TV GUIDE TV-55

Triad's new TV Guide is available now. It is a complete up-to-date catalog of Triad's *Correct Replacement TV Transformers, exhaustively checked for accuracy. Your jobber has copies of TV-55 in stock...or write us direct.

*Correct Replacement (*CR) transformers are mechanically correct and electrically correct ruggedized versions of original manufacturers' items built to give a longer more satisfactory life.

Triad *CR Transformers are listed in Sam's Photofact folders & CounterFacts and Riders Replacement Parts List.



WHAT'S 460-114-1-6-6-6-

The products described in this column are for your convenience in keeping upto-date on the new equipment being offered by manufacturers. For more complete information on any of these products, write direct to the company involved.

TRANSISTOR OSCILLATOR

General Radio Company, 275 Massachusetts Ave., Cambridge 39, Mass. is



currently offering a pocket-size transistor oscillator for audio-frequency testing, the Type 1307-A.

Completely self-contained, including batteries and output meter, the oscillator is small enough to be held in one hand. Two frequencies, 400 and 1000 cycles, are available with a maximum output of at least 2 volts across a 600-ohm load. The output voltage is adjustable and is read on the meter.

The unit uses a *p-n-p* junction transistor in a Hartley oscillator circuit. The output voltage is set by an adjustable resistance in series with the battery supply, thus conserving battery life when only low output is needed. Under average conditions, battery life is over 100 hours.

PEAK-TO-PEAK V.T.V.M.

Electronic Instrument Co., Inc., 84 Withers Street, Brooklyn 11. N. Y. has added a new peak-to-peak vacuumtube voltmeter to its Eico line of test equipment in wired and kit form.

Designed expressly for TV servicing, the new Model 249 comes with the company's dual purpose a.c./d.c. "Uni-Probe" which performs all functions—a half turn of the probe tip selects d.c. or a.c. ohms.

The circuit features stable push-pull




triode bridge circuitry, with accuracy unaffected by line voltage variation. It reads peak-to-peak voltage of complex and sine waveforms, r.m.s. voltage of sine waves, d.c. voltage and resistance. It provides for center-scale zero adjustments for TV-FM alignment and for calibration from outside the cabinet. The 7½" meter is electronically protected against burn-out.

Additional information on the Model 249 or Model 249K (kit) is available from the company.

VARIABLE CAPACITORS

The APC and MAPC types of variable capacitors are now available with extended shafts, according to *The Hammarlund Manufacturing Company*, Inc., 460 W. 34th St., New York 1, N. Y.

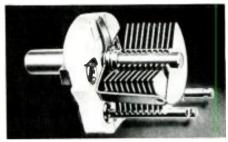At the request of amateurs, experimenters, and electronic equipment builders, the line has a half-inch shaft extension for knob control. The APC trimmer is designed for applications



where a compact air dielectric trimmer is required. The MAPC type is similar to the APC except that it is a miniaturized version.

ATR'S "SHAV-PAK"

American Television and Radio Co., 300 E. Fourth St., St. Paul 1, Minn. is now offering a new inverter which has been tradenamed the "Shav-Pak."

The unit is especially designed for operating standard a.c. electric shavers in autos, buses, trucks, boats, and planes. The unit plugs into the cigarette lighter receptacle on the dash and is small enough to be kept in the glove compartment.

A circular on the "Shav-Pak" is available on request.

SINGLE-SIDEBAND GENERATOR

A single-sideband generator especially designed for operation with the company's Model 5100 transmitter has been announced by Burker & Williamson. Inc., 237 Fairfield Ave., Upper Darby. Pa.

Designated as the Model 51SB, the generator offers SSB operation on all frequencies provided in the 5100. Tuning and operation are fast and uncomplicated, according to the company. No test equipment is required.

(Continued on page 152)



A fascinating field! A great future! A good job or independence in a business of your own! TV is growing by leaps and bounds-1227 new communities, 1845 new stations have been given the "go-ahead" Trained men are worth their weight in gold!

MODERN TRAINING BY COYNE RIGHT IN YOUR OWN HOME

Here is modern, up-to-the-minute Home Training in Television and Radio designed to meet the standards that have made the Coyne School famous for many years. You get personal supervision by members of Coyne instruction staff—men who know TELEVISION AND RADIO AND KNOW HOW

B. W. COOKE, President

SCHOOL

A TECHNICAL TRADE INSTITUTE CHARTERED NOT FOR PROFIT
Established 1899

500 S. Paulina Dept. 94HR5, Chicago 12-

TELEVISION ★ RADIO ★ ELECTRICITY ★ REFRIGERATION ★ ELECTRONICS

TELEVISION-RADIO "ELECTRICITY

TO TEACH IT-men who have helped train thousands of men and young men, Service men and Veterans.

LEARN TO EARN IN SPARE TIME

COYNE offers a most practical, down-to-earth Home Television Training. Simple, easy to follow step-by-step instructions, fully illustrated. So practical, you can quickly be earning money in Television and Radio and keep your present job while training. Let us show you that this is not only the newest, most up-to-the-minute Training in Television-Radio-Electronics—but also it costs you much less than you'd expect to pay. Send coupon today for details including Easy Payment Plan.

B. W. COOKE, President COYNE SCHOOL 500 S. Paulina St., Chicago 12 Dept. 91HR5

Send details of your offer on training checked below. This does not obligate me and no salesman will call. I am interested in:

- ☐ Television-Radio Home Training
- ☐ Electricity in Coyne Shops
- ☐ Television-Radio in Coyne Shops

. . State

Coyne, of course, also offers practical resident training in the Coyne Training Shops here in Chicago in the fields of TELEVISION-RADIO and ELECTRI-CITY. If you prefer to get information about our resident courses in either or both of these fields, then check on the coupon accordingly and mail it to us. Our fully illustrated 48 page Guide To Careers in Television-Radio and Electricity and complete details about our resident training will be sent you by return mall. No cost or obligation to you, of course, and no salesman will call on you.

IN THE GREAT SHOPS

OF COYNE AT CHICAGO

MAIL COUPON FOR INFORMATION

Fill in and mail coupon TODAY. Paste it on a postcard if you wish. Complete details will come by return mail. No cost no obligation and no salesman will call.





It's New! It's Terrific!

THE THE FM-80

World's Best by I. R. E. Standards

Never before in the history of Frequency Modulation has there been a tuner to match the remarkable, new FISHER FM-80. Equipped with TWO meters, it will outperform any existing FM tuner, regardless of price! The FM-80 combines extreme sensitivity, flexibility, and micro-accurate tuning. It has an unusually compact, beautifully designed chassis. Like its renowned companions, the FISHER FM-AM Tuners, Models 50-R and 70-RT, we predict the FM-80 will be widely imitated, but never equalled. Be sure; buy THE FISHER.

Only \$139.50

Outstanding Features of THE FISHER FM-80

• TWO meters; one to indicate sensitivity, one to indicate center-of-channel for micro-accurate tuning. • Armstrong system, with two IF stages, dual limiters and a cascode RF stage. • Full limiting even on signals as weak as one microvolt. • Dual antenna inputs: 72 ohms and 300 ohms balanced (exclusive?) • Sensitivity: 1½ microvolts for 20 db of quieting on 72-ohm input; 3 microvolts for 20 db of quieting on 300-ohm input. • Chassis completely shielded and shock-mounted, including tuning condenser, to eliminate microphonics, and noise from otherwise accumulated dust. • Three controls — Variable AFC/Line-Switch, Sensitivity, and Station Selector PLUS an exclusive Output Level Control. • Two bridged outputs. Low-impedance, cathode-follower type, permitting output leads up to 200 feet. • 11 tubes. • Dipole antenna supplied, Beautiful, brushed-brass front panel. • Self-powered. • weight: 15 pounds. • StZE: 12¾" wide, 4" high, 8½" deep including control knobs.

Price Slightly Higher West of the Rockies

WRITE TODAY FOR COMPLETE SPECIFICATIONS

FISHER RADIO CORP. · 21-23 44th DRIVE · L. I. CITY 1, N. Y.

Certified Record Revue

(Continued from page 60)

recording of some years ago, on the Oceanic label. Here she is "Salome" again, but a more matured, more experienced, and vastly more effective "Salome." Hers is a passionate, intense, and dedicated performance. She immerses her identity in the role and makes of "Salome" a terrifying and helievable creature. Her voice is a beautifully trained and responsive instrument. While she hasn't the great power of Ljuba Welitsch, the voice is strong enough for the requirements of the role and she displays an infinitely greater range of color and expression. Every nuance of the role is clearly delineated and in the Final Scene, the purity of her voice blazes forth, unsullied by bombast or strain. The rest of the cast sings superbly in this recording. I could have wished for a little less pontificating from the "Jokanaan" of Hans Braun, a minor fault. Patzak and Dermota were particularly effective in their portrayals and London has even gone to the expense of having such a stalwart as Ludwig Weber in the comparatively minor role of "1st Nazarene." The Vienna Philharmonic has rarely sounded better, and their playing was a miracle of precision coupled with sumptuous tone. Perhaps this is a sort of testament to the incomparable Strauss of the late Clemens Krauss. Few will deny his particular gift for interpreting the works of Richard Strauss. Where others obscured . . . he revealed. Where others conducted with their heads, he used his heart. This kindly and genial man is gone, but his Strauss will not soon be forgotten. The sound on this recording is considerably better than the recent Columbia, yet surprisingly, is not up to the very highest standards of London opera recording. String tone is generally quite good, smooth and free of annoying wiriness. But the dynamics are less than you would expect and there are inexplicable moments when the range seems somewhat restricted. Good percussion in "Salome's Dance." solid bass drum and very clean cymbals. All in all, a most memorable and moving experience. A comfortable recording and one which can stand repeated listenings as well as the test of time.

STRAUSS, RICHARD ALSO SPRACH ZARATHUSTRA DANCE OF THE SEVEN VEILS (SALOME)

The Chicago Symphony Orchestra conducted by Fritz Reiner. RCA Victor LM1806. RIAA curve. Price \$5.95.

While we are on the subject of Strauss and "Salome," let's take a listen to this disc, the first in a new collaboration between Victor and the Chicago Symphony Orch. This is an extraordinary record in more ways than meets the eye at first glance. For one thing this represents a new departure in policy for RCA. They are now naming the equipment and the recording techniques employed in the making of the record. What makes this really incredible is the fact that the information about the recording as printed on the jacket, is virtually an endorsement of the Mercury "Olympian" technique! As related on the jacket, RCA utilized a condenser mike (presumably a Telefunken) at the approximate distance over the conductor's podium as has been Mercury's wont. The heated cutter, variable pitch, and other matters of technique are also discussed. The result? The best doggone sound that Victor ever turned out! This is no discredit to Victor or their There is certainly no patent or engineers. monopoly in the idea of using an overhead

Telefunken mike. Nor is this the whole story on the search for better sounding recordings. Rather this new sound shows that Victor made a study of various new techniques and was not above admitting and adopting to a technique previously foreign to them. There is certainly nothing wrong in this . best thing that could ever happen to the industry is free competition. The sound that Victor obtained bears witness to this. Really exceptional quality. The "Zarathustra" is full of rip-snortin' hi-fi effects. Huge brass sonorities, very solid percussion, very live "breathy" woodwinds, and a superb string tone. Dynamic range and frequency range tone. Dynamic range and frequency range are far beyond previous Victor recordings. Reiner is, of course, an old hand with Strauss. In "Zarathustra" he plays the game fairly close to the vest. No errant tempi for him, nor overblown dynamics. If the Clemens Krauss-London version did not exist, this would certainly be the recording of choice. But a little ton much fusciness characteristics. of choice. But a little too much fussiness obscures the broader meanings and shadings in the score, and on the whole. Reiner's is a much more impersonal version. The London recording was more than hi-fi for its day, but in this department it is outgunned by this present recording. Except for the low C in the basses which begins a fugal development (and which come through with greater intensity in the London), this has greater dynamics, greater clarity and resolution. Transients of tympani and bass drum and cymbal are much cleaner and have more impact in this recording. The "Salome's Dance" is given a supercharged reading by Reiner and it is not likely to be outsounded by any competing version. The Chicago Orchestra plays magnificently for Reiner, although it would be unkind not to mention that part of this precision is certainly a legacy from Rafael Kubelik. Altogether a most auspicious start for Victor with a new recording technique. The record conformed perfectly to the RIAA curve and surfaces were

BARTOK

CONCERTO FOR ORCHESTRA

Minneapolis Symphony Orchestra conducted by Antal Dorati. Mercury MG 50033. RIAA curve. Price \$5.95.

Here is an absolutely stunning performance of what many believe to be Bartok's greatest work. It would be a picayune and biased critic who could find fault with this recording. The performance is a triumph of the first order for Dorati. He is white-hot in the intensity of his interpretation. Yet he never allows his obvious zeal and devotion to the score to obfuscate, nor to amend or reshape the philosophy of Bartok. It is a respectful performance, nowhere at variance with the composer's wishes or intent. This reverent approach is undoubtedly a reflection of the friendship that existed between Dorati and Bartok. As a work by Bartok, the "Concerto for Orchestra" is somewhat of a paradox. By this I mean that although this is perhaps the most intricate and complex of all Bartok scores, with more than its share of dissonance and atonality, it is also the Bartok that is most readily assimilated by the public. Believe me when I tell you that if you've never been able to "take" Bartok, this is the score that can change your mind. In its infinitely varied color and contrasts, Bartok has utilized the widest resources of the modern orchestra. In the strings alone, you will hear more unusual techniques than in almost any other composition you can name. Pizzicato, spiccato, double bridging ... the whole bag of tricky violin gym-nastics can be heard. The other choirs in the orchestra are similarly treated. The complexity of the score calls for a virtuoso orchestra and the Minneapolis responds magWE ARE PROUD TO ANNOUNCE

The Greatest Advance

IN AMPLIFIER DESIGN
IN TWENTY YEARS!


FISHER Z-MATIC PAT. PEN

The unusual, the choice—both are a regular and traditional product of our engineering laboratories. But never before have we offered a technological advance so obviously needed, so long overdue, as the exclusive FISHER Z-Matic. Regardless of the speaker system, be it a modest 8" unit or a giant assembly, the vast acoustic improvement contributed by FISHER Z-Matic is instantly apparent and truly astonishing. For Z-Matic has at one stroke eliminated the energy-wasting, distortion-producing mismatch that has prevented the complete union of speaker and amplifier ever since the advent of electronic sound reproduction. Z-Matic is now standard equipment on all FISHER amplifiers.



50-Watt Amplifier · Model 50-AZ

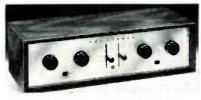100 watts peak! World's finest all-triode amptifier. Uniform within 1 db, 5 to 100,000 cycles. Less than 1% distortion at 50 watts. Hum and noise 96 db below full output. Oversize, quality components and finest workmanship. \$159.50



Master Audio Control · Series 50-C

"Finest unit yet offered." — Radio and TV News. 25 choices of record equalization, separate bass and treble tone controls, loudness balance control. 5 inputs and 5 independent input level controls, two cathode follower outputs.

Chassis, \$89.50 . With cahinet, \$97.50

What Z-Matic Does

Multiplies the efficiency and effective audible range of any speaker system, regardless of size.
 The continuously variable Z-Matic control permits any setting, according to personal taste or the requirements of the speaker system.
 Eliminates need for oversize speaker enclosures and automatically corrects inherent deficiencies in speaker or speaker housing.
 Z-Matic must not be confused with tone, equalization, loudness balance or damping factor controls. It is an entirely new development.
 Only FISHER amplifiers have Z-Matic.

A Word to Our Patrons

Your FISHER 50-A or 70-A amplifier can be readily equipped with Z-Matic. A complete kit of parts and easy-to-follow instructions are available at a cost of only \$2.50 to cover handling. Give serial number and model.



25-Watt Amplifier • Model 70-AZ

50-watts peak! More clean watts per dollar. Less than ½% distortion at 25 watts (0.05% at 10 watts.) Response within 0.1 db, 20-20,000 cycles; I db, 10 to 50,000 cycles. Hum and noise virtually non-measurable! \$99.50

Prices Slightly Higher West of the Rockies

WRITE TODAY FOR COMPLETE SPECIFICATIONS

FISHER RADIO CORP. • 21-23 44th DRIVE • L. I. CITY 1, N. Y.

nificently. You will find that in the course December, 1954

Fine Additions

TO COMPLETE YOUR HOME MUSIC SYSTEM

FISHER

ACCESSORIES



MIXER-FADER · Model 50-M

NEW! Electronic mixing or fading of any two signal sources (such as microphone, phono, radio, etc.) No insertion loss. Extremely low hum and noise level. High impedance input; cathode follower output. 12AX7 tube. Self-powered. Beautiful plastic cabinet. Only \$19.95



PREAMPLIFIER-EQUALIZER · 50-PR

Professional phono equalization. Separate switches for HF roll-off and LF turn-over; 16 combinations. Handles any magnetic cartridge. Extremely low hum. Uniform response, 20 to 20,000 cycles. Two triode stages. Fully shielded. Beautiful cabinet. Self-powered. \$22.95



PREAMPLIFIER-EQUALIZER · 50-PR-C WITH VOLUME CONTROL

50-PR-C. This unit is identical to the 50-PR but is equipped with a volume control to eliminate the need for a separate audio control chassis. It can be connected directly to a basic power amplifier and is perfect for a high quality phonograph at the lowest possible cost.

\$23.95



HI-LO FILTER SYSTEM · Model 50-F

Electronic, sharp cut-off filter system for suppression of turntable rumble, record scratch and high frequency distortion — with absolute minimum loss of tonal range. Independent switches for high and low frequency cut-off. Use with any tuner, amplifier, etc. \$29.95



PREAMPLIFIER · Model PR-5

A self-powered unit of excellent quality, yet moderate cost. Can be used with any low-level magnetic cartridge, or as a microphone preamplifier. Two triode stages. High gain. Exclusive feedback circuit permits long output leads. Fully shielded. Uniform response, 20 to 20.000 cycles. \$12.57



PROFESSIONAL PHONO CARTRIDGES

America's first factory-sealed, moving coil phonograph cartridge. You are the first to handle the cartridge you buy. High compliance improves low frequency response, reduces record hiss and wear. Exclusively with diamond stylus. Model 50-LP (33-45) or Model 50-ST (78).

Each \$29.75

Prices Slightly Higher West of the Rockies

WRITE TODAY FOR COMPLETE SPECIFICATIONS

FISHER RADIO CORP. · 21-23 44th DRIVE · L. I. CITY 1, N. Y.

of a season, few orchestras will program this work, because of the difficulties involved. The Minneapolis under Dorati plays the work quite frequently and this experience accounts for the cohesive and fluent ease of their performance. Soundwise, this is an incredible recording. It will tax your pickup and speaker system to the utmost. The exceptionally clean string tone, the brilliant blare of weighty brass, the super-articulate woodwinds and the impact and accuracy of the very large percussion section is accented by the violently contrasting dynamics. One of the most distortion-free recordings I have ever heard. Everything considered, this recording is a tremendously exciting and stimulating experience and is unreservedly recommended. The RIAA curve was adequate for the recording with a slight bass boost adding an extra fillip of balance. Quiet sur-

BRAHMS

CONCERTO FOR VIOLIN AND ORCHESTRA IN D MAJOR

Nathan Milstein, violinist with Pittsburgh Symphony Orchestra conducted by William Steinberg, Capitol P-8271. RIAA enrve, Price \$5.70.

The newest and best of the thirteen recorded versions of this concerto in the LP catalogue. This is a pretty strong statement. considering such formidable enmpetition as the Stern-Beecham effort on Columbia and the Menuhin-Furtwangler on Victor. Nevertheless, the warm, fluent reading of Milstein and the sympathetic collaboration of Steinberg and the Pittsburgh Symphony, justifies the praise. No "tempo tampering" here, nn razzle-dazzle. Just superb straightforward musicianship and integrity of purpose. Capitol has furnished the recording with a warm, glowing sound, quite different from their usual technique. A splendid balance is maintained between orchestra and soloist and the acoustic perspective gave just the right "pres-ence." The RIAA curve did not need adjustment. Quiet surfaces.

WALTON CONCERTO FOR VIOLA AND ORCHESTRA

William Primrose, violist with The Royal Philharmonic Orchestra conducted by Sir Malcolm Sargent, HINDEMITH

DER SCHWANENDREHER

William Princrose, violist with Columbia Chamber Orchestra conducted by John Pritchard. Columbia ML4905. NARTB curve. Price \$5.95.

Here we have two prime examples of the artistry of the great William Primrose. To be sure, these works are modern and not the usual province of Primrose. But before you flee, let me hasten to add that these works fall into the category of "lyric or listenable modern." Neither the Walton nor "Der Schwanendreher' will assault your ear with very much atonality or dissonance. Throughout both of these interesting works, Primrose displays the virtuosity which makes him the premier exponent of the viola, and his tone in the opening movement of the Walton has to be heard to be believed. Rich and darkly resonant, it is a thing of ineffable beauty. Primrose gets effective and understanding orchestral support from both organ-izations. First class sound is a feature of both these works, and there are some amusing and clever hi-ti effects to be heard in the scherzo of the Walton. Both works have been recorded at very high amplitudes without, however, the usual penalty of "pre-echo," to mar the sound. Acoustic perspec-tive and solo/orchestral balance are nicely handled. Highly recommended to the audiophile of an inquiring and unprejudiced

The NARTB curve did not require adjustment. Moderately quiet surfaces.

MOZART

SYMPHONIES #25, #29, #33 Vienna State Philharmonia conducted by Jonel Perlea. Vox PL8750. NARTB

curve. Price \$5.95.

The beginning or budget-minded audiophile certainly owes a debt of gratitude to Vox. For some time now they have been putting out super bargain records . . ords with more than 60 minutes total playing time. Contrast this with the early days of LP when some records had as little as 18 to 20 minutes covering a 12" disc! In money alone, this Vox policy has been saving some people as much as 60% of the cost of acquiring certain works. Nor has Vox slighted the quality of the recordings with the extra time. As in their other issues of this type, this potpourri of Mozart symphonies is well recorded and the performance does not need any apologies. Perlea is a most versatile fellow. Here he is tilting with the delicacy and charm of Mozart and his last record was the fire and thunder of Tchaikovsky's "1812 Overture"! His readings are solid and substantial, with little of conductorial eccentricities to quibble about. His competition is tough to be sure . . Beecham and von Karajan among others. But if they outdo him in polish and understanding, he has the edge in the better sound he is afforded. Good clean string tone and excellent woodwind reproduction characterize these symphonics, and the whole adds up to a most attractive buy. The NARTB curve was adequate. Good

BERLIOZ PROGRAM

Orchestre des Concerts Lamoureux conducted by Willem Van Otterloo, Epic LC3054, NARTB curve, Price \$5.95.

This is another good bargain record, with no less than seven familiar Berlioz pieces for your money. Included are such favorites as the "Trojan March." "Dance of the Sylphs," the "Roman Carnival Overture" and the "Rakoczy March." Otterloo seems to know his way with these scores and gives a competent, if not overly inspiring, reading of them. The orchestra plays quite well and the sound is the best from Epic to date. Good balance is maintained and the string tone has little of the edginess that was objectionable in some of the previous Epic releases. Some nice sharp percussion, in those works calling for it. Another good buy for the beginning audiophile, who is trying to augment his usually meagre library. The NARTB curve was better with a little bass and treble cut. Moderately quiet surfaces.

SCHUBERT SYMPHONY #9

NBC Symphony Orchestra conducted by Arturo Toscanini. RCA Victor LM1835. RIAA curve. Price \$5.95.

The retirement of Arturo Toscanini and the disbanding of the late, lamented NBC Symphony was a severe blow to the musical world. How great this loss is, is heightened and brought close to home when you realize there will be no further recordings like this great Schubert "oth." The only crumb of satisfaction is that we do have a brilliant new recording of this work, to supplant the older Toscanini version which was notably deficient in sonic virtues. As I have said before, I have not been among those who blindly worshipped everything the Maestro conducted. But in certain areas, he was incomparable. I have always felt that his reading of the Schubert "oth," was the ultimate in our time, the model to be held up to the light for lesser men to see and profit therefrom. Nor has time dimmed the luster of his performance in this present recording.



World's **Finest**

BY I.R.E. **STANDARDS**

MODEL 70-RT

FISHER

Professional **FM-AM TUNERS**

 ${f T}^{
m HE}$ truest index to the quality of FISHER Tuners is the roster of its exacting users. An Eastern FM station chose the FISHER to pick up selected New York and Washington programs direct, for rebroadcast to its own community. Reception of FM stations over 150 miles distant, terrain permitting, is a regular occurrence, if you own a FISHER Professional FM-AM Tuner, 70-RT or 50-R.

MODEL 70-RT

Features extreme sensitivity (1.5 mv for 20 dh of quieting); works where others fail. Armstrong system, adjustable AFC on switch, adjustable AM selectivity, separate FM and AM front ends. Complete shielding and shock-mounting on main and subchassis. Distortion below 0.04% for 1 volt output. Hum level; better than 90 db below 2 volts output on radio, better than 62 db below output with 10 mv input on phono. Two inputs. Two cathode follower outputs. Self-powered. Exceptional phono preamplifier with enough gain for even lowest-level magnetic pickup. Full, phono equalization facilities. 15 tubes. Six controls, including Bass, Treble, Volume, Channel/Phono-Equalization, Tuning and Features extreme sensitivity (1.5 my for Channel/Phono-Equalization, Tuning and Loudness Balance. Beautiful Control Panel. SIZE: 1434" wide, 812" high, 914" deep.



Ill Identical to the 70-RT but designed for use with an external preamplifier-equalizer, such as the FISHER Series 50-C.





MASTERPIECE OF TUNER DESIGN



MODEL 7C-RT

\$18450

MODEL 50-R

\$16450


PRICES SLIGHTLY HIGHER

Write for Full Details

FISHER RADIO CORP. 21-23 44th DRIVE LONG ISLAND CITY 1, N.Y.

105 December, 1954

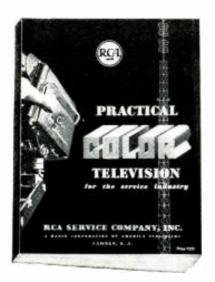Color's bigger than ever! AND THE NEW 2ND EDITION OF



IS MORE THAN EVER A MUST

Color television receivers at much better prices are due to hit dealers' floors any time now. And when color television starts moving in volume . . every technician must be ready for this new, different, profitable field. There's not a day to lose. Get your copy of the brand new 2nd edition of PRACTICAL COLOR TELEVISION ... and get it right away!

Here is the latest practical color service information you can get from any source. Included in its 86 pages are: Principles of Color Television

... Detailed Circuit Diagrams ... Operating Instructions . . . Antenna Requirements . . . Test Recommendations . . . and much, much more. Time-tested information . . . brought up to the minute by RCA, pioneer in compatible color television.

\$2.00 a copy . . . and worth far more in future color television profits for you! See your RCA Parts and Tube Distributor, or mail the coupon ... today.

RCA SERVICE COMPANY, INC.

A Radio Corporation of America Subsidiary CAMDEN, NEW JERSEY

RCA Service Co., Inc. Commercial Service Section Comden, N. J.
Please send me copies of "Practical Color Television" at \$2.00 each. Check or Money Order forenclosed.
NAME
COMPANY
STREET
CITY ZONE STATE

There is still the insight, the understanding. Still the inflexible beat and the firmness of purpose. Still the heaven-storming power and beauty. And all this transcendental performance is cloaked in splendid wide-range sound. What a great pity that Toscanini and his men could not have been afforded this kind of recording over the past few years. The sound of the NBC is newly revealed in clean luminous string tone, great brass sonorities and percussion with solid authority. Dynamic range is at last appropriate to the music and Toscanini's demands. We can be thankful that at least this once, Toscanini was able to erect a sonic edifice that will stand as a monument to his extraordinary genius. To paraphrase a famous beer ad . . . if you like Schubert, you'll love this recording. The RIAA curve did not need adjustment. Very quiet surfaces.

Pre-recorded Tapes

RODGERS, RICHARD VICTORY AT SEA

NBC Symphony Orchestra conducted by R. Bennett. RCA Victor pre-recorded tape, ½ track, 7½ ips. Price \$14.95.

Still more of the tape in the first Victor pre-recorded tape release. For me this has the least musical substance of what has been offered, but at the same time, is the most striking example of the superiority of tape over disc. The music is consciously programmatic, to be used as a background score for the superb documentary film of the same name. As with much of this type of music, it can't help but fall into the trap of too much bombast and cliche. There are some moments where the melodic gift of Dick Rodgers shines through, but for the most part it's obscured by "mood" music. However, this very fact makes it a good demonstration tape. All sorts of colorful orchestration is used throughout the work, and audiophiles will delight in the clean, edgeless string tone, the soaring French horns, the bright punchy brass and the crisp and precise percussion. As with the other tapes, the great dynamic range is the most notable There was no evidence of overload or distortion and the tape hiss level was barely noticeable. More next month, possibly some of the pop material like Sauter--30-Finegan.

CHECK V.O.M. CONNECTION

By H. LEEPER

WHEN your volt-ohmmeter seems un-stable or inaccurate, check the connections on the dry cells used on the low ranges of the ohmmeter. The operator of an instrument, such as the vacuumtube meter shown, may forget about these batteries.

New cells are, of course, needed at intervals.

It is best to check the voltage of such batteries with a voltmeter other than the one contained in the same case, as certain connections are made in some instruments which would result in meter -30damage.

Check batteries in your instruments often.





ALL-STEEL

MULT DRAWERS

INTERLOCKING

Multi-Drawers are handy allsteel storage cabinets perfect for storing easily-lost small parts like condensors, small tubes, switches, nuts and bolts! Precision-made, finished in durable two-tone green enamel, complete with card holder. Available at your dealer's in two sizes—42c ea, in the small size (illus.), \$1.28 for the large.

EASY TO ASSEMBLE

*Units interlock rigidly at top, bottom, sides to fit ony space.



SOME DEALERSHIPS OPEN

*Once again, enough steel is avoilable to make Multi-Drawers available to new dealers! Write today

THE CINCINNATI VENTILATING CO. INC. THIRD & MADISON STS., COVINGTON, KY.

NOW! YOU'LL REALLY KNOW HOW TO USE **OSCILLOSCOPES!**

Here, at last, is a practical book

Here, at last, is a practical book that makes it easy for you to learn to use the oscilloscope FULLY on all types of AM. FM and TV service work and dozens of other applications besides!

MODERN OSCILLOSCOPES AND THER USES, by Jacob H. Ruiter, Jr. of Allen B. DuMont Labs contains 326 fact-janumed pages of just the help you need—written so you can easily understand it. The book shows exactly how the 'scope works; how to use it on all service jobs from troubleshooting to realigning; how to make connections; how to adjust circuit components; how to set controls and how to analyze patterns. You get exact procedures on how and where to use your 'scope'... not just theory! 370 illustrations including pattern photos make things doubly clear.



why and exactly how to y 0 U 7 scope.

> How to Interpret patterns

How to handle tough jobs in less time

10-DAY FREE TRIAL

Dept,	RN-124,	RIN	IEHAR	T &	CO.,	INC
222 M	1		Mass	Vac	- 14	M V

Send MODERN OSCILLOSCOPES AND THEIR USES for 10-day FREE EXAMINATION. It I decide to keep the book, I will then remit \$6.00 plus a few cents postage in tull payment. If not, I will return book postpaid and owe you nothing.

NAME.				٠.		 	 ٠	• • • •	 • • •	
ADDRI	38					 	 		 •••	
4 1 2 22 2 2 2		11.5	C-FIS	. 77	112					

OUTSIDE U.S.A.—Price \$6.50 cash wit Money back it book is returned in 10 days.

Section 2012 The Control of the Cont **ELECTRONICS'** NEW

We have just been appointed distributors for PRECISION RADIATION, PENTRON, HALLICRAFTERS and other top commercial equipment!

 \bigstar \bigstar We will ship all items in these two columns PREPAID! You pay no shipping costs!

WANT \$10,000?

Get Government Bonus by Locating Uranium Ore! MODEL 111-The "Scintillator"



ALL—Ine "Scintillator"

AEC No. SPX11A—Portable Scintillation Counter. Many times more sensitive than Geiger Counters. Lightweight, simple to operate. Detects at depths of a few feet to a few hundred feet depending on conditions. Primarily for URANIUM detection. Shockproof, Waterproof, Tropicalized.

CONTRACTOR TO A TIME TO A	
SPECIFICATIONS	
Probe size	3"
Probe weight	hs.
Box weight4 B	DS.
Ranges	
.05, .25, .5, 2.5 and 5 MR HR \$495	υÜ

MODEL 108—"Snooper"



Sensitive as some of the larger Geiger Counters, the 108 fits easily in hip pucket or pack, Requires no experience to operate. Comes complete with earphones, ore sample and instruction looklet.

5	P	E	CI	F	ıc	Α	T	10)	¥:	s	
S	iz	e	11	11	nr	0	١.					



MODEL 107-"Profes-MODEL 10/—"Froressional Geiger Counter"
AEC No. SGM49B—A Geiger
Counter of the highest sensitivity, accuracy and stability,
Has external prode. The best
Geiger Counter made for field
work. For use in Uranium detection, Civil Defense and
Laboratory.

SPECIFICATIONS

NATIONAL PROPERTY OF DEPOTOR DEPOTOR DEPOTOR DEPOTOR DEPOTOR DEPOTOR DEPOTOR DESCRIPENTARION DE LA PROPERTY DE DESCRIPENTARION DE DESCRIPENTARION

31₂"



MODEL 117—"Special Scintillator'

A highly sensitive Scintillation
Counter at a moderate price. An
ideal field instrument because of its
ruggedness, compactness and light
dustrial, Laboratory, or Uranium use.

PROSPECTORS! Are you looking for price-or uranium! If uranium—stop kidding and order one of the really fine instruments above!

FREE! With order, 143 p. book with full-color illustrations on uranium prospecting!

HALLICRAFTER **SPECIALS**

We Stock the Entire 1955 Line and We Pay All Shipping Costs to Your Door!

S-38D Receiver, 540-32,000 KC, \$49.95 S-53A Receiver, 540-54,500 KC, \$89.95 S-93 Portable Receiver, for SWL, Marine, Aircraft \$99.95 AND ALL OTHERS!

ASK FOR INFO ON OUR EASY TIME-PAYMENT PLAN FOR ALL **MAJOR PURCHASES!**

The New PENTRON!

A Miracle in Hi-Fi at Low Price!



Sensational New CT-1 Recorder

MONOMATIC single-knob control! Your kids can work it! 7½ and 3¼ inches see, record and play back forward and play back forward and backward (dual track). Instatumeous automatic brenking on both reels. Fast forward, fast rewind. Flutter less than 0.5% at 7½ IPS. Exclusive new heads. Two-hour capacity. In attractive 24 one teather-trying case. Records and plays in any position, even while carrying it!

\$9950 Audiophile's net

Prepaid, no shipping cost!

Editing-Key Model TR-4



Prepaid, no shipping costi

3-Speaker Hi-Fi Model HT-225



Prepaid, no shipping cost!

New AM-FM Tuner! Model AFM Tape-Mate

Magnificent performance, professional quality, low-noise grounded-gold R.F. Stage, 5uv sensitivity for 30 dh quieting, Armstrong Discriminator? Automatic Frequency Control, with in-out switching for weak stations. Flat 20-20,000 cps. Separate bass and treble controls. Includes phono preamp with 3 equalization positions, Selector switch choises tange, FM, AM, crystal phono, or magnetic phono. I volt cathode-follower output feeds any amplifier. Flywheel tuning on illuminated slide-rule dial. Beautiful panel is ideal for built-in installations, Not the chempest, but the best at any price? Audiophile net. Prepald, no shipping cost!

Prepaid, no shipping costi

GIFT BUYERS!

Order NOW to insure delivery before Xmas!

NEW MODEL 27-C TESTER \$9.95

(Postage paid!)

RANGES: AC and DC volts (p5/27) 250 1000, IU MA 6-1 IO 100, U MA 6-1 IO 100, Ohms 9-10K, 100K, Grey bakehte panel, metal case. Our tests show them to be within 1%. With test lead and standard penlight battery.

24-HOUR TIME CLOCK SWITCH 90% DISCOUNT!

nistructions. Guaranteed.

(Dealers: Write for quantity discounts.)

(24-NCH PIPE SIZE SOLENOID VALVE. 18

(24-NCH PIPE SIZE SOLENOID VALVE. 18

(24-NCH G. 3A or 24V. to 12V. 6A, or 12V. to
mechanism . \$2.95

TRANSFORMER. 115 v. 60 cycles to 24 v.

(6A, 101 acove solenoid & many other uses. 98c

SELENIUM RECTIFIER. 30 vAC max. 1.2A, Juli
wave. For above transformer & solenoid. \$1.98

POWER FROM THE SUN

Brand new development, brand new units (not surplus). Inunional size SUN BATTERY puts out 2 ma anto 10 ohns in average sunlight. Series-jurallel them for greater output, With data sheet. \$1.98; 3,785.00 (RYSTAL MIKE, GYEAWAY). Sensitive incaring-and capsule sealed in compact, flat container with tunied commands. Crisp clear fit-level output. Heel for the container of the commands of the container with tunied to mindle. The container with tunied capsule sealed in compact, flat container with tunied capsule sealed. Heel for the container of the c

DC ROTARY VOLTAGE CHANGER, 6 VDC to 12 Vit @ 10 A: 12:24 VDC @ 5 A: 23:12 VDC @ 5 A: 23:12 VDC @ 15 A: Sultable for car, matthe, arenaft, radio receivers. No need to change dynamotor, band change motor. \$5.95

INVERTERS-400 CYCLE AC

B-CAST, LIGHTHOUSE, AERO

MN-20C femote controlled navigational direction inder and companient on receiver. Manual 197 moor singlet, complete installation, including receiver, control tox, loop, azimuth control. Left-Right Indicator, place loop transmission line, hear momenter, plure to the transmission line, flex shafts, and schematics.

Receiver & Loop Brand New, with tubes, (Areassaries may be used.)..., \$69.50 (Shipping wt. 75 lbs.)

BABY WINCH



Highly versatile. Use as which barbecue soft drive, hear rotation, or any other heave which requires a low speed, high torque surge of power. Has two output drives. One is spreaded-to-drived while driving ratchet-coupled cable driving the coupled with a perfectly on 8 to 24 V, 60 ey acc. Complete with simple instructions. NEW. .59.95

HERE'S YOUR AMPLIFIER!

Accept our years of building and testing amplifiers as your ginde to the best, and yet a surprisingly inexpensive amplifier. BROURS Model 22A, Ontifut tubes are—hold your hat—2.34 push-buill: Cyazy? No. Just stuly load lines and you will agree. Low its, low and seedlator. Has everything, Unique separate base and trelle controls. 6-position phono qualizer on built-in preaimp, choice of 6 inputs. Next and compact and all I none package! And all for \$129.99 only (Audiophille's net).

\$45.00 HI-FI HEADSET AT \$7.95

Uses annular grouved nia-tic titre cunes with voice coils as in speakers and padded channos ear mufts inset music reproduction, 600 ohms. Checked out with freshly laundered ear pads and long facilities thirte cord with phone itps. (Shp., wt. 3. lbs.), 57.95

G. L. ELECTRONICS, INC.

905 S. Vermont Ave., Los Angeles 6, Calif. Minimum order \$2.50 total, 25% deposit required. All prices F.O.B. Los Angeles. Calif. buyers add sales tax.

The Model TV-50 GENOMETER

A versatile all-inclusive GENERATOR which provides ALL the outputs for servicing: -


A. M. Radio

F. M. Radio

Amplifiers

Black and White TV

Color TV

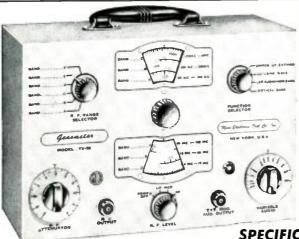

7 Signal Generators in One!

- ✓ R. F. Signal Generator for A.M.
- ✓ R. F. Signal Generator for F.M.
- Audio Frequency Generator
- **∠** Bar Generator
- Cross Hatch Generator
- ✓ Color Dot Pattern Generator
- Marker Generator

SPECIFICATIONS:

R. F. SIGNAL GENERATOR:

The Model TV-50 Genometer provides complete coverage for A.M. and F.M. alignment. Generates Radio Frequencies from 100 Kilocycles to 60 Megacycles on fundamentals and from 60 Megacycles to 180 Megacycles on powerful harmonics. Accuracy and stability are assured by use of permeability trimmed Hi-Q coils. R.F. is available separately, modulated by the fixed 400 cycle sine-wave audio or modulated by the variable 300 cycle to 20,000 cycle variable audio. Provision has also been made for injection of any external modulating source.

VARIABLE AUDIO FREQUENCY GENERATOR:

In addition to a fixed 400 cycle sine-wave audio, the Model TV-50 Genometer provides a variable 300 cycle to 20,000 cycle peaked wave audio signal. This service is used for checking distortion in amplifiers, measuring amplifier gain, trouble shooting hearing aids, etc.

BAR GENERATOR:

This feature of the Model TV-50 Genometer will permit you to throw an actual Bar Pattern on any TV Receiver Screen. Pattern will consist of 4 to 16 horizontal bars or 7 to 20 vertical bars. A Bar Generator is acknowledged to provide the quickest and most efficient way of adjusting TV linearity controls. The Model TV-50 employs a recently improved Bar Generator circuit which assures stable never-shifting vertical and horizontal bars.

CROSS HATCH GENERATOR:

The Model TV-50 Genometer will project a cross-hatch pattern on any TV picture tube. The pattern will consist of non-shifting, horizontal and vertical lines interlaced to provide a stable cross-hatch effect. This service is used primarily for correct ion trap positioning and for adjustment of linearity.

DOT PATTERN GENERATOR (For Color TV)

Although you will be able to use most of your regular standard equipment for servicing Color TV, the one addition which is a "must" is a Dot Pattern Generator. The Dot Pattern projected on any color TV Receiver tube by the Model TV-50 will enable you to adjust for proper color convergence. When all controls and circuits are in proper alignment, the resulting pattern will consist of a sharp white dot pattern on a black background. One or more circuit or control deviations will result in a dot pattern out of convergence, with the blue, red and green dots in overlapping dot patterns.

MARKER GENERATOR:

The Model TV-50 includes all the most frequently needed marker points. Because of the ever-changing and ever-increasing number of such points required, we decided against using crystal holders. We instead adjust each marker point against precise laboratory standards. The following markers are provided: 189 Kc., 262.5 Kc., 456 Kc., 600 Kc., 1000 Kc., 1400 Kc., 1600 Kc., 2000 Kc., 2500 Kc., 3579 Kc., 4.5 Mc., 5 Mc., 10.7 Mc. (3579 Kc. is the color burst frequency.)

The Model TV-50 comes absolutely complete with shielded leads and operating instructions.

\$4750 NET

SHIPPED ON APPROVAL NO MONEY WITH ORDER - NO C. O. D.

Try it for 10 days before you buy. If completely satisfied then send \$11.50 and pay balance at rate of \$6.00 per month for 6 months. No Interest or Carrying Charges Added! If not completely satisfied return unit to us, no explanation necessary.

MOSS ELECTRONIC DISTRIBUTING CO., INC. Dept. D-84, 3849 Tenth Ave., New York 34, N.Y.

Please rush one Model TV-50. I agree to pay \$11.50 within 10 days and to pay \$6.00 per month thereafter. It is understood there will be no carrying, interest or any other charges, provided I send my monthly payments when due. It is further understood that should I fail to make payment when due, the full unpaid balance shall become immediately due and poyable.

Name							
Address							
CityZoneState							



Model 670-A

Superior's new SUPER MET

A COMBINATION VOLT-OHM MILLIAMMETER PLUS CAPACITY REACTANCE INDUCTANCE AND DECIBEL MEASUREMENTS

SPECIFICATIONS:

D.C. VOLTS: 0 to 7.5/15/75/150/750/1,500/7,500 Volts A.C. VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts OUTPUT VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts D.C. CURRENT: 0 to 1.5/15/150 Ma. 0 to 1.5/15 Amperes RESISTANCE: 0 to 1,000/100,000 Ohms 0 to 10 Megohms CAPACITY: .001 to 1 Mfd. I to 50 Mfd. (Good-Bad scale for checking quality of electrolytic condensers) REACTANCE: 50 to 2,500 Ohms, 2,500 Ohms to 2.5 Megohms INDUCTANCE: .15 to 7 Henries 7 to 7,000 Henries DECIBELS: -6 to +18 +14 to +38 +34 to +58

ADDED FEATURE:

Built-in ISOLATION TRANSFORMER reduces possibility of burning out meter through misuse.

The Model 670-A comes housed in a rugged, crackle-finished steel cabinet complete with test leads and operat-



Superior's new Model TV-11

SPECIFICATIONS:

- ★ Tests all tubes including 4, 5, 6, 7, Octal, Lock-in, Peanut, Bantam, Hearing Aid, Thyratron, Miniatures, Sub-Miniatures, Novals, Sub-minars,
- Miniatures, Sub-Miniatures, Novals, Sub-minars, Proximity fuse types, etc. Uses the new self-cleaning Lever Action Switches for individual element testing. Because all elements are numbered according to pin-number in the RMA base numbering system, the user can instantly identify which element is under test. Tubes having tapped filaments and tubes with filaments terminating in more than one pin are truly tested with the Model TV-II as any of the pins may be placed in the neutral position when necessary.
- when necessary.

 The Model TV-II does not use any combination type sockets. Instead individual sockets are used for each type of tube. Thus if is impossible

to damage a tube by inserting it in the wrong

- socket.

 ★ Free-moving built-in roll chart provides complete data for all tubes.

 ★ Newly designed Line Voltage Control compensates for variation of any Line Voltage between 105 Volts and 130 Volts.

 ★ NOISE TEST: Phono-jack on front panel for plugging in either phones or external amplifier will detect microphonic tubes or noise due to faulty elements and loose internal connections.

The model TV-II operates on 105-130 Volt 60 Cycles A.C. Comes housed in a beautiful hand-rubbed oak cabinet complete with portable cover. lator incorporated in this model will detect leakages even when the frequency is one per minute

EXTRA SERVICE—The Model TV-11 may be used as an extremely sensitive Condenser Leakage Checker. A relaxation type oscil-

SUPERIOR'S NEW MODEL TV-40


TOBE TEST

A complete picture tube tester for little more than the price "make-shift" adapter!! of a

The Model TV-40 is absolutely complete? Self-contained, including built-in power supply, it tests picture tubes test such tubes, that is, by the use of a separate instrument which is designed each stept to test the ever increasing number of picture tubes?



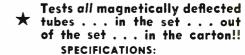Simply insert line cord into any 110 volt A.C. outlet, then attach tester socket to tube base (ion trap need not be on tube). Throw switch up for quality test . . . read direct on Good-Bad scale. Throw switch down for all leakage tests.



- Tests all magnetically deflected picture tubes from 7 inch to 30 inch types.
- Tests for quality by the well established emission method. Alf readings on "Good-Bad" scale.
- Tests for inter-element shorts and leakages up to 5 megohms.

Name

Address..... City...... Zone... State......

· Tests for open elements.

Model TV-40 C.R.T. Tube Tester comes absolutely complete—nothing else to buy. Housed in round cor-nered. molded bakelite case. Only

MONEY WITH ORDER -- N

Try any of the above instruments for 10 days before you buy. If completely satisfied then send down payment and pay balance as indicated on coupon. No Interest or Carrying Charges Added! If not completely satisfied return unit to us, no explanation necessary.

MOSS ELECTRONIC DISTRIBUTING CO., INC. 3849 Tenth Ave., New York 34, N. Y. Dept. D-84

Please send me the units checked. I agree to pay down payment

within 10 days and to hay the mouthly balance as shown. It is understood there will be no carrying, interest or any other charges, provided I send my mouthly payments when due. It is further understood that should I rail to make payment when due, the full unpaid balance shall become immediately due and Dayable.

□ Model 670-A.....Total Price \$28.40 \$7.40 within 10 days. Balance \$3.50 monthly for 6 months.

☐ Model TV-11......Total Price \$47.50 \$11.50 within 10 days. Balance \$6.00 monthly for 6 months.

Model TV-40.......Total Price \$15.85 \$3,85 within 10 days. Balance \$4.00 monthly for 3 months.

December, 1954 109

Ham News from hallicrafters chicago 24, Illinois

......

IN CANADA: BOX 27 TORONTO 17: ONTARIO

Model SX-96 SELECTABLE SIDEBAND RECEIVER

- Covers Broadcast 538-1580 kc plus three S/W 1720 kc—34 Mc.
- Full precision gear drive dial system.
- Double conversion with second oscillator crystal controlled.
- Selectable side band reception of both suppressed carrier and full carrier transmissions.
- · Mixer type second detector.
- · CW operation with AVC on.
- · Delayed AVC.
- Calibrated bandspread "S" meter double superhet.
- 10 tubes, 1 rectifier and voltage regulator.



MANUFACTURERS' LITERATURE

The various listings presented in this section are for your convenience. The bulletins, unless otherwise indicated, are available to all our readers. For prompt attention write directly to the manufacturer for this literature.

MOBILE ANTENNA HARDWARE

K-W Engineering Works, 3145-A North 48th Street, Milwaukee 16. Wisconsin, has issued a data sheet covering its "Universal" mobile antenna hardware line.

The catalogue sheet covers mobile antenna base sections, antenna extensions, and accessories designed to provide the amateur radio mobile operator with a complete range of base sections and extensions from 6 to 36 inches in 6 inch steps, plus collets, female and male couplings, etc.

SEALED PANEL METERS

A new 2-color, 2-page data sheet describing its 1½-inch sealed square panel meter has been released by DeJur-Amsco Corp., 45-01 Northern Blvd., Long Island City 1, N. Y.

The publication describes features and gives detailed specifications, actual size illustrations, schematic diagrams, ranges, resistance, and ordering information on the line. The instruments are designed for front or rear mounting and are available with various scale markings.

The Electronic Sales Division of the company will provide a copy of this data sheet, Model 152, on request.

COLLINS TRANSMITTER

An 8-page booklet describing the company's new 17L-4 v.h.f. transmitter has been released by Collins Radio Company of Cedar Rapids, Iowa.

The booklet describes in detail the 25-watt. 360 channel, v.h.f. transmitter for aircraft communication. The publication includes a block diagram, outline drawing, complete specifications, and performance data on the transmitter as well as details and specifications on associated equipment to be used with the unit.

GLASS PRODUCTS DATA

Corning Glass Works, Corning, N. Y., has announced the publication of a new catalogue of glass products for the electronic industry.

The catalogue includes descriptive and application information for fixed glass dielectric and trimmer capacitors; accurate grade, high temperature, power, and high-frequency resistors, and other components made of glass.

Also included in the new publication is descriptive material covering new compositions and production methods in glass such as glass-to-metal seals, soldering metal-to-glass, photosensitive glass, and fused silica.

Copies of the new catalogue (NP-54)

are available from the New Products Technical Information Department of the company.

MOBILE POWER PLANTS

D. W. Onan & Sons, Inc., Minneapolis 14, Minn., is offering a special issue of its company publication, "Power Points Digest." which discusses the use of electric generating plants in mobile service.

Many interesting mobile installations are described in this pocket-size, two-color, 20-page booklet. When writing for a copy of this publication, please specify Vol. 10, No. 4, of "Power Points Digest."

BACKGROUND MUSIC

Magnecord, Inc., 1101 S. Kilbourn Avenue, Chicago 24, Ill., has prepared a colorful 12-page brochure describing its new background music service.

The purpose of the promotion piece is to present dramatically the major advantages of the company's background music. Emphasis is placed on the scientifically blended musical programs from the *RCA Victor* library of recorded music, and performance features of the new *Magnecord* continuous music reproducer. The instrument automatically plays eight hours of music, continuously or intermittently, without musical repetition, using magnetic tape reels.

RADIO SHACK'S CATALOGUE

Radio Shack Corporation, 167 Washington St., Boston 8. Mass., is now offering copies of its 1955 electronic parts mail-order catalogue.

The new edition lists and illustrates 30,000 radio, TV, and electronic products in 224 pages and has a 32-page roto section devoted exclusively to hi-fi custom music systems. It includes a manufacturers' index on the front cover, an 18-category thumb index, and an extensive product listing. The front cover index has over 250 manufacturers and the product index lists over 1500 items.

The catalogue is available without charge upon request.

PRINTED CIRCUIT REPAIR

Admiral Corporation's national service department, 201 E. North Water Street. Chicago 11, Ill., has just published a six-page illustrated manual covering the service and repair of printed circuits used in all of the company's radios and in many of its TV receivers.

Copies of the new printed circuit service manual, No. S559, are available

Remember QUALITY CANNOT BE UNDERSOLD This is our 34th YEAR as



DOUBLE CONYAGI

The equivalent of 40 dipoles

Newest development for Newest development for long distance TV reception, MONEY BACK GUARANTEE. This is a BIG ANTENNA. Reflectors 9 feet long, Conical elements over 10 feet long. Solid rugged wind proof construction.

15t Price \$15.95

RADAR TYPE TV ANTENNA

For UMF and VMF RECEIVES ALL CHANNELS 212 miles reception recorde 125 miles common. This unbea able antenna has been reinforct to withstand 150 mile winds.

Satisfaction guaranteed or your money back. Mast, List Price \$49.95. \$19.95 Your Cost



CONICAL TV ANTENNA

Doudbie bay array, with bars \$7.25

4 Bay array, with harness and stacking \$14.95

UHF BOW TIE ANTENNA

TV MASTS AND

HARDWARE

Bargain Chimney Mount Net \$1.49

Stainless Steel Chimney Mount. \$2.50
Net

Twin lead ins each 3c Mortar nail insulator each 8c each 17cn foot mast. Seamless, expanded end, sturdy enough for the largest arrays.

Factory assembled, single-bay Each Two-bay array with matching

10 Element conical rugged through. \$3.95

PREMIER Unconditionally Guarantees All Tubes For One Full Year VERY BEST BRANDS AVAILABLE FOR IMMEDIATE DELIVERY. INDIVIDUALLY BOXED.

SEKI DES	I DENUTO NAMI	TWOLE LAW IMIM	COINTE DELIVE	KI. INDIVIDUALL	I BUALU.
DA461.19	5AC5GT89	6F5GT PA-	6X8 1.29	12BH7 89	35Y4 AC -
0Z4 59c	EAC7 1.49	6F5GT 59c	6Y6G COA	128Y7	15 74 95 ¢
0Z40 JJU	6AF4 1.36	6F7 1.59	676G 624/84 69C	128271.19	35 Z4 61
1A5GT .79	6AG5 99	6F8G 1.59	7 44 95	12F5GT69	35 25 51
I A/GI	6AG7 1.49	6G6G	7 AS 1.19	12H6	35/51 7)
1B3GT .95	6AH6 1 E9	6H6GT #9	7 A E	1235GT 69C	35 950
185 29c	6AJ5 2.56	6J5GT .59	7A7 79C	12K7GT 09C	37 33"
THEGT 59	6A #5 89 6A #6 1.19	1.16	784 89	12Q7GT	38 39/44 88C
IJAGT 59c		6J7G	7 H5 89	1258	41
11.4 39 C	6AG5 69c	6J8G 1 13	7 HE 99	12SA7GT69	40.
LL6 1.29	6A06. 79	6K5GT 69	785 89c	12SC7 95	
ILA4119	6AQ7 1 19	6K6GT 59 6K7GT 69	788. 09C	12SF5GT55	
1L A6 1.19	6AR579	6K7GT 69 6K8GT 113	7C4 1.29	12St 7	15/5 69
	6ATE 59 6AS5 89	6L5G	70589 705 30	12SH2GT	4 89 c
11.051.19	6AU5GT 129		70779c	12S 17GT /	47 07 6
11E3 119	6AU659	GL 6GA	765 76	125 J 7 GT 69	50A5 .95
LL H4 119	6AV5GT 89	6L7 1 19	7E6 79 C	12\$L7GT	2082
11. N5 1.19	6AV6 59	6N6G 1.29	7E7 17 G	12SN7GT95	2003 000
INSGT TO	9834	6N7GT 1.19	7F7	125 U7 LO-	50C6G 1 79
1P5 GT 79c	5883/9	6P5GT 89	7 F 8 1.49 7 G 7 1.19	125 07 GT 69 C	50 x6
5 D4	6AX 69 6AY5GT 89	6R7GT 69	7 G7 1.19 7 H2 95	1.223 95	50Y6 95
15495	6B4G 129	6S4 59		1447 OF a	51 70 .
	5H8GT 1.19	657GT 1.19	717 7kJ 1.19	14AF7 934	58 130
69c	6BA6 59	658G1 1.13	717 73	1486 00 -	7 (L7 1.49
104:		6SA7GT 69C	7 N.F	1488 03 G	70L7GT 1.47
105	6BC5 69 6BD5GT 89 6BE5 59 6BF5 CO	6SC7 DJC 6SD7GT99	7 g 7 79 7 F 1 19 7 S 7 1 19	1405 1.19	714 790
IXZA QQ	PR0301 83	6SD7GT	757 110	14C7 95c	77 63
2A6 07C	6BF5 CO.	SF5GT59	777 7	14/8 1 00	78/6D6
2A1	6BF5 69c		7w7. 115	1.29	BD
2B389		65 H7 69 C	7 Y Q6	14 (1/ 95	
28789	6BG6 1.89	6SH7GT69	7X7 79c	14 W7 119	83 1 49 84/6Z469
2E5 .89 2 X2 /87979	68% 69c	6SJ7GT .79	7Y4 / 9C	1437 119	
31 FA 1 29	5BK7 1.19	6SJIGT 59c	7 Z 4 89 1 Z A 7 1.49	198G6 1.89	85
304 69	4BK7 1.19 4BL7 79	6SL7GT69	12A8	1978 89	VR90 \$1 19
3Q5GT 89	4BL7 79 BN6 1 19	6SN7GT79	12AH7 1.49	24A 69	VR150 1.17
3Q4 .69 3Q5GT 89 3S4 .69	6006G . 119	65/12	12AL5 En-	25AC5GT . 1 19	
3v4 .95 5 14 .1.29	68Q6GT . 119	65 07 GT 59 C	12AT6 43	25 BQ6GT. 1.19	VI51 29 C
5 T4 1.29 5 U4G 69	1.29	6S R7GT	12AT7 89 12AU6 69	25 BQ6GT. 1. 1 J 25 L6GT 59	1171.7 1.49
5 U4G 69 5 V4G 89	6827 1.23 6C4 59	6SS7 99 6T8 .89	12AU7 .79	25 W4GT69	117 N7 1.89
		6116	12AV6 .59	25.25 .69	117P7 1 #9
5W4GT 59C	£C6 60	SUGGT AU	12AV7 .89	2526GT 69	11773 55
5Y3GT 49	ECR6 U/L	606GT 69C	12AW6 1.19	32L7GT 95	11726 1.19
5 Y 4G	£C8 1 29	F08 83	12AX4 .69	26 59 c 27 5 A5	7158 5 10
5 x 4G 97C	EC 266 1.89	V3 1 29	IZAX/ by	27 JJC	807 149
6A7 89	CC 66 1.09		12AY7 189 12BA6 59	35 A5	866A 149
6A8GT 1.29	ECF6 ED6/78 1,19	6W6 69	12BA7 1 19		1299 40 .
6AB4 69	6D8G 1.19	6X4 59c		35L6 07C	1619 49
oAB7 1.19	6E5 69	EXSGT DYC	12BE6. 69C	35W4 .59	2051 46

10% DISCOUNT ON ORDERS OF 100 TUBES OR MORE— 5% DISCOUNT ON 50 TUBE ORDERS

300 OHM TWIN LEAD



UHF TUBULAR 300 OHM LINE 1.000 ft.\$29.50 100 ft. \$3.95

All Channel Foam Line, 100 ft. for \$6.95. 50 ft. for \$3.95.

FOUR CONDUCTOR Rotor Cable Clear or Brown. Very Special, \$14.95

FILTER CONDENSERS

0 by each \$\Psi\$ 5 ft. DURABLE MAST, heavy Rauge 1\(^1/4\), alignment of the interlocking end. Slip two sections together for a ten-footer. 5 sections = 25 ft. Each section \$1.25 MISCELLANEOUS BUYS

I. F. TRANSFORMER—
456 Kc. 19c
PILOT LIGHTS. Type No. 47
10 for 39c: 100 for \$2.95
VOLUME CONTROL WITH
5WITCH. 2" shaft; 1 meg.
1/2 meg. 1/4 meg. ... 34c
SINGLE ION TRAPS. ... 19c
DOUBLE ION TRAPS. ea. 29c

TUBE KITS

BEST BRANDS AT BEST PRICES

	RE	CTI	F	IEI	RS
	65	mH.		. \$.69
	75	mil.			.79
-	100	mii.			.89
	150	mit.			1.29
	250	mil.			1.65
	300	mil.			1.75
- 1	350	mit.			1.95
1	400	mil.			2.45

SELENIUM

FP Type or Tubular with Leads—Fresh Stocks Always

n myu.	43U V .	.33	AO IIII G.	300.	11.
B-8	450V.	.45	20.	50V.	15
10-	450V.	.39	25-	50V.	.19
10-10	450V.	AE	50-	50V.	.29
20-	450V.	.45	100-	50V.	.29
20-20	450V.	.49	20 mfd.	150V.	.35
30-	450V.	.45	20-20	150V.	A C
30-30	450V.	.59	30	150V.	.45
40	450V.	.49	30-30	150V.	.49
40-40	450V.	CO	40	150V.	.45
60	450V,	.69	40-20	150V.	
60-40	450V.	.89	40-40	150V.	.49
80	450V.	.69	50-30	150V.	.49
80-40	450V.	1.29	1		

OUTPUT TRANSFORMER—for 50L6, 29c; for 6V6, 39c

only 354, 1T4, 1S5, 1R5. List Value \$7.80. 4-Tube Kit 1U4, 354, 155, 1R5. List Value \$7.80. All Four 1U4, 354, 1S5, 1R5. List Value \$7.80. All Four Tubes for 11723, 1U5, 354, 1R5, 1T4, AC-DC Portable Kit. All for 12AT6, 12BA6, 12BE6, 3SW4, 50B5.

COAXIAL SPEAKERS

voice coil

coakial speaker. Take advantage of

TV set's FM sound. This speaker

thes and replaces 80% of all TV

SPEAKER KIT

Complete with heavy magnet 6 x 9 PM speaker, grille, screen, switch kit, switch plate and bracket, all wiring harness and complete instructions.

REGENCY RC-53

BRAND NEW TV PICTURE TUBES

SIZE All Tubre Have Pipe Comments of the Comme	Daylight Type Dark "A" of SIZE SERVA 16" . 21.95 16 PAR 16" . 22.20 16 PAR 16" . 22.20 17 PAR 16" . 22.95 17 PAR 17" . 22.95 17 PAR 17" . 26.90 17 PAR 17" . 26.90 17 PAR 17" . 26.90 19 PAR 18" . 28.90 19 PAR 19" . 28.90 19	\$12E PRICE 20094 20" 27.95 20094 20" 27.95 20094 20" 27.95 20.94 21" 30.10 21594 21" 30.95 21594 21" 36.95 21594 21" 36.95 21594 21" 31.95 24594 21" 31.95 24594 24" 60.53.95 24594 24" 75.95 27594 27" 78.55 27594 27" 79.95 277994 27" 79.95 277994 27" 79.95 277994 27" 79.95 277994 27" 79.95 277994 27" 79.95 277994 27" 79.95 277994 27" 79.95 277994 27" 79.95 277994 27" 79.95 277994 27" 79.95 277994 27" 79.95 27" 79.

RESISTOR KITS

Insulated $\frac{1}{2}$, 1 and 2-wattassortment of most used values, I. R. C. Ohmite, Stackpole, Speer.

100 for. \$2.95

P M SPEAKERS

Flyback Trans-former TV Hori-zontal output, universal replacement, 14,-500 V.

2.49 ea.



All channel UHF Converter. Much more gain than strips, and fits any set. Only ... \$14.96

PICTURE TUBES

Soldering
Gun
Extra long narrow tips to reach tight spots. Practically indestructible, Cally indestructible, 135 watts!

New WEN "Quick HOT"

21" TV CONVERSION KIT COMPLETE WITH CABINET AND NEW TUBE

15 Month Guarantee Now you can make that conversion. This table model cabinet eliminates your bottle neck. Supplied complete with 21 picture tube, 70 plate, 49 back transformer and width coil, very easy to install and all for \$50.00

TV CONVERSION KITS

ALL NEW TUBES
15 Month Guarantee
Easily installed consist-
70 degree yoke, beauti-
ful mask, flyback trans-
former and width coil. 17" Kit, as above, complete\$25.95
20" Kit, as above, complete 29.95
21" Kit, as above, complete 34.95 24" Kit, Rectangular 79.95
24" Kit. Round 69.95
27" Kit, as above, complete. 99.95
24" & 27" Rectangular Kits contain

Write for our FREE BARGAIN CATALOG

TERMS: 25% DEPOSIT with order, balance C.O.D. ALL shipments F.O.B. Chicago. ORDERS LESS THAN \$5.00—\$1.00 SERVICE CHARGE. CABLE ADDRESS: CONTULAB. These prices supersede all previously advertised prices, subject to change

PREMIER TV RADIO SUPPLY, division of CONTINENTAL CORPORATION

3239 West North Avenue, Chicago 47, Illinois ARmitage 6-5550 December, 1954


A Hot am News from

CHICAGO 24, ILLINOIS

IN CANADA: BOX 27 TORONTO 17, ONTARIO

Model HT-30 SINGLE SIDEBAND TRANSMITTER/EXCITER

- . Highly stable VFO with full 100:1 ratio gear drive system built-in.
- Stability comparable to most crystals .01%.
- Ample gain for 55 db microphone with hum and noise 40 db down.
- · Full 40 watt lineal peak power output.
- Unwanted sideband at least 40 db down.
- Undesired beat frequency down 60 db or more.
- T. V. I. suppressed.
- Provisions for coaxial output fitting.
- Built-in voice control circuit with bias switching for final amplifier.
- AM-CW-SSB-19 tubes plus voltage regulator and 2 rectifiers.

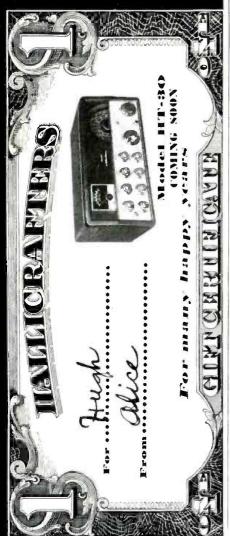

without charge from all of the company's distributors or from the service department direct.

COMPONENTS CATALOGUE

Herman H. Smith, Inc., 2326 Nostrand Ave., Brooklyn 10, N. Y., has issued a new components catalogue listing its complete line of plugs, jacks, connectors, switches, terminals, and hundreds of other electronic components and accessories.

The 24-page publication includes schematic dimensional diagrams which will be of interest to the engineer as well as the purchasing agent.

When writing for a copy of this publication, please specify Catalogue No.

WIRE AND CABLE DATA

Chester Cable Corp. of Chester, N. Y., has issued a six-page folder describing and illustrating its line of wires and cables for the radio, electronic, and television industries.

Included in the listings are TV leadin; coaxial cables; microphone cables; intercom, control, and audio cable; twisted pairs; phono pickup arm cable; h.f. lead wire; antenna loop wire; telephone cable, etc.

VARIABLE INDUCTANCES

An informative four-page bulletin describing shop and laboratory application of a kit of eight permeabilitytuned inductances covering a range of from 1 to 1000 µhy, is now available from United Technical Laboratories of Morristown, N. J.

The bulletin is a reprint of John T. Frye's article "Using Calibrated Variable Inductances" which appeared in the August issue of Radio & Television NEWS

NEW "RADIO'S MASTER"

The new 1954-1955 (19th) edition of "Radio's Master" has been released by United Catalog Publishers, Inc., 110 Lafayette St., New York 13, New York.

This 1440-page catalogue, bound in hard covers, contains more than 85.000 items, over 9000 illustrations—all with full descriptions and specifications.

The catalogue may be purchased from parts distributors throughout the country. For a list of distributors handling this catalogue, write the publishers direct.

"CONTROLA-TONE" FLYER

Controla-Tone Company, 111 No. Tacoma Ave., Tacoma 2, Wash., is now offering a small flyer which explains and describes its new, improved L-pad model remote volume control.

This two-color folder illustrates how the unit can be installed and used with any TV receiver.

SOLA BOOKLET

Sola Electric Co., 4633 W. 16th Street, Chicago 50, Ill., has released copies of its latest publication, "The Sola Constant Voltage Transformer; Theory of Design and Operation.'

The 20-page, fully-illustrated booklet has been written for electrical engi-

TG-34A CODE KEYER

Self-contained automatic unit, Self-contained automatic unit, reproduces code practice signals recorded on paper tape. By use of built-in speaker, provides code-practice signals to one or more persons at speeds from 5 to 25 WPM.

BRAND NEW, in 2400 F BRAND NEW. in \$18.95

TG-10 CODE KEYER, complete with 7 tubes and \$17.50

FL8-A RADIO FILTER \$1.59

ŀ	HEADPHONES Excel	ent BRAND
Model	Description Us	
HS-23	Bleb Impedance \$2.	25 \$4.35
HS-33	Low Impedance 1.	79 4.65
HS-30	Low Imp. (featherwt.) 1.	49 1.85
H-16 U	High Imp. (2 units) 2.	75 7.95
CD-307A	cords, with PL55 plug and	

		Excellent	BRAND
Model T.17	Carbon Hand Mike		\$7.99
T-30	Carbon Throat Mike	.33	.69
T.45	Navy Lip Mlkc		1.25
RS-38	Navy Type	1.95	5.99
T-24	Cargon Mike		3.99

SCR-274 COMMAND EQUIPMENT

ı	Type		USED	Excellent	BRAND
	BC-453	Revr. 190-550 Ke	18.50	\$21.50	\$37.50
ı	BC-454	Heyr. 3-6 Mc	8.25	11.25	19.50
-	BC-455		7.95	10.95	15.45
ı	BC-456			2.75	4.65
	BC-457	Xmtr. 4-5.3 Mc	11.95	14.50	22.95
		Xmtr. 5.3-7 Mc	7.95	9.75	21.95
I	BC-459		11.95	12.95	21.25
-		Nmitr. 3-4 Mc	18.95	27.95	1111
I		3-Reyr Control Box.		1.49	1.95
		Xmtr. Control Box.		1.25	1.49
		ver Rack		1.79	2.95
ı	2.Trans	mitter Back		1.59	3.25
_	Single	Transmitter Rack			3.25

FAMOUS BC-645 XMITTER-RECEIVER



Makes wonderful mobile rig for 420-500 Me. Easy to convert for phone or tig to to convert for phone CW 2-way communicate CONVERSION DI GRAM INCLUDED. T swell rig arrabally cover \$1000-yours practically a song! get it all, in original flory carton. IRA

NEW tory carron. BRAND NEW, complete with 17 titles, less power supply. Ships, wt. 25 lbs.... \$29.50 PE-101C DYNAMOTOR for BC-645, has 12-24V input (easy to concert for 6V Battery operation) \$4.85 UHF ANTENNA ASSEMBLY. \$2.45

TOT BC-045 CONVERSION BOOKLET. Instructions \$2.50 for most useful surplus rigs.

DYNAMOTORS

) I NA	MP	7101	(2	
Туре	fni	out	Out		ccellent Used	BRAND
DM-49	14V	3.4A	172V	.138A	1.95	3.95
DM-42A	14V	46A		030 /2 8 215 /260	12.95	16.95
DM-43A	28 V	23 A		030/2/8 215/260	29.50	
DM-32A	28V	1.1A	250V	.05A	2.95	7.50
DM-34D	12V	2.8A	220V	A080.	11.95	
DM-35D	12.51	/ 18.7A	625 V	.225A	9.95	
D M - 36	28V	1.4A	220V	A080.	9.95	
D M-37	25.51	9.2A	625 V	.225 A	12.95	
D M-28	28V		224V	.07A	1.95	4.95
D M- 53 A	28V	1.4A	220V	A080.	2.95	6.95
D M-33 A	28V 28V	5A. 7A.	575V 540V	.16A .25A	1.95	3.95

GOULD 6-VOLT STORAGE BATTERY

Amp. Hour Rating, Navy landard, Black Bubber Case, BRAND NEW\$5.95



WILLARD 6-VOLT MIDGET STORAGE BATTERY

WILLARD 2-VOLT STORAGE BATTERY

WILLARD Z-YOLI 31-CRAD REW Plastic Case S1.95
1-QUART ELECTROLYTE, enough for two cells. \$1.45 include 25% Deposit with order-Balance MINIMUM ORDER 53.00, All Shipments Our Warehouse N.Y.C.

Radio Supply Co. Dept. N-12 51 Vesey St., New York 7, N. Y., CO 7-4605

neers and others interested in the underlying electromagnetic relations of the *Sola* constant voltage principle. It contains schematic diagrams, vector diagrams, performance curves, and photographs illustrating typical assemblies.

The "Globe Scout"

(Continued from page 55)

There are several precautions to be observed when tuning up the transmitter so that proper operation is insured. When tuning the oscillator on the 20-, 15-, or 10-meter bands, two resonance points will be found. One point of resonance is double the 40meter crystal frequency and the other is triple the 40-meter crystal frequency. The doubling resonance point is at approximately 34 full capacity, or when the indicator arrow is toward the left side of its scale. The tripling resonance point is at approximately 14 of full capacity, or when the arrow is toward the right side of its scale.

When operating on the 20- or 10-meter band, tune the oscillator to the doubling resonance point. When operating on the 15-meter band tune the oscillator to the tripling resonance point.

When tuning the final plate control on the 160-meter band two resonance points will be observed. One will be toward maximum capacity or when the arrow is toward the left side of its scale. This is the 160-meter resonance point. The other resonance point is close to minimum capacity of the tuning capacitor, the arrow towards the right side of the scale. On the 15meter band there are also two resonance points. One resonance point is at 20 meters and will be found at approximately 1/2 of full capacity. The other and correct resonance point is at approximately 14 of full capacity or with the arrow facing towards the right side of its scale.

Summing up, the tuning capacitor settings for each band are given in Table 1 with the fractions indicating the approximate quantity of full capacity.

A long wire antenna is not recommended when operating in a TV fringe signal area. A doublet or folded dipole, half-wave antenna at the operating frequency will give much better results. The long wire, or end-fed antenna, may be used only if it is approximately ½ wave long at the operating frequency.

The main objective is to reduce the standing wave ratio on the feed line to a minimum; this will automatically reduce harmonic radiation and TVI. This point cannot be over-emphasized as it is very important in the suppression of TVI and BCI and, at the same time, permits a much better signal radiation from the antenna. A little extra time spent on a properly tuned antenna system will more than repay the operator in better QSO's and less radiated interference.



20" CORNER FOLDED HORN FOR 8" AND 12" SPEAKERS

THE LITTLEST REBEL, The KR-5, approaches Klipschorn performance on light, middle bass. Heavy pipe organ bass is even more amazing with smooth, clean reproduction completely free from unmusical boom and distracting distortion. This latest Klipsch design by Cabinart, fifth in the CABINART-KLIPSCH REBEL series, is available in all fine woods, utility birch and, for portable hi-fi, strikingly smart leatherette.

Wall mount the Rebel 5, hang or set it in a corner. Place it on a table — a bench — a shelf — anywhere! Performance ... absolutely unbelievable! See your nearest Cabinart hi-fi dealer or write for catalogs.

Finished \$48.00

Utility \$33.00



75 North 11th Street, Brooklyn 11, N. Y.

* Trade Mark



CHICAGO 24, ILLINOIS

IN CANADA: BOX 27 TORONTO 17, ONTARIO

Model SX-99 RECEIVER

Here is everything you could wish for in a DX receiver. Covers Broadcast Band 540-1680 kc plus three short-wave bands 1680 kc-34 Mc calibrated for the 10, 11, 15, 20, 40 and 80 meter amateur bands over a large easy-to-read dial. Features for the amateur—"S" meter, separate bandspread tuning condenser, crystal filter, antenna trimmer, one r-f, two -if plus 3.2 and 500 ohm speaker terminals.

Gray-black steel cabinet with brushed chrome trim and piano hinge top, 18% x 81/2 x 11". Shipping weight 36 lbs.

Seven tubes plus rectifier. 105/125 V. 50/60 cycle AC. \$149.95 (less speaker). Use Hallicrafters R-46A Speaker.



Tube Checker

(Continued from page 50)

ment is calibrated so that all good tubes read "6" on the meter with the proper input signal.

The tube types to be plugged into each socket are printed on the instrument, together with the correct input for each tube. The most common tubes are listed on top, the others in back. For example: "6AU6-3" would appear next to one of the 7-pin sockets, indicating the 6AU6 goes there and the input control is set at 3.

Two other controls used are a selector switch for 6 or 12 volt heaters, and a selector switch to read either half of a twin tube. This last switch is inoperative for single tubes.

The meter has a 1 milliampere, 50-ohm movement. It is protected from accidental overload by a spring-return "push-to-read" switch. This normally shunts the meter with a 5-ohm resistor, and reduces the reading by a factor of 10. If the shunted reading is higher than 1 on a 0-10 scale, the operator knows something is wrong, without banging the needle of his in-

strument. In a later model, now under construction, a tuning eye is used as the indicator instead of the "pushto-read" switch.

The instrument has another excellent feature. The 6AG5 socket has a 5-megohm resistor in series with its grid. This has practically no effect on a good tube, but a gassy tube will show very little output. This is due to the excessive loss in the grid circuit of a gassy tube. A great many troubles in sync circuits and a.g.c. circuits can be traced to this cause. The tubes tested in the 6AG5 socket are very often used in TV receiver sync and a.g.c. circuits.


A circuit diagram of the tube checker is shown in Fig. 2. The pin connections of the 15 test sockets are listed in Table 1. The letters in the table refer to points in the circuit diagram.

The 6AC7 socket will also take the 6SJ7, 6SK7, 6AG7, 6SG7, 6SH7, and 6SS7. The 6BL7 socket also takes the 6SL7, 6SN7, and 6BX7. The 6K6 socket takes the 6V6, 6J5, 6F6, 6W6, and 6SA7. The 6BQ7 socket will also test the 12AT7, 12AU7, 6BK7, 6BX7, 12AV7, 12AX7, and 12BH7. The 6AU6, 6CB6, 6AH6, 6AK5, 6AK6, 6BA6, 6BC5,

TUBE				TUB	E SOCI	KET PI	N CON	NECT:	IONS	
	SOCKET	1	2	3	4	5	6	7	8	9
6AC7 6BL7 6K6 6H6 6SQ7 7A5 7F7 6BQ7 6T8 6AB4 6AB4 6AL5 6AT6 7B6	8-pin 8-pin 8-pin 8-pin loctal loctal 9-pin 9-pin 7-pin 7-pin 7-pin 7-pin	G A A A J I L F E A	A A F I C G G C C I	CCI GCB J C A A A A G	F H B L C G A A A D D D D C	CKFH BHDDD L	B C C I F K K H	DADDACCHC CHICC	I D C L D D C F C	IF

Table 1. Pin connections for the fifteen test sockets used in the checker.


Fig. 3. Two 6 v. filament transformers can be used instead of 12 v. unit, T.

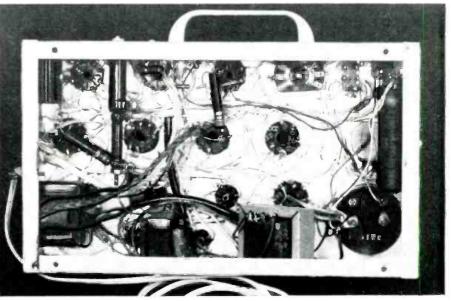

RADIO & TELEVISION NEWS

ECT to YOU

from the manufacturer

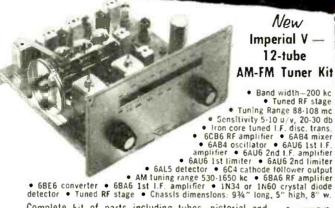

New Imperial V — 12-tube **AM-FM Tuner Kit**

Band width—200 kc
 Tuned RF stage
 Tuning Range 88:108 mc

Complete kit of parts including tubes, pictorial and schematic diagrams

Wired and tested, \$5.00 additional

NEW Approved policy



Now, for the first time you can buy high-quality audio, test, TV, AM-FM receiving equipment at unheard-of low prices!



New Approved policy eliminates percentages to "middlemen"—brings equipment direct from factory to you for buys that can't be beat . . . anywhere!

New

Model A-800 Pre-Amp kit



- Floated tubes to prevent tube microphonism 3 input connectorsridated tubes to prevent tube microphonism — 3 input connectors— magnetic, crystal, radio • Input selector switch • Overall gain control 6 position equalizer switch for GE and Pickering cartridges High-low tone controls approx. 15 db • Tubes: 2-7F7 Power required: 6.3v AC or DC, .6 amp., 180-220v DC at 7 milliamps

\$1595 Kit with complete, illustrated instruction book

New V-5 AM Receiver Kit

New V-9 FM Receiver Kit

THE BINAURAL TWINS

\$3750

Start Your Hi-Fi Installation the Economical Way

New A-465

Field Strength Meter

0-100 Microvolts Full Scale

12 Channel High Gain (standard coil) cascode turret

(standard coil) cascode turret tuning front end • 6BQ7—RF • 616 oscillator-mixer • 6CB6 high gain 1st 1.F. • 6AU6 high galn 2nd 1.F. • 1N34 crystal diode (meter rectifier circuit) 2nd detector • 6AU6 amplifier (for earphone or scope use) picture carrier only

\$5950

- Self-contained AC power supply
 Tuning range 530-1650 kc

 68A6 RF Amplifier

 68B6 St 1.F. amplifier

 68A6 St 4.F. amplifier

 6AL5 detector

 6C4 cathode follower output

 Sensitivity 5 microvolts
 Iron core tuned coils throughout

 Dimensions 934" x 5" x 5"%"

#65 selenium rectifier 3 section variable cond. Tuned RF stage Complete kit of parts, including AC power supply, tubes, pictorial and schematic diagrams.....

\$2450

- Self-contained AC Power Supply
- 3 section variable condense Tuning range 88-108 mc

- Band width 200 kc
 Sensitivity 10 microvolts 20 db
 Tuned RF stage
 Iron core tuned I.F.—disc.
- trans. 6CB6 R.F. amplifier

- 6AB4 mixer
 6AB4 oscillator (temp. compensated)
 6AU6 1st I.F. amplifier
- 6AU6 2nd 1.F. amplifier
 6AU6 1st limiter
 6AU6 2nd limiter
 6AL5 detector
 6C4 cathode follower output
 265 selenium rectifier
 Dimensions 9¾4" x 5" x 5%8"

Complete kit of parts including AC power supply, tubes, pictorial and schematic diagrams..... \$2950

New A-900

UHF Signal Generator 450-900 MC on Fundamentals

- Power supply: 115-125v, 60 cycles 3" calibrated output meter, 1 volt 1 volt minimum across the

- band 50 ohm terminated output
- cable Large 6" dial, accurately calibrated in megacycles and spot channels Stable operation—low
- Statie operation = 10w leakage RF attenuator 0-120 db total Drift after warmup negligible 400 cycle internal modulation

- Separate modulation control
 Cavity tuning system
 Dimensions: 12" x 10" x 8"

Wired and tested with tubes and instruction book

\$5950

Wired and tested with tubes and instruction book

or scope use) picture carrie only of signal indicator, 6" large face, 0-500 microammeter Seff-contained power supply 115 volts, 60 cycles Calibrated in relative microvolts—2 scales: 0-100 microvolts and UHF railbrated.

UHF calibrated reference scale
 Panel mounted "Off-On" Indicator
 300 or 72 ohm output
 UHF strips available on order

FREE CATALOG OFFER!

Write today for free complete Approved catalog!

ORDER DIRECT FROM ELECTRONIC INSTRUMENT CORP. 928 BROADWAY NEW YORK 10, N. Y.

December, 1954

NEW STOCK OF FIRST QUALITY

All tubes individually boxed ... unconditionally guaranteed for one year

GIFT OFFER! One 6BG6G tube will be shinned FREE with any order accompany. ing this ad.

Type Price 1A7GT .53 .53 .53 .54	Type Price 523	6BF5 48 6BF6 18 6BK5 75 6B 16 51 6B 16 51 6B 16 51 6B 16 77 6B 16 90 6B 27 85 6B 27 85 6B 27 60 6C 4 41 6C 86 51 6C 86 51 6C 86 42 6F6 42 6F5 42 6F5 41	Type Price 6166 78 607 40 684 41 6886T 65 68A76T 45 68K76T 45 68K76T 45 68K76T 48 671	Type Price 12AL5	
				12BZ7	TYPE 8033 117Z333 117Z6GT65

FREE *REE \$7.20 list value Bonus Box of three 65N7 tubes and 25 as-sorted resistors with each order of \$25 or more.

SAME DAY SERVICE

48 Hour Postal Delivery To West Coast TERMS: Save all freight and postage charges. All orders accompanied by full remittance will be shipped POSTAGE PAID anywhere in the continental U.S.A. 25% deposit required on C.D.D.'s. Minimum order \$10.00. Open accounts to rated firms only.

Send for Free complete tube listing and monthly specials! Get on our moiling list.

_	S	P	E	C	ĺ	A	Ĺ	!—	-t	i	Ш	J	Á	N	1
	•			•			-		•				,,,		

1R5	.44	6BQ6GT73
1X2	.57	6BZ783
5U4G	.40	6K6GT34
6AF4	.89	6SN7GT48
6AU6	.36	6U865
6AX4GT	.49	12507
6BA6	.48	258Q6GT75
6BA7	.49	25L6GT37
6BL7GT	.65	50L6GT44

ELECTRIC COM

428 Harrison Ave.,

Harrison, N. J.

Dept. RN-12

Phone HUmboldt 4-9848



Now you can consistently make professional recardings under the most gruelling field conditions. Tapes will faultlessly play back on all professional and home recorders. Ruggedly designed for maximum dependability and topnotch efficiency Combines unlimited versatility of performance with extreme simplicity of operation Choice of fourteen models available for every conceivable application

Incorporates a multi-purpose VU monitoring meter for precise setting of recording level without earphone monitoring. Meter also accurately indicates condition of "A" and "B" batteries. Five single speeds as well as two, three and 4-speed models available. Units weigh anly 19 lbs. with batteries and meosure 6½" x 9½" x 14¼" Higher speed models meet NARTB standards. All recorders are guaranteed for One Full Year.

Write for complete technical specifications and direct factory prices to Dept. RE

AMPLIFIER CORP. of AMERICA 398 Broadway, N. Y. 13, N. Y. *1. M. Feg # 5 Pot Off.

For that Extra Margin of Safety...

COPPER **PLATED** GROUND RODS

Bring Extra Profits

Simple! Practical! Lowpriced! Of smooth-drawn steel, pointed for easy driving and copper-plated for rust prevention and to assure clean electrical contact. Available in four popular styles. in 4', 6' and 8' lengths, 38", 1/2" and 5/8" diameters. Send for special Ground Rod Bulletin and prices.



5424 HIGHLAND AVENUE NIAGARA FALLS, N. Y.

6BH6, 6BJ6, 6BE6, and 6AJ5 can all be checked in the 6AG5 socket. The 6AT6 socket also tests the 6AV6; the 6SQ7 socket, the 6SR7. In the 7A5 socket, the following tubes may be checked: 7C5, 7A8, 7A4, 7A7, 7B4, 7B5, 7B7, 7C7, 7AG7, 7G7, 7C6, 7H7, 7J7, 7L7, 7Q7, 7S7, 7B8, 7T7, 7V7, and 7W7. The 7F7 socket also checks the 7H7, 7N7, and 7AF7. The 6C4 and 6J6 may be tested in the 6AB4 socket; the 7E6 and 7X7, in the 7B6 socket. The 6H6, 6AL5, 6T8, and 6U8 soekets aecept no other tubes. In addition, any 12-volt tube can be tested in the same socket as its 6-volt equivalent. -30-

SSB Audio Test Unit

(Continued from page 51)


the proper value as the capacity is so large; a few micromicrofarads only change the frequency a few cycles. A toroid coil was used because it could be fastened close to the chassis without changing inductance, and it is a very stable inductor. Toroids are available commercially at 1.5 henrys. The core material is available so you can wind your own less expensively with a shuttle-and lots of patience. Besides saving a little of your hard earned cash, the project is interesting and instructive.

Varying the plate voltage over a 20 volt range does not change the frequency more than a few cycles. The possibility of using the small air piwound inductors or iron inductors was not investigated because of the lower "Q" and was assumed they would not be as stable as the toroid type; also the oscillator would be much larger

physically.

Owners of the SSB exciters will appreciate the simplicity of this oscillator which can either be plugged into the mierophone jack or used with a toggle switch so that either the microphone or the audio signal will go to the output jack J_3 . When the signal of 1225 cycles is fed into the microphone jack, the maximum audio output is .1 volt r.m.s.; back the gain knob down about a third to prevent overloading the SSB exciter. Ripple adjustments to the 20A exciter can now be carried out according to the instruction book, or you can have a tone signal to tune your transmitter -30controls

Fig. 2. Response of the average commercial 90° phase shift network used in SSB exciter.

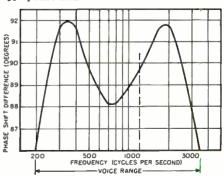



Nothing else equals the satisfaction you get from owning and operating the equipment of your choice—especially when Walter Ashe makes it so pleasantly money-saving with his fabulous "SURPRISE" Trade-In Allowance on used (factory-built) test or communication equipment. This year give yourself the best Xmas present ever. Trade used equipment now. Wire, write, phone or use the handy coupon below.



NATIONAL NC-98. 9 tubes, crystal filter. Less speaker. Net \$149.95.



HAMMARLUND HQ-140X. Less speaker. Net \$264.50.



JOHNSON VIKING RANGER TRANSMITTER-EXCITER KIT. Less tubes. Net \$179.50. Wired and tested, less tubes. Net \$258.00. Set of tubes for Ranger. Net \$22.61.

All prices f. o. b. St. Louis Phone CHestnut 1-1125

CENTRAL ELECTRONICS MULTIPHASE SINGLE SIDEBAND EXCITERS



MODEL 10B EXCITER KIT.

10 watts peak output. Net \$129.50.

Wired and tested. Net \$179.50.



MODEL 20A EXCITER KIT. 20 watts peak output. Net \$199.50. Wired and tested. Net \$249.50.



1125 Pine Street, St. Los		
☐ Kush "Surprise" trade-	In Offer on my	
for		
	and model number of new equip	ment desired)
Rush New 1955 Cata	log.	
Name		
Nome		
Address		

--- EDEE CATALOGI-----

Send for your copy today



Line!

Everything you need from one manufacturer to trade up from low-end to top models in easy stages...without moving from brand to brand!







eceded.

JOBBERS! DEALERS! Never before have you been able to get a complete line of 3-speed, 45 RPM phonos and record changers and tape recorders from one source! Here's your chance to fill all your requirements through one nationally known manufacturer who also can supply you with mechanisms as well as proper accessories. Write for full information!

7 PHONOGRAPHS

Model 2601 Hi-Fi Portoble—A super engineered luggage type phono with console hi-fi volume.

Model 601 "INTERMIX" Portable—A smartly styled portable with the only record changer that does not require "stacking" the only record changer that does not require

Model 1601 3-Speed Portoble—A quality model portable phono with 6" speaker. Fine for rumpus rooms.

"INTERMIX" changer. Suitable for use anywhere.

Model 600 Table Top - A good quality service phonograph with 3-speed, non-intermix changer.

Model 604 Record Player—A high quality player with detachable speaker-mounted cover for remote control operation.

Model 1100 Record Player-A low end inexpensive 3-speed record player.

3 TAPE RECORDERS

Model 2900 Hi-Fi 2-Speed—Combines full fidelity performance with simple, easy operation. Has everything...at a price!

Model 9037 2-Speed Recorder—A high quality tape recorder with many CRESCENT Hi-Fi features. A perfect step-up from low end to high end models.

Model 903-907 Tope Recorder - A true low end leader. Out-performs many more expensive models. 3¹/₂₄ IPS or 7¹/₂₂ IPS styles.

3 NEW 45 RPM MODELS

Model 453 Portable Phono—A beautiful, lightweight, portable phonograph made only by CRESCENT. A "must" for anyone selling phono's.

Model 452 Toble Phono - A favorite anywhere! Has 3-tube amplifier and 4" x 6" speaker.

Model 451 Plug-In Changer—Has same 45 RPM mechanism as other CRESCENT models...comes complete with A.C. cord & plug and phono cable and plug assembly.

NEW! NATIONAL ADVERTISING PROGRAM

Now CRESCENT tells its story to America's millions through CRESCENT advertising this fall and winter in the POST, BETTER HOMES, LOOK, NEW YORKER, EBONY! These ads... plus Crescent's other promotional programs . . . assure you greater sales and profits for the critical Christmas season.

CRESCENT Industries, Inc., 4900 West Touly Avenue, Chicago 31, Illinois



PLUG IN TUNERS AM--FM-SHORTWAVE

Connect to any TV set, HI FI or PA Amplifier, or Tape Recorder in a few minutes. FM unit (only \$13.95) will work in automobile and can be easily connected to car radio. AM broadcast model \$14.95. Balanced heaters no carrier hum. Fractional power requirements.

Write for literature

KUHN ELECTRONICS 20 GLENWOOD CINCINNATI 17, OHIO

Get Your FCC Commercial Operator License

We specialize in rapid and thorough preparation for FCC examinations. Correaration for FCC examinations, Correspondence or resident training. Results guaranteed. Write for free booklet.

GRANTHAM School of Electronics

Dept. 103-C. 6064 Hollywood Blvd. Hollywood 28, Calif. (Phone HO 2-1411)

MOVING?

Be sure Radio & Television News follows you. Please send your change of address to Radio & Television News

Circulation Department

64 E. Lake St., Chicago 1, III.

Transistor Meter Amplifier

(Continued from page 75)

ealibrated and ehecked, the complete instrument may be used as an ordinary meter (except for the occasional battery replacements) in most applications ealling for the more sensitive instrument. Thus, the instrument deseribed is used as an 0-100 microammeter in experimental test work. However, this is not the only possible application.

If a sensitive meter having a fullrange reading between that obtained in the modified instrument (meter and amplifier) and that obtained with the basic meter movement is desired, one of two methods may be used to reduce the sensitivity of the modified instrument. The easiest method is to simply connect a shunt across the "meter" terminals of the completed instrument to change its range to the one desired.

An alternative method is to connect a shunt resistor across the basic meter movement $(M_1 \text{ in Fig. 2A})$. The resistance value to use in either case can best be determined experimentally, taking the desired range and the existing full-seale range into aecount.

Irrespective of the method used, eare must be taken that the maximum current ratings of the transistor and the basic meter movement are not ex-

An instance of where it might be desirable to change the basic range of the modified meter can be given, using the model shown in the photographs as an example.


Suppose that a meter having a fullscale deflection of 200 microamperes is required for a particular series of tests. This range is between the range of the modified meter (0-100 microamperes) and that of the basic meter movement (0-1 ma.). To obtain this range, the modified meter would be used, together with a shunt resistor across the external terminals.

The modified meter may also be employed in a voltmeter circuit by using a series multiplier resistance. makes it possible to obtain a voltmeter having a rating of 10.000 ohms/volt using a 0-1 ma. basic movement (which normally will give no more than 1000 ohms/volt sensitivity).

To determine the resistance required for a particular voltmeter range, simply divide the voltage range desired by the full-seale meter current in amperes. As an example, the multiplier resistor required to give a 5-volt range to a 0-100 microampere meter is determined as follows:

$$R = \frac{5}{.0001} = 50,000 \text{ ohms.}$$

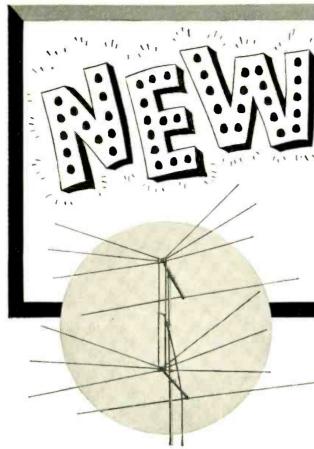Another method is to consider the modified meter in terms of its "ohmsper-volt" rating and to simply multiply by the voltmeter range desired. A 0-1 ma. meter has a 1000 ohms/ volt rating, a 0-500 μa. meter has a



PHILCO TWO-BAY SUPER CONICAL

Strong signal pick-up on all VHF-UHF channels. Ideal for fringe area reception... aluminum construction with dowelled elements: Part No. 45-3096-2. Single bay design: Part No. 45-3096.

PHILCO

Super Performance


TV ANTENNAS

BUILD CUSTOMER CONFIDENCE ... MORE SALES FOR YOU!

Designed to outperform any equivalent antenna in its class, each Philco Super Performance TV Antenna provides the finest picture possible...long life and ease of installation. Powerful Conical . . . allaluminum VHF Yagis, engineered for quick rigging . . . light weight. Stacked versions provide top-quality fringe area reception. Only six UHF Yagis cover the entire UHF spectrum. Here's powerful reception on all channels . . . the kind that builds customer confidence . . . more sales for you!

GET YOUR PHILLO FREE RIDE"

That's right! Ride any way you like it... or earn all of them! They're yours FREE with PHILCO FREE RIDE TICKETS... and there's no waiting! Collect your selected "ride" as soon as you have the necessary number of tickets. You can enjoy Rollfast Roller Skates; Radio Flyer Coaster Wagon; Rollfast Bicycle; BMC Juvenile Tractor; Airplane Trip for Two; ½ Ton Panel Dodge Truck; Plymouth Plaza Sedan. Concentrate your parts and accessories purchases on PHILCO and make double profits... profits through the great readymade PHILCO market of PHILCO owners and PLUS

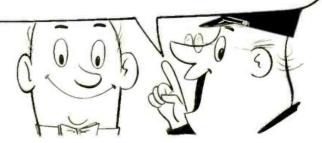

PROFITS with these great FREE RIDES . . . all at no extra cost to you. Don't wait . . . register NOW! Get started on your FREE RIDE with PHILCO!

SEE YOUR PHILCO DISTRIBUTOR FOR DETAILS



PHILCO CORPORATION

ACCESSORY DIVISION

"A" AND ALLEGHENY AVE., PHILADELPHIA 34, PA.

ELECTRICAL ENGINEER



Major in Electronics or Power BS Degree in 36 months

Prepare now for a career as an electrical engineer or engineering technician - and take advantage of the many opportunities in these expanding fields.

You can save a year by optional year 'round study. Previous military, academic, or practical training may be evaluated for advanced credit.

Enter Radio and Television - courses 12 to 18 months

You can be a radio technician in 12 months. In an additional 6-months you can become a radio-television technician with Associate in Applied Science degree. Color television instruction is included in this program.

These technician courses may form the first third of the program leading to a degree in Electrical Engineering. Twenty-one subjects in electronics, electronic engineering and electronic design are included in these courses.

Courses also offered: radio-television service (12 mos.); electrical service (6 mos.); general preparatory (3 mos.).

Terms — January, April, July, September

Faculty of specialists. 50,000 former students-annual enrolment from 48 states, 23 foreign countries. Non-profit institution. 51st year. Courses approved for veterans. Residence courses only.



MILWAUKEE SCHOOL OF ENGINEERING

Dept	WAUKEE SCHOOL OF ENGINEERING RT-1254, 1925 N. Milwaukee Street vaukee I, Wisconsin
	FREE illustrated booklets
7.4116	Career in Electrical Engineering.

I am	interested	in
		(name of course)
Name		
Addr	P\$8	

City Zone State

If veteran, indicate date of discharge.....

2000 ohms/volt rating, a 0-200 μ a, meter has a 5000 ohms/volt rating, a 0-100 µa. meter has a 10,000 ohms/volt rating, and a 0-50 µa, meter has a 20,000 ohms/volt rating.

Using the example given, the ohms/ volt rating of the 0-100 µa, meter is 10,000 ohms/volt. For a 5-volt meter, the resistor would be 5 x 10,000 or 50,-000 ohms

It should not prove too difficult to build a complete multimeter, including current, voltage, and ohmmeter ranges, using the basic transistor amplifier circuit described, but adding appropriate sclector switches, multiplier resistors, etc. Such an instrument might be called a "transistor meter" to distinguish it from its blood-brother, the 'vacuum-tube voltmeter.'

The basic transistor meter amplifier described is capable of considerable modification to suit it to particular needs. It may even be feasible to "cascade" two or more direct-coupled transistor amplifiers to obtain truly fantastic sensitivities, although the author has carried out no experiments along these lines at this writing.

In any case, the transistor meter amplifier extends the usefulness of basic meters in another direction. In the past it has always been feasible to reduce the sensitivity of a basic meter, but not to increase it. This difficulty has now been overcome.

Choosing Your Enclosure

(Continued from page 47)

throughout the room which will completely unbalance the music from one side of the room to the other. Splattering and fluttering of high frequencies may result due to many successive back and forth reflections.

At the other extreme, a completely "dead" room would be just as undesirable. In the bathroom with its hard, tiled walls, your voice will ring out. In a well-crowded clothes closet, your voice is muffled. The same thing is true of your music room. Too many drapes, curtains, or too much carpeting may so completely deaden the room that all the life and brilliance of the music will be lost. Good music halls require a small, controlled amount of reverberation. So does your music room. Keep the draperies and other hangings down to a reasonable minimum. It is good practice to prevent parallel wall surfaces from being perfectly reflective. Hard plaster surfaces should be partly covered by acoustical material so that reflections between parallel walls are eliminated. In general, if about 30 per-cent of the wall area is draped so that there are no opposing reflective surfaces, good sound reproduction will result. The floor should, of course, be carpeted for, after all, it is your living room and after going to the trouble of assembling a good sound system you want to be able to relax in surroundings as comforting to the eye as to the ear.

COMPANY

SAME DAY SERVICE!

WHOLESAL ★ 100% GUARANTEED ★

BRANDED!

6BD5 IAAP .29 .59 7F8 IAT .49 6BE6 .39 717 ... IR3 6BG6 .99 7K749 7U5 ... IRAP **6BH6** 106 6B16 .49 7Z4 .39 .. ,69 6RKT 12415 **IETGT** .39 6BL7 12AT6 .69 .39 .. ,99 6BN6 12AT7 .69 1H5 .49 6BQ6 .79 12AU6 .39 .. .79 1 L4 .49 **6BQ1** 12AU7 .59 IL6 .59 6BY5G . .59 124V6 39 .. ,39 ILA6 6BZ779 12AVT .69 ILC5 .39 6C439 12AY7 .59 ...39 ILC6 .49 6CR6 12BA6 .39 .40 1 N5 6CD6 .99 12BA7 .59 .49 185 SCUSGT .99 12BF6 .39 .39 .59 155 6F639 12BH7 .49 ITA 6FT 12SA7 49 ITSGT . .69 616 125K7 49 .49 1114 618 .79 12SN7 .59 1115 .3939 6K6 12517 .59 1 X 2 59 **6L6** .69 12507 .39 .29 2A3 6N6 .69 1457 .79 .29 2A7 654 .39 19BG6 .99 .99 19T8 .. 3AGT 658 .59 .69 .49 .49 304 6SA7 25BQ6 .79 .59 305 6SD7 .49 25L6GT .39 354 .49 6SK7 49 25W4GT .39 .49 3 V 4 6SL7 .59 25Z639 .39 5114 6SN7 .59 35B5 .39 5V4 .49 6**SQ**7 .39 35C5 .39 .29 .49 5Y3 6SR7 35W4 .29 6T8 ... 5Y4 .49 .69 35Z3 . .29 5**Z**3 .29 **6U8** .69 35**Z**5 .29 ,49 6AB4 .39 6V6 35/51 .29

Surprise Package of Radio & TV Parts

6W4GT . .39

7A4/XXL .39

7B449

. . . .49

.. .49

.. .19

....49

. .49

.29

.29

.49

.49

6X4 ...

7A7 ...

6X5

7A6

TA8

7B5

7B6

787

.49 | 7F7

TAKT

3 lbs. of parts including resistors, controls. coils, IF cans, etc. Easily worth \$10.00

.49

.69

.69

.39

.49

.49

.39

.49

.59

6AG5

6AJ5

6AK5

6AL5

6A05

6AT6

6BA6

6BA7 ..

6AS5 ...

6AU6 . . .39

6AV6 . . .39

6B719

36 ...

39/44

49

50B5

50C5 ...49

50L6 ...

75

76

77

117L7GT .99

80

.59 | 11723 . .29

.29

.29

.29

.29

.49

.49

.29

.29

.29

.29

FREE! with every order of \$29 or more-tamous "Ownall" magnetic screw driver kit. Includes all sizes—Philips head, long handles to get in those tight spots, etc. 7 screwdrivers in all. May be purchased outright. List value \$4,89 \$1,99 ach; 3 for

MINIMUM ORDER ST.00

25% deposit with order. Balance COD, if full renit-tance is sent, nlease include bostage. Excess money will be refunded. We have more than 250 types in stock at all times. Order your other needs at similar savings or write for quotations, Quantity users—write for special discounts!





HI-FI ON A TEACART

(This Month's Cover)

BUSY housewives who enjoy good music of their choice even while performing their daily chores will be intrigued by the novel "hi-fi teacart" shown on this month's cover. Most homemakers are used to wheeling their cleaning equipment with them from room-to-roomwhy not do the same for the entertainment unit that helps to lighten her tasks as much as her vacuum cleaner or floor waxer?

Pictured on the cover are the essential ingredients for a simple, portable hi-fi system that can be moved from room-to-room with ease. The idea is of interest to the audio dealer as an unusual and salable merchandising gimmick and to the audiophile as a convenient method of mounting standard components to provide portability to his hi-fi system.

Before our eagle-eyed readertechnicians swamp us with letters pointing out the missing interconnections, may we say that Mrs. Audiophile has just been surprised with this exciting Christmas present from hubby and he refuses to hook it up until he gets outside of his turkey dinner.

We were particularly impressed with the excellent color photography represented by this cover. We also felt that many of our readers would be interested in the idea developed here and that they might wish to follow suit and mount their audio gear on a teacart in a similar manner.

We are indebted to Regency for submitting an outstanding composition for our annual Christmas cover. The audio equipment used in this particular setup includes the new Regency HF-150 high-fidelity amplifier, the Webcor "Diskchanger," and the Jensen "Duette" reproducer.





FIX ANY RADIO OR TV SET EVER MADE....easier....better....faster

Rodio & TV Receiver TROUBLESHOOTING AND REPAIR

by Ghirardi & Johnson

822 pages, 417 illustrations Price \$6.75

(See special offer in coupon)

This big, 822-page book brings you the kind of PROFESSIONAL training that helps you handle the toughest radio-television-electronic service jobs as slick and as accurately as you now do the easy ones!

do the easy ones!

For service beginners, Radio & Television Receiver TROUBLE-SHOOTING AND REPAIR is a complete, easily understood professional training course. For experienced servicemen, it is the ideal way to "brush up" on specific jobs; to develop better troubleshooting methods and shortcuts; and to find quick answers to puzzling service problems.

and to find quick answers to puzzing service problems.

Step by step, it takes you through each service procedure . . , from lo-cating troubles quicker and with less testing to repairing them faster and

You learn to deal with any kind of trouble in any kind of receiver. No guesswork. No aimless testing.

Here are just a few of the subjects covered: Components and Their Troubles, 8asic Troubleshooting Methods; "Static" and "Dynamic" Testing; bles; &asic Troubleshooting Methods; "Static" and "Dynamic" Testing; Practical Troubleshooting Tips and Ideas; AC/DC, 3-way Portable and Battery-set Problems; Servicing Communications Receivers; A Complete Guide to Television Service; AM, FM and TV Realignment Mace Easy; Resistor, Capacitor, Inductor and Transformer Problems; Servicing Tuning, Selector and Switching Mechanisms; Loudspeakers; Servicing Recorders and Record-playing Equipment ... and dozens more. Use coupon. Read it for 10 days at our risk.

LEARN BASIC CIRCUITS....and watch service 'headaches' disappear!

Rodio & TV Receiver AND OPERATION

by Ghirardi & Johnson

669 pages, 417 illustrations Price \$6.50

(see special offeri)

It's amazing how much easier you can repair radio and television sets and even industrial electronic equipment when you know all about their circuits. You locate troubles in a jiffy because you know what to look for and where to look. You handle jobs lots faster, better . . . and more profitably. Radio & Television Receiver CIRCUITRY AND OPERATION give you a complete understanding of basic circuits as well as their varieties. It teaches you to recognize them . . to understand their peculiarities , . . to

know their likely "troublespots" . . . and how to eliminate guesswork and useless testing.

Throughout, this new book brings you the kind of above-average professional training that fits you for the bigger, better-pay jobs. Covers all circuits used in modern television and radio receivers, amplifiers, phono pick-ups, receivers, amplifiers record players, etc.

Price only \$6.50 . . . o see money-saving combination offer in coupon. 10-day FREE examination.

Make your training library complete. Have ALL the latest data at your fingertips. Get both these books at only \$12.00 for the two . . . YOU SAVE \$1.25.

FREE EXAMINATION . . . easy terms!

٠.	Dept. RN-124, RINEHART & CO., INC., 232 Madison Ave., New York 16, N.Y. Send hooks indicated for FREE EXAMINATION. In 10 days, I will either tentit price inticated plus a few cents postage or return books postpaid and owe you nothing. Radio & TV CIRCUITRY RADO OPERATION (Price SHOOTING AND REPAIR (Price \$6.75) COMBINATION OFFER., Both books only \$12.03 (Regular price separately \$13.25, you save \$1.25) (Combination offer is payable at rate of (53 plus postage) after 10 days if you decide to keep books, and \$3 a month thereafter until \$12 has been paid)
i	Name
į	Name
į	Name Address City, Zone, State
	Address



Brings You A Chance to Win A

FREE FORD V-8

Plus 49 Other Big Prizes

Selenium Diode



Application Contest

INTERNATIONAL RECTIFIER COR-PORATION'S Selenium Diode Application Contest is open to you. Here is a chance to cash in on your ability and ingenuity.

Just illustrate and explain a new application for International Rectifier Corporation's SELENIUM DIODES.

Pick up an official entry blank from your Parts Distributor. He has one or will be glad to get one for you. Have the entry blank countersigned by your Distributor's Salesman and send it to us before January 1, 1955. The entry blank will give you all the rules and information.

Our Judges

DR. LEE de FOREST United Engineering Labs, L. A.

J. T. CATALDO Int'l. Rectifier Corp, El Segundo

F. W. PARRISH Int'l. Rectifier Corp, El Segundo

For Entry Blanks

PARTS DISTRIBUTOR

Your Ability and "Know-How"

Can Win A

FREE FORD FOR YOU!

GET YOUR ENTRY BLANK TODAY!

CONTEST ENDS JANUARY I, 1955



International Short-Wave

(Continued from page 70)

level 1659 with interval signal; English noted 1715-1730 parallel 7.671 which was weaker signal. (Cox, Dela.) Heard opening in English to North America 1745 on 9.700. (Pearce, England) Announces English for North America as 1745-1800, 1930-1945, 2000-2030, 2300-2330. (Ferguson, N. C.)

Burma—Rangoon, 4.777A. noted 0900 in Burmese; 0915 started "Voice of Burma" session in English; fair level. (Morgan, Calif.) Relays BBC news 1000 and closes 1015 with "God Save the Queen"; fair level but with CWQRM in N. Z. (Harwick)

Canada—Montreal noted in English 1345-1400 over CHOL, 11.720, and CKCS, 15.320. (Wilcox, Mo.)

Cape Verde Islands—CR4AA, Praia, noted 1645 to 1700 closedown in Portuguese, when played "A Portuguesa." (Mathieu, Mass.) Noted opening in same manner 1500. (Pearce, England)

Ceylon—Radio Ceylon, 9.520. noted 1050 with music. (Pearce, England) Opening Hindi Service there 2030, with QRM to and from Copenhagen on same channel. (Morgan, Calif.) Heard on 7.110 with VOA relay 0900. (Morgan) Heard on 11.770A at 2030-2045. (Sutton, Ohio)

China—Radio Peking's 2200 news is noted only on 15.385 now; 15.060 then carries Home Service in Chinese in parallel (at 2350) with 11.830; the 0400-0430 English session is generally audible on 6.105, 6.201, 7.500; 6.700 (this channel varies, but transmitter is same one reported as on 6.800, 6.780, 6.750, 6.746) has Home Service then. Noted on 15.08 at fair level 1700 in Chinese to as late as 2230. Home Service heard 0300 on 9.040, 9.080, 7.500, 6.230, 6.200. (Balbi, Morgan, Calif.)

Colombia—HJKH, 5.070A. Sutatenza, has fine signal 1800-0200 sign-off (some days closes 0100). (Saylor, Va.) HJBB, "Voz de Cucuta," 4.815, noted 2030 at fair level; HJFC. "La Voz Armenia," 6.010, noted 2115 in Spanish. (Nyquist, Sweden)

Cook Islands—ZLIZA. 6.180, 500 watts, is scheduled Tues. and Thurs. 2000-2100, Wed. 2330-2400. (N. Z. DX Times)

Costa Rica—TIFC, 9.647, good in English from around 2200; requests reception reports. (McGraw, Ohio; Himber, Calif., others)

Cuba—COCO, measured 9.532, Havana, noted 0710 in Spanish. (Ferguson, N. C.)

Czechoslovakia—Radio Prague, 9.550, noted with English to North America 1930-2000. (Kelley, North Shore SWL Club, Jacksonville, Fla.) And parallel over 11.760; has repeat at 2305 over 9.550, 9.655A. (Foster, Ill.) English for Europe noted 1400-1430 on 9.504. (Pearce, England)

Denmark — Copenhagen broadcasts to the Faroe Islands on Sun. 0900-1000 over 9.520. (Radio Sweden)

Dominican Republic-HI2L, 5.055A,

Ciudad Trujillo, is good level around 2230, announces for "Voz del Tropico." HIIZ, 6.112, is fair level in Spanish around 2130. (Foster, Ill.) Has disc session 1730-1800 daily in both Spanish, English. (Powers, Ohio)

Ecuador—HCJB, 9.743, noted 0600 at fair level in Quebec. (Fleischman)

Egypt—Radio Cairo, 9.475. noted with news 1330. (Crago, Md.; Young, N. Y., others) Has news 0800 on 17.725 for Southeast Asia. (Pearce, England) Heard on 9.790A at 1715 in Arabic. (Morgan, Calif.)

El Salvador—YSAXA, 11.945, San Salvador, noted Tues, with Spanish-English lesson 1915-1930 (may be other days too). (Powers, Ohio)

Ethiopia—Niblack, Ind., has logged Radio Addis Ababa on new 15.342AV at 1357 when identified in English; usually is buried by VOA relay at Tangiers on 15.345.

Finland—Helsinki's 6.120 outlet is heard in Sweden QSA3 around 0900-1000. (DX-Radio, Sweden) OIX4, 15.190, noted 0600 with news. (Sutton, Ohio)

France—Paris, 11.700, is good level in *English* for British Isles 1500-1600. (Lilley, Md.) And parallel over 6.045 (best) and 9.625. (Sutton, Ohio) Paris, 11.920, noted at strong level ending Arabic session 1400. (Niblack, Ind.)

French Equatorial Africa—Radio Brazzaville noted back on 9.440 parallel 11.970 around 1700-2040 closedown and again after 2400. (Balbi, Calif.; Ferguson, N. C., others) Has musical request sessions Sun. 0545-0630 (should be on 15.595, 6.025) and 1815-1900, should be on 9.440, 11.970). (Catch, England, others) Requests should be sent to P.O. Box 108, Brazzaville, Fr. Equatorial Africa.

French West Africa—Radio Dakar, 4.950, is heard in Japan 1500 or 1530 to 1600 when closes with "La Marseillaise." (JSWC) Noted again on 9.562A with news in French 0230.

Germany—RIAS, 6.006, Berlin, is solid signal at 1757; news in German 1800. Stuttgart, 6.030, is fair level with news in German by man 1800. (Cox. Dela.) Sudwestfunk, 7.265, Baden-Baden, noted 1740 with dance music; at 0300 with news in German; NWDR, Hamburg, 6.075, noted 1645 with news in German, with light music when 0115. (Pearce, England) tuned Cologne, 5.980, noted 0130 with news in German; on 11.795 at 1745 with news in German and music. (Sanderson, Australia)

Greece—Radio Athens is again using 9.607 (instead of 11.718) for news 1245-1300 closedown. (Astrom, Jonsson, Sweden; Pearce, England) Forces Station, 7.420, Athens, heard closing 1704 with Greek National Anthem. (Pearce)

Greenland — Astrom and Jonsson, Sweden, say a Greenland station is heard on 3.200 and 1500 kc. at 0430-0645.

Guatemala — TGNB, 9.668, noted 2240 in English. (Brooks, Kans.) Is again using TGNC, 11.850, in parallel. (Continued on page 126)



catayette scores again with an almost unwellevable price on the Collaro 3-speed Automatic record changer. We made a spectacular buy and we are passing the savings on to you. Here's the finest changer made. Manufactured in England—with a world-wide reputation. It plays all sizes and all speeds automatically. It's packed with quality features that the Hi-Fidelity enthusiast will appreciate Jam-price ball bearing mounted one arm; automatic suit-off after last record; powerful fait cooled hum-shielded 4-pole motor with sift-alianing office bearings; automatic muting switch; weighted ball-bearing mounted constant speed turntable; rubbardings—and more! Bassize 113," x 124,". Depth below base 212.". Sing. Wr. 19 lbs. Available either less cartridge with plus-in shell. COLLARO Model 3/531 changer

SPECIAL

Net 31.50 COLLARD Model 3/531 with Turnover Ceramic cartridge 45 RPM SPINDLE

Slips on in blace of regular spindle, eliminating use of center inserts on 45 RPM records, GSA Spindle Net 3.23

st Tape Buy Ever! CARDWELL UHF CONVERTER ! 1200 FT. REEL

Genuine Plastic Base RECORDING TAPE Shpg. Wt. 14 0z.

100X-200X-300X

accuracy and long losting service.
Triple position tweet holds 3
achromatic color-corrected objec-

tives for magnification of 100%.

200X and 300X power! Heavy base and stand--inclines through 90° Dual hoob focusing by rack and pinlan, Adjustable plano sub-stage

mirror. High-grade microoptics used throughout! Complete with

fitted wooden carrying case and slides, Shpg. Wt. 41/2 lbs.

Precision built for

__ NET 7.45

Shop, Wt. 14 02:

LAFAYETTE made a terrific deal with one of the leading manufacturers of recording table to supply us with their regular tape which sells for almost tape our price. WE GUARANTEE ABSOLUTE SATISFACTION OR YOUR MONEY MACHINE TO THE METERS OF THE METERS O

3 LENS TURRET MICROSCOPE

HIGH FIDELITY

AMPLIFIER KIT

10 WATT - BUILT-IN

PREAMPLIFIER For

FREAMPLIFIER For

G.E. Reluctance Cartridge
REQUENCY RESPONSE: 20-20,000 CYCLES

Designed for installations where high quality reproduction is required. Separate tone nontrols for bass and treble. Inverse feedback circuit. Specification. Power output 10 waits or 32 db less than 3% distortion. Frequency Response: 20 to 20,000 cps ± 1 db. Tone Control produces maximum bass boost of * 8 db at 100 cps. Treble Control produces maximum treble boost + 10 db at 10,000 cycles. Hum: —76 db below rated output. Tole Complement: 1-88CT, 1-88LT, 2-895GT, 1-57LT. Power Cansumption 70 waits 110-120 volts 60 cycles. Ships. W. 15 lbs. Complete with 3D diagrams and instructions.

TWIN LENS IMPORTED CAMERAS

21/4 x 21/4 NEGATIVES

With F3.5 Coated Lens A 69.50 VALUE!

only at Lafayette

Shpg. Wt. 7 lbs

Built-in Flash Synchronization

9 Speed Shutter 1 to 1/200 Sed

Double Exposuro Prevention
 Matched Coated Lonses are
 Coupled in Helical Mount
 Accepts 120 Roll Film

Stock No. 29.95

Fingertip Focusing Sportsfinder

List 42.50 Net 13.95 ea.

Singly 14.45 ea. Outstanding Value. The Cardwell ES-1 UHF converter covers the entire UHF spectrum—channels 11-85. Has-9AF4 oscillator, 60-B6 IF amplifier and IN72 crystal diole. Features printed circuit oscillator, high week glad (3 to 4 thres), high sensitivity, constant L/C ratio tuner, 25-1 gear drive. Has AC cord and plug, 3-50-8 switch for UHF, VHF and OFF, Handsonie word cabinet 81/4 x 61/4 x 31/2" with easy reading dlal. Shpg. Wt. 41/2 lbs.

SARKES TARZIAN VHF TUNER

Brand new - covers en-tire VHF spectrum. It is an exact dunificate of thousands now in use in many chassis including the Sylvania 540 and 520 ceries. Has 7" long con-centric shafts. Excellent

With a Tubes
Complete
Complete certes, this colors con-centric shafts. Excellent gain, halse factor, image and LF rejection. For 10 me IF systems. Coundete with 6BC3 and 6x8 tubes and shields. Shpa. Wt. 1 lbs. Worth 4 times the price!

TL-24-In lots of 3 each....

DUAL STYLUS - TRIPLE PLAY

DIAMOND and SAPPHIRE 112 LIST \$31-00

Replacement for All G.E. RPX-050 Triple-Play Cartridges Net 11.95 Stock No. PK-29

Latest Type

Complete

With 2

30 POWER TELESCOPE

Weighs only 8 ounces! . All metal-chrome trimmed Weighs only 8 ounces! • All metal—chrome trimme Precision machined body. Hand ground, bard dated, achromatic lenses. Sharp, clear, hrilliant makes in the same manner as the bihardists. Used in hunting—sparts—vacuationing. For long distance of close up views. Brinks objects 30 times closer! Highly nollshed midsel tubes for smooth, easy shiding focusing. Collapses to 7° extends to 14%?. Not a chemity made for (descence, But one of Lafavette's linest optical barkains. As always you must be satisfied—or return for immediate refund. Sings. Wt. 1 lb.

NEVER BEFORE AT THIS PRICE

IMPORTED DIRECT PRISM-COATED LENSES BINOCULARS

. ALL-METAL CONSTRUCTION INDIVIDUAL FOCUS

COMPLETE WITH LEATHER CASE & STRAPS

F-15. 7 x 35 with case .Net 22.50 F-103, 7 x 50 with case F-104, 12 x 50 with case Net 32.50 with order, Add 10% Fed. Tax

9.95

This instrument is one of the best buys that Lafa yette has ever offered in a Wide Range AC-DO MULTITESTER Ideal portable unit that meets the need for a compact, yet jugged test instrument. Has ease of operation usually follows:

strument. Has ease of operation usually FOUND DNLY IN MORE EXPENSIVE INSTRUMENTS. Has 1090 0hms/
well tensitivity on both AV or DC. Uses full 3" rectangular meter with larse, easy to read scale. Uses 172
precision resistors, Joweled D'Arsonval inferoamp meter
movement. Ranges, AC-DC and output volts 0-3, 0-27,
0-279, 9-1000V; DC current 0-1, 9-10, 0-109 D.C. MA.
Resistance 0-10K and 0-100K 0hms. In hancsone sturdy
bakelite cu-e. Size 143" x 33", "x 193", Supplied Complete with test leads and batteries. A Must for every
serviceman, shop. Laboratory or exherimenter—and at
Lafayette's Price you can afford to own one. Shop. Wt.
236 108.

MODEL RW-27C—Complete......in Lots of 3 9.45 Single. ea. 9.95

WESTERN ELECTRIC HEARING AID

Our price \$14.95 \$185.00

Brand new, in original Western Brand new, in original Western Electric's jeweler's case. Sup-plied with receiver, receiver cord, battery cord and plug (less batteries). Money back guarantee. Act now while they last! Uses Burgess XX30E and 8R batteries at \$1.55 per set.

3.95

2

WESTERN MICROPHONE ELECTRIC • Western Electric Magnetic Head

• UTC Ouncer Transformer

A terrific value! High impedance mike with -55 db output level. Compact, modern, slim styling. Contains W.E. 2334 magnetic head and UTC ouncer. Silver plastic casing with detachable desk stand. Lightweight - only il ounces. Complete with 6 it. cable. Net 3.95 PA-23

PRECISION DRAFTING SET

PRECISION DRAFTING SET

11 Pieces—Fitted Felt-Lined Case
Made In Germany, of heavy brass, nickel
plated and polished, instruments include 5's "Compass with pencil and pen points and lengthening bar. 5's" Divider, three 3's" videwheel bow dividers
with needle point, pon boint and benefit
point. 5" Ruling pen, extra handle for
pen or pencil, capsule with extra handle for
makes this an exceptionally versalie set.
Your maney bask—if this set is not
worth twice our price?
F-13. Net 2.75

GERMAN ARMY KNIFE

First Time At Under \$8



At Under \$8

Made in Salinten. West Germany of super line steel. Sharp enough to shave with: Finest all round sporting AID made: Includes a 24" salver type blade. 14," utility hade, standard server driver. Philips a rew driver. 3" compound to their saw blade reasure punchawl blade, can opener, and bottle treatment. Shug, Wt. 1 lb. F-661. Vet 3 95 F-61.

REGAL UNIVERSAL UNDERDASH AUTO RADIO

This universal mounters and the state of the state of most cars and crucks. Has a 4 this plus rectifier circuit using mue each 618%,

Net 24.95

Jette NEW YORK, N.Y. 100 Sixth Ave. BRONX, N.Y. 542 E. Fordham Rd NEWARK, N.J. 24 Central Ave. PLAINFIELD, N.J. 139 West 2nd St. BOSTON, MASS. | 110 Federal St. DEPT. RL

Include postage with order.

December, 1954

McGEE OFFERS \$100,000 STOCK OF CUSTOM RADIO CHASSIS

NEVER BEFORE AT SUCH LOW PRICES! EVEN SAVE ON COAXIAL SPEAKERS AND RECORD CHANGERS



(A) HALLICRAFTERS S-78A





(C) JACKSON AM9A

PICK YOUR CHASSIS FROM THESE THREE EACH ONE AN OUTSTANDING McGEE VALUE!

9-TUBE HI-FIDELITY \$39.55

RECEIVES BROADCAST 550 TO 1650 K.C.

12 Watts Audio • Separate Tone Controls

(C) Jackson Model AM9A, 12 watth high fidelity audio amplifier and broadcast tuner combined, at less than you would normally pay for the amplifier alone. Push-pull 6V6 output. Frequency response from 30 to 15,000 cps. Inputs for crystal or G.E. variable reluctance pickup tone controls. Advantage of the property of the controls of th

11-TUBE FM-AM HALLICRAFTERS

Regular \$89.50

89.50 \$**69**95 McGEE's SALE PRICE

★ HIGH FIDELITY ★ AUTOMATIC FREQUENCY CONTROL

a) Hallicrafters Model 5-78A, 11 tube FM-AM superhet custom chassis. Size $73_0'''$ 2½'' x 11' deep. Complete with tubes knobs, escutcheon, diagram and instruction cereives broadcast 540 to 1700 kc. plus FM 88 to 138 mc. AFC holds FM stations refect tune. Quitout transformer matches 3.2 ohm or 500 ohm. High fidelity respons to the complex of the com

variable reluctance Cartridge, \$3.55 extra.
S-78A Hallicrafter 11 tube FM-AM chassis. Ship. wt. 22 lbs
5-78A Hallicrafter with our CU-14Y 12" coaxial PM speaker
\$-78A Hallicrafter with our P15-CR 15" coaxial PM speaker\$89.95
3/352 Collaro 3 speed record changer, less cartridge, \$38,95 extra.
3/352 Collaro changer with G.E. RPX-052 Golden Treasure cartridge, \$58.95 extra-
45 RPM spindle for Collaro changer, \$2.50 extra.

8-TUBE JACKSON FM-AM \$3995 REGULAR \$59.95 VALUE- ONLY 1000 TO SELL

REGULAR \$59.75 VALUE- ONLY 1000 TO SELL

SPEAKER

B) Model FA8C, Jackson 8 tube FM-AM custom chassis. Receives broadcast

\$40 to 1600 kc, and FM 88 to 108 mc. 9° etched glass silde rule dlai. Chassis

size 7' x 13' x 7' high. Full superhet circuit with AVC. Complete with tubes:

12AT7, 6815, 2-6845, 6AL5, 6AT6, 6AQ5 and 6X4. Output transformer matches

3.2 or 8 ohm speaker. Input for crystal pickup with radio-phone switch on front

of chassis. Full size "High-Q" ferrit loop stick antenna mounted on chassis.

Separate antenna for FM. Has bass boost tone control. Knobs, escutcheon,

diagram and instructions included.

Model FA8C, 8 tube FM-AM radio chassis. Ship. wt. 12 lbs. Sale price \$39.95.

Model FA8C with our CU-14Y 12' coaxial PM speaker, both for \$49.95.

Model FA8C with our CU-14Y 12' coaxial PM speaker, both for \$49.95.



McGee's Famous 12 AND 15 INCH COAXIAL P.M. HIGH FIDELITY SPEAKERS

12-Inch Model CU-14Y

Model CU-14Y. 12" high fidelity coaxial PM speaker. Response from 30 to 17,500 cps. Full 6.8 oz. Alnico V magnet in the 12" woofer. Special coaxially suspended high frequency tweeter. Built-in crossover network. Only two wires to connect to your radio or amplifier. Matches 3.2 to 8 ohm output. Don't confuse this speaker with many cheap speakers that are offered. This is a fine quality speaker. Stock No. CU-14Y. Sale price \$12.95 each, two for \$25.00.

Model P15-CR, 1S" high fidelity coaxial PM speaker. Response down to 20 cps. and up to 17.500 cps. Full 21½ oz. Alnico V magnet in the 15" woofer. Specially made, coaxialty suspended 5" high frequency tweeter. Built-in crossover network. Only two wires to connect. Matches 3.2 to 8 ohm output transformer. A regular \$62.50 list speaker. Model P15-CR, McGee's Sale Price, \$23.95.

REG. \$48.75 COLLARO CHANGER 3-SPEED HI-FI. 3-SPEED HI-FI, IMPORTED FROM ENGLAND McGEE'S SALE PRICE

McGEE'S SALE PRICE

Regular \$85.00 list Collaro Model 3/352. 3 speed automatic record changer on sale at McGee for only \$38.95. Famous imported English changer popular among audio enthusiasta all over America. Plays all 3 speed and all 3 sizes. Intermixes 10" and 12" records of the same speed. Shuts off automatically after the last record. Heavy duty motor and turntable gives even speed operation. Rubber pallet on turntable. Compensating spring shifts weight of tone arm for LP and standard records. Plug-in head compensating spring shifts weight of tone arm for LP and standard records. Plug-in head cervice steet. Large 45 RPMs spridle \$2.50 extra. Changer size. 144% long, 124,4" wide. 43,4" above motor board and 2%" below. Ship. Wt. 20 los. Model 3/352 Collaro changer, less cartridge \$38.95. With G.E. RPX-052 Golden Treasure variable reluctance cartridge \$58.95.

ENGLISH GARRARD CHANGERS
RC-80 WITH GE \$5851 RC-90 WITH GE RPX-052 \$8811
RPX-052 Garrard "Crown" Model RC-90, new 3 speed

RC-80 WITH GE \$4.55

Garrard "Triumph" Model RC-80, 3 speed automatic record changer. Plays all 3 sizes automatic: record changer. Plays all 3 sizes automatic: record changer. All of the features of the RC-80, plus many new developments of turntable gives constant speed. Muting ignore turntable gives constant speed. Muting change cycle. Complete with two separate plug-in shells for either crystal or GE, variable reluctance can be recorded as terminated by the record of the records. New 4 pole heavy duty AC motor and heavy turntable eliminates wow. The record of the records of the record of the records of the recor



WALNUT RADIO-PHONO-CABINET Made for \$900.00 Class Capehart Cost Over \$200.00 to Build

RADIO **PHONO** COMBO CABINETS

For \$800.00 Class Sets (Pictured to

SALEI

No. K-275 (left illustration). Walflut radio-phono cabinet 42" h. 42" w. 22" deco. Made for Capehart selling for \$900. Radio chassis area 14" h. 11½" w. Changer compartment 14"x 26" w. 12" balle completely enclosed. Cabinet weighs approx. 175 lbs. Ship. wt. 275 lbs. Sale price \$59.95.

WALNUT RADIO-PHONO CABINET Made for \$700.00 Class Capeharts \$595 Made for \$700.00 Class Capeharts

-175B (right illustration), Walnut radio-phono cabinet 37" h. 0. 21" deep. Radio area 1412" wide. Changer compartent 2512" wide. Minged top iffts in two sections. Baffle for 12" speakers. Made for \$700 Capehart combination. Ship. t. 160 lbs. Sale price \$55!95.



\$100.00 LIST \$3995 **AUTO RADIO**

AUTU NADIU

6 AND 12 VOLT MODELS

No. 981323. 8 tube 12 volt
Buick radio. Custom made for
150. 51. '52 Buick. Also '53

Buick special onty. Cost over \$100 retail. Push-but.

ton tuning, tone control, built-in 8 speaker. Per Built-in 8 speaker, tone control, built-in 8 speaker, tone control built-in 8 speaker, tone control point of the price only \$39.55.

ACCE DANIA COMPANY

F.O. SEN

21" 34 DOOR MAHOGANY CAB.....\$59.95 (b) No. 27-34MA. Mahogany with 3/4 doors for 21°, Chassis area 27°, w 223/4 m 21.5°, w 223/4 deep. Chassis area 27°, w 24°, w 25°, w 25

21" MAHOGANY FULL DOOR CAB....\$44.95 (c) No. 21-FDT. 21" full door mahogany. 39" h. 27" w. 22" deep. Chassis area 24" w. 2112 h. 1834" deep. Balle for 12 speaker, Panel cut for 21" tube. Made for a \$395 set by a famous TV factory. Ship. wt. 75 lbs. Sale price \$34.95.



TELEVISION CONSOLE CABINETS AT LESS THAN FACTORY COST! FOR YOUR TV CHASSIS-MODELS FOR 27 INCH TO 16 INCH CHASSIS

27" MAHOGANY FULL DOOR CAB... \$59.95 | 21" MAHOGANY CAB.... (a) No. 27-MA. Mahogany with full doors for 21", 24" and 27" TV. 43" h. .01/a" w. 23" deep. Chassis area 273/a" w. 25" h. 181/a" deep. Saffle for 10" speaker, A brautiful cabinet that cost the factory over \$100, Made for a \$600 TV set, \$hip, wt, 90 lbs. Sale price \$59.95. Blank Panel \$5.00 extra.

(d) No. 21-0FM, 21" Mahogany open front, 37" Mahogany open front, 37" Mahogany open front, 37" h. 25½" w. 20½" deep. Chassis area 24" w. 21½" h. 18½" deep. Bahle for 10" speaker, 5mall overall, be plenty big enough for 21 set. 24" or a \$295 TV set. 3hp. wt. 63 19s. 3ale price \$24.95. IT" MAHOGANY FULL DOOR CAB....\$29.95

(e) No. AH-430. Mahogany with full doors. 36" h. 24" w. 213/4" deep. Chassis area 22" w. 173/4" h. 183/4" deep. Blank pinel. Holds 17" TV easily. Baffle for 10" speaker. Ship. wt. 80 lbs. On sale at less than it cost a famous TV factory. Sale price. \$29.95.

(f) walnut /2 DOOR CABINET... \$24.95
(f) No. AH-85A. Walnut with half doors. 36° h. 2034° w. 211/2° deep. Chassis area 19° w. 181/4° h. 181/4° h.

17" TV CAB. WITH PHONO DRAWER \$19.95 (g) No. SE-21. TV-phono comb. 40" h. 24" w. 18½" deep. Blank panci. TV chassis area 19" h. 20¾" w. Changer drawer 19½" w. 13" deep. Bafile for 10" speaker. Mahogany finish. Ship. wt. 75 lbs. Sale Price \$19.95.



MIKE-PHONO-BROADCAST OSCILLATOR \$795

Sensational new 1955 model microphone-phono oscillator for the broadcast band. Have own miniature radio station that broadcast only in your own home. Plugs in to 110 volt house current. Input jacks for crystal mike or record player. Priced with tubes 12KS and 70L7. Stock No. LE-3, ship. wt. 3 lbs. Sale price \$7.95. Crystal mike and desk stand \$4.95 extra.

McGEE RADIO COMPANY

PRICES
F.O.B. KANSAS CITY
SEND 25% OR FULL
REMITTANCE WITH ORDER.
BAL. SENT C.O.D.

OUR NEW ADDRESS IS 1901 McGEE St., KANSAS CITY, MISSOURI

McGEE'S YEAR END BARGAIN SALE! **VALUES**

TRAVLER PERSONAL PORTABLE RADIO \$1495



McGee's Xmas Special.

Model 5300, Travler personal portable radio. Attractive two tone gold and brown case of sturdy plastic with metal grill. 4 tube superhet with full size 3" Alnico V spraker. Has ferrit stick loop antenna for added sensitivity. Exceptionally fine tone and good volume for a radio so small. Case size, 6" 9" x 2" threk. Uses cells for "A." Handy carrying handle folds into case when not in only \$14.95. Battery kit \$1.95 extra.

50-WATT BOOSTER AMPLIFIER





50-WATT BOOSTER AMP.

2-Mike Pre-Amp \$12.95 Extra. Not a Kit, but a Manufactured Amp.

A sensational value. A 50 watt booster amplifier with push-pull, parallel 6L6 output bes. Connect to your present amplifier as a booster or use with the PR-2X pre-amplifier allow the use of 2 microphones and one low level input. The amplifier has not input key with 1 vot input giving 50 watts of audio. Amplifier has a 6 lb. potted case high lelity output transformer with taps at 4-8-16-60 and 250 ohms. 225 mil power transmer and 504G rectifier. Includes tubes: 4-6-16, 7N7 and 504G. Two variable tone with the control chassis size, 8 × 61/2 x 18-1/2 to 10 million to 10 mi

TRUMPETS AND SPEAKERS FOR AMP



25-Watt Weather-Proof **Dut-Door** Speaker

HORN AND DRIVER

25 watt driver and 3½ foot air col-umn re-entrant trumpet. The standard type outdoor trumpet and driver most widely used. Drivers are 100% weatherproof. Trumpet is spun alu-minum. Offered to you at a consider-able saving. Ship. wt. 20 lbs. Stock No. MCG-H25, Sale price \$27.95.

12" PM AND LEATH-ERETTE BAFFLE, \$7.95 LOTS OF 10, \$7.50 EA.



Order From This 2-Page Ad. **DEALERS-SERVICEMEN** WRITE US-For Our Big Catalog and Bargain Flyers!

Bel-Com 2-Way Loudspeaker Intercom 5 FUN FOR THE KIDS-PRACTICAL FOR ADULTS



Here is the ideal Christmas gift for the children as well as a practical intercom for the home or office. New Bel-Com self-powered 2 station intercom more than the children as well as a practical intercom for the home or office. New Bel-Com self-powered 2 station intercom more than the children as a carbon of the children of the chi

78 RPM-AMPLIFIED RECORD PLAYER \$895



3-TUBE AMPLIFIER

6 x 9 Speaker, Leatherette Cabinet,
you can have a good quality low cost record player for the hios' room,
only \$8.88 buys this \$2.50 km of the hios' room,
only \$8.88 buys this \$2.50 km of \$2.

3-STATION INTERCOM MASTER



SUB-STATIONS \$3.95 EACH STATE STATE SUB-STATIONS \$3.95 EACH Powerful 3 station intercom master housed in a chrome plated metal cabinet 71/2" x 6" x 5". Full 3 tube ampliner for AC-DC operation. Press-to-law witch ampliner for AC-DC operation. Press-to-law witch appear of cabinet. Volume control, officen switch with one to three allocated on either side of the end with one to three its pressed, or when call-back switch is pressed at the sub. Ship. wt. 10 lbs. Model MPM-A3, 3 station master, \$16.95. Matching sub-station, Model PM-A5, complete with 5" Alnico V PM speaker and call-back switch. \$3.95 each or 3 for \$10.00. Requires 3 wire intercom cable, \$1.95 per 100 ft., \$500 ft. for \$8.95.



10 WATT PORTABLE P.A. SYSTEM 10" PM SPEAKER CRYSTAL MIKE \$34.95

PA-12. 5 tube 10 watt portable P.A. system. Push-pull 7C5's. U.L. approved amplifier with good frequency response. Inputs for crystal microphone and phono. Separate volume controls and variable speaker. Amplifier fits in bottom of case. Case size, 21 x 16 x 13". Snap-on removable back. Complete with tubes, crystal mise on non-removable desk standship, wt. 40 lbs. Sale price only \$34.95.

6-TUBE 2 BAND \$ 495 RADIO KIT





6 tube, 2 band AC DC radio kit, complete with

radio kit, complete with speaker and plastic cabinet. Popular with schools and colleges for training in radio. Recast and 6-18 mc shortwave. Full 2 gang superhet with 5" speaker and slide ruie dial, A complete kit with tubes: 12/8, 2-125K7, 125Q7, 50L6 and 35Z5, diagram and instructions. Cabinet 13" x 5½" x 6½" x 6½". Ship, wt. 12 lbs. Model ME6-2, Net \$14.95.

RADIO-TV SERVICEMEN CLASSIFIED BARGAIN LISTINGS. SPECIAL BARGAIN LISTINGS!



TUNERS
\$12.95 EACH
2 FOR \$25.00

TV-2000 series Stand
ard Coil cascode tuners
complete with \$16 and
68K7 or \$607 tubes.
Thousand of TV ets use this famous tuner.
LF. circuit. This tuneru will give 2 to 1
better reception than the old pentode type.
Many servicemen replace all older tuners
with this cascode model. Available with
either 27% or 41% shaft length. A tremendous pulse makes our low \$12.95
Stock No. TV-2000-3. Sale price \$12.95
each, 2 for \$25.00.

NEW RCA TUNER \$7.95

irand new famous 20121 RCA 1.7.7 achannel uner complete with 3.616 tubes. Com-tone complete with 3.616 tubes. Com-plete with 3.616 tubes. Com-plete with 3.616 tubes. Com-plete with 3.616 tubes. Com-tone complete with 3.616 tubes, all price only \$7.95.

Builders-Experimenters! 295
TV Tuners Less Tubes
TV tuners for experimenters and builders.
Your choice of our Type 4 Sarkes-Tarzian
tuner or General Instrument Stock No.
GI-13X for only \$2.95, less tubes. Type 4
As 1/4" diameter channel elector
and screwdriver adjustment for fine tuning,
it does not have the concentric fine tuning,
shaft. Sale price. less tubes \$2.95. The
GI-13X, General Instrument tuner is of
the tuning condonser type instead of a coil
GI-13X general instrument tuner is of
the tuning condonser type instead of a coil
control of the tuning condonser type instead of a coil
price, less tubes only \$2.95. 3-6J6 tubes
required.

24"-27" MAHOGANY TV **CABINET \$39.95**



STANDARD COIL



STANDARD COIL
TV BOOSTER
\$7.95

Model B-51, Standard Coil TV booster only
\$7.95. Brand new in factory cartons. Utilizes printed circuit high frequency circuits or 7 volton on high channels. One and 5 or 5 volton on high channels. One and 5 or 5 volton channel selection. Mas 6AKS tube. Modern design dark brown plastic cabinet 8 "x41/x". For 110 volt 60 cycle AC operation. Ship, wt. 5 lb. Sale price \$7.95, 2 for \$15.00.

78 RPM phono motors with turntable, for 110 volt, 60 cycle operation. Stock No. NR-1. Sale price \$1.29 each. \$5.00
Portable cases intended for tape recorders of various types. Stock No. NR-2, \$6.99 \$2.99 each. 3 assorted for
General Electric Model = 1201, 12", 14.5 oz. Alnico V magnet, PM speaker. \$14.95 Stock No. NR-3
12" RCA PM speaker with 3.2 oz. magnet. Stock No. NR-4. \$3.95 each \$10.50
12" Television speaker, Field coil type with 90 to 100 ohm field. \$1.49
6 x 9", 1000 ohm field speaker. 990 Stock No. NR-6

Kit of 50 assorted TV knobs. \$1.99 Stock No. NR-10. \$1.98 Kit of 50 assorted Radio knobs. 79c Stock No. NR-11. 79c Kit of 50 assorted set screw type radio knobs. Stock No. NR-12. \$1.49

\$1.99 Rit of 25 assorted radio and TV small tube sockets. All late production. 496 Stock No. NR-23 Rit of 10 single TV controls. Plant \$1.99 Model B-51, Standard Coil TV booster only S7.95. Standard Coil TV booster only S7.95. Standard moint factor carbons. Utilizes printed circuit high frecarbons. Stock No. NR-14.

Solot No. Ship, wit of 10 assorted TV focus coils. Stock No. NR-15.

Some magnet types. Stock No. NR-14.

Kit of 10 assorted TV hardware, 99c to the find and bolts. Ecok No. NR-14.

Kit of 10 assorted TV hardware, 99c to the find and bolts. Ecok No. NR-15.

Some magnet types. Stock No. NR-14.

Kit of 10 assorted TV hardware, 99c to the find and bolts. Ecok No. NR-15.

Some magnet types. Stock No. NR-14.

Kit of 10 assorted TV hardware, 99c to the find and bolts. Ecok No. NR-15.

Some magnet types. Stock No. NR-16.

Stock No. NR-15.

Some magnet types. Stock No. NR-16.

Stock No. NR-15.

Stock No. NR-15.

Stock No. NR-15.

Stock No. NR-15.

Sto

INDIVIDUALLY CARTONED ELECTRONIC RADIO & TV TUBES

MeGoc offers you a wide selection of good quality TV and Radio tube types. Individually cartoned. Our private bran 1. These are not set mfg's, culls, but a carefully inspected private line of tubes with a full 6 months' guarantee. Types listed are in stock in good quantity at this time. Thousands sold. Order 50 tubes and take 10% off the listed prices.

44 -47 MANUGANI IY					
CABINET \$39.95 Large mahogany open face cabinet for 27" or 24" television chassis "44" high, 32 company open face cabinet for 27" or 24" television chassis "44" high, 32 company open, 32 compa	155 59 681 174 55 681 175GT 59 681 1U4 59 681 1U2 159 681 1U2 159 681 1U2 159 681 104 59 681 104 59 681 104 59 681 104 69 681 105	UG 49 64 75 59 64 77 99 65 77 199 65 65 75 96 65 65 65 65 65 65 65 65 65 65 65 65 65	BGT 89 A7GT 59 C7GT 59 D7GT 69 F5GT 49 F7GT 59 A7GT 59 A7GT 59 A7GT 59 A7GT 59 A7GT 59 A7GT 69 A7GT 69 A7GT 69 A7GT 69 A7GT 69	GU8 7: 6V6GT 5: 6W4GT 5: 6W4GT 5: 6X4 3: 6X7 6: 6X7	9 128Y7
McGEE RADIO	COMPANY	PRICES F.O.B. KANSA SEND 23% OR FU REMITTANCE WITH C BAL. SENT C.O.D	ORDER. 1901 MA	OUR NEW ADD	DRESS IS S CITY, MISSOURI
December, 1954					125

(Ferguson, N. C., others) "La Voz de las Americas," 6.950A, noted from around 1900 to 0200 sign-off; fair to weak signal, CWQRM is heavy and has QRM. (Saylor, Va.) TGWA, 9.760, is good level around 1900. (Foster, Ill.)

Haiti-4VEH has "Listeners Post" at 0930-1000 Sat. on 9.654 (actually measured 9.656), and Mon. 2030-2100 on 9.666. (Kapp, Calif.; Gates, Conn.; Foster, Ill.; Hicks, Ga., others) 4VRW, Radio Haiti, is noted on 6.165A (some list this one as on 6.216A) on Thur, 2155-2230 with "Musical Caravan" session in English. (Peterson, Texas) Radio Commerce, 6.088A, noted closing in French 2230. (Leon Levy, N. Y.)

Holland-Radio Nederland, 6.025. Hilversum, heard ending English for North America 2210, fair level in N. Y. (Leon Levy)

Hong-Kong - ZBW3, 9.525, noted

0445 with music and news. (Sanderson, Australia)

Honduras-HRQ, "Voz de Suyapa," San Pedro Sula, 6.125, noted closing 2325 with English as well as Spanish announcements; good level but with bad heterodyne. (Niblack, Ind.)

Hungary-Radio Budapest, 11.910, noted with news 1705 tune-in. (Parsons. Pa.)

Iceland-TFJ, 12.175, noted Sun. only 1115-1130 in Icelandic. (Nyquist, Sweden) Burns, Ill., says he heard this one on a Sun. at 1505 with music.

India-Madras, 9.590, heard from 1115 opening to past 1230 in native; peaks around 1140; Delhi is heard on 11.620 now to Asia 0830-0945, news 0835A. (Morgan, Calif.) Delhi noted on 11.850 with news 1930. (Sanderson, Australia)

Indo-China-"La Voix du Vietnam,"

Saigon, has Vietnamese 1745-1900 (to 0000 Sun.), 2300-0000, 0530-0830; French 1900-1930, 0000-0030, 0800-0900; Chinese 2230-2300, 0430-0530; English 0830-0900, on 838 kc., 1090 kc., 6.165, 7.290, 9.620 (has French 0800-0900 on 838 kc., 7.290 only), Radio Dalat, 1440 kc., 7.265, has Vietnamese 1200-1330, 2331-2345, 2115-2230; French 2231-2330; Moi 1331-1430 (Sun. only). Radio Hue, 7.205, has Vietnamese 1000-1045, 2100-0000, 1500-1530; French 0001-0100. (Scheiner, N. J.) Radio France-Asie, 15.430. Saigon, noted in English 0430-0515. (Sutton, Ohio)

Iran-Radio Teheran, EPB, 15.100 noted with news and music 1518-1532 sign-off at fair level. (Parsons, Pa.) EQO, 3.785, has been heard well in Britain in parallel. (ISWL, England)

Iraq-Radio Baghdad, 3.295A, noted with English 1415-1500 closedown; the 11.705A channel is parallel, announced for "Overseas Listeners," while 3.295 is intended "for local listeners," (Pearce, England) Heard on 11.705A at 0000 with Arabic news and music. (Sanderson, Australia)

Israel—Tel Aviv, 9.008, still noted with news 1515. (Cox, Dela.; Ferguson, N. C.) "Voice of Zion" session in English noted 1615-1700 (or later some days). (Crago, Md.; George, Ont., others)

Italy-Rome, 9.575A, is good signal 2130-2150 closedown in English. (Mc-Graw, Ohio, others) Rome has news in French 0455-0510 closedown on 21.560. (NNRC) Heard with news in Italian on 9.630 at 1810-1815. (Backus, Va.) Milan, 6.240, noted 1745 with dance music, very high level in England. (Catch)

Japan-JOA3, 9.695, Tokyo, noted with news 0430, followed by native music. JKD21, 6.005, Tokyo, noted at fair level 0530 in Japanese. (Saylor, Va.) JOZ, 3.925, Tokyo, commercial outlet, heard 0430 with Western music and news in Japanese. (Sanderson, Australia) The Home Service outlets noted 0455 with (English) news over JKH, 7.2575, JKJ, 7.285. (Morgan. Calif.) Also over 4.910. (Cushen, N. Z.)

Kushmir-Broadcasting stations at Srinagar and Jammu have been handed over to India for administration. (Radio Times of India)

Kenya Colony-Nairobi, 4.885, noted 1300 with newscast. (Catch, England) Heard on 3.315 at 1330-1500; verified for this channel via airmail in three weeks. (Collett, N. Z.)

Kuwait-Al Kuwait, 5.000, is heard in Sweden 1500-1600 closedown. (Etersvep, Sweden)


Liberia-ELBC, 6.022A, Monrovia, is fair in N. Z. 1500-1530 in Arabic. (N. Z. DX Times)

Madagascar - Radio Tananarive, 9.515, noted breaking through some days from 2230 opening. (Cox. Dela.)

Malaya-Radio Malaya, 6.025, Kuala Lumpur, has news 0630. (Balbi, Himber, Calif.) Heard parallel on 7.200, (Sanderson, Australia) Singapore, BFEBS, 9,690, Singapore, heard with news 0530. (Saylor, Va.) Noted closing on this channel 0745; good level on

Unhouncing New **FAIRCHILD** 220 SERIES

CARTRIDGE

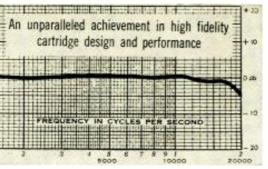

From Fairchild now comes a development so startling that it virtually obsoletes every other quality cartridge on the market. Look at the response curve! No peaks-completely uniform response to 17,000 cycles-and slow roll-off beyond-giving smooth natural sound!

Then compare the Fairchild 220 to these other well-known cartridges. Peaks and jagged response curves mean rough sound-unnatural harshness even in the mid-range.

The NEW Fairchild 220 Cartridge incorporates the famed moving-coil design, the only truly linear reproducing principle,



heatures, too! • 4 to 6 db higher output!


- Still higher compliance!
- Still lower moving mass!
- Even less record wear!

Identify the NEW Fairchild 220 by its sparkling silver finish, symbolizing its peerless performance.

Hear the NEW Fairchild 220 Series Diamond Cartridges at your audio dealer. You compare! Unequalled performance at only \$37,50

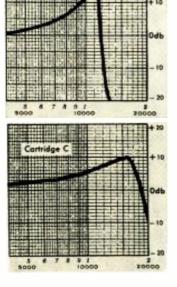STILL AVAILABLE STILL UNEXCELLED BY CONVENTIONAL REPRODUCERSI The Fairchild 215 Series Cartridges now at the lowered price of \$29.75











INDICATOR SCOPE

LOWER SHIPPING costsi BIGGER SELECTION

ID6A/APN4



Made to operate in confinction with Radio Revolver Rb/AFN-4. Unit includes one 5" scope tube, crystal controlled standard oscillator, sweep circuits, marker pulses. Good cond. Weight 40 lbs. \$19.95

OF ELECTRONIC EQUIPMENT

MICA CAPACITOR

00005 MFD, 300V, Made by Cornell-Dubiler Co. Ideal cap, for lab, and experimental use. \$2.95

UHF FM TRANSCEIVER APG-17

2 wait FM transmitter-receiver radar set, frequency range 1475-1525 MC. The antenna system consists of 2 double-bay cylindrical parabulas to operate in the above trequency. Electronic computer unit has air cooled power supply for the transceiver. Computer installation. Brand new......P.U.R.

A HAM'S DREAM!



TG-10 CODE KEYER Self-Contained Automatic unit for code practice signals from an inked type recording. Complete with 7 tubes and electric eye: Audin freq. cutput of 800 C18. Size: 11 x 24 x 18½ —110·220 VAC 60 cy. 78 RPM motor can be used for a turntable—Power unit can be used for a turntable—Power unit can be used for a System—wt. \$14.95

BC-604 35 W. FM TRANSMITTER

For 20-27 Mt', band, Ideal for 10-11 factors, Complete with tubes, temperature controlled crystal oven with selematic. Less dynamotor and crys-tals, Excel cond. Wt. 60 lbs. \$11.95

UHF TRANSMITTER-RECEIVER APS-13

\$395

Freq. range 415-420 MC. 5 stages of 30 MC. IF



30 MC. IF amplifier Complete with R.F. and I.F. sections. Less dynamotor, tubes. and tube shields. with schematic. Excel. cond. Weight 14 lbs.

500 ft. Reel. Ea. 14.93
5BPI 5" SCOPE TUBE. Ea. 14.93
4.95

BC-610 TUNING UNITS: TU-49 3.2-4.0 Mc; TU-50 4.0-5.0 Mc-Ea. \$2.95. Wt. ea. 4 lbs.

All shots, F.O.S. whee, N. Hollywood or Chicago. Call, or Illinois residents add sales tax. 25% deposit required. Specify shipping instructions and ADD SHIPPING COSTS TO EACH ORDER. All Items subject to prior sale and change of price without notice. Direct all mail to N. Hollywood or Chicago mailing address.

LOCATIONS FOR EVERYTHING IN ELECTRONICS!

- ★ 7460 VARNA AVE., NORTH HOLLYWOOD, CALIFORNIA (Mailing address: Box 3878 N. Hollywood, Cal.)
- ★ 2441 SOUTH MICHIGAN AVENUE, CHICAGO 16, ILLINOIS
- ★ 2005 EMPIRE AVENUE, BURBANK, CALIFORNIA

All buyers of electronic equipment are invited to use our expanded facilities. They have been established to speed up service, save you money on transportation costs, and give you a greater inventory to choose from.

Mail order buyers, direct your mail to either the North Hollywood or Chicago mailing address—whichever is closer. Western buyers visit our Burbank sales-showroom to inspect or purchase equipment.



ARB NAVY RECEIVER

DU-1. DIRECTION FINDER LOOP AMPLIFIER for ARB receiver. With tubes and loop. Excellent condition. With. \$19.95

PE-101C DYNAMOTOR

COMMAND EQUIPMENT

REC'EVERS 199 to 550 KC Famous Lazy 5 Q'er. 10.95 Rt'-454 3 to 6 MC. 7.95 Rt'-455 6 to 9.1 MC. 7.95

234-258 MC RECEIVER

11-tube UIF tunable receiver with sche-matic. Like new.

\$14.95 Wt. Rack\$3.50 Control Box.... 1.50

Relay adjustable from 0.2 to 1.0 amps. External push-button reset. Euclosed in glass case. Hand \$4.95 calibrated adjustments. Wt. 4 lbs. NEW. Ea. \$8.00 2 for \$8.00

SPECIAL PURPOSE

TYPE NO. SC-M CURRENT RELAY

ECHO BOX

A hand tuned ring box with an associated dipole which picks up the RF energy from the radar set. Frequency range of 3140-3640 MC. Ideal unit for experimental lab. Wt. 7 lbs. \$4.95 New Condition

RT-7/APN-1

RT-7/APN-1

Transmitter-receiver unit with a frequency range of 420-460 mc FM. Ideal set for getting started in frequency-modulation theory. This set uses 14 tubes including a voltage regulator circuits, counter circuit. Many precision resistors, relays and tube sackets, Real buy for experimental use. LESS TUBES, DYNAMOTOR AND WORBULATOR. With schematic, Wt. \$4.95

TRANSMITTER-RECEIVER

| dition. WL 43 105. A stal 505. | SOUND POWERED HANDSET. Ex. cond. Ea. \$5.50 2 for \$10.00 T-26 CHEST MIKE. New \$1.45 TA.12 50W TRANSMITTER. 40, 80 meters. Ideal for -26 CHEST MIKE, New, A-12 50W TRANSMITTER, 40, 80 tneters, 1di or mobile. With tubes, Excellent cond. W MP.28 POWER SUPPLY. Excellent cond. Wt.

NEW HAM CIRCULAR! Ask for your FREE copy!
Drastic reductions on selected hot items!

220-420 MEG. TRANSMITTER



200-710 MC. Tunable Trans-mitter, 10 W. output. Two 368type tubes as push-pull oscillators. Write band video amplifier. Less tubes. Ex- \$9.95 cellent condition..... \$3:39 With tubes, Wt. 45 lbs. \$14.95

SALES, INCORPORATED

Visit our sales-showroom at 2005 EMPIRE AVE., BURBANK, CAL. Phone: Victoria 9-2834

Western Mailing Address P. O. BOX 3878, NORTH HOLLYWOOD. CAL. Office-Warehouse: 7460 Varna Ave., N. Hollywood, Cal. Phones: STanley 7-6005, POplar 5-1810

Central Mailing Address 2441 S. MICHIGAN AVE., CHICAGO 16, ILL.
Phone: Calumet 5-9313
(CABLE ADDRESS: ARROWSALES, N. HOLLYWOOD, TELEGRAPH ADDRESS: WUX, N. HOLLYWOOD, CAL.)

Learn COLOR TV For Only \$2.10!

INTRODUCTION TO COLOR TELEVISION

by M. Kaufman, Engineer, CBS Color En-

gineering Labs and H. Thomas, Senior Project Engineer, Federal Telecommunication Labs

Read this book and you'll have a good understanding of Color TV! Written by two color TV experts, it gives you the whole story-explains everything you want to know about the color system -explains the color TV receiver! Contains no complicated phrasing-this is a clear, understandable introduction to a great new field! Everyone . . . service technicians, students, engineers, experimenters . . . will find this book invaluable! The only book that explains color circuitry! Special feature: 2 complete schematics of typical color TV receivers!

Chapters: Introduction-Fundamentals of color for TV—The Color TV system— The color TV receiver—Adjustment of color IV receivers-Glossary-Index.

144 (51/2 x 81/2") pp., color illust., only \$2.10

HIGHLIGHTS OF COLOR TELEVISION

by John R. Locke, Radio-TV Dept., General Electric Co.

A quick, inexpensive summary of the main features of the color TV system, written for the man who is completely familiar with black and white TV. Gives you all the major points at a glance!

Chapters: Introduction-Colorimetry-The color signal—The transmitter—Color receiver-The shadow mask tri-color picture tube-Some receiver details-General Comments-Index.

48 (51/2 x 81/2") pp., illust., only 99c.

COLOR TV DICTIONARY

by J. Richard Johnson

If you're stumped by the new color TV terms that everyone's using. this is the book you've been looking for! A complete explanation of color TV terminologynew words that everyone interested in color TV must be familiar with! Much, much more than a dictionary-over 50 illustra-

72 (51/2 x 81/2") pp., illust., only \$1.25

Rider books are sold by parts jobbers and book stores throughout the country. If YOUR dealer doesn't have these books, mail this coupon to us!

	PHN																Υ	.(С.				· ·		
	lni Hi	1100	due	rti	OI	1	t	0	(Co	ol	O	ı°	7	Γ	V		Di	C	ti	O)17	18	li'	У
No	ıme.																						ŧ		
Ad	ldres	s												,											
Cit	y &	Sta	ite .				4			•							•					v			

11.820 parallel 11.955 with BBC news relay 0800. (Boord, W. Va.) Heard on 7.120 at 1100-1115 with BBC news relay; CWQRM. (Sutton. Ohio)

Mexico-XESC, 15.205, noted 1700 at good level; XEQQ, 9.680, heard closing on a Sun. 2130 (Hathaway, Ill.) XEOI. Radio Mil. 6.010, noted 2300-2400 at fair level, all-Spanish. (Duering. Alta.)

Monaco Radio Monte Carlo, 7.349, noted at good level 1345, some QRM.

New Caledonia-Radio Noumea is scheduled 1400-1500, 1900-2100, 0200-0530 (news in French 1430, 1500, 2000, 0300); lists 3.355, 6.035, 1 kw. each; heard in Maryland 0300. (Zahner)

Nicaragua-YNWW, Radio Sport, Granada, has moved from 7.850 to 5.943A, heard opening 0700A and going past 2030. (Stark, Texas; Niblack, Ind.)

Nigeria-Lagos, 4.800, noted 1430 with drum interval signal; another day at 1325 ending news, then with native music 1330. (Catch, England)

Norway—Radio Norway is good some days on 9.610 and 7.210 in transmission to North America (East Coast) 2000-2100. (Saylor, Va.) And to West Coast on 7.210 at 2300-2400; wants reception reports. (Gay, Calif.)

Pakistan - Radio Pakistan, 15.335, noted with news 0300; with news on 9.484 at 0945-1000. (Pearce, England) Heard on 11.726 at 2110 with music; English announcement at 2129 followed by news 2130. (Sutton, Ohio) Now uses 9.545 parallel 7.010 for English to Turkey 1415-1500 and to United Kingdom 1500-1545. (Radio Australia)

Panama - Niblack, Ind., notes HORT. 6.060, Radio Balboa, at good level 1930.

Paraguay - Radio Encarnacion, 11.950, is heard in Sweden around 1500, (DX-Club Tellus, Sweden)

Peru-Lima, 6.082, good level with English 2330-2345A. (Parker, N. H.) Note English is now Mon.-Fri. at 2330 (instead of 2300 as formerly). (Gay, Calif.: Rowell, Minn.; Sutton, Ohio, others)

Philippines DZH7, 9.730, Manila, noted at fair level 0500. (Saylor, Va.) Tested directional antennas for first time over this one recently. (Radio Australia)

Poland-Warsaw schedule for English to North America this winter reads 0600-0630. 9.570: 0715-0745, 0745-0815, 11.740; 1715-1745, 1945-2015, 2315-2345, 0030-0100, 6.025. Pearce, England, notes Warsaw with English 0130-0200 on 9.615, 6.195, and at 1430-1500 over 5.995. Rowell, Minn., hears Warsaw in Polish on 9.525 at 1400-1500, weak

Portuguese Guinea-CQM4, Bissau, is using 7.937A now, noted closing 1800 with "A Portuguesa." (Fairs, England, via URDXC)

Roumania-Bucharest still noted in English for North America on 9.570 at 2200-2230, 2330-2400. (Sutton, Ohio) And parallel over 6.142A. (Crago. Md.) Good level on latter channel 1745 in English. (Cox. Dela.) Noted in Norway around 1700-1800. (Kristiansand S. DX Club, Norway) Has English for





deposit required on ALL orders, balance of Minimum order; \$2.50.
SEND FOR NEW FREE CATALOGUE! ELECTRONICS Columbia 2251 W. WASHINGTON BLVD.
LOS ANGELES 18, CALIFORNIA

Europe 1730-1800 on both 6.142A and 9.570. (Pearce, England)

Sarawak—Radio Sarawak, 4.870, noted with news 0800; closes now 0830 with "God Save the Queen."

South Africa—SABC, 4.895, Johannesburg, is noted in Japan 1400-1600 in Afrikaans. (JSWC)

South Korea — HLKA, 2.510, Scoul, noted 0830-0900 in Korean language; "Radio Vagabond," 6.890; heard 0854 with talk in English, call at 0855, then music; bad QRM. (Morgan, Calif.)

Spain—Radio Cuerto de Santa Maria has mored from 7.210 to 7.085A. noted 1600-1700 when left air suddenly: fair level, some CWQRM. (Saylor, Va.) Leon noted on 6.834 in Spanish 1630-1745. (Sutton, Ohio) Madrid's listed 9.363 channel has been "wandering" a great deal lately—reported as low as 9.330A, as high as 9.370A. Radio Sweden says Madrid is heard in Ireland on 5.990 at 0730-1200.

Sweden—Stockholm, 9.620, noted with English 1930-2000. (Parsons, Pa.) Winter schedule for English to Western North America is 1600-1615, 0000-0015, 9.535; to Eastern North America 0700-0715, 11.705; 1930-2000, 2100-2145, 9.620. (Hicks, Ga., others)

Switzerland—Winter schedule of Berne to North America (East Coast) is 2030-2215, HER3, 6.165, HER2, 6.055, HER4, 9.535, while uses same channels to Western North America at a new time of 2315-2400. (Morgan, Calif., others) Leon Levy, N. Y., notes a good signal on 15.305 in Berne's beam to India-Pakistan 0945-1130 in English.

Syria—Damascus, 9.555, is good level 1700 in English. (Lilley, Md.) Noted with French to 1630, English news 1645 and commentary 1715; closes 1730. (Leon Levy, N. Y.)

Tuhiti—FZP8, 6.135 Papeete, noted 2331 with man in Tahitian language, popular music, good level but much QRM; heard on 7.120 at 0018 with man in French, music good level. (Morgan, Calif.) (Continued on page 130)



BUILD 15 RADIOS AT HOME **-**With the New Improved 1955 • Progressive Radio "EDU-KIT" Complete 0 0 NOW INCLUDES S 4 High Fidelity, Signal Tracer, ш Code Oscillator ATTRACTIVELY GIFT PACKED FREE SOLDERING IRON ₹ • FREE SOLDERING IRON . NO ADDITIONAL PARTS NEEDED EXCELLENT BACKGROUND FOR TV 10 DAY MONEY-BACK GUARANTEE SCHOOL INQUIRIES INVITED 0 • ABSOLUTELY NO KNOWLEDGE OF RADIO NECESSARY 2 WHAT THE PROGRESSIVE RADIO "EDU-KIT" OFFERS YOU The Progressive Radio "Edu-Kit" offers you a home study course at a rock bottom price. Our Kit is designed to train Radio Technicians, with the basic facts of Radio Theory and Construction Practice expressed simply and the basic facts of Radio Theory and Construction Practice expressed simply and the Radio Reception, Radio Train and the Radio Reception, Radio Train Construction of the Radio Reception, Radio Train Construction of the Radio Reception, Radio Pout Will learn how to identify Radio Symbols and Diagrams; how to build radios, using regular radio circuit schematics; how to mount various radio parts; how to wire and solder in a professional manner. You will learn how to operate to the Receivers, Transmitters, and Audio Amplifiers. You will learn how to operate to the Professional manner of the Radio, will learn code. You will receive training for F.C.C. I I ₹ THE KIT FOR EVERYONE The Progressive Radio "Edu-Kit" was specifically prepared for any person who has a desire to learn Radio. The Kit has been used successfully by young and old in all parts of the world. It is not necessary that you have even the slightest background in science or radio. The Progressives Radio "Edu-Kit" is used by many Radio Schools and Clubs in this country and abroad. It is used for training and rehabilitation of Armed Forces Personnel and Veterans throughout the world. The Progressive Radio "Edu-Kit" in the world. The Progressive Radio "Edu-Kit" is used for training and rehabilitation of Armed Forces Personnel and Veterans throughout the world. The Progressive Radio "Edu-Kit" is used for training and rehabilitation of Armed Armed Company of the World Σ 0 I PROGRESSIVE TEACHING METHOD The Progressive Radio "Educkit" cross complete with instructions, These instructions are arranged in a clear, simple and progressive manner. The theory of Radio Transmission, Radio Reception, Audio Amplification and servicing by Signal Tracing is clearly explained. Every part is identified by photograph and diagram. You will learn the function and theory of every part used by Doing. The Progressive Radio "Educkit" uses the principle of "Learn by Doing." Therefore you will build radios, perform jobs, and conduct experiments to illustrate the principles which you learn, These radios and the experiments to illustrate the principles which you learn. These radios are conding to the best of the experiments to the experiments of the ⋖ Þ : ⋖ THE PROGRESSIVE RADIO "EDU-KIT" IS COMPLETE You will receive every part necessary to build 15 different radio sets. Our kits contain tubes, tube sockets, chassis, varialie condensers, electrolytic condensers, mica condensers, paper condensers, resistors, line cords, selenium rectifiers, tie strips, coils, hardware, tubing, etc. Every part that you need is included. These parts are individually packaged, so that you can easily identify every item. A soldering iron is included, as well as Electrical and Radio Tester. Complete, easy-to-follow instfuctions are provided. In addition, the "Edu-Kit" now contains lessons for servicing with the Progressive Signal Tracer, F.C.C. instructions, quizzes, high fidelity instructions. The "Edu-Kit" is a complete radio course, down to the smallest detail. 2 ⋖ TROUBLE-SHOOTING LESSONS Trouble-shooting and servicing are included. You will be taught to recognize and repair troubles. You will build and learn to operate a professional Signal Tracer. You receive an Electrical and Radio Tester, and learn to use it for radio repairs. While you are learning in this practical way, you will be able to do many a repair job for your neighbors and friends, and charge fees which will far exceed the small cost of the "Edu-Kit." Here is your opportunity to learn radio quickly and easily, and have others pay for it. Our Consultation Service will help you with any technical problems which you may have. ⋖ Δ 0 FREE EXTRAS • ELECTRICAL & RADIO TESTER • ELECTRIC SOLDERING O IRON • TY BOOK • RADIO TROUBLE-SHOOTING GUIDE • CONSULTATION SERVICE • QUIZZES • F.C.C. TRAINING ▶ Progressive "Edu-Kits" Inc., 497 Union Ave., Dept. RN-36, Brooklyn 11, N.Y. MAIL TODAY—Order shipped same day received. 10-Day Money-Back Guarantee. Include ALL FREE EXTRAS Send "Edu-Kit" Postpaid. I enclose full payment of \$19.95 (U.S.A. only). Send "Edu-Kit" Postpaid. 1 enclose full payment of \$20.95 (Outside U.S.A.). 210-250 V. Adapter for "Edu-Kit"—\$2.50. Send "Edu-Kit" C.O.D. I will pay \$19.95 plus postage (U.S.A. only). Wish additional information describing "Edu-Kit". No Obligation. Send me FREE Radio-TV Servicing Literature. No Obligation.

PROGRESSIVE "EDU-KITS" INC. 497 UNION AVE., Dept. RN-36,Brooklyn 11, N. Y.

SAVE! CLOSEOUT SAVE! COMMAND SETS

NEVER BEFORE!... NEVER AGAIN!

"Q" 5'rs 190-550 KC \$T

\$10⁹⁵

274N and ARC 5 EQUIPMENT



i ype		
BC-455	Revr. 6-9 Mc. Used, \$3 bes—Like New	05
with to	ıbesLike New	133
BC-456	Modulator. Used with tubes	
	Sold as is, bess tubes	2.95
BC-696	Xmtr. As is, Less tubes	9.95
BC-457	Xmtr. 4-5.3 Mc. Used, with tubes	6.95
	Sold as is, Less tubes	3.95
BC-458	Xmtr. 5.3-7 Mc. Used, with tubes	6.95
	Sold as is, Less tubes	3.95
BC-459	Xmtr. 7-9.1 Mc. Used, with tubes	
	Sold as is, less tubes	5.95
BC-450	3 Revr. Control Box. Used	
BC-451	Xmtr. Control Box. Used	1.49
3 Receiv	er Rack. Used	1.49
2 Xmtr	Pack. Cand	1 49

METERS— WESTON ● SANGAMO

44 E3 I C	M A DWI	10AMU
All New. All 0-5 Ma 0-15 Ma	D.C. 2" Square	
0-50 Ma	\$3.29 each	("numeric")
0-100 Ma	oΓ	
0-200 Ma	3 for \$9.00	
0-300 Ma	3 101 37.00	1
0-500 Ma		
0-2 Ma		\$f.95
Voltmeter. 2" 8	q., 0-20. Volts	3.29
DC Voltmeter.	2" Sq.==0-300 Ve implete	01ts W/Est.
RF Ampmeter.	2" Sq. F to .5 Am	D 2.95
Ampmeter 2" 1-1.	—0 to 50 Augustia	2.29
Ampmeter 2" Su	. 0 to 50 Amp DC. MI New.	.\$3.29; 3 for 9.00
0 - 100 Malls		.\$3.95; 3 for 9.00
21/2" Rd. 0 30 3	titis. Kariirii	3.95
2" Rd. 0-ab Ma.	. 0 to 5 Ma. Mov	**************************************
Thermocouple, 2	" rd. 350 Mill. H.	F 3.29
Amp. Meter. No), (j))-i1-(i1),	
"S" Meter		t sed 2.49
on any Ireq. from	ATTER, 100 wart a 350-9050 ke, by a ng mut	ising proper plug-
Novice Band		99c

SAM'S SURPLUS

1306 BOND STREET

LOS ANGELES 15, CALIF

CASH WITH ORDER, Include 40% sales tax with California orders—plus approximate Postage. Excess will be refunded. Approximate shipping weight per unit: 15 lbs.

Taipeh, noted at good level 0600 with news in Chinese; faded out around 0700. (Saylor, Va.) "Voice of Free China," Taipeh, has English for Western North America 2200-2230 and 2330-2400 and to Europe at 0230-0330 over BED3, 11.920, BED6, 11.736. (Pearce, England, others) BED7, 7.130, eloses usually around 0815 to 0830, but sometimes is heard as late as 0915; opens again with VOA relay at 1000 running to 1030 when closes with no anthem nor any native announcement. The 11.736 channel should parallel. (Morgan, Calif.) BED32, 9.778A, noted 0500 with Western music, English-Chinese lesson, (Sanderson, Australia) Tanganyika-Radio Dar-es-Salaam,

Taiwan (Formosa) - BED36, 7.300,

Tanganyika—Radio Dar-cs-Salaam, 5.050, is heard in Sweden around 1000. Has CWQRM. (Etersyep, Sweden)

Tangier—WTAN, "The Voice of Tangier," now uses 6.025 at 0800-0830 (Sun. 0800-0900) instead of 7.305; has German each Tue, at 1530-1600 on 7.305, and other days uses this channel for other languages around that time; has tested recently on 7.175; wants reception reports. (WRH; Pearce, England)

Thailand—HSK9, 11.670A, is noted in New Zealand at good level in special transmission to Thai Forces in Korea (parallel 6.001) at 0430-0520; is fair in Australia with English on the 11.670A channel from 0525. (Radio Australia)

Trinidad—Radio Trinidad, 6.085A, noted at good level 0500; started to fade around 0520. (Neal, Md.) Heard 1900 on 3.275, weak level in Dela. (Cox)

Turkey—TAT, 9,515, Radio Ankara, noted with news, music 1815-1830 in North American beam. (Backus, Va.) Radio Ankara has resumed Mailbag session Sun. 1615-1700 over TAP, 9.465, TAS 7.285. (ISWC. London) The weekday English session at 1600 for Western Europe should now be on these channels.

Uganda - Kumpala, 5.026, is heard in

Sweden 1045-1215 closedown; CWQRM. (Etersyep, Sweden)

USI (Indonesia)—YDF6, 9.710, Djakarta, noted with English 0930-1030. (Beggs, Ariz.) Has improved signals in Eastern USA 0615 when has news. (Boord, W. Va.) Djakarta noted opening 1115 over YDF2, 11.785, with Indian-type program, fair level. (Balbi, Calif.) YDB4, 3.377, Djakarta, heard opening in Indonesian language 0430, fair level in N. Z. (Hardwick) Rudio Sweden lists new Djakarta outlets as YDF4, 17.810, YDF8, 9.865, 100 kw.

Vatican—HVJ, 11.865, noted 1330 ending English and leaving air. (Ferguson, N. C.) And on 9.646. (Sutton, Ohio)

Venezuelu—Maraeaibo, 4.805A, good level 1845 and yet at 2230 elosedown. (McGraw, Ohio)


Yugoslavia—Radio Belgrade, 6.100, noted with news 1715. (McGraw, Ohio) Heard opening with English for Europe at 1330 on 6.100 parallel 7.200. Pearce, England)

Press Time Flashes

Jim Moore, Calif., advises that Charles Gustave Gallagher, veteran SWL, passed away recently. During World War II, "Gus," as he was affectionately known, and Fred Wolfe, now also deceased, copied messages from prisoners-of-war and relayed them to loved ones. Literally thousands of these messages were relayed, and in the possessions "Gus" left behind are eards and letters from thousands of grateful families, Jim writes.

Detailed information on the new setup of World Friendship Society of Radio Amateurs is available direct from the secretary, Bob Kenny, c/o Mrs. S. Cain, R. R. 1, Kleinburg, Ontario, Canada. Headquarters of this club was moved from Britain to America this year.

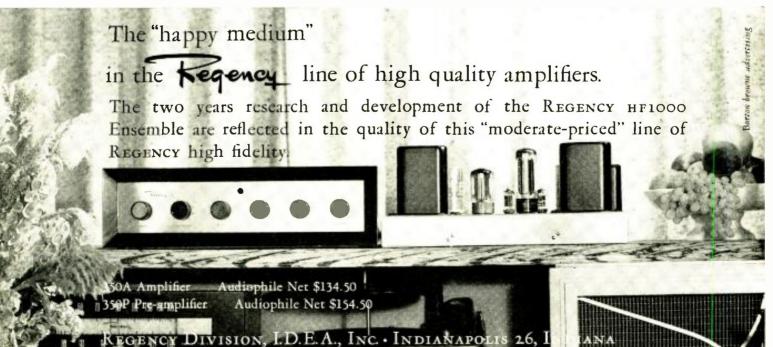Clandestine Yugoslav Emigrant Station, 6.885A, noted at fair level from 1600 tune-in to 1730 sign-off; no Eng-



lish noted. (Saylor, Va.) AFN. 3.188, Frankfurt, Germany, heard 1515 with weather report. (Pearce, England) Radio Abidjan, Ivory Coast, lists present schedule on 4.945 with 5 kw. as 0145-0230, 0715-0830, 1330-1630; sent letter verification via airmail. (Pearce) Heard in N. Z. at 1530 in French, closing 1600. (Hardwick) DX-Radio, Sweden, reports Kathmanduran, Nepal, testing on 9.856 at 0900; not confirmed

A station announcing as "Voice of Vietnam," probably in Indo-China, has been heard in Australia at 0500-0600 on measured 11.904 and 15.018. (Radio Australia) Was first reported by Balbi, Calif., heard on 11.910A. At press time, Balbi, Calif., noted Radio France-Asie, Saigon, Indo-China, using 11.790 with news for Europe 1100, while the 9.755 outlet had news in French (formerly, this was reversed).

Present schedule of the Far East Network, AFRS, Tokyo, over a 10 kw. transmitter, is 0530-1000 and 1600-1800 on 6.160 and 1815-0515 on 11.750. (Cushen, N. Z.) JOZ2, 6.055, and JOZ, 3.925, Tokyo, commercial stations, have an "economic" report in English daily (except Sat., Sun. and market holidays) 0310-0320 which includes financial and market reports. (Balbi, Calif.) Noted with news in Japanese 0900 and closing around 0910. (Morgan, Calif.) A Dutch speaker heard by Cushen, N. Z., on 3.390 around 0500 is believed to be Hollandia, Dutch New Guinea, on a new channel.

Budapest, Hungary, has English for North America 1930-2000, 2300-2330 on 11.910, 9.833, 7.220; English for Europe 1500-1530, 1700-1730 on 11.910, 7220; has special English session for Britain on Sun. only 0600-0630, repeated 1100-1130 on 9.833. (Pearce, England) Winterschedule of Radio Norway to North America is to East Coast 2000-2100, to West Coast 2300-2400 over 6.130, 7.210, 9.610; on Sun. extends program by 20 minutes for "Norway This Week" (English). (WRH)

Radio Pakistan, 11.723A, noted 2100 with BBC news relay. YDJ2, Indonesia, is closer 7.096 now than listed 7.100; heard 1017 with man in Indonesian language. DZH8, 15.300, Manila, noted 2250 at fair level with Asian program and music. New NHK, Tokyo, point-to-point relay noted on 6.190 with QRM to TGWB (Guatemala) at 2345; in clear after TGWB closes around 2400; excellent when returned 0120. BCOF, 6.105, Kure, Japan, noted fading in 0215 at poor level with talk in English. (Morgan, Calif.) The 6.190 NHK outlet closes down 0300. (Balbi, Calif.)

Acknowledgment

Thanks for the FB cooperation during 1954, fellows! Here's wishing all of you the best of holiday seasons—and may DX galore come your way during 1955! Keep your reports coming to Kenneth R. Boord, 948 Stewartstown Road, Morgantown, West Virginia, U.S.A.



1954's MOST EXCITING CHRISTMAS GIFT

A nationwide smash hit in only a few short months!

Unsurpassed for the hobbyists, the experimenters, the electronics-minded friends on your gift list!

Practical . . . information-packed . . . easy-to-understand . . . it's the only how-to-build-it, how-to-use-it, how-it-works magazine in the electronics field.

Order Christmas Gift Subscriptions now for all your friends at these Special Low Rates:

1st gift subscription	only	\$3.00
2nd gift subscription	only	2.00
Each additional gift subscription.	only	1.50

And don't forget to include your own subscription!

POPULAR ELECTRONICS • 366 MADISON AVE. • NEW YORK 17, N. Y.

Please enter the follow POPULAR ELECTRONICS at	ing Christmas gift subscriptions to these special low rates:							
·	0 2nd gift subscription. \$2.00 onal gift \$1.50							
Name	Name							
Address	Address							
City Zone_ State_	CityZoneState							
Name	Donor's name							
Address	Address							
CityZoneState_	CityZone_State							
R-12-4 I also wish to include my own subscription at the above rates.								
(Use separate sheet of paper for additional gift orders.)								
POPULAR ELECTRONICS • 366 MADISON AVE. • NEW YORK 17, N. Y.								

December, 1954

HANDLE TOUGH SERVICE JOBS



the big book

that SHOWS

as slick as you do the easy ones!

The one best way to get The one best way to get ahead in Itadio-Television-Electronic service is to learn to work by the latest PROFESSIONAL methods. Then no job will "stump" you a not even the toughest ones.

Radio & TV Receiver Troubleshooting and Re-pair by Ghirardi & Mid-dleton is exactly that kind of a book. From radio and TV alignment to puzzling "intermittent" troubles

types of service, it teaches you fast, professional timble shooting and repair methods. Step-by-step charts explain the right way to do things so you cannot rail to understand them. Ideal as a complete training course for beginners. Tops for servicemen who want to "brush up" on speedthe jobs; develop faster, better methods; or find quick answers to puzzling service problems. Book contains \$22 big pages, 417 clear illustrations and hundreds of self-review test questions that make things doubly easy to learn.

Dept. RN-124, RINEHART & CO., INC., 232 Madison Ave., New York 16, N. Y. send me the 822-range Radio & Television gener TROUBLE-SHOOTING AND REPAIR handle for 16 days free trial. I will then either return b to you postpaid or send you \$6.75 uptus postage I dicade to keep it.

Address

ITSIDE U.S.A -\$7,25 cash only. Moncy back if ok is returned in 10 days.

EVERY PRICE SLASHED!!!

FOR YEAR-END STOCK CLEARANCE!

T.V. CABINETS table Beautiful Mahogany ven x 151½" H. x 19" Deep. Opening: 1114; 11 With safety glass & 121½" mask. Can be adapted larger screen sets or makes a handsome \$5.6.

TATS . . Brand New:

JUMBO RADIO-ELECTRONICS PARTS KIT!

WANT TO SAVE HEAL MONEY OF PARTS & IT!

Over 1,000 Already Sold!

WANT TO SAVE HEAL MONEY OF PARTS?. Well, here's a "Gold Mine" of new & surplus inventory odds & ends AT A FRACTION OF ORIGINAL COST!!

LBS, T FULL, LBS, T FULL,

5395

ALNICO MAGNETS!! the many types always

ALNICO MAGNETA the many types in stock.

POLISHED BAR—D/16"X7/32"X7/32"X1/32"

12 \$1.00: 100 \$7.50

12 \$1.00: 100 \$7.50

12 \$1.00: 100 \$7.50

13 \$1.00: 100 \$7.50

14 \$1.00: 100 \$7.50

15 \$1.00: 100 \$7.50

16 \$1.00: 100 \$7.50

17 \$1.00: 100 \$7.50

18 \$1.00: 100 \$7.50

18 \$1.00: 100 \$7.50

18 \$1.00: 100 \$7.50

18 \$1.00: 100 \$7.50

18 \$1.00: 100

RADIO CORP.

Broadcast Recorder

(Continued from page 43)

the lever farther to the left opens the head-closing mechanism wide to give full access to the heads and tape for marking or cutting and simultaneously brakes the motors to hold the reels. Actuation of the head-closing and pressure-roller mechanism is controlled by a die and cams solidly positioned on the control lever shaft by a D-shaped hole. The cams actuate the mechanism by means of grooved cam-follower rollers. The mechanism is simple, positive, and not subject to abnormal wear.

The tape spooling control lever of the coaxial system is interlocked to the tape drive control lever by a positive pivot action so that neither lever can be operated unless the other is in the "Stop" position. Moving the lever releases the brakes and varies the balance of torque in the spooling motors by means of a rheostat to give control of the rewind speed in either direction. This permits the user to rapidly shuttle the tape to locate any desired point on the reel preparatory to utilizing the "Cue" position of the tape drive control level.

The "Record" function is controlled by a rectangular push-button located in the lower head cover. This button is positively interlocked to prevent accidental erasure of the tape. It will not function in the "Run" position. The tape drive control lever must be in the "Stop" position and the "Record" button held down while the lever is moved to "Run." Returning the lever to the "Stop" position automatically releases the "Record" button and, since this must be done in order to place the recorder in "Cuc" or "Rewind" condition. this operation is virtually foolproof.

The design of the magnetic transducers used in this broadcast recorder was a direct outgrowth of the specialized requirements of the motion picturc industry's rigorous requirements for "CinemaScope" sound, a four-channel stereophonic system using magnetic sound tracks on both sides of the sprocket holes.

All of the electronic components of the broadcast recorder are mounted on a 514-inch by 19-inch relay rack panel, connected to the drive mechanism by multiple contact connectors. This amplifier panel contains the power supply. erase and bias supply amplifiers, the record amplifier, playback preamplifiers, and output amplifier. All lowlevel circuit filaments are filtered d.c.

The microphone input is a threecontact jack, feeding a high-gain triode stage through an octal plug that is adapted for a highly shielded microphone input transformer with input windings for 50 and 250 ohm inputs, balanced and unbalanced. The output of this stage is bridged by a bridging input for high-level unbalanced signals. The record amplifier is a straightforward triode cascade system with equalization to conform to the NARTB

HENRY DARES TO GIVE YOU THIS

100% SATISFACTION or Your Money Back at end of 10 day Trial Bob Henry, GUARANTEE WOARA Butler, Mo. Ted Henry W6UOU Los Angeles

New NC98

National



Cash Monthly Cash Down Payments Price

SW-54 \$5.00 \$2.61 \$49.95 12.00 6.54 119.95 20.00 10.89 199.95 NC-183D 40.00 21.77 399.50 HRO-60 54.00 29.00 533.50

DOWN

18 monthly payments of \$8.00 Cash price \$149.95

Now for the first time, a crystal filter, an S-Meter, choice of electrical bandspread on amateur or SWL bands, an RF stage and 2 IF stages.



SERVICE We WANT you to be SATISFIED

Ask any Ham about Henry We have All National Receivers in stock for immediate delivery, also National parts.

Write, wire, phone or visit either store today.

Butler 1, Missouri Phone 395 **Henry Radio Stores** BRadshaw 2-2917 11240 West Olympic Blvd. Los Angeles 64

Depend on the COMPLETE line of ROHN

"SUPERIOR DESIGN" towers and accessories


for LARGER PROFITS MORE SATISFACTION GREATER EASE IN HANDLING

3 added towers to solve ALL your needs



"All-Purpose" tower-


Fulfills 75% of your general tower needs—is structurally as sturdy—yet costs less than the well-known Rohn No. 10 Towet. Ideal for home and industrial installations, communicatrial installations, communica-tion requirements...eliminates stocking many different tower models. Self-supporting to 50 ft. or girid to 120 ft. Easy to climb for first, efficient servicing. Util-izes "Magic Triangle" which insures far greater strength and stability. Permanent hot-dipped galvanized coating. Dependability - a teature customers demand — is assured with the Rohn No. 6 Tower...de-signed to stand up for years to the rigors of weather and climatic conditions.

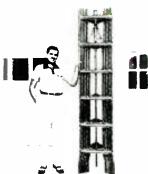

Package Tower

"Space Saver" - cuts storage space 300% or more!

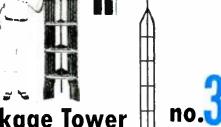Popular PT-48 has almost 50' of sturdy tower within a compact 8' x 20" package! Magic Triangle" de-sign is adapted to a pyramid shape using a wide 10" base with progressively decreasing size upward. creases your overhead . . . c.sv to transport and assemble — cuts ship-ping costs. Galvanized throughout. Available in heights of 24, 32, 40, 48, 50 and 64 feet!



tower

Heights up to 200' or more when guyed Self-supporting up to

Sturdy communication or TV tower that "stands up" to all the stresses of weather and climatic conditions . . . will with-stand heavy wind and ice loading. Heavy gauge tubular steel, electrically welded throughout. Weather resistant, non-corrosive double coating provides durable finish. All sec-tions in 10' lengths. Only 2-4 manhours required for installing 50'

also




Fold-over tower

For experimenters, TV service departments and retailers. Use this kit with regular Rohn tower sections. Simple



ROHN **Telescoping** Masts

Heavy-duty hot-dipped galvanized steel tubing and rigid joints give extraordinary strength, Quick installation . . . mast attached to base—antenna fixed, then mast hoisted quickly to desired height. Utilizes special clamp and guy ring arrange-ment. Flanged interior section; crimped exterior section gives mast stability that can't be beat. Complete with guy rings and necessary erection parts. In 20, 30, 40 and 50 ft. sizes. Bases

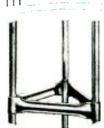

Both Towers Feature

THE ROHN MAGIC TRIANGLE

For structural superiority, famed wrap-around magic triangle "design is featured in these all-steel towers. Towers have full 2½" wide corrugated cross-bracing welded to tubular steel legs. The exclusive design assures dependable strength and permanence.

and a complete line of ROHN accessories —all galvanized



PEAK ROOF MOUNT

Heavy duty for quick, secure mounting of tower to top of peak roof. Flanges hinged, fastened to roof with 2 lag screws in each



PEAK and **MOUNTS**

For mounting of mast or pole to roof or wall. Heavy-duty steel. Variable sizes. Models for most every need.



FLAT ROOF MOUNT

For all types flat surfaces, 3-1" solid steel projections permit first section of tower to be mounted directly on roof mount by inserting usual %" bolts.



DRIVE-IN BASE

Set on top of ground...3-4' drive rods driven through base into ground. First tower section secured to rods with single bolt in each leg. Instant erection.



MAST BASES

Complete line of telescoping mast hases for every requirement, ac-commodating masts from 1"-24" diameter. Also available—drivein mast bases.



SERVICE **TABLE**

Perfect answer for television servicing, display and storage. Truly one of the finest of its kind in economy price range.





TUBING

Heavy-duty, hot-dipped galvanized steel tubing. Machined to perfection. Extra sturdy joints slotted for full, perfect coupling.

ALSO AVAILABLE

Rotator posts for mounting rotator to tower; House Brackets; Guying Brackets; UHF Side Arm Mounts; Mounts for Additional Antennae on a Tower; Erection Fixtures; Guy Rings; Installation Accessories; and dozens of other

For complete catalog and prices, see your authorized Rohn Representative or Distributor; or write or wire direct.



Manufacturing Company 116 Limestone, Bellevue Peoria, Illinois

December, 1954 133

The Finest UHF Converter Ever **Designed**



- ✓ Precise Impedance Match
- **√** Higher Gain
- **Lower Noise Factor**
- ✓ Automatic 'on/off'
- ✓ Dual Speed Tuning

Check with your supplier today. Also ask about the Model '99' at \$19.95 . . . or write Dept. WM-4

BLONDER-TONGUE LABORATORIES, INC. Westfield, New Jersey

curve effected by a selective feedback circuit over the last two stages.

The erase and bias amplifier is a balanced push-pull Colpitts circuit, feeding the bias to the record head from a separate winding on the oscillator coil through a bias level control.

The playback preamplifier is of alltriode cascade design and conforms strictly to the NARTB playback curve.

The metering circuit is of the v.t.v.m. type, with a selective switch to measure bias current, record current, and output level. The bias reading has an adjustment by which the meter reading is set to 100 after the proper bias has been determined for any given type of tape. This makes it possible to check the bias supply easily without reference to an arbitrary value.

The output amplifier is fed through a fader control, taking its signal from either the input or tape playback preamplifier. This permits making A-B checks during a recording with no click to indicate switching surges. The output stage is a cathode follower. with a plug-in transformer provision for zero-level, 600-ohm balanced line operation.

From the foregoing details, it becomes obvious that this new broadcast recorder offers many advantages to the recording engineer and the serious audiophile. -30-

SHIELDED ADAPTER


By ARTHUR TRAUFFER

WE occasionally run across amplifiers, preamplifiers, and other pieces of audio or test equipment, which use phono pin-jacks for the mike input connection. Since the conventional female mike connectors do not fit phono pin-jacks, some sort of adapter is needed to make a quick connection. The writer made a simple shielded adapter as follows:

As shown in photo at bottom, all you need is an Amphenol 75-PCIM (or equivalent) chassis unit, and a common phono pin-phig. Total cost about 25c. The assembly is shown in the photo

at the left. Remove the nut, washers, and lug, from the chassis unit. Insert the pin-plug in the hole in the chassis unit, as shown, and solder all around at the joint to make a scenre assembly. The two parts can be held in a vise or C-clamp while doing this soldering. Now pass a short length of bare copper wire (about 22 gauge) through the unit and solder at both ends, as usual. You now have a shielded adapter that will fit any female mike connector to any phono pinjack.

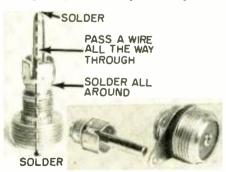(Left) Method for assembling the shielded adapter. (Bottom) Components required.





FICO SCOPE DEMODULATOR PROBE

KIT \$3.75 WIRED \$5.75

LOW CAPACITY PROBE

KIT \$3.75

WIRED \$5.75

DIRECT PROBE KIT \$2.75

WIRED \$3.95



VTVM PROBES

VTVM RF PROBES

KIT \$3.75

WIRED \$4.95

PEAK-TO-PEAK PROBES KIT \$4.95

WIRED \$6.95



Sensational High Voltage Probe

Model HVP-2 . . . ONLY \$4.95

© 54 Extends range of VTVMs & VOMs to 30 KV

Write for FREE Catalog RP-12

ELECTRONIC INSTRUMENT CO., INC. 84 Withers Street . Brooklyn 11, N. Y.



Steve-El brings you Fully Guaranteed tubes for one year at Below Wholesale Prices. All tubes individually boxed.

183	.52	6SL7	.49	12BE6	.41
155	.46	6SN7	.54	12SL7	.49
114	.46	6T8	.56	125N7	.51
1X2A	.61	676	.39	19T8	.64
6AG5	.51	6W4	.44	258Q6	.66
6AK5	.66	6X4	.36	25L6	.38
6AC7	.73	7C4	.49	25W4	.47
6AL5	.39	12A6	.46	5085	.47
6AT6	.37	12AT7	.56	57AS	.49
6AU6	.43	12AV7	.58	578	.49
68C5	.47	12AX4	.52	117Z3	.39
68G6	1.19	128A6	.43	807	.99
6BQ6	.81	l			_
6CB6	.44	Ι Ι,	Write	Dept. RN	.12
616	.51			nplete list	
616	.86		TOT COL	ubiaia iisi	٠' ا

tubes and other bargains.

FREE 1955 Catalog!

Minimum order \$5.00.

TEVE-EL Electronics Corp New York 7, N. Y

Spot Radio News (Continued from page 16)

The televised picture can be photographed with an open-lens camera to obtain well-defined pictures for a permanent record.

THERE ARE STILL A NUMBER of technical problems, affecting the national defense, to be solved, according to the Department of Commerce's National Inventor's Council.


Specifically, it has been revealed, there are about 200 problems, and many of them obtain in the field of electronics. The government reports that some divisions of the military need a coaxial r.f. switch, miniature hermetically - sealed transistor cartridges, and a precision method for the growth of large single silicon crystals.

Because of the diminishing supply of natural quartz, the military has asked that synthetic quartz and all piezoelectric materials which offer a possibility as substitutes should be investigated. Materials now under study by the Signal Corps and a number of university and college labs include aluminum phosphate crystals, nepheline, tournaline, and various types of

water-soluble crystals.

Improved electronic telegraph printers are also urgently needed. Washington says. Existing approaches have been on the basis of producing an electronic printer having high speed, or up to 300 words-per-minute. However, it has been found that at these high keying speeds, the pulse lengths of the standard teletype code are so short that they have an inherent deleterious effect on high-frequency long-range radio operation. Some work has been done on schemes which seek to overcome this problem by using other types of transmission code. One type investigated employs multi-tone transmission of five audio frequencies. As with the standard teletype code, these five frequencies would afford thirtytwo possible "on" and "off," or "mark" and "space" combinations. However, they would be transmitted simultaneously, as a single tone, thereby permitting transmission at five times the speed of standard teletype signaling. using the same code pulse length. It is felt, though, that there would be a great disadvantage in going to another type of code, because inter-operation with existing equipment would not be possible. It would be more desirable to provide an electronic printer that would operate from standard tele-Definite consideration code. should be given, the council declares. to the provision of an electronic printer to replace the existing mechanical printer that will operate at a speed of 100 words-per-minute. It is believed that the design and development of such a device would result in a lightweight and simple printer.

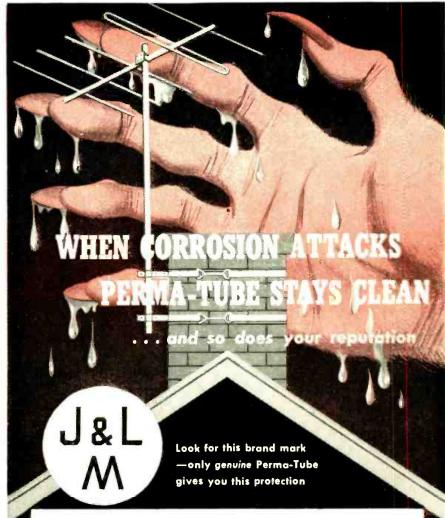
Solutions to these problems or ideas that might lead to solutions can be



Here's why PERMA-TUBE backs up quality service:

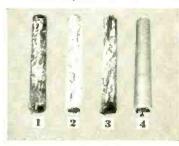- 1. PERMA-TUBE IS CORROSION-PROOF . . . it's treated with vinsynite—then coated *inside* and *outside* with a metallic vinyl resin base. It's guaranteed to be free from rust in a salt spray test of 500 hours minimum to an American Society of Testing Materials Specification B117-49T. This assures long life.
- PERMA-TUBE IS STURDY . . . it's made of special, high-strength J&I. Steel.
- 3. PERMA-TUBE IS EASILY INSTALLED . . , it's the only mast with both ends of the joint machine fitted.

Here's proof of how PERMA-TUBE resists corrosion:



Test samples after 1440 hours ASTM salt spray test

- Coated Mechanical Tubing . . , note that galvanized coating is gone and underlying steel is severely corroded.
- Coated Mechanical Tubing ... note that paint coating is nearly destroyed and zinc coating is corroded.
- Galvanized Mechanical Tubing ... note zinc and steel are corroded.
- 4. PERMA-TUBE . . . note that Perma-Tube is relatively unharmed,



For further details on product and installation, write for a copy of the Perma-Tube booklet. Jones & Laughlin Steel Corporation, Dept. 495, 3 Gateway Center, Pittsburgh 30, Pa.

Jones & Laughling
STEEL CORPORATION - Pictsburgh

December, 1954

SAVE ON INSTRUMENTS!

do better testing with your old instruments avoid buying new ones you don't really need

No sooner do you buy one expensive new test instrument than another new type comes along that is supposed to be better. But is it?

Almost any radio-TV man has paid good money for instruments he didn't really need. And lots of perfectly good old instruments are gathering dust on benches because their owners don't know how to use them to best advantage.

That's why Rufus Turner's look BASIC ELECTRONIC TEST INSTRUMENTS can save you money and help

MENTS can save you money and help you work faster and more accurately in the bargain. It's a down-to-earth instru-

The instrument quide for SERVICEMEN, AMATEURS, **EXPERIMENTERS**



by Rufus P. Turner 254 pages, 171 illus., Price only \$4

Just what instruments do you really

need—and why?
This great book answers your instrument This great book answers your instrument duestions . . saves you money . helps you work better. faster and more accurately. Covers all standard types from simple meters to capacitance checkers, oscillators, 'scopes and dozens more. Also gives full details on the newer ones such as grid-dip oscillators; TV sweep and marker penerators; TV inearity pattern and square-wave generators; distortion meters and many more.

quickly make round, square,

key and "D" openings with

Greenlee Radio Chassis Punches

In 11/2 minutes or less you can make a smooth, accurate hole in metal, bake-

lite or hard rubber with a GREENLEB

Punch. Easy to operate . . . simply turn

with an ordinary wrench. Wide range

of sizes. Write for details. Greenlee Tool

Co., 1892 Columbia Ave., Rockford, Ill.

GREENLEE

ment guide that can help you in dozens of ways—from showing new uses for old instruments—to helping you extend their ranges and modernize them, to explaining work-saving short cuts and avoiding un-

necessary instrument purchases.

Over 60 types . . . from the latest TV pattern generators to special-purpose bridges, general-purpose instruments all the old standbys... are clearly scribed and their uses explained. clearly de-

CHOCK FULL OF TIME-SAVING

You see exactly how to use VOM's, oscilloscopes, etc., in new time-saving ways. You learn to make an accurate bridge from old instruments; how to speed up and greatly simplify TV service by using power drain measurements; how to calibrate shunts and multipliers; how to measure r-f impedance with a simple Tructwork; how to get the most out of a grid-dip oscillator.

a grid-dip oscillator . . . and scores of other money-saving tips. Use for 10-day compon today fo FREE TRIAL.



10-DAY

Dept. RN-124, RINEHART & CO., Inc. 232 Madison Ave., New York 16, N. Y.

Send Turner's BASIC ELECTRONIC TEST IN-STRUMENTS for 10-day FREE EXAMINATION, If I decide to keep book, I will then remit \$4.00 plus postage. Otherwise I will return book postpaid promptly and one you nothing.

	Name
	Address
•	City, Zone, State
Ī	OUTSIDE U.S.A Price \$4.50, cash only. Money back if book is returned postpoid in 10 days.

New York's Radio Exchange SAVE HOURS OF WORK AT PRICES AS NEVER BEFORE WHOLESALE AND EXPORT ONLY STANDARD BRANDS FIRST QUALITY

FULLY GUARANTEED JAN and NON-JAN

		Each			Each
5000	1A7GT	\$.49	15000	6J5GT	\$.35
10000	1C6	.10	10000	6G6G	.38
3000	1D86T	.60	5000	6K6GT	.45
2000	1 H5GT	.39	5000	6K7G	.28
1000	1LA6	.45	5000	6L7G	.35
2000	1N22	.45	1000	6N7G	.60
5000	1N4YA	.55	5000	6S7G	.35
5000	154	.38	2000	6SA7GT	.50
1000	2A7	.25	2000	6SG7	.45
10000	3B7	.35	2000	65J7	.45
3000	3D6	.35	3000	6SK7	.42
6000	6AB7	.50	2000	6SK7GT	.45
6000	6AC7	.69	8000	6SH7	.45
3000	6AG5	.45	1000	605	.55
2000	6AK5	.70	5000	6X5GT	.38
5000	6B7	.70	5000	6Y7G	.24
5000	6BA6	.42	1000	7C5	.57
2000	6BE6	.42	1000	7C7	.57
5000	6B8G	.29	2000	7 Z 4	.49
5000	6C8G	.42	1000	12J5GT	.38
5000	606	.38	1000	12K8	.43
5000	6D6	.45	5000	12SC7	.46
2000	6ES	.50	15000	12SK7	.46
5000	6FS	.27	5000	125R7	.46
5000	6F7	.35	1000	12SJ7	.42
5000	6F86	.38	1000	12Z3	.19
5000	606	.38	2000	19	.19
5000	6H6	.33	5000	78	.49
5000	6H6GT	.27	10000	89	.06
10000	6J5	.39			

IN WHOLESALE QUANTITY ONLY **HUNDREDS OF OTHER TYPES**

Receiving, Transmitting, Radar, Klystons, Magnetrons, also Micro-Wave Test Equipment



CABLES: TELSERUP

sent on to the council where they will be examined and evaluated.

OFFICIAL PERMISSION to start "payas-you-see" broadcasting has been requested by the prexy of Skiatron TV, which holds a franchise to operate the "Subscriber-Vision" coding and decoding system. In a petition filed with the Commission, it was said that subscription TV offered the best and most immediate method of solving the ultra-high problem.

Pointing out that the FCC needs no further evidence of the economic plight of u.h.f. stations, the code-picture operator said that none of the recommendations made for assisting ailing u.h.f. stations has the inherent potentialities for the u.h.f. broadcasters that subscription television service can af-

"We believe," the brief continued. "that a u.h.f. station will be able to derive sufficient additional revenue from 35 hours of subscription television service per week to enable it to build an audience, and thereby compete effectively with the established v.h.f. stations."

The three-year head-start in subscription TV proposed, it was said, would furnish to each u.h.f. operator an opportunity to improve substantially his economic situation. Instead of trying unsuccessfully to compete with the v.h.f.'s for the advertising dollar, Washington was told, the u.h.f. stations with subscription television will then be able to transmit selected programs of a type and quality not now available. And the sale of u.h.f. converters and adapters, now the bottleneck, the petition added, will thus receive a direct stimulus by the Commission's adoption of the modification proposed; for a large segment of the public will then be willing to add converters to their receivers, so as to obtain a supplementary service that does not now exist.

THE ARMY SIGNAL CORPS will procure approximately two-million tubes during the fiscal year of '55 for its own use, and about two and a quarter-million tubes for the Air Force. About 200 different types will be purchased for the Signal Corps and 130 types for the Air Force.

Some of the more popular types that the Signal Corps will use include 1AD4, 1N70, 1S5, 6AQ5, 1LH4, 1N21B, 2D21W, 6V6GTY, 6X4W, and 1R5. The latter is particularly important to the military; for the Signal Corps will need 297,000 and the Air Force over 400.000. Also high on the Air Force list is the 3Q4; they'll be using over 267,000 of this type. Another key tube on the Air Force spec list is the 6SL7WGT; over 75,000 will be bought.

THERE WERE 409 TV stations in operation, as this column was being prepared, according to official Commission records. Three stations, two in Louisiana and one in Sioux City, Iowa, all v.h.f. units, have gone on the air

CRICALS = Guaranteed to oscillate! Your choice of frequencies!

NUMBERS LISTED ARE FUNDAMENTAL FREQUENCIES IN KILOCYCLES

FT-243	Lots of 5 or m	more, Ea ore, Ea Ea.	39с	34 c
4035 4980 5660	5773 3 5880	6273 5 6400 6725	6875 7475	7673 3 7825
4080 5030 5675	5780 5906 7	6275 6406 6 6750	6900 7506 6	7675 7873 3
4165 5205 5700	5806 7 5940	6300 6425 6775	6925 7525	7706 6 7875
4190 5300 5706	7 5806 7 5950	6325 6673 3 6800	6950 7573 3	7725 7906 6
4280 5437 5 5725	5852 5 5973 3	6350 6675 6802	6975 7573	7773 3 7925
4397 5 5485 5740	5873 5 6240	6373 3 6700 6802	7450 7606 6	7775 7973 3
4490 5500 5750	5875 6250	6373 6700 6 6805	7473 3 7625	7806 6 7975

4430	3300	3730	36/3	9230	03/3	6706 6	9030 /	4/3 3	7023	7000 0	1313
		1	CR-	1A	Lo Lo In	ots of 10 ots of 5 dividuall	or mor or mor y. Ea.	re. Ea e. Ea.	 74c 79c	6	9 c
	9-9	6350 6380 6450	6530	6750		7180 7230 7550	7670 7790 8007	8013 8155 7 8200	8250 8272 8284	8290 8308 8340	8374 8392 8400

FI	-171	Lots of 5	or more. I		79 0
2123 2125 2131 2145	2280 2415 2282.5 2435 2290 2442.5 2300 2467 2305 2470	2780 3205.5 2835 3215	3510 3682.5 3520 3695 3550 3700 3562 3712.5	3870 4012 5 3880 4037 5 3945 4050 3950 4080	4310 6210 4345 7165 4350 7950
1151 8 1940 2045 2191 1562.5 2010 2065 2220 1738 2030 2082 2258 1746 2040 2105 2260	2320 2532.5 2340 2545 2360 2550 2390 2557 2405 2582	2911 3237.5 2940 3250 2967 3322.5 2990 3400 3010 3422.5	3570 3790 3580 3807.5 3637.5 3810	3975 4177.5	4400 9200 4/35 9590

Largest selection in the world!

ALL CRYSTALS TESTED FOR ACTIVITY! 1-DAY SERVICE FOR EVERYTHING IN STOCK!

NOVICE BAND

FT-243 FUNDAMENTAL **FREQUENCIES**

Lots of 10 or more. Ea. Individually. Ea.

YOUR CHOICE OF FREQUENCIES! 3701, 3702, 3703 through 3748 **METERS** in steps of I KC.

METERS

7176, 7177, 7178 through 7198 in steps of I KC.

DOUBLING TO 3588, 3589, 3590 through 3599 METERS: in steps of I KC.

SINGLE SIDE BAND—FT-241-A



(B)	Lat	ടെറി	5 or m	ore. F	lach					89c
7	Ind	ividu	illy. Eac	ch						99¢
44		450 451	453 454	456 457	459 461	463 464	466 468	470 472	474 475	477 479
4.4	0	462	466	46.0	462	46.6	460	472	476	480

MISCELLANEOUS & SHIP BAND FREQUENCIES

81.95 KC, Octal tube type (Used in	2670 KC, DC-34 2.99
SCR-584 & SPM-1\$3.99	2738 KU, type 1-C 2.99
200 KC, FT-241 CR2 U 1.99	2738 Kt. FT-213 2.99
200 Kt, Type Dt+15 in octal tube	2738 KC, MC-7 2.99
base type holder 1.99	2801 KC, DC311 2.99
327.8 Kt., No. D-168312, (Used in	2907 KC, Dt.34 2.99
TS-102 AP 9.95	2951 KC, DC-31 2.99
500 KC, FT-211 1.99	2973 KC, DC-31 2.99
1000 KC, Type DC-9, in octal tune	2977 KC, DC-34 2.99
base type holder 3.45	2983 KC, DC-34 2.99
2000 KC, FT-243 1.99	3000 KC FT-213 1.99
2009 KC, DC-34 2.99	3021 KC, DC-33 2.99
2110 KC DC-34 2.99	3023 KC, DC-31 2.99
2126 KC, DC:34 2.99	30 13 KC, DC-34 2.99
2112 KC, DC-31 2.99	3053 KC, DC-31 2.99
2166 KC, DC-34 2,99	3055 KC, DC-34 2.99
2171 KC DC-31 2.99	3088 Kr. FT-243
2182 KC, DC334 2.99	3093 KC, DC-31 2.99
2182 RC. FT-213 2.99	3093 KC, FT-243 2.99
2206 KC, DC-34 2.99	3098 KC, FT-213 2.99
2500 KC, FT-243	3103 KC, FT-243 2.99
2359 KC, DC34 2.99	3123 KC, DC-34 2.99
2567 KC, bC-34 2.99	3125 KC, DC-34 2.99
2629 KC, DC-31 2.99	3188 KC, FT-243 2.99
2632 KC, FT-213 2.99	3193 KC, DC-31 2.99
2637 KC, DC-34 2.99	3193 KC, FT-213 2.99
2637 KC FT-243 2.99	3198 KC, FT-213 2.99
2638 KC DC34 2.99	3203 KC, FT-213 2.99
2638 KC, FT-243 2.99	5000 KC, FT-243 1.99
2670 KC, FT-213 2.99	to.000 KC. Type SR-5 Blifey, In
00 17 KC ET-919	CR-1 hulder 1.99

COMPLETE SETS!

	SCR-609 Set of 120 FT-243 Xtals.\$48.00 SCR-610 Set of 120 FT-243 Xtals.\$48.00
SCR-510 Set of 80 FT-243 crystals \$32.00	TRC-1, TRC-3, TRC-4P.U.R. SCR-608 Set of 120 FT-241 Xtals.\$48.00

DC-34 & DC-35 CRYSTALS Your Choice. Eq. only 2415 2643 2894 3161 3480 3750 3905 4055 4215 4435 2422 2665 2895 3190 3485 3760 3920 4065 4235 4440 2435 2685 2899 3201 3201 376 3005 4886 4235 4440

			1258	2435	2685	2899	3201	3500	3765	3925	4080	4240
		0	2 275	2446	2710	2925	3270	3520	3770	3935	4085	4255
			2280	2466	2711	2926	3279	35 40	3775	3940	4090	4275
1690	1890	2090	2295	2467	2725	2960	3280	3550	3790	3950	4095	4280
1705	1910	2105	2300	2478	2732	2971	3297	3575	3792.5	3960		4305
1720	1930	2106	2315	2491	2745	2980	3311	3580	3807 5	3965	4115	4310
1738	1950	2131	2326	2500	2764	3000	3317	3610	3825	3985	4130	4325
1746	1970	2155	2335	2510	2775	3010	3365	3630	38 30	3995	4135	4335
1770	1990	2175	2340	2527	2/76	3027 5	3385	3650	3850	4012.5	4150	4345
1790	2010	2195	2355	2540	2807	3077.5	3390	3655	3855	4015	4155	4350
1810	2030	2202	2360	2586	2816	3095	3395	3665	3870	4020	4175	4370
1830	2050	2215	2375	2587	2831	3117	3412.5	3680	3885	4030	4177.5	
1850	2075	2220	2350	2605	2851	3149	3422.5	3695	3890	4035		4397.5
1870	2082	2235	2395	2625	2853	3155	3462	3700	3895	4050	4210	4415

. S. CRYSTALS. INC..

805 S. UNION AVE., LOS ANGELES 17, CALIF.





RAINBOW GENERATOR

Model 150
Patent Pending

NEW CIRCUITS incorporated in this instrument greatly simplify the TEST and ALIGNMENT of color TV circuits. NEW LINEAR PHASE SWEEP produces the COMPLETE PHASE RESPONSE CURVE, ossuring greater accuracy with foster olignment and elimination of color bar drift problems.

APPLICATIONS

**MASTER PHASE CONTROL test and alignment **CHROMA DEMODULATOR test and alignment (either I/Q or R-Y/B-Y) **QUADRATURE TRANSFORMER test and alignment **MATRIX CIRCUIT test and alignment **BURST AMPLIFIER test and alignment **PHASE DETECTOR CIRCUIT alignment for reference oscillator **REACTANCE CONTROL and REFERENCE OSCILLATOR adjustment **3.58 MC TRAP alignment **TROUBLESHOOTING and PHASE ALIGNMENT in the hame by picture patterns.



WHITE DOT GENERATOR

THE WHITE DOT GENERATOR ENABLES COMPLETE ALIGNMENT OF ALL COLOR CONVERGENCE CIRCUIT PLUS SUEL AS GENERAL TROUBLESHOOTING BY SIGNAL TRACING.

APPLICATIONS

OPVNAMIC CONVERGENCE—vertical and horizontal test and adjustment • DC CONVERGENCE—test and adjustment • DEFLECTION COIL—positioning for best convergence • BEAM MAGNETS—alignment for best convergence • DYNAMIC PHASE ADJUSTMENT—vertical and horizontal • FOCUS—test and adjustment of DC and dynamic focus • TROUBLESHOOTING of all circuits offecting convergence • LINEARITY—test and adjustment of horizontal and vertical sweep linearity.

FREE LITERATURE ON REQUEST

WIN-TRONIX

WINSTON ELECTRONICS, INC.

Dept. 101, 4312 Main Street Philadelphia 27, Pa. and boosted the number of commercial TV broadcasters.

ANOTHER MOVE to spark u.h.f. was made by the Commission, when they issued a ruling stating that telecasters could now own five v.h.f. and two u.h.f. stations. The proposal to increase ownership was made a year ago and the network owners agreed that the plan would serve to stimulate interest in the high channels.

Madame Commissioner Frieda Hennock dissented, asserting that additional ownership by multiple owners would not serve to solve the u.h.f. problem. In her opinion the revised rule sanctioned monopoly. She also felt that the numerical limitation did not take into account locations and markets of singly-owned operations.

Pending a firm decision on the high channels by the Senate investigating committee, a ruling on satellite or slave-station operation, and other complex hearing-room actions, few authorizations were being issued to new telecasters. At this writing, only the grants shown on this page were approved.

THE COMMUNICATIONS ENGINEER has played a stirring role in American industry and he will continue to blaze new trails that will benefit everyone. So viewed Merle E. Floegel of the Commission, during an address in Houston, Texas, before the IRE professional group on vehicular communications.

Describing the progress made in traffic control through mobile radio, the FCC spokesman said that one of the more recent developments has been in the regulation of auto traffic along the turnpikes; the high speed toll roads now springing up all over the land. He felt that the successful operation of these new wide-lane roads would not be possible without adequate communication.

Doctors and veterinarians, whose practices are in remote areas, the IRE audience was told, have also found

NEW TV GRANTS SINCE FREEZE LIFT

Continuing the listing of construction permits granted by FCC since lifting of freeze. Additional stations will be carried next month.

Visalia 43 13 16 16 17 17 17 17 17 17	192-198 316 644-650 22.73 210-216 316 800-806 99.1 524-530 216 626-632 190 192-198 222 180-186 316 210-216 238
---	--

NEW CALL LETTER ASSIGNMENTS

Florida Michigan	Tampa Grand Rapids	WFLA-TV KCRG-TV	8 9	180-186 186-192	

*ERP=(effective radiated power, kw.) . . =Call letters to be announced

NEW TV STATIONS ON THE AIR

(As of November 25, 1954)

The following new stations bring the lists published in previous issues up to date.

STATE, CITY	STATION	CHANNEL	FREQUENCY RANGE (IN MC.)	WAV	VIDEO ELENGTH N FT.)	VIDEO POWER (IN KW.)
Ālabama						
Montgomery Indiana Waterloo-	WSFA-TV	12	204	1-210	4.79	316
Ft. Wayne	WINT	15	476	-482	2.06	20.5
Kansas			•••		2.00	
Wichita	KAKE-TV	10	192	2-198	5.08	316
North Carolina						
Chapel Hill	WUNC-TV	4	66	3-72	14.61	100
Tennessee						
Jackson	WDXI-TV	7	174	-180	5.61	56.2
Wisconsin						
Milwaukee	WTVW	12	204	-210	4.79	251
Wausau	WSAU-TV	7	174	-180	5.61	89.8
Canada						
Calgary,						
Alberta	CHCT-TV	2	54	-60	17.8	100
Saskatoon,						
Sask.	CFOC-TV	8	180	-186	5.43	100
	nel 27. Norfolk	. Virginia, ha	s gone off the air.	KOPI	R-TV, chan	nel 4. Butte
Montana, has be						·

The frequency of the video carrier =1.25+ channel lower freq. limit. Total number of TV stations now on the air in U.S.: 410 (122 of which are u. h. f.) †Educational.

that radio-communication systems are extremely beneficial not only in serving humans, but livestock on the farms throughout the country.

Motion picture companies have also found radio communication almost indispensable to their operations, the FCC expert continued. When shooting out-of-door scenes, radio contact has been found to play an important part in coordinating action of widely separated groups, serving to time appearance before the eamera with split-second precision.

The FCC report also disclosed that radio equipment is now installed on vehicles used in conjunction with the maintenance of buildings and grounds of large universities, in orchards and cemeteries, on ranches, golf eourses, and hunting clubs; and it will also be found installed on lift trucks used for material handling in warehouses, factories, and refineries. Even some of the drive-in restaurants have begun to use two-way for relaying orders from the ear hops to the kitchen.

One of the most novel applications has been in the advertising field for skywriting, it was revealed. It's no longer necessary for a skywriter in a single plane to trace his message slowly in the sky. Instead, seven planes, flying at uniform speed, in straight-line formation, one alongside the other, can release puffs of dense white smoke at proper intervals and form a stream of block letters, or a single letter. This is done by controlling the valves in the smoke chambers by coded signals, which are transmitted by radio from a command plane, usually the center one of the seven. A separate signal automatically controls the valve in each plane.

In his opinion, the FCC expert said the most important role of the communications engineer is that of designing a system that will assist in coordinating the activities of an organization and thereby reducing non-productive time to a minimum. Certainly it is evident, he stressed, the book shows that American engineers have met his challenge and rung up an enviable record of achievement in radio-communications industrial history. . . . L.W.



Replace with RRco. rectifiers and diodes and insure long life and dependable performance ahead. Thousands of servicemen agree they're wonderful medicine!

SELETRON SELENIUM RECTIFIERS



Millions in use in radio and TV...as original equipment and replacements.

GERMANIUM DIODES



Video Detectors 1N60 and 1N64. U. H. F. Mixers 1N72 and 1N110. Other R.E.T.M.A. types available too.

We also manufacture germanium transistors.




SEE YOUR FAVORITE PARTS JOBBER

Seletron and Germanium Division RADIO RECEPTOR COMPANY, INC.

In Radio and Electronics Since 1922 SALES OFFICES: 251 WEST 19TH ST., NEW YORK 11, N.Y. FACTORIES IN BROOKLYN, N.Y.

Just Out

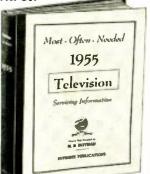

New SUPREME 1955 TV Manual AMAZING BARGAIN

The new 1955 TV manual is the scoop of the year. Covers all important sets of all makes in one giant volume. Your price for this mammoth manual is only \$3. This super-value defies all competition. Other volumes at only \$3 and \$2 each. Each manual has a whole year of service material. Includes all data needed for quicker TV repairs. Practically tells you how to find each fault and make the repair. More pages, more diagrams, more New Edition service data per dollar Covers all important 1955 Sets the best for less. Get SUPREME.

COVERS ALL POPULAR SETS

Supreme TV manuals have all needed service material on every popular TV set of every important manufacturer. Here is helpful, practical, factory-prepared data that will really make TV servicing and adjustment easy for you. Benefit and save with these amazing values in service manuals. These giant TV manuals have complete circuits, alignment facts, test patterns, response curves, service hints, all recommended changes, voltage charts, waveforms. and many double-page diagram blueprints. Here is your TV service material to help you do more expert work quicker; and priced at only \$3 and \$2 per manual covering a full year of material. Be ready to repair any model by having in your shop all nine TV volumes listed in coupon below. Or try the new 1955 TV manual to see what an amazing bargain you get for only \$3. Send trial coupon for prompt shipment, or ask your jobber.



The repair of any television set is really simple with Supreme TV service manuals. Every set is covered in a practical manner that will simplify troublethat will simplify trouble-shooting and repair. This is the help you need to find toughest faults in a lifty. Each \$3 TV volume covers a whole year of service ma-terial. New Television Servicing Course will aid you in learning TV. Be wise, buy Supreme Manuals only

139

TELEVISION SERVICING COURSE

Let this new course help you in TV servicing. Amazing bargain, complete, only \$3, full price for all lessons. Glant in size, mammoth in scope, topics just like a \$200.00 correspondence course, Lessons on picture taults, circuits, adjustments, short-cuts, UHF, alignment tacts, hints, antenna problems, trouble-shooting, test equipment, picture analysis. Special, only

RADIO DIAGRAMS



Here is your complete source of all needed EAD10 dragrams and service data to one original from most recent indies to pre-war old-times; home radios, an sets, combinations, changers, and hortables. Sensational values. Still sold at pre-Korean prices. Only \$2 for most almost the sensation of the

Sold by All Leading Parts Jobbers

December, 1954

NO-RISK TRIAL ORDER COUPON

SUPREME PUBLIC	ATIONS, 1760 Balsam, Highland Park, ILL
Radio Diagram Manuals	Rush today Radio manuals checked M at lef
Mast Often-Needed Series	and TV manuals below. Satisfaction guaranteed
1951 Radio Manual \$2.50	🗆 New 1955 Television Manual. \$3. 🔲 1954 TV, \$3
	□ 1052 TV V

Most-Often-Needed Series	and iv maintais below. Satisfaction guaranteed
See full description at left.)	
1954 Radio Manual, \$2.50	
1953 Diagrams	☐ 1953 TV Manual, \$3. ☐ UHF Manual, \$1.50
1952 Radio EACH	☐ 1952 Television Manual, \$3. ☐ 1951 TV, \$3
1951 Diagrams \$2.50	☐ 1950 Television Manual, \$3. ☐ 1949 TV, \$3
	1
] 1949 Radio)	□ 1948 TV. \$3. □ 1947 TV & FM, only \$2
□ 1948 🖺 \ PRICED	☐ Television Servicing Course, complete, only\$3
1947 5 AT ONLY	l
] 1946 Z	☐ 1 am enclosing \$ Send postpaid.
1942 § > S47	☐ Send C.O.D. I am enclosing \$deposit.
3 1941 0	
1 10 10 =	

| 1940 | 1940 | 1939 | 1939 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | 1940 | Name:

www.americanradiohistory.com



hallicrafters COMMUNICATIONS EQUIPMENT



S-38D RECEIVER

Smort new styling in this world-wide performing compact receiver

Fine for the new amoteur or as a reliable standby set. Communications type controls for standard broadcast plus 3 short-wave bands, 1650 kc to 32 mc. Sensitive built-in speaker. Headphone tip jacks. CW ascillator. Engineered throughout to give years of good service.

S-38D, complete with tubes...

\$4995



S-85 RECEIVER

Newly styled 10, 11, 15, 20, 40 and 80 reception. Tuning 540 kc to 44 mc. Automatic noise limiter, code reception with 3-position tone control and code pitch cantrol. One r-f, two i-f stages. Separate, calibrated bandspread. Built-in specker, headphone jack. Controls for sensitivity, band selector, tuning, volume, AVC an/off, noise limiter an/off, AM/CW, tone, code pitch and standby/receive.

S-85, complete with tubes

S11095

5-85, complete with tubes.... 119.95 5-86, same as \$-85 but AC/DC



S-94 & S-95 CIVIL PATROL RECEIVERS

These new high performance receivers are more than 10 times as sensitive as the older S-81, 5-82: under 1½ µv. Have greatly increased audio power and include an adjustable built-in relay squelch, which completely disables the audio system until a signal is received. Low noise grounded grid r-f amplifier. Built-in speaker, with provision far headphones.

\$5995 5-94, cavers 30 to 50 mc..... S-95, covers 150 to 173 mc.....59.95



HT-20 **100 WATT** BANDSWITCH TRANSMITTER **IVI-SUPRESSED**

All spurious autputs above 40 mc at least 90 db below full rated output. All stages metered with 6-position switch. Output tuning indication. Frequency range of 1.7 mc to 31 mc continuous on front panel control. 10-pasition crystals selector switch; provision for plug-in VFO an xmtr power supply. 7 tubes plus 5 rectifiers.

\$44950 HT-20, complete with tubes

Anywhere in the world -


order by mail direct from Harvey. Enclose estimated shipping charge. Excess will be refunded.



NEW AUDIO EQUIPMENT

Electro-Voice, Inc., Buchanan, Michigan is currently marketing the Model A20C, a 20-watt amplifier which combines the company's "Circlotron" circuit with a new critical damping control

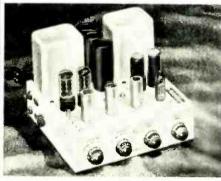All d.c. is removed from the output transformer permitting cool, optimum



utilization of the output tubes. damping factor control permits perfect match of the amplifier output impedance to the critical damping resistance of the speaker as well as to the type of enclosure.

Power output is 20 watts rated, 40 watts on peak. Frequency response is 20 to 20.000 cps \pm .1 db at full 20 Inputs include "ultra-linear" phono, magnetic phono, tape or TV, tuner or TV, hi-Z microphone while the controls consist of a function selector, record compensation, level, loudness, bass, treble, damping factor, and two hum adjustments on the chassis.

SCOTT FM-AM TUNER

Scott Radio Laboratories, Inc., 1020 N. Rush Street, Chicago 11, Ill. is now offering the Model 5001X FM-AM tuner to the audio trade.

The tuner features a separate power amplifier chassis and includes automatic frequency control, new selector switch for automatic level, and fre-



quency compensation to NARTB, LP, "Ortho," AES, and RIAA recording standards.

The chassis is chrome plated and has a hand-formed, genuine leather dial board. The tuner has seven controls, fourteen tubes, including the tuningeye and rectifiers.



Pay by Money Order or Check. P.O.'s accepted to 50% deposit with C.O.D.'s, Prices F.O.B. Los Ar

WORLD'S MOST AMAZING BARGAIN CATALOG

1954 EDITION-OVER 320 PCS SAVE 85% on SURPLUS ocked with SENSATIONAL

FACTORY CLOSE-OUTS and GENERAL MERCHANDISE!

GENERAL MERCHANDISE!
Fully Illustrated. Packed with
thousends of Bargains in Hand &
Power Tools, Radio Speakers, Ear
Phones, Electronics, Godgess,
Electric Meters & Blowers, all
types of Hydraulic Equipment,
Ourdoor & Sports Equip, Comeros,
Precision Instruments, Microscopes, plus many, many more.

SAVE : 85% - PALLEY S 000010 Mar mar marin

Send 50c To cover the cost of Handling and Mailing. CREDITED to your first

PALLEY SUPPLY CO. 2263 E. VERNON AVE., /DEPT. TP-12
Los Angeles 58, California

Save time — Step up

efficiency in **ELECTRONICS DESIGN**

ELECTRON

Here's a wealth of technical helb for efficiently handling electronies design problems—help that gives you answers already worked out by the country's top electronics ment—help that can save you hours of research and experimentation!

You'll find electronics mathematics and theory in concise form—design practices for hundreds of pieces of electronics equipment—and even the results of advanced electronics accovered experiments. Radio, television, facsimile, sound, and scores of other phases of electronics are covered—and it's all condensed, classified, and indexed for rulek, ensy use.

ELECTRONICS DESIGN LIBRARY

Edited by Markus and Zeluff, Electronics Magazine 4 vols., 2151 pp., 9 x 12, 3534 illustrations

Special price saves you \$6.00 Regular cata-logne price of books totals \$39.00; under this offer, price is only \$33.00, on easy terms.

4 vols., 2151 pp., 9 x 12, 3534 illustrations
Contains 1083 articles culled from recent issues of Electronics—the cream of information essential to design of electronics saves you \$6.00
Regular catalogue price of hooks totals \$39.00; under this offer, price this offer, price is column and price for Communication Engineers. Engineers.

EASY TERMS!

10 DAYS.	FREE	EXAMI	NATI	ON
----------	------	-------	------	----

McGraw-Hill	Book	Co.,	Inc.	Dept.	RTN-12
330 West 42r	nd St.,	New	York	36, N.	Υ.

Send me for 10 days' examination the ELECTRON-ICS DESIGN LIBRARY. In 10 days I will remit \$8.00. plus few cents delivery, then \$5.00 a month until \$33.00 is paid. If not satisfied, I will return books nosthaid. (We pay delivery if you remit with

this compon; same reim			remat wi	1421
(PRINT) Name				
Address				
City	Zone .	State		
Company				
Position				ill

The separate high-fidelity power amplifier is on a separate chrome chassis. It provides response flat from 30 to 15,000 cps with power output of 20 watts. A bulletin on this new unit is available on request.

LOW-PRICED SPEAKERS

A new low-priced line of 4" and 5" speakers is now available from Hevpner Manufacturing Company of Round Lake, Illinois.

The company advises that new manufacturing techniques permit the low price without impairing quality. Either a break or a cast magnet can be used in the construction with plugs. transformers, and/or brackets being supplied according to the customer's specifications.

Write the company direct for details on this new line.

NEW STEPHENS CABINET

An improved and redesigned version of the company's "Tru-Sonic" Model 617 cabinet with enclosed two-way loudspeaker system is now being marketed by Stephens Manufacturing Corp., Culver City, California, as the "Crusader."

The cabinet houses a complete twoway system consisting of the new 103LX low-frequency loudspeaker and 800-cycle crossover network. In addition, the audio system includes a Model 216 high-frequency speaker associated with a 2 x 4 multicellular



horn affording 40 degrees vertical and 80 degrees horizontal dispersion of high-frequency energy.

Constructed of birch hardwood in either silver hammertone or natural finish, the cabinet measures 2012" deep, 26" wide, and 36" high. It employs a modified bass reflex using rear horn loading to lower the fundamental resonance of the low-frequency diaphragm.

"MARK 30A" POWER AMPLIFIER

Brociner Electronics Laboratory, 344 E. 32nd St., New York 16, N. Y. is in production on a new 30-watt power amplifier and companion audio control center, both using the company's printed circuit production technique.

The "Mark 30A" is rated at 30 watts at 1 per-cent intermodulation distortion. At 20 watts the IM distortion drops below .2 per-cent and below this level is reduced to a virtually unmeasurable level. The entire amplifier

BLOWERS:



BLOWER AND HEATING ELEMENT

110 Volt 60 cycle: Blower 100 CFM; Heating Element can be turned on & off separately from blower Used to preheat Transmitter Tubes. Gov't. Surplus—#2570 \$10.95

115 V/60 100 CFM-Single, #1C939 \$ 8.	95
119 A 40 100 OLW - Studie: 2 10022	
115 V/60 100 CFM-Dual. #1C880	244
115 V 60 108 CFM-Pancake #20067 14.	50
115 V 60 140 CFM-Single Flange #1C807 13.	95
115 V 60 275 CFM-Dual Flange #2C069 21.	95
6 VDC 100 CFM—Single, #6100	50
6 VDC 150 CFM—Flange, #6150	95
24 VDC 10 CFM-Min,-Single #2410 5.3	
24 VDC 20 CFM-MinDual # 2420 7.	95

DYNAMOTORS

HEAVY DUTY MOBILE DYNAMOTOR:

44.00					
INPUT VOLTS:	OUTPU VOLTS:	T: MA.	STOCK No.	PRIC USED:	
14 VDC	230	90	D M - 21	\$6,95	
14	330	150	BD.87	3.115	\$5.95
14	250	50	O M - 25	6.95	8,97
i i	1000	350	BD-77	14.95	19.95
28	230	100	DA-IA	3.95	6.97
24	250	60	D M - 32	2.95	6,95
24	575	160	DM-33	2.95	
28	210	125	L1Y-22	5,95	
28	1000	350	PE-73	8.95	
12 or 24	500	50	USA 0515		4.95
12 or 24	275	110	USA 0516		4.95
6 or 12	500	160	PE-103	29,95	
12	230	90	PE-133	4.95	6.95
ii voc	185	210	DM-40	2.95	4.95
14 VOC	350	175	BD-83	3.95	4.95

PE-101 DYNAMOTOR—6 or 12 Volt. (Reprints of original CQ conversion articles—Oct. Dec., '52 Issues—(urnished.) This is the Oynamotor the Hams have been talking about! Early adapted to supply 625 V. © 150 MA. and 325 V. 125 MA. @ 12 Volts—0 300 V. 90 MA. and 160 V. 110 MA. \$4.95

POWER SUPPLY -24 VDC-3 Amp output: 115 Volt 60 cycle input. Completely filtered with 0-75 VDC Output Meter & 2 Tungar Bulbs-Used, Tested. \$12.05 GEARED HEAD MOTOR—110 Volt 60 cycle—1.9 RPM. Size: 2'2" x 2'/2" x 2'/2". Torque: 75 oz. in. NEW: \$1.05

THIS MONTH'S SPECIAL: FL-8 & FL-5 FILTERS: BOTH For \$1.59

ANTENNA EQUIPMENT

MAST BASES-INSULATED:



MP-22 BASE — (Illustrated) Ins. spring action; direction of bracket can be raised or lowered easily.....\$2.95

MP-48 BASE-Insulated

RECORDER, SIGNAL GENERATOR-AMPLIFIER, & Voltage REGULATOR

AMPLIFIER, & Voltage REGULATOR
RECORDER, SIGNAL GENERATOR—AMPLIFER,
AND VOLTAGE REGULATOR UNIT of BC-963
TRAINER—Used for assimilated Radar identification
when used with BC-142 Scope. Signal Generator generates various AC wave forms. Recorder was used to
record difference in scope and generator wave forms a
guided by operator, 110 Volt 60 cycle operation—with
Manual. Shipping Weight: 270 lbs.
OR AVAILABLE AS SEPARATE ITEMS:
SIGNAL GENERATOR—AMPLIFIER: Can be adjusted for various wave forms, 110 Volt 60 cycle operation. Voltage regulated supply 300 Volt 100 MA. 6.3,
5.4.; 5 Volt 3 A. Power Supply, 15 Tubes: 1/7A6,
3/7A8, 37FT, 37N7, 15Y3GT, and 4/YRI150

With Tubes and	210 05
With Tubes and Manual	413.33
RECORDER—Complete with 115 V. 60	cycle 1/125
HP Gear Head Motor, Veeder Counter, Pen, etc. and with Manual	20 019
Pen, etc. and with Manual	\$13.33
CONSTANT VOLTAGE REGULATOR—	\$12 DE
CONSTANT VOLTAGE REGULATOR— 115 V. 60 cycle, 80 VA, Sola #30726	\$12.33

METERS:

WESTON AC AMMETER:

(Pictured.) In portable leather case, with Test Leads, 2½", 0.15 AC and \$5.95 0.3 AC Scale



TS-291/U VOLTOHMMETER—Meter 3" Sq., 1000 ohms per volt. D'Arsonval Movement—0.300.600 VDC Scale and 0-1 Meg. Case size: $3\frac{1}{2}$ " x $5\frac{3}{3}$ " x $2\frac{1}{4}$ ". W/Test Leads P/O 1-56 Test SetNEW: $\frac{3}{2}$.19.100 NEW:

BC-306 Ant. Tuning Unit f/BC-375-191. Used: \$2.95
BC-455 Comm. Rec.—6 to 9.1 MC w/Tubes. Used: 7.95
R-25/ARC-5 Rec.—1.5 to 3 MC. No Tubes. Used: 10.95
R-27/ARC-5 Rec.—6 to 9.1 MC. No Tubes. Used: 5.95
BC-459 Trans.—7 to 9 MC—w/Tubes. Used: 5.95
BC-456 Modulator—w/Tubes. Used: 5.95
BC-605 Amplifier—w/Tubes. Used: 6.95
BC-709 Amplifier—Used: \$2.50 New: 3.95
BC-327 Amplifier—Used: \$1.95 New: 2.95
BC-212G Amplifier—Used: \$1.95 New: 2.95

TRANSFORMERS-115 V. 60 CYCLE PRI.:

600 VCT/100 MA—6.3 V/5 A.: 5 V/3 A\$4 650 VCT/50 MA—6.3 V/2.5 A: 6.3 V/.6 (Rect. 6x5) 1	
350 VCT/40 MA—6.3 V/2.4 A; 6.3 V/.6 (Rect. 6x5) 1 2500 V/.015 A; 2.5 V/175 A; 6.3 V/.6A	
1890 V/12.6 MA Tapped 2.5 V. 2 Å	
5 Volt CT-25 A; 10.000 V. Ins. Open Frame	.95 .95 .95

Choke	12.5 Hy/100 MA	15
	12Hy/250 MA., 180 Ohm	
Choke	I5 Hy/I65 MA., I25 Ohm	15
Choke	5 Hy/150 MA., 85 Ohm	50

BC-463 RADIO NEW ITEM MODULATOR

And TRANSMITTER ——20 Watt Crystal controlled Transmitter. Freq. coverage 67 to 74 MC. Automatic A.F. Tone Source for Five Freq. Output Meter 0-18 & 0.180 VDC & MA Readings. Complete with Tubes: 1815: 8/1215GT: 2 12SM7: 2 6V6GT; 2/6L6; 1 V R-150: & Crystal. Also 20 Watt Modulation Trans. \$16.95 Motor, & Fan. Excellent Cond.—Price.... \$16.95

CORDS—CABLES—PLUGS:

CD-605 w/C-410 Trans. & PL-55 F/HS-30\$	0.79
CD-604 w/C-410 Trans. & PL-54	.71
CD-874 w/JB-47 Box & PL-55	.7:
CD-265 w PL-68 Ea. End	.71
CD-501 BC-654 to PE-103 Dynamotor	2.75
CD-280 15 Ft. Single #8 Shielded-15 Ft	1.5
CABLE-F/BC-375-191-PL-59-64 or 61 Ea. End	
Each	
CABLE-TCS-Rec. to P.S. or Trans. to PS. Each	3.00

COAXIAL CABLE & CONNECTORS

CD-1071 CORD-With PL-259 Plugs each end. 50 ohm coax 2 Ft. long. Prices: 59¢ Each-Or in Lots of 10 @ 500 Ea.
PL-259—Plug. Ea. End & 32"—RG-54 U—58 ohm.500
SO-239 Chassis Conn. f/PL-259 (Removed)...3 for \$1,00
UG-21/U—Plug ea. end & 32"—RG-11/U—75 ohm.500
UG-22/U—With 4" Coaxial Cable..............500


AS PREVIOUSLY ADVERTISED

Address Dept. RN . Minimum Order \$5.00 . Prices F.O.B., Lima, Ohio • 25% Deposit on C.O.D. Orders

RADIO SALES

132 SOUTH MAIN ST. LIMA, OHIO

TV SERVICEMEN: here's the help you need

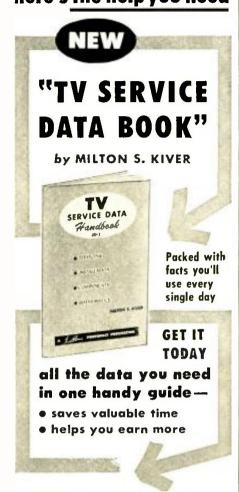

Instant TV Servicing and Installation Reference: Instant IV Servicing and Installation Reference: Have at your finger-tips all of the most frequently needed charts, tables and formulas you require in Television servicing and installation. Includes charts on fuses, color codes, attenuator pads, monochrome signal specifications, guy wire lengths, etc.—all the data you'll ever want in your daily work. Save valuable time on calculations by quick reference to the calculations by quick reference to the tables of mathematical constants and electrical formulas. Speeds your work for greater earnings.

Trouble-Shooting Guide: Includes section on TV trouble-shooting. Lists common trouble symptoms and tells how to locate defective components. Recommends most effective methods for use of test probes and other accessory equipment. You'll want to keep it handy in your tube caddy for quick reference at the bench or in the field. It pays for itself in a single day's work. Over 100 pages, $5\frac{1}{2} \times 8\frac{1}{2}$.

norm over roo pageoro, and	72 .
ORDER JB-1. \$ 50	ORDER TODAY
HOWARD W. SAMS € CO.,	INC
Order from your Parts Jobber today, or write to Howard W. Sams & Co., Inc., 2203 East 46th St., Indianapolis 5, Ind.	
My (check) (money order) for \$	

enclosed. Send.....copy (ies) of "TV Service Data Book" (JB-1, \$1.50).

Name.....

(outside U.S.A. priced slightly higher)

ventilation is provided by the use of perforated metal for most of the chassis.

measures 3½" x 12" x 9". Adequate

The companion 30C audio control center is a self-powered preamplifier that provides complete facilities for



selection of radio, TV, tape or phono inputs, separate turnover and roll-off controls for record compensation, continuously adjustable bass and treble controls, and a loudness control. The audio control measures 31/2" x 10 1/4" x 6". Three tubes are used.

AMPLIFIER KIT

Tech-Master Corp., 75 Front Street, Brooklyn 1, New York is now offering a deluxe amplifier kit, based on the Williamson circuit with modifications, the TM-15A.

This 20-watt unit has distortion less than .25 per-cent at normal listening levels. For ease of assembly and wiring, all tube sockets and terminal strips come riveted in place on the chassis. Complete step-by-step pictorial diagrams and schematics permit the builder to complete the construction in record time.

A companion preamplifier-equalizer kit, the TM-15P, which has four input channels and a selector switch for FM, AM, or TV, crystal or reluctance pickups, tape recorder or other signal source, is also available from the com-

SPEAKER SYSTEM

Gramercy Sound Associates of 175 Fifth Ave., New York 10, New York is




now offering an 8" speaker system which incorporates the Goodmans "Axiette 101" speaker.

The speaker, an English hi-fi unit. employs a hyperbolic cone with a stepped, plastic-impregnated linen suspension. Frequency response is 40 to 15,000 cps. flux density is 13,500 gauss.

The cabinet which houses this speaker is made of ¾" wood and is available in hand-rubbed mahogany or

PHOTO FLASH

100 W. SEC. STROBE OUTFIT

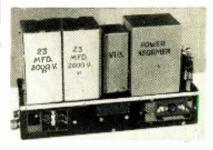



LAMP ASS'Y & FLASH BULB

LEARN THE CODE AS THE F.C.C. SENDS IT

TG-34-A CDDE KEYER_115/2:10 VAC 60 cycle
—Compact carrying case 10 9/16 x 103g x
15 1:1/16."—Sh. W. 45 lbs.—Ilas self contained speaker—Complete w/tubes & manual

BRAND NEW. \$22.95

USED, excet. \$14.95

TG-10 CDDE KEYER-115 YAC 60 evele-in standard metal cathinet 11 x 24 x 1819"—WI. 63 lbs.—W/tubes & photo-cell—Used, exect 519.95 Either Keyer used with printed paper tape or use self contained oscillator for hand keying.

NO. 1 CODE FREE EITHER ORDER

**TNDIVIDUAL TAPES for the following lessons—#1. #2. #8. #11—New in metal containers—ea...\$1.25 ±2. ±8. ±11-Now in metal containers—ca...\$1.25 WESTINGROUSE PX.14 D.C. ARMETER.11/2 acute taev. .1—1—10 anns. Gpen face portable. P.M. mowing coil. .005 ohns—53.1 meter face—41/2. 51/3×11/2"—with test leads & leather carrying case. BRAND-NEW in ordg. box. . \$9.95

AARON ELECTRONIC SALES

Detroit 7, Michigan 3830 Chene Street

Have You Seen **POPULAR ELECTRONICS?** It Is Now on Sale!

PREPARE FOR A GOOD JOB!

BROADCAST ENGINEER ELECTRONICS RADIO SERVICING

Television Servicing

(Approved for Veterans)
SEND FOR FREE LITERATURE

BALTIMORE TECHNICAL INSTITUTE 1425 EUTAW PLACE, BALT, 17, MD.

blonde finishes on birch veneers. Total weight is 35 pounds. It measures 24'' high, $10\frac{1}{2}''$ deep, and 17'' wide.

Literature on the Model 101 is available on request.

WEATHERPROOF COAXIAL

University Loudspeakers, Inc., 80 S. Kensico Ave., White Plains, N. Y. is marketing a full-range weatherproof coaxial loudspeaker, the Model BLC, which offers good reproduction for p.a. applications.

The Model BLC measures 22½" in diameter and 9" deep. The unit comprises a low-frequency woofer that is coupled to a balanced compression-type exponential horn. The horn starts with a large 8" throat which extends to the 22½" diameter mouth, giving highly efficient low-frequency response. Coaxially mounted, to conserve space, is a separate high-frequency tweeter with its own driver unit. coupled to a wide-angle horn incorporating the company's patented "reciprocating flares" principle. A built-in frequency dividing network provides for crossover at 2000 cps.

SHURE STUDIO MICROPHONE

Shure Brothers. Inc., 225 W. Huron Street, Chicago 10, Illinois has just introduced a new studio microphone, the Model 333.

The unit is a uni-directional microphone which features extended fre-



quency response (30-15.000 cps \pm 2½ db), the company's patented "Uniphase" system, small size, and slim design.

The new microphone, while designed specifically for TV studios, motion picture studios, radio stations, and professional recording studios, is suitable for professionals and hi-fi enthusiasts who want quality recording in the home.

A copy of catalogue 33 describing this microphone is available from the sales division of the manufacturer.

PREAMP-EQUALIZER

Fairchild Recording Equipment Co., 154th Street and Powells Cove Blvd., Whitestone 57, N. Y. is now marketing its Model 240 preamplifier-equalizer.

This completely redesigned and restyled unit incorporates several new circuit advances, including one-knob control for both program selection and record equalization. An exclusive "Balanced Bar" control system allows tailoring the tonal content to best suit

December, 1954

ELECTRICAL ENGINEERS

01

PHYSICS GRADUATES

with experience in

RADAR of ELECTRONICS

or those desiring to enter these areas...

The time was never more opportune than now for becoming associated with the field of advanced electronics.

Because of military emphasis this is the most rapidly growing and promising sphere of endeavor for the young electrical engineer or physicist.

Since 1948 Hughes Research and Development Laboratories have been engaged in an expanding program for design, development and manufacture of highly complex radar fire control systems for fighter and interceptor aircraft. This requires Hughes technical advisors in the field to serve companies and military agencies employing the equipment.

As one of these field engineers you will become familiar with the entire systems in-

volved, including the most advanced electronic computers. With this advantage you will be ideally situated to broaden your experience and learning more quickly for future application to advanced electronics activity in either the military or the commercial field.

Positions are available in the continental United States for married and single men under 35 years of age. Overseas assignments are open to single men only.



Never Heard T PA

READ ABOUT THE GOODMANS AND OTHER GOODMANS LOUDSPEAKERS

ROCKBAR CORPORATION, DEPT. BL-5 215 East 37th Street, New York 16, N. Y.

Please send complete description of the Axiom 80 and other Goodmans Loudspeakers.

Name	
Address	
City	ZoneState

the acoustics of the room. In addition, a carefully-engineered listening level control has been included to set



the range within which listening is to be done.

The unit features a low-noise cascode-input stage and a special selfcontained power supply which contributes to its high gain and low noise.

CONVERSION KIT

Dynamu Magnetronics Corporation, 21 N. Third St., Minneapolis 1, Minn. has developed a "conversion kit" which contains heads and all of the necessary components to convert home type and professional tape recorders to "studio quality" units.

Complete, illustrated step-by-step instructions are included covering the installation and electrical changes that are required. Currently, two kits are available, one for recorders using two heads and the other for three-head units.

Pentron, Airline. Revere, RCA. Wilcox-Gay, Knight, Masco, Concertone, Mugnecorder. Mugnecordette. and Webcor recorders can be converted with the kits. For details on the model number conversion kit to use with a specific recorder, write the company direct.

PORTABLE AUDIO UNIT

Amper Corporation of 934 Charter Street, Redwood City, California has come up with a 25-pound portable amplifier-loudspeaker unit, the Model 620.

The new portable incorporates a specially-designed loudspeaker with a



complementary 10-watt audio amplifier in an acoustically correct enclosure. Response of the 620, measured in air by accepted acoustical standards, is essentially flat from 60 to 10,-000 cycles. The unit is encased in a Samsonite luggage-type carrying case.

"UNIVERSAL ADAPTER"

Audak Company. 500 Fifth Ave., New York 36, N. Y. is introducing a universal adapter which permits the

QUARTZ CRYSTALS

FT-243-.093" PIN DIA .-. 486" PIN SPC

FOR HAM AND GENERAL USE . GUARANTEED

49c each - 10 for \$4.00

Low Frequency—FT-241A for SSB, Lattice Filter etc., .093* Pins, 486* SPC, .marked in Chanel Nos. 0 to 79, 34th Harmonic and 270 to 389, 72nd Harmonic Listed below by Fundamental Frequencies, fractions omitted. 5910 6370 6450 6470 6497 6522 6547 6610 7350 7380

TUNING UNITS TUNING UNITS
Channels 10 & 12
—foundation coils
and condenser for
80 meter VFO or
exciter—less xtals
98c

add 20c postage for every 10 crystals (orless)

49c each-18 for \$4.80 99c each - 10 for \$8.00

Spec.-200 KC without holder-59c, 3 for \$1.50

Spec .- 200 KC or 500 KC in FT241 A Holder. \$1.79 ea.

Indicate second choice; subst. may be necessary



.520 TENTH ST. N. W. - WASH. D. C., DEPT. N.

and Engineers

BETTER TV RECEPTION

New 2nd Edition

IT COVERS ALL YOU WANT TO KNOW ABOUT

fringe and low-signol areas

BETTER TV RECEPTION has become the standard guide for the installation technician and a papular text for TV enthusiasts.

better reception 😘 in fringe and low signal areas

Book No E&E-TR2

\$2.50 per copy (paperbound) at our store



For Additional Coverage

RADIOTELEPHONE LICENSE MANUAL. Typical

RADIO HANDBOOK. GIANT 13TH EDITION. A one-volume library of radio information with extensive, simplified theory. Detailed how-to-build-it data on dozens of items of practical radio equipment. Book No. E&E-RH13 ...\$6.00*

SURPLUS RADIO CONVERSION MANUAL. VOL.
1. Practical conversions. Write for list of contents. Book No. E&E-SM1......\$2.50* SURPLUS RADIO CONVERSION MANUAL. VOL.
2. Companion to Volume 1.
800k No. E&E-5M2......\$2.50*

*Plus any tax.



RADIO & TELEVISION NEWS

My Dealer Is...

company's tone arms to be used with practically any cartridge of any make.

The special compass-pivoted construction, which requires no springs and uses only three parts, maintains uniform point pressure irrespective of climatic changes, offers practically no restraint upon the stylus travel, has virtually no frontal oscillation, and keeps the cartridge in full view, thus permitting accurate stylus-to-record alignment.

FOLDED HORN CABINET

G & H Wood Products Co., 75 North 11th Street, Brooklyn 11, N. Y. has recently added the "Klipsch-Cabinart KR-5" to its line of speaker cabinets.

This corner folded horn, designed to accommodate either 8- or 12-inch speakers, is available in finished, unfinished, or leatherette-covered models. The cabinet performs exceptionally well using the University 6201, Electro-Voice triaxial 12", or the Altec-Lansing 601A.

The KR-5 weighs 25 pounds and measures 21" high. 16%" wide, and 14" deep. It can be wall-mounted, corner-hung, placed on a table, a bench, or a shelf.

A.F. CURVE TRACER

Maico Company, Minneapolis, Minn. recently introduced a new and improved version of its audio frequency curve tracer.

The new unit features a 12" cathoderay tube to make it especially suited for research, quality control, and production line testing of receivers, microphones, speakers, filters, transformers, and other partial or complete audio assemblies. -30-

FM-Only Tuner (Continued from page 73)

with a single flick of the finger. A fine tuning knob is provided for exact tuning of weak stations in the pres-

ence of severe interference.

The over-all dimensions of the tuner are but $4\frac{1}{2}$ " x 13" x $10\frac{1}{4}$ ". The instrument is housed in a metal case which provides protection from dust, and is styled so that the tuner can be used "as is" on a shelf or table. If cabinet mounting is desired, this can be accomplished readily with a simple escutcheon without removing front panel or adding shaft extensions.

Designed to surpass the quality requirements of the best FM transmitters and to operate without noise and interference under the most adverse conditions, this new tuner combines all significant technical features and refinements known at this stage of the art. The over-all circuitry is shown in Fig. 2. Unique operating convenience, attractive styling, and moderate cost make it applicable to serious home music systems as well as to professional broadcast monitoring.

modern select designs for best maintain modern circuits or



Signal, Marker, and Pattern Generator for UHF and VHF.

"DO-ALL"

Model 750

Versatile in concept, the RCP Model 750 can check and test alignment of front ends, IF's sound and pix trups, linearity, synes, sweeps, positioning, focus and deflection.

- FEATURES:
 Inductiner insures accuracy of within ½ of 1% over the entire range of 9 Mc to 900 Mc.
 All VIIF frequencies are on fundamentals.
 RF's and IF's are clearly calibrated on a large eiched aluminum dial.
 Steady horizontal bars, vertical bars and crosshatch pattern individually produced on all channels.



Greatest testing performance ever hullt into a compact instrument. Tests all tubes in current radio and television receivers, as well as in color TV receivers; checks transmitting, hearing and, bullasts, guscous rectifiers, an I tuning indicators. A streamline approach to tube test charts allows for simple and speed, operation and permits easy, rapid addition of new tabe test data. bata is also given on current color TV tubes. Checks CR picture tubes, both black and white and color, with CR adapter cabe (available at slight additional cost). Black and white picture tubes can readily be reactivated with this tester.

Only \$51.95 Net Only \$51,95 Net

See Your Local Parts Distributor or WRITE DEPT. RN-12 for LATEST RCP CATALOG



RADIO CITY PRODUCTS COMPANY EASTON, PENNSYLVANIA

ENJOY 3 COLOR TELEVISION FILTER SCREEN NOW

Changes dull eye-straining black and white pictures into beautiful color tones, Seconds to attach. No tools used. Helps eliminate glare. Order direct. Send \$1 for screen size up to 16". \$1,25 size 17", \$1.50 size 20", \$2 size 21", \$2.50 size 24", \$3 size 27". We pay postage except on C.O.D. orders. Satisfaction guaranteed. Inquiries from dealers also welcomed.

Zingo Products, Johnstown 19, New York

"Snooper" Geiger Counter



PRECISION RADIATION INSTRUMENTS 2235 RT S. La Brea, Los Angeles 16, Calif.



Superhet Kit



ROCKET 115K-Latest Single Hand superhet circuit for ultimate in sensitive reception and tonal quality. Kit includes all necessary parts, punched chassis, attractive bakelite mahogany cabinet, built-in loop antenna, iron core IPs, big Ainleo V spkr.; tubes: 125K7, 125A7, 25Q7, 50L6, 3325. Automatic vol. control, beam power output. Tunes 540 to 1700 Kc. Simple step-by-step instructions included.

Plaza 812K 2-Band AC-DC Super Kit..net \$20.75 Globemaster 814K 3-Band Super Kit..net \$24.75 All kits supplied less were and solder. Please include 25% deposit with C.O.D. orders, Dept. N-11.

CORONA RADIO & TV CO 370 Broodway New York 13.

December, 1954

"SHALL I BUY A TURNTABLE OR A RECORD CHANGER?"



GET THE FACTS

from one of America's leading manufacturers of professional recording and playback equipment. Plus a FREE Strobe Disc for checking Turntable Speeds. Write today.

			ANY, I		1 1, N.
					bles ar
Name	*481.47974		400 8741	 	
Addres	S	.4		 · ·	
City			7000	***	

RADIO-TV Service Industry News

AS REPORTED BY THE TELEVISION TECHNICIANS LECTURE BUREAU

AS THE year draws to a close it is both interesting and educational to look back and review what happened in the electronics industry during 1954 and appraise the immediate and possible future effects of the year's developments on the fortunes of independent electronic service as a business.

Color Television

The Federal Communications Commission's Christmas gift to the public last year was the acceptance of industry-developed standards for a system of compatible color television. The industry-wide National Television System Committee (NTSC) accomplished a truly remarkable achievement in developing and proving out the basic standards for this color television system in the comparatively short period of time it required to accomplish its objectives,

At the outset, there were many optimistic reports about the number of color television receivers that could be produced during the first year of the life of compatible color TV. Some early estimates freely predicted the production of more than a quarter of a million color television sets by the end of 1954.

A number of manufacturers produced fifteen-inch sets to test consumer reaction to quality of color and to price. While there was a tremendous interest in the new medium and an enthusiastic response to the quality of color reproduction, the small screen sets failed to attract many purchasers. About mid-year, the nineteen-inch color television receiver became a practical reality with a twenty-one inch set in the offing. Now, at year's end, it looks as if 1955 will see the industry's aggressively competitive manufacturers well on their way to making the general public color TV conscious and hungry for sets.

During the developmental stages of an entirely new product it is difficult to forecast the pattern that will eventually be created to handle the work of its installation, maintenance, and service. However, just as monochrome television created entirely new servicing facilities and techniques over that required for radio, so will color television change the service picture to adequately take care of its more complex needs.

The first requirement for color television servicing is the need for a vast army of trained technicians. Electronic and production engineers have proven time and time again that once the basic technology for a commercial product has been determined from practical experience all production barriers are quickly surmounted. Because of this factor, it would be quite possible for the production of color television receivers to outstrip the available, trained technical manpower to handle the installation and servicing.

This situation points up the tremendous educational job that faces the entire television industry and one that is of particular importance to the independent service industry.

Fortunately, the industry as a whole and individual manufacturers and technical book publishers have been making a wealth of technical training material available to the independent service industry.

Every operator of an independent service business should assume some personal responsibility in the programs to train color television technicians in his own area or locality. Service businessmen should take an active part in the formation of all-industry committees in their communities to work with educational authorities to make the RETMA-sponsored technician upgrading programs available in their local trade schools.

For some time to come set manufacturers will have to stay in close touch with their receivers in the hands of purchasers. The best qualified estimates about the amount of service that will be required on the average color set is ten calls per year. It is also estimated that the average time required on each service call will be two hours. The warranty contracts now in force seem to be priced on the basis of these estimates.

It would be unwise for any service business operator to accept contract service on color television receivers at current contract rates without some positive assurance from the set manu-

POLICY MEANS GREATER PROFIT BARGAINS

RECORDER

DUAL SPEED Stock No. 33/4" and 71/2" AMP-19 1954 MODEL \$999 4A10

Reg. \$149.95

Reg. \$149.95

It's ready to play—complete with latest Prest-O-Matie Push Button Keyloard. Features ? Record Level Indicators, Itadio-Phono-TV Injut Jack, Hecord Lock Button. Fast Forward and Teverse. External Sheaker Jack. Foot Control Outlet. Line Companies of the Property of the Control outlet. Line Control outlet. Line Control Course. Inspect of the Property of



1200 Ft. Tape on 7" Dia. Reel



STOCK NO. X.249 STOCK NO. X.245 LOTS OF \$1.59 12. EACH. \$1.59 Single. ea. . . \$2.19 Lots of 6, ea. 1.79

This famous braint tope exhibity acids for \$5.50-nit Olson gives you a 71% lscount. Perfect in every speect, this duality tape is muous for its low noise yeal and uniform output, req. response 50-15,000 ps-red oxide base—14" tide, fleg. \$1,27, seven included—hits all tastic ree included—hits all tape its clinic speed and prediction of the seven control of the cont

Espey HI-FI AM-FM RADIO CHASSIS

Complete with 10 Matched Tubes, Knobs, \$4995 Escutcheon, Antennas and Hardware, Only

Golden Classic Custom

Hi-Fidelity Amplifier



Espey Chassis with 12" Magnavox Espey Chassis complete with 12" Speaker—570CK NO. AS-117— Co-axial Speaker—170CK NO. ONLY ... 559.95

ONLY

S52.56 A5-118 ONLY

OLSOI scoops the mattern with this tremendous Hi-Fi Buy. Sells for S147.36, but Olson put cash on the line so you ce shall be selled to the line so you ce chassis backed in orthogonal designed for Quality Installation chassis backed in orthogonal control of the selled the orthogonal chassis backed in orthogonal current of the orthogonal chassis backed in orthogonal chassis backed in orthogonal chassis backed in orthogonal chassis backed in orthogonal chassis of the property of the chassis of the chasis of the chassis of the chassis of the chassis of the chassis of

With Crystal Turn-over Cartridge and 2 Precious Tip \$2895

With GE V.R. Turn-about Cartridge and 2 Precious Tip Needles. STOCK \$32.95

NEW WEBSTER-CHICAGO (Webcor) **ALL-SPEED AUTOMATIC DISKCHANGERS**

Now you can save \$20.00 on the intest model Webcor rd changers. Your choice of either model, Ideal for with Espey Chassis or any radio, amplifier or TV set installation.

Plays a 1" stack of 7", 10" or 12" records at 33 1/8, 5 or 78 RPM. Features include automatic adjustment for any dia. record stack, improved spindle and automatic shut-off after last record. For 115 V. AC cy. Base size 133%" x 12" x 8½. Shpg. wt. 13 lbs. Webcor Mounting Base-STOCK NO. X-363, ea. \$4.95. Shpg.



Guaranteed to bring unexcelled listening pleasure and technical perfection at the most reasonable price. Delivers 10 full writs constantly, with much thirdler peaks. Wide range flat vesponse from 20 to 30,000 cycles at less than 15 to 107 distortion. Features include phono carridge selector switch, treble and task boosts, faur injusts: 1 mike, 1 and 1, crystal phono and 1 magnetic phono. Push-null antibut—4 88 and 16 ohms. Built-in Fre-amp. Can be used with any PM 5 feet of the property of



Nationally Advertised Tester-SUPER METER

Combination Volt-Ohm-Millinneter PLUS Capacity, Reactance, Inductance & Decibels Complete with In-structions and Test Leads

| Measures capacity | Capacity |

Electron-O-Jr. Sound System Kit



Stock No. \$695 Reg. \$19.95
CAN BE ASSEMBLED IN TWO HOURS

CAN BE ASSEMBLED IN TWO HOURS hield Christmas (fift. That hay you know can now hulld and operate a complete 1-tube plus rectiner-ambilities of electronics. Institute 5 PM Speaker, Dual Electronics. Institute 5 PM Speaker, Dual Electronics. Condenser, 75 ma Selection control and knob. Input and Output Transformers. Carbon granulas and Country Transformers. Carbon granulas and Country Transformers. Carbon granulas of the Country of the Cou



12" CO-AXIAL SPEAKER

Stock No.

5-168

\$1295

\$1295

highest of notes with utmost elections for better heat dissipation. Shop wt. 6 lbs.

▲ ▲ COMBINATION DEAL! ▲ ▲ ▲ Golden Classic Amplifier & 12" Co-Axial Speaker

Save plenty when you order this spe-cial Dison combination. You get the GG to the left Amplier Pitts the 12° Co. Set Str. Full as described above for this drastically reduced price. Sips. wt. 19 lbs.

Stock No. AS-112

GIANT TV ANTENNA KIT

Complete kit—nothing Stock No. AU-24 ception on all Ville channels. Rusliproof Ahrevatt Aluminum. Contains: 2 six-element content bays. 1 pair ment content bays. 300 ohm lead-in. 3 standoff insulators. 2 screw-res standoffs. 1 menting have. 1 may eling.

al toys. Dalmast sections. 60 ft.

al toyst. Salmast sections. 2 screescale. I section 3 standorf handators. 2 screemuttag hand large street.

I clamp assy. I pipe street.

I tag belts and full hastructions. Save—order 12 sets—
only 8119.50. Shpt. wt. each

13 lbs. Express only.



ALLIANCE TV TENNA-ROTORS

Standard Model F-4 \$1875

STOCK NO. AU.15 and lamp indicates and of 360° rotation. control box & rotar_ hpg. wt. 12 lbs.



STOCK NO. AU-12 Control bar on top-Control bar on top-with direction point-er. Control box & rotor-shpg. wt. 12 lbs.



STOCK NO. \$2625 Fully automatic—set it and forget it. Control hox and ro-tor—shpg. wt. 13 lbs.

A-Conductor Cable
Stock No. W-62 5 905
100 ft. only 5 905
Horon-Sipp.
Wt. 3 lbs.
Thrust Bearing
for Heavy Antennas.
Slipg.

STOCK NO. AU-13 52.91

- WHOLESALE

Get Olson's LOWER than wholesale prices on famous brands—brand new and Double Guaranteed by Olson and Manystacturer. Send for your FREE copy now—it's mailed bi-monthly with new low bargains each mailing.

Mall orders for merchandise on this page to:

232 RESISTORS KIT

\$395

December, 1954



Value Packed with 200 M2-watt, 20-4 and 2 and 2 swatt; and 12-5 to 25 watt wirewound resistors worth over \$24.50.5-10 -200% tolerances, telludes III.C. Clarostat. Centralian, etc. 100% Observed to the control of the

HOOK-UP WIRE

OF 5-T. A5-T E D

Deluxe

\$197

3 kHT (15-100 Ft. Cods)-55.00
Every foot absolutely perfect. Includes solid and stranded types-cotton, rubber or plastic insulated, 300 volt, 75° C Helictest wire. Most of the code of th

"Powerfone" Cradle-Phones

Self-powered with Built-in Buzzers Complete two

\$595 SET STOCK NO. X-448

3 complete sets. each. . . . \$4.95 6 complete sets, each \$4.50 12 complete sets, each \$3.95

12 complete sets, each \$3.95

Perfect for Christmas Giving,
Works up to one mile, burable,
dependable, Lifetime electro-magnet carphone, Gold-plated diaphragm carron mike. Connects in
2 seconds—blace on table or mount
on wall. Complete—you get 2
telenhones with built-in buzzers, 2
eradies, 2 batteries, 50 ft. double
cable. Handsome Gift Carton,
Money-back Guarantee if not twice
as Good as you Expected! Shpg.
wt. 4 lbs.



OLSON RADIO WAREHOUSE 275 E. MARKET ST., AKRON 8, OHIO 275 E. MARKET ST., AKRON 8, OHIO
Send remittance with order (Add for postage 5e for
sent dollar's worth ordered—10c for each dollar's worth
If you are more than 1000 miles away, 01,50N kEto the state of the stat

QUANTITY	STOCK NO.	DESCRIPTION	PRICE	TOTAL
NAME		TOTAL		
ADDRESS	ZONEST	ADD POSTAGE .		

OLSON BARGAIN STORES TO SERVE YOU IN: Pittsburgh, Pa. Chicago, III. Cleveland, O. 5918 Penn Ave. A Chicago, III. Cleveland, O. 2020 Euclid Ave. Visit the store nearest you

MINIATURE ELECTRIC MOTOR STOCK NO. X-403 \$119

3 FOR 52.95, SINGLE ...

Ideal for running model cars, boats, remote control. Operates on 3 to 6 Voits pc. 5 pole one bearings and Almice 6 Magnet. Shaft Size 1 Vg. 8 4 3 4 2 4 3 8 ppg. vt. 1 lb.

WAREHOUSE 275 EAST MARKET ST., AKRON 8, OHIO WORLD'S LARGEST MANUFACTURER OF CUSTOM BUILT TELEVISION

SILVER ROCKET 630 CHASSIS Featuring Syncromatic Tuning

NO DRIFT UHF-VHF-DX

ONLY THE MATTISON 630 ELIMINATES DRIFTING APART OF PICTURE AND SOUND ON UHF, VHF and DX RECEPTION. SELECT YOUR CHANNEL.. SOUND IS AUTOMATIC. (Syncromatic tuning is an exclusive Mottison 630 Circula) cuit)

Tube Complement: 29 tubes 3 rectifiers 1 CRT

SILVER ROCKET 630 Chassis with built in UHF Tuner



All Channel JUHF Tuner

UHF Cascode I.F. amplifier aids additional I.F. stage. Very important because UHF transmitters operate with moderate power and RECEIVER must be sensitive to give top notch UHF performance.

SILVER ROCKET 630 CHASSIS with TUNEABLE **BUILT-IN BOOSTER** for Better DX Reception

Tube
Complement:
2B tubes
3 rectifiers
1 CRT

Select Your Channel . . SOUND IS SOUND IS AUTOMATIC!



Tuneable *J* Booster

Broad band single knob control pre-amplifier built in to eliminate long leads which may cause regeneration and attenuation of signal. • ONLY THE MATTISON 630 CHASSIS HAS AN ALL CHANNEL TUNEABLE BUILT-IN BOOSTER THAT INCREASES SIGNAL STRENGTH UP TO 10 TIMES.

ALL CABINETS MADE IN MATTISON'S OWN CABINET FACTORY. AVAILABLE IN EVERY FINISH AND STYLE, WRITE FOR COMPLETE

DEALERS! SERVICE MEN! Here is your opportunity to become the "important" TV Dealer in your area for THE FINEST CUSTOM-BUILT LINE OF TV RECEIVERS. FREE! Write for Mattison's merchandising portfolio explaining the "UNASSEMBLED PLAN" and "\$1,000,000 FLOOR PLAN."



• Mattison Television & Radio Corp. 10 West 181st St., Dept. RN, N. Y. 53, N. Y. facturer for subsidization if his receivers required a higher average number of service calls or if the service time required exceeded two hours on an average.

Because of the need for extensive operational information on their sets and the many unknowables about the amount of service they will require, set manufacturers will maintain a rigid control over placement of service contracts and in the supervision of service on their receivers. It is quite likely that some set distributors may establish the personnel and facilities to give factory-supervised service under programs that will provide for the gradual shift to independent service firms as service requirements become better known.

Good service association could speed the time when color TV service will be shifted to the independents by working closely with distributors and their color television servicing organizations.

Association Developments

Perhaps the most outstanding development in independent service during the year was the rapidly-widening interest in association activities and the formation of new service associations in practically every section of the country. This interest in cooperation clearly reflects the growing concern among established service businesses over the future of independent service in the fast-growing industry and the desire to stabilize the business of servicing on a higher plane of business ethics and technical proficiency.

Studies of the memberships of new service associations indicate that a stable service industry has been created in the cauldron of competition. The members of this industry have come to realize that the basic problems of service business stability can only be accomplished through the close cooperation of ethical competitors. There is also a recognition that technical competence alone is not sufficient for the successful operation of a service business. The growing interest in management factors reflected everywhere in the development of service selling programs of various types and in the elements of service business management presages a new and potent force at work in the activity of electronic servicing.

Another event of interest during the year was the formation of another regional association to bring together practically all of the individual associations of various types in its area to formulate programs that embrace all of the elements of electronic servicing. The Eastern Television Service Conference, Inc., comprising 37 service associations located in states along the Atlantic seaboard, completed its organizational pattern and held its first full-fledged series of meetings in Philadelphia early in the year.

The associations that banded together to form the ETSC include those organized by service dealers, dealers



...GIVE the indispensable electronics magazine!



Readers depend on the authoritative coverage, the important articles, the vital information in every issue on . . .

- TELEVISION
- RADIO
- AUDIO
- MICROWAVES
- COMMUNICATIONS
- RADAR
- NEW PRODUCTS

It's the Christmas gift your friends in electronics will appreciate most.



USE THE HANDY ENVE-LOPE FACING THIS PAGE TO ORDER GIFT SUBSCRIP-TIONS AND YOUR OWN AT THESE SPECIAL RATES.

with service departments, and employed technicians. The conference was held in connection with a 3-day color television symposium sponsored by the Council of Radio & Television Service Associations of Philadelphia. Officers elected by the delegates included Harold "Dusty" Rhodes of Patterson, N. J., as chairman; Bert Bregenzer of Pittsburgh, Pa., as vice-chairman; John Rader of Reading, Pa., treasurer; and Ferdinand J. Lynn of Buffalo, N. Y., secretary. Trustees of the corporation include Roger K. Haines of Haddonfield, N. J., Albert M. Haas of Philadelphia, Pa., and Max Liebowitz of New York City.

By means of their dynamic house organ, the "TSA News," the Television Service Association of Michigan has succeeded in crystalizing the thinking of legitimate service businessmen in all parts of the state about the dire need for and effectiveness of cooperation through association. The Detroit TSA, nationally known for its successful efforts in combatting unethical service practices with full cooperation of their Better Business Bureau and local law enforcement agencies, continued to set the pace for tangible results from cooperative effort. The Greater Detroit Electronics Parts Show, a cooperative venture sponsored by twelve independent parts jobbers in Detroit and Pontiac, represented the first project of its kind in the area held exclusively for dealers and service technicians.

The annual clinic and fair sponsored by the Texas Electronic Associations brought hundreds of service businessmen to Dallas from all parts of Texas and from adjoining States. The attendance far exceeded that recorded at the first state-wide affair held in Forth Worth in 1953.

Delegates from member associations made tentative plans to expand the activities of the state association to interest service business operators in communities where local associations are impractical.

The annual NATESA convention, held in Chicago late in September, brought delegates from member associations in all parts of the country and interested observers from many nonaffiliated associations. Included among the observers was a service operator from Caracas, Venezuela, whose efforts may result in the broadening of NATESA to become an international

The primary purpose of the annual NATESA convention is to permit committees to complete the final details of their assignments before presentation to the membership for approval and the election of officers for the ensuing year.

The consensus among observers who attended the convention was that the organization is structurally sound and merits the wholehearted support of all service and dealer organizations. It was noted that there is an homogeneity and enthusiasm among the present member associations of NATESA that



Airborne LOng RAnge Navigational equipment! Determine the exact geo-graphic position of your boat or airplane!

AN/APN4 Loran set. Frequency range 1700-2000 KC, complete with 116B/APN4 indicator, R9B/APN4 receiver, crystal and blugs.

R-65/APN-9 LORAN Indicator, LATEST MODEL UNIT. Complete in one light weight case. Accurate on a maximum range of up to 1600 statute miles, within 157 of the distance from the ground transmitter. The finest unit available at any price! \$295.00

BRAND NEW. Only

10-64/APN-4 LORAN Indicator. Uses 5CP1 Cathode ltay Tube. Easily converted to test oscilloscope, panadapter, analyzer, visual counter, etc. Contains externelly accurate 100 KC crystal to time sweeps and marker pips at 2, 20, and 100 KC or 50, 50th and 250th memberships at 2, 20, and 100 KC or 50, 50th and 250th memberships at 2, 20 and 100 kC or 50, 50th and 250th memberships at 2, 20 and 100 kC or 50, 50th and 250th memberships at 2, 20 and 100 kC or 50, 50th and 250th memberships at 2, 20 and 100 kC or 50, 50th and 250th memberships at 2, 20 and 100 kC or 50, 50th and 250th memberships at 2, 20 and 100 kC or 50, 50th and 250th memberships at 2, 20 and 100 kC or 50 the section of the counter circuits for FM demodulation, or to time camera shutters, etc. Double deek chassis. 5CP1 mounted in full tube shield, lots of octal sockets (used 25 tubes). Less small tubes. COMPLETE with 5CP1 Crystal, and schematic in cabinet 1912 xW xW xW with the they last

160 METER RECEIVER

High Voltage Power Supply; can be easily for 110 VAC, 60 cycle operation, complet with instructions, brand new, less tubese.	\$9.95
6B4G-6H6 or 6SK7 NEW	
RCA TV GENERATOR-WR-59A, used. Exc.	\$89.50
AT4/ARN-1 ANTENNA-Brand New, Exc., MOTOROLA REC., XMTR., and POWER	SUPPLY.
Type T-69-20, 30 to 40 Mc. AM, 6VDC. Used, good, less tubes	\$29.50
RL-42 BEAM ROTATOR—Used, good— \$1.95 cm: 3	for \$4,25
3" DUAL SCALE PANEL METER-0-1 KV and 0-10MA	, \$3.95

CORDS FOR BC369 CD-515 and 513.,...es. \$2.50 SURPRISE PACKAGE

20 hs. of MISCELLANEOUS ELECTRONIC EQUIPMENT—WORTH MUCH MORE THAN \$1.95

BC-611—WALKIE-TALKIE-CHASSIS, complete. but less tubes, outer case, and speakers, \$24.95

OIL CONDENSERS-8 mfd @ 600 VDCca. \$0.98 .2 @ 4000ea. 2.2.2. @ 4000 V. TUBES-10 FOR \$3.00

957 955 9006 9002 125Q7 211 1F4

SPECIAL TUBES 5R4GY95c 371B95c 6L6 (1614) ...95c 720BY\$9.95 VR15095c 307A95c

TURE RARGAIN 4AP10 \$1.95 each 5FP7 3CP1 4 for \$7.00 5CP1. New\$4.95 ea.

WIRE-Cotton covered. No. 22, solid enameled 1000 ft. 12 V. DYNAMOTOR-Output 440 V, 400 MA. \$9.95 8C-347 INTER-PHONE—Amp. used, 95c; less tubes

AN/APRS—An Airborne superhet radar search rec. Freq. range 1000 to 3000 MC. Rec. has a 10 MC IF band width operating from 80/115 VAC, single Phase 80 to 2800 cps. and one amp at 26 VDC. \$250.00 Complete with tubes......

25% Deposit required with orders PHONE: Calumet 5-1281-2-3

WRITE FOR NEW BULLETIN AND PRICES.

Remote Control DOX and brists for story property ARC-5/R-28 2 MTR RCVR-2 moter superhet, absolutely one of the BENT available today! Tunes from 100 to 156 mes, in four crystal chainels. Easily converted to continuous tuning.) Complete with \$15.95 verted to continuous tunings. Complete with \$15.95 10 tubes. Excellent. T-23.ARC-5 Transmitter. 100-150 MC. \$22.95 Complete with tubes. Used. Exc. \$22.95 APN-1 Magnetic Units. You can build "Versatile Sweep Frequency Generator." \$5.95 MV (APT'S Transmitter—operates over a freq. of 300 to 1400 MC outbut 30 Watts. The carrier freq. is 10 1400 MC outbut 30 Watts. The carrier freq. is 10 2 MC of the MC of t moles-modulated with effective random noise fred, up to 2 MC.

Complete with tubes. \$99.50
T-26 Telephone chest unit with F-1
S2.39
Western Electric Transmitter. \$2.39
Historia Electric Transmitter. \$1.50
Western Electric Transmitter. \$1.50
Western Electric Transmitter. \$1.50
Western Electric Transmitter. \$1.50
Used only \$1.50
List S0 to 00 eyele. complete with tubes, photocell and carrying case. \$14.95
List S0 to 00 to 00

COMMAND EQUIPMENT (274N-ARC5, ATA)

D-101 27V@1.75 285VC-.075 amps . . . 1.95 Carlson Stromberg Chest Mike—New \$1.29 ea.

Carlson Stromberg Chest Mike—New ... \$11.29 ea.

CRYSTALS

100 assorted: FT 241, FT 243,
DC 34, DC 35, Excellent ... \$100 per 100 \$14.95

DC 34, DC 35 excellent ... \$100 per 100 \$14.95

DC 34, DC 35 excellent ... \$100 per 100 \$14.95

DC 34, DC 35 excellent ... \$100 per 100 \$14.95

PE103 Excellent ... \$100 per 100 \$14.95

PE104 Vibrator Supply ... \$24.95

PE104 Vibrator Supply ... \$24.95

PE104 Vibrator Supply ... \$100 per 100 per 100

SPECIAL! Your choice of any of these 4 for \$1000

2 Meter Converter-Easily converted to two meters
—Used-Excellent. complete with conversion in
structure. OUTSOASD AMPLIFIER—Excellent.

verted to 2 meters-Used Excellent, complete with
conversion instructions.
—e. \$3.95

RT/34 APS 13 TRANSCEIVER—Used as a tail
warning radar on 415 MC. Containing a 30 MC IF
strip and various other parts, those units have
been stripped of RF sections and all tubes, but are
less the section of the section o

NAVY ARB RECEIVER

195 KC thru 9 Mc. Includes broadcast band, Excellent. \$19.95
Complete with tubes and dynamotor Like New \$29.95

dynamotor Like New

MN-26-C Remote Controlled Navigational Direction
finder and communications receiver. Manual DV in
Self contained dynamotor supply. Complete installation, including receiver, control loox, loop azimuth
control. Left-Hight Indicator, plugs, loop transmission
line and fiex, shafts, oper. & main. manual. Ideal for
ERAND NEW

MN-20-E Loop. Brand New

MN-20-E Loop. Brand New

MN-26-E Receiver sex. freq. 150-1250 KC. \$39.50

2.9-6mc.

MIKES. HEADSETS & MICROPHONES

MIKES, HEADSETS & MICROPHONES
T-28 Telephone chest unit with P-1 Western Electric Transmitter.
HS-33 Telephone Chest unit with P-1 Western Electric Transmitter.
HS-33 Telephone Chest Che

BROADCAST BAND RECEIVER

Navy ADF Receiver Dz.1. made by RCA. Continuous 15 to 1750 kc in 6 bands, gear-train tuning with vernier and coarse scales, broad or sharp band-pbas. CW or MCC. All controls of the property of the coarse of the c

ALL ITEMS F.O.B. CHICAGO

R W ELECTRONICS

N.J.R.T. TUBES 70% 10 90%

GUARANTEE ALL NIRT TUBES ARE BRAND NEW AND FULLY GUARANTEED FOR ONE YEAR

Туре	Price	Туре	Price	Туре	Price	Туре	Price	Туре	Price
1A7GT	.45	6AL5	.39	6BZ7	.95	6W4GT	.45	12V6GT	.50
1B3GT	.67	6AQ5	.39	6C4	.39	6W6GT	.45	12X4	.35
1H5GT	.38	6AQ6	.36	6086	.45	6X4	.39	19BG6G	1.15
1L4	.50	6AQ7	.68	6CD6G	1.15	6X5GT	.35	19T8	.75
INSGT	.62	6AR5	.45	6F6	.45	7E6	.40	25BQ6GT	.75
1R5	.48	6AS5	.50	6H6	.53	7 X 6	.58	25L6GT	.45
155	.40	6AT6	.39	615	.40	7L7	.77	25W4GT	.45
1T4	.48	6AU4GT	.70	616	.50	12AL5	.40	35A5	.49
104	.48	6AU5	.82	6K6GT	.39	12AT6	.35	3585	.38
105	.40	6AU6	.45	6L6	.62	12AT7	.65	35C5	.38
1X2	.65	6AV6	.39	6R7	.49	12AU6	.38	35L6GT	.45
3A4	.45	6AX4GT	.59	654	.39	12AU7	.55	35W4	.45
304	.48	6BA6	.40	6S8GT	.51	12AV6	.50	35Z5GT	.45
3Q5GT	.48	6BA7	.57	6SA7GT	.41	12AV7	.60	45	.53
354	.48	6BC5	.49	6SB7Y	.76	12AX4GT	.55	50B5	.41
3V4	.50	6806	.45	6SC7	.59	12AX7	.55	50C5	.41
5U4G	.55	6BE6	.39	6SD7GT	.39	12BA6	.40	50L6GT	.59
5Y3GT	.39	6BF5	.55	65K7GT	.39	12BA7	.57	70L7GT	1.07
5Y4G	.39	68G6G	1.20	6SL7GT	.49	12BE6	.41	76	.42
6AB4	.42	6BH6	.45	6SN7GT	.55	12BH7	.65	81	1.25
6AF4	.92	6BJ6	.41	6SQ7GT	.37	128Y7	.65	117L7GT	1.19
6AF6	.75	6BK7	.89	6T8	.75	12BZ7	.65		
6AG5	.49	6BL7GT	.65	6U7	.56	12SL7GT	.49	117P7GT	1.39
6AH4	.67	6BQ6GT	.77	6U8	.59	125N7GT	.50	117Z3	.39
6AK5	.59	6BQ7A	.92	6V6GT	.45	12SR7met	.55	807	1.25

T.V. PIX TUBE BRIGHTENER

\$1.39 FREE SENSATIONAL "MAGI CLOCK" MYSTERY ELECTRIC CLOCK

You can see through it . . . what makes it work? List price . . . \$18.15 . . . yours absolutely free with order of \$75.00 or more . . . or with orders totalling \$100.00 over a period of 30 days.

Many 7 volt types not listed. All tubes individually boxed. For orders under \$10 add \$1 handling charge. Tubes offered subject to prior sale. Prices subject to change. All orders shipped F.O.B. 25% deposit on c.o.d. shipments. Make checks payable to New Jersey Radio and Television Tube Co. SEND FOR FREE TUBE LISTING.



NEW JERSEY TELEVISION SUPPLY CO.

Sole Distributor of NJRT Tubes

906B WESTFIELD AVE., ELIZABETH, N. J. EL. 5-3900

FACTORY REPAIRS

HI-PO TV RECTIFIER TUBES

LAST LONGER

Makes Picture brighter, larger

ON ALL MAKES AND TYPES OF

TEST EQUIPMENT

Send units via parcel post-will quote after inspection. Write for NEW FREE Catalogue

GENERAL ELECTRONIC DIST. CO. 🛂 . 100 PARK PLACE, NEW YORK 7, N. Y. . 🍱



LABORATORY DESIGNED for UHF and VHF1 It's NEW!

MOSLEY

2-WAY

TV ANTENNA SWITCH

- · Positive rotory oction!
- · Silver-to-silver contacts!
- · Compact size!
- · Solderless easy to install!
- · Low cost!

Another PREMIUM QUALITY MOSLEY Accessory for BETTER TV INSTALLATIONS! STATE OF THE PARTY OF THE PARTY



will inspire many presently nonaffiliated associations to join the national organization as its 1954-1955 program unfolds.

Service Association Objectives

A study of the published objectives of service associations released during the year reveals an interesting concordance in what is badly needed to stabilize servicing and to make it a worthwhile venture as a business enterprise. The following list represents a cross-section of the needs of the industry that were specified in all association programs during the year.

Public Relations-The set owning public is still inclined to look upon television receivers as comparatively simple devices that are easy to repair. Also, there is a marked tendency to put up with degraded pictures rather than to spend money on maintenance.

Service operators are universally of the opinion that a strong public relations program in the interests of competent electronic service is a responsibility of the over-all industry. They feel that the set manufacturers have over-simplified television in their advertising and thus are primarily responsible for the general set-owner attitude about service and the qualifications for handling it efficiently. They are of the opinion, too, that component manufacturers and parts distributors have a sufficient stake in the profitable sale of service that they should assume some of the responsibility for the badly needed public relations programs.

It is widely felt that television broadcast stations should, for the protection of their own investments, carry out regular educational programs to setowners about picture quality. Television set-owners are the broadcast station's customers. The quality of the pictures cannot be any better than the reproduction that appears on the viewer's screen. Surveys have shown that almost half of the owners of television sets are now watching degraded pictures on their screens because they do not realize the sets need adjustment or service.

Since there is no indication that television will replace radio as the major medium for information, the degree of its long-range success will depend upon its ability to attract and hold audiences as the major vehicle for entertainment. For this reason service people feel that continuing programs about picture fidelity should be a must with every television broadcasting station.

Elimination of Bait Advertising-Service associations are inclined to essume the responsibility for fighting the use of bait advertising and its associated evils in their communities. Wherever effective associations have been formed and they have gone on record with a code of ethics to which members must adhere, the local Better Business Bureau has been highly cooperative in helping to weed out unethical service companies.

Technician Identification—For many

years associations have been striving to find some plan which would provide for recognition of the competent electronic technician and make it tough for the pseudo-serviceman to mess up the industry through his fumbling activities. This need for some system of technician identification has led many service people to advocate the licensing of electronic technicians on either a local or state-wide basis.

While most service business operators have realized the need for a practical and effective system of identification, the majority have feared that the evils of political control through any form of licensing would far outweigh any advantages that it might gain. The result is that plans are now underway both on local and national levels for the service industry itself to establish an identification plan that through widespread publicity would provide all of the advantages of licensing without the dangers inherent in political control.

Consumer Sales—There probably is not one service association in the country that did not go on record this year against the indiscriminate sale of replacement products to consumers. It is claimed by many service operators that consumer knowledge of dealer costs of replacement tubes and parts poses one of their biggest problems in maintaining good customer relations and one that is tough to handle.

Many parts distributors have recognized the growing need for concentrated selling of replacement products to bonafide service technicians and service businesses only. These distributors have instituted systems of customer identification to eliminate overthe-counter sales to consumers. Where such systems have been installed the distributors report an enthusiastic response from their technician-service customers.

Technician Training—Service association members fear that unless some cooperative plan is developed for training technicians in the practical phases of color television circuitry as it is employed in production-line receiver models. a bad state of confusion will develop. They point out that during the early days of monochrome TV, lack of coordination in the scheduling of technical lectures by the various manufacturers brought about a situation where as many as three different meetings were scheduled in the same town on the same night.

Many associations now plan to offer set and equipment manufacturers a lecture coordination service in their areas to minimize the possibility of confusion and lack of attendance due to multiple meetings.

As the year draws to a close it appears as if the service industry will go into the new year in common agreement on all major objectives. There are strong indications that national unity will be achieved in the very near future which will permit the independent service industry to present a solid front in fulfilling its programs.



The Newest and Handiest Waveform Analyzers. For the first time a Cathode Ray Tube is incorporated into a probe small enough to be held in the palm of a hand ..., only $1\frac{1}{2}$ round by $7\frac{1}{2}$ long. The waveform is even sharper and clearer MINIATURE DSCILLOSCOPE Model MO-1 The smallest and most compact oscilloscope on the market yet an industrial giant. MINIATURE DSCILLOSCOPE round by /½ long. The waveform is even sharper and clearer than on larger scopes. The control cabinet is small and compact occupying less than ½ so, foot on the bench and is connected to the Probescope by a 3½ ft. shielded cable. The back of the cabinet is provided with a holder for the probe and cable. INPUT IMPEDANCE: Horizontal and vertical, 2.2 megohms shunted by approximately 15 MMFD. SENSITIVITY: 100 MV vert. full scale; 1 volt horiz. full scale; FREQUENCY RESPONSE: Vert. SPECIFICATIONS: INPUT IMPEDANCE: 2.2 megohms shunted by cap. of 100 MMFD. with Cathode Follower Input. Price \$77.95 f.o.s. N.Y.E. SENSITIVITY: 100 MV full scale, vertical input only. FREQUENCY RESPONSE: Flat to 7 cycles to ZOO KC — 3 db; Horiz. 4 cycles to 100 KC — 3 db. SWEEP RATE: 20 cycles to 30 KC in 5 steps. SIZE: 9" high, 6" wide, 5" Price \$77.95 F.O.B. 60 KC — 3 db point. SWEEP RATE: 20 cycles to 30 KC in 5 steps. SIZE: 9" w., 6" h., 5" d. Price \$79.95 F.G.B. N.Y.C. 44-05 30th AVENUE LONG ISLAND CITY 3 N. Y. PROBESCOPE CO.>



TN-65/APQ-15 Makes a 2-METER TRANSMITTER

COAX SPECIALS!

51.5 OHM COAXIAL CABLE similar to above. 500 it. roll 100 ft. roll RG-34/U 71 OHM COAXIAL CABLE.	24.95
625 dia, 5 KW r ting, 8 oft rolls with PL-173 plug at one end, New.	
SO-153 CHASSIS PLUG to match PL-173	.98
RG-59 COAX. 25-ft, length with PL-	1.95

701A XMTR. TUBES complete with dope sheet. Hurry. \$2.95 each or 2 for \$5 FILAMENT TRANSFORMERS for above \$2.95 \$2.90 ppd.

SAVE ON TRANSFORMERS:

MINIATURE LINE MATCHING
TRANSFORMERS 151
Gulus 25c for postage & handling)
Gulus 25c for postage & handling)
For the control of the c

Ratiof 6 MW 200-5000 cy, 500 v.
BMS lost,
MS los

EXCITER UNIT FOR WILCOX XMTR.

APS 13 Makes a 420 MC RADIOPHONE

When converted with our easy-to-follow schematics and instructions Rance in most cases easi to meters. Fine for communication, ranches, farms, \$3.95 \$3.95



ctc State of the Complete with RF sections, cavers to klet and 30 MC LF, strip less tubes dying for all minor parts not needed for conversion wit 13 lbs. COMPLETE APS-13, New ... \$19.95

TEST EQUIPMENT
TS-45-\$125 1017 PULSE GENERATOR, \$49.50
AN APA-10 PANORAMIC ADAPTOR \$99.50
TSX-45E PULSE ANALYZER write for prices
TEST OSCILLATOR larged with Model ZA Jiliya
75 MC langling coults.

NEW METERS

NEW METERS
Removed from New Equipment
0-4 AMPS rf GE 3" Round enclosed in aluminum
case. For accurate Xmtr. In Hags. \$3.95
COMBINATION! Chalce of 3" Black distraction?
AA Anti-tan Mirr Anna 3 Tasel acceptant
GO-0-60 MICRO AMPS. Western Lectric. . \$4.95
Westron Freq. METER. 1 acc. \$1.495
TS-24/ARR-2 YEST SET. Gold plat described in the characteristic and the control of the contro

RCA SURPLUS TY CAMERA

FREE CATALOG! All shipments ouse! No COD's please—Calif. buyers



Dept. RL 4109 Burbank Blvd., Burbank, Ca'if CABLE: Harjo Phone: Victoria 9-2411

What's New in Radio

(Continued from page 100)

The 51SB includes such extras as voice-operated and push-to-talk controls, a speaker de-activating circuit, TVI suppression, and unitized construction for quick and easy removal of any major section. Completely selfcontained, the 51SB requires no external accessories with the exception of a microphone.

Complete information on this unit is contained in Bulletin 51SB which is available on request.

TY TUBE-CONTINUITY CHECKER

Visulite Company, 423 Broome Street, New York 13, N. Y. is now offering an inexpensive continuity tester which will check instantly the



filaments of loctal, octal, and all miniature tubes simply by plugging them into the sockets provided.

In addition, the new unit checks filaments of picture tubes, fuses, appliances, motors, electric circuits by means of the test leads provided. It operates on 110 volts a.c. or d.c. Builtin resistors prevent danger of shock or burning out of the items under test.

The instrument comes complete with test leads and an instruction sheet.

ROTARY RELAY

Automatic Electric Sales Corporation. 1033 W. Van Buren St., Chicago 7, Ill. has developed a single can-type rotary relay which is said to be capable of replacing whole banks of relays. or combinations of relays and stepping switches.

The Series OCS is small, light, and resistant to shock, vibration, and temperature changes. It measures $3\frac{1}{4}$ " x 2 7/16" x 1 25/32" in size and weighs from 14 to 20 ounces, depending on

Complete information on this unit which combines relay and stepping switch functions is available from the company.

OUTPUT TRANSFORMERS

Microtran Company. 84-11 Rockaway Beach Blvd., Rockaway Beach, N. Y. is now offering a push-pull driver and output transformer line that has been designed to be used with highpower alloy junction transistors.

To avoid switching transient volt-

RECORDING TAPE (Plastic Base) 40% OFF (NEW)

- 1200 ft. plastic tape with plastic reel included. Each reel individually boxed. Choice of nationally famous top quality brands such us:

 Welcor (12806) 3.20; Reeves (SPN-12) 3.20; Audio (1251 3.25; Nentch 111-A) 3.25; Encore 3.25; FREE! A 7.95 tape carrying case included with purchase of 12 new tapes!

* * * * * * * * * * * * * USED RECORDING TAPE (PLASTIC BASE)

ATTENTION: Radio Statisms, electronic calculators, industrial users: We have the new 1½ or 2 mil mylar. "sound-plate." "lifetime, plate, we will thuy or exchange your present 1 mil mylar or plastic tapes,

1.99 for 7"-1200 foot .99 for 5"- 600 foot .59 for 4"- 300 foot .29 for 3"- 150 foot Plastic reeis included with all above sizes

* * * * * * * * * * * * USED "MYLAR" TAPE (1 Mil)

(Impact Strength 9 Times Greater Than Plastic Tage)



1200 ft. (7" reel)...2.59 1800 ft. (7" reel)...3.89

New empty plastic reels in boxes for easy labeling. 3" 10¢: 4" 22¢: 5" 24¢: 7" Professional reel (2/4" hub) 29¢ ea. EMPTY BOXES: 3" 3¢: 4" 5¢; 5" 5¢: 7" 5¢ ea.

We carry all brands of new tape, recording blanks, tape recorders. etc., at low prices. PLEASE IN-CLUDE SUFFICIENT POSTAGE.

COMMISSIONED ELECTRONICS CO.

2503 Champlain St. N.W.

Washington 9, D. C.



WE WILL HELP YOU to start learning TV the practical way by assembling a TRANSVISION TV KIT in EASY STAGES. For only \$39 you get PACKAGE #1 (standard first pkp. for all of our kits). This Package gives you the BASIC CHASSIS and over 150 TV COMPONENTS with complete Industrial of the property of the prop structions. Drawings. Photos. and Service Booklet. When ready, you order the next stage (pkg. ±2), etc. Low prices make your complete kit a terrific buy.



- A CONTROL OF SAME	🗫 Shows 6 Great TV Kits:
1	EXCLUSIVE: Only Transvision TV Kits are adaptable to UNF. Ideal for
4 194	FRINGE AREAS. No Previous Technical Knowledge required. Write now
N America	
. nG	TRANSVISION
117	THE OLDEST NAME IN TV RITS
No. of Lot, Lot, Lot, Lot, Lot, Lot, Lot, Lot,	

NEW ROCHELLE, N. Y. ---- MAIL THIS COUPON TODAY ---

į	TRANSVISION, INC., NEW ROCHELLE, N. Y. Dopt. RN.12
	☐ I'm enclosing \$
	Name
	AddressState

RADIO & TELEVISION NEWS

37


ages in the class B output stages and to maintain good circuit balance, bifilar windings are used. Frequency response is 200 to 4000 cycles. Power level is 2 watts.

The driver transformer provides a suitable match to the 25-ohm input impedances of the output stage. The output audio transformer matches a 4-ohm speaker load.

MINIATURE EARPHONES

The Fenton Company, 15 Moore Street, New York 4, N. Y. is now offering a line of clip-on miniature earphones for every requirement.

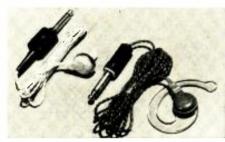Some suggested uses for these hearing-aid quality earphones are dietat-



ing machine transcribing, monitoring, phone order desk, simultaneous listening, radio communication, private sampling of recordings in music stores, etc.

These new "Fen-Tone" clip-ons are available in 128, 1000, and 2000 ohm models with flesh colored plastic clasp or earmold.

REPLACEMENT FLYBACKS

Five new correct replacement flyback transformers have been added to the TV replacement line offered by *Triad Transformer Corporation*, 4055 Redwood Ave., Venice, California.

All of the new units are ruggedized versions of original equipment and are electrically and mechanically interchangeable with the manufacturer's original equipment. Three of the new units are designed for use in *Admiral* receivers while the other two are for *Emerson* receivers.

A copy of the company's TV replacement guide, TV-54, contains model numbers and chassis for which the new transformers are suitable and is available on request.

RENEWAL PICTURE TUBES

The Tube Division of Radio Corporation of America. Harrison, N. J. is now marketing two 70-degree TV picture tubes, 14" and 21" types, for replacement service applications.

The RCA-14HP is a 14" reetangular glass tube with a screen size of 11%" by 8½". It has low-voltage electrostatic focus and magnetic deflection. It has a diagonal deflection angle of 70 degrees, a maximum high-voltage rating of 14.000 volts, design-center value. It features a spherical "Filterglass" facculate.

The RCA-21YP4-A is an aluminized 21" rectangular version with a screen size $19\frac{1}{8}$ " by $14\frac{3}{16}$ " and a spherical "Filterglass" faceplate. Its other specifications are the same as the 14" ver-



Nothing else to buy for soldering, sealing, cutting, mending, joining and smoothing.

SEE NEW WELLER GUNS & KITS AT ELECTRONIC PARTS DISTRIBUTORS

Junior SOLDERING GUN

- New, Compost Design
- Heats in 5 Seconds
 Over 100 Watts
 - Trigger Switch Control
- Dual Spotlights

An ideal soldering tool for shop or home No other soldering gun or iron offers the professional quality, practical features and low price of the Weller JUNIOR.



ELECTRIC CORPORATION 810 Packer St., Easton, Pa.

MODEL

SOLDERING GUNS • SOLDERING KITS • POWER SANDERS



December, 1954

JUST OU1 Ask to See It•

HOW TO FIX 500 ILLUS **ELECTRIC** IRONERS ROASTERS DRYERS BROILERS VACUUMS HEATERS WIRING MOTORS WASHERS CASSEROLES
OIL BURNERS
PERCOLATORS
FOOD MIXERS
REFRIGERATORS
ALSO MANY

A Shop Companion & Ready Reference for Electric & Gas Home Appliance Servicemen, Mechanics & Dealers covers Servicing & Repairs, Tells How to Locate Troubles, How to take Appliances Apart. How to Repair, How to Assemble & Connect, Gives testing methods, wiring diagrams & complete service data. Answers Your Questions, EASY TO READS OTHER GAS AND ELECTRIC AND ELECTR APPLIANCES

Questions. EASY TO REAL)

4 COMPLETE - PAY SI A MO.
TO GET THIS ASSISTANCE FOR YOURSELF SIMPLY FILL IN AND MAIL COUPON TODAY.

AUDEL, Publishers, 49 WEST 23rd ST. New York 10, Mail AUDELS HOME APPLIANCE SERVICE GUIDE 1841 for examination. If O.K. I will send you SI in 7 days; then rem monthly until 84 is paid, Otherwise, I will return book prom

Name	-	_	-	-	-	-	_	_	-	_	_	_	_	-	_	_	_	-	-	_	_	-	_	_	_	_	_	_	_	_
Address	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_
Occupation	n	910		_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_		_	_	_	_	_	_	_	_	_	_
Employed	by	<i>.</i> _	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	_	R	N
	_		_		_				_								_		-	-	_		_	_		,		-		

ECTRICAL EDUCATOR TY-EASY AS A. B. C. TRIAL t us mail it to you for tree TRIAL nth if satisfied. Drdertoday! W. 23d St. New York Dept. RN

HERE IS LATE INFORMATION IN A HANDY FORM FOR RADIO AND TELEVISION REPAIRMEN, SERVICEMEN AND STUDENTS





Phonograph Pick-Ups, etc.

IT PAYS TO KNOW!

The Basic Principles—
Construction—Installation—Operation—Repairs—
Trouble Shooting. Shows
How to get Sharp, Clear
T.V. Pictures. Install Aerials—How to Test. Explains
Color Systems, Methods of
Conversion, Terms, etc. Includes Ultra High Frequency (U.H.F.)—Valuable for Quick Ready Reference & Home Study. Tells How to Solve T.V.
& Radio Troubles—Answers Your Questions.

~	2444						
				mation			
	7 D	AY	TEST	-ASK	TO	SEE	ITI
	F	F	IAN	LOR	DE	:R	

AUDEL, Publishers, 49 W. 23 St., N.Y. IO, N.Y. Mail AUDELS T. V. RADIO SERVICE LIBRARY 2 Vols. \$5 on 7 days free trial, if O. K. I will remit \$1 in 7 days and \$1 monthly unit \$6 is paid, Otherwise i will return them.

Name	
Address_	
Occupation	
Employed by	RN

sion with the exception that the maximum high-voltage rating is 18,000 volts.

INSPECTION MIRROR

General Coment Mfg. Co., 919 Taylor Avenue, Rockford, Ill. is now offering another service tool in its already extensive line.

The new item is an illuminated inspection mirror which is similar in appearance to a dentist's oral inspection mirror. It is 121/4" long and enables the technician to inspect the most inaccessible parts of any TV chassis.

No external cords or connections are required as the unit is powered by two penlight cells. From its anodized aluminum case, the battery illuminates a bulb which transmits its light along a 6" transparent Lucite rod to the hinge-mounted mirror on the "business end" of the tool. Shock and shorting are eliminated by the dielectric materials used in the construction.

DUAL-VARIABLE CAPACITOR

McCoy Electronics Company, Mt. Holly Springs, Pa. has developed a new miniature dual variable capacitor for subminiature receivers and transmitters.

Dimensions, exclusive of shaft, are only 13/16" x 11/16" x 1 1/16". Capacitance ranges up to 385 µµfd. per



section with at least 10:1 ratio from maximum to minimum. Both rotors and both stators are isolated for flexibility of circuitry.

Other specifications include: shaft diameter 3/16" or ¼"; standard shaft length, ¾"; weight ½ ounce. Additional details will be supplied by the company on request.

SHIELD CANS

A line of rectangular cans for use as high-voltage shields, transformer cases, capacitor housings, and similar applications on electronic, electrical, TV, radio, and related equipment has been developed by George D. Ellis & Sons Inc., American and Luzerne Streets, Philadelphia 40, Pa.

Twenty-five different sizes of rectangular and square base cans from $2\frac{1}{8}$ " x $1\frac{3}{4}$ " to $7\frac{1}{2}$ " x $7\frac{1}{2}$ " are available and most sizes can be made to any required body height from 2" up to 9". A variety of access openings, with closures, ventilating hole patterns, fastening fixtures, etc. can be provided.

U.H.F. FRINGE ANTENNA

Clear Beam Antenna Corp., 21341 Roscoe Blvd., Canoga Park, California is now offering a new antenna which has been specifically designed for the reception of fringe u.h.f. signals.
The "Duo-Quad UHF Radar"

COMPARE ON A SQUARE



the superior transient response of Jim Lansing Signature extended range speakers

GEN

A combination of tight electrical and rigid mechanical coupling account for the exceptional transient response of Jim Lansing Signature units.

Tight electrical coupling results from high flux density and close voice coil tolerances. Rigid mechanical coupling is achieved by use of a 4" voice coil with a 4" dust dome attached directly to it. Thus, cone area between coil and suspension is kept relatively small; compliance between coil and dome is eliminated.

Structurally, when a 4" voice coil and dome are used with a curvilinear cone, a shallow piston assembly is made possible. This shallow form factor permits a better distribution of highs than would a deep cone.

Remember, only Jim Lansing Signature Speakers are made with 4" voice coils.

James B. Lansing Sound, Inc. manufacturers of precision transducers

> 2439 Fletcher Drive Los Angeles 39, California

*CATHODE RAY TUBE SPECIALS

One Year Guarantee STAN-BURN 21.10 12LP4 24.45 12LP4 18.75 12LP4A 18.75 12LP4A 12.10 12JP4 Q. E. * 108P4A . \$14.9\$
* 108P4A . \$14.9\$
* 10FP4A . 21.10
* 12KP4A . 24.45
* 12QP4A . 81014
* 24.45
* 210P4A . 81014
* 21.00
* 12UP4B . 26.75
* 14CP4 . 81014
* 24.50
* 15CP4 . 81014
* 15CP4 . 30.95
* 15CP4 PO . 30.95
* 15CP4 PO . 31.25
* 15CP4 PO 18.75 12QP4
21.00 12JP4
226.75 12UP4
236.75 15UP4
24.50 15UP4
30.95 18UP4 or
31.25 18JP4 or
31.25 18JP4 or
31.25 16JP4
28.35 16KP4
28.36 16KP4
28.36 16KP4
28.50 17KP4
31.25 16KP4
31.25 16KP4
31.25 16KP4
31.25 16KP4
31.25 16KP4
31.50 19KP4
38.50 19KP4
38.50 19KP4
38.50 19KP4 38.50 19FP4 41.50 19FP4 30.00 19AP4 37.50 19AP4 42.00 20CP4 31.80 21EP4 36.33 21AP4 78.50 24AP4

QUANTITY CRT USERS

We will give you DUD allowances if you ship them
to us Prepaid, 10 CRT's minimum shipment, WRITE,
FOR DETAILS.

AUTHORIZED DISTRIBUTORS for General Electric, Kenrad, Tung-Sol, National Union, De Wald, Regal, Automatic and General Motors.

Automatic Custom-Built Radios for Plymouth, Ford. Chovrolet and many others, always in Stock. We carry a Complete line of HI-FIDELITY and sound equipment. Send us your requests.

We also carry a complete line of popular makes of Radio Tubes at \$0'10 discount. Also many other serical purpose and transmitting types, and all electronic parts and equipment at lowest prices. Send us a list to your requirements for prompt quotations.
Terms: 20% with order, Balance C.O.O. All prices F.O.E., NEW YORK Warehouse. Minimum order \$5.0.S. Write for our latest price list and Mi-Fi catalog to Dept. RN-12. Fparts and equivof your requivof your requivorms: 20%
F.O.E., NEW Write for our Dept. RN-12.

ELECTRONICS CO. 1697 BROADWAY . NEW YORK 19, N.Y.

tenna is composed of a four-stack bowtie cross-polarized dipole fans. For positive ghost rejections a closely spaced all-aluminum reflector screen is utilized.

A double-stacked version is also available for extreme u.h.f. fringe conditions. It is a side-by-side arrangement on a specially designed all-aluminum "H" frame featuring strength and fast assembly.

Printed Wiring TV

(Continued from page 59)

certain that such wiring will become popular in TV receivers. From the service technician's viewpoint, printed wiring techniques are not a particular time saver, nor are repairs greatly facilitated. It is necessary to stock special new parts such as tube sockets, potentiometers, capacitors, etc., made expressly for printed wiring. Locating defects in printed assemblies is not much different from conventional methods except that a more uniform layout is usually used. The major drawback in servicing printed wiring lies in the repair or replacement work for any parts which are mounted on the printed wiring strip. Great care and usually a more time consuming procedure is required to make such repairs without incurring new damage. Although some of the manufacturers feature complete printed assemblies as replacement for defective sections, conventional parts replacement and substitution for suspected components are possible and often economical. -30-


Bandswitching Transmitter

(Continued from page 69)

tuning capacitor. Another shield surrounds the 6146 wiring to isolate it from the oscillator. This shield also supports the low voltage input filter capacitor. Another shield runs between the speech amplifier and the 807's, and also supports the driver transformer.

The bias supply components are attached to the rear chassis lip, as is the filament transformer for the 5R4GY's.

Some information is in order concerning the filament wiring. The low voltage power transformer, T_{ij} , has a filament winding (X-X) which is used to supply the final and modulator tubes V_{3} , V_{4} , V_{11} , and V_{12} as well as furnish 6.3 volts to the back-connected filament transformer used in the bias pack. An additional filament transformer, T_2 , is used to feed the exciter and speech amplifier tubes. Although not indicated on the schematic in the interests of clarity, each side of the filament wiring is bypassed to ground through .005 µfd. ceramic capacitors, connected at each tube socket. The relay control leads are similarly by-passed by $C_{\pi 2}$ and $C_{\pi 3}$ where they leave the chassis. Shielded cable is used for the key and a.c. leads. A bottom plate, preferably made of perforated

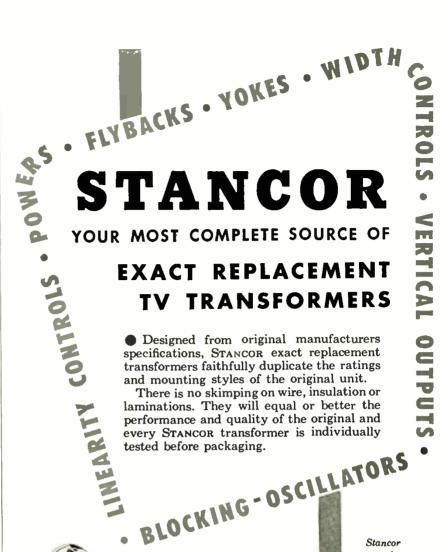

NEW...and typical of STANCOR

exact replacements is the DY-13A Deflection Yoke, exact re-placement for all Muntz 24" and 27" sets. There are no leads to solder—the DY-13A plugs into the set. Bulletin 495 listing models using this yoke is available from your distributor or from STANCOR.

transformers are listed in: Photofact Folders Counterfacts Radio's Master File-O-Matic



CHICAGO STANDARD TRANSFORMER CORPORATION

3584 ELSTON AVENUE . CHICAGO 18, ILLINOIS

EXPORT SALES: Roburn Agencies, Inc., 431 Greenwich Street, New York 13, N. Y.



155 December, 1954



TUBES 60% TO 90% TUBES \$ SPECIAL-OF-THE-MONTH! 12L8-20g ea. 6 for \$1.00

		Same as 164	4 tube.		
2822	.29	39/44	.19	836	
2C26	.09	114B	.19		.99
2C26A	.09	215A	.09	841	
3822	.89	221A	.19	843	.15
3D6	.29	316A	.19	864	.19
6SL7	.49	388A .	.49	1626 7193	.19
7C4	.29	471A . 532A	.99	E1148	3 9 7
12C8	.49	722A	.79	RK34	.79
12L8	.20	826	.29	V R92	.14
15R	.35	832A	5.45	VT127	.09

CHECK THESE GREAT SAVINGS!

lent, used . 3.29 \$4.65s COMPASS LEFT TO RIGHT INDICATOR. 3.29 \$4.65s COMPASS LEFT TO RIGHT INDICATOR. 3.29 \$4.62a 360 degree Selson operated NAVIGATOR'S INDICATOR. part of ARN-7. BRAND NEW. 7.95

HEADSETS

BRAND ...\$4.65



MICROPHONE SUPER-SALE

44 MIKE—magnetic type consisting of Mike Unit McCo. Cord CO-287, Plug FL-179 and Jack JK-20 45 MIKE—Carbon Lip Mike. 45 MIKE—Carbon—BRAND NEW. 5-13 MANOSET—BRAND NEW.

BC-221 Frequency Meter
Real Valuel QUANTITY IS LIMITED

so first come, first served. They
are just like new, with original callbration charts. Range 125-20,000
KC with crystal check points in all
ranges. Complete with \$139.50

Standard with AC power supcrystal and tubes. \$139.50

MODULATED TYPE \$179.50

MODULATED TYPE with AC Power Suphly. \$199.50

KEQ. METERS

These Frequency Meters are factory treated, checked
for frequency alignment and GUARANTEEO.



,	PRICES	SLAS	HED!!			
HS-33 HEADSE	T used				\$1	.49
ENGLISH TYPE,	(L-35.		* * * * *	* * * * *		.10
CR-1A/AR CRYS	TALS-80	38.25	KC. 80	01.436	ic.	
8258 S7KC-8	read New		,			40



rield
Telephones
Army surplus, completely reconditioned and



SAVE! SCR-522 RECEIVERS

less oscillator assembly, frequency shifter and tubes. Contains all Coils, Transformers, Resistors, \$4.95 Condensers and other valuable parts..each \$4.95 SPECIAL! 2 for \$8.00

• • • • • • • • • • • • • • • MINIMUM ORDER \$2.00

nediate delivery—send 25% deposit on C.O.D. rs. If sending full remittance, allow for postage save C.O.D. cherges. All shipments F.O.B., N.Y.C. phouse. (N.Y.C. residents add sales tax.)

PLATT ELECTRONICS CORP. Dept. A, 125 West 17th St., N. Y. 11, N. Y. PHONE: CHelsea 2-1100

sheet metal should be used to completely cover the bottom side of the chassis, as a ventilated TVI shield.

The transmitter was housed in a cabinet originally belonging to an SX-42 receiver, which, with its perforated metal access cover, makes a very neat appearance, and an absolute minimum of TVI. Since the photographs were made, decals have been added to conveniently identify the controls, and add somewhat to the professional appearance of the transmitter.


Coaxial cable should be used to feed to the antenna, and a good ground should be made to the chassis of the rig.

Operation

A few initial checks should be made before operating the rig, to make sure that everything is functioning properly. The low voltage power supply should be checked for approximately 300 volts output, and the bias voltages set to the previously specified values. The operating bias on the 6146's will be about 85 volts when the proper six ma. of grid current flows, with 75 volts of this bias being obtained from the bias supply. Without turning on the high voltage, the exciter should be tuned up using crystal and c.w. operating settings. Only 2 or 3 ma. are obtained at the multiplier grid. The oscillator plate current should never be allowed to exceed 50 ma., but in this unit the current normally only rises to about 40 ma, when the excitation is removed. The multiplier, of course, is cut off, and the final will standby at approximately 50 ma. Should the plate currents at any time be found to be excessive, the tube should be checked for traces of gas. A few ohms added in the oscillator cathode will serve to hold the tube down, should it be necessarv.

The multiplier plate runs from 10 to 30 ma. under normal operating conditions, depending upon the screen excitation control setting. Once the final grid is set up to draw 6 ma., the screen voltage can be set at the reduced voltage condition by means of the tune-up switch, plate voltage applied to the final and its operation checked, under load. The plate voltage will be about 650 volts, and the screen voltage when at full power will run around 150 volts. Incidentally, a 100 watt bulb makes a good dummy load for testing, and its brilliance will be an indication of the r.f. output. The rig should be checked on all bands, and given a test run to check for any indications of overheating, and may then be put into operation. A final cathode current of about 230 ma. has been found to be a satisfactory operating value.

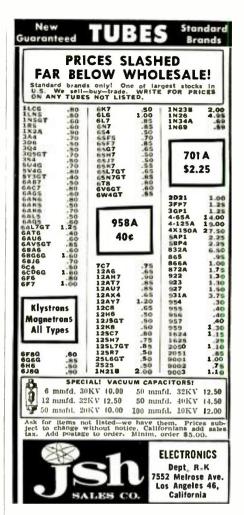Operation and adjustment is primarily a matter of becoming familiar with the various controls and their functions. The setup of the pi-network is conventional. A data sheet #710, available from the E. F. Johnson Company, covers the proper settings and gives other design information. It should





FOR THE LEASTEST . . .

Unlimited thrills from any TV set, new or old. More programs, more variety, more pleasure from a few dollars invested in a Granco converter to tune in those local UHF stations. Install it yourself in a few minutes.



MODEL S L U

ASK YOUR DEALER!

be pointed out that, in this particular construction, it was found advisable to omit the .6 microhenry coil sometimes added in series with the variable inductor, in order to obtain somewhat better C/L ratios, particularly at 28

The rig should be tuned in the c.w. position, and then switched over to AM making sure that the high voltage is off while switching to avoid arcing. In the phone position, the exciter cathode is open until the high voltage switch is closed, which allows a single switch to control the transmitter for send-receive conditions.

When shifting frequency around a band, such as is common with v.f.o. operation, it will be found that only the rotary inductor need be moved slightly to keep the output network tuned, and the exciter tuning capacitors are broad enough to require only slight readjustment when large frequency shifts are made.

Operation is a pleasure, and considerable comment has been made as to the fine quality of the signal on the air. Anyone interested in duplicating the transmitter will be well pleased with the finished unit, besides enjoying the satisfaction of a commercial appearing rig which has been "home made.'

All-Purpose Enclosure

(Continued from page 49)

sound. The self-contained tweeter in the 12TRX is now employed.

Thus, five different combinations of units are available at the turn of a switch. Because the "Fold-a-flex" enclosure may be adjusted for three types of baffling it is possible to hear and to analyze fifteen distinct performance effects.

This may seem unnecessary from a practical sense. It probably is-but such a system has its place in the modest hi-fi showroom for consumer demonstration and does reduce inventory requirements for cabinets of different types. And it permits a convenient means for the study of the behavior of loudspeakers under widely varied conditions.

NATESA ELECTS

AT the meeting following the opening day dinner of the recent 5th national convention and trade show of the National Alliance of Television & Electronic Service Associations (NATESA) held in Chicago, the following officers were elected for 1955:

Frank Moch, national president; Bertram Lewis, treasurer; Ray Neiswonger, secretary general; Fordinand Lynn, vicepres. eastern div.; Milton Klarsfeld, sce'y, eastern div.; Fred Colton, vicepres. cast central div.; Charles Burns, see'y, cast central div.; Vincent Lutz, vice-pres. west central div.; William Briza, see'y, west central div.; Horace Collins, vice-pres, western div.; and Edward Failing, see'y, western div.

December, 1954

For top-notch equipment:

LOOK TO hallicrafters

For top-notch service: LOOK TO



"The World's Most Personalized Radio Supply House"

THE HALLICRAFTER SX-96

WOGFQ

ONLY \$13.62 PER MONTH \$25.00 DOWN 18 Mos. to Pay \$249.95 CASH

R-46A Speaker \$19.95

Selectable side band receiver with improved stability through temperature compensation of the HF oscillator circuits and use of the crystal control second conversion oscillators. Precision gear drive dial system on main tuning and bandspread dials. Includes 50 Kinghly selective IF system, AVC-noise limiter and grey-black cabinet with brushed chrome trim. Ship. wt. 43 lbs

THE HALLICRAFTER S-85



ONLY \$9.54 PER MONTH \$12.00 DOWN 12 Mos. to Pay \$119.95 CASH

The receiver with the 10, 11, 15, 20, 40 and 80 meter amateur bands and separate bandspread tuning condenser. Has tuned RF stage, two IF stages for better selectivity, BFO pitch control, AVC-noise limiter and receive/standby. Sever tubes plus rectifier. Broadcast bands: 510-1680 Kc. Three short wave bands: 1660 Kc-34 Mc. Chrome-trimmed, grey-black steel cabinet. Shipping wt. 36 lbs

OTHER LATE MODEL HALLICRAFTERS

Figure Only 10% Down Model Pay Per Month Cash Price \$ 49.95 S-38D \$ 3.97 S-93 7.95 99.95 SX-99 11.92 149.95 SX-62A 19.07 349.95 HT-30 19.07 349.95 SX-88 32.40 595.00

SEND FOR OUR COMPLETE FREE CATALOG!

and information about

- * 500 watt, band-switching Globe King
- The new, low-cost "Plumber's Delight" beams
- Our 10% down payment plan
- Over 600 items of Reconditioned Egpt



ALL PRICES SUBJECT TO CHANGE WITHOUT NOTICE

Please send me 🗌 New Free Catalog and full information on the items checked below! Quote your top Trade-In offer for my: (Name and Make of Equipment)



☐ \$X-96			nent De Other.			
Globe	King	□ N	ew WRI	В	eams	
□ Down	Payment	Plan	☐ Rec	On	Equip.	List
IAME						
DDRESS						

"SAVE \$\$\$" THOUSANDS OF BARGAINS Send Stamp for our

GIANT CATALOG

UNITED RADIO CO. 58A MARKET ST. NEWARK, N. J.

DIOS PHONOGRAPHS HI-FI

Write for FREE Brochure RADIO KITS, INC. . 120 Cedar St., N. Y. 6

GET INTO ELECTRONICS



You can enter this uncrowded, interesting lie d. Defense expansion, new developments demand trained specialists. Study all phases radio & electronics theory and practice; TV; FM; broaddevelopments demand ly all phases radio & electronies theory and plactice; TV; FM; moat-casting; servicing; avoidton, narine, police (actio, 18-month coutse. Prepare for good pay. Gradi-ates in demand by malor companies. Bigh School or caultalent required, Begin Jan, March, June, Sept. Campus life. Write for catalog.

VALPARAISO TECHNICAL INSTITUTE Dept. RD Valparaiso, Indiana

Perma-Power better merchandise that sells!

TV VOLTAGE REGULATOR



10 Volt Line Adjustor

Normal Line Volts

10 Volts Increase

10 Volts Decrease

300 Watts. Returns full height & width of picture. Eliminates intermittent sync.

made better!



UNIVERSAL TV TUBE

Isolation type transformer gives 6.3 V for cathade — filament short or 7.8 V to increase emission. • It's parallel • It's series • It's isolation • It's electrostatic • It's universal.

better! made

H·B·G **HORIZONTAL BAR GENERATOR**



for quick TV set adjustment and alignment!

- For adjustment of vertical linearity and height controls
 Accurate positioning of focus coil or
- magnet
 Precise setting of yoke
 Complete with instructions

made better!



MODEL "A" BATTERY ELIMINATOR

for 105-125V., 50/60 cycles 95 For 1½ valt radios with 4 to 6 tubes.
Gives nearly constant power from varying line valtages. Universal sockets for all battery plugs.

Available from electronic parts distributors Illustrated literature upon request

manufactured by 4727 N. DAMEN AVE., CHICAGO 25, ILL Manufacturers of electronic equip

EXPORT: Scheel International, 4237 N. Lincoln, Chicago 13

Within the Industry

(Continued from page 30)

The new facilities will be used to house the specifications and drafting department, the machine shop, and stock and supply areas . . . NORTH HILLS ELECTRIC CO., INC. has moved to 203-18 35th Ave. in Bayside 61, N.Y.

ALBERT A. PULLEY, manager, general recording, RCA Victor Records Divi-

sion, Radio Corporation of America, has been elected president of the Audio Engineering Society, succeeding Jerry B. Minter, president of Components Corp. of Denville, N. J.



The new president has been with RCA and its predecessor company since 1920 when he joined the test department of General Electric Company. He was transferred to the radio department, working first on radio transmitters and then on the G-E disc recording system. When RCA assumed these interests in 1930, Mr. Pulley shifted to Camden, N. J.

Col. Richard H. Ranger, president of Rangertone. Inc., was elected executive vice-president of the society. William J. Mahoney, Jr. of Arthur-Sumpson Enterprises, Inc. of Cincinnati was named central vice-president and Richard F. Hastings of Ealy & Hustings, North Hollywood, Cal. was chosen western vice-president.

C. J. LeBel, founder and first president of the society was re-clected secretary for his fourth consecutive term. Ralph A. Schlegel was also renamed treasurer.

OLSON RADIO WAREHOUSE, INC. with headquarters in Akron, Ohio, has opened a new store at 5918 Penn Ave., Pittsburgh, Pa. Leonard D. Berringer has been named manager of the new facility . . . DELCO RADIO DIVISION of Kokomo, Indiana has established a Semi-Conductor Division in conjunction with its Radio Engineering Department. Dr. E. George Roka is in charge of the new department . . . The formation of a Vernistat Division has been announced by THE PERKIN-ELMER CORPORATION of Norwalk, Conn. The new division will manufacture a new type of precision variableratio transformer . . . VIDAIRE ELEC-TRONICS MFG. CO. has been incorporated and will henceforth be known as the VIDAIRE ELECTRONICS MFG. CORP. There are no changes in personnel nor management . . . GENERAL CERAMICS CORPORATION of Keasbey, N.J. has acquired ADVANCED VACUUM PRODUCTS. INCORPORATED of Stamford, Conn. which will be operated as a whollyowned subsidiary . . . Technical writing service for manufacturers of electronic equipment is being offered by a newly formed firm known as SANDS ASSOCIATES with headquarters at 533 E. Micheltorena St., Santa Barbara, California. The new firm is headed by Leo G. Sands who has been associated with such firms as RCA, Philco, Bogue, Bendix and Langevin . . . FEDERAL PACIFIC ELECTRIC COMPANY of Newark, N.J. has acquired the transformer firm of GARDNER ELECTRIC MANUFAC-TURING COMPANY of San Francisco.

JACK E. WILLSON has been appointed audio products manager for National Company, Inc. of

Malden, Mass. A recipient of a Navy Technical Development Award for his development of bomb release equipment, Mr. Willson comes to his new post from the



Collaro Division of Rockbar Corporation. From 1948 to 1952 he served as eastern sales manager for Electro-Voice, Inc.

As head of the division, he will create new markets and build sales for the company's new hi-fi line.

THIRTY-FIRST BOARD of DIRECTORS and Officers RETMA 1954-55



GREATEST TUBE BUYS

Every Tube GUARANTEED 12 Months

BRANDED—BULK PACKED IN ORIGINAL MFR'S NESTED CARTONS OR INDIVIDUALLY BOXED EVERY TUBE METER & CHASSIS TESTED FOR TOP QUALITY

			· · · - · - ·	• • • • • • • • • • • • • • • • • • • •			UALIII	
0A2\$.87	1554						
0A3/		1SA64					125H770	35Z5GT .59
VR75.	.97	1T4		adian affanad ta			12SJ7SS	3635
0A4G	.60	1044	Merchan	ndise offered her	ein is obtained	i from Receiver	125K7GT .49	
0B2	.74	107	° Manufacturer	s' surplus, vari	ous governmen	t agencies and		3735
0B3/		1054	ather surplus	sources. Most of	i Abic manahand	ion is bound now	12SL7GT .49	39-4435
VR90.	.90		orner surplus	SORICES. MOST O	inis merchana	ize iz prana new	12SN7GT .50	4240
* N 50 .	.50	1X25	and the bald	ince is removed	from Govern	ment and other	12507GT .53	4353
0C3/		2A39	' I sauinment W	e unconditionally	auarantee eve	ev tubo vou buv	125R749	45Z340
VR105		2A54		,	gaaraniee eve	iy labe you buy.	12Z3 39	
	.95	2A64					111111111111111111111111111111111111111	46 45
0D3/		2A76						4645
VR150	.85	ı	6AQ7GT .68	6G6G63	6V638		148465	4785
0Z4	.58	2B7 6		6H649	6W4GT41	1 7Z445	14A557	4938
1A4P	.35	2X23		1	6W6GT41	12A649	14A753	50L6GT .61
1A5GT .	.40	2X2A 1.1	4 6AT636	6J5		12A798	14AF759	50X662
		3A44	4 6AU640	6J650	6X439		14B645	
1A7GT .	.45	3A59	0 6AV5GT .79	6J7 49	6X535			50Y6GT .57
1AB5	.38		6AV636	6J8G90	6X870		14B863	5647
1B3GT .	.67	JABGT5	p	6K6GT39	7A445			5753
1C5GT .	.40	3B73			7A555		7 1 2 2 1 1 1 2 2	5856
		3D63		6K7G38	723 135	12AU636		70L7GT 1.00
1C7G	.37	3LF4		6K8G64	7A665		14E665	702701 1.00
1D7GT	.75	304 4		6L6G99	7A765		14E780	
1E7GT	.35		6BA755	6L6GA99	7AD790			71A52
1F4	.40	3Q5GT4		6N795	7AG755		14F765	76
1F5G	.44	3\$4		04753			14F890	77
21.50				60749	7AH755		14H757	78 , .43
1H4G	.40	3V45 5T4 1.2		1 - 4 - 1 - 1 - 1 - 1 - 1	l	12AX755	14N7 67	81 1.10
1H5GT	.38				7B444		147467	1
1J6G	.59	5U4G4		65439	7B555		2010 11 102	8267
1L4	.45			657G55	7B655		l	8267 8377
1L6	.61	5V4G7		6SA7	7C4 55		19	
120	.61	5 Y 3 G			7C765		19BG6G 1.15	1 72 1111 122
	.59	5Z33		65C775	1	12BE645	19T8 75	
1LA4		6A64		65D7GT .38	7E559		22	89Y29
1LA6	.75	6A78		65F5GT .45	7E640	12BH760	25AV4GT .80	
1LB4	.77	I	6BQ6GT .75	6SF7 58	7F764	12C834	1 1	117L7GT 1.17
1LC5	.59	6A86	5	65G7 40	7F890	12F5GT35	25BQ6GT .75	117Z338
1LC6	.75	6AB44		1	7G780	12H645	25L6GT .40	117Z4GT .73
		6AB77		65H760	l	12J5GT39	25W4GT .45	117Z6GT .70
1LD5	.49	6AC5GT .9		6SH7GT .50	7H756		25Z5	205193
1LE3	.75	6AC76	B 6C654	65J7 54	73775	12J7GT57	25Z6GT .40	1031
1LG5	.75	l	6C8G85	65K7	7K780		25200140	
1LH4	.75	6AFS8	•	65L7GT49	7L777			9001 1.47
1LN5	.55	6AF6G7	6 6CB642		7N757		2642	9002
		6AG54	7 6CD6G . 1.05	65N7GT .48	7117 101	1258GT .60	27	9003 1.30
INSGT .	.61	6AG79		65Q749	707	1 -23001 .60	32L7GT .95	9006 67
1PSGT	.56	6AH69		6SR745	7R759		35C5 .37	803 2.95
1Q5GT	.55		6E576	65T7			35L6GT .45	
1R4	.81	6AK55		6T8	75783 7V787			
185	.47	6AK55		0.0	7W785		==	807 1.25
IN3	.4/			6U7G45	/ / · · · · · · · · · · · · · · · · · ·		35W459	814 3.50
154						125F7GT .68	35Y444	836 7.95
134	.55	6AQ63	5 6F8G69	1 6U859	7X657	1 125G770	35Z340	866A 1.45

Minimum Order: \$10.00. Terms: 25% with order balance C.O.D. Please include postage. All prices subject to change without notice. F. O. B. New York City. Mail Order Division:

TRANSAMERICA ELECTRONICS CORP. 115 Liberty Street New York 6, N. Y.

Now brings you a compact Flyback—Yoke—Continuity Tester...in 1 low cost unit



THREE TESTERS IN ONE

for only

- Checks low and high impedance yokes and
- Detects even one shorted turn.
- An improved Continuity Checker: Checks condensers for opens, electrical shorts, or leakage. Ordinary continuity testers will not do this.

TV Component Tester

PERFORMS SIX VITAL **FUNCTIONS**



It's terrific as a

- PICTURE TUBE TESTER
- FLYBACK & YOKE TESTER
- SELENIUM RECTIFIER TESTER
- CONDENSER TESTER
- CONTINUITY TESTER
- PICTURE TUBE REACTIVATOR

30 DAY TRIAL: Try these Transvision TESTERS for 10 days. Then, I you are not 1000g satisfied, you may return them, Your purchase price, less 100g (our cost of handling and repacking) will be promptly refunded.

TRANSVISION, INC. NEW ROCHELLE, N.Y.

TRA	NSVISION, INC., New Rochelle, N. Y. Dept. RN-12
()	Send
()	Enclosed find \$deposit, Balance C.O.D. I accept your 10 Day Trial terms.
Nam	
Addt	ess
City.	State
му.	Jobber is
	JOBBER INQUIRIES INVITED

Vibration Amplifier

(Continued from page 65)

tening to and interpreting vibrational movement in machinery, the transistor vibration amplifier has been found to have another valuable application.

When the point of the probe is moved lightly across a material surface, a sound is produced in which the frequency depends on the number of surface irregularities encountered (and the speed of movement) and in which the amplitude depends on the degrees of surface irregularity.

Used in this fashion, the instrument permits the operator to determine even very small differences in the surface smoothness of various materials.

Best results are obtained when the probe is held at a slight angle, with the apex facing away from the direction of movement. The probe tip should make firm, but light, contact with the surface of the material being checked.

When comparing the surface smoothness of two different materials or objects, special care must be taken to move the probe across each surface at exactly the same speed. Otherwise, the results are somewhat difficult to interpret.

The user will soon discover additional applications for the transistor vibration amplifier as he works with it.

-30-

HISS REDUCTION

By JAMES A. McROBERTS


[16. I shows the partial schematic diagram of a Magnavox ratio detector output circuit which has been modified to remove the high frequency hiss sometimes present in FM detector outputs. A 5 μμfd, ceramic condenser has been added as shown by the dotted lines. The addition of this condenser shunts a large proportion of the radio frequency to ground and eliminates r.f. hiss. condenser serves two other minor purposes

1. Further desemphasizes the audio. 2. Removes 4.5 mc. r.f. which might be passed along to the remainder of the audio system and built up in the audio amplifier, only to re-enter the video and

ouse grain in the picture.

Other makes of sets have been improved by increasing the value of this first condenser from 1 to 5 $\mu\mu$ fd. Some sets rely on the lead dress to furnish the capacity and often simply dressing the lead from the ratio transformer tertiary coil to the chassis will suffice. -30-

Fig. 1. Partial schematic of the ratio detector circuit used in a Magnavox TV.

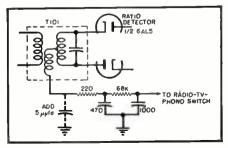

NEW... "Self-Supporting"

Gable Mount

Reduces Installation Costs Increases **Television Sales Eliminates Guy Wires** Speeds Antenna

Installations



Yes, now you can reduce the cost of your installations and home trials more than 75% . . . with MILLS handy "Self-Supporting" Roof Clamp.

NOW ... one man can easily erect a firm-

ly supported antenna from a ladder against the house in just a few minutes.

MILLS Gable Mount eliminates roof damage...often caused by other type installations.

It is sturdily constructed of Cast Aluminum . . . and proved practical and satisfactory . . . on hundreds of homes.

Send for further infor-mation and attractive dealer prices today.

MILLS PRODUCTS CO.

Burr Oak 3, Michigan



TERMINAL'S Sensational

Complete FM-AM Phono Radio System All brand new. Fully guaranteed. Ready to plug to-gether and play. Consisting of famous name com-ponents as follows:

CRAFTSMEN C800A De Luxe FM-AM Tuner Net \$159.50 CRAFTSMEN C500A Ultra Fidelity Amplifier Net \$99.50 GARRARD RC80 3 Speed Record Changer Net \$49.50 Special "45" Spindle Net \$3.50

ELECTRO-VOICE 12 TRXB Triaxial Speaker Net \$59.70

GENERAL ELECTRIC RPX-050 Triple Play Magnetic Pickup

This Complete System NOW at TERMINAL

Tolal regular Net \$379.90

Net \$8.20



Never before such fine Hi-Fi at such low cost See and hear it at our Sound Studios or send for Bulletin RN-12. Write today.



1954 INDEX VOLUMES 51-52

As a service to our readers we are again presenting a complete listing of all feature articles which appeared in RADIO & TELEVI-SION NEWS during 1954. We suggest you keep this for reference.

AMATEUR

ANTENNAS		
The Ground Plane Grows Up (Harrison, W6ULD).	49	Мау
The Inverted Ground Plane (Sem-kow, W71IP)	155	Nov.
3-Bands, 1-Vertical (Harrison, W6ULD)	66	June
CONVERTERS		
(Stanley)The Easy Way		Oct.
MISCELLANEOUS		
Amateur's 4-Tube Miniature Super- het (Popenoe, Jr., W6IWM) A New Slant on TVI (Geiser, W1-	43	Feb.
ZEO)	130	Sept.
A Pioneer Amateur Station (Wat-	32	July
A Subminiature Code Practice Oscillator (Garner, Jr.)		Feb.
LJU)		June
Crystal Substitute (Donald) Junk Box "Sending Iron" (Robber-	47	Mar.
son)	44	Nov.
Provides Emergency Service (Mc-		
Kay, W5LIM)		Oct. Mar.
"Self-completing" Electronic Key (Gallagher, W5HZB)	90	Mar.
The Signal Bouncer (Robberson)		Арг.
TRANSMITTERS		
A "Basket Chassis" Transmitter (So-	40	*
A "Basket Chassis" Transmitter (Sodaro, W6ZRT) A 146 mc. Civil Defense Station (Pustarfi, W2HDQ & Daly, W2-	42	Jan.
YBZ)	35	Apr.
Transmitter (Johnson, W3TRR)		Dec.
Compact 2-Meter Rig (Smith) Completing "Three Tubes on 2 Me-	63	Мау
ters" (Wels. K2AVB)	46	Aug.
QRZ Mobile (Wortman, W2LJU)		Jan. Feb.
The "Globe Scout" (Meyerson, WØGFQ)	54	Dec.
Two-in-the-Hand (Part 1) (Wagner, W6WGD)	31	Aug.
Two-in-the-Hand (Part 2) (Wagner,		
W6WGD)		Sept.
W1DFS)	38	July
AM-FM		
MISCELLANEOUS		

MISCELLANEOUS

High Performance Headphone Ra-

December, 1954



KUEHNE MFG. CO.

TV TOWER DIVISION MATTOON, ILLINOIS

Say Kee Nee

For catalog sheets, see your "Kee Nee" Man ar write direct.



PATENT PENDING

MORE JOBS than graduates

scellent opportunity for p sional growth and advan Demand for our engineering graduates exceeds supply.

Effective placement. Study in this world famed college established 1884. Quarters start Jan., March, June. Sept. Approved for Korean Vets.

Bach, Sci. degree in 27 months


Electronic Engineers

Complete Radio Eng. courses . . TV. UHF and FM. Also Mech., Civil, Elec. Chem. Aero. and Adm. Eng.: Bus. Adm. Acct. Small classes. Well-equipped labs. Modest costs. Prep. courses. Write Jean McCarthy, Director of Admissions for Catalog and Campus View Book.



161

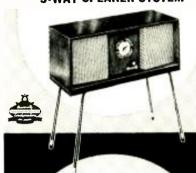The UNIVERSITY Companion HI-FIDELITY **3-WAY SPEAKER SYSTEM**



Here within the confines of a small, versatile enclosure has been engineered a high fidelity 3-way loudspeaker system to enhance the spatial qualities characteristic of true concert hall listening. Exclusive clock feature turns the system on or off remotely or automatically arise or retire with music, record on tape while away.

Every Room ...a Music Room

The Companion is at home in any room ... at one's easy chair, on an end table, within a bookcase, in a functional headboard, in the den, or on wrought iron legs (optional) anywhere in the home.

 $E_{
m xclusive}$ University Diffusicone produces full-bodied bass and mid-range. "Reciprocating Flares" principle of driver-driven tweeter assures wide angle clarity and brilliance over the full range of the highest musical tones. True electrical separation of high, middle and low frequencies with professional inductance/capacitance crossover network. Balance control adjusts performance to your own particular taste.

> ite Desk No. 35 for descriptive literature LOUDSPEAKERS, INC. 80 So. Kensico Ave. White Plains, N.Y.

dio (Gottlieb)		Feb. Dec.
Superregenerative Transistor Receiver (Hughes, W9VHJ) The C900 FM Tuner (Hermann) The FM-Only Tuner (von Reckling-		Mar. Sept.
hausen, Casey & Pomper) The Model FM-80 Tuner		Dec. Nov.
SERVICING		
Auto Radio Service Checkpoints (Ledbetter)		Aug. Mar.
Servicing Midget Receivers (McRoberts)		Sept.
Troubleshooting 3.Way Portables (McRoberts)		July
AUDIO		
AMPLIFIERS		
A Heavy-Duty Audio Amplifier (Krauss)		Aug.
A Low-Powered Phono Amplifier (French)	42	Oct.
A Simple—Yet Good Quality—Preamp (Finlay)	42	Nov.
A 35-Watt "Infinite Feedback" Au-		T 1

A Heavy-Duty Audio Amplifier (Krauss)	48	Aug.
(French)	42	Oct.
A Simple—Yet Good Quality—Pre- amp (Finlay)	42	Nov.
dio Amplifier (Boegli) A Tone-Compensating Preamp	39	July
(Daniel)	56	Oct.
Audio Amplifier-Preamp for Home Use (Cheilik)		Nov. Sept
Simplified Cross-Coupled Amplifier (Boegli)	62	Мау
The "Linear Standard" Amplifier (Knapp) The "Mark 12" (Brociner) The RCA Model SV-1 Preamp (Wort-		May Oct.
man)		Åug. Feb.
MICCELL ENFOLIC		

Acoustic Measurements for the Au-

MISCELLANEOUS

diophile (Fleming)	38	Sept.
A Four-Channel Audio Mixer (Carroll)	57	Nov.
A New Line of Hi-Fi Speakers (Olson & Preston)	69	Feb.
A Transistor Phase Inverter (Caldwell)	71 51	Sept. Āug.
Checking Your Audio System (Konins)	59	May
Choosing Your Hi-Fi Loudspeaker (Cohen)	37 66	Nov. Sept.
Elimination of R.F. Interference in Audio Systems (Part 1) (Coriell).	56	June
Elimination of R.F. Interference in Audio Systems (Part 2) (Coriell). E-V Model 666 (Souther & Burroughs)	44	July
Horns for the P.A. Technician (Co-	63	Mar.
hen)	43	Āpr.
Speakers (Hubelbank) New Mixer-Fader New Multichannel Mixer	56 82 71	Apr. Nov. Oct.
Pages from a Tape Editor's Note- book (Part 3) (Hoefler) Pages from a Tape Editor's Note-	40	Jan.
book (Part 4) (Hoefler) Power Amplifier Output (Sodaro,	50	Feb.
W6ZRT)		Mar. July
Servicing Hi-Fi Amplifiers (Fidelman)	60	Nov.
The "Compleat Fidelity" (Part 3) (Drenner)	44	Jan.
(Chernof)	50	Nov.
Tubes (Hafler)	43	June
	150	0-4



TURNTABLE AND CHAIRSIDE CABINET

Twenty-five pound turntable—3 speeds—no rubber idlers-endless belt drive-professional performance free of rumble and wow -heavy-duty constant speed motor.

NEW: chairside cabinet for turntable provides record storage space in front and adequate ventilation for amplifier in rear.

Unique external mounting arrangement for remote type pre-amps at rear of cabinet. Roll top covers turntable during playing to reduce settling of dust on the delicate rec-

Choice of blonde or mahogany finishes. Users net price for turntable and cabinet \$160.00.

Write for details today

COMPONENTS CORP. DENVILLE, NEW JERSEY

YOU'LL SAVE AT "WHOLESALE"

Subminiature Pocket Tester

Only 3" x 4" x 11/4"



595 Model A1000

Low voltage tester (0-1000 volts) AC, DC, High voltage tester (50kV) Signal tracer, Andro oscillator, Condenser tester, AGC substitution voltage supply, Visual autput meter, Continuity Tester.

Regal HI-FI AM-FM Tuner Built-in 10 W. HI-FI Amplifier



lias full bass control, full tredde control. Ten tubes for high efficiency FM band 88 to 108 me. Huilt in FM \$49.95

SNYDER BROAD BAND YAGIS

- Higher Gain Than Conventional Yagis
- For Fringe Ultra Fringe

High signal level for sharp, bright pictures, insharp, bright pictures, inwith universal U clamps,
ch. 7 thru in-



Write for FREE "FYI" Bulletin No. 201

311 W. Baltimore St. BALTIMORE 1, MD.

RADIO & TELEVISION NEWS

(Taylor, W8NAF)152 Oct.

PHONO How's Your Rumble? (Mitchell) Let's Look at Changers (Sheneman). Reducing Turntable Rumble (Lang,		
	72	Sept.
Players (Burstein)	74	Sept.
	70	Nov.
Mac's Radio Service Shop (Frye) Servicing Tape Recorders (Rockwell) The Broadcast Recorder (Berlant) The New "600"	86 74 43	Jan. Mar. Mar. Dec. Sept.
SPEAKER HOUSINGS All-Purpose Enclosure for 12" Sys-	E 0	h7
tems (Part 1) (Read)		Nov.
tems (Part 2) (Read)	48	
ure (Cohen)		Dec.
The "Diffusicone-8" Enclosure	61	
The DU-201 "Duette"		Mar. Feb.
The Karlson Speaker Enclosure (Karlson)	58	Jan.
TONE CONTROLS A Bass-Boost Control (Ferres)	52	July
A Feedback Loudness Control (Williams)	34	Mar.
An Outboard Bass-Booster (Ferres)	54	May
Simplified Design of Feedback Equalizers (Rose)	54	Sept.
		Apr.
The Curve that Conforms		Apr. July
BOOK REVIEWS		
An Introduction to Radio and Tele- vision (Phillips, Grogan & Ryan)		
Analyzing and Tracing TV Circuits		
(Kiver) Automatic Record Changer Service Manual (Vol. 5) (Sams Staff)1		Dec.
Basic Radio Manual (Sams Staff)1 Beginning Television Production	38	
(White)		July
ceiving Valves (Jager)		Mar.
Staff)	99	Apr. Jan.
(Cook & Carr)		Āpr.
(Fischer & Jacobs)		June
cus)		
Guide to Audio Reproduction (Fidel-		Oct.
man)		Mar.
	82	Nov.
Hi-Fidelity (Trend Staff) High Fidelity Techniques (Newitt)lt Highlights of Color Television	82 86	Nov. Dec. Jan.
High Fidelity Techniques (Newitt) It Highlights of Color Television (Locke, Jr.)	82 86 00 29	Dec. Jan. June
High Fidelity Techniques (Newitt). 11 Highlights of Color Television (Locke, Jr.)	82 86 00 29	Dec. Jan. June Sept.
High Fidelity Techniques (Newitt). It Highlights of Color Television (Locke, Jr.)	82 86 00 29 75	Dec. Jan. June Sept. Oct.
High Fidelity Techniques (Newitt). It Highlights of Color Television (Locke, Jr.)	82 86 00 29 75 69	Dec. Jan. June Sept. Oct. Nov.
High Fidelity Techniques (Newitt). It Highlights of Color Television (Locke, Jr.)	82 86 00 29 75 69 82	Dec. Jan. June Sept. Oct. Nov.

December, 1954



WORTH MORE WHEN YOU BUY THEM ... WORTH MORE WHEN YOU SELL THEM

Because they're designed for better performance on tomorrow's more crowded bands . . . because they're built with heavier components . . . because testing is more rigid . . . new National receivers have always been the biggest values in amateur radio used National receivers have always commanded the biggest re-sale prices. Invest wisely - in a National!



write Dept. RN 1254 for new receiver catalog National Company, Inc., 61 Sherman St., Malden 48, Mass.

RECEIVING

THREE TOP BRANDS ONLY! AT TREMENDOUS SAVINGS OVER REGULAR WHOLESALE

OTHER TUBES AVAILABLE AT SAME LOW, LOW PRICES

Latest Cade Dates • Boxed • Fully RTMA Guaranteed 6AK5 6AL5 6AQ5 6AU6 6AV6 6BA6 12AU7 .85 12BA6 .73 12BE6 .78 12SA7 .80 12SK7 .77 12SQ7 .67 35W4 .49 1.42 1.52 .76 .92 .62 .95 1.06 .63 .48 .80 1.30 6BQ7 1.30 68G7 1.42 12AU,
63 68G7 1.52 128A4
7.6 6C86 .76 128E6
6.67 6J6 .92 12SA7
6.0 6K6 .65 12SK7
.71 6SN7 .85 12SG7
1.98 6V6GT .75 3SW4
1.28 6W4 .70 3SZS
1.42 12AT 1.05 50L6 1 X 2 5 U 4 .78 .80 .77 .67 .49 .51 1.25 6BG6 .83 6BK7 1.40 6BQ6 Send for FREE catalog of additional tubes and parts

Check These BIG BARGAIN Prices Brand New Pix Tubes Full One Year Guarantee

DU MONT AND R.C.A. LICENSED

Dept. R-12
TERMS: 25% Check or Maney Order. Balance C.O.D., F.O.B. New York. Satisfaction Guaranteed or money back in 10 days.

Unique Centralab plan provides 4,000 dual-control combinations

And your Centralab distributor has them IN STOCK



With Centralab's new Fastatch* front and rear units, it's a snap front and rear units, it is a snap to get the right replacement for practically any dual control, current or future (including color TV)! See for yourself:

Snap front unit . . . (with outer shaft cut to length)

To rear unit...

(with blue shaft cut to length)

Snap on switch (from Fastatch KB series)

Add the knobs

-and there's your custom dual



That's all there is to it—sounds easy, doesn't it? It is! no lugs There are no loose parts. to bend .. no tricky assembling. Fastatch front and rear units are completely assembled, tested, and guaranteed by Centralab Ask your Centralab distributor to show you Fastatch Duals, And

send coupon for bulletin 42-218 *Trodemork

Centralab

Tear out coupon and mail today!

A Division of Globe-Union Inc. 910L E. Keefe Avenue, Milwoukee 1, Wisconsin
Send me free bulletin 42-218.
Name
Company
Address.
CityZoneState

I to a last to the Calast TV /V and from any S
Introduction to Color TV (Kaufman &
Thomas)
Most-Often-Needed 1954 Radio Dia-
grams and Servicing Information
(Beitman)169 Oct.
Most-Often-Needed 1954 Television
Servicing Information (Beitman)139 Apr. Most-Often-Needed 1953 Radio Dia-
grams (Beitman)124 Mar.
On The Air (Manyell) 86 May
Practical Television Engineering
(Helt)
Radio Amateur Question & Answer
License Guide (American Elec-
tronics Co.)125 Mar.
Radio Data Charts (Beatty & Sowerby)124 Mar.
Radio Troubleshooting Guidebook
(Rider & Johnson) 88 May
Receiving Tube Substitution Guide-
book (Middleton, H. A.)
Output Systems (Thomas)103 Aug.
Specialized Auto Radio Manual (Vol. 1-A) (Rider Staff)103 Aug.
(Vol. 1-A) (Rider Staff)103 Aug.
Specialized Auto Radio Manual (Vol. 3-A) (Rider Staff)175 Sept.
Specialized Auto Radio Manual
(Vol. 5-A) (Rider Staff)183 Nov.
Specialized Home and Portable
Radio Manual (Rider Staff)131 June Technician's Guide to TV Picture
Tubes (Remer)
Techniques of Television Produc-
tion (Bretz)
Television, A World Survey (UNESCO)
Television Servicing (Buchsbaum) 130 June
Television Servicing Course (Beit-
man)
Television Tube Location Guide
(Sams Staff)
The Electronic Musical Instrument
Manual (Douglas)
The Magic of Electronics (Bukstein)



2-BAY 16-ELEMENT CONICAL ARRAY Adapters Sturdy 3/6" Elements

\$499 IN LOTS OF EACH THREE SINGLE LOTS \$5.30

Single LOTS \$5.30 Ever be to has National Hectronic if BARCAN like the We made special purchase in the tack been made in the been made in the been arrive has mid the arrive has nearly 11.15.

clement array movines ultradimental control (2-law) 18clement array movines ultradimental control (2-law) 18clemental cont



360 Super Directronic

Directronic

ELECTRONICALLY ROTATES
IN ALL DIRECTIONS VMF.
UMF CHANNELS 2-83.
Powerful, 24 element 2 lay
linestronic asterina is cler
through the lifeting area
by 11-ast, as elector switch,
No motors or electricity 1 lay
tremely high gain, COM
FILTE 4-9-SITION
LIBERTHONIC BEAM ELEMENT
TREAX CARLE, INVESTAL
U-CLAMPS, Order model
AX 124, Money back II nos
salisfied.

NEW CATALOG AVAILABLE

ational Electronics HOUSE OF TV VALUES 112 Delco Building Cleveland 3, Ohio

EARN MORE MONEY-A PROFESSIONAL TECHNICIAN

Get down-to-earth practical TV training with WTI experts for the top paying \$5,000-\$10,000 per year jobs.

UHF-COLOR-VHF

SEND FOR

WHF—COLOR—VHF
Master the latest, up-to-the-minute
TV and Color TV developments.

WESTERN TV offers real experience on live equipment in our BIG SHOPS AND LABORATORIES in the shortest practical time under expert instructors. Graduates are in big demand because they have the "field experience" necessary for immediate "bench" or supervisory positions. You learn every phase of Radio and TV servicing (AM, FM, VHF, UHF). WTI men win fast promotion ___ can demand better pay __ develop highly profitable businesses of their own with the latest and most PRACTICAL PERSONALIZED TRAINING BEHIND THEM. YOU concentrate all your time on being a PROFESSIONAL TV SERVICE TECHNICIAN—non-essential math and engineering theory omitted. YOU CAN EARN WHILE YOU LEARN. Special Finance Plan.

APPROVED FOR VETERANS. Find out how you can get into the TOP PAY GROUP—Send for this fact-packed book NOW!

WESTERN TELEVISION INSTITUTE

America's Leading Television Servicing School

1	Western Televisio 341 W. 18th St.,	n Institute, Bept. R-124 Los Angeles 15, Calif.
١	Without obligation booklet. (No sale NAME	n. please send FREE fully illustrated sman will call.)
i	ADDRESS	
I	CITY	ZONE STATE

Radio-TV Service Industry News..106 Nov. Radio-TV Service Industry News..146 Dec.

GENERAL

CIRCUITS (THEORY) Half-Wave Rectifier Circuit (Catal-		
do) Measuring Resistance Between	47	Мау
Tube Elements (Austin)	96	Jan.
MISCELLANEOUS		
A Citizens Band Garage Door Control (Smith, W8VVD)	35	Feb.
A Modern Metal Locator (Turner, K6AI)	35	Sept.
A Photoelectric Contrast Control (Vogelgesang)	89	Oct.
A Phototransisterized Photoelectric Counter (Sokal & Seed)	52	June
A Simple Geiger Counter (Fechter & Boyd)	35	July
High-Speed Photography (Vogel- gesang & Hilmanowski)	36	Aug.
A Transistor Metronome (Garner, Jr.)	50	Jan.
A Transistorized Applause Meter (Garner, Jr.)	82	Mar.
munications System (Kenn & So-kal)	52	Мау
kal)	64	Dec.
"Bootstrap" Interval Timer (Hillman, W6QHK) Certified Record Revue (Whyte) Lectronic Memory (Bukstein) Headphones for Radio and TV (Renné) I Married a TV Technician (Kessler)	58 50 60 62 60 76 116	Apr. May June July Aug. Sept. Oct. Nov. Dec. Dec.
Mac's Radio Service Shop (Frye) Mac's Radio Service Shop (Frye) Mac's Radio Service Shop (Frye) Mac's Radio Service Shop (Frye) Mcre Old Time Operators Report	76 74 74 66	Jan. Apr. May July
(Bowers) "Old Timer" Ormsby (Bowers) Outdoor Soldering (Robberson) Quartz Crystal Etching (Brizendine.	83 118	June Aug. Oct.
W4ATE) Radio Astronomy (Smith) Remote Controls for Marine Radio	38 35	May June
telephones (Robberson). Save That Rectifier (Fath). The Design and Construction of Vacuum-Tube Tesla Ccils (Kaw-		June July
cyn & Marshall)	45 68 66	Jan.
(Dorf) The Theremin (Mocg, K2AMH) The Universal Vibrato (Dorf) Transistorized Moisture Detector	47 37 52	Jan.
(Garner, Jr.)	52	Sept.
ciations	85	Mar.
(Garner, Jr.) Wireless Operators of Old (Bowers) Wireless Ops of Old (Bowers)	90	Mar.
POWER SUPPLIES		
A Transister Power Supply (Garner, Jr.)	74	Nov.
Power Supply for Referming Electro lytics (Amerose)		Oct.

For QUALITY - PERFORMANCE - DEPENDABILITY

Tubes Guaranteed 1 FULL YEAR

Same Day Service

 All Tubes Individually Boxed 300 Types Always in Stock

- 6	4				00.							
1	Туре	Price	Туре	Price	Туре	Price	Type	Price	Түре	Price	- 4 F -	Price
1	OA2	.74	5Y3GT	.37	6CD6	1.11	7AF7	.53	12]5	.42	35L6GT	.51
1	OA4	.68	5Y4	.51	6CF6	.64	7AG7	.69	12 j 7	.49	35W4	.47
ı	OB2	.81	5 Z 3	.45	6CS6	.51	7AH7	.79	12K8	.59	35 Y 4	.54
1	OC3	.72	6A6	.51	6D6	.59	7B4	.44	1207	.59	35Z3	.59
1	OD3	.70	6A7	.69	6E5	.48	7B5	.45	12S8GT	.62	35Z4	.47
1	OZ4M	.65	6AB4	.44	6F5GT	.39	7B6	.69	12SA7GT	.65		.47
1	1A5	.49	6AC5	.69	6F6	.59	7B7	.49	12SC7M	.63	35 Z5GT	.39
1	1A7GT	.47	6AC7M	.86	6G6	.42	7C4 7C5	.59 .69	12SF5 12SG7	.50 .51	36	
١	IAX2	.62	6AF4	.90 .56	6H6GT	.41	7C5 7C6	.59	12S[7M	.67	45	.55
-	1B3GT	.73	6AG5 6AG7M	.99	616	.52	7E5	.59	12SK7GT	.63	45 (Spec.)	
-	1C5 1E7	.43	6AH4	.57	617	.43	7E6	.30	12SL7GT	.57	4525	.49
ı	1G6	.29	6AH6	.73	6K5	.47	7E7	.59	12SN7GT	.52	46	.69
-	1H4	.30	6AJ5	.65	6K6GT	.45	7F7	.79	12SQ7GT	.56	50A5	.55
-	1H5GT	.49	6AK5	.55	6K7	.44	7F8	.79	12SR7M	.49	50B5	.52
-	1L4	.46	6AK6	.59	6L6	.64	7G7	.89	12V6GT	.46	50C5	.51
١	ILA4	.59	6AL5	.42	6L7M	.68	7H7	.59	12X4	.38	50L6GT	.61
-1	1LA6	.69	6AM8	.78	6N7M	.63	717	.79	14A4	.69	50136	.49
	1LB4	.69	6AQ5	.50	6Q7	.45	7K7	.69	14A5	.59		.49
	1LC5	.59	6AQ6	.37	6R7	.69	7L7	.59	14A7 14AF7	.63	5076	
١	iLC6	.79	6AQ7	.70	6S4	.48 .79	7N7 7Q7	.69	14B6	59 . 63	50Y7	.50
ı	ILD5	.59	6AR5	.45	6S7M 6S78	1.90	7R7	.89	14B8	.63	55	.49
	1LE3	.59 .69	6 A S 5 6 A S 6	.50 1.49	6S8GT	.53	787	.79	14C5	.79	56	.49
١	1LG5 1LH4	.69	6AT6	.41	6SA7GT	.55	7V7	.89	14C7	.79	57	.58
	ILN5	.59	6AU4GT	.68	6SD7GT	.41	7 X 6	.54	14E6	.75	58	.60
ı	INSGT	.67	6AU5GT	.82	6SF5GT	.46	7X7	.70	14E7	.88	70L7	.97
	IP5GT	.57	6AU6	.46	6SG7GT	.41	7Y4	.69	14F7	.65	75	.49
	1Q5GT	.58	6AV5GT	.83	6SH7GT	.49	724	.59	14F8	.69	76	.44
- 1	1H5	.62	6AV6	.40	6SJ7GT	.41	12A6	.54	14H7	.59	77	.57
	154	.59	6AX4GT	.65	6SK7GT	.53	12A8GT	.61	14J7 14N7	.30	78	.47
	135	.51	6B4	.54	6SL7GT	.48	12AL5	.37	14N7 14R7	.84	80	.43
	1T4	.58	6BA6	.49	6SN7GT	.59	12AQ5 12AT6	.52	1487	.89	83V	.68
	1T5	.59	6BA7 6BC5	.57 .54	6SR7GT	. 46 .45	12AT7	.72	1437 14W7	.30	84/6Z4	.46
	IU4 1U5	.57 .50	6BD5	.59	6SS7GT	.43	12AU6	.46	14X7	.69		.59
	103 1V	.43	6BD6	.45	6T4	.99	12AU7	.60	14Y7	.62	85	
	1X2A	.63	6BE6	.51	618	.80	12AV6	.39	19BG6	1.39	117L7	.99
	2A3	.30	6BF5	.41	6U5	.57	12AV7	.73	19T8	.69	117P7	.99
	2W3	.38	6BF6	.37	6Ü6	.59	12AX4	.67	19V8	.79	11723	.37
1	2X2	.49	6BG6G	1.25	6U8	.78	12AX7	.63	24A	.39	117Z6	.69
	3A4	.45	6BH6	.53	6V6GT	.50	12AY7	.69	25AV5G1		807	.99
	3B7	.27	6B]6	.49	6W4GT	.47	12AZ7	.59	25BQ6G7 25L6GT		866 A	1.39
	3D6	.27	6BK5	.80	6W6GT	.57	12B4	.60 .49	25W4GT	. 51 .59	1274	.30
	3E5	.46	6BK7	.80	6X4 6X5GT	.37	12BA6 12BA7	.60	25Z5	.66		
	3LF4	.69	6BL7GT	.83 .59	6X8GT	.75	12BD6	.45	25Z6	.49	Hi-Po-567	1.39
ı	3Q4 3Q5GT	.48 .69	6BN6 6BQ6GT	.98	6Y6G	.48	12BE6	.51	26	.45	1619	.27
	354	.58	6BQ7	.90	7A4	.47	12BF6	.39	27	.39	1626	.27
	354 3V4	58	6BZ7	.90	7A5	.59	12BH7	.63	32L7	.89	1629	.27
	5AZ4	59	6C4	.40	7A6	.69	12BY7	.65	35	.58	615	.27
	5T4	.79	6C5	.39	7A7	.69	12BZ7	.65	35 A 5	.58	7193	.27
	5U4G	.55	6C6	.58	7A8	.68	12C8M	.34	35B5	.52		.27
	5W4GT	.50	6CB6	.54	7AD7	.79	12H6	.56	I 35C5	.51	954	.21

TERMS:
196 deposit must accompany
orders—balance C.O.D. All
ments D.B. Evington wareO.ORDERS UNDER \$10—\$1.00
DLING CHARGE . . . Subject

PLEASE:

Send full remittance . . . allow for postage and save C.O.D. charges! We refund all unused money!

Phone: Essex 5-2947 Tubes in bold Type Cover 90% of Demand.

'Integrity Is Our Chief Asset' 115 COIT ST., IRVINGTON II, N. J.

1000 ELECTRONIC **QUESTIONS & ANSWERS"**

By R. J. Fredericks

A new manual containing 1000 interesting problems and puzzles encountered in everyday, practical work. Chapters cover all principal topics, including Test Emitiment, FM, TV, III-FI, Transmitters, Receivers and many others, Ideal bractice for service and lab technicians, anateurs, expetimentes and students. ORDER TODAY!

10-day money back guarantee.

RADIO SOUND PUBLICATIONS Box 38, Utopia Station, Flushing 66, N.Y.

Radio engineering is a big field. There's room for You in it—if you're good. Get first-class training at Indiana Tech. Intensite, specialized course, including strong basis in mathematics and electrical engineering, advanced radio theory and design, telectricin, electronics, Modern laboratories. Low rate. Also B.S. DEGREE IN 27 MONTHS in Aeronautical, Chemical. Civil, Electrical and Mechanical Engineering. G.I. Government approved. Enter December, March, June, September, You can earn part of your expenses right here in Fort Wayne while you are studying.

INDIANA 1	TECH	NICAL	COLLEGE
9124 E Washington	Blvd .	Fort Wayne	2. Indiana

Please send me free information on B.S. Engineering Degree in 27 months as checked.

8	Radio Civil	Televisio	n hanical	Aeronautical Electrical	
2 me					
ddres	s				

TUNG-SOL TECHNICAL DATA PAYS OFF IN SERVICE!



T-58 700 pages-600 tube types



NEW! 1954 Edition! T-70 200 pages of data on CR tubes, receiving and special tubes, dial lamps



T-31 300 blueprint base diagrams for 1100 tube types

Here's the most practical set of tube reference books in the industry—all the information you need for everyday jobs!
They're easy to read—easy to use (always lie flat when open). You'll get work done faster with Tung-Sol Technical Data Books. Askyourtube supplier about them.

TUNG-SOL ELECTRIC INC., Newark 4, N. J. Sales Offices: Atlanta, Chicago, Columbus, Culver City (Los Angeles), Dallas, Denver, Detroit,



Tung-Sol makes All-Glass Sealed Beam Lamps, Miniature Lamps, Signal Flashers, Picture Tubes, Radio, TV and Special Purpose Electron Tubes and Semiconductor Products.

SHORT-WAVE Short-Wave (Boord)	73 76 84 73 70 65 64 90 70 76	Jan. Feb. Mar. Apr. May June July Aug Sept Oct. Nov. Dec.
INDUSTRY		
Aerial "Private Eye" Traces TV Signals From Catswhiskers to Color—An Editorial (Read) Looking Ahead (Schulman) Magnetic Recording 1888 to 1954	31 43	July Mar.
(Wortman)	59	July
(Berliner) Parts Show Exhibitors Radio Servicing in South Africa	157	July May
(Holman) Resistor Trial by Test (Entrekin) Sonic Liquid Level Indicator	. 68	Feb.
(Kielich) The ARTSNY Story The Convair Analogue Computer		
(Horwitz) TV on Mt. Fuji (Kasahara) World's Most Powerful Radio Trans-	120	
TELEVISION	112	ren.
ANTENNAS A New Antenna Coupling System (Harris)	117	Sont
Antenna Antics (Margolis) Home-Built U.H.F. Antennas (Haw-	90	Oct.
kins)		
tions? (Ledbetter)	44	Dec.
Design (Wade)	76	
(Carpenter) The Continuous Evolution in TV Antennas (Noll & Mandl)	41 64	Nov.
The Tri-Pole Antenna (Lo)	104	Feb.
& Kobler)	63	Apr.
MISCELLANEOUS		7
A Video-Magnetic Tape Recorder A U.H.F. Booster (Steidley, W4IYB) Build Your Own TV Color Converter (Part 1) (Stanley)	35	Aug. Dec.
Community TV (Buchsbaum) Fundamentals of Color TV-Color		May
Analysis (Part 1) (Kiver) Fundamentals of Color TV—The	68	Маг.
NTSC System (Part 2) (Kiver) Fundamentals of Color TV—The Tri-	59	Åpr.
Gun Receiver (Part 3) (Kiver) Fundamentals of Color TV—Tri-Gun Receiver Circuits (Part 4) (Kiver)	40	Мау
Fundamentals of Color TV—Chromi-	47	June
nance Circuits (Part 5) (Kiver) Fundamentals of Color TV—The	60	July
Color Signal (Part 6) (Kiver) Fundamentals of Color TV—Color Synchronization (Part 7) (Kiver)		Åug.
Fundamentals of Color TV—Deflec- tion and High Voltage (Part 8) (Kiver)		Sept.

WRITE FOR OUR LATEST CATALOG GENERAL RADIO 783A Output Power Meter Exc. GENERAL RADIO 720 Heterodyne Frequency Meter 10-3000 mc. Exc. GENERAL RADIO 620A Heterodyne Frequency Meter Panel Mounting 33KC-33MC. Exc. 375.00 Mounting 33KC-33MC. Exc. 170A BOONTON Q-Meter 30MC. 200MC Exc. TS.323 UR Frequency Meter 20480MC. Exc. TS-173 UR Frequency Meter with 110VAC. Supply. 90-450 MC. Exc. RT18 ARC1 Transmitter Receiver with Tubes and Dynamotor 100156 MC. 10 Channel Exc. PUR* 350.00 PUR* BC-348 Receivers 200-500KC, 1.5-18MC. 28V.DC. Input ... Exc. 99.50 PUR* PUR* 150.00 129.95 200.00 TS62 AP Echo Box. Exc. IE-19A Test Set 100-155 MC. Exc. GENERAL RADIO 723A 1000 Cycle Vacuum Tube Fork with Power Supply New PE-206 INVERTER New TS33 AP Test Set Frequency Range 8700-9500 MC. for measuring CW. Pulsed Signals on Radar Sets. 200.00 14.95

WANTED! ALL TYPES OF RADIO AND ELECTRONIC SURPLUS

PHOTOCON SALES

417 N. Foothill Blvd.

*PUR-Price Upon Request

SYcamore 2-4131 RYan 1-6751

150.00

Pasadena 8. Calif. RY CABLE: Photocon, Pasadena

PUT THE HIGH



Whether you specialize in high fidelity service, custom building or simply want to build a top-notch outfit for yourself, this big 512-page book will guide you every step of the way. Helps you get better results at less cost. Shows what to do . . . what mistakes to avold. Gives you a full understanding of the many different methods,

a full understanding of the many different methods, circuits. designs. equip-ment. components and other subjects that are de-bated whenever hi-fi fans get together.

Fidelity Techniques

by John H. Newitt

The book that says goodbye to guesswork in choosing, building and servicing hi-fl equipment.

512 pages 203 pictures Price \$7,50

A COMPLETE GUIDE

Written by one of the nation's leading experts, High Fidelity Techniques is complete, authentic and easy to understand. From beginning to end. It is chock full of how-to-do-it tips, service hints, custombuilding ideas and data, charts and diagrams of the most helpful sort.

10-DAY FREE EXAMINATION!

	Dept. RN-124, RINEHART & CO., INC. 232 Madison Ave., New York 16, N, Y.	1
Ī	Send HIGH FIDELITY TECHNIQUES for 10-day FREE EXAMINATION. If I like book. I will then promptly send \$7.50 (plus a few cents post- age) in full payment. Otherwise, I will return book postpaid and owe you nothing:	
	Name	
	Address	
i	City. Zone. State	

RADIO & TELEVISION NEWS

B-Y Demodulation Systems (Part 9) (Kiver) 63 Nov.


Mac's Radio Service Shop (Frye). . 62 Aug. Mac's Radio Service Shop (Frye).. 74 Oct. My Start in TV Servicing (Stanley). 66 Jan.

74 Feb.

Mac's Radio Service Shop (Frye)...

The CBS Patching Bay The Chromatic Color Picture Tube (Buchsbaum) TV Booster for U.H.F. (Lange) TV Cinderella (Lucas, Jr.)	18 1 1 2 2 8 1 1 2 1 2 1 2 1 2 1 2 1 2 1	Mar. feb. Mar. Apr. May June May June May June July Aug June July Aug June July Aug June July Aug Mar Apr May June Aug Mar Apr Moc Aug June July Aug July
TV Stations on the Air TV Test Equipment—How to Choose,	57	Jan.
	48	Mar.
SERVICE NOTES		
An Unusual TV Phase Detector	73	Nov.
(Frieborn)	58	Sept.
(Gary)	59	Āug.
baum) Economy Model TV Sets (Buchs-	52	Feb.
baum)	68	Oct.
Find the Open Filament (Weiss)l Installing a Color Picture Tube		Oct.
(Buchsbaum) Know Your 1954 Admiral TV Re-	46	July
ceivers (Admiral Corp. Service Dept.)	57	Feb.
Know Your 1954 Motorola TV Receivers	45	Jan.
Know Your 1954 Stewart-Warner TV Receivers (Massie)	59	Mar.
1954 TV Receiver Specifications	77 46	Mar. Apr.
1954 TV Receiver Specifications		May
1954 TV Receiver Specifications		June July
1954 TV Receiver Specifications 1954 TV Receiver Specifications	58	Aug.
1954 TV Receiver Specifications		Sept.
1954 TV Receiver Specifications 1954 TV Receiver Specifications	56 56	Nov. Dec.
Positive Grid Circuits in TV Receiv-	62	Feb.
ers (Kiver)	38	
(Buchsbaum)	188	Feb.
Service Hints on Crosley TV Sets Service Hints on Motorola TV Sets		June Jan.
Service Hints on Stewart-Warner		
TV Sets	100	Mar.
cuits (Mandl)	52	Dec.
baum)		Dec.
The Crosley "Super-V" (Youger) Television Troubleshooting Meth-		June
ods (Frieborn)	64 60	Mar. Āug.
Troubleshooting the Turret Tuner (Lowe)	54	Jan.
TVI Troubleshooting (Part 1) (Quirk)		May
TVI Troubleshooting (Part 2) (Quirk)	38	June
TVI Troubleshooting (Part 3) (Quirk)	55	July
TVI Troubleshooting (Part 4) (Quirk) U.H.F. Fringe Installations (Buchs-	36	Āug.
baum)	40	Apr.



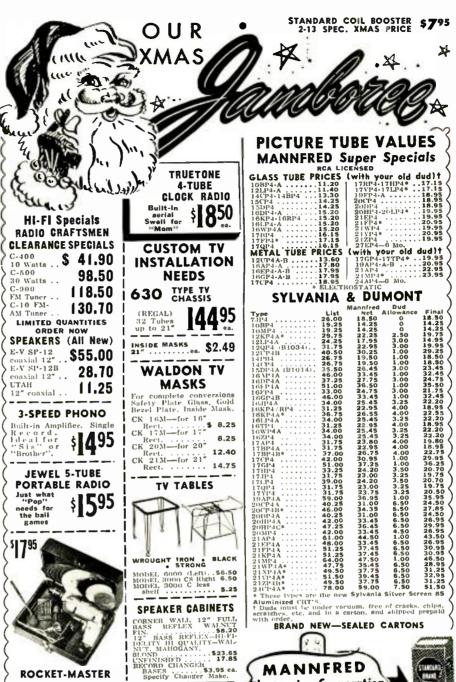

TERMS \$5.00 minimum order. F.O.B. L.I.C., N. Y. 25% Deposit with C.O.D. orders.

Electronics Corporation EXeter 2-6000 21-26 36th Ave., Long Island City 6, N.Y.

SCHEMATICS—CONVERSIONS FOR SURPLUS GEAR

NEW LIST! MANY ADDITIONS! Sand stamped, self addressed anvalope for List C. Add 25c for chart explaining AN nomenclatura.

P. F.

ROX 1220 GOODHEART BEVERLY HILLS, CAL.

Have You Seen POPULAR **ELECTRONICS?** Now on Sale at Your **Favorite Newsdealer**

LEARN CODE TO

It is easy to learn or incresse speed with an instructoffaph Code Teacher. Affords the quickest and most practical method yet developed. For beginners or advanced students. Available tapes from beginner's albhabet to typical messages on all substitutions of the cody processes on all substitutions of the cody of the c

ENDORSED BY THOUSANDS!

The Instructorraph Code Teacher literally takes the place of an operator-instructor and enables anyone to learn and master code without further assistance. Thousands of successful operators have "acquired the code" with the Instructorraph System. Write today for convenient rental and purchase plans.

INSTRUCTOGRAPH COMPANY

4711 SHERIDAN ROAD, CHICAGO 40, ILLINOIS

STANDARD **BRAND TUBES**

"AT THE NEW LOW PRICES"

- Individually boxed.
 Only 1st quality

 Latest Dating
 No private label, electrical or mechanical rejects.
 No rebrands or rewashed "bargains."

AUTHORIZED DISTRIBUTORS
CBS-HYTRON—EIMAC—WESTING-HOUSE AND OTHERS

Tube Orders Over \$25.00, with full remittance, PREPAID to you in U.S.A.

remitte	ince,	PREPAID TO YO	u in 0.3.A.
Type 0Z4 1A5GT 1A7GT 1B3GT	Net	Type Net 6BF585 6BF670 6BG6G1.80	Type Net
OZ4	.50	6BF585 6BF670 6BG6G1.80	7N795
1ASGT	1 00	68C6G 1.80	7R71.30
183GT	.85	I 68M68U I	757 1.25
1 H5GT	.75	6BJ670	777 1.30
114	.85 1.10 1.00	68K5 90	7W71.30
	1.10	68K7A1.10	7X685
11.AG	1.00	GRNG 1 15	794 .70
1LB4	1.00	6806GT 1.20	724
1LC5	1.00	6BQ7A 1.20	12AL570
1LA4 1LA6 1LB4 1LC5 1LD5	1.00	6BX7GT .1.25	12AT650
1LE3	1.00	68Y5G1.30	12417
11 84	1.00	6C4	12AU7
1LN5	.95	6CB670	12AV655
1N5GT	.90	6CD6G1.75	12AV795
1Q5GT	1.15	6CF61.00	12AW6 85
1R4	1.00	6CM61.10	124440165
154	.90	6C5670	12AY71.75
155	.70	6CU61.70	12AZ790
1T4	.70	6E5 1.00	1284 90
ITSGT	1.05	6F5	12BA665
105	65	6F6G80	12BE670
1v	.95	6H650	12BH795
1V2	.70	6.4 4.95	12BY795
1X2B	.85	615	12827 1.00
ILM4 ILM5 INSGT INSGT IR4 IR5 IR5 IS4 IS5 IT4 IT5GT IU4 IU5 IV2 IX2B 2021 IX2B 2021 IX2B 3A4 IX3B IX4 IX4 IX4 IX4 IX5B IX4 IX4 IX5B IX5B IX4 IX5B IX5B IX4 IX5B IX5B IX5B IX5B IX5B IX5B IX5B IX5B	1.00 1.00	681.6 70 681.7 70 681.7 70 681.7 1.15 680.6 1.15 680.6 1.15 680.7 1.12 680.7	7244 70 12AL7 50 12AL7 60 12AL7 60 12AL7 80 12AL
344	.55	6K6GT60	12KHGT 1.10
3A5	.90	6K7M80	12Q7GT80
3LF4	1.15	6K81.20	125A7GT65
304	1.00	61 6CA 1 30	1256790
354	.85	6L6M 1.50	1251770
3V4	.75	6L7G1.25	125K7GT65
5AW4	1.35	6N71.15	125L7GT . 1.00
SHAGT	1.33	607G 80	125N/G180
5V4G	.90	607GT 80	1444 1.00
5W4GT	.70	654 60	14451.50
3V4 5R4GY 5U4G 5V4G 5V4G 5V4G 5X4G 5X4G 5X4G 5X4G 5X4G 6A8G 6A8M 6A84	.80	6581.10	144785
SY3GT	.45	6CS7 75	148670
574G	80	65F575	1458 1 20
524	1.25	65G770	14171.35
6A8M	1.00	65H7 80	14N71.00
6A8GT 6A84 6A87 6AC5GT 6AC7G 6A67G 6AF4 6AF4 6AG5 6AG7	1.05	65K7GT 65	140795
SAR7	1.35	65L7GT80	1457 125
GACSGT .	1.15	65N7GT75	14W71.30
6AC7	1.10	65Q7GT60	198G6G 2.00
GAEA	1 30	6T4 1.30	19T81.20
BAFE	1.20	6TH95	25AV5 . 1.20
GAGS	.75	6U5 90	25L6GT65
6AG7	1.20	608 1.00	25W4GT70
SAMAGT	.85	SVSGT 65	252570
6AJS	1.75	6V6M 1.30	252661
6AF6 6AG7 6AH4GT 6AH4GT 6AJ5 6AK5 6AK5 6AL3 6AL3 6AL3 6AN5	. 75	6W4GT60	358565
6AK6	.80	6W6GT80	35C570
SALT	1.50	6XSGT SO	35L6GT65
SAMB	1.25	6X895	3575GT 45
6AN4	1.50	6Y6G1.00	50A570
6AN4 6AN5 6AN8 6AQ5 6AQ6	3.50	784 80	508570
6405	.70	7A695	35C570
6AQ6	.55	7A780	50L6GT65
6AQ7	1.20	7A8 85	7017 1.55
6AR5	.65	784 80	80 60
6AQ7 6AR5 6AR6 6A56 6A57 6AT6 6AU4GT 6AU5GT 6AV6 GAV5GT	2.50	78670	831.15 117L7GT .2.50 117N7GT .1.95 117P7GT .1.95
6A57G	3.75	787 RO	117L7GT . 2.50 117N7GT . 1.95
6AT6	55	7C4 1.25	117P7GT 1 95
BAUGGE.	95	70580	83 . 1.15 117L7GT 2.50 117N7GT 1.95 117P7GT 1.95 117Z3 . 70 117Z4GT 1.00 117Z6GT 1.00
SAUSGT.	.60	70670	117Z4GT . 1.00
GAVSGT	1.05	7E5 1 10	11726GT . 1.00
GAUSGT. GAVSGT GAVSGT GAX4GT. GAX5GT. GBAG.	1.10 .60 .1.05	7E5 1.10 7E6 1.15 7E7 1.20 7F790 7F8 1.20	
GAX4GT.	80	7E61.15 7E71.20 7F790	1824 3.80
SAXSGT.	65	7F790 7F81.20	1824 3.80 58P1 3.00
CBA5	90	7F81.20	2111.75 8031.90
		7H775	8031.90
6BD5	1.40		866-A1.25 872-A(GE) 2.75
6806	.1.40 .75 .70	7J71.35 7K71.20 7L71.15	16204.50
GBE6	70	7L71.15	16204.50 -ANO OTHERS

3,000 VOLT MULTITESTER C: 0.15, 10.0 750 3000 olds.

C: 0.15, 15 300 750 3000 volts.

D: 0.15, 15 300 750 3000 volts.

D: MA: 0.15, 150, 750 m.

Resistance: 0.10,000, 100,000 ohms.

Complete with battery, test leads. Only 31/2" W x 41/4" H x 13/4" deep. Brand New @ only \$9.95.

SPECIAL-PURPOSE TUBES
Write for our complete listing on XMTG, Industrial,
Special-Purpose and Crystal Biodes. We stock over
2,000 types at excellent prices.

TWO-COLORED TUBE CARTONS, with new Safety Partitions. Prevents Tube Breakage. This Super-Gloss Red and Black Carton is the Most Distinctive Box Available Today Minimum: 100 any one size. Onantity prices on request. Boxes F.O.B., N.Y. N.Y. SIZE (GSN7, GW4, etc.). 5.0125 (ARGE GT. (183, 58Q6GT, etc.). 0125 (ARGE GT. (504G, 68G6G, etc.). 025

Terms: 25% with order, balance C.O.D. All merchandise quaranteed. F.O.B., N.Y.C. PHONE: REctor 2-2562

ELECTRONICS CORP. 136-F LIBERTY ST. N. Y. 6, N. Y.

INDEX dvertisers

DECEMBER 1954

While every precaulion is taken to insure accuracy, we cannot guarantee against the possibility of an occasional change or omission in the preparation of this index.

ADVERTISER Aaron Electronic Sales. 142 Acro Products Company 168 Airex Radio Corp. 169 All Channel Antenna Corp. 12 Allied Radio Corp. 9 American Television & Radio Co. 14 Anproved Electronic Instrument Corp. 115 Arrow Sales Incorporated 127 Ashe Radio Co. Walter 117 Asse Radio Co. Walter 117 And Magnecord, Inc. 116 Magnecord, Inc. 117 Magnecord, Inc. 117 Magnecord, Inc. 117 Magnecord, Inc. 118 Magnecord, Inc. 119 Magnecord, Inc. 119 Maniler View Electronics Maniler View Electronics And Magnecord, Inc. 119 Magnecord, In	th Cover 167 169 148 124, 125 140 160
Aaron Electronic Sales. 142 Acro Products Company 168 Airex Radio Corp. 169 All Channel Antenna Corp. 12 Allied Radio Corp. 9 American Television & Radio Co. 14 Anullifier Corp. of America 116 Approved Electronic Instrument Corp. 115 Arkay Radio Kits 157 Arrow Sales Incorporated 172 Ashe Radio Co. Watter 117 Are Magnecord, Inc. Manllory & Co. Inc., P. R. 4 Mannfred Electronics Corporation. Mannfred Electronics Corporation. Mannfred Electronics Orporation. Mannfred Electronics Orporation. Mannfred Electronics Ma	th Cover 167 169 148 124, 125 140 160
American Television & Radio Co. 14 Amplifier Corp. of America 116 Approved Electronic Instrument Corp. 115 Arkay Radio Kits. 157 Arrow Sales Incorporated 127 Ashe Radio Co. Watter 117 Mosey Electronics Distributing Co., Inc.	124, 125 140 160
	120
Audel Publishers	93
Barry Electronics Corp. 170 National Electronics of Cleveland Bell Telephone Laboratories 26 National Radio Institute Belden 13 National Schools Blonder Tongue Labs. 134 Newcomb	3, 19, 20 23
Boland & Boyce, Inc	97
Cabinart	140
Centralab	158
Cincinnati Ventilating Co., Inc., The	18
Commissioned Electronics Co. 152 Component Corporation 162 Component Corporation 162	92
Concord Radio 155 Corona Radio & TV Co. 145 Coyne School 101 Crescent Industries, Inc. 118	151
DeVry Technical Institute. 5 Delco Radio 21 RCA Institutes. Inc. RCA Institutes. Inc. RCA Cervice Company, Inc.	29, 97
Editors & Engineers. Ltd. 144 Radiart Corp. 153 Radio City Products Company.	6
36, 129, 134 Radio Sound Publications. Electron Tube Wholesalers, Inc. 169 Radio & Television News. Electro-Voice 8 Rad-Tel Tube Co.	165 148 165
Erie Resistor Corporation. 106 Raytheon Manufacturing Co	130
Fair Radio Sales. 141 Rider Publisher, Inc., John F. Finney Company 11 Rinehart & Co., Inc.	136, 166
G. L. Electronics. 107 General Cement Mfg. Co. 93 General Electric .34. 35 General Electric .34. 35	142
General Electronic Dist. Co. 150 Sangamo Electric Company. 97 Sarkes-Tarzian. Inc. 97 Sordbeart, R. E. 167 Sprague Products Co.	96 10 15
Granto	32
Hallicrafters	92 163
Heath Company	139
Hughes Research and Development Labora- tories	116
Instructograph Company 167 International Resistance Co. 3rd Cover International Rectifier Corporation 122 International Rectif	.152, 160 100
JFD Manufacturing Co. Inc	157
Kay-Townes Antenna Company 98, 99 Kedman Company 161 Kuehne Mfg. Co. 161 Walsco Electronics Corporation	120
Kuhn Electronics	153
Leotone Radio Corp. 132 Liberty Electronics, Inc. 136 L. I. Radio Co. 169 Zingo Products	157

Classified Continued from Page 169

FREE: Get our monthly electronic lists. Dlck Rose, Everett, Wash.

TUBES and equipment bought, sold, and exchanged. For action and a fair deal write B. N. Gensler, W2LNI, 136F Liberty, N. Y. 6, N. Y. AN/APR-4, other "APR-," "ARR-," "TS-," "IE-," ARC-1, ARC-3, ART-13, everything surplus; Tubes, Manuals, Laboratory equipment. Describe, price in first letter. Engineering Associates, 431 Patterson Rd., Dayton 9, Ohio.

ciates, 434 Patterson Rd., Dayton 9, Ohio.

FORTY Complete VIIF Radio Terminals. These are designed for telephone service in the 72-76 mc. band, and are ideal for setting up a communication system along a pipeline, railroad, or in mountainous or bush country. Each terminal consists of the following: 1—Link Radio Type 1498F Transmitter; 1—Link Radio Type 1498F Power Supply; 1—Link Radio Type 1498F Receiver; 1—Budelman 200 watt Power Amplifier; 1—Type PP13 Power Supply; 1—Federal Type 101B V-F Ringer; 500 ft. —Type RG 8U Coaxial Cable; 2—Welded steel Yagl Antennas—5 element; 1—Lister Diesel-Generator set, 2KW. P. J. Plishner, 550 Fifth Avenue, New York City.

SPEAKER, New Altec-Lansing 602-4—Econo. 2450

SPEAKER, New Alter-Lausing 602-A. Foran, 3452 Hackett, Milwaukee, Wisconsin.

TELEVISION Receivers, working, \$30 up. Repairable, \$10. W4A11, 1420 South Randolph, Arlingable, \$10. W4A ton 1, Virginia.

TV-FM antennas, All types including UHF, Mounts, Accessories. Lowest prices. Wholesale Supply Co., bept. H., Lunenburg, Mass.

RADIO Diagrams \$1.00, Television \$2.00. Give make, model, Diagram Service, 672-RN, Hartford 1, Conn.

III F1 Bargain Collaro 3-532 Intermix 15 Spindlednal ceramic cartridge-mounting board—\$36.95 Prepaid. Crescent Triomatic-dual cartridge-automatic shut-off—Mounting board \$21.95. Prepaid. Low Prices—Cartridges, timers, etc. Write Today, Fidelity Unlimited, 63-03-39 Ave., Woodside, N. Y.

30-40 MC-AM Crystal Controlled 10 tube receivers 6 volts DC with tubes and one vibrator. Less crystal. Spera 37-10 33 Street, L.1.C., N. Y.

CODE—Practice oscillator kit. Complete with transistor and battery \$14.95 postpaid. Caldwell, Box 685X, 1421 Arch St., Phila. 2, Pa.

CATHODE Ray Tubes, Sylvania 5FP14, New Original Carton. \$5.00 Postpald. Shore Sales Co., Kilgore, Texas.

TELEVISION Sets \$17.95 up. Jones Radlo, 1115 Rambler, Pottstown, Pa.

ALUMINUM Tubing, Angle and Channel Plain and Perforated Sheet. Willard Radcliff, Fostoria, Olio. BIAGRAMS for repairing radios \$1.00. Record-Changers \$1.50. Television \$2.00. Give Make, Model. Diagram Service, 672-RN, Hartford 1, Connecticut.

WANTED

WILL buy 8 each ARC-3—R77 Receivers—\$125.00. T67 Transmitters \$90.00. J68 Power Unit \$75.00 state condition. Purchasing Dept.—Trans-Texas Airways, Houston 17, Texas.

TOP Dollar Pald for ART-13's, dynamotors, parts racks and all other component parts. Write: Har Sales Co., 4109 Burbank Blvd., Burbank, Calif.

WILL Buy All ART-13/type T-47A \$200.00, ART-13/type T-47 \$150.00, BC-788C \$100.00, R5/ARN-7 \$125.00, ARC-3 complete \$250.00, BC-318 modified \$35.00, BC-318 modified \$55.00, ARC-1 Radio \$150.00, BC-312 Receiver \$40.00, BC-312 Receiver \$50.00. Ship Via Express C.O.D. Subject to Inspection To: H. Finnegan, 49 Washington Avenue, Little Ferry, N. J.

WANTED: Type R19/TRC-1 Receivers. Box 543, Radio & Television News.

WANT: Surplus electronic equipment such as ART-13, DY-17, APR-4, APN-9, BC-610, BC-939, BC-348, ARC-1, RTA-1B. Cash or trade for Viking, Ranger, National, Hammarlund, Elmac, Gonset, Hallicrafters, etc. Alltronics, Box 19, Boston 1, Mass., Richmond 2-0048.

RECORDS

25-50% DISCOUNT on guaranteed factory fresh LP records, and pre-recorded tape. Send 20¢ for complete LP catalogue. Record Sales, 4710 Caro-line, Houston 4, Texas.

CORRESPONDENCE COURSES

USED correspondence Courses and Books sold and rented. Money back guarantee. Catalog free. (Courses bought.) Lee Mountain, Pisgah, Ala.

USED Correspondence Courses. Books Bought. Sold, Rented. Educational Exchange, Summerville

BUSINESS OPPORTUNITIES

500 PenniPrints \$5. Sell your idea with Penni-Prints. Your ink drawings, plans, forms, details, layouts, newspaper clippings, testimonials, electrical diagrams, reproduced 8½ x 11. Your photos 8 x 10 prints 2000 for \$20.00. Easily folded for mailing. Free estimates. Pennil'rint Co., Dept. 21, P.O. Box 1159, Chicago 90.

HELP WANTED

TELEVISION Jobs-Names and addresses of companies to contact. \$1.00. Fitzgerald, Dept. A-14, 3038 West Wellington Avenue, Chicago 18, Illinois.

SITUATIONS WANTED

TELEVISION Parts Man, Young, Thoroughly Ex-Perienced Wishes re-horate. Preferably Florida. Box 544, Radio & Television News.

MISCELLANEOUS

BUILD amazing electronic brain which can play game. Details, 25c. Bernard Gott, Apt. 5-D, 213-02 73 Ave., Bayside 61, N. Y.

TEST Equipment repaired and calibrated by Factory staff. All makes. Superior, Simpson, Triplett, Eico. Prompt service. Free estimate. Our nineteenth year. Douglas Instrument Laboratory, 176 Norfolk Avenue, Boston 19, Mass.

TEST Equipment repair—Kit construction. Free Information. Bigelow Electronics, Beulah, Mich.

200 UNMARKED ceramicons. Mixed values \$1.00, Schneider, Box 214, Scaford, N. Y.

Mc's Speaker Reconing. Low prices. 506 N. Ward Street, Benton, Illinois.

ALL makes speakers repaired. Amprite Speaker Service, 70 Vesey St., New York City 7.

RADIO-TV Repair, Colorado. Small shop grossing enough to pay out in five months. Free pictures C-4174 Continental, 804 Grand, Kansas City, Mo.



FAIRCHILD 240

Balanced-Bar PREAMPLIFIER

Now from Fairchild, world famous for professional studio equipment, comes an outstanding development for home music systems

The new Fairchild 240 is the result of extensive engineering research and an elaborate Series of listening tests designed to discover and overcome weaknesses in exist-

ing preamplifiers.
These theoretical and engineering studies have brought

into reality this great new idea in high fidelity amplification-THE NEW FAIRCHILD 240 BALANCED-BAR PREAMPLIFIER!

Combining matchless external beauty with a new easyto-service interior design, the 240 features amazing simplicity and flexibility of control. Operation is so simple it seems instinctive! Yet all conventional controls are included plus many exclusive with the 240

BALANCED-BAR CONTROL—this great Fairchild innovation allows you to match tonal balance between your high fidelity system and the acoustical properties of your own listening room . . . automatically!

LISTENING LEVEL CONTROL—provides the most pleasant low-level listening you ever heard! Plus correct balance at normal listening levels—all achieved without complex adjustments or loss of control by operator. And the amazing LLC operates independently of volume control!

HIGHEST GAIN—LOWEST NOISE—achieved by modifying famous radar and TV cascode input circuit to audio amplification and by careful design, using highest quality components. Note these exciting features!

See the wonderful Fairchild Balanced Bar Preamplifier today!

single knob selects channel or equalization An extraordinary achievement in performance, cabinet design volume control — unaffected by tone and operating simplicity! Better audio dealers everywhere are

proudly presenting the 240 . . . the greatest preamplifier ever produced ... at only \$9850

"studio-type" wiring and layout

1 no ringing at any level

optimum input impedance for all cartridges

complementary taper dual volume control eliminates need for more than one phono input

20 db additional gain easily available for high level input channels if needed

2 output unaffected by load power factor



3_exceptional stability include: 4. exclusive fool-proof balance adjustment

CHILD RECORDING. BTH AVENUE & 154TH STREET, WHITESTONE, N. Y.

December, 1954



SPEEDWAY 1/4" ELECTRIC DRILL JACOBS GEARED CHUCK MODEL 200J

HI-TORQUE (Powerful) UL Appvd, 2400RPM 115 Volt AC DC motor, Geared Chuck & Key, With 9 Drills in case, 1425 (RM) 1534-25 1637 AC DC Motor w 9 drill-&case, \$29.95 MAND-\$AW Finest Swedish Steel, Sandylk Grade, Cross Cut \$10.95 Rev. \$20.95 Cross Cut \$10.95 Reg....\$3.95





NEW "LENK" 180 Watt Perfect Balance SOLDERING GUN

other soldering run offers all these fea-es at any price. 115VAC 180 Watt. light ight 28 ozs., switch 180 deg. Korodless b. Heavy Duty Transformer, Positive Trig-

asy action. \$7.45 NEW FAMOUS MAKE GUNS GTD 4 soldering gun 135W. \$7.89 5 soldering gun 250W. 8.77 4 dual heat 100-150W. 9.65 5 dual heat 200-275W. 10.53

FILAMENT TRANS.
2.5VCT/10A 12.5KVINS. \$5.50; 3 for \$14
2.5VCT/10A 5KVINS. \$5.50; 3 for \$14
2.5VCT/10A 5KVINS. \$5.50; 3 for \$1.75
2.5VCT 12A 15 KVINS 10.95; 2 for \$1.75
24V 1.25A CSD. \$1.98; 2 for \$3.49
2.5V/2A Sel Rect Xfmr. \$4.98; 2/\$8
PRI 110 6 220V Sec 10.6V/1.27A, 12.4
VCT/3.5A \$4.98; 2/\$5.00



5BPI C'RAY TUBE...EA. Lots Sold Singly\$2.25

NEWLY IMPORTED AC-DC VOM MODEL TS-52 MULTITESTER

\$6.49 Ea. Lots of 3 Sold Singly \$6,89 (+40c Ea. Shipping U.S.A. Only)

the tal. Shipping U.S.A. Only) heet. VOH. Deserted, Precision sistors, Jeweled deroamp meter scales for easy surface readings, vivid Red & Black california attom. This is an exceptional baw for the properties of the source of

METER SALE

5MA Tuning Meter 2", 51.29
0-1MADC 11½ RND) MR45WOOLDCMA \$8.33 Reg., 53.95
0-100MADC 1183 RND MR450-100MADC 1183 RND MR450-100MADC 1142 RND MR450-100MADC 1142 RND MR45W ... 53.95
0-800VDC Weston 301/31½ " 80 1000MADC 1142" RND MR45W ... 58.95
1-1500VDC Weston 301/312 Ros 58.95
1-1500VDC U142" RND/\$12.05 Ros 58.95 | C/112" IND MINDSW. \$3.95 | Weston 301/313" \$Q 1000R-25.00 List \$8.95 | C114" RNI/\$12.95 Reg. \$5.95 | Westinghouse 3" \$Q \$4.95 | ADC_will-Shunt; "AN" \$4.98 | GTD, OIL CONDENSER





CIRCUIT BREAKERS



SENSATIONAL Slim . Jim Hi . Gain DYNAMIC MIKE

DYNAMIC MIKE

& TILT STANO

Hand, chest or table
use. Compact width
only 7 ozs. Wick Head
only 8 ozs. Wick Head
ozs. Wick

Postpaid U. S. A. Only..., Lots of 3 Sold Singly. Ea. \$3.98 Mobile Clamp....25¢

SELSYNS—SYNCHROS	
AY1/Autosyn 26V/400Cy/E.P	\$3.98
AYS Autosyn/26V/400Cy E.P.	53.96
CK-2 Low-In-Servo Motor E.P.	\$20.00
AY20 Autosyn/26V/400Cy E.P	54.98
C44968 Sync Rptr 115V/60Cy	\$16.00
C56701 Syn Rptr 115V 60Cy	521 00
C56776 Syn Rptr/115V/60Cy	\$15.00
C56776 Syn Rptr/1134/ducy	521.00
C69406-1 Syn Rptr/115V 60Cy	. 321,00
C78166 Voltage Rcvr/115V/60Cy C78248 Syn Trans/115V/60Cy \$16	, 340,50
C78248 Syn Trans/115V/60Cy 310	5; 2 928
C78249/Syn Diff/115V 60Cy 57	2 312
C78386 Sync Transf 115V 60Cy	. 529.50
C78670/Sync Special, SOV SOCy	. \$21.00
2J1F1 Syn Gn/115/57.5V/400Cy.\$5	; 2 518
2J1F3 Sync Gen 115 57.5V/400Cy	\$9.00
211G1/Svn Tr 57.5 57.5V/400Cy.\$6	5: 2 5 11
2J5HA1 Gen/115/105V 60Cy	. \$57-00
2JD5HA1 Syn Mtr 11\$ 105V/60Cy	. \$57.00
1CT/Sync Trnsf 90/55V 60Cy	. \$59.00
SCT MK111 MOD2, 90 55V 60Cy .	.543.00
5F MK4 MOD IV 115V 60Cy	\$43.00
5G MK1 MOD6 115 90V-60Cy	\$45.00
5G5pecial KS5950/115V 90V-400Cy	527
6G Svn Gen/MK2/MOD 1V/115V/60	540

BROW-LITE

BROW-LITE
A must for Radio-TV
Service. Throws light
where you want 2
work, Worn with or
work, Worn with or
without glasses. Powerful focused 25 ft.
beam. Adjustable angle up & down. With
batterlos. Postpaid tribs item only U.S.A.
\$\$\frac{1}{2}\text{ for \$320.00.}\$

TUBES

OA2 VR75 10.4 3D22 10.4 3D23 10.4 3D

NEW "TABTRON" SELENIUM RECTIFIERS ENGINEERED FOR INDUSTRIAL USE

e manufacture power rectifiers to your specifications. Con-et "TAB" for first delivery on any rating, from one amp up-and above 1000 amps, convection or fan cooled. Single 3-phase to your spec's. NEW LOWER PRICES,

NE	N RECT	TIFIER &	TRANS	SFORME	R 1	NEW RI	CTIFIER	CHOK	S
100	56.00	99.50	Q	324.00	390.75	795.85	39.95	359,90	719.95
50	29,75	54.50	Q	175.00	195.75	405.85	23.95	179.90	359.95
30 36	22.50	42.50	88.00	135.00	165.75	295.85	14,95	134.90	269.95
30	18.00	34.50	72.00	110.00	128.75	235.85	ğ"	117.90	225.95
24	14.50	29.00	58.00	81.50	94.75	190.85	9.95	89.90	159.95
20	12.00	23.00	49.00	72.00	82.75	168.85	7.95	50.90	97.95
12	7.50	14.50	30.00	44.50	54.75	99.85	5.95	41.90	81.95
10	5.95	11.50	25.00	41.50	44.75	84.85	4.75	36.90	71.95
6	4.10	8.00	17.50	29.95	34.75	54.85	3.25	20.90	39.95
4	3.50	6.50	14.50	22.00	26.75	38.85	2.95	18.90	36.95
2	2.00	2.75	6.00	9.25	15.75	28.85	, g	15.90	30.95
	5 1.35	\$ 2.35	5 4.60	\$ 7.50	\$12.75	522.25	5 2.10	\$14.90	\$28,95
	14VDC	28VDC	56VDC	100VDC	118VDC	217VDC	12VDC	150V DC	300V DC
Max	18VAC*	36VAC*	72VAC*	130VAC*	144VAC*	266VAC*	30VAC	120VAC	240VAC
mH	Wave Br	idge.°					C. T.	2 04/	ASE BRG.

NEW HIGH
CURRENT PWR
SUPPLIES GTD*

CURRENT PWR SUPPLIES GTD Variable 0-28VDC. Completely Built. Ready to Go. Fall Wave Scientum. Variace. Volt. & Antp. Meters. Switch, Terminals & Fuse. In Bry Bry. Steel Cabinet. Standard 115V 60 cyclingut. 22liv to order. * One Year Change Number 128V64 0-28VDC at 24 Amp. 89.00 T28V504 0-28VDC at 12 Amp. 89.00 T28V504 0-28VDC at 12 Amp. 129.50 T28V504 0-28VDC at 10 Amp. 129.50 T28V504 0-28VDC at 10 Amp. 39.50 T28V504 0-28VDC at 50 Amp. 39.50 T28V504 0-28VDC

NEW RECTIFIER XFMRS
Primary 115V 60 Cyc
Sec 18-15-9-0-9-15-18V
(36-30-18VCT Common Ct)
4 Amp \$ 8.65; 2 \$15.75
24 Amp* \$ 535.75; 2 \$69.95
00 Amp* \$ 559.00; 2 \$112
lind Amp* \$ 59.00; 2 \$12
lind Amp* \$ 108.00; 2 \$210
18 Volt only 2 Amps \$ 108.00; 2 \$320

*DUAL PRIMARY 115 & 230 VOLT.



ş ., ç

CH07/4 Amp/.07HY/.0RES/10±...\$7.95 CH01/12 Amp/.01HY/.1RES/12±..14.95 CH004/24 Amp/.004HY/.025R/20±.29.95

NEW BATTERY CHARGER RECTIFIER

866A KiT and XFORMER
(2) 866A Tubes 4 Sockets, Transformer Rated: Pri 115V 60 evc Sec. 2.5VCT/10 Amp Hi-Voit 7.5VV Insulation ...,34.98

8476.98 Reg. Spec. Write for Hi-Fi Gram.



PRECISION LABORATORY POTENTIOMETER

Wire wound 20,000 ohm 234 "
Diameter/4" shaft special 5.5° / 10 Thrn. \$7,98 HELIPOT 1000-ohm/0.5° / 10 Thrn. \$7,98 MICROPOT 20,000-ohm/0.1° / 10TT. \$7,98 HELIPOT 50,000-ohm/0.5° / 10TT. \$7,98 HELIPOT 50,000-ohm/0.5° / 10TT. \$7,98 HELIPOT 50,000-ohm/0.5° / 10TT. \$7,98

OIL CONDENSERS


OIL CONDENSERS

NEW WAREHOUSE LIST
.00025MFD 23KV . \$4; 2 \$7
.0016MFD 15K . . \$7; 2 \$2 \$2
.5MFD 6007 . 25e; 6 for \$1
.5MFD/1500V . 85e; 3 for \$2
.5MFD 600V . . 30c; 3 for \$1
.5MFD/600V . . 35e; 3 for \$2
.5MFD/300V . . \$7.98; 2 for \$1
.5MFD/600V . . \$7
.5

.69 3574 .89 3574 .66 41 .58 452 .58 452 .58 452 .68 5085 .98 5085 THAT'S " THAT'S • BUY AUY NEW YORK 6, N. Y., U. S. A. 111 LIBERTY STREET DEPT, 12-RN

PRINTED IN U.S.A.

13.97 | 69Q7GT | 14.90 | 65R7 | 14.90 | 14.90 | 14.90 | 14.90 |

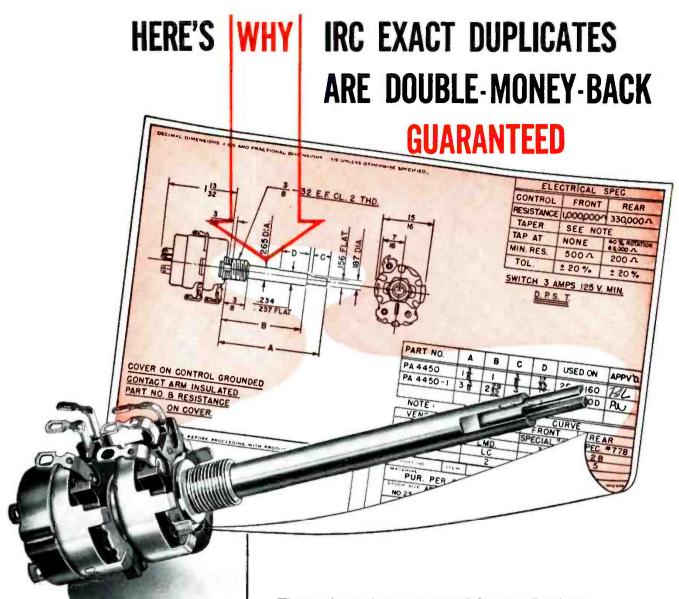

ONLY IRC GUARANTEES

SATISFACTORY MECHANICAL FIT

AND ELECTRICAL OPERATION

OR DOUBLE-YOUR-MONEY-BACK

The typical manufacturer's specifications shown here are exactly duplicated by IRC QJ-180 control. CONCENTRIKIT assembly includes P1-229 and R1-312 shafts with B11-137 and B18-132X Base Elements, and 76-2 Switch.



The mechanical accuracy of IRC Exact Duplicate Controls or universal CONCENTRIKIT equivalents is based on set manufacturers' procurement prints. Specifications on those prints are closely followed.

Shaft lengths are *never less* than the set manufacturer's nominal length—never more than $\frac{3}{2}$ " longer.

Shaft ends are precisely tooled for solid fit.

Inner shaft protrusion is accurately duplicated for perfect knob fit.


Alterations are never needed.

For Exact Duplicate Controls, specify IRC. Most Service Technicians do.

INTERNATIONAL RESISTANCE CO.

415 N. Broad Street, Philadelphia 8, Pa.

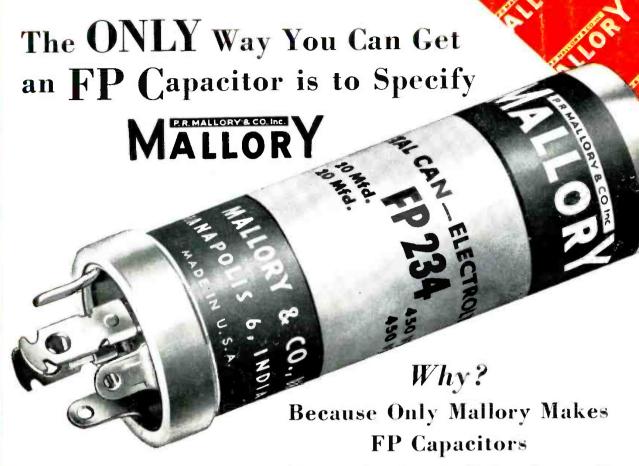In Canada: International Resistance Co., Ltd., Toronto, Licensee



They were introduced by Mallory. For over 15 years they have set the standard of quality and performance in the industry. And they are available only from Mallory.

Imitations are available, of course, but they aren't FP's... and they won't have this combination of features that are exclusively Mallory—

- 85°C construction
- Ability to handle high ripple currents
- Well suited for voltage doubler circuits
- Ideal for use with selenium rectifiers
- Genuine fabricated plate anode
- Corrosive impurities held to less than 7 parts in 10 million
- Long shelf life
- Long service life
- Fast, twist prong mounting
- Standardized can size

MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
RECTIFIERS • POWER SUPPLIES • CONVERTERS • MERCURY BATTERIES

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

Mww.americania/lighistory.co.

When you ask for

FP Capacitors...

be sure you get

Mallory, not an

imitation.