

ELECTRONIC TECHNICIAN / DEALER

WORLD'S LARGEST TV-RADIO SERVICE & SALES CIRCULATION

MAY 1969  A HARPER & BROTHERS PUBLICATION

FRISFWM10R12392N869AD3A17966B
WILLIAM W FRISSE
7176 GALE RD
ATLAS MI
48411



SIGNAL STRENGTH METERS

COLOR SYSTEM TROUBLESHOOTING

SOLID STATE CURVE TRACER

The Seven-Year Itch.

Remember when we introduced you to our Television Analyst (model 1076)? That was over seven years ago, and she's still the only diagnostic tool of her kind. But now there's a new number. A smart looking, professional model (1077) with designs on your heart.

Sure your old model still works. Why not? It was made by B&K.

But, of course, she can't do some of the groovy things the new model can do. Like testing TV sets with UHF. And testing transistorized TV sets with complete safety by matching the impedances of transistorized circuitry.

The 1077 analyzes every stage in color and black-and-white TV sets—without external scopes or wave-form interpretation. And

she does it with a standard test pattern (or special pattern slide transparencies for color circuitry), all of which we supply. She does it all: from antenna input terminals to the grid of the picture tube, using the unique B&K signal substitution technique.

When you do get together with our Television Analyst, she'll eliminate those hours you wasted on tough dogs, intermittents and general TV troubleshooting. (Hours for which you often don't charge the customer.)

Here are some more of her good points: VHF and all UHF RF channels; IF; video; sync; chroma;

audio; bias supply; AGC keying pulse; and signals for complete analyzing of sweep circuitry, including flyback yoke test, and horizontal and vertical driving signals.

Got the itch? Contact your distributor for complete details on how to start a new life with a Television Analyst. Or write for Bulletin 1077.

Model 1077. Net \$379.95



A Division of DYNASCAN CORPORATION
1801 W. Belle Plaine • Chicago, Illinois 60613
Where electronic innovation is a way of life.

B&K
puts an end
to test equipment.
We've developed
Silent Partners.



... for more details circle 106 on postcard

COMPLETE MANUFACTURER'S CIRCUIT DIAGRAMS
AND TECHNICAL INFORMATION FOR 6 NEW SETS

GROUP
201

SCHEMATIC NO.

SCHEMATIC NO.

AIRLINE1223
TV Model GHJ-14549A


PHILCO-FORD1226
TV Chassis 19P22

MAGNAVOX1224
Color TV Chassis T933

TRUETONE1227
TV Model 3912

MOTOROLA1225
Color TV Chassis TS924B,C


ZENITH1228
TV Chassis 13Z12, 13Z12S

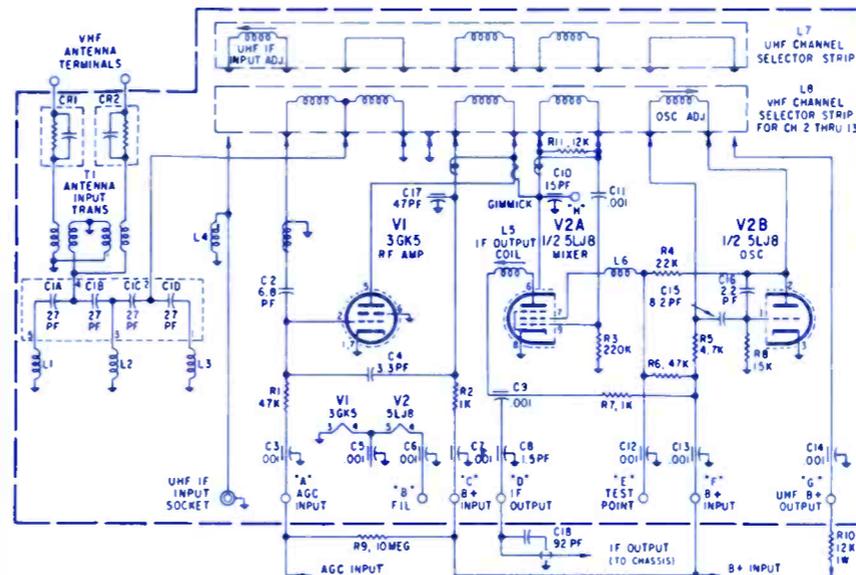

NOTES:
1. ALL RESISTORS ARE 1/2 WATT, UNLESS OTHERWISE NOTED.
2. CAPACITOR VALUES ARE IN MFD, UNLESS OTHERWISE NOTED.
3. TUNER IS SHOWN IN VHF CHANNEL POSITION.


VHF Tuner Schematic Diagram

ELECTRONIC TECHNICIAN/DEALER is published monthly by Harbrace Publications, Inc., Harbrace Building, Duluth, Minnesota 55802, a subsidiary of Harcourt, Brace & World, Inc. Subscription rates: One year \$5, two years \$8, three years \$10, in the United States and Canada. Other countries: One year \$9, two years \$14, three years \$18. Single copies 60¢. Second class postage paid at Dansville, New York and at additional mailing offices. Copyright 1969 by Harbrace Publications, Inc. POSTMASTER: Send Form 3579 to ELECTRONIC TECHNICIAN/DEALER, Harbrace Building, Duluth, Minnesota 55802.



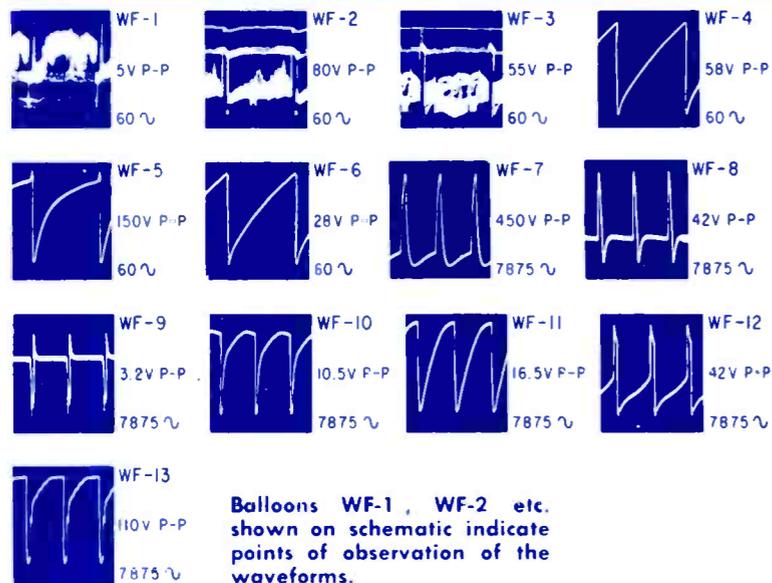





Balloons WF-1, WF-2 etc. shown on schematic indicate points of observation of the waveforms.

SYMBOL	DESCRIPTION	AIRLINE PART NO.
C20A,B,C,D	40-200-250-10µf 200v elec	034-018800
C106	330pf 500v 5% mica	045-007200
C115	15pf 4KV 10% disc cer	825-150016
R11	12512 4w 10%	054-059500
R13	3.60012 5w 10% WW	053-362510
R164	4.512 10w 10%	053-458110
R174	9.612 thermistor	057-056500
R26A,B	contr, 100012 (A), vol, 500K	
	(B) w/on-off switch	055-051600
R27A,B	bright 5M (A), vert hold, 1.5M (B)	055-051700
R69	vert lin 5M	055-035000
R71	height 5M	055-035100
R111	horiz freq adj 50K	055-041700
R123	horiz hold 75K	055-032000
SR20	diode sel AFC det	033-002000
SR27	rectifier silicon 1.0a 900PIV	064-003500
AT83	x-former audio output	031-008301
FC23A	filter choke	032-002301
L126A	coil video peak	111-012600
L127A	coil video peak	111-012700
L128A	coil peak	111-012800
L202	coil horiz freq	110-020200
L203	x-former sound take-off & 4.5MHz trap	109-020300
L204	x-former if output & video det	109-020400
L206A	coil sound quad	109-020601
L208	x-former if interstage	109-020800
L262	def yoke	027-026200
L267	coil choke 2 used	111-026700
L388	coil line filter	111-038800
TR78B	x-former vert output	033-007802
TR94	x-former horiz output chassis brid assy	033-009400
F19	circ brkr 1.75a	073-041100
CC206	couplate sync take-off tuner, VHF	099-001900
	tuner, VHF	134-020600
	tuner, VHF	066-017300
		006-020500

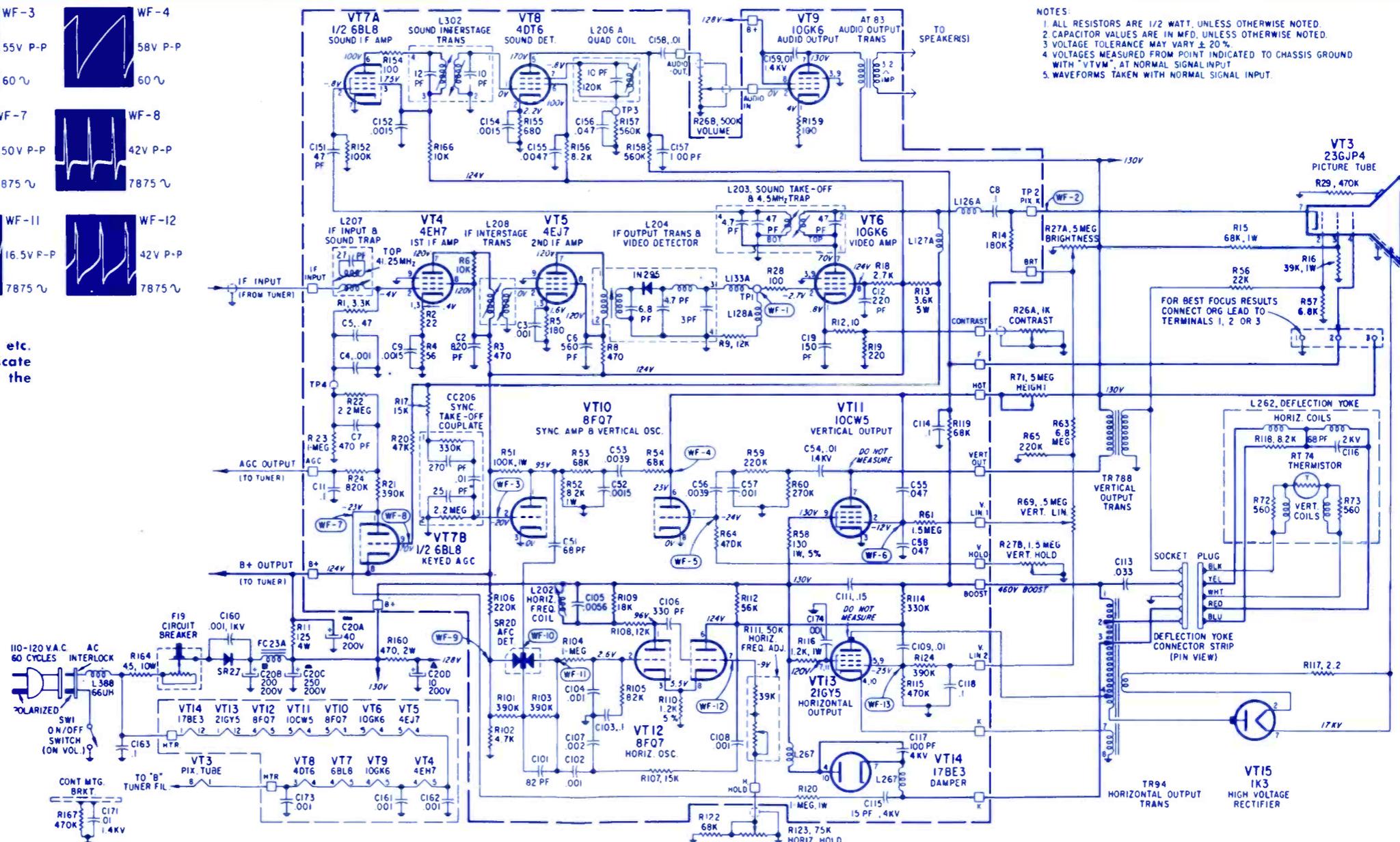

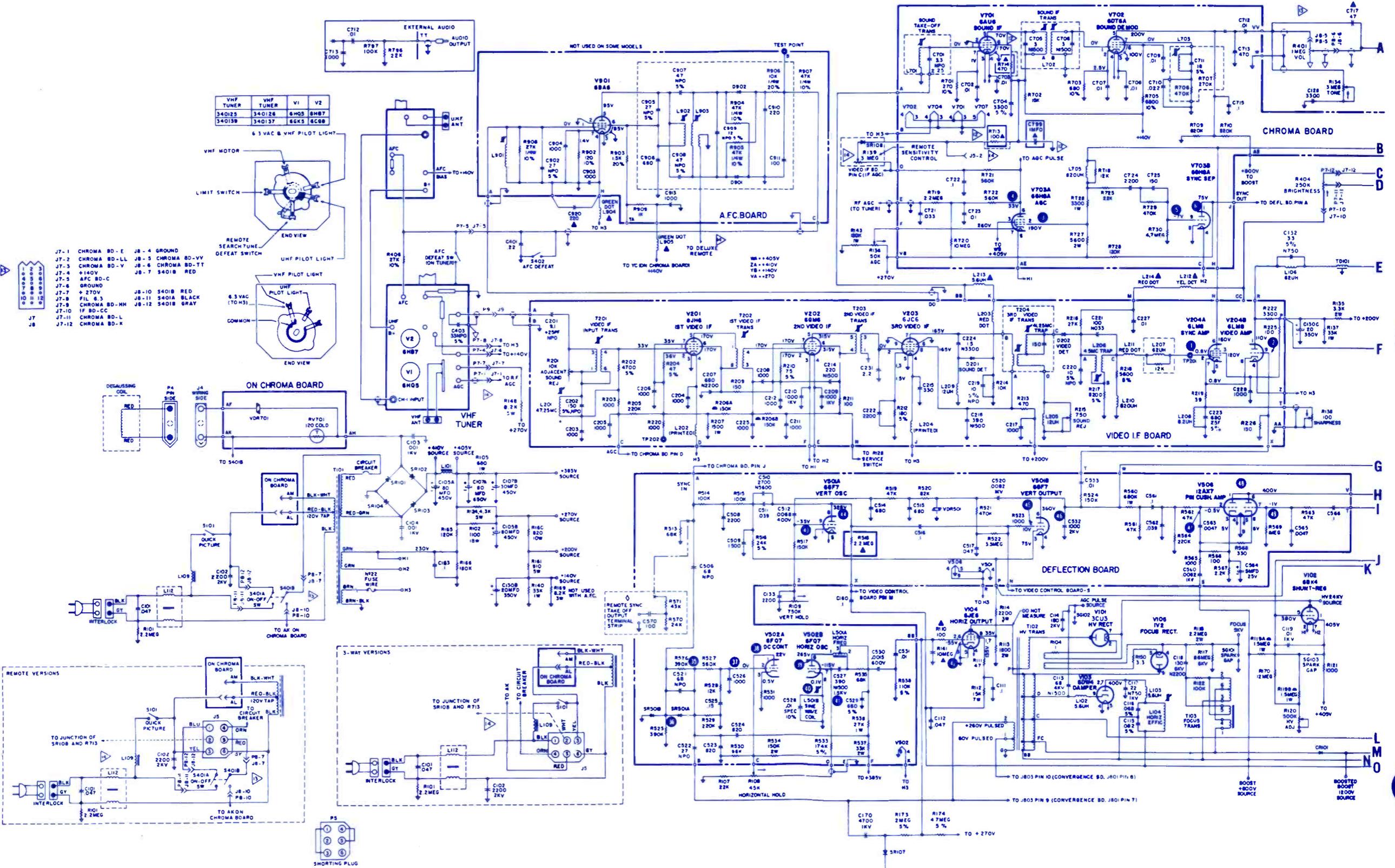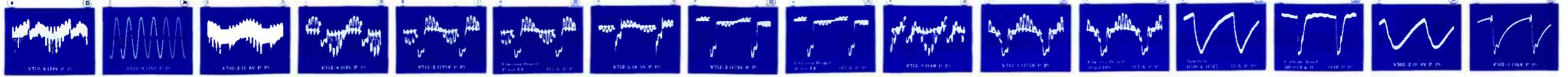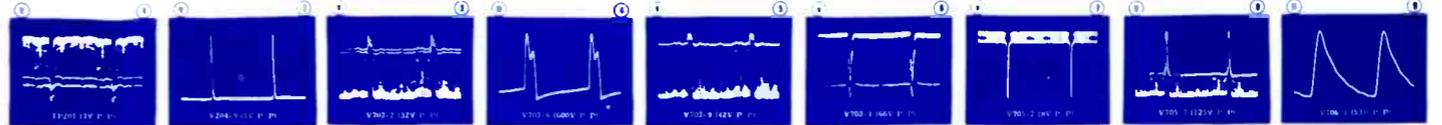
NOTES:
1. ALL RESISTORS ARE 1/2 WATT, UNLESS OTHERWISE NOTED.
2. CAPACITOR VALUES ARE IN MFD, UNLESS OTHERWISE NOTED.
3. VOLTAGE TOLERANCE MAY VARY ± 20%.
4. VOLTAGES MEASURED FROM POINT INDICATED TO CHASSIS GROUND WITH "VTVM" AT NORMAL SIGNAL INPUT.
5. WAVEFORMS TAKEN WITH NORMAL SIGNAL INPUT.



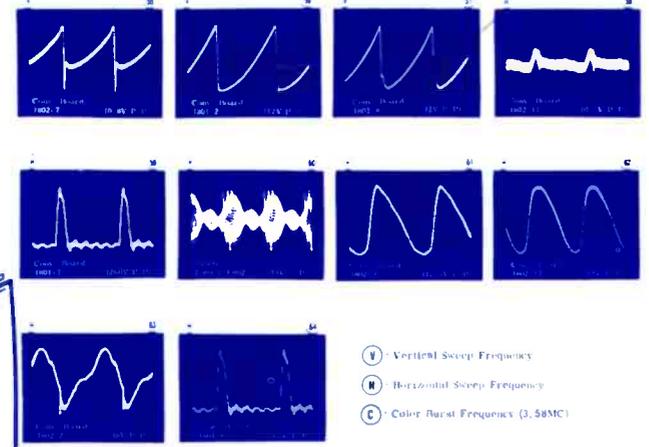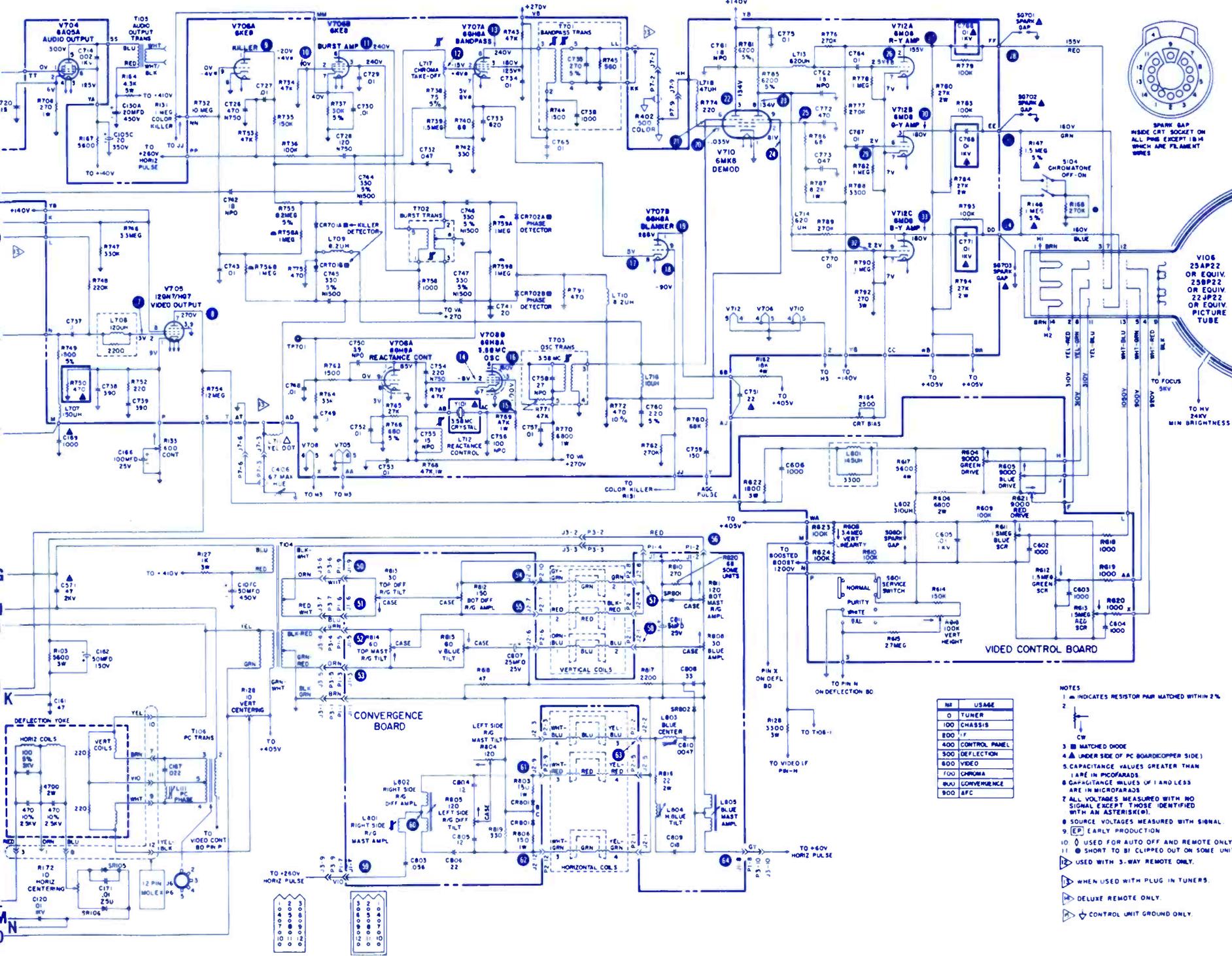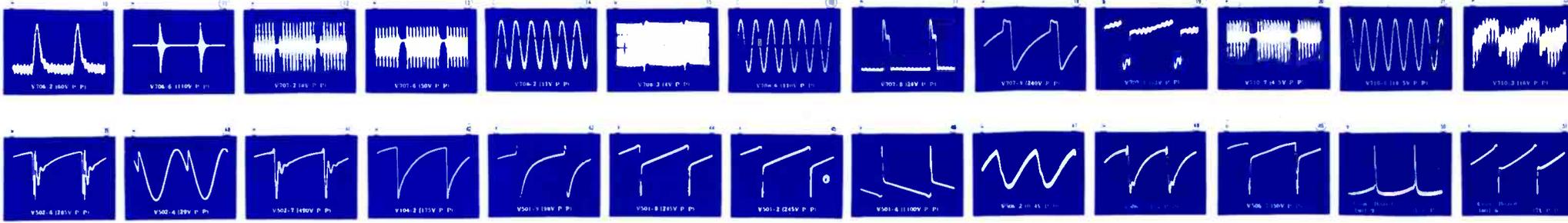

WAVE FORMS & PEAK TO PEAK VOLTAGES

SYMBOL	DESCRIPTION	MAGNAVOX PART NO.
T101	power xformer	300251-1
T102	horiz output xformer	361197-2
T103	vert output xformer	361306-1
T104	vert output xformer	320217-2
T105	audio output xformer	320130-3
T106	pin cushion xformer	361134-3
T701	bandpass xformer	361192-1
T703	3.58MHz xformer	361198-2
L101	react choke	320124-6
L104	horiz efficiency coil	361022-3
L112	line radiation choke	361250-1
L501	horiz osc & sin wave coil	360960-3
L701	sound take-off coil	360845-2
L702	sound lf coil	360846-3
L703	4.5MHz quad coil	360847-2
L713	620µh peak coil	360853-11
L717	chroma take-off coil	360959-3
	def yoke	361290-102
C105	elect 80/80µf 450v 20µf 350v	270071-12
C105	elect 80/80µf 450v (ext. audio version)	270071-13
C107	elect 80/30/50µf 450v	270071-7
C113	cer 68pf 10% 4000v (N1500)	250475-24
C130	elect 20µf 450v 20/20µf 350v	270023-42
C130	elect 20µf 450v 20µf 350v (ext. aud ver)	270023-43
C579	mco 68pf 5% 500v	250364-350
C570	mco 100pf 10% 500v	250224-430
R102	1.1K 10% 18w (WW)	240088-4
R103	5.6K 10% 3w (fixed film)	230193-5629
R112	15K 10% 7w (fixed film)	230161-3
R117	66M 20% (okv breakdown)	240082-71
R160	820 10% 10w WW	230144-98
R765A,B	1M 10% 5w matched within 2%	230144-98
R759A,B	1M 10% 5w matched within 2%	230144-98
C406	5.2pf = 67pf trim	see chart
R108	45K horiz hold	220146-69
R109	750K vert hold	220146-50
R120	500K high volt	220189-4
R126	10 vert cen	220181-1
R131	1M color killer	220208-34
R133	600Ω contr	220146-29
R134	3M tone	220146-26
R136	50K agc	220208-33
R138	100 sharpness	220146-62
R139	3M remote control sensitivity	220208-51
R164	2500 CRT bias	220181-11
R172	horiz cen	220181-12
R201	10K adj sound rej	220182-1
R215	750 sound rej	220166-4
R401	1M vol	see chart
R402	500 color	see chart
R404	250K bright	see chart
R605	9000 blu dr	220166-24
R611	1.5M blu scr	220166-17
RV701	thermistor	230170-2
TD101	delay line	360949-5
VDR501	varistor	230167-5
VDR701	varistor	230175-2
	cir brkr	180723-2

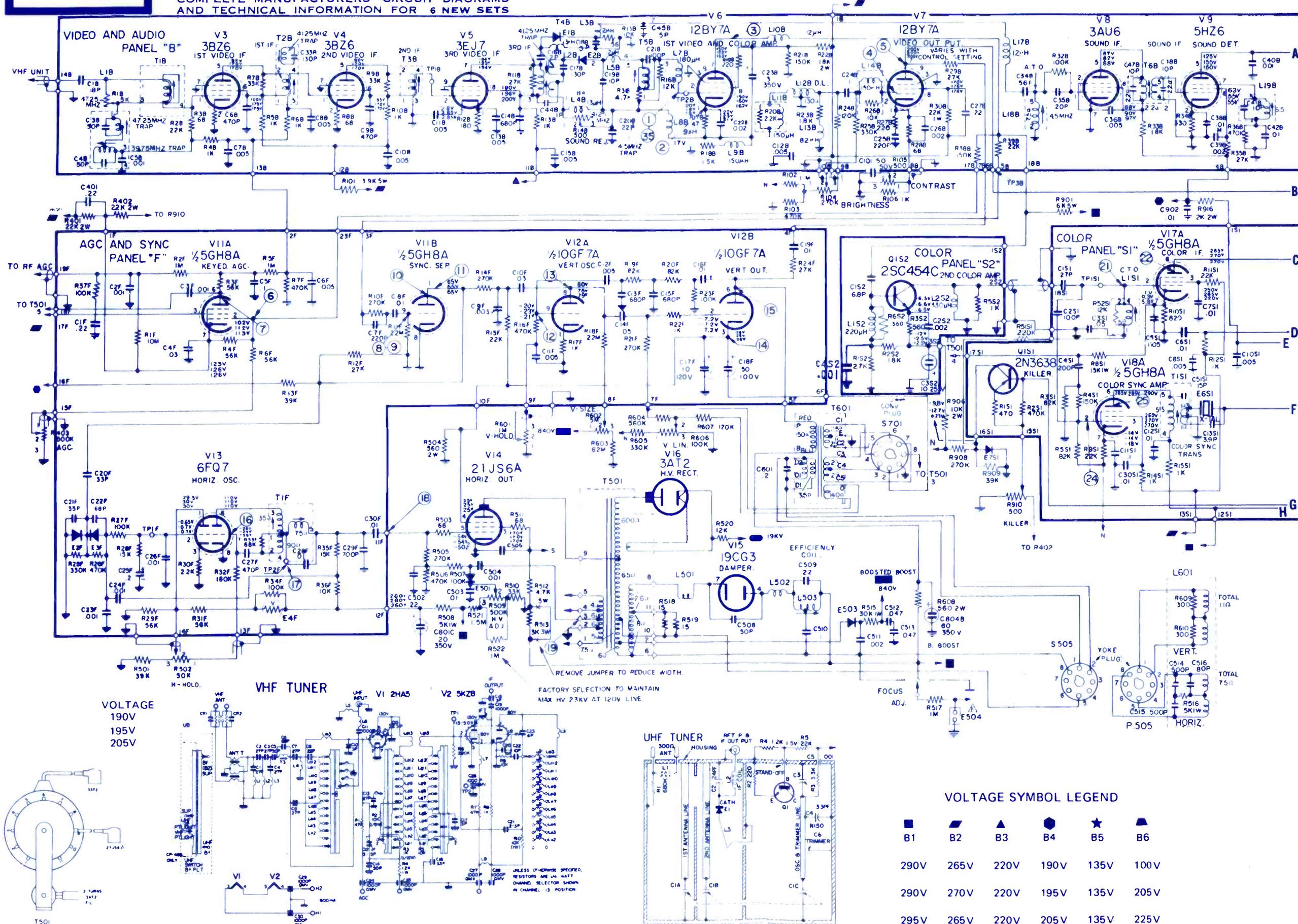

VOLTAGE
190V
195V
205V





VOLTAGE SYMBOL LEGEND

B1	B2	B3	B4	B5	B6
290V	265V	220V	190V	135V	100V
290V	270V	220V	195V	135V	205V
295V	265V	220V	205V	135V	225V

TYPE OF SIGNAL AND ORDER OF LISTING.
VOLTAGE ZERO SIGNAL (TUNER SET BETWEEN CHANNELS).
NORMAL SIGNAL (AIR COLOR PROGRAM).
STANDARD COLOR BAR GENERATOR.

NOTE:
CONDITIONS OF NORMAL AIR SIGNAL - 5 VOLTS PEAK TO PEAK MEASURED FROM GRID TO CATHODE OF FIRST VIDEO AMP AND APPROX. -0.5 VOLTS RF AGC BIAS.
CONDITIONS OF COLOR BAR GENERATOR - 1 VOLT PEAK TO PEAK MEASURED FROM GRID TO CATHODE OF FIRST VIDEO AMP AND APPROX. -0.2 VOLTS RF AGC BIAS.

MOTOROLA
Color TV Chassis TS924B,C

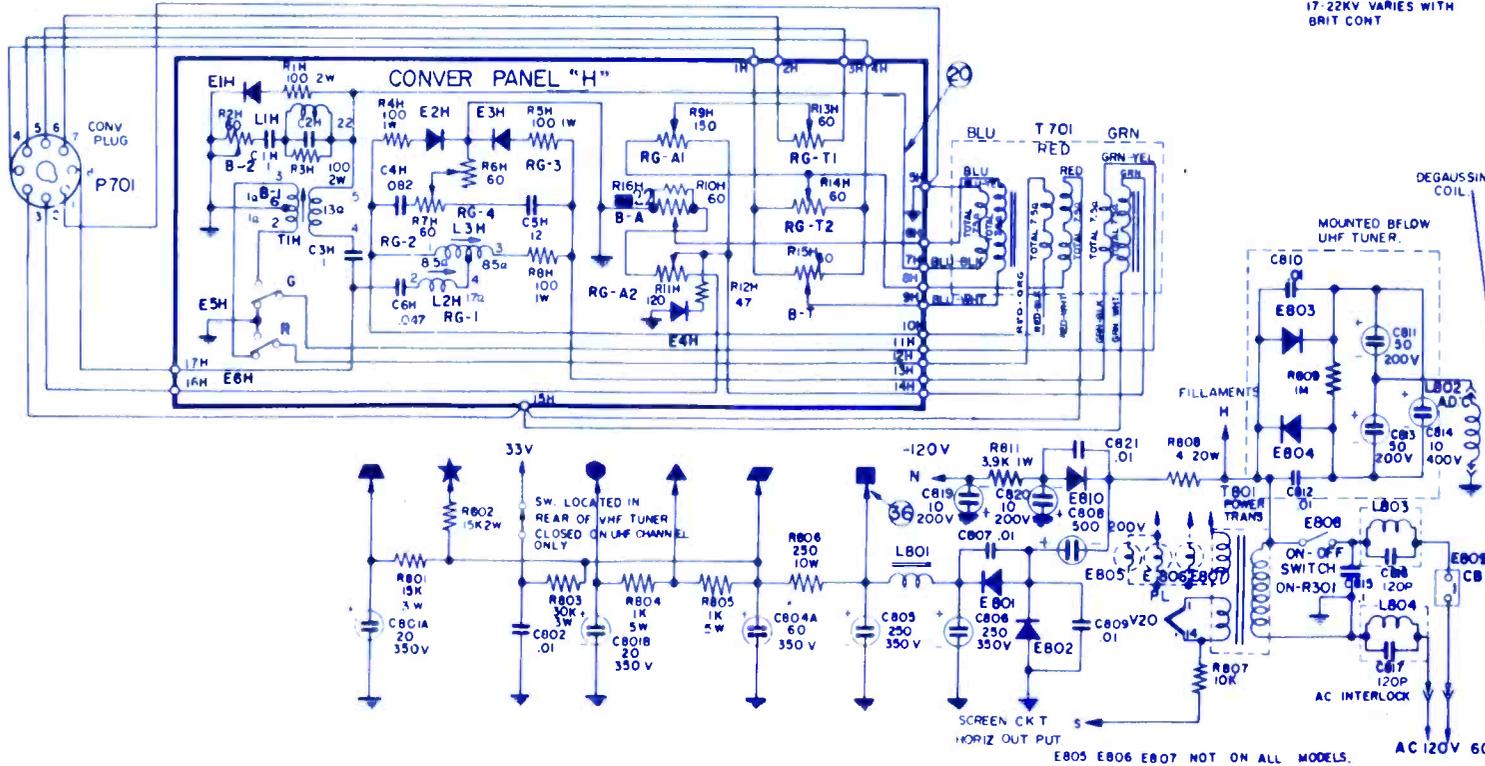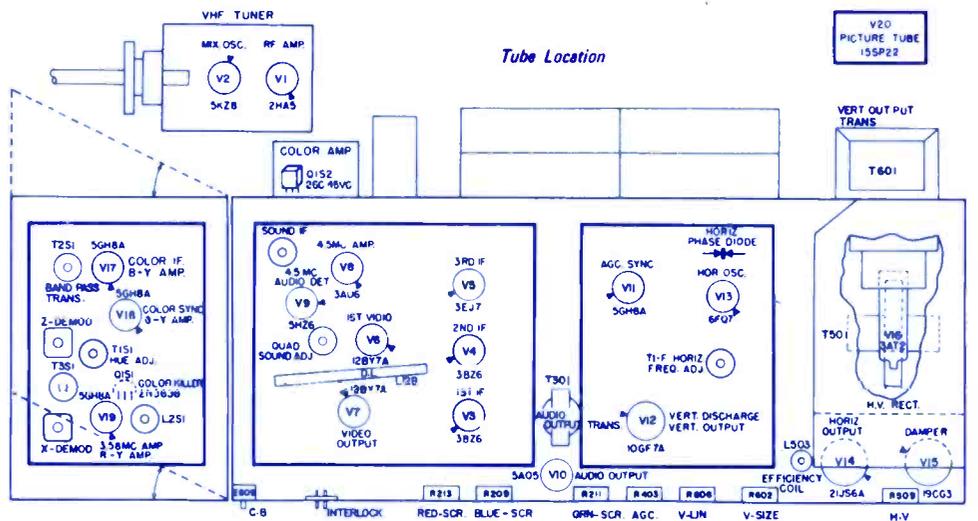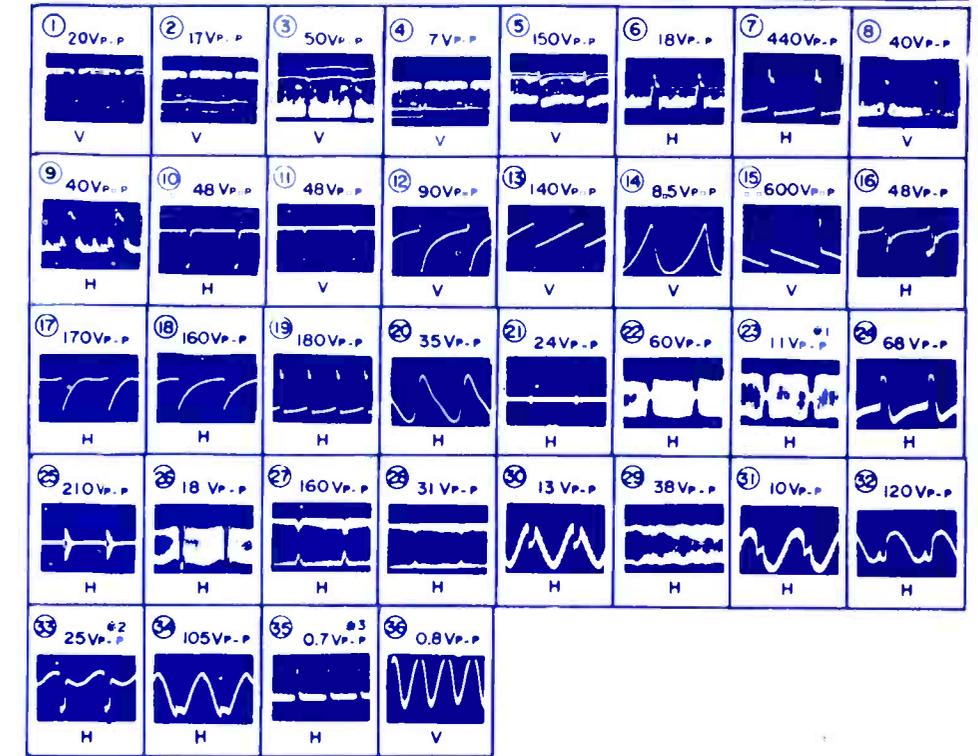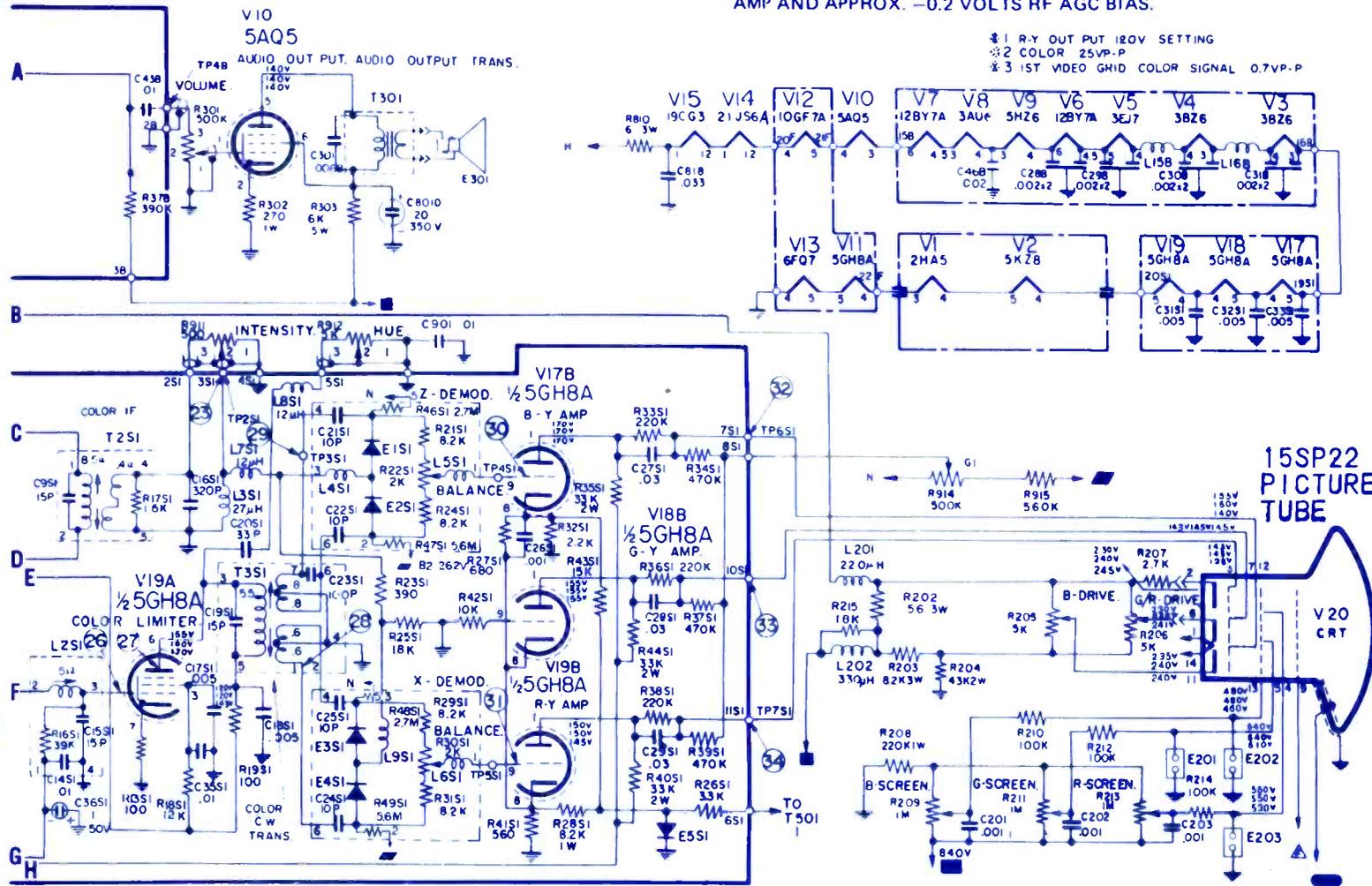


SYMBOL	DESCRIPTION	MOTOROLA PART NO.	
C27F	- 470pf 10% 500v silver mica	21510052A38	
C508	- 50pf 10% 5kv	21D90161A08	
C514	- 500pf 10% 3kv	21D90161A13	
C515	- 500pf 10% 3kv	21D90161A13	
C516	- 56pf 10% 5kv N1500	215180A73	
C801	- C801A/20µf C801B/20µf C801C/20µf		
C801D	- 20µf 350v lyric	21D90161A35	
C804	- C804A/60µf C804B/60µf 350v lyric	21D90161A36	
E18	- crystal diode 1N60	48C65837A02	
E808	- dual diode	48D90056A01	
E4F	- varistor	68D90069A01	
E809	- circuit breaker	80C66390A15	
	vert pin cushion phase	24P65171A45	
	vert pin cushion corrector	24P65171A46	
L88	- compensating 2µh	24B90083A01	
L128	- delay line	24B90094A01	
L158	- choke, RF	24B90128A01	
L188	- audio take off	24B90093A01	
L198	- quad incls. C418	24B90163A01	
L51	- peaking incls. R5251	24B90216A01	
L351	- filter	24B90154A01	
L252	- compensating 330µh	24B90129A01	
L503	- horiz efficiency	24B90084A01	
L801	- filter choke	25C90097A01	
L802	- deg coil. CRT	24B90130A01	
Q151	- color killer 2N3638	48B90165A01	
Q152	- 2nd color amp 25C45AC	48C90172A01	
R18	- IF trap 5K	18B90056A02	
R148	- sound reject 500Ω	18B90056A03	
R2H	- B2 60Ω	18890062A01	
R6H	- 2 60Ω	18890160A01	
R11	- A2 120Ω	18890160A02	
R14H	- T2 60Ω	18890160A01	
R2251	- balance 2K	18890056A01	
R140	- bright 270K	18890123A01	
R105	- contr 500Ω	18C90059A01	
R205	- B-drive 5K	18C90060A01	
R301	- G-screen 1M	18A90051A01	
R403	- vol 500k inds on/off switch E808	18A90057A02	
R502	- horiz hold 50K	18D90056A01	
R509	- HV adj 500K	18B90049A01	
R601	- circuit breaker	18890053A01	
R602	- vert size 5M	18B90061A01	
R606	- vert lin 100K	18A90057A01	
R910	- color killer 500Ω	18B90122A01	
R911	- intensity 500Ω	18A90052A01	
R912	- hue 5K	18B90055A01	
T18	- 1st IF interstage	24B90074A01	
T48	- video det	24B90081A01	
T58	- 4.5MHz trap incls C218, R168 & R318	24C9022A01	
T1F	- horiz osc incls C28F	24B90082A01	
T151	- color xformer incls C5151	24B90218A01	
T251	- color IF incls C951 & R1751	24B90072A01	
T351	- phase incls C1951 & C2351	24C90219A01	
T301	- audio output	24C90220A01	
T501	- HV xformer complete in TS924C & later	24P65171A49	
T601	- vert output	25C90099A01	
T701	- conv yoke	24C90092A01	
T801	- filament CRT C14TS924	25C690100A01	

SYMBOL	DESCRIPTION	TRUETONE PART NO.
R219	Control AGC	15-167009
R314(SW701)	control SW & vol	15-167010
R505	carbon (Spec.) 1.2M ±10% 1/2w	15-140004
R517	control vert hold	15-167011
R518	control vert size	15-167012
R519	control vert lin	15-167012
R626	control horiz hold	15-167014


R718	control contrast	15-167015
R719	control bright	15-167016
C705	cer 6.8pf ±0.5% 500v	13-130064
C708A	elec 200µf/200	15-138002
C708B	µf/50µf ±20%	15-138002
C708C	180v	15-138002
C712	special 0.1µf ±20% u1	15-139002
M501	copistor	15-139001
L201	47.25MHz trap coil	15-094008
L301	SIF det coil	15-094009
L601	horiz stobi coil	15-094007
T201	1st VIF & 50.35MHz trap trans	15-094003

T202	2nd VIF trans	15-094004
T203	VIF det trans	15-094005
T301	1st SIF trans	15-094006
T302	audio output trans	15-097002
T501	vert output trans	15-097003
T601	horiz output trans	15-097004
T701	SIF take-off & 4.5MHz trap trans	15-094002
T702	power choke trans	15-097005
D201	diode IN87A	15-085061
F701	fuse 1.6a	15-204001
	def yoke	15-097006
	VHF tuner	15-078001
	UHF tuner	15-078002


VHF ANT. TERMINAL TELESCOPIC VHF ANTENNA

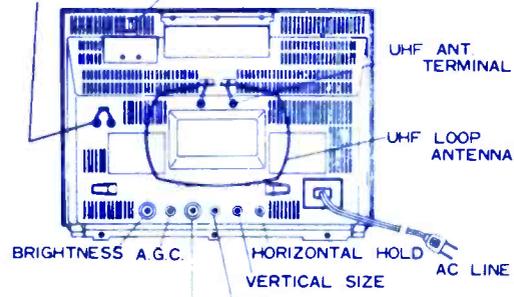


UHF TUNER MODEL UT6-2U2

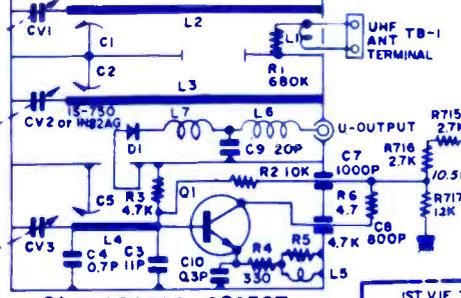


TB101 VHF ANT. NT6-7U2

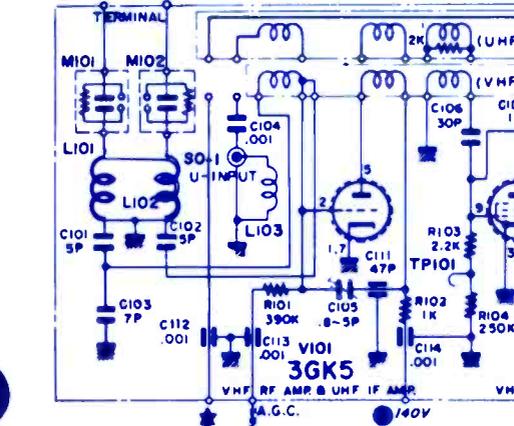

VOLTAGE SYMBOL LEGEND

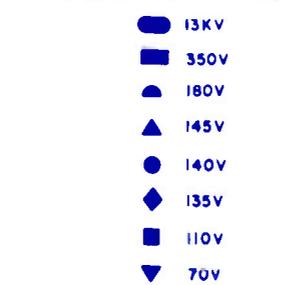

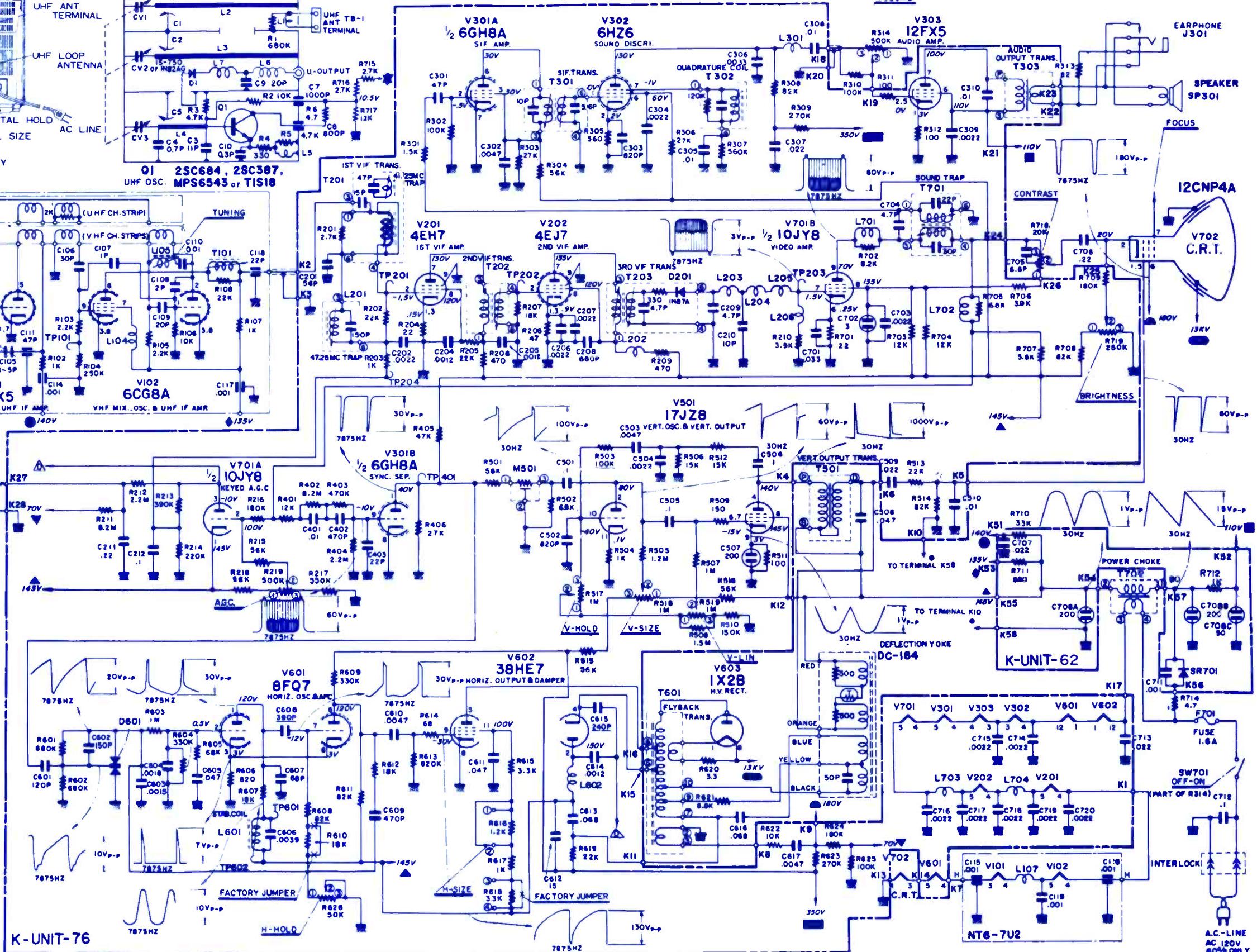DC VOLTAGE MEASUREMENTS
ARE AT NO SIGNAL CONDITION.






MAY • 1969

COMPLETE MANUFACTURERS' CIRCUIT DIAGRAMS
AND TECHNICAL INFORMATION FOR 6 NEW SETS

SPECIFICATIONS

POWER USED AT CHASSIS	120V 60 CYCLES	OVERLOAD PRO- TECTION (AC LINE)	SOUND POWER OUTPUT
13Z12	120 Watts	Pigtail Fuse (1.8A)	1 Watt
13Z12S	120 Watts	Pigtail Fuse (1.8A)	1 Watt

22-5506	C18A - 300uf elec cap 175V	Part of 17
22-5506	C18B - 200uf elec cap 150V	20-1424
22-5506	C18C - 200uf elec cap 150V	95-2567
22-5506	C18D - 100uf elec cap 150V	5-64875
03-6483	R8 - 250K 1/2W	5-64852
03-6483	R9 - 250K 1/2W	5-60558
03-6483	R10 - 10K 1/2W	5-29299
03-6483	R11 - 5K A.G.C. cont	95-2518
03-6483	R12 - 7M vert size cont	95-2518
03-6483	R13 - 1M vert hold cont	95-2518
03-6483	R14 - 300K vert lin cont	199-091
03-6483	R15 - det series peaking coil	97-4
03-6483	L4 - choke coil	136-65
03-6483	L5 - det shunt peaking coil	Part of R9
03-6483	L6 - sound take-off coil winding 555	Part of T5
19-0000	19 - quad coil winding 555	
110-0000	110 - filter coil	
111-0000	111 - filter choke	
112-0000	112 - 2nd IF coil 555	
113-0000	113 - 3rd IF coil 555	
114-0000	114 - 3rd IF coil 555	
115-0000	115 - 3rd IF coil 555	
116-0000	116 - sound take-off coil 555	
117-0000	117 - sound take-off coil 555	
118-0000	118 - sound output xformer	
119-0000	119 - vert output xformer	
120-0000	120 - 120V 1A xformer	
121-0000	121 - 120V 1A xformer	
122-0000	122 - 120V 1A xformer	
123-0000	123 - 120V 1A xformer	
124-0000	124 - 120V 1A xformer	
125-0000	125 - 120V 1A xformer	
126-0000	126 - 120V 1A xformer	
127-0000	127 - 120V 1A xformer	
128-0000	128 - 120V 1A xformer	
129-0000	129 - 120V 1A xformer	
130-0000	130 - 120V 1A xformer	
131-0000	131 - 120V 1A xformer	
132-0000	132 - 120V 1A xformer	
133-0000	133 - 120V 1A xformer	
134-0000	134 - 120V 1A xformer	
135-0000	135 - 120V 1A xformer	
136-0000	136 - 120V 1A xformer	
137-0000	137 - 120V 1A xformer	
138-0000	138 - 120V 1A xformer	
139-0000	139 - 120V 1A xformer	
140-0000	140 - 120V 1A xformer	

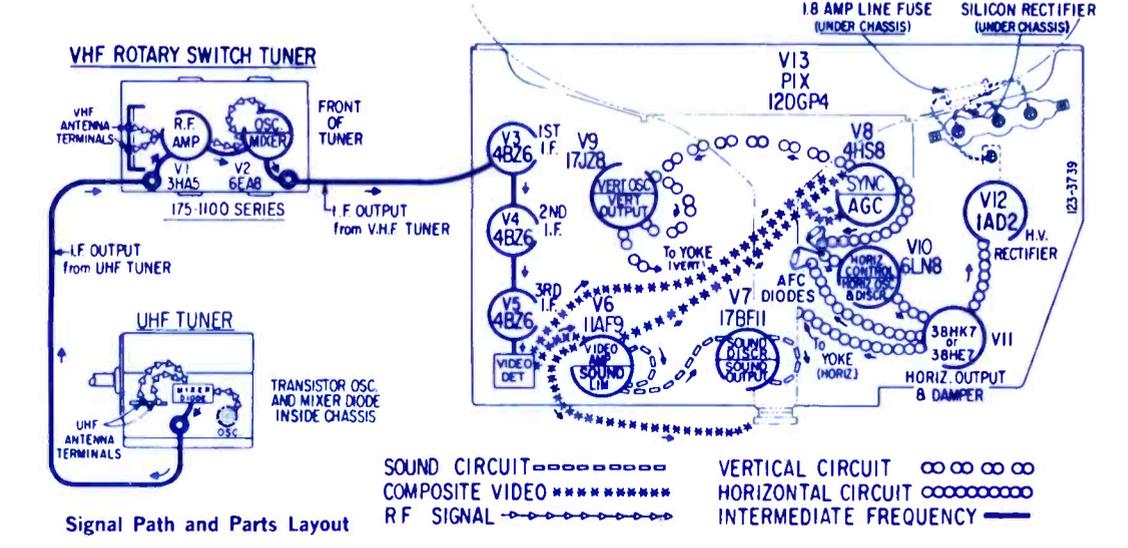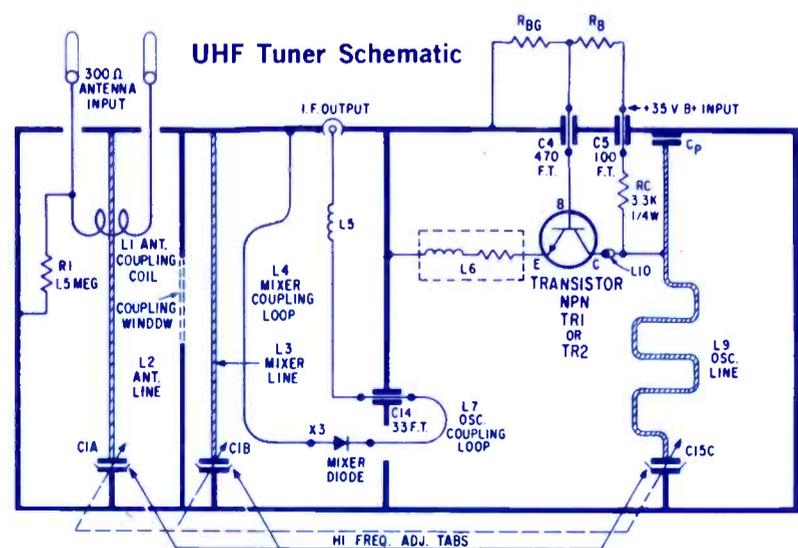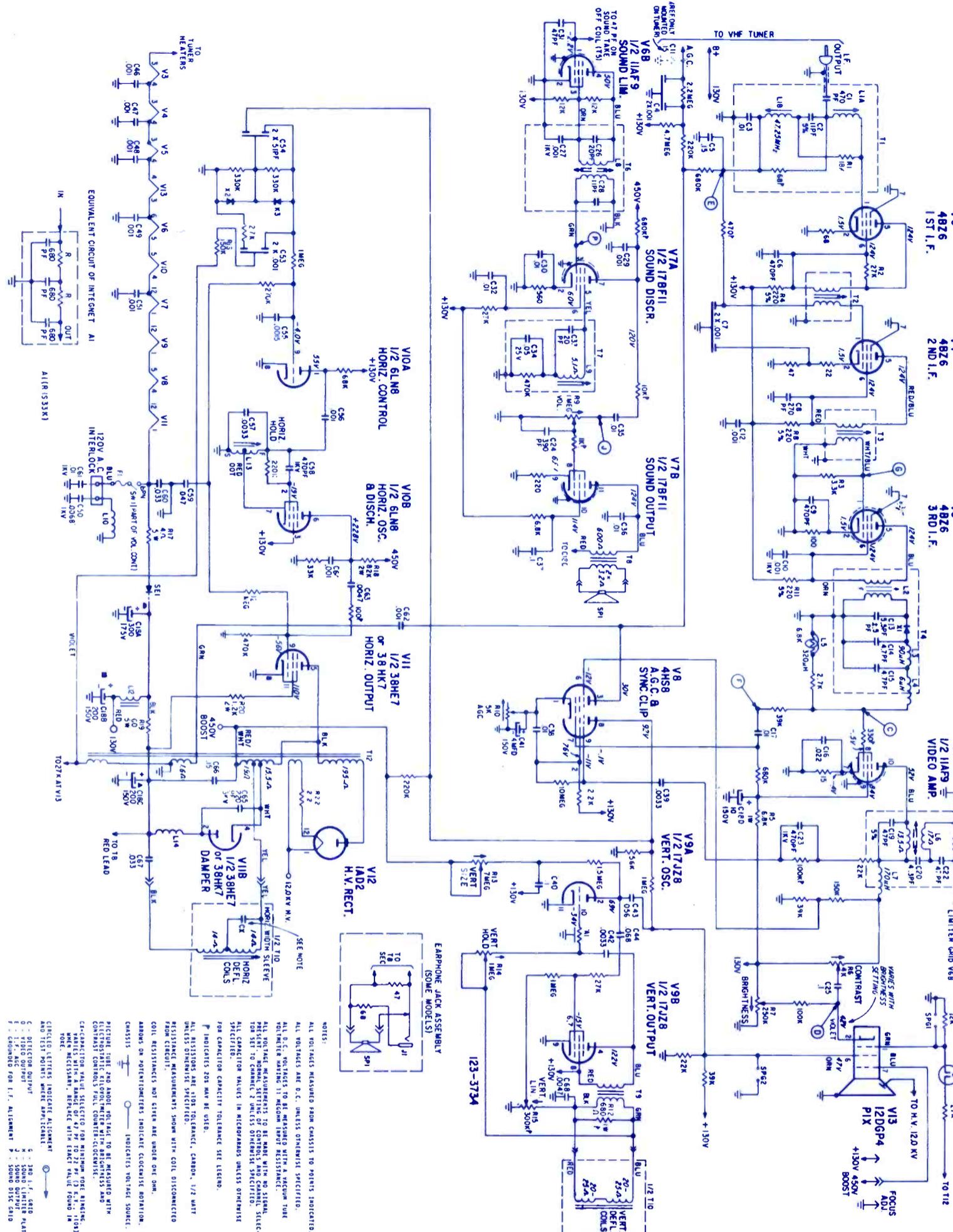



OVERHAUL

\$9.75

GUARANTEED for 1 Year

OVERHAUL \$9.75 • REPLACEMENT TUNERS... \$10.45

Nine-seventy-five buys you a complete tuner overhaul—including parts (except tubes or transistors)—and *absolutely no hidden charges*. All makes, color or black and white. UV combos only \$15.

Guaranteed means a full 12-month warranty against defective workmanship and parts failure due to normal usage. That's 9 months to a year better than others. And it's backed up by the only tuner repair service authorized and supervised by the world's largest tuner manufacturer—Sarkes Tarzian, Inc.

Four conveniently located service centers assure speedy in-and-out service. All tuners thoroughly cleaned, inside and out... needed repairs made... all channels aligned to factory specs, then rushed back to you. They look—and perform—like new.

SEND ORDERS FOR UNIVERSAL AND CUSTOMIZED REPLACEMENT TUNERS TO OUR OFFICE IN INDIANAPOLIS.

Prefer a universal replacement? Sarkes Tarzian will give you a universal replacement for only \$10.45. This price is the same for all models. The tuner is a new tuner designed and built specifically by Sarkes Tarzian for this purpose. It has memory fine tuning—UHF plug-in for 82 channel sets—universal mounting—hi-gain—lo-noise.

ORDER TUNERS BY PART NUMBER, AS FOLLOWS:

Part #	Intermediate Frequency	AF Amp Tube	Osc. Tube	Mixer Tube	Heater
MFT-1	41.25 mc Sound 45.75 mc Video	6GK5	6LJ8	Parallel	6.3V
MFT-2	41.25 mc Sound 45.75 mc Video	3GK5	5LJ8	Series	450 MA
MFT-3	41.25 mc Sound 45.75 mc Video	2GK5	5CG8	Series	600 MA


Prefer a customized replacement tuner? The price will be \$18.25. Send us the original tuner for comparison purposes, also TV make, chassis and model numbers.



TUNER SERVICE CORPORATION FACTORY-SUPERVISED TUNER SERVICE

MIDWEST 817 N. PENNSYLVANIA ST., Indianapolis, Indiana (Home Office) TEL: 317-632-3493
EAST 547-49 TONNELE AVE., Jersey City, New Jersey TEL: 201-792-3730
SOUTH-EAST 938 GORDON ST., S. W., Atlanta, Georgia TEL: 404-758-2232
WEST SARKES TARZIAN, Inc. TUNER SERVICE DIVISION 10654 MAGNOLIA BLVD., North Hollywood, California TEL: 213-769-2720

WATCH FOR NEW CENTERS UNDER DEVELOPMENT

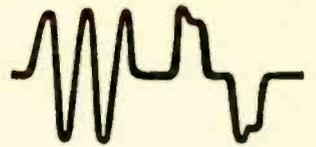

Versatile Sonalert® Signal makes a great ingenuity tester

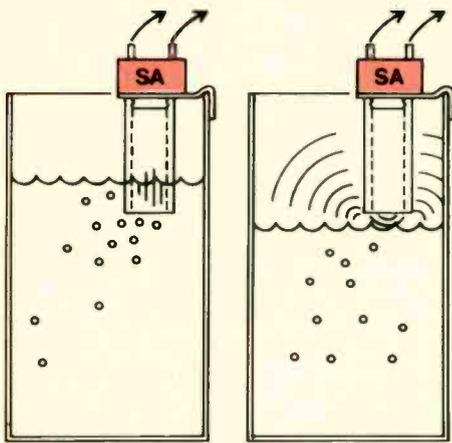


Fig. 1—Trapped Sound System



Fig. 2—Mechanical System

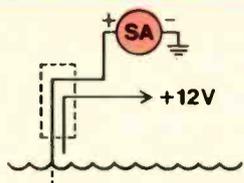


Fig. 3—Simple Electronic System

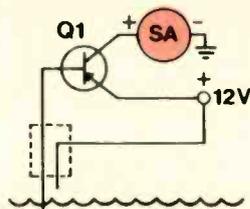


Fig. 4—High Output Electronic System

Crank up your inventive powers and put them to work with Sonalert®, the low-drain, solid-state tone signal that gives a big sound with just a few milliamp drive. More than likely you can come up with some great ideas for your shop, home or car. Ideas for fun, safety—and, perhaps, profit.

Just to give you a few clues, let's take a look at the way would-be Edisons turned Sonalerts into interesting ideas. We've picked four ways in which others have used this new signaller for one application: liquid level alarm.

One of the simplest is a compact system that requires no trigger circuits or complex mechanical devices. All you have to do is install a glass or plastic tube on the unit's nose cone, and hook the Sonalert to a power source. (See figure 1.) Insert the tube into the liquid to the level required for alarm. Since the tube is immersed, no sound can escape. Once the fluid falls below the critical level, out comes a loud, clear, unmistakable signal. Here's an ideal system for use in explosive atmospheres; Sonalert produces no arcs or sparks.

Figure 2 shows a mechanically actuated system—float and switch. It's made up by mounting a float ball on a lever arm that actuates a plunger switch in series with the Sonalert and power source. Reliability might be a problem because of mechanical failures.

For greater reliability, the simple electronic system (figure 3) is hard to beat. Fluid acts as the switch to close the circuit between Sonalert and the source. Just one problem presents itself. The sound level from Sonalert is proportional to current flow. If the liquid is not a good conductor, current flow may be too low.

To overcome this limitation, a high output electronic signal system was developed (refer to figure 4). Here transistor Q1 acts as a low resistance switch; and current flow to the Sonalert is maximum as long as there is enough base current flowing through the fluid to hold Q1 ON.

Here are four variations on one theme. Bet you can come up with some great ideas on your own. Try. If you can't, we've got more tips for you in booklet No. 9-406 that's yours for the asking at your Mallory Distributor's. It's chock-full of information: how Sonalert works, ratings, specs, mounting instructions and more tips. You can write for a copy, if you prefer. Mallory Distributor Products Company, a division of P. R. Mallory & Co. Inc., Indianapolis, Indiana 46206.

DON'T FORGET TO ASK 'EM— *“What else needs fixing?”*

ELECTRONIC TECHNICIAN / DEALER

WORLDS LARGEST ELECTRONIC TRADE CIRCULATION

MAY 1969 : VOL. 89 NO. 5

**HUGH "SCOTTY"
WALLACE**
Publisher

PAUL DORWEILER
Editor

JOSEPH ZAUHAR
Technical Editor

MORTON WARNOW
Field Editor

DONNA BUTLER
Production Editor

BOB ANDRESEN
Art Editor

LILLIE PEARSON
Circulation Manager

JOHN KESSLER
Manager, Reader Services

JUDI LeMAY
Advertising Production

OFFICES

71 Vanderbilt Ave.
New York, N.Y. 10017
Phone: (212) 686-2200
Telex: 01-26286

43 East Ohio St.
Chicago, Ill. 60611
Phone: (312) 467-0670
Telex: 02-53549

1901 West 8th Street
Los Angeles, Calif. 90057
(213) 483-8530

Harbrace Building
Duluth, Minn. 55802
Phone: (218) 727-8511
Telex: 02-94417

MARKETING REPRESENTATIVES

HUGH "SCOTTY" WALLACE
Chicago: (312) 467-0670

ALFRED A. MENEGUS
New York: (212) 686-2200

DONALD D. HOUSTON
Los Angeles: (213) 483-8530

ROBERT UPTON
Tokyo, Japan
I.P.O., Box 5056

HARBACE PUBLICATIONS, INC.

JAMES MILHOLLAND, JR.
President

DEAN MYHRAN
Executive Vice President

RICHARD MOELLER
Treasurer

LARS FLADMARK
Senior Vice President

HARRY RAMALEY
Vice President

BEN MARSH
Vice President

JAMES GHERNA
Art Director

WILLIAM SWAIN
Director of Marketing Services

DOUG HEDIN
Ad Production Manager

39 SIGNAL STRENGTH METERS

Versatility is the theme of part one in this series which describes the signal strength meter as well as its importance to the TV service technician and antenna installer

44 LOW COST SOLID-STATE CURVE TRACER

Here's an interesting instrument you can build and connect to any scope for an actual waveform presentation of a transistor's operation

48 COLOR SYSTEM TROUBLESHOOTING

One of the latest solid-state devices to find its way into a color TV receiver is the "IC chip" for color demodulation explained in this timely article with troubleshooting information

52 CONTRAST NOW—TOMORROW WHAT?

The "black screen" filter, which is still relatively new to many technicians, is humorously discussed in this Bob and Scoot feature

56 TESTLAB REPORT ON HEATH MODEL IT-18 AND EICO MODEL 385

This month's testlab discusses the Heath in-circuit/out-of-circuit transistor tester and the EICO battery-powered, transistorized color bar generator

58 RADIOS FOR RADIOMEN

The old saying about the shoemaker's kids is put to the acid test as this month's dealer explains what two-way radio can mean to a service business

61 ELECTRONIC LIGHTNING DETECTOR

This short, but interesting feature, explains an unusual electronic device designed by a Canadian technician for tracking electrical storms

22 EDITOR'S MEMO

24 LETTERS TO THE EDITOR

30 TECHNICAL DIGEST

34 BOOK REVIEWS

64 DEALER SHOWCASE

74 COLORFAX

76 NEW PRODUCTS

78 NEWS OF THE INDUSTRY

86 CATALOGS AND BULLETINS

94 AD INDEX

COVER

Transistors and digital circuits in everything from model planes to test instruments is the theme of this month's cover which shows the Hickok digital test instrument and solid-state scope, the Darcy digital voltmeter, Setchell Carlson's move to transistor plug-in boards for color TV and the latest Heath digital proportional radio control system for model enthusiasts.

TEKFAX • 16 PAGES OF THE LATEST SCHEMATICS • GROUP 201

AIRLINE: TV Model GHJ-14549A

MAGNAVOX: Color TV Chassis T933

MOTOROLA: Color TV Chassis TS924B,C

PHILCO-FORD: TV Chassis 19P22

TRUETONE: TV Model 3912

ZENITH: TV Chassis 13Z12, 13Z12S

ELECTRONIC TECHNICIAN/DEALER is published monthly by Harbrace Publications, Inc., Harbrace Building, Duluth, Minnesota 55802, a subsidiary of Harcourt, Brace & World, Inc. Subscription rates: One year \$5, two years \$8, three years \$10, in the United States and Canada. Other countries: One year \$9, two years \$14, three years \$18. Single copies 75¢ in the United States and Canada; all other countries: \$2.00. Second class postage paid at Dansville, New York, and at additional mailing offices. Copyright 1969 by Harbrace Publications, Inc.

POSTMASTER: Send Form 3579 to ELECTRONIC TECHNICIAN/DEALER, Harbrace Building, Duluth, Minnesota 55802.

The FM-2400C provides an accurate standard frequency signal for testing and adjustment of mobile transmitters and receivers at predetermined frequencies between 25 and 500 MHz. Up to 24 crystals may be inserted into the meter. The frequencies can be those of the radio frequency channels of operation, and/or of the intermediate frequencies of the receivers between 5 MHz and 40 MHz. Frequency stability (standard) $\pm .001\%$ from 32° to 122°F. Frequency stability with built-in thermometer, calibrated crystals and temperature corrected charts, .00025% from

+25°F to +125°F. (.000125% special 450 MHz crystals available)

FM 2400C (Meter Only).....	\$445.00
RF Crystals	
Hi Band.....	\$24.00 ea.
Lo Band.....	15.00 ea.
IF Crystals.....	8.00 ea.

Write for free catalog.



CRYSTAL MFG. CO., INC.
10 NO. LEE • OKLA. CITY, OKLA. 73102

TV Helps Sets NBS Time Standard

The National Bureau of Standards scientists and engineers have borrowed from commercial television in Denver to design a system whereby the clock that controls the broadcasts from station WWV in Fort Collins, Colo., may be kept within a millionth of a second of the atomic clock in Boulder.

The technique uses the television synchronizing pulse on the TV carrier wave.


This is how it works. A TV table model set is operated at the NBS atomic clock end in Boulder, and another at the NBS broadcast station end in Fort Collins. Both TV sets are tuned to the same Denver TV channel and both are connected to sensitive electronic equipment which records the arrival of the periodic pulses on the carrier wave. The sync pulses are a known distance apart and are easily identified by electronic devices which "tag" them as they arrive at the location of each recording device. In the present case, the distance from crest to crest of succeeding pulses is about 11.8 miles.

The equipment records the time of arrival of these pulses at the "atomic clock" in Boulder and at the radio stations in Fort Collins. The time delay between the TV transmitter near Denver and the Boulder and Fort Collins receivers is accurately known to a tenth of a millionth of a second. From this information NBS scientists calculate the time difference between two clocks. Once the difference is known, even if it is only a few millionths of a second, corrections may be made to synchronize the Fort Collins radio station clock with the atomic clock in Boulder.

The absolute accuracy of the measurement is conservatively set at plus or minus a millionth of a second.



Paul A. Horvick

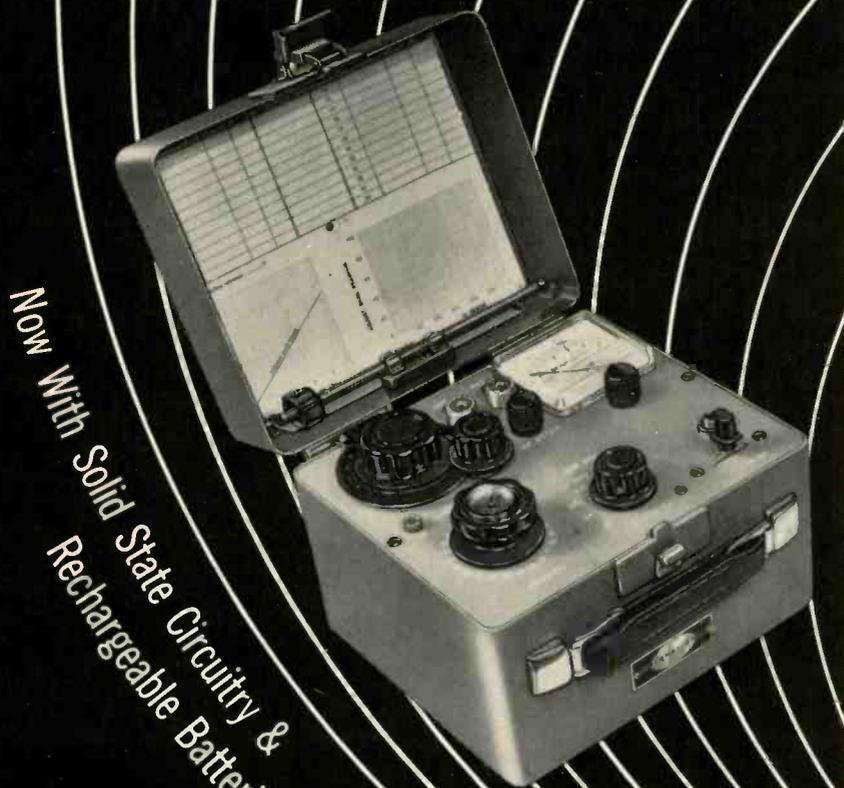

Now With Solid State Circuitry & Rechargeable Batteries

ICM FM-2400C frequency meter...


- Completely Portable
- Tests Predetermined Frequencies 25 MHz - 500 MHz

... for more details circle 125 on postcard

New reliable profitable

JFD

Program Center Amplifiers

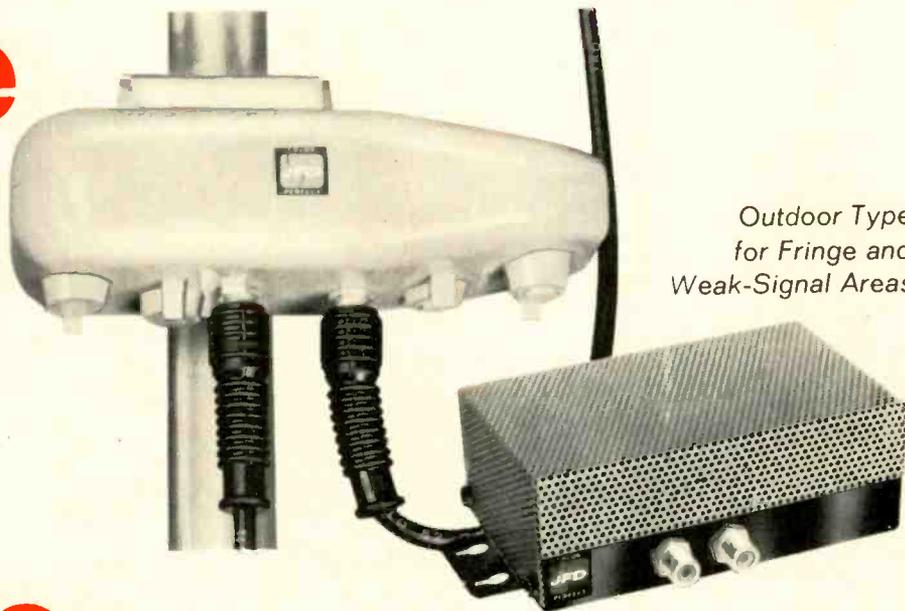

Outdoor Type
for Fringe and
Weak-Signal Areas



Indoor Type
for City and
Suburban Areas

JFD Program Centers — the result of three years of research and development — are here! Now you can equip any home with a complete entertainment system!

- Operate up to 4 (or more) TV sets and FM receivers from one antenna.
- Solid state silicon overlay transistors with silicone sealed printed circuitry provide higher gain, less noise . . . ultra-reliable performance.
- Deliver true-to-life color . . . crisp black and white pictures.
- Available for 300 ohm or 75 ohm VHF and VHF/UHF/FM installations.

The ONLY amplifiers so RELIABLE in performance that they are backed by an exclusive SIX (6) MONTH INSTANT REPLACEMENT GUARANTEE! With this performance (and insurance), how can you miss?

JFD

**Program Center and Snow Plow
INSTANT REPLACEMENT
GUARANTEE**

This unit is guaranteed 100% for a period of six months. If, within a period of six (6) months after it was purchased, it does not operate for any reason whatsoever (including lightning strike, line surge or static build-up,) or otherwise fail to perform satisfactorily we will replace it with a brand new unit instantly — absolutely **FREE! NO QUESTIONS ASKED!**

Write today for your Program Center promotional kit and home antenna systems manual

JFD ELECTRONICS CORP. 15th Avenue at 62nd Street, Brooklyn, N. Y. 11219

©1969. JFD


"See us at the NEW Electronics Show, Booth C100, Suite 4120-4122, Hotel Sahara, Las Vegas, May 21-23."

ARROW AUTOMATIC STAPLE GUNS

CUT WIRE & CABLE INSTALLATION COSTS

... without cutting into insulation!

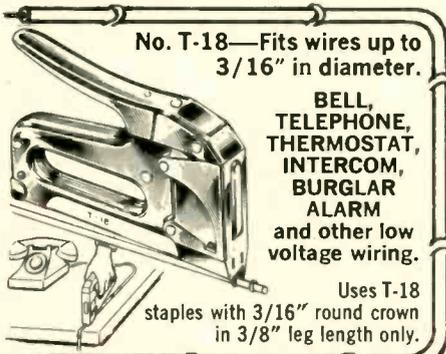
SAFE! Grooved Guide positions wire for proper staple envelopment! Grooved Driving Blade stops staple at right depth of penetration to prevent cutting into wire or cable insulation!



No. T-18—Fits wires up to 3/16" in diameter.

BELL,
TELEPHONE,
THERMOSTAT,
INTERCOM,
BURGLAR
ALARM
and other low
voltage wiring.

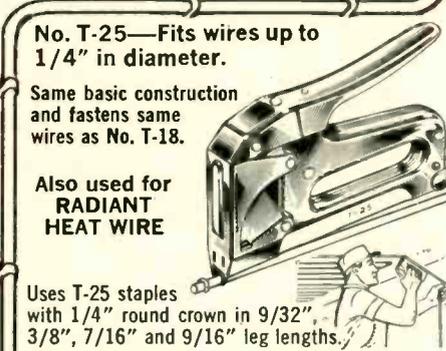Uses T-18
staples with 3/16" round crown
in 3/8" leg length only.



No. T-25—Fits wires up to 1/4" in diameter.

Same basic construction
and fastens same
wires as No. T-18.

Also used for
RADIANT
HEAT WIRE

Uses T-25 staples
with 1/4" round crown in 9/32",
3/8", 7/16" and 9/16" leg lengths.

T-18 and T-25 staples also available in Monel and with beige, brown and ivory finish at extra cost.



No. T-75—Fits wires and cables up to 1/2" in diameter.

RADIANT HEAT
CABLE,
UF CABLE,
WIRE CONDUIT
COPPER TUBING
or any non-metallic
sheathed cable.

Also used as
DRIVE RINGS
in stringing wires.

Uses T-75 staples with 1/2"
flat crown in 9/16", 5/8" and
7/8" leg lengths.

Arrow Automatic Staple Guns save 70% in time and effort on every type of wire or cable fastening job. Arrow staples are specially designed with divergent-pointed legs for easier driving and rosin-coated for greater holding power! All-steel construction and high-carbon hardened steel working parts are your assurance of maximum long-life, service and trouble-free performance.

Ask your Electrical Supply Dealer or write for further details.

ARROW FASTENER COMPANY INC.
Saddle Brook, New Jersey 07863
"Pioneers and Pacesetters
For Almost A Half Century"

... for more details circle 104 on postcard

ET/D

LETTERS TO THE EDITOR

Readers' Aid

Perhaps one of your readers can help me locate a schematic or instructions on a Philco Model 7030 Dynamic tester. I think it is used for signal tracing, but the people at Philco say that manuals are no longer available. If someone can send me a copy I will be glad to pay the cost.

IRVING KOHN

Anchor Electronics
300 Valley St.
Sausalito, Calif. 94965

I enjoy your magazine very much and I am writing in hopes that one of your readers can help me. I am trying to obtain the latest roll chart and/or operating manual for a Simpson Model #330 tube tester. I am willing to pay a reasonable price.

JOHN D. TRIPLETT

39474 Blue Fin Way
Fremont, Calif. 94538

I have been a subscriber to ELECTRONICS TECHNICIAN/DEALER for many years and found it very helpful. But now I have a special problem. I need a schematic and manual for an Eico Model 400 scope. I have tried everywhere. Maybe one of your readers has information on this unit.

R. BERTRAN

425 W. 25th St.
New York, N.Y. 10011

I have a Test-O-Matic tube checker made by Shell Electronics Mfg. Corp. of Westbury, N.Y. There are no numbers on it, but a supplementary chart showed Model 18. As this corporation is no longer in business, perhaps you or one of your readers can help me get a tube chart for it.

WILLIAM A. GRAUNKE

5933 Old Redwood Hwy.
Santa Rosa, Calif. 95401

I hope one of your readers can help me. I have been looking for a schematic of an old GE AM/FM/SW radio receiver, Model X415 built in 1948. I am also looking for a schematic of a Japanese AM/FM transistor radio, Royal-Model 300. Any help would be appreciated.

JAMES WAHL

414 Superior Ave.
Crystal Falls, Mich. 49920

We have a Schaub-Lorenz radio in for repair and cannot obtain parts for it. The manufacturer is located in West Germany. Possibly you or your readers can supply us with information on this unit. Your assistance is deeply appreciated.

STANLEY J. PEPERA

Video TV & Appliance
717 Gratiot Ave.
Saginaw, Mich. 48602

I have a Hi Fi system I would like to sell and to do so, I need some information on it. It was made by Stan White, purchased from Leonard Radio in New York and called the Esquire. It was built in 1957 or 1958. I would appreciate any information your readers can furnish on this system.

RICHARD G. RAPP

33 Wyoming St.
Commack, N.Y. 11725

Perhaps one of your readers can help me obtain a schematic for the Weston Model 983 oscilloscope. A reply from the company indicates that it no longer makes scopes and cannot furnish any data. Also, my compliments on a magazine unsurpassed in its field.

THOMAS E. HAMBLIN

P.O. Box 82
King George, Va. 22485

We would like to obtain a schematic of the following TV sets and information on where we can get parts near the Chicago area. The set is a Rocket TV, Model No. 8-HL, Egawadenki Kenkyusho; Tokyo, Japan.

GEORGE KALEC

9033 S. Meade Ave.
Oak Lawn, Ill. 60453

I have a Webcor Model 152-5 phono player and I need a motor, part #15X229-5. It was ordered from Webcor but they said it was no longer available. Could one of your readers help me?

RICHARD WOLF


Box 155
Wishek, N.D. 58495

I would appreciate any circuit information on a Superior Model TV 50. Some tubes are missing and after writing several letters, I learned that Superior is no longer in business.

W. EVERETT SWIFT

160 Maskwonicut St.
Sharon, Mass. 02067

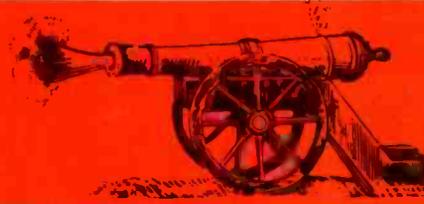For window-size blow-ups,
send 10c to Sprague Products Co.,
85 Marshall St., North Adams, Mass.
01247, to cover handling/mailling.
Order yours now, so you'll be able
to display it well before July 4th.



EVERY DAY IS 

INDEPENDENCE



DAY



FOR YOU AND YOUR
★ **INDEPENDENT** ★ ★
TV SERVICE DEALER



Your independent TV Service Dealer is in business for himself because he too wants to exercise his independence just as you do. You purchased your TV or radio set where you wanted to . . . when you wanted to . . . and at the price you decided was right.

Your TV service dealer is also an independent in the things he buys in his day-to-day work. He buys repair parts where he can get the highest quality and the best service. And, he trained himself in his own way, on his own time, at his own expense, to be able to do the very best for YOU.

He stands or falls on what you think of him and his work. He has to do good work to keep your business . . . and he knows it!

We're lucky in these United States that every day is Independence Day. Independent buying, selling, and servicing is the very lifeblood of American business. Let's keep it that way.

**THIS MESSAGE WAS PREPARED BY SPRAGUE PRODUCTS COMPANY,
DISTRIBUTORS' SUPPLY SUBSIDIARY OF SPRAGUE ELECTRIC COMPANY, NORTH ADAMS, MASSACHUSETTS FOR . . .**

YOUR INDEPENDENT TV-RADIO SERVICE DEALER

The Complete Line

FINCO[®] MATV EQUIPMENT

Get all your MATV needs from one reliable source. Use genuine FINCO MATV equipment and FINCO Color Spectrum Antennas. Free layout service. Write:

THE FINNEY COMPANY
34 W. Interstate Street, Dept. 110-5
Bedford, Ohio 44146

... for more details circle 119 on postcard

NEW FROM INJECTORALL



HERE'S PROOF!

PROOF that "SUPER 100" tuner cleaner is BETTER!

Tested by a leading independent laboratory against competitive products!

	SUPER 100	A	B	C
CLEANING	Excellent	Good	Fair	Fair
LUBRICATION	Good	Fair	Fair	Poor
PLASTIC ATTACK	None	None	None	None
FLAMMABILITY	None	None	None	None
CONDUCTIVITY	None	None	Slight	Slight
ANTI-STATIC PROTECTION	Excellent	Fair	Poor	Poor
DRIFT	None	Slight	Yes	Yes

SUPER 100 TUNER CLEANER . . . for COLOR and Black and White TV tuners 6 oz. spray can with INJECTORALL steel needle CAT. NO. 100-6 net \$2.10 Buy it at your Electronic Dealer. For free catalog on the complete line, write to:

INJECTORALL ELECTRONICS CORP.
Great Neck, New York 11024

... for more details circle 124 on postcard

ET/D

LETTERS TO THE EDITOR

My problem is obtaining a schematic for a Triplett TV-FM signal generator/marker Model 3434. Triplett was unable to supply it. Possibly one of your readers has one to loan me which I could have copied.

AVON BAUMAN & SONS
3255 Magnum Lanes
Atlanta, Ga. 30311

I would appreciate any information you can give me on finding a schematic for a GE Model OFM-1 oscillograph.

CHARLES F. BERRY
19202 2nd Ave. S.
Seattle, Wash.

Public Image

In my opinion the radio and TV technician has one of the worst jobs in the world. I am speaking from experience. My education began in high school when I took correspondence courses in communication electronics, communication engineering, black and white TV servicing, color servicing and built my own black and white and color sets. I have a first class radio-telephone license.

Fortunately I worked for the Post Office for the required number of years to enable me to retire. My pension is ample for my needs. However I love electronics and still do servicing, but only sets that are brought to me.

What burns me up is the public's image of the TV technician. The average person equates us on the same level as a grease monkey in a gas station. The nearest comparison of the type of work would be that of an electrician. However, the comparison in pay is pitiful. The electrician draws a wage of \$5 to \$10 an hour. He has no money invested in expensive testing equipment, he does not need schematics on every job he does and he does not need to keep up with the newest developments by reading technical magazines and books.

There is hope on the horizon with the new black and white and color sets using more and more solid state devices at the home, service will be confined to only the simplest troubles. Eventually the day of the half-trained tube technician will end. He will have the choice then of either upgrading himself through further study or find another job.

MATHEW RUSKOSKI
Pittsburgh, Pa.

"Gentlemen ...it's time to bring home the bacon."

Almost any company that's been doing business abroad has been doing well. That's good for you, your company and world business in general. But right now, your country needs those profit dollars to help reduce our balance-of-payments deficit. You can help by bringing home as much of that income earned abroad as you possibly can. Why not put the wheels in motion today? It'll give you a good feeling.



Published as a public service in co-operation with The Advertising Council and the Department of Commerce.

GE redesigns tubes to satisfy these tough customers before you get them!




Reach for this when you ask,
"What else needs fixing?"

Tube designers at General Electric work for a real *tough customer*. He's our design chief Chris McCool — a stickler for longer life and greater reliability in tubes for replacement use. If a production type can be made better, he'll see to it. His GE designers found a way to dissipate plate heat for less operating fatigue . . . resulting in longer life. They pioneered an improved cathode coating that resists flaking which used to cause shorts. Microphonics in horizontal output tubes were eliminated in another design. These are just a few examples of tubes redesigned by GE for your replacement needs. They're part of the "service designed" line — dependable tubes you can stake your reputation on. Stock up now at your GE distributor.

288-25

GENERAL  ELECTRIC



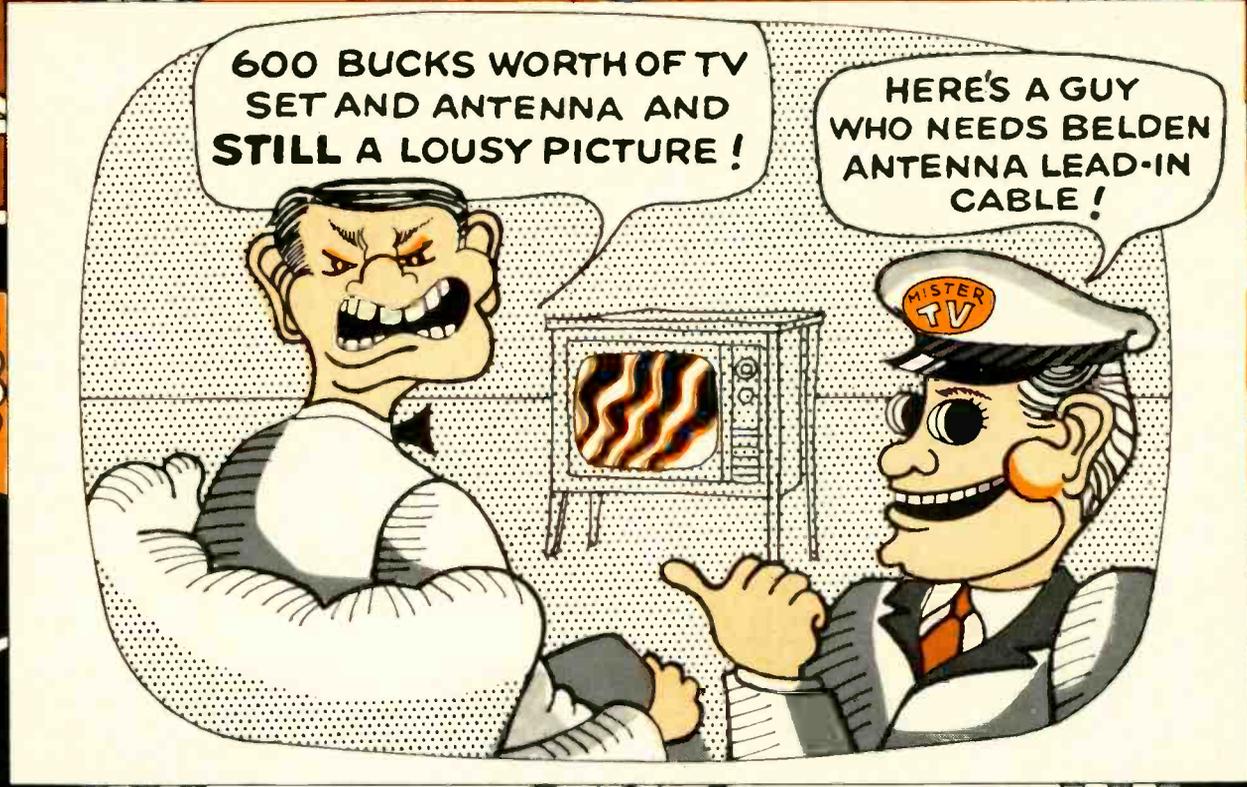

Color or UHF set perfect? Antenna perfect? Then obviously there's a missing link. Check that antenna lead-in cable. Old, worn-out, weather-beaten cable, or the ordinary flat ribbon kind designed for black and white VHF, causes more fuzzy, distorted pictures than you can count. It's your opportunity to upgrade these customers to a cable matched to their particular signal reception situations. One of Belden's Big Four—the link to perfect reception.

FOR CONGESTED AREAS...
8290 SHIELDED PERMOHM®



In congested, in-city areas, stray electrical interference and noise are at their worst. For perfect, all-82 channel reception—color or B/W—replace old cable with Belden's 8290 Shielded PermoHM. Its aluminum Beldfoil® shielding prevents pickup of ghost signals and electrical noise by the lead-in. Weather-proof and water-proof. You can tape it right to the mast. Or install it underground, in conduits—even in rain gutters.



AWG & (Stranding)	Color	Nom. O. D. (inch)	Nom. Velocity of Propagation	Nom. Capacitance (mmf/ft.)	Nom. Attenuation per 100'		Standard Package Lengths in ft.
					mc	db	
22 (7 x 30)	Brown	.305	69.8%	7.8	57	1.7	50', 75', 100' coils have terminals attached.
		x			85	2.1	
		.515			177	3.2	
		213			3.5		
		473			5.4		
		671			6.6		
		887			7.7	Available in counter dispenser.	
							250', 500' spool.

Copperweld, 2 conductors, orange polyethylene insulation and web between conductors, cellular polyethylene oval insulation, Beldfoil shield, stranded tinned drain wire, polyethylene jacket.

BELDEN 8285 - PERMOHM

FOR FRINGE AREAS...

8285 PERMOHM®

Antenna cable in uncongested or fringe areas picks up little electrical interference. But does get a lot of weathering, which degrades an already weak signal. These customers need encapsulated cable. Belden 8285 Permohm. Its special polyethylene jacket protects the energy field, regardless of weather conditions. It delivers the strongest signal of any unshielded twin lead under adverse conditions. Requires no matching transformers and connectors. For all 82 channels, color or B/W.



AWG & (Stranding)	Color	Nom. O. D. (inch)	Nom. Velocity of Propagation	Nom. Capacitance (mmf./ft.)	Nom. Attenuation per 100'		Standard Package Lengths in ft.
					mc	db	
22 (7 x 30)	Brown	.255 x .468	73.3%	5.3	100	1.4	50', 75', 100' coils have terminals attached. Available in counter dispenser. 250', 500' coils and 1000' spool.
					300	2.8	
					500	3.8	
					700	4.8	
					900	5.6	

Copperweld, 2 conductors parallel, orange polyethylene insulation and web between conductors, cellular polyethylene oval jacket.

FOR LOCAL BLACK AND WHITE...

8275 CELLULINE®



BELDEN 8275 CELLULINE 75 OHM UHF TRANSMISSION LINE PA1 NOS 278275

Cracked, corroded, weathered cable, full of dirt and moisture, loses signal strength; prevents any TV set from delivering a quality picture. Upgrade B/W VHF and local UHF customers to Belden 8275 Celluline. Performance is improved because all possible moisture between conductors has been eliminated. Abrasion-resistant and weather-resistant for a long, long service life. And, it requires no end sealing.

AWG & (Stranding)	Color	Nom. O. D. (inch)	Nom. Velocity of Propagation	Nom. Capacitance (mmf./ft.)	Nom. Attenuation per 100'		Standard Package Lengths in ft.
					mc	db	
20 (7 x 28)	Brown	.300 x .400	80%	4.6	100	1.05	50', 75', 100' coils in counter dispenser. 250', 500', 1000' spools.
					200	1.64	
					300	2.12	
					400	2.5	
					500	2.98	
					700	3.62	
					900	4.3	

Bare copperweld; 2 conductors parallel, polyethylene jacket with inert gas filled unicellular polyethylene core.

BELDEN DUOFOIL

FOR MATV AND CATV...

8228 DUOFOIL® COAX

Got an apartment or townhouse complex in your area? Motels or hotels? Or is CATV coming? Use Belden's new 75 ohm coaxial cable—8228 Duofoil. Shielding is 100%—sweep tested 100%. Spiral wrapped drain wires provide long flex life. Small diameter saves space in conduit installations. Use Duofoil for all coaxial color and B/W VHF, UHF and CATV applications.



AWG & (Stranding)	Color	Nom. O. D. (inch)	Nom. Velocity of Propagation	Nom. Capacitance (mmf./ft.)	Nom. Attenuation per 100'		Standard Package Lengths in ft.
					mc	db	
18 Solid, Bare	Black	.242	78%	17.3	50	1.5	100', 500', 1000' spools.
					100	2.1	
					200	3.1	
					300	3.8	
					400	4.5	
					500	5.0	
					600	5.5	
					700	6.0	
					800	6.5	
					900	6.9	

Don't forget to ask them what else needs fixing.

See your local Belden distributor for full details or to order. For a free copy of the recent reprint article, "Electronic Cable," write: Belden Corporation, P.O. Box 5070-A, Chicago, Illinois 60680.

BELDEN

8-6-84

... for more details circle 109 on postcard

ADMIRAL

Polyester Film Capacitor Identification

Many current Admiral electronic products use a rectangular green plastic capacitor with both leads at the bottom. Polyester film such as Du Pont's Mylar is used as the dielectric.

Some capacitors of this type have the value printed on the case (.01, 0.02, etc.); others have the value printed in code. The code consists of the first two digits of the picofarad value plus a digit indicating the number of zeros that follow. For instance: 223 is 22000pf or .022 μ f, 103 is 10000pf or .01 μ f, etc.


The letter M or K indicates tolerance: M is 20 percent, K is 10 percent. The working voltage and vendor code also appear on many. Most of this type that we have seen have this information arranged on four separate lines.

Radio Chassis 24A5/24A5A—Overheating Resistors

Increasing the tolerances of components and high line voltage can cause failure of resistors R48, R100, R106 and CR2. If you find these resistors overheating, replace R106 with a 47 Ω , 1w, 60B14-470; R100 with a 220 Ω , 1w, 60B14-221; R48 with an 82 Ω , 1/2w, 60B8-820. Check CR2 and replace if shorted. All three resistors must be changed at the same time. Kink the leads to hold them off the board.

Radio Chassis 13H1—Audio Distortion

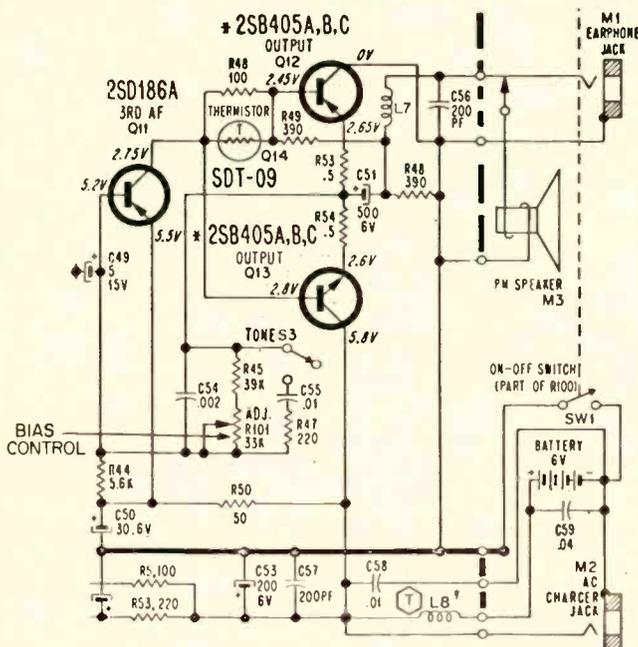Audio distortion on the model Y847R radio using the 13H1 chassis may be caused by a defective bias control, R101, 2075B89-50. This small control is located on the




circuit board just to the left of the speaker magnet. If the control is defective, moving it usually causes the distortion to be intermittent. The problem is a poor connection where the lug is riveted to the control element—we suggest replacement of the control. The replacement control must be adjusted according to the procedure given in service

manual S1214—if it isn't, you may still have distortion or high current drain.

21HJ5 Horizontal Output Tube Replaced by 21JV6

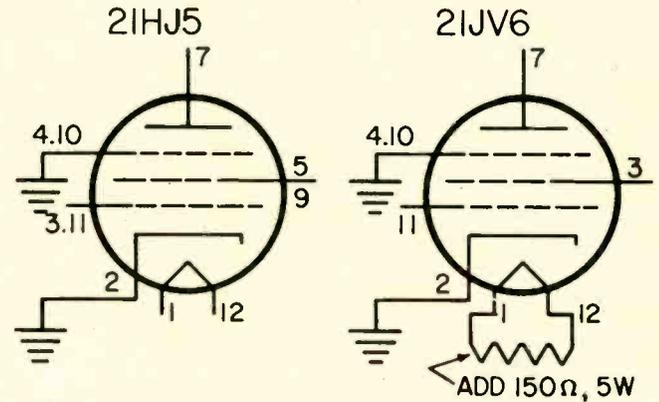The 21HJ5 tube used for horizontal output in the monochrome TV chassis covered by service manuals S924, S955, S956, S957 and S971 is no longer available. The



13GB5 tube, which replaced the 21HJ5 in later runs of these chassis, has been suggested as a substitute. However, this substitution required changing the tube socket and other components. We can now supply the 21JV6 which will replace the 21HJ5 with only slight rewiring of the original socket and the addition of a resistor across the heater.


To replace the 21HJ5 with a 21JV6: (1) Remove leads from pin 3 and connect to pin 11. (2) Remove leads from pins 5 and 9 and connect to pin 3. (3) Add a 61C20-44 (150 Ω , 5w) resistor between pins 1 and 12. In areas with low line voltage, this resistance may be increased to 180 Ω (do not exceed 180 Ω).

The following chassis may have used the 21HJ5: 16L3B,C; 16UK3B,C; 16UA4C,D; 16UE4C,D; 16UL3B,C; 16M3B,C; 16B4C; 16F4U; 16P3B; 16UM3B,C; 16UB4C; 16G4U; 16K3B,C; 16A4C,D; 16E4C,D.

The 21JV6 tube is available through an Admiral distributor.

TV Chassis TG2-2/9in. TV—Vertical Hold Problem

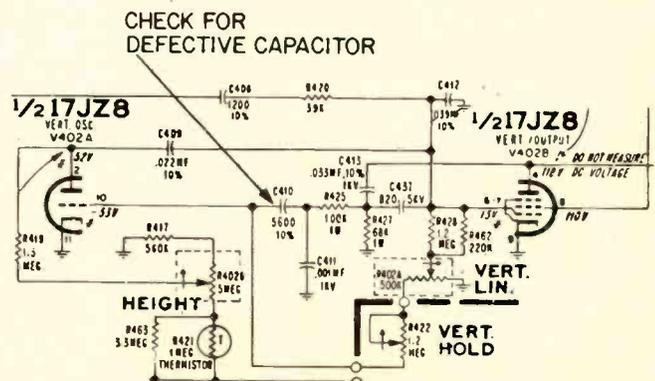If the picture in a 9in. TV set will not roll down with the vertical hold control and it acts like a linearity control, check for a defective C410, a 5600pf capacitor in late




production models, connected to the vertical oscillator grid.

The part number of this capacitor is incorrectly listed in S1044E as 65C80-56; please change it to 65C80-78. We are temporarily substituting the previously used capacitor, 65C80-25 (4700pf).

MAGNAVOX

Tape Model 1V9022—Battery Installation Recorder

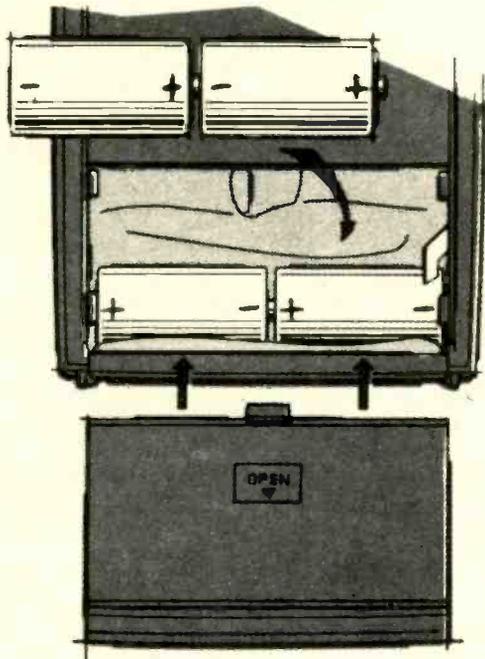Reports indicate the "C" size battery cells have been installed incorrectly in the field as a result of misreading the




battery outline provided on the plastic pull-out tab. This will result in jamming of the tape in the PLAY or RECORD positions.

RCA VICTOR

Portable Clock Radio Model RZS—Transistor Clock Circuit

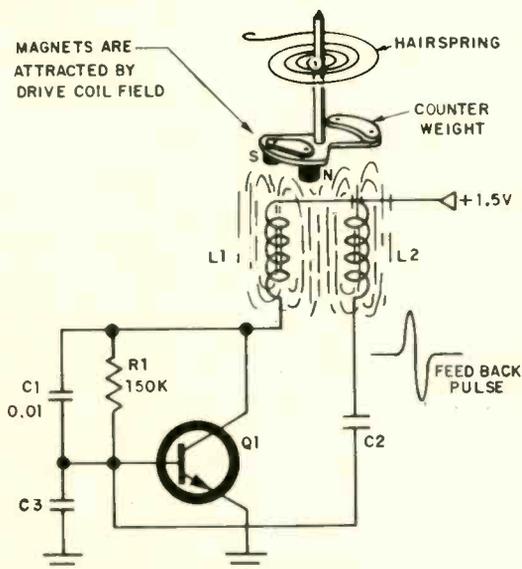Two portable clock radios in this year's product line, the RZS 43 and RZS 45, employ an interesting transistor



circuit to drive the clock mechanism. The transistor clock circuit closely resembles a blocking oscillator. In place of

Continued on page 88

Speedy solutions to servicing problems from LECTROTECH



ONE YEAR WARRANTY

TT-250 Transistor Analyzer

GOOD/BAD TRANSISTOR TESTING IN OR OUT OF CIRCUIT

Now—positive Good/Bad in-circuit and out-of-circuit testing. Also tests diodes and rectifiers. In-circuit testing measures dynamic AC gain. No transistor leads to unsolder or disconnect. Out-of-circuit testing measures transistor Beta on 2 scales: 0 to 250 and 0 to 500. Automatic biasing . . . no calibration required. PNP or NPN determined immediately. The TT-250 measures transistor leakage (Icbo) directly in micro-amperes and, for diodes and rectifiers measures reverse leakage and forward conduction directly to determine front-to-back ratio. Simple Good/Bad test instantly determines condition of power transistors. Panel has Power Transistor Socket. Measures leakage current of transistor electrolytics at test voltage of 6 volts. Size 10½" x 7" x 4". Wt. 5½ lbs. NET \$87⁵⁰

For Color and Black & White



ONE YEAR WARRANTY

CRT-100 Picture Tube Analyzer

Features line voltage adjustment to insure all tube voltages are correct regardless of line voltage. Critical Grid-to-Cathode Leakage is read on sensitive meter for greatest accuracy. Leakage in all other elements indicated on neon lamp. Tests all black and white and all color tubes for leakage, shorts and emissions and tests each color gun separately to a standard set of test conditions. With variable G-2 voltage, each grid is normalized to a reference cut-off voltage. This method, used by tube manufacturers, simulates tube performance in color receiver. Rejuvenates, removes shorts from picture tubes for increased brightness and tube life. Life expectancy test predicts remaining useful life of all type picture tubes. Complete with Plug-in Type Test Cables and Set-up Chart. NET \$89⁵⁰



See your distributor or write DEPT. ET-5

LECTROTECH, INC.

4529 N. Kedzie Ave., Chicago, Illinois 60625

... for more details circle 127 on postcard

B&K
puts
an end
to
test
equipment.

Business today has become an extremely complex, sophisticated operation. From mining to space research, man continually strives to develop more advanced methods for getting the job done faster, easier, better, and economically.

To keep pace with these developments, B&K has stopped making test equipment. In its place, we've developed "Diagnostic Silent Partners" ... a series of professional equipment that opens up a whole new concept in the field of electronic servicing. The "Silent Partners" are more than just ordinary pieces of test equipment. They're Insurance Analysts, Marketing Consultants, Customer Relations Specialists, Stockbrokers, Profit Coordinators ... *they're everything you need to make your business a success!*

For years now, B&K has been hailed by service engineers everywhere as the leader in electronic servicing equipment. We like that kind of reputation—and we aim to keep it! But we're realistic. We know that in order to maintain our reputation, we have to do more than just manufacture top-quality test equipment. We know that our diagnostic equipment must not only work flawlessly, but must also stimulate your sales and promote customer confidence in your abilities as a professional service

engineer. That's why we designed the "Silent Partners."

Look at the B&K 465 CRT Rejuvenator/Checker, for example. We call it the "Customer Relations Specialist." Why? Because of its special ability to consistently create repeat customers. It actually shows the customer, right in his own home, the true condition of his picture tube. This not only boosts new tube sales; but it also instills confidence in your integrity and ability. The result... *a satisfied customer for life!*

So, if you're looking for just ordinary test equipment, don't bother with B&K. But, if you're looking for outstanding diagnostic equipment that will improve your service and make it more profitable, get in touch with your nearest B&K distributor.



B & K, Division of DYNASCAN CORPORATION
180 1/2 W. Belle Plaine • Chicago, Illinois 60613
Where electronic innovation is a way of life.

... for more details circle 107 on postcard

Silent Partner 465
Rejuvenator/Checker



Silent Partner 1450
Oscilloscope/Vectorscope



Silent Partner 177
Professional VTVM



Silent Partner 1245
Color Generator



Silent Partner 1077
Television Analyst

Silent Partner 415
Sweep/Marker Generator



We've developed Silent Partners.

ET/D BOOK REVIEWS

99 WAYS TO IMPROVE YOUR TV RECEPTION, by *Len Buckwalter*, published by *Howard W. Sams & Co.* 128 pages, 5½ x 8½. \$2.95.

This book discusses antennas, lead-ins, boosters, rotators, couplers, interference and improvements. It explains ways of improving on the basic antenna installation and covers such things as proper grounding, antenna orientation and interference. The chapter on lead-ins explains the var-

ious types, when they should be used, why and how to install them with subsequent information detailing installation practices and improvements to the TV, antenna and lead-in. The book covers most of the areas concerned with proper TV reception including some practical hints on color adjustments. Since the information is aimed toward the customer, the dealer may find it a welcome addition to his book sales rack as a customer education work.

ADVANCED AND EXTRA-CLASS AMATEUR LICENSE HANDBOOK by *Howard S. Pyle*, *W7OE*, published

by *Howard W. Sams & Co., Inc.* \$3.95 paperback.

This timely handbook answers the needs of amateurs with General, Conditional and Technician class licenses for a study guide to higher class licenses. The book is written by a man who knows what amateur radio is about because he has been at it for 60 years. It is divided into 13 chapters covering all of the necessary subjects such as RF oscillators, power supplies, modulation, advanced RF theory and many others. The later chapters get into actual study material for the advanced and extra class licenses with a section devoted to typical questions and answers. Amateurs and technicians alike will find this handbook a useful reference for communications electronics.

Image Builder.



B&K 1245 Station Quality Color Generator

Thanks to color television, you're working in a vastly expanded market. It's highly competitive; and you have to do a first-rate job to stay on top of your competition. That's why B&K developed the 1245 Color Generator. It's the "Silent Partner" that makes a good impression. One that sells your customer on you and builds your image as a top-notch professional technician.

The B&K 1245 Portable Color Generator is the leader in the service industry. No other color generator on the market can compare in quality and performance.

All solid-state, the 1245 offers instant operation in all service environments. It eliminates waiting, warm-up, or adjustment. And you receive the brightest, cleanest patterns possible.

Being fully portable, the 1245 has only two front-panel controls for ease of operation—AC power/color level and

pattern selector. Station-quality waveforms provide complete protection against obsolescence. A well-defined back porch on the horizontal sync pulse makes it easier to converge the color tube. And the built-in gun killer works on any picture tube, both foreign and domestic.

So if you're looking for a portable color generator that can solve color servicing problems fast, the B&K 1245 is your answer. It's not just a color generator. It's a "Silent Partner," designed to give you more time to create new sales by cutting servicing time to a minimum.

B&K Color Generator.
Model 1245. Net: \$134.95.

B&K Division of Dynascan Corp.
1801 W. Belle Plaine
Chicago, Illinois 60613

B&K puts an end to test equipment.
We've developed Silent Partners.



... for more details circle 108 on postcard

ELECTRONICS REFERENCE DATABOOK by *Norman H. Crowhurst*, published by *TAB Books, Inc.* 232 pages, over 100 illustrations, 45 tables. \$7.95 hardbound, \$4.95 paperback.


In going through this reference book, the ten chapters devoted to everything from basic units to transmission lines appear quite thorough. In most cases the charts are preceded by a brief explanation of applications, background information and source. It does get deep in one particular area where the book discusses the "J" operator used in design calculations, and most likely a technician would find this portion of no interest. However, for the most part the tables, graphs and formulas are pertinent to electronic technicians. The book also includes tables of line losses, information on FET's, IC's, vacuum tubes and other material not normally found in one source.

College tuition covers only about 1/3 the cost of a college education.
Help supply the other 2/3.

GIVE TO THE COLLEGE OF YOUR CHOICE.



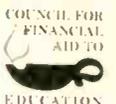advertising contributed for the public good



AID TO HIGHER EDUCATION CAMPAIGN

More than 5 million two-way transmitters have skyrocketed the demand for service men and field, system, and R & D engineers. Topnotch licensed experts can earn \$12,000 a year or more. You can be your own boss, build your own company. And you don't need a college education to break in.

HOW WOULD YOU LIKE to earn \$5 to \$7 an hour... \$200 to \$300 a week... \$10,000 to \$15,000 a year? One of your best chances today, especially if you don't have a college education, is in the field of two-way radio.

Two-way radio is booming. Today there are more than five million two-way transmitters for police cars, fire trucks, taxis, planes, etc. and Citizen's Band uses—and the number is growing at the rate of 80,000 per month.

This wildfire boom presents a solid gold opportunity for trained two-way radio service experts. Most of them are earning between \$5,000 and \$10,000 a year *more* than the average radio-TV repair man.

Why You'll Earn Top Pay

The reason is that the U.S. doesn't permit anyone to service two-way radio systems unless he is *licensed* by the FCC (Federal Communications Commission). And there aren't enough licensed experts to go around.

This means that the available licensed expert can "write his own ticket" when it comes to earnings. Some work by the hour and usually charge at least \$5.00 per hour, \$7.50 on evenings and Sundays, plus travel expenses. Others charge each customer a monthly retainer fee, such as \$20 a month for a base station and \$7.50 for each mobile station. A survey showed that one man can easily

maintain at least 15 base stations and 85 mobiles. This would add up to at least \$12,000 a year.

How to Get Started

How do you break into the ranks of the big-money earners in two-way radio? This is probably the best way:

1. Without quitting your present job, learn enough about electronics fundamentals to pass the Government FCC License. Then get a job in a two-way radio service shop and "learn the ropes" of the business.

2. As soon as you've earned a reputation as an expert, there are several ways you can go. You can move out, and start signing up your own customers. You might become a franchised service representative of a big manufacturer and then start getting into two-way radio sales, where one sales contract might net you \$5,000. Or you may be invited to move up into a high-prestige salaried job with one of the same manufacturers.

The first step—mastering the fundamentals of Electronics in your spare time and getting your FCC License—can be easier than you think.

Cleveland Institute of Electronics has been successfully teaching Electronics by mail for over thirty years. Right at home, in your spare time, you learn Electronics step by step. Our AUTO-PROGRAMMED® lessons and coaching by expert instructors make everything clear and easy, even for men who thought they were "poor learners."

Your FCC License... or Your Money Back!

By the time you've finished your CIE course, you'll be able to pass the FCC License Exam with ease. Better than nine out of ten CIE graduates are able to pass the FCC Exam, even though two out of three non-CIE men fail. This startling record of achievement makes possible our famous FCC License Warranty: you'll pass the FCC Exam upon completion of your course or your tuition will be refunded in full.

Find out more. Mail the bound-in post-paid card for two FREE books, "How To Succeed In Electronics" and "How To Get A Commercial FCC License." If card has been detached, use coupon below.

ENROLL UNDER NEW G.I. BILL

All CIE courses are available under the new G.I. Bill. If you served on active duty since January 31, 1955, or are in service now, check box on card for G.I. Bill information.

CIE Cleveland Institute of Electronics

1776 East 17th Street, Cleveland, Ohio 44114

Please send me without cost or obligation:

1. Your 44-page book "How To Succeed In Electronics" describing the job opportunities in Electronics today, and how your courses can prepare me for them.
2. Your book on "How To Get A Commercial FCC License."

Name _____ Age _____

(PLEASE PRINT)

Address _____


City _____ State _____ Zip _____

Accredited Member National Home Study Council ET-51

How to get into one of today's hottest money-making fields—servicing 2-way radios!



He's flying high. Before he got his CIE training and FCC License, Ed Dulaney's only professional skill was as a commercial pilot engaged in crop dusting. Today he has his own two-way radio company, with seven full-time employees. "I am much better off financially, and really enjoy my work," he says. "I found my electronics lessons thorough and easy to understand. The CIE course was the best investment I ever made."

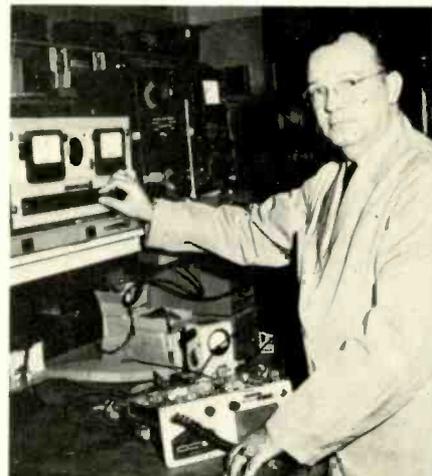

Business is booming. August Gibbemeyer was in radio-TV repair work before studying with CIE. Now, he says, "we are in the marine and two-way radio business. Our trade has grown by leaps and bounds."

Every minute is longer up there.

You can save as many as 20 or 30 of those long minutes when you put up one of our larger antennas, because they're pre-assembled. Our snap-joints take only seconds to lock in place.

Sylvania antennas are equipped with a double boom (for strength and rigidity).

All have strong, seamless, half-inch tubular elements (not rolled-over strips of aluminum).

All aluminum parts are gold-alo-

dized inside and out (not sprayed, but dipped)

Even more care goes into the electronics.

We've peaked our antennas for flat response over the entire 6 MHz bandwidth of each TV channel. Flat response is absolutely necessary for good color reception. Otherwise, color rendition may be lost.

You also need high gain—that's obvious. But coupled with high directivity to knock out interference. Polar

patterns from our antennas show almost complete rejection of signals from the rear and sides.

We designed our antennas so you wouldn't have to (1) climb back up there or (2) fiddle around up there.

We know that the fiddler on the roof is just fiddling his own money away.

For more information on our line of antennas see your Sylvania distributor.

SYLVANIA
GENERAL TELEPHONE & ELECTRONICS



**Here's where we
can save you time.**

Signal Strength Meters

If you install antennas, MATV systems
or troubleshoot TV 'front-ends,'
you should consider the use
of a signal strength meter (SSM)
as a basic aid to increase
efficiency and profit

■ The installation of a TV antenna has for years followed a rather standard pattern—not referring to the nuts and bolts of putting up towers, guy wires and the like, but in the method used to aim the antenna for the best signal. The technician normally turns the antenna for the best picture and the customer is happy. Some technicians use a portable TV on the roof and this system works fine for a simple home TV installation.

But if you install MATV systems, you need an instrument that will tell you when you have the antenna set for the best possible signal. MATV systems are gaining popularity with motel operators, hotels, resorts and now, home owners. It's a big market and one that many service-dealers are getting into because it is a natural for an existing TV sales and service business.

USES FOR AN SSM

However, a typical MATV installation can cost hundreds of dollars. When you sell one, you want to be sure it is installed correctly. That means you will need the proper tools — a portable signal strength meter is one of the most useful. Besides using it to set antenna for maximum signal direction, it is invaluable in checking distribution amplifier gain, line losses and other branches of the installation critical to an efficient system.

The signal strength meter can also be used when bidding on complex MATV systems,

such as used in motels and apartment buildings. First use the meter to take an initial survey of the signal strengths available in the area. This can be done by taking a reading of the available channels with the meter connected to an existing antenna or by using a portable antenna of your own. Some service-dealers have crank-up antennas and towers mounted right on their service vehicles for this purpose. With an idea of the local signals, you can then take the antenna combination you propose to install and establish amplifier, tap-off and splitter requirements with nothing left to guesswork.

In your shop, an SSM can be used to measure hum modulation in TV amplifiers, pre-amplifiers and front-ends. You will be able to determine noise figures, signal-to-noise ratio and gain. You can also make performance and frequency response evaluations in other passive and active equipment operating in the VHF, FM and UHF ranges. And since SSM units are portable, their applications easily extend to field use.

In the customer's home you will find a signal strength meter invaluable for precisely tuning 300Ω twinlead traps for the elimina-

TEKLAB REPORT . . .

The Packard Bell color tv set scheduled for coverage in this month's Teklab report was not received in time to permit the report to be included in this issue.

Signal Strength Meters ...

tion of frequency interference. The meter will also provide a rapid and positive indication of whether a problem of signal loss is in the TV set, the antenna, preamplifier or the distribution system. This is easily checked by comparing readings on the meter with the values in db that you know should exist at specific locations in the system.

HOW AN SSM WORKS

Basically, an SSM (signal strength meter) is a sensitive tunable RF microvolt meter. For TV applications it is normally calibrated to indicate microvolts or decibels (dbmv) of average composite signal developed across a 300 or 75Ω load. (Fig. 1) Not all SSM me-

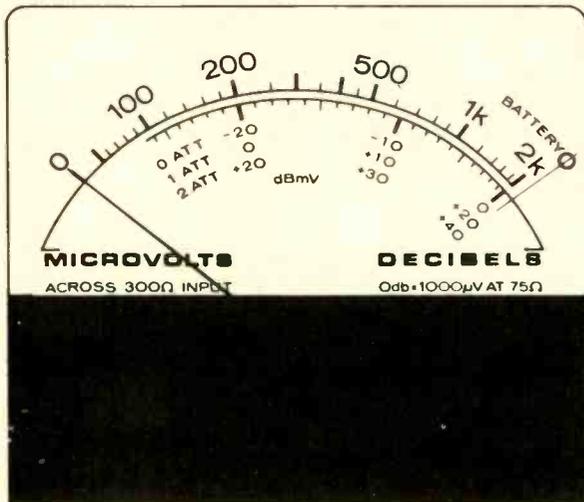


Fig. 1--Typical signal strength meter face reads dbmv and microvolts.

ters indicate average signal, some read peak.

In simplified form, the SSM has a receiving antenna, a tuning circuit and a diode detector in series with a microammeter. (Fig. 2)

Capacitor, C2, would be of such value that the RC time constant resulting from its dis-

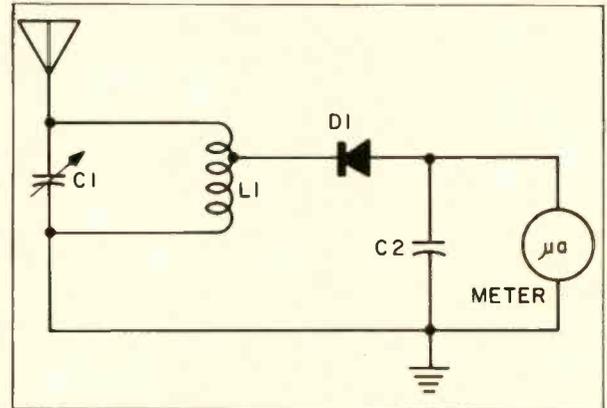


Fig. 2--Simplified schematic diagram of SSM circuit.

charge through the internal resistance of the meter would provide an indicated average of the detected composite signal level. However, this simplified circuit alone would not be adequate for accurate measurements of low signal levels. Amplification is required and the non-linearity of the diode would tend to produce erroneous meter readings. More elaborate SSM circuits of precision signal strength meters are shown in Fig. 3 and 4. The UHF and VHF sections have calibrated input attenuators to allow signal measure-

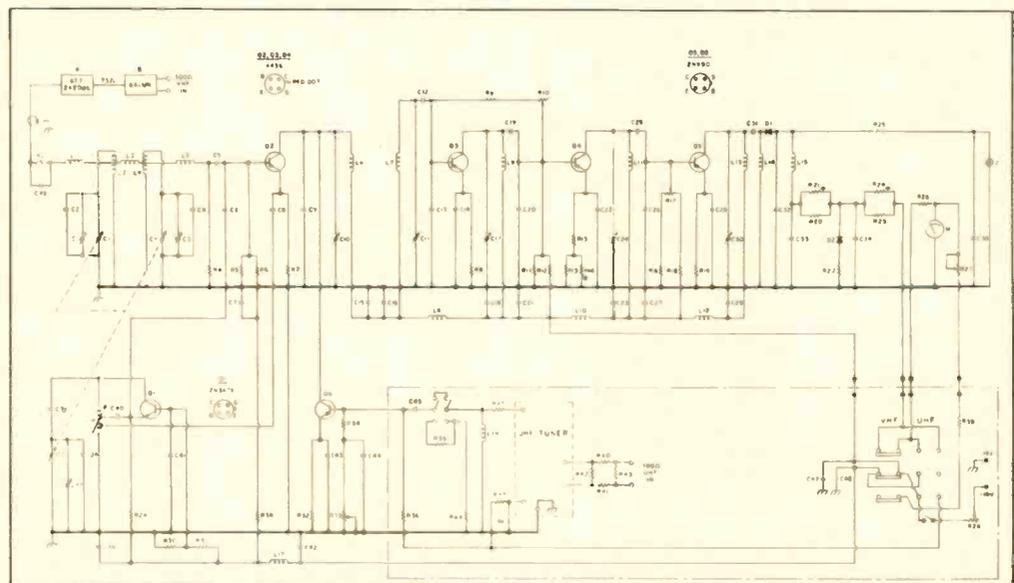


Fig. 3--Schematic diagram of SSM model 718 (Courtesy Jerrold).

Signal Strength Meters . . .

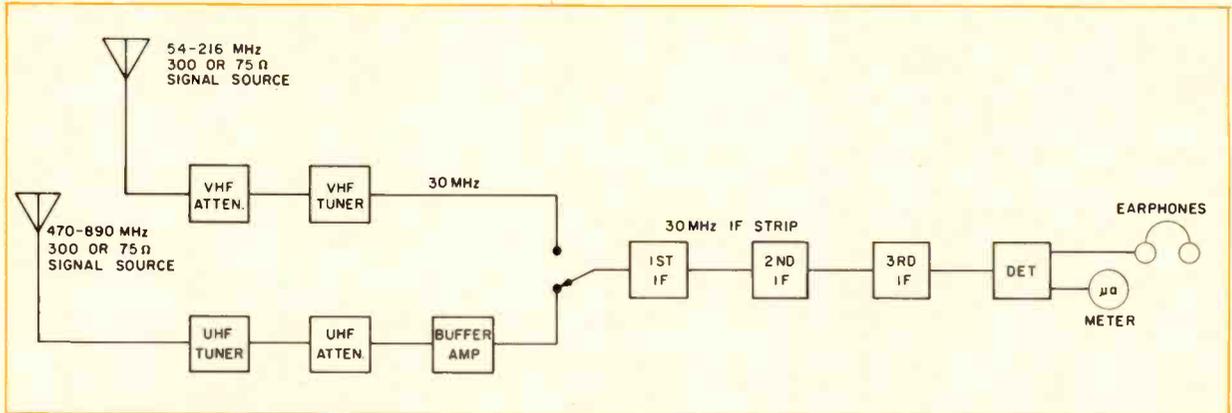


Fig. 5--Block diagram of SSM.

ings of the UHF and VHF average composite signal strength.

When using an SSM to check gain and loss in a MATV system, coaxial cable or twin lead is normally connected directly to the instrument and requires no special accessories. Some units have built-in matching transformers and input jacks for connecting either type of lead-in, others provide an external matching device.

However, for other measurements a probe is often necessary and can be easily made by attaching a standard test probe to one end of a low-loss shielded 75Ω cable and terminating the other end in a suitable connector.

To install the probe, a 1/2 in. section of shielding should be exposed, unwoven and all but a small group of adjacent strands eliminated. To these remaining strands of shielding solder a length of insulated wire with an alligator clip at the other end. This will serve as the ground connection to the chassis being tested.

The remaining free end of the test cable

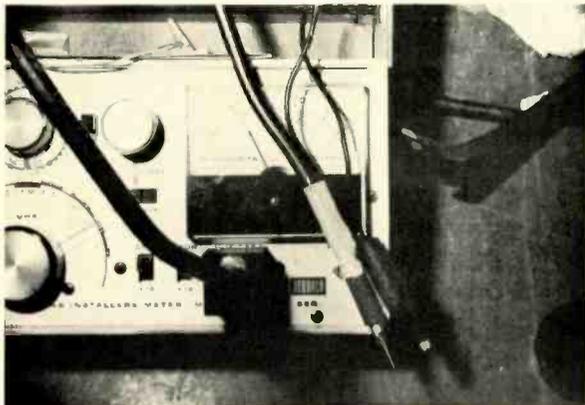


Fig. 6--Shows completed probe used for signal tracing.

should be trimmed back and an F59 or equivalent connector attached to it as shown in Fig. 6. This will permit insertion of the test assembly into the 75Ω VHF or UHF input terminal of the SSM. Some signal strength meters have a readily accessible detector output jack. After determining what type of plug it takes, an assembly can be made for visually monitoring this detector output with your oscilloscope. The connector for the scope end would, of course, depend upon the type of scope input.

UNDERSTANDING THE DECIBEL

The true amplification and gain of RF amplifiers and preamps with 300 or 75Ω input and output impedances such as used in MATV can be determined by doing a little figuring. But before you get excited about complicated formulas, bear in mind that a signal strength meter reads in dbmv and microvolts directly, so all of the data required for figuring voltage amplification, voltage gain and power gain is readily available. All you have to do is plug in the values.

You don't have to be a mathematician to handle the decibel, but you do have to start thinking with numbers of a different kind.

The most important thing to know about the decibel (db for short) is that it doesn't say "how much" or "how many" like the "10" in 10 dollars, it says "so many times." It's something like the word "twice." And, like "twice," it doesn't have any meaning in terms of quantity ("how much") unless you specify "so many times" *something*. For example, 6db always means (in voltage) "two times" or "twice as many."

The funny thing about the db is the non-linear relationship as shown in these examples.

6 db = 2 x	20 db = 10 x
10 db = 3.14 x	30 db = 31.4 x
12 db = 4 x	40 db = 100 x
18 db = 8 x	60 db = 1000 x

Notice that while 10db is approximately 3 x, 20db = 10 x. The gain is about three times greater by doubling 10db. But if you double 20db to get 40db, you get 100 x, which is 10 times greater. All this comes from the way the db is derived. And because of its behavior, it makes all kinds of systems figuring simple. It's best that you try to follow the reasoning behind the db. We will start with the following formula--and don't let it scare you.

$$\text{db} = 20 \log \frac{E_1}{E_2}$$

Saying it in English, it goes like this: The db is equal to 20 times the common logarithm of the major (larger) voltage divided by the minor (smaller) voltage. Solving it goes like this. Suppose we have an amplifier and want to find its voltage gain in db. Being an amplifier, its output will be larger than its input, so the output voltage is the "major" voltage. Divide the output by the input, the formula says, so let's assign some values. Say the output voltage is 100 and the input 10, then $100 \div 10$ equals 10. Now the formula is reduced to:

$$\text{db} = 20 \log 10$$

Now we have to find the common logarithm of 10. This is what causes most TV repairmen to gulp--they forgot their logarithms as soon as possible after leaving high school. But there's no mystery about the common log. The common log, or logarithm to the base 10, is only that little number that goes above and to the right of a number, the exponent, like in 10^2 ; but when used as the log, it is the exponent required to raise 10 to the number we have in mind.

As an example, 2 is the logarithm of 100, since 10 raised to the second power (10^2) equals 100. Now, every number we know can be expressed as a power of 10, and mathematicians have spent years compiling log tables to the tenth decimal place. In our particular problem, we have to find the exponent which makes 10 equal to the base of the common logarithm, which is also 10. This one's easy--it's 10^1 , so that the common log of $\frac{E_1}{E_2}$ equals 1. The formula

$$\frac{E_1}{E_2}$$

now looks like this:

$$\text{db} = 20 \times 1, \text{ and db (gain)} = 20$$

We have found out that the amplifier's gain is 20db. Of course, if we'd found a fractional number, like 18.5 when we divided E_1 by E_2 , we'd need a log table to find the common log of 18.5. This you will never need as long as you have a conversion chart handy which converts the ratio expressed by $\frac{E_1}{E_2}$ directly to db.

One of the puzzling things about the db is 0db. 0db isn't "nothing"--it's something. It's the same as saying "there is a relationship of one to one"--in other words no gain--no loss. It works out like this, and we can use the amplifier we had before, but now we find the input is 10v and the output 10v. The formula then looks like this:

$$\begin{aligned} \text{db} &= 20 \log \frac{E_1}{10 E_2} \\ &= 20 \log \frac{10}{10} \\ &= 20 \log 1 \end{aligned}$$

since 10 divided by 10 is 1.

The question now is what exponent will raise 1 to 10? This is a funny one, the logic of which has escaped mathematicians--they only know it works--look:

$$\begin{aligned} 10^2 &= 100 \\ 10^1 &= 10 \\ 10^0 &= 1 \\ 10^{-1} &= .1 \end{aligned}$$

We can see the sense behind the first, second and fourth expression, but the third only makes sense because it fits *and* works. Let's put it into the formula: $\text{db} = 20 \times 0$, and therefore the amplifier's gain is 0db.

This boils down to the fact that when we say 6db, we mean that we are talking about something which is twice as great as 0db, since 0db is one times and 6db is two times. The question always comes--"What's 0db?" The answer is--0db is anything you choose to make it! In audio, committees of engineers have assigned a value to 0db which they agreed upon. In TV systems you can specify what you like. It can be the antenna signal, for instance, or you can choose 1000 μ v read across 75 Ω impedance. This is a pretty good signal for a TV set.

The great advantage of using the db is that

Continued on page 90

Low Cost Solid-State 'Curve Tracer'

Build this tester to simplify servicing transistorized equipment

■ For a small cost, this transistor "curve tracer" can be built and connected to your present scope. This "go-no-go" test will save you many hours of servicing time. However, do not confuse this device with an instrument called a dynamic characteristic curve tracer which will give you the family of characteristic curves for operation of transistors.

To service transistor devices rapidly and positively, a scope tracer is employed to provide in-circuit as well as out-of-circuit testing of solid-state components. This is not a new testing method, only the application for fast servicing is proposed.

Basically, we are sweeping the junction of a transistor with 6.3vac so that it may be viewed on the scope conducting or not conducting during alternate plus or minus portions of the ac sinewave. This display can be observed on a regular service oscilloscope with no power applied to the transistor unit under test.

We are not so concerned about the intricacies of the waveforms obtained as we are in a "go" or "no go" type of check. Shown in Fig. 1 are some sample drawings of basic waveforms that will be obtained from pure circuit loads.

In Fig. 2 note the typically good semiconductor wave shapes - sharp, crisp trace junctions.


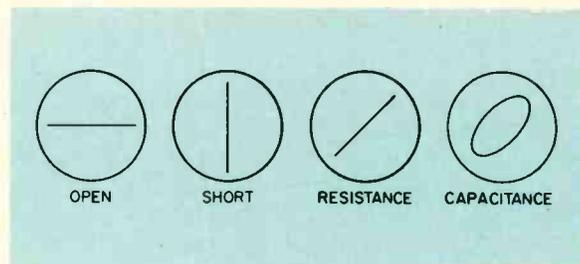


Fig. 1--Basic waveforms that are obtained from pure circuit load checks.

Fig. 2--Good semiconductor waveforms as they appear on the "curve tracer" CRT with sharp, crisp trace junctions.

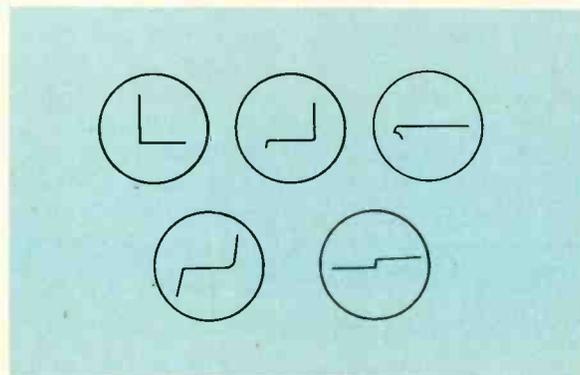

tions, or twins of the waveforms on the CRT.

In actual circuit applications, a combination of these two waveforms will be seen. Fig. 3 shows in-circuit waveforms. Capacitance and resistance may mask the true response; however, in the waveforms of a good transistor there will be a clue to a sharp junction or a current change. This is your clue to identify

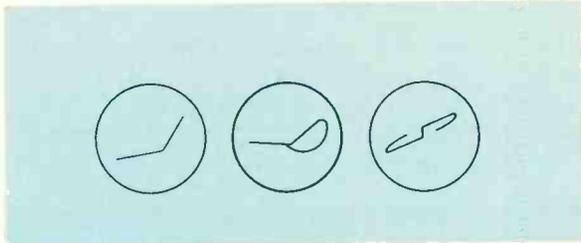


Fig. 3--In-circuit checks will display waveforms shown for a good semi-conductor or diode.

a good transistor or diode from a defective one.

A defective transistor will display three basically different scope patterns illustrated in Fig. 4. Notice the unsharp or rounded corner junction for a transistor that exhibits some leakage.

To completely check the transistor with a two-lead tester, three checks are made. Polarity of the leads is not important and the checks can be made very rapidly, from the emitter to collector, base to collector, or base to the emitter. You don't have to determine which test points are E, B, or C of


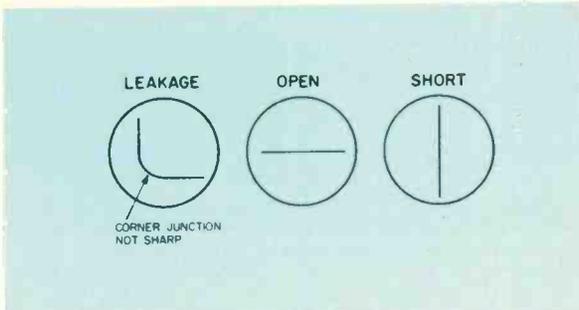


Fig. 4--Three basic waveforms produced by a defective transistor.

Fig. 5--Tests from the base to emitter or collector of a good transistor will produce typical diode waveforms shown.

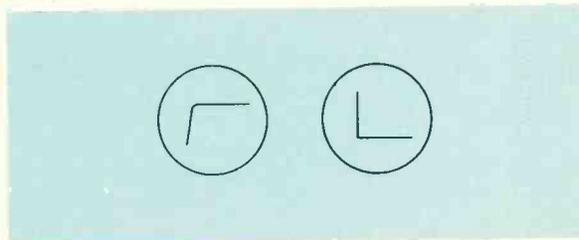

the transistor. Most base to emitter or collector tests of a good transistor will indicate a typical diode pattern as shown in Fig. 5.

At times, emitter to collector patterns may look like the displays depicted in Fig. 6 or the scope pattern may appear as an open condition as shown in Fig. 7, but the transistor will be good. Check as many different types of good transistors, so that you will know what waveforms to look for.

As you gain proficiency, it will be very easy

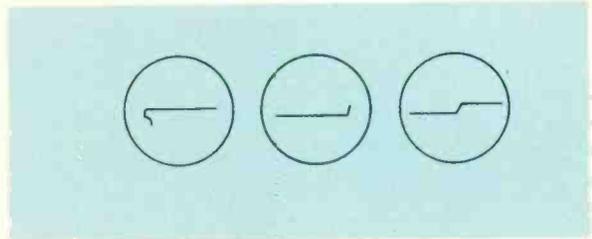


Fig. 6--Some emitter to collector waveforms will look like this.

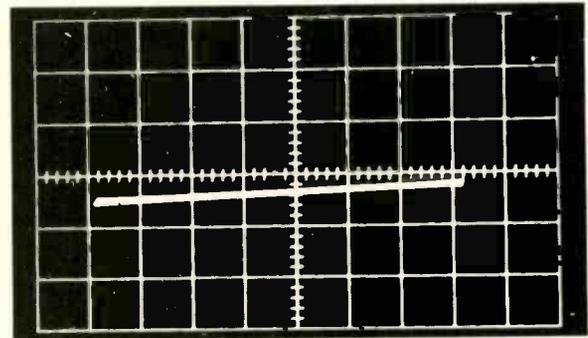


Fig. 7--A normal waveform taken from the emitter to collector of transistor.

to pick up the very difficult service problems, caused by installation of a wrong type transistor or the correct type installed incorrectly. A circuit test, emitter to collector, indicating a base to emitter or collector type pattern would expose this error.

Caution should be used on tests made on the unijunction transistor (G.E. type 5E29); a good device may look like a defective transistor with a leakage. The waveform will have a rounded curve. This tester would not be of value for unijunction checks and FETs would be ruined.

APPLICATION OF THE CURVE TRACER

The following are some advantages of the in-circuit quick tester: (1) enables the testing of equipment without power applied, (2)

'Curve Tracer' ...

rapid accurate servicing by a semi-skilled technician, (3) servicing without reference schematics is possible in many instances, (4) checks and confirms performance (except beta) of all semiconductors with only an additional equipment cost of less than \$8, (5) enables the service technician to repair equipment that he may not be familiar with, as well as equipment without technical infor-


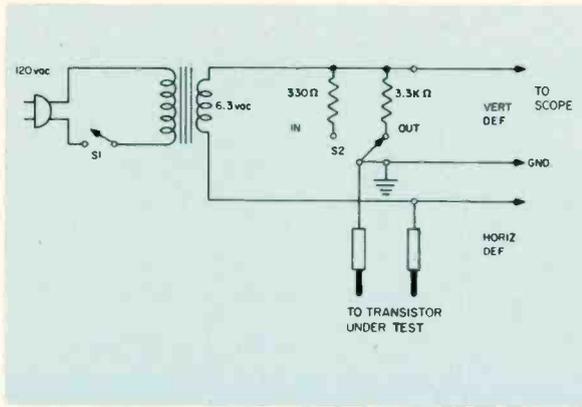


Fig. 8--Schematic of the transistor or diode tester.

Fig. 9--The complete setup of the oscilloscope and "curve tracer."

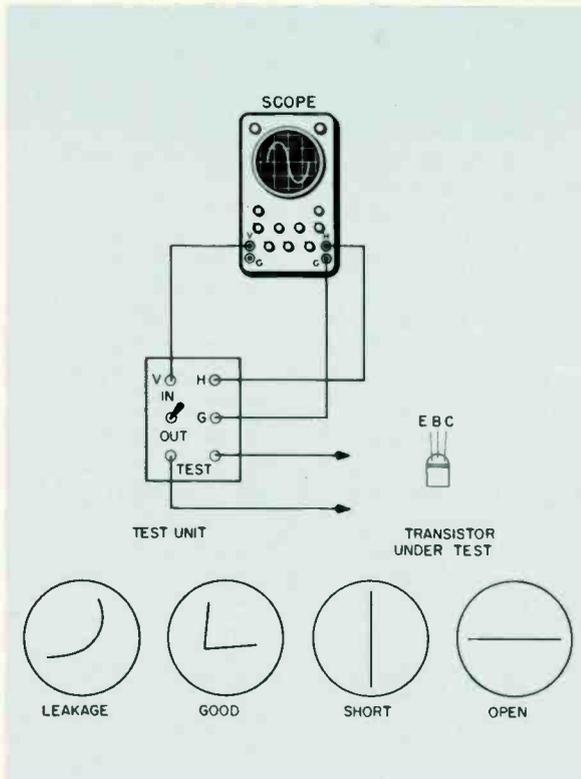

mation, (6) Diode checks can be made in the circuit along with the transistors (one defective diode can cause as much equipment malfunction as a defective transistor).

A speed check was made with this tester on a Motorola TS-915 solid-state color chassis. It contains more than 60 transistors and over 26 diodes but it took less than 20 minutes to check them all. One defective transistor was located and replaced, putting the set back into proper operation.

Fig. 8 shows the simple schematic for the in- or out-of-circuit transistor or diode tester. To calibrate this unit, without a load across

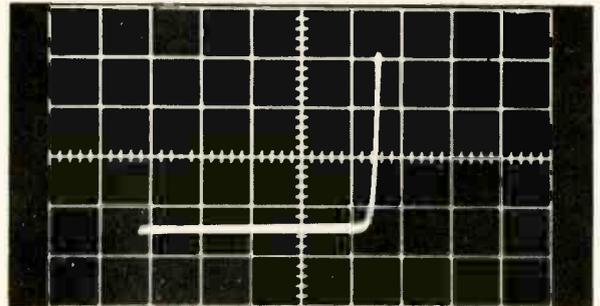


Fig. 10--Actual oscilloscope waveform showing a good transistor with probes connected from emitter to collector.


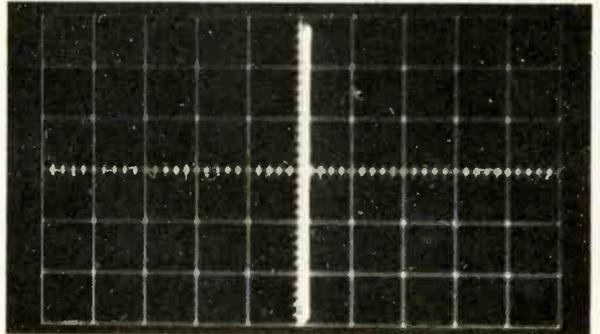


Fig. 11--Waveform showing a shorted transistor.

Fig. 12--Waveform showing an open emitter to base of the in-circuit transistor with a slight loop indicating capacitance in the circuit.

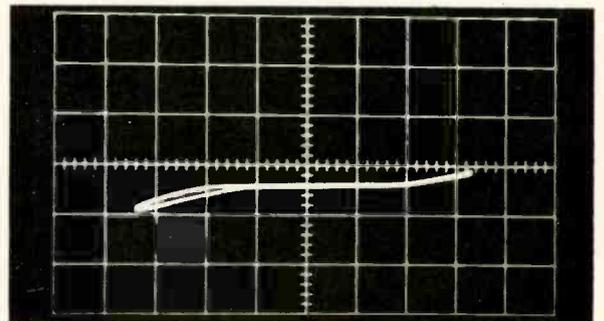

the test leads, adjust the scope's horizontal amplifier to scan about 3 in. of width. With the two test probes shorted, adjust the scope's vertical amplifier gain to scan a line about 3 in. high. Fig. 9 shows the complete setup of the oscilloscope and curve tracer.

The following are actual waveforms of transistors checked in the circuit:

In Fig. 10 a good transistor trace is shown with probes connected from emitter to collector, and a shorted transistor waveform is shown in Fig. 11. In Fig. 12 the waveform denotes an open emitter to base of the in-circuit transistor with a slight loop indicating

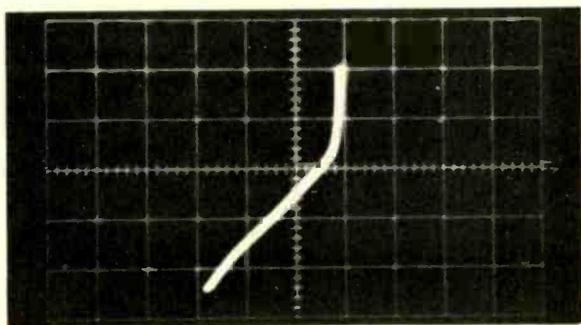


Fig. 13--Waveform showing transistor with base to collector leakage.


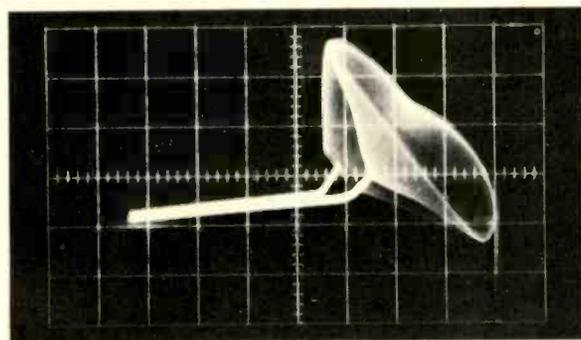


Fig. 14--A weird looking waveform taken from emitter to collector of a good transistor with inductance and capacitance in circuit.

Fig. 15--Waveform showing an intermittently shorted transistor producing a cross pattern waveform.

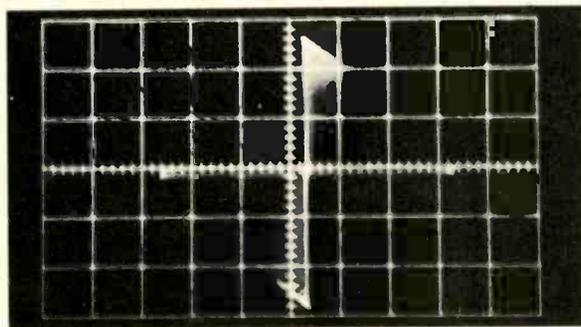

some capacitance in the circuit being checked.

Leakage is shown in the waveform of Fig. 13 measured from the base to collector of this transistor. However, the oscilloscope waveform in Fig. 14, showing a sharp bend, proved this transistor to be good. This semiconductor was in a circuit that contained both inductance and capacitance, but was detected by this tester. An intermittently shorted transistor is illustrated in Fig. 15 showing cross pattern waveform effect.

SERVICING SOLID-STATE STEREO EQUIPMENT

In most cases, a stereo amplifier will have two relatively identical channels. If the transistors are "even numbered" in the left channel then the same transistor should be found in the right channel with an even type number.

Troubleshooting this equipment can be done by comparing each "twin stage" response, enabling even an inexperienced technician to make a rapid diagnosis of either transistor or circuit component failure.

All stages of the amplifier can be checked and repaired before reinstalling the unit. In many cases, the repairs will be complete and a limited power test can be made with confidence. If the amplifier does not operate, use a scope, preferably with a dual-trace plug-in amplifier and signal trace, by comparing the left and right channel waveshapes.

MAKING STEREO CHECKS

- (1) Always make a complete visual check for burnt parts.
- (2) Use the touch and smell technique for indications of excessive heat even though burnt parts are not evident.
- (3) Make a complete visual check for indications of previous service repairs or damage.
- (4) Remember, always check transistors before installing and recheck transistors in-circuit after installation. Transistors can be damaged during installation or removal.
- (5) All diodes can also be checked rapidly along with the transistors.
- (6) Check the service tickets for other tips and clues as to what the trouble may be or call your stereo customer should more information be needed.

The "curve tracer" can also be used for continuity checks of the printed circuit foil for cracks or defective solder joints. Flex the board and watch the scope waveform for your point to point continuity test. Even shorted or open capacitors and coils can be located with this test method. ■



Color System Trouble Shooting

Familiarize yourself with the IC or 'chip'--you will be seeing more of them in the future

■ One of the most used controls on a color receiver is labeled HUE or TINT. This control is a part of the color synchronization circuit. The function of the control is to shift the phase of the 3.58MHz oscillator in the receiver so that the demodulator axes occur at the proper phase angles. This is accomplished by controlling the phase of the CW feed to the phase discriminator. By controlling the phase of the separated burst signal in the burst amplifier we can obtain hue control. In some circuits the plate tank coil of the burst amplifier is tunable. If the plate tank is tuned to 3.58MHz, the phase shift in the amplifier is zero (or 180deg). Tuning may be accomplished by a variable capacitor in shunt with the plate tank, or by a variable resistor in series with the tuning capacitance.

To adjust the tint control properly, the viewer looks at the picture and adjusts for proper flesh tones. When proper flesh tones are obtained, the demodulation axes are proper and the phase shift between the 3.58MHz oscillator and the transmitted burst signal is approximately correct.

With the NTSC (National Television System Committee) system a shift of more than 3 deg of the 3.58MHz color subcarrier could cause a noticeable shift in the flesh tones of a color picture.

Let's review a few troubleshooting and alignment methods to keep that color picture in normal balance.

THE COLOR BURST SIGNAL

The TV station transmits (during a color program) a minimum of 8Hz of 3.58MHz on the back porch of the horizontal sync pedestal. To produce good stable color, the TV receiver must retrieve a clear 3.58MHz color burst signal. This is the function of the color burst separator and amplifier stages. We will use a Zenith 20Y1C38 (Fig. 1) color chassis for most of these checks.

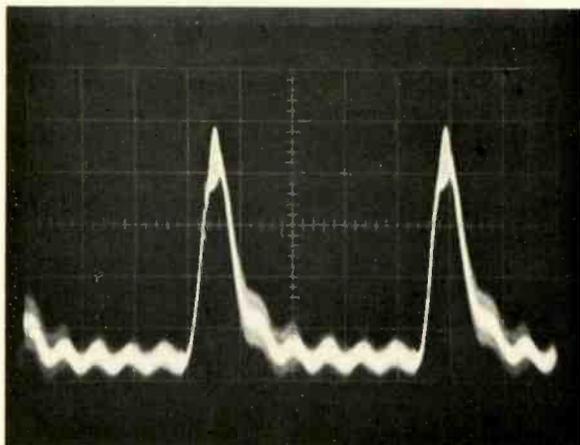


Fig. 2--A normal color burst signal taken from pin 2 of the burst amplifier tube.

lograph wavetrace. The top trace is color burst information at V16, burst amp plate pin 7, while the bottom trace is simultaneously compared with the keying pulse at pin 2 of the same tube.

A balanced 3.58MHz color burst signal will be taken at the secondary of L40, AFC and ACC phase detector transformer. The dual-trace oscilloscope waveform that should be found at this stage is shown in Fig. 5 and this

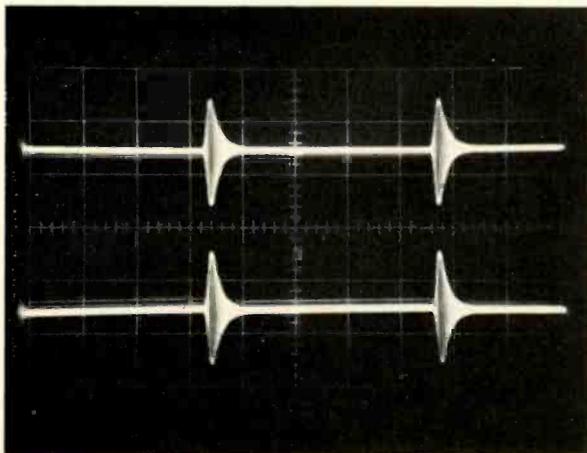


Fig. 5--The dual-trace oscilloscope waveform shows a balanced 3.58MHz color burst signal taken at the secondary of the AFC and ACC phase detector transformer.

burst pulse should measure 60v P-P. If this pulse is unbalanced, check the following components, C158, C159, R95A, R95B and the phase transformer, L40. Check other scope waveforms (Fig. 1) for proper operation.

TROUBLESHOOTING AND ALIGNMENT OF THE COLOR AFC CIRCUIT

The following "time saving" service techniques should be used for alignment of the 3.58MHz color oscillator in Zenith color sets.

Voltage measurements should be taken at test point "W" (color AFC circuit)--refer to Fig. 1.

If the receiver has AFTC (automatic fine tuning control) provisions, turn AFTC switch to the OFF position while making these adjustments.

A properly operating color set will generally read about zero voltage when measured with a VTVM at test point "W" under no signal condition (tuner set between channels). Should this voltage exceed 1v (positive or negative), several different symptoms may appear as follows: (1) complete absence of color information; (2) intermittent loss of color sync; (3) color dropout; (4) critical fine tuning range for color and (5) delay in color "lock-in" when changing from one channel to another.

Some of the probable causes for voltages in excess of 1v at test point "W" under no

signal conditions are as follows: (1) a faulty 3.58MHz CW oscillator and control tube; (2) a defective AFC phase detector (tube or solid-state diode)--one diode may be conducting considerably more than the other; (3) an open or leaky section in one of the two dual .001 μ f capacitors in the AFC phase detector circuit; (4) a defective 42 μ h choke at test point "W"--this choke is important for stability of the oscillator; (5) component leakage or value change in the anti-hunt network (from test point "W" to ground); (6) incorrect setting of the 3.58MHz color oscillator frequency adjustment, L44 and (7) the 2.2M resistors have changed value (not matched) in the AFC phase detector circuit--these resistors must be matched to within 2 percent of each other.

The range of correction voltage at test point "W" to maintain color sync for the 3.58MHz color oscillator with color signal should be approximately 5v (positive or negative) for optimum pull-in range. The inability to develop this range of voltage may result in several varied troubles as will now be noted.

The following information can be used to check the pull-in range (voltage correction range) at test point "W": (1) feed a color signal to the tuner antenna terminals, (2) connect a VTVM from test point "W" to ground, (3) ground test point "K," killer voltage can be measured at this point (ground to open color channel), (4) adjust the slug of the color oscillator frequency coil (L44) by turning it clockwise as viewed from the bottom of the chassis. Check the voltage reading on the VTVM. About 5v negative should be present with the color pattern remaining in sync. Adjust the slug counter clockwise. The negative voltage should slowly approach zero, then reverse polarity and approach about 5v positive with the color pattern remaining in sync. Change polarity of your VTVM. This range (approximately ± 5 v) is considered normal and correct for consistent color sync.

If this range is considerably less than ± 5 v, circuit troubleshooting is then necessary. The following service tips are suggested: (1) Check or replace the color oscillator and AFC phase detector tubes; (2) Check all components from test point "W" to ground. A prime suspect would be the .1 μ f capacitor C163; (3) Check the 42 μ h choke at test point "W," L43; (4) With the oscilloscope, check for presence of burst signal at the phase detector coil, L40; (5) Check the dual .001 μ f capacitors (two are used) in the color AFC phase detector circuit, and also capacitors or cold solder joints in the screen grid circuit of the burst amplifier tube; (6) The 3.58MHz crystal may also be defective (replace and align oscillator for zero beat); (7) Oscillator coil,

L44, may be faulty (substitute with new coil).

The adjustment of the 3.58MHz oscillator must be made correctly.

The procedure for adjusting the 3.58MHz CW oscillator to "zero beat" with an "on the air" color program is as follows: (1) Tune in a color program and observe color on the CRT. (2) Ground test points "K" and "W" on the chassis. Should the color be "running" across the screen at a rapid rate, it is an indication that the 3.58MHz oscillator requires tuning for a "zero" beat condition. (3) Adjust the core of the color oscillator frequency coil, L44, until the color band movement comes to a near standstill. Continue to tune the 3.58MHz oscillator coil while noting colors on the screen. Tune until the color on the screen becomes a solid hue. At this point, all color has come to a standstill.

Use caution when making this adjustment as an error can easily be made. It is possible to adjust the core until two or more "red" and "blue" wide diagonal bars are seen to be at a standstill. This is not "zero" beat, but can easily be mistaken for it. Proof of "zero" beat can be made by removing the ground from test point "W" and connecting a VTVM from this point to ground. A reading of up to $\pm 2.5v$ may be present. When the 3.58MHz oscillator is correctly set for "zero" beat, the voltage measured at test point "W" will be virtually zero (or less than $\pm 1v$). Remove the VTVM and again ground test point "W" if further adjustment is necessary.

Proper alignment of the 3.58MHz color oscillator will solve many color sync and fade out complaints.

IC 'CHIP' COLOR DEMODULATOR

Some new Zenith color chassis employ an

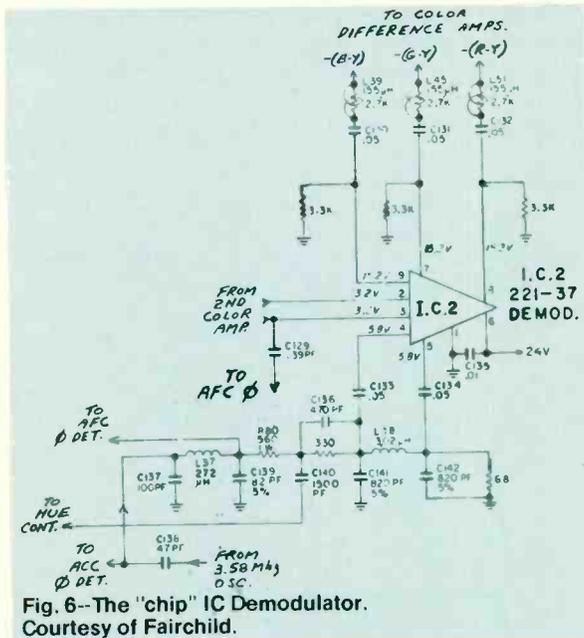


Fig. 6--The "chip" IC Demodulator. Courtesy of Fairchild.

IC "chip" (IC 221-37) for the color demodulator.

This IC contains two double-balanced synchronous detectors that are coupled to a matrix system where the desired color difference signals are developed. Shown in Fig. 6, the output of the second color amplifier is coupled to an IC stage or "chip". This "chip" is designed to plug into a conventional 9-pin miniature socket and is keyed accordingly.

Two chroma signals of opposite polarity are coupled to terminals two and three. The dual-trace scope waveform (Fig. 7) shows the color difference signals of $-(R-Y)$, $-(B-Y)$

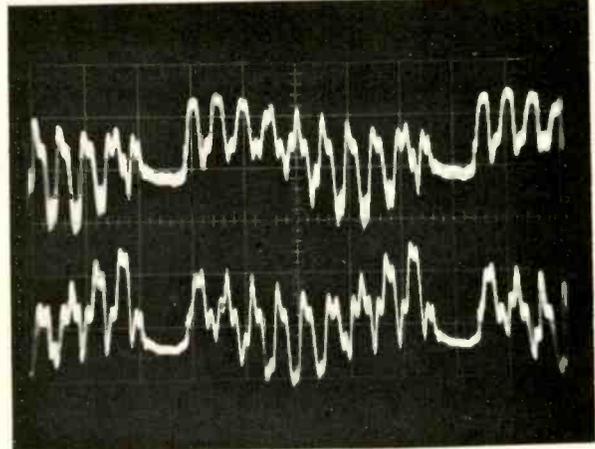


Fig. 7--The dual-trace waveform shows the color difference signals of $-(B-Y)$ top waveform and $-(R-Y)$ bottom waveform which will appear at terminals eight and nine of the IC demodulator.

chroma signal output which will appear at terminals eight and nine of the "chip." Oscillator injection reference (3.58MHz-CW) is injected at terminals number four and five. A dual-trace triggered scope signal waveform of this CW signal is shown in Fig. 8. Please note the 3.58 MHz CW signal has been superimposed on the scope for an exact phase check of the 104deg signal shift.) The oscil-

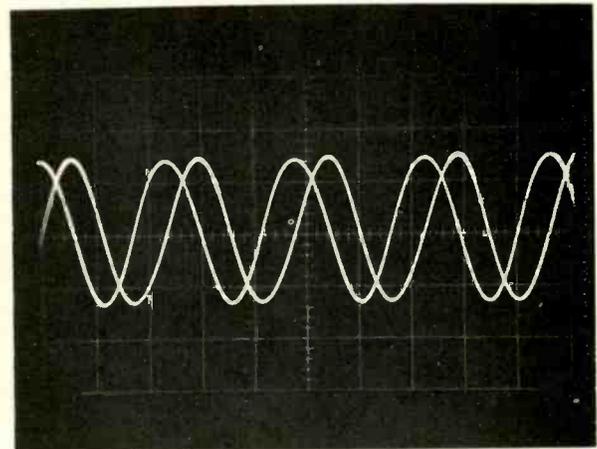


Fig. 8--A dual-trace triggered scope waveform of the CW signal. The 3.58MHz CW signal had been superimposed on the scope for an exact phase check of the 104deg signal shift.

Continued on page 92

Contrast Now-- Tomorrow What?

Bob tells Scoot about filters for CRTs--and a little of what's to come in this business

■ "I've seen some crazy gimmicks foisted on the public, but this 'black-screen' gimmick is the worst yet."

Scoot was talking mostly to himself, but Bob took the cue and, in his usual fashion, came to the manufacturer's defense.

"You and a lot of others seem to think that everything a manufacturer tries to sell the public is some kind of gimmick. Scoot, for the most part, the engineers have to sell the marketing people on new ideas and the ideas have to be sound or they won't budge."

"Oh boy! Me and my big mouth. OK, bright guy--defender-of-the-great-American-manufacturer--what does a dark glass in front of a CRT do to the picture besides cut down on the light?"

"Well, as you know, several TV makers have picked up the dark filter idea, Scoot. Now, it should seem reasonable to you that if it were only a gimmick, the other manufacturers would say that it was only a gimmick and go about their business. Right?"

"I'm not convinced."

"And I'm not through. To answer your question, I'll only say that the dark filter increases the contrast."

"How can you say that? I know that the blacks will be 'blacker' but the whites will be darker, too."

"Not so, Scoot. At least, not quite. Although the blacks will be 'blacker' and the whites darker, too, the difference between the two will be greater. In other words, there will be more contrast."

"That's double-talk if I ever heard double-talk."

"Then keep quiet and I'll explain. The darkest object you can have in a picture cannot be any 'blacker' than the screen itself. What makes it appear black, even though it is relatively light, is the contrast between the screen and the lighter picture elements."

"Now, the reason you see the phosphor on the screen when the set is switched off,

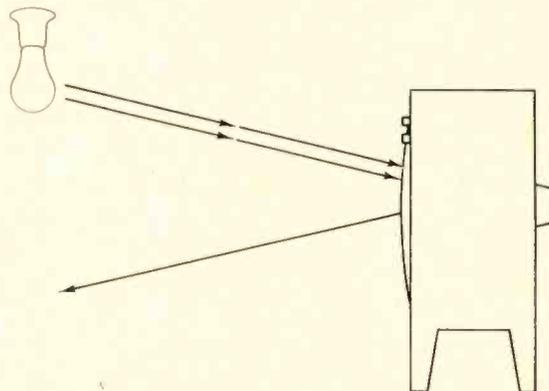


Fig. 1--Reflected light allows you to see the screen when there is no light from the set itself.

is because the light hitting the phosphor is reflected to your eyes. Look here."

Bob scribbled a picture on the scratch pad on Scoot's bench (Fig. 1).

"Light coming from the phosphor when the set is on follows the same paths to the eye, but it is not reflected."

Bob drew another sketch (Fig. 2).

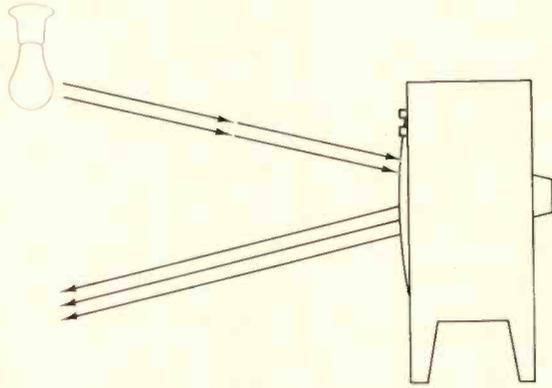


Fig. 2--When the set is turned on, light from the phosphor overpowers the reflected light and makes the screen appear black.

"The reflected light is not as strong as the light emitted by the phosphor so the eye sees a contrast: black and white.

"In a very bright light, like sunlight, still another factor is involved. The sunlight not only reduces the contrast, it overloads the CRT phosphor and reduces the phosphor output."

"That all sounds good, Bob. But what about the dark glass, what does it do for the picture?" "Well, for one thing, it can reduce external light reaching the CRT and may prevent 'overloading' the CRT phosphor. But the really big effect is that the external light must go through the filter twice while the light emitted by the tube only goes through it once."

Bob drew another sketch, adding a filter

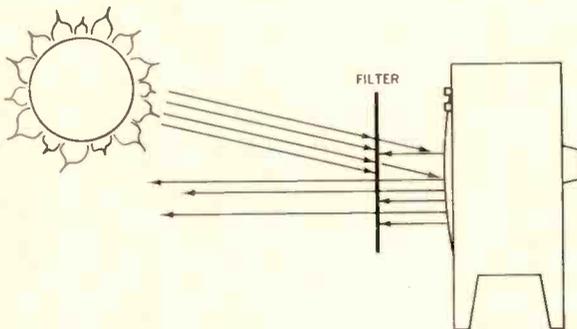


Fig. 3--A 50 percent transmission filter demonstrates how only 25 percent of the reflected light is seen but 50 percent of the phosphor light is seen.

to the TV set as shown in Fig. 3.

"I think I'm beginning to see the light, Bob."

"Good, let's make an example just to make sure. Let's look at a few rays of light and see how this filter works. Just for the sake of this example, let's say that the filter will transmit 50 percent of the light that strikes it and absorbs 50 percent.

"If four rays of light strike the filter, then only two go through. OK? And when the CRT reflects these, only one will get through to the eye. In other words, only 25 percent of the light that strikes the filter is reflected to the eye. That's what makes it look dark.

"On the other hand, two of the four rays emitted from the CRT will pass through the filter to the eye. So, what would be a four-to-four ratio without a filter--a perfect wash-out--becomes a two-to-one with the filter. Of course, this ignores a few minor points and the ratio only holds true for a filter with a 50 percent transmission characteristic."

"I'll be darned. I never thought of it that way."

"Obviously, jug-head. While we're at it, we may as well get you acquainted with polarized filters, too. We're going to be using them on that CCTV job at the steel mill.

"We don't have to discuss all the angles of linearly polarized light. Let's just say that there are two kinds: left polarized and right polarized. Normal light, like we're working in, is about 50-50."

Bob pulled a cheater cord from a bench drawer and tied one end to the handle. Then he slid it between the back rungs of an old chair and with a flick of his wrist produced a wave motion (Fig. 4).

"See, Scoot, the chair doesn't block the cord's motion when I swing it up-and-down. But, when I swing it sideways the rungs hit

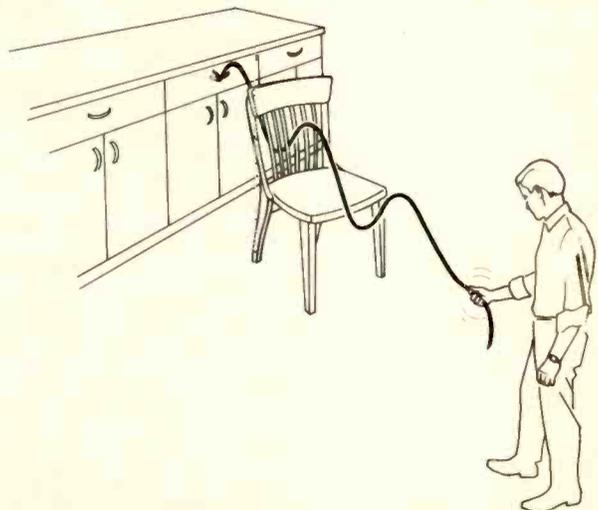


Fig. 4--A swinging cheater cord and the rungs of a chair can be used to demonstrate the function of polarizing filters.

it and don't let the waves form. They can pass through in only one direction or plane.

"If we put a polarizing filter in front of ordinary light, we get only polarized light out-likeso."

Bob took a book from the shelf behind his desk, brushed off the dust, opened it at a faded yellow marker and pointed to a drawing at the top of the page (Fig. 5).

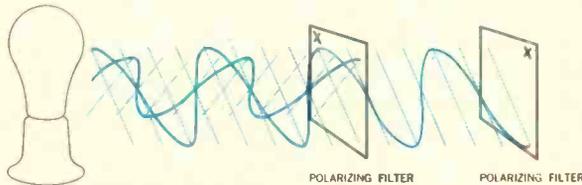


Fig. 5--Polarizing filters can be employed to stop virtually all light when they are rotated out of phase.

A thin smile appeared on Scoot's face. "I'm really in for it now."

"As I was saying, Scoot, we assume that half the light is left polarized and the other half right polarized. The material in the first filter--like the chair rungs--permits only the light waves polarized in one direction to pass through--the others are stopped by the filter.

"The second filter is like the first one except it's rotated 90deg--I'll use a little reference-'X' on the two filters to show it. Now the imaginary rungs in this second filter are in a direction that would allow the waves already blocked to pass through--if they were still around. Instead, these 'rungs' block the remaining light waves."

"Oh, I get it now--it sounds simple, Bob. And, I suppose any smooth surface--like the face of a CRT--will reverse the polarized light traveling through this filter--the filter catching what's left--the reflected light--the second

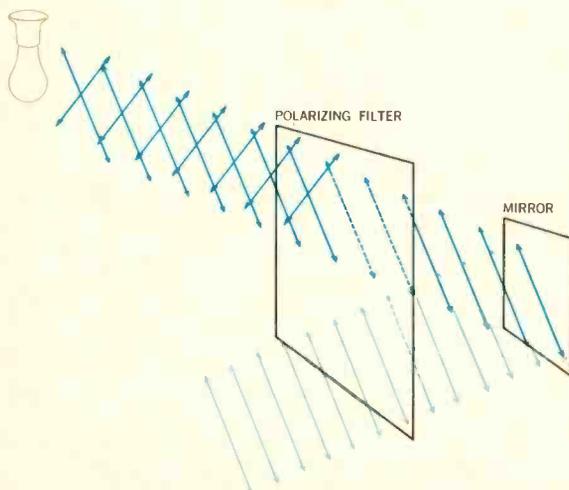


Fig. 6--When light is reflected from a smooth surface, the angle of polarization is not reversed.

time through. You know--if left polarized light got through the filter, it would become right polarized light when reflected and the filter would block its return."

"It sounds like a good idea, Scoot, but you're wrong. A single polarized filter--like the ones we've been talking about--wouldn't do any more good than the regular filters we just talked about--the fact that the light becomes polarized wouldn't help much."

"Then why have you been talking about polarized filters when I've got TV sets to fix--those polarized filters are just some other 'gizmos' to help increase sales."

"You're just getting ahead of me, Scoot, we'll see why your idea doesn't work and what can be done to make it work. Here, look at the next page in the book (Fig. 6)--then you'll see that a smooth surface, or even a mirror, doesn't reverse the polarity of left or right polarized light. While you're studying that, I'll set up a simple demonstration of some principles you'll have to learn before we can go any further."

Bob connected the sinewave output of an audio signal generator to both the horizontal and vertical inputs of a scope (Fig. 7).

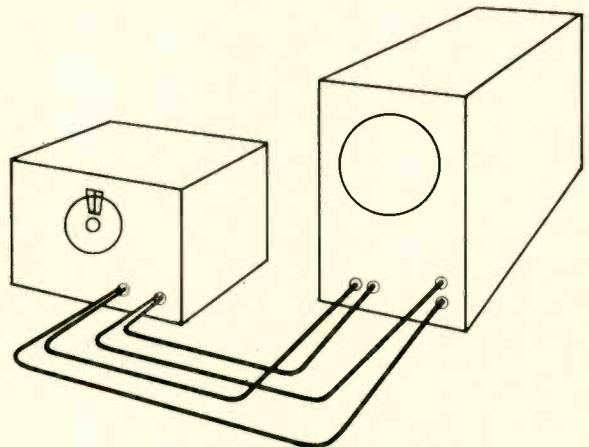


Fig. 7--An audio signal generator and scope are used to demonstrate the effective components of polarized light.

"Now look at the screen, Scoot. When I turn the scope's phase control so that the little green dot moves left-and-right in phase with its up-and-down motion, then we have a single diagonal line (Fig. 8 phase=0°). The two motions cause the dot to move diagonally up-and-down--like a wave of right polarized light.

"By turning this phase control knob some more, I can change the horizontal and vertical signals so that they are 180deg out of phase. Now the dot--instead of moving to the right when it moves up--is moving to the left when it moves up. This motion forms another diagonal line (Fig. 8 phase=180°) resembling

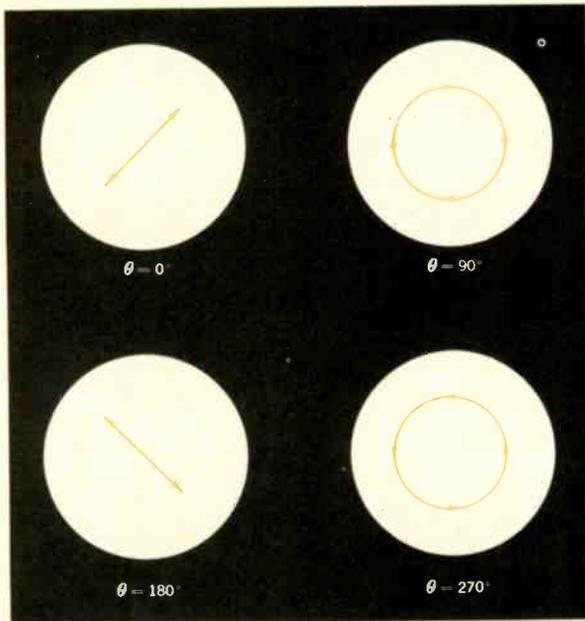


Fig. 8—Patterns formed on the scope are dependent on the phase relationship between the horizontal and vertical sinewaves.

a wave of left polarized light. Although for both diagonals the dot moves in a straight line, its movement along that line is a combination of movements up-and-down and right-and-left. One combination of movements can be said to exist for right polarized light—a different combination can be said to exist for left polarized light.

“You see, Scoot, though the dot appears to be moving only along one diagonal line or the other, we can think of it as also being a combination of horizontal and vertical motions from the two inputs on the scope.”

“No comment.”

“Well, Scoot, it’s the phase angle between the two motions that determines whether the dot’s motion forms a right or left diagonal line. When the horizontal and vertical waves are in phase, they form a right diagonal line—when the horizontal wave is 180deg behind the vertical wave, a left diagonal line is formed.

“By adjusting the phase control knob so that the horizontal motion is 90deg behind the vertical motion, the dot appears to rotate clockwise (Fig. 8 phase = 90°)—turning the knob further makes the horizontal motion 270deg behind the vertical motion—now the dot appears to be rotating counterclockwise (Fig. 8 phase = 270°).”

“So am I.”

“Turn to the next page marked in the book—there’s a couple of diagrams there that might clear up what I’m trying to get through your thick head.

“Let’s say that the polarizing filter in the first diagram (Fig. 9) permits only right polarized light to pass through it. But directly

behind this filter is a retarding element.”

“A what?”

“A retarding element—its a thin piece of transparent material that is able to slow up waves traveling in one plane, while not those in another plane. The filter shown here slows up the horizontal component waves of the right polarized light, while allowing the vertical component to travel through at the normal rate. This, in effect, alters the phase angle between the two component waves.”

“You don’t say.”

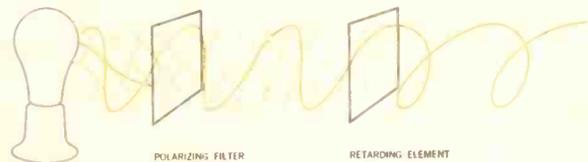


Fig. 9—Circular polarizers contain a linear polarizing filter and a quarter-wave retarding element.

“Look—the right polarized light is like that right diagonal line that we had on the scope—its horizontal component was in phase with its vertical component. The retarding element is able to slow down the horizontal component—once the polarized light has passed through the retarding element the horizontal component is 90deg behind the vertical component—the retarding element having changed the right polarized light into circular polarized light—rotating clockwise.”

“Oh I get it, Bob, then the light from the lamp travels to the polarizing filter—only right polarized light traveling through. The retarding element changes this right polarized light to circular polarized light, which is rotating clockwise.”

“Good for you, Scoot—you may get this yet!”

“Now, once we get through the next figure (Fig. 10), we may have you understanding these circular polarizers.

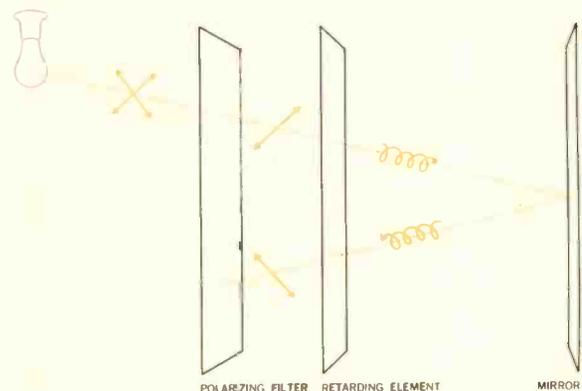


Fig. 10—The phase shift of light in the retarding element permits the virtual elimination of reflected light in the linear polarizing filter.

Continued on page 82

HEATH MODEL IT-18


A Heath Model IT-18 in-circuit/out-of-circuit transistor tester is assembled and evaluated by our ELECTRONIC TECHNICIAN/DEALER lab technicians

■The Model IT-18 was assembled in about two hours. The entire circuit wires to the five operating controls and one test socket on the metal chassis. A sensitive, easy-to-read microammeter takes up more than half the space of the unit which is relatively simple to construct.

The tester is a bi-polar device using a single "D" cell for power and weighs only 2 1/4 lb. We tried the tester on several transistors, some which we knew were good and others defective. The unit provided practical gain (Beta) values for the good transistors which were plugged into the test socket. However, as the manufacturer states, in-circuit tests for gain are dependent on the shunt resistances in the transistor circuit. So if you need accurate beta values, remove the transistor from the circuit and measure it. The IT-18 tester will not check special purpose devices such as FET's

zener diodes or other high leakage units. Also, do not make in-circuit transistor tests with power on the circuit.

This tester will also tell you whether a transistor is an NPN or PNP by using the polarity switch and BETA CAL controls. The meter circuit is designed to calibrate only when the polarity switch is in the proper position; if you have the wrong polarity selected, it will not calibrate. The instructions with the tester are complete to the point of explaining how beta and ICBO or ICEO leakage tests are accomplished and works very well for normal shop measurements. If you do transistor work, as most technicians do today, it can save you valuable time by telling you when you have a normal or defective transistor before you go to all the trouble of unsoldering it. The Model IT-18 is priced at \$24.95. ■

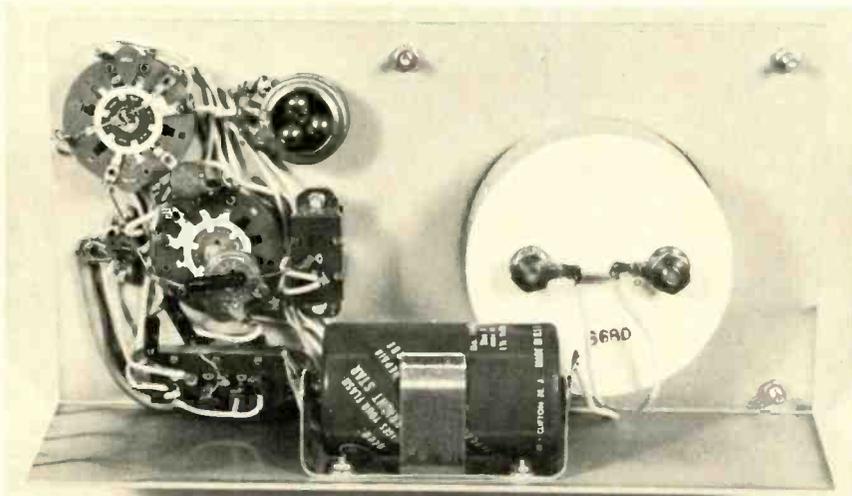

Model IT-18 in-circuit/out-of-circuit transistor tester measures gain (beta) and leakage. The circuit is basically a low impedance, common-emitter amplifier using the transistor being tested to complete the circuit.



for more details circle 900 on postcard

ELECTRONIC TECHNICIAN/DEALER

EICO MODEL 385

Construct this solid-state color bar generator and get a professional unit at a low cost

■ One of the features noticed first was the compact design of this color bar generator. The small size makes it useful for in-home testing and it will fit the normal tube caddy. The case is made of steel and comes with a convenient handle.

This color generator may not have all the test features of the higher-priced units but it does have the essential patterns such as: (1) horizontal and vertical test patterns for dynamic convergence adjustments, (2) crosshatch and dot patterns for both static and dynamic convergence adjustments, (3) color bars, brightness-keyed for troubleshooting and alignment of the chroma circuits.

All five patterns are crystal-controlled which is necessary for good color reproduction.


This gated rainbow generator is completely solid-state (13 transistors and 6 diodes) which eliminates warmup time and is self-powered by six "C" cells.

We tested the color generator on a late model color TV and the unit produced normal test patterns. Although the generator is adjusted for a display on channel 3 (61.25 MHz), a strong local signal on that frequency did produce some co-channel interference. Another channel on the generator would be desirable.


The generator features a socket type gun killer for the 90 deg CRT which allows one color or any combination of two or more colors to be eliminated from the display on the CRT. The socket stores in the case when not in use. Adapter sockets are also available for the 70 and 110 deg CRT.

The over-all circuit employed in this generator is shown in the block diagram. Basic pattern timing starts with a crystal-controlled (187.2kHz) oscillator Q1. The square wave output of this stage drives a divide-by-12 counter (Q2, Q3 and Q4). A con-

Continued on page 83

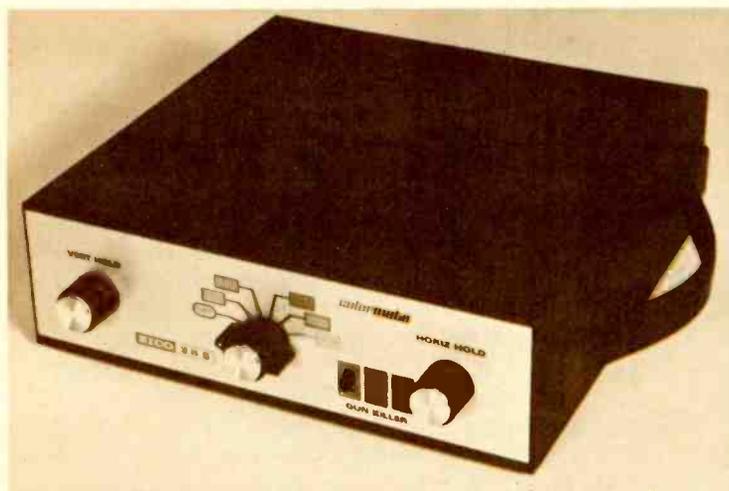

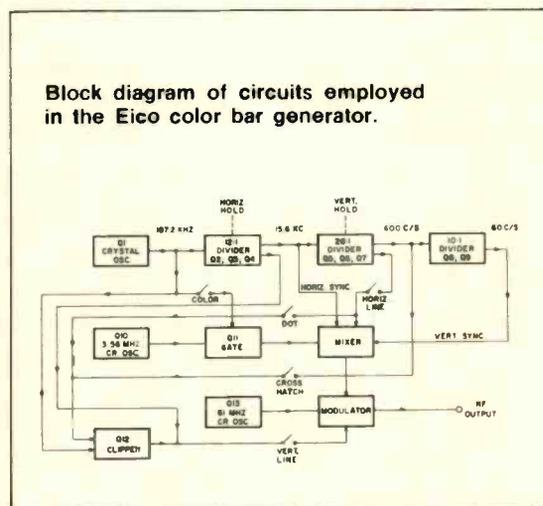Eico Model 385 solid-state color bar generator.



for more details circle 901 on postcard

Radios for Radiomen

Using two-way radio for field communication can increase service efficiency and sales

■ "That color TV set of mine went on the fritz right in the middle of a ball game," the unhappy customer said over the phone to his dealer. "Can you send a repairman over here right away?"

"Well, it might be a while," the dealer said. "The service truck is out on calls."

"How long will it take?"

"Well, sir, I don't rightly know."

"What do you mean, you don't know . . . get hold of him and find out!"

"He had a whole list of job orders when he left the shop," the dealer pointed out. "By now I don't know where he is."

"Well, call him and ask!" the customer demanded. "You've got two-way radio communication like everybody else in the service business, haven't you?"

"W-e-e-l-l, no."

"What! And you're in the radio business?" the customer snorted. "I've heard about the shoemaker whose children have no shoes, but this is ridiculous." He slammed down the phone and dialed a competitor.

Fireside TV Service, whose ad in the Chicago classified phone book features the line, "Radio Dispatched," is one of the rapidly growing number of electronics service organizations who are turning to two-way radio as a control tool and service facility.

"We average a couple of dozen calls a day which we facilitate by radio," says Howard Perlstein, Fireside's shop manager. "We figure that seven out of ten 'cold' calls come in as a result of that ad in the phone book about our service trucks being radio dispatched for faster service. Considering how much better service we can give our customers and how much more efficiently we can make

use of a service man's time, we find that the limited use of two-way radio by our competition is downright incredible."

Utilization of two-way radio within the electronics service industry itself is below the norm in most other service industries, according to a spokesman for a leading manufacturer. "Most of the radio and TV people at the consumer level are still missing the boat," he says. "And it's their own boat."

However, many technicians and dealers feel that this situation is partly attributable to the manufacturers themselves. "They confuse us," a Houston shop owner avers. "Sure, I've considered two-way, but you should see all the literature about it I've got on my desk. Field communications equipment, Citizens Band radio, business band, high band, low band, UHF band, FM, paging units . . . all claiming that they've got the best answer."

Although the subject is complicated by the diversity of equipment available, it becomes less confusing when it is noted that broadcast communication for commercial use is still a comparatively new field and that many of the equipment salesmen have a tendency to become over-enthusiastic. Loading up users with far more equipment than they can possibly use is common, and much of it is unnecessarily complex, too.

Some of the claims can be pretty wild. One manufacturer even claims that two-way radio will cut down on phone bills, which is exaggerated when total costs are considered. The industry is also fond of proclaiming the fact that there are now more than two million users of two-way radio, but often neglects to add that this figure includes police cars and taxi-cabs.

Two-way radio is a tool that costs money and its cost can be justified only by the firm that needs it -- just as a dealer who specializes in selling new sets would seldom have much need for any elaborate testing equipment. Or the shop specializing in hotel and hospital work, where the men go to the same job every day until quitting time, would have little use for a field communications setup. Many electronic technicians and dealers do not need two-way radio. But the ones who do, need it badly.

Competition is so keen and technology so standardized in most parts of the country today that two-way radio can often be the competitive edge that makes the difference. When a customer calls for service and the repairman rings the door bell before the customer gets a chance to hang up the phone, as sometimes happens, word of that kind of service gets around the neighborhood fast.

Instant communication can also increase the working productivity of a busy truck,



especially when new calls come in for stops in the neighborhood where the truck is already operating. The shop can often "fill the slots" by catching the truck between stops for interim job orders in what can be the most flexible of schedules. When an order is occasionally canceled, the shop can notify the truck accordingly to save an unnecessary trip.

Accidents happen, too. Trucks or other equipment can break down. Or the wrong tools or parts may have been taken to a job, which can be run out by a delivery man. Wrong or illegible addresses on work orders are not unknown in the service industry, either.

In residential neighborhoods, in particular, a man in the field may find getting to a phone difficult, or at least time consuming. And how does the shop reach him when he's needed?

"The means to keep in constant contact with our three trucks in the field simplifies administration when all the shopman has to do is 'call up' the man on the job for progress reports," says Jim Lyons, the service manager for Fireside TV. "This can even mean that our operating costs per job ticket are lower than if we didn't have that kind of field control. We definitely use two-way radio as a competitive weapon, which is all the more meaningful because most of the other radio and TV servicemen not only don't have two-way radio of their own for field communication, they don't even know everything about it."

The vast majority of electronic technicians and dealers neither sell nor service two-way communications equipment, and a capsule rundown may be in order.

Simplest of all is Citizens Band radio, uni-

versally known as CB. The FCC has set aside 23 channels in the AM wave length for the exclusive use of "all ordinary citizens" and no other broadcasting is allowed within their frequency range. No license is required for the purchase or operation of CB radio with an input power of 100 milliwatts or less.

Higher-powered CBs require an FCC license which now costs \$9.25 including a book of regulations, but no tests are required and the licensing is actually little more than a registration. The license is good for five years and renewable on request. Application blanks are available from any FCC office, or from many of the specializing distributors.

The height of a transmitting tower is limited by law, but the regulations allow the user to install an antenna on his existing TV antenna.

All 23 CB channels are shared by other CB users. This chummy setup makes each channel almost like a telephone party line. The CB transceiver can be anything from a walkie-talkie type model to a full-scale three-unit base station.

CB desk-top models, or units designed for installation under the dash in a truck or car, are easier to use than walkie-talkies because all the operator has to hold is the palm microphone. Biggest advantage of desk-top models, though, is the fact that they are higher powered than walkie-talkies and can be hooked into a rooftop antenna. The higher the antenna, the more distance (watt for watt) the signal will go.

The cheapest mike models, even some at 5w with 12-channel capabilities, cost less than the best walkie-talkies. Lower-priced ones may have crystals for only one-channel operation, but better models include the full 23

Radios...

channels. Additional refinements get the prices up to around \$300 for a good set that approaches amateur equipment in transmission and reception quality.

The biggest trouble with CB is its success. It is relatively new. But in just a few years, it has also become one of the most crowded networks. A large city, for example, might have 10,000 CB users all looking for an open "party line" at the same time. . .and with only 23 channels to select from, CB is all but choking itself to death.

In most of the heavily populated sections of the country, about the only hope for a fighting chance with CB is in single sideband equipment.

Sideband transceivers usually incorporate all the best features available for CB, and most of them sell in the \$275 to \$325 bracket. As of now, users of sideband enjoy a relatively uncluttered field, but only because the development is so new. The CB field is just too wide open, and there are not many parts of the country left where a businessman can still operate with relative freedom.

CB compared to FM is like playing golf on a municipal course compared to playing at a private country club. Most "serious" users of two-way radio prefer FM for five reasons:

1. The choice of operating frequencies is wider.

2. The field itself is not as crowded, and although many FM users do share channels, their use and selection of channels is more strictly regulated by the FCC.

3. Input power can go up to 330w-66 times more powerful than CB's maximum allowable wattage.

4. An FM user can put up higher transmitting towers and communicate over distances far beyond the capabilities of CB.

5. Frequency modulation itself normally reduces the noise and interference from vehicle ignition systems, roadside power lines and other man-made noise sources which can make messages on AM (including CB) difficult to understand.

Getting a license to operate an FM station is tougher than CB and not available to the casual applicant. Prospective users are considered only after proving their need as well as their responsibility. They can expect to wait several months for an okay and assignment of individual channel rights.

Not counting the expense of putting up the tower, costs for a base station can start in the neighborhood of \$500. The average

cost is more likely to be closer to \$1000. FM is split into low band, high band and UHF band operations in a range from 25 to 470 MHz. High band is the most crowded.


Terrain characteristics, local congestion and the usual interference factors all go into determining how expensive a system the user will need. Lower-watt units cost less to operate than high-powered stations, and the more complicated the system, the more maintenance it is likely to need. Lightly powered low-band mobile units start at about \$300, while transistorized models for medium range are usually around \$500 or \$600.

Powerful portable units, which a serviceman can carry around like an over-sized lunch pail, are also available at prices all the way up to \$685.

Paging units small enough to be worn in a shirt pocket and which do no more than signal the wearer with a beep tone to get to the nearest telephone are in wide use because of their selective signaling - - only one man hears the beep. Other pagers, which can cost up to \$190 each, permit the reception of "private line" voice messages through the use of a special one-way transmitter that can cost from \$250 up.

One of the best two-way radio communications is through Mobilephone facilities operated by local telephone companies. They not only provide the ultimate in transmission equipment and facilities, but also take care of maintenance. Mobilephones are not cheap, though. The user usually pays a minimum of \$40 a month, which entitles him to 100 "unit calls." This means that each call costs at least 40 cents - - not counting anything against the cost of the handset-equipped transceiver itself, which runs around \$1500 in many parts of the country.

But as one southside service-dealer says, "I couldn't care less about what's going to happen five years from now, our two-way radio system paid for itself easily during the first six months we had it, not only in extra business but in cutting costs as well. We have a \$150 walkie-talkie in each of our two trucks and another in the shop. Nobody is ever any further away than the button on the transceiver. The total investment of less than \$500 at current bank rates is actually 'worth' less than \$40 a year - - and we can save that much in wasted gasoline alone. Sure, we have our troubles with walkie-talkie equipment, but it is certainly a lot better than no communications at all."■

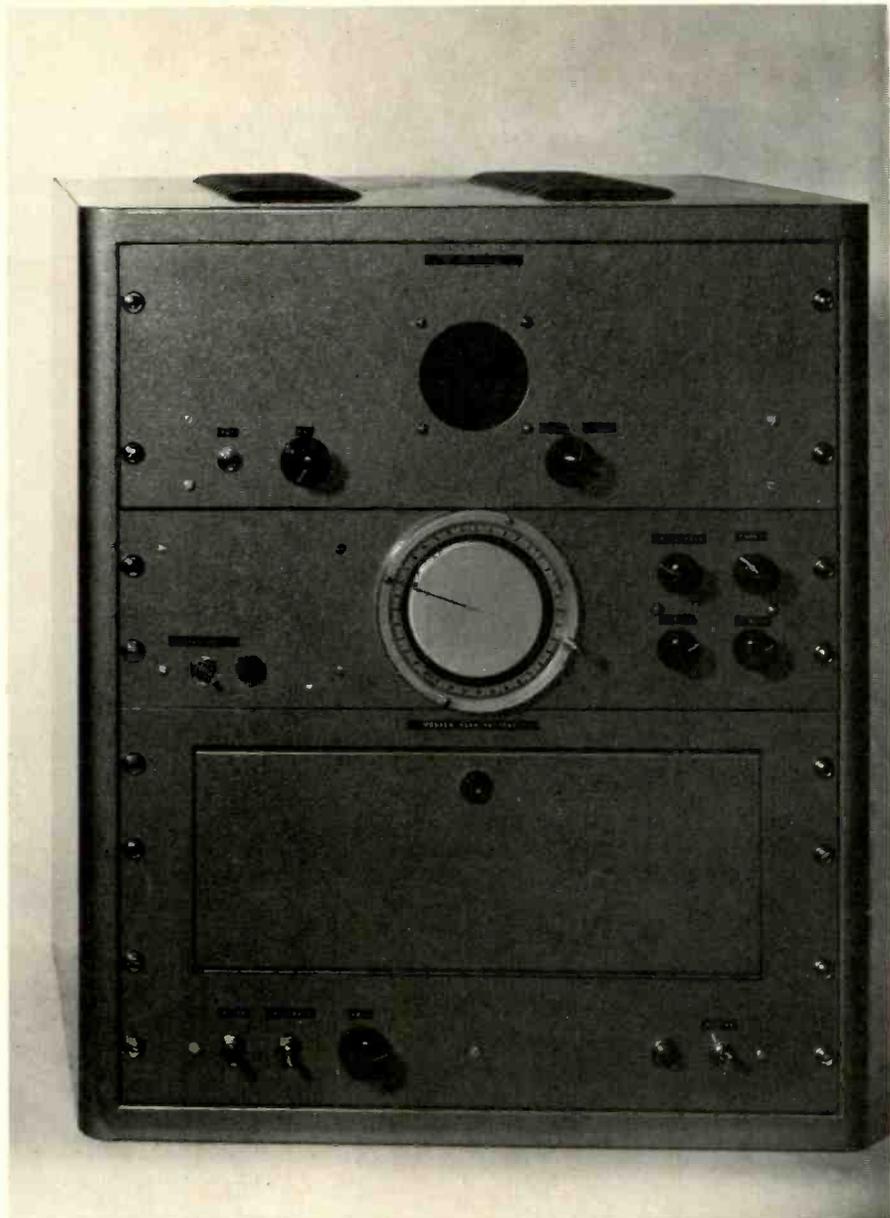

Cathode ray tube lightning detector (Courtesy British Columbia Forest Service)

Electronic Lightning Detector

■ Lightning is a dread enemy of the forest, a fact well known by the people who must depend on forest resources for a living. Lightning accounts for approximately 35 percent of the forest fires, and poses a difficult situation because hard-to-locate "sleeper" blazes can smolder for some time before suddenly bursting into flame.

But the threat of fire by lightning may be coming to its long-lived conclusion. Alex Stewart, a member of the IEEE for about 35 years, has developed an electronic device which can trace the striking path of lightning. As a technician with the British Columbia Forest Service, he began experimenting with a cathode ray tube direction finder which can track the path of electrical storms.

After two years of development his idea was put to the test and proven able to show where


Lightning Detector . . .



Lightning causes approximately 35 percent of forest fires (Courtesy BC Forest Service)

lightning was causing a fire. The value of the device naturally lies in the fact that fire fighting could be rushed to the newly formed blaze—before it had time to build and destroy millions of acres of valuable timber. The unit has a built-in alarm system which makes it unnecessary for the “look out” men to constantly monitor the scope face. The lightning detector features a dual track tape system which is used to tie the observer’s reading of a bearing on the scope to a fixed time scale to coordinate observations from other stations.

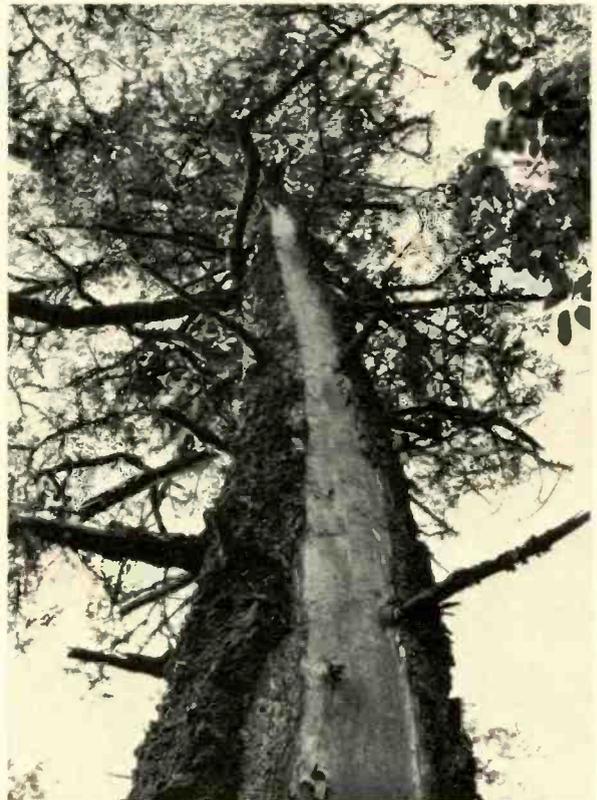The method of operation is to record WWV time signals on one tape track while recording the observer’s voice reading bearings from the scope on the other track. Then two tapes from two stations are then played back together and bearings at any fixed point in time are plotted to give a position for the lightning stroke. ■



A giant fir tree struck by lightning could have caused widespread fire if not located in time.

This little part plays a big role in radio.

This box gives you top revues.



The transistor is no bit player when it comes to radio performance. That's why Delco transistors are manufactured under controlled conditions that assure high reliability. And why they're thoroughly tested before being placed in the familiar blue and black box.

Delco Radio engineers are leaders in auto radio design and transistor technology.

Delco radios are original equipment on over half of the cars on the road.

That United Delco box is your guarantee of genuine OEM

quality replacement parts. And just 12 Delco transistors replace over 7,500 other types.

Doesn't it make good sense to stock the best?

Remember these facts when you re-order. And remember, too, that your United Delco supplier handles the most recognized name in the parts business.

Next time you think little, think big. Think Delco.

DELCO RADIOD, Div. of General Motors, Kokomo, Ind.



MARK OF EXCELLENCE



For additional information on products described in this section, circle the numbers on Reader Service Card. Requests will be handled promptly.

Two-Way Radio

700

An all solid-state Messenger Model 123 citizens two-way radio is introduced. The unit features full 23 channel operation and includes a special compression circuit that puts maximum audio into the radiated signal to extend the communication range. Power input to the final amplifier is the maximum allowable 5w. The re-




ceiver reportedly has $0.4\mu\text{v}$ sensitivity with sharp filtered 7kHz selectivity to pull in distant stations while rejecting interference from adjacent channel users. A noise limiter reduces ignition and other forms of radiated noise interference. The solid-state circuitry is temperature compensated to operate from -22° to $+140^\circ$ F. A variable squelch control is provided to reduce background noise by silencing the receiver until a message is broadcast. Other features include automatic volume control to keep the receiver output nearly constant regardless of incoming signal strength and a panel meter to monitor both incoming signal strength and transmitter output power. Only $2\frac{1}{2}$ in. high by $6\frac{3}{16}$ in. wide by $8\frac{3}{4}$ in. deep, this radio can be installed in many small, under-the-dash areas. The unit weighs 5 lb and is priced at \$169.95. E. F. Johnson.

Cassette Receiver

701

Introduced is the 2560 Compact Casseiver System, combining an AM/FM stereo receiver and a stereo cassette recorder with a matched pair of air-suspension speakers. With this system, the audio enthusiast can listen to AM, FM, stereo FM, or pre-recorded cassettes. He can also record onto cassettes from records, stereo microphones, a reel-to-reel tape recorder, or directly from the system's own stereo AM/FM tuner. The receiver section of the Cassette system features a patented Field Effect Transistor front end circuitry, reportedly resulting in virtual elimination of all cross modulation and drift for increased sensitiv-

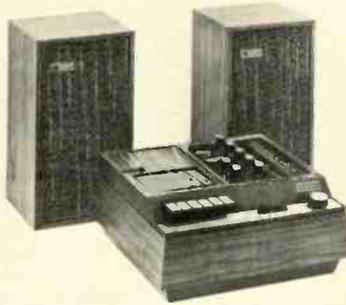ity. FET circuitry is also used to provide a wider range of tone control. Integrated circuits are employed both in the IF section and in the preamplifier for higher gain and lower distortion. The cassette mechanism is powered



by a synchronous ac motor, which is claimed to eliminate annoying flutter and wow. Control features of the 2560 Compact Casseiver are as follows: (Receiver Section) LOUDNESS; BALANCE; TREBLE; BASS; Power ON/OFF; Speakers ON/OFF; TUNING knob; Power light; Stereo indicator light; Input selector; Tape monitor. (Recorder Section) LEFT and RIGHT RECORD LEVEL controls; Left and Right record level meters; Dual microphone inputs; Headphone output; Resettable digital counter; and individual controls for opening the cassette section, RECORD, STOP, PLAY, REWIND and FAST FORWARD. The net price is \$399.95. Scott.

Portable Color TV

702

Introduced are three lightweight 12in. diagonal measurement portable color television receivers with transformer-powered 22kv chassis that employ 49 solid-state devices such as




transistors and diodes in 80 percent of the circuitry. The new 12in. models are reportedly the first color sets of this size produced in the United States.

In the portables, important signal processing circuits such as the tuner assembly, 3-stage amplifier, low voltage power supply and color amplifier are all transistorized. The new models carry the company's three year replacement warranty on the color picture tube. The color sets, which can be easily moved from room to room, are available in black, white and walnut grained cabinets. They include such features as automatic gain control, automatic degaussing, dipole telescopic antennas, super scope VHF/UHF tuning system, front mounted speaker and 75sq. in. of viewing area. The 2017P in a deluxe walnut cabinet has a suggested list price of \$269.95. Admiral.

Audio Control Centers

703

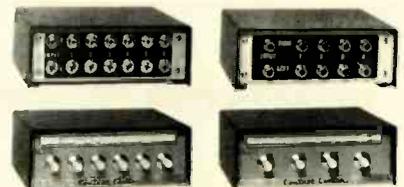A series of control centers allowing selection of up to four or six stereo speaker systems for simultaneous operation is introduced. The unit provides sound in every room throughout the house with push-button operation.




The "push-ON and push to RELEASE" switches allow the user to optionally place the speaker systems of his choice—from one to six speaker pairs—in operation. The control unit has a black metal case with the appearance of leather, contrasting brushed aluminum escutcheon plate, ivory white push buttons identification plate and easily accessible rear panel connectors to suit the particular system. Requiring no external power for operation and containing no internal resistors that may affect impedance matches, it is claimed ideal for stereo or monaural speaker distribution, microphone input mixing or receiver monitoring. The Model CC4 controls up to four channels and the Model CC6 up to six channels. Size: $5\frac{1}{8}$ in. x $2\frac{1}{8}$ in. x $3\frac{9}{16}$ in. Alco.

Stereo Music System

704

Introduced is the Model 35-140, a 40w stereo music system in contem-

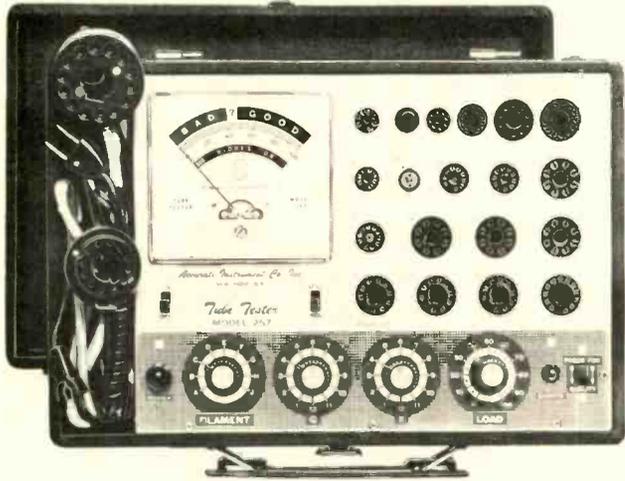The New 1969 Improved Model 257 **A REVOLUTIONARY NEW TUBE TESTING OUTFIT**



COMPLETE WITH ALL ADAPTERS AND ACCESSORIES, NO "EXTRAS"

STANDARD TUBES:

- ✓ Tests the new Novars, Nuvisitors, 10 Pins, Magnovals, Compactrons and Decals.
- ✓ More than 2,500 tube listings.
- ✓ Tests each section of multi-section tubes individually for shorts, leakage and Cathode emission.
- ✓ Ultra sensitive circuit will indicate leakage up to 5 Megohms.
- ✓ Employs new improved 4½" dual scale meter with a unique sealed damping chamber to assure accurate, vibration-less readings.
- ✓ Complete set of tube straighteners mounted on front panel.

The Model 257 is housed in a handsome, sturdy, portable case. Comes complete with all adapters and accessories, ready to plug in and use. No "extras" to buy. Only

BLACK AND WHITE PICTURE TUBES:

- ✓ Single cable used for testing all Black and White Picture Tubes with deflection angles 50 to 114 degrees.
- ✓ The Model 257 tests all Black and White Picture Tubes for emission, inter-element shorts and leakage.

COLOR PICTURE TUBES:

- ✓ The Red, Green and Blue Color guns are tested individually for cathode emission quality, and each gun is tested separately for shorts or leakage between control grid, cathode and heater. Employment of a newly perfected dual socket cable enables accomplishments of all tests in the shortest possible time.

\$47⁵⁰

NOTICE

We have been producing radio, TV and electronic test equipment since 1935, which means we were making Tube Testers at a time when there were relatively few tubes on the market, way before the advent of TV. The model 257 employs every design improvement and every technique we have learned over an uninterrupted production period of 32 years.

Accurate Instrument Co., Inc.

SEND NO MONEY WITH ORDER PAY POSTMAN NOTHING ON DELIVERY

Try it for 10 days before you buy. If completely satisfied then send \$10.00 and pay the balance at the rate of \$10.00 per month until the total price of \$47.50 (plus P.P., handling and budget charge) is paid. If not completely satisfied, return to us, no explanation necessary.

ACCURATE INSTRUMENT CO., INC.

Dept. 652, 2435 White Plains Road, Bronx, N.Y. 10467

Please rush me one Model 257. If satisfactory I agree to pay \$10.00 within 10 days and balance at rate of \$10.00 per month until total price of \$47.50 (plus P.P., handling and budget charge) is paid. If not satisfactory, I may return for cancellation of account.

Name _____
Address _____
City _____ Zone _____ State _____

Save Money! Check here and enclose \$47.50 with this coupon and we will pay all shipping charges. You still retain the privilege of returning after 10 day trial for full refund.

. . . for more details circle 101 on postcard

porary cabinetry. This unit features all of the elements necessary for stereo reproduction in a pre-assembled compact design. The receiver-amplifier delivers sound on AM/FM and stereo FM and through its Garrard automatic changer with a magnetic cartridge to reproduce mono or stereo records. The unit, featuring two acoustically suspended speaker systems, is finished in an oiled walnut cabinet and brushed aluminum control panel.

Speakers measure 17½ in. x 10 in. x 5½ in. depth. Specifications: 40w music power at 8Ω reportedly less than



1% H.D. at listening levels; 40db channel separation. Frequency response 25-25,000Hz. Separate bass

and treble controls. Built-in overload protection. Tuner section: 3.5μv for 20db S/N on FM. 300Ω FM antenna and built-in ferrite loop for AM. Has stereo headphone jack and tape-in tape-out jacks. Turntable: Garrard with 4 pole shaded "Induction Surge" motor with magnetic cartridge and diamond stylus. Automatic cutoff turns off all power on last record. Claricon.

Turntable

705

Introduced is the Model 600 top-of-the-line turntable. The base incorporates an illuminated power switch that permits the complete receiver system to be shut off automatically by the turntable after the last record has been played. The turntable comes



complete with a base and dust cover ready to plug into a system. The unit has a cast turntable and an adjustable control which applies a continuously corrected degree of compensation to neutralize the inward skating force and eliminate distortion caused by unequal side wall pressure on the stylus. In addition, the turntable has a MICROMETER STYLUS PRESSURE adjustment which permits 1/3g settings from 0 to 6g; it also has a STEREO MUTING switch for complete silence during the record change cycle. Another feature is the CUEING and PAUSE control lever, which allows the listener to raise or lower the pickup arm at any time and return it to the same groove. BSR.

Communications Microphone 706

Introduced is the "level-limiter" microphone which is claimed to eliminate overload distortion resulting from excessive input while increasing the average level on normal speech. The Model 500-PS is readily adapted to two-way radio and is suited for public safety, as land, maritime or air-mobile operation. The microphone contains a silicon solid-state circuit, which reportedly provides 40db


Continued on page 72

One company dominates the sound column field...

ARGOS.

And you reap the profits! Why? Because as an Argos TSSD (Total Sound System Distributor), you have the tools to do the job right, starting with the product itself. Argos "Sound Directors" are not just boxfuls of speakers. Each is a carefully engineered sound system designed to do a specific job, with models for voice reinforcement, background music, hi-fidelity, big rooms, little rooms, indoors or out. They're also easy to install and aim with Argos' exclusive Speedy Mounting Clips and Focus Gauge.

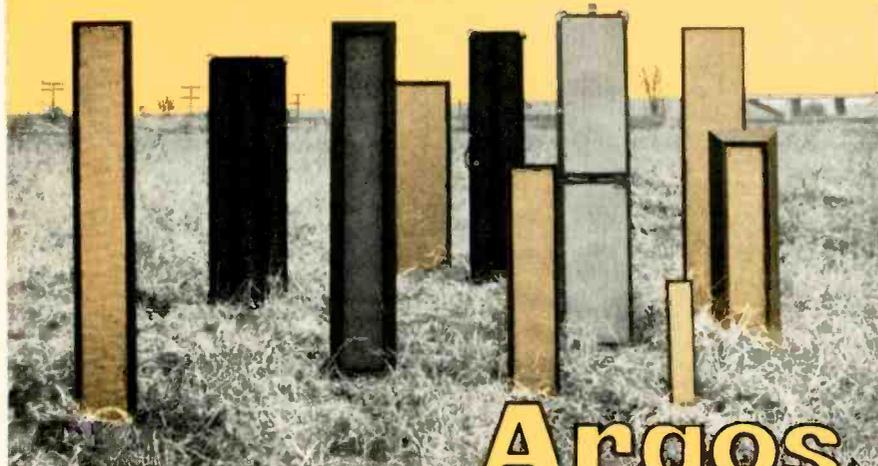Fifteen minutes with our booklet, "Sound Solutions to Sound Problems with Sound Columns," will help you solve 95% of the speaker system problems that come your way. But it takes more than even this to be the industry's leading sound column people. Let us show you the rest. Write today.



Argos
PRODUCTS COMPANY
600 South Sycamore Street
Genoa, Illinois 60135

See the "Block Buster" Display Deal at the N.E.W. Show Booth C119

... for more details circle 103 on postcard

How do you “install” confidence when you install an RCA color picture tube?



The surest way to compliment a customer is to agree with his opinion. This is pretty easy to do when it comes to deciding which brand of replacement color picture tube to install in his set.

Here both set owner and service technician agree — and by a wide margin — on RCA! And for one very good reason: RCA's reputation...for experience, quality, and proven performance...over the years. More years than anyone else in the business.

Place your confidence in the company that perfected the color TV system in use today. Introduced more technical innovations than any other company. Stays on top of the state-of-the-art not just in technology, but in tube sizes as well.

Whether it's an all-new RCA HI-LITE or the popular priced quality rebuilt RCA Colorama — when you recommend RCA — you'll not only flatter your customer, you'll also be protecting your own hard-earned service reputation. That's because RCA picture tubes are designed to protect the biggest reputation in the COLOR TV industry.

RCA Electronic Components, Harrison, N.J.

RCA

An Extraordinary Offer

to introduce you to the benefits of Membership in
ELECTRONIC TECHNICIAN'S BOOK CLUB

for a limited time only you can obtain

ALL **3** OF THESE UNIQUE BOOKS . . . yours for only \$**199**
...with Trial Club Membership

May we send you these three unique servicing handbooks as part of an unusual offer of a Trial Membership in Electronic Technician's Book Club?

Popular Tube & Transistor Substitution Guide

NOW—the most-needed substitution data for *both* tubes and transistors all in one handy, brand-new volume! No longer do you have to refer to one substitution manual for tubes and another for transistors—everything is here in one quick-reference guide. Designed to fit into your tube caddy or on your workbench, this guide lists 99% of the tubes and transistors you'll ever need to replace. Moreover, only readily-available and comparably-priced substitutes are listed—no longer do you have to search through lists of tubes and transistors you'll rarely see in use, or search through pages of irrelevant material to find a substitute.

This brand-new volume contains 8 Big Sections—four devoted to tubes and four to transistors. Section 1 provides you with a cross-reference of popular American receiving tubes, listing substitutes which have similar or superior characteristics and which require no mechanical changes or circuit modifications. In each case the *best* substitute is listed separately from others you may use. Section 2 lists substitutes for popular tube types found in commercial and industrial equipment. American substitutes for popular foreign types are presented in Section 3, while Section 4 includes base diagrams keyed to the tube listings in each section.

The transistor portion begins with Section 5, which contains a complete listing of popular American types and the most readily-available, popularly-priced substitutes. Section 6 lists American substitutes for the most often encountered foreign transistors. Section 7 is a listing of general-purpose replacements for popular original equipment types. Section 8 includes base diagrams which are keyed to the original type listings.

You'll find this guide to be one of the most practical everyday aids you've ever used. It will enable you to repair many sets for which replacement tubes and transistors are not available. 160 pps., 8 Sections. Long-life, flexible simulated leather cover for lasting convenience.

TV Servicing Guidebook: Problems & Solutions
Here's a new book for professional

TV Service Technicians—a benchman's handbook detailing shop-proven service procedures which will pinpoint ALL TV circuit troubles—monochrome and color!


Calling upon his many years of on-the-job experience, the author describes 30 separate troubleshooting approaches, each predicated on specific symptoms, to help you nail down any TV problem quickly . . . eliminate waste motion—cut troubleshooting time to the bone. The author has categorized all TV troubles—both color and B & W—according to 62 classic symptoms. He then describes the servicing procedures proved most successful in his shops. And you won't have to wade through page after page of dreary theory discussions to get the information you want. The text—illustrated with over 100 schematics and photos—gets to the point quickly, excluding extraneous theory and unrelated facts and figures.

Chapter 1 details initial setup procedures for color TV receivers, including gray-scale tracking, color screen adjustments, purity, degaussing, convergence, etc. Chapter 2 is devoted exclusively to color problems—no Y signal; no color; excessive red, green, or blue; incorrect colors; pastels; "confetti"; "worms"; etc. An entire chapter is devoted to the CRT and its trouble symptoms. To eliminate unnecessary replacement, many repairs are suggested. Chapter 4 lists seven video troubles, what causes them, and tells how to correct them. Chapter 5 analyzes the 13 basic high voltage faults, including flyback, yoke, and the oscillator circuits. Horizontal and vertical deflection circuits are explored for defects in Chapter 6. Chapter 7 exposes elusive sync and AGC troubles, from sync takeoff to integrator and AFC circuits. Chapters 8 and 9 encompass troubles peculiar to sound and power supply circuits.

In all, there isn't a TV trouble you won't be able to cure with the information presented in this book. 176 pps.; over 100 illustrations, including numerous waveform photos; 9 Chapters. Hardbound.

Semiconductors From A to Z

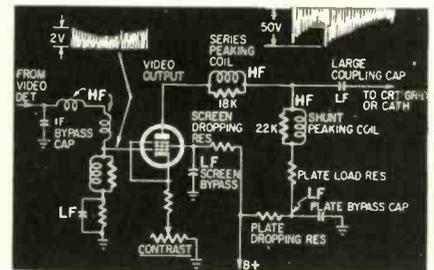All you need to know about the entire range of transistors and semiconductors used today. Written in language anyone can understand, this book explains how various semiconductor devices work and how they are used, with complete descriptions of all the




Literally scores of easy-to-use schematic diagrams are contained in all these new books. (Example shown greatly reduced in size)

common and unique circuits used in modern technology. With the wealth of knowledge incorporated in this book you'll be eminently qualified to service any type of solid-state equipment.


The content begins with a review of how basic semiconductors work, including types and function, how a transistor conveys a signal, transistor biasing and self-biasing techniques, effects of temperature on operation, factors limiting transistor frequency response, etc. Succeeding chapters delve into the mystical arena of field-effect transistors by explaining the differences between FETs and regular transistors. You'll understand junction FET applications, frequency response, temperature effects, and the treatment given depletion-type and enhancement-type MOS FETs in the most down-to-earth explanation you'll ever find.

Considerable attention is given to integrated circuit applications—variable-current and constant-current sources, unbalanced differential amplifiers, IC applications in FM and TV receivers, TV sound circuits, discriminator circuits, and cascade amplifier networks. The use of varicaps is also covered, as well as unijunction transistors, field-effect diodes, zener diodes, SCR diodes, 4-layer diodes, diacs, and triacs. The final chapters deal with constant current and voltage regulating systems and DC-to-AC-to-DC converters. Hardbound.

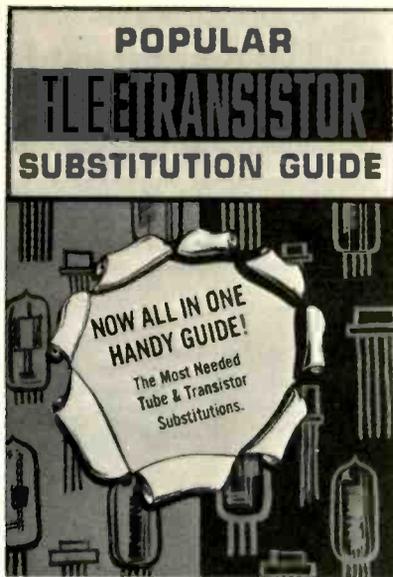
Popular Tube & Transistor Substitution Guide, TV Servicing Guidebook, and Semiconductors From A to Z are handsome, hardbound books, indicative of the many other fine offerings made to Members . . . important books to read and keep . . . volumes with your specialized interests in mind.



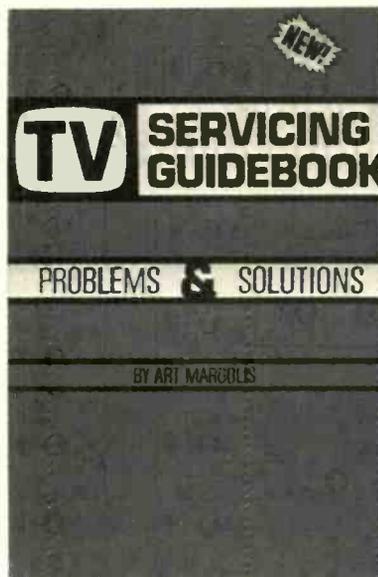- BRAND-NEW & Original
- Covers BOTH Tubes & Transistors
- Long-Life Vinyl Cover
- Lists U.S. & Foreign Types



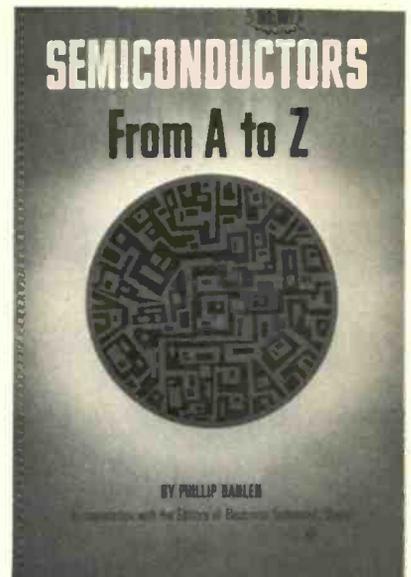- 176 pages • over 100 illus.
- Scores of waveform photos
- Covers both B & W and Color
- Unique step-by-step guide



- 256 pages • over 300 illus.
- Permanent Hardbound Volume
- 26 Fact-Filled Chapters
- Practical & down-to-earth

How You Profit From Club Membership

This is just a sample of the help and generous savings the Club offers you. For here is a Club devoted exclusively to seeking out only those titles of interest to you as an electronic technician (no hobby or "fringe" books are offered). Membership in the Club offers you several advantages:

1. Charter Bonus. *Popular Tube & Transistor Substitution Guide*, *TV Servicing Guidebook*, and *Semiconductors From A to Z* carry a publisher's retail price of \$19.85. But they can be yours for only \$1.99 with your Trial Membership.

2. Continuous Savings: The Club guarantees to save you 15% to 75% on the books you need.

3. Editorial Advisory Services: The Club's Editorial Advisory Board selects *only* the important books of direct interest to you.

4. Wide Selection: Members are annually offered over 50 of the authoritative books on all phases of electronic servicing. The Club makes it a point to offer new books, along with standard classics . . . lists books from *all* publishers—not just one or two.

5. Prevents You From Missing New Books: The Club's FREE monthly *News* gives you advance notice of important new books . . . books vital to your continued professional advancement.

This extraordinary offer is intended to prove to you, through your own experience, that these very real advantages can be yours . . . that it is possible

to keep up with the professional literature published in your specific area of interest . . . and to save substantially while so doing.


How the Club Works

Forthcoming selections are described in the FREE monthly *Club News*. Thus, you are among the first to know about, and to own if you desire, significant books. You choose only the main or alternate selection you want (or advise if you wish no book at all) by means of a handy form and return envelope enclosed with the *News*. As part of your Trial Membership, you need purchase as few as four books during the coming 12 months. You would probably buy at least this many anyway . . . without the substantial savings offered through Club Membership.

Limited Time Offer!

Here, then, is an interesting opportunity to enroll on a trial basis . . . to prove to yourself, in a short time, the advantages of belonging to the only Book Club devoted *exclusively* to electronic servicing. We urge you, if this unique offer is appealing, to act promptly, for we've reserved only a limited number of Handbooks for new Members.

To start your Membership on these attractive terms, simply fill out and mail the postage-paid Airmail card today. You will receive *Popular Tube & Transistor Substitution Guide*, *TV Servicing Guidebook*, and *Semiconductors From A to Z* for FREE 10-day inspection. SEND NO MONEY! If you are not delighted with these quality hardbound books, return them within 10 days and your Trial Membership will be cancelled without cost or obligation. Electronic Technician's Book Club, Blue Ridge Summit, Pa. 17214.

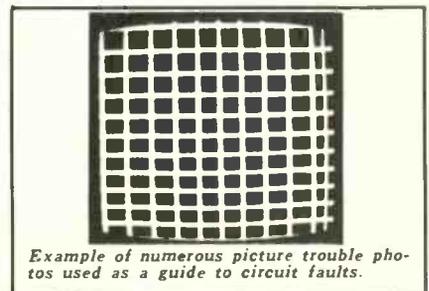

Example of numerous picture trouble photos used as a guide to circuit faults.

Typical Savings Offered Club Members on Recent Selections

RCA Color TV Service Manual	List Price \$7.95; Club Price \$4.95
Electronics Reference Data Book	List Price \$7.95; Club Price \$4.95
Digital Computer Analysis	List Price \$10.95; Club Price \$7.95
How To Test Almost Everything Electronic	List Price \$5.65; Club Price \$3.95
How to Use Your YOM, VTVM & Scope	List Price \$6.95; Club Price \$4.95
Modern Electronic Troubleshooting	List Price \$7.95; Club Price \$4.95
Installing Hi-Fi Systems	List Price \$7.95; Club Price \$4.95
Electronic Circuit Design Handbook	List Price \$14.95; Club Price \$7.95
Repairing Home Audio Systems	List Price \$7.95; Club Price \$6.50
FET Applications Handbook	List Price \$12.95; Club Price \$7.95
Handbook of Semiconductor Circuits	List Price \$7.95; Club Price \$4.95
Pinpoint TV Troubles in 10 Minutes	List Price \$6.95; Club Price \$4.95
Easy Way To Service Radios	List Price \$6.95; Club Price \$3.95
Practical Color TV Servicing Techniques	List Price \$7.95; Club Price \$4.95
On the Color TV Service Bench	List Price \$6.95; Club Price \$4.95
Transistor Circuit Guidebook	List Price \$6.95; Club Price \$4.95
Mathematics for Electronics	List Price \$10.95; Club Price \$7.95
Transistor Projects	List Price \$5.95; Club Price \$2.95
Radio Operating Questions & Answers	List Price \$9.25; Club Price \$7.95
Electronic Musical Instruments	List Price \$10.00; Club Price \$7.95

SEND NO MONEY! Simply fill in and mail postage-paid Airmail card today!

Oaktron takes the time to make it better!

Oaktron provides you with the top speaker value for your money. People expect a little more from Oaktron, and we're not going to disappoint them. Why settle for less, write today for your FREE catalog.

See you at the NEW Show, Las Vegas, Nevada

AKTRON

Oaktron Industries, Inc.
1000 Thirtieth St., Monroe, Wis. 53566



... for more details circle 130 on postcard

ET/D DEALER SHOWCASE

Continued from page 66
dynamic range low distortion compression. Frequency response is automatically controlled by voice level to prevent garbling and allow optimum



intelligibility. The standard model operates from 10.5 to 18vdc between -30 and +65°C, and has attack time of 1ms, released time of 0.25s and harmonic distortion of less than 5% over full compression range. Vega Electronics.

Portable TV

707

Announced is the Model 6912 B/W TV with a 75sq in. screen. The set offers a tuner which employs frame grid circuitry for VHF and solid-state circuitry for UHF. This tuner, plus the signal amplification provided by three



MODEL 6912 TV

IF stages is said to insure reception in fringe areas. The cabinet, two-tone green with a recessed aluminum handle, contains a 4in. speaker and built-in antennas. Other features include: keyed automatic gain control; ear-phone jack for private listening; 18 tubes, 4 diodes and 1 transistor. The picture tube operates from a 13 kv supply and is claimed to eliminate dust buildup. The unit measures 11½ in. high, 16½ in. wide and 11¾ in. deep. List price is \$99.95. Broadmoor.

LIMITED TIME OFFER! LADIES PHOTO BILLFOLD

YOUR GIFT FROM PERMA-POWER
WHEN YOU BUY EITHER OF THESE
BRITENER DEALS

BIGGEST SELLER IN TV HISTORY

Perma-Power Vu-Brite
Model C-401. (Parallel
wiring, duodecal base.)
Buy 12 at the
money-saving \$9⁹⁵
package price of



WORLD'S MOST USEFUL BRITENER

Perma-Power Tu-Brite
Model C-212. (Works
on any 110° button base
set.) Buy 5 at the
money-saving \$10⁹⁵
package price of



and the billfold is **FREE** and the billfold is **FREE**

Always rely on Perma-Power Briteners to extend useful picture tube life for months, preserve excellent customer relations for years!

Perma-Power

Division of Chamberlain Manufacturing Corporation
5740 North Tripp Avenue, Chicago, Illinois 60646

... for more details circle 131 on postcard



40 VUES wallet holds all your pictures, identification and credit cards, as well as coins and folding money. Available in a variety of fashion colors. You can give her several, because these Briteners are your fast movers!

Krylon® Crystal Clear is standard equipment for all installation and service work. It prevents many of the causes of picture


fading and high voltage losses and keeps lead-in connections tight. It's the repairman's handiest repairman.



Borden Chemical, Division of Borden Inc



radio-tv repairman

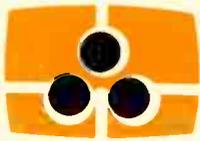

COLORFAX

ADMIRAL


Color TV Chassis K-10—Service Note

Before removing or installing an 8AC10 or 12AC10 col- or amplifier tube in the current 12, 14 and 16in. hybrid color television models, pull the ac cord! If you don't, transistor Q20 or Q21 is almost sure to be ruined. Make a habit of disconnecting power before making or breaking any connections on transistorized equipment. Surges, arcs and transients can instantly ruin transistors. Please note this information in your S1225 service manual.

Color TV Chassis K-10—Keyed AGC Circuit

The AGC system employs three transistors and one rectifier; two NPN transistors are used for the AGC gate and AGC amplifier, and a PNP for the RF delayed AGC. The chassis has a "keyed forward" type of AGC applied to the RF amplifier and first IF.

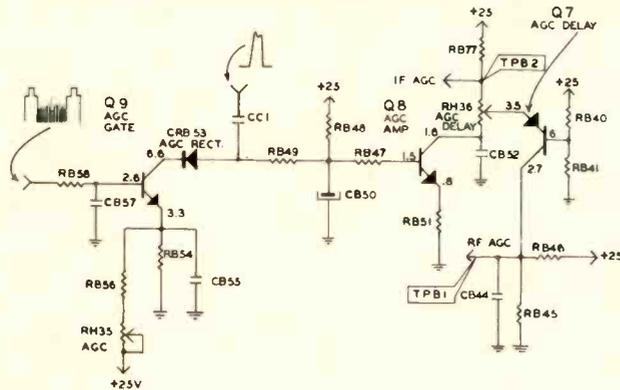A composite signal is taken from the emitter of the first video amplifier and fed to the base of transistor Q9 through



an RC isolating network. The base emitter junction is reverse biased but the sync pulses are of sufficient positive amplitude to drive the base positive and cause the transistor to conduct.

The sync pulses are directly proportional to the strength of the signal and using them as the source for AGC control will give control of the IF and RF sections proportional to the signal strength at the first video amplifier stage.

The emitter of AGC gate transistor, Q9, is attached to the 25v B+ by the 2K AGC control. Adjusting this control varies the positive voltage across the emitter resistor which in turn controls the conduction of Q9 during sync time and reverse biases it during scan time.

The collector receives a positive-going, horizontal pulse through rectifier CRB53. Transistor Q9 conducts in direct proportion to the signal blanking pulse on the base. Rectifier CRB53 conduction builds up on capacitor CC1 and charging capacitor CB50. A positive voltage is also present at CB50 through resistor RB48 from a 25v source. The balance is at a voltage lower than the positive 25v, depending on the signal strength. This voltage is applied to the base of Q8.

IF AGC: Assuming the signal level has increased, the following will occur. As the voltage is decreased on the base of Q8, it decreases the current flow through the collector which reduces the voltage drop across the load resistor RB77. This increases the AGC voltage applied to

the base of transistor Q1 causing an increased flow of current through it. This in turn does two things: (1) It increases the voltage drop across the extra high resistor RA17, thus lowering the voltage of the collector of Q1 and reducing the amplification. (2) It changes the impedance relationship of LA20 and LA2 to Q1 causing an impedance mismatch further reducing the stage gain.

RF AGC: The collector of the AGC delay transistor Q7 is connected to ground through RB45. With no current flow through Q7, a residual bias supplied through RB46 keeps the RF amplifier at maximum gain. The base of the AGC delay transistor Q7 is supplied by a voltage divider network, consisting of RB40 from the 25v positive voltage supply and RB41 to ground. This holds the base to about 6v positive.


The emitter of the AGC transistor Q7 is connected to the positive power supply through resistor RB77 and the control RH36. As the incoming signal strength increases, the dc amplifier Q8 will conduct less. The collector voltage will become more positive and this potential will be applied to the emitter of Q7. With very weak signals, the AGC delay control RH36 is adjusted so that the base emitter junction of Q7 is reverse biased. To make this stage conduct, increase the voltage drop between the base and the emitter until it reaches its conduction voltage (emitter 6.5v). It will be increasing the emitter voltage in a positive direction. This would be equivalent to moving the base voltage in a more negative direction. Notice that this is a PNP operating inverted. Once forward bias is established, it will induce collector current flow through RB45.

The over-all effect will be seen as an increasing positive voltage at its collector which is the RF AGC source. This positive voltage will forward bias the RF transistor Q51 and the over-all gain of the system will be reduced. For weak signals, the RF amplifier is biased to full efficiency through RB46.

GENERAL ELECTRIC

Color TV Chassis KE—Quick Removal of Cabinet Backs

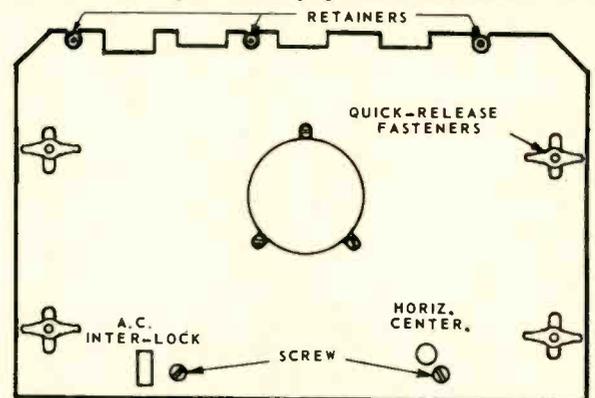In the near future it will be possible to quickly remove the masonite backs from KE line color television cabinets by removing only two screws instead of the usual nine. To accomplish this, the masonite cabinet backs have been redesigned to use four quick-release fasteners (two at each side) and three permanently positioned retainers at the



top rear of the cabinet. One screw is located adjacent to the ac interlock and the other screw is near the HORIZONTAL CENTERING control. To remove the back: (1) Remove the two screws. (2) Rotate the quick-release fasteners until they are vertical (parallel with opening). (3) Remove the masonite back by pulling out at the bottom to disconnect the ac interlock and then carefully pull down about 1/2 in. to release the top of the cabinet back from the three retainers. Now pull the back straight out and away from

the cabinet. Precaution: ALWAYS HOLD THE CABINET BACK FIRMLY DURING DISASSEMBLY TO PREVENT THE BACK FROM DROPPING AND HITTING THE PICTURE TUBE NECK. THIS PRECAUTION APPLIES TO THE DISASSEMBLY OF ANY CABINET BACK. To replace the back: (1) Push the back under the three retainers at the top of the cabinet. (2) Push in at the bottom and connect the ac interlock. (3) Rotate the four quick-release fasteners to a horizontal position (across the holes). (4) Replace the two screws.

**Color Chassis KE—Service Information
KE Chassis—Power Supply Diode Failures**

Whenever a CR109 or CR110 power supply diode failure occurs, you should add .001 μ f, 1kv (ET22X58) capacitors across diodes CR109 and CR110. A capacitor is packed with each replacement diode. This provides added protection against voltage surges which may damage the diode.

These capacitors were added to production sets starting with Ser. No. OS4E.

Preset Fine Tuning Adjustment Shifts

Investigation has shown that some complaints of this nature are caused by interference between the channel selector and fine tuning knobs because of the selector knob being pushed on too far.

At present, the production line is adding a thin washer between these knobs to prevent interference. In later production, the knobs will be revised to prevent the condition and eliminate the washer.


The simplest solution is to pull the selector knob out slightly so that it does not rub on the fine tuning knob. You may be able to eliminate some service calls by instructing the customer to do this.

In the event that you find cases where the problem re-occurs, contact your General Electric television distributor for washers to be placed between the knobs.

MAGNAVOX

Color TV Chassis T931/T933/T938—Defective 6LM8 Video/Sync Amplifier and 6JC6A 3rd Video IF Amplifier

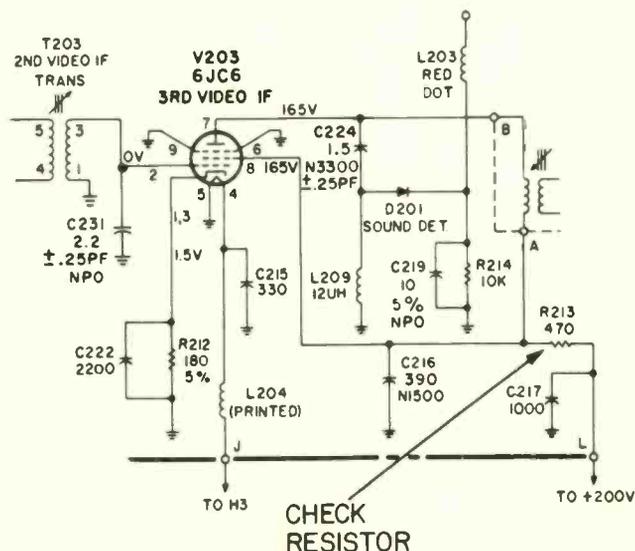Low contrast, deterioration of picture quality, low chroma output and poor sync are all possible symptoms of a defective 6LM8 tube. The symptoms may be more or less pronounced depending upon the condition of the tube. Check the 6LM8 tube as a possible cause when these symp-




ptoms are noted. Sometimes the failure of the 6JC6A 3rd video IF tube will result in failure of the plate/screen load

resistor, R213. Check the condition of this 470 Ω , 1/2w resistor when replacing a defective 6JC6A tube.

MOTOROLA


Color TV Chassis TS-915—No High Voltage

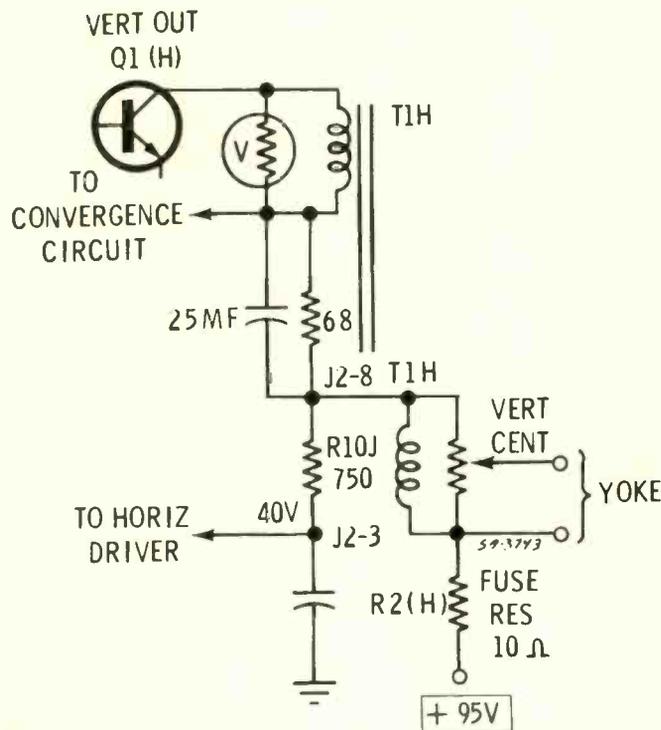Symptom: No raster and a check reveals there is no high



Continued on page 93

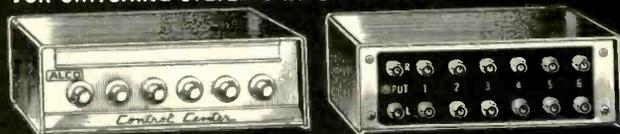NEW — AUDIO CONTROL CENTER
FOR SWITCHING SYSTEM'S INPUT OR OUTPUT



Control up to 4-6 complete stereo speaker systems, located in every room in your house. Or... use it to switch in or out various inputs such as tuners, tape recorders, phonos, etc. No impedance worries. Attractive black leatherette finish; employs easy-to-use push-push switches. Size: 5 1/2" x 2 1/2" x 3 1/4". See your dealer today.

AE DIVISION
4-CHANNEL RCA JACK 19.95
6-CHANNEL (Shown) 26.95
ALCO ELECTRONIC PRODUCTS, INC., NO. ANDOVER, MASS. 01845

10 Watt Power INTERCOM & Paging System

Designed to offer the latest in solid state and more operational features. Master and remote originate calls by making use of "tone" calling. Indicators continue to display calls until contact is completed. Simplified 2-wire installation. 8-transistor, 5-station master. 115 VAC.



MASTER \$69.95

AE DIVISION
ALCO ELECTRONIC PRODUCTS, INC., NO. ANDOVER, MASS. 01845

... for more details circle 144 on postcard

For additional information on products described in this section, circle the numbers on Reader Service Card. Requests will be handled promptly.

VHF Broad Band Amplifier 708


Announced are solid-state VHF broad band distribution amplifiers, Models M-104 and M-105, designed for color and monochrome installations. The systems are intended for small apartment houses and multiple installations of approximately 25-30



outlets such as TV dealer showrooms. The split band design of the amplifier presents greatly improved signal ability and a reported 24db gain in the low-band and 26db in the high-band. Electrical specifications are the same for both models except that the M-105 has separate low-band and high-band inputs at 75Ω. The M-104 features a low noise input circuit to offer the installer a choice of 300 or 75Ω input with separate level controls on each band for maximum flexibility. Noise figure on the low-band is 5.5db and on high-band is 6.5db. Finco.

Antennas 709

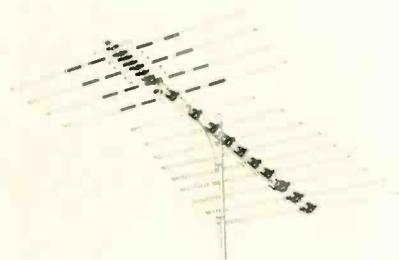Introduced is a new series of television antennas that provide improved





color and monochrome reception on all TV channels—VHF and UHF—as well as radio reception on the FM band. An optional extra UHF element

is available which is claimed to increase gain an average of 35 percent on difficult channels. The five antenna models in the series, available for direct 300Ω installation and convertible to 75Ω operation by means of snap-on transformers, are designed for use in areas classified from "local" to "deep fringe" in signal strength. The antennas are compact, lightweight and factory preassembled for easy mast mounting. List price is from \$21.95 to \$64.95. Jerrold.

MATV Attenuators 710

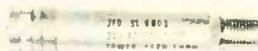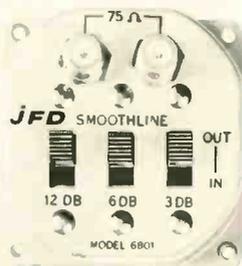A line of fixed and variable attenuators has been designed specifically for 82 channel cable powered MATV systems. The Model SL-6801 is vari-



able from 0 to 21db in 3db steps. The "F" type connectors are used for input and output with attenuation selected by heavy-duty slide switches. The Models SL-6803, SL-6806, SL-6812 and SL-6820 are fixed at attenuations of 3db, 6db, 12db and 20db, respectively. All attenuators in the new line pass UHF as well as VHF, providing uniform attenuation across the entire TV-FM spectrum. They also pass ac and dc power for cable powering applications. The Model SL-6801 variable lists for \$22.50 and the fixed attenuators list for \$5.95 each attenuator. JFD.

VOM Kit 711

A new VOM in kit form for technicians features 38 measuring ranges. The meter has 5000 ohms/volt ac-dc sensitivity with input protection on all voltage, current and db ranges. Precision 1 percent resistors are used

throughout. Operating controls include a ZERO/OHMS adjust, RANGE switch and FUNCTION switch to provide full scale readings on a 4½ in. two-color meter. The VOM has eight scales: ac-dc volts at 0-1, 5, 10, 50,



100, 500 and 5K; ac-dc current at 0-1, 10, 100ma, 1a; ohms at 0-5K, 50K, 500K and db readings from -20 to +76db in six ranges. The unit measures 6¾ in. x 5¼ in. x 2¾ in. and comes with a battery, test leads, carrying strap and operating manual. Price is \$19.95. Allied.

VTVM 712

Announced is the Model LV-76A Vacuum Tube Voltmeter, a multi-purpose instrument suitable for laboratories, service shops and schools.



Its construction makes it particularly adaptable for field use. The instrument has seven dc and seven ac ranges from 1.5v to 1500v. The re-

istance ranges cover from 10Ω mid-scale to $1G\Omega$ full scale. The input impedance is $1M$ and the frequency response is $20Hz$ to $4MHz$. Accuracy is ± 5 percent full scale. Only one test probe is used for all measurements which permits maximum operating ease. The dc polarity reversing switch makes it unnecessary to reverse the test leads when making transistor circuit tests. Price is \$54. Leader.

713 Blue Lateral and Purity Assembly


A single unit, blue lateral and purity assembly is introduced as a replacement for similar assemblies on any size American rectangular color picture tube. The 7604 assembly registers blue, red and green beams simultaneously within .06in. A single



wheel rotates two magnetic rings in opposite directions to provide blue beam lateral convergence. Purity correction is accomplished by individual adjustment of the two purity rings. The magnets are said to compensate for misregistration up to .005in. in any direction. Net price \$3.96. Miller.

Service Kit 714

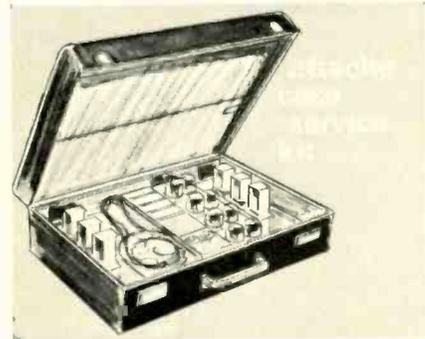Introduced is an attractive, lightweight, durable service kit in an attaché case. The kit is designed to assist you in servicing color television



receivers in the home. It consists of one complete set of PC boards with tubes (not including convergence board assembly) at a price less than you would pay for the "boards" alone. The boards provide a quick, effective

Continued on page 84

FAR SUPERIOR TO ANY VTVM OR VOM

-- and for less money only \$69.95



NEW FIELD EFFECT MULTIMETER

Here is the revolutionary new approach to circuit testing, the solid state Sencore FIELD EFFECT METER. This FE14 combines the advantages of a VTVM and the portability and versatility of a VOM into a single low-cost instrument. This is all made possible by the use of the new space age field effect transistor that is instant in action but operates like a vacuum tube in loading characteristics. Compare the features of the FIELD EFFECT METER to your VTVM or VOM.

Minimum circuit loading — 15 megohm input impedance on DC is better than a VTVM and up to 750 times better than a 20,000 ohm per volt VOM — 10 megohm input impedance on AC is 20 times better than a standard VTVM. The FIELD EFFECT METER is constant on all ranges, not like a VOM that changes loading with each range.

Seven AC peak-to-peak ranges with frequency response to 10MHz. Seven center scales down to 0.5 volt. Five ohmmeter ranges to 1000 megohms. DC current measurements to 1 ampere. Full meter and circuit protection. Mirrored scale. Low current drain on batteries — less than 2 milliamps. Built-in battery check. Unbreakable all-steel vinyl clad case. Optional Hi-Voltage probe adds 3KV, 10KV and 30KV ranges with minimum circuit loading for greatest accuracy in the industry... \$9.95.

FE16 HI-ACCURACY FIELD EFFECT METER.

All of above features, plus unmatched accuracy — 1.5% on DC, 3% on AC. High-style meter, knobs, and special meter-tilting handle. \$84.50.



SENCORE

NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT

426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101


... for more details circle 133 on postcard

NEW!
AVAILABLE ONLY FROM

South River

HEAVY-DUTY • TV/FM ANTENNA

7½ ft. TRI-MOUNT ROOF TOWER

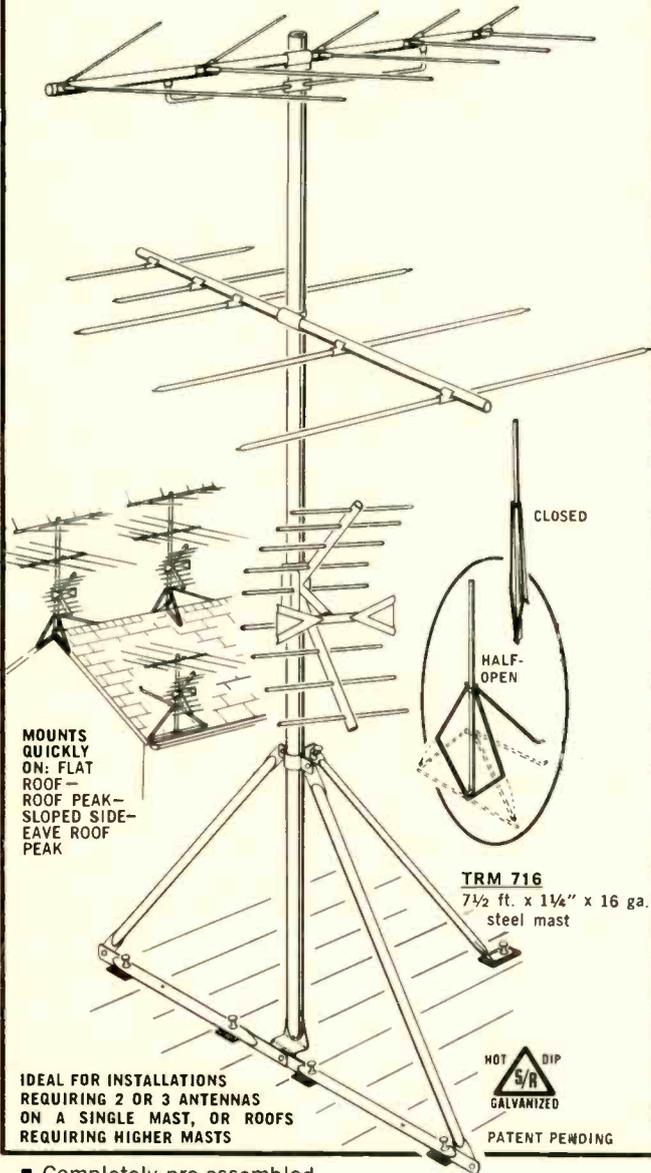

IDEAL FOR INSTALLATIONS
REQUIRING 2 OR 3 ANTENNAS
ON A SINGLE MAST, OR ROOFS
REQUIRING HIGHER MASTS

HOT
5/R
DIP
GALVANIZED

PATENT PENDING

- Completely pre-assembled; shipped folded; opens like an umbrella
- Self-supporting antenna mast roof mount
- Single-wing nut secures tri-mount in desired mounting position
- Complete with hardware including special mounting nails and roof-sealing pitch patches
- No guying required
- Made of heavy-gauge, hot-dip galvanized, rust-proof steel mast
- Also available in kits with wire, insulators, etc.

SEND FOR COMPLETE DATA SHEET

SOLD THROUGH DISTRIBUTORS

SOUTH RIVER METAL PRODUCTS CO., INC.

SOUTH RIVER, NEW JERSEY 08882 / (201) 254-5252

Visit Us at the Sahara Hotel, Las Vegas—Booths E 121-123—May 21-23

... for more details circle 136 on postcard



NEWS OF THE INDUSTRY

Chemtronics To Introduce New Contact Cleaner

Chemtronics Inc., a leading manufacturer of chemicals for the electronic industry, plans to celebrate its 12th year in business by introducing a new contact cleaner. The product is formulated specifically for gold and silver plated contacts. The cleaner employs a foaming action to clean and polish precious metal contacts, then leaves a permanent lubricant claimed to prolong contact life, reduce friction, and maintain low contact resistance. Based in Brooklyn, N.Y., Chemtronics' product line includes a variety of tuner cleaners and lubricants, contact cleaners, high voltage insulators, clear insulating sprays, tape recorder and record player cleaners, glass and plastic cleaners, penetrating and lubricating oils, solders, glues, rubber drive wheel, belt and cord restorers, and component coolers for locating thermal intermittents.

Clad Metal Parts Improve Color TV Sets

Clad metal parts that bend with temperature change are said to be helping RCA television sets provide optimum color performance from cold turn-on to full warm-up. The thermostat metal components, a key part of RCA's "Perma-Chrome" system, allow the picture tube to compensate continually and automatically for temperature changes associated with set warm-up. It is claimed that the viewer gets an optimum picture immediately and consistently instead of having to wait until the set is fully warmed up, which generally takes over an hour. A picture tube equipped with "Perma-Chrome" reportedly can be accurately adjusted for optimum color reproduction within minutes. This simplifies adjustments at the factory and eliminates the possible need for readjustment in the home.

Thermostat metal is one of the oldest clad metals—two or more metals bonded together for a combination of properties. It is the critical element in home and auto temperature-control systems in which its characteristic of changing shape with changing temperature is useful for opening and closing electrical switches.

Texas Instruments Inc., one of the producers of the RCA components, sees a trend toward employing this characteristic to compensate for troublesome temperature changes in various instruments and machines.

Objective of the system and its thermostat metal components is to keep energy particles—electrons—accurately aimed at the appropriate red, green and blue phosphor dots they excite to produce color images. The electrons emanate from one of three electron guns located in the neck of the picture tube and are orientated in such a manner to excite one of the three types of phosphor. Colors other than red, green and blue are produced by varying the number of electrons that strike each of the phosphor dots in a given trio. True color reproduction depends on each phosphor dot being struck only by electrons from the proper electron gun. This is accomplished by inserting a shadow mask between the electron guns and the face of the tube.

The shadow mask is a thin steel sheet with hundreds of thousands of tiny holes to permit the passage of electrons. When properly positioned, it will permit the passage only of those electrons aimed at the center of the correct phosphor dot. As the tube heats up during normal operation, however, the mask expands. The former resulted in

I'm glad you asked that question...

Who offers the most profit in tuner service? They tested us and learned:

Would you believe PRECISION TUNER SERVICE does?

If you're one of our thousands of long-time customers, you've already had it proven to you DAY AFTER DAY.

But, if you're not, you'll want to know how we got all those happy customers—(steady, satisfied customers, that is)

- PRECISION TUNER SERVICE is dependable . . . quality work . . . no complaints . . . just conscientious service!
- PRECISION TUNER SERVICE uses only ORIGINAL PARTS . . . no home-made or make-do inferior merchandise! (This is why we charge extra for major parts!) You get your tuner back in ORIGINAL EQUIPMENT condition.
- PRECISION TUNER SERVICE is fastest! Speedy 8-hour service . . . every time. No phone calls. No wondering.
- PRECISION TUNER SERVICE is more profitable! The cost is less . . . up to \$5.50 less than other tuner service! Major parts, tubes, transistors charged at net price. UV Combos—\$14.95

**AND NOW FOR EVEN FASTER SERVICE—
A BRANCH PLANT IN TEXAS AND CALIFORNIA, TOO!**

Why don't you test us and find out?
Don't make it easy on us . . .

***don't give us a break!
you get...***

Fast 8 hr. Service!
\$8⁹⁵

1 Yr. Guarantee

For finer, faster PRECISION TUNER SERVICE,
send faulty tuner with tubes, shields and all
broken parts to:



PRECISION TUNER SERVICE

one of the OLDEST and LARGEST tuner service companies in the country

WEST: 2325 WALDORF
TURLOCK, CALIF. 95380
TEL. 209, 632-2928

HOME OFFICE: 1210 S. WALNUT
BLOOMINGTON, IND. 47401
TEL. 812, 339-9653

SOUTH: 332 W. TYLER
LONGVIEW, TEX. 75601
TEL. 214, 753-4334

good color near the center of the tube and poor color—or “misregister”—around the edges where displaced holes in the shadow mask caused electrons to strike phosphor dots improperly.

RCA's solution to this problem in the system is a shadow mask mounted at four points on thermostat metal brackets supplied by Texas Instruments. Instead of restraining the shadow mask at its mounting points, the clad metal brackets themselves change shape and let the mask move evenly toward the face of the tube. This keeps the holes in the mask aligned with the phosphor dots and electron beams that must coincide.

Proper register and true color reproduction are achieved everywhere on the tube regardless of elapsed time from turn-on.

The Thermostat Metals Branch of Texas Instruments produces the mounting brackets from B-1 thermostat metal, a 50-50 combination of low-expansion “Invar”—36 percent nickel and 64 percent iron—and a high-expansion material consisting of 22 percent nickel, 3 percent chrome and 75 percent iron.

The clad metal brackets, which measure 1 x 2 x 0.040in., are spotwelded between the shadow mask frame and alloy steel cantilever springs at four symmetrical mounting points at the top, bottom and sides of the tube. The brackets are made with a longitudinal fold between two flat areas which are spot-welded to the mask frame and the cantilever springs. The brackets change shape with temperature along the folds. Cantilever springs attach to the tube by means of bosses in the glass. Clad metal brackets help provide an

economical solution to the expansion problem.

**Finco Mobile Display Unit
Begins National Tour**


The fully equipped FINCO Mobile Display and Research Laboratory from the Finney Co. of Bedford, Ohio, has begun a tour of the country which will eventually take it to all 50 states. The 30ft. self-contained unit brings demonstrations of FINCO MATV systems products and design techniques directly to FINCO distributors, staffs and technicians.

In addition to demonstrating the operation of system components, the mobile unit is equipped to research and solve individual problems which might arise in the actual installation of a MATV system.

In charge of the unit is Roger Priebe, FINCO MATV systems field representative. As the unit moves from territory to territory, Priebe will work with each regional manager in his respective area. Demonstrations will be attended by an estimated 7500 industry persons.

The Finney Co., a nationally recognized leader in the electronics industry, manufactures FINCO antennas for color and black-and-white television, FM, stereo and monaural reception and electronic components and accessories as well as master antenna systems (MATV).

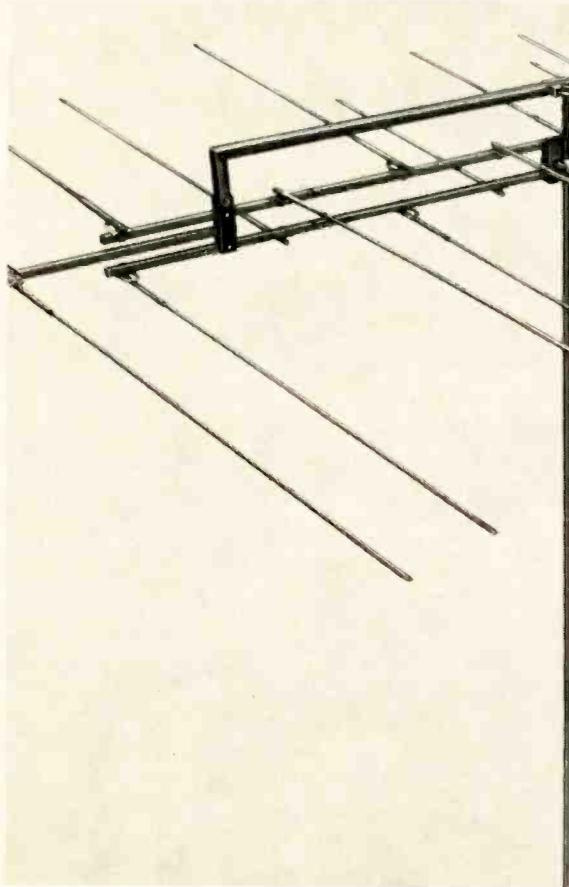**FOR MORE INFORMATION
ON ADS AND NEW PRODUCTS,
SEE READERS' SERVICE, PAGE 95.**



**Engineered for outstanding
reception-
Zenith outdoor antennas
for color TV!**

The best color TV deserves the best antenna. And you can confidently sell Zenith antennas for optimum reception in any signal area. Zenith quality features include:

- Capacitor coupled cap-electronic VHF dipoles.
- Tapered UHF grid driver.
- Staggered square UHF directors.
- Low impedance, triple boom construction.
- Gold-color alodized coating, for greater corrosion resistance and electrical conductivity.

For quality-engineered antennas and accessories, see your Zenith Distributor.

Why not sell the best **ZENITH**
The quality goes in before the name goes on

... for more details circle 143 on postcard

Laboratory or General Purpose

Triplett meets
the need
precisely

Whatever your testing needs, wherever you're working, there's a Triplett portable tester to meet the requirements — as perfectly as the skills of dedicated craftsmen can guarantee. For example, here are four winners from Triplett's great 630 Series:



**MODEL 630-A
LABORATORY V-O-M**

- 1 $\pm 1\frac{1}{2}\%$ DC, $\pm 3\%$ AC accuracy.
- 2 One selector switch minimizes chance of incorrect settings and burnouts.
- 3 Rugged $5\frac{1}{2}$ " suspension meter movement with $4\frac{1}{2}$ " mirrored scale.

\$7100



**MODEL 630-APL
LABORATORY V-O-M**

- 1 $\pm 1\frac{1}{2}\%$ DC, $\pm 3\%$ AC accuracy.
- 2 One selector switch minimizes chance of incorrect settings and burnouts. Polarity reversing for DC.
- 3 Suspension meter movement diodes protected against instantaneous overloads.

\$7100



**MULTI-PURPOSE V-O-M
MODEL 630-PL**

- 1 One selector switch minimizes chance of incorrect settings and burnouts. Polarity reversing for DC.
- 2 4.4 Ohms center scale, 0.1 ohm to 100 megohms resistance.
- 3 Meter movement diode protected against instantaneous overloads.

\$6100



**MULTI-PURPOSE V-O-M
MODEL 630**

- 1 One selector switch minimizes chance of incorrect settings and burnouts.
- 2 4.4 Ohm center scale, reads from 0.1 ohm up to 100 megohms resistance in 4 ranges.
- 3 20,000 ohms per volt DC sensitivity; 5,000 AC.

\$6100

See your Triplett representative or distributor for free demonstration.

TRIPLETT ELECTRICAL INSTRUMENT CO.



BLUFFTON, OHIO 45817

DON'T FORGET TO ASK 'EM "WHAT ELSE NEEDS FIXING?"

... for more details circle 139 on postcard

CONTRAST NOW . . .

Continued from page 55

"Only right polarized light passes through the polarizing filter. The horizontal wave component of this light is in phase with the vertical component. When passing through the quarter-wave retarding element a phase shift occurs--the horizontal wave component then lagging 90 deg behind the vertical--the light wave rotating clockwise. This light wave is still rotating clock-

wise after it has been reflected off the mirror and re-enters the retarding element. After again traveling through this element, the horizontal component lags an additional 90 deg behind the vertical component--it is then a total of 180 deg behind the vertical wave component--this being the phase angle of left polarized light. Left polarized light can't travel through this polarizing filter and so the reflected light is stopped."

"I get it now, Bob. Only right

polarized light passes through the polarized filter--right polarized light has horizontal and vertical wave components in phase with one another. After first traveling through the retarding element the horizontal component lags 90 deg behind the vertical component, and upon returning it lags an additional 90 deg or a total of 180 deg behind the vertical component--this relationship of components forms left polarized light, which is absorbed by the filter."

"Good for you, Scoot! By traveling twice through the retarding element, the right polarized light becomes left polarized light--the polarizing filter being positioned for removing left polarized light."

"What's this gray piece of plastic doing near the back of the book?"

"That's a sample of the circular polarizer we've been talking about."

"The linear polarizer is on one side, Scoot, and the quarter-wave retarding element is bonded on the other side of the filter--that's why it looks like only one piece of plastic."

Scoot removed the polarizer from the book and, with the bench light shining over his shoulder, held it in front of the screen of a TV set.

"Just as I told you, Bob, an hour's lesson and the 'gizmo' doesn't even work!"

"Turn it over, Scoot. You probably have the retarding element facing you instead of between the polarizer and the CRT. I can just see it now--you'll have all the circular polarizers on that CCTV job facing the wrong side out."

Scoot turned the filter over.

"Say, it does make the CRT look black!"

"Yes, Scoot, and when you get around to fixing that TV set, you'll see that since the light from the CRT isn't polarized, it can come out through the polarizer. The filter may polarize that light, but it won't remove it as it gets rid of the reflected light."

"And speaking of fixing TV sets--that reminds me, Scoot--you've missed another coffee break and had better get started fixing this set." ■



CHAN NEL LOCK

**For You Who Know Good Tools . . .
And Won't Buy Any Other Kind**

If you're one of those discriminating hand tool users who know and demand only the best, chances are you're already a Channellock customer. You know the beauty of full-polished, drop-forged steel, the smooth working precision-made working parts, the fine, hand honed cutting edges that distinguish hand

tools by Channellock. What you may not know is the wide choice of Channellock quality tools available to you. You can treat yourself to an arm-chair visit with the entire Channellock family in our color catalog. Let us send you a copy, no charge.

TOOLS BY
CHAN NEL LOCK
MEADVILLE, PA.

. . . for more details circle 111 on postcard

Continued from page 57

trol in this divider (HORIZ HOLD) determines the frequency of the horizontal sync pulses and vertical lines displayed on the CRT. The output of Q1 also drives clipper Q12 when the function switch is in the crosshatch or dot position.

The output from the divide-by-12 counter drives a divide-by-26 counter (Q5, Q6 and Q7). A control in this circuit (VERTICAL HOLD) determines the frequency (number) of the horizontal lines as well as controlling the vertical sync frequency.

The output from the 26:1 counter then drives a divide-by-10 counter which generates the actual vertical sync.


Transistor Q10 is a crystal-controlled 3.56MHz oscillator that generates a rainbow color signal which is passed to gate Q11. The gate circuit is driven to produce the color bars.

Transistor Q13 is a crystal-controlled oscillator operating on TV channel 3 (61.25MHz). The block diagram also shows the various interconnections made by the pattern selector switch to create the horizontal lines, vertical lines, crosshatch, dot and color-bar patterns.

Kit construction is simplified by employing printed circuit boards with "reference designation" letters representing the part stamped on the board. Next month's testlab report will cover the Darcy DM330 digital multimeter and the B & K Model 1077 Analyst. ■

Specifications: RF Output: 10,000- μ V into 300 Ω on TV channel 3. Horizontal Lines: 7 visible lines. Vertical Lines: 8 visible lines. Crosshatch: 7 horizontal by 8 vertical lines. Dots: 56 medium-sized dots (two scanning lines thick). Color Bars: 8 stable and distinct standard color bars. Master Pattern Oscillator: 187.2kHz, crystal-controlled. Chroma Oscillator: 3.65MHz, crystal-controlled. RF Oscillator: 61.25MHz (TV channel 3), crystal-controlled. Crystals: All crystals accurate to 0.005%. Size: 8 1/2in. wide, 3in. high, 8 1/2in. deep. Weight: 4 1/2 lb. Power Supply: Six "C" cells (1 1/2v).

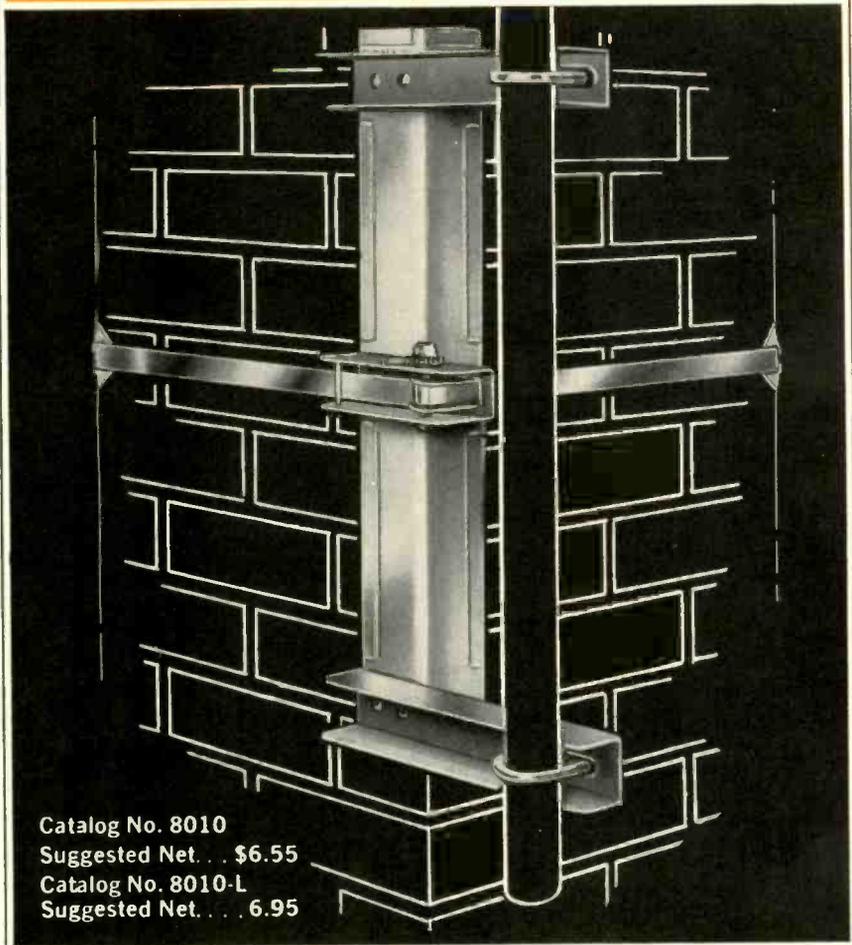CHIM-MOUNT HEAVY DUTY SINGLE STRAP RATCHET CHIMNEY MOUNT



Catalog No. 8010
Suggested Net. . . \$6.55
Catalog No. 8010-L
Suggested Net. . . 6.95

EASY, IMMEDIATE INSTALLATION

This rugged, all-weather unit defies the elements. Of one-piece durable construction with aluminum corner guards that makes application faster, easier, safer and neater. Vertically straight installation is sure.

Always insist on GC  . . .
you'll get more for your money, every time!

GC ELECTRONICS DIVISION OF HYDROMETALS, INC.
MAIN PLANT: ROCKFORD, ILL. U.S.A.

Giant New **FREE** Catalog! . . . Only GC gives you everything in electronics . . . has for almost 40 years. Write for your copy today!

GC

ELECTRONICS



has everything in
TV HARDWARE



. . . for more details circle 121 on postcard

Continued from page 77

method of troubleshooting. Boards are currently used in the color portables and will be incorporated into production of future models. Included in the cover is a convenient pouch to carry your service data, order blanks, schematics, etc. Setchell Carlson.

Knobs Antenna 715

Four different knob styles are introduced. Depending on the style, the

series is suitable for commercial product applications such as stereos, Hi Fi components and intercoms or on in-



strument and control panels. In standard form the knob is flat with a molded recess on top. A second style may be specified with a metallic ring

around the top. A third version has a spun aluminum inlay inserted in the recess. Another variation is provided with a spun aluminum cap covering the top of the knob. All knobs in the series have serrated sides. Each of the styles in the 900 series is available in six new sizes: 1/2, 3/4, 7/8, 1 1/8 and 1 1/4 in. Depending on the diameter, knobs vary in height from 5/8 to 13/16 in. All but the smallest sizes are furnished optionally in two brass insert shaft sizes: 1/4 and 1/8 in.; a single set screw is standard. Kurz-Kasch.

Transcription Turntable 716


Introduced is a transcription turntable, model TD-125. The unit incorporates an electronic transistorized drive system to reduce the motor rotation speed which the manufacturer claims results in reduced audible



rumble. Other features include an electronic speed selector and pitch control, three speeds—16, 33, 45 rpm—dynamically balanced 12in. diecast turntable and replaceable tonearm board for mounting your choice of tonearm. Elpa.

Noise Source Locator 717

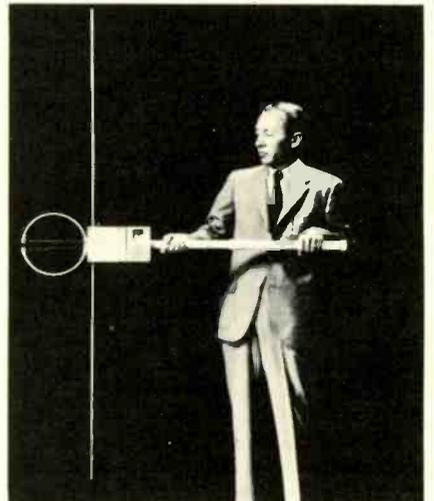Introduced is the model TNL2, a lightweight, self-powered noise source locator. With this instrument, it is reportedly possible to tell without trian-




gulation, the direction from which noise impulses are being propagated along any given power line. The unit pinpoints sources of interference to TV and communications reception. Price \$595. International.

introducing the "third generation" of the famous A/S MAGNUM family,

model M-227
MIGHTY MAGNUM III

CB BASE STATION ANTENNA

Suggested Resale: **\$36⁹⁵**

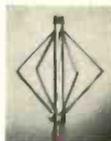

New "Stati-Lite Diamond"!

Drastically reduces noise, prevents static charge accumulation, helps to lower angle of radiation.

4 dB gain!

More true gain than ever before—increases effective radiated power to 13 watts!

New Power-Tip radials!

Power-loaded radials provide lower radiation angle, increased range, far more compact configuration!

Dual Phasing coil!

Optimizes impedance match, for excellent bandwidth characteristics, VSWR less than 1.4 to 1.

the antenna specialists co.

Division of Allen Electric & Equipment Co. 12435 Euclid Ave., Cleveland, Ohio 44106
Export Offices: 2200 Shames Dr., Westbury, N.Y. 11690
Also available in Canada.



Write for full color, illustrated technical brochure today!



Look for the "Stripes of Quality"!

... for more details circle 102 on postcard

THE PROFIT-MAKER!



- REBUILDS ANY SIZE ROUND OR RECTANGULAR COLOR PICTURE TUBES . . . AVERAGE COST PER TUBE \$7.80
- REBUILDS ANY SIZE BLACK AND WHITE PICTURE TUBE . . . AVERAGE COST PER TUBE \$1.80
- FREE INSTALLATION AND TRAINING ANYWHERE IN THE CONTINENTAL U.S.A.
- FREE SUPPLIES FOR REBUILDING YOUR FIRST 50 PICTURE TUBES
- EXTREMELY EASY TO OPERATE
- INCLUDES LAMINATING AND DELAMINATING EQUIPMENT FOR REBUILDING BLACK AND WHITE AND COLOR BONDED-FACE PICTURE TUBES.
- INCLUDES ALL TOOLS FOR REBUILDING ROUND AND RECTANGULAR COLOR PICTURE TUBES
- INCLUDES ALL TOOLS FOR REBUILDING BLACK AND WHITE PICTURE TUBES

RT COLOR CHAMPION

CRT COLOR CHAMPION . . . \$2,875.00

Mail Coupon Today for FREE CATALOG

C.R.T. Equipment Company, Inc.
2740 Old Lebanon Road
Nashville, Tennessee 37214

Telephone (615) 883-0215

(Please Print)

Name _____

Firm Name _____

Address _____

City _____

State _____ Zip _____

... for more details circle 116 on postcard

NEW ENDECO Desoldering Kits

MODEL
300-K
KIT
SHOWN



All you need to handle almost any desoldering and resoldering job!

Kit 300K includes the famous Endeco pencil desoldering iron Model 300, six different size tips (.038 to .090) for any job, tip cleaning tool, and metal stand for iron . . . all in a handy lifetime steel storage box. \$19.90 net. Model 300K-3 with a 3-wire cord \$20.90. Also a similar kit for military users. Kit 100K with large Endeco iron (Model 100A) is \$27.40, and 3-wire Kit 100AD-3 \$28.40.

SEE YOUR DISTRIBUTOR OR WRITE




**ENTERPRISE
DEVELOPMENT
CORPORATION**

513 E. 65th St., INDIANAPOLIS, IND. 46220

. . . for more details circle 118 on post

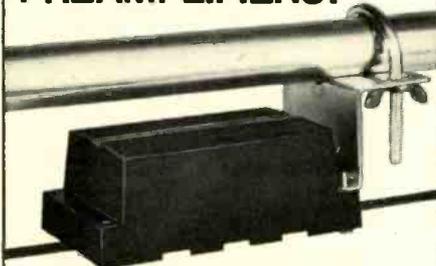WINEGARD BREAKS PRICE BARRIER ON FRINGE AREA TV PREAMPLIFIERS!



**SOLID
STATE
RD-300** **\$19.95** LIST

Perfect for weak signal areas where there are no local TV or FM stations. Gain of +15db amplifies VHF and FM, reduces snow, strengthens weak, faded pictures. Special lightning protected circuit. Mounts on any antenna except Super Colortrons. Includes power supply. A tremendous value!

© Copyright 1969



Winegard
ANTENNA SYSTEMS

WINEGARD COMPANY • 3019-3 KIRKWOOD STREET
BURLINGTON, IOWA 52601

. . . for more details circle 142 on postcard

ET/D

**CATALOGS &
BULLETINS**

Consumer Electronics Annual 400

A 36-page booklet devoted exclusively to consumer electronics is available. It can be used by employees to answer consumer inquiries. The 1969 edition will not be published until midyear. However, a limited quantity of 1968 booklets are still available at reduced prices as follows: 1-10 copies, 50 cents each; over 10 copies, 25 cents each. EIA.

Instruments 401

A 68-page catalog describes instruments for research and development, in industry as well as for educational purposes. Included are full specifications, illustrations and many schematics for: Malmstadt-Enke spectroscopy system, instrumentation laboratory chart recorders, recording pH electrometers, polarography system, Berkeley Physics Laboratory, and Heath oscilloscopes, power supplies, voltmeters, signal generators, testers, bridges, etc. This catalog also introduces a major new development, the Heath/Malmstadt-Enke Modular Digital System. Among other new products is a Log/Linear Current Recording System. It reportedly can resolve currents as low as 1 picoampere, such as those used in spectrophotometry or gas chromatography.

A Heath/Solartron Oscilloscope System is also shown for the first time, featuring true double beam, DC-15MHz bandwidth and 100 μ V/cm sensitivity. Heath Co.

Soldering Iron Tips 402

A 28-page, two-color soldering iron tip catalog is available. Featuring drawings of tips in diameters from 1/8 to 1 1/2 in., the new file folder style catalog is designed to enable tip users to specify diameter, length, point shape, shank style and point tinning requirements when ordering. A complete selection of diamond, cone, chisel, screwdriver, bevel, turned down and tapered tips is illustrated, as well as plug, sleeve and threaded shank styles. Leading brands and models of soldering irons for these tips are also listed. The soldering iron tips are iron plated to resist corrosion and pitting. They also feature the patented shank

ATR

**PRODUCTS
FOR
MODERN
LIVING**



**ATR UNIVERSAL
INVERTERS**

A.C. Household Electricity Anywhere . . . In your car, boat or plane!
To Operate • Tape Recorders • TV Sets • Dictating Machines • Radios • Public Address Systems • Electric Shavers • Record Players • Food Mixers • and Emergency Lighting. NET
12U-RHG (12 V.) 175-200 W. Sh. Wt. 27 lbs. 79.66
28U-RHG (28 V.) 150-175 W. Sh. Wt. 27 lbs. 96.66



**ATR "A" Battery
ELIMINATOR**

For Demonstrating and Testing Auto Radios—TRANSISTOR or VIBRATOR OPERATED!
Designed for testing D.C. Electrical Apparatus on Regular A.C. Lines.

MAY ALSO BE USED AS A BATTERY CHARGER
MODEL 610C-ELIF . . . 6 volts at 10 amps. or 12 volts at 6 amps. Shipping weight 22 lbs.

USER NET PRICE **\$59.82**

**ATR AUTO RADIO and
COMMUNICATION**

**LONGER-LIFE
VIBRATORS**

"The Best by Test!"




ATR ELECTRONICS, INC.

Quality Products Since 1931

ATR St. Paul, Minnesota 55101—U.S.A.

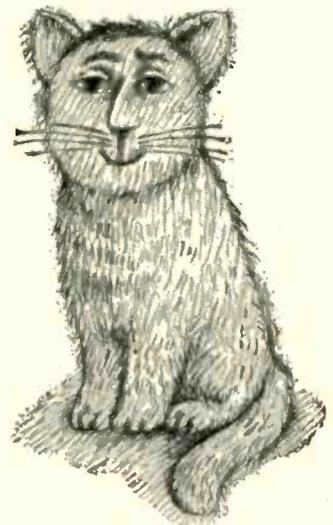. . . for more details circle 105 on postcard



**What's one life to
a guy who thinks
he has nine.**

You only have one life to live. Don't treat it lightly. Annual checkups are the first line of defense against cancer. It's nice to find out you're as healthy as you feel. Help yourself with a checkup. And others with a check.

American Cancer Society

plating which eliminates heat induced scaling and corrosion, and are warranted not to stick or seize in the soldering iron barrel. Cuprox tips, available in the same sizes and configurations, are nickel plated over a core of high quality copper. Plato.

Correspondence School 403

Offered is a 384-page manual explaining the function, operation and objectives of ICS. It also lists and explains the 266 study courses with a synopsis of the more than 1500 instruction texts used in these courses. This manual is an informative reference for use in building programs of study. It is also used by ICS sales representatives in designing training programs for industry. ICS.

Antennas 404

A four-page brochure introduces a line of antennas designed for maximum sensitivity on Monitor Radio. The line includes three groups of fixed and mobile antennas. There are three mobiles and one base (MR-3) antenna in the high band (130-174MHz)



group. The mobile antennas differ in mounting method—MR-1 is a roof mount, MR-2 is a trunk lip mount and MR-9 is a magnetic mount antenna. In the low band (25-50MHz) there are 2 antennas—MR-4, a fixed antenna, and MR-5, a mobile antenna that includes a heavy-duty, stainless steel whip and the chrome-plated "low ball" mount. Three antennas cover both ranges: MR-6, a cowl mount that replaces AM auto antennas; a receiver mounted model (MR-7) and a dual range fixed antenna MR-8. All antennas are factory pretuned across all bands specified. Hy-Gain.

USE ZIP CODE

We invite you to compare our solid state BC-382 with any other 82-channel booster-coupler—at any price!



There must be a reason why Winegard's 4-set BC-382 outsells everything else around. And there is. Simply enough, the BC-382 works to perfection, yet costs you less! It's the perfect solution for connecting 3 or 4 TV sets or outlets to a single antenna. Ideal, of course, for small home systems. Compare features and price with any other VHF-UHF-FM booster-coupler. See why so many dealers prefer the Winegard BC-382.

- **Solid State Circuitry**—for extremely high uniform gain and outstanding reliability throughout the life of the installation.
- **Overlay Silicon Transistors**—temperature tested from -60° to $+200^{\circ}\text{C}$ for positive temperature stability.
- **Flat Response**—over the full operational bandwidth for perfect color reception.
- **High Input Levels**—prevent overload and insure the most efficient use of signals.
- **High Isolation Between Outputs**—prevents interaction between tv sets.
- **Unique Lightning Protection Circuit**—fast switching diode across base-emitter junction of input transistor effectively shunts to ground lightning surges which would damage most amplifiers.
- **Switchable FM Trap**—Winegard (and only Winegard) incorporates an FM trap in each booster-coupler. Allows you to drastically reduce FM signals, preventing overload and cross modulation. Where excessive FM is not a problem, trap can be switched out, restoring full FM amplification.
- **3-Wire Ground**—standard 3-wire ground cord connects circuit board and chassis ground to electrical ground of home wiring, to provide lightning protection and better stability.
- **Rugged Steel Housing**—same high quality construction that has helped make Winegard commercial equipment famous. No plastic!
- **Self-Contained**—comes complete with mounting bracket, screws and connectors. Nothing else needed. Easy to install.

BC-382 (300 ohm) \$39.95 list
BC-782 (75 ohm) \$44.95 list

Three VHF-FM models also available. Write for Fact-Finder #276.

 **Winegard**
ANTENNA SYSTEMS

WINEGARD COMPANY • 3009-2 KIRKWOOD ST. • BURLINGTON, IOWA 52601

© Copyright 1969

... for more details circle 141 on postcard

NEW Heathkit® Solid-State Color Bar — Dot Generator

Continued from page 31



Kit IG-28
Only \$79.95*

Advanced Integrated Circuitry Delivers 12 Patterns Plus Clear Raster ... No Divider Chain Adjustment ... No Flicker, Bounce or Jitter


- All solid-state construction using Integrated Circuitry
- No divider chain adjustments
- Stable pattern display — no flicker, bounce or jitter
- Produces 12 patterns plus clear raster
- Instant switch selection of all functions
- Exclusive 3x3 display plus standard 9x9 display of all patterns
- Horizontal lines only one raster thick for added accuracy
- Variable front panel tuning for channels 2 through 6
- Variable front panel positive and negative video output
- Front panel negative going sync output
- Two handy AC outlets on front panel
- Built-in gun shorting circuit with lead piercing connectors
- Front panel switchable crystal controlled sound carrier
- Copper-banded transformer to reduce stray fields
- Safe three-wire line cord
- Fast, easy construction with two circuit boards and two wiring harnesses

Advanced Design. The new Heathkit IG-28 is one of the most stable, versatile Color and B&W TV service instruments available. In addition to the exclusive Heath "3 x 3" display of patterns illustrated, it also produces the familiar 9 x 9 displays ... plus a clear raster for adjusting purity without upsetting the AGC. Fifteen J-K Flip-Flops count down from a crystal controlled oscillator to eliminate divider chain instability and adjustment.


Time-Saving Versatility ... gives you front panel tuning for channels 2 thru 6 ... front panel variable plus and minus video output ... front panel sync output ... two convenient AC outlets ... built-in gun shorting circuits and grid jacks ... vectorscope capability ... crystal controlled sound carrier ... banded transformer to eliminate stray fields ... zener-regulated power supply ... safe three-wire line cord ... fast circuit board-wiring harness assembly. For the versatility you couldn't get before ... put the new IG-28 on your bench now.

Kit IG-28, 8 lbs. \$79.95*

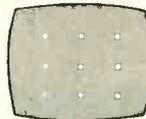Standard 9x9 Displays plus Exclusive Heath "3 x 3" Display



3x3 Dot

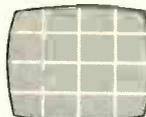


3x3 Cross Hatch




3x3 Shading



3x3 Color Bars

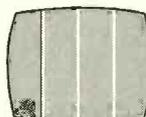

3x3 Vertical

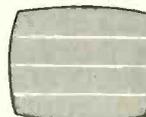


3x3 Horizontal

the blocking oscillator transformer, the clock drive circuit uses two air core coils wound together and positioned in proximity to the balance wheel in the clock.

The transistorized drive circuit provides pulses of magnetic energy that alternately attract and repel the magnets mounted in the balance wheel assembly, causing it to oscillate. The reciprocating motion of the balance wheel can be compared to its counterpart in an ordinary clock or wrist watch.

When battery voltage (1.5v) is applied to the clock drive circuit, transistor Q1 is slightly forward biased by resistor R1 (150K) causing a small collector current. This collector current creates a magnetic field about coil L1. The polarity of the magnetic field produced by L1 is such that it attracts the magnet in the balance wheel, causing it to rotate in a direction that brings the magnet closer to the

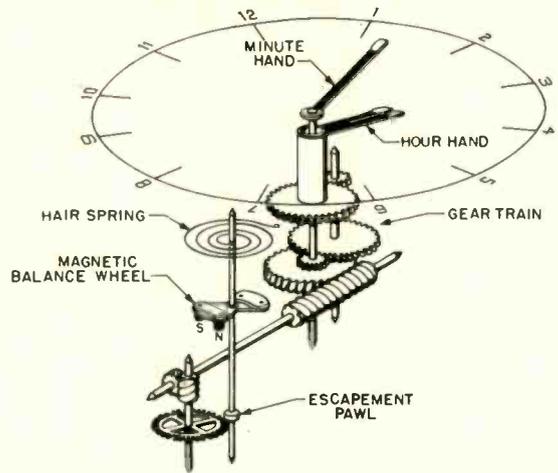

coil assembly. The moving magnet induces a pulse of voltage in coil L2 which is part of a feedback network connected to the base of transistor Q1. The positive feedback pulse developed by coil L2 tends to increase forward bias on transistor Q1, causing magnetic energy and further deflection of the balance wheel.

As the balance wheel pivots toward the L1-L2 coil assembly, mechanical energy is stored in the hair spring and the balance wheel, letting it rotate past the magnetic coil assembly. Further rotation of the balance wheel causes the south pole of the magnet to cross the L1-L2 coil assembly. The polarity of the magnetic field produced by the balance wheel magnets reverses, and the polarity of the voltage induced in coil L2 also reverses, creating a voltage pulse of opposite polarity on the base of transistor Q1. The reverse bias afforded by the feedback pulse cuts off transistor Q1 and the mechanical energy stored in the balance wheel assembly drives the wheel back to its original position—allowing the cycle to be repeated at a rate of approximately 5 pulses per second. The exact period of balance wheel oscillation is determined by the mechanical resonance of the hair-spring/balance wheel assembly—not by the electrical components—just as in a conventional clock.

The mechanical energy produced by the oscillation of the balance wheel is transmitted by a small pawl located on the end of the balance wheel assembly. The back and forth motion of the pawl moves the first gear (in the gear train) one tooth at a time—as the balance wheel moves back and forth. The illustration details the mechanical coupling between the balance wheel and the hands of the clock.

HEATH COMPANY, Dept. 24-5
Benton Harbor, Michigan 49022

Please send my FREE 1969 Heathkit Catalog.

Enclosed is \$ _____ plus shipping.

Please send model (s) _____

Name _____

Address _____

City _____ State _____ Zip _____

Prices & specifications subject to change without notice.
*Mail order prices; F.O.B. factory.

TE-200

... for more details circle 123 on postcard

Audio Connectors 405

A new catalog describes a line of audio connectors, standard microphone connectors, adapters, RF connectors, Y connectors, AC receptacles and phone jacks. The catalog includes specifications, detailed drawings, application hints and prices for single and multiple conductor models. It provides engineers and designers with an up-to-the-minute guide to the latest in audio connectors and related components. Switchcraft.

Automotive Speakers 406

A new automotive loudspeaker replacement guide is available. Covering model years 1960 through 1969 inclusive, the guide lists replacement loudspeakers for all American and foreign automobiles and reportedly is the most up-to-date reference and replacement guide now available to electronic distributors and service technicians. Printed in an easy-to-use 8½ x 11in. format with "universal" punching, the new guide is available without charge. Jensen.

Tools 407

A 24-page catalog of hard-to-find tools describes each tool and its application. The catalog contains a collection of useful tools rarely sold by industrial distributors or stores, such as electronic pliers, jewelers' tools, sensitive drillers, precision tools, flexible shaft machines, unusual solders, soldering jigs, hard-wire cutters, screw and nut starters, glass drills, miniature files, riffers and reamers. Also shown are soldering machines, endless hacksaws, divider setters, diamond glass cutters and rust remover devices. Brookstone.

Microphones 408

An eight-page microphone and accessory brochure is offered. The brochure includes the complete line of professional and entertainer series of microphones, stands, bases, mixers and accessories. Geloso.

MATV Systems 409

An MATV planning manual, a basic text of systems design and planning, is offered. Written for technicians who want to educate themselves in the MATV business, the booklet describes MATV systems products, as

well as the fundamentals of system design and design calculations. Also included in the manual are sample VHF and all-channel systems, a db to voltage multiplier chart, coax cable and transmission line guide, TV channel assignments and a glossary of the most used MATV terms. Finney.

Instruments 410

A 12-page catalog describes the company's complete line of advanced electronic test equipment. The new catalog, Form No. 458, features five new test instruments, including a sweep and marker generator, combination oscilloscope/vectorscope, color

generator and two transistor/FET testers. Other instruments included are field effect meters, tube testers, CRT testers, field strength meters and special purpose instruments, all with performance data and prices. Sencore.

**411
Switches and Panel Components**

An eight-page catalog features a line of miniature switches and front panel components. The catalog lists an expanded line of miniature switches, keyboard switches, push-button modules, machined aluminum knobs, ceramic terminal strips, readout indicators, pilot light assemblies and miniature lamps. Product descriptions,

ANNOUNCING SPACE AGE**FOAMING ACTION
TUN-O-FOAM****CLEANS, POLISHES,
& LUBRICATES CONTACTS
EACH TIME CHANNEL
IS CHANGED****SPACE AGE
LUBRICANT
DOESN'T DRY OUT
FOAMS AWAY
DIRT AND CORROSION**

TUN-O-FOAM is a new generation of tuner sprays. It is not simply a cleaner with a little residue of lubricant. It is a space age lubricant that cleans as it lubricates. Ordinary lubricants are hydrocarbon compounds which dry out rapidly. TUN-O-FOAM is a space age lubricant in which the carbon has been replaced by a rugged, synthetic element. The result is a long-lasting lubricant capable of withstanding extremes of temperature and maintaining lubricity over thousands of channel changes. Thus, no matter how hot the chassis runs, TUN-O-FOAM will not cake up or dry out. Especially well suited to silver and gold plated contacts, it is the same type of lubricant used in today's spacecraft — the finest ingredients ever put into a can. Each time the tuner is rotated, the contacts are cleaned, polished and lubricated. Yet TUN-O-FOAM is non-abrasive. It will not wear away contacts, and it cannot cause detuning.

**TRY TUN-O-FOAM. IT'S GUARANTEED TO BE THE BEST TUNER
LUBRICANT/CLEANER YOU'VE EVER USED OR YOUR MONEY REFUNDED.****CHEMTRONICS**

1260 RALPH AVENUE

BROOKLYN, N.Y. 11236

FOR EXPORT: ROBURN AGENCIES INC., NEW YORK, N.Y. 10013

IN CANADA: PERFECT MANUFACTURING LTD., MONTREAL 9, CANADA

... for more details circle 112 on postcard

Signal Strength Meters . . .

Continued from page 43

you can add and subtract numbers in db when computing a system, and the numbers stay small. Otherwise, you would have to divide or multiply at each step, and your computations would involve large, complex numbers.

CALCULATING GAIN IN MATV SYSTEMS

Since the data for calculating voltage amplification, voltage gain and power amplification is readily available, all you have to do is plug the values into the formulas.

The formulas to determine true amplification or gain of RF amplifiers and preamps with 300 or 75Ω input and output impedances are:

- (1) Voltage Amplification $(A_v) = E_{out}/E_{in}$
- (2) Voltage Gain or Power in db = dbmv out - dbmv in
- (3) Power Amplification $(A_v) = \text{Antilog} (.1 [\text{dbmv out} - \text{dbmv in}])$.

Remember that stage gain measurements made with very small input signals may yield results different from those you might get with a larger input signal. This is because of amplifier efficiency characteristics.

To determine voltage amplification (A_v) in a typical MATV installation using the above formulas, we will assume that your measured input signal (E_{in}) was 1000 μV and the output signal (E_{out}) was 2000 μV . According to the formula, $A_v = 2000 \mu V / 1000 \mu V = 2$.

Voltage gain and power gain are easily computed from a reading in db. Going back a little, we indicated that a 2 times amplification was equal to 6db. From formula (1) we found that the voltage amplification was 2, or 6db. Therefore, formula (2) tells us that voltage or power gain is dbmv out - dbmv in. Plugging in our values, 6db (dbmv out) - 0db (dbmv in) = 6db.

To determine power amplification we will again assume that the input signal was 0db and the output signal was 6db. From the formula Power Amplification $(A_v) = \text{Antilog} (.1 [6\text{dbmv} - 0\text{dbmv}]) = \text{Antilog} (.1 [6]) = 4$. In this formula, .1 times 6 = .6. To find the Antilog of .6 you will have to consult a table of common logarithms. The table indicates that the Antilog of .6 is approximately 3.98 which is rounded off to 4.

If the input impedance (Z_{in}) of the device you are measuring is approximately equal to the output impedance (Z_{out}), but not equal to 75 or 300Ω, amplification measurements

(either power or voltage) will be reasonably accurate, although the actual dbmv or μV meter indications will be in error. When Z_{out} is not equal to Z_{in} , the presence of a signal can be detected, but determination of gain would require a knowledge of the circuit and the signal strength meter.

A porcelain isolation/coupling capacitor may be used between the probe tip and the test point to reduce the effects of circuit loading by the SSM. A typical low-capacity probe is shown in Fig. 7. A low-capacity probe is

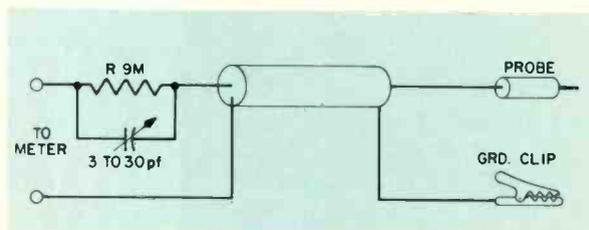


Fig. 7--Schematic diagram of low capacity probe which can be used to reduce circuit loading.

generally designed with a 10 to 1 attenuation factor, so if the meter has an input impedance of 1MΩ, a 9MΩ resistor will provide the 10 to 1 ratio.

The trimmer capacitor is used to compensate for frequency response. As a rule of thumb, the trimmer is selected so that its reactance at the test frequency is equal to ten times the lower of the two impedances (Z_{out} and Z_{in}) of the equipment under test. Actual dbmv and μV readings will be off. But with this technique it is generally possible to make relative gain checks without fear of circuit detuning, overloading or upsetting AGC bias.

SIGNAL TRACING TV FRONT ENDS

Signal tracing essentially has the same objective as the stage gain measurements previously described. The main difference is that signal tracing does not normally require specific gain computation but concerns itself with the presence or absence of a signal and its relative gain or loss in a passive device. Fig. 8 shows a block diagram of a typical TV RF section. The troubleshooting procedure should provide you with some helpful techniques that can be used in the shop or the customer's home.

First, tune the SSM and TV receiver to a given channel. Then check the signal level at the tuner input (antenna terminals). For an accurate reading, connect the downlead directly to the SSM. The minimum acceptable reading should be close to 1000 μV or

illustrations and prices are included. Alco.

Semiconductors 412

A 64-page transistor and diode catalog lists a complete line of semiconductor discrete devices. The catalog presents key parameters and package outline dimensions along with a numerical index that quickly locates the device of interest. The listings are grouped by applications for the reader's convenience. They include diodes, small signal transistors, dual transistors, Field Effect Transistors, power transistors, communication devices, silicon-controlled rectifiers, specialty diode products and electro-optical devices. Fairchild.

Microphones 413

A 20-page catalog describes a line of microphones, including several recently developed models. Included in the catalog are professional cardioid dynamic, mobile and transistorized mobile, base station, paging, public address and tape recording microphones, plus microphone cartridges, stands and accessories. The publication includes technical sections and product descriptions, specifications, photographs and list prices on each microphone. Turner.

Tape Recorder 414

A new 16-page illustrated catalog describes the portable cassette and reel-to-reel models, cassette, 8-track and reel-to-reel tape decks, Radiocorders and stereo tape systems. Applications, features and specifications of the complete line are included in the tape recorder catalog. Concord.

Last year, 7,000 people died because they found excuses for not wearing seat belts.

This year, our ads could take away those excuses and save quite a few lives.

Unless the ads don't find their way into your magazine.

Then, what's your excuse?



Imagine a doctor without a stethoscope



Imagine an engineer without a slide rule



Imagine a professional service technician without a Sencore Mighty Mite V.



STANDARD OF A PROFESSION!

The Mighty Mite has become the standard of the industry with over 50,000 used daily by competent professional servicemen from coast to coast. The Mighty Mite checks them all; tubes large and small . . . and it checks them critically too. 100 megohm grid leakage sensitivity, individual tube element shorts test and cathode emission test at full rated current make the Mighty Mite really tough. It's tough on tube tests, tough in appearance with vinyl case and cover, and mighty tough on competition. But, it's not tough on your pocketbook at only

See your Sencore distributor today. He has the TC142 Mighty Mite in stock. **\$84.50**



SENCORE
NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT
426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

. . . for more details circle 134 on postcard

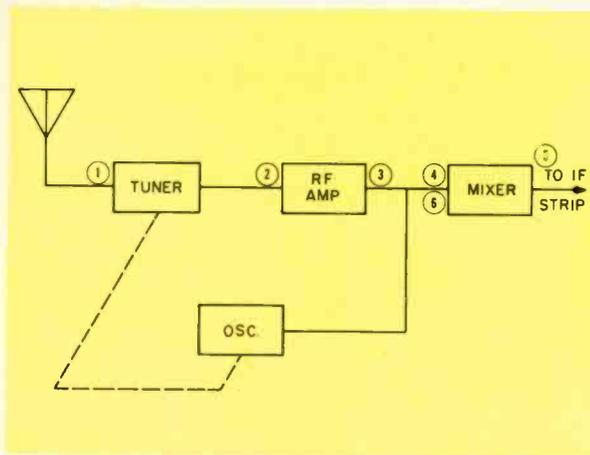


Fig. 8--Block diagram of typical TV RF section.

Odbmv. If this is satisfactory, reconnect the antenna to the antenna terminals and again check the input signal level. This time use the test probe assembly (impedance mismatch may result in a lower reading).

Note the reading across the antenna terminals, then move the probe to the grid (or base) of the RF amplifier. A standard tube test-adaptor socket will provide access to the tube pins if necessary. The probe readings at the antenna terminals and the RF grid are normally within 25 percent of each other. The reading at the grid will be lower because of circuit detuning by the tube adaptor.

Lack of signal at the RF grid would indicate a problem in the antenna balun (RF transformer), coupling capacitors or the appropriate section of the tuning switch assembly.

Next, check the collector or plate (if cascade stage, check output plate) signal. This reading should show a higher reading than that measured at the grid. A relatively strong signal indicates satisfactory interstage coupling (via the tuner). The signal should also be detected at the mixer plate (although a non-linear device, the mixer's component input frequencies will be present at the output).

The mixer grid can then be checked for presence of the oscillator injection signal. This may be done by tuning the SSM approximately 41MHz up from the channel center frequency. For example, channel six covers from 82 to 88MHz. Channel center is 85MHz. Tuning the SSM to about 126MHz should bring in the oscillator signal. If alignment of the tuner is necessary a standard sweep-marker generator and scope should be used. Future articles on the signal strength meter will cover its use in making receiver sensitivity, frequency response, noise figure, signal-to-noise and antenna tests. ■

Color System . . .

Continued from page 51

oscope will tell you if it is the IC or other circuit components which are defective. Also, if the "chip" is defective, incorrect voltage readings at the terminals should reveal if replacement is necessary.

Although the chroma output of the second color amplifier (at the collector) is approximately 6v P-P, the step-down for impedance matching of L34 (2nd color amplifier transformer) to the "chip" input results in approximately 0.75v P-P input to terminals two and three. A power supply input of 24v is applied across terminals one and six. Amplification through the "chip" is greater than 10 times, providing adequate signal amplitude to the color difference amplifier grids. The operation of the "chip" (similar to the switch-type tube operation) is such that the 2nd harmonic (7.2MHz) of the 3.58MHz must be trapped in the output circuit. (The 3.58MHz fundamental is automatically canceled within the "chip.") This is provided by the coils L39, L45 and L51 in the output circuit which provides a high impedance to this frequency (7.2MHz). In addition, these coils also aid in providing the necessary response of the color-difference signals.

The transmission line which couples the color oscillator reference signals to the "chip" is similar to other color chassis.

However, the phase of the signals at various take-off points is slightly different and component values also differ. It should be noted that the values of components are rather critical and although failure of any one is unlikely, the exact replacement should be made when necessary. When servicing these "chip" circuits, do not substitute or use components that are only "close" in value.

The hue control is connected to the transmission line so that only the injection signals to the "chip" are affected. The AFC and ACC reference signal are unaffected.

A small capacitor (.39pf) is connected from one of the chroma inputs of the demodulator to the AFC phase detector. This capacitor provides a feedback of the burst signal from the AFC phase detector which eliminates any tendency toward 3.58MHz radiation.

The TV technician must become more proficient in troubleshooting these IC's as we will be seeing many more "chips" in electronic products in the near future. ■

SERVICING THE SOLID STATE CHASSIS by *Homer L. Davidson*. Published by **TAB Books, Inc.**, 256 pages, 200 illustrations. \$7.95 hard-bound, \$4.95 paperbound.

This book discusses a number of solid state equipments including TV, pocket radios, ac-dc, AM-FM, auto and multi-band receivers. It also covers auto tape players, phonographs, tape recorders and stereo amplifiers. These subjects fill all but two of the 12 chapters. A preliminary chapter on general transistor testing and the ending chapter on troubleshooting tips round it out. The chapters are all complete in their particular analysis of circuit problems and they are backed up with appropriate schematics, diagrams and waveforms. In most cases the writer attempts to provide a general view of the circuit then plugs in circuit defects with typical causes and cures. The troubleshooting procedures are for the most part sound, but in a few instances they include some very general and broad statements. However, the service technician who finds his labors divided among a variety of solid state equipments will appreciate much of the knowledge and technique this book provides.

Colorfax . . .

Continued from page 75
 voltage. Possible Cause: Open vertical fuse resistor, R2(H). The fuse is located on convergence panel door. Procedure: Use voltmeter to check for 95v at both terminals of the resistor. Do not jumper fuse terminals. If resistor is open, check for a short at the load end. Suspect a shorted vertical transistor. See illustration for details on how this open resistor causes loss of high voltage. Analysis: The fuse resistor protects the vertical output transformer and associated parts should the transistor short. A 40v supply (was 26-28v in previous models) is secured from this circuit through R10J at terminal J2-3. This 40v supplies the horizontal driver stage. Thus, if the fuse opens, there will be no raster because of no high voltage. The fuse not only protects the vertical output transformer, but it avoids a horizontal line if the vertical transistor shorts and blows the fuse.

USE ZIP CODE

NOW - CHECK ALL TRANSISTORS IN OR OUT OF CIRCUIT . . .

Flick function switch to left to check all regular transistors.

Flick function switch to right to check any FET.



all regular transistors plus the new field effect transistors.

You won't be stopped when you run into the new FETs that are wired into the latest hi-fi, newest TV receivers and nearly every other new device coming on the market. For the very first time, you can check them all, in or out of circuit. The TF151 works every time using tried and proven signal injection techniques. New, improved tests on special RF transistors and the latest high power transistors, mean that the TF151 is the only up-to-date transistor tester on the market. A new, exclusive setup book in rear compartment guides you to every test for over 12,000 transistors and FETs. The book is not needed for general service troubleshooting. Regular transistors are checked for beta gain and I_{co} leakage. FETs are checked for transconductance and I_{gss} leakage. **only \$129⁵⁰**

Your distributor just got this new tester in stock. See him, it obsoletes all others.



SENCORE

NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT
 426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

. . . for more details circle 135 on postcard

MAKE YOUR OWN TUNER TEST!


If you're like most professional TV technicians, you clean the tuner of every chassis you service.

But how careful are you in choosing your tuner spray? The wrong spray can cost you a lot in aggravation and callbacks.

That's why we ask you to

MAKE THIS TEST YOURSELF

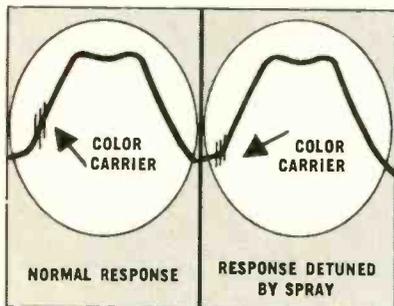1. Tune in a good color picture on any color set.
2. Spray the tuner with anything but a Chemtronics Spray.
3. You will see the color fade and disappear almost immediately, due to the changes of capacitance in tuned circuits caused by the spray.



4. Wait about 10 minutes for the spray to dry. Unfortunately, the color will not come back.
5. Spray the tuner with Chemtronics TUN-O-WASH.
6. Wait about two minutes and color will be restored.

WHAT THIS TEST MEANS TO YOU

Most tuner sprays leave a residue of slow drying, petroleum base lubricant. This saturates the coils and other components causing a shift in response as shown in illustration.

To compensate for this shift, you often adjust oscillator slugs. Then, when the set has played in your customer's house for a week or two, the residue dries out, shifting the oscillator back toward its original frequency. If the customer can't compensate for this drift with the fine tuner, you have a callback on your hands. Even if the drift is not too severe, the remaining residue picks up dirt and eventually "gunks up" the tuner.

TUN-O-WASH IS LIKE NO OTHER SPRAY ON THE MARKET

TUN-O-WASH is a powerful, high pressure spray designed to do just one job superlatively well. It melts away grease, oil, dirt and corrosion quickly and completely. It leaves absolutely no residue behind. Tests show that TUN-O-WASH is at least 10 times as effective as any other tuner spray in degreasing gunked up tuners.

Use TUN-O-WASH as your first step in repairing any tuner. It gives you a clean start in much the same way as the ultrasonic bath used by tuner specialists — but without harmful vibration. You'll be surprised at how many tuners you can repair the TUN-O-WASH way.

Then, once the tuner is restored to good working condition, you can lubricate it with a light spray of Chemtronics famous COLOR-LUBE, guaranteed not to detune, attack plastic parts or "gunk up." COLOR LUBE uses a unique synthetic lubricating formula developed specifically for color TV tuners.



Giant 24 oz. can only \$3.25 dealer net.



1260 RALPH AVENUE • BROOKLYN, N.Y. 11236

... for more details circle 113 on postcard

ET/D AD INDEX

Accurate Instruments	65
Alco Electronics Products, Inc.	75
Antenna Specialists	84
Argos Products	66
Arrow Fastener Co.	24
A.T.R. Electronics Inc.	86
B & K Division	2nd Cover, 32, 33, 34
Belden Corporation	28, 29
Borden Chemical Inc.	73
Channelock, Inc.	82
Chemtronics, Inc.	89-94
Cleveland Institute	35, 36, 37
Cornell-Dubilier	3rd Cover
C. R. T. Equipment	85
Delco Radio Div.	63
Enterprise Development	86
Finney Company	26, 94
G. C. Electronics	83
G. E. Tubes	27
Heath Company	88
Interjectorall Electronics	26
International Crystal	22
JFD Electronics	23
Lampkin Labs	94
Lectrotech	31
Mallory Distributor	20
Multicore Sales	94
Oaktron	72
Perma-Power	72
Precision Tuner	79
RCA General Purpose	4th Cover
RCA Picture Tubes Division	67
Sencore	77, 91, 93
South River Metal	78
Sprague	25
Sylvania	38
Triplett Electrical	81
Tuner Service Corp.	19
Winegard	86, 87
Zenith Sales Corp.	80

"HOW TO MAKE MONEY in Mobile Radio Maintenance"

AUTHORITATIVE GUIDEBOOK ABOUT THE BOOM IN TWO-WAY MOBILE-RADIO. GIVES FACTS FIGURES, PAY RATES. WRITE TODAY! FREE

LAMPKIN LABORATORIES, INC.
Div. 11 - BRADENTON, FLA 33505


Color TV WINDOW ANTENNA

by **FINCO**

Outperforms any indoor antenna!

FCW-VU VHF-UHF
List: **\$14.95**

FCW-V VHF ONLY
List: **\$11.95**

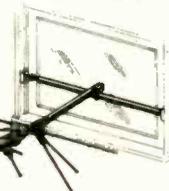

- Unique swivel design zeros-in directly on stations.
- Aluminum construction with gold-corodized, corrosion-proof finish on antenna.
- Fits horizontally or vertically in windows up to 42" wide or high.
- Extension bars available for larger windows.

Write or Catalogue 20-462 Dept. 110-5



THE FINNEY COMPANY

34 West Interstate St., Bedford, Ohio 44146

... for more details circle 120 on postcard

WORLD'S FINEST 5-CORE SOLDER

ERSIN MULTICORE

NEW EASY DISPENSER PAK

ONLY 69¢



BUY IT AT RADIO-TV PARTS STORES

MULTICORE SALES CORP., WESTBURY, N.Y. 11591

... for more details circle 129 on postcard

ELECTRONIC TECHNICIAN/DEALER

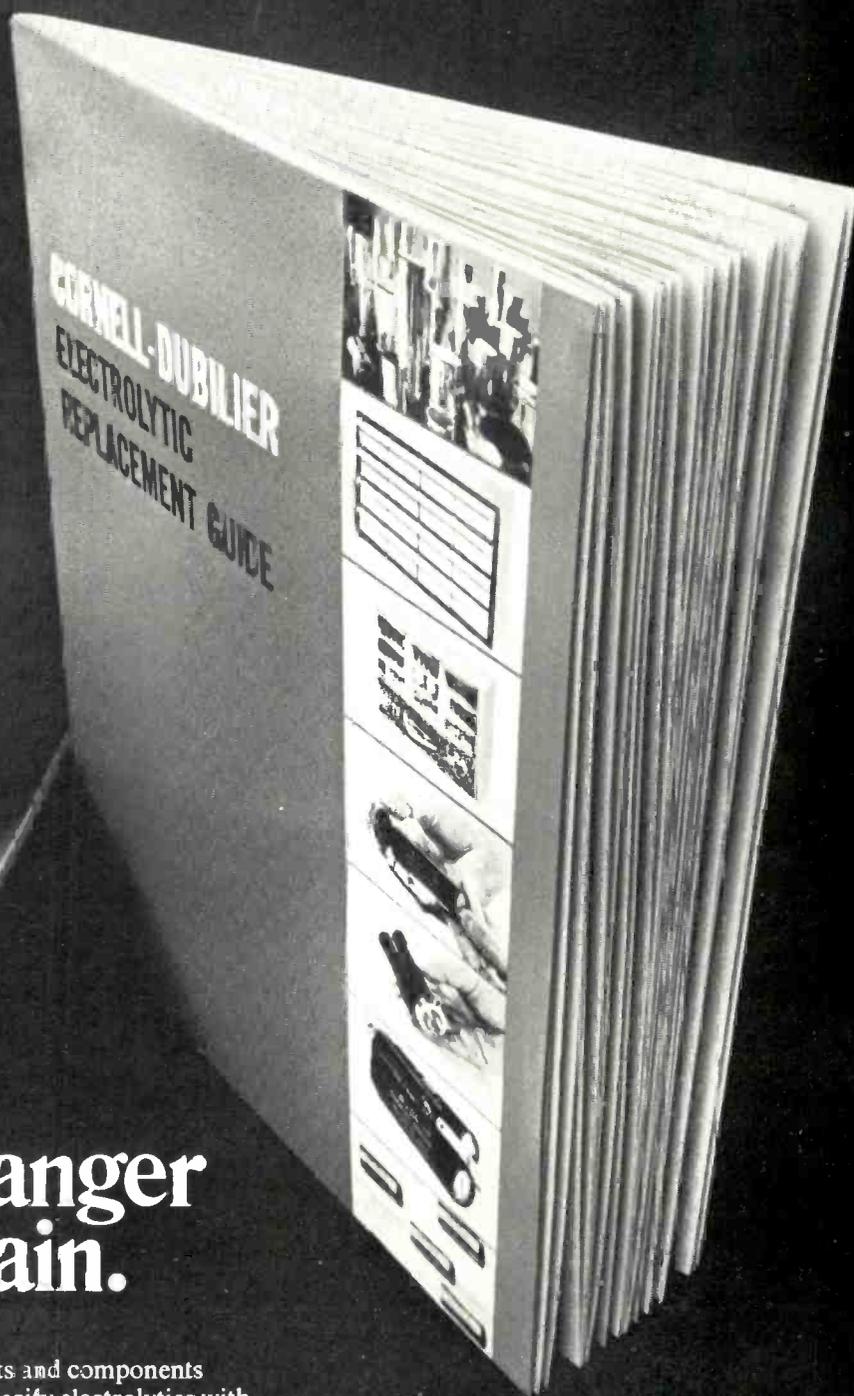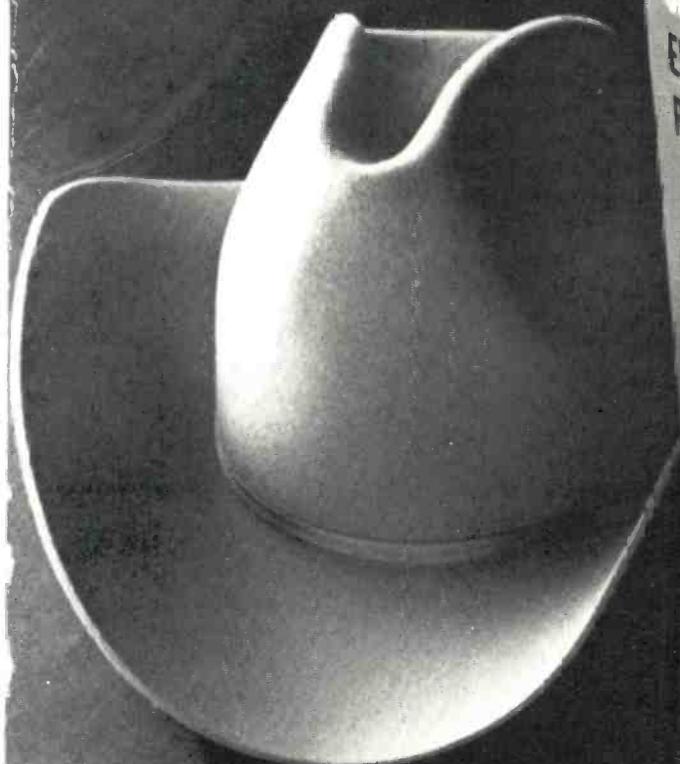... for more details circle 115 on postcard



The Wide Ranger Rides Again.

And you sure need the Ranger back.

You see the guys who design the circuits and components want to keep costs at a minimum. So they specify electrolytics with the minimum capacity and voltage to do the job.

And that's the trouble. That's why there are thousands of different sizes and ratings for twist prong capacitors.

Then there's the label problem. The manufacturers meet the broad standard tolerances laid down by E. I. A. But it's not possible to build these capacitors to very close tolerances. So most capacitors are made to exceed the capacity shown on the label.

For example, a capacitor marked 100 mfd. at 300 volts could in fact measure from 90 mfd. to 200 mfd. and still be within tolerance.

So we decided to make things a little simpler. We examined over 20,000 capacitors and put together a new line of 248 Wide Range Twist Prongs that can replace 97% of all electrolytics you're ever going to come across.

And they're all listed in the new Cornell-Dubilier Electrolytic Replacement Guide. Plus a complete listing of the line by voltage and capacities; a complete reference to major competitors' products; 100% reference to all color TV chassis original manufacturers' part numbers and a cross reference to major black and white TV chassis. Write today for your free copy.

CDE **CORNELL-DUBILIER**




Give her this...

Use RCA's attractive new, red and black, die-cut "What Else Needs Fixing?" business calling cards to increase *your* business! When you give Mrs. Housewife a card as you arrive at her home, you trigger her thinking... remind her of some other electronic device or appliance that may need fixing. The Electronic Industries Association estimates that you'll have a 50% chance of getting an additional job on the spot, measurably increas-

ing your profit-per-call. In effect, it gives you a second no-cost call. They'll work equally well on in-store customers, too. The cards are available only through Authorized RCA Tube Distributors as our way of supporting this important industry program. For the name of your nearest Distributor offering these business-building calling cards write Dept. 451, RCA Electronic Components, Harrison, N. J. 07029.

so she'll read this!

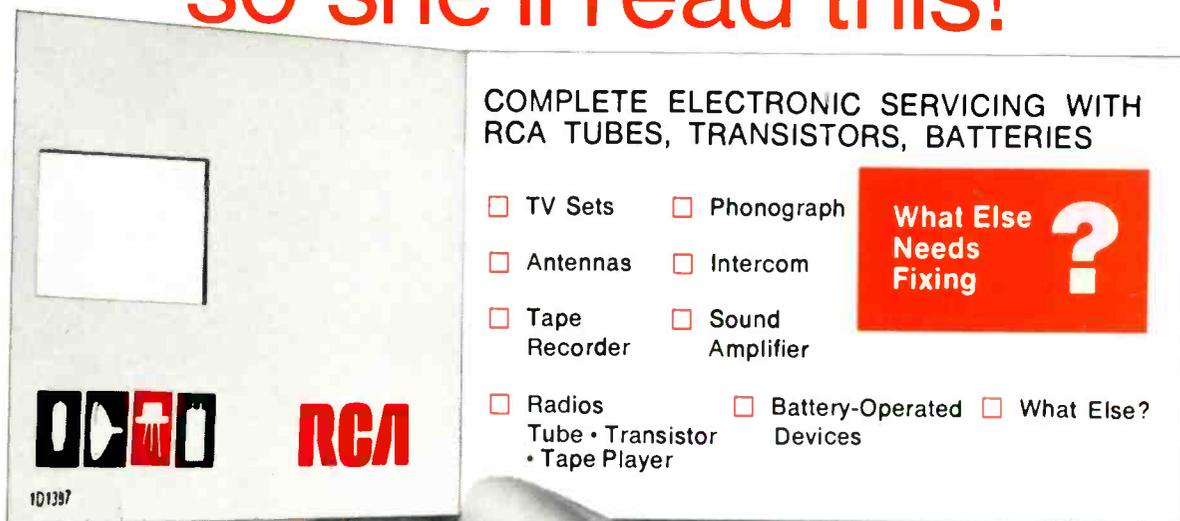

RCA